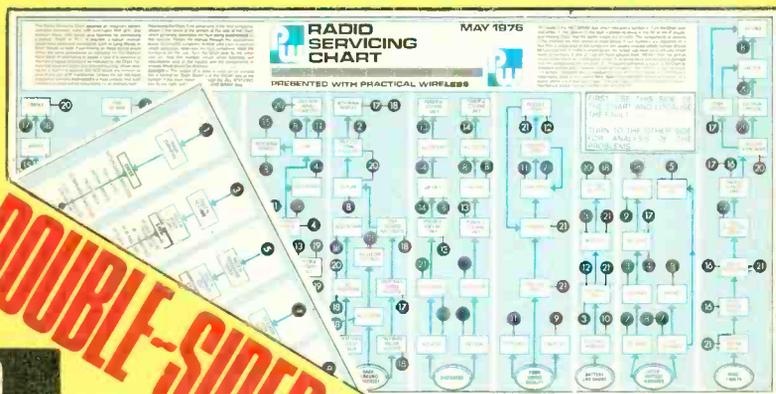


# PRACTICAL WIRELESS

MAY 1976

35p

## FREE INSIDE!



**DOUBLE-SIDED**

**RADIO SERVICING CHART**

**TANGO  
SWING  
MARCH  
SAMBA  
MAMBA  
CHA CHA  
WALTZ  
ROCK  
FOXTROT  
SHUFFLE**  
with our

**RHYTHM GENERATOR**



ALSO:  
a 3-band RF  
mini-amplifier

PART 1



# TRAMPUS ELECTRONICS LTD

58-60 GROVE RD.,  
WINDSOR, BERKS.  
SL4 1HS.  
TEL. 54525.

ADD 8% VAT TO PRICES MARKED \*  
AND 25% VAT TO ALL OTHER PRICES  
OR AS CURRENT VAT LEGISLATION.  
SEND C.W.O. (EXCEPT GOV'T DEPT)  
POST & PACKING 20P FOR THE UK.  
BARCLAYCARD & ACCESS BY POST.  
OR £5 MIN ON TELEPHONE ORDERS.  
CATALOGUE LIST FREE SEND SAE.  
MONEY BACK IF NOT SATISFIED.

## YOU WON'T BELIEVE OUR PRICES


### FAST FAST SERVICE

NORMALLY 24 HOURS  
ON EX STOCK ITEMS.

### QUALITY PRODUCT

FULL SPEC. DEVICES,  
NO REMARKS, REJECTS,  
OR FLOORSWEEPINGS.

ADD VAT  
TO PRICES

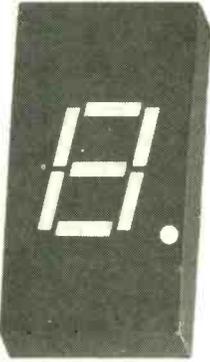

#### OPTO ELECTRONICS

ALL FULL SPECIFICATION LED  
DL707 LITRONIX COM ANODE &  
DL704 LITRONIX COM CATHODE  
0.3" 0-9 & DEC POINT 89pea \*  
DL747 JUMBO DISPLAY 0.6"  
LED 0-9 DP.COM ANODE £1.75 \*  
3015F FILAMENT DISPLAY £1.25 \*  
DISCO ETC STROBE TUBE £5.00ea \*

#### RED LEOS IIp

209 STYLE OR 0.2" NO CLIP 11p\*  
TIL209 OR 0.2" RED & CLIP 13p\*  
GREEN LED LARGE OR SMALL 22p\*  
ORANGE LARGE OR SMALL 22p\*  
ORP12 57p \* 2N5777 33p\*  
TEC12 IC PHOTO DETECTOR 81p\*

#### IC'S LOW PRICES

703 RF/IF	26p	MC1303	£1.47
709 7099	22p*	MC1310	£2.09
709 DIL 14	28p*	MC1312 SQ	£1.50
710 DIL 14	31p*	MC1318	£2.50
723 Regul'r	45p*	MC1330	75p
741 DIL 8	20p*	MC1339	£1.49
741 DIL 14	31p*	MC1350/1/2	75p
741 7099	31p*	MC1466 /9	£3
747 2x741	67p*	MFC4000 i/w	59p
748 DIL 8	27p*	NE536 .PETOPA	£2*
7805 5V	£1.39	NE540	£1.10*
7812 12V	£1.39	NE555 2vr	£1 *
7815 15V	£1.39	NE555 TIMER	41p*
7900 Series	£3 *	NE556 2x"	84p*
76013 6W AF	75p	NE560 PLL	£4.00
CA3046	59p	NE561 PLL	£4.00
CA3048	£2.20	NE562 PLL	£4.00
CA3054	£2	NE563	£2.25
ICL8038	£2.69*	NE565	£2.50
LM300	£1.50*	NE566	£1.55
LM301 OPA	41p*	NE567	£2.20
LM304 0-40V	£3*	SN72741	741 20p*
LM308 H1 Bo	95p*	SN76660 IF	75p
LM309K 5V	£1.75*	SN76611 IF	£1
LM372 IF	£2.00	TAD100 & IF	£2.2
LM377 2x2W	£3	T8A800	89p
LM380 60745	89p	T8A810 7WAF	80p
LM381	£2	T8A820	£1.49
LM3900 40PA	63p*	ZN414 RX	99p

#### TRANSISTORS

PRICE EACH-	MATCHING	20p*
AC127 & 128	10p*	INS.BUSH SET 6p*
AC176	15p*	TIP29 & 30 43p*
AC187 & 188	18p*	TIP31 & 32 54p*
AD149	45p*	TIP41 63p*
AD161 & 162	33p*	TIP42 67p*
BC107	8p*	TIP2955 99p*
BC107B	12p*	TIP3055 67p*
BC108	7p*	T1543 UJCT 26p*
BC108B	12p*	ZTK107/8/9 11p
BC109	8p*	ZTK300 & 304 20p
BC109C	12p*	ZTX500 & 504 42p
BC147/8/9	9p	2N706 & 708 11p*
BC157/8/9	12p	2N2646 UJT 38p*
BC167/8/9	12p	2N2904 & 5 20p*
BC177/8/9	18p	2N2926brovgy 9p
BC182/3/4A&L10p	2N3053 16p*	
BC212/3/4A&L12p	2N3054 42p*	
BCY70/1/2	16p*	2N3055 115W 37p*
BD131 & 132	39p*	2N3055 RCA 60p*
BFR88 250V	35p	2N3702/3/4/5 8p
BFY50	14p*	2N3706/7/8/9 8p
BFY51	14p*	2N3710 & 11 8p
BFY52 & 53	14p*	2N3819E FET 12p
BSX190/20/21	16p*	2N3820 FET 40p
MJ2955 TO3	75p*	2N3823E FET 16p
NJE2955	89p*	2N3904/5/6 15p
MJE3055	64p*	2N4289 mini 31p
MPU131 PUT	49p	2N5457 FET 45p

**2N3055 37p**  
**BC109 8p**  
**BFY51 14p**  
**FET3819 14p**  
**741 8pin 20p**  
**NE555 42p**  
**7400N 9p**

#### CMOS LOGIC



#### 7400 series TTL IC's

##### NEW MOTOROLA

CD4000	15p*	CD4028	73p*
CD4001	16p*	CD4046	£1 *
CD4002	16p*	CD4047	73p*
CD4009	45p*	CD4049	45p*
CD4011	17p*	CD4054	94p*
CD4013	45p*	CD4059	£1 *
CD4016	45p*	CD4060	90p*
CD4017	82p*	CD4071	17p*
CD4018	82p*	CD4081	17p*
CD4022	77p*	CD4510	£1.19*
CD4023	16p*	CD4511	£1.90*
CD4024	63p*	CD4528	£1.10*
CD4027	45p*	CD4558	£2.35*

7400N	9p*	7450/3/4	12p*	7491	60p*	74155	65p*
7401	10p*	7460	12p*	7492	13p*	74157	90p*
7402/3	11p*	7470	26p*	7493	38p*	74160/1	95p*
7404	13p*	7472	22p*	7495	58p*	74162/3	95p*
7405/6/7	25p*	7473/	26p*	7496	68p*	74164	£1.20
7408/9/10	9p*	7474	25p*	74100	£1 *	74165	£1.20
7411/12	20p*	7475	44p*	74107	30p*	74175	95p*
7413	26p*	7476	28p*	74120	£1 *	74180	£1 *
7417	27p*	7480	40p*	74121	26p*	74181	£2 *
7420/27	26p*	7481	95p*	74122	42p*	74185	£3 *
7430/32	16p*	7482	72p*	74123	58p*	74190	£1.40*
7440	12p*	7483	80p*	74141	64p*	74193	£1.10*
7441	64p*	7485	£1.20*	74143	£2 *	74195	75p*
7442	59p*	7486	33p*	74147	£2 *	74196	£1 *
7445	75p*	7489	£2.70*	74151	65p*	74197	£1 *
7447	67p*	7490	37p*	74154	£1.30*	74198/9	£2 *



#### AUDIBLE WARNING BLEEPER

12VOLT 35mA. SPARKLESS £1\*

TGS GAS DETECTORS £2 ea\*

LOGIC PROBE FOR TTL etc £5\*

#### TRANSISTOR TESTER

TTC TESTS ALPHA, BETA Ico

NPN/PNP & DIODES NOW £13\*

C1000 MULTIMETER £3.49\*

BENCH POWER SUPPLY P1076

3-12V 1A ONLY £3.99 \*

ALL ANTEX SOLDERING IRONS

#### CAPACITORS

CERAMIC 22pf to 0.1 uf 50V 5p.

ELECTROLYTIC IN 10, 25 & 50V.

2UF/10V, 10, 50, & 100uf 25V

& 10V 7p ea. 50VOLT 10p ea.

1000 uf 25V 18p. 200/500uf 9p.

#### POTENTIOMETERS

LIN OR LOG 2, 2K to 1 MEG. 16p

PRESETS 6p. RESISTORS 1p. ea 1W

HEATSINKS TO5/18 7p. \*TO3 15p\*

TV4 PLASTIC POWER 16p\*

TO3 EXTRUDED 4" FINNED 39p\*

DIN PLUGS ALL 12p. SOCKETS 9p.

ALL CASES AB5/AB7 50p\* AB13 69p\*

AB13 69p\* AB9 59p\* AB12 40p\*

TRANSFORMERS 100mA 6, 9 or 12V 89p\*

1/2A/1A 6/12 or 12/24 £2 ea \*

#### cassettes

LOW NOISE NOT REJECTS.

C60 33p ea TEN FOR £2.70

C90 42p ea TEN FOR £3.65

#### DIODES

OAS1 & OAS1 GERMANIUM 5p.

1N4001 1A50V & 1N4002 5p\*

1N4004 6p\* 1N4007 9p\*

1N4148 & 1N914 SILICON 4p.

ZENERS BZY88 400mW 9p.

ZENERS 1W 17P. Z1Jnoieel 1

BRIDGE RECTIFIER 1A50 18p

1A400V 25p. 4A100V 45p

SCR's TRIACS

SCR's TAG1/400 1A400V 40p\*

1A50V 25p\* 1A 600V 65p\*

C106D 4A400V SCR ONLY 47p\*

TRIAC SC146D 10A 400V 11p.

10A 400V INT. Diac £1.25\*

16A 400V DISCO TRIAC £1.75\*

16A 400V INT. Diac £2.\*

DIACS: BR100 25p\*

BULK OFFERS PER 100off each.

1N4001 £2.50\* 1N4004 £3.50\*

AC128 £10 \* AC176 £12 \*

BC107 £6.80\* BC108 £6.80\*

BC109 £7.00\* 2N3055 £7.80\*

NE555 £37 \* 741C(8) £18 \*

#### BARGAIN PAKS

£1 ea. Full spec.

PAK A 10 RED LEDS our choice 11\*

PAK B 5 741C OP AMP 8 PIN 11\*

PAK C 4 2N3055 11\*. D 12 BC109 11\*

PAK E 10 BC182 11\*. F 11 2N3704 11\*

PAK G 8 BFY51 11\*. H 9 2N3819 11\*

PAK J 9 2N3053 11\*. K 40 1N914 11\*

NEW PAK M 4 PLASTIC 3055 90W 11\*

#### Oil sockets

TOP QUALITY NYLON SOCKETS, HALF PRICE 8, 14, OR 16 PIN 12p\*

SOLDERCON PINS: 100 65p\* 1000 £3.50

SLIDER CLEARANCE WHILE STOCKS LAST ALL 10p ea.

TELEPHONE 54525

# PRACTICAL WIRELESS

VOL. 52 NO. 1

ISSUE 831

MAY 1976

BRITAIN'S PREMIER MAGAZINE FOR THE DO-IT-YOURSELF RADIO AND ELECTRONICS CONSTRUCTOR

## EDITOR

Lionel E. Howes, G3AYA

## ASSISTANT EDITOR

Eric Dowdeswell, G4AR

## ART EDITOR

Peter Metalli

## PRODUCTION & NEWS EDITOR

Colin Riches

## TECHNICAL SUB-EDITOR

Bill Tull

## TECHNICAL ARTIST

Alan Martin

## SECRETARIAL

Karen O'Neil  
Jill Austin

## ADVERTS MANAGER

01-261 6275 Roy Smith

## CLASSIFIED ADVERTS

01-261 5762 Colin R. Brown

Advertisement correspondence and enquiries to the Advertisement Manager, Roy Smith, Practical Wireless, Kings Reach Tower, Stamford Street, London, SE1 9LS

Published by IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. Tel. 01-634 4444

## BINDERS

Binders (£2.10 from May 1st) and indexes 45p (inc. VAT) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London, SE1 0PF.

## BACK NUMBERS

We regret that we are unable to supply back numbers of Practical Wireless. Readers are recommended to enquire at a public library to see copies. Requests for specific back numbers of Practical Wireless and Television can be published in our CQ Column.

## ● NEWS & COMMENT

- 24, 25 NEWS . . . NEWS . . . NEWS . . .
- 34 BOOKS RECEIVED
- 38 LETTERS—readers voice their views
- 46, 57 HOTLINES on recent developments—*Ginsberg*
- 47 NEXT MONTH IN PRACTICAL WIRELESS
- 58, 59 PRODUCTION LINES—news on products of interest—*Colin Riches*
- 60 CQ! CQ! CQ! CQ! CQ!
- 65 P.W. READERS' PCB SERVICE
- 70 TELEVISION—contents of our 'sister' magazine
- 73 ON THE AIR—Amateur Bands—*Eric Dowdeswell, G4AR*  
Broadcast Bands SW—*Derek Bell*  
Broadcast Bands MW—*Charles Molloy*
- 78 KINDLY NOTE—notes on published articles

## ● CONSTRUCTIONAL

- 26 3-BAND R.F. MINI AMPLIFIER—*F. G. Rayer*
- 29 TAKE 20, No. 74 (Snap Machine)—*David Andrews*
- 32 A.F. SIGNAL SOURCE—*W. Mooney*
- 48 RHYTHM GENERATOR—*A. S. Webb B.Sc.*
- 66 SIMPLE LOGIC INDICATOR—*Peter Hemingway*

## ● OTHER FEATURES

- 30 TECHNICROSS—Puzzle No. 13
- 31 SPECIAL PRODUCT REPORT—Bi-Pre-Pak 'Super Spark' Capacity Discharge Ignition Kit
- 37 GOING BACK—*Colin Riches*
- 41 GENERAL SERVICING, Part 3, Valve Radios—*Les Lawry-Johns*
- 62 ECONOMY CONVERSIONS—*B. B. Rafter*
- 69 IC OF THE MONTH—Motorola MC1312P Quadraphonic Decoder

**EXTRA THIS MONTH!**

**DOUBLE-SIDED RADIO SERVICING CHART**

## COPYRIGHT AND QUERIES

© IPC Magazines Limited 1976. Copyright in all drawings, photographs and articles published in "Practical Wireless" is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by "Practical Wireless" to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

We regret that we cannot answer technical queries by telephone nor can we provide information or advice on manufacturers' products other than that given in the magazine. We will endeavour to assist readers who have queries relating to articles published but we cannot offer advice on modifications to our published designs. All correspondents expecting a reply should enclose a stamped addressed envelope.


# CLEARANCE OFFER!

## SEW PANEL METERS

AT GREATLY REDUCED PRICES
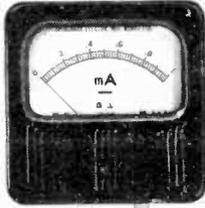
### BAKELITE PANEL METERS—MODEL MR 65

Dimensions: Front 80mm x 80mm square  
Panel Hole: 65mm diameter  
Accuracy ± 2.5%



#### RANGES

100µA	5A DC	150V AC*
500µA	10A DC	300V AC*
50-0-50µA	15A DC	500V AC*
100-0-100µA	30A DC	1A AC*
500-0-500µA	50A DC	5A AC*
1mA	5V DC	10A AC*
1-0-1mA	10V DC	20A AC*
5mA	15V DC	30A AC*
10mA	20V DC	50A AC*
50mA	50V DC	500mA AC
100mA	150V DC	50mV DC
500mA	300V DC	100mV DC
1A DC	30V AC*	
2A DC	50V AC*	


**£2-95 each**

25µA £3-95 each  
50µA £3-25 each  
VU Meter £3-40 each  
P/P + Ins. 15p

\* Moving iron (all others are moving coil).
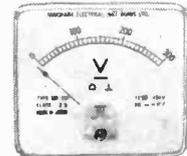
### CLEAR PLASTIC PANEL METERS—MODEL MR 85P

Dimensions: Front 110mm x 120mm wide  
Panel Hole: 85mm  
Accuracy ± 2.5%



#### RANGES

**£3-95 each**

1A Meter 1mA £4-55 each  
VU Meter £4-55 each  
P/P + Ins. 15p.

50µA	10mA	50V DC
100µA	50mA	150V DC
200µA	100mA	300V DC
500µA	500mA	15V DC
50-0-50µA	1A DC	300V AC
100-0-100µA	5A DC	1A AC*
500-0-500µA	15A DC	5A AC*
1mA	30A DC	10A AC*
1-0-1mA	10V DC	20A AC*
5mA	20V DC	30A AC*

\* Moving iron (all others are moving coil).

### EDUCATIONAL METERS—MODEL ED 107

High quality moving coil meters ideal for school use and many other applications. Housed in strong black plastic cases. Clear view front. 3" mirror scale. Fully insulated terminals will accept either spade or 4mm plug.  
Dimensions: 100mm wide x 90mm deep x 105mm high overall.  
Accuracy ± 2%



#### SINGLE RANGE MODELS

50µA	1A DC	15V DC
100µA	5A DC	20V DC
50-0-50µA	5V DC	50V DC
1mA	10V DC	300V DC
1-0-1mA		

#### DUAL RANGE MODELS

500mA/5A DC	5V/15V DC
5V/50V DC	1A/15A DC

**£5-95 each**

P/P + Ins. 15p

Available for personal shoppers at LASKYS




481 Oxford Street, W.1. 01-493 8641  
311 Edgware Road, W.2. 01-262 0387  
42 Tottenham Court Road, W.1. 01-636 0845  
3 Lisle Street, W.C.2. 01-437 8204

MAIL ORDERS AND ACCOUNT ENQUIRIES TO HEAD OFFICE.  
LASKYS, CUSTOMER SERVICES DIVISION,  
DEPT. 'J' AUDIOTRONIC HOUSE, THE HYDE HENDON, NW9 6JJ.  
Telephone: Mail Order 01-200 1321 or 01-200 0037  
(24 hour answerphone) Accounts: 01-200 0444  
Telex: 924920  
Access, Barclaycard and Diners Club accepted at all branches or by telephone at head office.  
ALL PRICES INCLUDE VAT.



RSC

## DISCO SYSTEM 40 WATT

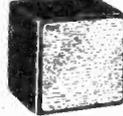

Consisting of Twin Turntable Console with Pre-Amp and built-in Power Output. Sep. vol. controls for each T/table. H/phone monitoring facilities. Sep. Bass and Treble controls. Mic. Vol. control. Neon Mains Indicator. Plus Pair 12" Spkrs. in matching Rexine covered cabinets.  
Terms: Dep. £15-99 and 18 fortnightly paymts. £5-41. (Total £113-37)  
**AS ABOVE LESS SPEAKERS** carr. £3 **£79-95**  
Terms: Dep. £9-00 and 18 fortnightly payments £4-61 (Total £91-98).

## MOBILE DISCO CONSOLE £59-95

MIC. JACK. PHONE JACK. MONITOR VOL. CONTROL. MONITOR SELECTOR DECK (1) Vol. Control. DECK (2) Vol. control. Mic. Vol. Control. Treble Control. Bass Control ON/OFF Switch. Neon Indicator. Twin Turntables.



Terms: Dep. £7-95 and 18 fortnightly paymts. £3-33. Total £67-89.

## POWER (SLAVE) AMPLIFIER 100 WATT

Suitable for use with above or other DISCO-Consols. Also for increasing output of lower-powered Amplifiers. Terms: Dep. £9-00 and 8 mthly payments of £5-22 (Total £50-76) carr. £1



## TITAN GROUP/DISCO SPKRS

GUARANTEED FOR 5 YEARS

T12/35 12" 35w	£14-00	£10-95
T12/60 12" 60w	£21-00	£14-95
T12/100 12" 100w	£36-00	£23-95
T15/60 15" 60w	£27-00	£17-99
T15/70 15" 70w	£28-00	£19-95
T15/100 15" 100w	£39-50	£28-95
T18/100 18" 100w	£44-00	£29-95



Imp. 8-15 Ω

## SPECIAL OFFER FOR ONE MONTH ONLY FANE CRESCENDO

12 BASS 12" Super Bass Guitar Speaker  
Our Price **£33-95**  
Carr. Free  
Rec. Ret. Price **£49-30**

#### MONTHLY PAYMENTS

MODEL	DEPOSIT	TOTAL
Model T12/35	(P) £4-90 + 8 at £2-62	£25-88
Model T12/60	(P) £5-90 + 8 at £2-37	£23-98
Model T12/100	(Ea) £4-99 + 8 at £3-00	£28-85
Model T15/60	(Ea) £3-99 + 8 at £2-25	£21-99
Model T15/70	(Ea) £4-95 + 8 at £2-37	£23-81
Model T15/100	(Ea) £6-00 + 8 at £2-37	£23-86
Model T18/100	(Ea) £6-95 + 8 at £3-37	£33-81

## R.S.C. TRANSFORMERS, L.F. CHOKES & RECTIFIERS

FULLY GUARANTEED. Impregnated and Interoiled where necessary.

Primaries 200-850v. 500/s. Screened ALL PRICES INCLUDE VAT

MIDGET CLAMPED TYPE	21-75
260v. 60mA 6.3v. 2a.	£1-85
250-0-250v. 60mA 6.3v. 2a.	£2-60
FULLY SHROUDED UPRIGHT MOUNTING	£2-60
250-0-250v. 60mA 6.3v. 2a. 0-5-6.3v. 3a.	£4-35
300-0-300v. 130mA 6.3v. 4a. C.T. 6.3v.	£5-20
1a. for Mullard 510 Amplifier	£5-20
350-0-350v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4-35
350-0-350v. 150mA 6.3v. 4a. 0-5-6.3v. 3a.	£5-20
425-0-425v. 200mA 6.3v. 4a. C.T. 5v. 3a.	£9-85
425-0-425v. 200mA 6.3v. 4a. 6.3v. 4a. 5v. 3a.	£10-00
450-0-450v. 250mA 6.3v. 4a. C.T. 5v. 3a.	£10-45

TOP SHROUDED DROP-THROUGH TYPE	£2-60
250-0-250v. 70mA 6.3v. 2a. 0-5-6.3v. 2a.	£2-90
250-0-250v. 100mA 6.3v. 3a.	£2-90
250-0-250v. 100mA 6.3v. 2a. 6.3v. 1a.	£3-20
350-0-350v. 80mA 6.3v. 2a. 0-5-6.3v. 2a.	£3-80
200-0-250v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4-35
300-0-300v. 100mA 6.3v. 4a. 0-5-6.3v. 3a.	£4-35
300-0-300v. 130mA 6.3v. 4a. 0-5-6.3v. 1a	£4-35
suitable for Mullard 510 Amp.	£5-20
350-0-350v. 100mA 8.3v. 4a. 0-5-6.3v. 3a.	£4-35
300-0-350v. 150mA 6.3v. 4a. 0-5-6.3v. 3a.	£5-20

FILAMENT OR TRANSISTOR POWER PACK  
Type: 12v. 1a. £1-10. 6.3v. 1.5a. £1-06. 6.3v. 2a. £1-10. 6.3v. 3a. £1-70. 6.3v. 6a. £2-60. 12v. 3a. or 24v. 1.5a. £2-60. 0.9-18v. 1.1a. £2-26. 0-12-25-42v. 2a. £3-19  
AUTO (STEP UP/STEP DOWN) TRANSFORMERS  
0-110/120v. 200-230-250v. 50-80w. £2-90 150 watts £6-20, 250 watts £8-87, 500 watts £9-84  
CHARGER TRANSFORMERS  
0-9-18v. 1.1a. £2-08. 2ja. £2-26. 3a. £2-32. 5a. £2-84. 6a. £3-19. 8a. £2-46

OUTPUT TRANSFORMERS  
Standard Pentode 5000 to 3 ohm, or 7000 ohm to 3 ohm £1-12.  
Push Pull 8 watts EL84 to 3 ohm or 15 ohm £1-68; Push Pull 10-12 watts 6v. 6 to 3 ohm or 15 ohm £2-61; Push Pull 10-12 watts to match 6v. 6 to 3, 5, 8 or 15 ohm £2-72; Push Pull P1E4 to 3 or 15 ohm £1-12; Push Pull Ultra Linear for Mullard 610 etc. £4-35; Push Pull 15-18 watts, sectionally wound 6L6 KT66 etc. from 3 or 15 ohm. £3-71p. Push Pull 20 watt high quality sectionally wound EL34 6L6 KT66 etc. to 3 or 15 ohm, fully shrouded. £6-37p.

SELENIUM RECTIFIERS  
F.W. (Bridged)  
All 6/12 v. D.C. output. Max. A.C. input 18v. 1a 45p, 2a 57p, 3a 65p, 4a 85p, 5a £1-15.  
L.F. CHOKES 150mA. 7-10H. 250 Ω £1-88; 100mA. 10H. 200 Ω £1-10. 60mA. 10H. 400 Ω £1-00

HI-FI ITEMS  
PREVIOUSLY ADVERTISED INC.  
DISCOUNT LINES  
ARE STILL AVAILABLE.  
RSC PRICES INCLUDE VAT

# RSC 100 WATT DISCO SYSTEM

50 WATT SPEAKER

AT FANTASTIC LOW PRICES!

50 WATT SPEAKER

HEADPHONES MICROPHONE

TWIN TURNTABLE WITH PRE-AMP. and POWER AMPLIFIER Complete with lid

- Units listed below
- (a) DISCOMAJOR TWIN TURNTABLE CONSOLE with integral 100W amplifier
  - (b) PAIR OF HI-FI M'PHONES
  - (c) MATCHING 'MIKE'
  - (d) PAIR 50 WATT SPEAKERS Black Rexine covered Cabinets Size approx. 18" x 18" x 8"
- (a) (b) (c) & (d) Carr. £24-00
- £159-95**

## TDI DISCO CONSOLE

Incorporating twin BSR MP90 type turntables and Sonotone or Acos Cartridges with diamond styl. Separate Vol. controls for each turntable. Also MONTROING FACILITIES plus Treble and Bass Controls. Separate input for 'mike' with vol. control. Black Vynide covered Cabinet with lid. Or DEP. £14-95 and 18 fortnightly pymts. £5-47 (Total £138-41) Carr. £1-50

**£99-95**

DEP. £19-95 & 18 fortnightly.

Payments of £9-19 (Total £185-37)

## STEREO VERSION

Of Above System  
Or DEPOSIT £24-95 and 18 fortnightly pymts. £209-95 Carr. £5-00

## TD2S STEREO VERSION OF ABOVE

Terms DEPOSIT £20 and 18 fortnightly payments £6-71 Carr. £1-60 (Total £140-78)

## FANE DISCO 60C SPKR UNITS

Supplied with above in lieu of £12/50 units  
Fabulous specialist range Spkr in heavy Vynide covered for cabinets with protective Corner pieces. List Price £87-00 pr. **£25** extra

SYSTEMS UP TO 300 WATTS OUTPUT AT UNBEATABLE PRICES Send for Catalogue

## DISCOMASTER TWIN TURNTABLE POWER CONSOLE £119-95

Twin McDonald MP60 type turntables. Sonotone or Acos cartridges with Carr. diamond styl. Facilities at TD1 Console but with built-in 100 watt Power Amp. £2-50 plifier, complete with lid. Or Dep. £18-95 and 18 fortnightly pymts £6-78 (Total £185-99)

STEREO VERSION £155 or DEPOSIT £25 and 18 fortnightly pymts £8-30 (Total £174-40) Carr. £3

## R.S.C. COLUMN SPEAKERS IDEAL FOR VOCALISTS AND PUBLIC ADDRESS

All types 15 Ohms covered in Vynide & Vynair

TYPE C132 40-50 WATTS £27-95

Incorporating two exceptionally efficient 13" x 8" speaker units. Dep. £3-95 and 8 monthly payments £3-50 (Total £31-95) Carr. 65p

TYPE C480 70 WATTS Fitted four 12" 25 watt Highly sensitive high flux speakers with high power voice coils. Size approx. 54" x 14" x 11". Dep. £9-00 and 12 mthly pymts. £4-00 (Total £57-00) Carr. 85p

**£49-95**

## ALL RSC PRICES INCLUDE VAT

INTEREST on Credit Purchases REFUNDED settled in 3 months

## SUPER MINSTREL 10 W GUITAR AMP.

Incorporating Tremolo and 10" Speaker. Output 10 watts R.M.S. Continuous. 3 Jack Inputs for Microphone and Instrument. Main Moon Controls: Volume, Tone, Tremolo Speed, Tremolo Intensity.

Terms: DEPOSIT £7-78 and 8 monthly payments £3-40 (Total £28-93) Carr. free

**£29-99**

## RSC PHANTOM 50 COMBO AMP. £59-95

Rating 50 watts. 3 inputs. 2 vol. controls—Bass, Treble Presence. Carr. £1-50 Suitable for Lead or Rhythm Guitar, mic. Radio, Tape etc. Inc. High Flux 18" 50w Speaker. Dep. £7-95 & 8 monthly payments £7-48 (Total £67-79).

## PHANTOM 50/GP all purpose version of above. £69-95

Extra high sensitivity. Suitable for Bass Guitar. Carr. £1-75  
Or Dep. £9-95 & 8 monthly payments £8-70 (Total £79-55)

## FAL PHASE 50-4 AMPLIFIER 50 WATT

Solid state. 4 Sep. controlled inputs Plus master vol. control. Ind. Bass and Treble Controls. Protection against serious o/p overloading. O/p for spkrs. 8 to 16 ohms. Size 17" x 7" x 7". 200-250v. A.C. mains. O/p 50w. R.M.S. Deposit £8-80

& 8 mthly. payments £5-75. Total £24-80 Carr. Free.

**£48-60**

## FAL PHASE 50-4 WITH L12/2 70 W TWIN SPEAKER UNIT

Vynide covered. Fitted with protective corner pieces. Carr. £2-50. **£88-00**  
Or Dep. £10-00 & 12 monthly payments £7-07 (Total £102-04)  
or with

## L125 100 W TWIN SPKR UNIT

Suitable for all purposes inc. Bass Guitar Carr. £2-50 **£94-50**  
Terms. Dep. £14-50 & 18 fortnightly payments £5-15 (Total £107-20)

## FANE CRESCENDO SPEAKERS

FULL RANGE AVAILABLE AT ALL BRANCHES



## I.S.E. JINGLE MACHINES JINGLE 8+

Employing Standard 8 Track Cartridge Or Dep. **£37-95**  
£4-85 & 8 monthly pmts £4-85 (Total £48-65).



## HEAVY DUTY CABINETS

Black Vynide covered. Fitted Protective Corner Pieces. Cut for various Speaker Combinations. Carr. £1 each unit. Sizes approx.:

18" x 18" x 9"	£10-95
24" x 24" x 12"	£19-95
36" x 24" x 12"	£26-95
36" x 24" x 12"	£26-95
30 1/2" x 28 1/2" x 12"	£28-95

## LIQUID WHEEL from PROJECTORS £29-95

## 'SOUND TO LIFE' SYSTEM PULSAR special price £106-95

complete kit  
Dep. £14-95 and 18 fortnightly pymts. £5-98. (Total £121-69). Super SL Unit. 1000 watt per channel. Manual override buttons. 2 spotbanks with 6 bulbs (3 sep. colours) 5 yd. and 10 yd. leads, fitted plugs. Units sold sep.

FAL SOUND-TO-LIFE UNIT £21-60

3-WAY SPOT BANK Excluding Bulbs Each **£16-20**

COMPLETE SYSTEM Carr. £1-50 **£55**  
Incl. 2 Spotbanks and bulbs.


## New Branches at YORK CARLISLE, DEWSBURY and PRESTON

- OPEN ALL DAY SATURDAYS (5 Day Week)
- BRADFORD 10 North Parade (Closed Wed.). Tel. 25349
  - BOLTON 23 Deansgate. (Closed Wed.). Tel. 33512
  - BIRMINGHAM 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)
  - CARLISLE 8 English Street. (Closed Thurs.). Tel. 38744
  - COVENTRY 17 Shelton Sq., The Precinct. Tel. 25993
  - DERBY 97 St. Peter's Street. (Closed Wed.). Tel. 41381
  - DARLINGTON 19 Northgate (Cl. Wed.). Tel. 68043
  - DEWSBURY 9/11 Kingsway (Closed Tues.). Tel. 480558
  - DONCASTER 3 Queensgate, Waterdale Centre. (Closed Thurs.). Tel. 63069

Barclaycard and Access accepted

- All items subject to availability. Prices correct at 5.3.76 E. & O.E.
- GLASGOW 101 Lothian Rd. (Cl. Wed.). Tel. 229 9501
  - LONDON 7 Whitfrigate (Closed Thurs.). Tel. 248 4188
  - LEICESTER 32 High Street (Closed Thurs.). Tel. 56420
  - LEEDS 5-7 County (Mecca) Arcade, Briggate (Closed Wed.). Tel. 458252
  - LIVERPOOL 35 Dawson's Way, St. John's Shopping Centre (Closed Wed.). Tel. 458252
  - LONDON 238 Edgware Road, W.2. (Closed Thurs.). Tel. 723 1829
  - MANCHESTER 60A Oldham Street (Closed Wed.). Tel. 236 8778
  - MIDDLESBROUGH 103 Linthorpe Rd. Tel. 210585 (Closed Wed.)

- MAIL ORDERS & EXPORT ENQUIRIES TO—AUDIO HOUSE, HENSCOMBER LAKE, LEEDS, 13. Tel: Pudsey (09735) 77831.
- MAIL ORDERS MUST NOT BE SENT TO SHOPS TERMS G.W.O. or C.O.D. No C.O.D. under £1. POSTAGE 40p PER ORDER OR AS QUOTED.
- TRADE SUPPLIED. LARGE S.A.E. REQUIRED FOR FREE CATALOGUE
- NEWCASTLE UPON TYNE 24 Newgate Shopping Centre, 59 Graining St. (Closed Wed.). Tel. 21469
  - NOTTINGHAM 19/19A Market Street (Closed Thurs.). Tel. 48068
  - PRESTON 41 Friargate Walk, St. Georges Shoppg Pk. Tel. 51979
  - SHEFFIELD 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.). Tel. 20718
  - STOCKPORT 8 Little Underbank (Closed Thurs.). Tel. 480-0777
  - SUNDERLAND 5 Market Sq. (Closed Wed.). Tel. 70573
  - YORK 5 CHURCH ST. (Closed Wed.) Tel. 34355

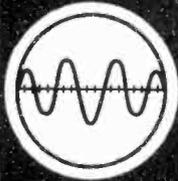

# TUAC

TRANSISTOR UNIVERSAL AMPLIFICATION CO. LTD.  
163 MITCHAM RD. LONDON SW17 9PG 01-672 3137/9080

## MONO DISCO MIXER WITH AUTO FADE



Designed for the discerning D.J. of professional standard. Offering a vast variety of functions. Controls: Mic Vol; Tone, over-ride depth, auto/Manual Sw; Tape Vol; L & R Deck Faders; Deck Volume; Treble and Bass; H. Phon Vol Selector; Master Vol on/Off Sw. Max output 1V RMS.  
Specification: Deck Inputs—50mV into 1M $\Omega$ ; Deck Tone Controls—treble +20 -10dB at 12kHz, Bass +22 -15dB at 40Hz; Mic Input—200 ohms upwards, 2mV into 10k $\Omega$ ; Mic Tone Control—Total Variation Treble 15dB, Total Variation Bass 10dB; Tape Input—30mV into 47k $\Omega$ ; Power Requirements—30-50 volts at 50mA.

**£31.50**

PANEL SIZE  
18 x 4 1/2 in.  
DEPTH 3 in.

## PRE AMPLIFIERS



### VA08

Designed for use with TUAC power amplifier modules. Extensive research has gone into various wide range tone control circuits to produce superb sound quality. Thousands are already in use in high quality professional amplification systems.

**VA08** Vol, Treb, Mid and Bass controls. Hi. IMP. FET, I/P suitable Mid. Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 1kHz Bass +20 -10dB at 40Hz.

**£6.50**

**VA06** Vol, Treb, and Bass controls. Sensitivity 8mV. Treb +28 -15dB at 12kHz, Bass  $\pm$ 18dB at 40 Hz.


**£5.50**

**SVA08 STEREO PRE AMP** Vol, Treb, Mid and Bass controls, I/P suitable, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treble +35dB at 16kHz. Mid +20 -15dB at 4kHz. Bass +20 -10dB at 40Hz Plus Full Balance Control. Full I/C operation supply voltage  $\pm$  15VDC.

**£12.50**

## ★ TUAC AMPLIFIER MODULES ★ POWER AND QUALITY ★

- 125 watts RMS continuous sine wave output

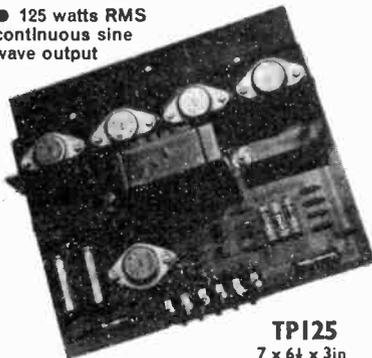


**TP125**  
7 x 6 1/2 x 3 in

**£19.50**

- 4 R.C.A. 150 watt 15 amp output transistors

- Rugged layer wound driver transformer
- Short—Open—and Thermal overload protection
- Only 8 connections

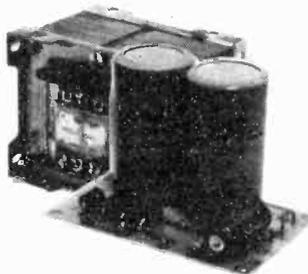Power supplies vacuum impregnated. Transformers with supply board incorporating pre-amp supply.



**PS 250** for supplying 2 TP125s

**£22.00**

**PS 60/60** for supplying 2 TL60s

**£19.50**

**PS 125**  $\pm$  45 volts for TP125

**£13.75**

**PS 100**  $\pm$  43 volts for TL100

**£12.00**

**PS 60**  $\pm$  38 volts for TL60


**£11.50**

**PS 30**  $\pm$  25 volts for TL30

**£7.50**

**PSU 2** for supplying disco mixer

**£5.50**

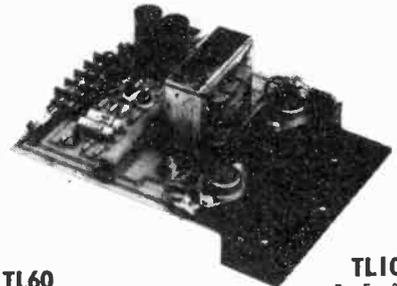

**TL60**  
5 x 5 x 3 in

- 60 watts RMS continuous sine wave output
- 2 R.C.A. 110 watt 15 amp transistors

**£13.50**

**TL100**  
5 x 5 x 3 in


- 100 watts RMS continuous sine wave output
- 2 R.C.A. 150 watt 15 amp transistors

**£16.25**

Specification on all power modules. All output power ratings  $\pm$  0.5dB; Output impedance 8-15 ohms; THD at full power 2% typically 1%; input sensitivity 60mV into 10k $\Omega$ ; Frequency response 20Hz-20kHz  $\pm$ 2dB; Hum and noise better than -70dB.
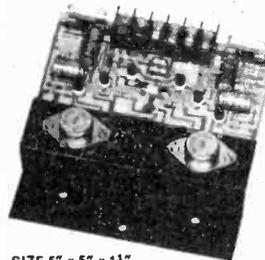
### STOCKISTS—CALLERS ONLY

Geo. Matthews, 85/87 Hurst Street, Birmingham (Tel. 021-622 1941)  
Arthur Sallis Ltd., 28 Gardner St. (Tel. Brighton 65806)  
Bristol Disco Centre, 26 The Promenade, Gloucester Road (Tel. Bristol 41666)  
Socodi, 9 The Friars (Tel. Canterbury 60948)  
Cookies Disco Centre, 132 West St. (Tel. Crewe 4739)  
A1 Music Centre, 88 Oxford Street, Manchester (Tel. 061-236 0340)  
Damon Electronics, 99 Carrington Street (Tel. Nottingham 53880)  
Electra Centre, 58 Lancaster Road (Tel. Preston 58488)  
Mitchell Electronics, 64 Winchester Street (Tel. Salisbury 23689)  
Mitchell Electronics for Southampton area



SIZE 5" x 5" x 1 1/2"

### TL30 New from TUAC TL30 D.C. coupled power amplifier module.

- OUTPUT POWER 30 WATTS RMS CONTINUOUS SINE WAVE
- OUTPUT IMPEDANCE 8-15 OHMS
- T.H.D. AT FULL POWER 0.5%
- SIGNAL TO NOISE RATIO -85dB
- INPUT SENSITIVITY 60mV INTO 50K OHMS
- FREQUENCY RESPONSE 25Hz-50kHz
- 8 TRANSISTORS
- 4 DIODES
- ONLY SIX CONNECTIONS

**£9.75**

Send large stamped addressed envelope with all enquiries or send £1 (refundable against purchase) for fully illustrated 20 page catalogue.

# FUZZ LIGHTS




RED GREEN  
BLUE AMBER

240 volt a.c. Long Life Candle Bulb, Revolving Reflector, adds a new dimension to disco lighting effects.


**£19.50**

# TUAC

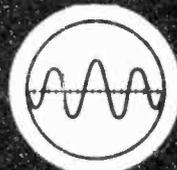

MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT.  
PERSONAL SHOPPERS MON TUES THURS FRI and SAT  
9 a.m. - 6 p.m. WED 9 a.m. - 1 p.m.

## TUAC STEREO DISCO MIXER

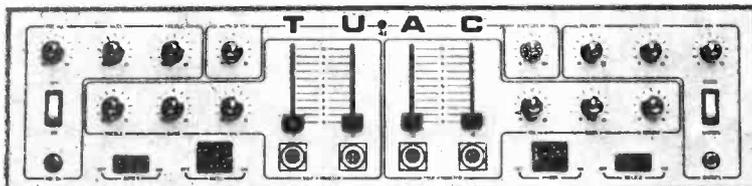

**INPUTS.** Four identical stereo inputs available with any equalisation. Two magnetic and two flat supplied as standard. High quality slider control on each channel. Volume treble, and bass controls for each pair of sliders. Sensitivity mag., 3mV (R.I.A.A. comp.). Flat 50mV at 1kHz. Bass controls  $\pm 13\text{dB}$  at 60Hz. Treble controls  $\pm 18\text{dB}$  at 15kHz.


**OUTPUTS.** Up to 3 volts (+12dB) available. Attenuated output for TUAC Power Modules. Rotary Master and Balance controls. Band width 15Hz-25kHz  $\pm 1\text{dB}$ .

**P.F.L.** Output 250mV into 8 ohms. Rotary Volume Control. Monitoring facility for all 4 channels. Selection via touch sensitive illuminated switches. Switched visual cue indicator.

**MISCELLANEOUS FACILITIES.** Two illuminated deck on/off switches. Mains illuminated on/off switch. Auto fade illuminated on/off switch. Mains powered with integral screen and back cover. Complete with full instructions.

**£75**

Size: 25in long x 6in high x 3in deep

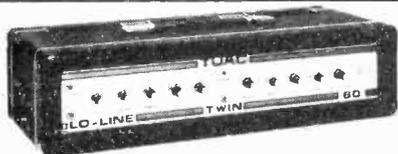

**TWIN 60**

- ★ Lo-Line Twin 125 (125 watts version) **£98.00**
- ★ Lo-Line 60 (single pre-amp version) **£65.00**
- ★ Lo-Line 125 (single pre-amp version) **£81.00**
- ★ Lo-Line 125 slave output power, 125 watts R.M.S. **£70.00**

**£80.00**


Output power 60 watts R.M.S. Four inputs, two channels each with volume, treble, middle and bass controls. Variable wave form control

▲▼ All Lo-Line Amplifiers are 25in long x 11in high x 6in deep ▲▼

## NEW TUAC LO-LINE STEREO 250 125 WATTS PER CHANNEL — £130
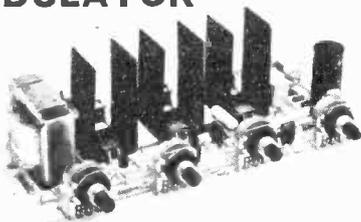
### 3 CHANNEL LIGHT MODULATOR


- RCA 8A Triacs
- 1000W per channel
- Each channel fully suppressed and fused
- Master control to operate from 1W to 100W
- Full wave control
- 12 easy connections



**£15.50** (Single Channel Version 1500 Watts **£7.25**)
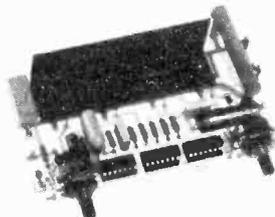
### 4 CHANNEL SOUND TO LIGHT SEQUENCE CHASER—4LSMI

- RCA 8A Triacs
- 1000W per channel
- Fully suppressed and fused
- Switched master control for sound operation from 1W to 125W
- Speed control for fixed rate sequence from 8 per minute to 50 per second
- Full logic integrated circuitry with optical isolation for amplifier protection
- Full wave control
- 13 easy connections



Patents applied for **£17.25**

### ADD SEQUENCE CHASING AND DIMMING EFFECTS TO YOUR TUAC 3 CHANNEL LIGHT MODULATOR



- Speed Control 3 per min. to 10 per sec.
- Full logic integrated circuitry
- Dimmer control to each channel
- 9 easy connections

**SEQUENCE DIMMER MODULE—3SDMI £11.75**

### HOW TO ORDER BY POST

Make cheques/P.O.'s payable to  
TUAC LTD (PW5)  
or quote Access/Barclay Card No.  
and post to TUAC LTD (PW5)  
163 Mitcham Road, London, SW17 9PG  
We accept phone orders against  
Access/Barclay Card Holders  
Phone: 01-672 3137/9080

**ALL PRICES INCLUDE V.A.T. POSTAGE AND PACKING FREE**

ACCESS & BARCLAY CARDS ACCEPTED JUST SEND OR PHONE US YOUR NUMBER. H.P. ENQUIRIES INVITED

# TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH

NO HIDDEN EXTRAS—Prices include VAT and P & P. EXCEPT WHERE CARRIAGE WILL BE ACCORDING TO WEIGHT & DISTANCE—BRS.

Wide range of Audio accessories & semiconductors.

CALLERS WELCOME (MON.-FRI.) OR SEND FOR LISTS.

**MAINS ISOLATING**  
PRI. 120/240V  
SEC. 120/240V  
CENTRE TAP WITH SCREEN  
Ref. VA (Watts) £

07*	20	3-97
149	60	5-84
150	100	6-67
151	200	10-43
152	250	12-67
153	350	14-99
154	500	17-21
155	750	23-69†
156	1000	33-01†
157	1500	37-68†
158	2000	42-03†
159	3000	66-40†

\*115V or 240V Sec. only.

**12 and or 24 Volt**  
PRIMARY 240-250 VOLTS  
Ref. Amps

111	12v	5	0.25	1-97
213	1-0	0-5		2-64
71	2	1		2-80
68	3	1		4-60
18	4	2		3-98
85	5	2		4-91
70	6	3		5-36
108	8	4		6-41
72	10	5		6-86
116	12	6		7-42
17	16	8		9-13
115	20	10		13-52
187	30	15		16-86
226	60	30		19-08†

**50 VOLT RANGE**  
Prim. 200-240V  
Sec. 0-19-25-33-40-50V  
Ref. Amps

102	0-5	£ 4-46
103	1-0	£ 4-60
104	2-0	£ 6-26
105	3-0	£ 7-63
106	4-0	£ 9-83
107	6-0	£ 15-08
118	8-0	£ 16-46
119	10-0	£ 19-17†

**SWITCHES**  
SPST TOGGLE 3 FOR £1-06  
DPDT TOGGLE 6 FOR £1-30  
DPDT SLIDE 6 FOR £1-06

**ANTESOLDERING IRONS**  
15W £3-17 18W £2-92 25W £2-71  
SOLDERING IRON KIT £4-17  
STAND FOR ABOVE £1-49

**MAGNETIC TO CERAMIC CARTRIDGE CONVERTER**  
OPERATING VOLTAGE 20-45V  
ONLY £3-51.

**COMPONENT PAKS**

200 Mixed value resistors (count by weight)  
150 Mixed value capacitors (count by weight)  
30 Mixed value precision resistors 1/2w 2%  
15 Assorted pots & pre-sets  
10 Reed switches  
3 Micro Switches  
20 Assorted tag strips & panels  
ALL AT 95p PER PACK.

**HIGH VOLTAGE**  
Mains Isolating  
Prim. 200/220 or 400/440V  
Sec. 100/120 or 200/240V  
VA Ref. Amps £

60	243	5-77
350	247	13-33
1000	250	28-44†
2000	252	47-65†

**SCREENED MINIATURES**  
Ref. mA Volts £

238	200	3-0-3	1-98
212	1A, 1A	0-6, 0-6	2-71
13	100	9-0-9	1-96
235	330, 330	0-9, 0-9	2-04
207	500, 500	0-8-9, 0-8-9	2-73
208	1A, 1A	0-8-9, 0-8-9	3-94
236	200, 200	0-15, 0-15	1-95
214	300, 300	0-20, 0-20	2-82
221	700 (DC)	20-12-0-12-20	4-28
206	1A, 1A	0-15-20, 0-15-20	4-70
203	500, 500	0-15-27, 0-15-27	4-18
204	1A, 1A	0-15-27, 0-15-27	5-14
112	500	12-15, 20, 24, 30	2-68

**HIGH QUALITY MODULES**

3 Watt RMS AMPLIFIER	£3-06
5 Watt RMS AMPLIFIER	£3-50
10 Watt RMS AMPLIFIER	£3-86
25 Watt RMS AMPLIFIER	£5-13
125W RMS AMPLIFIER	£17-41
PRE-AMP for 3-5-10W	£8-30
PRE-AMP for 3-5-25W	£17-05
POWER SUPPLIES 3-5-10W	£1-68
POWER SUPPLIES 25-100W	£3-93
TRANSFORMER 3W	£2-42
TRANSFORMER 5-10W	£3-08
TRANSFORMER 25W	£3-95

**AUDIO KIT 25W**

3+25W Amplifiers  
1+ Pre-Amp  
1+ Power supply  
1+ Transformer  
1+ Front Panel  
1+ Kit of parts to include on/off switch, neon ind. Stereo headphone socket. Plus Instructions book £35-53.

**30 VOLT RANGE**  
Prim. 200-240V  
Sec. 0-12-15-20-24-30V  
Ref. Amps £

179	0-5	2-58
3	2-0	4-85
20	3-0	5-99
21	4-0	6-92
51	5-0	8-32
117	6-0	9-33
88	8-0	12-38
89	10-0	12-71

**AUTO TRANSFORMERS**  
Ref. VA Auto Taps (Watts) £

113	20	0-115-210-240	2-44
64	75		4-07
4	150	0-115-200-220-240	5-45
66	300		7-51
67	500		11-46
84	1000		17-25
93	1500		20-54†
95	2000		27-44†
73	3000		39-67†

**BRIDGE RECTIFIERS**

50V	2A	0-60
100V	2A	0-66
100V	6A	1-03
200V	1A	0-60
200V	2A	0-60
400V	2A	0-78
400V	4A	0-97
600V	2A	0-85
1000V	2A	0-97
500V	10A (PM 7A6)	2-71

**TEST METERS**

AVO 8 MK5	£61-54
AVO 72	£24-24
AVO TT 169	£24-54
AVO Cases and Accessories.	AVO

**CARTRIDGES**

Magnetic Sonotone 100	£5-85
Ceramic E.E.I.C.S 2000	£2-95

**TEAK AUDIO KIT 25W**  
Teak veneered cabinet  
16:1+11:1+3:1; aluminium chassis, heat sink and front panel brackets plus back panel and sockets etc. £12-16

**60 VOLT RANGE**  
Prim. 200-240V  
Sec. 0-24-30-40-48-60V  
Ref. Amps £

124	0-5	3-46
126	1-0	4-75
127	2-0	6-67
125	3-0	9-58
123	4-0	11-45
40	5-0	12-41
120	6-0	14-56
121	8-0	17-01†
122	10-0	20-95†
189	12-0	21-87†

**CASED AUTO TRANSFORMERS**  
240V mains lead input & USA 2 pin outlets.

20VA	£4-33	Ref 113W
150VA	£7-80	Ref 4W
500VA	£13-37	Ref 67W
1000VA	£19-88†	Ref 84W
2000VA	£31-00†	Ref 95W

**ON SITE TOOL ISOLATORS**  
240 to 110V - 500VA to 2kVA  
(as BS3535) Send for details

**POWER UNIT**  
CC12-05 Output Switched  
3-4-5-6-7-9-9-12V  
at 500mA. £4-92.

**STEREO FM TUNER**  
4 Pre-selected stations supply 20-35V. 90mA Max. £25-20

## Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

# prehard electronics

<b>TRANSISTORS</b>	<b>SAE FOR LISTS &amp; GIFT SIL 108 &amp; Plastic BC 108 while stocks last</b>	<b>INTEGRATED CIRCUITS</b>	<b>LED</b>
AC125 20	BC132* 50	12BC178B 18	125R Red 20p
AC128 20	BC135* 50	12BC179B 19	125A Amber 27p
AC127 20	BC136* 50	18BC182B* 11	126Y Yellow 27p
AC128 20	BC137* 50	18BC182L* 11	TIL209 Red 25p
AC132 35	BC138 15BC183B* 10	BC268B 13	
AC131 20	BC139 35BC183L* 10	BC269 13	
AC142 17	BC140 22BC184B* 12	BC287 20	
AC151 24	BC142 24BC184L* 11	BC290 27	
AC153 27	BC147A* 9BC186 25	BC301 26	
AC176 20	BC182 18	BC302 24	
AC188 20	BC203 30	BC313 38	
AD181 42	BC304 27	BD136* 37	
AD182 42	BC307A* 16	BD138* 39	
AF114 24	BC308A* 14	BD137* 44	
AF116 24	BC309B* 16	BD138* 47	
AF118 24	BC317A* 12	BD139* 54	
AF117 24	BC307 12	BD156* 75	
AF118 47	BC109B 12	BD166* 34	
AF124 50	BC158A* 12BC158A* 12	BD235* 70	
AF126 30	BC161* 15	BC298* 18	
AF126 28	BC116* 15	BC337* 18	
AF139 34	BC117* 18	BC338* 18	
AF186 50	BC118* 10	BC461 35	
AF239 37	BC126* 14	BC462 35	
		BC463 35	
		BC464 35	
		BC465 35	
		BC600 35	

# SAXON ENTERTAINMENTS LTD

# SYSTEM 7000

professional standards · realistic prices

## SAI208D—120 WATTS RMS POWER AMP


Uses 150W 16A RCA devices

All three types include

- 10 Transistors 4 Diodes—Fibre Glass P.C.B.
- Typical Distortion—0.4%; Noise—80dB
- Short, Open Circuit proof—Load line limiting
- Only FOUR Connections—Simplicity!
- High sensitivity (240mV) suits most mixers
- 30 Hz—40kHz  $\pm$  1dB Frequency response
- Single supply line—no output capacitor needed (95v)
- Standard 8 $\Omega$  output—will operate on other impedances
- Compact—6" x 3" x 1½" (15 x 8 x 4cm)
- All individually tested before despatch

All units individually tested and guaranteed

**SAI208D £19.50**

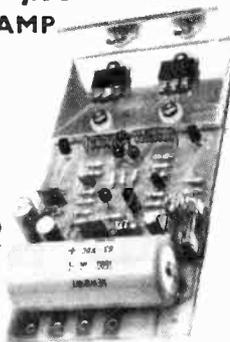

In the same series

**SA608**  
60 W. RMS  
into 8 $\Omega$  (65V)  
**£12.50**

**SA308**  
30W. RMS  
into 8 $\Omega$  (48V)  
**£9.50**

Large SAE brings leaflet

## POWER SUPPLIES

on glass-fibre P.C.B., high grade transformer, fully fused and ready to wire:

PM120/1 for one SA1208 **£11.60**


PM1202 for two SA1208D **£15.30**

PM601/2 for one or two SA608 **£10.50**

PM301/2 for one or two SA308 **£8.80**
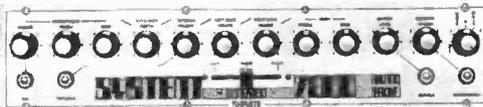
## SYSTEM 7000—DISCO CONTROL UNIT

- Complete and ready to plug in
- Totally encased—no soldering at all
- Tough, bold, two tone stainless panel—for panel mounting or freestanding
- Inputs for 2 ceramic cartridges/tape/microphone
- Individual deck controls AND left/right fader
- Low noise (–80dB) 20 Hz–50kHz  $\pm$  1dB
- Suits all Saxon amplifiers and most other makes
- ½ watt headphone monitor—five position switch with mute positions



- Controls—L. to R.: Mic, Vol/Treble/Bass, Autofade depth, L/Deck Vol, R/Deck Volume, Tape Volume, Treble, Bass, Master, Monitor Volume, Monitor Selector-On-Off

MONO **£34.50**

STEREO **£49.50**

## In Modular Form

Printed circuit sub-assembly version of disco control unit: All electronics included. Only plugs, socket and one switch required.

MONO **£18.50** STEREO **£27.50**


FRONT PANEL FOR ABOVE **£3.50**

## SYSTEM 7000 LIGHTING CONTROL UNIT

- Full control of 3kW of lights (1kW/channel)
- Audio control plus sequence plus override
- Variable speed sequence with slider function control
- Stainless steel two tone panel—matches mixer
- 13 transistors 8 diodes—advanced control circuitry
- High audio sensitivity—operates from any amplifier
- Attractive Bondene case—free standing or panel mounting
- Individual tone controls plus master audio control

Inc. case and plug—ready to use

**£38.00**

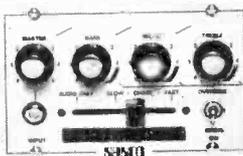

## SUPERFECT MODULE

On P.C.B. requires only plug/socket/panel for mounting as desired **£27.75**

## Soundlite 3kw Converter Module

O/P up to 1kW/channel: Individual tone and master controls: RCA 8A triacs: Scintillating Light Display: Operates from any amplifier: Glass-fibre PCB: Unbeatable value at

**£15.50**

## SYSTEM 7000 MODULAR MIXING with panels as illustrated

- COMPLETELY WIRED WITH STAINLESS PANEL
- Up to 20 channels mono, stereo or mixed
- Inputs for all sources inc. mag. cartridge
- Wide range bass and treble controls
- ½W monitor power outlet
- Modern low noise circuitry
- Echo send/return facility
- 5cm matrix—bold panel
- Send for details
- Only one mixing module required
- Feeds most amplifiers
- 20Hz–30kHz  $\pm$  1dB
- Complete—ready to plug in or solder
- Individual monitor buttons

INPUT Mono **£8.50**  
Stereo **£12.00**

MIXER Mono **£8.50**  
Stereo **£12.00**



## IN PCB MODULAR FORM

With same facilities and performance as complete units with panels as illustrated. Up to 20 input modules may be used with one mixer. On glass-fibre PCB's. Soldered or edge connections.

IM.7001/M mono input **£5.50**  
IM.7001/S stereo input **£9.00**  
IM.7002/M mono mixing **£5.50**  
IM.7002/S stereo mixing **£9.00**

## SAXON STROBES

### SUPERSTROBE

- 1 flash/2 sec up to 20 flashes/sec **£24.75**
- Compact black Bondene case
- Ideal for the mobile disco or smaller club

### PRO-STROBE

- External trigger—audio up to 240V
- Use with Soundlite for rainbow strobe effect
- Smart, tough Bondene case 8in x 8in x 5in.
- Giant 80 watt tube Discharge energy up to 6 Joules **£38.50**

## 150 WATT LIQUID WHEEL PROJECTOR

- Complete with wheel
- 150 watt tungsten lamp
- Wide range of extra effects may be attached
- Sturdy construction
- Adjustable feet
- Spare wheels **£4.90**

**£29.20**



**Loudspeakers** 127/50W high grade chassis units: 14000 gauss: presence dome: **£14.50**

**Cabinets** Attractive range of speaker and other cabinets at our showrooms. Enquiries welcomed.

**ACCESSORIES**  
Mics: Headphones: Special Lamps.

PRICES include carr. and packing. VAT must be added to all orders at 8%. C.O.D. 65p extra: S.A.E. all enquiries please.

Send or phone your ACCESS or BARCLAYCARD No. for prompt attention. After 5.0 p.m. leave your message on our answer-phone.

Orders by post—Please make cheques or crossed P.O.'s payable to

## SAXON ENTERTAINMENTS LTD.

327-333 WHITEHORSE ROAD, CROYDON, SURREY CR0 2HS

Telephone: 01-684 6385/0098

Shop Hours 9am–5pm (Lunch 12.30–1.30): Sat. 9.30am–5pm. Prices and specifications subject to alteration without notice. Mail Order desk 10am–4pm Mon–Fri.

## TRADE ENQUIRIES

Send for name and address of your nearest wholesale supplier.

DIGITAL : CLOCKS : KITS : CALCULATORS

"ALPHA": 4 GREEN .5" HIGH DIGITS

Alpha Module (excl. case) . . . . . Kit	Alarm	Std.
Alpha Module (excl. case) . . . . . Built	13 00	10 00
Alpha complete: Perspex Case Kit	14 00	11 00
Alpha Clock: Perspex Case . . . . . Built	15 50	12 50
	21 50	17 50

ALARM

- Tilt Snooze - AM/PM ● Mains failure Ind. ●
- Auto-Control Brightness by Photocell ●

"DELTA": 4 RED .5" HIGH LEDs

Delta Module (excl. case) . . . . . Kit	Alarm	Std.
Delta Module (excl. case) . . . . . Built	11 00	9 00
Delta complete: Perspex Case . . . . . Kit	11 50	9 50
Delta Clock: Perspex Case . . . . . Built	15 00	12 00
Delta complete: Teak Case . . . . . Kit	21 00	17 00
Delta Clock: Teak Case . . . . . Built	15 70	12 70
	21 70	17 70

Perspex Case Colours: Black, White, Red, Green, Blue, Orange  
Built Modules and Clocks: state 12 or 24 hour (Delta 12hr only).  
Complete Clocks: 2 Year Guarantee

"NOVUS" CALCULATORS

650 Mathbox . . . . £5.40 ● 850 Mathbox . . . . £6.75  
4510 Mathematician . . £16.20 ● 6020 Statistician . . £21.60

Module kits  
£9:00

INCLUDING VAT, P. AND P.  
SATISFACTION GUARANTEED

- Modern 2 Part Case
- Drilled P.C.B.
- 4 Digit Display 0.5 inch high
- All components included
- Even Mains lead included
- Full instructions
- Assembly Drawing
- Circuit Diagram

You supply only mains plug and standard tools - Easy!



C.W.O. PULSE ELECTRONICS (PW12), 202 Shefford Road, Clifton, Shefford, Beds. SAE complete range

BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX  
All prices inclusive of V.A.T. at 25% Telephone 6743

OB2	45	6BA6	41	6K70	35	12E1	3-51	35A3	78	DF91	80	PCF86	50	Q8150/15	VP41	88	ACY21	85	BY127	23
OZ4	56	6BC8	90	6K8G	58	12J7GT	70	35C8	85	DF96	85	PCF200	1 00	QV06/20	VR105	59	ACY22	80	BY210	33
1A3	65	6BE6	41	6L1	234	12K5	1-17	35D5	90	DK40	82	PCF201	105	3-50	VU111	80	ACY28	23	BY211	33
1A5GT	59	6BH6	75	6L6GC	88	12K7GT	50	35L6GT	88	DK92	1 15	PCF801	85	7-15	VU120	1 17	AD140	47	BY212	33
1A7GT	60	6BJ6	84	6L7	59	12K8	85	35W4	80	DK96	70	PCF802	50	R19	VU120A	AD140	47	BY213	33	
1B3GT	59	6BK7A	85	6L18	64	12Q7GT	50	35Z3	89	DL96	64	PCF806	80	TH233	1 00	AD161	59	FBY11A	29	
1BGT	50	6B7A	64	6L19	2 00	12R3T	80	3E2AGT	82	DM70	80	PCH200	1 00	TP2620	1 00	W107	75	AF114	33	
1L4	75	6B77	1 20	6LD20	88	12S6T	85	3E2ZGT	80	DM71	1 78	PCL82	45	UAB80	47	W229	1 17	AF115	20	
1N5GT	26	6BR8	1 25	6N7GT	70	12SH7	50	4 2	1 00	DY87/6	41	UBC41	60	UAB80	47	X86	1 46	AF117	25	
1R5	60	6BR7	1 84	6Q7G	50	12SJT	80	43	1 00	DY802	47	UBC81	60	UAB80	47	Z759	5 85	AF121	29	
1R4	39	6BW6	1 00	6Q7GT	60	12SJT	78	50B5	1 00	E80CC	2 57	UBC81	60	UAB80	47	Y86	1 46	AF122	29	
1U4	70	6BW7	85	6Q7(M)	84	12R8T	78	50C5	70	E80F	2 20	UBC81	60	UAB80	47	Y86	1 46	AF123	29	
1U5	88	6BZ6	57	6R7G	70	14H7	84	50CD6G	80	E80C	1 20	UBC81	60	UAB80	47	Y86	1 46	AF124	29	
2D21	60	6C4	47	68A7	55	1487	1 10	1 46	E89CC	70	EF91	50	UBF89	47	Y86	1 46	AF125	29		
2GK5	75	6C5G	59	68C7GT	60	18AQ5	65	50EHS	88	E180F	1 17	UBF89	47	Y86	1 46	AF126	29			
2X2	70	6C6	47	68G7	52	18Q6	7 00	50L6GT	1 00	E182CC	3 00	UBF89	47	Y86	1 46	AF127	29			
3A4	60	6C9	2 00	68H7	55	20D1	80	85A2	75	E1148	62	UBF89	47	Y86	1 46	AF128	29			
3D6	47	6CB6A	47	68J7	54	20P2	88	85A3	75	EAD0	40	UBF89	47	Y86	1 46	AF129	29			
3Q4	98	6CD6G	1 60	68K7GT	52	20L1	1 29	90A3	2 98	EAT6	1 49	UBF89	47	Y86	1 46	AF130	29			
3Q5GT	70	6CG8A	88	68Q7	50	20P1	1 00	90C1	88	EAB0C8	45	UBF89	47	Y86	1 46	AF131	29			
384	47	6CL6	78	6V8G	30	20P3	94	90C6	2 81	EAC91	85	UBF89	47	Y86	1 46	AF132	29			
3V4	82	6CL8A	94	6V8GT	53	20P4	1 17	150B2	1 00	EAF42	88	UBF89	47	Y86	1 46	AF133	29			
4CB6	75	6CM7	88	6X4	47	20P5	1 50	2185G	53	EAF501	80	UBF89	47	Y86	1 46	AF134	29			
5C08	75	6CJ5	88	6X3GT	50	25A8G	70	807	1 17	EB34	35	UBF89	47	Y86	1 46	AF135	29			
5R4GY	94	6CW4	1 17	7B6	88	25L6G	70	5702	1 20	EB91	23	UBF89	47	Y86	1 46	AF136	29			
5U4G	80	6D3	75	7B7	82	25Y6	80	5763	1 78	EB041	88	UBF89	47	Y86	1 46	AF137	29			
5V4G	59	6DE7	88	7H7	88	25Z4G	50	8057	1 00	EB831	45	UBF89	47	Y86	1 46	AF138	29			
5Y3GT	55	6DT6A	88	7Y7	2 00	25Z5	75	6060	1 00	EBF80	40	UBF89	47	Y86	1 46	AF139	29			
5Z3	88	6EW6	88	7Y4	80	25Z6G	80	6067	1 00	EBF83	50	UBF89	47	Y86	1 46	AF140	29			
5Z4	55	8E5	1 17	7Z4	80	28D7	2 00	7193	82	EBF89	40	UBF89	47	Y86	1 46	AF141	29			
5Z4GT	55	8F1	80	8D7	70	30A5	78	9002	59	EBL21	2 84	UBF89	47	Y86	1 46	AF142	29			
630L2	80	6F2G	1 17	10C24	76	30C15	80	9006	50	ECB6	50	UBF89	47	Y86	1 46	AF143	29			
6A8B	1 48	6F13	80	10D7	88	30C17	85	9006	1 17	ECB8	90	UBF89	47	Y86	1 46	AF144	29			
6A07	60	6F14	88	10F1	88	30C18	85	9006	1 17	ECB8	90	UBF89	47	Y86	1 46	AF145	29			
6A05	35	6F16	78	10F9	78	30F5	75	DD	1 00	ECC33	2 00	UBF89	47	Y86	1 46	AF146	29			
6A16	80	6F18	64	10F18	60	30FL2	1 10	AC6P8N	50	ECC35	2 00	UBF89	47	Y86	1 46	AF147	29			
6A15	76	6F23	80	10I.D11	82	30FL3	1 10	AC7/TH1	100	ECC40	1 20	UBF89	47	Y86	1 46	AF148	29			
6A16	47	6F24	1 00	10P13	88	30FL3	84	1 00	ECC81	40	EM85	1 80	UBF89	47	Y86	1 46	AF149	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF150	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF151	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF152	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF153	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF154	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF155	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF156	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF157	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF158	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF159	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF160	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF161	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF162	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF163	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF164	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF165	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF166	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF167	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF168	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF169	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF170	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF171	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF172	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF173	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF174	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF175	29		
6A16	80	6G7	85	12AV6	53	30P19	80	1 35	ECX189	80	EM87	1 10	UBF89	47	Y86	1 46	AF176	29		
6A16	80	6G7	85	12AV6	5															

# 15-120 Watts!

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag. cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

## HY 5

Pre-amplifier

**FEATURES**  
Complete pre-amplifier in single pack  
Multi function equalisation  
Low noise  
Low distortion  
High overload  
Two simply combined for stereo

**APPLICATIONS**  
Hi-Fi  
Mixers  
Disco  
Guitar and Organ  
Public address

**SPECIFICATIONS**  
INPUTS. Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; Input Impedance 47kΩ at 1kHz.  
OUTPUTS. Tape 100mV; Main output 500mV. R.M.S.  
ACTIVE TONE CONTROLS. Treble ±12dB at 10kHz; Bass ± at 100Hz.  
DISTORTION. 0-1% at 1kHz. Signal/Noise Ratio 68dB.  
OVERLOAD. 36dB on Magnetic Pick-up.  
SUPPLY VOLTAGE ± 16-50V.

Price £4.75 + £1.19 VAT, P & P free.

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of: I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

## HY 30

5 Watts into 8Ω

**FEATURES**  
Complete Kit  
Low Distortion  
Low Distortion  
Short, Open and Thermal Protection  
Easy to Build

**APPLICATIONS**  
Updating Audio Equipment  
Guitar Practice Amplifier  
Test Amplifier  
Audio Oscillator

**SPECIFICATIONS**  
OUTPUT POWER. 15W R.M.S. into 8Ω  
DISTORTION. 0-1% at 15W.  
INPUT SENSITIVITY. 500mV.  
FREQUENCY RESPONSE. 10Hz-16kHz-3dB  
SUPPLY VOLTAGE. ±18V.

Price £4.75 + £1.19 VAT, P & P free.

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

## HY 50

25 Watts into 8Ω

**FEATURES**  
Low Distortion  
Integral Heatsink  
Only five connections  
7 Amp output transistors  
No external components

**APPLICATIONS**  
Medium Power Hi-Fi systems  
Low power disco  
Guitar amplifier

**SPECIFICATIONS**  
INPUT SENSITIVITY. 500mV.  
OUTPUT POWER 25W RMS into 8Ω  
LOAD IMPEDANCE. 4-16Ω  
DISTORTION. 0-04% at 25W at 1kHz  
SIGNAL/NOISE RATIO. 75dB.  
FREQUENCY RESPONSE. 10Hz-45kHz -3dB.  
SUPPLY VOLTAGE. ±25V.  
SIZE 105 x 50 x 25mm

Price £6.20 + £1.55 VAT, P & P free.

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

## HY 120

60 Watts into 8Ω

**FEATURES**  
Very low distortion  
Integral heatsink  
Load line protection  
Thermal protection  
Five connections  
No external components

**APPLICATIONS**  
Hi-Fi  
High quality disco  
Public address  
Monitor amplifier  
Guitar and organ

**SPECIFICATIONS**  
INPUT SENSITIVITY. 500mV.  
OUTPUT POWER. 60W RMS into 8Ω.  
LOAD IMPEDANCE. 4-16Ω  
DISTORTION. 0-04% at 60W at 1kHz.  
SIGNAL/NOISE RATIO. 90dB.  
FREQUENCY RESPONSE. 10Hz-45kHz -3dB.  
SUPPLY VOLTAGE. ± 35V  
SIZE 114 x 50 x 85mm.

Price £14.40 + £1.16 VAT, P & P free.

The HY200 now Improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

## HY 200

120 Watts into 8Ω

**FEATURES**  
Thermal shutdown  
Very low distortion  
Load line protection  
Integral heatsink  
No external components

**APPLICATIONS**  
Hi-Fi  
Disco  
Monitor  
Power slave  
Industrial  
Public Address

**SPECIFICATIONS**  
INPUT SENSITIVITY. 500mV. OUTPUT POWER, 120W RMS into 8Ω.  
LOAD IMPEDANCE. 4-16Ω. DISTORTION, 0-05% at 100W at 1kHz.  
SIGNAL/NOISE RATIO, 90dB. FREQUENCY RESPONSE, 10Hz-45kHz -3dB  
SUPPLY VOLTAGE, ± 45V. SIZE 114 x 100 x 85mm.

### POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus £1.19 VAT P/P free  
PSU50 suitable for two HY50's £8.20 plus £1.55 VAT P/P free  
PSU70 suitable for two HY120's £12.50 plus £1.00 VAT P/P free  
PSU90 suitable for one HY200 £11.50 plus £0.92 VAT P/P free

Price £21.20 + £1.70 VAT, P & P free.

TWO YEARS GUARANTEE ON ALL OF OUR PRODUCTS.


**I.L.P. Electronics LTD.,** CROSSLAND HOUSE, NACKINGTON, CANTERBURY, KENT CT4 7AD.  
Tel (0227) 63218.

REG. OFFICENO.: 103 2630



Please supply..... Total Purchase Price.....  
I Enclose, Cheque  Postal Orders  Money Order  Please debit my Access account  Barclaycard account  Account number.....

Name & Address .....

Signature.....

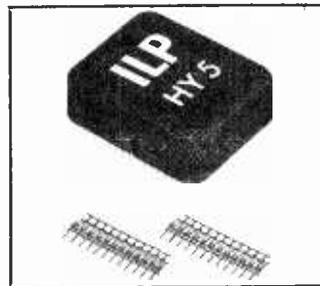

Available  
June 76

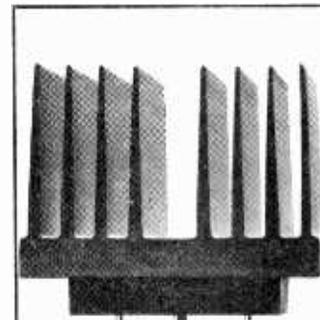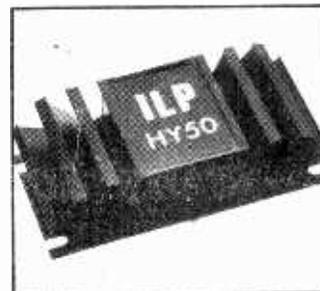



# SEMI-CONDUCTORS

## Linear IC's

Type	Quantities	Type	Quantities	Type	Quantities
	1 25 100+		1 25 100+		1 25 100+
72702	0-46 0-44 0-42	SL701C	0-48 0-42 0-37	76003	£1-39 £1-34 £1-39
72709	0-23 0-21 0-19	SL702C	0-48 0-42 0-37	76023	£1-39 £1-34 £1-39
72709P	0-19 0-18 0-17	TAA293	0-74 0-66 0-56	76550	0-88 0-88 0-83
72710	0-32 0-31 0-28	TAA293	0-93 0-88 0-83	LM380	0-93 0-90 0-88
72741	0-28 0-27 0-26	TAA350E1	£1-57 £1-57	*NE555	0-45 0-43 0-40
72741C	0-28 0-25 0-24	HA703C	0-28 0-24 0-22	*NE556	0-88 0-88 0-83
72741P	0-28 0-27 0-26	HA709C	0-19 0-18 0-17	ZB4800E1	£1-39 £1-34 £1-39
72747	0-79 0-74 0-61	HA711C	0-32 0-31 0-28	ZN414	£1-11
72748P	0-35 0-33 0-31	HA712C	0-32 0-31 0-28		
SL291C	0-46 0-42 0-37	HA723C	0-45 0-43 0-40		

## ★ 74 Series TTL IC's

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS

Type	Quantities	Type	Quantities	Type	Quantities
	1 25 100+		1 25 100+		1 25 100+
7400	0-09 0-09 0-08	7448	0-80 0-78 0-76	74122	0-50 0-48 0-48
7401	0-10 0-09 0-08	7450	0-12 0-11 0-10	74123	0-58 0-56 0-54
7402	0-11 0-10 0-09	7451	0-12 0-11 0-10	74141	0-90 0-88 0-86
7403	0-11 0-10 0-09	7453	0-12 0-11 0-10	74145	0-96 0-94 0-92
7404	0-13 0-12 0-11	7454	0-12 0-11 0-10	74150	£1-30 £1-25 £1-20
7405	0-13 0-12 0-11	7455	0-12 0-11 0-10	74151	0-78 0-74 0-72
7406	0-25 0-24 0-23	7470	0-25 0-24 0-23	74153	0-95 0-93 0-91
7407	0-25 0-24 0-23	7472	0-22 0-21 0-20	74154	£1-50 £1-45 £1-40
7408	0-15 0-14 0-13	7473	0-28 0-24 0-22	74155	0-80 0-78 0-78
7409	0-15 0-14 0-13	7474	0-27 0-23 0-23	74156	0-88 0-78 0-76
7410	0-09 0-09 0-08	7475	0-48 0-46 0-44	74157	0-95 0-93 0-91
7411	0-23 0-22 0-21	7476	0-25 0-24 0-23	74160	£1-00 0-98 0-96
7412	0-26 0-25 0-24	7480	0-50 0-48 0-46	74161	£1-00 0-98 0-96
7413	0-28 0-28 0-25	7481	£1-02 £1-00 0-98	74162	£1-00 0-98 0-96
7416	0-28 0-27 0-26	7482	0-83 0-81 0-79	74163	£1-00 0-98 0-96
7417	0-28 0-27 0-26	7483	0-88 0-96 0-94	74164	£1-25 £1-20 £1-15
7420	0-12 0-11 0-10	7484	0-90 0-88 0-86	74165	£1-25 £1-20 £1-15
7422	0-28 0-27 0-26	7485	£1-25 £1-20 £1-15	74166	£1-48 £1-44 £1-39
7423	0-30 0-28 0-26	7486	0-32 0-30 0-29	74174	£1-00 0-95 0-90
7425	0-30 0-28 0-26	7489	£2-90 £2-80 £2-70	74175	0-95 0-93 0-91
7426	0-30 0-28 0-26	7490	0-37 0-35 0-33	74176	£1-16 £1-11 £1-06
7427	0-30 0-28 0-26	7491	0-60 0-58 0-56	74177	£1-16 £1-11 £1-06
7428	0-42 0-38 0-36	7492	0-43 0-42 0-41	74180	£1-18 £1-11 £1-06
7430	0-12 0-11 0-10	7493	0-43 0-42 0-41	74181	£2-90 £1-90 £1-85
7432	0-30 0-28 0-26	7494	0-43 0-42 0-41	74182	0-90 0-88 0-86
7433	0-38 0-37 0-35	7495	0-70 0-68 0-66	74184	£1-67 £1-62 £1-58
7437	0-30 0-28 0-26	7496	0-68 0-66 0-64	74190	£1-50 £1-45 £1-40
7438	0-30 0-28 0-26	74100	£1-00 0-98 0-96	74191	£1-50 £1-45 £1-40
7440	0-12 0-11 0-10	74104	0-40 0-38 0-36	74192	£1-15 £1-10 £1-05
7441	0-84 0-82 0-80	74105	0-40 0-38 0-36	74193	£1-15 £1-10 £1-05
7442	0-85 0-83 0-81	74107	0-38 0-34 0-32	74194	£1-15 £1-10 £1-05
7443	£1-10 £1-05 £1-00	74110	0-56 0-54 0-52	74195	0-80 0-78 0-76
7444	£1-10 £1-05 £1-00	74111	0-83 0-81 0-78	74196	£1-00 0-98 0-96
7445	0-95 0-80 0-85	74118	0-90 0-88 0-86	74197	£1-00 0-98 0-96
7446	£1-10 £1-05 £1-00	74119	£1-25 £1-20 £1-15	74198	£2-10 £2-00 £1-90
7447	0-87 0-85 0-83	74121	0-26 0-28 0-25	74199	£1-95 £1-90 £1-85

Devices may be mixed to qualify for quantity price. (TTL 74 series only). Data is available for the above series of I.C.'s in booklet form. PRICE 35p.

## ★ DTL 930 Series

Type	Quantities	Type	Quantities	Type	Quantities
	1 25 100+		1 25 100+		1 25 100+
BP930	0-14 0-13 0-13	BP944	0-15 0-14 0-13	BP962	0-14 0-13 0-12
BP932	0-15 0-14 0-13	BP945	0-28 0-26 0-23	BP963	0-42 0-40 0-38
BP933	0-15 0-14 0-13	BP946	0-14 0-13 0-12	BP964	0-42 0-40 0-38
BP935	0-15 0-14 0-13	BP948	0-28 0-26 0-23	BP967	0-42 0-40 0-38
BP936	0-15 0-14 0-13	BP951	0-65 0-60 0-56	BP969	0-42 0-40 0-38

## ★ DIL Sockets

Type	Quantities
	1 25 100+
TSO14 14 pin type	0-31 0-28 0-25
TSO16 16 pin type	0-32 0-29 0-26
TSO24 24 pin type	0-89 0-84 0-82
BPS8 8 pin type (low cost)	0-14 0-12 0-10
BPS14 14 pin type (low cost)	0-15 0-13 0-11
BPS16 16 pin type (low cost)	0-16 0-14 0-12

**VRT**  
PLEASE ADD 8%  
TO ITEMS  
MARKED ★  
REMAINDER  
ADD 25%

## ★ Voltage Regulators

TO-3 Plastic Encapsulation  
 HA.7805/L129 5V  
 (equiv. to MVR5V) £1-25  
 HA.7812/L130 12V  
 (equiv. to MVR12V) £1-25  
 HA.7815/L131 15V  
 (equiv. to MVR15V) £1-25  
 HA.7818/18V  
 (equiv. to MVR18V) £1-25

## Untested LIN Paks

Manufacturers "Fall Outs" which include Functional and part Functional Units. These are classified as "Out-of-spec" from the makers' very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
ULIC709	10 x 709	0-60
ULIC710	7 x 710	0-60
ULIC741	7 x 741	0-60
ULIC747	5 x 747	0-60
ULIC748	7 x 748	0-60

## Mammoth IC Pak

APPROX. 200 PIECES  
 Assorted fall-out integrated circuits, including: Logic 74 series, Linear, Audio and D.T.L. Many coded devices but some unmarked—you to identify.

OUR SPECIAL PRICE £1-20\*



Postage and Packing add 25p unless otherwise shown. Add extra for airmail. Minimum order £1.

## ★ Indicators

3015F Minitron 7 Segment Indicator £1-11

## ★ Untested TTL Paks

Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 x 7400	0-60	UIC70	8 x 7470	0-60
UIC01	12 x 7401	0-60	UIC71	8 x 7472	0-60
UIC02	12 x 7402	0-60	UIC73	8 x 7473	0-60
UIC03	12 x 7403	0-60	UIC74	8 x 7474	0-60
UIC04	12 x 7404	0-60	UIC75	8 x 7475	0-60
UIC05	12 x 7405	0-60	UIC76	8 x 7476	0-60
UIC06	8 x 7406	0-60	UIC80	5 x 7480	0-60
UIC07	8 x 7407	0-60	UIC81	5 x 7481	0-60
UIC10	12 x 7410	0-60	UIC82	5 x 7482	0-60
UIC13	8 x 7413	0-60	UIC83	5 x 7483	0-60
UIC20	12 x 7420	0-60	UIC86	5 x 7486	0-60
UIC30	12 x 7430	0-60	UIC90	5 x 7490	0-60
UIC40	12 x 7440	0-60	UIC91	5 x 7491	0-60
UIC41	5 x 7441	0-60	UIC92	5 x 7492	0-60
UIC42	5 x 7442	0-60	UIC93	5 x 7493	0-60
UIC43	5 x 7443	0-60	UIC94	5 x 7494	0-60
UIC44	5 x 7444	0-60	UIC95	5 x 7495	0-60
UIC45	5 x 7445	0-60	UIC96	5 x 7496	0-60
UIC46	5 x 7446	0-60	UIC100	5 x 74100	0-60
UIC47	5 x 7447	0-60	UIC121	5 x 74121	0-60
UIC48	5 x 7448	0-60	UIC141	5 x 74141	0-60
UIC50	12 x 7450	0-60	UIC151	5 x 74151	0-60
UIC51	12 x 7451	0-60	UIC154	5 x 74154	0-60
UIC53	12 x 7453	0-60	UIC183	5 x 74183	0-60
UIC54	12 x 7454	0-60	UIC199	5 x 74199	0-60
UIC60	12 x 7460	0-60	UIC X1	25 Assorted	£1-50

# BI-PAK

P.O. BOX 6, WARE · HERTS

# Sinclair SCIENTIFIC KIT

B.6.6.2.9-01


ONLY  
**£6.50**  
+50p  
p&p



LASKYS now offer this Sinclair Scientific Calculator for a fraction of the original cost. All parts are supplied - all you need provide is a soldering iron and a pair of cutters, complete step-by-step instructions. Assembly time is about 3 hours. The Sinclair Scientific performs logs, trig and arithmetic at the touch of a button.
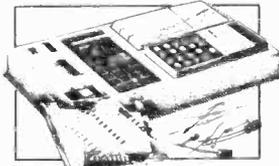
## FEATURES OF THE SINCLAIR SCIENTIFIC

Functions summary Four arithmetic functions: (+, -, ×, ÷). Sin and Arcsin, Cos and Arccos. Tan and Arctan, Automatic squaring, Automatic doubling, Log10 and Antilog10, giving quick access to xy (including square and other roots). Scientific notation. Display shows 5-digit mantissa and 2-digit exponent, both signable. 200 decade range. —9.9999 x 10<sup>-99</sup> to 9.9999 x 10<sup>99</sup>. Post-fixed operators. Post-fixed operators (reverse Polish notation): allow chain calculations of unlimited length. 'Upper and lower case' operation. Basic arithmetic keys each have two extra functions. Pocket-sized. 4 1/2" x 2" x 1/2". Weight: 4oz. Trim-fit plastic carrying case.



LONDON 481 Oxford Street, W1. 01-493 8641  
10 Tottenham Court Road, W1. 01-637 2232  
33 Tottenham Court Road, W1. 01-636 7605  
42 Tottenham Court Road, W1. 01-636 0845  
257 Tottenham Court Road, W1. 01-580 0670  
3 Lisle Street, WC2. 01-437 8204  
118 Edgware Road, W2. 01-723 9789  
133 Edgware Road, W2. 01-723 6211  
311 Edgware Road, W2. 01-262 0387  
345 Edgware Road, W2. 01-723 4453  
382 Edgware Road, W2. 01-723 4194  
109 Fleet Street, EC4. 01-353 5812  
152 Fleet Street, EC4. 01-353 2833  
BIRMINGHAM 116 Corporation St. 236-3503  
BRENT CROSS Unit D19 Brent Cross Shopping Centre, Now open  
BRISTOL 16-18-20 Penn Street. 20421  
CHATHAM The Pentagon Centre. 407104

CROYDON 1045 Whittigt Centre. 681 3027  
COLCHESTER Unit AS Lion Walk Shopping Centre, using FEBRUARY  
DARTFORD The Arndale Centre. 32 3481  
KINGSTON 38/40 Eden Street. 5461271  
LEICESTER 45 Market Place. 537878  
LEWISHAM 29 Riverside, The Centre. 3182297  
NORTHAMPTON 78 Abington St. 35753  
NOTTINGHAM 5-7 Lower Parliament St. 48987  
OXFORD 16 Westgate Church. 722870  
READING 6 Friars Walk, Friar St. 595459  
RICHMOND 32 Hill Street. 9481441  
ROWFORD 86 South Street. 20218  
SOUTHEND 205/206 Church Hill West. 612241  
SLDUGH 65 Queensmere Centre. 7524401  
SWINDON 12 Brunel Plaza.  
TUNBRIDGE WELLS 53/57 Camden Rd. 23242  
WOLVERHAMPTON 30 Wulfrum Way. 23384



To LASKYS CUSTOMER SERVICES DIVISION (Dept. J2)  
Audiotronic House, The Hyde, London NW9 6JJ. Tel: 01-200 1321

Please send me . . . Sinclair Scientific Calculator Kits at £6.50 plus 50p p&p

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_

SIGNATURE \_\_\_\_\_

TOTAL PURCHASE PRICE \_\_\_\_\_ (inc. p/p & Ins.)

Please send me FREE Hi-Fi catalogue price list

I enclose cheque  postal order  money order

I wish to pay by Barclaycard/Access/Diners Club and my number is \_\_\_\_\_

Registered in England No. 347947 at Lower Grosvenor Place, London SW1 0EX

# Marshall's

A. Marshall (London) Ltd Dept: PW  
42 Cricklewood-Broadway London NW2 3ET Tel: 01-452 0167/2  
Telex: 21492

& 85 West Regent St Glasgow G2 2OD Tel: 041-332 4133

& 1 Straits Parade Fishponds Bristol BS16 2LX

Tel: 0272 654201/2

& 27 Rue Danton Issy Les Moulineaux Paris 92 Tel: 644 2356

Catalogue price 25p Trade and export enquiries welcome

Our range covers over 7,000 items. The largest selection in Britain

## Top 200 IC's TTL, CMOS & Linears


CA3020A	£1.80	CD4049	45p	NE555V	70p	SN7442	65p	SN74151	68p
CA3028A	79p	CD4050	45p	NE556	£1.30	SN7446	84p	SN74153	£1.20
CA3035	£1.37	CD4510	£1.25	NE560	£4.48	SN7447	80p	SN74157	76p
CA3046	70p	CD4511	£1.94	NE565	£4.48	SN7448	90p	SN74160	88p
CA3048	£2.11	CD4516	£1.25	SL1414	£2.35	SN7450	16p	SN74161	88p
CA3052	£1.62	CD4518	£1.87	SL610C	£2.35	SN7451	16p	SN74162	88p
CA3089E	£1.96	CD4520	£1.87	SL611C	£2.35	SN7453	16p	SN74163	88p
CA3090C	£4.23	LM301A	48p	SL612C	£2.35	SN7454	16p	SN74164	£1.60
CA3130	88p	LM308	£1.17	SK20C	£3.50	SN7460	16p	SN74165	£1.60
CD4000	18p	LM309K	£1.88	SL21C	£3.50	SN7470	29p	SN74167	£3.30
CD4001	18p	LM381	98p	SL23C	£5.24	SN7472	21p	SN74174	99p
CD4002	18p	LM381	£2.07	SL640C	£4.00	SN7473	31p	SN74175	70p
CD4006	99p	LM702C	75p	SN7400	16p	SN7474	31p	SN74176	£1.14
CD4007	18p	LM709	38p	SN7401	16p	SN7475	45p	SN74180	£1.10
CD4008	82p	TO99	38p	SN7401AN	29p	SN7476	30p	SN74181	£1.95
CD4009	42p	8DIL	45p	SN7402	16p	SN7480	42p	SN74182	£1.86
CD4010	52p	14DIL	38p	SN7403	16p	SN7481	£1.00	SN74191	£1.86
CD4011	18p	LM710	47p	SN7404	19p	SN7482	65p	SN74192	£1.15
CD4012	18p	LM723C	66p	SN7405	19p	SN7483	82p	SN74193	£1.15
CD4013	45p	LM741C	40p	SN7406	36p	SN7484	95p	SN74196	£1.60
CD4014	89p	TO99	40p	SN7407	36p	SN7485	£1.00	SN74197	£1.58
CD4015	89p	8DIL	40p	SN7408	19p	SN7486	29p	SN74198	£1.80
CD4016	45p	14DIL	38p	SN7409	18p	SN7490	58p	SN74199	£1.80
CD4017	88p	LM747	£1.05	SN7410	16p	SN7491	75p	SN76003N	£2.92
CD4018	88p	LM748	SN7411	20p	SN7492	45p	SN76013N	£1.95	
CD4019	52p	8DIL	44p	SN7412	22p	SN7493	45p	SN76023N	£1.60
CD4020	98p	14DIL	41p	SN7413	26p	SN7494	75p	SN76033N	£2.92
CD4021	88p	LM3900	61p	SN7416	28p	SN7495	68p	TAA263	£1.20
CD4022	51p	LM7805	£1.88	SN7417	22p	SN7496	58p	TAA300	£1.84
CD4023	18p	LM7812	£1.99	SN7420	16p	SN74100	£1.10	TAA350A	£1.96
CD4024	72p	LM7815	£1.99	SN7423	23p	SN74107	30p	TAA550	32p
CD4025	19p	LM7824	£1.99	SN7425	23p	SN74118	85p	TAA611C	£2.18
CD4027	43p	MC1303L	£1.50	SN7427	23p	SN74119	£1.75	TAA621	£2.03
CD4028	82p	MC1310P	£2.50	SN7430	15p	SN74121	32p	TAA661B	£1.03
CD4029	51p	MC1330P	90p	SN7432	22p	SN74122	42p	TAA631B	£2.35
CD4030	52p	MC1351P	80p	SN7437	28p	SN74123	28p	TAA651	£1.69
CD4031	98p	MC1455	£4.07	SN7438	28p	SN74141	75p	TBA800	89p
CD4037	88p	MC1468	£4.30	SN7440	16p	SN74145	72p	TBA810	98p
CD4041	70p	MC1469R	£2.75	SN7441AN	68p	SN74150	£1.20	TBA820	80p

London, Glasgow, Paris and now BRISTOL It's our service that makes us grow

## POPULAR SEMICONDUCTORS

2N696	22p	2N3906	19p	AF139	65p	BD139	71p	MPSA56	31p
2N697	16p	2N4037	42p	AF239	65p	BD140	87p	OC28	£1.48
2N698	82p	2N4036	67p	AF240	90p	BF115	29p	OC35	£1.16
2N699	51p	2N4061	79p	AF279	70p	BF154	20p	OC42	50p
2N706	14p	2N4062	15p	AF280	79p	BF154	20p	OC45	32p
2N708	17p	2N4289	34p	AL102	£1.00	BF159	27p	TIP29A	49p
2N916	28p	2N4920	£1.10	BC107	14p	BF180	35p	TIP29C	80p
2N918	32p	2N4921	83p	BC108	14p	BF181	36p	TIP31A	62p
2N1302	18p	2N4923	£1.00	BC109	14p	BF184	30p	TIP32A	74p
2N1309	26p	2N1478	20p	BC147B	20p	BF194	12p	TIP32B	74p
2N1306	31p	2N5294	48p	BC148B	9p	BF195	13p	TIP34A	£1.81
2N1308	47p	2N5296	48p	BC149B	11p	BF196	13p	TIP35A	£2.90
2N1711	27p	2N5457	29p	BC157A	16p	BF197	15p	TIP36A	£3.70
2N102	60p	2N5458	26p	BC158A	16p	BF198	18p	TIP41A	79p
2N2147	78p	2N5459	29p	BC167B	15p	BF244	21p	TIP42A	90p
2N2148	94p	2N6027	45p	BC168B	15p	BF257	47p	TIP2955	98p
2N2218A	47p	3N128	73p	BC169B	15p	BF258	53p	TIP3055	50p
2N2219A	52p	3N140	£1.00	BC182	12p	BF259	53p	TIS43	28p
2N2220	25p	3N141	81p	BC182L	12p	BF561	27p	ZTX300	13p
2N2221	18p	3N200	£2.49	BC183	12p	BF598	25p	ZTX301	13p
2N2222	20p	40361	40p	BC183L	12p	BF399	24p	ZTX500	13p
2N2369	20p	40362	45p	BC184	13p	BF379	24p	ZTX501	13p
2N2646	55p	40406	44p	BC184L	13p	BF399	32p	ZTX502	18p
2N2904	40p	40407	35p	BC212A	16p	BF330	34p	IN914	31p
2N2905	47p	40408	50p	BC212LA	16p	BF364	30p	IN375A	15p
2N2906	33p	40409	52p	BC213LA	15p	BF385	35p	IN4007	10p
2N2907	22p	40410	52p	BC214LB	10p	BF388	30p	IN4148	4p
2N2924	20p	40411	£2.00	BC237B	16p	BF550	30p	IN4044	22p
2N2926	12p	40594	74p	BC238C	15p	BF575	28p	IN4045	30p
2N3053	25p	40595	84p	BC239C	15p	BF552	20p	AA119	8p
2N3054	60p	40636	£1.10	BC257A	16p	BF339	48p	BA102	23p
2N3055	65p	40673	73p	BC258B	16p	ME0402	20p	BA145	18p
2N3391	28p	AC162	20p	BC259B	17p	ME0412	18p	BA154	12p
2N3392	15p	AC127	40p	BC30	34p	ME4102	11p	BA155	12p
2N3393	15p	AC128	35p	BC307B	17p	ME370	65p	BA193B	23p
2N3440	59p	AC151	27p	BC308A	15p	MJ481	£1.20	BB104B	45p
2N3442	£1.40	AC152	49p	BC309C	20p	MJ490	£1.03	BY126	12p
2N3638	15p	AC153	35p	BC327	23p	MJ491	1.45	BY127	15p
2N3702	12p	AC176	41p	BC328	22p	MJ2955	£1.00	BYZ11	51p
2N3703	13p	AC187K	35p	BCY70	17p	MJ340	48p	BYZ12	51p
2N3704	15p	AD188K	40p	BCY71	22p	MJ370	95p	CA47	6p
2N3706	55p	AD189	68p	BCY72	18p	MJ371	75p	OA81	18p
2N3708	14p	AD161	69p	BD121	£1.00	MJ520	60p	OA90	6p
2N3714	£1.38	AD162	69p	BD123	82p	MJ521	70p	OA91	6p
2N3716	£1.80	AF106	40p	BD124	67p	MJ2955	£1.20	OA200	8p
2N3771	£2.20	AF109	40p	BD131	40p	MJ3055	75p	BY164	57p
2N3773	£2.65	AF115	35p	BD132	50p	MJ3113	47p	5T22ac	20p
2N3789	94p	AF116	35p	BD133	41p	MPF102	39p	0A659	£1.00
2N3819	37p	AF117	35p	BD136	22p	MPSA05	25p	TIC44	29p
2N3820	29p	AF118	35p	BD137	24p	MPSA06	31p	CI06D	65p
2N3904	19p	AF124	30p	BD138	26p	MPSA55	21p	ORP12	60p

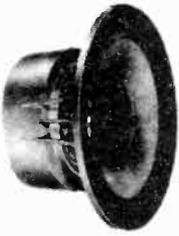Prices correct at April, 1976, but all exclusive of VAT. P.&P. 25p



# WILMSLOW AUDIO

## THE Firm for speakers!

### SPEAKERS

Baker Group 25, 3, 8 or 15 ohms  
 Baker Group 35, 3, 8 or 15 ohms  
 Baker Group 50/12 8 or 15 ohms  
 Baker Group 50/15 8 or 15 ohms  
 Baker Deluxe 12" 8 or 15 ohms  
 Baker Major 3, 8 or 15 ohms  
 Baker Super 8 or 15 ohms  
 Baker Regent 12" 8 or 15 ohms  
 Baker Auditorium 12" 8 or 15 ohms  
 Baker Auditorium 15" 8 or 15 ohms  
 Celestion G12M 8 or 15 ohms  
 Celestion G12H 8 or 15 ohms  
 Celestion G12/50 8 or 15 ohms  
 Celestion G12/50TC 8 or 15 ohms  
 Celestion G15C 8 or 15 ohms  
 Celestion G15C 8 or 15 ohms  
 Celestion HF1300 8 or 15 ohms  
 Celestion HF2000 8 ohms  
 Celestion MH1000 8 or 15 ohms  
 Celestion CO3K  
 Decca London ribbon horn  
 Decca London CO/1000/8 Xover  
 Decca DK30 ribbon horn  
 Decca CO/1/8 Xover (DK30)  
 EMI 14 x 9 Bass 8 ohms 14A770  
 EMI 8 x 5, 10 watt, d/cone, roll surr.  
 EMI 6 1/2" d/cone, roll surr. 8 ohms  
 EMI 5" mid range  
 EMI 8" roll surr. bass  
 EMI 5" mid range  
 Elac 59RM109 (15) 59RM114 (8)  
 Elac 6 1/2" d/cone, roll surr. 8 ohms  
 Elac 10" 10RM239 8 ohms  
 Eagle Crossover 3000Hz 3, 8 or 15 ohm  
 Eagle FR4  
 Eagle FR65  
 Eagle FR8  
 Eagle FR10  
 Eagle HT15  
 Eagle HT21  
 Eagle MHT10  
 Fane F29 multicell. horn  
 Fane Pop 15, 8 or 16 ohm  
 Fane Pop 25T, 8 or 16 ohm  
 Fane Pop 33T, 8 or 16 ohm  
 Fane Pop 50, 8 or 16 ohm  
 Fane Pop 55, 8 or 16 ohm  
 Fane Pop 60, 8 or 16 ohm  
 Fane Pop 70, 8 or 16 ohm  
 Fane Pop 100, 8 or 16 ohm  
 Fane Crescendo 12A, 8 or 16 ohms  
 Fane Crescendo 12BL, 8 or 16 ohms  
 Fane Crescendo 15/100A, 8 or 16 ohms  
 Fane Crescendo 15/125, 8 or 16 ohms  
 Fane Crescendo 18, 8 or 16 ohms  
 Fane 910 Mk II horn  
 Fane 920 Mk II horn  
 Fane HPX1 crossover 200 watt  
 Fane 13 x 8, 15 watt dual cone  
 Fane 801T 8" d/c, roll surr.  
 Goodmans Axlent 100  
 Goodmans Audiom 100 15 ohm  
 Goodmans Audiom 200 8 ohm  
 Goodmans Axlom 402 8 or 15 ohm  
 Goodmans Twinaxiom 8, 8 or 15 ohm  
 Goodmans Twinaxiom 10, 8 or 15 ohm  
 Goodmans 8P 8 or 15 ohm  
 Goodmans 10P 8 or 15 ohm  
 Goodmans 12P 8 or 15 ohm  
 Goodmans 12PS 8 or 15 ohm  
 Goodmans 12PD 8 or 15 ohm

### SPEAKERS

£8-64  
 £10-25  
 £14-00  
 £18-62  
 £13-75  
 £11-87  
 £18-12  
 £10-00  
 £18-25  
 £21-56  
 £12-95  
 £15-95  
 £16-50  
 £18-00  
 £26-95  
 £34-50  
 £7-75  
 £8-50  
 £13-50  
 £4-95  
 £32-00  
 £7-50  
 £19-06  
 £3-00  
 £13-25  
 £3-95  
 £4-37  
 £6-37  
 £3-30  
 £3-75  
 £4-25  
 £3-95  
 £1-75  
 £8-12  
 £8-62  
 £12-31  
 £15-62  
 £4-40  
 £6-81  
 £4-44  
 £9-06  
 £5-25  
 £7-50  
 £8-75  
 £12-50  
 £15-50  
 £17-25  
 £18-75  
 £27-95  
 £37-75  
 £36-50  
 £49-95  
 £57-95  
 £87-95  
 £14-95  
 £33-95  
 £2-50  
 £5-50  
 £9-95  
 £8-44  
 £13-90  
 £14-95  
 £22-00  
 £18-55  
 £10-95  
 £5-95  
 £6-25  
 £14-95  
 £16-50  
 £16-95

Goodmans 12AX 8 or 15 ohm  
 Goodmans 15AX 8 or 15 ohm  
 Goodmans 15P 8 or 15 ohm  
 Goodmans 18P 8 or 15 ohm  
 Goodmans Hifax 750P  
 Goodmans 5" midrange 8 ohm  
 Gauss 12" 200 watt  
 Gauss 15" 200 watt  
 Gauss 18" 200 watt  
 Jordan Watts Module 4, 8 or 15 ohm  
 Kef T15  
 Kef B110  
 Kef B200  
 Kef B139  
 Kef DNB  
 Kef DN12  
 Kef DN13 SP1015 or SP1017  
 Lowther PM6  
 Lowther PM6 Mk 1  
 Lowther PM7  
 Peerless K01DDT 4 or 8 ohms  
 Peerless DT10HFC 8 ohms  
 Peerless K040MRF 8 ohms  
 Peerless MT225HFC 8 ohms  
 Richard Allan CA12 12" bass  
 Richard Allan HP8B  
 Richard Allan LP8B  
 Richard Allan DT20  
 Richard Allan CN8280  
 Richard Allan CN820  
 Richard Allan Super disco 60W 12"  
 Richard Allen CG15 15" bass  
 Richard Allen Super Disco 10" 50 watt  
 Richard Allen Super Disco B" 50 watt  
 Radford BD25  
 Radford MD9  
 Radford MD6 dome mid range  
 Radford TD 3  
 Radford Crossover network  
 BD25 Mk II  
 STC 4001G  
 Tannoy 10" HPD  
 Tannoy 12" HPD  
 Tannoy 15" HPD  
 Wharfedale Super 10 RS/DD 8 ohms  
 Castle 8 RS/DD

### SPEAKER KITS

each £36-00  
 each £14-05  
 each £22-50  
 each £27-95  
 each £32-50  
 pair £42-00  
 pair £96-00  
 pair £73-00  
 each £11-50  
 pair £23-12  
 pair £53-00  
 pair £86-00

Peerless 1120  
 Richard Allan Twin assembly  
 Richard Allan Triple 8  
 Richard Allan Triple 12  
 Richard Allan Super Triple  
 Richard Allan RA8 Kit  
 Richard Allan RA82 Kit  
 Richard Allan RA82L Kit  
 Fane Mode One MK2  
 Wharfedale Linton II kit  
 Wharfedale Glendale 3XP kit  
 Wharfedale Dovedale III kit

### HI-FI

## ON DEMONSTRATION in our showrooms

Akai, Armstrong, Bowers & Wilkins, Castle, Celestion, Dual, Goodmans, Kef, Leak, Pioneer, Radford, Richard Allan, Rotel, Tandberg, Trio, Videotone Wharfedale etc.—Ask for our HiFi price list!

Complete RADFORD range in stock, Amplifiers, Preamps, power amps, low distortion oscillator, distortion measuring set etc.

All items guaranteed new and perfect. Prompt despatch.

PRICES INCLUDE V.A.T. & ARE CORRECT AT 26.2.76

Carriage: 50p per speaker. (12" and over 75p each)  
 Tweeters, crossovers 30p each  
 Kits 80p each (£1-60 pair)

Send stamp for free booklet "Choosing a speaker".

COMPLETE KITS IN STOCK FOR RADFORD STUDIO 90, MONITOR 180, STUDIO 270, STUDIO 360, HIFI ANSWERS MONITOR, HIFI NEWS NO-COMPROMISE, WIRELESS WORLD TRANSMISSION LINE, PRACTICAL HIFI AND AUDIO (GILES) MONITOR ETC.

Construction leaflets for Radford, Kef, Jordan Watts, Tannoy etc. free on request.

P.A. Amplifiers, microphones etc. by Linear, Shure, Eagle, Beyer, AKG etc.

FREE with orders over £10—"HiFi Loudspeakers Enclosures" Book

# WILMSLOW AUDIO


Dept. PW

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire P.A., HiFi etc: 10 Swan St. Wilmslow. HiFi, Radio etc: Swift of Wilmslow, 5 Swan St. Wilmslow. Telephone Wilmslow 29599 (speakers) 28213 (HiFi etc)

# RTVC
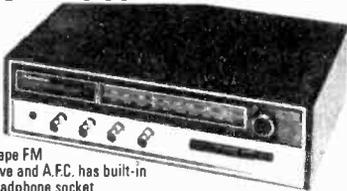
## ELIZABETHAN STEREO TUNER AMPLIFIER

This compact Tuner Amplifier gives you full medium wave and V.H.F. coverage and FM stereo. With inputs for your turntable and tape recorder. It has rotary tuning, Volume, Balance, Bass and Treble controls and push button selection switches for Phono/tape FM Stereo, FM mono, Medium wave and A.F.C. has built-in stereo beacon and switched headphone socket.



**Technical Specifications** 15 transistors, 11 diodes, integrated circuit. Power output 8 watts. Size of tuner amplifier: 4 x 10 x 15 1/2 approx. Finished in selected rosewood veneer with brushed aluminium front panel and matching controls. Output into 15 ohms speakers only. **£29.00** + p&p £1.50

## \*STEREO 21

INCORPORATING A GARRARD DECK  
Garrard 3 speed Deck automatic, manual facilities together with stereo cartridge and cueing device.



Stereo 21, easy to assemble audio system kit. No soldering required. The unit is finished in Sim Teak, and the acrylic top presents an unusually interesting variation on the modern deck plinth. Includes - 3 speed deck, automatic manual facilities together with stereo cartridge and cueing device. Two speakers with cabinets. Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions. Specifications - For the technically minded. Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel. Output impedance 8-15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs - radio, tape, etc., and outputs for taping discs. Overall Dimensions. Speakers approx 12" x 9" x 5". Complete deck and cover in closed position approx. 15 1/2 x 12 x 6. Extras if required. Optional Diamond Stylus £1.60. Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance £5.80.

COMPLETE ONLY  
**£23.20** + p&p £4.00

## BSR DECKS WITH PLINTHS AT FANTASTIC REDUCTIONS



**MP 60 Type (illustrated)** £16.00  
Less Cartridge p&p £2.00  
**C141 (not illustrated)** £12.00  
Auto. with Cue p&p £1.50  
Fitted Stereo Cartridge  
All plinths finished in matching Teak veneer.

## EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3" tweeter and matching crossover. Easily put together with just a few basic tools. Specification (each speaker): Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20 x 11 x 9 1/2 approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair.



**£22.00** pair complete  
+ £5.20 p&p

Complete with crossover Components and circuit diagram.

## THE 'COMPACT' EASY BUILD SPEAKER KIT

A compact bookshelf speaker system giving a high electro acoustic efficiency for the low powered amplifier. The professional finish can be obtained with the minimum of tools, the infinite baffle type enclosures come ready mitred and professionally finished, and fix together with masking tape till glue dries. The cabinet measures 12" x 9" x 5" deep approx finished in simulated teak, incorporating a quality 7" x 4" elliptical speaker, power handling 4 watts, flux density 30,000 maxwells, impedance 8-15 ohms nominal, voice coil dia 1/2" magnet size 2 1/2" approx.



**£6.00** + p&p £1.70  
PAIR INCLUSIVE

## EMI 350 KIT

**£7.25** + £1.20 p & p.

Complete with crossover Components and circuit diagram

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.)

## VISCOUNT IV STEREO AMP

NOW AVAILABLE IN KIT FORM! **30x30**  
WATTS RMS

**£27.50**  
+ p&p £1.50

### COMPLETE 20x20 SYSTEMS

#### SYSTEM 1A £69.00

The new 20 + 20 watt Stereo Amplifier incorporating the latest silicon transistor solid state circuitry, the RT-VC VISCOUNT IV gives you a powerful 20 watts RMS per channel into 8 ohms. Superb teak-finished cabinet, with anodised fascia to harmonise with any decor. Polished trim and knobs. The VISCOUNT IV has a comprehensive range of controls - volume, bass, treble, balance mono/stereo, mode selector, and scratch filter.

Front panel socket for stereo headphones. And a host of sockets at the rear - for left and right speakers, tape recorder, auxiliary, tuner, disc and microphone.

**SPECIFICATION:** 20 watts RMS per channel 40 watts peak. Suitable 8-15 ohms speakers. Total distortion at 10 watts better than 0.2%. Six switched inputs: 1. Magnetic PU. - 3 millivolts at 47 K ohms (R.I.A.A.); 2. Crystal/ceramic PU. - 50 millivolts at 50 K ohms (R.I.A.A.); 3, 4, 6. Tape Tuner/Aux. - 140 millivolts at 50 K ohms (flat frequency response); 5. Microphone - 3 millivolts at 50 K ohms (flat frequency response).

**CONTROLS:** Push button ON/OFF, stereo/mono, scratch filter. 6 position rotary selector. Individual rotary controls for treble, bass, balance and volume. Headphone socket, tape out socket. Aux. mains output. Frequency response: 25 Hz to 25 kHz at full rated output. Signal to noise ratio: better than -50 dB on all inputs. Tone control range: Bass ±15 dB at 50 Hz. Treble ±12 dB at 10 KHz. Power requirements: 250V A.C. mains at 80 watts. Approx size: 15 1/2 x 3 x 10. MP60 type deck with magnetic cartridge, de luxe plinth and cover. Two Duo Type 11a matched speakers - Enclosure size approx. 19 1/2 x 10 1/2 x 7 1/2 in in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling, 30 watts peak.

#### SYSTEM 2 £85.00

Viscount IV amplifier (As System 1a) MP60 type deck (As System 1a)

Two Duo Type 11a matched speakers - Enclosure size approx. 27" x 13" x 11 1/2". Finished in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts RMS, 8 ohms frequency range - 20 Hz to 18,000 Hz. Complete System with these speakers **£85.00** + £7.60 p & p.

**PRICES: SYSTEM 1a**  
Viscount IV R103 amplifier £27.50 + £1.90 p & p.  
2 Duo Type 11a speakers £30.00 + £6.50 p & p.  
MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 + £3.30 p & p.  
Total if purchased separately: £79.50  
Available complete for only: **£69.00** + £6.50 p & p.

**PRICES: SYSTEM 2**  
Viscount IV R103 amplifier £27.50 + £1.90 p & p.  
2 Duo Type 11a speakers £46.00 + £7.50 p & p.  
MP60 type deck with Mag. cartridge de luxe plinth and cover £22.00 + £3.30 p & p.  
Total if purchased separately: £95.50  
Available complete for only **£85.00** + £7.60 p & p.



**20x20 SYSTEM**

Complete System with these speakers **£69.00** + £6.50 p&p.

Scotland and the Orkneys P & P Surcharge  
System 1a £1.75 System 2 £3.50

Note: 30x30 kit available only as a separate item.

## PUSH BUTTON CAR RADIO KIT - THE TOURIST TT\*



**NO SOLDERING REQUIRED**

**NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO** £9.50 +£1.05 p & p.  
Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.  
**TECHNICAL SPECIFICATION:** (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide 2" high and 4 1/2" deep approx.

Speaker including baffle and fixing strip £2.00 +45p p & p. Car Aerial Recommended - fully retractable £1.60+40p p & p.  
The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £8.20+£1.05 p & p.**

## SPECIAL OFFER

The Tourist I Kit, same specification as Tourist TT complete with speakers, fixing kit and fully retractable aerial **£10.50** + p & p £1.50

## STEREO CASSETTE TAPE DECK KIT\*

Kit comprises of ready built cassette tape transport mechanism. Featuring pause control, solenoid assisted auto-stop, 3 digit tape counter, belt-driven balanced fly wheel, DC motor with electronic speed control, ready built and mounted record/replay PC board, and two VU meters, power supply, PC board, mains transformer. Input and output sockets and two level controls. Specification power source 240 AC 50Hz. Output more than 0.5v input mike -65dB 10KΩ DIN -47dB 100KΩ Track system 2 channel stereo record play-back Tape speed, 4.8CM/SEC. Frequency response 50-12,000Hz signal to noise ratio -42dB Recording system AC Bias Erasing system AC erase. Bias frequency 57KHz. Size of mechanism 8" x 5" x 3 1/2" approx. unit easy to mount into your cabinet 3" required to clear base of mechanism approx.




This is an advanced kit not suitable for those without electrical knowledge and those unable to solder.

**£32.50**

+ p & p £1.50 or send SAE for complete details

**NEW!**

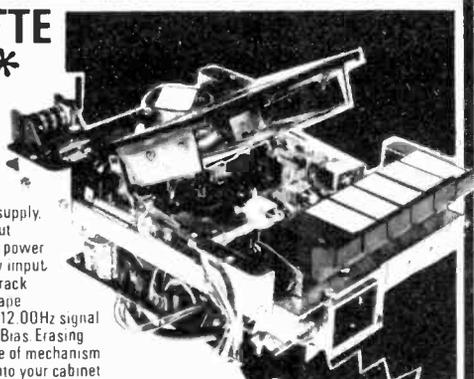

## \*DISCO AMPLIFIER



Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Output 20 watts RMS into 8 ohms (suitable for 15 ohms).  
Inputs \*4 electrically mixed inputs. \*3 individual mixing controls. \*Separate bass and treble controls common to all 4 inputs. \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State circuitry. \*Attractive styling.  
**INPUT SENSITIVITIES** - Input - 1), Crystal mic, guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity.) - Inputs - 2), 3), 4), Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2" **£20.00** +£1.35 p & p.

## 8 TRACK HOME CARTRIDGE PLAYER



Yours for only **£14.00** +£1.70 p & p.

Elegant self selector push button player for use with your stereo system. Compatible with Viscount IV system. Unisound module and the Stereo 21. Technical specification Mains input, 240V, Output sensitivity 125mV.

## SPECIAL OFFER

As above but complete with build yourself Unisound Amplifier Kit (see opposite panel) + 2 'Compact' easy to build speaker kits (see opposite page) **£25.00** + p & p £2.00

## BUILD YOUR OWN STEREO AMPLIFIER\*




For the man who wants to design his own stereo - here's your chance to start, with Unisound - pre-amp, power amplifier and control panel. No soldering - just simply screw together. 4 watts per channel into 8 ohms. Inputs - 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

Also available with 2 speakers (7"x4") **£10** + £1.75 p & p. **£8.95** £1.05 p & p.  
Also available with the 'Compact' (see opposite page) easy build speaker kit **£13.50** + £2 p & p.

**INCORPORATES:** Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP6D type single play professional series decks, fitted with crystal cartridges.

## PORTABLE DISCO CONSOLE\*

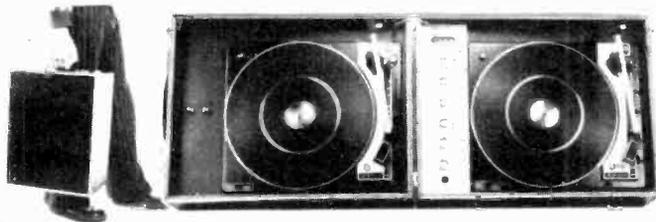

### TECHNICAL SPECIFICATION:

Pre-amp Output - 200mV  
Auxiliary inputs - 200mV and 750mV into 1 meg. Mic input - 6mV into 100K 240 volt operation.  
Turntables capacity - 7", 10" or 12" records. Rumble, wow and flutter Rumble Better than -35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kalee meter).  
Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

### Console size -

Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (app.)  
Unit Open - 35 1/2" x 13 1/2" x 4 1/2" (app.)  
This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.  
The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel.

Yours for only **£49.00** +£6.50 p & p.

All prices include VAT at current rates



**DO NOT SEND CARD**

Just write your order giving your credit card number

Mail orders to Acton. Terms C.W.D. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Leaflets available for all items listed thus \* Send stamped addressed envelope. All items subject to availability. Prices correct at 1st Mar. 1976 and subject to change without notice.

Minimum order on ACCESS/BARCLAYCARD - £11.

# R T V C

21C HIGH STREET, ACTON, LONDON W3 6NG  
323 EDGWARE ROAD, LONDON W2

Personal Shoppers EDGWARE RD: 9 a.m.-5.30p.m. Half day Thurs  
ACTON: 9.30a.m.-5p.m. Closed all day Wed.

# LYNX ELECTRONICS (LONDON) LTD

<b>Transistors</b>	BC183 10p*	BF257 30p	C106F 35p	2N896 14p
AC126 15p	BC183L 10p*	BF258 35p	CRS1-05 25p	2N897 12p
AC127 16p	BC184 11p*	BF337 32p	CRS1-10 25p	2N706 10p
AC128 13p	BC184L 11p*	BFW60 17p*	CRS1-20 35p	2N929 14p
AC128K 25p	BC207B 12p*	BFX29 26p	CRS1-40 40p	2N930 14p
AC141 18p	BC212 11p*	BFX30 30p	CRS1-60 85p	2N1131 15p
AC141K 28p	BC212L 11p*	BFX84 23p	CRS3-05 34p	2N1132 18p
AC142 18p	BC213 12p*	BFX85 25p	CRS3-10 45p	2N1304 20p
AC142K 28p	BC213L 12p*	BFX88 20p	CRS3-20 50p	2N1305 20p
AC176 16p	BC214 14p*	BFY50 20p	CRS3-40 60p	2N1711 18p
AC176K 25p	BC214L 14p*	BFY51 18p	CRS3-60 85p	2N2102 44p
AC187 18p	BC237 16p*	BFY52 19p	MJ480 80p	2N2369 14p
AC187K 25p	BC238 16p*	BFY64 35p	MJ481 £1.05	2N2369A 14p
AC188 18p	BC300 34p	BFY90 65p	MJ490 90p	2N2484 16p
AC188K 25p	BC301 32p	BR100 20p	MJ5340 40p*	2N2905 18p
AD140 50p	BC323 60p	BRY39 40p	MJ5371 60p	2N2905A 22p
AD142 50p	BC327 18p*	BSX19 16p	MJ5220 45p	2N2926R 10p*
AD143 46p	BC328 16p*	BSX20 18p	MJ5251 55p	2N2928O 9p*
AD149 45p	BC337 17p*	BSX21 20p	OA5 50p*	2N2929Y 9p*
AD161 35p	BC338 17p*	BSY95A 12p	OA90 8p	2N2929G 10p*
AD162 35p	BCY70 12p	BT106 £1.00	OA91 8p	2N3053 15p
AL102 95p	BCY71 18p	BT107 £1.00	OC41 15p	2N3054 40p
AL103 95p	BCY72 12p	BT108 £1.00	OC42 15p	2N3055 50p
AF111 20p	BD115 55p	BT109 £1.00	OC44 12p	2N3440 56p
AF115 20p	BD131 38p	BT116 £1.00	OC45 10p	2N3442 £1.20
AF116 20p	BD132 40p	BU105/5	OC70 10p	2N3570 80p
AF117 20p	BD135 38p	BU105/5	OC71 10p	2N3702 10p*
AF118 50p	BD136 39p	02 £1.90*	OC72 22p	2N3703 10p*
AF139 35p	BD137 40p	BY126 £1.80*	OC84 14p	2N3704 10p*
AF231 37p	BD138 40p	BY206 15p*	OC84 14p	2N3705 10p*
BC107 14p	BD139 8p	BY207 20p*	SC40A 73p	2N3705 10p*
BC107B 16p	BD181 86p	BYX36-300	SC40B 81p	2N3706 10p*
BC108 13p	BD182 92p	BYX36-600	SC40D 98p	2N3707 10p*
BC109 14p	BD183 97p	BYX36-600	SC40F 65p	2N3714 £1.05
BC109C 16p	BD184 £1.20	BYX36-900	SC41A 65p	2N3715 £1.15
BC117 19p*	BD230 90p	BYX36-900	SC41B 70p	2N3716 £1.25
BC125 18p*	BD231 90p	BYX36-1200	SC41D 65p	2N3771 £1.60
BC126 20p*	BD232 90p	BYX36-1200	SC41F 60p	2N3772 £1.60
BC141 28p	BD233 90p	BYX38-	ST2 20p	2N3773 £2.10
BC142 23p	BD237 90p	BYX38-	TIP29A 44p*	2N3819 28p*
BC143 23p	BD238 90p	BYX38-	TIP30A 52p*	2N3904 16p*
BC144 30p	BD239 90p	BYX38-	TIP31A 54p	2N3905 16p*
BC147 9p*	BDY20 80p	600 55p	TIP32A 64p	2N4124 14p
BC148 9p*	BDY38 60p	BYX38-	TIP34 £1.05	2N4290 12p
BC149 9p*	BDY60 60p	900 60p	TIP41A 68p	2N4348 £1.20
BC152 25p*	BDY61 65p	BYX38-	TIP42A 72p	2N4870 35p*
BC153 18p*	BF182 55p	1200 85p	IN2069 14p	2N4871 35p*
BC157 9p*	BF178 25p	BZY81 series	IN2070 18p*	2N4819 70p*
BC158 9p*	BF179 30p	zenera 20p	IN4001 4p*	2N4920 50p*
BC159 9p*	BF194 10p*	BZY83 or	IN4002 5p*	2N4922 58p*
BC160 32p	BF195 10p*	BZY88 series	IN4003 6p*	2N4923 64p*
BC161 38p	BF196 12p*	zeners 11p*	IN4004 7p	2N5080 20p*
BC168B 9p*	BF197 12p*	C106A 40p	IN4005 8p*	2N5081 25p*
BC182 11p*	BF224 17p*	C106B 45p	IN4006 8p*	2N5082 27p*
BC182L 11p*	BF244 17p*	C106D 50p	IN4007 10p*	2N5084 30p*

## NATIONAL CLOCK CHIPS

MMS314 £3.75, MMS316 £5.25, MMS317 £5.25

## DIGITAL DISPLAYS & LED'S

DL704	99p	DL747	1.75	2 RED LED ONLY	13p
DL707	99p	DL750	1.75	GREEN CLEAR AMBER	
				YELLOW	15p

## THYRISTORS

	8A	1A	3A	6A	8A	10A	15A
	(TO92)	(TO5)	(C106 type)	(TO220)	(TO220)	(TO220)	(TO220)
50	20	25	35	41	42	47	6
100	25	35	40	47	48	54	70
200	27	35	45	58	60	68	90
400	30	40	50	67	68	88	110
600		65	70	1.09	1.19	1.26	1.50

## TRIACS (PLASTIC TO-220 PKG, ISOLATED TAB)

	4A	(a)	(b)	6.5A	(a)	(b)	8.5A	(a)	(b)	10A	(a)	(b)
100 V	0.60	0.60	0.70	0.70	0.78	0.78	0.83	0.83	1.01	1.01	1.01	1.01
200 V	0.64	0.64	0.75	0.75	0.87	0.87	0.87	0.87	1.17	1.17	1.17	1.17
400 V	0.77	0.77	0.80	0.83	0.97	0.97	1.01	1.13	1.19	1.19	1.19	1.19
600 V	0.96	0.96	0.87	1.01	1.21	1.26	1.42	1.50	2.11	2.11	2.11	2.11

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

## 74 TTL mixed prices

	1-24	25-99	100+		1-24	25-99	100+		1-24	25-99	100+
7400	14p	12p	10p	7445	85p	71p	57p	7492	57p	46p	36p
7401	14p	12p	10p	7447	81p	75p	65p	7493	45p	40p	32p
7402	14p	12p	10p	7448	75p	62p	50p	7495	67p	55p	45p
7403	15p	12p	10p	7447A	95p	83p	67p	74100	£1.08	88p	72p
7404	16p	13p	11p	7470	30p	25p	20p	74107	35p	28p	22p
7408	16p	13p	11p	7472	25p	21p	17p	74121	34p	28p	23p
7409	16p	13p	11p	7473	30p	25p	20p	74122	47p	39p	31p
7410	16p	13p	11p	7474	32p	26p	21p	74141	78p	63p	53p
7413	20p	24p	20p	7475	47p	39p	31p	74145	68p	56p	48p
7417	27p	22p	20p	7476	32p	26p	21p	74154	£1.62	£1.48	86p
7420	16p	13p	11p	7482	75p	62p	50p	74174	£1.00	83p	67p
7427	27p	22p	18p	7485	£1.30	£1.09	87p	74180	£1.06	88p	71p
7430	16p	13p	11p	7486	32p	26p	21p	74181	£3.20	£2.50	£1.90
7432	27p	22p	18p	7489	£2.92	£2.80	£2.10	74192	£1.35	£1.14	90p
7437	27p	22p	18p	7490	49p	40p	32p	74193	£1.35	£1.14	90p
7441	75p	62p	50p	7491	65p	55p	45p	74196	£1.64	£1.34	99p
7442	65p	55p	43p								

## LINEAR IC'S

301A 8 pin DIL	35*	3800 14 pin DIL	70*	585 14 pin DIL	£2.00*
307	55*	709 8/14 pin DIL	35*	586 8 pin DIL	£1.50*
309K	99	741 8/14 pin DIL	28*	587 8 pin DIL	£2.00*
380 14 pin DIL	90*	748 8 pin DIL	36*	AC3046 14 pin DIL	50*
381 14 pin DIL	1.60*	555 8 pin DIL	45		

Matching charge 20p per pair. P & P 20p—Overseas 80p.

SEND SAE FOR COMPLETE LIST.

## HIGHAM MEAD, CHESHAM, BUCKS. Tel. (02405) 75154

VAT—Please add 8% except items marked \* which are 25%

# ELECTROVALUE

## the good components service

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue.

## CATALOGUE 8—ISSUE 2

With the first printing sold out, Issue No. 2 is up-dated on prices, etc. 144 pages. New Items. Opto-electronics. Diagrams of components, applications, I.C. circuits, etc. Post free 40p, including voucher for 40p for spending on order over £5 list value.

## DISCOUNTS

On all C.W.O. mail orders, except for some items marked NETT, 5% on orders list value 10% on orders list value 50 £10 or more 10% on £15 or more

## FREE POST & PACKING

On all C.W.O. mail orders in U.K. over £2 list value. If under, add 15p handling charge.

## PRICE STABILIZATION POLICY

Prices are held and then reviewed over minimum periods of 3 months—Next price review due April 1st 1976.

## QUALITY GUARANTEE

On everything in our Catalogue—No manufacturer's rejects, seconds or sub-standard merchandise.

## ELECTROVALUE LTD

All communications to Dept. 5/1, 28, ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 9HB. Telephone Egham 3903, Telex 284475. Shop hours 9-5.30 daily, 9-1 pm Sat.

NORTHERN BRANCH: 600, Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours Daily 9-5.30 pm; 9-1 pm Sat.




**Random Flasher Unit**  
Wired ready for use. Complete with three 100 watt coloured lamps that flash independently at random.  
**£18.95**



**TWIN BANK 6 LIGHT UNIT**  
(less lamps) LENGTH 14 1/2 inches  
BC Fitting **£9.55** EACH  
ES Fitting **£10.35** EACH



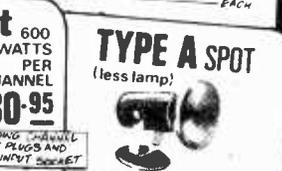**Sound to Light MASTER UNIT**  
600 WATTS PER CHANNEL  
**£30.95**  
INCLUDING 2 WATT OUTPUT PLUGS AND MAINS INPUT SOCKET



**TYPE A SPOT**  
(less lamp)  
BC Fitting **£1.95** EACH | ES Fitting **£2.12** EACH



**TYPE B 3 BANK UNIT**  
(Less Lamps)  
BC Fitting **£6.90** EACH | ES Fitting **£7.26** EACH



**TWIN BANK 12 LIGHT UNIT**  
Length 31 1/4  
(less lamps)  
BC Fitting **£15.60** EACH | ES Fitting **£17.00** EACH



**100 WATT SPOT LAMPS**  
RED, YELLOW, GREEN BLUE CLEAR  
3 lamps **£3.54**  
B.C. or E.S. Fitting

ALL PRICES INCLUDE V.A.T. AND POST & PACKING (These prices apply to the United Kingdom only.)  
Some prices for illustrated list & prices list.

**ALBEN ENGINEERING CO. LTD.**  
DEPT. P/W THE CRESCENT, WORSTHORNE, BURNLEY, LANCS. Tel. Burnley 20940





## "I MADE IT MYSELF"

*'Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.'*

# Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio . . . a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**No soldering—yet you learn faster than you ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course. **AT NO EXTRA CHARGE!** And this is a course anyone can afford. (You can even pay for it by easy instalments).

**So fast, so easy, this personalised course will teach you even if you don't know a thing today!**

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become somebody who makes things, not just another of the millions, who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire highpowered technical qualifications, because our famous courses go right up to City & Guilds levels.

**Send now for FREE 44 page book—see how easy it is—read what others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

print-a-kit now bring you

## PAK STRIP

(Pat. applied for)

The easiest way yet to mount D.I.L. IC's etc.

**PAK STRIP** is a thin, flexible fibre glass board with a self-adhesive backing.


You can bend it, drill it, cut it with scissors prick holes in it, solder to it, stick it to anything.

It is so versatile its many applications are limited only by the ingenuity of the user.

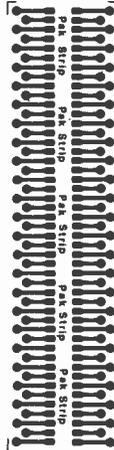
### Star points of PAK STRIP

- ★ Will cut with scissors
- ★ Has a self-adhesive backing
- ★ Can be used to surface solder D.I.L. IC's, light displays, etc.
- ★ Miniature and standard potentiometers can be mounted on the take-off leads
- ★ Type B can be used for grouping cables, mounting diodes, resistors etc.
- ★ No need to drill holes for nuts and bolts . . . just stick down . . .

REMEMBER! A surface soldered D.I.L. IC will remove easily.



Type A  
1 pitch for  
D.I.L. IC's etc.

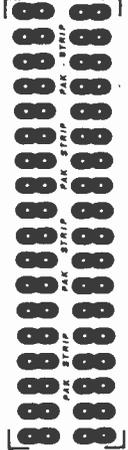

Type B  
General purpose  
group board

One Type A PAK STRIP will mount 11 8-pin D.I.L. IC's

Sample PAK STRIP . . . . . 35p plus a SAE VAT incl.

8" x 5" board with 6 strips . . . . . £1.00 VAT & Postage inc.

8" x 10" board with 12 strips . . . . . £3.00 VAT & Postage inc.

Please state Type A or B when ordering: S.A.E. for details.

TERMS: Cash with Order, or pro-forma invoice: Trade enquiries for quantity prices invited. Overseas add 25p per sheet.

*\*print-a-kit*  
REGISTERED

Electronic Supplies, 488 Sharrowvale Road, Sheffield S11 8ZP ENGLAND

## SOUTHERN VALVE COMPANY

P.O. Box 144, BARNET, Herts.

Telephone: 01-440 8641. Mail order only. Most leading makes.

### ALL NEW & BOXED VALVES

AZ31	75p	E240/1	59p	PD500	22-50	UL84	48p
DY86/7	40p	E280	38p	PFL200	81p	UY85	37p
DY802	46p	E281	33p	PL36	67p	UZ5	80p
EB91	21p	GY501	90p	FL81	55p	UZ6	75p
ECC81	35p	GE20	45p	FL81A	60p	UI01	80p
ECC82	37p	PC86	70p	PL82	42p	6/30L2	80p
ECC83	37p	PC88	70p	PL83	51p	6BW7	75p
ECC85	44p	PC97	44p	PL84	51p	6P23	80p
ECC86	52p	PC900	54p	PL500	83p	6P28	75p
ECH42	30p	PC84	44p	PL504	33p	6V6	55p
ECH81	40p	PC255	48p	PL508	21-10	10F1	75p
ECH83	90p	PC288	69p	PL509	22-00	20L1	92p
ECH84	57p	PC289	55p	PL519	23-10	20P4	98p
ECL80	57p	PC2189	58p	PL802	22-25	30C1	44p
ECL82	51p	PCF80	44p	PY33	57p	30C15	86p
ECL83	75p	PCF82	55p	PY81/3	45p	30C17	85p
ECL86	45p	PCF86	64p	PY36	45p	30C18	81-25
EF80	33p	PCF200	21-05	PY800	45p	30F5	86p
EF85	41p	PCF801	55p	PY801	45p	30FL1	21-08
EF86	57p	PCF802	60p	PY800	45p	30FL2	21-08
EF89	35p	PCF805	21-35	PY500A	21-10	30L1	44p
EF183	41p	PCF806	60p	UBF89	44p	30L15	86p
EF184	41p	PCF808	21-25	UCB6	51p	30L17	21-10
EH90	62p	PCH200	86p	UCH42	80p	30P12	86p
EL34	90p	PCL82	41p	UCH81	46p	30P19	21-00
EL41	64p	PCL83	55p	UCH82	46p	30P11	21-50
EL84	38p	PCL84	52p	UCL83	64p	30P13	27p
EL901	45p	PCL85	60p	UF41	75p	30PL14	21-80
EM64	49p	PCL805	68p	UF89	46p	30PL15	21-80
EY51	52p	PCL86	55p	UL41	80p	30P4MR	99p
EY86/7	40p	PCL200	21-30				

We offer return of post service. Post free over £10-00. Most other types available.

Items in stock at time of going to press but subject to possible market fluctuations if unavoidable.

TRADE. Representative will call West Country & S. Wales, also Suffolk, Norfolk, Hunts, etc.

Enquiries s.a.e. DISCOUNT PRICES, CWO only.

One valve post 7p, each extra valve 6p (maximum 50p) LISTS s.a.e. please.

POST  
TODAY FOR  
FREE BOOK

To: ALDERMASTON COLLEGE  
DEPT. CPW 17, READING RG7 4PF CPW17

Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London, EC2Y 5EJ Tel: 01-628 2721  
Yes. I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses

Name .....

Address .....

POST CODE .....



BIET

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



# Stirling Sound Products


FROM BI-PRE-PAK

## THANKS TO DEMAND AND STEPPED-UP PRODUCTION THIS HIGH-FIDELITY POWER AMPLIFIER MODULE

# SS.125 COSTS YOU £6.50 INCLUDING POSTAGE AND V.A.T.

Not only is this Stirling Sound's best audio amplifier yet; it rightfully qualifies as one of the best of its kind yet made available to constructors. Intended above all for high-fidelity, the characteristics of the SS.125 are such that it can be used in many other applications where dependability is the prime consideration. The SS.125 integrates well with other S.S. units as well as those of other manufacturers. Incorporates new circuitry using a complementary long-tailed pair input and full complementary output circuits to give lab standards of performance.

<b>OUTPUT</b>	25 watts R.M.S. into 8 Ω using 50V 22 watts R.M.S. into 4 Ω using 33V (Low imp. not less than 4 Ω)
<b>★ DISTORTION ★</b>	Less than 0.05% at all power levels (From 10Hz to 10KHz)
<b>FREQUENCY RESPONSE</b>	± 1dB 15 Hz to 30 KHz (4 Ω) ± 1dB 10 Hz to 30 KHz (8 Ω)
<b>HIGH Z INPUT</b>	100 Kohms (40dB gain/100x)
<b>INPUT SENSITIVITY</b>	150mV for 25W. R.M.S. out
<b>SIZE</b>	(Inc. built on heat sink type mounting bracket) 4½" x 3" x ½" high

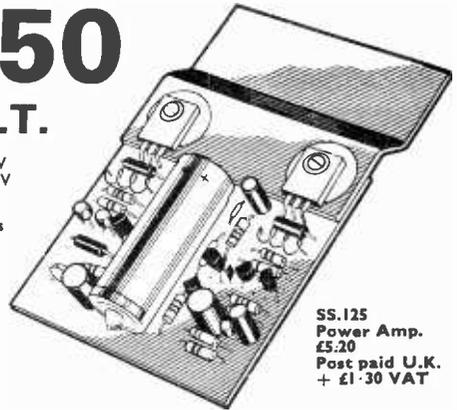

SS.125 Power Amp. £5.20 Post paid U.K. + £1.30 VAT

## More Stirling Sound Modules

All designed specially for low-budget needs with easy to follow instructions

### F.M. TUNER UNITS

- SS.201 Tuner front end. Ganged, geared variable tuning, 88—108MHz. A.F.C. facility **£5.00**
- SS.202 I.F. amp. A metre and/or A.F.C. can be connected (size 3" x 2") **£2.65**
- SS.203 Stereo decoder for use with SS.201 and 202 or any good F.M. tuner. A LED beacon may be attached (3" x 2") **£3.85**



SS.201



SS.203

### AUDIO MODULES

- SS.105 5 watt amplifier to run from 12V. (3½" x 2" x 2") **£2.25**
- SS.110 Similar to SS.105 but more powerful giving 10W. into 4ohms **£2.75**
- SS.120 20 watt module when used with 34 volts into 4 **£3.00**
- SS.140 Delivers 40 watts R.M.S. into 4 ohms using a 45V/2A supply such as our SS.345 the power and quality of this unit are superb—Size 4" x 3" x 2". **£3.75**
- SS.100 Active tone control stereo. ± 15dB lift-cut bass/treble **£1.60**
- SS.102 Pre-amp for ceramic **£1.60**
- SS.103 Active pre-amp (stereo) inc. R.I.A.A. and line feed back **£2.25**



SS.105




SS.140

### TERMS OF BUSINESS:

VAT at 25% must be added to total value of order except for items marked \* or (8%) when VAT is to be added at 8%. No VAT on overseas orders. POST & PACKING add 30p for UK orders unless marked otherwise. Minimum mail order acceptable—£1 Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.
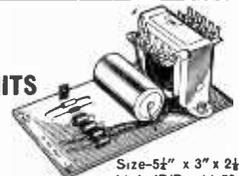
## ... And 5 NEW Stirling Sounds POWER SUPPLY UNITS

Robustly designed units in each of which is a stabilised take-off point to provide for tuner, pre-amp and control stages.



Size—5½" x 3" x 2½" high (P/P add 50p any model)

SS.312 12V/1A	£3.75	SS.334 34V/2A	£5.20
SS.318 18V/1A	£4.15	SS.345 45V/4A	£6.25
SS.324 24V/1A	£4.60	(all above are at 8% V.A.T.)	

## A new Stirling Sound Capacity Discharge Ignition Unit for your car the "Super-Spark" Mk.5.

Even better than the original B-P-P version, thousands of which are in use saving motorists appreciable time and money for petrol. Very easy to install. The Stirling Sound model incorporates switch for instant change to conventional ignition; immediate adaption to pos. or neg. earth return; anti-burglar immobilising switch, pre-set control for rev. limitation. There are no exposed parts, the unit, on p.c.b. being housed in strong enclosed metal box. With instructions and leads. Size 7½" x 4½" x 2½" ex. switches.

KIT **£7.95** BUILT & TESTED **£10.50**

### A USEFUL CATALOGUE—FREE

Send us a large S.A.E. with 10p stamp and we will send you the latest Bi-Pre-Pak catalogue free by return. Packed with useful lines, it's a real money saver.

TO STIRLING SOUND (BI-PRE-PAK LTD) 220/222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 0DF

Please send .....

..... for which I enclose £ .....

inc. V.A.T.

NAME .....

ADDRESS .....

PWSB

Order your Stirling Sound products from

# BI-PRE-PAK LTD

Co Reg No 820919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 0DF.

TELEPHONE: SOUTHEND (0702) 46344

CHEQUES/MONEY ORDERS PAYABLE TO BI-PRE-PAK LTD

# ESSENTIAL BOOKS FOR RADIO AMATEURS

1976 Edition

## RSGB AMATEUR RADIO CALL BOOK

Incorporates all new call signs and amendments notified between August 1974 and August 1975.

Also includes valuable operating data such as band plans, beacons, prefix list, ITU zone list, beam headings and QSL Bureau sub-managers, and lists of clubs and groups.

168 pages

Price £1.47 post paid

## RADIO DATA REFERENCE BOOK

by G. R. Jessop, CEng, MIERE, G6JP

An invaluable source of essential radio data conveniently gathered into one hard-bound volume measuring 5½in by 9in.

150 pages

Price £1.32 post paid

## AMATEUR RADIO TECHNIQUES

(5th edition)

by Pat Hawker, G3VA

Basically an ideas and source book, this ever-popular work brings together a large selection of new circuits and devices and many constructional and fault-finding hints.

In this latest edition some 50 pages of new material have been included and other sections have been revised and expanded.

304 pages Price £2.52 inc. p. & p. Over 700 diagrams

## RSGB LOG BOOKS

**TRANSMITTING:** Standard, 96p; de luxe, £2.44; minilog (for mobile and portable), 80p. All post paid.

**RECEIVING:** £1.20, post paid.

The **Receiving Log Book**, similar in format to the transmitting log books, is designed specially for the short-wave listener who wishes to make a proper record of amateur stations heard.

These are just a few of a complete range of technical publications, log books and maps for the radio amateur. Send a large stamped self-addressed envelope for the complete list.

The **RSGB** is the national society representing all **UK** radio amateurs. Membership is open to all interested in the hobby: write to the membership section and ask for full details.

# RADIO SOCIETY OF GREAT BRITAIN

35 DOUGHTY STREET, LONDON, WC1N 2AE TEL: 01-837 8688



**ALL PRICES INCLUDE V.A.T.**



**PERSONAL CALLERS ARE WELCOME!**

all items subject to manufacturers increase and availability



High Quality Construction Kits, stocked at all branches. Send for catalogue!

**AMPLIFIERS** P&P 95p ins. £1  
Sansui AU2200 £63.70  
AU400 £97.50  
Pioneer SA5300 £63.00

**RECORD DECKS** P&P 85p ins. 50p  
Gerrard SP25 Mk. IV £23.00  
Gerrard SP25 Mk. IV/G800 £36.85  
Plinth & Cover  
BSR MP60 £17.00  
Connaisseur BD1 Kit £16.56  
BD2 Chassis/SAU2 £42.68  
SAU2 Pick-up Arm £17.81  
SCUT Cartridge £7.43  
Pioneer PL12D £58.25  
Plinth-cover for Gerrard or BSR £5.31

**SPEAKERS** P&P 45p  
EMI 13" x 8", 3, 8 ohm plain £3.75  
13" x 8" Bass unit, 15 watt £7.25  
6½" 8 ohm, 10 watt £4.06  
8" 8 ohm, 10 watt £5.93  
8" x 5" C. Mag. 5 watt 3, 8 or 15 ohm £2.62  
8" x 5" Dualcone 8 ohm, 10 watt £4.12  
Elac 6½" 8 ohm Dualcone £3.06  
8" 8 ohm Dualcone £3.37  
Baker Group 25 12", 8 or 15 ohm £15.00  
Adastra 10" 10 watt, 15 ohm £4.68  
Goodmans 8" x 5" 8 ohm £2.12  
Global 8 ohm 5 watt (pair) £9.93  
Richard Allan 12" 60 watt 8 or 15 ohm £12.95  
Richard Allan 12" Dualcone £13.95

**WHARFEDALE SPEAKER BARGAINS**  
P&P 85p ins. 50p  
Chevin (pair) £31.87  
Denton 2 (pair) £40.00  
Linton 3 (pair) £59.50  
Linton 2 (kits) £26.18

**KIT FORM CABINETS**  
Teak Veneer P&P 85p ins. 50p  
12" x 8" x 4½" (8 x 5 or 7 x 4 cutout) £3.34  
12" x 12" x 7½" (10", 8 x 5, 8", 6½" and 3½") £4.75  
18" x 11" x 7½" (8" x 3½" or 13 x 8) £5.94  
22" x 14" x 7½" (12" x 3½" or 13 x 8) £7.18

**TWEETERS & CROSSOVERS**  
P&P 25p  
Cone Tweeter 8 or 15 ohm, 10 watt £3.68  
Cone Tweeter 8 ohm, 3 watt £1.93  
Horn Tweeter 8 ohm, 20 watt £7.72  
Dome Tweeter 8 ohm, 30 watt £7.18  
Crossovers CN23 (3 ohm) CN28 (8 ohm), CN126 (16 ohm) £1.75

**CARTRIDGES & STYLII**  
P&P 25p Cart. D.D. StylII  
Acos GP91/2SC or 3SC (ster. comp) £1.60 £1.20  
GP93/1 or 95/1 ster. cryst £1.60 £1.20  
GP94/1 or 96/1 ster. ceram. £2.00 £1.20  
GP101 cryst. comp. £1.00 —  
GP104 ster. ceram. £2.15 £1.20  
BSR X5M or H5X cryst. comp. £1.85 £1.20  
SX6M or SX6H cryst. ster. £2.25 £1.20

SC5M ster. ceram. £2.75 £1.20  
Sonitone  
9TAHC or 9TAHC G (Diam) £2.25 £1.20  
3509 ster. ceram. £2.25 £1.20  
Audio Technica AT55 £2.25 —  
Empire 999 REX £4.95 —  
Goldring G850 £3.50 £1.75  
G800 £5.25 £1.75  
G800H £6.25 £1.75  
S800E £9.06 £3.50  
Shure Carls & StylII  
M44G £6.10 £4.93  
M55E £7.81 £6.18  
M75ED Type 2 £14.66 £10.31  
M75EJ Type 2 £12.18 £7.81

**MICROPHONES** P&P 25p  
CM70 Planet stick metal, switch crystal £2.12  
DM160 Dynamic omni-dir. ball metal £8.18  
UD150 50K 600 ohm, uni-dir, ball metal £7.31  
CONDENSER MIKE 600 ohm, uni-dir. £10.62  
Casette STICK MIKE with R Control on/off switch (2.5 x 3.5 mm) J/Ply £1.50  
Casette STICK MIKE with R/Control (Phillips Type) £1.97

**BATTERY ELIMINATORS**  
P&P 25p  
240v Input 6, 7.5 or 9 volt output £2.75  
12v d.c. Input (specify output 6, 7.5 or 9 d.c.) at 300mA £4.62

**CASSETTES** P&P 25p  
Type Low noise Philips Memor- ex  
C60 37p 59p 81p 81p  
C90 48p 81p £1.18  
C120 59p £1.18 £1.67

**CASSETTE CASES** £0.13  
Cassette Head Cleaner £0.48  
BIB Stereo Test Cassette £2.32  
AMPEX Head Cleaner Demag £1.99

**TAPES** P&P 25p  
Std. LP DP Cases  
5" 59p 70p £1.08 32p  
5½" 70p 92p 38p  
7" 92p £1.19 £1.99 45p

**SINCLAIR PROJECT 80** P&P 25p  
Stereo Pre-amp £18.10  
Active Filter Unit £9.95  
Z40 15 watt Amp. £7.18  
Z60 25 watt Amp. £9.06  
P25 Power Supply for 240 £6.81  
P26 Power Supply for 240 £10.56  
P28 Power Supply for 260 £19.31  
FM Tuner £16.18  
Stereo Decoder £10.56  
Q16 Speaker £9.31  
IC20 stereo amp. kit £9.37  
P220 Power kit £8.56

Send 25p for complete catalogue.

PLEASE BRING THIS ADVERTISEMENT TO OBTAIN THE BENEFIT OF THESE SPECIAL PRICES


ALL MERCHANDISE FULLY GUARANTEED

**NEWMART ELECTRONICS**

Mail Order Dept PW4  
Belmont St, Monton,  
Eccles, Manchester.  
Tel: 061-789 5268

Manchester  
30-32 Shudehill, tel 061-832 7710  
Leeds  
4 New Market St tel 0532 42708  
Liverpool  
15 Whitechapel tel 051-236 0738

Why not  
**DIAL-A-COMPONENT?**

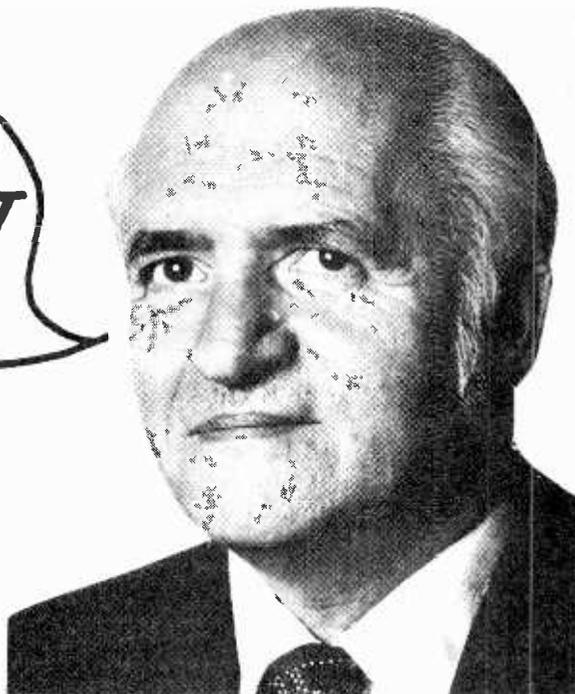

These days you can Dial-a-Van, Dial-a-Recipe, Dial-a-Pop Tune, even Dial-a-Wine. But Home Radio Components Ltd. have been offering such a service for years! Those of you who already own one of the renowned Home Radio Components catalogues already know all about it. For the benefit of those who are still struggling along without one, here is how you set about it.

1. Purchase a Home Radio Components Catalogue. (See details further on).
2. Join the HRC Deposit Account scheme, by simply signing the form enclosed in the catalogue.
3. Send it to HRC with your deposit. The deposit is half of whatever credit you require; i.e. if you want £10.00 you send £5.00.
4. You will receive back: a copy of your Agreement, special Order Forms, pre-paid envelopes for sending them, a Record Card on which to note your spending, and simple instructions to enable you to use the service to best advantage.

Now you are all set to dial your component orders any hour of the day, any day of the year—including Sundays, holidays, even Christmas day. You have your own exclusive

telephone number, which after business hours is connected direct to an answerphone.

*Like the idea?* Then send for your Home Radio Catalogue straight away. It costs only 54p plus 45p postage and packing, and it contains 6 vouchers each worth 5p when used as directed, so you can soon get back 30p of your investment. Moreover, if you join the Deposit Account scheme you will receive a new catalogue free whenever it is reprinted. It's hardly surprising that over a thousand customers are already using this simple method of buying their components. *Try it now—you'll never regret it.* Send 99 pence by cheque, Postal Order or Giro with the coupon below, and soon you'll be twirling your telephone dial whenever you urgently want some parts!

Today's finest Components Catalogue  
**54p plus 45p POST & PACKING**

The price of 99p applies only to customers in the U.K. and to BFPO Addresses.

Please write your Name and Address in block capitals

NAME.....

ADDRESS.....

.....

.....

HOME RADIO (Components) LTD., Dept. PW,  
234-240 London Road, Mitcham, Surrey CR4 3HD

(Regn. No. London 912966)




**POST THIS COUPON**  
with cheque  
or p.o. for  
**99p**



**HOME RADIO (Components) LTD, Dept. PW, 234-240 London Road, Mitcham, CR4 3HD Phone 01-648 8422**

# Build it yourself!

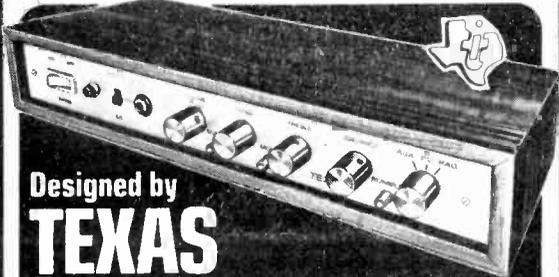

Designed by  
**TEXAS**

Featured by **PRACTICAL WIRELESS**  
SOLE U.K. DISTRIBUTORS - **HENRY'S**

Build the Texan stereo amplifier, then you can be doubly proud! For a start, you'll own a superb home entertainment unit. And have had all the pleasure of doing it yourself, with the Henry's kit.

**Look at the Texan specification**

Incorporating fully integrated stereo preamp and power amp, with 6 IC's, 10 transistors, 6 rectifiers and zener diodes. Plus stabilised, protected circuitry, glass fib pcb; Gardeners low-field low-line mains transformer; all facilities and controls. Slim design, chassis 14" x 8" x 2" overall, 20 watts per channel RMS, less than 0.1% distortion at 1 kHz.

★ Can be built Stage by stage  
Ask for leaflet 20.  
★ Everything necessary supplied. Full after sales service and guarantees.

**KIT PRICE**  
**£35.00**  
inc. VAT + £1 p&p

Built and tested  
**£45.00 inc. VAT**  
+ £1.00 p&p.

**THE NATURAL FOLLOW-ON - THE TEXAN FM TUNER KIT!**

**KIT PRICE**  
**£25.95**  
inc. VAT +  
50p p&p.

Build the matching Texan stereo tuner! Features advanced varicap tuning, Phase lock loop decoder. Professionally designed circuit. Everything you need is in the kit. From the glass fibre pcb to the cabinet itself. Excellent spec: 2.5 uV aerial sensitivity, 500 mV output (adjustable). Tuning range 87-102 MHz. Mains powered.

Built and tested £30.95 inc. VAT + 50p p&p.

**VIDEO SPORT**

... all the electronic excitement  
you could wish for!


★ OVER  
10,000  
ALREADY SOLD  
★ IDEAL  
GIFT

An up-to-the-minute game. Plugs into your own TV aerial socket. Switch on. And you're away! Choose your game - football, tennis or hole-in-the-wall. Absolutely safe. For you. Your children. And your TV. Mains powered.

List Price £42.50 inc. VAT + 50p p&p.

**HENRY'S PRICE - ONLY £29.50**

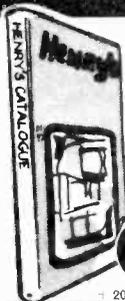**WHATEVER YOU DO, DON'T FORGET YOUR LATEST HENRY'S CATALOGUE!**



For this new edition, we have made hundreds of changes and additions. It has over 200 pages, containing virtually everything for amateurs and professionals. And you'll have no bother at all finding everything you want, because there's a complete alphabetical index as well as a section index. Together, they put you right on course for the items you need. From Sinclair projects to educational kits. Oscilloscopes to panel meters. Coils to capacitors. Transistors to valves. Loudspeakers to microphones - all at competitive prices. Over 200 pages of vital statistics - just for you! So send now for your copy.

- Over 5000 items inside!
- Every copy contains a free 50p voucher.
- Many new items.
- Over 200 pages.

**ONLY 50p**

**FREE** to Educational Establishments when ordered on official headed notepaper.

+ 20p carr/pack.

**Henry's**

**SELF-SERVICE CENTRES 404 and 309 EDGWARE ROAD, LONDON W2**  
Bargains galore - Call in and see for yourself!

404/6 EDGWARE ROAD, LONDON W2 01-402 8381

LOWER SALES FLOOR, 231. TOTTENHAM CT. RD., LONDON W1 01-636 6681

NEW MIDLANDS STORE

94/95 UPPER PARLIAMENT STREET, NOTTINGHAM, 0602-40403  
ALL MAIL TO HENRY'S RADIO, 303 EDGWARE ROAD, LONDON W2

**TRIMMERS** air spaced ceramic 20pf 10 for 80p. also min type 3/10pf 10mm dia 5 for 50p. **FEED-THROUGH CONDS** 1000pf/500v solder in type 10 for 50p. **ERIE** feedthrough filtercons 1750pf 250v solder in type high grade filters 10 for £1. **B.F.O. UNIT** 1.6Mc/s var freq with valve £2. **MINIATURE COILS** with scr cans & slugs 5mm dia formers 10 for 50p. **REMOTE Tx/Rx crystal selector** provision for 6 Rx & 6 Tx crystals Hc6/u type also 6x BC108 & 6x trimmers £1.60. **I.F. TRANS** min type 455/465Kc transistor type 3 for 65p. **TAPE HEADS** 8 track for 1" tape low imp £1.20. **MIN ROTARY SWT** 2p 5w 1/2 x 1/2" shaft 2 for 60p. **CRYSTAL FILTERS** all 10.7Mc/s min type 30Kc b.w. £1.30. 15 & 12Kc b.w. £1.60. **INTEGRATED CIRCS** three types CA3014 I.F. amp & disc. ULN-2111A wide band amp with product det. TAA300 audio amp 1 watt into 8 ohm one of each with data sheets £1.50. **AERIAL TUNING** coil ass Rx type, A as 8 coils & trimmers covering long to s.w. in scr box £1.70 type B as 6 coils & trimmers covering s.w. £1.20. **POLAR RELAYS** precision type as two coils of 3.5K octal base £1.50. **YAXLEY SWTS** larger type inst swts 8p 12w 8b & 2p 23w 2b £1.40ea. 7p 23w 7b £1.70 & 6p 12w 6b £1.20. **T.V. AERIAL FILTERS** made to fit in Ae lead fully scr box 4 x 1 1/2 x 1 1/2" fitted standard coax plug & sk. 4 for £1.20. **SPEAKER UNITS** small horn spk for use on M/Cycle 3 ohm with fix brk & cable spk 5 x 3" £2.50. **DIODES** 300PIV 5 amps on H/Sink stud mt type 4 for £1. **CRYSTALS** FT243 type in range 5-6 to 8.6Mc/s 25Kc spacing 5 different for £1.40 also Hc18 type min wire ended in range 13 to 19Mc/s ex equip 10 for £1.50. **TAG STRIPS** solder type 24 way 10 for 70p.

The following items are in S/Hand cond.

**MOD & H.T.** Inverter unit about 15w mod H.T. 200/400v at 150Ma 12v I/P with circ £4.80. **Tx SUB ASS** for 70/80Mc/s less valves with circ about 20w £2.40. **METER T.S.** in case 9 x 7 x 5" with 1Ma FSD meter, swts, etc £3.50. **VIDICON TUBES** standard 1" types P849D & P842 tested £9.60. **FLOURESCENT CHOKES** 5ft 65w £1.60 & 8ft 125w £2.20. **HEAVY DUTY VARIACS** for 240v 50c/s rated 20/25 amps with 200/250v driving motor with limit swts £40. **SCOPES MARCONI** type CT90 mains operation high speed pulse scopes triggered high speed T.B. with int time cal & Y shift voltmeter (note not suitable for general purpose use) supplied with copy of H/Book in transit case £26. **OPTICAL MIRRORS** 1 1/4" dia. 1 1/2" deep at centre with centre hole 3/4" dia precision unit £15. **TAPE DECKS** BSR type TD10 with two chan amps & P.U. £8.50 & TD2 with amps only £5.50. these two items callers only.

Above prices inc carr/postage & V.A.T. Above goods are new unless stated S/Hand. S.A.E. for list or enquiry, shop open Tues to Sat.


**A. H. SUPPLIES**

122 HANDSWORTH ROAD  
SHEFFIELD, S9 4AE  
Phone 44278 (0742)

# RADIO EXCHANGE LTD.

**ALL PRICES  
INCLUDE VAT**

## NEW EDU-KIT MAJOR

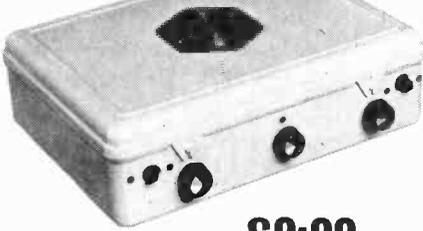

Completely Solderless Electronic Construction Kit. Build these projects without soldering iron or solder

- ★ 4 Transistor Earpiece Radio
- ★ Signal Tracer
- ★ Signal Injector
- ★ Transistor Tester NPN-PNP
- ★ 4 Transistor Push Pull Amplifier
- ★ 5 Transistor Push Pull Amplifier
- ★ 7 Transistor Loud-speaker Radio MW/LW
- ★ 5 Transistor Short Wave Radio
- ★ Electronic Metronome
- ★ Electronic Noise Generator
- ★ 21 Capacitors
- ★ Mica Baseboard
- ★ 2 Slider Switches
- ★ 1 Tuning Condenser
- ★ 3 12-way connectors
- ★ 3 Knobs
- ★ 6 1/2 yards of wire
- ★ Batteryless Crystal Radio
- ★ One Transistor Radio
- ★ 2 Transistor Regenerative Radio
- ★ 3 Transistor Regenerative Radio
- ★ Audible Continuity Tester
- ★ Sensitive Pre-Amplifier
- ★ 10 Transistors
- ★ 3 12-way connectors
- ★ 3 Knobs
- ★ 6 1/2 yards of wire

**Total Building Costs £9.99**  
P & P + Ins. 65p. (Overseas Seamail P & P £3.50)

## VHF AIR CONVERTER KIT

Build this Converter Kit and receive the Aircraft Band by placing it by the side of a radio tuned to Medium Wave or the Long Wave Band and operating as shown in the instructions supplied free with all parts. Uses a retractable chrome plated telescopic aerial, Gain Control, V.H.F. Tuning Capacitor, Transistor, etc.

All Parts including Case and Plans. P & P and Ins. 40p.




## NEW Everyday Series

Build this exciting new series of designs.

E.V. 5. 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9" x 5 1/2" x 2 1/2" approx. All parts including Case and Plans.

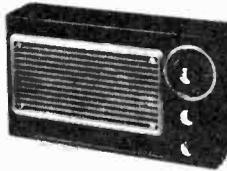**Total Building Costs £4.75** P & P + Ins. 50p



E.V. 6. Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull output.

All parts including case and plans. **Total Building Costs £5.50** P & P + Ins. 55p

E.V. 7. Case and looks as above, 7 Transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band SW1, SW2, SW3, powered by 9 volt battery. Push Pull output. Telescopic aerial for short waves. 3" Loudspeaker.

All parts including Case and Plans **Total Building Costs £7.05** P & P + Ins. 55p

## ROAMER TEN MARK 2

WITH VHF INCLUDING AIRCRAFT

Now with free earpiece and switched socket, 10 transistors. Latest 5" x 3" loudspeaker. 9 tuneable wavebands, MW1, MW2, LW, SW1, SW2, SW3, trawler band, VHF and local stations, also aircraft band. Built in ferrite rod aerial for MW/LW. Chrome plated, 6 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push pull output using 600mV transistors. Car aerial socket. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for aircraft band. Volume on/off. Wave change and tone controls. Attractive Case in rich chestnut shade with Gold Blocking. Size: 9" x 7" x 4". Easy to follow instructions and diagrams. Total building costs

**£11.87** P & P + Ins. 65p



## POCKET FIVE


NOW WITH 3" LOUSPEAKER  
3 Tuneable wavebands, M.W., L.W., and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5 1/2" x 1 1/2" x 3 1/2" approx. All Parts including Case and Plans. P & P + Ins. 50p.

**Total Building Costs £3.99**


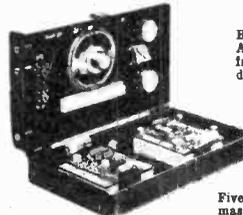
## EDU-KIT

Build Radios, Amplifiers, etc. from easy stage diagrams.



Five units including master unit to construct.


Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2" Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. All Parts including Case and Plans

**£6.99** P & P + Ins. 55p

## ELECTRONIC CONSTRUCTION KITS

**ECK 2** Self Contained Multi-Band V.H.F. Receiver Kit. 3 Transistors and 3 Diodes. Push/Pull output. 3" Loudspeaker, Gain Control. Superb 9 section swivel ratchet and retractable chrome plated telescopic aerial, V.H.F. Tuning Capacitor, Resistors, Capacitors, Transistors, etc. Will receive T.V. Sound, Public Service Band, Aircraft, V.H.F. Local Stations, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans

**£7.95** P & P and Ins. 55p.

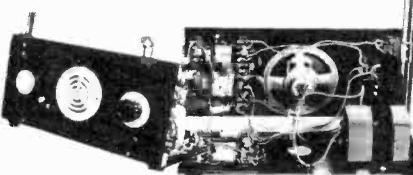

**ECK 4** 7 Transistors, 6 tuneable wavebands, MW, LW, Trawler Band, 3 Short Wave Bands. Receiver Kit. With 5" x 3" Loudspeaker.

Push/Pull output stage, Gain Control, and Rotary Switch. 7 Transistors and 4 Diodes. 6 section chrome-plated telescopic aerial. 8" Sensitive Ready Wound Ferrite Rod Aerial. Tuning Capacitor. Resistors, Capacitors, etc. Operates from a 9 Volt PP7 Battery (not supplied with kit). Complete kit of parts including construction plans.

**£7.25** P & P and Ins. 55p.



## EDU-KIT JUNIOR

Completely Solderless Electronic Construction Kit. Build these projects without Soldering Iron or Solder.

- ★ Crystal Radio Medium Wave Coverage — No Battery necessary.
- ★ One Transistor Radio.
- ★ 2 Transistor Regenerative Radio.
- ★ 3 Transistor Earpiece Radio Medium Wave Coverage.
- ★ 4 Transistor Medium Wave Loudspeaker Radio.
- ★ Electronic Noise Generator
- ★ Electronic Metronome.
- ★ 4- Transistor Push/Pull Amplifier.


All parts including Loudspeaker, Earpiece, MW Ferrite Rod Aerial, Capacitors, Resistors, Transistors, etc. Complete kit of parts including construction plans.

**£7.25** P & P + Ins. 55p

## JIFFY TESTER

Easy to build and operate. Fits in the pocket. A quick checker for continuity of resistors, chokes, diodes, transistors, circuit wiring (not mains) and loudspeakers. Complete with earpiece, jack plug and socket resistors, capacitors, components, etc. Complete kit of parts including construction plans.

**£3.15** P & P + Ins. 30p

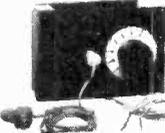

**TO RADIO EXCHANGE LTD.,**  
61A HIGH STREET, BEDFORD MK40 1BA  
Tel: 0234 52367.

Reg. No. 738372

ALL PRICES INCLUDE VAT

- ★ Callers side entrance "Lavelle's" Shop.
- ★ Open 10-1, 2.30-4.30. Mon-Fri. 9-12 Sat.

I enclose £.....

for .....

Name .....

Address .....

PW578

## SUBSCRIPTIONS - PRACTICAL WIRELESS AND TELEVISION MAGAZINES

WE are still receiving numerous letters requesting subscriptions to *Practical Wireless* and *Television* magazines. For those readers who are not aware, we regret that our magazines can no longer be supplied on direct subscription by IPC Limited due to escalating costs.

This action is very much regretted, but it should not mean that any reader is deprived of his/her regular copies of *Practical Wireless* or *Television*. Readers should order direct from their local newsagents. Any readers outside the UK who have difficulty in locating a supplier should write to the Editor and he will advise them of their local agent.

### Grimsby A.R.S.

THE Grimsby Amateur Radio Society has moved to a new QTH. The address is now the New Alexandra Social Club, Alexandra Road, Cleethorpes.

The meetings are held fortnightly on Thursday evenings at 8 p.m. Old and new members are always made welcome as is anybody with an interest in short wave listening, amateur radio, electronics etc.

If anyone would like further details, please contact *George Smith, G4EBK, Hon. Sec., 6 Fenby Close, Grimsby, South Humber-side, DN37 9QJ.*

### RNARS events

THE following is the 1976 calendar of events of the Royal Naval Amateur Radio Society, the headquarters of which, G3BZU, are located at HMS Mercury, Leydene, Hampshire. If you would like any further information, contact Mike Matthews, G3JFF at the above address.

16-24th April  
HMS Belfast activity period. GB3RN all bands. 24 hour day operation. Further details G3HZL QTHR.

20th June  
HMS Mercury Mobile Rally.

28-30th August  
Portsmouth Dockyard—Navy Days. GB3RN and displays in conjunction with HMS Mercury Communications Exhibit.

16-17th October  
JOTA scout camp and Amateur radio teach-in at HMS Mercury/G3BZU.

### Fuse Standards

THE British Standards Institution has published a revision of BS 88 now entitled *Cartridge fuses for voltages up to and including 1,000V a.c. and 1,500V d.c.* There are two parts: Part 1 *General requirements*, and Part 2 *Supplementary requirements for fuses of standardised dimensions and performance for industrial purposes.*

Part 1 specifies general requirements, including characteristics, construction, performance, and proving tests for all types of cartridge fuses. Subsequent parts will give supplementary requirements in different applications. Part 2 is for industrial purposes, and specifies fuses most commonly used in the United Kingdom. These two parts of BS 88 substantially agree with IEC publication 269. The earlier edition of the standard has been withdrawn.

BS 88 Part 1 price £5.50 and Part 2 £3.50 may be obtained from *BSI Sales Department, 101 Pentonville Road, London N1 9ND.*

### BBC Radio Leicester

BBC Radio Leicester's medium-wave service is transmitting from a new, improved aerial at Freeman's Common.

The medium-wave service, on 188 metres (1594kHz), can be received at distances of twenty miles or so from the transmitter in daytime, but after dark the coverage is restricted by interference from other transmitters. The vhf programme is transmitted on 95.1MHz.

### N. Radio Societies Association

THE Annual Convention and Exhibition of the N.R.S.A., which is sponsored by radio societies in the North of England, will take place at Belle Vue, Manchester on Sunday 25th April 1976.

The doors will open at 11am and there will be a large number of trade exhibitors, as well as club display stands. A trophy will be awarded for the best club stand and there will also be a variety of demonstrations connected with different aspects of amateur radio.

Other attractions will include a Grand Raffle, an Inter-Club Quiz and a Construction Contest.

Comprehensive talk-in facilities will be provided on 2 metres 145.5MHz (FM), 145MHz (AM), and on 144.290MHz (SSB); also on 4 metres 70.26MHz (AM & FM). There will be a GB3NRS HF bands station operating from the exhibition.

For long distance travellers it is hoped to offer talk-in through the local repeaters GB3MP (ChR6) and GB3RF (ChR7). Both these repeaters are scheduled to be on the air before the event, and there is considerable interest in mobile operation throughout the North West.

The N.R.S.A. is a non-profit making body which relies on the income from this convention and the small subscription from member societies in order to organize the following year's event. Further information can be obtained from the Publicity Officer:—*Mr. Gordon Adams, 2 Ash Grove, Knutsford, Cheshire, WA16 8BB. Telephone:—Knutsford 4040.*

### BBC Radio Medway-Hoo

BBC Radio Medway's medium-wave service on 290 metres (1034kHz) is now transmitted from a new aerial at Hoo and the old station at Gillingham has closed down.

The vhf service from Wrotham, on 96.7MHz, is unaffected by this change.

# NEWS...

# NEWS...

# NEWS...

## RTTY news

**T**HE British Amateur Radio Teleprinter Group announced the start on 7th March, 1976, of its RTTY News Bulletin service for radio amateurs.

Initially, the transmissions are made every Sunday according to the schedule below; later it is expected that more transmitting stations will be added to those listed.

The material transmitted will include test tapes for machines and systems plus news of specific RTTY interest.

The licence for GB2ATG is a broadcast, not a communications licence so transmitting stations will not be able to reply to any calls using this callsign.

Time	Frequency	Signal Characteristics	Transmitting Stations
1. 1200 hrs	3590kHz	45.45 bauds FSK 170Hz shift	G3IIR, G3OZF, GW3IGG
2. 1230 hrs	144.60MHz	(i) 45.45 bauds FSK, 850Hz shift	G3IIR, G3OUF, G3OZF
		(ii) 45.45 bauds AFSK, 170Hz shift, 2125/2295Hz tones	

## Summer School

**T**HE Department of Electrical Engineering Science at Essex University will be holding its annual Electronics Summer School for teachers during the week July 12-16 this year. Three courses will be run simultaneously. The "Linear Circuit Design" course is concerned with the use of transistors and operational amplifiers in analogue applications and the basic circuits of a hi-fi amplifier are investigated in detail. The "Digital Circuit Design" course concentrates on the use of the transistor as a switch and develops design using integrated logic circuits; a digital patch-board is used to introduce the concepts of combinational and sequential logic design.

"Small Computer Systems" is a new course which should be of interest to mathematics teachers as well as those interested in electronics; the aims of the course are to introduce a typical small computer, the PDP-8, to investigate how it is used and to discuss its function in schools.

Further information on the Summer School can be obtained from R. J. Mack, Department of Electrical Engineering Science, University of Essex, Wivenhoe Park, Colchester CO4 3SQ, telephone Colchester (0206) 44144, extension 2408 or 2299.

## Amateur Computer Club

**I**F you would like to find out more about the Amateur Computer Club, send a stamped, addressed envelope to J. T. C. Aslen, Club Secretary, 7 Doordells, Basildon, Essex. Telephone: Basildon 411125 or 0484-56712.

They have recently published a design for a low-cost computer and they think they will have working models by the middle of this year.

## Longleat Rally

**T**HE 19th Longleat Mobile Rally will take place at Longleat House, Longleat Park, near Warminster, Wiltshire, on Sunday June 27, 1976.

As in previous years, the trade stands will be housed in large marquees. The rally is to start at 10 a.m. and talk-in stations will be operational on 160m (1920kHz), 80m (3775kHz) and 2m (145.50kHz + VFO). Callsigns will be announced nearer the date. There will be a walking DF hunt at 3 p.m. on Top Band and there will be a Grand Raffle. Overnight camping will be allowed from 6 p.m. on Saturday 26th. Further gen from Brian Crocker, G3ULJ, Organiser, 36 Portland Street, Staple Hill, Bristol, BS16 4PT.

## Hot news from Heathkit



**H**EATHKIT announce their "Modulus" system of audio units. The range comprises a digital AM/FM tuner/2-4 channel preamp/control centre; a stereo receiver of "medium" or "high" power; and a 4-channel receiver "medium" or "high" power. You build in to your system what you want. Optionals include FM Dolby CD-4 Demodulator and SQ Decoder. All these items and more feature in the April/May 1976 Heathkit Catalogue supplement. — Heath (Gloucester) Limited, Dept. PW46, Gloucester, GL2 6EE.

## Barking Society

**T**HE Barking Radio and Electronics Society G3XBF/G8GPK, have recently started a new activity dealing with all aspects of closed circuit television. This section is attempting to build its own studio, but is hampered by a lack of members and may be forced to close. They feel there must be a need for a Video club in their area and have asked us to mention its formation in the News section of P.W. The society also runs a Morse Class on Tuesday evenings. Further details of any of their activities can be obtained from J. R. Wiles at Society HQ, Westbury Recreation Centre, Westbury School, Ripplè Road, Barking, Essex, IG11 7PT. (Telephone: 01-594 4009.)

# 3-BAND RF MINI-AMPLIFIER

F.G.RAYER

**T**HIS tuned RF amplifier will be found to provide quite substantial gain, and is of great help in bringing weak signals up to a level where they can be received properly. Even with a sensitive receiver having two RF amplifiers and a number of IF stages, it can result in the satisfactory reception of signals which are otherwise virtually impossible to copy.

With stronger signals, which would in any case be received satisfactorily, the unit helps to reduce second channel interference, which can be troublesome with some receivers. However, its main use is in improving reception where a poor aerial, or the low signal strength of the wanted transmissions, makes adequate reception otherwise impossible.



## CIRCUIT DETAILS

Three coils are used, L1, L2 and L3, Fig. 1. Switch S1 selects the required coil. One section of VC2 (208pF) is used for L2 and L3. For the lowest frequency range L1, VC1 is also in circuit, giving 384pF in all. As a result, three ranges as follows are obtained:—

- Range 1—15—32MHz
- Range 2—5.5—15MHz
- Range 3—1.6—5.5MHz

It is of course not essential to provide tuning in this way. But if a value of about 365pF is used for all bands, Ranges 1 and 2 will overlap considerably, while the use of 200pF or so for each band will curtail the coverage of L3 at the low frequency end.

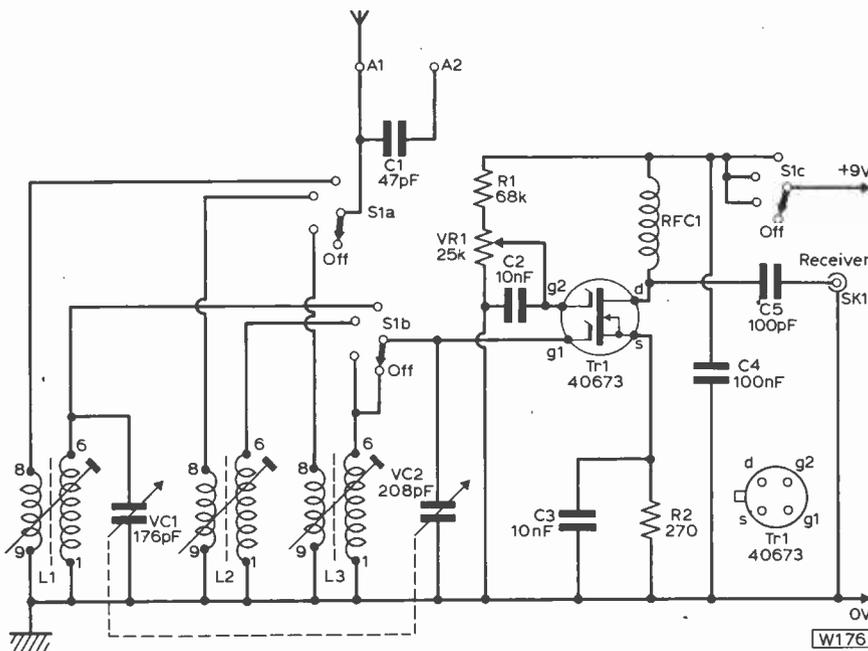


Fig. 1: Complete circuit diagram of the amplifier, showing the method of switching the coils to obtain a frequency coverage of 1.6MHz to 32MHz.

## ★ component list

<b>Resistors</b>	
R1 68k $\Omega$	R2 270 $\Omega$
VR1 .25k $\Omega$ Lin. potentiometer	
All resistors $\frac{1}{2}$ W 10%	
<b>Capacitors</b>	
C1 47pF	C4 100nF
C2 10nF	C5 100pF
C3 10nF	
VC1/VC2 Jackson type 00, 176/208pF gang.	
<b>Semiconductors</b>	
Tr1 40673	
<b>Miscellaneous</b>	
L1, 'Blue' valve type Range 3. L2, 'Blue' valve type Range 4. L3, 'Blue' valve type Range 5 (All coils Denco miniature dual purpose). RFC1, RF choke type Denco RFC5. Jackson type 4832 two speed drive with knobs. S1a, b, c, 3-pole 4-way rotary switch. 127 x 101 x 51 mm Universal chassis, with extra 127 x 101mm plate. (Home Radio). Four 12mm high rubber feet. Two insulated aerial sockets. Coax socket. Tag strip comprising 8 tags. Battery clip. Two matching control knobs.	

Results would be the same, but it is felt that having three ranges which include all bands from 1.6MHz to 32MHz in this way is probably better.

Switch section S1a/b Fig. 2 is for coil coupling windings while the third section of the switch, S1c, is for on-off purposes. An alternative aerial socket A2 is fitted for use instead of A1, when the unit is required to tune fairly sharply. Any end-connected aerial can be used.

Potentiometer VR1 allows amplification to be reduced when strong signals are present, as these might overload the receiver. This control however does not reduce gain to the level where no signals can be received.

Coupling to the receiver is from the RF choke

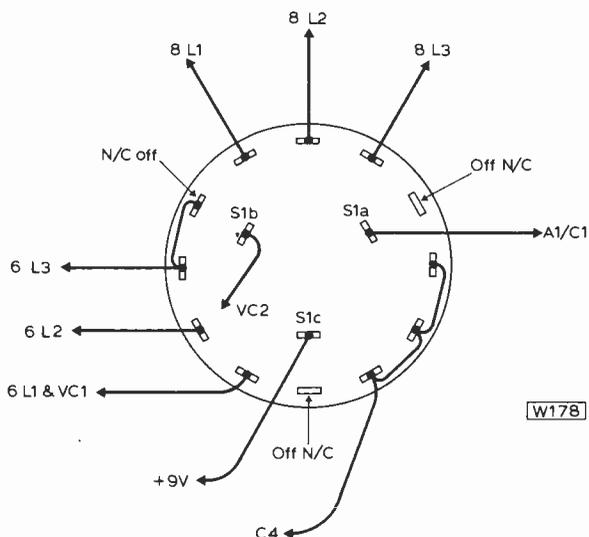


Fig 2: The three-pole four-way switch S1 is of the rotary type, and front panel mounted.


RFC1 and capacitor C5. This will work satisfactorily with receivers having a high nominal aerial input impedance. With receivers having a low impedance, overall gain can be increased by using an impedance matching coil, but this would either have to be tuned in addition to the aerial coils, or be a broad-band device.

When using the unit with communications type and similar receivers, it was found necessary to employ a screened co-axial lead to the receiver. The power supply is a small internal battery, the drain being only a few milliamps, depending on the setting of VR1.
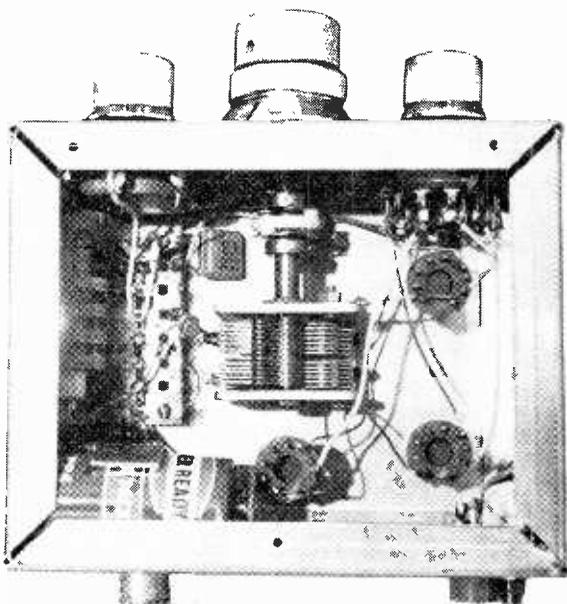
## CABINET

A low-cost and effective screening box and case can be made easily from a 127x102x51mm "universal chassis" with an extra 127x101mm flat plate, which is later attached with self-tapping screws for the top.

As the coil fixing bushes and core-adjusting screws



Plan view of the amplifier with the top plate removed. The ganged capacitor VC1/2 is driven via reduction gearing to provide precision tuning.

of the coils project through the bottom of the case, four plastic feet are required to raise it about 13mm. First drill one 127x51mm member for the front, and fit the switch, VR1, and drive. The bottom 127x51mm flat plate is screwed on, and can be drilled to take VC1/2, which is held with one or two 4BA bolts. Washers or other distance pieces are necessary to raise the gang slightly, to get it level with the drive coupling. The capacitor fixing screws must not be too long, or they will short circuit or damage the capacitor. A final lining-up of drive and capacitor is easy if the drive fixing holes are on the large side.

Nearly all wiring is completed before the sides and back of the case are fitted. The back is prepared by drilling it for the aerial sockets and co-axial outlet and a clip is made to hold a PP4 battery. When the back is fitted, one 4BA bolt is used for an earth connection.


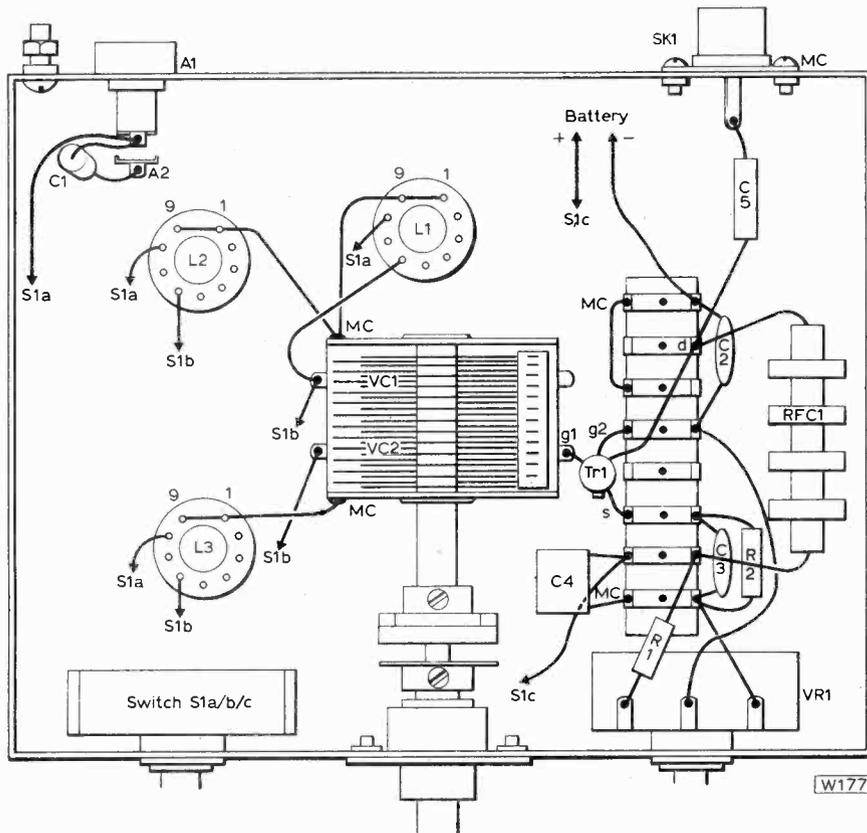


Fig. 3: The schematic shown here gives the location of all components, and the wiring between components and controls.
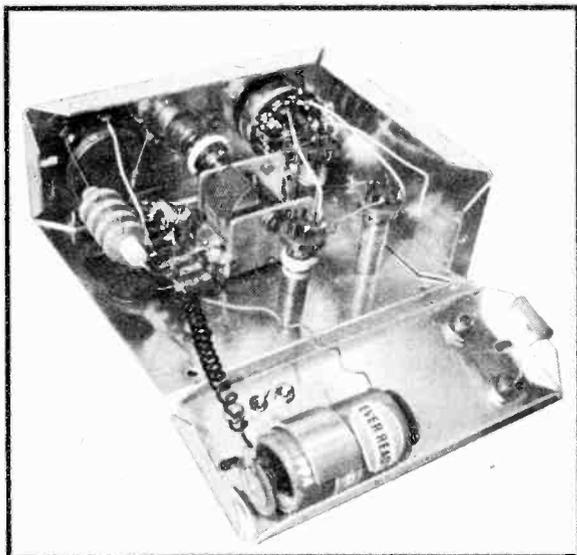
## WIRING DETAILS

Leads are run approximately as in Fig. 3. The tag-strip is raised on 12mm long bolts. As unnecessary coupling between gate 1 and drain circuits is likely to cause instability, G1 is connected directly to VC2. For the same reason, the drain lead is lengthened



The case is constructed from a single Universal Chassis with an extra plate. Size is approximately 101 × 127 × 51mm.

and taken to the tag holding C5 and the RFC, both adjacent tags being earthed as in Fig. 2. Tr1 is gate-protected, and no special precautions need be taken when fitting it, provided the soldering iron is earthed and overheating is avoided.

The coil pins may need scraping, before soldering. Lengthy heating should also be avoided here, or the pins may move. Connections to the switch can be seen from Figs. 2 and 3. All these leads must be reasonably short and direct.

When the sides and back are fitted, connections can be made to A1, A2 and the co-axial socket. The battery is placed with its positive end toward L1.

Earthing is provided by a terminal, or by the co-axial lead to the receiver. Having the latter unnecessarily long may reduce signal strength in some cases.

A frequency scale for the tuning need not be provided, as the amplifier is simply tuned to bring about an improvement in signal strength. With the unit switched to the Range needed for the receiver frequency, tuning should be found to peak up signals considerably. This will be most apparent with weak signals, or with the receiver AGC off. If the receiver has a tuning meter, this will show correct tuning. The coil cores are set to give coverage approximately as described. Exact coverage is not important, provided the ranges overlap slightly.

Should whistles accompany reception, especially with VR1 at maximum gain, Tr1 is oscillating. This is most likely when using an unshielded receiver aerial lead, especially if this is near the aerial connection to the unit. Tuning the booster should be found to peak up signals or aerial noise but not cause heterodynes or oscillation.

PW

# TAKE 20

DAVID ANDREWS

## No. 74 SNAP MACHINE

A series of simple transistor projects, using not more than twenty components.



### ★ components list

R1	22k $\Omega$	R6	4.7k $\Omega$
R2	22k $\Omega$	R7	22k $\Omega$
R3	100k $\Omega$	R8	100k $\Omega$
R4	470 $\Omega$	R9	470 $\Omega$
R5	4.7k $\Omega$	R10	22k $\Omega$
All $\frac{1}{2}$ W 10%			
LED1/2 MV5025 (or general purpose LED)			
Tr1	BSY95A		
Tr2	BCY71		
Tr3	BCY71		
Tr4	BSY95A		
S1/2	push-to-make buttons		
S3	push-to-break button		
S4	single pole on-off		
Veroboard, PP3 battery and connectors. Suitable case, about 130 x 65 x 40mm.			

THERE have been lots of designs for simple Snap indicators published. Most, however, suffer from the problem that indication of the winner only lasts as long as the competitor presses his button. For that reason the following design has a built-in memory which ensures that the winner is indicated for an indefinite period until a reset button is pressed.


For the benefit of those who have not come across a Snap indicator before let's briefly explain the object and principle of operation. For games of skill involving two people it is sometimes desirable to find out who answers the question first. Before attempting to answer, the person has to commit himself to answering by pressing a button which lights a lamp and inhibits the opponent's button and lamp from operating.

The psychological impact of the Snap indicator

enhances a game's excitement considerably. The indicator could equally well be used in conjunction with the classical "Snap" card game.
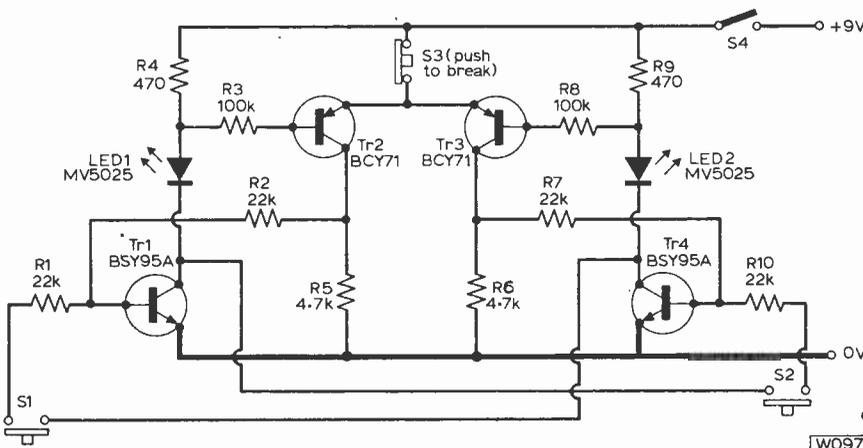
### Flip-flop circuit



Inspection of the circuit will show that Tr1 and Tr4 form a simple flip-flop which becomes cross-coupled when either of the push-buttons S1 or S2 is closed. This action illuminates the LED on the side of the push-button in question and prevents the opponent's LED operating. This circuit differs from many others by the inclusion of Tr2 and Tr3 which respectively act as "latches" to Tr1 and Tr4. If S1 is depressed Tr1 switches on and LED1 lights up. The collector potential of Tr1 falls to zero thus preventing any base current drive to Tr4 inhibiting the other player's



Complete circuit diagram of the Snap Machine, showing flip-flop Tr1 and Tr4, and latches Tr2 and Tr3.

W097

# Pw TECHNIGROSS PUZZLE No.13

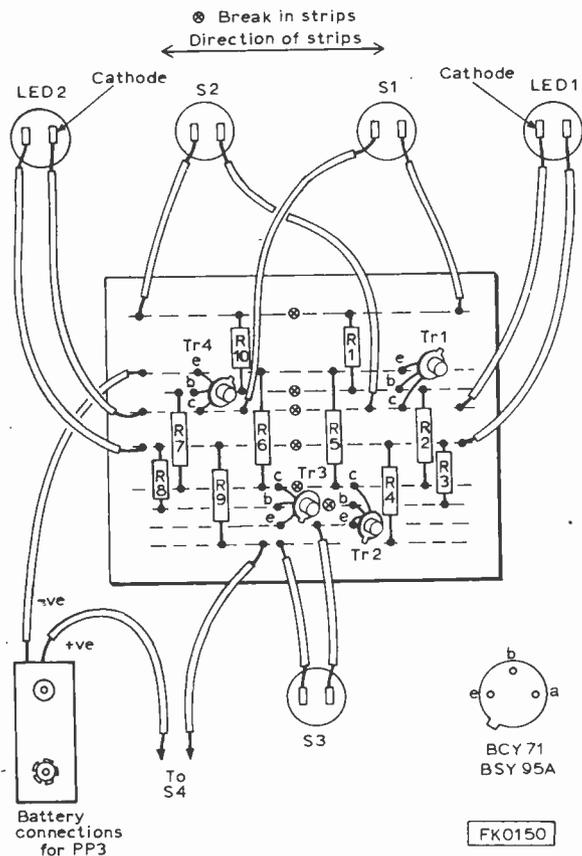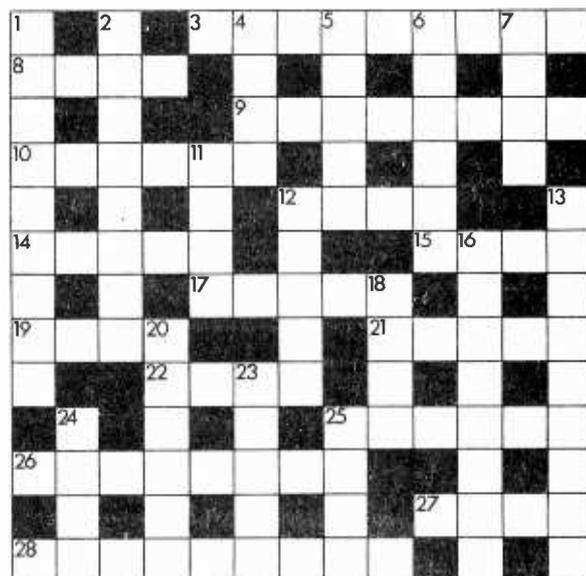

Component layout of the Veroboard panel and wiring to the switches and LED'S. The size of the board is for guidance only.

circuit. The potential at the positive end of LED1 also falls towards zero and this provides a source of base current for Tr2 which is a PNP device. The collector voltage of Tr2 rises towards the positive supply rail providing an alternative source of base current to Tr1 through R2.

If the player's finger is removed from the push-button this alternative supply of base current keeps Tr1 switched on and LED1 illuminated. At the same time the circuitry around Tr4 and LED2 is still inhibited, the only way to switch LED1 out and reset the circuit for another attempt is to break the circuit between the emitters of Tr2 and Tr3 and the positive rail, with the normally closed pushbutton S3.

## Board layout

Provided the layout is carefully followed there should be no problems in the assembly of this circuit. Use normally open push-buttons for S1 and S2 and a NORMALLY CLOSED one for S3. It is important to connect the LEDs with the right polarity. The CATHODE of the device should be connected to the collector of its driving transistor. Using the specified devices the cathode end can be identified by a very small indent on the base of the red plastic or by the fact that there is a wider shoulder on the top of the cathode lead-out wire. When using other LEDs check the polarity carefully. Pw

### ACROSS

- 3 Grateful for this lack of fidelity? (9)
- 8 Spoken part chorally introduced? (4)
- 9 Steamiest form of radio? (8)
- 10 Untrue of Dylan's radio play? (6)
- 12 Drily cut off but I shall shortly be heard! (4)
- 14 Gets the message and sticks to the script! (5)
- 15 Cine movement in southern France? (4)
- 17 Demand precision in complex acting? (5)
- 19 Coverage of the first garden programme? (4)
- 21 I love her broadcasting manner (5)
- 22 River said to be in slow motion (4)
- 25 Set off because of the French component? (6)
- 26 A tuner in civil aviation? (8)
- 27 One piece heard from the deepest bass? (4)
- 28 He sings of a drink and a lake (5, 4)

### DOWN


- 1 How to get on without feedback? (9)
- 2 Programme that takes the broader view? (8)
- 4 Toy with this in Children's Hour? (4)
- 5 A giant in Welsh programmes? (5)
- 6 & 20 Down She's on the air fitfully (6, 6)
- 7 Actors gloomy over this? (4)
- 11 The language you hear on Irish radio! (4)
- 12 Its creation may be quite a project? (5)
- 13 Welcome the end of transmission? (9)
- 16 An impressionable comic? (8)
- 18 Pitch of an oscillating note? (4)
- 20 See 6 Down
- 23 Kind of breakthrough the talkies made? (5)
- 24 He mustn't miss a word! (4)
- 25 A bit of percussion in our hearing? (4)

FOR AMUSEMENT ONLY  
ANSWERS NEXT MONTH

# SPECIAL PRODUCT REPORT

# BI-PRE-PAK
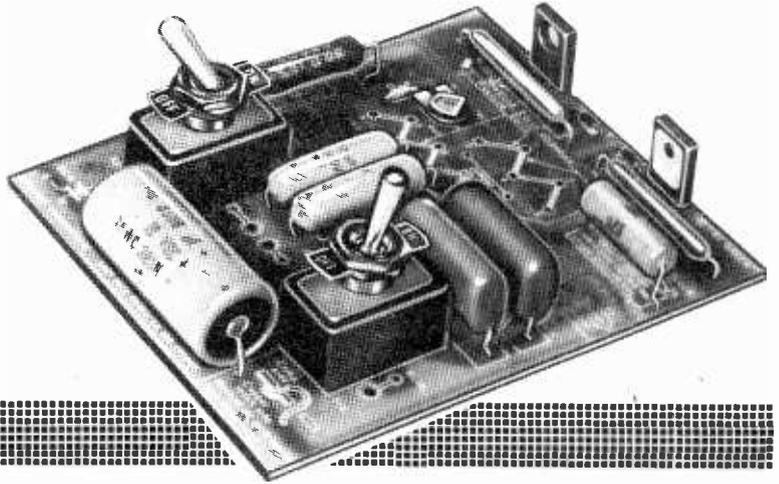
## 'Super Spark' CAPACITY DISCHARGE IGNITION KIT



In case you do not feel like wading through this review to the very end we will have the conclusions first! This kit is easy to assemble and to fit to a car. It worked first time and starting the car is much easier now, especially in cold weather. Is it a good buy? At £7.96+8% VAT it certainly is!

The circuit employed is similar to that which appeared in PW in June 1971, repeated in June and July 1972. However there are a few refinements which are very much worthwhile, all concerned with extra reliability. A two-transistor oscillator working at an audio frequency uses the primary winding of a transformer, the secondary feeds a bridge rectifier producing around 350V DC output. This is applied to a thyristor, the gate of which is triggered by the car's contact breaker on the distributor. The 350V pulse is fed via a 1 $\mu$ F capacitor to the primary of the coil. In case you are worried about 350V being applied to the 12V coil it should be pointed out that 350V is roughly the back voltage developed by the primary winding when the 12V supply is broken by the contact breaker, the basis of the ordinary ignition system.

### INFO

The general information sheet supplied with the kit tells me that a Mr. Kettering was responsible for the original system some 60 years ago, so I've learned something! This sheet is full or useful information but unfortunately it is poorly reproduced in a very small type face, the explanatory diagrams being almost unreadable. Bi-Pre-Pak are not alone in this sad habit of neglecting the all-important "gen" accompanying electronic equipment generally and kits in particular. It may seem to the seller to be an economy, saving a few pence in this manner, but I can assure all those guilty that they are making a big mistake. The second information sheet supplied deals with the assembly of the kit and installation instructions. This is better produced but even so the circuit diagram was broken up in parts due to poor reproduction. Mr. Davis of B-P-P has assured me that this matter and a few spelling errors are being attended to.

However, it must be said that the printed circuit board is one of the best ever seen. The amount of information printed on the board makes the aforesaid circuit diagram almost superfluous! The PCB was assembled in a couple of hours, without going mad. The ends of all component leads were scraped clean whether they needed it or not. An old habit, but it pays off, ensuring a good soldered joint every time. Little sketches of the transistors, diodes and the thyristor on the circuit diagram and the PCB eliminate any possible error here when it comes to wiring them in.

During assembly the PCB was laid across the open top of the die-cast aluminium box, a great help. This box may seem to be rather extravagant, representing a fair part of the cost of the kit, but it does have an excellent seal all round, rather important considering the muck that can be found in the engine compartment of the average car! To aid the sealing a piece of thin plastic sheet was interposed when the lid of the box was finally screwed down.

### ANTI-THEFT

To my mind the biggest feature of the kit, not sufficiently underlined by B-P-P, is the ability to switch back to normal ignition at any time thus eliminating that fear in the back of the mind that the electronic ignition might let you down one day! It is important to note that if the switches are placed in opposite positions the car is totally immobilised, which is much easier than removing the rotor from the distributor! These two switches are mounted on the PCB and used to mount the board on the lid of the box. The neon lamp protruding through the lid is one of those little "extras" that instil confidence, indicating that the unit is producing the 350V required, further confirmed by the high pitched whistle from the oscillator indicating that all is well.

### INSTALLATION

On applying 12V from a car battery in the workshop, nothing happened! No current was being drawn by the unit. A check revealed that the fuse had been omitted! This is a piece of fuse wire soldered across two points on the PCB, thus saving a fuseholder. The fuse duly fitted, the unit worked at once producing the 350V output at the rectifier. The PCB can be wired for positive or negative chassis but it should be noted that the black wire goes to the chassis regardless of the chassis polarity. The PCB is **not** electrically connected to the box so this lead must not be omitted.

The unit was fitted to a Triumph Herald 12/50 of 1965 vintage and tested during the very cold spell in February when temperatures were below freezing for several days on end. The box was bolted to the left-hand vertical panel

*continued on page 60*  
The photograph in the heading shows the printed circuit board which is fitted to the lid of the die-cast box by the locknuts on the switches. As can be seen the PCB is well annotated. The zig-zag lines are the alternative links for positive or negative chassis connections. The two transistors are mounted vertically at the extreme righthand end of the board.

# AF Signal Source

W. MOONEY


THE rapid decrease in the price of CMOS (4000 series) digital integrated circuits, and the amazing reduction in quiescent power consumption compared to the popular 74 series, makes experiment with these devices a tempting proposition. Quiescent power consumption is of the order of 10nW per gate for the 4000 series and is therefore negligible, whereas consumption by the 74 series is about 10mW per gate. Despite conflicting requirements of fast switching speed and low power consumption, these devices will still work well up to 10MHz.

The signal source described here, uses only one IC which contains two 3-input NOR gates and an inverter. The source provides a square-wave of about 1kHz at a voltage of 99% of the battery voltage. Two outputs are provided, one via a 1μF capacitor which should give a good square wave into high impedance loads, and a second output via a 100pF capacitor, picking off the RF harmonics for signal injection.

The current drawn from the battery is less than 30μA and increases with the application of a load to the output. The device will continue to work until the supply voltage drops to below 3V, when the off load current will be about 10μA.
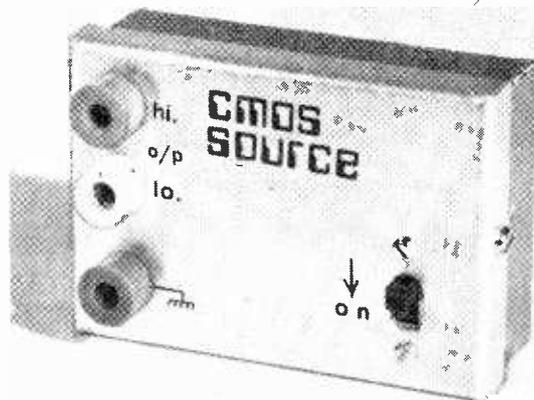
## Power consumption

In a normal N or P channel MOS gate as in Fig. 1a the quiescent power consumption is high because a load resistor is used. Therefore in this instance when the output is in the low state a current must flow through the resistor in order to decrease the output voltage. This resistor must be fairly low so as to drive the following stage when a low output is required. But if too low, the current required to produce a low state will be too high. A compromise is therefore arrived at. If the load resistor is replaced by a MOSFET of opposite polarity (Complementary)



to the lower MOSFET as in Fig. 1b the need for such a compromise is obviated as this load fulfils both requirements.

In the high output state the lower MOSFET switches off becoming, in effect, a high resistance of about  $10^{13}\Omega$  and the top MOSFET becomes a low resistance of about 300Ω. When a low output is required the resistors effectively change place, the upper MOSFET switching off and the lower MOSFET switching on. In the complementary MOSFET circuit (CMOS) the power consumed in the high or low state is therefore negligible and the great majority of the power is consumed during switching.

For a brief period during the switching action both MOSFETS will be equally on and will have a relatively low resistance. At this instant the current peaks to typically 1.5mA with a 10V supply rail. When the CMOS gate is in a normal digital environment carrying step pulses, the power consumed due to this effect is practically zero. The consumption is then purely due to the capacitance of the load, typically 5pF per gate.

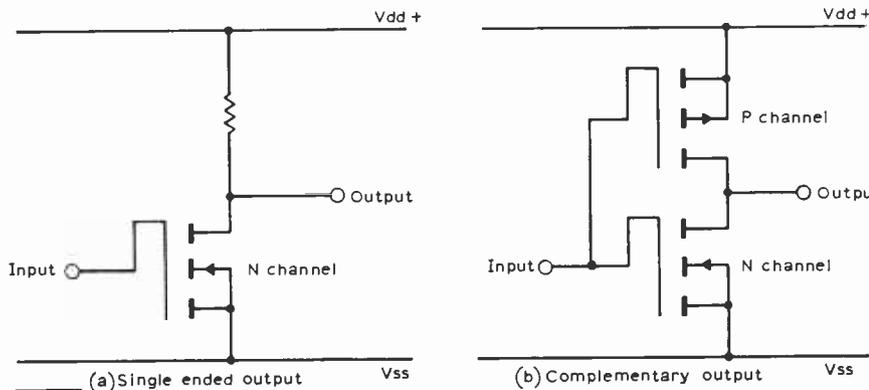


Fig. 1a: A normal N channel MOS gate with a single ended output. Fig. 1b: A similar device to that shown in Fig. 1a, but with the load resistor replaced with a P channel gate. This now forms a complementary output.

FK158

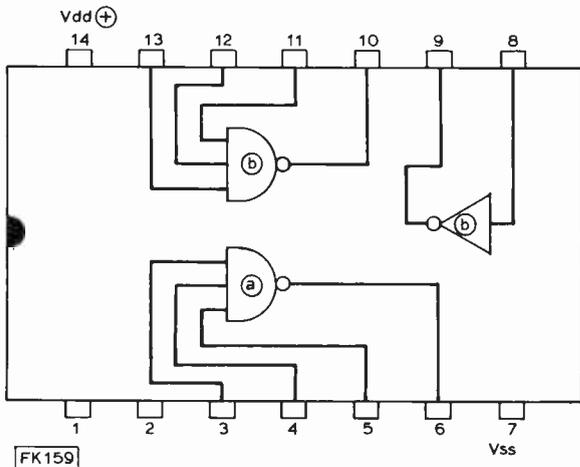


Fig. 2: Internal configuration of the CD4000. Gates 'a' and 'b' are NOR gates and 'c' is an inverter.

## Total power

The total power consumed ( $P_t$ ) by a particular gate carrying regular step pulses is therefore the sum of the quiescent power ( $P_q$ ) in the high or low state, and the switching power. The switching power is dependent on the frequency ( $f$ ), the voltage difference between the high and low states (approx. the supply voltage  $V_{dd}$ ) and the capacitance of the load ( $C$ ). Bringing these together we get:

$$P_t = P_q + CV_{dd}^2 f$$

This is arrived at from the familiar expression for the energy stored in a capacitor  $\frac{1}{2}CV^2$ .

In the source described here the conditions are somewhat different as the inputs to both gates are part of a timing circuit. This circuit slows down the transition through the high current portion of the transfer characteristic, giving a higher current drain than would be expected from the above expression. However at a maximum of  $30\mu A$  it still compares very favourably with an equivalent circuit using discrete bipolar devices.

## Circuit operation

The internal layout of the CD4000 IC used in this circuit is shown in Fig. 2, the parts marked (a) and (b) are the NOR gates and (c) the inverter. The circuit of the oscillator is shown in Fig. 3, all inputs to each gate are strapped together, the operation now being the same as that of the inverter where a low input produces a high output and vice versa. The circuit will be recognised as a multivibrator type of oscillator, the frequency determining components being  $C_1/R_1$  and  $C_2/R_2$ . In this circuit  $C_1 = C_2$  and  $R_1 = R_2$ , thus giving a squarewave of equal mark/space ratio.

Circuit operation is best understood by freezing the cycle at a point in time when the output of gate (a) has just jumped from zero up to nearly the supply voltage. The voltage on the input to (b) will follow this rise since  $C_1$  is discharged and the output of (b) will now be zero. The voltage on the input to (b) will slowly drop towards zero as  $C_2$  charges up, and at some point (about 40% of the supply voltage) will cause the output of (b) to jump quite rapidly to

## ★ components list

### Resistors

R1 10M $\Omega$

R2 10M $\Omega$

All resistors 10%  $\pm W$

R3 1M $\Omega$

R4 see text

### Capacitors

C1 100pF SM

C2 100pF SM

C3 100pF SM

C4 1 $\mu F$  50V elect.

### Semiconductors

IC1 CD4000

### Miscellaneous

S1, miniature slide switch. Aluminium box 76 x 50 x 25mm type AB12, available from Home Radio. Printed circuit board 45 x 25mm. Three 3mm plugs and sockets. Three 1.5V cells, type D23.

the high state. As  $C_1$  is discharged, the input to (a) will follow this increase causing the output of (a) to drop. It will now remain low until  $C_1$  charges through  $R_1$  to the point where the output of (a) goes high once more and the cycle repeats. At the times of the cycle when the output of (a) or (b) drops to a low state the associated capacitor will be charged up and this charge results in a negative voltage appearing on the following input. A lucky spin-off of the input protection circuitry now occurs as this negative potential forward biases certain diodes thus

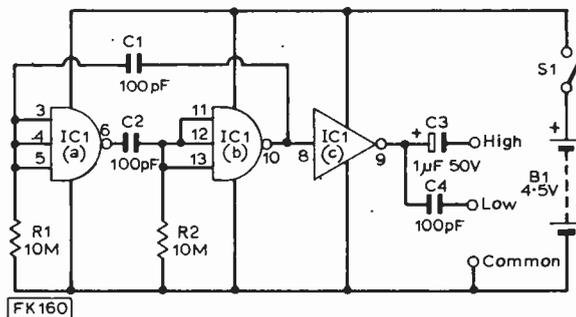


Fig. 3: The above drawing shows the complete circuit of the oscillator. With the component values shown, the output frequency is about 700Hz.

quickly discharging the relevant capacitor.

The output from gate (b) is passed through the inverter which isolates the oscillator from the load and squares up the waveform. The supply line is not decoupled as it is quite unnecessary and tends to make starting difficult by removing the switch-on kick. No specific arrangements have been made for starting but should the oscillator stop for any reason, simply switching off for a few moments, and then on again, will usually start the oscillator running.

## Construction

The device is constructed in a ready made aluminium box measuring 76 x 50 x 25mm. The PCB, Fig 4 switch and terminals were attached to the lid of the box as is the power source which consists of three 1.5V cells, type D23, connected to give over

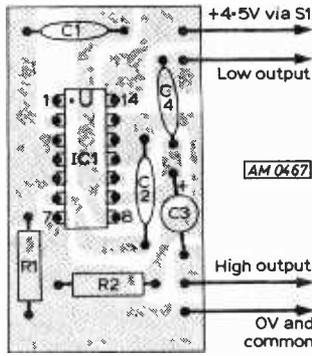
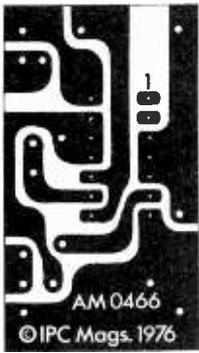


Fig. 4: PCB showing foil side to the left, and component overlay to the right. The board is shown full size.

4.5V when new. These small cells are not very popular but a little searching is worth while as they offer a considerable saving in space, being only about 10mm in dia. and 30mm long. A long life is expected of these batteries and they are therefore glued together and then to the case, making the connections by direct soldering. If it is decided to use mercury cells, direct soldering should be avoided for safety reasons.

The IC was found to be remarkably robust as the inputs are protected by an array of zener diodes to prevent static build up. However in the interests of good practice the soldering iron should be earthed and precautions taken to prevent personal static build up. The timing capacitors are silvered mica but any low leakage type will do. The output capacitors should have a suitably high working voltage if work with valve or high voltage transistor equipment is envisaged.

### The source in use

The output frequency of the device with the component values given here is about 700Hz. The square-wave is quite good with harmonics extending well into the short wave region. The output voltage is dependent on the supply voltage and the device will work well down to below 3V. Under 3V, however, starting becomes increasingly difficult. The quiescent current consumption at 3V is less than 10µA.

The device has been used for fault finding in AM receivers and audio amplifiers, although the use of a square-wave generator does not end here, especially if an oscilloscope is to hand. For example, the action

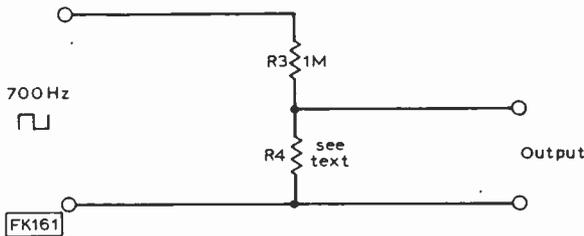


Fig. 5: The output amplitude of the Signal Source may be a little high for some purposes, and this simple attenuator should be used when necessary.

of tone controls and various filters can then be observed directly. One fundamental property of a symmetrical square-wave is that the RMS and aver-

age voltage are equal. This property was demonstrated with a prototype when the battery voltage was found to be 4.8V (20k ohm/Volt meter), the output indicated on the AC range was exactly 2.4V RMS.

Some form of potential divider should therefore be used before injecting the signal into the more sensitive stages of audio amplifiers, otherwise serious overload will occur giving misleading results. A simple attenuator as shown in Fig. 5 will be adequate, the value of R4 being altered as required. For example with 2.4V input and R4=1kΩ the output will be 2.4mV. Some levels to expect when dealing with AF stages are as follows:

Output from magnetic cartridge .....	3mV
Output from ceramic cartridge .....	80mV
Output from crystal cartridge .....	300mV
Output from cassette replay head .....	0.5mV
Input from, tape, tuner, or aux .....	100mV

Although it should be remembered that the battery life will be reduced by applying heavy loads to the source, it is possible to drive an 8Ω loudspeaker directly although this hasn't been tried for more than a few seconds. Dw

## BOOKS RECEIVED

### RADIO CONSTRUCTION FOR AMATEURS

By R. H. Warring

Published by Pitman Publishing Limited,  
Pitman House, 39 Parker Street, London WC2B 5PB

120 pages 21.5cms x 14cms.

Price £2.50

THIS book caters for both beginner and the enthusiast with some electronics experience. It sets out the theory of radio transmission, describes working components and circuit construction and provides over 30 working circuits. Chapter headings included are: Crystal Sets, More about Tuned Circuits, Transistors, Bias and Stabilisation, Regenerative and Reflex Receivers, FET's and IC's. etc.

### PRINCIPLES OF TRANSISTOR CIRCUITS (Fifth Edition)

By S.W. Amos

Published by Newnes-Butterworths,  
The Butterworth Group, 88 Kingsway,  
London, WC2B 6AB

320 pages 21cms x 14cms

Price £3.20

THIS Wireless World book has been updated quite extensively from the 4th edition by the inclusion of information on field-effect transistors and the expansion of the treatment of switching circuits. Chapter 1, Semiconductors and Junction Diodes deals with the basics of semiconductor physics and the principles of transistor operation. Following chapters include such subjects as Common-base and Common-gate Amplifiers, Bias and DC Stabilisation, Large Signal AF Amplifiers, IF Amplifiers, Pulse Generators and Further Applications of Transistors and other Semiconductor Devices.

Since Volume 1 was published back in 1959, Principles of Transistor Circuits has been regarded as a standard text book by schools and colleges and this latest edition brings this respected work right up to date so that it will still be acceptable as a standard course text.

# DORAM


## A PROFESSIONAL DEAL FOR AMATEURS

\*ORDERS BY RETURN OF POST \*NO QUIBBLE REPLACEMENT PART SERVICE  
\*QUALITY BRANDED PRODUCTS \*FREE UP DATE INFORMATION SERVICE

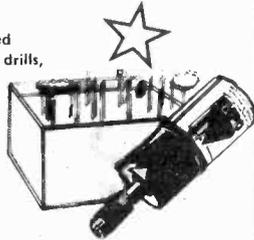
### TOOLS

The handy EXPO 12V d.c. drill is supplied complete with drill kit containing 4 small drills, two spare collets, two cutters, wire brush, soft buffer, grindstone and 9 various milling and reaming tools.

Drill & kit £9.50 + s  
Kit only £4.75 + s



### ORYX 60W SOLDERING IRON

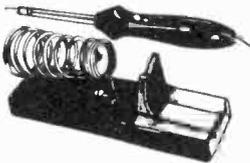

Temperature can be altered between 200-400°C.

Iron 240V £6.90 + s  
Stand £2.80 + s

### ISO-TIP CORDLESS IRON

Mains and 12V d.c. versions available  
£11.50 + s



### DE-SOLDER TOOLS

Three high-suction models available

SR2 £6.20 + s  
SR3 £5.20 + s  
SR3AS £4.80 + s  
Spare nozzle 60p ea. + s  
Please state type



### NICKEL-CADMIUM RECHARGEABLE CELLS

	Sim. to dry cell	nom. capacity	charge cur. (mA)	
HP7	0.5Ah	50	£1.10 s	
None	1.2Ah	100	£1.24 s	
HP11	2.0Ah	200	£1.80 s	
HP2	4.0Ah	400	£2.70 s	

### ELECTRONIC IGNITION UNIT

- \* High performance
- \* For 2 & 4 stroke engines
- \* Improved start/running
- \* 'Crisper' throttle response
- \* Reduce battery drain

Neg. earth or pos. earth

£15.00 + s

Please state type required



### BATTERY ELIMINATOR

Switched output 6, 7.5 or 9V at 250mA.  
D.C. pos. or neg. earth  
£3.15 + s



### SEMI-CONDUCTOR DEVICES

#### RECTIFIERS


IN 4001 5p ea.)  
IN 4002 6p ea.) + s  
IN 4003 6p ea.)

1.0A bridge (400V) 32p + H  
1.6A " (200V) 48p + H  
1.6A " (800V) 70p + H  
2.0A " (200V) 72p + H  
2.0A " (600V) 90p + H


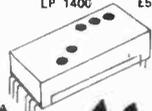
### MULLARD MODULES

LP 1173 £6.10 + H  
LP 1184/2 £6.58 + H  
LP 1185 £4.50 + H  
LP 1186 £6.32 + H  
LP 1400 £5.15 + H



## BIG PRICE REDUCTIONS

### TRANSISTORS

BC 107 12p s  
BC 108 11p s  
BC 109 12p s  
BFY 50 20p s  
BFY 51 19p s  
BFY 52 20p s  
2N 3055 62p s  
2N 2646 94p s  
TIP 2955 £1.14 s  
TIP 3055 61p s  
BC 237B 11p H  
BC 238C 10p H  
BC 239C 12p H  
ZTX 107 10p H  
ZTX 108 9p H  
ZTX 109 12p H  
ZTX 300 13p H  
ZTX 500 14p H  
MJE 340 62p H  
TIP 31A 36p H  
TIP 32A 40p H  
2N 381A 27p H  
3N 141 65p s  
CS 715 18p H  
10 for £1.50 H

(Similar to 2N 3819)  
BF 180 40p s  
BRY39 72p s



I.C.'s  
T05 Reg £1.10 s  
MVR 5 £1.55 s  
MVR 12 £1.55 s  
MVR 15 £1.55 s  
LM 339K £1.95 s  
7805 £1.50 s  
7812 £1.50 s  
7815 £1.50 s  
7824 £1.50 s  
215V D.I.L. £2.82 s  
TBA 231 £1.50 H  
TBA 800 £1.20 H  
TBA 810S £1.30 H  
TBA 820 £1.00 H  
ZN 414 £1.30 H  
ZN 424 £1.25 H  
741 Op-amp 36p s  
747 Op-amp (Dual 741) 95p s  
748 Op-amp 48p s  
555 TIMER 56p s  
556 (dual 555) £1.10 s  
HA 1156 £1.60 H (similar to MC1310P)  
ORP12 72p s  
8A Triac £1.18 s  
ZN 1034E £4.70 s

## 'INTERNATIONAL 25'

Build yourself a BIG SOUND amp at a budget price



As featured in 'ETI' Oct. 75 edition

#### FEATURES

- \* Triple Op-amp pre-amplifier
- \* Power 'Darlington's'
- \* Modern styling
- \* 25W per channel into 8 ohms.

Complete kit with assembly instructions

Overseas orders £34.50  
S.A.E. for full spec.


**£29.95 + £7.48 VAT**

### BOOKS (Z)

Hi-fi hints and tips 38p ea.  
Covers international transistor selector £2.95 ea.  
Electronic circuit design handbook — a must for electronic enthusiasts £4.50 ea.
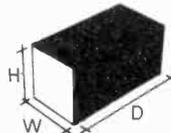
### 'SAMOS' CASES

Low-cost blue cover and white base PVC steel cases



S1 50W x 50H x 100D £1.03 + s  
S2 100W x 50H x 100D £1.17 + s  
S3 150W x 50H x 100D £1.31 + s  
S4 50W x 75H x 125D £1.47 + s  
S5 100W x 75H x 125D £1.68 + s  
S6 150W x 75H x 125D £1.97 + s  
S7 200W x 75H x 125D £2.19 + s

#### SPECIAL OFFER! !

If catalogue ordered simultaneously with order for SAMOS cases - case price less 25%

### CONDITIONS OF SALE

All prices are ex-VAT  
If affixed with s add 8%  
If affixed with H add 25%  
Z = Zero rated  
Package & Postage free for orders over £3.00  
Overseas orders add 15%  
Cash with order. Cheques/Postal Orders to Doram Electronics Limited, P.O. Box TR8, Leeds, LS12 2UF  
Small order handling charge of 40p for orders under £3.00

### DORAM'S NEW CATALOGUE — THE AMATEURS GOOD COMPANION



**ONLY 60p**

inc. post & packing.  
Free up-date service until Aug. 1976.

## DORAM

An Electrocomponents Group Company

NAME.....


ADDRESS.....

POST CODE.....

I enclose 60p. Please send me by return my Doram Catalogue. (Overseas orders except B.F.P.O. please add 30p for post and packing surface only).
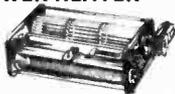
### TANGENTIAL BLOWER HEATER

240V 2KW can be switched for two speeds and 1KW Robust and efficient. Aperture 7 1/2" x 12" size overall length 10". Price £4.25 plus p. & p. 75p.



### DIGITAL DISPLAY INDICATOR

by KGM, Type M4, window size 1/2" wide, 1 1/2" high, depth 1 1/2", height 3 1/2" plus front flange (1/2" top and bottom). This is an Acrylic edgelit unit illuminated by 12V fluorescent tube bulbs (as our min. lamp type D) Currently sold at £14.00 plus, our price £3.95 inc. lamps, plus p. & p. 35p.



### MINIATURE LAMPS

Type (Dia.)	Size	Volt/Curr.	Type (Dia.)	Size	Volt/Curr.
A	3MM	5-6V 60 MA	D	3MM	2-5V 360 MA
B	4MM	4V 250 MA	E	4MM	5-6 60 MA
		5V 60 MA			6-3 200 MA
		12V 40 MA			14V 40 MA
		12V 100 MA	F	4MM	2-7V 80 MA
		14V 75 MA			12V 160 MA
		28V 40 MA			14V 80 MA
C	5MM	28V 40 MA			


Small telephone jack type 6 or 24V.  
Price: Types A-F £4.00 for 25, 50 and upwards 13p each Type G 45p each, p. & p. 20p per order.

### RIBBON CABLE

4 way side by side P.V.C. 7 strand red-green-blue-yellow (miniature) 50 metre reels £4.50. 250 metres £20 P & P 70p 50 metres. £1.50 250 metres.
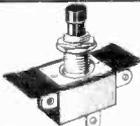
### CENTRIFUGAL BLOWER

240V powerful, efficient by Universal Electric. 3,100 r.p.m., Inlet dia. 4", outlet approx. 2 1/2" x 2 1/2", overall width 5", overall dia. 5 1/2". Price £4.75 plus p. & p. 75p.



### ARROW SWITCH

Press on/press off single hole fixing SP ST size 1 1/2" x 1 1/2" preslite extends 1/2". Rated 2 1/2 amps. Robust. Price for 5 (min. qty.) £1.75. 10 or more 30p each, p. & p. 30p for 5.

### MEM LIMIT SWITCH

Snap action 5 amps at 240/410 A.C. size base 3 1/2" x 1 1/2" x 1 1/2" plus heavy duty roller plunger 1 1/2" ext. or 1" when compressed. Very robust for fireless operation, weather proof. Price £2.20 plus p. & p. 25p.

### RELAYS

Octal base 2 C/O 6 amp contacts following voltages: 12V a.c. 48V d.c. 110 d.c. 230 a.c., at £1.25 each plus base 15p postage and packing 15p. 11-pin 3 C/O 6 amp contacts, following voltages: 115 a.c. 48 d.c. 24 d.c. all at £1.50 each, base 15p plus 15p p. & p.




### 10 K.W. ISOLATION TRANSFORMER

Prim. 200-240V sec. 120-0-120V, size 18" x 15" x 26" high, weight approx. 250lbs. Price £110 Inc. VAT delivery charge at cost.
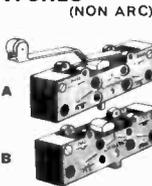
### CROUZET MICRO SWITCHES

Types A/B no. 83-112 n/o or n/c as desired, rating 5 a 240V, size 1 1/2" x 1 1/2" x 1 1/2" high. Can be stacked horizontally or vertically. In this mode, top switch can operate multiples. Type A has straight through plunger, whilst Type B is encased at bottom. Makers price approx. £1.40 each, our price 45p each (min. qty. 5) plus 15p per roller (as shown) plus 20p p. & p.



Type C miniature no. 83-132, size 1/2" x 1/2" x 1/2" high, plus tags, 5 a 250V. Price 30p each (min. 5) Lever 1/2" long 19/16" long either type 8p each, plus p. & p. 20p.



Type D similar to Type C, but with tags underneath, uses same lever as Type C or can be banked horizontally and double lever (as shown) supplied at 12p. Prices as type C.



Type E no. 83-131, 10 a 250V size 1 1/2" x 1 1/2" x 1 1/2" high, 30p each (min. 5) plus lever 1 1/2" long, 8p each plus p. & p. 20p each.



### NORPLEX COPPERCLAD FIBREGLASS

First grade material. 1 & 2 oz. copper size 43" x 37" thickness double sided 1/32" 1/16" 3/64" 2/32" single sided 1/32" & 1/64" all types £10 per sheet. Carriage £2 one sheet plus 50p additional sheets (G.B.).


### THUMBWHEEL EDGE SWITCHES

(Plessey) ten position 0-9 (single pole ten way) modular, any number may be banked. Contact rating 2a. A.C. or D.C., colour black, size overall 52.58 high x 12 wide x 49 mm deep. P.C. pitch, 156. Price £1.50 per unit, end mounting cheeks £1.00 per pair, p. & p. 30p any order.


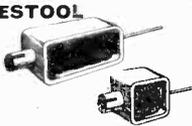
### SOLENOID BY WESTOOL

240 a.c. type MM6 31b pull. 2 1/2" x 1" x 1 1/2". Travel 1". £1.50 each, plus p. & p. 25p. 240 a.c. type MM4 21b pull. 1 1/2" x 1" x 1". Travel 1". £1.25 each, plus p. & p. 25p.



### MAINS SOLENOIDS

This little unit gives vertical lift of approximately 1in. through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2" 240V, a.c. Pull at coil is approximately 1lb. Price £1.25 plus p. & p. 20p.



### ALL PRICES INCLUDE V.A.T.

Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £10. Therefore, please remit cash with orders below this amount.

### MUFFIN "PANCAKE" FANS

As used in computers and other installations where silent continuous efficient cooling is needed. These fans are 115V, 50Hz drawing only 14 watts 4 1/2" x 4 1/2" x 1 1/2". They can be coupled in pairs for use on 240V dropping resistor can be supplied for 50p. ONLY £8.50 plus p. & p. 50p.



### SPRITE "PANCAKE" FANS

Similar to "Muffin", physically smaller, drawing only 9 watts but still giving extremely high efficiency with minimum fuss. 115V 50 Hz can be used in pairs from 240V a.c. dropping resistor supplied for 50p. Size: 3 1/2" x 3 1/2" x 1 1/2". (Large quantity available, special quotations). ONLY £4.50 plus p. & p. 50p.



### 6 DIGIT 24V d.c. COUNTER

Non re-set 3 watts, size 1 1/2" x 1 1/2" x 13/16". Brand new, Plastic encased. Price £2.25 plus p. & p. 25p.




### SOLDER GUN BY ETP

240V for instant heat and speedy soldering. 100 watts, built in hot lamp. Price £3.50 plus p. & p. 50p.
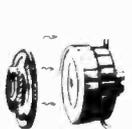
### BENDIX MAGNETIC CLUTCH

A superb example of Electro-mechanics! The main body is in two sections. The coil section is fixed and has a 1in sleeve. The drive section rotating on the outer perimeters. The uniting plate has 1in ID bearing concentric with main section and 18-tooth cog wheel. When energized transmission is extremely powerful, 24V d.c. at 240 MA. Our price just £2.70 plus 30p p. & p.



### PROGRAMME TIMER

12 bank, cam operated micro switches, infinitely variable switching 240V. Speed 15 r.p.m. (4 sec per rev). Price £3.95 plus p. & p. 70p.



### SHADED POLE GEARED MOTORS

110 r.p.m. 240 a.c., high Torque, approximate overall size 3 1/2" x 3 1/2" x 2 1/2" and spindle dia. 1/2". Price £3.50 plus p. & p. 50p.



### SYLVANIA SWITCH

Complete with magnet, normally closed, arm vacuum sealed. 1 1/2" long 1/2" dia. 10 for £2.50, 50 for £11.00, 100 for £18.00 plus p. & p. 30p. for 10 to 100.



### LIGHT DEPENDENT RESISTORS

Matched pairs, Pioneer type 174 similar to orp 12 resistance 1K to 40K, dia 3/8" with 1/8" flanges. £1.50 for two pairs (minimum) 10 or more pairs 50p. per pair plus p. & p. 15p.

### EDGE CONNECTORS (CINCH)

Single contact sockets, 27 way 15, can be cut to length, moveable end mounts, 10 pieces (minimum) for £4.00 plus p. & p. 25p.

# ELECTRO-TECH

COMPONENTS LTD.

317 and 364 EDGWARE RD., LONDON, W2.

Tel: 01-723 5667 01-402 5580

WE ARE OPEN 9-6 MON. TO SAT.

VISIT OUR NEW BIGGER AND BETTER SHOP—NOW OPEN AT 364 FOR A WIDE RANGE OF INTERESTING ITEMS!

## Capacitor Discharge IGNITION

**MAXIMUM PERFORMANCE**  

**MAXIMUM ECONOMY**  

**EASY COLD START**

**SYSTEM I**

Professional photoelectric ignition using L.E.D. light source and reflective disc. This machined aluminium disc gives a timing accuracy far superior to other methods and is simple to fit. Unit housed in diecast box 4 1/2" x 3 1/2" x 2 1/4". Price £18.80 (Kit £16.80) State car/model/measurement across cam lobes.

**SYSTEM II**

Contact breaker model as above less sensor. Price £12.80 (Kit £10.80) M/C Twin unit Price £15.00. S.A.E. for descriptive leaflet — ALL UNITS IN STOCK. Mail orders to CDI Electronic Systems Ltd, 275 Vale Road, Ash Vale, Aldershot, Hants. Demonstration/Callers to Hillside Motors, 292 Carshalton Road, Carshalton, Surrey, telephone 01-642 9973.

## poly-planar

### 20-Watt Full Range Speaker

Completely replaces the conventional cone speaker  
Super-thin construction permits new installation ideas.


Power capability: 40 watts peak. Frequency range: 40 Hz-20 KHz  
Sensitivity: 85 dB/M for 1 watt electrical input. Input Impedance: 8 ohms. Operating temperature range: -20°F to +175°F. Size (WxDxL): 1-7/16" x 1-3/4" x 1-11/16". Weight: 19 ounces.

£8.50 each Stereo pair £16.50  
INCLUSIVE OF VAT AND POSTAGE

## web europa

P.O. Box 9, Ruthin Clwyd

# GOING BACK...

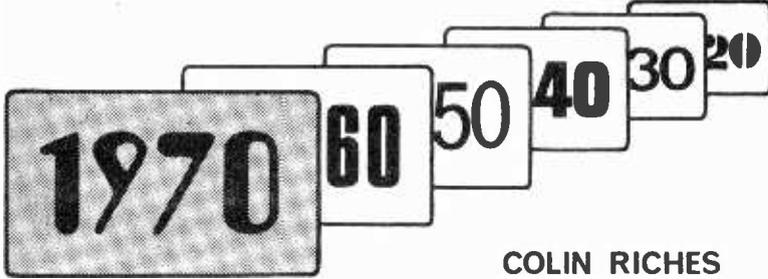

COLIN RICHES

## 'Mystery' Receiver


I HAVE received a letter from one of our younger Going Back enthusiasts—John Narborough, aged 16, from Uckfield in Sussex.

He tells me that he has quite a collection of vintage radio equipment and during his three or four years of being a PW reader, prompted by reminiscences from his dear old dad who used to dabble in radio in the '20s he has become extremely interested in the earlier days of wireless.



He says he is finding—much to his mother's delight—that it is becoming increasingly hard to find items of equipment (that do not have misguided high price tags) with which to "clutter" up the home. Nevertheless, John considers that he has one or two prizes in his collection.

John would like to know if any other Going Back readers could help him concerning the item in the two smaller photographs. The set is built into an oak cabinet which has a drop-down front. Three valveholders are mounted at the top with filament rheostats below. Also included are the usual tuning and reaction controls.

and a reaction control for some external piece of equipment—possibly a frame aerial—even though there are AE and E terminals on the panel. The wiring (it's a pity but a few of the components are missing) indicates that the set is probably an early '20s' design and there is a transformer wound "like a coil in cylinder form", the core of which comprises individual iron wires. Under the detector valve socket (centre) there is a screw-in variable grid leak and coil changing system of plugs and sockets. An engraved "wiper" type switch gives ranges from 200

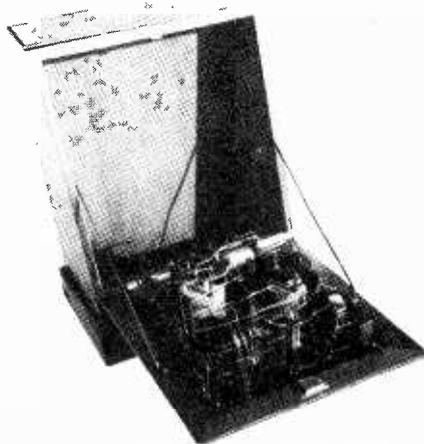

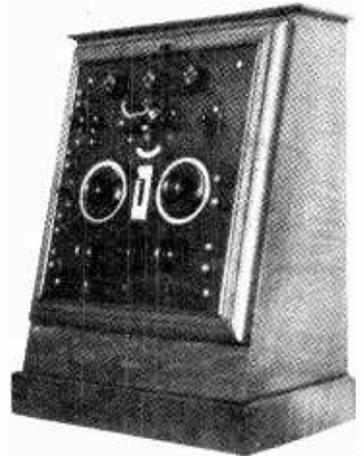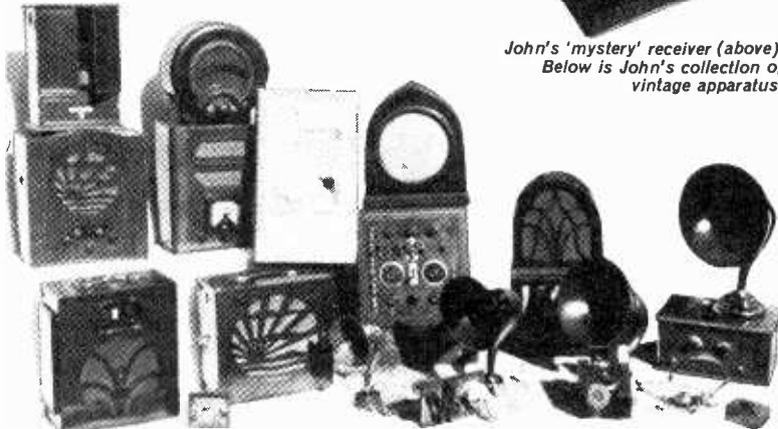John's 'mystery' receiver (above).  
Below is John's collection of vintage apparatus.



External view of the 'mystery' receiver.

to 3000 metres. Each valve holder has switches for its individual power supply.

John passes on a useful tip here—he only managed to decipher the wording on the controls by rubbing the ebonite panel with a cloth dipped in turps. This reveals the mark where the lettering used to be—but only while it is drying.

What John would like to know, if anyone would care to drop him a line is: who was the manufacturer and where do coils/frame aerial fit?

The set does not look home-brewed but could be a "limited quantity" set. The DPDT switches are made from a commercial front knob and a home-machined contact system of brass strip.

The larger picture shows some of John's collection. Creeping off the picture at bottom right is a Brown Microphone Amplifier which he has had working—even though the tone is rather shrill.

Anyone interested can contact John Narborough at *The Orchard, Rocks Lane, High Hurstwood, Uckfield, Sussex, TN22 4BN.*

## Vintage CQ!

### INFORMATION WANTED

... Circuit diagram or the Works Publication WP 137 (mentioned on label giving valve details) of a Burndapt Screened Portable. Valves are PM1HF, PM1A, PM12 and PM252. The set requires a 2V accumulator, 108V HT with 66V tapping and 18V (tapped every 1.5V) grid battery.—*John Hein, 13 Blane Avenue, Blane-field, via Glasgow, G63 9HU.*

Dear Sir,



### Early morning maths

While thumbing through my husband's *PW* (February), I noticed the Editors comments on digital watches. We have had a digital clock for over a year now, and although I can cope with the 24 hour system on it, I am still sometimes frustrated by having to mentally subtract numbers from 60 to find out how long it is to the next 'o'clock'.

My suggestion (I know nothing about the electronic practicability of it) is that we return to the 12 hour system, and that the display reads the minutes first, with 'to' or 'past' in the middle, i.e. 27 past 7 or 29 to 8. This would abolish the need for mental arithmetic early in the morning as the time to get up approaches!

Mrs F R Tasker (Hardwicke)  
PS. What happened to the crossword?

*This is fitted in when space permits—Ed.*

### Crystal controlled pendulum

Your editorial in the February issue of *Practical Wireless* caused me a little quiet amusement.

As a retired airline captain, I am used to learning to accept new instrument faces, hence the digital presentation causes me no pain. However, this does not deafen me to the complaints of the female side of my family ever since I constructed a digital clock. I am sure that quite a lot of people have to make a distinct effort to convert mere numbers

to a more conventional mental picture of time.

A few months ago, I wrote to another journal making such a point and asking if they would publish a circuit which would marry the accuracy of a crystal timer to a balance wheel or pendulum clock. This could be achieved by comparison perhaps, plus suitable correcting impulses. I said I was sure that this would please hobbyists and horologists not to mention their womenfolk! The editor did not agree, hence my amusement.

You, of course, refer only to wrist watches. In this case could not a miniature stepping motor drive conventional hands, as employed, I believe, in certain makes of watch?—E Rodley (Guildford).

### IC DFM

Is it not time to revisit the subject of the Digital frequency meter?

Surely, amongst the readership of *PW* there is someone capable of contributing a device of sound economic sense, from the vast array of ICs now available?—

**B A Martin** (Solihull)

*We hope to be satisfying people, such as Mr Martin, very shortly*  
—Ed.

### Heavy duty charge

As a reader of *PW* for many years and also a keen motorist (DIY), I submit a humble request for an article on a battery charger, something a little more sophisticated than the straight forward trickle charger. I would suggest a charging rate from about 2A to 8A (for rapid charge), and using full wave rectification. Suitable also for 6V or 12V batteries. I'm sure one could be built much cheaper than a commercially bought one.—C. Law (Blackburn)

*(Potential contributors—please note)*

### The price of stock

Reading Mr B. A. Pearson's letter of complaint re transistor prices in the March issue, stirs me from my customary lethargy (and it takes a lot to do that) and

prompts me to put another view which may not be popular with all your readers.

In the first place, the correct price for an OC71 of reputable make should have been 74p plus VAT. In the second place the dealer should be thanked for keeping this type of transistor in stock, bearing in mind the fact that these are not exactly the most sought-after transistors and in any case can be obtained in bulk at give away prices as seconds or surplus which the average dealer would not care to keep or sell.

The third item is this. The average man in the street knows nothing of the pitfalls involved in running a business (be it small or large). He knows he needs an OC71 and for convenience pops into his local dealer trusting that he will have some in stock. It could have been any one of hundreds of different types held in stock against the time they are needed (if they are) together with hundreds of valves, resistors, capacitors etc. Who pays for the stock which just lies there as a convenience? There is no way of knowing what will be asked for. If Mr Pearson thinks it is so lucrative I suggest he draws up an imaginary stock list, pays for it all (mentally that is, I doubt if he would be so bold as to do it) and then tries to sell it at 25p per go, that is if he has thought to stock the item required.—Les Lawry-Johns (Gravesend, Kent)

### Very puzzling

I have taken *PW* for some years now, and whenever possible attempt to complete the 'Technicross' puzzle. However, after many frustrating months, I feel that it would be beneficial to those taking part if the answers were published in the same issue as the puzzle. Waiting a month for the correct answers tends to lessen the enjoyment of the game.

Perhaps I may also suggest, that on the whole, the questions are a little obscure for the general readership of *PW*, including myself! Am I just a little thick or is this a generally held thought amongst the readership?—A W Bunting (Kent)

*We would be pleased to hear from other readers about their views on this feature.*

# NEW MULLARD & MAZDA VALVES

All individually boxed and guaranteed. Full trade discounts to bona fide companies. Price and availability lists on application.

## EXPRESS POSTAGE

12p for 1 Valve.  
Each additional Valve add 2p in UK

DM70	0.69	EF80	0.58	PC84	0.83
DY86/7	0.53	EF83	1.10	PC88	0.90
DY8C2	0.53	EF85	0.53	PC88	0.98
EABC80	1.16	EF86	1.50	PC89	0.78
EB91	0.78	EF89	1.47	PCC189	0.91
EC81	0.89	EF91	1.35	PCF80	0.63
EF80	0.83	EF92	1.51	PCF82	1.37
EF83	0.66	EF95	1.68	PCF86	0.73
EF89	0.50	EF183	0.89	PCF200	1.30
EC86	0.82	EF184	0.89	PCF261	1.30
EC88	0.86	EH90	0.91	PCF801	0.73
EC90	0.94	EL34	1.21	PCF802	0.78
EC97	0.69	EL36	1.15	PCF806	0.73
ECC181	0.84	EL84	0.59	PCH200	1.30
ECC22	0.83	EY86	0.81	PCL82	0.63
ECC83	0.53	EL85	0.89	PCL83	0.78
ECC84	0.63	EM81	1.24	PCL84	0.69
ECC85	0.78	EY51	0.89	PCL85	0.72
ECC88	1.06	EY86	0.50	PCL86	0.78
ECC189	0.77	EY86/87	0.53	PCL805/850	73
ECP80	0.63	EY88	0.81	PCL87	0.63
ECP82	0.90	EZ80	0.63	PD500	2.11
ECP86	0.76	EZ81	0.53	PL200	0.91
ECH81	1.50	GY501	1.10	PL36	1.08
ECH83	1.06	GZ34	1.06	PL81	0.91
ECH84	1.30	OC83	0.60	PL82	0.40
ECL80	0.78	OC86	1.05	PL83	1.58
ECL82	0.69	PC88	1.05	PL84	0.50
ECL83	0.72	PC97	0.53	PL84	0.78
ECL86	0.78	PC900	0.65	PL500	1.02

PL504	1.92	30C15/	
PL508	1.30	PCF800	1.22
PL509	1.77	30C17	1.29
PL512	2.03	30C18/	
PY33	0.73	PCF805	1.29
PY81/800	0.56	30F5/FF818	
PY82	0.70		1.35
PY88	0.63	30FL1/	
UB789	0.65	PC850	0.95
PY800	0.56	30FL2	1.02
PY801	0.56	30FL12	1.44
U26	1.22	30FL14	1.20
U91	1.17	30L1/PC834	
U193	0.56		0.83
UA1C80	1.01	30L15/	
UBC81	0.80	PCC805	1.35
UBC82	0.80	30L17	1.12
UC85	0.69	30P4MR	1.83
UCH81	1.30	30P1Z/	
UCH82	0.78	PC801	1.22
UL84	1.06	PC802	1.06
UY88	0.73	30P19/	
6/30L2/		PCL801	1.35
ECC804	1.20	30P13/	
6P23/EF912		PCL800	1.47
		30P14/	
		PCL81	1.72
		30P15	1.44
30C1/PCF80			
	0.63		

# NEW VALVES

Individually boxed and guaranteed but of European or other origin at greatly reduced prices. Quotations for any valve not listed. Send SAE for lists.

AZ1	1.00	EF37A	1.50	N78	5.00
AZ31	1.00	EF39	1.25	OA2	0.46
CLB31	1.40	EF80	0.35	OB2	0.45
CL53	1.60	EF85	0.45	PC86	0.65
CV31	1.00	EF86	0.50	PC89	0.65
DAF91	0.40	EF89	0.35	PC97	0.55
DCP96	0.60	EP91	0.40	PC960	0.55
DCP90	1.25	EP92	0.50	PC984	0.45
DF91	0.40	EP95	0.45	PC988	0.58
DF96	0.60	EP98	0.80	PC989	0.55
DK91	0.60	EF183	0.40	PCC189	0.85
DK92	1.00	EF184	0.60	PCF80	0.40
DK96	0.75	EL32	0.60	PCF82	0.43
DL92	0.50	EL33	3.00	PCF86	0.65
DL94	0.48	EL34	0.70	PCF801	0.60
DL96	0.55	EL36	0.60	PCF802	0.55
DY86	0.45	EL37	3.40	PCF805	0.90
DY87	0.45	EL41	0.90	PCF806	0.80
EY802	0.47	EL42	1.65	PCF808	1.00
EABC80	0.88	EL84	0.85	PCL82	0.45
EAF42	0.70	EL95	0.60	PCF83	0.70
EB91	0.80	EM80	0.55	PCL84	0.50
EB93	1.00	EM81	0.60	PCL85	0.60
EB94	0.78	EM84	0.40	PCL86	0.50
EB98	0.40	EM87	1.00	PCL805/850	0.60
EB93	0.40	EY61	0.45	PD500	1.50
EBF89	0.82	EY86	0.50	PEN45	0.85
EBL31	2.00	EZ40	0.60	PL36	0.63
ECC81	0.45	EZ41	0.75	PL81	0.55
ECC82	0.38	EZ80	0.30	PL82	0.50
ECC83	0.38	EZ81	0.31	PL83	0.50
EC84	0.85	GY501	0.81	PL84	0.50
ECC85	0.45	GZ30	0.65	PL500	0.95
ECC88	0.50	GZ32	0.65	PL604	0.85
ECH83	1.50	GZ34	0.75	PL508	0.90
ECH82	0.85	HN309	1.50	PL509	1.55
ECH81	0.85	KT61	3.00	PL802	2.00
ECH83	0.50	KT66	3.40	PK25	2.50
EC84	0.80	KT68	3.75	PK33	0.83
ECL82	0.42	KT81	1.75	PY81	0.50
ECL83	0.75	KT88	3.65	PY82	0.45
ECL86	0.55	KTW61	1.50	PY83	0.50
ECL800	3.00	MU14	1.00	PY88	0.63

PY500	1.10	6J5M	0.65
PY81/800	0.50	6J5G	0.45
PY801	0.55	6J6	0.35
SP41	2.00	6J7G	0.30
SP61	0.85	6J7M	0.65
UB21	1.50	6K6GT	0.80
U14	0.75	6K7G	0.85
U25	1.00	6K7M	0.45
U26	0.85	6K8G	0.45
U191	0.75	6K8M	0.70
UABC80	0.40	6K25	1.00
UAF42	0.78	6L6G	1.25
UB21	0.60	6L6GC	0.60
UBC81	0.50	6J1G	0.40
UBF80	0.50	6Q7M	0.60
UBF89	0.60	6BL7GT	0.55
UC85	0.60	6BN7GT	0.55
UCH42	0.80	6BG7GT	0.40
UCH81	0.50	6U6G	1.50
UCL82	0.40	6V6G	0.80
UCL83	0.70	6V6GT	0.40
UF41	0.75	6X4	0.45
UF89	0.50	6X5G	0.45
UL41	0.85	6X5GT	0.55
UL84	0.60	7B6	0.30
UY41	0.55	7B7	0.80
UY86	0.45	7C8	2.00
VR105/30	0.40	7C8	1.00
VR150/30	0.45	7H7	0.90
1R5	0.50	7R7	0.30
185	0.40	7R7	0.25
174	0.40	7Y4	0.30
384	0.40	12A7B	0.45
3V4	0.85	12A7T	0.45
5R4GY	1.20	12A9B	0.50
5U4G	1.25	12A9U	0.85
5U4GB	0.70	12A9T	0.85
5Y3GT	0.65	12BA8	0.50
5Z4G	0.95	12C6	0.60
6/30L2	0.60	12BE6	0.60
6AK5	0.45	30C15	1.00
6AM5	2.00	30C17	1.00
6AQ5	0.60	30C18	0.90
6A870	1.00	30F5	1.00
6A76	0.60	30FL1	1.00
6A96	0.40	30FL2	1.00
6BA6	0.38	30FL14	1.00
6BE6	0.45	30L15	0.95
6BB6	0.75	30L17	0.95
6B76	0.78	30P4MR	1.80
6BQ7A	0.55	30P12	1.00
6B77	1.20	30P19	0.95
6B87	1.40	30P11	0.95
6BWW6	1.00	30P13	1.10
6BW7	1.00	30P14	1.10
6C4	0.40	36W4	0.60
6CD6G	1.80	35Z4GT	0.70
6CH6	2.20	80CDBG	1.20
8074	0.90	80T9	1.00
92P3	0.90	813TT	1.75
6F25	1.00	813UBR	2.00
6P28	0.75	886A	2.00

# TRANSISTORS-INTEGRATED CIRCUITS

## EXPRESS POSTAGE


12p per order in UK

All transistors, I.C.'s offered are new and branded. Manufactured by Mullard, Texas, RCA, Ferranti, Motorola, ITT, Fairchild, Lucas, etc. Quantity discounts on application. Send SAE for full lists.

AA119	0.07	BD124	0.65	0A91	0.07	ZTX500	0.13	2N2904	0.20
AA213	0.12	BD131	0.42	0A200	0.08	ZTX501	0.15	2N2904A	0.25
AA215	0.10	BD132	0.50	0A202	0.09	ZTX505	0.18	2N2905	0.25
AC107	0.11	BF114	0.25	0A203	1.00	ZTX531	0.25	2N2905A	0.25
AC126	0.25	BF167	0.25	0C20	2.00	ZTX550	0.18	2N2906	0.20
AC127	0.25	BF173	0.25	0C23	1.25	1N914	0.08	2N2922	0.12
AC128	0.15	BF179	0.33	0C25	0.40	1N4001	0.05	2N3053	0.18
AC176	0.25	BF180	0.33	0C28	1.00	1N4002	0.07	2N3055	0.45
AC187	0.21	BF181	0.35	0C35	0.75	1N4003	0.08	2N3055	0.91
AC188	0.20	BF195	0.18	0C38	0.40	1N4004	0.07	2N3056	0.18
AC197	0.35	BF198	0.18	0C42	0.20	1N4005	0.10	2N3058	0.11
ADY39	0.75	BF197	0.18	0C44	0.20	1N4006	0.18	2N3703	0.11
AD140	0.40	BF200	0.32	0C45	0.20	1N4007	0.12	2N3703	0.11
AD149	0.75	BF261	0.25	0C71	0.25	1N4009	0.06	2N3704	0.14
AD161	0.44	BF898	0.25	0C72	0.35	1N4148	0.08	2N3705	0.15
AD162	0.44	BFW10	0.61	0C78	0.30	1B921	0.07	2N3706	0.11
AF116	0.25	BF188	0.24	0C78	0.30	1B2023	0.28	2N3707	0.18
AF118	0.25	BFY50	0.20	0C81	0.25	1B2051A	0.20	2N3708	0.07
AF186	0.48	BFY51	0.20	0C81D	0.28	1B2100A	0.20	2N3709	0.16
AF239	0.44	BFY52	0.20	0C81Z	0.45	1B8010	0.85	2N3710	0.11
AS727	0.83	BR100	0.40	0C83	0.60	2N696	0.15	2N3711	0.11
AS728	0.85	BY100	0.27	0C83	1.14	2N697	0.15	2N3819	0.68
BA102	0.25	BY126	0.14	0C170	0.30	2N706	0.32	2N4008	0.40
BA115	0.10	BY127	0.12	0C171	0.80	2N708A	0.18	2N4009	0.18
BA116	0.10	BZX61 series		0C200	0.75	2N1181	0.85	2N4010	0.18
BC108	0.12			0C201	1.50	2N1132	0.84	2N4011	0.20
BC109	0.12	BZY88 series		0C202	1.50	2N1302	0.18	2N4012	0.20
BC113	0.15	CR81-05	0.35	0C203	0.75	2N1303	0.18	2N4013	0.25
BC117	0.21	CR81-40	0.50	0C204	1.50	2N1304	0.32	2N4014	0.18
BC148	0.80	CR83-05	0.40	0C205	0.75	2N1305	0.18	2N4015	0.10
BC147	0.10	CR83-40	0.45	0C206	1.50	2N1306	0.28	2N4016	0.18
BC148	0.68	MJE340	0.67	0C207	0.75	2N1307	0.28	2N4017	0.18
BC169C	0.15	MJE370	0.68	0C208	1.14	2N1308	0.32	2N4018	0.14
BC185	0.18	MJE520	0.65	0C209	0.20	2N1309	0.80	2N4019	0.30
BO182L	0.18	MJE955	1.27	0C210	0.12	2N1813	0.81	2N4020	0.18
BO184L	0.18	MJE3055	0.70	0C211	0.20	2N1814	0.45	2N4021	0.11
BC338	0.15	MPP102	0.45	0C212	0.20	2N1815	0.45	2N4022	0.11
BC339	0.55	MPP108	0.88	0C213	0.20	2N1816	0.45	2N4023	0.11
BC373	0.18	MPP104	0.85	0C214					

# tecknowledgey in consumer ICs - and their applications.

## SGS Audio ICs

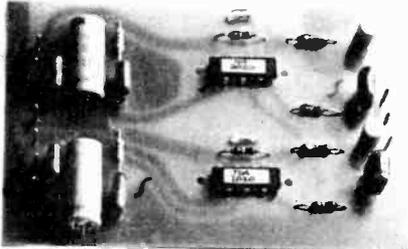

The much heralded TDA2020 is here. And just to make sure that you don't go wrong, so is the SGS application test circuit PCB for a stereo 15 + 15 (RMS) Hi Fi amplifier.

Prices :	IC	AUDIO	DISCRETES
TBA810AS	+HS	1.09	ZTX107/8/9 14p
TCA940E	+HS	1.80	ZTX413(LN) 17p
TDA2020		2.99	ZTX212/3/4 16p
<b>FM LINEAR</b>			
MC1350		0.70	BD 535 npn 7A/60v 52p
CA3089	+QC	1.94	BD536 pnp 53p
TBA120	+QC	1.00	BD377 npn 3A/50v 29p
<b>MPX LINEAR</b>			
MC1310P	+LED	2.20	BD378 pnp 32p
CA3090AQ	+LED	3.75	BD515 npn 2A/45v 27p
			BD516 pnp 30p
			BD609 npn 10A/90v 70p
			BD610 pnp 102p

## We've moved

To accommodate expanded R & D facilities, AMBIT has moved sales and administration to 25 High St. Brentwood. The existing 37 High Street premises are retained for the engineering activities.

One of the first products of this move has been the development of a TV sound tuner, from an "off air" system, using its own varicap UHF TV tuner, with ICIF amplifiers and block filters by TOKO. And then one of our best ever circuits - an electronic touch tuner, with scanning mode, and facilities for 6 preset stations. The unit is suitable for use with FM, and now AM of course, and offers a complete tuner system without any moving parts. Selection is by means of touch tuning in all cases, with manual scan and preset switching automatically interlocked.

Our R&D facilities are available for general consultancy to OEMs: further details on application. Standard project estimation fee, including project evaluation comment data is £15.00 payable in advance.

## Modules & Kits

### New modules:

8011	Totally touch tuned varicap controller	£14.99.
8005	Larsholt tunerset accessory unit, with pilot tone filter and audio stages, rectifier, IC stabilizer, meter driver circuits.	£4.99 (kit)
8001	55kHz low pass filter (mpx birdy filter)	£2.35 built £1.75 (kit)
2001	Stereo scratch and rumble filter, with continuously variable operating frequencies.	£5.80 (built) £4.60 (kit)
3000	Stereo control preamp - a wide dynamic range, low distortion AF preamp, with vol, bal, bass and treble controls.	kit £5.78
2020k	The TDA2020 stereo amp kit photographed on the left.	£7.85
7700	TV off air UHF sound tuner - built £26.00 (4 preset stations)	
9000 kit	AM/FM mpx tuner chassis, with mech. tuner	£17.50
7004 kit	MW/LW varicap tuner module, inc. ferrite rod	£9.95
7252	Hi Fi MOSFET FM tuner module by Larsholt	£24.00
7253	Hi Fi FET FM tuner module inc decoder	£24.00
5600	Hi Q MOSFET varicap tunerhead by TOKO	£11.25
EC3302	FET tunerhead from TOKO	£5.00

Complete FM Tuner kits, inc case, for use with the above modules: details SAE please. Prices range from £40 - £60.

Amongst our various accessories for entertainment electronics is a range of FM tuning, frequency and sig. strength meters with 12v, 50mA bulb. £2.50 ea.



**ambit international**  
 25 high street, brentwood,  
 essex. cm14 4rh.  
 tel: (0277) 216029  
 tlx: 995194

Free price list with an SAE, catalogue of modules and parts 40p. including postage and VAT.

General Terms: CWO please, official bodies and companies please note min. invoice £7.50. PP for CWO orders 22p per order. (UK and Eire). Overseas customers please include sufficient for postage. VAT is not included, and must be added at 25%. In stock orders despatched within 48 hours.

### MAINS TRANSFORMERS

PRI. 240v sec. 27/0/27v at 800 m/a, £2.25. P.P. 50p.  
 PRI. 110/240v sec. 50v at 10 amps, £10.00. P.P. £1.50.  
 PRI. 110/240v sec. 20/21/22v at 8 amp, £6.00. P.P. £1.50.  
 PRI. 110/240v sec. 23/24/25v at 10 amp, £7.00. P.P. £1.50.  
 PRI. 110/240v sec. 24/40v at 14 amp, £1.90. P.P. 60p.  
 PRI. 240v sec. 20/40/60v at 2 amp, £3.00. P.P. 70p.  
 PRI. 240v sec. 20v at 2 1/2 amp, £2.00. P.P. 50p.  
 PRI. 240v sec. 18v at 1.5 amp and 12v at 1 amp, £2.25. P.P. 50p.  
 PRI. 240v sec. 18v at 1 amp, £1.00. P.P. 30p.

### 12 volt MINI UNISELECTOR

11 way. 4 bank. (3 non-bridging 1 homing) £2.50. P.P. 35p.

### 24 volt MINI UNISELECTOR

11 way. 6 bank (5 non-bridging, 1 bridging) £2.00. P.P. 35p.

### SIEMENS MINIATURE RELAYS

6v 4c/o with base. 65p ea.  
 24v 2c/o with base. 50p ea.

### MAINS RELAY 240v

3 c/o 10 amp contacts. £1 with base.

### MINIATURE RELAYS

(1 1/2 x 1 1/2 x 3/4) 24 v. 4 c/o 40p

### GARRARD PLINTH & COVER

For Zero-100, etc. Finished in brushed aluminium and black, with hinged smoke grey perspex lid, £11.00.

SCR 1 amp 400 P.L.V. 35p.  
 5 amp 400 P.L.V. 40p.

### EDGE CONNECTOR

54 way -1 vero size etc.  
 Can easily be cut to any length 55p. P.P. 10p.

### CIRCUIT BOARD

P.C.B. 1/161 oz. COPPER

### FORMICA

Dim. 8.4 x 7.7 in 3 pcs., 75p.  
 Dim. 9.4 x 8.1 in 3 pcs., 90p.  
 Dim. 10.1 x 7.9 in 3 pcs., £1.00.  
 Dim. 13.1 x 9.4 in 3 pcs., £1.20.  
 Dim. 17.0 x 9.0 in 2 pcs., £1.20.

### BARGAIN PACK

10 pcs. 10.1 x 7.9 in. Plus free 1/2 etching Xtals, £2.80. P.P. 45p.

### FIBRE GLASS P.C.B.

Dim. 8 x 6, in 35p each.  
 Dim. 12 x 6 in, 60p each.  
 Dim. 12 x 12 in, £1.00 each.  
 Equals less than 1p sq.in.

### RESIST COATED P.C.B. FIBRE GLASS

6 x 6 in, 50p ea.  
 12 x 6 in, 90p ea.  
 12 x 12 in, £1.50 ea.  
 Post & Packing 10p per sheet.

### FERRIC CHLORIDE ETCHING XTALS

1 lb - 1 litre pack, 60p. P.P. 15p.  
 5 lb - 5 litre pack, £1.95. P.P. 55p.

### PRINTED CIRCUIT KIT

The no frills all value kit. Containing 4 pcs 8 x 7 Formica laminate, 1 pce 6 x 6 Fibre glass laminate, 1 lb Etching Crystals, 50 c.c. Resist ink, with instructions. £2.30. P.P. 50p.

### BLUE P.C.B. INK

Etch resist use with any pen. Much cheaper than ready loaded pens.  
 50 c.c. 55p. P.P. 10p.

### S-DECS AND T-DECS

S-DEC £1.90. T-DEC £3.60.  
 U-DEC A £4.20. U-DEC B £6.90. P.P. 25p.

### FIBRE GLASS BARGAIN PACK

200 sq. in. single & double sided pieces, 75p. P.P. 25p.

### OVERLOAD CUT-OUTS

Panel mounting 800 M/A. 1.8 amp. 10 amp. 55p ea.

### HIGH CAPACITY ELECTROLYTICS

250mfd/63 volt, 20p. P.P. 8p.  
 1000mfd/100 volt, 70p. P.P. 25p.  
 2200mfd/100 volt, 90p. P.P. 25p.  
 4700mfd/25 volt, 65p. P.P. 20p.  
 6800mfd/16 volt, 50p. P.P. 15p.  
 10,000mfd/25 volt, 75p. P.P. 25p.  
 25,000mfd/40 volt, £1.25. P.P. 30p.  
 47,000mfd/40 volt, £2.00. P.P. 50p.  
 100,000mfd/10 volt, £1.50. P.P. 50p.  
 160,000mfd/10 volt, £2.00. P.P. 50p.

### 3 GANG TUNING CAPACITOR

8.5pf to 320pf, 80p. P.P. 20p.  
 10.7 M.H.Z. canned I.F. Size 1 x 1/2 x 1/2 in, 65p. P.P. 10p.

### MINIATURE METERS

500 micro-amp (level-stereo beacon, etc.), scaled half black/half red. Size 1 x 1 in, 65p. P.P. 15p.

### RIBBON CABLE

8 way. 8 colours. Bonded flat slide by side.  
 10 Metres, £1.90.  
 100 Metres, £12.50.

**KINNIE COMPONENTS** 10 NELMES WAY, HORNCHURCH  
 ESSEX RM11 2OZ  
 HORNCHURCH 45167  
 MAIL ORDER ONLY. PERSONAL CALLERS BY APPOINTMENT

# GENERAL SERVICING

An occasional series by LES LAWRY-JOHNS

chatting this time on—

## 3-VALVE RADIOS

VALVED radios are still great favourites with many people. The main reason is economy, as a mains operated transistorised set large enough to provide the same bass response tends to be expensive whilst battery operated sets are either too small to sound good or are too expensive to run, bearing in mind the fact that a PP9 battery, for example, is now over 50p. In addition to this, some people have a sentimental attachment to their valve radios. We are quite fond of an old couple in their nineties, who have a 1933 Ultra! We will not go into the servicing of this type of set, however! Suffice to say that we have kept it going for them for more years than we care to mention.

### Transformerless

Valved radios generally fall into two types, the heavier type having a mains transformer and parallel-fed valve heaters and the lighter ones with no transformer and series heaters. The latter is more commonly encountered and we will consider this type first.

With no transformer to provide low voltage supplies, the normal 240V mains has to be adapted to provide the HT and heater requirements. If we accept that one of the mains supply leads, preferably the neutral, can be connected directly to the chassis or metalwork, the design can be simplified so that all that is necessary is a means of reducing the mains voltage to that required by the total number of valve heaters in series. This is usually done by inserting a wirewound resistor in the top end of the series chain to drop the voltage to that required. A tapping on this resistor can be used to supply the HT rectifier, which is usually a valve, and the current drawn by the HT must be added to that drawn by the valve heaters when calculating the value of the dropping resistor. The arrangement is shown in Fig. 1 except that a dial lamp and shunt resistor have been inserted into the chassis return to neutral (or one side of the mains at any rate).

The advantage of using a valve rectifier is twofold. First, the valve warms up slowly with the rest and therefore the HT builds up slowly as the rest begin to draw current. Therefore the HT is rarely more than, say, 200V. This takes the strain off all the capacitors on the HT line and leads to greater reliability. Secondly, the voltage drop across the rectifier heater in addition to that of the other valves reduces the rating of the dropper so that the heat concentration is reduced in this area. Obviously the

higher the total voltage of the valve heaters the lower the value of the dropper. This is why nearly all European radios of this type used 100mA valves of the "U" series (UY85, UL84, UCL82 etc.). Countries with a low mains voltage (say the US) of about 110V used a different range of valves taking more current and dropping less voltage. Some years ago it was quite common to find a series chain of 0.3A valves (25Z4, 25L6 etc.), or a 0.2A chain (CY31, CL33 etc.), a 0.15A chain or even a 0.16A would you believe! Also a 0.1A chain which is the most likely line-up to be found in sets of more recent origin.

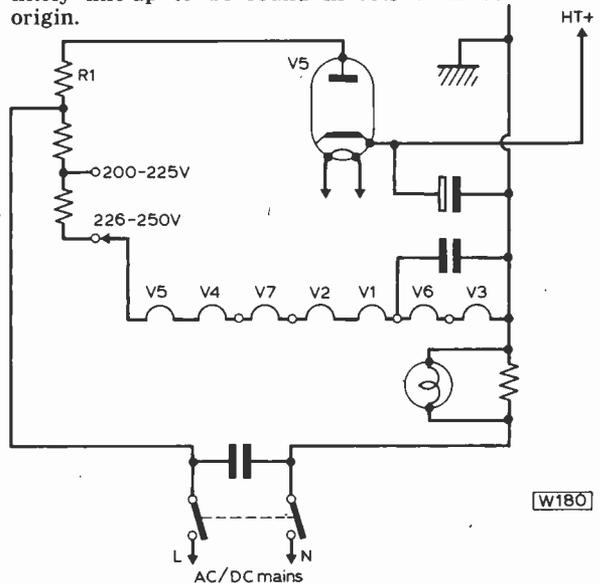


Fig. 1 In AC/DC receives the heater chain and HT supply were generally of this type.

The number of valves used could vary but the minimum was usually four including the rectifier, this line-up being, for example, UCH81 frequency changer, UBF89 IF amp, detector and AGC, UCL82 audio amplifier and output, and a UY85 rectifier. A variation on this theme was a UCH81 as above with another UCH81 as an IF amplifier and audio amplifier with a UL84 output, using two crystal diodes for detection and AGC. The one advantage with this system was the possibility of changing over the two UCH81s if the one in the FC stage was reluctant to oscillate (which is something they often did, or didn't!).

The main disadvantage of series-heated valves is

the fact that rectifier and output valves are well up the live mains end with only the dropper and perhaps the dial lamps (some designs) at a higher potential. This means that there is increased stress between the heater and the cathode of the valve with the consequent risk of breakdown, and induced hum in the case of the output valve. It comes as no surprise therefore to find the fault of "no valves glowing" is often due to the heater of the rectifier being open circuit. It is not that the heater just feels like failing, it is most often blown due to the failure of insulation, the high potential AC on the heater suddenly finding itself provided with a short cut via the main electrolytic capacitor and chassis. The rectifier heater is thus treated to an extremely gay life of somewhat short duration. If there are dial lamps in the way, these will probably fail also. A similar short in the output valve may or may not blow the heaters, only cause them (rectifier and output only) to glow brightly.

## Common faults

Now let us consider a few of the more common complaints and their cures. One of the most common is hum. Tackling this in a set with series heated valves is a little different from a set with parallel heaters. In the latter case one tends to reach for an electrolytic capacitor of adequate voltage rating, usually 350V or more, and connect this across the HT line in one of two places, reservoir section to chassis or smoothing section to chassis, to see which section is at fault. The series heated chain does add the probability of heater-cathode leakage so that although the test electrolytic capacitor can still be tried, one is not surprised if there is no difference. The next step is to see if the hum continues with the volume turned down. If it does, it is reasonable to suspect that the output valve (probably a UL84 or UCL82) has heater-cathode leakage or is drawing grid current, the net result being the same. So change the valve.

If the receiver uses a printed panel, there is the added possibility of leakage across the surface of the panel or through it. The affected area will usually



—set manufacturers often seem more concerned with appearances—

be blackened and a little cutting away of the plastic, perhaps combined with replacing the affected tracks with wire, may have to be resorted to. Set manufacturers seem often more concerned with appearance than efficiency and mount resistors close up to the panel with the leads cut short. Replacements should be made with longer leads so that the resistors stand well up off the panel, however ugly this may appear. Resistors, like politicians, should be open and above board!

Do not omit to check the grid resistor of the output valve which sometimes goes high particularly if the valve has been drawing grid current. A grid leak resistor of say  $1M\Omega$  or  $470k\Omega$  can often rise to many megohms leaving the grid floating and humming away to itself. Quite often the hum varies with the volume control setting and this means we have to look back to the preceding stages. Usually either the IF amplifier, say UF89, or the frequency changer (UCH81) is at fault and the latter, being more expensive of course, is usually the culprit!

## No results

One of the most common complaints is that the valves light up but there is precious little other activity. The usual reason is that the smoothing resistor has failed but one must not assume this. The output transformer could have an open circuit primary or there may be no supply to the rectifier due to an open circuit surge resistor (R1 in Fig. 1), perhaps little Johnny has moved or unscrewed the internal loudspeaker muting devices on the external speaker panel (you did it, but blame Johnny anyway).

So we must proceed logically. If there is a fine upstanding dropper it is no trouble to check all sections with a neon when the set is on or an ohmmeter when the set is off (if you're too lazy to switch the meter to the AC range and check the voltages on the dropper tags with the set on). Many sets did not use a single dropper however and the surge limiter may be a separate wirewound resistor



—one common complaint is hum—

mounted in a more inaccessible position. If the value cannot be read it can be assumed to be in the region of  $100\Omega$ . If a printed panel is used, the resistor may be intact but it could have parted company with its print beneath.

Assuming the rectifier is receiving its supply however, there should be HT on at least one of the main electrolytic capacitor tags. If there is a good voltage on one but not the other the smoothing resistor (or choke if it's an older set) could well be open circuit. The value of this will depend upon whether it has to pass the total HT current. Quite often, the output transformer primary is directly connected to the rectifier and therefore the anode current of the output valve does not pass through the smoothing resistor. In this case the value may be quite high, say about  $3k\Omega$ . If the voltages are ok at both the smoothing tags, check the voltage at the anode of the output valve. If output transformers have a bad habit it is that they go open circuit on the winding which feeds the anode! This means a new transformer. If an exact replacement is not to hand an alternative can be used, the important thing being that the correct impedance matching is maintained. Very generally speaking, a small battery output valve requires a high impedance, the normal type of valve encountered in mains operated sets a medium impedance, whilst a low impedance is only required for more high powered amplifier type valves (and output triodes if you can remember that far back).



—a hefty charge which can tickle you pink—

Don't forget that if there is no discharge path through the HT line, the reservoir capacitor can be left with a hefty charge which can tickle you pink if you let it! The capacity is not that used in TV receivers (about 100 to  $300\mu\text{F}$ ) which can really cause a spark but even a  $32\mu\text{F}$  on a 300V line can pack a punch which is not to be sneezed at!

The Thorn group made a large number of models with the "U" series of valves on a printed panel where not only the smoothing resistor had a habit

of becoming O/C but also parted company with its print, as did the surge resistor to the UY85 anode. These were fairly small wirewound resistors and serve as an illustration of what we have been going on about in the above text.

## The audio amplifier

Having checked the HT supply and output stage, and ensured the latter is operating under the correct conditions, with the cathode bias components in order (resistor the right value and the capacitor doing its job) check the output grid to ensure there is no positive reading. If there is such a reading, the valve could be drawing grid current, highly likely, or the coupling capacitor from the audio amplifier anode could be leaking, less likely but still a strong possibility. We then turn to the preceding stage which is normally either a separate triode section in the output valve or the triode section in a valve like a UABC80 (three diodes and a triode in one envelope). The only component likely to require attention is the anode load resistor which is normally about  $220k\Omega$ . This does tend to "go high" producing loss of volume and a peculiar form of distortion (stressing the sibilants, you could say). This is no trouble as the voltage at the anode will be very low and this itself suggests the resistor is the primary subject.

A low voltage need not be due to the resistor and if this proves to be of correct value, attention should be directed to the control grid. This is normally biased by a high value resistor of up to  $10M\Omega$ . If the coupling capacitor (the charge on this determines the bias with the resistor) is leaky, the bias is cancelled and the valve draws too much current. The voltage drop across the anode load is therefore excessive and is responsible for the condition. Some receivers do use cathode bias, and where this is so the cathode capacitor could be shorted, or the grid coupler could still be leaky, but most receivers have the cathode directly coupled to chassis as this simplifies the design.

Most sets have the volume control feeding the control grid and if the coupling capacitor is leaky the position of the control will vary the distortion to an extent. Which of course brings us to the vexed subject of noisy controls. Usually a squirt of cleaning fluid into a convenient gap in the housing will bring the control to heel but it is sometimes difficult to find or make a gap. The construction of the control either makes this operation very easy or very difficult and it is sometimes necessary to partially strip it or replace it completely. The control itself is not always responsible however and associated capacitors should be checked for leakage as control tracks do not take kindly to the passage of DC current. This is particularly so in the case of some makes of unit audios and radiograms of more recent origin but since these are transistorised this thorny subject will not be pursued further.

## The IF stage

The detector and AGC circuitry in valved receivers very rarely gives trouble so we may be forgiven for nipping smartly past these and delving into the IF stage. Once again this can be quite simple, with the cathode chassis connected and the control grid biased from the AGC line. Note that valves are always reversed biased, i.e. the control voltage pushing the

valve toward cut-off and is therefore negative-going. The HT supply to the anode and screen is via a decoupling resistor of some  $1k\Omega$  with a capacitor to chassis of from  $0.047$  to  $0.1\mu F$ . This decoupling point can be the screen pin of the valve base with a short lead to the IF transformer primary, or to the latter point with a short connection to the screen pin.

Separate supplies are often used so that the screen grid of the IF amplifier can be connected to the same electrode on the frequency changer base and two resistors are often used as a potentiometer to hold the screens steady, typical values being say  $22k\Omega$  from HT to the valve base with a  $47k\Omega$  to chassis. As the majority of the current passes through the upper resistor,  $22k\Omega$ , this is often the one to change value and thus drop the applied voltage. This is sometimes the cause of the complaint, "My radio has been getting weaker and weaker and now you can hardly hear it".

Instability is another common disorder and this can vary from whistles and screeches to non-operation due to the paralysing effect of the AGC being overloaded by the instability. This can be a trifle tedious to overcome and the normal remedies are not always effective. The usual first step is to try bridging the decoupling capacitors with a test  $0.05\mu F$  or similar. Bridging from screen to chassis may stop all complaints right away and you then go on your way rejoicing. But more extensive checking around may have to be resorted to, bridging other capacitors associated with the IF and frequency changer stages, the AGC line and the HT line. If none of these efforts produce results, check the alignment of the IF transformers, the valves, earth contacts (especially if these are riveted) and the main electrolytics.

## Frequency changer stage

For AM reception this is usually a conventional triode heptode such as a UCH81. The complaint of no normal reception with, perhaps, some background mush is often the result of the valve becoming defective and refusing to oscillate (triode section). When it is oscillating there should be a negative voltage on the triode grid. If this is absent a new valve will usually put things right. If it doesn't, a general check up on the capacitors and resistors, comparatively few in number, associated with the section will usually restore signals. A defective coil is sometimes difficult to locate if it is suffering from shorted turns but with a bit of luck the trouble may be the result of a badly soldered lead-out or even an open circuited lead-out which can be repaired.

The mixer section is similarly wired to the IF amplifier and the same remarks apply regarding resistors changing value, leaky decoupling capacitors and the like. It varies in the arrangement of the control grid which is blocked from the aerial coils as a rule with a fairly low value capacitor, say  $100pF$ , and with a fairly high value resistor connecting to the AGC line.

The aerial circuit may consist of a ferrite rod on which is mounted the tuning coils with leads to the tuning gang, the wavechange switch and chassis, but there are infinite variations on this theme. If there is no ferrite rod (the design is older) there is usually a cluster of coils around the wavechange switch and an open circuit on one may result in the others being put out of action. They are probably slug tuned for padding with separate trimmers for lining up the high frequency end of the scale. Where ferrite rods

are fitted the actual rod is the slug and the position of the coils on the rod is varied for padding on the low frequency end of the scale.

## VHF-FM

Receivers with these facilities have a separate section due to the higher frequencies involved. The aerial input can conveniently be a half-wave dipole made simply by opening up a piece of twin flex to the required length and stapling this in the cabinet. This is all very well in some areas but if serious listening is demanded a more elaborate system is needed with the correctly matched down lead,  $75\Omega$  coaxial on most UK stuff,  $300\Omega$  balanced twin on imported, as a rule. We will not go into the pros and cons of these different inputs here as they are pretty well known and have been discussed at length in previous issues.

The aerial input is taken to the tuning coils and thence to the first section of a double triode, as a rule, say a UCC85. The second half functions as an oscillator. Nine times out of ten replacement of this valve will restore normal signals if these fail suddenly, the tenth time being the result of defective resistors or capacitors. The actual tuning may be carried out by separate sections on the gang capacitor or by varying the position of the slugs in the aerial and oscillator coils. The output of this usually small section is fed to the IF stages, there may be more than one, through separate transformers to a ratio detector. The two diodes involved in this latter operation may be in a valve envelope (as in the UABC80 for example) or separate germanium or silicon diodes if the valve line-up does not include such a valve.

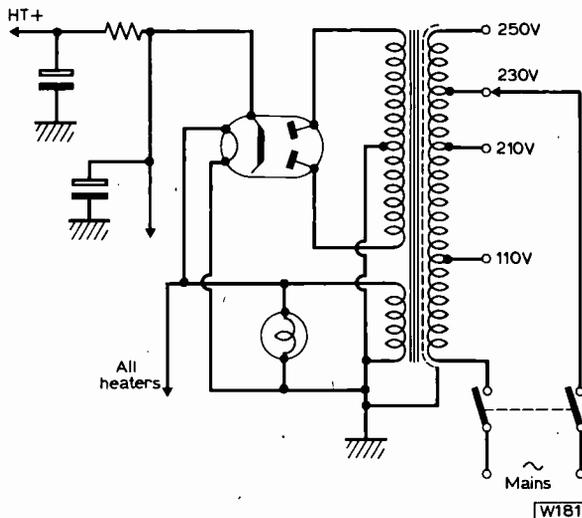


Fig. 2. AC-only sets have the conventional mains transformer with the valve heaters in parallel.

## AC-only sets

The advantage of using a mains transformer is that the valve heaters can be wired in parallel (all at the same low potential) so that the stress between the cathode and heater is largely removed, and that the chassis can be isolated from the mains. Note we said, "can be." Some receivers sacrifice this advantage

on the grounds of economy. Some transformer supplied sets use a series chain of heaters but this is all a matter of design considerations.

Some pretty weird and wonderful sets were imported some years ago using difficult valves which did tax one's resources but this is a story of its own which we may relate on another occasion. The average type of AC mains set which is likely to be encountered and which is probably worth renovating will have a transformer supplying a full wave rectifier and valves having 6.3V heaters (possibly 5V for the rectifier heater). The rectifier may have between 250 and 350V applied to its anodes from a centre tapped winding, the centre tap being chassis connected. The output of the rectifier is taken to the reservoir capacitor which may have a value of between 8 and 32 $\mu$ F. The circuit is then much the same as that previously described, using a smoothing resistor, a choke or part of the output transformer before the smoothing capacitor. The rectifier valve may be directly heated (cathode is the heater) which has a very fast warm up or indirectly heated (separate cathode) which warms up and becomes operative with the other valves. The latter imposes less stress on the capacitors, Fig.2.



—old timers which really need tracking down—

If a rectifier valve is difficult to obtain and it is decided to wire a couple of silicon diodes across the base, this stress must be recognised as the switch-on surge may be greater than the rating of the capacitors. To avoid this the inclusion of a thermistor between the rectifier output and the reservoir capacitor will add to the long term reliability of the receiver.

Valves such as the EZ80 and EZ81 are still generally available and should be used whenever possible. Older types such as the EZ40 and the like need a bit more finding but it is the old timers like the 5Z4 and 5Y3 which really need tracking down and it is here that the diodes may have to be used.

Little need be said about the other stages. They follow the lines already discussed but one is more likely to find different output stages in higher priced radiograms etc. For example, a cheaper type may use a single EL84 (or ECL86, for example) for each

channel if the instrument is stereo whilst higher quality grams which are more likely to be worth saving may have four such valves, two in push-pull for each channel. The complication arises not only in the output transformers but in the drive from the audio stage to the output pair. An output transformer primary may have five lead outs, HT to the centre tap, a tap for each screen (this provides a degree of feedback) and the outer taps for the anodes.

Valves in push-pull using differing grid drives so that some form of phase splitter is necessary. A common method is to use a triode suspended midway between the HT line and chassis with one output valve driven from the anode and the other from the cathode (when the anode is positive going, the cathode is negative thus providing the "I push, you pull" requirement). This in turn means that the grid of the triode is returned to cathode at a fairly high potential. There are so many variations on this theme that detailed description is impractical, at least in this article, so that one should not be surprised if the voltages in the driver stages appear abnormal. Stereo does at least supply us with a ready made comparison circuit so that if one side is working well we know what to expect in the side which isn't. Get the voltages right and most else falls in line. Where they are wrong, check the resistors for correct value and the capacitors for leakage. Then suspect the valves.

## Mail Order Protection Scheme

The Publishers of *Practical Wireless* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Practical Wireless* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

# HOTLINES

ON RECENT DEVELOPMENTS

## NOSEY!

Electronic noses have been around on the Amateur construction scene ever since suitable sensors became available. These, however, have found most use in such applications as fire/smoke detection etc.

A Watford company has managed some success with an explosives detector. It's called the unassuming name PD2, weighs a mere 22lbs and lives in an innocent-looking suitcase. The unit gives a positive response when explosives are detected. An audible alert sounds immediately after taking an air sample containing explosive vapour. The unit is so sensitive that it is able to detect the tiniest traces of explosives such as those which might be found on a persons hands after handling explosives—or on their clothing. The photograph shows a security officer checking a bag. If you want one of these units the UK price is around £2,150. Probably not a high price for something that nose what it's about.

## THE 'CHIT'

The NRDC (National Research Development Corporation) has encouraged many good ideas and another has just found its way into my hands. It's called CHIT, standing for CHeap Input Terminal and is manufactured at the National Physical

Laboratory. The approach used is quite ingenious. Two oblong lengths of resistive material are laid one on top of the other.

When a point (a pencil) is used to draw or write on the top oblong, the pressure causes the air gap between the two resistive surfaces to decrease and the two oblongs make contact at the point of impact. Electrodes are connected to each of the oblongs at their ends and when a current is passed through one of the oblongs, a uniform voltage gradient is developed along its entire length. The voltage at the exact point of contact i.e.: wherever the pencil tip happens to be pressing at any given instant in time, will be proportional to the pencil point's position on the x axis. The other oblong is used as a sort of wiper of a potentiometer and will attain this voltage. The two oblongs are switched, electronically, so that first one oblong is acting as a position indicator and the other the wiper of a pot, then the roles are reversed due to the electronic switching. Thus the point can be monitored in both x and y axis.

Using this method as an input terminal, handwritten characters can be transmitted, signatures verified, line drawings, circuits etc can be transmitted. Perhaps it won't be too long before you will write a letter on such a device and it will be transmitted at the same instant and received immediately. We seem to

have come a long way since the Penny Black back in 1840. If it comes, it could mean that many postmen will be looking for a new post—do you see?

## FLAT TV SCREENS

From time to time I have made comments about flat screen television "tubes". Research and development has been going on in this area for some time and the latest effort to come to my attention looks very promising. First, the US Airforce is going to try out the idea—and believe you me the American military do not waste time on impractical ideas no matter how clever they might be. The device is the brainchild of Hughes Aircraft who have vast expertise in many areas not the least of which is electronics. Some 18 months ago Hughes brought out a  $1\text{in}^2$  liquid crystal display which was capable of showing a television picture. The company successfully deposited a number of liquid crystal picture elements on a piece of silicon which also contained the excitation circuitry. Manufacturing defects caused problems but once these were overcome Hughes steamed ahead. Now, four on the line, miniature "tv screens" have been butted up together to form a  $2 \times 2\text{in}$ . display comprising a  $100 \times 100$  cell array.

It has been rumoured that the US Airforce has shown great interest in using the new approach for things like scan-converted radar, forward-looking infrared and possibly in head-up displays for gun aiming. In sunlight, it's difficult to see the cathode ray tube type of display whereas the LCD component is reflective and thus thrives in such conditions. Another distinct advantage is that crts commonly required high voltages—often thousands of volts. The LCD array requires only 25V. Plans are already afoot to produce a larger array and it is easily technically feasible.



The electronic sniffer type PD2

*Ginsberg*

MORE HOTLINES ON PAGE 57


*A versatile instrument you'll enjoy to make-no difficult components!*

**IN NEXT MONTH'S  
PRACTICAL  
WIRELESS**

**DIGITAL FREQUENCY  
METER**



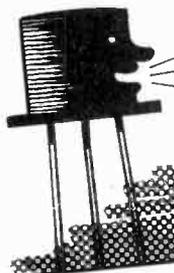You'll probably find that you have a lot of the components already! An interesting constructional project which will give much satisfaction when it's completed. Readout to, typically, 27MHz or more depending upon the IC's used. Gate times of 100 $\mu$ s to 1s. Input 60mV to 10V and time intervals 1ms to 9999s.




**Talking Transistors**

-getting to know how they work

**CONTINUED FROM THE SUPPLEMENT IN THE APRIL ISSUE**  
**FAULT-FINDING GUIDE**  
 TYPICAL SERVICING PROCEDURES  
 HINTS & TIPS - WHAT TO LOOK FOR

**ON SALE IN MAY**

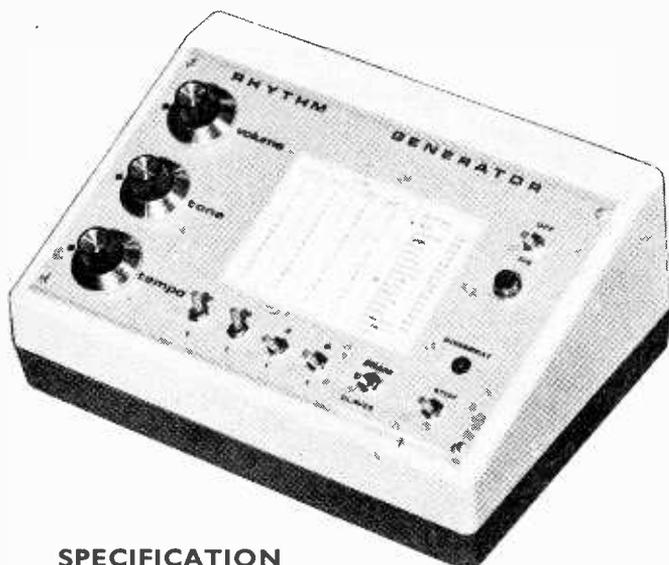

# RHYTHM

## PART 1

### SPECIFICATION

Output to external amplifier	500mV max. Variable
Number of rhythms	15
Number of percussion instruments	9
Tempo (useful range)	15 to 100 bars/min.
Number of elementary times per rhythm pattern	24 or 32
Number of bars per rhythm pattern	2 or 4
Supply voltages from internal power supply	+12V +5V -12V
Down-beat indication	LED
External stop and reset	Foot-switch socket
Rhythm selection	4-bit binary code

**M**ORE and more people these days are taking an interest in making their own music and to that end electronics is playing an ever-increasing part. Witness the number of constructional articles that have appeared for synthesisers, organs, electronic pianos, musical boxes, guitars etc. An essential part of most music is rhythm and what

CODE				Snare/Claves	RHYTHM
Input 8	Input 4	Input 2	Input 1		
1	1	1	0	S	Waltz 3/4
1	1	0	1	S	Jazz Waltz 3/4
1	1	0	0	S	Tango 2/4
1	0	1	1	S	March 2/4
1	0	1	0	S	Swing 4/4
1	0	0	1	S	Foxtrot 4/4
1	0	0	0	S	Slow Rock 6/8
0	1	1	1	S	Pop Rock 4/4
0	1	1	0	S	Shuffle 2/4
0	1	0	1	C	Mambo 4/4
0	1	0	0	C	Beguine 4/4
0	0	1	1	C	Cha Cha 4/4
0	0	1	0	C	Bajon 4/4
0	0	0	1	C	Samba 4/4
0	0	0	0	C	Bossa Nova 4/4
1	1	1	1	—	No selected rhythm

Fig. 2: Table of Rhythm selection input codes. This table may be cut out and stuck on the fascia of the unit.



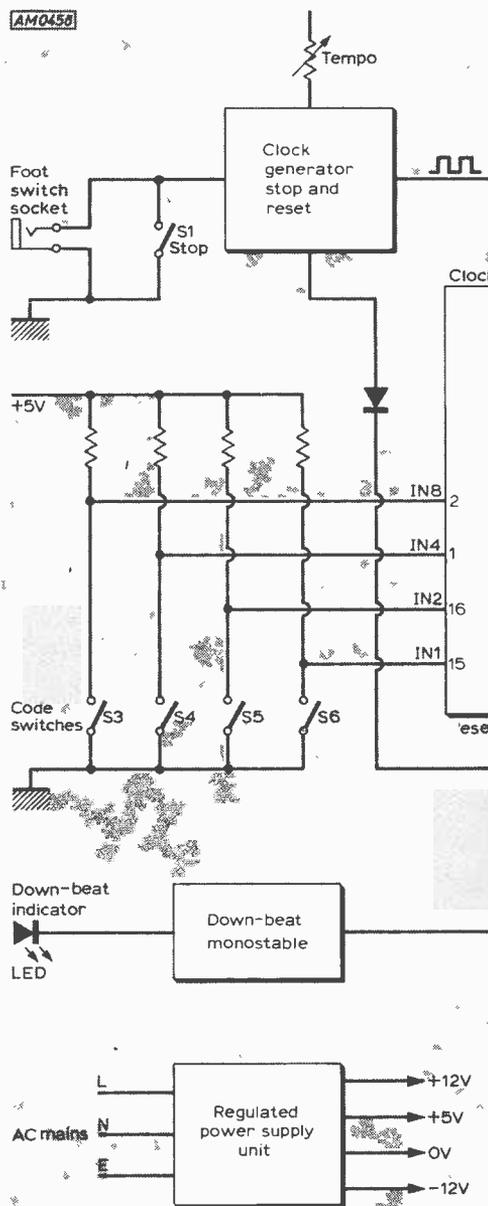


Fig. 1: Basic block diagram of the Rhythm Generator.

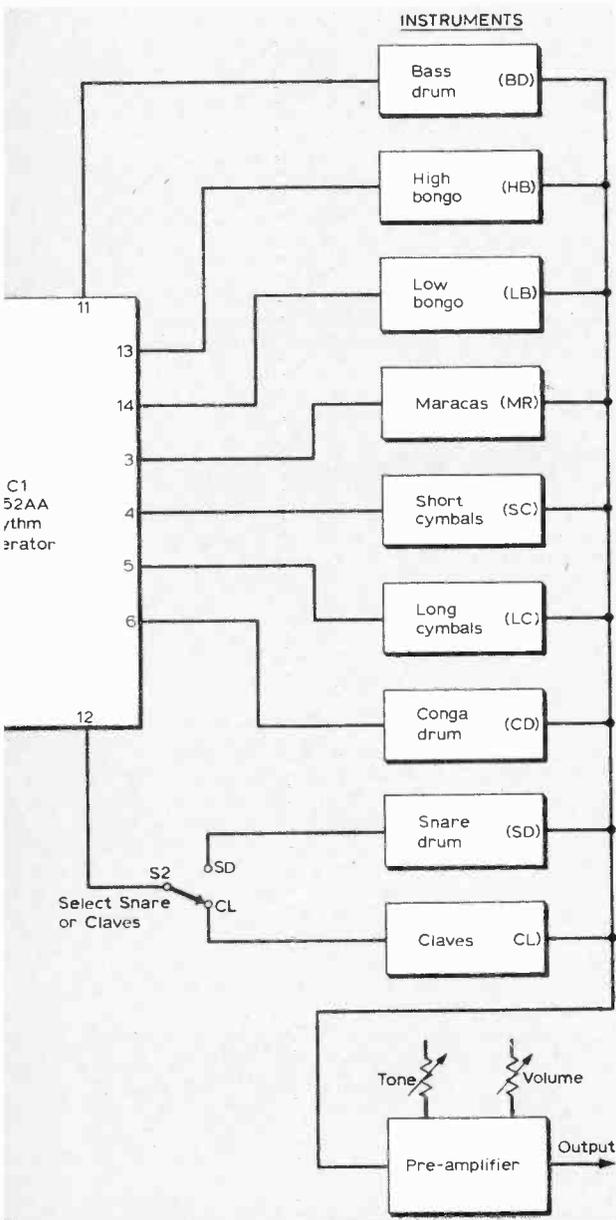

# GENERATOR

A.S.WEBB B.Sc

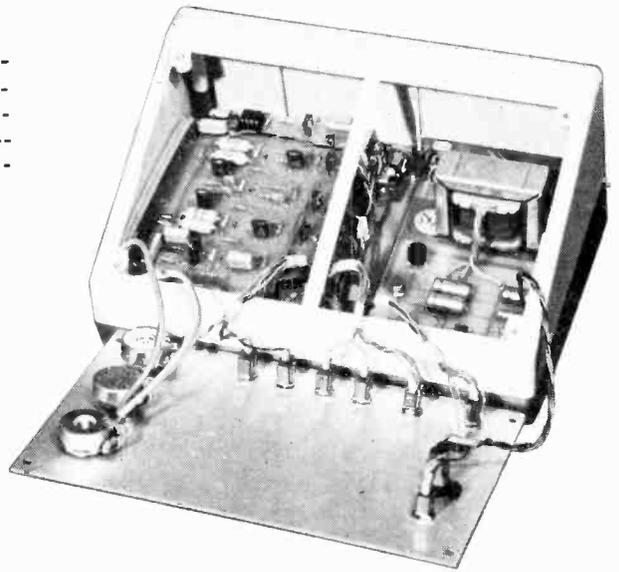

showing the M252AA integrated circuit as the heart of the system.

better method of turning a solo performance into a duo than with the addition of a drummer and full drum kit all contained in a box measuring little more than 205 x 152 x 102mm (8 x 6 x 4in)! In addition such a portable unit could well provide the rhythm section for a small group or a novel gimmick on the disco scene.

This article describes the construction of a Rhythm Generator containing **nine** percussion instruments which can be programmed to play any one of **fifteen** different rhythms. Emphasis has been placed on simplicity of construction and low cost without sacrificing the faithful reproduction of the sound of each instrument. Anyone who has had some experience of soldering and knows one end of a diode or electrolytic capacitor from the other, should, with a little care and patience, be able to make this unit. Several MOS (Metal Oxide Semiconductor) integrated circuits are used but for those who are not familiar with the handling of this type of device full instructions will be given. **In the meantime do not be tempted to remove them from the protective conducting foam packing.**

## Generator block diagram

Fig.1 shows the block diagram for the Rhythm Generator. The heart of the generator is the M252AA MOS integrated circuit manufactured by SGS-ATES. This device incorporates a memory programmed with fifteen different rhythm patterns which are selected by a 4-bit binary code. The four code inputs are designated IN8, IN4, IN2 and IN1 each one capable of being switched to '0' (i.e. '0'V, switch closed) or '1' (i.e. +5V, switch open) by S3, S4, S5, S6 respectively. Thus 16(2<sup>4</sup>) combinations are possible, fifteen of which are used to programme the following rhythms:— Waltz, Jazz Waltz, Tango, March, Swing, Foxtrot, Slow Rock, Pop Rock, Shuffle, Mambo, Beguine, Cha Cha, Bajon, Samba and Bossa Nova. Details of the particular codes are given in Fig. 2 with code 1-1-1-1 having no selected rhythm.

The chip is driven by a square wave from the

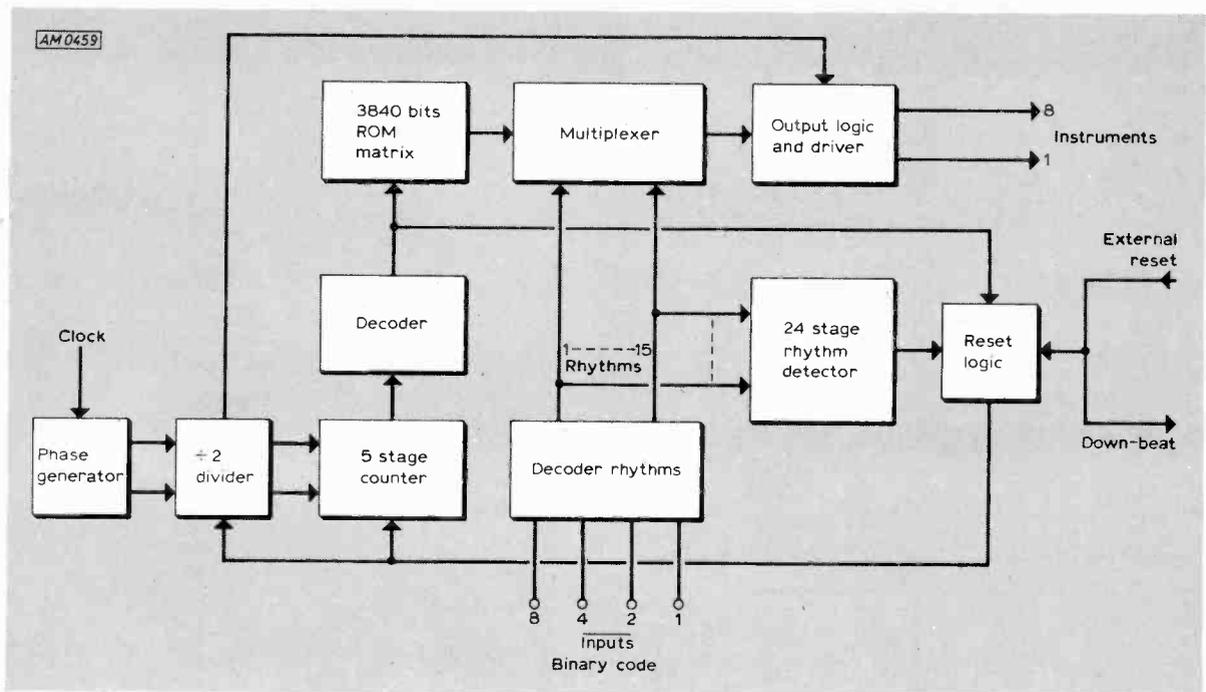


Fig. 3: Block diagram of the M252AA Rhythm Generator. Rhythms are selected by applying either a logic '1' or '0' to the input gates of the IC.

clock generator, the frequency of which determines the tempo of the rhythm. Once a code has been selected the various instruments are triggered in the correct sequence to provide the particular rhythm pattern. Only eight of the nine instruments are used at any one time, the snare drum being manually selected by S2 for the Waltz, Jazz Waltz, Tango, March, Swing, Foxtrot, Slow Rock, Pop Rock and Shuffle whilst the claves are used for the remaining South American rhythms. The outputs from the instrument simulators are combined and fed to a pre-amplifier incorporating volume and tone controls.

A down-beat indicator in the form of an LED is included to mark the beginning of each rhythm pattern. A combined stop and reset facility (S1) allows the generator to be stopped and restarted at the beginning of a bar. This feature permits the rhythm to be brought in on the down-beat after the introduction to a piece of music has been played. To make this easier while playing, a socket has been provided wired in parallel with the stop switch S1 on the panel, so that a foot operated switch may be connected.

## The M252 Rhythm Generator

The internal operation of the M252 IC is shown in Fig. 3. The clock input is first divided by two and this output drives a 5-stage counter which resets every 32 pulses for rhythms of 4/4 time and after every 24 pulses for 3/4 time. The counter states are then decoded to drive the ROM (Read Only Memory) matrix which has been pre-programmed with the fifteen different rhythms. The binary code that has been entered to select a rhythm is decoded and used to determine the reset point of the counter and to programme the multiplexer to select that

particular rhythm from the output of the memory matrix. This output is then fed to the driver circuit which modifies the pulses to make them suitable for triggering the percussion instruments. The output section also includes logic circuitry to reset the memory outputs to zero after each reading so that the output will always be able to provide the correct trigger edge during the following beat.

The internal reset pulse of the counter is routed to an output connection (pin 7) which, with the addition of a blocking diode to separate the signals, can furnish the down-beat indication as well as allowing the external resetting of the rhythm.

## Clock Generator

The clock generator circuit, see Fig. 4, is a simple astable multivibrator utilising two 2-input NAND gates (IC2b and IC2c) together with the timing components R3, VR1 and C1 to provide a square wave output to drive the M252 chip. By closing the STOP switch (S1) the clock is inhibited with its output remaining at '1' and at the same time the M252 is reset via IC2a and D1. Upon opening the switch the output immediately goes to '0' thus generating the first command pulse and the rhythm commences with the first beat of the bar i.e. the down-beat.

The frequency of the clock may be continuously varied from approximately 5Hz to 50Hz by the tempo control VR1. The relationship between the clock frequency and the rhythm tempo is given by the following formula:—

$$\text{No. of bars/min} = \frac{\text{Clock frequency} \times \text{No. of bars per rhythm pattern} \times 60}{\text{No. of counts per rhythm} \times 2}$$

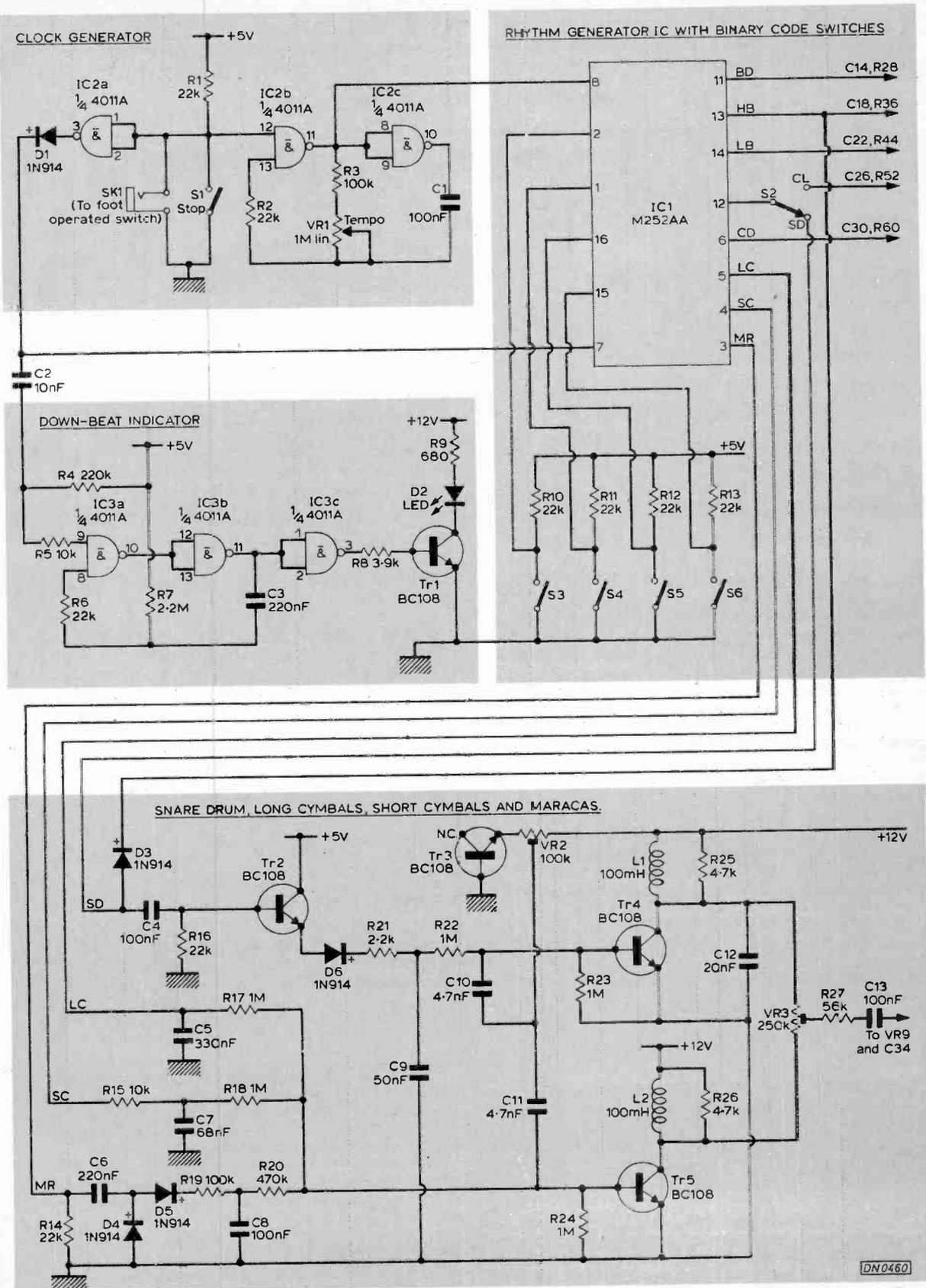


Fig. 4: Part of the circuit containing the clock generator, downbeat indicator, snare drum, long cymbals, short cymbals and maracas. These particular circuits are all housed on one PCB.


# The Black Watch kit

## £14.95!

★ **Practical**—easily built by anyone in an evening's straightforward assembly.

★ **Complete**—right down to strap and batteries.

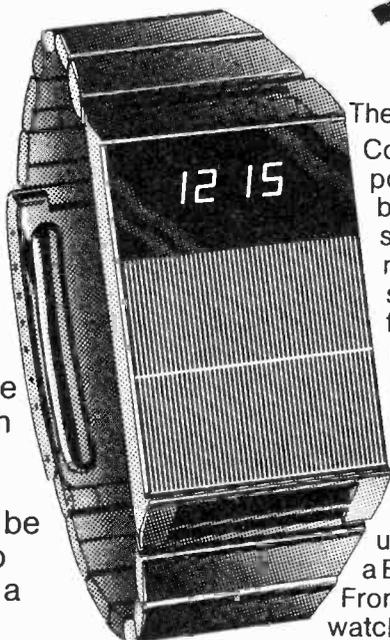★ **Guaranteed.** A correctly-assembled watch is guaranteed for a year. It works as soon as you put the batteries in. On a built watch we guarantee an accuracy within a second a day—but building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.





The Black Watch by Sinclair is unique. Controlled by a quartz crystal, and powered by two hearing aid batteries, it uses bright red LEDs to show hours and minutes, and minutes and seconds. And it's styled in the cool prestige Sinclair fashion: no knobs, no buttons, no flash.


The Black Watch kit is unique, too. It's rational—Sinclair have reduced the separate components to just four—and it's simple: anybody who can use a soldering iron can assemble a Black Watch without difficulty. From opening the kit to wearing the watch is a couple of hours' work.
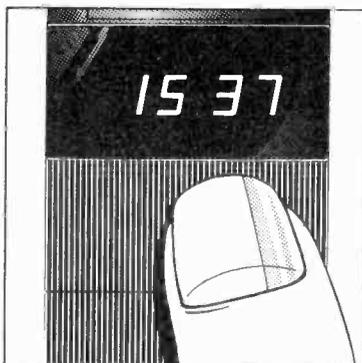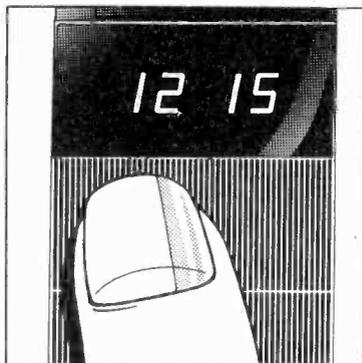
## Touch and tell

Press here for hours and minutes... here for minutes and seconds.



Batteries easily replaced at home.

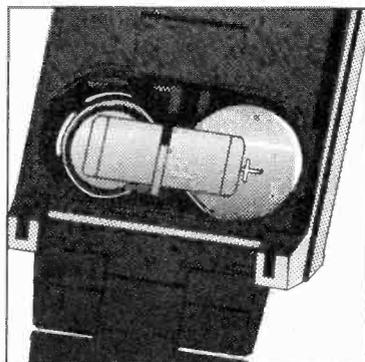

### The specialist features of the Black Watch

Smooth, chunky, matt-black case, with black strap. (Black stainless-steel bracelet available as extra—see order form.)

Large, bright, red display—easily read at night. Touch-and-see case—no unprofessional buttons.

Runs on two hearing-aid batteries (supplied). Easily re-set using special button—no expensive jeweller's service.

# The Black Watch – using the unique Sinclair-designed state-of-the-art IC.

## The chip ...

The heart of the Black Watch is a unique IC designed by Sinclair and custom-built for them using state-of-the-art technology – integrated injection logic.


This chip of silicon measures only 3 mm x 3 mm and contains over 2000 transistors. The circuit includes

- a) reference oscillator
- b) divider chain
- c) decoder circuits
- d) display inhibit circuits
- e) display driving circuits.

The chip is totally designed and manufactured in the UK, and is the first design to incorporate *all* circuitry for a digital watch on a single chip.
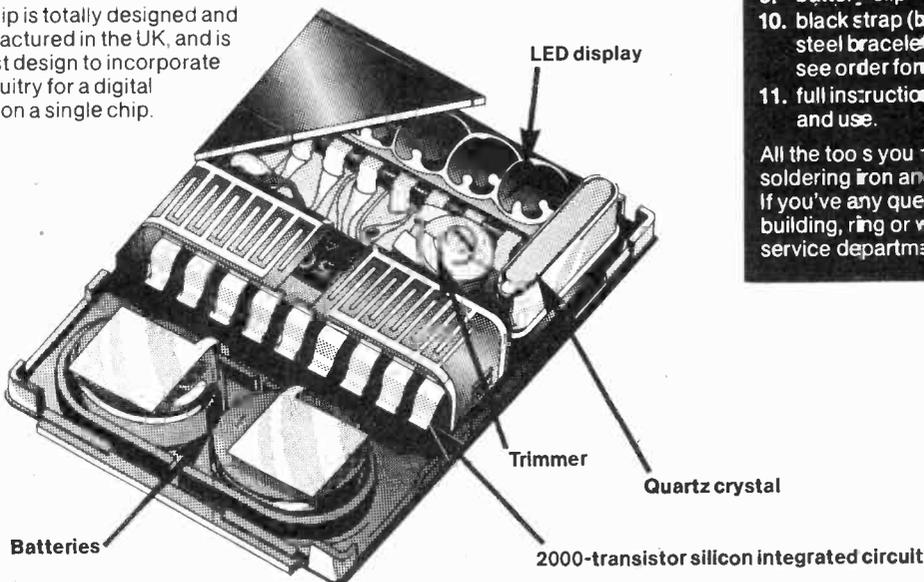
## ... and how it works

A crystal-controlled reference is used to drive a chain of 15 binary dividers which reduce the frequency from 32,768 Hz to 1 Hz. This accurate signal is then counted into units of seconds, minutes, and hours, and on request the stored information is processed by the decoders and display drivers to feed the four 7-segment LED displays. When the display is not in operation, special power-saving circuits on the chip reduce current consumption to only a few microamps.



# Complete kit £14.95!

## The kit contains

1. printed circuit board
2. unique Sinclair-designed IC
3. encapsulated quartz crystal
4. trimmer
5. capacitor
6. LED display
7. 2-part case with window in position
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra – see order form)
11. full instructions for building and use.

All the tools you need are a fine soldering iron and a pair of cutters. If you've any queries or problems in building, ring or write to Sinclair service department for help.

## Take advantage of this no-risks, money-back offer today!

The Sinclair Black Watch is fully guaranteed. Return your kit in original condition within 10 days and we'll refund your money without question. All parts are tested and checked before despatch – and correctly-assembled watches are guaranteed for one year. Simply fill in the FREEPOST order form and post it – today!

**Price in kit form: £14.95 (inc. black strap, VAT, p & p).**

**Price in built form: £24.95 (inc. black strap, VAT, p&p).**

# sinclair

Sinclair Radionics Ltd,  
London Road, St Ives,  
Huntingdon, Cambs., PE17 4HJ.  
Tel: St Ives (0480) 64646.

Reg. no: 699483 England. VAT Reg. no: 213817088.

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me

Total £

..... (qty) Sinclair Black Watch kit(s) at £14.95 (inc. black strap, VAT, p&p) .....

\* I enclose cheque for £..... made out to Sinclair Radionics Ltd and crossed.

..... (qty) Sinclair Black Watch(es) built at £24.95 (inc. black strap, VAT, p&p) .....

\* Please debit my \*Barclaycard/Access/ American Express account number

..... (qty) black stainless-steel bracelet(s) at £2.00 (inc. VAT, p&p) .....

Name (please print) \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

Signature \_\_\_\_\_

PW/5

FREEPOST – no stamp required.

\* Delete as required

# ★ components list

## Resistors

R1	22kΩ	R38	27kΩ
R2	22kΩ	R39	150kΩ
R3	100kΩ	R40	68kΩ
R4	22kΩ	R41	10kΩ
R5	10kΩ	R42	68kΩ
R6	22kΩ	R43	390kΩ
R7	2·2MΩ	R44	12kΩ
R8	3·9kΩ	R45	47kΩ
R9	680	R46	27kΩ
R10	22kΩ	R47	150kΩ
R11	22kΩ	R48	68kΩ
R12	22kΩ	R49	10kΩ
R13	22kΩ	R50	68kΩ
R14	22kΩ	R51	390kΩ
R15	10kΩ	R52	12kΩ
R16	22kΩ	R53	47kΩ
R17	1MΩ	R54	27kΩ
R18	1MΩ	R55	150kΩ
R19	100kΩ	R56	68kΩ
R20	470kΩ	R57	10kΩ
R21	2·2kΩ	R58	68kΩ
R22	1MΩ	R59	1MΩ
R23	1MΩ	R60	12kΩ
R24	1MΩ	R61	47kΩ
R25	4·7kΩ	R62	27kΩ
R26	4·7kΩ	R63	150kΩ
R27	56kΩ	R64	68kΩ
R28	12kΩ	R65	10kΩ
R29	47kΩ	R66	68kΩ
R30	27kΩ	R67	390kΩ
R31	150kΩ	R68	10kΩ
R32	68kΩ	R69	390kΩ
R33	10kΩ	R70	10kΩ
R34	68kΩ	R71	2·2kΩ
R35	100kΩ	R72	2·2kΩ
R36	12kΩ	R73	22kΩ
R37	47kΩ	R74	22kΩ

All ½ watt 5%

VR1	1MΩ linear	VR7	500kΩ
VR2	100kΩ	VR8	500kΩ
VR3	250kΩ	VR9	10kΩ
VR4	500kΩ	VR10	25kΩ linear
VR5	500kΩ	VR11	10kΩ log
VR6	500kΩ		

VR2 to 9 Skeleton Preset Subminiature Vertical

## Capacitors

C1	100nF	Polyester	C23	12nF	Polyester
C2	10nF	Mylar 10%	C24	40nF	Mylar 10%
C3	220nF	Polyester	C25	12nF	Polyester
C4	100nF	Polyester	C26	4·7nF	Ceramic
C5	330nF	Polyester	C27	1·5nF	Ceramic
C6	220nF	Polyester	C28	4·7nF	Ceramic
C7	68nF	Polyester	C29	1·5nF	Ceramic
C8	100nF	Polyester	C30	50nF	Mylar 10%
C9	50nF	Mylar 10%	C31	18nF	Polyester
C10	4·7nF	Ceramic	C32	50nF	Mylar 10%
C11	4·7nF	Ceramic	C33	18nF	Polyester
C12	20nF	Mylar 10%	C34	220nF	Polyester
C13	100nF	Polyester	C35	100nF	Polyester
C14	150nF	Polyester	C36	220nF	Polyester
C15	47nF	Polyester	C37	100μF	25 V
C16	150nF	Polyester	C38	100μF	25 V
C17	47nF	Polyester	C39	100μF	25 V
C18	33nF	Polyester	C40	10μF	25 V
C19	10nF	Mylar 10%	C41	10μF	25 V
C20	33nF	Polyester	C42	100μF	25 V
C21	10nF	Mylar 10%	C43	100μF	25 V
C22	40nF	Mylar 10%			

Capacitors C19, C20, C21, C23, C24 and C25 are the most important and 5% types could be used if available (see text).

Polyester are Mullard C280 except C23, 25, 31 and 33 which are C296A.

## Semiconductors

Tr1	BC108B	D10	1N914
Tr2	BC108B	D11	1N914
Tr3	BC108B	D12	1N914
Tr4	BC108B	D13	} Bridge Rectifier 100 PIV 1A
Tr5	BC108B	D14	
Tr6	2N1132 or equivalent	D15	
Tr7	BFY51 or equivalent	D16	5V6 zener 400mW
IC1	M252AA	D17	12V zener 400mW
IC2	CD4011A	D18	1N914
IC3	CD4011A		
IC4	CD4011A		
IC5	741 Op Amp		
IC6	Regulator 12V 100mA TBA 625B		
D1	1N914		
D2	LED 0·2"		
D3	1N914		
D4	1N914		
D5	1N914		
D6	1N914		
D7	1N914		
D8	1N914		
D9	1N914		

## Miscellaneous


T1	Mains Transformer 15-0-15 V 100mA
S1, S3, S4, S5, S6	SPST miniature toggle switch
S2	SPDT miniature toggle switch
S7	SPST miniature mains toggle switch
L1, L2	SC60 miniature Choke 100mH
F1	20mm Fuse 250mA anti-surge plus panel mounting fuseholder (12mm hole fixing)
SK1	2 way jack socket 6·5mm
LP1	Mains neon indicator
3	Printed circuit boards
1	16 pin DIL socket
3	14 pin DIL socket
1	8 pin DIL socket
1	Case type 65-2523E (Veroboard)
3	Knobs with graduated skirt dia. 30mm
4	Vero Stand-offs type B. 19mm long (22-1419H)

Length single screened wire. Length 3-core mains lead. Rubber grommets. Vero half pins type 18-0223 K

The author acknowledges the assistance of Watford Electronics with this project.

## COLLATED LIST FOR RESISTORS AND CAPACITORS

Resistors	Capacitors		
1	680Ω	2	1·5nF Ceramic
3	2·2kΩ	4	4·7nF Ceramic
1	3·9kΩ	3	10nF Mylar 10%
2	4·7kΩ	2	12nF Polyester (Mullard C296A)
9	10kΩ	2	18nF Polyester
5	12kΩ	1	20nF Mylar 10%
12	22kΩ	2	33nF Polyester (Mullard C280)
5	27kΩ	2	40nF Polyester
5	47kΩ	2	47nF Polyester
1	56kΩ	3	50nF Mylar 10%
10	68kΩ	1	68nF Polyester
3	100kΩ	5	100nF Polyester
5	150kΩ	2	150nF Polyester
4	390kΩ	4	220nF Polyester
1	470kΩ	1	330nF Polyester
6	1MΩ	2	10μF 25V
1	2·2MΩ	5	100μF 25V

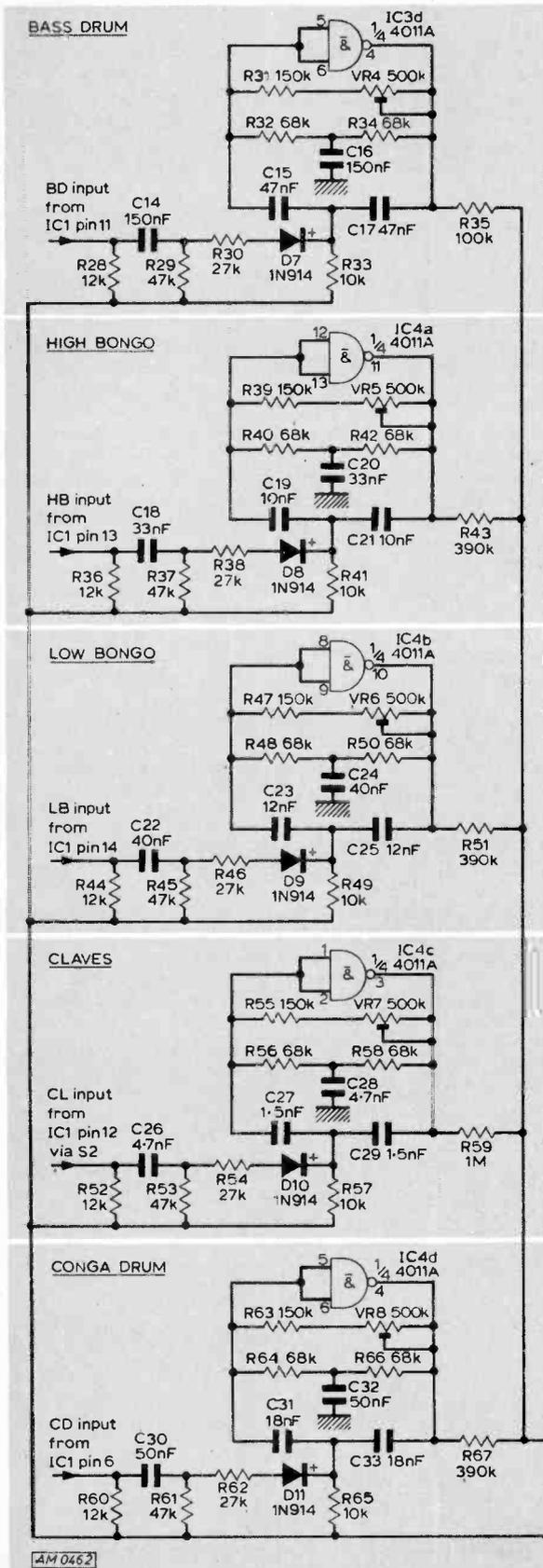

AM 0461


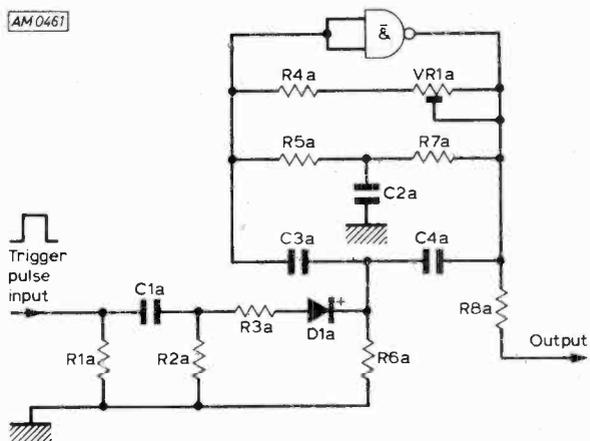
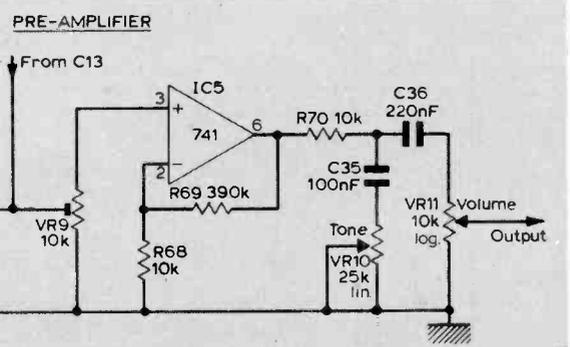


Fig. 5: Basic circuit of a damped sinusoidal oscillator, comprising a 'Twin-T' ringing oscillator utilising a NAND gate.

For rhythms of 4/4 time and for the March and Tango the number of counts per rhythm pattern is 32, each rhythm pattern covering two bars. The tempo is thus variable from approximately 9 to 94 bars/min. In the case of rhythms of 3/4 and 6/8 time the counter resets after 24 pulses and there are two bars per rhythm pattern giving a tempo from 13 to 125 bars/min.

The Shuffle, 2/4 time, has four bars per rhythm pattern and resets after 24 pulses giving a variation of 25 bars/min to 250 bars/min which is twice the tempo of the Waltz and over 2½ times that of the 4/4 rhythms, for the same setting of VR1. It is for this reason that the tempo control covers such a wide range and will need adjustment especially when

Fig. 6: Circuit diagram left shows the five ringing oscillators for bass drum, high and low bongos, claves and conga drum. All five circuits feed into a pre-amplifier. The circuit below shows the various power requirements for the IC's

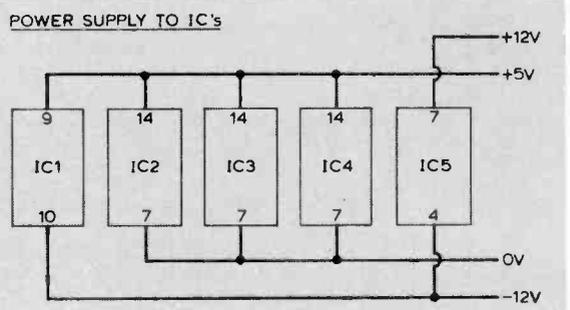

AM 0462

changing to the Shuffle. To facilitate the exact setting of the tempo, control knobs of the type with a graduated skirt are recommended.

The internal reset pulse of the generator chip is only 2 to  $3\mu\text{S}$  long so it is too short to light a lamp. It is also necessary that the lamp should light on the negative edge of the reset pulse which occurs at the beginning of the bar. The down-beat monostable circuit, see Fig. 4, comprises C2, C3, R4, R5, R6, R7, IC3a and IC3b. It lengthens the short down-beat trigger pulse to around 350mS by latching the output of IC3b to '0' until C3 has charged up to above the '1' input trigger level of IC3a. It operates on negative-going pulses only and the resulting '0' output from IC3b is inverted by the NAND gate IC3c to switch on Tr1 thus lighting the LED.

## Percussion Instruments

The percussion instruments may be divided into two categories, those that consist of damped sinusoidal oscillations and those consisting of damped filtered white noise. In the first category are included the bass drum, high bongo, low bongo, conga drum and claves. The general circuit shown in Fig. 5 consists of a simple twin-T ringing oscillator utilising a NAND gate which is adjusted to a point slightly below oscillation by VR1a. The different sound of each instrument is achieved by choosing the correct values of C2a and C3a to determine the required frequency of operation and by regulating its decay time (damping) by VR1a to obtain longer or shorter sounds.

The trigger pulse from the M252 is a square wave which must be differentiated by C1a and R2a and allowed one-way entry by diode D1a to produce a short pulse which is sufficient to set the oscillator ringing but not to interfere with the damping of the oscillation. Resistor R1a is necessary to keep the input at earth in the absence of a command pulse since the outputs of the M252 are open drain types.

Fig. 6 shows the circuit of the five ringing oscillators used and gives values for the three frequency determining capacitors for each instrument. The tolerance of these capacitors is not too critical but it should be kept within 20%, which is reflected in the types specified in the component list.

However, a problem does exist in the case of the high and low bongos. The frequency of operation and therefore the capacitor values of these two instruments is very close and 10% tolerance has been specified in this instance. This still means it is possible in an extreme case that the frequencies of operation could be identical and if this does occur 5% types may be substituted to overcome the problem.

In the second category falls the long cymbals, short cymbals and maracas, for which the basic type of circuit is shown in Fig. 7. Transistor Tr1b is switched on during the short trigger pulse from the M252 chip and charges C2b. This capacitor then discharges through R4b to the base of Tr3b. The white noise produced by Tr2b by the zener effect of the reverse biased base-emitter junction is also applied to the base of Tr3b via C3b. During the discharge of C2b, Tr3b can amplify this noise. The degree of amplification, however, follows the discharge curve of C2b and therefore a damping of a variable length is obtained depending on the values of C2b and R4b. The inductor L1b and the capacitor C4b allow selective amplification of certain frequencies to obtain a more realistic sound of the instrument being simulated.

The distinctive metallic sound of the snare drum caused in the real instrument by catgut snares stretched across the drum-head is realistically simulated by combining filtered white noise from this circuit with high bongo. The long cymbal and short cymbal circuits dispense with Tr1b and differ only in decay time. The maracas simulator is unusual in that it is the only instrument in which the sound increases gradually and then decays. This effect is achieved by means of an integrator-differentiator circuit D4, D5, R19, R20 and C8, see Fig. 4.

## Pre-amplifier

The outputs of the nine instruments are mixed and fed to the input of the pre-amplifier through the preset potentiometer VR9, Fig. 6. The active element of the amplifier is the ubiquitous 741 op.amp used in the non-inverting mode. A simple variable low-pass filter, C35 VR10, acts as a tone control and the output level is adjustable by means of the potentiometer VR11.

**PART 2**, to be published next month, will cover details of the power supply, PCB's, construction and setting-up.

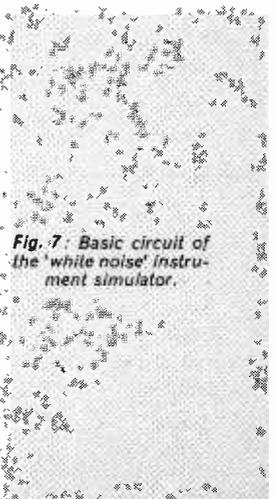
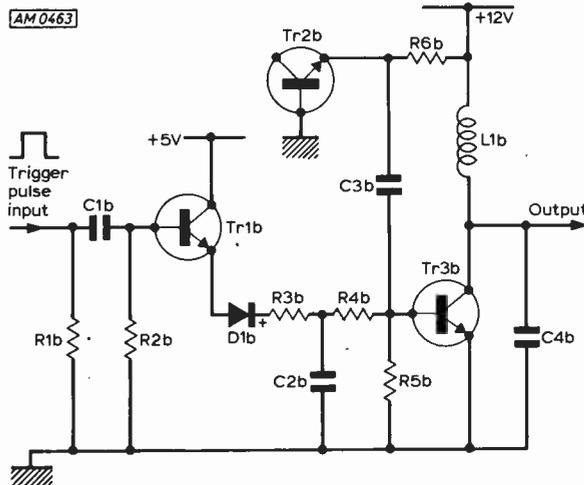


Fig. 7: Basic circuit of the 'white noise' instrument simulator.

MORE

# HOTLINES

ON RECENT DEVELOPMENTS

## THE FLASHER

If it's escaped your attention, the LM3909 chip is well worth looking at if you need some form of flashing light. In its simplest form the IC needs only a 1.5V battery and a suitable capacitor to make a flashing light which will keep going for a very long time—like two years with an alkaline cell. One useful circuit suggested by the manufacturers is to mount the chip, i.e.d. and capacitor into the base of a torch. The tiny flashing light can be seen in the dark making it easy to always find your torch. Ideas for toys, models etc. come readily to mind and I reckon that this IC will fast become a favourite with amateur constructors.

## LIQUID CRYSTAL PICS.

Electronics and photography have always been close allies for the hobbyist. Of interest to both will be the work being carried out at the Hughes Aircraft Company. Researchers there are working on what they call a light cell. The idea is to enhance the image being reproduced. To do this photographically is not so easy, and present electronic solutions are not ideal.

The Hughes approach is quite ingenious. The light from the desired image (i.e. the varying tones formed by the brightness of the light in the various parts of the image) is allowed to strike a cadmium-sulphide layer which modulates the resistivity of the photoconductive layer. This in turn varies the voltage which is applied to a liquid crystal layer. The characteristics of the liquid crystal can be altered thus giving control over the image which is finally transmitted. Resolution is presently 60 lines/millimetre and the device requires only 6V.

## COMPUTER-FACILITY FOR £7.50

A new general-purpose micro-processor shortly to be introduced by National Semiconductor, and priced around £7.50 in quantity lots, is expected to generate keen interest in present users of Random Logic.

SC/MP is an 8-bit PMOS micro-processor operating at 2 microsec cycle time and requiring only a single 12V supply with a useful margin of  $\pm 2V$ . It generates its own timing on the chip, and will be ideally suited to simple control and timing functions.

Designers working with appliance controls, building monitors, fuel-injection units, traffic signal control, word-processing systems, electronic toys, etc. will find the SC/MP right in both design and cost, claims N.S.

Multiple SC/MP can communicate with each other when they share a common bus. Logic on each chip senses when the bus is in use, so when one SC/MP ceases transmission (or reception) the next can take over. If it declines, the next but one is invited.

A simple control system can be developed using one SC/MP and a programme memory—which can be selected from a wide range of standard memory parts. Such a system could access up to 4 kilobits of memory and could provide the control logic for simple industrial systems, TV games, small traffic-control systems, etc.

## I.R. HEADSETS

A recent development in the West German colour television market has caused quite a stir among other Europeans. Apparently infrared audio headsets are now becoming in-

creasingly common as a standard fitment to the receivers. Another application of the infrared audio system is to teach children whose hearing is impaired. The infrared is transmitted to a minute IR receiver which is an integral part of the headphones thus leaving one free to move about anywhere within the range of the IR beam. One German company is readying a two-channel stereo transmission system. The signals for each of the two channels is modulated onto two separate carriers. These are set at 200kHz and 280kHz. These frequencies are then transmitted via the infrared beams.

## VIDEO DISCS

The video home-player scene has taken on a new look. A large French company recently confessed that it is going into production with an inexpensive optical video disc-player. What is interesting is that the company, looking some years ahead, sees the distinct possibility of cheap throw-away video discs which will be sold at newsagents just like magazines.

## GAMING CHIPS

In a previous issue (*Hotlines, Practical Wireless*, March 1976) I mentioned tv games. US semiconductor giant Fairchild has announced that it is going into this area in a big way. Plans haven't been completely revealed as yet but it would seem promising for the home constructor if this company were to start manufacturing chips specifically designed for things like tele-tennis, tele-football etc. Please note; they haven't started making them so don't look for ICs yet a while.

## OUR CQ "COLUMN"

If you wish to have a "CQ" request in *Practical Wireless*, we would be grateful if you could write it out in the same style we print it. This helps us to help you by saving time trying to take extracts from long letters and deciphering names and addresses.

Thank you.

Please mention

# PRACTICAL WIRELESS

when replying to  
advertisements

# PRODUCTION LINES

colin riches

## ITT SOUNDERS

ITT are marketing a range of piezo ceramic sounders. The smaller ones shown in the picture comprise a thin piezo-electric vibrator and solid-state oscillator. One very special feature of the units is their exceedingly low power consumption with high sound pressure level.

The circular device at the top left of the photograph is Model U2-50RD1D2H which gives a continuous short pulsed or long pulsed tone facility from 24V. Operating voltage is 5-35V at 10mA with an oscillating frequency of 2-7kHz. Sound level is over 90dB. The small black sounder (centre)—the U5-35R runs at 4mA with a continuous tone only. Output is over 70dB. The bottom left unit (U1-50RD2) has continuous or long pulsed tones and runs on 12V at 10mA. The bottom right unit (U3-5DR) is a 24V continuous tone sounder which draws 8mA.


The sounders make very good alarms for use inside the home i.e. they could be wired to fire alarms, smoke detectors, mains failure alarms for freezers etc. etc. and their very low current consumption makes them ideal for this purpose.

The horn-type sounder RHA 102 (top right) is a real "ear-splitter" which incorporates a sensitive drive unit and solid-state oscillator amplifier. Two separate tones are provided—warble at 1200Hz-1700Hz at 180 c.p. minute, and continuous 1000Hz, and these can be used individually by connecting the appropriate pair of wires to the 12V d.c. supply. Current consumption of this model is 400mA and it pushes out 98dB of noise making it eminently suitable for applications where warning signals are required e.g. fire and intruder systems, factories, hotels, vehicle alarms and so on. Prices, not yet fixed are believed to be quite reasonable. Further gen by sending a stamped addressed envelope to Mr. K. W. Stanton, ITT Components Group Europe, Standard Telephones and Cables Ltd., Materials Division, (Dept. P.W.) Edinburgh Way, Harlow, Essex SM20 2DE. Phone Harlow 26811.
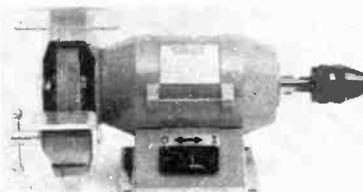
## BENCH GRINDERS


Industrial power tool manufacturers, Wolf Electric Tools Ltd., have introduced two new 5in (125mm) Bench Grinders to complement their 6in. and 8in. industrial model range. The new machines are designed for light industrial and home workshop use and those of you who are still of the "Chassis bashing fraternity".

Model 8252 is fitted with an 80 grit fine grinding wheel and a 60 grit coarse wheel while the more versatile model 8159 is fitted with a 80 grit grinding wheel and an 8mm chuck, enabling its use with small accessories for polishing, sanding etc.




Both models are supplied with adjustable tool rests and eye protection for grinding work. Recommended price of either model is, £41.95, excluding V.A.T. Wolf Electric Tools Ltd., (Dept. P.W.) Station House, Harrow Road, Wembley HA9 6TJ.

## EQUIPMENT CASES

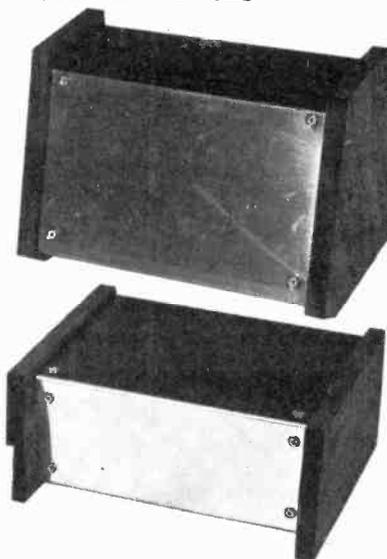

H.M. Electronics have announced two rather attractive equipment cases. Model DC.1 (with the sloping front) which, say the makers, was designed with digital clocks in mind, can also be used for mixer units, electronic dice or some of the many projects published in our pages. The second case is the Mini-bec case which measures 7in x 3in. (or the decimal 178mm x 76mm). Both units would give home-built equipment a really professional finish for they are well-made in aluminium with black crackle tops with teak end sections. In addition, the DC.1 has a green front panel. Prices: the DC.1 costs £3.75 + 75p post and packing incl. VAT and the Mini-bec is priced at £2.99 + 75p post and packing incl. VAT. Further information from H.M. Electronics, (Dept. P.W.) 275a Fulwood Road, Sheffield S10 3BD.

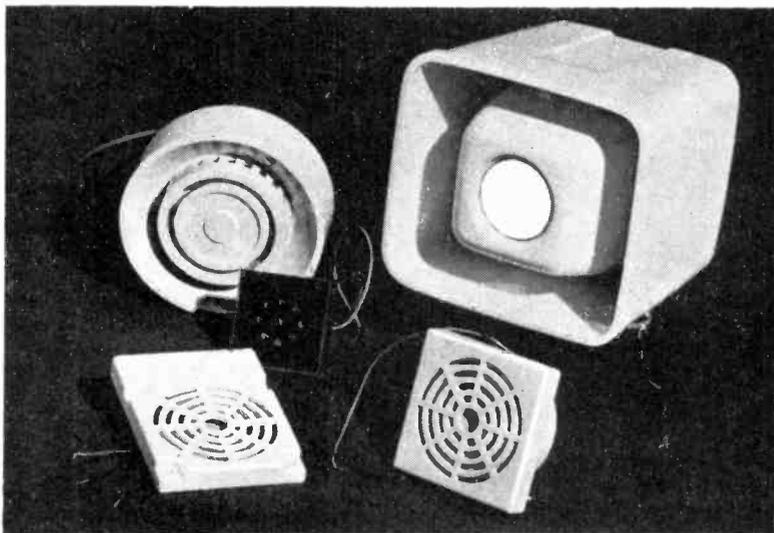


## ADC ACCUTRAC

A unique electronic turntable—the "Accutrac"—operated by remote control—has been introduced by Audio Dynamics Corporation, a subsidiary of BSR Ltd.

The Accutrac 4000, the first of three units on the market comprises three separate but interrelated component pieces; the automatic direct drive electronic turntable, a remote receiver and a hand-held cordless transmitter. From the comfort of an easy chair, listeners can programme exactly what they want to hear on a given album by selecting tracks indicated numerically on the transmitter. The message is then transmitted to the receiver, which is located in convenient proximity to the turntable and the receiver in turn activates the turntable's arm, which places the stylus precisely at the beginning of the track selected by the listener. The receiver's L.E.D. (Light Emitting Diode) winking "eye" lets the listener know that the information has been received and held in total memory.

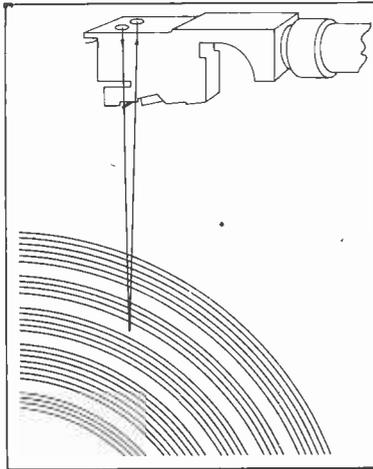Up to twenty-four commands can be programmed in any order required. The transmitter can also be pro-



grammed to reject, cue, repeat and clear, as well as play, in fact virtually all you have to do is to place a record on the turntable. Track selection can be determined by a quick look at the album jacket and favourite selections can be repeated over and over again without the listener even having to move an inch.


How does the Accutrac actually work? The Accutrac process begins with the logic circuitry built into the turntable, a direct drive unit. In the Accutrac system, there are electronic speed-sensing circuits within the motor itself, constantly monitoring the turntable's speed accuracy and instantaneously correcting the speed.

In a sense, Accutrac has 'eyes'. A tiny solid-state infra-red generator and detector is built into the special ADC LMA-1 cartridge (an advanced version of the XLM). The generator focuses a tiny beam of infra-red light onto the record and senses the surface of the disc. Although the arm is raised, lowered and moved automatically by its own servo-motor, it always tracks the groove with perfect freedom because from the instant the stylus touches the record, the arm is totally decoupled from the servo-motor and controls.

Separate control circuits for each speed allow individual adjustment and switching from 33 to 45 rpm now involves just a simple reliable switch—no mechanisms. In order to prevent floor shake, footsteps or acoustic feedback from reaching the stylus in the groove, the arm and motorboard are suspended on springs that have been computer-calibrated to provide maximum isolation and security. Price is about £300. *BSR Limited (Dept. P.W.), Powke Lane, Cradley Heath, Warley, West Midlands, B64 5QH, England.*

*Diagram showing the infra-red Tx/Rx (left). The Accutrac deck with remote control Tx/Rx (below).*
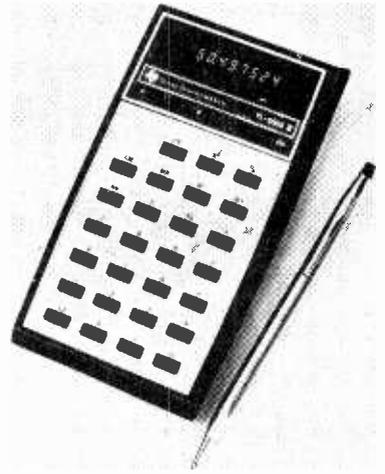
## 8-FUNCTION CALCULATOR WITH CONSTANT AND MEMORY ANNOUNCED BY T.I.



A new 8-function electronic calculator recently launched by the European Calculator Division of Texas Instruments Limited is designated the TI-2550-II. The new calculator features the basic five functions—add, subtract, multiply, divide, and percent—with an automatic constant on all five functions plus a full four-key memory (memory plus, memory minus, memory recall, and clear memory). In addition it features the widely used slide rule calculator functions of square root, square and reciprocal. Recommended retail price of this new calculator is £29.95 inc. V.A.T. and accessories.

The "reverse key" is especially useful to divide the quantity in the memory by the quantity in the display. The square root, square, and reciprocal keys operate only on the displayed quantity; they do not complete any pending operation. Thus, the calculator can easily solve problems such as the square root of the sum of squares without using the memory.


For maximum readability, the negative sign is always displayed immediately to the left of the first displayed digit. A ninth character on the extreme left of the display is used to indicate a quantity stored in the memory as an error and overflow indication.

Packaged in a 5.8 by 3.2 by 1.25 in. (14.7 x 8.1 x 3.2cm) case and weighing less than 8 ounces (230 grammes), the TI-2550-II comes with battery pack containing two fast-charge nickel-cadmium batteries, the AC9900 adapter/charger and owner's manual. *Texas Instruments Ltd., (Dept. P.W.) 165 Bath Road, Slough SL1 4AD Berkshire. Telephone Slough 35544.*

adjacent to the coil, keeping the connecting leads as short as possible, thinking that these new "electrics" might cause interference to the car's radio. In the event it was possible to switch from normal to electronic ignition without any difference being noted to the general noise level on the radio. The holes in the box were drilled out to take 1/4 in. bolts, one fitted with a soldering tag to take the black chassis lead from the unit. All existing push-on tags were retained, spade tags being fitted to the leads from the unit. At any time the unit can be removed and the wiring replaced in a couple of minutes.

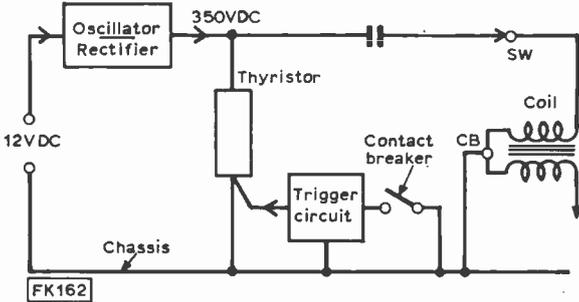
## ON THE ROAD

The installation instructions are very good. If more than one wire is found on the "SW" terminal of the coil all should be removed and connected to the blue wire from the unit. A short piece of insulating sleeving was fitted over each exposed connection and the wires taped together neatly. Some slack was left in the wires to allow for movement of the engine on its mountings.



Basic circuit of a capacity discharge ignition system. There are many variations of this theme to be found.

The Herald, normally driven by the daughter of the family, was left out in the open during the cold spell and the engine started every morning after the second go on the starter plus half the usual amount of choke. This was a distinct improvement on the normal performance in average temperatures. To the reviewer this aspect of electronic ignition is most important with the consequent saving in wear and tear on the battery and the starter. Performance at speed was noticeably better, the car seeming to have more power and to run more smoothly in the 60 to 70mph range, no doubt due to the virtual elimination of the contact breaker bounce problem at high engine speeds. There was a certain amount

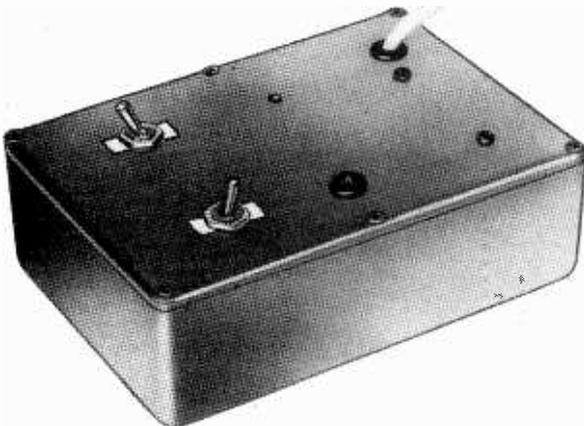

The completed unit, ready for installation in the car. The switches are shown in their 'anti-thief' positions. Electronic ignition is operative with both switches to the right and normal ignition when they are to the left. A small neon lamp protrudes through the grommet, bottom centre, lighting when the unit is functioning properly.

of rough running at low speeds especially when the foot was lifted from the accelerator. At this point no attention had been paid to the sparking plugs or contact breaker which had been in use for several thousand miles without attention other than checking the gaps from time to time.

## CONCLUSIONS

New plugs and contact breaker set were fitted and the rough running disappeared, gaps being set at the usual 25 and 15 thou respectively. Increased gap on the plugs is usually recommended with electronic ignition but this has not been tried yet. Daughter normally keeps a record of petrol bought and miles run so this was very useful in trying to assess whether there was an improvement in petrol consumption. It is unfortunate that a lot of rubbish is written about sensational improvements in this field with electronic ignition but it is seldom borne out in practice. An improvement of about two miles a gallon was found but a lot more mileage will have to be run before a definite figure could be given.

No doubt if the Herald were kept in tip-top order with frequent checks on engine performance with test equipment the electronic ignition would not make so much difference to its performance, except at high speeds, but the Herald was an ordinary car, receiving less care than it really deserves, yet it benefited considerably from the electronic ignition. Considering the price of the Bi-Pre-Pak kit it is a very good investment indeed.

The Super Spark Ignition Kit is available from Bi-Pre-Pak for £9.09 including VAT and post and packing from 222 West Road, Westcliff-on-Sea, Essex SS0 9DE. A.E.D.



## ISSUES WANTED

- ..issues of P.W. (either 1969 or 1970) containing details of a short wave converter (used RCA CA3028).—W. D. Smith, 46 Santon Way, Seascale, Cumb.
- ..issues of P.W. containing details of mods to the 19 set (? 1960).—D. Collings, c/o Glossop School, Talbot Road, Glossop SK13, Derbyshire.
- ..P.W. March and April 1971. Also P.W. May 1972. S. Brown, 12 Waverley Road, Middleton, Manchester, M24 3JG.
- ..P.W. July 1961 and August 1961—G. Farrer, 16 Duncan Road, Gillingham, Kent.

## INFORMATION WANTED

- ..manual and circuit diagram for Pye Ranger 2207V.—C. Sedgwick, 38 Eaton Road, Kempton, Beds., MK42 7RP.
- ..on Pamphonic type 601A, 601B (or Cossor 601A and 601B) amplifiers.—D. Evans, 29 Malton Road, Liverpool, L25 8QU.

## EQUIPMENT FOR DISPOSAL

- ..60 Practical Wireless's from 1971 to 1975, resistors, capacitors, (fixed and variable), transistors, (PNP and NPN with long leads), speakers (3 ohms to 35 ohms), valves (DL96, DAF types). Please send a stamped addressed envelope for a list.—J. Owens, 26 Ardd Fawr, Dolgellau, N. Wales.

# How to get a reputation overnight for making Hi Fi equipment as good as ours.



To be perfectly honest, it's not that difficult.

Simply go out and buy a Goldring CK2 turntable construction kit. Follow the simple step by step instructions.

And in no time at all you'll be the proud owner of a superb, hand built, precision engineered deck.

Which can hardly fail to make your reputation amongst those who know about HiFi. And all achieved with the minimum capital outlay: around £28.00.

The Goldring CK2 kit is, in fact, based around the rather more widely known G102 turntable.

Which means it's belt driven, to reduce wow, flutter and rumble to an absolute minimum. (The same system most really expensive decks employ.)

The pick-up arm features a viscously damped raising and lowering device.


For the protection of your records, there's an anti-skate mechanism. And with an

easily adjustable playing weight, the arm will accept a wide range of cartridges, such as the Goldring G800.

A final touch is that both the on-off function and speed selection are via neat rocker switches.

If you fill in the coupon, we'll send you our free colour brochure, which describes the CK2 construction unit in detail.

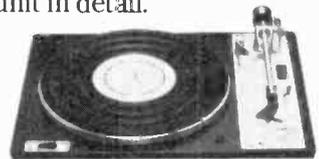And if you're serious about HiFi, you couldn't hope to ask for a better start than that.



To: Goldring Limited, 10 Bayford Street, Hackney, London E8 3SE.  
Please tell me more about the Goldring CK2 Construction unit.

Name \_\_\_\_\_

Address \_\_\_\_\_

PW 576



# Battery Economy in Transistor Radios

B.B. RAFTER

**S**OME of those hardest hit by the general heavy increases in dry battery prices over the last few years are the "senior citizens" who live on a tightish budget and rely to such a great extent for news, entertainment and especially "company" on their transistor portables, sometimes themselves quite senior! It is, of course, possible in many cases, though not in all, to replace batteries by a small mains unit and this will soon repay its cost by savings in replacements at anything between 52p and 85p a time. Perhaps the easiest sets to convert in this way are the portables of any vintage using the PP9 or equivalent battery, as this can usually be replaced by a mains unit of identical size, either bought complete, made up from data published, or from kits advertised or from the spares box.

Many portables, however, dating from the days before complementary symmetry in output stages, have a split secondary "single-ended" push-pull power

stage requiring a double 4.5V battery, and since the PP11 or similar now costs 85p, replacement is a big item in a modest budget. Here again, it is possible to buy a ready-made mains unit giving two 4.5V outputs, but they are more expensive than the single 9V units, not so easy to make up from the spares box, and I have never seen a kit for one.

The solution is, really, to convert the output stage of such a set from double 4.5V to single 9V working. Even if the user then continues to use batteries, this will bring down his replacement costs by over 30% from 85p to 52p and of course there are cheaper 9V mains units available and they are much simpler to make up. I recently came across an OAP faced with the problem of the expense of the P11 and I managed to convert his set from double 4.5V to single 9V working in what proved to be an extremely simple manner, once the PCB had been extracted from the case and examined. The set proved to have a fairly common split battery, push-pull output stage, as in Fig. 1. This had to be converted to single battery working with as little disturbance as possible of the existing PCB and the controls. In fact, it proved possible by re-soldering only two connections:—

Lead A from the speaker in Fig. 1 was cut where it entered the 4-pin battery plug and re-soldered to point X on the double pole switch at the back of the volume control.

Lead B from the speaker was transferred, on the PCB, from the negative side of the capacitor (100uF) to the positive side, at point C.

These changes thus produced the standard single 9V output stage, as in Fig. 2. All that remained was to change the battery plug from the original 4-pin (for two 4.5V outlets) to an ordinary 9V type, using the cut-away top from a defunct PP9 battery. The conversion was then complete, much to the pleasure of our old friend, for whom it will now be possible, if he so wishes, for me to make up a small 9V mains unit to enable him to use his beloved portable at minimum cost. P.W.

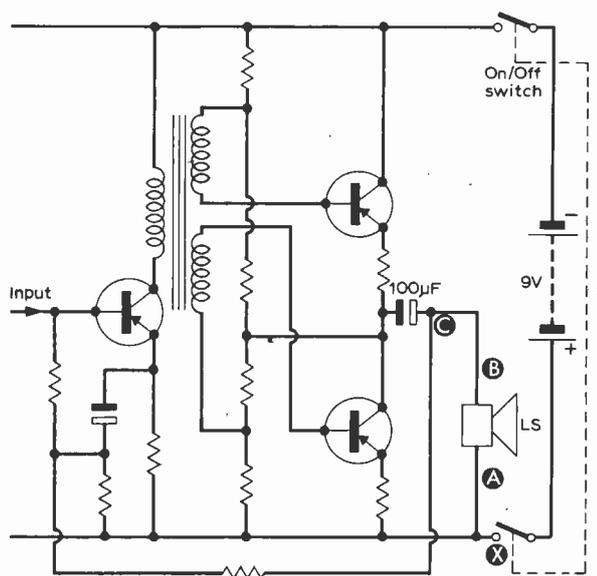
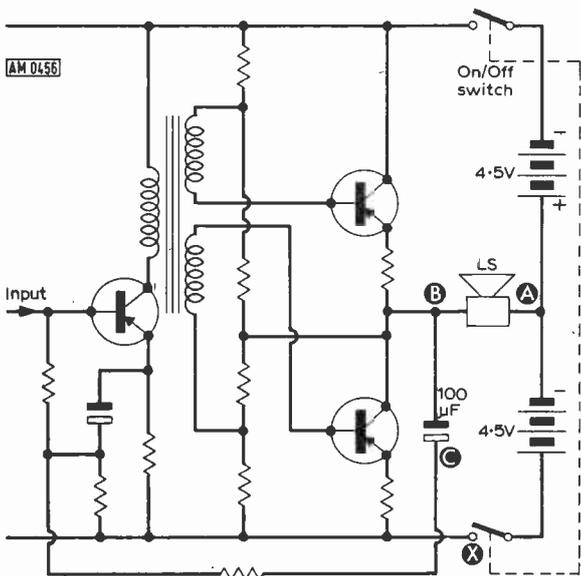


Fig. 1, left, shows a typical output stage using two 4.5V batteries. Fig. 2, right, is the same circuit converted to operate from a single 9V battery.

**'SPECIALIST' RANGE**

**5 Models for 5 purposes**

Illust. Model DISCO 60

All have ROBUST CAST ALUMINIUM CHASSIS and EXTRA HIGH POWER COILS.



**OUTSTANDING QUALITY FOR THE DISCRIMINATING PROFESSIONAL MUSICIAN**

Available in 8 or 15Ω Imp. 2 Year full Guarantee

- \*12" DISCO 60 Rec. Price £25.95  
Linen cone surround Extra Large TWEETER
- 12" GUITAR 60L £24.75
- 12" GUITAR 60B £24.95  
For use in multiples for Bass Guitar
- 12" PA10 £24.75  
General Purpose All above 60w R.M.S.
- 15" BASS 70 70W £37.75  
For all Bass Instr
- \*Available in handsome Vynide & Vynair covered Cabinet £43.50

**FANE CRESCENDO COLOSSUS**

**18" DIAM. 4" POLE**

Total Flux 366,000 For front or rear mounting



**200w R.M.S.**

Rec price inc. VAT **£99.95**

Weight 31½ lb Bass Resonance 23 Hz Range 22 Hz-3.2 kHz

**ELITE RANGE**

- CRESCENDO 12A 12L
- " " 12 BASS
- ALL 100 Watt R.M.S.
- CRESCENDO 15
- " " 15 BASS
- " " 18A
- " " 18 BASS
- " " COLOSSUS

Rec. Prices from **£49.30** inc. VAT

And don't forget our fast selling and reliable 'Budget Speakers'

- 'POP' RANGE**
- 'POP' 15 12" 15w £7.95
  - 'POP' 60 15" 60w £23.95
  - 'POP' 33T 12" 33w £11.50
  - 'POP' 70 15" 70w £25.95
  - 'POP' 50/2 12" 50w £14.99
  - 'POP' 100 18" 100w £39.95
  - 'POP' 55/2 12" 60w £20.95

Above are Rec. Prices inc. V.A.T. Guarantee is for 2 years.

Please send SAE with all enquiries

Distributors (Wholesale & Retail Trade)

**LINEAR PRODUCTS LTD., Electron Works, Armley, Leeds.**

Manufacturers enquiries to: **FANE ACOUSTICS LTD., 286 Bradford Road, Batley, Yorks.**

**HIGH FREQUENCY HORN UNITS**

**MODEL 910 Mk II**

Rating 50 watts with recommended filter. Rec. Price **£17.75**



**MODEL 920 Mk II**

significantly increased sensitivity. Rating with recommended filter 100 watts (as illust) Rec. Price **£49.95**

**HPXI HIGH POWER CROSS-OVER UNIT** Suitable for above Horn Units Rec. Price £2.70

Prices shown correct at Mar. 5, 1976

**TRANSFORMERS**

**MAINS SAFETY ISOLATING** Primary 240V. Sec. 120V or 240V. Please state which type you require. All types are screened and Centre tapped to earth.

V.A. (watts)	OPEN TYPE	P. & P.	CASED TYPE	SOCKETS 5 amp 15 amp	CARRIAGE	PLUGS FOR CASED TYPE complete set
	£	p	£			
50	3-98	62				
100	4-53	70				
200	7-26	80				
250	8-50	1-10				
350	10-59	1-18				
500	12-18	1-34	23-25	1	—	O.A. 1-20
750	18-65	O.A.	30-80	1	—	O.A. 1-20
1000	26-00	O.A.	37-77	2	—	O.A. 2-40
1500	29-65	O.A.	44-30	3	—	O.A. 3-60
2000	35-00	O.A.	51-85	1	1	O.A. 2-70
3000	55-00	O.A.	75-35	3	1	O.A. 5-10

**CASED TYPES** These are of extremely high quality to British Standard Specification, with resettable fused primary winding, and are fitted with covered outlet sockets. Housed in steel cases with carrying handles and 3ft of 3 core cable.

12V or 24V				MINIATURE TRANSFORMERS			
Primary 240V Please state which voltage				Primary voltage 240V			
AMPS	voltage	PRICE	P & P	Sec. volts	mA	PRICE	P & P
	£			£			
12V	24V			3-0-3	200	1-37	25
1	5	1-30	26	0-6 x 2	1A	1-86	45
2	1	2-05	45	0-9 x 2	330	1-34	26
4	2	2-52	62	0-9 x 2	500	1-83	45
8	3	3-76	62	0-9 x 2	1A	2-60	52
10	5	4-67	85	0-15 x 2	200	1-30	25
12	6	4-93	98	0-20 x 2	300	1-72	52
18	8	6-35	1-20	0-20 x 2	1A	3-08	72
20	10	9-27	1-20	0-15-27 x 2	1A	3-86	72

**QUANTITY DISCOUNTS**

- 1 to 24 off Basic Price
- 25 to 49 off 2½% off Price
- 50 to 99 off 5% off Price
- 100 to 249 off 10% off Price
- 250 to 499 off 15% off
- 500 to 999 off 20% off
- 1,000 to 1,999 off 25% off
- 2,000 and over 30% off

We manufacture Power Transformers to customers own special requirements, please send details of any Transformer you may require custom built. All queries must be accompanied by S.A.E.

**PLEASE ADD 8% V.A.T. TO TOTAL PRICE**

**S. G. Wright's Ltd., Bishop Wood Works, Rylands St., BURNLEY, Lancs. BB10 1RG Tel. 26934**

**SPRING MADNESS MIBAGN SALE**

- F.M. Tuners.** 8-transistor chassis with Stereo-decoder and L.E.D. Indicator ~~£16.60~~ ~~£10.90~~
- Aircraft-band receiver.** Just place near any radio ~~£5.97~~ ~~£3.90~~
- Echo-chamber.** (Endless tape). Variable delay ~~£2.00~~ ~~£34.50~~
- Field-strength Indicators.** 1-250 MHz ~~£25.00~~ ~~£3.30~~
- Stereo Amplifiers complete.** 3-watt. 8-ohm ~~£4.00~~ ~~£2.75~~
- 10-watt Amplifiers.** 12 volt D.C. 3/8/15-ohm. ~~£5.90~~ ~~£3.90~~
- Cartridges.** Acos GP 104. Ceramic/Diamond ~~£0.32~~ ~~£1.50~~
- Cartridges.** Acos GP 101. Crystal/Sapphire/Compatible ~~£1.00~~ ~~£0.50~~
- Speakers.** 2½"-8-ohm ~~£0.50~~ ~~£0.35~~
- Speakers.** Car Stereo. 8-ohm, 5-watt. In cabinets ~~£1.00~~ ~~£0.90~~
- Dynamic Tape Mikes with remote-control facility** ~~£1.00~~ ~~£0.90~~
- Crystal Tape Recorder Mikes** ~~£1.00~~ ~~£0.80~~
- Crystal Mike Inserts with bracket** ~~£0.30~~ ~~£0.20~~
- Indicators.** 12-volt L.E.D. in Chrome Bezel ~~£0.48~~ ~~£0.35~~
- "Bargain Bags"** 4lbs Caps/Resistors/Transistors/Diodes ~~£5.00~~ ~~£2.50~~
- Controls.** Volume/Pre-set (Rotary & Slider) Assorted 100 ~~£1.00~~ ~~£1.00~~
- Transistors.** 20 NPN/PNP. All new and marked ~~£1.00~~ ~~£1.00~~
- Transistors.** 100 NPN untested ~~£0.50~~ ~~£0.50~~
- Diodes.** 100 Germanium untested ~~£0.50~~ ~~£0.50~~
- Diodes.** 100 Silicon untested ~~£0.50~~ ~~£0.50~~
- Diodes.** 100 Zener untested ~~£1.00~~ ~~£1.00~~
- "Pack 1"** 100 resistors. 100 ceramics. 100 diodes ~~£1.00~~ ~~£1.00~~
- "Pack 2"** 100 resistors. 100 ceramics. 100 polystyrene ~~£1.00~~ ~~£1.00~~
- "Pack 3"** 100 resistors. 100 S/Mica/Ceramic. 100 Polyester ~~£1.00~~ ~~£1.00~~

ALL ABOVE ITEMS PLUS 25% VAT

- Fluorescent 12-volt Camping Lights.** 21" 13-watt ~~£8.00~~ ~~£4.90~~
- " " 8-watt ~~£7.00~~ ~~£3.90~~
- "Disco type 3-Channel flashing light units.** Built-in mike. No connection needed to amp ~~£19.95~~ ~~£17.50~~
- Multimeters.** AC 0-1000V. DC 0-1000V., 0-100 ma. 0-150kohm ~~£3.50~~ ~~£3.50~~
- Multimeters.** AC 0-500V. (10 ranges) DC 0-500V. (12 ranges) ~~£10.95~~ ~~£11.30~~
- DC Current 0-25ua to 0-10 amps (10 ranges) ~~£3.50~~ ~~£3.50~~
- Resistance 0-100ohms to 0-10Mohms. (4 ranges) ~~£10.95~~ ~~£11.30~~
- Panel Meters.** 0-50ua. 2½" x 1½" ~~£1.50~~ ~~£2.50~~
- Soldering Irons.** 15-watt. Pencil Bit. ~~£1.50~~ ~~£1.20~~
- Servisol Switch Cleaner (with Snorkel)** ~~£0.50~~ ~~£0.50~~
- Copper-clad Fibre Glass Board.** Single-sided. Square foot ~~£1.00~~ ~~£1.00~~
- Double-sided ~~£1.25~~ ~~£1.25~~
- "Fotolok"** Light sensitive spray for printed circuit making ~~£1.30~~ ~~£0.30~~
- Developer for same** ~~£0.30~~ ~~£0.30~~
- Ferric Chloride for etching** ~~£0.40~~ ~~£0.40~~

ALL ABOVE ITEMS PLUS 8% VAT

**G. F. MILWARD, 369 Alum Rock Road, POSTAGE: Below £10 50p**  
Tel. 021-327 2339 Birmingham B8 3DR. Above £10 Free

# GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 772501

All mail order and callers to this address please—callers only to 21 Deptford Broadway, SE8 (Tel. 01-692 2009), and 38 Lower Addiscombe Road, Croydon (Tel. 01-688 2950).

**PC ETCHING KIT Mk II**  
Contains 1lb Ferric Chloride, 100 sq ins copper clad board, DALO Quick Dri Etch resist pen, abrasive cleaner, 2 miniature drill bits, etching dish and instructions. £3.95

**7lb BARGAIN PARCELS**  
Hundreds of new components—pots, resistors, capacitors, switches, PC Boards with transistors, diodes and zeners, loads of odds and ends. Only £3.25

**TRANSISTOR PACKS**  
200 asstd. mainly out of spec. transistors, mostly unmarked—NPN PNP plastic, TO5 TO18 RF AF Small signal and TO3 power devices. About 75% useable devices. Only £1.00. 1,000 unmarked 1N4148 diodes, 95% OK. Only £4.00. 100 unmarked BC108, untested £2.10. 10 out of spec. 2N3055 £1.

**COMPONENT PACKS**  
400 asstd. carbon resistors £1.50  
250 HI-Stabs, 1, 2, 5% 1-1W £1.40  
100 Wirewounds 2-15W £2.00  
200 Miniature resistors, 1/2 and 1W, mostly carbon film £1.10  
200 poly, mica, ceramic caps £1.10  
100 Polyester, .01-2.2µF £1.30  
200 miniature electrolytics, but many unmarked to only £1.35  
15 Air-spaced and compression trimmers £1.10  
15 Useful switches, micro, toggle, rocker and rotary. £2.20.  
35 Crystals, mostly HC11U, at least 30 diff. freqs. 4-8MHz £1.00.

**COMPUTER PANELS**  
Large quantity always available: 3lb asstd. £1.75; 7lb £3.95; 56lb £3.00. Pack with about 500 components Inc. at least 50 transistors £1.00; Pack with 12 High quality panels, inc. IC's, power transistors, multitrn trim pots hundreds of small signal transistors, resistors, zeners, capacitors, etc. Only £2.75.  
7400 IC pack—20 74 series IC's on panels £1.20.

**PE Gas Ignitor Kit**, as featured in July 75 edition. Still only £3.00.

**FERRIC CHLORIDE**  
Anhydrous technical quality in 1lb double sealed packs, 1lb 85p; 3lbs £1.90; 10lbs £4.00; 100lbs £38.00.

**VEROBOARD**  
100sq ins asstd. sizes and pitches, about 8 pieces (All 0.1" if requested) £1.20.

**DEVELOPMENT PACKS**  
50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF, total 210 caps. £3.00.  
CR25 carbon film 1/3rd watt resistors, 5%, 10 of each value 10 ohms to 1M Total 810 resistors £7.50. Electrolytics, wire ended 25V working 10 each of: 2, 2, 4, 7, 10, 22, 47 and 100µF. 70 capacitors for £3.00. 400mW zeners 5% 10 each 3V to 30V, 250 in all. Only £14.00.

**TRANSFORMERS**  
All have mains primaries, 6.0-6V 100mA £1.00; 9.0-9V 100mA £1.07; 12.0-12V 50mA 85p; 12.0-12V 100mA £1.08; 24.0-24V 500mA £2.85; Multi-tapped transformer to give 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30V, or 12.0-12, or 15.0-15V. 1A version £3.15; 2A Version £4.45; 30.0-30V 1A £2.25; 6.0-6V 1A £1.05; 12.0-12V 1A £2.15; 25V 1.75A £2.00. 25V 50mA 85p; 12V 150mA 83p. Type LGC: 12V at 2-4A; 15-7V at 1-25A and 12V at 0-5A £2.50.

**ODDS AND ENDS**  
975kHz FT171B Xtal 50p; 20 33k or 1-8k 1% resistors; 85p; Connector blocks, 12 way 2A or 5A, both 85p; Magnets, ceramic 9mm dia. x 10mm long with 2.8mm hole through the middle. 10 for 15p; Capacitors: 2000µF 10V vert mntg; long leads 12 for £1.00; 100 + 400µF 275V 45mm dia x 12mm long 60p; 18000µF 25V 52mm dia. x 12mm long 85p; Telephone Inserts, 20Q balanced armature unit 30p; 250V 2 1/2A bridge rect 50p; 50V 1A 30p; Twin Phone Socket 8p; Crystal Mic Insert 1 1/2" dia 35p.

SEE PRACTICAL ELECTRONICS FOR INDIVIDUAL COMPONENT PRICES All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries or for list please. Send 10p for Multimeter catalogue—free on request on orders over £3. Official orders accepted from Schools, etc. Export/Wholesale enquiries welcome. Surplus components always wanted.

## MULTIMETERS



MODEL LT22

Probably one of the lowest priced meters featuring a mirror scale, overload protection and 20000 ohms per volt sensitivity. A modern styled meter with unusually clear scale markings. Ranges: DC Volts 0-0.5-2-5-10-50-250-1000 AC Volts 0-10-50-250-1000 DC Current 0-50A -25mA-250mA Resistance 0-50k-500k-5M (Mid Scale 300-3k-30k) dB's 4 ranges -20db to +42dB. Size 130 x 90 x 42mm. £9.90



MODEL C7077

An exceptionally sensitive meter, 100,000 ohms per volt, that will prove its worth in a very short time. It features 4 ohms ranges, measuring up to 100 megohms and has a mirror scale. Ranges: DC Volts 0-0.5-5-25-50-250-1000. AC Volts 0-10-50-250-500-1000. DC Current 0-10mA-2-5mA-25mA-500mA. Resistance 0-10k-1M-100M-100M (Mid Scale 130-13k-130k-1.3M) dB's -20 to +62. Size 152 x 102 x 44mm £15.30.

## VEROBXES & CASES

Case type 1410, 205 x 140 x 40mm £2.90  
1411, 205 x 140 x 75mm £3.25  
1412, 205 x 140 x 110mm £4.20

Plastic Boxes—Professional quality, two tone grey polystyrene boxes with threaded inserts for mounting PC boards.  
Type 2518, 120 x 85 x 40mm £1.52;  
2520, 150 x 80 x 50mm £1.75; 2522, 188 x 110 x 60mm £2.40; Sloping front type: 220 x 174 x 100/52mm £4.20.

## INTERCOM UNIT

Chassis 230 x 155mm with Celestion 3 ohm 110mm speaker, small buzzer, 3 pole 4 way tuning capacitor, twin stator type, silver plated, with padders on each section. Also numerous coils, R's C's, etc. Only £2.50.

## RF UNIT

A compact tuning unit containing 2 x CV4063 and 3 x CV4014 with screening cans, and a beautifully made 5 gang tuning capacitor, twin stator type, silver plated, with padders on each section. Also numerous coils, R's C's, etc. Only £2.50.

## HEAT SINK

Large finned matt black aluminium heat sink 230 x 200 x 35mm with 4 silicon power transistors, sim. to 2N3716, and 16 1 ohm 5W resistors. £3.00.

## RELAYS

Miniature plug in types: 1250 ohm 4c/o 48p; 700 ohm 4c/o 50p; PO 3000 type: 650 ohm 12V, with 6 heavy duty c/o contacts (Ex-except) 75p. 6 1/2" easily removable reeds in 3500 ohm coil 50p. Plug in relay, B7G base. 17mm dia. x 42mm long. 10kΩ coil, 1c/o contact 40p.

## SWITCHES

16A 250V on/off rocker 20p; 10A 250V on/off rocker with built in inon, 40p; Push-on, push-off DPCCO switch 15p; 10A 250V rocker, DPCCO Blassed 25p; 4 pole 3 way rotary switch, 32mm dia. 25p; Bank of 20 Open construction SPCCO mini switches, overall length 225mm, useful as cheap keyboard substitute. Only £1.30.

## WIREWOUND POTS

30k 5W; 200Ω 4W; 10k 3W; 1k 3W; 50Ω 3W; 80Ω 3W; 80Ω 3W; 100k 3W. All 25p each, any 10 £2.00.

## QUALITY STEREO SOUND.

ALMOST 1/2 PRICE OFFER! SOLENT AUDIO SYSTEM



MADE TO SELL AT DOUBLE THE PRICE IN CABINET FORM  
OUR PRICE £59.95  
\*Stereo Tuner Amplifier chassis with AM/FM radio covering long medium short and Stereo FM wavebands. Separate Base and Treble controls. 30 watts total power output (frequency response 25-20,000 Hz) AFC Switching, Tape record and playback facilities. Dimensions 18 1/2" x 9" x 3 1/2". The very latest BSR automatic record deck with cue and pause control. Two matching elliptical speaker units.

Order early limited stocks available cash price £59.95. Credit Sale £5.95 deposit 9 monthly payments of £7.00 (Total Credit price £68.95). P. & P. £3.00. Send £8.95 today.

Chassis only available for cash at £42.00.

Full 12 months Guarantee.  
CALLERS WELCOME.  
Access and Barclaycard  
telephone orders accepted

Stereo headphones supplied with every complete order.  
LEWIS radio PW/5/76 100 CHASE SIDE SOUTHGATE  
LONDON N14 5PL Telephones: 01-882-1644

## ENGINEERS

# FREE

## YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 44 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



CUT OUT THIS COUPON  
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- |                                     |  |  |
|-------------------------------------|--|--|
| Build-As-You-Learn                  | Electronic Engineering                   | Transistor Technology                    |
| AND ELECTRONICS (with kit)          | Computer Electronics                     | CITY AND GUILDS Installations and Wiring |
| Electrical Engineering              | Colour TV Servicing                      | CITY AND GUILDS Electrical Technicians   |
| Electrical Installations and wiring | C&G Radio, TV & Electronic Mechanics     | CITY AND GUILDS Telecommunications       |
| Electrical Draughtsmanship          | General Radio and TV Engineering         | Radio Amateurs' Exam etc. etc.           |
| Electrical Mathematics              | Radio Servicing, Maintenance and Repairs |  |

To ALDERMASTON COLLEGE Dept. EPW-15, Reading RG7 4PF EPW 15  
Also at our London Advisory Office, 4 Fore Street Avenue, Moorgate London, EC2Y 5EJ Tel: 01-628 2721

NAME (Block Capitals Please) ADDRESS POST CODE

Other subjects Accredited by C.A.C.C. Member of A.B.C.C. Age

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY


# EDITORIAL ANNOUNCEMENT

# NEW!

# PRACTICAL WIRELESS
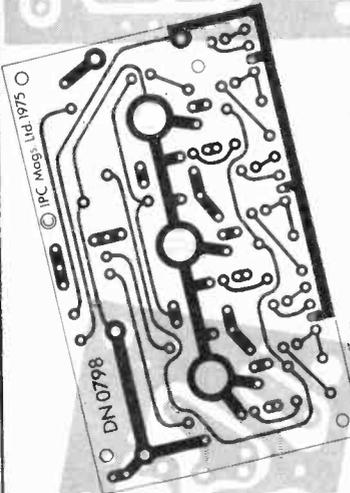
# PCB SERVICE FOR READERS

Our new PCB service is well under way and we are now able to add PCBs for two popular projects published prior to December 1975. All boards, except SRBP, are epoxy glassfibre, drilled and roller-tinned.



To:- READERS PCB SERVICES LTD, PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es

Issue	Project	Ref	Price	P/P		
Mar 75	Electronic Organ (set of two)	AM0315 AM0318	7.80 + 25		<input type="checkbox"/>	
Sep 75	Electronic Clock (set of three)	AM0387 AM0389 AM0392				2.40 + 15
Dec 75	Radio-Pickup Link	DN0792	0.98 + 12	<input type="checkbox"/>		
Dec 75	Random Number Selector	DN0793A	0.98 + 12	<input type="checkbox"/>		
Dec 75	Sound-To-Light Display	DN0798	1.15 + 12	<input type="checkbox"/>		
Dec 75	12V PA System	DN2/JM	0.98 + 12	<input type="checkbox"/>		
Dec 75	Disco System, Amplifier (2 required)	each AM0421	3.40 + 18	<input type="checkbox"/>		
Dec 75	Disco System, Light Modulator	AM0423	2.70 + 18	<input type="checkbox"/>		
Jan 76	Music Box	SRBP DN1/JM	2.25 + 18	<input type="checkbox"/>		
		glassfibre DN1/JM	3.00 + 18	<input type="checkbox"/>		
Jan 76	Emergency Light Unit	AM0419	3.50 + 18	<input type="checkbox"/>		
Mar 76	CMOS Crystal Calibrator	AM0438	1.19 + 12	<input type="checkbox"/>		
Apr 76	DF Receiver (set of two)	DN4/JM DN5/JM	1.92 + 15	<input type="checkbox"/>		
Apr 76	Wobulator	AM0443			1.08 + 12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33 + 15	<input type="checkbox"/>		

Post and packing is for one board or set of boards. Prices include VAT.

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. ACCESS welcome. Send card number only.


I enclose Postal Order/Cheque No..... for £..... made payable to READERS PCB SERVICES LTD.

NAME.....

ADDRESS .....

Post Code .....

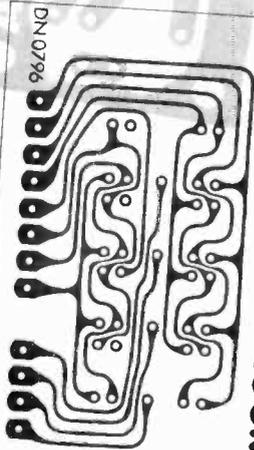Any correspondence concerning this service must be addressed to READERS PCB SERVICES and not to the Editorial offices.



**ELECTRONIC CLOCK**

© IPC Magazines Ltd.

# LOGIC INDICATOR

## SIMPLE

Peter HEMINGWAY

THIS device was designed as a result of reading an article in PW some 3 years ago (Logiprobe, by L. Cook, October 1972). The device described there was somewhat cumbersome, and prompted me to design a unit which was simpler, cheaper and more compact. The fact that this device is so simple means that it can be built into a small and very handy body, such as a felt-tip pen or as the prototype was, built into a discarded test probe.

### Circuit Details

The circuit is basically a potential divider with two LED's to indicate the current flow through their respective resistors. The value of the resistors is not too critical and can be of any value from  $330\Omega$  to  $1k\Omega$ . However, if resistors of less than  $330\Omega$  are used, damage to the LED's may result, and if too high a value, the LED's will be too dim. As R1 and R2 must be of the same value, they should also be of 10% tolerance, and  $\frac{1}{8}W$  so that they are able to fit into the case.

The LED's used in the prototype are 5mm types, one green to indicate logic 0 (or OV) and the other, red, to indicate logic 1 (or +1V). To cut the cost even more, 3mm diameter LED's could be used.



As previously stated the prototype was built into a test probe of slightly smaller dimensions than a felt-tip pen. The drawing opposite illustrates a cross section of the unit showing the internal wiring and components. The supply leads to the probe should be terminated in a pair of crocodile clips in order that the probe can be connected to the same power supply as that used by the TTL circuitry under test.

After the probe has been tested and found to be working satisfactorily, the wires and LED's are fixed in place with a glue such as polystyrene cement or Araldite.

### Testing

A quick method of testing the probe, is to connect the supply leads to their respective terminals of a 6V battery. If all is well, both LED's should light at half brightness (half brightness will also be displayed when the probe is connected to a point that is either floating or at an inadmissible voltage (e.g. 2-1V). When the probe is touched to a positive terminal, D1 (red) should light, and similarly when the probe is touched to the OV terminal, D2 (green) should light.

If these results are not obtained it is probably due to the fact that one or both diodes are connected the wrong way round.

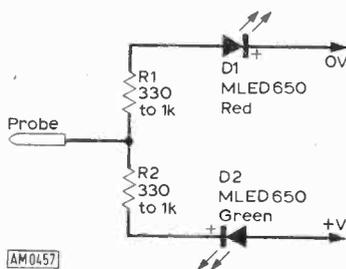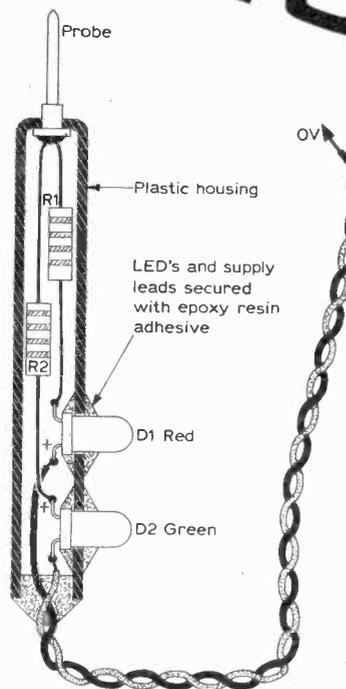

AM0457

### ★ components list

#### Resistors


R1\* 330 $\Omega$ -1k $\Omega$  R2\* 330 $\Omega$ -1k $\Omega$   
\*see text.

#### Semiconductors

D1 MLED 650(red) D2 MLED 650(green)
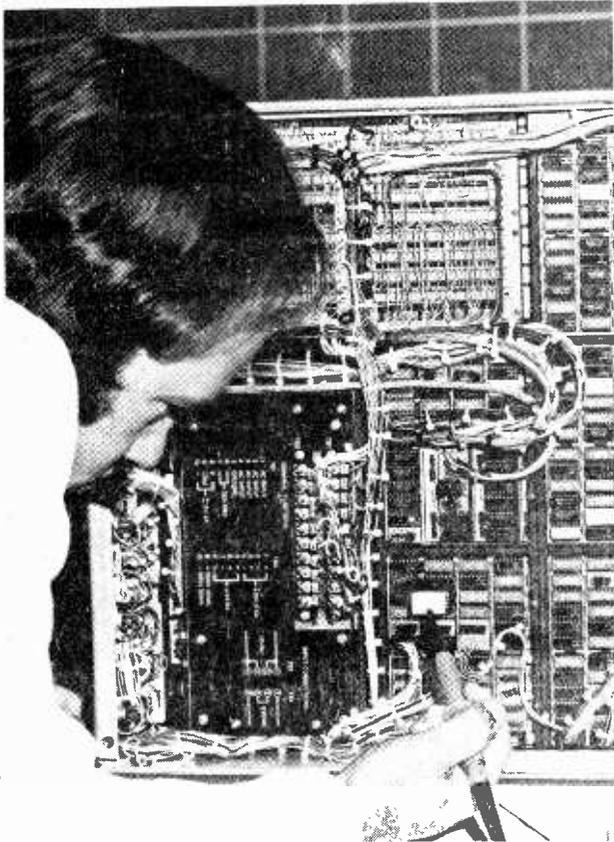
#### Miscellaneous

Felt-tip pen body or spare test probe. Two crocodile clips.  
Lengths of wire (two colours).



# This hobby brings big rewards.

A soldering iron and a screwdriver. If you know how to use them, or at least know one end from the other, you know enough to enrol in our unique home electronics course.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.


You build, see and learn as, step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered and add a new dimension not only to your hobby but also to your earning capacity.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A certificate is given at the end of every course.


## 1
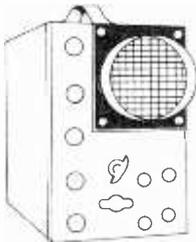
### Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.



## 2

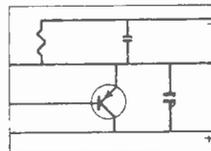

### Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.

## 3



### Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

## PLUS FREE GIFT!



ALL STUDENTS ENROLLING IN OUR COURSES RECEIVE A FREE CIRCUIT BOARD ORIGINATING FROM A COMPUTER AND CONTAINING MANY DIFFERENT COMPONENTS THAT CAN BE USED IN EXPERIMENTS AND PROVIDE AN EXCELLENT EXAMPLE OF CURRENT ELECTRONIC PRACTICE

Brochure without obligation to:  
**BRITISH NATIONAL RADIO WL56  
& ELECTRONICS SCHOOL, Dept  
P.O. Box 156, Jersey, Channel Islands.**

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

(Block caps please)

# Dolby™ Noise Reducer Kit



PRICE: £34.40 + VAT

'Wireless World'  
May, June, July '75

Trademark of Dolby Laboratories Inc.

The latest addition to our exclusive range of matching high fidelity units.

The Dolby Noise Reduction System is designed to reduce background noise on open reel or cassette tape recorders. Used in the signal path to and from the tape recorder, the unit will encode (Dolbyise) signals during recording, and, during playback, may be used to decode either your own encoded material, or commercially available Dolby encoded cassettes.

Featuring:

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

The kit includes:

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

Calibration tapes are available for open-reel use and for cassette (specify which) PRICE £1.80 + VAT\*

### Typical performance

Noise reduction better than 9dB weighted

Clipping level: 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level (typically 0.05% over most of band, rising to a maximum of 0.12%)

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output

Dynamic Range > 90dB  
30mV sensitivity

## S-2020TA STEREO TUNER/AMPLIFIER KIT

PRICE: £48.95 + VAT

### SOLID MAHOGANY CABINET

A high-quality push-button FM Varicap Stereo Tuner with Interstation mute combined with a 20W r.m.s. per channel Stereo Amplifier.



THD < 0.1% @ 20W  
Tuner S/N 30dB @ 1.8µV (mono)  
Toroidal Transformer

Please add VAT at 25% unless marked thus \* when 8% applies  
We guarantee full after sales technical and servicing facilities on all our kits

Please send SAE for complete lists and specifications  
Portwood Industrial Estate, Church Gresley,  
Burton-on-Trent, Staffs DE11 9PT  
Tel. Burton-on-Trent (0283) 215432. Telex 377106

## INTEGREX LTD.


Access  
Barclaycard

**A.S.P. LTD**  
(DEPT. PW4), SIMMONDS ROAD, WINCHEAP  
CANTERBURY, KENT Tel: (0227) 52436

# TRANSFORMERS VAT 8%
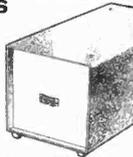
### CASED TRANSFORMERS

Housed in smart resin coated steel cases with 3 core power cable and outlet socket, fitted primary winding. Isolation types are fused with 3-pin outlet sockets and are available with 110 volt or 240 volt output (please state). Auto types are fitted with 2-pin flat style sockets up to 500VA. 3-pin sockets from 750 to 3000VA. See Auto Isolation Sections for prices. Plugs extra.



**SAFETY ISOLATING** See catalogue for full range.  
Prim. 120/240V. Sec. 120/240V. Centre Tap with screen.

VA (Watts)	REF. NO.	PRICE £	PRICE CAGED 2 £	PRICE PLUGS 2 £	PRICE OPEN £	POST £
60	149	9.03	0.98	4.70	0.72	
200	151	12.29	0.98	8.61	0.97	
250	162	13.81	0.98	10.31	1.18	

### AUTO TRANSFORMERS

See catalogue for full range. PRICE £

VA (Watts)	REF. NO.	PRICE £	PRICE CAGED 2 £	PRICE PLUGS 2 £	PRICE OPEN £	POST £
1500	93	23.28	0.95	19.22	O/A	

### MINIATURE & EQUIPMENT

Primary 240V with screen. See catalogue for full range.

Sec. 1	Sec. 2	MILLIAMPS	REF. NO.	PRICE £	PRICE POST £
3-0-3	200	238	1.56	0.34	
0-6	0-6	500	234	1.56	0.34
0-6	0-6	1000	212	2.12	0.46
0-9-9	—	100	13	1.60	0.34
0-9	0-9	330	235	1.62	0.34

### 12 & 24 VOLTS

Primary 200-240 Volts. See catalogue for full range.

12V AMPS	24V	REF. NO.	PRICE £	POST £
2	—	71	2.47	0.61
4	—	18	3.07	0.62
6	—	3	4.50	0.72
8	—	108	5.11	0.85

### 30 VOLTS

Primary 200/240V  
Secondary 12, 15, 20, 24, 30V

AMPS	REF. NO.	PRICE £	POST £
0.5	112	2.04	0.61
1	79	2.57	0.66
2	3	3.81	0.72
3	20	4.80	0.85
4	21	5.58	0.85
5	61	6.75	0.95
6	117	7.52	0.97
8	88	9.93	1.18
10	89	10.27	1.18

### 50 VOLTS

Primary 200/240V  
Secondary 19, 25, 33, 40, 50V

AMPS	REF. NO.	PRICE £	POST £
0.5	102	2.71	0.61
1	103	3.58	0.76
2	104	6.30	0.85
3	105	7.30	0.85
4	106	7.97	1.08
6	107	12.93	1.18
8	118	13.75	1.44
10	119	17.79	1.86

### 60 VOLTS

Primary 200/240V  
Secondary 24, 30, 48, 60V

AMPS	REF. NO.	PRICE £	POST £
0.5	124	2.51	0.72
1	126	3.75	0.72
2	127	5.36	0.85
3	125	7.91	0.97
4	123	9.20	1.18
5	40	10.22	1.18
6	120	12.10	1.36
8	121	15.74	O/A
10	122	20.10	O/A
12	189	18.67	O/A

### BRIDGE RECTIFIERS

One Amp	Price	Four amp	Price
50P.I.V.	0.25	100P.I.V.	0.55
100P.I.V.	0.25	200P.I.V.	0.59
200P.I.V.	0.28	400P.I.V.	0.65
600P.I.V.	0.30	600P.I.V.	0.75

Two Amp	Price	Six Amp	Price
50P.I.V.	0.35	50P.I.V.	0.65
100P.I.V.	0.40	100P.I.V.	0.70
200P.I.V.	0.45	200P.I.V.	0.80
400P.I.V.	0.50	400P.I.V.	0.90

Add 25% VAT on all prices.

### SPECIAL OFFER

#### 2 KVA ISOLATORS

Fully impregnated & screened  
2 Primary windings 110V each  
2 Secondary windings 116V each (2 matching transformers) £29.50 plus carriage  
VAT 8%.

## NEW! 2" and 4" PANEL METERS VAT 8%

Size: 60mm wide x 45mm high x 40mm deep.      Size: 110mm wide x 82mm high x 43mm deep


Movement	Ohms	I.R.	Movement	Ohms	I.R.
0-5 micro A	1250	0-50 micro A	1400		
0-100 micro A	580	0-100 micro A	730		
0-500 micro A	170	0-500 micro A	200		
0-1 mA	170	0-1 mA	200		
0-5 mA	170	0-5 mA	200		
0-10 mA	8	0-10 mA	6		
0-50 mA	0.5	0-50 mA	0.5		
0-100 mA	0.5	0-100 mA	0.5		
0-500 mA	0.5	0-500 mA	0.5		
0-1 Amp	0.5	0-1 Amp	0.5		
0-2 Amp	0.5	0-2 Amp	0.5		
0-25 Volt	15K	0-25 Volt	15K		
0-50 Volt	50K	0-50 Volt	50K		
0-300 Volt	300K	0-300 Volt	300K		
"S" meter	170	"S" meter	200		

Vu meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. VAT 25%. Lamps 95p per set. Plus 8% VAT.

FOR MULTI-METERS, INSTRUMENTS, RESISTORS, NEONS, TOOLS, POWER SUPPLIES, etc. Send for Catalogue.

NEW CATALOGUE 25p

NEW CATALOGUE 25p

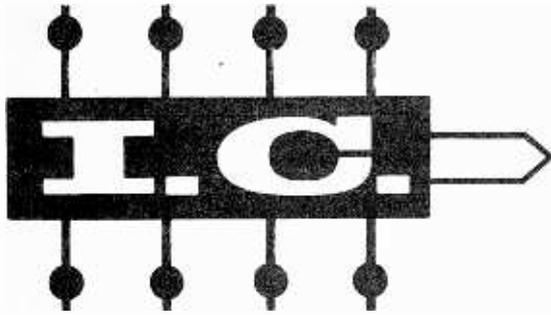

# OF THE MONTH

## Number 58 Motorola MC1312P Quadraphonic decoder

THE Motorola MC1312P and MC1313P are 14-pin dual-in-line devices which have been especially designed for decoding the two composite signals from quadraphonic records into the four separate audio channels. The matrix system used in these devices is suitable for use with inputs encoded on the "SQ" system which was developed by the Columbia Broadcasting System and which is now used by most of the large recording companies. It is also suitable for the decoding of SQ quadraphonic broadcast programmes, but it remains to be seen whether such material will be transmitted in the UK.

labelled  $R_T$  (for total right signal) in Fig.1, whilst  $L_T$  is the total left hand signal. The device essentially separates the total right hand signal into two separate audio signals, namely the right hand front signal ( $R_F$ ) at pin 11 and the right hand back signal ( $R_B$ ) at pin 14. These two output signals are fed to separate power amplifiers which feed the appropriate

### THE TWO DEVICES

The MC1312P is designed for home entertainment applications and introduces less harmonic distortion, typically 0.1%, than the MC1313P, typically 0.25%. The MC1313P is intended for use in quadraphonic vehicle systems where it provides an excellent performance at supply voltages as low as 8V.

The MC1312P has a higher typical input impedance, 3M $\Omega$ , than the MC1313P, 1.8M $\Omega$ . In addition, the MC1312P can provide outputs of up to at least 2V RMS whilst the MC1313P provides at least 0.8V RMS before the total harmonic distortion rises to 1%. The MC1313P has the advantage that it can operate in a cold vehicle at temperatures down to -40°C whilst the MC1312P characteristics are specified down to 0°C. The MC1312P has a lower signal to noise ratio, 80dB, with the input shorted, as opposed to 74dB for the MC1313P under certain conditions.

### TYPICAL CIRCUIT

A typical circuit for the use of either of these devices is shown in Fig.1. It is recommended that the component values shown should have a tolerance of  $\pm 5\%$  for optimum performance in this circuit. The absolute maximum permissible power supply voltage is 25V, but the MC1312P is usually operated from a 20V supply and the MC1313P from a 12V vehicle supply. The current consumption of the MC1312P is in the range 11 to 21mA and that of the MC1313P 6.5 to 12.5mA at their respective normal operating voltages.

The SQ encoded right hand channel signal is

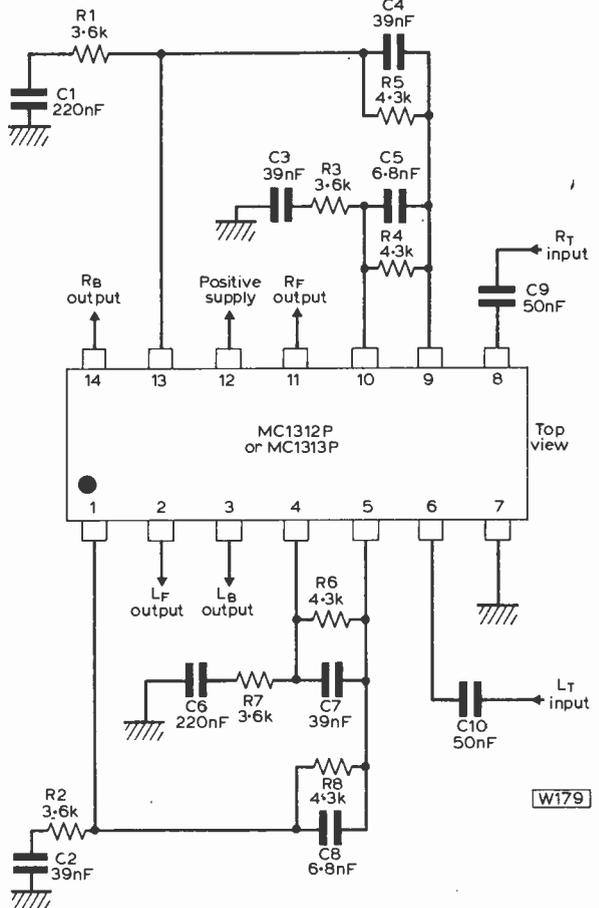


Fig. 1: Typical circuit utilizing the MC1312P or MC1313P. The devices are similar in application except for the supply voltage which is about 20V for the former and 12V for the latter.

loudspeakers. Similarly, the total left hand signal is separated to produce two audio output signals at pin 2 ( $L_F$ ) and at pin 3 ( $L_B$ ). The impedance at each of the four outputs is typically  $5k\Omega$ .

The two output voltages are about the same as the input voltage for that side, the tolerance in the signal amplitude ratios  $L_F/L_T$  and  $R_F/R_T$  being  $\pm 1dB$ . The balance between the two forward channels also has a tolerance of  $\pm 1dB$ . The amplitudes of the output signals to the two rear amplifiers are at a level of typically  $-3dB$  relative to those to the two front amplifiers.

Internally these devices contain two preamplifiers which are respectively fed with the input  $R_T$  and  $L_T$  signals via the blocking capacitors C9 and C10. These preamplifiers each feed two "all pass" networks, shown in Fig.1, which produce phase shifts of  $90^\circ$  without amplitude variations. Each phase shifted signal is fed into an internal resistor matrix together with the original output from the preamplifier, the two outputs from each matrix forming the required front and back signals.

It is generally desirable to enhance the centre front and the centre back separation. This is effected by connecting a resistor between pins 2 and 11 (front outputs) and between pins 3 and 14 (back outputs). For 10% front channel blending, a  $47k\Omega$  resistor may be connected between pins 2 and 11 and for 40% back channel blending a  $7.5k\Omega$  resistor between pins 3 and 14.

The devices are readily available from advertisers in this magazine.

PW

## NOW HEAR THIS!

TAPE HEADS FROM ONLY

**50p**

Fit a brand new head and transform the quality of your tape player. Large production runs of our standard cassette and cartridge heads for European & U.S. manufacturers enable us to offer single items at bulk-order discount prices.

## NOW *post* THIS!

<input type="checkbox"/> 50p Mono Cassette	Qty <input type="text"/>	<b>SAVE MONEY &amp; IMPROVE PERFORMANCE!</b> Fantastic value - they fit most tape players. Data sheets on full range <input type="text"/>
<input type="checkbox"/> 60p Stereo 8 Cartridge	Qty <input type="text"/>	
<input type="checkbox"/> £1.25 Stereo Cassette	Qty <input type="text"/>	
<input type="checkbox"/> I enclose cheque/P.O. in full payment for Qty. marked above. All prices incl. P&P		
NAME <input type="text"/>		
ADDRESS <input type="text"/>		
Money back if not satisfied		
<b>MAGNETIC COMPONENTS LTD Penryn, Cornwall TR10 8AR</b>		

PW

# TELEVISION

## IN THE MAY ISSUE

### DIRECT-READING CAPACITANCE METER

This simple battery-powered design, based on the use of an NE555 timer i.c., gives direct indication of capacitance values from a few picofarads up to  $10\mu F$ . A d.c. test voltage is used, allowing the measurement of polarised capacitors and the capacitance of reverse-biased semiconductor junctions.

### SERVICING THE TANDBERG CTV2-2 CHASSIS

The Tandberg CTV2-2 chassis is in many ways typical of the latest generation of large-screen,  $110^\circ$  deflection continental colour receivers, with a switch-mode power supply and making extensive use of i.c.s. W. S. J. Brice describes the various faults he has encountered.

### AERIAL PERFORMANCE

Roger Bunney and Ian Beckett have been investigating the relative performance of various well-known u.h.f. aerials. Their results form an interesting follow-up to Pat Hawker's recent articles.

### SMALL PICTURE AND RELATED FAULTS

Lack of height, bottom cramping and other forms of non-linearity, and field sync problems are common faults with older TV sets. John Law provides a comprehensive guide to the causes of such faults.

### FIELD TB CIRCUIT FOR THE PIL TUBE

Recent solid-state chassis use a wide variety of field timebase circuits. As an example of some of the latest techniques S. George investigates the circuit used in the Korting 55636 chassis, which is fitted with a PIL colour tube.

### WHICH PATTERN?

E. Trundle's test equipment survey next takes a look at the various patterns available to the service engineer.

**PLUS ALL THE REGULAR FEATURES**

TO.....  
(Name of Newsagent)


Please reserve/deliver the MAY issue of TELEVISION (40p), on sale April 20th, and continue every month until further notice.

NAME .....

ADDRESS .....

# ELECTRONIC DIGITAL CLOCK

## with alarm and snooze features

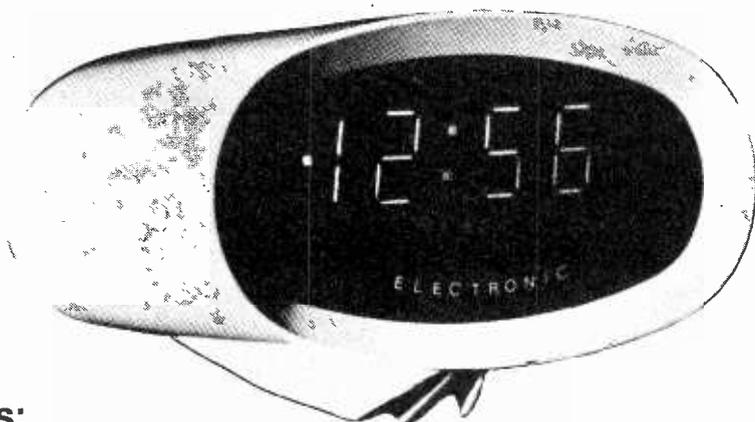

### Features:

- 0.7 INCH HIGH DIGITS
- VARIABLE INTENSITY
- 24 HOUR ALARM
- 5 MINUTE REPEATING, SNOOZE ALARM
- ALARM SET INDICATOR
- SNOOZE INDICATOR
- PULSING SECOND INDICATOR
- POWER INTERRUPT INDICATOR
- ALARM CANCEL FEATURES — TILT OPERATION
- ALARM TONE OUTPUT
- A.M. P.M. INDICATOR

Size: 130mm x 90mm x 95mm; Weight: 10oz; Power supply: 230 VAC  $\pm$  10% 50Hz

*Manufactured to high standards by a major American electronics corporation this superbly styled solid-state timepiece is made available to all readers fully guaranteed.*

## SPECIAL OFFER

# £12.48

+ 99 pence VAT

Mail order customers:  
Please enclose 55 pence for postage  
and packing.

# TM

## TIME MICROELECTRONICS

33, WATERIDGE ROAD, BASINGSTOKE, HANTS, RG21 2RA  
PHONE (0256) 66961

FREE TRIAL IN YOUR HOME. TRY OUT THE CLOCK IN YOUR HOME. IF DIGITAL TIME IS NOT FOR YOU RETURN IT IN ORIGINAL CONDITION WITHIN 10 DAYS AND WE'LL REFUND YOUR MONEY WITHOUT QUESTION.

Please send  electronic clocks as illustrated

I enclose cheque  postal order  money order

Name .....

Address .....

Signature .....

**Wire Wound Resistors.** Our selection of mixed values. 30 for £1.40. 100 for £3.50.

**Audio Amplifier Module.** Mullard LP1173. Output nominal 10 watt. Supply voltage +24vt. With data and circuit. £2.30.

**Vacuo Control Selector.** 4 way 25K. £1.50. 6 way 14.5K. £2.00. **Mains Droppers.** 10 mixed values £1.00.

**Edgewise Level Meters.** 200µA. Size 1" overall 50p.

**15 Assorted Switches** Micro, push button, etc. £1.90.

**Tag Strips.** 3 way to 7 way. 50 for £1.15.

**Chrome Plastic Knobs.** 3 Types 4 off each with spring clip. £1.25.

**Repenco & Denco Coils.** New boxed, our selection. 5 for £1.15.

**Ferguson Stereogram Chassis.** Model 3357. All transistor. Med/LW. FM. 3 wats per channel S/M. With connection data. Less tuning scale. £18.00. P/P free.

**Ferguson Stereogram Chassis.** MW. LW. FM. With tuning scale (5+5 wats sine wave) 15 ohms £26.25. P/P free.

**Copper Clad Laminats.** 8" x 7"—3 boards £11.00 + 8%.

**Ferric Chloride.** 1lb 65p + 8%.

**Repenco Transformers.** AF1. AF2. TT45. 46. 47. 49. 53. 20p each.

**Crystals HC6U.** (MHz) 12700; 12891.6; 9455.55; 9530.55; 9037.5; 9456.25; 52.01667; 52.02500; 37.7625; 51.56667; 52.03333; 8090.62; 9531.94; 9533.33, 50p each.

**Transfilter.** 455KC. AM. 5 for £1.00.

**Electrolytics.** 32/32/32µF, 325V. 2" x 1 1/2" 35p; 80µF 150V 1 1/2" x 1" 20p; 2000µF 30V, 2 1/2" x 1" 25p; 2000µF 35V 3" x 1" 30p; 470µF 100V 3" x 1 1/2" 25p; 2000/2000µF 25V 2" x 1 1/2" 35p; 700µF 250V 3 1/2" x 1 1/2" 30p; 16/16µF 275V 1 1/2" x 1" 20p; 4500/900/900µF 30V 2 1/2" x 1 1/2" 50p; 2500µF 40V 3" x 1 1/2" 40p; 470µF 25V 1 1/2" x 1 1/2" 35p; 4,000µF 25V 3" x 1 1/2" 40p; 32µF 450V 1 1/2" x 1" 30p; 8µF 16µF 450V 1 1/2" x 1 1/2" 30p; 1000µF 12V 1 1/2" x 1 1/2" 15p 5000µF 50V 2" x 1 1/2" 50p; 150/200/200µF 300V 3" x 1 1/2" 50p; 16/16µF 350V 2" x 1" 30p; 50/50µF 500V 3 1/2" x 1 1/2" 50p; 400µF 40V 1 1/2" x 1 1/2" 20p.

Try our parcel of small capacitors 20 mixed values £1.50 + post.

**Miniature Presets**—Selection of various values 10 for 65p.

**Coil Formers.** 50 mixec. £1.25.

**Slider Volume Controls.** 1K Lin; 100K Log; Meg Log; 25K Lin; 25K Log; 10K/100K Log; 100K/100K Log; 50K Log. 35p each.

**U.H.F. 625.** Transistor push button tuner (NSF Telefunken), as used on Decca MS2400. Brand new and boxed. Circuit diagram supplied. £3.00.

**Thorn T.V. 1F.** Chassis 950 Series (less valves) £1.60.

**Aluminium Chassis.** 7 1/2" x 5 1/2" x 2 1/2" 65p. 10" x 7 1/2" x 2 1/2" 75p. 11" x 7 1/2" x 2 1/2" 85p. + 8%.

**500 Metres.** 1/0148 TC. Single polythene lappac screen wire. £5.00 + 8%.

Please add 10% P/P. Unless stated free P/P. VAT 25% to be added to total order unless stated 8%. No goods despatched outside U.K.

**BSR Single Play Decks** with Cue-Fitted stereo cartridge. P146 £11.00. P153 £12.00.

**SURPLECTRONICS**  
216 LEAGRAVE ROAD,  
LUTON, LU3 1JD, BEDS.

**GIRO NO. 331 7056.** Access and Barclaycard accepted. C.W.O. only. Terms of business as in our Catalogue. Export Order enquiries welcome (£5 min.)

Official Orders accepted from Educational and Government Departments. All prices include VAT & P & P. E. & O.E. SHOP HOURS 9-12.30, 1.30-5.00 5 days. EXCEPT WEDNESDAY.

**1976 ISSUE** 66 PAGES—3 000 ITEMS FULLY ILLUSTRATED \*20p CREDIT VOUCHERS

\*ALL NEW STOCK \*SATISFACTION GUARANTEED \*DISCOUNTS \*NEW PRICE LIST For Cat. 4a—S.A.E.

Boxes - Cases - Kits - PC Materials - Tools - Resistors - Test Meters - Capacitors - Hardware - Semiconductors - Books - Pots - Coils - Audio Accessories - Screws - Connectors - Audio Modules - Veroboard - Transformers - Knobs - Calculators - Audio Leads - Batteries - S dec Storage Units - Heatsinks, etc., etc.

**SPECIAL CAPACITOR KITS**

C290 Kit—PC Mounting polyester 250V 5 of each value: 0.01, 0.022, 0.047, 0.1, 0.22µF, 2 of 0.47, 1µF. £1.98 net

C296 Kit—Tubular polyester, 400V, 5 of each value 0.01, 0.022, 0.047, 0.1, 0.22µF, 2 of 0.47µF, £2.67 net

Ceramic Kit—square plaque, 50V 5 of each value, 22, 33, 47, 100, 220, 330, 470, 1000pF, 220, 470pF, 0.01µF, £1.68 net.

**SPECIAL RESISTOR KITS (CARBON FILM 5%)** (Prices include post & packing) 10E12—W or 1W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 £5.29 net. 25E12 1W or 1/2W KIT: 25 of each E12 value, 22ohms—1M, a total of 1425 £12.64 net.

**B. H. COMPONENT FACTORS LTD.**

**MULTIMETER U4323**

22 Ranges plus AF/IF Oscillator 20,000/Volt. Vdc—0.5—1000V in 7 ranges Vdc—0.5—1000V in 6 ranges Idc—0.05—500mA in 5 ranges Resistance—5Ω—1MΩ in 4 ranges

Accuracy—5% of F.S.D. OSCILLATOR—1KHz and 465KHz (A.M.) at approx. 1 Volt. Size—160 x 97 x 40mm. Supplied complete with carrying case, test leads and battery. PRICE £9.95 net P. & P. 75p U4323

**MULTIMETER U4324**

34 Ranges. High sensitivity. 20,000Ω/Volt. Vdc—0.5—1200V in 9 ranges. Vdc—3—900V in 8 ranges. Idc—0.06—3A in 6 ranges. Iac—0.3—3A in 5 ranges. Resistance—25Ω—5MΩ in 5 ranges. Accuracy—dc and R—2 1/2% of F.S.D. ac and db—4% of F.S.D. Size—167 x 98 x 63mm. Supplied complete with storage case, test leads, spare diode and battery. PRICE £11.72 net P. & P. 75p U4324

**MULTIMETER U4341**

27 Ranges plus Transistor Tester. 16,700Ω/Volt. Vdc—0.3—900V in 8 ranges. Vdc—1.5—750V in 6 ranges. Idc—0.05—600mA in 5 ranges. Iac—0.3—300mA in 4 ranges. Resistance—2KΩ—2MΩ in 4 ranges. Accuracy—dc—2 1/2% ac—4% of F.S.D. Ite—10—350 in 2 ranges. Size—115 x 215 x 90mm. Complete with carrying case, test leads, and battery. PRICE £12.10 net P. & P. 75p U4341

**MULTIMETER U4313**

33 ranges. Knife edge with mirror scale. 20,000Ω/Volt. High accuracy, mVdc—75mV Vdc—1.5—600V in 9 ranges. Vdc—1.5—600V in 9 ranges. Idc—60—120 microamps in 2. Idc—0.6—1500mA in 6 ranges. Iac—0.6—1500mA in 6 ranges. Resistance—1KΩ—1MΩ in 4 ranges. db scale—10 to +12db. Accuracy—dc—1 1/2%. ac—2 1/2%. Size—115 x 215 x 90mm. Complete with carrying case. test leads and battery. PRICE £16.09 net P. & P. 75p U4313

(P.W.), LEIGHTON ELECTRONICS CENTRE  
59 North Street, Leighton Buzzard, LU7 7EG.  
Tel.: Leighton Buzzard 2316 (Std. Code 05253)

**FULL SPEC. LED'S**

Packs of 5—inc clips & data

	12.5" lens	10" lens	2" lens
RED	£0.75	£0.75	£0.75
GREEN	£1.20	£1.20	£1.20
YELLOW	£1.20	£1.20	£1.20
ORANGE	£1.20	£1.20	£1.20

**ECONOMY QUALITY LED'S**

MIXED BAGS ALL COLOURS OF ALL SIZES—IDEAL FOR EXPERIMENTS  
50—£5  
100—£9

**FULL SPEC LED SEVEN SEGMENT DISPLAYS**

0.3" COMMON ANODE  
L.H. DECIMAL  
RED, GREEN, YELLOW  
£1.35 ea inc data



**ECONOMY QUALITY**

0.3" COMMON ANODE—L.H. Dec. RE11 73p ea.

**PLASTIC BOXES—COLOUR GREY**



ABS—Ribbed inside on 5mm centres for 1.5mm PCB. Brass Corner inserts for securing top with 3mm screws. 62mm x 112mm x 31mm 1-9 52p ea; 10+ 48p. 120mm x 65mm x 40mm 1-9 66p ea; 10+ 62p ea; 150mm x 80mm x 50mm 1-9 75p ea; 10+ 71p ea.

**POLYSTYRENE—PLAIN INSIDE—TOP SECURED BY SELF TAPPING SCREWS**  
61mm x 112mm x 31mm 1-9 35p ea, 10+ 32p ea.

**SPECIAL OFFER**

SAMPLE PACK—4 BOXES—1 ea size £2.10  
P. & P. 25p per £1—minimum 25p.

**NEON INDICATORS**

150mm lead out wires

Types AA AH AG  
Fit 8mm hole and include spire clip for fixing  
RED, AMBER, CLEAR, OPAL —19p ea  
GREEN —26p ea

**TYPE MP**

Fits 6.4mm hole—nut fixing  
RED, AMBER, CLEAR, OPAL —22p ea

**LAMP HOLDER DE**



Takes either LES (with adaptor provided) or MIDGET FLANGE BULBS.  
Fits 13mm hole—nut fixing  
RED, BLUE, GREEN, AMBER, CLEAR, OPAL, ORANGE 25p ea (bulbs not provided)

QUOTATIONS FOR LARGER QUANTITIES ON REQUEST. ALL PRICES INCLUDE VAT AT 8%. ORDERS UNDER £10 please add 20p P.P. ORDERS FOR BOXES P.P. 25p per £1—Min. 25p to Max. £1.50 TERMS C.W.O.

**MICHAEL WILLIAMS ELECTRONICS**

47 Vicarage Avenue,  
Cheadle Hulme, Cheshire SK8 7JP



## AMATEUR BANDS

by Eric Dowdeswell G4AR

IT has always amazed me to realise that the act of sitting down and taking a written examination, successfully, should enable anyone to go on the air with 150 watts DC input, or the equivalent in SSB, without ever having touched a piece of radio equipment in their life! The results of the misuse of such a transmitter on the neighbouring TV's are not hard to imagine! Even if the transmission is 'clean' and up to the standards required by the Home Office the newcomer will not have the faintest idea on how to tackle TVI problems. Unfortunately, it is only after the 'black box' has been bought, at some expense, that these troubles come to light, which accounts for the number of commercial transceivers one sees for sale in our magazines, by newly licensed amateurs. And some other hobby gets another newcomer!

But it is no good carping about the problem if one is not prepared to suggest an alternative. The answer must be to return to the days when one could start with an 'artificial aerial' licence enabling experiments with transmitters to be made on a dummy load, followed by a minimum period on CW only with low power, say 25 watts and then on to the full licence. In this way a tremendous amount of experience can be gained and, above all, interest is continuously stimulated. Now, pushing buttons on the 'black box' soon palls, because one is learning precisely nothing other than the procedure of talking to another amateur and that's just as simple as talking on the telephone!

Nothing new in all this of course, so what's the snag? Just that the licensing authority would not be prepared to undertake the additional work involved. But in the interests of amateur radio could not the RSGB undertake to administer such a scheme? With official approval, of course, with the Home Office just issuing the bits of paper. Oh, well, just a thought!

Stephen Budd A8713 of Worthing reckons that since the sunspot numbers seem pretty constant now we could be at the bottom of the cycle so he's looking forward to better times. Well, I think we have been at the bottom for some time and in spite of the fact that new spots have already been seen for the new cycle it will be a year or so before any significant

improvement is noticeable. Paul Turner in Bishops Stortford turned his spell in bed with flu to good use by extending his aerial and putting his new QR666 close to hand. He likes this Trio model except that he feels he'd like a higher ratio drive on the bandspread to assist with resolving SSB on the higher frequency bands.

Now for the good news! Jeremy Hinton of Newcastle, Staffs., is now ex-A8962, thank goodness, and proud owner of G8LIZ for the moment but could have his G4+3 by this time, as he was about to take his Morse test any day. He couldn't wait to get on the air and so popped round to G8KTW's shack for a quick QSO with his new call.

Plenty of useful info in the latest Bulletin from Stew Perry W1BB for the 160m addicts. Like W8LRL who made WAC in two hours in the CQ 160m competition in January! As Stew says, 'WOW!' Seems OK1ATP write about his 160m beam in the Oct 75 QST. Anyone have any info on this? Depends whether it goes up or outwards before I could try it out! Stew worked EA8CR/9 for his No. 127 country on the band. Paul Barker in Sunderland zoomed in on the SSTV contest but bad conditions limited his results in Europe. The ARRL contest the same weekend didn't help either as no-one seemed to respect the accepted SSTV frequencies.

Peter Readings, not too far away from me, in Woking, was taken by my remarks on newcomers to amateur radio, in the March issue. He started in 1935 with a one-valve PW design for the short waves and getting back again now is brushing up for the RAE, in due course. Martin Chapple A9090 in Leamington Spa writes in for the first time. Aged 14, he was 'converted', as he puts it, to amateur radio when he visited a local special events amateur station. He progressed rapidly to a Trio 9R59DS and a 100ft wire and now contemplates a Microwave Module for 2m and 8-element yagi plus the same again for 70cm. He queries the many odd prefixes to be heard these days. The best way to find out where they are is to look at the ITU block allocations rather than the usual prefix list, which is obviously going to be out of date the moment it is printed. R. Berry of Colne thought he was interested in the VHF bands until he got his 9R59DS going on 20m and now has the DX bug. He heard TG9TI helping in the earthquake disaster which hit Guatemala.

Alan Doherty in Portrush, Co. Antrim found plenty on 80m in the early hours with 3D2KG pushing his total of countries heard on that band to 172. He has an FR400SDX and FR50B for keeping an ear on two bands at once! I wouldn't mind the FR400SDX by itself! His inverted-V on 80m is likely to be changed to a delta loop before long. More info, please! Peter



Allen A8677 was pleased with the improved results from using a 132ft wire and found ZL3NR/C on 80m, which can't be bad!

A most interesting letter from **Jim Durrant** G4CEX of Solihull, in which he supports my views on the lack of encouragement being offered to the newcomer by the RSGB. He plodded on alone "the only English book I found of help was the one by Frank Rayer" (well-known PW contributor). "When I got my ticket I joined the RSGB automatically but gave them up after a couple of years as a bad job . . . don't think I have seen one article in Radcom that would be of any use to a beginner". Need I say more? He continues "I wish the powers-that-be in the RSGB would take notice of your remarks and really do something for the novice!" Congrats Jim on sticking to it and I know you will not regret getting your ticket, in spite of the obstacles.

A letter in a similar vein from **A. J. Lees** of Bournemouth, copy to the RSGB, says he always recommends beginners to take PW "as this magazine has done more for beginners than any other magazine". He says "the newcomer eagerly scans Radcom to no avail and becomes disillusioned and thinks he has wasted his money". If you are listening regularly how about some reports OM?? **Alan Dixon** A9037 of Kingston sympathises with Steve Cottis who had trouble getting on an RAE course. Alan was only 14 when he started his course last September and has just heard that he has passed his RAE in

the December exam! Fantastic! So cheer up, Steve, it can be done.

Finally, a note from **Les Light** G3KDL, Hon. Sec. of the Radio Society of Harrow, club calls G3EFX and G8JMR. Meetings every Friday at 8pm at the Harrow Sea Cadets HQ, Woodlands Road, Harrow. Features during April are a debate on HF and VHF propagation and a talk on mobile operation by Fred Barnes G3AGP. Two evenings a month are kept for practical work and construction. So flock along folks, nothing to lose but your bus fare!

I have been asked to dispose of a Hallicrafters S108 receiver. Valves, thank goodness, MW to to 32MHz continuous, with amateur bands 10 to 80m on main dial, BFO, noise limiter and excellent manual. Condition is very good and has been checked out by yours truly. Sorry, but must be inspect and collect, which a buyer would probably prefer anyway!

### Log extracts

**S. Budd:**— 80m A4XGC CO2JA C31LC EA9FC FG7AR/FS7 HZ1SH PJ0USA OE6DK/YK ZL3GC ZL3NR/C 9Y4NP 40m VK3ZL 6W8FP 15m A4XGC ZD8AR 9V1SH 20m FG7AR/FS7 ST2SA (14250 0700 Fridays) VS6BL YB1HF 9N1MM

**P. Barker:**— 20m SSTV CT1JI F9XY I1SU I0PCB OZ5FG SM5EEP 20m A6XP EA8CR/9 OE6DK/YK OE7XBI (Olympic Games, Innsbruck)

**A. Doherty:**— 80m EA8CR/9 FL8DJ HK1CHL HP3XWB HR3JJR KL7HFQ PJ8CO VP2DQ 5Z4LW 3D2KG 20m YN7NHW

**P. Allen:**— 80m WB9AJF/6Y5 ZL3NR/C 15m TU2EI 5N2ESH OE6DK/YK (Golan Heights) C9MJ0 (Mozambique) 3B8CV

All stations are SSB except those of P. Barker, all SSTV.



## SHORT WAVE BROADCASTS

by *Derek Bell*

A "defector", if I may call him that, from the ranks of the licensed amateurs is **Allan King** G4BKM of London who forwards a sample of the duplicated report forms he sends out in search of QSL cards. These forms give all the relevant information in neatly spaced sections with the largest space devoted to the ten minutes of programme content that stations usually require. Despite this, Allan complains that Radio Pakistan turned down a request and on checking the tape recording of the broadcast all details were found to be correct. It seems to me to be a case of the station log being at fault!

Two more newcomers to the hobby ask questions that I must deal with in two sections, **A. B. Towler** of Newcastle on Tyne would like to know what to put into reception reports to gain QSL cards. This should comprise the following: time in GMT, frequency, your set and aerial type, the SINPO rating

of the signal, ten minutes verbatim of the programme content and your name and address. It also helps to say a few kind words and say "please"! Information on types of set, aerial systems etc can be obtained from the many very good leaflets issued by Radio Nederland, PO Box 222, Hilversum, Holland. I do not know of any duplicated report forms for sale but the Post Office air letter form should suffice provided that one does not have to send IRCs to the station.

**Sylvia Wood** of Godalming is our second newcomer although she is seeking help to get her RAE "ticket" so we may see her. Ah well! win some, lose some! The path to this side of our hobby starts by getting the Guide to Amateur Radio from the RSGB. Meantime, Sylvia, you will have to be content with joining we mere DX fanatics. The log you were asking about is usually a tattered notebook that the DXer keeps of the time, date, frequency and station name in order to jog his memory or give him a guide as to what was heard and at what time of year, since not only does reception vary with the season but we are now in the sunspot minimum of the solar cycle and it will be 1978 before we can expect the beginning of any improvement.

Midst all the gloom however, **David Sewell** sends us a selection of his best and these are Latin American stations. This aspect of our hobby attracts many listeners who like to specialise in these stations. since there are many differing styles and programme content is equally varied. Look forward

# CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL  
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.

1 ST. MICHAELS TERRACE, WOOD GREEN,  
LONDON N22 4SJ Phone 888-4474

## CLEAR PLASTIC PANEL METERS

Size 59mm x 46mm x 35mm these meters require a 38mm hole for mounting.

ME6 = 0 to 50 micro amp Full Scale

ME7 = 0 to 100 micro amp Full Scale

ME8 = 0 to 500 micro amp Full Scale

ME9 = 0 to 1 m/a Full Scale

ME10 = 0 to 5 m/a Full Scale

ME11 = 0 to 10 m/a Full Scale

ME12 = 0 to 50 m/a Full Scale

ME13 = 0 to 100 m/a Full Scale

ME14 = 0 to 500 m/a Full Scale

ME15 = 0 to 1 amp Full Scale

ME16 = 0 to 50 volts

ME17 = 0 to 300 volts

A.C. Full Scale

ME18 = "8" Meter

ME19 = "VU" Meter



OUR PRICE £3.00  
+ 8%

## WAFER SWITCHES

1 Pole 12 Way

2 Pole 2 Way

2 Pole 3 Way

2 Pole 4 Way

2 Pole 6 Way

3 Pole 4 Way

4 Pole 3 Way



27p each + 8%

## SCOOP PURCHASE MW-LW-FM STEREO TUNER

We supply a MW-LW-FM-Stereo Tuner fully wired and aligned on a 6" x 4" x 1 1/2" printed board, plus the Ferrite Aerial and switch which you connect following our complete instructions. Now you only need a 9-12 volt D.C. supply and you can feed this tuner into any Stereo Amplifier.

FANTASTIC VALUE AT £7.00 + 25% VAT

## POWER SUPPLY UNITS + 8%



PP1 switched 3, 4, 6, 7, 9 and 12 volts at 500 m/a, with on/off switch and pilot light. Size: 130mm x 55mm x 75mm.

ONLY £4.00

PP2 Switched 6-74-9 volt Battery Eliminator. Approx. size 2 1/2" x 2 1/2" x 3 1/2". Ideal for cassette recorders £3.25 PP3 Car converter. From 12v Pos. or Neg. to 6-74-9 volt. Easy to fit and transistor regulated £3.90

## LOW VOLTAGE STEREO AMPLIFIER

8 Transistor Stereo Amplifier with Vol'e, Base, Balance and Tone Controls. Approx. 3 watts into 8 ohm per channel needs a 9/12 volt DC supply and is complete on a 2 1/2" x 7 1/2" P/C board.

Ideal for domestic record players, etc. A Bargain at £5 + 25% VAT.

## ABS PLASTIC BOXES + 8%

Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels.

1005 = 105mm x 73mm x 45mm = 50p

1006 = 150mm x 75mm x 47mm = 72p

1007 = 184mm x 124mm x 60mm = £1.28

1021 = 106mm x 74mm x 45mm (sloping front) = 55p

## TELESCOPIC AERIAL

Nine section fully swivelling telescopic aerial with 4BA single bolt fixing or two hole fixing bracket.

Fully extended = 43" Fully closed = 7"

Our Price 50p + P/P + VAT @ 25%

## LOW NOISE LOW PRICE CASSETTES + 8%

Good quality tape in well made screw type cassettes. Presented in single plastic cases.

C60 = 33p C90 = 48p C120 = 60p

10% Discount on ten or more cassettes of one type.

## LOUDSPEAKERS + 25%

2 1/2" 8 ohm 60p

2 1/2" 40 ohm 60p

2 1/2" 8 ohm 60p

3" 8 ohm ceramic £1.25



10-INCH 8 OHM DUAL CONE Manufactured by "ELAC" to a very high standard these loud-speakers are a real bargain SPEC:—Size = 10" Dual Cone. Power = 10 Watts Frequency = 40-12000Hz + 25%. Our Price = £3.75p each


## BARGAIN PROJECT BOX.

A plastic box with moulded extrusion rails for PC or Chassis panels with metal front plate fitted with four screws (all supplied).

An ideal box to give a small project a professional finish SIZE: (Internal) 81mm x 31mm x 29mm.

OUR PRICE

40p. + 8%

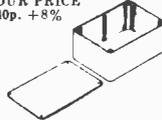

## MINIATURE RELAYS

Brand new range of British made Relays. Size 1 1/2" x 1" x 1/2". All two changeovers with 250v 1.5A contacts and suitable for fitting on 1mm Veroboard.

Type Volts Cur. Ohms

rrnt

27/A 12v 17M/A 700

21/A 12V 28M/A 430

12/A 6v 33M/A 185

All £1.30 each

# Get to the Point Quickly with ANTEX Model X25

prices include Vat p & p extra as shown in brackets

## Point 1

Near-perfect insulation. Breakdown voltage 1500 A.C. Leakage current 3.5 uA.

## Point 2

Top-efficiency in heat transfer. Element slides inside the soldering bit. 25 watts but equivalent in heat capacity to 60 watts.

## Point 3

High grade phenolic handle (own moulding!) Stainless steel shaft. — 3 core 0.4mm. Flexible lead.

## Point 4

Iron-coated bits that do not stick to the shaft but slide on and off easily. 3 tip sizes 2.4, 3.2 and 4.7mm.

## Point 5


Price with standard (3.2mm.) bit £3.20 (P+P 0.22) Spare elements £1.52 Spare bits £0.50 incl. V.A.T.

## Point 6

A well balanced tool — length 22cm. weight 50gr.
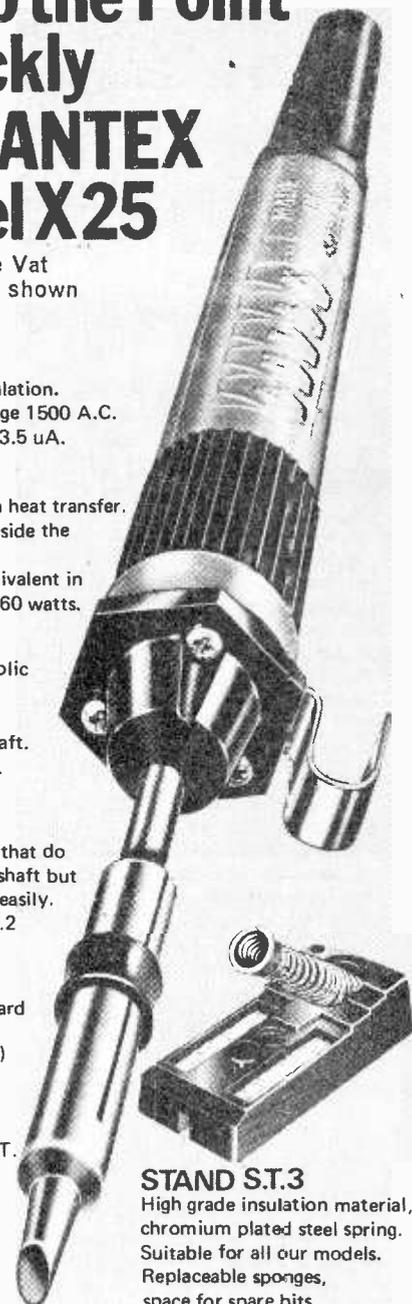
## STAND S.T.3

High grade insulation material, chromium plated steel spring. Suitable for all our models. Replaceable sponges, space for spare bits. Complete £1.37 (P+P 0.24)



From electrical, radio or car accessory shops or from Antex Ltd., Freepost (no stamp required) Plymouth. PL1 1BR Telephone 0752 67377/8

Please send the following:

Name \_\_\_\_\_

ANTEX colour catalogue. Address \_\_\_\_\_

I enclose cheque/P.O./Cash (Giro No. 258 1000)

PW/5/76

U.K. CARRIAGE 50p UNLESS OTHERWISE STATED

VAT—All prices are excluding VAT. Please add to each item the VAT rate indicated.




# CODAR®

TELECOMMUNICATIONS AND ELECTRONIC EQUIPMENT MANUFACTURERS



## AERIAL TUNER UNIT

### ★ R.Q.80

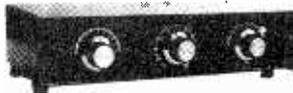

This new CODAR A.T.U. tunes 1-5-30MHz and is designed to match random length single wire aerials from a few feet of indoor aerial to long outdoor wires to the receiver. Hi-Q low loss air spaced CODARCOIL inductor with no less than 10 position tapping switch and tuned by two air spaced variable capacitors, gives exceptionally wide range of matching to all types of receivers. Compact size, handsome low slim line cabinet 9" x 5" x 2 1/2". Ready for use. Price £11.00 (carr. free + £2.75 VAT. "Well satisfied" Mr. Andrew. Devon.

### ★ P.R.40

R.F. PRESELECTOR



Will substantially improve receiver performance over 1.5/35 MHz. Three switched bands, Codar-coil low-loss airspaced inductor with F.E.T. and wide band R.F. amplifier gives outstanding performance. A must for the keen S.W.L. Price £11.00 (carr. free) + £2.75 VAT. "Fantastic" Mr. A. White, Lincs.

### ★ CODAR COIL-PACK

Complete unit 550 KHz-30 MHz in 4 switched bands. With Aerial trimmer. Aligned, tested, ready for use. Suitable for valve or F.E.T. Mixer/Osc. As used in the CR70A. Full instructions included for 450/470 KHz I.F. Price £7.99 (carr. free) + £1.99 VAT. "Just what I've been waiting for!" Mr. New, Sussex.

#### ★ CR70A

Due to the very large amount of orders for the hand-built CR70A communications receiver (UK and Export) now in hand—we regret that we are unable to accept orders until further notice.

#### ★ JUST OUT!!

The new "Mini Clipper RB"—ready built/tested (less PP6 battery) with 12 month guarantee—only £15.00 + £3.75 VAT!—Also Multiband RB ready built/tested (less batt.) £24.00 + £6.00 VAT!

Pay by ACCESS/BARCLAYCARD. Quote No. clearly on Order.



CODAR® TELECOM LTD., UNIT 2, BURRELL BUILDINGS, CHURCHILL INDUSTRIAL ESTATE, LANCING, SUSSEX. Tel: 090-63-61901

### ★ SHORT WAVE KITS

You'll be proud to say... "I built it!"

### ★ NEW!! MINI CLIPPER T.R.F. SHORT WAVE KIT

Tunes 550 KHz-30 MHz complete coverage with 4 miniature plug-in coils. Receives AM/CW/SSB. Electrical bandspread. Output for low impedance headphones or any 2/8 ohm speaker (optional extras). Full step by step pictorial instructions, simple to build. Printed circuit board. Steel cabinet. A quality Codar-Kit, 12 month guarantee. The ideal low cost starter Kit for the beginner S.W.L. to enjoy the fascinating hobby of long distance listening and collection of colourful Q.S.L. cards from all parts of the world! (Size and appearance similar to the RQ80). "Worked first time".... Mr. Short-Dudley Price complete (less PP6 battery) £10.80 (carr. free) + £2.70 VAT.

### ★ MULTIBAND-6 T.R.F. SHORT WAVE KIT

Tunes 550KHz-30MHz complete coverage with 4 miniature plug-in coils. Receives AM/CW/SSB. Separate electrical bandspread. Main tuning calibrated, vernier slow motion drive. Output for any external 2/8 ohm loudspeaker. Headphone jack. World-wide reception. Handsome styling, steel cabinet. Full pictorial instructions, easy to build, printed circuit board. Price complete (less PP6 battery) £18.00 (carr. free) + £4.50 VAT.

### ★ CODAR AERIAL-KIT

Approx. 50' stranded copper Aerial wire, plus 25' insulated lead-in wire, 4 insulators, leaflet hints and tips on types of aerial. Price £2.40 (post free) + 60p VAT.

### ★ FREE!!

Illustrated leaflets on request! (Stamp appreciated!) EXPORT CUSTOMERS! We offer world wide mail order, free quote/leaflets on request. (International Reply Coupon appreciated!) CODAR AIR SPACED COILS—Any quantity supplied—please state dimensions required, for free quote.

### FND500 Jumbo 0.5" CC Red LED now only £1-02

### ADVANCED CLOCK KIT

Complete kit including attractive slim case for 6 digit alarm clock with bleep alarm, snooze, high brightness driving of Jumbo LED displays, automatic intensity control—with optional add-ons of touch switch snooze control and crystal control/battery back-up. £26.80

### P.E. CAR CLOCK with Journey Timer

6 digit clock for use in any car with 12V battery, with an independent journey timer incorporated. Bright Jumbo LED display comes on with ignition—automatic intensity control. Complete kit of all parts needed including case, PCB's and all components. Full Instructions. £39.50

Easy to Build E.E. DIGITAL CLOCK (Jan. Issue). Kit of all components, including case etc., for this attractive clock with 12mm green display. Full instructions. £15.70  
50 Hz Xtal Timebase Kit for clocks (incl. advanced kit above). £8.28

<b>CMOS ICs</b>	CD4029 0.84	CD4059 3.64	CD4510 1.12	<b>Displays</b>
<b>RCA MOTO ONLY</b>	CD4030 0.46	CD4060 0.82	CD4511 1.28	SLT-01 5.80
	CD4031 1.82	CD4061 16.43	CD4514 2.56	DL704E 0.75
CD4000 0.17	CD4032 0.88	CD4062 7.33	CD4515 2.56	FND500 1.02
CD4001 0.17	CD4033 1.14	CD4063 0.90	CD4516 1.12	
CD4002 0.17	CD4034 1.56	CD4066 0.58	CD4518 1.03	<b>Display Int.</b>
CD4006 0.97	CD4035 0.97	CD4067 2.95	CD4520 1.03	SN75491 0.81
CD4007 0.17	CD4036 1.82	CD4068 0.18	CD4527 1.30	SN75492 1.02
CD4008 0.79	CD4037 0.78	CD4069 0.18	CD4532 1.16	CA3130 0.88
CD4009 0.46	CD4038 0.88	CD4070 0.18	CD4555 0.74	
CD4010 0.46	CD4039 2.86	CD4071 0.18	CD4556 0.74	<b>Flat Cable</b>
CD4011 0.17	CD4040 0.88	CD4072 0.18	MC14528 0.86	20WAY 1M
CD4012 0.17	CD4041 0.69	CD4073 0.18	MC14534 0.84	10M for 8.50
CD4013 0.46	CD4042 0.69	CD4075 0.18	MC14553 4.07	10WAY 1M
CD4014 0.83	CD4043 0.83	CD4076 1.27	MC14566 1.21	10M ter 0.80
CD4015 0.83	CD4044 0.77	CD4077 0.18	MCM14552	10M ter 4.80
CD4016 0.46	CD4045 1.15	CD4078 0.18		8.05
CD4017 0.83	CD4046 1.10	CD4081 0.18	<b>Clock Chips</b>	
CD4018 0.83	CD4047 0.74	CD4082 0.18	MK50253 5.80	
CD4019 0.46	CD4048 0.46	CD4085 0.59	MM5314 4.44	
CD4020 0.92	CD4049 0.46	CD4086 0.59	AY51224 3.66	
CD4021 0.83	CD4050 0.46	CD4089 1.27	AY51202 4.76	
CD4022 0.79	CD4051 0.77	CD4093 0.66	MK50250 5.00	
CD4023 0.17	CD4052 0.77	CD4094 1.33	<b>CMOS</b>	
CD4024 0.84	CD4053 0.74	CD4095 0.86	No VAT or	
CD4025 0.17	CD4054 0.85	CD4096 0.86	P & P	
CD4026 1.42	CD4055 1.08	CD4097 2.95	RCA1975 2.87	
CD4027 0.46	CD4056 1.08	CD4099 1.50	RCA1975 2.87	
CD4028 0.74	CD4057 20.35	CD4502 0.98	CMCMOS 2.77	

ADD VAT at 8% (Higher rate does not apply to any of above). 15p P & P on orders under £23—Despatch is by 1st Class Post. Price list and A.F.S. on an order, or on request (see SAV helps). Official orders welcomed (written or phoned)—Univs, Polys, Govt, Cos. etc. Export orders: no VAT, add 35p (Europe) £1 (overseas) for Airmail p & p. (No Export outside Europe for databooks and transformers).

SINTEL, 53n Aston Street, Oxford. Tel: 0865 49791

### VALVE BARGAINS

Any 5-64p, 10-£1-10, 50-£5. Your choice from the following list: ECH84, ECC82, ECL80, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PCL86, PFL200, PL36, PL504, PY33, PY81, PY800, PY88, EH90, 30FL1, 30FL2, 30PL14, 6F28

Colour Valves 30p each PL508, PL509, PY500/A.

Small Plastic Boxes (white) made out of high impact plastic with flack on lids. Ideal for most projects. All three types one price. Prices 15p each. Ten £1.38. Size (approx.): Type 1—3 1/2ins x 2 1/2ins x 1 1/2ins deep. Type 2—3 1/2ins x 2 1/2ins x 2 1/2ins deep. Type 3—3 1/2ins x 3 1/2ins x 1 1/2ins deep.

Prices include V.A.T. P. & P. under £1.15p, £1 to £3.20p above £3.30p. Overseas at cost. Money back guarantee on all orders.

### ELECTRONIC MAILORDER LTD.

62 BRIDGE ST., RAMSBOTTOM, BURY, LANCs. Tel. Rams. 3038

### AERIAL BOOSTERS

We make three types of Aerial Boosters all for set top fitting, with Co-ax Plugs and Sockets. B11—For Stereo and Standard VHF Radio. B12—For the older VHF Television, please state BBC1 and ITV Channels. B45—For mon. or colour this covers the complete UHF band. All Boosters are complete with Battery and take only minutes to fit.

Price £3.90 each.

### CJL CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT ALL PRICES INCLUDE P&P AND V.A.T.

<b>ANTEX SOLDERING IRONS</b> (with slide on & off bits)	<b>WIRE STRIPPER &amp; CUTTER</b> £0.85
15W 'C' miniature irons £2.30	<b>HAND DRILLS</b> Laytool precision, compact, 5/16" chuck £3.99
3/32" 1/8" 3/16" bits—each £0.45	<b>AERIALS</b> Extend 15-120cm £1.50
'C' Elements £1.10	<b>CASSETTE</b> 'Head Demagnetisers' Shaped pole-saves time £3.65
18W 'G' miniature irons £2.50	<b>EARPHONES</b> Stethoscope £1.25
3/32" 1/8" 3/16" bits—each £0.45	Crystal earphone, lead & plug £0.65
'G' Elements £1.35	Headphone, 2, 000 n. £3.20
15W CCN'Low leakage irons £2.70	<b>INTERCOMS</b> 2-station £6.35
3/32" 1/8" 3/16" bits—each £0.45	<b>MICROPHONES</b> Dynamic £2.15
'CCN' Elements £1.50	<b>PRINTED CIRCUIT KITS</b> -All items for producing p.c.'s £3.99
25W X25'Low leakage irons £2.30	<b>SIGNAL INJECTOR</b> -Audio through video signals, self contained £4.25
3/32" 1/8" 3/16" bits—each £0.47	<b>STEREO HEADPHONES</b> 8n. £4.85
'X25' Elements £1.15	<b>SPEAKERS</b> -75mm dia. 8n. £1.00
'SK1', 'SK2' Soldering Kits £3.85	
ST3 Stands-for all models £1.10	
<b>SOLDER</b> In Bib dispenser £0.45	



to Lara Venezuela on 4800 at 0220, Juventud Venezuela on 4900 at 0050, Barquisimeto Venezuela on 4990 at 0135. These were all pulled in on Dave's Trio 9R59DS with a trap dipole 25 feet high, but all the same, undoubtedly and verily, only for night-owls!

**Ian Walker** of Crouch End, London is baffled by a station he heard on 2300 and 2750 simultaneously. This came in on Ian's Sony ICF5500M via the set's telescopic aerial. The clue to the ident of this station is its claim to be "The voice of Soviet public opinion"! The station is Radio Peace and Progress and very little is known of its staff or its aims for that matter. Ian describes the programme content as documentary on political topics.

Just a short while ago the latest edition of the Radio RSA bulletin plopped on to the mat at chez Bell. This leaflet, a mere shadow of its former self, covers the period of the summer schedules starting in March and indicates that RSA will use 5980, 7270, 11900, 11970, 17780, 15155, 15220 and 21535kHz. Their signals are radiated, with short breaks, twenty four hours a day to various target areas and in different tongues, but, strangely, while they have English transmissions they only specify North America as an English target area while the other area is just designated "Europe".

**Robin Bayley** of Kingswood School, Wolverhampton reports the 15155 RSA service in German at 1800, on a Marconi R1475 with a long wire, plus NHK Tokyo on 15430 at 0805, TWR Bonaire on 11920 at 0030, Radio Nacional de Brazil on 11780 at 2100. Another youngster is **Stewart Fenwick** of Clack-

mannan in Scotland, who reports that Radio Pyongyang recently sent him a QSL after 106 days and I use this to mention that reports have been noticed of late that the station in Fukien, China has re-emerged after a long period, on 2430. This station is very rarely reported and I can remember at a European DX Council conference a German DXer showing me one of their QSLs, written on rice paper in Chinese, which he had waited a donkeys age to get. At this time he claimed the station was a small transmitter working mobile so if any one chances on them please let us know all the details.

**Ken Smith** of Ross-on-Wye has some enquiries to make about the Voice of America transmitter at Rhodes. He thinks that the frequency has changed for the 2100 session and asks for any information of new frequencies. As I have said above, it is about this time of year that the schedules change and so it is possible that this station has disappeared from its usual part of the spectrum. A reader who just wants to be known as "SS" suggests that the Radio Australia signal on 9745 mentioned recently, in fact comes from Melbourne as he monitored it over Christmas. This may well be since stations, through many causes, have to depart from the published schedules and the poor old scribe slaving over a hot tripe-writer can only rely on his friends who write in to keep him up to date. SS also craves info on "what to do with aerials", well, one thing not to do is to fasten them rigidly to trees, since, as happened to a friend of mine in the recent gales, the tree swayed and down came the lot! The answer to this is to secure the long wire with one of those rubber "ropes" that are used on motor cycle panniers and car roof racks. If it is an inverted "L" longwire have the foot of the "L" running down from the support post and not down the house wall, and feed into the house via a wire run from the far end of the aerial. That brings this session to a close so I will wish you and yours best 73s.

## BROADCAST BANDS

### MEDIUM WAVE DX

by **CHARLES MOLLOY**

**T**HIS MONTH **Alan Crookes** reports from his new QTH in Sheffield. He had to rebuild his loop after moving house but his 'shack' is now fully operational and he is using a Murphy B40A communications receiver to pull-in his medium wave DX. Stations logged include WINS, the all-news station in New York City, which transmits on 1010kHz with a power of 50kW and three locals in Newfoundland, CBN in St John's on 640kHz, CKVO in Clareville on 710kHz and CJON St John's on 930kHz. Alan points out that the announcement "VOCM Radio Service" from CKVO is misleading since CKVO is not mentioned in many station listings, including the 1975 World Radio and TV Handbook, as it came on the air as recently as December 1974. The VOCM Radio Service is a local network in Newfoundland with VOCM on 590kHz in St John's as the key station. Other members of

the network, in addition to CKVO, are CHCM in Marystown on 560kHz, CKCM in Grand Falls on 620kHz, CKGA in Gander on 730kHz and CKIM Baie Vert on 1240kHz, all of which have been heard recently in the UK. VOCM is one of the few medium wave stations in Canada to use the prefix V in its call sign; the majority start with the letter C. Newfoundland became the 10th province of Canada in 1949 but VOCM and four other well established broadcasters managed to hold on to their original call letters that were issued when the territory was still a Crown colony.

The World Radio and TV Handbook, generally regarded as the DXers 'bible' is published annually in Denmark and distributed in the UK by Billboard Publications. It is printed in English and can be ordered through bookshops. It costs £5. The WRTVH lists all known broadcasting stations (and TV stations) with the exception of low power locals in the USA and low power relays elsewhere. AM broadcasting stations are listed by frequency and there is a section for each country which gives the hours of transmission, addresses and QSL information. The less pretentious "Guide to Broadcasting Stations" at 80p is produced in the UK by Butterworth and is on sale in many bookshops. AM broadcasters in Europe and North Africa are listed along with a selection of the more powerful medium wave transmissions from other parts of the world.



This is a very useful book for the beginner. A similar publication "World Radio TV Listings" is available for 60p.

The Foreign Broadcasting Information Service of the United States Government produces "Broadcasting Stations of the World Part 2" at intervals of about two years. All broadcasting stations located outside the United States and in the frequency range 150kHz to 26MHz are listed. This bulky paperback can be obtained for \$2.50 postpaid from the Superintendent of Documents, Government Printing Office, Washington, DC 20402, USA. Quote Pr.Ex-7.9:972 Part 2 and be prepared for a wait of several weeks!

**Steve Whitt** (London) refers to a wavetrap which he inserted between his loop aerial and the input to his communications receiver, in order to reduce local interference on 1546kHz. It is a parallel tuned circuit which can be tuned across the medium wave band. It offers a high impedance at its resonant frequency and a low impedance at all others and when it is placed in series with the aerial lead, it will reduce the strength of an unwanted station, leaving others unaffected. A medium wave tuning coil and appropriate variable capacitor, or pre-set, to tune across the medium wave band, are the only components required. The coupling winding is not used. Tune the receiver to the unwanted signal, adjust the wavetrap for minimum signal strength and the receiver can be used normally.

**S. Lydon** (Kingston-on-Thames) has been trying, without success, to tune-in to the Irish Speaking Radio (Radio na Gaeltachta), a network of VHF and MW transmitters in the Republic of Ireland. There are three outlets on the medium waves; Connemara on 539kHz with a power of 2kW, Kerry on 962kHz with 1kW and Donegal on 1250kHz with 10kW. In spite of their proximity to England these stations are rather difficult to pick-up, mainly on account of co-channel interference. The writer, from his QTH

in North West England, can hear Connemara during the evening after dark, using a Marconi Mercury receiver and a medium wave loop. The station is on the air from 1800 to 2100 approximately and with a bit of luck might just be audible in the London area. Radio na Gaeltachta is an example where DX means Difficult rather than Distant. Torshavn in the Faroe Islands on 584kHz is another 'Difficult' station. Some DXers, including the writer, have had to wait for years before receiving a rather attractive QSL card as a reward for persistence.

**D. R. Mayhew** reports hearing Kinshasa in Zaire on 692kHz and Dakar in Senegal on 764kHz, using a Philips receiver and medium wave loop aerial. Medium wave stations in Africa are often heard well in the UK at this time of year. A loop is very useful for listening to this continent since the DX lies to the south and the interference from Europe, in general, comes from the east so it is not difficult to null-out the QRM. Stations to look for during the evening are Tenerife in the Canary Islands which broadcasts in Spanish on 620kHz; ELBC in Monrovia, Liberia which has English programming on 629kHz; Enugu, Nigeria which is a weak signal clear of interference on 1320kHz at 2300; Nouakchott, Mauritania on 1349kHz and, from the Republic of Guinea, Conakry which is a strong signal on 1403kHz after 2300hrs. There are two long wave stations in Africa, both coming in at good strength in the UK. From the top of a mountain near Azilal in Morocco the home service in Arabic is transmitted with 800kW on 209kHz, while from nearby Algeria the French programme comes from Tipaza with a power of 1500kW on 245kHz.

#### **BROADCAST BANDS**

**Short Wave** reports by the 15th of the month to Derek Bell c/o Practical Wireless, Fleetway House, Farringdon Street, London, EC4A 4AD.

**Medium Wave** Logs to Charles Molloy, 132 Segars Lane, Southport, PR8 3JG.

#### **AMATEUR BANDS**

Logs covering any Amateur band/s in band/alphabetical order by the 25th of the month to Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashtead, Surrey, KT21 2TW.

## **KINDLY NOTE!**

### **TELE TENNIS SCORING UNIT**

**September 75**

Some readers have queried the origin of the timing signals used for this unit. The signal Q3 originates at pin 13 of IC55, signal SP2 at pin 3 of IC56 and signal SP6 at pin 8 of IC57. Note also that IC32 is shown as a 7410 which should read 7400, as in circuit diagram.


## **AVAILABLE NOW!**

### **REPRINT OF PW'S TELE-TENNIS SERIES**

**July-November 74.**

**Send 75p + 10p (post & packing) to:-  
Editor (PW Tele-Tennis),  
Fleetway House, Farringdon Street,  
London, EC4A 4AD**

# Greenbank Electronics Established 1970

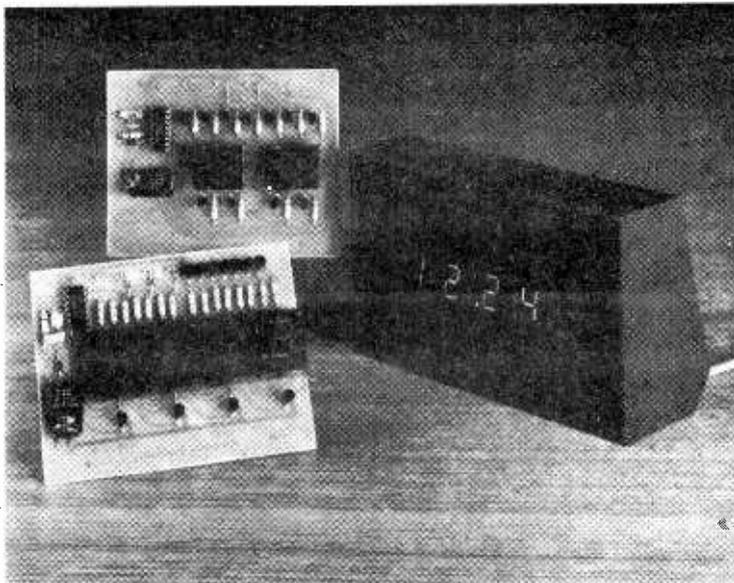

The illustration shows the two P.C.B. module kits already assembled, one has 8mm high digits, the other has 16mm high digits. Also shown is an example of a completed clock. Free on request: Data on AY-5-1224 and MK50253 clock chips, 4 and 6 digit alarm clock suggested circuits, quartz crystal timebase, and L.E.D. displays, (If you can send an S.A.E., it makes things a little easier for us).

## CLOCK CHIPS

AY-5-1224A 4 digit basic clock £3.50 MK 50253 4/6 digit alarm/snooze £5.50

**ECONOMY RED LED DISPLAYS** ('Class II' quality, but guaranteed by us, fully returnable if not satisfied):

DL-707E/DL-704E 8mm (0.3") 70p. DL-727E/DL-728E 12mm (0.5") Double Digit £1.80. DL-747E/DL-750E 16mm (0.6") £1.50.

**CMOS WITH DISCOUNTS!** (Any mix: disc. 10%, 25+, 25% 100+)

4000/14000	0-15	4023/14023	0-15	4043/14043	0-80	4066/14066	0-55
4001/14001	0-15	4024/14024	0-60	4044/14044	0-75	4067/—	2-95
4002/14002	0-15	4025/14025	0-15	4045/—	1-15	4068/14068	0-15
4006/14006	0-95	4026/—	1-40	4046/14046	1-10	4069/14069	0-15
4007/14007	0-15	4027/14027	0-45	4047/—	0-70	4070/14070	0-15
4008/14008	0-75	4028/14028	0-70	4048/—	0-45	4071/14071	0-15
4009/14009	N/S	4029/—	0-90	4049/14049	0-45	4072/14072	0-15
4010/14010	N/S	4030/14030	0-45	4050/14050	0-45	4073/14073	0-15
4011/14011	0-15	4031/—	1-80	4051/14051	0-75	4075/14075	0-15
4012/14012	0-15	4032/14032	0-85	4052/14052	0-75	4076/14076	1-25
4013/14013	0-45	4033/—	1-10	4053/14053	0-75	4077/14077	0-15
4014/14014	0-80	4034/14034	1-35	4054/—	0-95	4078/14078	0-15
4015/14015	0-80	4035/14035	0-95	4055/—	1-05	4081/14081	0-15
4016/14016	0-45	4036/—	1-80	4056/—	1-05	4082/14082	0-15
4017/14017	0-80	4037/—	0-75	4057/—	20-35	4085/—	0-55
4018/—	0-80	4038/14038	0-85	4059/—	10-60	4086/—	0-35
4019/14019	0-45	4039/—	2-85	4060/—	0-90	4089/—	0-65
4020/14020	0-90	4040/14040	0-85	4061/—	16-40	4093/14093	0-65
4021/14021	0-80	4041/—	0-65	4062/—	N/S	4094/—	1-50
4022/14022	0-75	4042/14042	0-65	4063/—	0-90	4095/—	0-85

## DIGITAL CLOCK P.C.B. MODULE KITS

(ex. VAT, p&p)

With 8mm digits **£9.29**

With 16mm digits **£12.53**

Features:—

- ★ High quality fibreglass P.C.B. 112 × 89mm (both types), a case is available as illustrated, or you can make your own.
- ★ All components mount on one side of the board for neatness and easy construction.
- ★ AY-5-1224A chip and L.E.D.s 'plug-in' for simple assembly and servicing.
- ★ Uses L.E.D. display (believed to have the longest lifetime of all electronic display types known at present).
- ★ A single 12V, 500mA, 50 Hz supply is the only input required (e.g. our 2 × 6V Min. Tr. @ £1.52 ex. VAT, etc.).
- ★ Eight pages of 'step-by-step' instructions are provided, and back up assistance if you need it—success guaranteed! Suitable for even the absolute beginner.
- ★ 12 or 24hr display modes.
- ★ Easily converted to give additional 4, range 'stop-watch' facility, for e.g. darkroom timer.
- ★ All parts available individually at no increase in price—buy only what you need.
- ★ Modules can be supplied already assembled and tested for an extra 75p (+ VAT etc.).
- ★ Module kits include: P.C.B., AY-5-1224A chip, 4 L.E.D. digits, transistors, diodes, resistors, capacitors, fuse and holder, pins.


## CA 3130 COS/MOS Operational Amplifier 75p

4096/—	0-85	14515/4515	2-35	14543/—	1-30
4097/—	2-95	14516/4516	1-10	14549/—	2-95
4099/—	1-50	14517/—	5-40	14552/—	8-05
		14518/4518	1-90	14553/—	3-50
		14520/4520	1-00	14554/—	1-20
		14521/—	2-00	14555/4555	0-70
		14522/—	1-90	14556/4556	0-70
		14524/—	N/S	14557/—	3-20
		14526/—	1-20	14558/—	0-90
		14527/4527	1-20	14559/—	2-95
		14528/4098	0-85	14560/—	1-35
		14529/—	1-30	14561/—	0-45
		14530/—	0-65	14562/—	5-25
		14531/—	1-25	14566/—	1-20
		14532/4532	1-60	14572/—	0-35
		14508/4508	2-35	14534/—	6-00
		14510/4510	1-10	14536/—	2-85
		14511/4511	1-25	14537/—	15-25
		14512/—	1-05	14539/—	1-05
		14514/4514	2-35	14541/—	1-80

Terms: C.W.O. Add VAT to all prices at 8%. Post etc., U.K. 10p per order, export 75p (no VAT). All orders processed on day of receipt
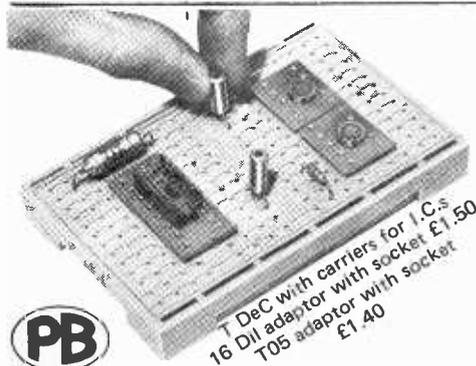
## GREENBANK ELECTRONICS (Dept. W5P)

94 New Chester Road, New Ferry, Wirral, Merseyside, L62 5AG, England. Tel:—051-645 3391



## FREE SUPER SOLDER BOARD WITH EVERY DEC BUILD CIRCUITS EASILY PUSH COMPONENT-IN NO SOLDERING

Designing circuits is easy with DeCs, just plug in your components. Each DeC breadboard is complete with step-by-step instructions. When circuit is designed, take components out and use them again OR plug components into SUPER SOLDER BOARDS for a perfect, finished P.C.B.

TO P. B. Electronics (Scotland) Ltd., 57 High Street, Saffron Walden, Essex. Please find enclosed P.C./Cheque value £

\_\_\_\_\_ S-DeCs + Free Super Solder Board £1.80

\_\_\_\_\_ T-DeCs + Free Super Solder Board £3.87

\_\_\_\_\_ U-DeCA + Free Super Solder Board £4.31

FULL POSTAL ADDRESS .....

**P.B.**  
P.B. Electronics (Scotland) Ltd.,  
57 High Street, Saffron Walden, Essex.  
Tel: Saffron Walden (0799) 22876.  
Practical Wireless, May 1976

## RETURN OF POST MAIL-ORDER SERVICE

**JUST RELEASED**

### R.C.S. 100 watt VALVE AMPLIFIER



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required, 5 speaker output. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier.  
Suitable carrying cabinet £14. Price **£85** carr. £2-50

### ANOTHER R.C.S. BARGAIN!

**ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM**  
This famous unit now available, 10 watts, 8 ohm.  
Price **£3-45** Post 40p



### 8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50 16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts. **£4-35**

10in round £4-95.

### TEAK VENEER HI-FI SPEAKER CABINETS

#### Fluted Wood Fronts

MODEL "A", 20 13 12in. For 12in. dia. or **£12-50** Post 10in. speaker. 95p

MODEL "B", 16 10 9in. For 13 8in. or **£6-95** Post 8in. speaker 75p

MODEL "C", 30 20 12in. Reflex cabinet will accept 1-12in. bass unit, 1 5in. mid range, 1 3in. tweeter. Teak finish. Grooved front **£21-50** Carr. £3

LOUDSPEAKER CABINET WADDING 18in. wide. 20p ft.

### GOODMANS CONE TWEETER

3in. diam. 18,000 C.P.S. 25 WATTS 8Ω **£3-60**

**BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.** Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt **£5-20** battery operated.



**STEREO VERSION OF ABOVE £6 85.**

**BARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. Mains Supply **£3-45**.

**THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.** Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V. LeadSet S.A.E. **£4-35** Post 40p



### WAFER HEATING ELEMENTS

**OFFERING 1001 USES** for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10" x 8" x 1/2". Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photographic and print drying equipment.  
Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Connector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails ideal for airing cupboards. Ideal for anti-frost device for the garage preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

**ONLY 40p EACH (FOUR FOR £1-50)**  
ALL POST PAID Discounts for quantity.

### BAKER MAJOR 12" £11-50



Post 60p  
30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£14-50**

Please state 3 or 8 or 15 ohms. Post 50p

### BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass resonance 55 cps.

**GROUP "25"**  
12in 30 watt  
3, 8 or 15 ohms. **£8-95** Post 50p

**GROUP "35"**  
12in 40 watt  
3, 8 or 15 ohms. **£10-50** Post 50p

**GROUP "50/12"**  
12in 80 watt professional model. 8 ohms or 15 ohms. **£14-50** Post 80p

**GROUP "50/15"**  
15in 75 watt  
8 or 15 ohms. **£19-50** post 90p

### MAJOR 50 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 2-way mixing. Output 8/15 ohm A.C. mains. Separate treble and bass controls. Guaranteed. Details S.A.E. **£49** Carr. £1-00



Latest 100 watt Model as illustrated **£68**

### 100 WATT DISCO AMPLIFIER CHASSIS

4 speaker outputs, vol., treble, bass controls **£52** or in cabinet £59.

### QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 1/2" thick wood cabinet. Size 18 1/2" x 18 1/2" x 9 1/2". Weight 23lb. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 8 1/2" Woofer £7-50. Carr. 85p. Rosewood Version £8-50. Carr. 85p. Baffle could be cut for larger speaker.

### P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watt each. As featured in December Practical Wireless. Price **£12-50** Cabinet extra £3.

### 8 inch PHILIPS LOUDSPEAKER

4 ohm, 4 watt, ceramic magnet **£1-95**

### MAINS TRANSFORMERS

6 VOLT 1 AMP. £1-00 3 AMP. £1-40  
12 VOLT 300 MA. £1-00 750 MA. £1-30  
16 VOLT 1 AMP. £1-00 2 AMP. £2-00

20 VOLT 1 AMP. £1-75 1 AMP. £2-00 3 AMP. £2-20

### E.M.I. TAPE MOTOR

4 pole, 240 v. Size 3 1/2" x 2 1/2". 1200 rpm. Spindle 1/2" in diameter. 120v version 75p. **£1-85** Post 45p



### E.M.I. GRAM MOTOR

120v or 240V a.c. 2,400 rpm 2-pole. Size 2 1/2" x 2 1/2". **£1-25** Post 35p

### BAKER DISCO SPEAKERS HIGH QUALITY - BRITISH MADE

### 2 x 12" CABINETS

for Disco or PA all fitted with carrying handles and corners. Black finish. Other cabinets in stock.

**50 WATT R.M.S. £43**

**70 WATT R.M.S. £46**

**100 WATT R.M.S. £55**



1 x 15" - 1 x 12" 100 WATT CABINET Size 36" x 24" x 15" **£63-50**. Ideal for Disco or PA work. High quality.

### SUPERB HI-FI


**12in 25 watts**  
A high quality loudspeaker. Its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.  
Bass Resonance 25cps  
Flux Density 16,500 gauss  
Useful response 20-17,000cps 8 or 15 ohms models.



**£17** Post 80p
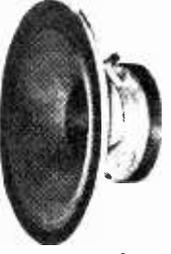
### AUDITORIUM

**12in. 35 watts**  
A full range reproducer for high power. Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discobosques.  
Bass Resonance 35cps  
Flux Density 15,000 gauss  
Useful response 20-14,000cps 8 or 15 ohms models.



**£15-50** Post 80p

### AUDITORIUM

**15in. 45 watts**  
A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discobosques. Electronic instruments and the home Hi-Fi.  
Bass Resonance 35cps  
Flux Density 15,000 gauss  
Useful response 20-14,000cps 8 or 15 ohms models.



**£19-50** Post 80p

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 68p

## RADIO COMPONENT SPECIALISTS 337 WHITEHORSE ROAD, CROYDON

Minimum post 30p. Components Lists 10p. Cash price includes VAT Access & Barclay cards welcome. Rail Selhurst. Tel. 01-684 1663

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30) **Practical Wireless, May 1976**

# B. BAMBER ELECTRONICS

Dept PW, 5 STATION ROAD, LITTLEPORT, CAMBS., CB6 1QE  
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

**BARGAIN OFFER**  
**MIXED COMPONENT PACKS**, containing resistors, capacitors, switches, pots, etc. All new (random sample bag revealed approx. 700 items), £2 per pack, while stocks last  
**TUNED COILS**, 2 section coils, around 1MHz, with a black smart tuning knob, which moves an internal core to vary the inductance, many uses, easily rewound, 3 for 50p  
**TWIN I.F. CANS**, approx. 1in x 1/2in x 1in high, around 3-5MHz, 2 separate transformers in 1 can, internally screened, 5 for 50p + 25% VAT

**SMALL MAINS SUPPRESSORS** (small chokes ideal for radio, Hi-Fi inputs, etc.) approx. 1/2in x 1/2in, 3 for 50p

**PERSEUS TUNER PANELS** (for FM Band 2 tuners) marked 88-108 MHz and Channels 0-70, clear numbers, rest blacked out, smart modern appearance, size approx. 5 1/2in x 1 1/2in, 2 for 35p

**Multiturn Pots**, 10 turn, 1/2in spindle (ex-equip) following values available, 2kOhm, 5kOhm 40kOhm, £1 each

**Lead suppressors** (10kOhm) for mobile plug leads, 4 for 50p

**1mA Meters**, 2 in square, plastic fronts (these have a paper scale stuck over the original marked 0-1mA which is easily peeled off and an internal 18K resistor which is easily removed), £1-75 each or 2 for £3

**R/S Midget** 3 pole 4 way, rotary switches 40p each

**SPECIAL OFFER**  
Miniature 50ohm Coax, high quality, PTFE insulation and blue PTFE cover, solid silver plated inner, and silver plated braid, approx 3m overall diameter (ideal for unit wiring of RF stages up to 23cm, etc.), 4 metres for 50p

**TRANSISTOR HEATSINKS**, to take 2 x TO18 transistors, screw in clamps, block size 1 x 1/2in, with holes for mounting, 3 for 50p

**HIGH QUALITY SPEAKERS**, 6 1/2in x 6in elliptical, only 2in deep, inverse magnet, 4 Ohms, rated up to 10W, £1-50 each, or 2 for £2-75 (qty. discount available) + 25% VAT.

**TV PLUGS AND SOCKETS**  
TV Plug (metal type), 5 for 50p  
TV Sockets (metal type), 4 for 50p  
TV Line Connectors (back-to-back sockets), 4 for 50p. Please add 25% VAT

**2-6pF**, 10mm circular ceramic trimmers (for VHF/UHF work) 3 pin mounting, 5 for 50p  
**TO3 transistor insulator sets**, 10 for 50p

**PC Board Withdrawal handles**, mixed coils 8 for 50p

**Solder**, 20 SWG, 60/40 alloy, approx 8 yds for 25p  
**HEAVY DUTY PLUGS AND SOCKETS** (III Into tin hole, pins enclosed, with covers for chassis mounting, or can be used for in-line connectors) Bargain pack of 3 plugs + 3 sockets + covers, 50p

**PROGRAMMERS** (magnetic devices). Contain 9 microswitches (suitable for mains operation) with 9 rotating cams, all individually adjustable, ideal for switching disco lights, displays, etc. or industrial machine programming. (Need only motion motor to drive cams, not supplied) 9 switch version £1-50, or 15 switch version £2

**HEAVY DUTY HEATSINK BLOCKS**, undrilled base area 2 1/2in x 2 1/2in, with 6 fins, total height 2 1/2in 50p each

**RV RELAYS**, Continental type, 2 pole change over, 35p

**RUBBER MAGNETS** 1in square, with mounting hole, 20 for 30p

**SPERRY 7-SEGMENT P.G.D. DISPLAYS**, digit height 0.3in red, with decimal points, 150V to 150V (nominal 180V) operation. These are high-volt industrial type and therefore brighter than normal displays. All brand new. AT THE BARGAIN PRICE OF 50p PER DIGIT. TYPE 332 (two digits in one mount) £1 each, TYPE 333 (three digits in one mount) £1-50. (Sorry, no single digit available.) Data Supplied

**BSX20** (VHF Osc/Mult), 3 for 50p  
**BC108** (metal can), 4 for 50p  
**PBC 106** (plastic BC108), 5 for 50p  
**OC200** Transistors, 6 for 50p  
**BFY51** Transistors, 4 for 60p  
**BCY72** Transistors, 4 for 50p  
**PNP** audio type TOS Transistors, 12 for 25p  
**BF152** (UHF amp/mixer), 3 for 50p  
**BA121** Varicap Diodes, 4 for 50p

1 1/2in polythene chassis mounting fuseholders, 6 for 30p  
Mullard Tubular ceramic trimmers, 1-18pF 6 for 50p

**I.C.**, a, some coded, 14 DIL type, untested 50p each, 20 for 25p.

PLEASE ADD 8% VAT UNLESS OTHERWISE STATED

**PLUGS AND SOCKETS**  
BNC Socket (Single-hole mounting type) Ex-equipment (special offer) 3 for 50p  
BNC Plugs (ex-equipment), 5 for £1

**N-Type Plug** 50 Ohm, 40p each, 3 for £1-50  
**N-Type Sockets** (4-hole chassis mounting, 50 Ohms in a small coax lead type), 50p each  
**PL250** Plugs (PTFE), brand new, packed with reducers, 85p or 5 for £3

**S202** Sockets (PTFE), brand new (4-hole fixing type), 30p each or 5 for £2-25  
**25-way ISEP** Plugs and Sockets, 40p set (1 plug + 1kt)

**Plugs and sockets** sold separately at 25p each  
**Plug and Round Free Sockets**, 3 pin, for mains input on test equipment, etc., 25p each  
**Bulgin Flat 2-pin Flex Connectors** non-reversible 40p each

**Mobile Converters**, 24V DC input 13.8V at approx 3-4A DC output, fully stabilised, £3-50 each (ideal for running 12V car radio from 24V lorry battery)

**Pkts** of 2BA Nuts (the self-locking ones with the nylon insert) 100 for 50p

We now stock **Spiralux Tools** for the electronic enthusiast. Screwdrivers, Nut Spanners, BA and Metric sizes, power rivet guns, etc. S A E for list

**I.F. Cans**, 1in square, suitable for rewind, 6 for 30p + 25% VAT

**Miniature earphones** with min jack plug, 2 for 50p + 25% VAT

**Dubilier Electrolytics**, 50uF, 450V, 2 for 50p  
**Dubilier Electrolytics**, 100uF, 275V, 2 for 50p  
**Plessey Electrolytics**, 470uF, 63V, 3 for 50p  
**TCC Electrolytics**, 1000uF, 30V, 3 for 50p  
**Plessey Electrolytics**, 1000uF, 160V, 60p each (3 for £1)

**Dubilier Electrolytics**, 5000uF, 35V, 30p each  
**Dubilier Electrolytics**, 5000uF, 50V, 60p each  
**Dubilier Electrolytics**, 5000uF, 70V, 85p each  
**ITT Electrolytics**, 6800uF, 25V, high grade, screw terminals, with mounting clips, 50p each  
**Plessey Electrolytics**, 10,000uF at 65V, 75p each

**Plessey Electrolytic Capacitors**, 0-0-4uF at 12-5KV DC, Screw terminals, £1-50 each  
**PLEASE ADD 25% VAT TO ALL CAPACITORS**

A LARGE RANGE OF CAPACITORS AVAILABLE AT BARGAIN PRICES, S.A.E. FOR LIST

**SPECIAL OFFER!**  
**MAINS TRANSFORMER**, TYPE 14.4, 14V at 4A £2-50

DIECAST BOXES (approx size in inches)	
4 3/4 x 3 3/4 x 1 1/2	85p
4 8/8 x 2 3/8 x 1 5/8	75p
4 8/8 x 2 3/8 x 1 1/2	85p
4 8/8 x 2 3/8 x 2	13 60p
4 8/8 x 2 3/8 x 3	11-45
4 8/8 x 2 3/8 x 4	11-55
4 8/8 x 2 3/8 x 5	12-25
4 8/8 x 2 3/8 x 6	12-85
4 8/8 x 2 3/8 x 7	12-85

Please add 8% VAT

**WELLER SOLDERING IRONS**  
**EXPERT**, Built-in spotlight illuminates work  
**Pistol grip** with fingertip trigger High efficiency copper soldering lip

**EXPERT SOLDER GUN**, £8-80 + VAT (54p)  
**EXPERT SOLDER GUN KIT** (spare bits case etc.), £9-80 + VAT (78p)

**SPARE BITS**, PAIR, 26p + VAT (2p)  
**MARKSMAN SOLDERING IRONS**  
SP15D 15W £2-32 + VAT (20p)  
SP25D 25W £2-52 + VAT (20p)

SP25DK 25W + bits, etc. kit £12-12 + VAT (25p)  
**MARKSMAN** STAND with spring for Marksmen Irons, £1-80 + VAT (14p)

**SPARE BITS**  
M78 for 15W, 42p + VAT (3p)  
M74 for 25W, 35p + VAT (3p)  
**TCP1 TEMPERATURE CONTROLLED IRON**  
Temperature controlled iron & PSU, £18-43 + VAT (£1-47)

**SPARE TIPS**  
Type CC single flat, Type K double flat fine tip  
Type CC each + VAT (8p)  
**ALL SPARES AVAILABLE**

**MULTICORE SOLDER**  
Size 5 Savbit 18 s.w.g. In alloy dispenser, 32p + VAT (3p)  
Size 12 SAVBIT Savbit 18s.w.g., 56p + VAT (4p)  
Size 12 SAVBIT 18s.w.g. on plastic reel £1-80 + VAT (19p)

**MINIATURE PLIERS** High quality Crescent made in USA, £4-35 + VAT (35p)  
**BIDE CUTTERS**, high quality 'Crescent', made in USA, £5-45 + VAT (44p)

Terms of Business: CASH WITH ORDER. MINIMUM ORDER £1. ALL PRICES INCLUDE POST & PACKING (UK ONLY). SAE WITH ALL ENQUIRIES Please. PLEASE ADD VAT AS SHOWN. ALL GOODS IN STOCK DESPATCHED BY RETURN

## PRACTICAL WIRELESS T.V. SOUND TUNER

IF Sub-Assembly (G8) £6-80. P & P 55p.  
Mullard ELC1043 Varicap UHF Tuner £4-20. P & P 30p.  
3-way Station Control Unit £1-20. P & P 25p.  
6-way Station Control Unit (Special Offer) £1-00.  
Resistors, Caps, Semiconds etc. £5-22. P & P 55p.  
Printed Circuit Board £1-00. P & P 25p.

Add 25% VAT to price of goods. P & P all items 65p.

Callers welcome at shop premises.

### MANOR SUPPLIES

172 WEST END LANE, LONDON NW6  
(Near W. Hampstead Tube Stn.) Tel. 01-794 8751

PLEASE MENTION  
PRACTICAL WIRELESS  
WHEN REPLYING TO  
ADVERTISEMENTS

## J. BIRKETT

### Radio Component Suppliers

25 The Strait, Lincoln, LN2 1JF  
Telephone: 20767

3 TO 5 VOLT SILICON SOLAR CELLS @ 35p each.  
250 VOLT GREEN MAINS NEONS @ 25p each.  
**SPECIAL OFFER 20 SILICON NPN PHOTO TRANSISTORS**  
Untested @ £1.  
50 TRANSISTOR ELECTROLYTIC CAPACITORS @ 57p.  
500 + 500 + 25 + 25p TUNING CAPACITORS with S.M. Drive @ 38p.  
VHF DUAL GATE MOS FET like 40673 @ 33p or 4 for £1-10.  
LARGE PACKET OF T03, TIP SERIES MICA WASHERS @ 50p.  
20 ITT BRANDED 250mV ZENERS Assorted @ 75p.  
20 STC SILICON 750mA DIODES Assorted PIV's @ 50p.  
100 SUB-MINIATURE CERAMIC PLATE CAPACITORS Assorted from 3-3 to .01uF at 57p.  
VHF TUNING VARACTOR DIODES Untested 20 for 45p.  
POSTAGE STAMP TRIMMERS 10pf, 30pf, 50pf, 150pf, 750pf, 1000pf. All at 6p each.  
60 ASSORTED WIRE WOUND RESISTORS 1 to 10 Watts @ 57p.  
500yd Reel of 14 Strand .0048 PVC CABLE @ £3 per reel.  
PLASTIC TRIACS 400 PIV 6 Amp @ 60p.  
PLASTIC SCR'S 400 PIV 6 Amp @ 40p.  
LARGE PACK OF POLYESTER CAPACITORS approx. 300 to 500 Pieces @ £1.  
TAPE RECORDER DIGITAL MECHANICAL COUNTER @ 20p.  
200 ASSORTED TUBULAR CERAMIC CAPACITORS @ 57p.  
400 PIV 10 Amp STUD MOUNTING TRIACS @ 60p.  
35 ASSORTED PRE-SETS AND SLIDERS @ 57p.  
STACKPOLE 5 Amp 240 Volt ROCKER SWITCHES @ 18p each, 4 for 60p.  
TAG ENDED ELECTROLYTICS 1000uF 64v.w., 2 1/2" x 1" @ 25p, 3300uF 64v.w., size 2 1/2" x 1 1/2" @ 30p, 4700uF 40v.w., size 2 1/2" x 1 1/2" @ 45p.  
PLASTIC POWER TRANSISTORS 30 watt NPN @ 22p, PNP @ 25p or 35p pair.  
BYX 95 1250 PIV 1 Amp SILICON DIODES @ 12 for £1-08.  
TRANSISTOR RF CHOKES 2-5MH @ 12p, 10MH Tapped @ 5 MH @ 15p.  
BD 187 4 Amp NPN POWER TRANSISTORS 40p each or 4 for £1-35.  
50 ASSORTED BRANDED TRANSISTORS NPN and PNP some with house numbers and some data at 95p.  
100 VOLT NPN TRANSISTORS BF 177 120 MHz 600mW @ 6 for 57p.  
ASSORTED SILVER MICA CAPACITORS 100 for 57p.  
250pf SOLID DIELECTRIC VARIABLE CAPACITORS @ 33p.  
ITT PNT2R METALISED FILM CAPACITORS 1.5uf 100v.w. @ 6 for 30p.  
150uf 10v.w. REVERSIBLE ELECTROLYTIC CAPACITOR size 1 1/2" x 1 1/2" @ 6 for 30p.  
25 ASSORTED TRANSISTOR I.F. TRANSFORMERS @ 57p.  
All items VAT PAID. Please add 20p post and packing for orders under £2. Over £2 Free.

# Sparkrite mk2

## Capacitive discharge electronic ignition

VOTED BEST OF 8 SYSTEMS TESTED BY 'POPULAR MOTORING' MAGAZINE



- \* Smoother running
- \* Instant all-weather starting
- \* Continual peak performance
- \* Longer coil/battery/plug life
- \* Improved acceleration/top speeds
- \* Up to 20% better fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions

### OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

**CALLERS WELCOME.** For Crypton tuning and fitting service - 'phone (0922) 33008

PRICES INCLUDE VAT, POST AND PACKING.

Improve performance & economy NOW

**POST TODAY!**

**Quick installation**  
No engine modification required

Electronics Design Associates, Dept., PW/5  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name .....

Address .....

QUANTITY REQD.	
Mk. 2 DIY Ass. Kit @ £11.80	
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's for £

Cheque No. ....

Send SAE if brochure only required.

## ENGINEERS

# FREE



YOURSELF FOR A

## BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow GUIDE TO SUCCESS should be read by every ambitious engineer. Send for this helpful 44-page free book NOW! No obligation, nobody will call on you. It could be the best thing you ever did.

### CHOOSE A BRAND NEW FUTURE HERE



CUT OUT THIS COUPON  
Tick or state subject of interest.  
Post to address below.

- |  |  |   |
|--|--|---|
| <input type="checkbox"/> ELECTRICAL & ELECTRONICS                    | <input type="checkbox"/> Radio, Servicing & Repairs              | <input type="checkbox"/> Painting & Decorating              |
| <input type="checkbox"/> Practical Radio & Electronics (with KIT)    | <input type="checkbox"/> Radio Amateur's Exam.                   | <input type="checkbox"/> MECHANICAL                         |
| <input type="checkbox"/> Electronic Engineering Certificate          | <input type="checkbox"/> AUTO & AERO                             | <input type="checkbox"/> A.M.S.E. (Mech.)                   |
| <input type="checkbox"/> General Elect. Eng. Certificate             | <input type="checkbox"/> Motor Mechanics                         | <input type="checkbox"/> General Mech. Eng.                 |
| <input type="checkbox"/> C. & G. Elect. Installations                | <input type="checkbox"/> C. & G. Motor V. Mechanics              | <input type="checkbox"/> Inst. Engineers & Technicians      |
| <input type="checkbox"/> Elect. Install. & Work                      | <input type="checkbox"/> General Auto Engineering                | <input type="checkbox"/> Maintenance Engineering            |
| <input type="checkbox"/> C. & G. Elect. Technicians                  | <input type="checkbox"/> A.M.I.M.I.                              | <input type="checkbox"/> Welding                            |
| <input type="checkbox"/> RADIO & TELECOM. COMMUNICATIONS             | <input type="checkbox"/> Air Registration Board Certs.           | <input type="checkbox"/> MANAGEMENT & PRODUCTION            |
| <input type="checkbox"/> Colour TV Servicing                         | <input type="checkbox"/> M.A.A./I.M.I. Dip.                      | <input type="checkbox"/> Computer Programming               |
| <input type="checkbox"/> C. & G. Telecoms. Technician's Cert.        | <input type="checkbox"/> CONSTRUCTIONAL                          | <input type="checkbox"/> Inst. of Cost & Managements Accts. |
| <input type="checkbox"/> C. & G. Radio, TV & Electronics Mech. Cert. | <input type="checkbox"/> Heating, Ventilating & Air Conditioning | <input type="checkbox"/> DRAUGHTSMANSHIP & DESIGN           |
| <input type="checkbox"/> Radio & TV Engineering Course               | <input type="checkbox"/> Architectural Draughtsmanship & Design  | <input type="checkbox"/> General Draughtsmanship            |
|  | <input type="checkbox"/> L.I.O.B.                                | <input type="checkbox"/> A.M.I.E.D.                         |
|  | <input type="checkbox"/> Carpentry & Joinery                     | <input type="checkbox"/> Electrical Draughtsmanship         |
|  | <input type="checkbox"/> Plumbing Technology                     |   |
|  | <input type="checkbox"/> General Building                        |   |



**G.C.E.**  
—58 'O' & 'A' Level Subjects  
—over 10,000 Group Passes!

## Aldermaston College

Dept. TPW 17, Reading RG7 4PF.

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5ET. Tel. 628 2721.

NAME (Block Capitals) .....

ADDRESS .....

Postcode.....

Other subjects of interest..... Age.....

Accredited by C.A.C.C. Member of A.B.C.C.

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# barclay

ELECTRONICS

TECHNOLOGICAL  
PRECISION PRODUCTS

## The NEWEST from NOVUS—the 4525

### PROGRAMMABLE SCIENTIST

The NEW 100 Step Programmable Scientific Calculator. Saves time and effort with complicated problems.

### THIS IS TRULY AN UNBEATABLE MACHINE!

8-digit—2 exponents • Common and natural logs and anti-log  
• Sine, Cos, Tan, and their inverse • Reciprocals •  $Y^X$  •  $X^2$   
• 4 Roll stack •  $\pi$  • Register exchange • Sign change  
• Memory • Memory +  $x^2$  • Degree radian conversion  
• Rechargeable (Recharger included in price) • Vynyl case (full instruction manual).



also the NOVUS 4520. Exactly as above but non-programmable **£21.15** + 8% V.A.T. **£42.69** + 8% V.A.T.

or the 4515 MATHEMATICIAN 8-digit 100 Step programmable, 3 level stack, recharger, case and instruction manual **£35.10** + 8% V.A.T.  
And the 4510 As the Mathematician but non-programmable. **£13.49** + 8% V.A.T.  
ALL WITH REVERSE POLISH LOGIC Novus Mains Ad'ctr for the 4510 **£2.90**

## SCIENTIFIC

- ALGEBRAIC**  
CBM SR4148 12digit 2exp. in ch. **£30.22**  
CBM 1800D 87224 **£24.50**  
**ROCKWELL 61R** 8-digit conversion including charger **£21.95**  
**ROCKWELL 63R** 8-digit + 2exp. inc. ch. **£31.50**  
**SINCLAIR OXFORD 300** 5-digit + 2exp. **£16.69**  
CBM 7919D 5-digit + 2exp. or 8-digit **£12.50**  
**REVERSE POLISH LOGIC**  
**SINCLAIR SCIENTIFIC** 5-digit + 2exp. **£13.50**  
**NOVUS 6010** 8-digit conversion **£18.25**  
**NOVUS 6020** 8-digit Financial **£18.25**  
**NOVUS 6025** 8-digit Financial 100 step programmable **£47.95**  
**NOVUS 6030** 8-digit statistical **£18.25**  
**NOVUS 6035** 8-digit statistical 100 step programmable **£47.95**  
ADD 8% V.A.T. + 55p. p.&p.

## The Superb CASIO fx-20



8-digit mantissa or 6-digit mantissa and 2-digit exponents.  $10^{99}$  to  $10^{-29}$  Algebraic logic. Bright Green display. Full floating point with underflow. Overflow and negative indicators. Sin, Cos, Tan, Inverse Sin, Inverse Cos, Inverse Tan. Log x and  $\ln x$   $e^x$ ,  $x^y$ ,  $\sqrt{\quad}$ , Reciprocal. Degree Radian conversion. Memory. + 8% V.A.T. Exponent key.

**ONLY £15.69** + 8% V.A.T.

**ALSO THE LARGER fx-15**  
Includes in addition a larger display,  $x^2$  key,  $\pi$  key. \* **£19.40** + 8% V.A.T.

**AND THE de LUXE fx-101**  
with similar functions to fx-15 but 8-digits + 2 \* **£24.03** + 8% V.A.T. to  $10^{-99}$ .

**ALL HAVE SEXAGECIMAL DECIMAL CONVERSION**

**OPTIONAL CASIO MAINS ADAPTOR £2.95.**

## SPECIAL OFFERS

### ONE OF THE MOST ADVANCED CALCULATORS Texas SR50A



The SR-50 is the full function portable slide rule calculator. Complex scientific calculations are solved as easily as simple arithmetic problems. The SR-50 features an algebraic keyboard with single function keys for easy problem solving.

**£35.00** + 8% V.A.T.  
• 10 digits + 2 exponents • Deg/ Rad Switch •  $\pi$  key •  $\pi^2$  Square Key •  $\sqrt{x}$  Square Root Key •  $1/x$  Reciprocal Key •  $x!$  Factorial Key • arc inverse Trigonometric Key • EE Enter Exponent Key • +/- Change Sign Key • CE Clear Entry Key • C Clear Key • hyp Hyperbolic Function Key • D/R Angle Change Key • log Common Logarithm Key •  $\ln x$  Natural Logarithm Key •  $e^x$   $e^x$  to the xth Power Key •  $y^x$  y to the xth Power Key •  $x^y$  y The xth Root of y Key • x/y Exchange Key • STO Store Key • RCL Recall Key • = Sum and Store Key

### TEXAS SR51A

All the functions of the SR-50A plus many more are features of this powerful scientific calculator. • Additional functions include linear regression, mean, variance, standard deviation, permutation, random number generator and 20 basic conversions (and their Inverses). • Three independent user accessible memories. • Fixed or floating decimal option.

**£46.25** + 8% V.A.T.

• Both calculators complete with rechargeable batteries, adapter/charger, carry case and Owners Manual.

### VATMAN SCIENTIFIC by DECIMO NEW GREEN DISPLAY



8-digit and 2 exponents. Single function colour-coded keyboard with click-keys. Bright Green display. CE key, C key,  $Y^X$ ,  $E^x$ ,  $\ln$ ,  $\log$ ,  $10^x$ , Sin, Tan, Cos, Inverse Sin, Cos, Tan, D.M.S. key to delete each 1 digit of last entry. Key, key,  $X^2$  key. Full memory. Sign change key. Exponent key.  $10^{99}$  to  $10^{-99}$ . Attractive soft Vynyl carrying case. Maximum battery life 20 hrs.

**£26.90** + 8% V.A.T. Mains Adaptor **£3.**



NEW!

### DECIMO DIGITAL CLOCK/RADIO AS ON T.V.

Recommended Price £50  
OUR PRICE **£35.50** incl. VAT plus  $\text{£}1 \text{ p} \& \text{ p}$

This is the most unique clock/radio in the country today having a soft  $1\frac{1}{2}$ " high orange-glow digital readout which is completely silent and non-pulsating. In a beautiful teak style cabinet with up-to-date VHF/MW radio. You can awake to soft music or alarm—and if you want up to 10 minutes more—just press the 'Drowsie' button. (Automatic 80 minute 'sleep' button in case you drop off while the radio's on!

### THE NEW SINCLAIR SCIENTIFIC

Only  $1\frac{1}{2} \times 2 \times \frac{1}{2}$ " yet has—8 digits or 5 + 2 exponent. Using the new chip, it has full algebraic logic and many more functions: Algebraic logic constant on all four arithmetic functions—

FUNCTIONS: C & CE key • sin • cos • tan • arcsin • arccos • arctan • reciprocal key • E to the x key • natural log • antilog •  $\pi$  key • memory + • memory — • memory exchange and memory cancel • EE exponent • change notation • PLUS a degree radian

**ONLY £13.50** + 8% V.A.T.



## And NOW the watch with 10 FUNCTIONS! The PULSTRONIC



Hours	12:00	Date	18 02
Mins	12:30	Date + Mnth	18 02
Secs	09	Day of week	WE

Self-adjusting 4 yr calendar  
Auto-hold & fade-out  
P.M. Setting indicator

This is the only watch we know that gives the date and month in correct order e.g. 29 : 02, 29th Feb. Single button control, water/shock resistant anti magnetic, silent. Accurate to within a few seconds a year. Hrs, Mins, Secs, Date + Mth, Day of week (WE). Self-adjusting calendar. Auto hold & fade-out. A.M. P.M. setting indicator. In Satin finish stainless-steel with polished bevelled edges. AND matching bracelet. 10 FUNCTIONS. 1 Yr Full Guarantee

**£37.40** plus  $\text{£}1.00 \text{ p.} \& \text{ p.}$

## ORDER FORM

To: BARCLAY ELECTRONICS Dept 6PW  
1115, FINCHLEY ROAD, TEMPLE FORTUNE, LONDON N.W. 11.

All goods fully guaranteed. If not satisfied—money refunded if returned undamaged within 7 days

PHONE CALLS AND PERSONAL CALLERS, WELCOME MON-THURS BETWEEN 2 and 5 pm. SUNDAYS 10 am - 1 pm. 01-458 4755

Please send me .....

with/without optional mains adaptor. I enclose cheque/money order

total value  $\text{£} \dots\dots\dots$  including 55p to cover packing.

NAME .....

ADDRESS .....

barclay  
ELECTRONICS

## SPECIAL OFFER

### IN4148 SWITCHING DIODES

10 For 30p 50 for £1·25  
100 For £1·50 1000 for £10

## LIMITED OFFER

BC107 — BC108 — BC109 9p each  
100 for £7·50

## POPULAR BRANDED TRANSISTORS

BC147 — BC148 — BC149 — BC157 — BC158 — BC159 — BF194 — BF195 — BF196 — BF197  
8p each. 100 for £6·50. Type numbers may be mixed for quantity discount.

### 8 PIN DIL 741's NEW LOW PRICES

1 + 25p 10 + 22p 25 + 20p 100 + 18p

1 Amp diodes IN4001 IN4002 IN4003 4p each 30 for £1  
IN4004 IN4005 IN4006 6p each 30 for £1·50

ZENER DIODES BZY88 400 MW 3·3V to 33 VOLTS 7p each 100 for £6·00

MULLARD FERRITE CORES LA3 100 to 500 kHz 54p  
LA5 30 to 100 kHz 81p, LA7 L 10kHz 81p  
LA13 for W.W. OSCILLOSCOPE £1·50

ASSORTED RESISTORS CARBON AND CARBON FILM TYPES ¼ WATT to 3 WATTS (25 DIFFERENT VALUES)  
300 for only £1·50

### WIRE-ENDED GLASS NEONS 20 FOR £1


PLESSEY/T.C.C. CAPACITORS WIRE-ENDED ·02/300V, ·02/350V, ·03/350V, ·05/350V, ·25/250V. 100 OF ANY VALUE  
£2·00 OR 100 OF YOUR OWN CHOICE.

PLEASE NOTE THAT ALL PRICES INCLUDE POSTAGE AND V.A.T. AT 8 OR 25% AS APPROPRIATE

## MAIL ORDER ONLY XEROZA RADIO

1, EAST STREET, BISHOPS TAWTON, BARNSTAPLE, DEVON

## INTER-LOCKING PLASTIC STORAGE DRAWERS

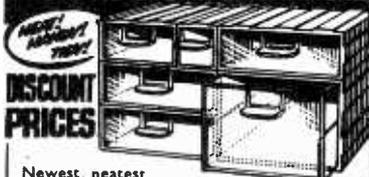

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. ID and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

AS SUPPLIED TO POST OFFICE,  
INDUSTRY & GOVERNMENT DEPTS.

**SINGLE UNITS (1D)** (5ins × 2½ins × 2½ins) £2·40 DOZEN.

**DOUBLE UNITS (2D)** (5ins × 4½ins × 2½ins) £4·20 DOZEN.

**TREBLE (3D)** £4·20 for 8.

**DOUBLE TREBLE 2** drawers, in one outer case (6D2), £5·90 for 8.

**EXTRA LARGE SIZE (6D1)** £5·40 for 8.

### PLUS QUANTITY DISCOUNTS!

Orders over £20, less 5%.  
Orders over £60, less 7½%.

**PACKING/POSTAGE/CARRIAGE:** Add 75p to all orders under £10. Orders £10 and over, please add 10% carriage.

**QUOTATIONS FOR LARGER QUANTITIES** Please add 8% V.A.T. to total remittance

## FLAIRLINE SUPPLIES

(Dept PW5)

124 Cricklewood Broadway, London NW2  
Tel. 01-450 4844

## NEW CLOCK CHIPS AND CLOCKS

In addition to National, Mostek and Caltex clock chips, we are now selling a range of General Instrument chips.

AY-5-1202. 12 or 24 hour. 50 or 60 Hz. Interfaces directly with Futaba 5LT01 £4·76

AY-5-1230. Similar to 1202. ON/OFF programmable alarm. In 7 segment mode can drive 5LT01, or BCD to drive logic or TV display chips. £5·25

**MISTRAL CLOCK KIT**  
Uses AY-5-1202 + Futaba 5LT01. Complete kit including case. £11·58

**CHEVIOT ALARM CLOCK**  
24 hour 4 digit alarm clock, 0·5in. green display, tilt to snooze. Finished clock—not kit. £21·85

5LT01. Green Phosphor Diode. Futaba 5LT01 display has 4 digits with AM/PM. Seconds indication on colon. Requires multiplexed input. £5·80

5LT02. Similar to 5LT01. Requires non-multiplexed input, e.g. MM5316. £5·80

5LT03. 5 digit multiplexed for use as counter or DVM module. £5·80

**TERMS:** CWO, Access, Barclaycard (simply quote your number and sign). Credit facilities to Accredited account holders.

# BYWOOD

68 Ebbwens Road, VAT: All prices  
Hemel Hempstead, exclude VAT (8%)  
Herts HP3 9QRA P/P: 15p  
TEL: 0442 62757

## INTRODUCING THE



## MINISONIC 2 Electronic Music Synthesiser

As Demonstrated "live" at the Audio Fair 1975 Based on the original P.E. Minisonic, the Mk. 2 is a three octave keyboard instrument which sets new standards of performance and flexibility. Designed for construction by the amateur electronics enthusiast or do-it-yourself musician, the Minisonic 2 has a truly "professional" sound which has to be heard to be believed.

- ★ Finished case plus panels
- ★ Two VCOs (3Hz-50kHz)
- ★ VCO cross modulation
- ★ Variable Portamento
- ★ VCO sync. facility
- ★ Fixed Variable Span
- ★ Envelope indicators
- ★ Pan pots at output
- ★ Push Button Patching
- ★ Headphone amplifiers
- ★ Low Current drain
- ★ Mains/Batt. Operation

A complete kit of parts is available to build this fabulous instrument or to convert your Mk. 1 Minisonic.

Ready made instruments are also available, complete with guarantee plus instruction booklet.

Want to know more? For full details send a 9 x 4in S.A.E.

**EATON AUDIO** Dep PW PD Box 3  
ST. NEOTS CAMBS.  
PE19 3JB



**DRILL CONTROLLER**  
Electronically changes speed from approximately 10 revs. to maximum. Pull power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £2-50 plus 45p post and VAT. Made up model also available.

**PERMEABILITY TUNERS**

M.W. two stage ideal for use with ZN414 or similar circuit. Price 15p each + post and VAT 15p.

**MAINS TRANSISTOR PACK**

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: FP1, FP3, PP4, PP6, PP7, PP9 and others. Kit comprises: main transformer rectifier, smoothing and load resistor, condensers and instructions. Real snip at only £1-50. VAT + postage 60p.

**NUMICATOR TUBES**  
For digital instruments, counters, timers, clocks, etc. Hi-vac XNII Price £1-25 each, 20p Post and VAT.

**DC HIGH CURRENT PANEL METERS**

3 1/2" wound wide angle 240 movement meters, flush mounting fitted with external shunts, made by Crompton Parkinson, brand new, still in maker's cartons. These are a real bargain at £5-50 each. Reasonable quantities available in the following ranges 0-15 amps, 0-20 amps, 0-30 amps, 0-40 amps, Post and VAT 80p each.

**TAPE DECK**  
In metal case with carrying handle, heavy flywheel and capstan drive. Tape speed 3 1/2". Main operated on metal platform with tape head and guide. Not new but guaranteed good working order. Price £1-50 plus VAT and Postage £1-50.

**SOUND TO LIGHT UNIT**

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450w). Unit in box all ready to work. £7-95 plus 95 VAT and postage.

**SPIT MOTOR**

200-250V Induction motor, driving a Carter gearbox with a 1 1/2" output drive shaft running at 5 revs p.m. for roasting chickens, also for driving models—windmills, coloured disc lighting effects, etc. £2-50 plus 50p post and VAT.

**OVEN THERMOSTAT**

Made by the famous Diamond H Company, this has a sensor joined by a capillary to a variable control and when fitted with a knob is ideal for many ovens or Processes, 50p each + post and VAT 15p

**MAINS TRANSFORMERS**

All standard 230-250 volt primaries	£	p
1v .....	1 amp (special)	1-78
2-4v .....	5 amp	85
6-3v .....	2 amp	1-25
6-3v .....	3 amp	1-75
9v .....	1 amp	-95
9v .....	3-5 amp	2-50
12v .....	1 1/2 amp	1-50
12v .....	1 amp	1-00
6-3v-0-8-5v .....	1 amp	1-50
18v .....	1 amp	1-50
24v .....	2 amp	2-25
24v .....	3 amp	3-50
12-0-12v .....	50mA	1-30
6-0-6v .....	50mA	1-20
8-0-8v .....	1 amp	1-50
25-0-25v .....	2 amp	3-50
25v .....	1 1/2 amp	1-95
50v .....	2 amp & 6-3v	4-50
60v .....	5 amp & 6v	7-50
30v .....	8 amp	4-50
30v .....	37 amp	22-00
80v tapped 70v & 70v .....	4 amp	5-50
330v-60mA & 6-3v .....	1-5 amp	1-75
275-0-275v at 90mA & 60-4v .....	3 amp	3-25
EHT Transformer 5000v		
23mA .....	(intermittent)	5-60
Charger Transformers		
6v and 12v .....	2 amp	1-50
6v and 12v .....	3 amp	3-25
6v and 12v .....	5 amp	3-50

Add 90p per £1 to cover postage and VAT

**HONEYWELL PROGRAMMER**

This is a drum timing device, the drum being calibrated to equal divisions for switch-setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 3 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips, thus 16 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control. Boiler firing. Dispensing and Vending machines. Display lighting animated and signs. Signalling, etc. Price from makers probably over £20 each. Special snip price £9-95. £1-00 Post and VAT. Don't miss this terrific bargain.



**BREAK-DOWN UNIT**

Contains hundreds of useful parts some of which are as follows—66 silicon diodes equivalent OA91, 68 resistors, mostly 1 watt 5% covering a wide range of values 4 x .1 mfd 400 mfd condensers, 15 x .01 mfd 100v condensers, 2 EF chokes 8 x B9 valve holders, 1 x 4H choke, 1 x 115v transformer, 1 boxed unit containing 4 delay lines also tag panels, trimmer condensers, suppressors, etc., on a useful chassis sized approx 9" x 5" x 7". Only 75p (the 66 diodes would cost at least 10 times this amount). This is a snip not to be missed. Post and VAT 75p.

**HORSTMANN 24-HOUR TIME SWITCH**

With 6 position programmer. When fitted to hot water systems this could programme as follows:


Programme	Hot Water	Central Heating
1	Off	Off
2	Twice Daily	Off
3	All Day	Off
4	Twice Daily	Twice Daily
5	All Day	All Day
6	Continuously	Continuously

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated. Size 3in x 3in x 2in deep. Price £4-25. 80p Post and VAT. As illustrated but less case.



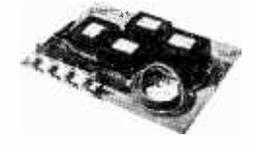**MULLARD UNILEX**

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone in easy-to-assemble modular form and complete with a pair of Goodmans speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £15-50 including VAT and postage.



**THIS MONTH'S SNIP**

**HIGH POWERED TRANSFORMER**

Rated at 250 Watts, upright mounting varnish impregnated. Its primary is for 230/240 volts 50 cycles, it has four secondaries each 10v very high current windings. Just a few of the circuits it can power are: 10-0-10v at up to 12 amps; 20-0-20v at up to 6 amps; single 10v at 25 amps; single 20v at 12 1/2 amps; single 30v at 9 amps; single 40v at 6-5 amps. This can be used for charging or for amplifiers, etc., there being an earth screen between primary and secondaries. A transformer like this to-day would cost at least £15 from the makers; however, we are making a special offer at £3-50 + 28p, post £1 + 8p each. Grab some while you can, our stock may not last long.

**TWIN OUTPUT POWER PACKS**

These have two separately B.C. smoothed outputs so can operate two battery radios on a stereo amp without cross modulation (they will of course operate one radio-tape-cassette-calculator in fact any battery appliance and will save their cost in a few months). Specs: Full wave rectified double insulated mains transformer—total enclosed in a hard P.V.C. case—three core mains lead—terminal output—when ordering please state output voltage 41v, 6v, 7 1/2v, 9v, 12v or 24v. Price £3-95. Post and VAT included.

**ONLY £1-50 FOR SEVEN ELECTRIC MOTORS**

7 powerful batt. motors as used in racing cars and power models. Output and toys vary for use in hundreds of projects—Tools, toys, models, etc. All brand new reversible and for 1 1/2-12v batts. Wiring diag. inc. VAT P Post 40p. FREE plan for min. power station.



**BLACK LIGHT**

As used in discotheques and for stage effects etc. Virtually no white light appears until the rays impinge on luminous paint or white shirts, etc. We offer 9" tubes complete with starter, choke, lamp holders and starter-holder. Price £2-75 + 30p post. Tubes only £2. Post & VAT 50p. 175 Watt model £8-50 + 92p Post and VAT.

**MULTIPLE CONTACT PANEL**

Size approx. 4 1/2 x 2 1/2" have 200 contacts each across referenced for easy identification. Contacts are spring loaded and gold "pip". Ideal for the circuit bread-boarding (resistors, etc., plug straight in) or for working out printed circuits, for electronic novelties, puzzles, combination locks, etc., ex-unused computer panels, price only £2 + 16p. IE. only 1p per contact, probably less than the value of the gold pip. Post + 11p.

Monthlv list available free; send long stamped envelope.

**TERMS:** Where order is under 25 please add 30p surcharge to offset packing expenses.

**J. BULL (ELECTRICAL) LTD.**

(Dept. P.W.), 103 TAMWORTH ROAD, CROYDON CR0 1XX.

O.C.P. 70 photo transistor by Mullard, very popular for circuits such as infra-red burglar alarms, smoke detectors, etc. A big buy enables us to offer at the very favourable price of 85p each + 2p, or 5 for £1 + 8p.

Microwitch bargain, made by Fye, Honeywell, Burgess and similar first class makers originally for the Post Office, in fact they have been fitted to Post Office Equipment which was never put into use. They are a changeover microswitch with 10 amp contacts offered at the very low price of 20 for £1 + 8p. Post 40p + 8p.

Junction boxes free. We are coming to the time of the year when additional wiring and home alterations are usually carried out and as a special offer to all having our cable to install in immersion heaters, ring mains, etc., we are giving free this month six junction boxes with every 100 yard coil of 7/029 (4mm twin and earth cable). Our price for this cable, which is only approximately one half of the regular price anyway, is 88 + 54p. Carriage £2-50 + 20p—don't miss this bargain.

Super slick microphones, Japanese made, extremely good quality and performance. Impedance 50 Kohms. The microphone is intended for hand holding but stands as available if required. Price £4-50 + £1-15p. Post 40p + 10p.

Tuner Cassette as described in March "Practical Wireless". Please note we can supply the ferrite slab and the Z.N. 414 IC. Price for these two items £2-25 including post and VAT. Copy of the circuit supplied on request.

Burglar Alarms. More and more burglars seem to be shirking on the properties of people who cannot be bothered to install burglar alarms. We can offer the intruder alarm as described in "Everyday Electronics" September issue. This is a good circuit and not too expensive. Price is £3-83 + 81p. Post 40p + 10p.

Thermally protected motor. American made 1" stack. This revs. at 2400 RPM, suitable for fan or similar application. Special feature is the trip which cuts off the mains should the motor over-heat. Price £1-40 + 13p. Post 25p + 2p.

Amplifier in case with speaker, marketed by Brush Relay. This is in good quality cabinet with back and elliptical speaker. The amplifier is the Newmarket PC 4 module, together with volume control, size 9 1/2" x 6" x 3 1/2" deep, the amplifier can be powered by an internal 9v battery or from external mains source. Very useful amplifier for around the home or in the workshop for troubleshooting, or for testing out a quick lash up. Limited quantity of these, offered at bargain prices of £4 + £1. Post 40p + 10p.

Task veneered double cabinet. We believe that this was made from one of the Leak systems. It is 28" x 4 1/2" high x 8" deep made of thick board with sound/vent holes and should be ideal to house amplifier and tuner, or amplifier and one speaker. Very high quality cabinet which would cost £4 or 25 to make today. Price £3 + 50p + 80p + 30p.

Disco Dimmers made by Ultra Electronics, this is a variable controller which can be fitted behind a panel or into a standard switch box and it will control by 1250 watts along your similar non-inductive load. Very special price only £3 + 24p + 30p + 3p.

Black Light Lamp 175 watts—230/240v pear-shaped back outer glass which obscures all visible radiation but emits long wave ultra violet (black light). This lamp provides a convenient way of fluorescing a discotheque, club, dance hall, party do, and being adirect plug in replacement of a tungsten lamp it is very convenient for temporary use anywhere. Price £6-50+50p. Post 50p + 4p.

Some more Relay bargains. Miniature plug-in type with persep dust cover 700 ohm 12v DC working. 4 sets of gold-plated changeover contacts 1/2 amp. Normally an expensive relay. Our price £1 + 8p.

Mains Relays 230/240v. AC operated with 10 amp changeover contacts, open type, one screw fixing 3 sets changeover contacts £1 + 8p each. Three Changeover persep covered plug-in types £1-25 + 10p each. 800 ohm 12v AC. 2p each. Available with following coil voltages 12v AC, 50v AC 230/240 AC. Also still available the most versatile type 600 relay which, having a double wound coil, is suitable for working off 6, 12 or 24v. DC or mains through series resistor. This has multiple contacts and the price is 40p + 3p each.

Sound Transducer balanced armature type, 600 ohm imp. in capsule, size diameter 1 1/2" by 1/2" thick. Useful in digital equipment or for audio monitoring, or as a microphone or speaker, good quantities available. Board price 50p + 4p less our usual quality discounts.

Venner Clock Replacements. 24 hour clock motor with threaded driving shaft. Standard replacements in many Venner time switches. Price £1-50 + 12p. Post 30p + 3p.

Stereo Pre amplifier. Mullard reference LP1189/2. This is a dual input hi-fidelity amp, has a frequency response of 20 Hz to 50 KHZ. Its sensitivity 150mV at input 1 or 320mV at input 2. The bass and treble control ranges are plus or minus 14dB, distortion better than 2%. All components are mounted on printed circuit wiring board, overall size of which is approx. 3" square. Connections are brought out to 22 tags which provide for high and low impedance inputs, stereo outputs, bass and treble lifts, volume and balance controls. We will supply complete with diagram of conditions, price £1-50 + 37p. Post 30p + 7p.

Special Instrument offer is a Russian made Galvo, very sensitive precision instrument, full scale deflection 7-0-7uA. This is a bench mounting instrument of extremely high sensitivity (3uA per division) size approx 6 1/2" x 9 1/2" x 2". Price £3-50 each + 75p. Post 50p + 4p.

Photo Multiplier Tubes. U.S. made, R.C.A. type No. 4555. These tubes have a gain of a million or more—regular price around £30 each, our price £6-75 + 54p each. Brand new in original maker's cartons.

# VAT INCLUSIVE PRICES

Fully branded devices from  
RCA, TEXAS, MOTOROLA,  
MULLARD, etc.

Add 20p P & P—No other extras

## TTLs by TEXAS

7400	13p	7484	103p
7400	20p	7485	130p
7401	15p	7486	32p
7402	15p	7487	281p
7403	17p	7490	43p
7404	17p	7491	81p
7404H	22p	7492	48p
7405	17p	7493	43p
7406	41p	7494	81p
7408	39p	7495	70p
7408	17p	7496	84p
7409	22p	7497	291p
7410	15p	74100	116p
7410	20p	74107	32p
7411	24p	74118	90p
7412	25p	74121	32p
7413	34p	74122	52p
7414	65p	74123	73p
7416	32p	74126	75p
7417	32p	74132	75p
7420	15p	74136	81p
7421	43p	74141	70p
7422	19p	74145	75p
7423	36p	74148	173p
7425	33p	74150	135p
7427	40p	74151	77p
7428	39p	74153	92p
7430	15p	74156	82p
7432	28p	74158	82p
7437	28p	74156	82p
7440	15p	74160	107p
7441	70p	74161	107p
7442	64p	74162	107p
7443	118p	74163	107p
7444	118p	74164	130p
7445	81p	74166	136p
7446	75p	74174	131p
7447	81p	74175	92p
7448	75p	74176	131p
7450	18p	74177	108p
7451	17p	74180	108p
7453	17p	74181	322p
7454	18p	74182	89p
7450	18p	74185	146p
7470	29p	74190	50p
7472	27p	74191	158p
7473	32p	74192	130p
7474	32p	74193	130p
7475	48p	74194	116p
7476	32p	74195	83p
7480	54p	74196	99p
7481	103p	74197	108p
7482	75p	74198	214p
7483	85p	74199	197p

## C-MOS ICs

4000	19p	4030	59p
4001	19p	4042	150p
4002	19p	4043	218p
4007	19p	4046	150p
4009	67p	4047	188p
4011	19p	4054	210p
4012	19p	4054	210p
4013	55p	4055	210p
4016	54p	4056	145p
4017	123p	4060	250p
4018	247p	4069	40p
4020	270p	4079	40p
4022	180p	4081	29p
4023	19p	4082	29p
4024	125p	4082	29p
4025	19p	4082	29p
4026	200p	4510	142p
4027	81p	4511	200p
4028	152p	4518	108p
4029	189p	4528	130p

## MULLARD MODULE

LP1186 VARICAP 810p

## LOW PROFILE DIL SOCKETS by TEXAS

8 pin 13p, 14 pin 14p,  
15 pin 15p, 24 pin 50p  
INSULATORS: Mica + 2  
Bushes for TO3 or TO66 5p

## VOLTAGE REGULATORS

FIXED—Plastic 3 Terminals

1 Amp Positive	
5V	7805 150p
12V	7812 150p
15V	7815 150p
18V	7818 150p
24V	7824 150p
1 Amp Negative	
5V	7905 215p
12V	7912 215p
15V	7915 215p
18V	7918 215p
24V	7924 215p

## DUAL VOLTAGE REGULATOR

1468 ±15% 100 mA  
16 pin DIL 324p  
Adjustable by resistors  
from ±8V min to ±20V max

## VARIABLE VOLTAGE REGULATOR

723 2V to 37V 150 mA  
14 Pin DIL 45p

## TRANSISTORS

AC125	18p	BC184	14p	BFR39	37p
AC126	13p	BC187	32p	BFR40	37p
AC127	13p	BC212	14p	BFR79	37p
AC128	12p	BC213	15p	BFR80	37p
AC176	12p	BC214	17p	BFR88	37p
AC187	14p	BC337	24p	BFX30	32p
AC189	14p	BC478	32p	BFX84	28p
AD149	48p	BCY70	20p	BFX85	27p
AD181	39p	BCY71	24p	BFX86	28p
AD182	39p	BD123	108p	BFY87	22p
AF114	18p	BD124	70p	BFY88	26p
AF115	18p	BD131	39p	BFY50	17p
AF116	18p	BD132	43p	BFY51	16p
AF117	18p	BD135	54p	BFY52	17p
AF139	35p	BD136	55p	BRV39	39p
BF209	43p	BD139	78p	BSX19	18p
BC107	10p	BD140	87p	BSX20	19p
BC108B	10p	BF115	24p	BU105	175p
BC108C	11p	BF167	25p	BU108	312p
BC147	9p	BF170	25p	MJE340	49p
BC148	9p	BF173	27p	MJ2855	81p
BC149	10p	BF178	30p	MJ2955	107p
BC150	11p	BF179	35p	MPSA06	37p
BC158	13p	BF180	35p	MPSA12	62p
BC159	13p	BF181	35p	MPSL06	78p
BC169C	9p	BF182	35p	MPSU56	99p
BC171	12p	BF185	24p	OC2	70p
BC172	11p	BF186	24p	OC3	70p
BC173	13p	BF194	13p	OC41	19p
BC177	20p	BF195	11p	OC42	19p
BC178	17p	BF196	17p	OC45	19p
BC179	20p	BF197	17p	OC71	25p
BC182	12p	BF200	40p	TP29A	22p
BC183	12p	BF257	34p	TIP29C	62p
		BF258	39p	TIP30A	60p

## OP AMPS

301A	Ext. Comp. 8 pin DIL	40p
536T	FET. Op. Amp TO 99	300p
709	Ext. Comp. 8/14 pin DIL	30p
741	Int. Comp. 8/14 pin DIL	25p
747	Dual 741 14 pin DIL	76p
748	Ext. Comp. 8 pin DIL	40p
778	Prog. Op. Amp. TO 99	153p
1458	Dual Op. Amp. 8 pin DIL	75p
3130	CMOS/Bipolar Mosfet 8 pin DIL	108p
3900	Quad. Op. Amp. 14 pin DIL	60p

## LINEAR I.C.s

CA 3028A	Diff. Cascade Amp. TO 99	112p
CA 3046	5 Transistor Array 14 pin DIL	55p
CA 3048	Quad. Low Noise Amp. 16 pin DIL	250p
CA 3053	Diff. Cascade Amp. TO5/DIL	45p
CA 3090E	FM IF System 16 pin DIL	250p
CA 3090AQ	FM Stereo Decoder QIL	500p
ICL8038B	VCO Function Generator 16 pin DIL	600p
ICL8038CC	VCO Function Generator 16 pin DIL	300p
LM 380N	2W Audio Amplifier 14 pin DIL	115p
LM 381N	Stereo Pre Amp 14 pin DIL	200p
MC1310	FM Stereo Decoder 14 pin DIL	220p
MC1312/3/5	SO Quad Decoder	137p
MFC4000B	1W Audio Amplifier PCB	75p
MFC6040	Electronic Attenuator PCB	130p
NE555V	Timer 8 pin DIL	40p
NE556V	Dual 555 14 pin DIL	108p
NE561B	PLL with AM Demod 16 pin DIL	350p
NE562B	PLL with VCO 16 pin DIL	350p
NE565	PLL 14 pin DIL	200p
NE566V	PLL Function Gen 8 pin DIL	165p
NE567V	PLL Tone Decoder 8 pin DIL	200p
2567	Dual 567 15 pin DIL	400p
SN72710	Diff. Comparator 14 pin DIL	54p
SN72733	Video Amplifier 14 pin DIL	150p
SN76013N	Audio Pwr Amp with Int HS	175p
SN76023N	Audio Pwr Amp with Int HS	175p
TAA861B	FM IF Amp Lim/Detector QIL	150p
TBA841B	Audio Amp 14 pin DIL	300p
TBA800	5W Audio Amp QIL	112p
TBA810	7W Audio Amp QIL	125p
TBA820	2W Audio Amp QIL	100p
TDA2020	20W Audio Amp QIL	405p
XR2240	Prog Timer/Counter 16 pin DIL	400p
ZN414	TRF Radio Receiver TO18	140p

Basic data sheet on above ICs at 10p each† S.A.E.

## OPTO-ELECTRONICS

PHOTO. TRANSISTORS	LEDs	
OCPT70	33p TIL209 Red	15p
OCPT71	120p TIL211 Green	32p
2N5777	43p TIL32 Infrared	81p
LDRs	0.2"	
ORP12	60p Red	17p
ORP60	75p Green	22p
ORP61	75p Yellow	32p

## SEVEN SEGMENT DISPLAYS

3015F	Minitron 0.3"	130p
DL704	Com. Cathode 0.3"	160p
DL707	Com. Anode 0.3"	160p
DL747	Com. Anode 0.6"	250p
OPTO-ISOLATORS		
Phototransistor TIL112 (IL 12)	6 Pin DIL	151p
Photodarlington ILCA55	6 Pin DIL	270p
DRIVERS		
75491	Quad Segment Driver 14 Pin DIL	78p
75492	Hex Dlgit Driver 14 Pin DIL	97p P & P.

TIP30C	72p	40594	81p
TIP31A	56p	40595	81p
TIP31C	68p	40596	92p
TIP32A	68p	BF244	45p
TIP32C	85p	MPF102	37p
TIP33A	97p	MPF103	37p
TIP33C	120p	MPF104	37p
TIP34A	124p	MPF105	37p
TIP34C	160p	2N3819	27p
TIP35A	290p	2N3820	50p
TIP35C	290p	2N3823	54p
TIP36A	297p	2N5457	32p
TIP36C	360p	2N5458	32p
TIP41A	70p	2N5459	32p
TIP42A	76p	3N128	81p
TIP2955	78p	3N140	92p
ZTX108	19p	3N141	81p
ZTX300	19p	40603	63p
ZTX500	19p	40673	54p
ZTX504	60p	UJTS	
2N877	14p	T1543	34p
2N698	32p	2N2160	88p
2N706	13p	2N2646	38p
2N708	19p	2N4871	37p
2N918	43p	PUJT	
2N930	19p	2N6027	60p
2N1131	19p	DIODES	
2N1132	19p	1N4132	19p
2N1304	23p	OA4	9p
2N1305	23p	OA70	10p
2N1306	23p	OA81	10p
2N1307	30p	OA85	11p
2N1613	22p	OA90	7p
2N1711	22p	OA91	9p
2N1893	32p	OA95	9p
2N2219	22p	OA200	8p
2N2220	19p	OA202	10p
2N2221	22p	1N914	4p
2N2222	22p	1N916	11p
2N2369	15p	1N4148	4p
2N2484	32p	RECTIFIER	
2N2904	22p	BY100	31p
2N2905	22p	BY126	15p
2N2906	22p	BY127	15p
2N2928B	107p	1N4001	8p
2N2928OG	11p	1N4002	6p
2N3053	19p	1N4004	7p
2N3054	43p	1N4005	7p
2N3055	54p	1N4007	8p
2N3439	72p	ZENER	
2N3442	151p	2.7 to 33V	
2N3702	14p	400mW	11p
2N3703	14p	1W	
2N3704	14p	TUNNEL	
2N3705	14p	AEY11	75p
2N3706	12p	VARIAC	
2N3708	11p	BB105	33p
2N3709	11p	NOISE	
2N3707	14p	Z5J	140p
2N3773	240p	BRIDGE	
2N3866	90p	RECTIFIERS	
2N3904	22p	1A 50V	25p
2N3905	22p	1A 100V	27p
2N3906	22p	1A 400V	31p
2N4058	19p	1A 600V	37p
2N4060	19p	2A 50V	40p
2N4123	22p	2A 100V	48p
2N4124	22p	2A 400V	58p
2N4125	22p	4A 100V	75p
2N4126	22p	6A 50V	65p
2N4289	24p	6A 100V	70p
2N4371	142p	TRIACS	
2N3448	173p	Amp Volts	
2N3904	22p	3 400 130p	
2N4403	34p	6 400 162p	
2N5089	34p	6 400 194p	
2N5401	62p	10 400 200p	
40360	43p	10 500 270p	
40361	41p	40430	108p
40362	43p	40485	108p
40410	59p	40669	105p
40409	59p	DIAC	
40411	243p	BR100	27p

## SCR THYRISTORS

1A 50V TO5	43p
------------	-----

**SINCLAIR IC20**

IC20 10W + 10W stereo IC amplifier kit with free booklet and printed circuit £6.95.  
 PS20 Power supply kit for the above £4.95.  
 VP20 Volume, tone-control and preamp kit £7.95.  
 SP20 10W 4 ohm speaker for IC20 £2.95.

Send sae for free leaflet.

**JC12 AMPLIFIER**

6W IC audio amp with free data and printed circuit £1.95\*

**DELUXE KIT FOR JC12**

Includes extra parts for the pcb and vol, bass and treble controls for mono version £2.29. Stereo model with balance control £4.95.

**JC12 POWER KIT**

Supplies 25V 1 Amp £2.95.

**JC12 PREAMP KITS**

Type 1 for magnetic pickups, mics and tuners. Mono £1.55. Stereo £3.10. Type 2 for ceramic or crystal pickups. Mono 85p. Stereo £1.70.

**LOUDSPEAKERS FOR JC12**

8in x 5in 8 Ohms 5W £2.50.

SEND SAE FOR FREE LEAFLET ON KITS.

**SINCLAIR PROJECT 80**

FM tuner £13.25. PZ5 £3.95. Q16 £10.95. PZ6 £8.70. PZ8 £9.10. Trans for PZ8 £5.40. Z40 £5.75. Stereo 80 £11.95. Project 805. Project 805Q £18.95. Quad decoder £14.95. 260 discontinued but we stock 30W similar amp £10.30.

**PRINTED CIRCUIT KIT £3.95\***

Make your own printed circuits. Contains etching dish, 200 sq. ins. of copper clad board, 1 lb ferric chloride, etch resist pen, small drill bit, laminate cutter and instructions.

**MAINS TRANSFORMERS**

8-0-8V 100mA 95p. 9-0-9V 100mA 95p. 18V 1A £1.85\*. 0, 12, 15, 20, 24, 30V 1A £2.95\*. 12-0-12V 1A £1.95\*. 0, 12, 15, 20, 24, 30V 2A £4.90\*. 20V 2.5A £2.20. 6 and 9V trans are DC rated, others are AC volts.

**SINCLAIR BLACK WATCH**

Fully assembled with black strap £20.95\*. Bracelet £2\*.

**SINCLAIR CALCULATORS\***

Cambridge £7.95. Cambridge Memory £11.20. Scientific £8.95. Oxford 100 £6.95. Can. Sci £14.95. Oxford 300 £16.95. Programmable scientific £25.95. Mains adaptor for programmable and Oxfords £3.19. Mains adaptor for Cambridge and Scientific £3.15.

**CBM CALCULATORS\***

796MD £6.45. 897D P.O.A. SR1800 P.O.A. 776MD 7 digit/mem/const £5.95. SR7919D 8 digit/mem/1r/10g/pi/powers/scientific notation £13.20. SR4148R with mains unit £34.95. Mains unit for other machines £2.95.

**CASIO CALCULATORS\***

Personal mini 6 + 6 digits £5.95. Pocket 8S 8 digits/% const £8.25. Memory 8R 8 digits/%mem/const £9.25. FX20 £10.95. Mains adaptor for all models £3.95.

**24 HR DIGITAL CLOCK KIT\***

Includes pcb, mains power supply, attractive case, 0-5in jumbo green display, clock chip, and all other parts. Displays hours and minutes separated by a pulsating colon. Kit £12.50. Built £13.50. Send sae for free leaflet.

**S-DECS AND T-DECS\***

Special Offer—25p or 50p off orders accompanied by 25p or 50p PB Electronics adverts.

S-DeC £2.24

T-DeC £4.05

u-DeC A £4.45

u-DeC B £7.85


IC carriers:—

16 dli: plain £1.07

with socket £2.21

10 TO5: plain 99p, with socket £1.95.

SST1 60p. SSU1 60p. SSN1 80p.

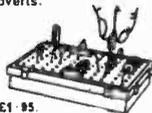**BATTERY ELIMINATOR BARGAINS**

**55-WAY SUPER**  
 New switched model. 3 to 30V in 1V steps. Fully stabilized. 1A output. Kit £7.95. Assembled £10.95. 2 Amp model. Kit £9.95. Built £12.95.

**6-WAY SPECIAL**

Switched output of 3/4/6/7/9/12V at 500mA with 4-way multi-jack plug and free matching socket £5.80.

**6-WAY DOUBLE RADIO MODEL £6.80**

Similar to above, but with press-stud battery connectors. 3 + 3/4 + 4 1/2 + 6/7 + 7 1/2 + 9/12 + 12V at 250mA. Also gives 15/16/24V single.

**3-WAY MODEL**

Switched output of 6/7 1/2/9V at 250mA with 4-way multi-jack plug and free matching socket £2.95\*.

**RADIO MODELS**

50mA with press-stud battery connectors for radios, etc. 6V £2.95. 9V £2.95. 4 1/2 + 4 1/2V £4.45. 6 + 6V £4.45. 9 + 9V £4.45.

**CASSETTE MAINS UNITS**

7 1/2V output to run cassette recorders from the mains. Complete with 5 pin DIN plug £3.45.

**CAR CONVERTORS**

Input 12V DC. Output 6/7 1/2/9V DC 1A regulated £3.95\*.

**BATTERY ELIMINATOR KITS**

Send sae for free leaflet on range.  
 100mA radio type with press stud battery terminals. 4 1/2V £1.95. 6V £1.95. 9V £1.95.  
 50mA double radio type with press stud terminals. 4 1/2 + 4 1/2V £2.75. 6V + 6V £2.75. 9V + 9V £2.75. 100mA cassette type with 5 pin DIN plug. 7 1/2V £1.95.  
 Stabilized 8-way type with voltage stabilizer to give low hum. 3/4/6/7 1/2/9/12/15/18V 50mA £2.95.  
 Heavy duty 12-way type 4 1/2/6/7 1/2/9/11/13/14/17/21/28/34/42V. 1 Amp £3.95. 2 Amp £5.95.

**SWANLEY ELECTRONICS**

Dept. PW, PO Box 68, Swanley Kent

Post 30p on orders under £2, otherwise free. Prices include VAT. (Overseas customers deduct 7% on items marked \*, otherwise 20%). Official orders from schools, government labs, etc. welcome.

# IMPORTANT NOTICE TO ALL VEROBOARD STOCKISTS

Vero Electronics Limited are printing a list of Vero board stockists. This list will be distributed to amateur electronic constructors throughout the U.K. Whether you purchase Vero board from a wholesaler or direct, please forward your business name and address for inclusion in this list to:

Vero Electronics Limited.  
 Retail Department  
 Industrial Estate  
 Chandler's Ford  
 Hants SO5 3ZR



## Unbeatable VALUE

**Genuine GOLDRING Stylus P. & P. 25p**

G800	£2.35	G850	£1.95
G800/H	£2.35	G800/E	£4.42

**MICROPHONES P. & P. 25p**

UD 130—Cardioid dynamic dual impedance 600 and 50kΩ	£6.58
ECM81—Cardioid condenser omni-directional 600 and 50kΩ Impedance	£11.99
RX201—Cardioid dynamic 600Ω echo mike, 4 transistors, 1.5 sec reverberation time, with volume control and on-off switch	£9.93
Philips type cassette mike	£1.65
Cassette stick mike with remote control	£1.30
Gem 2 station intercom (baby alarm)	£3.85

**CASSETTES (Low Noise) P. & P. 25p**

	1-5	Over 6
C60	35p	32p
C90	43p	40p
C120	55p	52p

**SOLDERING IRONS P. & P. 25p**

12V d.c. 15 watt	£1.24	250V a.c. 40 watt	£1.40
------------------	-------	-------------------	-------

**CABINET KITS P. & P. 85p per pair**

12" x 8" x 4 1/2" (8" x 5" or 7" x 4" cutout)	£2.90 each
12" x 12" x 7 1/2" (10", 8" or 8" x 5" cutout)	£4.05 each
18" x 11" x 7 1/2" (8" and 3", 8" x 5" or 8" cutout)	£5.10 each
22" x 14" x 7 1/2" (13" x 8" or 12" and 3" cutout)	£6.15 each

**ALL PRICES INCLUDE VAT**

Items subject to availability and manufacturers' increase. U.K. only.

**Riversdale Electronics**  
 Mail Order Department **PW5**

P.O. Box 470, Manchester M60 4BU

# Do Something Useful for a Change!

Do it in your spare time. And enjoy it. And, perhaps, you'll save yourself some money. The secret is to be practical about the way you spend your spare time.

These practical magazines show you how.


Every month these six popular titles are packed with fascinating and constructive projects – full instructions for making your own furniture and fittings for the home as well as electronic gadgets for home, car or hobby.

See which 'practical' can widen your range of interests, whether in home-improvement, hi-fi or electronics – and on jobs you really could call useful.



Over the past decade, this widely-read magazine has gone from strength to strength. *Practical Electronics* brings the latest technology within reach of the home constructor. April issue: 8-page constructor. Sound Effect Units. SUPPLEMENT

35p

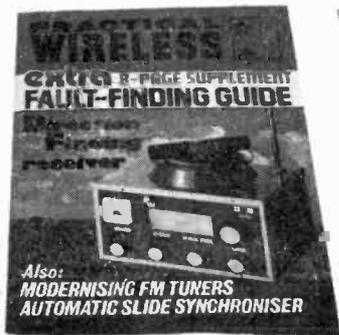

For over 40 years Britain's premier magazine for the do-it-yourself radio and electronics constructor. See how *Practical Wireless* makes technicalities crystal clear even to the newcomer. April issue: 8-page supplement – Fault Finding Techniques.

35p



The only electronics magazine catering exclusively for the beginner. *Everyday Electronics* projects are easy to construct and their theory is simply explained. April issue: 8-page supplement – Beginner's Construction Guide.

30p



The only magazine catering for those interested in the technical side of television in the home. *Television* covers servicing, maintenance, construction and modification. April issue: 8-page supplement. TV Test Patterns and Signals.

40p



Every aspect of the sound scene is covered in *Practical Hi-Fi & Audio*, which month by month shows you how to choose, match and improve your equipment. April issue: 12-page supplement – Buying on a Budget.

30p



Whether you are a home-improvement enthusiast, hobbyist or model-maker, there is the coverage you need on all aspects of wood and timber crafts. April issue includes a 16-page pull-out booklet 'Woodworking Terms', and a super radial arm saw to be won.

OUT MARCH 19 40p

## Be Practical...Get a 'Practical' Today!

If you are unable to obtain a copy of any of the above titles from your newsagent, please contact: Sales Manager, IPC Magazines Ltd., 66 Great Queen Street, London WC2B 6DD.

# Practical Wireless Classified Advertisements

The pre-paid rate for classified advertisements is 14p per word (minimum 12 words), box number 35p extra. Semi-displayed setting £12.00 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL WIRELESS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the GMG Classified Advertisement Manager, PRACTICAL WIRELESS, IPC Magazines Ltd., Room 2337, King's Reach Tower, Stamford Street, London SE1 9LS for insertion in the next available issue. (01-261 5846).

## Receivers and Components

**COMPONENTS GALORE**, pack of 500 assorted Radio, TV and Electronic components, a real bargain at a realistic price. Send only £1.50 c.w.o. This applies only to United Kingdom and Ireland. Overseas prices by arrangement. Caledonian Components. PO Box 3, Glenrothes, Fife, Scotland.

**COMMUNICATIONS RECEIVER** modules. Small superhet circuit boards requiring only controls and tuned circuits. 9 volt. Mosfet mixer, IC IF, BFO, Prod. Det. Excellent AM/CW/SSB results reported by delighted users. From £11.50. SAE details. PR Goldedge Electronics, Millend, Stonehouse, Glos.

### Precision Polycarbonate Capacitors

All High Stability - extremely Low Leakage

440V AC RANGE			63V DC RANGE		
Value (µF)	Dimen- sions (mm)	Price	Value µF	±1%	±2%
0.1µF	L 10	8p	0.01µF & 0.1µF	86p	49p
0.15µF	27 12 7	51p	0.22µF; 0.33µF;	87p	50p
0.22µF	33 16 8	64p	0.47µF	87p	50p
0.25µF	33 16 8	64p	1.0µF	82p	62p
0.33µF	33 16 8	64p	1.5µF	89p	71p
0.47µF	33 19 8	80p	2.2µF	96p	76p
0.5µF	33 19 8	80p	3.3µF	111p	86p
0.68µF	50 8 19	98p	4.7µF	116p	91p
1.0µF	60 8 19	110p	6.8µF	131p	106p
1.5µF	60 8 25	121p	10µF	146p	121p
2.0µF	60 8 25	144p	15µF	161p	136p
			22µF	186p	161p

**TANTALUM BEAD CAPACITORS**—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8µF at 16V/25V or 35V; 100µF at 16V/20V or 25V; 220µF at 6V/10V or 18V; 330µF at 6V or 10V; 470µF at 3V or 6V; 1000µF at 3V. ALL at 12p\* each; 10 for £11.00, 50 for £5.00, 100 for £2.00.\*

**TRANSISTORS V.C.O.'s**

BC107/8/9 8p	*BC212/212L 14p	2N3702/4 11p
*BC114 12p	*BC213/213L 11p	2N3055 25p
*BC147/8/9 10p	*BC214/214L 11p	OC71/2 12p
*BC153/154 12p	*BF194/5 12p	NE555Timer 61p
*BC157/8/9 12p	*BFY501/2 20p	741C 8pin DIL 32p
*BC182/182L 11p	AF178 30p	2N414 11.5p
*BC183/183L 11p	A2294 35p	2N7003ND 21.5p
*BC184/184L 12p		

**POPULAR DIODES**—1N914 5p, 5 for 45p, 18 for 90p; 1N4148 5p, 4 for 45p, 14 for 90p; 1N4149 5p, 11 for 50p; 24 for £1.00, 1N4148 5p, 6 for 87p, 12 for 45p; 1N4001 8p; 002 8p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p

**LOW PRICE ZENER DIODES**—400mW. Tel. ±5% at 5mA: 3V; 3V3; 3V6; 4V7; 5V1; 5V6; 6V2; 6V8; 7V5; 8V2; 9V1; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each, 5 for 33p, 10 for 65p, 50 for £3.12. SPECIAL OFFER: 100 Zeners (may be mixed) for £6.00.

**RESISTORS**—High stability, low noise carbon film 5%, 1W at 40°C, 1W at 70°C. E12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p\* each, 50p\* for 10 of any one value, 70p\* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2MΩ (730 resistors) 25p.

**SILICON PLASTIC RECTIFIERS**—1.5 amp, wire-ended D027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

**BRIDGE RECTIFIERS**—2 1/2 amp: 200V 40p; 300V 40p; 500V 50p.

**SUBMINIATURE VERTICAL PRESETS**—0.1W only: All at 5p\* each: 50; 100; 220; 470; 680 ohm; 1K; 2K2; 4K7; 6K8; 10K; 15K; 22K; 47K; 100K; 200K; 680K; 1M; 2M5; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with \* which are 25%.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies. **MARCO TRADING (Dept. W5)**, The Old School, Edkinston, Nr. Wem, Shropshire. Tel: Whizall 464/466 (STD 094 878) (Proprs. Minicost Trading Ltd.)

Yes, still the same JUMBO bottle  
Beware of imitations

175cc **P.C.B. Ink** £1.50

Quick drying ferric chloride etch resist ink, applied by pen or brush.

**MAWSON ASSOC.**  
64, Brookbank Road, London SE 13

FULL SPEC. NEW DEVICES, BY RETURN			
BC107	10p	ZTX504	25p
BC108	10p	2N3055	40p
BC109	10p	2N3819	39p
BC182L	10p	1N914	4p
BC183L	10p	1N4148	4p
BC184L	10p	1N4002	4p
BC212L	14p	1N4003	4p
BC213L	14p	1N4004	5p
BC214L	14p	1N4007	9p
TIP29A	46p	3A/800V	Reel
TIP30A	49p		15p
TIP31A	51p		
TIP32A	55p	1A/200V	26p
TIP41A	72p	2A/600V	33p
TIP42A	78p		
TIP2955	64p	741 8 pin	25p
TIP3055	49p	555 Timer	49p
TIS43(UUT)			
	35p	<b>DISPLAYS</b>	100 £1
ZTX300	15p	<b>LED 7-Seg.</b>	1000mf/6V
ZTX304	25p	0.375; £1.15	10/30p
ZTX500	15p	0.5; £1.49	100/£1.50

**REGU-LATORS**  
TO-20  
7805 (5V) £1.59  
7812 (12V) £1.59  
7815 (15V) £1.59  
7824 (24V) £1.59

**BRIDGES**  
1A/200V 26p  
2A/600V 33p

**CAPACITORS**  
10mf/12V  
100 £1  
1000mf/6V  
10/30p  
100/£1.50

**DIL I.C.'s**  
741 8 pin 25p  
555 Timer 49p

**DISPLAYS**  
100 £1  
1000mf/6V  
10/30p  
100/£1.50

V.A.T. Inc. P and P. at 20p.  
Display data—S.A.E. Please.  
Tel.: Kingston Blount 52683.

**AUDIO-OPTICS**  
19, Middleway, Chinnor, Oxon.

**NEW COMPONENTS BY RETURN.** BC109C 12p, BC182L 10p, BC184L 11p, BC212L 12p, BC214L 13p, BD529 65p, BD530 65p, BDY56 £1.75, BFR39 35p, BFR79 35p, 2N5457 45p, 2N5459 45p, MP5A12 40p, MC1310P £2.70. Inclusive prices. P & P 10p. All components brand new and guaranteed. I. G. Bowman (Dept PW), 59 Fowey Avenue, Torquay, S. Devon.

**POLYESTER CAPS C280** 1 250V 4 for 5p  
**REED SWITCHES** Large / Small 10p ; **BAR MAGNETS** 7p ; Large red L.E.D.S. 25p 3 for £1  
5 yards CONNECTING WIRE, ass'td. colours 10p  
**BURGlar ALARM** 13V DC 75p enamelled.  
**COPPER WIRE** 32, 34, 36 S.W.G. 1p ft.  
**LOUD 6V D.C. MOTOR DRIVEN SIRENS** £1.25  
**CAPACITORS or RESISTORS** Assorted pkt. 25p  
Prices include VAT. Add 12p postage.

**GRIMSBY ELECTRONICS**  
84 Tennyson Road, Cleethorpes, Humberside  
100's of Bargains at our Lambeth Road Component shop (open Saturdays). 1976 List 9p.

**TRIACS (Plastic)** TAG250 400V/10A 67p (3+64p); Diacs 19p, 8-pin dil ICs 741 24p, 555 44p, Mini Mains Transformers 100mA 6.0-6V 85p, 12.0-12V 95p, 2N3055 36p, 300W Dimmer Kit £1.95. P&P 15p. Add 8% VAT. T. K. Electronics, 106 Studley Grange Road, London W7 2LX.

**AERIAL WIRE, HARDWARE, VERO PRODUCTS**  
Resistors, 1/4W, 1/2W 5%, 2.20-2.2M 1p  
Capacitors, all types, from 3p  
**Denco D.P. Colls.** 1-5 Green, 74p; 1-5 B, Y, R, W, 8p; 6-7 B, Y, R, 8p  
**IFT's** 13/14/15/16/17, 86p. VAT not included.  
P. & P. 20p. S.A.E. for full lists.

**CLEVELAND SUPPLIES (PW)**  
P.O. BOX 20, REDCAR  
CLEVELAND

**METAL BOXES / INSTRUMENT CASES.** Range of over 100 standard sizes with punched holes to your specification if required. B.M.S. cut to size. Components. Audio equipment, kits and complete. 2 x 6 1/2 p stamps for lists. Nottingham Audio Services, 13/15, Foxhall Road, Nottingham NG7 6NA.

**TESTED** MIXED MINIATURE ELECTROLYTIC CAPACITORS  
6V - 63V

50 PACK ..... 1-68 MFD **£1.00**  
100 PACK ..... 1-68 MFD **£1.84**  
50 PACK ..... 10-1000 MFD **£1.52**  
100 PACK ..... 10-1000 MFD **£2.52**

**CASH WITH ORDER PLUS 25% VAT**

**P & P INCLUDED**

**M.C.L. (Dept. C)**  
12 OAKINGTON AVE  
RAYNERS LANE  
HARROW, MIDD.

**500 COMPONENTS.** Resistors, capacitors, diodes, transistors, pots, coils, etc. Identified, formed leads, fall-out, and surplus. Good value at £1.60. All inclusive (U.K. postal rates only). CWO please to L. Penseny, PW Bankhead Farm, South Queensferry, West Lothian.

**WENTWORTH RADIO**  
1A Wentworth Ct. Alston Road, Barnet Herts.  
Telephones 01-440-0409—01-441-2328

TBA520Q	£2.20	BC107/8/9	0.09
TBA550Q	£3.00	BT106	0.95
TBA750Q	£2.15	1N4148	0.05
TBA990Q	£2.85	2N3055	0.41
R2010B	£1.80	TIP29C	0.34
SN76227N	0.80	TIP30C	0.46

**COMPONENTS—UNITS—VALVES SEND S.A.E. FOR LISTS**  
Minimum order 75p. P&P 5p. per item.  
Minimum 15p plus 25% V.A.T.

**ALL PRICES SUBJECT TO FLUCTUATION**

**BRAND NEW COMPONENTS BY RETURN:** Electrolytics—16V, 25V, 50V—0.47, 1.0, 2.2, 4.7, 10 mfd.—5p. 22, 47—5½p. (50V—6p) 100—7p. (50V—8p) 220—8p. (50V—10p) 500—11p. (50V—16p) 1000/25V—18p. Subminiature bead-type tantalums—0.1/35V, 0.22/35V, 0.47/35V, 1.0/35V, 2.2/35V, 4.7/35V, 10/20V, 22/16V, 47/6V, 100/3V.—11p. Mylar Film 100V.—0.001, 0.002, 0.005, 0.01, 0.02.—3p. 0.04, 0.05—3½p. Mullard tubular polyester 400V E6 series 0.001-0.022—3½p. 0.033-0.1—4½p. Mullard miniature C333 ceramics 63V E12 series 2%, 1.8 pf.—47 pf.—3p. 56 pf.—330 pf.—3½p. Polystyrene 63V E12 series 10 pf.—1000 pf.—3p. 1200 pf.—10,000 pf.—4p. Miniature Highstab. carbon film resistors ½W E12 series 5% 1Ω-10MΩ. (10% over 1MΩ) 1-2p. Postage 10p. Prices VAT Inclusive. The C.R. Supply Co., 127, Chesterfield Road, Sheffield S8.

## Educational

GO TO SEA as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

### C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians, Telecomms Technicians and Radio Amateurs.

### COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

### TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

**INTERNATIONAL  
CORRESPONDENCE SCHOOLS,**  
Dept. 778S, Intertext House, London SW8 4UJ.  
Or Phone 01-622 9911 (All Hours)

**MANCHESTER EDUCATION COMMITTEE.** Tenders are invited for the purchase of second-hand audio-visual aids equipment. Further details and forms of tender from Supplies Officer, Stores Department, New Cross, Manchester, M4 5ES, returnable by 10th May, 1976.

## TAPETALK

### THE NATURAL WAY TO LEARN

Two C60 cassettes entitled

**THE SCIENCE OF SOLDERING**  
£5.44 plus 55p VAT/P. & P.

**TAPETALK, P.O. Box 99 (PW)**  
Milton Keynes MK3 5BR  
Tel.: Milton Keynes (0908) 77710

## Electrical

**STYLI & CARTRIDGES.** For the best at keenest prices send SAE for free illustrated list to Felstead Electronics (PW), Longley Lane, Gatley, Ches. SK8 4EE.

## Ladders

**LADDERS.** Varnished. 25½ft extended, £24.05, carriage £1.40. Leaflet, aluminium ladders and loft stairways. Tel: Telford 586644.

## Service Sheets

### SERVICE SHEETS—COLOUR TV MANUALS

Service Sheets for Black and White TV, Radios, Record Players and Tape Recorders 50p. Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers.  
**B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA etc.**  
Please send a Stamped Addressed Envelope for a prompt reply.

**G. T. TECHNICAL INFORMATION SERVICE**  
10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA  
MAIL ORDER ONLY

## LARGE SUPPLIER OF SERVICE SHEETS

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)  
ALL AT 50p EACH

**"PLEASE ENCLOSE LARGE S.A.E WITH ALL ENQUIRIES & ORDERS"**

Otherwise cannot be attended to  
(Uncovered P.O.s please, original returned if service sheets not available.)

### PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

## C. CARANNA

71 BEAUFORT PARK  
LONDON, N.W.11 6BX

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative. Free TV fault tracing chart or TV list on request with order.

Mail order or phone 01-458 4882  
Large Stocks of Colour Manuals  
NO OVERSEAS MAIL PLEASE

**SERVICE SHEETS,** radio, TV etc. 10,000 models. Catalogue 24p. plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

**BELL'S TELEVISION SERVICES** for service sheets, manuals & books on radio/TV etc. Service sheets 50p plus SAE. Service sheet catalogue 25p. Back issues of magazines from April '74 onwards cover price plus 12p post. Free booklists on request. SAE with enquiries please to B.T.S., 190 Kings Road, Harrogate, Yorkshire. Telephone Harrogate (code 0423) 55885.

## Tape Recorders

### MUSICASSETTES FOR HIRE

Over 3,000 titles to choose from, for as little as 2p per day. Many special benefits to members. Free brochure from:

**THE STEREO CASSETTE LENDING LIBRARY,** Room 16, SHERWOOD HOUSE, SIMMONDS ROAD, CANTERBURY CT1 3JL

## TAPETALK

### THE CLEVER WAY TO LEARN

TWO C60 Cassettes entitled  
**INTRODUCING ELECTRONICS**  
£5.44 plus 55p VAT/P. & P.

**TAPETALK, P.O. Box 99 (PW)**  
Milton Keynes MK3 5BR  
Tel.: Milton Keynes (0908) 77710

**SERVICE SHEETS** for Radio, TV, Tape Recorders, Stereo, etc., with free fault-finding guide, 50p and SAE, Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

## For Sale

**DISCOLIGHTS.** Best! Cheapest! Reliable! Bumper catalogue: Aarvak Electronics, 12a(P) Bruce Grove, N17 6RA. 01-808 8923.

**MICROPHONES:** AKG D202EI, £45.00; AKG D190C or E, £20.00; AKG D224, £60.00; Sennheiser MD211N, £45.00. All brand new and boxed. Please add 25% for VAT. All other AKG and Sennheiser mikes, SAE for quote. J. J. Francis (Wood Green), Ltd., Manwood House, Matching Green, Harlow, Essex. Tel: Matching 476.

### COPPER CLAD LAMINATE FOR PRINTED CIRCUITS

Single sided 1/16" paper base—1.5p/sq. inch. Single sided 1/16" glass-epoxy—2.0p/sq. inch. Any rectangular sizes cut to your requirements. Please send cash with order. Price includes postage and packing.  
**SIMTECH ENGINEERING LTD**  
Dedham Road, Ardleigh, Colchester, Essex, CO7 1QA  
Telephone 0206 230133

**FOR SALE:** Codar AT5+AC PU, £20. Deliver Tyne Wear, Nesbitt, 34 West Dene Drive, North Shields.

## Wanted

**WE BUY** New Valves, Transistors and clean new components, large or small quantities, all details, quotation by return. **WALTON'S,** 55 Worcester Street, Wolverhampton.

### TOP PRICES PAID for NEW VALVES and TRANSISTORS

popular T.V. and Radio types.

**KENSINGTON SUPPLIES (C),**  
367 Kensington Street, Bradford 8, Yorkshire.

**PCR.3** Receiver Coils and dialglass or will buy complete if items wanted are intact and good condition. A. J. Brennan, 29 Elmfield Street, Cheetham, Manchester 8.

**REASONABLE** price paid pre-1960 P.W's. Details and price please. Box 130.

**WANTED EX-GOVERNMENT** TR1936, I.F. Strips 10U/254 and Parts Manuals Radio/Radar 10A, 10B etc. B.H. Avionics Ltd., Biggin Hill Aerodrome, Kent. Tel No. B.H. 71465.

## Miscellaneous

**BUILD THE TREASURE TRACER MK III Metal Locator**



- Varicap tuning
- Britain's best selling metal locator kit; 4,000 sold
- Weighs only 22oz. Fitted with Faraday shield
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- Five transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £12.50 Built & tested £17.50  
Post 85p - £1.90 VAT 8% Post 85p - £1.40 VAT 8%

MINIKITS ELECTRONICS,  
4 CLEVELAND ROAD,  
LONDON, E18 2AN (Mail order only)

**THE SCIENTIFIC WIRE CO**

Copper - Nickel Chrome - Eureka - Manganin Wires.

Enamelled - Silk - Cotton - Tinned Coverings.

No minimum charges or quantities.  
Trade and Export enquiries welcome.

S.A.E. Bring List.  
P.O. BOX 39, LONDON, E4 9BW

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from heavy duty PVC faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range, competitive prices start at a low 75p. Examples: width, depth, height, 8in x 5in x 3in, £1.55; 10in x 6in x 3in, £2.20; 12in x 6in x 3in, £2.70; 14in x 6in x 3in, £2.95; 10in x 8in x 3in, £2.75; 12in x 8in x 3in, £3.20; 14in x 8in x 3in, £3.60; 12in x 10in x 3in, £3.60; 8in x 4in x 4in, £1.80; 10in x 6in x 4in, £2.70; 12in x 6in x 4in, £2.85; 14in x 6in x 4in, £3.25; 12in x 8in x 4in, £3.60; 14in x 8in x 4in, £3.80; 7in x 7in x 5in, £2.65; 8in x 10in x 6in, £3.60; 12in x 8in x 7in, £4.00; 14in x 8in x 7in, £4.80; 12in x 10in x 7in, £4.25; 12in x 12in x 7in, £4.40; 14in x 10in x 7in, £5.00; 12in x 10in x 8in, £5.00; 14in x 10in x 8in, £5.30; 14in x 12in x 7in, £5.20; 12in x 12in x 8in, £5.50; 14in x 12in x 8in, £5.80. Plus 72p carriage and 8% VAT. 16in x 8in x 8in, £7.60; 16in x 10in x 8in, £8.40; 18in x 8in x 8in, £9.50; 18in x 10in x 8in, £10.30; 19½ in x 8in x 8in, £11.50; 19½ in x 10in x 8in, £12.30. Plus carriage £1.25 plus 8% VAT. Over 400 models to choose from. Prompt despatch. Free literature (stamp would be appreciated), Bazelli, Dept. No. 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

**ENAMELLED COPPER WIRE**

S.W.G.	1 lb reel	½ lb reel
10 to 19	2.40	1.35
20 to 29	2.45	1.40
30 to 34	2.60	1.50
35 to 40	2.85	1.60

All the above prices are inclusive of postage and packing in U.K.

**COPPER SUPPLIES**  
102 Parrawood Road, Withington,  
Manchester 20 Tel: 061-445 8753

**DO-IT-YOURSELF** loudspeakers for hi-fi are our speciality. Full range of components and accessories including chassis speakers, crossovers, sound absorbent, grille fabrics etc. always available. We stock the fabulous value Helme speaker kits complete with full and easy instructions, also Peerless and Wharfedale kits. Just about the lowest prices anywhere! Send 8½p stamp for bargain list to: Audioscan, Dept. PW575, 4 Princes Square, Harrogate, North Yorkshire.

**TEXAN AMPLIFIER PARTS**

Pack 1 Res, 80p, Packs 2-3 Caps, £3.50, Pack 5 Switches £1.50. Pack 6 Pots, £1.50. Pack 7 Semi Conductors, £8.25, P.C. Board £3.00. Front Panel £2.50, Chassis £3.00, Case £3.50, p.p. extra 25p except chassis 50p and case £4.00. Tax extra 25%. Send S.A.E. for details of this and other amplifiers from 1 watt-100 watt.

**TELERADIO ELECTRONICS**  
325, FORE STREET, LONDON, N.9.  
01-867-3719

**COLCHESTER COMPONENTS SHOP.**  
Now open Sunday-Thursday 12-6 p.m.  
J. K. Electronics, 11 Mersea Road,  
Colchester 64433.

**TRANSMIT!**

- ★ **Unique TRANSMITTER/RECEIVER Kit.** No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £7.95 for yours now!
- ★ **Psychedelic MINI-STROBE Kit.** Take a pocket-sized lightning storm to Disco's & parties. 'Brain-freeze' 'em with vari-speed stop-motion flashes. Includes super case too. Send £3.50 now! (all prices include V.A.T., packing & postage.)

Send remittance to:  
**BOFFIN PROJECTS,**  
4 CUNLIFFE ROAD,  
STONELEIGH, EWELL, SURREY  
(Mail order U.K. only)  
Or for more details, send 20p for lists

**NOTCH OUT QRM!**

Tunable Audio Notch Filter rejects heterodyne and CW interference FAST. Goes between RX and speaker. EASY TO MAKE. All parts, case, instructions, money back assurance, ONLY £5.30 post free

**CAMBRIDGE KITS**  
45 (Box E), Old School Lane, Milton,  
Cambridge.

**12 VOLT 21" 13 Watt Fluorescent Lighting** (by Thorn/AE) with diffuser & on/off switch. Ideal caravan, boat, emergency lighting, etc. Guaranteed.



£5.50 inc. VAT & Post. List price £7.02 inc. VAT

**SALOP ELECTRONICS** 23 Wyle Cop,  
Shrewsbury, Shropshire Tel. 53298

**ALUMINIUM SHEET AND BOXES** cut and folded to your design. Sheet: 22, 20, 18 S.W.G. 0.5p/sq inch; 16, 14 S.W.G. 1p/sq inch. Boxes: 22, 20, 18 S.W.G. 1p/sq inch; 16 S.W.G. 1½p/sq inch; 14 S.W.G. 2p/sq inch. Maximum length of any side: 2ft. Maximum depth of box: 1 ft. Please add 8% VAT. P&P 25p per item. SAE for special quotes (UK only). Trade enquiries welcomed. Simtec Electronics (UK) Ltd., Unit 37, Faircharm Trading Estate, St. Mary's Mills, Leicester. Tel: (0533) 824380.

**MINI ACCUMULATORS**

2 volt MULTI-USE Sealed Lead Acid Rechargeable Cells.

Size LA50-1.4" X 1.1" X .44", 3 for £2.15 inc. P. & P.

Size GA2-1.7" X 1.3" X .5", 3 for £2.65 inc. P. & P.

Suits Fi-Cord

**GARFIELDS**, 295 Rye Lane, London, S.E.15

**H. M. ELECTRONICS**  
275a FULWOOD ROAD, BROOMHILL,  
SHEFFIELD S10, 3BD.

**BEC. CABINETS** (Ilite'd)



**METAL CASES**  
**DRY TRANSFER LETTERING**

Send 15p for leaflets (Refundable)  
Trade enquiries invited

**NICKEL CADMIUM** fully sealed rechargeable batteries. Equivalent dry cell sizes. Discount. S.A.E. brings full details by return. Charges available. Sandwell Plant Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands, B73 6PP. 021-354 9764.

**RECORD from TV**



Make **SOUND RECORDINGS** from a TV set using this **ADAPTOR** with your cassette recorder or use it with your Hi-Fi or headphones. Completely Safe. Fully isolated. Leads, connectors and full instructions included. £6 inc. post and VAT or write for leaflet!

**CROWBOROUGH ELECTRONICS**  
(PW) Eridge Road, Crowborough,  
Sussex

**1LB PACKS** of assorted copper laminates for 60p plus p/p 30p. Cash with order to Crossley & Bradley, 248 Slater Lane, Leyland, Lancs.

**PRINTED CIRCUITS and HARDWARE**

Readily available supplies of Constructors' hardware, Aluminium sheet and sections. Printed circuit boards, top quality for individual or published designs. Prompt service. Send 15p for catalogue.

**Ramar Constructor Services,**  
Masons Road, Stratford on Avon,  
Warwicks. Tel. 4879

**GLASS FIBRE P.C.B.s.** Send 1:1 master and 7p per square inch tinned or 9p per square inch drilled and tinned PLUS 30p per board. Send for quotation on double sided boards. Discount for quantity. **PROTO DESIGN**, 4 Highcliffe Way, Wickford, Essex SS11 8LA.

**HELME**



**DO-IT-YOURSELF HI-FI STEREO SPEAKER KITS**

The best value around!  
Send for details

**HELME AUDIO PRODUCTS LTD.**  
Dept. PW  
SUMMERBRIDGE  
HARROGATE YORKS

Tel: Darley 279 (Std Code 0423 72)


**BUILD YOUR OWN**

You are invited to send S.A.E. for lists of our very extensive range of high quality amplifier, pre-amps, F.M. tuners, instruments. Radiocontrol ignition units and many other kits. Please state requirements.

**TELERADIO ELECTRONICS,  
325 FORE STREET, EDMONTON,  
LONDON N9**

**RADIO.** Learn from the beginning. 16 vintage circuit diagrams, receivers and transmitters with notes. £1. Allister, 58 Wavell Road, Maidenhead, Berks, SL6 5AD.

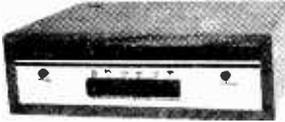**THE P.E. 'VARICAP'  
STEREO PUSH BUTTON  
TUNER**



Using the latest Mullard modules for R.F. and I.F. circuits—pre-aligned for ease of construction—this KIT has an F.M. tuner with stereo decoder, push button tuning, self regulated power supply, etc., etc., for highest quality reproduction.

**Price £43.50  
inc. V.A.T. P & P**

S.A.E. for FREE brochure

We also still supply ALL components for the P.E. 'GEMINI' STEREO AMPLIFIER. Send 55p + 12p P&P for a full constructional booklet containing performance details, specification assembly instruction and fault finding guide.

**ELECTRO SPARES**

Dept. P.W.  
288, Ecclesall Road, Sheffield, S11 8PE

**LOW-COST I.C. MOUNTING** for any size DIL package. 100 Soldercon sockets 60p. 7 and 8 hole plastic supports 5p/pair. Quantity rates. SAE details and sample. Trial pack 60p. (P & P 10p/order). P.K.G. Electronics, Oak Lodge, Tansley, Derbyshire DE4 5FE.

**Synthesiser  
"Sounds  
Supreme"**

by **Dewtron** (25% VAT extra.)

Famous kits, e.g. waa-waa complete kit £4.50; Fuzz kit £6.50 P&P 25p under £10. Ring Modulator modules £11. "Mister Bassman" Bass Pedal Units and whole range of synthesiser modules, musical novelties, etc. Catalogue 20p from D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

**Books and Publications**

**T.V. REPAIRS MADE EASY**

4 easy to follow repair manuals cover the mono sets and 3 cover the colour sets from the early dual standards to date.

Priced at only £7.50 each, you just send make/model no. (chassis type if possible plus cost to receive manual covering the set by return. P & P 50p up to 3, £1 over 3.

British Colour T.V. Circuit Diagram Manuals in 2 vols. cross referenced to the above repair manuals at £8.50 (p. & p. £1) each. All mono sets circuits in 1 huge manual for same price.

**T.V. TECHNIC, 76 CHURCH ST., LARKHALL  
LANARKS ML9 1HE  
Tel. (0698) 883334.**

**START YOUR OWN BUSINESS  
REWINDING ELECTRIC MOTORS**

This unique instruction manual shows step by step how to rewind motors, working part or full time, without previous experience. Everything you need to know easily explained, including where to obtain materials, how to get all the work you need, etc. A goldmine of information and knowledge.

Only £3.65 plus 25p P&P.

**Magnum Publications Dept PWS**

Brinksway Trading Estate, Brinksway, Stockport SK3 9BZ.

Overseas Distributors wanted.

**Technical Books—  
Radio & Electronics**

World's Radio & TV Stations (International Edit.) £0-70  
**WORLD RADIO TV HANDBOOK 1976**  
 (Incorporating How to Listen to the World) ..... £5-00  
 Boys Book of Crystal Sets ..... £0-35  
 Television Timebase Circuits ..... £1-20  
 Radio TV and Industrial Tube & Valve Equip ..... £0-70  
 How to get the best out of your Tape Recorder ..... £1-70  
 Practical Electronic Science Projects ..... £0-85  
 Jack Darr's Service Clinic ..... £1-60  
 Transistor Circuits for Modern Test Equipment ..... £0-70  
 Modern Tape Recording Handbook ..... £0-85  
 1st Book of Transistor Equip. and Substitutes ..... £0-50  
 Hi Fi, PA & Disco Amplifier Design Handbook ..... £0-70  
 Radio Servicing Problems ..... £0-75  
 Electronic Circuits for the Amat Photographer ..... £0-87  
 52 Projects using IC 741 or Equivs ..... £0-85  
 TV Fault Finding ..... £1-15  
 Transis Circuits for Rad. Control'd Models ..... £0-50  
 Practical Stereo & Quadrophony Handbook ..... £0-85  
 Radio Amateur Operator's Handbook ..... £0-85  
 Coil Design & Construction Manual ..... £0-50  
 Radio TV & Electronics Data Book ..... £0-70  
 79 Electronic Novelty Circuits ..... £0-85  
 The Complete Car Radio Manual ..... £0-85  
 Radio Technicians Bench Manual ..... £3-40  
 Servicing Transistor Radio Receivers ..... £0-95  
 1st Book of Hi Fi Loudspeaker Enclosures ..... £0-50  
 2nd Book of Hi Fi Loudspeaker Enclosures ..... £0-70  
 Manual of Electronic Circuits for the Home ..... £0-60  
 Modern Crystal Set Circuits for Beginners ..... £0-45  
 Electronic Novelties for the Motorist ..... £0-60  
 2nd Book of Transistor Equip. & Substitutes ..... £1-10  
 Handbook of Electronic Musical Novelties ..... £0-60  
 Transistorised Novelties for Hi Fi Enthusiast ..... £0-45  
 Fault Location Exercises in Rad. & TV Vol. 1 ..... £1-00  
 Fault Location Exercises in Rad. & TV Vol. 2 ..... £1-60  
 Colour TV Picture Faults ..... £2-80  
 Practical Transistor Novelty Circuits ..... £0-50  
 Boys Book of Practical Radio & Electronics ..... £0-70  
 Radio Receiver Construction using ICs & Transis. .... £0-70  
 ICs & Transistor Gadgets Construction Handbook ..... £0-70  
 Integrated Circuits Equiv. & Substitutes Handbook ..... £0-85  
 Audio Technicians Bench Manual ..... £3-40  
 Radio Antenna Handbook for Long Dist. Receptn. .... £0-90  
 Guide to Printed Circuits ..... £3-40  
 Diode Characteristics Equiv. & Substitutes ..... £1-10  
 Electronic Gadgets & Games ..... £0-90  
**PRICES INCL. POST & PACKING** ..... Send S.A.E. for Lists

**RADIO BOOK SERVICE**  
40 Elwill Way, Beckenham BR3 2RZ

**Cassettes**

**LOW PRICE POSTAL SERVICE  
ALPHA COMPACT CASSETTES**

C60 — 35p C90 — 45p C120 — 55p  
 Low noise. Professional Quality.  
 Post 4p each. Minimum 16p. Maximum 60p.

Cambridge Technical Developments Ltd.  
8 Seymour Street, Cambridge

**ORDER FORM PLEASE WRITE IN BLOCK CAPITALS**

Please insert the advertisement below in the next available issue of Practical Wireless for ..... insertions. I enclose Cheque/P.O. for £.....  
 (Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).


NAME .....

ADDRESS .....

Send to: Classified Advertisement Manager  
**PRACTICAL WIRELESS, G.M.G. Room 2337,  
 King's Reach Tower, Stamford Street,  
 London SE1 9LS Telephone 01-291 5846**

Rate  
 14p per word, minimum 12 words. Box No. 35p extra.

Company registered in England. Registered No. 53626. Registered office: Tower House, 8/14 Southampton Street, London WC2E 9QX.

U.S.A. Govt. Electronics Engr. (retd.), W70E claims "VFA 5ft below ground, same as dipole; elevated 15ft., one "S" point UP on dipole."

# ABOVE ALL IT'S THE ANTENNA THAT MATTERS —TRANSMITTING AND RECEIVING!

MINIMUM RF LOSS and VERY LOW ANGLE FIRE ensures FURTHER MINIMUM SIGNAL LOSS from ionosphere and Earth Bounce, making DX—COMMONPLACE—with only MILLIWATTS of RF power, in spite of the present Sunspot minima. Send stamp for PROOF!

YOU just CANNOT AFFORD R.F. LOSSES — and S.W.L's, remember, the SAME antenna\* is used for RECEIVING the DX — YOU SURE CAN'T WORK 'EM — IF YOU CAN'T HEAR 'EM !! — the \*JOYSTICK V.F.A. — the \*QRP ANTENNA (230cm—7' 6") that handles ALL your R.F. — "FLEA POWER" or KILOWATT — EFFICIENTLY !!!

— AS SUPPLIED TO H.M. GOVT. COMMUNICATIONS H.Q. —

PRICES INCLUDE V.A.T. INSURANCE AND DELIVERY BY POST OR CARRIER

JOYSTICK V.F.A., £18.00; JOYMATCH A.T.U.'s:— 111 (Med. wave — 30 MHz), £18.00; 111A (1.6-30 MHz), £18.00; 111B (L match, 1.6-30 MHz), £16.20; LO-Z500 (1.8 thru 30 MHz, 500w), £23.35; "RC" (pre-production prototype "impossible" location A.T.U.—S.W. bands) £9.56; BUDGET LINE: A.T.U. 1.6-30 MHz, £8.90; A.T.U. Medium and S.W. bands, £8.90 (both in kit form, £7.40); Aerial Bandswitch (complete aerial system, medium and SW bands), £7.40; Artificial Earth, £7.40; DX CRYSTAL SET (Home and World-Wide reception) ready to use, £4.86; Comm. Headphones 8 ohm, £4.90; Field Strength Meter, £2.11; Set valves 9R59DS, £6.21; Coaxial cable 50 or 75 ohms, per 10 metres, £1.55; SYSTEM "A": VFA + 111B, £32.96; SYSTEM "X": VFA + either 111 or 111A, £34.47; SYSTEM "D": VFA + Aerial B'switch, £24.63; SYSTEM "J": VFA + LO-Z500 + F/S meter, £41.03; SYSTEM "RC": VFA + "RC", £27.56.

## PARTRIDGE SUPER PACKAGE

COMPLETE RADIO STATION FOR ANY LOCATION. Comprising: Trio QR666 Gen. Cov. RX, Headphones VFA., System "A", all connecting cables, del. (our risk). ASSEMBLED IN SECONDS!

£206.93

Send stamp for details and expert advice.

Just telephone your card number

BOX 5



Phone 0843 62535

(or 62839  
after office hours)

G3CED G3VFA



## H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

### 1976 "DX" RECEIVER

Complete kit—Price £6.00 (incl. p. & p. & V.A.T.). Customer writes: "I think the performance is astonishing for such an inexpensive and foolproof kit. I would wholeheartedly recommend this kit to anyone, however inexperienced, as an antidote to T.V.-itis, and as an entry into a fascinating hobby".

This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.

Send stamped envelope for details.  
"H.A.C." SHORT-WAVE PRODUCTS  
P.O. BOX No. 16, EAST GRINSTEAD,  
SUSSEX RH19 3SN

## FREE Brochure on New KITS



Whether professional, student, teacher or amateur the field of electronics can open up a new world for you.

Please send to: 12 150 stamp addressed envelope

CROFTON don't just sell kits, we offer you a technical back up service to ensure your success

The following is a selection of some of the more popular kits...

- ★ Mullard CCTV Camera
- ★ PE CCTV Camera
- ★ 'Mistral' Digital Clock Kit £12.50 incl. VAT. p. & p. 50p. Made up £18.00 incl. VAT. p. & p. 50p
- ★ Electronic Ignition
- ★ Sound Operated Flash
- ★ PW Tele-Tennis Game
- ★ UHF Modulator
- ★ Bench Power Supply
- ★ Wobbulator
- ★ All ETI Top Projects
- ★ Many of the Elektor Projects

NOTE PCBs for most published projects available to order

### CROFTON ELECTRONICS LTD

Dept. B, 35 Grosvenor Road, Twickenham, Middx. Tele. 01-891 1923

## 4 STATION INTERCOM



£17.25

Solve your communication problems with this

4-Station Transistor Intercom system (1 master and 3 Subs). In robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 75p.

### MAINS INTERCOM NEW MODEL

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On off switch and volume control. Price £31.24 per pair P. & P. 75p.

## NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



£12.95

VAT £1.04

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/Off switch, volume. Direct tape recording model at £13.95 + VAT £1.12 P. & P. 70p. 10-day price refund guarantee.

WEST LONDON DIRECT SUPPLIES (PW5)  
160 KENSINGTON HIGH STREET, LONDON, W8

# WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD HERTS, ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 37774

**ALL DEVICES BRAND NEW AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 25p\* TO ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST, AIR/SURFACE. (SEND 25p FOR OUR CATALOGUE).**

**VAT** Applicable to U.K. Customers only. All prices are exclusive of VAT. Please add 8% to devices marked\* To the rest add 25%.

Callers welcome to our retail shop at 33, Cardiff Road, behind Watford Football Ground, Monday to Saturday. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type. (Values are in  $\mu$ F).  
400V: 0-001, 0-0012, 0-0015, 0-0018, 0-0022, 0-0033 5p; 0-0047, 0-0068, 0-01, 0-015, 0-022 8p; 0-033, 0-047, 0-068 8p; 0-1, 0-15, 0-22, 10p; 0-33, 0-47, 18p.  
160V: 0-1, 0-15 4p; 0-22 5p; 0-33 6p; 0-47 10p; 0-68 15p; 1-0 18p; 1-5 20p; 2-2 24p; 4-7 28p  
**DUBLIER:** 1000V: 0-01, 14p; 0-022, 15p; 0-047, 16p; 0-1, 19p; 0-47 43p.

**POLYESTER RADIAL LEAD P.C. TYPE** (Values are in  $\mu$ F).  
250V: 0-01, 0-015, 0-022 5p; 0-033, 0-047, 0-068, 0-1 5p; 0-15 7p; 0-22, 0-33 9p; 0-47 10p; 0-68 14p; 1-0 19p; 1-5 24p; 2-2 28p.

**ELECTROLYTIC CAPACITORS:** Axial lead type. (Values are in  $\mu$ F).  
250V: 1000 $\mu$ F, 40p; 100V: 20, 6p; 63V: 0-47, 1-0, 1-5, 2-2, 5, 3-3, 4-7, 6-8, 8, 10, 15, 22, 33, 47, 68, 100, 12p; 50V: 1-0, 6p; 2-2, 15p; 1000, 42p; 40V: 33, 100, 8p; 470, 22p; 2200 40p; 35V: 1000, 38p; 30V: 3500, 41p; 25V: 8, 10, 22, 40 6p; 80, 100, 160 8p; 220, 13p; 470, 17p; 640, 21p; 1000, 27p; 2200, 34p; 3000, 39p; 4700, 47p; 16V: 10, 40, 125, 250, 8p; 470, 11p; 1000, 150p, 18p; 4700, 46p; 10V: 4, 100, 8p; 640, 10p; 1000, 14p; 2200, 18p. **TAG-END TYPE:** 70V: 2500, 98p; 4700, 111p; 50V: 2000, 72p; 25V: 4700, 48p; 16V: 4700, 36p.

**TANTALUM BEAD CAPACITORS:** Axial lead type. (Values are in  $\mu$ F).  
35V: 0-1 $\mu$ F, 0-22, 0-33, 0-47, 0-68, 1-0, 2-2 $\mu$ F, 3-3, 4-7, 6-8, 25V: 1-5, 10, 18V: 10 $\mu$ F, 22, 10V: 10 $\mu$ F, 33, 6V: 47 $\mu$ F. Price: 11p each.

**NYLAR FILM CAPACITORS**  
100V: 0-001, 0-002, 0-005, 0-01 $\mu$ F 4p  
0-015, 0-02, 0-04, 0-05 $\mu$ F, 0-1 $\mu$ F 5p  
0-15, 0-2 50V: 0-47 $\mu$ F 6p

**CERAMIC CAPACITORS**  
50V d.c. Plaque type 25mm leads.  
Range: 0-5pF to 10,000pF 3p  
0-015 $\mu$ F, 0-022 $\mu$ F, 0-033 $\mu$ F, 0-047 $\mu$ F 4p

**JACKSONS VARIABLE CAPS.**  
Dielectric 0-1 36pF 240p  
100/300pF 86p 0-2 385pF 240p  
500/50pF 85p 0-208/176 240p  
'D' 2 speed with slow  
Drive unit motion drv. 280p  
& coupling knobs C804 5, 10, 15, 20,  
6-1 Ball Drive 100, 150pF 195p  
4511/DAF 87p 'L' 3x310pF 372p  
Drum 54mm 30p 0-3x25pF 323p

**CERAMIC TRIMMER CAPACITORS**  
2-7pF, 4-15pF, 6-25pF: 8-30pF 17p each  
**MINIATURE**  
3-10pF, 3-30pF: 10-40pF 15p

**60p COMPRESSION TRIMMERS**  
3-40pF 18p  
20-250pF 27p  
100-500pF 32p  
1250pF 45p

**SILVER MICA**  
4-7, 6-8, 12, 18, 22, 33, 50, 82, 85, 100, 120, 250pF 330pF 7p each

**DENCO COILS**  
Dual Purpose 'DP' Rng. 1-5 B.Y.R.W. 69p  
6-7 B.Y.R. 60p  
1-5 Green 74p  
Transistor Tuning coils 'T' Type Rng. 1-5 B.Y.R. W 78p  
RFC 5 choke 76p  
IFT 13/14/15/16/17 70p  
IFT 18/465 of 1-6m 80p  
TOC 1 75p  
MW 5F.R. 72p  
MW/LF 5FR 94p

**EARPHONES**  
Magnetic 2-5mm plug 15p  
3-5mm plug 15p  
Crystal 3-5mm plug 30p

**SPEAKERS**  
8 0-3W 23", 21", 3" 56p  
64 2 1/2" 60p

**POTENTIOMETERS (AB or EGEM)**  
Carbon Track, 0-25W Log & 0-5W Lin values  
1K  $\Omega$  (LIN. ONLY) Single gang 17p  
5K $\Omega$ -2M $\Omega$  single gang 10p  
5K $\Omega$ -2M $\Omega$  single gang D/P switch 37p  
5K $\Omega$ -2M $\Omega$  dual gang stereo 50p

**SLIDER POTENTIOMETERS**  
0-25W log and linear values 50mm  
5K $\Omega$ -500K $\Omega$  single gang 40p  
10K $\Omega$ -500K $\Omega$  Dual gang 52p  
50K $\Omega$  Lin 150mm WS 150 £3-00

**RESISTORS-Erie make**  
Carbon, Miniature, High Stability, Low Noise  
POWER Tol. RANGE Val. 1-99 100+  
0-25W 5% 2-2 $\Omega$ -4-7M E24 1p 0-8p  
0-5W 5% 2-2 $\Omega$ -4-7M E12 1p 0-8p  
1W 5% 2-2 $\Omega$ -10M E12 3p 2p  
100 off price per value not mixed.



**RHYTHM GENERATOR**  
Build this PW (May & June '76) Easy build Low cost Rhythm Generator. We are the sole suppliers of the complete Kit including the Case, predrilled printed front Panel and the three Fibre-glass P.C. Boards. Price including VAT Complete Kit £41-85 (p.&d. and insur. £1-00) Ready Built £48-85 (available in limited quantity) P&P 1-00 Send SAE for complete list. (Demonstration on at our retail shop)

**VEROBOARD\*** Pitch 0-1 0-15 0-15 (copper clad) (plain)  
2 1/2 x 3 1/2" 32p 24p 15p  
2 1/2 x 5" 35p 35p 20p  
2 1/2 x 3 1/2" 35p 35p 15p  
3 1/2 x 5" 49p 41p 25p  
2 1/2 x 17" 105p 73p 60p  
4 1/2 x 17" 145p 115p 75p  
3 1/2 x 17" 185p — 110p  
Pkt of 36 pins 22p  
Spot face cutter 52p  
Pin insertion tool 72p

TRANSISTORS		BD139*		OC29*		TIS43		2N2906*	
AC125*	D	BD140	45	OC35*	54	TIS44	25	2N2907*	
AC126*	14	BD145*	55	OC36*	58	TIS107	12	2N2907A	
AC127*	14	BD150	55	OC41	18	ZTX108	12	2N2908	
AC128*	14	BD154	20	OC42	18	ZTX109	13	2N29260	
AC141*	24	BF115*	22	OC44	18	ZTX300	14	2N2926R	
AC142*	24	BF177	26	OC45	18	ZTX301	14	2N2926Y	
AC146*	25	BF178*	28	OC70	17	ZTX302	18	2N3011	
AC176*	14	BF179*	33	OC71	17	ZTX303	15	2N3053*	
AC187*	14	BF180	33	OC74	28	ZTX304	24	2N3054*	
AC193*	15	BF190	12	OC76	37	ZTX311	13	2N3055*	
AC197*	35	BF184	32	OC81	18	ZTX341	19	2N3614*	
ACY18	28	BF185	30	OC81D	24	ZTX300	14	2N3615*	
ACY19	25	BF194	10	OC82	18	ZTX501	13	2N3702	
ACY20	24	BF195	10	OC83	28	ZTX502	18	2N3703	
ACY21	29	BF196	14	OC84	34	ZTX503	14	2N3704	
ACY22	16	BF197	15	OC130	190	ZTX504	47	2N3705	
ACY39	78	BF244	12	OC141	157	ZTX505	28	2N3706	
AD140*	48	BF256*	32	OC201*	80	2N698*	13	2N3707	
AD149*	48	BF257*	32	OC202*	90	2N706*	12	2N3710	
AD161*	35	BF258*	35	TIC44*	30	2N708	15	2N3711	
AD162*	35	BF259*	35	BF39	30p	TIP29	43	2N3712*	
Mtch. pr.*	60	BF30	30p	BF40	30p	TIP29A	45	2N3717*	
AF115*	18	BF42	28	BF43	28	TIP29C	48	2N3737*	
AF116*	18	BF44	28	BF45	28	TIP29D	68	2N3738*	
AF117*	18	BF46	28	BF47	28	TIP30	52	2N3819	
AF121*	33	BF48	28	BF49	28	TIP30A	54	2N3820	
AF124*	30	BF50	25	BF51	25	TIP30B	64	2N3821	
AF125*	30	BF52	25	BF53	25	TIP30C	64	2N3822	
AF126*	30	BF54	25	BF55	25	TIP31	54	2N3823	
AF127*	30	BF56	25	BF57	25	TIP31A	58	2N3824	
AF139*	33	BF58	25	BF59	25	TIP31B	70	2N3825	
AF178	49	BF60	25	BF61	25	TIP31C	84	2N3826	
AF179	59	BF62	28	BF63	28	TIP32	84	2N3827	
AF180	55	BF64	28	BF65	28	TIP32A	88	2N3828	
AF181	55	BF66	28	BF67	28	TIP32B	88	2N3829	
AF186	60	BF68	28	BF69	28	TIP32C	99	2N4058	
AF186	60	BF70	28	BF71	28	TIP33	99	2N4061	
AF239	34	BF72	28	BF73	28	TIP33B	112	2N4871	
AF252	31	BF74	28	BF75	28	TIP33C	112	2N4872	
ASV29	40	BF76	28	BF77	28	TIP33D	112	2N4873	
ASV29	40	BF78	28	BF79	28	TIP34	110	2N4874	
BC107	9	BF80	28	BF81	28	TIP34A	115	2N4875	
BC108*	12	BF82	28	BF83	28	TIP34A*115	115	2N4876	
BC108*	12	BF84	28	BF85	28	TIP34B	167	2N4877	
BC109*	12	BF86	28	BF87	28	TIP34B*167	167	2N4878	
BC109*	12	BF88	28	BF89	28	TIP35	250	2N6027*	
BC117	20	BF90	28	BF91	28	TIP35A	270	2N6028*	
BC147	7	BF92	28	BF93	28	TIP36	330	3N140*	
		BF94	28	BF95	28	TIP36A	330	3N141*	
		BF96	28	BF97	28	TIP36A*	330	3N142*	
		BF98	28	BF99	28	TIP36B	330	3N143*	
		BF100	28	BF101	28	TIP36B*	330	3N144*	
		BF102	28	BF103	28	TIP36C	330	3N145*	
		BF104	28	BF105	28	TIP36C*	330	3N146*	
		BF106	28	BF107	28	TIP36D	330	3N147*	
		BF108	28	BF109	28	TIP36D*	330	3N148*	
		BF110	28	BF111	28	TIP36E	330	3N149*	
		BF112	28	BF113	28	TIP36E*	330	3N150*	
		BF114	28	BF115	28	TIP36F	330	3N151*	
		BF116	28	BF117	28	TIP36F*	330	3N152*	
		BF118	28	BF119	28	TIP36G	330	3N153*	
		BF120	28	BF121	28	TIP36G*	330	3N154*	
		BF122	28	BF123	28	TIP36H	330	3N155*	
		BF124	28	BF125	28	TIP36H*	330	3N156*	
		BF126	28	BF127	28	TIP36I	330	3N157*	
		BF128	28	BF129	28	TIP36I*	330	3N158*	
		BF130	28	BF131	28	TIP36J	330	3N159*	
		BF132	28	BF133	28	TIP36J*	330	3N160*	
		BF134	28	BF135	28	TIP36K	330	3N161*	
		BF136	28	BF137	28	TIP36K*	330	3N162*	
		BF138	28	BF139	28	TIP36L	330	3N163*	
		BF140	28	BF141	28	TIP36L*	330	3N164*	
		BF142	28	BF143	28	TIP36M	330	3N165*	
		BF144	28	BF145	28	TIP36M*	330	3N166*	
		BF146	28	BF147	28	TIP36N	330	3N167*	
		BF148	28	BF149	28	TIP36N*	330	3N168*	
		BF150	28	BF151	28	TIP36O	330	3N169*	
		BF152	28	BF153	28	TIP36O*	330	3N170*	
		BF154	28	BF155	28	TIP36P	330	3N171*	
		BF156	28	BF157	28	TIP36P*	330	3N172*	
		BF158	28	BF159	28	TIP36Q	330	3N173*	
		BF160	28	BF161	28	TIP36Q*	330	3N174*	
		BF162	28	BF163	28	TIP36R	330	3N175*	
		BF164	28	BF165	28	TIP36R*	330	3N176*	
		BF166	28	BF167	28	TIP36S	330	3N177*	
		BF168	28	BF169	28	TIP36S*	330	3N178*	
		BF170	28	BF171	28	TIP36T	330	3N179*	
		BF172	28	BF173	28	TIP36T*	330	3N180*	
		BF174	28	BF175	28	TIP36U	33		

**WATFORD ELECTRONICS** (Continued from other side)

<b>CHOKE</b> Miniature 00mH 20p	<b>FOOT SWITCH*</b> + Pedal £2-80	<b>Connectors*</b> Snap on PPs 6p Snap on PPs 9p	<b>JACK PLUGS</b>		<b>SOCKETS</b>	
		2 5mm 3 5mm Std. MONO Std. STEREO	Screened chrome 10p 14p 19p 32p	Plastic body 10p 14p 13p 18p	Open metal 8p 10p 13p 15p	Moulded with break contacts 17p 22p
<b>NOBS*</b> fits 1/2" shaft th grub screw, except (push fit) & K8 (for iders).			<b>DIN</b>		<b>Plugs</b>	
Black or White pointer type Slim silvered aluminium Black 1 1/2" with chrome rim Black serrated. Metal top with line indicator 33mm diam. Black fluted metal top and skirt calibrated 0-10. 37mm diam. PK2 as K5, pointer on skirt Black, knurled, tapered. Metal top & skirt. Calib. 0-10, 30mm Black or silvered for slider pot		9p 10p 15p 20p 22p 22p 8p	2 pin Loudspeaker 3, 4, 5 (180° & 240°)	12p	Sockets	
<b>ANEL METERS*</b> Full scale x 46 x 35mm req. 1 1/2" hole			<b>CO-AXIAL (TV)</b>		10p 8p	
50µA 0-100mA 100µA 0-500mA 500µA 0-1 Amp 1mA 0-50V DC 1mA 0-300V DC 10mA "S" 10mA "VU"	50µA-0-50µA 100µA-0-100µA 500µA-0-500µA £3-95 each EDGWISE 89 x 32 x 70mm 0-1mA, 0-500µA Price £4-14		<b>PHONO</b> assorted colours Metal screened		7p 5p (Single) 12p 10p (Triple)	
<b>TRANSFORMERS MAINS</b> (p&p)			<b>BANANA</b> 4mm 2mm		6p 7p 7p 7p	
many 220-240V -6 (Miniature) 100mA -9 (Miniature) 100mA 0-12 (Miniature) 100mA 2-0-22 500mA 0-15 100mA 24-20-15-12-0 (MT79AT) 1A* 24-20-15-12-0 2A* 0-18V 1A* 0-15 1A* V 1A* 2-0-12 500mA 0-12 1A* Pulse Transformer 1:1 44 Mini Driv. Pri 20K Sec 1K 700 Mini O/P Pri 1-2K Sec 3-2Ω 1T Mini O/P Pri 1-2K Sec 8Ω	50p 90p 90p 195p (20) 225p (48) 340p (62) 230p (20p) 195p (48) 330p (48) 237p (48) 185p (48) 110p 54p 54p 42p	<b>LAMP HOLDERS AND LAMPS*</b>				
		<b>LES HOLDER</b> Dome shaped, Red, Blue, Green, Yellow, White		14p		
		<b>LES BULBS</b> 6v and 12v		7p		
		<b>MES HOLDERS</b> Chrome cover, Red or Amber, Jewelled top		50p		
		<b>MES BULBS</b> 3-5V 6V 12V		7p		
		<b>NEONS</b> Mains. Sealed with Resistor. Sq. Top, Red or Grn. Round Top Red 21p Neon with leads, 95V AC (No resistor) 9p				
		<b>SWITCHES*</b>		<b>SLIDE 250V:</b>		
		<b>TOGGLE:</b> 2A, 250V		1A DP 10p		
		<b>SPST 20p</b>		1A DP C/O 12p		
		<b>DPDT 24p</b>		1A DP 8p		
		<b>SUB-MIN TOGGLE</b>		<b>PUSH BUTTON</b>		
		SP changeover 45p		Spring loaded		
		SPST on/off 40p		SPST on/off 55p		
		DPDT 6 tag 84p		SPDT C/over 85p		
		DPDT Centre off 80p		DPDT 6 Tag 85p		
		<b>SWITCHES* PUSH BUTTON:</b>				
		Push on/Push off, spring loaded		44p		
		Miniature Non Locking		15p		
		Push to Make		25p		
		Push to Break		25p		
		<b>ROCKER</b> (white): 10A 250V		25p		
		SP changeover centre off		20p		
		<b>ROCKER:</b> (black) on/off 10A 250V		46p		
		<b>ROCKER:</b> illuminated (white)		26p		
		lights when on. 3A 240V				
		<b>ROTARY:</b> 1p/12w, 2p/6w, 2p/2w, 2p/4w, 3p/3w, 3p/4w, 4p/2w, 4p/3w				

**TECHNICAL TRAINING IN ELECTRONICS TELEVISION AND RADIO SERVICING**

ICS can provide the technical knowledge that is so essential to your success, knowledge that will enable you to take advantage of the many opportunities open to the trained person. You study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

- City & Guilds Certificates:**  
**Telecommunications Technicians**  
**Radio, TV, Electronics Technicians**  
**Technical Communications**  
**Radio Servicing Theory**  
**Radio Amateurs**  
**Electrical Installation Work**  
**MPT Radio Communications Certificate**

- Diploma Courses:**  
**Colour TV Servicing**  
**Electronic Engineering and Maintenance**  
**Computer Engineering and Programming**  
**Radio, TV, Audio Engineering and Servicing**  
**Electrical Engineering, Installation and Contracting**

**POST OR PHONE TODAY FOR FREE BOOKLET.**

**ICS To: International Correspondence Schools**

Dept. No. 7775, Intertext House, LONDON SW8 4UJ or telephone 622 9911

Subject of Interest: \_\_\_\_\_  
 Name: \_\_\_\_\_  
 Address: \_\_\_\_\_  
 Tel: \_\_\_\_\_

**INDEX TO ADVERTISERS**

Alben Engineering ... .. 16	Flairline Supplies ... .. 84	Radio Component Specialists ... .. 80
Ambit International ... .. 40	G.T. Technical Information Service ... .. 90	Radio Book Service ... .. 92
Antex Ltd. ... .. 75	Garfields ... .. 91	Radio Exchange Ltd. ... .. 23
A.S.P. Ltd. ... .. 68	Golding Ltd. ... .. 61	Ramar Construction Services ... .. 91
Audio-Optics ... .. 89	Greenbank Electronics ... .. 77	Radio Society of G.B. ... .. 20
A.H. Supplies ... .. 22	Greenwell Electronics ... .. 64	R.S.C. (Hi-Fi) ... .. 2, 3
	Grimsby Electronics ... .. 89	R.S.T. Valve Mail Order Co. ... .. 39
		Radio & T.V. Components Ltd. ... .. 14, 15
		Riversdale ... .. 87
Bamber, B. ... .. 81	H.A.C. Short-Wave Supplies ... .. 93	Salop Electronics ... .. 91
Barclay Electronics ... .. 83	H.M. Electronics ... .. 91	Saxon Entertainments Ltd. ... .. 7
Barrie Electronics ... .. 6	Harverson Surplus ... .. 17	Scientific Wire Company, The ... .. 91
Bentley Acoustic Corp. Ltd. ... .. 8	Helme Audio ... .. 91	Simech Engineering Ltd. ... .. 90
B. H. Component Factors Ltd. ... .. 72	Henry's (Radio) Ltd. ... .. 22	Sinclair Radionics Ltd. ... .. 52, 53
Bi-Pak Ltd. ... .. 10, 11	Home Radio Components Ltd. ... .. 21	Sintel ... .. 76
Bi-Pre-Pak Ltd. ... .. 19		Southern Valve Co. ... .. 18
Blrket, J. ... .. 81	I.L.P. Electronics Ltd. ... .. 9	Stereo Cassette Lending Library ... .. 90
Boffin Projects ... .. 91	Integrex Ltd. ... .. 68	Surpletronics ... .. 72
British Institute of Engineering Technology ... .. 18, 64, 82	Intertext I.C.S. ... .. 95, 90	Swanley Electronics ... .. 87
British National Radio & Electronics School ... .. 6, 67	Kensington Supplies ... .. 90	
J. Bull (Electrical) Ltd. ... .. 85	Kinnie Components ... .. 40	Tape Talk ... .. 90
Bywood Electronics ... .. 84		T.V. Technical Publications ... .. 92
	Lasky's Radio ... .. 2, 12	Technomatic Ltd. ... .. 86
	Lewis Radio ... .. 64	Teleradio Electronics ... .. 91, 92
	Linear Products ... .. 63	Time Micro Electronics ... .. 71
	Lynx Electronics ... .. 16	Trampus Electronics ... .. Cover ii
		Tuac Ltd. ... .. 4, 5
	M.C.L. ... .. 89	
	Manor Supplies ... .. 81	Vero Electronics ... .. 87
	Magnetic Components Ltd. ... .. 70	
	Magnum Publications ... .. 92	Watford Electronics ... .. 94, 95
	Maplin Electronic Supplies ... .. Cover iv	Web Europa ... .. 36
	Marco Trading ... .. 89	Wentworth Radio ... .. 89
	Marshall, A. & Sons ... .. 12	West London Direct Supplies ... .. 93
	Mawson Associates ... .. 89	Michael Williams Electronics ... .. 72
	Milward, G. F. ... .. 63	Wilmslow Audio ... .. 13
	Minikits Electronics ... .. 91	Wrights, S. G. ... .. 63
	Newmart Electronics ... .. 20	Xeroza Radio ... .. 84
	Orchard Electronics ... .. 6	Z. & I. Aero Services ... .. 96
	Partridge Electronics Ltd. ... .. 93	
	P.B. Electronics ... .. 77	
	Pulse Electronics ... .. 8	
	Precision Petite ... .. 86	



# CHROMASONIC electronics

Dept. 1 56, Fortis Green Road,  
Muswell Hill, London, N10 3HN.  
telephone: 01-883 3705

## C - MOS

Part No.	1-24	25-99	100up
CD4000AE	19p	17p	14p
CD4001AE	19p	17p	14p
CD4002AE	19p	17p	14p
CD4003AE	£1.75	£1.33	£1.06
CD4007AE	23p	19p	15p
CD4008AE	£1.75	£1.46	£1.17
CD4009AE	Use	CD4049*	
CD4010AE	Use	CD4050*	
CD4011AE	19p	17p	14p
CD4012AE	19p	17p	14p
CD4013AE	59p	50p	46p
CD4014AE	£1.75	£1.46	£1.17
CD4015AE	£1.75	£1.46	£1.17
CD4016AE	55p	48p	44p
CD4017AE	£1.29	£1.07	93p
CD4018AE	£1.89	£1.56	£1.25
CD4019AE	80p	65p	53p
CD4020AE	£1.97	£1.64	£1.31
CD4021AE	£1.97	£1.64	£1.31
CD4022AE	19p	17p	14p
CD4027AE	£1.83	£1.53	£1.27
CD4028AE	£1.26	£1.05	84p
CD4025AE	19p	17p	14p
CD4076AE	£2.79	£2.32	£1.86
CD4077AE	98p	82p	65p
CD4078AE	£1.89	£1.56	£1.15
CD4079AE	£1.89	£1.56	£1.15
CD4030AF	71p	59p	47p
CD4035AE	£1.75	£1.46	£1.17
CD4040AE	£2.01	£1.69	£1.34
CD4047AE	£1.49	£1.24	99p
CD4066AE	£2.15	£1.79	£1.44
CD4067AE	69p	56p	46p
CD4068AE	69p	56p	46p
CD4051AE	£2.78	£2.32	£1.85
CD4052AE	£2.78	£2.32	£1.85
CD4056AE	£2.12	£1.76	£1.41
CD4060AE	£2.39	£1.99	£1.55
CD4066AE	£1.13	94p	75p
CD4068AE	28p	24p	19p
CD4069AE	28p	24p	19p
CD4070AE	28p	24p	19p
CD4071AE	28p	24p	19p
CD4072AE	28p	24p	19p
CD4073AE	28p	24p	19p
CD4074AE	28p	24p	19p
CD4075AE	28p	24p	19p
CD4076AE	28p	24p	19p
CD4077AE	28p	24p	19p
CD4078AE	28p	24p	19p
CD4079AE	28p	24p	19p
CD4080AE	28p	24p	19p
CD4081AE	28p	24p	19p
CD4082AE	28p	24p	19p
CD4083AE	28p	24p	19p
CD4084AE	28p	24p	19p
CD4085AE	28p	24p	19p
CD4086AE	28p	24p	19p
CD4087AE	28p	24p	19p
CD4088AE	28p	24p	19p
CD4089AE	28p	24p	19p
CD4090AE	28p	24p	19p
CD4091AE	28p	24p	19p
CD4092AE	28p	24p	19p
CD4093AE	28p	24p	19p
CD4094AE	28p	24p	19p
CD4095AE	28p	24p	19p
CD4096AE	28p	24p	19p
CD4097AE	28p	24p	19p
CD4098AE	28p	24p	19p
CD4099AE	28p	24p	19p
CD4100AE	28p	24p	19p

## I.C. SOCKETS

Pin Sockets, pins in strips of 100. Just snap off what you need. 65p per strip.

Dual in line

8 pin 13p	24 pin 26p	105
14 pin 15p	28 pin 31p	8 pin 31p
16 pin 15p	36 pin 39p	10 pin 35p



## FREE CIRCUITS

Our 8 Page A4 Audio I.C. Booklet is supplied FREE with purchases of Linear I.C.'s worth £1.00 or more. (35p. if sold alone) Contains circuits and pin connections.

15 Amplifiers 250 mW to 20 watts

5 Audio Pre-Amplifiers

1 Tape Pre-Driver

1 Instrument Amplifier (Bifer)

1 General Purpose Mini Amplifier

1 D.C. Controlled Gain Control

1 Micro-mini radio (2 I.C.'s)

## PHOTO-DARLINGTON

Vcc0 25v 2N5777  
Vcc0 25v  
Vcc0 8v  
Pd 250 mA  
Pc 200 mW  
Hie 2500

35p

## LINE-O-LIGHT

NEW LED linear cursors each device contains 10 light emitting diodes in a 20 pin dual in-line package. Ideal for solid state analogue meters or dials. Type 101 RED £2.76. Complete with leaflet.




## LINEAR I.C.'s

555 (8 pin dip) V	55p	AY-1-0212	£6.93	LM2111	£1.12	SN76001N (TAA611)	£1.82
555 (10-99T)	81p	AY-1-5051	£1.44	LM3900	89p	SN76003N	£3.30
556 (14 pin dip)	£1.29	AY-5-1224	£3.95	LM3909	66p	SN76013N	£1.98
703 (RF/IF Ampl)	68p	AY-5-3500	£6.59	MC1303L	£1.94	SN76023N	£1.98
709 (8 pin dip)	38p	AY-5-3507	£6.59	MC1306P	85p	SN76227NIMC13271	£1.89
709 (10-99)	45p	AY-5-4007	£7.94	MC1310P	£2.10	SN76537N	£1.81
709 (14 pin dip)	39p	BHA0002	£3.01	MC1312P	£2.52	SN76550-2(TAA550)89p	
710 (8 pin dip)	39p	CA2111	£3.01	MC1314P	£4.34	SN76552-2	81p
710 (10-99)	45p	CA3045	£1.19	MC1315P	£4.85	SN76660N(TBA120)	75p
710 (14 pin dip)	44p	CA3046	£1.69	MC1327P	£1.48	SN76666N (CA3065)	£1.12
711 (10-99)	44p	CA3053	88p	MC1330P	89p	TAA963	£1.50
711 (14 pin dip)	44p	CA3065	59p	MC1350	68p	TAA970	£2.16
720 (A, A, B, R, A)	£1.76	CA3065	£1.60	MC1351	92p	TAA970A	£1.87
723 (10-99)	£1.09	CA3075	£1.44	MC1352	92p	TAA970	£2.75
723 (14 pin dip)	55p	CA3078	£1.26	MC1357	£1.60	TAA970	£2.43
741 (8 pin dip)	30p	CA3080	£1.86	MC1358	£1.60	TAA970	£2.43
741 (10-99)	43p	CA3081	£1.86	MC1375	£1.23	TAA970	£3.45
741 (14 pin dip)	36p	CA3082	£1.86	MC1455(555T)	65p	TAA970	£2.75
747 (14 pin dip)	£1.04	CA3089E (TDA1200)	£2.43	MC1456CG	£1.77	TAA970	£5.03
748 (8 pin dip)	42p	CA3120E	£1.76	MC1458CP1	89p	TAA970	£2.75
748 (10-99)	46p	CA3130	84p	MC1468G	£2.30	TBA1205	£1.25
748 (14 pin dip)	49p	CA3130E	84p	MC1495L	£4.48	TBA231	£1.02
753 (F, M, 1st, 1, F)	£1.08	CA3401E (LM3900)	68p	MC1496G	£1.01	TBA281 (723)	£2.59
75491	88p	CA3600E	£1.44	MC3201P	£1.85	TBA281	£3.16
75492	£1.10	C17001	£5.34	MC3401P	81p	TBA281	£3.85
Regulators 100 mA		LM0051 (10-3)	£1.46	MFC4000B	87p	TBA281	£3.29
78105WC (10-92)	60p	LM0361 (10-3)	£1.46	MFC4005A	85p	TBA281	£3.29
7812WC (10-92)	60p	LM0371 (10-3)	£1.46	MFC6030A	85p	TBA281	£3.29
7815WC (10-92)	60p	LM129 (10T-32)	85p	MFC6040A	£1.01	TBA281	£3.29
Regulators 100mA		LM130 (10T-32)	85p	MM5314	£4.80	TBA258	£1.03
781505WC (TBA625A)	90p	LM131 (10T-32)	85p	MM5316	£9.99	TBA258	£1.03
7812A2WC (TBA625B)	90p	LM3011 (10-99)	65p	MVRSV	£1.45	TBA258	£1.03
7815A2WC (TBA625C)	90p	LM3015 (8 pin dip) 57p		MVR12V	£1.45	TBA258	£2.79
Regulators 500mA		LM301A (10-99)	67p	MVR15V	£1.45	TBA258	£2.79
78M05HC	£1.35	LM301A (SIB pin dip) 59p		MVR15V (T0-3)	£1.45	TBA258	£1.21
78M10HC	£1.35	LM307 T (10-99)	59p	NE5401	£1.25	TBA258	£1.21
78M15HC	£1.35	LM307 S (8 pin dip)	57p	NE546A	£1.25	TBA258	£1.21
78M18HC	£1.35	LM308 T (10-99)	£1.96	NE555V	89p	TBA258	80p
78M24HC	£1.35	LM308A T (10-99)	£7.92	NE556	£1.29	TBA258	£4.71
Regulators 1A		LM308A S (8 pin dip) 6.90		NE560B	£5.06	TBA258	£4.71
7805KC (10-3)	£2.09	LM309K	£2.34	NE561B	£5.06	TBA258	£4.71
7817KC (10-3)	£2.09	LM339	£2.25	NE562B	£5.06	TBA258	£4.71
7818KC (10-3)	£2.09	LM370N	£2.85	NE563B	£2.96	TBA258	£4.71
7818KC (11-3)	£2.09	LM371	£2.08	NE565N	£2.63	TBA258	£4.71
7824KC (10-3)	£2.09	LM372	£2.08	NE566V	£1.87	TBA258	£4.71
Regulators 1A		LM373	£2.08	NE567V	£2.63	TBA258	£4.71
7815UC (10-220) £1.72		LM377N	£1.99	SD6000	£1.22	TDA1054	£1.25
7817UC (10-220) £1.72		LM378N	£2.99	SL414A	£2.09	TDA1200	£2.43
7818UC (10-220) £1.72		LM379N	£2.71	SL415A	£2.75	TDA1405	80p
7819UC (10-220) £1.72		LM380	£1.25	SL437D	£7.50	TDA1412	80p
7824UC (10-220) £1.72		LM381	£1.85	SL440	£2.84	TDA1415	80p
7840UC (10-220) £1.72		LM382	£1.66	SN75491N	88p	TDA2010	£3.00
ICL8030	£3.52	LM1820	£1.03	SN75492N	£1.10	TDA2020	£3.75

ZN414 Leaflet free with devices (10p alone)  
MC1310, 2, 4 & 5 Leaflet free with devices (10p alone)

## 3 1/2 DECADE DVM I.C.

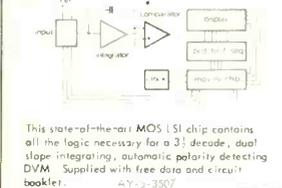


OUR PRICE ONLY £6.59  
(Data and Circuit) Booklets alone 70p

## The AY-51224 tick-tock

Another marvel from G. A 16 pin 12-74Hz clock I.C. with 25 pin capability and low external parts count. Supplied with manufacturers detailed leaflet £3.95p (inc. VAT) Leaflet alone 20p. Full Kit (including case) available to order. (excl 1975. Phone Clive for details)
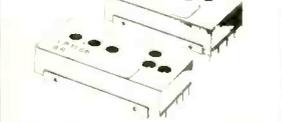
## MULLARD MODULES

Still make the simplest, highly reliable F.M. tuner.




LP1186 Varactor front end	£8.60
LP1185 I.F. Strip	£6.95
LP1400 Multiplex decoder	£9.02

## 74 TTL


Part No.	1-24	25-99	100
7400	14p	12p	10p
7401	14p	12p	10p
7402	14p	12p	10p
7403	14p	12p	10p
7404	16p	13p	11p
7408	16p	13p	11p
7409	16p	13p	11p
7410	16p	13p	11p
7413	16p	13p	11p
7417	27p	22p	20p
7418	27p	22p	20p
7420	16p	13p	11p
7427	27p	22p	18p
7430	16p	13p	11p
7432	27p	22p	18p
7433	27p	22p	18p
7441	75p	62p	60p
7442	65p	55p	43p
7445	85p	71p	57p
7447	81p	75p	65p
7448	75p	62p	60p
7447A	90p	83p	67p
7470	30p	25p	20p
7472	25p	21p	17p
7473	30p	25p	20p
7474	32p	26p	21p
7475	47p	39p	31p
7476	32p	26p	21p
7489	75p	63p	50p
7485	£1.20	£1.09	97p
7486	32p	26p	21p
7489	£2.92	£2.80	£2.10
7490	49p	40p	32p
7491	65p	55p	45p
7492	57p	46p	36p
7493	45p	40p	33p
7495	67p	57p	45p
74100	£1.08	£1.48	97p
74107	35p	28p	23p
74121	34p	28p	23p
74122	37p	30p	25p
74141	78p	63p	51p
74145	68p	58p	48p
74154	£1.62	£1.48	86p
74171	£1.00	£1.83p	67p
74180	£1.06	£2.80	71p
74181	£3.20	£2.50	£1.90
74192	£1.35	£1.14	90p
74193	£1.35	£1.14	90p
74196	£1.64	£1.34	99p

## LED DISPLAYS

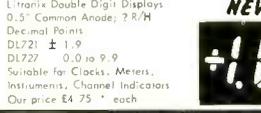

Litron's Double Digit Displays  
0.5" Common Anode, 9.8" H, Decimal Points  
DL721 ± 0.9  
DL722 ± 0.9  
Suitable for Clocks, Meters, Instruments, Channel Indicators  
Price £4.75 each

## DIGITAL SWITCH

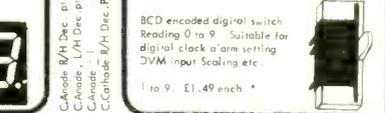

BCD encoded digital switch  
Reading 0 to 9. Suitable for digital clock alarm setting  
3V/10V Input Scaling etc.  
1 to 9. 49.19 inch

## LIGHT EMITTING DIODES

Part No.	0.125" dia lens (TTL 200)	0.16" dia lens	0.2" dia lens (MLED 650)
Red	16p	15p	13p
Green	16p	15p	13p
Orange	27p	24p	23p
Yellow	34p		

# More than just a catalogue!

**READY MADE ALARM CLOCK MODULE!**  
\* CAN CONTROL A RADIO, TOO!

**ONLY £8.60**  
INC. V.A.T. & P.I.P.

Just add transformer and switches!



This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied with module shows how simple it is to connect an audible alarm, and your battery or mains radio. A smart case will be available shortly. Data sheet available separately. Please send s.a.e.

Note: details not in catalogue.

- BRIGHT 4 DIGIT 0.5 INCH DISPLAY
- FLASHING COLON (1HZ)
- SWITCH-FOR DISPLAY SECONDS
- ALARM SET INDICATOR
- P.M. INDICATOR
- POWER FAILURE INDICATION
- SLEEP TIMER
- SNOOZE TIMER
- AUTOMATIC DISPLAY BRIGHTNESS (NEEDS C4S CELL)
- TIME CAN BE SET ACCURATELY TO WITHIN ONE SECOND
- LEADING ZERO BLANKING



Really good value for money at just 40p. **132 Pages**


**100W per channel**

## STEREO DISCO



YOU MUST SEE OUR PRICES BEFORE YOU BUY (S.a.e. please for details)

## The 4600 SYNTHESISER

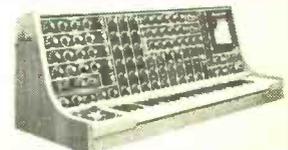

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or S.A.E. please for specification

## GRAPHIC EQUALIZER



A really superior high quality stereo graphic equaliser as described in Jan. 1975 issue of ETI. We stock all parts (except woodwork) including all the metal work drilled and printed as required to suit our components and PCB's. Complete reprint of article—price 15p.

## ELECTRONIC ORGAN



Build yourself an exciting Electronic Organ. Our leaflet MES51, price 15p, deals with the basic theory of electronic organs and describes the construction of a simple 49-note instrument with a single keyboard and a limited number of stops. Leaflet MES52, price 15p, describes the extension of the organ to two keyboards each with five voices and the extension by an octave of the organ's range. Solid-state switching and new footages along with a pedal board and a further extension of the organ's range are shown in leaflet MES53, priced at 35p

### NO MORE DOUBTS ABOUT PRICES

Now our prices are **GUARANTEED** (changes in VAT excluded) for two month periods. We'll tell you about price changes in advance for just 30p a year (refunded on purchases). If you already have our catalogue send us an s.a.e. and we'll send you our latest list of **GUARANTEED** prices. Send us 30p and we'll put you on our mailing list — you'll receive immediately our latest price list then every two months from the starting date shown on that list you'll receive details of our prices for the next **GUARANTEED** period **before** the prices are implemented! — plus details of any new lines, special offers, interesting projects — and coupons to spend on components to repay your 30p

**NOTE:** The price list is based on the Order Codes shown in our catalogue so an investment in our super catalogue is an essential first step.

Call in at our shop, 284 London Road, Westcliff on Sea, Essex. Please address all mail to

**MAPLIN ELECTRONIC SUPPLIES**  
P.O. Box 3 Rayleigh Essex SS6 8LR.

I enclose Cheque/P.O. value \_\_\_\_\_ PW  
For \_\_\_\_\_ copy/copies of your Catalogue  
Name \_\_\_\_\_  
Address \_\_\_\_\_

**MAPLIN ELECTRONIC SUPPLIES** P.O. Box 3 Rayleigh Essex SS6 8LR.