

DEC  
1977

# practical WIRELESS

45p

BLYTK

## LABORATORY POWER UNIT

also:  
TRAFFIC  
LIGHT  
CONTROLLER  
&  
SOLID-STATE  
TUNING  
INDICATOR



**A  
SPECIAL  
OFFER**



**Soldering Kit**

# T.T.L. 74 I.C.'s By TEXAS, NATIONAL, I.T.T., FAIRCHILD Etc

7400 14p	7413 30p	7432 25p	7454 15p	7491 35p	74121 25p	74139 100p	74156 70p	74174 100p	74189 350p
7401 14p	7414 60p	7437 25p	7460 15p	7491 75p	74122 40p	74141 60p	74157 70p	74175 75p	74190 140p
7402 14p	7416 30p	7438 25p	7470 30p	7492 45p	74123 60p	74142 270p	74160 90p	74176 100p	74191 140p
7403 14p	7417 30p	7440 15p	7472 25p	7493 40p	74125 50p	74143 270p	74161 90p	74177 100p	74192 120p
7404 14p	7420 15p	7441 65p	7473 30p	7495 60p	74126 50p	74144 270p	74162 90p	74178 140p	74193 120p
7405 14p	7422 20p	7442 80p	7474 30p	7496 70p	74130 130p	74145 75p	74163 90p	74179 140p	74194 100p
7406 40p	7423 25p	7446 85p	7475 30p	7497 80p	74131 100p	74147 230p	74164 125p	74180 100p	74195 100p
7407 40p	7425 25p	7447 75p	7476 30p	7498 100p	74132 65p	74148 160p	74165 125p	74181 200p	74196 100p
7408 20p	7426 25p	7448 70p	7483 85p	74107 30p	74135 100p	74151 65p	74166 125p	74182 75p	74197 100p
7409 20p	7427 25p	7450 15p	7485 100p	74109 50p	74136 80p	74153 65p	74167 325p	74184 150p	74198 100p
7410 15p	7428 40p	7451 15p	7488 30p	74115 90p	74137 100p	74154 120p	74170 200p	74185 150p	74198 100p
7411 20p	7430 15p	7453 15p	7489 250p	74120 90p	74138 125p	74155 70p	74173 150p	74188 350p	74199 185p

## SEMICONDUCTORS by MULLARD, TEXAS, MOTOROLA, SIEMENS, I.T.T., R.C.A.

AA113 10p	BA138 16p	BC168B 14p	BC548C 14p	BF123 45p	BF336 35p	BY164 50p	OC140 150p	TIP35A 230p	2N1305 30p
AA144 10p	BA148 16p	BC168C 15p	BC549B 13p	BF125 45p	BF337 35p	OC171 40p	OC171 40p	TIP35C 280p	2N1308 30p
AAZ17 30p	BA154 12p	BC169C 15p	BC549C 14p	BF127 50p	BF338 35p	C1120 30p	OC200 80p	TIP36A 350p	2N1308 60p
AC121 30p	BA157 15p	BC171 12p	BC550C 13p	BF166 30p	BF584 30p	C1164 20p	ORP12 70p	TIP41A 70p	2N1711 25p
AC126 19p	BA173 15p	BC172C 12p	BCY34 80p	BF167 25p	BFW58 20p	E100 42p	R1039 150p	TIP41B 75p	2N2219A 22p
AC127 19p	BA216 16p	BC178A 16p	BCY70 15p	BF173 25p	BFX29 30p	E300 47p	TIP29 45p	TIP41C 80p	2N2483 30p
AC127/01 25p	BA316 16p	BC182 10p	BCY71 20p	BF179 35p	BFX81 130p	E430 125p	TIP29A 47p	TIP42A 80p	2N2906 18p
AC128 18p	BA316 16p	BC182L 12p	BCY72 15p	BF179C 40p	BFX84 25p	MJE340 45p	TIP29C 75p	TIP42B 85p	2N2907 20p
AC151 25p	BA316 16p	BC183 10p	BD121 85p	BF180 30p	BFX85 30p	MPSA06 75p	TIP30 55p	TIP2955 70p	2N3053 20p
AC153K 40p	BA316 16p	BC183L 12p	BD123 100p	BF181 30p	BFX87 25p	O A10 40p	TIP30A 58p	TIP3065 55p	2N3054 50p
AC176 20p	BB105A 40p	BC184 10p	BD124 85p	BF182 30p	BFX88 25p	O A47 15p	TIP30B 65p	TIS90 25p	2N3055 60p
ACV17 35p	BC107 10p	BC184L 12p	BD131 35p	BF183 30p	BFY50 20p	O A90 6p	TIP30C 80p	TIS91 25p	2N3439 50p
ACV21 30p	BC108 10p	BC186 24p	BD132 35p	BF186 25p	BFY51 20p	O A91 6p	TIP31 55p	IN914 5p	2N3702 11p
AD149 60p	BC108C 15p	BC205 14p	BD133 45p	BF194 10p	BFY52 20p	O A202 8p	TIP31A 58p	IN3754 10p	2N3703 12p
AD161 40p	BC109 10p	BC212 11p	BD135 40p	BF195 10p	BFY90 125p	OC23 200p	TIP31B 65p	IN4001 5p	2N3705 12p
AD182 40p	BC109C 10p	BC212L 12p	BD136 40p	BF196 10p	BR101 35p	OC25 75p	TIP31C 70p	IN4002 5p	2N3706 11p
AD161/2M 90p	BC113 12p	BC213L 12p	BD137 40p	BF198 25p	BRV39 35p	OC35 75p	TIP32 60p	IN4003 5p	2N3711 12p
AF114 22p	BC125 20p	BC214 13p	BD139 38p	BF199 25p	BRV56 35p	OC35 75p	TIP32A 65p	IN4004 5p	2N3715 300p
AF15 22p	BC126 15p	BC258 13p	BD140 40p	BF200 30p	BSX20 20p	OC42 35p	TIP32B 85p	IN4005 5p	2N3772 175p
AF16 22p	BC146 12p	BC294 35p	BD141 80p	BF204 30p	BSY40 25p	OC43 35p	TIP32C 90p	IN4006 6p	2N3819 25p
AF17 22p	BC147 10p	BC303 35p	BD182 80p	BF224 20p	BSY95 20p	OC45 35p	TIP33 100p	IN4007 7p	2N3866 85p
AF18 40p	BC148 10p	BC317 15p	BD207 70p	BF225 20p	BT00A 80p	OC71 25p	TIP33A 105p	IN4148 4p	2N3904 15p
AF125 25p	BC148C 14p	BC323 60p	BD233 50p	BF241 16p	BU105 150p	OC72 30p	TIP33B 115p	IS44 4p	2N4062 14p
AF139 35p	BC149 10p	BC328 13p	BD263 65p	BF257 26p	BU208 220p	OC75 30p	TIP33C 130p	2N495A 90p	2N4126 20p
AF239 45p	BC157 10p	BC338 12p	BDY10 100p	BF258 26p	BY100 20p	OC81 25p	TIP34 115p	2N697 15p	2N5081 35p
ASV26 40p	BC158 10p	BC547 12p	BDY62/01 90p	BF259 30p	BY126 15p	OC81D 25p	TIP34A 115p	2N829 20p	2N5133 35p
BA114 9p	BC159 10p	BC547B 13p	BF120 50p	BF274 15p	BY127 18p	OC83 50p	TIP34B 145p	2N930 20p	2N6027 50p
BA121 9p	BC167A 12p	BC548 12p	BF121 45p	BF324 30p	BY133 22p	OC84 50p	TIP35 225p	2N1302 25p	2SD234 50p

**BZY88**  
400M.W.  
Zeners

OV7 10p
2V4 10p
2V7 10p
3V0 10p
3V3 10p
3V6 10p
3V9 10p
4V7 10p
5V1 10p
5V6 10p
6V2 10p
6V8 10p
7V5 10p
8V2 10p
9V1 10p
10V 10p
11V 10p

**BZY88**  
Zeners 850p

12V 10p
13V 10p
15V 10p
18V 10p
20V 10p
22V 10p
27V 10p
30V 10p
33V 10p
100 Mixed
Zeners 850p

SN76013ND 125p
SN76013N 180p
SN76023ND 125p
SN76023N 180p
SN76227N 180p
SN76228N 180p
SN76666N 100p
ZN414 120p

**CA3090AQ 400p**

TA A300 150p
TA A350 190p
TA A550 50p
TA A570 220p
TA A651B 140p
TA A700 390p
TAD100 250p
TAD110 200p
TBA120S 125p
TBA120T 125p
TBA540 300p
TBA540Q 400p
TBA550Q 400p
TBA560 400p
TBA641A12 250p
TBA720 230p
TBA800 100p
TBA820 100p
TBA990 250p
TCA2270Q 250p
TCA270S 250p

**LM301A 65p**

LM307N 65p
LM308T O5 130p
LM308 8 DIL 130p
LM309K 180p
LM317K 325p
LM348N 200p
LM380N 110p
LM555 35p
LM710 TOS 60p
LM710 P 65p
LM723 TOS 60p
LM723 14 DIL 75p
LM741 25p
LM748 45p
LM11303N 155p
LM3900 90p
NE555 35p
NE556 100p
NE562B 400p

**ELECTROLYTIC CAPACITORS**

330/35 16p
330/50 18p
470/10 12p
470/25 16p
470/35 18p
470/50 22p
680/25 25p
1000/16 25p
1000/35 30p
1000/63 50p
2200/10 28p
2000/35 50p
2200/16 35p
2200/63 75p
2200/100 120p
3300/16 40p
3300/25 42p
3300/63 80p
4700/40 50p
4700/63 120p

**POLYMER CAPACITORS**

22/50 6p
33/50 7p
33/63 6p
33/25 6p
33/40 6p
33/50 7p
47/10 6p
47/16 6p
47/25 6p
47/35 6p
47/50 7p
100/10 6p
100/16 6p
100/25 6p
100/30 6p
100/63 10p
125/15 6p
220/16 10p
220/25 12p
220/50 20p
330/25 15p

**SPECIAL OFFERS**

BC147 100 ASSOR. TED FOR £7.50p
BC148
BC149
BC157
BC158
BC159
BF194
BF195
BF196
BF197
IN4148 100 for 150p
741 Op AMPS 100 for £20
555 TIMERS 100 for £30

**RELAYS**

24V 3 C.O. H.D. 11 Pin Plug IN £1.00 Each
-------------------------------------------

**ASSORTED POLYMER CAPACITORS**  
100 for £3.90

**BYX94 DIODES**  
1250 PIV 1 Amp. 100 for £6.00

**MULLARD**  
4500/54V C.432 Screw Terminal 75p

**RESISTORS CARBON FILM 5%**

2.2W 2p
2.2Ω-4-7M 2p
5W 2.5p
2.2Ω-4-7M 2.5p
1W 2.2Ω-10 MEG 3.5p

**POTENTIOMETERS**

1K Lin 30p
5K Lin 30p
10K Lin 30p
25K Lin 30p
50K Lin 30p
100K Lin 30p
250K Lin 30p
500K Lin 30p
1 Meg Lin 30p
2 Meg Lin 30p
5K Log 30p
10K Log 30p
25K Log 30p
50K Log 30p
100K Log 30p
250K Log 30p
500K Log 30p
1 Meg Log 30p
2 Meg Log 30p

**ROTARY SWITCHES BY LORLIN**

1P 12W 40p
2P 6W 40p
3P 4W 40p
4P 3W 40p

**MULLARD POT CORES**

LA3 100-500 KHz 75p
LA4 10-30 KHz 100p
LA5 30-100KHz 100p
LA7 < 10KHz 100p

LA13 FOR W.W. OSCILLOSCOPE 200p

**SPECIAL SCOOP OFFERS**

**LEDS 125 OR 2 RED ONLY 100 for £9.00 1000 for £60.00**

**SPECIAL QUOTATION FOR LARGER QUANTITIES**

**WESTINGHOUSE THYRISTORS**

300 Volts 16 Amp 250p
-----------------------

**CMOS**

4000 20p	4023 20p	4055 140p
4001 20p	4024 100p	4056 145p
4002 20p	4025 200p	4060 130p
4006 120p	4026 200p	4066 55p
4007 20p	4027 85p	4069 30p
4009 70p	4028 155p	4071 30p
4011 20p	4029 130p	4072 30p
4012 20p	4030 60p	4081 20p
4013 55p	4032 150p	4082 30p
4015 90p	4043 220p	4082 30p
4016 55p	4046 150p	4510 145p
4017 110p	4047 115p	4511 200p
4018 250p	4049 70p	4516 140p
4020 140p	4050 50p	4518 140p
4022 100p	4054 130p	4528 130p

**BRIDGE RECTIFIERS**

1A 50V 25p	V/REG. 140p
1A 100V 30p	
1A 200V 30p	
1A 400V 35p	7812 140p
1A 600V 40p	7815 140p
2A 50V 35p	7818 140p
2A 100V 50p	7824 150p
2A 200V 55p	

**SKELETON PRE-SET POTENTIAL DIVIDERS**

0-1W 50N-5M mini vert & horiz 7p

25W 100N-3.3M horiz. 7p

25W 200N-4.7M vert. 8p

**TANTALUM BEAD CAPACITORS**

35V: 0.1µF, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8, 25V 1-5, 10, 15V 4.7, 10, 22, 100V 4.7, 15, 25, 33
-----------------------------------------------------------------------------------------------------------------

Price 14p each

**DIL SOCKETS**

8 Pin 13p
14 Pin 14p
16 Pin 15p

**BZX61 Zeners**

6V8 1.3W 15p
9V1 15p
11V 15p
13V 15p
15V 15p
22V 15p
30V 15p
39V 15p
43V 15p
47V 15p
51V 15p
56V 15p
68V 15p
72V 15p
160V 15p

# XEROZA RADIO

306 ST. PAUL'S ROAD,  
HIGHBURY CORNER, LONDON, N.1  
TELEPHONE 01-226 1489

Easy access to Highbury via Victoria Line (London Transport) British Rail

LARGE STOCKS OF NEONS, NUMICATOR TUBES, SINGLE AND MULTIPHASE HIGH CURRENT RECTIFIER STACKS, CAPACITORS OF ALL TYPES INCLUDING PHOTO-FLASH AND MOTOR START, TV TUNERS ALSO SOME HIGHLY TECHNICAL EQUIPMENT AND PARTS FOR INDUSTRIAL USERS AND SCHOOLS FOR PERSONAL CALLERS

Manufacturers (Large and Small) we welcome your enquiries. Overseas Buyers/Agents etc. let us know your requirements.

DECEMBER 1977 · VOLUME 53 · NUMBER 8

**BRITAIN'S LEADING JOURNAL FOR THE RADIO & ELECTRONIC CONSTRUCTOR**

Published by IPC Magazines Ltd., Westover House, West Quay Road, POOLE, Dorset  
BH15 1JG

**News and Views**

- 564 **EDITORIAL**—Calling all Constructors
- 565 **NEWS . . . NEWS . . . NEWS**
- 574 **KINDLY NOTE**—Sine/square wave generator, October 1977. IC of the month, November 1977.
- 586 **HOTLINES**—Recent developments in electronics. . . . . *Ginsberg*
- 587 **PRACTICAL WIRELESS**—Pre-view of our next issue
- 593 **NEW BOOKS**—Comments on the latest books in the electronics field.
- 593 **PW READER'S PCB SERVICE**—Prices and details of the PCBs available
- 599 **TELEVISION**—Details of the December issue
- 600 **PRODUCTION LINES**—Information on the latest products. . . . . *Bill Tull*
- 609 **ON THE AIR**—Amateur Bands . . . . . *Eric Dowdeswell G4AR*  
     SW Broadcast bands . . . . . *Charles Molloy G8BUS*  
     MW Broadcast Bands . . . . . *Charles Molloy G8BUS*  
     VHF Bands . . . . . *Ron Ham BRS15744*

**For our Constructors**

- 566 **PORTABLE PA AMPLIFIER**  
A simple design based on two ICs, with mixing facilities for two inputs. . . . . *S. H. Davies*
- 577 **LED TUNING INDICATOR**  
An inexpensive substitute for a centre-zero meter . . . . . *J. P. Macaulay*
- 581 **THE PW 'JUBILEE' ELECTRONIC ORGAN—4**  
Metalwork and wiring details for the calculator keyboard version . . . . . *M. J. Hughes MA, C.Eng, MIERE*
- 584 **TRAFFIC LIGHT CONTROLLER**  
Add realism to your model railway layout with this unit . . . . . *P. Chambers*
- 588 **LABORATORY POWER SUPPLY**  
A versatile triple-output unit for driving TTL, CMOS or discrete circuitry on the bench . . . . . *J. Thornton-Lawrence GW3JGA*
- 595 **S-DECNOLOGY Project No. 11**  
This month we present a Car Courtesy Light delay unit, which keeps the interior light on long enough to find your keys, etc . . . . . *David Gibson*
- 598 **ALL BAND SHORT WAVE RECEIVER—2**  
Concluding details . . . . . *F. Rayer G3OGR*
- 602 **DESIGN YOUR OWN PROJECTS—4**  
An impedance matching amplifier to aid recording and playback between unmatched pieces of equipment  
*Toby Bailey and Bob Whitaker*

**General Interest**

- 570 **SO YOU WANT TO PASS THE RAE?—4**  
This month's element of the course deals with AC, Inductors and transformers . . . . . *John Thornton-Lawrence GW3JGA and Ken McCoy GW8CMY*
- 578 **SPECIAL PRODUCT REPORT**  
Chroma-Chime Kit
- 594 **A MERE 20 YEARS**  
A brief review of communications satellites since the days of Sputnik 1 . . . . . *Ron Ham BRS15744*
- 604 **IC OF THE MONTH**  
The Thomson CF series of motor speed regulators are considered in detail . . . . . *Brian Dance M.Sc*

★ **Special Offer**

569 S&R Brewster 18W Soldering Iron Kits

**COPYRIGHT**

© IPC Magazines Limited 1977. Copyright in all drawings, photographs and articles published in 'Practical Wireless' is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by 'Practical Wireless' to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

# Latest Title



In the well established  
*Master Series*

## Master In-Car Entertainment

Author: Vivian Capel

Whether you are stuck in the frustrating immobility of a traffic jam, or suffering the boredom of a long car journey, you are sure to find facilities for in-car entertainment a great boon. Published information on the choice and installation of mobile audio equipment has not kept pace with the rapidly growing interest in the subject. This book fills the gap in a highly informative, easy-to-read manner. Written by an expert, and illustrated with many attractive two-colour diagrams, it sets out the relative merits of mono, stereo and quad in the car, and describes cartridge and cassette players as well as giving helpful advice on choosing between the systems.

### CONTENTS:

The Car Equipment Scene. Mono Stereo or Quad? Mobile Tape Players. The Cartridge Player. The Cassette Player. Cassette or Cartridge? Car Radios. Car Antennas. Interference Suppression. Installing the System. Trouble Shooting.

1977                      128 pages                      £2.50

### A SELECTION OF OTHER USEFUL BOOKS

Beginner's Guide to Electronics — 3rd Edition T. L. Squires and C. M. Deason	1975	240 pages	£2.25
Beginner's Guide to Transistors — 2nd Edition J. A. Reddihough	1975	160 pages	£2.25
Beginner's Guide to Radio — 8th Edition Gordon King	1977	240 pages	£2.75
Foundations of Wireless and Electronics — 9th Edition M.G. Scroggie	1975	552 pages	£3.75
Radio Circuits Explained Gordon King	1977	175 pages	£5.50

ORDER NOW

from your local Bookseller or from

**Newnes Technical Books**  
Borough Green, Sevenoaks, Kent TN15 8PH


CHINAGLIA DINO — ELECTRICAL AND ELECTRONIC TEST EQUIPMENT MANUFACTURERS

PRESENT THE
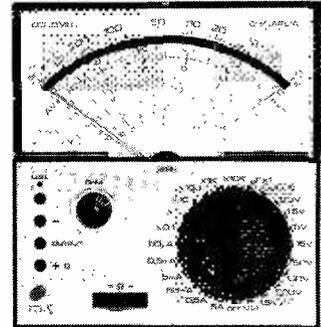
## DOLOMITI

20k $\Omega$ /V a.c. and d.c.

A NEW HIGH SENSITIVITY MULTIMETER WITH ALL THE FEATURES YOU WILL EVER NEED



Accuracy: D.C. ranges,  $\pm 2.0\%$ , A.C. &  $\Omega$  ranges  $\pm 2.5\%$ .

39 ranges: d.c. V, 0-150mV, 500mV, 1-5V, 5V, 15V, 50V, 150V, 500V, 1-5kV; d.c.I., 0-50  $\mu$ A, 500  $\mu$ A, 5mA, 50mA, 0-5A, 5A; a.c. V, 5V, 15V, 50V, 150V, 500V, 1-5kV; a.c.I., 5mA, 50mA, 0-5A, 5A; dB — 10 to +65 in 6 ranges;  $\Omega$  0-0.5k $\Omega$ , 5k $\Omega$ , 50k $\Omega$ , 500k $\Omega$ , 5M $\Omega$ , 50M $\Omega$ ; pF 50k pF, 500k pF.

Automatic overload protection and high current range fusing.

Scale mirror and fine pointer for accuracy of reading. Single knob main range switching and all panel controls. C.E.I. Class 1 movement with sprung jewel bearings. Extended 92mm scale length for extra clarity. Compact ABS case 125 x 131 x 37mm. Weight 750g with batteries. Supplied complete with carrying case, fused leads, handbook and full 12-month guarantee. Optional 30kV d.c. probe available.

Meter £45.90 incl. VAT (£1 P. & P.)

30kV Probe £12.85 incl. VAT

For details of this and the many other exciting instruments in the Chinaglia range, including multi-meters, component measuring, automotive and electronic instruments please write or telephone.

# ALGON

19 MULBERRY WALK . LONDON SW3 6DZ TEL: 01-352 1897

## Your career in Electronics?

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Fullest details will be gladly sent without any obligation.

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, W.D. 12

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

(Block caps please)

# RSC 100 WATT DISCO SYSTEM

ALL RSC PRICES INCLUDE VAT



AT A FANTASTIC LOW PRICE

Consisting of  
(1) TWIN T/TABLE CONSOLE with PRE-AMP, and POWER OUTPUT STAGES  
(2) & (3) PAIR 50 WATT LOUD-SPEAKERS including 12" UNITS

Price includes High Quality Dynamic Stick Microphone and VAT

Terms: Deposit £30.00 and 18 fortnightly pymts. £9.80 (Total £206.40) Carr. £4.00

**£179.95**

Also available 200 WATT SYSTEM **£199.95**

## TD1 DISCO CONSOLE


Incorporating twin BSR type turntables and Sonotone or Acos Cartridges with diamond styli. Separate Vol. controls for each turntable. Also MONITORING FACILITIES, plus Treble and Bass Controls. Separate Input for 'mike' with vol. control. Black Vynide covered Cabinet with lid **£119.95** Or Dep £16.49 & 18 f'tnly pymts. £6.75 (Total £137.99) Carr. £3.

## TD2S STEREO VERSION OF ABOVE

**£125.00** Terms DEPOSIT £20 and 18 fortnightly payments £6.89 Total £144.02 Carr. £3

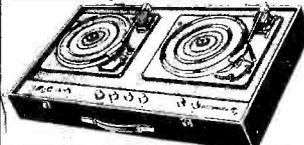
## DISCOMAJOR/100 TWIN TURNTABLE POWER CONSOLE £139.95

Twin Full size BSR turntables, Sonotone or Acos Cartridges with Diamond Styli. Facilities as TD1 Console but with built-in 100 watt Power Amplifier complete with lid. Terms: Deposit £19.95 and 18 fortnightly payments £7.70 (Total £158.55)



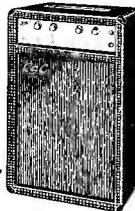
## DISCOMAJOR/200 £159.95 Carr. £4.00

200 watt version of above. Terms: Dep. £29.95 and 18 fortnightly payments £8.60 (Total £184.75)



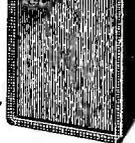
## RSC PHANTOM 50 COMBO AMP. £69.95

Rating 50 watts. 3 inputs, 2 vol controls—Bass, Treble Presence. Suitable for Lead or Rhythm Guitar, mic., Radio, Tape, etc. Inc. High Flux 12" 50w Speaker. Dep. £10.95 & 8 monthly payments £8.71 (Total £80.63)



## 100W POWER (SLAVE) AMPLIFIER

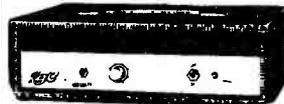


Suitable for use with DISCO-Consoles. Also for increasing output of lower-powered Amplifier. Dep. £9.00 and 8 mthly pyts of £6.05 (Total £57.40) Carr. £1.50 **£49.95**

100 + 100W MODEL **£69.95** Carr. £1.50
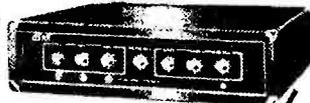
## TITAN TA/50A 50W AMPLIFIER

Solid state, 3 sep. controlled inputs plus Master control. Bass, Treble & Presence Controls. Vynide covered cab. with corner protectives. List price £60. Terms: Dep. £9 & 8 monthly payments £6.05. (Total £57.40) Carr. £1.



**£49.95**

Matching Cabinets 1 x 12" £29.95, 2 x 12" £49.95

## TITAN TA/100A 100W AMPLIFIER

TWIN CHANNEL—4 INPUTS (NORMAL OR BRIGHT) **£69.95** Carr. £1.50  
A De-luxe professional unit with many facilities. R.M.S. Rating. Matching 2 x 12" 120w Cabinet speaker £49.95 with above only. Carr. £1.50



**INTEREST REFUNDED** on Credit Purchases settled in 3 mths

## TITAN 'ADD-ON' HIGH FREQUENCY HORN UNITS



**MODEL TS2H**  
Inc. Pair of highly sensitive Horns. Range 3-15 kHz Imp 16Ω. Use with 8 or 15Ω 2 x 12" or 1 x 15" or 18" Drive Unit for increased sound clarity and projection. Rating 100 watts. Either model **£27.95** Carr. 75p Terms: Dep £6.95 & 8 mthly pyts £3.12 (Total £31.91)



**MODEL TH**  
With single super efficient Horn. Range 3-15 kHz. Imp 8Ω. Use with max 8Ω 2 x 12" or single 15" or 18" 8Ω Drive Units. Maximum amplifier power output to be 100 watts. Comparable with units at twice the cost.

## RSC MAINS TRANSFORMERS TYPES FOR VALVE RADIOS & AMPLIFIERS (Inc. L.F. CHOKES & OUTPUT TRANSFORMERS). As previously advertised still available.

**FILAMENT OR TRANSISTOR POWER PACK**  
12v. 1a. £1.10, 6.3v. 1.5a £1.06, 6.3v. 2a £1.10, 6.3v. 3a £1.70, 6.3v. 6a £2.60, 12v. 3a or 2a: 1.5a £2.60, 0.9-1.5v. 1.1a £2.26, 0.12-25-42v. 2a £2.19, CHARGER TRANS 0.9-15v. 1.1a £2.03, 2.1a £2.26, 3a £2.32, 5a £2.84, 6a £3.19, 8a £3.48.

**AUTO (STEP UP/STEP DOWN) TRANSFORMERS** 0-110/120v, 200-230-250v, 80w. £2.80; 150w. £5.20; 250w. £6.37; 500w. £9.84.

## New Branches at HANLEY WOLVERHAMPTON and LIVERPOOL



**OPEN ALL DAY SATURDAYS (5 Day Week)**  
**BRADFORD** 10 North Parade (Closed Wed.) Tel. 25349  
**BOLTON** 23 Deansgate. (Closed Wed.) Tel. 33512  
**BIRMINGHAM** 30/31 Great Western Arcade. Tel. 021-236 1279 (Closed Wed.)  
**CARLISLE** 8 English Street (Closed Thurs.) Tel. 38744  
**COVENTRY** 17 Shelton, Sq., The Precinct. Tel. 25983  
**DERBY** 97 St. Peter's Street (Closed Wed.) Tel. 41361  
**DARLINGTON** 19 Northgate (Cl. Wed.) Tel. 68043  
**DEWSBURY** 9/11 Kingsway (Closed Tues.) Tel. 468058  
**DONCASTER** 3 Queensgate, Waterdale Centre. (Closed Thurs.) Tel. 63069  
**EDINBURGH** 101 Lothian Rd. (Cl. Wed.) Tel. 229 9501  
**GLASGOW** 326 Argyll St. (Cl'd Tues.) Tel. 248 4158



All items subject to availability. Prices correct at 26.9.77 E. & O.E.  
**HANLEY** Stoke-on-Trent, 44 Piccadilly  
**HULL** 7 Whitefriargate (Closed Thurs.) Tel. 20605  
**LEICESTER** 32 High Street (Closed Thurs.) Tel. 56420  
**LEEDS** 5-7 County (Mecca) Arcade, Briggate  
**LIVERPOOL** 35 Dawson's Way, St. John's Shop-5-ping Centre Tel: 708 9380 (Cl. Wed.)  
**LONDON** 238 Edgware Road, W.2. (Closed Thurs.) Tel. 723 1629  
**MANCHESTER** 60A Oldham Street (Closed Wed.) Tel. 236 2778

- ★ DISCOMAJOR POWER DISCO CONSOLE with integral Power Amplifier.
- ★ TWIN FULL SIZE BSR turntables with cueing device.
- ★ CARTRIDGES with Diamond Styli
- ★ 3 SEPARATE VOLUME CONTROLS for each turntable and Mic.
- FULL HEADPHONE MONITORING FACILITIES
- CONSOLE COMPLETE WITH LID

## TITAN 100W BASS BINS £99.95

High quality 15" high flux Bass Unit and J104 Horn Tweeter in folded horn enclosure providing amazing level of sound output. Terms Dep. £14.95 and 18 fortnightly payments. £5.58 (Total £115.39) Carr. £3.



## FANE HIGH POWER SPEAKERS

Power ratings R.M.S. Cont. 2 YRS GUARANTEE \*Gauss 14000 Imp 8-15 ohms. CARR FREE.

- POP 33T 12" 33w £12.95** Dual cone.
- \***POP 50/2 12" 50w £15.99** Deposit for Pair £8.00 and 8 monthly payments £3.54 (Total £36.32)
- \***POP 75 12" 70w £19.99** Gauss 17,000 lines. Deposit £5.00 and 8 monthly payments £2.38 (Total £24.04)
- \***POP 60 15" 60w £25.95** Deposit £7.00 & 8 monthly payments £2.87 (Total £29.96)
- \***POP 100 18" 100w £44.95** Deposit £10.00 & 8 monthly payments £5.17 (Total £51.36)

## RSC

Stockist of LIGHTING by PULSAR

★ GROUP Equipment by CARLSBRO

★ FULL RANGE OF SPEAKERS by FANE

★


★

## TITAN GROUP/DISCO SPEAKERS GUARANTEED 5 YEARS

Carr. £1, under £18, over this add 5p per £1.

	Value	RSC Price
T12/45 12" 45w	£15.00	£11.95
T12/60A 12" 60w	£21.00	£13.95
T12/100 12" 100w	£36.00	£25.95
T15/60 15" 60w	£26.00	£16.99
T15/70 15" 70w	£28.00	£19.95
T15/100 15" 100w	£41.00	£29.95
T18/100 18" 100w	£47.00	£36.95

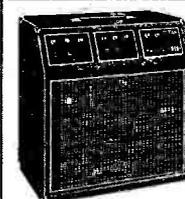**CABINETS FOR ABOVE** Heavy duty, finished in black Vynide with Vynair fronts, protective corner pieces Various sizes and cut-outs. TE1 1 x 12" £10.95. TE2 2 x 12" £16.95. Low Deposit Terms on orders over £20.



## TITAN TA/100C COMBO

100w R.M.S. Amp. incorporating a fabulous Fane Crescendo 12" 100 watt spkr for really superlative results with Lead Guitar **£119.95** Carr. £5

Or Dep £17.95 & 18 f'tnly pays £6.69 (Total £138.37)

## FANE HIGH FREQUENCY HORNS 'J' SERIES

**MODEL J44** Imp 8Ω Size approx. 3 3/4" x 3 1/4" x 3" Rating 30-50 watts Range 3-15 kHz **£7.95** Carr Free

**MODEL J73** Imp 8Ω Size approx 7 1/4" x 3" x 6 1/4" Rating 50 watts Range 2-20 kHz

**MODEL J104** Imp 8Ω Size approx 10 1/4" x 3 1/4" x 7 1/4" Rating 50-70 watts Range 2-15 kHz



## FAL DISCO LIGHTING SYSTEMS from £58.95

Incl 2 Spotbanks and bulbs  
**JINGLE MACHINES from £37.95**  
**ECHO CHAMBERS from £53.95**  
**COLUMN SPEAKERS from £29.95**  
**GROUP DISCO SPKRS in CABINETS from £11.95**

Carr. Free **£11.75**

Carr. Free **FREE £15.50**

**HIGH POWER 'CROSS OVER' (value £2.99) SUPPLIED WITH ABOVE**  
Impedance or total impedance of 12", 15" or 18" Drive units must not exceed impedance of single horn or pair in series. Pair J44, Single J73 or J104 suitable for amplifier power up to 100 watts subject to above and with HPX2R 'Cross-over'

**MAIL ORDERS & EXPORT ENQUIRIES TO—**  
**AUDIO HOUSE, HENCKNER LANE, LEEDS, 18. TEL: 0532 577831.**  
MAIL ORDERS MUST NOT BE SENT TO SHOPS  
TERMS C.W.O. or C.O.D. No. C.O.D. under £3. POSTAGE 50p PER ORDER OR AS QUOTED. Phone or Write for FREE CATALOGUE.  
**MIDDLESBROUGH** 103 Linthorpe Rd. Tel. 247096 (Closed Wed.)  
**NEWCASTLE UPON TYNE** 59 Greinger St. (Closed Wed.) Tel. 21460  
**NOTTINGHAM** 19/19A Market Street (Closed Thurs.) Tel. 48068  
**PRESTON** 41 Frlargate Walk, St. Georges Shoppg Prec. Tel. 51979  
**SHEFFIELD** 13 Exchange Street (Castle Mkt. Bldg.) (Closed Thurs.) Tel. 20716  
**STOCKPORT** 8 Little Underbank (Closed Thurs.) Tel. 480-0777  
**SUNDERLAND** 5 Market Sq. (Closed Wed.) Tel. 70573  
**WOLVERHAMPTON** 6, Wulfrun Way (Cl'd Thurs.) Tel. 26612



# Handy size Reels & Dispensers

**OF THE WORLD'S FINEST CORED SOLDER TO DO  
A PROFESSIONAL JOB AT HOME**

Ersin Multicore Solder contains 5 cores of non-corrosive flux that instantly cleans heavily oxidised surfaces and makes fast, reliable soldering easy. No extra flux is required.

**SAVBIT**  
handy solder dispenser

Contains 2.3 metres approx. of 1.22 mm Ersin Multicore Savbit Solder. Savbit increases life of copper bits by 10 times.  
Size 5 49p

For soldering fine joints

Two more dispensers to simplify those smaller jobs. PC 115 provides 6.4 metres approx. of 0.71 mm solder for fine wires, small components and printed circuits.  
PC115 57p  
Or size 19A for kit wiring or radio and TV repairs. 2.1 metres approx. of 1.22 mm solder.  
Size 19A 53p

handy size reels of **SAVBIT,**  
**40/60, 60/40 & ALU-SOL** solder alloys

These latest Multicore solder reels are ideal for the toolbox. Popular specifications cover all general and electrical applications, plus a major advance in soldering aluminium. Ask for a free copy of 'Hints on Soldering' containing clear instructions to make every job easy.

Ref.	Alloy	Diam. mm	Length metres approx.	Use	Price
Size 3	40/60 Tin/Lead	1.6	10.0	For economical general purpose repairs and electrical joints.	£1.79
Size 4	ALU-SOL	1.6	8.5	For aluminium repairs. Also solders aluminium to copper, brass etc.	£2.42
Size 10	60/40 Tin/Lead	0.7	39.6	For fine wires, small components and printed circuits.	£1.79
Size 12	SAVBIT	1.2	13.7	For radio, TV and similar work. Increases copper-bit life tenfold.	£1.79

**BIB WIRE STRIPPER & CUTTER**

Fitted with unique 8-gauge selector and handle locking device. Sprung for automatic opening. Strips flex and cable in seconds.

Pat. No. 1443913 Model 8B 86p

**SOLDER-WICK**

Absorbs solder instantly from tags, printed circuits etc. Only needs 40-50 Watt soldering iron. Quick and easy to use. Non-corrosive.

Size 18 97p

Sole U.K. Sales Concessionaires.

**Bib Hi-Fi Accessories Limited,**

Kelsey House, Wood Lane End, Hemel Hempstead, Herts. HP2 4RQ.

Prices shown are recommended retail, inc. V.A.T. From Electrical and Hardware Shops. In difficulty send direct, plus 20p P&P. Prices and specifications subject to change without notice.

MAIL ORDER DEPT.:-

## CRESCENT RADIO LTD

I ST. MICHAELS TERRACE, WOOD GREEN, LONDON, N22 4SJ

TELEPHONE: 888-4474

### 3 KILOWATT PSYCHEDELIC LIGHT CONTROL UNIT

1000 WATT PER CHANNEL. Three channel. Bass, Middle, Treble. The input of this unit is connected to the loudspeaker terminals of an amplifier and the required lighting is connected to the output terminals of the unit thus enabling you to produce a fascinating sound to light display. Full instructions supplied or S.A.E. for details. Fantastic Value at £20.00 + 8% VAT.

### LOUDSPEAKER SELECTION + 12 1/2% VAT

- 2 1/2" 8, 40 and 75 ohm at £1.10 (Please state which impedance is required)
- 5" 8 ohm CERAMIC at £1.70
- 8" GOODMAN'S Audiom SPA' 8 ohm at £5.26
- 10" 'ELAC' Dual Cone 8 ohm 10 watt at £4.75

**EFFECTS PROJECTOR "150"** (150 watt) Ideal for disco work, this versatile machine takes a range of accessories and is of a sturdy metal construction. Comes complete with bulb and 6" Liquid Wheel. Ready to use. A bargain at £34.00 + 8% VAT.

**PIEZO ELECTRIC HORN UNITS** 100 watt New High Quality, High Power Tweeter. No Xover required. Freq. Response. 3-8KHz to 28KHz. Spec. Sheet sent on receipt of S.A.E.

OUR PRICE: £9.35 each + 8% VAT.

ACCES AND BARCLAYCARD ACCEPTED—PHONE ORDERS WELCOMED ALL PRICES INCLUDE POSTAGE—PLEASE ADD V.A.T. AS SHOWN—S.A.E. WITH ALL ENQUIRIES PLEASE.

Personal callers welcome at: 104-106 HIGH ROAD, WOOD GREEN, N22. Phone: 888-3206 and 13 SOUTH MALL, EDMONTON N9 Phone: 803-1685

### POWER SUPPLY UNITS + 8% VAT

PP1—Switched 3, 4, 6, 7, 9, 12v at 500mA with on/off switch and pilot light. Approx. size: 130 x 55 x 75mm. ONLY £6.00.  
PP2—Switched 6, 7, 9v at 800mA. This is a sealed, moulded unit fitted with a 3 pin 13A mains plug. Approx. size: 75 x 55 x 45mm. ONLY £4.00.  
PP3—DC/DC Power supply for cars. Switched 6, 7, 9v at 500mA from 12v DC input. Approx. size: 125 x 68 x 45mm ONLY £6.25.  
PP4—Stabilized Power supply. Switched 3, 6, 7, 9v at 400mA with on/off switch and pilot light. Approx. size: 115 x 78 x 55mm. ONLY £7.00.  
PP5—Heavy duty 12 volt power supply. 1.5A at 12 volt. Approx. size: 165 x 90 x 95mm. ONLY £8.00.

### ALUMINIUM BOXES + 8% V.A.T.

AB7 = 5 1/2" x 2 1/2" x 1 1/2" = 83p  
AB8 = 4" x 4" x 1 1/2" = 75p  
AB9 = 4" x 2 1/2" x 1 1/2" = 83p  
AB10 = 5 1/2" x 4" x 1 1/2" = 83p  
AB11 = 4" x 2 1/2" x 2" = 83p  
AB12 = 3" x 2" x 1" = 68p  
AB13 = 6" x 4" x 2" = £1.00  
AB14 = 7" x 5" x 2 1/2" = £1.20  
AB15 = 8" x 6" x 3" = £1.79  
AB16 = 10" x 7" x 3" = £1.92  
AB17 = 10" x 4 1/2" x 3" = £1.66  
AB18 = 12" x 5" x 3" = £1.98  
AB19 = 12" x 8" x 3" = £2.19 (please note: all sizes are approx.)

### BARGAIN TRANSFORMERS


240v primary, 12-0-12v 500mA secondary. Approx. size: 60 x 40 x 50mm. Fixing centres 75mm. PRICE: £1.90 + 8% VAT. Also available Mains transformer with 18v 500mA sec. Price and size same as above.

V-Q

WAS MADE FOR YOU

VERO

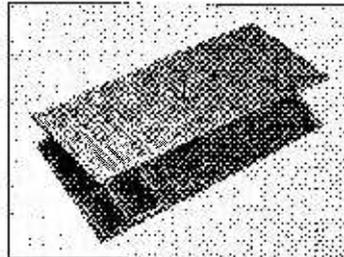VERO QUAD BOARD was designed to provide a simple circuit board capable of accepting nearly all types of integrated circuits, plus transistors, resistors, capacitors and many other components.



ASK FOR V-Q — IT WAS MADE FOR YOU

No track cutting. 1,624 holes on 0.1" x 0.1" matrix. Packed complete with layout sheet. Fits Vero Plastic Cases 1237, 1238 and 1239. Costs about 90p from your local shop or mail order company. Send for our booklet describing many other products made for you, S.A.E. 7" x 9" plus 10p to:

VERO ELECTRONICS LTD. RETAIL DEPT.  
INDUSTRIAL ESTATE, CHANDLERS FORD,  
HANTS. SO5 3ZR.

## DIY SPEAKER KITS

**15-WATT KIT IN CHASSIS FORM**  
When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the enclosures illustrated below Size 13" x 8" (approx.) woofer (EMI), tweeter, and matching crossover components. Power handling capacity 15 watts rms, 30 watts peak.  
**£17.00 PER STEREO PAIR**  
+ P & P £3.40

## EASY-TO-BUILD WITH ENCLOSURE

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching crossovers. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms, 30 watts peak, each unit.  
**£28.00 PER STEREO PAIR**  
+ P & P £5.50 (approx.)

## COMPACT FOR TOP VALUE

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £8.50 - just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready mitred and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is in wood simulate. Complete with two 8" (approx.) speakers for max. power handling of 7 watts.  
**per stereo pair £8.50**  
+ P & P £2.20

**SPEAKERS** Two models - Duo IIb, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/2" (approx.).  
**★ £34 PER PAIR**  
+ P & P £6.50

Duo III, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" (approx.).  
**★ £52 PER PAIR**  
+ P & P £7.50

## EASY TO BUILD RECORD PLAYER KIT

Ideally suited for the constructor who requires a complete stereo unit at a budget price, comprising ready assembled stereo amp. module, Garrard auto/manual deck with cueing device, pre-cut and finished cabinet work. Output 4 watts per channel, phones socket and record / replay socket.  
**£26.95**  
+ P & P £4.05

## CAR RADIO KIT

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control. The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture. Size approx. 7" x 2" x 4 1/2". 12 volts pos or neg earth (altered internally) p & p £1.50  
**£12.50**  
Output 4 watts into 4 ohms.

**FREE TO PERSONAL SHOPPERS BUYING CAR RADIO KIT** ELECTROMATE Rear window heater modern line element all wiring and switch worth **£300**



**SPECIAL OFFER**

**TO PERSONAL SHOPPERS**  
See Below

## 20 x 20 WATT STEREO AMPLIFIER

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminium rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic. magnetic and crystal pick-ups, tape, tuner, and auxiliary Rear panel features two mains outlets. DIN speaker and input sockets, plus fuse. 2U + 20 watts rms, 40 + 40 watts peak.  
**★ £29.90**  
p & p £2.50

**★ FREE** To cash or cheque personal shoppers

A 4 channel Stereo Adaptor to all buyers of the Viscount 20 x 20 Amplifier at **£29.90** limited offer. Available separately at **£3.95**

## SPECIAL OFFER

For example - Duo speaker system II or III Viscount Amplifier, MP60 type turntable complete

**DEDUCT 10% DEDUCT 15%**

on complete stereo systems using starred Products

**ADD-ON STEREO CASSETTE TAPE DECK KIT**  
Designed for the experienced D.I.Y. man. This kit comprises of a tape transport mechanism, ready built and tested record/replay electronics with twin V.U. meters and level control ready for mating together with the mechanism.

Specifications: Sensitivity - Mic. 0.85mV @ 20K OHMS; Din. 40mV @ 400K OHMS; Output - 300mV RMS per channel @ 1KHz from 2K OHMS source: Cross Talk - 30db; Tape Counter - 3 Digit - Resettable; Frequency Response - 40Hz - 8KHz ± 6db; Deck Motor - 9 Volt DC with electronic speed regulations; Key Functions - Record, Rewind, Fast Forward, Play, Stop & Eject. p & p £2.50  
**£19.95**

Pair of Dynamic microphones **£3.95** + £1.00 p & p.  
Optional extras: Mains transformer **£2.50** + £1.00 p & p.

**STEREO CASSETTE** record/replay fully built P.C. board incorporating 4 I.C.s.  
**GRUNDIG 5 1/2"** tape 1800 ft. **£1.20** each. 5 for **£5.00**

**PAIR STEREO 8 WATT SPEAKERS** 8" bass units with 3 1/2" approx. tweeters power handling 8 watts imp 8ohms. Size 16 1/2" x 11" x 8 3/4" approx. **£12.95**

**SLIMLINE** Record Player Plinth accepts BSR T/T GOODMAN 5" approx. 7 watt bass speaker **£9.50**

**AM. FM. TURNER P.C.B.** with Mullard L.P. 1186, 1185, 1181 modules **£9.00**

**100K** Multiturn Varicap tuning pots 6 for **HEAVY DUTY FIBRE GLASS COPPER CLAD BOARD** 25" x 17" x 1/8" Approx. per sheet only **£1.90**

**DECCA DC1000** Stereo Cassette Record, deck P.C.B. complete with switch oscillator coils and tape-heads and circuit diagrams. **£2.95**

**AM. FM. STEREO MULTIPLEX CAR RADIO**/cassette player in dash fitting Negative earth 5 watts output **£36.00**

I.C. Stereo 8 Track to Cassette adaptor converts any 8 track player to cassette player. **£18.95**

**Personal Shoppers Only!**

## BSR TURNTABLES

**BSR MP60 TYPE**  
Single play record player (Chassis form) **£15.95**  
less cartridge. P & P **£2.55**

Cartridges to suit above  
**ACOS MAGNETIC STEREO** ..... **£4.95**  
**CERAMIC STEREO** **£1.95**

**BSR automatic record player deck (Chassis form)** with cueing device and stereo ceramic head. P & P **£2.55**

**TURNTABLE** illus. diamond stylus, and de luxe plinth and cover. Ready wired **★ £29**  
+ P & P **£4.50**

## 30 x 30 WATT AMPLIFIER KIT

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched, drilled and formed. Cabinet is finished in teak veneer. Silver fascia and easy-to-handle aluminium knobs.  
Output 30 + 30 watts rms, 60 + 60 peak.  
**£29.00**  
p & p **£2.50**  
**NOW AVAILABLE** fully built and tested. **£35.00** + P & P **£2.50**

## DECCA 20 WATTS STEREO SPEAKER

This matching loudspeaker system is hand made, kit comprises of two 8" diameter approx. base drive unit, with heavy die cast chassis laminated cones with rolled P.V.C. surrounds, two 3 1/2" diameter approx. domed tweeters comp with crossover networks  
**£20.00**  
£4.00 p & p stereo pair

Order giving your credit card number ONLY

**ALL PRICES INC. VAT AT 12 1/2%**  
GOODS NOT DESPATCHED OUTSIDE UK  
All items subject to availability. Price correct at 29/9/77 and subject to change without notice.  
We are unable to show all our products.

Send stamped addressed envelope for further details.

**RTVC**

323 EDGWARE ROAD, LONDON W2  
Personal Shoppers EDGWARE ROAD 9.30am - 5.30pm. Half day Thurs.  
21c HIGH STREET, ACTON, LONDON W3 6NG  
ACTON: Mail Order only No callers

## PORTABLE MONO DISCO



with built-in pre-amplifiers  
Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single play professional series record decks. Plus all the controls and features you need to get fabulous disco performances. p & p **£6.50**  
Simply connects into your existing slave or external amplifier. **£64.00**

## 45 WATT MONO DISCO AMP

**£35.00**  
+ P & P **£2.50**  
Size approx. 13 3/8" x 5 1/2" x 6 1/2"  
Here's the mono unit you need to start off with. Gives you a good solid 45 watts rms, 90 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.  
**£35.00**

## 70 & 100 WATT MONO DISCO AMP

Size approx. 14" x 4" x 10 1/2"  
Sloping fascia, you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth acting, vertically mounted slide controls - master volume, tape level, mic level, deck level, PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading 70 watt **£57** in. VU meter monitors output level. 100 watt **£65**  
Output 100 watts RMS 200 watts peak. p & p **£4.00**



**BSR BDS95 TYPE**  
Belt drive turntable unit, 2 speed, semi automatic operation **£24.95**  
+ P & P **£2.55**

## PRACTICE GUITAR AMPLIFIER WITH BUILT-IN SPEAKER

This budget practice amplifier, has been specially designed for the amateur, who requires a quality self-contained unit with all facilities. 2 inputs - 1 for mic or guitar, the 2nd for record player or cassette deck, it also can be used for cine-sound amplification. 2 volume controls, 1 for each input, also base and treble controls. Power output with internal speaker, 10 watts RMS, with remote speaker (not supplied) 20 watts **£32.50**  
RMS. Size approx. 17" x 9" x 11". + P & P **£3.00**

## HOME 8 TRACK CARTRIDGE PLAYER

Automatically switches programmes monitored by indicators, with manual override track selection. This unit will match with the Unisound modules and is compatible with the Viscount IV amplifier with Sim teak cabinet, approx. 9" x 8" x 3 1/2". p & p **£2.50** **£16.50**  
Output 125 Mw

## PYE STEREO GRAM CHASSIS

(Complete with circuit diagrams)  
Complete ready to install - Wave bands LM, VHF STEREO, VHF MONO. Controls for tuning volume, balance, bass and treble. Power output 7 watts R.M.S. per channel 14 watts peak 8 ohms. 2" x 8" approx chassis speakers and BSR auto record player deck. **£35.00**  
**PERSONAL SHOPPERS ONLY**

# GREENWELD

443 Millbrook Road Southampton  
SO1 0HX Tel: (0703) 772501

BUY A COMPLETE  
RANGE OF COM-  
PONENTS AND  
THESE PACKS  
WILL HELP YOU

★ **SAVE ON TIME**—No delays in waiting for parts to come or shops to open!

★ **SAVE ON MONEY**—Bulk buying means lowest prices—just compare with others!

★ **HAVE THE RIGHT PART**—No guesswork or substitution necessary!

ALL PACKS CONTAIN FULL SPEC, BRAND NEW, MARKED DEVICES—SENT BY RETURN OF POST. VAT INCLUSIVE PRICES.

**K001** 50V ceramic plate capacitors, 5%, 10 of each value 22pF to 1000pF. Total 210, £3.35

**K002** Extended range, 22pF to 0.1µF. 330 values £4.90

**K003** Polyester capacitors, 10 each of these values: 0.01, 0.015, 0.022, 0.033, 0.047, 0.068, 0.1, 0.15, 0.22, 0.33, 0.47µF. 110 altogether for £4.75

**K004** Mylar capacitors, min 100V type. 10 each all values from 1000pF to 10,000pF. Total 130 for £4.45

**K005** Polystyrene capacitors, 10 each value from 10pF to 10,000pF, E12 series 5%, 160V. Total 370 for £12.30

**K1006** Tantalum bead capacitors, 10 each of the following: 0.1, 0.15, 0.22, 0.33, 0.47, 0.68, 1, 2.2, 3.3, 4.7, 6.8, all 35V; 10/25 15/16 22/16 33/10 47/6 100/3. Total 170 tanis for £14.20

**K007** Electrolytic capacitors 25V working, small physical size, 10 each of these popular values: 1, 2.2, 4.7, 10, 22, 47, 100µF. Total 70 for £3.50

**K008** Extended range, as above, also including 220, 470 and 1000µF. Total 10 for £5.90

**K021** Miniature carbon film 5% resistors, CR25 or similar, 10 of each value from 10R to 1M, E12 series. Total 610 resistors, £6.00

**K022** Extended range, total 850 resistors from 1R to 10M £8.30

**K041** Zener diodes, 400mW 5% BZY88, etc., 10 of each value from 27V to 36V, E24 series. Total 280 for £15.30

**K042** As above but 5 of each value £8.70

**PC ETCHING KIT MK III**  
Now contains 200 sq. ins. copper clad board, 1lb. Ferric Chloride, DALO etch-resist pen, abrasive cleaner, two miniature drill bits, etching dish and instructions. £4.15

**FERRIC CHLORIDE**  
Anhydrous technical quality in 1lb double sealed packs. 1lb £1.00; 3lb £2.18; 10lb £5.60; 100lb £39.00

**MOTORS**  
240V ac 60 rpm. High torque, drive to 6mm shaft 20mm long. Size 70mm dia x 55mm £2.20.

**LED DIGIT DRIVER**  
ITT type 7105, 16 pin DIL package. Supplied with data sheet. 8 for £1.

**VERO OFFCUTS**  
Pack A, All 0.1" Pack B, All 0.15" Pack C, Mixed Pack D, All 0.1" plain

Each pack contains 7 or 8 pieces with a total area of 100 sq. in. Each pack is £1.40. Also available by weight, 1lb £3.45, 10lb £28. We are also VERO wholesalers—Trade price list on request from Bone Fide Companies.

Our retail shops at 21 Deptford Broadway, London, SE8 (01-692 2009) and 38 Lower Addiscombe Road, Croydon (01-885 2950) stock some of the advertised goods for personal callers only. Ring them for details.

All prices quoted include VAT and UK/BFPO postage. Most orders despatched on day of receipt. SAE with enquiries please. **MINIMUM ORDER VALUE £1.** Official orders accepted from schools, etc. (Minimum invoice charge £5). Export/Wholesale enquiries welcome. Wholesale list now available for bona-fide traders. Surplus components always wanted.

## VEROCASES

Plastic top and bottom, ally panels front and back.

Type		£3-70
1410 205 × 140 × 40mm		
1411 205 × 140 × 75mm		£4-17
1412 205 × 140 × 110mm		£5-20
1237 154 × 85 × 40mm		£2-83
1238 154 × 85 × 60mm		£3-05
1239 154 × 85 × 80mm		£3-75

## PLASTIC BOXES

Professional quality, two tone grey polystyrene with threaded inserts for mounting PC Boards.

Type		£2-24
2518 120 × 65 × 40mm		
2520 150 × 80 × 50mm		£2-68
2522 188 × 110 × 60mm		£3-72

Slipping front version.

Type		£6-90
2523 220 × 174 × 100/52mm		
1798 171 × 121 × 75/37-5mm		£4-65

Gen. purpose plastic potting box 71 × 49 × 24. In black or white 40p. Hand Controller box, shaped for ease of use in the hand, 94 × 61 × 23mm 64p.

## RELAYS and SOLENOIDS

12V DC enclosed, 2 10A c/o contacts £1. Open construction relay with 2 10A c/o contacts, coil rated 24V ac, but works well on 6V DC 60p.

240V ac enclosed, 11 pin plug in base. 3 10A c/o contacts, £1.20.

240V ac open, 2 15A c/o contacts £1.50. 6V miniature low profile for PC mounting, 0.1" pitch. 2 pole c/o 137R coil—RS price £2.71—our price £1.60.

Solenoid, rated 48V DC, but work on 24V. 10mm push or pull action. Single hole fixing. Size 27 × 18 × 15mm. Made by Varley. Only 40p.

## WIRE AND FLEX

Flex pack—5m of 5 diff. colours, thick or thin. 25m for 25p. 25 way (14/0076) cable with braided overall screen and PVC sheath. 40p/m.

## EDGE CONNECTORS

Special purchase of these 0.1" pitch double-sided gold-plated connectors enables us to offer them at less than one-third their original list price!

18 way 41p; 21 way 47p; 32 way 72p; 40 way 90p; 43 way 97p; 49 way 111p.

## SOLAR CELLS

As used on space labs, etc., these tiny cells give 500A @ 0.5V in sunlight. Ideal for powering small C-MOS projects, etc. Can be banked together for greater power output. Size 19 × 6.5mm. 3 for £1; 10 for £3; 25 for £7; 100 for £25.

## POWER PACK

Wood grained metal case 90 × 80 × 75mm containing mains transformer giving 6V @ 200mA, 2 co-ax. sockets, PC board with 12" fuseholder R's C's, etc. Only £1.

## S-DECS & T-DECS

S-DEC Breadboard	£2-10
T-DEC Breadboard	£3-75

**1977/78 CATALOGUE NOW AVAILABLE — MUCH BIGGER AND BETTER, WITH 50p DISCOUNT VOUCHERS ONLY 30p, Plus 15p POST.**

## COMPONENT PACKS

400 asstd. carbon resistors	£1-50
100 Wirewounds 2-15W	£1-50
200 Miniature resistors, ½, ¼, and ⅓W	£1-30
200 poly, mica, ceramic caps	£1-20
100 polyester, .01-2-2uF	£1-00
200 PC resistors	75p

## FIBREGLASS PCB

Large quantity of offcuts, all usable pieces. 200 sq. ins. single-sided, double sided or mixed £1-50.

## 5V 12A REGULATED POWER SUPPLY

Brand new boxed fully stabilized PSU. Complete with instruction manual. Load regulation 0.15% Thermal & Electronic overload protection. Only £24.00.

ICs



TRANSISTORS



RESISTORS



DESPATCHED ON DAY ORDER RECEIVED

SWITCHES



LAMPS



PLUGS, SOCKETS



# ACE

**ORDERING IS EASY WITH THE UNIQUE COMBINED CATALOGUE/ORDER FORM**


ACE MAILTRONIX LTD  
Dept. PW Tootal Street  
Wakefield, W. Yorkshire WF1 5JR

SEND STAMP ADDRESSED ENVELOPE NOW FOR THE EASY TO USE ACE ORDER FORM CONTAINING 500 TOP QUALITY POPULAR ELECTRONIC COMPONENTS AT PRICES YOU CAN AFFORD. P&P FREE ON ORDERS OVER £2, OTHERWISE 20p. ALL PRODUCTS GUARANTEED ONE YEAR IF CORRECTLY USED. SOME EXAMPLES FROM THE COMPETITIVE ACE RANGE WITH VAT INCLUSIVE PRICES ARE SHOWN BELOW

BC107/108/109 Metal	13p	¼W Resistors CF±5%	3for6p
BC207/208/209 Plastic	11p	Minpresets Horiz/vert.	8p
2N3055	65p	Electrolytic 100, F25v	10p
741 Op Amp—8pin	30p	Polyester C280 0.1, F	8p
555 Timer	50p	LED Red 0.2"	15p
W04 1A Bridge	31p	Phono plugs	8p
7400 TTL	15p	Mintoggle SPST	80p
IN4148 Diode	4p	Wire-PVC Stranded 10m	25p
IN4001 Rec	5p	Veroboard 0.1 2.5x3-75	50p
BZY88 Zeners	12p	S-DEC Breadboard	216p

Get an ACE up your sleeve!

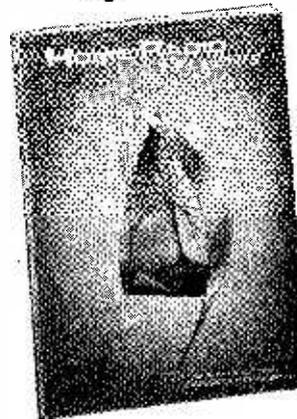**THIS is the Catalogue you need to solve your component buying problems!**



- The finest components catalogue yet published.
- Over 200 A-4-size pages.
- About 5,000 items clearly listed and indexed.
- Nearly 2,000 illustrations.
- Bargain List sent free.
- At £1.40, incl. p. & p., the catalogue is a bargain.

Send the coupon below now.

HOME RADIO (Components) LTD., Dept. PW., 234-240 London Road, Mitcham, Surrey CR4 3HD

POST THIS COUPON with cheque or P.O. for £1.40

Please write your Name and Address in block capitals

NAME .....

ADDRESS .....

.....

.....

HOME RADIO (Components) LTD., Dept. PW., 234-240 (Regn. No London Road, Mitcham, Surrey CR4 3HD London 912966)

# U.K. RETURN OF POST MAIL-ORDER SERVICE ALSO WORLD WIDE EXPORT SERVICE

## R.C.S. 100 watt MIXER/AMPLIFIER ALL VALVE CHASSIS



Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker outputs. A/C mains operated. Slave output. Produced by demand for a quality valve amplifier. Send for details.  
Suitable carrying cabinet £16. Carr. £2. Price **£94** carr. £2-50

## ANOTHER R.C.S. BARGAIN!

ELAC 9 + 5in. HI-FI SPEAKER TYPE 59RM  
This famous unit now available, 10 watts, 8 ohm.

Price **£3.45** Post 40p



## 10" ELAC HI-FI SPEAKER

Large ceramic magnet.  
Response: 50-12,000 cps.  
Bass resonance 55 cps.  
16 ohm impedance  
10 watts. Post 40p

**£4.50**

## TEAK VENEER HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 12in. For 12in. dia. or 10in speaker. **14.50** Post £1.60 Illustrated.

MODEL "B" BOOKSHELF  
For 13 x 5in. or 8in. **£8.50** Post £1 speaker

R.C.S. BOOKSHELF CABINET  
Size 16in. x 6in. x 5in. approx.  
Response 50 to 14,000 cps. 6 watts rms.  
8 ohms. **£16 pair** £1-30

LOUDSPEAKER CABINET WADDING  
18in. wide, 20p ft.



## GOODMANS CONE TWEETER

3 1/2in. diam. 18,000 C.P.S. 25 WATTS 8 Ω **£3.25**  
8in. Audax 15 watts £4.95.  
5in. EMI mid range £5.  
10in. 30 watt GOODMANS woofer 4 ohm £10.95.

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£6.75**

TWO CHANNEL STEREO VERSION OF ABOVE £8.50

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated or Mains Supply £2.95.

## THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/240V.  
Leaflet S.A.E. **£4.95** Post 40p



## WAFER HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/2in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photo-copiers and print drying equipment.

Ideal for home handyman and experimenters. Suitable for Heating Pads, Food Warmers, Convecter Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing onboards. Ideal for anti-frost device for the garage—prevents frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR £1.50)

ALL POST PAID—Discounts for quantity.

BLANK ALUMINIUM CHASSIS, 18 s.w.g. 2 1/2in. sides 6 x 4in. 70p; 8 x 6in. 90p; 10 x 7in. £1.15; 14 x 8in. £1.50; 16 x 6in. £1.45; 18 x 8in. 87p; 16 x 10in. £1.70. All boxes, many sizes in stock.

## DE LUXE BSR HI-FI AUTOCHANGER

Plays 12in. 10in. or 7in. records Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2in. Above motor board 3 1/2in. Below motor board 2 1/2in.



With CERAMIC STEREO/MONO CARTRIDGE **£17.50**  
Cueing Device, Bias Compensator, Balanced Arm, All Post 75p  
GARRARD MINTCHANGER, Plays All Records **£9.95**  
BSR P128 with Ceramic Cartridge **£19.50**

## BAKER MAJOR 12" £15.00



Post £1  
90-14,500 c/s. 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s rated 25 watts. NOTE: 4 or 8 or 16 ohms must be stated.

## MODULE KIT

30-17,000 c/s with tweeter, crossover, baffle 19 x 12 1/2in. Please state 4 or 8 or 16 ohms. **£19.00**

Post £1-60

## BAKER SPEAKERS "BIG SOUND"

Robustly constructed to stand up to long periods of electronic power. As used by leading groups.  
Useful response 30-13,000 cps.  
Bass resonance 55 cps.

### GROUP "25"

12in. 30 watt  
4, 8 or 16 ohms.

**£12.00**

Post £1

### GROUP "35"

12in. 40 watt  
4, 8 or 16 ohms.

**£14.00**

Post £1

### GROUP "50/12"

12in. 60 watt professional model. 4, 8 or 16 ohms.  
With aluminium presence dome.

**£21.00**

Post £1-60

### GROUP "50/15"

15in. 75 watt  
8 or 16 ohms.

**£26.00**

Post £1-60

Send for leaflets on Disco, P.A. and Group Gear.



## BAKER 150 WATT QUALITY TRANSISTOR MIXER/AMPLIFIER



Professional amplifier using advanced circuit design. Ideal for disco, groups, P.A. or musical instruments. 4 inputs 4 way mixing. Master treble, bass and volume controls. 3 speaker output sockets to suit various combinations of speakers.  
4-8-16 ohm. Slave output. A/C mains. Guaranteed. Details S.A.E. **£72** Carr. £1-00


## 100 WATT DISCO AMPLIFIER

MADE BY JENNINGS MUSICAL INSTRUMENTS  
4 Speaker outputs volume, treble, bass, controls  
CAN BE USED AS 100 WATT SLAVE **£59** Carr. £1

## B.S.R. SINGLE PLAYER DECK

3 speed. Plays all size records.  
Stereo Cartridge. Cueing device,  
Ideal Disco Deck.

**£13.50** Post 75p

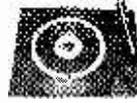

## DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Will control up to 500 watts AC mains. **£3.25**

Post 35p

STEREO PRE-AMP KIT. All parts to build this pre-amp. 3 inputs for high medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. **£2.95** Post 35p

## P.W. SOUND TO LIGHT DISPLAY

Complete kit of parts with R.C.S. printed circuit. Three channels. 600 to 1,000 watts each.  
As featured in Practical Wireless. Price **£14.00**  
Cabinet extra £3.

200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights. Edison Screw Fitting 75p. Each.

## MAINS TRANSFORMERS


Post 50p  
6 VOLT 1/2 AMP. £1.00 3 AMP. £1.40  
12 VOLT 300 MA. £1.00 750 MA. £1.30  
30 VOLT 5 AMP. AND 34 VOLT 2 AMP. C.T. £3.45  
20 VOLT 1 AMP. £2.00 3 AMP. £2.30 20-0-20 VOLT 1 AMP. £2.95  
30 VOLT 1/2 AMP. £2.50 40 VOLT 2 AMP. £2.95  
0-20-40-50 VOLT 1 AMP. £3.50 2 x 15 VOLT 6 AMP. £11.

GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at  
2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V £5-30  
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £5-30  
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8-50  
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11-00  
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £14-50

## R.C.S. BOOKSHELF SPEAKERS

13 x 10 x 6in.  
50 to 14,000 cps.  
8 watts rms. 8 ohms

**£16 pair** Post £1-30

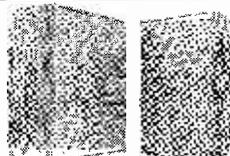

## BAKER DISCO SPEAKERS HIGH QUALITY—BRITISH MADE 2 x 12" CABINETS

For Disco or PA all fitted with carrying handles and corners. Black vinylene covered. Other cabinets in stock. SAE for leaflet

60  
WATT  
R.M.S.  
**£52**  
Carr. £3

80  
WATT  
R.M.S.  
**£56**  
Carr. £3

100  
WATT  
R.M.S.  
**£69**  
Carr. £4



1 x 15" + 1 x 12" 100 WATT CABINET  
Size 36" x 24" x 15" **£75.00.** Carr. £5  
Ideal for Disco, Organ or PA work.  
High quality. Full range.

## "SUPERB HI-FI"

### 12in 25 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.  
Bass Resonance 25cps  
Flux Density 16,500 gauss  
Useful response 20-17,000cps  
8 or 16 ohms models.

**£22.00** Post £1-60

## "AUDITORIUM"

### 12in. 35 watts

A full range reproducer for high power. Ideal for Hi-Fi and Discotheques, Electric Guitars, public address, multi-speaker systems, electric organs.  
Bass Resonance 35cps  
Flux Density 15,000 gauss  
Useful response 25-18,000cps  
8 or 16 ohms models.

**£21.00** Post £1-60

## "AUDITORIUM"

### 15in. 45 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home Hi-Fi.  
Bass Resonance 35cps  
Flux Density 15,000 gauss  
Useful response 20-14,000cps  
8 or 16 ohms models.

**£26.00** Post £1-60

Loudspeaker Cabinet Wadding 18in wide, 20p per ft.

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables, 68p.

## E.M.I. 13 1/2 x 8in SPEAKER SALE!

With tweeter. And crossover. **£7.95**  
10W. State 8 or 8 ohm. Post 45p

15W model **£10.50**  
8 ohms. Post 65p

GOODMANS 20W Woofer **£9.95**  
Size 12 x 10in 4 ohms. Post 65p



# RADIO COMPONENT SPECIALISTS

Minimum post 30p. Components List 20p.

Cash price includes VAT.

Access & Barclay cards welcome.

Rail Selhurst.

Tel. 01-684 1665

Practical Wireless, December 1977


337 WHITEHORSE ROAD, CROYDON

Open 9-6 Wed. 9-1 Sat. 9-5 (Closed for lunch 1.15-2.30)
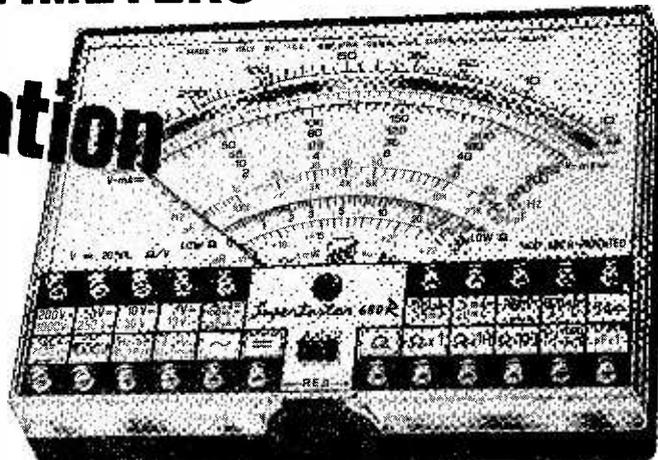
## I.C.E. MULTIMETERS

**TWICE the information  
in HALF the size**

The I.C.E. range of multimeters provide an unrivalled combination of maximum performance within minimum dimensions, at a truly low cost. Plus, a complete range of add-on accessories for more ranges, more functions.



### Supertester 680R (illustrated)

- \* 20kΩ/V, ±1% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 80 Ranges – 10 Functions
- \* 140 × 105 × 55mm

**£25.25 + VAT**

(For Mail Order add 80p P&P)

### Supertester 680G

- \* 20kΩ/V, ±2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 48 Ranges – 10 Functions
- \* 109 × 113 × 37mm

**£19.95 + VAT**

(For Mail Order add 80p P&P)

### Microtest 80

- \* 20kΩ/V, ± 2% fsd on d.c.
- 4kΩ/V, ±2% fsd on a.c.
- \* 40 Ranges – 8 Functions
- \* Complete with case – only 93 × 95 × 23mm

**£14.95 + VAT**

(For Mail Order add 80p P&P)


All I.C.E. multimeters are supplied complete with unbreakable plastic carrying case, test leads, etc. and a 50-plus page, fully detailed and illustrated Operating and Maintenance Manual.

Now available from selected stockists. Write or phone for list, or for details of direct mail-order service.



Electronic Brokers Ltd.  
49-53 Pancras Road, London NW1 2QB  
Tel: 01-837 7781
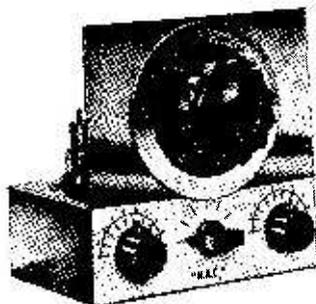
## H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality. "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Special offer AR8 valves—70p each.

### 1977 "DX" RECEIVER

Complete kit—Price £7.20 (incl. p. & p. and V.A.T.).

Customer who sent us five QSL cards, one from each continent writes: "Other countries of interest which I have heard are Korea, Japan, Sri Lanka, Liberia and many others. I was very surprised at the simplicity of the set, compared to its efficiency."

This kit is ready to assemble and contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Full range of other S.W. kits, including the famous model "K plus" (illustrated above). All orders despatched within 7 days. Send now for free descriptive catalogue of kits and components.

**SORRY, NO CATALOGUES WITHOUT S.A.E.**

"H.A.C." SHORT-WAVE PRODUCTS  
P.O. Box No. 16, 10 Windmill Lane  
Lewes Road, East Grinstead, West  
Sussex RH19 3SZ

## VALVE BARGAINS

Any 5-64p, 10-£1.20, 50-£5.00. Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL86, PCL805, PL504, PY81/800, PY88, 30PL14, 6F28, PFL200.

Colour Valves—PL508, PL509, PL519, PY500/A. All tested. 35p each.

Aerial Splitters—2 way, 75 OHMS, Inside Type, £1.50.

## AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11—For TH stereo and standard VHF/FM radio.  
B12—For the older VHF television—Please state channel numbers.

B45—For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs and sockets. Next to the set fitting. £4.20

## 100—C280/I CAPACITORS

Values from .01uF to 1.5uF, 250v/w. Price £1.50 (mixed packs).

## 100—ELECTROLYTICS

From 1uF to above 500uF. Mixed voltages. Price £2.00 (mixed packs).

All prices include VAT, P&P 30p per order. Please send uncrossed P.O. or cheques for returning if we are out of stock of capacitor bargain packs. Exports welcome at cost.

## ELECTRONIC MAILORDER LTD.

62 BRIDGE STREET, RAMSBOTTOM,  
BURY, LANCs.  
TEL: RAMS (070 682) 3036

## A KAISER battery recharger cuts down battery costs

Anyone who uses battery-powered equipment is only too aware of the spiralling cost of primary cell batteries. Fortunately, there is an answer — rechargeable nickel cadmium batteries coupled with the Kaiser recharge unit.

The mains-powered Kaiser unit is strongly constructed and of compact size. Although of advanced technical design, it operates extremely economically and will recharge 1 to 6 N.C. batteries within fourteen hours. The correct polar positions for the batteries are clearly shown, but should they be incorrectly inserted, no damage will result either to batteries or unit.

Further details of all Kaiser recharge units and N.C. batteries are available from

*Each 2 Mains*

136-144 Granville Road,  
London NW2 2LD

# CHROMASONIC electronics

56 Fortis Green Road  
Muswell Hill London N10 3HN  
Telephone 01-883 3705

## TRANSFORMERS

6-0-6V	100mA	1.00*
9-0-9V	75mA	1.00*
12-0-12V	100mA	1.15*
0-9-17V	1A	2.15*
0-9-17V	1A	3.25*
0-9-17V	4A	4.35*
20-0-20V+	1A	3.25*
24-0-24V	500mA	2.15*
0-19-25-33-40-50V+	1A	3.25*
0-19-25-33-40-50V+	1A	3.25*
0-19-25-33-40-50V+	2A	5.45*
0-12-15-20-24-30V+	1A	3.25*
0-12-15-20-24-30V+	2A	4.35*

Please add an extra 50p to items marked +

## DIODES

BA114 15p	BY105 25p	OA81 10p
BA115 25p	BY126 12p	OA200 10p
BA145 25p	BY127 12p	OA202 10p
BA148 20p	BY133 25p	IN814 5p
BA155 15p	BY182 1.65	IN4003 7p
BA156 15p	BY250 30p	IN4007 8p
BA X16 12p	OA47 12p	IN4148 5p
BB105B 5p	OA79 12p	IN5401 15p
BY103 25p	OA90 10p	IN5407 25p

## BRIDGES

1A 50V 25p	1A 400V30p	2A 50V 40p
1A 100V 25p	1A 600V 35p	2A 100V 45p
1A 200V 25p	1A 100V 40p	2A 100V 50p

## LIGHT EMITTING DIODES

9-125 (inc. clip)	1+	10+	100+
TIL209 Red	15p	13p	11p
TIL212 Yellow (H.B.)	27p	22p	17p
TIL216 Red (H.B.)	27p	22p	17p
TIL232 Green (H.B.)	27p	22p	17p

0.2" (Inc. Clip)  
TIL220 Red 15p 13p 11p  
TIL224 Yellow (H.B.) 30p 26p 20p  
TIL228 Red (H.B.) 30p 26p 20p  
TIL234 Green (H.B.) 30p 26p 20p  
(H.B.)—High Brightness.

## POLYESTER CAPACITORS

Mullard C280 Series 250v	6p	0.47µf	12p
0.01µf	5p	0.068µf	10p
0.015µf	5p	0.10µf	6p
0.022µf	5p	0.15µf	6p
0.033µf	5p	0.22µf	8p
0.047µf	5p	0.33µf	8p

Mullard C281 Series 400v

0.01µf	10p	0.068µf	15p	0.47µf	35p
0.015µf	10p	0.10µf	15p		
0.022µf	10p	0.15µf	15p		
0.033µf	12p	0.22µf	15p		
0.047µf	15p	0.33µf	20p		

## HEATSINKS

TO 92	7p*	TO 5 (5F)	9p*
TV 2	25p*	TO 18 (18F)	11p*
TV 3	25p*	U1 (TBA800)	16p*
TV 4	24p*	U2 (TBA10A5)	21p*
TV 5	24p*	U3 (TDA2020)	52p*
TV 16	33p*	AY 14	51p*
CH 106	31p*	1-18 E-17	80p*
3-15 E-18	1.10*	(For 1xTDA2020)	
(For 1xTDA2020)		3-15 E-19	1.57*
(For 2xTDA2020)			

Transistor Covers  
TO66 and TO3 12p\*

## ZENERS

BZ788	400mw 2.7V-33v	20p
12S	1w 3.6V-100v	10p

## I.C. SOCKETS

8 pin 10p	16 pin 14p	28 pin 30p*
14 pin 12p*	24 pin 26p*	40 pin 44p*
I.C. pins 100 54p*	1,000 23.78*	

## CERAMIC CAPACITORS

Mullard 632 Series	56pf	Mullard 630 Series	390pf
1-8pf	10pf	470pf	1800pf
2-2pf	12pf	560pf	2200pf
2-7pf	15pf	680pf	2700pf
3-3pf	18pf	820pf	3300pf
3-9pf	22pf	1000pf	3900pf
4-7pf	27pf	1500pf	4700pf
5-6pf	33pf	2000pf	4700pf
6-8pf	39pf	2200pf	5600pf
8-2pf	47pf	2700pf	3300pf

6p each

Mullard 629 Series  
0.01uf 0.022uf

## PLUGS AND SOCKETS

DIN Connectors	Plugs	Sockets	Line Couplers
1	14p	10p	18p
2	14p	10p	18p
3	14p	10p	18p
4	14p	10p	18p
5 (180)	14p	10p	18p
5 (240)	14p	10p	18p
6	14p	10p	18p
7	14p	10p	18p

## T.T.L.

Just a selection. Send for full list

7400 16p*	7430 16p*	7474 27p*	74121 27p*
7401 16p*	7441 56p*	7475 40p*	74123 49p*
7402 16p*	7442 52p*	7476 30p*	74141 41p*
7403 16p*	7445 70p*	7485 76p*	74145 65p*
7404 17p*	7447 59p*	7486 27p*	74151 49p*
7408 18p*	7448 65p*	7489 2.32*	74154 45p*
7410 16p*	7451 16p*	7490 38p*	74174 72p*
7413 27p*	7470 27p*	7492 41p*	74192 86p*
7420 16p*	7472 22p*	7493 41p*	74193 86p*
7427 28p*	7473 27p*	74107 27p*	74196 79p*

## C.Mos

4000 18p*	4014 1.00*	4024 78p*	4051 86p*
4001 18p*	2015 97p*	4025 18p*	4052 86p*
4002 18p*	4016 53p*	4026 1.76*	4060 1.16*
4006 1.09*	4017 97p*	4027 58p*	4068 22p*
4007 18p*	4018 58p*	4028 87p*	4070 22p*
4009 62p*	4019 58p*	4029 1.18*	4071 22p*
4010 62p*	4020 1.08*	4040 1.08*	4081 22p*
4011 18p*	4021 97p*	4042 83p*	4082 22p*
4012 21p*	4022 86p*	4049 58p*	4510 1.24*
4013 58p*	4023 19p*	4050 58p*	4511 1.54*

## POLYSTYRENE CAPACITORS

100pf	100pf	1000pf	10,000pf (0.01uf)
22pf	120pf	1200pf	
150pf	150pf	1500pf	
220pf	220pf	2200pf	
330pf	330pf	3300pf	
470pf	470pf	4700pf	
560pf	560pf	5600pf	
680pf	680pf	6800pf	
820pf	820pf	8200pf	

6p each

## JACK CONNECTORS

Type	Plastic	Chrome	Sockets	Line Couplers
2.5mm	15p	25p	12p	
3.5mm	15p	25p	12p	
Mono	—	30p	20p	
Stereo	—	37p	25p	

PHONO Connectors

Plugs	Sockets
Plastic Moulded 10p	1 way 8p
Chrome Screened 15p	2 way 12p
	3 way 12p
	4 way 14p

CO-AXIAL Connectors

Plug	Surface Socket	Coupler
16p	16p	43p

## LINEAR INTEGRATED CIRCUITS

uA703 (TO99)	£1.00	LM370N	£2.75	SL415A	£2.47
uA709 (8 pin DIL)	41p	LM371	£1.75	SL410A	£2.38*
uA709 (14 pin DIL)	41p	LM372N	£1.75	SN75491N	95p*
uA709 (TO99)	50p	LM373N	£2.99	SN75492N	£1.15*
uA709 (8 pin DIL)	50p	LM380N	£1.95	SN76001N	£1.40
uA710 (TO99)	55p	LM380N-8	£1.95	SN76003N	£2.45
uA710 (14 pin DIL)	55p	LM380N	£1.95	SN76013N	£1.60
uA711 (TO99)	98p	LM381N	£1.75	SN76015N	£1.60
uA711 (14 pin DIL)	98p	LM382N	£1.35	SN76033N	£2.45
uA741 (8 pin DIL)	25p	LM390N	65p	SN76544N	£1.55
uA741 (14 pin DIL)	42p	LM3905N	£1.50*	SN76532N	£1.55
uA741 (TO99)	45p	LM3909N	70p*	SN76532N	65p
uA847 (14 pin DIL)	90p	MC1303/LM1303N	£1.80	SN76565N	£1.00
uA748 (8 pin DIL)	42p	MC1310P	£1.80	SN76560N	65p
uA748 (14 pin DIL)	60p	MC1312P	£2.15	TAA283	£2.50
uA748 (TO99)	65p	MC1314P	£3.50	TAA320A	75p
uA753 (8 pin DIL)	£1.95	MC1315P	£6.10	TAA350A	£2.70
AY-1-0212	£8.50	MC1327P/TDA1327	£1.50	TAA570	£2.50
AY-1-5051	£1.65	MC1330P	£1.15	TBA120S	£1.00
AY-5-1224A	£3.39*	MC1350P	£1.00	TBA520Q	£2.00
AY-5-3507	£5.99*	MC1351P	£1.00	TBA530Q	£2.00
AY-5-4007	£7.99*	MC1352P	£1.00	TBA540Q	£2.00
CA3045	£1.50	MC1352P	£1.00	TBA540Q	£2.00
CA3046	80p	MC1352P	£1.00	TBA540Q	£2.00
CA3053	85p	MC1352P	£1.00	TBA540Q	£2.00
CA3075	£2.00	MC1352P	£1.00	TBA540Q	£2.00
CA5080	80p	MC1352P	£1.00	TBA540Q	£2.00
CA3081	£1.50	MC1352P	£1.00	TBA540Q	£2.00
CA3082	£1.50	MC1352P	£1.00	TBA540Q	£2.00
CA3089/TDA1200	£2.30	MC1352P	£1.00	TBA540Q	£2.00
CA3090C	£2.25	MC1352P	£1.00	TBA540Q	£2.00
CA3123C/LM1820	£1.50	MC1352P	£1.00	TBA540Q	£2.00
CA3097E	£1.75	MC1352P	£1.00	TBA540Q	£2.00
CA3130S	99p*	MC1352P	£1.00	TBA540Q	£2.00
CA3140S	99p*	MC1352P	£1.00	TBA540Q	£2.00
CA3160S	£1.00	MC1352P	£1.00	TBA540Q	£2.00
CA3600E	£1.75	MC1352P	£1.00	TBA540Q	£2.00
LM301AN (8 pin)	40p	MC1352P	£1.00	TBA540Q	£2.00
LM301AN (TO99)	50p	MC1352P	£1.00	TBA540Q	£2.00
LM308N (8 pin)	90p	MC1352P	£1.00	TBA540Q	£2.00
LM308T (8 pin)	£1.40	MC1352P	£1.00	TBA540Q	£2.00
LM339N	£1.00	MC1352P	£1.00	TBA540Q	£2.00

## SILVER MICA CAPACITORS

2-2pf	10p	68pf	10p	500pf	15p
3-3pf	10p	75pf	10p	560pf	15p
5pf	10p	82pf	10p	680pf	15p
10p	10p	100pf	10p	820pf	15p
18pf	10p	120pf	10p	1000pf	20p
20pf	10p	150pf	10p	1500pf	20p
22pf	10p	180pf	10p	1800pf	20p
25pf	10p	200pf	10p	2200pf	20p
27pf	10p	220pf	10p	2700pf	20p
30pf	10p	250pf	10p	3600pf	30p
33pf	10p	270pf	15p	4700pf	30p
39pf	10p	300pf	15p	5000pf	30p
47pf	10p	330pf	15p	6800pf	40p
56pf	10p	390pf	15p	8200pf	40p
50pf	10p	470pf	15p	0.01uf	40p

## SWITCHES

D.P.D.T. toggle	50p*
S.P.S.T. toggle	30p*
D.P.D.T. Slide	12p*
D.P.D.T. Slide Miniature	15p*
Push to Make Miniature	18p*

## RESISTORS

Type	Range	Value	Price
1/2 watt 5% Carbon film	E12 Series 10R-1M	2p each	
1 watt 5% Carbon film	E24 Series 3-3R-10M	2p ea.	
1 watt 5% Carbon film	E12 Series 10R-1M	5p each	

## POTENTIOMETERS

5K 250K	Lin and Log less Switch (inc. in Lin)	27p
10K 500K	Lin and Log Dual less Switch	75p
25K 1M	Lin and Log with Switch	60p
50K 2M</		

### SUPERSOUND 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high  $\times$  6" wide  $\times$  7 1/2" deep. AC 200/250V. PRICE  $\pounds$ 15.00. P. & P.  $\pounds$ 1.20.

### HARVERSON MODEL P.A.

#### TWO ZERO

An advanced solid state general purpose mono amplifier suitable for Public Address system, Disco, Guitar, Gram, etc. Features 3 individually controlled inputs (each input has a separate 2 stage pre-amp). Input 1-5mV into 47k. Input 2-5mV into 47k. (suitable for use with mic. or guitar etc.). Input 3 100mV into 1 meg. suitable for gram, tuner, or tape etc. Full mixing facilities with full range bass & treble controls. All inputs plug into standard jack sockets on front panel. Output socket on rear of chassis for an 8 ohm or 16 ohm speaker. Output in excess of 20 watts R.M.S. Very attractively finished purpose built cabinet made from black vinyl covered steel, with a brushed anodised aluminium front escutcheon. For ac mains operation 200/240v. Size approx. 12 1/2" w.  $\times$  5" h.  $\times$  7 1/2" d. Special introductory Price  $\pounds$ 28.00  $\pounds$ 2.50 carr. & pkg. Mullard LP1159 RF-IF Module 470 kHz  $\pounds$ 2.25 + P. & P. 20p. Full spec. and connection details supplied. Pye VHF/FM Tuner Head covering 88-108 M/Hz. 10.7 M/Hz I.F. output. 7.8 Volt  $\pm$  earth. Supplied pre-aligned, with full circuit diagram with precision-seared FM gang and 323Pf + 323Pf A.M. Tuning gang only  $\pounds$ 3.15 + P. & P. 35p.



### MAINS OPERATED SOLID STATE AM/FM STEREO TUNER



200/240V Mains operated Solid State FM AM Stereo Tuner. Covering M.W. A.M. 540-1605 KHz VHF/FM 88-108 MHz. Built-in Ferrite rod aerial for M.W. Full AFC and AGC on AM and FM. Stereo Beacon Lamp Indicator. Built in Pre-amps with variable output voltage adjustable by pre-set control. Max o/p Voltage 600mV RMS into 20K. Simulated Teak finish cabinet. Will match almost any amplifier. Size 8 1/2" w.  $\times$  4" h.  $\times$  9 1/2" d approx. **LIMITED NUMBER ONLY at  $\pounds$ 28.00 +  $\pounds$ 1.50 P. & P.** Push Button Switch bank. 8 Buttons giving 16 S/P C/O interlocked switches plus 1 Cancel Button Plus 3 d/p c/o. Overall size 5"  $\times$  2 1/2"  $\times$  1". Supplied complete with chrome finished switch buttons. 2 for  $\pounds$ 1.80 + 20p P. & P.

#### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL34s in push-pull. Super reproduction of both music and speech with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL34s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 25p + SAE (Free with parts). All parts sold separately. ONLY  $\pounds$ 13.50 P. & P.  $\pounds$ 1.40. Also available ready built and tested  $\pounds$ 18.00 P. & P.  $\pounds$ 1.40.

#### "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2"  $\times$  14 1/2"  $\times$  1 1/2" deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only  $\pounds$ 8.40 each + p. & p. (one 90p, two  $\pounds$ 1.10). Now available in either 8" round version or 4 1/2"  $\times$  8 1/2" rectangular. 10 watts RMS 60Hz-20KHz  $\pounds$ 5.25 + P. & P. (one 65p, two 75p).

**SPECIAL OFFER.** 6 1/2" long throw, roll surround, ceramic magnet 8 ohm 10 watt speaker chassis. Specially suitable for Hi Fi.  $\pounds$ 3.95 + 75p P. & P.

2" PLASTIC CONE HF TWEETER 4 ohm,  $\pounds$ 3.50 per matched pair + 50p P. & P.

### HARVERSONIC SUPERSOUND 10 + 10 STEREO AMPLIFIER KIT

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integral pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge—instructions included. Output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metalwork, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification; Power output: 14 watts r.m.s. per channel into 5 ohms. Frequency response  $\pm$  3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M  $\Omega$ ; Full power bandwidth:  $\pm$  3dB 12-15,000 Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w.  $\times$  8" d.  $\times$  2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 25p plus large S.A.E. **AMPLIFIER KIT**  $\pounds$ 13.50 P. & P. 80p (Magnetic input components 33p extra) **POWER PACK KIT**  $\pounds$ 5.50 P. & P. 95p **CABINET**  $\pounds$ 5.50 P. & P. 95p

**SPECIAL OFFER—only  $\pounds$ 23.75 if all 3 items ordered at one time plus  $\pounds$ 1.25 p. & p.** Full after sales service. Also avail. ready built and tested  $\pounds$ 31.25. P. & P.  $\pounds$ 1.50.

#### HARVERSONIC STEREO 44

A solid state stereo amplifier chassis, with an output of 3-4 watts per channel into 8 ohm speakers. Using the latest high technology integrated circuit amplifiers with built in short term thermal overload protection. All components including rectifier smoothing capacitor, fuse, tone control, volume controls, 2 pin din speaker sockets & 5 pin din tape rec./play socket are mounted on the printed circuit panel, size approx. 9 1/2"  $\times$  2 1/2"  $\times$  1" max. depth. Supplied brand new & tested, with knobs, brushed anodised aluminium 2 way escutcheon (to allow the amplifier to be mounted horizontally or vertically) at only  $\pounds$ 9.00 plus 50p P. & P. Mains transformer with an output of 17v a/c at 500mA/a can be supplied at  $\pounds$ 1.50 + 40p P. & P. if required. Full connection details supplied.

**STILL AVAILABLE.** 3 Valve Audio Amp. 4 1/2 w. output  $\pounds$ 8.50 +  $\pounds$ 1.40 P. & P. Also HSL 'FOUR' amplifier kit.  $\pounds$ 8.00 +  $\pounds$ 1.40 P. & P.

All prices and specifications correct at time of press and subject to alteration without notice.

## HARVERSON SURPLUS CO. LTD.

(Dept. P.W.) 170 HIGH ST., MERTON, LONDON, S.W.19. Tel.: 01-540 3985

A few minutes from South Wimbledon Tube Station.

Open 9.30-5.30 Monday to Friday. 9.30-5 Saturday. Closed Wednesday.

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. SEND SAE WITH ALL ENQUIRIES.

## BURGLAR ALARM

### EQUIPMENT SUPPLIES (TRADE)

Bell boxes plastic coated steel	$\pounds$ 5.25
Magnetically operated door switch surface type	$\pounds$ 9.65
Magnetically operated door switch flush type	$\pounds$ 9.60
Vibro sensitive switch	$\pounds$ 2.75
Pressure pads large 29" $\times$ 15" 4 wires	$\pounds$ 1.75
Pressure pads stair tread size 4 wires	$\pounds$ 1.50
Aluminium window foil 100ft, self adhesive	$\pounds$ 2.00
Take off blocks for window foil per pair	$\pounds$ 0.40
Heavy duty 6" bell 12V	$\pounds$ 7.75
Siren 12V	$\pounds$ 6.00
3" bell	$\pounds$ 2.25
Key switch single pole + chrome plate	$\pounds$ 3.00
Battery for above large HP1	$\pounds$ 2.50
Kojak horn	$\pounds$ 16.00

### CONTROL UNITS

Battery operated model	$\pounds$ 14.00
Battery and mains model	$\pounds$ 19.00
B.S. 4737 model battery + mains	$\pounds$ 32.00
D.I.Y. battery model	$\pounds$ 11.00
D.I.Y. battery + mains	$\pounds$ 15.00

ALL PRICES + 12 1/2% VAT—NO VAT EXPORTS

## ASTRO ALARMS

25 STOCKTON ROAD, SUNDERLAND, TYNE & WEAR, ENGLAND. TEL: 0783 77825

SAE FREE LIST FOR SPECIAL EQUIPMENT

DISCOUNTS PER ITEM  
5+ 10%  
25+ 15%  
100+ 20%  
POST FREE

## PRACTICAL WIRELESS T.V. SOUND TUNER

(Nov. 75 article by A. C. Ainslie)

Copy of original article supplied on request

IF Sub-Assembly (G8)  $\pounds$ 6.80. P & P 75p.  
Mullard ELC1043 V'cap UHF Tuner  $\pounds$ 4.50. P & P 35p.  
3-way Station Control Unit  $\pounds$ 1.20. P & P 25p.  
6-way Station Control Unit (Special Offer)  $\pounds$ 1.00.  
Power Supply Prtd Circuit Board  $\pounds$ 1.00. P & P 30p.  
Res, Caps, Semiconds, etc. for above  $\pounds$ 5.80.  
Mains Transformer for above  $\pounds$ 2.50. P & P 30p.  
Add 12 1/2% VAT to price of goods. P & P all items 85p.

Callers welcome at shop premises.

## MANOR SUPPLIES

172 WEST END LANE, LONDON NW6 (Near W. Hampstead Tube Stn.) Tel. 01-794 8751

For Semi-Conductors including

Small Signal Transistors  
Power Semi-conductors  
TTL, CMOS, I.Cs  
Linear I.Cs  
Signal and Power Diodes  
Zener Diodes  
Magneto Resistors  
Hall-effect devices  
Magnetic Proximity Switches  
Opto-electronic devices

Go to

**ELECTROVALUE**

TO MAKE THE BEST OF

For passive components

including

Plastic Film Capacitors  
Electrolytics  
Semi-precision capacitors  
Transformers  
Pot Cores  
R.M. Cores  
Ring Cores, etc.

Go to

**ELECTROVALUE**

THE PROJECTS YOU BUILD

The Open Door to Quality

It's the Electrovalue Catalogue No. 8 (4th edition black and white cover) with completely up-dated prices. 144 pages, well illustrated. 40p post free with 40p voucher usable on orders for  $\pounds$ 5 or more. Send for yours now and order in confidence.

GOODS SENT POST FREE IN U.K.

FOR C.W.O. ORDERS. Keenly competitive prices plus ATTRACTIVE DISCOUNTS and only best quality goods.

**ELECTROVALUE LTD**

(Dept. P.W.11) 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB.  
Phone: Egham 3603. Telex: 264475.

North—680 Burnage Lane, Burnage, Manchester  
Phone: (061) 432 5945.

**SENSATIONAL NEWS!**

**Hi-Fi Stereo at prices everyone can afford**

**Hi-Fi Stereo Speakers**

OUR PRICE **£4.95**

Specify matching 16mm x 25mm terminals. Includes complete leads for DIN connection.



**Hi-Fi Stereo BSR Antiknacker**

OUR PRICE **£12.95**

1. Special BSR Antiknacker. 2. 16mm x 25mm terminals. 3. 16mm x 25mm terminals. 4. 16mm x 25mm terminals. 5. 16mm x 25mm terminals.



**Hi-Fi Stereo Tantalum Amplifier chassis**

OUR PRICE **£29.95**

30 watts total power output. 16mm x 25mm terminals. 16mm x 25mm terminals. 16mm x 25mm terminals. 16mm x 25mm terminals.



**Hi-Fi Stereo Cassette deck**

OUR PRICE **£39.95**

16mm x 25mm terminals. 16mm x 25mm terminals. 16mm x 25mm terminals. 16mm x 25mm terminals.



1.E.W.I.S. Radio 100 Chase Side, Southgate, London N14 5PL—Tel: 01-882 1644. CALLERS WELCOME—ACCESS & BARCLAY CARD ORDERS ACCEPTED.

**LYNX ELECTRONICS (LONDON) LTD**

92 BROAD STREET, CHESHAM, BUCKS

Tel. (02405) 75154

P. and P. 30p — Overseas 90p — Matching 20p per pair. ACCESS WELCOME  
VAT 8% except for items \* which are 12½% — No VAT Overseas.

**RETURN POST SERVICE**

Prices correct as at 31st July '77

**THE HOME COMPUTER FORUM**

Our Seminar will be held on 26th November at the Wembley Conference Centre, 10.00 a.m. — 5.00 p.m. We hope to have five speakers from various backgrounds, but all specialists in the microcomputing/software field. The NASCOM B microcomputer will be launched at the seminar. Tickets at £3.50 each are now available together with a newsheet on the seminar. Please write or phone for details. Only 400 seats are available and 115 have been sold at press time.

**SUPER SAVERS**

MM5314	3.25	TIL209	0.10
MM5316	3.85	FCS8000	} 2.95
MC1310P	0.95	3½ Digit Disp.	
SG309K	0.95	FCS 8024	} 3.50
		4 Digit Disp.	

**THYRISTORS**

PIV	1A (TO5)	3A (ST-UD)	3A (C 106)	4A (TO 220)	6A (TO 220)	8A (TO 220)	10A (TO 220)	16A (TO 220)
200	0.35	0.50	0.45	0.40	0.58	0.60	0.88	1.14
400	0.40	0.60	0.50	0.45	0.67	0.86	0.98	1.40
600	0.65	0.95	0.70	—	1.09	1.19	1.28	1.80

BT106 £1.00, BT107 £1.60, BT108 £1.60, BT109 £1.00, BT116 £1.00, 2N325 £0.50.

**IMPORTANT NOTICE**

All schools, colleges, universities and amateur radio and electronic clubs may deduct 10% off pre-VAT prices. Offer valid till 31st October.

**TRIACS—Plastic TO-220 Package Isolated Tab**

	4A		6-5A		8-5A		10A		15A	
	(a)	(b)								
100V	0.60	0.50	0.70	0.70	0.78	0.78	0.83	0.83	1.01	1.01
200V	0.64	0.54	0.75	0.75	0.87	0.87	0.97	0.97	1.17	1.17
400V	0.77	0.78	0.80	0.83	0.97	1.01	1.13	1.19	1.70	1.74
600V	0.96	0.99	1.01	1.10	1.21	1.26	1.42	1.50	2.11	2.17

N.B.—(a) without internal diac. (b) with internal diac.

**PRICE LIST**

20p

Diodes contd	
BYX36-900	0.18
BYX36-1200	0.21
BYX38-300	0.50
BYX38-600	0.55
BYX38-900	0.60
BX38-1200	0.65
BZX61 Series	0.26
BZX83 Series	0.11
BZY88 Series	0.11
OA5	0.50*
OA10	0.40
OA85	0.12
OA90	0.08
OA91	0.08
OA200	0.08
BA156	0.12
BA157	0.22
BA158	0.22
BA159	0.25
BY206	0.15
BY207	0.20*
BYX36-300	0.12
IN4005	0.08
IN4008	0.08
IN4007	0.10
IN4148	0.04

**TTL7400 Series**

7400	0.16	7405	0.16	7410	0.16	7415	0.16	7420	0.16	7425	0.16	7430	0.16	7435	0.16	7440	0.16	7445	0.16	7450	0.16																																																																				
7401	0.16	7402	0.16	7403	0.16	7404	0.16	7406	0.16	7408	0.16	7409	0.16	7410	0.16	7411	0.16	7412	0.16	7413	0.16	7414	0.16	7417	0.16	7418	0.16	7419	0.16	7421	0.16	7422	0.16	7423	0.16	7424	0.16	7426	0.16	7427	0.16	7428	0.16	7429	0.16	7431	0.16	7432	0.16	7433	0.16	7434	0.16	7437	0.16	7441AN	0.16	7442	0.16	7443	0.16	7444AN	0.16	7445	0.16	7447AN	0.16	7448	0.16	7449	0.16	7451	0.16	7452	0.16	7453	0.16	7454	0.16	7455	0.16	7456	0.16	7457	0.16	7458	0.16	7459	0.16

**Regulators**

723	1.45	724	1.45	725	1.45	726	1.45	727	1.45	728	1.95	729	1.95	730	1.95	731	1.95	732	1.95	733	1.95	734	1.95	735	1.95	736	1.95	737	1.95	738	1.95	739	1.95	740	1.95	741	1.95	742	1.95	743	1.95	744	1.95	745	1.95	746	1.95	747	1.95	748	1.95	749	1.95	750	1.95
-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------	-----	------


**NPN TO-3 Power Transistors**

Fully tested. Similar to 2N3055 except: BVCEO = 50+ HFE(gain) = 20+ at 3A, VCE SAT < 1.3V at 3A. 5 pps £1.00, 25 pcs £4.00, 50 pcs £7.50, 100 pcs £13.00. TO-18 NPN Transistors. Medium Voltage, High Gain unmarked. Similar to BC107/8/9. 25 pcs £1.20, 100 pcs £3.50. TO-3 Hardware. Mica Washers, Solder tag, Nuts, Bolts, 50 sets for 65p. Rectifiers DO-4 Package. 10A 50V 0.45. 10A 100V 0.50. 10A 200V 0.60. 10A 400V 0.75. Please specify Polarity, Stud Cathode or Stud Anode. Ideal for Power Supplies, Inverters, etc.

**Transistors**

AC126	0.15	BC147	0.09*	BD132	0.40	BFX30	0.23	OC45	0.32	2N3053	0.20	CMOS PLASTIC	
AC127	0.16	BC149	0.09*	BD135	0.36*	BFX45	0.23	OC46	0.20	2N3055	0.20	4000BE	0.20
AC128	0.16	BC157	0.09*	BD137	0.40*	BFX88	0.25	OC70	0.30	2N3137	1.10	4001BE	0.20
AC128K	0.25	BC158	0.09*	BD138	0.48*	BFX87	0.20	OC72	0.22	2N3442	1.20	4002BE	0.20
AC141	0.22	BC159	0.09*	BD139	0.48*	BFX88	0.20	OC84	0.40	2N3570	3.60	4006BE	1.05
AC141K	0.34	BC160	0.32	BD144	2.20	BFY11	1.10	OC139	1.30	2N3702	0.10*	4007BE	0.20
AC142	0.18	BC161	0.32	BD157	0.66	BFY18	0.50	OC140	1.30	2N3703	0.10*	4008BE	0.93
AC176	0.16	BC168	0.09*	BD181	0.86	BFY40	0.50	OC170	0.25	2N3704	0.10*	4009BE	0.52
AC176K	0.32	BC169C	0.41*	BD182	0.92	BFY41	0.60	OC170	0.25	2N3705	0.10*	4011BE	0.20
AC187	0.18	BC182	0.11*	BD184	1.20	BFY50	0.20	TIP29A	0.44*	2N3706	0.10*	4012BE	0.20
AC187K	0.36	BC182L	0.12*	BD232	0.60	BFY51	0.18	TIP30A	0.52*	2N3707	0.10*	4013BE	0.50
AC188	0.18	BC183	0.10*	BD233	0.48	BFY52	0.19	TIP32A	0.64	2N3708	0.09*	4014BE	1.00
AC188K	0.32	BC183L	0.10*	BD237	0.55	BFY53	0.25	TIP42A	0.72	2N3709	0.09*	4015BE	0.95
AD149	0.80	BC184	0.11*	BD238	0.60	BFY54	0.35	2N404	0.40	2N3710	0.10*	4016BE	0.54
AD161	0.35	BC184L	0.12*	BD238	0.60	BFY90	0.90	2N497	0.20	2N3711	0.10*	4017BE	1.00
AD192	0.35	BC184L	0.12*	BD410	2.30	BSX19	0.16	2N697	0.20	2N3715	1.70	4018BE	1.10
AF114	0.20	BC186	0.20*	BD411	2.50	BSX20	0.18	2N706	0.15	2N3716	1.80	4019BE	0.50
AF115	0.20	BC187	0.24*	BDY10	1.00	BSX21	0.20	2N706	0.15	2N3717	1.60	4020BE	1.12
AF116	0.20	BC207B	0.11*	BDY11	2.00	BSX22	0.18	2N711	0.15	2N3722	1.90	4021BE	1.03
AF117	0.20	BC212L	0.11*	BDY20	0.80	BSY52	0.28	2N1132	0.16	2N3773	2.20	4022BE	0.95
AF118	0.20	BC212L	0.11*	BDY38	0.60	BSY53	0.39	2N1302	0.40	2N3775	0.10*	4023BE	0.20
AF118	0.20	BC213	0.12*	BDY60	1.60	BSY54	0.33	2N1303	0.40	2N3775	0.10*	4023BE	0.20
AF124	0.25	BC213L	0.14*	BDY61	1.75	BSY55	0.33	2N1304	0.45	2N3775	0.10*	4024BE	0.86
AF125	0.25	BC214	0.14*	BDY62	1.75	BSY56	0.33	2N1305	0.45	2N3775	0.10*	4025BE	0.86
AF126	0.25	BC214L	0.15*	BDY95	1.15	BSY76	0.20	2N1306	0.50	2N4870	0.35*	4026BE	1.55
AF139	0.35	BC214L	0.15*	BDY96	1.96	BSY78	0.75	2N1307	0.50	2N4918	0.60*	4027BE	0.62
AF239	0.37	BC237	0.16*	BF179	0.30	BSY95A	0.15	2N1308	0.60	2N4919	0.70*	4028BE	0.91
AL102	1.45	BC300	0.34	BF180	0.30	BU105	1.80*	2N1309	0.60	2N4920	0.50*	4029BE	1.10
AL103	1.30*	BC301	0.32	BF181	0.30	BU105/02	1.90*	2N1711	0.24	2N4921	0.50*	4030BE	0.55
AU107	3.90*	BC302	0.40	BF182	0.30		1.90*	2N2102	0.44	2N4922	0.50*	4041BE	0.80
AU110	1.60*	BC303	0.46	BF183	0.30		3.00*	2N2171	0.24	2N4923	0.50*	4042BE	0.83
AU113	1.60*	BC303	0.46	BF184	0.20		2.50*	2N2172	0.24	2N4924	0.50*	4043BE	1.00
BC107B	0.12	BCY30	0.55	BF184	0.20		1.60*	2N2369A	0.14	2N4925	0.50*	4044BE	0.94
BC108	0.12	BCY32	0.60	BF185	0.20		1.60*	2N2483	0.20	2102A-6	3.60	4046BE	1.32
BC108B	0.12	BCY33	0.55	BF194	0.10*		1.60*	2N2484	0.16	2112A-4	4.75	4049BE	0.54
BC109	0.12	BCY34	0.55	BF196	0.12*		1.90*	2N2646	0.50	6508	7.95	4050BE	0.50
BC109B	0.12	BCY38	0.55	BF197	0.12*		2.40*	2N2711	0.20	2102	2.50	4059BE	0.34
BC109C	0.12	BCY38	0.55	BF224J	0.18*		2.40*	2N2712	0.15	2107	10.00	4070BE	0.20
BC111	0.16*	BCY39	1.15	BF244	0.17*		2.60*	2N2904A	0.20	2112	4.50	4071BE	0.50
BC119	0.25	BCY40	1.30	BF257	0.30		0.80	2N2905	0.18	2513	8.50	4072BE	0.26
BC125	0.16*	BCY54	1.60	BF336	0.35*		0.90	2N2905A	0.22	2602	2.50	4082BE	0.26
BC126	0.20*	BCY70											

# CHASSIS & CASES

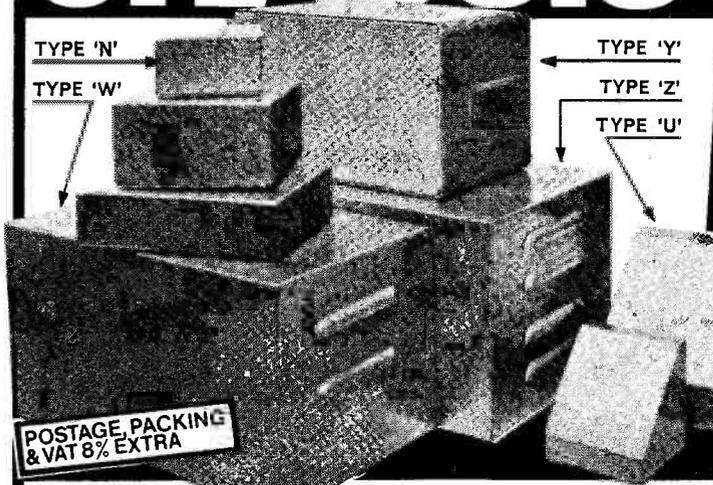

POSTAGE, PACKING & VAT 8% EXTRA

### BLANK CHASSIS

#### FOUR-SIDED 16 SWG ALUMINIUM

Size	Price	Base	Size	Price	Base
6" x 4" x 2"	75p	34p	10" x 8" x 2 1/2"	£1.45	70p
7" x 4" x 2"	70p	37p	12" x 7" x 2 1/2"	£1.50	74p
8" x 4" x 2"	85p	40p	12" x 9" x 2 1/2"	£1.70	86p
8 1/2" x 5 1/2" x 2"	£1.05	40p	13" x 8" x 2 1/2"	£1.70	86p
10" x 7" x 2"	£1.10	53p	14" x 7" x 2 1/2"	£1.65	86p
12" x 4" x 2 1/2"	£1.05	59p	14" x 10" x 2 1/2"	£1.80	83p
12" x 4" x 2 1/2"	£1.15	46p	15" x 10" x 2 1/2"	£1.95	£1.08
12" x 5" x 3"	£1.45	52p	15" x 10" x 3"	£2.05	£1.15
		59p	17" x 10" x 3"	£2.45	£1.28

#### TO FIT OUR CASES

Size	Price	Base
7" x 5 1/2" x 1 1/2"	80p	45p
11" x 5 1/2" x 1 1/2"	90p	45p
11" x 6 1/2" x 1 1/2"	£1.10	69p
12" x 6 1/2" x 2"	£1.25	69p
14" x 6 1/2" x 2"	£1.35	74p
15 1/2" x 9 1/2" x 2 1/2"	£1.65	£1.00
17 1/2" x 9 1/2" x 2 1/2"	£2.15	£1.22
	£2.35	£1.35

PANELS: Any size up to 3ft. at 86p sq. ft. 16 s.w.g. (18 s.w.g. 58p)

### INSTRUMENT CASES

#### 16 SWG ALUMINIUM, SILVER HAMMER FINISH

TYPE 'U'	W	D	Price
3" x 3" x 3"			£1.40
4" x 4" x 4"			£1.75
5 1/2" x 4 1/2" x 4 1/2"			£2.20
8" x 6" x 6"			£3.00
9 1/2" x 7 1/2" x 3 1/2"			£3.25
12" x 7" x 7"			£4.20
16" x 10" x 6"			£6.15
15" x 9" x 9"			£6.45

TYPE 'W'	W	D	Price
8" x 6" x 6"			£4.20
11 1/2" x 5" x 7"			£4.70
12" x 7" x 7"			£5.40
15" x 9" x 8"			£7.45

#### TYPE 'Y' Louvers on back

*L	W	D	Price
8" x 6" x 6"			£4.65
12" x 7" x 7"			£5.95
15" x 7" x 9"			£6.90
15" x 9" x 7"			£7.40

#### TYPE 'Z'

17" x 10" x 9"			£8.80
19" x 10" x 8 1/2"			£9.25

#### TYPE 'N' chassis with base plate

4" x 4" x 2"			£1.75
6" x 6" x 2"			£2.50
8" x 6" x 2"			£2.50

\*L = side to side. W = back to front. D = top to bottom  
 Type "U" has removable bottom or back, type "W" removable front, type "Y" all-screwed construction, type "Z" removable back + front.

### CHASSIS WITH BASE

#### Plain Aluminium

5" x 4" x 2 1/2"	£1.10	(16s.w.g.)
3" x 2" x 1"	55p	(16s.w.g.)
4" x 2 1/2" x 1 1/2"	65p	"
4 1/2" x 3" x 2"	75p	"
3 1/2" x 3 1/2" x 2 1/2"	80p	"
6 1/2" x 2 1/2" x 1 1/2"	80p	"


## H.L. SMITH & CO. LTD.

287-289 EDGWARE ROAD, LONDON W2 1BE  
 TELEPHONE: 01-723 5891
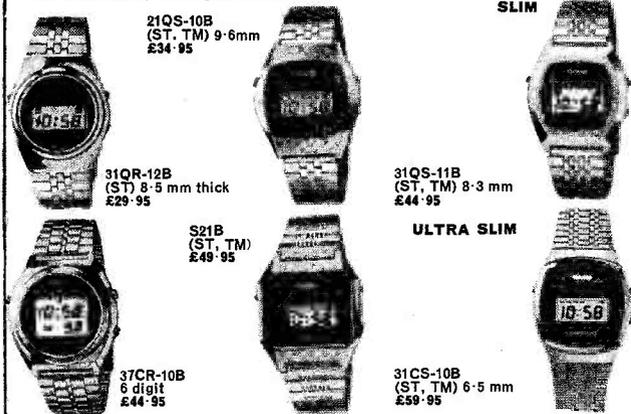
## NEW FROM CASIOTRON

Casiotron watches are probably the success story of the decade and rightly so!

We proudly announce a new range of these superb quality watches at lowest ever prices. They all have a constant liquid crystal display of hours, minutes, seconds, AM-PM/day, date and month, with night illumination and automatic 28, 30 and 31 day calendar. In new ultra slim Stainless Steel cases, with mineral glass face, they are anti-magnetic, shock resistant and water resistant to 100 feet. Most have a Stopwatch (ST) from 1 second to 13 hours and some also have Dual Time Zone (TM), second time memory. Display life expectancy of over 6 years. Can be easily changed at low cost.



LADIES MODEL 27CL-10B £49.95. Available soon: ALARM WATCH with stopwatch  
 Many other digital and quartz analogue watches, Stopwatches, clocks, car clock, T/V games, Casio scientific calculators. Accurist, Citizen, Ibcio, N-S, Fairchild Timeband etc.  
 Send 15p for our illustrated catalogue. Lowest discount prices.  
 Prices include VAT, P&P. Send cheque, P.O. or phone your credit card number to:-

**TEMPUS** Dept. P.W.,  
 19/21 Fitzroy Street,  
 Cambridge CB1 1EH  
 Tel. 0223 312866



## Wilmslow Audio

THE firm for speakers!

SEND 10P STAMP FOR THE WORLD'S BEST CATALOGUE OF SPEAKERS, DRIVE UNITS, KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST.

- ATC ● AUDAX ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EMI ● EAGLE ● ELAC ● FANE ● GAUSS ● GOODMANS ● HELME ● I.M.F. ● ISOPHON ● JR ● JORDAN WATTS ● KEF ● LEAK ● LOWTHER ● MCKENZIE ● MONITOR AUDIO ● PEARLESS ● RADFORD ● RAM ● RICHARD ALLAN ● SEAS ● TANNOY ● VIDEOTONE ● WHARFEDAILE

## WILMSLOW AUDIO (Dept. P.W.)

SWAN WORKS, BANK SQUARE, WILMSLOW, CHESHIRE SK9 1HF  
 Discount HiFi Etc. at 5 Swan Street and 10 Swan Street  
 TEL: WILMSLOW 29599 FOR SPEAKERS  
 WILMSLOW 26213 FOR HIFI

## SOUND TO LIGHT UNIT

Add colour or white light to your amplifier. Will operate 1, 2 or 3 lamps (maximum 450W). Unit in box all ready to work. £8.95 plus £1.00 VAT & Postage.



## MAINS OPERATED SOLENOIDS



Model TT2—small but powerful lin. pull—approx. size  $1\frac{1}{2} \times 1\frac{1}{2} \times 1\frac{1}{2}$  in. £1.00.  
Model 4001/—2 in. pull. Size  $2\frac{1}{2} \times 2 \times 1\frac{1}{2}$  in. £1.50.  
Model TT10—1 1/2 in. pull. Size  $3 \times 2\frac{1}{2} \times 2$  in. £4.50.  
Prices include VAT & postage.

## PP3/PP9 REPLACEMENT MAINS UNIT

Japanese made in plastic container with leads size  $2'' \times 1\frac{1}{2}'' \times 1\frac{1}{2}''$ , this is ideal to power a calculator or radio, it has a full wave rectified and smoothed output of 9 volts suitable for a loading of up to 100mA. £2.53.



## 3 NEW BOOKS BY G. C. DODDS

Practical Test Equipment describes the theory, the construction, and the operation of 7 instruments for beginners to make from readily obtainable components: Transistor Tester—Transistor checker—Square wave oscillator—AC Bridge—Signal injector and signal tracer combined in a Multi Checker—Dual range ohm meter, the final chapter deals with a range of test leads and give more detailed notes on signal injecting and signal tracing.  
Published price 75p our price 50p.

Practical Electronic Projects describes the construction and uses of 9 projects for beginners, all made from easily obtainable parts describes construction and operation of:—Windscreen wiper delay—Electronic Siren—Drum beat simulator—Lamp dimmer—Light/Dark operated switch—electronic bird, emotional state indicator—telephone amplifier—Solar powered radio.  
Published price 75p our price 50p.

Shortwave Receivers for Beginners after a few pages of general notes on wave bands, band spreading etc. the author gives constructional details of a one transistor radio then a two transistor and finally a multi stage receiver with band spreading and reaction.  
Published price 60p our price 45p.

FREE If you purchase the other two you get the shortwave one free.

## RADIO STETHOSCOPE


Easiest way to fault find, traces, signal from aerial to speaker, when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything. Kit comprises transistors and parts including probe tube and twin stetho-set. £3.95 VAT and postage inc.



Breakdown Parcel—four unused, made for computer units containing most useful components, and these components unlike those from most computer panels, have wire ends of usable length. The transistors for instance have leads over 1' long—the diodes have approx. 4' leads.

List of the major components is as follows:—17 assorted transistors—38 assorted diodes—60 assorted resistors and condensers—4 gold plated plugs in units which can serve as multipin plugs or as hook up boards for experimental or quickly changed circuits (note we can supply the socket boards which were made to receive these units). The price of this four units parcel is £1 including VAT and post (considerably less than value of the transistor or diodes alone) DON'T MISS THIS SPLENDID OFFER.

## MINI-MULTI TESTER

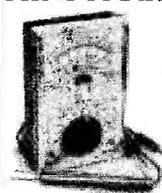

Amazing, deluxe pocket size precision moving coil instrument—jewelled bearings—1000 opv—mirrored scale.  
11 Instant ranges measure:—DC volts 10, 50, 250, 1000 AC volts 10, 50, 250, 1000 DC amps 0-1 mA and 0-100 mA Continuity and resistance 0-150K ohms.  
Complete with insulated probes, leads, battery, circuit diagram and instructions.

Unbelievable value only £3.50p + 50p post and insurance.

## FREE

Amps ranges kit enable you to read AC and DC current from 0-10 amps, directly on the 0-10 scale. It's free if you purchase quickly but if you already own a mini tester and would like one send £1.50p.

## MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost any one in easy-to-assemble modular form and complete with a pair of Plessey speakers this should sell at about £30—but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £14.00 including VAT and postage.



## SHORTWAVE CRYSTAL SET

Although this uses no battery it gives really amazing results. You will receive an amazing assortment of stations over the 19, 25, 29, 31 metre bands. Kit contains chassis front panel and all the parts £1.90—crystal earphone 55p including VAT and postage.



## MEASURING A.C. AMPS with POPULAR MULTI-TESTERS

This is not usually possible because a current transformer is required—We can now offer a kit of parts to make a suitable transformer which will enable you to measure A.C. amps directly on your Multi-tester two ranges would be available—usually 0-1 amp and 0-10 amps. This current transformer is quite easy to construct with our kit and we provide full instructions—price £2.55 post and V.A.T. paid.

## ROOM THERMOSTAT

Famous Satchwell, elegant design, intended for wall mounting. Will switch up to 20 amps at mains voltage, covers the range 0-30°C. Special snip this month £3.00, post and VAT paid.



## MAINS RELAYS



With triple 10 amp changeover contacts—operating coil wound for 230 volts AC, chassis mounting, one screw fixing, ex unused equipment 60p each, 10 for £5 post and VAT paid.

## LEARNERS PLEASE NOTE

P.W. associated publication "Everyday Electronics" is just starting a series called Teach in 78. This is a practical course with simple theory explained. We are offering a kit of parts for the practical side for £3 deposit and 5 monthly payments of £2 or £12 cash.

## CENTRAL HEATING HEARTS

Randal (illustrated) replacement in 3060 etc. £6.75.  
HORTSMAN £6.30.  
SMITHS Controller 10/100 complete in wall mounting case £7.50.



## THIS MONTH'S SNIP FLUORESCENT TUBE INVERTER



For camping—car repairing—emergency lighting from a 12v battery you can't beat fluorescent lighting, it will offer plenty of well distributed light and is economical. We offer Philips inverter for 12" 8 watt miniature tube for only £2.75 with tube and tube holders as well.

## TANGENTIAL HEATER UNIT



A most efficient and quiet running blower-heater by Solatron—same type as is fitted to many famous name heaters—Comprises mains induction motor—long turbo fan—split 2 kw heating element and thermostatic safety trip—simply connect to the mains for immediate heat—mount in a simple wooden or metal case or mount direct onto base of say kitchen unit—price £4.95 post £1.50 control switch to give 2kw, 1kw, cold blow or off available 60p extra.

3kW MODEL  
£5.95 +  
£1.50 p & p

## TERMS:

Cash with order—but orders under £6 must add 50p to offset packing etc.  
BULK ENQUIRIES INVITED. PHONE: 01-688 1833

**J. BULL (ELECTRICAL) LTD**  
(Dept. PW), 103 TAMWORTH RD.  
CROYDON CR9 1SG

## IT'S FREE

Our monthly Advance Advertising Bargains List gives details of bargains arriving or just arrived—often bargains which sell out before our advertisement can appear—it's an interesting list and it's free—just send S.A.E. Below are a few of the Bargains still available from previous issues.

20 Amp Car Starter/Charger kit still available £7.95p, post and VAT paid.

Solo Mastermind. Practical Wireless, October issue, describes this novel device which we think will be very popular now with the dark evenings, we can offer all the electronic components as follows:

Transistor type BCY 71—8 required	27p each
Transistor type BC 109—8 required	15p each
General purpose silicon diodes	10p each
2 Pole 6 way midget wafer switch—8 required	40p each
Push to make switch	25p each
Pack of 12 Resistors (note 2.2K are selected 5% type)	50p pack

1mA Panel meters, oblong, full vision, Japanese make—2 required £2.70p each

or Round ex equipment 1mA meters scaled 0-10 £2 each

Plain knobs—4 required 15p each

Pointer knob—4 required 15p each

EP3 Battery clip—1 required 25p each

1 Veroboard size  $3\frac{1}{2}'' \times 1\frac{1}{2}''$  25p each

Or all the above parts purchased as a parcel £13.50p with the Japanese meters £12.50p with round meters.

Humidity Stats. These are damp sensitive devices, in fact the metal frame which is the vital part expands with increasing dampness, breathing on it for instance will switch on a micro switch which can control a water spraying arrangement to increase humidity or a fan heater to lower the humidity. We have two models, the Ranco J11 which is a preset model, rated 3 amps 250v, has a screwdriver control for setting up, once set it cannot easily be tampered with. Overall size of this is  $3\frac{1}{2}''$  long and  $1''$  wide and  $1\frac{1}{2}''$  deep. Price of this is 65p + 5p. The other model is by Honeywell of America and is a little larger, overall size  $3\frac{1}{2}''$  long  $1''$  wide  $2''$  deep is adjustable by spindle which comes out of the front end and to which can be fitted a normal control knob. This operates 5 amps at 240v AC, price £1.00 + 8p.

Bridge Rectifiers suitable for instruments encapsulated and wire ended 100 volts 2 amp 50p + 4p.

Ditto suitable for power circuits, "battery charging" etc. 200v, 10 amp. Price £1.25p + 6p each.

Time and Set Switch, with the cost of heating going up and up it is not good economics to leave the heating on when there is no-one at home. On the other hand it is not nice to come home to a cold house so the time and set switch made by Smiths could be the answer. This is mains driven device which has contacts capable of switching 25 amps. Delay of up to 18 hours is possible with this. Glass fronted and with control knob this is a nice looking instrument, easy to mount in a box or on a panel, made by Smiths price £4.35p + 35p. Post 50p + 4p.

100w 8 ohm Speaker Units. Just right for the Disco made by Kelly Acoustical, we can thoroughly recommend these are £27.50p + £2.20p, carriage £3.00 + 24p. We feel certain that at this price these will be quickly snapped up so advise early action.

Water Pump ex Washing Machine. We believe that this comes from the Indesit Automatic Machine, these are really for callers as obviously you must have the right one. Price £7.00 + 56p.

12 Hour Switch On made by Crouzet, this device consists of 12 hour mains operated motor mounted on a chassis with two 5 amp trip switches. Through the front a chrome and red push switch which would protrude through the panel, in fact the main unit being held behind the panel with two screws depressing the switch, starts the motor and switches on controlled circuit and after 12 hours the motor will have rotated completely and will then switch off itself and the main circuit. There is obviously many uses for this device, one being to charge batteries for 12 hours or to switch on lighting or heating for 12 hours and no doubt many other uses will be found for it. £3.95p + 32p.

Bead Thermistor, glass encapsulated. This is a very sensitive device, you can see it decreases its resistance as you hold it in a warm hand. Resistance at 60°F is approx. 18k, at 100°F (approx. blood heat) it drops to 2k so you can see it is quite a sensitive device, ex unused G.P.O. equipment, price 50p + 4p.

Experimenters Resistor Assortment. Parcel comprising 500 1/2 and 1/4 watt carbon resistors 10 each of 50 different values covering 10 ohms to 20 megs. Supplied with a copy of the resistor colour code £4.00 + 50p.

Resistors in Bulk, we have over 2 million resistors covering values from 1 ohm to 50 meg ohms 1/4, 1/2, 1 and 2 watt types, price 75p per 100 for 1/4 and 1/2's, £2 per 100 for 1 watt, £4 per 100 for 2 watt. List your requirements and state if near value may be sent if any out of stock. V.A.T. is 12 1/2%.

Electrical Tape made by Scotch, this is polyester film, thermosetting pressure sensitive, yellow, 1 1/2" wide and is on a big reel 66m (70 yards approx.) Price 50p + 4p.

McMurdo Plugs & Sockets. Some additional types have arrived so we now have in stock 8 way plug and socket, price 40p + 4p per pair, 12 way 50p + 4 p per pair, 25 way 60p + 4p per pair.

Time Delay Module, mains working perspex type cover plugs into BTG base. Connect this through a mains relay and in 15 seconds approx the relay will close. If you want it to latch then use a relay with spare contacts to maintain the circuit to the coil. The delay as set is approx. 15 seconds, screwdriver control can alter this, still bigger alternatives to the 15 second time delay can be made by replacing the 1 pre set resistor with an external pot. The module contains a 4 amp 400v SCR, an FET transistor, all ancillary components also circuit is supplied. Priced at only £1.50p+12p. it is obviously quite a bargain.

# TRANSFORMERS

ALL EX-STOCK—SAME DAY DESPATCH. VAT 8%

## 12 AND 24 VOLT OR 12-0-12V PRIMARY 220-240 VOLTS

Ref	12V	24V	£	P & P
111	0-5	0-25	2-20	0-45
213	1-0	0-5	2-64	0-78
71	2	1	3-41	0-78
18	4	2	4-03	0-96
70	6	3	5-35	0-96
108	8	4	6-98	1-14
72	10	5	7-67	1-14
116	12	6	8-99	1-32
117	16	8	10-39	1-32
115	20	10	13-18	2-08
127	30	15	17-05	2-08
186	60	30	26-82	0-0A

## 30 VOLT RANGE

Ref	12V	24V	£	P & P
112	0-5	2-64	0-78	
79	1-0	3-57	0-96	
3	2-0	5-27	0-96	
20	3-0	6-20	1-14	
21	4-0	7-44	1-14	
51	5-0	8-37	1-32	
117	6-0	9-92	1-45	
88	8-0	11-73	1-64	
89	10-0	13-33	1-84	

## 60 VOLT RANGE

Ref	12V	24V	£	P & P
124	0-5	3-88	0-96	
126	1-0	5-88	0-96	
127	2-0	7-60	1-14	
125	3-0	10-54	1-32	
123	4-0	12-23	1-84	
40	5-0	13-85	1-64	
120	6-0	15-68	1-84	
121	8-0	19-05	2-08	
122	10-0	24-03	2-08	
189	12-0	27-13	2-08	

## AUTO TRANSFORMERS

Ref	VA (Watts)	Volts	£	P & P
113	20	0-115-210-240	2-48	0-71
64	75	0-115-210-240	3-95	0-96
4	150	0-115-200-220-240	5-35	0-96
66	300	0-115-200-220-240	7-75	1-14
67	500	0-115-200-220-240	10-99	1-64
84	1000	0-115-200-220-240	18-78	2-08
93	1500	0-115-200-220-240	23-36	2-08
95	2000	0-115-200-220-240	34-82	2-08
73	3000	0-115-200-220-240	48-00	2-08

## CASED AUTO TRANSFORMERS

VA	£	P & P	Ref
20	4-96	0-96	113W
150	8-48	1-14	4W
200	9-82	1-45	65W
250	10-49	1-45	69W
350	12-53	1-64	53W
500	15-73	1-64	67W
750	18-55	1-76	83W
1000	22-68	1-84	84W
1500	26-62	2-08	83W
2000	37-63	2-08	95W

## MAINS ISOLATING (SCREENED)

Ref	VA (Watts)	£	P & P
07	20	4-40	0-79
149	60	6-20	0-96
150	100	7-13	1-14
151	200	11-16	1-50
152	250	12-79	1-84
153	350	16-28	1-94
154	500	19-15	2-15
155	750	29-06	2-08
156	1000	37-20	2-08
157	1500	45-06	2-08
158	2000	54-88	2-08
159	3000	79-05	2-08

## HIGH VOLTAGE MAINS ISOLATING

Va	Ref	£	P & P
60	243	5-89	1-32
350	247	14-11	1-84
1000	250	35-65	2-08
2000	252	54-25	2-08

Our wide range of transformers are too numerous to list, please call (open 9am-5pm Mon-Fri) or send your requirements. Electrofil & semiconductor stockists. Panel, Multi Meters, Audio accessories, send 15p stamps for lists.

## SCREENED MINIATURES

Ref	mA	Volts	£	P&P
235	200	3-0-3	1-89	0-55
212	1A	0-6, 0-6	2-85	0-78
13	100	9-0-9	2-14	0-38
235	330, 330	0-9, 0-9	1-99	0-38
207	500, 500	0-8-9, 0-8-9	2-59	0-71
208	1A, 1A	0-8-9, 0-8-9	3-53	0-78
236	300, 300	0-15, 0-15	1-99	0-38
214	300, 300	0-20, 0-20	2-56	0-78
221	700 (DC)	20-12-0-12-20	3-41	0-78
206	1A, 1A	0-15-20-0-15-20	4-63	0-96
203	500, 500	0-15-27-0-15-27	3-99	0-96
204	1A, 1A	0-15-27-0-15-27	5-39	0-96
239	50	12-0-12	1-99	0-38
S112500		12-15-20-24-30	2-64	0-78

## PLUS

Item	Price
High Quality Modules	£3-66
25 Watts RMS Amplifier	£4-57
35 Watts RMS Amplifier	£6-95
125W RMS Amplifier	*£15-95
PRE-AMP for 25W	£13-88
POWER SUPPLIES 5-10W	£1-30
POWER SUPPLIES 25W	£3-75
TRANSFORMER 5-10W	£3-09
TRANSFORMER 25W	£4-79
P & P Modules 35p. Trans 96p.	VAT 12½% *VAT 8%

## MUSIC CENTRE KIT

FM Stereo Tuner + MW/LW, Output 2 x 8-5W rms.	£24-12 Inc.
-----------------------------------------------	-------------

## BLOB BOARD (Pack of 3)

2.5" x 5.1" .1" or 2.5" x 5.1" .15"	£0-75
3.75" x 5.1" .1" or 3.75" x 5.1" .15"	£1-14
10" x 6" .1" or 10" x 6" .15"	£3-78

## ELECTRONIC CONSTRUCTION KIT

10 projects (including electronic organ). No soldering needed £7-29. VAT 8% P & 70p

## COMPONENT PACKS

200 Mixed value resistors (count by weight)  
150 Mixed value capacitors (count by weight)  
30 Mixed value precision resistors ½W 2%  
15 Assorted pots  
10 Reed switches  
15 Wire wound resistors—mixed wattage  
1 Pack wire 50 metres assorted colours  
25 pre-sets assorted types and values  
Please state pack required. 60p per pack  
VAT 12½% P & P 40p

Prices correct 23-6-77. Please add VAT after P & P.

## BRIDGE RECTIFIERS

Ref	Volts	£	P&P
200V	2A	£0-45	0-29
400V	2A	£0-55	0-29
200V	4A	£0-65	0-29
400V	4A	£0-80	0-29
400V	6A	£1-05	0-29
500V	10A*	£2-35	0-29

## TEST METERS

Item	Price
AVO 8 MK5	£53-95
AVO 71	£23-00
AVO 73	£37-80
AVO MM5	£21-94
AVO TT169 in circuit	
Transistor Tester	£29-00
U4315 Inc. case	£14-95
VAT 8% P & P £1-15	
AVO cases and accessories	VAT 12½%

## AUDIO KIT 25W

2+25W Amplifiers  
1+ Pre-Amp  
1+ Power supply  
1+ Transformer  
1+ Front Panel  
1+ Kit of parts to include on-off switch, neon ind. Stereo head-phone socket. Plus instructions book £27-50  
Teak veneered cabinet aluminum chassis, heat sink and front panel brackets plus back panel and sockets etc. £3-29  
P & P £1-73 VAT 12½%

## RECORD DECK

BSR P123R Single Player with Cartridge £16-90 P&P £1-50 VAT 12½%

## TRANSFORMERS SPECIAL OFFER

BE1 Prim 0-120, 0-120V (120 or 240V) Sec 24V 10A £5-50 P & P £1-86  
BE2 Prim 0-90-110, 200-220-240V Sec 0-110V 0-20-24V 2-5A £2-25 P & P 95p VAT 8%  
BE3 100V line to 4.0 7/10V £2-65 P & P 66p  
BE4 Prim 120 or 240V 9-0-9 1A £1-88 P & P 0-38

## CARTRIDGES

AT55 £4-43  
SONOTONE £4-95  
BT4HC £2-63  
ACOS £2-18  
GP93-1 £2-40  
GP96-1 £2-40  
B.S.R. £2-25  
SX6M £2-92  
SC12M £2-92  
SHURE M75-6S £10-92  
M55E £12-42  
VAT 12½% P & P 25p

## POWER UNITS

Stabilised 3-6-7.5-9V/400mA multiplier outlet £5-95  
3300 fits into 13A socket 6-7.5-9V 300mA multiplier outlet £3-30  
RBE 3, 4-5, 6, 7-5, 9, 12V 500mA DC plus outlet £5-32  
VAT 12½% P & P 55p

## DECS SOLDERLESS BREAD-BOARDING

S Dec 70 contacts £1-90  
T Dec 208 contacts £3-65  
U Dec "A" for I.C.s etc £3-99  
V Dec "B" for I.C.s etc £6-89  
VAT 8% P & P 40p

## ANTEX SOLDERING IRONS

15W £3-75 18W £3-75  
25W £3-40 Stand £1-40  
VAT 8% P & P 43p

## TI MINI-MULTIMETER

DC-1000V AC-1000V DC-100mA Res-150KΩ 1000Q/V Bargain £5-38  
VAT 8% P & P 62p

## STEREO FM TUNER PHASE-LOCK LOOP

4 Pre-selected stations, Varicap tuning, switched AFC, LED Beacon.  
£20-45 VAT 12½% P&P 40p

## Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/7/8  
NEAREST TUBE STATIONS: ALDgate & LIVERPOOL ST

# You can work wonders with your free time.

There's immense satisfaction in making your own equipment. And you'll get excellent results with Heathkit.

Every kit is absolutely complete down to the last nut and bolt. The quality is the best. And each kit has an easy to follow instruction manual that explains exactly what to do at each step.


So you enjoy assembling your kit and you finish with first-class equipment every time.

That's why Heathkit are so successful. And that's why the range is the biggest in the world.

It's all in the new edition of the free Heathkit catalogue. Everything from the simplest to the most sophisticated. Alarms, digital clocks, testers, transceivers and lots more... even the tools are there!

See for yourself. Send the coupon now.

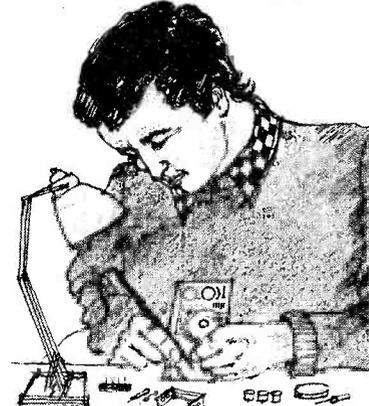- NEW CATALOGUE
- NEW TEST INSTRUMENTS
- NEW DIGITAL BATHROOM SCALES
- NEW AMATEUR RADIO EQUIPMENT
- NEW AUDIO SYSTEMS AND MANY OTHER NEW ITEMS



**The new Heathkit catalogue. Out now FREE.**

To: Heath (Gloucester) Ltd., Dept. PW-127, Gloucester, GL2 6EE. Please send me my Heathkit catalogue. I enclose an 11p stamp for postage.

Name \_\_\_\_\_


Address \_\_\_\_\_

Postcode \_\_\_\_\_

HEATH  
Schlumberger

ACCESS AND BARCLAYCARD WELCOMED

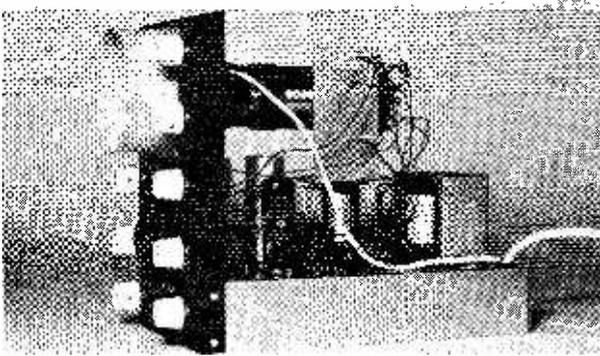
Showrooms at 233 Tottenham Court Road, London (Phone 01-636 7349) and Bristol Road, Gloucester (Phone Gloucester 29451).



**'There's only one way to master electronics... to see what is going on and learn by doing.'**

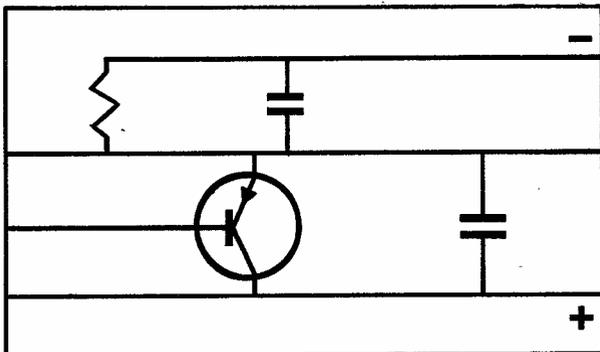
### 1 Build an oscilloscope.

As the first stage of your training, you actually build your own Cathode ray oscilloscope! This is no toy, but a test instrument that you will need not only for the course's practical experiments, but also later if you decide to develop your knowledge and enter the profession. It remains your property and represents a very large saving over buying a similar piece of essential equipment.


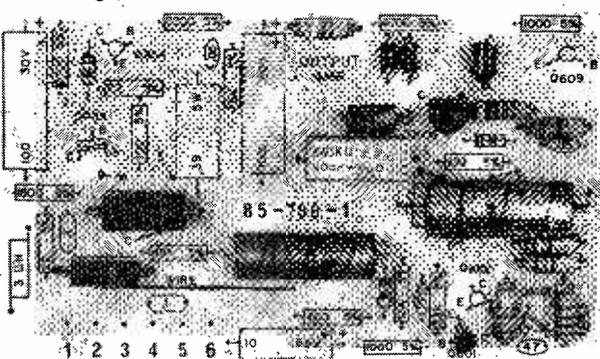
### 2 Read, draw and understand circuit diagrams.

In a short time you will be able to read and draw circuit diagrams, understand the very fundamentals of television, radio, computers and countless other electronic devices and their servicing procedures.



### 3 Carry out over 40 experiments on basic circuits.

We show you how to conduct experiments on a wide variety of different circuits and turn the information gained into a working knowledge of testing, servicing and maintaining all types of electronic equipment, radio, t.v. etc.

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to further your career in electronics or as a self-employed electronics engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write, at any time, for advice or help during your work. A Certificate is given at the end of every course.



All students enrolling in our courses receive a free circuit board originating from a computer and containing many different components that can be used in experiments and provide an excellent example of current electronic practice.

To find out more about how to learn electronics in a new, exciting and absorbing way, just clip the coupon for a free colour brochure and full details of enrolment.

Write to:- British National Radio & Electronic School  
P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

WB 127


# DeC-IT and BLOB-IT

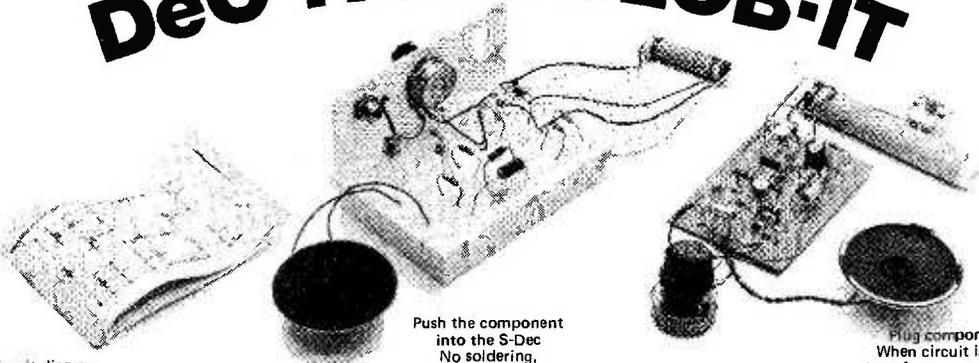

Each circuit diagram has the holes numbered into which the components are inserted.

Push the component into the S-Dec No soldering.

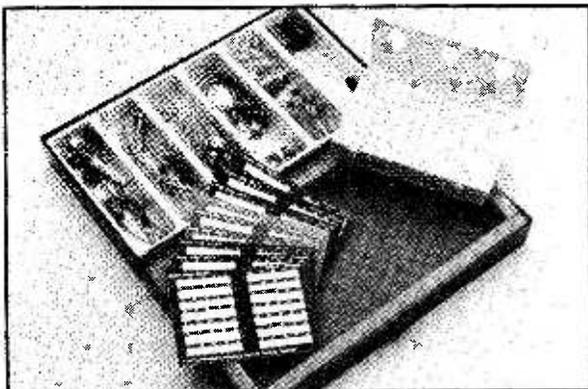Plug components in and out. When circuit is proved working, transfer component by component to exactly same numbered position in Blob-Board.



## S-De-K-IT

The perfect kit for beginners, students, professionals and all users of discrete components. This S-De-K-IT contains 1 S-Dec + control panel, 9 Blob-Boards, 20 double ended Leads + Instruction book to build (no components) Electronic Flasher + Binary Counter + LC Oscillator + 3 Stage Amplifier, Morse Practice Oscillator, Radio Receiver, Radio-Microphone, Light Operated Switch, CR Oscillator, Wien Network Oscillator, S-De-K-IT complete in ABS box, with component tray.

Normally £6.38 only £4.95 + £1.00 Post and VAT

NB The discrete components to build the above S-De-K-IT are listed but not supplied. This is because using discrete or surplus components you can buy all the components very cheaply from your local component supplier.

P.B. Electronics (Scotland) Ltd.  
57 High Street, Saffron Walden, Essex. CB10 1AA England.  
Telephone: Saffron Walden (0799) 22876 Telex: 817185.

## Dawes Electronic

121 Dawes Road, London SW6

Tel 01 831 3975

Memories CPU's, Clocks, etc.		TTL 7400 SERIES		Linears (H, TOS, A-B, 14-16 dii, V, 8 dii T, TO220, K, TO3)	
1101 256 RAM	125p	00	12p 92	39p	
1103 1K RAM	160p	01	13p 93	39p	
1702 2K Eprom	£3.95	02	14p 94	60p	300H 99p
2102 1K Static	169p	03	15p 95	49p	301V 37p
2107B4 4K Dyn	£3.98	04	16p 96	59p	302H 59p
2513 64 x 8 x 5	£4.70	05	16p 100	96p	304H 59p
2518 Hex 32 & 40	£3.20	06	25p 107	26p	305H 75p
2708 8K Eprom	£2.00	07	17p 109	49p	307V 56p
5013 1K Shift	£2.68	08	17p 121	27p	308V 75p
5203 2K Eprom	£8.00	09	17p 122	43p	309K 130p
5280 1k Dyn RAM	125p	10	14p 123	55p	310H 75p
5282 2K Dyn RAM	125p	11	18p 125	62p	311V 120p
5311 Clock	£2.99	12	27p 132	85p	312H 225p
5314 Clock	£2.95	13	27p 132	85p	318V 175p
5316 Clock	£2.95	14	112p 141	85p	319A 80p
7001 Clock	£3.85	15	30p 145	85p	320K-5, 12
7488/82523 Prom	189p	16	29p 150	82p	15, 24V 125p
8080A CPU 8 Bit	£19.90	17	26p 151	65p	324A 134p
8216 Bus Driv	£3.50	18	14p 153	76p	339A 180p
8224 C1 Gen	£7.00	19	27p 160	65p	340T-5, 12
8228 Sys Con	£8.25	20	14p 153	76p	15, 24V 125p
8255 Per Intfice.	£12.90	21	27p 164	114p	370A 57p
		22	27p 155	86p	380AV 100p
		23	27p 154	114p	381A 150p
		24	27p 155	86p	546V 90p
		25	27p 157	75p	550A 68p
		26	27p 158	66p	555V 30p
		27	27p 160	67p	556A 99p
		28	12p 161	106p	560B 318p
		29	63p 162	97p	565A 179p
		30	52p 163	97p	566V 175p
		31	52p 164	114p	567V 175p
		32	69p 165	165p	709A 30p
		33	75p 166	115p	710A 32p
		34	87p 170	179p	711A 37p
		35	75p 173	119p	
		36	65p 174	108p	
		37	50p 131	175p	
		38	45p 132	182p	
		39	35p 133	162p	
		40	27p 134	177p	
		41	14p 180	87p	
		42	14p 181	312p	
		43	26p 182	85p	
		44	25p 190	162p	
		45	27p 191	162p	
		46	27p 192	162p	
		47	35p 193	162p	
		48	28p 194	93p	
		49	95p 195	93p	
		50	27p 197	100p	
		51	230p 198	150p	
		52	189p 199	230p	
		53	30p 200	430p	
		54	89p 270	85p	
		55	91		

(All prices include V.A.T. Min. order £3.00 + 20p p. & p.)

Mixed Nuts and Bolts, screws, eyelets, Grommets\*, etc. @ 50p per lb + Postage and Packing @ 50p.

Mixed Resistors, mainly Erie make, mixed value, 500 @ £1, 250 @ 60p, 100 @ 30p.

Mixed Capacitors. 500 @ £1.25, 250 @ 70p, 100 @ 40p.

IS Coils AM & FM OSC. Disc made by Toko, Mixed 25 @ 50p or 3p each

Mixed Potentiometers 10 @ 75p

Knobs @ 2p each

Aerial Coils, MW & LW @ 3p each

With Ferrite Rod @ 12p each

Car Radio, Push Button Switches @ 25p each

Push Button Switches: Single @ 3p each

Triples @ 8p each: Fours @ 12p each

Sixes @ 18p each

RF & HT Choke @ 2p each

Car Radio Transformers @ 10p each

VHF Diode Tuner @ £1 each

Gang Condensers @ 25p each

Transistors—AC 127 6p each

Electrolytic Capacitors: 400 uf 16v, 125 uf 16v, 400 uf 10v, 10 uf 16v

All at 3p each

Polystyrene Caps. 10 - 68 - 100 - 130 - 1000 all 5% Tol 30 VDC Working, 100 - 200 - 320 - 390 - 1200 - 1300 - 1800 all 2 1/2% Tol 30 VDC Working 200 - 300, both 10% Tol 30 VDC Working, 1300 2 1/2% Tol 125 VDC Working, all @ 1p each.

Potentiometers. Slide 100K Log Dual, 1MΩ Lin Single and Dual @ 5p each

Rotary Single, 100K Lin @ 10p each

Rotary Doubles, 100K Lin, 100K Log, 470K Log, 20K Lin, 1MΩ Log 20K + 80K @ 10p each

Card Wheel 1 1/2" Dia. All @ 2p each\*

Transistor-Diode metal mounting clip or Cooling Clip @ 1p each

5 pin Dia Socket @ 4p each

2 pin Aerial Socket @ 4p each

Plastic/wire indicator bar\* @ 1p each

FM Oscillator Coil—RF Coil\* @ 2p each

Black Plastic Cable Clips\* Large 5 @ 1p

Various Size Tag boards\* 5 @ 5p

Black Plastic Feet\* 6 @ 2p

Very Limited First Come First Served

Speaker Sockets 2 Pin @ 3p each

Change Plugs @ 2p each

Terminal Pins—Electronic 100 @ 10p

Support Clips\* @ 1p each

Slide Switch, Skeleton Type @ 5p each

Limited No. only @ 3p each

Sockets @ 3p each


PLEASE NOTE THAT ALL ITEMS ARE SUBJECT TO V.A.T. All items marked with star @ 8%, all others 12 1/2%. PLUS POSTAGE and PACKING @ 35p per £1 order. EXCEPT NUTS and BOLTS @ 50p. Minimum Order £1. TERMS: CASH WITH ORDER REGRET MAIL ORDER ONLY.

## KKS TRADING COMPANY

DEPT R.C.

38 OAKDENE

CHESHUNT, HERTS EN8 9JA

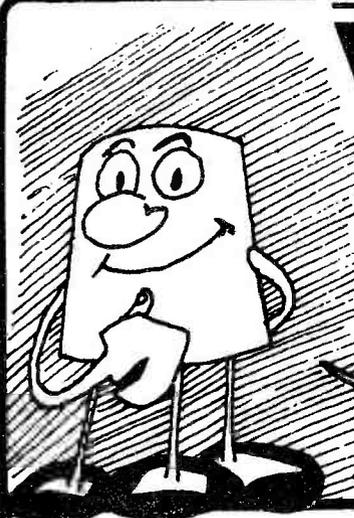

# WHAT'S NEW?

ME, IK2

does electronics interest you? discover, learn, perfect, and..enjoy yourself

Teaching Kits represent, without a doubt, the most economical and most absorbing method of understanding Electronics perfectly, even starting at zero, without effort, while practising your favorite pastime. Each kit allows you to make more than 100 experiments, which will lead you to master the theory and practise of circuits. Only the quantity, supply, and direct sale allow us to maintain these prices, so don't wait, we will be obliged to raise the price.

**a economic and passionate method, from introduction to new job opportunities!**

The manuals teach you the techniques of the kit clearly and in detail, at its most recent level, starting from zero, and guide you in making an infinite number of experiments, assemblies, apparati, enjoyable, often useful, always instructive, and absorbing.

A laboratory in your home : mini, to be sure, but serious and technically important : Electronic voltmeter, logic indicators. On epoxy resin board, you wire the assemblies using the numerous parts furnished. You are sure to understand everything and succeed, and if any point remains unclear, our engineers will reply to all your questions, send only a envelope with your name and adress for an answer.

### ik2 semiconductors:

Including the most advanced techniques.  
The kit also constitutes an excellent base, even for preparation for official exams. And everything one needs to know to approach specialization in the best conditions.  
Everything one needs to know -in theory as well as practise- (an infinite number of experiments) about : diodes, transistors zener, phototransistor, FET, MOS, thyristors, triacs, diacs, etc. to use them rationally, to conceive assemblies, and master the theory of semiconductors needed in the repair of any apparatus.

### the material:

1 EPOXY RESIN experiment board, large size. All componants needed to make your own : -A electronic voltmeter, -A LF Measures Amplifier, - 4 logic indicators.  
And also numerous componants needed to make assemblies and experiments: diodes, transistors, (small signal and power), diac, zener, triac, LEDs, phototransistor, MOS, Integrated circuit, Resistors, capacitors, loud speaker, VC, Coil former, potentiometers, ammeter, operational amplifier, etc..


### the manual:

Large size, abundantly illustrated, particullary wel detailed.  
CERTAIN TITLES ONLY : -Introduction, laboratory, electricity, resistors capacitors, alternating phenomena, diodes, transistors, amplifier, MOS and CMOS technology, filters, oscillators, applications, transistors changing state, thyristors, triac, AM broadcasting, AM Receivers, radio control, troubleshooting, etc.. More than A HUNDRED experiments explained.

### possibilities:

SOME EXAMPLES : beyond the lab : amplifier-oscillator- games, caterpillar effect, light modulator, broadcasting, radio Receiver, measuring instruments, radio control, gadgets, etc...

more than 100 experiments

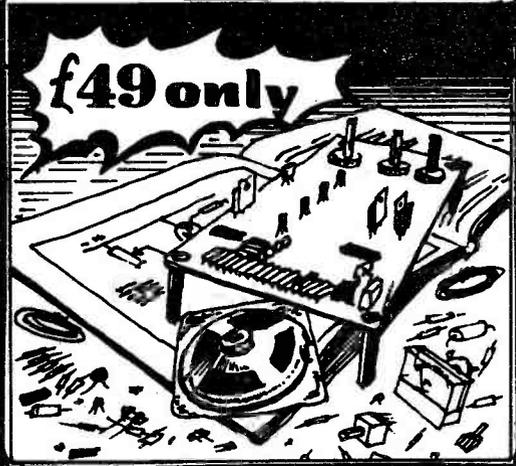

**DON'T WAIT!**


**SAGA ENGLAND**  
p.o. box: 401  
KING'S LANGLEY, HERTS  
WD4 9PB  
SAGA FRANCE : 1 RUE PROSPER DELFAU  
30160 BESSEGES FRANCE.

complete and mail coupon today (Block letters)

Please send me \_\_\_ (QTY) IK2 teaching Kit(s)  
I enclose Cheque/Postal order for \_\_\_ £  
NAME \_\_\_\_\_  
ADRESS \_\_\_\_\_  
POST CODE \_\_\_\_\_

# BI-PAK

High quality audio

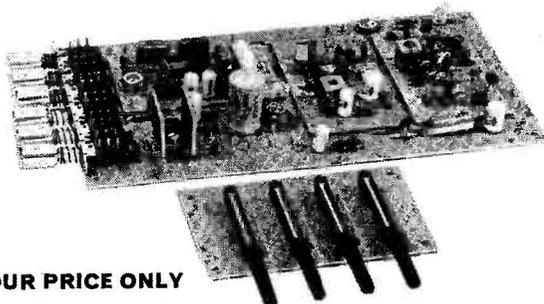

OUR PRICE ONLY

**£20.45**

The 450 Tuner provides instant programme selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls.

Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T461.

The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

## STEREO FM TUNER

Fitted with Phase Lock-loop

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

**Typical Specification:**  
Sensitivity  $3\mu$  volts  
Stereo separation 30db  
Supply required 20-30v  
at 90 Ma max.

## STEREO PRE-AMPLIFIER PA 100



A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

Frequency Response + 1dB  
20Hz-20KHz.  
Sensitivity of inputs:  
1. Tape Input 100mV into 100K ohms  
2. Radio Tuner 100mV into 100K ohms  
3. Magnetic P.U. 3mV into 50K ohms  
P.U. Input equalises to R1AA curve within 1dB from 20Hz to 20KHz. Supply 20-35V at 20mA. Dimensions—289mm x 89mm x 35mm.

**£13.75** p & p 45p


### MK60 AUDIO KIT:

Comprising: 2 x AL60's 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs. 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £35.00 plus 62p postage.**

### TEAK 60 AUDIO KIT:

Comprising: Teak veneered cabinet size 162" x 11 1/2" x 32", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets, etc. **KIT PRICE £13.25 plus 62p postage.**

**VAT ADD 12 1/2%**

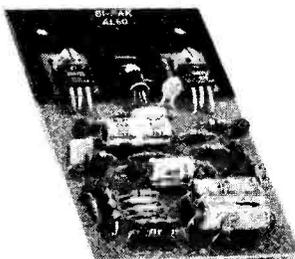

**AL 60**

25 Watts (RMS)

- Max Heat Sink temp. 90C.
- Frequency response 20Hz.
- Distortion better than 0.1 at 1kHz.
- Supply voltage 15-50v.
- Thermal Feedback.
- Latest Design Improvements.
- Load—3, 4, 5, or 16ohms.
- Signal to noise ratio 80db.
- Overall size 83mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.


ONLY **£4.35**

## Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (r.m.s.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm, 105mm, 30mm. Incorporating short circuit protection.

**INPUT VOLTAGE** 33-40V. A.C.  
**OUTPUT VOLTAGE** 33V. D.C. Nominal  
**OUTPUT CURRENT** 10mA-1.5 amps **£3.75**  
**OVERLEAD CURRENT** 1.7 amps approx.  
**DIMENSIONS** 105mm x 63mm x 30mm  
**TRANSFORMER BMT80** £5.40 + 86p postage

## STEREO 30 COMPLETE AUDIO CHASSIS

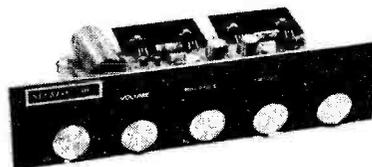

7 + 7 WATTS R.M.S.

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel, knobs, mains switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins.).

**TRANSFORMER £3.25** plus 50p p & p.

**TEAK CASE £5.45** plus 70p p & p.

**£16.25** P & P 45p.

# equipment mono and other modules for Stereo

**THE MEDIUM POWERED AL 80**  
**35<sup>RMS</sup> W power Amp!**

ONLY

**£6.95**  
 +8% VAT



**A High Fidelity Power Amplifier with a maximum Power Output of 35 watt R.M.S., which has a maximum operating voltage of 60v. A MUST for all Hi-Fi users.**

Maximum supply voltage	15-60v
Power output for 2% THD	35 watts R.M.S.
Harmonic distortion	0.1%
Load impedance	368e16 ohm
Input impedance	50K ohm
Frequency response +3dB	20Hz-40KHz
Sensitivity for 25 watts O/P	280mV R.M.S.
Max. Heat sink temperature	90°C
Dimensions	102mm x 64mm x 15mm
Mounting	2, 4BA fixing holes in heat sink
Fuse requirements	1.5A

**MPA 30**



Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new Bi-Pak M.P.A. 30 which is a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. Used in conjunction are 4 low noise high gain silicon transistors. It is provided with a standard DIN input socket for ease of connection. Supplied with full, easy-to-follow instructions.

**£2.85**

**VAT ADD 12<sup>1</sup>/<sub>2</sub>%**

**POSTAGE & PACKING**

Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

**NEW AL30A**

## 10w R.M.S. AUDIO AMPLIFIER MODULE

The AL30A is a high quality audio amplifier module replacing our AL20 & 30. The versatility of its design makes it ideal for use in record players, tape recorders, stereo amps, cassette & cartridge players. A power supply is available comprising of PS12 together with a transformer T538, also for stereo, the pre amp PA12.

### SPECIFICATION:

- Output Power 10w R.M.S.
- Load Impedance 8 to 16 ohms
- Sensitivity 90mV for full output
- Frequency Response 60Hz to 25KHz - 20db
- Supply 22 to 32 volts
- Input Impedance 50K
- Total Harmonic Distortion less than .5% (Typical; .3%)
- Max Heat Sink Temp 80°C
- Dimensions 90 x 64 x 27mm




**ONLY £3.65**

## AND for those who need more P-O-W-E-R

**AL250**

**125<sup>RMS</sup> W**

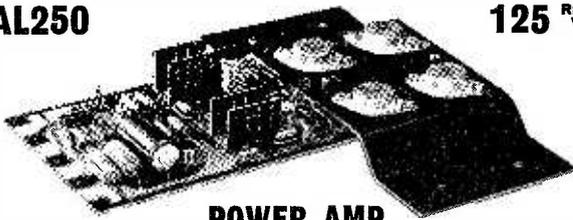

**POWER AMP**

**Specially designed for use in— Disco Units, P.A. Systems, high power Hi-Fi, Sound reinforcement systems**

### SPECIFICATION:

Output Power: 125 watt RMS Continuous	Total harmonic distortion
Operating voltage: 50-80	50 watts into 4 ohms: 0.1%
Loads: 4-16 ohms	50 watts into 8 ohms: 0.06%
Frequency response: 25Hz-20kHz Measured at 100 watts	S/N ratio: better than 80dBs
Sensitivity for 100 watts output at 1kHz: 450mV	Damping factor, 8 ohms: 65
Input impedance: 33K ohms	Semiconductor complement: 13 transistors 5 diodes
	Overall size: Heatsink width 190mm, length 205mm, height 40mm

**ONLY £15.95 + 8% VAT**

**PS12**

**£6.70**

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL-30A Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.  
**Frequency Response 20Hz-20KHz (-3dB)**  
 Bass and Treble range ± 12dB  
 Input Impedance 1 meg ohm  
 Input Sensitivity 300mV  
 Supply requirements 24V. 5mA  
 Size 152mm x 33mm

**PA12**

Power supply for AL-30A, PA12, S450 etc. Input voltage 15-20v A.C. Output voltage 22-30v D.C. Output Current 800 mA Max. Size 60mmx 43mmx26mm.

Transformer T538 £3.20

**£1.30**

**BI-PAK**

**DEPT. P.W.12 P.O. BOX 6 WARE HERTS**  
 COMPONENT SHOP: 18 BALDOCK STREET WARE.

**EDITOR**

Geoffrey Arnold

**ASSISTANT EDITOR**

Eric Dowdeswell G4AR

**ART EDITOR**

Peter Metall

**TECHNICAL EDITOR**

Ted Parratt, BA

**NEWS & PRODUCTION EDITOR**

Bill Tull

**TECHNICAL ARTIST**

Alan Martin

**TECHNICAL SUB-EDITOR**

Frank Ogden

**SECRETARIAL**Linda Walji  
Belinda Mould**EDITORIAL OFFICES**Westover House, West Quay Road,  
POOLE, Dorset BH15 1JG**ADVERTISING MANAGER**

01-261 5000 Roy Smith

**CLASSIFIED ADVERTISING**

01-261 5762 Colin R. Brown

**ADVERTISING OFFICES**King's Reach Tower, Stamford Street,  
London SE1 9LS**BINDERS**

Binders, for either the old or the new format, are £2.85 and Indexes are 45p (Inc VAT) and can be obtained from the Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF. Remittances with overseas orders for binders should include 60p to cover despatch and postage.

**BACK NUMBERS**

We are very glad to announce the re-establishment of a PW Back Numbers Service for our readers. In future back numbers dated from June 1977 only will be available from our Post Sales Department for 65p, which includes postage and packing. Cheques and Postal Orders should be made payable to IPC Magazines Ltd.

Send your orders to:- Post Sales Department, IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

# Calling all Constructors

IF YOU'RE an electronics enthusiast, then whether you are lucky enough to have a room set aside for your hobby, or you just commandeer the kitchen table from time to time, you will need some sort of tool kit and at least one or two bits of test gear.

In this issue we have two items of particular interest, the first being a special offer of a soldering iron kit at some twenty per cent below the normal retail price. With four different-sized bits, this iron should be able to cope with all your PCB joints and plenty more besides. This offer is exclusive to *PW* readers.

Our cover subject this month is one of those pieces of equipment that, once you've got it, you wonder how you ever managed without. When working on experimental circuits, or just doing some servicing, a good stabilised power supply unit is so much easier to use than a lash-up of batteries and potential dividers. This particular design offers two independent outputs, one for driving TTL and the other for CMOS, operational amplifiers or discretes.

As many of you will know, almost all the constructional projects published in *PW* are written by outside contributors, and we are always on the look-out for interesting articles from our readers. Don't be put off by the fact that a few authors' names seem to crop up fairly regularly—it's an open stage. The only qualifications are that your project is likely to be of interest to a reasonable number of other readers, and that the components required must be currently available through retail sources. Articles should preferably be typewritten, double-spaced on one side of the paper only, with all drawings on separate sheets. Try to follow as far as possible the style used in the magazine. Next month, we hope to publish a more comprehensive guide for budding authors.

If you're not sure whether it's worth going to the extent of writing a complete article about your project, just drop us a line giving the basic details of what it does and how it does it. We'll tell you if it looks promising. Remember, you don't have to be an accomplished technical author. If your idea is worth publishing, *PW* staff can do whatever is required to put it into shape. We look forward to hearing from you!

Geoffrey Arnold.


## PLEASE NOTE

We do not operate a Technical Query Service except on matters concerning constructional articles published in *PW*. We do not supply service sheets or information on commercial radios, TV's or electronic equipment.

All queries must be accompanied by a stamped self-addressed envelope otherwise a reply cannot be guaranteed.
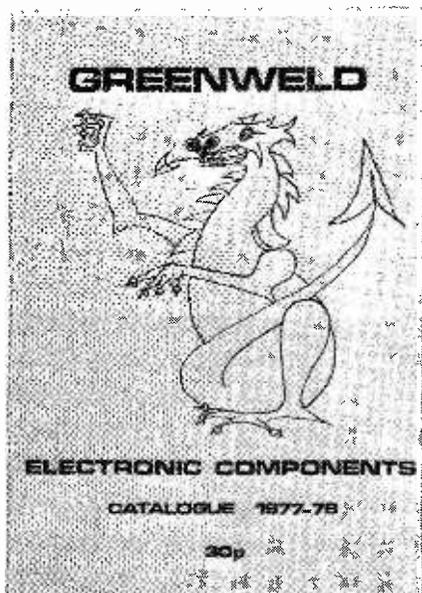
## Component catalogue

In these penny-pinching days the electronic enthusiast needs every help if he is to continue building projects and eat as well! Sifting through *PW* will usually account for most of your much needed components but they're so spread out that postage robs you of any financial advantage you may have gained. The answer is to purchase most, if not all from a single supplier—and to do it from a comprehensive catalogue. Greenweld who regularly advertise in *PW* have just



launched their latest catalogue which contains over 4000 items, hundreds of which are illustrated, and range from multimeters to IC's to semiconductors and switches.

Included in the catalogue are five 10p vouchers which can be used against any component purchased. The price for the catalogue is 30p plus 15p postage and can be obtained from Greenweld, 443 Millbrook Road, Southampton. Tel: 0703 772501.

## All change

Readers who were unfortunate enough to have had to take their Philips or Pye radio in for servicing will no doubt be familiar with the initials CES—for the

uninitiated (Combined Electronic Services). Well now that you are all familiar with this name you can now forget it, because as from September 1st, Philips have been running these service departments up and down the country under the new name "Philips Service".

Philips Service will comprise 25 Service Centres for spares and repairs with the main centre still sited at Woddon, Croydon. In fact, Philips claim that this new system will enable them to introduce a new pricing policy, which could lead to price reductions on certain spare parts. For those customers unable to get to one of the Centres, the now all-too-familiar computer situated at Woddon should speed up and give a better service to those orders sent by post.

*Philips Electrical, Century House, Shaftesbury Ave., London. Tel: 01-437 7777.*

## Exit the inch

Like it or not the days of Imperial measure are numbered (no pun intended) and that total metrication is creeping ever closer and closer with the almost inevitable conclusion that accompanied decimalisation of our money—someone somewhere will make a pretty 'fast buck'.

The reason that metrication has fuelled the inflation fires can almost be put down to one thing, and that is ignorance. If a manufacturer 'rounds' his product up to the nearest whole penny or to the nearest kilo, and in the latter case charges more than he should for the extra weight, the public should make it known to the authorities, and refuse to buy the commodity. But how can honest 'Joe Soap' do this if he doesn't know what a kilo is, what 500ml means, and how-on-earth, can he ask for a shirt with a size 39 collar?!

The people who teach the public, such as school teachers and examiners, and for people in trade, industry, publishing, journalism and printing the Metrication Board has produced a style guide for teaching and using SI Units. The Booklet, titled 'How To Write Metric' is roughly divided into two sections—'The Teaching of SI Usage' and 'Rules and Guidelines'. The guide ends with a wide selection of SI Units and symbols, derived

units, prefixes, base units and supplementary units. Priced at 50p each or £20 for 50 copies they can be obtained from HMSO 49 High Holborn, London WC1V 6HB. The reference number is ISBN 0 11 700867 2.

## RAE examples

A couple of months ago we published a list of Colleges who are running the Radio Amateurs Examination Course. A useful addition to any course is a book containing past question and answers, properly set out, with diagrams in a form that the examiners like to see. The RSGB now publishes a book titled 'Radio Amateurs Examination Questions and Answers', which has been compiled with the assistance of the City and Guilds of London Institute.

The book is arranged in the same format as the UK examination, with chapter titles as follows: Licensing conditions, Transmitter interference, Elementary electricity and magnetism, Elementary alternating current theory, Thermionic valves and semiconductors, Radio receivers, Low power transmitters, Propagation, Aerials, and Measurement.

Containing 118 pages and costing £1.70, copies can be obtained from RSGB, 35 Doughty Street, London, WC1. Tel: 01-37 8688.

## BSI to the rescue?

You remember that little story we published some months ago on this page, about the new International 16A plug that was being considered by the UK?—Well, they have considered it, that is the British Electrotechnical Committee have, and they've approved it. We must add though that this approval is for the first draft only, and does not commit this country to accept any further proposals or to final adoption of the system.

If The British Standards Institute were to publish a document on this system they would require that all socket-outlets should have shutters, and would require a minimum recess depth of 9mm in order to provide assurance that live parts cannot be touched. Also the Institute would require socket-outlets and adaptors to be fused. As yet, these features are not included in the IEC draft.

# PORTABLE P.A. AMPLIFIER

S.H.DAVIES



A small amplifier which will operate from a 12V Battery is often useful. This particular example was intended for loud-hailing from a small motor boat, so the amplifier was designed with mobile PA applications, in mind. The prototype was used to drive an ordinary boxed speaker, but a small horn type would be far more suitable, and less bulky. Another likely application is for audio systems for cars and boats, fed by a cassette player and tuner or small radio. With alterations to the preamplifier circuitry, many variations on the basic circuit given are possible. Only two active devices are used—a quad operational amplifier and an IC power amplifier. This will drive any speaker from 4 ohms upwards, and has an output power of 2.5W into 4 ohms. To increase the amplifier's versatility a music input and comprehensive tone controls are included. The music input accepts signals from any cassette recorder or tuner having an output of 50mV or more.

## Preamplifier

The circuit of the preamplifier is shown in Fig. 1. It uses the quad Norton amplifier which is an unconventional operational amplifier in that it amplifies the difference between two currents rather than two voltages.

The IC will work using any voltage between 4V and 18V. However a stable supply is needed, so the Zener stabilised circuit of Fig. 2 is used to give a stable 10V. The small capacitor C13 across the electrolytic is essential to decouple the supply at high frequencies in order to prevent instability.

## Microphone Mixer Stages

The microphone preamplifier (IC1a) is designed for a low-impedance microphone, and therefore has to give a considerable amount of voltage gain. With VR1 at maximum, the gain is about 115. The gain is reduced by decreasing VR1, increasing the amount of negative feedback. C2 prevents changes in VR1 from affecting the biasing of the amplifier by blocking d.c. The input circuitry is a little more complex than appears necessary. To obtain a 600 ohm input impedance, it would be usual to make R2 600Ω and omit R1. However to avoid loss of bass, C1 would then need to be about 250μF, which is bulky. Use of a higher value than this for R2 reduces C2 to a sensible size. The input impedance is then reduced to about 600 ohms by R1 (for use with a 2k microphone omit R1).

The music preamplifier (IC1b) is very similar in operation to the microphone stage. However to obtain a high input impedance R6 must be large, unless more complex circuitry is used. This restricts the stage gain to one-third, but this is offset by the small amount of gain in the mixer stage, giving an overall sensitivity of about 50mV music for full output.

## Tone Control Circuit

This is the standard Baxandall circuit, and has unity gain. The amplifier is biased by R15 and R16. The non-inverting input is grounded, effectively disconnecting the current mirror. The voltage at the inverting input is a fairly constant 0.5V whatever the input current, and use is made of this to set the output voltage to the correct value. The quiescent voltage

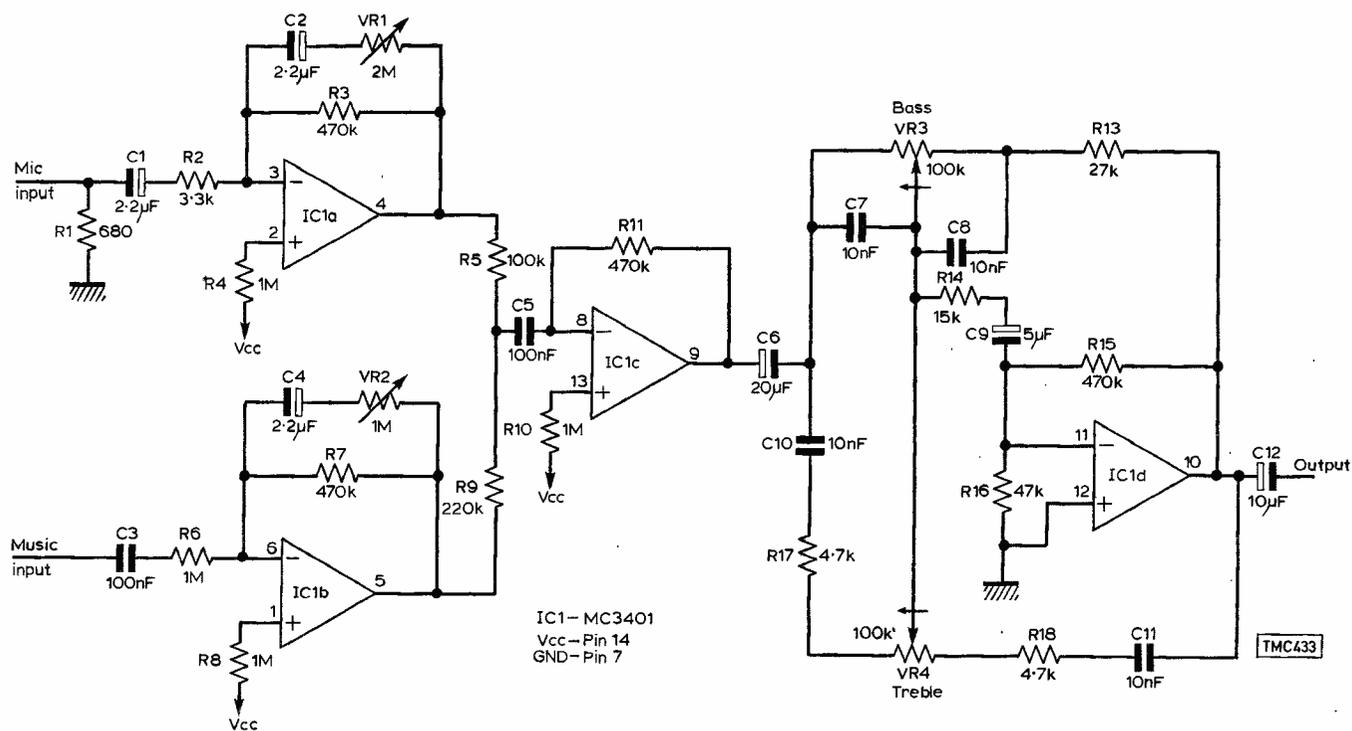


Fig. 1: The main (quad Norton) preamplifier circuit diagram.

Note: R12 (27kΩ) has by an oversight been omitted. The junction of C6 and C7 should be broken, and R12 interposed.

at the output will be that which gives 0.5V at the inverting input—about 5V here.

The other amplifiers are biased by the more usual method. A 1MΩ resistor from the supply rail (R4, R8, R10) to the non-inverting input gives about 10μA through the current mirror. This is balanced by an equal current through a 470k resistor connected between the inverting input and output, setting the quiescent output voltage to half supply voltage—5V here. It is worth remembering that in the first case the output voltage is a fixed multiple of the voltage at the inverting input terminal, and therefore is substantially independent of the supply voltage. In the second case, however, the output voltage is a fixed fraction of the supply voltage. Thus the second method of biasing should be used where large variations in supply voltage are envisaged, to give the maximum possible undistorted output voltage swing.

## ★ components

### Resistors

R1	680Ω
R2	3.3kΩ
R3	470kΩ
R4	1MΩ
R5	100kΩ
R6	1MΩ
R7	470kΩ
R8	1MΩ
R9	220kΩ
R10	1MΩ
R11	470kΩ
R12	27kΩ
R13	27kΩ
R14	15kΩ
R15	470kΩ
R16	47kΩ
R17	4.7kΩ
R18	4.7kΩ
R19	100Ω
R20	2.7Ω (see text)

### Capacitors

C1	2.2μF	15V
C2	2.2μF	15V
C3	100nF	
C4	2.2μF	15V
C5	100nF	
C6	20μF	15V
C7	10nF	
C8	10nF	
C9	5μF	15V
C10	10nF	
C11	10nF	
C12	10μF	15V
C13	220nF	
C14	100μF	15V
C15	10μF	15V
C16	10μF	15V
C17	20μF	15V
C18	100μF	15V
C19	100μF	15V
C20	100nF	(see text)

VR1 2MΩ log  
 VR2 1MΩ log  
 VR3 100kΩ 1in. preset  
 VR4 100kΩ 1in. preset

### Semiconductors

IC1 MC3401; IC2 LM380; D1 1N4001; ZD1 10V, 400mW Zener

### Miscellaneous

S1 SPST Toggle; FS1 1A Fuse; Case 203mm × 95mm × 50mm; Veroboard (2 pieces); Line Fuseholder; 4 Knobs; 2 Jack Sockets; DIN Speaker socket; 14-pin IC Socket; 2 large crocodile clips; Power supply cable; Loudspeaker 4-15Ω.

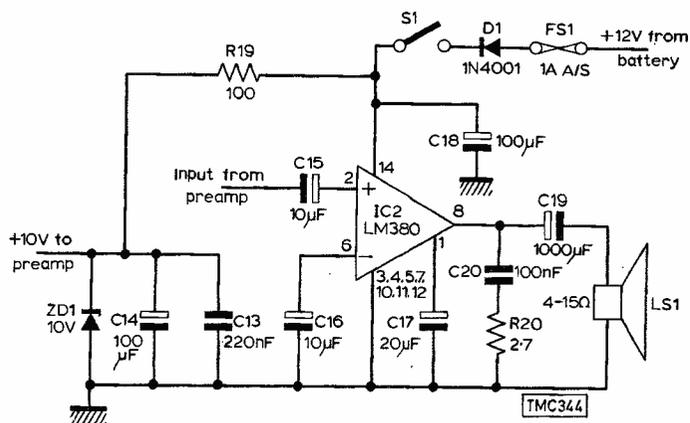


Fig. 2: Zener-stabilised supply and power amplifier circuitry. C19 is 100MFD and not 1000MFD as shown.

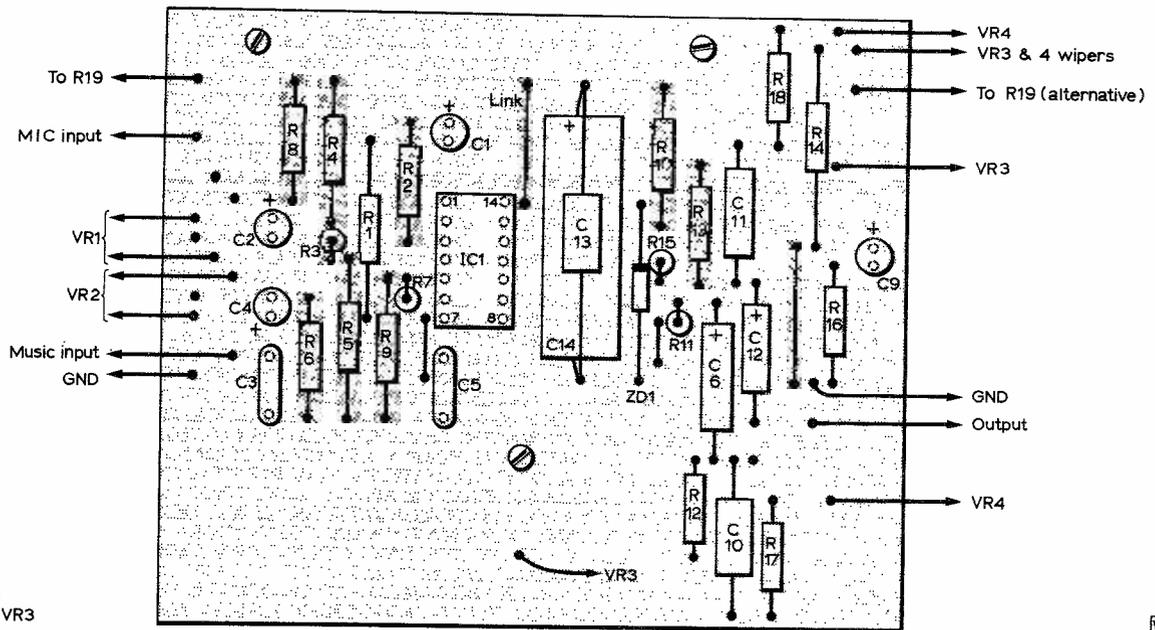


Fig. 5 (below):—a general view of the inside of the unit.

Fig. 3: Pre-amplifier board, with component layout.

### Power Amplifier

The circuit is shown in Fig. 2, and uses an LM380 amplifier. Briefly, it is an audio amplifier with its gain internally fixed at 50, giving a sensitivity of about 50mV for full output. It will drive a 4 ohm load with a supply of up to 14V, producing an output of 2.5W.

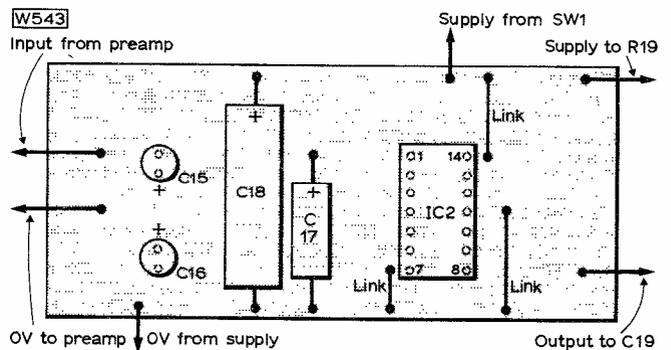


Fig. 4: The wiring of the output stage board.


### Construction

The power and pre-amplifiers are built on separate pieces of 0.1 matrix Veroboard. Layouts for these are given in Figs. 3 and 4. The completed unit may be housed in a proprietary aluminium box, with a slightly sloping front. The internal layout can be seen from Fig. 5, and is not critical. An IC socket is recommended for IC1, but not for IC2, since this will reduce the heatsinking by the circuit board.

Some attention must be paid to the heatsinking of IC2. No heatsink is required with load impedances greater than 8 ohms, provided the case is well ventilated. With impedances down to 4 ohms a heatsink area of at least 4 square inches is required.



# special offer!

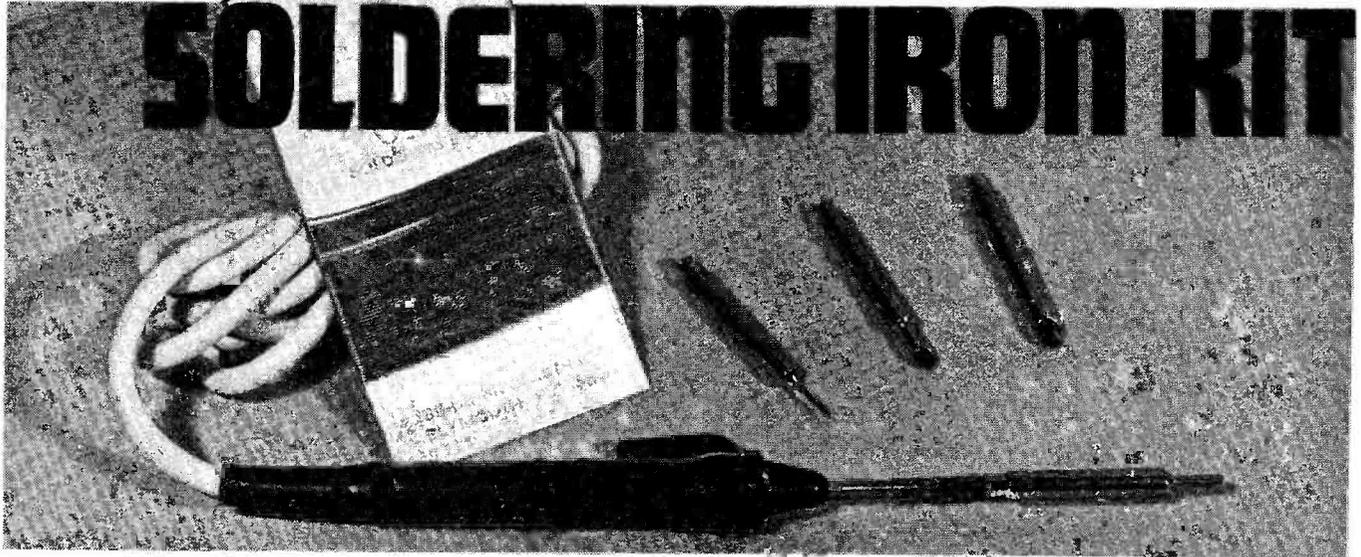

## SOLDERING IRON KIT

This month we offer to PW readers the chance to buy a miniature soldering iron kit at a substantial saving on normal prices. Why not treat yourself—or, with the festive season fast approaching, perhaps you could persuade your nearest and dearest to get one for your Christmas stocking.

A choice of two packs is available, each containing an S & R Brewster miniature 18 watt soldering iron. This slim lightweight iron has a built-in suspension hook, is about 190mm in length and is fitted with some 1.85m of 3-core mains lead. It is suitable for operation on 220-240V, giving a power of 16-18 watts, and complies with Consumer Protection Regulations, BS No. 3456 2/14.

Also in each kit are four interchangeable bits—one each of No's 19 (1.5mm tip size), 20 (3.0mm), 21 (4.5mm) and 22 (6.0mm). An instruction leaflet will be included in each kit.

The packs available to readers are as follows:—

**PACK A:** The iron and four bits as described above. The recommended retail price of such a pack would be £4.73 including VAT; the special "all-inclusive" price to readers is £3.75.

**PACK B:** The iron and four bits as PACK A, PLUS 6m of Multicore Savbit solder 22 SWG and one 1 amp fuse. The recommended retail price of this pack would be £5.29; the special "all-inclusive" price to readers is £4.15.

*Practical Wireless, December 1977*

Please complete both parts of the coupon below in **BLOCK CAPITALS**.

**To: PRACTICAL WIRELESS,**

**Dept. PWL1, Rochester X, Kent, ME99 1AA.**

Please send me the Soldering Iron Kit(s) as indicated below.

I enclose P.O./Cheque No. .... Value .....

	PACK A AT £3.75	PACK B AT £4.15
No. of packs required		

**Name:** .....

**Address:** .....

**Tel. No. (Home or Work)** .....

	PACK A	PACK B
No. of packs required		

**Name:** .....

**Address:** .....

**From: PRACTICAL WIRELESS,  
Dept. PWL1, Rochester X, Kent, ME99 1AA**

.....Cut Round Dotted Line.....

Orders are normally despatched within 28 days but please allow time for carriage. You will be notified if a longer delay may be expected.

Remittances must be by postal order or cheque (name and address on back of cheques, please) crossed, and made payable to IPC Magazines Ltd. This offer is open to readers in England, Scotland, Wales, Northern Ireland, and Channel Islands only. It is **not available** in Eire or Overseas.

Offer closes on 30th December, 1977.

# So you want to pass the R.A.E. (Radio Amateurs' Examination)?


No. 4

John Thornton Lawrence GW3JGA & Ken Mc Coy GW8CMY

The passing of the Radio Amateurs' Examination, set by the City and Guilds, requires a certain level of theoretical technical knowledge. Whether one considers that this level is too high or too low is beside the point. The course that follows is intended, with the help of certain external aids, to prepare the reader to pass the examination. It will not teach him all about electronics!
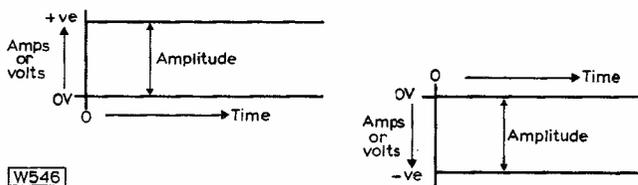
## Alternating current


In the previous sections we have dealt with direct current and we know that D.C. maintains a steady value, either positive or negative in polarity, as shown graphically below. Alternating Current (A.C.) on



W546

the other hand, varies in a special way and to understand this, we return to the magnetics section. You will remember that when a conductor is moving in a magnetic field, the direction of the induced voltage (and the resultant induced current) depends on the direction of movement and the direction of the magnetic field.

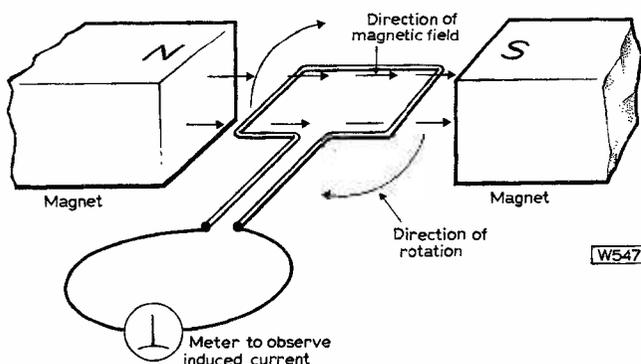Let us imagine two bar magnets, a loop of wire and a current meter, arranged:



The loop is rotated and, using Fleming's Left Hand Rule, we look in detail at the induced currents in the loop, as shown in Fig. 14. In (a) no current flows because the direction of movement of the conductors forming the loop is parallel to the direction of the magnetic field. In (b) current begins to flow in the direction shown, as the conductor cuts across the field. In (c) maximum current flows as the conductors now cut the field at right angles. In (d) the current is decreasing and at (e) again no current flows. Here the position is similar to (a) except that conductors A and B are transposed. This means that when moving

to (f) and beyond, conductors A and B are then cutting the field in the opposite direction. This results in the flow of current being reversed every half revolution. This is shown graphically in Fig. 15 and it can be seen that in one revolution, the current starts at zero, rises to a positive maximum and falls to zero again, then rises to a negative maximum and again falls to zero, thereafter the pattern is repeated for every revolution of the loop. If the rotation is continuous and at a constant speed then the **peak amplitude** of the voltage (and resultant current) waveform and the **period** are also constant.

## The Sine Wave

The shape of the alternating waveform we have observed is called **sinusoidal** or a **sine wave** because the amplitude of the voltage or current at any point during the cycle is related to the trigonometrical function called the 'sine' of the angle of rotation. Fig. 16 will help you to remember some of the terms used when referring to sine waves. The amplitude at the peak of a sine wave is known as the **peak value**. Because the instantaneous value is continuously varying between the peak value and zero, the value which is equivalent in heating effect to D.C. lies between these values. It is known as the **root mean square** or **rms value** and it is this rms value which we use when stating the mains supply voltage, transformer ratings, etc. The rms value is 0.707 of the peak value and conversely, the peak value is 1.414 the rms value. For example, the peak value of the 240 volt mains supply is  $240 \times 1.414 = 339$  volts. The peak value is of particular interest when specifying the maximum voltage rating of components in an A.C. circuit.

In Fig. 16, a 2Hz sine wave is shown, each period or cycle occupying 0.5 second.

As a further example, suppose that the time of one period was 1 ms (1/1,000 second) then there would be 1,000 cycles or periods in 1 second and the frequency would be written as 1,000 Hz or 1 kHz.

$$f \text{ (frequency)} = \frac{1}{t \text{ (time of one period)}}$$

$$\text{and } t = \frac{1}{f}$$

## Now test yourself:

Q. If the time of one period of an alternating current supply is 0.02 second (or 0.0166666 second if you live in the U.S.A.) what is the frequency?

A. The answer to this one is engraved on the front of your electricity supply meter.

The alternating current supply to your home is generated at the power station in a similar manner to the mechanically rotating coil we have just described. The alternating current passing from an Amateur VHF transmitter to the aerial is generated



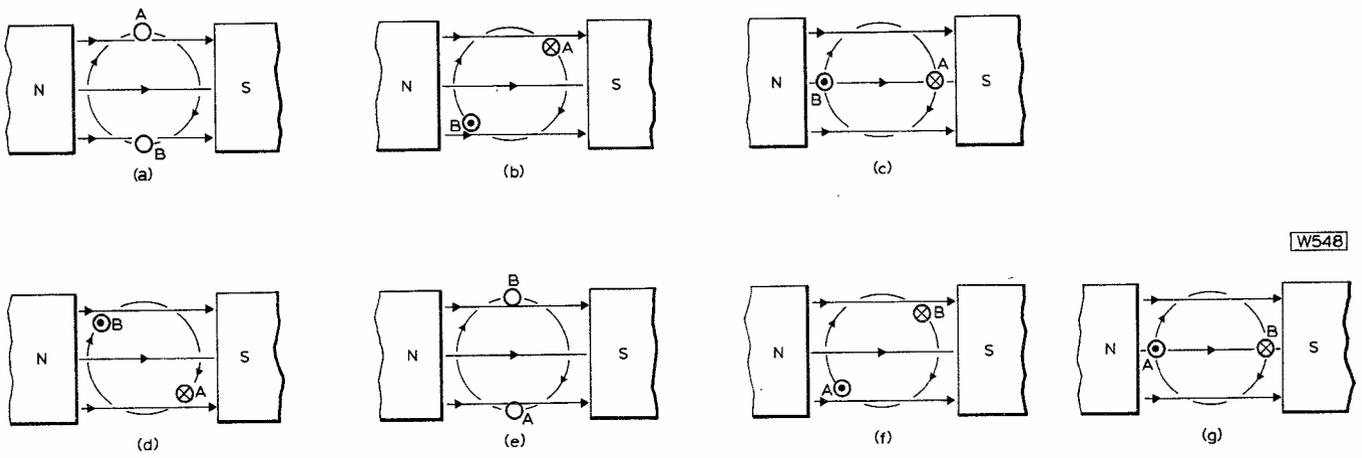


Fig. 14: (above) and Fig. 15 (below).

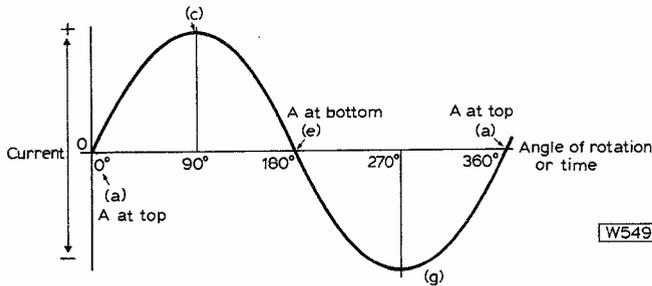

W549

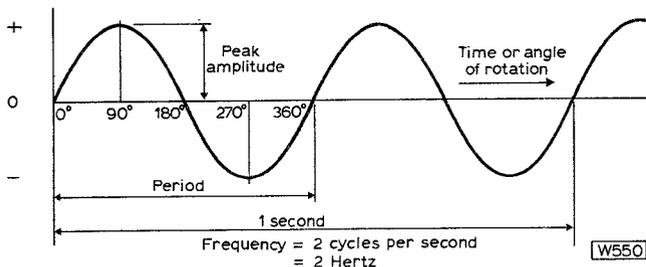by a valve or transistor oscillator and amplifier. The frequency may be 145MHz (145,000,000 cycles-per-second) but the alternating current is still a sine wave and it has the same properties as its lower frequency compatriot.



W550


Fig. 16: 2Hz sine wave, showing peaks.

### Self Inductance

When a conductor is carrying A.C., the magnetic field produced by the current varies in both amplitude and direction. This variation of the magnetic field around the conductor induces, by self inductance, a voltage (back e.m.f.) in the conductor and this produces a current which opposes the 'main' current producing it (Lenz's Law).

In a straight conductor, the self induced current is smaller than if the conductor is wound into a coil or solenoid. Here the magnetic field lines surrounding each conductor also pass through adjacent conductors and induce currents in these which also oppose the 'main' current. The effect is shown diagrammatically in Fig. 17. The self inductance of a coil depends on a number of factors including the number of turns, the diameter of the conductor, the permeability of

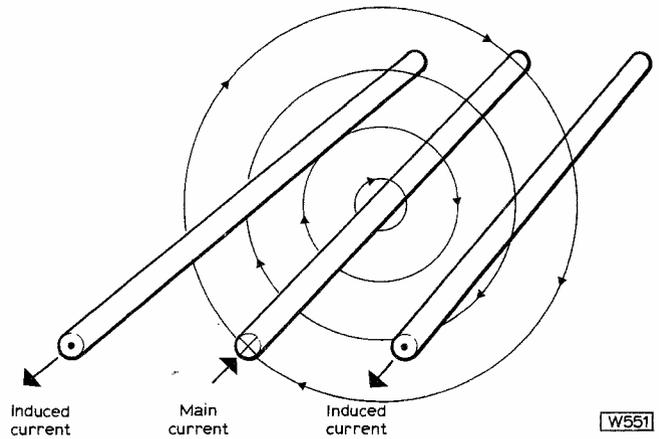the material in the core, and the volume and general configuration of the coil. The unit of self inductance or inductance is the Henry (H) and practical coils or inductances may have values from a few microhenrys ( $\mu\text{H}$ ) to several millihenrys (mH) for radio frequency use and up to many tens of Henrys for low frequency purposes.




W551

Fig. 17
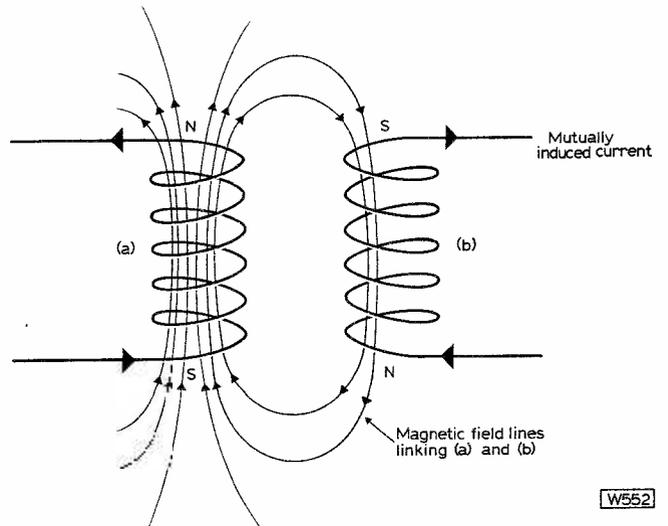
### Mutual Inductance

Mutual inductance is easier to visualise than self inductance and is shown in diagram form in Fig. 18:



W552


Suppose we pass a current through coil A in the direction shown. The resultant magnetic field lines link it with B and induce a voltage and resultant current in that coil. (Note that the current flowing in coil B is opposite to that in A. See Memory Aid Fig. 7.)

If an alternating current is made to flow in A, then for each change in current direction there will be a change in magnetic field direction and a resultant change in the induced voltage and current in B. In other words, an alternating current in A produces an alternating current in B. The circuits are electrically isolated but magnetically linked or coupled by the 'magnetic circuit'. You will no doubt recognise this as the action of a transformer.

all of the primary field lines pass through the secondary winding. The losses in the windings themselves result from power being dissipated as heat due to the ohmic resistance of the copper wire used. With careful design, transformers can be made where these losses are very small indeed, in fact a modern power transformer can have an efficiency as high as 98%.
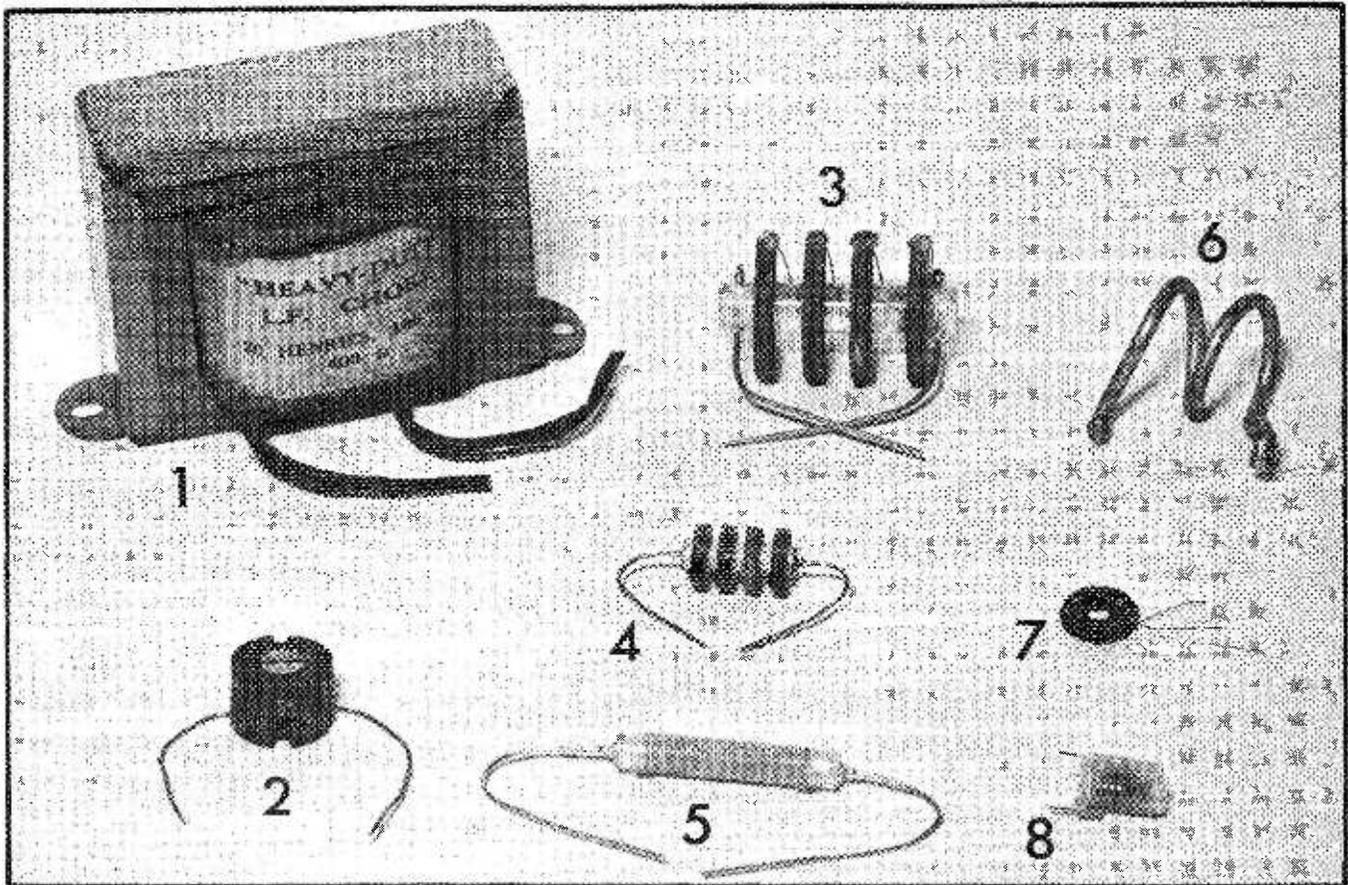
### Transformer types

Transformers come in many shapes and sizes. The construction may vary between two "hairpins" of heavy gauge wire making a transformer that will couple power out of a VHF or UHF transmitter, to



1: Heavy duty L.F. choke. 2: Ferrite pot-core inductance. 3: Transmitting H.F. choke. 4: H.F. choke. 5: VHF choke. 6: VHF transmitter tank coil. 7: Ferrite toroid inductance. 8: VHF tuning inductance.

### The Transformer

A Transformer consists of two (or more) coils or 'windings' magnetically coupled, so that an alternating current in one coil, the **primary**, produces an alternating current in the other, the **secondary**. The method of magnetically coupling the coils depends largely on the frequency of the alternating current with which it will be used.

Providing that the primary and secondary windings have the same number of turns then the secondary current will be almost equal to the primary current and the secondary voltage almost equal to the primary voltage. It will not be exactly equal because of losses in the magnetic circuit and in the resistance of the windings. The losses in the magnetic circuit are mainly due to a loss of induced current because not

the heavy, laminated iron cored, version found in the mains transformer. The primary and secondary windings need not be physically placed side by side. Often they are wound one on top of the other, or adjacent, end to end. The windings may also share a common core material, such as in the mains transformer. This serves to concentrate the linking magnetic field, improving the efficiency of the magnetic circuit. The windings may also form part of a tuned circuit, as in the case of the I.F. transformer, which we will be dealing with later.

### Basic rules

There are some basic rules that apply to transformers, particularly low frequency and power types, which define the relationships between **primary and secondary current**, **primary and secondary voltage** and the **numbers of turns** in the primary and secondary windings. These are best summarised in some

simple equations, but let us first define the quantities involved.

- Primary current =  $I_p$
- Secondary current =  $I_s$
- Primary voltage =  $V_p$
- Secondary voltage =  $V_s$
- No. of primary turns =  $N_p$
- No. of secondary turns =  $N_s$

In these equations we will ignore the losses which occur since they are relatively small, so that:

$$\frac{V_{\text{secondary}}}{V_{\text{primary}}} = \frac{\text{No. of secondary turns}}{\text{No. of primary turns}}$$

$$\text{or } \frac{V_s}{V_p} = \frac{N_s}{N_p}$$

also:

$$\frac{I_p}{I_s} = \frac{V_s}{V_p}$$

We may combine these two equations, as follows:

$$\frac{I_p}{I_s} = \frac{N_s}{N_p} = \frac{V_s}{V_p}$$

Using these equations it is possible, if we know some of the quantities involved i.e. current, voltage, no. of turns, to calculate the others without too much trouble.

#### Example 1

A mains transformer has a 250 volt primary winding and a secondary winding that provides 15 volts for use in a low voltage supply unit. How much current can be drawn from the secondary if the primary current is 0.5 amps?

The part of the equation we require is:

$$\frac{I_p}{I_s} = \frac{V_s}{V_p}$$

putting in the values that we know:

$$\frac{0.5}{I_s} = \frac{15}{250}$$

Rearranging we get:

$$I_s = \frac{0.5}{0.06} = 8.33 \text{ amps (say 8 amps)}$$

So we have found that we may draw 8 amps from the secondary winding, at 15 volts.

#### Example 2

A mains transformer has the following windings:

- Primary 240 volts
- Secondary (a) 1000 volts
- Secondary (b) 12 volts

The primary winding consists of 1,440 turns of wire. Assuming there are no losses, calculate the turns required for the secondary windings (a) and (b).

$$\frac{N_s}{N_p} = \frac{V_s}{V_p} \text{ therefore } N_s = N_p \times \frac{V_s}{V_p}$$

$$N_s (a) = 1440 \times \frac{1000}{240} = 6000 \text{ turns}$$

$$N_s (b) = 1440 \times \frac{12}{240} = 72 \text{ turns}$$

## CONSTRUCTION

### Inductances and Chokes

In a practical circuit the actual value of the inductance and its construction is governed largely by the frequency and the characteristics of the circuit in which it is to be used. A selection of inductors and chokes is shown in the photograph.

Low frequency laminated iron-cored chokes are used for filtering purposes in D.C. power supplies. The winding is carried on a bobbin, through which the core is assembled. In audio frequency circuits, chokes may also be wound and enclosed in a ferrous material 'pot-core'.

Intermediate and low radio frequency coils are usually layer wound on a former or tube, sometimes in several sections to reduce self capacitance. Tuning coils are wound on a former inside which is a threaded core of iron dust material which can be

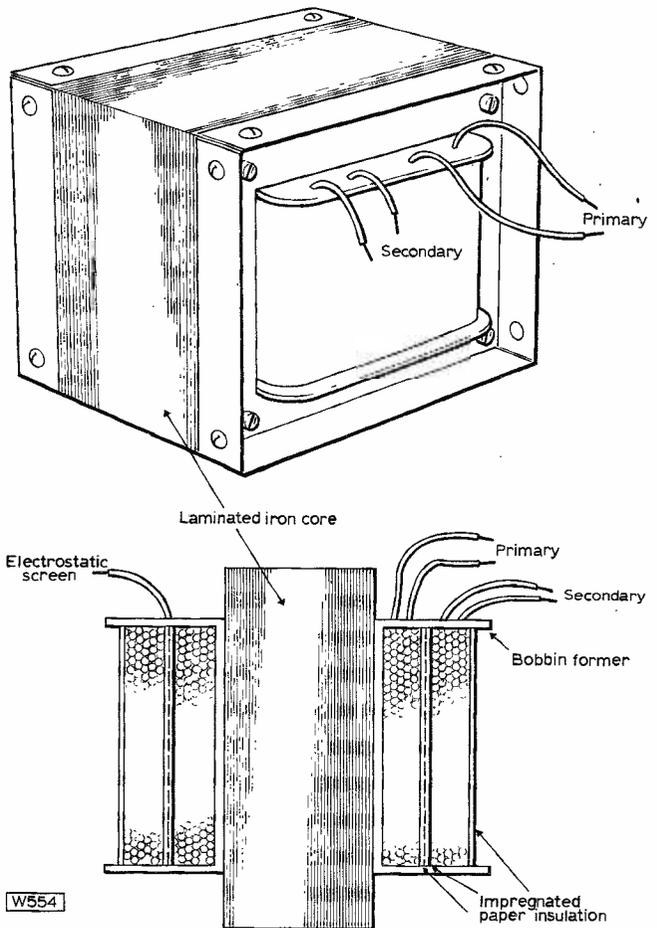


Fig. 20: Mains transformer-physical construction.

screwed in and out to adjust the inductance to the exact value required. Coils for HF and VHF are usually made of thicker wire wound on low-loss formers or self supporting with an air 'core'. At UHF inductors may be in the form of strips or lines of flat strip or rod and bear little physical resemblance to a conventional coil.



Fig. 21: Mains transformer (18V rectifier trans.). 2: Transistor driver transformer. 3: I.F. transformer. 4: Miniature I.F. transformer. 5: R.F. transformer coil. 6: Broadband R.F. transformer.

## Transformers

The mains transformer has windings designed to suit the expected operating conditions. If the transformer has to provide a high value of current (as in our Example No. 1) then the windings are of heavy gauge (diameter) wire, appropriate to the current, so that the overall resistance of the winding is small and the power lost, also small. The mains transformer often has an electrostatic screen between the primary and secondary windings. This is connected to 'earth' and prevents any capacitive leakage or other effects from affecting the secondary windings. The windings themselves consist of enamel covered copper wire wound on a bobbin with layers of insulating material between each winding. The core is made up of thin laminations of special iron to reduce 'eddy current' losses. Eddy currents are produced in the core by induction (remember that iron is also a conductor) and the laminations provide many breaks in the electrical continuity of the core material thus preventing the flow of eddy currents while leaving its magnetic properties largely unaffected.

Transformers for audio frequencies are similar in construction to power transformers but the core material is specially made to operate over a wide frequency range and to cause negligible distortion.

I.F. (Intermediate Frequency) transformers usually consist of two windings which are each tuned to the operating frequency by associated capacitors and adjustable tuning iron dust cores. The magnetic coupling between the windings is critical and is set in manufacture to provide the desired selectivity characteristic.

R.F. (Radio Frequency) transformers vary widely in design and construction and may be wound on a former with or without an adjustable core. R.F. transformers for use over a wide range of frequencies are sometimes wound on a ferrite ring. The secondary winding may be separate from or interwound with the primary.

# KINDLY NOTE!

## IC of the month—Nov 1977

We apologise to our readers, and to Ferranti Ltd., for misquoting the type number of the timer IC on the cover and contents page of the magazine. The number should be ZN1034E, as given in the article.

## Low Distortion Sine/Square Wave Generator, October 1977

In Fig. 1 the connection from the switch S2a 'Sine' position should go only to VR5, and not to S3 or VR2. The PCB is correct. If the circuit is constructed on other than our PCB, using Fig. 1, the effect of the error will be that the output attenuator will be inoperative on 'Sine'.

Resistors R4 (3.3k $\Omega$ ) and R5 (680 $\Omega$ ) are shown transposed on the PCB. The circuit diagram is correct.


## Solo Supermind, October 1977

The case details should be "R.S.Comps. code 509-276, with a front panel size of 250mm x 130mm. If inaccuracies are noted in meter deflection, resistors R1 to R8 (all 2.2k $\Omega$ ) should be changed to 2k $\Omega$  high stability (metal oxide).

# The Sinclair PDM35.

## A personal digital multimeter for only £29.95

(+8% VAT)

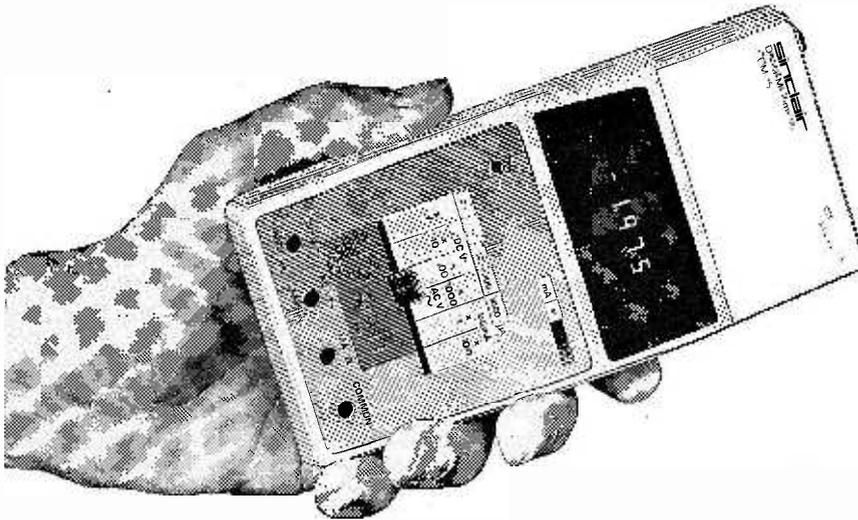

### Now everyone can afford to own a digital multimeter

A digital multimeter used to mean an expensive, bulky piece of equipment.

The Sinclair PDM35 changes that. It's got all the functions and features you want in a digital multimeter, yet they're neatly packaged in a rugged but light pocket-size case, ready to go anywhere.

The Sinclair PDM35 gives you all the benefits of an ordinary digital multimeter – quick clear readings, high accuracy and resolution, high input impedance. Yet at £29.95 (+8% VAT), it costs less than you'd expect to pay for an analogue meter!

The Sinclair PDM35 is tailor-made for anyone who needs to make rapid measurements. Development engineers, field service engineers, lab technicians, computer specialists, radio and electronic hobbyists will find it ideal.

With its rugged construction and battery operation, the PDM35 is perfectly suited for hand work in the field, while its angled display and optional AC power facility make it just as useful on the bench.

### What you get with a PDM35

3½ digit resolution.

Sharp, bright, easily read LED display, reading to ± 1.999.

Automatic polarity selection.

Resolution of 1 mV and 0.1 nA (0.0001 μA).

Direct reading of semiconductor forward voltages at 5 different currents.

Resistance measured up to 20 MΩ.

1% of reading accuracy.

Operation from replaceable battery or AC adaptor.

Industry standard 10 MΩ input impedance.

### Compare it with an analogue meter!

The PDM 35's 1% of reading compares with 3% of full scale for a comparable analogue meter. That makes it around 5 times more accurate on average.

The PDM35 will resolve 1 mV against around 10 mV for a comparable analogue meter – and resolution on current is over 1000 times greater.

The PDM35's DC input impedance of 10 MΩ is 50 times higher than a 20 kΩ/volt analogue meter on the 10 V range.

The PDM35 gives precise digital readings. So there's no need to interpret ambiguous scales, no parallax errors. There's no need to reverse leads for negative readings. There's no delicate meter movement to damage. And you can resolve current as low as 0.1 nA and measure transistor and diode junctions over 5 decades of current.

### Technical specification

#### DC Volts (4 ranges)

Range: 1 mV to 1000 V.

Accuracy of reading 1.0% ± 1 count.

Note: 10 MΩ input impedance.

#### AC Volts (40 Hz-5 kHz)

Range: 1 V to 500 V.

Accuracy of reading: 1.0% ± 2 counts.

#### DC Current (6 ranges)

Range: 1 nA to 200 mA.

Accuracy of reading: 1.0% ± 1 count.

Note: Max. resolution 0.1 nA.

#### Resistance (5 ranges)

Range: 1Ω to 20 MΩ.

Accuracy of reading: 1.5% ± 1 count.

Also provides 5 junction-test ranges.

**Dimensions:** 6 in x 3 in x 1½ in.

**Weight:** 6½ oz.

**Power supply:** 9 V battery or Sinclair AC adaptor.

**Sockets:** Standard 4 mm for resilient plugs.

**Options:** AC adaptor for 240 V 50 Hz power. De-luxe padded carrying wallet. 30 kV probe.

### The Sinclair credentials

Sinclair have pioneered a whole range of electronic world-firsts – from programmable pocket calculators to miniature TVs. The PDM35 embodies six years' experience in digital multimeter design, in which time Sinclair have become one of the world's largest producers.

### Tried, tested, ready to go!

The Sinclair PDM35 comes to you fully built, tested, calibrated and guaranteed. It comes complete with leads and test prods, operating instructions and a carrying wallet. And getting one couldn't be easier. Just fill in the coupon, enclose a cheque/PO for the correct amount (usual 10-day money-back undertaking, of course), and send it to us.

We'll mail your PDM35 by return! Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ, England. Regd No: 699483.

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.

Please send me \_\_\_\_\_ (qty) PDM35(s)  
@ £33.00 (inc £2.40 VAT and 65p P&P)  
each: \_\_\_\_\_ £ \_\_\_\_\_

\_\_\_\_\_ (qty) De-luxe padded  
carrying case(s) @ £3.00 (inc VAT  
and P&P) each: \_\_\_\_\_ £ \_\_\_\_\_

\_\_\_\_\_ (qty) AC adaptor(s) for  
240 V 50 Hz power @ £3.00  
(inc VAT and P&P) each: \_\_\_\_\_ £ \_\_\_\_\_

I enclose cheque/PO made payable  
to Sinclair Radionics Ltd for  
(indicate total amount): \_\_\_\_\_ £ \_\_\_\_\_

I understand that if I am not completely  
satisfied with my PDM35, I may return it  
within ten days for a full cash refund.

Name: \_\_\_\_\_

Address: \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

PW/12

 **sinclair**  
World leaders in fingertip electronics

TTLS by TEXAS		74L's		CMOS		OP. AMPS.		NE531V 140p		MEMORY I.Cs		MPSA56 40p		2N2907A 25p		DIODES		OA202 10p		
7400	14p	7497	290p	74LS00	30p	4000	20p	CA3130	108p	709	40p	1702A	EPROM	£10	2N2926RB	8p	BY127	12p	IN14	4p
7401	14p	74100	140p	74LS02	30p	4001	20p	CA3140	108p	733	150p	2102-2	RAM	216p	2N2926GB	11p	OA47	9p	IN196	7p
7402	16p	74105	75p	74LS04	30p	4006	95p	CA3160	120p	741	25p	2107	RAM	864p	2N3053	22p	OA81	15p	IN4001/2	6p
7403	16p	74106	75p	74LS08	30p	4007	20p	LM301A	40p	747	75p	2112-2	RAM	470p	2N3054	65p	OA85	15p	IN4003/4	7p
7404	24p	74107	36p	74LS10	32p	4008	115p	LM316N	40p	748	40p	3003A	3 U.	410p	2N3405	65p	OA90	9p	IN4005/7	5p
7405	25p	74108	80p	74LS13	35p	4009	150p	MC1324N	130p	776	216p	AY-1013	UART	725p	2N3442	151p	OA91	9p	IN4145	4p
7406	40p	74110	60p	74LS20	32p	4010	60p	MC1458P	75p	3500	70p	803-2513	ROM	850p	OC71	32p	OA95	9p	IN5401/3	15p
7407	40p	74111	75p	74LS22	34p	4011	20p					R20088	225p	2N3644	54p	OA200	9p	IN5404/7	20p	
7408	22p	74116	216p	74LS27	45p	4012	20p					R2010B	225p	2N3702/3	14p					
7409	22p	74118	160p	74LS30	30p	4013	55p					TIP29A	50p	2N3704/5	14p					
7410	18p	74119	225p	74LS34	150p	4014	115p					TIP29C	62p	2N3706/7	14p					
7411	26p	74120	130p	74LS35	45p	4015	90p					TIP30A	50p	2N3708/9	14p					
7412	25p	74121	32p	74LS73	60p	4016	50p					TIP30B	50p	2N3773	320p					
7413	40p	74122	52p	74LS74	60p	4017	100p					TIP31A	76p	2N3819	27p					
7414	85p	74123	75p	74LS75	75p	4018	110p					TIP31C	60p	2N3820	50p					
7416	40p	74125	70p	74LS83	120p	4019	52p					TIP32A	63p	2N3823	70p					
7417	40p	74126	65p	74LS85	144p	4020	120p					TIP32C	85p	2N3866	97p					
7420	18p	74128	82p	74LS86	65p	4021	115p					TIP33A	87p	2N3895/6	22p					
7421	43p	74132	81p	74LS90	80p	4022	100p					AC176	20p	2N4058	19p					
7422	28p	74136	81p	74LS95	80p	4023	100p					AC187B	20p	2N4060	19p					
7423	36p	74141	85p	74LS107	55p	4024	80p					AD149	60p	2N4123/4	22p					
7425	33p	74142	300p	74LS112	120p	4025	22p					AD182	45p	2N4125/6	22p					
7426	43p	74145	95p	74LS123	110p	4026	170p					AD188	45p	2N4401/3	34p					
7427	40p	74147	205p	74LS138	140p	4027	65p					AF114/5	22p	2N4402/7	34p					
7428	40p	74148	160p	74LS139	140p	4028	95p					BF258	30p	2N4437	87p					
7430	18p	74150	130p	74LS144	110p	4029	120p					AF127	40p	2N4471	60p					
7432	37p	74151	81p	74LS153	200p	4030	55p					AF139	40p	2N5179	75p					
7433	43p	74153	81p	74LS157	130p	4033	250p					AF239	40p	2N5245	45p					
7437	37p	74154	160p	74LS158	150p	4034	240p					BF139	40p	2N5246	99p					
7438	37p	74155	97p	74LS160	180p	4035	130p					BF108/B	10p	2N5401	62p					
7440	16p	74156	97p	74LS161	180p	4040	120p					BF109	16p	2N5402/3	40p					
7441	85p	74157	97p	74LS162	180p	4042	90p					BC109C	11p	2N5459	40p					
7442	75p	74159	250p	74LS163	180p	4043	100p					BC147	9p	2N5485	45p					
7443	120p	74160	100p	74LS164	120p	4044	100p					BC148	8p	2N5607	70p					
7444	120p	74161	100p	74LS165	125p	4046	140p					BC157	11p	2N6027	60p					
7445	108p	74162	100p	74LS173	230p	4047	100p					BC158/9	13p	2N6247	200p					
7446	108p	74163	100p	74LS174	180p	4049	55p					BC196	15p	2N6254	140p					
7447	75p	74164	120p	74LS175	160p	4050	57p					BC172	11p	2N6259	19p					
7448	85p	74165	150p	74LS181	375p	4051	110p					BC177	20p	2N6292	70p					
7450	18p	74166	160p	74LS190	200p	4054	120p					BC178	17p	2N6306/7	75p					
7451	18p	74167	320p	74LS191	200p	4055	140p					BC179	20p	2N6307	90p					
7453	18p	74170	260p			4056	135p					BC182/3	12p	2N6311	22p					
7454	18p	74171	260p			4060	130p					BC183	12p	2N6312	22p					
7460	18p	74173	190p	74C00	25p	4062	65p					BC187	32p	40360	43p					
7470	38p	74174	120p	74C02	25p	4067	425p					BC212	14p	40361/2	43p					
7472	32p	74175	97p	74C04	27p	4068	24p					BC213	12p	40409/10	17p					
7473	36p	74176	130p	74C08	27p	4069	27p					BC214	16p	2N2218	25p					
7474	37p	74177	120p	74C10	21p	4070	65p					BC451	40p	2N2218	25p					
7475	45p	74178	160p	74C14	10p	4071	27p					BC452	40p	2N2222	22p					
7476	37p	74181	324p	74C42	110p	4072	27p					BCY70	35p	2N2369	15p					
7480	54p	74182	150p	74C48	230p	4073	30p					BCY71	24p	2N2484	32p					
7481	108p	74184	250p	74C73	75p	4076	170p					BD124	140p	2N2646	52p					
7482	90p	74185	190p	74C74	70p	4081	21p					BD131/2	65p	2N2904/A	22p					
7483	99p	74186	950p	74C85	200p	4082	24p					BD135/6	54p	2N2905/A	22p					
7484	105p	74190	120p	74C86	65p	4083	120p					BD139	55p	2N2905/B	22p					
7485	120p	74191	120p	74C90	90p	4086	120p					BD140	60p	2N2906/A	22p					
7486	36p	74192	100p	74C93	90p	14502	180p					BDY56	225p	40872	85p					
7488	340p	74193	100p	74C107	125p	14503	90p					BF115	25p	40872	85p					
7490	36p	74194	160p	74C151	260p	14507	55p					BF167	25p							
7491	90p	74195	110p	74C157	250p	14508	300p					BF170	25p							
7492	58p	74196	160p	74C180	155p	14510	160p					BF173	30p							
7493	36p	74197	130p	74C181	65p	14511	160p					BF179	35p							
7494	90p	74198	250p	74C182	155p	14516	120p					BF180/1	35p							
7495	75p	74199	250p	74C163	155p	14515	160p					BF184/5	24p							
7496	90p	74221	175p	74C164	140p	14528	130p													

# B. BAMBER ELECTRONICS

Dept. P.W.5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE  
Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

**PLEASE ADD 8% VAT UNLESS OTHERWISE STATED**

**A MERRY XMAS TO ALL OUR CUSTOMERS PLUS A XMAS PRESENT FROM US IN THE FORM OF A 10% DISCOUNT ON ALL ORDERS RECEIVED FROM 1st to 31st DECEMBER**

For items in our current ads and lists only

**THIS OFFER IS FOR 1 MONTH ONLY**

Slider Switches, 2 pole make and break (or can be used as 1 pole change-over by linking the two centre pins), 4 for 50p.

**A NEW RANGE OF QUALITY BOXES & INSTRUMENT CASES.**

Aluminium Boxes with Lids.

AB10	5 1/4 x 4 1/2	60p
AB13	8 x 4 x 2	80p
AB14	7 x 5 x 2 1/2	£1.00
AB15	8 x 6 x 3	£1.30
AB16	10 x 7 x 3	£1.50
AB17	10 x 4 1/2 x 3	£1.30
AB25	6 x 4 x 3	£1.00

Vinyl Coated Instrument Cases  
Light Blue tops and White lower sections. Very smart finish.

WB1	5 x 2 1/2 x 2 1/2	60p
WB2	6 x 4 1/2 x 1 1/2	£1.10
WB3	8 x 5 x 2	£1.60
WB4	9 x 5 1/2 x 2 1/2	£1.80
WB5	11 x 6 1/2 x 3	£2.00
WB6	12 x 7 1/2 x 3 1/2	£2.20
WB7	12 x 6 1/2 x 5 1/2	£2.50
WB853	8 x 5 1/2 x 3 1/2	£2.00

**MAINS TRANSFORMERS.** Type 60/2, Mains input 200-210-220-230-240-250V a.c., output 0-20-40-60V at 2A, 10 to Metal and Plastic case, approx. 7 1/4 x 4 x 4, fully fused (ideal for PSU) £3.00 each.

**MAINS TRANSFORMERS.** Type 15/300 240V input, 15V at 300mA output, £1.50 each.

**MAINS TRANSFORMERS.** Type 45/100, 240, 220, 110, 20, 0V input, 45V at 100mA output, £1.50 each.

**PLEASE ADD 8% VAT UNLESS OTHERWISE STATED**

**MAGNETIC DEVICES PROGRAMMERS.** Contain 9 fully adjustable cams and 9 change over micro-switches (rated approx. 1A at 240VAC). Needs slow-motion motor to drive (not supplied). Ideal for disco lights, sequence switching, etc. ex equipment £1.50 each.

**VIDICON SCAN COILS** (Transistor type, but no data), complete with vidicon base £5.50 each. Brand New.

**FULL RANGE OF BERNARDS/BABANI ELECTRONICS BOOKS IN STOCK. S.A.E. FOR LIST.**

**NEW FOR THE VHF CONSTRUCTOR.** A range of tuned circuits on formers with slugs and screening cans. Frequencies quoted are approximate, and range can be greatly extended by using varicap capacitors in parallel.

Type S (1/4 in square, dummy type).  
Type SA 20 to 30MHz (when 33pF fitted in parallel).  
Type SB 35 to 50MHz (with link winding).  
Type SC 70 to 100MHz (with link winding).  
Type SD 135 to 175MHz (with link winding).  
Type M (Min. 1/4 in square types).  
Type MA 19 to 28MHz (when 33pF fitted in parallel).  
Type MB 22 to 32MHz (when 33pF fitted in parallel).  
Type MC 25 to 35MHz (when 33pF fitted in parallel).  
Type MD 38 to 50MHz (when 33pF fitted in parallel).  
Type ME 45 to 80MHz (when 33pF fitted in parallel).  
Type MF 100 to 200MHz (without slug) when 0.30pF variable fitted in parallel.  
All the above coils available in packs of five only (same type) at 50p per pack of 5.

**SEMICONDUCTORS**

BSX20 (VHF Osc/Mult), 3 for 50p.  
BC108 (metal can), 4 for 50p.  
PBC108 (plastic BC108), 5 for 50p.  
BFY51 Transistors, 4 for 50p.  
BCY72 Transistors, 4 for 50p.  
PNP audio type T05 Transistors, 12 for 25p.  
BF152 (UHF amp/mixer), 3 for 50p.  
2N818 Fet., 3 for 60p.  
BC148 NPN SILICON, 4 for 60p.  
BC158 PNP SILICON, 4 for 60p.  
BAY31 Signal Diodes, 10 for 35p.  
BA121 Varicap Diodes, 4 for 50p.

741CG op amps by RCA, 4 for £1.

**RED LEDs** (Min. type) 5 for 70p.

**PLASTIC PROJECT BOXES** with screw on lids (in black ABS) with brass inserts.  
Type NB1 approx 3 1/2 in. x 2 1/2 in. x 1 1/2 in. 40p each.  
Type NB2 approx. 3 1/2 in. x 2 1/2 in. x 1 1/2 in. 50p each.  
Type NB3 approx. 4 1/2 in. x 3 1/2 in. x 1 1/2 in. 60p each.

**MULLARD 85A2 85V STABILISER VALVES** (Brand New) 70p each or 2 for £1.20.  
T03 transistor insulator sets, 10 for 50p

# L.E.D.

# TUNING INDICATOR

J.P. MACAULAY

Most modern FM tuners either employ, or make provision for, a centre zero meter to indicate when accurate tuning has been achieved. However, a suitable meter can be expensive and requires hole-cutting and drilling of chassis to fit. These thoughts prompted the author to design and build a completely solid state equivalent which will cost the constructor less than £1, assuming that all the components are bought new.

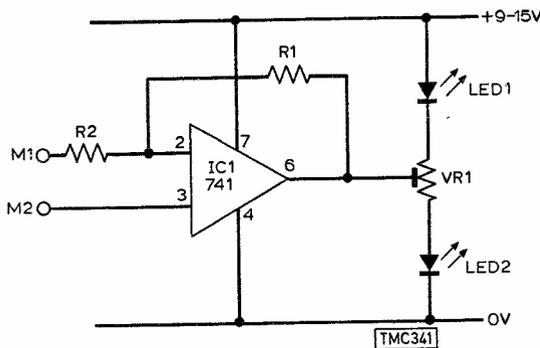


Fig. 1: Circuit of the tuning indicator.

## Circuit Outline

By using a 741 op amp in the differential mode and driving a pair of LED from the output a very simple circuit can be realised employing only 6 basic components. The circuit diagram is shown in Fig. 1. Here the dc voltage across the meter output terminals is applied to the inverting and non-inverting inputs of the op-amp, pins 2 and 3 respectively.

Since very few components are employed the circuit can be constructed on a small piece of Veroboard and supported by the LED mounting clips. A suitable layout is shown in Fig. 2. The prototypes which have so far been constructed have been tried on a number of tuners which already possessed a tuning meter and the circuit described has been found to be virtually as accurate.

With the circuit wired into the tuner a check is made that both LED are illuminated. A point off-station is tuned so that only inter-station noise is being received, and VR1 adjusted until both LED are equally illuminated.

## ★ components

### Resistors

R1 1MΩ, R2 2.2kΩ, both ¼ watt, 5% carbon, VR1 1kΩ horizontal preset.

### Semiconductors

IC1 741, LED 1 and 2, 0.2" diam, 50mA max, colour to choice.

### Miscellaneous

Veroboard 0.1" matrix, 47mm × 38mm, LED clips.


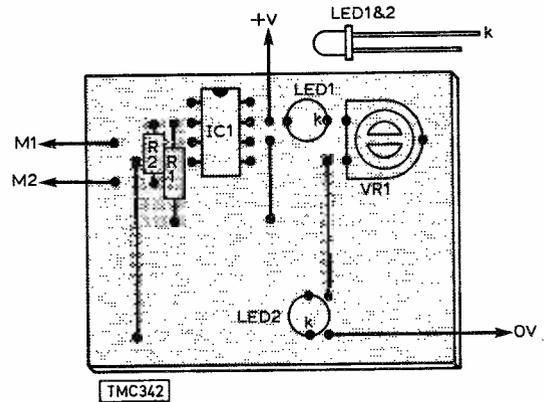


Fig. 2: Physical layout.

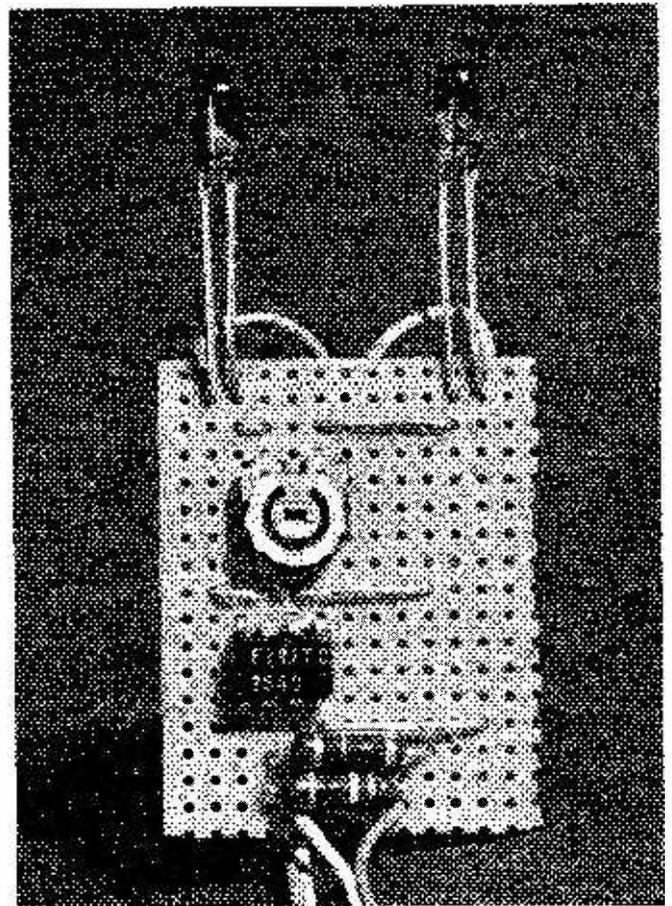


A station is tuned in, and as tuning proceeds the LED will vary in brightness, the correct tuning position being the point where they are both equally illuminated.

**SPECIAL  
PRODUCT  
REPORT**

# CHROMATRONICS

## the 'chroma ~chime'

KIT

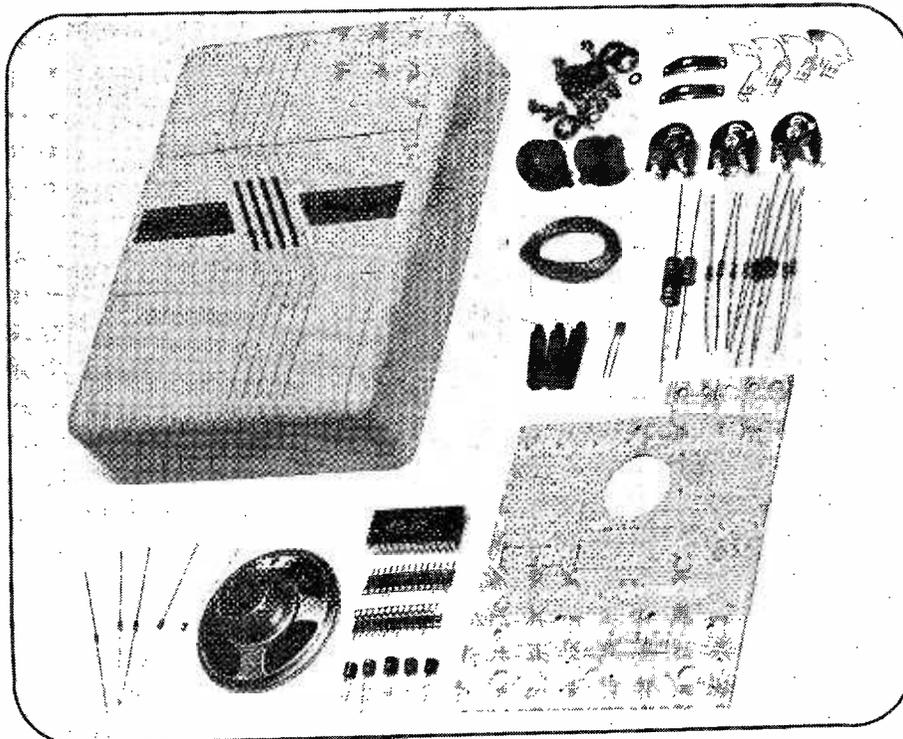

The Chroma-Chime is an electronic door chime which provides a selection of 24 different tunes. Readers may already have seen advertisements for the complete unit, which has also been featured on TV.

The heart of the design is a microprocessor chip, produced for Chromatronics by Texas Instruments, and containing all the necessary software (programs) to generate the various tunes. Now, the electronics enthusiast can buy a kit from which he can make up his own chime unit, and probably his first microprocessor-based project, to boot.

Besides the microprocessor itself, the circuit uses five transistors, four diodes and handful of resistors and capacitors, all mounted on a single printed circuit board. The loudspeaker and batteries (two PP3 etc.) are the only off-board components.

Provision is made for the connection of two circuits to external bell-pushes (Front and Back doors?). Closing one of the pushes will cause the unit to play whatever tune has been selected on the two internal switches. Closing the other push will play one tune which is pre-selected by the manufacturer.

Apart from the Tune Selector switches, the other controls are three preset potentiometers which are used to set the Volume, Speed (Tempo) and Tone (Sustain) of the tune.

### Assembly

The kit is supplied complete down to the last screw—even a coil of p.c. solder is included. In the sample kit supplied for review, the loudspeaker had been slightly damaged in transit, but we are assured by Chromatronics

that this item is normally packed in a protective bag, so the problem should not arise again.

Building up the kit is very straightforward, following the instructions given in the comprehensive assembly manual. The time required is quoted as about three hours, but the experienced constructor should be able to manage it in not much over half that time.

The microprocessor is an MOS device which is, of course, susceptible to damage from static electricity. For added safety in assembly, Soldercon sockets are provided for mounting this component. A variety of different transistor types may be included, according to availability. Included in the assembly manual is a table covering every possible type and its leadout configuration. Except, that is, the ones supplied with the review kit! The transistor manufacturer had supplied devices marked with a standard type number but having a non-standard pattern of leadouts. You will not be surprised to learn that the unit did not work when first switched on. Again, Chromatronics assure us they now have this problem under control.

### Results


After sorting out the transistor problems, the unit worked well, providing its allotted selection of tunes. The volume is possibly a bit low for some houses, particularly when TV viewing or Hi Fi listening is in progress. However, terminals are provided for connecting an extension loudspeaker, and a purpose-designed unit will be available shortly.

The kit costs £18 including VAT and postage and packing. It is available from **Chromatronics, River Way, Harlow, Essex.**

# KEEP YOUR COOL
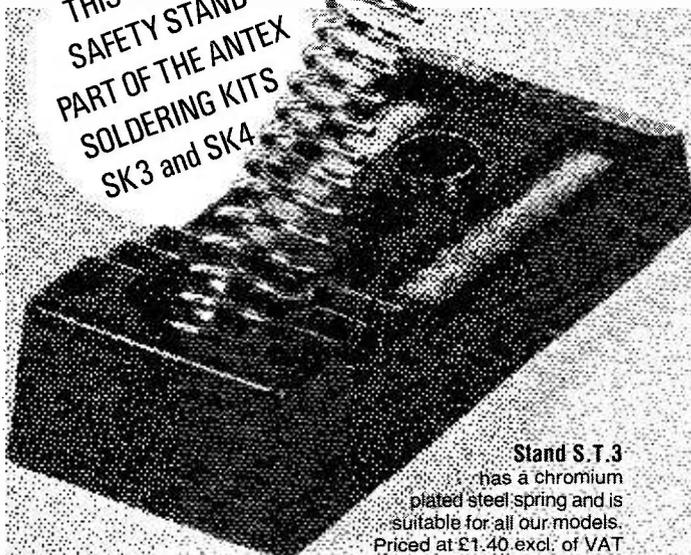
## WITH ANTEX SOLDERING IRONS...

THIS UNIQUE SAFETY STAND - PART OF THE ANTEX SOLDERING KITS SK3 and SK4



Stand S.T.3 has a chromium plated steel spring and is suitable for all our models. Priced at £1.40 excl. of VAT

With the new Antex soldering stand you have the assurance that with the iron tucked neatly into the strong angled spring coil you have maximum safety when preparing or waiting for the iron to heat. Moulded into this stand is provision for six alternative bits, and two small sponges for cleaning bits.

This sturdy plastic stand is a useful addition to any household or workshop. The SK3 and SK4 kits comprise of a full instruction card mounted with either the CX miniature soldering iron or the larger X25 general purpose iron. Included in both of these kits is the safety stand.

All the range of Antex soldering irons are made on the principle of putting the heating element inside a shaft, then the desired bit is eased over the shaft, giving maximum heat transference, this is why so often a small Antex iron can do the job of a larger conventional iron. The precision made slide on bits are slit to make them easily interchangeable.

### Our comprehensive range is sure to meet your need.

**Model CX-17 watts**

... a miniature iron with the element enclosed first in a ceramic shaft, then in stainless steel. Virtually leak-free. Only 7 1/2" long. Fitted with a 3/32" bit. Range of 5 other bits available from 1/4" down to 3/64".

**Model X25-25 watts**

A general purpose iron also with a ceramic and steel shaft to give you toughness combined with near-perfect insulation. Fitted with 1/8" bit and priced at £3.40 excl. of VAT. Range of 4 other bits available. B.E.A.B.-APPROVED.

**Model SK3 KIT**

Contains both the model CX soldering iron and the stand S.T.3. Priced at £4.80 excl. of VAT it makes an excellent present for the radio amateur modelmaker or hobbyist.

**Model SK4 KIT**

With the model X25 general purpose iron and the ST3 stand and its B.E.A.B. safety label, this kit is a must for every toolkit in the home.

**Model SK1 KIT**

This kit contains a 15 watt miniature soldering iron, complete with 2 spare bits, a coil of solder, a heat sink and a booklet, "How to solder." Price £5.30 excl. of VAT.

**Model MLX KIT**

The soldering iron in this kit can be operated from any ordinary car battery. It is fitted with 15 feet flexible cable and battery clips. Packed in a strong plastic envelope it can be left in a car, a boat or a caravan, ready for soldering in the field. Price £3.95 excl. of VAT.

Stocked by most of the well-known wholesalers and many retailers. Or direct from us if you are desperate.



Please send the following ..... I enclose cheque/P.O./Giro No 258 1000

..... Name .....

Please send the ANTEX colour brochure  Address .....

.....

**ANTEX LTD. FREEPOST, PLYMOUTH PL1 1BR TEL. 0752 67377 P.W.12.77**  
**MAYFLOWER HOUSE, PLYMOUTH, DEVON PL1 1BR**

# WIRELESS TIME :



approx. 3/4 full size digits shown here

National's MA1012 LED digital clock module is a complete clock & alarm unit, operating from 50 or 60 Hz mains, and offering all the features you would expect: Hours-minutes display in bright 0.5" leds with optional seconds, sleep and snooze alarms, fast and slow setting, AM/PM indicator, switched alarm outputs - but best of all *no RFL*. Thus the MA1012 is suitable for use in any radio/tuner applications, and requires just 1.75 x 3.75 x 0.7" total. (Ex. transformer). £9.45 per module, isolating mains transformer £1.50 each. (\*8% vat) Two modules, and two transformers for £20.00 (+8% vat)

In the latest *Ambit* catalogue: more TOKO coils, chokes, filters etc., data on the short wave coil sets, a revised price list, micro-microphone inserts, special offer lines etc.

## DETECKNOWLEDGEY

Metal locator principles and practise, including some of the facts and information manufacturers of £100+ detectors would rather you didn't know. £1.00 each.

The Bionic Ferret 4000 - a VCO metal locator based on the PW seekit, including all parts, plasticwork, ready wound coil etc. Inc. free copy of *detecknowledgy*. £34.26 in pp and VAT at 8%.

Special announcement: The Bionic Radiometer metal locator is at last to be released. A full VLF discriminator, with simultaneous display of ferrous, non-ferrous and foil objects. With a little practise, you can actually find objects obscured by junk. Outperforms units costing £150+. *Digital control*. Demo available at Brentwood, on sale soon for less than £75.SAE info:

# COMPONENTS

Herewith the list of first quality parts and modules for wireless, inc. Europe's largest range of signal coils and inductors. 1/2m in stock!

CA3089E	FM IF	1.94	BC413	lo noise	0.18	MFL 2.4 kHz ssb mech.
KB4402	FM IF	1.94	40238	shld RF	0.25*	filter for ssb gen/IF 455kHz
HA1137W	FM IF	2.20	BF224	6ghz RF	0.22	with matching transfs. 9.95
TBA120	FM IF	0.75	BF274	.7ghz RF	0.18	MFH series 4/5/7kHz band-
TBA120S	FM IF	1.00	ZTX212	50v/.3w	0.17	width @ 455kHz
sn76660n	FM IF	0.75	ZTX213	30v/.3w	0.16	1.95
ua720	AM rad	1.40	ZTX214	30v/.3w	0.17	MFK series 7/9kHz bw 1.65
CA3123E	AM rad	1.40	ZTX451	60v/1w	0.18	EC3302 3cct v/cap fm 7.50
HA1197	AM rad	1.40	ZTX551	60v/1w	0.18	EF5600 5cct v/cap fm 12.95
TBA651	AM rad	1.81	BD515	45v/10w	0.27	EF5800 6cct v/cap fm 15.25
MC1350	agc gain	1.00	BD516	45v/10w	0.30	EF5801 (5800+osc op) 17.45
ua753	fm gain	1.80	BD535	60v/50w	0.52	8319 4 v/c, mos mixer 11.45
LM1496	Bal mix	1.25	BD536	60v/50w	0.53	7252 complete fm mono
MC1310P	mpx dec	2.20	BD809	80v/90w	0.70	tunerset.afc,agc,mute 26.50
KB4400	as above	2.20	BD610	80v/90w	1.20	7253 complete fm stereo
ca3090a	mpx dec	4.35	BF256	1ghz fet	0.34	tunerset.afc,agc,mute 26.50
HA1196	mpx dec	4.20	E176	p ch swt	0.38	7020 10.7MHz fm if 6.95
LM380	2w AF	1.00	MEM614	(40822)	0.38*	7030 linear phase fm if 10.95
LM381	preamp	1.81	MEM616	(40673)	0.67*	93090 ca3090agc dec 8.36
tda2020	15w AF	2.99	MEM680	lo noise	0.75*	92310 1310 decoder 6.95
tca940E	10w AF	1.80				91196 ha1196 decoder 12.99
tba810as	7w AF	1.08	BA102	vhf varic	0.30	91197 mw/v/cap tun.1.35
LM3390	op amp	0.39*	BA121	vhf varic	0.30	7122 3 v/c mw (OR lw) tuner
7805UC	op amp	0.34*	BB104	dual var.	0.45	KIT 15w tuning 9.00
tda1412	op amp	0.68*	BB105	uhf varic	0.40	810k 7w af kit comp. £3
78M20	5v/1amp	1.55*	mvam2	dual AM	1.48	940k 10w af kit 3.95
78M24	12v/1A	0.95*	mvam115	15v/AM	1.05	tda2020k pr. tda2020 ics,
ua5723cn	20v/1A	1.20*	mvam125	25v/AM	0.90	pcb, heatsinks for pa 9.35
NE550a	variable	0.80*	<b>TOKO Coils &amp; Filters</b>			
tas550b	as above	0.80*	10mm & 7mm (rad cont)			All mpx decoders feature
ic18038cc	32v ref	0.50*	AM IFts with cap	0.30		TOKO pilot tone filters.
NE569v	sig gen	4.50*	FM IFts with cap	0.33		<b>Tuners: complete</b>
NE567v	timer	0.70*				Larsholt signalmaster Mk 8
NE560B	vco	2.50*	YHCS11098AC2	0.30		Best fm tuner kit under £100
NE561B	tone dc	2.50*	YHCS12374AC2	0.30		Looks as good as it sounds.
NE565K	hf pll	3.50*	YHCS11100AC2	0.30		Full instructions 86.95
MC1312	hf pll	3.50*	KALS4520A	0.33		Audiomaster amp. Matching
11C90	quad	1.50	KACSK586HM	0.33		25+25w rms amp. 79.00
ZTX107	50v/.3w	0.14	LLC238	7mm	0.33	carriage on above £3 extra ea.
ZTX108	30v/.3w	0.14	LLC4827	7mm	0.33	<b>Misc.</b>
ZTX109	30v/.3w	0.14	LLC4828	7mm	0.33	FX1115 beads 10A.25
			CF510.7	ceramic	0.50	MW/LW ferrite rod ant 0.90
			BLR3107N	mpx	1.90	min. foil trimmers (see pi)
			BBR3132	6pole fm	2.25	22: 100k pots for tuning.45
						RFchokes: 1uH to 120mH

VAT is extra at 12½%, except where otherwise shown (\*8%). PP now 25p per order. Catalogue 45p (inc). Pse send A5 or larger SAE with enquiries. Price lists free with an SAE. Full range of components etc available to callers at our new easy-to-get-to premises.

**ambit INTERNATIONAL**

Number 2, Gresham Road, Brentwood, Essex. CM14 4HN  
 telephone (0277) 216029  
 Our new premises are only 200 yards from Brentwood station - with parking facilities outside the door !!

# SWL'S—YOU OWE YOUR RX A GOOD ANTENNA!

The World-famous JOYSTICK VFA (Variable Frequency Antenna) SYSTEMS continue to prove their worth in many amateur stations world-wide and in Government communication. Tunes continuously 0-5/30-00 MHz. and can be installed in any location. Comes in easily assembled form, carriage paid, 12½% VAT included. Growing testimonials from many users on our files.

SYSTEM 'A' £36-00  
 SYSTEM 'J' (improved 'Q') £42-60

## PARTRIDGE SUPER PACKAGES

Complete Radio Stations for any Location  
 All Packages feature the World Record Joystick Aerial (System 'A') with 8' feeder, all necessary cables, matching communication headphones. Delivered Securior our risk. ASSEMBLED IN SECONDS! BIG CASH SAVINGS!

PACKAGE No. 1 As above with R.300RX £210-55  
 SAVE £17-28!

PACKAGE No. 2 is offered with the FRG7 RX £193-11  
 SAVE £12-21!

PACKAGE No. 3 Here is a lower-price high-quality package, featuring the all-solid state SMC 73 Rx., with all the Partridge extras. SAVE £17-28! £154-86

RECEIVERS ONLY, inclusive delivery, etc.  
 R.300 £184-50 FRG7 £162-00 SMC73 £128-81

For further details, send 9p stamp. You can phone your Access or Barclaycard number, ring 0843 62535 (or 62839 after office hours).

Box 5, Partridge Electronics Ltd.

Partridge House, Prospect Road, Broadstairs CT10 1LD

G3CED

(Callers by appointment)

G3VFA

# TRAMPUS ELECTRONICS LTD



A SEMICONDUCTOR POWERHOUSE TRAMPUS ELECTRONICS LTD., 55-60 GROVE RD., WINDSOR, BERKS. SL4 1HS. (Trade, Export & retail.) Tel: Windsor (07535) 54825. Callers welcome Mon-Sat 9 a.m.-5 pm Fast Service. On Ex Stock product same day despatch normally. Quality Devices, Manufacturers Specifications, Lowest prices. Barclay Card & Access by post or telephone 25 minimum.  
 VAT: Add 8% to prices marked \*. Add 12½% VAT to all other prices. Post & Packing 20p U.K. Send CWO, except Gov. Depts. etc. Money back if not satisfied. Catalogue sale list free. Send SAE.

**IC's** All price each

555 DIL8 Timer	37p*
723 TO99 Reg.	47p*
723 DIL 14 pin	69p*
741 DIL 8 pin OP amp	25p*
741 DIL 14 or TO99	36p*
747 Dual 741	89p*
748 DIL 14 pin	29p*
748 DIL 14 W/AF	61p*
7805 Plastic or TO3	£1*
7812 or 15 Plastic	£1.50*
7813 or 78023	£1.69
8038 Sig. Gen.	£5*
A751224 Clock	£2.50*
LM340	50p*
LM301 DIL 14 pin	29p*
LM301 DIL 8 pin	59p*
LM309K TO3 5V	£1*
LM318 70V US	£2.25*
LM3504 2W AF	£1*
LM3900 Quad OPA	75p*
MC1310 Yes only	75p*
NE555 Timer	37p*
NE556 2 x 555	£1*
SN76611 & 601F	£1.25
TEA 810 W/AF	£1*
LEDS 1/2" dia.	11p*
Red no clip	15p*
2" Red & clip	29p*
Colour Leds	29p*
DISPLAYS (Red Led)	19p*
0-3" DIL704/2	65p*
0-3" DIL 707/2	65p*
0-3" DL747/2	£1*
TGS308 Gas Detector	£5*
399p Med/Short Tuner	£1*
Audible warning bleeper 12V 100mA	£1.49*
Dalc PCB Pen 2 tips	74p*
SRBP 6" x 4"	60p*
FEC	£2*
PCB etching kit	£2*


**TRANSISTORS**

BC107, 108 or 109 all	9p*
BC107B	15p*
BC108B or C	15p*
BC109B or C	15p*
BC147/8/9	25p*
BC167/8/9	10p*
BC177/8/9	20p*
BC193/3/4 or L	19p*
BC212/3/4 or L	14p*
BCY70/71/72	20p*
BD131 or 132 ea.	39p*
BFY50, 51 or 52	20p*
MJ2955 (PNP 3055)	£1.50*
MJE2955	£1.40*
MJE3055	55p*
ORP12	50p*
TIP 26, 30, 31, 32C	60p*
TIP41A or 42A	65p*
TIP41C or 42C	£1*
TIP2955	65p*
TIP3055	55p*
TIS43 UJT	30p*
2N2648 UJT	30p*
2N2904 ORS	30p*
2N2906 YG	15p*
2N3053	24p*
2N3055 115W	45p*
2N3442 120V 3055 £1*	50p*
2N3702/3/4/5/6	10p*
2N3704	19p*
2N3706 or 23e	19p*
2N3904/5/6	20p*
2N4547 FET	50p*
INS Bush sets ea.	10p*
Matching	Add 20p*
DIODES GA 31/91 5p	5p*
IN4148 & IN914 Silicon	4p*
IN4001 5p* IN4004 7p*	7p*
B2Y88 Zeners 400mV	10p*
Bridge: 1A 50V	25p*
6A	£1*

**FULL SPEC. PAKS**

Pak A: 10 x LEDs	£1*
Pak B: 4 x 741C	£1*
Pak C: 3 x 2N3055	£1*
Pak H: 6 x 2N3819e	£1*
Pak I: 6 x 2N 3819e	11*
Pak K: 4 x 1N914	£1*
Pak N: 25 x OA81/91	£1*
Pak M: 3 x 2 amp. PNP/NPN pairs 60 volt (total 6)	£1*
Pak W: 20x mixed 10V electrolytic 2-100uf	£1
More paks in free lists.	
<b>CAPACITORS:</b> Ceramic 5p Electrolytic 1v-100v 7p	
Heatinks: TO18/TO5	5p*
TO3	
Solder Dispenser 18 SWG	35p*
<b>SOLDERCON 100</b>	45p*
1000 £4*	
<b>DIL SOCKETS 8 or 14 or 16</b>	15p*
CMOS: Many stocked i.e.: 4001 or 2 23p 4008/10 59p* 4011 20p* 4049 or 89 23p*	
<b>SCR &amp; TRIACS:</b> ST2 25p* Brido 40p* C106A400V55p* 1A 400V 50p* 1A600V 69p*	
<b>TTL 7400N SERIES</b>	
7400 14p* 7485/86 10p*	
7401 8p* 7490 49p*	
7404 20p* 7491 50p*	
7408/9 10p* 7403/5 59p*	
7413 39p* 74107 20p*	
7417/20 29p* 74121 39p*	
7430 8p* 74123 39p*	
7440 15p* 74141 80p*	
7441 79p* 74157 50p*	
7447 84p* 74193 50p*	
7448 60p* 74194 50p*	
7470/72 29p* THIS	
7473/4 35p* AD FOR	
7475 40p* SPECIAL	
7476 30p* PRICES	
7478/2/3 10p* SHOWN	

M.J. HUGHES, MA, C.Eng., MIERE

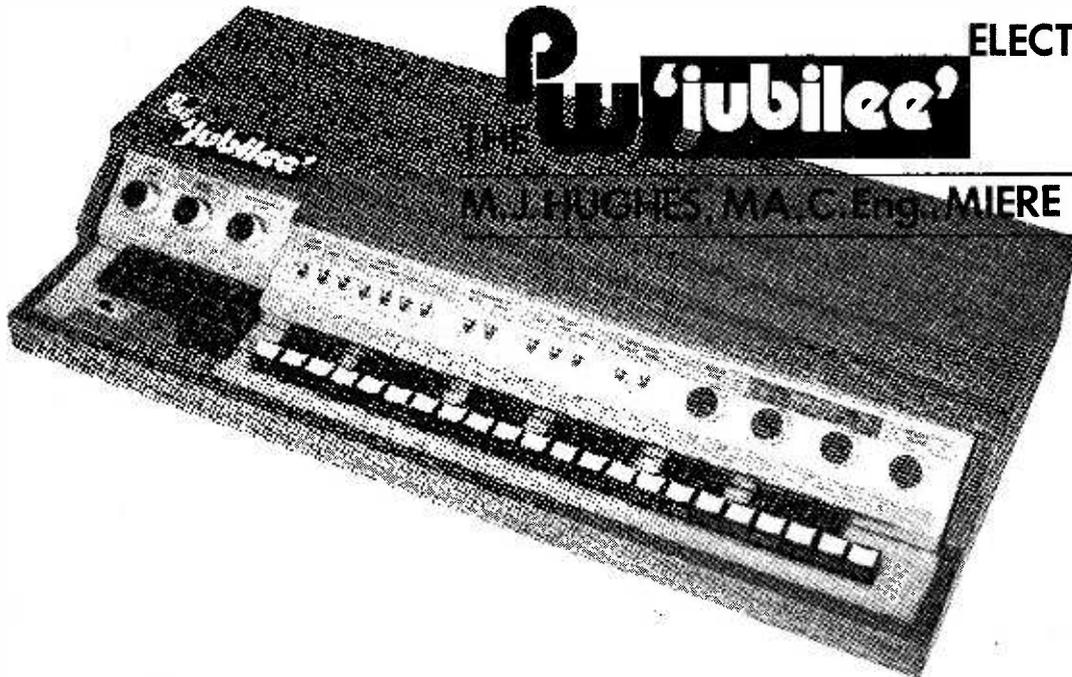

This part describes the assembly of the cabinet and off board interconnections for the calculator keyboard version of the instrument. The slight variations required for the conventional keyboard version will follow next month.

## Back panel wiring

In the prototype, the front and back panels were cut and folded out of 14 swg aluminium sheet. The rear panel is shown in Fig. 1. The large bracket at one end carries the mains transformer while the narrower flange running the full length takes self tapping screws to fasten the chassis into its cabinet. Four small brackets fix the printed circuit board into place on the back panel. Their height is critical to the final assembly of the chassis into its cabinet; read on before starting any mechanical work! These brackets should be fixed to the back panel so as to register exactly with the centres of the fixing holes on the PCB. Drill these for self tapping screws. At the same time mark and drill clearance holes at the front of the transformer platform for the mains transformer mounting bolts, which also secure the PCB at the front of the cut out.

When fitting the voltage regulators, make allowance for any variation from the specified devices. The prototype used a TO-3 encapsulation for IC21. No insulating kit is needed for this as its can should be in electrical contact with the panel. Bolt a solder tag under one of its fixing screws.

When using a plastic version, the same comments apply. The same cannot be said for IC22 (the  $-12V$  regulator). It is *most important* that a mica washer and insulating bush are used when fixing this.

The mains input cable should be clamped to the back panel and the earth wire connected to a solder tag mounted under the clamp. The neutral connection should go straight to the transformer and the live should, at this stage, be left long enough to reach the front left hand corner of the PCB—where the mains switch will be mounted. Connect the side terminal of the fuse holder to the other input of the mains transformer and then link the two secondary pairs to their respective pins of the PCB. Refer to Fig. 1.

Solder up all the chassis tag connections. All must go to the same solder tag under IC21. This cannot be stressed too highly otherwise nasty earth loop problems and instability are likely! Connections to this solder tag come from the PCB pins located as follows:


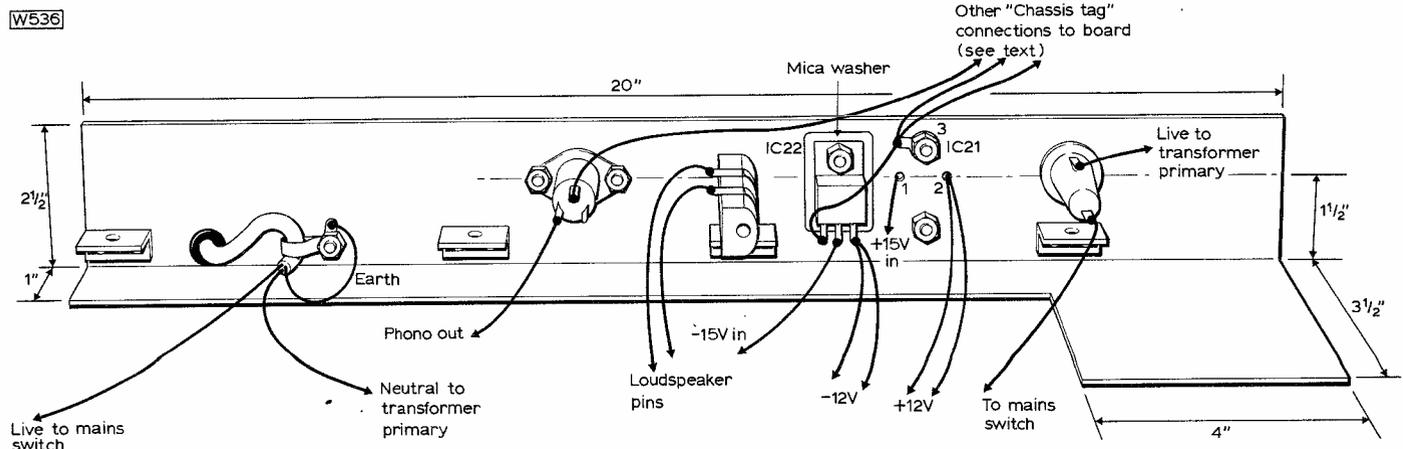


Fig. 1: Back panel assembly. The dimensions are for guidance only.

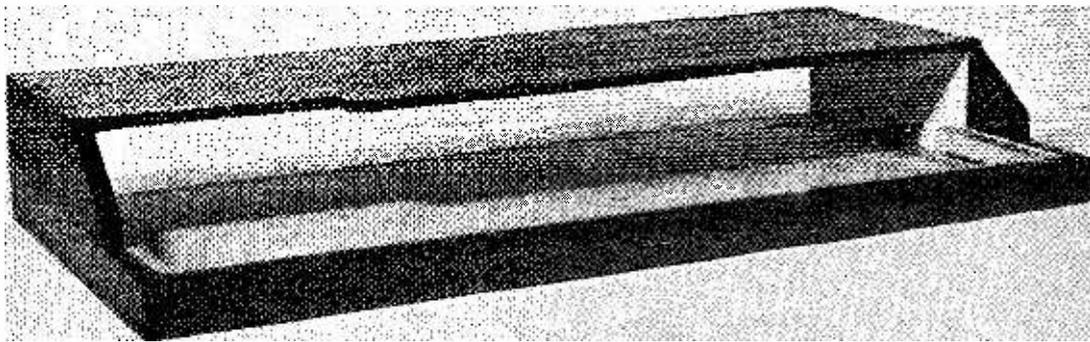



The photograph shows the plywood sleeve cabinet as used for the prototype calculator keyboard version. Note that the front of the cabinet has a pair of runners to give extra support to the keyboard section of the printed circuit board.

Start by cutting out the two end plates—these set the overall height and the depth of the step together with the angle of the bends. See Fig. 2 for details.

The main panel is cut and folded out of one piece. Use a fine saw and cut a slot to allow for the different positions of the bend at the 'dog's leg'. Using the smaller end plate as a template, fold the front panel for the accompaniment end of the keyboard. Start with the bottom flange then draw the material from the vice or clamp to put in the small angle bends at the top of the vertical and sloping sections. If you need to extend the slot this can be done quite easily. When folded, the end plate should fit *under* the top flange of the panel and the bottom flange of the end plate should be flush with that of the main panel.

Move to the other end of the work piece and put in the bends for the melody section of the keyboard; this time use the larger end plate as a template. Try to ensure that the sloping panel is parallel over both sections and then use a liberal quantity of Araldite to glue the end plates into position. Run a fillet of the glue under the inside edges where the sloping and vertical parts of the panel butt on to the end plates. Cut a filling piece and glue into the gap left between the two parts of the front panel. Use plenty of glue to fill any gaps or irregularities in the fit.

When the glue is rock hard—leave for at least 24 hours—mark and drill the front panel for the potentiometers and switches. Marry the panel to the PCB so that the vertical edges are just clear of the push button keys and mark positions for fixing holes along the underside flange by spotting through the PCB in the six marked locations. Self tapping screws should be used; drill the holes undersize.

At the left hand end of the panel (accompaniment end) drill a hole for a nut and bolt through the PCB and into the flange under the end piece. This hole should go through the copper area which is at earth (chassis) potential. A solder tag should eventually be fixed on this screw and a bonding connection made to the front panel with a wire soldered to the body of one of the potentiometers. **Note**—it is no good relying on connection through the end piece because the Araldite will have acted as an insulator! Drill a similar hole through the PCB and end piece at the melody end but keep the position clear of any of the PCB wiring. Fix the completed front panel to the PCB

—forming threads for the self tapping screws, etc—before progressing further. Make sure that all the push buttons will operate without fouling anything.

### Front panel wiring

Remove the front panel and finish it off with a rub down and give it several coats of hard polyurethane based silver lacquer. Fix all the controls in place and connect them with flying leads to their respective board pins (see Fig. 3 for details). This operation is best done with the front panel tilted forward over the push buttons. Use screened leads for connections to VR7 (Melody Volume), VR13 (Accompaniment Volume), VR17 (Drums Volume) S3, 4 and 5 (Melody Voicing) and S6 and 7 (Accompaniment Voicing). Lightweight stereo screened pairs help cut down the number of separate leads required. Always use the earthing pin on the PCB associated with the respective 'live' terminals for each potentiometer or group of switches. **Do not** link all the earth connections on the front panel controls together or you will get major earth loop problems!

Note that the switches should be orientated as follows: S1, 2, 3, 4, 5, 6 and 7 should normally be closed in the 'Up' condition; S8 to S13 inclusive should normally be open in the 'Up' condition. When S14 a and b is 'Up'—in the Vamp OFF condition—the poles should be connected to +12V at the positive end of C17.

Screw the front panel into place—not forgetting the solder tag and bonding link going from the left hand end plate to the body of one of the potentiometers. Finally, mount the mains slide switch in front of the accompaniment keys. A small LED may be fitted next to the switch connected via a 470 ohm resistor across the -12V supply and ground. The cathode should go to the more negative voltage. Connect the live mains input lead to the main switch and run another wire from the latter to the central terminal of the fuse holder. The organ is now complete.

---

**Next month—the variations required for conventional keyboard instruments, setting up the preset controls and fault tracing.**

---

# TRAFFIC LIGHT CONTROLLER



## Outline

This design uses TTL ICs to simulate the appearance of traffic lights. The "lights" consist of three LEDs which go on and off in the sequence followed by actual traffic lights. Applications of this circuit might be found in model town and railway layouts, or (with a little modification) as a yes/no decision maker. The sequence displayed must be: red, red/yellow, green, yellow, and back to red again. In addition the red or green periods (which are equal) must be longer than the yellow or red/yellow periods (which are also equal). The circuit follows this succession in a continuous cycle.

## Circuit Description

The circuit consists of four distinct sections; these are the oscillator, the counter, the decoder and the display.


The oscillator is a SN7413, dual four input nand Schmitt which, together with R1 and C1, generates a series of pulses. The frequency is set by C1 (1000 $\mu$ F) which gives reasonable timing for a model layout. These pulses are fed to a SN7490 decade counter, which advances by one whenever an input pulse is detected. When it reaches nine, it resets to

zero; in this way the continuous cycle is produced. The count appears in binary at pins 12, 9, 8, 11 (1, 2, 4, 8 respectively). This count is taken to IC3, which is a SN7441A binary to decimal decoder. It has ten output pins which are normally high, but which go low in conjunction with the binary input. For example, when binary 0101 appears at the input pins, output pin 14 (associated with decimal 5) goes low. Since the decoder input cycles from zero to nine, the decoder outputs will do the same. These outputs are in four groups, each controlling a particular display function.

## The display

This consists of three LEDs, arranged one above the other as in conventional traffic lights. The red LED is driven from counts zero, one, two and three; the

Fig. 1: The main circuit diagram.

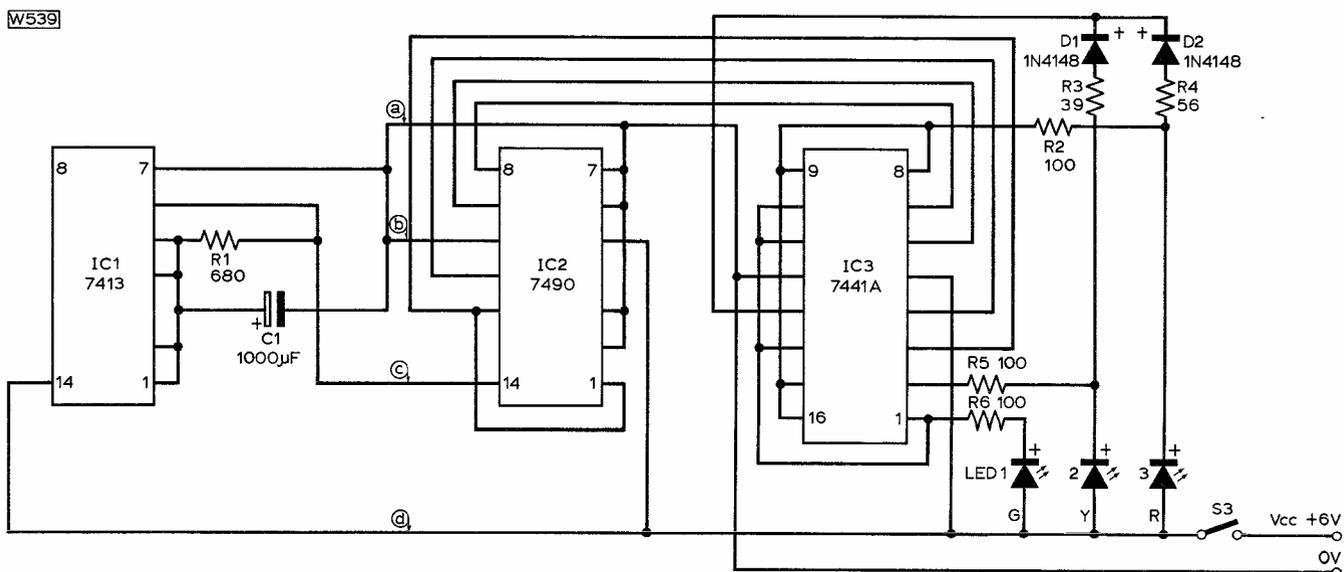

green LED from counts five, six, seven and eight; and the yellow LED from count nine. Count four drives both the red and yellow LEDs, via diodes D1 and D2. These prevent the yellow LED lighting during counts zero, one, two and three, and the red LED lighting during count nine.

## ★ components

Resistors	
R1	680Ω
R2	100Ω
R3	39Ω
R4	56Ω
R5	100Ω
R6	100Ω
R7	10kΩ
Capacitors	
C1	1000μF, 25V
C2	10μF, 6V
C3	100μF, 6V
Semiconductors	
IC1	SN7413
IC2	SN7490
IC3	SN7411A
Tr1	BC109C
D1 and D2	general purpose silicon
LED 1	Green, LED 2 Yellow, LED 3 Red
Miscellaneous	
Relay 14 pin DIL reed type (Doram), Veroboard 0.1" matrix 50mm x 45mm, S1 2 pole, 2 way. S2 push-to-make switch, S3 Single pole, one-way, 6V batteries, Case.	

## Construction

The unit is constructed on a piece of 0.1in Veroboard which measures 50 x 45mm. Layout details, including modifications for the decision maker, are shown in Fig. 3

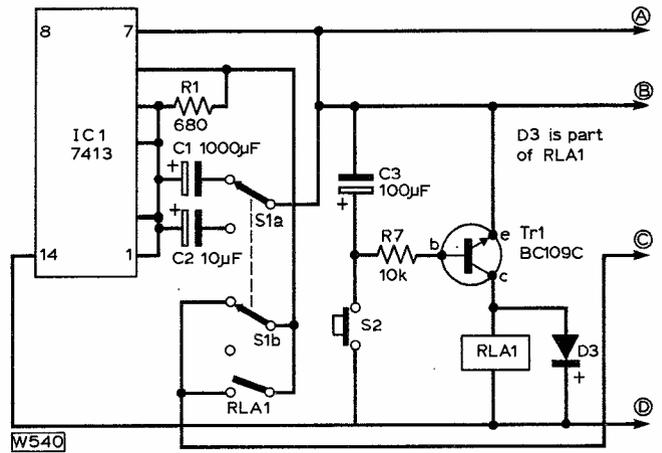


Fig. 2: Modifications around IC1 for use in "random" mode.

## Modifications for Decision Maker

These modifications, detailed in Fig. 2, allow the circuit to be turned into a form of "coin tosser". When switched in C2 determines the oscillator frequency, and sets it much faster than C1. The input to the 7490 is also disconnected from the oscillator, but is reconnected when the relay (a 14-pin DIL reed type) is energised. The relay is operated by Tr1, which has a delay circuit C3/R7. When S2 is pushed, C3 charges to the supply potential and holds Tr1 on. As C3 slowly discharges through R7 and Tr1 base, it provides a delay of a few seconds, holding the relay on after S2 has been released. When RLA1 de-energises, the counter is again disconnected from the oscillator, and the display freezes in one state. When the switching speed of the display and the time delay on RLA1 are combined, it becomes impossible to predict just how the display will stop—in other words, the outcome is random. Should the display halt at a state which includes a yellow light, S2 may be pushed again.

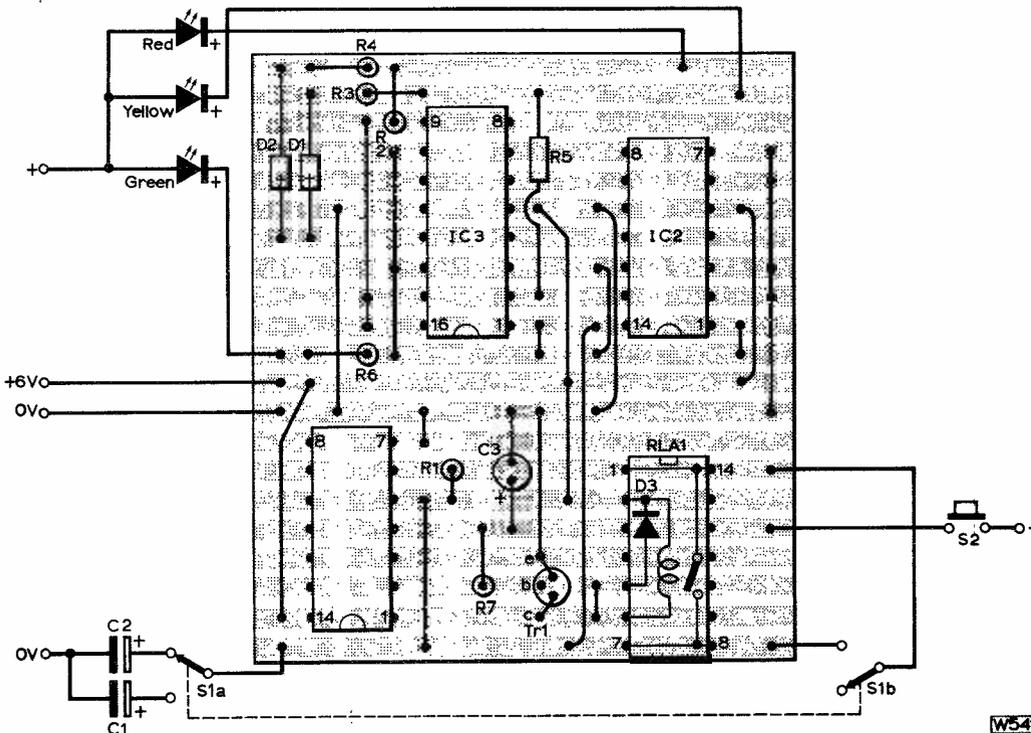


Fig. 3: General Veroboard layout of composite unit.

# HOT LINES

## A REVIEW OF RECENT DEVELOPMENTS

In general, the author does not have any more information on products than appears in the article.

### Loud mouthed chips

If noise annoys your neighbours, they will not be very pleased to hear about one of the latest IC chips to arrive on the US market. It is a 28-pin device which has the sole purpose in life of generating noises! But it isn't quite so strange as might first appear. The manufacturers are aiming the new chip mainly at the toy and games market and they've taken the job very seriously.

The chip is a mixture of bipolar logic circuitry and injection logic (I<sup>2</sup>L). Crammed into its tiny area, the device has noise oscillator, noise generator, noise filter, SLF (super low frequency) oscillator, VCO (voltage controlled oscillator), mixer, system-enable logic section, one-shot circuitry, envelope and generair modulator, attack/delay logic, and an amplifier. In very large quantities the device will sell for just one dollar.

The beauty of the device is that it only requires external resistors and capacitors to programme virtually any desired sound. For example it would be possible to have a sound like a submarine engine, then the throbbing of a heavy bomber aircraft, the screech of bombs falling followed by the sound of an explosion. The latter sound is aided by the one-shot oscillator in the device. This caters for sounds which last for less than two seconds, whereas other sections of the chip concentrate on allowing continuous sounds like sirens etc. The user may provide switching logic to switch in different sets of components. However, the chip manufacturers are rumoured to be currently working on a complementary chip which is designed to programme this device giving a series of several "standard" sounds.

The chip is not available in the UK, but readers might care to toy with some ideas for sounds they'd like to produce as and when it does become available. Do I detect someone saying "Hear hear"?

### Where there's smoke

Some time back a sensor was launched onto the market which detected smoke and chemical fumes. Various electronics journals subse-

quently published circuitry using these sensors. For those interested in this area of electronics — great news brothers.

A British company has manufactured a chip for use with ionization smoke alarms. The device replaces some 30 discrete components. The magic number you're looking for is MEM4962; a single chip LSI (large scale integration) package which harbours an FET input, detector, voltage comparator, oscillator, trigger, horn driver, and CMOS output stage; in fact, just about all the circuitry you need to make a sensitive electronic nose to detect combustion—just add the sensor and alarm device. Please note; manufacturers very seldom if ever supply direct to the public.

### Under water warmth

Microwave ovens are gaining popularity. Their ability to cook food in very short times and using minimal power are plus factors. The latest application of microwave heating is that of "cooking" divers while they plod happily round the sea bed. This work is currently going on at the University of Newcastle upon Tyne.

The Newcastle "chefs" viewed current methods of keeping divers warm at great depths with no real enthusiasm. One method relies on heating gas near the diver's suit. Another approach uses energy transmission which involves very heavy electrical currents and much copper connecting material.

Workers at Newcastle use a horn antenna fed at 8GHz with some 3kW of power. This power is transmitted down the diver's air hose which has a high dielectric material lining. The air is heated safely and transferred to the diver.

Ingenious though this may be, I don't think there's any real substitute for a good coal fire!

### PW on a disc

When the laser was first publicised it was hailed as a solution in search of a problem. But with the passing of time, this has changed. A new video disc storage system has appeared

which employs a laser beam. A disc of thin, transparent plastic, about the size of an LP record, has one side coated with a very fine layer of metal.

The recording tracks are made by burning minute holes in this metallized surface with a laser beam. The holes are typically a bare one micrometre in diameter.

In this way, the manufacturers are able to store some 18,000 separate pictures. Any individual picture may be called up in just one second. The system has various applications varying from storage of video signals, to the compact storing and playback of things like photographs for police work.

Just think, you might one day buy a whole year's *Practical Wireless* on a single LP.

### Out for the count

Frequency counters have come a long way over the years. Many Hams will smile wistfully at the mention of a BC221 with its little dial and a set of interpolation figures to enable the user to work out what the frequency was.

A newcomer to the frequency measurement range is the FC600A. This beautiful little beastly can be held on the palm of your hand. It gives an eight digit digital readout of frequency from 6Hz to 600MHz. The weight is only 1½lbs.

The counter oscillator has an ageing rate of just 3ppm (three parts per million) per year and is guaranteed accurate to within 5ppm over its operating temperature range of 0°C to +55°C. And it's economical to run, drawing only 300mA from a 12V supply.

Just in case you want one the cost is around 595 dollars (about £350) and the size is 5½ x 3½ x 1½in.; about the size of a well stocked wallet.

A stylized, cursive signature logo for 'Ginsberg' in black ink.


NEXT MONTH IN...

# practical WIRELESS

ON SALE DEC. 2ND.
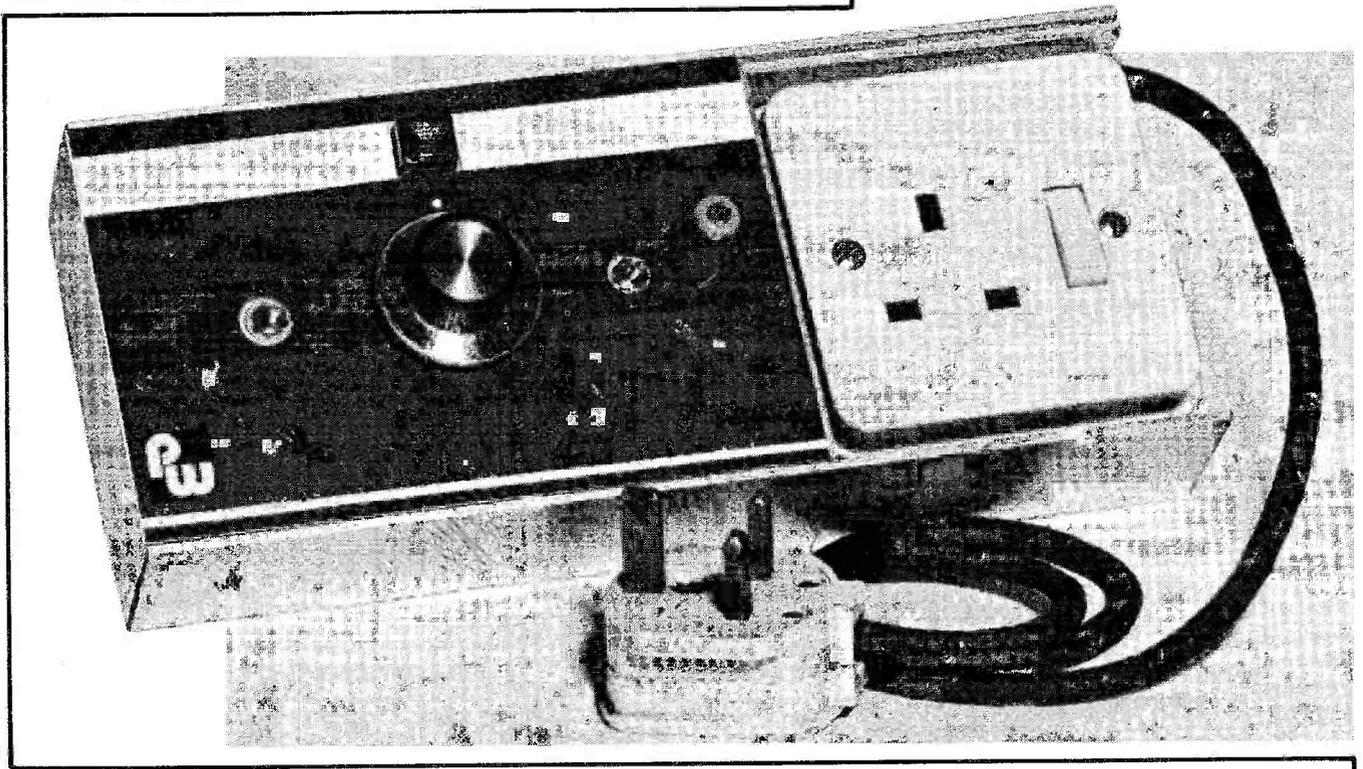
## **PROPORTIONAL POWER CONTROLLER**

Earlier methods of room temperature control fade into technical obscurity as our Proportional Power Controller leaps into the future! Using zero voltage switching technique, the unit provides interference-free temperature control of resistive loads (such as bar type electric fires) in the convenient range 40° F to 80° F.



### plus **Aerial Performance Test Set**

Constructing aerials from a book and taking their radiation patterns for granted is one thing. Testing model aerials, or even full-sized ones, and plotting their characteristics is something else. Fred Judd G2BCX, inventor of the very popular 'ZL Special' aerial, shows how to tackle the problem scientifically.

**&**

### **HF Direct Conversion Receiver**

This ultra simple direct conversion short wave receiver offers a performance comparable to a £200 double conversion superhet. Intended for SSB and CW, the selectivity is controlled entirely by the AF passband—this makes alignment and operation easy. It uses a dual gate FET for optimum noise performance and a balanced mixer for good AM and spike noise rejection.

# Laboratory Power U

When building any electronic equipment, some form of power supply is required for testing and experimental purposes, even though the equipment power supply, in its final form, may be batteries or even a purpose-built mains powered unit.

The ability to vary the supply voltage, to simulate the effect of a failing battery for example, is a desirable feature when testing certain equipment. Many circuits require bipolar supplies (dual rail) while a fixed +5V for TTL is a definite asset. To anyone who has struggled to test a new circuit with partly discharged batteries or some hairy hook-up to give 5 volts for the logic, this Lab Power Supply will certainly take some of the exasperation out of experimentation.



## Description

The Lab Power Supply provides three individual power supplies: +5V 0-400mA for TTL, 0 to +15V 0-100mA, 0 to -15V 0-100mA for op. amps and general transistor circuitry.

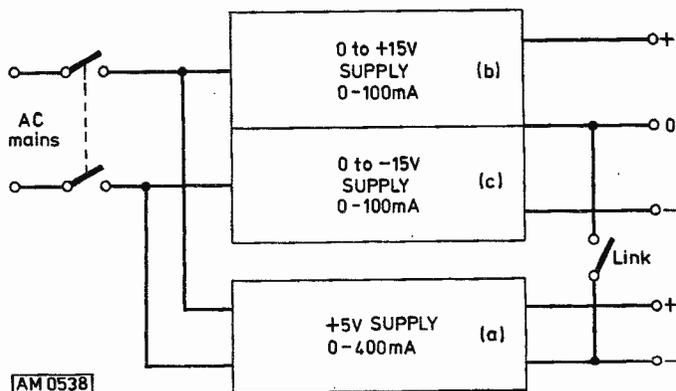


Fig. 1: Block diagram.

The +5V is fully floating while the bipolar supply has a common zero volt connection as shown in Fig. 1. This arrangement provides a fixed supply for TTL and a fully variable supply which may provide up to 30V at 100mA, with the supplies in series, or 0 to +15V and 0 to -15V with a common 0V connection.


In conventional usage, the 0V output of the 5V TTL supply and the centre 0V of the dual supply would be joined together. To do this, a link switch is provided to join or 'common' the 0V connections. This switch may be set to the un-linked position when full isolation of the supplies is required.


## Circuit

The full circuit diagram is shown in Fig. 2. The 5V supply is shown in the lower part of Fig. 2 and comprises a mains transformer T2, full-wave bridge rectifier BR2, smoothing capacitor C5 and integrated circuit regulator IC3. Current and voltage metering is provided by R19-22 and R23 respectively. These are
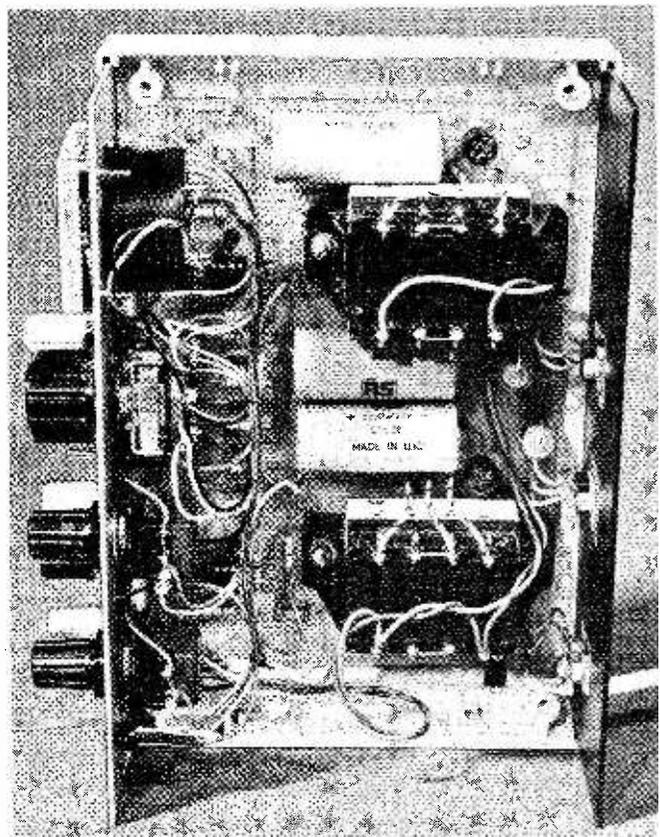
## J. THORNTON-LAWRENCE GW3JGA

connected to the meter by S3. The rather unusual resistor arrangement for monitoring current avoids the difficulty of making up a low resistance shunt for the meter. The recommended resistors for R19-21 are 2% thick film types and for R22, 2% metal oxide, giving a worst case error of about 7%.



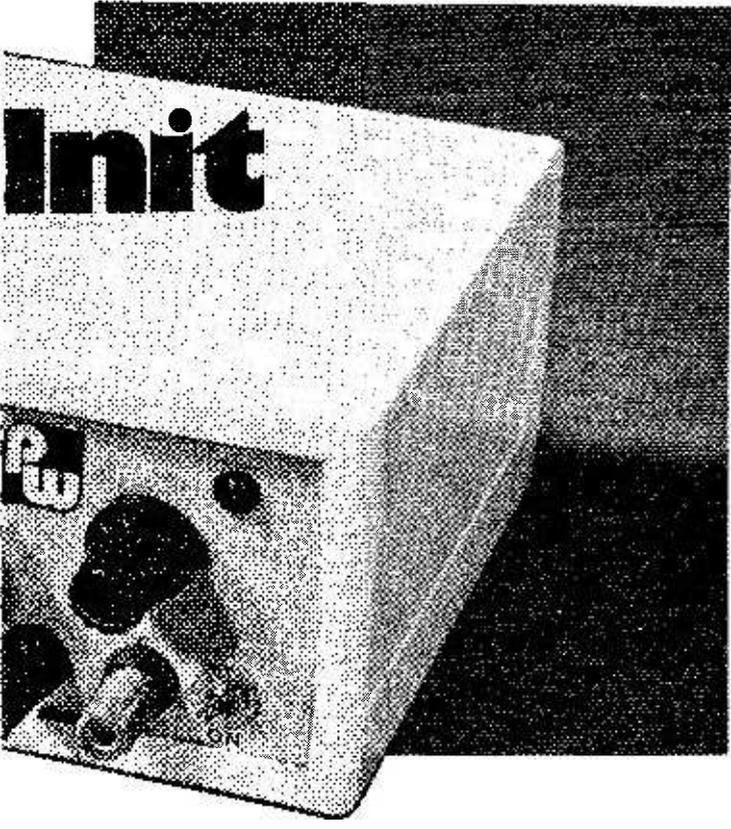

For voltage monitoring, the meter is switched in series with R23, giving 20V full scale deflection.

In the variable supplies, the mains transformer T1, bridge rectifier BR1, and smoothing capacitors C1 and C2 generate a dual 20V supply line. From these rails, regulated lines of +10V, +5V, -5V and -10V are provided by corresponding Zener diodes D1, D2, D3 and D4. These voltages are fed to various parts of the circuit.

### Variable regulator circuit

The basic regulator circuit is shown in Fig. 3. It consists of a 741 operational amplifier used as a summing amplifier and a power transistor, Tr1, connected as an emitter follower. The output from the emitter follower is fed back to the inverting input of the 741 and so provides negative feedback. This causes the output of the emitter follower to maintain the voltage at the inverting input equal to the non-inverting input, i.e. at zero volts.

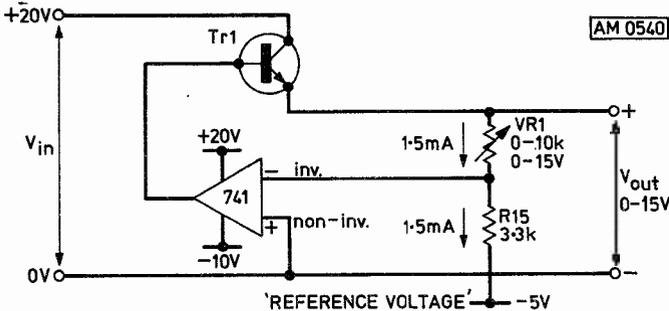


Fig. 3: The basic schematic of the variable voltage section. Fig. 2, the complete circuit diagram, is shown on page 589.

A negative current of 1.5mA is set up through R15 by connecting the bottom end to -5V. An equal but opposite polarity current comes from TR1 emitter (the output terminal) through VR1 to cancel out this

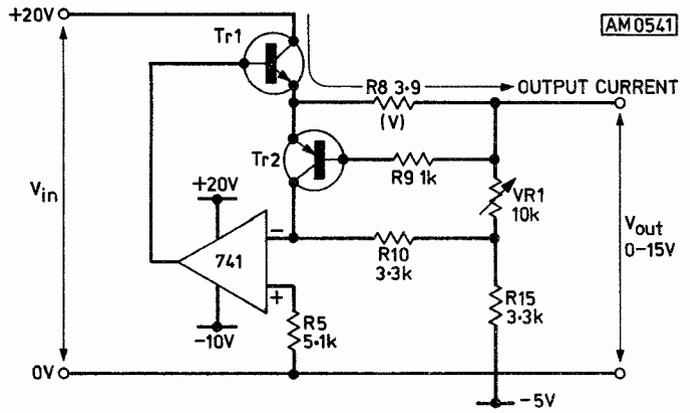


Fig. 4: The current limiting circuitry.

negative current thus maintaining the 'summing junction' at 0V. With VR1 set at zero resistance, +1.5mA will be provided with the output terminal virtually at 0V; with VR1 set to maximum (10k $\Omega$ ), Tr1 emitter and the output will now move to +15V to maintain +1.5mA through VR1. Therefore, at any setting of VR1 the output voltage will be equal to the voltage drop across VR1 produced by 1.5mA through it.

### ★ components

#### Resistors

R1 680 $\Omega$ $\frac{1}{2}$ W	R13 330 $\Omega$ 2%
R2 680 $\Omega$ $\frac{1}{2}$ W	R14 3.9 $\Omega$ 2% $\frac{1}{2}$ W thick film
R3 330 $\Omega$	R15 3.3k $\Omega$
R4 680 $\Omega$	R16 3.3k $\Omega$
R5 5.1k $\Omega$	R17 20k $\Omega$ 2%
R6 5.1k $\Omega$	R18 20k $\Omega$ 2%
R7 330 $\Omega$ 2%	R19 3.9 $\Omega$ 2% $\frac{1}{2}$ W thick film
R8 3.9 $\Omega$ 2% $\frac{1}{2}$ W thick film	R20 3.9 $\Omega$ 2% $\frac{1}{2}$ W thick film
R9 1k $\Omega$	R21 3.9 $\Omega$ 2% $\frac{1}{2}$ W thick film
R10 3.3k $\Omega$	R22 1.2k $\Omega$ 2%
R11 3.3k $\Omega$	R23 20k $\Omega$ 2%
R12 1k $\Omega$	

All  $\frac{1}{2}$ W 5% carbon film, except where stated.

VR1 10k $\Omega$  1W wire wound VR2 10k $\Omega$  1W wire wound

#### Capacitors

C1 2200 $\mu$ F 25V
C2 2200 $\mu$ F 25V
C3 10 $\mu$ F 25V
C4 10 $\mu$ F 25V
C5 2200 $\mu$ F 25V
C6 220nF
C7 470nF

#### Semiconductors

Tr1 TIP31	IC1 741
Tr2 BC214	IC2 741
Tr3 BC184	IC3 7805
Tr4 TIP32	BR1 1A type
	BR2 1A type

#### Switches

S1 DPDT
S2 SPST
S3 2 pole 6 way

#### Transformers

T1 Primary 240V, secondary two windings each of 15V 0.2A
T2 Primary 240V, secondary two windings each of 4.5V 0.6A

#### Miscellaneous

PC (from Readers PCB service, if required), Meter 0.1 mA, terminals, knobs, mains lead, hardware, cabinet (21 x 8 x 14cms).

AM 0539

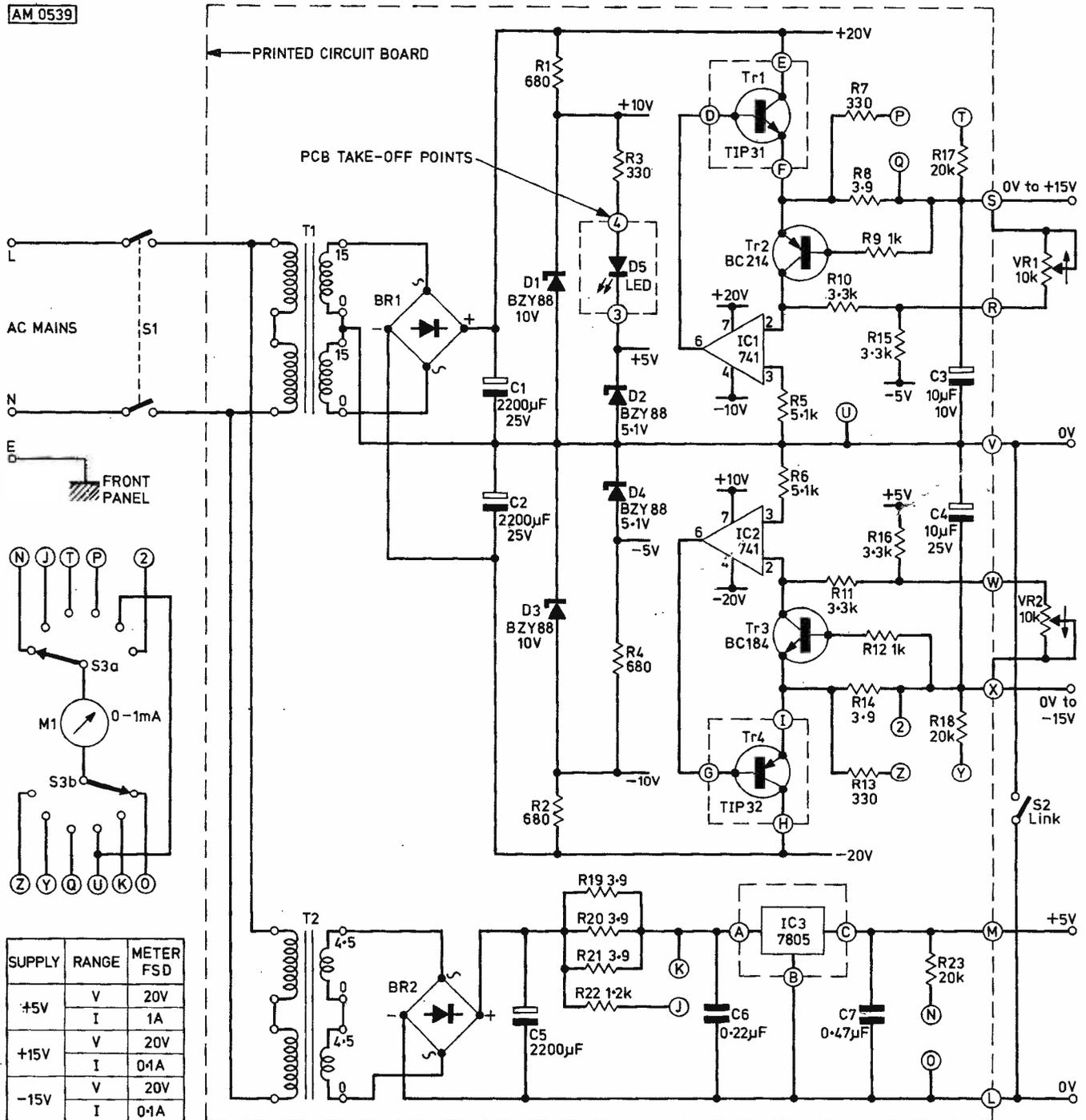


Fig. 2: The complete schematic. The mains transformer primaries are not connected to the printed circuit board. As such, they are not indicated by reference letters which correspond with Fig. 6, the PCB overlay.

Rotation of VR1 produces a linearly variable output voltage of 0-15V.

When a current is drawn from the output terminal, this tends to reduce the output voltage slightly and this negative change is at once apparent at the 'summing junction' and so produces a positive change at the output and restores the output voltage to the correct value again, or almost so. This amplified correction gives the characteristically low output impedance that can be obtained from electronic voltage regulator circuits.

## Regulator with current limiting

The circuit with the additional components is shown in Fig. 4. A current sampling resistor, R8, monitors the load current. This resistor is between the emitter and base of Tr2 and when the load current produces a sufficient voltage drop across R8, Tr2 turns on causing positive current to flow from the collector of Tr2 to the 'summing junction'. This results in a negative polarity change in the output, ensuring that the output current does not rise to a dangerously high value. Tr2 will turn on when the emitter-base voltage (V) reaches about 0.55V:

$$I_{\max} = \frac{0.55V}{3.9\Omega} = 140\text{mA approx.}$$

The resistor R8 performs a dual purpose in that with R7 (see Fig. 2) it provides a meter shunt for monitoring output current, giving a full scale deflec-

tion of the panel meter for 100mA. The shunting arrangement is similar to the +5V supply circuit previously described.

R9 is included in the base circuit of Tr2 to limit the base current to a safe value and R5 is included in the non-inverting input of the 741 to balance the small voltage off-sets produced by the input currents of the device. C3 is fitted across the output terminals to provide a low output impedance at medium and high frequencies. The negative supply is a mirror image of the positive supply.

The panel meter has a basic sensitivity of 1mA full scale deflection and is switched to various parts of the circuit for output voltage and current measurements.

## Construction

The prototype was housed in a Verobox. The printed circuit board carrying all the components was fixed to tapped pillars provided in the base of the Verobox. The front and rear panels fit into slots in the base and cover.

The printed circuit board layout is given in Fig. 5. The overlay, Fig. 6, shows numbered interconnection points where the wiring from the front and rear panels is connected. These points are also identified on the circuit diagram shown in Fig. 2. The only connections not identified in this way, are those to the mains transformer primaries, as they do not connect with the PCB. The primaries of the transformers are fed from S1, the double-pole on/off switch.



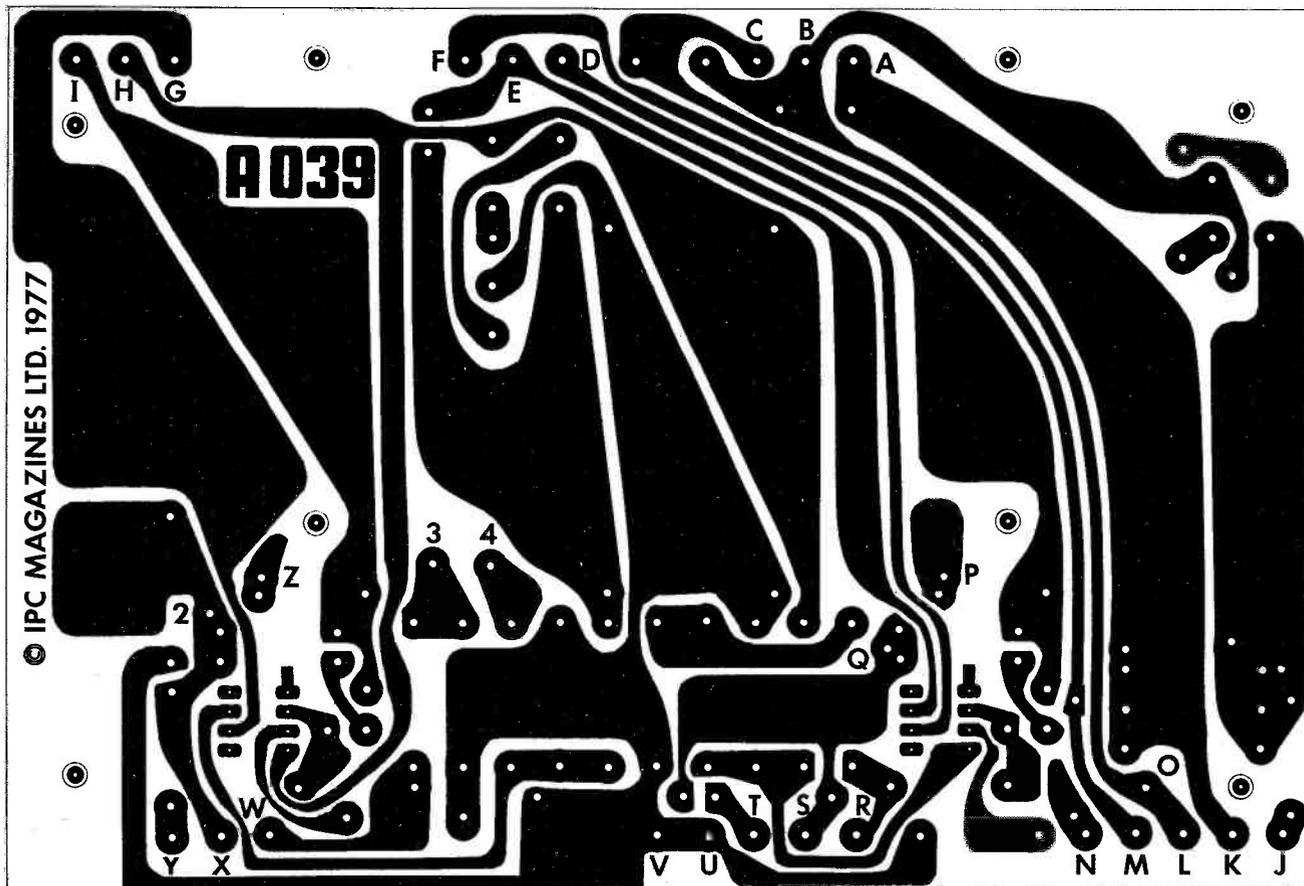


Fig. 5: The PCB shown copper side. The scale factor is one; ready made boards may be obtained from the PW Readers' PCB service. Details page 593.  
Fig. 6: Component overlay. This drawing is shown on page 591 (overleaf). The reference letters refer to the circuit diagram.

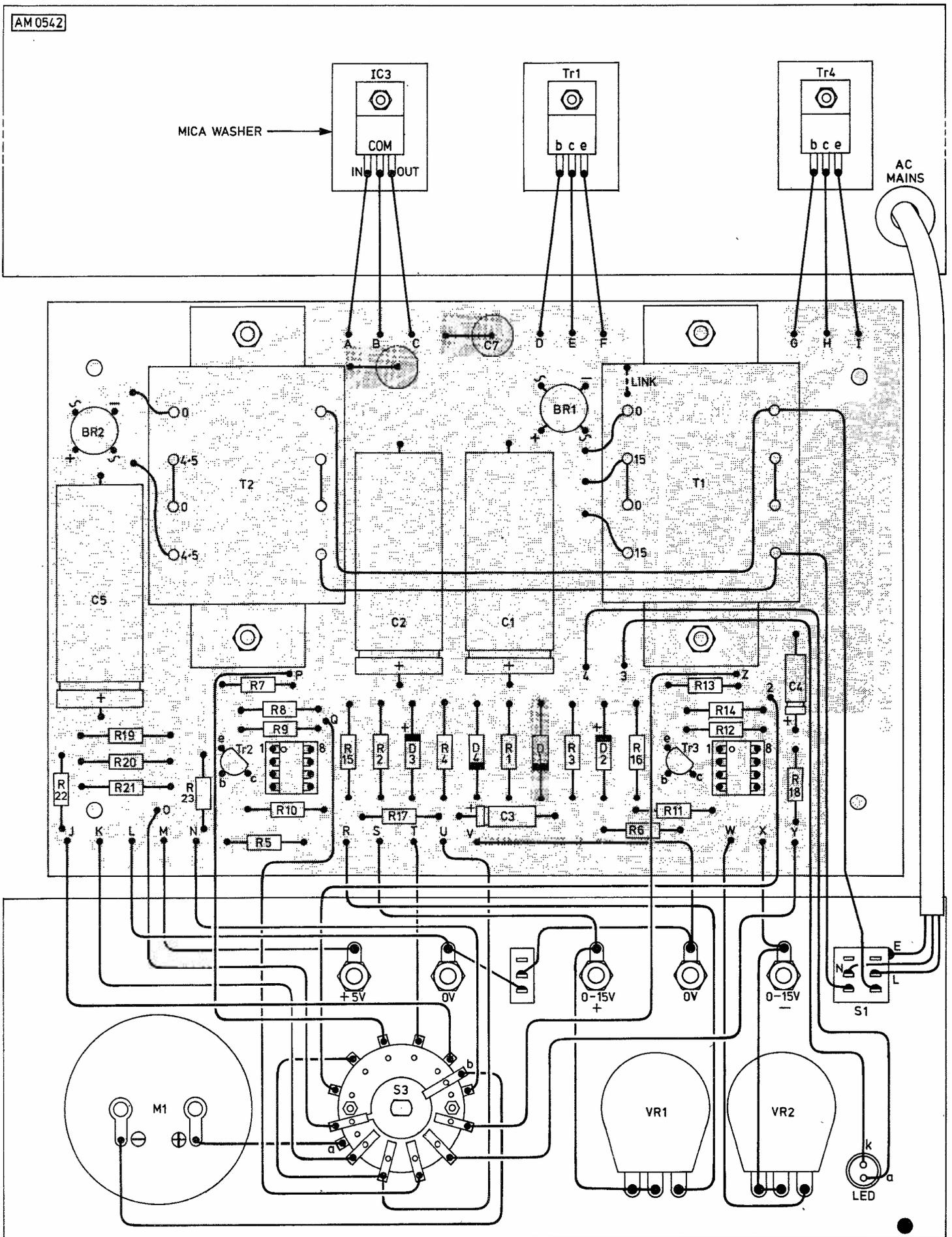

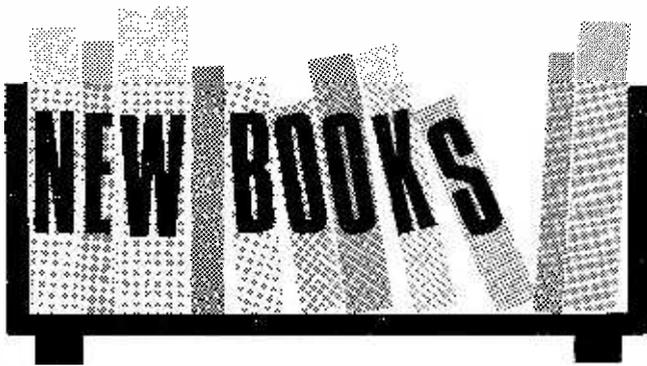

**ELECTRONICS FAULT DIAGNOSIS**

by Ian R. Sinclair

Published by Fountain Press, Argus Books Ltd., 14 St. James Road, Watford, Herts. 108 pages £2.75

This book is unusual in several respects: it maintains a 100% educational aspect in the classic questions and answers textbook style while being *informative* at the same time. The author has managed to define closely the ability and technical understanding of his readership thus obviating the boring preliminaries of very basic theory; this book is not for beginners.

The content comprises about 50 or 60 circuits, each complete and functional, with accompanying descriptions of normal circuit operation. For each, the author provides tables of voltage readings, as well as 'scope diagrams where necessary, taken from critical points in the circuit. While one set of readings will correspond to normal circuit operation, others have been taken with various hypothetical fault conditions. The reader is left to work out which is the correct set of figures, given several fixed points to work from, and which sets correspond to various component failures. The format is certainly educational and occasionally mind bending—even for the more gifted amongst us. Answers of course are at the back.

What the book amounts to is a collection of technical puzzles capable of stretching professionals and amateurs alike. More surprising, it works at several levels of understanding; this mostly results from the author's policy of including the easy circuit examples first with more difficult ones further on. Interest is maintained by the nature of the circuits given. He has carefully avoided the textbook trap of including oft-quoted, boring circuits such as astables and the like. They are there but in heavily disguised form within larger circuit building blocks. One gets the feeling that the author is as happy with a soldering iron as he is with a typewriter. Indeed, most seem very efficient and would find ready application in many areas of amateur electronics—which is far more than can be said about most circuits published in text books.

Frank Ogden

**A PRACTICAL INTRODUCTION TO DIGITAL ICs**

By D.W. Easterling

Published by Bernards Ltd., The Grampians, Shepherds Bush Road, London, W6 7NF.

76 pages 95p

The title 'A Practical Introduction to Digital ICs' over-describes the content of this 76 page volume. More precisely, the latter deals with practical applications (sic) of six members of the 74 series. These applications are mostly adjuncts to a digital timer described in the penultimate chapter. It has to be said that the overall impression is one of confusion, inaccuracy and lack of aspect.

Throughout the book, the author seems unable to decide  
*continued on page 606*

**READERS PCB SERVICE**

To:- READERS PCB SERVICES LTD,  
 PO BOX 11, WORKSOP, NOTTS

Please supply PCB/s as indicated by tick/s in box/es.....

Issue	Project	Ref	Price	P/P
Dec 75	Sound-To-Light Display	DN0798	1.15+12	<input type="checkbox"/>
Dec 75	Disco System, Amp. (2 req'd) each	AM0421	4.40+22	<input type="checkbox"/>
Dec 75	Disco System, Light Modulator	AM0423	3.50+22	<input type="checkbox"/>
Mar 76	CMOS Crystal Calibrator	AM0438	1.19+12	<input type="checkbox"/>
Apr 76	Wobbulator	AM0443	1.08+12	<input type="checkbox"/>
Apr 76	Auto. Slide Synchroniser	AM0441	2.33+15	<input type="checkbox"/>
June 76	Dig. Freq. Meter (set of 5) A015 and 4x A004	A015 and A004	3.17+15	<input type="checkbox"/>
July 76	Transistor Tester	A002	3.08+18	<input type="checkbox"/>
July 76	Disco Preamplifier	A003	0.65+12	<input type="checkbox"/>
Aug 76	Cassette Player Power Supply	A001	0.65+12	<input type="checkbox"/>
Sep 76	Capacitance Meter	A009	2.59+14	<input type="checkbox"/>
Oct 76	Digital Car Clock (set)	A011/012/013	2.58+12	<input type="checkbox"/>
Oct 76	Interwipe	DN8JM	0.80+12	<input type="checkbox"/>
Oct 76	Video-Writer (set)	D002/3/4/6 A007	21.44+50	<input type="checkbox"/>
Oct 76	Hazard Flasher	D005	0.76+12	<input type="checkbox"/>
Nov 76	Low Level Battery Indicator	A016	0.40+12	<input type="checkbox"/>
Nov 76	Electronic Thermostat	A017	1.30+12	<input type="checkbox"/>
Nov 76	Cirtest Probe	A018	0.48+12	<input type="checkbox"/>
Nov 76	Burglar Alarm	A019	0.50+12	<input type="checkbox"/>
Dec 76	Chromachase	A021	5.70+22	<input type="checkbox"/>
Jan 77	Oscilloscope Calibrator	A023	1.25+12	<input type="checkbox"/>
Jan 77	Icelert	A020	1.45+12	<input type="checkbox"/>
Jan 77	Polyphon, motor and main boards	A025/4	7.90+20	<input type="checkbox"/>
	Polyphon, tune disc blank, (SRBP)	A008*	0.90+15	<input type="checkbox"/>
Feb 77	Transistor Checker	A026	1.18+12	<input type="checkbox"/>
Mar 77	FM Stereo Touch Tuner	D023/4/5	7.50+20	<input type="checkbox"/>
Apr 77	Tug 'o' War (set)	A029/030	2.88+12	<input type="checkbox"/>
Apr 77	Gas/Smoke Sensor Alarm	A028	0.65+12	<input type="checkbox"/>
May 77	2-Way Intercom	D019	1.28+12	<input type="checkbox"/>
May 77	Protected Battery Charger	A027	2.38+12	<input type="checkbox"/>
May 77	Seekit Metal Locator	A031	3.38+12	<input type="checkbox"/>
June 77	Reverberation Amplifier	A032	2.38+12	<input type="checkbox"/>
June 77	Versatile AF Generator	A033	2.38+12	<input type="checkbox"/>
June 77	Tele-Games	D029	3.22+18	<input type="checkbox"/>
July 77	20W IC Amplifier	A034	1.38+12	<input type="checkbox"/>
July 77	Radio 2 Tuner	A035	1.68+12	<input type="checkbox"/>
July 77	Digital Clock Timer	A036	3.28+12	<input type="checkbox"/>
Aug 77	Shoot (Telegames)	D035	1.55+15	<input type="checkbox"/>
Aug 77	Atomic Time Receiver	D036	2.65+15	<input type="checkbox"/>
Aug 77	Morse Code Tutor Cards (SRBP)	A037	4.75+15	<input type="checkbox"/>
Sept 77	Jubilee Electronic Organ	A038	19.00+75	<input type="checkbox"/>
Sept 77	Electronic Car Voltage Regulator	D037	1.25+12	<input type="checkbox"/>
Oct 77	Audio Level Indicator	D039	0.98+12	<input type="checkbox"/>
Oct 77	Sine-Square Wave Generator	D040	2.35+15	<input type="checkbox"/>
Nov 77	Laboratory Power Supply	A039	3.50+12	<input type="checkbox"/>

Post and packing is for one board or set of boards. Prices include V.A.T. Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required.

I enclose Postal Order/Cheque ACCESS welcome.

No..... Send card number only.  
 for £..... made payable to READERS PCB SERVICES LTD

NAME .....

ADDRESS .....

.....

..... Post Code.....

Any correspondence concerning this service must be addressed to READERS PCB SERVICES and not to the Editorial offices.

# A MERE 20 YEARS

R.HAM BRS15744

Within the past 20 years, man has achieved his dream of centuries and become clever enough to leave his own world and visit another. In fact, it was barely 12 years from October 1957, when the Russians launched the first artificial earth satellite, to July 1969 when the Americans placed two men on the moon.

It all began on October 4, 1957, when a 23in polished sphere, called Sputnik-1, and weighing 184lb, began orbiting the earth every 96.2 minutes, sending the first radio signals back to earth from a man-made space-craft. Very soon, radio enthusiasts throughout the world were working out orbit times and tuning their communications receivers around 20MHz to hear the bleeping signals as Sputnik-1 passed over. A month later, Soviet scientists put the dog Laika into earth orbit aboard their 1120lb Sputnik-2 and in February 1958 the Americans launched their first satellite, Explorer 1.

As the years passed by, hundreds of satellites were successfully launched by both the Americans and Russians and through their combined efforts a great deal of scientific knowledge has been gained.

## Marconi's Day

Just four years and two months after the conquest of space began, the first amateur radio satellite, Oscar-1 (Orbiting Satellite Carrying Amateur Radio) was sending signals back to earth on 145.008 MHz. Thanks to the United States Government Oscar-1 was placed in orbit, as a "piggy-back" passenger, by a USAF Thor-Agena rocket while on another mission from the Vandenberg base in California. At that time, amateur radio had much worth-while publicity because Oscar-1 was launched on December 12, 1961,

the 60th anniversary of the day that Marconi and his colleague Kemp, situated on Signal Hill, Newfoundland, heard for the first time in our history, a wireless signal which had originated from the other side of the Atlantic.

Technically minded people throughout the world praised the Project Oscar Association (formed by a group of American radio amateurs) for making it reality, that a 101lb capsule, carrying a tiny VHF transmitter was orbiting the earth and sending the letters 'hi'-'hi'-'hi' in morse code from space. Further satellites in this series were launched by American rockets in 1962, 65, 70, 72 and 74 of which the last two, Oscars 6/7, are both communications satellites and still operational. (Details in *Practical Wireless*, December 1976.)




The QSL card received by the author confirming his reception of signals from Australis Oscar 5.

In January 1970 Australis-Oscar 5, constructed by amateurs in Melbourne, Australia, was launched and its signals, a series of variable tones, gave information about the satellite's attitude, battery condition and temperature. This data was received on 144.05MHz and, by ground command, on 29.45MHz was recorded by a team of regular observers on special log sheets distributed by Bill Browning, G2AOX, for the occasion.
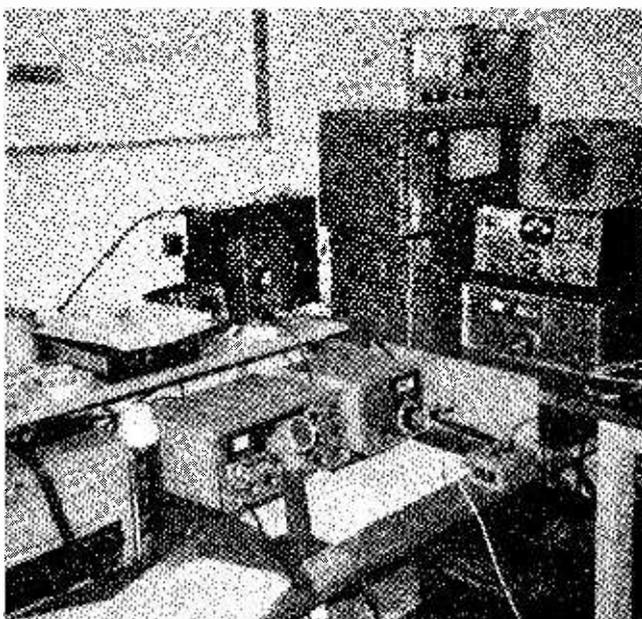
## Communications Satellites

Satellites provided the answer for faster communications around the world and, although the first "active" communications satellite Courier-1b, only operated for 17 days, by July 1962 the first television pictures had bridged the Atlantic via Telstar-1, followed in December 62 by Relay-1.

In July 1963 Syncom-2 was placed in synchronous orbit some 22,000 miles over the Indian Ocean, followed in 1964 by Syncom-3, in 1965 by Early Bird-1. In January 1967 Intelsat-2b was stationed, also in synchronous orbit, above the Pacific Ocean and was used to link Apollo programme stations together in addition to its commercial duties. The first "passive"



The equipment installed at the clubroom of the Mid-Sussex Amateur Radio Society for co-ordinating the launch of Oscar 7.

# S-DeCnology


DAVID GIBSON

11



THIS MONTH

## 'Automatic Courtesy Light'

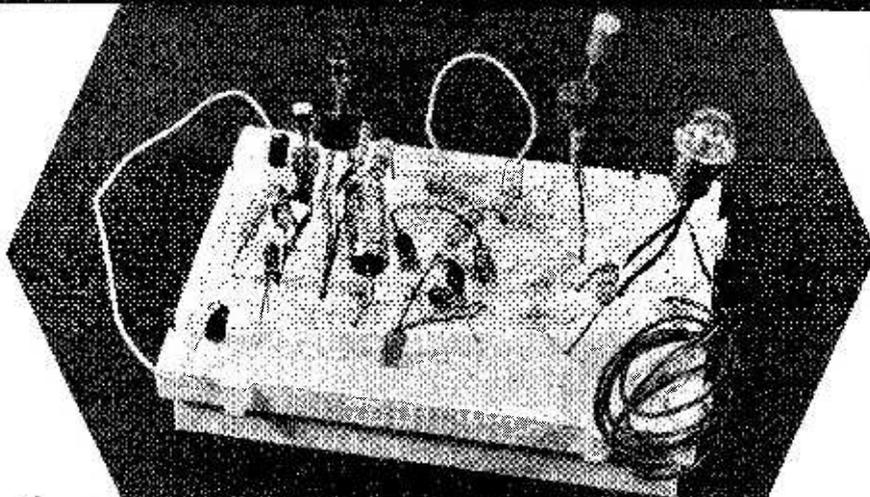

Throughout this series, electronics has been employed to amuse, assist or entertain. The circuit shown in Fig. 1 must surely come under the heading of 'useful'.

The basic idea is that a momentary contact is made which causes a light to switch itself on. After a pre-determined period, the light automatically switches itself off. It remains off until there is another contact (this need only be for a fraction of a second) when it will again illuminate and, after a set period, switch off again automatically.

It is envisaged that numerous uses could be found for an automatic courtesy light. For example, the bell push on a front door could form the contacts. When pushed, the light would come on just long enough for the keyhole to be found.

### Circuitry

At first sight, the circuit of Fig. 1 may look unfamiliar and yet careful examination will show that

it is merely a multivibrator connected for mono-stable operation. Transistors Tr2 and Tr3 form the mono-stable. Note the absence of a capacitor which (in an astable) would be inserted in place of R6.

The result is that the mono-stable normally remains in one state: with one transistor on and the other off. By making a momentary contact across S-DeC holes 65 and 70, it causes Tr2 to switch on and Tr3 to switch off. The result is that Tr1 now conducts and lights the lamp LP1 in its collector lead.

This new stable state is not permanent however. It only lasts for a finite time which is dependent upon the value of the resistor pushed into S-DeC holes 4 and 14; and on the value of the capacitor C1. After a time (which depends on these C1/R5 values) the circuit will automatically revert to its original state. It will remain in this state until the contacts are again shorted. See Fig. 2 for component layout.

### Components

Variation of R5/C1 gives a measure of control over the timing period during which lamp LP1 is on. Using the values shown, the lamp remains on for a period of 15 seconds. Changing the value of C1 to 330µF increased the 'on' period of LP1 to approximately one minute. Variation of R5 might be useful in some applications but it suggested that the minimum value of resistance should be 47kΩ. It is possible to use a potentiometer for R5 but in this event a 47kΩ resis-

you will need . . .

R1 5.6kΩ	C1 100µF (see text)
R2 1.8kΩ	C2 0.01µF
R3 5.6kΩ	Tr1 AC126
R4 150kΩ	Tr2 BC109
R5 150kΩ	Tr3 BC109
R6 10kΩ	LP1 6V 100mA bulb
R7 5.6kΩ	B1 6V battery
One S-DeC	Three transistor holders

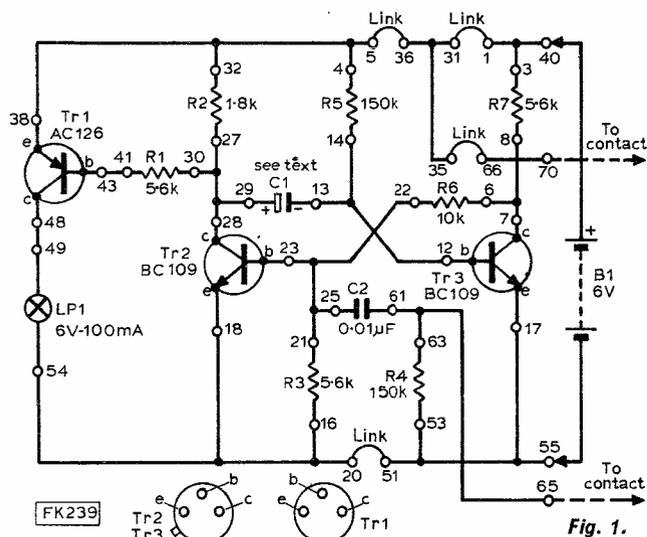


Fig. 1.

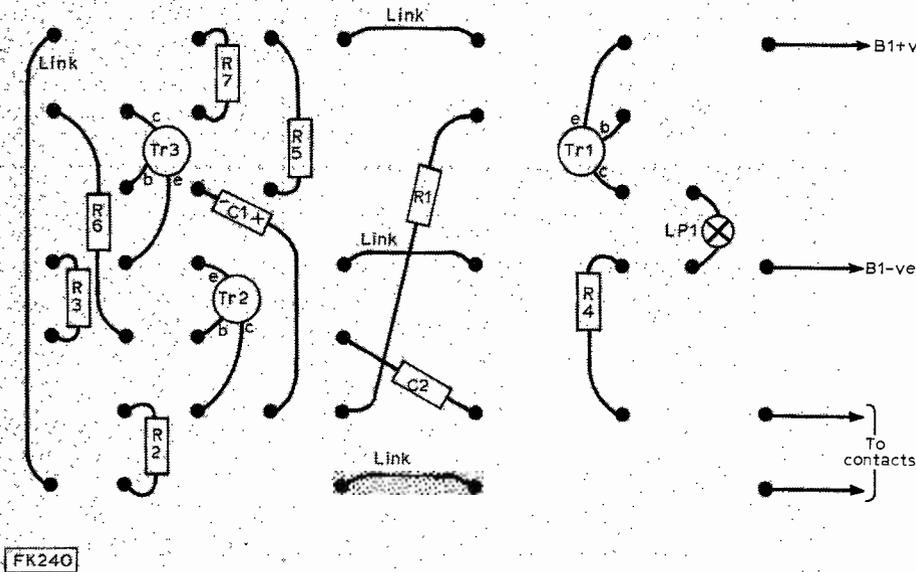


Fig. 2: The S-DeC layout for this month's project shown actual size. Alternative transistor types may be used to those shown in the circuit. However, make sure that their leadout configurations are in accordance with the layout. Also note that Tr1 is a PNP type while the others are NPN.

tor should be wired in series with the pot, thus ensuring a minimum value at all times.

Lamp LP1 should not be rated at greater than 100mA, and 6V should be considered the ideal voltage for general use with the circuit. If the light is to be on for only short cycle times, say not longer than 15 seconds, then up to 12V may be used. With 6V applied and a 330µF capacitor for C1, the quiescent current drawn by the total circuit was barely 1.25mA. Using a 4.5V battery, this dropped to approximately 0.9mA.

## Contacts

The contacts which short together momentarily can be the bared ends of the wires from S-DeC holes 70 and 65. These might be fixed to a door (or whatever) in such a way that when the door opened the two bared ends brushed against each other. For other applications any type of switch or bell-push would be suitable, and a reed switch with magnet should be an elegant and reliable method.

TRANSISTORS:	19p	13p*	38p	14p*	45p	90p	14 Pin DIL:	ZENER DIODES:	PRECISION POLY-CARBONATE CAPACITORS		
AC107	BC117	BD136	BF273	OC72	7447A	14 Pin DIL:	400mW + - 5% 3V-33V	All High Stability—extremely Low Leakage			
AC107	BC118	BD137	BF336	OC75	7450	20p	18Ω each: 10/95p	440V Value	A.C. RANGE		
AC117	BC125	BD138	BF337	OC77	7453	22p	3V3-200V	Dimen-	Dimensions (mm)		
AC126	BC126	BD139	BF458	OC81D	7460	22p	18Ω each: 10/£1.75	sions (mm)	L D		
AC127	BC132	BD140	BF459	OC82D	7470	22p	100 ohm to 1M—7p* each: 50 for	Price			
AC128	BC134	BD145	BF596	R2008B	7473	36p	£3-00*. 100 for £5-00*	each			
AC128K	BC135	BD182	BF597	R2010B	7474	36p		0-1	27	12-7	£1.34
AC141	BC136	BD183	BF617	TIP23	7475	52p		0-15	27	12-7	£1.52
AC141K	BC137	BD184	BF741	TIP31A	7476	52p		0-22	33	16	£1.66
AC142	BC138	BD187	BF743	TIP32A	7482	52p		0-25	33	16	£1.78
AC142K	BC139	BD188	BF744	TIP33	7490	52p		0-33	33	16	£1.92
AC153K	BC140	BD189	BF745	TIP34	7492	52p		0-42	33	19	£2.08
AC154	BC142	BD232	BF746	TIP41A	7493	52p		0-5	33	22	£2.24
AC176	BC143	BD234	BF747	TIP42A	7496	52p		0-68	50-8	19	£2.48
AC178	BC147	BD235	BF748	TIP42B	7499	52p		1-0	50-8	22	£2.64
AC179	BC147A	BD236	BF749	TIP42C	7499	52p		1-5	50-8	25-4	£3.14
AC187	BC147B	BD237	BF750	TIP3055	74121	43p		2-0	50-8	25-4	£3.74
AC187K	BC148	BD238	BF751	TIP3055	74122	43p					
AC188	BC148B	BD239	BF752	TIP3055	74122	43p					
AC188K	BC149	BD240	BF753	TIP3055	74122	43p					
AC193K	BC149B	BD241	BF754	TIP3055	74122	43p					
AC194K	BC149C	BD242	BF755	TIP3055	74122	43p					
AC194K	BC149D	BD243	BF756	TIP3055	74122	43p					
AC194K	BC149E	BD244	BF757	TIP3055	74122	43p					
AD140	BC153	BD245	BF758	TIP3055	74122	43p					
AD142	BC154	BD246	BF759	TIP3055	74122	43p					
AD143	BC157	BD247	BF760	TIP3055	74122	43p					
AD149	BC157A	BD248	BF761	TIP3055	74122	43p					
AD161	BC158	BD249	BF762	TIP3055	74122	43p					
AD162	BC158B	BD250	BF763	TIP3055	74122	43p					
AF114	BC159	BD251	BF764	TIP3055	74122	43p					
AF115	BC159B	BD252	BF765	TIP3055	74122	43p					
AF116	BC159C	BD253	BF766	TIP3055	74122	43p					
AF117	BC161	BD254	BF767	TIP3055	74122	43p					
AF118	BC167B	BD255	BF768	TIP3055	74122	43p					
AF121	BC168A	BD256	BF769	TIP3055	74122	43p					
AF124	BC168B	BD257	BF770	TIP3055	74122	43p					
AF125	BC169B	BD258	BF771	TIP3055	74122	43p					
AF126	BC169C	BD259	BF772	TIP3055	74122	43p					
AF127	BC170	BD260	BF773	TIP3055	74122	43p					
AF139	BC170B	BD261	BF774	TIP3055	74122	43p					
AF178	BC170C	BD262	BF775	TIP3055	74122	43p					
AF179	BC171	BD263	BF776	TIP3055	74122	43p					
AF180	BC171A	BD264	BF777	TIP3055	74122	43p					
AF181	BC171B	BD265	BF778	TIP3055	74122	43p					
AF186	BC172	BD266	BF779	TIP3055	74122	43p					
AF239	BC172B	BD267	BF780	TIP3055	74122	43p					
AF279	BC172C	BD268	BF781	TIP3055	74122	43p					
AS567	BC173	BD269	BF782	TIP3055	74122	43p					
AU110	BC173B	BD270	BF783	TIP3055	74122	43p					
AU113	BC176	BD271	BF784	TIP3055	74122	43p					
BC107	BC177	BD272	BF785	TIP3055	74122	43p					
BC107A	BC177A	BD273	BF786	TIP3055	74122	43p					
BC107B	BC177B	BD274	BF787	TIP3055	74122	43p					
BC108	BC178	BD275	BF788	TIP3055	74122	43p					
BC108A	BC178A	BD276	BF789	TIP3055	74122	43p					
BC108B	BC178B	BD277	BF790	TIP3055	74122	43p					
BC108C	BC179A	BD278	BF791	TIP3055	74122	43p					
BC109	BC179B	BD279	BF792	TIP3055	74122	43p					
BC109A	BC182	BD280	BF793	TIP3055	74122	43p					
BC109B	BC182B	BD281	BF794	TIP3055	74122	43p					
BC109C	BC182C	BD282	BF795	TIP3055	74122	43p					
BC113	BC183	BD283	BF796	TIP3055	74122	43p					
BC114	BC183B	BD284	BF797	TIP3055	74122	43p					
BC115	BC183L	BD285	BF798	TIP3055	74122	43p					
BC116	BC183LB	BD286	BF799	TIP3055	74122	43p					

communications satellite, Echo-1, launched August 1960, was a 100ft diameter balloon with a metallised surface for reflecting radio signals. Later, in January 1964, came the 135ft diameter Echo-2 which was used in a co-operative programme with the USSR. Many radio amateurs took part in the Echo experiments.

## The Permit


Around April '62 the question arose as to whether amateurs would be contravening the terms of their licence if they listened to satellite signals outside the recognised amateur bands. However, as a result of discussions between the Radio Services Department and the RSGB the Post Office decided that if an amateur wishes to receive signals emitted by artificial earth satellites engaged in scientific space research, for the purpose of making observations on the technical characteristics of such signals, or otherwise carrying on technical investigations in radio technique, they will authorise him to do so.

## Conquest of the Moon

It was only 11 years and 7 months from the flight of Sputnik-1 to the day when Neil Armstrong and Edwin "Buzz" Aldrin landed on the moon, after a journey which had been pioneered by a series of earth satellites. Between July 1964 and March 1965 Rangers 7, 8 and 9 sent back a total of 17,000 TV pictures from their three journeys to the moon. In May 1966 Surveyor-1 made a successful soft landing and in 13 days it sent more than 11,000 pictures of the lunar terrain back to earth. In August 1966 Luna-Orbiter-1 photographed some two million square miles of the moon's surface while on earth, men were being trained in the Gemini, Mercury and Apollo capsules ready for that great moment in July 1969 when a radio signal from the moon, 240,000 miles away, carried the message: "this is Tranquility Base, the Eagle has landed."

When Neil Armstrong left the Eagle and set foot on the moon he said "one small step for Man . . . one giant leap for Mankind" and I think that sums up the whole of the space programme over the past 20 years.
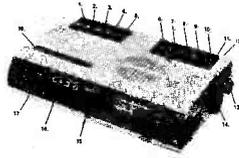
# Our finger is right on the button when it comes to SCIENTIFIC PRODUCTS at the right price



1. Fast forward time set.
2. Slow forward time set
3. Green glow indicator set
4. Alarm set
5. Alarm off
6. Standby mode/selector
7. Time setting pointer
8. AM/FM selector
9. Preset Memory Auto switch
10. Power On/Off
11. (Emission) Radio alarm selector
12. Emergency socket
13. Volume control
14. Tuning control
15. Alarm setting
16. Alarm operating light
17. Alarm (Emission) and Radio time setting button
18. Section speaker button

### THE NEW LIGHT SENSOR CLOCK RADIO

This ultimate fully solid state a.m./f.m. clock radio has everything you need. A high Green display that automatically dims when the lights are out to an unobtrusive glow. Wake to music or bleeper alarm, or at the slightest touch on the snooze plate have 9 min. more or more, etc., or fall asleep to music. It automatically switches off 1-59 min. Push button switch controls, volume control. Excellent a.m./f.m. radio ear socket. Only £49.95. Similar clock radio but with switch to dim and button for snooze red display £39.95. Stereo £59.95. Add £1 to any one for P. & P.

### L.E.D. NEW RANGE L.C.D.



**2AED Gents.** Hr. Min. sec. Mth. Date. Day. £9.95  
**3AED luxury finish Gents.** Hr. Min. Sec. Month. Date Day. £14.95  
**2LAO Ladies** Hr. Min. Sec. Month. Date. Day £12.95  
**3LAD Ladies Dress** Bark finish. Hr. Min. Sec. Mth. Date. Day. £16.95  
**1UD unisex** Hr. Min. Sec. Mth. Date. Day. £14.95  
**QUARTZ ANALOG.** The Familiar Face. But with the Quartz accuracy. 3 year Bat. Life. Stainless Steel. Date. 5/hd. £40.95  
 All prices quoted are for stainless steel with adjustable matching bracelets. For gold plate add £1.50 to price.  
 All our watches have manufacturer's back-up service and full guarantee for 12 months.


**2LC Gents (Hr. M.)** b/ltte. Sec. Date. Mth. £17.95  
**GLC Gents.** (Hr. Min. Sec.) B/ltte. Mth. Date £24.95  
**4LC Gents.** (Hr. Min. Sec.) B. ltte. Month. Date. Day. Stopwatch. 10/100th sec. £37.95  
**5LC Gents.** World time (Hr. Min. Sec. Day). Date. Month. 3 time zones stop watch. Counter. £45.95  
**6LC Gents.** Chronograph (Hr. Min. (Sec.) or date) Date. Day. Chronograph functions stop lat. acc. time £49.95  
**6LCL Ladies.** (Hr. Min.) B. ltte. Sec. Month. Date. £39.95  
**SOLAR WATCH** (Hr. Min. Sec.) B. Ltte. Month. Date. £59.95  
 (Functions in brackets are continuously on display)

### RADIO TV CASSETTE

The wonderful portable machine has everything you want for your personal pleasure on holiday abroad, anywhere in the world. TV as well! 3in. T.V.H.F. and U.H.F. Radio M.W./F.M. and Short wave Radio. Cassette tape recorder output 3 watts. Bass, Treble, tone controls mixing facilities beat cut switch, review pause. Auto stop record facilities Bat Mains car. Our price only £198.95. Add £1.50 for P. & P.


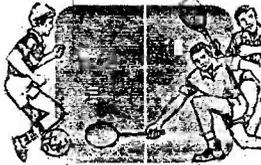
### TV GAMES LATEST IN HOME ENTERTAINMENT



**SETS**  
**MARK 1**—Football Tennis Squash £19.95  
**MARK 2**—D/L Football Tennis Squash Solo/Practice £27.50  
**MARK 2**—Hr. As Mark 2 in colour £38.50  
**MARK 3**—D/L Football Tennis Squash Solo/Practice £47.50  
**MARK 3C**—As Mark 3 in colour £54.95  
 All games have auto service auto scoring on screen selectable bat sizes and ball speeds realistic noises and fits all TV. Add £1 for P. & P.  
 We are major suppliers to government depts., large companies, schools, etc. All products are guaranteed for 12 months. Send your order with. Cheque/Barclycard/Cash to Dept. ET. All prices include VAT. Add 85p for P. & P. unless otherwise stated.  
 Open. Mon.-Thur. 9.30-5.30. Fri.-Sun. 10-1pm.

The New 36 Step Scientific Programme from Sinclair Algebraic logic has all scientific functions log., trig., sin., tan., cos., rad./degree, exp., etc. plus a programme calculator with conditional and unconditional branch instructions. Our price only £14.95. Set of 4 programme books giving 294 programmes £4.95. Mains adaptor £2.95.



**Texas**  
**58** 480 program steps up to 60 memories **£78.95**  
**59** Card programmable 960 steps 100 memories **£208.95**  
**57** 50 step programmable **£42.95**  
**PC190A** Print cradle for use with 59, 52, 56, 58 **£175.95**  
**51** multi fully sci 3 mem **£33.95**  
**41** Financial **£27.95**  
**5200** Desk top **£42.95**  
**CBM**  
**pr100** 72 steps programmable **£37.95**  
**N60** Navigator **£89.95**  
**SR61** Statistician **£89.95**  
**4/5199R** 92 steps Pre programmable sci **£24.95**  
**4148** Full sci. **£19.95**  
**Sinclair**  
 New Cambridge programmable **£14.95**  
 Set of 4 libraries **£4.95**  
 Micro Quartz Car Clock **£18.95**  
**Hewlett Packard**  
 HP.25, HP.67, HP.23, HP.91, HP.97, HP.11, etc. Prices on application.  
**Sharp**  
**E18120** LCD recharge % Mem **£20.95**  
**Lc 8029** LCD Folding pen **£23.95**  
**Casio**  
**CQ1** Time, stop watch, calc., Alarm set alarm 4 diff. times and 4 diff. tones **£29.95**  
**MC1** New LCD. Calculator Clock, Stopwatch **£34.95**  
**SD1** Mem. calc., time measurement, Net, Time, Lap, & split time **£26.95**  
**Pro FX1** Card programmable **£129.95**  
**FX201** Programmable **£48.95**  
**FX202** Prog with facility for keep prog. when off **£47.95**  
**FX2000** LCD Sci **£24.95**  
**FX 110** Full Sci **£17.95**  
**LC220** Lod in Wallet **£17.95**  
 Rechargeable free.

### NEW PHONE



The Phone that you don't have to get out of bed in order to dial. All is contained in the hand piece. Not GPO approved but everybody else approves. Fully guaranteed. White, red, ivory, pastel blue and green. £55. Ordinary push button for those who don't like to work their fingers too hard £149.95.

### VINTAGE CAR RADIOS

### WIRELESS INTERCOM



Just plug each unit into house mains up to 1 mile distance depending on conditions, no other wires or batteries needed, excellent for offices, warehouses, homes etc. Identical units. Volume control, on/off switch, pilot light. Talk and lock buttons. £33.95 P. & P. 95p.

### 1931 ROLLS ROYCE

### 1928 LINCOLN (Illustrated)

Replica models beautifully finished. Makes a lovely present £15.75.

## Supurb 2-Way Walkie Talkies

**MVF** only £37.95 per pair range up to 3km approx. 100mW call buzzer compact strap volume control.  
**MV 100** only £25.50 per pair range up to 5km approx. 1 watt 3 channel int. circuit PET V control-call buzzer carr. case earphone.  
**MV 2500** only £198.95 per pair range 10kms approx. 2.5 watt 2 channel superhet squelch V. control call buzzer carr. case earphone all sets 30% longer range at sea. These sets are solidly made to the highest standards. For export and Yachtsmen.  
 All our goods are full guaranteed for 12 months. We also stock a range of desk, print outs, ordinary calcs. Specialist calcs. Cassette, radio Stereo, etc. Tell us your requirements and we will supply. If you are not fully satisfied please return goods to us in proper condition within 10 days and we will send you a refund.



**barclay** ELECTRONICS


1115 FINCHLEY RD  
 TEMPLE FORTUNE TEL: 01-  
 LONDON N.W.11. 458 4755

# all band short wave converter

Part 2

F. RAYER G3OGR

# converter

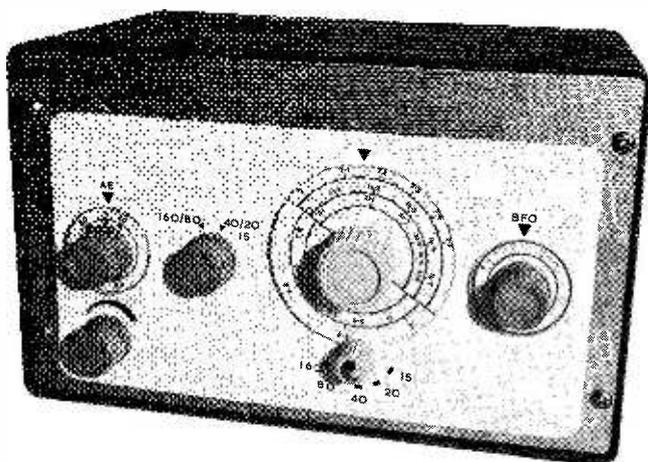

## Tuning Adjustments

L1, L2 and L3 and the trimmers can be set before adding the BFO and 5.5MHz FET stage. L3 and the trimmers determine the bands covered, so they must be adjusted correctly. Either of the following methods can be used:

1. If the associated receiver covers at least some of the correct oscillator frequencies, and if its calibration is reasonably accurate, the oscillator frequency can be checked by placing its aerial lead (preferably screened except near the end) near L3. It will then be possible to pick up the oscillator carrier. As the converter output is to be 5.5MHz, there will be 5.5MHz difference between the required band frequencies and the oscillator. For example, for 1.8 to 2.0MHz the oscillator will tune to 7.3 to 7.5MHz. TC1 and L3 are adjusted until this is achieved. All the required oscillator frequencies were listed earlier. If a required band cannot be reached with some of the trimmers, the core of L3 is slightly moved to correct this, until adjustment of the five trimmers alone allows all five bands to be covered.

2. An alternative method is to use a signal generator, or to find amateur band signals, working the converter into the receiver in the usual way. The core of L3 is sealed after adjustment.

Subsequently adjust the core of L1 so that 7MHz signals are peaked with VC1 fully closed, and 21MHz is reached with VC1 nearly completely open. L2 has more than adequate coverage for 160 and 80m and the core is set so that VC1 gives resonance with both bands. VC1 will allow tuning of signals 11MHz away from the required bands, in the way explained, so the five resonant points for the wanted bands should be marked on the dial of this control. The core of L4 is simply adjusted for best volume or sensitivity.

## IF Unit

The IF stage is assembled on a metal chassis about 75 x 50 x 40mm (3 x 2 x 1½in) high, as in Fig. 7, made from scrap metal. Coil L5 is wound on a 7mm diameter former. Begin at point 1 and wind on thirty-three turns to 32SWG enamelled wire, finishing at point 2. C18 is across this winding, its leads projecting under the chassis. Winding 3-4 is ten turns, close to the main winding.

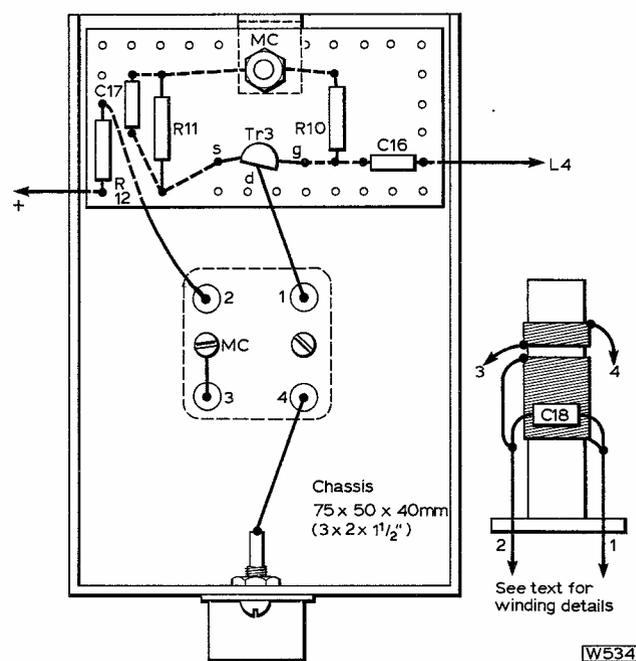


Fig. 7: Layout and wiring for the optional IF amplifier stage.

The small board in Fig. 7 is mounted by a bracket, which is the chassis and negative return. Output from 4 goes to a co-axial socket on the unit. The coil core is set to peak signals, as for L4.

## BFO Unit

Fig. 3 is the circuit, and Fig. 8 the layout of this stage. L6 is wound on a 7mm diameter former, with core, and has thirty turns of 32SWG wire, close wound, centre-tapped for the chassis connection. R14 and R15 allow the shorting of VC3, to put the stage out of use, thus avoiding a separate switch. The extreme corner of one moving plate is bent outwards, so that it firmly contacts a fixed plate when the capacitor is closed.

A satisfactory level of BFO coupling was obtained by running an insulated lead from VC3 (marked IF) and looping this round the centre pin of the output socket in Fig. 7. When this stage is fitted, set VC3

half open, tune in an AM or CW signal and adjust the core of L6 for the usual zero beat position. Rotating VC3 either way should then cause a heterodyne, rising in pitch.

65 x 35mm (2 1/2" x 1 3/8") 0.15" matrix


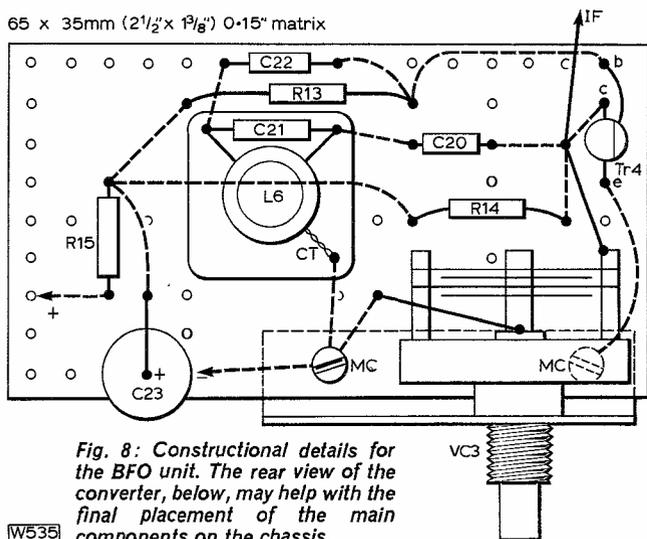


Fig. 8: Constructional details for the BFO unit. The rear view of the converter, below, may help with the final placement of the main components on the chassis.

W535

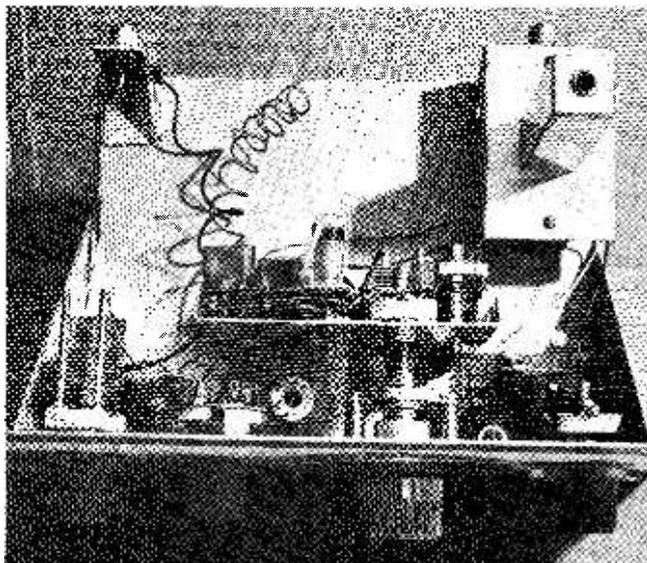

The converter is ideal for use with the general coverage type of communications receiver, but can of course be used with other receivers. A screened aerial lead from receiver to converter is necessary, and should not be longer than necessary. This can provide an earth connection from converter to receiver, which is essential.

The likelihood of 5.5MHz breakthrough depends on the screening and other factors. A very small adjustment of receiver tuning above or below 5.5MHz will have little important effect on calibration, but if the shift away from 5.5MHz is substantial the converter ought to be re-aligned to suit the actual IF output to be used. Chances of 5.5MHz breakthrough will be very much reduced by using an aerial tuner, which will also allow best results with very weak signals. It is also possible to fit a 5.5MHz trap in the aerial lead at the converter. It is essential to turn back VR1 with strong signals to avoid overloading the receiver.

# next month in Television

## ● TEN YEARS OF COLOUR!

Next month's issue is a special one to commemorate ten years of colour TV broadcasting in the UK. Pat Hawker sets the scene with an account of the debate over the choice of colour system – whether to go for NTSC, SECAM, PAL or one of the other variants. E. Trundle describes ten years' experience of servicing colour receivers, from the early valved monsters to today's solid-state, slim-line sets with in-line gun c.r.t.s. And Harold Peters takes you behind the scenes with an account of the problems the setmakers have had to solve.

## ● VCR SERVO FAULTS

Dealing with faults in VCR servo circuits is a relatively new aspect of the servicing scene. Steve Beeching describes a logical approach to finding out where the trouble lies in the twin servo (head and capstan) system used in the Philips N1500 series of VCRs.

## ● CO-CHANNEL NOTCH FILTER

In some locations different ITV programmes are available on the same channel. Whichever is selected, there is the problem of co-channel interference. The vision carrier offset makes it possible to use a notch filter to reduce the interference however. Alan Latham describes an interesting RC notch filter with an f.e.t. amplifier to increase the Q factor. This can be inserted in the luminance channel.

**PLUS ALL THE REGULAR FEATURES**

**ORDER YOUR COPY ON THE FORM BELOW:**

TO.....  
(Name of Newsagent)

Please reserve/deliver the **DECEMBER** issue of **TELEVISION** (50p), on sale November 21st, and continue every month until further notice.

NAME.....

ADDRESS.....

# PRODUCTION LINES

bill tull


## Philip's kits

Complete Kits manufactured by a reputable company usually have one big advantage over a project whose components have been bought 'piece-meal'—and that is the finished object looks professional. Of course by buying a complete kit, you have everything you need at once, together with instructions and probably useful hints and tips about the pitfalls a builder is likely to come across. A range of electronic kits have now been made available by Philips, and com-



prise a wide variety from a small multi-purpose amplifier to a studio-quality mixer unit. An illustrated catalogue giving full details of the complete range of kits is available from the distributors, and with every kit there is a money-back guarantee.

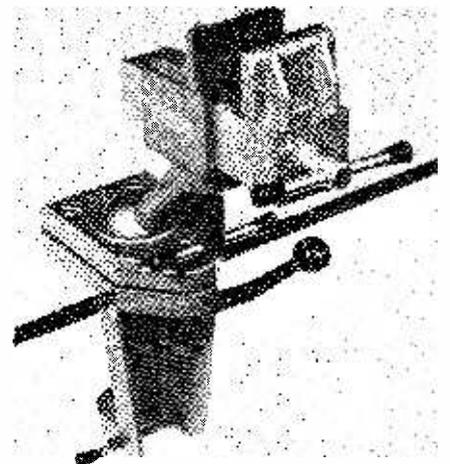
*SST Distributors (Electronic Components) Ltd., West Road, Tottenham, London N17. Tel: 01-808 4884.*



*Practical Wireless, December 1977*
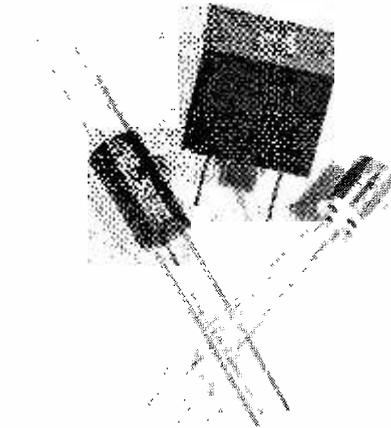
## Coupled and amplified

A 50W audio power amplifier and a new family of LED/Photocell opto-couplers are two new products to come out of NSL. The amplifier, which is mounted on its own heatsink is claimed to have a frequency response from 15Hz up to 25kHz with the addition



of only one external capacitor and power supply. Notated the Epitek 5070A, distortion is put at less than 0.15% at full power, with the additional advantages of S/C protection and automatic thermal shut-down over 70°C.

opposite ends, and a  $\frac{3}{4}$ in square module. The latter has the added advantage of housing either one or two cells. Prices range from £2.90 to £5.00 plus VAT each, and for the Epitek 5070A power amplifier the price is £16.50 plus VAT for 1off but including P&P.

*National Semiconductors Ltd., Stamford House, Stamford New Road, Altrincham, Cheshire. Tel: 061-928 3417.*

The opto-couplers which have been given the title '5S family' are encapsulated in a clear epoxy, with the detectors rated at 320V/250mW, with an LED current of 25mA, giving maximum on, and minimum dark resistances of 2k ohms and 100M ohms respectively. These coupled pairs are available in either 4pin TO5 size can, a cylindrical shaped package in which the detector and LED leads emerge at

of only one external capacitor and power supply. Notated the Epitek 5070A, distortion is put at less than 0.15% at full power, with the additional advantages of S/C protection and automatic thermal shut-down over 70°C.

## Get a grip on it!


Ideally suited to the electronic constructor is a new vice from Greenwood Electronics. If you've ever tried drilling a chassis or soldering components to a tag strip or PCB you know that a third hand is a necessity. This new vice, labelled the Oryx Model 1B is equipped with 3.5in jaws and is fully adjustable to rotate through 360° and can be locked in any position. Replaceable nylon jaw linings are included which protect delicate surfaces, while the finish is in stove enamelled green. The Oryx bench vice sells for £19.95 plus VAT.

*Greenwood Electronics, Portman Road, Berkshire. Tel: Reading 595844.*
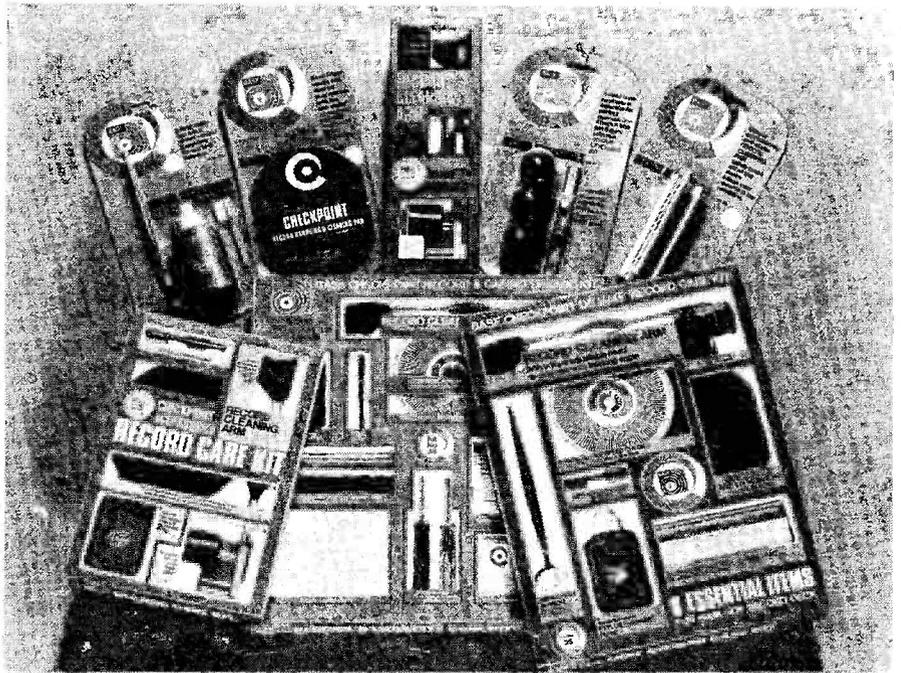
## Packed-up


The latest products to join the bubble-pack band wagon are a range of record and cassette care accessories from BASF. Called Checkpoint products, BASF state that 'they are the result of careful research into what the market really needs, and that the series is therefore limited to useful, non-gimmicky products'. The items which make up the Checkpoint range are too numerous to list, but for the record enthusiast there are nine packs available, for the cassette and reel-to-reel enthusiast, 25 packs, and for the lucky person who has both record and cassette player, one pack.

As can be seen from the photograph, some of the packs are really comprehensive, with, for example, the Record and Cassette Care Kit containing such goodies as a record cleaning arm, cleaning pad, stylus cleaning fluid and brush, inspection mirror, two screwdrivers, index cards, self-adhesive



cassette labels, stroboscope speed check discs and a cleaning cloth. Packs start at around 30p for the Record Cleaning Cloth and extend up to £7.94

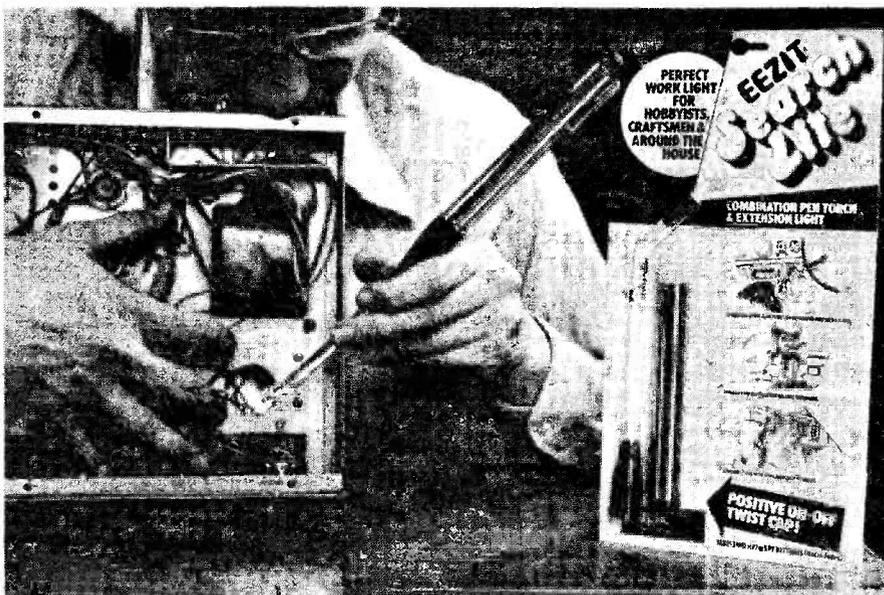for the Record and Cassette Care kit. BASF (UK) Ltd., Haddon House, 2-4 Fitzroy Street, London W1. Tel: 01-637 8971.



## Now you see it . . .

When you connected-up the PW 'Interwipe', or tried to repair that faulty TV, probably the most difficult problem that presented itself to you was in actually seeing what you were doing. There are many instances when the DIY enthusiast, electrician, technician or ordinary hobbyist needs a source of light that he can shine round corners.


Now, throwing a little light on this subject is GSPK (Sales) Ltd, who are marketing a torch that is designed to illuminate all those inaccessible spots. Called the 'Search Lite' it comprises a slim 140mm pen light and a 165mm detachable clear acrylic extension piece. It requires either HP7 or SP7 batteries.

Priced at £1.99 incl. VAT it should be available just about everywhere. GSPK (Sales) Ltd., Hookstone Park, Harrogate, Yorks. Tel: 0423 886641.
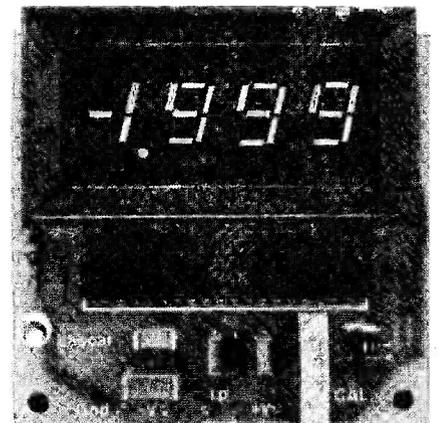
## Display digits

A 3½ digit panel meter, featuring auto-polarity, auto-zero, and an accuracy of 0.1% has recently been announced by Lascar electronics. Available with sensitivities of either 199.9mV or 1.999mV FSD, the purchaser can also choose between a 0.3in or a 0.43in red LED display. Over-range input is indicated by suppression of the last three digits, and the left-hand decimal point is programmable. Measuring 76 × 70 × 10mm, both versions can be obtained for the 'not unoriginal sum' of £19.99.

Lascar Electronics, PO Box 12, Module House, Billericay, Essex, Tel: 02774 3394.





idea is to make the signal current taken by the base of the transistor negligible compared with that flowing in  $R_F$  and the signal source. Under these conditions the current gain becomes  $R_f/R_L$  and the voltage gain from the unloaded source to output is then  $R_f/R_s$  where  $R_s$  is the source resistance. This is essentially a current amplifier and the feedback will not be realised unless the source is a current source i.e. has a high internal impedance.

It is fairly clear that our application is one that requires a voltage amplifier and so we will base our design on the circuit of Fig. 2(a). Given the basic framework of the circuit, let us now proceed with the detailed design.

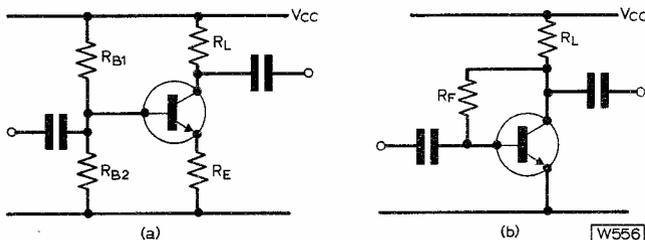


Fig. 2: Series and shunt feed-back circuits.

## Design

The first thing to do is to decide on the static (i.e. DC) voltages and currents and select a suitable transistor. In the higher echelon of the designing business it is normal to design the circuit, find out what specifications are needed for the transistor and then select the transistor type from the multitudes available. It is a lot easier here to say that we will use a BC109 because it has high gain, low noise, and is readily available. Readers who have ever looked up data on the BC109 will have found that most of it is given for a collector current of 2mA, but 1mA seems quite adequate for this job. Our supply voltage is 9V and it is sensible to space out our collector and emitter voltages as much as possible so as to have a large margin for possible error. Let's settle for an emitter voltage of 2.7V and a collector voltage of  $9 - 2.7 = 6.3V$ . This means that we will require a base voltage of about  $2.7 + 0.6 = 3.3V$ . This stage of the design is shown in Fig. 3: all that we have used here is Ohm's Law and the well known facts that the forward bias on the base-emitter junction of a silicon transistor is about 0.6V and that the emitter and collector currents will have about the same value.

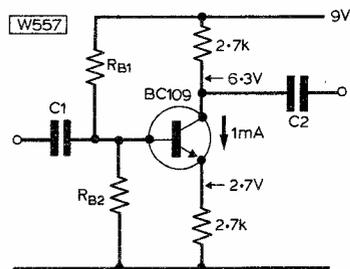


Fig. 3: Initial voltage requirements.

## Bias Network

The time has now come to assign values to  $R_{B1}$  and  $R_{B2}$ . There is a rule of thumb which states that the current flowing down the resistor chain should

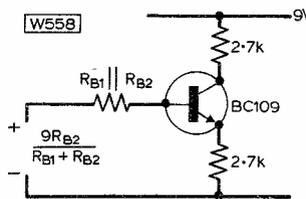


Fig. 4: Bias network equivalent circuit.

be at least five times, and preferably ten times, the maximum base current. There is, however, a much better way of calculating the resistor values: this involves regarding the bias network as a simple voltage source with an internal resistance. In our case the voltage is given by  $\frac{9R_{B2}}{R_{B1} + R_{B2}}$  and its internal impedance is  $R_{B1}$  in parallel with  $R_{B2}$  (written  $R_{B1} \parallel R_{B2}$ ). An equivalent circuit of the bias network is shown in Fig. 4. We must now decide how great we can allow this source impedance to be. Now the static DC gain ( $h_{FE}$ ) of a BC109 at  $I_c = 2mA$  is quoted as 200-800, so let us play safe and assume a value of 150. In this case the maximum base current

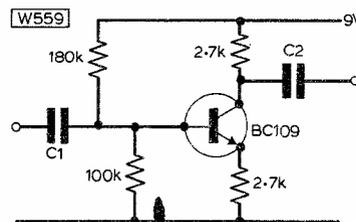


Fig. 5: The potential divider values.

is going to be  $1/150$  mA. It is probably quite safe to let this have the effect of dropping the bias voltage by half a volt, so we set a maximum on  $R_{B1} \parallel R_{B2}$  of

$$\frac{1}{2} \div \frac{1}{150} \text{ k}\Omega = 75\text{k}\Omega.$$

So we want a potential divider which produces a voltage of about 3.3V off load and which has an impedance of about 75k $\Omega$ . A calculation reveals that  $R_{B1} = 180\text{k}\Omega$  and  $R_{B2} = 100\text{k}\Omega$  satisfy these conditions and have a source impedance of about 64k $\Omega$ . If you calculate it yourself you will find that these values give almost exactly five times the current in the divider as is expected in the base, confirming the value of the rule of thumb approach. The method that we have used is, however, more instructive and is applicable to cases when there are several different supply rails. Anyway, back to business: we have now reached the stage shown in Fig. 5.


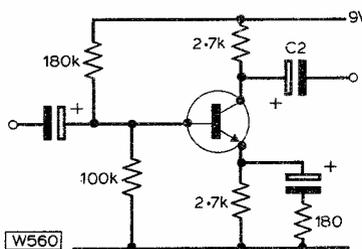


Fig. 6: Decoupling added to modify impedance.

## Gain and Impedance

It is now time to look at the voltage gain of our circuit. At the moment it is just less than one, so to realise our aim of a gain of ten at audio frequencies we will need to reduce the impedance to AC signals at the collector. This is done with a decoupling capacitor. We have already mentioned that the gain

*continued on page 606*

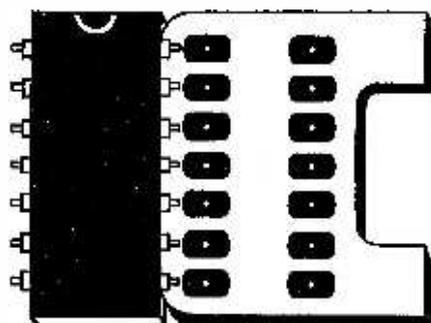

# OF THE MONTH 65

Brian DANCE M.Sc

## THOMSON-CSF SPEED REGULATORS

It is very important that the speed of small motors used in tape recorders and record players shall remain constant or the frequencies of the audio notes reproduced in the loudspeaker will vary. The speed of mains driven synchronous motors is locked to the frequency of the mains supply but the speed of battery-driven motors used in portable equipment can vary with the ambient temperature and with the supply voltage, whilst variations in the mechanical resistance opposing the movement of the motor spindle can also result in speed variations.

### Regulator Devices

A series of monolithic motor speed regulator devices manufactured by Thomson-CSF Ltd. can be used in extremely simple circuits to stabilise the motor speed. It is important to note that these devices can be employed only for the speed regulation of small permanent magnet DC motors; an entirely different type of motor speed regulator is required for use with AC motors.

Although the devices to be discussed have been developed especially for use with portable tape recorder or record player motors and for similar equipment used in road vehicles, they can also be used to regulate the speed of any small DC motor. Indeed, they can be used in applications not involving motors where one requires a voltage source which increases in value with the current taken from the output. However, care must be taken to ensure that the maximum permissible output current is not exceeded.

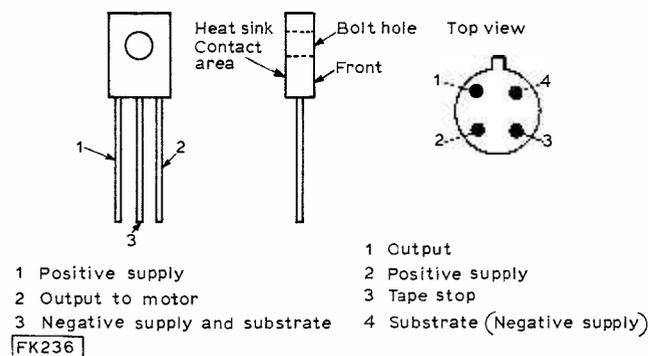


Fig. 1: Packaging and pin connections.

### Types

The TCA900 and TCA910 devices are encapsulated in a plastic package of the type shown in Fig. 1; this is known as the TO-126, SOT-32 or CB-16 package. The rear metal face of this package is designed so that it can be clamped to a heat sink if necessary.

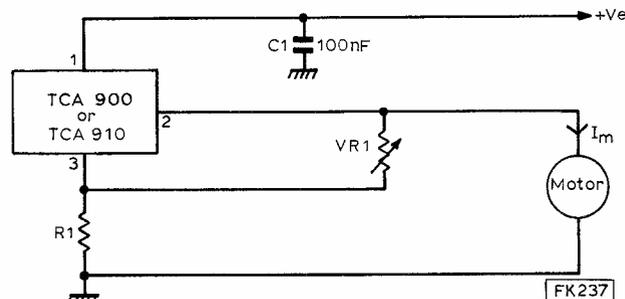


Fig. 2: The basic control circuitry.

The TCA900 and the TCA910 have different operating voltages. The TCA900 must not be used with a supply voltage above the absolute maximum limit of 14V or it may be damaged; this device is especially suitable for controlling the speed of motors in portable cassette players operating from power supplies in the range 5.5V to 12V. (The operating voltage should always be somewhat less than the maximum permissible value). The TCA910 has the higher absolute maximum voltage rating of 20V and is suitable for use with motors operating from supplies of up to 18V. For example, equipment in a vehicle operating from the nominal 12V (which can rise during charging) should use the TCA910.

The ESM900 and EM910 devices are rather similar electrically to the other two types, but incorporate a circuit for automatically stopping the motor at the end of a tape when the conducting aluminium foil at the end shorts a pair of stop contacts in the tape transport mechanism. The ESM900 has an operating voltage range similar to the TCA900, whilst the ESM910 has the same operating voltage ratings as the TCA910.


The ESM900 and the ESM910 are encapsulated in the TO-12 type of package shown in Fig. 1; it is a circular metal transistor-like package with four leads, the additional lead being used for the tape stop contacts. If no heat sink is used, the package of Fig. 2 can dissipate a maximum of only 0.5W at ambient temperatures up to 60°C, whilst the plastic package of Fig. 1 can dissipate up to 0.8W at ambient temperatures up to 70°C without any heat sink. The plastic package can dissipate up to 3.3W with a heat sink of thermal resistance 15°C/W at ambient temperatures up to 70°C.

### Circuit

The circuit for use with the TCA900 and the TCA910 is shown in Fig. 2 and is striking for its simplicity. The speed of the motor can be adjusted by means of VR1 which should normally have a value of between 2kΩ and 5kΩ. The maximum output cur-

Continued on Page 606
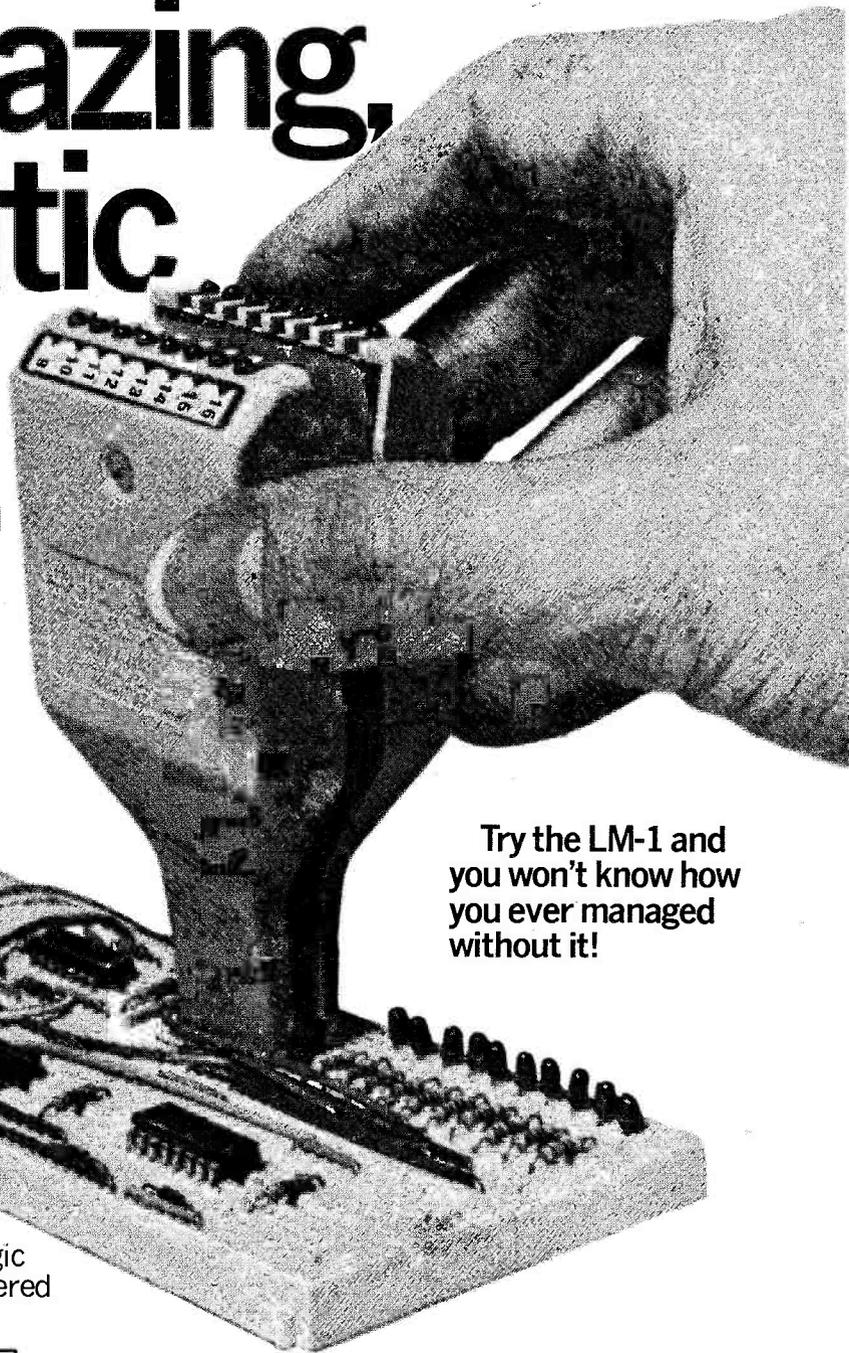
# The amazing, automatic Logic Monitor LM-1.




Just clip it over your IC.  
It instantly and accurately shows both static and dynamic logic states, on a bright, 16-LED display.  
It finds its own power.

It cuts out guesswork, saves time, and eliminates the risk of short-circuits.

LM-1 is suitable for all dual-in-line logic ICs; DTL, TTL, HTL, CMOS; up to 16 pins.

LED on = logic state 1 (high), LED off = logic state 0 (low), and each LED is clearly numbered 1 to 16 in the conventional IC pattern.

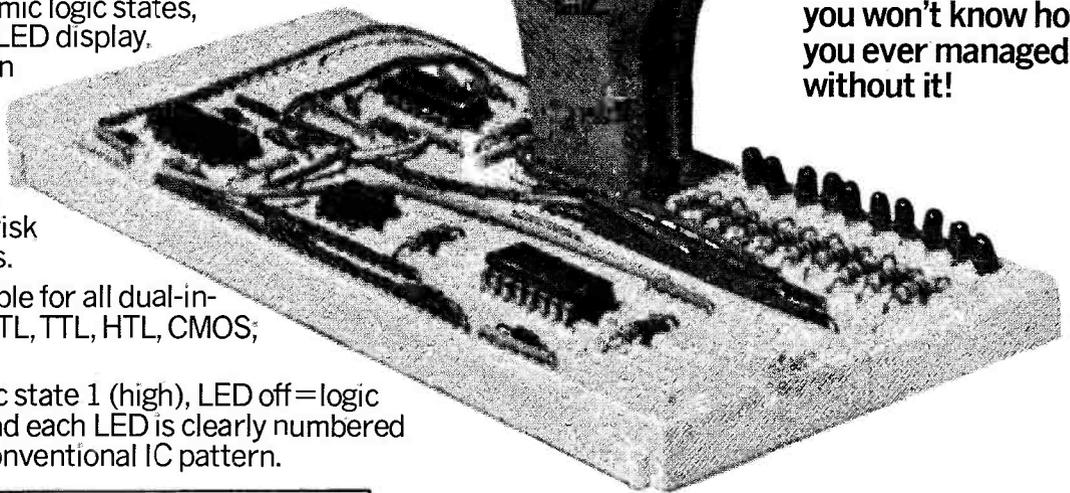Try the LM-1 and you won't know how you ever managed without it!



## Brief specification

Input Threshold	2V ± 0.2 volts.
Input Impedance	100,000 Ohms
Input Voltage Range	4 volts minimum 15 volts maximum across any two or more input leads
Maximum Current Drain	200 mA @ 10 volts
Maximum Input Frequency*	10,000 Hz 50% duty cycle
Operating Temperature Range	0°C to 50°C
Weight	3 ounces (85 grams)
Maximum Dimensions	4.0 x 2.0 x 1.8" / 102 x 51 x 45 mm

\*LM-1 will respond to signals up to 0.1MHz when the input signal swing exceeds the threshold voltage by more than 0.5 volts.

## Applications

Design, breadboarding, testing and checking new logic systems.  
Direct real-time monitoring of logic function in operating equipment.  
Long-term testing of individual ICs.  
Identification of unused elements, to find room for an extra gate, clock etc.  
Observing relationships between ICs on different boards of multiple board systems (you need more than one LM-1 to observe simultaneously, of course).  
Plus dozens of other uses. You'll find them.

## It's Easy to Order

Ring us (01-890 0782) with your Access, Barclaycard or American Express number and your order will be in the post that night.  
Alternatively, send a cheque, or postal order (don't send credit cards!) and it still only takes a few days.  
Otherwise ask for our complete catalogue.

# ONLY £28.70

Plus 8% VAT, plus post and packaging, total £31.50, including box and instruction manual.

CONTINENTAL SPECIALTIES CORPORATION



CONTINENTAL SPECIALTIES CORPORATION (UK) LTD., SPUR ROAD, NORTH FELTHAM TRADING ESTATE, FELTHAM, MIDDLESEX TW14 0TJ. TELEPHONE: 01-890 0782.  
REG IN LONDON: 1303780 VAT NO: 224 8074 71 \*TRADE MARK APPLIED FOR ©CSC (UK) LTD 1977. DEALER ENQUIRIES WELCOME TELEX: 8813669 CSCLTD.

rent from any of the devices under discussion is 0.5A. The voltage between pins 1 and 2 should not be less than about 1.5V, as the drop-out voltage between these terminals at which correct operation ceases is typically 1.2V. The capacitor C1 provides the normal power supply decoupling at high frequencies which should be used with all types of linear integrated circuits.

The value of R1 should be about 8.5 times the resistance of the motor, but a higher value of R1 may result in oscillation. A lower value of R1 will result in the speed regulation being impaired when variations in the mechanical load imposed on the motor occur. Typical values for R1 are in the region of 100 to 400Ω.

## Tape Stop

The circuit for the use of the ESM900 and the ESM910 is shown in Fig. 3. The pin connections differ from those of Fig. 2 and a stop switch is shown. The typical current which must pass between the contacts in the tape transport mechanism to stop the motor is 2mA; the motor starts again when the

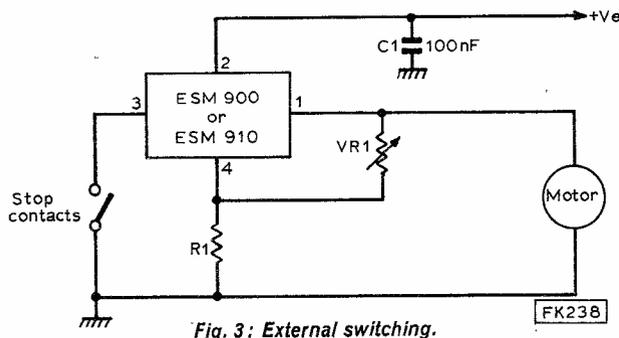


Fig. 3: External switching.

aluminium foil at the end of the tape is removed from the contacts. This stop mechanism may be used for other purposes when a motor must be stopped.

The value of R1 in Fig. 3 should be about 10 times the resistance of the motor, but otherwise the performance is almost identical with that of the other two devices of Fig. 2.

## Conclusion

One may regard these devices as over-compensated voltage regulators. The voltage supplied to the motor is not merely kept constant as the load current increases, but actually increases with the load current.

The devices are available from Phoenix Electronics Ltd., 46 Osborne Road, Southsea, Hants., PO5 3LT, and other advertisers in PW.

## DESIGN YOUR OWN PROJECTS—continued from page 603

is the ratio of the load resistance to the impedance in the emitter so for a gain of ten we want, to be on the safe side, the AC impedance at the collector to be about 200Ω. We already have  $25/I_e = 25\Omega$  internally which we mentioned earlier, so 180Ω in series with a capacitor should be fine (see Fig. 6). As for the value of the capacitor, we want its impedance to be small compared with the 180Ω for the lowest frequency at which we want the circuit to operate. If we take this frequency to be 30Hz, and say that the

impedance should be about 20Ω at 30Hz then we have, using the expression for the impedance of a capacitor,

$$X = \frac{1}{2\pi fC}$$

$$20 = \frac{1}{2\pi \cdot 30C} \quad \text{so} \quad C = \frac{1}{1200\pi}$$

so a value of 250μF should be adequate.

Now for a check of the input impedance of the circuit. This is given by the input impedance of the transistor in parallel with the bias network. We said before that the transistor's input impedance is  $h_{FE} \times R_e$ .  $h_{FE}$  for the BC109 should be at least 200, so this becomes 40kΩ. Now 40kΩ in parallel with 64kΩ (the bias network) will give a value well over the 20kΩ required by the specification, so we're OK here. We can easily allow C1 to have a value of 2kΩ at our

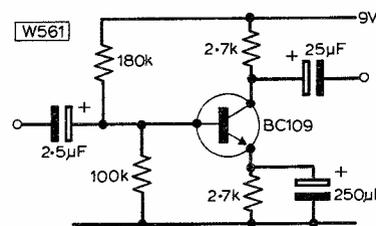


Fig. 7: The completed circuit of the matching amplifier.

low frequency limit, so anything over about 2.5μF should be adequate. At the output it seems reasonable to let C2 have an impedance of about 20Ω at 30Hz so this gives  $C2 = 25\mu F$ . The final design is shown in Fig. 7.

## BOOK REVIEW—continued from page 593

the degree of detail to present to the reader. Or even who his readers are. In one glib breath he talks about "four dual-rank master/slave flip-flops internally connected to provide separate divide-by-two and divide-by-five counters." In another he describes a bottle of nail varnish for marking unknown ICs: "Partly serviceable devices are always handy for experimental work, and it is a good plan to mark them so that the good sections are easily identified. Coloured nail varnish is ideal for this purpose. It comes in bottles complete with a little brush for immediate use, and quickly dries." It could have been safely assumed that even the most butch amongst the potential readership would know all about the properties and packaging of nail polish.

The author is pedantic in detail yet leaves yawning gaps in useful information. Accepting that the book is intended to deal more with devices than Boolean algebra and system organisation, it gives virtually no mention of logic families other than the 74 series. Of these it deals only with simple gates, flip-flops (JK type), a counter, Schmitt trigger and a line decoder (for driving Nixie gas tubes). It mostly fails to do justice to this limited repertoire; from simply reading the book, one would never learn about shift registers, adders, latches and the exclusive OR. Never mind compounded functions within LSI packages (remember that the book is supposed to be about hardware). As for C-MOS, who ever heard of it anyway?

As reviewer, I could take issue with the few design circuits that the author has provided. I could get bitchy about unnecessary chapters such as the one concerning the salvaging of unidentified ICs from gash equipment. I could make unpleasant noises about the lack of useful chapters, or even useless ones (76 pages for 95p). However, I won't. I will simply say that it's a tough job writing about logic devices—or anything—for beginners and that the author simply isn't up to it.

Frank Ogden





## SUPER TOUCH SENSITIVE PIANO

ALL THE CHARACTERISTICS OF A REAL PIANO HAVE BEEN POSSIBLE WITH ELECTRONICS

- Featuring:—Pianissimo and Fortissimo playing technique
- Natural speaking time—higher notes have shorter sound and the lower notes have longer sound.
- Higher notes have slightly louder sound than the lower notes.
- Perfect key up and key down effect of a real piano. When a key is depressed and held down the sound decays slowly, and when the key is released the sound decays rapidly.
- Loud and Soft Pedal:—When the loud pedal is depressed and the note is played and released the sound decays slowly, but when the loud pedal is released the sound decays instantly.

ALL THIS MAKES OUR ELECTRONIC TOUCH-SENSITIVE PIANO THE FINEST IN THE WORLD.

Complete kit price **£199** carr. £6, plus £25.62 VAT.



## MAYFAIR MK II ELECTRONIC ORGAN

Specification: 11 voices, 4 pitches, sustain, upper & lower 4 octave split keyboard

Complete kit price **£175** carr. £6, plus £22.62 VAT.

THE ORGAN MANIACS WILL BE AROUND FOR 100 YEARS!

To enable us to keep our prices low our advertisement will not be appearing as regularly.

We are the only London stockists for keyboards, pedal boards, consoles, key-contacts, stop switches, organ i.c.'s, and all specialised components for electronic music.

**ORGAN AND PIANO KITS:** To maintain our success we will only sell professionally designed and 100% proven kits.

Our organs and pianos can be purchased from most music stores as we are now supplying to the trade.

Sorry no catalogue at present, if you are keen visit our showroom without obligation.

Now available from stock. Mayfair Mk II Electronic Organs ready built £285 inc. VAT plus carr. £6. Hurry, send your order to-day.



**ELECTRONIC MUSICAL INSTRUMENTS**

12 Brett Road, Hackney, London E8 1JP

Tel: 01-986-8455/986-5063

Component Shop: 40a Dalston Lane E8 2AZ

Tel: 01-249-5624

## J. BIRKETT

Radio Component Suppliers

25 The Strait, Lincoln LN2 1JF Tel: 20767

NKT214 PNP TRANSISTORS SIMILAR TO OC71 at 10p, 6 for 50p.  
 100-0-100uA TUNING METER  $1\frac{1}{2} \times 1\frac{1}{2}$  at 90p.  
 50 ASSORTED TANTALUM BEAD CAPACITORS from .33uF to 15uF @ £1.50.  
 MINIATURE 2 POLE 4 WAY ROTARY SWITCH @ 20p.  
 ELECTRET MICROPHONE INSERT with FET Pre-Amp @ £1.85.  
 PHONO SOCKETS Single @ 5p, Double @ 10p, Triple @ 15p, Quad @ 20p.  
 NPN SILICON PHOTO TRANSISTORS @ 15p, PHOTO DARLINGTONS @ 22p.  
 50 AC128 TRANSISTORS Branded but Untested @ 57p.  
 30 AF117-OC170 TYPE TRANSISTORS Untested @ 57p.  
 500 yd REEL OF PVC CABLE 25 Strand .004 for £3.  
 2 PIN DIN SOCKETS Single @ 10p, Double @ 18p.  
 MAINS PUSH ON PUSH DPT SWITCH Less Knob @ 15p.  
 UNMARKED GOOD BFV5 TRANSISTORS at 6 for 57p.  
 RCA CA3089 FM I.C. at £1.40.  
 TEXAS THYRISTORS TIC 47 200 PIV 300mA @ 18p each.  
 OPTO ISOLATORS TYPE IL-74 with data @ 50p.  
 100 MULLARD C280 CAPACITORS Assorted for 57p.  
 RCA PNP 3 Watt TRANSISTORS 40410 at 18p. each.  
 POWER TRANSISTORS MP8112 @ 15p, MP8113 @ 15p.  
 AUDIBLE ALARM SYSTEM For Car Seat Belts with Transistors and I.C. No details at 75p.  
 50 BC107-8-9 TRANSISTORS Untested for 57p.  
 MULLARD LP1186 VARI-CAP FM FRONT END @ £4.85.  
 BD187 4 AMP NPN POWER TRANSISTORS at 25p, 5 for £1.  
 5.5 MHz CERAMIC FILTER at 27p each.  
 100 MINIATURE SILICON DIODES BA Series for 57p.  
 10 x 10pf DIFFERENTIAL AIRSPACED TRIMMER @ 22p.  
 20 ASSORTED VARI-CAP DIODES Untested for 45p.  
 CRYSTALS 10X TYPE 5 MHz @ 50p, 10XAJ 600 KHz @ 50p, 7 MHz @ 60p, 8 MHz @ 60p.  
 30 ASSORTED 10XAJ TYPE CRYSTALS @ £1.10.  
 20 ASSORTED FT 241A CRYSTALS 72 to 96 MHz @ £1.10.  
 SOLDER-IN FEED THRO's 6.8pf, 300pf, 1000pf @ 20p doz.  
 TO39 NPN 5 WATT DARLINGTON TRANSISTORS @ 20p each.  
 ZN 414 RADIO I.C. With data @ £1.  
 250pf SOLID DIELECTRIC VARIABLE For above @ 33p.  
 50 VOLT SUB-MINIATURE DISC CERAMICS 22, 27, 100, 150, 1000, 2200pf, .01uF. All at 20p doz.  
 BCX36 or BCX37 TRANSISTORS at 8 for 50p.  
 UNIJUNCTIONS T1543 @ 20p, MEU21 @ 22p, 2N4871 @ 22p, MU 4894 @ 22p, 4JD5E29 @ 22p.  
 VHF POWER TRANSISTORS Unmarked 2N3866 at 3 for 75p, 2N3553 at 3 for £1.10, 2N3375 @ £1 each.  
 CAMBION R.F. CHOKES 22uH. @ 5p each.

VHF TEST SET type 210 provides RF O/P over range 20 to 88Mc/s in 4 bands, approx. 10 Mill/v O/P CW or pulse mod at approx. 30Kc. Also contains noise generator with 50Ma meter, 2 Mc/s int. calibrator. These units have int. p.u. but this is not suitable for 50c/s (req. 250v ht & 6.3v). Supplied in case with ae rods, cal. charts circ. & notes £10.80. **PANEL METERS** all new American surplus 100Ua scale 0 to 100, 2" dia. £3. 1 Ma scale special marked yell, green, yell., 2" dia. £1.30. 200 Ua scale special marked red, green red, 2 1/2" dia., £1.70. 500-0-500Ua scale special marked lead & lag, 1 1/2" dia., £1. 150-0-150Ua scale plain with ct mark, 2 1/2" dia., £2. 200v FSD scale marked reflex volts, 2" dia., £2. 500 Ua scale marked 0 to 5Kv linear, 2" dia., £2. **VALVE TESTER** adaptors Mx 949, for use with 1-177 American valve testers, will extend range of this tester to include B9a & L.p. Tx types with circ., £5.40. **BATTERIES** sealed rechargeable lead acid 6volt by Dryfit, two sizes, 1.8 A/HR, size 2 1/2 x 2 1/2", £5.40 & 2.6 A/HR, size 5 1/2 x 1 1/2 x 2 1/4", £6.50 both new. **SOLID STATE** power swt opto coupled control 5 to 15 volts dc, with handle 240v at 5 amps or 13 amps on heatsink, okay for sound to light units, £2.40. **HEATERS** tubular flat 240v, 150w, approx. size 6 1/2 x 10", were used for film drying, new £1.50. **CRYSTALS** mixed 10x & 10xj types in range 4 to 8 Mc/s, 20 for £2.20. **STANDARD** crystal dual 100Kc & 1 Mc/s in 10X case with suggested circ., £2.80. **TEST SET** 501 portable unit contains meter 50Ua, will measure res., volts to 250 & 1Kv. in case with battery holder, etc., £5.40 **WIRE** flex insulated, okay for aerial wire 25 m, for 85p. **TUNING COND** dual gang 240pf per section, air spaced ceramic insl. & shaft, suitable LP Tx shaft, size 3/4 x 7/8", new £2.50.


Above prices include carr./postage & Vat.

SAE for list 18 or enquiry, goods ex. equipment unless stated new.

Shop open Tues. to Sat.
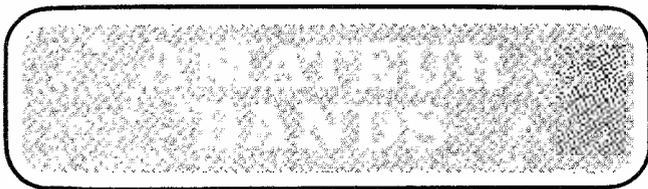
## A. H. SUPPLIES

122 HANDSWORTH RD., SHEFFIELD S9 4AE Ph. 444278 (0742)



by **Eric Dowdeswell G4AR**

It will come as a surprise to readers to learn that *PW*, with certain other magazines of the Practicals Group, is moving to Poole, Dorset, in the very near future, together with a new Editor. Yours truly will not be going with them but I hope to continue the column as an outside contributor. So do keep writing to me, at my home QTH.

Reports are rather scarce again this month, so far. I am off to Greece for a couple of weeks and I hope to be able to squeeze in some more news at the end, from the letters that will have arrived in the meantime. We start off with **Nick Smith** (Leamington Spa), who first wrote in 1975 but who has obviously learned a lot since then! His trusty Bush valved radio has finally given up the ghost so he is looking for something a little more sophisticated. What better source of ads than Short Wave Mag or Radcom OM? The price bracket is £20-£30, so if you can help Nick drop him a line at 59 Wellington Road, Lillington, Leamington Spa.

**Michael Walker**, aged 15, is full of praise for the White Rose Radio Club up in Leeds and enjoyed getting his hands on some exotic gear at one of the Field Days. He will have started on his RAE course by now, so good luck, Michael. One year older **Tom Higgins** of Letterkenny, Co. Donegal, says he found the column "inspiring" and has been listening now for about a year and he too hopes to take the RAE when he can find time away from his regular studies. At the moment he has a home-brew TRF set but his problem is getting a decent aerial up, plus TV QRM. A shorter aerial, well away from the TV set, might be an answer OM.

Yet another young man who should now be in the throes of swotting for the RAE is **Robin Bayley**, in Kemberton, Salop. He has just passed an electronics exam at the local college which ought to be a good start towards getting a ticket. He still finds time to look around the HF bands. FP8 and HK0 can't be bad on 80m in the summer! Regular log-sender **Brian Harrison** tells me of a new club just formed in Hastings, using the call G6HH, the first club there, apparently, since the '30s. If you want any more info then you'd better write to Brian at 99 Farley Bank, Hastings, Sussex. Brian stuck to SSB on 10, 15 and 20m. He found a new prefix on 15m in the form of P29JS, better known as New Guinea. A51RG in Bhutan is a very rare one indeed so let's hope it turns up trumps with a QSL!

**CLUB NEWS** The first issue of the *Edinburgh and District ARC's* newsletter "Ham News" looks good and the club has many interesting events coming up. Meetings

Tuesday nights at the high spot of Edinburgh, the club-room of the Edinburgh Astronomical Society, at 1930 hrs. President **Norman King** has just passed his RAE so hopes to be active soon while the call GM4HAM has been reserved for the club and should be issued before very much longer. Secretary is Jim Martin, 22 Ross Gardens, Edinburgh EH9 3BR, telephone 667 8707. Another newly-formed group is the *Brighton and District RS* and their newsletter is also very well produced and printed. Hon. Secretary is **Nigel Hewitt**, G8JFT, of 74 Carlyle Street, Brighton, Sussex. However, I must castigate both Hon. Secretaries for not putting their addresses, or anyone else's for that matter, on their broadsheets! Callsigns are just not enough! The same as the use of "QTHR" in ads always annoys me! It takes a while for newly-licensed people to get into the call books and anyway a callbook is not always to hand. Why not put the town, at least?

Yet another new club is the *Ormskirk ARC*. For the moment meetings are held at members' homes, on Wednesday evenings. They make a point of being on VHF on those evenings from 1930 to 2030 hrs on 145MHz so try to QSO for details or contact **Peter Kay**, G4GCB, at 24 Laurel Avenue, Burscough, Ormskirk, Lancs.

**Paul Farnsworth** of Adlington, Lancs, writes again to say he now has his home-brew set going. It is the design in the May 77 issue of *Radio Constructor*. One problem that comes up time and time again, in correspondence from newcomers to the amateur bands, is whether to buy or build a receiver. Unless the writer is experienced in the construction of electronic gear my answer always is "buy one"! Then a start can be made on listening while the enthusiasm is running hot and there is a fair chance that the newcomer can find the bands quite easily. There is nothing so depressing as spending weeks or even months on making a set and then running into alignment and calibration problems. Another bit of advice is never to rely upon the dial calibration of any set, particularly if it is secondhand. If an internal calibrator is fitted all well and good but otherwise an external crystal-controlled calibrator is, to my mind, just as important at the outset as the receiver itself.

Plenty of logs sent to me contain the calls of stations which are obviously outside the ends of an amateur band, because the user has relied upon the dial calibration. In some cases, of course, the stations concerned are rightfully using a shared band and only experience aided by a prefix list can sort this matter out. A suitable calibrator starts with a 1MHz crystal with dividers down to 100kHz, and 25kHz, or preferably, 10kHz.


## Log extracts

**B. Harrison:**— 20m A51RG DX1PH HZ1BS OF1AJ/OJO (Faroes) 15m KG6JEH P29BB TAI1MB 10m EA9FJ HI8MRF LU2MHG PJ2FR 8R1J (Guyana) 9Y4NP

**R. Bayley:**— 80m A2GCO AP2AD FP8DH HK0COP 40m DU1DBT FP8DX HK0CAT KH6PP 20m VK9XY ZL3AK 15m EA9CR VK6WH

**T. Higgins:**— 80m ZS5LB 40m VP1EDE

All stations were received on SSB.

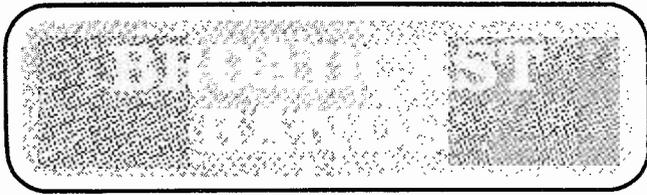

## SHORT WAVE BROADCASTS

by **Charles Molloy G8BUS**

The recent tests on 5925kHz by Austrian Radio (ORF) which have now been completed, have brought some comment from DXers about out-of-band transmissions. It is not illegal, as has been suggested, to operate outside the international shortwave bands. The ITU (International Telecommunications Union) regulations allow out-of-band broadcasting provided no interference is caused and many authorities, including the BBC, make use of this facility. There is incidentally, an interesting in-band programme from ORF on 6155kHz at 1805GMT when Austrian Short-wave Panorama can be heard in English.

The areas beyond the band edges are used, not only by well-established broadcasters but also by countries coming onto the short waves for the first time and looking for space. These areas are interesting places for the DXer to explore. Egypt and Israel seem to concentrate around the band edge as do China and some Eastern European outlets. Stations heard recently by the writer include:

- 5935kHz Riga, Latvia with programmes in Latvian and Swedish at 2020
- 6205 Mebo 2 in Libya, testing with pops in the evening
- 6225 Peking with Chinese music at 2100
- 6230 Cairo at 2045
- 9915 Delhi in English at 2210
- 11620 Delhi in English at 1925
- 11655 Tel Aviv in English at 2000
- 12085 Kuwait in English until sign-off at 2000

Kuwait is also reported at 1930 by **Robin Beyley** from Kemberton, Salop, who uses a Marconi R1475 and long-wire.

Following up last month's request for information on Radiostantsia Rodina, **Charles Hardie**, St Andrews reports hearing this programme on 14200kHz at 2000 using his JVC portable radio/TV which has a telescopic aerial. Charles asks about a peculiar sound, almost like a machine gun, on and around 7MHz and 9MHz. This noise is over-the-horizon shortwave radar coming from somewhere in Eastern Europe. It jumps about in an unpredictable way and is believed to be linked to ionospheric sounding equipment in such a way that the radar automatically operates near to the critical (penetration) frequency so that optimum propagation is obtained. This type of transmission is contrary to the ITU regulations and it has led to a number of international protests. If it continues and is copied by other countries then it will eventually put an end to all international broadcasting on the short waves.

**Tony Cook** writes from Gibraltar to say that he keeps his HAC radio permanently tuned to Radio Nederland because their programmes are so good. DX reported by Tony covers Peking on 9100kHz at 2030, Johannesburg (Radio RSA) on 9585 at 2030 and Jerusalem on 9425 at 2030. **Roy Patrick** (Mackworth, near Derby) has a Trio 9R59D communications receiver and a Joystick antenna with which he pulled in the Voice of Kenya on 4915kHz in the 60m band, Budapest in English on 5955, Malta Calling on 5990 on Saturdays at 2045, Ankara on 9515 in English at 2200, Lisbon 9740 in English at 2030, Israel on 11655 in English at 2200. Roy mentions that he does quite a lot with Latin Americans on 60m during the winter and reports of this would be of interest to readers.

**Simon Hicks** writes from Swindon to say that Radio Nederland will be altering their format from 90 to 50 minutes on November 7. Full details of the times and the frequencies in use are obtainable from Radio Nederland, PO Box 222, Hilversum, Holland. Simon gives news

of a new 90 minute programme from Radio Finland which is on the air on Sundays at 1325 GMT on 11755kHz for Europe and 15105 for North America. A DX programme is included in this transmission.

November is the first month of the winter season on the short waves as many international broadcasts will be on new schedules and there will be changes of frequencies. The four seasonal schedules issued by the International Frequency Registration Board (IFRB) of the ITU are:

November schedule, for the period November to February.

March schedule, March and April.

May schedule, May to August.

September schedule, for September and October.

Thus there are two periods of four months and another two periods of two months when changes may occur. Although some countries do not change at every period the majority do change. Up-to-date information is to be had for the asking from most stations and DXers need not be put off if the station's address is not announced over the air. Radio Finland, Helsinki, Finland will certainly find this station even although the full address is PO Box 528, Helsinki 10.

News of activity on the 11m band (25605kHz to 26095kHz) comes from St Leonards-on-Sea where **Harold Brodribb** picked up Tel Aviv in Hebrew on 25065 between 1430 and 1540GMT using his CR100 receiver and an outdoor aerial. A number of Italian speaking stations, probably Citizens Band, were heard around 27MHz indicating that the higher frequencies are gradually picking up again. This is the first report of a logging on 11m for some time.

A letter from **R. J. Irvine**, Birmingham, asks if a varicap is the same as a variable capacitor. No it is not the same, but it does the same job by providing a capacitance that is easily adjustable and therefore can be used for tuning. The traditional variable capacitor is a mechanical device that has a spindle attached to a set of moving vanes. When the spindle is rotated one way, the moving vanes mesh with a set of fixed vanes to increase the capacitance between them. Turning the spindle the other way will decrease the capacitance.

A varicap is a semiconductor variable capacitor. It is really a reverse-biased diode whose capacitance depends on the value of the bias voltage. The latter is applied to the varicap by means of a potentiometer, and the combination of the two provide a convenient means of tuning a receiver when space is limited.

In the July issue of PW, **John McFadden** asked if it is possible to hear Latin American stations working with less than 1kW. **Harold Buggins** (Cowley) has a verification letter from HHCN Port au Prince, Haiti at the time when they were using 150W on 5660kHz and also a QSL card from PZH5 Paramaribo, Surinam, when it was on 5945kHz with 300W. Are these really LATIN Americans? One is French speaking and the other Dutch!

Harold has been DXing on and off since 1939 and he recalls how he won a prize of two pounds of coffee beans from TGWA Guatemala in 1940 for being the most distant listener to one of their programmes. Every Latin American country has been verified except Bolivia which is still on the wanted list.




## MEDIUM WAVE DX

by **Charles Molloy G8BUS**

A new station in Newfoundland is reported by **Alf Cosham** who lives in Steyning in Sussex. Listening on approximately 620kHz with his Trio 9R59D receiver and 75ft longwire at 0520 on September 8 he heard the call CJYQ

# THE DYNAMIC DUO

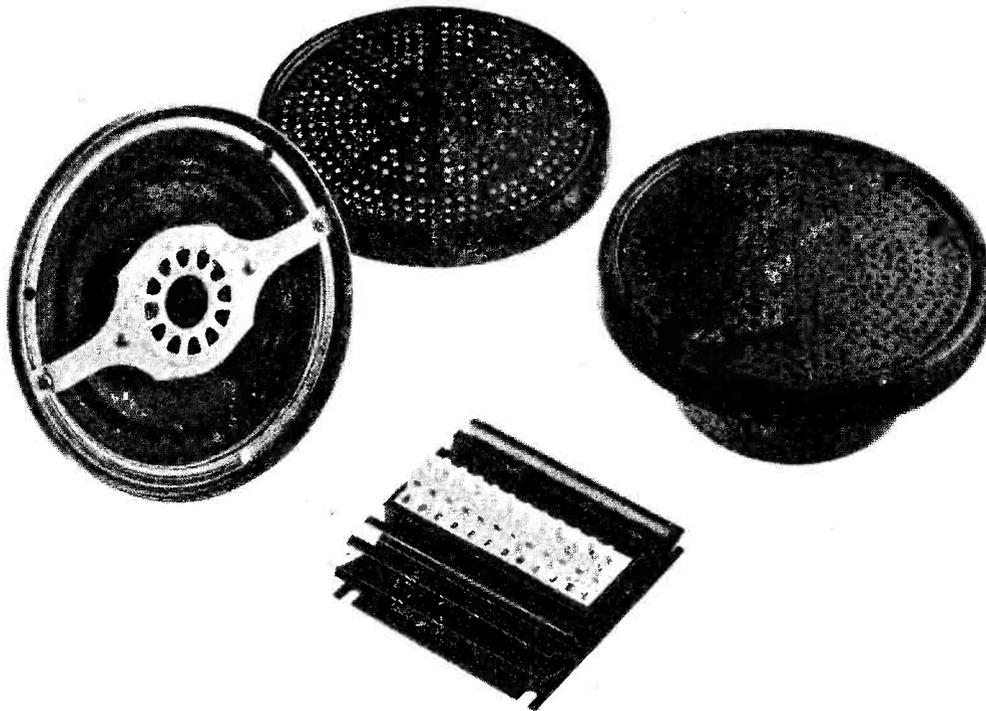

The C15/15 is a unique Power Amplifier providing Stereo 15 watts per channel or 30 watts Mono and can be used with any car radio/tape unit. It is simply wired in series with the existing speaker leads and in conjunction with our speakers S15 produces a system of incredible performance.

A novel feature is that the amplifier is automatically switched on or off by sensing the power line of the radio/tape unit hence alleviating the need for an on/off switch.

The amplifier is sealed into an integral heatsink and is terminated by screw connectors making installation a very easy process. The S15 has been specially designed for car use and produces performance equal to domestic speakers yet retaining high power handling and compact size.

**C15/15**  
 15 Watts per channel into 4Ω  
 Distortion 0.2% at 1KHz at 15 watts  
 Frequency response 50Hz - 30KHz  
 Input Impedance 8Ω nominal  
 Input sensitivity 2 volts R.M.S. for 15 watts output  
 Power line 10 - 18 volts  
 Open and Short Circuit protection  
 Thermal protection  
 Size 4 × 4 × 1 inches

**Data on S15**  
 6" Diameter  
 5½" Air Suspension  
 2" Active Tweeter  
 20oz Ceramic magnet  
 15 watts R.M.S. handling  
 50 HZ - 15KHz frequency response  
 4Ω Impedance

C15/15 Price £17.74 + £2.21 VAT P & P free

S15 Price pre pair £17.74 + £2.21 VAT P & P free

**TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS**

**I.L.P. Electronics Ltd.,**  
**Crossland House,**  
**Nackington, Canterbury,**  
**Kent CT4 7AD.**  
**Tel. (0227) 63218.**

Please Supply .....  
 Total Purchase Price .....  
 I Enclose Cheque  Postal Orders  Money Order   
 Please debit my Access account  Barclaycard account   
 Account number .....  
 Name & Address .....  
 Signature .....



and a reference to Newfoundland. Alf was probably listening to CJOX Grand Bank Newfoundland on 610kHz which is part of the CJON network. The 'CJON Radio Service' is a network of stations in Newfoundland centred on the 50kW CJON 930kHz in St John's. Others, in addition to CJOX are CJNW Musgravetown on 670, CJCN Grand Falls on 680 and CJCR Gander on 1350kHz. A station at St Anthony is under construction according to the World Radio Handbook but no frequency is given. Unfortunately, this mini-network often carries a single programme and the announcement will either be 'CJON Radio Service' or a list of the calls of the members of the network. All this is very confusing to the DXer. Probably CJYQ is the new station at St Anthony but it might be a change in callsign of one of the members of the network.

Another chain of privately owned stations with VOCM in St John's on 590kHz as the key station, includes CHCM in Marystown on 560, CKCM Grand Falls on 620, CKVO Clarenville on 710 and CKGA Gander on 730 and this network, too, sometimes carries a common announcement. The CBC is represented by CBT in Grand Falls on 540kHz right at the bottom of the band, CBN in St John's on 640, CBY in Corner Brook on 990 and a real challenge to the DXer, CBG in Gander on 1450 with only 250W.

Newfoundland is a fascinating place for the medium wave DXer. The majority of the stations mentioned here, including CBG, have been logged in the UK. There are others as well including two religious outlets with the old V prefix, VOWR on 800 and VOAR on 1230kHz, both in St John's. Finally, there is an AFRTS outlet at the US base in Argentinia Bay which transmits with 50W on 1480 and it too has been heard in the UK.

I have always been interested in the medium waveband writes **Malcolm Laugharne** from Oxford who DXes with a Philips portable receiver. "Interference is bad when I use the mains earth and using the ATU I get a lot of whistling." A transistor portable is designed for use with its internal aerial and many of these receivers especially the more sophisticated ones, perform very well on the medium waves as they are. Trouble is inevitable though if an attempt is made to hot-up performance with a longwire aerial, with or without an ATU. Even where an external aerial socket is provided this is usually for use with a car aerial. Overloading and the generation of whistles will occur unless the longwire is very loosely coupled to the receiver via a capacitor of about 5pF. A mains earth may be unsuitable for use with any sort of receiver if the earth wire is long or it is a third conductor as part of the house wiring. Malcolm is thinking of changing to a communications receiver and this is probably the best thing to do if the portable is not living up to expectations.

Is it possible to hear Torshavn, Faroe Island, in the UK and does this station have English programming, asks Malcolm. Torshavn is on 584kHz with a power of 5kW but it shares this channel with high power outlets in Austria, Spain, USSR and Tunisia and also with a 10kW local station in Paris. Torshavn has been logged by the writer at 0715 when it signs on for the day but there is so much QRM that reception is very difficult. The language used is Faroese. A high power station at Torshavn is planned for the new channel on 531kHz which is allocated to the Faroe Island under the new Geneva Plan which comes into operation in the autumn of 1978 and when this comes on the air it will provide an interesting new country for medium wave DXers.

**Derek Taylor** (Preston Lancs) has swapped his DX160 for a Yaesu Musen FRG7. When used along with a 48in loop the new rig pulled in three Latin Americans, Radio Oriental Montevideo in Uruguay on 770kHz at 0144, Radio Margarita, Venezuela on 1020 at 0035 and Radio Litoral also in Venezuela on 1130 plus the VOA relay in Kavalla in Greece on 791kHz at 2000. Two recent QSLs from North America are from WWWE 1100kHz in Cleveland, Ohio, and Radio 1470 (kHz) WLAM which is owned and operated by 'The Great Down East Wireless Talking Machine Company Incorporated'.


Libreville, Gabon, on 1554kHz has been logged and

identified at 2310GMT by **Harold Emblem** who DXes in Mirfield, Yorkshire, with an Eddystone 730 and a medium wave loop. This channel is occupied during the evening by Nice which transmits with a power of 300kW. Once Nice is off the air for the night then the only QRM is from Kaunas in Lithuania which occasionally has an English programme at this time. Libreville signs-off at midnight GMT. Another African reported by Harold is Ougadougou in Upper Volta on 746kHz which sent a QSL in six weeks.

An Eddystone 680 communications receiver and an 80ft longwire with ATU are used for MW DXing by newcomer to the band **S. E. Webb** of Reading. He reports that some of the North Americans heard were so clear at the time that he felt sure they must have been relayed by AFN. Highlights from the log are CHCM Marystown in Newfoundland on 560kHz, WOR New York City on 710, CBM in Montreal on 940, CFRB in Toronto on 1010kHz, WHN New York on 1050, WCAU Philadelphia on 1210 and WMEX in Boston on 1510. From midnight onwards is the time to look for these stations.

A new reporter to this column is **J. Edwards** who lives at Bryn near Wigan in Lancashire. With a Realistic DX160 receiver and a 100ft longwire with ATU, CBNM in Marystown, Newfoundland, was heard on 740kHz, WINS in New York on 1020 and WHAM in Rochester N.Y. on 1180, all between 0130 and 0300. A loop is now under construction. **David Harley** of Chesterfield has not been so lucky. Two attempts to locate CJON on 930 and WINS on 1010 with a homebrew receiver were unsuccessful. "All I got for an early setting of my alarm was an unidentified Spaniard" (or Latin American?). Propagation on the medium waves over the North American path is uncertain. Sometimes reception is good and at other times it is bad with stations inaudible. Try around midnight during the winter and if unsuccessful try again a few nights later. Poor conditions seldom last for long on the medium waves.

The Voice of Peace is back on the air again with tests on 1540kHz and it should be audible in the UK after dark. When it was last operational it could be found with English announcements sandwiched between Mainfingen, West Germany, on 1538kHz and the UK local radio channel 1546kHz. The Voice of Peace will QSL if an International Reply Coupon is enclosed with the reception report which should be sent to PO Box 4399, Tel Aviv, Israel.

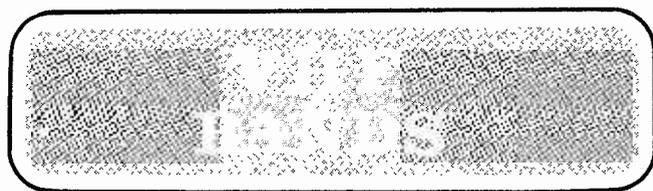

by **Ron Ham BRS15744**

The tropospheric opening on Sunday, September 11, will be remembered for a long time and thanks to the vigilance of our readers, much of the event is herewith recorded for posterity.

It all began around midday on August 27, when, after a period of unsettled weather, the atmospheric pressure went above 30.0in and was still there on September 21 when this report was prepared. By midnight on the 28th the AP was 30.3in and gradually fell back to 30.0in by noon on the 30th. True to form, the VHF's opened up with the higher AP and at 2124 on the 27th, **Alan Baker**, G8LGO, Newhaven, heard PAOCIS and at 2258 on the 28th he had a half-hour, solid copy, QSO with GW8EQH on 2m SSB.

Just before midnight on the 28th, I received 539 signals from both the Emley Moor and Sutton Coldfield beacons on 70cms and at 0015 on the 29th I heard signals via the 2m repeaters in Buxton and the Bristol Channel area. It is worth remembering that the aerial polarity of the repeaters is vertical, therefore I was getting better results on my vertically polarised dipole than I did with my horizontal beam.

During the evening of the 29th, **Ken Smith**, BRS 20001, Horsham, heard several French stations on 2m and G8LGQ worked a couple, heard a GD, and had a contact with GU3JHM/P on Alderney. Around this time both Ken and myself noted the predominant number of French broadcast stations in Band II.

By midnight on Friday, September 2, the AP was rising again just right for the weekend 2m contest, at midday on the 4th it was 30·3in and throughout the day continental broadcast stations were audible in Band II and GB3SUT on 70cms was 539.

The Martlet Contest Group, G4DZO/P, situated on Firle Beacon, near Eastbourne, some 700ft ASL on the South Downs Way, worked 346 contest stations during the 24 hour event and heard well over 400. It is not surprising that the group, comprising of G3XUS, G8LGQ, and recent members of the Cambridge University Wireless Society, were delighted with their efforts when they had EA1CR (923km), northern Spain, several French stations near Andorra, DB5FG/LX/P, HB9AYX and HB9AMH/P among their DX in addition to stations from Germany through to the Channel Islands, southern France to Yorkshire and very strong signals from Cornwall and GW.

These competitors used 150 watts of SSB from an IC201 transceiver plus G8LGQ's home-brew 4CX250B linear, into a 10-element Yagi approximately 45ft AGL.

Before the contest began, **John Branegan**, Fife, heard GM3PLR/P testing on top of Cairngorm mountain and during the event he heard GM4BWT/P, G3FPJ/P Yorkshire, G14COJ/P, and three GWs all with a loft mounted 7-element Yagi. Although John normally gets strong signals from the Angus beacon, GB3ANG, and varying strengths from the Northern Ireland beacon, GB3GI, he uses them, along with his barometer and the Central Scotland repeater, to indicate the prevailing 2m conditions. On August 28, John, using his newly acquired Microwave Modules 2m converter into his FRG-7, heard a contact between G3GZX, Merseyside, and GM3OGJ on SSB as well as G stations working through the CS repeater.

By the end of the contest the AP was down to 30·2in where it remained until 0200 on the 9th when it rose sharply to 30·4in by 1400 and set the stage for the big tropospheric disturbance which accompanied the falling AP on the 10th and 11th.

At 1430 on the 10th, **Pete Simmons**, G3XUS, Newhaven, called **Alan Baker**, saying "There is a lift on, I have worked HB9, do you want one?". As a result, Alan worked HB9MHN/P, Lucerne, and F1KBF in Paris. Pete, only 300 metres from Alan said "Mind your front end I am going after him". Alan heard other HB9s and then joined the queue and eventually worked F1CYO/P near Bordeaux. The signal paths were good down to central France, at 2320, Alan, using 10W, contacted F1ELY, Montrevil, via the FZ2THF repeater (RO 145·600MHz) and at 2334 he worked F9PH, the repeater controller, who was particularly interested in the QSO Alan had a few minutes previously with G2BHW in Cornwall, a distance of 2000km from Newhaven to Falmouth via this Vichy repeater.

The tropospheric influence over VHF/UHF signals expanded rapidly and at 0820 on the 11th, I counted 17 very strong signals from continental broadcast stations between 87-100MHz and by evening Band II, like the 2m band and the TV bands were in total disorder.

Like many others, **Gordon Goodyer**, BRS 37345, Petworth, often lost colour on his UHF TV as the signals fluctuated, and it was this interference that sent Gordon, Cyril Fairchild and several others hurrying to their shacks to look around 2m. Gordon heard amateur stations from the extremes of G, GW, EI, and GM, while Cyril, mainly an HF man, with only a loft ground-plane aerial, heard GM, GU, DJ, F, ON, PA0, and OH, and has never received such strong signals from the Wrotham and French 2m beacons.

The direct paths between PA0 and GW seemed very easy and both ends were also getting into the London repeater with little difficulty. I heard a rock-crushing signal from PE1ABX/M working through GB3LO and PE1AJE via

Reports on the various bands are welcome and should be sent direct by the 15th of the month to:

**AMATEUR BANDS** Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashstead, Surrey KT21 2TW. Logs by bands, each in alphabetical order.

**MEDIUM and SW BANDS** Charles Hally G5EUS, 132 Segars Lane, Southampton, PO6 3JG. Reports for both bands must be kept separate.

**VHF BANDS** Ron Ham BRS15744, Faraday, Greyfriars, Storrington, Sussex RH20 4HE.

GB3SN, with a vertical dipole feeding my receiver. I also heard signals through the Ipswich and Bristol Channel repeaters while G8LGQ worked G and F stations via the Belgian repeater, ON0HT (R2), and at 0123 on the 12th, he had QSOs with Dutch stations via the Antwerp repeater, ON0AN (R8). How many more, like Alan, stayed on the air until past 0400 on the 12th working the strong continental signals which presented themselves on FM, SSB, or via the repeaters? A delighted G8LGQ said afterwards that at 0125 on the 11th he contacted EA1CR, Gijon, and heard the Cornish beacon, GB3CTC, from his home QTH for the first time.

**Joost Berden**, G3RND, Isle of Wight, sent a copy of his barograph chart for the period September 5-11 which compares favourably to mine, he also sent a map of Europe with the area EI to ON and F to GW and north of London ringed, Joost is of the opinion that a great deal of ducting took place within this region. Around 2000 on the 11th, he had solid-copy QSOs on both 2m and 70cms with stations in Antwerp after which he had contacts on 2m with stations in Liverpool, Norfolk, and the Midlands, and points out that his signal was reaching them at 9 plus, but their signals were much weaker with him, while EI9Q was very strong on the back of Joost's 2m beam.


It is not uncommon for beam headings to become less critical during a tropospheric opening as Joost pointed out in his letter; "G3AUS (Exeter) maximum signal on 70cm, changing direction of beam had no influence on his signal". Both the Cornish and Wrotham beacons were 9 plus 20dB (usually S2) with Joost.

During the evening of the 12th the AP rose again sharply and by noon on the 13th it reached 30·5in setting the scene for another VHF opening. As the AP fell on the 14th, I counted 11 continental broadcast stations in Band II and received signals from both GB3SUT and GB3EM on 70cms. At 2200 on the 14th, **Alan Baker** was driving along Brighton sea front and heard GU5MEM/A working a GW via FZ8THF and at 2346 he contacted DD2EK and OE9NHI, from home, via an unidentifiable German repeater.

While our VHF addicts reaped their DX harvest, our solar observers also found life interesting. Both **Cmdr Henry Hatfield**, Sevenoaks, and **John Smith**, Cranleigh, have been watching the progress of several sunspots, optically, since late August. Henry, using his spectrohelioscope, located a small flare on September 9, and a filament on the 15th, and on the 12th he observed the largest sunspot group for three years. Henry, John and myself recorded radio noise, associated with these sunspots, around 136MHz, on August 28, 31, and September 7, 8, 11, 14, 15, 16, 17, 19 and 20. The most intense solar activity was on the 19th which was no doubt responsible for the Delinger type fade out, affecting some HF bands on the same day.

**John Branegan** has now built his own orbital plotter for OSCAR and has found that the down link, with 9 or 10 orbital passes each day, is an excellent reference for comparing home made VHF aerials. At 1148 on August 30 John heard KV4, in Virgin Islands via OSCAR-7 and says that there was a QSL rush after him, I'm not surprised.

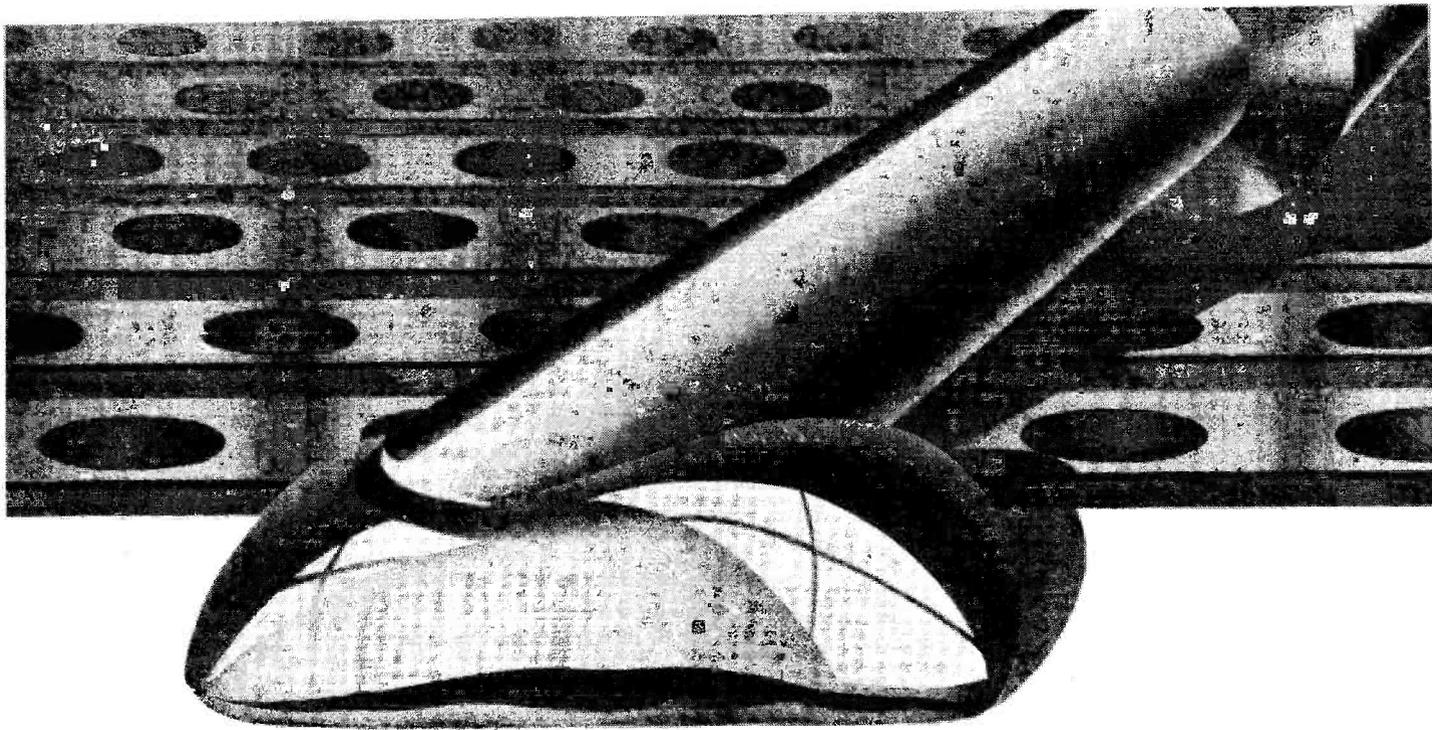Thanks again for your most interesting and detailed reports and I look forward to hearing from you all again in the future.



# The Blob Story.

Yes, they have got a funny name: Blob Boards.

And if you've never heard of them, you might wonder what on earth they're for.

After all they sound more like sci fi than practical electronics.

But in fact there is a good reason for the name.

It actually describes the way these printed circuit boards work. You just put a tiny blob of solder onto circuit board and component and you've made a perfect contact.

Every time.

There are of course a few other printed circuit boards around.

But we think the prices are a bit shocking.

Our prices, we think you'll agree, are more down to earth.

These Blob Boards are about half the price of the few comparable alternatives.

And unlike those alternatives, on most Bandridge Blob Boards you won't have to break the contact rails to make your circuit. So you'll be able to use them again and again.

The roller tinned copper on Blob Board makes soldering easy, and it won't corrode, so


they'll work for as long as you want them to.

You'll find a Bandridge Blob Board for every circuit you'll ever want to make, from the simplest to the most complex.

And if you're using Bandridge solderless DEC's for your prototypes you'll be pleased to learn that there's a Blob Board that exactly matches every DEC.

So when you're looking for a circuit board it'll be worth your while remembering Blob Boards.

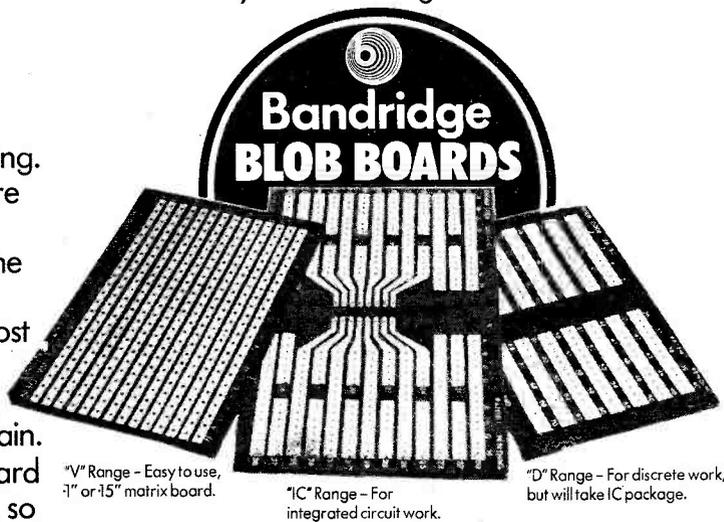As if you'd ever forget a name like that.



"V" Range - Easy to use, 1" or 1.5" matrix board.

"IC" Range - For integrated circuit work.

"D" Range - For discrete work, but will take IC package.



# SAXON ENTERTAINMENTS LTD

## SYSTEM 7000—GUARANTEED MODULES FOR ALL DISCO/PA APPLICATIONS

### POWER AMPLIFIER MODULES 30—240 WATTS



- Fully tested & guaranteed.
- Full RMS Sine Wave output.
- Distortion typically 0.2%
- 10 Transistors, 4 Diodes.
- Response 30HZ-30KHZ.
- Fully short & open circuit proof.
- Sensitivity suits most mixers.
- Built-in surge suppression & compensation.
- Twin D.C. & output fuses.
- Top-grade components throughout.

30 Watts rms	60 Watts rms	120 Watts rms	240W rms
SA308 30W rms/ 8 ohms £9-95	SA604 60W rms/ 4 ohms £13-25	SA608 60W rms/ 8 ohms £14-25	SA1208 120W rms/ 8 ohms £14-95
	SA1204 120W rms/ 8 ohms £14-95	SA1208 120W rms/ 8 ohms £21-00	SA2404 240W rms/ 4 ohms £29-50

### POWER SUPPLIES FOR THE ABOVE MODULES—READY WIRED & FUSED ON GLASS FIBRE PCB

PM301 For 1/2 SA308 £10-90	PM601/4 For 1/2 SA604 £13-50	PM601/8 For 1/2 SA608 £13-50	PM1201/4 For 1 SA1204 £13-50	PM1201/8 For 1 SA1208 £13-50	PM1202/4 For 2 SA1204 £22-50	PM1202/8 For 2 SA1208 £22-50	PM2404/1 For 1 SA2404 £22-50
-------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------	---------------------------------------

### SYSTEM 7000 COMPLETE DISCO MIXERS (With Autofade)

Mono or Stereo



- Ready to plug in & use
- Automatic Mic override
- Two tone panel
- Twin deck & mic & tape inputs
- Left/Right deck fader
- 20Mz-20kHz Noise—77 dB

The choice of the professional D.J.

Controls: Mic volume, Bass, Treble, A/Fade Depth, Tape, L/Deck, R/Deck volumes, Bass, Treble, Master, Headphone volume, Selector & On/Off.

Mono 18v £39-50 Mains £45-75 Stereo 18v £57-50 Mains £63-75

**IN MODULAR FORM**—All you require is front panel (see below) knobs & sockets etc. All electronics are assembled & tested.

- Specification as for complete mixer
- All Potentiometers supplied & fitted
- Low cost do it yourself with step by step easy to follow instructions.

Mono £22-50 Stereo £33-50 Panel £3-95 Supply unit £9-50

### SYSTEM 7000 LIGHTING CONTROL UNIT MK II (Four channel)



Has your light unit got?

- 4,000 W handling
- Sequence facility
- Smart 2 tone panel
- Advanced IC circuitry
- Top grade components
- All your needs in one superbly designed unit
- Integral dimmers
- Automatic audio level
- OURS HAS!

ONLY £44-50

### IN MODULAR FORM—THE QUADRAFECT

£22-50

(Panel £2-95)

As with the mixers the Mk II L.C. unit may be purchased in module form with all controls, requiring only a panel, case & knobs etc. There are 13 simple connections

- 1-240w Audio
- 8A RCA triacs
- 0.5-20Hz Sequence
- Fully suppressed

### CUSTOM MIXER MODULES (Complete or in printed circuit form only)

Make your own mixer, mono or stereo, up to 2 channels, with full monitoring facilities, and provision for echosend/return etc.

- Inputs for low and high 2 mic, ceramic & magnetic cartridge etc.
- Up to 20 input modules per single mixing module
- Feed most types of amplifier—accepts all inputs
- Professional low noise circuitry 20 Hz-30kHz
- Infinitely adaptable—Extremely economical

**COMPLETE MODULES** With facia panel, Knobs & sockets, Monitor buttons, Ready wired & tested

Mono input £8-95 Mono mixing stage £8-95  
Stereo input £12-50 Stereo mixing stage £12-50

- 0-5W headphone circuit
- Full range bass/treble controls
- Noise—80dB

### PRINTED CIRCUIT MODULES

With controls fitted, requires only sockets, facia & knobs

Mono Input £5-95 Mono mixing stage £5-95  
Stereo Input £9-50 Stereo mixing stage £9-50

Power supply for up to 20 channels—PPM18—£8-50.

### SYSTEM 7000 SOUND—LITE (3-CHANNEL)

IN COMPLETE OR MODULAR FORM

(Modular form illustrated)

- Complete unit similar to Mk II unit above
- Long established & proven design
- 3 Channels—100W per channel
- RCA 8A Triacs—Individual channel fuses
- 1-240 W Input—master audio level plus Bass/Middle/Treble

**COMPLETE UNIT**—Fully cased with rear terminations—just plug in & go!

£26-75

**MODULAR FORM** Facia & knobs etc.

Needs only 11 simple connections

£19-75

(Panel £2-95)

### COMPLETE DISCO SYSTEMS

WITH TWO YEAR GUARANTEE—LOW INTEREST CREDIT

FROM ONLY £16-05

DEPOSIT

#### CENTAUR 100W

STEREO

with TWIN LOUDSPEAKERS, SOUND to LIGHT SEQUENCER PLUS DISPLAY.  
£225 + £10 carr. (Dep. £28-80, 12 months at £21-38 or 24 months at £12-01)

#### SUPER CENTAUR 200 W

STEREO

As above but with 200 WATTS OUTPUT & larger TWIN CABINETS.  
£275 + £10 carr. (Deposit £32-80, 12 months at £29-39 or 24 months at £15-21)

#### GXL CENTAUR 200W

STEREO

As the SUPER CENTAUR but with extra large twin 200 WATT CABINETS, DECK LIGHTS, DECK STARTS & SUPERIOR DECKS.

£349 + £10 carr. (Deposit £42-72, 12 months at £36-58 or 24 months at £20-54).

- Cue Light + Head Phone monitoring
- Mic & Tape Inputs
- Crossfade & Override
- Logic Circuitry
- Lightshow
- Complete and ready to use
- Extremely Rugged construction
- Twin BSR Decks



Send today for Free Illustrated Leaflet on Saxon Complete Discos & Package PA Systems.

All Equipment subject to a Two Year Guarantee.

Deliveries in the UK by our own vans.

50W MINI DISCO £139-50 + £5 carr. (Dep. £16-06, 12 months at £13-30 or 24 months at £7-46)  
100W MINI DISCO £159-50 + £5 carr. (Dep. £22-65, 12 months at £14-73 or 24 months at £8-27)

Two extremely compact mono systems complete with loudspeakers and leads.


■ TWIN BSR DECKS ■ HEADPHONE MONITORING ■ MIC INPUT

100W PACKAGE P.A. £145 + £7-50 carr. with twin loudspeakers and PIEZO HORNS  
Dep. £19-70, 12 months at £13-70 or 24 months at £7-73.

SEND YOUR SPECIAL REQUIREMENTS FOR A CUSTOM DISCO QUOTATION

### SYSTEM 7000
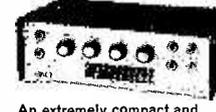
#### MINOTAUR 100—All Purpose Wide Range Amplifier



- 100W rms ± 1dB
- Standard 8 ohm output
- Twin mixed inputs accept a wide range of signals
- 30HZ-30KHZ ± 2dB
- 23dB bass/treble

A four Input, high power amplifier which will deliver up to 150 watts output. An absolute must where multiple mixing & power are required

- Four Individually mixed Inputs
- Wide range bass/treble + master

An extremely compact and versatile amplifier with full protection and a clean, attractive appearance. Ideal for all groups, disco's & clubs

- Vynide covered case
- Fully short proof
- Superb value for money

£49-50

#### SAXON 150 HEAVY DUTY AMPLIFIER

£59-00

### STROBES & PROJECTORS (We stock the full Pluto range) Send for details

#### SUPERSTROBE £22-50

- 2-3 Joules
- 80W Tube for long life
- Compact 4" x 4" x 4"

#### PRO-STROBE £37-50

- 6-8 Joules
- External trigger
- Long Life tube timer circuit



#### 150 WATT LIQUID WHEEL PROJECTOR

- Accepts all accessories
- C/w with wheel & motor plate
- Sturdy steel construction
- Remarkable value—Sold elsewhere at £39-50 Our price is only: £37-50

### ACCESSORIES

Condenser mics ECM77 600 ohm £15-00  
ECM81 Dual Impedance £14-85. Crown headphones £7-50  
Heavy duty boomstand £14-50

All prices subject to VAT @ 8% except SA303/PM301, mics. & headphones (12%)  
Add 50p post & packing on all orders except where already shown.  
Ordering: By Telephone —Access, Barclaycard or COD Ring (01) 684 6385/0098  
By post —Send cheque or crossed P.O.'s or 60p for COD or send in your Access/Barclaycard NUMBER ONLY

327-333 Whitehorse Road, Croydon, Surrey CRO 2HS  
24 House Ansafo service (01) 634 6385

### PIEZO HORNS!!

UP TO 150 WATTS HANDLING.  
NO X-OVER REQUIRED £7-50 ea.

Exporters to 17 countries—enquiries welcomed  
Ring Sue Abegg on (01) 684 6385 for U.K. trade enquiries

# Get a great deal from Marshall's

A. MARSHALL (LONDON) LTD. DEPT. P.W.

LONDON—40-42 Cricklewood Broadway, NW2 3ET  
Tel. 01-452 0161. Telex 21492  
and at 325 Edgware Road, W2. Tel. 723 4242

GLASGOW—85 West Regent Street, G2 2QD  
Tel. 041-332 4133

BRISTOL—1 Straits Parade, Fishponds Road, BS16 2LX  
Tel. 0272 654201

CALL IN AND SEE US  
9-5.30 Mon-Fri.  
9-5.00 Saturday

EXPRESS  
MAIL ORDER  
Tel Orders  
on Credit Cards  
£10 minimum.



## POPULAR SEMICONDUCTORS

2N706	28	2N5294	40	BC178	20	BF167	35	MJE520	45	LM380-8	90
2N708	28	2N5296	40	BC179	23	BF173	35	MJE521	65	LM380N	90
2N1131	30	2N5298	40	BC182	11	BF177	25	MPF102	30	LM381A	2.45
2N1322	37	2N5447	15	BC183L	14	BF178	25	MPSA05	40	LM381N	1.60
2N1711	30	2N5448	15	BC183	12	BF179	30	MPSA06	25	LM382N	1.25
2N2102	60	2N5449	19	BC183L	14	BF180	35	MPSA06	25	LM384N	1.45
2N2218	33	2N5457	32	BC184	12	BF181	35	TIP29A	45	LM388N	80
2N2219	35	2N5458	33	BC184L	14	BF184	15	TIP29C	60	LM389N	1.00
2N2220	35	2N5459	29	BC212	14	BF185	15	TIP30A	40	LM702C	75
2N2221	20	2N5484	34	BC212L	17	BF186	15	TIP30C	55	LM703C	75
2N2222	25	2N6122	41	BC213	14	BF197	17	TIP31A	50	LM709N	65
2N2368	25	2N6122	41	BC213L	16	BF198	18	TIP31C	66	LM710C	60
2N2369	25	2N6123	43	BC214	16	BF200	35	TIP32A	55	LM710N	60
2N3053	26	2N6126	45	BC237	14	BF224J	20	TIP32C	75	LM723C	85
2N3054	60	AC126	45	BC238	12	BF244A	35	TIP41A	70	LM723N	75
2N3055	70	AC127	45	BC239	15	BF245A	40	TIP41C	90	LM741C	60
2N3441	85	AC128	45	BC257	17	BF257	37	TIP42A	80	LM741N	40
2N3442	1.35	AC151	40	BC258	18	BF258	45	TIP42C	1.00	LM741-8	40
2N3702	13	AC152	50	BC259	18	BF259	49	TIP2955	65	LM747N	90
2N3704	15	AC153	55	BC307	15	BF336	38	TIP3055	55	LM748-8	55
2N3706	16	AC153K	55	BC308	15	BF337	45	TIS43	45	LM748N	55
2N3708	13	AC176	50	BC309	15	BF338	48	TIS50	65	LM1800	75
2N3771	1.95	AC176K	65	BC327	20	BF339	28	TIS61	23	LM1808	1.92
2N3772	2.00	AC187K	60	BC328	19	BF340	28	TIS62	45	LM1828	1.75
2N3773	2.90	AC188K	60	BC347	12	BF341	28	TIS88A	40	LM3301N	85
2N3819	36	AD161	1.00	BC548	12	BF379	28	TIS90	20	LM3302N	1.40
2N3820	38	AD162	1.00	BC549	14	BF380	27	TIS93	33	LM3401	70
2N3823	80	AF106	50	BC551	15	BF381	28	LM301A	67	LM3900	75
2N3904	21	AF109	75	BC558	12	BF382	29	LM301N	40	LM3905	1.60
2N4036	67	AF139	69	BC559	14	BF330	39	LM304	2.45	LM3909	68
2N4037	55	AF239	65	BC558	25	BF384	35	LM307N	85	MC1310	1.91
2N4058	20	AF240	1.14	BCY70	25	BF385	30	LM308C	1.82	MC1458	91
2N4059	15	AF279	80	BCY71	28	BF386	30	LM308N	85	NE555	40
2N4060	20	AF380	85	BCY72	24	BF387	30	LM309K	1.85	SN7400	16
2N4124	17	BC107	15	BD115	80	BF388	30	LM317K	3.00	SN7404	16
2N4126	17	BC108	15	BD131	51	BFY50	25	LM318N	2.26	SN7404	26
2N4289	20	BC109	15	BD132	54	BFY51	25	LM323K	6.46	SN7410	20
2N4303	30	BC140	35	BD135	27	BFY52	25	LM339N	1.40	SN7441	1.03
2N4304	1.70	BC141	40	BD136	38	BSX21	32	LM348N	1.50	SN7447	1.10
2N4319	65	BC147	12	BD137	38	BU104	1.65	LM360N	2.75	SN7448	1.10
2N4320	75	BC148	12	BD138	38	BU105	1.40	LM370N	2.50	SN7474	43
2N4321	50	BC149	14	BD139	40	BU126	1.90	LM371N	1.70	SN7490	61
2N4322	55	BC160	35	BD140	40	BU204	2.02	LM372N	1.70	SN7492	61
2N4323	70	BC161	35	BD438	50	BU205	2.50	LM373N	2.80	SN7493	61
2N5086	27	BC167	12	BD439	50	BU206	2.20	LM374N	3.10	SN7495	1.03
2N5192	75	BC168	12	BDX18N	1.70	BU240	58	LM377N	1.75	SN7421	49
2N5193	75	BC169	12	BDY20	1.00	MJE370	60	LM378N	1.41	SN7441	63
2N5245	34	CD177	20	BDY56	1.90	MJE371	60	LM378S	3.95	78023N	1.45

Prices correct at 15 Sept. 1977, but please add VAT p&p 40p

## OPTOELECTRONICS

Full range of Opto devices in our new catalogue



**LEDs**  
3mm Red 19p, Gr 25p, Y 25p  
5mm Red 21p, Gr 25p, Y 25p  
TL209 19p, ORP12 84p  
BPX 25 1.65

## DISPLAYS

7 Segments  
Single Double Display  
DL704 2.00 3.00 0-3in Red  
DL707 2.00 3.00 0-3in Red  
DL747 2.50 3.40 0-5in Red  
DL750 2.50 3.40 0-5in Red

## TRIACS Plastic Pack 400V

6 amp	70	16 amp	1.10
8 amp	75	20 amp	1.70
12 amp	85	25 amp	2.00

## DIACS

ST2 20p  
BR100 48p

## BRIDGES

Full range of Bridge Rectifiers and Diodes listed in new catalogue

## THYRISTORS Plastic C106 116

4 amp 100V	0.35	8 amp 100V	0.43
4 amp 200V	0.40	8 amp 200V	0.49
4 amp 400V	0.49	8 amp 400V	0.62

WHY NOT PAY US A VISIT AT OUR NEW CENTRAL LONDON BRANCH AT 325 EDGWARE ROAD, W2, ABOUT 100 YARDS NORTH OF THE WESTWAY FLY-OVER. EXTENSIVE STOCK RANGE. MANY SPECIAL OFFERS TO PERSONAL SHOPPERS ONLY.

## SPECIALIST CONSUMER

# NEW CATALOGUE

Stocking Distributors Officially Appointed

- NATIONAL ● VERO
  - TEXAS ● ANTEX
  - MULLARD ● ELECTROLUBE
  - SIEMENS ● SIFAM
  - SESCOSEM ● ARROW HART
- MAKES COMPONENTS BUYING EASY

## ORDER NOW!



35p Post Paid or 25p To Callers  
LARGE 32 PAGES packed with over 8500 LINE ITEMS

"What is a microprocessor?"

A complete teach yourself course with cassettes + brochure - £9.95 inclusive of VAT and p&p.

# NEWMART for all your hi-fi needs.

Stockists of: Amstrad · Teleton · Akai · Sansui · Wharfedale · Pioneer · Rotel · Garrard · Connoisseur

## BATTERY ELIMINATORS P&P 25p

240v input, 7-5 or 9v output at 00mA ... £3.25

## CARTRIDGES & STYLII P&P 25p

Acos GP91/3CS (ster. comp) £1.80 £1.20

GP93/1 or 95/1 ster. cryst £2.00 £1.20

GP94/1 or 96/1 ster. ceram. £2.00 £1.20

GP101 cryst. comp. £1.00 —

GP104 ster. ceram. £2.60 £1.20

BSR X5M or X5H cryst. comp. £1.75 £1.20

SX6M or SX6H cryst. ster. £2.25 £1.20

Sonotone 9TAHC or 9TAHC/G (Diam.) 3509 £2.60 £1.20

Audio Technica AT55 £2.25 —

Goldring G850 £3.75 £1.75

G800 £5.50 £1.75

G800E £9.96 £3.75

Shure Cartridges & Stylis M44G/M44C £7.70 £6.20

M55E £9.20 £7.15

M75ED Type 2 £17.15 £12.65

M75EJ Type 2 £14.30 £8.78

M.O. prices only. VAT Inc. Subject to Availability & manufs. increase. Send 30p for Catalogue, Barclay/Access.

Callers Welcome at Manchester 30-32 Shudehill Tel. 061-332 7710. Leeds 4 New Market St. Tel. 0532 42708. Liverpool 15 Whitechapel. Tel. 051-236 0738

## SPEAKERS P&P 85p

EMI 13" x 8", 8 ohm Plain £3.40

8" x 5" C. Mag. 5 watt, 3.8 or 15 ohm ... £2.35

8" x 5" Dualcone 8 ohm, 10 watt ... £3.70

8" x 5" Dualcone 10" Dualcone ... £4.10

Richard Allen 30w 12" 8 or 15 ohm ... £12.20

## MICROPHONES P&P 45

UD 130 50K/600 ohm uni-dir. ball metal ... £8.35

Cassette Stick Mic. with R/Control ... £1.65

Cass. Stick Mic. with R. Control (Philips type) ... £1.93

## CASSETTES P&P 1-3 25p, 4 and over 55p

Low Noise £0.37 £0.48 £0.75

Philips £0.79 £1.08 £1.73

Memorex £0.96 £1.38 £1.90

Cassette Head Cleaner £0.55

Big Head Cleaner De- magnetiser ... £1.99

## TAPES P&P 1-3 35p, 4+ 65p

5" Std LP Cases £0.59 £0.70 £0.32

5 1/2" £0.70 £0.92 £0.38

7" £0.92 £1.19 £0.43

## RECORD DECKS P&P £1.65

GARRARD 355B Belt Drive Chassis ... £26.95

BSR MP60 (P128r) ... £17.35

Plinth & Cover for Garrard, BSR ... £4.95

BD1 Kit ... £17.25

**Random FLASHER UNIT**  
Wired ready for use Complete with three 100 watt coloured lamps that flash independently at random.  
£18.95

**TWIN BANK 6 LIGHT UNIT**  
(less lamps) LENGTH 14 1/2 inches UNIT  
B.C. Fitting £9.55 EACH  
E.S. Fitting £10.35 EACH

**Sound to Light MASTER UNIT**  
600 WATTS PER CHANNEL  
£30.95  
INCLUDING CHANNEL OUTPUT PLUGS AND MAINS INLET SOCKET

**TYPE A SPOT**  
(less lamp)  
B.C. Fitting £1.95 EACH | E.S. Fitting £2.12 EACH

**TYPE B 3 BANK UNIT**  
(Less Lamps)  
B.C. Fitting £6.90 | E.S. Fitting £7.26

**TWIN BANK 12 LIGHT UNIT**  
Length 31 1/2 (less lamps)  
B.C. Fitting £15.60 | E.S. Fitting £17.00

100 WATT SPOT LAMPS RED, YELLOW, GREEN Minimum 3 lamps BLUE CLEAR £1.40 each £4.20  
B.C. or E.S. Fitting

Send 20p for illustrated leaflet & price list

ALL PRICES INCLUDE V.A.T. and POST & PACKING (These prices apply to the United Kingdom only)  
**ALBEN ENGINEERING CO. LTD.**  
DEPT. P.W. THE CRESCENT, WORSTHORNE, BURNLEY, LANCs. Tel. Burnley 20940

# STRIKE YOUR OWN BARGAIN WITH Stirling Sound

**NO EXTRAS TO PAY FOR POSTAGE OR V.A.T.**

**THE SCHEME**  
 Choose from any of the 9 power amplifier (with heat sink if necessary) modules shown in our ad and the Stirling Sound power supply unit best likely to suit. Refer to the published prices (which already include V.A.T. and post free in U.K.) Add the prices together; when you send the money.


**DEDUCT 5%**  
 If you order UNIT ONE at the same time that you order a power amp. and power unit as above, when you send the money for the total order.

**DEDUCT A FURTHER £1.00**  
 If you order UNIT TWO at the same time that you order a power amp. and power unit as above, when you send the money for the total order.

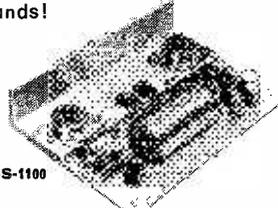**DEDUCT £1.18**

■ Britain's most go-ahead module manufacturers

**CHOOSE THE ITEMS YOU WANT AND BUY THEM THE STIRLING SOUND BARGAIN WAY** whether for a new system, to up-grade what you use now, to build a disco or P.A. outfit, perhaps even a domestic intercom or any other device where an amplifier could be used. Whatever it be, there's a Stirling Sound power amp for it up to 100 watts R.M.S. (+1dB into 4Ω) together with stereo tone control/pre-amps if required. Build with Stirling Sound now! See what you save and hear how good it sounds!



SS-1100

Made in our own U.K. factory and sold direct to you



SS-370

**SATISFACTION GUARANTEED**

**AMPLIFIERS 3 to 100 WATTS R.M.S.**

Ready assembled on P.C.B.s, tested and guaranteed. Easy to connect. With instructions. Output ratings +1dB.

SS.103 Typically 3 watts R.M.S. using 14V/4Ω I.C. amp. Input 100mV **£2.85**

SS.103-3 Stereo version of above, 2 I.C.s **£5.00**

SS.105 5 watts R.M.S. into 3Ω using 13.5V. Sensitivity—30mV. THD—0.3% 3½" × 2" × 1" **£3.95**

SS.110 10 watts R.M.S. into 4Ω using 24V. Sensitivity—60mV. THD—0.3% 3½" × 2" × 1" **£4.65**

SS.120 20 watts R.M.S. into 4 using 34V. Sensitivity—80mV. THD—0.3% 3½" × 2" × 1" **£5.15**

SS.125 25 watts R.M.S. into 8Ω using 50V. Sensitivity—140mV. Distortion—Less than 0.05% into 8. S/N better than 70dB. **£7.25**

SS.140 40 watts R.M.S. into 4Ω using 45V. Sensitivity—300mV. Distortion typically 0.1%. 5" × 3½" × 1½". **£6.50**

SS.160 64 watts R.M.S. into 4Ω using 50V. Sensitivity—350mV. Distortion typically 0.1%. 5" × 3½" × 1½" **£8.50**

SS.1100 100 watts R.M.S. into 4Ω using 70V/2A. Input sensitivity—500mV. Distortion at half-power, typically 0.1%. 5" × 3½" × 1½". **£10.50**

HS.160 Multi-finned heatsink for SS.140 or SS.160. **£0.75p**

HS.1100 Ditto for SS.1100 **£1.50**

**POWER UNITS**

Every unit is tested under working conditions before despatch, and guaranteed. All units except SS.312 include a stabilised low voltage take off point (13-15V) for pre-amp, tone control units etc. Outputs quoted are minimal unloaded ratings.

SS.312	12V/1A	£6.60
SS.318	18V/1A	£6.95
SS.324	24V/1A	£7.65
SS.334	34V/2A	£8.75
SS.345	45V/2A	£10.75
SS.350	50V/2A	£11.75
SS.360	60V/2A	£12.75
SS.370	70V/2A	£14.75

SS.310/60 Stabilised power supply; variable in output from 10V to 50V/2A and short-circuit protected **£17.75**

SS.300 Power stabilising unit variable from 10 to 50V/8A max. for adding to existing un-stabilised supply units. **£5.50**

**UNIT ONE**

Combined stereo pre-amp and active tone control unit. Input sensitivity 50mV for 200mV out. 10-16V operation. Bass ±15dB at 30Hz; Treble ±15dB at 10KHz; Balance control; Volume control. For ceramic p.u., radio or tape inputs. WITH FREE CONTROL PANEL FASCIA. **£9.00**

**UNIT TWO**

With control facilities similar to UNIT ONE but for magnetic cartridge input. Input sensitivity—5mV for 200mV out (can be varied) WITH FREE CONTROL PANEL FASCIA **£12.43**

CONTROL PANEL FASCIA FOR UNITS ONE OR TWO **0.50p**

**SS.100**

Basic active stereo tone control module to provide ±15db on bass at 30Hz and on treble at 10KHz. **£3.00**

**SS.101**

Stereo pre-amp suitable for ceramics, tape, radio, etc. **£2.75**

**WHEN ORDERING**

ALL PRICES QUOTED INCLUDE V.A.T. AND GOODS ARE SENT POST FREE IN U.K. Owing to time between sending our ad. to this journal and the time it appears, prices may be subject to alteration without notice. E.&O.E.

Pay by Access or Barclaycard—Simply let us have your No. Dept PW1277

**Stirling Sound**

37 VANGUARD WAY, SHOEBURYNNESS, ESSEX Telephone (03708) 5543 Shop—220-224 West Road, Westcliff-on-Sea, Essex S0 9DF Phone Southend (0702) 351048


Practical Wireless, December 1977

Improved circuitry and performance standards. More to choose from. Pay by Access or Barclaycard if desired.

<b>To STIRLING SOUND</b>	
Please supply .....	NAME .....
.....	ADDRESS .....
.....	.....
for which I enclose £.....	.....
	PW1277

## INVERTERS

KIT FORM or BUILT UP.

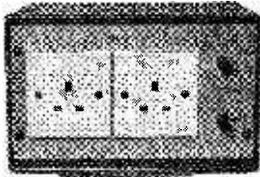


240v-50Hz from your 12v car battery.

O/P Powers available. 25W-40W-75W-150W-300W-400W-500W-1kW-1.5kW. Various battery I/P voltages available.

## AUTOMATIC INVERTERS

These units have built-in battery charger which functions whilst mains are healthy. Upon mains failure unit automatically switches to inverter operation ensuring no interruption of supply. Send S.A.E. for price lists.

## RHYTHM GENERATOR

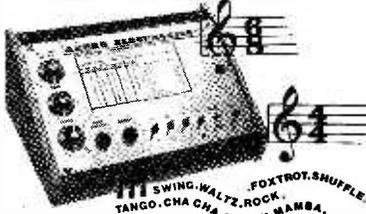

15 different rhythms, 9 percussion instruments. Tempo range 15 to 100 bars/min. Full kit of parts available at £39.50 + £1.20 P. & P. + VAT at 8%. Price assembled and tested add £12. Parts available separately, send S.A.E.

We reserve the right to alter published prices in the event of component or postal increases.

## P.E. ORION STEREO AMPLIFIER & TUNER



May be mounted slim line or stacked as above. Parts available separately for both units.

20 + 20 Watts r.m.s. into 8 ohm load. Distortion less than 0.1% 100Hz-10kHz. Frequency response  $\pm 1$ dB 20 Hz to 20kHz. Hum level virtually nil with volume full on. This is a power amplifier of superb quality incorporating the very latest design features. Professional hi-fi enthusiasts have classed it as fantastic and real value for money. The CCT incorporates a low flux transformer and inputs for disc, tape, tuner, etc.

## TUNER UNIT

May be purchased separately in matching slim line case. As full kit or individual parts. Send S.A.E. for price list and specification sheets.



## LOUDSPEAKERS

8 inch system

This system is designed for use with above amplifiers rated up to 25W r.m.s. per channel at 8Ω. May be incorporated in an enclosure 295 x 490 x 295mm (11.5 x 19.3 x 11.5in) approx. external, constructional details of which are given with each bass unit, to provide an overall frequency response of 50Hz to 22kHz. Four-element cross-over, ready constructed on p.c.b. Output leads have push-on receptacles to suit speaker tags. Cross-over frequency is 2.8kHz approx.

## POWER UNIT

Regulated



Voltage adjustable from 1-35v at 2 amps. Short circuit protected. Voltage and current meters incorporated. Full Kit of parts £48 + 8% VAT or assembled and tested £58 + 8% VAT.

## ASTRO IGNITION



SAVE FUEL

Complete kit of parts for this proven and tested system. (£11.90 + 60p P. & P.) + 8% VAT or ready built with only two connections to alter.

(£14.90 + 60p P. & P.) + 8% VAT.

Consider the advantages:

Fuel economy. Faster acceleration. More power. Excellent cold starting. Smoother running. No contact breaker burning. Less exhaust gases.

## TRANSFORMERS

SPECIAL OFFER

Miniature Mains Trans.

6-0-6v-6VA.

12-0-12v-6VA.

(£1.29 + 25p P. & P.) + 8% VAT

Transformer and coils manufactured to customer specifications both in High Volume and Small Order capacity.

TRADE AND EXPORT ENQUIRIES WELCOMED ON ALL PRODUCTS:

## ASTRO ELECTRONICS

Springbank Road  
Chesterfield (31475)  
Derbyshire

N.B.—DELIVERIES ON ALL ITEMS MAY TAKE UP TO 28 DAYS, DEPENDING ON AVAILABILITY AND DEMAND. CASH IN REGISTERED ENVELOPE OR POSTAL ORDERS CAN REDUCE TIME BY NOT HAVING TO CLEAR CHEQUES

## Complete digital Clock Kits TEAK OR PERSPEX CASE



NON ALARM £12.50  
ALARM £15.50

### FEATURES

- 4 LED digits  $\frac{1}{2}$ " high. Red.
- 12 hour display with AM/PM indication

- Mains frequency accuracy
- Easy to build: all components included
- Beautiful real wood case or Perspex: White, Black, Red, Blue, Green
- Flashes to indicate power cuts

"DELTA"  
6" x 2 $\frac{1}{2}$ " x 3"

### NON-ALARM

Complete kit including case .. £12.50  
Ready Built .. £14.50  
Module kit excluding case .. £9.50  
Ready Built .. £10.00

### ALARM

Pulsed Alarm Tone. Automatic Brightness control.  
9 minute Snooze. Simple Setting.  
Complete kit including case .. £15.50  
Ready Built .. £17.00  
Module kit excluding case .. £13.00  
Ready Built .. £13.50

TIMER FACILITY: Stopwatch use up to 9min 59secs .. extra 50p.

### EXCELLENT VALUE

● LCD gents watch. 5-function, Backlight. Chrome case. Black strap £17.28  
● 4 Function Calculator .. £4.00

### GUARANTEED

DISPLAYS: FND 500  $\frac{1}{2}$ " LED £1.19 each; 6 for £6.48  
NSB5430  $\frac{1}{2}$ " red LED stick of 4 £4.32 SLTO2  $\frac{1}{2}$ " green phosphor stick of 4 £5.40

CLOCK CHIPS: 50253N Alarm 12/24hr. 4/6 digit £5.67  
50362N Calendar clock £7.75 MM 5385N 12hr, 4 digit Alarm £4.32  
6 Decade Up/Down Counters: 50395/6/7 £13.10

MICROPROCESSOR: Z80 C.P.U. £22.68  
Z80CTC £15.70 1702A UV Erasable PROM £11.35  
Z80 PIO £15.70 2102NA 1K Static RAM £2.70  
UV PROM Eraser £103.00 + £5.00 p. & p. 4KX1 16-pin Dyn. RAM £7.05

RECHARGEABLE BATTERY SET Super Value £8.10  
Includes: 4 AA (1.2v) Nickel Cadmium batteries (separately £1.08 each)  
3/6v switched Universal Mains Adaptor with 4 plug connector for most calculators (separately £3.78) plus battery holder.

ELECTRONIC DOORBELL. Warbling tone. Runs off PP3 £5.40

payment with order to:

**BARON (P.W.)**  
SOUTHVIEW HOUSE, 6 GOWER ROAD,  
ROYSTON, HERTS Tel. ROYSTON 43695



All prices include post, pack. & VAT

## BARGAIN PARCELS SAVE POUNDS

Huge quantities of electronic components must be cleared as space required. 1000's of capacitors, resistors, transistors. Ex equipment panels, etc. covered in valuable components. No time to sort. Must sell by weight. 7 lbs £4.95, 14 lbs £7.95, 28 lbs £12.00, 56 lbs £20.00, 112 lbs £30.00.

### BARGAIN PACKS

Handy Packs  
4 aluminium boxes 128 x 44 x 38mm ideal for signal injectors, etc. £1.00  
Self fluxing enamelled copper wire 18 & 22 swg on 2 oz reels 2 for £1.10  
100 miniature reed switches ideal for burglar alarms, model railways, etc. £2.20  
15 2-Pole Reed relays on board operate at 12 volts £2.45  
6-Pole 12 volt reed relays on board £2.45  
High quality computer panels smothered in top grade components: 5 lbs £4.75  
10 lbs £8.95  
New U.H.F. transistor TV tuners, 4 push-button type £2.50  
Rotary type with slow motion drive £2.50  
Aluminium TV coax plugs 10 for £1.00  
20mm anti-surge fuses your selection 500mA to 3-15A 12 for £1.00  
Hardware packs each containing 100's of items including BA nuts & bolts, nylon, self-tapping, Posidrive, "P" clips, cable-clamps, fusholders, spire nuts etc, etc. £1 per pound  
100 assorted "P" clips. £1  
Belling Lee outdoor triplexers, UHF, Band 1, Band 2. 50p each 3 for £1

100 mixed polyester caps £1.40  
100 mixed modern miniature ceramic plate caps most values to 1000 PF £2.20  
100 mixed polystyrene caps to 5000 PF £2.20  
100 mixed electrolytics £2.20  
100 mixed wirewounds £1.00  
200 printed circuit resistors £1.00  
25 mixed pots + presets £1.00

Semiconductor Bargains  
100 new and marked silicon and germanium transistors including BC148, BF194, BC183, etc. £3.95  
200 new and marked transistors including 2N3055, AC128, BFY50, BD131, etc. £6.95  
100 mixed diodes IN4148, etc. £1.20  
100 mixed diodes including zener, power and bridge types £3.30  
200 unmarked mixed transistors. lots of interesting types including power. Send 60p for samples £4.50  
25 new and marked integrated circuits including 555, 741, 7400, 7490, TBA 800, CD4001, etc. £4.70  
BR 101 full spec. 5 for £1.00  
DY 51 EHT Rectifier £1.00  
TBA120A 50p each

### Component Bargains

300 mixed resistors  $\frac{1}{2}$  and  $\frac{1}{4}$  watt £1.00  
200 modern mixed caps most types £3.30

### DE LUXE FIBRE GLASS PRINTED CIRCUIT ETCHING KITS

Includes 150 sq. ins. copper clad f/g board, 1 lb ferric chloride, 1 dalo etch resist pen, abrasive cleaner, 2 mini drill bits, etch tray and instructions—only £5.30.

### REFILL PACKS FOR ABOVE

150 sq. ins. fibre glass board £1.50 5 lbs ferric chloride to mil spec. £4.00  
Dalo pen 50p instruction sheet 20p  
1 lb ferric chloride to mil spec. £1.00

### T/V SURPLUS

Brand new ITT C.T.V. triplers. fit Decca "Bradford" chassis—£2.50 each, 5 for £10.  
Pye and Philips "Ga" C.T.V. panels various types. All incomplete but invaluable for spares or completing. 6 assorted panels for £7.50.  
Thorn B & W T/V bottom panel "950" series. Manufacturers surplus £1.50 each.  
Pye 11U contrast controls. 10 for £1  
Thorn tape motors mains £1.20 each  
Pye EHT bases, DYSI, etc. 10 for £1  
Ceramic p/c mounting valve bases PL509, PL508, etc. 10 for £1

30p P & P ON ALL ABOVE ITEMS. SEND CHEQUE OR POSTAL ORDER WITH ORDER TO: SENTINEL SUPPLY, 20A, DEPT. PW, WADDON RD., CROYDON, SURREY

# RST VALVE MAIL ORDER CO.

## CLIMAX HOUSE, FALLSBROOK ROAD, LONDON SW16 6ED

### SPECIAL EXPRESS MAIL ORDER SERVICE

#### SEMICONDUCTORS

AA119 0.20	AA130 0.13	AA132 0.15	AAZ13 0.25	AAZ15 0.31	AAZ17 0.25	AC107 0.75	AC125 0.30	AC128 0.25	AC127 0.25	AC128 0.25	AC141 0.20	AC141K 0.30	AC142 0.20	AC142K 0.25	AC176 0.25	AC187 0.25	AC188 0.25	AC177 0.65	AC178 0.65	AC179 0.65	AC180 0.65	AC181 0.65	AC182 0.75	AF106 0.45	AF114 0.45	AF115 0.45	AF116 0.25	AF117 0.45	AF139 0.45	AF186 1.50	AF239 0.45	AFZ11 2.75	AFZ12 2.75	ASY26 0.45	ASY27 0.50	ASZ15 1.25	ASZ16 1.25	ASZ17 1.25	ASZ20 0.75	ASZ21 1.50	AU110 1.70*	AU113 1.70*	AU116 1.70*	BA145 0.15*	BA148 0.15*	BA154 0.10*	BA155 0.12	BA156 0.13	BAW62 0.05	BAK13 0.07	BAK16 0.07	BC107 0.12	BC108 0.12	BC109 0.13	BC113 0.15	BC114 0.18*	BC115 0.19*	BC116 0.19*	BC117 0.22*	BC118 0.22*	BC125 0.18*	BC135 0.15*	BC136 0.19*	BC137 0.16*	BC147 0.10*	BC148 0.10*	BC149 0.13*	BC157 0.12*	BC158 0.11*	BC159 0.13*	BC167 0.13*	BC170 0.16*	BC171 0.14*	BC172 0.13*	BC173 0.15*	BC177 0.19	BC178 0.18	BC179 0.20	BC182 0.11*	BC183 0.11*	BC184 0.12*	BC212 0.14*	BC213 0.14*	BC214 0.17*	BC237 0.17*	BC238 0.17*	BC301 0.45	BC303 0.40	BC307 0.20*	BC308 0.18*	BC327 0.22*	BC328 0.18*	BC337 0.19*	BC338 0.18*	BCY30 1.00	BCY31 1.00	BCY32 1.00	BCY33 0.90	BCY34 0.90	BCY40 1.25	BCY42 0.30	BCY43 0.32	BCY58 0.23	BCY70 0.22	BCY71 0.22	BC119 0.13*	BD115 0.60	BD121 1.50	BD123 1.50	BD124 1.00	BD131 0.51	BD132 0.54	BD135 0.55*	BD136 0.36*	BD137 0.37*	BD138 0.40*	BD139 0.43*	BD158 0.35	BD144 2.00	BD181 1.38	BD182 1.48	BD237 0.80	BD238 0.85	BDX10 0.75	BDX32 2.25	BDY60 0.75	BF115 0.39	BF152 0.25	BF153 0.25	BF154 0.25	BF159 3.45	BF160 3.00	BF167 0.75	BF173 0.75	BF178 0.48	BF180 0.45	BF182 0.45	BF183 0.45	BF184 0.39	BF185 0.37	BF194 0.11*	BF195 0.12*	BF196 0.14*	BF197 0.13*	BF224 0.30*	BF244 0.35*	BF257 0.37	BF258 0.42	BF259 0.45	BF336 0.50	BF337 0.53*	BF338 0.55*	BF339 0.55*	BF351 1.38	BF352 1.38	BF353 1.38	BF999 1.38	BF1000 1.38
------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	-------------	------------	-------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	-------------	-------------	-------------	-------------	-------------	-------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	------------	------------	------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	-------------	------------	------------	-------------	-------------	-------------	-------------	-------------	-------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	-------------	------------	------------	------------	------------	------------	------------	-------------	-------------	-------------	-------------	-------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	------------	-------------	-------------	-------------	-------------	-------------	-------------	------------	------------	------------	------------	-------------	-------------	-------------	------------	------------	------------	------------	-------------

#### VALVES

AZ31 1.10*	CCB31 1.50	CL33 2.81	CY31 0.90*	DAF91†
------------	------------	-----------	------------	--------

# ESSENTIAL BOOKS for RADIO AMATEURS

## GUIDE TO AMATEUR RADIO (16th edition) by Pat Hawker, G3VA

This book has been deservedly popular for many years as an introduction to amateur radio—what it is, how it works, and how to get started in this exciting hobby.

Most of the questions usually asked by the newcomer are answered in an introductory chapter, and then the book takes the reader from the first steps in setting up a receiving station to the basic theory and practice of aeriels, transmitters and receivers, and how to obtain a transmitting licence. Operation of an amateur station is discussed, and there are lists of Q-codes, amateur radio call sign prefixes and other useful data.

Chapter titles are: This is amateur radio; Getting started; Communications receivers; Amateur transmitters; The licence examinations; Operating an amateur station; Workshop practice; Amateur radio equipment; The RSGB and the radio amateur.

112 pages £1.38 post paid

## THE RADIO AMATEURS' EXAMINATION MANUAL (7th edition) by G. L. Benbow, G3HB

A pass in the Radio Amateurs' Examination is required before the authorities will grant an amateur radio transmitting licence, and the aim of this book is simple: to provide sufficient information to enable its readers to pass that examination. This new edition has been revised to take account of the changes in licence conditions which took place at the beginning of 1977.

Chapter titles are: Becoming a radio amateur; Elementary electrical principles and calculations; Thermionic valves and their applications; Introduction to semiconductors; Power supplies; Receivers; Transmitters; Measurements; Propagation and aeriels; Interference; Licence conditions; Tackling the radio Amateurs' Examination.

87 + viii pages £1.60 post paid

## RADIO AMATEURS' EXAMINATION QUESTIONS AND ANSWERS

This new book is a collection of model answers to typical Radio Amateurs' Examination questions, and should prove invaluable to candidates as a revision aid. The answers given are complete with diagrams and worked calculations where necessary, and demonstrate the sort of answer required to achieve a good pass mark.

118 pages £2.00 post paid

## RECEIVING STATION LOG BOOK

One of the essential features of a listener's station is a well-kept log book of stations heard. The RSGB Receiving station Log Book is specially designed for the listener to the amateur bands, with columns for date, time, frequency, call sign of station heard, signal report, mode, other station being contacted and its report given, remarks and QSL information.

Plastic comb binding £1.46 post paid


These are just a few of a complete range of technical publications, log books and maps for the radio amateur. Send a large stamped self-addressed envelope for the complete list.

The RSGB is the national society representing all UK radio amateurs. Membership is open to all interested in the hobby: write to the membership section and ask for full details.



**Radio Society of Great Britain**  
35 DOUGHTY STREET, LONDON, WC1N 2AE

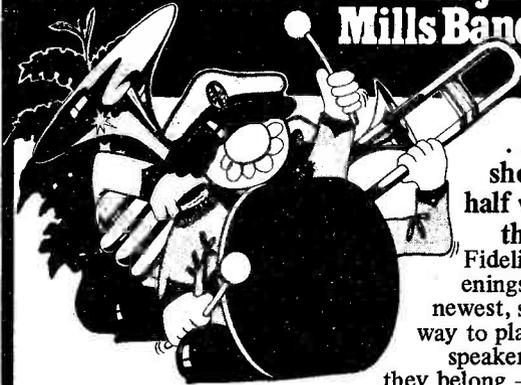Your carpet is no place  
for the Black Dyke  
Mills Band



... they should be half way up the wall! Fidelity Fastenings are the newest, smartest way to place your speakers where they belong — on the

wall. Almost undetectable when fitted they are easily adjustable and allow your speaker system to be placed in the best possible acoustical position, where they stay due to the rubber friction mounting. Fidelity Fastenings take a weight of up to 50 lbs and your speakers are easily lifted off for dusting and redecorating. Available from all good Audio and Hi-Fi shops and stores at £5.49. Look for the red and black box.

If you have any difficulties in obtaining your Fidelity Fastenings, write for details of your nearest stockists to:

**Fidelity Fastenings**

The Ridgeway, Iver, Buckinghamshire,  
Tel: (0753) 654222.

## FANE SPECIALIST RANGE SPEAKERS

Each designed to produce the individual sound requirement for its purpose. ★ Robust Cast Aluminium Chassis. ● Linen Cone surround. Extra strong six strut steel chassis with plunzed windows on 15" models.



- ★ 12" DISCO/80 80w Fitted large Tweeter Cone ● £28.95
- ★ 12" DISCO/100 100w Cone ● £29.95
- ★ 12" GUITAR/80L 80w For Lead Guitar ● £26.95
- ★ 12" GUITAR/80B " Prs rec for Bass Guitar ● £27.95
- ★ 12" PA/80 80w Dual Cone. For general purpose P.A. ● £26.95
- 15" BASS/85 85w For Bass Guitar ● £39.95
- 15" BASS/100 100w For Bass Guitar ● £42.00


DISCO '80'

## 'POP' RANGE SPEAKERS

### HIGH FREQUENCY HORNS

**J44** Range: 2.5KHz-15KHz Power: 50w with HPX2R 30w with HPX1R Imp: 8 ohms Size approx 3½" x 3½" x 3" **£7.95**

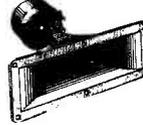**J73** Range: 2.5KHz-20KHz Power: 50w with HPX1R Imp: 8 ohms Size approx 7½" x 3" x 6½" Rec Price **£11.75**



- 12" POP 33T 33w ● £14.95
- 12" POP 50/2 50w ● £16.99
- 12" POP 75 70w ● £22.95
- 15" POP 70 75w ● £29.95
- 18" POP 125 100w ● £47.95

**J104** Range: 2KHz-15KHz Power: 50watt with HPX1R 70watt with HPX2R Imp: 8 ohms Size approx 10½" x 3½" x 7¾" **£16.95**

**920/2** Range: 1 KHz-18KHz Power: 100w with HPX1. Imp: 8 ohms Rec. Price **£59.95**

**HIGH POWER "CROSS-OVERS"**  
HPX1R (3.5KHz) ● £2.99  
HPX2R (5KHz)

Impedance or total impedance of Bass Drivers not to exceed 8Ω. Otherwise use series Horns or attenuation provided with HPX1R and HPX2R.

2 years guarantee on speakers & Horns Rec. Prices INCLUDE VAT.

FANE SPEAKERS ARE SUPPLIED TO MOST LEADING U.K. MANUFACTURERS OF GROUP AND DISCO EQUIPMENT

Distributors (Wholesale & Retail) Rec. prices shown correct at 23.9.77.  
**LINEAR PRODUCTS LTD, ELECTRON WORKS, ARMLEY, LEEDS**  
Manufacturers & Export enquiries to:—  
**FANE ACOUSTICS LTD, 286 BRADFORD ROAD, BATLEY, YORKS**

# 15-240 Watts!

## HY5 Preamplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally. The desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack—Multi-function equalization—Low noise—Low distortion—High overload—Two simply combined for stereo.

**APPLICATIONS:** Hi-Fi—Mixers—Disco—Guitar and Organ—Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV; Ceramic Pick-up 30mV; Tuner 100mV; Microphone 10mV; Auxiliary 3-100mV; input impedance 4-7k $\Omega$  at 1kHz.


**OUTPUTS:** Tape 100mV; Main output 500mV R.M.S.

**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz; Bass  $\pm$  at 100Hz.

**DISTORTION:** 0-1% at 1kHz. Signal/Noise Ratio 65dB.

**OVERLOAD:** 38dB on Magnetic Pick-up. **SUPPLY VOLTAGE**  $\pm$  16-50V.

**Price** £5.22 + 65p VAT P&P free.

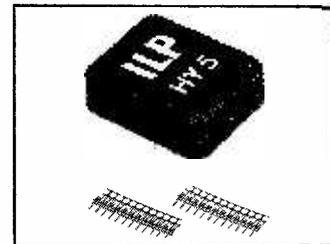

## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. It features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete Kit—Low Distortion—Short, Open and Thermal Protection—Easy to Build.

**APPLICATIONS:** Updating audio equipment—Guitar practice amplifier—Test amplifier—audio oscillator.


**SPECIFICATIONS:**

**OUTPUT POWER** 15W R.M.S. into 8 $\Omega$ ; **DISTORTION** 0-1% at 1.5W.

**INPUT SENSITIVITY** 500mV. **FREQUENCY RESPONSE** 10Hz-16kHz—3dB.

**SUPPLY VOLTAGE**  $\pm$  18V.

**Price** £5.22 + 65p VAT P&P free.

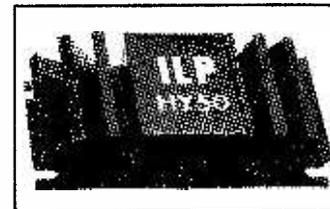

## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion—Integral Heatsink—Only five connections—7 amp output transistors—No external components

**APPLICATIONS:** Medium Power Hi-Fi systems—Low power disco—Guitar amplifier


**SPECIFICATIONS:** **INPUT SENSITIVITY** 500mV

**OUTPUT POWER** 25W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-0.04% at 25W

at 1kHz **SIGNAL/NOISE RATIO** 75dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB.

**SUPPLY VOLTAGE**  $\pm$  25V **SIZE** 105 50 25mm

**Price** £6.82 + 85p VAT P&P free

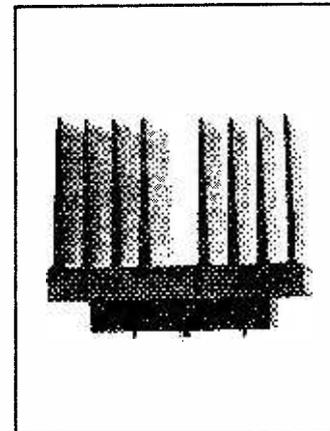

## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range. Designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion—Integral heatsink—Load line protection—Thermal protection—Five connections—No external components

**APPLICATIONS:** Hi-Fi—High quality disco—Public address—Monitor amplifier—Guitar and organ

**SPECIFICATIONS**

**INPUT SENSITIVITY** 500mV.

**OUTPUT POWER** 60W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-0.04% at 60W

at 1kHz **SIGNAL/NOISE RATIO** 90dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

$\pm$  35V

**SIZE** 114 50 85mm

**Price** £15.84 + £1.27 VAT P&P free.

## HY200 120 Watts into 8 $\Omega$

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—Integral heatsink—No external components

**APPLICATIONS:** Hi-Fi—Disco—Monitor—Power slave—Industrial—Public Address

**SPECIFICATIONS**

**INPUT SENSITIVITY** 500mV

**OUTPUT POWER** 120W RMS into 8 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-0.05% at 100W

at 1kHz **SIGNAL/NOISE RATIO** 96dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

$\pm$  45V

**SIZE** 114 50 85mm

**Price** £23.32 + £1.87 VAT P&P free.

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s "Big Daddy" of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown—Very low distortion—Load line protection—No external components.

**APPLICATIONS:** Public address—Disco—Power slave—Industrial


**SPECIFICATIONS**

**OUTPUT POWER** 240W RMS into 4 $\Omega$  **LOAD IMPEDANCE** 4-16 $\Omega$  **DISTORTION** 0-1% at 240W

at 1kHz **SIGNAL/NOISE RATIO** 94dB **FREQUENCY RESPONSE** 10Hz-45kHz—3dB **SUPPLY VOLTAGE**

$\pm$  45V **INPUT SENSITIVITY** 500mV **SIZE** 114 100 85mm

**Price** £32.17 + £2.57 VAT P&P free.

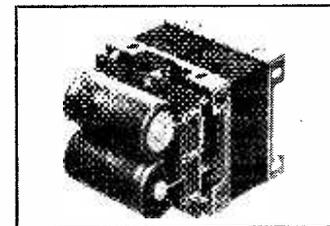

## POWER SUPPLIES

PSU36 suitable for two HY30's £5.22 plus 65p VAT. P/P free.

PSU50 suitable for two HY50's £2.82 plus 85p VAT. P/P free.

PSU70 suitable for two HY120's £13.75 plus £1.10 VAT. P/P free.

PSU90 suitable for one HY200 £12.65 plus £1.01 VAT. P/P free.

PSU180 £23.10 + £1.85 VAT.

BI £0.48 + £0.06 VAT.

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. ELECTRONICS LTD., GROSSLAND HOUSE, NACKINGTON, CANTERBURY, KENT, CT4 7AD.

**I.L.P. ELECTRONICS LTD.,**  
**GROSSLAND HOUSE, NACKINGTON,**  
**CANTERBURY, KENT, CT4 7AD.**

Please Supply \_\_\_\_\_  
Total Purchase Price \_\_\_\_\_  
I Enclose Cheque  Postal Orders  Money Order   
Please debit my Access account  Barclaycard account   
Account number \_\_\_\_\_  
Name and Address \_\_\_\_\_  
Signature \_\_\_\_\_

**TV GAMES IN FULL COLOUR**  
At last it's here! The new Swanley colour encoder kit £7.50. Adds different colours to the frame, ball, bats and background of the AY-3-8500 TV games.  
AY-3-8500 £6.95. Black and white TV games £11.95. Rifle kit £4.95. Send sae for our gigantic free data leaflet.

**NEW COMPONENT SERVICE**  
Resistors 5% carbon E12 1Ω to 10M 1/2W 1 1/2p. 1W 3p. Preset pots subminiature 0.1W 100Ω to 4M7 9p. Potentiometers 1/2W 4K7 to 2M2 log or lin. Single 30p. Dual 95p. Polystyrene Capacitors E12 63V 22pf to 8200pf 3p. Ceramic Capacitors 50V E6 22pf to 47000pf 3p. Polyester Capacitors 250V E6 0.1 to 1mf 5p. 15, 22, 33mf 7p. 47mf 11p. Electrolytics 50V 47, 1, 2, 22 3p. 25V 5, 10mf 5p. 16V 22, 33, 47mf 6p. 100mf 7p. 220, 330mf 9p. 470mf 11p. 1000mf 18p. Zener Diodes 400mW E24 3V3 to 33V 8 1/2p.

**MAINS TRANSFORMERS**  
6.0-6V 100mA 94p. 9.0-9V 75mA 94p. 0/12/15/20/24/30V 1A £3.85. 12.0-12V 50mA 94p. 0/12/15/20/24/30V 2A £5.15. 6.3V 1 1/2A £2.30. 6.0-6V 1 1/2A £2.75. 9.0-9V 1A £2.39. 12.0-12V 1A £2.69. 15.0-15V 1A £2.89. 30.0-30V 1A £3.59.

**PRINTED CIRCUIT KITS ETC\***  
Contains etching dish, 100 sq ins of pc board, 1lb ferric chloride, etch resist pen, drill bit and laminate cutter £3.95. 100 sq ins pc board 80p. 1lb FeCl 1.05. Etch resist pen 75p.

**S-DECS AND T-DECS\***  
S-Dec £1.94. T-Dec £3.61.  
u-DeCA £3.97. u-DeCB £6.67.  
IC carriers with sockets:  
16 dit £1.91. 10T05 £1.79.

**SINCLAIR CALCULATORS\***  
Cambridge Scientific Programmable £13.95. Prog. Library £4.95. Cambridge Scientific £8.45. Oxford Scientific £10.60. Mains Adaptors £3.20.

**BATTERY ELIMINATOR BARGAINS**  
**TV GAMES POWER UNIT**  
Stabilized 8 1/2V 100mA £3.20.

**3-WAY MODELS**  
With switched output and 4-way multi-jack connector Type 1: 3/4 1/2 5V at 100mA £2.30. Type 2: 6/7 1/2 9V 300mA £2.90.

**100MA RADIO MODELS**  
With press-stud connectors. 9V £3.45. 6V £3.45. 9V+9V £5.15. 6V+6V £5.15. 4 1/2V+4 1/2V £5.15.

**CASSETTE MAINS UNIT**  
7 1/2V with 5 pin din plug 150mA £3.65.

**FULLY STABILIZED MODEL £6.40.**  
Switched output of 3/6/7 1/2 9V 400mA stabilized.

**CAR CONVERTERS 12V INPUT**  
Output 9V 300mA £1.80. Output 7 1/2V 300mA £1.80.

**BATTERY ELIMINATOR KITS**  
Send sae for free leaflet on range.

**100mA radio types with press stud battery terminals.**  
4 1/2V £2.10. 6V £2.10. 9V £2.10. 4 1/2V+4 1/2V £2.50. 6V+6V £2.50. 9V+9V £2.50.

**Cassette type 7 1/2V 100mA with din plug £2.10.**  
Transistor stabilized 8-way type for low hum. 3/4 1/2 6/7 1/2 9/12/15/18V. 100mA £3.20. 1 Amp £6.40.

**Heavy duty 13-way types 4 1/2 6/7 8 1/2 11/13/14/17/21/25/28/34/42V. 1 Amp £4.85. 2 Amp £7.95.**

**Car converter kit Input 12V DC. Output 6/7 1/2 9V DC 1A transistor stabilized £1.95.**

**Stabilized Laboratory power kit Switched 1 to 30V in 0.1V steps. 1 Amp £12.45. 2 Amp £14.95.**

**BI-PAK AUDIO MODULES**  
ES40 tuner £21.95. AL60 £4.86. PA100 £14.95. MK60 audio kit £36.45. Stereo 30 £17.95. SPM80 £3.75. BMT80 £4.25. Send sae for free data.

**JC12, JC20, JC40 AMPLIFIERS**  
JC12 6W 1C audio amp with free data and printed circuit £1.95.  
Also new JC40 20W model with pcb £3.95. Sensational new JC20, 10W integrated circuit amp with pcb £5.95. Send sae for free leaflet on all 3 models and associated power supply and preamp kits.

**FERRANTI ZN414**  
1C radio chip £1.44. Extra parts and pcb for radio £3.85. Case £1. Send sae for free data.

**SWANLEY ELECTRONICS**  
DEPT. PW, PO BOX 68,  
32 GOLDSSEL RD., SWANLEY, KENT

Post 30p. Prices include VAT. Official orders welcome. Overseas customers deduct 7% on items marked \* and 11% on others.

**MAINS INTERCOM**  
NO BATTERIES NO WIRES ONLY  
**£29.99**  
PER PAIR + VAT £3.76

The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 4-mile on the same mains phase. On/off switch. Volume control. Useful as inter-office intercom. between office and warehouse in surgery and in homes. P. & P. 99p.

**4-STATION INTERCOM**  
**£19.95**  
+ V.A.T. £1.60

Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospitals and Office. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 60ft. A Battery and other accessories. P. & P. 90p.

**NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER**

**ONLY £14.95**  
+VAT £1.20

Latest transistorised Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for "conference" calls: leaves the user's hands free to make notes, consult files. No long waiting, saves time with long-distance calls. On/off switch, volume, conversation recording model at £18.95 + VAT £1.96. P. & P. 69p.

10-day price refund guarantee on all items.  
**WEST LONDON DIRECT SUPPLIES (PW10)**  
169 KENSINGTON HIGH STREET, LONDON, W8  
01-887 5548

**SOUTHERN VALVE CO., UPPER FLOOR,**  
8 POTTERS ROAD, NEW BARNET, HERTS.  
TEL: 01-440/8641. MAIL ORDER ONLY

"QUALITY" branded valves guaranteed 3 months. BVA, etc. (SEE LISTS)  
Note: Prices correct at time of going to press. MIN. ORDER 75p! POSTAGE 12p 1st valve (large 14p), extra valves 6p, max. 75p. SAE lists, VAT included. C.W.O. only, no C.O.D. TOP QUALITY OUR EVERY AIM! Return of post service.

AZ81 80p	EZ80 40p	PCL86 65p	UL41 75p
DY86/7 49p	EZ81 40p	PCL200 40	UL84 52p
DY802 50p	GY50L £1.10	PCL200 40	UY85 40p
EB91 10p	CZ20 75p	PE500 £2.25	U26 80p
ECC81 36p	PC86 65p	PE1200 75p	U26 60p
ECC82 36p	PC88 65p	PL36 70p	U191 60p
ECC83 36p	PC97 72p	PL81 50p	6J30L2 75p
ECC86 40p	PC900 49p	PL81A 55p	6BW7 68p
ECC88 60p	PC900 49p	PL82 35p	6F23 60p
ECH42 80p	PCC84 35p	PL83 40p	6F28 70p
ECH81 50p	PCC85 44p	PL84 48p	6L6 89p
ECH83 82p	PCC88 82p	PL500 90p	10F1 65p
ECH84 82p	PCC89 80p	PL504 90p	10F1 70p
ECL80 82p	PCC189 55p	PL508 £1.30	20L1 70p
ECL82 50p	PCF80 45p	PL509 £2.30	20P4 70p
ECL83 68p	PCF82 50p	PL519 £2.80	30C1 50p
ECL86 60p	PCF86 58p	PL802 £2.45	30C15 78p
EF80 32p	PCF200	PY33 50p	30C17 78p
EF85 38p		PY81/2 40p	30C18 £1.45
EF86 52p	PCF801 60p	PY88 58p	30F5 50p
EF89 42p	PCF802 57p	PY800 50p	30FL2 £1.05
EF183 42p	PCF806	PY801 50p	30L1 35p
EF184 42p		PY500 £1.33	30L15 52p
EH90 56p	PCF806 75p	PY500A £1.33	30L17 70p
EL34 40p	PCF808	UBF89 40p	30L19 50p
EL41 70p		UC85 46p	30P13 90p
EL84 40p		UCH49 72p	30PL1 £1.40
EL90/1 47p	PCH800 95p	UCH81 50p	30PL3 £1.00
EL909 £2.75	PCL82 54p	UC182 55p	30PL14
EM84 50p	PCL83 70p	UC183 58p	UC183 £1.10
EY81 60p	PCL84 48p	UC185 58p	30PL15 £1.00
EY86/7 38p	PCL85	UC1 70p	
EY800A £1.60	PCL 62p	UF89 45p	
	805		

**Please mention Practical Wireless when replying to adverts.**

**Sonic**  
HI-FI DISCOUNT CENTRES

**DISCOUNT SPEAKERS**  
Imp 8 or 15Ω as app.  
Guarantees:  
TITAN 5 years  
FANE 2 years  
OTHERS 1 year  
**ALL PRICES INC. VAT**  
Prices correct at 4.10.77

**HI-FI TYPES**

5" FANE 501 Mid or Full range	Sp. Price	£4.95
8" x 5" 15w Various makes	Sp. Price	£3.34
8" A.F. Model 80 Dual Cone	Sp. Price	£5.98
8" A.F. Model 83 Dual Cone	Sp. Price	£6.98
FANE 805	Sp. Price	£5.98
FANE 804	Sp. Price	£4.95
FANE 801 Dual Cone	Sp. Price	£7.95
FANE 807 808T Dual Cone	Sp. Price	£3.95
FANE 80707P	Sp. Price	£4.75
WH'FEDALE L'TON 3XP kit Pr.	£60.70	£42.95
10" DENTON 2XP Kit Pair	£39.15	£27.95
10" GLENDALE 3XP KIT	£82.44	£59.95
10" FANE MODE ONE KIT	Sp. Price Pair	£19.99
10" ELAC Model 10RM	Sp. Price	£3.85
12" FANE 121/15LR 20w	Sp. Price	£7.95

**GROUP/DISCO TYPES**

12" FANE POP 15	Sp. Price	£4.99
12" FANE POP 25T 25-30w	Sp. Price	£9.95
12" TITAN T12/4E 45w	£15.80	£10.95
12" TITAN T12/60A 60w	£22.50	£12.95
12" TITAN T12/100A 100w	£31.00	£22.95
12" CELESTION G12M	£16.50	£12.99
12" CELESTION G12H 30w	£22.00	£15.95
12" CELESTION G12/50 50w	£25.75	£17.50
12" CELESTION G12/50TC	£28.00	£17.95
12" GOODMANS 12 PD	Sp. Price	£18.95
12" GOODMANS 12 PG	Sp. Price	£17.95
12" FANE 'SPECIALIST' P.A. 80	£26.95	£16.95
12" " " DISCO 80	£28.95	£17.95
12" " " GUITAR 80L	£26.95	£16.95
12" " " GUITAR 80B	£27.95	£17.95
12" FANE CRESCENDO 12A 8Ω	£57.35	£39.95
12" FANE " " 15Ω	£57.35	£39.95
12" FANE " " 12L 8Ω	£59.95	£41.95
12" FANE " " 15Ω	£59.95	£35.95
12" FANE " " 12 BASS 8Ω	£56.70	£39.95
12" FANE " " 15Ω	£56.70	£29.95
15" FANE POP60 60w 15Ω	£25.95	£12.95
15" TITAN T15/60 60w	£26.00	£18.95
15" TITAN T15/70 70w	£28.00	£20.95
15" TITAN T15/100 100w	£41.00	£28.95
15" FANE 'SPECIALIST' BASS 85	£39.95	£29.95
15" " " BASS 100	£42.00	£31.50
15" GOODMANS 15P	Sp. Price	£23.95
15" CELESTION G15C	£36.00	£26.95
15" FANE CRESCENDO 15/100A 8Ω	£47.00	£39.95
15" FANE " " 15Ω	£72.95	£39.95
15" FANE CRESCENDO BASS	£76.00	£49.95
15" " " 15/100LT	£74.69	£49.95
15" " " 15/160 160w	£95.00	£65.95
15" " " 15/125A	£95.00	£69.95
15" " " COLOSSUS 200w	£108.00	£69.95
15" TITAN T18/100 100w	£47.00	£39.95
18" GOODMANS 18P	Sp. Price	£39.95
18" CELESTION G18C	£53.00	£39.95
18" FANE CRESCENDO 18A	£101.95	£69.95
18" FANE CRESCENDO BASS	£89.95	£59.95
18" " " COLOSSUS 200w	£115.00	£69.95

**HORN UNITS (Carr. 75p)**

CELESTION MH1000 25w	£17.00	£13.75
FANE 910 MK II 50w	£17.75	£10.99
" " 920 100w	£59.95	£39.95
" " 144 750w	£11.75	£8.95
" " 73 50w	£11.75	£8.95
" " 1104 50-70w	£16.95	£12.95

**HIGH POWER 'CROSS-OVERS'**  
FANE HPX1R or HPX2R Carr. 35p £2.99

**ADD-ON HIGH FREQUENCY UNITS**  
F.A.L. 'Add-on' Carr. £1 £51.84 £35.95  
TITAN T1H 70w Carr. £1 Sp. Price £25.95  
TITAN T2H 100w Carr. £1 Sp. Price £25.95  
TITAN T2H Sp. Price £26.95

**HI-FI SPEAKER SYSTEMS**


LEAK 3020	Pair	£128.56	£84.95
LEAK 3030	Pair	£175.84	£114.95
LEAK 3050	Pair	£245.80	£162.95
WHARFEDALE DENTON 2XP	Pair	£68.45	£47.95
LINTON 3XP	Pair	£49.77	£69.95
CHEVIN XP	Pair	£45.76	£31.95
GLENDALE 3XP	Pair	£137.45	£96.95

Also for personal shoppers only  
**AMPS, T'ABLES, JINGLE MACHINES, DISCO CONSOLES, LIGHTING, CABINETS, CREDIT TERMS AVAILABLE** orders £20 over

Phone orders accepted from Access & Barclay card holders.  
Branches at  
**GLASGOW**  
403 SAUCHIEHALL STREET  
Tel: 141 332 0700  
**NEWCASTLE**  
24 NEWGATE SHOPPING CENTRE  
Tel: 0632 25168  
**MIDDLESBROUGH**  
106 NEWPORT ROAD  
Tel: 0642 217402  
Mail Orders & Export enquiries to Middlesbrough Branch. Add 55p carr. on Hi-Fi kits. Otherwise add 85p (12" spkr.) £1.25 (15" £2.18")
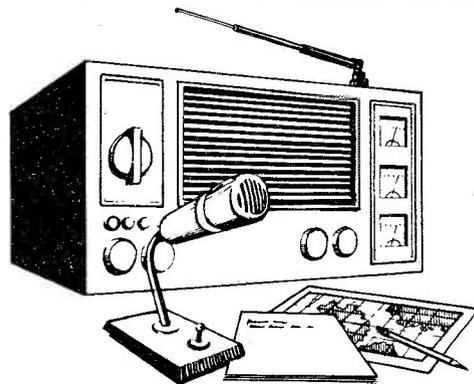
# Electronics. Make a job of it....

Enrol in the BNR & E School and you'll have an entertaining and fascinating hobby. Stick with it and the opportunities and the big money await you, if qualified, in every field of Electronics today. We offer the finest home study training for all subjects in radio, television, etc.; especially for the CITY AND GUILDS EXAMS (Technicians' Certificates); the Grad. Brit. I.E.R. Exam; the RADIO AMATEUR'S LICENCE; P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servo-mechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam successes. We are the only privately run British home study College specialising in electronics subjects only. Full details will be gladly sent without any obligation.



## Become a Radio Amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

**Free!**

Brochure without obligation to:

### British National Radio & Electronic School

P.O. Box 156, Jersey, Channel Islands.

NAME \_\_\_\_\_


ADDRESS \_\_\_\_\_

Block caps please

WL 12

## VDU/MACRO COMPUTER

with so many  
features...

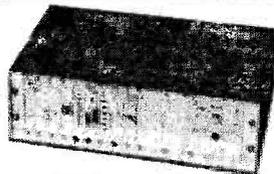

- \* Rock Steady Pictures
- \* Crystal Controlled
- \* Telephone Interface
- \* Tape Programmable
- \* Software Available
- \* Ideal for Education
- \* Expandable Memory
- \* Repeat Facility
- \* Tab Key
- \* Video or UHF Output
- \* Games and Things on Tape
- \* Ready-Built or in Kit Form
- \* Expandable Number of Lines
- \* Selectable Flashing Characters
- \* Forward and Reverse Typing Mode
- \* Automatic Tape Stop/Start

COME ALONG AND PLAY MASTERMIND or S.A.E. FOR INFORMATION

**CROFTON ELECTRONICS LIMITED**  
35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX • Tel. 01-891 1923

## H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION

### NEW - MODEL 'T' TWIN TRANSISTOR RECEIVER

AT LAST—a transistorised kit at a price you can afford, that is suitable for the amateur constructor.

This is a fully transistorised high performance short-wave receiver, with F.E.T. regenerative detector, followed by a high-gain audio stage for working into medium/high impedance headphones.

The set uses a well-known range of plug-in coils giving good sensitivity and selectivity, and many hours of listening may be enjoyed using a single PP3 type battery.

COMPLETE KIT £9.70 inc. p & p and V.A.T.

**"H.A.C." SHORT-WAVE PRODUCTS**  
P.O. Box No. 16, 10 Windmill Lane  
Lewes Road, East Grinstead, West Sussex RH19 3SZ



4 1/2 in x 3 1/2 in METER. 30µA,  
50µA or 100µA, £4.78. P. & P. 19p.

### MICROPHONES FOR TAPE RECORDERS

- DM228R 200 ohm with 3.5 & 2.5mm Jack Plugs £1.30
  - DM229R 50K with 3.5 & 2.5mm Jack Plugs £1.60
  - DM18D 200 ohm with 5 & 3 pin DIN plug £1.75
- Postage on above microphones 11p.



### CARDIOID DYNAMIC MICROPHONES

- Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £8.02. P. & P. 35p.

**42 x 42mm METERS**  
1mA, 500mA, £2.92, 11p P. & P.

**60 x 45mm METERS**  
50µA, 100µA, 500µA and 1mA  
VU METER £4.13, 13p P. & P.

**EDGEWISE METERS**  
90mm x 34mm, 1mA £3.40, 19p P. & P.

### MULTI- METER

Model ITI-2  
20,000 ohm/  
volt, £10.05.  
P.&P. 33p.



### TRANSFORMERS

Primary 240V		
6-0-6V	100mA	£0.75
9-0-9V	75mA	£0.75
12-0-12V	50mA	£0.85
12-0-12V	100mA	£1.05
Post on above transformers 30p.		
9-0-9V	1A	£1.80
12-0-12V	1A	£2.15
15-0-15V	1A	£2.36
30-0-30V	1A	£3.10
6-3V	1 1/2A	£1.80
6-0-6V	1 1/2A	£2.20
Post on above transformers 45p.		

All above prices include V.A.T. LARGE S.A.E. for NEW LIST  
Special prices for quantity quoted on request.

**M. DZIUBAS**  
158 Bradshawgate · Bolton · Lancs. BL2 1BA



### NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

### Receivers and Components

#### VALVES

Radio - T.V. - Industrial - Transmitting  
We Dispatch Valves to all parts of the world by return of post, Air or Sea mail, 2700 Types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00 closed Wednesday 1.00. We wish to purchase all types of new and boxed Valves.

**COX RADIO (SUSSEX) LTD.**  
Dept. P.W. The Parade, East Wittering,  
Sussex PO20 BBN  
West Wittering 2023 (STD Code 024366)

**SURPLUS TRANSISTOR Amplifier Modules**  
75p each. Ex GPO Multimeters 20,000Ω/V DC, with leads and leather case, £8.00, plus 50p P&P. Ex GPO Cutters and Pliers, 75p each. Archer, 9 Pine Grove, Maidstone, Kent.

#### BRAND NEW COMPONENTS BY RETURN.

**Electrolytic capacitors 16V, 25V, 50V.**—0.47, 1.0, 2.2, 4.7 & 10mfd.—5p, 22, 47—5p. (50V—8p), 100—7p (50V—8p) 220—8p, (50V—10p) 470—11p, (50V—16p) 1000/16V—15p, 1000/25V—18p, 1000/50V—22p.

**Subminiature bead tantalum electrolytics**—0.1, 0.22, 0.47, 1.0, 2.2 @ 35V, 4.7/25V—11p, 10/25V—13p, 22/16V, 47/6V, & 100/3V—15p.

**Mullard miniature ceramic E12 series 2% 63V.** 10pf. to 47p—3p, 56pf. to 330pf.—4p.

**Vertical mounting ceramic plate 50V.** E12 series 22pf-1000pf. E6 series 1500pf-47000pf.—2p.

**Polystyrene E12 series 63V horizontal mounting.** 10pf to 1000pf—3p, 1200pf. to 10000pf.—4p.

**Mullard polyester 250V vertical mounting E6 series.** 0.01 to 0.1—4p, 0.15, 0.22—5p, 0.33, 0.47—8p, 0.68—11p, 1.0—13p, 1.5—20p, 2.2—22p.

**Mylar (Polyester) Film 100V vertical mounting.** 0.001, 0.002, 0.005—3p, 0.01, 0.02—4p, 0.04, 0.05—4½p.

**Miniature resistors Highstab E12 series 5%, Carbon Film 0.25W 1Ω to 10MΩ (10% over 1MΩ)—1p. Metal Film 0.125W, 0.25W & 0.5W 1Ω to 2MΩ.—1½p. Metal Film 1W, 27Ω to 10MΩ.—2p ea.**

1N4148—3p, 1N4002—5p, 1N4006—7p, 1N4007—8p, BC107/39, BC147/8/9, BF157/8/9 & BF194 & 197—8p. Fuses, 20mm, glass, 1½" glass & 1" ceramic, 2½p. Post 10p. (Free over £4.00) Prices inclusive of VAT.

**THE C. R. SUPPLY CO.**  
127, Chesterfield Rd., Sheffield S8.

## SMALL ADS

The prepaid rate for classified advertisements is 20 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £6.80 per single column centimetre. All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

### CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

- Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
- The publishers reserve the right to refuse or withdraw any advertisement.
- Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

## BARGAIN SUPPLIES

New equipment PCB's with 100% re-usable components.

- Invertor 24v DC in 240v AC out **untested £1.00**
  - Boards with a minimum of 2 × TIP41/A type selected for high speed **50p.**
  - Boards with a min of 300v thyristor, plastic transistor, capacitors etc. **50p.**
  - Ex. equip. 2N3055 type **30p.**
  - Our selection min 4 boards **£2.00.**
- P & P 10p per item. 20p overseas.

Digital multimeter parts.

- DMM. plastic case cut out and silk screened **£4.99.**
- 4 pole 1-6 way rotary switch **£1.95.**
- Pointer knobs ¼" spindle approx. 1" diam. **30p.**
- 10M, 1M, 100K, 10K, 1K. Precision resistors (1%) set. Attenuation **£1.30.**
- Push to make switches **30p.**

**R. JONES SUPPLIES, 3 Centre Vale Close, Littleborough, Lancs.**

### ORCHARD ELECTRONICS

I.C.s TTL, C/Mos. Linear. Capacitors. Resistors. (E12) SIL/Rectifiers. Diodes. LED. Thyristors. Zeners. Voltage Reg. DiL Sockets. Bridge Rectifiers. Potentiometers. Presets. Triacs. Diac. Plugs. Sockets. Cable. Vero. Carefully selected range, excellent despatch service. Same day turn round. S.A.E. List. Suppliers to A.E.R.E. U.K.A.E.A. Governments Depts. Schools. Universities. Manufacturers. Accounts opened for trade and amateur. Join the professionals. Phone by 4 p.m. Goods out 1st class by 5 p.m. Try us and prove it!

**ORCHARD ELECTRONICS**  
Flint House, High Street, Wallingford,  
Oxon. Telephone 0491-35529

**TIRRO ELECTRONICS**, the mail order division of **RITRO ELECTRONICS UK** offers a wide range of components to the amateur enthusiast. Large SAE or 20p brings list. **GRENFELL PLACE, MAIDENHEAD. BERKS. SL6 1HL.**

### TOUCH CONTROLLED LIGHTING KITS

These KITS replace conventional light switches and control 300W of lighting. No mains rewiring required. Insulated Touch Plates. Easy to follow instructions. **TSD300K—TOUCHSWITCH & DIMMER** combined. ONE touch plate to switch light on or off. Brightness controlled by small knob—**£5.20.**  
**TS300K—TOUCHSWITCH.** TWO touch plates ON and OFF—**£4.60.**  
**TSA300K—AUTOMATIC.** ONE touch plate. Light turns off after preset delay—**£4.00.**

LD300K—LIGHT DIMMER KIT—£2.80.		
400V TRIACS	BULK OFFERS	CMOS
Plastic	BC148	4001 18p
3A	555	4007 18p
8.5A	741	4011 18p
12A	8A/400V Triac	4013 5p
15A	DL727 dual 0.5" 7 seg.	4015 8p
20A	LED Display	4018 5p
6.5A with trigger	555 36p (3 for £1)	4017 8p
Diac	741 24p (5 for £1)	4049 50p

**CLOCK 1KW APPLIANCE TIMER KIT inc. AY-5-1230, 0.5" LED display, triac, switches, boc, pcbs, etc. £15.95**  
**AY-5-1230 CLOCK APPLIANCE TIMER IC £4.85**

**QUANTITY DISCOUNTS ON REQUEST**  
Add 8% VAT + 25p P&P. Mail Order Only to:  
**T. K. ELECTRONICS (PW)**  
106 Studley Grange Road, London W7 2LX

**BARGAIN PACK 100 Transistors.** High Power, Audio, RF, GEN. Purpose. Fine selection of branded makes, all new and marked. Value at least £15. Only £5 inc. P&P CWO (UK ONLY). Instant refund if not delighted. A. Philpott, 171 Great Brays, Harlow, Essex CM18 6DT.

**NOSTALGIA COLLECTING**

### VINTAGE RADIO

1920 to 1950

Receivers, valves, components, service data, historical research, books, magazines, repairs and restorations. A complete service for the collector and enthusiast of vintage radio.

S.a.e. with enquiries and for monthly newsheet. Full 1977 catalogue, 70p post paid.

**TUDOR REES (Vintage Services), 64, Broad Street, Staple Hill, Bristol, BS16 5NL. Tel. Bristol 565472.**

### Radio Receivers

**MULTIBAND RADIOS.** 12 band . . . Marine, Aircraft, LPSB, HPSB, UHF (430/470), SW1/4, MW, LW, FM, RF gain. BFO. £150. **GRUNDIG SATERLIT** £199. BFO Units, £16.50. **SHARP MW/Aircraft**, £13. Langtons, High Street, Rocester, Staffordshire. SAE lists.

### For Sale

**NEW ISSUES** of "Practical Wireless" available from April 1974 edition up to date. Price 65p post free. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0243) 55885.

### Wanted

**WANTED.** CLARE PENDAR Keyboard ASC11 Coded with strobe type KB6 or similar. Phone 0723 69127.

**WANTED.** New Valves, Transistors. Top prices, popular types. Kensington Supplies (C), 367 Kensington Street, Bradford 8, Yorkshire.

**SURPLUS???** Turn it into cash. Phone 0491 35529 (Oxon).

**WANTED NEW** Valves, transistors, I.C.s, amplifiers, receivers, televisions (Anything Useful) any quantity. Stan Willets, 37 High Street, West Bromwich. Tel: 021-553 0186.

## Service Sheets

### SERVICE SHEETS — COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p. Please send large Stamped Addressed Envelope. We can supply manuals for most makes of Colour Television Receivers by return of post.  
**B.R.C. PYE ECKO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA FERGUSON H.M.V. MARCONI AND MANY MORE**

Let us quote you. Please send a Stamped Addressed Envelope for a prompt reply. Also comprehensive T.V. repair manuals by J. M. Court. S.A.E. for details. MAIL ORDER ONLY

**G. T. TECHNICAL INFORMATION SERVICE**  
 10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA

**BELL'S TELEVISION SERVICES** for Service Sheets on Radio, TV, etc., 75p plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 65885.

**SERVICE SHEETS** for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide, from 50p and SAE. Catalogue 25p and SAE. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex.

### LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS

TV, Radio, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, Radiograms.  
 All at 75p each except Colour TV & Car Radios

Please state if circuit will do, if service sheet not in stock, large s.a.e. with all enquiries and orders otherwise cannot be attended to. Uncrossed P.O.'s or crossed P.O.'s returned if service sheets are not available. All service men, please note, we operate a same day return service, all claims of non-delivery should be made within seven days. No overseas mail please. Mail order only or phone 01-458 4882. Free TV fault tracing chart or TV list on request with order.

**C. CARANNA, 71 BEAUFORT PARK, LONDON, NW11 6BX NO CALLERS PLEASE**

**SERVICE SHEETS**, Radio TV, etc., 10,000 models. Catalogue, 24p, plus SAE with orders, enquiries. Telray, 154 Brook Street, Preston PR1 7HP.

### Educational

**GO TO SEA** as a Radio Officer. Write: Principal, Nautical College, Broadwater, Fleetwood FY7 8JZ.

## TELEVISION TRAINING

**12 MONTHS'** full-time course in Radio & TV for beginners. (GCE—or equivalent—in Maths. and English).

**26 WEEKS'** full-time course in Mono & Colour TV. (Basic electronics knowledge essential). **13 WEEKS'** full-time course in Colour TV. (Mono TV knowledge essential).

These courses incorporate a high percentage of practical training.

**NEXT SESSION** commences on January 3rd.

Prospectus from: **London Electronics College, Department B12, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.**

### Aerials

#### G2DYM AERIALS

TXers and S.W.L.'s.—Have a proper aerial system, anti-TVI, individually designed, purpose built for your particular interests, QTH and Equipment by and ex-BBC Transmitter and Aerial Engineer. Details 7" x 12" 9p SAE and 3, 9p stamps.

**LAMBDA ANTENNA STUD FARM, WHITEBALL, WELLINGTON, SOMERSET**

#### AERIALS FOR FM & TV

Types for all bands I to V available

TV UHF	Price	DX 87 Ch21-60	Price
Fuba XC 391	£38-90	DX 87 Ch21-60	£22-75
DX43 Ch21-68 FM	£14-50	Exa08 Panel Ch21-68	£11-25
Fuba Uka St. 8	£33-33	DX9-H	£22-75
DX7-H	£19-00	DX5-H	£12-50

All above have anodised alloy finish. Cables, Rotators, Masts, Lashings, M/H Amps, Dist Amps, etc. Carriage free mainland UK orders above £25. Carr. 21 otherwise.

**AUDIO WORKSHOPS LTD., 33 London Road, Southborough, Tunbridge Wells, Kent. TN4 9PB Tel: Tun. Wells (0992) 39222. Access/Barclaycard**

### Books and Publications

**SIMPLIFIED TV REPAIRS.** Full repair instructions individual British sets £4-50, request free circuit diagram. Stamp brings details unique. TV Publications (Ause PW), 76 Church Street, Larkhall, Lanarkshire.

#### RADIO BOOK SERVICE

50 Projects using IC CA3130 (R. A. Penfold)	£1-05
50 CMOS IC Projects (R. A. Penfold)	£1-05
A Practical Introduction to Digital IC's	£1-05
28 Tested Transistor Projects (R. Torrance)	£1-05
50 Projects using Relays, S.C.I.'s & R.I.C.'s (F. G. Rayer)	£1-20
How to build your own Metal & Treasure Locators (F. G. Rayer)	£0-95
Practical Repair & Renovation of Colour TVs (C. F. Miller)	£1-05
Fun & Games with your Electronic Calculator (J. Vine)	£0-95
How to build Advanced Short Wave Receivers (R. A. Penfold)	£1-30
Radio Antenna H'book for Long Distance Reception	£0-95
50 (Fe) Field Effect Transistor Projects (F. G. Rayer)	£1-05
Servicing Transistor Radio Receivers	£0-95
Solid State Short Wave Receivers for Beginners	£1-05

PRICES INCLUDE POSTAGE & PACKING... S.A.E. FOR FULL LIST  
 3 BRISTOL COURT, WICKHAM RD, BECKENHAM KENT BR5 2UW

**HOW TO START A BUSINESS.** By popular demand a fully illustrated manual has now been produced, showing, in easy, step by step, stages, how to rewind ARMATURES & FIELD COILS as used in Vacuum Cleaners, Drills and Portable Tools. Chapters on taking data, materials required, test instruments required, rewind instructions, charts, etc. How to cost instruction manual £4-00 plus 30p P & P. CWO, COPPER SUPPLIES, 102 Parrswood Road, Withington, Manchester 20, Dept. PWA.

#### THE DALESFORD SPEAKER BOOK

by R. F. C. Stephens.

This book is a must for the keen home constructor. Latest technology DIY speaker designs. Contains full plans for infinite baffle and reflex designs for 10-100 watts, also unusual centre-base system for those who want Hi-Fi to be "Heard and not seen". £1-95 (£2-20 post paid, \$5 Overseas).

**VAN KAREN PUBLISHING**  
 5 SWAN STREET  
 WILMSLOW  
 CHESHIRE

### Ladders

**LADDERS.** Varnished. 20ft 9in extd., £25-33. Carr. £1-90. Leaflet. Also alloy ext. up to 62½ft. The Ladder Centre (WLS), Halesfield (1), Telford, Salop. Tel: 586644. Callers welcome.

### Miscellaneous

#### MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination. Cassette B: 12-24 w.p.m. for professional examination preparation.

Morse by light system available. Morse Key and Buzzer Unit for sending practice. Prices each Cassette (including booklets) £4; Morse Key and Buzzer £4. Prices include postage etc., Overseas Airmail £1-50 extra.

**MHEL ELECTRONICS (Dept PW)**  
 12 Longshore Way, Milton,  
 Portsmouth PO4 8LS

**OUTSTANDING HI-FI FM TUNER**, comprises 7 transistor superhet design with Varicap tuning, AFC. Latest silicon circuitry, full coverage 88-102MHz. Supplied built and tested with metal front, panel and instruction sheet. Only £9-95 plus 30p P&P. **GREGG ELECTRONICS**, 86-88 Parchmore Road, Thornton Heath, Surrey.

#### ARMATURE & COIL WINDING ENAMELED COPPER WIRE

Only top quality materials supplied. All orders dispatched within 24 hrs.

S.W.G.	1 lb reel	1/2 lb reel
10 to 19	£2-95	£1-60
20 to 28	£3-15	£1-80
30 to 34	£3-45	£1-90
35 to 40	£3-65	£2-10

All prices are inclusive of P. & P. in U.K.

**COPPER SUPPLIES, 102 Parrswood Road, Withington, Manchester 20. Tel: 061-445 8783**

**FREE POWER TRANSISTOR** when you send 35p for list of electronic components at competitive prices. Taylor, 41 Woodhouse Hill, Fartown, Huddersfield.

**BUILD THE TREASURE TRACER MK III Metal Locator**



- Varicap tuning
- Britain's best selling metal locator kit!
- Fitted with Faraday shield.
- Speaker and earphone operation
- 4,000 already sold
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Thoroughly professional finish
- As seen on BBC1 and BBC2 TV
- You only need soldering iron, screwdriver, pliers and snips
- 5V transistor circuit

Send stamped, addressed envelope for leaflet

Complete Kit £15-95 Built & tested £20-95  
 Post £1-20 + £1-37 VAT Post £1-20 + £1-77 VAT

**MINIKITS ELECTRONICS,**  
 6 CLEVELAND ROAD,  
 LONDON, E18 2AN (Mail order only)

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from P.V.C. faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low 90p, chassis punching facilities at very competitive prices. 400 models to choose from, free literature (stamp would be appreciated). **BAZELLI**, Dept No 25, St. Wilfrid's, Foundry Lane, Halton, Lancaster LA2 6LT.

### GOT YOURS YET?

**FREE DX** from firing WHISTLES and CW QRM with a **TUNABLE AUDIO NOTCH FILTER** only £7-90  
**ADD 100-600 KHz** with an **LF CONVERTER**. Antenna tuning, feeds 3-5-4 MHz receiver only £8-80  
**FIND DX** with a **CRYSTAL CALIBRATOR**. EQUAL LEVEL 1 MHz, 100, 25 KHz to VHF only £13-80  
**Make SURE** your **ANTENNA IS OKAY** with an **ANTENNA NOISE BRIDGE**, 1-150 MHz only £8-20  
**EXPLORE** 10-150 KHz with a **VLF RX** only £9-70  
**PLAY** your favourite **TUNE** on a **PROGRAMMABLE CHIME**, for DOORBELL or car only £17-90  
**ACCURATE** time with a **60 KHz TIME RECEIVER**, ferrite rod, logic and audio outputs only £13-70  
**LINEAR OKAY?** Two Tone Oscillator only £7-49  
**SOUND** one "S" point **LOUDER** with a **SPEECH COMPRESSOR**, switched Hi-Fi/DX only £8-80  
**LF SIG GEN**, 10Hz-200KHz, sine/sq only £9-80

Each easy-assembly kit includes ALL parts, printed circuit, case, battery, screws, etc., instructions, postage, money back assurance. **SEND TODAY.**

#### CAMBRIDGE KITS

45 (P2) Old School Lane, Milton, Cambridge.

**IMMEDIATE BY RETURN DELIVERY.** Large range of miniature synchronous motors, many speeds 1 rev per hour to 1 rev per 2 days. £1-10 to £2-50 each. 3 and 4 digit mechanical counters, 45p to 85p. 10 amp micro switches at 20p. SAE for list. **WALES (ELECTRICAL) LTD., Queen St., Newton Abbot.**


#### ENAMELED COPPER WIRE

swg	1 lb	8oz	4oz	2oz
14-19	2-40	1-20	-69	-59
20-29	2-45	1-60	-82	-50
30-34	2-80	1-70	-89	-64
35-40	2-85	1-90	1-04	-75

Inclusive of P&P and VAT.

SAE brings Catalogue of copper and resistance wires in all coverings.

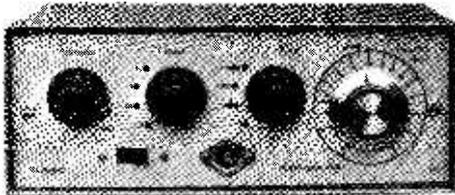**THE SCIENTIFIC WIRE COMPANY**  
 PO Box 30, London E4 6JY  
 Reg. Office: 22 Coningsby Gardens,



**HIGH QUALITY  
Very Low Distortion  
Audio Signal Generator**

**AN IDEAL INSTRUMENT FOR HI-FI TESTING**

A J. Linsley Hood design

**PRICES**, assembled instrument, plastic case £23, metal case £26. (Kit, £19.50). Tax extra 8%, P.P. and Ins. £1. Specification. Frequency range: 10 Hz-100 kHz in 4 steps. Output: 10mV-1 volt in 3 steps. Sine- and Square-wave forms: Dist. below .02%. Attenuator: Powered by 5V battery.

Other instruments: Millivoltmeter, Frequency Meter, Reg. P.S. Units. THD Analyser. Also Hi-Fi Amp kits 10-100 F.M. Tuners, Kei Speaker Units.  
S.A.E. for further information to:

**TELERADIO ELECTRONICS**

325, Fore Street, Edmonton, London, N.9. Telephone: 01-807-3719.

**KIT OF PARTS** for Nelson-Jones Tuner, Railway model controller, Capacitor discharge power supply etc. Semiconductor knobs, meters, resistors, capacitors. S.A.E. for price list. R. B. ELECTRONICS, 24 Springfield Park, Holyport, Maidenhead 39798.

**GAS-SMOKE SENSORS. COMPLETE CIRCULAR UNITS.** Brand New, uses TGS 105 sensor runs from 24v DC. Supply can be modified to 12 volt, identical unit described in P/E Sept. '76. Complete with Data + MOD Sheets £12.96.

IC's 555 Timer 45p. 5-µa 739 dual preamp ceramic 14 pin DIL IC's £1.50. 5-TILL 116 OPTO isolator 6 pin DIL £1.50.

**TRANSISTORS**, 10 AC128 £1.50, 10 AC176 £1.50, 10 AC188 £1.50, any mixture, all devices are full spec. and guaranteed. No remarks, quantity discounts, available on request. Also a few CMOS CD4001 in packs of 25 for £3 per pack in antistatic tube unsealed. **PROPMT DELIVERY.** All prices include VAT + PP To: RF SERVICES, 50-51 Deptford Broadway, London SE8. 01 692 4284.

3½ DIGIT DVM MODULE kit, Autozero, autopolarity only £37.50. SAE details. MLC, 116 College Road, Southwater, Horsham, Sussex.

**SINTEL KITS, COMPONENTS, CMOS etc.**

MOT. CMOS Databk 3.50 RCA CMOS Databk. 5.45  
6800 Appl. Man. 12.95 Z80 Ass. Lang. Prog.Man. 7.50  
NS TTL Databk. 2.10 Z80-CPU Man. 5.60

All Items CWO (Books-No VAT) 35p p&p.  
Full range in our FREE CATALOGUE which will be sent by return. **SINTEL, P.O. BOX 75F, 209 Cowley Road, Oxford Tel.: (0865) 49791.**

**ENAMELLED COPPER Wire**—odd reels—14 to 46 gauges. £1.50 a lb collected. SAE list of sizes. Punford, 2 Elliswick Road, Harpenden, Herts.

**H. M. ELECTRONICS**

275a FULWOOD ROAD, BROOMHILL, SHEFFIELD S10, 3BD.

**BEC CABINETS** (illus'd)



**METAL CASES  
DRY TRANSFER LETTERING**

Send 15p for leaflets (Refundable)  
Trade enquiries invited

**Electrical**

**STYLI, CARTRIDGES, AUDIO LEADS**, etc. For keenest prices send SAE for free list to: Felstead Electronics (PW), Longley Lane, Gatley, Cheadle, Cheshire SK8 4EE.

**NOTICE  
TO  
READERS**

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.*

**ORDER FORM PLEASE WRITE IN BLOCK CAPITALS**

Please insert the advertisement below in the next available issue of Practical Wireless for ..... insertions.

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).


NAME .....

ADDRESS .....

.....

Send to: Classified Advertisement Manager

**PRACTICAL WIRELESS,**  
G.M.G. Classified Advertisement Dept., Rm. 2337,  
King's Reach Tower, Stamford Street.  
London SE1 9LS Telephone 01-261 5846

Rate  
20p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered office: King's Reach Tower, Stamford Street, London SE1 9LS

# BUILD YOUR OWN HI-FI SYSTEM

*Satisfaction! Economy!  
Pleasure!*

Enjoy the satisfaction of building your own hi-fi system and save your money into the bargain.

Starting with this issue, Practical Hi-Fi & Audio shows you how to construct an amplifier, bookshelf loudspeakers and a record turntable, all from readily available components.

Inside this issue: building a pair of bookshelf loudspeakers.

## SPECIAL SUPPLEMENT

What was new at the Harrogate Audio Show, the Audio Fair at Olympia and the High Fidelity 77 Autumn Exhibition.

## SPECIAL CHRISTMAS OFFER

**A third BASF LH Super  
Cassette FREE!**  
When you buy two!  
**ALSO 100 BASF Checkpoint  
Cassette Care Kits to be won!**

**PRACTICAL  
HI-FI &  
AUDIO**

December issue 40p  
On sale Friday, November 18

# Sparkrite mk2

## Capacitive discharge electronic ignition kit



- \* Smoother running
- \* Instant all-weather starting
- \* Continual peak performance
- \* Longer coil/battery/plug life
- \* Improved acceleration/top speeds
- \* Optimum fuel consumption

Sparkrite Mk. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm: It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

### THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

### OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

**CALLERS WELCOME.** For Crypton tuning and fitting service — phone (0922) 33008.

**PRICES INCLUDE VAT, POST AND PACKING.**

### IMPROVE PERFORMANCE & ECONOMY NOW

Note—Vehicles with current impulse tachometers (Smiths code on dial RV1) will require a tachometer pulse slave unit. £3.35 inc. V.A.T. p & p.

E.D.A. 82 BATH STREET, WALSALL, WS1 3DE.

**POST TODAY!**

**Quick installation  
No engine modification  
required**

Electronics Design Associates, Dept., P.W.12  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652

Name .....  
Address .....

	QUANTITY REQD.
Mk. 2 DIY Ass. Kit @ £11.80	
Mk. 2 Ready Built Negative Earth @ £14.97	
Mk. 2 Ready Built Positive Earth @ £14.97	
Ignition Changeover switches @ £4.30	
R.P.M. Limit systems in above units @ £2.42	

I enclose cheque/PO's  
for £

Cheque No.

Send SAE if brochure  
only required.



# WATFORD ELECTRONICS

(Continued from opposite side)

DIODES		*BRIDGE RECTIFIERS		SPEAKERS	
AA119	15	1A50V	20	8Ω 0-3W	2 1/2" x 2 1/2"
AAZ15	15	(plastic case)		2 1/2" x 2 1/2"	65
AEY11	60	1A50V	20	40Ω 2-5"	58
BA100	10	1A100V	22	64Ω 2-5"	65
BA102	10	1A200V	25	8Ω 5W	190
BY100	24	1A600V	26	7" x 4"	205
BY126	14	1A500V	34	16Ω 5W	
OA9	75	2A200V	35	7 x 4"	
OA47	12	2A100V	44		
OA70	12	2A200V	46		
OA78	12	2A100V	53		
OA81	15	2A100V	95		
OA85	12	4A1200V	75		
OA90	6	4A400V	79		
OA91	6	4A1600V	105		
OA95	6	4A800V	120		
CA200	8	6A100V	73		
CA202	8	6A200V	78		
IN914	4	4A600V	85		
IN916	5	BY164	56		
IN4001/2*	5	VM18	40		
IN4003*	6				
IN4004/5*	6				
IN4006/7*	7				
IN4148	4				
IS44	20				
3A/100V*	18				
3A/400V*	20				
3A/600V*	27				
3A/1000V*	30				
6A/800V	50				
SCR's Thyristors		ZENERS		LAMP HOLDERS AND LAMPS*	
1A50V	38	Rng: 3.3V-33V		LES HOLDER Domes shaped, Red, Blue, Green, Yellow, White	16
1A100V	42	400mW	9	MES BULBS 6v and 12v	9
1A200V	47	1-3W	17	MES HOLDERS Chrome cover, Red or Amber, Jewelled top	58
1A400V	52			LES OR MES Batten Holders	10
1A600V	70			MES BULBS 3-5V 6V 12V	9
3A50V	43			NEONS Mains, Sealed with Resistor, Sq. Top, Red or Grn. Round Top Red 2 1/2 Neon Open with leads, 95V AC	9
3A200V	60				
3A400V	110				
3A600V	120				
5A400V	120				
7A400V	125				
8A400V	150				
BT106	150				
C106D	55				
TIC44	25				
TIC45	45				
2N4444	191				

OPTO ELECTRONICS*		SWITCHES*	
LEDs + Clip	7 Segment Displays	TOGGLE 2A 250V	460
TIL209 Red	5-LT-01 Futaba	SPST	28
TIL211 Grn	TIL312-3 C.A. An	DPST	34
TIL212 Yellow	TIL313 3" C.Ch	DPDT	38
0-2" Red	TIL321 5" C.A. An	4 pole on/off	54
0-2" Yellow, Grn, Amber	TIL322 5" C.Ch		
OCP70	DL704 3" C.Ch		
ORP12	DL707 3" C.Anod		
ORP17	DL717 16" An		
2N5777	FND357		
	XAN351 3" Green		
	XAN825 6" Green		
	MINITRON 3015F		
	DRIVERS		
	75491 75; 75492		

VOLTAGE REGULATORS*		SLIDE 250V	
723 DIL	45 Plastic Case	1A DP	14
TBA625B	95 78L82A WC 1A 8V	1A DP C O	16
T03 Can Type	LM320-12	1A DP	13
1A 5V	170 MC7805 1A 5V	4 pole 2-way	24
1A 12V	130 MC7812 1A 12V		
1A 15V	180 MC7815 1A 15V		
1A 18V	190 MC7818 1A 18V		
1A 20V	210 FT8N2A 1A 24V		
LM309H	140 Variable Type		
LM323K	LM325N ± 15V		
MVRS	LM325N ± 12V		
MVR12	LM327N ± 5-12		
1A -5V	220 LM317K 20W 1-5A		
1A -12V	220 + 1-2V to 37V		

SWITCHES* PUSH BUTTON:	
Miniature Non Locking	25
Push to Make 15p	25
ROCKER (black) 10A 250V	28
ROCKER: Illuminated (white) lights when on, 2A 240V	72
ROTARY: (Adjustable Stop) 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way	45
ROTARY: Mains 250V AC, 4 Amp	42

KNOBS* fit 1" shaft with grub screws, except K2 (push fit) & K8 (for sliders).	
K1 Black or White pointer type	8
K2 Silver/Black Plastic	12
K4 Black serrated, Metal top with line indicator 33mm diam.	22
K4A As above but 25mm diam.	20
K5 Black fluted metal top and skirt calibrated 0-10, 37mm diam.	26
K6 PK2 as K5, pointer on skirt.	26
K7 Black, knurled, tapered, Metal top & skirt, Calif. 0-10, 30mm dia.	25
K8 Black or silvered for slider pot	10
K12 Aluminium plastic with line indicator 22mm	16
K15 Black plastic ribbed body, white indicator line, 15mm diam, tapered coloured insert tops, Red, Blue, Yellow 19mm height.	16
K16 As above but 23mm diam	20

**COLOUR ADAPTOR** for your existing Black & White TV GAMES. Complete Kit including PCBs, UHF/VHF Modulators. Price: 989p incl. VAT (p&p 45p). Colour Encoder and UHF/VHF Modulator only 595p incl. VAT. UHF or VHF Modulators Modulated £3.50 incl. VAT.

**SPECIAL OFFER**  
The "Olympic" TV Games Kit £25.49 incl. VAT (95p p&p insured). "OLYMPIC" Kit in colour £34.85 incl. VAT (95p p&p insured). "Sure Fire Rifle" Kit for Olympic £9.50 incl. VAT 40p p&p. "Sure Fire Rifle" Kit for other games £10.50 incl. VAT + p&p.  
TV GAMES IC AY-3-8500 £4.50\* AY-3-8550 £7.50\*.

**STOP PRESS . . .** Watford Electronics announce the introduction of their "ECONOGAME" the obvious answer to CHEAP yet reliable TV GAMES. This simple to build Kit comes complete with AY-3-8500 IC, Fibre Glass PCB, Semiconductors and full instructions. All you need to complete the Kit is, two pots, switches, loudspeaker and control boxes. The finished board fits our NJSF1 Box (£1.85\*) to complete an attractive yet inexpensive TV Games Unit. Price only £10.45 incl. VAT (45p p&p insured).

JACK PLUGS		SOCKETS		VEROBOARD* Pitch			
Screened chrome	Plastic body	Open metal	Moulded with break	0-1	0-15 (copper clad)	0-15 (plain)	
2-5mm 12p	8p	8p	8p	21 x 3 1/2"	36p	29p	
3-5mm 15p	10p	8p	8p	21 x 5"	43p	39p	
MONO 23p	15p	13p	20p	35 x 3 1/2"	43p	40p	
STEREO 31p	18p	15p	24p	35 x 5"	48p	53p	
				35 x 7"	134p	107p	
				35 x 17"	173p	143p	
				45 x 17"	222p	145p	
DIN		Plugs		Sockets		In line	
2PIN Loudspeaker	3, 4 & 5 pin Audio	13p	8p	20p			
CO-AXIAL (TV)		14p	14p	14p			
PHONO		10p	8p 1-way				
assorted colours metal screened	8p 2-way	12p	15p 3-way				
BANANA		4mm 10p	10p				
	2mm 10p	10p	10p				
	1mm 8p	8p	8p				
	3mm 8p	8p	8p				
WANDER		3mm 8p	8p				

**VERO WIRING SPOOL\* 365p**  
We are stockist of all Vero Products. Send SAE for our free list.  
**BLOB BOARDS\***  
We now stock the full range of Blob Boards.

# INDEX TO ADVERTISERS

ACE Mailtronix Ltd. ....	550	Electronic Brokers ....	552	Newmart Electronics ....	618
A. H. Supplies ....	608	Electronics Design Associates ....	629	Orchard Electronics ....	626
Alben Engineering ....	618	Electronic Mail Order ....	552	Partridge Electronics Ltd. ....	580
Alcon Instruments ....	546	Electrovalue ....	554	P.B. Electronics ....	560
Ambit International ....	580	Elvins Electronic Musical Instruments ....	608	Radio Book Services ....	627
Antex Ltd. ....	579	Fidelity Fastenings ....	622	Radio Component Specialists ....	551
Astro Alarms ....	554	G3DYM Aerials & Project ....	627	Radio Exchange Ltd. ....	cover iii
Astro Electronics ....	620	G.T. Technical Information Service ....	627	R. F. Products ....	632
Bandridge ....	615	Greenweld Electronics ....	550	R. F. Services ....	628
Bamber B. ....	576	H. A. C. Short-Wave Supplies ....	552, 625	R. S. C. (Hi-Fi) ....	547
Barclay Electronics ....	597	H. L. Smith ....	556	R. S. T. Valve Mail Order Co. ....	621
Baron Electronics ....	620	Harversons Surplus ....	554	Radio Society of Gt. Britain ....	622
Barrie Electronics ....	558	Heathkit ....	558	Radio & T.V. Components Ltd. ....	549
Bentley Acoustic Corp. ....	616	Henry's Radio ....	632	Saga Ltd. ....	561
Bi-Pak Ltd. ....	562, 563	Home Radio ....	550	Saxon Entertainments ....	617
Bi-Pre-Pak Ltd. (Stirling Sound)....	619	I.L.P. Electronics Ltd. ....	611, 623	Scientific Wire Co., The ....	627
Birkett J. ....	608	Jones R Supplies ....	626	Selray Book Co. Ltd. ....	616
British National Radio & Electronics School ....	546, 559, 625	K. K. S. Trading ....	560	Sentinel Supply ....	620
J. Bull (Electrical) Ltd. ....	557	Linear Products ....	622	Sintel ....	628
Bush Meissner ....	552	London Electronic College ....	627	Sonic (Hi-Fi) ....	624
Butterworths ....	546	Logic Leisure (Telecraft) ....	612	Southern Valve Co. ....	624
Caranna C. ....	627	Lewis Radio ....	555	S. R. L. Minimeter (Sinclair) ....	575
Cambridge Kits ....	627	Lynx Electronics ....	555	Swanley Electronics ....	624
Chromatronics ....	607	Manor Supplies ....	554	Technomatic Ltd. ....	576
Chromasonics ....	553	Maplin Electronic Supplies ....	cover iv	Teleradio ....	628
Colomor (P.C. Radio) ....	612	Marco Trading ....	596	Tempus ....	556
Continental Specialists ....	605	Marshall A. & Sons ....	618	T. K. Electronics ....	626
Copper Supplies ....	627	Mhel Electronics ....	627	Trampus Electronics ....	580
Cox Radio (Sussex) Ltd. ....	626	Minikits Electronics ....	627	Tudor Rees (Vintage Services) ....	626
C. R. Supply Co. ....	626	Multicore Solders (Bib Hi-Fi) ....	548	Van Karen Publishing ....	627
Crescent Radio Ltd. ....	548			Vero Electronics ....	548
Crofton Electronics ....	625			Watford Electronics ....	630, 631
Dawes ....	560			West London Direct Supplies ....	624
Dziubas M. ....	625			Wilmslow Audio ....	556

Head Office and Warehouse  
 44A WESTBOURNE GROVE  
 LONDON W2 5SF  
 Tel: 727 5641/2/3

# Z & I AERO SERVICES LTD.

Please send all correspondence and Mail-Orders to Head Office

Retail Shop  
 85 TOTTENHAM COURT ROAD  
 LONDON W1  
 Tel: 580 8403  
 Open all day Saturday

## AC/DC TAUT SUSPENSION MULTIMETERS (Made in USSR)




TYPE	U4312	U4313	U4315
Sensitivity D.C.	667 o.p.v.	20,000 o.p.v.	20,000 o.p.v.
Sensitivity A.C.	667 o.p.v.	2,000 o.p.v.	2,000 o.p.v.
D.C. Current	300 $\mu$ A-6A	60 $\mu$ A-1.5A	50 $\mu$ A-2.5A
A.C. Current	1.5mA-6A	0.6mA-1.5A	0.5mA-2.5A
D.C. Volts	75mV-900V	75mV-600V	75mV-1000V
A.C. Volts	300mV-900V	15V-600V	1V-1000V
Resistance	0-02-3k $\Omega$	1K-1M	300 $\Omega$ -500k $\Omega$
Capacity	—	0.5 $\mu$ F	0.5 $\mu$ F
Accuracy	1% D.C., 1.5% A.C.	1.5% D.C., 2.5% A.C.	2.5% D.C., 4% A.C.

Price complete with pressed steel carrying case and test leads.

£14.50      £17.50      £14.95

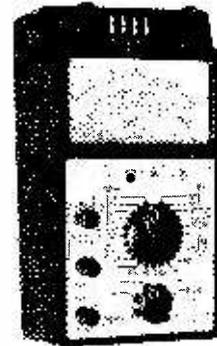TYPES U4313 & U4315 PROVIDED WITH ANTI-PARALLAX MIRROR SCALES



### TYPE U4341

Sensitivity:  
 16700 $\Omega$ /V D.C.,  
 3300 $\Omega$ /V A.C.

Ranges:  
 D.C. current: 0.06-  
 0.6-6-60-600mA  
 A.C. current 0.3-3-30-  
 300mA  
 D.C. Voltage: 0.3-1.5-  
 6-30-60-150-300-  
 900V  
 A.C. Voltage: 1.5-7.5-  
 30-150-300-750V  
 Resistance: 2-20-  
 200k $\Omega$ -2M $\Omega$   
 Transistor collector  
 cut-off current 60 $\mu$ A  
 Transistor D.C. current  
 gain in two  
 ranges 10-350  
 Accuracy: 2.5% D.C.  
 4.0% A.C.  
 5% D.C.  
 current gain  
 Power supplies: 4.5V  
 battery  
 (Eveready 1289)

Complete with steel carrying case, test lead, battery and instruction manual £14.50

**NO OVERLOAD PROTECTION IS INCORPORATED IN THESE INSTRUMENTS**



### TYPE U4324

Sensitivity: 20,000 $\Omega$ /V D.C.  
 4,000 $\Omega$ /V A.C.

D.C. Current: 0.06-0.6-60-600mA-3A  
 A.C. Current: 0.3-3-30-300mA-3A  
 D.C. Voltage: 0.6-1.2-3-12-30-60-120-600-1200V  
 A.C. Voltage: 3-6-15-60-150-300-600-900V  
 Resistance: 500 $\Omega$ -5-50-500k $\Omega$   
 Accuracy: D.C. 2.5%; A.C. 4% (of F.S.D.)

PRICE complete with test leads and fibreboard storage case £14.50

THE ABOVE PRICES ARE EXCLUSIVE OF VAT (at present 8%) HANDLING AND POSTAGE CHARGES £1.25 PER INSTRUMENT

OUR NEW 1976/1977 CATALOGUE IS NOW READY AND WILL BE SENT ON RECEIPT OF REMITTANCE FOR £0.30

**BULK PURCHASE — EXCLUSIVE TO HENRY'S**  
**ALLOWS US TO SELL AT SUCH FANTASTIC PRICES!**

**QUALITY ITEMS**  
 Compare performance and specification with units costing 3 times as much!

**DIGITAL 24 HOUR CLOCK**  
 WITH BUILT-IN ALARM

AS USED IN BRAUN DIGITAL CLOCKS

**NORMALLY £24 WITH CASE**

- SILENT RUNNING
- LARGE ILLUMINATED NUMERALS
- AC MAINS • SIZE 6 $\frac{3}{8}$  x 2 $\frac{3}{8}$  x 2 $\frac{3}{4}$

Mechanism only: £6.00  
 Mechanism and case: £7.99  
 Complete unit: £8.99

THREE FOR £16.50      THREE FOR £22      THREE FOR £25  
 POST & VAT INCLUSIVE

Send cheque, P.O./M.O. for the correct amount which includes VAT and P & P or pay by Access/Barclaycard. Send name, card number (if applicable) and address to:

**HENRY'S RADIO**  
 404 EDGWARE ROAD,  
 LONDON W2

TRADE & EXPORT ENQUIRIES contact MIKE BAKER 01-723 1008

**HENRY'S Radio**

FREE ILLUSTRATED EQUIPMENT & COMPONENT LIST  
 S.A.E., 9 $\frac{1}{2}$ " x 6 $\frac{1}{2}$ " 12 $\frac{1}{2}$ p STAMP

**Interested in V.H.F.?**

Send for **FREE CATALOGUE**

MODULES FOR 2 METRE RECEIVERS AND TRANSMITTERS, 4 METRE RECEIVERS, FRONT ENDS, PRODUCT DETECTORS, FM DISCRIMINATORS, V.F.O.'s + CB RECEIVERS (FOR EXPORT)

**R. F. PRODUCTS**

Ring 647 7898 or  
 Write: 19 CHURCH LANE WALLINGTON, SURREY SM6 7NQ U.K.

**IT'S EASY WHEN YOU KNOW!**

To avoid missing your copy of PRACTICAL WIRELESS—simply complete this order form and hand it to your newsagent.

**ORDER FORM**

To: ..... (name of newsagent)  
 Address .....

Please reserve/deliver every month one copy of PRACTICAL WIRELESS until further notice.


My Name .....

Address .....

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, POOLE, Dorset BH15 1JG. Printed in England by Index Printers, Dunstable, Beds. Sole Agents for Australia and New Zealand—Gordon and Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T. and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# RADIO EXCHANGE LTD.

## NEW ELECTRONIC MASTER KIT

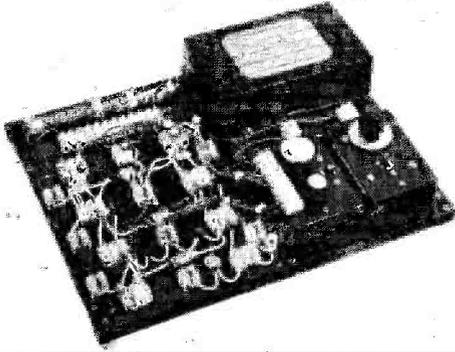


WITH SPECIAL MULTI-BAND V.H.F. TUNER MODULE TO CONSTRUCT. A completely Solderless Electronic Construction Kit, with ready drilled Bakelite Panels, Nuts, Bolts, Wood Screws etc. Also in the kit: Transistors, Capacitors, Resistors, Pots, Switches, Wire, Sleeving, Knobs, Dials, 5" x 3" Loudspeaker and Speaker Case, Crystal Earpiece, etc. Also ready wound Coils and Ferrite Rod Aerial. These are the Projects you can build with the components supplied with the kit, together with comprehensive Instruction Manual Pictorial and Circuit Diagrams.

**PROJECTS:** V.H.F. Tuner Module ★ A.M. Tuner Module ★ M.W. L.W. Diode Radio ★ Six Transistor MultiBand V.H.F. Earpiece Radio ★ One Transistor M.W. L.W. Radio ★ Two Transistor Metronome with variable beat control ★ Three Transistor and Diode Radio M.W. L.W. ★ Four Transistor Push Pull Amplifier ★ Eight Transistor MultiBand V.H.F. Loudspeaker Receiver ★ Variable A.F. Oscillator ★ Jiffy MultiTester ★ Four Transistor and Diode M.W. L.W. Radio. ★ A.F. R.F. Signal Injector ★ Five Transistor Push Pull Amplifier ★ Sensitive Hearing Aid Amplifier ★ Three Transistor and Diode Short Wave Radio ★ Signal Tracer ★ Three Transistor Push Pull Amplifier ★ One Transistor Class A Output Stage to drive Loudspeaker ★ Sensitive Transistor Pre-Amp ★ Transistor Tester ★ Sensitive Three Transistor-Regenerative Radio ★ Four Transistor M.W. L.W. and Diode Tuner ★ Five Transistor M.W. L.W. Trawler Band Regenerative Radio ★ Five Transistor V.H.F. MultiBand Tuner ★ Three Transistor Code Practice Oscillator ★ Five Transistor Regenerative Short Wave Radio ★ Four Transistor and two Diodes M.W. L.W. Loudspeaker Radio ★ Seven Transistor M.W. L.W. Radio with Loudspeaker Push Pull output ★ One Transistor Home Broadcaster. **£14.99 + P & P £1.10**
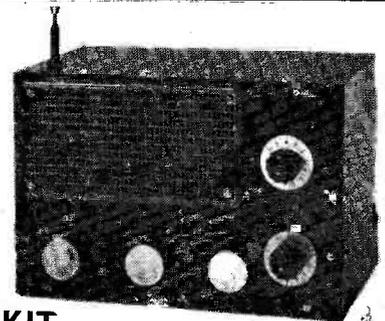
## NEW ROAMER TEN MODEL R.K. 3


**MULTIBAND V.H.F. AND A.M. RECEIVER. 13 TRANSISTORS AND FIVE DIODES. QUALITY 5" x 3" LOUDSPEAKER.**  
 WITH Multiband V.H.F. section covering Mobiles, Aircraft, T.V. Sound, Public Service Band, Local V.H.F. Stations, etc. and Multiband A.M. section with Airspaced Slow Motion Drive Tuning Capacitor for easier and accurate tuning, covering M.W.1, M.W.2, L.W. Three Short Wave Bands S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in Ferrite Rod Aerial for Medium Wave, Long Wave and Trawler Band, etc., Chrome Plated 7 section Telescopic Aerial, angled and rotatable for peak Short Wave and V.H.F. reception. Push-Pull output using 600mW Transistors. Gain, Wave-Change and Tone Contr-ols. Plus two Slider Switches. Negative Feedback circuit and SPECIAL POWER BOOSTER SOCKET AND RESISTOR, to virtually double gain if required. Powered by P.P.9—9 volt Battery.

Complete kit of parts including carrying strap. **£14.79 + P & P £1.10**  
 Building Instructions and operating Manuals.


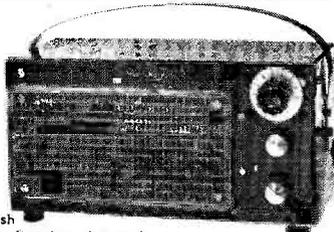
## NEW MODEL R.K.1

MultiBand A.M. Receiver. M. W. L. W. Trawler Band and Three Short Wave Bands. Seven Transistors and Four Diodes. Push Pull Output stage. 5" x 3" Loudspeaker. Internal Ferrite Rod Aerial. Kit includes all parts to build it up including Carrying Strap, Rubber Feet and ready-drilled Panels. Comprehensive Instruction Manual for stage by stage construction. Uses P.P.9 Nine Volt Battery.




**£8.99 + P & P 90p**

## ELECTRONIC CONSTRUCTION KIT
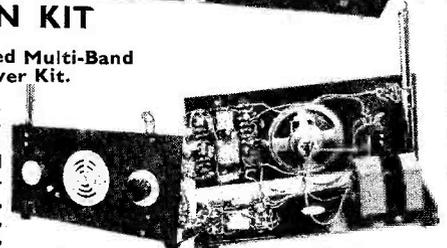
### E.C.K. 2 Self Contained Multi-Band V.H.F. Receiver Kit.


8 transistors and 3 diodes. Push pull output. 3in. loudspeaker, gain control, 7 section chrome plated telescopic aerial V.H.F. tuning capacitor, resistors, capacitors, transistors, etc. Will receive T.V. sound, public service band, aircraft, V.H.F. local stations, etc. Operates from a 9 volt P.P. 7 battery (not supplied with kit)




Complete kit of parts **£7.95 + P & P and Ins. 90p**
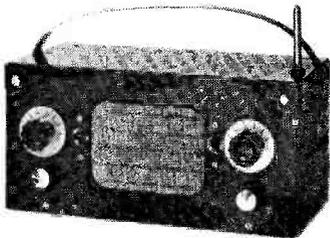
## NEW MODEL R.K.2

MW, LW and Air Band Receiver. Eight Transistors and Four Diodes. 3" Loudspeaker, Telescopic Aerial, Internal Ferrite Rod Aerial. Complete with Carrying Strap, and ready-drilled Panels and all components necessary for construction. A sensitive Receiver with the additional luxury of an Air Band section to pick up Aircraft from many miles away. Full Instruction Manual enables stage by stage construction. Uses P.P.9 Nine Volt Battery.



**£9.99 + P & P £1.10**

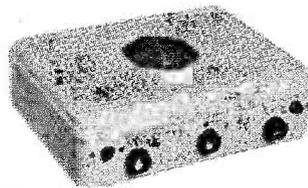

## EDU-KIT MAJOR COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

Complete kit of parts including construction plans Total building costs

**£9.99**

+ P & P and Ins. £1.10

- 5 Transistor Push Pull Amplifier
- 7 Transistor Loudspeaker. Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- 24 Resistors
- Earpiece
- 2 Slider Switches
- 21 Capacitors
- Mica Baseboard
- 1 Tuning Condenser
- 10 Transistors
- 3 12-Way Connectors
- 1 yard of sleeving, etc.
- 5" x 3" Loudspeaker.
- 2 Volume Controls
- 3 Knobs
- Ready Wound MW/LW/SW Coils
- Ferrite Rod
- 66 yards of wire

## E.V.6.

Build this exciting new design. E.V.6. 6 Transistors and 2 diodes. MW/LW. Powered by 9V battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3in. loudspeaker. Attractive case with red speaker grille. Size 9in. x 5½in. x 2½in. approx. All parts including Case and Plans.



Total Building Costs **£5.95 + P & P and ins. 90p**

**ALL PRICES INCLUDE VAT**

## V.H.F. AIR CONVERTER KIT

Build this converter kit and receive the aircraft band by placing it by the side of a radio tuned to medium wave or the VHF band and operating as shown in the instructions supplied free with all parts.

Uses a retractable chrome plated telescopic aerial, gain control, V.H.F. tuning capacitor, transistor, etc. All parts including case and plans



**£4.95 + P & P and Ins. 60p**

## To: RADIO EXCHANGE LTD

61A High Street, Bedford MK40 1SA

Tel.: 0234 52367 REG NO. 788372

- Callers side entrance "Lavells" Shop.
- Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

I enclose £..... for.....

Name .....

Address .....

PW1277

# MAPLIN

TRUSTED  
ORDERED  
1/1/60

in a modern world of electronics

## 100W RMS STEREO DISCO

A genuine 100W RMS per channel (Both channels driven) stereo disco with auto fade on microphone, VU meters, full monitoring and cueing facilities and a very high quality light show. Complete construction booklet MES41 price 25p. Cabinet comes complete with lid and carrying handles.



## T.V. GAME

A fascinating TV game kit that plays football, tennis, squash and practice for only £21.59. Reprint of construction details 35p. Add-on rifle kit only £10.60.

## WIDE RANGE OF COILS & CHOKES

Component section in our catalogue includes a wide range of coils, pot cores, ready-wound coils and chokes from microHenries to Henries, plus ranges of Denco coils and i.f. transformers etc.



## ELECTRONIC ORGAN

The only organ you can build in stages and tailor to your requirements as you go along—and at each stage you'll have a fully working instrument! We haven't got the gimmicks yet—(they're coming soon) but we have got the most beautiful sounds—you won't find them on any organ less than twice our price. So get our MES50 series leaflets now! 65p buys the three available so far.



## 10 CHANNEL STEREO GRAPHIC EQUALISER

A new design with no difficult coils to wind, but a specification that puts it in the top-flight hi-fi class. All this for less than £70 including fully punched and printed metalwork and woodwork. Send for our component schedule now. Full construction details price 40p.



Who says the Maplin Catalogue's worth having?

"in our 'musts' for readers-to-collect list"—P.E.

"contains . . . just about everything the DIY electronics enthusiast requires"—P.W.

"probably the most comprehensive catalogue we have ever come across"—E.E.

"has been carefully prepared and is very well presented.—R.E.C.

"make the job of ordering components an easy, accurate and enjoyable pastime"—P.W.

"Only one word describes the publication—superb!" E.T.I.

OVER 60,000 COPIES SOLD DON'T MISS OUT! SEND 60p NOW

MAPLIN ELECTRONIC SUPPLIES  
P.O. Box 3, RAYLEIGH, ESSEX SS6 8LR  
Telephone: Southend (0702) 715155

Shop: 284 London Road,  
Westcliff-on-Sea, Essex.

(Closed on Monday)  
Telephone: Southend  
(0702) 715157

Our bi-monthly newsletter keeps you up to date with latest guaranteed prices—our latest special offers—details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

POST THIS COUPON NOW  
FOR YOUR COPY OF OUR  
CATALOGUE PRICE 60p

Please rush me a copy of your 216 page catalogue. I enclose 60p, but understand that if I am not completely satisfied I may return the catalogue to you within 14 days and have my 60p refunded immediately.

NAME .....

ADDRESS.....



PW 12