

FOR THE RADIO ENTHUSIAST...


Practical Wireless

SEPTEMBER 1981

Australia \$1.25
New Zealand \$1.30
Malaysia \$4.50
IR 90p (inc. VAT)

65p

BEGINNER'S SHORT-WAVE RECEIVER

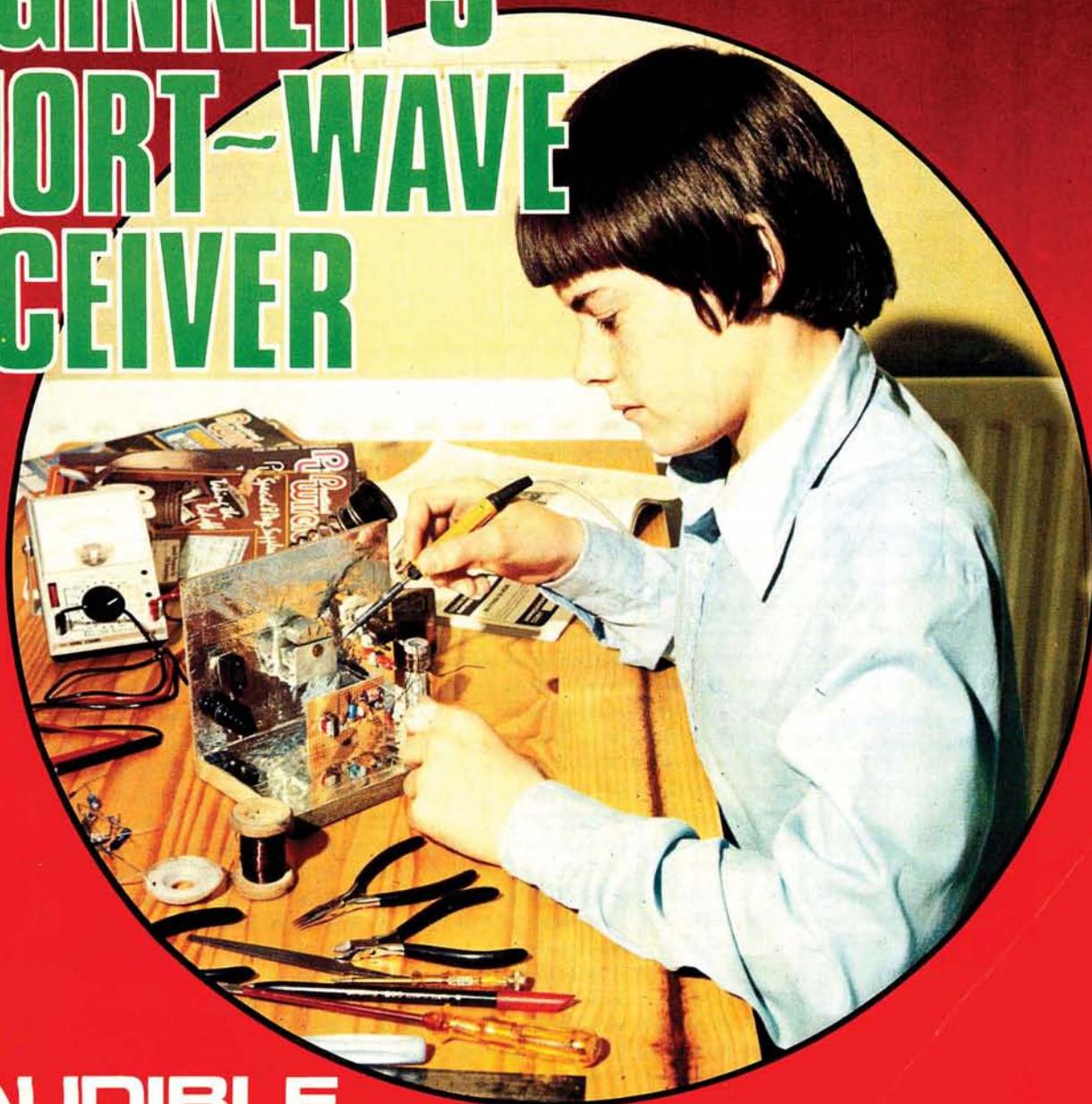

also **AUDIBLE
FIELD-STRENGTH METER**
and **VHF MOBILE ANTENNAS**

Bredhurst electronics

HIGH ST., HANDCROSS, W. SUSSEX O444 400786

H.F. TRANSCEIVERS



FT 101Z MK III FM

£529

FT 101ZD Mk III FM

£599

inc. VAT.

2M FM MOBILES

NEW



A very compact 25W 2m FM Mobile with 5 memories and scanning. Phone for price.

TRIO TR 7730

HANDHELDS FOR 2M



NEW

YAESU FT 208R

£190

AIRBAND RECEIVERS



R517

£49.50 inc. VAT.

Tunes 118-144 MHz

H.F. RECEIVERS




TRIO R1000

£305

inc. VAT & carriage

V.H.F. SCANNERS

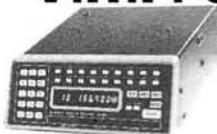

SX 200N

£264 inc. VAT & carriage



BEARCAT 220FB

£258 inc. VAT & carriage

TRANSCEIVERS

H.F.

TRIO TS 130V	£450
SWAN 100 MX	£418
YAESU FT 707S	£454
TRIO TS 130S	£547
TRIO TS 530S	£561
YAESU FT 101Z Mk III	£529
YAESU FT 707	£529
YAESU FT 101ZD Mk III	£599
SWAN ASTRO 150	£613
SWAN 102 BX	£798
YAESU FT 107M	£690
TRIO TS 830S	£726

2M F.M. MOBILES

F.D.K. MULTI 7000 EX	£189
AZDEN PCS 3000	£219
ICOM IC 255E	£255
TRIO TR 7800	£276
TRIO TR 8400 (70 cm)	£329
TRIO TS 7730	p.o.a.

HANDHELD F.M.

ICOM IC2E	£169
YAESU FT 208R	£190
TRIO TR 2300	£166
TRIO TR 2400	£198
STANDARD C78 (70 cm)	£219

MULTIMODES

STANDARD C58 (portable)	£249
YAESU FT 290R (portable)	£229
F.D.K. MULTI 750E	£289
ICOM IC 260E	£339
TRIO TR 9000	£371
YAESU FT 480R	£359
ICOM IC 251E	£495
TRIO TR 9500	p.o.a.

RECEIVERS

H.F.

YAESU FRG 7	£189
LOWE SRX 30D	£195
TRIO R 1000	£305
YAESU FRG 7700	£309
YAESU FRG 7700M with members	£389
J.R.C. NRD 515 (THE BEST)	£948

2M F.M./MARINE

SEARCH 9	£45
A.O.R. AR22	£83
F.D.K. TM56B	£89
SX 200N SCANNER	£264
BEARCAT 220FB SCANNER	£258

AIRBAND

R 517 HANDHELD	£49.50
BEARCAT 220FB SCANNER	£258.00
SX 200N SCANNER	£264.00

ACCESSORIES

DRAE POWER SUPPLIES. 13-8V Fully protected

4 AMP CONTINUOUS	£27.95 (£1.50)
6 AMP CONTINUOUS	£44.95 (£2.00)
12 AMP CONTINUOUS	£69.00 (£2.50)
24 AMP CONTINUOUS	£99.00 (£5.00)

MORSE EQUIPMENT

HK 707 Up/Down Key	£10.50 (£0.50)
MK 704 Squeeze Paddle	£19.50 (£0.50)
EK 121 Elbug	£29.95 (£0.75)
EKM 12 Matching side tone monitor	£10.95 (£0.50)
EK 150 Electronic Keyer	£74.00 (—)
EK 1024 Memory Keyer	£126.00 (—)

ACCESSORIES

SAFETY MICROPHONES

ADONIS MM202S Clip on	£20.95 (£0.50)
ADONIS MM202H Head band + Up/Down	£29.00 (£0.50)
ADONIS MM202FU Swan Neck + Up/Down	£30.00 (£0.50)
DAIWA RM940 Infra red link	£45.00 (£0.50)

DESK MICROPHONES

YAESU YM34 (Dual Impedance)	£18.80 (£1.50)
TRIO MC50 (Dual Impedance)	£25.76 (£1.50)
SHURE 444D (Dual Impedance)	£29.95 (£1.50)
SHURE 526T series II Power Mic	£39.95 (£1.50)
ADONIS AM502 Compressor Mic	£39.00 (£0.75)
ADONIS AM802 Compressor Mic 30/P's	£59.00 (£0.75)

TEST EQUIPMENT

DRAE WAVE METER 130-450 MHz	£24.95 (—)
FX1 WAVE METER (700K-250 MHz)	£28.00 (£0.75)
TRIO DM801 Dip Meter (Up to 250 MHz)	£51.00 (£0.75)

DUMMY LOADS

DL 20 (30W Max) PL259	£5.00 (£0.50)
DL 60 (60W Max) PL259	£8.80 (£0.50)
DL 60 (60W Max) N Type	£16.50 (£0.50)
DL 150 (150W Max) PL259	£14.95 (£0.75)
DL 1000 (300W Cont. 1kW Max) PL259	£29.95 (£1.50)

T.V.I. PROBLEMS

YAESU FF 501 DX Low pass filter (1kW)	£22.25 (£0.75)
TRIO LF 30A Low pass filter (1kW)	£18.40 (£0.75)
TV 130 Low pass filter (150W)	£5.95 (£0.60)
HP 4A High pass filter (TV down lead)	£5.95 (£0.50)
Ferrite Rings Top quality 1 1/2" dia - Per pair	£0.80 (£0.20)

HEADPHONES

YAESU YH55	£9.95 (£0.50)
YAESU YH77 New lightweight	£10.75 (£0.50)
TRIO H54	£10.35 (£0.50)
TRIO H55 (Luxury 'phones)	£21.85 (£0.50)

SWR/POWER METERS

DAIWA SW 110A	£35.00 (£0.75)
DAIWA CN 620A Cross pointers HF/2M	£52.80 (—)
DAIWA CN 630 Cross pointers 2M/70 cm	£71.00 (—)



MAIL ORDER - RETAIL CALLERS 9-5.30 PM.
HIGH ST., HANDCROSS, W. SUSSEX. 0444 400786



TO ORDER ANY OF THE ABOVE ITEMS SIMPLY WRITE, ENCLOSING A CHEQUE OR PHONE YOUR CREDIT CARD NUMBER

EDITORIAL OFFICES
Practical Wireless
Westover House
West Quay Road
Poole, Dorset BH15 1JG
☎ Poole 71191

Geoff Arnold T. Eng(CEI) G3GSR
Editor

Dick Ganderton C.Eng., MIERE, G8VFH
Assistant Editor

Peter Metalli
Art Editor

John Fell G8MCP
Technical Editor

Alan Martin G8ZPW
News & Production Editor

Elaine Howard G4LFM
Technical Sub-Editor

Rob Mackie
Technical Artist

Keith Woodruff
Assistant Art Editor

Sylvia Barrett
Secretarial

ADVERTISEMENT OFFICES
Practical Wireless
King's Reach Tower
Stamford Street
London SE1 9LS
Telex: 915748 MAGDIV-G

Dennis Brough
Advertisement Manager
☎ 01-261 6636
☎ 01-261 6872

Roger Hall G8TNT (Sam)
Ad. Sales Executive
☎ 01-261 6807

Claire Gerrish
Secretary
☎ 01-261 6636

Colin R. Brown
Classified Advertisements
☎ 01-261 5762

Dave Kerindi
Make-up & Copy
☎ 01-261 6570

COPYRIGHT

© IPC Magazines Limited 1981. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Practical Wireless

SEPTEMBER 1981 VOL. 57 NO. 9 ISSUE 894

contents

- 20 Introducing SSTV—2**
M. J. Axson G8WHG
- 23 The Craziest Ever Radio Set**
Eric Westman
- 25 IC of the Month — HA11225, KB4441 FM Receiver Devices**
Brian Dance
- 29 Air Test**
Lowe FX-1 Wavemeter
- 33 Audible Field Strength Meter**
Ted Nield GW3ARP
- 36 Passport to Amateur Radio—2**
John Thornton Lawrence GW3JGA
- 40 PW "Exe" Microwave Transceiver—4**
Dick Ganderton G8VFH, John M. Fell G8MCP and Owen Cockram G8OWZ
- 44 Beginner's Short Wave Receiver**
R. J. Howgego G4DTC
- 49 Radio Special Product Report**
Grundig Satellit 1400 General Coverage Receiver
- 54 VHF Mobile Antennas**
D. O. White G3ZPA

We regret that, due to pressure on editorial space, Part 5 of PW "Stour" and Uncle Ed's Column have had to be held over

- | | |
|---------------------------|----------------------------|
| 87 Advert Index | 43 Next Month |
| 29 Air Test | 63 On the Air |
| 17 Comment | 47 Out of Thin Air |
| 31 Hotlines | 59 Production Lines |
| 25 IC of the Month | 17 Services |
| 51 Mods | 52 YL Column |
| 18 News | |

DAIWA POWER METERS

CN620A 1.8-150 MHz up to 1KW
 CN630 140-450 MHz up to 200W
 CN650 1.2-2.5 GHz up to 20W

£52.81 inc VAT
 £71.00 inc VAT
 £95.00 inc VAT




CARRIAGE ON METERS £1.25
 CARRIAGE ON MIKE SYSTEM £1.50

DAIWA CORDLESS INFRA RED MIKE

RM 940 £45.00 inc VAT
 S9 spare sensor £6.50 inc VAT
 M9 spare mike £13.00 inc VAT
 Windshield for mike 75p each.

The Daiwa infrared mike system, comprising of a control box, sensor and infrared mike enables you to dispense with the hand mike and cable when operating in your car or shack. By using an infrared beam audio is transmitted from the mike to the sensor and then to the control box which activates the transmitter. To transmit, press the locking switch on the mike and talk. To receive, release the switch and your rig immediately returns to receive. When you have finished your contact return the mike to its slot in the control box and the mike nicad battery is maintained at full charge. For those of you who like fresh air and drive with all windows open there is a matching wind shield available at an additional 75p. So there we are, the latest technology to bring safety to your mobile operation, the Daiwa infrared mike.

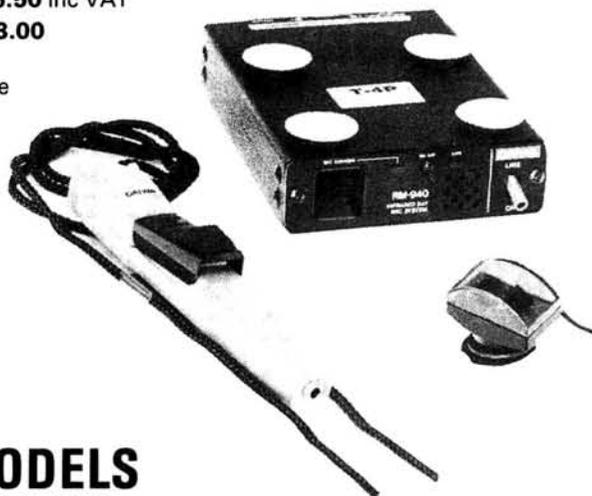

POWER SUPPLIES



THE 3 MODELS

ALL MODELS 240 VOLTS A.C. INPUT.

the PP1305 4 amp 13.8 volts d.c. £18.40 inc. VAT.
 the PP137 7 amp 13.8 volts d.c. £32.00 inc. VAT.
 the PP1310 10 amp 13.8 volts d.c. £49.50 inc. VAT.
 Carriage £2.00

JRC Japan Radio Co., Ltd.
 Since 1915

NRD 515

The NRD 515 is a PLL-synthesised communications receiver of the highest class featuring advanced radio technology combined with the latest digital techniques.

The new NRD 515 is full of performance advantages including general coverage, all modes of operation, PLL digital VFO for digital tuning, 24-channel frequency memory (option), direct mixing, pass-band tuning, etc. JRC's 65 years of radio communications experience will give you "the world at your fingertips".

The NRD 515 is but a single item from the JRC product range which extends all the way to full marine radio installations for supertankers.



NRD 515 SYNTHESISED HG RECEIVER £948.75 inc VAT
 NHD 515 MULTI CHANNEL MEMORY UNIT £161.00 inc VAT
 NVA 515 LOUDSPEAKER £27.60 inc VAT
 CFL 260 600Hz CW FILTER £34.50 inc VAT

LOWE ELECTRONICS

CHESTERFIELD ROAD MATLOCK DE4 5LE TEL 0629 2817



TRIO *pacesetter in amateur radio*



TR-7800 2 METRE FM TRANSCEIVER
The only 2 metre FM mobile £276



TS770E 2m/70cm DUAL BANDER
"towards new horizons" £785.91



TR2300
2M PORTABLE
£166.75



TR-8400 70cm FM TRANSCEIVER *"70cm is on the move."*
£329.13




TR-9000 2M MULTIMODE
"A new direction" £371.91

TR-2400 2M HAND PORTABLE *"handshake"* £198.95




R-820 AMATEUR RECEIVER £690

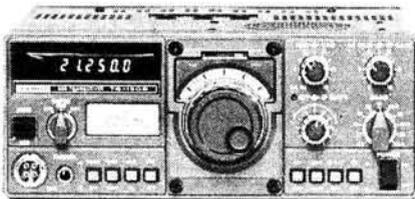

TS 130 S/V *"a big little rig"* £547/£450



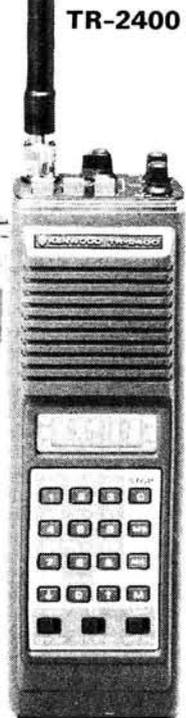TS 830S 160-10M TRANSCEIVER
"top notch" £726.57



R1000 GENERAL COVERAGE RECEIVER
"hear there and everywhere" £305.90



TS180S 160-10M TRANSCEIVER £679.65
PS30 POWER SUPPLY UNIT £85.00

NOTE PRICES AS OF JULY 1981
ALL PRICES INCLUDE VAT. CARRIAGE ADDED TO ALL ITEMS £4.50.

HEAD OFFICE AND SERVICE CENTRE

Chesterfield Road, Matlock, Derbys. Tel. 0629 2817 or 2430.

Open Tuesday-Friday 9-5.30, Saturday 9-5.00. Closed for lunch 12.30-1.30.

For all that's best in ham radio, contact us at Matlock.

For full catalogues send 70p in stamps with your address. Mark enquiry PW.





the amateur's professional friends

Several new products from Icom will be introduced onto the market shortly and when we recently saw the prototypes in Japan we realized just how popular they are going to be. Just to wet your appetites here are a couple of examples:-

IC-290E



£359

IC-290E TWO METRE MULTIMODE MOBILE

The IC-290E incorporates all the features you could want in a multimode mobile to make it easy to use when driving. A standard 6000kHz repeater offset shift is built into its computer's memory but if necessary this can be altered from the front panel for unusual shifts that may be required (such as say 1.6MHz for some transvertors). There are five programmable memories and these can be used in either simplex or duplex mode. Any one of these memories can also be designated as a PRIORITY CHANNEL which can be checked once every five seconds if you wish for that private message you may be expecting. Scanning can be controlled either from the front panel or from the HM10 microphone. There are options to scan the whole band, any selected part of it, or just the memory channels. You do NOT lose the repeater shift when scanning or using either of the VFOs in simplex. Unlike many of its competitors you do have TWO VFOs which can also prove a very useful feature. Further improvements include a brighter frequency readout, a LED bar-type S-Meter and power output meter and the ideal tuning rates of 25kHz per step on FM and 100Hz per step on SSB. Both these rates can be changed to 1kHz steps by use of the TS button on the front panel. For repeater operation both + and - shifts are available and it is possible to listen on the repeater input channel merely by pressing a button. Internal controls allow you to vary scan speed, scan delay time etc. Semi break-in CW and CW sidetone are also available.

Put all these features into an attractive case, add the world wide renowned ICOM quality and performance, and you must see that this is the choice for you. And just as an extra remember that you get a full two year's warranty if you purchase your transceiver direct from THANET or one of our agents listed in this advertisement.

IC-25E



£259

ICOM HAVE GOT IT RIGHT AGAIN!

Again ICOM seem to have got everything right with its new 25W FM mobile. It is one of the smallest around and yet is packed with features which make it really handy to use while still maintaining the very high quality expected in ICOM transceivers.

Like its bigger multimode brother, the IC-25 has TWO VFOs, FIVE MEMORIES (which can be used in either simplex or duplex mode), a PRIORITY CHANNEL (which can be any one of the frequencies stored in the memories), full DUPLEX and REVERSE DUPLEX operation, and a crystal controlled tone burst. Again the display is brighter and there is a LED Bar-type S-Meter and relative power output meter. The choice of the frequency steps is 25kHz and 5kHz. Like the IC-290 multi-scanning functions are available either from the front panel or remotely using the HM-10 scanning microphones.

Again we feel that this beautifully designed and constructed piece of equipment is bound to "sell like hot cakes" - and again remember that if you buy one directly from Thanet you will get a full two year's warranty and any work will be carried out in our excellently equipped workshop. One of our engineers has been out to ICOM in Japan for a two week course to learn the "tricks of the trade".

What about other new products? - well you may well ask but we won't be giving too much away just yet. But how about a 70cm version of the IC-2E and a fully automatic antenna tuner to start off with?

Buy direct from us and get two years warranty on all equipment

WE STOCK CUSHCRAFT ANTENNAS

H.F.			INC. VAT
A3	20/15/10	3ele Beam 8dB gain	£147.00
ATV5	80-10	Trapped Vertical	£74.40
ATV3	20/15/10	Trapped Vertical	£34.00

VHF (144MHz)

A3219	19ele Long 'Boomer' Yagi 16.2dB gain	£62.00
214B	14ele Jnr 'Boomer' Yagi 15.2dB gain	£49.50
ARX2	Ringo Ranger 6dB gain vertical	£24.75
A144-4	4ele Yagi 9.0dB gain	£16.25


A144-7	7ele Yagi 10.0dB gain	£20.31
A144-11	11ele Yagi 11.3dB gain	£25.72
DX120	20ele Array 13.2dB gain	£47.20
ARX2B	Ringo Ranger II	£28.75
ARB2K	Conversion Kit for Ringo to Mk II version	£12.75

WE ALSO STOCK:-

J-BEAM ● MICROWAVE MODULES ● YAESU ● WESTERN
RSGB BOOKS ● BEARCAT ● JIL ● TAL ANTENNAS
● VIDEO GENIE

Thanet Electronics

IC-2E
£169

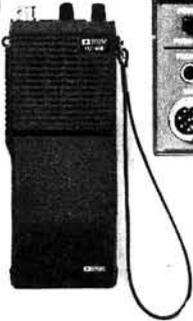

IC-251E



£495

IC-451



£599

The Largest Selling Amateur Transceiver in the World

CHECK THE FEATURES:

FULLY SYNTHESIZED – Covering 144-145.99s in 400 5kHz steps.

POWER OUTPUT – 1.5W with fine 9V rechargeable battery pack as supplied – but lower or higher output available with the optional 6V or 12V packs.

BNC ANTENNA OUTPUT SOCKET – 50 ohms for connecting to another antenna or use the Rubber Duck supplied.

SEND/BATTERY INDICATOR – Lights during transmit, but when battery power falls below 6V it doesn't light indicating the need for a recharge.

FREQUENCY SELECTION – by thumbwheel switches, indicating the frequency.
+5kHz SWITCH – adds 5kHz to the indicated frequency.

DUPLEX SIMPLEX SWITCH – gives simplex or plus 600kHz or minus 600kHz Transmit.

HI-LOW SWITCH – reduces power output from 1.5W to 150mW reducing battery drain.

EXTERNAL MICROPHONE JACK – If you do not wish to use the built-in electret condenser mic an optional microphone/speaker with PTT control can be used. Useful for pocket operation.

EXTERNAL SPEAKER JACK – for speaker or earphone. This little beauty is supplied ready to go complete with nicad battery pack, charger, rubber duck.

A full range of accessories in stock

IC ML1	
10 Watt Mobile Booster for IC2E	£49.00
BPS 11 Volt Battery Pack	£30.50
BP4 Empty Battery Case For, 6 x AA Cells	£5.80
BP3 Standard Battery Pack	£17.70
BP2 6 Volt Pack	£22.00
BC30 Base Charger For Above	£37.00
BC25 Mains Charger As Supplied	£4.25
DC1 12 Volt Adapter Pack	£8.40
HM9 Speaker/Microphone	£12.00
CP1 Mobile Charging Lead	£3.20
IC1/2/3 Cases	£3.60 each

Icom produce a perfect trio in the VHF base station range ranging from 50 Metres thru 2 Metres to 70cms. Unfortunately you are not able to benefit from the 5M product in this country, but you CAN own the 215E for your 2 Metre station and the 415E for 70cms.

Both are really well designed and engineered multi-mode transceivers capable of being operated from either the mains or a 12 volt supply. Both contain such exciting features soan facilities, automatic selection of the correct repeater shift for the band concerned, full normal and reverse repeater operation, tuning rate selection according to the mode in use, VOX on SSB, continuous power adjustment capability on FM and 3 memory channels. Of course they are both fitted with a crystal controlled tone burst and have twin VFO's as have most of ICOMs fully synthesized transceivers. These two transceivers have now become really popular throughout the World – so why not pop a note on our ansafone for more details?

Thanet for



ICOM

143 RECVLVER ROAD,
BELTINGE, HERNE BAY,
KENT. TEL: (02273) 63859

NOW with TWO YEARS WARRANTY

PROFESSIONAL EQUIPMENT FOR THE AMATEUR



IC720A
£849



IC-2KL
£799 + psu



The main problem that the amateur of today has to deal with is deciding just which rig out of the many excellent products available he is going to choose. Technology is advancing at such a rapid rate and getting so sophisticated that many cannot hope to keep up!

Perhaps one way of dealing with the problem is to look at just what each model offers in its basic form without having to lay out even more hard earned cash on "extras". The IC720A scores very highly when looked at in this light. How many of its competitors have two VFOs as standard or a memory which can be recalled, even when on a different band to the one in use, and result in instant returning AND BANDCHANGING of the transceiver? How many include a really excellent general coverage receiver covering all the way from 100kHz to 30MHz (with provision to transmit there also if you have the correct licence)? How many need no tuning or loading whatsoever and take great care of your PA, should you have a rotten antenna, by cutting the power back to the safe level? How many have an automatic RU which conceals itself when the main tuning dial moved? How many will run full power out for long periods without getting hot enough to boil an egg? How many have band data output to automatically change bands on a solid state linear AND an automatic antenna tuner unit when you are able to add these to your station?

Well you will have to do quite a bit of hunting through the pages of this magazine to find anything to approach the IC-720-A. It may be just a little more expensive than some of the others – but when you remember just how good it is, and of course the excellent reputation for keeping their secondhand value you will see why your choice will have to be an IC-720A!

To complement the excellent IC720A HF Transceiver, ICOM have produced the IC2KL linear amplifier. It is of a similar size and matches the IC720A perfectly. It produces 500W output on SSB, CW, AM and RTTY, needing 80-100W of drive.

As with the IC720A it will operate from 1.6MHz to 30MHz continuously at full output power, but you still need an antenna that matches. It will follow the IC720A, automatically changing bands WITH NO TUNING – the operating is done from the prime mover. This automatic facility can be overridden for use on rigs other than the IC720A, but can be added to the IC701 and the IC720. The IC2KL employs a heat pipe cooling system for the heatsink of the power transistors.

This is a new technology used to transfer the heat, has a high conductance, several hundred times that of copper and a very quick response. The use of this system enables a very compact design for which ICOM is the leader.

This advanced design includes protection circuits against Mismatching, Overheating, Overcurrent, Overdriving, Over Output Power and the PA units unbalancing. Its spurious emissions are more than 60dB below peak power output and third order distortion more than 30dB below each tone of a two tone test could a valve linear ever be as good as this?

The IC2KL has a matching power supply the IC2KLPS delivering 40vDC at 25A continuous for 10 minutes maximum.

IC2KLPS (Power Pack) £199.00

AGENTS (PHONE FIRST – evenings and weekends only)

Scotland Jack GM8GEC (031-665-2420)
North West Gordon G3LEQ (Knutsford (0565) 4040)
Ansafone Service available

Wales Tony GW3FKO (0874 2772)
Midlands Tony G8AVH (021-329-2305)



Thanet for ICOM

TWO YEARS WARRANTY ON ALL EQUIPMENT

IC-730



£574

ICOM'S answer to your HF mobile problems – the JC730. This new 80m-10m 8 band transceiver offers 100W output on SSB, AM and CW.

Outstanding receiver performance is achieved by an up-conversion system using a high IF at 39MHz offering excellent image and IF interference rejection, high sensitivity and above all wide dynamic range. Built in Pass Band Shift allows you to continuously adjust the centre frequency of the IF pass band virtually eliminating close channel interference. Dual VFO's with 10Hz, 100Hz, and 1KHz steps allows effortless tuning and what's more a memory is provided for one channel per band. Further convenience circuits are provided such as Noise Blanker, Vox, CW Monitor, APC and SWR Detector to name a few. Provided the IC730 is kept connected to its supply its CPU will remember your instructions even when turned off! Built in fan keeps the finals cool and remember there is no tuning to be done. A built-in Speech Processor boosts talk power on transmit and a switchable RF Pre-Amp is a boon on today's crowded bands. Full metering, WWW reception and connections for transverter and linear control almost completes the IC730's impressive facilities. Use this rig as a high class mobile or with a suitable 13v psu as your main base station. Give us a ring and ask for a full spec. to be sent to you.

IC-202S



£169

The IC-202S is a very well designed 2m SSB portable. It offers 3W pep output on USB, LSB and CW. Large battery capacity (HP11 type) or Nicads if you wish. A special VXO circuit to provide smooth tuning and crystal stability needed for SSB operation on 2m; Each of the four 200kHz band positions allows operation anywhere in 2m (Supplied with 144-144.2 and 144.2-144.4). Top of the band Oscar xtals available for "crosspond working".

It has a DC socket and SO239 sockets for mobile or base station working barefoot or as a prime mover. Mobile mounting brackets, Nicad packs chargers, cases all available options. You must agree, a very versatile well proved rig. The 70cm twin of the 202S having very similar feature covering the frequency range of 432-435.2MHz. Their versatility is well worth an enquiry.

IC-24G



£169

The famous IC240 has been approved given a face lift, and renamed the IC24G. Many thousands of 240s are in use, and its popularity is due in part to simplicity of operation, high receiver sensitivity and superb audio on TX and RX. The new IC24G has these and other features. Full 80 channels (at 25kHz spacing) are available and read out is by channel number – selected by easy to operate press button thumbwheel switches. This readout can clearly be seen in the brightest of sunlight. Duplex and reverse duplex is provided along with a crystal controlled tone call Hi-10W and low-1W RF output is available along with a 12½kHz unshift should the new channel spacing be necessary. The old IC240 proved to be the most reliable rig we have ever sold – the IC24G, because it is so similar, looks like following the same pattern.

Remember, for mobile use a rig MUST be easy to operate to be safe. Send for technical details.

Thanet Electronics

143 RECVLER ROAD,
BELTINGE, HERNE BAY, KENT
TEL: 02273 63859



THREE FOR FREE FROM GSC



Available from selected stockists
ELECTRONICS BY NUMBERS

Electronics by Numbers
Projects No 10, No 11, No 12

EXPERIMENTOR BREADBOARDS


No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP 4B.

EXP 325 £1.60 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.



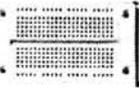EXP 350 £3.15 Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.



EXP 300 £5.75 The most widely bought bread-board in the UK. With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.




EXP 600 £6.30 Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.



EXP 650 £3.60 Has .6" centre spacing so is perfect for MICROPROCESSOR applications.



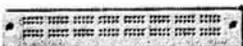EXP 4B £2.30 Four more bus-bars in "snap-on" unit.



The above prices are exclusive of P&P and 15% VAT.

THE GSC 24 HOUR SERVICE
TELEPHONE (0799) 21682
With your Access, American Express, Barclaycard number and your order will be in the post immediately
GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Ltd, Dept. 6TT
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477

No. 10 SOIL MOISTURE TESTER

No more wilting houseplants with this soil moisture test. Just place the probes into the soil and it will light up to tell you whether the soil is "too wet" or "too dry". You don't even need green fingers.


No. 11 DIGITAL ROULETTE

The suspense and excitement of the casino in your own home. Just press the button, the circle of lights go round and there is the sound of the roulette wheel as well, both gradually slowing down to reveal the winning number.

No. 12 EGG TIMER

How do you like your eggs done, hard or soft, just set the timer and it will sound when the egg is done to your liking. Long battery life because it switches itself off automatically. So get cracking now!

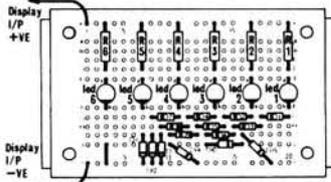Want to get started on building exciting projects, but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instructions in our FREE 'Electronics By Numbers' leaflets, ANYBODY can build electronic projects. For example, take one of our earlier projects, a L.E.D. Bar Graph;



You will need: One EXP 300 or EXP 350 breadboard 15 silicon diodes
6 resistors 6 Light Emitting Diodes
Just look at the diagram, Select R1, plug it into the lettered and numbered holes on the EXPERIMENTOR BREADBOARD, do the same with all the other components, connect to the battery, and your project's finished. All you have to do is follow the large, clear layouts on the 'Electronics by Numbers' leaflets, and ANYBODY can build a perfect working project.

For full detailed instructions and layouts of Projects 10, 11 and 12, simply take the coupon to your nearest GSC stockist, or send direct to us, and you will receive the latest 'ELECTRONICS BY NUMBERS' leaflet.

If you have missed projects, 1, 2 and 3, or 4, 5 and 6, or 7, 8 and 9, please tick the appropriate box in the coupon.

PROTO-BOARDS

The ultimate in breadboards for the minimum of cost. Two easily assembled kits.



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

PROTO-BOARD 6 KIT £9.20



PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

PROTO-BOARD 100 KIT £11.80

IT'S EASY WITH G.S.C.
TO RECEIVE YOUR FREE COPY OF PROJECTS 10, 11 and 12

Just clip the coupon

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate box(es) the breadboard(s) you require.

For immediate action

The GSC 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post immediately.

EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN DIP.	UNIT PRICE INC P&P & 15% VAT	Qty req.
EXP 325	130	1	£ 2.70	
EXP 350	270	3	£ 4.48	
EXP 300	550	6	£ 7.76	
EXP 600			£ 8.39	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus-Bar	£ 5.00	
EXP 4B	Four 40 Point Bus-Bars		£ 3.50	

PROTO-BOARDS	CONTACT	IC CAPACITY 14 PIN DIP.	UNIT PRICE INC P&P & 15% VAT	Qty req.
PB6	630	6	£11.73	
PB100	760	10	£14.72	

NAME

ADDRESS

I enclose cheque/P.O. for £.....
Debit my Barclaycard, Access,

American Express card No.

..... Expiry date

If you missed project No's 1 to 9 tick box


For Free catalogue tick box

GSC (UK) Ltd., Dept. 6TT Unit 1, Shire Hill Estate, Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682. Telex: 817477.

RX 80 MkII - A DIY SOLID-STATE-OF-THE-ART MODULAR DUAL CONVERSION RECEIVER SYSTEM FOR THE ENTHUSIAST

• AS DESCRIBED IN JAN/FEB/MAR 81 RADCOM BY TONY BAILEY-GSWPO : REPRINTS £1 inc

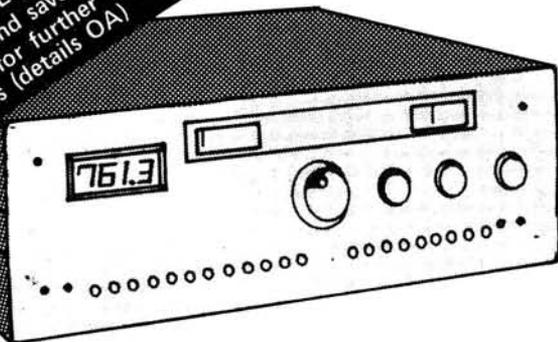CLUBS & COLLEGES:
Buy 5 kits and save 10%
Buy more for further reductions (details OA)



- * LOW DRIFT VARICAP TUNING (READILY ADAPTABLE FOR SYNTHESISED/ HUFF&PUFF STABILIZATION)
- * DUAL CONVERSION BASED ON A 3-4 MHz SSB IF, WITH MECHANICAL IF FILTER, AUDIO DERIVED AGC, BALANCED MIXER, WITH ON-BOARD AF AMP AND VOLTAGE REGULATOR
- * CAPACITY FOR UP TO 12HF/VHF/UHF 1 MHz WIDE CRYSTAL CONTROLLED CONVERTERS WITH TRACKED RF TUNING
- * EACH CONVERTER SELF CONTAINED - SO MORE CAN BE USED EXTERNALLY IF REQUIRED. RF PATHS ARE DC SWITCHED AT LOW IMPEDANCE

PRICES

RX 80 Mk II tuneable 3-4MHz SSB receiver/IF with MFL series 2.4kHz mechanical SSB IF filter ..£42.66
A/A but with low cost 4kHz CFM2 series filter ..£32.42
HF Converters, including crystal for the following bands:
1-2MHz, 7-8MHz, 10-11MHz, 14-15MHz, 18-19MHz, 21-22MHz ..£9.10 ea
24-25MHz, 28-29MHz, 29-30MHz ..£25.00
Hardware: Case, meters, pots, knobs (exc. DFM) ..£25.00
Complete RX 80, 6 converters, switches, case, PSU ..£132.50

CURRENT OPTIONS INCLUDE

- * LCD DFM with built in IF offset, interface PCB ..£23.75
- * HUFF/PUFF vfo stabilizer ..£9.60
- * NBFM adapter inc 8kHz multielement ceramic IF filter ..£9.95
- * Constant Z PIN diode attenuator ..£4.95
- * 12v low RF noise mains PSU ..£7.95

PLANNED ADDITIONS TO THE SYSTEM

- 3-4MHz IF frequency synthesiser
- 'UP Conversion' front end system
- AM IF adapter ■ Noise blanker
- VHF/UHF converters with helical filters



PRICES EXCLUDE VAT (15%). Postage 50p on orders under £12. Free postage on orders over £12, except please note any order including HARDWARE should be accompanied with a £2 carriage charge. General price lists are available FOC with an SAE - full AMBIT catalogues including a multitude of radio parts/components £1.80 a set - or 70p per section.

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
AMBIT international 200 North Service Road, Brentwood, Essex

The World's Radio Broadcasting Stations and European FM/TV

C R Both

The World's Radio Broadcasting Stations provides the radio enthusiast with information on stations likely to be heard during worldwide listening.

European long, medium and FM stations and the world's short wave stations are listed in groups by country in order of frequency. Wavelength, power, map coordinates and the name of the town are given.

European VHF and UHF TV stations are also listed by country and accompanied by details of their power, signal polarisations, programme information, town location and map coordinates.

213 x 143 mm 226 pages
0 408 01156 4 £5.50 Paperback

ORDER NOW from your local bookseller

In case of difficulty send cash with order to Patricia Davies, Marketing Manager at the address below.

Newnes Technical Books a division of Butterworths
Borough Green, Sevenoaks, Kent TN15 8PH

(PW 9/81)

AH ELECTRONICS

20 BARBY LANE, HILLMORTON,
RUGBY, WARWICKSHIRE CV22 5QJ.
TEL: 76473 EVE 71066.

Mail Order Only or callers by appointment.
All prices include VAT but add 50p post & packing.

VHF RF POWER TRANSISTORS:-				
Type	Gain (db)	Output	Volts	Freq. (MHz)
2N6083	5.7	30w	12	175
PT4555	8	25w	12	150
SD1212-6	8.2	3w min.	12	175
PT4556	7	40w	12	80
PT4236A	10	1w min.	12	175
PT4236B	10	11w	12	88
PT4236C	6	35w	12	88
2N5070	13	25w pep	24	30
8F16A	10	1w	12	175
2N3866	10	1w	28	175

CB 27MHz RF POWER TRANSISTORS:-
2SC2028 £1.90, 2SC2078 £2.90, 2SC1306 £2.75, 2SC1307 £3.25.
TA7205P 6 watt audio IC 12v. ex-new equipment & tested £1.50.
TDA1010 9 watt audio IC ± 14v. single in line type £1.50 ea.
MDAB00 8 amp 50 volt bridge rectifier OK for 12 volt PSU 70p ea.

LOW PROFILE RELAY 12 volt 2 pole change over OK for 50 watts RF ± 145MHz. New only £2.25.
FETS/MOSFETS:-
3SK51 (40673) 70p, 3SK60 (sim. 3N204) 80p, 3SK88 26db gain 1.1db NF ± 150MHz £1.40, 8F8B4 18db 3db nf ± 200MHz 75p, E5655 (2N3919) 30p, 1S88A 40p, BF256 38p, 2N4381 "p" chan. 40p.

BIPOLAR VHF/UHF RF AMPS:-
BF166 25p, BF180 30p, BFY90 95p, BF152 15p, BF576 (pnp 1200MHz ft) 20p, 2N4957 (pnp UHF RF amp. 3db nf ± 1GHz) 30p, ST2110 (2N918 B5X20) 15p.

VHF/UHF SWITCHING DIODES BA243 (VHF) 20p. BA244 (UHF) 25p.
VHF/UHF VARICAP DIODES ITT210 20p, B5105 set of 4 60p, BB141 25p.
TIL209B LEDs 1" dia. "red" only 10p, 10 for 75p.

PL259 PLUGS 50p, reducers for UR43/UR76 15p.
SO239 SOCKETS 50p. PL258 couplers 60p.
BNC 50 Ohm flange sockets 70p.

CO-AXIAL disc ceramics 100pf 100 volt OK UHF/SHF decoupling-pkt 20 for 25p.
10.7MHz CRYSTAL FILTER ±3.5KHz ± 3db, 910 ohm. ITT0240E923L £7.00.
10.7MHz CRYSTAL FILTER ±7.5KHz ± 3db, 910 ohm. LQU/445/901B ex-equipment £6.00.

10.7MHz CRYSTAL FILTER SSB type BP4133 (LSB only available), 200 ohm imp. small size 38 x 18 x 15mm. New £4.00 each.
21.4MHz CRYSTAL FILTER ±7.5KHz ± 3db. imp. approx. 2k ohm. New £5.00.

2 KILO BOX BROKEN CAR RADIO BOARDS OK for spares £3.00 plus £1.50 pp.
OXLEY PTFE FEEDTHROUGH INSULATORS 4mm hole size 6p each. 25 for £1.00.
GLASS FEEDTHROUGH INSULATORS solder in type silver plated requires 4mm hole 60p per 100.

1000pf 500v. FEEDTHROUGH CAPACITORS solder in type requires 3mm hole 30p per 10.
MIXED DISC CERAMIC CAPS. 1 to 220pf bag of 100, ideal for the VHF constructor. All Eric miniature types £1.40 per 100.
MIXED BAG RESISTORS all 1/2 watt vertical pre-formed type with long leads. Bag of 250 plus £1.60.

BALUN CORE 2 hole type 13 x 8 x 8mm 15p each, 10 for 80p.
48.00MHz HIG/LU crystals. New £2.00 each.
1000pf 250v LEADLESS DISC CERAMICS 5mm dia. 10 for 25p.

Coming shortly two meter linear amps 60 & 80 watt output in kit form or ready built. Watch this space or ring for details.



TRANSFORMERS

INCREASED PRODUCTION CAPACITY BRINGS LOWER PRICES

95 TOROIDAL TYPES
From 30va to 625va

TYPE	SERIES NO	SECONDARY Volts	R.M.S Current	PRICE
30va 70 x 30mm 0.45 Kg regulation 18%	1X010	6 + 6	2.50	£4.48 + 0.87p P&P + 0.80p V.A.T.
	1X011	9 + 9	1.66	
	1X012	12 + 12	1.25	
	1X013	15 + 15	1.00	
	1X014	18 + 18	0.83	
	1X015	22 + 22	0.68	
	1X016	25 + 25	0.60	
1X017	30 + 30	0.50		
50va 80 x 35mm 0.9 Kg 0.9 Kg regulation 13%	2X010	6 + 6	4.16	£4.93 + £1.10 P&P + 0.90 V.A.T.
	2X011	9 + 9	2.77	
	2X012	12 + 12	2.08	
	2X013	15 + 15	1.66	
	2X014	18 + 18	1.38	
	2X015	22 + 22	1.13	
	2X016	25 + 25	1.00	
2X017	30 + 30	0.83		
2X028	110	0.45		
2X029	220	0.22		
2X030	240	0.20		
80va 90 x 30mm 1 Kg regulation 12%	3X010	6 + 6	6.64	£5.47 + £1.43 P&P + 1.04 V.A.T.
	3X011	9 + 9	4.44	
	3X012	12 + 12	3.33	
	3X013	15 + 15	2.66	
	3X014	18 + 18	2.22	
	3X015	22 + 22	1.81	
	3X016	25 + 25	1.60	
3X017	30 + 30	1.33		
3X028	110	0.72		
3X029	220	0.36		
3X030	240	0.33		
120va 90 x 40mm 1.2 Kg regulation 11%	4X010	6 + 6	10.00	£6.38 + £1.43 P&P + £1.17 V.A.T.
	4X011	9 + 9	6.66	
	4X012	12 + 12	5.00	
	4X013	15 + 15	4.00	
	4X014	18 + 18	3.33	
	4X015	22 + 22	2.72	
	4X016	25 + 25	2.40	
4X017	30 + 30	2.00		
4X018	220	1.71		
4X028	110	1.09		
4X029	220	0.54		
4X030	240	0.50		

Also available from ELECTROVALUE, MAPLIN, MARSHALLS, TECHNOMATIC and WATFOR.

TYPE	SERIES NO	SECONDARY Volts	R.M.S Current	PRICE
160va 110 x 40mm 1.8 Kg regulation 8%	5X011	9 + 9	8.89	£8.44 + £1.43 P&P + £1.48 V.A.T.
	5X012	12 + 12	6.66	
	5X013	15 + 15	5.33	
	5X014	18 + 18	4.44	
	5X015	22 + 22	3.63	
	5X016	25 + 25	3.20	
	5X017	30 + 30	2.66	
5X028	110	1.45		
5X029	220	0.72		
5X030	240	0.66		
225va 110 x 45mm 2.2 Kg regulation 7%	6X012	12 + 12	9.38	£10.06 + £1.73 P&P + £1.77 V.A.T.
	6X013	15 + 15	7.50	
	6X014	18 + 18	6.25	
	6X015	22 + 22	5.11	
	6X016	25 + 25	4.50	
	6X017	30 + 30	3.75	
	6X018	35 + 35	3.21	
6X026	40 + 40	2.81		
6X025	45 + 45	2.50		
6X028	110	2.04		
6X029	220	1.02		
6X030	240	0.93		
300va 110 x 50mm 2.6 Kg regulation 6%	7X014	18 + 18	8.33	£11.66 + £1.73 P&P + £2.01 V.A.T.
	7X015	22 + 22	6.82	
	7X016	25 + 25	6.00	
	7X017	30 + 30	5.00	
	7X018	35 + 35	4.28	
	7X026	40 + 40	3.75	
	7X025	45 + 45	3.33	
7X033	50 + 50	3.00		
7X028	110	2.72		
7X029	220	1.36		
7X030	240	1.25		

5-YEAR GUARANTEE

Toroidals have only half the weight and height of laminated equivalents, are appreciably more efficient, cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers. All I.L.P. Toroidal Transformers carry our full 5-year guarantee.

TYPE	SERIES NO	SECONDARY Volts	R.M.S Current	PRICE
500va 140 x 60mm 4 Kg regulation 4%	8X017	30 + 30	8.33	£15.53 - £2.05 P&P - £2.64 V.A.T.
	8X018	35 + 35	7.14	
	8X026	40 + 40	6.25	
	8X025	45 + 45	5.55	
	8X033	50 + 50	5.00	
	8X042	55 + 55	4.54	
	8X028	110	4.54	
8X029	220	2.27		
8X030	240	2.08		
625va 140 x 75mm 5.0 Kg regulation 4%	9X017	30 + 30	10.41	£21.54 - £2.20 P&P - £3.56 V.A.T.
	9X018	35 + 35	8.92	
	9X026	40 + 40	7.81	
	9X025	45 + 45	6.94	
	9X033	50 + 50	6.25	
	9X042	55 + 55	5.68	
	9X028	110	5.68	
9X029	220	2.84		
9X030	240	2.60		

All voltages quoted are for FULL LOAD. Add regulation figure to secondary voltage for OFF LOAD voltage.

● CHOICE OF 3 PRIMARY INPUTS
I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows (Secondaries can be connected in series or parallel):

For 110V Primary insert 0 in place of "X" in type number. For 220V Primary (Europe) insert 1 in place of "X" in type number. For 240V Primary (U.K.) insert 2 in place of "X" in type number.

THUS: 50va 240v. 6 + 6v 4.16a = 2.2 010.
● WHEN ORDERING (U.K. only). Simply send your order in envelope marked FREEPOST. NO STAMP REQUIRED. Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd. or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order. U.K. customers must include V.A.T. with payment.

GOODS DESPATCHED WITHIN 7 DAYS OF RECEIPT OF ORDER

To: I.L.P. ELECTRONICS LTD., CANTERBURY CT2 7EP

Please supply Transformer(s) No(s)

..... Total purchase price £.....

I enclose Cheque Postal Order International Money Order

Debit my Access/Barclaycard Account No.

NAME.....

ADDRESS.....

Signature.....



FREE POST T.1 GRAHAM BELL HOUSE ROPER CLOSE CANTERBURY CT2 7EP. Phone (0227) 54778 Technical (0227) 64723 Telex 965 780

T. POWELL

IONISER KIT

This negative ion generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions **£12.50**
A suitable case, including front panel, neon switch etc **£10.50**

P.W. KITS

- PW NIMBUS - Complete kit still available **£80.00 (without xtals)**
- Add-on base unit **£38.00**
- Wideband RF Pre-Amp **£7.50**
- AF Speech Processor **£18.00**
- Beginners 2 meter Converter **£15.00**
- Model Railway Controller **£21.50**
- VHF/UHF Repeater Station Timer (Main board only) **£22.50**
- Active receiving Antenna **£9.00**
- 6V to 12V Regulated Converter **£14.95**
- Tape Slide Synchroniser **£41.40**
- Boat Engine Hours Counter **£26.75**
- Ultra Fast Stereo Peak Indicator **£9.50**

SPECIAL OFFERS


- TOSHIBA TA 7205 **£2.50**
- PHILIPS SCOPE TUBES - 5" CV 2191/DG 132 **£12.65**
- MULLARD COMPUTER ELECTROLYTICS 21,000/40V **£4.50**

All prices include VAT and postage & packing
Callers: Please ring to check availability of kits before calling.

PLEASE NOTE OUR NEW ADDRESS:

Advance Works, 44 Wallace Rd., London N1.
Our 'Phone number is still: 226 1489

HOURS: Mon. to Fri. 9-5.30. Sat. 9-4.30.

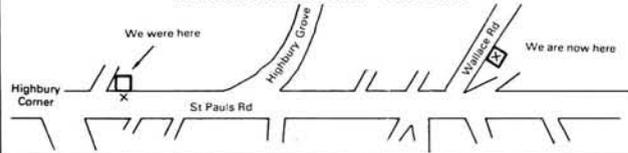

INTERESTED IN ELECTRONICS? TRY A ZEDPACK!

COMPONENTS AT A PRICE EVERYONE CAN AFFORD

- Z1 300 mixed 1/2 and 1/4 watt resistors **£1.95**
- Z2 150 mixed 1 and 2 watt resistors **£1.50**
- Z3 300 mixed capacitors, most types **£1.50**
- Z4 100 mixed electrolytics **£3.95**
- Z5 100 mixed polystyrene caps **£2.20**
- Z6 300 mixed printed circuit components **£1.95**
- Z7 300 mixed printed circuit resistors **£1.45**
- Z9 100 mixed miniature ceramic and plate caps **£1.20**
- Z10 25 assorted pots. **£1.50**
- Z11 25 assorted presets, skeleton etc. **£1**
- Z12 20 assorted vdr's and thermistors **£1.20**
- Z13 11b mixed hardware. Nuts, bolts self-tappers, sleeving, etc. **£1.20**
- Z14 100 mixed, new and marked, full spec. transistors. Pack includes:- BC148, BF154, BF274, BC212L, BC238, BC183L, PBC108 and, or lots of similar types. **£4.95**
- Z15 100 mixed diodes including:- zener, power, bridge, signal, germanium, silicon etc. All full spec. **£4.95**
- Z18 20 assorted zeners, 1 watt and 400mw **£1.50**
- Z20 10 assorted switches. Slide, push-button, multibank, miniature, reed etc. **£1.20**
- Delux FIBREGLASS printed circuit etching kits **£1.20**
- Includes 100 sq. ins. of copperclad F/G board, 1lb ferric chloride, (made for U.S. Army to MIL SPEC.), 1 dialo etch resist pen, abrasive cleaner, tweezers, etch resist dish and instructions. **OUR PRICE £5.95**
- 1lb of FeCl₃. **£2.25**
- 150 sq. ins. single sided board. **£2.20**
- 150 sq. ins. double sided board. **£3.30**
- UHF, Transistors T.V. TUNER with slow motion drive, AE skt. and leads. **£1.95**
- 100 Miniature reed switches. **£2.30**

MINIATURE MAINS TRANSFORMERS

Top quality. Split bobbin construction will give 4.5V-0-4.5V at 250MA, 1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. ONLY £1.3 for £2.50 PP3 Battery Connectors 10 for 50p

To: "GEMINI ELECTRONIC COMPONENTS" DEPT PW "THE WAREHOUSE" SPEEDWELL ST. LONDON S.E.8.

Please Quote ZED Code Where shown. Send Cheque* or Postal Order. Add 60p P&P + 15% VAT. *Schools etc. SEND OFFICIAL ORDER

ZED PACKS now available for Callers at 50 Deptford Broadway, London, S.E.8.

Miniature Press to Make Switches, Red knob. 3 for 50p
Subminiature S.P.C.O. Slide Switches. 6 for 50p.

Miniature D.P.C.O. Slide Switches. 6 for 50p.
Standard 2P, 3 Position Slide Switch, 4 for 50p.

4 x HP11 Battery Holders (2 x 2 Flat type) with leads. 2 for 50p.
Assorted Fuse Holders including 20mm. P.C. Panel and chassis types. Pack of 7 for 50p.

3.5mm Jack Sockets, switched. Enclosed type. P.C. or panel mounting. With nuts and washers. 4 for 50p.
3.5mm Jack Plug on 2m of screened lead. 3 for £1.

R.C. SUPPRESSORS
250V. 1" x 3/8" x 1/4". Ideal for fluorescent light suppression, car, and relays. Also for snubber networks. 3 for £1

ALTERNATOR RECTIFIERS
Make up to 60 amp 150V bridges. Ideal for High Power Battery Chargers. Type 4AF. Set of 4 (2 neg. case - 2 pos. case) £2.

Special Purchase enables us to offer Mullard C280 Polyester Capacitors (Liquorice Allsorts) at the unbeatable price of £2 for 100 mixed. These consist of factory clearance lots i.e. spillages, floor sweepings, cosmetic rejects etc. Also Mullard miniature electrolytics 200 mixed £2.

TELESCOPIC AERIALS
Chrome on brass, 9 section, 25" extended. Plugs into any 3.5mm jack socket. Ideal for S.W.R. meter portable TV, etc. ONLY £1

5 ASSORTED VIDEO GAME BOARDS, new but bits missing. Contain 100's of useful components. CMOS, IC's, Caps, Transistors, sockets, switches etc. ONLY £3.50.

BELLING LEE Coax. plugs. Aluminium 8 for £1

12V 1.3W Zeners 10 for £1

Aluminium finish, slider knobs. Standard fitting. 10 for £1

UHF MODULATORS
Calibrated to Channel 36 625 line UHF. Housed in metal box. 2 1/2" x 2" x 1 1/2". Complete with 9 feet of coax lead and TV plug. 9V operation, ideal for video games, computers etc. £2.50 ea with connection Data.

Vernitron FM4 10.7MHz ceramic filters 50p ea, 3 for £1.

Conquer the chip.



Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.


MASTER ELECTRONICS



LEARN THE
PRACTICAL WAY BY
SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.

MASTER COMPUTERS

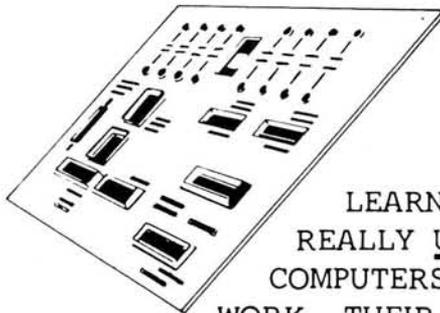

LEARN HOW TO
REALLY UNDERSTAND
COMPUTERS, HOW THEY
WORK - THEIR 'LANGUAGE'
AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.

FREE

Please send your **FREE** brochure without obligation to:-

Name

Address

BLOCK CAPS PLEASE

I am interested in :-

PW/9/811

PRACTICAL ELECTRONICS

COMPUTER TECHNOLOGY

OTHER SUBJECTS
(please state your interest)

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

READING, BERKS. RG1 1BR

GAREX (G3ZV1)

RESISTOR KITS a top-selling line for many years. E12 series, 5% carbon film, 10Ω to 1M, 61 values, general purpose ratings ¼W or ½W (state which)

Starter pack 5 each value (305 pieces) **£3.10**
 Standard pack 10 each value (610 pieces) **£5.55**
 Mixed pack, 5 each ¼W + ½W (610 pieces) **£5.55**
 Giant pack, 25 each value (1525 pieces) **£13.60**

NICAD RECHARGEABLES physically as dry cell: AA(U7) **£1.30**; C(U11) **£3.35**; PP3 **£5.55**. Any 5+: less 10%, any 10+: less 20%.

AMPLIFIER MODULE new, fully assembled 6W IC unit, 12V DC. Low impedance (4-8Ω) input and output for extrn. speaker amplification, with circuit **£2.75**

CRYSTALS FOR 28.5MHz 3rd. overtone, suit most 'CB' rigs. 28.5MHz Tx and 28.045MHz Rx. HC18U **£4.60 per pair**

CRYSTAL FILTER 10.7MHz, 12½kHz channel spacing, ITT type 901C **£6.90**

CO-AXIAL CONNECTORS & ADAPTORS see full list.

PL259 UHF plug with reducer **75p**; S0239 UHF socket, panel mtd. **60p**; 2 x S0239 inline coupler **£1**; 2 x PL259 inline coupler **£1**. Any 5+ connectors: less 10%

HT TRANSFORMER multi-tap pri.: 5 secs.: 35v 200mA, 115v 150mA, 50v 500mA, 150v 300mA, 220v 300mA **£5**

HT CHOKE top grade type, 9H 240mA **£3.50**

PYE CAMBRIDGE SPARES (our speciality, see full list). Ex. equip., fully guaranteed. Rx RF board 68-88MHz **£5.95**. 10.7MHz I.F. **£3.65**. 2nd mixer 10.7MHz to 455kHz **£3**. 455kHz block filter 12½kHz **£9.40**. ditto 25kHz **£3**. 455kHz AM I.F. **£3.65**. Audio bid. **£1.95**, and many more. Vanguard & Westminster spares also.

MONITOR RECEIVERS

SX-200 VHF-UHF AM-FM SCANNER

Covers 26-88MHz, 108-180MHz and 380-514MHz, AM + FM, it scans, seeks, memorises and beats all the others. See full details.

HF-12 POCKET SIZE FM 12 channel xtal controlled. 4MHz bandwidth in range 130-174MHz. With nicad and charger **£57.95** Xtals extra, see below.

SOUNDAIR 008 PORTABLE FM SCANNER 8 channel xtal controlled 140-170MHz. With nicad and charger. **£59** Xtals extra.

SR-9 top-selling monitor: 2m FM with 144-146MHz full coverage VFO + 11 xtal controlled channels; ideal for fixed, /M, /P use. 12V DC operation **£47.50**

Marine band SR-9, 156-162MHz, same spec. and price.

CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B All 2m channels from 0 (145.00) to 32 (145.80) incl. at **£2.46** (+15p post per order). Over 40 popular marine channels at **£2.85** (+15p post). Non-stock xtals made-to-order in 3 weeks at **£4.30** each. See list.

'SCAN-X' VHF/UHF BROADBAND FIXED STATION AERIAL **£19.90** Ideal for SX-200 and other VHF/UHF receivers.

We also stock the:

KDK 2025 2m SYNTHESISED TRANSCEIVER Full band coverage 25 or 12½kHz steps/10 channel memory/scans memories or selected band portion/3W or 25W Tx/all the features you need at **£225**

YAESU FRG 7700 GENERAL COVERAGE RECEIVER 150kHz - 30MHz AM/USB/LSB/CW and FM **£309**

MAINS PSU British made by GAREX 12 volt 1 Amp regulated, adjustable 10-16v **£15.95**

MAIN DISTRIBUTOR OF REVCO AERIALS & SPECIAL PRODUCTS (trade enquiries welcome)

PRICES INCLUDE UK POST & PACKING & 15% VAT.

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH, TRING, HERTS HP23 4LS.

Phone 0296 668684. Callers by appointment only.



WOOD & DOUGLAS

With the winter evenings approaching, the constructional season for radio amateurs is about to begin. If you are undecided on your winter project perhaps you can find something in our range of over 30 kits and modules to suit you.

70FM05TR In case you missed October's review of this single channel FM transceiver for 70 cms here are a few details. The receiver sensitivity is typically 0.4µV and uses dual gate MOSFETS and a high quality crystal filter. The audio output drives an 8Ω speaker. The transmitter gives 500mW of RF and has a modulator on the pcb. Both boards use readily available crystals and measure a very compact 6" by less than 1¼".

Kit **RX £38.50** Assembled **RX £47.25**
 TX **£17.80** TX **£25.95**

70MC06TR When one channel is not enough then by adding this two pcb set you will have 6 channels on tx/rx. This includes a toneburst for repeaters and a scanner to ease monitoring.

Kit **RX £18.60** Assembled **RX £26.05**
 TX **£11.30** TX **£18.10**

144SY25B An FM synthesiser for 25kHz steps at 144-146MHz. The output frequencies are 5-5, 11, 22 or 45MHz on receive and 6, 12 or 24MHz on transmit. This will feed most commercial radio telephones and also the PW NIMBUS. So for the cost of ten crystal channels you get full band coverage, crystal controlled toneburst, repeater ±600kHz offset, out of lock inhibit and channel selection by channel number.

Kit **£50.95** Assembled **£69.70**

INTERESTED? If you would like further details of these and our many other products then send a large SAE (please!) for the latest lists. The above prices include VAT at the current rate but please add 60p p&p on the total order. The prices include all items to make a working pcb module. We do not supply external hardware such as boxes or switches etc. This leaves you free to use the modules in whatever configuration you wish and yet have confidence that the electronics will perform well. We will gladly service any of our products providing it has been built as directed. We make a small charge for this facility depending on complexity. Kits when in stock are return of post otherwise 10-14 days. Assembled items 10-20 days.

9 HILLCREST, TADLEY
 BASINGSTOKE, HANTS RG26 6JB



VALVES

EY51 0.95	PD500/510 4.30	UAF42 1.20	5B/255M 11.50	6F12 1.50
EY81 0.65	PFL200 1.10	JBF80 0.70	5B/258M 8.80	6F14 1.15
EY88 0.65	JBL1 2.50	JBF89 0.70	5R4G1 1.30	6F15 1.30
EZ80 0.70	PL36 1.25	JBL21 1.75	5U4G 0.75	6F23 0.75
EZ81 0.70	PL81 0.85	JCC84 0.85	5V4G 0.75	6F24 1.75
6Y501 1.30	PL82 0.70	JCC85 0.70	5Y4G 0.75	6F33 10.50
GZ32 1.05	PL84 0.95	JCC86 0.85	5Y3GT 0.80	6G68 0.90
GZ33 4.20	PL84 0.95	JCC87 0.70	5Z3 1.50	6G88A 0.95
GZ34 2.30	PL504 1.45	JCC88 0.85	5Z4G 0.75	6H6 1.60
GZ37 3.90	PL508 1.95	JCC89 0.85	5Z4GT 1.05	6J4 1.35
GZ39 3.90	PL509 2.90	JCC90 0.85	6B0L2 0.90	6J4WA 2.00
KT66 6.30	PL519 3.20	JCC91 0.85	6B7 0.70	6J5 2.30
MH4 2.50	PLB02 3.20	JCC92 0.85	6AG5 0.60	6J6 0.65
ML6 2.50	PLB03 3.20	JCC93 0.85	6AG6 1.15	6J6W 0.90
N78 9.90	PLB04 3.20	JCC94 0.85	6AK8 0.65	6J7 1.20
OB2 0.70	PLB05 3.20	JCC95 0.85	6ALS 0.60	6J6C 2.95
OB2 0.80	PLB06 3.20	JCC96 0.85	6ALS5 0.60	6K7 0.80
PC88 0.95	PLB07 3.20	JCC97 0.85	6ALS5 0.60	6K7G 0.50
PC88 0.95	PLB08 3.20	JCC98 0.85	6ALS5 0.60	6K8G 2.65
PC88 0.95	PLB09 3.20	JCC99 0.85	6ALS5 0.60	6L20 0.70
PC88 0.95	PLB10 3.20	JCC100 0.85	6ALS5 0.60	6L20 0.70
PC88 0.95	PLB11 3.20	JCC101 0.85	6ALS5 0.60	6L20 0.70
PC88 0.95	PLB12 3.20	JCC102 0.85	6ALS5 0.60	6L20 0.70
PC88 0.95	PLB95 3.20	JCC185 0.85	6ALS5 0.60	6L20 0.70
PC88 0.95	PLB96 3.20	JCC186 0.85	6ALS5	

REMEMBER: When you deal with SMC you get:

The SMC 2-year guarantee on Yaesu. The speedy free Securicor service. The security of dealing direct with the largest authorised importer. The spacious, very well equipped, ably staffed test and service facility. The knowledge that we carry tens of thousands of pounds of spare parts. Our discreet "instant" H.P. Our personal export documentation scheme. Our in-person, or over the 'phone, time saving credit card acceptance. Our honest advice and evaluation of part exchange equipments' worth. Our deep interest and knowledge in most facets of our common hobby.

AND DO NOT FORGET THE FREE FINANCE SCHEME

Give us a ring for full details (subject to clearance and a minimum of £100 invoice) we will help you to enjoy new regular priced Yaesu, Gem Quad, Ascot, SMCHS, CDE, Hy Gain, Stolle, Channel Master, SMC, Hansen, MFJ, KLM, Mirage, and Hi-Mound - Tomorrow! (You pay only The Cash Price!!!).

POWER UNITS**RU120406 £15**

4 amps const. 6 amps surge @ 13.8V.
Low ripple. Post £1.50.

RS120810 £30

8 amps const. 10/11 surge @ 13.8V.
Full foldback etc. Post £1.50.

SS122535 £99

25 amps const. 35 surge @ 13.8V.
Foldback, short circuit proof etc. Post £2.00.

**FRG7700 £309**

0-15 30MHz General Coverage Receiver.
AM/SSB/CW/FM (Memory Version £389)

**FT202R
£109**

1W. 6 chnl.
2m
Handheld

**FT207R
£175**

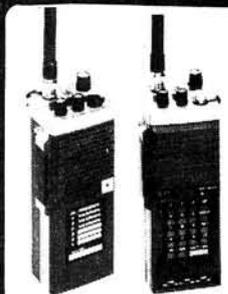
3W. 2m
12½ kHz
Synthesized

**FT404R
£179**

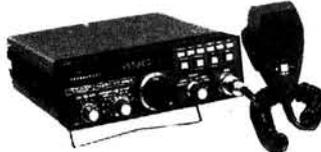
3W. 6 chnl.
70 cms
Handheld

**FT708R
£199**

1W. 70 cms
25kHz
Synthesized

**FRG7 £199**

0°5 30MHz General Coverage Receiver. 230V
ac. 12V dc. + Battery pack. AM/SSB

**FT480R £359**

2m, Synthesized. 25, 12½, 1kHz steps FM
1kHz, 100, 10Hz, steps SSB, 10W PEP.

**FT780R £409**


70cm, Synthesized. 100, 25, 1kHz steps FM.
1kHz, 100, 10Hz steps SSB, 10W PEP

**FT707 £529**

10-80m. 100W PEP, SSB, AM, CW. Variable IF
Bandwidth. Digital. 8 Bander. (10W model £455)

**FT902DM £799**

10-160m, SSB, CW, AM, FM, Deluxe
Digital, Kayer, fan, variable bandwidth etc.

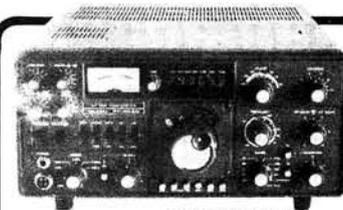**FT101ZFM £529**

10-160m, SSB, CW, Digital, Variable
IF width (FM or AM, Digital or Analogue).



PRICES INCLUDE VAT @ 15%



FREE SECURICOR DELIVERY



2 YEAR IMPORTER WARRANTY

**SOUTH MIDLANDS COMMUNICATIONS LIMITED**

S. M. HOUSE, OSBORNE ROAD, TOTTON, SOUTHAMPTON, SO4 4DN, ENGLAND

Tel: Totton (0703) 867333, Telex: 477351 SMCMM G, Telegram: "Aerial" Southampton

S.M.C. Agents

G3ZUL Stourbridge (03843) 5917
G8BGE Edinburgh (031665) 2420
G13WVY Tandragee (0762) 840656
G13KDR Bangor (0247) 55162
GW3TMP Pontybodkin (035287) 846/324
GW8EBB Swansea (0792) 872525
GJ4ICD Jersey (0534) 26788
G4EQS Redcar (0642) 480808

S.M.C. (Leeds) BRANCH

LEEDS.
Colin Thomas, G3PMS
257 Otley Road,
Leeds 16, Yorkshire.
Leeds (0532) 782326
9-5.30 Monday-Saturday

S.M.C. (Jack Tweedy) LTD

CHESTERFIELD.
Roger Baines, G3YBO
102 High Street,
New Whittington, Chesterfield.
Chesterfield (0246) 453340
9-5 Tuesday-Saturday

S.M.C. (Jack Tweedy) LTD

WOODHALL SPA,
Jack Tweedy, G3ZY
150 Horncastle Road,
Woodhall Spa, Lincolnshire
Woodhall Spa (0526) 52793
9-5: Tues-Sat (+ appointments)

TRIO



LAR



SHORT WAVE 'GOOD BUYS'

Buy from the Short Wave Specialists every time ... you'll get good service from professionals who know your hobby well. For example:



R1000 Communications Receiver for use at home and in your boat or caravan
PRICE

£305.90

SX200N Scanning Receiver 26 MHz to 512 MHz
PRICE

£264.00



SRX 30D. The most popular Short Wave listeners receiver. 0.2 - 30 MHz now with digital readout!
PRICE

£195.00

TS130S 200W pep mobile transceiver, with new bands fitted.
PRICE

£547.40



HERE IS A SELECTION OF TOP BUYS

TRIO EQUIPMENT

- HS5 Communications headphones, tailored response£21.85
- HS4 Communications headphones, tailored response£10.35
- LAR 1kW P.E.P. 3-way antenna switch£16.95
- LAR Antenna traps for multi-band dipole ..£12.50

VHF AMATEUR RECEIVERS

- SR9 Tuneable/crystal 2m FM receiver 144 146 MHz£46.00
- AMR217B Scanner. The best mains/battery operated FM Receiver 144-146 MHz£120.75

VHF/UHF CUSHCRAFT products available

- Famous Ringo Ranger 2m co-linear£32.00
- GDX2 VHF/UHF Discone Antenna 50-480MHz .£39.50

NEW HF VERTICAL ANTENNA

- HF5 80 10m vertical£48.50
- HF5R Optional radial kit for roof mounting£28.00
- LAR-Omni-Match S.W.L. Antenna tuner 200KHZ to 30MHZ£29.95
- CX3A 3-way S.W.L. Antenna Switch£5.50


All TRIO and ICOM Transceivers normally in stock. We always have a good selection of second-hand equipment plus a comprehensive range of accessories.



Leeds Amateur Radio
27 Cookridge Street, Leeds LS2 3AG
Tel: (0532) 452657 (Shop)
Mail Order/Service Department:
60 Green Road, Meanwood, Leeds LS6 4JP.
Tel: (0532) 782224

HOW TO BUY!

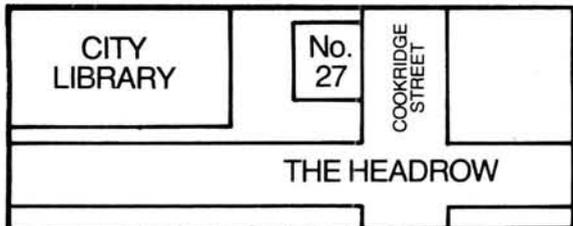By post - or 'phone your Barclaycard, Access or LAR Creditcard number. Alternatively, call in for a chat. The shop is just 10 minutes from Leeds City Station and there's easy parking if you travel by car. *Instant HP for licensed Amateurs *Extended Credit Terms Available. **A QUOTATION ON ALL CREDIT ITEMS IS AVAILABLE.** *Open 9.15 - 6.00 pm, Saturday 9.15 - 5.30 pm.



FROM THE SHOP - We're close to the station and car parks. Do call in and see Uncle Tom's cabin!

POST NOW!

Send 50p for Catalogue and Price List.

I enclose cheque for £ _____ Plus 50p for Brochure*
*delete if not applicable.

to purchase _____

Name _____

Address _____

PW1

Post to: Leeds Amateur Radio, 60 Green Road, Meanwood, Leeds LS6 4JP.

TO BARCLAYCARD/ACCESS/LAR
I authorise you to debit my Barclaycard/Access/
LAR Budget Account with the amount of £ _____



My No. is

Signature _____

TRIO DISTRIBUTOR, LAR are area distributors for CUSHCRAFT, Antenna Specialists, ICOM, Microwave Modules.



comment...

VHF For All

At last, the BBC has decided to re-arrange its v.h.f. services to give a better coverage for mobile and portable set users and to end the sharing of transmitters by incompatible services.

The BBC now recognises that the future of broadcasting in the UK lies with v.h.f. and not medium and long wave. So far, however, v.h.f. has not taken off with the listening public in the UK for a variety of reasons. Reception is not always satisfactory on portable and car radios, and there are significant gaps in the existing v.h.f. coverage.

However, the most serious defect in the v.h.f. system is the enforced sharing of programmes. This is something the BBC is compelled to do to try to squeeze a quart into a pint pot as there are more BBC services than available channels in the present allocation. The recent BBC Radio Network Working Party has recommended that all services shall be available on v.h.f. by the end of the eighties.

These proposals come up against a big problem in the UK—the use of the 100MHz to 108MHz part of the v.h.f. broadcast band by services such as the police and fire services. The Managing Director of BBC Radio, Mr Aubrey Singer, has stated that the BBC will now go all out to get these services removed and the top of Band II used for its internationally agreed purpose—domestic broadcasting.

The problems with poor reception by portable sets and car radios can be traced back to the 50's when the BBC, in its wisdom, envisaged only hi-fi receivers with properly installed antennas on the roof. Horizontal polarisation was chosen on its technical merits with little thought given to future developments in radio

technology. Unfortunately, portables and car radios use vertical antennas and this does not give the best results with the present transmitters. The BBC has now woken up to the problems and has decided to take advantage of the need to replace or update its present ageing transmitters by adding an equal power, vertically polarised signal to give every user the optimum signal into his antenna. The holes in the v.h.f. coverage are also to be filled in by relay stations to give a good signal to all but 0.3 per cent of the population.

To put these proposals into action, the United Kingdom must negotiate with other countries at the forthcoming International VHF Planning Conference in 1982, and will not be able to achieve the optimum plan unless it can co-ordinate its timetable with that of its West European neighbours. At present, part of the v.h.f. broadcasting band in the UK is still being used for mobile communication, notably for the fire and police services. They will need to be moved to quite different frequencies where they can operate just as effectively. According to the Crawford and Annan Reports, the move should have happened by now. However, the change could be as late as 1990 for part of the band and 1995 for the remainder. The BBC believes that the date should be brought forward to about 1986 to coincide with the date when other countries are expected to implement the new plan resulting from the '82, '84 conference. After all, these other services will be moving to a different part of the spectrum anyway—the big question is, how soon? The timing could make a critical difference to the benefit which the United Kingdom can derive from the outcome of the conference.

We can only hope that the BBC does manage to persuade the Home Office to clear the top of Band II so that it can be used for its rightful purpose and allow each programme to have its own separate transmitter.



services

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

SUBSCRIPTIONS

Subscriptions are available to both home and overseas addresses at £11.80 per annum, from "Practical Wireless" Subscription Department, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at 95p each, including post and packing to addresses at home and overseas.

Binders are available (Price £4.30 to UK addresses and overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

NEWS NEWS NEWS

RAE Courses

Courses to prepare students for the Radio Amateurs Examination (City and Guilds 765) will be available at the following locations:—

Birkenhead—*North Wirral College of Technology, Borough Road, Birkenhead, Wirral*, commencing during the week beginning 14 September. Enrolment 7, '8 and 9 September. Details from the Senior Lecturer, D. E. Owen G4GGB, Department of Electrical Engineering at the college, tel: 051-653 5555 Ext. 230.

Newcastle upon Tyne—*Gosforth Adult Association, Gosforth Secondary School, Gosforth, Newcastle upon Tyne*, on Tuesdays between 19.00 and 21.00hrs. Commencing in September, the Lecturer will be D. R. Loveday G3FPE and details are available from the Principal at the school or tel: (0632) 668439.

Bracknell—*Bracknell College, Department of Engineering & Science, Church Road, Bracknell, Berks.*, commencing 28 September. Enrolment 10, 11 and 14 September. Course Tutor will be G8KIL, further details from the college, tel: (0344) 20411.

Manchester—*Pendlebury High School, Cromwell Road, Swinton*, on Thursdays at 19.50hrs, commencing 1 October. Enrolment during week beginning 14 September. Details from Course Instructor, P. Whatmough G4HYE, tel: 061-794 3706.

Hemel Hempstead—*Dacorum College, Marlowes, Hemel Hempstead, Hertfordshire HP1 1HD*, commencing Wednesday 23 September between 18.30 and 21.00hrs. Enrolment 7 September. Further details from the Course Organiser, C. B. Burke G3VOZ, tel: (0442) 833300.

Durham—*New College, Durham*, commencing in September. Details are available from G3ZJY, QTHR, tel: (0385) 66773.

Bradford—*School of Technology and Design, Electrical & Electronic Engineering Division, Bradford College, Great Horton Road, Bradford, West Yorkshire BD7 1AY*, commencing September. Classes are normally held on Mondays, with Tuesdays available if enrolment numbers permit two classes to be run. Further details from the Course Tutor, P. Nurse G8ZXF, tel: (0274) 34844.

Nottingham—*Hucknall Further Education Centre, Portland Road, Hucknall, Nottingham*, on Mondays between 19.00 and 21.00hrs. Enrolment 14 September between 18.00 and 20.00hrs and the Course Tutor will be Alan Lake G4DVW.

Arnold and Carlton CFE, Digby Avenue, Mapperley, Nottingham, on Wednesdays between 19.00 and 21.00hrs. Enrolment 14, 15 and 16 September between 14.00 and 20.00hrs and the Course Tutor will be Alan Lake G4DVW.

Sutton Centre, High Pavement, Sutton-in-Ashfield, Nottingham, on Tuesdays. Enrolment 15 September between 19.00 and 21.00hrs and the Course Tutor will be Jack Tomlinson G3KTX.

West Bridgford CFE, Greythorn Drive, West Bridgford, Nottingham, on Mondays. Enrolment 14 and 15 September from 14.00 to 16.00 and from 18.00 to 20.00hrs and the Course Tutor will be Geoff Dover G4AFJ.

Belfast—*College of Technology, College Square East, Belfast BT1 6DJ*, on Tuesdays between 17.30 and 20.30hrs and on Thursdays between 18.00 and 20.00hrs, commencing 15 September. Enrolment early September and the Course Lecturer will be J. E. Wilson G12BX.

Weybridge—*Brooklands Technical College, Heath Road, Weybridge KT13 8TT*, on Wednesdays between 18.45 and 20.15hrs. Enrolment 7, 8 and 9 September, between 18.00 and 20.00hrs. Details from Mike Tooley G8CKT at the Department of Technology at the college, tel: (0932) 53300 Ext. 215/246.

North London—*Hendon College of Further Education, Silkstream Road, Burnt Oak, Edgware, Middlesex HA8 ODA*. Starting in September, the Course Organiser will be C. Holford. Details from the Department of Science and Technology at the college.

Leamington Spa—*Mid-Warwickshire College of Further Education, Warwick New Road, Leamington Spa CV32 5JE*, on Thursdays commencing 17 September. Enrolment 3 and 4 September from 09.00 to 12.00 and 14.00 to 16.00 and 18.00 to 20.00hrs. Further details from C. A. Smith, Department of Engineering at the College, tel: (0926) 311711.

Mobile Repeater?

Following 18 months of negotiations the Dorset 2m repeater on R1, GB3SC, finally went mobile and relocated to a new site in Central Bournemouth at the beginning of June.

After frantic preparation activity prior to the move, the repeater group members were surprised and relieved to obtain full talk-through within 75 minutes after closedown at the original location.

Although GB3SC is only 70m a.s.l. (the lowest sited 2m repeater operational in the UK) the choice of the new site has been fully justified in terms of servicing its allocated area without the often encountered excursions into already well served locations.

Group secretary, John Fell G8MCP, QTHR, welcomes reports from users or s.w.l.s and the group would be prepared to assist other groups of would-be repeater constructors.

Technical Books for the Amateur

The British Amateur Teleprinter Group has recently published a fully revised and re-illustrated 4th edition of their popular book titled "RTTY—The Easy Way."

Designed to take the reader, with no experience of r.t.t.y., from basic principles through to becoming a proficient operator, the book includes sections on suitable equipment, operating techniques and complete constructional data for building a suitable terminal unit.

Costing only £1.00 plus 15p postage, the book is obtainable from: BARTG, 100 Normandy Avenue, Beverley, North Humberside HU17 8PF.

The "Amateur Television Handbook" is a CQ-TV publication, produced by the British Amateur Television Club and written by John L. Wood G3YQC and Trevor Brown G8CJS.

The book is intended to deal in greater depth with the more complex and generally less-well publicised techniques used in the modern amateur TV station.

The handbook costs £2.00 plus 35p postage and is available from: BATC Publications, 14 Lilac Avenue, Leicester LE5 1FN.

EXceptional Response

Activity on the 3cm amateur microwave band should increase dramatically if the sales of *PW* parabolic dishes are anything to go by. Members of *PW*'s technical staff are seen here with a consignment of dishes awaiting collection by the Post Office from the Poole offices. From the back are G8ZPW, G8MCP, G4LFM and G8VFM. Almost 500 dishes have been sold and orders are still rolling in. For details of the dish offer see page 73.



Amateur Radio Supplies

Auto Marine Development Company originally set up to serve the radio market for cars, boats etc. has expanded substantially into the Amateur Radio field.

So much so that the company have recently opened a new showroom and are officially appointed Yaesu agents for the Greater Manchester Area. They also hold agencies for Microwave Modules, Jaybeam, TAL, Sota, Shure, Bantex, Mosley, LAR, Western and are area dealers for the complete Cushcraft range of antennas.

A catalogue is available from: *Auto Marine Development Company, 60 Orlando Street, Bolton BL2 1DU. Tel: (0204) 21059.*

Rallies and Events

Swindon and District Amateur Radio Club will be holding their Radio & Electronics 81 on Sunday 23 August at Park School, Marlowe Avenue, Swindon.

There will be talk-in on S22 and SU8, plus all the regular attractions. Further details from: *Ken Saunders G8SFM, QTHR.*

Torbay Amateur Radio Society G3NJA-G8IUI, has organised their Rally at the ITT Social Centre, Paignton, Devon on Sunday 30 August 1981.

Included among the usual rally attractions will be trade shows, refreshments and bar facilities. Further details from: *The Secretary, G4DZH, QTHR.*

News from Icom

Several owners of the Icom IC-720A have complained that a very strong signal from a Spanish station, operating on half their i.f. frequency, has been breaking through on their sets when they try to operate on 21MHz. Thanet Electronics Ltd. now have in stock plug-in filters that will cure the problem.

Thanet has also announced that they will soon have in stock a 70cm version of the IC-2E and that will soon be followed by marine and p.m.r. versions. It certainly looks as though Icom got it right when they designed the IC-2E because it has just been officially announced that this rig has now sold worldwide more than any other in the history of amateur radio.

Thanet Electronics Ltd., 143 Reculver Road, Beltinge, Herne Bay, Kent. Tel: (022 73) 63859.

Chalk Pits Museum

Once again the Chalk Pits Museum held another successful "Radio Communications Day" on Sunday 7 June. Among the many exhibitors were both static and active displays.

Margaret Brownlow spent most of her day operating GB2CPM despite the generally poor h.f. conditions, whilst the Sussex Repeater Group worked 40 stations during the 6 hours the museum was open.


One exhibit that created a great deal of interest was the amateur television display by the Worthing and District Radio Club. They had two mobile units operating on 70cm exchanging pictures with G8XEU stationed outside the old radio building. Many visitors were fascinated to see themselves on the screen. Roy Bray and Ray Davis spent all their time wandering around filming with a colour Akai camera and a National Panasonic Video.

The real highlight of the day was the handing over of a £3654.00 cheque from the Horsham District Council for the new radio building. Appropriately a model of the new building was placed by the entrance of the very old and leaking "temporary" hut. Work will be starting on the new building at the end of the year ready for the Radio Communications Days next year.

At the end of the day the exhibitors and members of the *PW* team were privileged to see a film by Bill Glue called "Radio Times". With this two part film Bill has won the Movie Maker 10 Best Films Award. It was a very professionally made film and well worth a visit if your club gets the chance to show the film.

It takes you through from the very beginnings of radio to the second world war, complete with authentic sounding recordings to go with it, just going to prove how hard Bill worked to produce this documentary.

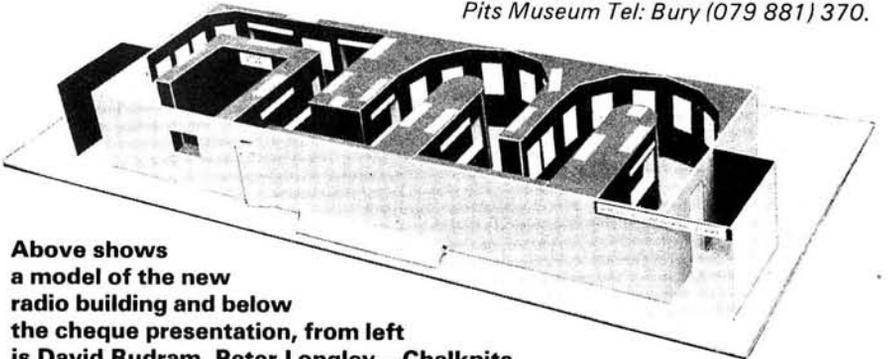Another Radio Communications Day is planned for 27 September. For further details please contact: *Chalk Pits Museum Tel: Bury (079 881) 370.*



Above shows a model of the new radio building and below the cheque presentation, from left is David Rudram, Peter Longley—Chalkpits Treasurer, Arthur Sheppard—Horsham Council Chairman and Ron Ham



INTRODUCING SSTV PART 2

M.J.AXSON BA G8WHG

Part 1 of this series considered the basic principles of SSTV with a brief outline of the currently available techniques. In this part we continue with an examination of scan conversion.

Fast to Slow-Scan Conversion

Before investigating the contents of the 'black boxes' used to convert fast-scan video signals to slow-scan standards, and vice versa, we should consider the parameters of fast-scan, with particular reference to the British 625 line system with 25 frames per second.

Actually only about 572 lines containing video information are transmitted, the time period during which the others would be sent being used for the transmission of the frame sync pulses and various control data, including a two line period for Teletext. In order to eliminate flicker, each frame is sent in two parts or fields, the first consisting of the odd numbered lines and the second the even numbered lines. These are then interlaced to produce the complete frame as shown in Fig. 8. Thus the field frequency is 50 Hz, the same as the mains frequency, and each field contains approx 285 lines of video information.

Comparing this with the SSTV standard of 120 lines per frame (although, for reasons which will emerge later, 128 lines is becoming the accepted norm), using every other line of the field will give approx 143 lines per frame. The slight loss of picture area can be compensated for by suitable masking of the camera viewfinder.

Various methods of scan conversion will be considered, but one factor common to all of them is that digital techniques are used. Conventional radio and TV systems employ analogue means to represent the signals. A typical analogue signal of a single line of video information is shown in Fig. 9 and it will no doubt be very familiar. This works well in a real-time situation, but this is not the case in scan conversion. A fast-scan camera will output the video data for one line in $1 \div 625 \times 25 \text{ secs} = 64 \text{ microseconds}$. This has to be stored so that it can be transmitted over a period of $7.2 \div 120 \text{ secs} = 60 \text{ milliseconds}$, a ratio of 937.5:1. The converse occurs in the receive situation, the slow-scan video data for one line being received over a period of 60 milliseconds, stored, and then output to the fast-scan receiver in 64 microseconds.

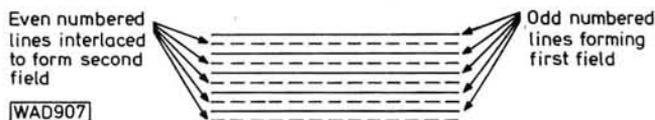


Fig. 8: Interlace of scanning lines

Theoretically, the input data could be stored on tape, which is then re-run faster, or slower, by a factor of 937.5:1, but this is not a very practical solution! There is no satisfactory way in which a continuously varying voltage can be stored at one speed and then be output at another speed differing by a factor of nearly 1000.

It will be seen from Fig. 9 that the analogue video signal varies between limits of 0V and 15V, and that a continually varying output is obtained. The line could however be divided up into a series of discrete locations, each being called a picture element, or pixel for short. Fig. 10 illustrates the principle for a line divided into 20 pixels. The average voltage in the analogue signal corresponding to each pixel is now read and rounded down to a whole number; e.g. 0.9V = 0V, 8.2V = 8V and so on.

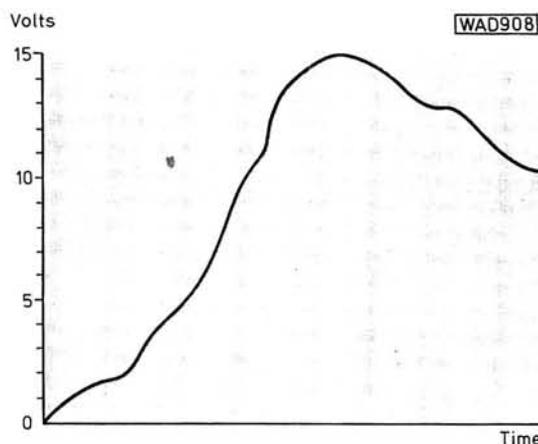


Fig. 9: An analogue signal of one line of video

Applying this principle to Fig. 9 gives the result shown in Fig. 11. The video information contained in the line can now be represented by a series of numbers, which in this case are:

0, 1, 1, 2, 3, 4, 5, 8, 10, 12, 14, 15, 14, 14, 13, 12, 12, 11, 11, 10.

Note that 0 represents black and 15 white so that we can reproduce a total of 16 tones of grey from black to white.



SSTV picture received by PW contributor Sam Faulkner

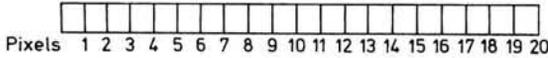


Fig. 10: Dividing the line into 20 pixels

The information to be recorded has now been reduced from a continuously varying signal to one made up of 16 distinct values, which is better but still not quite right, for it is not very easy to devise electronic circuits which will recognise as many as 16 different values and reproduce them rapidly and accurately.

What is easy to recognise is just two values, ON and OFF, or in digital language, 1 and 0. Thus instead of representing the different grey levels in decimal form, they are transformed to binary form; Table 2 shows the binary equivalents for decimal 0 to 15. Now the video information is contained in a series of 4-bit binary words, which can be handled very easily by digital electronic circuitry.

The line of video information in Fig. 11 will now be made up of 20 4-bit words: 0000, 0001, 0001, 0010, 0011, 0100, 0101, 1000, 1010, 1100, 1110, 1111, 1110, 1110, 1101, 1100, 1100, 1011, 1011, 1010.

Therefore the first task of the 'black box' fast to slow-scan converter is to transform the analogue output from the fast-scan camera into digital form, so one of the first circuits in the 'black box' will be a parallel analogue to digital (A-D) converter. Fig. 12 shows a circuit for a 2-bit A-D converter which could handle 4 different grey levels.

The incoming video signal is applied to a bank of comparators where it is compared with a reference voltage. If the video level is below 4 volts, all comparator outputs will be low. If more than 4 volts but less than 8 volts, A will go high with B and C remaining low. If more than 8 volts but less than 12 volts, A and B will be high and C low, whilst above 12 volts all outputs will be high.

These outputs are then applied to the encoder to produce a 2-bit binary word. If the video signal is below 4 volts or between 8 and 12 volts the least significant bit generated by the logic circuit will be 0. Between 4 and 8 volts and above 12 volts it will be 1. The most significant bit will be 1 when the voltage is above 8 volts. Table 3 summarizes the output of the 2-bit A-D converter.

In order to handle the 16 grey levels, the principle is simply extended by using a bank of 15 comparators and extending the logic circuitry of the encoder to produce the binary equivalents for 0 to 15 volts as shown in Table 2. It

Table 2

Decimal	Binary
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001
10	1010
11	1011
12	1100
13	1101
14	1110
15	1111

Table 3

Voltage	MSB	LSB
0 to 3.9	0	0
4 to 7.9	0	1
8 to 11.9	1	0
12 plus	1	1

is of course not necessary to build up a circuit from discrete components since complete A-D converters are available in standard d.i.l. packages, but it is worth while understanding the principles on which they operate.

The simplest form of fast to slow-scan converter is a line converter which, as the name implies, takes one line of video output from the camera, converts it to slow-scan standards for transmission and then returns to repeat the process until the whole 128 line frame has been completed. Fig. 13 shows the block diagram for such a converter.

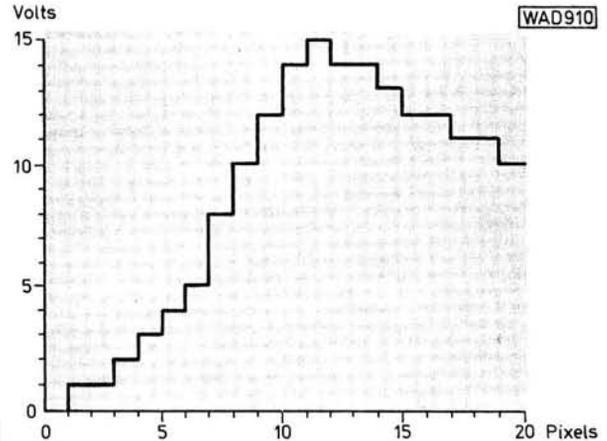


Fig. 11: Digital representation of signal

Video from the fast-scan source is applied to the video stage where the video level is controlled between the required black and white levels. The signal is also fed to the sync separator and the fast-scan sync pulses are used to trigger the fast-speed clock which allows the digitised video information for one line to move from the A-D converter into the shift-register memory.

continued on page 39▶▶▶

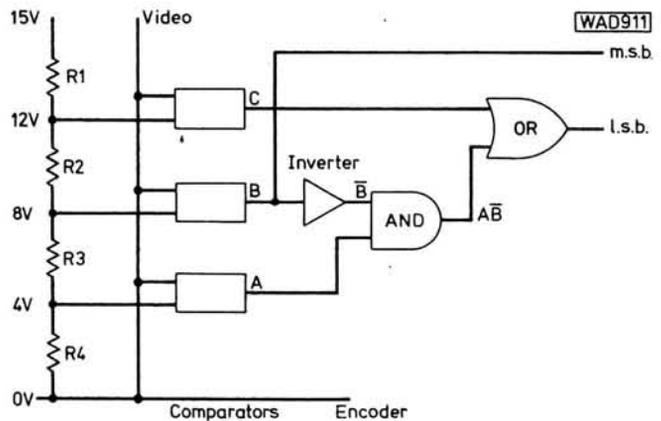


Fig. 12: 2-Bit A-D Converter



Auto Marine



Your Official Yaesu Dealer in Greater Manchester for the North West.

Distributor of Jaybeam Antennas. Main Cushcraft Dealer. Agent for TAL, LAR, Microwave Modules, Western, Revco, Mosley, Drae, Shure.


We carry a full range of station equipment including SWR and Power Meters, Connectors, Co-Axial Cables and Switches, Rotators, Power Supplies and a Full Stock of RSGB Books and Maps.

Our prices are competitive. Just send SAE for our catalogue and price list. Special package deal for new licensees setting up station.

Credit Card and Hire Purchase facilities with written quote on request. Telephone answering machine after hours. Open Tuesday to Saturday. Monday by appointment.

Western

MOSLEY

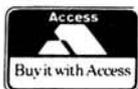

AUTO MARINE DEVELOPMENT COMPANY

60 ORLANDO STREET, BOLTON 'Phone (0204) 21059



**YOUR
SOMMERKAMP
IMPORTER**

**1 Railway Road,
Blackburn, Lancs. Telephone: 51842.
(Telephone Evenings: Bolton 592929 G4GHE)**



THE LATEST SOMMERKAMP - FRG7700 COMMUNICATION RECEIVER. 150KHz-30MHz multimode, digital frequency readout, 12 programmable memories, variable bandwidth, built-in clock/timer. **PRICE £389.00**

SOMMERKAMP 2 METRE RIGS

TS280 Mobile 80 ch. 50 watt **£199.00**. Low power version 10 watt **£159.00**. FT480 Mobile 30 watt **£359.00**

SOMMERKAMP H.F. RIGS

FT2770 (= FT101 with extras) **£659.00**. FT307 (= FT107 with extras) **Price on application**. FT767 (= FT707 with extras) **£559.00**

ROTATORS, ANTENNAS, GENUINE SOMMERKAMP SWR BRIDGES AND 12 VOLT POWER SUPPLIES.

*All prices include VAT. Barclaycard and Access welcome.
H.P. terms available. Part Exchange. SAE for details.*

**END OF RANGE SALE
(DIRECT FROM US ONLY)**

IC-260E



We have managed to buy some of the last of these famous 2 metre Multimode Mobiles from the manufacturers. We are passing the reduced price on to YOU

£299

WITH TWO YEARS GUARANTEE

Quote 'Practical Wireless' when you buy and ask for a **FREE SOLAR POWERED CALCULATOR** (It will work by candlelight)

Thanet for ICOM

143 RECULVER RD.,
BELTINGE,
HERNE BAY, KENT.
Tel: 02273/63059

the CRAZIEST ever radio set

ERIC WESTMAN

Everybody knows the story of Luigi Galvani and the frogs' legs. They don't? Well, it all began back in the 18th century when Mrs Galvani was preparing a tasty dish of frogs' hind legs for her husband's lunch. He was fond of them. Mrs G noticed that whenever she touched a skinned frog's leg with a metal implement, the leg jumped. So did Mrs Galvani!

She told her husband about it. But he still ate the frogs' legs. All except one—which he selflessly spared in the interests of science. Into its thigh muscles he implanted two metal electrodes, and to them he applied a weak current from a primitive wet battery. Straightaway the frog's leg jumped, Galvani didn't—his wife had told him what to expect.

Some months later, Galvani sat idly cranking the handle of an electrical machine, generating a stream of sparks. He often did this because it frightened his mother-in-law. Suddenly, he noticed that a frog's leg lying nearby was jumping like crazy, although there was no direct electrical connection to it. I should explain here that since his wife's discovery, Galvani always kept a few frogs' legs lying around the house in case of developments. They also came in useful as snacks, if the cat didn't get them first.

Now Galvani was too dumb to notice it—and I bet you didn't twig it either—but he had just discovered radio. Yep, one full century before Heinrich Hertz, who got all the credit anyway, Galvani had lighted on the main principle of wireless transmission. How so? Like this; the sparks from the electrical generator emitted electromagnetic waves, these were collected by the electrodes in the thigh muscle, and the nerve fibres and muscle salts combined to act as a detector of the waves. And Galvani missed it! He was lucky Mussolini wasn't around yet.

At this point we say *addio* to Luigi Galvani and skip a century and a half. Which brings us to around 1918 and to Dr Lefevre, a professor at the University of Rennes, France. France? Okay, so he was a *frog*—that's got that out of the way.

Dr Lefevre decided to hook-up a radio utilising Galvani's discoveries. From the output terminals of a crystal set he led two wires to a newly killed frog mounted spread-eagled on a vertical panel. Alright, the frog had just been *croaked*—no more puns *please*. Lefevre connected the wires to a nerve of the frog's thigh muscle. Then he tied one end of a thread around its kneecap and the other end to a pivoted lever mounted below the frog. Are you all

following Daddy? There's only one thing more; the lever was able to inscribe on a smoked paper sleeve surrounding a revolving drum. Something like a seismograph except it didn't need an earthquake to operate it, a bolt of lightning would do.

All set to make a test run, Dr Lefevre tuned-in his brainchild to FL. No indelicacy is intended by the use of these letters, they're the callsign of France's most powerful transmitter, the Eiffel Tower. In France, Eiffel is pronounced "eff-ell", FL—get it? Move down the class!



**It happens every hour,
on the hour!!**

Radio FL didn't have particularly interesting programmes. All it did was broadcast time signals in Morse. But that was fine by Dr Lefevre. The time signal impulses acted on the thigh muscle nerve, the muscle contracted and expanded, and the leg kicked accordingly. I haven't finished yet. The thread from the kicking leg then

continued on page 57 ▶▶▶



Lee Electronics Ltd

IT'S "STANDARD" SUMMER TIME

70cm PORTABLE/MOBILE



New From Standard
The C78 UHF FM Synthesized Transmittable
C78 £219.50

JUST LOOK AT THE FOLLOWING FEATURES:

- ★ Full 10MHz coverage 430-440MHz in 25kHz steps
 - ★ LCD digital readout
 - ★ S and RF power meter
 - ★ Programmable repeater shift and tone burst
 - ★ 5 Programmable memories for your favourite channels
 - ★ Full scanning facilities of vacant or occupied channels
 - ★ A full 1W/10W switchable RF power
 - ★ Up/down channel control on the microphone
 - ★ Can be used from dry cell or rechargeable batteries
 - ★ Optional mobile mount and 10W booster available
 - ★ ONLY 5"W + 2"H + 7½"D
- THE C78 IS MADE TO THE SAME HIGH STANDARD AS THE C8800 AND C7800 SO YOU CAN BE ASSURED OF FIRST CLASS QUALITY AND VALUE FOR MONEY
- PRICE: C78 - £219.50, Mounting Bracket - £19.95**
Carrying case - £6.95, Linear Amp (10W) - £72.50

2 METRE FM/SSB Portable/Mobile


C58



£235.00

- ★ L.C.D. display for low battery consumption
- ★ 100Hz/1KHz/25/12.5KHz/5KHz
- ★ Five programmable memories
- ★ Rit control for accurate ssb resolution
- ★ Effective noise blanker
- ★ Repeater and reverse repeater off set
- ★ A full one watt R.F. power
- ★ Automatic or manual tone burst
- ★ Full scanning facilities
- ★ Large range of optional accessories
- ★ Up/Down scan control on the microphone
- ★ Now available etc. 25W Amplifier £79.95

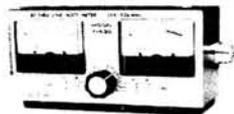TELECOM ANTENNAS - YAESU MUSEN - ICOM - F.D.K. - STANDARD Etc



T-435: VHF/UHF swr and power meter with 2/20/120 watt through line power measurement £34.95 inc. VAT. P&P 75p.



UH74 SWR and power meter switchable HF, 2m and 432MHz with remote head at £16.39 inc. VAT. P&P 75p.



SWR25: This ever-popular twin SWR and Power meter covers 3.5-150MHz at £12.00 inc. VAT. P&P 50p.

HELICAL ANTENNAS

- 2m with BNC plug £4.50
- 2m with PL259 plug £4.50
- 2m for Trio etc. £4.25
- 2m with AR240 screw P&P 25p £4.25

COAX SWITCHES

★ NEW SA-450 ★

High quality coax switch housed in a diecast box with SO239s

Frequency	3.5-500MHz
Loss	0.02dB
Weight	450gms
Max power	2.5kW
Impedance	50ohm



CT-1 Coax toggle, 3 SO239s £9.77 inc. VAT. P&P 25p.

CT-2 Coax toggle, 2 SO239s, 1 PL259 £6.85 inc. VAT. P&P 25p.



TS-120 Coax slide switch, 3 SO239s £6.75 inc. VAT. P&P 25p.



DL-30 Dummy load 25W DC-150MHz £6.35 inc. VAT. P&P 25p.
T-100 100W Dummy load DC-500MHz £20.12 inc. VAT. P&P 25p.
T-200 150W Dummy load DC-500MHz £35.60 inc. VAT. P&P 25p.

NEW PRICE
T200
£33.60



FT 290R
 YAESU 2m multimode portable
 10 mems - 2VFO's - 2.5W
£229



YAESU FT208

2m Handheld.
 LCD display (with nightlight).
 10 memories.
 25 or 50kHz steps for scanning
 Priority channel.
£190


All MICROWAVE MODULES products available

400 EDGWARE ROAD
 LONDON W2
 01-723 5521 Tlx: 298765



INSTANT H.P.
 & P/EX. WELCOME

Send 25p for full details of our range.

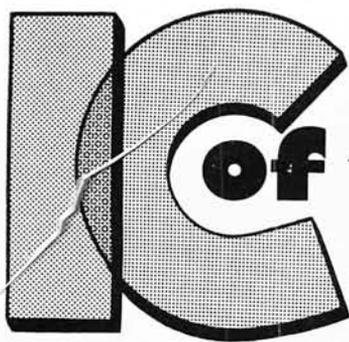

of the month

Brian DANCE M Sc

Hitachi HA11225 & Toko KB4441 FM Receiver Devices

The Hitachi HA11225 and the Toko KB4441 are direct pin-for-pin equivalents which are convenient to consider together in this article, even though they originate from two different manufacturers. These devices are high-performance f.m. limiter-demodulators rather similar to the CA3089 and CA3189 types, both in their connections and in their performance.

The main sections of these chips comprise a high gain 10.7MHz intermediate frequency amplifier which feeds a quadrature detector requiring a single- or double-tuned circuit. The output from the quadrature detector is taken to an audio pre-amplifier stage. The i.c.s. incorporate circuitry specifically designed for providing automatic gain control (a.g.c.), automatic frequency control (a.f.c.), muting when tuning between stations (so that the inter-station hiss noise does not reach the output), tuning meter circuitry and signal strength meter circuitry.

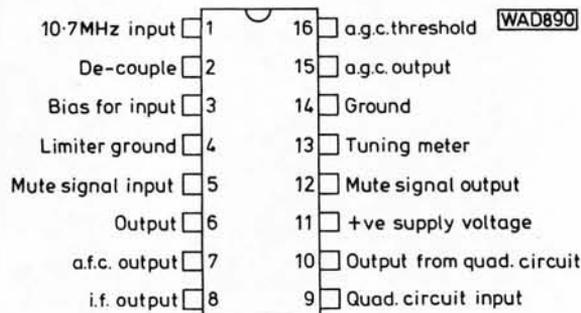


Fig. 1: Connections of the HA11225 and KB4441 devices

Circuit

The connections for the HA11225 and KB4441 devices are shown in Fig. 1 and a typical circuit in Fig. 2. The input to the circuit is obtained from a f.m. front-end unit (which it is much more convenient to purchase than to make, unless one has had experience of 100MHz circuit construction). The output from the front-end unit is the 10.7MHz intermediate frequency signal which is passed through 10.7MHz ceramic filters to provide selectivity before it is passed to pin 1 of the Fig. 2 circuit. The bias voltage from pin 3 passes through the 330Ω resistor to bias pin 1 at the correct point.

The amplified and limited 10.7MHz signal from pin 8 is passed through the 22μH choke shown to the quadrature tuned circuit which is damped by the 3.9kΩ resistor; the value of the latter has been chosen to provide about the

optimum compromise between signal-to-noise ratio and distortion.

The audio output is taken from pin 6. The output impedance at this pin is about 5kΩ, but is increased to nearly 10kΩ by the 4.7kΩ output resistor. Thus a 4.7nF capacitor to ground is required in the output circuit to provide the normal 50μs de-emphasis time-constant ($10\,000 \times 4.7 \times 10^{-9} = 50 \times 10^{-6}$ approximately). The 100nF output capacitor is employed to prevent any steady voltage from pin 6 being fed to the succeeding audio amplifier circuit.

It is important to note that the de-emphasis circuit comprising of the 4.7kΩ resistor and 4.7nF capacitor should be connected as shown only for monaural use. If a stereo signal is required, these components should be omitted and the 100nF capacitor connected directly to pin 6. The other side of the capacitor will be connected to the input of the stereo decoder circuit which, incidentally, will contain two 50μs de-emphasis circuits, one for each channel.

Muting

The output from pin 12 is a voltage, part of which is fed back to pin 5 so as to mute the circuit when one is tuning between stations. The signal level at which muting commences can be varied by means of the 10kΩ potentiometer. When the signal fed to pin 1 is at a level above this muting threshold, no muting will occur, but signals appreciably smaller than the threshold will not produce significant audio output.

An a.g.c. signal may be taken from pin 15 if required, but if a.g.c. is not to be used the extra connection to pin 15 may be omitted. Similarly, an a.f.c. signal may be taken from pin 7 if required (although various types of front-end require different types of a.f.c. signal).

The tuning meter will provide a zero reading when a signal is correctly tuned provided that the quadrature circuit is also correctly tuned. The use of this meter is optional. The signal strength meter in the pin 13 circuit can provide an indication of a very wide level of inputs, since it has a logarithmic response; the inclusion of this meter is also optional. The variable resistor in the pin 13 circuit sets the signal level at which an a.g.c. voltage is first applied to the tuner circuit from the a.g.c. output shown.

Performance

The absolute maximum power supply voltage rating of the HA11225 is 14V. As any voltage above this can cause

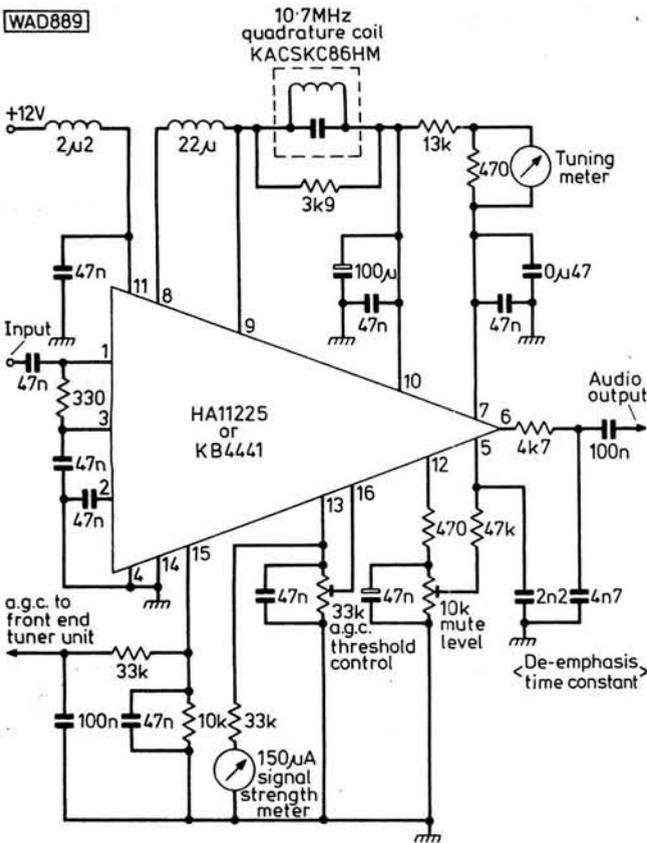



Fig. 2: A simple circuit for the use of these devices using a single-tuned KACSKC86HM quadrature coil

permanent damage, it is wise to regard the upper limit as being about 12V to allow a small margin of safety. The maximum permissible power dissipation in the chip is 590mW at an ambient temperature of 60°C. The quiescent current required from the power supply is between 16mA and 33mA, with 25mA being typical.

When the circuit is correctly limiting with relatively large input signals, audio output voltages of between 265mV and 510mV r.m.s. are obtainable when the input signal has its maximum deviation of $\pm 75\text{kHz}$ (i.e. the loudest signal). A typical signal-to-noise ratio of 84dB is quoted for these devices with a minimum value of 78dB with good input signals.

When a strong input signal at 1kHz, amplitude modulated to the 30 per cent level, is applied at the input, the output is not more than -45dB (typically -54dB)

Fig. 3: Variation of total harmonic distortion level with audio output frequency using a double-tuned quadrature coil

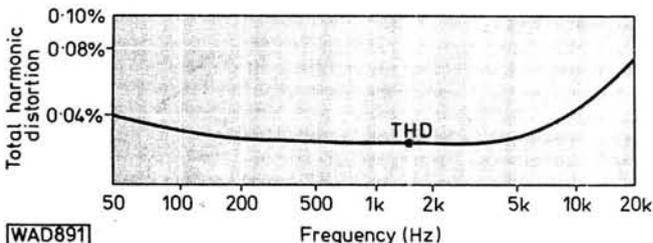

relative to that with a similar frequency modulated signal. This figure provides a measure of amplitude modulation rejection which gets rid of much unwanted noise (such as vehicle ignition noise) in the f.m. band.

When the circuit is muted, the audio signal level at the output can be reduced by as much as 85dB, that is, to a level at which it is virtually inaudible.

Distortion

The circuit shown in Fig. 2 employs a single quadrature tuned circuit for simplicity and provides an output with a total harmonic distortion level of the order of 0.5 per cent. A lower distortion level can be obtained by using a double-tuned circuit instead of the single-tuned quadrature coil and distortion levels of not more than 0.1 per cent (typically 0.03 per cent) are then possible.

Readers intending to use the double-tuned circuit are advised to use pre-aligned quadrature coils obtainable from the device supplier named below at a small surcharge, since the alignment of the two cores needs some experience.

The variation of the total harmonic distortion with audio frequency in the case of a typical device (HA11225 or KB4441) is shown in Fig. 3 for input signal deviations of $\pm 75\text{kHz}$.

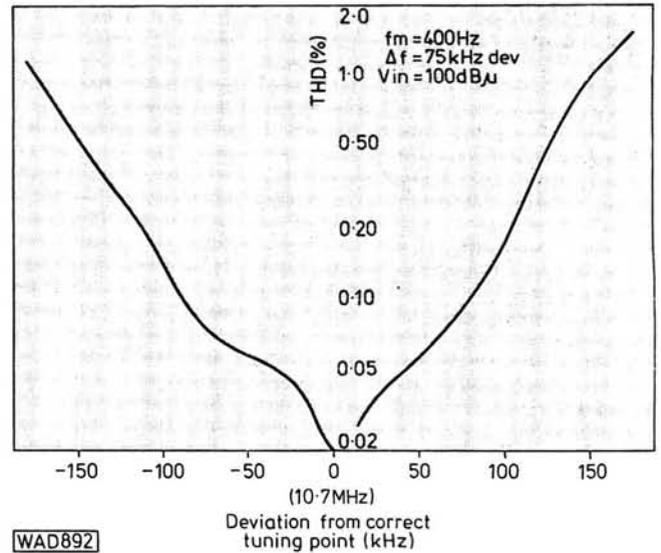


Fig. 4: Increase in total harmonic distortion as the tuning is adjusted on either side of the correct tuning point

The importance of accurate tuning is shown by the measured values in the graph of Fig. 4. As the tuning error increases, the distortion level increases rapidly. Both Fig. 3 and Fig. 4 data apply only in the case of a double-tuned quadrature circuit, not in the simpler circuit of Fig. 2.

Availability

The HA11225 and/or the KB4441 devices are available from Ambit International, 200 North Service Road, Brentwood, Essex, CM14 4SG, together with suitable chokes and coils for both single- and double-tuned quadrature demodulator circuits.

**G4JDT
HARVEY**

EAST LONDON HAM STORE

**G8SYG
DAVE**

H. LEXTON LIMITED 191 FRANCIS ROAD LEYTON E.10
TEL 01-558 0854 TELEX 8953609 LEXTON G

RADIO & ELECTRONIC ENGINEERS ENGINEERS ALWAYS AVAILABLE ON THE PREMISES
MAIN (UK) SERVICE CONTRACTOR TO HITACHI SALES (UK) LTD

EXCLUSIVE TO US IN THE UK. 2MTR LINEARS

200C:- 160W FM - 250W SSB £290
200 :- 350W FM - 500W SSB £499
Top of the Range:- 750W FM (1KW for satellite working) in excess of 1KW on SSB..... £600

NOW IN STOCK

ICOM PORTABLES



IC 2E FM £169
IC 202S SSB £17.70
IC 402 70cms. £242

ICOM MULTIMODES



IC 251 2MTR. £495
IC 451 70cms. £599
IC 260 2MTR. £299
IC 290E 2MTR £359

ICOM FM MOBILES



IC 24G £169
IC 255 £255
IC 25E £259

ICOM 720A G/C



IC 720A 200W £849
PS 15 Power Supply £95
PS 20 Power Supply with speaker £125
IC 730 200W £574
IC 2KL 500W Linear £800
IC 2KLPS Power Supply £199

ICOM ACCESSORIES

BP5 11V Battery Pack £30.50
BP4 Empty Case for 6 x AA Cells £5.50
BP3 Standard Pack £17.70
BP2 6V Battery Pack £22
BC30 Base Charger £37.00
DC1 12V Adaptor £8.40
WM9 Mic/Speaker £9
CP1 Mobile Charging Lead £3.20
LC1/2/3 Cases £3.50

**ALL ACCESSORIES AVAILABLE
SEE HOT LINE**

YAESU/SOMMERKAMP

FT 902DM WARC £799
FT 101ZD FM/AM £599
FT 707 £610
FP 707 Power Supply }
FC 707 ATU } POA
FV 707DM VFO } POA
FT 480 2MTR. Multimode } £359
FT 290 Portable 2MTR
multimode £229
FT 207R 2MTR £170
FT 767DX Sommerkamp £559
FT 101ZD Sommerkamp
(all options) £649
FT 902DM Fully Loaded £865

All accessories including
FV 902, FC 902, YP 901P,
YK 901 available.

FT 901 Also available POA
FT208 2M hand held £190

MICROWAVE MODULES

MMA 144V 2MTR Pre-Amp £34.90
MML 144/25 RF Amp £59
MML 144/40 £77
MML 144/100S (New, with
Pre-Amp) £129.95
MMT 432/144 2-70 Transverter £184
MMT 28/144 £99
MM 4000 RTTY (See it working in our
shop) £269

ROTATORS AND ACCESSORIES

DAIWA
DR 7600X £135
DR 7600R £144
DR 7500X £95
DR 7500R £105

KENPRO
KR 250 £44
KR 400 POA
HAM IV £145
CHANNELMASTER £42
CN 620 1.8-150MHz. PWR/SWR £52
CN 2002 2.5kW Auto ATU £190
JAYBEAM 9502 £50

RECEIVERS

R 1000 Kenwood P.O.A.
FRG 7700 Yaesu P.O.A.
FRG 7700 with
memory P.O.A.
IC 2001L Sony P.O.A.
Search 11 2MTR P.O.A.

CUSHCRAFT AMATEUR ANTENNA

HF A3 20/15/10 3 ele beam
8dB £165
ATV3 20.15.10 Trapped vertical £38
ATV4 10.15.20.40 Trapped
vertical £68
ATV5 10.15.20.40.80 Trapped
vertical £74
VHF A3219 19 ele boomer
16.2dB P.O.A.
214B 14 ele boomer 15.2dB £55.77

STANDARD

MM 2000 RTTY Receiver £169
C58 2M portable/mobile £247
C8800 2MTR Mobile £199
C7800 70cms. Mobile £250
C78 70cms. Portable £219
CMB8 Mobile mount £17.95
CDB 78 Power Amp. C78 £65
CL 8 Carry Case £6.95

A new standard 2mtr portable is due
in soon.

SWAN/CUBIC

100MX 235W £375
102BX 235W + PS5 £700
103BX WARC 235W £810
PS6 Power Supply £145
150MX Digital £561
15002 Linear £406
ST2A ATU TBA
ST3A ATU TBA
HF Mobile ant £80

TRIO/KENWOOD

TS830S HF Transceiver £700
TS130S HF Transceiver £530
TR9500 UHF Multimode (New) £470
TR7840 High power FM 2MTR
(New) £320
TR8400 UHF mobile £275
TR7800 VHF mobile £239
AT130 £72
AS30 £85
R1000 general coverage
receiver P.O.A.
+ Many accessories
TS7720 New FM £365
TR9000

NOW IN STOCK JAYBEAM

ARX 2 Ringo Ranger 6dB
Vertical £28.00
CS100 Communication
Speaker £12.50
A144.4 4 ele Yagi £19.00
A144.7 7 ele Yagi £24.00
A144.11 11 ele Yagi £29.00
DX120 20 ele Yagi £53.15
ARX2B Ringo MkII £32.00
ARB2K Conversion kit £14.20

RINGO MkI to Ringo MkII
Now available - Crossed Yagi with
phasing harness 17" long, weight
3.5lb, 10.5dBd gain £38
Also available Ringo Ranger MkII,
7dB gain £28.75

FULL RANGE IN STOCK
CATALOGUE AVAILABLE
SAE PLEASE

ALL ACCESSORIES AVAILABLE - PLUGS SKTS CO-AX 2MTR COLINEAR £31.50, 70CM COLINEAR £31.50

ALL POA PRICES ARE SUBJECT TO SPECIAL OFFERS - PHONE HOT LINE ... 556 1415
PRICES INCLUDE VAT AT THE PRESENT RATE OF 15%
OPEN MON-FRIDAY 9.00-5.30. SATURDAY 10.00-3.00. INSTANT HP FACILITY AVAILABLE
EASY ACCESS M2-M11-M1 NORTH CIRCULAR ROAD-EASY PARKING
APPOINTMENTS OUTSIDE HOURS BY ARRANGEMENT.





ALTRON
SM30

GIVE YOUR SIGNAL A HEAD START

The SM30 purpose designed telescopic tiltover mast, slim silhouette, structured for single winch operation extend from about 15ft up to 31ft tilts down to 3ft. Self supporting with many small to medium sized arrays or can be guyed for larger HF types.

NOTE THESE FEATURES

- *WALL OR POST MOUNTING. *ONE WINCH OPERATION.
- *OPTIONAL HEAD UNITS - PLATE OR 1 1/2" TUBE (extra).
- *SAFETY UP LOCK AND ANTI-DROP DEVICE.
- *GALVANIZED FINISH. *ENGINEERED TO B.S.I. STDS.

PRICES


SM30 post or wall mounting	£198.00
RT1 1 1/2" reducer tube	9.50
RH1 Rotator Head	25.00

Prices incl. VAT and UK carr. C.W.O.

ALTRON QM1 Q-MOUNT. The Quick Solution To A Tricky Problem!! Simply adjust to suit the opening size, screw out foot and lock into position!! Suitable for many CB, Amateur or TV aerials or even a small rotator. Fits most openings from 25" up to 42" (other sizes available). Universal mounting, no screws, up in a jiff!! Pats. Pending. Price £27.60 incl. VAT. C.W.O. UK. P & P £1.50.

WE DESIGN! WE MAKE! WE SELL DIRECT! YOU get unbeatable value.

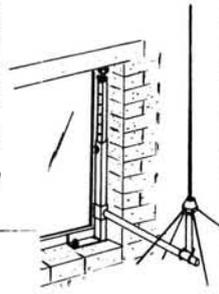Special applications considered. Send S.A.E. for further details or just phone.



ALLWELD ENGINEERING,
UNIT 6,
232 SELSDON ROAD,
SOUTH CROYDON CR2 6PL
Tel. 01-680 2995



COMMUNICATION CENTRE OF THE NORTH

The largest range of communications equipment available in the North. Full range of receivers, transceivers, antennas, power supplies, meters etc.

We are the only official TR10 stockists in the North West. Full range of equipment on display. Guaranteed after sales service.

We can offer a full range of receiver from the SR9 2m £46.00 to the Drake R7 at £989.

We shall be stocking a range of top quality CB equipment when available.

MK II MULTITUNER. In 1977 we introduced our latest design in antenna tuners. This has now been exported to over 75 countries and recommended on Overseas World Broadcasts including HCJB. Will match practically any antenna to most receivers.

£35.00 inc. VAT & POST

Part Exchanges welcome. Second hand lists daily. Send S.A.E. for details of any equipment. HP terms. Access/Barclaycard facilities. Open 6 days a week. 24 Hour Mail Order Service.

Phone 0942-676790.

STEPHENS JAMES LTD.

47 WARRINGTON ROAD,
LEIGH, LANCs. WN7 3EA.

S.E.M.

P.O. BOX 6, CASTLETOWN, ISLE OF MAN.
TEL: MAROWN (0624) 851277

S.E.M. ACTIVE MULTIFILTER

Will improve ANY receiver on ANY mode. Gives "passband tuning" and "Variable selectivity". Switched Hi-pass, Lo-pass, peak or notch. Selectivity 2.5KHz-20Hz tunable from 2.50Hz. PLUS another notch which can be used in any switch position and covers 100Hz to 10KHz. TRY ONE ON 14 DAYS APPROVAL. £57.00 ex stock.

S.E.M. EZITUNE

"In my fifty years on the air, this is the most useful gadget I've ever seen". Connects in aerial lead, produces S 9+ (1-170MHz) noise in receiver. Adjust A.T.U. for minimum noise. You have now put an exact 50 ohms load onto your transceiver. Fully protected, you can transmit through it, to save your P.A. and stop QRM. £25* ex stock.

S.E.M. TRANZMATCH

The most VERSATILE transmatching system. Will match from 15-5000 Ohms BALANCED or UNBALANCED at up to 1kW. Link coupled balun means no connection to the equipment which can cure TVI both ways. SO239 and 4mm connections for co-ax or wire feed. 160-10 metres TRAN Z MATCH £65.00. 80-10 metres £58.00. EZITUNE built in for £19.50 extra. (See above for details of Ezitune). NOW IN STOCK AGAIN.

THE SENTINEL AUTO Mk II 2 or 4 metre PRE-AMPLIFIER

These include NEW PROTECTION circuit to give MAXIMUM LEGAL through power rating. Completely new third generation DUAL GATE MOSFET pre-amp giving 1dB N.F. and 20dB gain with GAIN CONTROL and OFF switch (straight through when OFF). The High Q tuned circuits for high selectivity.

Size: 1 1/2" x 2 1/2" x 4" £25.00* ex stock.

SENTINEL STANDARD Mk II 2 or 4 metre PRE-AMPLIFIER

Same as the AUTO less R.F. switch 12V 5mA. £15.00* ex stock.

PA3

ONE cubic inch miniature 2 metre pre-amplifier. Same circuit as above. External gain can be added. Full instructions. £7.95 ex stock.

SENTINEL 2 METRE LINEAR POWER AMPLIFIER/PRE-AMPLIFIER

These units use the latest techniques and transistors for highest reliability and performance. Infinite SWR PROTECTED devices. ULTRA LINEAR, all modes. R.F. switched. Same POWER GAIN at lower drive powers. Supply 13.8V nominal. SO239s.

Three models:

1. SENTINEL 35

Twelve times power gain. 3W IN 36W OUT. 4 amps. Max. drive 5W. 6" x 2 1/2" front panel. 4 1/2" deep. £57.50 ex stock.

2. SENTINEL 50

Five times power gain. 10W IN 50W OUT. Max. drive 16W. Same size as the Sentinel 35. £69.50 ex stock.

3. SENTINEL 100

Ten times power gain. 10W IN 100W OUT. Max. drive 16W. Size: 6 1/2" x 4", front panel. 3 1/2" deep. 12 amps. £126.50 ex stock.

All available less pre-amp for £8.00 less.

SENTINEL H.F. WIDEBAND PRE-AMPLIFIER

2-40MHz 15dB gain. Ideal for 15 and 10 metres and OSCAR or an ACTIVE AERIAL. 9-12V. Size: 2 1/2" x 1 1/2" x 3". Two versions.

1. STANDARD

Performance as above. £10.00* ex stock.

2. AUTO

Same performance as above with a change over relay r.f. operated by your transceiver for direct connection in your aerial co-ax. £16.93* ex stock.

FREQUENCY CONVERTERS

SENTINEL DUAL GATE MOSFET 2 METRE CONVERTERS

N.F. 2dB Gain 30dB. IFs 2 metres: 2-4MHz, 4-6MHz, 28-30MHz. 4 metres: 28-28.7MHz. 9-12V. 15mA. £24.73 ex stock.

*Means Belling Lee sockets, add £1.90 for SO239s or BNC sockets. Ring or write for more information. Place orders or request information on our Ansaphone at cheap times.

S.E.M. EUROPA C 2 METRE TRANSCEIVER

100W Transmitter. 2dB N.F. receiver. £126.65.

PACKER COMMUNICATIONS

ATU

IMPROVE YOUR VSWR, POWER OUT AND RECEIVED SIGNALS with an ATU 145 antenna tuning unit as featured in Practical Wireless of July 1981. £19.95



REMEMBER You need a wavemeter to comply with the conditions of your licence. Our WM-2 keeps you legal. £22.45



TV1? We think that our UL-8 high pass filter is the best you can buy, but why not judge for yourself? For Ham and CB use. £6.85

For a full list of all our filters please send a S.A.E.

If you're HOLIDAYING IN THE LAKE DISTRICT, why not rent a rig from us. We are now the officially appointed YAESU agents for the Lake District and we stock the fabulous new FT 208R and the FT 290. Now you can hire or buy a hand portable while you enjoy the beauty of Cumbria.



Unit 4,
Station Industrial Estate,
Coniston, Cumbria.
Phone:- 09664 678.



air test

USER REPORTS ON SETS AND SUNDRIES

LOWE FX-1 Wavemeter

The UK Amateur Licence requires each licensee to have a method of ensuring "that his transmissions do not contain unwanted frequencies (i.e. harmonics and spurious frequencies)." The simplest and cheapest way of complying with this is by having an absorption wavemeter, and the licence says that such a wavemeter must have adequate scale length and accuracy, and that the frequency coverage must extend up to the second, and preferably the third, harmonic of the radiated frequency.

The Lowe FX-1 is an absorption wavemeter covering the frequency range 0.7–250MHz in seven bands: 0.7–1.6MHz, 1.5–3.5MHz, 3–7MHz, 7–18MHz, 18–48MHz, 42–110MHz and 85–250MHz, by means of plug-in coils. Each coil is protected by a heat-shrunk plastics sleeve, and the whole set can be stowed in a compartment in the back of the instrument, as shown in the photograph, so solving the usual problem of keeping the coils safe but to hand.


The tuning dial is 80mm in diameter, and overlaps the sides of the case, allowing easy single-handed operation. The scales vary between 18 and 33mm in radius according to band and provide adequate reading accuracy. The coils and scales are colour-coded and also letter-coded, to help in picking out the right scale for the coil in use (and *vice versa*).

The function switch has three positions: 1. "RF", in which indication of resonance is by means of a light-emitting diode driven by a single-transistor amplifier. An internal 9 volt battery (PP3 size) provides the power, the quiescent current consumption being just under 1mA. 2. "M", with resonance shown by means of a small edge-meter. 3. "O", at present unused, but intended to provide g.d.o. facilities with the addition of a small supplementary p.c.b. currently under development.

Modulation of a.m. signals can be checked by plugging a pair of headphones or an earpiece into the front-panel 3.5mm jack. The meter is disconnected when a jack plug is inserted. Relative field-strength measurements can be made by connecting a suitable antenna (short length of wire) to a terminal provided on the top of the case, alongside the coil socket.

The FX-1 is housed in a substantial sheet steel case, and measures 195 x 80 x 70mm overall, excluding a coil. Weight is approximately 0.8kg with the full set of coils carried in the stowage compartment.

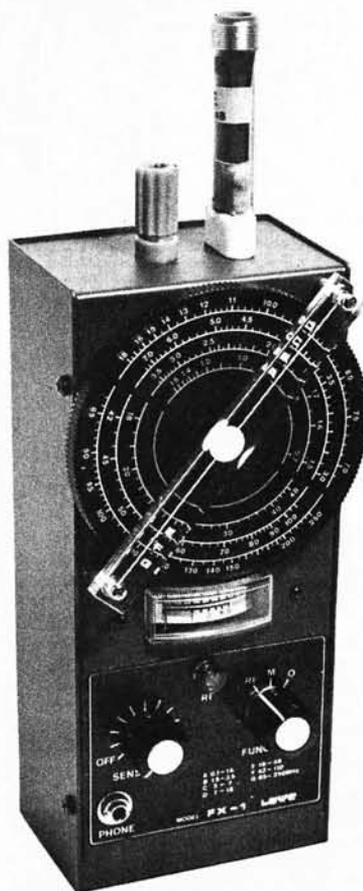For amateur use, the lowest frequency band of 0.7–1.6MHz will not be of much use, and it is a pity that the top frequency limit could not have been pushed up instead,



to include at least the second harmonic of the 2m band. The coil for the 85–250MHz range cannot be reduced in inductance, for it is already the "p.c.b. equivalent" of a hair-pin, so any increase in frequency would have to be achieved by reducing the value of the tuning capacitor, which would reduce the span of each range and mess up the calibration into the bargain. So there seems to be no scope for easy modification. Nevertheless, this is a handy unit, whose usefulness will be increased still further when the version with the g.d.o. becomes available. Existing owners of FX-1s will be able to fit this feature to their wavemeters if they wish (price to be announced).

The FX-1 is available, price £28.00 plus £1.00 post and packing (both including VAT), from **Lowe Electronics Ltd., Chesterfield Road, Matlock, Derbyshire DE4 5LE, telephone Matlock (0629) 2817**, to whom we offer our thanks for the loan of the review unit.

WORLD BEATER!

TR-7

Some interesting facts
on the
DRAKE TR-7
transceiver



- ★ No other amateur transceiver has such a rugged broad banded, no tune up solid state p.a. capable of giving so high an output power over so long a period.
- ★ Only one other transceiver has receiver specifications that can equal the TR-7 and that one costs a great deal more money.
- ★ Built in general coverage receive and the capability to transceive on any future amateur bands between 1.8 and 30 MHz.
- ★ Built in 150 MHz frequency counter.
- ★ Optional Noise Blanker that can deal with the Russian Woodpecker.

R. L. DRAKE PRICE LIST

Model	Description	Inc. VAT	Carr.	Model	Description	Inc. VAT	Carr.
TR-7/DR-7	Transceiver/Gen. Cov. Receiver Digital	1035.00	5.00	SP-75	Speech Processor	79.35	2.00
PS-7	Power Supply 120/240v for TR-7	207.00	5.00	CW-75	Electronic Keyer.....	59.80	2.00
PS-75	Sideband Duty P.S.U. for TR-7 120/240v	138.00	5.00	P-75	Phone patch	59.80	2.00
RV-7	Remote V.F.O. for TR-7	132.25	2.00	7804	Service Manual for TR-7	18.50	2.00
MS-7	Matching Speaker for TR-7 and R-7 ...	29.90	2.00	7805	Service Manual for R-7	18.50	2.00
R-7/DR-7	Digital Receiver 0-30 MHz	989.00	5.00	7037	TR-7 Service Kit.....	37.95	1.00
SL-300	CW Filter for TR-7 and R-7 (300 Hz) ...	39.10	0.50	L-7E	Linear Amp. 2kw. 10m-160m with tubes (2)	897.00	10.00
SL-500	CW Filter for TR-7 and R-7 (500 Hz) ...	39.10	0.50	3-500Z	Tube for L-7E and L-75E.....	69.00	2.00
SL-1800	SSB/RTTY Filter for TR-7/R-7 (1800 Hz)	39.10	0.50	L-75E	Linear Amp. 1kw 10-160m with tube (1).....	598.00	5.00
SL-4000	AM Filter for R-7 Receiver (4000 Hz)..	39.10	0.50	TV-42LP	Low Pass Filter 100w	10.35	1.00
SL-6000	AM Filter for TR-7 and R-7 (6000 Hz)	39.10	0.50	TV-3300LP	Low Pass Filter 2kw	18.40	1.50
AUX-7	Range, Prog. board and 1 Receive module	32.20	1.00	7073	Hand Microphone for TR-7	18.40	1.00
RRM-7	Range receive modules for Aux-7 (500 KHz)	5.75	0.50	7077	Desk Microphone for TR-7	29.90	2.00
RTM-7	Range rcv. modules for Aux-7 (500 KHz)	5.75	0.50	DL-300	Dummy Load 330w.....	20.70	1.00
NB-7	Noise Blanker for TR-7	66.24	1.00	DL-1000	Dummy Load 1000w.....	37.95	2.00
NB-7A	Noise Blanker for R-7 Receiver.....	66.24	1.00	CS-7	Remote control ant. switch 5 way (7 line)	115.00	5.00
FA-7	Fan for TR-7 and PS-7	20.70	2.00	B-1000	Balun for MN-7 and MN-2700 4:1 ...	20.70	1.00
MMK-7	Mobile mounting kit for TR-7	34.50	2.00	Manuals	Spare Operating Manuals.....	6.00	1.00
MN-7	ATU/RF Wattmeter. 160-10 m (250w)	124.20	5.00	Interface	R-7/TR-7 connecting cable.....	20.70	1.00
MN-2700	ATU/RF Wattmeter 160-10m (2kw) ..	207.00	5.00	AK-75	Multiband Antenna	23.00	2.00
WH-7	RF Wattmeter/VSWR Bridge (HF)	59.80	2.00	AA-75	Antenna Insulator Kit	2.30	0.50
				HS-75	Headset.....	9.95	1.00



Importers & Distributors for Hy-Gain, CDE, Rockwell-Collins, Macrotronics Bencher,
R. L. Drake, Ten-Tec, A E A, Bearcat, stockists of all Amateur & Computer Products

LONDON'S AMATEUR RADIO STOCKIST

... just around the corner from West Hampstead Station (Jubilee Line)

RADIO SHACK LIMITED
TELEX 23718

188 BROADHURST GARDENS, LONDON, NW6 3AY
TELEPHONE 01-624 7174

HOTLINES

A REVIEW OF RECENT DEVELOPMENTS

In general, the author does not have any more information on products than appears in the article

Regulators for Cars

Did you know that the innocent 12V in your motor car can develop 100V spikes on its supply line? An i.c. regulator could be the answer, but at what cost? And, remember, those temperatures: from Wigan winters to Harpenden heatwaves.

Now for the good news: meet the L2600 series. These devices suppress spikes, and supply a well regulated voltage. In quantity, they could sell for as little as one lonely US dollar each. To date, 5V, 8.5V and 10V versions have been in evidence, and at least one major car manufacturer is reported to be using the 5V devices.

By restricting the current to 500mA, the manufacturers have kept the price down. This current is sufficient for the dashboard illumination and electronics. By simply spending another \$1.45 (approx.) on an additional *npn* device, this current capability can be increased to 20 amps.

Fabricating the L2600 devices was no simple task. Input voltages up to +30V need to be accommodated, as do -18V reverse inputs. Handling of positive spikes up to +120V, and negative ones 'down' to -90V was also necessary. The temperature range extends from -50 to +150°C, which should cover all likely environments, including Harpenden! Built-in protection guards against such things as excessive temperature dissipation. Should this rise above 150°C, then current in the output transistor base is guided to ground. A pair of internal semiconductors constantly monitor the temperature, and divert base current if the limit is exceeded.

Solid State Camera

It had to come: the electronic cine camera. Sony caused quite a stir by showing just such a unit, but both industry and trade are puzzled. Sony's president is already quoted as saying that the company will not go into production until industry standards are settled and agreed. But although it may be some time before solid state cameras are on the market, it is interesting that current technology has the ability to produce a working unit.

Heart of the camera is a charge-coupled-device (c.c.d.) sensor that has 490 × 470, or 279 300 picture elements. Note that this bit of light-sensitive, electronic wizardry is contained on a chip 10.1 × 12.1mm. Draw it on a piece of paper; then imagine it split up into 279 300 tiny picture elements.

A microcassette is used for recording. It measures some 13 × 35 × 56mm, and has a special high-coercivity, metal tape that is 14µm thick. Recording/filming time is 20 minutes. Inside, the two rotating recording heads are scaled down miniatures of their bigger brothers used in the company's Betamax video recorders. Two different rotating heads are used for playback in order to ensure optimum signal-to-noise ratio. Once the 'film' has been 'exposed', the camera (it measures 60 × 171 × 191mm) is plugged into a small table top unit, and this may be connected directly to any standard television receiver.

Chips for Scrooge

I never cease to be amazed at just how mean the makers of integrated circuits are when it comes to using up precious area on a silicon chip. But now, they're getting really Scrooge-like.

Take the AMCC 1259. It's a complete microcomputer on a chip measuring only 170 × 199mil. This is a c.m.o.s. device and is fabricated using ion implantation, a technique where ions of the desired impurity are 'fired' at the silicon host chip(s) in a vacuum chamber. The velocity of the impure ion 'bullets' can be precisely controlled. Also, by varying the angle of the silicon to these 'bullets', one can control just how deeply the ions are allowed to penetrate. By these means, very precise doping impurity levels can be achieved.

An advantage of all this is that the AMCC 1259 needs only a single 1.5V battery, and draws a truly miserly 3µA: like an electronic vampire that's slimming! The basics of the i.c. are programmable logic arrays (p.l.a.), and

it is intended for timing and control work, although electronic games and toys look a natural market.

The chip accepts five push-button inputs, and has 48 outputs that can drive liquid crystal display segments. There is also an oscillator and divider chain from which all internal timing signals are derived: the user merely adds an external 32kHz crystal. It even has an alarm circuit that requires only a single transistor amplifier and speaker (or whatever) to give audible warning outputs. Eight-bit address register, and r.a.m., are all packed in (somehow). Some 256 program steps are addressable, and up to 64 r.a.m. locations can be uniquely addressed.

All in an area 170 × 199mil, and taking only 1.5V at 3µA. Mean man, like really mean.

High-temperature Regulator

Then there's yet another voltage regulator. This one comes under the heading of, "High-temperature Hybrid". A 15V device, it can operate up to +275°C. Its sister component, one "Model 4160", is a 12-bit a. to d. converter that can operate up to +200°C without missing codes. The manufacturers guarantee it. Wonder what a 'hotted up' version would do?


Light-pipe

And finally, a light-pipe imaging device. Most devices have had low resolution so far; typically less than 100 dots/inch. The new light-pipe can improve this figure to 240 dots/inch. The pipe can connect to a flat surface and could be used in such things as copiers. Because the illuminated ends would be so very close to the recording medium, no additional optics, such as lenses etc. would be required. Could be a useful device for 'Spot the Ball' competitions.

Ginsberg

Western

ALUMAST

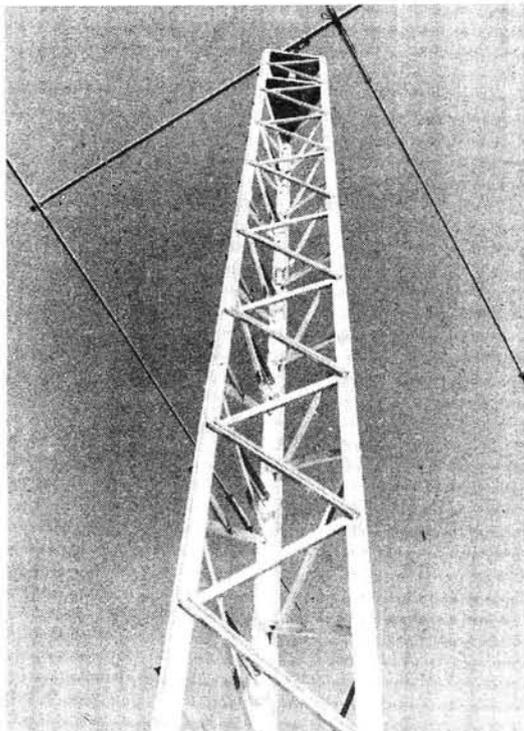

The ALUMAST is a 15in (375mm) wide triangular cross section lattice sectional aluminium mast based on a 10ft (3.05m) section length. It is supplied "knocked-down" in a tubular carton for ease of transport, but can easily be assembled needing no special tools or skills. The system includes top plate with bearing sleeve, rotor plate and a choice of a fixed base frame (FB-1) or one with hinge joints (HB-1) to enable the mast to be pivoted at ground level. Guy brackets are available for use at heights above 30ft.

- Made from high strength corrosion resistant alloy using WESTERN'S EXCLUSIVE 'W' section leg extrusions.
- Easy assembly using bolts and "Nyloc" locking nuts for security.
- Free-standing to 30ft (9.15m) with a typical tri-bander plus VHF/UHF antennas.
- Heights to 200ft (61m) with appropriate guy configurations (ask us for quotes).
- Lightweight - only 25lb (11kg) per 10ft (3.05m) section.
- 30ft (9.15m) mast is delivered in a tube only 10ft 6in (3.2m) long, 6in (0.126m) dia.

A COMPLETE 30ft (9.15m) MAST for £240.35
375/PSS/3; HB-1; RMP-1; TP-1

FULL PRICE LIST		
375/PSS/3	30ft mast (3 sections)	£184.00
375/PSS/1	Additional 10ft section	£62.68
HB-1	Hinged base unit	£31.05
FB-1	Fixed base unit	£21.85
RMP-1	Rotor mounting plate	£12.08
TP-1	Top plate with sleeve	£13.23
GB-1	Guy brackets (set of 3)	£11.50

All prices include carriage and VAT at 15%
For Scotland - add £10 extra carriage

Western Electronics (UK) Ltd

FAIRFIELD ESTATE, LOUTH, LINCS LN11 0JH
Tel: Louth (0507) 604955 Telex: 56121 WEST G

MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.

- ★ Practise anywhere, anytime at your convenience.
- ★ Generates a random stream of perfect Morse in five character groups.
- ★ D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- ★ Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.



ACTIVE RECEIVING ANTENNAS

Datong active antennas are ideal for modern broadband communications receivers - especially where space is limited.

- ★ highly sensitive (comparable to full-size dipoles).
- ★ Broadband coverage (below 200 kHz to over 30 MHz).
- ★ needs no tuning, matching or other adjustments.
- ★ two versions AD270 for indoor mounting or AD370 (illustrated) for outdoor use.
- ★ very compact, only 3 metres overall length.
- ★ professional performance standards.



Price **£49.45**
Prices: Model AD270 (indoor use only) **£42.55**
Model AD370 (for outdoor use) **£56.35**
Both prices include mains power unit.

VERY LOW FREQUENCY CONVERTER

If your communications receiver gives poor results below 500 kHz Model VLF is the answer.

- ★ Connects between antenna and receiver input.
- ★ Converts signals between DC and 500 kHz to the range 28 to 28.5 MHz with low noise and high sensitivity.
- ★ Crystal controlled for high stability.
- ★ Quality construction in diecast aluminium box (size 112 x 62 x 31mm), SO239 connectors, LED indicator, in/out switch.
- ★ Operates from internal 9 volt battery or external supply (5-15 volts DC).

Price: only **£25.30**
Our full catalogue plus further details of any product are available free on request.
All prices include VAT and postage and packing.

DATONG ELECTRONICS LIMITED

Spence Mills, Mill Lane,
Bramley, Leeds LS13 3HE
England.
Tel: (0532) 552461

Lee Electronics Ltd



YAESU FRG7700

- One-touch frequency selection from long wave to short wave with 12 channels capable direct memory circuitry. (With memory type only).
- 150kHz to 29.999MHz full coverage high stability dual PLL system.
- Strong for cross modulation.
- Automatic band pass filter selection.
- 3 filters for AM reception.
- 2 steps of AGC... fast/slow.
- Narrow band FM reception capability.
- Timer facility.
- Back up battery.
- Sinpo coded signal strength meter.
- Receiver noise blanker circuitry.
- 12 kinds of attenuator.
- High quality audio sound.
- Dimmer control.
- AC + DC operation.

FRG7700 £309

FRG7700m (with memories fitted) £389

INSTANT H.P. (with Bankers Card) & P/EX. WELCOME

Receive Pre-Amp worth £15 FREE with every FRG7700

400 EDGWARE ROAD
LONDON W2
01-723 5521 Tlx: 298765



Send 25p for full details of our range.



audible FIELD-STRENGTH METER

Ted NIELD GW3ARP

This rather novel device was designed to overcome the obvious difficulty of watching the readings of a distant meter whilst, at the same time, trying to make circuit adjustments to the transmitter, antenna etc., often from a position where it is physically impossible to see the meter. Whatever reliance may be placed upon checks made on the transmitter itself, using dummy loads or power measurements, there is something much more satisfying in using the actual radiated r.f. field and making one's adjustments according to observed results. In the case of v.h.f. antenna adjustments this is particularly so.

Whilst the measurement of field strength in absolute terms is a difficult matter requiring expensive specialised equipment, the measurement of relative field strength is comparatively simple, and this is all that is required.

To achieve our present purpose what is needed is to convert field strength into terms of audio frequency—the stronger the r.f. field the higher the note, a form of analogue to digital conversion.

Fig. 3 shows in block diagram form the stages involved. Stages A and B each employ a CA3140 operational amplifier, the use of this *p*-m.o.s. input type in preference to the older 741 type confers two main advantages: higher gain and the ability to use a single-ended power supply.

A conventional take-off point following the detector stage is provided as an extra feature for use with an external 0-5V d.c. meter, enabling the device to be used in the ordinary way if desired.

Detector Stage

The output of a simple voltage doubler type detector is fed to the non-inverting input at pin 3. A variable degree of d.c. negative feedback from pin 6 is fed via R2 to the inverting input at pin 2 providing control over the gain. The voltage at pin 6 is basically zero in the absence of a signal, and a d.c. voltmeter (0-5V) plugged into SK1 will show a rising output as the r.f. input from L1 tuned circuit increases with increase of field strength. Resistor R2 will vary the sensitivity or gain of the circuit. So far we have a

conventional field strength meter with a high degree of sensitivity. A one watt 2m transmitter at 50 metres will give full scale deflection using a 50cm ($\lambda/4$) pick-up antenna.

Analogue to Digital Converter

This consists basically of another CA3140 in a square-wave oscillator arrangement. The potentiometer R1 and diode D3 form a limiting circuit, limiting the negative excursion at the non-inverting input of the operational amplifier (pin 3). When no r.f. signal is present, the output voltage of IC1 is zero, and the full negative swing takes place, but as the voltage at the anode of D3 rises the negative swing is progressively limited, causing the operating frequency of the oscillator to rise.

**CONSTRUCTION
RATING**

Beginner

BUYING GUIDE

Constructors of this project should have no difficulty in obtaining all the relevant components. Note L1 consists of $3\frac{1}{2}$ turns closewound on the core, tapped one turn from the bottom.

**APPROXIMATE
COST**

£12

★ components

Resistors

$\frac{1}{4}$ W 5% Carbon

47 Ω	1	R3
15k Ω	2	R8, 9
100k Ω	2	R5, 6
1.5M Ω	1	R4

Miniature horizontal pre-set

10k Ω	1	R1
220k Ω	1	R7

Wirewound linear potentiometer

10k Ω	1	R2
--------------	---	----

Linear potentiometer with d.p.s.t. switch

100k Ω	1	R10
---------------	---	-----

Capacitors

Sub-miniature ceramic

2.2pF	1	C1
680pF	1	C2
4.7nF	1	C3

Polypropylene

22nF	1	C7
0.1 μ F	2	C5, 6

Electrolytic 10V

10 μ F	1	C4
------------	---	----

Semiconductors

Diodes

OA91	2	D1, 2
1N4148	2	D3, 4

Transistors

2N2926	1	Tr1
--------	---	-----

Integrated Circuits

CA3140	2	IC1, 2
--------	---	--------

Miscellaneous

DIN speaker socket (1); 8-pin d.i.l. holders (2); 5cm diameter speaker 50–100 Ω (1); knobs (2); SO239 chassis mounting socket (1); 18 s.w.g. enamelled copper wire; 7mm diameter inductor core.


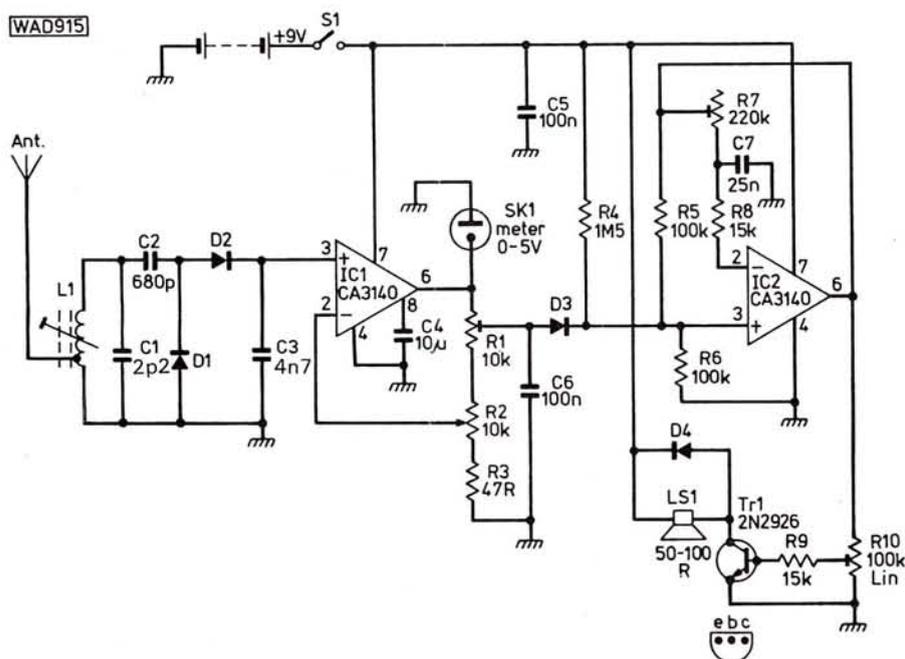


Fig. 1: Full circuit diagram for the audible field strength meter

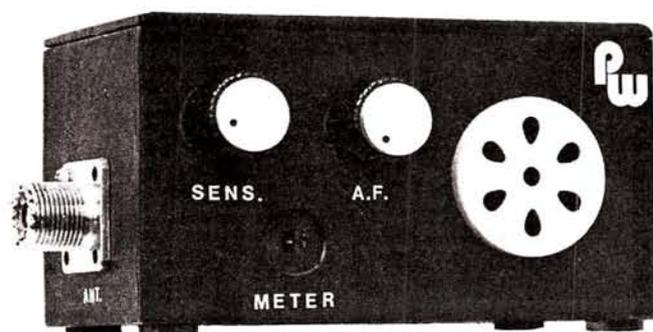

Output Stage

The output stage works in Class B, taking an increasing current as the volume is increased by R10. Most of the current is consumed in this stage, the i.c.s taking only about 3mA the pair. Therefore in the interests of battery life, it pays to keep the volume as low as is practicable. The actual transistor is not critical as long as it is an npn device of the 2N2926 type.

Some explanation should be given for the 10 μ F capacitor C4 between pin 8 of IC1 and earth. Earthing this pin causes the output voltage to fall to zero; consequently, this capacitor increases the rise time, this delay smooths out rapid variations of pitch which would

otherwise occur and render the result far less musical to the ear!

The prototype was built into a homemade hardboard box approximately 125 x 65 x 65mm and was provided with an SO239 socket, but a $\frac{1}{4}$ wavelength of coathanger wire suitably fixed into the "live" is all that will normally be required.

The circuit was constructed on a small p.c.b. measuring approximately 113 x 50mm. Eight pin d.i.l. holders were used for the two i.c.s, with the bottom of the former for L1 stuck through a hole drilled in the board in which it was fixed with Araldite. The extremities of the coil were soldered to the appropriate strips of the p.c.b.

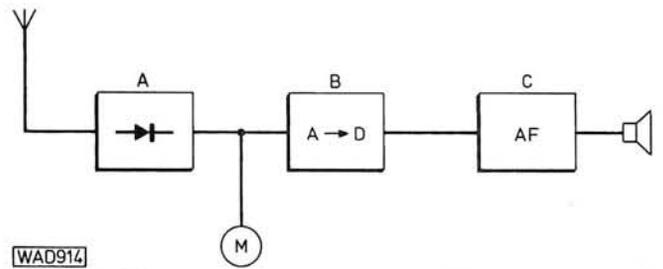


Fig. 3: Block diagram of the audible field strength meter


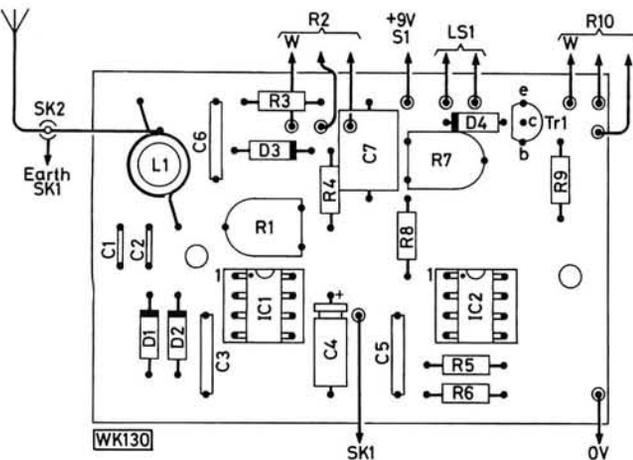
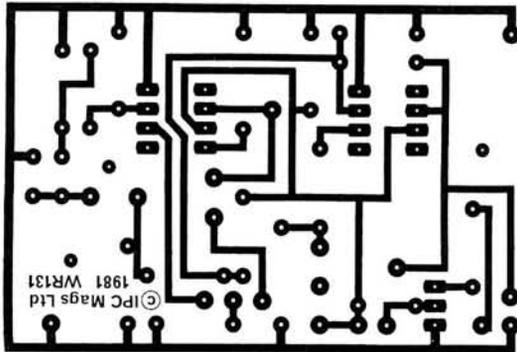


Fig. 2: Track pattern and component layout of the meter

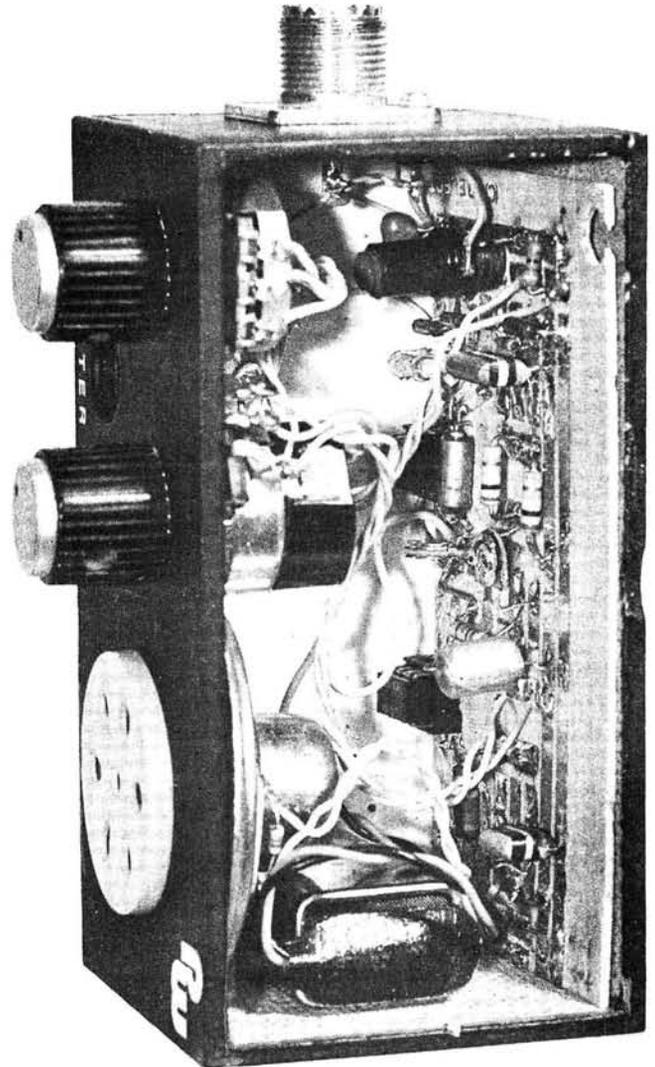

Setting Up Procedure

First connect a 1MΩ resistor from pin 3 of IC1 to the positive supply line. Move the slider of R1 towards the pin 6 end until the pitch of the note ceases to rise, then back off slightly.


Next adjust R7 until this note, which is the highest note of the range, is at a suitable pitch (about 2.5kHz), then remove the 1MΩ resistor and the lowest note will now be heard at about 100Hz.

Place the device in a suitable r.f. field and tune the core of L1 for the highest note (in conjunction with the sensitivity control). It will be found that the tuning is fairly broad and that some variation to the parallel tuning capacitor C1 may be called for. Also, tuning in a strong field with the sensitivity turned down is much easier than

trying to tune in a weak field with the sensitivity turned up. Note that R2 sets the d.c. output voltage of IC1 for a given r.f. field.

In use the device will consume between 3 and 50mA according to the setting of the audio gain. For convenience S1 is ganged to R10.

In practice, the unit is placed in a suitable part of the r.f. field and the sensitivity set to produce a note in mid-range. The desired adjustments are made to the transmitting equipment, using the pitch of the note to indicate optimum adjustment, the highest pitch denoting the greatest output. It may be necessary to reset the sensitivity control at some stage, as the adjustments proceed. In many cases a dummy load may be used to prevent unnecessary radiation, otherwise one would naturally select a portion of the band not in use.

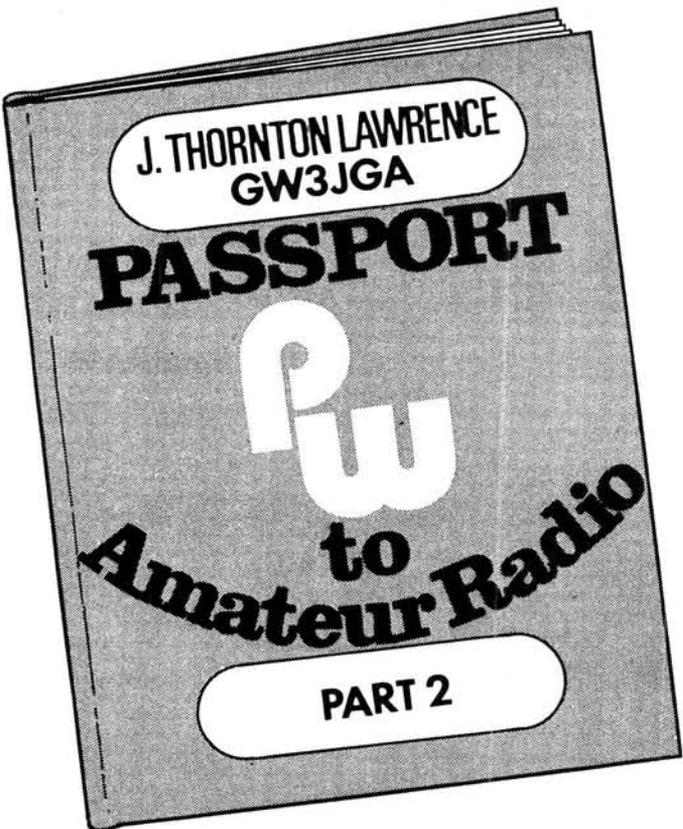

Last month we looked at the idea of becoming a Radio Amateur, now we take a closer look at the licence and studying for the RAE.

Before you can set up an "Amateur Wireless Station" you must first obtain an Amateur Licence, which is issued by the Radio Regulatory Department of the Home Office. There are two types of Licence, Class A and Class B. In order to qualify for the principal type Amateur Licence A, you will need to satisfy certain requirements, as follows:

- (1) be over fourteen years of age
- (2) be a British subject
- (3) have passed the Radio Amateur Examination
- (4) have passed the Post Office Morse Code Test
- (5) have paid the Licence fee (currently £8.00)

The Amateur Licence A allows operation on all the Amateur Bands.

The requirements for the Amateur Licence B are the same as for the A Licence with the exception of (4), the Morse Test, which is not required.

However possession of the B Licence only allows operation on the 144-146MHz (2 metre) band and higher frequency amateur bands.

Full details of the Amateur Licence, Radio Amateur Examination and Morse Test are given in an excellent 38 page publication *How to become a Radio Amateur*. This is essential reading and is available, free of charge, from:

Home Office,
Radio Regulatory Department,
Radio Regulatory Division,
Licensing Branch (Amateur),
Waterloo Bridge House,
Waterloo Road,
London SE1 8UA.

The RAE is conducted by the City and Guilds of London Institute and candidates must sit the examination at a recognised examination centre (normally the local Technical College or Evening Institute). The exam is held twice yearly in May and December. Special arrangements can be made for disabled or blind candidates.

The form of the RAE was changed in 1978-79, from the old traditional script answer type to the new multiple choice "Objective Testing" type. This is known as the "756, Radio Amateurs' Examination 1979-1981" (the format of this examination will continue substantially unchanged in 1982).

In the past, many would-be radio amateurs failed or did not attempt the RAE simply because they were unable to set down, in words, the answers to the questions. However, the multiple choice question overcomes this problem and the result has been a significant increase in the numbers sitting and passing the new form of the RAE.

Objective Testing

An Objective Test is defined as a series of questions each of which has only one predetermined correct answer, so that subjective judgement in marking is eliminated. The RAE is carried out using a four-option multiple choice type of objective question. In this type, a question is asked or implied, followed by four possible answers or options, only one of which is correct. The candidate is required to select the correct answer.

The questions are normally chosen to test the candidate's "factual recall", "comprehension" and "application". In general, the "factual recall" question tests the candidate's ability to remember the facts which he has been taught, and a "comprehension" question tests his understanding of what he has been taught. An "application" question, while requiring him both to know and understand what he has been taught, asks him to go further and apply his knowledge and understanding to a given problem.

An example of a "factual recall" question is given below: Class A3J-J3E amplitude modulation uses:

- a. only the upper sideband with a bandwidth of about 4kHz
- b. either one of the sidebands with the carrier suppressed
- c. morse telegraphy using either sideband
- d. one telephony sideband with reduced carrier

In a pre-test conducted to see how candidates would answer the question, the results were as follows:

- a. 6 per cent
- b. 64 per cent (correct answer)
- c. 8 per cent
- d. 19 per cent

no answer attempted 3 per cent.

The number of candidates choosing a particular answer is shown as a percentage of the total number of candidates. The next example is of a "comprehension" question:

In a series-resonant circuit, to halve the resonant frequency the LC product must be:

- a. halved
- b. doubled
- c. quadrupled
- d. tripled

In a pre-test conducted with this question, the results came out rather differently.

- a. 17 per cent
- b. 55 per cent
- c. 23 per cent (correct answer)
- d. nil

no answer attempted 5 per cent.

As you can see, the majority chose answer b which was unfortunately incorrect!

Since $f = \frac{1}{2\pi\sqrt{L \times C}}$, halving the frequency would mean doubling $L \times C$ and doubling the square root of the LC product would require quadrupling the LC product itself

(answer c). Finally, an example of an "application" question dealing with Ohm's law.

Fig. 6 shows the relationship between V and I in a d.c. circuit. The resistance of the circuit is:

- a. 8Ω
- b. 2Ω
- c. 0.5Ω
- d. 0.2Ω

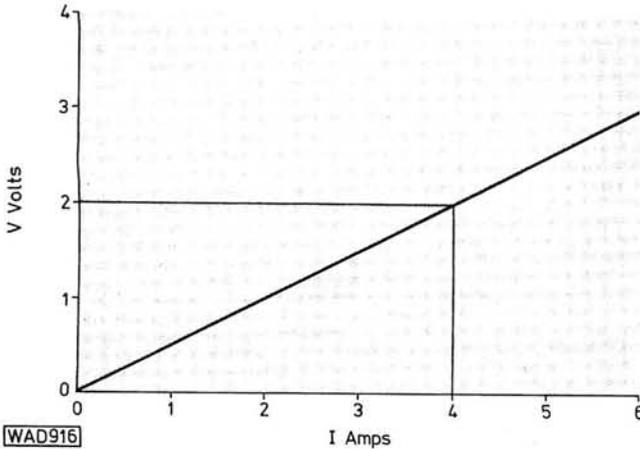


Fig. 6

The results of the pre-test conducted with this fairly easy question are as might be expected.

- a. 8 per cent
 - b. 6 per cent
 - c. 83 per cent (correct answer)
 - d. 2 per cent
- no answer attempted 1 per cent.

Advantages and Disadvantages

From the examiner's point of view, there are several advantages in Objective Testing. Because it is possible to have a greater number of questions, the paper can include questions on all areas of the syllabus, whereas traditionally only a limited number of topics can be covered. Also no "choice" questions are included, so all candidates answer the same questions.

The preparation of the question paper can be more systematic in covering the syllabus, and pre-tests can be held to estimate the degree of difficulty of each question before it is included in an examination paper. Marking is completely objective and eliminates the possible variations due to points awarded by different markers or by the same marker on different occasions.

From the candidate's point of view, there is less emphasis on his ability to express himself in his own words, his performance depends primarily on his technical knowledge and understanding. He is not hampered by time as adequate time is available. All things being equal his paper will be marked more accurately and impartially, and the results should be available to him sooner.

There are a number of common objections to Objective Testing, the most common being the view that someone with no knowledge can, by guessing the answers, obtain adequate marks. However, the City and Guilds of London Institute state that experience has shown that a rational elimination of one or more of the incorrect options is also likely and that applying a correction factor for guessing does not have a significant effect on the rank order of candidates. The policy of the City and Guilds is, therefore, not to apply a correction factor for guessing.

Another objection is that candidates should be tested on their ability to express themselves in writing. In the case of the RAE this ability is not one of the essential factors, whereas knowledge and understanding are. Objective Testing is, therefore, considered suitable for this examination.

From The Candidate's Viewpoint

The candidate will answer his multiple choice examination paper on special answer sheets using a pencil. He should attempt all questions and should find little difficulty in completing the answers in the time allotted. If he has difficulty in expressing himself but knows and understands the items in the syllabus, then this type of examination will be to his advantage. If he does not know the subject then it is highly unlikely that guessing will help him to gain marks. If he knows all the items in the syllabus reasonably well the overall result is likely to be better than knowing some items very well and some not at all, as all parts of the syllabus will be tested. There are no "choice" questions or "likely" subjects.

Examination Pattern

The RAE consists of two separate papers, a 1 hour paper containing 35 multiple choice questions on Licensing Conditions and Transmitter Interference and a second paper of $1\frac{3}{4}$ hours containing 60 multiple choice questions on Operating Practices, Procedure and Theory. Details are given below.

765-1-01 Licensing Conditions and Transmitter Interference

1 hour	
Syllabus	Number of Questions
Licensing Conditions	23
Transmitter Interference	12
	35

There will be a break of 15 minutes between the two papers.

765-1-02 Operating Practices, Procedures and Theory

$1\frac{3}{4}$ hours	
Syllabus	Number of Questions
Operating Practices	5
Electrical Theory	11
Semiconductors	7
Radio Receivers	9
Transmitters	8
Propagation and Antennas	14
Measurement	6
	60

It has been customary when preparing for the old style script examination, to go through past years' examination papers and practise answering the questions.

Because multiple choice questions for the RAE are extracted from a "bank" of pre-tested questions and because these are on returnable answer sheets, "previous years' questions" as such, are not available for practise. However, a selection of typical sample questions for practise purposes are available from the City and Guilds of London Institute, and details are given as follows.

Syllabus and Question Paper

The syllabus upon which the examination is set is contained in a pamphlet No. 765, *Radio Amateurs' Examination*. A copy of the syllabus, plus a set of 40 sample ques-

tions from the paper (price 80p) can be obtained by post only from:


The City and Guilds of London Institute,
Sales Section,
76 Portland Place,
London W1N 4AA.

The syllabus is also reproduced in Appendix C of the Home Office publication *How to become a Radio Amateur*.

One of the important factors when embarking on a new hobby or area of interest, is to find sources of help and information. This is particularly true in amateur radio, where both technical and practical knowledge is needed.

It is very useful to attend meetings of your local radio club or society, as you will then have the opportunity to see amateur radio equipment being used and will be able to obtain guidance and help when you are purchasing or building things for yourself.

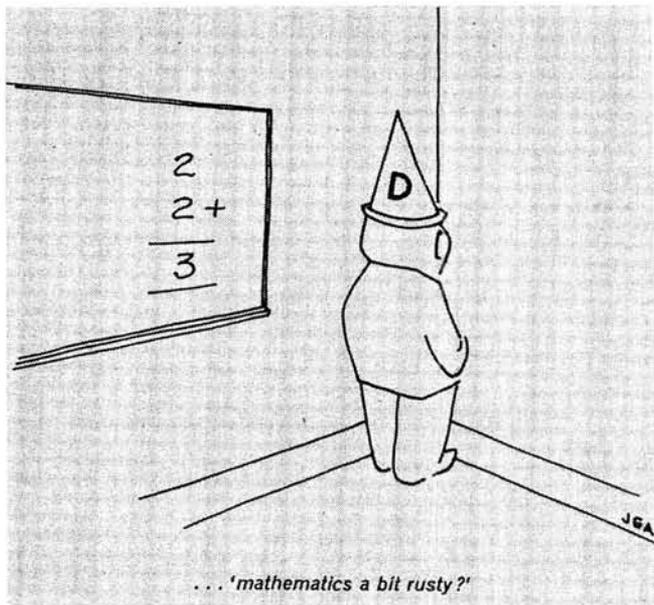Membership of the RSGB is also very useful, as then you can take advantage of the QSL Card Bureau, the Slow Morse Transmissions, a discount on RSGB publications, and obtain information about radio clubs and societies which are affiliated to the RSGB. The annual subscription includes the supply, by post, of the Society's monthly journal *Radio Communication (RadCom)*.



Studying for the RAE

The method of studying for the RAE depends on your personal circumstances. The various ways are:

Evening classes

Correspondence course

Home study, with or without some tuition

If you live near a technical college or school which runs evening classes, then this is probably the best way for you to study. Details of these courses appear in various radio magazines and in the local press. The cost of tuition and examination fees varies from place to place but these will be known when registering, usually in September.

It is often advantageous to contact your local evening institute ahead of time, stating your interest in the RAE as, without prior knowledge of the need, the institute may not have considered putting on such a course. Courses can only be run providing there is a sufficient number of candidates and liaison with the local radio club is often a way of overcoming this problem.

Correspondence courses or home study for the RAE require continuous and regular work sessions. Home study requires a lot more personal discipline to get through the more difficult items, as you will find it a great temptation to leave them until the end, when it is usually too late! It is always useful and particularly so in the case of home study, if you can enlist the help of a local radio amateur or suitably qualified friend, who will talk-through any problems you may have.

As far as textbooks are concerned, these can be divided into two categories, the "essential" and the "desirable but not essential". Those concerned directly with becoming a radio amateur are essential reading. They are:

(1) *The Radio Amateur's Examination Manual (8th Edition)* by G.L. Benbow G3HA. RSGB £2.73.

(2) *A Guide to Amateur Radio (18th Edition)* by Pat Hawker G3VA. RSGB £3.07.

The books in the second category are much more comprehensive and naturally cost more; they are:

Radio Communication Handbook Volume 1 & 2 (5th Edition) RSGB £10.20 and £9.06 respectively.

All items can be obtained from:

RSGB Publications (Sales),
35 Doughty Street,
London WC1 2AE.

Here we are then, you have registered at your local evening institute for the RAE course, the books are ordered and you are ready and waiting to get down to the "nitty gritty".

Arithmetic

Let's start with arithmetic (I always think that the word arithmetic is less daunting than mathematics). There are going to be some calculation questions in the RAE and if you can do these correctly, you can gain "full marks" on each question in a matter of seconds. Even fairly straightforward electrical calculations can present very real difficulties if you have not seen the sharp end of a blackboard pointer since you left school, so the purpose of this section is to remind you of the basics involved.

If you have read through the instruction book of a pocket calculator you will know that there are four "basic arithmetical functions", namely, addition, subtraction, multiplication and division.

Addition and Subtraction

So far as the problems that you will meet in the RAE are concerned, addition and subtraction will take care of themselves, for example, $3 + 7 = 10$ and $4 - 2 = 2$.

Multiplication and division may be written down in several different ways, so here are a few alternatives.


Multiplication

$a \times b$ can also be written as $a.b$ or simply ab .

Division

$a \div b$ can also be written as $\frac{a}{b}$. Thus $1 \div 2$ is the same as $\frac{1}{2}$ (one upon two or one over two).

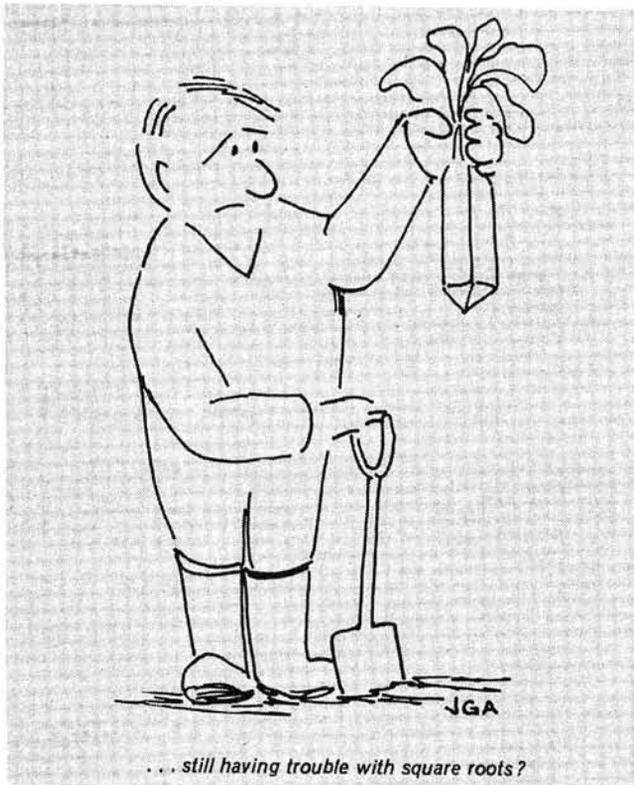Now for the not-so-basic arithmetic functions, reciprocals, squares and square roots.



Reciprocals

The reciprocal of "a" is $\frac{1}{a}$ or from division $1 \div a$ or one upon a, and to put it numerically, the reciprocal of 4 is $\frac{1}{4}$ and 100 is $\frac{1}{100}$.

This function, together with the squares and square roots, occurs often in resonance and frequency calculations.

Squares

If a number is multiplied by itself the answer is known as the square of the number. For example $a \times a$ is written as a^2 or a squared. Thus a^2 is the square of a. And, to put it numerically, 9 is the square of 3, since $3 \times 3 = 9$.

Square Roots

The square root of a number is a figure which, when multiplied by itself, is equal to the original number. For example the square root of 9 is 3 because when 3 is multiplied by itself, it equals 9, written $\sqrt{9} = 3$. Similarly, $\sqrt{25} = 5$ (because $5 \times 5 = 25$) and $\sqrt{4}$ or root 4 = 2 (because $2 \times 2 = 4$) and so on.


Incidentally, not all square roots are whole numbers. For instance, $\sqrt{2}$ has been calculated to at least 50 decimal places, but is most often used as 1.41 or 1.414. Finally, $\sqrt{2} \times \sqrt{2} = 2$ and $\sqrt{5} \times \sqrt{5} = 5$ and $\sqrt{25} \times \sqrt{25} = 25$.

Problems in the actual RAE which involve square roots are likely to work out exactly to some simple figure, as the question will be arranged to test your knowledge and application of the formulae rather than your ability to do extensive mental calculations.

**NEXT MONTH: ELECTRICAL UNITS
AND OHM'S LAW**

INTRODUCING SSTV—2


▶▶▶ continued from page 21

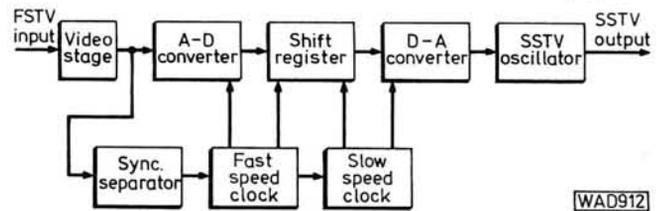

WAD912

Fig. 13: Block diagram of a digital fast to slow-scan line converter

For simplicity, in our example we divided the line into 20 pixels, but in practice many more are used. Optimum overall definition occurs when the vertical and horizontal resolving powers are equal, so for a 128 line square SSTV picture the line is divided up into 128 pixels. Since each pixel is represented by a 4-bit word, the shift register must have a capacity of 512 bits. The shift register memory will be loaded with the digitised video information for the one line in approx 65 microseconds. The fast-speed clock then triggers the slow-speed clock which allows the information to move out of the shift register at the slow-scan speed of 60 ms per line. This has completed the conversion and the digitised information could be transmitted directly. This will probably be the mode adopted in the future when most amateurs have scan conversion equipment, but at the present time a D-A converter is used to convert the signal back to analogue form for transmission (Fig. 14).

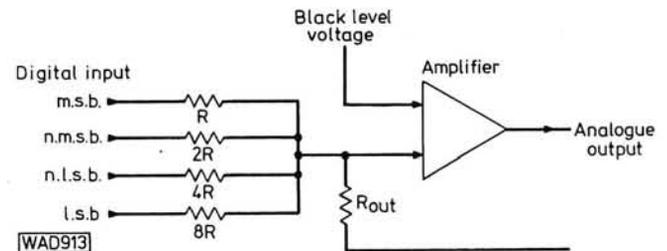

WAD913

Fig. 14: 4-Bit D-A converter

The D-A conversion is effected by controlling the gain of an amplifier by a series of binary weighted resistors, which are brought into circuit when the corresponding bit is 1. A d.c. voltage equal to the video black level voltage is applied to the input of the amplifier. When all the bits are at 0, the amplifier acts as a unity gain voltage amplifier, thus the output will be the video black level voltage. As any bit becomes 1, the appropriate resistor will be brought into circuit, which will increase the gain of the amplifier, thus the output will be proportional to the binary code presented to the converter. This output is then used to frequency modulate the SSTV oscillator between 1.6 kHz and 2.3 kHz, the black and white frequencies.

When the transmission of the line data has been completed a sync pulse at 1.2 kHz is inserted and the conversion process is repeated for the next line. In 7.2 secs all 120 lines comprising the frame will have been transmitted, but as mentioned before, it is becoming common practice to transmit a further 8 lines of grey scale at the bottom of the picture, so making the frame up to 128 lines (2⁷). The grey scale makes for easier alignment of the receiver, and also allows the interesting possibility of transmitting the sending stations' call sign on every frame.

Part 3 of this series will examine the 'black box' used at the receiving station to convert slow-scan back to fast-scan standards suitable for display on a conventional TV receiver.



'EXE'

MICROWAVE TRANSCEIVER

Part 4

Dick GANDERTON G8V FH , John M.FELL G8MCP & Owen COCKRAM G8OWZ

By now you should have a working 10GHz wide-band f.m. transceiver all ready and waiting for your first microwave QSO. Obviously it is useless setting up the equipment and calling CQ-CQ-CQ and expecting a reply. The chance of another amateur being on the same frequency as you and actually beaming his signals your way is extremely remote. In fact, most microwave QSOs are arranged in advance and this is where it is useful in the early stages to have a friend building a PW Exe as well.

With your friend you can start with short hops of a few hundred metres to get the equipment sorted out and get some sort of feel for microwave operation. There is no real substitute for practical experience.

IF Alignment

As was explained in the first part of this series, the i.f. of both transceivers must be the same. This can be achieved by simply calibrating the i.f. Tune control using known broadcast stations and extrapolating upwards. This is not too bad for short hops where you can literally talk to your partner, but for longer distances where you cannot have frequent meetings and have to rely on some form of radio talkback a more precise means of i.f. tuning is needed.

A simple alignment aid can be constructed at little cost using the design shown in Fig. 11. A simple crystal controlled oscillator is used with a tuned collector load arranged so as to allow the required harmonic to be fed to the small antenna. The prototype used a readily obtainable cheap TV crystal with a fundamental frequency of 4.43MHz. In this case, the 23rd harmonic is selected to give an output at 102MHz. Other crystals could be used to give different frequencies. Obviously, though, it is essential for both you and your partner to use the same frequency. Again, you can calibrate the i.f. Tune control.

Construction

The calibrator is built on a piece of p.c.b. using the copper as a ground plane. The components are built up as shown in Fig. 12, ensuring that leads are kept as short as possible and that all the joints made to the ground plane are well made. The PP3 battery is also soldered to the ground plane to ensure that the metal case of the battery does not affect the stability of the oscillator.

The complete calibrator can be housed in a suitable case. The on-off switch is mounted in the case lid and the antenna brought out via a small grommet.

In use, the calibrator is switched on and held close to the input of the 100MHz i.f. module. The i.f. Tune control is then adjusted for reception of the carrier put out from the calibrator. It is advisable to check for other harmonics to satisfy oneself that the correct harmonic has been selected. The photograph shows the various harmonics generated by the calibrator displayed on a Marconi Instruments spectrum analyser.

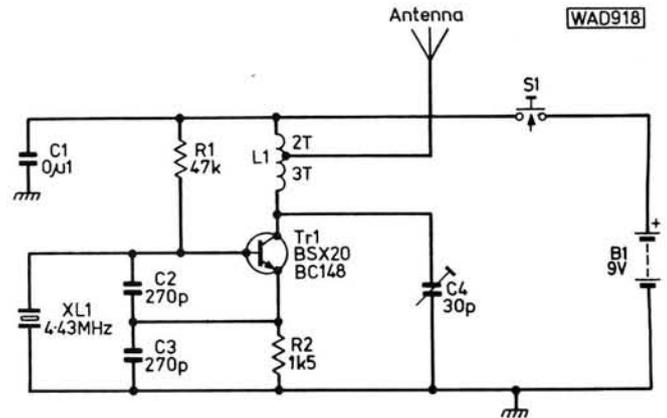


Fig. 11: Circuit diagram of the i.f. alignment aid


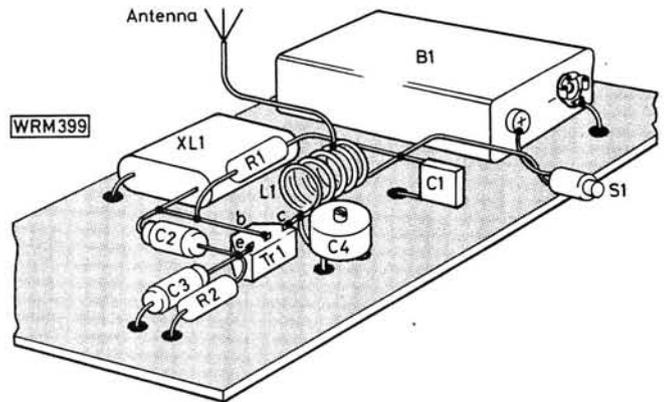


Fig. 12: Component layout details of the oscillator

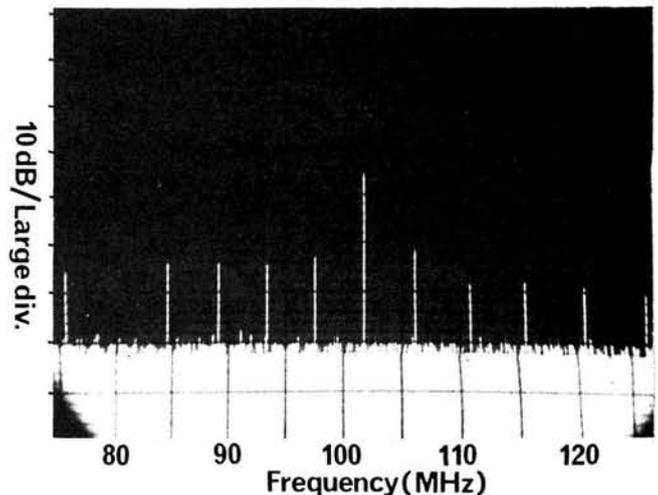

Spectrum analyser photograph showing relative harmonic output and amplitudes

Operating with the Exe

Having aligned your 100MHz i.f. to coincide with your partner's *PW Exe* you are now ready to attempt your first QSO over a short range.

Set up the two Exe units on their tripods and point the antennas towards each other. Decide which of the two stations will run with a.f.c. in and then slowly adjust the micrometer tuning control on one station only until you receive the signal from the other station. This is easily recognisable as a sharp ping in the speaker. One station must have its 1kHz tone switched on to provide some modulation. Now, carefully adjust the tuning controls for optimum reception of the 1kHz tone and then try switching in the a.f.c. and note the result.

If the signal disappears, then try switching the a.f.c. to the other sense. If the modulator is set correctly then the a.f.c. should hold the Gunn oscillator frequency at its set value. A useful addition is a voltmeter to monitor the Gunn diode voltage. With such a voltmeter, which need not be super-accurate, it is easy to keep track of the operation of the a.f.c. as well as making it simple to set the Gunn diode voltage correctly at the start.

You should now be in a position to attempt to pass speech over the link. The tone should be switched off and the microphone plugged in. You should be able to transmit speech simultaneously in both directions if you have set the i.f. correctly and have tuned one station i.o. high and the other i.o. low.

Beacons

There are several 10GHz beacons dotted around the UK and these are very useful when testing the functioning of a microwave station. Using a known beacon it is possible to calibrate the micrometer readings in terms of frequency. For example, if you listen to a beacon with a known frequency of 10.100GHz you can make a note of the setting of the micrometer and then use this for future reference.

Beacon hunting can be frustrating at times, especially if you try it on your own. If you can receive the beacon early on then it is not so bad, but you can spend fruitless hours searching up and down the band for a particular beacon not knowing if it is working or if conditions are such that it is impossible to hear the beacon.

Longer Paths

When you are confident that your equipment is working correctly and that you know how to operate it over short distances you are ready to try longer line-of-sight paths. The popular way of achieving longer paths is to use two suitable hilltops which are unobstructed by other hills and which allow you a clear take-off without trees or buildings getting in the way. You should be equipped with an Ordnance Survey map(s) covering both sites, and plot the

Readers who intend to operate the *PW Exe* should be in possession of the appropriate licence issued by the Home Office to those who have passed the City and Guilds Radio Amateurs' Examination. Details may be obtained from: The Home Office, Radio Regulatory Department, Amateur Licensing Section, Waterloo Bridge House, Waterloo Road, London SE1 8UA.

path on the map. This will allow you to work out the compass bearing from your station to the other site and thus you can accurately align your dish, using a small compass. You must be prepared to spend some time and effort in getting the dish properly lined up both horizontally and vertically. A small circular spirit level is useful for the vertical alignment and could be attached permanently to the lid of the diecast box.

The tripod should be anchored by guy-ropes and pegs to prevent it being blown over or accidentally moved.

Some form of reliable talk-back is required and this can be either 2m or 70cm to suit you and your partner. There is an agreed talk-back frequency used by microwave enthusiasts, particularly during cumulative activity periods and obviously it is important to adhere to this if you intend to work contests later on. The frequency agreed for the talk-back calling channel is 144.330MHz u.s.b. Talk-back equipment should be positioned so that you can use it without have to keep walking away from the microwave station.

The RSGB organises the Cumulative Activity Periods and members can obtain details by subscribing to the monthly *Microwave Newsletter*. This useful publication gives information on current developments and amateur activity on all the allocated microwave frequencies. The RSGB also organises Microwave Roundtables where members can discuss developments and cross-fertilise ideas on all aspects of microwave working. Further details are available from RSGB headquarters.

The Cumulative Activity Periods provide a means of getting as many operators out working as possible. However, some operators take it extremely seriously and it is probably advisable not to operate during these 'contests' unless you can set-up properly. These 'super-enthusiasts' do not take kindly to having a complete beginner tuning up and down the band when they are trying to get their gear tuned in for a really long distance QSO. Get a fair amount of operating under your belt with your partner before venturing out and seeking unknown operators.

★ components

Resistors

$\frac{1}{4}W$ 10%

1.5k Ω	1	R2
47k Ω	1	R1

Capacitors

Ceramic

270pF	2	C2,3
0.1 μ F	1	C1

Min. Trimmer

30pF	1	C4
------	---	----

Semiconductors

Transistors

BSX20	1	Tr1
-------	---	-----

Inductors

5T, 6mm dia. 18 s.w.g. L1 (see text)

Miscellaneous

Crystal 4.43MHz (see text); Copper-clad board 90 x 70mm; Case to fit board, plastic or metal.

Buying Guide

Microwave Heads

Pascal Electronics, Hawke House, Green Street, Sunbury on Thames, Middlesex, TW16 6RA.
 Plessey Optoelectronics and Microwave Ltd.
 Wood Burcote Way, Towcester, Northamptonshire, NN12 7JN.
 Electronic Workshops, 5 Burston Road, London SW15.
 Chordgate Ltd. (Dept C), 75 Faringdon Road, Swindon, Wilts.

Waveguide and Flanges

Earth Stations, 22 Howie Street, London SW11 4AR.
 JMG Electronics, 50 East Street, Horsham, Sussex.
 Electroforms and Components Ltd., 90 High Street, Whetstone, Leicester LE8 3LQ.
 N. Foot, 29 Wheelers Lane, Bear Cross, Bournemouth BH11 9QQ.

Microwave Semiconductors

Pascal Electronics.
 J. Birkett Radio Component Suppliers, 25 The Strait, Lincoln LN2 1JF.

Antennas

PW Editorial Offices, Westover House, West Quay Road, Poole BH15 1JG, or Hatfield House, Stamford Street, London SE1 9LS.
 M & B Radio, Leeds, 86 Bishopgate Street, Leeds LS1 4BB.
 MuTek Ltd., Bradworthy, Holsworthy, N. Devon, EX22 7TU.
 Plessey Optoelectronics and Microwave Ltd.

General Mechanical Items

K.R. Whiston Ltd., New Mills, Stockport SK12 4PT.
 Also consult Yellow Pages directory.

Reference Material

The Microwave Column—RSGB Radio Communication journal.
 Ham Radio Magazine.
 VHF Communications magazine.
 RSGB v.h.f.—u.h.f. Manual, Third Edition.
 Microwave Newsletter, RSGB

Operational UK 10GHz Beacons

		QRA	NGR	BEACON KEEPER
GB3IOW	10-1GHz	ZK34a	SZ494772	G8IDZ
GB3ALD	10-12GHz	YT30a	CI865798	G3JHM
GB3LEX	10-4GHz	ZM24d	SK485108	G8CAC
GB3XGH	10-4GHz	YN57d	SJ567721	G3PFR

WARNING

Microwave energy can cause damage to the tissues of the eye. Whilst there is no risk during normal working of the *PW Exe* under no circumstances should you look down the waveguide or into the microwave head cavity during operation.

Miscellany

At the start of this series we mentioned alternative microwave heads. One of these was the Wessex Alarms unit and this is readily available on the surplus market at around £8.00 for just the microwave unit.

Although it is possible to use this unit with the *PW Exe*, and some readers have already done this, its disadvantages make it less attractive than the AEI or Plessey units.

However, it can be used to make a useful bench frequency standard to allow you to work the *PW Exe* without having to find a beacon or disturbing your friend to provide the necessary signal.

By using your *PW Exe* calibrated for reception of a 10.1GHz beacon it is possible to retune the Gunn oscillator to give 10.1GHz with a known fixed voltage on the Gunn diode. The screw behind the Gunn diode post is the tuning screw and this is carefully adjusted inwards until you hear the 'ping' in the Exe speaker. You will, of course, need the 1kHz tone. Remember to keep the Schottky mixer diode shorted out as this is not used for this application.

Mention was made of the usefulness of a voltmeter to measure the Gunn diode voltage. The same meter can also be used to check the Schottky mixer diode current and a suitable circuit is given in Fig. 13. The meter and associated switching can be mounted on the rear of the diecast box to the left of the a.f.c. switch.

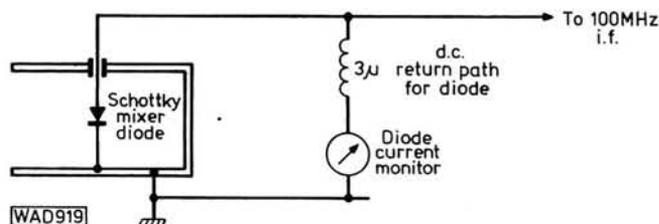


Fig. 14: Schottky mixer diode current monitor circuit

The Future

The response to this project has been remarkable and already several readers have built systems based on this design. We would like to hear from readers who have built and used the *PW Exe*. In particular, we are interested in hearing of the path lengths worked, conditions etc.

Practical Wireless will continue to cover microwaves with other projects and ideas.

Acknowledgments

We would like to thank a number of local amateurs for their help and encouragement during the development phase of this project. In particular G8MXW, G8OWZ, G8MCQ and G3VPF.

Next month in *Pw*

Free Inside

Practical
wireless

OCT
1981

70cm Repeaters

DATA CARD

the
key to
morse

Channel	Repeater Input (MHz)	Repeater Output (MHz)
RBO	434·600	433·000
RB2	434·650	433·050
RB4	434·700	433·100
RB6	434·750	433·150
RB10	434·850	433·250
RR11	434·875	433·275
	434·900	433·300
	434·925	433·325
	434·950	433·350
	434·975	433·375

There is a lot more to c.w. than just sending a stream of dots and dashes and it is not really so difficult to learn. We hope to dispell some of the fears that haunt many potential Class A licensees


NiCad CELLS (USES & ABUSES)

NiCad cells can be very economical, but if they are treated correctly their life can be extended for many more charge and discharge cycles. In this article we tell you how to get the most from your NiCad cells



ON SALE
4 SEPT.

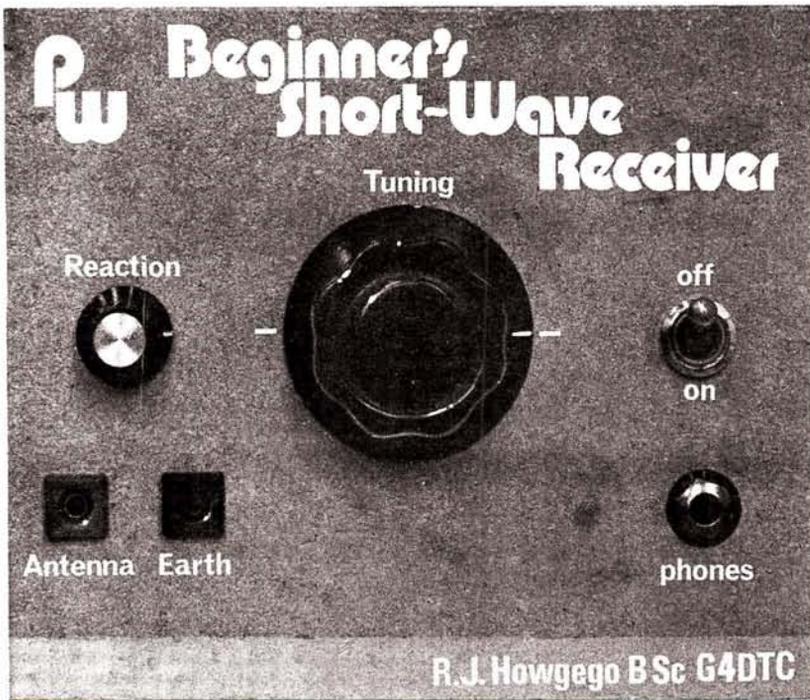The callsigns of all amateur repeaters in the U.S. with the prefix GB3 followed by two unique letters are identified on the map only by their callsigns together with the allocated channel number.




This circuit was developed in response to the demands of a number of young s.w.l.s, most of them absolute beginners, for a simple but effective short-wave receiver.

It was felt that the following criteria should be satisfied:

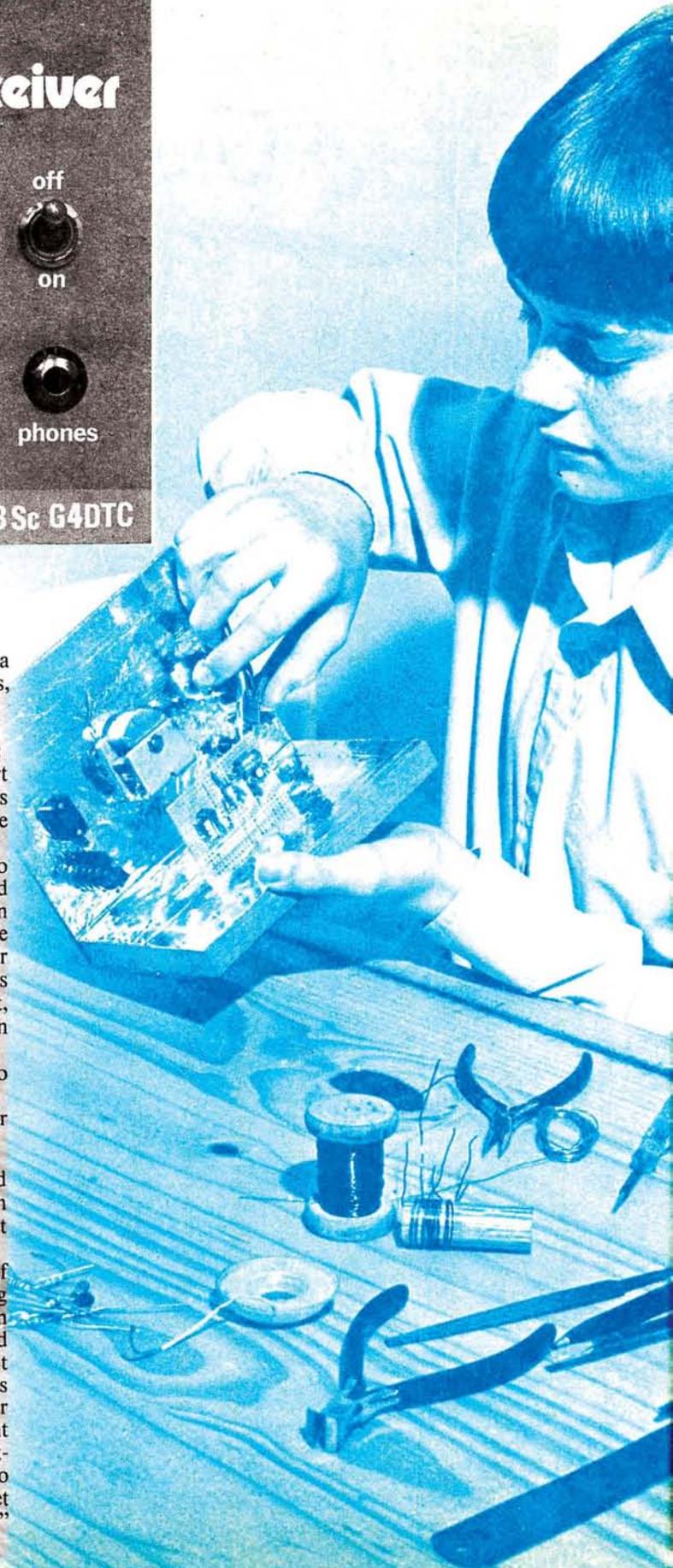- 1) The price should be kept to a minimum. If every part is bought new the total outlay will be about £12 but this may be halved if suitable variable capacitors are already to hand.
- 2) Since the s.w.l.s concerned were potential radio amateurs it was essential that the design gave good results on the amateur bands. This receiver brought in DX at loudspeaker strength and on 80 metres the results were comparable with the standard amateur transceiver. In fact, in comparison with the author's £200 FRG7 it was found that, with careful adjustment, most signals audible on the FRG7 could be resolved on the simple receiver.
- 3) The receiver should work first time and require no alignment.
- 4) There should be no metalwork, costly boxes or glamorous dials.

The present design uses a wooden base and hardboard front panel but it was found necessary to line these with kitchen foil to prevent hand-capacity effects and a slight 50 Hz hum noticeable on c.w. and s.s.b. signals.

To minimise the cost the ancient and educational art of coil winding was revived and details of two coils covering 3.5-30 MHz have been included. The circuit will function quite happily at all frequencies between 150 kHz and 100 MHz although at very high frequencies adjustment becomes somewhat critical. A low impedance output is provided as it was thought more likely that low, rather than high, impedance headphones or speaker might already be available. Hi-Fi stereo headphones gave excellent results and it was found that the three-way stereo jack plug connected well with the two-way socket provided. Adequate loudspeaker volume for "personal" listening was provided by all but the weakest stations.



Circuit Description

The field effect transistor (f.e.t.) Tr1 operates as a regenerative detector in a way that will be well-known to more mature readers familiar with the equivalent valve circuit. C2 tunes the receiver to any frequency within a band determined by the number of turns on coil L2. Some of the amplified signal appearing at Tr1 drain is fed back to L2 by L1, the amount of feedback being controlled by C1. C1 is adjusted so that the feedback is almost sufficient to cause the circuit to oscillate.

At this point the gain of Tr1 is considerable, the circuit becomes highly selective and most effective for the reception of a.m. signals. For c.w./s.s.b. signals feedback is increased just beyond the point of oscillation, resulting in extreme sensitivity. The detected signal is isolated by the r.f. choke and passed to Tr2 which is a simple audio amplifier.

Almost any *n*-channel f.e.t. will operate as Tr1 but the 2N3819 was found to produce the best audio output of those tried and is probably the most readily available. Similarly almost any small *npn* transistor will work as Tr2.

Component values are not critical but should be within 20 per cent of those suggested. Any small output transformer will do for T1 such as Eagle LT700 or those found in "Hong Kong" pocket radios, most of which have three connections on one side and two on the other. The centre wire of the three should be cut off and the remaining two used as the primary connections; the opposite pair are the secondary (loudspeaker) connections. Similarly C2 may be any small variable capacitor such as those found in pocket radios, or the larger type used for valve receivers; in all cases only one tuning gang should be used, the other(s) ignored. A slow motion drive for C2 is desirable for tuning above 10 MHz and essential if the receiver is intended primarily for s.s.b. C1 could be a Jackson Type C804 and C2 a Jackson Type O if new components are being bought.

Construction

The front panel, a piece of 170 × 100mm hardboard, is drilled to take the panel controls and sockets as shown in Fig. 2. This is nailed or screwed onto a piece of 12.5mm thick wooden board measuring about 170 × 150mm which forms the base. Holes will also need to be drilled to take the particular arrangement of bolts for fixing C2 to the panel. A single sheet of kitchen foil is cut to size (270 × 170mm), glued with Copydex or Unibond to the inside surface of the base and panel and rubbed out flat. The front panel components are then mounted, taking care that both variable capacitors make electrical contact with the foil.

Most of the components are soldered to a piece of Veroboard 95 × 64mm having a 0.15in. matrix and this should be assembled next. The copper tracks must be cut as shown in Fig. 2 with a Vero cutting tool or a hand-held 5mm drill.

The components are inserted as shown in Fig. 2, soldering them as close as possible to the board and taking care not to bridge the copper tracks with solder. Two tags, bent at 90°, are soldered to the lower part of the board for fixing the board to the wooden base. Four lengths of bare wire, each about 100mm long, should be soldered to the copper side of the board for later connection to the variable capacitors and antenna and earth sockets. Five Veropins are inserted as shown and form the soldering points for the coils.

The Veroboard layout must now be checked thoroughly and the completed board screwed onto the base so that the tags hold it vertically behind the front panel. At the same time the four bare leads may be cut to size and soldered to

★ components

Resistors

¼W 10%		
2.2kΩ	1	R2
4.7kΩ	1	R3
330kΩ	1	R4
1.8MΩ	1	R1

Capacitors

Ceramic plate

100pF	1	C3
10nF	1	C4
47nF	1	C5

Electrolytic, axial lead

47μF 10V	1	C6
220μF 10V	1	To be fitted between A2 and K2 on Veroboard if needed + to A2

Variable, see text

100pF	1	C1
300pF	1	C2

Semiconductors

Transistors

BC108	1	Tr2
2N3819	1	Tr1

Miscellaneous

2.5mH choke (Repanco CH1); Transistor output transformer (see text); 4mm sockets (2); 0.15in. Veroboard 95 × 64mm; ¼in. moulded jack socket; Toggle switch; Knobs (2); 9V battery and connector; 26 s.w.g. enamelled copper wire; Cooking foil; Wood, screws etc.

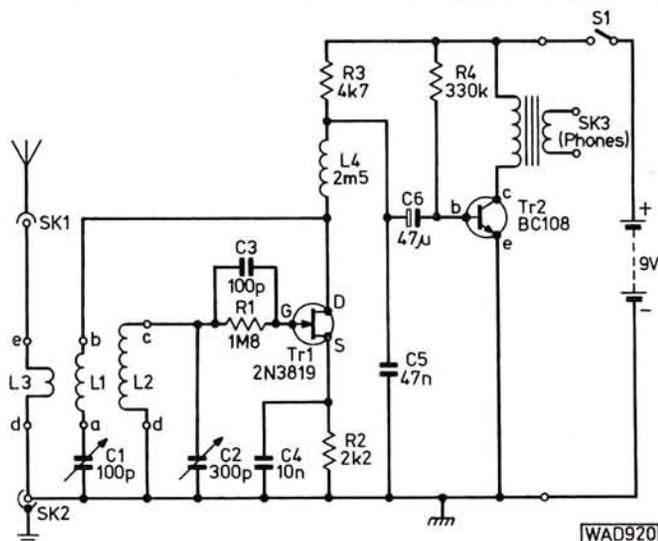


Fig. 1: The circuit diagram of the s.w. receiver

Coil Winding Details

	Number of turns		
	L1	L2	L3
3.5 to 11 MHz	9	36	6
9 to 30 MHz	4	10	3

All coils close-wound with 26 s.w.g. enamelled wire on 16 mm diameter plastic former.


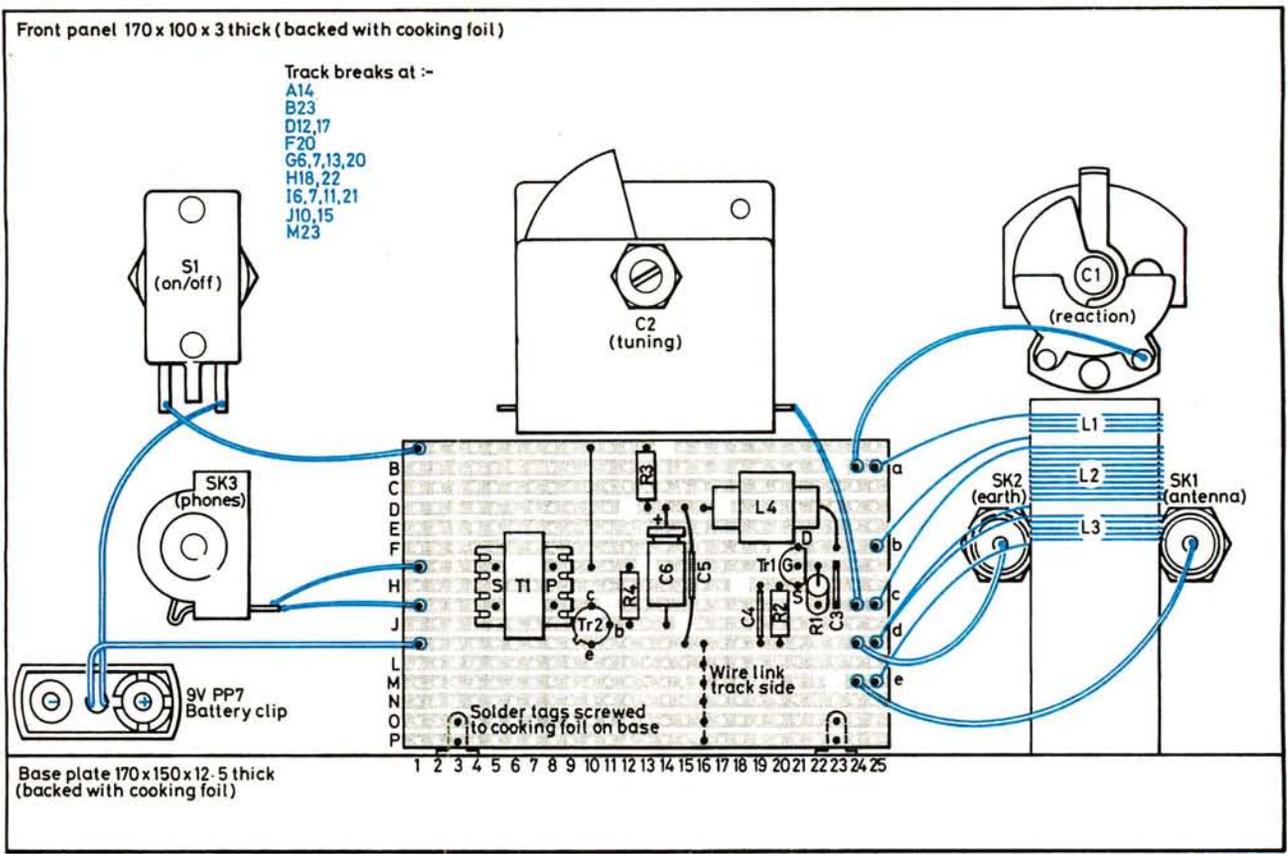


Fig. 2: Interwiring and Veroboard layout. This drawing is to scale to allow the front panel layout to be copied

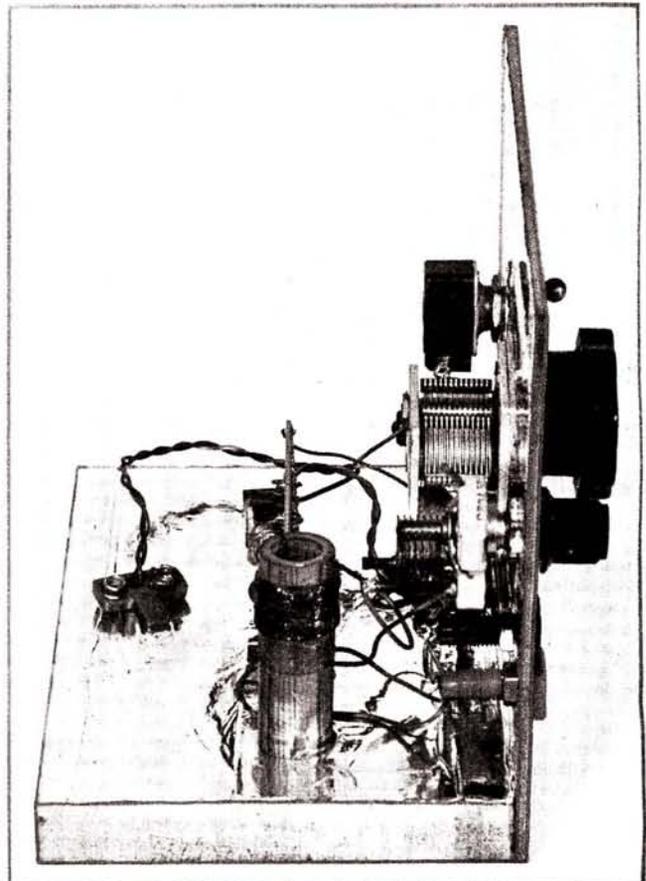

the variable capacitors' fixed vanes and antenna and earth sockets. The switch, output socket and battery connector leads may now be wired to the Veroboard. The wiring is checked, battery and headphones connected and the power switched on. If a loud hum emanates from the headphones when a finger is placed on C3 the circuit is probably functioning correctly.

All that remains is for the coils to be wound and it is recommended that the coil covering 11–3.5MHz be tried first. A 76mm length of plastic or paxolin tube having a diameter of about 16mm will be required for each former and the author found some small plastic phials used for holding Christmas glitter to be ideal. The plastic stopper provided could be screwed onto the receiver base and the coils then pushed onto the stopper before soldering the coil connections to the Veropins. Holes can be drilled through the tube to anchor the ends of the windings and each winding may be painted with French polish to keep it in shape. Although the number of turns is not critical it is essential that, when looking from one end of the coil L1 and L2 are wound in the same direction, as indicated in Fig. 2. The enamel is scraped off the ends of the wires which are soldered directly to the Veropins and the wiring is then complete.

Operation and Calibration

Although many stations will be received on only a short piece of wire the longest possible antenna is recommended. An earth connection will normally produce a slight improvement but is not essential. Adjust C1 so that the vanes are fully unmeshed and rotate C2 until a station is found. If nothing is heard close C1 slightly and repeat the procedure. Once a station is found, further rotation of C1 will considerably increase the volume of the signal up to a

point at which the circuit begins to oscillate. This is evident when a whistle accompanies each station tuned in. The circuit should be held just below this point of oscillation when tuning a.m. stations or just beyond it for c.w./s.s.b. signals. With a little practice this technique is quite easily mastered.

A paper dial is glued to the front panel around the tuning control which is then ready for calibration. An r.f. signal generator makes calibration easy and accurate and younger readers might be advised to seek out such instruments in their school physics laboratories.



CONSTRUCTION RATING **Beginner**


BUYING GUIDE

All the components for this project can be obtained from a number of our regular advertisers

APPROXIMATE COST **£12**

However, an alternative technique is to advance C1 beyond the point of oscillation, at which point the receiver will radiate a signal at the frequency set by C2. This radiated signal may then be found on an already calibrated receiver and the frequency marked on the dial. Failing this, if the coil winding details have been followed precisely and hence the tuning range approximately known it is possible, by tuning slowly across the band, to recognise the various amateur and broadcast bands and gradually piece together the calibration in this way.

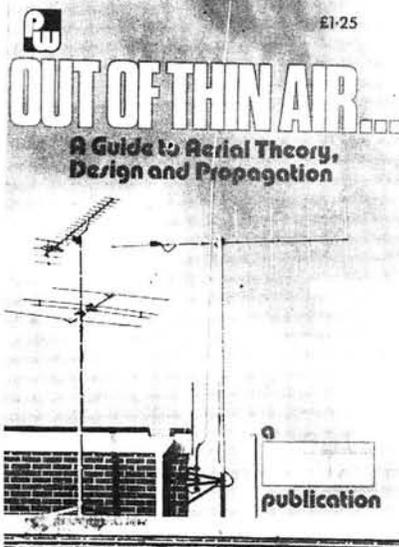Once the constructor is familiar with coil winding techniques other smaller or larger coils may be tried, eventually providing access to a large part of the radio spectrum.



Aerials and aerial accessories are very definitely among the most popular topics covered in *Practical Wireless*. In response to requests from readers, we've reprinted a selection of articles from the past three years, plus two new features—one by Ron Ham on v.h.f. propagation, the other describing the "Ultra-Slim Jim", a new version of that most popular 2-metre aerial design by Fred Judd.

Out of Thin Air has 80 pages, 295 x 216mm, and is available from Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, price £1.50 including postage and packing to UK addresses, or £1.80 by surface mail overseas. Please ensure that your name and address are clearly legible.

OUT OF THIN AIR

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me.....copies at £1.50 each to include postage and packing (£1.80 surface mail overseas)

I enclose P.O./Cheque No..... Value

UK remittances must be by crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....
.....

..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

— Cut round dotted line —

MAIL ORDER

FROM



by two way
FREEPOST

MORSE KEYS		
HK 707	Straight Up/Down keyer	£11.44
BK 100	Semi-automatic mechanical bug	£17.88
MK 702	Up/Down keyer on marble base	£22.43
MK 702	Manipulator	£22.43
MK 704	Squeeze paddle	£14.38
MK 705	Squeeze paddle on marble base	£22.43
EKM 1A	Morse code practice oscillator	£8.63
MK 1024	Automatic memory keyer	£135.13
EK 150	Semi/Automatic keyer	£74.75

LINEAR AMPLIFIERS		
2M10-80P	144MHz 10W input/80W output with 9dB preamp	£138.00
2M25-150P	144MHz 25W input/150W output with 9dB preamp	£184.00
2M10-150P	144MHz 10W input/150W output with 9dB preamp	£209.88
2M3-150P	144MHz 3W input/150W output with 9dB preamp	£209.88

G. WHIP Mobile Antennas		
Tribander 10-20 Slide		£24.73
L.F. Coil 40/80/160 MTS		£6.56
L.F. Whip Telescopic		£3.34
Multimobile 10-20 Auto		£28.75
M/Mobile Coil 40/80/160		£6.56
M/Mobile Whip Telescopic		£3.34
Flexiwhip 10M Mast		£17.25
F/Whip Coils 40/80/160		£6.56
Base Standard		£4.49
Base Heavy Duty		£5.75
Extenarod		£11.50

SHURE MICS		
201	Hand ceramic omnidirectional high impedance	£14.49
202	Hand ceramic noise reducing high impedance	£15.18
401A	Hand controlled magnetic high impedance	£16.56
401B	Hand controlled mag. low impedance (200 ohms)	£16.56
444	Desk adjustable height controlled magnetic	£32.43
526T	Desk controlled response transistor preamp	£39.33

DUMMY LOADS		
DL20	30W DC-150MHz with PL259 connector	£6.33
T-80	80W DC-500 MHz with SO239 connector	£22.94
T-150	150W DC-500MHz with SO239 connector	£32.78

STILL HELPING WHERE IT HURTS

Here's a list below to make buying easier for you - Work it out yourself - You'll see - It really is easy!

Product	List Price	Deposit	12 Payments
Yaesu FT 902DM	£799	£312	£40.55
Yaesu FRG 7700/S	£309	£119	£15.89
Yaesu FRG 7700/M	£389	£160	£19.01
Yaesu FT 1012D/FM	£599	£250	£29.05
Yaesu FT 1012D/AM	£585	£225	£30.02
Yaesu FT 1012/FM	£529	£190	£28.27
Yaesu FT 1012/Am	£515	£195	£26.61
Yaesu FL 2100Z	£385	£155	£19.20
Yaesu FT 225RD	£565	£220	£28.76
Yaesu FT 707	£529	£200	£27.49
Yaesu FT 290	£229	£100	£10.82
Standard C78	£219	£99	£10.04
Standard C58	£247	£107	£11.69

Many Other Items Available on Similar Terms
Call for Details

MICROWAVE MODULES		
MMT 432/28S		£149.00
MMR 432/144R		£184.00
MMT 28/144		£199.00
MMT 144/28		£99.00
MMC 28/136		£27.90
MMC 28/156		£27.90
MMC 28/144		£27.90
MMC 144/any IF		£27.90
MMC 144/28LO		£29.90
MMC 70/any IF		£27.90
MMC 432/28S		£34.90
MMC 432/144S		£34.90
MMC 1296/any IF		£32.20
MMC 050/500		£69.00
MMA 28 preamp		£14.95
MMA 144V preamp		£34.90
MMV 1296/28		£32.20
MML 144/100 linamp		£142.60
MML 432/100 linamp		£228.85
MML 144/25 linamp		£59.00
MML 432/50 linamp		£119.00
MM2000		£169.00

UNADILLA/REYCO		
Antenna Traps-		
Precision moulded coil forms stainless - hardware - Aluminium tube irritid finish - Coated aluminium wire. Fully waterproofed.		
Available 7/14/21 MHz		£11.99
W2AU BALUN		
3.5/30 MHz 2.5 Kw with Lighting Arrestor - Suitable Vees, Yagis, Doubles, Quads etc.		£11.99
STANDARD		
C8800 2m, Tcvr		£252.00
C7800 70cms Tcvr		£275.00
DENTRON		
GLA 1000 Linear Amp 10/80 1Kw		£295.00
MLA 2500 Linear Amp 10/160 2Kw		£699.00
MT 3000 3Kw Tuner/SWR/Dummy Load		£275.00

FDK Multi 700EX	£199.00
FDK Multi 750E	£299.00
Send 30p for our bumper bundle literature	
No Quibble Guarantee Same Day Despatch All Items Advertised	

MONITOR RECEIVERS		
SWAN CUBIC		POA
103 due here shortly		
Swan Cubic 1500 Z linear amplifier		POA

USED EQUIPMENT
Over 100 pieces HF/VHF equipment available. Call for details.

ROTATORS		
Skyking SU 4000		£79.00
Emoto 502CXX		£139.75
KR 400		£105.00
AR 40		£59.00
KR 950 2A		£50.00
Rotor Bearing		£12.00

SWR/RF POWER METERS		
SWR 25 3.5/170 MHz		£12.94
LEADER LPM 885-HF 1Kw		£58.00
HANSON 3.5/150MHz 200w		
		£28.75
REECE UHF 74 144/432		£16.28
HANSON FS 500H 1.8/60MHz 2Kw		£67.85
OSKAR SWR 200 3.30 MHz 2Kw		£40.00

Choose your AMTECH here		
Amtech 100 Mobile Match		£16.95
Amtech 200 Random Wire ATU 10-160m 200w pep		£29.95
Amtech 300 Random and Coax Fed ATU 300w pep		£43.95
Amtech CW 250 - The most outstanding CW filter available		£24.90
Amtech Channelguard - A plug in device to eliminate those unwanted stations	Decoder	£15.25
	Sender	£7.25
Amtech FM7: FM Demodulator for FRG 7		£11.90

ANTENNAS		
Wide range in stock including JAYBEAM - HYGAIN - CUSHCART - ASP TELECON - HOKUSHIN etc.		
Bantex 5/8 whip complete antenna		£8.99
Bantex 1/2 whip complete antenna		£3.50

NO POSTAGE REQUIRED

**AMCOMM SERVICES (PW1),
FREEPOST,
HARROW HA2 0BR.**

Please send me.....

at.....enclosed cheque/P.O. for

.....or charge my VISA/ACCESS

Nr.....

Name.....

Address.....

..... Post Code

AMCOMM SERVICES

194 NORTHOLT ROAD, SOUTH HARROW, MIDDX.
Telephone: 01-864 1166, 01-422 9585
Opposite South Harrow Tube Station on Piccadilly Line

Showroom Opening Hours	
Tuesday to Saturday	9-5.30
Sunday	by Appointment

All items over £100
available on easy terms
at List Price



GRUNDIG

Satellit 1400

GENERAL
COVERAGE
RECEIVER

The name of Grundig has long been synonymous with quality in the field of radio, TV and hi-fi, and the Satellit 1400 certainly maintains that reputation. It is a portable receiver for mains/battery operation, about the size and shape of an attache case, complete with a carrying handle on top. There are nine wavebands:

FM87.5–108MHz
LW145–320kHz
MW520–1620kHz
SW1 1.6–3.5MHz
SW2 3.5–7.7MHz
SW3 7.7–12.5MHz
SW4 12.5–18.2MHz
SW5 18.2–23.5MHz
SW6 23.5–28MHz

covering all the long, medium and short wave broadcast bands, plus all the h.f. amateur bands except for 10m. On the review model, the actual limit was 28.075MHz, so you could get some c.w., but it's a pity the whole 10m band couldn't have been squeezed in. The broadcast and amateur bands are all marked on the tuning scale.

Features

On the v.h.f. f.m. band, varicap diode tuning is used, the line-up being: dual-gate MOSFET r.f. amplifier, followed by bipolar mixer, i.f. amplifier with two tuned transformers (10.7MHz), double ceramic filter, i.c. demodulator/a.f.c./inter-station muting. A switching-type converter i.c. generates the 30V tuning supply from the nominal 9V d.c. supply used for the rest of the receiver.

On long and medium waves and SW1, a single superhet with an i.f. of 460kHz is adopted. Ganged capacitor tuning is used, and the line-up is: MOSFET r.f. amplifier, i.c. local oscillator/mixer, ceramic filter, two a.g.c.-controlled i.f. amplifiers with four tuned transformers. For a.m. a conventional diode detector is used, but on s.s.b. a product detector is switched in instead. The b.f.o./c.i.o. is LC controlled, with a small padding inductor for the front-panel clarifier control. The 460kHz i.f. stages can be switched to a manual gain control as an alternative to the a.g.c. mentioned above.

On SW2–SW6, the receiver becomes a double superhet with a first i.f. of 2MHz. The r.f. stage is another dual-gate MOSFET, with separate amplified a.g.c. derived from the tuning meter amplifier. An i.c. local oscillator/mixer of the same type as used to generate the 460kHz i.f. signal, feeds into a chain of four tuned circuits and thence to the SW1 single superhet circuit, which is fixed-tuned at 2MHz.

As well as the 175mm-long tuning scale, a 5-digit frequency read-out using a 12.5mm high liquid crystal display is provided. Like all digital circuitry, the frequency counter is liable to generate r.f. interference, and a switch has been provided to turn it off when not required. Since it consumes quite a lot of power (30mA approximately), this is advisable when operating from the internal batteries. The main dial has a 0–100 logging scale, which seems somewhat pointless when a digital read-out is fitted.


The audio amplifier chain comprises three transistors, followed by the bass and treble tone controls, tone-compensated volume control, and an i.c. power amplifier giving 2W output on battery operation, or 4W on a.c. mains where the i.c. supply voltage is increased. As well as the normal internal loudspeaker, an additional tweeter can be switched in when receiving good-quality f.m. broadcasts. Sockets are also provided for a 4Ω external loudspeaker (2-pin DIN), and headphones ($\frac{1}{4}$ in jack) of 4–2000Ω impedance. Connecting either mutes the internal loudspeaker(s).

Inputs and outputs for connecting a tape recorder or gramophone pick-up, and an output to drive an external audio amplifier, are provided before the tone controls. Both use 5-pin DIN sockets.

The power supply arrangements are very versatile, offering the following options:

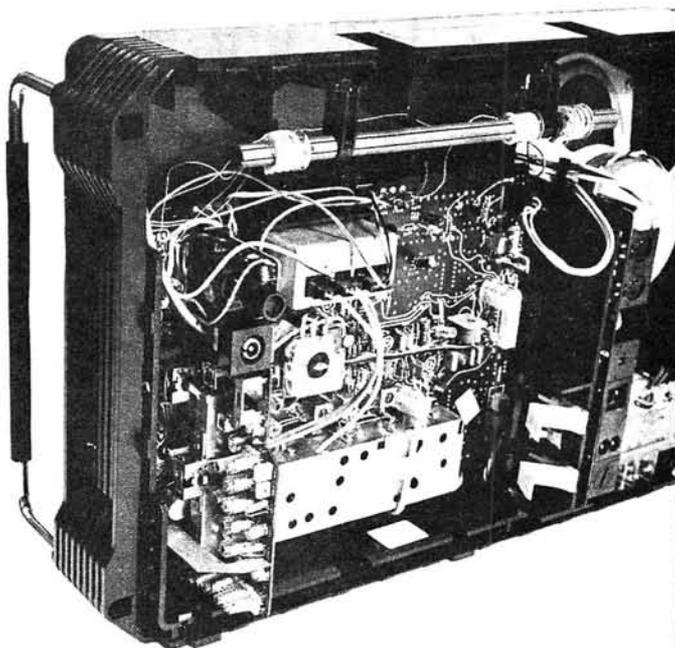
1. Mains operation from 110/127V or 220/240V 50/60Hz supplies, maximum consumption 16VA.
2. External battery operation from 10/16V d.c. supplies (e.g., a 12V car battery).
3. Internal dry batteries (6 off HP2 or equivalent) giving a quoted life of around 86–112 hours, depending on the frequency band in use. (Counter switched off.)
4. Internal rechargeable battery, giving a quoted life of some 32–43 hours (counter switched off), and capable of being charged from the internal power pack when a.c. mains are available, taking approximately 15 hours from a fully discharged state.

When operating on internal batteries, the lamps illuminating the tuning scale, digital frequency read-out and



tuning/battery state meter are normally switched off to conserve power, but can be brought on by pressing a spring-loaded switch.

For long and medium waves, the antenna is an internal ferrite rod, and there is no way of using an external antenna in its place, which is a drawback so far as the m.w. DXer is concerned. For the short waves and v.h.f. band, a telescopic antenna extending to a maximum of 1.44m is provided, but this can be switched off to use an external antenna. A rear-panel trimmer control allows the external antenna tuning to be peaked. Some 20-30dB of attenuation can be inserted into the antenna circuit on short waves by means of the LOCAL/DX switch.

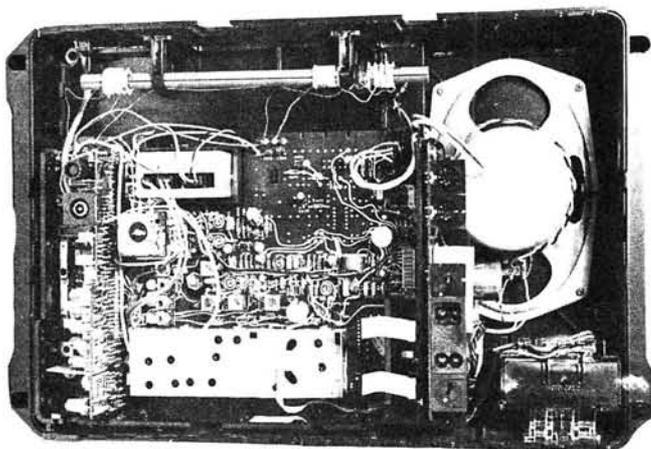

Results

Due to circumstances beyond our control, it was not possible to make any measurements of sensitivity, selectivity, etc., during the trial period, but extensive listening tests were made on all bands.

On v.h.f. f.m., sensitivity and selectivity were very good, and audio quality excellent, fully justifying the use of the tweeter on this band. The a.f.c. circuit is rather imprecise in its action, but the tuning stability without it is quite satisfactory. The tuning scale is marked with channel numbers as well as frequency.

The long and medium waves perform well, with adequate selectivity to separate stations at 9kHz intervals cleanly and

with reasonable quality. A few "birdies" were noted on the long waves during darkness hours, probably due to image interference from strong medium wave broadcast stations.

On the short wave broadcast bands, selectivity is just about optimum for a.m. reception, giving good results on speech and music. For s.s.b. and c.w. on the amateur bands, selectivity does leave something to be desired, inevitably because the i.f. bandwidth is fixed. However, the Satellit 1400 does perform very creditably on these modes, and the sensibly limited range of the clarifier control helps a lot. The main tuning control is a two-speed arrangement, using concentric knobs of approximately 37mm and 43mm diameter. The "fast" control takes eight turns to traverse the tuning scale, and the "slow" one is geared down by about 5.6:1 on that. The tuning rate on the "slow" control varies between about 50kHz and 170kHz per revolution on the various h.f.



amateur bands. There is very slight backlash on the tuning control, normally a thing which annoys me intensely, but this backlash I can only describe as smooth, and not a real problem.

I noticed no spurious signals on the h.f. bands, apart from a strong buzz at 24MHz from the digital frequency counter circuitry. The Operating Instructions booklet warns of possible interference from this source at multiples of 4MHz, but this was the only one which I found.

Accessories supplied with the receiver are a power lead for a.c. mains operation and an envelope of data. Apart from an interesting-looking booklet on DXing and lists of stations, all unfortunately in German only, there is quite a good multi-language Operating Instructions booklet and a complete circuit diagram with d.c. test voltages marked.

The Satellit 1400 measures 267 x 412 x 120mm, and weighs 5.5kg without batteries fitted, and must be worthy of consideration by anyone looking for a receiver for worldwide listening on the broadcast bands. Its performance on the amateur bands is less good, but still acceptable. It is available through Grundig authorised dealers in the UK (see your local *Yellow Pages* under "Television and Radio Shops"), at around £180.00 including VAT.

We are grateful to **Grundig International Ltd., Newlands Park, London SE26 5NQ, telephone 01-659 2468**, for the loan of the review receiver.

G. C. Arnold

MODS

IMPORTANT—The ideas presented here are suggestions only, and as they are untried by this magazine, we cannot accept responsibility for any resultant damage, however caused. Before alterations are attempted, care should be taken to ensure that any guarantee is not invalidated, and it should also be borne in mind that modifications usually have an adverse effect on resale prices. In cases where specialist skills or equipment are needed, most dealers will undertake the work for a reasonable fee.

Roger Hall G8TNT(Sam)

No. 9

Icom IC-2E

In response to the Icom IC-2E semi-reverse repeater mod that I described in Mods No. 7 (June 1981), Andrew G8MLM has written in with an improvement on Thanet's original suggestion that the $\pm 600\text{kHz}$ switch should be modified to give the normal -600kHz shift in one position and semi-reverse in the other, $+600\text{kHz}$ position. Andrew pointed out that although the mod works, the $\pm 600\text{kHz}$ switch is awkward to manipulate. He has suggested substituting a standard Icom volume control for the existing squelch control. This has no effect on the action of the squelch as both controls have the same value, $10\text{k}\Omega$, but, as the volume control has a built in switch that is normally used to activate the tone burst, we now have a spare switch that Andrew suggests can be used instead of the $\pm 600\text{kHz}$ one. Carrying out the mod this way means that you can listen on the input by just pressing the squelch control instead of fiddling around with the $\pm 600\text{kHz}$ switch. Thanks for passing on a nice idea Andrew.


Trio TR-2400

Neil GW6APS wrote to me with a request for a switchable high/low power mod for the Trio TR-2400. Fortunately I subscribe to the Users International Radio Club, an organisation that publishes two newsletters every month, one for Icom users and one for Trio/Kenwood users. These newsletters are always packed with mods and the Trio/Kenwood newsletter for January 1980 contained the one that Neil has asked for. Robert Pohorence N8RT is the publisher and the editor of the newsletters and he has given me permission to reprint his articles and so for Neil, courtesy of the UIRC, here is a mod that was originally supplied by Harrison Clark KA2R. As this mod was first published in America you may find that there are some minor differences between the circuit of your European set and the one described here.

This mod makes use of the fact that if the 10Ω emitter resistor of Q14 is increased in value, then the output power is decreased proportionately. Harrison's suggestion for the switching is to disable the sub-tone switch and then to use it as a high/low power switch but it is also possible to fit an additional s.p.s.t. sub-miniature switch instead.

Remove the covers from the set and then locate the sub-tone switch and cut the wire that is connected to the centre. Tape it up and tuck it out of the way somewhere because it won't be used again. Now install a 15Ω $\frac{1}{4}$ watt resistor from this point on the switch to chassis. Next locate Q14 on the X44-1330-10 board and remove its 10Ω emitter resistor, R55. Replace it with a 33Ω $\frac{1}{4}$ watt one. Finally, connect a wire from the emitter of Q14 to the point on the board marked "SUB".

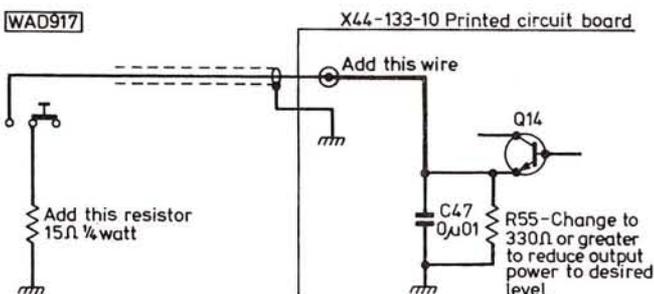Before turning the set on, you should connect one side of an ohmmeter to the chassis and the other side to the emitter of Q14. If, when the sub-tone switch is turned on and off, the meter indicates approximately 10Ω and 33Ω you can then disconnect the meter, re-assemble the set and turn it on.



If you decide that you would like an even lower output, simply increase the value of the Q14 emitter resistor, but keep in mind that the value of the emitter resistor and the sub-tone switch resistor when connected in parallel must equal 10Ω if you want to maintain full output power when the switch is open.

When this mod was originally published in the newsletter it was read by Jon K. Lobe N3BDS, and he wrote a letter that was then published in the March 1981 Trio/Kenwood newsletter. He pointed out that his TR-2400 is slightly different because his R55 is 4.7Ω and not 10Ω as stated in the Trio circuit diagram. He overcame this problem by using a 5.6Ω resistor on the sub-tone switch instead of a 15Ω one. He also noticed that the emitter by-pass capacitor (C47) is different in his set, but as there is no need to change it for this mod, it would appear to be irrelevant.


In his letter Neil also asked if I have details of an external power supply that could be used to run the TR-2400. If you can Neil, try and obtain a November 1980 copy of *PW* because it was in that issue that the first Mods page appeared and one of the first mods that appeared in that issue was for the circuit that you have asked for. If you can't find a copy, the address of our back numbers department is at the front of this magazine and they will be able to let you have one. I should point out that Trio/Kenwood have said, via the pages of the UIRC newsletter, that they do not recommend this mod as it is possible for the set to be seriously damaged in the event of the regulator device becoming short circuited.

Wanted

Brian G4ETN would like any mods for the AR-240. He has heard that it is possible to fit an automatic tone burst, an external microphone and an external power supply and he would like to hear about them, or any other mods that you may know of for this set.

If you can help with any mods, or if you have any mods or requests that you would like published, please write to: R. S. Hall, Practical Wireless, King's Reach Tower (Hatfield House), Stamford Street, London SE1 9LS.

73's
Sam G8TNT

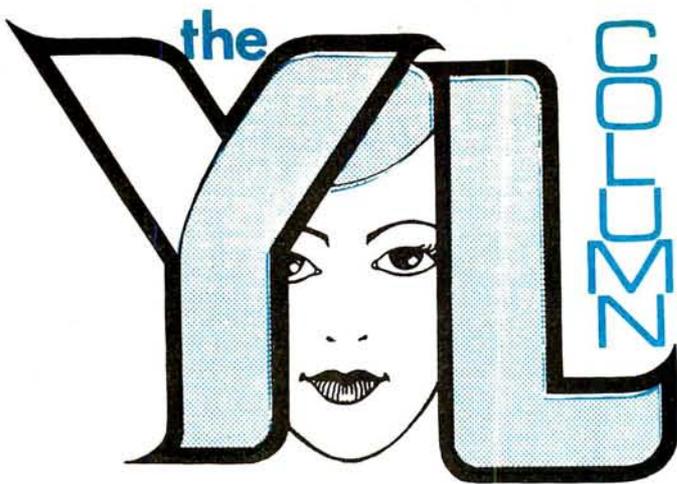

Elaine HOWARD G4LFM

Back again for another month. Firstly, thanks for the letters I've received since I wrote the last YL column, at least I know that I'm not the only one who reads it! I heard from Gloria G8ZYL, Carolyn G4LIL and Mary G8ZUN—all December RAE passes with new callsigns.

Gloria had both a word of praise and a moan for her local amateurs. Firstly the praise—not long after she was first licensed she was taken ill and needed to keep in contact with her husband G8STO who is “on the road” all day long. What better than to use the rig and the local repeater, that was until the batteries in her portable rig faded. She then managed to reach the shack and connect the rig to the power supply. Some of the local amateurs who had heard her on earlier began to get worried when the silence fell, and between them all they managed to keep Gloria in touch with her husband so he knew how she was getting on throughout the day. As Gloria said in her letter, it's good to have the radio if you cannot keep in touch by phone.

Now for the moan—as always, there seem to be a few who want to spoil a good thing for others. Gloria said that some people seem determined to upset the local YL's and other amateurs. “Insulted, run down and generally been harassed” were her words, which they find hardly fair. She finished her letter on a fighting note, “I enjoy my hobby and no-one is going to put me off the air.”

Carolyn and Mary wrote to me just to let me know they have read the column and tell me their callsigns. Both ladies claim to be non-technical but with the RAE behind them they have every reason to be pleased with themselves. Mary said that her fiancé was studying Morse for his Class A licence, but her French degree was taking precedence over her Morse learning.

For the first few weeks after I had my callsign I suffered from lack of sleep like most new amateurs. There always seemed to be people willing to talk to you—whatever the time of day or night. One thing I think I will remember for a long time is my first CQ call on 2m. For the first week or so all I did was reply to other people calling CQ.

I eventually plucked up the courage to call CQ; as soon as I had finished I hoped that no-one would reply because I was sure that I wouldn't have the nerve to carry on a QSO. Then after a few calls when I did get a reply things were very much easier. I'm sure a lot of amateurs soon forget what it was like to be newly licensed, but it does take a great deal of nerve. It was a good thing that I did practice on 2m before I ventured on the h.f. bands because there is a huge difference between operating methods.


I was on the air for seven hours all told one Sunday, it really was as interesting as I had been told it would. I managed to contact two Japanese stations, numerous Russians and many stations in Europe on different bands. It's now a case of waiting until I get the next chance to use the h.f. bands.

The first Italian station I ever worked turned out to be an Englishman who lived half of his time in Italy and the rest in Weymouth (not far from here). Strange what a small world it is. One very interesting contact I did have on 10m was with a YL from Finland called Inga. I was delighted to hear another YL's voice on the air so I waited until she finished her previous QSO and then I called her. She told me that she was quite active on the h.f. bands and enjoyed the hobby a great deal.

Even on 2m I have had some excitement: there I was happily scanning the band when the scanning stopped on S20, a station was calling for help. In the dark and dusty corners of my memory stirred the recollection of how to handle an emergency. It was a long time ago—but there are some things you never quite forget. The problem seemed to be that a car was on fire on one of the local dual-carriageways; being a base station with a land line it was obvious I could do something. All the others who could hear what was happening got things right too, so between us all the Fire Brigade was called and the excitement was over.

Oh, yes, before we go any further, I know you can't use the *PW* Exe for cooking, but what's the first thing you think of when the word “microwaves” is used? Mind you, think how useful the project could be if it had a dual function, communications and cooking!

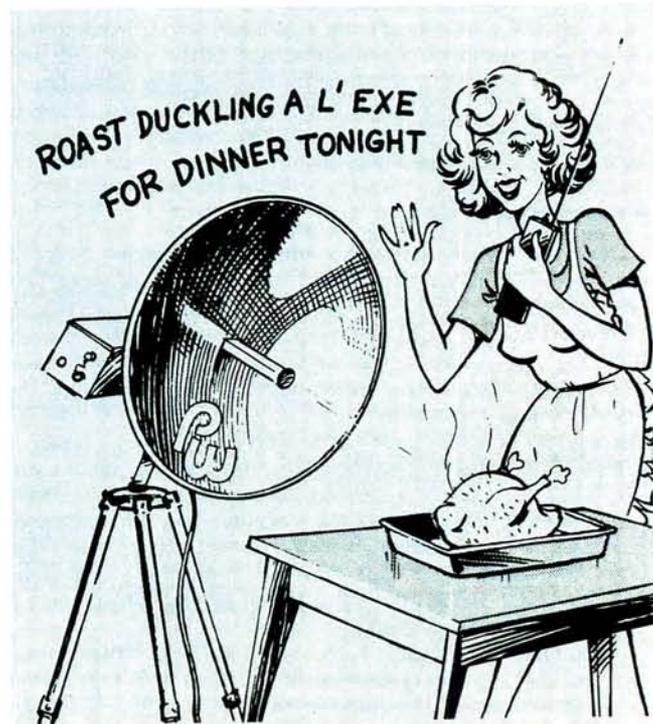I'm now set up with a lovely little base station (well, I think so), my IC2E serves as a base station, mobile station and a portable rig. With the aid of a power supply, regulator battery pack and a Slim Jim it has done very



continued on page 57▶▶▶

WATERS & STANTON ELECTRONICS

18/20 MAIN ROAD, HOCKLEY, ESSEX. TEL (0702) 206835

4,000 SQ FT DEVOTED TO RADIO COMMUNICATION

24 HOUR TURN ROUND ON ALL ORDERS!

"SUCH NICE PEOPLE"

5 miles from Southend-on-Sea
Why not bring the whole family for a day out?



PS134 4 AMP 13.8v POWER SUPPLY, STABILISED & SHORT CIRCUIT PROOF
£24.95 plus £1.50 p&p

This is the power supply that we've been advertising and selling for several months. It really is a robust little unit with a transformer 50% larger than its competitors. Some cheap power supplies get hot, hum and even go bang! This one stays silent and keeps on working. It is fully protected against short circuit and overload and is capable of delivering 4 amps continually at 13.8v DC. Ideal for transceivers.

PROFESSIONAL AIRCRAFT MONITOR R517 £49.50

(as supplied to pilots, ground crew etc.)



The R517 is a professional aircraft monitor receiver, having superb sensitivity and capable of tuning across the entire aircraft band 118-143MHz. For easy tuning there is both a coarse and fine tuning control. In addition there is a 3 position switch for selecting xtal controlled channels (xtals £3.00 extra) for your local airport. The unit is completely portable running off self-contained batteries.

AR22 VHF FM MONITOR
AMATEUR MODEL £83 inc. VAT
MARINE BAND £89 inc. VAT



Truly amazing! The AR22 tunes across the 2 metre FM band 142-148MHz (also includes Police and Fire Brigade) in 5kHz steps. So small it will fit into a shirt pocket and yet nothing is sacrificed in terms of performance. Price includes rechargeable batteries, mains charger, fly aerial etc. You won't find a smaller monitor anywhere.



TRIO R1000
COMMUNICATIONS RECEIVER
OUR PRICE £305 (Free Securicor Delivery)

The R1000 has really caused a stir in the receiver market! Its performance matches professional receivers costing many times more and with our new competitive price of £305 it must be the best value on the market today. Full digital readout from 200kHz (actually it operates right down to 20kHz but with reduced sensitivity) means accurate tuning and the 30 position band selector switch means really good bandspread for easy operation. Other features include noise blanker (a really good one!) built-in speaker, digital clock/timer and both 230v AC/12v DC operation. (Yes we include the 12v DC kit free!) Each model is fully checked and delivered anywhere in the U.K. within 24 hours of receipt of payment!

28MHz FM!

NEW AZDEN PCS2800 27MHz model also available



£179 inc. VAT

The World famous Azden range of transceivers is now being imported by us. Here you see the 28MHz FM model as used by Practical Wireless in their recent CB tests. We can offer you a 27MHz version at the same price which includes the new UK channels. Digital readout, scanning, remote control etc. Send S.A.E. for details.



SWR/POWER/FIELD STRENGTH MEASURING METER
SPECIAL OFFER

£11.95 + 60p p&p

As used by CB and Amateur radio operators.

The YW3 is used by amateur radio and CB operators around the World. It's offered to you at a really low price because we import them direct from Japan. It tells you the VSWR, power output and field strength and covers 3.5 to 150MHz. If you want the strongest signal in town - you'll find the YW3 the sure answer.

NO MORE TV INTERFERENCE FROM CB OR AMATEUR!
GLOBAL

HP4A £5.95

Post free.

If you're suffering T.V. interference, here's a brand new device specially designed and made for us in Japan. The HP4A now offers about 100% cure against TV interference because of its advanced design, yet it has no effect on the picture. Be prepared, keep one handy!



AZDEN 2M TRANSCEIVER
UNBEATABLE PRICE £219

SUPER DEAL



25 watts!

- * 144-146MHz FM
- * Digital Readout 25kHz or 12½kHz
- * 8 memories (programmable)
- * Programmable scanning
- * Remote mic control
- * Detachable control head
- * Complete with all accessories

IMPORTED DIRECT BY US
12 MONTHS WARRANTY

SHORTWAVE LISTENER ATU



GLOBAL AT1000
£31.95
carriage free

The ultimate in ATU's, specially designed to enhance the performance of all short wave receivers - no other model can approach its performance.

- NEW PRODUCTS ALWAYS ARRIVING
- HUGE STOCKS HELD
- IN STORE SERVICING
- INSTANT CREDIT
- NEW ITEMS:-

TS830, TS530, TR8400, TR9500
FT290, FT209, FT708 etc.

TELEPHONE FOR LATEST PRICES
14p STAMP FOR FULL CATALOGUE

STOP PRESS:- SEND 14p STAMP FOR NEW 1981 CATALOGUE ON RADIO COMMUNICATIONS

MAIL ORDER SLIP to: Waters & Stanton Electronics, Warren House, Main Road, Hockley, Essex.


Name..... Goods required

Address.....

.....

.....

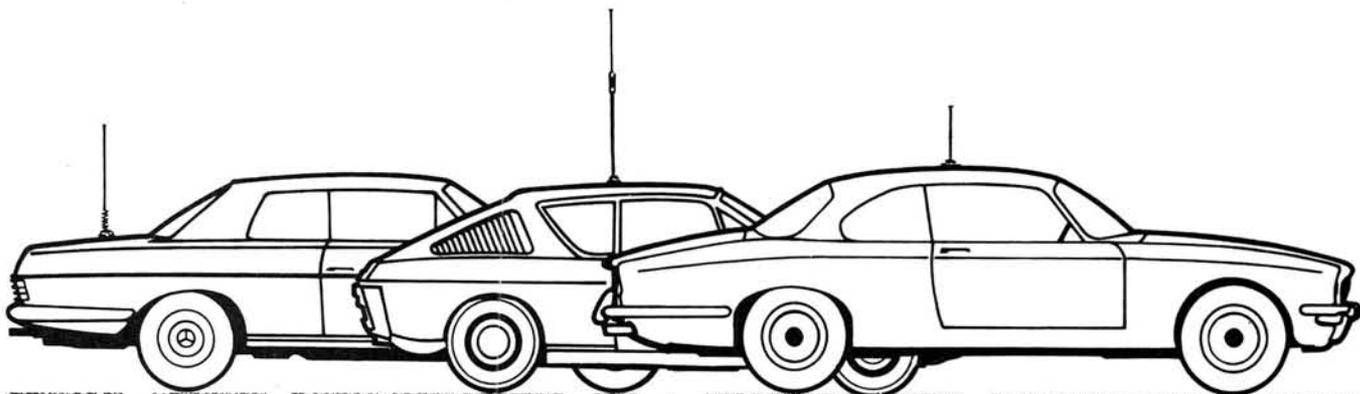Please rush me the above. Cheque enclosed for £...../Please charge to credit card No.....



v.h.f. mobile antennas

D.O.White G3ZPA

Whether you are a licensed radio amateur, short wave listener or just interested in the v.h.f. bands in general, if you wish to participate from your motor vehicle this article on mobile antennas will be of interest.

Ground-plane

You may have encountered the term 'ground-plane' antenna and in the mobile context any of these antennas will become ground-plane types when mounted over the large metallic plane of the vehicle roof.

quired operating frequency using the practical formula:—

$$70358 \div \text{frequency (MHz)} = \text{length (mm)}$$

At a frequency of 145.000MHz this will result in an element length of 485mm at resonance.

As previously noted the impedance when mounted on a good metallic ground-plane will be 40 ohms. By way

Polarisation

The majority of v.h.f. and u.h.f. radio signals emanating from public authority and radio amateur antennas utilise vertical polarisation. In other words the electrical part of the radiated field is emitted vertically whilst the magnetic component is radiated horizontally, perpendicular to the electric field.

The principal reasons for selecting vertical rather than horizontal polarisation are as follows:

1. It makes for simple unobtrusive antennas with an associated ease of mounting to the vehicle.
2. Simple single element antennas will give an omni-directional, all round, coverage yielding equal strength signals independent of the direction that the vehicle is pointing.
3. Vertical polarisation has been widely accepted as the standard for mobile working throughout the country.

Types of Vertical Mobile Antennas

The main types of vertical mobile antennas fitted to vehicles today can be summarised as follows:—

Quarter wave	($\lambda/4$)
Half wave	($\lambda/2$)
Five eighths wave	($5/8\lambda$)
Seven eighths wave	($7/8\lambda$)

Quarter Wave Antenna

This is the simplest, cheapest and most common of all the mobile antennas in use, particularly favoured by the various public authorities.


The $\lambda/4$ antenna will radiate an omni-directional signal, of even strength, when placed in the centre of the roof of a motor vehicle. If mounted on the gutter or the wing of a car the radiation pattern will become distorted with the maximum radiation usually towards the main body of metal of the vehicle.

The impedance of a $\lambda/4$ ground-plane whip antenna can be shown to be approximately 40 ohms. When mounted on a roof rack or gutter the impedance becomes difficult to determine because of the uneven ground system.

Coaxial feeder cables suitable for connecting this form of antenna to its associated transmitter or receiver usually have a characteristic impedance of 50 or 75 ohms. In this case 50 ohm cable would be the best for matching purposes.

On a voltage standing wave ratio (v.s.w.r.) meter the indicated mismatch should be approximately 1.5:1, which is slight.

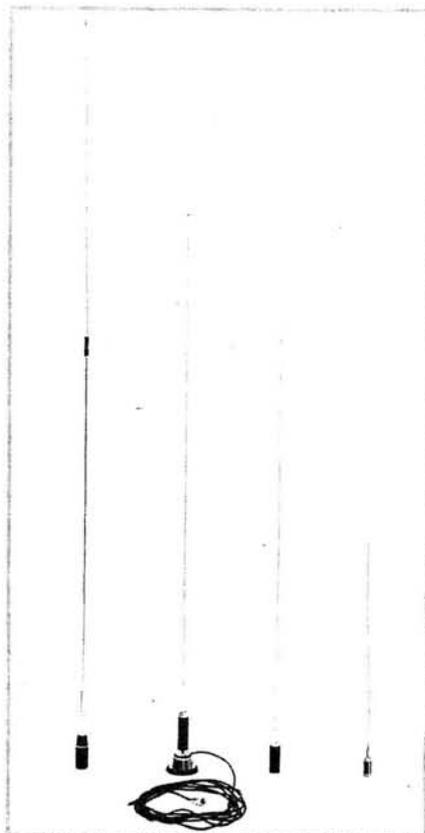
The following example demonstrates the method used to obtain the physical length of the $\lambda/4$ antenna at the re-




A selection of widely used mobile antennas

WRM400

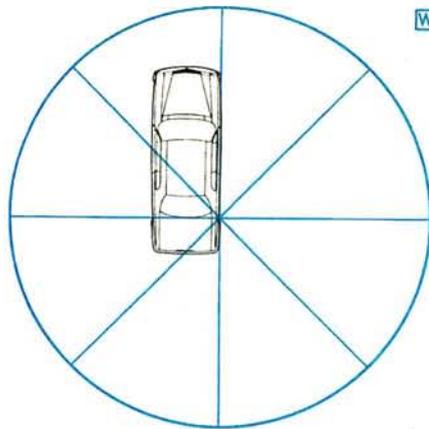
◀ Radiation pattern plots of popular mobile antennas



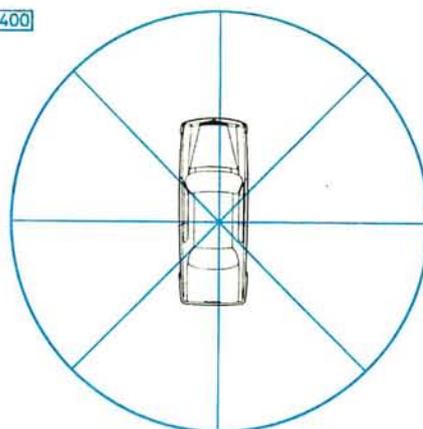
$\lambda/4$ antenna mounted on the rear wing



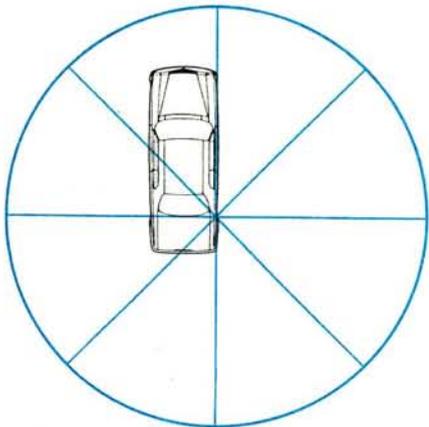
$\lambda/4$ antenna mounted centrally on the roof



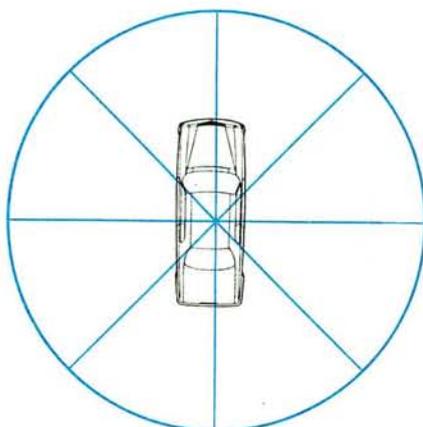
$5/8\lambda$ antenna mounted on the rear wing



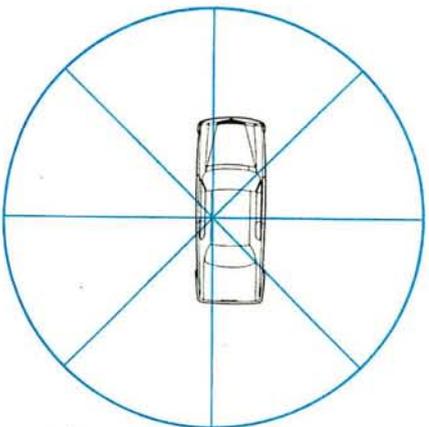$5/8\lambda$ antenna mounted centrally on the roof




$\lambda/4$ antenna gutter mounted

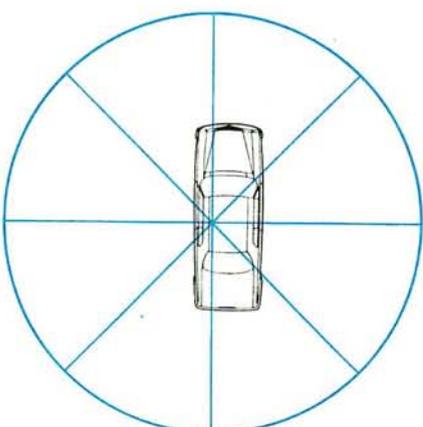

$5/8\lambda$ antenna gutter mounted

WRM401

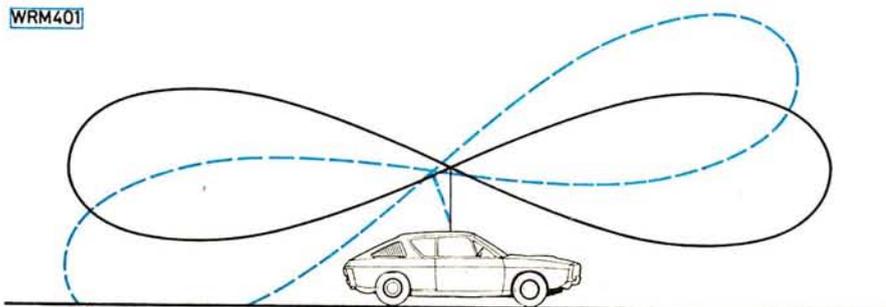

◀ Fig. 1: $5/8\lambda$ antenna radiation pattern—solid line vehicle stationary—dotted line vehicle on the move

of experiment, if the length of the $\lambda/4$ element is extended the indicated v.s.w.r. can be made to fall towards 1:1, a very good match. Unfortunately, the antenna will no longer be resonant at the required operating frequency but at some lower frequency determined by its new overall length. The base impedance will however be nearer to 50 ohms but possessing a small amount of inductive reactance.

Antenna Matching

A classic system used for matching the impedance at resonance uses the transmission line transformer technique shown in Fig. 3. With the frequency used in our example calculation, 318mm of 50 ohm coaxial cable connected between the $\lambda/4$ antenna and a 75 ohm feeder will allow an ideal match.

Five Eighths Wave Antenna

There is a relationship between the gain of an antenna and its directivity; any achievement of gain in a particular direction is always accompanied by a loss in another.


When a claim is made of gain in a vertical antenna, what is actually meant is that less radiation occurs in a skyward direction and more radiation is transmitted in a horizontal direction.

The angle made between the centre maximum of the radiated wave and ground is known as the radiation angle; the lower the angle the further the signal will go before it becomes too weak to be heard.


The $5/8\lambda$ antenna was derived for this very purpose; by increasing the length of the antenna the high current portion is elevated much further up the element resulting in a lower radiation angle towards the horizon.

From the radiation angle plots it can be seen that the $\lambda/4$ antenna radiates at approximately 44° whilst the $5/8\lambda$ radiates at only 30° . The resultant concentration of energy, nearer to the ground, produces an apparent gain of 3dB over the $\lambda/4$ antenna system.

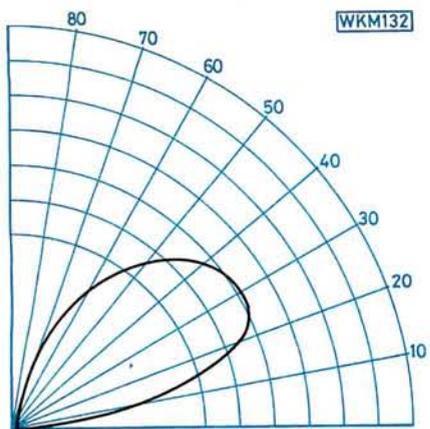
In general the greater the length of a vertical antenna, compared to a $\lambda/4$,



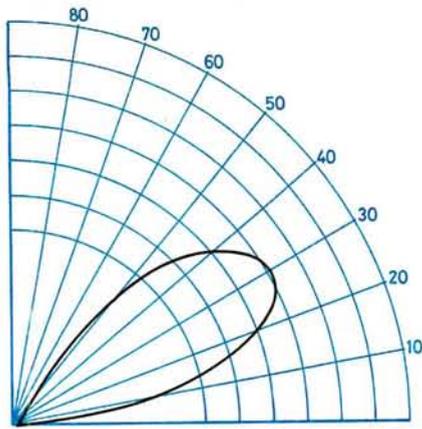
$\lambda/4$ antenna, gain 0dB radiation angle 44°



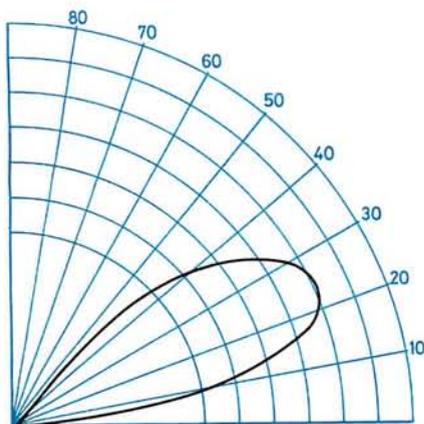
$\lambda/2$ antenna, gain 2dB radiation angle 35°



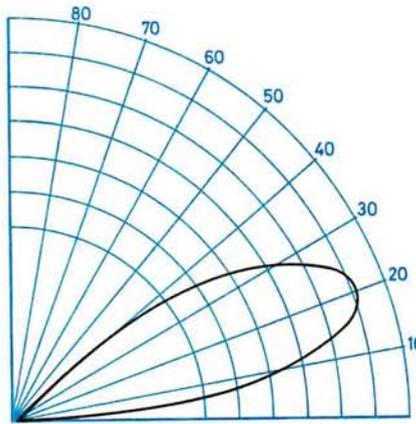$5/8\lambda$ antenna, gain 3dB radiation angle 30°



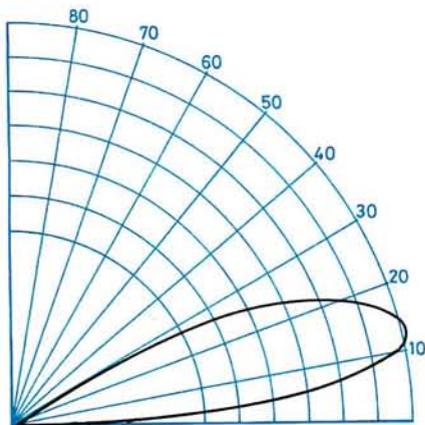$7/8\lambda$ antenna, gain 4dB radiation angle 25°



PW Slim Jim, gain 5.5dB radiation angle 15°

the lower the angle of radiation will become. This applies equally for reception, allowing the $5/8\lambda$ to receive low angle signals better than high angle ones.

One other important factor influences reception and this is termed the capture area of the antenna. A $\lambda/4$ vertical antenna at 70MHz will perform

far better than a vertical $\lambda/4$ at 430MHz because, due to its greater length it is able to intercept more of the wanted signal. It is not possible to connect a coaxial feeder directly to a $5/8\lambda$ antenna due to the high impedance mismatch. What is required is a means of tricking the r.f. energy into thinking that it is feeding into a $3/4\lambda$ antenna, as this is the nearest length likely to allow a match.

To achieve this matching condition it is necessary to insert an additional $\lambda/8$ into the base of the $5/8\lambda$ element. By winding the additional material into a coil form the overall physical length is kept at approximately $5/8\lambda$ but the all important electrical length becomes $3/4\lambda$ with a corresponding reduced base impedance of 68 ohms and a close match to 75 ohm feeder. A typical v.s.w.r. reading for 75 ohm systems would be 1.2:1 and with a 50 ohm feeder 1.4:1.

At our example frequency of 145.000MHz the $5/8\lambda$ antenna would have a length of 1245mm from its tip to the top of the $\lambda/8$ coil section. As supplied most commercial antennas of this type are produced overlength to

◀ Fig. 2: Radiation angle plots—gain figures are referenced to the test $\lambda/4$ antenna mounted on the vehicle

allow the user to trim for lowest indicated v.s.w.r. A disadvantage of the $5/8\lambda$ and other extended vertical antennas is that they will bend over towards the rear of the vehicle when travelling at speed. This effect distorts the normal radiation pattern, as illustrated in Fig. 3, and reduces the effectiveness of the antenna. At slow speeds the antenna can swing about its base mount giving rise to rapid signal fluctuations known as 'flutter', again caused by the continual change of radiation angle.

Flutter effects can also be observed when the vehicle is passing through built-up, wooded or hilly areas. In this case the flutter is created by multi-path propagation of the signal resulting from reflection from the various obstructions within the direct signal path. The minute time delays caused by the variations in path length produce signal phase changes at the receiver input with a corresponding change in signal strength.

Apart from the audible variations in signal strength a good illustration of flutter effect can be obtained by observing the "S" meter. Results are more pronounced with f.m. systems when operated under low level signal conditions due to the so called threshold effect, where a small increase in signal strength will produce a substantial increase in signal to noise ratio.

Antenna Comparisons

Four different types of antenna, suitable for mobile operation, have been evaluated by the author and the following conclusions are the result of these lengthy tests. All gain figures quoted are referenced to the value from the $\lambda/4$ antenna.

1. The $\lambda/4$ antenna was found to be the most consistent for mobile use, being the least prone to flutter fade, although its overall gain was low.
2. The $5/8\lambda$ gave an increase in gain but, due to the bending effect whilst on the move, inconsistent results must be expected. The radiation pattern was found to be somewhat distorted when mounted in any position other than the centre of the roof but in all positions produced superior performance to the $\lambda/4$. This is probably due to the fact that

THE CRAZIEST EVER RADIO SET

▶▶▶ continued from page 23

jerked the lever up and down and this drew zigzags on the smoked paper in time with the impulses from FL. (Don't keep saying that!) The world's first Frog's Leg Radio was a success! And Dr Lefeuve's gold half-hunter was a minute and a quarter slow.

That, in brief, is the true story of the craziest radio of all time. Why didn't it catch on? Because it suffered from a serious defect: rigor mortis. After only a few hours' use the frog would no longer operate, and the bother of frequently plugging-in a replacement amphibian killed the FLR dead—like the frog. So the thermionic valve triumphed, and men came to boast of their "six-valve superhet" instead of their "six-frog superhet". Maybe Galvani wasn't so dumb after all.

There's a postscript to this amazing history. Some years ago, the writer had a yen to build a working replica of Dr Lefeuve's hook-up. Not having a frog, he downgraded the project to a static model fitted with an ersatz croaker moulded in green Plasticine. Since his infant daughter had only orange Plasticine, and the frog she moulded was a dead ringer for a hippopotamus, the scheme was abandoned altogether.

Yet it lurks in the background. Frogs are out, I can't catch one. But the cabbage patch is teeming with fauna ranging from wireworms to next-door's tomcat. Somewhere in there must be a suitable substitute.

Is mankind ready for the world's first Blackbeetle Radio? ●

THE YL COLUMN

▶▶▶ continued from page 52

well. The antenna is propped up in the window sill as it is impossible to have an outside antenna at the moment. That is far more convenient than when I was using the NiCads and the helical whip antenna that comes with the rig. To use our local repeater I had to find a position in the room that I could access it and then stay there! If I so much as moved, then my transmission would drop out of the repeater, which was not very easy as the only place I seemed to be able to stand was very precarious to say the least. It tended to be rather doubtful balancing positions on chairs and the end of the bed, which risked life and limb. Things have become far less dangerous now and it makes talking to people so much easier, but doesn't provide others with quite so many laughs at my expense.

I find it very useful to have a rig that just fits into a handbag (or pocket); it can then travel everywhere with me. Seeing that I do quite a lot of travelling I get lots of chances to operate in many different locations. Mind you, when you are out and using the rig portable you collect plenty of funny looks and whispered comments. People in the street don't quite know what to make of the sight of you strolling down the main road deep in conversation with a small plastic box!

That's all the space used up for this month, I would still like to hear from any other YL's: let me know if you have something you want to say. So, 33's until I write next time.

the high current part of the antenna is located well above the metallic bodywork. The $\lambda/4$ performed extremely badly when placed anywhere on the vehicle other than the centre of the roof.

3. The $\lambda/2$ antenna gave 1dB less gain than the $5/8\lambda$ but otherwise appeared to behave exactly as the former.
4. The $7/8\lambda$ antenna gave a gain of approximately 4dB compared to the

$\lambda/4$ and was the best of the four antennas tested in terms of relative gain. Unfortunately the $7/8\lambda$ also suffered from the effects of bending and its 1740mm length did result in several collisions with overhead obstructions!

A cure may be effected by using nylon monofilament fishing line, but subsequent removal operations take longer.

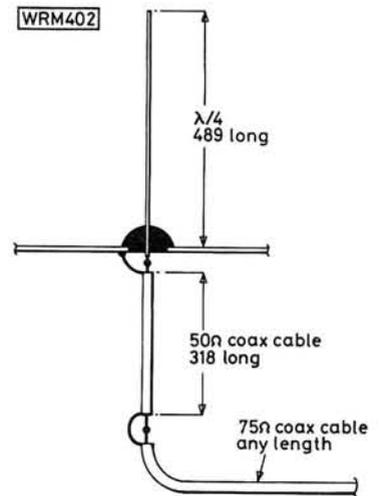


Fig. 3: Coaxial matching transformer system ▶

PW Slim Jim mobile antenna ▼



Mobile Slim Jim

One further antenna was tested out to see how it would perform under mobile conditions and consisted of an 'ordinary' Slim Jim, constructed from aluminium tube. This reasonably rigid device was mounted on a short length of wooden broom stick and supported from the roof rack. The results obtained were quite astonishing and a gain figure of 5.5dB was recorded, with no signs of flutter fade. If a suitable means could be devised to overcome low-flying obstacles this format would be a winner. ●

AMATEUR RADIO EXCHANGE



A SPECIAL ANNOUNCEMENT THIS MONTH FOR OUR FRIENDS AND CUSTOMERS IN THE NORTH WEST.

Our first branch outside London is about to open in St. Helens under the management of that well-known technical wizard Mike, G8EWU. As you would expect, he will be stocking a good, representative range of rigs by YAESU, ICOM and TRIO/KENWOOD plus a wide selection of accessories.

We promise you will be made as welcome at 136 Gladstone Street, St. Helens (near the Rugby ground) as you always have been at Ealing. The only thing missing will be Brenda's coffee!


FT-707

The ultimate in HF mobile transceivers from Yaesu. All the new bands, and all the latest technology. **PHONE FOR PRICE INCLUDING FREE MIC.**



FT-101 Mk III

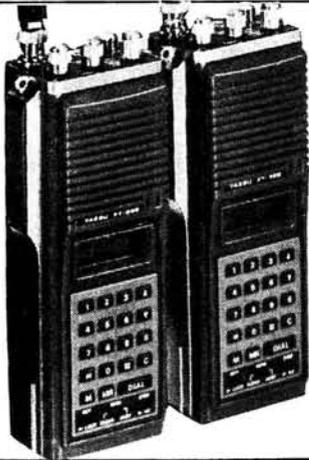The tried and tested Yaesu HF base station, now with audio peak filter and reject notch filter as standard and choice of AM or FM. **PHONE FOR PRICES INCLUDING FREE COOLING FAN AND MIC.**



FT-208/FT-708

Yaesu's marvellous new hand-held for either 2m or 70cm operation. Its LCD display (with night lamp feature) is coupled to a 4-bit microprocessor giving 10 memories, up/down scanning in 25 or 50kc steps (manual or auto) plus memory scan and scanning between two desired frequencies, priority channel with search-back, keyboard entry allowing split frequency for non-standard repeaters ... and lots more. **PHONE FOR PRICES**

TRIO/KENWOOD - LATEST MODEL IMPROVEMENTS

Three best-sellers in the range up-rated with new model designations. The TS-520 and TS-820 become the TS-530S and TS-830S respectively, both with all the new bands, IF shift etc ... and the TR-7800 becomes the TR-7850, now giving 40W out.



PHONE FOR PRICES



YAESU's LATEST ... the new all-mode 2m portable FT-290R

So many features *10 memories *Memory scan *2 VFOs *Band scan *Clarifier *FM/LSB/USB/CW *LCD readout *Real S-meter *Priority channel *2.5W out **PHONE FOR PRICE**



FRG-7700

Yaesu's latest receiver with FM right across the band now offers all these optional extras *Memory facility *FRT-7700 Aerial Tuning Unit at only **£34.75** *Four VHF converters running from 50MHz up to 170MHz. **BASIC RECEIVER £299 inc. VAT and FREE HELISCAN AERIAL**

	Converter specifications * Phone for Prices		
FRV-7700A	118-130MHz	130-140MHz	140-150MHz
FRV-7700B	118-140MHz	140-150MHz	50-60MHz
FRV-7700C	140-150MHz	150-160MHz	160-170MHz
FRV-7700D	118-130MHz	140-150MHz	70-80MHz

LICENSED CREDIT BROKERS. *Ask for written quotation. INSTANT HP AND 6 MONTHS NO INTEREST HP TERMS AVAILABLE FOR LICENSED AMATEURS AND BANK/CREDIT CARD HOLDERS.



Credit Card Sales by telephone

Prices are correct as we go to press, but owing to currency fluctuations etc may vary by publication date. Please phone for latest information. All prices include VAT, but p & p/carriage are extra.

**Closed Wednesday, but use our 24-hour AnsaFone service
2 NORTHFIELD ROAD, EALING, LONDON, W13 9SY. TEL: 01-579 5311**

So easy for Overseas visitors - Northfields is just seven stops from Heathrow on the Piccadilly Line.

PRODUCTION LINES

ALAN MARTIN G8ZPW

Enclosures

Eldon Electric Ltd. stock an enormous range of enclosures from floor-standing cabinets to miniature die-cast aluminium boxes and are prepared to supply their products to the general public on a one-off basis.


Our photograph shows three examples of their "Compact" series of enclosures supplied in three different materials.

There is a choice of 76 separate sized cases which range from 50 x 45 x 30mm to 600 x 310 x 110mm and are manufactured in die-cast aluminium, polycarbonate and ABS. All the enclosures have recessed sealing gaskets in the cover which affords protection to IP65.

In the aluminium range the covers are secured by captive stainless steel screws. Covers for both the polycarbonate and ABS enclosures are retained by "quick release" stainless steel fasteners and can also be supplied with optional transparent covers for a small extra charge. Mounting plates and external mounting brackets are available for any of the enclosures.


As an example of prices across the three ranges, the CM160 (die-cast aluminium) measures 125 x 80 x 54mm and costs £6.00, the CK621 (polycarbonate) measures 160 x 80 x 55mm and costs £4.40 and the CK622 (ABS) measures 160 x 80 x 55mm and costs £3.50. Prices quoted include carriage but 15% VAT must be added.

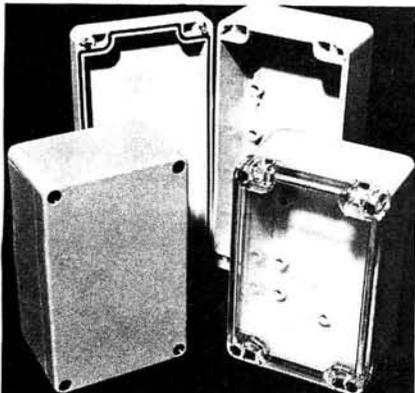A catalogue covering the "Compact" series (OB80) is available along with information and prices on the whole of their product range from: *Eldon Electric Ltd., Lovett Road, Staines TW18 3AH. Tel: (0784) 61851.*



New Soldering Irons

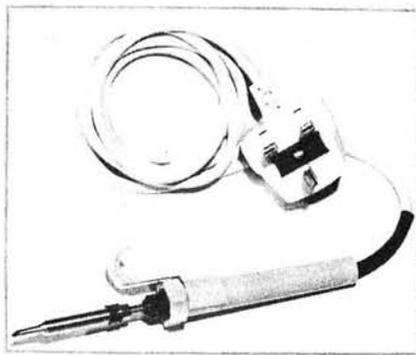Antex (Electronics) Ltd., of Plymouth, Devon, has introduced a new "Ready to go" range of soldering irons for industrial and domestic use. The CS and XS miniature irons are fitted with a fused, moulded 3-pin mains plug and 0.75mm² cable. The anti-roll handle and the new first finger guide/protector are made from extra tough engineering plastic.



With a power consumption of 17W, the CS model produces a maximum tip temperature of 420°C. The larger 25W model produces up to 400°C with much greater thermal capacity for use as a general purpose soldering iron.

On sale at a recommended selling price of £5.30 plus VAT, the CS and XS soldering irons are available from electrical suppliers, hardware and chain stores.

Antex (Electronics) Ltd., Mayflower House, Plymouth, Devon. Tel: (0752) 67377/67378.

Low-cost d.f.c. Kit

Timestep Electronics Ltd. can supply a low-cost digital frequency counter kit called the DFC-4.

The DFC-4 will provide direct frequency readout to at least 150MHz, and the in-built ROM circuitry provides automatic offset for both 10.7MHz (f.m.) and 470kHz (a.m.) operation; both these offsets can be reprogrammed if required. Although primarily designed for l.w., m.w. and f.m. operation, it can also function as a direct frequency counter.

Connection to most receivers is simple and readout is via a flicker-free fluorescent display which also indicates a.m., f.m., kHz and MHz. With sensitivity of 1mV a.m. and 10mV f.m., the counter is powered from its own fully isolated mains power supply unit.

Timestep offer the DFC-4 in two kit forms, the complete kit costs £12.50 and a cost-saving kit, which omits the commonly available resistors and capacitors, costs £10.50, both prices include VAT, but £1.50 p&p must be added.

Both kits for the DFC-4 or further details (please send s.a.e. for details) are available from: *Timestep Electronics Ltd., 48 Egremont Street, Glemsford, Sudbury, Suffolk. Tel: (0787) 280154.*

The Shape of Things to Come

Fidelity Radio Ltd. has just issued a photograph of their starter unit for the 27MHz f.m. Citizens Band radio service, which the Government plans to introduce in the autumn.

The basic unit, the CB-1000 FM, is expected to retail at around £60, with a more sophisticated version selling at approximately £80.

Fidelity Radio Ltd., Victoria Road, London NW10.



We're giving away this soldering iron worth over £10.



Choose any of 10 selected kits from the Heathkit catalogue as your first order, and we'll give you a superb soldering iron worth over £10. Plus a 10% discount!

These kits have been specially designed with first-time kit builders in mind. So even if you've never built an electronic kit before you won't find it difficult. In fact, the simple to follow step-by-step instructions make it easy to build any Heathkit kit.

And with your special offer discount you can afford to see just how easy it is.

Full details of this FREE offer are available in the Heathkit 48 page catalogue. So send the coupon for your copy now.

To: Heath Electronics (UK) Limited, Dept. PW9, Bristol Road, Gloucester, GL2 6EE.

Please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name _____

Address _____

NB: If you are already on the Heathkit mailing list you will automatically receive a copy of the latest Heathkit catalogue without having to use this coupon.




HEATHKIT

HEATH ZENITH



VHF WAVEMETER

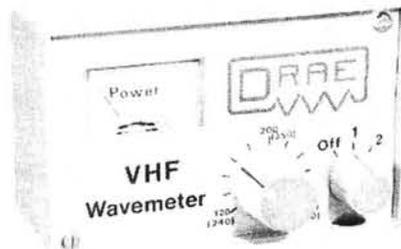

Covers 135-450MHz. With Varicap Tuning in two overlapping ranges. Designed to fulfill the home office requirements for 2 metre operation.

£24.95 Inc. VAT and carriage

FULLY PROTECTED 13.5 volt TRANSCEIVER POWER SUPPLIES

4 Amp £27.95 - £1.00 Carr.
6 Amp £44.95 - £2.00 Carr.
12 Amp £69.00 - £2.00 Carr.
24 Amp £99.00 - £3.00 Carr.

DAVTREND LIMITED
89, Kimbolton Road,
Portsmouth, Hants.
Ports (0705) 816237

Access Cards Accepted
All Prices Include VAT.
MANUFACTURED IN UK.

"Rubber Duck to Logi Baird, say good buddy, where do I get transistors and I.C's for C.B. and R.F. applications?"

"ANGLIA of course!! they are the UK's leading supplier of Motorola & Japanese types"

ANGLIA COMPONENTS
BURDETT ROAD, WISBECH
CAMBS PE13 2PS
Tel: 0945 63281
TELEX 32630

ROBOT '400' SSTV



State of the art, full brightness, non fading pictures on a normal TV monitor. Full sound/receive facilities & easy to operate. Send 14p stamp for details & special prices of new & s/hand SSTV gear.

There are approx 14000 SSTV stations transmitting from 130 countries.

AERO & GENERAL SUPPLIES (SSTV)

Building 33, East Midlands Airport,
Castle Donington, Derby DE7 2SA.
Tel: (0332) 812446. Telex: 37522.

PRODUCTION LINES

PCB Designing Aid


UNO Sales, the Croydon based manufacturer and distributor of drawing office products, have introduced a range of templates specifically designed to meet the requirements of designers and illustrators.

Part of the range consists of a series devoted to the electronics and electrical industry. One in particular, the DT609 p.c.b. layout template, should be very useful to the constructor who wishes to design his own p.c.b.s.

The DT609 template cutouts are twice full size and include pad spacings patterns for capacitors, resistors, transistors, i.c.s and edge connectors.

Technical templates are available from good drawing office suppliers and cost approximately £6.45.

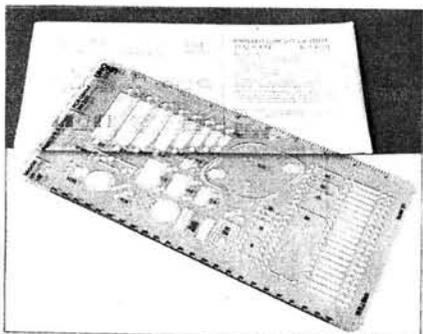UNO Sales, A. West & Partners Ltd., 684 Mitcham Road, Croydon CR9 3AB. Tel: 01-684 6171.



Latest from Trio

The very latest from Trio is the TR-7730, a really compact 2m f.m. mobile transceiver which measures only 147.5 x 51.5 x 198mm.

Possessing plenty of convenient operating features, such as five memories, memory scan, automatic band scan, Up/Down manual scan and the r.f. output power can be switched

from 25W to 2W.

The TR-7730 should be available in the UK by the time this issue of *Practical Wireless* is published (early August), but for confirmation of availability and further details contact: *Lowe Electronics Ltd., Bentley Bridge, Chesterfield Road, Matlock, Derbyshire DE4 5LE. Tel: (0629) 2817.*

Signal Generator

Sinclair Electronics Ltd. has recently introduced the LSG-16, a wideband mains operated signal generator with a frequency range of 100kHz to 100MHz (300MHz on harmonics) over six positions. It can be modulated internally at 1kHz or between 50Hz and 20kHz from an external source. Crystal oscillator facility is also provided for 1MHz to 15MHz.

The LSG-16 is housed in an attractive professional case and competitively priced at £55.00 plus VAT.

Further details can be obtained from:



Sinclair Electronics Ltd., London Road, St Ives, Huntingdon, Cambs. Tel: (0480) 64646.



Two New Rigs from Icom

Icom has recently announced the introduction of two new rigs. First, the IC-25E, a very compact 2m f.m. mobile transceiver that features 25W output, five memories, 1kHz or 25kHz v.f.o. steps, programmable priority channel, automatic repeater selection with alternative frequency splits available, full reverse repeater at the touch of a button and two scanning modes (all the band or just the memories) which

The photograph shows left the IC-25E and right the IC290-E

can be instigated from the front of the rig or from the microphone. There are also several controls under the top plate that can be used to adjust the length of time the scanner spends on each channel and the speed at which it scans. The large digital display is extremely bright and should remain visible even in bright daylight, as should the i.e.d. combined r.f. out/S-meter.

The IC-290E has been introduced as a replacement for the IC-260E which

will now be withdrawn. It has basically the same specification as the IC-25E and as it is a multimode operates on c.w., f.m. and s.s.b. and also has an RIT button. Facilities for listening on repeater inputs is another feature.

Further details of price and availability for both the rigs are obtainable from: *Thanet Electronics Ltd., 143 Reculver Road, Beltinge, Herne Bay, Kent. Tel: (022 73) 63859.*

OFF THE SHELF DELIVERY ON THESE

FLUKE

BRAND NEW FROM FLUKE . . . NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:

A peak hold switch which can be used in AC or DC for volts and current functions.

Audible continuity testing and level detection for sensing logic levels.

A temperature (°C) range for use with a thermocouple.

£155

Carriage and Insurance £3

The following accessories are in stock now

Y8008 Touch and Hold Probe	£29.00
80K-40 High Voltage Probe	£51.00
81RF RF Probe to 100 MHz	£35.00
80T-150C Temperature Probe (C)	£66.00
80I-600 Clamp-on AC Current Probe	£61.00
80J-10 Current Probe	£22.00



HERE IT IS . . . THE EVER POPULAR 8022A HAND-HELD DMM

Consider the following features:
6 resistance ranges from 200 ohm-20 ohms.

8 current ranges from 2mA-2A AC/DC.

10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC.

Pocket size - weighing only 370 gms.

Full overload protection - will withstand 6kv spikes.

Rugged construction - virtually indestructible.

Meets tough military specs. - drop proof.

In line, pushbutton operation for single-handed useage.

Incorporates low power CMOS chip for low power consumption.

All this plus a 2-year full guarantee.



£89

Carriage and Insurance £3

Soft carrying case
£8 extra

Even more sophisticated the Fluke 8020A.

Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.


Price £125

Carriage and Insurance £3.00

A handsome soft carrying case is included (this model only)

OFF THE SHELF DELIVERY ON THESE

FLUKE

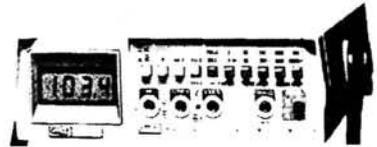

8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.

The 8010A and 8012A feature:
10 voltage ranges from 200mv-1000v dc, 200mv-75v ac.
3 conductance ranges from 2mS-200nS.

6 resistance ranges from 200Ω-20mΩ - the 8012A has two additional resistance ranges 2Ω and 20Ω.

10 current ranges from 200μA-2A AC/DC - the 8010A has two additional current ranges 10A AC and 10A DC.

80 10A £167 80 12A £218

Carriage and Insurance £3.

The 8010A is also available with two rechargeable Nicad size C batteries installed in option -01 a+ £193.00.

PLEASE ADD 15% VAT TO ALL ORDERS except where items marked "VAT Included". CALLERS WELCOME.

We are open 9 a.m.-6 p.m. Monday-Saturdays. We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities.

ELECTRO-TECH COMPONENTS LTD.

364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667


M&B RADIO

INVERTED VEE DIPOLES

ONLY £32.00

MULTIBAND 10-11-15-20-40-80 meters

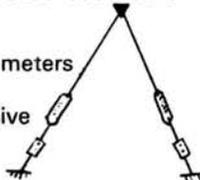- 2kW Handling Power
- Heavy Duty Stranded Non-corrosive & Plastic Coated
- Total Length 26 meters




RADIATION DETECTOR

ONLY £2.70

COMPLETE WITH INFORMATION

- Metal Cased
- Quartz Fibre Type
- Contains 3 Lenses
- Only the Size of a Pen

DETECT RADIATIONS BEFORE IT IS TOO LATE

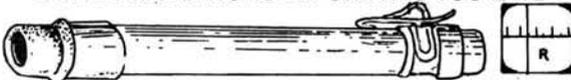

BOSCH 2.5kW 40uF Capacitor £8.00

- Mini Transformers 12 volt 250mA £1.00 p&p inc.
- Transformers 12-0-12, 24-0-24 500mA £3.25 VAT p&p inc.
- Auto Wound 240 to 110v, 6.3A £9.00
- Transformer 15-0-15 volt, 5A £6.50

VAT & P&P EXTRA UNLESS STATED

M&B RADIO 86 BISHOPSGATE STREET
TEL (0532) 35649 LEEDS LS1 4BB

FIRE! BURGLARY! ASSAULT! INTRUDERS!

Summon help when you require it - not afterwards when its too late!

Protect yourself and family from some of the bad things in life with Wireless Alarm Systems you can install in minutes NOT days, associated with wired systems. Our range of cordless security devices which are of the highest quality for home or business can give you that secret extra protection. HO & GPO approved equipment available. For the enthusiast, purchase separate transmitter & receiver devices, to build your own equipment.


Send for further details to:



A. R. Williams
Security
Aids

Reg. Office,
Park Chambers
7 Inverness Place,
London W2 4RG

Tel. 01-221 1422.

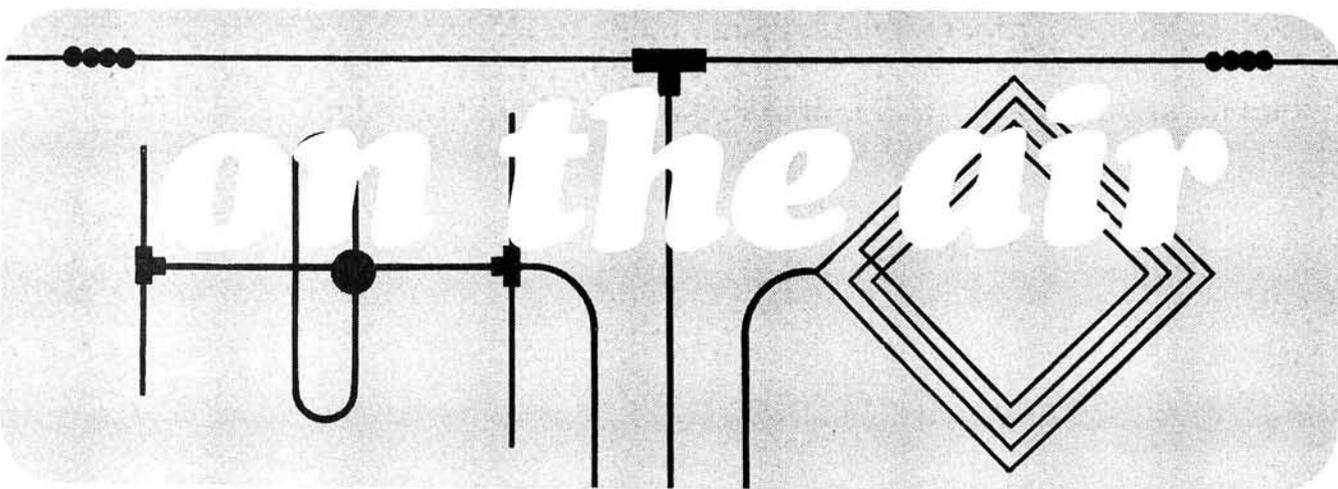

Amateur Bands

by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR
Silver Firs, Leatherhead Road,
Ashted, Surrey KT21 2TW.
Logs by bands in alphabetical order.

With the release next year of one of the three amateur bands allocated at the WARC in 1979, many amateurs will be lashing up temporary antennas in order to see what the new 10MHz band can offer. There will probably be a spate of transverters for use with existing rigs and, hopefully, *PW* will come up with a design. Whether it will be worthwhile including facilities for the other two new allocations, 18 and 24MHz, is very much a matter of speculation, since their release date is indefinite at the moment and could be of the order of years.

For the listener with a general coverage receiver the problems of using the new bands are few, mainly tuning the a.t.u. to the appropriate frequency, once the band limits have been ascertained. If dipole antennas are being used then another cut for 10MHz can be soldered in parallel with an existing one.

For anyone with an amateur-bands-only receiver then an external converter would seem the only answer, preferably crystal controlled and feeding into the set which is then used as a tunable i.f. stage. While 3.5 to 4MHz is a favourite spread for this particular application, the risk of breakthrough of powerful signals in this segment is very real and perhaps the 28MHz band would be better for the tunable i.f. stage. Anyway, signals on this band are going to fall off in the next few years as we slide down the slippery slope of the present solar cycle!

With such a converter, coverage of all three new bands would be wise from the outset, involving only a few extra components. Naturally, anyone buying a communications receiver today should ensure that it does cover the 10, 18 and 24MHz bands, and while this would seem very obvious there is one new set being advertised for several hundred pounds that does not do so! The same reasoning applies to transceivers, of course, where the vast majority are amateur-bands-only. We might even be getting some good bargains before long in transceivers and receivers that do not meet our future requirements in much the same way as the 22-channel 27MHz CB sets became dirt cheap once 40 channels were allocated, forming a good foundation for a 28MHz set-up.

Come to think of it, the present illegal CB a.m. rigs in this country may also come on to the surplus market before long, once the legalised f.m. service gets under way; another oppor-

tunity for *PW* to get some designs organised for converting such rigs to our 28MHz band?, followed by a linear, of course. Nothing new in this idea, but little has appeared in print on the subject, since such basic sets are illegal, as they stand, in the UK. The Government might be delighted if a few tens of thousands of such rigs were converted for the 10m band!

My piece on receiver i.f. filters seems to have been well received, so next month I propose to chat on the pros and cons of single and multiple frequency conversion in receivers.

Club Time

A veritable explosion of reports from secretaries, so many of the club names mentioned may be new to the column. Owing to space restrictions (note the smaller type face recently), famous club names may be missing, but be assured they are as active as ever.

Consensus of opinion is that the recent "radio only" policy of *PW* is more likely to mean readers of the type acceptable to the average club.

Southdown ARS. Feature is the Dreaded Draw where, every month, the committee draws members' names from the hat for the honour of writing a short article for the club newsletter. What a clever idea! The SARS, with other local clubs, was very active organising stations and social events at the recent IARU Region 1 conference at Brighton. Try R. E. Holtham G4EKS, 2 Benbow Avenue, Eastbourne, E. Sx, for up-to-date info on club activities, or ring Eastbourne 32777. Meetings first Monday at 7.30 at Chaseley Home for Disabled Ex-Servicemen, Southcliff, Eastbourne, with Arthur Milne G2MI of QSL bureau fame discoursing on amateur radio of the past at the August meeting.

Edgware & District RS. Second and fourth Thursdays, 8pm, Watling Community Centre, 145 Orange Hill Road, Burnt Oak, Edgware, Middx, only event in August being s.s.b. f.d. briefing on the 27th. General news on club, details of slow morse from G3ASR, plus club net info from Howard Drury G4HMD, 39 Wemborough Road, Stanmore, or 01-952 6462.

Sutton Coldfield RS. Meets at S.C. Public Library, Sainsbury Centre, second and fourth Mondays, 7.30. Talks, discussions, etc, for the welcome visitor on radio and allied subjects. Contact sec Derek Turner G8TUR, 10 Jervis Crescent, S.C., W. Mids or (021) 353 2061.

Cheltenham ARA. Following the sad loss of Edgar Janes G2FWA, news is that member Bill G2AGX has also passed away. Meetings at the Old Bakery, Chester Walk, Clarence Street, on first Thursday and third Friday. EME tests are discussed by G4ERP and G8PZD on Aug 6, and the 21st is natter-night, always a jolly occasion, ideal for the visitor popping in for the first time. Do contact Grant Cratchley G4ILI, 47 Golden Miller Road, Cheltenham, or 43891. Club is organising coach trip to the ARRA exhibition at Donington Park on Oct 30, so get your name down now!

Dartford Heath DF Club. No regular pm meetings but frequent d.f. hunts, which Margaret Burchmore G8LXX, 49

School Lane, Horton Kirby, Dartford, Kent, will gladly tell you about on request.

University College of N. Wales ARS (GW3UCB). Aug 2 has the club engaging in the 2m QRP contest from Cynn-y-Brain with a 2m meteor scatter trial on the 11-12th from the same QTH and a 4m trophy contest on the 16th. All go, isn't it! Club recruitment is in full swing, and Simon Brown GW4ELI, School of Eng. Science, Dean Street, Bangor, Gwynedd, would be particularly glad to hear from any s.w.l. or licensed amateur considering a degree course, especially in electronic engineering.

Wirral ARS. First and third Weds, 7.45pm, Sports Centre, Grange Road West, Birkenhead, with G4KVP running a quiz on Aug 5 and a live demo of slow-scan TV by G4CZR on the 19th. Latest issue of newsletter has G3TKN holding forth, very practically, on DX working on 80m. More from G. O'Keeffe-Wilson G8VPP, 20 South Drive, Upton, or 677 1531.

Wigan College of Technology RS. Club in process of formation with call G4KOG, with college offering RAE course in Sept, projected code classes and practical evenings, with a "wealth of test equipment and expert advice", so what more could one ask? Senior lecturer J. Hesford G8WLS at the college, Parsons Walk, Wigan, or 494911, can help on any aspect.

Southgate RC. Second Thursday at the Scout Hut, Wilson Street, Winchmore Hill, London N21, just two mins from W'more Hill BR station. Interesting newsletter *Bandspread* has details of RAE classes and code sessions for its 130 or more members, and following a recent club vote it's "no smoking" at lectures. Write to PRO Stuart Lindell G4IEH, 73 Old Park Ridings, Winchmore Hill, London N21, or 01-360 4936.

Stevenage & District ARS. First and third Thurs, 8.15, Senior Staff Canteen, British Aerospace, Plant B, Gunnelswood Road, Stevenage. Aug 6 is natternight and club station on the air with a beginner's night on the 20th. Make a note of Sept 3 when Mike Waterman chats on video recorders. Contact S. Clarke G8LXY, 126 Putteridge Road, Luton, Beds, or try the f.m. net on 145-25MHz Mondays at 2000 local.

Mid-Sussex ARS. At the QTH of G3ZMS, Marle Place, Leylands Road, Burgess Hill, W. Sx, at 7.45. although during August meetings will be informal. Recent highlight was presentation of two trophies in club constructional contest. Club was another of those concerned with the GB11ARU venture at Brighton. Details from G3ZMS, as above.

Wireless Preservation Society. Bit off the usual track but advance notice of annual get-together on Sunday, Sept 20, at the National Wireless Museum, Arreton Manor, near Newport, IOW, from 2.30pm. Talk-ins GB3WM on S22 and (SYLEDIS permitting) GB31W on RB4. More from Doug Byrne G3KPO, Arlington House, 34 Pellhurst Road, Ryde, IOW, or it might be easier to ring Ryde 62513.

School of Engineering Radio Club (G3IHH). At the REME Arborfield Garrison, near Reading, Berks, every Thursday, 1930 hours. Excellent newsletter tells of activities such as film nights, visit to the Rascal plant, socials, satellite communication, and many practical projects. Very wisely, the club is considering buying CB f.m. equipment in due course for contacting the many students at the School who will be similarly equipped but perhaps unaware of the club's activities. Write to John Northcott, at Shardcroft, 328 Nine Mile Ride, Wokingham, Berks, Eversley 732218, who will tell how to reach the club.

East Antrim ARC. The Carntall Hall at 8pm on Sept 8 for the AGM will be a good opportunity for visitors to find out all about this club, where new members are especially welcome. Sec is Jim Welsh G14JXM, 20 Bryantang Brae, Doagh, Ballyclare, Co Antrim, BT39 0RJ.

Chichester & District ARC. It's room 34A, Lancastrian Wing, Chichester High School, Basin Road, Chichester, first and third Thurs at 7.30pm, although August is a closed month. However, Sept 1 sees Peter Brooks enlarging on electronic games machines. More from S. Talbot G8FCX, 31 Pier Road, Littlehampton, W. Sx, or Littlehampton 5082.

City of Belfast YMCA RC. "Increasing number of members reading *PW* with recent orientation towards radio, and amateur radio in particular", says hon sec Paul McTaggart G16BJO. Club holds famous old call G16YM with own shack in Belfast YMCA, meetings at 7pm, Tuesdays. The tri-bander antenna is 100ft over street level! Try Paul at YMCA Radio Club, 12 Wellington Place, Belfast BT1 6GE.

Harwell ARS (G3PIA). Third Tuesday of the month, 7.30pm, in the Social Club, AERE, Harwell, with visitors assured of a

warm welcome. RAE classes look like adding nearly a dozen new licences before very long, with local CBers expressing a lot of interest in the club's activities. So says Ann Stevens G8NVI, 78 Whitehorns Way, Drayton, Abingdon, Oxon, who will be pleased to answer your queries. Drayton 430 will also do.

Torbay ARS. Fridays, 7pm, Bath Lane, rear of 94 Belgrave Road, Torquay, with a general meeting on last Sat of month at same QTH. Big event to come is the Torbay Rally at ITT Social Centre, Old Brixham Road, Paignton, on Aug 30, with trade stands, prize draws and refreshments, hard and soft. Talk-in on S23 with G8NJA and through GB3TR. Have a word with L. G. Mays G2CWR, Atlantis, Clennon Avenue, Paignton, for more details.

Mexborough & District ARS. Fridays, 7pm, at Harrop Hall, Dolcliffe Road, Mexborough, with meeting details from Ian Abel G3ZHI, 9 Grove Terrace, Maltby, Rotherham, or R'ham 814911.

Gloucester ARS. Thursdays, 7.30pm, Chequers Bridge Centre, Painswick Road, Gloucester, with other outdoor activities like d.f. hunts, picnics, etc, during the summer (?) months. Pat Perkins, 40 Carlton Road, Gloucester, will fill you in.

Fareham RC. From Sept to Dec meetings every Wednesday, at 7.30pm, Portchester Community Centre, Room 12, with forthcoming events dealing with TVI matters, club 80m receiver project and computers. Three members are already working on the *PW* Exe transceiver project but why blame me if *PW* ran out of dishes at Ally Pally! I wasn't even there! Brian Davey G4ITG, 31 Somervell Drive, Fareham, Hants, or F'ham 234904 will help with the details.

Bury RS. Second Tuesday of the month with other Tuesdays for morse tuition, construction projects and operation of club station G3BRS or you can just have a "noggin and natter". Just go along, that's all. Aug 11 is a d.f. foxhunt event, with notice of a talk on meteor scatter techniques by G8JHL on Sept 8th. More from Peter Butterworth, 6 Wilton Avenue, Prestwich, Manchester M25 8HB, or on (061) 798 0970. Congrats, Peter, on your excellent calligraphy, it's a pleasure to look at as well as to read!

North Bristol ARC. Meetings at SHE7, Braemar Crescent, Northville, Bristol, every Friday at 7.30pm for lectures, RAE classes, code instruction and club projects. I'm sure club sec W. E. Bidmead, 4 Pine Grove, Northville, Bristol BS7 0SL, will be pleased to tell you what "SHE7" is. Afraid I don't know!

Andover RAC. Second Wednesdays and fourth Tuesdays at the Wolverdene, Love Lane, 8pm, says club treasurer Bill Wynn G4EUQ, 263 Oak Close, Middle Wallop, near Stockbridge, Hants.

Loughborough Falcon ARC. Every Friday, 8pm, at Brush Sports and Social Club, Fennel Street, L'boro, Leics, although during this time of the year d.f. hunt station G3RAL is kept pretty busy, with signal reports welcomed. Try around 1850kHz a.m./c.w. Routine matters mean RAE classes, morse tuition and constructional work. Write, only, to Jim Smith G4DZL, 91 Anson Road, Shepshed, Leics, or try the 2m f.m. net on S17-145-425MHz Tuesdays from "eight till late"!

Cray Valley RS. Advance notice of popular s.w.l. contest on Sept 12 1800GMT to Sept 13 1800GMT, with up to 18 hours logging time, but there is a multi-op section, plus phone and c.w. sections. Details from CVRS chairman Owen Cross G4DFI, 28 Garden Avenue, Bexleyheath, Kent DA7 4LF. Member G3VLX recently activated 9H3AM on the h.f. bands with over 1500 QSOs. Meetings Christchurch Centre Hall, Eltham High Street, Eltham, London SE9, at 8pm, on first and third Thursdays, and don't miss G8UVD describing his "Dopplescan" d.f. system for the 2m band on Aug 6th.

Now the DX

ISWL sec **Ed Baker** (Cramlington, Northumberland) has acquired a Hallicrafters SX62A which pleases him mightily getting CT2AK, N6YK/VP2A on 80m, CO2MQ and M1IPA on 40, plus 9Y4NP and FO8DX on 20m. The antenna is 20m long. From C. Griffiths in Northam, Devon, come reports of 9G1SJ, C31VE, 5N2EME, ZB2BL and OY9K on 14MHz, DU7RLC on 21 and 6W8AR on 28MHz with his CR150 and two long wires.

YL **Anne Edmondson** still awaits her BRS number from the RSGB but already belongs to the RNARS (1743). Her DX200

and short wire brought in YC6NH (QSL Box 1, Medan, Indonesia), VP2MDG (QSL W6FDG) and N2APR/4X4 of PO Box 5707, Jerusalem 91056, with M1C, HI3BEA, SV0BL, U4DP (QSL UK4ABZ), VP2AK (QSL Box 1156, Antigua), 8Q7AZ on the 20m band. Ah, yes, QTH is Edinburgh.

First report from **Graeme Caselton** BRS44984 of Orpington, Kent, where a BC348 is in use with a 50ft inverted-V. This set is an "R" model and covers 10m where HH2BW, 9M2CW and TU2JQ were captured, with PJ2MN, VP8AGY (QSL G4DEP) on 15m plus EA8TE, W9RBD/VP9 and FM7AV on 20m, with nothing special on 80 or 160m. I suspect this last-mentioned state of affairs ought to be looked into as 80m, in particular, is very active with DX.

Another first timer for the column is **Stephen Pearson** of Arundel, W. Sx, also using a BC348 on 20m where he found VP8HZ, VP2VJ, DU1EH, 9H1ET and EA8LD, after only a few months in the hobby. In Truro, Cornwall, **Bill Rendell** has not been too active on the bands of late but does mention the whopping signal from VP8QI who has now moved from Faraday Base on Argentine Is. to Rothera Base on the SE side of Adelaide Is. with QSLs to G4CHD.

Just along the corridor from my office resides **Frank Ogden** G4JST of *Electronics Weekly* (and ex-PW!) and over a lunchtime noggin he tells me he has just completed an all-band s.s.b. rig, and was delighted to work a DF7 on 10m when using only 50mW input while testing the rig. The DF sent Frank an excellent tape recording of the QSO as a memento. QTH is Ardingly, West Sussex.

Just to prove me wrong about no c.w. reports for the column, **Jim Dunning**, of Prestatyn, Clwyd, reels off 4U6ITU on 3.5MHz, C31DB, N6YK/VP2A on 7MHz, EA8TY, FM7AV, HSSAID, ZB2EO, ZS4T and 9X5AB on 14 with dozens on 21MHz like CP8DK, CX7AQ, D4CBC, HH2VP, HK0BKX, JT0WA, SV11W/5 in the Dodecanese, TU4BD, ZC4AR, ZL2FH, and 9X5AB again. 28MHz wasn't quite so exciting, with N6YK/VP2A again, ZD8TC and 4U6ITU. Interesting DX on s.s.b. included C5AAP and ZS2KG on 21, but the best, possibly, is yet to come! Jim also copies RTTY stuff so, at long last, Dennis Sheppard, of Earl Shilton, Leics, gets a companion in this mode. A 7B machine uses an all-i.c. design terminal unit to record local or off-air traffic on to a tape cassette. DX on RTTY runs to EA8RU, K4VDM, LX2LH, Y53UA on 14MHz with 21 coming up with FP8DF, K4ZS, and Y53UA again among others. Receivers are an AR88 and SRX30 and two short wires.

Dave Coggins, of Knutsford, Cheshire, hasn't found conditions too good generally with his FRG7700M receiver, but he did get two QSL cards from VR6TC on Pitcairn for reports of one, and one and a half years ago, just to cheer him up! With a two-element quad on 10m and inverted-L on other bands plus a.t.u. Dave logged something on all bands with EL2AU, S79WHW, TU2JD, ZE1AR, 3D6BE on 10m, KH6AFM, TY9ER, ZK1AR, 9X5PP on 15, AH8A on American Samoa, VK9NS and VR6TC on 20m while on 40m it was KG4WM for a rare one, TG9AL, VK2WC and 6W8AR. CW was copied from several UA-land stations on 160m.

John Kaczmarek BRS46526 of London SW10, has got going finding that an a.t.u. did wonders for his FRG7700M from the 100ft wire. Best find was VP2MDG on Montserrat on 21MHz band. Present plans call for a go at the RAE in 1982, probably sticking to a "B" ticket for a while. Well OM, it is well worth while having a go at the code, too, if you possibly can, and anyway, it's cheaper in the long run to get the full ticket right away!

Something strange going on! Several readers report getting a QSL card from GB4RS special event station which infers that their report was the only one received. "Unique" is the word used on the card, but someone seems to have got it wrong somewhere!

As usual, reports by around the 15th of the month please, with a few more logs covering c.w. operation very welcome.

One last note. The East Herts College at Turnford will be offering an RAE course over three terms from September this year aiming at the May, 1982, exam. Times probably between 7 and 9pm Mondays, but up-to-date details from Jim Sleight G3OJI, 18 Coltsfoot Road, Ware, Herts, or (0920) 4316 of the Chesham and District Radio Club, which meets at the Church Rooms, Church Lane, Wormley, not far from the College, at 8pm on Wednesdays.

Medium Wave Broadcast Band DX

by Charles Molloy G8BUS

Reports to: Charles Molloy G8BUS
132 Segars Lane, Southport PR8 3JG.

As the nights start to grow longer it is worth having another look at DX from North America. In the June issue we saw that it is possible to hear North America during that month although reception is limited to the maritime provinces of Canada and the eastern states of the USA. There must be a path of darkness between transmitter and receiver. Signals peak up for a short period at sunrise in the UK which corresponds in mid-June to sunset on the eastern seaboard of North America and, if the path is open, we get half an hour or so of very good reception. What is the situation then a couple of months later?

North America East Coast

Signals will now fade in when sunset occurs at the North American end of the path, provided of course that propagation is favourable. Reception will then settle down for a couple of hours until the arrival of sunrise in the UK when signals will peak up again before fading out. This is the pattern for the rest of the year. Signals peak up as they fade in and peak up again as they fade out. During winter, these peaks occur at times of heavy QRM so they pass largely un-noticed, though occasionally CJYQ in St John's, Newfoundland, is logged in the early evening as it peaks in.

North America West Coast

As the period of darkness increases, how far west will nighttime extend when sunrise occurs in the UK? By the last week in August dawn in the UK corresponds roughly to sunset along the west coast of North America. Signals from that area will then get a double boost, just like those from the east coast in June. This occasion marks the start of a six week season during which the west coast can be heard well in the UK while Europe can be logged by DXers in north west USA and British Columbia in Canada.

Thanks To You
From KOMO

Dear Mr. Molloy:

Thank you for your letter reporting reception of KOMO. We are always very pleased to hear from our DX listeners. Your log of our programming is correct and we are pleased to send you this card as verification of your report of Sept. 18, 1964.

J. Mr. Kenna
KOMO
ENGINEERING DEPT.

KOMO

100 FOURTH AVENUE NORTH SEATTLE 9, WASH

KOMO in Seattle

My first logging of the west coast was at 0530 UTC on September 18th 1964 when I listened for half an hour to KOMO on 1000kHz, which is located in Seattle in the state of Washington. Others followed including KING on 1090kHz which is also in Seattle, KFBK on 1530kHz in Sacramento, California, and two stations in Portland, Oregon, KEX on 1190kHz and KYMN (now KXYI) on 1520kHz. This was at a time of low sunspot activity which favours medium wave propagation. What about the present?

Last year, DXers in Seattle and Victoria BC pulled in a number of European medium wave stations between September 27th and October 3rd. DXers in the UK seemed to have missed this opening but two stations have been picked up recently in the UK—KEX on 1190 and CJVB in Vancouver on 1470kHz.

So if you can make the effort to get out of bed half an hour before sunrise during September you may be lucky enough to hear some real North American DX. Some frequencies to try are 1000, 1090, 1220, 1410, 1470 and 1530kHz, and the time zone is Pacific Standard Time (or daylight saving) which is 8 hours back. A communications receiver and m.w. loop antenna is essential for this sort of DXing and don't forget to have your tape recorder at the ready.



Thanks for letting us know
you heard our programs . . .
We hope you continue to
enjoy listening to *KFBK*
Verifying reception Sept. 8, 1965
at 9 PM PST & Sept. 10, 1965
Sacramento, California
50,000 WATTS • 1530 KC.

KFBK in Sacramento



kymn
50,000 WATT RADIO VOICE
REPUBLIC BROADCASTING, INC. PORTLAND, OREGON, U.S.A.

KYMN in Portland, Oregon

TVI

These letters stand for Television Interference and the interference (QRM) referred to is QRM picked up by television receivers. TVI means interference with the reception of TV programmes. There is another type of TV QRM which is radio interference produced by TV receivers. In the United States this sort of QRM is called i.t.v. (interference from TV) but as this term might cause some confusion in the UK I'll just call it TV buzz. What is TV buzz, how does it occur, who does it affect and what can be done about it?

A TV set operating on the 625 line system generates a strong signal at 15.625kHz in order to produce the lines on the screen. This signal also produces a buzz at intervals of 15.625kHz across the long, medium and tropical bands. In severe cases these harmonics can be heard on the international s.w. bands as well but usually it is only the lower frequencies that are affected. TV buzz is radiated in three ways: direct from the TV set which

is the main cause of QRM, from the TV antenna and its feeder, from the TV set into the house mains wiring which then acts as an antenna.

A letter from reader **Norman King** started me off on this subject. Norman lives on the top floor of a four-storey block of flats in Scotsburgh in the RSA and he is troubled with TV buzz which he thinks is coming from the 220 volt mains wiring.

What can be done about it. The first thing is to find where it is coming from. An ordinary portable receiver with internal antenna will help track it down. Tune across the medium waves to a point on the scale where the buzz is audible. Then use the receiver as a detector and try to find a spot where the buzz is weak. You might also try it with your own TV switched off, for if you live in flats the buzz may be coming from a neighbour's TV.

In general, if you use a battery operated receiver near a window as far away from the TV set as you can get and you have a whip antenna mounted on the window ledge with a screened lead to the receiver, you stand a good chance of reducing TV buzz. I've found I can null out buzz at my QTH using a m.w. loop which can be used for m.w. DXing provided you don't move it, or as a passable antenna for the tropical or short-wave bands.

Radiation from Mains Wiring

If you are sure this is happening then fit a mains suppression filter in the mains lead between the TV set and the mains socket. A typical suppressor is the RS Components 238-435 which is rated at 2 amps and attenuates in the range 150kHz to 30MHz. This means that it can be used with equipment that consumes no more than 480 watts on 240 volt mains and that radio frequencies within the long, medium and short wave broadcast bands will not pass through it. Has anyone been successful in dealing with TV buzz? It is quite a serious problem for some DXers.

Readers' Letters

Reader **David Appleyard**, who lives at the university town of Uppsala in Sweden, has built a medium wave loop and his first catches with it "during this period of extremely short nights up here" are Damman in Saudi Arabia on 1440kHz which knocked out Luxemburg at 1950 and Metro Radio in Newcastle on 1153kHz at 0100. David has been on a month long visit to New Zealand where "I enjoyed the most sensational listening I have ever known". Using up to 1500m of antenna (Bev...e) at Tiwai Point, South Island, he picked up La Voz de Cuba 600kHz, TWR Bonaire 800kHz and a number of stations in eastern USA including the 5kW WSIX in Nashville on 980kHz. Wouldn't it be wonderful to have a 1500m longwire!

"The longwaves are quite interesting" writes **Edward Baker** of Cramlington in Northumberland who has received QSL cards from Baku 218kHz, Algeria 251kHz, Yerevan in Armenia on 254kHz, Poland 227kHz and Czechoslovakia on 272kHz. A Realistic DX100L is in use by **Colin Watson** (Cumbernauld) who pulled in Manx Radio 1368kHz and Dublin on 1278kHz during the daytime. **Harold Brodribb** of St Leonards-on-Sea is another local radio enthusiast. He used his AR88LF, which covers the top end only of the medium waves above 1484kHz, to pull in the 250 watt Kings Lynn on 1602kHz. The antenna is a longwire and reception was during the day. Harold reckons that the good reception he experiences to the north and the south west is due to the sea path in those directions.

"I had my letter answered over Radio Finland's Airmail (Mondays at 2030 on 254kHz, 558kHz and 963kHz) and Radio Sweden's Mailbag (Sundays on 1179kHz at 1830, 2100 and 2315)" writes **Simon Hamer** of New Radnor. He reports the medium wave reception on his Grundig Melody Boy is improved by connecting a 20 metre antenna and earth to it. Harold Brodribb has had a different experience. He followed Simon's advice (July issue) and connected a longwire via a loop to a portable and got "dreadful second channel whistles even when using the socket provided by the maker". It probably depends a lot on the particular receiver but it is a dodgy practice to connect a longwire to a portable designed to work off its internal antenna.

Short Wave Broadcast Bands

by Charles Molloy G8BUS

Reports: as for medium wave DX, but please keep separate.

Antennas for DXing is a subject that is endless. My preference is for the end fed (longwire) used with an antenna tuning unit (a.t.u.) but many DXers prefer the half wave dipole and its variant the inverted V. These two are directional antennas, maximum pick up being broadside-on to the wire and both give a boost to signals in the band for which they are cut. On other bands these antennas are non-directional and they give no gain. There is also the inverted L which is really a longwire with download and both have similar properties. Is there any other antenna we can try.

The Windom is a cross between the inverted L and the half wave dipole (see Fig. 1) and it has some of the properties of each. It is a non-directional antenna, which may be handy at a QTH where a choice of direction is not available. The windom is an all-band antenna and can be used with an a.t.u. but it does, so it is claimed, produce optimum results on the waveband for which it is cut and on half and one quarter that wavelength.

The horizontal part (L) equals half a wavelength minus 5 per cent at the lowest frequency to be used and the download is attached to a point $0.36L$ from either end, the end nearer the house being more convenient. An antenna cut for the 49m band (6MHz) could be 23.75 metres in length with the download 8.55 metres from the end. It will perform well on the 49m, 25m (12MHz) and probably on the 13m (21MHz) bands. If this is too long then one for the 31m band (9MHz) could be 15.4 metres with the download at 5.55 metres from the house and this antenna should work reasonably well on the 31m and 16m (18MHz) bands. There is plenty of scope for the experimenter here.

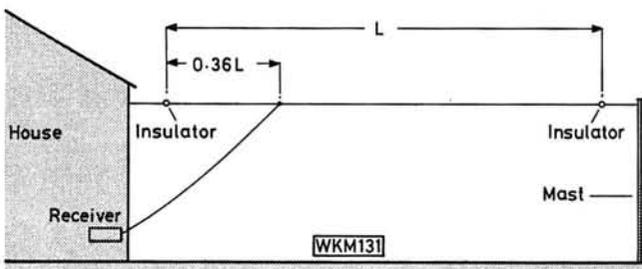


Fig. 1

Reception Reports

"I would be grateful if you would sometime in your column give a model example of a short-wave report as I wish to start collecting QSL cards" writes **Stephan Rogalson** from Birmingham.

The model medium wave reception report in the February 1981 issue will do when writing to stations in the Tropical Bands or to short-wave stations that are not broadcasting to your area. Times have changed though, when writing to international broadcasters who are beaming to your part of the world. These are no longer experimental transmissions. The stations know they are being received well in the target area so what they want is feedback from the audience about the programmes.

This point was made forcibly by the Two Bobs during a Swiss Short-Wave Merry-go-round programme recently. What they said in essence was that "you wouldn't send a reception report to your local TV or radio station so why send one to us?" They went on to say that Swiss Radio International has a network of reception monitors who provide all the reception information that is required by their engineering section. SRI will however issue a QSL card to listeners who write in, but what they are asking for is comment on the programme. "If you don't like our programmes write and say so and get them changed."

I read somewhere recently that the BBC Monitoring Station at Caversham have a continuous check on Radio Canada International's transmissions to Europe. If this is so then it is hardly surprising if RCI are not over enthusiastic about reception reports from listeners in the UK. On the other hand this station's Sunday Weekend Magazine programme is built round listeners' letters which has led to some interesting mini-talks on a variety of subject. You can also experience the thrill of hearing your name broadcast all over the world.

Many stations run a letterbox type of programme. This is what stations want, so if you supply material for their programmes or comment on them, you can reasonably expect a QSL or listener card in return.

When writing to a DX station such as Radio New Zealand, which does not beam to Europe, then the traditional type of report is in order. You are asking for a verification of reception so you have to supply "evidence" that you really pick them up.



QSL card from Iceland (12-175MHz) received by Martin Whittington

Return postage in the form of an international reply coupon is appropriate in this case as you are not one of the station's audience and they are really doing you a favour in answering at all.

The European DX Council produces the EDXC Reporting Guide which "explains how to write a constructive reception report in English and other languages". It is aimed at the DXer and a DX vocabulary is included. Further details of this and other EDXC publications are obtainable by sending an SAE to EDXC, PO Box 4, St Ives, Huntingdon, PE17 4FE.

International Listeners Guide

I have recently taken out a subscription to this 16 page A5 size guide to programmes on the international short-wave bands. The ILG, which comes out four times a year in March, May, September and November, is a directory of external broadcasts in English to Europe and overseas. It gives the times, frequencies, target areas and relay stations in use throughout the day and there is also some information about programme structure, world news and commentaries and important English language DX programmes.

A specimen copy of the English version of the ILG (there is also a German version) is available for one IRC from Bernd Friedwald, Merianstr 2, D-3588 Homberg, FRG-West Germany. The annual subscription is DM7 or 10 IRC. This publication is of particular interest to the s.w. programme listener as it indicates what is on the air throughout the 24 hours.

NORTHERN COMMUNICATIONS

AMATEUR • COMMERCIAL • MARINE

AND NOW FOR SOMETHING REALLY NEW!




Send for details

-12V DC earth
144-146 MHz or
VHF Marine.

15 x 19 x 5 cms.
Mobile bracket
+ Int speaker inc.

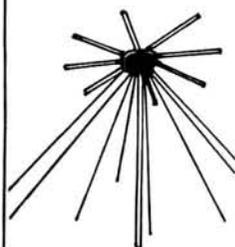A VHF monitor receiver with **VFO** plus **12** optional scanning channels for **£46.00** inc. VAT. Crystals **£2.25** each. Carriage free.



NORCONE 512 (66-512 MHz)
It's here! A no compromise, precision made full 16 element discone antenna made in Britain. Standard S0239 connector, with cover. Supplied with 1" diameter, 30" mounting support mast and complete instructions.

An ideal partner for the SX200N "Bearcat" and other scanning receivers. It may also be used for transmission and in particular where antenna space is limited.

Full coverage of 70.144.432MHz Amateur bands plus Aircraft, Marine and Commercial bands.

£25.95 p.p. £1.75

MK-1. In line vertical mounting kit for 1" to 2" mast.

£2.45 p.p. £0.75

MK-2.

Chimney lashing kit, including hardware and lashing wire. **£2.95** p.p. £1.00

CK-1. Low loss coaxial cable kit, 10 metres, with connectors and fixing clips. **£3.75** p.p. £0.75

ZL-12 COMPACT YAGI

13db gain, compact 2 metre Yagi. 10'6" boom, lightweight rugged design. Hundreds of this award winning antenna already in use. Send for details.

£28.75 p.p. £1.75

ZL-8 SUPER COMPACT YAGI

9db gain, super compact 2 metre Yagi. 6'0" boom, lightweight rugged design. Ideal for limited spaces and portable operation. Send for details.

£17.95 p.p. £1.75

SX200N HOT NEWS!

Scanning Receiver NEW MODEL!

New model of this superb unit now with:
Plug in modules - for easy service.
Increased AF Output - for better reception.
Improved Image Rejection - to cut out unwanted signals.
Increased Selectivity - to cut out adjacent channels.
Plus many more interesting features.

£264.00 inc. VAT.
Carriage £1.50

SPECIAL OFFER!

SX200N + Norcone 512. Complete inc. VAT. and delivery. **£285.00**

YAESU FT707 TRANSCEIVER

This most popular of compact HF rigs is currently the number one selling station amongst our extensive range of amateur radio equipment which includes such names as: CUSHCRAFT, JAYBEAM, FDK, STANDARD, SWAN, AZDEN, MICROWAVE MODULES, NAG, SEM and many more. Don't just take our word for it come and try the FT707 or better still order yours now!

FT707 100W **£529.00**
FP707 PSU **£109.00**
FC707 ATU **£80.50**
FV707 VFO **£186.30**

Customer satisfaction and good service is our trademark!

STANDARD C78 UHF PORTABLE

Amazing new 70 cms Transceiver. Send for details. **£209.00**

Prices include VAT @ 15%

299-303, Claremont Road, Halifax HX3 6AW,
West Yorkshire. G3UGF.

Tues-Sat. 9.45am-5.30pm.

Telephone (0422) 40792.

24 hour Ansafone Service.



LISTEN TO THE WORLD

WITH A
RECEIVER
FROM

Catronics

Best Selection
LOWEST
PRICES

MEDIUM WAVE/SHORT WAVE

Trio R-1000 is a high class general coverage receiver covering 30 bands between 200kHz and 30MHz with a PLL synthesiser. Both digital display readout (1kHz resolution) and analog display (10kHz resolution) are provided for easy and accurate tuning. The R-1000 also includes a quartz digital clock with timer, three IF filters, RF ATT and tone control, etc. to ensure the best receiving conditions for each mode 240V AC/12V DC supply. **Catronics Price £305.**

AIRBAND (VHF)

Signal R517 portable, fully tuneable 118 to 143MHz with provision for 3 crystals (extra) 1.8µV sensitivity. Fine Tuning control. Telescopic aerial. **£49**

Lowe AP12 portable 12 crystal controlled channels, rechargeable batteries & charger included. Micro-computer tuning 0.5µV sensitivity **£89** + crystals **£2.80 ea.**

MARINE/AMATEUR (VHF)

Search SR9 - fully tuneable coverage - provision for 11 crystals. Fine tuning and Squelch controls. 12Vdc supply. **EXCELLENT VALUE at only £46**

DAIWA SR11 - fully tuneable coverage plus 6 channel scanning facility giving tune/scan/manual modes of operation. Variable squelch control. 12V d.c. supply. **£78** + crystals **£2.80 ea.**

Belcom AMR217B - automatically scans up to 7 crystal controlled channels with provision for 10 additional fixed channels. 240Vac/12Vdc supply. Incl. 8 channels. **£120**

Lowe DS10 portable, 10 crystal controlled channels automatically scanned. Rechargeable batteries & charger included. Telescopic aerial **£75** + crystals **£2.80 ea.**

SYNTHESISED SCAN - AIR/MARINE ETC

SX200N - The ultimate scanner for 32,000 channels covering 26-88, 108-180, 380-514MHz AM and FM, 16 memory channels, 2 speed scan, 3 squelch modes & Digital Clock display. Listen to 10m-70cm Amateur, Aircraft, and Marine Bands 240V a.c./12V d.c. supply. **New version with improved filters etc. ALL FOR ONLY £264.50**

Bearcat 220FB - fully synthesised Scanner covering 66-88, 144-174, 420-512MHz FM plus 118-136MHz airband. 240Vac/12Vdc supply. **Catronics Price £258**

Regency K100 - fully synthesised to search 30-50, 144-174, 440-512MHz + 10 selectable scan channels. 240V ac/12V dc. **SPECIAL OFFER: ONLY £170**

Additional crystals for above receivers: Airband & Marine, £2.80; Amateur, £2.40.

All prices include VAT but add carriage: Mains receivers, £5.50; others £1.50.

EASY TERMS available. Access and Barclaycards welcome

Catronics LTD.

COMMUNICATIONS HOUSE,

(Dept. 189) 20 WALLINGTON SQUARE,
WALLINGTON, SURREY, SM6 8RG.

Tel. 01-669 6700 (9 a.m. to 5.30 p.m. Sat 1 p.m.) Closed lunch 12.45-1.45

Photo Acoustics Ltd

MICRO COMMUNICATIONS DIVISION

Number ONE for:-

**TRIO
ICOM
YAESU
and
FDK**



TR9000

SOUND ADVICE!

Talk to our
experienced
Staff—

G3TGE - DEREK
G3TLE - ROY
G8PWS - STEVE
G8BNR - DICK



TS830S

58 HIGH ST., NEWPORT PAGNELL
BUCKS. TEL: (0908) 610625

255a ST. ALBANS RD.,
WATFORD. TEL: 32006



CREDIT CHARGE
MAIL ORDER



Time Signal Stations

The reference to these stations in the July issue prompted reader **Alan Procter** of Bristol to reply. Alan uses a Drake R7 receiver with 30 metre longwire and he reports that CHU in Canada can also be heard on 3.33MHz in the 90m band when Radio Rwanda on 3.30MHz is off the air. ZSC in Cape Town is recognisable regularly on the three higher frequencies which are 22.245MHz, 17.018MHz and 12.724MHz, mainly because of their distinctive brief transmissions. JJY in Japan comes through occasionally on 10MHz and 15MHz.

DX Heard

An R1000 receiver and 30 metre longwire with antenna tuning unit (a.t.u.) are in use by **Jim Edwards** who prefers this receiver to the FRG7 on account of the narrower filters (better selectivity). He mentions hearing Paramaribo on 4.85MHz at 0415 and Apite on 5.005MHz at 0615, both stations being in Surinam on the north east coast of South America. Jim wonders if any reader has heard of a Hartley Tuner which covers the l.w., m.w. and s.w. bands, the valve types being VP4B, TDD4, TH4B, TV4A. Replies direct to Jim please at 7 Clifton Road, Bryn, Nr Wigan, Lancs, WW4 OA2.



QSL card from Denmark received by reader Ken Wilkins. This station broadcasts in Danish only.

More DX comes from **Mathew Phillips** who has come back to DXing after a long break. With his re-aligned HR0, longwire and a.t.u. he pulled in Uruguay on 15.27MHz at 0020, Radio Gobo Brasil on 15.265 MHz at 0015, Radio el Mundo Argentina on 15.290MHz at 0040 and Radio New Zealand on two channels, 15.485MHz at 0810 and 11.945MHz at 0830, plus an unidentified on 10.005MHz at 1745 with either Arabic or Indian music. Mathew is looking for the 1.7 to 4MHz coil pack for his HR0. Anyone who can help can contact him at 4 Nether Court, Halstead, Essex, CO9 2HE.

Readers' Letters

The confusion, in my mind at least, between the Voice of Hope and the Voice of Peace has been cleared up by **Gavin Robertson** of Edinburgh. The Voice of Hope is the short wave service of a station which also operates a m.w. and TV station in Israeli occupied Lebanon. The station will verify reports as Gavin received a QSL card recently from Hotel Arazim, Metulla, Israel, and there is also an American address which is PO Box 7466, Van Nuys, California 91409, USA. This station has been heard on 6.215MHz. The Voice of Peace broadcasts from a coaster off Tel Aviv on 1530kHz medium wave and their address is PO Box 4399, Tel Aviv, Israel.

Gavin edits a section of "Communication" which is the monthly journal of the British DX Club. A sample copy can be obtained for return postage from the club secretary at 55 Boudary Rd., Worthing, West Sussex, BN11 4LL.

Practical Wireless, September 1981

VHF Bands

by **Ron Ham BRS15744**

Reports to: **Ron Ham BRS15744**
Faraday, Greyfriars, Storrington,
Sussex RH20 4HE.

Although I spent most of June 7th at the Chalk Pits Museum and missed all the fun, I heard from one of my readers that there were so many stations on 2m, due to a tropospheric opening, that he had great difficulty in working the extra DX caused, in the late afternoon, by an extensive Sporadic-E and as it turned out, this was only one of several DXy days during the first three weeks of June.

Solar

Both **Cmdr Henry Hatfield**, Sevenoaks, and I recorded a solar noise storm, at 136 and 143 MHz respectively, between May 18 and 22 and individual bursts of noise on May 27 and June 12 and 16. Despite the poor weather conditions **Ted Waring**, Bristol, did get a few glimpses of the sun and counted 60 sunspots on May 16, 35 on the 19th, 8 on June 3, 14 on the 9th and 28 on the 13th.

The 10m Band

Conditions were generally poor for h.f. and for long periods on many of the 34 days between May 18 and June 20, 10m was completely dead, not even a beacon signal broke the silence, a point confirmed by a near neighbour of mine, **Ron Munn G2ALO**. During the 34 days, I heard signals, at varying strengths, from the International Beacon Project stations in Australia VK5WI on 3 days, Bahrain A9XC on 16 days, Bermuda VP9BA on 2 days, Cyprus 5B4CY on 20 days, Germany DL0IGI on 16 days and DK0TE on 3 days, Mauritius 3B8MS and Norway LA5TEN on 5 days, South Africa ZS6PW on 8 days and Venezuela YV5AYV on 3 days. Ted Waring's beacon log, covering the period May 15 to June 14, is similar to mine and we both found that 5B4CY was the most consistent beacon signal on the band. Despite the poor conditions I did hear signals from amateur stations in Australia on May 30 and June 1 and 13 and from Japan on May 29 and June 5.

RTTY

Earlier this year, **Jim Usher** RS46955, Bournemouth, began listening on the amateur bands and now has a Yaesu FRG7700 receiver fed by two long-wire antennas and a MM2000 RTTY unit feeding its signals to a Binatone 12 inch TV receiver. Jim has enrolled on an RAE course and hopes to take the exam in December. Good luck to you Jim and congratulations to G8PWX, Newcastle-on-Tyne, who, between 2000 and 2100 on June 21 almost certainly put up a first, when he made a RTTY contact with LA3EQ on 70cm and to G8RBY, Melton Mowbray, who established another possible first soon after, by working the Norwegian station on 2m RTTY. Between May 18 and June 20 I logged 60 RTTY stations on 20m spread over 12 countries, CN, DJ, EA, F, HA, I, LA, OE, OH, OZ, SM and UK and at 1400 on May 20, I copied both sides of a QSO between OE8LKK and OH2HN and at 1308 on June 12 I logged DL3WL calling CQ DX giving me my first RTTY signal on 10m.

Sporadic-E

During an extensive Sporadic-E disturbance on 2m around 1730 on June 7, **Phil Hodson**, G8RBY, Melton Mowbray, heard

AMATEUR ELECTRONICS UK



Your number one source
for **YAESU MUSEN**



NEW **FT-101ZD**
Mk. III

Now from YAESU comes the latest version of the renowned FT-101 - AM/FM option, notch filter, audio peak filter, variable bandwidth - UNBEATABLE VALUE. **£599.00**

FT-480R High technology all-mode 2 metre mobile



The most advanced 2 metre mobile available today - USB, LSB, FM, CW full scanning with priority channel, 4 memory channel, dual synthesized VFO system. **£359.00**

FT-707 All solid-state HF mobile transceiver

£529.00



The definitive HF mobile rig, digital, variable IF bandwidth, 100 watts PEP SSB, AM, CW (pictured here with 12 channel memory VFO).

FRG-7 General coverage receiver

A precision built high performance Wadley Loop receiver, rugged and reliable - proved by the tens of thousands in use around the globe.



£199.00

FRG-7700 Synthesized general coverage receiver

The very latest in receiver technology from YAESU. Receives AM (3 band widths), USB, LSB, CW and FM - memory option with 12 channels and automatic band selection.



£309.00

ALL PRICES INCLUDE V.A.T.

Amateur Electronics UK

508-516 Alum Rock Road - Birmingham 8
Telephone: 021-327 1497 or 021-327 6313
Telex: 337045

As from March 1st, our new opening hours are
9.30 - 5.30 Tues. to Sat. continuous and CLOSED all day Monday.

AGENTS

NORTH WEST - THANET ELECTRONICS LTD, GORDON, G3LEQ, KNUTSFORD (0565) 4040.
WALES & WEST - ROSS CLARE, GW3NWS, "GLENVIEW" NEWPORT ROAD, MAGOR, GWENT (0633) 880 146.
EAST ANGLIA - AMATEUR ELECTRONICS UK - EAST ANGLIA, DR T. THIRST (TIM) G4CTT, NORWICH 06325 805
NORTH EAST - NORTH EAST AMATEUR RADIO, DARLINGTON 0325 56989
SOUTH EAST - AMATEUR ELECTRONICS, UK - COASTAL, CLIFTONVILLE, KEN) KEN McINNES, G3FTE, THANET (0643) 291297, 9 a.m. 10.30 p.m.

a station in Poland and worked another in Russia, **John Cooper**, G8NGO, Cowfold, worked 4 SPs and 1 UB. **J.R. Matthews**, G3WZT in nearby Partridge Green, worked 2 UCs, 2 UBs and a SP and another Sussex station, **Harold Goble**, G4FDQ, Lancing, worked 70 year old **Edward Kawczynski**, SP8CK, who has been on the air since 1929 and was as pleased as Harold was to make the contact because it was his first 'G' QSO on 145 MHz. For most of June 9, all bands from 28 to 100 MHz were disturbed by Sporadic-E and although the 10m band was quiet, I received 599 signals from DLOIGI and DK0TE and 559 signals from LA5TEN. During the afternoon, **Barry Ainsworth**, G4GPW, Lancing, heard 599 plus signals from ZB2VHF on the 6m band. **Walter Carmichael**, a member of the British DX Club from Haywards Heath, Sussex, using a Technics ST8044L tuner and a 3-element beam, heard strong signals in Band II from broadcast stations in Yugoslavia and like myself heard orchestral music on 101 MHz frequently interrupted by the announcement—"This is a test transmission from the Belgian Radio Television, in co-operation with mobile services in the United Kingdom. The frequency is 101 MHz"—any ideas? **Ken Smith**, BRS20001 also heard the Yugoslavian stations among the many continentals in Band-II and at midday both **Harold Brodribb** and I counted 31 east-European broadcast stations between 66 and 73 MHz and at 1845 most of them were still there and exceptionally strong. "This was the most remarkable v.h.f. opening I have ever heard" said Harold who like many other readers sent me a detailed report. Similar, but some less intense disturbances occurred on May 21 and 26 and June 2, 8, 10, 11 and 12 when, at the peak of each event I counted 18, 13, 33, 27, 34, 54 and 12 east-European stations respectively, between 66 and 73 MHz. **Edward Baker**, Cramlington, Northumberland, also logs these broadcast stations with a Hallicrafters communications receiver and **R.C. Taylor**, Glasgow, using an Armstrong 624 and a temporary indoor antenna for Band II, heard Italian stations at 1650 on June 2nd, Spanish stations between 1807 and 1936 on the 8th and Yugoslavian between 1805 and 1835 on the 11th. It is important for readers to keep in mind that the propagation of radio signals in Band II (88-108 MHz) can be influenced by both Sporadic-E and tropospheric openings and it is not unusual to have both together during the mid-summer months.

Tropospheric

The atmospheric pressure remained steady at 30.0 inches (1015mb) from midday on June 2nd to noon on the 7th and, true to form, as it fell, a v.h.f. opening occurred and G4DFQ with his Multi 800D and a Ringo Ranger Colinear antenna worked into Dorset, London and France on 2m f.m. from his home in Lancing. During the morning of the 7th, **John Williams**, Cheltenham, was listening to Radio 3 f.m. and became aware of other music breaking through, so he tuned his Fidelity RAD 26, with its telescopic antenna, higher in frequency and heard flamingo style music from a Spanish station and later in the day G8NGO worked stations in DL, F, G, GJ, HB9, ON and PA on 2m s.s.b. The pressure began to rise again at midday on June 12 and after reaching a peak of 30.4 inches (1029mb) at 0800 on the 13th the v.h.f.s opened and as the pressure fell, **Mike Rowe**, G8JVE, Chichester, worked many French stations on the Mediterranean coast and stations in EA, HB9 at 20 over S9, ON and PA0 on 2m s.s.b. **Gloria Hills**, G8ZYL, Gillingham, worked several ONs around 2300 and earlier at 2045, **Alan Baker**, G4GNX, Newhaven, worked EA1XH with 59 signals, like Gloria on 2m s.s.b. As usual **Simon Hamer**, Presteigne, sent an interesting log for Band II covering the openings on May 24 and 29 and June 4, 7, 12 and 15 when he received signals from stations in Belgium, France, Germany, Italy, Spain, BBC radios London, Medway and Solent and ILR stations Capitol, LBC and Thames Valley. During this DX hunt Simon heard adverts, discussions, pop-music, country and western music, news, jazz, the French national anthem at close-down and a talk about flower pruning. For the past 4 years, **Derek Cooper**, G8CUP and G8KAH, both in York, have kept a regular sked on 144.365 MHz at 1700 on Fridays and Saturdays with PE0RTM and PE1AGN. "We don't always make it, but it's worth trying" said Derek. It sure is Derek because this is one way of learning a great deal about a particular signal path.

Practical Wireless, September 1981

Where are you all?

On June 14, I met husband and wife team Roy and Gloria Hills, G8STO and G8ZYL, at the Chalk Pits Museum and as we sat in the sun and talked about radio Gloria said "from one YL to all the others, where are you? and what about a sked". She often works **Elaine Howard**, G4LFM, our Technical Sub-Editor, and although Gloria is a keen contest worker and DX hunter on 2m she is looking forward to getting her G4 call so that she can chase the DX on the h.f. bands. Both Roy and Gloria are members of the Medway Amateur Receiving and Transmitting Society and are often heard working through the Kent repeater, GB3KN R4. Roy has a great interest in v.h.f. RTTY and uses a Creed 75 printer and BARTG ST5 terminal unit for receiving and a home brew electronic key board for transmitting. At contest time on 2m Roy and Gloria join forces with G4LZV, G4JJX, G8VJU, G8XLH and G8ZTE and as a group they enter the events with the club call-sign G8MWA.

Hard Boiled?

At 2220 on August 26, 1976, a QSO lasting more than 4 minutes took place on 2m s.s.b. between G8EGG in Surrey and G8CUP in York. Later both stations exchanged QSL cards appropriately marked.

News Items

During Sporadic-E events on June 2nd to 8th inclusive, Phil Hodson, G8RBY, heard a Polish voice on 144.596MHz and wonders if this is a harmonic from a broadcast station around 72.25MHz. Any ideas? Can anyone help **Derek Cooper**, G8CUP, QTHR, with a genuine ex-RAF manual, or photocopy, for a R1224 which he is renovating.

Many amateurs from all over the country attended the first meeting of the UK Horizontal FM Group on May 16 when a sound and progressive constitution was formed. The gathering elected **Paul Hancock**, G8UAV, Chairman, **Arthur Dorsett**, G8YLH, Secretary, **Rod Walker**, G8WJF, Treasurer and **Mitch Tribe**, G8PMT, Contest Officer. The group is organising contests, rallies, a field day for the disabled and are applying for affiliation to the RSGB. Further information is available from G8YLH, The Coach House, Dogmersfield Park, Dogmersfield, Hants. The membership fee is £1 per annum and the group net is on Monday, Wednesday and Friday evenings at 1930 BST on 144.670MHz and listener reports, to the secretary, are welcome.

TV
by Ron Ham BRS15744
Reports: as for VHF Bands,
but please keep separate.

It is obvious from my postbag that the number of TV DXers is growing, especially now that several well known Japanese manufacturers are incorporating 625 line Band I and III tuners in their domestic sets. In fact the Sanyo 9300 pn VCR has 8 buttons all capable of tuning through Bands I, III and V. Although it is not always possible to receive the sound on the v.h.f. bands owing to the differing international systems, the DX picture alone can give much pleasure, particularly during an atmospheric disturbance.



Members of the London TV DX Group. T. Ampí (left) with Wendy Evans, George Grzebieniak and Norman Reynolds

Sporadic-E

"Absolutely fabulous conditions on Bands I and II resulting in some really excellent video from many countries" writes Sam Faulkner and that just about sums it up for most of my readers. Although the larger Sporadic-E disturbances occurred on May 21 and 26 and June 2, 7, 8, 9, 10, 11 and 19, there were several short lived events which also produced some good DX on the other days. Detailed information about these events came from David Appleyard, Uppsala, Sweden, T. Ampí, London, Edward Baker, Cramlington, Northumberland, Harold Brodribb, St Leonards-on-Sea, Sussex, Mike Evans, London, Sam Faulkner, Burton-on-Trent, Keith Hamer, Derby, Michael Hahn, Rainham, Essex, Simon Hamer, Presteigne, Wales, Ian Rennison, Horsham, Sussex, Andrew Rogers, Bristol, Philip Sado, London, Garry Smith, Derby, John Thompson, Gillingham, Kent, B. Walsh, Romford and Nicholas Wythe, Folkestone, Kent. Between them they received programmes and test cards from stations in Albania RTS, Austria ORF, Belgium BRT and RTBF, Bulgaria BT, Czechoslovakia CST-O1 and TN, Finland YLE-HLKI, East and West Germany DDR-F and ZDF respectively, Holland NED-2, Hungary MTV and MTU-1 Budapest (Fig. 2), Iceland RUU, Italy RAI, Norway NRK, Gulen, Melhus, Gamlemsveten and Hennes, Poland (Fig. 3) TP and TVP, Portugal RTP, Spain RTVE and Control Central RTVE, Sweden TVI, USSR TSS (Fig. 4) and Yugoslavia JRT (Fig. 5) and RTU. My readers reported seeing adverts for Coca Cola, Fiat cars, Gillette and Kellogg's cornflakes and among the identifiable programmes were American police films with subtitles, Bullfights, Circus, cycle racing, children's specials, cartoons (Figs. 6, 7), dancing, football, a variety of films. T. Ampí watched one from Yugoslavia about Samuel Morse and the Telegraph, news including the landing of the Salyut space-craft, Mr Brezhnev giving out medals, the shots fired at the Queen and the launch of Ariane, motor-cycle racing, Travel (Fig. 8), tennis, and many bits of technical films impossible to identify because very often programmes and test cards, from different stations, are fighting for predominance on the screen. A typical example

of this was seen between 1300 and 1340 on June 11, when rock crushing pictures, often in colour, were received from Iceland and Norway with my beam toward them but when the beam was turned toward Poland, the pictures from Iceland were still strong enough to overpower the Polish signal during periods of deep QSB. Test cards from Poland and Spain were received during the afternoon and early evening of June 19 by Brian Renforth, Chippenham, Wilts. Brian is 15 years old and a keen TV DXer and I look forward to more reports from him in the future.

Tropospheric

At 1530 on June 11, T. Ampí received test cards from Belgium BRT UTU-2 on Channels 25 and 62 and again on the 12th with the addition of RTBF1 on Ch 52. At 2245 on the 12th I saw a clock showing 2345 followed by a test card, BRT UTU-1 on Ch E10. This clock appeared again at 1845, on the 13th, showing 1945 on Ch E10, followed by the news. Toward the end of this mild tropospheric opening, I received strong test cards from RTBF1 on Ch E8 and BRT UTU-1 on Ch E10 at midday on the 15th.

SSTV

Norman Reynolds, G8YXL, London, has installed Slow Scan television equipment and would like to arrange skeds with other SSTV enthusiasts on 2m. So far, using his Trio communications receiver and a Robot 400 SSTV converter, Norman has received pictures from France, Germany, Spain, Switzerland and the USA. Despite the poor conditions on 10m, Sam Faulkner managed to log signals from DL, EA, I7, LU, OH, ON, W1, WO and ZS6 between May 14 and June 10, using mainly the 28-680MHz calling channel. Signals from EA8RX showing pictures of himself, equipment and various circuits were excellent during the evening of May 17 Sam told me and at 1716 the EA worked WDOFNL. Later Sam saw a portrait of ZS6BFU while he was in QSO with a W and said that European SSTV stations were received during the Sporadic-E disturbances on May 31 and June 7 and 8. He also received SSTV pictures from JAIDEQ and JAIPGH which he stored on audio cassette tape (Figs. 9, 10).

Equipment

Among my new contributors, Mike Evans is using a 5in National Panasonic 5060 fed with a 6-element antenna for Band I, a 3-element for Band III and a 91-element for u.h.f., all driven by a Stolle 2010 rotator. Andrew Rogers has a Teleng up-converter and a 3-element wide-band antenna and John Thompson uses a JVC 3040 and Practical Wireless wide-band preamp fed with an 'H' aerial for Band I, a 9-element for Band



SSTV equipment installed by Norman Reynolds G8YXL



Fig. 2 (N. Wythe)

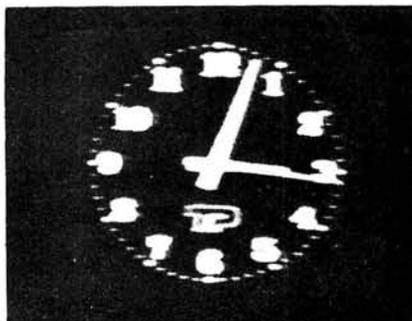


Fig. 3 (N. Wythe)

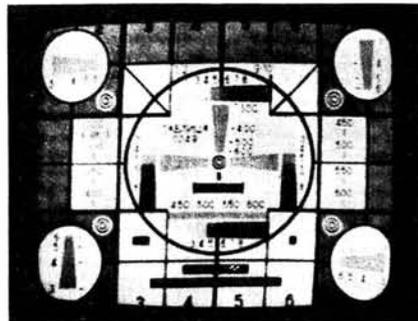


Fig. 4 (N. Wythe)



Fig. 5 (N. Wythe)

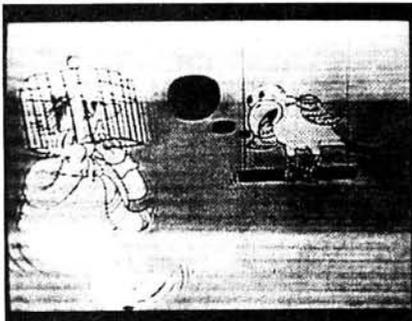


Fig. 6 (R. Ham)



Fig. 7 (R. Ham)



Fig. 8 (R. Ham)



Fig. 9 (S. Faulkner)



Fig. 10 (S. Faulkner)


III and should by now be using a JVC CX610GB colour set. Edward Baker tunes the Band I TV sound channels on a Hallicrafters SX62A communications receiver and for vision he uses a Baird TV receiver fed with a Band I dipole. B. Walsh began TV DXing last September and now uses a varicap tuner via a 'G8' selectivity module into a Rank TV161 receiver fed with crossed dipoles in the loft and Brian Renforth feeds one of Hugh Cocks's converters into a Baird 8807 receiver fed by an 'X' antenna for Band I, a 6-element Yagi for Band III and a 43-element Fuba for u.h.f.

"Pause"

My thanks to J.F. Coulter, Winchester, Harold Brodribb and B. Walsh for telling me that the caption "PAUZE" I referred to in my July column is most likely to come from a Dutch station meaning pause or break.

Finally I apologise for putting the wrong caption on Fig. 4 in my July column; this should have been Rumania and not Italy as I said.

PW EXE PARABOLIC DISH OFFER

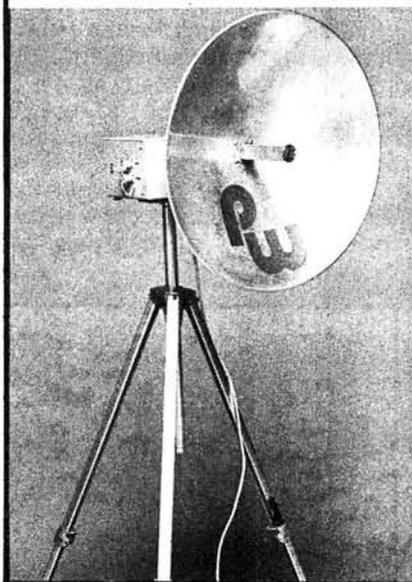


The antenna system designed for the PW Exe uses a specially designed and spun aluminium dish and arrangements have been made for the supply of this special item to our readers.

Although designed primarily for the PW Exe project, this 128mm focal length, 460mm black anodised aluminium parabolic dish should be useful for many other projects in the future, some of which are more than just "pie in the sky".

The special offer price is £7.50 if collected direct from PW offices. Post and packing is £2.00 for one dish and £2.50 for two dishes. Please make your cheques or postal orders payable to IPC Magazines Ltd.

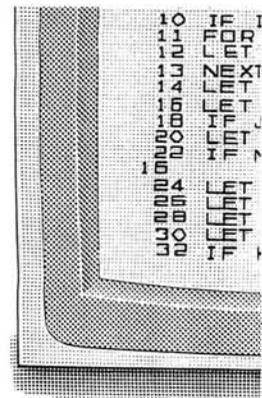New! Sinclair ZX81 Personal Computer. Kit: £49.⁹⁵ complete



Reach advanced computer comprehension in a few absorbing hours

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. At £99.95, the ZX80 offered a specification unchallenged at the price.

Over 50,000 were sold, and the ZX80 won virtually universal praise from computer professionals.

Now the Sinclair lead is increased: for just £69.95, the new Sinclair ZX81 offers even more advanced computer facilities at an even lower price. And the ZX81 kit means an even bigger saving. At £49.95 it costs almost 40% less than the ZX80 kit!

Lower price: higher capability

With the ZX81, it's just as simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8KBASICROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, or to select a program off a cassette through the keyboard.

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

Proven micro-processor, new 8KBASIC ROM, RAM – and unique new master chip.


**Built:
£69.⁹⁵
complete**



Kit or built – it's up to you!

The picture shows dramatically how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

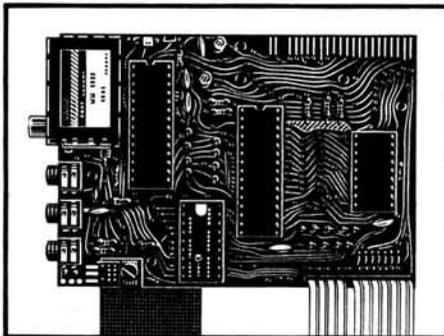Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



New Sinclair teach-yourself BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs. You need no prior knowledge – children from 12 upwards soon become familiar with computer operation.



```

N IIR I=N THEN GO TO 6
=1 TO N
(X)=I(I(X))
X
=0
=J+1
N OR J=N THEN GO TO 48
=J+1
T R(J)R(T) THEN GO TO
P R(J)
R(J)=R(T)
(T)=P
=J-1
1 THEN GO TO 16

```

If you own a Sinclair ZX80...

The new 8K BASIC ROM used in the Sinclair ZX81 is available to ZX80 owners as a drop-in replacement chip. (Complete with new keyboard template and operating manual.)

With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 – including the ability to drive the Sinclair ZX Printer.

Coming soon- the ZX Printer.

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumerics across 32 columns, and highly sophisticated graphics. Special features include COPY, which prints out exactly what is on the whole TV screen without the need for further instructions. The ZX Printer will be available in Summer 1981, at around £50 – watch this space!



16K-BYTE RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.



How to order your ZX81

BY PHONE – Access or Barclaycard holders can call 01-200 0200 for personal attention 24 hours a day, every day.
BY FREEPOST – use the no-stamp-needed coupon below. You can pay by cheque, postal order, Access or Barclaycard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.

- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.

- Unique syntax-check and report codes identify programming errors immediately.

- Full range of mathematical and scientific functions accurate to eight decimal places.

- Graph-drawing and animated-display facilities.

- Multi-dimensional string and numerical arrays.

- Up to 26 FOR/NEXT loops.

- Randomise function – useful for games as well as serious applications.

- Cassette LOAD and SAVE with named programs.

- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.

- Able to drive the new Sinclair printer (not available yet – but coming soon!)

- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.

sinclair ZX81

Sinclair Research Ltd,
 6 Kings Parade, Cambridge, Cambs.,
 CB2 1SN. Tel: 0276 66104.
 Reg. no: 214 4630 00

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY.

Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack(s).	18	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt **TOTAL £** _____
 *I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ _____
 *Please charge to my Access/Barclaycard/Trustcard account no. _____

 *Please delete/complete as applicable. Please print.
 Name: Mr/Mrs/Miss _____
 Address _____

FREEPOST – no stamp needed. PRW09

ELECTROVALUE

BEST SELLERS...

RECHARGEABLE CELLS by SANYO-CADNICA size AA 89p, C 2.27, D 3.76, PP3 4.10 with lugs; AA 1.06, C 2.43, D 3.99, CHARGERS PP3 4.75, AA 4.95, A, C or D 7.60.

PLASTIC BOXES PB1 116 x 77 x 35 mm 62p, SMALL ALU BOXES FROM 55p.

BREADBOARDS Euro 5.70N, Verobloc 2.63, Bimboard 8.03 BUZZER 6-15V 80p.

CAPACITORS polystyrene 47-4700pF each 7p, C280 0.01-0.22 6p, 0.033-0.11 7p, 0.22 9p, 1µF 26p, Polyester (PCN7.5 mm) 0.001-0.0033 6p, 0.0047 7p, 0.056-0.066 8p, 0.082-1 9p, 0.22 12p, Variable, Dilecon 1000F 2.08, 5000F 3.21, Electrolytic µF/N 1/63, 2/263, 4/740, 10/25, 22/10 a 10p, 10/40, 22/25, 22/40, 47/25, 100/10 a 11p, 2/25, 100/16, 100/25, 100/40, a 13p, 220/25, 470/16 or 25 a 16p and many, many other values and types. 6000 quantity DISCOUNTS.

CONNECTORS 1/2 Jack plug 32p, skt 12p, 3.5 mm jackplug 17p, skt 14p, 2.5 mm 12p, DIP header 14 pin 38p, 16 pin 43p, 24 pin 77p, Quick-test mains block 5.25, D-type 25 way plug 1.50, skts 2 18, hood 1.52, UHF plug 40p, skt 40p, BNC plug 75p, sg, skt, 64p, Din 2 pin plug 8p, skt 8p, 5 pin 180° 17p, skt 8p, 6 pin plug 18p, skt 14p, Fuse holders 20 mm panel 22p, chassis 6p, 1 1/2 panel 40p, Chassis 13p, Fuse links from 3p.

HARDWARE large range of nuts, screws, spacers, washers, brackets etc. Etc. Heat sinks T03 25p, T05 12p, T06 27p, T0220 25p, T01 12p, large 2 x T03 from 1.72.

INTEGRATED CIRCUITS Hundreds of types. 741 18p, 555 23p, CA3140E 40p, LM380N 95p, S5668 2.14, TC965 1.20, Ken logic IC prices.

IC holders 8 pin 5p, 14-40 pin 1p per way. **QUANTITY DISCOUNTS.**

KNOB Screw fitting 1/2, pointers from 15p, skirted from 16p, collet from 38p.

LOUDSPEAKERS 2 1/2" 8 or 64 ohms 93p, 1 1/2" 98p, **MAGNET** 1" x 1/2" sq 40p.

MAGNET resistors from 1.60N. Multimeters FULL ICE range & accessories. Meters, panel 60 x 45 mm 50, 100, 250, 500µA, 1, 5, 10, 50, 100, 500mA, 1A ea 4.80.

Test leads 70p pr. Test leads from 1.40 pr.

OPTOELECTRONICS LED's red 7p, yellow 9p, green 11p, ultra-bright all colours ea 21p.

18 T8xR pair TIL32 & TIL78 42p each.

POTENTIOMETERS carbon 20 mm dia 100R-2M2 lin, 220R-4M7 log single ea. 29p. 1K-2M2 lin, 4K7-2M2 log duals ea 81p. Add 51p if required with switch.

Sliders mono 72p, stereo 1.18, bezel 34p. Wirewound 25R-10K 3 watt ea 1.50.

PRINTED CIRCUIT MATERIALS 300 x 150 mm clad SFRP 1.25, Fibreglass 1.90. 500 gm ferric chloride labgrade 3.40, Positive 20 photo resist 75 ml 1.65. Etch resist pen 1.05, silver paint 3 gm 4.14N. RELAYS 12V coil 3P2W 10A contacts 2.90.

RESISTORS 1W, 1/2W, 1/4W ea 2p. Metal oxide TR5 2% 5p, film MR25 5p.

SEMICONDUCTORS examples from large range IN4007 6p, IN4148 3p, RCA2N3055 70p, BC107-9 family 14p, BC182/212 family 9p, BFR34A 63p, BFT65 1.19, TIP31A/24 ea 44p, TIP41A/24 ea 55p, TIP255/3055 ea 59p.

POWER DARLINGTONS 300V TIP150, 350V BU124 85p, 600V BU181 1.75.

THYRISTORS 400V TIC106D 5A 38p, TIC126D 12A 60p.

TRIACS 400V TIC206D 4A 48p, TIC226D 8A 55p, TIC236D 12A 85p, TIC246D 16A 95p.

SOLDER 500 gm 60/40 20SWG 7.30N & MULTICORE range.

IRONS anti-C, CCN, CX or X25 ea 4.00N. Dvys 50 temperature controlled 11.50N. 150 WTP cordless with charger 24.00N. Dvys SOLDER SUCKER 6.00N.

SWITCHES slider DPDT min 18p std 20p, Wavechange IP12W, 2P6W, 3P4W, 4P3W ea 40p. Time switch 13A 3 on 3 off per day 14.68N. Min toggles silver contacts SPDT 57p, DPDT 80p, SPDT 1.64, 4PDT 2.75, DIL gold plated 4PST 95p, 10PST 2.10.

TITAN mini drills 12Vdc 10.28N, drill kit 12.06N. Drill stand 12.00N.

PLIERS CX 4.70, cutters 6.10, wire strippers 4.95 MICROSEAR 2.10. Vero wiring system kit 4.42, extra wire 1.17 per two-reel.

COMPUTERS NASCOM & GEMINI ranges. MICROVALUE add-ons & software.

BEST SERVICE

★ **KEEN BUYERS!** A S.A.E. BRINGS COMPREHENSIVE PRICE LIST (Valid 3 mths.) COVERING CATALOGUE '81. ACCESS AND BARCLAYCARDS ACCEPTED

★ **EVERYTHING BRAND NEW & GUARANTEED HARD TO FIND ITEMS**

★ **KEEN PRICES & DISCOUNTS**

★ **SPECIAL QUANTITY DISCOUNTS**

★ **SPEEDY TURN ROUND ON ORDERS**

★ **NO P/P CHARGES ON U.K. C.W.D. ORDERS OVER £5.75** (Add handling charge of 40p if under).

★ **PLEASE ADD 15% V.A.T. TO TOTAL VALUE OF ALL ORDERS.**

★ **Shop Hours - 9-5.30 - Sats. 9-1 pm.**

ELECTROVALUE LTD. DEPT. PWS, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB.
Phone Egham 33803 (STD 0784 - London 87). Telex 284475
Northern Branch (Personal Shoppers only) 880 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

MARCO TRADING

ZENER DIODES: 400mw, 3V to 33V 8p each, 100 for £6.00 (your mix). 1 Watt, 3V to 200V 15p each, 100 for £12.50 (your mix).

I.C. SOCKETS: 6 pin a 7p, 8 pin a 8p, 14 pin a 10p, 16 pin a 11p, 18 pin a 13p, 20 pin a 16p, 24 pin a 20p, 28 pin a 28p, 40 pin a 32p. **QUANTITY PRICES ON APPLICATION.**

RESISTORS: 1W, Low Noise, High Stab. 5% Tolerance, Carbon Film, E12 Series, 2.2 ohm to 10M 2p each, 15p/10, 100 for 95p, 1000 mixed in 100's only £8.00.

SPECIAL RESISTOR PACK: 10 of each value 2.2Ω to 2MΩ, 730 resistors only £6.00. Amazing value. 1W Resistors, E12 range from 2.2 ohm to 10M. All 5%. 5p each. 2W Resistors, E12 range from 100 ohm to 10M. All 5%. 8p each.

CERAMICS: 83V Working. Subminiature, Low Tolerance, 1/8W 100nF 4p each.

TANTALUMS: 35V, 0.1µ, 0.15µ, 0.22µ, 0.33µ, 0.47µ, 0.68µ, 1.0µ a 12p each, 2.2µ, 3.3µ, 4.7µ, 6.8µ, 35V a 14p each, 10/35V 18p, 22/35 38p, 47/10V 25p, 33/10V 25p, 100/3V 20p, 68/3V 20p each.

L.E.D.s: 3mm RED 12p each, Green 18p each, Yellow 18p each, incl. Clips. 5mm RED 12p each, Green 18p each, Yellow 18p each, incl. Clips. 100 RED (3 or 5mm) for £5.50 excluding Clips.

SKELETON PRE-SETS: 1000 to 1M Vertical & Horizontal, all a 6p each, 100 (your mix) for £4.50. **BRIDGE REC'S:** 1A 50V 36p, 2A 200V 44p, 25A 50V £2.38, 25A 100V £2.41.

TRANSISTORS: BC107/8/9 10p, BC147/8/9 8p, BC182/3/4 9p, BC172 8p, BF220 28p, BC212/3/4 9p, 212/3/4 10p, BF180/81 28p, AC128 20p, AD161/2 45p, 2N3055 45p, 2N3819 23p, 2N3053 20p, BC125 10p, BF262/3 30p, 1N4001 5p, 1N4007 8p, 741 20p, NE555 25p, LM380 80p.

CMOS 4001B 20p, 4011B 20p, 4076 90p, 4081 20p, ZN414 90p.

ELECTROLYTICS: A is Axial; R is Radial; 1/63C A 7p, 2/25 R 4p, 4/725 R 5p, 10/16 R 4p, 22/16 R 4p, 22/63 R 8p, 25/25 A 3p, 47/16 R 5p, 47/25 A 6p, 100/3 A 5p, 100/16 R 6p, 220/16 A 9p, 470/16 A 12p, 1000/16 A 16p, 1000/63 A 62p, 4700/16 R 55p, 2200/40 A 65p, 4700/63V 76 £1.90.

Brand New 3-channel chart recorders £65.00 (P+P £8)
Multimeters V4324-20,000 O.P.V.
BARGAIN PRICE £11.00 (P+P £1.50)

TRANSFORMERS



British made transformers at very attractive prices.

Primary	Secondary	Current	1+	10+	100+
240v:	4.5-0-4.5v	400mA	50p	45p	35p
240v:	6-0-6v	100mA	58p	52p	43p
240v:	6-0-6v	500mA	65p	60p	48p
240v:	9-0-9v	200mA	75p	70p	58p

EUROPEAN ADAPTORS



Manufacturers note: We can supply FROM STOCK, 1000+ quantities of the above transformers and adaptors below.

These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit the UK shaver socket.

REF.	D.C. Voltage	Current	1+	10+	100+
EOB	4.5V	200mA	50p	45p	32p
EM3	6V	200mA	£1.00	80p	55p
EO9	6V	400mA	£1.50	£1.25	85p
ET4	9V	150mA	£1.50	£1.25	85p

Please note that there is no extra P/P charge on the above transformers & adaptors. Export please add Sea/Air mail at cost. Callers welcome Mon-Fri 9-5.

This advert is only a fraction of our range, send 25p for our latest catalogue. Please add 35p P/P to all orders. (Free over £5.00). Add 15% VAT to total. Send orders to:
Dept. PWS, MARCO TRADING,
The Old School, Edstaston, WEM, Shropshire SY4 5RJ.
All orders despatched by return of mail. **Tel: (094872) 464/465.**

SOUND INVESTMENT



Replacement tape heads from Monolith could mean a big improvement in sound quality from your tape recorder. A full catalogue is available, price 50p, which features a wide range of heads for cassette and reel to reel machines, as well as replacement motors, tape transports, etc.

Universal cassette heads to EIAJ standard, hole centres 17mm apart, 12mm from head face:

B12-02	Mono record/playback	£ 4.62
B24-01	Stereo playback	£ 4.62
B24-02	Stereo r/p	£ 7.66
B24-07	Stereo r/p for Dolby systems	£ 9.05
C42RPH02	Stereo r/p sendust head, suitable for chrome & metal tapes	£10.67
C42RPH04	Stereo r/p glass ferrite, the ultimate long life, high performance head	£13.34
C42RPS18	Stereo twin gap r/p long life head for record monitoring	£28.99
C21ES18	Mono/Stereo erase head	£ 2.13
C44RPH03	Four channel/track r/p	£15.15
C22ES04	Twin half track erase	£ 5.43

Ex stock deliveries, all prices include VAT. Post and packing 40p.

MONOLITH

electronic products

The Monolith Electronics Co. Ltd., 5/7 Church Street, Crewkerne, Somerset TA18 7HR. Tel: 0460 74321. Telex: 46306 MONLTH G.

MODULAR ELECTRONICS

95 HIGH STREET SELSEY, Nr CHICHESTER, SUSSEX. TEL: SELSEY (024361) 2916
DISTRIBUTOR FOR SOLID STATE MICROWAVE (THOMPSON-CSF) RF PRODUCTS. GBROS

Type	P/wt	Gain	Volts	Freq.	Price
2N3866	1w	106B	28	175MHz	£0.82
2N4427	1w	106B	12	175MHz	£1.06
2N3553	2.5w	96B	28	175MHz	£1.17
2N5913	2w	74B	12	470MHz	£1.81
2N1127	4w	124B	12	175MHz	£2.42
2N6080	4w	124B	12	175MHz	£4.72
2N1143	10w	104B	12	175MHz	£6.80
2N6081	15w	63B	12	175MHz	£7.48
2N6082	25w	574B	12	175MHz	£8.83
2N6084	40w	454B	12	175MHz	£12.85
SD1428	45w	654B	12	175MHz	£13.28
SD1416	70w	674B	12	175MHz	£24.15
SD1477	100w	804B	12	175MHz	£28.75
2N5590	10w	524B	13.6	175MHz	£6.33
2N5911	25w	444B	13.6	175MHz	£7.48
2N5944	2w	96B	12	470MHz	£4.78
2N5945	4w	86B	12	470MHz	£8.83
SD1135	5w	754B	12	470MHz	£5.20
SD1136	10w	64B	12	470MHz	£7.77
2N5946	10w	96B	12	470MHz	£10.93
SD1088	25w	644B	12	470MHz	£18.40
SD1089	40w	434B	12	470MHz	£25.30
SD1434	50w	604B	12	470MHz	£28.45

ITT 10 7MHz XTL Filters 25KHz £8.05
HP 5082 2800 Hot Car Diodes £1.12
HP 5082 2835 Hot Car Diodes £0.98
HP 5082 3080 Pin Switch Diodes £0.98
Motorola MC12013L + 10 Prescaler IC with full data/instructions £11.50
DBI103 Varicap Diodes £0.50
TIP33 £0.58; 2N918 £0.50; BF180 £0.50; BF115 £0.50; 2N5179 £0.82; BF909 £1.15; ST1210 100MHz/2N2369a £0.30.

TRIMMERS
Tetter PTFE 1 10pF 33p, 7mm or Stripline. DAU PTFE Film 1 9pF or 15 18pF 2Bcs. Surplus 2.5-25pF 10mm 15p.
SPRAGUE (Grade 1) Mica Trimmers (500v) for R.F. Amps. 2.5-75pF 81p, 4-20pF 85p, 7-40pF 88p, 16-100pF 98p, 25-150pF £1.09, 40-200pF £1.15.

HEATSINKS single sided ideal for RF amps. Redpoint GM1 2.6 deg/w £1.90.
Radiospares 4 Deg/w 100mm long £1.00.

FINISHED MADE UP AND TESTED EQUIPMENT

PA2 Preamplifier for 2 meters, using the latest UHF stripline MOSFET the BF900 1 1/2" square for fitting in the rig 50Q in/out imp. Only £8.05 with instructions.
PAU2 432MHz Preamp. stripline using the BFR34a 14dB gain N/F < 2dB £8.63.

LOW NOISE SMALL SIGNAL SEMICONDUCTORS.

BR90 Mul T Pack 2.5dB N/F 1GHz	£2.82
BFR91 Mul T Pack 2.5dB N/F 1.2GHz	£3.45
BFR34a T Pack 4dB N/F GHz	£2.25
BFT66 Low Interm. T072	£2.59
SD306 "D" MOS MOSFET	£2.60
40673 RCA MOSFET	£0.92
BF900 UHF MOSFET Equiv 3SK88	£1.30

LINEAR AMPLIFIER MODULES. without Ch/Over. Size 55x92mm with thermal interface 50Q.
PM2 10 0.4w in 10w out 13.8v £18.40
PM2 15 1.5w in 15w out 13.8v £19.55
PM2 25 4w in 25w out 13.8v £20.99
CPM LINEAR AMPS with full RF Changerover size 82x102mm preamp can be fitted in RX.
SPEC. AS FOR PM Series. Specify CPM type and add £7.48 to PM series prices.

UNELCO Cased RF Mica Caps. Following Pfs
10/20/30/40/50/60/70/80pF £1.81; 100/150/180/200pF £1.73; 1000pF £1.84.
PTFE Sheet 0.25mm 300mm Square £2.30
PFE 951 170 12V Aerial Releas. SPST. Good to 1296MHz £2.50
Silver Plated RG43 Type £8.60

Barclaycard or Access on orders above £10.
POST AND PACKING ADD 50p TO ALL ORDERS.
Orders sent 1st Class Post where weight permits.
SAME DAY DISPATCH ON ALL IN STOCK ITEMS.
Minimum invoice order to approved customers £15.00.
ALL PRICES NOW INCLUDE VAT AT 15%.

CHATTER-BOXES SERVED HERE.



Realistic is the biggest name in Citizens Band Radio and accessories – and you will be able to buy the full range at Tandy – the world's largest retailer of CB equipment!

REALISTIC®
CB from Tandy


TTLS BY TEXAS		74221 160p		74LS192 140p		74C157 250p		LINEAR I.C.s		MC1496 100p		TRANSISTORS		TIP41C 78p		2N3866 90p		DIODES	
7400	11p	7497	180p	74251	140p	74LS193 140p	74C160 155p	AY1-0212	600p	MC1340	120p	AC127/8	20p	BFY51/2	22p	2N3903/4	18p	BY127	12p
7401	12p	74100	130p	74259	250p	74LS195 140p	74C161 155p	AY1-1313	600p	MC3360	120p	AD149	70p	BFY56	33p	2N3905/6	28p	OA47	8p
7402	14p	74104	85p	74265	90p	74LS196 120p	74C162 155p	AY1-5050	212p	MC3390	120p	AD161/2	45p	BFY90	33p	2N4036	85p	OA81	15p
7403	14p	74105	85p	74278	290p	74LS201 190p	74C163 155p	AYS-1224A	225p	NE535	130p	BC107/8	11p	BRY39	45p	2N4038	15p	OA85	15p
7404	14p	74109	55p	74279	140p	74LS240 175p	74C164 120p	AYS-1315	600p	NE531	100p	BC109	11p	BU105	190p	2N4050	12p	OA90	8p
7405	18p	74110	55p	74283	190p	74LS241 175p	74C173 120p	AY5-1317	760p	NE543K	225p	BC119	11p	BU108	250p	2N4061/2	18p	OA91	8p
7406	32p	74110	55p	74284	400p	74LS242 175p	74C174 190p	AY5-1320	320p	NE556	250p	BC149	10p	BU208	220p	2N4123/4	22p	OA95	9p
7407	32p	74111	20p	74285	400p	74LS243 175p	74C175 210p	CA5019	80p	NE557	250p	BC157/8	10p	BU205	220p	2N4125/6	22p	OA200	10p
7408	18p	74116	200p	74290	150p	74LS244 190p	74C192 150p	CA3046	70p	NE561B	425p	BC159	11p	BU208	240p	2N4289	20p	OA202	10p
7409	18p	74118	130p	74293	150p	74LS245 290p	74C193 150p	CA3048	225p	NE562B	425p	BC169C	12p	BU406	145p	2N4401/3	27p	OA205	10p
7410	15p	74119	210p	74294	200p	74LS246 290p	74C194 220p	CA3088E	72p	NE566	155p	BC172	12p	MJ2501	225p	2N4427	90p	IN516	7p
7411	24p	74120	110p	74298	200p	74LS257 120p	74C195 110p	CA3088E	72p	NE566	155p	BC177/8	17p	MJ2501	225p	2N4471	60p	IN4148	4p
7412	20p	74121	28p	74365	150p	74LS259 175p	74C221 175p	CA3090A	Q375p	NE567	175p	BC181	11p	MJ2955	100p	2N5087	27p	IN4001/2	5p
7413	30p	74122	48p	74366	150p	74LS298 240p	4000	CA3130E	100p	RC4151	400p	BC187	30p	MJ3001	225p	2N5089	27p	IN4003/4	5p
7414	60p	74123	48p	74367	150p	74LS373 200p	4000	CA3140E	70p	RC8151	750p	BC212/3	11p	MJE340	65p	2N5172	27p	IN4005	6p
7416	27p	74125	55p	74368	150p	74LS374 195p	4001	CA3160E	75p	TBA810	100p	BC214	12p	MJE2955	100p	2N5178	27p	IN4006/7	5p
7417	27p	74126	60p	74369	200p	74LS374 195p	4002	CA3160E	75p	TBA810	100p	BC217	30p	MJE3055	70p	2N5181	27p	IN4007/3	14p
7420	17p	74128	75p	74393	200p	81LS96	400p	CA3160E	75p	TBA810	100p	BC218	11p	MJE3055	70p	2N5194	90p	IN4007/3	14p
7421	40p	74132	75p	74490	225p	81LS97	400p	CA3160E	75p	TBA810	100p	BC219	11p	MJE3055	70p	2N5245	40p	ZENER	2.7V-33V
7422	22p	74136	60p	74 LS	90p	81LS98	400p	CA3160E	75p	TBA810	100p	BC221	11p	MJE3055	70p	2N5296	55p	400 mW	8p
7423	34p	74141	70p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC222	11p	MJE3055	70p	2N5401	50p	1W	15p
7425	30p	74142	200p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC223	11p	MJE3055	70p	2N5457/8	40p	SPECIAL	
7426	40p	74145	90p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC224	11p	MJE3055	70p	2N5460	40p	OFFERS	
7427	34p	74147	190p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC225	11p	MJE3055	70p	2N5460	40p	£10 + 741	
7428	36p	74148	150p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC226	11p	MJE3055	70p	2N5460	40p	£16	
7430	17p	74150	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC227	11p	MJE3055	70p	2N5460	40p	100+ 555	
7432	30p	74151A	70p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC228	11p	MJE3055	70p	2N5460	40p	£20	
7433	40p	74153	70p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC229	11p	MJE3055	70p	2N5460	40p	RCA 2N3055	
7435	35p	74154	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC230	11p	MJE3055	70p	2N5460	40p	BRIDGE	
7438	35p	74155	90p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC231	11p	MJE3055	70p	2N5460	40p	RECTIFIERS	
7440	17p	74156	90p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC232	11p	MJE3055	70p	2N5460	40p	1A 50V 21p	
7441	70p	74157	70p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC233	11p	MJE3055	70p	2N5460	40p	1A 100V 25p	
7442A	60p	74159	190p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC234	11p	MJE3055	70p	2N5460	40p	1A 400V 30p	
7443	112p	74160	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC235	11p	MJE3055	70p	2N5460	40p	2A 50V 35p	
7444	112p	74161	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC236	11p	MJE3055	70p	2N5460	40p	2A 100V 35p	
7445	100p	74162	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC237	11p	MJE3055	70p	2N5460	40p	2A 400V 45p	
7446A	83p	74163	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC238	11p	MJE3055	70p	2N5460	40p	3A 500V 72p	
7447A	70p	74164	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC239	11p	MJE3055	70p	2N5460	40p	4A 100V 35p	
7448	80p	74165	130p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC240	11p	MJE3055	70p	2N5460	40p	4A 400V 100p	
7450	17p	74166	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC241	11p	MJE3055	70p	2N5460	40p	6A 50V 90p	
7451	17p	74167	200p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC242	11p	MJE3055	70p	2N5460	40p	6A 100V 90p	
7453	17p	74170	240p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC243	11p	MJE3055	70p	2N5460	40p	10A 400V 220p	
7454	17p	74172	70p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC244	11p	MJE3055	70p	2N5460	40p	25A 400V 400p	
7460	17p	74173	120p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC245	11p	MJE3055	70p	2N5460	40p		
7470	36p	74174	93p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC246	11p	MJE3055	70p	2N5460	40p		
7472	30p	74175	85p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC247	11p	MJE3055	70p	2N5460	40p		
7473	34p	74176	90p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC248	11p	MJE3055	70p	2N5460	40p		
7474	30p	74177	90p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC249	11p	MJE3055	70p	2N5460	40p		
7475	30p	74178	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC250	11p	MJE3055	70p	2N5460	40p		
7476	35p	74180	90p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC251	11p	MJE3055	70p	2N5460	40p		
7480	50p	74181	200p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC252	11p	MJE3055	70p	2N5460	40p		
7481	100p	74182	90p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC253	11p	MJE3055	70p	2N5460	40p		
7482	84p	74184A	150p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC254	11p	MJE3055	70p	2N5460	40p		
7483A	90p	74185	150p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC255	11p	MJE3055	70p	2N5460	40p		
7484	100p	74186	900p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC256	11p	MJE3055	70p	2N5460	40p		
7485	110p	74187	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC257	11p	MJE3055	70p	2N5460	40p		
7486	34p	74191	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC258	11p	MJE3055	70p	2N5460	40p		
7489	170p	74192	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC259	11p	MJE3055	70p	2N5460	40p		
7490A	30p	74193	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC260	11p	MJE3055	70p	2N5460	40p		
7491	36p	74194	100p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC261	11p	MJE3055	70p	2N5460	40p		
7492A	45p	74195	95p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC262	11p	MJE3055	70p	2N5460	40p		
7493A	45p	74196	95p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC263	11p	MJE3055	70p	2N5460	40p		
7494	36p	74197	80p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC264	11p	MJE3055	70p	2N5460	40p		
7495A	70p	74198	150p	74LS	140p	81LS98	400p	CA3160E	75p	TBA810	100p	BC265	11p	MJE3055	70p	2N5460	40p		
7496	65p	74199	150p	74LS															



MICROWAVE MODULES LTD

**NEW
PRODUCT**

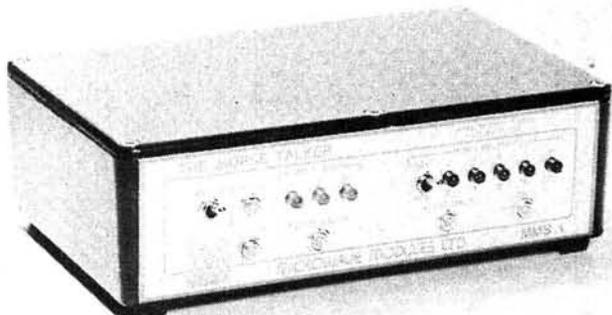THE MORSETALKER THE PRODUCT THAT SPEAKS FOR ITSELF!!



FEATURES

- ★ Complete self contained speaking morse tutor
- ★ Latest state of the art microprocessor speech synthesis system
- ★ Suitable for beginners & proficient operators alike
- ★ Wide speed range: 2-20 WPM
- ★ High speed option: 12-48 WPM
- ★ Variable group length & single character facility

DESCRIPTION

This unique product is a self-contained and SPEAKING MORSE TUTOR and, unlike a random morse generator, the MMS1 incorporates a microprocessor speech synthesis system which provides talk back of the morse after transmission, giving the pupil the opportunity of checking his proficiency. This unit represents a truly cost-effective means of obtaining a full class A amateur licence, without having to rely on a third party for instruction.

The unit requires only a DC power supply, 9 to 13.8 volts, to enable operation and this should be connected to the power socket located on the rear panel via the supplied plug.

To give this product appeal not only to the beginner but also to the proficient operator we have incorporated six 'learning levels'. In this way it is a simple matter to become more and more proficient, even after passing the Morse Test.

The six ranges are:-

LETTERS ONLY	: A-F, A-M, A-U, A-Z.
NUMBERS ONLY	: 0-9
LETTERS & NUMBERS	: 0-Z

Also for each of the above ranges the user can select:-

- | | |
|------------------------------|-------------------|
| 1) One letter | } BEFORE TALKBACK |
| 2) Five letters (One word) | |
| 3) Fifty letters (Ten words) | |

In addition a useful facility is provided in that continuous morse can be sent. (No talkback facility in this mode).

Morse can be sent in the range 2-20 words per minute (w.p.m.) in 2 w.p.m. increments. Speed selection is made by depressing the front panel mounted switch marked 'SPEED SELECT'. However, at speeds of 12 w.p.m. or less, characters are sent at 12 w.p.m. but the spacing is adjusted for the selected speed. In this way morse rhythm will be instilled, since this is the essence of good morse rather than the 'dots and dashes' approach. The incorporation of a crystal-controlled reference ensures totally accurate character and space, lengths and intervals thereby producing a perfect rhythm.

The MMS1 contains an internal loudspeaker which may be supplemented by either headphones or an external loudspeaker, by connection to the socket marked 'EXTERNAL SPEAKER' located on the rear panel. The available audio output level at this socket is 250mW. In addition a tape recorder socket is also located on the rear panel, so that recordings may be made at any time, without disabling the internal loudspeaker.

It is also possible to use the internal sidetone oscillator for sending practice and this may be achieved by connecting a suitable morse key to the socket marked 'KEY'. (N.B. - This facility does not provide talkback).

The MMS1 utilises 2 microprocessors, 2 memory I.C.'s and various other integrated circuits and semiconductors. All circuitry is constructed on high quality glass-fibre printed circuit board, and the unit is housed in a highly durable black diecast enclosure.

Price: £99 inc. VAT.

HIGH SPEED OPTION

As an optional extra an alternative higher speed EPROM memory I.C. can be purchased providing a 12-48 w.p.m. speed range in 4 w.p.m. increments. Also supplied with this EPROM is an easily attachable label to amend the indicated speed range on the front panel.

ALL MICROWAVE MODULES PRODUCTS ARE FULLY GUARANTEED FOR 12 MONTHS (INCLUDING PA TRANSISTORS)



WELCOME

MICROWAVE MODULES
BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND

Telephone: 051-523 4011 Telex: 628608 MICRO G

CALLERS ARE WELCOME, PLEASE TELEPHONE FIRST

HOURS:
MONDAY-FRIDAY
9-12.30, 1-5.00

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or are already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

- Telecommunications Technicians
- Radio, TV Electronics Technicians
- Technical Communications
- Radio Servicing Theory
- Radio Amateurs
- Electrical Installation Work
- Also MPT Radio Communications Certificate

Diploma Courses

- Colour TV Servicing
- Electronic Engineering and Maintenance
- Computer Engineering and Programming
- Radio, TV and Audio, Engineering and Servicing
- Electrical Engineering, Installations and Contracting

Qualify for a New Career

Home study courses for leading professional examinations and diploma courses for business and technical subjects:—

G.C.E.	Engineering	Purchasing
60 subjects	Farming	Sales
at "O" & "A" levels	Heating	Storekeeping
Accountancy	Industrial	Work Study
Air Conditioning	Management	
Building	Mechanical	

POST OR PHONE TODAY FOR FREE BOOKLET.

ICS To: International Correspondence Schools

SINCE 1890
Dept. 276L Intertext House, London
SW8 4UJ or telephone 622 9911

Subject of Interest

Name

Address

Telephone Number


RST

VALVE MAIL ORDER CO.
Climax House
159 Fallsbrook Road, London SW16 6ED
SPECIAL EXPRESS MAIL ORDER SERVICE

AZ31	1-10	EM87	1-50	PY81	0-84	6AN5	4-74	607	2-20
CL33	2-00	EN91	3-50	PY82	0-80	6AN8A	3-45	6SA7	1-45
DY86/7	0-84	EY51	1-75	PY83	0-70	6AQ5	0-96	6SC7	1-50
DY802	0-84	EY88	0-84	PY88	0-88	6AR5	1-98	6SR7	1-60
E88CC	3-36	EY500A	1-94	PY500A	1-80	6AS6	4-98	6SK7	1-30
E180F	8-40	EZ80	0-84	PY800	0-84	6AS7GA	6-75	6SL7GT	2-68
E810F	14-47	EZ81	0-84	PY801	0-84	6AT6	0-85	6SN7GT	1-60
EABCB80	1-20	GY501	2-75	QQV02-6	12-56	6AU5GT	4-32	6SS7	1-80
EB91	0-82	GZ32	1-24	QQV03-10	5-80	6AU6	1-04	6SG7M	2-50
EBF80	0-50	GZ33	4-00	QQV03-20A	6B7	6AW8A	3-39	6J8	0-80
EBF89	0-85	GZ34	2-50		17-50	6B7	1-50	6V6GT	1-60
EC91	7-56	GZ37	4-00	QQV06-40A	6B8		1-75	6X4	1-20
ECC33	3-50	KT61	3-50		36-34	6BA6	1-00	6X5GT	0-85
ECC35	3-50	KT66	10-00	QV03-12	4-46	6BA7	5-12	7C5	2-95
ECC81	0-88	KT77	8-00	R18	4-25	6BE6	1-08	7C8	2-25
ECC82	0-72	KT88	12-00	R19	1-20	6BH6	1-52	7S7	2-25
ECC83	0-88	N78	9-00	SP41	6-00	6BJ6	1-08	12A76	1-20
ECC85	1-20	OA2	1-60	SP61	2-00	6BN6	1-65	12A77	0-88
ECC88	1-90	OB2	2-55	U19	13-75	6BQ7A	3-72	12A78	0-88
ECC91	8-93	OC3	1-32	U25	1-16	6BR7	4-00	12A79	0-88
EF80	1-08	OD3	1-92	U26	1-44	6BR8	1-75	12BA8	2-19
ECH35	2-00	PC86	1-40	U37	9-00	6BS7	4-00	12BA9	3-43
ECH42	1-15	PC88	1-40	UABC80	1-25	6BV6	4-00	12BY7	2-70
ECH81	1-20	PC92	1-28	UBF89	1-20	6BV7	1-52	12HY7A	2-70
ECL80	1-00	PC97	1-20	UCH42	1-20	6BZ6	2-37	12HG7	4-17
ECL82	1-00	PC90	1-20	UC81	2-32	6C4	0-88	30FL1/2	1-12
ECL83	1-50	PCF80	1-00	UCL82	1-04	6C8	1-75	30P4	1-20
ECL86	1-20	PCF82	1-00	UCL83	1-44	6CB6A	2-49	30P19	1-20
EF37A	3-50	PCF86	1-60	UF89	1-44	6CD6GA	5-07	30PL13	1-80
EF39	2-75	PCF801	1-60	UL41	2-50	6CH6	8-50	30PL14	1-68
EF41	2-00	PCF802	1-50	UL84	1-20	6CL6	3-72	75C1	2-35
EF42	2-00	PCF805	1-60	UY41	1-25	6CW4	7-98	85A2	2-39
EF50	1-50	PCF808	1-60	UY85	1-04	6D05	5-94	150B2	3-02
EF54	5-00	PCH200	1-60	VR105/30	1-92	6EA8	2-94	150C2	1-92
EF55	2-50	PCL82	1-00	VR150/30	1-92	6EH5	1-85	150C4	2-39
EF80	0-80	PCL83	2-00	Z759	16-80	6F6	1-75	572B	27-50
EF86	1-52	PCL84	1-00	Z803U	7-90	6GK6	2-87	805	20-00
EF91	1-80	PCL85	1-08	2D21	3-50	6H6	1-50	807	3-75
EF92	5-81	PCL86	1-08	3B28	16-80	6HS6	3-77	811A	15-93
EF183	0-80	PCL805	1-08	4CX250B	3-60	6J5	2-50	812A	15-88
EF184	0-84	PD500	3-60		27-50	6J6	3-50	813	74-67
EH90	1-40	PL200	1-50	5R4GY	2-00	6J7	2-50	866A	8-85
EL32	1-50	PL36	1-20	5J4G	1-52	6JB6A	4-56	872A	16-87
EL33	3-50	PL81	1-20	5V4G	1-52	6JS6	5-58	931A	14-76
EL34	2-20	PL82	1-20	5Y3GT	0-85	6K4N	1-25	2050	6-96
EL36	1-60	PL83	2-22	5Z3	1-50	6K6GT	1-30	5763	3-75
EL81	2-50	PL84	1-08	5Z4GT	1-50	6K7	1-50	5814A	3-72
EL84	1-00	PL504	1-40	6/3DL2	1-56	6K8	1-75	5814B	3-72
EL86	2-50	PL508	1-80	6A871	1-50	6K9	1-75	6082	6-85
EL91	7-14	PL509	3-20	6AH6	4-71	6L6G	2-50	6146A	8-96
EL95	1-32	PL519	3-20	6AK5	3-60	6L6GC	2-50	6146B	7-06
EL360	8-50	PL802	2-96	6AL5	0-82	6L7	2-00	6883B	11-19
EM81	1-00	PY33	1-10	6AM6	1-80	6LQ6	6-72	6973	3-87

Open daily to callers: Mon-Fri 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only - Tel. 01-677 2424-7.
Quotations for any types not listed S.A.E.
Prices excluding VAT add 15%
Post and packing 35p per order
Telex 948708
Prices correct when going to press

ELDON

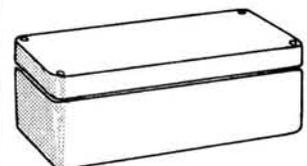

We have for years supplied industry and individuals alike, with all kinds of enclosures, from plastic to stainless steel, from one off to one thousand and one off.

The COMPACT range (illustrated) is usually available by return of post in ABS poly-carbonate or aluminium. Another advantage is that they are sealed with a rubber gasket giving dust and water protection to IP 65 (BS 5490).

If you like to order, want a brochure or just have an enclosure problem you would like to discuss, please contact:

PETER HUGHES
or
JENNY CHEETAHM
Eldon electric limited
Lovett Road, Staines, TW18 3AH.
Tel. Staines (0784) 61851 Telex: 934717.



DEACs
VARTA BUTTONS
(1.24V PER CELL)

225mA DKZ 25mm dia x 9mm	600mA DKZ 34 1/2 mm dia x 10mm
4-8V Pack £3-20	£5-55
6-0V Pack —	£6-94
9-6V Pack —	£11-10

VAT included
P+P 70p per order
RECHARGEABLE BATTERIES.

CYLINDRICAL NICADS HP7 Size (500mAh) £1-00; HP11 (1800mAh) £2-35; HP2 (4000mAh) £3-20; PP3 £4-00; PP3 Charger £5-00; 1 to 4 HP7 nicads charger £7-45.

CONSTANT CURRENT CHARGER - Switched 9mA/25mA/50mA/120mA/200mA/400mA output - charges 1 to 12 nicads - £14-95.

V & F SMALLCRAFT (POPLAR) LTD
38, STONELEIGH ROAD, CLAYHALL, ILFORD, ESSEX IG5 0JD
Tel: 01-550-6642
LIMITED TRADE DISCOUNTS POSSIBLE ON DEACs.



Multicore makes for a better job...

The biggest name in solder worldwide




Tool Box Reels

3 flux-cored solders that cover a range of electrical and non-electrical applications. ARAX 40/60 tin/lead size 11 £4.14 each. ALU-SOL size 4 £7.36 each. ERSIN 40/60 tin/lead size 3 £4.14 each.

Solder Cream

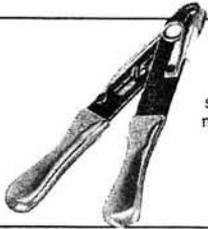For precision soldering. Solder Cream is a mixture of solder powder and flux. Electrical/electronic ("Ersin" flux) size BCR10 £1.49. Metal joining ("Arax" flux) size BCA14 £1.49. Stainless steel and jewellery ("Arax" flux) size BCA16 £3.22.



Wire Strippers & Cutters

No tool box is complete without this handy wire stripper which will adjust to most sizes of flex and cable. Easy grip plastic coated handles. Automatic opening. Handle locking device. Ref 9 £2.69.



Handy Dispensers

Size 19A 5-core solder Ersin flux 1.22mm dia for electrical work £0.97.
Size PC115 extra thin gauge for small electrical components £1.27.
Size SV130 5-core Savbit specially for copper bits and wires £1.61
Size AR140 Arax solder for all metal repairs except aluminium £1.38.
Size AL150 Alu-sol for most metals especially aluminium £1.93.
Size SS160 for stainless steel and silver jewellery £2.53.

Soldering Flux Paste - Ersin

A fast, non corrosive rosin flux for general and electrical soldering applications. Use with Ersin Multicore solder. Size RF10 £0.74.
Arax soldering flux paste also available for general metal working. Size AF14 £0.74.



Ersin 5-core Dispenser
Handy dispenser for all electrical and electronic applications. Size 6 £0.62.

Savbit Dispenser

Handy dispenser ideal for radio, TV and similar work. Reduces copper erosion. Size 5 £1.09.




... Bib makes for a better sound




Electronic Cassette Head Demagnetizer

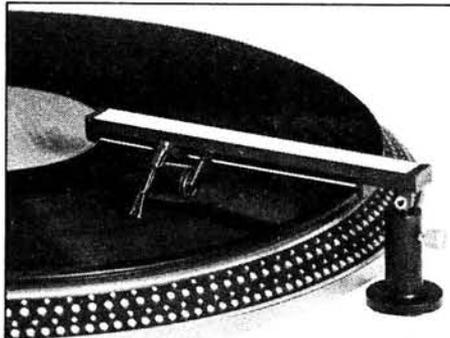Demagnetizes the tape heads to improve performance and reduce background noise. Audible tone indicates demagnetizing action.
Works on all cassette machines including in-car.
No external power needed. Ref 23 £10.49.



Bib Groove-Kleen

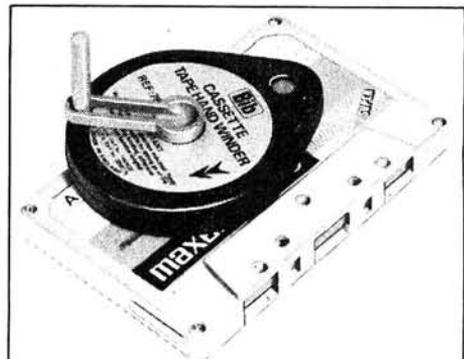For single play turntables. Velvet pad and tracking brush track across the record as it plays picking up harmful dust to improve sound-performance.
Ref. 101B £4.69 British Patent Number 1519881



Cassette Tape Hand Winder


Winds a C90 cassette in 60 seconds - faster than most cassette machines. Especially ideal for battery powered recorders to save consumption when used on fast wind.
Ref 78 £1.66. British Patent Number 1443628

Bib Groove-Guard-XL-2
Unique formula liquid, when applied to record, gives anti-static protection and helps reduce friction between stylus tip and groove. Complete with pump spray dispenser and special cleaning pad. Treats up to 12 LPs. Ref 27 £2.60.



Record Valet and Liquid

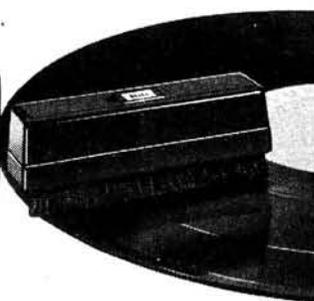Handy kit contains special anti-static fluid and velvet record cleaning pad. Ideal to remove dust and other particles from records and provides an anti-static effect to help keep your records clean.
Ref 47 £3.45.



Tape Head Cleaning Kit

Contains everything needed to clean and maintain the heads, capstan and pinch wheel on all types of cassette and tape machines. Kit includes cleaning and polishing pad, special liquid and handy inspection mirror. Ref 25 £2.48.
British Patent Number 1485069.



Bib Audio/Video Products Limited
Kelsey House, Wood Lane End,
Hemel Hempstead,
Hertfordshire HP2 4RQ.
Telephone: (0442) 61291.

All prices given are recommended retail including VAT. If you have difficulty in purchasing your Multicore solder product or Bib Hi-Fi accessory, send direct to the address above quoting the reference number and including your remittance plus 40p P&P. Send SAE for free colour catalogue showing complete range.



When replying to Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

Receivers and Components

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal freq standards, baud rates, MPU, and all magazine projects inc: HC33/U: 1.0, £3.75, 2.5625 MHz, £3.50. HC18/U: 4.0, 5.0, 6.0, 7.0, 8.0, 9.0, 10.0, 10.7, 12.0, 15.0, 16.0, 18.0, 20.0, 38-6667 MHz, £3.35. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 8 weeks from £4.10, 2-3 week service available. **FILTERS** Your best source for 5 and 8 pole and monolithics for AM, CW, SSB, FM, on 455 kHz, 1.6, 9.0, 10.7, 21.4 MHz, etc. Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEDD ELECTRONICS
G3EDW, Merriott, Somerset, TA16 5NS.
Tel: 0460 73718

BALLARD'S OF TUNBRIDGE WELLS have moved to 54 Grosvenor Road, no lists. S.A.E. all enquiries phone Tunbridge Wells 31803.

CRYSTALS MADE TO ORDER within 6 weeks. 4-105MHz, wire or pins. £3.90 each inclusive. **HARTLEY CRYSTALS**. Green Lane, Milford, Godalming, Surrey GU8 5BG.

Southern Valve Co.,

2nd Floor, 6 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. SAE Lists. Cash with order. Same Day Postal Despatch. Telephone afternoons preferred. Not Thursday.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.
Philip Bearman, 6 Potters Road, New Barnet, Herts.
Tel: 01-449 1934/5 (1934 Recording Machine).
Closed Thursday. Telephone for Shop Hours.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. Forresters (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

WE REPAIR/RESTORE valve type communication receivers with a one year guarantee. For a free quote telephone Corby 61697. Vintage British Radio Components Co., 22 Thurso Walk, Corby, Northants. "Barclaycard/Visa welcome".

VHF TUNERS.

140-150MHz. 10.7MHz IF mechanically tuned (inc s/m drive) Mosfet RF amplifier section £8.75 inc pp. Identical 65-75MHz versions ideal 4M/E. Europe Fm band and airband models available. 10.7MHz Wideband FM IF module £4.00.
TVDX equipment, VHF/UHF converter £10.50.

SAE Data, Lists.

H. Cocks, Cripps Corner, Robertsbridge, Sussex.
Tel. 058083 317.

SMALL ADS

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £9.50 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Manager, Practical Wireless, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

1920's ONWARD valves, wireless, 1000s modern components. Lists 25p. S.A.E. Sole Electronics, PW, 37 Stanley Street, Ormskirk, Lancs.

BRAND NEW COMPONENTS BY RETURN

HIGH STABILITY RESISTORS.
1W Carbon Film E12 Series 1R-10M. (E24 2R-6M2)—1p
1W, 1/2W & 1W Metal Film E12 Series 10R-2M2—2p

CAPACITORS.
MULLARD Min. Ceramic E12 100V 2% 1.8pf. to 47pf.—3p
2% 56pf. to 330pf.—4p. 10% 390pf. to 4700pf.—4p
Plate Ceramic 50V Wkg. Vertical Mounting.
E12 22pf. to 1000pf. & E6 1K5pf. to 47Kpf.—2p
Miniature Polyester 250V Wkg. Vertical Mounting.
.01, .015, .022, .033, .047 & .068 mlds.—4p
0.1—5p. 0.15 & 0.22—6p. 0.33 & 0.47—8p
0.68—11p. 1.0—15p. 1.5—20p. 2.2—22p

ELECTROLYTIC. Wire Ended (Mfda/Volts).

0.47/50	5p	22/25	5p	100/25	7p	470/25	11p
1.0/50	5p	22/50	5p	100/50	8p	470/40	15p
2.2/50	5p	47/16	5p	220/16	8p	1000/15	15p
4.7/50	5p	47/25	5p	220/25	8p	1000/25	18p
10/50	5p	47/50	5p	220/50	10p	1000/40	35p
22/16	6p	100/16	7p	470/16	11p	2200/16	20p

TANTALUM BEAD SUBMINIATURE ELECTROLYTICS.

0.1, 0.22, 0.47, 1.0, 2.2 + 35V & 47 + 6.3V—14p
4.7/16V & 25V—15p. 10/16 & 22/16—20p. 10/25—29p
10/35V, 22/16V, 47/6.3V, 68/3V & 100/3V—30p
15/25, 22/25, 47/10—35p. 47/16—80p. 220/16—£1.20
Polystyrene 63V Wkg. E12 Series Long Axial Wires.
10 pf. to 820 pf.—3p. 1000 pf. to 10,000pf.—4p

TRANSISTORS.

BC107/8/9	10p	BC182L	8p	BF197	10p
BC147/8/9	10p	BC184L	8p	BFY50/51/52	18p
BC157/8/9	10p	BC212L	8p	BFX88	25p
BC547C/8C/9C7	BCY70	15p	2N2926	7p	
BC557C/8C/9C7	BF194	10p	2N3055	50p	

8 Pin D.I.L. Ic's 741 Op/amp—18p. 555 Timer—24p
Holders 8 pin—9p. 14 Pin—12p. 16 Pin—14p. 28 Pin—25p
40 Pin—30p.

DIODES (p.i.v./amps).

75/25mA	1N4148	2p	1250/1A	BY127	10p
100/1A	1N4002	4p	400/3A	1N5404	14p
800/1A	1N4006	6p	60/1.5A	S1M1	5p
1000/1A	1N4007	7p	30/150mA	AAY32	12p

ZENER DIODES.
E24 Series 3V3 to 33V 400mW—8p. 1W—14p
L.E.D.'s 3 mm. & 5 mm. Red—10p. Green, Yellow—14p
Grommets for 3 mm.—13p. Holders for 5 mm.—2p
FUSES 20 mm. Glass. 100mA to 5A. 0.5—3p. A/S.—5p
VOLTAGE REGULATORS +5V, 8V, 12V, 15V 100mA—35p
5V, 8V, 12V, 15V, 18V & 24V 0.5A—60p. 1A—65p
PRESSET POTENTIOMETERS
50mW & 1/4W 100R to 1M0—7p.

THE C. R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN.
V.A.T. Inclusive Prices, Postage 51p
(FREE over £5.00)

T.V. PRE AMP with built in TVI filter £16.10. See August issue for other TVI filters. Apex Enterprises, 329 Welford Road, Leicester. 0533 704284.

RADIO, TELEVISION, industrial valves. Free lists. Access. Barclaycard. Vintage Wireless Co., 64 Broad Street, Bristol BS16 5NL. (0272) 565472.

Wanted

ELECTRONIC COMPONENTS PURCHASED. All types considered - Must be new. Send detailed list - Offer by return - WALTONS, 55A Worcester Street, Wolverhampton.

WE BUY SURPLUS ELECTRONIC COMPONENTS. PCB's etc, for cash. Tel: (0703) 785862.

Personal

CHRISTIAN SINGLES HOLIDAYS. Weekend houseparties, friendship, contacts nationwide. C.F.F. Dept/B89, Edenthorpe, Doncaster.

NOTICE TO READERS

Whilst prices of goods shown in advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

For Sale

TRIMPHONES, push-button, ex-GPO. Fully reconditioned. £36 + £2.00 p.p. 0385-711544.

EUROPA 70cms. SU20 Fitted. Plus slim Jim VGC. Details Terry, Farnborough 47436.

CR100 RECEIVER (60KHZ-30MHZ) £40. 2M Converter with power-pack £10. Ring Humphreys Barnstable (0271) 5452.

NEW BACK ISSUES of "Practical Wireless" available 90p each post free. Cheque or uncrossed P/O returned if not in stock. Bell's Television Service, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

Books and Publications

STATION LOGBOOKS with invaluable reference information £2.25. Mobile Minilogs 80p. Callsign Window Stickers £1.50. Beauprint, Meltham Road, Honley, Huddersfield. Trade/Club enquiries welcome. Tel. 0484-662824.

OUT OF PRINT BOOK SERVICE. 17 Fairwater Grove (E), Cardiff. Send S.a.e. for details.

BOOKS, BOOKS, BOOKS. Large range of radio and electronics books in stock. Send s.a.e. for lists. Servio Radio, Dept. PW9 156-158 Merton Road, Wimbledon, London SW19 1EG.


WHY NOT START YOUR OWN BUSINESS REWINDING ELECTRIC MOTORS. A genuine opportunity to success. **LARGE PROFITS.** You can't help but make money if you follow the easy, step by step, instructions in our fully illustrated manual showing how to rewind Electric Motors, Armatures and Field coils as used in Vacuum Cleaners, Electric Drills and Power Tools. **NO PREVIOUS KNOWLEDGE IS REQUIRED,** as the manual covers in 13 chapters, where to obtain all the work you need, materials required, all instructions, rewind charts and how to take data etc. A gold mine of information. How to set up your home workshop and how to cost each job to your customer. £4.80 inclusive of P&P. UK. CWO to: INDUSTRIAL SUPPLIES, 102 Parrswood Rd., Withington, Manchester 20. Dept. PW.

Record Accessories

STYLI, Cartridges for Music Centres, etc., Free list no. 30 for S.A.E. includes Leads, Mikes, Phones etc. Felstead Electronics, Longley Lane, Gatley, Cheshire, SK8 4EE.

Rally

SWINDON RADIO AND ELECTRONICS RALLY

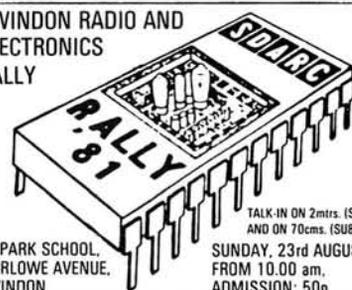

AT PARK SCHOOL, MARLOWE AVENUE, SWINDON

TALK-IN ON 2mtrs. (S22) AND ON 70cms. (S28)
SUNDAY, 23rd AUGUST
FROM 10.00 am.
ADMISSION: 50p

Miscellaneous

DIECAST weathersealed boxes 4" x 2" x 3" containing elec. ignition circuit on PCB. Approx 200. 60p each, you collect. Reigate 45408.


UK AIRCRAFT FREQUENCIES List including spot frequencies of airports, air traffic control services, weather reports, navigation beacons, etc. £1. **UK MARINE FREQUENCIES LIST** including spot frequencies of coast stations, (plus broadcast times), port operations, navigation beacons, etc. £1. **INTERNATIONAL DISTRESS FREQUENCIES CHART** 75p. Prices include postage, same day despatch. PLH Electronics, 20 Vallis Road, Frome, Somerset BA11 3EH.

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass. Board approx. 1mm thick £1.70 sq. ft. Post/Packing 75p. **WHITE HOUSE ELECTRONICS**, P.O. BOX 19, Castle Drive, Penzance, Cornwall.

C.W.A.S. ALARM. Send now for the latest discount catalogue of Professional Burglar Alarm Equipment. C.W.A.S. Alarm, 11 Denbrook Walk, Bradford BD4 0QS, W. Yorks. Phone 0274 682674.

NEAT! TIDY! HANDY! 1D 2D 3D 6D

INTERLOCKING PLASTIC STORAGE DRAWERS

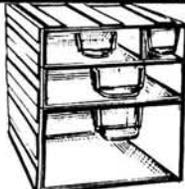

AS SUPPLIED: TO POST OFFICE & GOVT DEPTS

Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

SINGLE UNITS (1D) (5in. x 2 1/2in. x 2 1/2in.) £4.90 **DOZEN**
DOUBLE UNITS (2D) (5in. x 4 1/2in. x 2 1/2in.) £7.50 **DOZEN**
TREBLE (3D) £7.50 for 8
DOUBLE TREBLE 2 drawers, in one outer case (6D2), £10.90 for 8
 Extra large size (6D1) £8.50 for 8
 Orders over £60, less 5%. Packing/Postage/Carriage: Add £1.30 to all orders under £10. Orders £10 and over, please add 10% carriage.

QUOTATIONS FOR LARGER QUANTITIES
 Please add 15% V.A.T. to total remittance.
 All prices correct at time of going to press.

FLAIRLINE SUPPLIES (PW9) 124 Cricklewood Broadway, London N.W.2. Tel: 01-450 4844.

THE SCIENTIFIC WIRE COMPANY

PO Box 30, London E.4
 Telephone 01 531 1568

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 29	2.76	1.50	0.80	0.60
30 to 34	3.20	1.80	0.90	0.70
35 to 39	3.40	2.00	1.10	0.80
40 to 43	4.75	2.60	2.00	1.42
44 to 47	5.90	3.40	2.39	2.00
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.50	3.75	2.20	1.40
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.85	2.36	1.34	0.90
----------	------	------	------	------

Prices incl. P&P and VAT. Orders under £2 add 20p.

SAE for list of Copper/Resistance Wire.

Dealer enquiries welcome.

Reg. Office 22, Coningsby Gardens.

ELECTRONIC KITS. Largest range of kits in the U.K. Everything from stroboscopic lights to transmitters, at unbeatable prices. Send S.A.E. for free catalogue to: **EASTLING ELECTRONICS (Kits)**, 64b Hawthorne Road, Winton, Bournemouth.

DX SHORTWAVE MARITIME RADIO station list, worldwide. 100 stations, 950 frequencies, £1.75. B. J. Philipson, 20 Church Meadow, Rhydymwyn, Clwyd.

LOSING DX?

RARE DX UNDER QRM? DIG it OUT with a Tunable Audio Notch Filter, between your receiver and speaker. BOOST your DX/QRM ratio, 40dB notch, hear WEAK DX. £13.80.

CAN'T FIND DX? Get SPOT-ON with a Crystal Calibrator, between your antenna and receiver, 1MHz, 100, 25KHz MARKERS. £23.80.

ANTENNA FAULT? Check with an Antenna Noise Bridge, MEASURE resonance 1-150MHz and radiation resistance 2-1000 ohms. £15.70.

TIME WRONG? MSF CLOCK is ALWAYS CORRECT - never gains or loses. SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, parallel BCD output, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, RIGHT TIME. £62.80.

60KHz RUGBY RECEIVER, as in MSF Clock, serial data and audio outputs. £17.90.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (PW) Old School Lane, Milton, Cambridge.

MORSE CODE TUITION AIDS

Cassette A: 1-12 w.p.m. for amateur radio examination.
 Cassette B: 12-24 w.p.m. for professional examination preparation. Each Cassette are type C90.
 Morse Key and Buzzer unit for sending practice.
 Price each Cassette (including booklets) £4-75. Morse Key and Buzzer £4-75.
 Prices include postage etc. Overseas Airmail £1-50 extra.

MHEL ELECTRONICS (Dept 2), 12 Longshore Way, Milton, Portsmouth PO4 8LS.

MISCELLANEOUS PW/PE/ETI/EE from 1971 - over one hundred, inc. complete volumes. Offers? Bosham 573177.

7400's NEW FROM 7p. Send SAE lists Skates Music, 1A Manor Road, Bishopsteignton, Devon. TQ14 9SU. 06267 78856.

PARAPHYSICS JOURNAL (Russian translators): Psychotronic generators. Kirlianography. Gravity Lasers, Telekinesis. Details: SAE 4 x 9" Paralab, Downton, Wilts.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from P.V.C. Faced steel. Hundreds of people and industrial users are choosing the cases they require from our vast range. Competitive prices start at a low £1.05. Chassis punching facilities at very competitive prices. 400 models to choose from. Suppliers only to Industry and the Trade. **BAZELLI**, (Dept No. 25), St. Wilfrid's, Foundry Lane, Halton, Lancaster LA1 6LT.

AMPLIFY THE WORLD with Klifco. Modules - Chassis - & Hi Fi + free advice. 60 + 60W from £11.95! - Leaflets S.A.E. **KLIFCO**, 1 Regent Road, Ilkley LS29 9EA.

GRUNDIG stabilised power supply 2 amp push-button selection 0-25 volt. Meter indicates voltage/current, overload protected, strong metal case £20.00 + £5.00. Also millivoltmeters, multimeters, isolation transformers, signal generators/tracers. All in working order. Ring 0391 841 631 (after 6pm) or S.A.E. to A. Moore, 5 St. Joseph's Park, Ballycruttle, Downpatrick.

PRE-PACKED. Screws, nuts, washer, solder tags studding. Send for price list. A1 Sales (PW), P.O. Box 402, London SW6 6LU.

Courses

RADIO AMATEURS EXAMINATION

Classes are held on Tuesday, Thursday and Friday evenings at Paddington College, 25 Paddington Green, W2 (Nr Edgware Road, Tube Station) in connection with the Amateur Licence A and B. Please contact:

The Course Tutor,
David Peace G4KKM
01-402 6221 EXT 54.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for insertions

I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME.....

ADDRESS.....

Send to: Classified Advertisement Manager

PRACTICAL WIRELESS,
Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS Telephone 01-261 5846

Rate
 28p per word, minimum 12 words. Box No. 60p extra.

Educational

CAREERS in Marine Electronics, Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JS. Tel. 03917 79123.

TECHNICAL TRAINING

Get the training you need to move up into a higher paid job. Take the first step now—write or phone ICS for details of ICS specialist homestudy courses on Radio, TV, Audio Eng. and Servicing, Electronics, Computers, also self-build radio kits. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 277L Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

COLOUR TV SERVICING

Learn the techniques of servicing Colour TV sets through new homestudy course approved by leading manufacturers. Covers principles, practice and alignment with numerous illustrations and diagrams. Other courses for radio and audio servicing. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 277L Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

CITY & GUILDS EXAMS

Study for success with ICS. An ICS homestudy course will ensure that you pass your C. & G. exams. Special courses for: Telecoms, Technicians, Electrical Installations, Radio, TV & Electronics Technicians, Radio Amateurs. Full details from:

ICS SCHOOL OF ELECTRONICS

Dept. 277L Intertext House, London SW8 4UJ

Tel. 01-622 9911 (all hours)

State if under 18

J. BIRKETT

Partners: J. H. Birkett, J. L. Birkett

Radio Component Suppliers

25 The Strait, Lincoln. LN2 1JF

EDDYSTONE TRANSMITTING VARIABLES 30 - 30pf (60pf) = £2.20.
FERRANTI WIRE ENDED DIODES 800 PIV 750mA 12 for £1.
500 METRE REEL OF PVC CABLE 13 Strands .019 at £10 carriage paid.
80M CRYSTALS 10X Type.3642.5KHz or 3750KHz. Both 40p each.
MINIATURE CERAMIC TRIMMERS 2.5 to 6pf, 3 to 10pf, 4.7 to 20pf, 7 to 35pf, 10 to 40pf, 10 to 60pf, All at 15p each.
MAINS TRANSFORMERS 240 Volt input, Output 24 volt Tapped at 14 volt 1 amp = £1.30 (P&P 30p).
JUMBO ORP12 CADMIUM SULPHIDE PHOTOCONDUCTIVE CELL Type RPY18 = £1.65 each.
LEAD SULPHIDE PHOTOCONDUCTIVE CELL RPY 75 with data = 3.50.
RPY75A WITH GERMANIUM FILTER = £4.50.
ORP62 CELL with data = £1.30.
SUB-MINIATURE AXIAL RED LEDS—COY60 = 20p each.
MULLARD PHOTO TRANSISTORS BPX 70 = 50p.
SLOTTED OPTO INFRA RED SOURCE SWITCH = £1.50.
X BAND GUNN DIODES with data = £1.65.
SOLDER-IN FEED THRU 6.8pf, 27pf, 300pf, 1000pf. 20p doz.
4500 PIV 2 AMP DIODES at £1.50 each.
VARIABLE CAPACITORS 10 - 10 - 10pf = 75p each.
6.2 VOLT WIRE ENDED 2 WATT ZENERS = 15p, 5 for 60p.
HEWLETT PACKARD HOT CARRIER DIODES 5082-2800 = 40p.
VHF FETS J304 = 30p, 8F 256C = 4 for 75p.
FERRITE BEADS FX1115 = 15p doz, 1/2" Long Type 6 for 10p.
MULLARD SUB-MINIATURE DISCS 1000pf 63v.w., 25p doz.
DISC CERAMICS 1uf 18v.w., 22uf 7v.w., 5uf 12v.w., All 5p each.
VERNITRON FM4 10.7MHz FILTERS = 3 for £1.
MINIATURE CERAMIC TAG STRIPS 12 way Opp15p, 21 way = 20p.
3/16" COIL FORMERS with core at 6 for 25p.
TOROIDAL TRANSFORMERS 240 Volt Input, Output 30 Volt 500mA = £2.30.
H.F.-VHF POWER TRANSISTOR 5878LY 40 watts, 26 to 70 MHz = £3 each.
2 CHANNEL HIGH SPEED DRIVER WITH SPST J FET SWITCHES Type DG182 with data = £1.15 each.
POWER TRANSISTORS 2N4348 140 Volt 10 amp = 65p, 2N6212 PNP 350 volt 2 amp = 65p, SDT 96306 300 Volt 50 amp at £1.65, OC 36 = 50p.
GENERAL PURPOSE NPN TRANSISTORS BSY95A = 6 for 50p.
TRW UHF POWER TRANSISTORS useful up to 980MHz FT 1200MHz 12 Volt 2 watt out Type PT 4642 = £2.50.
VARIABLE CAPACITORS 5pf = 75p, 10 - 10 - 10pf = 75p, 250 - 250pf = 85p, 200 - 200 - 20pf = 75p, 250 - 250 - 20 - 20 - 20pf = 75p.
R. F. CHOKES 10U.H., 33U.H., 330U.H., All at 7p, 1000U.H. = 12p.
MULLARD BLY55 175MHz 13 Volt 4 watt 400mW Drive = £4.
MULLARD 175MHz 40 watt 5 watt Drive, 570BLY 28 volt = £8.30.
MULLARD 1000pf 63v.w., DISC CERAMICS at 25p doz.
MULLARD UHF POWER MODULE BGY22C, 380-412MHz, 2.5 watt = £12.50.

Please add 30p for post and packing. Orders over £3 post free.

Service Sheets

30,000 SERVICE SHEETS IN STOCK COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios £1.25 - Tuners £1.25 - Tape Recorders, Record Players, Transistors from £1.25 - Car Radios, Stereograms, Radiograms from £1.25 - Except Colour TV Circuits from £2. - State, if circuit will do, if sheets are not in stock. All TV sheets are full length 24 x 12", not in Bits & Pieces. All other Data full lengths. Free Fault Finding Chart or TV Catalogue with order. Crossed P.O.s returned, if sheets not in stock. S.A.E. please.

C. CARANNA

71, Beaufort Park, London NW11 6BX
01-458 4882 (Mail Order)

OSCILLOSCOPE repair and calibration. Quick service, competitive rates. W.I.R. Electronics 01-367-6816.

SERVICE SHEETS, Radio, TV etc., 10,000 models. Catalogue 25p. plus S.A.E. with orders, enquiries, TELRAY, 5 Henderson Street, Preston PR1 7XP.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, TV etc., £1.00 plus S.A.E. Colour TV Service Manuals on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, W. Yorkshire. Tel. (0423) 55885.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

G.T. TECHNICAL INFORMATION SERVICE 76 CHURCH ST., LARKHALL, LANARKS.

Any full size service sheet - still only £1 + s.a.e.

Thousands of different sheets & manuals in stock (many of these only obtainable from us)

Repair data your named T.V. £6 (with circuits £8)

Domestic Equipment, exploded diags, circs, etc. in 2 huge binders £26.50

S.A.E. for free newsletter, price lists, any quotation, bargain offers, unique T.V. publications.

2 big catalogues list thousands service sheets/manuals plus £4 vouchers for £2 + large s.a.e.

Complete British Colour TV circuits, etc. in 3 huge binders only £39.50

Phone: 0698 883334 anytime. Callers 4-6 pm weekdays, Sat. after 10.

Aerials

ANTI-TV1 TRAP DIPOLES

1981 Range: Shortwave Listener Aerials

Indoor models £14.50 & £27.50
 Outdoor models £30.00 & £36.00
 Lists 10 x 8 in 17p SAE, Aerial Guide 50p
 Indoor and Invisible Aerials £3.50

Callers Welcome Tel: 03986-215

G2DYM, Uplowman, Tiverton, Devon.

TV-DX

FM-DX and all domestic reception requirements - Fringe or 'Local' Aerials, Amplifiers, Boosters, Filters, Hardware - and the knowledge. Our new 1981 Catalogue costs 45p. SAE all enquiries, please.

*ROGER BUNNEY'S TVDX BOOK (2ND EDITION) £2.35 inc. post + packing.

SOUTH WEST AERIAL SYSTEMS (PW)

10, Old Boundary Road, Shaftesbury, Dorset.
Tel. (0747) 4370.

COPPER AERIAL WIRE 14swg hard drawn 70' £5.34, 140' £8.84 inc. VAT. Postage £1.75 T.M.P. Electronics Supplies, Britannia Stores, Leeswood, Nr. Mold, N. Wales.

PROGRESSIVE RADIO

ALL ORDERS DESPATCHED BY RETURN POST

NICADS. 'AA' size 95p, 'C' 2AH £2.60p, 'D' 1.2AH £2.40p, 'D' 4AH £3.60p.
BEREC UNIVERSAL NICAD CHARGER, charges 'AA', C or D cells, up to 4 of each type £9.25p.

SWITCHES. Min. toggles, SPST 8x5x7mm 42p. DPDT 8x7x7mm 55p. DPDT c/off 12x11x9mm 77p. HEAVY DUTY-DPDT 240VAC 10 Amp 35p. PUSH TYPE, push on 16x6mm 15p, push to break version 17p, MERCURY (TILT) SWITCH, 1"x1/2" 35p.

NSA1198 8 1/2 digit multiplexed displays, com. cath. with data sheet £1.45p.
SPECIAL OFFER TIL209 Red LED's 10 for 75p. 0.2" LEDs, red, yellow, green 10p each.

MICROPHONE OFFERS: P.A./C.B. hand held mikes with thumb switch + curly lead, 1.600Q dynamic £3.95p, 2. 600Q noise cancelling type £7.25p, 3. CB power type with volume control £7.95p. EM103 Electret Condenser Mike, 600Q, Omni, 50-1600Hz, aluminium case 172 x 22mm with battery £7.25p.

ANTEX SOLDERING IRONS: Models C15, CX17 and X25 all £4.45 each.
STABILISED POWER SUPPLY, 240 vac input 13.8 volts at 3/5 Amps DC output, £14.75p.

JUMPER TEST LEAD SETS. 10 pairs of leads with insulated cross each end 90p.

40KHZ TRANSUDCERS, RX/TX £3.50 pair.

STC BREAK GLASS FIRE ALARM UNITS, new with mounting box £1.50p.
MINIATURE SOLID STATE BUZZERS. 2 voltages available, 6 or 12VDC 75p each, Loud 12 volt buzzers 65p.

Cash with order please, official orders welcome from schools etc., please add 30p postage and packing. VAT inclusive. New catalogue at printers. Sorry for delay. All S.A.E.'s sent are being held until catalogue is ready.

31, CHEAPSIDE, LIVERPOOL L2 2DY

MIGHTY NINETY PACKS ALL 90p

BUY SIX PACKS AND GET A SEVENTH PACK FREE!

POSTAGE UP TO 4 PACKS 15p PER PACK. 5 PACKS OR MORE POST FREE.

MM1	300 1/2 watt pre-formed resistors.	MM31	15 assorted trimmer caps.
MM2	200 1/2 and 1 watt resistors.	MM32	15 30pf beehive trimmers.
MM3	100 1 and 2 watt resistors.	MM34	25 min. glass reed switch.
MM4	50 wire wound resistors.	MM40	50 polystyrene capacitors.
MM5	100 metal oxide resistors.	MM42	10 BC107 transistors.
MM6	12 assorted potentiometers.	MM43	10 BC108 transistors.
MM7	25 assorted pre-set resistors.	MM44	10 slide switches sp/co.
MM8	50 assorted electrolytic caps.	MM51	10 .2" red led.
MM9	100 assorted ceramic caps.	MM52	10 .125" red led.
MM10	100 mixed caps, poly, ceramic, elect, mica, etc.	MM53	20 0.1 mfd 25V ceramic disc.
MM13	20 assorted transistors.	MM54	20 0.1 mfd 25V ceramic disc.
MM14	40 1N4148 diodes.	MM58	2 x CA723 voltage reg.
MM22	8 .2" LED's with clips 4 red, 2 yellow, 2 green.	MM61	3 x TIP31 transistor.
MM23	1lb nuts, screws, washers, etc.	MM62	30 mixed polyester caps.
		MM63	C280, Siemens, etc.

Microwave Modules as described in Practical Wireless "Exe". Project (Wessex Alarms) complete with horn. £8.00 + 50p postage.

CHORDGATE LTD (Dept C)

75 Faringdon Road, Swindon, Wilts. Tel. (0793) 33877

Retail premises at above address.

TRANSFORMERS +VAT 15%

30 VOLT RANGE (Split Sec)
Sec Voltages available 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref.	30V Amps	Price	P&P
112	5 1	2.90	1.00
79	1 2	3.93	1.00
3	2 4	6.35	1.20
20	4 6	7.39	1.44
21	4 8	8.79	1.60
51	5 10	10.86	1.80
117	6 12	12.29	1.72
88	8 16	16.45	1.96
89	10 20	18.98	1.84
90	12 24	21.09	O.A.
91	15 30	24.18	O.A.
92	20 40	32.40	O.A.

UK Postage as quoted.
Overseas postage extra.
Voltages stated are on full load

Continuous Ratings

60 VOLT RANGE (Split Sec)
Pri 120/240V. Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 or 24V-0-24V or 30V-0-30V.

Ref.	60V 30V Amps	Price	P&P
124	5 1	4.27	1.20
126	1 2	6.50	1.20
127	2 4	8.36	1.60
125	3 6	12.10	1.72
123	4 8	13.77	1.96
40	5 10	17.42	1.84
120	6 12	19.87	2.04
121	8 16	27.92	O.A.
122	10 20	32.51	O.A.
189	12 24	37.47	O.A.

50 VOLT RANGE (Split Sec)
Pri 120/240V Sec 50V Voltages available 5, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V

Ref.	50V 25V Amps	Price	P&P
102	5 1	3.75	1.20
103	1 2	4.57	1.20
104	2 4	7.88	1.44
105	3 6	9.42	1.60
106	4 8	12.82	1.72
107	6 12	16.37	1.84
118	8 16	22.29	2.20
119	10 20	27.48	O.A.
109	12 24	32.88	O.A.

MAINS ISOLATORS (SCREENED)
Pri 0-120: 0-100-120V 120, 220, 240V Sec 60-55-0-55-60 twice to give 55, 60, 110, 115, 120, 125, 175, 180, 220, 225, 230, 235, 240.

Ref.	VA	Price	P & F
*07	20	4.84	1.20
149	20	7.37	1.20
159	100	8.38	1.44
151	200	12.28	1.72
152	250	14.61	2.04
154	500	22.52	2.20
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-240V Sec 115 or 240V State sec. volts required.

CASED AUTO TRANSFORMERS
240V cable in 1.5V USA flat pin outlets

VA	Price	P & P	Ref.
20	6.55	0.95	56W
75	8.50	1.20	64W
150	11.00	1.44	49W
250	13.39	1.44	69W
500	20.13	2.24	67W
1000	30.67	2.20	84W
2000	54.97	O.A.	95W

AUTO TRANSFORMERS

Voltages available: 105, 115, 190, 200, 210, 220, 230, 240, for step up and step down.

Ref.	VA (Watts)	£	P&P
113*	15	2.73	1.00
64	80	4.41	1.20
4	150	5.89	1.20
53	350	10.00	1.44
67	500	12.09	1.84
94	1000	20.00	2.20
93	1500	25.61	O.A.
95	2000	38.31	O.A.
73	3000	65.13	O.A.
80S	4000	84.55	O.A.
57S	5000	98.45	O.A.

*0.115, 220, 240.

TRANSFORMERS OFFERS

"New" Constant Voltage Transformers (1%)
For "clean" mains to computers or peripherals. No transient spikes to damage I.C.'s etc.

AK250	£98.00
AK500	£129.00
AK1000	£149.00

Appointed Distributors of Galatruk stabilisers & Voltsafe cutouts.

15V CT Range (7.5V-0-7.5V)

Ref.	500 mA	P & P
171	1A	2.30
172	1A	3.26
173	2A	3.95
174	3A	4.13
175	4A*	6.30

NEW RANGE TRANSFORMERS

Pri 120/240V
2 windings 0-36V-48V/36V-0-36V 48V-0-48V 72V or 96V.

Amps	Ref.	Price	P&P
1.0	431	8.12	1.44
2.0	432	13.35	1.22
3.0	433	16.17	1.96
4.0	434	20.65	2.04
5.0	435	29.30	2.20
6.0	436	36.69	O.A.
8.0	437	40.03	O.A.

Split Bobbin Type. Pri 0-115, 0-115, Sec 0-12-15-20-24-30 to give 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24, 30V, 2 amps £4.65, P&P £1.10 - VAT.

OTHER PRODUCTS

AVO TEST METERS

AVO 8 MK5. Latest Model	£116.40
AVO 71 Electronics & TV Service	£45.40
AVO 73 TV Service	£63.90
AVO MM5 Minor	£40.50
AVO EM272 316KΩ/Vol input Z	£67.10
AVO DA116 L.C.D. Digital	£121.70
AVO DA211 L.C.D. Digital (Hand Held)	£57.00
AVO DA212 L.C.D. Digital (Held)	£74.00
Battery MEGGER BM7/500V	£65.30
Wee MEGGER hand crank	£97.20

All Avos Meggers & accessories available.
Plus P&P £1.32 + VAT 15%

SPECIAL OFFER
Multimeter 20KΩ B/V - with combined audio/F. test oscillator at 1 KHz and 465 KHz AC/DC to 1000 volts DC. Current to 500mA resistance to 1MΩ. Size 160x97x40mm
£8-50 P & P £1.00 VAT 15%.

EDUCATIONAL METERS (Moving Coil)

0-10A, 0-30V. Freestanding large scale easily read meters with top screw terminals for quick connections. £4.50 P&P 66p - VAT. Size 75 x 78mm scale.

SPECIAL OFFER

25W Soldering Iron to BS Spec. £1.75 P&P 30p + VAT 15%.

Antex Soldering Irons CN240 15W & 25W £4.58 each. Safety Stand £1.75 P&P 52p each.

P.W. Purbeck oscilloscope transformer 250-0-250; 6-3V; 12.9V (author approved) £9.42 £1.04

Precision De-Solder Pumps - Spring loaded quick action button release for one hand working. Large £5.10 P&P 35p + VAT. Small £4.75 P&P 30p + VAT. Replacement tips Small 65p + VAT. Large 86p + VAT.

Telephones - Latest model 746, boxed, 2 tone grey £11.50 + VAT, Ivory £12.50 + VAT, P&P £1.20 + VAT.

METAL OXIDE RESISTORS £1 per 100 (Electrosil) TR4 5% 390Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/1K2/1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K/110K/120K/130K/180K/220K/270K/300K. P&P 50p + VAT.

100W Soldering Gun includes bulb for spot-on joints £5.39 + VAT.

BATTERY ELIMINATORS

Plugs into 13A socket 3, 6, 7, 5, 9, 12V DC - 30mA output £5.10 P&P 60p + VAT.

PANEL METERS

43mm - 43mm	82mm - 78mm	Price	P&P
0 50mA	0 50mA	6-70	6-70
0 500µA	0 500µA	6-70	6-70
0 1mA	0 1mA	6-70	6-70
0 30V	0 30V	6-70	6-70

BRIDGE RECTIFIERS

100V 25A	£1.80	500V	£2.20
100V 50A	£2.20	PM7A6	
200V 2A	£0.52	12A	
200V 4A	£0.75	£3-75	
400V 1A	£0.25		
400V 4A	£0.98	P&P 20p	
400V 6A	£1.44	VAT	

Jewellers Screwdriver Set £2.00 + VAT, P&P 40p + VAT.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/7/8
NEAREST TUBE STATIONS: ALDgate & LIVERPOOL ST

Mullard Modules
LP1175 LP1179 LP1186 LP1157
IF Strip AM.FM varicap Med & Long
Front end tuner
Pair £5.75 £5.00 £2.50
Complete with Data

Ultra Sonic Transducers 40KC/S
Complete on 18" Screened cable £1.75 each
Pairs £2.95

Ultra sonic Transmitter
Complete unit (uncased requires 1.5V) £3.25

Foster Dynamic Microphones
200 ohm impedance: £1.75 Pair
Moving coil Complete on Chassis

Stereo Cassette Tape Heads
Quality replacement for most recorders with mounting plate. Record/Replay
£1 each
set of 4 £3.50
Common anode
14 Pin Dil

Hewlett - Packard Displays
Half inch red common anode definitely the brightest with replace (DL707)
Excellent character appearance, evenly lighted segments, wide viewing angle, body colour improves 'Off' segment contrast. Categorized for luminous intensity, use of like categories yields a uniform display. Consumption as low as 3mA per segment, designed for multiplex operation. Standard 14 pin dual-in-line package configuration.

(5082-7650) HIGH EFFICIENCY & VERY BRIGHT
ONLY £1.00 each
SET OF 6 £5


Vero Computer Frames
19x8" with 64 runners & guides.
List price £43. Our price £17.95.

National 4116 Dynamic (16K RAM)
200 N/Seconds £1.95
Less 10% per 4. 15% per 8.

All items new stock - delivery by return post
All items inclusive of VAT & Post Paid. Quantity Discounts 15% per 10, 20% per 50.

SCOOP ONLY £29.95 +VAT

Professional ASCII Keyboards

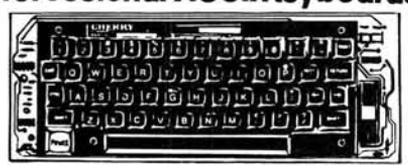

The 'CHERRY' Computer Keyboard

- BRITISH MADE
- 52 KEY 7 BIT ASCII CODED
- POSITIVE STROBE +5V - 12V
- FULL ASCII CHARACTERS
- PARALLEL OUTPUT WITH STROBE
- POWER LIGHT ON CONTROL
- CHIP BY GENERAL INSTRUMENT (G.I.) TTL OUTPUT
- SUPERBLY MADE SIZE 13 x 5.5 x 1.5 ins.
- BLACK KEYS WITH WHITE LEDGENS
- ESCAPE SHIFT RETURN & RESET KEYS
- CONTROL REPEAT & BELL
- Complete with DATA

Ideal for use with TANGERINE, TRITON, TUSCAN, APPLE and most computers. Ex-Stock from HENRY'S

This is definitely the BEST BUY FULLY GUARANTEED Supplied BRAND NEW in manufacturers original packing. Just post remittance total £35.95 (incl. VAT & Post)

404 Edgware Road, London, W2, England. 01-723-1008

PM COMPONENTS LTD

VALVE & COMPONENT SPECIALISTS
CONINGSBY HOUSE, WROTHAM RD., MEOPHAM, KENT.

VALVES	PL508	1.48	6080	4.20	BC213L	0.09	BU108	1.69	
DY86	0.55	PL509	2.30	6146B	4.45	BC214	0.09	BU205	1.30
DY802	0.60	PL802	2.50	7025	1.50	BC214L	0.09	BU208	1.39
E180F	5.25	PY88	0.74	7360	7.50	BC237	0.09	BU208A	1.52
EABCB0	0.56	PY500A	1.35	7591	2.35	BC238	0.08	MJ340	0.40
EBF89	0.70	PY81	0.65			BC307	0.09	OC71	0.22
ECC81	0.55	QQV02/6	10.50			BC327	0.10	R2008B	1.70
ECC82	0.55	QQV03-20A				BC337	0.10	R2010B	1.70
ECC83	0.60	12.25				BC461	0.30	R2540	2.48
ECC85	0.60	QQV06-40A				AC126	0.22	BC478	0.20
ECC88	0.65					AC127	0.22	BC547	0.10
ECC807	1.30	QV03-12	3.50			AC128	0.28	BC558	0.10
ECF80	0.65	TY2-125A	45.00			AC141K	0.34	BC549A	0.08
ECF82	0.60	U19	11.95			AC176	0.22	BC557	0.07
ECF81	0.58	UC81	0.65			AC176K	0.31	BC558	0.07
ECL82	0.58	UC82	0.76			AC187	0.26	BD131	0.32
ECL83	1.13	UL84	0.78			AC187K	0.28	BD132	0.35
ECL86	0.74	UY85	0.70			AC188	0.22	BD133	0.40
EF37A	3.60	Z759	2.79			AC198	0.10	BF183	0.29
EF80	0.48	2D21	0.95			AD161	0.39	BD136	0.30
EF86	0.70	2K25	10.00			AD161/2	1.04	BD137	0.28
EF89	0.75	4CX250B	26.60			AD162	0.39	BD138	0.30
EF91	1.22	5U4G	0.85			AF127	0.32	BD139	0.32
EF93	0.65	6CD6GA	4.00			AF139	0.42	BD140	0.30
EF94	0.55	6GK6	2.50			AF239	0.42	BD144	1.20
EF95	0.78	6J6	0.65			BC107	0.10	BF115	0.35
EF183	0.56	6J5C	2.55			BC107B	0.10	BF176	0.24
EF184	0.56	6KD6	3.95			BC108	0.10	BF179	0.34
EL34	1.54	6L8CC	1.75			BC108C	0.10	BF180	0.29
EL84	0.60	6X4	0.60			BC109B	0.10	BF183	0.29
EM84	0.70	6SN7GT	0.69			BC140	0.31	BF194	0.11
EZ80	0.56	6V6GT	0.90			BC141	0.25	BF195	0.11
EZ81	0.56	757	2.00			BC142	0.21	BF196	0.11
GZ32	0.85	12A7	0.55			BC143	0.24	BF197	0.11
GZ33	3.25	12AU7	0.55			BC147	0.09	BF198	0.10
GZ34	2.00	12AX7	0.55			BC148	0.09	BF199	0.14
KT61	3.50	12BA6	0.80			BC149	0.09	BF200	0.10
KT66	4.95	12BE6	1.05			BC157	0.10	BF257	0.28
KT77	5.00	12BH7	0.95			BC158	0.09	BF258	0.25
KT88	6.00	12HG7	3.25			BC159	0.09	BF259	0.26
N78	8.90	30F12	0.95			BC160	0.28	BF336	0.34
PCF80	0.60	85A2	1.20			BC170B	0.10	BFX29	0.30
PCF80	0.70	90C1	1.69						

WATFORD ELECTRONICS

33/35, CARDIFF ROAD, WATFORD, HERTS, ENGLAND
TEL. WATFORD (0923) 40588. TELEX 8956095

ALL DEVICES BRAND NEW. FULL SPEC. AND FULLY GUARANTEED. ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.O. OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS OFFICIAL ORDERS ACCEPTED (TELEPHONE ORDERS BY ACCESS NOW ACCEPTED Minimum £10.00 please). TRADE AND EXPORT INQUIRY WELCOME. P & P ADD 50p TO ALL ORDERS UNDER £10.00. (excluding VAT). OVERSEAS ORDERS POSTAGE AT COST.

VAT Export orders no VAT. Applicable to U.K. Customers only. Unless stated otherwise, all prices are exclusive of VAT. Please add 15% to the total cost including p & p.

We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/Br. Rail Station: Watford High Street. Open Monday to Saturday 9 a.m.-6 p.m. Ample Free Car Parking space available.

POLYESTER RADIAL LEAD CAPACITORS: 250V;
10n, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 13p; 680n 19p; 1µ 23p; 1.5µ 40p; 2.2µ 46p.

ELECTROLYTIC CAPACITORS (Values in µF): 500V: 10 52p; 47 78p; 63V: 0.47, 1.0, 1.5, 2.2, 3.3, 8p; 4.7 9p; 6.8, 10 10p; 15, 22, 12p; 33, 47 12p; 100 19p; 1000 70p; 50V: 4.7, 12p; 68 20p; 220 24p; 470 32p; 2200 90p; 40V: 4.7, 15, 22, 9p; 330 90p; 470 120p; 25V: 1.5, 6.8, 10, 22 8p; 33 9p; 47 9p; 100 11p; 150 12p; 220 15p; 330 22p; 470 25p; 680, 1000 34p; 2200 50p; 3300 76p; 4700 92p; 18V: 4.7, 10p; 9p; 125 12p; 220 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 3300 74p; 4700 79p.

TANTALUM BEAD CAPACITORS: 35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8, 10 22p; 15 22p; 16V: 2.2, 3.3, 16p; 4.7, 6.8, 10 18p; 15 36p; 22 30p; 33, 47 40p; 100 75p; 10V: 15, 22 36p; 33, 47 35p; 100 55p.

POLYESTER (MYLAR) CAPACITORS: 100V: 1nF, 2n, 4n, 4n7, 10n 6p; 15nF, 22n, 30n, 40, 47 7p; 56, 100n, 200 9p; 50V: 470nF 12p.

CERAMIC CAPACITORS 50V
Range: 0.5pF to 10nF 4p
15nF, 22nF, 33nF, 47nF 5p 100nF 7p

POLYSTYRENE CAPACITORS
10pF to 1nF, 8p 1.5nF to 12nF, 10p.

RESISTORS—5% carbon, High Stab. Miniature, Low Noise.
Range Val. 1-99 100+
0.25W 202-4M7 E24 2p 1p
0.5W 202-5M1 E12 2p 1p
1W 202-10M E24 5p 3p
2% Metal Film 10Q-1M E24 6p 4p
1% 0.5W 51Q-1M E24 10p 8p
N.B. 100+ price applies to Resistors of each type not mixed values.

VEROBOARDS: 0.1" VQ Board 150p
Clad Plain DIP Board 340p
2.1x3.3" 75p 52p Vero Strip 130p
2.1x5.1" 83p
3.1x3.3" 83p
3.1x5.1" 99p
3.1x7.1" 326p 211p
4.1x7.1" 426p
Pkt of 100 pins 50p
Spot face cutter 118p
Pin insertion tool 162p

COPPER CLAD BOARDS
Fibre Single-Sided SRBP
Glass Double-Sided 9.5" x 8.5"
6" x 6" 90p 110p 95p
6" x 12" 150p 200p

FERRIC CHLORIDE 1 lb 195p + 40p p&p
DALO ETCH RESIST PEN plus Spare Tip 95p

SOLDERCON PINS 100 pins 60p; 500 pins 275p
VERO WIRING PEN + spool 310p; comb 6p

DIL SOCKETS Low profile wire edge connectors TEXAS
8 pin 8p 25p
14 pin 10p 35p
16 pin 10p 42p
18 pin 16p 52p
20 pin 22p 60p
22 pin 25p 70p
24 pin 25p 70p
28 pin 28p 80p
36 pin — 105p
40 pin 30p 99p

DENCO COILS Dual Purpose DP 42p
VALVE TYPE RFT 5 chokes 140p
RFT 7 (19mH) 160p
Rds. 1-5 Bl. Yl. 122p
6-7 B. Yr. 110p
1-5 Green, R 120p
T-type (Transistor Tuning) 152p
Ranges: 1-5 Bl. Yl. MW 5FR 122p
Red, White 150p MW/LW 5FR 154p

JACKSONS VARIABLE CAPS. Dielectric 0-2-365pF with slow motion Drive 450p
500pF 00-2-2081/76 395p
6.1 Ball Drive 150p
451/DAF 160p motion drive 450p
Dial Drive 4103 C804: 5pF: 10 250p
6.1/36:1 75p 5pF 290p
Drum 5pF 50p 290p
0-1-365pF 32p 100-150p 35p
00-2-365pF 395p 'L' 3x310pF 725p
00-2-500pF 500p 00-3x250pF 550p

TRANSISTORS		OC170/1		85		2N3771		179		LS15		15		LS221		60	
AC125	35	BD144/5	198	OC200	85	2N3772	195	LS20	15	LS240	96	LS241	96	LS242	85	LS243	85
AC126/25	110	BD205	110	TI29	34	2N3773	270	LS21	15	LS244	85	LS245	118	LS246	118	LS247	118
AC128	25	BD214	115	TIP29A	36	2N3819	22	LS22	15	LS248	65	LS249	65	LS250	65	LS251	65
AC147/2	30	BD245	45	TIP29B	56	2N3820	45	LS26	18	LS252	40	LS253	40	LS254	40	LS255	40
AC176	75	BD278	65	TIP29C	67	2N3821	30	LS27	18	LS256	40	LS257	40	LS258	40	LS259	40
AC177/18	70	BD434	55	TIP30	48	2N3866	90	LS28	20	LS260	40	LS261	40	LS262	40	LS263	40
AC191/20	75	BD517	75	TIP30C	58	2N3903/4	18	LS30	18	LS264	40	LS265	40	LS266	40	LS267	40
AC192/22	75	BD695A	99	TIP31A	45	2N3905/6	15	LS32	15	LS268	40	LS269	40	LS270	40	LS271	40
AC198	75	BD696A	99	TIP31C	55	2N4037	46	LS33	16	LS272	40	LS273	40	LS274	40	LS275	40
AD148	79	BDY56	190	TIP32A	48	2N4058	10	LS37	16	LS276	40	LS277	40	LS278	40	LS279	40
AF16/2	42	BF175	55	TIP32B	60	2N4172	80	LS38	16	LS280	40	LS281	40	LS282	40	LS283	40
AF106	70	BF167	29	TIP33A	65	2N4427	80	LS40	16	LS284	40	LS285	40	LS286	40	LS287	40
AF118	95	BF180	38	TIP33C	78	2N4859	78	LS42	35	LS288	40	LS289	40	LS290	40	LS291	40
AF139	40	BF194/5	12	TIP34A	74	2N4871	55	LS47	40	LS292	40	LS293	40	LS294	40	LS295	40
AF178	75	BF196/7	12	TIP34C	88	2N5172	18	LS48	80	LS296	40	LS297	40	LS298	40	LS299	40
AF239	78	BF198/9	16	TIP34E	160	2N5179	45	LS49	80	LS299	40	LS300	40	LS301	40	LS302	40
BC107	10	BF200	12	TIP35C	185	2N5193	75	LS51	15	LS303	40	LS304	40	LS305	40	LS306	40
BC107B	12	BF224	24	TIP36A	170	2N5305	24	LS54	15	LS307	40	LS308	40	LS309	40	LS310	40
BC108	10	BF244	30	TIP36C	199	2N5457	36	LS55	30	LS311	40	LS312	40	LS313	40	LS314	40
BC108B	12	BF248	30	TIP41A	55	2N5485	60	LS56	33	LS315	40	LS316	40	LS317	40	LS318	40
BC108C	12	BF256	35	TIP41B	68	2N5642	75	LS63	25	LS319	40	LS320	40	LS321	40	LS322	40
BC109	10	BF257/8	32	TIP42	60	2N5777	45	LS67	25	LS323	40	LS324	40	LS325	40	LS326	40
BC109B	12	BF259	35	TIP42B	75	2A5175	60	LS74	20	LS327	40	LS328	40	LS329	40	LS330	40
BC109C	12	BF274	42	TIP42C	90	2SC495	70	LS76	20	LS331	40	LS332	40	LS333	40	LS334	40
BC140	30	BF336	40	TIP21	99	2SC496	70	LS78	24	LS335	40	LS336	40	LS337	40	LS338	40
BC141/2	30	BF451	35	TIP142	120	2SC1096	85	LS83	50	LS339	40	LS340	40	LS341	40	LS342	40
BC143	30	BF594	30	TIP144	120	2SC1173	125	LS85	70	LS343	40	LS344	40	LS345	40	LS346	40
BC147	9	BF635	39	TIP295	60	2SC1206	150	LS86	38	LS347	40	LS348	40	LS349	40	LS350	40
BC147B	10	BF639	23	TIP305S	60	2SC1307	220	LS88	30	LS351	40	LS352	40	LS353	40	LS354	40
BC148	9	BF640/21	23	TIS43	32	2SC1449	85	LS91	80	LS355	40	LS356	40	LS357	40	LS358	40
BC148B	10	BF719	23	TIS44/5	45	2SC1678	140	LS92	36	LS359	40	LS360	40	LS361	40	LS362	40
BC148C	10	BF800/1	24	TIS88A	50	2SC1923	50	LS93	36	LS363	40	LS364	40	LS365	40	LS366	40
BC149	9	BF898	105	TIS90	30	2SC1945	225	LS95	45	LS367	40	LS368	40	LS369	40	LS370	40
BC149B	10	BF929/84	28	TIS91	32	2SC1963	90	LS96	120	LS371	40	LS372	40	LS373	40	LS374	40
BC153/4	27	BF956	28	TIX307	12	2SC1987	90	LS97	43	LS375	40	LS376	40	LS377	40	LS378	40
BC157/8	10	BFX87/8	28	TIX109	12	2SC1969	198	LS109	30	LS379	40	LS380	40	LS381	40	LS382	40
BC159	11	BFY5/2	23	TIX300	13	2SC2028	85	LS112	30	LS383	40	LS384	40	LS385	40	LS386	40
BC160	45	BFY56	32	TIX301/2	16	2SC2029	180	LS113	40	LS387	40	LS388	40	LS389	40	LS390	40
BC167/8	10	BFY64	35	TIX303	25	2SC2078	195	LS114	35	LS391	40	LS392	40	LS393	40	LS394	40
BC169	10	BFY81	120	TIX304	18	2N1401	112	LS115	40	LS395	40	LS396	40	LS397	40	LS398	40
BC169C	10	BR339	40	TIX314	25	2SC2314	85	LS122	44	LS399	40	LS400	40	LS401	40	LS402	40
BC170	15	BSX20	20	TIX326	30	2SC2166	165	LS124	105	LS403	40	LS404	40	LS405	40	LS406	40
BC172/3	11	BSY95A	25	TIX341	30	2SC1679	190	LS125	30	LS407	40	LS408	40	LS409	40	LS410	40
BC177/8	10	BU105	170	TIX500/1	14	2N6027	32	LS126	30	LS411	40	LS412	40	LS413	40	LS414	40
BC179/81	20	BU205	190	TIX501/2	15	3N128	112	LS132	45	LS415	40	LS416	40	LS417	40	LS418	40
BC181	10	BU208	200	TIX503	18	3N140	112	LS133	35	LS419	40	LS420	40	LS421	40	LS422	40
BC184	10	E421	250	TIX505	25	40311	60	LS136	60	LS423	40	LS424	40	LS425	40	LS426	40
BC182L	10	MD800/1	250	TIX531	25	40313	125	LS138	35	LS427	40	LS428	40	LS429	40	LS430	40
BC183L	10	MJ400	150	TIX550	25	40315	68	LS139	38	LS431	40	LS432	40	LS433	40	LS434	40
BC184L	10	MJ491	175	TIX697	23	40316	85	LS151	39	LS435	40	LS436	40	LS437	40	LS438	40
BC187	26	MJ295	90	TIX698	40	40381	50	LS153	39	LS439	40	LS440	40	LS441	40	LS442	40
BC187B	10	MJE340	200	TIX699	48	40382	50	LS155	39	LS443	40	LS444	40	LS445	40	LS446	40
BC192L	10	MJE365	100	TIX706A	19	40408	95	LS158	35	LS447	40	LS448	40	LS449	40	LS450	40
BC213	10	MJE371	100	TIX708	19	40411	280	LS157	35	LS451	40	LS452	40	LS453	40	LS454	40
BC213L	10	MJE295	99	TIX918	35	40467	95	LS158	35	LS455	40	LS456	40	LS457	40	LS458	40
BC214	10	MJE305	70	TIX113/2	24	40468	60	LS160	41	LS459	40	LS460	40	LS461	40	LS462	40
BC214L	10	MPF102	66	TIX1303	60	40594	90	LS161	41	LS463	40	LS464	40	LS465	40	LS466	40
BC217	14	MPF103/4	36	TIX1304	65	40595	95	LS162	41	LS467	40	LS468	40	LS469	40	LS470	40
BC237	14	MPF106	40	TIX167B	160	40603	90	LS163	41	LS471	40	LS4					



Just **50p** will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

★ Lowest prices — Largest stocks ★

★ Expert staff — Sound advice ★

★ Choose your DIY HiFi Speakers in the comfort ★ of our listening lounge.

(Customer operated demonstration facilities)

★ Ample parking ★

★ Access · Visa · American Express accepted ★



☎
0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



HART KITS

WINTON TUNER

Complete designer approved kits (including pre-aligned AM front end) will be available from us for this excellent design. Phone or write for your free copy of lists.

WINTON AMPLIFIER

We have taken over the supply of kits for this high performance 'PW' design. Size and appearance match above tuner. Reprints of all articles describing design 85p VAT and post free.

VFL 910 VERTICAL FRONT LOADING CASSETTE DECK

Very high quality cassette mechanism as used in our Linsley Hood cassette recorder kit. Wow and flutter .09%. Memory counter. Sendust alloy head. 12V DC. Frequency generating feedback servo motor. Oil damped eject. £31.99 + VAT.

SF925 FRONT LOADING SOLENOID CONTROL CASSETTE DECK

Having full solenoid control of all functions this deck has numerous uses, most obvious is microcomputer drive, particularly since there is a facility to read the tape in the fast modes. Deck is full hi fi quality and is fitted with memory counter, Hall IC for auto stop and stereo R/P head. Price only £38.90 + VAT.

HART TRIPLE E PURPOSE TEST CASSETTE TC 1

Sets up tape speed, head azimuth and VU level all without test instruments. Fantastic value at only £2.70 + VAT.

CASSETTE HEADS

We hold large stocks of cassette heads ranging from mono to 4 track for domestic and industrial use including the fabulous HS16 sendust alloy super head at £8.20 + VAT. Remember your tape machine is only as good as its head. A worn head will lose the high frequency information on the tape and a very worn head will chew up the tape as well. Full technical spec of all heads is in our lists.

Write or phone for your copy of our free lists.

HART ELECTRONIC KITS LTD

Penylan Mill,
Oswestry, Shropshire SY10 9AF.
Tel: 0691 2894
Telex: 35661 HARTEL G.

INDEX TO ADVERTISERS

A.H. Supplies	78
A.J.H. Electronics	11
Aero & General Supplies	60
Allweld Engineering	28
Amateur Electronics	70
Amateur Radio Exchange	58
Ambit International	10, 11
Amcomm Services	48
Anglia Components	60
Antex Electronics	Cover 3
Auto Marine Development Company	22
Barrie Electronics	85
Bedford Audiocomm	88
Bib Hi-Fi	81
Birkett J	84
Bredhurst Electronics	Cover 2
British National Radio & Electronics School	13
C.Q. Centre	10
Cambridge Kits	83
Caranna C	84
Catronics	68
Chordgate Ltd	84
Cocks Hugh	82
Colomor (Electronics) Ltd	14
Crimson Components	8
C.R. Supply Co	82
Datong Electronics	32
Davtrend Ltd	60
Elden Electronics	80
Electrovalue Ltd	76
Electro-Tech Components Ltd	62
Flairline Supplies	83
G.S.C.	9
Garex Electronics	14
Gemini Electronic Components	12
Gemini Communications	22
Golledge Electronics PR	84
GT Technical Information Service	84
G2 Dym Aerials & Projects	84
H.A.C. Shortwave	8
Heath Electronics Ltd	60
Henry's Radio	85
Hart Electronics	87
I.C.S. Intertext	80, 84
I.L.P. Electronics Ltd	12
Intel Electronic Components	10
Lee Electronics	24, 32
Leeds Amateur Radio	16
Lexton Harvey	27
Lowe Electronics	2, 3
M & B Radio	62
Macdonald Publishers Ltd	88
Maplin Electronic Supplies	Cover 4
Marco Trading	76
Mhel Electronics	83
Microwave Modules	79
Modular Electronics	76
Monolith Electronics Ltd	76
Newnes Technical Books	11
Northern Communications	68
Osmabet	78
P.M. Components	85
Packer Electronics	28
Paddington College	83
Photo Acoustics Ltd	68
Powell T	12
Progressive Radio	84
R.S.T. Valve Mail Order	80
Radio Component Specialists	8
Radio Shack	30
S.E.M.	28
Science of Cambridge	74, 75
Scientific Wire Company	83
South Midlands Communications	15
South West Aerial Systems	84
Southern Valve	82
Stephens-James Ltd	28
Swindon Radio & Electronic Rally	82
Tandy Corporation (UK) Ltd	77
Technomatic Ltd	78
Tempus	88
Thanet Electronics	4, 5, 6, 7, 22
V & F Smallcraft	80
Waters & Stanton	53
Watford Electronics	86
Western Electronics	32
West London Direct Supplies	8
Williams AR	62
Wilmslow Audio	87
Wood & Douglas	14

RADIO AND TELEVISION SERVICING 1980-81 MODELS

Editor
R N Wainwright, T.Eng. (CEI), F.S.E.R.T.

The latest volume in the Radio and Television Servicing series—

- Quick reference to hundreds of models
- Essential service information—Television (Colour and Monochrome), Radio—(Portables, Clock Radios, Cassettes, In-car, Unit Audio, Record Players)
- Latest design techniques described
- Receiver adjustment and alignment
- Manufacturers' recommended modifications

Receiver makes covered in *Radio and Television Servicing 1980-81 Models*:

Television Receivers (Colour and Monochrome) Alba, Bush, Crown, Decca, Dynatron, Ferguson, G.E.C., Grundig, Hitachi, I.T.T., J.V.C., Murphy, National, Philips, Plustron, Pye, Roberts Video, Sanyo, Sony, T.C.E., Toshiba, Ultra, Vega, Waltham.

Radio Receivers (Tape Recorders, Record players, etc.) Alba, Binatone, Bush, Crown, Ferguson, Fidelity, Hacker Sound, Hitachi, J.V.C., Murphy, Philips, Pye, Roberts Radio, Sanyo, Sharp, Sony, Ultra, Vega, Waltham.

An essential reference book for all service engineers. £17.50 13 August

Previous volumes available are as follows:
 1968-69 (£4.25) 1971-72 (£6.00) 1973-74 (£6.50) 1974-75 (£7.00) 1975-76 (£8.50) 1976-77 (£9.50) 1977-78 (£10.00) 1978-79 (£11.50) 1979-80 (£14.50)

Enquiries to Sales Dept., Macdonald and Company Publishers Ltd., From booksellers, or in case of difficulty, please use the form below.

To: The Sales Department, Macdonald and Company Publishers Ltd., 8 Shepherdess Walk, London N1.

Please send me copy (ies) of RADIO AND TELEVISION SERVICING 1980-81 Models at £17.50 per copy (post paid).

I enclose my cheque/PO for £
 (made payable to Macdonald and Company Publishers Ltd.) or debit my —

Access American Express
 Diners Club Barclay Card

My card number is

Signature Date

GIRO A/C No. 205/4221

Name

Address

Please allow 28 days for delivery

MACDONALD
 Macdonald & Co. (Publishers) Ltd.


THE LAST WORD IN POCKET CALCULATORS

The ultra-capacity calculator with "Computer Talk" programming via upper and lower case dot matrix scrolling display

CASIO FX602P

- * 88 memories, up to 512 steps
- * Full memory retention
- * A variety of jump commands
- * Up to 9 sub-routines, up to 9 levels
- * 33 parentheses

RRP £84.95 **ONLY £74.95**

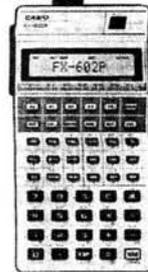

- * LCD alpha/numeric (dot matrix) scrolling display with 86 characters
- * Variable range of input capacity from 32 program steps with 88 independent memories to 512 steps with 22 memories.
- * Memory and program retention when switched off.
- * Up to 10 pairs of unconditional jumps (GOTO). Manual jump (GOTO).
- * Conditional jumps and count jumps. Indirect addressing.
- * Up to 9 subroutines, up to 9 depths (levels).
- * 50 built-in functions, all usable in programs.
- * PAM (Perfect Algebraic Method) with 33 parentheses at 11 levels.
- * An almost infinite number of programs can be stored on cassette tape via optional FA-1 adapter. (Price £19.95).
- * Two lithium batteries last approx. 660 hours (continuous) with Auto Power Off after approx. 6 minutes non-use.
- * Dims: 9.6 x 71 x 141.2mm (3/8 x 2 1/2 x 5 1/2"). Wallet.

Send 20p for details of Casio's best selling products.

Including:-

- FX3500P. 38 step programmable for only £22.95.
- CA90 and CA91. Calculator alarm watches with Digital Space Invader Game. Stopwatch, Dual Time from £19.95.
- VL-1. Mini synthesiser with Record/Playback, 5 instrument voices, 10 rhythm accompaniments etc. Only £35.95.

PRICES include VAT, P&P. Return of post service. Send cheque, P.O. or phone your ACCESS or BARCLAYCARD number to/

TEMPUS Dept. PW, Beaumont Centre, 164-167 East Road, Cambridge CB1 1DB. Tel: 0223 312866.

AZDEN

The Scanning Tranceivers with detachable control head.



PCS-3000 £215
 2M FM 25 watts (illustrated)

PCS-2800 10M 10 watts £179
 (cable kit extra)

FDK DOWN IN PRICE
MULTI-700 FM £189
MULTI-750 2M FM/SSB £285



Main Yaesu Dealer

Phone for details on latest models.

Also in stock: BANTEX, JAYBEAM, M/M RSGB PUBLICATIONS ETC.

Bedford 0234 854133

AUDIOCOMM

76 BEDFORD ROAD,
 KEMPSTON, BEDS

CREDIT SALE, ACCESS, BARCLAYCARD, CREDITCHARGE.



INTRODUCING THE NEW "READY TO GO" SOLDERING IRON
WITH BUILT-IN FINGER PROTECTION FROM

A N T E X

Models XS-BP (25 watt) and CS-BP (17 watt) have moulded-on safety plugs, 'unbreakable' handles and detachable hooks-cum-finger-protectors.

High class insulation by ceramic shaft, negligible leakage.

Long life iron and nickel plated bits, easily interchanged, slide on or off stainless steel shafts which enclose the heating elements for maximum efficiency of heat transfer.

Both models available for 240v, 115v, 24v or 12 volt. R.S.P. £5.30 plus V.A.T.

ANTEX LIMITED, Mayflower House, Plymouth, Devon PL1 1BR. Telephone: (0752) 667377.

MAPLIN make it easy...

in
HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)



in
SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our
CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.
On sale now in all branches
WH Smith price £1.

In case of difficulty check the coupon below.

by
MAIL ORDER
A fast service
You can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

make it easy... with MAPLIN

The
Maplin Matinee
Amazing value for
only £299.95 plus £99.50
for cabinet if required
(Carriage Extra).

Easy to build,
superb specification.
Comparable with organs selling for
up to £1,000.



MAPLIN ELECTRONIC SUPPLIES LTD.

Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____

Address _____

PW981

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911