

OCTOBER 1983 90p

Australia \$1.50
New Zealand \$1.60
Malaysia \$4.95
IR £1.30 (inc. VAT)

Practical Wireless

THE RADIO MAGAZINE

Test Gear Special




**Sensitive
Capacitance Meter**

QRP SWR Bridge

**QRP RF
Wattmeter**

PLUS

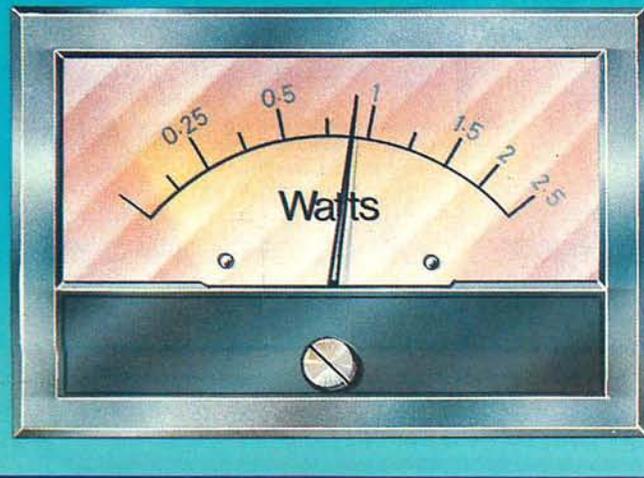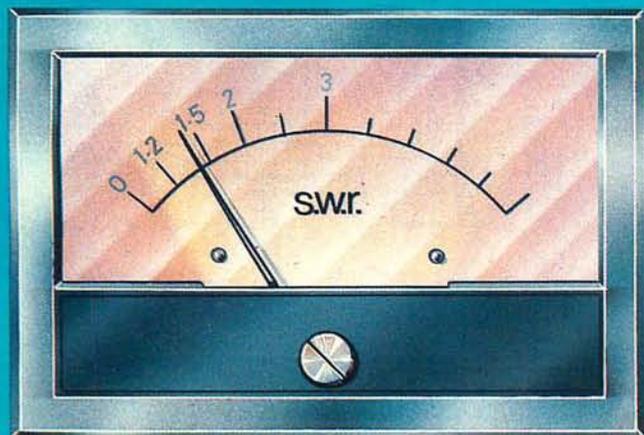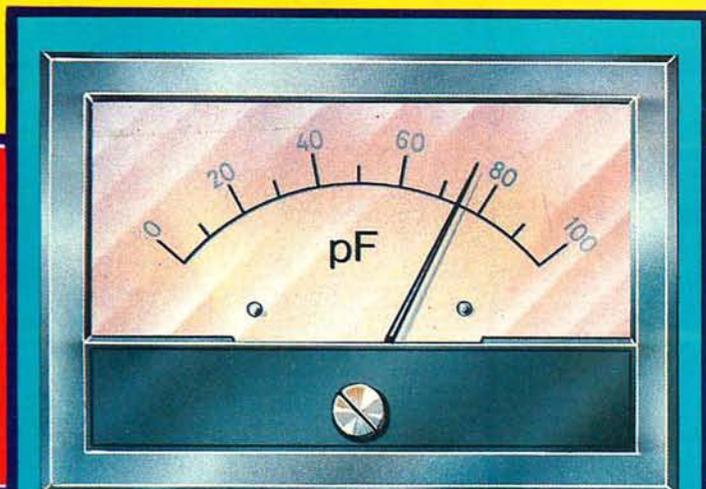**Simple Wavemeter
For 144 MHz
Digital Calibrator**



AUTHORISED DEALERS FOR ALL EQUIPMENT WE SELL



YAESU FRG7700 Gen Cov Receiver £335 inc VAT & Carriage



YAESU		£	c&p
FT1	H.F. Transceiver - Gen. Cov. Receive	1450.00	(-)
FT102	Amateur Band H.F. Transceiver	839.00	(-)
SP102	Matching speaker	49.00	(2.00)
FC102	Matching A.T.U. 1.2kW.PEP/AV	225.00	(2.00)
FC902	All Band A.T.U.	135.00	(1.50)
SP901	External Speaker	31.00	(1.50)
FT77	HF mobile transceiver 9 band	515.00	(-)
FP700	Power supply/speaker	110.00	(-)
FC700	A.T.U.	99.00	(1.00)
FT757GX	H.F. Amateur Bnd Tx Gen. Cov. Rx	POA	
FC757AT	Automatic A.T.U.	POA	
FP757GX	Power Supply	POA	
FT726R(2)	Multimode multiband base station C/W 2M	699.00	(-)
FT230R	Transceiver 2M 25W F.M. mobile	255.00	(-)
FT290R	Transceiver 2M 2.5W Multimode portable	285.00	(-)
FT790R	Transceiver 70cm 1W Multimode portable	349.00	(-)
NC11C	Trickle Charger (240V ac)	9.20	(0.75)
MMB11	Mobile mount	24.90	(1.00)
CS1A	Soft carrying case	3.85	(0.75)
FL2010	Linear Amp. 2M 10W	59.00	(1.20)
FT480R	2M Multimode mobile transceiver	POA	(-)
FT780R	70cm Multimode mobile transceiver	POA	(-)
FT208R	Handheld 2M F.M. transceiver	199.00	(-)
FT708R	Handheld 70cm F.M. transceiver	229.00	(-)
NC9C	Trickle charger (240V ac)	8.00	(0.75)
NC8C	Base Fast charger	50.00	(1.50)
PA3	Battery eliminator and charger (12V dc)	14.20	(1.00)
FRG7700	H.F. Receiver 0.15-30MHz all mode	335.00	(-)
FRG7700M	FRG7700 c/w 12 channel memory	399.00	(-)
MEMG7700	Memory Unit	98.00	(1.00)
FRT7700	Antenna tuner/switch	42.50	(1.00)
FRA7700	Active Antenna	38.70	(1.00)
YM34	Stand mic 500/50K 8 pin	23.40	(1.50)
YM38	Stand mic 500/50K 8 pin + SCAN	27.20	(1.50)
YD148A	Stand mic 600/50K 4 pin	22.60	(1.50)
MD18B	Stand mic 600/50K 8 pin + SCAN	49.80	(1.50)
FF501DX	Low pass filter	25.70	(1.00)
FSP-1	Mobile speaker 8 ohm 6W	9.95	(0.75)
YH-55	Headphones 8 ohm	9.95	(0.75)
YH-77	Lightweight headphones	9.95	(0.75)
QTR24D	World time clock (quartz)	31.40	(1.00)

ICOM		£	c&p
IC-751	New H.F. Transceiver	POA	(-)
IC-740	H.F. 9 Band Transceiver	769.00	(-)
IC-720A	H.F. Tx + Gen. Cov. Rx	949.00	(-)
IC-PS20	P.S.U. for above with Speaker	155.00	(-)
IC-PS15	P.S.U.	119.00	(-)
IC-2KL	H.F. Linear 500 Watts O/P	915.00	(-)
IC-2KLPS	P.S.U. for above	256.00	(-)
IC-AT500	1.8-30MHz Auto A.T.U.	349.00	(-)
IC-AT100	3.5-30MHz Auto A.T.U.	249.00	(-)
IC-271E NEW	2M Multimode Base Station	POA	(-)
IC-290E	2M Multimode Mobile	379.00	(-)
IC-25E	2M FM Mobile 25W	269.00	(-)
IC-2E	2M Handheld	179.00	(-)
IC-4E	70cm Handheld	199.00	(-)
IC-BC30	Base Charger	45.00	(1.50)
IC-HM9	Speaker + Microphone	12.00	(1.00)
IC-ML1	10 Watt 2M Booster IC2E	59.00	(1.00)
IC-SM5	Desk Mic (8 pin for Icom only)	29.00	(1.00)
IC-R70	General Cov. Receiver	499.00	(-)


F D K		£	c&p
Multi 700AX	2M FM Mobile 25W	215.00	(-)
Multi 750X	2M Multimode	315.00	(-)

WELZ		£	c&p
SP15M	SWR PWR Meter HF/200W	35.00	(1.00)
SP45M	SWR PWR Meter 2M/70cm 100W	51.00	(1.00)
SP200	SWR PWR Meter H.F./2M 1KW	69.95	(1.50)
SP300	SWR PWR Meter H.F./2M/70cm	97.00	(1.50)
SP400	SWR PWR Meter 2M/70cm 150W	69.95	(1.50)
SP600	SWR PWR Meter H.F./2M/20KW	97.00	(2.00)
SP10X	SWR PWR Meter H.F./2M	24.45	(0.75)
SP350	SWR PWR Meter H.F./2M/70 200W	59.95	(1.50)
SP380	SWR PWR Meter H.F./2M/70cm	49.00	(1.00)
AC38	A.T.U. 3.5 to 30MHz 400W PEP	65.00	(1.00)
CT15A	15/50W Dummy Load (PL259)	7.95	(0.75)
CT15N	15/50W Dummy Load (N type plug)	13.95	(0.75)
CT300	300/1kW Dummy Load	49.50	(2.00)

COAXIAL SWITCHES		£	c&p
-	2 Way Toggle Switch (H.F./2M)	6.00	(0.50)
SA450	2 Way Diecast - SO239 (500MHz)	10.00	(0.75)
SA450n	2 Way Diecast - N plugs (500MHz)	12.95	(0.75)
CH20A	2 Way WELZ - SO239 (900MHz)	17.95	(1.00)
CH20N	2 Way WELZ - N plugs (900MHz)	31.95	(1.00)
-	5 Way Western Rotary (H.F.)	15.95	(1.00)
-	3 Way LAR Rotary (H.F.)	19.95	(1.25)

TRIO		£	c&p
TS830S	9 Band TX General Cov Rx	1216.00	(-)
TS830S	160-10m Transceiver 9 Bands	697.00	(-)
VFO230	Digital V.F.O. with Memories	243.00	(2.00)
AT230	All Band ATU/Power Meter	135.00	(2.00)
SP230	External Speaker Unit	41.00	(1.50)
TS430S	160-10m Transceiver	736.00	(-)
PS430	Matching Power Supply	112.00	(3.00)
SP430	Matching Speaker	29.44	(1.50)
MB430	Mobile Mounting Bracket	11.27	(1.50)
FM430	FM Board for TS430	34.50	(1.00)
TS130S	8 Band 200W Pep Transceiver	559.00	(-)
TS130V	8 Band 20W Pep Transceiver	456.00	(-)
VFO120	External V.F.O.	98.00	(1.50)
TL120	200W Pep Linear for TS120V	167.00	(1.50)
MB100	Mobile Mounts for TS130/120	18.60	(1.50)
SP120	Base Station External Speaker	26.40	(1.50)
AT130	100W Antenna Tuner	93.00	(1.50)
PS20	AC Power Supply - TS130V	57.96	(2.50)
MC50	Dual Impedance Desk Microphone	30.80	(1.50)
MC35S	First Microphone 50K ohm IMP	14.70	(0.75)
MC30S	First Microphone 500 ohm IMP	14.70	(0.75)
LF30A	HF Low Pass Filter 1kW	21.00	(1.00)
TR9130	2M Multimode	433.00	(-)
TS9500	70cm Multimode	419.00	(-)
BO9A	Base Plinth for TR9130	39.00	(0.50)
TR7730	2M FM Compact Mobile 25W	199.00	(-)
TR2300	FM Portable	152.00	(-)
VB2300	10W Amplifier for TR2300	65.70	(1.50)
MB2	Mobile Mount for TR2300	21.00	(1.50)
TR3500	70cm Handheld	250.00	(-)
TR2500	2M FM Synthesised Handheld	232.00	(-)
ST2	Base Stand	51.90	(1.50)
SC4	Soft Case	13.80	(0.50)
SMC25	Speaker Mike	16.10	(1.00)
PB25	Spare Battery Pack	25.00	(1.00)
MS1	Mobile Stand	31.90	(1.00)
R600	Gen. Cov. Receiver	257.00	(-)
R2000	Synthesiser 200KHz-30MHz Receiver	398.00	(-)
HC10	Digital Station World Time Clock	67.70	(1.50)
HS5	Deluxe Headphones	23.00	(1.00)
HS4	Economy Headphones	11.27	(1.00)
SP40	Mobile External Speaker	14.26	(1.00)

MINI- PRODUCTS HQ-1

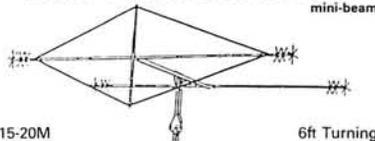

10-15-20M 1200 watts 6ft Turning Radius

£139 (£5 carriage)

MOBILE SAFETY MICROPHONES		£	c&p
ADONIS AM 2025	Clip-on	24.50	(-)
ADONIS AM 202H	Head Band + Up/Down Buttons	34.50	(-)
ADONIS AM 202F	Swan Neck + Up/Down Buttons	37.00	(-)

DATONG D70 MORSE TUTOR £56.35



DATONG PRODUCTS		£	c&p
PC1	Gen. Coverage Converter HF to 2M	137.42	(-)
VLF	Very Low Frequency Converter	29.90	(-)
FL1	Frequency Agile Audio Filter	79.35	(-)
FL2	Multi-mode Audio Filter	89.70	(-)
FL3	FL2 + Auto Notch	129.37	(-)
ASP	Auto RF Speech Clipper (4pin plugs)	82.80	(-)
D75	Manually controlled RF Speech Clipper	56.35	(-)
RFC/M	RF Speech Clipper Module	29.90	(-)
D70	Morse Tutor	56.35	(-)
AD370	Outdoor Active Antenna	64.40	(-)
AD270	Indoor Active Antenna	47.15	(-)
MK	Keyboard Morse Sender	137.42	(-)
Codecall	Selective Calling Device	33.92	(-)
RFA	Wideband Preamp/Filter	33.92	(-)
DC144/28	2M to 28MHz converter	39.67	(-)
MPU	Mains Power Unit	6.90	(-)
ANF	Auto notch filter (Audio)	67.85	(-)
SRB2	Auto Woodpecker Blanker	86.25	(-)

MICROWAVE MODULES		£	c&p
MMT144/28	2M Transverter for HF Rig	109.95	(-)
MMT432/28S	70cm Transverter for HF Rig	159.95	(-)
MMT432/144R	70cm Transverter for 2M Rig	184.00	(-)
MMT70/28	4M Transverter for HF Rig	119.95	(-)
MMT70/144	4M Transverter for 2M Rig	119.95	(-)
MMT1296/144	23cm Transverter for 2M Rig	184.00	(-)
MML144/30	2M 30W Linear Amp	69.95	(-)
MML144/100S	2M 100W Linear Amp (10W I/P)	139.00	(-)
MML144/100LS	2M 100W Linear Amp (3W I/P)	159.00	(-)
MML432/30	70cm 30W Linear Amp (3W I/P)	99.00	(-)
MML432/100	70cm 50W Linear Amp	109.95	(-)
MML432/100	70cm 10/100W Linear Amp	228.64	(-)
MM2001	RTTY to TV Converter	189.00	(-)
MM4000	RTTY Transceiver	269.00	(-)
MMCS50/28	6M Converter to HF Rig	29.90	(-)
MMC70/28	4M Converter to HF Rig	29.90	(-)
MM144/28	2M Converter to HF Rig	37.90	(-)
MMCA32/28S	70cm Converter to HF Rig	29.90	(-)
MMCA32/144S	70cm Converter to 2M Rig	37.90	(-)
MMCA35/600	70cm ATV Converter	27.90	(-)
MMK1296/144	23cm Converter to 2M Rig	69.95	(-)
MMD050/500	500MHz Dig. Frequency Meter	75.00	(-)
MMD600P	600MHz Prescaler	29.90	(-)
MMDP1	Frequency Counter Probe	14.90	(-)
MMA28	10M Preamp	16.95	(-)
MMA144V	2M RF Switched Preamp	34.90	(-)
MMF144	2M Band Pass Filter	11.90	(-)
MMF432	70cm Band Pass Filter	11.90	(-)
MMS1	The Morse Talker	115.00	(-)

TELEREADERS (CW & RTTY)		£	c&p
TONO 550		299.00	(-)
TONO 9000		669.00	(-)

POWER SUPPLIES		£	c&p
DRAE	4 AMP 30.75 (1.50) 12 AMP 74.00 (2.00)		
	6 AMP 49.00 (2.00) 24 AMP 105.00 (3.00)		
BNOS	6 AMP 48.00 (-) 25 AMP 125.00 (-)		
	12 AMP 86.00 (-) 40 AMP 225.00 (-)		

ROTATORS		£	c&p
Hirschman	RO250 VHF Rotor	45.00	(2.00)
9502B	Colorator (Med. VHF)	56.95	(2.00)
EMR400	Ainco	89.95	(2.50)
KR400RC	Kenpro - inc lower clamps	125.00	(2.50)
KR600RC	Kenpro - inc lower clamps	175.00	(3.00)

DESK MICROPHONES		£	c&p
SHURE 444D	Dual Impedance	45.95	(1.50)
SHURE 526T	Mk II Power Microphone	56.00	(1.50)
ADONIS AM 303	Preamp Mic. Wide Imp.	29.00	(-)
ADONIS AM 503	Compression Mic 1	39.00	(-)

TEST EQUIPMENT		£	c&p
Drae VHF	Wavemeter 130-450MHz	27.50	(-)
DM81	Trio Dip Meter	71.00	(0.75)
MMD50/500	Dig. Frequency meter (500MHz)	75.00	(-)



MAIL ORDER
Mon-Sat. 9-12.30/1.30-5.30

All prices correct at time of going to press.

BREDHURST ELECTRONICS

RETAIL
Mon-Sat. 9-12.30/1.30-5.30



Goods normally despatched within 24 hrs. **HIGH STREET, HANDCROSS, WEST SUSSEX. TEL. 0444 400786**

E.&O.E.

Practical Wireless

FOR THE **Radio** ENTHUSIAST ...

OCTOBER 1983 VOL. 59 NO. 10 ISSUE 919

Contents

Staff

- 27 Air Test**
Standard C7900/C8900 u.h.f./v.h.f. mobiles.
Icom IC-505 50MHz transceiver
- 30 Amateur Wireless Before 1914—2**
G. R. Jessop G6JP
- 40 Sensitive Capacitance Meter**
E. W. Nield GW3ARP
- 43 Digital Calibrator**
E. A. Rule
- 48 Simple Wavemeter for 144MHz**
James A. Brett G6EBR
- 49 General Purpose Buffer Amplifier**
M. J. Darby
- 50 QRP SWR Bridge**
Tony Smith G4FAI
- 53 QRP RF Wattmeter**
Tony Smith G4FAI
- 58 Antennas—9**
F. C. Judd G2BCX
- 63 Basic QSOs in Spanish—2**
*Gareth W. Roberts GW4JXN and
Idefonso Sevilla EA7BWX*

EDITORIAL OFFICES

Practical Wireless
Westover House
West Quay Road
Poole, Dorset BH15 1JG
☎ Poole 671191

Geoff Arnold T.Eng(CEI) G3GSR
Editor

Dick Ganderton C.Eng., MIERE, G8VFH
Assistant Editor

Steve Hunt
Art Editor

John Fell G8MCP
Technical Editor

Alan Martin G8ZPW
News & Production Editor

Elaine Howard G4LFM
Technical Sub-Editor

Rob Mackie
Technical Artist

Keith Woodruff
Assistant Art Editor

Sylvia Barrett
Secretarial

ADVERTISEMENT OFFICES

Practical Wireless
King's Reach Tower
Stamford Street
London SE1 9LS
Telex: 915748 MAGDIV-G

Dennis Brough
Advertisement Manager
☎ 01-261 6636
☎ 01-261 6872

Roger Hall G4TNT (Sam)
Ad. Sales Executive
☎ 01-261 6807

Claire Gerrish
Secretary
☎ 01-261 6636

Barbara Blake
Classified Supervisor
☎ 01-261 5897

Ian Sweeney
Make-up & Copy
☎ 01-261 6570

Regulars

- | | | |
|------------------|--------------------|------------------|
| 95 Advert Index | 19 News | 34 Products |
| 37 Benny | 39 Next Month | 33 PW Programs |
| 17 Comment | 67 On the Air | 18 PW RUIS |
| 62 Did You Know? | 66 Out of Thin Air | 17 Services |
| 38, 56 Letters | 66 Passport | 24, 62 Swap Spot |

COPYRIGHT © IPC Magazines Limited 1983. Copyright in all drawings, photographs and articles published in *Practical Wireless* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Practical Wireless* to ensure that the advice and data given to our readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

Practical Wireless, October 1983

LOWE SHOPS in matlock,

TELEPHONE 0629.2817 2430 4057 4995

Lowe Electronics in Matlock, located on the Chesterfield road out of Matlock, that is the A632 and open Tuesday to Friday from 9am to 5.30pm (closed for lunch 12.30 to 1.30) and Saturday, open all day from 9am to 5pm. A visit to Matlock can be an outing for the family, the local scenery, the Heights of Abraham, Lovers Walk etc. Ample free parking in our car park and when you have browsed then lunch in one of the towns pleasant restaurants. Amateur Radio with the family in mind.

in glasgow,

TELEPHONE 041.945.2626

Lowe Electronics in Glasgow, located at 4/5 Queen Margarets Road, which you will find off Queen Margarets Drive (take Great Western road out of the City and turn right at the Botanical Gardens traffic lights). A quiet sedate part of the city, easy street parking and a warm welcome from Sim, our shop manager. Open all day from Tuesday to Saturday, 9 am till 5.30pm during the week and 9am till 5pm on Saturday. Whilst in the area the Botanical Gardens are well worth a visit. The Glasgow Shop has a full display of our range of amateur radio products and a stock room to meet your every demand. For your Amateur Radio needs visit Lowe Electronics in Glasgow.

in darlington,

TELEPHONE 0325.486121

Lowe Electronics in the North East of England, set in the delightful market town of Darlington, the shop displays the full range of amateur products sold by the company. Our address in the town is 56 North Road, that is the A167 Durham road out of Darlington. Open Tuesday to Friday from 9am till 5.30pm, Saturday from 9am till 5pm (closed for lunch 12.30 to 1.30). A huge free car park across the road, a large supermarket, bistro restaurant and banking facilities combine to make a visit to this delightful market town a pleasure for the whole family.


in london,

TELEPHONE 01.837.6702

Lowe Electronics in London, our shop in the Capital City, easily found on the lower sales floor of the Hepworths' shop on Pentonville Road, within 3 minutes walk of Kings Cross railway station. Open all day Monday to Saturday, six days a week, from 9.30am to 5.30pm during the week and from 9.30am to 5pm on Saturday, a warm and courteous welcome, together with sound advice awaits those who enter. The entire range of amateur products is on display, backed by a considerable amount of stock. When in the City, visit Lowe Electronics.

The TW4000A is the latest step forward in Trio's programme of providing today's radio amateur with the very best in equipment. Following the success story of the Trio TS780 dual band base station transceiver, the TW4000A gives the mobile operator a superb FM transceiver for both 70 centimetres and the 2 metre band. Not only for mobile operation is the TW4000A perfect but also for s/hack use where the rig with its scanning and dual band facilities enable the enthusiastic amateur to keep in touch with the local scene.

- The TW4000A covers in one compact transceiver both the 2 metre band (144.000 to 146.000 MHz) and also the full 10 MHz of the 70 centimetre band (430.000 to 440.000 MHz). Measuring 60mm high, 161mm wide, 217mm deep and weighing only slightly more than 2.0 kg, the TW4000A is smaller than most current 2 metre transceivers.
- Added to the exceptional receive performance, now a Trio standard by which others are judged, is the TW4000A's 25 watt capability on both 2 metres and 70 centimetres. Using the TW4000A not only can you hear weak signals on either band but they can hear you too. A HI/LO switch reduces the output power to 5 watts when required.
- A green backlit liquid crystal display gives frequency, memory channel, repeater offset, VFO A or B, scan function, channel occupied and "ON AIR" information. Brightly illuminated, the display can easily be ready under unfavourable conditions. All important controls are illuminated for easy operation during darkness.
- Ten memory channels are provided which store frequency, band and repeater offset (on 2 metres minus 600 KHz shift, on 70 centimetres plus 1.6 MHz shift). Memory 1 is used for priority watch, memories 8 and 9 for instant recall and memory 0 for split channel use (cross band operation). An internally fitted lithium battery gives memory backup.
- Frequency scan is extremely versatile in that the rig can be programmed to scan either all memory channels or those holding either 2 metre or 70 centimetre frequencies. The rig can also be programmed to skip those channels which the operator does not wish to monitor. The scan direction can also be changed by using the UP/DOWN switch on the microphone. In order that an important contact is not missed, when in priority watch mode, the rig switches back from the frequency in use to memory channel 1 for one second out of ten. The two most used frequencies can be placed in memories 8 and 9 respectively, common channel scan checking each alternatively for approximately 5 seconds.
- Two VFO's are provided tuning in either 5 or 25 KHz steps, the UP/DOWN shift switch on the microphone providing control.
- Full repeater facilities are included giving the correct frequency shift, 1750 Hz access tone, and of course the essential reverse repeater shift.

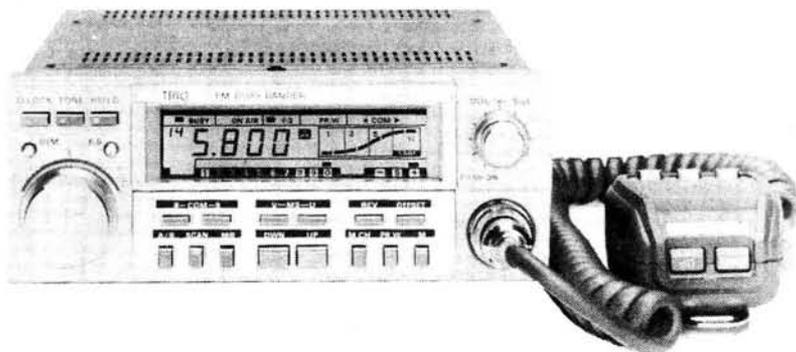

70centimetres & 2metres, 2 bands, 1 rig, **TW4000A**

DUAL BAND FM MOBILE
VOICE MODULE VS1

£469.00 inc VAT.
£24.50 inc VAT.

Now, an opportunity for you to buy at a greatly reduced price the **LOWE TX40** c.b. transceiver. Now priced at £29.50 carriage £3.00, the **LOWE TX40** is a reliable, well built and popular rig. A de-luxe version of the transceiver fitted with an additional filter is available for an additional £8.50. Take this opportunity to buy at this fantastic price a **LOWE TX40** c.b. transceiver.

LOWE ELECTRONICS

Chesterfield Road, Matlock, Derbyshire. DE4 5LE.
Telephone 0629 2817, 2430, 4057, 4995. Telex 377482.
(Delivery of stock items normally by return of post)





South Midlands

FREE FINANCE

on regular priced YAESU and many other lines.
(Invoice Balances over £120)

SMC's SUMMER SALE OF YAESU



FANTASTIC PRICE REDUCTIONS ON OVERSTOCKED ITEMS AND DISCONTINUED LINES : LIMITED STOCKS AVAILABLE

**FTV107R Transceiver Grey
c/w 2m module**



£89.00

FV90/DM Digital VFO



£119.00

FTV901R



£139.00

**Transverter
c/w 2m module
fitted**

£119.00



FV101DM Keyboard VFO

All prices include VAT and Delivery

**FTV707R
£99.00**



Transceiver c/w 2m module

**Special Low Price
due to bulk
purchase**



**FT102 £839
NOW ONLY
£685**

SMC HAS ACQUIRED FROM YAESU THE LAST FT225RD.

Now's your chance to buy one of the most sought after 2m multimode transceivers ever!!!

This transceiver is up for Dutch Auction, so make us an offer and you too could be using a radio like the DX Kings or the many contest winners. ● Closing date for offers Wednesday, October 12th. Normal SMC Guarantee.



NOW AVAILABLE FOR HIRE – 60ft TRAILER MOUNTED TOWER.

Available most weekdays and weekends, except VHF NFD!!

REMEMBER

Only authorised Yaesu dealers have direct contact with the factory in Japan, and only if you buy your radio from an authorised dealer can you be assured of spares and service back up. So **BEWARE** of grey importers who offer sets a few pounds cheaper, they may not be around if your set goes wrong!!

SMC SERVICE

Free Securitor delivery on major equipment.
Access and Barclaycard over the phone.
Biggest branch agent and dealer network.
Securitor 'B' Service contract at £4.49.
Biggest stockist of amateur equipment.

FREE FINANCE

On many regular priced items SMC offers
Free Finance (on invoice balance over £120).
20% down and the balance over 6 months or
50% down and the balance over a year.
You pay no more than the cash price!!

GUARANTEE

Importer warranty on Yaesu Musen products.
Abyly staffed and equipped Service Department.
Daily contact with the Yaesu Musen factory.
Tens of thousands of spares and test equipment.
Twenty-five years of professional experience.

**HEAD OFFICE S.M. HOUSE, RUMBRIDGE STREET, TOTTON, SOUTHAMPTON, SO4 4DP, ENGLAND,
&
MAIL ORDER Tel: Totton (0703) 867333, Telex: 477351 SMCMM G, Telegram: "Aerial" Southampton**

Communications Ltd.

MAIN DISTRIBUTOR FACTORY BACKED



ANTENNAS VHF

JAYBEAM				
4Y/4M	Yagi 4 element	7dB	£29.90	£2.20
PM/12/4M	Phasing harness 2-way		£16.10	£1.50
HO/2M	Halo head only	0dBd	£5.98	£1.20
HM/2M	Halo with 24" mast	0dBd	£6.55	£1.20
C5/2M	Colinear omniriver	4.8dBd	£54.62	£2.50
LW5/2M	Yagi 5 element	7.8dBd	£14.37	£2.50
LW8/2M	Yagi 8 element	9.5dBd	£17.82	£2.50
LW10/2M	Yagi 10 element	10.5dBd	£24.15	£2.50
LW16/2M	Yagi 16 element	13.4dBd	£35.07	£3.20
14Y/2M	Yagi 14 element	12.8dBd	£36.23	£3.20
PBM10/2M	10 ele Parabeam	11.7dBd	£44.85	£3.20
PBM14/2M	14 ele Parabeam	13.7dBd	£55.77	£3.20
Q4/2M	Quad 4 element	9.4dBd	£29.32	£2.50
Q6/2M	Quad 6 element	10.9dBd	£39.10	£2.50
Q8/2M	Quad 8 element	11.9dBd	£44.85	£2.50
D5/2M	Yagi 5 over 8 slot	10dBd	£25.30	£2.50
D8/2M	Yagi 8 over 8 slot	11.1dBd	£34.50	£2.50
5X/2M	Yagi 5 ele crossed	7.8dBd	£28.17	£2.50
8X/2M	Yagi 8 ele crossed	9.5dBd	£35.65	£2.50
10X/2M	Yagi 10 ele crossed		£46.00	£2.50
PMH2/C	Harness cir polarisation		£9.77	£1.50
PMH2/2M	Harness 2-way 144MHz		£12.65	£1.50
PMH4/2M	Harness 4-way 144MHz		£28.75	£1.50
C8/70	Colinear Omni Vertical	6.1dBd	£62.10	£2.50
D8/70	Yagi 8 over 8 slot	12.3dBd	£25.87	£2.50
PBM18/70	18 ele Parabeam	13.5dBd	£32.20	£2.50
PBM24/70	24 ele Parabeam	15.1dBd	£42.55	£2.50
LW24/70	Yagi 24 element	14.8dBd	£27.02	£2.50
MBM28/70	28 ele Multibeam	11.5dBd	£21.27	£2.50
MBM48/70	48 ele Multibeam	14.0dBd	£35.65	£2.50
MBM88/70	88 ele Multibeam	16.3dBd	£48.87	£2.50
8X/70	Yagi 8 ele crossed	10dBd	£42.55	£2.50
12X/70	Yagi 12 ele crossed	12dBd	£52.90	£2.50
PMH2/70	Harness 2-way		£10.35	£1.50
PMH4/70	Harness 4-way		£22.42	£1.80
CR2/23CM	Corner reflector	13.5dBd	£40.25	£2.50
PMH2/23CM	Harness 2-way		£31.05	£1.50

SMC-HS				
SMC6DX1	Discone 80-480MHz 3dBj 3.3'		£40.25	£2.50
SMC6DX2	Discone 50-480MHz 3dBj 6.2'		£49.45	£2.50
GDXA	Discone 100-440MHz 3dBj		£33.75	£2.50
SMC-VHFL	Discone 65-520MHz Rx only 5.0'		£15.70	£2.50
SMC6P23	Colinear 2M 3 x 1/4 wave 7.8dBj 14.6'		£39.85	£2.50
SMC6P144W	Colinear 2M Multi 1/4 wave 6.5dBj 10.2'		£27.60	£2.50
SMC6P2M	1/4 wave c/w ground plane 3.4dBj 4.6'		£18.00	£2.50
SMCSQ144	2M Swiss Quad for vertical mounting		£57.60	£2.50
SMC6P432X	Colinear 70cm 3 x 1/4 wave 6.8dBj 5.6'		£29.90	£2.50
SMC7Q2V	Colinear 2.8dBj 2M, 5.7dBj 70cm 3.6'		£29.90	£2.50
SMC2H6S	6M HB9CV 2 Driven elements		£19.95	£2.50
SMCHS770	144/432 Duplexer 50W 30dB isolation		£15.35	£1.50

SMC2QW	Element 144MHz 1/4 wave adBj	£2.30	£1.50
SMC2NE	Element 144MHz 5/8 wave 3.0dBj	£6.90	£1.80
SMC2VF	Element 144MHz 1/2 wave 3.0dBj	£11.50	£1.80
SMC78F	Element 144MHz 7/8 wave 4.5dBj	£13.80	£2.00
SMC78B	Element 144MHz 7/8 wave 4.5dBj	£13.80	£2.00
SMC88F	Element 144MHz 8/8 wave 5.2dBj	£18.80	£2.00
SMC2S8	Element 432MHz 2 x 5/8 5.5dBj	£12.65	£1.80
SMC3S8	Element 432MHz 3 x 1/2 6.3dBj	£16.85	£1.80
SMC70N2M	2M 2.7dBj 70cm 5.1dBj	£16.85	£1.80
SMCHS770	144/432 Duplexer 50W 30dB isolation	£15.35	£1.50
SMC6CCA	Gutter clip 4 mtrs Cable	£9.95	£1.80
SMC6SMM	Magnetic base c/w 4M cable	£9.95	£1.80

2M ASCOT ANTENNAS MOBILE			
(The keenest prices)			
Complete with bases and cable			
340COM	1/2 x Standard	£6.10	£1.50
310COM	1/2 x Swivel	£8.10	£1.50
344COM	1/2 x Sprung	£10.38	£1.50
440COM	1/2 x Standard	£7.71	£1.50
330COM	1/2 x Swivel	£10.00	£1.50
341COM	1/2 x Sprung	£12.31	£1.50
092	Magnetic Mount	£10.75	£1.50
350	1/2 x Standard	£14.26	£1.50
351	1/2 x Sprung	£15.01	£1.50
091	Magnetic Mt 1/2 x	£10.75	£1.50

NB: PRICES INCLUDE VAT AT 15%
Carriage extra, mainland rate shown

ANTENNAS HF

HY GAIN				
12AVO	Vertical 10, 15, 20, 14.0'H		£50.60	£2.75
14AVO/WB	Vertical 10, 15, 20, 40 18.0'H		£64.40	£2.75
18AVT/WB	Vertical 10, 15, 20, 40, 80M 25.0'H		£113.85	£2.75
14RMO	Roof mounting kit 12AVO			
14AVO & 18AVT			£38.52	£2.75
18V	Vertical 10, 15, 20, 40, 80M 19.0'H		£36.22	£2.75
103BA	3Ele Yagi 10 metres 17.0'LE 8.0'B		£67.85	£3.50
105BA	5Ele Yagi 10 metres 18.5'LE 24.0'B		£155.25	£3.95
153BA	3Ele Yagi 15 metres 23.0'LE 12.0'B		£90.85	£3.50
155BA	5Ele Yagi 15 metres 24.5'LE 26.0'B		£236.90	£5.90
203BA	3Ele Yagi 20 metres 35.0'LE 16.0'B		£178.25	£4.90
204BA	4Ele Yagi 20 metres 36.5'LE 26.0'B		£286.35	£7.30
205BA	5Ele Yagi 20 metres 36.5'LE 34.0'B		£396.75	£9.40
402BA	2Ele Yagi 40 metres 43.0'LE 16.0'B		£247.25	£6.50
DB10/15A	3 Ele Yagi 10-15M 23.0'LE 13.0'B		£196.95	£4.80
TH3JNR	3 Ele Yagi 10-15-20M 24.2'LE 12.0'B		£202.40	£3.50
TH2MK3	3 Ele Yagi 10-15-20M 27.3'LE 6.0'B		£169.05	£3.50
TH3MK3	3 Ele Yagi 10-15-20M 27.0'LE 14.0'B		£274.85	£5.30
TH5DXX	"Thunderbird" 5 Ele 31.0'LE 18.0'B		£419.75	£6.70
TH6DXX	"Thunderbird" 6 Ele 31.1'LE 24.0'B		£396.75	£8.50
TH7DXX	"Thunderbird" 7 Ele 31.0'LE 20.0'B		£511.75	£8.75
HYQUAD	2 Ele Quad 10, 15, 20M 13.5'TR 8.0'B		£354.20	£6.00
18TD	Dipole Tape 10, 15, 20, 40, 80M 132		£121.90	£2.80

JAYBEAM				
VR3	Vertical 10-15-20M. DC Short 6 lb 13.5'H		£46.00	£2.50
TB3	3 Ele Yagi 10-15-20M 14.6'TR 14.1'B		£189.75	£5.40
MINI BEAM				
C4	Vertical Miniature 10-15-20M 8lb 11.5'H		£59.00	£2.50
HQ1	"Mini" Quad beam 10-15-20M 11.0'LE 4.5'B		£139.00	£4.00
G4MH MINI BEAM				
	Mini Beam 10-15-20M		£82.50	£4.00
SMC TRAPPED DIPOLE	10-80M 119' Potted Traps.			
SMCTD/HP	14SWG H/D C _u traps 1000W PEP		£43.41	£2.50
SMCTD/P	Portable C _u /terylene 75' coax		£59.80	£2.50
SMCHPT	High Power 7MHz 1000W Per pair		£15.52	£1.80

SMC-HS ANTENNA				
SMCHF5V	Vertical 10, 15, 20, 40, 80M 15.7'		£54.80	£2.50
SMCHF5R	Radial kit loaded 6.5'-7.3'		£34.90	£2.50
SMCHF3VNB	Vertical 10-18-24M 1000W PEP 16.0'H		£51.35	£2.50

NB: PRICES INCLUDE VAT AT 15%
Carriage extra, mainland rate shown

ANTENNA ROTATORS

	Type			
RLD3	Bell	5 Core Light Duty	£40.25	
505	Bell	5 Core Light Duty	£40.25	
AR30	Offset	5 Core Light Duty	£56.35	
KP250	Bell	6 Core Lighter Duty	£54.91	
9502B	Offset	3 Core Lighter Duty	£56.92	
AR22	Bell	4 Core Medium Duty	£67.85	
9508	Offset	3 Core Medium Duty	£80.21	
AR40	Bell	5 Core Medium Duty	£90.85	
BT1	Bell	5 Core 4 Preset Medium	£91.43	
KR400	Bell	6 Core Medium matches K8500	£112.12	
KR500	Thro	6 Core Elevation	£112.12	
AR50	Bell	5 Position Medium	£113.85	
KR400RC	Bell	6 Core Medium Duty	£114.94	
CD45	Bell	8 Core Heavy Duty	£136.85	
KR600RC	Bell	8 Core Heavy Duty	£163.30	
HAM IV	Bell	8 Core Heavier Duty	£258.75	
KR200RC	Bell	8 Core Heavier Duty	£314.52	
TX2	Bell	8 Core Very Heavy Duty	£327.75	
H300	Bell	8 Core Digital Readout	£493.35	

Control Cable			
RC4W	4 Way 28p/mtr	Carriage	£1.80
RC5W	5 Way 33p/mtr	Carriage	£1.80
RC6W	6 Way 51p/mtr	Carriage	£1.80
RC8W	8 Way 55p/mtr	Carriage	£1.80
9523	Support Bearing		
	9502	£15.81	Carriage £2.50
KC038	Lower Mast Clamp		
	KR400/600	£12.07	Carriage £2.50

Prices including VAT and carriage, but accessories are extra unless sent with rotators.

STATION ACCESSORIES

HANSEN				
FS710H	1.8-60MHz 15/150/1500W Pep		£89.70	P&P FOC
FS710V	50-150MHz 15/150W Pep		£88.70	FOC
FS50HP	1.8-80MHz 20/200/2000W Pep		£88.70	FOC
FS50VP	50-150MHz 20/300W Pep		£89.70	FOC
FS500H	1.8-80MHz 20/200/2000W Pep		£69.75	FOC
FS500V	50-150MHz 20/200W Pep		£69.75	FOC
FS300H	1.8-80MHz 20/200/1000		£46.40	FOC
FS300V	50-150MHz 20/200		£46.40	FOC
FS200	1.8-150MHz 20/200 Pep		£50.60	FOC
FS001M	1.8-30MHz 20/200W Pep		£51.35	FOC
FS601MH	1.8-30MHz 200/2000W Pep		£51.35	FOC
FS800M	1.8-30MHz 20/200W Pep		£51.35	FOC
FS600M	430-440MHz 5/20W Pep		£51.35	FOC
FS210	1.8-150MHz 20/200W Auto SWR		£55.20	FOC
FS301M	2-30MHz 20/200W		£36.65	FOC
FS301MH	2-30MHz 200/2000W		£36.65	FOC
FS302M	50-150MHz 20/200W		£36.65	FOC
FS711H	2-30MHz 20/200W Head		£36.80	FOC
FS711V	50-150MHz 20/200W Head		£36.80	FOC
FS711U	430-440MHz 5/20W Head		£36.80	FOC
HB1	FS711H Coupler		£23.75	FOC
VB1	FS711V Coupler		£23.75	FOC
UB1	FS711U Coupler		£23.75	FOC
FSSE	3.5-150MHz 20/200/1000W HF		£37.20	FOC
FS5S	1.8-150MHz 20/200/1000W HF		£37.95	FOC
FS7	145&(432MHz 5/20/200 144		£41.00	FOC
SWR3S	3.5-150MHz 20/200/1000W HF		£25.00	FOC
SWR3S	3.5-150MHz F/S Meter ant.		£28.46	FOC
SWR508	3.5-150MHz Twin Meter		£26.45	FOC
FS20D	3-150MHz 5/20W		£37.95	FOC
FS800	1.8-150MHz 6/30/150W		£115.00	FOC
JD				
JD110	1.5-150MHz 10/100W		£13.80	FOC
MIRAGE				
MP2	50-150MHz 50/500/1500W Pep		£100.00	FOC
SMC				
S3-30L	Mini CB		£8.80	FOC
T3-170L	3.5-170MHz Relative		£14.95	FOC

MORSE KEYS				
BKU1	Squeeze Key		£30.30	£1.20
HK703	Straight Key		£25.70	£1.20
HK704	Straight Key		£17.65	£1.20
HK706	Straight Key		£14.60	£1.00
HK707	Straight Key		£13.75	£1.00
HK710	Straight Key		£36.40	

THE ONLY BRAND WORTH GOING FOR WITH ANY FREQUENCY

...is the brand that gives you the best service in every aspect of Amateur Radio, and its name is - ICOM from Thanet Electronics.

ICOM's Latest The IC-751 HF Transceiver



Think about the IC-740.

One of the most popular amateur bands transceivers, make a few improvements such as adding 36 memory channels, doing away with mechanical bandswitching and then add full HF receive capability (0.1-30 MHz) which is even an improvement on the famous R70 and you get a pretty good idea of what the IC-751 is like. It is fully compatible with Icom auto units such as the AT-500 and IC-2KL and a further option for computer control can be added. There is also a digital speech synthesizer option which will be ideal for blind operators. For power supplies you have the option of the IC-PS35 (which fits inside) or the PS-15/PS20 range for external use.

As you would expect there is a built in speech processor, a switchable choice of a J-FET pre-amp, straight through or a 20dB pin diode attenuator and two VFOs allowing split frequency operation.

Other standard features include: 36 memory channels with scan facility and start/stop timers, a marker, 4 variable tuning rates, Pass Band Tuning, notch, variable noise blanker, monitor switch, DFM (direct feed mixer) in the front end, full break-in on CW and AMTOR compatibility. The first IF is 70.045 MHz. Any XIT and RIT adjustment is shown on the display. The transmitter features high reliability 2SC2904 transistors in a low IMD (-32dB @ 100W) full 100% duty cycle. Power is restricted to 40W on AM and adjustable from 10W on all modes. FM and the IC-FL44A crystal SSB filter are both fitted as standard. As you can see from this brief description the IC-751 is certainly a transceiver worth considering - Why not call us for details?

NEW! IC-271, VHF Multimode Base station



Icom have made improvements to the popular IC-251 and brought it up to date.

Power can be adjusted up to 25W on all modes SSB, CW and FM. Squelch works on all modes and a listen-input facility has been added for Repeater work. There is a switchable front end pre-amp. RIT shift is shown on the display. Why not call us for further details? Options include:

Speech synthesizer announcing displayed frequency.
22 Channel memory extension - with scan facilities.
10 Hz tuning facility. SM5 desk mic. Internal chopper PSU (IC-740S)

IC-R70, HF Receiver



The R-70 covers all modes (when the FM option is included), and uses 2 CPU-driven VFO's for split frequency working, and has 3 IF frequencies: 70MHz, 9MHz and 455KHz, and a dynamic range of 100dB. It has a built-in mains supply.

Other R-70 features include: input switchability through a pre-amplifier, direct or via an attenuator, selectable tuning steps of 1KHz, 100Hz or 10Hz, adjustable IF bandwidth in 3 steps (455KHz). Noise limiter, switchable AGC, tunable notch filter, squelch on all modes, RIT, tone control. Tuning LED for FM (discriminator centre indicator). Recorder output, dimmer control.

The R-70 also has separate antenna sockets for LW-MW with automatic switching, and a large, front mounted loudspeaker with 5.8W output. The frequency stability for the 1st hour is ± 50 Hz, sensitivity- SSB/CW/RTTY better than $0.32 \mu\text{V}$ for 12dB (S+N) - N, Am- $0.5 \mu\text{V}$, FM better than 0.32 for 12dB Sinad. DC is optional

Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM Thanet ICOM



AMATEUR ELECTRONICS UK

Your number one source for YAESU MUSEN



THE SYMBOL OF TECHNICAL EXCELLENCE

When you buy from Amateur Electronics UK you are dealing with a **FACTORY APPOINTED IMPORTER** with the largest stocks of equipment and spares in the country. Our delivery and after-sales-service is second to none and for your convenience we offer the following facilities ● On- the-spot credit sales (against recognised bank or credit cards) ● Interest free finance (50% deposit - balance over 12 months) ● Free Securicor delivery on all major items ● **FACTORY BACKED EQUIPMENT** - write or phone for all the details.

YAESU - Latest...

Latest news from YAESU - Expected in August is the new FT-757GX all-mode HF transceiver - 160 thru ten

of course plus general coverage RX. FM and all options fitted including dual VFO's, eight memories, programmable memory scan, full break-

in on CW, 100 watts PEP/DC output at 100% duty cycle and all this in a package measuring 238W x 93H x 238Dmm!

KEEP AHEAD WITH THE YAESU FT-102!

STOP PRESS

We are pleased to announce a new price breakthrough on this superb transceiver — phone or write for details.



FRG-7700 HIGH PERFORMANCE COMMUNICATIONS RECEIVER



YAESU's top of the range receiver. All-mode capability, USB, LSB, CW, AM and FM 12 memory channels with back-up. Digital quartz clock feature with timer. Pictured here with matching FRT-7700 Antenna tuner and FRV-7700 VHF converter.

FT-708R/208R SYNTHESIZED UHF/VHF TRANSCEIVERS

- NC-7 - Standard charger
- NC-8 - Standard/quick charger/DC Power supply
- NC-9C - Compact charger (220-234V)
- PA-3 - Car adapter
- YM-24A - Speaker/microphone
- FL-2010 - 10 watt power amplifier for FT-208R
- FL-7010 - 10 watt power amplifier for FT-708R

FT-290R/790R 2m & 70cm PORTABLES

10 memories, 2 VFO's, LCD display, C size battery, easy car mounting tray, FT-290R 0.5 low/2.5 high watts out FT-790R 0.2 low/1.0 high watts out (incorporates speech compressor).



FT-230R/730R 2m & 70cm FM MOBILES

- Two independent VFO's ● 10 memories
- Priority function ● Memory and band scan
- 12.5/25KHz steps (25/100KHz FT-730R)
- Large LCD readout.



FT-480R/780R 2m & 70cm MOBILES

The most advanced 2 metre and 70 cm mobiles available today — USB, LSB, FM, CW full scanning with priority channel, 4 memory channel, dual synthesized VFO system.



FAST MAIL ORDER!!!

BY CREDIT CARD OR CHEQUE

TET ANTENNA SYSTEMS



AX210N	10 ele. yagi for 2m crossed	74.95	(n/c)
H810F2T	2 ele. 10m mono band beam	51.50	(n/c)
H810F3T	3 ele. 10m mono band beam	74.95	(n/c)
H815F2T	2 ele. 15m mono band beam	60.66	(n/c)
H815F3T	3 ele. 15m mono band beam	93.46	(n/c)
H815M2SP	VP mini size 15m 2 ele.	69.50	(n/c)
H815M3SP	VP mini size 15m 3 ele.	102.30	(n/c)
H834D	4 ele. tri band beam 10/15/20m	222.90	(n/c)
H833SP	3 ele. tri band beam 10/15/20m	192.50	(n/c)
H835C	Tri band array 10/15/20m	283.95	(n/c)
H835T	5 ele. 10/15/20m	278.50	(n/c)
MV38H	Vertical for 10/15/20m	37.99	(n/c)
MV48H	Vertical for 10/15/20/40m	48.90	(n/c)
MV58H	Vertical for 10/15/20/40/80m	63.95	(n/c)
ML44	Loop antenna 10/15/40/80	105.60	(n/c)
SQ22	Phased 2 ele. swiss quad 2m	58.95	(n/c)
SQY06	6 ele. quagi 2m	45.75	(n/c)
SQY08	8 ele. quagi 2m	52.75	(n/c)
H81210S	10 ele. dual driven yagi 2m	47.99	(n/c)
TE214	14 ele. long yagi 2m	74.40	(n/c)
SL3270	9 x 2 ele. (18) slot fed 70cm	77.20	(n/c)
H823SP	2 ele. tri band beam 10/15/20m	135.60	(n/c)
SL218	9 x 2 ele. (18) slot fed 2m	144.79	(n/c)
TPH2	Phasing harness 2m	17.25	(n/c)
QUY10	10 ele. quagi 70cm	67.90	(n/c)
SQ007	70cm 2 ele. phased swiss quad	66.99	(n/c)
SQ10	Swiss quad 10m	97.50	(n/c)
SQ15	Swiss quad 15m	106.90	(n/c)

YAESU ANTENNAS

Base			
RSL145GP	1/2 wave base ant. 2m	21.20	(1.50)
RSL435GP	1/2 wave co-linear 70cm	31.60	(1.50)
HF Mobile			
RSL3.5	3.5MHz resonator & whip	12.21	(0.50)
RSL7.0	7.0MHz resonator & whip	11.80	(0.50)
RSL14.0	14.0MHz resonator & whip	11.45	(0.50)
RSL21.0	21.0MHz resonator & whip	11.20	(0.50)
RSL28.0	28.0MHz resonator & whip	11.00	(0.50)
RSL2A	Mast to suit above	5.00	(0.50)
RSM2	Gutter mount/Feeder/PL259 suit above	10.94	(0.75)
VHF Mobile			
RSL145	2m 1/2 wave fibreglass whip	12.10	(0.50)
RSL145S	2m 1/2 wave steel whip foldover	9.25	(0.50)
RSL150SS	2m 1/2 wave PL259 shock spring	3.90	(0.50)
RSM2	Gutter mount/Feeder/PL259 (RSL145)	10.94	(0.75)
RSM4M	Heavy duty mag/Feeder/PL259	13.25	(1.00)
UHF Mobile			
RSL453S	1/2 wave antenna	15.50	(0.50)
ANTIFERRECE ANTENNAS			
VHF Mobile			
TAP3009	1/2 wave 3db snap-in hinged whip	13.00	(3.00)
TAP3677	1/2 wave 3db snap-in shock coil	14.56	(3.00)
TAP3002	1/2 wave unity gain snap-in hinged whip	9.96	(3.00)
UHF Mobile			
TAP3462	1/2 over 1/2 wave 3db	16.86	(3.00)
TAP3697	1/2 over 1/2 wave 5db	20.00	(3.00)
K220	Mag mount/Feeder to suit above	11.96	(2.00)

Please send your order direct to Dept. SH at our main address below, including carriage charges where applicable and your full delivery address.

Amateur Electronics UK
504-516 Alum Rock Road - Birmingham 8
Telephone: 021-327 1497 or 021-327 6313
Telex: 334312 PERLEC G
Opening hours: 9.30 to 5.30 Tues. to Sat.
continuous - CLOSED all day Monday.

Carriage charges shown apply to UK mainland only.
 All prices include VAT Goods by return
 All prices subject to alteration without notice.

Simply phone or write and leave the rest to us

Antennas Various/Accessories

HQ1	Mini beam 10/15/20m 2 ele. 1kW	139.00	(4.00)
C4	Vertical 10/15/20m	48.50	(3.00)
G4MH	Mini beam 10/15/20	88.00	(4.00)
KTLM-4	Gutter mount/Cable assy. SO239	6.90	(0.50)

DATONG PRODUCTS

PC1	50KHz to 30MHz receive converter	137.42	(0.50)
VLF	Very low freq. converter	29.90	(0.50)
FL1	Frequency agile audio filter	79.35	(0.50)
FL2	Multimode audio filter	89.70	(0.50)
ASP/A	Auto RF speech clipper (YAESU)	82.80	(0.50)
ASP/B	Auto RF speech clipper (TRIO)	89.70	(0.50)
D75	Manual RF speech clipper	56.35	(0.50)
RFC/M	RF speech clipper module	29.90	(0.50)
D70	Morse tutor	56.35	(0.50)
AD270	Active dipole RX ant. (indoor)	47.15	(0.50)
AD370	Active dipole RX ant. (outdoor)	64.40	(0.50)
MK	Morse keyboard	137.42	(0.50)
DC144/28	2m converter	39.67	(0.50)
RFA	Broadband preamplifier	33.92	(0.50)
MPU	Mains power unit	6.90	(0.50)

MICROWAVE MODULES

Transverters			
MMT28/144	10m transverter	109.95	(2.50)
MMT70/144	4m transverter	119.95	(2.50)
MMT432/144R	70cm transverter	184.00	(2.50)
MMT1296/144	23cm transverter	184.00	(3.00)
MMT70/28	4m transverter	119.95	(2.50)
MMT144/28	2m transverter	109.95	(2.50)
MMT432/28S	70cm transverter	159.95	(2.50)

Linear Amplifiers

MML28/100S	10m 100W linear amp.	129.95	(3.00)
MML70/50S	4m 50W linear amp.	85.00	(2.50)
MML70/100S	4m 100W linear amp.	139.95	(3.00)
MML144/30LS	2m 30W linear amp. 1-3W in	69.95	(2.50)
MML144/50S	2m 50W linear amp.	85.00	(2.50)
MML144/100LS	2m 100W linear 1-3W in	159.95	(3.00)
MML144/100S	2m 100W linear 10W in	139.95	(3.00)
MML432/50	70cm 50W linear amp.	109.95	(3.00)
MML432/100	70cm 100W linear amp.	228.60	(4.00)
MML1296/10	23cm 10W linear amp.	199.00	(2.50)
MML432/30	70cm 30W linear amp. 1-3W in	99.00	(3.00)

Converters

MM1000KB	ASC11 morse converter with keyboard	99.95	(3.00)
MM4001	RTTY to TV converter	189.00	(2.50)
MM4001KB	RTTY transceiver	269.00	(2.50)
MM4000KB	RTTY transceiver with keyboard	299.00	(4.00)
MMC28/144	10m to 2m converter	29.90	(1.00)
MMC50/28	6m to 10m converter	29.90	(1.00)
MMC70/28	4m to 10m converter	29.90	(1.00)
MMC70/28LO	4m to 10m with LO	32.90	(1.00)
MMC432/28S	70cm to 10m converter	37.90	(1.00)
MMC432/144S	70cm to 2m converter	37.90	(1.00)
MMC435/600	UHF ATV converter	27.90	(1.00)
MMC1296/28	23cm to 10m converter	34.90	(1.00)
MMC1296/144	1296MHz low noise converter	69.95	(1.00)
MMK1691/137.5	1691MHz meteorite converter	129.95	(2.50)

Morse Talkers

MMS1	Morse tutor 2-20WPM Side tone	115.00	(2.50)
MMS2	Morse tutor (advanced) 6-32WPM + speak back	169.00	(2.50)

Amateur TV

MTV435	70cm 20W (PSP) transmitter	149.00	(2.50)
MMC435/600	Converter ATV UHF output	27.90	(1.00)

Preamplifiers

MMA144V	2m preamp RF switched	34.90	(1.00)
MMA28	10m preamp	16.95	(1.00)
MMA1296	23cm preamp	34.90	(1.00)

Frequency Counters

MMD650/500	500MHz digital meter	75.00	(1.00)
MMD600P	600MHz pre scaler	29.90	(1.00)
MMDP-1	Probe	14.90	(0.50)

Filters

MMF144	2m band pass 40W max.	11.90	(1.00)
MMF452	70cm band pass 40W max.	11.90	(1.00)

Various

MMS384	384MHz signal source	29.90	(1.00)
MMR15/10	15dB 10W attenuator	11.90	(1.00)

HI-MOUND Morse KEYS

HK702	Up down keyer marble base	24.50	(0.50)
HK704	Up down keyer	16.88	(0.50)
HK705	Up down keyer	12.50	(0.50)
HK706	Up down keyer	13.75	(0.50)
HK708	Up down keyer	11.96	(0.50)
HK808	Up down keyer marble base	39.57	(0.50)
MK704	Twin paddle keyer	10.95	(0.50)
MK705	Twin paddle keyer marble base	22.00	(0.50)

MOULDINGS

IK	lambic keyer	19.95	(0.50)
----	--------------	-------	--------

TOKYO HY POWER

HC150	HF ATU SWR/Power meter		
	200W PEP	62.50	(n/c)
HC2000	HF 2kW ATU SWR/Power meter		
	6 POS ant. switch, 6 to 1 vernier high Q coils 2kW peak 1kW continuous	276.55	(n/c)

Antenna Rotators & Accessories

9502	Channel master med duty up to 8 ele.	57.00	(3.50)
9523	Alignment bearing for 9502	15.81	(1.25)
KR400	Med/Heavy duty 180° meter	90.85	(3.50)
KR400RC	Med/Heavy duty 360° meter Load 200Kg 1 1/2"-2" masts	114.94	(3.50)
CASTING	Lower casting set	15.00	(1.25)
KR600RC	Heavy duty 360° meter Load 200Kg Rot600Kg/cm BAKE 4000Kg/cm 1 1/2"-2" masts	163.30	(3.50)

Antenna Switches

SA450	SO239 connectors 1 in 2 out	9.75	(0.50)
SA450N	"N" type connectors 1 in 2 out	12.75	(0.50)

Baluns

BL50A	RAK 50 ohm ferrite BALUN 1:1 1.8-38MHz 1kW	12.88	(1.50)
BL-40X	Balun 2K PEP 1k	11.52	(1.50)

Dummy Loads

T30	30W DC 500MHz PL259	6.61	(0.50)
T100	100W DC 500MHz SO239	20.12	(1.00)
T200	200W DC 500MHz SO239	31.36	(1.50)
T210	Wide band 10W 1.2G-2.4G	24.50	(0.75)
AW05	Pocket RF wattmeter 5W up to 500MHz BNC	19.75	(1.00)

DRAE PRODUCTS

DRAE4	4 amp PSU	30.75	(2.00)
DRAE6	6 amp PSU	48.00	(2.50)
DRAE12	12 amp PSU	74.00	(3.00)
DRAE24	24 amp PSU	105.00	(4.00)
DRAE WM	135-450MHz wavemeter	27.50	(1.00)

"N" Connectors (Silver Plated)


N58	"N" Male connector RG58	2.25	(0.25)
N8	"N" Male connector RG8	2.40	(0.25)
N308	"N" T adaptor (three female)	2.40	(0.25)
N307	"N" L adaptor (1 male 1 female)	2.40	(0.25)
N306	"N" Double female adaptor	1.90	(0.25)
N310	"N" Double male adaptor	2.50	(0.25)
NB304	"N" Female to BNC male adaptor	2.10	(0.25)
N402	"N" Plug to SO239	2.05	(0.25)
N403	"N" Socket to PL259	2.00	(0.25)
N404	"N" Socket to SO239	1.80	(0.25)

TOKYO HY POWER

HL32V	VHF 30W linear 1-5W drive HI-LOW output	53.50	(n/c)
HL82V	VHF linear preamp output meter 2-12W in 35-85+ out	144.50	(n/c)
HL160V	VHF linear preamp output meter 1-10W in 160W+ out	242.40	(n/c)
HL45U	UHF linear preamp 2-15W in 10-45W out	119.75	(n/c)

YAESU

YH55	Headphones Low Z	10.00	(0.50)
YH77	Lightweight headphones Low Z	10.00	(0.50)

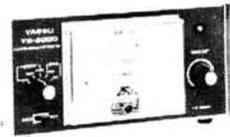

SWR/Power Meters

YAESU			
YS200		52.90	(n/c)
YS2000		69.79	(n/c)
Other Makers			
RF2000	Twin meter 3.5-150MHz F/Scale 200/2000W	18.25	(1.00)
YM1X	Twin meter 3.5-150MHz F/Scale 12 or 120W	14.99	(1.00)

COMPUTERS

Commodore 64, 64K, sprites, sound chip etc.	343.85	(n/c)
Vic 20 + C2N dataset + intro to base part 1 + 4 games. Special price	139.99	(3.00)
Commodore 1541 174K disk drive	299.00	(n/c)
Vic 3K ram pack	29.95	(0.25)
Vic 8K ram pack	44.95	(0.25)
Vic 16K ram pack	74.95	(0.25)
Vic 20 reference guide	9.95	(0.25)
Commodore 64 reference guide	14.95	(0.50)
C2N dataset	44.95	(1.75)
Spectrum 48K	129.95	(1.75)
Spectrum 16K	99.95	(1.75)
ZX Printer	39.95	(0.50)
Plus selection of software for all models.		


or attractive H.P. terms readily available for on-the-spot transactions. Full demonstration facilities. Free Securicor delivery.

RST

MAIL ORDER CO.
Langrex Supplies Ltd.,
Climax House,
159 Fallsbrook Road, Streatham, SW16 6ED.
SPECIAL EXPRESS MAIL ORDER SERVICE

AZ31	4.75	EM87	2.50	PY81	1.50	6AN8A	3.50	6Q7	3.75
CL33	4.00	EN91	7.05	PY82	1.50	6AQ5	2.25	6SA7	3.00
DY86/7	1.50	EY51	2.75	PY83	1.25	6ARS	3.50	6SC7	2.75
DY802	1.50	EY88	1.75	PY88	2.00	6AS6	8.66	6S7	3.25
EB8CC	7.46	EY500A	3.00	PY500A	4.00	6ASTGA	3.75	6S7	3.50
E180F	9.90	EZ80	1.50	PY800	1.50	6AT6	1.25	6SL7GT	3.00
EB10F	21.26	EZ81	1.50	PY801	1.50	6AUSGT	5.00	6SN7GT	3.00
EABC80	1.50	GY501	3.00	QQV02-6	16.50	6AU6	2.50	6S7	2.75
EB91	1.50	GZ32	2.50	QQV03-10	14.10	6AW8A	3.75	6SG7M	2.50
EBF80	1.50	GZ33	4.75	QQV03-20A	48.38	6B8	3.25	6UBA	2.25
EBF89	1.50	GZ34	3.00	QQV06-40A	48.38	6B8	3.25	6V6GT	2.25
EC91	8.00	GZ37	4.75	QQV03-12	6.80	6BA6	1.50	6X4	2.00
ECC33	4.50	KT61	5.00	R18	9.24	6BA7	5.00	6X5GT	1.75
ECC35	4.50	KT66	8.00	R19	2.50	6BE6	1.50	75C1	4.50
ECC81	1.75	KT77	8.00	SP41	6.00	6BH6	2.50	85A2	4.45
ECC82	1.75	KT88	11.00	SP61	4.00	6B16	2.25	90C1	6.00
ECC83	1.75	N78	15.00	SP19	13.75	6BN6	2.00	150B2	6.50
ECC85	1.75	OA2	3.25	SP61	4.00	6BQ7A	3.50	150C2	3.75
ECC88	2.10	OB2	4.35	U19	13.75	6BR7	6.00	150C4	4.00
ECC91	8.90	OC3	2.50	U25	2.50	6BR8A	3.50	12AX7	1.75
ECC90	1.55	OD3	2.50	U26	2.50	6BS7	6.00	12BA6	2.50
ECH35	3.00	PC86	2.50	U37	12.00	6BW6	6.00	12BE6	2.50
ECH42	3.50	PC88	2.50	UJAB80	1.25	6BW7	1.50	12BY7A	3.00
ECL80	3.00	PC92	1.75	UBF89	1.50	6C4	1.75	12HG7	4.50
ECL81	1.50	PC97	1.75	UCH42	2.50	6C6	1.75	30FL1/2	2.50
ECL82	1.50	PC900	1.75	UCH81	2.50	6CB6A	2.50	30P4	4.50
ECL83	3.00	PCF80	2.00	UCH82	1.75	6CD5GA	5.00	30P19	2.50
ECL86	1.75	PCF82	1.50	UCL82	2.75	6C6	3.75	30PL13	1.80
EF37A	5.00	PCF86	2.50	UFB9	2.00	6C6	2.75	30PL14	1.80
EF39	2.75	PCF801	2.50	UL41	3.50	6C6	2.75	75C1	4.50
EF41	3.50	PCF802	2.50	UL84	1.75	6D6	1.75	85A2	4.45
EF42	4.50	PCF805	1.70	UY41	2.25	6DQ5	6.00	90C1	6.00
EF50	2.50	PCF808	1.70	UY85	2.25	6E8A	3.00	150B2	6.50
EF54	5.00	PCF820	3.00	VR105330	2.50	6E8B	3.00	150C2	3.25
EF55	3.50	PCL82	2.00	VR150/30	4.00	6E8H	1.85	150C4	6.00
EF80	1.75	PCL83	3.00	Z759	25.00	6F6	3.00	57Z8	30.00
EF86	1.75	PCL84	2.00	Z803U	19.00	6G6	2.75	807	45.00
EF91	2.95	PCL85	2.50	ZD21	3.25	6H56	3.77	811A	18.33
EF92	6.37	PCL86	2.50	3B28	40.00	6J5	4.50	812A	18.33
EF183	2.00	PCL805	2.50	4CX250B	40.00	6J6	8.93	813	125.86
EF184	2.00	PD500	6.00	SR4GY	3.50	6J7	4.75	866A	20.03
EH90	1.75	PFL200	2.50	5U4G	3.00	6J7	4.75	872A	20.00
EL32	2.50	PL36	2.50	5V4G	2.50	6B6A	5.00	931A	18.50
EL33	4.00	PL81	1.75	5Y3GT	2.50	6SEC	6.00	2050	7.00
EL34	3.00	PL82	1.50	5Z3	4.00	6SN	2.50	5763	4.50
EL36	2.50	PL84	2.50	5Z3GT	2.50	6K4N	2.75	5814A	4.00
EL81	5.25	PL84	2.50	6J3OL2	1.75	6K6GT	3.00	5842	12.00
EL84	2.75	PLS04	2.50	6AB7	3.00	6K8	3.00	6080	14.00
EL86	2.75	PLS08	2.50	6AH6	5.00	6KD6	7.00	6146A	8.25
EL91	9.69	PLS09	6.00	6AK5	5.99	6LEG	3.00	6146B	8.25
EL95	2.00	PLS19	6.00	6AL5	1.50	6LGC	3.00	6883B	8.25
EL360	8.50	PL802	6.00	6AP6	6.02	6L7	2.50	6973	4.00
EM81	2.50	PY33	2.50	6AN5	4.75	6LQ6	7.50	7360	10.00
								7586	12.00
								7587	18.50

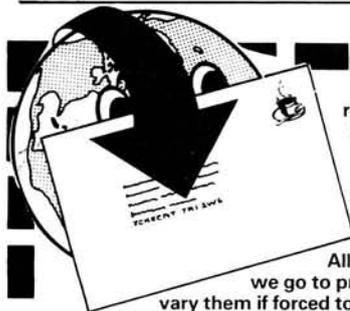Open daily to callers: Mon-Fri 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Saturday
Terms C.W.O. only, allow 7 days for delivery. Tel. 01-677 2424-7.
Prices excluding VAT add 15% Quotations for any types not listed S.A.E.
Post and packing 50p per order
Telex 946708 Prices correct when going to press



Same-day dispatch on orders received by midday, with delivery by Securicor or Insured Post at our option. Mail order terms are carriage-free to mainland UK on orders £100.00 or over. £1.00 per item please towards carriage/packing on orders under £100.00. All prices include VAT and are correct as we go to press. However, we reserve the right to vary them if forced to do so by the time this advertisement appears. Phone for up-to-date information, or send 50p for our full Stock List.



373 UXBRIDGE ROAD, ACTON, LONDON W3 9RH
Tel: 01-992 5765/6/7 Just 500 yards east of Ealing
Common station on the District and Piccadilly Lines and 207 bus stops outside.

136 GLADSTONE STREET, ST HELENS, MERSEYSIDE
Tel: 0744 53157 Our North West branch run by Peter (G4 KKN), just around the corner from the Rugby Ground.

Closed Wednesday at Acton and Monday at St Helens, but use our 24-hour Ansafone service at either shop.

NEW CONFIDENTIAL FREQUENCIES BOOK

This all new edition of the world-acclaimed "Confidential Frequency List" is bigger and better than ever with 30% more stations listed, over 9000 between the international broadcasting and amateur radio bands, in the 4-28 MHz range. In addition to listings by frequency, there is a new reverse listing by call sign as well as frequency for easier location. All listings reflect present and post-WARC assignments. A complete list of Coastal CW stations plus Embassy, Aeronautical, Military, Time Sigs., Feeders, Volmet, Fax, Interpol, and more. All with new details on schedules, emergency channels, alternates, and many more never-before published IDs.

Price: £8.95 Update £2, p&p £1

AMATEUR



FT-757 GX

Yaesu's answer to the TS 430 - All modes HF TRANSCEIVER which can be used as a 'mobile or base station' with the following superb features.

- ★ General coverage receiver capabilities.
- ★ Function controlled by three Microprocessors.
- ★ Triple conversion receiver with dynamic range - better than 100 Dbs.
- ★ Unlimited clarifier range - UFO frequency and Memory function computer capabilities.
- ★ Computer aided and manufactured - full break-in on C.W.
- ★ 100% continuous 'duty cycle' of 100 watts.

£695



NEW FROM VOLKER WRAASE

Digital SSTV/FAX Converter

Both receiver and transmitter have the following specifications. COLOUR SSTV - Frame-sequential and high resolution line-sequential (256 interlaced red & green pixels per line). 2 full colour, full resolution picture memories.

- 32 SEC SSTV HIGH RESOL.
- 16 SEC SSTV
- 8 SEC SSTV
- FACSIMILE

- 2 full resolution, 256x256x6 bits memories.
- 4 picture memories.
- 6 picture memories.
- 2 picture memories, transmits 240 lines per minute, receives also 480, 120, 180, 90, 60 lines per minute. AM/FM demodulator selectable. Automatic phasing on 300Hz start signals (GEOS, METEOSAT, WAFAX).

OPTIONS:

- KEYBOARD - for superimposing alphanumeric information onto the pictures.
- PRINTER-INTERFACE - for printing pictures out of the memories (128x128 pixels/16 shades of grey).

PRICE ON APPLICATION

SPECIAL OFFERS



FT 102 ONLY £695

All modes (FM optional) - All bands - 100db dynamic range - Variable bandwidth - I.f. shift - Adjustable noise blanker - Three 6146B's - Facilities for checking TX I.F. signal - Mic amp + many more features.



FT 290R ONLY £249

10 memories - 2 VFO's - LCD display 70cm all-mode portable.

Hurry as these prices are for a limited period only!

RADIO EXCHANGE



YAESU	
FT980 CAT	NEW all mode transceiver with AM/CW/FM/SSB/AFSK 1190.00
FT102	160-10M 9-Band Transceiver NEW 695.00
FT ONE	Gen. Coverage Transceiver NEW 1345.00
FT90R	70cm all-mode portable NEW 309.00
FT1012FM	160-10m 9-Band Transceiver 535.00
FT1012DFM	160-10m 9-Band Transceiver 599.00
FC902	9-Band atu, swr/pwr etc. SPECIAL 99.00
SP901	External speaker 31.00
FL2100Z	9-Band 1200W linear 475.00
FT77	8-Band solid state 100W 469.00
FP707	230 volts AC power supply 99.00
FC707	Aerial tuner (unbalanced only) 85.00
MR7	Metal rack for above 15.70
MM92	Mobile mounting bracket 16.00
FRG7700	SSB/AM/FM recvr. dig. readout 319.00
MEM7700	Memory unit for above 90.00

CONVERTERS FOR ABOVE	
FRV7700A	118-150MHz 78.45
FRV7700B	50-60MHz & 118-150MHz 84.70
FRV7700C	140-170MHz 74.75
FRV7700D	70-80MHz & 118-150MHz 80.90

FRT7700	Receiver aerial tuner 42.00
FF5	LF filter for above 9.95
FT480R	2m all-mode transceiver 365.00
FP80A	230V AC power supply 63.00
FT780R	70cm all-mode transceiver 399.00
FT790RD	SPECIAL 1983 version with ARE mods 249.00
NC11C	AC charger 9.00
CSC-1	Carrying case 3.45
MMB 11	Mobile mounting bracket 22.25
FT208R	2m synthesized portable FM 199.00
NC9C	AC charger 8.00
FT708R	70cm hand held 209.00
YH55	Headphones, low Z 10.00
YH77	Lightweight h/phones, low Z 10.00

ICOM	
IC740	Multimode H.F. transceiver inc. HF transceiver and gen. cov. rec. SPECIAL OFFER 599.00
IC751A	New multimode receiver 499.00
ICR70	Power supply for 720A 109.00
IC271	2m multimode base station NEW 569.00
IC25E	2m synth compact 25W mobile 259.00
IC290H	2m multimode mobile 25W 419.00
IC2E	2m FM synthesised handheld 169.00
IC4E	70cm handheld 189.00
ICL1 2 3	Soft cases 4.25
ICM9	Speaker/microphone 15.00
ICCP1	Car charging lead 3.75
ICBP2	6V Nicad pack for IC 2E 33.00
ICBP3	9V Nicad pack for IC 2E 23.00
ICBP4	Empty case for 6 x AA Nicads 6.95
ICBP5	11.5V Nicad pack for IC 2E 44.00
ICDC1	12V adaptor pack for IC 2E 9.75

TRIO-KENWOOD	
TS430S	Gen. coverage multi-mode NEW 699.00
TS930	Gen. coverage transceiver NEW 1100.00
TS130S	8-Band 200W pep 425.00
AT130	100W antenna tuner 79.00
TR2500	2m FM synthesised handheld 217.00
HC10	Digital desk World Clock 58.75
DM801	Dip meter 69.00
R600	Gen. coverage receiver 225.00
R2000	Gen. coverage receiver 395.00
TW400	Unique dual-band 2m/70cm mobile/base station P.O.A.

SCANNING RECEIVERS	
AR3000	ARE Communications 720 channel synthesised air band receiver 99.00
AS32320	Fairmate VHF/UHF scanning receiver, air band/military/police 149.00
ATC720	FDK Air Band 720 channel air band handheld 149.00
ATC720SP	Professional version of above 189.00
SX200N	JLL 16 channel memory, synthesised AM/FM 299.00
MK4000	Maximal-Mickey 8 channel memory, 70 80MHz, 140-176MHz, synthesised 99.00
BC100FB	Bearcat 16 channel memory, synthesised, handheld 345.00
BC150FB	10 channel memory, synthesised 144.90
BC2020	20 channel memory, AM/FM, synthesised 269.00
BC250FB	50 channel memory, synthesised 289.00

TONO	
THETA 9000E	RTTY CW/ASCII, Tx/Rx 669.00
THETA 550	RX only 299.00

AMPLIFIERS	
UC70	430MHz 55W + preamp 159.00
2M 50W	144MHz 30 50W 69.00
2M 100W	144MHz 100W + preamp 129.00
MR 150W	144MHz 130 150W + preamp 169.00
MR 250W	144MHz 250W + preamp 325.00

TASCO	
TeleReader CWR685	RTTY CW/ASCII 769.00
TeleReader CWR670E	As above Rx only 345.00
TeleReader CWR610E	Basic unit 189.00

TOKYO HY-POWER	
HL32V	VHF 30W linear 1.5W drive HI LOW output 53.50
HL82V	VHF linear preamp output meter 2-12W in 35-85 + out 144.50
HL160V	VHF linear preamp output meter 1-10W in 160W + out 242.40
HL45U	UHF linear preamp 2-15W in 10-45W out 119.75
HC150	HF ATU SWR/Power meter 200W PEP 62.50
HC2000	HF 2kW ATU SWR/Power meter 6 POS ant. switch, 6 to 1 vernier high Q coils 2kW peak 1kW continuous 276.55

HI-MOUND MORSE KEYS	
HK702	Up down keyer marble base 24.50
HK704	Up down keyer 16.68
HK705	Up down keyer 12.50
HK706	Up down keyer 13.75
HK708	Up down keyer 11.96
HK808	Up down keyer marble base 33.57
MK734	Twin paddle keyer 10.95
MK705	Twin paddle keyer marble base 22.00

BNOS ELECTRONICS	
12/6A	Power supply, 13.8V, 6 amp fully protected 48.30
12/12A	Power supply, 13.8V, 12 amp, fully protected 86.40
12/24A	Power supply, 13.8V, 25 amp, fully protected 125.45
12/40A	Power supply, 13.8V, 40 amp, fully protected 225.40

DRAE	
FULLY PROTECTED POWER SUPPLIES	
4 amp	30.75 6 amp 49.00
12 amp	74.00 24 amp 105.00

VHF Wavemeter 130/450MHz 27.50
Morse Tutor 49.00

ALINCO	
ELH 230	2M RF amp 3W in/30W out 39.00
ELH 720	70cm RF amp 1W in/18W out 59.00
EMR 400	Rotator - heavy duty 39.00

TET ANTENNAS	
AX210N	10 ele. yagi for 2m crossed 74.95
HB10F2T	2 ele. 10m mono band beam 51.50
HB10F3T	3 ele. 10m mono band beam 74.95
HB15F2T	2 ele. 15m mono band beam 60.66
HB15F3T	3 ele. 15m mono band beam 93.46
HB15M25P	VP mini size 15m 2 ele. 69.50
HB15M35P	VP mini size 15m 3 ele. 102.30
HB34D	4 ele. tri band beam 10/15/20m 222.90
HB33SP	3 ele. tri band beam 10/15/20m 192.50
HB35C	Tri band array 10/15/20m 283.95
HB35T	5 ele. 10/15/20m 278.50
MV38H	Vertical for 10/15/20m 47.99
MV48H	Vertical for 10/15/40m 48.99
MV58H	Vertical for 10/15/20/40/80m 63.95
MLA4	Loop antenna 10/15/40/80 105.60
SO22	Phased 2 ele. swiss quad 2m 58.95
SOY06	6 ele. quagi 2m 45.75
SOY08	8 ele. quagi 2m 52.75
HB210S	10 ele. dual driven yagi 2m 47.99
TE214	14 ele. long yagi 2m 74.40
SSL720	9 x 2 ele. (18) slot fed 70cm 135.60
HB23SP	2 ele. tri band beam 10/15/20m 144.79
SSL218	9 x 2 ele. (18) slot fed 2m 17.25
TPH2	Phasing harness 2m 67.90
OYU10	10 ele. quagi 70cm 66.99
SQ007	70cm 2 ele. phased swiss quad 97.50
SQ10	Swiss quad 10m 106.90
SQ15	Swiss quad 15m 106.90

ANTENNA SWITCHES	
SA450	SO239 connectors, 1 in, 2 out 9.75
SA450N	N type connectors, 1 in, 2 out 12.75

ROTATORS	
KR250	Kenpro Lightweight 1-1/2" mast 54.00
9502B	Coloroto (Med. VHF) 56.60
KR 400RC	Kenpro-inc. lower clamps P.O.A.
KR 600RC	Kenpro-inc. lower clamps P.O.A.

BENCHER	
BY1	Keyer Paddle (black base) 38.50
BY2	Keyer Paddle (chrome base) 48.50
BY3	Keyer Paddle (gold plated) 52.00
ZA 1A	Balun 3.5-30MHz for dipoles 15.00
ZA 2A	Balun 14-30MHz for beam ant. 17.25

ADONIS MICROPHONES	
202HD	Head set mic with control box and fet head 29.00
202HM	Headphones unit, fet mic with control box 39.20
MS10	Mobile speaker and message pad, visor mount 16.25

WELZ PRODUCTS	
SP200	1.8 160MHz 20 200W 1kW PWR SWR Meter 69.95
SP300	1.8 150MHz 20 200W 1kW PWR SWR Meter 97.00


SP400	130-500MHz 5-20-150W PWR/SWR Meter 69.95
SP600	1.8-500MHz 20-100-2kW PWR/SWR Meter 97.00
SP15M	1.8-160MHz 5-20-200W PWR/SWR Meter 35.00
SP45M	130MHz-470MHz POWER/SWR Meter 51.00
SP-10X	Compact version of SP15M 24.45
SP250	1.8-60MHz 20-200-2kW 49.50
SP350	1.8-500MHz 5-20-2kW 59.95
SP380	Compact version of SP300 (200 watts max) 49.00
AC38	3.5-30MHz ATU 400W PEP (8 bands) 65.00
CT15A	15-50W dummy load. (PL259) 7.95
CT15N	150/400W dummy load. ('N' plug) 13.95
CT150	150/400W dummy load. Rated 250MHz (SO239) 35.50
CT300	300/1kW dummy load 250MHz (SO239) 49.50
CT03N	3W dummy load 1.3GHz ('N' socket) 30.00
CH20A	2 way coax switch 1kW 900MHz (SO239) 17.95
CH20N	2 way coax switch 1kW 1.3GHz ('N' socket) 31.95
TP05X	50-500MHz power meter with load 13.95
TP25A	50-500MHz 25W power meter with load 17.50
TP20G	30-1500MHz power meter with load 139.00
CA35A	Static discharge protector. DC 500MHz 300w SO239 10.75
CA23N	Static discharge protector. DC 1500MHz 300w 'N' 12.60

MICROWAVE MODULES	
MMT 144 28	2M Transverter for HF Rig 109.95
MMT 432 28S	70cm Transverter for HF Rig 159.95
MMT 432 144R	70cm Transverter for 2m Rig 184.00
MMT 70 28	4m Transverter for HF Rig 115.00
MMT 1296 144	23cm Transverter for 2m Rig 184.00
MML 144 30LS	2m 30W linear Amp (3W1/P) 69.95
MML 144 50S	2m 50W linear Amp (10W1/P) 85.00
MML 144 100S	2m 100W linear Amp (10W1/P) 139.95
MML 432 20	70cm 20W linear Amp (3W1/P) 85.00
MML 432 50	70cm 50W linear Amp 109.95
MML 432 100	70cm 100W linear Amp 228.65
MM 2001	RTTY to TV converter 189.70
MM 4001	RTTY transceiver 269.00
MM 400KB	RTTY transceiver with keyboard 299.00
MMC 50 28	6m converter to HF Rig 29.90
MMC 70 28	4m converter to HF Rig 29.90
MMC 144 28	2m converter to HF Rig 29.90
MMC 432 28S	7cm converter to HF Rig 37.90
MMC 432 144S	70cm converter to 2m Rig 37.90
MMC 435 600	70cm ATV converter 27.90
MMK 1296 144	23cm converter to 2m Rig 69.95
MMD 050 500	500MHz dig. frequency meter 75.00
MMD 600P	600MHz prescaler 29.90
MNDP 2	Frequency counter probe 14.90
MMA 28	10 meter pre amp 16.95
MMA 144V	2m RF switched pre amp 34.90
MMF 144	2m band pass filter 21.90
MMF 432	70cm band pass filter 11.90
MMS 1	The morse talker 115.00
MMS 2	Advanced morse trainer 169.00

DATONG	
PCI	Gen. Cov. Converter HF on 2m 137.42
VLF	Very Low Frequency Converter 29.90
FL1	Frequency Agile Converter 79.35
FL2	Multi mode Audio Filter 89.70
FL3	FL2 with auto notch NEW 129.37
ASP	Auto R.F. Speech Clipper (Trio or Yaesu plug) 82.90/89.70
D75	Manually controlled R.F. Speech clipper 56.35
RFC M	R.F. Speech Clipper Module 29.90
D70	Morse Tutor 56.35
AD 270	Indoor Active Filter (inc. PSU) 54.05
AD 370	Outdoor Active Filter (inc. PSU) 71.30
MK	Keyboard morse sender 137.42
PTS1	Programmable tone squelch system (two units) 45.99
RFA	Wideband preamplifier 33.92
MPU	Mains Power Unit 6.90


muTek	
SLNA 70s	70MHz switched preamp 37.10
SLNA 70u	70MHz unswitched preamp 22.40
SLNA 70ub	Unboxed SLNA 70u 13.70
SLNA 144s	144MHz switched preamp (now 0.9dB nf typical!) 37.10
SLNA 144u	144MHz unswitched preamp 22.40
SLNA 144sb	Unboxed SLNA 144u 13.70
BLNA 432ub	Optimized preamp for FT290RD NEW 27.40
TLNA 432s	1.3dB nf sub-min 432MHz preamp 13.70
TLNA 432u	432MHz bipolar unswitched preamp 74.90
TLNA 432ub	Unboxed TLNA 432u 29.40
GLNA 432u-1	432MHz gasfet unswitched preamp 0.8dB nf/13dB gain PLA
GLNA 432u-2	432MHz gasfet unswitched preamp 0.65dB nf/13dB gain PLA
BLNA 129ub	1.3GHz bipolar unswitched preamp 1.8dB nf/12dB gain 24.50
GLNA 129ub	1.3GHz two-stage ultra-low noise gasfet unswitched preamp 20dB gain 82.25
HDR A 95u-1	1.5dB n/8.5dB gains high dynamic range band II preamp (input intercept + 22dBm) 32.90
HDR A 95u-2	11.5dB gain variant (input intercept + 16dBm) 32.90
BBBA 500u	20-500MHz broadband high dynamic range preamp 29.00
BBA 860u	250-860MHz broadband low-noise preamp 22.60
XBPF 700ub	Band IV-V bandpass tv filter 2.95
PPSU 012	12v (nominal) mains psu for BBBA 500u and BBBA 860u 6.90
RPCB 144ub	FT221/225 replacement front-end board 71.00
RPCB 251ub	IC211/251E replacement front-end board 76.90

AMPLIFIERS

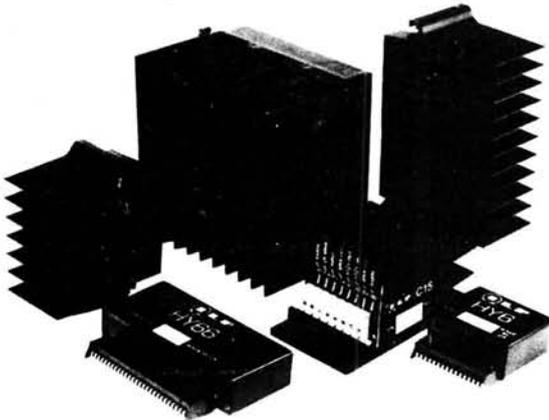

Over the last few years we have received feedback via the general public and industry that our products are from Taiwan, Singapore, Japan, etc... ILP are one of the few 'All British' electronics Companies manufacturing their own products in the United Kingdom. We have proved that we can compete in the world market during the past 12 years and currently export in excess of 60% of our production to over twenty different countries - including USA, Australia and Hong Kong. At the same time we are able to invest in research and development for the future, assuring security for the personnel, directly and indirectly, employed within the UK. We feel very proud of all this and hope you can reap some of our success.

I.L.Potts - Chairman

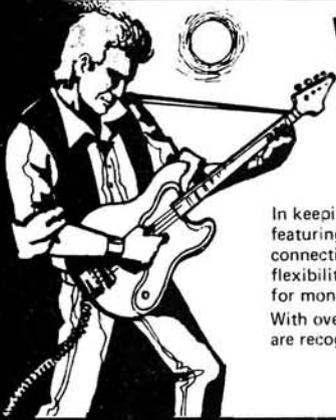

WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4-8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4-8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY6060	30 + 30	4-8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15v/ μ s. Rise time: 5 μ s. S/N ratio: 100db. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz >400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre-amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre-amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre-amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre-amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93	PSU 52X	2 x HY124	£17.07
PSU 41X	1 or 2 HY60, 1 x HY6060, 1 x HY124	£13.83	PSU 53X	2 x MOS128	£17.86
PSU 42X	1 x HY128	£15.90	PSU 54X	1 x HY248	£17.86
PSU 43X	1 x MOS128	£16.70	PSU 55X	1 x MOS248	£19.52
PSU 51X	2 x HY128, 1 x HY244	£17.07	PSU 71X	2 x HY244	£21.75

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4-8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£30.41
MOS 248	120	4-8	<0.005%	<0.006%	± 55	120 x 78 x 80	850	£39.86
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 100	1025	£45.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Slew rate: 20v/ μ s. Rise time: 3 μ s. S/N ratio: 100db

Frequency response (-3dB): 15Hz - 100KHz. Input sensitivity: 500mV rms. Input impedance: 100K Ω . Damping factor: 100Hz >400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

Robust construction.

£9.14 (inc. VAT)

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz

S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω . Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

Model Number	For Use With	Price inc. VAT
PSU 72X	2 x HY248	£22.54
PSU 73X	1 x HY364	£22.54
PSU 74X	1 x HY368	£24.70
PSU 75X	2 x MOS248, 1 x MOS368	£24.70

TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

*Gold service available.
21 days manufacture for urgent deliveries.

*Orders despatched within 7 days of receipt for single or small quantity orders.

*5 year no quibble guarantee.

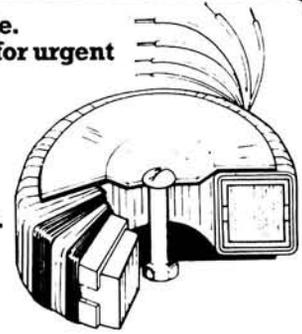

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
15 VA 62 x 34mm 0.35Kg Regulation 19%	0x010	6+6	1.25	£5.12 + p & p £0.78 + VAT £0.89 TOTAL £6.79	120 VA 90 x 40mm 1.2Kg Regulation 11%	4x010	6+6	10.00	£7.42 + p & p £1.72 + VAT £1.37 TOTAL £10.51	300 VA 110 x 50mm 2.6Kg Regulation 6%	7x013	15+15	10.00	£10.88 + p & p £2.05 + VAT £1.94 TOTAL £14.87
	0x011	9+9	0.83			4x011	9+9	6.66			7x014	18+18	8.33	
	0x012	12+12	0.63			4x012	12+12	5.00			7x015	22+22	6.82	
	0x013	15+15	0.50			4x013	15+15	4.00			7x016	25+25	6.00	
	0x014	18+18	0.42			4x014	18+18	3.33			7x017	30+30	5.00	
	0x015	22+22	0.34			4x015	22+22	2.72			7x018	35+35	4.28	
	0x016	25+25	0.30			4x016	25+25	2.40			7x026	40+40	3.75	
	0x017	30+30	0.25			4x017	30+30	2.00			7x025	45+45	3.33	
						4x018	35+35	1.71			7x033	50+50	3.00	
						4x028	110	1.09			7x028	110	2.72	
			4x029	220	0.54	7x029	220	1.36						
			4x030	240	0.50	7x030	240	1.25						
(encased in ABS plastic)														
30 VA 70 x 30mm 0.45Kg Regulation 18%	1x010	6+6	2.50	£5.49 + p & p £1.10 + VAT £0.99 TOTAL £7.58	160 VA 110 x 40mm 1.8Kg Regulation 8%	5x011	9+9	8.89	£8.43 + p & p £1.72 + VAT £1.52 TOTAL £11.67	500 VA 140 x 60mm 4Kg Regulation 4%	8x016	25+25	10.00	£14.38 + p & p £2.40 + VAT £2.52 TOTAL £19.30
	1x011	9+9	1.66			5x012	12+12	6.66			8x017	30+30	8.33	
	1x012	12+12	1.25			5x013	15+15	5.33			8x018	35+35	7.14	
	1x013	15+15	1.00			5x014	18+18	4.44			8x026	40+40	6.25	
	1x014	18+18	0.83			5x015	22+22	3.63			8x025	45+45	5.55	
	1x015	22+22	0.68			5x016	25+25	3.20			8x033	50+50	5.00	
	1x016	25+25	0.60			5x017	30+30	2.66			8x042	55+55	4.54	
	1x017	30+30	0.50			5x018	35+35	2.28			8x028	110	4.54	
50 VA 80 x 35mm 0.9Kg Regulation 13%	2x010	6+6	4.16	£6.13 + p & p £1.35 + VAT £1.12 TOTAL £8.60	225 VA 110 x 45mm 2.2Kg Regulation 7%	6x012	12+12	9.38	£9.81 + p & p £2.05 + VAT £1.78 TOTAL £13.64	625 VA 140 x 75mm 5Kg Regulation 4%	9x017	30+30	10.41	£17.12 + p & p £2.55 + VAT £2.95 TOTAL £22.62
	2x011	9+9	2.77			6x013	15+15	7.50			9x018	35+35	8.92	
	2x012	12+12	2.08			6x014	18+18	6.25			9x026	40+40	7.81	
	2x013	15+15	1.66			6x015	22+22	5.11			9x025	45+45	6.94	
	2x014	18+18	1.38			6x016	25+25	4.50			9x033	50+50	6.25	
	2x015	22+22	1.13			6x017	30+30	3.75			9x042	55+55	5.68	
	2x016	25+25	1.00			6x018	35+35	3.21			9x028	110	5.68	
	2x017	30+30	0.83			6x026	40+40	2.81			9x029	220	2.84	
80 VA 90 x 30mm 1Kg Regulation 12%	3x010	6+6	6.64	£6.66 + p & p £1.72 + VAT £1.26 TOTAL £9.64	250 VA 110 x 50mm 2.5Kg Regulation 7%	6x025	45+45	2.50		9x030	240	2.60		
	3x011	9+9	4.44			6x028	110	2.04						
	3x012	12+12	3.33			6x029	220	1.02						
	3x013	15+15	2.66			6x030	240	0.93						
	3x014	18+18	2.22											
	3x015	22+22	1.81											
	3x016	25+25	1.60											
	3x017	30+30	1.33											
	3x028	110	0.72											
	3x029	220	0.36											
3x030	240	0.33												

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows.

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

For 110V primary insert '0' in place of 'X' in type number

For 220V primary (Europe) insert '1' in place of 'X' in type number

For 240V primary (UK) insert '2' in place of 'X' in type number

Also available at Electrovalve.

NEW PRODUCTS

HYBRID REGULATOR MODULES

The HR314 and HR614 regulated power supplies provide a constant 13.8 volt d.c. output at up to 3 Amp or 6 Amp respectively. The modules are encapsulated to an integral heatsink and are fully short circuit protected making them suitable for home or bench running of CB, car stereos or any 12 volt d.c. equipment required for many hobby or professional applications.

HR314 £10.23 inc. VAT

HR614 £18.51 inc. VAT

TECHNICAL SPECIFICATIONS

MODULE	HR314	HR614
Output Voltage	+13.8v ±5%	+13.8v ±5%
Output Current	Up to 3A	Up to 6A
Current limit (nominal)	3.5A approx	7A approx
Maximum Input Voltage	+30v	+30v
Minimum Input Voltage	+16v	+16v
Maximum Input Voltage for nominal output current	+20v	+20v
Maximum output current at 30v input	1.8A approx	3.5A approx
Output ripple (100Hz) - See Note 1	+10mV rms	+10mV rms
Size in mm.	76 x 68 x 40 high	120 x 78 x 40 high

POWER SUPPLY UNITS: comprising toroidal transformer plus 90 x 50 x 55 mm high printed circuit board containing smoothing and rectification


PSU31X Suitable for running one HR314 at full rated current. £13.17 inc. VAT
PSU56X Suitable for running one HR614 at full rated current. £19.13 inc. VAT

For 110v operation insert 0 in place of X — brown primary leads.

220v (Europe) operation insert 1 in place of X — pink primary leads.

240v (UK) operation insert 2 in place of X — orange primary leads.

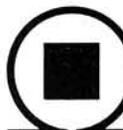For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.



Post to ILP Electronics Ltd, Trillick Bell House, Rogate Close, Canterbury CT2 7EP Kent, England.
Telephone (0227) 54778 Telex 9615781

ILP ELECTRONICS LTD.

SETTING UP A STATION . . .

The obvious thing you're going to need as an SWL is a decent HF receiver, so why not drop in to Photo Acoustics and listen to these, for a start . . .



The new high technology ICOM R70 at £499

The memorable new TRIO R2000 at £398.82



Trio's low budget high quality receiver The Trio R600 at only £257.60



To complete the range for you to hear, we have the top quality Yaesu FRG 7700 at £335 and the budget conscious Lowe SRX 30D at only £215.

NOW AVAILABLE



- VIC 20 COMPUTER + RECEIVE AND TRANSMIT RTTY MODULE ONLY £249.90 inc.
- COMMODORE 64 COMPUTER + RECEIVE AND TRANSMIT RTTY MODULE ONLY £339.90 inc.
- SWL VERSION
- VIC 20 COMPUTER + RECEIVE RTTY MODULE ONLY £239.90
- COMMODORE 64 COMPUTER + RECEIVE MODULE ONLY £329.90

Specifications in brief:

- * Variable baud rates
- * Normal/Reverse receive switch
- * Split screen
- * 25 Pre-programmed messages and 8 user entered
- * 425Hz Commercial shift
- * Selective call with printer
- * Morse indent for class 'A' Licenses

Modules available separately, please ring for prices Allow 14/21 days for delivery of the Modules

PLEASE NOTE - PRICES SUBJECT TO ALTERATION WITHOUT NOTICE

See the Professionals

You'll find all you need at Photo Acoustics. We can offer help and advice, the chance to try out the gear and financial facilities too. We offer Creditcharge Instant Finance and accept Access and Barclaycard. Part exchange welcome. Come and see us: Derek G3TGE, Roy G3TLE & Kerry G6IZF - or phone 0908 610625.

Photo Acoustics Ltd.
● OF NEWPORT PAGNELL ●

Four minutes from the M1. Exit Junc. 14. Head for the High St., Newport Pagnell. We're at No. 58. Parking at rear, opposite, or round the corner in Silver St.



SCARAB SYSTEMS

39, Stafford Street, Gillingham, Kent ME7 5EN.
(0634-570441)

AMATEUR RADIO PROGRAMS

RTTY

	ZX.81	SPECTRUM
Cassette & PCB	£13.45	£15.00
Complete package	£25.10	£29.55
Assembled & Tested	£30.00	£35.00

BBC-B £9.20 VIC-20 } Prices to be
 PET £7.50 Dragon 32 } announced.
 MPTU-1 RTTY/AMTOR terminal unit for use with all computer based systems. £69.70.

Morse Tutor programs all at £5.00 each for:-
 BBC-B* DRAGON 32* TRS-80* SPECTRUM*.

MORE BBC. PROGRAMS.

CW.QSO. Complete Rx/Tx program £7.50
 MULTIFILE. A versatile filing system £10.25
 TELLTEX. 21-page VIDEO MAGAZINE £15.00

All prices include VAT & postage. Please allow 14 days delivery.

Write for further details of these and other programs.

WANTED Amateur Radio, Technical & Business software for all popular home micro's.



NORTHERN COMMUNICATIONS

"NEW!"

The Nortower 30'

At long last it's arrived.
 The Tower you can afford!

This is the tower that we always wanted to offer to you but couldn't, so now we've made it for ourselves! A realistic, no nonsense tower made for us, in Britain with British Standard materials, hot dipped galvanised steel construction and supplied complete with 900lb winch and rope.

The beauty of our eye pleasing design is in its ease of installation and minimum closed height of 12'6". This does away with the need for costly tilt overs and makes it ideal for wall mounting, particularly against a garage or house extension.

A wide variety of accessories are available and customers special requirements can be catered for. This even includes a planning service, if required!

"Nortower 30." 30 foot galvanised tower, including winch and rope £279.00 inc. VAT
 Wall Brackets (pair required) @ £22.00 each

Stand offs available 6", 9", 12"
 Special Wall Bracket 18", 24" Price on request
 Bell Housing: for Rotator + Bearings (not inc.) £29.00
 Hinge Base and tilt overs to order Price on request
 Trailer towers to order Price on request

Delivery arranged OR why not even Cash and Carry!
 Finance Scheme from £30.00 deposit and £11.00 per month . . . interest 2.25% pm. 30.6% apr.



Cushcraft
ANTENNAS

ORDER NOW or send large SAE for full details to:

NORTHERN COMMUNICATIONS
 299-303 Claremount Road, Halifax, West Yorkshire HX3 6AW.
 Tel: 0422 40792

THE AMCOMM HOTLINE



CALL 01-422 9585 (THREE LINES) NOW



YAESU FT 757 GX

Here is a little General Coverage gem that **does it all and has it all** - Usual high consideration for the SSB man and - Lo and behold **total consideration for the CW man** - if you are into both you're on to a real winner - Look closely - no extras! Everything you'll need already installed. **Full Break In-CW Filter - Iambic keyer** - 25 Khz marker - IF/Shift width - Noise blanker - Switchable AGC and RF preamp plus a lot more including **AM and FM fitted as standard. Twin V.F.O's**, RX coverage 150 Khz to 29.999 Mhz - transmit **160 to 10 metres with a commercial version** also available. Dimensions 238 x 98 x 238 mm and weighing only 4.5Kg - A real smash at a price you're going to like - send or call for full details and price. Tel: 01-422 9585.

YAESU FT102 9 Bander.



See the reviews on this rig and call us...we'll tell you some more.

ICOM 745/751/271


Three new ones just around the corner, two HF general coverage transceiver and one VHF base for 2M, stock should be with us by the time you read this, call 01-422 9585 for more information.

YAESU FT290RB



The biggest selling 2M rig ever...hands up if you haven't got one. Call 01-422 9585, we'll tell you how to own one.

YAESU FT101ZD Mk III

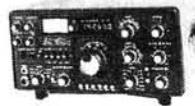

Available while they last, complete with FC902 ATU at £649.

YAESU FT980




Bob and Stan called us soon after we delivered, Bob said "At last a rig that does it all and does it right", Stan doesn't say a lot, "Magic" was his only comment.

ICOM 740 9 Band Transceiver



You'll hear nothing but good words on this one, ask an owner then call us on 01-422 9585.

ICOM 290H

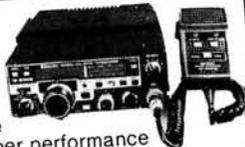

2M Multimode with same super performance as the 290E but with 25 Watts.

YAESU 726R



All mode base station, 2M, 70cms and 6M, think what three rigs would cost you and work out the value for money on this one. Call 01-422 9585, we'll give you the info and the price.

YAESU FT77



Probably the best HF mobile ever made, low frills and low bills, call 01-422 9585 and we'll tell you how low.

YAESU FT1

Yaesu say it's number one...one journal said "A lot of radio for a lot of money". If you can afford it...get the best, call for quote.



ICOM R70 Gen.Cov.Rx.



Silky smooth appearance with a silky smooth performance, thousand pounds value for well under £500, call 01-422 9585.

YAESU FT 208R/FT708R Handhelds



Loads of facilities at extremely competitive price, call 01-422 9585.

Amcomm Services,
194, Northolt Road, South Harrow,
Middlesex HA0 2EN.
Telephone: 01-422 9585 (3 lines)
Telex: 24263.

OPPOSITE SOUTH HARROW TUBE STATION ON THE PICCADILLY LINE

FAIR DEAL POLICY

At Amcomm, we believe we are here to do much more than sell boxes off the shelf. We are specialists in amateur radio equipment and our management and staff are all amateur radio enthusiasts. We sell nothing else. Many firms can give you a so-called fair deal, at the time of purchase, but only a handful of companies in the U.K. are fully equipped to give you a total after-sales service. Amcomm is one, with a wide range of spares, and speedy access to factory stocks, we offer a complete service. Whether you buy now or bought 10 years ago. What's more, we pride ourselves on being able to service everything we sell ourselves. Don't take our word for it, find out for yourself, ask around on the air, you'll keep coming up with the same answers, good competitive prices and excellent after-sales service. Go on, ask around.

SHOWROOM OPENING HOURS
TUE-FRI 10.00am-6.00pm CONTINUOUS
SAT. 9.00am-5.00pm CONTINUOUS

ASK FOR DETAILS
OF OUR INTEREST FREE AND
LOW DEPOSIT H.P.

All goods despatched within 24hrs. of receipt of payment (Saturdays excluded).

Be on a Winner!

A.R.R.A.
presents the

TWELFTH
AMATEUR RADIO AND ELECTRONICS
EXHIBITION

BIGGER AND BETTER THAN EVER...

ON

6th, 7th & 8th OCTOBER 1983

AT

THE EXHIBITION CENTRE
DONCASTER RACECOURSE

(LEGER WAY)

MAGNIFICENT EXHIBITION HALL EXCELLENT CATERING AND BARS

FREE CAR PARKING

ADMISSION: £1.50
OAP's & CHILDREN £1.00
PARTIES OF 15 AND OVER:
£1.25 (inc. postage)

Contact:

FRED HOPEWELL (G4PGC)
48 GLADSTONE STREET
LOUGHBOROUGH
LEICESTERSHIRE LE11 1NS

£500
VOUCHER PRIZES
IN
FREE
RAFFLE!

TALK-IN BY G3UER

(S22 & SU8)

**THE ODDS ARE 100-1 YOU
WILL ENJOY THE SHOW!**

See you at Doncaster!

Merriman

THE MERRIMAN REPORT—Review of the Radio Spectrum (30–960MHz)*—published on 27 July, was not what many people had expected. When the Interim Report was published last September, it recommended that closure of the 405-line TV services in Bands I and III should be speeded up and the bands used to expand land mobile services.

No such forthright recommendations on spectrum allocation appear in the Final Report, except to say that conventional terrestrial TV broadcasting cannot expect to get any more frequencies, either for the actual broadcast channels or for ancillary services (radio microphones, OB links, etc.), and may in fact have to be squeezed still more. Instead, the report concerns itself almost entirely with the operation of the administrative system which controls frequency allocation, assignment and monitoring.

The report says little that is new, but it does draw together and present clearly and forcefully, many of the factors affecting current and future use of the spectrum. It discusses publicly several things which have before been talked of only behind closed doors—in particular the position of the Radio Regulatory Department (RRD).

Originally, the RRD was part of the Post Office, staffed by engineers and administrators with a background in telecommunications. When the Post Office became a public corporation in 1969, those parts of it (including the RRD) which dealt with matters more appropriate to Government were detached and formed into the Ministry of Posts and Telecommunications

(MPT). This was disbanded in 1974 and responsibility for radio regulation then passed to the Home Office.

Through this series of moves, the functioning of the RRD remained largely unchanged, but its staff were now isolated in a small department and limited, so far as any sort of career structure was concerned, by being virtually the only technology-based part of the Home Office. Expertise in radio regulatory matters was lost each time a staff-member was promoted outside the RRD (the report mentions one engineer-turned-administrator who had moved on to the Prison Service), and new staff coming in from outside had to struggle whilst they learned to cope with work in an unfamiliar and highly technical subject.

It is our experience (and, according to evidence given to the Merriman committee, that of many other radio users) that individual staff members at the RRD are competent and unfailingly helpful. We have thrown a few brickbats in the direction of RRD in the past, but I think it fair to say that the Department is able to function at its present level of efficiency only because of the devotion of these staff, and despite the organisation under which they have to work and the pitiful undermanning.

It is to be hoped that the recent move of the RRD to the Department of Trade and Industry (recommended in the Report) will bring benefits by the closer contact with technology.

A summary of the recommendations of the Merriman Report will appear in our next issue.

*Cmd 9000, HMSO, £8.40, ISBN 0 10 190000 7

QUERIES

While we will always try to assist readers in difficulties with a *Practical Wireless* project, we cannot offer advice on modifications to our designs, nor on commercial radio, TV or electronic equipment. Please address your letters to the Editor, "Practical Wireless", Westover House, West Quay Road, Poole, Dorset BH15 1JG, giving a clear description of the problem and enclosing a stamped self-addressed envelope. Only one project per letter please.

Components for our projects are usually available from advertisers. For more difficult items, a source will be suggested in the "Buying Guide" box included in each constructional article.

PROJECT COST

The approximate cost quoted in each constructional article includes the box or case used for the prototype. For some projects the type of case may be critical; if so this will be mentioned in the Buying Guide.

INSURANCE

Turn to the following page for details of the PW Radio Users Insurance Scheme, exclusive to our readers.

CONSTRUCTION RATING

Each constructional project will in future be given a rating, to guide readers as to its complexity:

Beginner

A project that can be tackled by a beginner who is able to identify components and handle a soldering iron fairly competently. Generally this category will be used for simple projects, but sometimes for more complicated ones of wide appeal. In this case, construction and wiring will be dealt with in some detail.

Intermediate

A project likely to appeal to a wide range of constructors, and requiring only basic test equipment to complete any tests and adjustments. A fair degree of experience in building electronic or radio projects is assumed.

Advanced

A project likely to appeal to an experienced constructor, and often requiring access to workshop facilities and test equipment for construction, testing and alignment. Constructional information will generally be limited to the more critical aspects of the project. Definitely not recommended for a beginner to tackle on his own.

SUBSCRIPTIONS

Subscriptions are available at £13 per annum to UK addresses and £14 overseas, from "Practical Wireless" Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. Airmail rates for overseas subscriptions can be quoted on request.

BACK NUMBERS AND BINDERS

Limited stocks of some recent issues of *PW* are available at £1 each, including post and packing to addresses at home and overseas.

Binders are available (Price £5.50 to UK addresses, £5.75 overseas, including post and packing) each accommodating one volume of *PW*. Please state the year and volume number for which the binder is required.

Send your orders to **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF**. All prices include VAT where appropriate.

Please make cheques, postal orders, etc., payable to IPC Magazines Limited.

PW RADIO USERS INSURANCE SCHEME



Practical Wireless Radio Users Insurance Scheme was devised by Registered Insurance Brokers B. A. LAYMOND & PARTNERS LIMITED following consultation with PRACTICAL WIRELESS to formulate an exclusive scheme designed to meet the needs and requirements of: Amateur Radio Enthusiasts ● CB Radio Users ● Taxi Companies and Fleet Users with Radio Telephones. A copy of the Policy can be inspected at the offices of B. A. Laymond & Partners Ltd., or of Practical Wireless in Poole.



SPECIAL FEATURES

- All Risks Cover ● "New Lamps for Old" Cover (as defined in policy) ● Index Linked Cover to combat inflation ● Includes Personal Liability cover against damages payments of up to £500000 to members of the public ● Licence protection—covers legal costs arising from any breach of your licence conditions ● Equipment covered anywhere in the UK, Channel Islands and Isle of Man, but not Northern Ireland and Eire ● Fixed Antennas (Aerials) covered ● Frequency, Power and SWR Meters and similar radio-related test equipment covered ● 30 days cover on Western Europe included Free of Charge ● Absolute Security as this scheme is underwritten by a leading member of the British Insurance Association on the London Insurance Market ● Practical Wireless radio receiver and transmitter projects covered (when stated in feature) ● Available to Clubs and Organisations ● Available to Companies

†Write directly to B. A. LAYMOND & PARTNERS LTD, for a special application form and full details enclosing the coupon below.

Cover for property contained in vehicles is subject to a Limit of Liability of £250, increased to £750 where the vehicle is protected by a reputable audible alarm, correctly set and operational.

When the vehicle is unattended, mobile equipment secured so that tools or a key are required to remove it must be disguised or concealed from view. Portable and mobile equipment not so secured must be removed and placed in a locked boot or otherwise concealed from view, or removed from the vehicle entirely. Equipment not in a secure building or vehicle must not be left unattended.

B. A. Laymond & Partners Ltd., Practical Wireless and the Underwriters wish to make it clear that it is an offence to instal or use a radio transmitter in the UK except under the authority of a licence granted by the Secretary of State and it is not their intention to provide cover for or to encourage or condone the illegal use of CB and/or other communications equipment.

How Much Will It Cost?

Claims will be settled after deduction of an excess in the following manner:

Sum to Insure	£1000	£3000	£5000
Annual Premium	£20	£35	£45

Type of Loss	Excess
From saloon cars and hatchbacks with fully concealed luggage compartments	15% of claim (minimum £25)
From estate cars, vans and hatchbacks without concealed luggage compartments	25% of claim (minimum £25)
All others:	Sums insured up to £3000 £25 Sums insured up to £5000 £50

The premium is charged on sums insured in pre-selected bands. Thus equipment totalling £3750 would be in the band up to £5000, and the premium would be £45. Quotations for larger sums available on application.

How To Insure

Complete the application form below to obtain immediate insurance cover. Photocopies will not be accepted

APPLICATION FOR PRACTICAL WIRELESS RADIO USERS INSURANCE SCHEME					PW10/83
Name in full (State Mr, Mrs, Miss or Title)					
Address					
					Post Code
Occupation		Age	Phone No. (Home)	(Work)	
I/We hereby apply to insure the equipment detailed below					
BLOCK LETTERS	Manufacturer's Name	Model	Serial No.	Description of equipment to be insured e.g. Base station; Mobile; CB; etc.	VALUE £
	1				
	2				
	3	Antennas (Aerials), s.w.r. meters, etc.			
Please continue list of equipment on a separate sheet if necessary					TOTAL SUM TO INSURE £

DECLARATION: I/We hereby declare that: 1. The sums insured represent the full replacement value of the equipment. 2. I/We have not* had insurance cancelled, declined, restricted, or other terms imposed in any way other than the normal Policy terms. 3. This proposal shall be the basis of the contract and that the contract will be on the Underwriters normal terms and conditions for All Risks and Legal Costs/Expenses cover unless otherwise agreed. 4. I/We have not* sustained any loss or damage to any radio communications equipment or been involved in litigation relating to use of radio equipment during the past three years, whether insured or not. 5. All the above statements made in connection with this proposal are true and no material information has been withheld. 6. I/We understand no liability shall attach until this proposal shall have been accepted by Laymond's and the premium paid in full and a Certificate issued.

* If you have, please give details on a separate sheet.

Date

Signed

Rush us details of PW Club Insurance
PW Company Insurance

DELAY IN ARRANGING COVER COULD COST YOU A GREAT DEAL OF MONEY. COMPLETE THIS APPLICATION AND POST WITH YOUR PREMIUM MADE PAYABLE TO "LAYMOND'S" NOW. ADDRESS TO: PRACTICAL WIRELESS (INSURANCE), B. A. LAYMOND & PARTNERS LTD., 562 NORTH CIRCULAR ROAD, LONDON NW2 7QZ. TELEPHONE: 01-452 6611.

Transfer of Amateur Radio Licensing to the Post Office

All amateur radio licences will be issued and renewed by the Post Office Headquarters in Chesterfield on behalf of the Secretary of State for Trade and Industry from 19 September.

The transfer of the operation from the Radio Regulatory Division was announced on 28 July by Mr Alex Fletcher, minister responsible for corporate and consumer affairs in the Department of Trade and Industry, in reply to a Parliamentary question from Mr Geoff Lawler MP (Bradford North).

Mr Fletcher said, "The Post Office, who will computerise the operation as soon as possible, are prepared to guarantee a turn-round in normal conditions of five working days and at peak times of ten. This will help to ensure that the recent improvement in the speed of issue of these licences is maintained".

Currently the Post Office carry out the issue of Citizens' Band radio licences on behalf of the Secretary of State. Unlike CB licences at present, there will be **no provision for the issue of amateur licences over the**

counter at Post Offices. All applications for amateur radio licences will be processed by post.

Any application for a new licence on or after 19 September, should be sent to the *Radio Amateur Licensing Unit, Chetwynd House, Chesterfield, Derbyshire S49 1PF, tel: (0246) 207555*, from whom application forms may be obtained. An amateur holding a current licence which is due for renewal in October or thereafter will be sent a fee reminder by the Post Office. Renewals for October will be issued during the week commencing 19 September.

Radio Rally

The third North Devon Radio Rally is to be held in the Bradworthy Memorial Hall (near Holsworthy) on Saturday 5 November between 10.30am and 5.00pm.

There will be all the usual rally attraction including bring and buy stand etc. Plus talk-in on 144MHz (S22).

Further details from: *K. J. Nicholls G8MXI, QTHR.*

More and Faster Ceefax

More information, and faster access times, for users of the BBC Ceefax service could be the result of a decision announced recently by Aubrey Singer, Managing Director of BBC Television.

Extra digital information could be added to the Ceefax signal, reducing the average waiting time for a page to five or six seconds. At the same time, the number of pages of information could be increased by using six television lines carrying data rather than the four used at present.

Improvements in receiver technology should now make it possible to add data to lines 13 and 14, without impairing the quality of normal reception. The digital pulses of Ceefax are carried within the normal television signal, while the receiver scanning spot is returning to the top of the screen between pictures.

Tests need to be made to ensure there will be no impairment to normal television pictures. If these tests are satisfactory the BBC will be seeking Home Office authority to start an extended service in the Spring of 1984.

BBC Engineering Information Department, Broadcasting House, London W1A 1AA.

Pw RADIO USERS INSURANCE SCHEME Club Discount Scheme

SUMS INSURED	UP TO £1000	UP TO £3000	UP TO £5000	
INDIVIDUAL PREMIUM	£20	£35.00	£45.00	
Premium (per member) for club Master Policies	5-10 members	£18	£31.50	£40.50
	11-25 members	£17	£29.75	£38.25
	26-50 members	£16	£28.00	£36.00
	51-100 members	£15	£26.25	£33.75
	101+ members	£14	£24.50	£31.50

Do you belong to a radio club or society? Did you know that premium discounts of up to 30 per cent are available to members where the club has effected a Master Policy with the PW Radio Users' Insurance Scheme? The more members that participate, the better the rate—the table tells you how much you and your fellow club members could save.

Write directly to B. A. Laymond & Partners for further details and an application form, enclosing the coupon from the facing page.

RAE Courses

Courses to prepare students for the Radio Amateurs Examination (City and Guilds 765) will be available at the following locations:

Canterbury—*College of Technology, Canterbury. Tel: (0227) 66081.* To be held on Monday evenings, with enrolment on 12 September and the Course Tutor will be G3LCK.

Cheshunt—*East Herts College, Turnford, Herts. Tel: Hoddesdon (0992) 66451.* On Mondays between 7.00 and 9.00pm, starting in September. Final details from either Jim Sleight G30JI (QTHR). Tel: Ware (0920) 4316, or Mr J. France at the college. Subject to demand a Morse Course may also be run.

Crawley—*Sara Robinson School, Ifield, Crawley, West Sussex, on Monday or Thursday between 7.00 and 9.00pm, starting 19 and 22 September. Enrolment 12 and 14 September between 7.00 and 9.00pm. Further details from Steve Webb G4GHO. Tel: Crawley (0293) 25742.*

Derby—*Derby College of Further Education, Wilmorton, Derby DE2 8UG. Tel: (0332) 73012, commencing 28 September, enrolment 12 and 13 September. Further details from, the Course Tutor, F. Whitehead G4MLL at the college.*

Durham City—RAE classes and Morse classes will be available in the city, details from J. F. Greenwood G3ZJY (QTHR). Tel: (0385) 66773.

Hendon—*Hendon College of Further Education, Williams Building, The Burroughs, Hendon NW4 4BT. Tel: 01-202 3811 Ext. 7. Starting 27 September between 7.30 and 9.30pm. Enrolment 13 and 14 September between 2.00 and 8.00pm. For further information contact either A. M. McDonagh or Chris Holford at the college.*

Melton Mowbray—*Melton Mowbray College of Further Education, Asfordby Road, Melton Mowbray, Leics. LE13 0HJ. Tel: (0664) 67431, enrolment on 6 and 7 September. Further details from either the college or the Course Tutor, K. G. Melton G3WKM. Tel: (0664) 68810.*

Newquay—*Tretherras School, Newquay, Cornwall, on Mondays between 7.00 and 9.00pm starting 26 September. Enrolment at the school on 21 September between 6.30 and 8.30pm or by post to the Adult Education Principal, MCCFE, Palace Road, St. Austell, Cornwall. Further details from the Course Tutor, Bob Lawrence G4LDA. Tel: Wadebridge (020 881) 3649. A Morse class will be available if required.*

Sandiacre—*Sandiacre Adult Education Centre, Friesland School, Nursery Avenue, Sandiacre, near Nottingham NG10 5HG, enrolment at the centre on 13 September at 7.15pm, classes start the following Tuesday at 7.15pm. The Course Tutor will be G3VGW and further details are available from the Principal, Mr. H. G. Crowther at the centre.*

St. Austell—*Mid-Cornwall College of Further Education, St. Austell, Cornwall, commencing 27 September between 7.00 and 9.00pm. Enrolment by post or at the college on 21 September between 6.30 and 8.30pm. Further details from the Course Tutor, J. S. Kennedy G4DND (QTHR). Tel: St. Columb (0637) 880 479.*

Stevenage—*Stevenage and District Amateur Radio Society will hold a "Beginner's Evening" at 8.00pm on the 8 September in the Fairlands Community Centre. If sufficient interest is shown, the society will run an RAE class on Thursdays, starting 15 September at the centre. Further details from the Secretary, Cliff Barber G4BGP, 13 The Sycamores, Baldock, Herts. Tel: (0462) 893736.*

Thanet—*A 20 week course commencing 29 September between 7.30 and 9.30pm. In addition to the RAE syllabus, students will construct one or two practical projects. The lecturer will be Dr. Ken Smith G3JIX, and further information and enrolment can be arranged at any Hilderstone Adult Education Centre in Thanet, or by post from Hilderstone House, St. Peters, Broadstairs, Kent.*

"Two Emma Toc" Again

After a break of sixty years the callsign used by Marconi's original Wireless Telegraph Company to introduce Britain's first public entertainment broadcasts was re-launched on Saturday 2 July 1983 by the newly formed Marconi Radio Society.

Practical Wireless was honoured to be among the many guests invited to Marconi Space & Defence Systems' Stanmore headquarters to witness the famous callsign, now prefixed with 'G' to accord with current UK practice, being transmitted to amateur stations around the world.

The event was made all the more interesting as the station used British-made KW Electronics equipment.

One of the special guests was Eric Godsmark, Regional Secretary of the International Amateur Radio Union, who is seen in the picture presenting a pennant to George Benbow G3HB,



Chairman of the Marconi Radio Society (left).

Marconi's Wireless Telegraph Company Ltd. was first granted an experimental licence in the summer of 1920 to use 2ET to introduce news bulletins. The licence was rapidly revoked by the authorities after a concert had been broadcast featuring a Danish tenor. The Wireless Society of London, now the RSGB, persuaded the Postmaster General to allow the station to use the callsign for entertainment purposes and the first scheduled entertainment broadcast in the UK was transmitted on 428.6kHz from Writtle, near Chelmsford, on 14 February 1922, under the callsign "Two Emma Toc". Transmissions, which were restricted to thirty minutes every Tuesday evening, ceased in January 1923.

Welsh Amateur Radio Convention

The Welsh Amateur Radio Convention celebrates its tenth anniversary this year and will be held on 25 September. Once again the venue will be the Oakdale Community College, Blackwood, Gwent and admission will be £1.

There will be all the usual trade stands and a lecture programme featuring a lecture on amateur satellites generally and OSCAR 10 in particular, by Ron Broadbent G3AAJ, Hon. Sec. of AMSAT-UK. Also there will be a tape/slide presentation of a DXpedition and a general interest film.

Doors open at 10.00am and Mr. D. E. Baptiste CBE, President of the RSGB, will officially open the Convention at 11.00am. There will be "talk-in" on S22—take exit 27 on the M4—plus the usual high standard of refreshments will be available.

Further details from: R. B. Davies GW3KYA, Convention Secretary, 16 Vancouver Drive, Penmain, Blackwood, Gwent NP2 0UQ. Tel: (0495) 225825.

Practical Wireless, October 1983

OSCAR-10

Following our interim report last month we now have the "final" orbital data for this latest and most successful AMSAT space vehicle.

To date everything — r.f. wise — is performing exactly as planned. As reported last month, a controlled burn of the satellite's kick motor was expected to increase the inclination angle from the initial 26° up to approximately 57° — this manoeuvre was attempted in the early hours of the 26 July and produced no discernable position change. It is believed that the failure of the kick motor is due to either rupture of the propellant tank/fuel line, or damage to the motor caused by impact of the launch vehicle final stage, shortly after the initial launch separation. This should not have occurred and again is believed to be as a result of incorrect manoeuvring of the launch vehicle. These delicate positional changes are brought about by selective venting of residual gas storage tanks on the launcher. A further problem created by this collision was a slight misalignment of the 144MHz antenna.

In practical terms, the failure of the

correction burn will result in the anticipated 16 hours per day coverage over the northern hemisphere being reduced to 11 hours with its large "footprint" slowly shifting towards the East. In many ways this is not such a bad thing as it will allow, initially, a much more evenly distributed coverage of the Northern and Southern hemispheres.

Should it be necessary to attempt to alter the inclination angle, OSCAR-10 does have a magnetorquer device aboard, which could be used to alter the angle in 0.5° increments. However, this method requires power from the already tightly budgeted solar cell/battery system and will probably only be used for routine alignment corrections.

Parameters — August/September: OSCAR-10, Catalogue Number 14129, taken from revolution 58. All figures rounded-up:

Inclination — 25.8°; RA of node — 250.01; Eccentricity — 0.604; Mean Anomaly — 333.5°; Mean Motion — 2.05 rev/day; Semi-major Axis — 26 106.2km; Anom. Period — 699.5 minutes; Apogee — 35 505km;

Perigee — 3951km.

Updates on this data are available from the bi-monthly AMSAT Calendar.

Full details of the Phase IIIB device, including pictures, spread over 45 pages, will appear in the August issue of *OSCAR News* which is available to all AMSAT-UK members.

In the words of Karl Meinzer DJ4ZC at the European Command Centre, the complete verification of all sub-systems indicates that OSCAR-10 is: "the most perfect amateur satellite yet put into earth orbit".

AMSAT-UK have asked *PW* to remind readers that it is essential that no non-space transmissions within the internationally recognised frequency limits 145.800–146.000MHz be made. Problems have already been experienced by the European Control Station as a result of indiscriminate f.m. transmissions in this section of the band.

For further details of AMSAT activities, send an s.a.e. (essential) to: *Hon Sec, Ron Broadbent G3AAJ, AMSAT-UK, 94 Herongate Road, London E12*, to whom we once again offer our thanks for this information.

GB2MOD Special Event Station

GB2MOD is a special event station associated with the National Mod of Scotland, which is an annual festival to encourage the study and practice of national songs, poetry and the Gaelic language. Also events being contested will include folk groups, drama, choral, fiddling, violin, accordion, piano, clar-sach, piping and shinty—a ball game not unlike hockey.

This year, the Mod will be held at Motherwell, situated in the Clyde Valley area of Central Scotland, between the 8 and 14 October 1983.

The special event station, GB2MOD, will be operational from Motherwell, as and when propagation allows, on the following frequencies: c.w.—

28.07MHz (s.s.b.—28.51MHz), 21.07MHz, (21.31MHz), 14.07MHz (14.21MHz), 7.02MHz (7.06MHz), 3.57MHz (3.67MHz) and 144.07MHz (144.33MHz).

A special event QSL card in both the English and Gaelic languages, financed by Motherwell District Council, will be available for all contacts via the Bureau or direct on receipt of the appropriate IRC's and an sae.

Further details from: *GM3PXX, Mid Lanark Amateur Radio Society, Wrangholm Hall, New Stevenson, Motherwell, Scotland.*

New Catalogues

Toolrange Ltd., the Reading based company who specialise in the supply of purpose-made toolkits and tools for industry, announced recently that their latest full colour 176-page catalogue is now available.

The 1983/84 catalogue continues to be one of the most successful mail order catalogues in Europe, containing over 3000 quality lines, with a special emphasis being placed on tools and production aids for the electrical and electronics industry.

The new Toolrange catalogue can be obtained free by contacting: *Toolrange*

Ltd., Upton Road, Reading RG3 4JA, Berkshire. Tel: (0734) 22245.

The *Ambit Concise Catalogue*, Number six is now available.


With over 100,000 copies of the complete "parts and prices" catalogue in annual circulation, this Summer '83 edition is published in two formats; one for *Ambit's* rapidly developing industrial marketing activities—available free on request to all bona-fide industrial, commercial and educational establishments; and a consumer/enthusiast edition, currently on sale at most newsagents throughout the UK—or direct from *Ambit*—priced at 80p. As usual the new issue features many new lines and price reductions, superceding all previous issues.

Ambit International, 200 North Service Road, Brentwood, Essex CM14 4SG. Tel: (0277) 230909.

Electronic Brokers have produced a new full colour catalogue of their new test and measurement equipment from Philips, Fluke, Hameg and ICE.

Being the official distributors, these products are available on fast delivery from stock at prices that will be hard to beat anywhere else in the market.

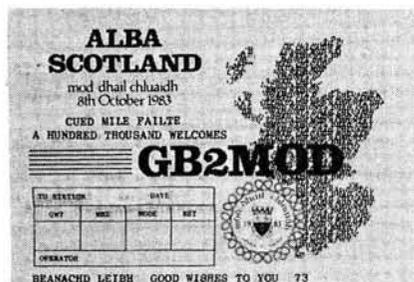The catalogue is available free, from: *Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-833 1166.*



The Special Event QSL Card

Practical Wireless, October 1983

Repeater News

Final proposals for v.h.f. Phase 6 and u.h.f. Phase 7 repeaters were sent to the Home Office on 28 June 1983, they include:

Phase 6 (v.h.f.): GB3BB—Brecon on R4, GB3BI—Inverness on R5, GB3LU—Lerwick on R3, GB3OC—Orkney on R2 and GB3PA—Paisley on R1.

Phase 7 (u.h.f.): GB3AH—Swaffham (Norfolk) on RB13, GB3BE—Bury St. Edmunds on RB6, GB3CA—Carlisle on RB13, GB3CY—York on RB13, GB3DS—Worksop on RB13, GB3GD—Leicester (RTTY/Data) on RB12, GB3GU—Guernsey on RB13, GB3HK—Hawick (Roxburgh) on RB14, GB3KB—Biggin Hill on RB0, GB3KR—Kidderminster on RB4, GB3LA—Leeds (City) on RB11, GB3OM—Omagh on RB15, GB3PP—Preston (Lancs.) on RB15, GB3SZ—Bournemouth on RB15, GB3WI—Wisbech (Cams.) on RB15 and GB3YS—Yeovil on RB2.

These proposals, judging by past experience, should be processed by the Home Office within six months. However, the site vetting procedure is far more complex these days and involves consultation with approximately 40 departmental committees/outside authorities such as the Ordnance Survey Office and the IBA.

QRM: The v.h.f. repeater GB3YJ (R7)

at Leamington Spa has encountered problems recently from a newly installed public service transmitter which has been co-sited and transmits within 600kHz of the band. Removal of this interference will involve extensive filtering and it is believed that an application for a site change is in the pipeline.

Repeater Working Group: Since the committee structure revisions brought about by the RSGB forward planning group, the RWG (like all other RSGB committees) has had to provide a list of tasks to be undertaken during the forthcoming year (July 1983 to June 1984). These are summarised as follows:

1. To agree with the DTI new terms of reference for licensing v.h.f./u.h.f. repeaters, and to apply for approximately 10 v.h.f. and 20 u.h.f. licences.
2. To work towards a reduction in the amount of time taken by operating groups in putting installations on the air after a licence has been issued.
3. To devise specifications and bandplans for RTTY/Data repeaters.
4. To produce publishable service area maps of v.h.f./u.h.f. repeater networks.
5. To produce a number of technical advice pamphlets for use by Repeater Groups.
6. To discuss with the h.f. committee the practicalities of an experiment in the operation of 29MHz repeaters. The

h.f. committee is currently in dialogue with the RWG on this.

7. To seek DTI permission for the addition of 10GHz inputs to 433MHz repeaters.

8. To obtain a licence for an experimental unit to provide more data about the use of pilot s.s.b. (GB3SF) as a mode for v.h.f. mobile stations.

On Air: The following repeaters have recently become operational:

GB3HB—St. Austell on RB15, GB3PW—Powis on R3, GB3VS—Bridgwater on RB13, GB3MM—Midlands (1.3GHz) and GB3AA—Alveston (1.3GHz).

Back on Air: The following repeaters have returned to operational status: GB3BN—Bracknell, GB3LW—London, GB3CK—Charring and GB3HC—Hereford.

Late News: The RWG are to hold an Open Meeting at the ORM on October 15 at Inverness. Members of the RWG are always available to give lectures to affiliated RSGB Groups. Details from RSGB HQ.

Proposals for the Luton and Dunstable area and Wakefield unfortunately could not be submitted in v.h.f. Phase 6 as they are still negotiating channels and siting.

The 1.3GHz group at Brentwood GB3BW returned their licence and an application has been made to transfer the unit to the Bedford area.

The International VHF FM Guide

As a (valuable) source of information on f.m. repeater and simplex operations on 144MHz and above throughout the world, the 1983 edition (6th) of the *International VHF FM Guide* is probably the most comprehensive publication of its type available.

Containing over 128 pages of data (UK version) covering topics such as reciprocal licensing arrangements, preferred operating frequencies/channels, repeater and beacon locations plus technical facts are all available; the book also includes a detailed description with service area maps of all UK 144MHz repeater installations.

Regarding data on foreign countries, did you know that Mexico has 35 repeaters, several of which are located at over 4000m a.s.l.?—it's all here.

The guide is available from most radio dealers or direct from the producers Julian Baldwin G3UHK and Kris Partridge G8AUU at: 41 Castle Drive, Maidenhead, Berks. SL6 6DB.

The book costs £2.00 from dealers

or £2.30 by post to UK addresses, or £2.35 to Europe and £3.50 overseas by air. An overseas edition which does not include the extensive UK data costs £1.50 to Europe by surface mail and £2.10 overseas by air.

Microwave Society

A recent request made to our Editor for permission to reproduce items from the *PW Exe* microwave transceiver project, has resulted in us receiving details of a recently formed group of microwave enthusiasts calling themselves The Microwave Society.

The society has been formed to encourage microwave activity by providing practical advice and information. During winter months informal meetings are held, at various venues, to provide an opportunity for social contact and technical discussion. Also the society produce their own newsletter, entitled *Waveguide* together with a comprehensive information pack that comes with membership—this contains several practical constructional

details of 10GHz wideband f.m. system components.

Further details and applications for membership can be obtained by contacting: *Glen Ross G8MWR, 81 Ringwood Highway, Coventry. Tel: (0203) 616941.*

Beacon Callsign Change

The Sydney, Australia 10 metre beacon on 28.262MHz, formerly VK2WI, has changed callsign to VK2RSY.

The beacon operates from the Wireless Institute of Australia NSW Division's transmitting station at Dural, which is 25km northwest of Sydney and runs 25W output power to a vertical half-wave antenna.

Reception reports would be most welcome and should be sent via the Bureau, to the *Wireless Institute of Australia, New South Wales Division, PO Box 1066, Parramatta, NSW 2150*, or direct to Jeff Pages, VK2BYY, the officer at Dural, who notified us of the change.

Practical Wireless, October 1983

It's an ill wind that . . .

The following item is extracted from an article entitled *VHF Propagation Report*, by Jim Stewart WA4MVI, published in the April 1983 issue of *The Lunar Letter Magazine*.

With the sporadic-E season under way, WA4MVI presented his thoughts on this DX propagation mechanism. Jim worked next door to the US Weather Service for several years and was able to obtain weather data covering large areas of the US, which allowed him to make a rapid comparison between weather patterns and "lift" conditions.

Jim's "best guess" at the mechanisms at work with Sp-E is that "wind shears", abrupt changes in direction and velocity of adjacent masses of "air", result in tremendous charged ion clouds being formed, static electric principle, if you wish, and these clouds act as a near perfect mirror to radio energy. Winter Sp-Es are most likely a result of horizontal shears as various masses pass each other, sometimes at high velocities such as with Jetstreams.

The summer Sp-E season seems to come and go with the thunderstorm season each year. This type of ionisation appears to result from vertical shears as are associated with severe

thunderstorms. Severe thunderstorms are those which penetrate the "tropopause", the region of the atmosphere where air temperatures begin to warm again with increasing height, and produce tornado and hail potential. They can occur as isolated airmass types or be associated with a weather front. It is very likely that a severe thunderstorm area which has grown to between 18.2km and 21.3km will have a 144MHz opening as a result!

The common opening usually shows that a superstorm was near the path midpoint and in a few rare cases, at one end of the opening, with the storm in the immediate area of one end of the path.—This summer, after you're sure lightning danger has passed, fire up on the bands and watch for this rare event.

In general, watch for a severe storm warning area about 800 to 1200km from you, and if your source has "tops" info on altitude of the area 17km is a good average altitude associated with 50MHz and anything above 20km may correlate with a 144MHz opening. The actual cloud or reflecting medium is much higher and may move in some direction other than the storm area.

Any feedback on this to Ron Ham please.

Morse Courses

Readers who intend taking the Post Office Morse Test will be interested to know that classes are available at the following locations:

Beckenham—Beginners Class commencing 20 September between 7.15 and 9.15pm at *Beckenham Adult Education Centre, 244 Croydon Road, Beckenham, Kent. Tel: 01-650 4208.* The Class Tutor will be Mr. Henschel.

An Intermediate Morse Class commencing 20 September between 7.30 and 9.30pm at *Beckenham Adult Education Centre, 28 Beckenham Road, Beckenham, Kent. Tel: 01-650 4208 and 01-650 1383.* The Class Tutors will be Steve Palmer and Peter Grant.

Dudley—*Dudley College of Technology, The Broadway, Dudley, West Midlands*, starting in September and the Class Tutor will be David A. Cherrington G4FIF. Interested parties should contact the college.

Grantham—*St. Hugh's CE Comprehensive School, The Avenue, Dysart Road, Grantham NG31 7PX. Tel: (0476) 4815*, commencing 12 September between 6.30 and 8.00—enrol at the class. Full details from the school or the *College for Further Education, Stonebridge Road, Grantham. Tel: (0476) 3141.*

New Low-cost Slow-scan TV System

A slow-scan TV system, currently undergoing field tests in prototype, will bring slow-scan TV within easy reach of the average amateur pocket.

Designed and built by Davtrend Ltd., it will be introduced in late summer with the launch of the Model SST-1000 Slow-scan Receiver, which will be offered at a highly competitive price of less than £200.

New Electronics Club

I have received notification that a new electronics club which intends to have nationwide appeal has been formed.

The "National Electronics Correspondence Club" has been organised, in the words of their secretary, E. Foley: "Primarily to be of use to the hobbyist in remote areas who may be unable to use local facilities where they exist (especially the disabled hobbyist), by providing a communications link between those sharing similar interests within the hobby."

"Members will receive a bi-monthly newsletter containing hints and tips on project construction, topical features,

Practical Wireless, October 1983

The receiver will have facilities for accommodating a transmitter p.c.b. that will upgrade the equipment for two-way communications. This p.c.b. will be introduced at a later date to coincide with the launch of the full transceiver system, designated as the SST-2000 Slow-scan Transceiver.

System specifications will be standard; that is, 128 by 128 discrete picture elements, each encoded into 16 grey shades to produce one picture every 8.5 seconds.

points of view, circuit ideas and members' advertisements, plus special offers on components, tools etc., and each member will be at liberty to correspond with the club and other members for help and advice on aspects of electronics."

Membership is £4.50 per annum, which includes the newsletter, administration and postage costs.

Interested parties should write enclosing 25p for full details and membership application (refundable on membership) to: *Mr E. Foley (Secretary), 95 Albert Road, Levenshulme, Manchester M19 2FU. Tel: 061-225 7684.*

Davtrend Ltd., who have recently moved premises from Portsmouth to Gosport, also manufacture and design a comprehensive range of power supplies and converters.

Davtrend Ltd., Sanderson Centre, Lees Lane, Gosport, Hants. PO12 3UL. Tel: (070 17) 20141.

JOTA

The special event station GB2ST will be operated on behalf of the Scouts of Tomintoul, during "Jamboree on the Air" on 15 and 16 October.

Operation will be on all bands between 1.8 and 28MHz throughout the weekend and contacts will be attempted with Scout stations worldwide. A special QSL card is to be produced and all contacts will be confirmed.

Tomintoul is the highest village in the Highlands of Scotland and is best known for its links with tourism and the Glenlivet whisky industry.

For further details or to arrange skeds, contact: *Barry Horning GM4TOE, Old Schoolhouse, Tomachlaggan, Kirkmichael, Tomintoul, Banffshire. Tel: (080 74) 376.*

Swap Spot

Have Canon FD 300mm telephoto lens. Excellent condition. Would exchange for good quality h.f. station accessories e.g. a.t.u./power/s.w.r. meter. Tel: Rod, 0745 560212 (GW4SLK) evenings and weekends only (Mostyn, Clwyd). **S983**

Have radio telephone GR497 TX, 24 channels TT21 valves, marine band RX, solid state, s.s.b., power unit, Xtal controlled. Details on request. Would exchange for 144MHz TX/RX or scanning RX. E. Allison, 138 George Street, Mablethorpe. Tel: 7805. **S991**

Have 48K Spectrum, recorder and software. R107 s.w. receiver in good condition, Hitachi stereo cassette deck, Rotel stereo amp. Would exchange for Yaesu h.f. transceiver. S. Barron, 276 Shelley Road, Wellingborough, Northants NN8 3EE. **T005**

Have FT208R plus cash adjustment. Would exchange for Ten-Tec Argonauts 515. Also have IC2E. Would exchange for Datong FL3. S. Keen, 30 Bath Road, Chiswick, London. Tel: 01-995 7339. **T021**

Have SEM 144MHz transmatch, SEM 144MHz pre-amp unused, fit inside rig. Also SEM 3-way antenna switch, good to 144MHz. All mint condition. Would exchange for audio notch filter or active RX antenna, w.h.y. G6RBY. Tel: 01-446 4932. **T025**

Have Sharp MZ80K computer, boxed and in mint condition, including three languages. Would exchange for best h.f. transceiver offered, or w.h.y. Roy Greenwood G6OVE. Tel: 0274 673829 (Bradford, W. Yorks). **T40**

Have Cinerex zoom Super 8 cine outfit, dual gauge projector, zoom camera with auto exposure. All in good condition. Would exchange for rotator and control for Mini Beam. Tel: 01-672 1833 (Tooting). **T41**

Have Harrier CB, matching p.s.u., magmount antenna, s.w.r. meter, a.t.u., all leads, microphone and base antenna. Would exchange for 144MHz receiver, s.w.l. a.t.u., broadband pre-amp., multimeter or w.h.y. Base antenna to be dismantled and collected. Prew, 25 Springfield Road, Stirling. Tel: 62290. **T42**

Have No 19 set, ex-army v.h.f., h.f. transceiver with power supply and a.t.u.—needs cleaning up. Would exchange for anything useful in electronics or radio. Tel: Landrake 540 (Cornwall). **T63**

Have a wide range of *English Free Radio* magazines dating back to '72—*Wavelength*, *Script*, *Radio Guide*, *Monitor*. Would exchange for UK/American fiction and non-fiction paperbacks. Van Landschoot Hendrick, Rapenbrug 10, B9990 Maldegem, Belgium. **T68**

Have Walther .177 Universal match air rifle, including case etc. Cost over £300, used three times—top grade gun. Would exchange for receiver or any amateur radio gear. John Neno. Tel: Cheltenham 28942. **T69**

Have Yaesu FT-227R, 1-10W 144MHz f.m. transceiver, value £100. Would exchange for colour TV, 35mm camera or good ladies cycle, or w.h.y. Tel: Coventry 504982. **T78**

Have Hitachi hi-fi stack system, CrO₂/metal compatible tape deck with a.p.s.s., 3-waveband digital tuner, 50W amplifier, matching 2-way speakers and headphones. As new and boxed. Would exchange for FT-480R and p.s.u. Tel: Southampton 814333 (ask for Andy King). **T79**

Have Trio TR7010 s.s.b. transceiver, good condition. Also have mic, packing and leads—value £100. Would exchange for f.m. handheld, Sony 2001 receiver, 12VQRO2MPA or faulty FT-290 or w.h.y. Jim Morris G8NHC, "Kirkham", Sea Road, Winchelsea, East Sussex. **T80**

Have Midland 3001 CB radio and Harrier CBX CB radio, both with fitting kits and 2 x 3A p.s.u.s for both. Would exchange for Yaesu FRG-7 communications receiver. Tel: Bracknell 52601. **T112**

Have Kenwood remote v.f.o., model v.f.o. 180. New and unused. Would exchange for rotator, 144MHz beam, linear—all answered. 91 Sydney Street, West Belfast BT13 3GA. Tel: 757733. **T113**

Have three 16mm Bell and Howell sound projectors plus 3 speakers and 3 transformers and spools. One projector needs very slight attention, other good. Would exchange the lot for SX200N scanner or good 144MHz rig. Steele, Mayberry, Chilbolton, Stockbridge, Hants. **T127**

Have muTek 144MHz mobile halo, as new with mountings, cost approximately £36. Would exchange for Discone antennas, approximately 55-475MHz, or 2C39 valves, coaxial relays for 1296MHz, waveguide 16 and flanges, w.h.y. Tel: Dave G8PQG Oxford 67165. **T134**

Have new and boxed Audioline 341 legal CB (unwanted gift). Would exchange for Katsumi MC902 speech processor. Tel: Wilmslow 527250 (1630-2130). **T143**

Have antique wireless in mint condition, known as "the Peoples Set". Would exchange for HW8 QRP or 144MHz, w.h.y. Write or call E. O'Reilly, 66 Sandown Park, Ballymena, Co. Antrim BT43 6LE. All letters answered—s.a.e. please. **T144**

Have ZX81 plus 16K RAM (both under guarantee) plus software. Would exchange one or more items for good airband monitor. P. Mann, 21 Northgate, Oakham, Leics LE15 6QR. Tel: 0572 3943 (day) or 812834 (evening). **T145**

Have 16K ZX81. Would exchange for 144MHz s.s.b./c.w. transceiver or 144MHz f.m. synthesised plus cash. G. Helks G6TTC. Tel: 0924 271044 (Ossett, W. Yorks). **T152**

Have a battery pocket TV; Avo 7 test meter; 'scope working but needs repair; Ekco console a.c. radio, motor driven tuning, very old, working order. Would exchange for video recorder. Thorley, 60 Ballinson Road, Blurton, Stoke-on-Trent. Tel: 328167. **T159**

Have ZX81 plus 16K RAM and cassette recorder, p.s.u. etc. Also Maxcom f.m. CB radio, p.s.u., Thunderpole II antenna. Would exchange for a good communications receiver—Yaesu FRG-7 etc., or a small 144MHz transceiver. Tel: 0926 55391 ask for Mark (Kenilworth). **T173**

Have 147 l.p.s.—wide choice. Would exchange for receiver to cover amateur bands or transceiver with good receiver stage, f.m. CB transceiver, ZX81 plus 16K or w.h.y. J. Mackenzie, 9 Lammarview, Chirnside, Duns, Berwickshire, TD11 3UN. **T185**

PW "SWAP SPOT"

Got a camera, want a receiver? Got a v.h.f. rig, want some h.f. gear to go with your new G4? In fact, have you got anything to trade radio-wise?

If so, why not advertise it FREE in our new feature SWAP SPOT. Send details, including what equipment you're looking for, to "SWAP SPOT", *Practical Wireless*, Westover House, West Quay Road, Poole, Dorset BH15 1JG, for inclusion in the first available issue of the magazine.

A FEW SIMPLE RULES: Your ad. should follow the format of those appearing above; it must be typed or written in block letters; it must be not more than 40 words long including name and address/telephone number. Swaps only—no items for sale—and one of the items MUST be radio related. Adverts for ILLEGAL CB equipment will not be accepted.

TRIO TS-430S



£736
inc. VAT

COLLINS KWM-380 Amateur Bands



Transceiver 1.8-30MHz
Receiver 1.8-30MHz
£2199

DRAKE TR7A £1099.95



The most famous of the
General Coverage Transceivers

**NEW
LOW
PRICE**

DRAKE TR5



DRAKE's low cost Transceiver
£552.00

**CAN YOU
BEAT THIS
FOR VALUE?**


BEARCAT SCANNERS



BC-100FB **£345.00**
Hand held 16 channel
programmable

NEW!

BC-20/20FB

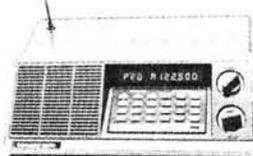

40 Channels
AM/FM
£258.75

BC-200FB 10 channel **£184.95**
BC-150 16 channel **£144.90**

**DON'T
MISS THIS
CHANCE!**


DRAKE R7A




General Coverage Receiver
£1069.50

BENCHER PADDLES

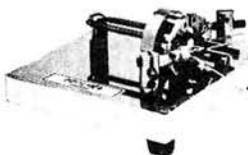BY-1 Black Base **£37.95**
BY-2 Chrome Base **£48.30**
BY-3 Gold plated **£92.00**
ZA-1A Balun **£15.00**
ZA-2A Balun **£17.25**
ZY-2 CW Audio Filter **£57.50**



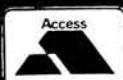TRIO - YAESU - ICOM
FDK - KDK - DATONG - HUSTLER
SHURE - ASTATIC - Hy-GAIN
TELEX - MICROWAVE MODULES
HAL - DAVTREND - AVANTI and
EVERYTHING ELSE IN AMATEUR RADIO




RADIO SHACK LTD

(Just around the corner from West Hampstead Station on the Jubilee Line)

Giro Account No. 588 7151 Telephone 01-624 7174 Telex: 23718

188 BROADHURST GARDENS,
LONDON NW6 3AY



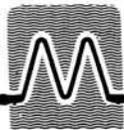

MICROWAVE MODULES LTD

MML144/30-LS £69.95 (P&P £2.50)
MML144/100-LS £159.95 (P&P £3)

These products have been specifically designed for the many low power multimode 2 metre transceivers, and have a switchable input for either 1 or 3 watt levels.


The MML144/30-LS provides 30 watts RF output power, whilst the MML144/100-LS will provide 100 watts. Both units require 13.8V DC and include an ultra low-noise receive preamp (3SK88), which can be controlled from the front panel.

An RF vox circuit is incorporated with switched delay times, suitable for FM or SSB, thus making the unit simple to operate.

When the DC supply voltage is removed, a straight through path is made so that the transceiver can be used barefoot, without disconnecting any leads.



MML144/30-LS

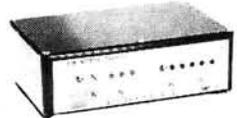

MMS 1



MMT432/144-R

MML432/50 £109.95 (P&P £3)
MML432/100 £228.65 (P&P £4)

These amplifiers are compatible with any 10 watt 70 cm multimode equipment, and can be supplied for ATV use at no extra charge.

The MML432/50 provides 50 watts RF output power whilst the MML432/100 will provide 100 watts.

Both units require a 13.8v DC supply and include an RF vox circuit, thus making operation simple. (The MML432/50 also includes a low-noise receive preamplifier).

Current drain is 8 amps for the 50 watt version and 18 amps for the 100 watt.

MMS1 £115 (P&P £2.50)

MMS1 - The Morsetalker An ideal morse tutor, which sends random morse code in the range 2-20 w.p.m., and provides speech talkback of the morse so that the pupil may check his/her ability.

Letters and numbers can be selected and the alphabet is formatted in 4 sections to aid learning. Group lengths of 1, 5 and 50 characters can be selected, and the facility to send continuous morse without speech talkback is included.

A 12 volt DC supply is all that is needed and the unit can be used in a vehicle from the standard battery.

MMS2 £169 (P&P £2.50)

MMS2 - Advanced Morse Space Trainer This unit is based on the MMS1, and boasts the same basic features, with the following additions:—

1. The pupil may key in his/her own morse code. In this way, sending proficiency can be perfected.
2. An uprated speed range: 6-32 w.p.m.

MMT432/28-S £159.95 (P&P £2.50)

MMT432/28-S This transverter provides coverage of 432-436 MHz in two ranges, switch selectable, and is compatible with any 10 metre transceiver having a low-level output. (5-500mW).

The unit produces an output power of 10 watts and incorporates a low-noise receive converter, which together provide high performance in all respects.

MMT432/144-R £184 (P&P £2.50)

MMT432/144-R Similar to the unit above, this transverter is compatible with 2 metre multimode transceivers, and incorporates a repeater shift of 1.6 MHz.

An attenuator is supplied to allow use with transceivers having an output power of 10 watts nominal. (An alternative attenuator allowing other levels is available to order).

MOVE UP TO THE PEACE AND QUIET ON 70 cm!

Goods normally despatched within 10 days



MICROWAVE MODULES
 BROOKFIELD DRIVE, AINTREE, LIVERPOOL L9 7AN, ENGLAND
 Telephone: 051-523 4011 Telex: 628608 MICRO G
 CALLERS ARE WELCOME, PLEASE TELEPHONE FIRST

HOURS:
 MONDAY TO FRIDAY
 9-12.30, 1-5.00

OUR ENTIRE RANGE OF PRODUCTS WILL BE EXHIBITED AND ON SALE AT MOST OF THE 1983 MOBILE RALLIES BY OUR SALES TEAM. SEE YOU THERE.

MASTER ELECTRONICS NOW!

The PRACTICAL way!

YOUR CAREER...YOUR FUTURE...YOUR OWN BUSINESS...YOUR HOBBY
THIS IS THE AGE — OF ELECTRONICS!
 the world's fastest growth industry...

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.



CACC

British National Radio & Electronics School Reading, Berks, RG1 1BR.

VALVES

A1065	1.40	1A3	0.85	6AV6	0.85	6LD20	0.70	19AC5	0.85
A2293	8.80	1L4	0.50	6AX4GT	1.30	6K66A	2.70	19G3	11.50
QOV03-25A		1R5	0.60	6AX5GT	1.30	6O7G	1.30	19G6	8.50
	36.50	1S4	0.45	6BE6	0.65	6SA7	1.00	19H5	39.55
QOV06/40A		1S5	0.45	6BG6G	1.60	6SG7	1.15	20D1	0.80
	16.10	1T4	0.45	6BJ6	1.30	6SJ7	1.05	20F2	0.85
QV03-12	4.20	1U4	0.80	6BD7A	0.85	6SK7	0.95	20E1	1.30
SP61	1.80	1X2B	1.40	6BR7	4.80	6SN7GT	0.80	20P1	0.65
TT21	23.00	2021	1.10	6BW6	6.20	6SR7	1.10	20P4	1.25
TT22	18.50		1.85*	6BW7	1.80	6S07	0.95	20P5	1.35
U25	1.15	2K25	16.95	6C4	0.50	6V6G	1.50	25L6GT	0.95
U26	1.15		24.50*	6C6	0.55	6V6GT	0.95	25Z4G	0.75
U27	1.15	2X2	1.15	6CH6	8.20	6X4	0.95	30C15	0.50
U191	0.85	3A4	0.70	6CL6	2.75	6X4WA	2.10	30C17	0.50
U281	0.70	3AT2	2.40	6CW4	8.50	6X5GT	0.65	30C18	2.45
U301	0.65	3D6	0.50	6CX8	3.80	6Y6G	0.90	30F5	1.15
U600	11.50	3D22	23.00	6D6	0.70	6Z4	0.70	30FL2	1.40
U801	0.90	3E29	19.00	6F6	1.60	7B7	1.75	30FL12	1.25
UBC41	1.20	3S4	0.60	6F6GB	1.10	8B8N8	2.95	30FL14	2.15
UABC80	0.75	4B32	18.25	6F7	2.80	9D2	0.70	30L15	1.10
UAF42	1.20	5B/254M	16.90	6CY5	1.15	9D6	2.90	30L17	1.15
UBF80	0.70	5B/255M	14.50	6F8G	0.85	10C2	0.85	30P12	1.15
UBF89	0.70	5B/258M	12.50	6F12	1.50	10F18	0.70	30P13	1.50
UCB84	0.85	5C22	29.90	6F14	1.15	10P13	1.50	30PL14	2.45
UCB85	0.70	5R4GY	1.20	6F15	1.30	11E2	19.50	35L6GT	1.40
UCF80	1.30	5U4G	0.75	6F17	3.20	12A6	0.70	35W4	0.80
UCH42	1.65	5V4G	0.75	6F23	0.75	12AT6	0.70	35Z4GT	0.80
UCH81	0.75	5Y3GT	0.95	6F24	1.75	12AT7	0.65	50C5	1.15
UCL82	0.95	5Z3	1.50	6F33	10.50	12AU7	0.60	50C6BG	1.35
UF41	1.35	5Z4G	0.75	6FH8	4.20	12AV6	0.95	75B1	1.25
UF80	0.95	5Z4GT	1.05	6GA8	1.95	12AX7	0.65	75C1	1.70
UF85	0.95	6/30L2	0.90	6GH8A	0.95	12BA6	0.90	76	0.95
UL84	0.95	6AB7	0.70	6H6	1.60	12BE6	1.25	78	0.95
UM80	0.90	6AC7	1.15	6J4	1.35	12BH7	1.95	80	1.70
UM84	0.70	6AG5	0.60	6J4WA	2.00	12BY7A	2.30	85A2	1.40
UY82	0.70	6AH6	1.15	6J5	2.30	12C8	0.65	2.55*	
UB85	0.85	6AK5	0.65	6JS5GT	0.90	12E1	18.95	807	1.25
VR105/30	1.25	6AK8	0.60	6J6	0.65	12J5GT	0.55	813	1.90*
VR150/30	1.35	6AL5	0.60	6J6W	0.90	12KGT	0.70	813	19.32
X66	0.95	6AL5W	0.85	6J8C	2.95	12K8GT	0.80	88.50*	
X61M	1.70	6AM5	4.20	6J8CC	2.95	12Q7GT	0.60	829B	14.00
XR1-6400A		6AM6	1.50	6JL6	5.85	12SC7	0.65	832A	8.90
	125.00	6ANBA	2.50	6K7	0.80	12SH7	0.65	866A	3.80
Z759	19.00	6AQ4	3.40	6KD6	4.50	12SJ7	0.70	866E	6.25
Z800U	3.45	6AQ5	1.80	6L6M	2.80	12SQ7	1.45	931A	13.80
Z801U	3.75	6AS6	1.15	6L6G	2.50	12SQ7GT	0.85	954	0.60
Z803U	16.00	6AT6	0.90	6L6GC	2.65	12Y4	0.70	955	1.20
Z900T	2.45	6AUG	0.60	6L6GT	1.25	13B3	0.70	956	0.60
				6L7G	0.65	13D5	0.90	957	1.05
				6L8	0.70	13D6	0.80	1625	1.80
				6LQ6	2.95	1457	1.15	1629	1.85

VALVES and transistors

Telephone enquiries for valves, transistors, etc. retail 749 3934, trade and export 743 0899.

*SPECIAL QUALITY
 £15 75p, £15 £20 90p, over £20 free

PRICES MAY VARY Delivery by return of post.

COLOMOR 907/3530 London

(ELECTRONICS) LTD.
 170 Goldhawk Rd., London W.12

Tel. 01-749 3934

Open Monday to Friday 9-1 pm, 2.00-5.30 pm.

STANDARD C7900/8900 UHF/VHF Transceivers

During the last two months I have been evaluating Standard's *ultra-slim* f.m. 10W u.h.f. and v.h.f. mobile transceivers. With the C7900 (432MHz band) and the C8900 (144MHz band) describing the operation and performance of one rig is very much like describing that of the other. There are few apparent operating variations between the two rigs and these are to accommodate the various anomalies of semi-duplex repeater operation.

Probably the first thing that you notice about these rigs is their size, or rather the lack of it, just 31 x 138 x 178mm each. This means that even when the two rigs are mounted together in the mobile bracket they don't take up much more room than your average single-band mobile rig—they also only weigh just over 1kg each. Each rig is supplied with a mobile bracket, and the two can be bolted together.


Receiver performance of both rigs has certainly not been sacrificed as a result of their size. In sensitivity terms they were more than capable of supporting the available output power, and probably would still have a generous balance in favour of receive capability with a good bit more power.

The rigs were easy to operate mobile, with very positive action on the main tuning control. The vertical slide switch for repeater shift/simplex operation also proved much better than was anticipated at first glance. I had visions of moving the main tuning switch every time I tried moving from repeater shift to simplex. This didn't prove to be the case, the switch can be moved into the required position easily—usually using the thumb—as the switch has a positive "click-stop".

The front panel has sufficient controls without falling into the trap of becoming over cluttered with semi-essential appendages.

It was nice to have both bands as this provided the opportunity to work full duplex between 144MHz and 432MHz. During the review period a dual-band antenna and diplexer were used with success and full duplex operation was achieved—even whilst mobile on several occasions.

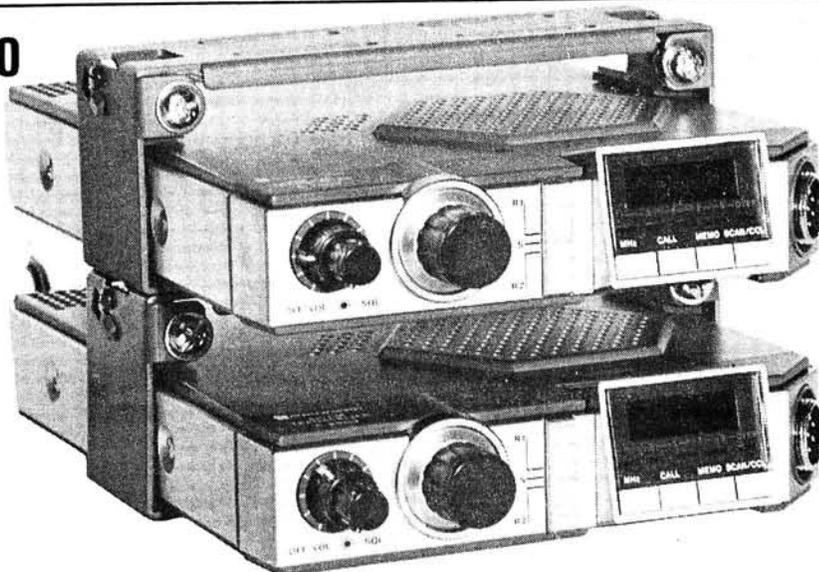The only "grouse" about the operation was that as you change the fre-



quency using the UP/DOWN button on the mic or one of the function buttons is pressed the rigs "bleep" to indicate the operation. Personally I would like to have the facility to disable this feature as and when required!

Repeater Operation

When using the repeater shift this is where the rigs really differ. On 144MHz you have to put the repeater input on to the main display, then switch from simplex operation to the R1 position on the vertical slide switch. This did take some getting used to but using the memories did help; I stored the local repeater input frequencies in the memories. Listening on the input is easy, all you have to do is switch from the R1 position back to the S position (centre "click" position).

For 432MHz you must remember to put the repeater shift (1-600) in memory shift, otherwise even if you move the repeater switch the transmit frequency stays the same. To listen on the input you have to move from the R2 position to the R1 position, again nice and quick.

Pressing the p.t.t. twice in close succession provides a 1750Hz tone burst for repeater operation in addition to the front panel CALL button facility.

Other Facilities

The memories are simple to program as long as you read the instructions in the handbook carefully. That way you understand what the various lights mean as they start or stop "blinking".

There are three different scanning routines available. You can scan the

whole of the band, 1MHz of the band or between the frequencies stored in Memories 4 and 5. Unfortunately you can't scan the five memories in turn—but you can't have everything I suppose. There is no memory back-up when the supplies are removed.

The main frequency display can be tilted upwards through an angle of 15 degrees, which is useful when the rigs are mounted horizontally. In bright sunlight the red l.e.d. displays did prove difficult to read, but this can be overcome if you mount them in sufficient shadow in the car.

The power leads have interesting connectors on them, the positive and negative leads are protected from one another by a plastics sleeve on the positive lead coming from the battery. This should ensure that the rig is not connected up with the power leads the wrong way round.

All stations contacted gave good audio reports: "natural sounding" was the most common remark—which makes a pleasant change. The audio from the speakers was also good, but external speakers were much better under mobile conditions. The internal speakers are only 65mm diameter and are situated on the top of the unit, thus when they are stacked together the lower rig has its speaker partially covered.

Price

The C7900 costs £239 and the C8900 costs £219, both prices include VAT. The rigs are available from **Lee Electronics Ltd., 400 Edgware Road, London W2. Tel: 01-723 5521** to whom we offer our thanks for the loan of the review models.

Elaine Howard

AIR TEST

USER REPORTS ON SETS AND SUNDRIES

ICOM IC-505 50MHz Transceiver



There seems to be a general feeling among the amateur fraternity not licensed for 50MHz that this band is the "Mecca" of all amateur bands. This is far from true as the propagation conditions since permits were issued have not been predictable and few "openings" by "sporadic E" or tropospheric ducting have occurred during the limited operating hours from 2330 to 0830 clock times. Some weak aurora has been observed but did not produce any contacts from this location. However, the Gibraltar v.h.f. beacon on 50.035MHz has been heard at very good strength in the afternoon from about 1300-1800 hrs.

Location

Tests were conducted from Bransgore, 10km south east of Ringwood, South West Hampshire, QTH Locator ZK23g. Bransgore is situated between the Avon Valley and the edge of the New Forest. My location is 22.5m a.s.l. and badly screened to the North East, East and South East by the New Forest. It is below cliff level along most of the coastline, the cliffs being on an average 30m a.s.l. It is without doubt a very poor v.h.f. location.

Antennas Used

A 3-element Yagi was used for about half the period of the trials at 7m, then followed by a 5-element Tonna at heights from 7 to 10m when a Strumech 9m crank-up mast was installed. The antennas are not ideally situated as there are evergreen trees at least 15m high from South East to South West. The internal vertical telescopic antenna was not used due to lack of strong enough signals. (Normal polarisation of antennas on 50MHz is horizontal.)

Transmission Modes Used

Mainly c.w., although some s.s.b. was used when signals were strong

enough, unfortunately this did not happen very often! The ratio of c.w. to s.s.b. was approximately 80 percent:20 percent.

Operating Comments

The IC-505 was compared with the main station equipment which consists of a converted Europa, valved transverter and an FTDX-401 transceiver using 28-30MHz as part of the driving source and main receiver. The output on 50MHz from the Europa is approximately 40-50W p.e.p. A separate calibrated standard receiver was also used to compare the sensitivities of both the IC-505 and Europa.

Overall results proved that when conditions were average the IC-505 was about one "S" point (6dB) down on the Europa combination on transmit. On receive there was very little if any difference except that the tuning control of the "505" was better, and, with the two rates of tuning, a delight to handle.

The FINE tuning setting of the "505" was ideal for "winkling out" the very weak c.w. signals which could easily be missed with the faster tuning rate. However, the fast tuning rate made tuning from 50-52MHz much quicker. It is a very good combination. The shaft encoder digital tuning with its "stepped frequency" tuning was a little unusual to start with but was soon adjusted to—mentally! The electronic "dial lock" facility was also very much appreciated. The scanning facility was not used because stations on 50MHz are constantly changing frequency. However, thankfully there are no "channels" on 50MHz—yet! The setting up procedure is not too clear in

the instructions unless the author is a "bit thick"—not having handled any equipment with a scanning facility before!

Other Operating Comments

The noise blanker is only partly effective and certainly not as good and effective as the one on the Trio TR7010 which is occasionally used at this station on 144MHz.

The c.w. sidetone is too loud and the audio gain control has to be adjusted most times when going from receive to transmit. It would be a distinct advantage if the sidetone could be adjusted independently of the receive audio setting by a pre-set internal control. Further, the keying delay time appears to be fixed and requires a minimum speed of about 15 w.p.m. to prevent the receiver coming on between words—good for "break in" but annoying when trying to send c.w. slowly.

The internal speaker is probably adequate if the rig was taken portable, but the author found the use of an external speaker much better.

The IC-505 is not very tolerant of antenna mismatch. It was found that with a v.s.w.r. of about 1.4 to 1 and less than 1.5 to 1 the carrier "broke up" on c.w. and emitted numerous spurious emissions on either side of the chosen frequency. On s.s.b. it produced a very rough "spitchy" transmission! It appears to be that the phase lock loop goes out of lock unless the v.s.w.r. is kept low. The set was operated at all times from a stabilised p.s.u. at 12.8 volts. It was not operated from the internal batteries except for occasional receive sessions.

Comments on Handbook


The handbook on the whole is not too bad. However, it would be a great help in circuit tracing if the location and

functions of the major components were tabulated in SECTION VIII and not just shown as two small annotated photographs.

All the information is available in the circuit diagram and printed circuit layouts but due to their size very time consuming to locate. The function of preset resistors, diodes and transistors is considered to be very helpful. Some are obvious but others leave a lot to the imagination.

Summing Up

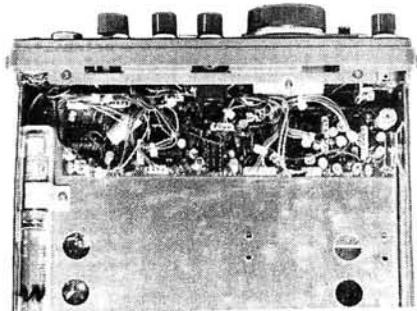Summing up the IC-505 is a very nice piece of equipment which, with the addition of a legal linear amplifier, would make an excellent home station. It is very suitable for portable or mobile operation but as yet, this is not allowed under the terms of the present 50MHz permit. The IC-505 was used for a total number of 60-75hrs, and performed satisfactorily during this time.



An internal view of the IC-505

PW briefly evaluated the IC-505 in their test facility and the table below shows the results obtained.

Transmitter

spurious (worst case)

-63dB at 100MHz

-56dB at 106MHz

output (c.w.)

0.3W — LOW POWER p.a. off (0.54A)

2.4W — HIGH POWER p.a. off (0.87A)

0.8W — LOW POWER p.a. on (1.1A)

8.3W — HIGH POWER p.a. on (2.62A)

Receiver (measured at 51.0MHz)

squelch opens at -104dBm, closes at -112dBm

audio 10% distortion—1.5W output

12dB SINAD—0.36µV e.m.f.

10dB S+N/N—0.27µV e.m.f.

"S" meter

"S"1 = -106dBm

"S"5 = -97dBm

"S"9 = -92dBm

+20dB = -87dBm

+60dB = -53dBm

Stations worked

These were . . .

*G3COJ	High Wycombe, Bucks.
*G3NOX	Saffron Walden, Essex
*G3TCU	Godalming, Surrey
G3LTF	Essex
G4CUT	Cambs.
*G4GLT	Near Leicester
G5KW	Land's End
GW3MHW	Nr Aberyswyth
GW4HXO	St Davids Head
GJ3YHU	Jersey—Channel Islands
GW3HBK	Glamorgan

Most of these stations were worked several times. Those marked * were also worked on s.s.b.

Stations heard

GM3WOJ
GM3WCS
GM4DIJ
GW3LDH
ZB2VHF (ZB2BL)*

With the exception of ZB2VHF all these were heard by meteor scatter and could not be contacted probably due to the low power of the equipment. The station marked * was not "worked" on the home equipment either!

There are only 40 stations licensed to use 50MHz of which the Northern Ireland and Scottish Stations (total 13) are doubtful. Perhaps when conditions improve or we get some aurora or sporadic-E propagation it may be possible to break the "country barrier".

The RSGB Comments

The present usage of 50-52MHz by 40 UK amateurs with special research licences came after many years of negotiation by the RSGB. The work started around 1975 as a preparation for the 1979 World Administrative Radio Conference at which RSGB hoped that it would be possible to achieve some recognition within ITU Region 1 for a 50MHz allocation. At the Conference, a vote to allow administrations to give amateurs access to this part of the spectrum was narrowly defeated by only a few votes. Despite this, RSGB continued to liaise with the UK licensing authority and through them with the BBC and finally achieved agreement for a limited experiment earlier this year (1983). So far the research has gone well and as




anticipated unexpected modes of propagation have shown up. This remains an on-going experiment of the type very suited to radio amateurs. For the future, RSGB is hopeful at some stage of achieving a permanent UK allocation at 50MHz which is a part of the spectrum which naturally gives rise to many most exciting forms of propagation.

Price

The Icom IC-505 costs £299 inc. VAT for c.w. and s.s.b. modes only, the f.m. unit costs £32.50. Other extras are a NiCad battery pack at £49; charger unit at £6.50 and a case at £16.50. The review model was loaned by **Thanet Electronics, 143 Reculver Road, Herne Bay, Kent. Tel: 02273 63859** and I would like to thank them for their co-operation.

W. James G6XM

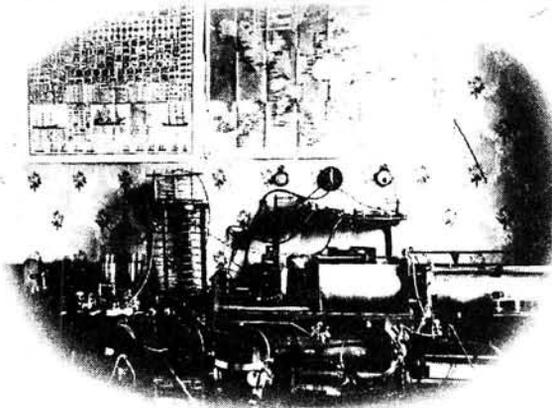**See on the Air—
VHF Bands every
month for the latest
reports on 50MHz
operation**



Amateur Wireless Before 1914

by G. R. Jessop G6JP Part 2

Last month we started to look at some of the pieces of equipment that went to make up amateur wireless stations of the day. This month, we continue to look at some actual amateur wireless experimenters and the equipment they used on the air.

By 14 March 1914 Gamages, who had been in the forefront of supplying components for the wireless experimenters, produced the second edition of their *Directory of Experimental Wireless Stations in the United Kingdom*. This volume showed that some 403 stations had been licensed and a further 365 receiving licences were pending. The map in Fig. 2.1 shows how these were distributed.


It is of interest to note just how widespread amateur wireless activity was in the year before the First World War.


The location of the individual stations, as might be expected, was generally in the areas of industrial activity—although in a few cases they were “out-in-the-country”.

It is also interesting to note that the early operations were on widely different wavelengths, the range of transmission was very limited and the power varied from about 5 watts to 500 watts. The level of power was to some extent dependent on the primary source of power—batteries, mains supply or dynamo. This sort of information is shown in the charts of Fig. 2.2.



Fig. 2.1: Distribution of experimental transmitting stations at the end of 1913

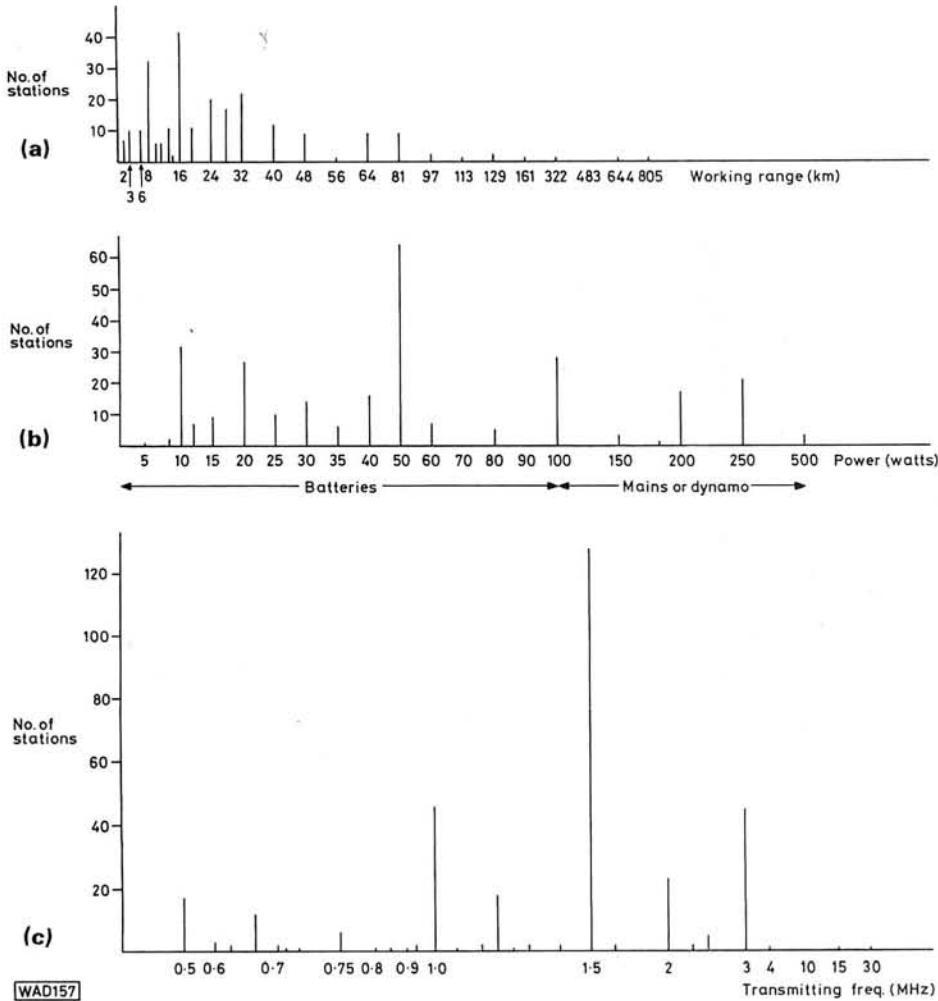

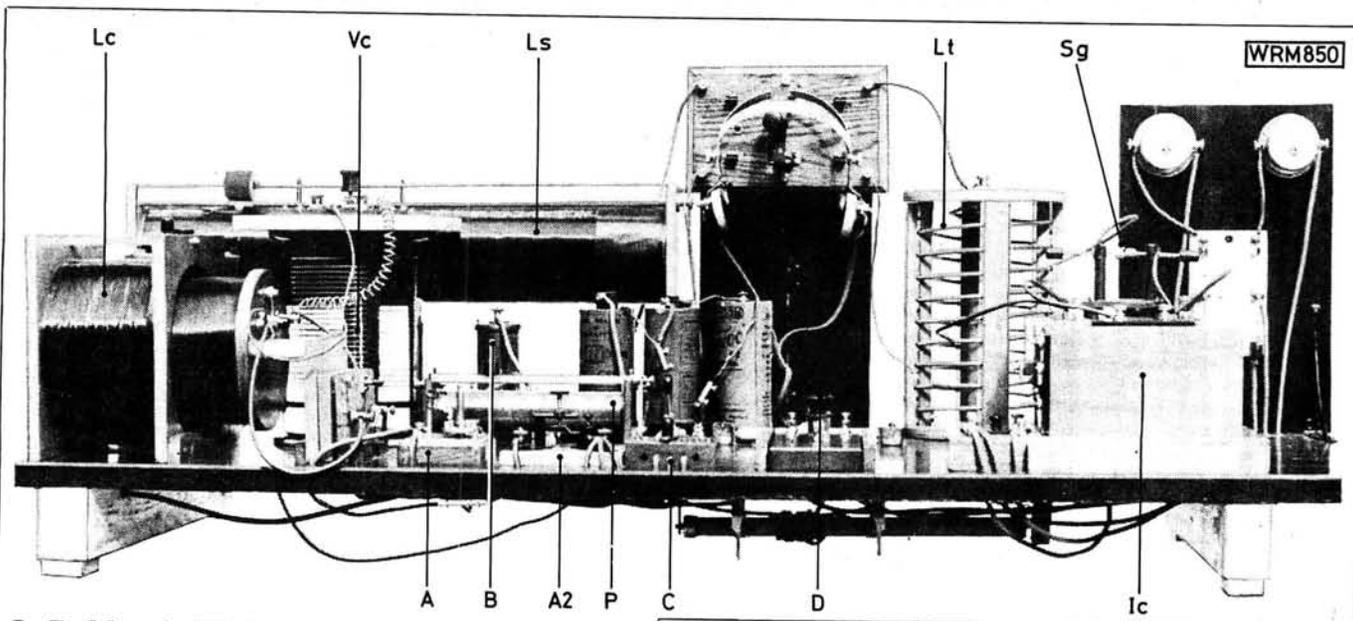

G. R. Marsh NXJ

later 2IW—Winchester

This station was originally quoted as having a power of 20 watts from accumulators operating on 1.5MHz (200m), with a range of 914km!

The equipment was typical of the pre-1914 period, the transmitter being a simple induction coil (Ic) and spark gap (Sg). Tuning appears to have been accomplished by taps on the coil (Lt). The Morse key is shown at D.


The receiver was fairly comprehensive having the choice of a large slider inductance (Ls) or loose coupler (Lc) together with a large variable capacitor (Vc) for tuning. A selection of detectors were available, a multicrystal Perikon type (A), Perikon detector (A2), Electrolytic type (B) and point contact or carborundum type behind the selector switch (C), voltage control by potentiometer (P) from "bell ringing" dry cells.

It is clear from the picture that the majority of the items were home constructed.

L. Claude Wilcox WUX

later 2FL—1913, Warminster, Wilts


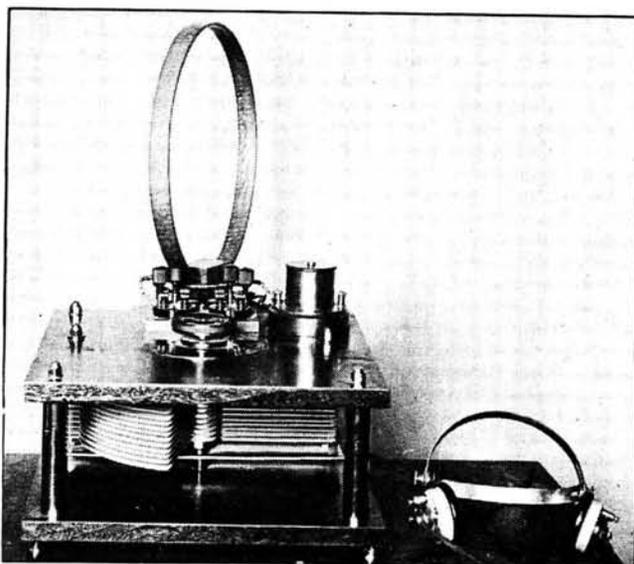
In this station the power was a quarter of a kilowatt on 500kHz (600m).



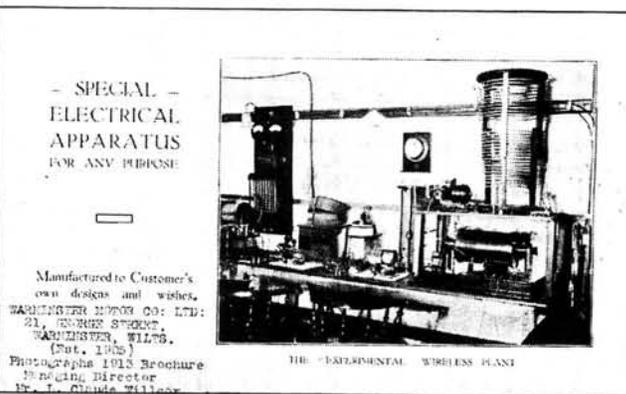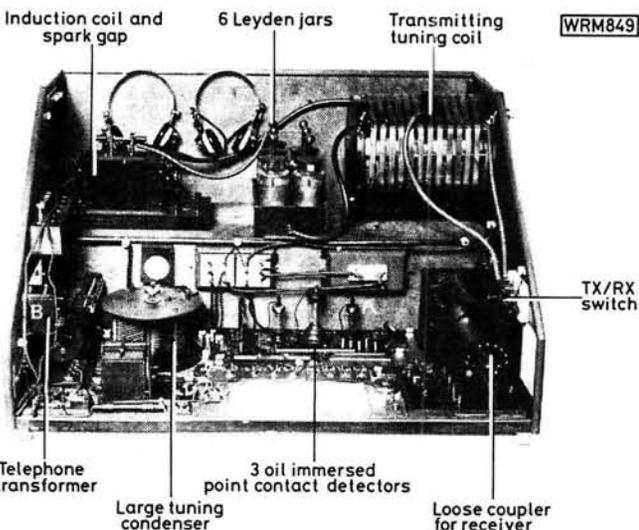F. Catherly

1913—Parkstone, Dorset

This compact transmitter and receiving equipment was housed in a relatively small cabinet, transmitting on a frequency of 3MHz (100m) with low power 5-7 watts derived from dry cells.



The receiver was tuned by a two-slider inductance and a selection of different detectors, including the popular Perikon type. This photograph was widely known as it appeared on the cover of the *Gamages Directory of Experimental Wireless Stations in the UK*.

Practical Wireless, October 1983

L. McMichael MXA*

later 2FG—1913, London

The first wireless experiments he conducted were about 1902, when he succeeded in ringing a single stroke railway signal bell at distances up to 183m using a transmitter with a 203mm spark coil, the receiver detector was a coherer with nickel and silver filings. After a break of some ten years he returned in 1912 to the more advanced state of wireless communication. The transmitter he then used ran up to 150 watts to a 152mm coil on 1.09MHz (275m) with a stated range of 64km.

His receiver was capable of tuning up to 30kHz (10 000m) using a large slider tuned circuit, his crystal detector was a Perikon type, the range of the receiver was stated to be 2414km.

* A founder of the Wireless Society of London 1913.



World War I

At the outbreak of World War I all holders of amateur licences received a telegram from the Post Office. This effectively halted any further amateur experiments for the next few years.

August 1st 1914

To.....In accordance with your wireless licence Post Master General requires you to remove at once your aerial wires and disconnect your apparatus. One of his officers will shortly call upon you.

King, Secretary Post Office.

For Your Bookshelf

World at Their Fingertips by J. Clarricoats. This book is now going out of print but no doubt can be obtained either secondhand or from libraries; it was originally available from the RSGB.

The Story of Radio 1-3 by W. M. Dalton. Published by Adam Hilger Ltd.

Early Wireless by Anthony Constable. Published by Midas Books.

A book list of relevant material can be obtained from the Vintage Wireless Co., 64 Broad Street, Staple Hill, Bristol.

Practical Wireless


THE RADIO MAGAZINE

ZX81 RADIO PROGRAMS

Have you tried using your ZX81 home computer to further your favourite hobby?

The *Practical Wireless ZX81 Radio Programs*—1 cassette has eight useful and interesting programs for the radio amateur.

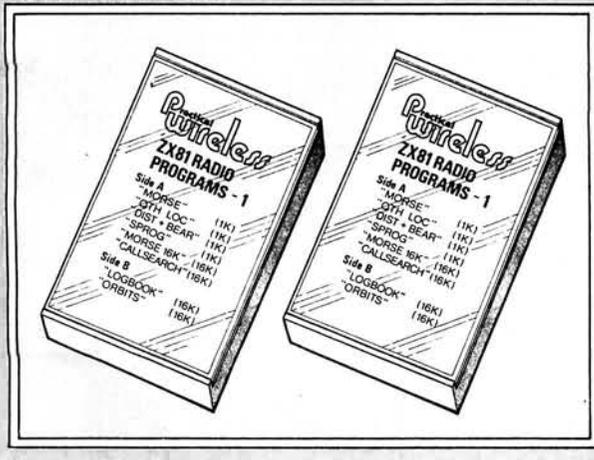Track amateur satellites, keep a log, learn Morse, find your sproggies. These, and more, are on the cassette which is available by post from *Practical Wireless, Westover House, West Quay Road, Poole, Dorset*, price £3.50 inc. VAT and postage or from *PW* stands at selected rallies.



Practical Wireless, October 1983

Practical Wireless

THE RADIO MAGAZINE

ZX81 RADIO PROGRAMS

Learn Morse the PW way using the ZX81+16K as your tutor. This program teaches you Morse code to the level needed to pass the Post Office Morse Test. As well as the cassette and ZX81+16K you will need a simple output port and practice oscillator as described in PW August 1983.

The cassette will be available from PW stands at selected Rallies and Exhibitions, price £5.00, or by post from—*Practical Wireless Cassette Tape Offer, Department PWC1, Rochester X, Kent ME99 1AA* price £5.75 inc. post, packing and VAT.

PW STRUCTURED MORSE LEARNING COURSE

Use either side of tape
Load as "M" (16K)

An output port and Morse practice oscillator are required for use with this program. A suitable circuit appeared in PW August 1983. Any output port designed for use with the ZX81 can be used providing the output goes HIGH for address 8192,2 and LOW for 8192,0

IMPORTANT

Many cassette recorders impress a brief and inaudible spurious pulse onto the tape when the play button is pressed. ON NO ACCOUNT STOP OR START THE TAPE OTHER THAN AT THE BEGINNING OR END. Disregarding this warning could result in permanent damage to the recorded program.

Products

Icom's Latest 144MHz Base Station

In addition to the two new Icom rigs I mentioned in Products last month, comes the IC-271E, an improved and updated 144MHz (2m) all mode base station, based on the popular IC-251.

Among its many features, r.f. power can be adjusted up to 25W on all modes—s.s.b., c.w. and f.m.—and an extremely low-noise p.i.l. system is employed allowing frequency setting to within 10Hz, achieving true v.f.o. action. Plus a listen-input has been added for repeater work.

Other standard features of the IC-271E include; 32 memories with full function capability; up/down buttons; dial lock; switchable pre-amp; duplex check; receive audio tone control; S-meter; selectable centre-zero discriminator meter and dual v.f.o.s.



Optional extras include; speech synthesiser announcing displayed frequency; 22 channel memory extension—with scan facilities; 10Hz tuning facility and internal "chopper"


(switched mode) power supply unit.

The IC-271E costs £569 and is obtainable from: Thanet Electronics, 143 Reculver Road, Herne Bay, Kent. Tel: (02273) 63859/63850.

Battery Protector

S & W Battery Charging Ltd. have developed a new device to prevent premature battery failure and to reduce the costs of battery maintenance, which is simply inserted between the charger and the battery.

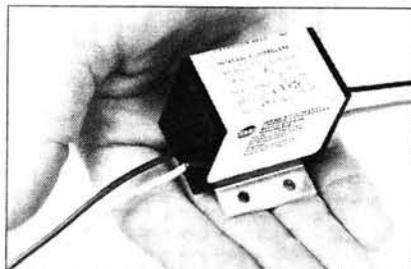Hardly larger than a matchbox, the unit constantly monitors battery voltage without interrupting the system. Once the cells are fully charged, the controller will pass only



sufficient current to maintain the battery in a fully charged condition

without overcharge.

The controller may be adjusted externally to give a variety of voltages between 9 and 16V, thereby making one unit suitable for a wide range of lead acid or nickel cadmium batteries.


Priced at £18.98, which includes VAT and carriage, the controller is available direct from: S & W Battery Charging Systems Ltd., Nailsea Trading Estate, Southfield Road, Nailsea, Bristol BS19 1JL. Tel: (0272) 855161.

Design Awards

Among the 1983 winners of Design Council Awards were two items of particular interest to the hobbyist.

Of most direct application were the "Safety First" 4mm silicone rubber test leads manufactured by Greenpar Connectors Ltd., Harlow. The plugs fit standard 4mm sockets, but incorporate an automatically operated safety shroud which protects the user against touching a live pin when plugging in or out. The plugs also stack one into the other, so that multi-connections can be simply made.

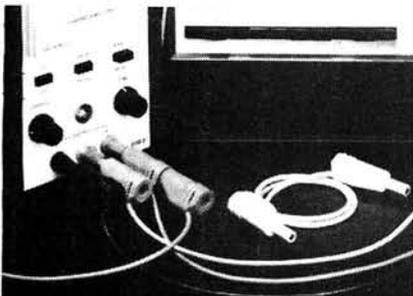The plugs and leads, rated at 16A and 2kV r.m.s., come in six bright




colours for easy identification and lengths of 0.5m, 1m and 2m, although we understand that at present only five colours and one length (1m) are available from Farnell or direct from: Greenpar Connectors, Studland Park Avenue, Newmarket, Suffolk CB8 7EA. Tel: (0638) 668081.

Conceived originally by Worcester schoolmaster Peter Huxtable as a hose clamp, the Dandy Clip consists of a flexible threaded nylon band, with a nut and collar for tightening. The two ends of the flexible band, threaded only on the outside face, are pushed through the collar and, back to back, form the full diameter of a threaded screw. The nut then tightens the clip around any object with a diameter from 100 mm down to 5 mm. By joining several Dandys together the upper limit can be extended.

Made of non-corroding high-density nylon, the clip is both tough and reusable, and because of its flexibility, will secure objects of any cross section. It retails in d.i.y. supermarkets for around £1, and could prove very useful in field-day antenna rigging and similar applications.

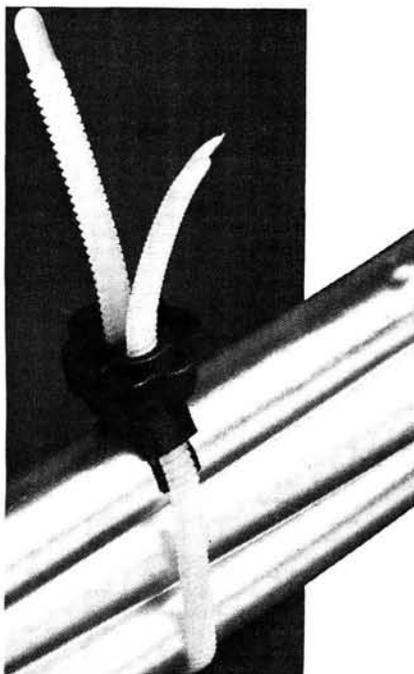The Dandy Clip is manufactured by Wonderclip Ltd. of Bilston, and distributed in the UK by W. Armes & Son Ltd.



WATERS & STANTON ELECTRONICS

18/20 MAIN ROAD, HOCKLEY, ESSEX (0702) 206835
12 NORTH STREET, HORNCHURCH, ESSEX
TELEPHONE (04024) 44765

INTERESTED IN HAM RADIO?

... THEN COME TO THE EXPERTS

WE CAN OFFER YOU A GOOD DEAL ON ALL POPULAR BRANDS

**BACK IN STOCK
SONY ICF2001
SHORT WAVE RECEIVERS £159!**

YAESU - ICOM - TRIO - FDK - WELZ - AZDEN - JAYBEAM

TRIO R600 £257.50



If you're a beginner just starting out in radio you'll be delighted with the performance that the R600 offers you. Considering the electronics that are packed into this receiver, the price is remarkably low. A few years ago this performance would have cost you twice as much. Full digital readout and really simple tuning in of SSB signals makes this one of the few top receivers that the beginner should consider. With all the gloom and doom one hears about in the news these days, why not put a pair of headphones on your head, plug them into the R600 and whisk yourself away into the wonderful world of wireless. Signals from the Australian outback or the flying doctor, radio amateur expeditions on some remote Pacific island, signals from Russian amateurs or young American novices, the latest World news even before the BBC reports it, aircraft over the Atlantic, shipping distress frequencies; all this and much more is possible on this little receiver. So don't delay any further, send today for full details and introduce yourself to an exciting new hobby.

TRIO NEW R2000 £398.75



The R2000 is Trio's latest communications receiver covering the entire spectrum from 150KHz to 30MHz. It boasts a whole host of features that make it probably one of the best buys in radio communications receivers currently available today. Its uncompromising design provides facilities for AM, SSB, CW and FM reception with 3 separate filters automatically switched in. The factory fitted memory module provides for 10 separate frequencies to be programmed in any mode and for automatic scanning of all channels. In addition, pre-programmed segments of the band may also be scanned making it one of the most versatile designs available. As an added feature an internal battery with an estimated life of 5 years retains the memory even when the power is disconnected. The rate of tuning is controlled electronically and has 3 speeds to suit all types of operation. Another novel feature is the squelch control that is effective on all modes for suppressing background noise when no signal is present. Other features include noise blanker, dual AGC, clear digital display down to the nearest 100Hz, dimmer switch, 24 hour quartz clock, front mounted speaker, tone control, RF step attenuator, dual impedance aerial terminals, 230v AC or optional 12v DC operation, built-in timer etc, etc.

★ PART EXCHANGE WELCOME* - PHONE FOR QUOTATION ★

YAESU FRG7700

£335



The FRG7700 is for the advanced listener or for the enthusiast who demands the best in short wave reception. The receiver covers the complete spectrum 200kHz to 30MHz with a highly accurate digital display. The receiver offers excellent sensitivity and selectivity and has separate detectors for AM, FM and SSB, plus switched bandwidth on AM. Other controls include automatic gain control, noise blanker, attenuator, squelch, rf gain control and clock with timer. There is also facilities for fitting an optional 12 channel memory unit. The receiver runs from 230v AC mains or 12v DC and there is an optional aerial tuner to go with it. And if you are interested in VHF, there is a complete range of specially designed converters to go with the receiver that covers the amateur, aircraft and marine bands, etc. Why not send today for our coloured brochure and get to know more about what the FRG7700 has to offer.

ICOM R70

£499



The R70 is possibly the ultimate in receivers designed for the amateur market. We've tested this thoroughly and are convinced that this receiver offers everything that the enthusiast could ever wish for. If anything can pull the signals in, this one will. Frequency coverage is 100kHz to 30MHz in 30 bands. A 3 stage rate of tuning enables easy tuning for all modes, AM, SSB, CW and FM (the latter requires the optional FM module). The dual VFO enables 2 separate frequencies to be used and the bright digital display gives precise frequency readout down to 100Hz with absolute stability. Great emphasis has been put on selectivity and in addition to independent filters for each mode, there is a separate selectivity control. This enables the bandwidth to be continuously varied down to 500Hz. Another control provides a variable notch filter to prevent heterodyne interference - now you can really dig deep for those elusive DX signals. Another nice feature on this receiver is its excellent sensitivity even on very modest aerials. This is obtained by the use of a well designed front end incorporating switched pre-amplifier and attenuator. Other features include dual-mode noise blanker, dual AGC action, transmitter monitor, dimmer switch, dial lock, RIT control, squelch control, tone control, FM tuning indicator, forward facing speaker, 230v AC power requirements, etc, etc.

NEW BRANCH OPEN 12 NORTH ST., HORNCHURCH, ESSEX.


only minutes from M25

AIRBAND MONITORS

CD-6000

£99

ATC-720

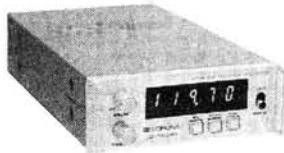

110-140 MHz 12V DC
5kHz steps. 1 watt audio output.
Excellent sensitivity.

Completely synthesized
118-136 MHz
25kHz steps
0.5W sensitivity.
Rechargeable batteries.
Helical aerial.
230V AC charger.
Professional design.

TELEPHONE FOR
FREE ADVICE ON
AIRBAND MONITORS.

BRAND NEW SCANNER!

SAIKO SC-7000

CLEAR DIGITAL DISPLAY
70 MEMORIES.
COMPREHENSIVE SCANNING.
230V AC & 12V DC.
60-89MHz; 140-179MHz;
108-138MHz; 380-519MHz.



This amazing receiver covers the major portions of the VHF and UHF spectrum. Both AM and FM modes are catered for and the large digital display give clear indication of frequency being received, memories, locked out channels etc. It has excellent sensitivity and is one of the best scanners we have so far come across. Ideal for listening to amateurs, aircraft, marine and public service traffic it represents state of the art sophistication to wide band monitoring. Available from stock.

£259
IN STOCK

SEND SAE FOR
1983 CATALOGUE

ALL ITEMS IN STOCK
SENT BY RETURN

BARCLAYCARD ACCESS AND INSTANT CREDIT

E.&O.E.

MAIL ORDER SLIP to: Waters & Stanton Electronics, Main Road, Hockley, Essex.

Name.....

Goods required

Address.....

.....

Please rush me the above. Cheque enclosed for £.....

Please charge to credit Card No.....



RADIO AND TELEVISION SERVICING

1982-83 MODELS

Editor: R. N. Wainwright,
T. Eng (CEI), F.S.E.R.T.

This volume, like its predecessors, continues to provide the only comprehensive reference source for a large range of domestic entertainment products currently available from retail outlets.

The first part of this volume contains manufacturers' circuits and service information for the main classes in a wide selection of colour and monochrome receivers. The second section presents a selection from the numerous available types of audio equipment, including portable and clock radios, in-car units, cassette recorders, combinations and unit audio systems. The usual addendum gives cross-references to relevant information detailed in earlier volumes, together with supplementary servicing information abstracted from the technical bulletins issued by the manufacturers during the year.

Price: £22.50
On sale now

Previous volumes are still available. Enquiries to the Sales Department, Macdonald & Co.

From booksellers, or in case of difficulty, please use the coupon below:-

To: Cash Sales Dept. Macdonald & Co.,
Maxwell House, Worship Street,
London EC2A 2EN.

Please send me copy(ies) of RADIO AND TELEVISION SERVICING 1982-83 MODELS.

I enclose a cheque/PO made out to Macdonald & Co (Publishers) Ltd for
Please allow 28 days for delivery.

Name

Address

.....

.....PW

Macdonald
a BPCC plc company

Silver 70

ANTENNA

SUPERB 70CMS BAND AERIAL

- †High Gain - 16db
- †Low VSWR - better than 1.2 at 432MHz
- †Wide Bandwidth - greater than 10MHz
- †Low Weight - 1.1kg
(wind loading 0.080 sq.metre)
- †British Made throughout
- †2 years guarantee

Still only
£31.95
plus £4.50 Securicor
delivery

All mast fittings
and clamps included

BUY NOW FROM...

Hall Aerials
52 Hatfield Crescent
Bedford

PM Electronic Services
2 Alexander Drive
Newhall
Merseyside

Northern
Communications
259/300 Clarendon Rd
Halifax
West Yorks

Our newest stockist...
BAC Communications
Barnsley Aerial Centre
54 Sheffield Road
Barnsley
South Yorks

**Ant
Products**

Ant Products All Saints Industrial Estate Baghill Lane Pontefract West Yorks tel.(0977) 700949

Send cheque or
money order
TODAY

COMMUNICATION CENTRE OF THE NORTH

The largest range of communications equipment available in the North. Full range of receivers, transceivers, antennas, power supplies, meters. Ali tubing - wall brackets etc.

We are the only official TRIO stockists in the North West. Full range of equipment on display. Guaranteed after sales service.

RECEIVERS

TRIO R600 Solid State Receiver	£257.60
TRIO R2000 Solid State Receiver	£398.00
JRC NRD515 Receiver	£985.00
YAESU FRG7700 Receiver	£335.00
Diawa 2m FM Receiver	£46.00
CD600A Airband Receiver	£99.00
DRAKE R7A Solid State Receiver	£1,039.00

Please send SAE for full information and up-to-date prices as these fluctuate to change in sterling rates.

For the caller a wide range of Aluminium Tubing, Clamps, etc. at competitive prices, i.e. 12' x 2" Ali Tubing **£9.00.**

+ VHF - Aircraft Band Converters and Receivers.

Part Exchanges welcome. Second hand lists daily.

Send S.A.E. for details of any equipment.

HP terms. Access/Barclaycard facilities.

Open 6 days a week. 24 Hour Mail Order Service.

Phone 0942-676790.

STEPHENS JAMES LTD.

47 WARRINGTON ROAD,
LEIGH, LANCs. WN7 3EA.

Products

Mains Operated Electronic Iron

Litesold have recently introduced a mains-voltage electronically temperature controlled soldering iron, entitled the EC50.

The iron incorporates an electronic temperature control circuit mounted inside the handle, which operates in response to a thermistor fitted inside the bit-mount. Power to the 50W heating element is controlled by a triac operated by a zero-voltage switching i.c., to minimise spiking and r.f.i., and the iron is fully earthed so that it may be used on sensitive equipment and components.

A special feature of the design is that the low-voltage supply necessary for the control circuit is obtained by means (for which a patent is pending) which does not involve fitting a drop-resistor in or near the handle. This problem has previously prevented a mains iron of this type being made to run with a sufficiently cool handle.

The control circuit provides a proportional control band, so that power to the heating element is only fully on or

off outside a temperature band centred on the set value. Within this proportional band, power is supplied in regular pulses of equal interval but of a length which varies according to the difference between "actual" and "set" temperatures. This feature provides extremely close control, with no swing or overshoot. An internal neon indicator glows through the translucent handle when the element is energised.

Access is provided to the temperature control potentiometer, and settings may be varied from approximately 280 to 400°C. Standard setting is 370°C.

Priced at £28.00 plus VAT and 50p p&p, the EC50 mains operated electronic iron is obtainable from: *Light Soldering Developments Ltd., Spencer Place, 97/99 Gloucester Road, Croydon CR0 2DN. Tel: 01-689 0574.*



conditions, the new Draper pliers are all manufactured in induction hardened chrome vanadium steel with blue pvc coated handles. A lap joint combined with precision machined jaws ensures accurate register at the tip of the nose of the pliers, and the handles are spring loaded to minimise user fatigue.

The range includes both short, straight, and bent needle nose pliers, along with flat nose, plain, thin jaw and angle head cutting pliers. All are ideal for miniature electronic assembly work and precision engineering applications.

Priced at between £5.26 and £6.85 each (plus VAT), these quality precision instrument pliers are available from most good tool stockists.

Draper Tools Ltd., Hursley Road, Chandler's Ford, Eastleigh, Hants SO5 5YF.


If you please

Please mention this column when applying to manufacturers or suppliers featured on this page.

Precision Pliers Range

A range of seven precision instrument pliers have been added to the Draper selection of high quality hand tools specifically intended for the discerning engineer and electronic constructor markets.

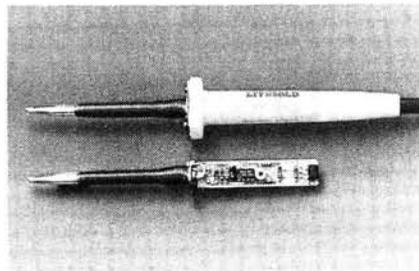Intended to provide lifelong trouble free service, under everyday working



Benny



Letters

The letter from Mr Rumbelow in our August issue about the recent Radio Amateurs' Examination provoked a deluge of similar complaints from equally fed-up aspiring amateurs.

We haven't the room to print them all, but here is a selection of their comments. Copies of all the letters have been forwarded to the City & Guilds.

Sir: I was pleased to read the letter from R. M. Rumbelow in your August issue of *Practical Wireless*, regarding the RAE in May.

I, my wife and two friends too had difficulty with this examination, and was pleased to know that another potential Radio Amateur feels as we do and other friends and acquaintances who took the examination in May, here in the county of Cornwall.

We all bought the book *Radio Amateurs Examination Manual*, tenth edition 1982-1985 syllabus by G. L. Benbow, on the advice of other radio amateurs, we sent away for and received *How to become a radio amateur* from the Home Office. Also we had the sample questions from the City and Guilds Institute and we all thought these were the kind of questions we were to expect in the exam. We had books from the library, we spent many months and worked very hard until we were confident in what we learned. Like Mrs Rumbelow, we were deflated after the exam we too thought the questions were distorted, it was difficult to know what was being asked.

We would be interested to know what amount of letters you receive on this, also would you be willing to ask the City and Guilds Institute for their comments.

*D. J. MacDonald
Truro, Cornwall*

"... I, too suffered, taking the exam in May, following some eight months attendance at night classes... I have not received the results of the exam, but I must say I fear I did not fare well..."

Halfway through the second paper... I could not understand some of the questions... I read them again, and again, and it was only after a minute or two that I realised what the examiner wanted...

... I did not feel happy that the questions asked bore sufficient relation to the course I had been on...

One other point was... having to fill in a separate (computer) sheet with my answers... which, in my view, was a badly designed form... There was the possibility of a high margin for transcription error when working under pressure."

*T. Carruthers
Worthing, Sussex*

"... A little group in my area decided to take a home study course through the winter... involving us in a lot of expense, fees, books, travelling etc..."

... the big day arrived, so feeling fairly happy with the amount of knowledge acquired... we arrived to take the exam... My first impression, having read the papers through, was that I had taken the wrong course, it should have been English. I felt completely deflated..."

So, Mrs Rumbelow, please do not feel you have let your husband down, I am sure that given a fair chance you and all of us would have passed, but all we can do is wait and see the outcome of the results..."

*Mr A. B. Hocking
Truro, Cornwall*

"... I paid over £50 for a postal course and coupled that with 26 weeks at night school... so I sallied forth into the examination room with a certain degree of confidence.

The first part arrived on the desk and was dealt with methodically and with confidence. The second part at first seemed to cover all I had been led to believe... after the 7th or 8th question I began to realise that all was not well. I read the paper through, and re-read it, ... firmly convinced that I had been well and truly conned, as it bore no relation to previous test papers... there can be no doubt in my mind that I have failed..."

... I can only conclude that the Examination Body have decided that there are too many amateurs already and in May 1983 opted to make things difficult.

My condolences to Mrs Rumbelow, I know just what she has gone through."

*Richard Welch
RSARS, Grimsby*

"... I have spent thirty years in the Electronics/Radio trade and frequently take part in exams set by my company. I too studied according to the *RAE Manual* and was more than taken aback by the exam papers, particularly the lack of mathematical problems.

I cannot stress too strongly my anger and frustration at something I had intended to enjoy."

*R. W. Lannon
Cardiff, S. Glam*

"... I thought that my wife and I were alone in our reaction to the examination of May 16..."

... We were quite buoyant after Paper 1, as we felt that all our efforts were paying off, we certainly worked considerably harder for the RAE than for 'A' levels. Paper 2, whilst containing much that was reasonable was unrepresentative of the available text books, the questions often couched in terms apparently designed to confuse or to exclude those of limited vocabulary.

... most of us have mentally prepared ourselves for failure and a December retake..."

... If the rules of the game have been changed I wish someone would tell me, as I'm going to crack this exam or bust!"

*Michael & Margaret Rochester
Oakham, Rutland*

"... I expended considerable time and money in a course to prepare for this exam... various past papers as could be legally acquired were appraised and thoroughly practised..."

... every single person in my examination room later expressed—first anger then dismay, the Part 2 had been set by someone totally out of touch with previous questioning techniques and obviously hell-bent on concentrating on obscure areas of radio theory not previously muted... In effect, the examiner seemed to have ignored all suggested guide lines and set an entirely new strain of question..."

An impromptu meeting outside revealed many embittered individuals... others were not disposed to try again..."

... a repetition of this type of mistake will only breed discontent and a large number of pirates—exactly the opposite of what is intended."

*K. R. Nunn
Gt. Yarmouth, Norfolk*

"... My husband, two friends and I spent many months, money and brainwork studying for this exam. Old wireless sets and countless spare parts were shown to me and my friend... because we're not technically minded and could not tell between a resistor and transformer. At the end of all this hard work, our spouses were proud with us for learning

Practical Wireless, October 1983

Letters

what we did, and proud of themselves for being patient tutors. We spent hours learning the formula . . .

Imagine our horror when we sat and looked at our questions, the disappointment and deflation we felt. We came away that night feeling we did not know the first thing about anything. We await our results with confidence of our failure.

*Mrs P. MacDonald
Truro, Cornwall*

" . . . Speaking personally, I knew nothing before we started the course and felt really proud to gain the knowledge to sit the RAE . . . To my amazement I felt confused and shaken when I read the papers and did my best to answer the questions . . .

I know every aspect cannot be covered but surely with all the formulae required the papers could have had a wider selection. When I think of the agony of remembering the formulae, Q codes etc., I could have easily been reduced to tears . . .

" . . . I hope those 'little grey men' who make out the papers for us in December will have a few scruples and make it a fairer paper."

*Mrs Josie Hocking
Truro, Cornwall*

" . . . Having put a lot of effort and study into preparing for the exam and using the sample papers and the *RAE Manual* . . . I was absolutely horrified when I saw what was written on the second paper, there was hardly anything which we had been told to study in the syllabus, on the paper at all . . ."

*Mr J. Angiolini
Taynuilt, Argyll*

" . . . on reading Part 2 of the paper was thoroughly disillusioned. Where were the formulae etc., I had spent so long learning? . . . on the night the paper was nothing like what I had been led to believe . . . I thought I was being examined on how I interpreted the questions and not on my knowledge of the subject . . .

I have started to revise in readiness for December's exam, not having heard the results yet, but not very confident. This has made me more determined to pass . . ."

*B. Clayton
Kirkham, Lancs*

" . . . After studying every Tuesday night for the past nine months . . . we felt fairly confident as to a reasonable chance of passing the exam . . .

" . . . Paper 1 was quite fair, but then came Paper 2 and that is another story. A vast number of the questions we had not even covered, and those that we had were phrased in such a way as to be at least very confusing.

" . . . examiners, . . . please take into account two things: Put the questions which are relevant and likely to be covered by the average syllabus; Phrase them in every-day English . . . We then may stand a better chance of passing and joining the ranks of those who have passed and are enjoying themselves on the airwaves."

*R. R. Matthews & R. Richardson
Leicester*


" . . . It is wrong when one spends perhaps £100 on books etc., to get the technical facts correct, to find that the C & G go right away from the sample questions in the RAE books . . .

I was disappointed in the way questions were put. Is this a way of keeping the numbers down on two metres?"

*Mr E. W. Stannard
Ipswich, Suffolk*

Next month in

On Sale 7th October

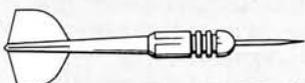MORE  **DART** 
QRP TOP BAND TRANSMITTER
IF Signal Generator
Directional Response Indicator

Test Gear


144MHz QRP Contest

This is to certify that
was placed . . . in the results
of the above contest

EDITOR, Practical Wireless

PLUS
your favourite regulars in



Sensitive Capacitance Meter

E.W. Nield GW3ARP

Have you ever wanted to measure the value of a capacitor in the range 0 to 100pF with reasonable accuracy? The customary bridge circuit is useless below 100pF. Even a more sophisticated linear-reading type using a monostable logic circuit was found to be no better with these low values. It was for these reasons, and the fact that, like most experimenters I possess a large number of unmarked components salvaged from TV tuners and the like, that this project was designed. It is also useful in measuring the exact value to which a trimmer has been set, or for replacing a "twisted pair" makeshift trimmer with a more respectable fixed component. The working principles may or may not be original, but the device certainly is, and most important—it does the job.


The unit is very sensitive and can easily detect the difference in capacity between, say, 3.3 and 3.8pF, so enabling accurate matching to be done. It will, in fact, record as little as 0.2pF, yet is at the same time stable and easy to use, and not affected by "hand capacitance" variations.

The values are read directly from a linear scale in two ranges: 0 to 10pF and 0 to 100pF. No attempt has been made to cover higher values with extra ranges, although this could be done, as there are many other simple designs capable of doing this, but which are not much use below 100pF and non-starters below 10pF.

Circuit Principles

The system operates by applying a 12kHz square wave of fixed amplitude to a capacitance potential divider (Fig. 1). The upper arm consists of the unknown capacitor C test, and the lower of a fixed capacitor. The voltage developed across the latter can be made substantially proportional to the value of C test, and this voltage is first amplified then rectified and finally indicated on a meter.

As stated, the test capacitor forms the upper arm of a capacitance potential divider, the longer arm being C1 or C2 according to which range is in use. The signal appearing across this lower component has a potential which is independent of the frequency of the multivibrator (IC1) and which need not therefore be stabilised as to frequency but only in the amplitude of its output signal. This is achieved simply by means of a Zener diode regulator so that supply voltage variation will not affect the accuracy of the meter.

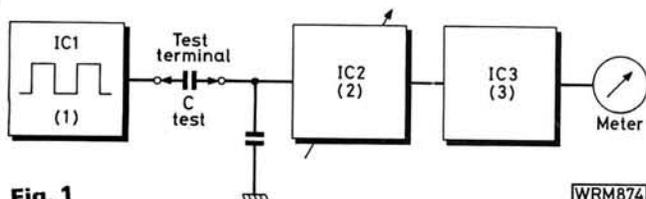

The ratio of capacitance between the maximum test capacitance (10pF or 100pF) to that of C1 or C2 has been made high in order to ensure that the signal voltage across the lower capacitor varies in a substantially linear fashion. This ratio will be seen to be about 10:1.

Amplification Stage

The signal across C1 (or C2) in Fig. 2 is applied to the inverting input of the operational amplifier IC2 and fed back degeneratively via R7 which, in conjunction with the variable resistor R1 (or R2), determines the loop gain of the stage according to the formula $A_v = R7/R1$ or $R2$.

Since the input voltage to pin 2 is referenced to zero volts, the normal tendency for the output at pin 6 to go negative on positive half-cycles is clearly impossible, as it would need to fall below zero to do so. The stage therefore



All components for this useful project are available from normal sources advertising in *PW*

£12

Intermediate


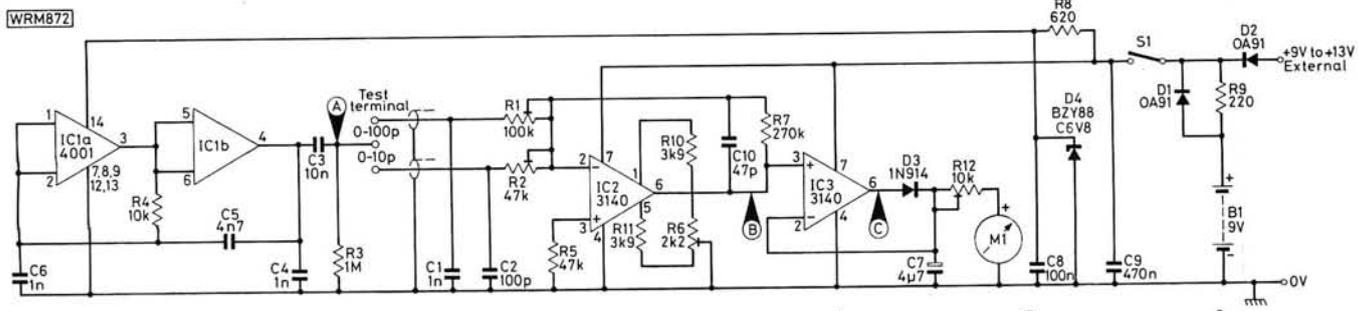


Fig. 2: The complete circuit diagram of the sensitive capacitance meter. The waveforms shown adjacent are peak-peak volts at full scale (100pF range)

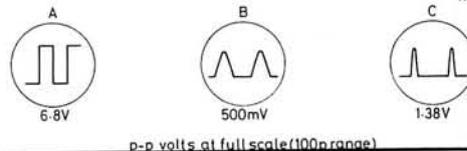

acts like a Class C amplifier in that only parts of the negative half-cycles at pin 2 are amplified, these giving a positive-going output at pin 6. A combination of a.c. and d.c. feedback ensures a linear input/output voltage relationship. The MOSFET op. amp. was chosen in preference to the usual 741 as it will continue to operate on these negative half-cycles, when its input voltage falls below earth potential. This avoids the complication of double or split supplies.

should be noted that this scale may be consulted although the actual range in use is nominally different (0–500mV in this case). If the nearest range is, say, 0–250mV it is a simple matter to add a suitable series resistance, whilst if the meter is one scaled to read 0–120 the simplest plan is to calibrate the two ranges to read 0–12pF and 0–120pF full scale, using 12pF and 120pF capacitors for the setting-up procedure as described later.

Peak Voltage Detector

Since the output of IC2 is of high impedance, a further stage has to be employed as an impedance converter in order to drive the comparatively low impedance of the meter circuit. IC3 is an operational amplifier combining this function with that of a peak voltage detector and provides a d.c. output equal to the peak value of the pin 3 input. It is, in fact, connected as a unity gain voltage follower and precision rectifier. The usual non-linearity encountered in simple diode rectifier circuits due to the junction voltage (0.65V with silicon devices) is, in this circuit, reduced in proportion to the open loop gain of the op. amp., which is in excess of 10^5 . Thus, the circuit will produce a d.c. output equal to the peak value of the a.c. input down virtually to zero!



The a.c. waveforms at three crucial points in the circuit are shown, for the benefit of those with access to an oscilloscope.

The Indicating Instrument

The constructor has the choice of using either a panel meter and building this into the circuit, or merely providing a meter output socket for use with an external multi-range testmeter set to a suitable voltage or current range. The first alternative is ideal but expensive, whereas the latter is economical and, if one has a handsome testmeter with a large scale, it gives one the benefit of this feature. Against this one has to consider the slight inconvenience of “connecting up” whenever the device has to be used. The circuit has accordingly been arranged to provide for either choice.

If the second choice is made, then it is clearly an advantage if one of the meter scales reads 0–10 (or 0–100) and it

Fig. 3: Component overlay and p.c.b. track pattern details, shown full size

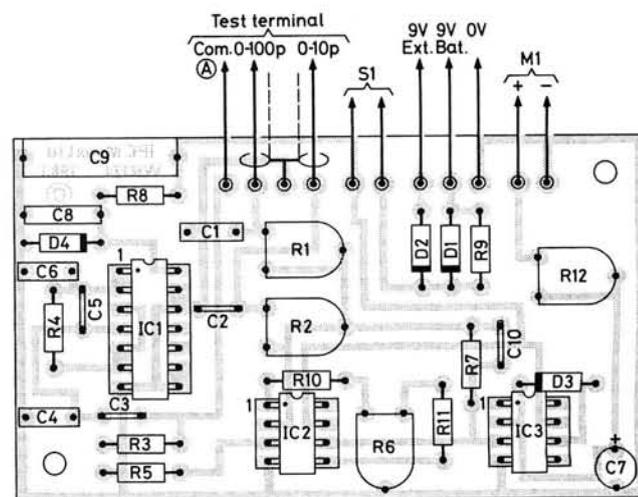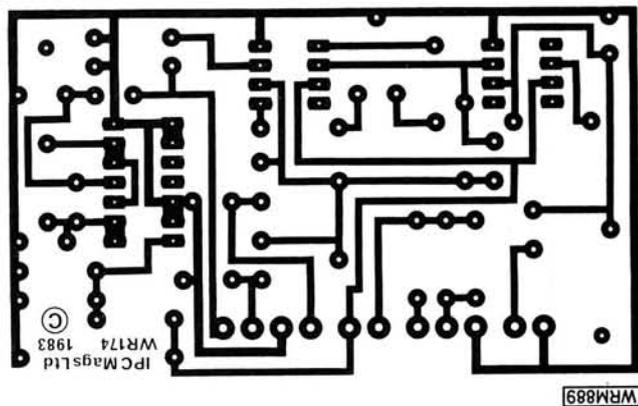

★ components

Resistors

Carbon Film $\frac{1}{4}$ W 5%

220 Ω	1	R9
620 Ω	1	R8
3.9k Ω	2	R10,11
10k Ω	1	R4
47k Ω	1	R5
270k Ω	1	R7
1M Ω	1	R3

Potentiometer

Miniature horizontal Preset

2.2k Ω	1	R6
10k Ω	1	R12
47k Ω	1	R2
100k Ω	1	R1

Capacitors

Miniature ceramic

47pF	1	C10
100pF	1	C2
1nF	3	C1,4,6
4.7nF	1	C5
10nF	1	C3

Polyester

0.1 μ F	1	C8
0.47 μ F	1	C9

Tantalum Bead

4.7 μ F 16V	1	C7
-----------------	---	----

Semiconductors

Diodes

OA91	2	D1,2
1N914	1	D3

Integrated Circuits

4001	1	IC1
3140	2	IC2,3

Miscellaneous

Panel Meter 100 μ A f.s.d.; Feed-through insulators (2); Miniature toggle switch s.p.d.t. (1); Speaker socket (2); Integrated circuit holders 8 pin (2) 14 pin (1); Battery (PP3) and connector.

Test Terminals

Much thought was given to the exact form which these should take. The final arrangement was decided upon as being simple, and avoiding switching with its extra stray capacities and the need for extra leads between the p.c.b. and the panel. As shown in the photograph of the prototype separate feedthrough terminals are fitted on the front panel; the p.c.b. is mounted directly behind on stand-off pillars. The oscillator lead, fitted with a small crocodile clip, also passes through a rubber grommet positioned between the test terminals.

In use, one end of the capacitor under test is held in the crocodile clip, and holding the clip, the other end of the capacitor is touched against the appropriate terminal. The meter reading is unaffected by the clip being held. Touching the other terminal at the same time does upset the readings considerably, but this is easily avoided.

Construction


The p.c.b. is fitted, components underneath, in an aluminium box. The lid becomes the bottom cover and the external components are arranged as shown. The box measures approximately 100 x 100 x 40mm and is earthed to the 0V line at some convenient point such as the socket fixings.

The layout of the p.c.b. is not critical but the i.c.s should be fitted in holders. The usual precautions must be taken when handling the c.m.o.s. integrated circuits and it is recommended that they are left in their wrapping until needed. The leads to the test points, and clip, are brought out of the board on the side opposite to the components so as to keep them short—single screened lead with pvc covering is used to connect the test points and their screens earthed to the p.c.b. This screening is necessary to eliminate stray capacity which would otherwise exist between themselves and the lead from the oscillator.

Setting-up

This is done using 5 per cent (or better) tolerance components of 10pF and 100pF and involves two main steps:—

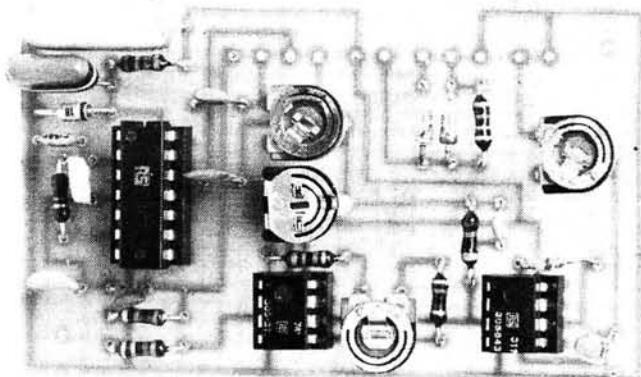- 1) **Null setting procedure.** Stop the multivibrator by grounding pins 1 and 2. Adjust the 10k Ω preset so that the meter reading just falls to zero. It is important that this point is not exceeded or the gain of IC3 will be reduced, particularly at the low end of the scale. It is as well, once the whole setting-up procedure has been completed, to measure the 10pF capacitor on the 100pF range and to adjust the null setting if necessary to give a correct reading.
- 2) **Gain adjustment.** Fit each reference capacitor in turn and adjust the appropriate preset to read full scale in each case. It will be found that the settings are interdependent, but no difficulty should be experienced. If a panel meter is used, the above routine should be carried out with the preset set at mid-scale.



continued on page 47▶▶▶

Digital Calibrator E.A. Rule

Most constructors have at some time or another felt the need for an accurate source of marker frequencies so that test and other equipment could be calibrated. In particular when constructing receivers a source of markers at precise points would make the job of dial calibration much easier. The unit to be described fills just such a need. It is simple to construct, has no expensive parts and puts out accurate marker pips at selected spacing right up into the u.h.f. frequency bands. The widest spacing of the markers is at 4MHz intervals and the closest at 2.5kHz intervals. A total of 15 different marker spacings are available.

The Circuit

The block diagram of the circuit used is shown in Fig. 1, and the front panel photograph gives the 15 different marker spacings available.

The master oscillator uses a 4MHz crystal oscillator and a 7404 i.c. The output from this is passed to a 7473 i.c. which is used to divide the 4MHz by one, two or four. The output from this stage therefore is at 4, 2, or 1MHz. This output is passed on to another 7473 which also divides by one, two or four, giving final outputs at: 4, 2, 1, 0.5 and 0.25MHz.

This divided output goes to a 7490 which divides by ten and is followed by a further 7490 also dividing by ten. Thus the outputs from the 7473 at 4, 2, 1, 0.5 and 0.25MHz can be divided further by a factor of 10 or 100 times. The lowest marker spacing available is 2.5kHz.

The complete circuit diagram is shown in Fig. 2. The crystal oscillator uses two sections of the 7404, IC1 as the actual oscillator and one section as a buffer amplifier. Precise adjustment of the crystal frequency is obtained by adjustment of trimmer C3. All other sections of the 7404 are unused.


The 4MHz square wave from the 7404 is passed to the first divider, IC2, which is a 7473 dual JK flip-flop. This is switched by applying voltages via S2 and D1/D2 so that it divides by one, two or four times. This output goes to a similar stage, IC3, which is switched in a similar manner by S2, D3/D4. The switching is arranged so that the final output from these stages is at 4, 2, 1, 0.5 or 0.25MHz.

This output can be selected by S3b and passed directly to the output socket. It is also passed on to IC4, a 7490 decade counter which is used to divide its input frequency by ten, before being selected by S3a and passed to the output socket. Additionally the output of IC4 also passes to IC5 which is a similar stage and divides by a further ten times, with its output selectable by S3b.

Final ratios available from the original crystal frequency are: 1, 2, 4, 8, 16; 10, 20, 40, 80, 160; 100, 200, 400, 800, 1600. These ratios are given in full as other crystal frequencies could be used to provide other marker spacings if required.

So that unwanted signals do not occur at the output the two divide by ten stages, IC4/5 have their supply voltages switched off when not in use. This is carried out via S3 and D5. The use of the steering diodes D1 to D5 avoids the use of more complicated switches and keeps costs down.

The power supply section uses a 12VA transformer with an output voltage of 6-0-6 volts r.m.s. feeding into a fullwave rectifier circuit consisting of D6 and D7. Rectified output is passed to the 2200µF reservoir capacitor C9. The smoothed voltage is fed into a regulator IC6, an LM309K. Capacitor C10 is mounted close to the input of IC6 to prevent oscillation. The regulated output from IC6 is at five volts.

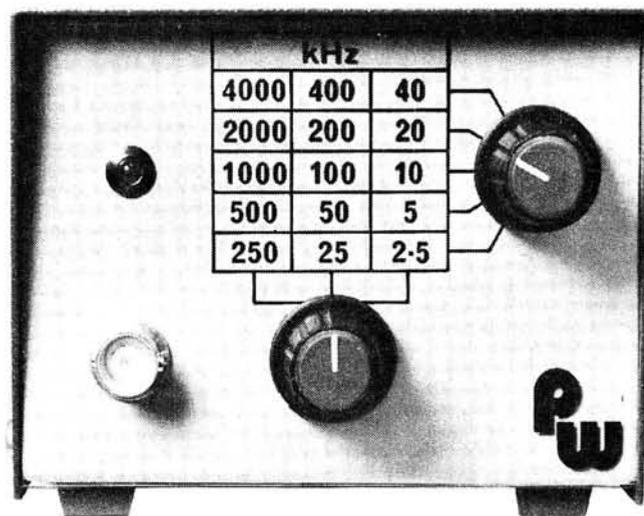

The Digital Calibrator front panel showing marker spacings

Capacitors C1, 5 - 8 are mounted close to the i.c. devices and decouple any residual square wave from the supply rail—these should not be left out as the square waves obtained have a very fast rise time and could cause malfunction of the dividers if their respective pulses were passed on via the supply line.

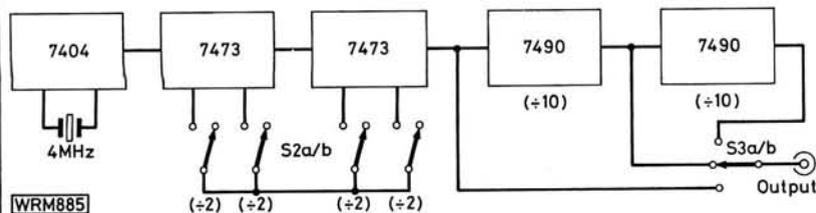


Fig. 1: Schematic block diagram of the Digital Calibrator outlining the division process used to obtain the final marker spacings, harmonics of which are usable well into the u.h.f. regions

Switch S1 is used to isolate the mains supply and a switch rated at 240 volts a.c. must be used (a number of the imported miniature toggle switches are only rated at 125 volts).

Construction

The layout of a suitable printed circuit board and component locations are given in Fig. 3. No i.c. sockets were used on the original board but can be used if required. Although a p.c.b. layout is shown the author used plain Veroboard for the prototype using the actual component wires and "stretched" 22 s.w.g. tinned copper wire to simulate the track; the layout was as shown but using wire instead of copper track. This method is used by the author for all his prototypes and in practice works very well. (Even the *PW* Winton amplifier and tuner were constructed this way at first.) The advantage of building prototypes in this way is that it enables changes to be made quickly and also gives the "final" layout which can be copied into a printed circuit form. Even v.h.f. r.f. circuits can be constructed this way with 100 per cent success.

Be careful to insert the i.c.s, diodes and electrolytic capacitors the correct way round. Printed circuit terminal pins are used where shown but if pins are not available then tinned copper wire can be used, or "fly" leads soldered into place before fitting the p.c.b. into the main chassis.

BUYING GUIDE

All components for this project are available from advertised sources within *PW*. The crystal used for the prototype was obtained from IQD, North Street, Crewkerne, Somerset, TA18 7AR; Part No: A120B

£20

Intermediate

Final Wiring

This is also shown in Fig. 3—the actual layout is not critical and no problems should be encountered. Be very careful to wire the correct switch tag to the correct diode, otherwise there is no telling what the final divided frequency might be!

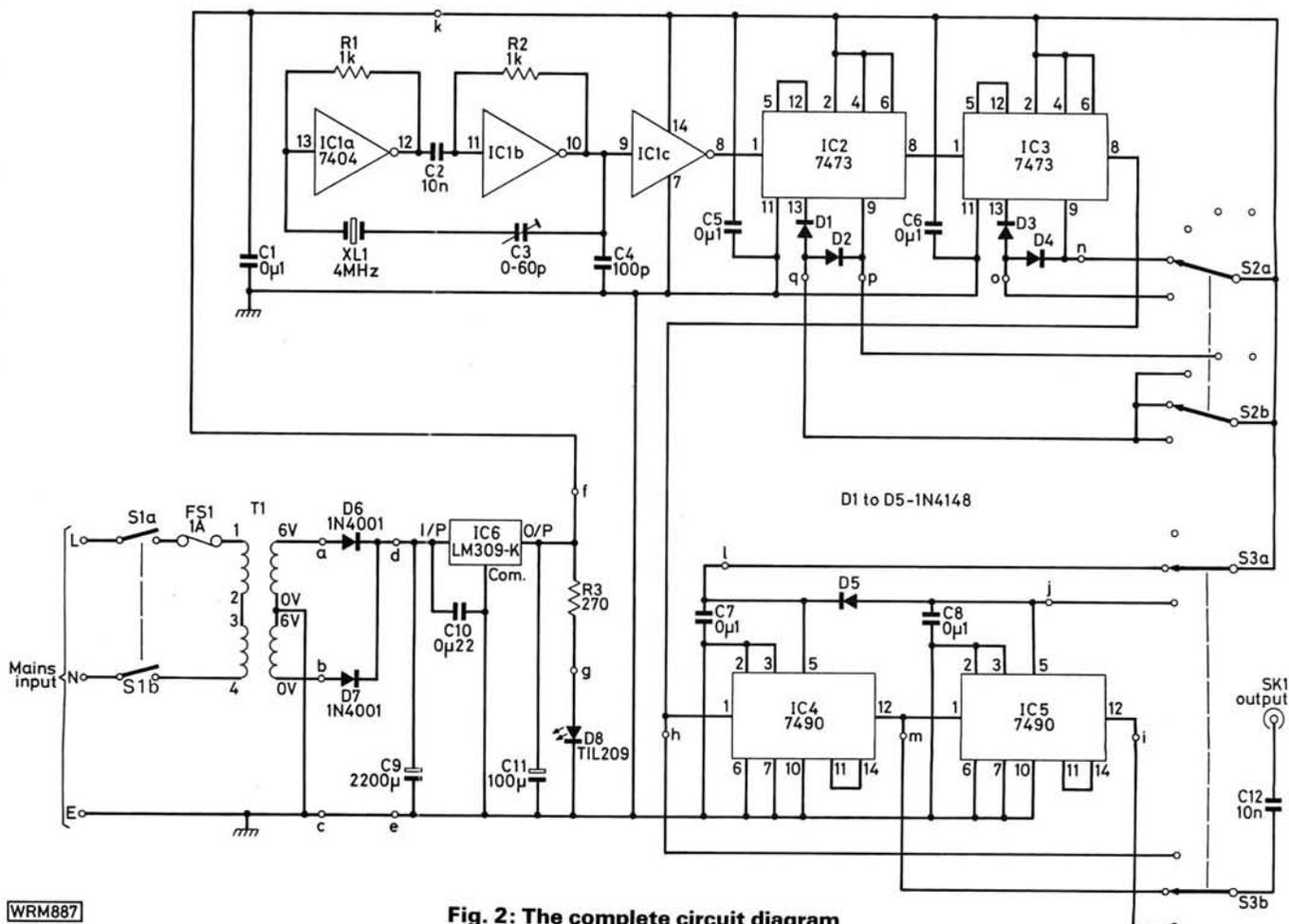


Fig. 2: The complete circuit diagram

WRM887

© IPC Magazines Ltd 1983 WR173

WRM888


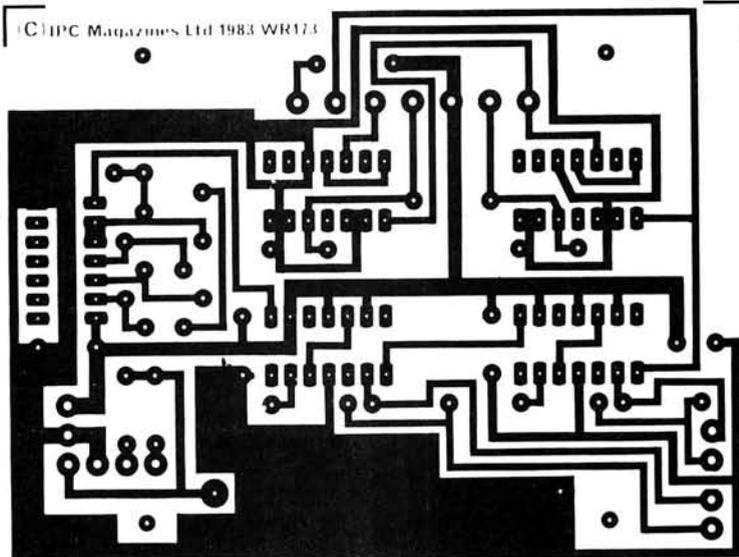


Fig. 3: Component placement/interconnection details and full size p.c.b. track pattern

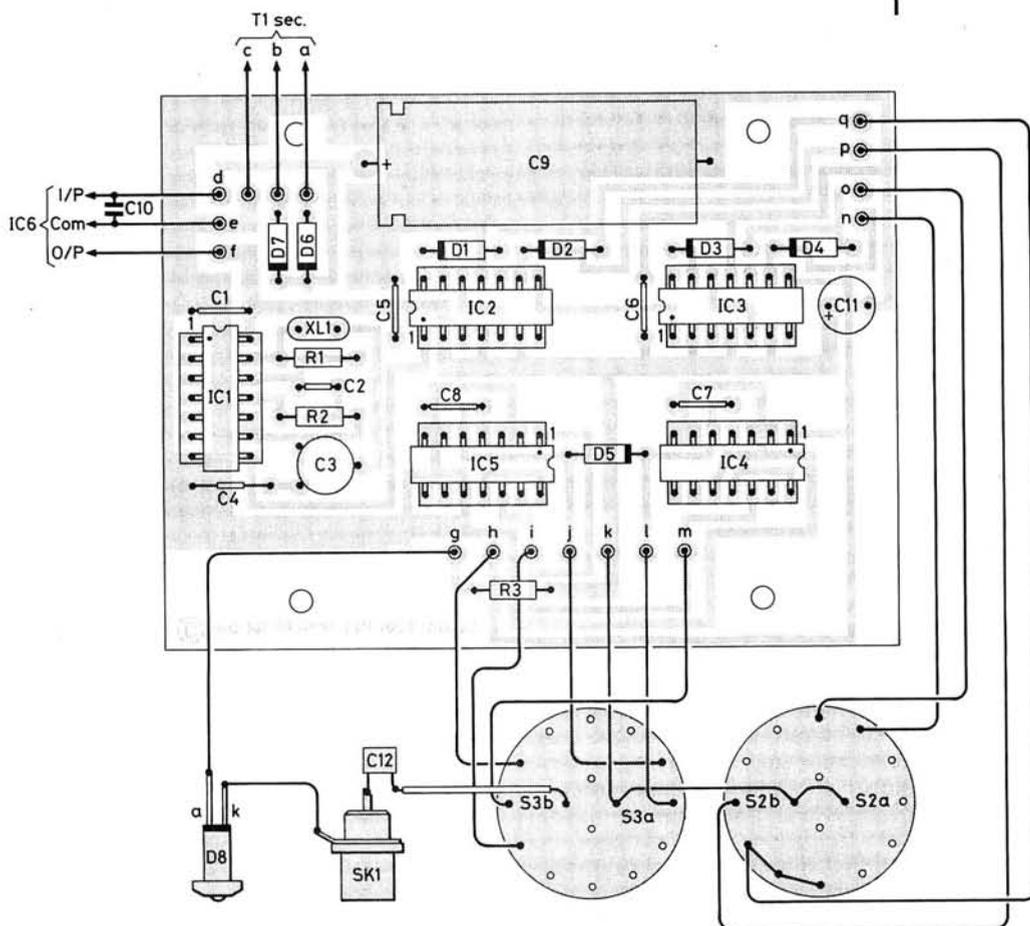

Although no fuse was fitted into the prototype chassis it is suggested that one be fitted where indicated. A 1 amp rating should prove suitable. The actual transformer connections will depend on the make used, the connections shown are for the RS 207-633. This transformer has the secondary connections along the bottom nearest to the chassis—mains connections are on the top and easy to touch, so be careful when working on the unit with the cover removed. The transformer is held in place by two

4BA screws and nuts, and is best fitted after the wiring to IC6 has been completed. Leave the wires connected to the p.c.b. long enough so that it can be lifted for service, should the need arise.

Testing

Once wiring is completed a final check should be made that all the components on the p.c.b. are inserted the correct way round.

★ components

Resistors

$\frac{1}{4}$ W 5% Carbon film

270 Ω	1	R3
1k Ω	2	R1, 2

Capacitors

Polyester

0.22 μ F	1	C10
--------------	---	-----

Ceramic disc

100pF	1	C4
10nF	2	C2, 12
0.1 μ F	5	C1, 5-8

Electrolytic single-ended

100 μ F (16V)	1	C11
-------------------	---	-----

Electrolytic double-ended

2200 μ F (25V)	1	C9
--------------------	---	----

Air spaced trimmer

60pF	1	C3
------	---	----

Semiconductors

Integrated circuits

7404	1	IC1
7473	2	IC2, 3
7490	2	IC4, 5
LM309K	1	IC6

Diodes

1N4148	5	D1-5
1N4001	2	D6, 7
TIL209	1	D8

Miscellaneous

6-0-6V 12VA transformer RS 207-633; 2p 5w midget wafer (S2a/b); 2p 3w midget wafer (S3a/b); d.p.s.t. miniature toggle (S1); Case 100 x 70 x 170mm; 4MHz Crystal HC18/U, load capacitance 30pF; BNC socket (1); Knobs (2); Fuse 20mm 1A with holder; Veropins and p.c.b; Integrated circuit d.i.l. sockets 14pin (5).

Before switching on disconnect the lead from the output of IC6 to terminal pin f. Switch on and check that the output voltage of IC6 is at 5 volts. The output from the rectifier diodes should be around 8 to 9 volts depending on the actual mains input voltage. If these voltages are correct, switch off and reconnect the lead to terminal pin f.

If an oscilloscope and/or frequency counter are available, connect the output of the calibrator to these and switch on. With both rotary switches fully anti-clockwise the output should be 250kHz and have a peak-to-peak amplitude of approximately 4.5 volts. Next switch S2 fully clockwise. The output frequency should now be 4MHz—adjust C3 for the exact frequency.

Check the frequencies on the other switch settings against the front panel markings (assuming a 4MHz crystal was used). The actual amplitude should be similar on all settings and show a square wave with a fast rise time. You may have to allow for the fall off in your oscilloscope if it has a limited bandwidth when checking the square wave shape at higher frequency outputs.

To check the calibrator without an oscilloscope or frequency counter a receiver covering the m.w. and if possible the l.w. is required. However, any receiver may be used providing you know the *actual* frequency of at least one station.

Using, for example, the BBC Radio 4 transmitter on 200kHz, couple the output of the calibrator to the receiver either by a two turn loop, if the receiver has a ferrite rod, or other suitable means. Only loose coupling will be required as the calibrator has a very high output. Using the 200kHz BBC signal, switch the calibrator to give marker pips every 200kHz. A low beat note should be heard. This beat will only be a few cycles per second or even minutes—adjust C3 for zero beat. It should be possible to set the frequency so that the beat drifts in and out of phase approximately once every few minutes. However, even if trimmer C3 is at one of its limits, the error is not likely to be more than around 0.2 per cent which is accurate enough for most practical jobs around the workshop.

If other stations on other frequencies are used for calibrating they should be stations with frequencies which are a multiple of one of the calibrator harmonics so that a beat can be obtained. As the calibrator has harmonics up into the u.h.f. range, stations in the v.h.f. f.m. band could also be used, or any known shortwave station. For example, WWV on 2.5, 5, 10MHz etc. Use the largest marker spacing which will provide a suitable harmonic and this will avoid error.

Calibrator Uses

At first the use of a 4MHz fundamental frequency may seem odd as most calibrators use a 1MHz or 100kHz source. However, there are very good reasons for the choice of this frequency. First, the crystal is available from several sources at very reasonable prices and second, this frequency provides harmonics covering the most useful range for calibrating receivers and test equipment.

For example, the v.h.f. f.m. band in the UK has channel spacings of 200kHz. This means that if you set the calibrator to give either 200 or 400kHz marker spacings you will be able to calibrate your f.m. receiver for either each channel or each alternative channel, depending on the length of your tuning scale. There will also be a marker available on 10.7MHz, a useful check on the i.f. frequency.

On a m.w. or l.w. receiver there are marker pips available every 10kHz which is suitable for calibrating these very accurately. As an example let us consider the calibration of an h.f. band receiver. Let us assume that we want to calibrate a band from 6.9MHz to 12.5MHz.

First, set the calibrator to give markers at 4MHz intervals. This will give two calibration points on the receiver,


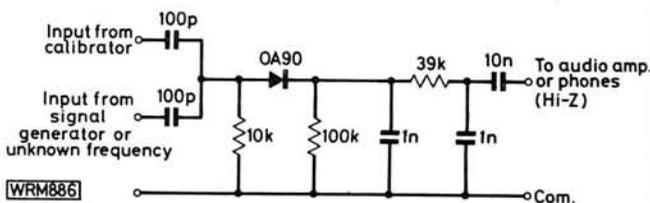


Fig. 4: Diode detector circuit suitable for beating the output from a signal generator with the Calibrator output. The generator should be tuned for zero beat at each calibration point required

one at 8MHz and the other at 12MHz. Having marked these on the tuning scale, switch the calibrator to give 1MHz pips and counting from the 8 and 12MHz markers, mark off each 1MHz point along the tuning scale. Then switch to give 100kHz markers and counting from each of the 1MHz marks already placed on the scale, mark off the 100kHz (or 0.1MHz) points. This procedure can be repeated for the 25, 10, 5, or 2.5kHz marker as required.

Always start with the widest marker spacing and identify these first. Then always count the other closer spaced marker pips from these. Taking our example, we would at first have a calibration point at 8 and 12MHz. Then we would add the 1MHz marks. Having done this we would have a point marked for 7MHz and 12MHz. With calibrator set for 100kHz marker spacing we would count down from 7MHz one marker pip which would be our required 6.9MHz. We would also count up from 12MHz for 5 of the 100kHz marker pips and this would give us our 12.5MHz. In this way we have set our band limits of 6.9 and 12.5MHz. Other frequency bands would be calibrated in a similar manner.

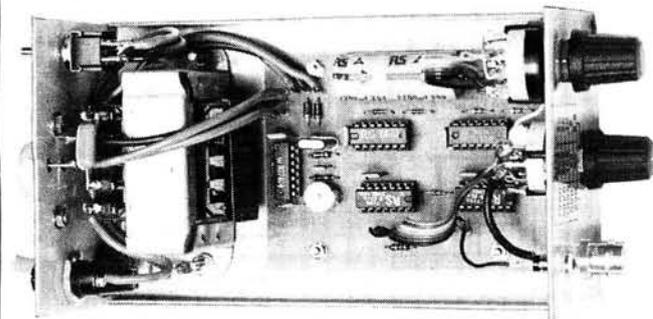

As we know the actual frequency coming from the calibrator on its fundamental frequency, at each setting of the switches, we must know how long each square wave pulse takes and this can be used to give precise timing pulses for calibrating (oscilloscope time bases etc.) test equipment.

For example, if we set the calibrator to give 10kHz markers, each square wave pulse will be exactly 100µs long. To find the time in microseconds simply divide 1 000 000 by the frequency.

As a further example, the 4MHz output will give square waves of $\frac{1\,000\,000}{4\,000\,000} = 0.25\mu\text{s}$

To calibrate a signal generator the output has to be mixed with the output from the calibrator so that the "beats" can be counted. The circuit in Fig. 4 shows a simple diode detector which should prove suitable for most applications. As when calibrating a receiver, start with the highest marker spacing and work down to the closer ones. However, be careful because with a generator it is possible to be misled by its harmonic output. For example, you may be trying to get a calibration point at 1MHz, but if the generator is set to 500kHz or even 250kHz the harmonics of these will also beat with the 1MHz marker. However, this could be checked by trying other combinations of frequencies. A 1MHz marker, for example, will not beat with the 250kHz output as strongly as the one which is correctly at 1MHz. In general the strongest "beat" is the correct one but it is possible to get exceptions.

There are many other uses that can be found for this digital calibrator, and these will become apparent as it is used around the workshop. In fact after a while you will wonder how you managed without such a device!

SENSITIVE CAPACITANCE METER

▶▶▶ continued from page 42

Supply

Either an external or internal 6-F22 (PP3) supply may be used, with automatic diode changeover between the two. If external, the voltage may be anything between 9V and 13V as the zener controls the generator output level. When the external supply voltage exceeds that of the battery, D1 prevents excessive current flowing into the battery, whilst the 220Ω resistor provides a "topping up" current and prolongs battery life. If the supply voltage is less than that of the battery, D2 prevents the battery current from flowing into the external circuit. Under these

circumstances the battery takes over. The total current drain is 5-6mA.

Astable Multivibrator

This uses half of a CD 40001 (or CD 4011) chip, unused gates being grounded, and a square wave output of approximately 6.8V peak-peak at about 12kHz is generated.

Digital Multimeters

The unit can be further modified to include a direct digital readout facility.

As most d.v.m.s include a 0-200mV range, it is a simple matter to include a divide by five network to reduce the 500mV output to 100mV. Using the 200mV range on the d.v.m. this gives a readout directly in picofarads. Readings down to unit values may easily be taken on the "HIGH" range, or, if greater accuracy is required, the "LOW" range may be used for values below 10pF, dividing the readout by ten of course.

It will be seen from Fig. 4 that the use of a simple changeover switch enables the one output socket to be used for both analogue or digital multimeters.

A small Veroboard panel carries the additional components and is fitted to the rear panel together with the changeover switch.

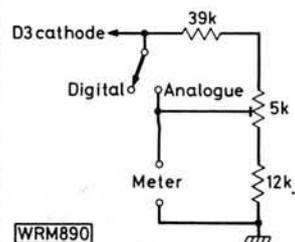


Fig. 4: Details of the digital/analog metering direct readout facility

Simple Wavemeter For 144 MHz

James A. Brett G6EBR

This article describes a simply made absorption wavemeter covering approximately 100 to 300MHz.

The amateur radio licence regulations require that a satisfactory method of frequency measurement is used to ensure that emissions are only within the amateur band being used. The Home Office have stated that with crystal controlled equipment this requirement can be satisfied by an absorption device of suitable range and accuracy to ensure that the correct harmonic of the crystal frequency is selected. They further state that the device must cover up to at least the second harmonic.

Design Principle

The principle of the absorption wavemeter is very simple. When a tuned circuit consisting of a coil and capacitor is placed in an r.f. field, maximum circulating current is induced when the circuit is tuned to resonance at the frequency of the r.f. field.

This circulating current produces a voltage across the coil, part of which is tapped off and rectified to produce a current to operate a meter indicator. By tapping off only a small portion of the voltage across the coil the damping effect on the tuned circuit, or reduction in *Q* factor, is quite small. The tuning of the wavemeter is quite sharp and certainly good enough to ensure selection of the correct harmonic of any crystal oscillator likely to be found in a 144MHz (2m) transmitter.

Construction

Exact dimensions of the mounting holes etc. will depend on the size of the components selected—layout is, however, important to ensure reliable results.

The variable capacitor C1 should be positioned as close to the inside edge of the plastics box as possible and the coil located adjacent to this side. This keeps the stray capacity to a minimum and ensures that the required range is covered.

The coil is wound with 1.5mm diameter bare copper wire on a smooth rod former, 9mm in diameter. With so few turns on the coil and by drilling only small holes to suit the wire gauge, the coil will be firm enough not to require any further fixing. A third hole is drilled through the enclosure wall to allow connection of the detector diode.

Calibration

This can easily be carried out using a Dip oscillator or reliable signal generator to establish the frequency coverage of the wavemeter. Care should be taken not to place the wavemeter too close to the Dip oscillator coil as the frequency of the oscillator can easily be "pulled".


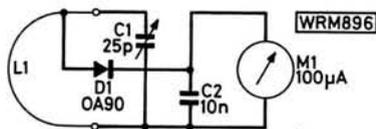
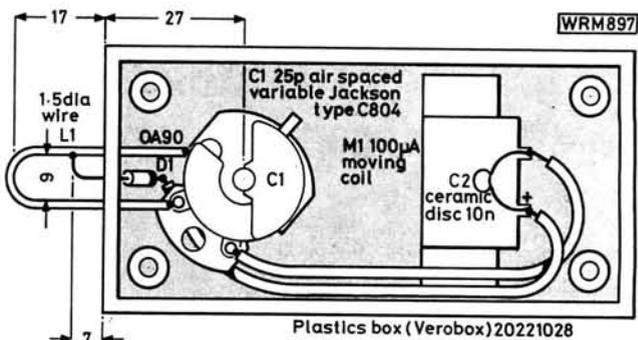


Fig. 1 (above): Shows the circuit diagram of the Simple 144MHz Wavemeter. The layout below shows the general arrangement of components built into the plastics enclosure. For reliable operation it is essential that the relative positions of L1, D1 and C1 are maintained

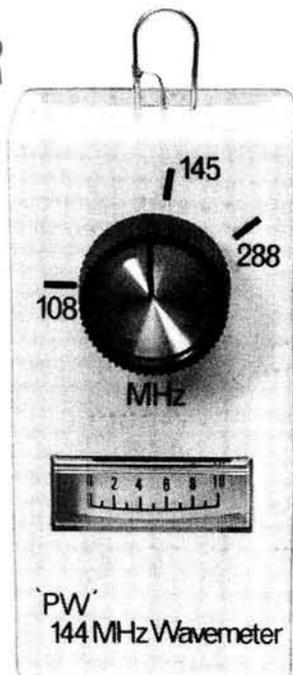

BUYING GUIDE

The Jackson capacitor used in this project is available from the following sources: Ambit International, Bi-Pak, Electrovalue and Maplin Electronic Supplies Ltd. All other components are readily obtainable from regular advertisers in this magazine

Approximate Price
£5.50

Construction Level
Beginner

Suitable frequency reference points can be marked onto a paper label. A light coat of varnish or even a covering of Sellotape will ensure permanence.

Unfortunately, not all Dip oscillators will go up to 292MHz, which is the second harmonic of the highest frequency of the 144MHz amateur band. The author, whose own Dip oscillator only covered up to 250MHz, found a convenient method of providing a reference signal at the second harmonic.

A 1W transceiver confirmed the 145MHz calibration point but produced no other indications, which is to be expected from a properly aligned device. When the

transceiver output was fed into an external 10W amplifier and the antenna tuner slightly off-set a small reading was obtained on the wavemeter. For this method to work the coil of the wavemeter needed to be placed in fairly close proximity to one of the coils of the tuner unit, which was operated with its covers off. The point on the dial was in the area expected, bearing in mind the 250MHz point already obtained from the Dip oscillator. No other response other than the large response at 145MHz was found. This point was therefore taken as a reliable calibration point for 292MHz. This technique should only be used in conjunction with low voltage/output p.a. devices. ●

General Purpose Buffer Amplifier

M.J. Darby

One of the most common requirements in the research laboratory, and also in many aspects of audio work, is a simple amplifier with a high input impedance and a fairly low output impedance which can act as a buffer between two circuits. A gain of about ten times is often useful, but sometimes one requires a gain of about unity. The amplifier should be able to deliver a reasonable output voltage without appreciable distortion and should have a fairly wide bandwidth so that it can be used at reasonably high frequencies.

Circuit

The simple two transistor circuit shown in Fig. 1 will satisfy these requirements and is very useful in many applications. The resistors R1 and R2 bias Tr1 via R3, the signal from the collector of Tr1 is fed to the base of Tr2. Negative feedback is applied from the potential divider in the collector circuit of Tr2 to the emitter of Tr1. The feedback raises the input impedance of the circuit and reduces the output impedance; in addition, it controls the gain.

At signal frequencies C3 effectively by-passes R6 so that R5 and R7 provide the negative feedback to the emitter. When output 1 is employed, the gain is $(1 + R7/R5)$ or about ten times (20dB) with the values shown. If a very

stable gain is required, metal film or metal oxide resistors may be used for R5 and R6.

This circuit was designed primarily for a gain of ten. However, output 2 is also available and provides a gain of about unity, but the impedance at this output is somewhat greater than that at output 1.

At very low frequencies, the full value of R6 becomes effective in the feedback loop and provides a low closed loop gain. This ensures that the quiescent output 1 potential is not far from the average of the two supply line potentials. Thus the working point is stabilised and this enables one to obtain a relatively high output voltage swing.

The transistor Tr1 should be a low noise, high gain, low current n.p.n. type such as the 2N929, 2N930, 2N484, C450, BFY77, BC109 or any similar type. A general purpose medium to low current p.n.p. transistor may be used for Tr2, suitable types being the 2N3702, 2N3703, 2N3905, 2N3906, V435, etc.

Performance

The input impedance of the circuit shown consists of a resistance of over 1MΩ in parallel with a capacitance of a few pF. The output impedance of pin 1 is less than 100Ω at frequencies up to the 100kHz region. The bandwidth extends from a few Hz to a few MHz at the -3dB points.


The maximum output voltage swing is obviously affected by the value of the power supply voltage used. The maximum peak-to-peak output voltage is normally well over half the power supply voltage used, but may be limited to a somewhat smaller value at frequencies over about 500 kHz. The power supply current is only of the order of 1mA.

The circuit is very suitable for use as a low noise amplifier. The noise increases with the input source resistance and with the bandwidth. The noise referred to the input is less than 50μV with a 100kΩ source impedance and about 10μV with a 1kΩ source impedance, both of these figures being for a 1MHz bandwidth.

Although simpler circuits can be made using integrated circuits, the resulting circuit will not normally have such a fast response or such a low noise level.

This circuit has been used mainly as a general purpose amplifier with oscilloscopes, etc. ●

Fig. 1: The circuit of a buffer amplifier having a high input impedance and a low output impedance together with two output voltage levels

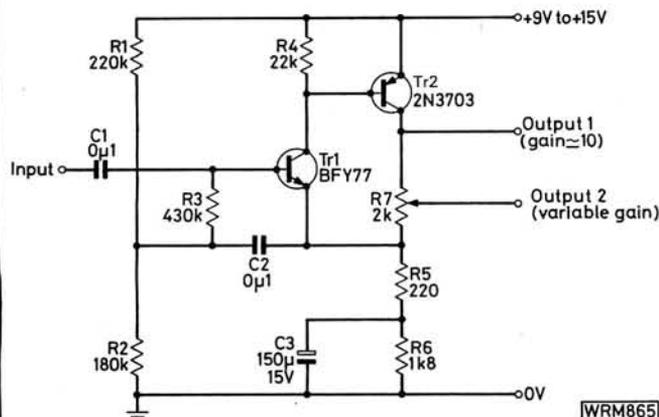

QRP SWR Bridge

Tony Smith G4FAI

Low power (QRP) operating is becoming increasingly popular nowadays on the amateur bands and offers the advantage that much of the equipment can be home-constructed in simplified form without the need for many of the precautions required when operating at higher power levels.

Opinion on what constitutes low power varies between different countries, and between different operators in those countries, but the G-QRP Club's definition—less than 5 watts input, and the (American) QRP Amateur Radio Club International's maximum of 5 watts output, are the sort of power levels referred to in this article.

Transmitters need to "see" a specified load, usually 50 or 75 ohms, at their output. Whether the antenna in use is already matched to the required impedance, or whether the match is obtained through an antenna tuning unit (a.t.u.), a standing wave ratio (s.w.r.) bridge enables the effect of the load on the transmitter to be monitored and adjusted as required (Fig. 1). Many modern transmitters automatically reduce their output power if a mismatch is presented by the antenna system, and the bridge is then a most useful device to assist in obtaining optimum performance at all times.

When a transmitter transfers power to a feeder line of the correct impedance, and the feeder terminates at an antenna also presenting the correct impedance, all of the power is taken and radiated by the antenna. When the antenna has the wrong impedance, i.e. the feeder is not correctly terminated, a portion of the power is reflected back down the feeder in the form of standing waves. The ratio between the forward power and the reflected power is the standing wave ratio, and the function of an s.w.r. bridge is to indicate that ratio at the point where the bridge is located in the feeder line.

The Circuit

The design shown in Fig. 2 is a simple unit for QRP operation on all authorised frequencies up to 30MHz, based on a toroidal transformer T1. The secondary winding of T1 samples a small amount of r.f. power (both forward and reflected) which is divided by the bridge circuit and rectified by diodes D1 and D2. Forward and


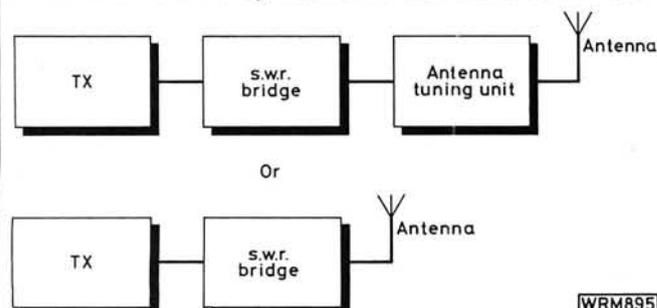


Fig. 1: Where to place the s.w.r. bridge—the length of feeder between the TX and the bridge should be as short as possible

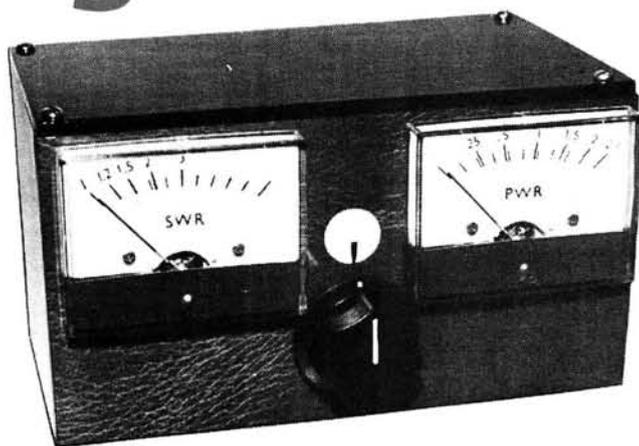

reflected readings are obtained simultaneously on the two meters M1 and M2, and the bridge is matched and balanced at the required load impedance by C1 and C2. Brief details are given in Fig. 5 of an alternative, less expensive, single meter version.

The bridge also measures forward power and, although it should not be regarded as a laboratory instrument, its accuracy should be sufficient for all practical purposes.

The project is housed in an easily constructed wood/hardboard case, partly to keep the cost down and partly to enable the constructor to have the satisfaction of creating a completely "home-brewed" unit. A metal case can be used if desired and the feed-through capacitors C4 and C5 would then no longer be required.

Construction

Details of the case can be seen in the photos. The main assembly is simply held together by nails and glue. Holes for the nails are pre-drilled, slightly undersize, to prevent the wood splitting. The front panel is secured by panel pins and glue and the top and rear panels are secured by woodscrews to facilitate access and setting-up.

In the prototype the nails and panel pins were punched below the surface level of the case and all gaps, holes, and irregularities made good with filler and rubbed down. The case, plus rear panel, was painted inside and out with matt black paint, and the top cover with black gloss. The front and sides were covered with Fablon after the meter holes had been cut out.

The holes for the meters were cut by marking the position of the meters on the front panel and drilling a series of small holes round the inside of the circle. The meter holes were then finished off with a half-round file. Exact details and measurements for meter and potentiometer mounting will depend on the particular meters obtained for the project.

Virtually any meters can be used having a 100µA linear full-scale deflection and these represent the main cost of the project. It is worth getting the best quality possible to ensure a long life in the meter mechanism. Those used in the prototype had a front face size of 60 × 45mm, a panel cut-out of 38mm diameter, and an accuracy of 2.5 per cent.

The components are mounted on Veroboard as shown

BUYING GUIDE

The components used for this project can be obtained from many of the advertisers in this magazine

Approximate Cost

£15

Construction Rating


BEGINNER

The trimmer capacitor on the side of the bridge showing a low reading (reflected power) should be adjusted to obtain the lowest possible reading. The connections to the sockets should then be reversed and the same adjustment made with the trimmer for the second meter. This procedure may have to be repeated once or twice until finally both meters, when indicating reflected power, read zero, and the bridge is then balanced. During this process the potentiometer should be adjusted so that whichever meter is indicating forward power is set at full-scale deflection.

Calibration—SWR

Either meter can be used for forward or reflected power indication, depending on which socket is used for input or output. For s.w.r. readings both meters are used and that showing forward power needs only to indicate f.s.d. For reflected power opinions differ on the need for detailed calibration. The most important marking is at a point exactly halfway across the scale which represents an s.w.r. of 3:1. Any s.w.r. in excess of that is undesirable, and in some cases may be detrimental to the TX in use. An s.w.r. of 2:1 is more acceptable, especially with low power, but overall with QRP working the aim should be to achieve a ratio of 1:1 which is a meter reading of zero.

In one sense, therefore, there is only a need for a centre marking to indicate maximum permissible s.w.r. whilst the aim is simply to get a minimum reading as near to zero as possible. More detailed calibrations are shown on the front cover providing an indication of intermediate ratios.

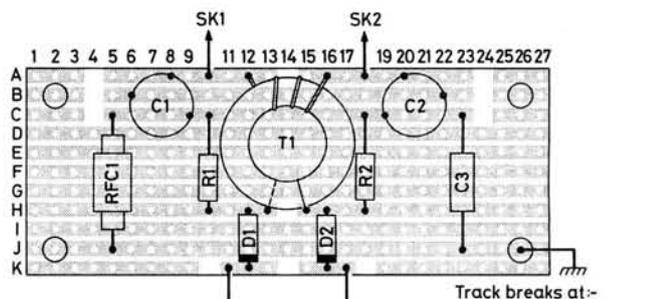


WRM891

Fig. 3: The component locations on the Veroboard; the mounting holes should be drilled very carefully to avoid damaging the board

A4,14,24
B4,24
C4,24
H14
K10,14,18

in Fig. 3. Matched diodes are required and a simple matching circuit is shown in Fig. 4. The circuit board is fitted on spacers inside a small aluminium box with 15mm woodscrews passing through the board, the spacers, the bottom of the box, and the earthing plate, into the floor of the case.

The input and output sockets are mounted at the rear of the box and holes need to be drilled in the rear panel of the case to allow access to the sockets. Phono sockets were used in the prototype, as these are frequently used for QRP operation, but any type can be fitted to suit the constructor's needs. Care must be taken when fitting the sockets to ensure that they do not prevent the lid fitting properly on the box. Similarly, the box must be fitted in the case leaving room for the lip of the lid between the box and the rear panel.

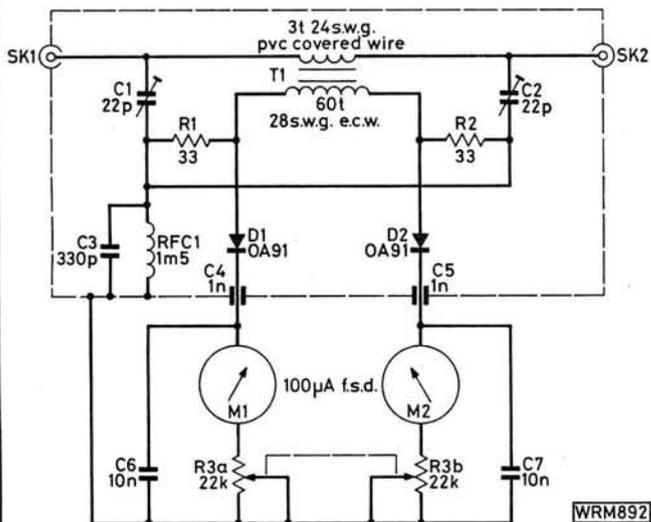

WRM892

Fig. 2: The circuit diagram of the QRP s.w.r. bridge

The connections to the meters are routed via feed-through capacitors, C4 and C5, which are intended to be soldered to chassis. As the box is aluminium this presents some difficulty. In the prototype holes were drilled in the box (making sure the lid was not obstructed) which were marginally smaller than the diameter of the capacitors. The holes were carefully enlarged with the tang of a small file until the capacitors could be secured with a press-tight fit and finally secured with a dab of "super-glue". This arrangement has proved quite satisfactory but purists might prefer to solder the capacitors to a small rectangle of tin plate and bolt the assembly to the side of the aluminium box. The wiring-up of the meters and the dual potentiometer should present no difficulty.

Setting-up

Once the unit is assembled the bridge needs to be balanced. This is achieved by connecting the TX to one of the rear sockets via a short length of coaxial cable having the same impedance as the TX output. A further length of the same cable connected to the other socket should be terminated by a non-inductive dummy load of the same impedance. This can be made up from one or more carbon resistors to obtain the resistance and wattage required.

If a radio-frequency (r.f.) carrier, at the highest frequency to be used, is now applied through the unit one meter should indicate a high, and the other a low, reading.

Calibration—Power

Forward power readings can also be obtained since the circuit provides a reasonably uniform indication of r.f. power, irrespective of frequency, over its range of operation.

Calibration does, unfortunately, require an external means of measuring r.f. power for comparison purposes, and the article on page 53 describes a simple wattmeter which will fulfil this function. Basically, for those already having access to r.f. measurement, the forward meter is set to f.s.d. when the desired maximum r.f. power passes through it into a dummy load. The setting of the pointer on the control knob is then noted, i.e., a mark is made on the front panel so that the setting can be returned to whenever power readings are required. With the control at this setting further, lower, r.f. powers are fed through the unit and the meter scale marked accordingly.

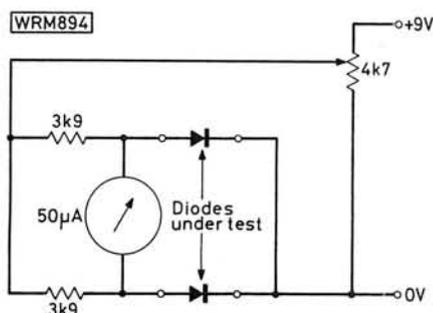



Fig. 4: A simple diode matching circuit. The two resistors should be matched with an ohmmeter. As the voltage is increased by rotating the potentiometer the meter should not deflect more than 1µA from its no-current setting. It may be necessary to test several diodes before a matched pair is obtained

Operation

The bridge should be connected to the TX as already described. The output can either be connected to an antenna via an a.t.u. or directly to a coaxially fed antenna.

Power is applied from the TX and the meters observed. An a.t.u., if used, should be adjusted to obtain minimum s.w.r., which in most cases should be 1:1. Care should be taken to ensure that the forward meter reads f.s.d. but the pointer should not be allowed to go further so that it is against the end-stop as this may damage the meter.

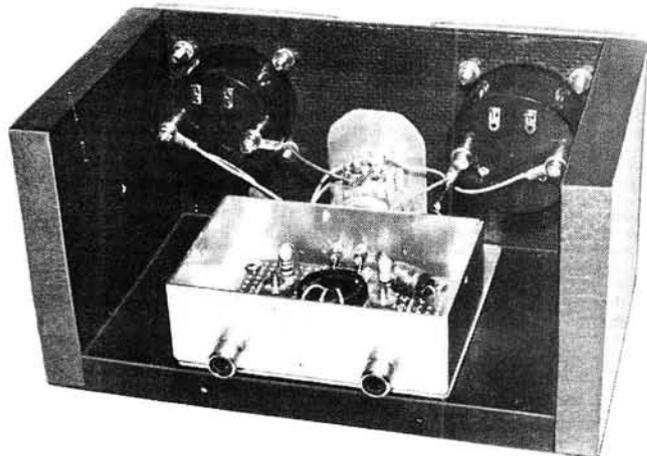If the bridge is connected directly to an antenna feed



line it will show the s.w.r. presented by the antenna system to the bridge without any immediate adjustment being possible. By checking the s.w.r. at different frequencies across a band it will, however, show the effective bandwidth of the system and indicate whether alterations to the dimensions of the antenna are necessary to bring it to resonance at a higher or lower frequency.

By leaving the bridge permanently in circuit the effect of the antenna system on the TX output can be constantly monitored and frequency changes effected quickly, es-

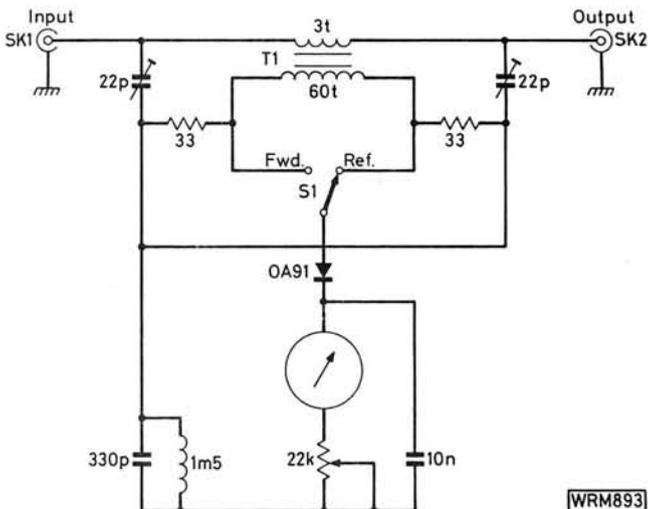


Fig. 5: A single meter version of the s.w.r. bridge

★ components

Resistors

Carbon film 1/4W 5%

33Ω 2 R1,2 (Matched, see text)

Potentiometers

Dual-ganged

22kΩ (Lin) 1 R3

Capacitors

Ceramic

10nF 2 C6,7

Feed-through

1nF 2 C4,5

Polystyrene

330pF 1 C3

Miniature trimmer

2-22pF 2 C1,2

Semiconductors

Diode

OA91 2 D1,2 (Matched, see text)

Miscellaneous

Meter 100µA f.s.d. (2); RF Choke 1.5mH (1); Toroidal core T68-2 (1); Veroboard 0.1 inch matrix 24 holes x 10 tracks; Metal box 73 x 51 x 25mm; Phono sockets (2); Pointer knob; Enamelled copper wire 28 s.w.g. (1.3m); Insulated wire 24 s.w.g. (100mm).

pecially when an a.t.u. or alternative antennas are in use. It should be borne in mind, however, that a satisfactory s.w.r. indication on the meter does not necessarily mean that an antenna is performing well. The s.w.r. is measured only at the point in the feed line where the bridge is located and not (usually) at the antenna itself. A dummy load illustrates this point. It can present an s.w.r. of 1:1 through a matching feeder and yet be virtually non-radiating.

With an effective antenna the bridge is invaluable, but its only constant function is to give warning if too high an s.w.r. is presented to the TX output terminals.

An s.w.r. bridge is a valuable part of every radio operator's station. It is a useful tool when constructing antennas and exercises an essential control function when

they are in use. Because of its simplicity it is an ideal project for home construction, especially for beginners, and with good quality components it will last for years. QRP operation itself offers enormous scope for home construction and experimentation and a unit such as this should be an integral part of every QRP station.

Warning


The unit as described is suitable only for low power operation. The circuit is capable of operation up to about 100 watts but different components, and a different form of construction, would be required to take account of the higher power requirements. ●

QRP RF Wattmeter

Tony Smith G4FAI

Measurement of r.f. power is often thought to be difficult or expensive. This is a simple project which contradicts both assumptions, provided meters or multimeters and a d.c. power supply are readily available, as is quite likely in the average radio amateur's shack. It is described in its basic form and also in a slightly more exotic version having variable instead of fixed components to permit experimentation and greater flexibility in use.

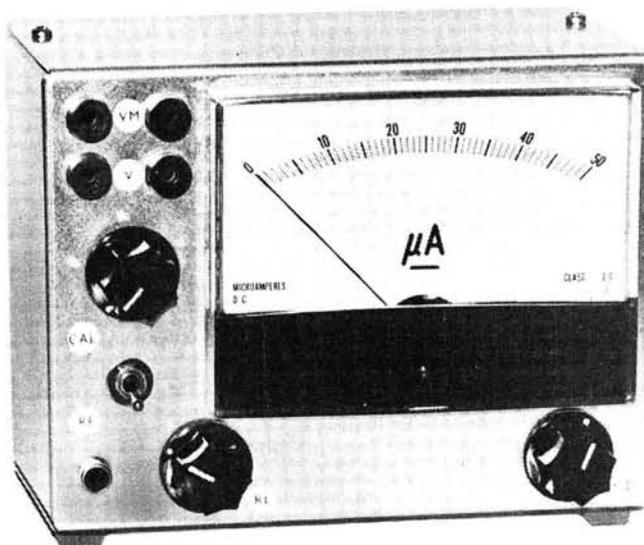As described it is intended for QRP (low power) measurement but higher powers can be measured by using more substantial components and a higher voltage source.



Basic Circuit

When r.f. is applied across R1 (Fig. 1) the a.c. peak voltage developed is rectified by diode D1 and this charges capacitor C1 to the same peak voltage.

The voltage activates meter M1 which has previously been calibrated in watts by the application of volts d.c. via S1 as explained later. R1 is, in effect, a dummy load of 50 ohms capable of dissipating the power to be measured. As an example, 3 × 150 ohms 1 watt non-inductive resistors in parallel would provide a 50 ohm, 3 watt, load.

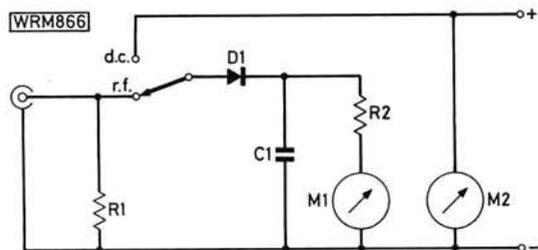


Fig. 1: The basic circuit

Meter M1 can be external to, or built into, the unit. A 50–100μA meter is required, or a multimeter set to the appropriate range. R2 is a series resistor, the value of which is calculated to permit full scale deflection (f.s.d.) of the meter at the maximum voltage to be used for calibration.

Meter M2 is an external voltmeter or multimeter for measuring the applied voltages used in the calibration calculations. The voltage supply must be variable in order to calibrate different power levels. If only a fixed voltage supply is available the circuit can be adapted to provide a variable supply.

Calibration

Resistor R2 is required to set the meter (M1) at f.s.d. for the maximum power to be measured. The calibrating voltage E for this power can be obtained from:

$$E = \sqrt{2RW}$$

where W is the power to be equated to volts and R the value of R1. If, for example, W = 2.5 watts and R = 50 ohms then

$$E = \sqrt{2.5 \times 100} = 15.81 \text{ volts}$$

The series resistance R2 can now be calculated using Ohm's Law:

$$R = E/I$$

where E is the voltage required to give f.s.d. and I is the sensitivity of the meter, say 50μA.

$$R = \frac{15.81}{5 \times 10^{-6}} = 316\,200 \text{ ohms}$$

A series resistor of this value will, therefore, result in f.s.d. on the meter when 15.81 volts d.c. is applied via S1. If S1 is switched to r.f. an applied r.f. power of 2.5 watts will also result in f.s.d.

Calibration for lower powers can be made by use of the same formula, $E = \sqrt{2RW}$, and this is all that is necessary if the wattmeter is to be used for one power range only, e.g., 0-2.5 watts.

Alternatively using $W = E^2/2R$ enables any given calibration voltage to be equated to r.f. power.

Variations

If R1 could be made adjustable this would enable an exact resistance value to be selected for the load. It would also permit the output impedance of a transmitter to be checked by adjusting the load, and subsequently measuring its value, to obtain minimum indication on an s.w.r. bridge.

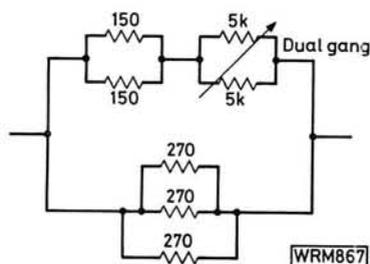


Fig. 2: A variable QRP load

A method of obtaining a variable QRP load is shown in Fig. 2. The limiting factor is the power rating of the potentiometer used with the fixed resistors. Standard potentiometers are usually rated about 0.5-1 watt with linear progression but only half that if logarithmic. A constructor intending to try this arrangement should check the power rating of the component to be used with the supplier. In the example shown a 1 watt dual potentiometer is used with the gangs in parallel to give a rating of 2 watts which, in the circuit given, will provide a variable load from approximately 40 to 85 ohms with a conservative dissipation of 3 watts.

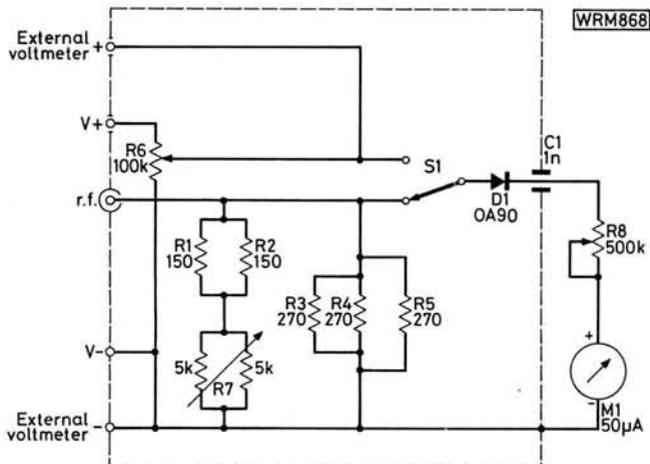


Fig. 3: The circuit diagram of the prototype. Note that C1 is now a feed-through capacitor providing r.f. isolation for M1 as an additional function

Another useful variation is to make R2 adjustable. This enables instant achievement of meter f.s.d. if different power ranges are to be used, simply by substituting a 500kΩ linear potentiometer for R2.

If a variable power supply is not available a fixed supply can be used across a 100kΩ linear potentiometer with the slider providing the variable voltage required, and also the point where the voltage can be measured.

A prototype was made up incorporating the variations discussed and the circuit is shown in Fig. 3.

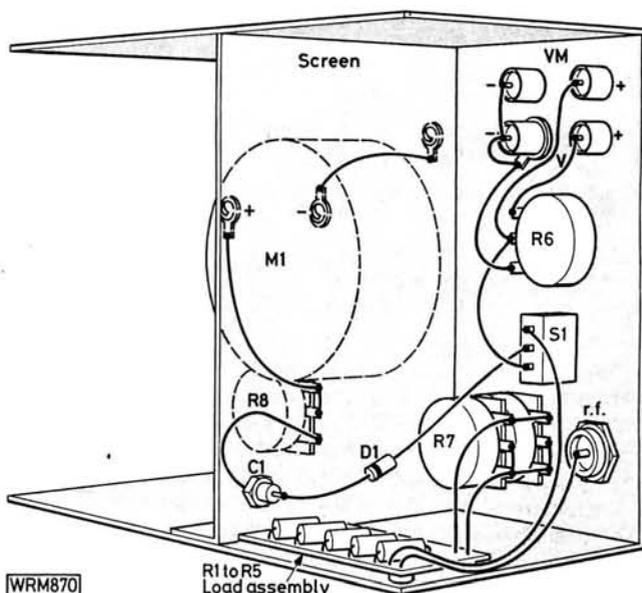


Fig. 4: A cutaway internal view of the prototype. Note the voltage input earthing tag is taken from the phono socket and carefully enlarged to fit the thread of the wander plug socket. The feed-through capacitor is soldered to a washer or piece of tinplate which is then bolted to the dividing screen

Construction

The unit is housed in a standard aluminium box. Layout of the prototype is given in Fig. 4. An extra large faced meter was used in order to obtain a clearly numbered and divided scale. No attempt was made to calibrate the meter

BUYING GUIDE

All the components used in this project are readily available from advertisers in this magazine

Approximate Cost

£7.50

Construction Rating

BEGINNER

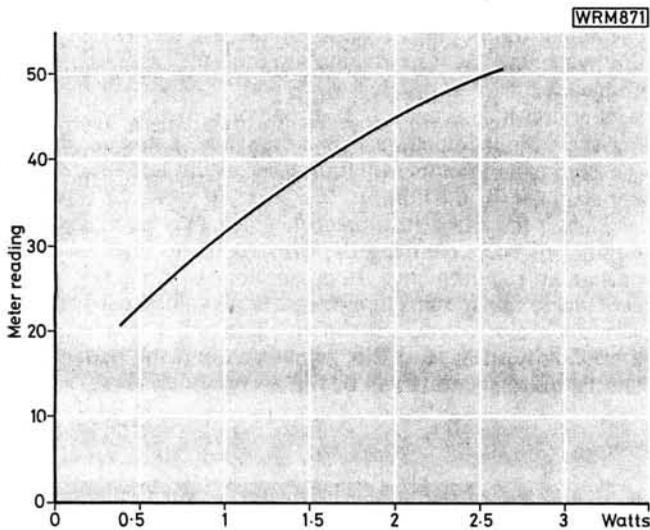


Fig. 5

since it was decided to make up tables and graphs for various power ranges to be read off from the existing 0-50 scale (Fig. 5). Three pairs of connecting leads were made up—for the calibrating power supply; the external voltmeter; and for measuring the load resistance via the r.f. input socket. The final terminations of these leads depend on the meters and power supply to be used.

As described there is a certain amount of simple metal work required, holes to be drilled, a slight cutting away of part of the case to clear the components mounted at the front, and a dividing plate fitted internally to provide r.f. isolation between the meter and the load. A larger case, or smaller meter, would simplify this process. The fixed resistance dummy load assembly is shown in Fig. 6; it should be mounted at the bottom of the case via two spacers as shown in Fig. 4.

Calibration Procedure

- 1) Decide on the range required.
- 2) Calculate the calibration voltage for maximum and intermediate power as described in the section on Calibration. Note the powers and corresponding voltages on the chart—see Fig. 5 for an example.
- 3) Turn CAL and FSD controls fully anti-clockwise.
- 4) Switch to CAL and connect the power supply and external voltmeter (M2) via the appropriate sockets.
- 5) Advance CAL control until M2 indicates the desired maximum voltage.
- 6) Adjust the FSD control for full scale deflection on M1.
- 7) Note the meter (M1) reading and the chart against the voltage.
- 8) Reduce the CAL control to the next lowest voltage and note the scale reading as before.
- 9) Continue with consecutively lower powers.
- 10) Draw the graph using the data obtained.
- 11) Switch to RF. Connect the unit to the transmitter. Use the meter indication and graph to read off the power in watts.
- 12) If graphs are prepared for other ranges, repeat processes 3) to 6) before using the unit for any particular range.

W	2.5	2	1.5	1	0.5
E	15.81	14.14	12.25	10.00	7.07
Meter Reading	50	45	39	32.5	23

Example: 0.5—2.5W range into 50Ω load using formula $E = \sqrt{2RW}$

★ components

Resistors

Carbon 1W

150Ω	2	R1,2
270Ω	3	R3,4,5

Potentiometers

Dual-ganged

5kΩ + 5kΩ (lin)	1	R7
-----------------	---	----

Single

100kΩ (lin)	1	R6
500kΩ (lin)	1	R8

Capacitors

Feed-through

1nF	1	C1
-----	---	----

Semiconductors

Diodes

OA90	1	D1
------	---	----

Miscellaneous

Meter 50μA f.s.d.; Socket (see text); Wander plugs and sockets red (2), black (2); Miniature toggle switch s.p.d.t.; Case 152 × 114 × 76mm Maplin AB31; Veroboard 0.1inch matrix 24 holes × 10 tracks; Spacers 6BA × 6.5mm (2); Nuts, washers and screws 6BA × 12mm (5); Solder tag 6BA (1), Aluminium sheet 130 × 90mm.

Uses

The most obvious use of the unit is to measure the output power of a QRP transmitter into a given load. The load is usually the stated output impedance of the transmitter, but equally it could be the known impedance of a particular antenna. One fascinating application is to use the wattmeter to set the transmitter output to, say, 100mW and see how far it is possible to work with that level of power.

The unit can be used to calibrate the forward power of an s.w.r. bridge of the type described elsewhere in this issue. When varying levels of r.f. power are applied through the bridge to the wattmeter the readings from the latter can be noted and used to calibrate the scale of the bridge using the needle of the s.w.r. meter as a marker. To obtain reasonable accuracy the bridge should be balanced against the same load impedance as the wattmeter before calibration.

If an a.t.u. is used with the transmitter, comparisons can be made between power delivered direct to the wattmeter and via the a.t.u. This may reveal power losses through the a.t.u. which can be minimised by experimenting with other a.t.u. settings.

In construction or adjustment work the meter can be used to compare output power with d.c. input to the out-

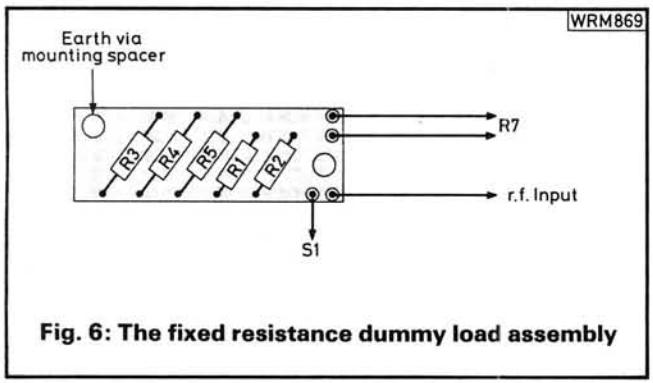


Fig. 6: The fixed resistance dummy load assembly

put stage. With QRP working the efficiency of this stage can make the difference between success and failure, and the wattmeter is an invaluable tool for assessing this efficiency.

Mention has already been made of a method of checking the output impedance of a transmitter and no doubt the keen experimenter will find other useful and interesting applications for the unit.

This is an interesting project which can be made in a number of ways enabling the constructor to meet his own particular requirements. It is possible to obtain ± 5 per cent accuracy if the components and values used in the formula are measured accurately. The meters should have a sensitivity of at least 20k ohms/volt and the better they are the more accurate will be the power indication.

Letters

SWL Souvenirs

Sir: In reply to the letter "Long Time Short Wave Listener" in the August issue. I would like to add that, I am also 64 years of age and have been interested in s.w. radio the same length of time as Mr Jenkins.


I still have my old B.L.D.L.C. Badge No. 5409 and a Log Book of the same period, together with my British Short Wave League and Short Wave League (USA) badges. I also have another badge which I doubt if anyone else has, and that is the G5IT Radio Circle Badge. This was a BBC station which, unfortunately I cannot remember where the station was.

Mr Jenkins mentions QSL cards for W2XAD and W2XAF—in addition I have W2XE, W3XAL, Radio Tokyo, Radio Hungary HAT, CMCM/COCM Havana Cuba, W1XAL, VK2ME and many amateur station cards of the same period.

My original receiver was an Eddystone Short Wave 4 t.r.f. receiver—battery powered, then the Eddystone Short Wave Converter which I fed into an early Marconi 4-valve superhet.

My old RSGB number was BRS3656, which I can still remember.

*Tom Bingham
Reading, Berks.*

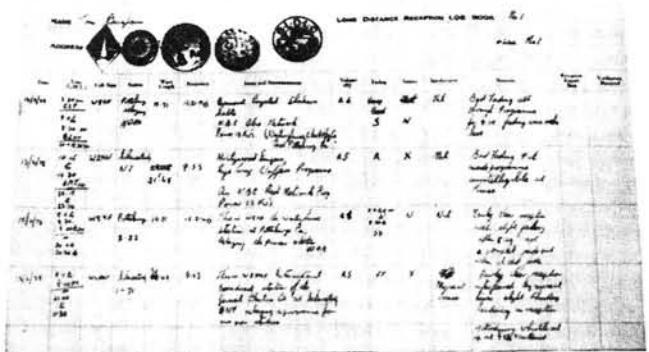

Sir: As a regular reader since the first issue of PW I was very interested to read in the August issue Letters "Long Time SWL" from A. J. Jenkins, with his reference to the B.L.D.L.C.

I too was a member, but unlike him I have both my badge and certificate. The latter is dated 13 October 1937, registered No. 3961 and it is signed by "Thermion". I also listened to W2XAD and W3XAF, although my main pastime was trying to copy the amateurs on 14MHz c.w. A lot of water has gone under the bridge since these days, and I look back on them as being happy days, in spite of the simple receivers, 0-V-1 etc. I doubt if the youngsters of today will ever see their like.

Now aged 66, I started listening to the amateurs in 1931 and I'm still as interested as I was then.

*B. J. Clark G3BEC
Yeovil*

Sir: Reference the letter from Mr A. J. Jenkins of West Molesey, Surrey and concerning the B.L.D.L.C. Although at that time the holder of a Post Office artificial aerial transmitter licence under the callsign 2BCX, I too was a member of the B.L.D.L.C. and a keen s.w.l.

I retained both the badge and certificate of membership for many years, but these no longer exist. However, Mr Jenkins will be aware that at least one member, or ex-member, is still alive and active if only from the number of articles that have and are still being published in PW under my name and callsign. Now, of course, the callsign has the prefix G.

I wonder if Mr Jenkins has the impression that both amateur radio and short wave listening was taken much more seriously then than it is now? Anyway 73 from Mr. J to Mr. J.

*F. C. Judd G2BCX
Cantley, Norfolk*

Sir: Taking up Mr Jenkins challenge, I write to say that not only have I still got my B.L.D.L.C. Badge but a clean certificate No. 5768 issued 12.1.38

After using the short wave listening as a training ground I have been licensed for over 30 years and still enjoy the hobby very much.

Talk of W2XAD etc. does bring back very pleasant memories of my youth.

*Jack Brooker MBE G3JMB
Haywards Heath, W. Sussex*



ELECTRONIC HOBBIES FAIR

Alexandra Palace, London – October 27-30, 1983

We are sorry to announce the cancellation of this year's Electronic Hobbies Fair, planned for 27th–30th October.

In spite of a significant success last year, the continuing recession is hitting the electronics hobby industry pretty hard. This has meant that many companies feel that this year they cannot sensibly allocate the resources of time, money and manpower involved in participation in exhibitions.

We feel that any exhibition sponsored by *PW* must offer the visitor a full range of components, equipment, projects and demonstrations from a wide selection of companies across the industry. As we cannot be absolutely sure of doing just this, we have decided, with regret, that we must disappoint our readers now rather than in October. *Practical Wireless* would like to thank those companies who had undertaken to support the Electronic Hobbies Fair this year. With our apologies for the disruption of their plans we combine our hopes for a future event in a more buoyant business climate.

Every month is the right frequency

When you're building a major project from a *PW* design, you want to be sure of getting every issue in sequence! Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (incl. p & p) U.K. £13.00 and Overseas £14.00. Airmail rates for overseas subscriptions can be quoted on request.



Practical Wireless SUBSCRIPTION ORDER FORM

Please send me *Practical Wireless* each month for one year. I enclose a Sterling cheque/international money order for..... (amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss _____

ADDRESS _____

POSTCODE _____

Make your crossed cheque/MO payable to IPC Magazines Ltd., and post to: *Practical Wireless*, Room 2613, King's Reach Tower, Stamford Street, London SE1 9LS.



Part 8 of this series dealt with multi-band vertical and ground plane antenna systems. This month the topic is the stacking and baying of v.h.f./u.h.f. arrays.

Antenna systems consisting of a number of dipoles each having r.f. power applied simultaneously, are known as "active arrays" and the dipole elements may be *stacked*, one above the other, or *bayed* side by side in line with each other as shown in Fig. 9.1. This illustration also shows how stacking and baying may be combined in what are usually known as "colinear arrays" although the directivity and gain of all active arrays depends ultimately on the phase relationship of the currents flowing in all the elements.

Multi-element active colinear arrays are rarely used for amateur radio applications because they are too large. However the simple colinear antenna consisting of up to four vertically stacked dipoles, is commonly used for v.h.f. and u.h.f. omni-directional operation and has the advantage of a small amount of gain over a single dipole. Active antenna arrays of this nature may be orientated to provide either horizontally or vertically polarised radiation.

There are two main requirements when constructing arrays of this nature. The first is accurate matching between the transmission line sections used to couple the elements and also between these and the main feed line from the transmitter. Secondly, all elements must be driven in the correct phase relationship with each other to obtain whatever directivity and gain the array has been designed to provide.

Parasitic Beam Antennas

Parasitic beams are in some respect phased arrays of $\lambda/2$ elements except that the "passive" elements (reflector and directors) are powered by mutual coupling. Correct phasing of the currents in each element is determined by the spacing between them. Complete beam antennas of this nature can however be stacked, bayed or both, and driven in phase with each other to achieve greater effective gain than would be obtained by a single beam. *This technique does not, as many suppose, provide twice the dB gain figure quoted for a single beam—far from it in fact.* For example, if a beam has a quoted gain of 10dB, then stacking another identical beam with it will **not** provide a total

gain of 20dB. The theoretical gain obtained from stacking (or baying) two identical beams is 3dB ($\times 2$). Even this cannot always be achieved because of losses due to mutual coupling and imperfect phasing.


Cost Versus Extra Gain

It is worth considering whether that extra 3dB gain really warrants the cost of using two antennas which in turn create extra weight and offer higher windage and thus more strain on the rotator and support mast. In addition other items such as matching devices and connectors are also required.

It could prove much less costly and more convenient to use a single beam but with a higher gain. If I may quote an example, the 12-element ZL Special beam for 144MHz and fairly well known to *PW* readers, has a gain of approximately 13dBd. To obtain another 3dB by stacking a pair means a complete additional antenna and therefore twice the cost. The G2BCX 16-element 144MHz beam, also featured in *PW*, not only gives that extra 3dB (gain 16dBd) but costs relatively little more to make than a single 12-element ZL Special and is not that much longer either.

Antenna Gain and ERP

Whilst two identical stacked beams will theoretically provide twice the radiated power otherwise obtained from a single antenna, it is worth considering the *effective radiated power* (e.r.p.) obtainable with various degrees of antenna gain and different levels of power from the transmitter. As an example consider an antenna with a gain of 12dBd, that is 12dB over a single $\lambda/2$ dipole, and a transmitter delivering 10 watts of r.f. power. Assuming no loss in the feed cable, due to even a small amount of

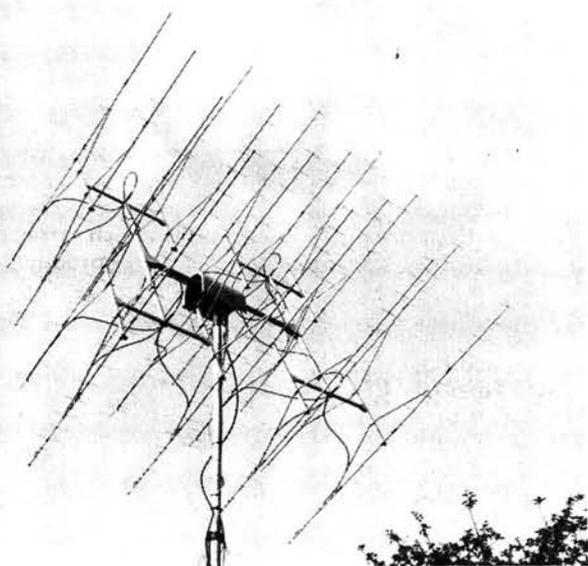

A very impressive array of stacked and bayed antennas! This system, which is fully steerable for 432MHz e.m.e. operations, consists of sixteen 21-element Tonna Yagis

Random Electronics

Practical Wireless, October 1983

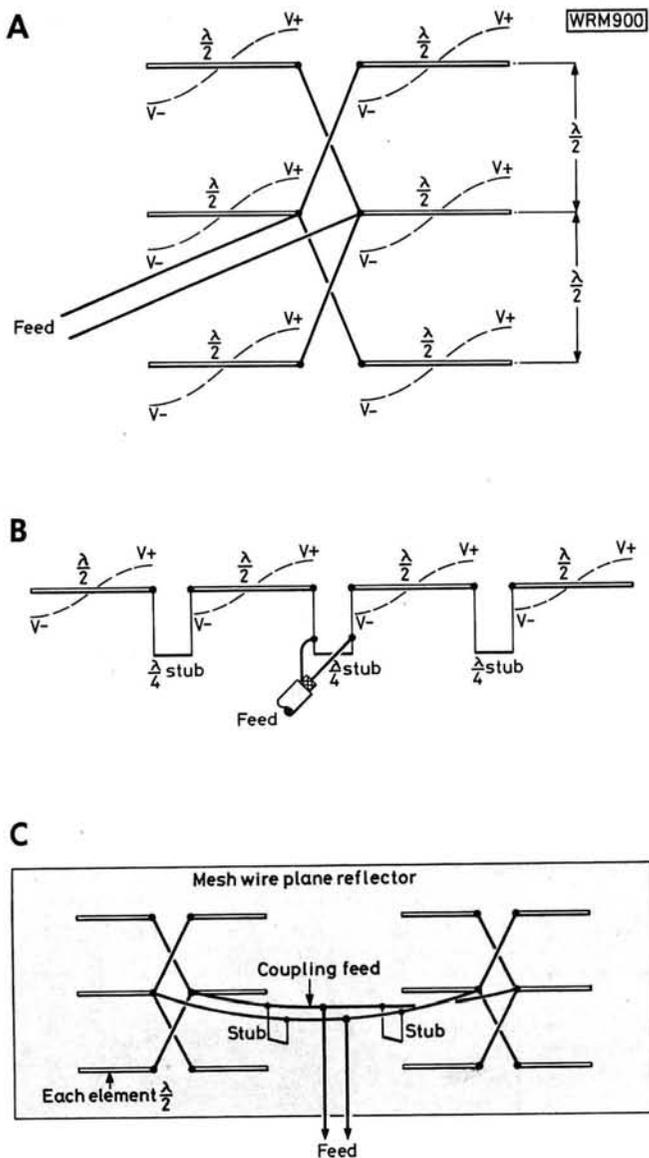


Fig. 9.1: (A) Six $\lambda/2$ stacked antennas each driven in phase—an active or colinear curtain array. Dotted lines show in-phase voltage in each element. (B) Four $\lambda/2$ elements bayed (end-to-end) and fed in-phase via $\lambda/4$ stubs. A colinear array of this nature is often used vertically for omni-directional radiation. (C) Two arrays, similar to (A), stacked and bayed with each element driven in-phase. Complex matching systems are usual with arrays of this nature. Such arrays are usually backed by a plane reflector to produce high forward gain

v.s.w.r. and no losses in the antenna itself, in other words assume that all the power supplied to the antenna is radiated, with 10 watts fed to a dipole the power radiated will be 10 watts. With the beam antenna with its gain of 12dBd, the real power gain is 15.85 which means that with 10 watts fed to the antenna the effective radiated power will be $10 \times 15.85 = 158.5$ watts. If, on the other hand, we purchase another identical beam and stack both to obtain the theoretical 3dB extra gain, what will be the e.r.p.? The gain of the stacked pair will be $12 + 3 = 15$ dBd which is a real power gain of 31.62. The e.r.p. will be 10×31.62 or 316.2 watts.

Instead of an extra beam and phasing harness etc. we might consider using a small linear amplifier, with say 50

watts output. With the same single beam and its real gain of 12dBd, the e.r.p. with the linear in use would be $50 \times 15.85 = 792$ watts. Another antenna would no doubt be less costly than a linear amplifier (and power unit) but it may be a case of which is the most convenient.

One other example—a beam antenna with a gain of say 16dBd. The real power gain is 39.81 so with 10 watts the e.r.p. would be 398.1 watts. A power of 25 watts to the antenna would yield 995.25 watts and with 50 watts the e.r.p. would be 1990.5 or nearly 2kW!

On the other hand what would be possible with a 16dBd gain pair, stacked and using a linear amplifier with 100 watts output? Gain from the stacked pair gives $16 + 3 = 19$ dBd, power gain 79.43. Total radiated power: $100 \times 79.43 = 7943$ watts (7.943kW). So perhaps it really amounts to how much radiated power you require, the cost involved and possible objections from neighbours or local planning authorities.

The photograph on page 58 is of a 432MHz moon bounce (e.m.e.) antenna system consisting of 16×21 element Tonna beams giving a total gain of 30dBi (isotropic) or 27.85dBd giving a power gain of 610. With 100 watts input to the system the e.r.p. would be in the region of 61 000 watts (61kW). The beamwidth of this array is about 5 degrees!

Combination Stacked or Hybrid Beams

Before considering the stacking and/or baying of quite separate but identical beam antennas, it may be worth considering antennas employing the skeleton slot principle of driving a stacked system of directors and reflector i.e. two antennas in one assembly. Of these there are the Jaybeam Ltd D5/2M and D8/2M—both are for operation on 144MHz. The D5/2M has a quoted gain of 10dBd and the D8/2M 11.1dBd.

For the 432MHz band there are the D8/70 which has a gain of 12.3dBd, the MBM48/70 with a gain of 14dBd and the MBM88/70 with a gain of 18.5dBi (isotropic) or 16.35dBd. The D8/70 is a skeleton slot type, similar to its 144MHz counterpart, whilst the others employ a square loop driven element and reflector with crossover phased directors which although not strictly stacked systems, do offer a considerable amount of gain.

General Principles—Stacked and Bayed Antennas

The separation distance between two antennas stacked (one above the other) or bayed (side by side) can be between 1 and 2.5λ at the frequency of operation but should not be less than λ . Closer spacing increases the mutual coupling between the antennas resulting in reduced gain and a wider than normal beamwidth. The recommended minimum is 1.5λ . However, when antennas are stacked the vertical beamwidth is narrowed but the horizontal, or azimuthal, beamwidth remains the same as for a single antenna. When a pair are bayed the horizontal beamwidth becomes narrower but the vertical beamwidth remains the same.

The length and impedance of phasing lines used to couple a stacked or bayed pair depends on the feed impedance of the antennas themselves and the spacing between them. A basic example is shown in Fig. 9.2 (A) in which a pair of folded dipoles are stacked one wavelength apart. The section of open wire line coupling the pair may be of any impedance, say 300 or 400 Ω , but because the antennas are connected in parallel by the open line, the feed impedance at the centre is halved. This is the same as connect-

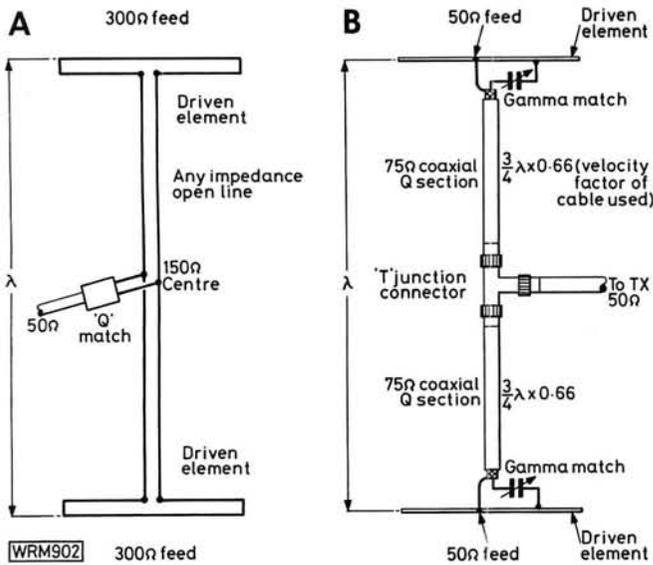


Fig. 9.2: (A) Two stacked folded dipoles fed in-phase via an open line (see text). (B) Two gamma matched dipoles with 50Ω feed impedance, phased by a pair of 75Ω "Q" sections of coaxial cable

ing two pure resistors of equal value in parallel, the resultant total resistance being halved. To match this system to a 50Ω coaxial feed a $\lambda/4$ line transformer would be required.

Next we come to an arrangement more in keeping with the now commonly used 50Ω transmitter output and antennas with an input impedance also of 50Ω, including of course the use of coaxial cable of the same impedance to couple one to the other. The example shown in Fig. 9.2 (B) consists of a pair of dipoles with a gamma match to provide a 50Ω feed impedance. The phasing harness consists of two "Q" sections each of 75Ω, the length of each line being an odd number of $\lambda/4$ sections, in this case three. The actual physical length of each is determined by the velocity factor of the cable. If the example shown was required for operation on 145MHz each of the 75Ω "Q" sections would be $2.06 \times 0.75 \times 0.66 = 1.02$ metres in length (0.66 is an average cable velocity factor).

This method can also be applied to a stacked pair of Yagi type beam antennas providing the feed impedance of

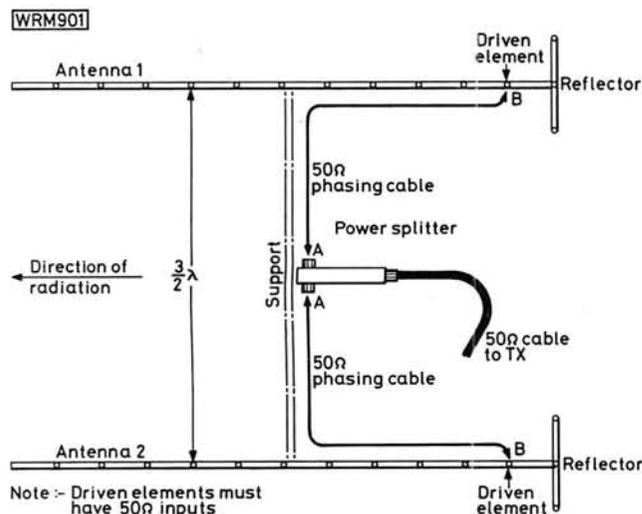


Fig. 9.3: A pair of beam antennas stacked $3\lambda/2$ apart phased and fed via a two-way power splitter and phasing lines an equal number of $\lambda/2$ multiples long

each is 50Ω. For wider spacing between the antennas e.g. 1.5λ , each "Q" section line would need to be longer, in this case 1.25λ . So for operation on 144MHz the "Q" line lengths would now be $2.06 \times 1.25 \times 0.66 = 1.7$ metres. This is once again assuming a cable velocity factor of 0.66. With some cables this may be higher and must be taken into account when determining the length of coaxial cable used for phasing lines. It is important not to make these lines unnecessarily long, particularly at u.h.f., so it is a case of using the minimum number of odd $\lambda/4$ lengths consistent with the physical length required for the spacing between the antennas and the most convenient routing of the cables themselves.

It should be noted that ready built phasing harnesses made by Jaybeam Ltd are available from most large dealers, and can be obtained for two or four antenna systems. These harnesses can be used with antennas having an input impedance of 50 or 75Ω and operate with standard 50Ω coaxial cable to the transmitter. Further details available from Jaybeam Ltd, Kettering Road North, Northampton NN3 1EZ or appointed dealers.

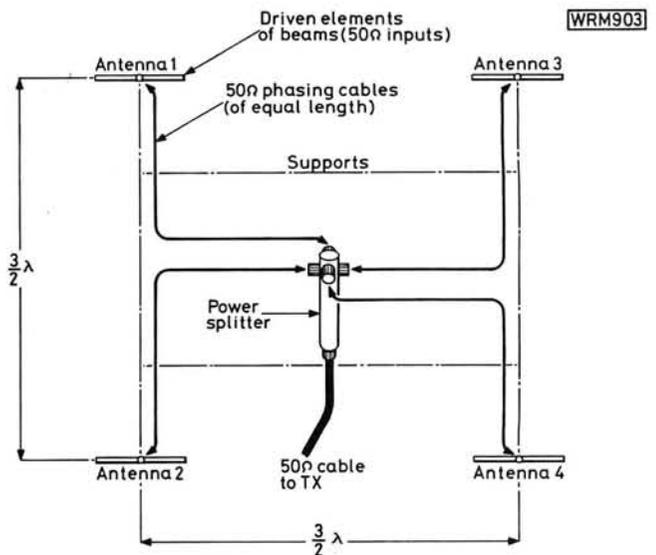


Fig. 9.4: Four beam antennas stacked and bayed $3\lambda/2$ apart and fed via a four-way power splitter through phasing lines each an equal number of $\lambda/2$ multiples long

Power Splitters

These are a relatively new innovation and may well replace the more conventional cable phasing harnesses. Providing they are made to a good specification, power splitters ensure minimum matching loss and therefore more likelihood of obtaining the expected 3dB extra gain from a stacked identical pair, or 6dB from four identical antennas stacked and bayed.

Power splitters such as those produced by Tonna have N type connectors and are available with 50Ω input and outputs to couple and phase antennas with a 50Ω feed impedance. Devices are available for use on 144 and 432MHz and are available for either band with two or four outputs. (There are also special models for 1296MHz with either two or four outputs but these can only be used with Tonna antennas for this frequency band).

An arrangement for an identical pair of stacked Yagi type antennas is shown in Fig. 9.3 which is a side view showing the two way power splitter located midway between the two antennas. The physical length of the 50Ω coaxial phasing and coupling cables to cover each of the distances A to B is determined from:

$$K \times n \times \lambda/2$$

where K = Velocity factor of cable used.
 n = The equal number of half-wavelengths of cable needed to cover the route A to B.
 λ = Wavelength in metres at the frequency of operation.

For example for operation on 145MHz. If the *physical length* between A and B is 3.5 metres then the phasing line length will be greater than this. A $\lambda/2$ section at 145MHz is $150/145 = 1.03$ metres. The distance A to B is 3.5 metres which in $\lambda/2$ sections at this frequency is $3.5/1.03 = 3.39$ but we have to take the velocity factor of the cable into account which for UR67 is 0.667. As the number of $\lambda/2$ sections must be complete this suggests that the 3.39 metres as above, must be rounded up to four. Taking the velocity factor into account this would give:

$$0.667 \times 4 \times 1.03 = 2.78 \text{ metres.}$$

This is still not enough unless a shorter route is taken and this is not to be recommended. With five $\lambda/2$ sections we would get 3.34 metres, still not enough but with six $\lambda/2$ sections we obtain: $0.667 \times 6 \times 1.03 = 4.12$ metres, which is the *minimum* adequate length of cable to cover each route A to B as shown in Fig. 9.3 allowing the phasing cables to be secured to the antenna support and booms.

In Fig. 9.4 we have an arrangement for four stacked and bayed antennas spaced $3\lambda/2$ apart. The power splitter is located as centrally as possible between the antennas to obtain similar physical lengths of cable between each A to B route. Again it is a case of first determining the largest A to B distance but it is important that each cable is the same length. Use the longest A to B distance and from this derive the number of complete $\lambda/2$ sections of cable, taking the velocity factor into account as in the example already given. Tonna power splitters are supplied with a table giving phasing line lengths to meet physical length requirements for either 145MHz or 432MHz and for cables with velocity factors of 0.8, 0.875 and 0.667.

Equally important is that the phasing cable connections to each antenna are made the same way as in Fig. 9.5 otherwise phasing will be altered resulting in low gain and distorted or split main lobes. Details of Tonna power splitters can be obtained from appointed dealers or from the

4 antennas stacked and bayed

2 antennas stacked

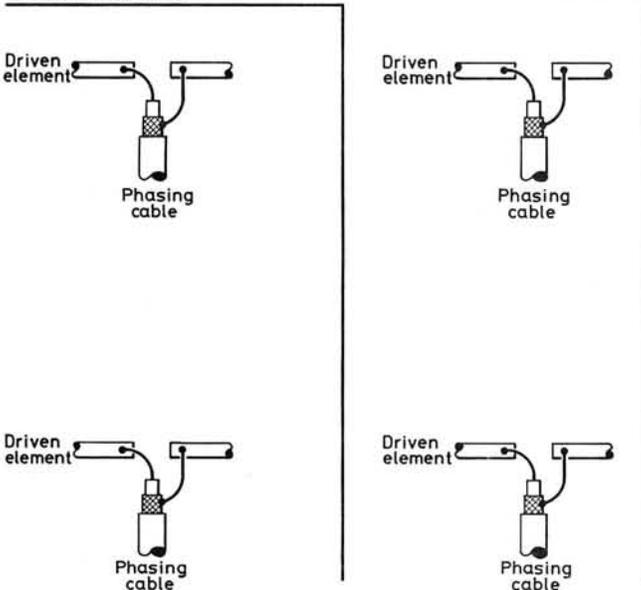


Fig. 9.5

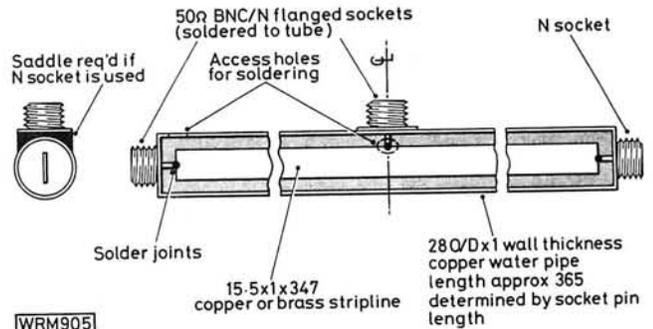



Fig. 9.6: A "practical" 50 Ω low loss 432MHz antenna combiner as built by G8MCP/G8MCQ and successfully used for e.m.e. work

UK agents Random Electronics, 12 Conduit Road, Abingdon, Oxon OX14 1DB.

Although the illustrations of Figs. 9.3 and 9.4 show arrays set up for horizontal polarisation they can of course be turned through 90 degrees to provide vertical polarisation.

Gain—Power Gain—ERP

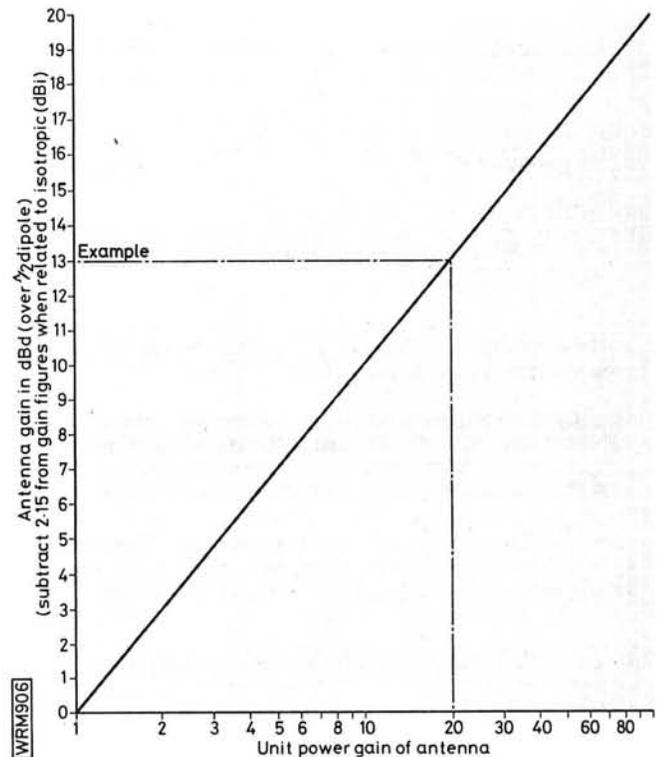For a quick appreciation of effective radiated power obtainable from antenna systems the graph (below) gives the *unit power gain* for gain in dBd (over $\lambda/2$ dipole).



The graph covers up to 20dBd and to determine e.r.p. it is only necessary to multiply the power fed to the antenna by the unit power gain. The dotted line example shows the power gain related to 13dBd as almost 20 (actual figure 19.95) so with 25 watts applied to the antenna terminals, the e.r.p. would be $19.95 \times 25 = 498.75$ watts.

Remember that with two identical antennas stacked the gain is that of a single antenna plus 3dB and with four stacked and bayed that of a single antenna plus 6dB. Two only bayed (side by side) with about $3\lambda/2$ spacing between centres will also provide the extra gain of 3dB.

GAREX (G3ZVI)

SX200-N THE ULTIMATE SCANNER



RESISTOR KITS a top-selling line for many years. E12 series, 5%, carbon film, 10Ω to 1M, 61 values, ratings 1/4W or 1/2W (state which). Starter pack 5 each value (305 pieces) **£3.10**
Standard pack 10 each value (610 pieces) **£5.55**
Mixed pack, 5 each 1/4W + 1/2W (610 pieces) **£5.55**
Giant pack, 25 each value (1525 pieces) **£13.60**
SR-9 monitor: 2m FM with 144-146MHz full coverage VFO + 11 xtal controlled channels; ideal for fixed, M/P use. 12V DC operation **£47.50**

Marine band SR-9, 156-162MHz, same spec. and price.

CRYSTALS FOR NR-56, SR-9, SR-11, HF-12, TM-56B All 2m channels from 0 (145.00) to 33 (145.825) incl. also 144.80, 144.825, 144.85 Raynet at **£2.46** (+20p post per order). Over 40 popular marine channels at **£2.85** (+20p post).

CRYSTAL FILTER 10.7MHz, 12½kHz spacing, ITT 901C **£6.90**

CRYSTAL FILTER 25kHz spacing type 909B **£6.90**

PYE RADIOTELEPHONE SPARES (see full list). Ex. equip., fully guaranteed. **CAMBRIDGE AM10** 10.7MHz I.F. **£3.65**. 2nd mixer **£3**. 455kHz block filter 12½kHz **£9.40**. Ditto 25kHz **£3**. 455kHz AM I.F. **£4.95**. Audio bd. **£1.95**

WESTMINSTER W15/W30 AM RX RF 68-88MHz or 148/174MHz **£6.95**. 10.7MHz IF (inc. 12½kHz xtal filter) **£8.25**. 2nd Osc **£2.10**. 455kHz IF **£5.65**. 455kHz block filter (12½kHz) **£7.35**. Squelch **£1.45**. QQ206-40a (quick-heat) RF tested **£11.95**. Aerial relays **£1.50**

PYE SPARES ARE OUR SPECIALITY - COMPLETE UNITS ARE ALSO AVAILABLE

GAREX FM DETECTOR & squelch conversion for Pye R/T equipment. Ready assembled, full instructions. Tailor-made, easy-fit design, replaces existing squelch board, with minimum of modifications. For AM Cambridge **£6.30**; for Vanguard AM25B (Valve RX) **£6.10**; for Transistor Vanguard AM25T **£6.95**

MAIN DISTRIBUTOR OF REVCO AERIALS & SPECIAL PRODUCTS

(trade enquiries welcome).

PRICES INCLUDE UK POST & PACKING & 15% VAT.



GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH, TRING, HERTS HP23 4LS.

Phone 0296 668684. Callers by appointment only.

Goods normally despatched by return



- * MICROPROCESSOR CONTROLLED 32,000 CHANNELS
- * AM & FM ALL BANDS
- * WIDER COVERAGE: 26-58, 58-88, 108-180, 380-514MHz; includes 10m, 6m, 4m, 2m, & 70cm Amateur bands.
- * 5kHz & 12½kHz FREQUENCY INCREMENTS
- * 16 MEMORY CHANNELS WITH DIRECT ACCESS
- * SPECIALLY DESIGNED FOR EUROPEAN MARKET
- * 2 SPEED SCAN SCAN DELAY CONTROL
- * 2 SPEED SEARCH UP AND DOWN
- * SEARCH BETWEEN PRESET LIMITS UP AND DOWN
- * 3 SQUELCH MODES inc. CARRIER & AUDIO
- * RELAY OUTPUT FOR Aux. CONTROL
- * INTERNAL SPEAKER, ALSO EXTERNAL SPEAKER & TAPE OUTPUTS
- * LARGE GREEN DIGITRON DISPLAY BRIGHT/DIM
- * AM-PM CLOCK DISPLAY
- * 12V DC, 230V AC OPERATION
- * FACTORY-BACKED SPARES & SERVICE, 12 MONTH WARRANTY & THE ALL-IMPORTANT PRE-DELIVERY CHECK BY GAREX, THE MAIN SERVICE & SALES AGENTS.

£299 INC. VAT Delivered

NEW

★ REVCON ★

NEW

A new top quality 16-element, all British made, VHF/UHF broadband fixed station aerial from Revco. Ideally suited to SX200 and other VHF/UHF Receivers.

PRICE £24.95 inc

Swap Spot

Have a 4m sailing dinghy. Would exchange for a mobile h.f. rig. Tel: Dave 0676 42036 (Coventry). T188

Have "Metrohm" 500V insulation test meter, case plus test leads. Would exchange for wavemeter of g.d.o. or w.h.y. Tel: Dave Stoke-on-Trent 721904 (evenings). T189

Have Grundig Satellit 1400SL, 1 month old, cost £165 plus Webley Vulcan 177 air rifle cost £75. Would exchange for any good receiver 0.5MHz-30MHz, anything considered but prefer FRG-7700 or Lowe SRX30D. 35 The Oval, Didcot, Oxon. T211

Have Pye Bantam 3-channel f.m. TX/RX with mic. Would exchange for two Pye Cambridges with power leads, must be f.m. and in full working order. 27 Crichton Road, Pathead, Midlothian, Scotland EH37 5RA. Tel: 0875 320 642. T221

Have Atari TV video game, b/w or colour, with three games. Would exchange for SX200N, two Pye Westminsters with mic, Pye ten channel or any other two way radio—must be f.m. 27 Crichton Road, Pathead, Midlothian, Scotland EH37 5RA. Tel: 0875 320 642. T222

Have Pulsar Zero 4000 light controller, will handle inductive loads, e.g. pin spots, projectors, neons and ballasted fluorescents. Modes include sound to light, flip-flop, flashing, manual flash, full on or off, etc. Master controls for standby, shimmer, dim/full on, forward/reverse, lightchase/darkchase, speed control, etc. Would exchange for an 144MHz rig. Please write with details to Andy, 6 Sedgfield Close, Salford 5, M5 4JL. T223

Have Icom IC2E 144MHz synthesised f.m. rig with auxiliary pack and eliminator, also a 10-channel scanner unit with 8 crystals fitted and NiCads. Would exchange for a camera or w.h.y. Tel: 01-524 2886. T243

62

Did You Know...

That the earliest wireless telephony microphones had to be cooled by water?

The speech or music of the very earliest wireless telephony transmissions was imposed upon a carrier produced, not by valves as in later apparatus, but by a high-frequency alternator. Since conventional microphones could not carry currents of more than one-hundredth of an ampere, special microphones had to be constructed for use with these alternators, and cooled by water, air or even oil. In the case of a low-power high-frequency alternator, it was sometimes sufficient to use a battery of a large number of conventional microphones connected in parallel, and one Italian inventor even constructed a microphone in which the carbon granules themselves circulated in order to cool. More usually, the microphones had an electrically conducting fluid behind the diaphragm, such as acidulated water, which could carry a current as great as 15 amperes. These contrivances were very makeshift, and it was not until valve transmitters were introduced that wireless telephony really came into being.

Eric Westman

Practical Wireless, October 1983

BASIC QSOs

PART 2

in Spanish

G.W.Roberts GW4JXN and Ildefonso Sevilla EA7BWV

Net Working

I think it is (XYZs) turn.
I've forgotten whose turn it is.
Over to . . . with the group.
Break.
Over.

Cre que el cambio es para (XYZ).
He olvidado para quien el cambio.
El cambio para . . . con el grupo.
Break.
Cambio.

Crayo jay el cambio es para (XYZ).
Ay olvihdahdo para cwee-en el cambio.
El cambio para . . . con el grupo.
Break.
Cambio.

Rig and Antenna

The rig here is . . .
I'm using a . . . transceiver.
I have here a . . . receiver and . . . transmitter/with a linear amplifier.
I am putting out 10, 20, 50, 100, 150 watts.

The rig is home brew with modifications.
My antenna is a dipole/is a trap dipole.
A beam with three elements.
With horizontal/vertical/circular polarisation.
With a gain of . . .
A quad/a long wire/an end fed Zeppelin.

A centre fed Zeppelin.
The antenna is about . . . metres above ground level.
The QTH is . . . metres above sea level/at sea level/below sea level.
The antenna has a rotator.
I'll turn the antenna on you during the next over.

I rotate the antenna by hand.
The antenna is in the garden/attic on a . . . metre high mast.

I am testing the rig.
I am glad of your report.
I like my . . . I want to change my . . .
How do you like your . . .

Mi equipo es . . .
Estoy usando un . . . transceiver.
Tengo aqui un . . . receptor y . . . transmisor/con amplificador linear.
Estoy poniendo en antenas diez, veinte, cincuenta, cien, ciento cincuenta watos.
Equipo casero con modificaciones.
Mi antena es un dipolo/es un dipolo con trampa.
Direccional con tres elementos.
Con polarizacion horizontal/vertical/circular.
Con una ganancia de . . .
Una cuadracubica/hilo largo/una Zeppelin alimentada en extremo.
Una Zeppelin alimentada en centro.
La antena tiene . . . metros de la tierra.
Mi QTH està a . . . metros sobre nivel del mar/al mismo nivel del mar/bajo nivel del mar.
La antena tiene un rotor.
Voy a rotar la antena hacia su direccion durante el prōximo cambio.
Muevo la antena a mano.
La antena esta en el jardin/atiko/en un mastil de . . . metros.

Estoy probando el equipo.
Estoy contento de su reportaje.
Me gusta mi . . . Quiero cambiar mi . . .
Le gusta su . . .

Mee equeepo es . . .
Estoy wsando oon . . . transceiver.
Tengo aki oon . . . retheptor ee . . . transmissor/con ampliefecahdor linear.
Estoy ponyendo en antenas dee-eth, vaynte, seenkooentah, see-ehenseenkooentah watos.
Ayqueepo kasayro con modifikathiones.
Mee antena es oon deepolo/es oon deepolo con trampa.
Direkthional con trehs elementos.
Con polarithathion orizontal/vertical/sircoolar.
Con oona gananthia day . . .
Oona kwadracobika/eelo largo/oonaa zepelon alimentahda en extremo.
Oona zepelon alimentahda en thentro.
La antena tee-enay . . . metro day la tee-erra.
Me cootay-ah esta a . . . metros sovre neevel del mar/al mesmo neeval del mar/bacho neevel del mar.
La antena tee-ene oon rotor.
Voy a rotar la antena athia soo diretsion doorante el proximo cambio.
Mooayvo la antena a mano.
La antena esta en el chardin/atiko/en oon mastil de . . . metros.
Estoy provando el aykweepo.
Estoy contento day soo reportache.
May gwsta me . . . Key-ero kambiar me . . .
Le goosta soo . . .

Weather and Radio Conditions

The temperature is . . .

Today the weather is fine/sunny/(very) cold/hot/misty/windy.

It is raining.

It is snowing.

The snow is 30cm thick.

The weather has been fine.

Today/yesterday/during the weekend it has been raining.

It has been snowing.

Winter/spring/summer/autumn has come.

The wind has been strong.

There has been thunder and lightning.

Working conditions are poor/bad/moderate/good/very good/excellent.

All the bands are open.

The 10, 15, 20, 40, 80 metre band is closed/open to North/Central/South America. Eastern/Northern/Southern/Western Europe, Asia, Australasia, Africa, the Far East, Japan.

I have just heard a . . .

I can hear but cannot work a . . .

There is an opening on 2 metres.

This lift is getting better/getting worse. Let's hope it lasts.

Nice to speak to you under lift conditions.

It is . . . o'clock approximately here local time/GMT.

What time is it in . . . ?

La temperatura es . . .

Hoy el tiempo es bueno/soleado/(frio) caluroso/niebla/viento.

Esta lloviendo.

Esta nevando.

Hay treinta centimetros de nieve.

El tiempo ha sido bueno.

Hoy/ayer/durante el fin de semana ha llovido.

Ha nevado.

Invierno/Primavera/Verano/Otoño ha llegado.

El viento ha sido fuerte.

Ha habido tormentas y relámpagos.

Mis condiciones de trabajo son malas/moderadas/buenas/muy buenas/excelentes.

Todas las bandas estan abiertas.

La 10, 15, 20, 40, 80 metros esta cerrada/abierta para el Norte/Centro/Sur America. Para Europa del Este/Norte/Sur/Oeste, Asia, Australasia, Africa, Extremo Oriente, Japon.

Acabo de escuchar a . . .

Puedo escuchar pero no puedo trabajar un . . .

Hay apertura en 2 metros.

Esta elevacion esta mejorando/empeorando. Esperemos que dure.

Que bien poder hablar en condiciones elevadas.

Son las . . . aprox hora local/GMT.

Que hora es en . . . ?

La temperatura es . . .

Oy el tee-empo es boeno/solayahdo/(freeo) kaluroso/nee-eva/vee-ento.

Esta liovee-endo.

Esta nayvando.

Ay trehinta thentimetros day nee-eve.

El tee-empo a seehdi boeno.

Oy/ayer/doorante el fin day semana a liovihdo.

A nevahdo.

Invee-erno/preemavera/verano/otonio a liegahdo.

El vee-ento a seehdo foerte.

A avido tormentas ee relampagos.

Mees condithiones day trabacho son malas/mohderahdas/booenas/mooeee booenas/ekthelente.

Tohdas las bandas estan aviertas.

La 10, 15, 20, 40, 80 metros esta therrahda/avee-erta para el nortay/thentro/sur america. Para oyropa del estay/nortay/sur/oyestay, asia awstralasia, afrika, extremo orientay, chapon.

Akavo day eskootshar a . . .

Pooayhdo eskootschar pero no pooayhdo trabachar oon . . .

Ay apertura en dos metros.

Esta elevathion esta mechorando/empeorando. Esperemas kau dooray.

Kay bien pohder avlar en kondithiones aylevahdas.

Son las . . . aprox ora local/GMT.

Kay ora es en . . . ?

Arranging a Sked

May I speak to you again?

Are you free tomorrow/this time next week at . . . hours GMT?

How about this frequency or alternatively let's try the 10, 15, 20, 40, 80 metre band?

No I'm sorry, I am not free at that time.

I am usually on 20 metres at . . . GMT on (days of week) except . . .

I have to go to bed/to work now.

Puedo hablarle de nuevo?

Esta libre mañana/a la misma hora la proxima semana a las . . . horas GMT?

Esta bien esta frecuencia o podemos probar la banda de 10, 15, 20, 40, 80 metros?

No lo siento, no estoy libre a esa hora.

Estoy en 20 metros sobre las . . . GMT los (days of week) excepto . . .

Tengo que irme a la cama/a trabajar ahora.

Pooayhdo ablarlay day nooayvo?

Esta liebre nanianan/a la mizma ora la proxima semana a las . . . oras GMT?

Esta bei-en esta frekooenthis o pohdaymos provar la banda day 10, 15, 20, 40, 80 metros?

No lo see-ento, no estoy libre a esa ora.

Estoy en vehinte metros sovre las . . . GMT los (days of week) exepto . . .

Tengo kay eerme a la kama/a travachar aora.

Technical

I have a new rig/linear/antenna which I am testing.

Is my modulation OK? Your modulation is good/bad.

What is my exact frequency?

I'm using a speech compressor.

Does this make any difference?

Thank you for the test.

Tengo nuevo equipo/linear/antena que estoy probando.

Esta mi modulacion bien? Su modulacion es buena/mala.

Cual es mi frecuencia exacta?

Uso el procesador ahora.

Se nota la diferencia?

Muchas gracias por las pruebas.

Tengo nuayvo ekuuepo/linear/antena kay estoy provando.

Estamee modoolathion bee-en? Soo modoolathion es booena/mala.

Kwal es mee fraykooenthia esacta?

Ooso el prothesahdor aora.

Say nota la diferenthia?

Muchas grathias por las prooayvas.

Next month We will complete the phrases with their pronunciation and have a glossary of useful technical terms

G4JDT
HARVEY

EAST LONDON HAM STORE

H. LEXTON LIMITED

191 FRANCIS ROAD LEYTON E.10
TEL 01-558 0854 TELEX 8953609 LEXTON G
01-556 1415

DRESSLER AMPLIFIERS

These are high power 240V linears using 4C x 150 or 4C x 250 or 4C x 350 Eimac Tubes NOT using the grounded Grid system.
Fully protected, no thermal damage to PA finals possible.



DRESSLER AMPLIFIERS

D70 70cm 200wfm 400 PEP £700.00
D200 2mtr 300wfm 600w PEP £595.00
D200S 2mtr 400wfm 1KW PEP £695.00
D200C 2mtr 100w. Few left at £275.00

GASFET DRESSLER PRE-AMPS

VV2 £44.00
VV200GAAS 150W £75.00
VV200GAAS 750W £85.00
VV200GAAS 1KW £85.00
Non switching £22.00
VV2RPS S0259 £24.00
VV2RPS N Type £24.00
VV7RPS S0259 £22.00
VV7RPS N Type £24.00
New VV200 VOX £84.00 250w PEP VOX



Powered by the linear or with separate interface.

0.7 - 0.9dB signal to noise
0.2dB insertion loss

GASFET MASTHEAD PREAMPS

3SK97 GASFET Available separately £5.00

COMPUTERISED ROTATOR CONTROL

We are expecting delivery in early March of a revolutionary new rotator. When under automatic control it has several unique features including:

- Control is handled by an 8 bit CPU
- it can rotate to a specified angle
- it can scan between two specified angles
- it will scan 360 degrees continuously
- single step rotation available
- continuous steps over a certain range
- 360 continuous steps
- rotation to a direction stored in a memory
- scanning between directions stored in the memory
- changing the origin of rotation
- adjustable scanning speed
- adjustable step angle and pause duration
- data can be stored and cleared from the memory
- Manual operation is also possible



£350.00

ICOM

IC740 HF 100W £699.00
IC720 RHF 100W G/C £850
IC730 HF 100W £586.00
IC2KL Linear £850.00
IC2KLPS P.S.U. £230.00
PS15 P.S.U. £110.00
PS20 P.S.U. £145.00
AT500 A.T.U. £325.00
RX70 Receiver £475.00

ICOM

IC2E 2mtr fm portable £179.00
IC4E 70cm fm portable £190.00
IC25G 2mtr 25w fm £235.00
IC290 2mtr 10w fm/ssb £366.00
IC251 2mtr 10w fmkw/ssb/base £425.00
IC451 70cm 10w fmkw/ssb/base £630.00
IC490 70cm/fm/ssb mobile £445.00
IC271 NEW P.O.A.
ICSP3 Speaker £39.00
ICSM5 Mic £29.00

ICOM

Accessories
ICLC/1/2/3 case £4.25
ICWM9 SP/Mic £12.00
ICBP2 6V pack £29.50
ICBP3 9V pack £20.00
ICBP4 empty pack £6.95
ICBP5 12V pack £39.50
ICCP1 charging lead £3.75
ICDC1 12V car pack £9.75
LC8 leather case £18.95
BC30 Base Charger £45.00

WELZ

SP200 1.6-160MHz 20-200-1KW £69.00
SP300 1.8-150MHz 20-200-1KW £97.00
SP400 130-500MHz 5-20-150W £69.00
SP15M 1.8-160MHz 5-20-200W £35.00
SP10X small £24.00
SP45 130-470MHz £50
SP250 1.8-60MHz £49.00
SP350 1.8-60MHz £59.00
AC38 ATV 3.5-30MHz £65.00
CT150 150W Dummy £35.00
CT300 300W Dummy £49.00
CH20A 2 way Coax Switch £17.50
CH20N 2 way Coax Switch N Type £31.00

YAESU

FT1 Gen. Coverage Tx/Rx £1200.00
FT980 Gen. Cov. Cat System £1050.00
FT757 Gen. Coverage P.O.A.
FT102 150W 10m-160m £750.00
FC102 A.T.U. £200.00
FV102 V.F.O. £225.00
SP102 Speaker £45.00
FT77 - NEW - £450.00
FP700 £95.00
FC700 £90.00
FTV700 D.M. £185.00
FRG7700 Gen. Coverage Rx £295.00
FRG7700 M £370.00

YAESU

FT790 FM/SSB £290.00
FT290R with mods FM/SSB £265.00
FT208 2mtr portable FM £195.00
FT708 70cm portable FM £205.00
FT230 2mtr FM mobile £220.00
FT730 70cm FM mobile £240.00
FT726 I6-20-70 (X Band) £635.00
FRV7700A 118-150 £60.00
FRV7700B 50-60/118-150 £75.00
FRV7700C 140-170 £65.00
FRV7700D 70-80/118-150 £72.00
FR7700 Aerial Tuner £42.00
FRA7700 Active Antenna £40.00
FF5 Filter £9.95
MMB11 FT290 Car Mount £24.00
NC11C Charger £9.50
NC8 Base Charger FT208/708 £45.00

TRIO/KENWOOD

TS930 Gen. Coverage Rx/Tx £1150.00
TS830 100W H.F. £675.00
TS530 100W H.F. £575.00
R2000 £380.00
TS430 inc. FM £730.00
TR9130 £415.00
TR2500 2mtr portable £215.00
TW4000 P.O.A.
AT230 £135.00
SP230 £41.00
DM801 GDO £70.00
R600 Receiver, AM/SSB £230.00
TR3500 70cm portable £230.00

Morse Readers

AEA MBA RO CW/RTTY reader (i.e.d.) £195.00
Tasco CWR 600 CW/RTTY reader (u.h.f.) £160.00
Tasco CWR 610 CW/RTTY reader (u.h.f.) £180.00
Tasco CWR 685 CW/RTTY reader (monitor) Tx/Rx £750.00
Tasco CWR 675 (monitor) £420

DATONG

D70 Morse Tutor £56.35
PC1 Gen. Coverage converter £137.00
FL1 Agile filter £79.35
FL2 Active filter £89.70
FL3 Angle filter & notch £129.37
ASP Auto clipper £82.80
D75 Manual clipper £56.35
RFC Speech clipper £29.90
AD270 Indoor active ant. £47.15
AD370 Outdoor active ant. £64.40
RFA Wide band AMP £33.92
ANF Auto notch & filter £67.85

DUE TO FLUCTUATIONS IN THE EXCHANGE RATE, PRICES ARE SUBJECT TO ALTERATION.

MORSE KEYS

Morse keys Swedish brass key £49.00
HiMound HK707 £12.95
HiMound MK705 £11.50
HiMound HK702 £12.95
Kenpro squeeze key KP100 electronic key £65.00
Kenpro KR200 Memory keyer £149.00
Daiwa DK210 Electronic £47.00

POWER SUPPLIES

Alinco EP 2500 25 amp IC Regulated with S/C protection £89.00
also
Daiwa PS300 £130.00

DAIWA

RM940 Mic. Infrared £45.00
CN620A. 1KW SWR £57.00
CN1001. Auto A.T.U. £156.00
CN2002. 2kW Auto A.T.U. £228.00
CN518. 2.5KW A.T.U. £175.00
CNW419. 500W PEP. Gen. Coverage A.T.U. £130.00
AF406. Active filter £63.00
AF606 P.L.L. Active filter £113.00
DR7500X £125.00
DR7500R £163.00
DR7600X £176.00

TONNO

2M-50W Linear amp. 1.3Win £59.00
2M-70W Linear amp. 10Win £90.00
2M-100W Linear amp. 10Win £129.00
7M-60W ATV £290.00
500 - CW/RTTY Terminal £290.00

TONNA

50 5 ele £34.00 432 21 ele £29.00
144 4 ele £14.00 435 21 ele ATV £29.00
144 9 ele £17.00 432 19 ele £20.00
144 9 ele cross £32.00 432 19 ele cross £34.00
144 9 ele portable £20.00 1296 23 ele £25.00
144 13 ele portable £31.00 144/432 9+19 ele cross £34.00

STANDARD

See the new Standard C5800 Multimode 25W SSB/FM/CW 2mtr £359.00
C58 2mtr FM/SSB/CW
C78 70cm portable
C7900 70cm mobile £339.00
C8900 2mtr mobile £219.00
C5800 2mtr FM/SSB 25W £359.00
C1100 2mtr portable £139.00
Plus All Accessories

SCANNING RECEIVER

Scanning Receiver SX200N £295.00
CD6000 AIR £110.00

TET

HB33T £189.00 HB35C P.O.A.
HB34T £202.00 SQ22144 £55.00
HB35T P.O.A. SQ220x144x4 £90.00
SQ007 70cm P.O.A.

DAYFRAME

TB3 3 ele Triband £189.95 5XY/2M 5 ele cross £28.17
VR3 Triband vertical £46.00 Q4/2M 4 ele Quad £29.32

ROTATORS

Kenpro KR250 £44.95
Hirshmann HR250 £55.00
Kenpro KR400RC £110.00
Kenpro Elevation rotator £85.00

HOXIN

GP5 2mtr colinear £33.00 DX1 discone Tx-Tx £34.00
6.4Db Vertical HF5DX 80-40-20-15-10 mtr £84.00

ALL ACCESSORIES AVAILABLE - PLUGS SKTS CO-AX 2MTR COLINEAR £33.00 70CM COLINEAR £33.00



PRICES INCLUDE VAT AT THE PRESENT RATE OF 15%
OPEN MON - FRIDAY 9:00-5:30. SATURDAY 10:00-3:00. INSTANT HP FACILITY AVAILABLE
EASY ACCESS M2-M11-M1 NORTH CIRCULAR ROAD-EASY PARKING

VISA

PASSPORT TO AMATEUR RADIO

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me.....copies at £1.50 each to include postage and packing (£1.80 surface mail overseas)

I enclose P.O./Cheque No.....Value

UK remittances must be by crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....

.....


..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International plc

— Cut round dotted line —

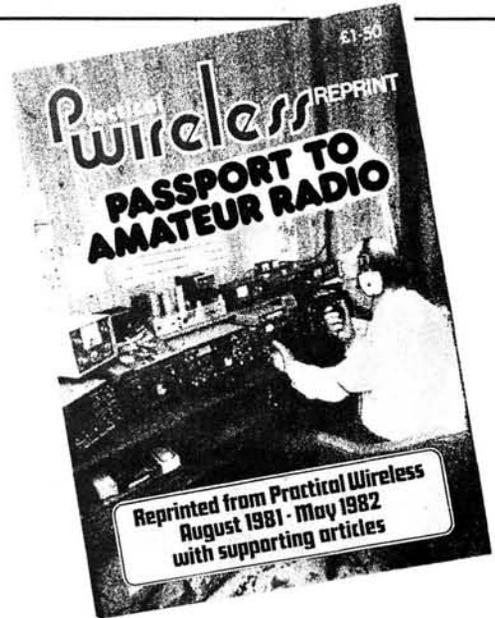

PASSPORT TO AMATEUR RADIO

You've asked for it—now you can get it! John Thornton Lawrence's popular series reprinted all in one book, along with a selection of other articles from *Practical Wireless* that will be useful to the up-and-coming student of amateur radio.

Passport to Amateur Radio reprint has 88 pages, 273 x 203mm, and is available from **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, price £1.50 including postage and packing to UK addresses, or £1.80 by surface mail overseas.** Please ensure that your name and address are clearly legible on the coupon.

OUT OF THIN AIR

Please send your order and remittance to:

**IPC Magazines Ltd., Post Sales Department,
Lavington House, 25 Lavington Street,
London SE1 0PF**

Please send me.....copies at £1.50 each to include postage and packing (£1.80 surface mail overseas)

I enclose P.O./Cheque No.....Value

UK remittances must be by crossed postal order or cheque (name and address on back please) and made payable to IPC MAGAZINES LTD

NAME
(BLOCK LETTERS)

ADDRESS
(BLOCK LETTERS)

.....

.....

..... Post Code

Remittances with overseas orders must be sufficient to cover despatch by sea or air mail as required. Payable by International Money Order only

Company registered in England. Regd. No. 53626

A subsidiary of Reed International Limited

— Cut round dotted line —



Aerials and aerial accessories are very definitely among the most popular topics covered in *Practical Wireless*. In response to requests from readers, we've reprinted a selection of articles from the past three years, plus two new features—one by Ron Ham on v.h.f. propagation, the other describing the "Ultra-Stim Jim", a new version of that most popular 2-metre aerial design by Fred Judd.

Out of Thin Air has 80 pages, 295 x 216mm, and is available from **Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, price £1.50 including postage and packing to UK addresses, or £1.80 by surface mail overseas.** Please ensure that your name and address are clearly legible.

Practical Wireless, October 1983

on the air

AMATEUR BANDS by Eric Dowdeswell G4AR

Reports to: Eric Dowdeswell G4AR, Silver Firs, Leatherhead Road, Ashted, Surrey KT21 2TW.
Logs by bands in alphabetical order.

Following on from last month's chat on the development of the superhet receiver I mentioned the crystal-controlled converter used in front of a tunable i.f. system, usually a communications receiver. This gives a fixed tuning range whatever the signal frequency, constant calibration and good overall stability since the tunable i.f. is working at a comparatively low frequency.

When wide frequency coverage is required the number of crystals needed is prohibitive, the practical answer being a form of frequency synthesiser using a single crystal, often 1MHz. At this point we need to digress and consider the phase-locked loop circuit (p.l.l.) Fig. 1, comprising a phase-sensitive detector, low pass filter, d.c. amplifier and a variable frequency oscillator whose frequency can be controlled by a suitable d.c. voltage. This control voltage is generally applied to a variable capacity diode (varicap) in the reverse direction so that its effective capacity varies with applied voltage, Fig. 2.

The phase-sensitive detector will produce an output when two signals of about the same frequency are applied to its inputs, the amplitude of the output depending upon the relative phase of the two signals. The low pass filter eliminates any noise or h.f. signals that may appear at the output of the phase-sensitive detector. The output voltage of the d.c. amplifier is used to control the frequency of the voltage controlled oscillator (v.c.o.), the effect being for the v.c.o. to become locked, or synchronised, with the input signal. This is a form of negative feedback, better known in audio amplifiers as a means of improving linearity.

So far we don't seem to have achieved very much but in practice it means being able to lock the v.c.o. to a very weak signal that may be accompanied by extreme noise, even when the noise level is greater than the signal level, while the output will be a clean signal devoid of noise.

If the p.l.l. circuit is incorporated in a network such as shown in Fig. 3, using a 1MHz crystal, the output will be at 1MHz intervals, as selected by the output switch, all locked to the crystal and having the same stability as the crystal. It may all seem very complicated but most of the circuitry required can be found on a single integrated circuit needing only a few discrete components to produce a working frequency synthesiser.

Such a frequency synthesiser forms an important part of the well-known Wadley

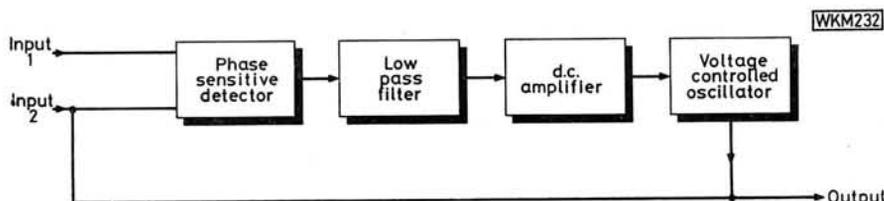


Fig. 1: The four basic stages required to form a voltage controlled oscillator or phase-locked loop circuit (p.l.l.)

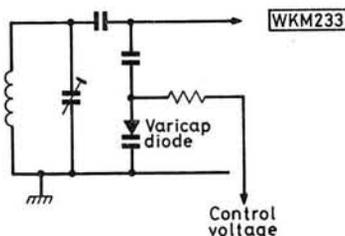


Fig. 2: The d.c. control voltage is applied to a varicap diode which acts as a variable capacitor across the tuned circuit, its value depending upon the applied voltage

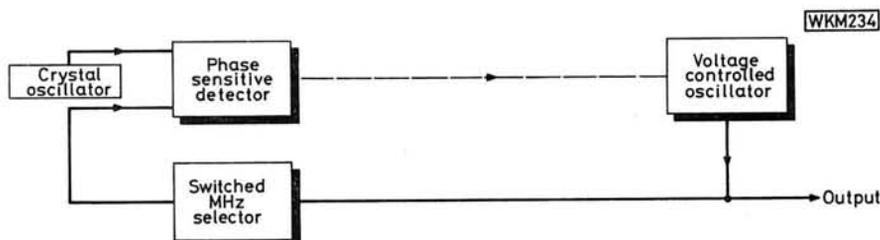


Fig. 3: Here the p.l.l. circuit includes a circuit that provides integral harmonics of the basic 1MHz crystal frequency right through the required receiver tuning range, selected by a simple switch

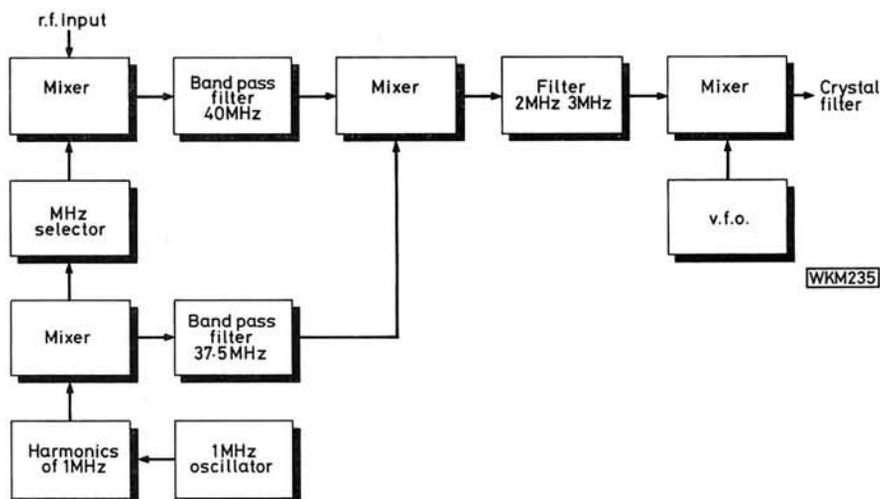


Fig. 4: Simplified diagram of the Wadley Loop system which was used by Racal in some of its famous communications receivers

Loop design for a superhet, Fig. 4, in which the variable oscillator works at v.h.f. (40.5MHz to 69.5MHz) with complete coverage for the medium wave band to 30MHz or so, in 1MHz bands. The clever part of the design enables any frequency drift in the v.h.f. oscillator to be cancelled out. Spurious responses are a problem, with several local oscillators operating in the circuit so that strict attention must be paid to complete screening.

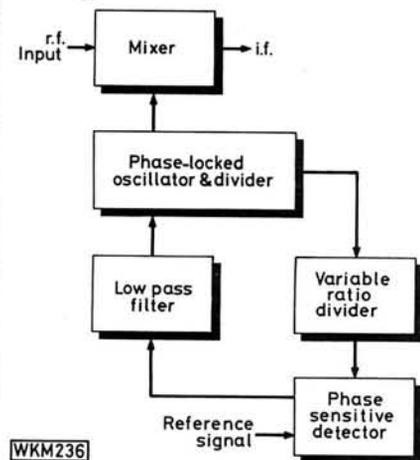


Fig. 5: The type of circuit used in many modern receivers using full frequency synthesis with the tuning at 10 or 100Hz intervals, suitable for frequencies into the u.h.f. range

In a modern superhet the frequency division is carried right down to 100Hz or even 10Hz, selected by the tuning knob which, although it appears to give continuously variable tuning as with conventional capacitor tuning, is actually in a series of steps of 10 or 100Hz. A digital frequency readout display complements the frequency synthesiser. The essential stages of a superhet are shown in very basic form in Fig. 5, as far as the frequency generation circuits are concerned for the first mixer stage, replacing the single oscillator stage of the conventional superhet.

DX Round-Up

Regular **Dave Coggins** up in Knutsford, Cheshire, bought himself an old AR88 and has been having fun comparing it to his FRG-7700 and not sur-

Club Time

Clubs will soon be coming to the end of their outdoor summer activities, field days, special event stations, DF hunts and the like. Discussions back at the club will be held to find out why things didn't quite go as planned, why gear broke down, and, above all, what's going to be done about it for next year.

Hopefully, club secs and PROs will be badgering their committees to get the forthcoming winter's programme of lectures, film shows and other events organised, at least

prisingly, to me anyway, it "performs a lot better and on 1.8MHz (160m) it puts the 7700 to shame!" With the FRG-7700 he copied HH2SD, VK1HF for a rare prefix, and 9X5SL on 28MHz, followed by KH6IJ, KL7H, VK9NS on Norfolk Island and 9V1VP, all on 21MHz. Dave mentions the odd Euro on the 10 and 18MHz bands but little else. What has happened to these new bands of ours as no-one ever seems to mention them.

New to the column is **John Buckley** in Cork, Eire, who has a Trio QR666 with 15m of wire not far off the ground, but a vertical for 14/21MHz is on the stocks. Logged by John on 14MHz were CO2JA, FY7CH, J73DF in Dominica Republic, 5T5RY (QSL F6FNU) and PY1EFM/PY0T wanting cards to POB58 Rio de Janeiro. This last must get the award of the most ridiculous call for DX purposes! On 21MHz he got AP2SQ, C30LAC with cards to EA5AQX, and YJ8RG in the New Hebrides.

Desmond Chambers in Newport, Co. Mayo, Eire, is a regular reader but writes in for the first time with news of his activities with his Panasonic RF2600 and 40m-long wire antenna, although the set only goes up to 18.5MHz. His present college studies in electronics will give him a pass in the equivalent of the RAE over there if he succeeds so with some c.w. practice he hopes to have his EI call early next year. Only decent DX on 7MHz was 4X4MS/5N0 with C31MC, C6ADC on 14MHz.

The RAF, Manston, Kent is the home of **Terry Jenner** with his R2000 receiver and 30m-long wire. A good one on 3.5MHz was 6W8AR plus CP8HD and Polish special event station SNOJP to celebrate the visit of the Pope recently. On 14MHz it was AP2MQ, VS5PP and ZL2DM for his first ZL. Best on 21MHz were 5N8MYE and 7Q7LW POB 24, Mtakatake.

In Wellington, Somerset, **David Price** has an FRG-7 and multiband dipole and looking at all bands from 28 to 7MHz. On 28MHz it looks like J20WYC only, but on 21MHz he logged 9J2BH, 6Y5SG, VP2KBH (QSL K8EFS), Y11BGD (QSL POB5864, Baghdad) and CE0ZAD. Up to 14MHz and CO2HQ and FC9UC, then 7MHz and a nice one in ZL4AV, and FM7WS, CE0ZAD and LU6ATD. Best on 3.5MHz was 6W8AR who said QSL via DJ3AS.

Fairly good on all bands except 28MHz was the verdict of **Viv Doidge** in

in skeletal form. Personally speaking I hope that more and more clubs who seek publicity and an increase in membership will get such a programme to me as soon as possible so that there will be no need for the sec to rush details to me of fixtures that have been dreamed up at the last moment.

Some clubs are excellent in that respect while others are appalling, yet I'm quite sure that a cross-section of the membership of clubs would show little change across the country. It is just that some clubs utilise the talent available while others do not. What about your club?

Callington, Cornwall, with his FRG-7700 and matching a.t.u. plus a long wire. He did very well indeed on 3.5MHz with A82LC, CE6EAT, FM7WS, VK6HD and ZS3GB followed on 7MHz by CX6TV, TU2LE, VP2KBK, ZL4PO/C on Chatham Island for an excellent rare one, and 7P8CM. On 14MHz he captured HC8RS on the Galapagos Islands, J6LJ, JX9VCA (QSL LA7JO), VP2VD and ZK1CG.

Michael Burke of Falkirk, Scotland, is on the amateur bands for the first time after working on the CB band. He now has an Eddystone 840C and a 30m-long wire antenna. So far it is mostly Yanks and Euros on 14MHz but I'm sure he will soon get the hang of it.

In Sandbach, Cheshire, **David Freeborough** has got his GCE's out of the way and so is hard at it studying for the RAE. His Panasonic RF3100 and whip antenna did fairly well on 21MHz with AP2SQ, CP9HD, FY0ESE, HC1JB, HH2JR, HL1E, T77C in San Marino, VP2KBK, VP2MDG and YC1WS plus A82LC.

Exams have also been the bane of **Dave Shapiro** (Manchester) but he did manage to get out with the Bury RS on their VHF NFD site and do some logging. His DX-200 and homebrew a.t.u. and 20m-long wire caught FM7WS and HV2VO (Vatican Observatory) on 7MHz, and then TI2J on 14MHz, plus C6ANU, FG7BP, HH2N, HR3JJR, HL1AGO, JY1 (King Hussein), J88AB, S79ARB, TL8ER, TR8DX, TU4AT and T77C, all on 21MHz.

In Colchester, Essex, **Andy Durrant** has managed to get a 10m mast up in the air and is busy playing with different antennas, all feeding his AR88. So far he has 10m and 20m-long wires with a switching box so that he can compare results. On 21MHz he found HL1ALA, CR4NH, 9Y4VU (POB 76, San Fernando), plus on 14MHz 6Y5MC, J2LA in Djibouti, AL7DN in Alaska, VP2MO, V3PMR, ZK1CH (QSL ZL1SD), and a Russian special in U2UM and cards to UK2BBB at the usual QTH, F0CH/FC (QSL HB9TL) and TF5TP.

Not too much in the way of DX reports this month and hardly a comment on the new WARC bands and nary a note on the c.w. portions of our bands. I used to get several a month at one time, and surely there are more prospective G4's around now than ever before, so do let me know what you are hearing on c.w.

Acton, Brentford & Chiswick ARC G3IUU Tuesday Sept 20 at 7.30, the Chiswick Town Hall, Chiswick High Street, London W4 with visitors most welcome, and members invited to bring up their own AR problems for general discussion. Sec is W. G. Dyer G3GEH, 188 Gunnersbury Avenue, Acton, London W3.

Atherstone ARC G4LCQ G6ARC Top Band DF forms the subject for the meeting on September 8 to be delivered by G8SYE. Normally second and third Thursdays at the Tudor Centre, Colleshill Road, Atherstone says sec Mike Wooding G6IQM, 16 Hill Top, New Arley, near Coventry.

B.N.O.S.

ELECTRONICS

HIGH QUALITY R.F. CONNECTORS AT CHEAP CONNECTOR PRICES

CONNECTORS SUFFIXED 'S' DENOTES SILVER PLATED ALL OTHERS ARE NICKEL PLATED WITH DELRIN INSULATOR

UHF CONNECTORS

Plugs	Price
BU01 PL259 for 0.4in cable (UR67)	0.50
BU01A Reducer for 0.2in cable (UR43)	0.11
BU01B Reducer for 0.25in cable (UR90)	0.11
BU02 PL259 as BU01 with metric thread	0.75
BU03 PL259 for 0.2in cable (UR43)	0.62
BU04 PL259 push on connector for UR67	0.73
BU05 PL259 elbow connector for UR43	0.79
BU06 PL259 solderless connector for UR67	0.55
BU07 PL259 solderless connector for UR43	0.55
BU08 As BU07 but push on type	0.99
Sockets	
BU11 S0259, 4 fixing hole type	0.42
BU12 S0259 single hole, inside nut type	0.55
BU13 S0259 single hole, outside nut type	0.55
BU14 S0259, 2 hole fixing type	0.42
BU15 S0259 inline socket for UR43	0.65
BU16 Chassis mount elbow socket for UR43	0.85
Couplers	
BU21 S0259 back to back female	0.85
BU22 S0259 back to back male	1.32
BU23 S0259 elbow male to female	0.98
BU24 Double female single male T coupler	1.35
BU25 Triple female T coupler	1.55
BU26 Female to female lightning arrestor	1.12
BU27 Female to male lightning arrestor	1.30
BU28 Triple female single male X coupler	2.05
BU29 Chassis mount back to back female	0.98
Adaptors	
BU35 UHF male to N male	N/A
BU36 UHF male to N female	2.93
BU37 UHF female to N male	2.93
BU38 UHF female to N female	2.65
BU39 UHF female to phono/car aerial male	0.65
BU40 UHF male to phono female	0.65
BU41 UHF female to 3.5mm jack plug	0.68
BU42 S0259 to push on PL259 adaptor	0.85

★★ Also see BNC adaptors ★★

BNC CONNECTORS

Plugs	Price
BB01S For 0.2" cable (UR43)	0.98
BB02S For 0.25" cable (UR90)	1.05
BB03S Elbow for 0.2" cable (UR43)	N/A
Sockets	
BB11S Chassis mount 4 fixing hole type	0.98
BB12S Single hole long thread type	0.96
BB13S Single hole short thread type	0.90
BB14S Inline socket for 0.2" cable (UR43)	0.99
Couplers	
BB21S Back to back female	1.24
BB22S Back to back male	1.90
BB23S Elbow male to female	2.17
BB24S Double female single male T coupler	2.61
BB25S Triple female T coupler	2.34
BB26 Back to back female chassis mount	1.36
Adaptors	
BB31 BNC male to UHF male	1.63
BB32 BNC male to UHF female	1.29
BB33 BNC female to UHF male	1.45
BB34 BNC female to UHF female	1.15
BU35 BNC male to phono female	0.95
BU36 BNC female to phono male	0.95
BU37 BNC female to 3.5mm jack plug	1.15

★★ Also see 'N' type adaptors ★★

N TYPE CONNECTORS

Plugs	Price
BN01S For 0.2" cable (UR43)	2.45
BN02S For 0.33" cable (RG-56,21/U)	2.45
BN03S For 0.4" cable (UR67)	2.45
BN04S For 0.55" cable (UR83 & RG14/U)	2.93
Sockets	
BN11S Chassis mount 4 fixing hole type	1.58
BN12S Chassis mount 2 fixing hole type	1.58
BN13S Single hole fixing type	1.25
BN14S Inline socket for UR67 cable	2.05
BN15S Inline socket for UR43 cable	1.86
Couplers	
BN21S Back to back female	1.85
BN22S Back to back male	2.73
BN23S Elbow male to female	2.54
BN24S Double female single male T coupler	3.75
BN25S Three female T coupler	3.05
Adaptors	
BN31S N male to BNC male	N/A
BN32S N male to BNC female	2.05
BN33S N female to BNC male	1.95
BN34S N female to BNC female	1.63

★★ Also see UHF adaptors ★★

HIGH QUALITY NICAD BATTERIES

Format	Capacity	Prices
AA	0.50Ah	1-9 10-24 25-99
*AA	0.50Ah	0.90 0.85 0.82
*AA	0.50Ah	0.96 0.91 0.88
*AA	0.25Ah	1.20 1.14 1.08
*A	0.45Ah	1.53 1.45 1.38
*RR (sub C)	1.20Ah	1.70 1.61 1.52
C	2.20Ah	2.40 2.30 2.20
D (sub D)	1.20Ah	2.40 2.30 2.20
D	4.00Ah	3.50 3.32 3.15
*D	4.00Ah	3.59 3.41 3.24
*F	7.00Ah	6.85 6.50 6.20
*SF	10.00Ah	10.50 9.50 8.90
PP3	0.11Ah	4.35 4.10 3.85

Denotes solder tags fitted

NICAD CHARGERS

AC1	Soft Mazda AA charger, charges 1 to 4 AA cells	£5.90
MC2	Altai Multicharger, charges 1 to 4 AA, C, D cells plus 1 PP3 cell.	8.50
PC3	Soft Mazda PP3 charger, charges 1 or 2 PP3 cells.	6.90
MC4	Jackson Multicharger, charges 1 or 2 AA, C & D cells.	7.25
MC5	Jackson Multicharger, charges 2 or 4 AA, C & D cells or 1 or 2 PP3 cells.	8.50

FERRITES

Ferrite rings for TVI suppression (data supplied).	
Small type, 1 1/2" dia x 1/2" (FX1588 material)	0.42
Large type, 1 1/2" dia x 1/2" (FX1588 material)	0.80
Ferrite Beads.	
Single hole type 4mm dia (FX1115)	0.05
Six hole type 6mm dia (FX1898)	0.15

PREAMP TRANSISTORS

3SK88	145MHz, 26dB gain, 1-1dB NF	0.95
BF981	145MHz, 18dB gain, 0.7dB NF	1.20
BFR91	432MHz, 18dB gain, 1.9dB NF	1.35

R.F. POWER TRANSISTORS

MRF260	145MHz, 10dB gain, 5W output	6.56
MRF261	145MHz, 6dB gain, 10W output	8.74
MRF262	145MHz, 6.3dB gain, 15W output	14.40
MRF264	145MHz, 5.2dB gain, 30W output	15.26
MRF221	145MHz, 6.3dB gain, 15W output	17.60
MRF247	145MHz, 7dB gain, 75W output	40.74
MRF245	145MHz, 6.4dB gain, 80W output	44.25
MRF475	1.5-30MHz, 10dB gain, 12W PEP	4.95

All figures for gain & output power are minimum values, full data supplied with all orders. Send SAE for free data sheet on any of the above transistors.


OUR GUARANTEE

Our aim is to provide you with high quality products at realistic prices, to give you the best value for your money.

All products that carry our logo are designed and built by our engineers in the UK and carry a full 12 month guarantee which includes all parts and labour. We are so confident that our products are simply the best that we offer to repair your line at component cost for up to 5 years from date of purchase. That means we will repair, calibrate and return to you free of charge.

All other products sold by us carry our standard 12 month guarantee.

BNOS 'A' SERIES POWER SUPPLIES

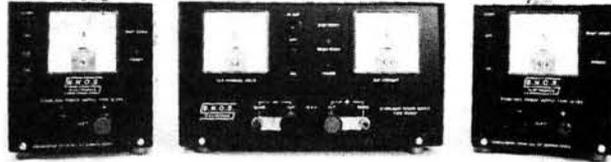

12/6A £48.30
 * 13.8V, 6A continuous output
 * 7A maximum output current
 * 10A current meter
 * 10A output terminals
 * LED shut down indicator
 * Fully protected

12/12A £86.40
 * 13.8V, 12A continuous output
 * 15A maximum output current
 * Large 20A current meter
 * 15A output terminals
 * LED shut down indicator
 * Fully protected

12/25A £125.45
 * 13.8V, 25A continuous output
 * 30A maximum output current
 * Large 30A current meter
 * 30A output terminals
 * LED shut down indicator
 * Fully protected

12/40A £225.40
 * 13.8V, 40A continuous output
 * 50A maximum output current
 * Large 50A current meter
 * Large output voltmeter
 * LED shut down indicator
 * LED out of regulation indicator
 * Output sensing terminals
 * Fully protected

UK AGENTS

Amateur Radio Exchange
 373 Uxbridge Road
 Acton, London.
 01-992 5765

Bredhurst Electronics
 High Street
 Handcross, West Sussex
 0444-400786

Dewsbury Electronics
 176 Lower High Street
 Stourbridge, West Midlands
 0384-390063

Radio & Electronic Services
 Le Grenier
 Rohais, St Peter Port
 Guernsey, C.I.
 0481-28837



Scotcomms
 23 Morton Street
 Edinburgh
 031-657 2430

★★★ THE BNOS RANGE OF 2 METRE LINEAR/PRE-AMPLIFIERS ★★★

This new range of 144MHz solid state Linear Amplifiers has been introduced to use with the increasingly popular low and high power transceivers currently available. Utmost care has been taken to produce a reliable unit with performance characteristics and extra features previously not available in the UK. The pre-amplifier* uses the highly regarded BF981 ultra low noise MOSFET transistor at 12dB gain level to give significant improvement in system performance. The LED bargraph power meter* facility gives clear bright indication of peak power available during transmission. Modern push button switches are used for all function controls* and high brightness square LED's for function indication.

*on LPM models only.

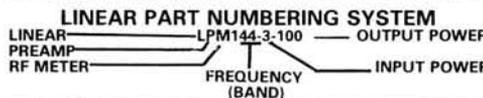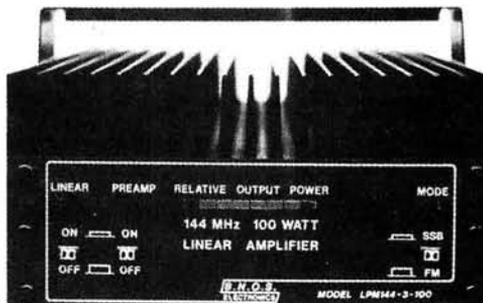Model available to suit the following transceivers:- FT290, C58, IC2, TR9000, IC290, FT480, etc.



FEATURES

- * Continuous rated RF output power (RMS)
- * Linear all mode operation
- * Straight through mode when switched off
- * RF and HARD switched change over with selectable delay
- * Excellent input match to drivers
- * Unique over drive protection circuit
- * All connectors supplied
- * Mobile mount
- * Extra low noise receive preamp
- * Designed and built to commercial standards in the UK by B.N.O.S. Electronics.

PRICES

L144-1-100	1 Watt input linear	138.00
L144-3-100	3 Watt input linear	138.00
L144-10-100	10 Watt input linear	115.00
LPM144-1-100	1 Watt input linear/preamp	172.50
LPM144-3-100	3 Watt input linear/preamp	172.50
LPM144-10-100	10 Watt input linear/preamp	149.50
L144-25-160	25 Watt input linear	155.00
LPM144-25-160	25 Watt input linear/preamp	189.50
L144-10-180	10 Watt input linear	178.00
LPM144-10-180	25 Watt input linear/preamp	212.50

ALL GOODS ARE NORMALLY EXSTOCK AND ARE DESPATCHED BY RETURN POST. TELEPHONE CREDIT CARD ORDERS WELCOMED.



BNOS Electronics, Dept PW, Greenbarrow, Dutton Hill
 Gt Dunmow, Essex CM6 3PT. Tel: (0371 84) 767

All prices inclusive of VAT. SAE for further details

POSTAGE FREE ON ALL MAINLAND UK ORDERS OVER £5,
 for orders under £5 please add 60p for P&P



BUSINESS HOURS
MONDAY TO SATURDAY
 9.00 am to 6.00 pm.

S.E.M.

UNION MILLS, ISLE OF MAN Tel: MAROWN (0624) 851277



PLEASE NOTE that all our Dual Gate MOSFET 2m pre-amp and Power/Pre-amps have always used the BF981.

S.E.M. TRANZMATCH

The most VERSATILE Ant. Matching system. Will match from 15-5000 Ohms BALANCED or UNBALANCED at up to 1kW. Link coupled balun means no connection to the equipment which can cure TV1 both ways. SO239 and 4mm connectors for co-ax or wire feed. 160-10 metres TRANZMATCH **£75.50**. 80-10 metres **£67.50**. EZITUNE built in for **£24 extra**. (See below for details of EZITUNE). All ex-stock. We sell many more with EZITUNE fitted.

3 WAY ANTENNA SWITCH 1kW SO239s. Good to 2 metres. **£15.00 Ex stock**. Or 4th position to earth output **£17.50 Ex stock**.

S.E.M. 2 METRE TRANZMATCH. 5 1/2" x 2", 3" deep. SO239s. **£24.90 Ex stock**.

S.E.M. EZITUNE (with New Look)

Because no similar unit is made, it's usefulness is not appreciated until you have used one.

We could not improve its performance, so we improved its appearance. Clean up the bands by tuning up without transmitting.

Connects in aerial lead, produces S9 + (1 - 170MHz) noise in receiver. Adjust A.T.U. or aerial for minimum noise. You have now put an exact 50 Ohms into your transceiver. Fully protected, you can transmit through it, save your P.A. and stop QRM. SO239s. **£29.50 Ex stock**. P.c.b. to fit any A.T.U. **£24 Ex stock**.

NEW. RF NOISE BRIDGE. Adjustable 0-1,000 ohms, 3" x 1 1/2" x 2" only. SO239s, 1-170MHz. **£29.50 Ex stock**.

SENTINEL 2M LINEAR POWER/PRE-AMPLIFIERS

Now feature either POWER AMP alone or PRE-AMP alone or both POWER AND PRE-AMP or STRAIGHT THROU when OFF. Plus a gain control on the PRE-AMP from 0 to 20dB. N.F. around 1dB with a neutralised strip line DUAL GATE MOSFET (BF981).

Ultra LINEAR for all modes and R.F. or P.T.T. switched. 13.8V nominal supply. SO239 sockets.

Three Models:

1. **SENTINEL 35** Twelve times power gain. 3W IN 36W OUT. 4 amps. Max. drive 5W. 6" x 2 1/2" front panel, 4 1/2" deep. **£62.50 Ex stock**.
2. **SENTINEL 50** Five times power gain. 10W IN 50W OUT. Max. drive 16W 6 amps. Same size as the Sentinel 35. **£74.50 Ex stock**.
3. **SENTINEL 100** Ten times power gain. 10W IN 100W OUT. Max. drive 16W. Size: 6 1/2" x 4" front panel, 3 1/2" deep. 12 amps. **£115 Ex stock**.

POWER SUPPLIES for our linears 6 amp **£34**. 12 amp **£49**.

SENTINEL AUTO 2 METRE or 4 METRE PRE-AMPLIFIER

1dB N.F. and 20dB gain, (gain control adjusts down to unity) 400W P.E.P. power rating. Use on any mode. 12V 25mA. Sizes: 1 1/2" x 2 1/2" x 4". **£28.00* Ex stock**.

PA5 Same specification as the Auto including 240V P.S.U. **£33.00***

SENTINEL STANDARD PRE-AMPLIFIER. No R.F. switch. **£15.00* Ex stock**.

PA3. 1 cubic inch p.c.b. to fit inside your equipment. **£10.00 Ex stock**. 70cm versions of all these (except PA5) **£4.00 extra**. All ex stock.

S.E.M. AUDIO MULTIFILTER (Improved appearance).

To improve ANY receiver on ANY mode. The most versatile filter available. Gives "passband" tuning, "variable selectivity" and one or two notches. Switched Hi-pass, Lo-pass, peak or notch. Selectivity from 2.5KHz to 20Hz. Tunable from 2.5KHz to 250Hz. PLUS another notch available in any of the four switch positions which covers 10KHz to 100Hz. 12V supply. Sizes: 6" x 2 1/2" front panel, 3 1/2" deep, all for only **£57.00 Ex stock**.

SENTINEL AUTO H.F. WIDEBAND PRE-AMPLIFIER 2-40MHz, 15dB gain. Straight through when OFF. 9-12V. 2 1/2" x 1 1/2" x 3". 200W through power. **£19.55* Ex stock**.

SENTINEL STANDARD H.F. PRE-AMPLIFIER. No R.F. switching. **£12.62* Ex stock**.

S.E.M. IAMBIC KEYS

The ultimate auto keyer using the CURTIS custom LSICMOS chip. Tune and sidetone Switching. **£34.50 Ex stock**. Twin paddle touch key. **£12.50 Ex stock**.

S.E.M. VISA 80 METRE RECEIVER

Already a great success. If you want an 80 metre (3.5-3.8MHz) Rx. Only 2 1/2" x 6" x 3". 12 volt operation. I.W. o/p. This is for you. **£45**.

FREE. CONVERTERS from 10KHz to 2 metres in stock.

12 MONTHS COMPLETE GUARANTEE INCLUDING ALL TRANSISTORS.

Prices include VAT and delivery, C.W.O. or phone your credit card number for same day service.

*Means Belling Lee sockets, add £1.90 for SO239s or BNC sockets. Ring or write for more information. Place orders or request information on our Ansaphone at cheap rate times.

Goods normally by return.

THE 2m switched preamplifier

mu Tek limited's SLNA 144s is the better alternative to the previous generation of in-line, rf-switched 2m preamplifiers.

- **Low noise:**
Noise measure of 0.9dB typical
- **Gain:**
15dB typical
- **Bandwidth:**
144-146MHz ± 1dB, more than 45dB rejection at 130 and 160MHz. Compare this with the older generation!
- **Power Handling:**
100W through power
- **Advanced switching control:**
 - rf sensing with switch selectable 'fast' and 'hang' modes!
 - single line ground to transmit control for hard switched applications eliminates annoying relay noise experienced with other amplifiers!
 - rf over-ride of hard-switching function to prevent expensive accidents!
 - straight-through operation with power off. Failsafe!
- **Power and control connections:**
via feedthrough capacitors—minimises supply-line pick-up and noise problems.
- **RF connectors:**
50Ω BNC
- **Case:**
Diecast, size 50 x 100 x 25mm (excluding connectors)
- **Plus internationally acclaimed muTek quality!**

Price: **£37.10 (p&p £1.20) inc VAT**

muTek limited — the rf technology company

Bradworthy, Holsworthy, Devon EX22 7TU (0409 24) 543

Please allow up to 28 days — we try to be faster

PRACTICAL WIRELESS P.C.Bs

We have in stock PCBs for every Practical Wireless project from 1978, so delve into those back issues of Practical Wireless and find that project you promised yourself you would build, then give us a call and we will be pleased to quote you for the PCBs.

E.G. January 1980 AF Speech Processor WR068 **£2.98**
Full Kit for above **£23.50**

This is just one of the many exciting projects you can build from Practical Wireless.

Aug 1982	PW 28 Mhz Pre-amp	WR153	£2.00
Aug 1982	PW Morse Show	WR152	£8.00
Oct 1982	PW Cranborne	WR154	£12.00
Oct 1982	PW Cranborne	WR155	a Set
Nov 1982	PW Cranborne	WR159	£3.00
Nov 1982	PW Repeater Time Out Alarm	WR156	£2.00
Nov 1983	PW 435 Mhz Input Pre-amp		£3.00
Nov 1982	PW 605 Mhz Output Amp		£3.00
Feb 1983	LMS Regenerative Receiver	WR160	£2.50
Feb 1983	VHF/UHF Dummy Load	WR162	£2.50
Apr 1983	Durley Sinad	WR164	£2.00
Apr 1983	Durley Sinad	WR163	£3.50
June 1983	PW Seven	WR165	£2.50
June 1983	PW Seven	WR166	£3.25
June 1983	PW RTTY	WR167	£4.50
July 1983	Marchwood Power Unit	WR161	£3.00
July 1983	PW Seven	WR169	£2.75
July 1983	PW Seven	WR168	£2.00
July 1983	PW Prescaler	WR172A	£3.00
July 1983	PW Prescaler	WR171	£1.75

Suppliers of R.S. Components.

Barclaycard Visa Please send Cash with Order

Access



C. BOWES ELECTRONICS LTD

28 Stockport Road, Cheadle SK8 2EA

Tel: 061 428 4497 Extension 5

Goods by Return



on the air

Aylesbury Vale RS Plenty of meat in the club's *Newsletter* with general news of amateur radio doings far and wide, members' letters and technical items like trials and tribulations with the ZL special on 144MHz, by G8VEL. Meetings every four weeks on a Tuesday at 8, the Stone Village Hall, Stone, the September feature being a lecture by S. J. Davies G4KNZ on an introduction to microwaves on the 6th. Better tell you now of the October 4 date which is Robin Hewes G3TDR describing a 1.8/3.5MHz transceiver. For more details ring Cathy Clark on (0844) 51461 but she may be QRL studying for the RAE she expects to take in December.

Banbury ARS Unfortunately I can't give you the date on which a lecture will be given on the very interesting work on satellites being done at the well-known Kettering Grammar School but I'm sure sec John Burrell G8OZH, 6 Blenheim Croft, Brackley, Northants (B'ley 702900) will know by now. It's all at St Pauls Church Hall, Warwick Road, B'bury, on the last Friday, scene also of junk sales, film shows, lectures and suchlike, not forgetting a monthly DF hunt.

Biggin Hill ARC Hon sec is Ian Mitchell G4NSD, 37B The Grove, Biggin Hill, Westerham, Kent, who says the club meets on the second and third Tuesdays, at the Biggin Hill Memorial Library. A recent family day out was combined with an equipment junk sale which proved extremely popular and sounds like a very good idea to me. Two birds with one stone and all that sort of thing. Now, on September 20 the evening is devoted to RTTY matters and the subject on October 18 will be amateur satellites. Ian can also be reached on Biggin Hill 75785.

Brighton & District ARS G4GQR G8OMR Alternate Wednesdays at 7.30 at the Marmion Road YMCA, Brighton, which means September 21 when the vision side of amateur radio will be dealt with by the Worthing & District TV Repeater Group. For further info it's Wendy Firmager, 26 Brownleaf Road, Brighton.

Bury RS At the Mosses Community Centre, Cecil Street, Bury, Lancs at 8, main meeting on second Tuesdays, remaining Tuesdays are informal, but note that the Centre is closed on September 20. On the 13th Norman Kendrick G3CSG details his experiences in the last war with the Japanese equivalent to our Morse code. Visitors and potential members are invited to contact sec Brian Tyldsley G4TBT, 4 Colne Road, Burnley, or try Burnley 24254.

Cheshunt & District ARC G4ECT G6CRC Wednesdays at 8, Church Room, Church Lane, Wormley, with natter nites on September 7 and 21 and an outing to the Brookmans Park transmitter site on September 14. On September 28 the club will welcome the RSGB's Assistant General Manager John Nelson for a talk. The nearby East Herts College at Turnford will be running an RAE course from September aiming at the May '84 exam, while a beginners' class in the Morse code is also being organised in the area. Details of both the RAE and code classes from chairman Jim Sleight G3OJJ, 18 Coltsfoot Road, Ware, Herts otherwise ring him on (0902) 4316.

College of Technology, Belfast ARS G12BX Formed at the beginning of the year the club meets most lunchtimes using the club

station on the v.h.f. and h.f. bands. Talks on such subjects as SSTV by G18PDT and on 432MHz fast scan TV by G18RKC are planned, so watch GB2RS for details. Anyone interested in giving a talk on AR matters should contact the sec James Barr, 121 Kitchener Street, Belfast BT12 6LF, otherwise at the college on B'fast 227244 ext 243.

Cornish Radio Amateur Club A change of venue makes it now the Church Hall, Treleigh, on the old Redruth bypass, while the computer group of the club meets at the Social Clubroom of the SWEB in Penryn Street, Redruth, also a new spot. Too late to tell you of September meetings of the main club but the computer section will have G3VWK talking on basic computer routines on September 19. Wide-ranging club mag *Cornish Link* makes an interesting read, but more from PRO S. Rodda G4PEM, Cliff Hotel, Penrose Terrace, Penzance, which is where (0736) 3948 also resides.

Edgware & District RS G3ASR G8ERS New publicity officer for the club is David Wilkins G4JLU, 802 Kenton Lane, Harrow Weald, Middx. Meetings second and fourth Thursdays at 8, 145 Orange Hill Road, Burnt Oak, Edgware, Middx include code classes augmented by slow Morse over the air from G3ASR on Top Band and 144MHz. Forthcoming events include Basic Programming by John Bluff G3SJE on September 22 and a Sunday afternoon DF hunt on October 2.

Fareham RC Club programme is littered with NN/OTA's which after some thought I resolved as natter-nite and on-the-air! as on September 7, 21 and October 5. In between on September 14 G8GNB talks on safety in the shack while old timer G6NZ outlines the history of the RSGB on the 28th. So it's every Wednesday at the Portchester Community Centre, in Room 12 at 7.30, says sec Brian Davey G4ITG, 31 Somervell Drive, Fareham, Hants and F'ham 234904.

Farnborough & District RS Club membership now 98 so if you get in quick you might be the hundredth, for free! Second and fourth Wednesdays at 7.30 in the Railway Enthusiasts Club, Access Road, off Hawley Lane, F'boro. Features for September are a pre-AGM discussion on the 14th (AGM on November 9) and a constructional contest on the 28th. I don't usually mention past events but the club thoroughly enjoyed the chat on antennas from Louis Varney G5RV. Club PRO is Chris French G8ZAJ, 26 Wood Street, Ash Vale, near Aldershot, Hants, otherwise A'shot 29469.

Fingal RC EI2FRC Now has new TS120S rig for the h.f. bands with trapped vertical antenna and active on club nights with 144MHz net on Mondays at 8. On September 5 Harry EI2W will deal with 50 years of amateur radio, at the club's premises at the Scout Hall, Ballygall Road East, Dublin 11. More info from sec. Gerry Birkhead EI9DZ, 103 Roselawn Road, Castleknock, Co Dublin, Eire. He can also be reached on Dublin 210261.

Flight Refuelling ARS G4RFR G6SFR On Sunday September 4 it's G6DUN dealing with earthing and electrical safety and a week later G3VMO describes amateur radio operating overseas. G8MCQ runs a "Nick's Rambles" session on Sunday 18th and the month ends with John Reid showing the use of radio in remote control and telemetry, on the 25th. As

you will have guessed it is Sundays, at the Sports and Social Club, Merley, Wimborne, Dorset, and Mike Owen G8VFX, "Hamden", 3 Canford View Drive, Canford Bottom, Wimborne will be glad to advise you on times of meetings etc or buzz him on (0202) 882271.

Leighton Linlade RC G4LLR G6LRC Looks like the first and third Mondays from 7pm at the Vandyke Community College, Room A64, Vandyke Road, Leighton Buzzard with the AGM on September 5 with better things on the 19th when it's time for a return quiz contest with the Milton Keynes lads and lassies. Sat/Sun September 10/11 is BATC international contest weekend with the club participating. More from Pete Brazier G6JFN, Kingsway Farm, Miletree Road, Leighton Buzzard, Beds or you can get him on 052 523 270.

Maltby ARS On its first birthday the club boasts a membership of 50 with regular attendances of 35 or more. Every Friday at 7, at the Methodist Church Hall, Blythe Road, Maltby, with Morse code classes and a computer section, the main item of the evening starting around 8.45. DF hunts are expected to be a further addition to the club's activities very soon. PRO is Alex Paduick, 22 Falcon Way, Dinnington, Sheffield S31 7NY.

Midland ARS A reminder of the 48-hour Marathon On-the-Air from the club at 294a Broad Street, Birmingham, starting at 1700Z on Friday September 23 using special callign GB4MAR using h.f. and 144MHz bands. Details of this from R. Blaikie G4OGR, 22 Eileen Road, Sparkhill, B'ham or K. L. Townsend G4PZA on 021-474 6517. On general club matters Tom Brady G8GAZ at 57 Green Lane, Great Barr, B'ham will be glad to help.

Mid-Sussex ARS G2ZMS Programme details, temporarily, from Bob Hedge G4MMI on Hurstpierpoint 833559, or Corner House, Manor Gardens, Hurstpierpoint. Club gossip is well catered for in club mag *Mid-Sussex Matters* and I see that Louis Varney G5RV is a member of the club, although he seems to be in CX-land much of the time now. Club foregatherers at the Marle Place Adult Education Centre, Leylands Road, Burgess Hill, W. Sussex on second and fourth Thursdays but contact Bob for latest info.

Mid-Warwickshire ARS First and third Tuesdays it is, at 61 Emscote Road, Warwick, with visitors most welcome at any meeting. September 6 is junk sale time with an evening DF hunt organised for the 20th. Carol Finnis G4TIL, 37 Stowe Drive, Southam, Warks is your contact for more club info, or on (092681) 4765.

Nene Valley RC G4NWZ G6GWZ Every Wednesday at 8, the Dolben Arms, Finedon, near Wellingborough, Northants, and a nice choice of items for September, like satellite working described by G4HME on the 7th, RTTY by computer by G8GIK on the 14th, and a lecture on QRP working by expert George Dobbs G3RJV on the 21st. RAYNET is the subject for G4NUG on the 28th. Waiting to fill in the details is Lionel Parker G4PLJ, 128 Northampton Road, Wellingborough, Northants.

North Bristol ARC G4GCT Briefly, every Friday at 7, the Self-Help Enterprise Centre, 7 Braemar Crescent, Northville, Bristol. By the time you read this Ted Bidmead G4EUV, 4 Pine Grove, N'ville, will be able to tell you about the forthcoming programme of events.

Northern Heights ARS The Bradshaw Tavern on Wednesday at 8 preceded by a code class at 7.30. No up-to-date programme available so contact sec Brian Aspinall G6CJL, 11 Buck Street, Denholme, Bradford, 'f'one B'ford 834442.

Perth & District Radio Group Every Tuesday evening at its own clubroom in the Perth City Sports and Social Club, Leonards Street, Perth from 8.30. In addition Wednesdays sees Morse code classes under way coupled with club constructional projects. The club has its own station on h.f. and belongs to the local RAYNET group. Computer addicts are also catered for, some linking them to RTTY equipment. More from sec R. H. Barnes GM6ESY, Pittendyrie Cottages, Moneydie, near Luncarty, Perth, Scotland.

Radio Club of Thanet G2IC It is still the Grosvenor Club, Margate, second and fourth Tuesdays which, on September 13, means a talk by a member of the RSGB's Interference Committee, followed on the 27th by a visit from an official of the SE Electricity Board. The club is also running an RAE course starting about the time you read this. Sec is Ken Lown G4PTE, 119 Sea Road, Westgate-on-Sea, Kent (0873) 32198.

Ripon & District ARS Thursdays at 7 starting with RAE and Morse code classes, then coffee and the evening's chat, talk, lecture or whatever not to mention the possibility of a demo of AR gear or a film. All at the St John Ambulance Hall, Ripon. Sec is Peter Fautley G6CUG, Parkside, Thornton-Le-Street, Thirsk (0845) 24945.

Salop ARS G3SRT HQ is the Albert Hotel, Smithfield Road, Shrewsbury at 8 every Thursday with highlight for September being the fourth and final DF hunt on the 29th. More details from sec D. Goddard G3UQH, 4 Gravels Bank, Minsterley, Shropshire.

Spalding & District ARS G4DSP Second Friday of the month at 8, Maples Room, White Hart Hotel, Market Place, Spalding, Lincs. with a visit from a Mike Bowthorpe on September 9 which doesn't mean much without a call sign, if he has one! More from sec Ian Buffham G3TMA, 45 Grange Drive, Spalding, Lincs. Now, on October 14 there is a talk on computers in amateur radio by Terry

Roberts G6IDW which sounds a lot more interesting!

Stevenage & District ARS Aluminium for antennas is the subject for September 6 by G4MEO while a special event is the Beginners Evening showing off amateur radio at the Fairlands Community Centre on Thursday September 8. Normally it is the first and third Tuesdays at 8 at TS Andromeda, Fairlands Valley Park, Shephall View, Stevenage, Herts, with code classes a bit earlier at 7.15. Club net is on Sundays on 145-250MHz at 7pm. For more details try Cliff Barber G4BGP, 13 The Sycamores, Baldock, Herts, also 893736.

Stourbridge & District ARS G6OI G6RSR First and third Mondays at 8, at the Garibaldi, Cross Street, Stourbridge. From an excellent programme that goes right through to next March I see that there is a meeting on September 5 to make final arrangements for the Stourbridge Carnival taking place on the Saturday September 10 when the club will be running a demonstration station. Dave Yates G3PGQ talks on s.w.r. and matching circuits on the 19th. October 3 is de-briefing time for the past contest season, no doubt with determination that this year's goofs won't be repeated next year, if there were any of course. Sec is Malcolm Davies G8JTL, 25 Walker Avenue, Quarry Bank, Brierley Hill, or ring 038 482 4019.

Sutton Coldfield RS Second and fourth Mondays, at the Central Library, Sainsbury Centre, SC at 7.30, September 12 being a natter nite, with a chat on test equipment by John Symes G3LNN and Richard Burrows G8ALO on the 26th. Sec is Derek Turner G8TUR, 10 Jervis Crescent, SC.

Swale ARC G4SRC Special event station GB2LBC will be run at the London Bible College on Friday to Sunday September 9 to 11 on h.f. and v.h.f. bands on the occasion of the 26th anniversary of the World Association of Christian Radio Amateurs. You will want to know that the LBC is not in London but at Green Lane, Northwood, Middx, if you feel like calling in. More from Brian Hancock G4NPM, Leahurst, Augustine Road, Minster, Sheppey, Kent or Minster 873147.

Torbay ARS G3NJA G8NJA Meets every Friday and last Saturday in the month at Bath

Lane which is at the rear of 94 Belgrave Road, Torquay. Principal event is on September 24 when G3PBV holds forth on v.h.f./u.h.f. operation. Club sec is Margaret Rider, 7 Kingston Close, Kingskerswell, S. Devon, also (08047) 5130 who just happens to be the XYL of G6GLP.

Wakefield & District RS G3WRS Walter Parkin G8PBE has gone to great lengths to explain the situation in his area where there are several clubs active, to ensure prospective members find the club best suited to them. There is his own club about 0.5km south of the city centre, the North Wakefield RS 5km north and the Pontefract RS about 16km from Wakefield on the outskirts of Pontefract. The W. Yorks Police RS is confined to its own staff and is located near to Wakefield city centre. The Wakefield group meets on alternate Tuesdays at 8 at the Holmfild House, Denby Dale Road, W'field, which is a municipally-owned mansion with good parking facilities. Dates look like September 6 which is on-the-air cum natter nite and the 20th when it's Home Brew Evening, equipment that is! On October 4 Computers for Beginners is the theme for Steve Wright G4CPC and a break for all on the 18th when it's pie and peas time. Back to sec Walter Parkin who lives at 14 Cleveland Grove, Lupset Park, Wakefield, W. Yorks and will be glad to assist with any enquiries.

Wimbledon & District RS An RSGB feature film, subject unknown at the moment, should prove popular on Friday September 30. Earlier, on the 9th, it's club clinic time, an evening devoted to getting that odd bit of gear going again, with the help of all concerned. Pop along any Friday around 8 to the St John Ambulance HQ at 124 Kingston Road, London SW19 where you will be most welcome. Contact Geoff Mellett G4MVS at 26 Paget Avenue, Sutton, Surrey beforehand if you wish or phone 01-644 8249.

A note for newly-formed clubs. Don't miss the opportunity to publicise your club in these columns if you are looking for new members. It's quite free, just write direct to me with the details of club meeting place, times, and day/s of the month and of any events that have been organised which are at least six weeks away.

MEDIUM WAVE BROADCAST BAND DX by Charles Molloy G8BUS


Reports to: Charles Molloy G8BUS, 132 Segars Lane, Southport PR8 3JG.

The current decline in solar activity with consequent move from higher to lower frequencies by some short wave broadcasters is also having an effect on medium wave DXing. July 1 this year at my QTH found CJYQ in St John's, Newfoundland, on 930kHz, peaking up out of the noise at 0012UTC. This is the earliest I can remember hearing North America in midsummer. Half-an-hour later the signal was strong enough to monitor, so I thought I'd have a look for carriers from possible DX from the United States. On went the b.f.o. and sure enough there was a whistle on 1130kHz, hopefully from WNEW in New York City. The interval between sunset in Newfoundland and New York is at a minimum in summer because the terminator, which is the

dividing line between day and night on the earth's surface, lies in a NNE-SSW direction at sunrise at that time of year. Just as well, as DXing finishes shortly after sunrise in the UK and the nights are short.

The next couple of hours brought another six Canadians, VOXM on 590kHz, CBNA/600, CKYQ/610, CKCM/620, CDBGY/750, CKLM/1570, plus WMRE in Boston on 1510, WNEW on 1130, WCAU Philadelphia 1210, WBAL Baltimore 1090 and WHN on 1050. The latter, in spite of an annoying heterodyne, was a fairly solid signal for half-an-hour with a sports commentary and YL announcer giving the identification "WHN in New York". The receiver used was my modified DX160 with 30m

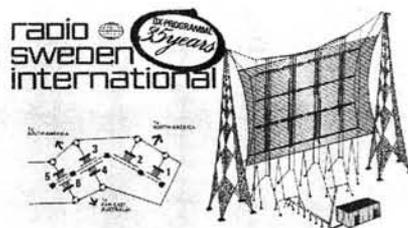longwire when I could get away with it and a loop when I could not. I can switch from loop to longwire as required.



Sweden—card to commemorate 35th anniversary of Sweden Calling DXers sent by Shoyab Patel

The prospect of some good DX on the medium waves this winter makes this an opportune moment to introduce the band to the newcomer. There are more broadcasters on the medium waves than on all of the short wave bands put together, some 4000 in the United States alone, so the potential for DXing is certainly there. The problem, of course, is how to winkle it out.

DX Likely to be Heard

North America, with the exception of Alaska, Central and South America, the Caribbean, all of Africa, most of Asia including Japan, have been logged in the UK. Alaska is not heard as the track is over the north magnetic pole where absorption of radio signals is high. The Pacific and Australasia have not been logged in the UK in recent times.

There is one criteria that must be met for reception to be possible. There has to be darkness along the path between TX and RX. During daylight the D layer of the ionosphere, which absorbs signals in the medium wave part of the spectrum, will be in existence. The best DX will be heard at times of low solar activity, the peak occurring at the minimum of the 11-year sunspot cycle. The next one is expected in 1987.

Make a Start Now

The eastern coasts of North and South America plus the Caribbean are a good hunting-ground for the beginner. At this time of the year CJYQ should be audible by 2300UTC on 930kHz, provided the North American path is open. The letters CJYQ make up the callsign which is used frequently either in full or in abbreviated form, such as "Q Radio" or "Q93". Every medium wave station in Canada and the United States has a callsign which it is obliged to use for identification, and this of course helps the DXers.



WHN New York City on 1050kHz

Listen for the out-of-band Caribbean Lighthouse on 1610kHz which sends out religious programming from Anguilla. There is also the Voice of America relay in Antigua on 1580kHz. Both of these stations are heard regularly in the UK. There is a different band plan in Region 2 (the Americas) than in Europe. Every station in Region 2 is on a frequency which is a multiple of 10kHz. Listen on these DX channels for Spanish, which may be from Colombia or Venezuela, or for Por-

tuguese which will be from Brasil. A full list of medium wave stations in Region 2 will be found in the *World Radio and TV Handbook*.

Slow deep fading is normal with DX on the medium waves. A strong station can fade to inaudibility in a minute or two and then come slowly back again. You can often recognise DX by this phenomenon, so tune slowly and if a channel sounds promising stay on it for a few minutes.

Receivers

A communications receiver and a medium wave loop antenna are normal tools of the trade for the serious DXer. They are by no means essential though, but the internal ferrite rod antenna used by portable receivers is really inadequate on its own except for the strongest of DX signals. The problem with these receivers is that they do not usually take kindly to a longwire and they cannot be used with a loop but it is always worth experimenting. A vintage valved receiver, designed for use with an external antenna and earth, often performs well for the DXer. Make the best use of whatever equipment is available. Tune carefully and slowly, investigating weak signals. If you tune quickly across the band then it is unlikely you will hear much DX even when using a powerful receiver.

Codes

As well as the abbreviations mentioned last month there is the Q Code used by amateurs. Some of these have crept into DXing. QRM is man-made interference, usually from another broadcaster. QRN is static (atmospherics), QSL is a verification of reception from a broadcaster, often in the form of a QSL card. QSB means fading while QTH is your home address. The full Q Code can be found in many amateur radio books along with the meanings appropriate to that branch of the hobby.

Technical Abbreviations

The labelling on the front panel of a RX, especially a communications set, may puzzle some users. The markings AGC stand for automatic gain control, which is an anti-fading device. With some sets there is a switch marked AGC FAST/SLOW. The slow position is for speech or music, while the fast position is used when listening to c.w. or s.s.b., though it is worth experimenting here. The letters SSB is single sideband, speech sounds like a duck quacking unless it is processed by a product detector. Then BFO is a beat frequency oscillator which is used to make some types of morse audible and there is a b.f.o. tuning control to adjust the pitch. The b.f.o. can also be used to unscramble a s.s.b. signal.

The control marked RF GAIN adjusts the sensitivity of the radio frequency sec-

tion of the receiver. A control marked ATT means attenuator. This does a similar job to the r.f. gain control but in a different way. It reduces the strength of the incoming signal from the antenna before it is processed by the rest of the receiver. The AF gain is just the volume control which adjusts the strength of the audio frequency signal before it is applied to the loudspeaker, and ANL is the automatic noise limiter which reduces the strength of some types of noise.



TransWorld Radio Montecarlo is on 1467kHz sent by Philip Hodgson

Readers' Letters

"Hello, I have decided to write in and tell you about my m.w. loggings," writes Vincent Stevens from Belleville in RSA. Using an FRG-7 with 25m longwire he pulled in a number of stations in North America and the Caribbean, most of them, surprisingly, heard regularly in the UK. The exceptions are KOA on 850kHz in Denver, Colorado, XERF in Mexico on 1570kHz, Volcano Radio (AFRTS) Ascension Island on 1602kHz. "I find the portion of the band 1500kHz to 1600kHz the best for DXing," concludes Vincent, which agrees with an observation made to me by Arthur Cushen of New Zealand a few years ago. He regularly logged European stations at the top of the band. The answer, I think, is that the F layer of the ionosphere is involved above 1500kHz as well as the more usual E layer propagation we find on this rather wide medium wave band.

Old timer John Ratcliffe from Southport in Queensland, Australia, writes to say: "I have been interested in m.w. DXing since 1923." Well, the medium wave is sometimes called the oldest DX band. In fact, at one time it was the only band! John started DXing with a one-valve regenerative receiver which in 1925 pulled in the 100 watt KFOX in Long Beach, California, for him. Currently he uses a National transistor job which brings regular reception of New Zealand some 1500 miles away. John is of the opinion that long range reception on the medium waves has declined over the years. It is difficult to answer this. At one time there were few stations on the medium waves and few domestic electric appliances in use so one could DX with simple equipment. Nowadays, most of us live in a fog of electrical noise while broadcasting in Europe alone pumps some 100 Megawatts into the ionosphere. None-the-less, I feel there might be something in John's claim.

SHORT WAVE BROADCAST BANDS by Charles Molloy G8BUS

Reports: as for Medium Wave DX, but please keep separate.

What sort of gear do you use? That is a question sometimes put by readers and since the set-up in my shack is by no means a static one, it might be interesting to have another look at it. There are two communications receivers. A realistic DX160, which is a low-priced transistor job no longer in production but easily obtained secondhand, and a BRT400 which is one of the more recent valved receivers designed about 30 years ago. Two antennas are in use. A 25 metre longwire running from house to a mast at the bottom of the garden and a length of wire in the loft. At the moment only one receiver can be used at a time, with a choice of antennas via a switch. An external digital readout unit can be switched to either set and the longwire is connected via an a.t.u. An audio notch filter, tape recorder, and a valve pre-selector are also available though the seldom used pre-selector is currently out of action. There was a smell of burning and the fuse blew!

Two Antennas

One would expect the longwire plus a.t.u. to pull in the DX, while the loft antenna would be the one for dealing with strong signals when programme listening. In practice, I switch antennas if not satisfied with reception, and the results are quite unpredictable. Co-channel QRM can often be reduced by changing antennas, so clearly the two have directional properties. The moral seems to be, put up more than one antenna if you can and have a switch so that you can select each in turn.

Transistors or Valves

The DX160 is the receiver normally in use. I like its compactness, layout of the controls, ease of handling and instant response to the ON/OFF switch. It has been modified to give improved selectivity and there is now a coaxial socket at the rear for the lead from the digital readout. The BRT400 has the edge for difficult reception having better selectivity. There is also a phasing control which moves a null across the i.f. passband. The BRT400 though is in a different category and the cost of a modern equivalent could be prohibitive.

The DX160 has a tendency to overload with strong signals, but not so much as I'd expected. It is easily cured by backing-off the combined r.f./attenuator control. Occasionally, I hear weak c.w. as a background to a strong signal. This is probably the result of oscillator harmonics. Just before packing up some medium wave DXing last July at 0430, I heard the VOA *Breakfast Show* on 1570kHz. It could not be heard using the BRT400. Some arithmetic followed. With

an i.f. of 455kHz the receiver oscillator would be 2.025MHz. The fifth harmonic is 10.125MHz, subtract 455kHz and we have 9.670MHz in the 31m band. I retuned to 9.670 and to my amazement there it was. The VOA transmitter at Greenville in the USA according to the *International Listening Guide*.

My impression after handling the DX160 is that the shortcomings of transistorised gear have been highlighted while the good points have been ignored. No smell of burning and blown fuse with the DX160! My next receiver, when I can afford one, will be a product of modern technology. The way is forward, not back.

WWV on the 'phone

The letters WWV make up the call sign of the Time Signal and Frequency Standard station operated by the US National Bureau of Standards at Boulder in Colorado. WWV can be heard in the UK on 10MHz, 15MHz and 20MHz depending on the time of day, the station being on the air continuously. At 18 minutes past the hour there is a propagation announcement which gives the A and K indices, the solar flux and a forecast for the following day. Reader Barry Davis of Warrington informs me that WWV maintains a 24 hour telephone service as well, which plays a recording of the propagation announcement. It can be reached direct from the UK by dialling 010-1-303-497-3235.

Sure enough, after a short pause came ringing out tone, and then the announcement which took approx. 25 seconds. The first 15 seconds covered the solar flux, A and K indices, which is probably all that most of us require. To recap from the May 1982 edition. Solar flux is on a scale going up to 200 and refers to the previous day, the A index goes up to 400 and is also for the previous day, the K index scale goes up to 9 and is updated every 3 hours (6 hours by WWV). Generally speaking, the higher the value of the solar flux, which is a measure of the degree of ionisation of the ionosphere, and the

lower the values for the A and K indices which relate to the earth's magnetic field, then the better it is for the propagation of radio waves on the short wave bands. Medium wave DXing will look for a low value for the solar flux (sunspot minimum).

The provision of a telephone service from WWV is to be welcomed. The station is seldom an outstanding signal at my QTH and reception is at its worst when conditions are unsettled and this, of course, is the time when the information is most valuable. There is also the difficulty facing the DXer in the UK who is not also a licenced amateur for, believe it or not, he is not supposed to listen to WWV! You need a licence. On the debit side there is the cost of a telephone call, even a short one, to Colorado. The peak rate is from 6 am to 8 pm Monday to Friday, so obviously it is better to avoid these times. There is also the uneasy feeling that for a DXer to turn to the telephone is a step in the wrong direction.

Radio Cairo

Although Egypt is a major broadcaster on the short waves, its English Programme is one of the less conspicuous. This is a pity as the content of the programme is both varied and interesting. In the space of an hour and a half there can be as many as 8 separate features which lead to variety and enable the listener to taste something fresh or unusual without the danger of boredom.



Cairo—An Egyptian pop group?

A selection from the weekly programme schedule for the second half of 1983 includes the *World of the Pharaohs*, *Tourism in Egypt*, *Tales and Legends*, *This is Islam*, *Stamp Collectors Club*, *Cairo Magazine* and *City of a Thousand Minarets*. Between the main items are interludes of music, old and new, from East and West.

Radio Cairo is on 9.805MHz (30.59m) nightly from 2115 to 2245 UTC. To quote their schedule, "we wish you all enjoyable listening and look forward to receiving your letters, reception reports, comments and suggestions".

ALOHA

WWVH



WWVH in Hawaii is a sister station to WWV sent in by R. S. Hunt

KEEN DX'ers (. . . and Competitors!) . . . please note a NEW 6 BAND QUAD! the DX-26Q

Covers 14, 18, 21, 24, 28 and 145MHz!

This quad has been engineered by G3NMH (our M.D.!) and is already giving a very good account of itself on the HF bands. By the way, G3NMH was, apart from winning a number of RSGB HF Contests, Second in a CQ World-Wide SSB Contest (using a quad), so you'll agree that he has some expertise in these matters. The larger captive area of the quad helps give this antenna the fantastic performance for which the quad is renowned.

So, order your DX-26Q NOW from **Western** and PENETRATE THE ETHER (OR QRM!) with the DX-26Q "Penetrator".

Models Available/Prices inc. VAT/Carr.

DX-26Q 2-ele. on 14, 18, 21, 24, 28 + 145MHz	£225
DX-24Q 2-ele. on 14, 21, 28 + 145MHz	£213

Enjoy the new frequency allocations
 14 . . . 18 . . . 21 . . . 24 . . . 28MHz with the NEW **Western** DX-51 PENETRATOR!

Features

2Kw p.e.p. Power Handling – VSWR of 1.6:1 – Max. Wind Survival 100m.p.h. – Longest Element Length 24ft. – Wind Load at 75m.p.h./100m.p.h. is 23/41lbs. – Surface Area 2.3 sq.ft. – Mast Dia. 1½" – Weight 11lbs.

THIS ROTARY DIPOLE AT ONLY **£90.85** inc. Carr/VAT.

PUBLIC ANNOUNCEMENT

In case you should think otherwise, **Western** are authorised agents for Yaesu and Trio/Kenwood equipment. Our worried competitors are spreading false information to combat decreasing sales.

It should be clearly understood that **Western** provide full after-sales-service for either brand of equipment which we sell. This Company's reputation has been built-up by providing a high standard of service. We provide factory spares for both brands and have an extensively equipped Service Department.

We do not buy Trio/Kenwood in the UK and will not be a party to the UK Trio marketing system. We prefer to buy from sources outside the UK and we sell at prices which We decide. If you want an 'alternative' supplier with courteous service, selling at reasonable prices, then you know whom to support. IT IS IN YOUR INTEREST TO SUPPORT YOUR INDEPENDENT SUPPLIER!

And if you still believe that the "Trio" brand is any different from the "Kenwood" brand, we would like to refer you back to page 190 of "Radio Communication" March 83, amongst other magazines, where the Kenwood label is displayed in the photograph (and it wasn't ours!).



CALL **Western** FOR YOUR YAESU AND TRIO REQUIREMENTS
 A selection from the range . . . **LOWEST PRICES . . . FINE SERVICE**
 YAESU WAS INTRODUCED TO THE UK BY '**Western**'.
BUY WHERE EXPERIENCE COUNTS!



TR-9130 2m. ALL-MODE TRANSCEIVERS HF ALL-MODE FT-102
£399 **£799**



OPEN: MON-FRI., 8-12, 1-5PM – SAT. 9-12 NOON.

Western Electronics (UK) Ltd

FAIRFIELD ESTATE, LOUTH, LINCNS LN11 0JH
 Tel: Louth (0507) 604955 Telex: 56121 WEST G
 NORTHERN IRELAND AGENTS:
 Tom & Norma Greer GMTGR - GMTBP
 Tel: Drombo (023 126) 645



GEMSCAN 70



2 YEAR WARRANTY – TRADE AND EXPORT ENQUIRIES WELCOME

Freq. range:

- 60–89 MHz
- 108–138 MHz
- 140–144 MHz
- 144–148 MHz

- 70 CHANNELS MEMORY
- DIGITAL CLOCK
- 2 SCAN RATES
- AUTOMATICAM/FM SWITCH
- LOCKOUT AND PRIORITY FACILITY
- AUTOMATIC SEARCH AND STORE



Freq. range:

- 148–179 MHz
- 380–470 MHz
- 470–519 MHz

- DISPLAY SWITCHABLE
- COUNT FACILITY
- STORE FACILITY
- MEMORY BACKUP
- EPROM PROGRAMMABLE
- AUTOMATIC TAPE RECORDER CONTROL
- AC/DC 2-WAY POWER SUPPLY

£258

We also carry a range of products from other manufacturers such as JAYBEAM, MICROWAVE MODULES, L.A.R., DATONG, CUSHCRAFT etc.

A selection of marine, commercial and p.m.r. equipment is also available.

ALL PRICES MAY CHANGE OWING TO CURRENCY EXCHANGE FLUCTUATIONS.
All prices include VAT. HP terms available. Part Exchange, Access and Barclaycard welcome.
Goods normally despatched by return of post.

New Address

102 DERBY STREET, BOLTON.
ROY G4GHE Tel: 0204-392226

Your official Sommerkamp Importer

We now stock a comprehensive range of electronic components.



9.30-5.30 Mon-Sat. Closed Wed. p.m.

BECOME A RADIO AMATEUR

Train now for the Radio Amateur Licence examination. No previous knowledge needed, only a few hours per week of home study for 3 to 6 months. Post coupon now for details or tel. 0734 51515 (24 hr service)



British National Radio & Electronics School Reading, Berks. RG1 1BR



FREE brochure without obligation from:—
British National Radio & Electronics School
READING, BERKS. RG1 1BR

Name

Address

PW/10/846

BLOCK CAPS PLEASE

J. BIRKETT

13 THE STRAIT, LINCOLN. LN2 1JD. Phone. 20767

VHF WIRE ENDED R.F. CHOCKES. 1 U.H., 4.7 U.H., 10 U.H., 47 U.H. All @ 10p each, 100 M.H. @ 20p.

SILICONEN POWER FET VK10KM @ 50p.

HC6U CRYSTALS. 3.495, 5.051, 6.017, 9.030, 10.0062, 10.1125, 10.125, 10.212, 10.514, 11.100, 15.300, 15.800, 18.006, 44.3, 45.9, 46.1, 46.5, 48.3, 50.1MHz All @ £1 each.

MICROWAVE NPN TRANSISTOR. FT 4GHz. 18 Volt, 50mW at 2GHz @ £1.95.

OP-TO ISOLATORS PLESSEY TYPE DPX003. @ 5 for 60p.

50 ohm PUSH ON BNC PLUGS, 50 ohm BNC SOCKETS. Both @ 3 for £1.15.

TRW R.F. POWER TRANSISTORS. No details. PT31961 T05 Case @ 45p, PT31962 Stud Mounting @ £3.95, PT31963 Stud Mounting @ £3.95.

MULLARD SUB-MINIATURE CERAMIC PLATE. 63v.w., 0.01uf 25p doz.

FERRITE BEADS. FX1115 @ 15p doz, 3" Long Type @ 6 for 10p.

25 NATIONAL BSY39 (BSX20) TRANSISTORS @ 60p.

MULLARD TYPE FILM TRIMMERS. 10pf, 35pf, 60pf, 125pf. All @ 15p each.

UNUSUAL COLLINS UHF VARIABLE CAPACITOR AND TUNED CIRCUIT @ 85p.

ITT PMT CAPACITORS. 0.1uf 400v.w. @ 6 for 25p, 0.1uf 100v.w. @ 5p each.

BUTTERFLY 25x25pf VARIABLES. Pre-Set, Spindles easily extended @ 50p.

25 FERRANTI ZTX108 (BC108) TRANSISTORS for 60p.

EX-GPO 20K ohm PER VOLT MULTI-METERS. All with some Fault. Movement O.K. @ £3 each, 4 for £10, P.&P. £1. Please add 30p for post and packing, unless otherwise stated. Orders over £3 post free. Goods Normally by Return.

Accurate Digital Multimeters at Exceptional Prices

SPECIFICATION MODELS
6010 & 7030

- * 10 amp AC/DC
- * Battery: Single 9V drycell. Life: 200 hrs.
- * Dimensions: 170 x 89 x 38mm.
- * Weight: 400g inc. battery.
- * Mode Select: Push Button.
- * AC DC Current: 200µA to 10A
- * AC Voltage: 200mV to 750V
- * DC Voltage: 200mV to 1000V
- * Resistance: 200Ω to 20MΩ
- * Input Impedance: 10MΩ
- * Display: 3 1/2 Digit 13mm LCD
- * O/Load Protection: All ranges

28 RANGES, EACH WITH FULL OVERLOAD PROTECTION



7030
-1% Accuracy
£35.95

6010
-5% Accuracy
£29.95

NEW
HM102 BZ
£13.00

NEW ANALOGUE
HM 102 BZ
SPECIFICATION

With continuity
buzzer and
battery scale

- * DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- * AC Voltage: 0-10, 25, 100, 250, 1000 volts, 10,000 ohms/volt.
- * Decibels: -20 to +22dB
- * DC Current: 0-50, 500µA, 0-5, 50, 500mA
- * Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale.
- * Power Supply: One 1.5 V size 'A' battery (incl)
- * Size & Weight: 135 x 91 x 39mm, 280g.

ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road, Wembley, Middlesex HA9 8BH, England



Telephone 01-902 4321 (3 lines) TELEX No. 923985

Please allow 15 days for delivery.

These are acknowledged over the air in *Listeners Mail* at 2150 on Sunday and in Reception Reports at 2150 on Wednesday. The station also QSLs, the address being Radio Cairo, External Services, Europe Section, English Programme, PO Box 566, Cairo, Egypt.

Readers' Letters

"Why do broadcasters not use the 13.7MHz (22m) band? I presume 13.6MHz to 13.8MHz is an internationally agreed band," asks **Kevin Lewis** of Belfast. Well, yes, it is but it has not come into use yet. Presumably the waiting period is to allow current users time to move, but my guess is that it will be full of broadcasting stations before the official opening. According to the ILG, the Voice of Israel is already on 13.725 at 1800 and 2000 with programming in English.

I have another problem writes fifteen-year-old **Philip Hodgson** from Uffington. "Say I hear Radio Qatar and want to



RFE-RL sent in by Kevin Lewis

receive a QSL. What station and programme details should I give being that I cannot understand the language and the music is unfamiliar." A tape recording is the easy but expensive way out. English will probably be understood so try to catch the station signing on or off when it may be easier to describe what is heard. If there is an English programme, e.g. *Radio Cairo*, then write to that. Anyone any ideas? Philip, who uses an FRG-7700 and "Random



Pakistan sent in by R. McDonald

Shortwire Antenna" (I like that one), reports some interesting loggings on the lower frequencies. SABC Radio 5 was heard on 3.250MHz at 2110, Ghana on 3.366 at 2126, Radio Falkland Islands Broadcasting Station on 2.370 at 0052, SW Africa on 3.270 at 2050, SABC English Service on 3.295 at 2103.

The last word is from **D. Baines**, who would like to contact anyone who has fitted digital readout to the Realistic DX-100L. Replies, please, to 93 Wheal Rose, Porthleven, Helston, Cornwall.

VHF BANDS by Ron Ham BRS15744

Reports to: Ron Ham BRS15744, Faraday, Greyfriars, Storrington, West Sussex RH20 4HE.

QSOs across the pond and new beacons on 50MHz, Malta worked on 144MHz, another award for Peter Lincoln, short skip on 28MHz, and what with plenty of sporadic-E and tropo to liven up both the amateur and broadcast bands, there is lots to write about.

Solar

"The sun has been quiet all the month, no flares seen and nothing violent on 136 or 196MHz" writes **Cmdr Henry Hatfield**, Sevenoaks. He checks the sun daily with his radio telescopes and as often as the weather permits with his now famous spectrohelioscope. I recorded a few individual bursts of noise, Fig. 1, at 143MHz on June 21 and 24 and July 1 and 14 and, like Henry, found the sun very quiet. This was just as well because

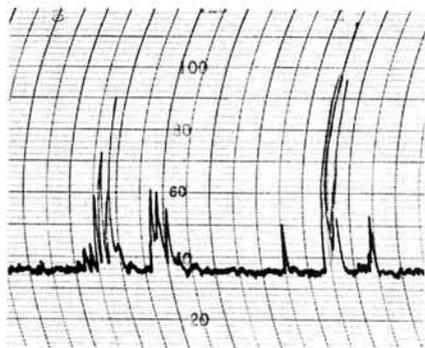


Fig. 1: A pair of solar noise bursts lasting seven minutes, recorded by the author on June 24

there were enough other types of anomalous propagation about during the period to keep us on our toes.

While making routine solar observations, **Ted Waring**, Bristol, counted 28 spots on the sun's disc on June 18, 50 on the 22nd, 16 on July 8 and 23 on the 13th.

The 50MHz (6m) Band

I see in the July issue of *Six News* that there are three new beacons, PJ2B 50.015MHz, ZS6VHF 50.025MHz and ZS1SIX 50.945MHz to look out for. *Six News* is the information sheet of the UK 6m Group and is full of the latest gen. Readers wishing to contribute or get more information about the publication should contact the Editor G4JCC, 52 Salterns Lane, Hayling Island, Hants PO11 9PJ, or for membership of the group, £5 per annum, write to Peter Turner G4IIL, Flat 6, 132 Marine Parade, Brighton, Sussex.

On June 18, **David Newman G4GLT**, Leicester, worked 15CTE crossband 50/28MHz and heard the Cyprus 50MHz beacon 5B4CY peaking 569 from 0858 to 1120. He reports that VE1YX received signals from the UK beacon, GB3SIX 50.020MHz, at good strength from 2330 to midnight GMT. Between 2130 and 2300GMT both the 28 and 50MHz bands opened up to VE1 and W1 and permit holders G13ZSC, GJ3RAX, GU2HML and GSKW had QSOs with VE1YX and several W1 stations by, what was almost certain to have been, double hop sporadic-E. At 0625 on the 20th, David had a crossband contact

with CT1WB, a direct 50MHz QSO with ZB2BL, a crossband with TF1T at 1952 and at 2100, heard 5B4CY on 50MHz at 539. David logged 5B4CY again at 1636 on June 21, 1812 on the 24th, 1630 on the 28th and 0650 on July 2. At 1846 on July 1, David was amazed to hear WA1OUB on 50.100MHz and very soon had a crossband QSO with him and later, at 2257GMT, had a direct 50MHz contact with TF1T who also holds a 50MHz permit. In Knutsford, **Dave Coggins** logged c.w. and s.s.b. signals from GW3LDH on June 13, 20, 21, 22 and 23, G3USF on the 27th, G3OHH on July 1 and G4GLT on the 5th. After listening for a while in the wee hours of July 2, Dave heard the QSO between TF1T and G3OHH and reports hearing signals from the Gibraltar 50MHz beacon ZB2VHF during the early mornings of June 20 and 21 and the evenings of the 23rd and 28th and July 7. Further to the fantastic strength of ZB2VHF on June 12, which I mentioned in our September issue, **John Fell G8MCP**, tells me that he heard it at 1214, with only 150mm of wire in the antenna socket of the Spectrum Communications RC6-2 converter.

The 28MHz (10m) Band

Although there were a variety of opinions in your letters about the 28MHz band, the general theme was the short skip which often provided a lot of activity. During the afternoon of July 3, **Richard Brownlow G4LCV**, operating a TS1305S, Kenwood a.t.u. and a 3-band quad at the Chalk Pits Museum station

GB2CPM, made c.w. contacts with G3JZI and stations in America, Czechoslovakia, East Germany and Hungary. When **Gerry Brownlow** G3WMU did his spell at the controls he worked into Sweden and Yugoslavia on s.s.b.

Between June 12 and July 11, **Norman Hyde** G2AIH, Epsom Downs, heard or worked stations in Brazil, Czechoslovakia, Denmark, East and West Germany, France, Hungary, Italy, Norway, Poland, Portugal, Spain, Sweden, the USSR and Yugoslavia. He writes, "The 28MHz band has been most interesting, the two highlights being the short skip conditions on July 1 and 2 and again from the 6th to 8th, which is shown in the reception of European beacons" (Fig. 2).

"I found 28MHz not very good for DX" writes **Peter Lincoln**, Aldershot, and reports hearing signals from South Africa and plenty of close European countries during the sporadic-E events which affected the 28MHz band. Dave Coggins noted sporadic-E events on most days between June 16 and July 7 with outstanding events on June 19 to 22 inclusive and July 4 and 6. He writes, "Some really fabulous signals have been rolling in here at block-busting strengths" giving EI9Q, GU4LJC and GM3ZET in Shetland in QSO with his good friend G4HZW, Knutsford as examples and adds, "On July 3, EI stations were coming through with 59 plus signals throughout the day". During his checks on 28MHz f.m. Dave logged strong signals from stations in 7 countries, DH4, HB9, LA, LX, OZ, SM and YU. At various times between June 18 and July 5, **Bill Kelly**, Belfast, logged signals from Argentina, Bogota, Bolivia and Paraguay. "Lots of Europe and Scotland on 29MHz f.m." writes **Peter Lewis** G6NSU, Devon, about the opening on June 21. European signals were very strong during the sporadic-E disturbance early on July 17 and having invested in a Tono Theta 550 communications terminal, I checked the low end of the band and logged, from the video screen, strong c.w. signals from 4 DLs and an SM all calling CQ DX. Dave Coggins told me about the opening to VK around 0830 on June 26 when he logged a VK5 and 3 VK6s and the openings to North America on July 4, 5 and 6 when he heard N9QX and VE3ABH. **Tony Usher**

G4HZW had QSOs with a number of these stations and on the 5th the band remained open in that direction until 0145.

28MHz Beacons

From 1502 to 1538 and again at 2219 on July 1, David Newman heard the Canadian beacon VE3TEN by multi-hop sporadic-E. **Bill Kelly** and **Dave Coggins** reported hearing a new beacon on a few days between June 20 and July 7, sending "Test de DF0THD, QTH EJ14h, Pse QSL" on 28.325MHz. Dave also heard LU1UG on June 28. "On the evening of July 1, both the LA and DF beacons sounded rather rough in tone" writes **Ted Waring**, who along with **Dave Coggins**, **John Coulter**, **Norman Hyde**, **Henry Hatfield**, **Bill Kelly**, **David Newman** and I produced logs to compile the monthly beacons heard chart (Fig. 2) which many people find a useful reference.

28MHz Satellites

At 1819 on June 29, **John Coulter**, Winchester heard the following, "VV many happy returns of the day little bird OSCAR 10 good luck in final orbit de RS Sputnik AR", being continually broadcast on 29.331MHz.

Sporadic-E

During a sporadic-E disturbance which reached the 144MHz band briefly at 1045 on July 2, **Graham Wood** G3VPC, Wimborne, worked a station in Malta on s.s.b. **Harold Brodribb**, St Leonards-on-Sea logged 32 east-European f.m. broadcast stations between 66 and 73MHz at 1115 on July 2. These signals are usually very strong and I counted 36 such stations in this frequency range at 1745 on June 22, 12 at 1740 on the 24th and again at 1900 on the 28th, 21 at 1325 on July 1. I also counted about the same as **Harold** during the evening of the 2nd, 32 at 0810 on the 3rd, 19 at 1015 on the 6th, 31 at 1821 on the 17th and 10 at 1003 on the 19th. Broadcast stations, like beacons, are very good propagation indicators because they are operational for most of the day.

Tropospheric

The atmospheric pressure, which plays such a major part in v.h.f. propagation, hovered around 30.1in (1019mb) at my QTH from June 20 apart from a drop to 29.9 (1012) for about 12 hours on the 30th and 14 hours on July 17, after which it rose to 30.2 (1022) and remained steady around this level until the 19th, when I closed this month's report.

In Belfast, **Bill Kelly** logged signals through the 144MHz repeaters GB3AR and MP in Wales, AY in Scotland and AS in Cumbria as well as many mainland stations who worked through LY and WT in Northern Ireland and heard QSOs with EI7DAR in Eire. **Bill** also heard a station in West Donegal working through GB3AR, "over 480km" said **Bill**. **John Fell** G8MCP worked **Doug Port** G6INU/EI3VJV on 144MHz s.s.b. while he was on holiday 16km south of Wexford, at 0807 on July 5.

At 1835 on July 12, I heard stations in DJ and PA0 working through the Kent 144MHz repeater GB3KN on R4. **PDOLWR** in Arnhem told a "G" that he heard QSOs on 144MHz between Denmark and Portugal and Hamburg and London. Such was the state of the band, many repeaters were up on most channels and in a 10 minute spell at 0135 on the 13th, I logged DC5KD, DK8JF/M, ON1BSE and PE1HLK working a G6 through the Kent repeater. **John Fell** worked 15 Dutch and 10 German stations on 144MHz in about 45 minutes around 0900 that day.

Contests

Flight Refuelling Amateur Radio Society were out for the VHF NFD on July 2/3, operating from a site some 198m a.s.l. on the Purbeck Hills.

The equipment used on the 70MHz (4m) band, under the call sign G4LFM/P, was an FT-101, G4HUP transverter and 8-element ZL special antenna. On 144MHz the club call G4RFR/P was used along with an FT-221R, 175W valve linear and 4 by 14-element Parabeams. For 432MHz G4RAM/P, a Trio TS-780, 200W valve linear, muTek mast head pre-amplifier and 4 by 24-element quad loop Yagis were used. Finally on 1296MHz G3VMO/P, an FT-290, Microwave Modules transverter, 20W valve linear and 4 by 24-element quad loop Yagis were in action. Having looked at this lot, who said valves were finished, hi! At the end of a most enjoyable event the FRARS have every right to say they are well satisfied with 165 QSOs on 70MHz including GM, 511 from 14 countries on 144MHz, 172 from 8 countries including HB9 on 432MHz and 49 from 7 countries with a best DX of 457km on 1296MHz.

Congratulations to **Horsham** and **District Amateur Radio Club** on their VHF NFD efforts being reported, along with a picture, in the West Sussex County Times on July 22. The reporter stressed the

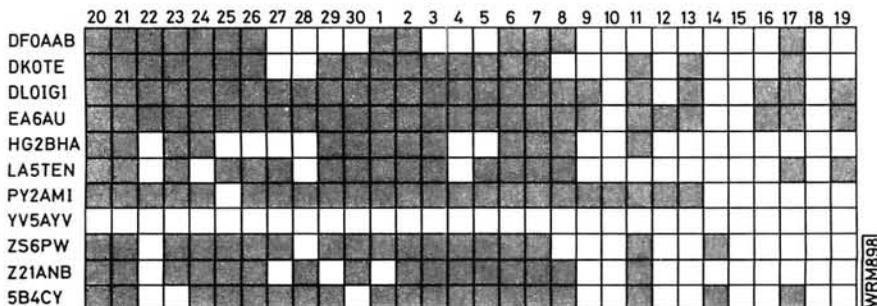


Fig. 2: Distribution of beacon signals

points that 30 club members took part in the event and that nearly one and a half tons of equipment were needed to establish their four stations and had to be taken to a high spot on the Sussex Downs.

Microwaves

On June 26 Ron Allen G2DSP, Terry Allen G4ETU and a visitor from the USA G4/WB6YLI, took the Allens' 10GHz gear to Trundle Hill, a high spot near Chichester, and made six QSOs, three of them by the WB6. He plans to have his own gear next year when he should be operational from the Eastbourne area.

Band II

Richard Hunt, Tadcaster, received a QSL card (Fig. 3) and sticker (Fig. 4) from the Belgian German language station BRF acknowledging his report on their v.h.f. signals. "I think readers might find this interesting. The station transmits on 88.5 and 94.9MHz with 50kW and 1.5kW respectively", says Richard.



Fig. 3: Belgian QSL card received by Richard Hunt

Throughout the period mid-June to mid-July, Band II really suffered, much to the delight of the DXers, from both sporadic-E and tropospheric disturbances. The sporadic-Es were sudden and short lived and the tropo ebbed and flowed with the slightly varying high pressure and the heat of the day and coolness of the night.

"There were good openings on Band II from June 17 to 24 and on the 30th and July 1", writes Leo Nolan, Athlone. With his Hitachi TRK-8000E and 6-element Yagi he logged BBC radios Cumbria, Cleveland, Lancaster and Scotland, Manx Radio and ILR Downtown, Red Rose and West Sound. Leo also heard Italian, Norwegian and Spanish stations in the band on June 17 and July 1. Harold Brodribb received between 10 and 18 French broadcast stations on July 2,

3, 5, 8, 9, 11, 12 and 14. While situated near Crowborough on July 1, I heard five French stations between 96 and 104MHz using the rod antenna attached to my Plustron TVR5D.

At 2330 on June 18, Simon Hamer, New Radnor, received signals from Holland NOS-1 from Cusselstein, Goes, Markelo, Smilde and Wieringermeer between 87 and 93MHz. During the first forty minutes of the 19th, Simon logged BFBS from Bielefeld, Langenberg and Visselhovede and the German station



Fig. 4: BRF sticker received by Richard Hunt

NDR II Steinkimmen, SDR 1 Heidelberg, Radio Bremen-1 Bremen, WDR II Langenberg and Teotoburgerwald, between 93 and 102MHz.

"Belgian and Dutch stations have dominated the scene for the last few days and this morning at 0500, it was the turn of the Germans" writes Michael Welch, London. Among the DX signals Michael heard were Radio Renascenca (Portugal), 98.6MHz on July 7 and Radio Shape 103.3MHz at 2359 onwards on the 11th. For a short period during the early evening of June 7, he received SEB (Southern European Broadcasting Service) on 106MHz. Following the report he sent to the Dept of the Army in New York about the station, Michael received a reply signed by a US Army Commander who confirmed his report and said that the transmitter was SEB-San Vito at Brindisi, Italy and broadcast daily, with 1kW, for 24 hours on 106 and 107MHz.

In Dublin, Raymond O'Connor, heard German, Italian and Spanish stations and identified AFN Berlin, NDR, Radio LUNAS Italy and SKR (East Germany) on June 16, 17, 18 and 20.

"The Swedish f.m. radio monopoly was shattered on the evening of July 2 as stray signals from the continent rained down on this parched wireless wasteland!", writes David Appleyard, Upsalla. He adds, "At 1700 Germans and Italians were hammering in on the lower half of Band II and between 1800 and 2000, the accent was on France and French-speaking stations". David counted 22 frequencies between 87.9 and 105.2MHz that were providing his Pan-

asonic DR49 and music centre with everything from drama to pop and some transmissions in "impressive stereo".

RTTY

Apart from the usual Europeans, Peter Lincoln copied RTTY signals from EA9JE, PZ1AP, VP2MJL, UA9DFC, 9M2DW and several from north America during the month preceding July 11. "The callign from EA3CJF (Fig. 5) was made up from the letter 'X' and I was pleased that during the transmission the Telereader gave perfect copy", writes Peter. He earns our congratulations, not only for having his camera at the ready for interesting pictures but also on receiving the Century Club award from the ISWL for 100 countries confirmed through his general listening. He is now working towards the "50" confirmed in the RTTY mode.

Although my RTTY viewing was curtailed during the month, I did log stations from 15 countries, DK, DL, EA, F, G, HB9, I, ON, OH, OK, OZ, VK, W1, YS and YV3 on 14MHz and one DJ on 21MHz. On July 8, I installed a Trio 2000 receiver and Tono Theta 550 communications terminal for RTTY and I must say it all performs very well. The digital readout and the 8 memories on the Trio are most useful for RTTY and quick checks on the 28MHz beacons. As yet I have not explored the full possibilities of the Tono terminal, but so far I like what I've seen and I will tell you more in due course. Down in Rye, Norman Jennings copied RTTY signals from 25 European countries between June 12 and July 13 including OH0BT. At times signals from CE3, FM7, HC4, JA, VE, W9JER/9Q5, XT2 and YV on 14MHz were outstanding but getting on the thin side with the poorer conditions towards the end of the period. Norman's count of Italian RTTY stations received is now 89 and referring to his general listening says "One has to pick the times these days" as he proved when he caught 9M2DW at 1600 on July 7 on 21MHz.

RTTY Contests

The British Amateur Radio Teleprinter Group are holding their Autumn VHF Contest for RTTY enthusiasts between 1800GMT on October 10 and 1100GMT on the 11th, with a compulsory rest period of four hours during the event. The contest is open to licensed amateurs within Zones 14 and 15 who are permitted to use RTTY, and s.w.l.s whose entries will be scored separately. Certificates will be awarded to the top scorers in each section, single operators UK and Europe, multi-operators UK and Europe and s.w.l.s. The Ealing Challenge Cups will be awarded to the winners of the single and multi-operator sections. All logs, postmarked no later than October 8 (and requests for more detailed information about the event) to Ted Double, 89 Linden Gardens, Enfield, EN1 4DX.

Our congratulations to the Ealing and District Amateur Radio Society G3UUP/P and P.D. Barrett Group G2BRS, C. Desborough G3NNG and M. Bourbon ON7CB, and F. Van Oostenbrugge NL 4483 who were the winners and runners up respectively of the 144MHz multi-operator, single-operator and s.w.l. sections of BARTG's Spring VHF/UHF contest. Results in the same order for 432MHz were Ealing and District and Worthing and District Amateur Radio Society G8GCP/P, and C. Desborough and J.E. Neal G4NQC. For 1296MHz Ealing again and E Grossmith Group G3WOH and C. Desborough and J.E. Neal. The committee wish to thank G4SQG and ON7PC for their check logs. What about it readers, if you don't want to enter, how about sending Ted a check log.



Fig. 5: RTTY callsign received by Peter Lincoln

Tailpiece

John Oliver, the Secretary of the SINGER OWNERS CLUB, has a 1½ litre Singer LeMans car, registration ALV53, which is one of two specially made for the Liverpool City Police and delivered to the Chief Constable on 24

July 1935. If any reader can supply bits or help with advice about the original radio installation for this car, or knows the whereabouts of the other one ALV52 or ALV54, please contact John at Dormer Cottage, Woodham Park Way, Woodham, Weybridge, Surrey.

The Scottish Borders Repeater Group held their first mobile rally at Lilliards-edge Caravan Park (on the A68) recently and this successful event helped the group's funds considerably. A similar event on the same site is planned for next year. The Group own and maintain the two 144MHz repeaters, GB3BT at Berwick upon Tweed R4 and GB3SB at present near Duns R2, although they hope for a site near Selkirk. Membership of the Group is £4 and details are available from Bruce McCartney GM4BDJ, "Cairndhu", Walter Street, Langholm, Dumfriesshire.

Congratulations to Chichester Club member, 15-year-old Gregory Brown who passed the RAE last October and now, with a Trio 2300 and 7/8ths antenna is often seen "Push-Bike" mobile using his call sign G6NKM. Greg has been interested in radio for three years and as a Scout he has taken part in JOTA.

For the third year in succession, the Chichester and District Amateur Radio Club can be well pleased with the impressive display of all aspects of amateur radio which they laid out at the Priory Park Guildhall for the 908th Chichester Festival on July 8th and 9th. Last year's QSL cards from Australia, Japan, Scandinavia and the USSR were among the exhibits along with home-made gear for audio and ATV, demonstrations of computing, h.f., v.h.f., microwaves, teleprinter and television communications were shown to the public and the club's ATV group interviewed, by sound and vision, the members of the TVS crew who came to film for television their part of the Chichester festivities. Many visitors were fascinated by the array of antennas in the

park which included a wire dipole for the i.f. bands, a Tribander for the h.f. bands, colinear for 144MHz, a Tonna for the satellite uplink and a Multibeam for ATV.

During the 3 weeks prior to July 5, the Horndean and District Amateur Radio Club put on special event stations GB2MMR at the RNARS Mercury Rally and GB2HRC for the Horndean Community Carnival, plus giving radio coverage to a long procession of floats.

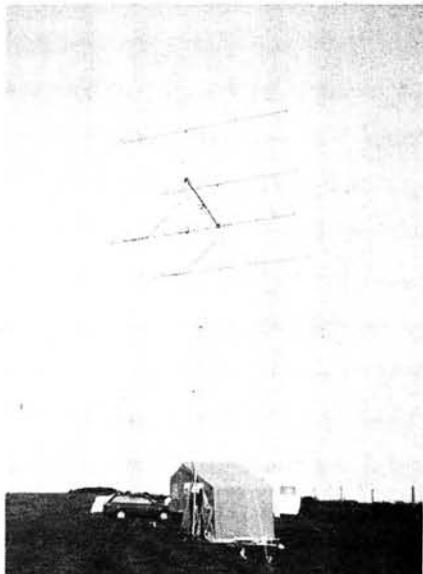


Fig. 6: FRARS 144MHz contest station antennas G6DUN

Their station at Mercury worked non-stop for 3 days and in all made 474 different contacts spread over 33 countries. "The interest taken by the public in both events was incredible and leaflets were flowing in all directions" writes club secretary Dan Bernard G4RLE, who told me that contacts with both special stations qualify for double points in the HRC awards. Details, s.a.e. to Jonathan Kay G6DWT, QTHR.

TELEVISION by Ron Ham BRS15744

Reports: as for VHF Bands, but please keep separate.

Another first for SSTV, plenty of DX from both amateur and commercial television due to lots of activity with contests, holidaymakers working portable, a good drop of sporadic-E and the summer fine weather tropo.

Amateur Television

Nick Foot G8MCQ operated portable during the British Amateur Television Club's Summer Fun ATV Contest, from a site 183m a.s.l. in Dorset. He used 4 by 24-element quad loop Yagis built by John Fell G8MCP, a Wood and Douglas ATV transmitter driving a single 4CX250B, a muTek TLNA432s pre-amplifier for the receiver and a Thorn Videostar camera. He worked 16 stations between 1107 and 1508 on June 19, about 2000 points.

On the same day, R. O. Wade, Tadworth, ventured into the world of ATV with a Fuba CLOU 45c antenna, Fortop ATV converter and a Panasonic TR-5030G. He was delighted when he received pictures from G3WRU, G4CRJ, G4IOF, G4TVC, G6CAQ, G6WOR, G8DTQ and G8MNY. He found it "A most enjoyable day" especially when he noticed the 144MHz talk-back frequency on G6CAQ's transmissions and he was able to listen to the links as well as seeing the pictures.

Sporadic-E

"What a fantastic month for sporadic-E with a bit of tropo thrown in" wrote Roger Wallis, Solihull on July 5. This means that my problem is to give, in

limited space, a comprehensive account of the situation. "Where I go my faithful TVRC5D goes with me", writes I. Dunworth G4SNL, Saltash who was delighted while away from home in June and using the receiver's own rod antenna to see test cards from a French station on the 17th and Iceland on the 21st. Like Mr Dunworth, I usually take my TVR5D with me and while at Sissinghurst Castle in Kent, at 1745 on July 1, I received, with the rod antenna, a strong test card from RUV Iceland on Ch.E3 55.25MHz. Then at 1800, one of the Russian analogue clocks appeared on Ch.R1 49.75MHz showing 2100, followed by their news caption BPEMR and a male and YL news readers. At 2037 on the 3rd, I saw a Russian YL news reader, with a digital clock showing 2337, present

BI-PAK BARGAINS

DEE CONNECTORS GOLD PLATED		
	Order No.	Price Ea
Plugs 9 way	1747	£0.80
15 way	1748	£1.10
25 way	1749	£1.60
Sockets 9 way	1750	£1.10
15 way	1751	£1.60
25 way	1752	£2.10
Covers 9 way	1753	£1.40
15 way	1754	£1.40
25 way	1755	£1.40

EDGE CONNECTORS GOLD PLATED		
	Order No.	Price Ea
Suitable for ZX81 23 way	1756	£1.85
Spectrum 28 way	1757	£2.10

RIBBON CABLE		
	Order No.	Price Ea
25 way multi-coloured	1758	£1.50 (per metre)

D.I.L. PIN HEADERS		
	Order No.	Price Ea
Gold pin for high contact reliability. Insulating covers included.		
Pins 14	2227	.60
16	2228	.65

D.I.L. SOCKETS TEXAS LOW PROFILE		
D.I.L. PCB	Order No.	Price Ea
8 pin	1601	.08
14 pin	1602	.10
16 pin	1603	.11
18 pin	1604	.16
20 pin	1605	.18
22 pin	1606	.22
24 pin	1607	.24
28 pin	1608	.27
40 pin	1609	.30

VOLTAGE REGULATORS		
100 MA TO-92 Case	Order No.	Price Ea
POS + 5V	78L05	.28
12V	78L12	.28
15V	78L15	.28
18V	78L18	.28
24V	78L24	.28
NEG - 5V	79L05	.55
12V	79L12	.55
15V	79L15	.55
18V	79L18	.55
24V	79L24	.55

1 AMP TO-220 Case		
POS +	Order No.	Price Ea
5V	MVR7805	.40
12V	MVR7812	.40
15V	MVR7815	.40
18V	MVR7818	.40
24V	MVR7824	.40
NEG - 5V	MVR7905	.50
12V	MVR7912	.50
15V	MVR7915	.50
18V	MVR7918	.50
24V	MVR7924	.50

ANTEX SOLDERING IRONS AND ACCESSORIES		
Soldering Irons Model	Order No.	Price Ea
XS 25 Watt	1931	£5.20
C230 17 Watt	1972	£5.30
C250 15 Watt	1948	£4.60
MLX 12V 25 Watt	1928	£5.46
SK1 Kit 15 Watt	1935	£6.95

REPLACEMENT BITS & ELEMENTS		
FOR MODEL SX & X25	Order No.	Price Ea
Size 1" (3mm)	1932	£0.65
3/16" (4.7mm)	1933	£0.65
3/32" (2.3mm)	1934	£0.65
Element	1935	£2.10
FOR MODEL C230		
Size	Order No.	Price Ea
3/32" (2.3mm)	1944	£0.65
1" (3mm)	1945	£0.65
3/16" (4.7mm)	1946	£0.65
3/64" (1mm)	1924	£0.65
Element	1969	£2.10
FOR MODEL C250		
Size	Order No.	Price Ea
3/32" (2.3mm)	1949	£0.65
5/32" (4mm)	1950	£0.65
3/16" (4.7mm)	1951	£0.65
3/64" (1mm)	1970	£0.65
Element	1952	£1.80

FOR MODEL MLX Order as Model SX		
FOR MODEL SK1 Order as Model CX230		
ANTEX ST4 IRON STAND		
For all ANTEX SOLDERING IRONS		
Order No.	Price Ea	
1939	£1.60	

AEG-TELEFUNKEN 7 SEGMENT LED DISPLAYS			
10mm .4 inch 10 pin D.I.L. R/H decimal point	Order No.	Price Ea	
Com Anode RED	1585	£1.00	
Com Anode GREEN	1586	£1.10	
Com Anode YELLOW	1587	£1.10	
Com Cathode RED	1588	£1.00	
Com Cathode GREEN	1589	£1.10	
Com Cathode YELLOW	1590	£1.10	

13mm .51 inch 10 pin D.I.L. R/H decimal point			
Order No.	Price Ea		
Com Anode RED	1591	£1.00	
Com Anode GREEN	1592	£1.10	
Com Anode YELLOW	1593	£1.10	
Com Cathode RED	1594	£1.00	
Com Cathode GREEN	1595	£1.10	
Com Cathode YELLOW	1596	£1.10	

20mm .8 inch 18 pin D.I.L. L/H decimal point			
Order No.	Price Ea		
Com Anode RED	1597	£1.85	
Com Cathode RED	1598	£1.85	

LINEAR DISPLAY (BARGRAPH)			
Ten LED elements housed in 20 pin package to form a compact linear bar display. Can be end stacked to create bargraphs of various lengths.			
Order No.	Price Ea		
RED	1558	£2.50	
GREEN	1559	£2.50	
YELLOW	1560	£2.50	

AEG - TELEFUNKEN SHAPED LEDS			
IF = 20mA	Order No.	Price Ea	
RED 1.6V			
GREEN 2.7V			
YELLOW 2.4V			
3mm RANGE CYLINDRICAL			
RED	1561	.20	
GREEN	1562	.23	
YELLOW	1575	.23	
SQUARE			
RED	1562	.20	
GREEN	1569	.23	
YELLOW	1576	.23	
TRIANGULAR			
RED	1563	.20	
GREEN	1570	.23	
YELLOW	1577	.23	

5mm RANGE RECTANGULAR			
RED	1564	.20	
GREEN	1571	.23	
YELLOW	1578	.23	
CYLINDRICAL			
RED	1565	.20	
GREEN	1572	.23	
YELLOW	1579	.23	
SQUARE			
RED	1566	.20	
GREEN	1573	.23	
YELLOW	1580	.23	
TRIANGULAR			
RED	1567	.20	
GREEN	1574	.23	
YELLOW	1581	.23	

LIGHT EMITTING DIODES			
Miniature LED body dia. .125"	Order No.	Price Ea	
TIL209 RED	1501	.09	
TIL211 GREEN	1502	.12	
TIL213 YELLOW	1503	.12	

Standard LED body dia. .2"			
Order No.	Price Ea		
FLV117 RED	1504	.09	
FLV310 GREEN	1505	.12	
FLV410 YELLOW	1506	.12	

OTHER LED'S			
Order No.	Price Ea		
RL209 clear .125" illuminating RED	1522	.12	
FLV111 clear .2 illuminating RED	1523	.12	
COX21 flashing LED RED	1524	.45	
COX95 dual LED RED/GREEN	1525	.60	
COY98 Infra Red LED .2/	1527	.30	

OPTO ISOLATORS			
Order No.	Price Ea		
IL74 Single	1515	£0.55	
ILD74 Double	1516	£1.16	
ILQ74 Quad	1517	£2.10	

BULGIN PLUGS & SOCKETS		
Order No.	Price Ea	
P780 3 pole outlet skt mates with P770 6A 250V AC	1630	£0.64
P770 3 pole connector mates with P780 6A 250V AC	1631	£1.68
P782 2 pole outlet skt mates with P772 & P672 6A 250V AC	1632	£0.54
P772 2 pole connector mates with P782 6A 250V AC	1633	£1.42
P597 connector mates with P590 10A 250V AC	1635	£1.10
P587 connector mates with P580 & P579 6A 250V AC	1636	£1.06
P580 inlet skt mates with P587 & P589 6A 250V AC	1638	£0.64

SAZ097 3 pole connector mates with SAZ096 5A 6VAC/DC 5A 110V AC 5A 250V AC 1A 500V AC		
Order No.	Price Ea	
P636 6 pole connector mates with P635 3A up to 50V	1641	£1.06
P635 6 pole inlet skt mates with P636 3A up to 50V	1642	£1.00
P552 8 pole outlet skt mates with P551 6A 250V AC	1644	£0.86
P551 8 pole connector mates with P552 6A 250V AC	1645	£2.78

VIDEO LEADS		
Order No.	Price Ea	
BNC plug to BNC plug 2 metres 75 ohms Coax. Betamax to Betamax	121	£2.70
BNC plug to UHF plug 2 metres 75 ohms Coax. Betamax to VHS	122	£2.50
UHF plug to UHF plug 2 metres 75 ohms Coax. VHS to VHS	124	£2.30
UHF Coaxial plug to UHF Coaxial socket. 2 metres 75 ohms low loss cable	131	£2.20
UHF Coaxial plug to UHF Coaxial plug. 2 metres 75 ohms low loss cable	134	£2.40

UHF PLUGS SOCKETS & ADAPTORS		
Description	Order No.	Price Ea
PL259 standard plug	1715	.40
SO239 socket 4 hole fixing	1716	.38
SO239 socket single hole fixing	1717	.40
PL258 double end female coupler	1718	.40
NC555 reducer for PL259 (small)	1719	.16
NC556 reducer for PL259 (large)	1720	.16
M359 right angle coupler PL259 to SO239	1721	.80
M358 T Connector Female-Male-Female	1722	.98
NC563 In-line coupler PL259 x 2	1723	.60

BNC PLUGS, SOCKETS & ADAPTORS (50 ohms)		
Description	Order No.	Price Ea
BNC115 50 ohm standard plug	1724	.75
BNC1502 chassis mounting skt	1725	.75
BNC1503 chassis mounting skt single hole fixing	1726	.75
BNC1520 BNC male to SO239 female	1727	.85
BNC1521 BNC female to PL259 male	1728	.95
BNC line socket	1732	.95

SWITCHCRAFT QD PLUGS & SOCKETS		
Order No.	Price Ea	
A3F Cord Plug (female)	1734	£1.50
A3M Cord Plug (male)	1735	£1.30
D3M Chassis Skt (male)	1736	£1.15
D3F Chassis Skt (female)	1737	£1.90

OUR GREAT NEW CATALOGUE
Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices. There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast stocks "in stock" for fast immediate delivery all items in our Catalogue are available exstock. The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.
To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p

"BCSBB"
BI-PAK COMPONENT & SEMICONDUCTOR BARGAIN BOX
This collection of Components & Semiconductors for the hobbyist is probably the most value packed selection ever offered. It consists of Resistors, carbon & wirewound of various values. Capacitors: All types sorts & sizes including electrolytics. Potentiometers, single, dual, slider & preset. Switches, Fuses, Heatsinks, Wire, P.C. Board, Plugs, Sockets etc. PLUS a selection of Semiconductors for everyday use in popular Hobby Projects, these include: SCR's, Diodes, Rectifiers, Tnacs & Bridges as well as a first class mix of Transistors & IC's. In all we estimate the value of this BCSBB - in current retail catalogues to be over £25. So help yourself to a great surprise and order a Box today for just **£6.50 ONLY** at BI-PAK. You can call us on 0920-3182/3442 and order it with your Barclaycard or Access Card - 24hr Answerphone Service NOW Order No: V.P.85.

BI-PAK

Send your orders to Dept. PW10 BI-PAK PO BOX 6, WARE, HERTS.
SHOP AT 3 BALDOCK ST., WARE, HERTS.
TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182, GIRO 389 7006.
ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order.
Total Postage add 75p per Total order.



Books for radio amateurs

RSGB Publications

A Guide to Amateur Radio (new 19th edn)	£3.44
Amateur Radio Awards (2nd edn)	£3.41
Amateur Radio Operating Manual (2nd edn)	£4.92
Amateur Radio Techniques (7th edn)	£6.20
HF Antennas for All Locations	£6.91
Radio Amateurs' Examination Manual (10th edn)	£3.42
Radio Communication Handbook (paperback 5th edn)	£10.91
RSGB Amateur Radio Call Book (latest 1983 edn)*	£5.70
Teletypewriter Handbook (new 2nd edn)	£13.84
Television Interference Manual (2nd edn)	£1.85
Test Equipment for the Radio Amateur (2nd edn)	£6.00
VHF/UHF Manual (new 4th edn)	£10.31

Logbooks

Amateur Radio Logbook	£2.45
Mobile Logbook	£1.14
Receiving Station Logbook	£2.72

Wall maps

Great Circle DX Map	£2.12
IARU QTH Locator Map of Europe	£1.43
QTH Locator Map of Western Europe	£1.43
World Prefix Map (in full colour)	£2.17

Morse instruction

RSGB morse course Stage 1 (to 5wpm)	£3.84
-------------------------------------------	-------

*Publication of the 1984 edition is planned for early 1984.

Other Publications

A Course in Radio Fundamentals (ARRL)	£3.77
Active Filter Cookbook (Sams)	£12.71
All About Cubical Quad Antennas (RPI)	£3.50
Amateur Television Handbook (BATC)	£2.32
ARRL Electronics Data Book	£4.18
Beam Antenna Handbook (RPI)	£4.84
Better Short Wave Reception (RPI)	£3.90
Care & Feeding of Power Grid Tubes (Varian)	£3.53
English-French QSO Instruction	£1.71
FM & Repeaters for the Radio Amateur (ARRL)	£4.30
Hints and Kinks for the Radio Amateur (ARRL)	£3.62
How To Troubleshoot and Repair AR Equipment	£10.47
International VHF FM Guide (latest 1983 edn)	£2.45
Radio Amateur Call Book (1983 US listings)	£16.93
Radio Amateur Call Book (1983 DX listings)	£16.23
Radio Amateurs Handbook 1983 (ARRL)	£9.63
Radio Frequency Interference (ARRL)	£3.13
RTTY the Easy Way (BARTG)	£1.32
Satellite Tracking Software for the RA	£4.47
Secrets of Ham Radio DXing (Tab)	£6.74
Simple Low-Cost Wire Antennas	£3.38
Solid-state Basics (ARRL)	£4.56
Solid-state Design for the Radio Amateur (ARRL)	£6.53
Television for Amateurs (BATC)	£1.96
The ARRL Antenna Book (new 14th edn)	£8.78
TTL Cookbook (Sams)	£8.44
UHF-Compendium Parts 1 and 2	£13.43
Understanding Amateur Radio (ARRL)	£4.73
World Atlas (RACI)	£2.21
World Radio TV Handbook 1983	£12.25
10m FM for the Radio Amateur (Tab)	£4.23
80m DXing (CTI)	£3.62

Prices include postage, packing and VAT where applicable. Postal terms: cheques/POs with order (not stamps or book tokens). Giro account no: 533 5256.

PLEASE ALLOW UP TO 28 DAYS FOR DELIVERY

The RSGB is the national society representing all UK radio amateurs and membership is open to all interested in the hobby, including listeners. The Society also publishes a complete range of books, log books and maps for the radio amateur. Contact the membership services section for more information about amateur radio, the RSGB and its publications.



Radio Society of Great Britain
Alma House, Cranborne Road,
Potters Bar, Herts EN6 3JN
Telephone Potters Bar 59015

DEWSBURY ELECTRONICS



West Midlands only authorised TRIO dealer



Now in stock! TWA 4000A



The dual band FM mobile transceiver
Come in and try it for yourself

Also stockists of DAIWA-WELTZ-DAVTREND-TASCO TELEREADERS
MICROWAVE MODULES-ICS AMTOR-AEA PRODUCTS
DRAE-BNOS-JRC

Dewsbury Electronics, 176 Lower High Street,
Stourbridge, West Midlands.

Telephone: Stourbridge (0384) 390063.

Hire purchase available.



AUDIO FILTERS MODELS FL2, FL3, FL2/A

see us at
A.R.R.A.
Doncaster Oct. 6, 7, 8

Model FL3 represents the ultimate in audio filters for SSB and CW. Connected in series with the loudspeaker, it gives variable extra selectivity better than a whole bank of expensive crystal filters. In addition it contains an automatic notch filter which can remove a "tuner-upper" all by itself.

Model FL2 is exactly the same but without the auto-notch. Any existing or new FL2 can be up-graded to an FL3 by adding Model FL2/A conversion kit, which is a stand-alone auto-notch unit. Datong filters frequently allow continued copy when otherwise a QSO would have to be abandoned.

Prices: FL2 £89.70, FL3 £129.37, FL2/A £39.67

ACTIVE RECEIVING ANTENNAS

Datong active antennas are ideal for modern broadband communications receiver:—especially where space is limited.

- highly sensitive (comparable to full-size dipoles).
- Broadband coverage (below 200 kHz to over 30 MHz).
- needs no tuning, matching or other adjustments.
- two versions AD270 for indoor mounting or AD370 (illustrated) for outdoor use
- very compact, only 3 metres overall length. • professional performance standards.

Prices: Model AD270 (indoor use only) £51.75 Both prices include mains power unit. Model AD370 (for outdoor use) £69.00

MORSE TUTOR

The uniquely effective method of improving and maintaining Morse Code proficiency. Effectiveness proven by thousands of users world-wide.

- Practise anywhere, anytime at your convenience.
- Generates a random stream of perfect Morse in five character groups.
- D70's unique "DELAY" control allows you to learn each character with its correct high speed sound. Start with a long delay between each character and as you improve reduce the delay. The speed within each character always remains as set on the independent "SPEED" control.
- Features: long life battery operation, compact size, built-in loudspeaker plus personal earpiece.

Price: £56.35

Our full catalogue plus further details of any product are available free on request. All prices include VAT and postage and packing. Goods normally despatched within 3 days subject to availability.

Barclaycard, Access Orders—Tel: (0532) 552461



write to dept. P.W.
Spence Mills, Mill Lane
Bramley, Leeds LS13 3HE
England
Tel (0532) 552461

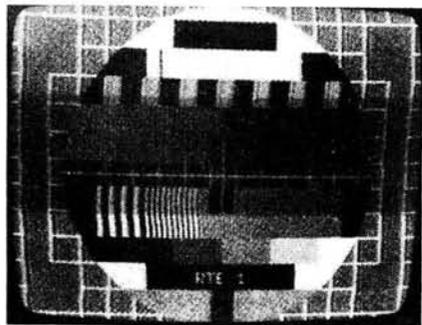


Fig. 1: Test card from Ireland

David Appleyard

their late night news. Over in Sweden, **David Appleyard**, using a National portable and indoor "V" antenna by the window of his 3rd floor flat in Uppsala, received a test card from RTE 1, Fig. 1, on Ireland's Ch.B 53.75MHz at 1030 on July 3. Then around 1050 the RTE clock came up showing 1150 (Fig. 2), followed at 1200 by High Mass, the start of the day's programmes. On June 17, Alan Taylor's wife was monitoring Band I and came across a test card or programme announcement with a picture of a dog with a bow on its neck in the centre of the screen. This gave way to a picture of a YL in what looked like a Chinese Red Army outfit followed by some oriental writing down the left side of the screen. Any ideas?

"Monday June 20 was a cracking day" writes **E. Weaver**, Redditch, who, along with contributors **Harold Brodribb**, St Leonards on Sea, **Paul Drinkwater**, Sut-

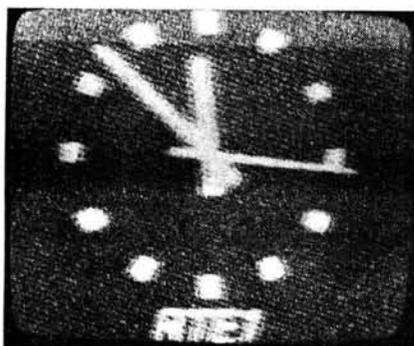


Fig. 2: RTE clock

David Appleyard

ton Coldfield, **Simon Hamer**, New Radnor, **David Newman**, Leicester, **Raymond O'Connor**, Dublin, **Alan Taylor** his wife and father, Coventry and **Roger Wallis**, supplied me with the information to make up the sporadic-E analysis chart (Fig. 3), covering the period June 20 to July 19. Among the test cards seen were those from Italy (Fig. 4) Ch.IB 62.25MHz, USSR (Fig. 5) on Ch.R1 and Yugoslavia (Fig. 6) on Ch.E3 55.25MHz, all sent to me by Roger Wallis. From your letters and my own observations the Hungarian, Italian, Norwegian and Russian clocks were seen, captions such as Budapest, Bucaresti, CST, CST-01, dt, Emission Experimental Teletexto TVE, EZO, Gamonitiero 3, HOBOTON, Norge Bagn, Gamlem, Hemnes, Kongsberg, Melhus and Steigen, NCT, OTK, RTVE, Aitana and Lamuela, Telewizja Polska, TVE Valencia and TVP NDT. Simon Hamer would like to know the meanings of the words, Dagskra, Frettir, Kiwanisk and Kvoldsins, he received from Iceland and another mystery caption RZYM. Many of you reported seeing programmes about ancient battles, cartoons, dancing, fashions, film reviews, medicine, music, news, weather and wild life and such sporting events as athletics, football, tennis and a rodeo.

Tropospheric

During the evening of June 25, **Brian Walsh**, Droitwich, on holiday in Norfolk, returned his set and received excellent u.h.f. pictures from Holland NED-1 and 2. From 2100 he watched *Rock Werchter 82*, *Avros Sports Panorama*, *Nos Journaal* and *Studio Sport* from Holland. After 2215 he saw *Starsky and Hutch* on the German station ZDF followed by *Heute* and the programme schedule for the 26th.

On June 18, Roger Wallis, who uses a card index system for his TVDX records, received pictures from Holland and Germany WDR 1 on Ch.32 and ZDF on Ch.37, Belgium Ch.8 on the 21st and ZDF again on the 25th. Alan Taylor's father, a medium wave, 14 and 28MHz DXer, was using Alan's Plustron TVR5D and received Dutch TV on Ch.29 on the

18th and RTBF-1 and a Dutch station in Band III on the 19th. Around 2300 on the 21st, **George Garden**, Bracknell, received varying strength colour pictures from Central TV's Waltham transmitter on Ch.61 and BBC2 Ch.55 from Tacolneston. After a slight variation of antenna direction at 2230 George logged Anglia TV from Sandy Heath on Ch.24.

The co-channel interference which upset the u.h.f. channels on July 7 was bad enough to make the national news and was reported in the *Daily Mirror* on the 8th under the heading of Telly Turmoil. While parked in Ashdown Forest at 1934 on July 1, I received very strong, negative pictures from France on at least 8 positions on the Plustron's dial between Chs.21 and 54. On the 13th I saw a male announcer on Ch.E10 with the caption Tagesthemen above him, any ideas? Band III was open again early on the 14th when, at 0824 I received test cards on Ch.E7 from Denmark and Germany NDR1 on Ch.E10 and from East Germany DDR with the OK caption and news on Ch.E5.

"This fine weather is certainly giving excellent TVDX, the u.h.f. bands are crammed with German and of course Dutch television around this area", writes **David Girdlestone** from Norwich. He adds "On Anglia Television's regional programme, *About Anglia* they read a letter from a man in Holland who likes watching British television programmes, so I sent Anglia Television a letter telling them that I often watch Dutch television programmes here in Norwich and enclosed a couple of photos, one test card and one Dutch commercial. Last Friday, 15th, in *About Anglia* they read my letter and showed my photos on the screen". Well done David, good bit of PR, I hope the Dutch viewer saw them. During the week leading up to the 16th, David received strong colour pictures from Holland Nederland 2 (Fig. 7), saw the commercials for Omo (Fig. 8) and Treets (Fig. 9), and Roger Moore in an episode of the *Persuaders* (Fig. 10), with Dutch sub-titles.

SSTV

The "Midlands" G station I referred to in our August issue who transmitted a page of *PW* to F3RT, was **Eric Cockerill** G4GOZ, Barnoldswick. He uses a Robot 400 SSTV converter, Philips camera, Swan Astro 150 transmitter and HQ1 Minibeam antenna. The picture I published of Leo F3RT was received by Peter Lincoln in Aldershot and Eric says, "Many of the other SSTV stations photographed by Peter, I have worked". Hope to hear more of your SSTV activities Eric and the same goes for F3RT.

Peter received three new countries on 14MHz, CE3UT who was in QSO with a German station and KP4YD calling CQ on June 14 and 8P6NC who was working LU5NA on the 26th. During several afternoons before July 11, Peter copied pictures from stations in Denmark, Germany, Italy, Scotland and Yugoslavia. At

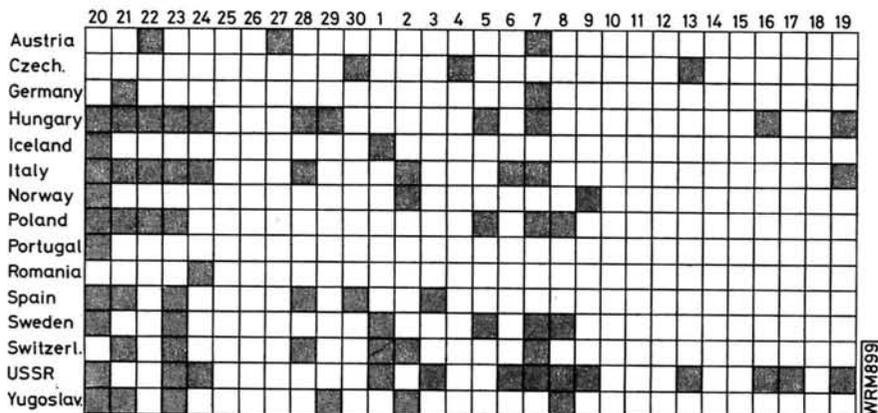


Fig. 3: Distribution of TV signals received in the UK

W1R899

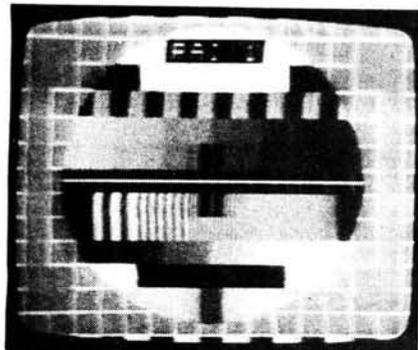


Fig. 4: Test card

Roger Wallis

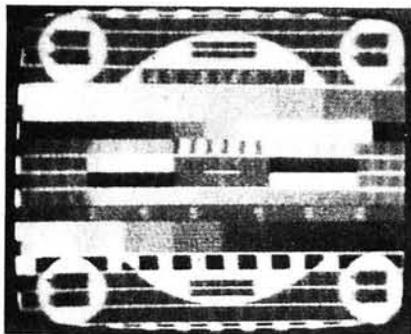


Fig. 5: Russian test card

Roger Wallis

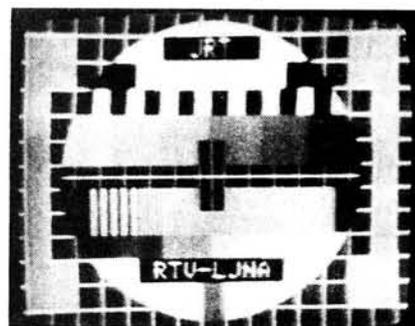


Fig. 6: Test card

Roger Wallis



Fig. 7: DX TV signal

David Girdlestone



Fig. 8: Dutch commercial

David Girdlestone



Fig. 9: Advertisement on Dutch TV

David Girdlestone

2027 on June 18, while the 144MHz band was open, Richard Thurlow G3WW, March, received SSTV signals from PE1DWQ off the back of his 2 by 16-element Tonna array. Richard's SSTV CQ at 2036 was answered by DK2TB in Hamburg and at 2050 by DF8BZ in Leer. At 2114, G4DYB, Sheffield, called Richard and they were soon joined by G4NJI, Rotherham and 2-way colour pictures were exchanged. At 2218, Richard received a QRZ from PE1BNI and their 2-way SSTV QSO gave Richard his 1876th 2-way first QSO'd station. On June 19, PE1ITA on 144MHz made it 1877 and PY2EUZ on 28MHz put it at 1878. Between June 20 and July 7, he worked OK1PDQ, F6AZT, WB9YZS, OH7UE, ON7SG, HB9CNV, WB2CDX, VE3LLG, 8P6NC Barbados (also his 113th country) and DL3GBZ on 14MHz, plus G4FAE on 144MHz the score went up to 1889. On July 7, Richard and his old friend ZS6BTD in Johannesburg made a first 24 seconds

single-frame colour 2-way QSO between South Africa and the UK. Our congratulations to both stations.

Other Stations

"I have always had the impression that the amount of know-how required for TV would have to be considerable. However I have found it to be quite straightforward", writes E. Weaver a new TVDXer from Redditch. He purchased a Plustron TVR5D, built a Band I dipole from the formula in Roger Bunney's book *Long Distance Television Reception*, installed a Wolsey Colour King antenna for u.h.f. and is well satisfied with the results. His equipment was ready for switch-on on June 17 and at 0815 he tuned through Band I and at 0836, up came the Grunten caption on Ch.E2. "I could hardly believe my eyes, a DX picture in the first half hour from scratch" he wrote and added,



Fig. 10: Received from Holland

David Girdlestone

"What an exciting and encouraging start".

Paul Drinkwater sent an impressive log for July 7 and was among my readers who identified several TV captions in his report.


**SEE SPECIAL
ANNOUNCEMENT
ON PAGE 57
OF THIS ISSUE**



Tandy®

The Largest Electronics Retailer In The World

Compact 3 1/2-Digit 16-Range Multimeter

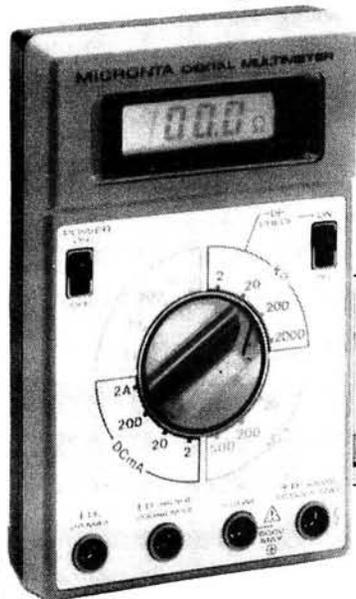

£34⁹⁵

*Ideal For The
Electronics Hobbyist*



- Fused and Overload Protected
- 10 Megohm Input

Digital accuracy at a practical price! DC volts: 2-20-200-2000V (max. 1000V), AC volts: 2-20-200-2000 (max. 500V), accurate from 45 Hz to 10 kHz. DC Current: 2-20-200mA-2A. Resistance: 2-20-200-2000k Ohms. 5^{3/16} x 3^{1/4} x 1^{7/16}". Includes spare fuse, test leads. Requires 2 "AA" batteries. 22-189

27 Ranges - 30,000 Ohms/Volt Multimeter

£22⁹⁵

*Ideal For
Workshop And
Field Testing*



- Colour-Coded 4" Mirrored Scale
- Single-Knob Function Switch
- Polarity Reverse Switch

Features output jack and DC polarity reverse switch. DC Volts: 0 to 1000, 8 ranges. AC Volts: 0 to 1000, 5 ranges. DC Current: 0-10 amps, 5 ranges. Resistance Rx1, Rx10, Rx1000, Rx10,000 (10 ohms centre scale). dB: -10 to +62, 5 ranges. Requires one "AA", one 9v battery. 6^{1/4} x 4^{1/2} x 1^{3/4}" 22-203

Micronta™ 50K Ohms/V Multitester



£27⁹⁵

- Volts/Amps "Range-Doubler"
- 4 1/4" Mirrored Scale

Convenient single-knob function switch. DC Current: 0 to 10 amps. Resistance: Rx1, Rx10, Rx100, Rx1k, Rx10k. AC/DC V: 0 to 1000. Requires batteries. 22-204

Dynamic Transistor Checker



£9⁹⁵

- Makes Go/No-Go Tests On Small Signal and Power Types

Indicates relative current gain, "opens", "shorts". Socket plus hook clip leads for in-circuit tests. Output jacks for external meter or scope. 2^{3/4} x 4^{3/8} x 3^{1/16}". Requires "AA" battery. 22-025

Micronta™ Clamp Meter



£27⁹⁵

- Overload Protected
- Pointer Lock Switch

Measure AC current without disconnecting or breaking the line being checked. Large range selector is positioned for one-hand operation. Incorporates a pointer lock switch (for reading later). AC current: 0-6-15-60-150-300 amperes. Accuracy: ±3%. 22-160

Microwave Leakage Detector



£9⁹⁵

- Checks Microwave Oven Door Seals

Compact and light microwave leakage detector is easy to use - move along the door seals of your microwave cooker and the meter indicates the relative amount of microwave energy. **Not a certification instrument.** Measures just 1^{1/16} x 1^{7/8} x 4^{1/2}". 22-2001

OVER 340 STORES AND DEALERSHIPS NATIONWIDE
Check your phone book for the Tandy Store or Dealer nearest you



Known as Radio Shack in the USA
Prices may vary at dealers
Offers subject to availability

WOOD & DOUGLAS

We have moved! Our new manufacturing facility in Berkshire will provide an even better service for our extensive range. Credit card orders can also now be taken, ring for details.

NEW PRODUCTS for the exhibition season from our new factory facility.

144LIN25B 25W VHF LINEAR – A single stage higher power version of our popular 144LIN10B designed for the 2-3W output level FM or SSB equipments. The board retains the straight through mode in receive or when the power supply is disconnected and fits neatly into a small diecast box. Ideal for the FT290. Price details: **£29.95** in kit, **£40.25** as an assembled module.

6RX2 6M CONVERTER – You may not be one of the privileged 40 but you can at least listen on this compact high performance converter for 6M. It allows reception on the 2M band. The board has options for local oscillator output and r.f. gain adjustment. Price details: **£19.95** in kit, **£27.60** as an assembled module.

MPA2 MICROPHONE PRE-AMPLIFIER – A buffered output version of the MPA1. The board will now interface with low input impedance equipment without degrading the response. Price details: **£3.45** in kit, **£5.95** as an assembled module.

TVMOD1 Ch 36 MODULATOR – An alternative to imported UHF modulators giving adjustable frequency over the range 400 to 600 MHz. This enables system checks at 70cms or directly into your TV set in Band IV. The board has video gain and modulation preset adjustable. The output oscillator runs at 200-300MHz so it could be adapted to Band III. Price details: **£6.95** in kit form, **£10.15** as an assembled module.

Impressive new products but the best is yet to come...

In May a new design for a 50W h.f. transceiver will appear in Radio Communications. While it is a departure from our normal policy of marketing only our own designs we were so impressed by George Fare's (G30GQ) write up that we have offered to back the project with component kits. This will include PCB's and all components per our normal policy. Full price details are not yet available but a full kit should market for approximately £250 inc. VAT. Some provisional technical details are available, please ask.

When you purchase one of our products you are guaranteed success because we offer full back up and servicing on any item no matter how small. The confidence we have in the product is reflected in the range available and the low service return rate incurred. Why not try a kit today? We accept credit cards or written orders direct to our industrial premises or at rallies and exhibitions throughout the season. Enjoy your hobby more by building your next rig or accessory.

Unit 13, Youngs Development
Aldermaston, Reading RG7 4PQ
Tel 07356 5324. Telex 848702



ELECTROVALUE

THE P.W.
ENTHUSIAST'S

A-Z BUYING GUIDE

It's amazing what you'll find in the pages of our current summer price list, be you beginner, expert or professional. The list below gives some idea of the enormous stocks we carry, and our service is just about as good as meticulous care can make it. **WRITE, PHONE OR CALL FOR OUR SUMMER PRICE LIST NOW!**

**IT'S
FREE!**

**Good Bargains
Good Service
Good Choice**

Please mention this journal when applying

- | | | | |
|---------------------|---------------|------------------|-----------------|
| Access facilities | Connectors | Lamps | Semi-conductors |
| Aerosols | Discounts | Meters | Switches |
| Batteries | Electrolytics | Opto-electronics | Solder tools |
| Boxes | Ferrites | Potentiometers | Tools |
| Breadboards | Grommets | Pot Cores | Transformers |
| Computers & Equipmt | Hardware | Quantity prices | Vero products |
| Capacitors | I.Cs | Resistors | Visa facilities |
| | Knobs | Relays | Zener diodes |

ELECTROVALUE LTD., 28 St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB. Egham 33603 (London 87; STD 0784) Telex 264475; **Northern Shop** (Callers only) 680 Burnage Lane M/c M19 1NA. (061-432 4945) **EV Computing Shop**, 700 Burnage Lane, Manchester (061-431 4866).



Northampton
Communications

PHONELINK

A separate unit that enables any radio system to have a direct link to the telephone network.

Phone for further details:

Northampton Communications Limited
Communications House
76 Earl Street, Northampton. NN1 3AX.
Telephone: (0604) 33936 or 38202

SECURITY Alarm Systems

FREE COMPREHENSIVE CATALOGUE!

- **LOWEST DISCOUNT PRICES**
- **HIGHEST QUALITY EQUIPMENT**
- **FREE DIY DESIGN GUIDE**
- **FULLY ILLUSTRATED**
- **MICROCHIP CIRCUITRY**
- **QUICK DESPATCH SERVICE**
- **FULL INSTRUCTIONS**

SEND SAE OR PHONE

C-TEC SECURITY, Dept PW,
60 Market St, Wigan WN1 1HX.
Telephone (0942) 42444

Trade
Enquires
Welcome

GET THE COMPLETE PICTURE

— ORDER YOUR COPY NOW —

★ STILL THE ONLY CATALOGUE FOR THE COMPLETE RANGE OF COMPONENTS. BATTERIES, CRYSTAL FILTERS, RF POWER, MOSFET, TOKO COILS, CHOKES, ALPS PLOTTERS, SOLENOID CASSETTE MECHS ETC.

COMPONENTS FOR ELECTRONICS, COMMUNICATIONS & COMPUTING

ambit[®]
INTERNATIONAL

WORLD OF RADIO & ELECTRONICS
— CATALOGUE —

3x£1 DISCOUNT VOUCHERS
144 PAGES
80p

★ FIRST WITH ON-LINE COMPUTER SHOPPING


★ FIRST FOR INNOVATION

★ FIRST FOR VALUE

★ FIRST FOR CHOICE

★ FIRST FOR SERVICE

SUMMER '83

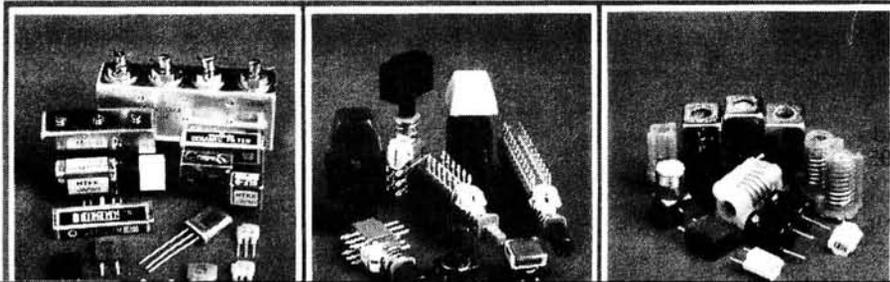


ambit[®] INTERNATIONAL

200 North Service Road, Brentwood, Essex CM14 4SG
Tel: (Consumer Sales/Enquiries) 0277-230909.
Tel: (Industrial Sales/Enquiries) 0277-231616.
Tlx: 995194 AMBIT G. Data 24hrs (RS232/300 baud) 0277-232628.
Catalogues normally despatched by return of post

LECTRO-LINES

101 Hainault Road, Romford, Essex RM5 3HF.
Tel. Romford 22018/9

AM/FM STEREO TUNER MODULE 3 BAND

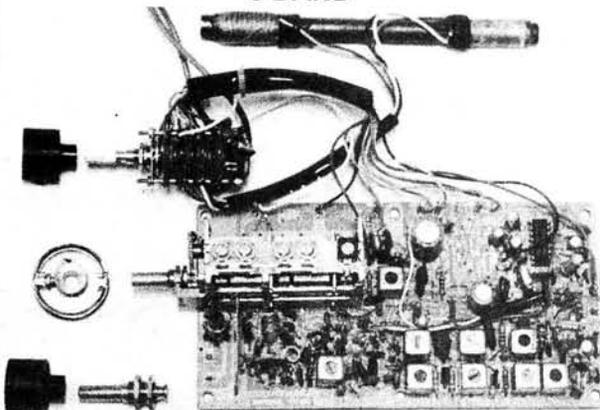

New boxed pre-aligned and tested. Complete with ferrite rod aerial, 6 way function switch, drive drum, cord drive, knobs, sample calibration scale and circuit diagram.

3 stage FM tuning, phase lock loop decoder, L.E.D. stereo indicator, FM sensitivity 2 uV.

Wavebands FM 88-108 MHz, LW 160-280 KHz,
MW 525-1650 KHz.

Output approximately 200 mV. Input 12v DC.

Price only £6.90 including VAT
plus £1.50 P & P Goods by return.

SPECIAL OFFER

THE ENFIELD EMPORIUM

ANTENNAS

ASP - Jaybeam -
Tonna - Cue Dee
Now in stock

WE STOCK THE FULL RANGE OF



EQUIPMENT AND ALL ACCESSORIES ARE AVAILABLE

ROTATORS

Kenpro - Diawa -
Hirschmann
Large selection in stock

TONO

Linears - RTTY
Decoders - Morse
Decoders - Full
range available

**FDK-
AZDEN**

ADONIS

Boom
microphones
available for
TR2500 - IC2E -
Yaesu 208/708

Secondhand Equipment

We always have a large selection of secondhand equipment in stock. Please phone for details.

Full range of
YAESU
(/SOMMERKAMP)
equipment
available

We stock a full range of
WELZ

Slim Jim - Only £7.50 inc. p+p.

PART EXCHANGES WELCOME

Stamped Addressed Envelope for brochure etc.

All prices include VAT. Goods normally despatched by return, but please allow up to 7 days.

281 HERTFORD ROAD, EDMONTON N9.

Telephone (01) 804 0128

Buses 249, 279 and 149 stop outside the door.


Opening hours: Mon-Thur 9-6; Fri 9-8; Sat 9-6 AND NOW Sun 9-1



Do you know what time it is!

When the globe of this digital clock is revolved, a red lamp indicating a major city in the world will blink, and the current time of that city will be displayed. At a glance know the current times of 24 different time zones. This mini-globe clock stands 195mm. high and also has an alarm fitted. This useful device should stop you getting your Amateur friends, on the other side of the world, out of bed in the middle of the night.

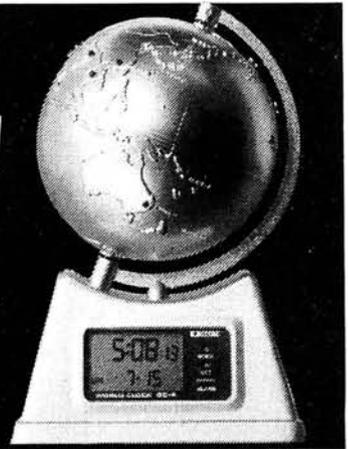Thanet Electronics 143 Reculver Road, Herne Bay, Kent
Tel: (02273) 63859/63850



L A R THE AMATEURS PROFESSIONAL SUPPLIER L A R

 <p>TRIO R2000 General Coverage All Mode Receiver</p> <p>PRICE £398 INC VAT CARR £5</p>	 <p>TRIO TR7930 2 Meter FM Transceiver Memory - Auto Scanning</p> <p>PRICE £305 INC VAT CARR £5</p>	 <p>TRIO 130V Mobile HF Transceiver SSB-CW All Amateur Bands</p> <p>PRICE £456 INC VAT CARR £5</p>	 <p>TRIO TS430S Base HF Transceiver General Coverage Receiver All Mode FM Optional</p> <p>PRICE £736 INC VAT CARR £5</p>
-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

LEEDS AMATEUR RADIO 27, Cookridge Street, Leeds. LS2 3AG. Tel. 452657

Please send for our Catalogue and/or Antenna Catalogue
60p EACH or £1.00 FOR BOTH PLUS PRICE LIST

Goods By Return Subject To Availability

SALES / SERVICE / MAIL ORDER Depts. 60, Green Road, Meanwood, Leeds. LS6 4JP. Tel. 782224







FREQUENCY COUNTERS


HIGH PERFORMANCE
HIGH RELIABILITY
LOW COST

EX-STOCK DELIVERY

The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

<ul style="list-style-type: none"> ★ Measuring typically 2Hz - 1.2GHz ★ Sensitivity < 50mV at 1GHz ★ Setability 0.5ppm ★ High Accuracy ★ 3 Gate Times 	<ul style="list-style-type: none"> ★ Low Pass Filter ★ Battery or Mains ★ Factory Calibrated ★ 1-Year Guarantee ★ 0.5" easy to read L.E.D. Display
-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

PRICES (Inc. adaptor/charger, P & P and VAT)		
METEOR 100 (100MHz)	£104.07	Illustrated colour brochure with technical specification and prices available on request.
METEOR 600 (600MHz)	£133.97	
METEOR 1000 (1GHz)	£184.57	

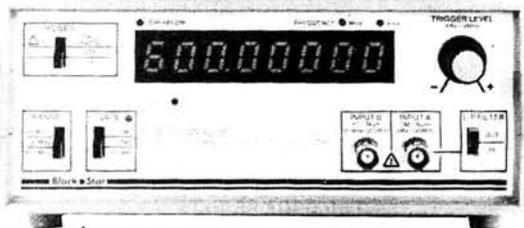



Designed and manufactured in Britain.



BLACK STAR LTD. 9A Crown Street, St. Ives, Huntingdon, Cambs, PE17 4EB, England.
Tel: (0480) 62440 Telex: 32339

R.F. POWER TRANSISTORS Many other types available				NEW VALVES National, Varian, Mullard, RCA, IIT,...					
2N3375	5.85	SD 1005	6.48	MRF 221	12.05	E80CC	15.00	6A8A	2.30
2N3533	1.50	SD 1006	1.80	MRF 231	9.36	E80F	13.30	6AU6GA	4.25
2N3733	3.20	SD 1012FL	7.50	MRF 234	13.80	E88CC	4.50	6AW8A	2.85
2N3866	1.00	SD 1013	7.50	MRF 237	2.75	E180F	8.00	6B8	3.10
2N3926	9.85	SD 1088	23.00	MRF 238	12.60	EC91	8.65	6B8A	3.40
2N3927	11.02	SD 1089	25.64	MRF 239	15.00	ECC81	1.19	6BH6	2.55
2N4416	0.75	SD 1098	32.82	MRF 240	18.55	ECC82	1.19	6BQ7A	3.45
2N4427	1.00	SD 1127	2.60	MRF 243	28.08	ECC83	1.19	6BR8A	3.50
2N4440	6.50	SD 1135	8.42	MRF 245	30.10	ECC88	2.30	6B26	2.50
2N5016	6.72	SD 1136	11.80	MRF 247	34.00	ECC91	3.75	6CB6A	2.30
2N5090	16.80	SD 1143	8.50	MRF 260	5.00	ECH81	2.50	6CD6GA	4.65
2N5109	2.01	SD 1219	11.40	MRF 261	7.00	EF86	1.35	6CL6	3.40
2N5179	0.86	SD 1229FL	7.80	MRF 262	10.40	EL34	2.68	6CW4	6.85
2N5485	0.62	SD 1272	10.20	MRF 264	11.00	EL84	1.00	6DK6	2.65
2N5486	0.66	SD 1272FL	10.20	MRF 314	25.06	K777	6.80	6DQ5	5.50
2N5589	4.70	SD 1407	22.50	MRF 401	10.84	PC92	4.00	6D06B	4.00
2N5590	6.85	SD 1410	19.68	MRF 406	11.83	PCF802	1.60	6EA8	2.50
2N5591	8.90	SD 1412	27.18	MRF 421	31.57	PCL805	1.00	6GK6	2.46
2N5635	5.20	SD 1416	30.00	MRF 422	35.52	PL509	4.75	6J4	4.20
2N5636	9.70	SD 1418	26.22	MRF 449A	14.00	PL519	4.75	6J5	4.30
2N5637	11.25	SD 1428	23.00	MRF 450A	11.40	PY500A	2.98	6J6A	4.90
2N5641	5.35	SD 1429	13.98	MRF 453	13.30	QV02-E	6.00	6J8A	4.05
2N5642	7.90	SD 1444	3.00	MRF 454A	16.80	/6939	15.75	6J86C	5.00
2N5643	13.00	SD 1488	26.25	MRF 455	13.80	QV03-10	6.00	6K6GT	2.75
2N5913	2.10	25C730	3.84	MRF 460	15.78	/6360	9.50	6KD6	5.60
2N5944	6.90	25C1165	5.88	MRF 464	31.57	QV03-20A	6.00	6L6	6.00
2N5945	8.95	25C1177	16.14	MRF 472	2.50	/6252	63.00	6SN7GTB	2.75
2N5946	11.40	25C1306	1.44	MRF 475	2.40	QV06-40A	6.00	6080	11.00
2N6080	5.10	25C1307	2.34	MRF 476	1.71	/5894	45.00	6146A	7.70
2N6081	6.75	25C1678	1.44	MRF 477	10.70	QV03-12	6.00	6146B	7.70
2N6082	8.45	25C1946A	18.54	MRF 515	2.70	/5763	5.80	6159B	18.00
2N6083	8.75	25C1947	9.24	MRF 604	1.60	UCL 82	1.60	6201	6.30
2N6084	11.70	25C1970	2.76	MRF 607	2.20	2D21	2.85	6360	6.00
2N6094	5.00	25C1971	7.50	MRF 629	4.10	3B28	14.95	6550A	6.70
2N6095	6.90	25C1972	10.32	MRF 646	26.24	4CX250E	37.20	6688	9.80
2N6096	8.40	25C2337	15.00	MRF 648	35.14	4CX350A	69.50	6689	12.24
2N6097	13.30	25C2538	1.62	MRF 901	2.58	5U4GB	2.50	6883B	7.70
						5670	3.40	6973	3.85
						5726	2.40	7360	9.50
						5763	4.05	7551	5.90
						5814A	3.50	7558	9.50
						5842	11.20	791A	3.80
						5965	3.25	786B	3.95
						6AH6	4.75	811A	14.75
						6AK5	3.55	812A	18.55
						6AK6	2.00	813A	60.00
						6AN5	4.40	866A	15.00
						6AN8A	3.20	872A	15.65
						6AQ5A	2.15	8298A	4.90
						6AS6	5.10	8417	5.80
						6ASTG	8.45	931A	18.20
						6AT6	1.35	12AY7	3.75
						6AU5GT	4.50	12BY7A	2.60

Normally stock items are shipped by return post.
We can supply nearly ANY TYPE OF VALVE or RF POWER TRANSISTOR - ring for quotation.

TERMS: Cash, Postal Order or Cheque with order
CREDIT: Accounts available subject to approved references
POSTAGE: Add 60p to order
VAT: All prices are excluding VAT, please add 15% to order
GUARANTEE: All goods brand new and to specification

SELECTRONIC

Radio, TV and Radio Communication Specialists

934 MHz UHF Radio Equipment

An easily installed radio system, with uses for small businesses, from home to small boats and a useful home to car two-way private radio system. Ranges of up to 200 miles are being obtained by present users.

We have in stock the full range of Reftec equipment i.e. Mobile Transceiver MTR 934/2 plus full range of aerials and fittings, etc.

S.A.E. for full details.

- ★ STOCKISTS OF AMATEUR RADIO EQUIPMENT: Yaesu, Trio, F.D.K. Tonna, Jaybeam, Revco etc.
- ★ REPAIRS & MODIFICATIONS BY EXPERIENCED & QUALIFIED STAFF.
- ★ CREDIT TERMS AVAILABLE.
- ★ TANDY MODEL 100 PORTABLE NOW IN STOCK.

For further information please ring:
Mike Machin on (0268) 691481.

203, HIGH STREET,
CANBY, INGHAM ISLAND,
ESSEX. SS8 7RN.

Tandy
AUTHORISED DEALER



AERIAL KITS ex Army comprising 10 3ft 1" screw sections plus 12ft whip aerial, intended to make a 42ft vertical, supplied with adaptor, guys, stakes, hammer, insulated base, carrying case, new unused in case. **£55. H.F. TRANS UNIT** part of Navy 619 equip, tunes 1.5 to 16Mc/s in 3 bands xtal or VFO, O/P 40 watts CW or AM as internal Aerial tuning unit, direct calibration, reqs ext power of 300/600V DC etc in neat case size 13x14x14" supplied with circ & notes full spec on list. **£125. F.M. TUNER HEAD** small 3 transis tuner 88 to 108Mc/s manual tuning as IF O/P of 10.7 Mc/s reqs supply of 12v DC 10 Ma can be used with S.W. Rx that will tune 10.7 Mc/s to make a Low band RT or Police freq convertor, will also Mod to make FM Radio mike, as provision for AGC & AFC new unused. **£4.75. MORSE KEYS** miniature key for use with A510 set new. **£3.50. AERIAL FEEDERS** twin 75 ohm feeder with dipole center approx 15 Mts new. **2 for £2.50. PANEL METERS** mostly M.C. type 2/3/4" dia new 4 different for **£6.50. TX ATU HF 2** to 16Mc/s part of C11 equipment 75 ohm I/P O/P for whip or long wire ext at 1 Kw with int 400 watt dummy tune up load, swr meter, aerial c/o relay, blower etc in case size 14x20x15" reqs 24v DC for relay & blower. **£65. RADIOSONDE MK.11** works on 27Mc/s transmits in turn audio tones from 3 sensors, press, temp & RH with chart & circ reqs 90/2v DC new. **£7.50** also type M.60 more modern type sends info in code reqs 3v supply new. **£12.50. METERS** Record Circa Scale 200/250V AC 50c M.I. 4x4x3 1/2" new **£15.** also Freq meters 45/65c/s 230v new. **£11.50. VALVE KITS** with CV type 6BA6x5, 6BE6x2, EF91x4, EB91x3, EL91. **£10. WAVEMETER CLASS. D. No. 2** covers 1.2 to 19.2 Mc/s in 4 ranges, Hetrodyne or Absorbtion for mains or 12v DC with charts, phones, leads, spare valves, inst book, etc. **£35. ARMY RADIO No. 31** old manpack set covers 40/48Mc/s in 200Kc steps Tx & Rx req ext dry batt with, F.M. with book. **£24.50. ARMY C.12 SET.** low power HF T/R cover 1.6 to 10Mc/s in two bands can be set up on two freqs, C.W. or AM on Tx uses 13 miniature valves in T/R plus 2 in intercom amp, pwr out 3/5 watts, this unit reqs ext p.u. valves wired for 12v, RF out 75 ohm reqs ATU for whip or long wire, good cond with book, modern version of 19 set. **£75.**

Above prices include carr/postage & VAT.

Allow 14 days for delivery, goods ex equip unless stated new, SAE with enquiry or 2x 16p stamps for List 32.

A. H. SUPPLIES

122, Handsworth Road, SHEFFIELD S9 4AE
Telephone: 444278 (0742)

SPECTRUM COMMUNICATIONS

SPEECH PROCESSOR, Amplifier, compressor, clipper and filter with level meter. Adjustable clip and output level, type SP100.

Kit inc. box £14.66, Built £20.65.

NOISE SQUELCH, Noise activated pulse blanking system suitable for F.M. rigs, type NS1000. Kit £7.02, Built £10.00.

TRANSMIT AMPLIFIER, 2 metre linear, 1-5W 1/P, 10-25W O/P, unswitched, type TA2. Kit £13.54, Built £19.54

RECEIVE PREAMPLIFIER, 2 metre, low noise, variable gain 0-20dB, carrier switched, RP2S/1. Kit inc. box £11.78, Built £19.50.

RECEIVE CONVERTERS, 2 metre, 4 metre or 6 metre, low noise <1.5dB, gain 26dB 10 metre IF, LO output, types RC2-10, RC4-10, RC6-10. Kit £14.30, Built £27.30.

TRANSMIT CONVERTER, 2 metre, 4 metre or 6 metre, 0.5W output, 0.1-1W 10 metre 1/P and low level LO I/P, types TC10-2, TC10-4, TC10-6. Kit £15.00, Built £23.50.

Delivery within 7 days subject to availability
Vat inc. prices, add 35p for P&P. Send SAE for product price list.

UNIT B6, MARABOUT INDUSTRIAL ESTATE, BARCLAYCARD VISA
DORCHESTER, DORSET. TEL 0305 62250

AMATEUR RADIO EQUIPMENT IN THE SOUTHWEST



YAESU

APPOINTED AGENTS FOR



FT ONE
FT 980
FT 102
FT 757 GX
FT 77
FT 726

FT 780R
FT 480R
FT 290R
FT 790R
FT 208

FT 708
FT 230
FT 730
FRG 7700

IC 2E
IC 4E
IC 25E
IC 45E
IC 251E

IC 271
IC 720
IC 730
IC 740
IC 751
IC 290E*
IC 290H
IC R70

All models normally always in stock
PLUS FULL RANGE OF ACCESSORIES

Ancillary equipment by: Microwave Modules, Mutek, Datong, Drae, Hansen, Hamp-tron, Tokyo, Hypower, Himound, Shure, Tono, Toyo, Welz and SEM.

Aerials by: Jaybeam, T.E.T. Hygain, G. Whip

TONO & TASCOS - RTTY/CW SEND/READERS

ALSO Connectors, Dummy Loads, Rotators, Cables, Valves, etc.

RSGB Publications - SAMS, ARRL

ACCESS - INSTANT CREDIT - BARCLAYCARD

Contact or visit - Mail Order on all items. Please allow 7 days delivery.

REG. WARD & CO. LTD.

GEORGE STREET, AXMINSTER, DEVON EX13 5DP

Reg G2BSW

Telephone (0297) 33163

Rodney G6LUJ

SMALL ADS

The prepaid rate for classified advertisements is 34 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £11.20 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Wireless and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance should be sent to the Classified Advertisement Dept., Practical Wireless, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5785).

NOTICE TO READERS

Whilst prices of goods shown in advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

Wanted

ELECTRONIC COMPONENTS PURCHASED. All types considered - Must be new. Send detailed list - Offer by return - WALTONS, 55A Worcester Street, Wolverhampton.

Veteran & Vintage

OVER 200 RADIO'S 1920s-1950s. SAE for list. Valve Radio's etc. repaired-restored. **RADIO VINTAGE**, 250 Seabrook Road, Seabrook, Hythe, Kent. CT21 5RQ. Phone (0303) 30693. Anytime.

VINTAGE VALVE WIRELESS RECEIVERS plus repairs, service information, spares, valves. S.a.e. information MR M. SMALL, 8 Cherrytree Road, Chinnor, Oxfordshire, OX9 4QY.

Software

ELECTRON, ORIC, BBC PROGRAMS: Morse Tutor £4. Locator gives distance, bearing, points, handles, Lat/Long, QRA, QTHL £4. BBC RTTY £4 (requires TU). Texas TI99 Locator £5. SAE details. **VOCKE SOFTWARE**, T. Tugwell, 11 The Dell, Stevenage, Herts.

MORSE CODE TRAINER. For 16K Spectrum £4.50 inc. post. W. CARTWRIGHT, 51 Oak Road, Oldbury, Warley, West Midlands B68 0BH.

BBC 'B' PROGRAM: calculates formulae listed R.A.E. Examination Manual: Cassette £8.50. HUGHES, Can-y-Gwynn, Flint Mountain, Clwyd CH6 5QG.

Books and Publications

WORLD RADIO TV HANDBOOK 1983, delivery expected late February. Introductory price includes first class letter post upon publication. Send £12.10 or Access/Visa number to: POINTSEA, 25 Westgate, North Berwick, East Lothian.

AIRCRAFT COMMUNICATIONS HANDBOOK (UK/EUROPE) including spot MF, HF, VHF, UHF, Frequencies, Military & Civil Airports, Air Traffic Control Centres, Long Range Stations, Meteorological Broadcasts, Broadcast Times, Navigation Beacons, Co-Ordinates, Callsigns, Maps, etc. £7.50, P/P £1. PLH ELECTRONICS, 70 Vallis Road, Frome, Somerset, BA11 3EJ.

Receivers and Components

MOST TYPES OF L.O.P.T. SUPPLIED. Colour £8.00, Mono £7.00, inc. P&P. Rewind service available. **PAP-WORTH TRANSFORMERS**, 80 Merton High Street, London SW19. 01-540 3955.

NOW OPEN IN NEWCASTLE

For the best in Electronic Components, Test Equipment and Accessories.

MARLBOROUGH

ELECTRONIC COMPONENTS

15 Waterloo Street, Newcastle NE1 4DE

Tel. 618377

Open 9am-6pm Mon-Sat - Easy Parking

Stockists of:

Transistors, Resistors, Capacitors, I.C. Diodes, Electronic Books, Etc.

VHF CONVERTER. 45-220MHz (Varicap) 23-30MHz tunable if O/P. £8.50. Satellite TV receiving equipment available at reasonable prices. SAE data, lists. H. COCKS, Cripps Corner, Robertsbridge, Sussex. Tel. 058083-317.

BOURNEMOUTH/BOSCOMBE. Electronic components specialists for 33 years. **FORRESTERS** (National Radio Supplies) late Holdenhurst Rd. now at 36, Ashley Rd., Boscombe. Tel. 302204. Closed Weds.

BRAND NEW COMPONENTS BY RETURN

HIGH STABILITY MINIATURE FILM RESISTORS 5%
 1W E24 Series 0.51R-10MΩ (Except 7MΩ)-1p.
 0.125W E12 Series 10R to 1MΩ-2p. 0.5W E12 Series 1R0 to 10MΩ-1p. 1.0W E12 Series 10R to 10MΩ-5p.
 1W Metal Film E12 Series 10R to 1MΩ 5%-2p. 1%-3p.

CAPACITORS.
SUBMINIATURE Ceramic E12 100V 2% 1.8pf. to 47pf.-3p.
 2% 56pf. to 330pf.-4p. 10% 390pf. to 4700pf.-4p.
Plate Ceramic 50V Wkg. Vertical Mounting.
 E12 22pf. to 1000pf. & E6 1K5pf. to 47Kpf.-2p.
Miniature Polyester 250V Wkg. Vertical Mounting.
 0.1, .015, .022, .033, .047 & .068 mfd.-4p.
 0.1-5p. 0.15 & 0.22-6p. 0.33 & 0.47-8p.
 0.68-11p. 1.0-15p. 1.5-20p. 2.2-22p.

ELECTROLYTIC. Wire Ended (Mfda/Volts).
 0.47/50 5p 22/25 6p 100/25 7p 470/25 11p
 1.0/50 5p 22/50 6p 100/50 8p 470/40 16p
 2.2/50 5p 47/16 6p 220/16 8p 1000/15 15p
 4.7/50 5p 47/25 6p 220/25 8p 1000/25 25p
 10/50 5p 47/50 6p 220/50 10p 1000/40 35p
 22/16 6p 100/16 7p 470/16 11p 2200/16 20p

TANTALUM BEAD SUBMINIATURE ELECTROLYTICS.
 0.1, 0.22, 0.47, 1.0, 2.2 @ 35V & 4.7 @ 6.3V-14p.
 4.7/16V & 25V-15p. 10/16V & 22/6-20p. 10/25-25p.
 10/35V, 22/16V, 47/6.3V, 68/3V & 100/3V-30p.
 15/25, 22/25, 47/10-35p. 47/16-80p. 220/16-£1.20.
Polyethylene 63V Wkg. E12 Series Long Axial Wires.
 10 pf. to 820 pf.-3p. 1000 pf. to 10,000 pf.-4p.

TRANSISTORS.
 BC107/8/9 12p BC182L 8p BF197 10p
 BC147/8/9 10p BC184L 8p BFY50/51/52 20p
 BC157/8/9 10p BC212L 8p 8FX88 25p
 BC547C/8C/9C 7p BCY70 15p 2N2926 7p
 BC557C/8C/9C 7p BF195 10p 2N3055 50p

8 Pin D.I.L. i.c.'s 741 Op/amp-18p. 555 Timer-24p.
 Holders 8 Pin-9p. 14 Pin-12p. 16 Pin-14p. 18 Pin-16p.
 24 Pin-22p. 28 Pin-25p. 40 Pin-30p.

DIODES (p.i.v./amps).
 75/25mA 1N4148 2p 1250/1A BY127 10p
 100/1A 1N4002 4p 400/3A 1N5404 14p
 800/1A 1N4006 6p 60/1.5A SIM1 5p
 1000/1A 1N4007 7p 30/150mA AAY32 12p

ZENER DIODES.
 E24 Series 3V3 to 33V 400mW-8p. 1W-14p.
L.E.D.'s 3 mm. & 5 mm. Red-10p. Green, Yellow-14p.
 Grommets for 3 mm.-11p. Holders for 5 mm.-2p.

FUSES. 20mm. Glass. 100mA to 5A, Q.B.-5p. A/S-8p.
VOLTAGE REGULATORS +5V, 8V, 12V, 15V 100mA-35p.
 5V, 8V, 12V, 15V, 18V & 24V, 1A-55p.

PRESET POTENTIOMETERS.
 50mW & 1W 100R to 1MΩ-7p.
PAIRS BATTERY SNAPS PP3-6p. PP9-12p.

THE C.R. SUPPLY CO.

127, Chesterfield Road, Sheffield S8 0RN.
 V.A.T. Inclusive Prices, Postage 15p
 (FREE over £5.00)

RADIO CANADA, Peking, Australia, Voice of America. A Vega 206 (6xSW/MW/LW) pulls these and dozens more. £23.45. Year's guarantee. Return despatch. **CORRIGAN RADIOWATCH**, Building 109, Prestwick Airport, KA9 2RT.

CRYSTALS Brand new high-precision. You benefit from very large stocks held for industrial supplies. All normal frequency standards, baud rates, MPU, and all magazine projects inc: HC33/U: 1-0. £3.75. 2.5625 MHz. £3.50. HC18/U: 4-0. 5-0. 6-0. 7-0. 8-0. 9-0. 10-0. 10-7. 12-0. 15-0. 16-0. 18-0. 20-0. 38.6667 MHz. £3.35. Selected freqs stocked in Glider, Marine and 27 MHz bands. Any freq made to order in 8 weeks from £4.50, 2-3 week service available.
CB Beat "Bleed-Over" with our special 10.695 MHz, 7 kHz BW. HC 18/U Filters £4.00 each. Quantity discounts. Many crystals stocked for CB conversions.
 Prices inc. VAT and UK post. SAE lists.

P. R. GOLLEGE ELECTRONICS
 G3EDW, Merriott, Somerset, TA16 5NS.
 Tel: 0460 73718

ELECTRONIC BARGAIN SUPPLIES

MINIATURE TRANSISTORISED BFO UNIT.
 Enables you to receive C.W. and S.S.B. transmission. Fully transistorised (tunable). Very compact. Fits anywhere. Single hole fixing. Brand new with fitting instructions. £6.95. PP 50p.
LIGHTWEIGHT HEADSETS (Govt. release). Brand new 600 ohms impedance. A bargain at £3.50. PP £1.50. 2 pairs for £7.50 post free.

THE GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK

Gives detailed information and circuit diagrams for British and American Government Surplus Receivers, Transmitters and Test Equipment etc. Also suggested modification details and improvements for surplus equipment. Incorporated is a Surplus/Commercial cross referenced valve and transistors guide. The standard reference work in this field. Only £7.50 p.p. £1.50. No VAT on books.

HALF-PRICE TRANSFORMER SALE. TYPE 1. Midget clamped type. Input 200/250V. 50 c/s. Output 250-0-250V. 60ma. 6.3v at 2 amps. Price £2.50. P&P £1.50. 2 for £7.00 post free.
 TYPE 2. Upright mounting, fully shrouded. 425-0-425V. 200ma. 6.3v. at 4a. C.T. plus 6.3v at 4a. Plus 5v at 3a. Should be £25.00 each. OUR PRICE £7.50. P&P £2.50. Ideal for valve amplifiers incl. RSC and Linear. TYPE 3. 450-0-450V. 200ma. 6.3v at 4a. C.T. 5v at 3a. Should be £25.00. OUR PRICE £8.00. P&P £2.50. Ideal for group valve amplifiers and also for transmitters. ALL ABOVE TRANSFORMERS HAVE MAINS INPUT. ARE BRAND NEW AND FULLY GUARANTEED. Trade enquiries welcome.

GENUINE AFV TANK HEADSETS AND MIKE £3.50 per pair, p.p. £1.50. 2 pairs £7.50 post free. All headphones fitted with ex-ministry plug. Standard jack plugs available 25p each. 2 for 40p. Headphone extension sockets available at 25p each. 2 for 40p. Impedance 600 ohms. All headphones in good condition.
SCOOP PURCHASE. PYE POCKET PHONE RECEIVERS. Type PF1 normal freq. 450mHz. Supplied in used condition less battery. £4.50 each. Carr. £1. 2 for £9 post free. 4 for £16 post free.

PYE POCKET PHONE PF1 DATA AND INSTRUCTIONS. Contains circuits, layouts, operating and modification details for amateur use etc. £1.50 post free.

CAPACITOR BARGAIN PACKS. Bulk purchase enables us to offer a pack containing 500 new standard polyester capacitors. 0.0 (MFD-0.22MFD). 100 to 600v working. PRICE £8 per 500 lot. PP. £1. 1000 lot £16.50 post free. Trade enquiries invited.

RIDICULOUS RESISTOR SALE. Brand new 1 watt carbon film resistors, 5% tolerance. High quality resistors made to exacting specifications. E12 range. 1R0 to 10M. In lots of 1000 (25 per value). ONLY £8. per 1000. Post free. Lots of 5000 for £35.

STEEL SOUND TO LIGHT UNIT CASE. Drilled for controls etc. Smart appearance with blue hammer finish. 178mm x 158mm x 62mm. Useful for housing many other projects. Price £2.25. P&P 75p.

MINIATURE MAINS TRANSFORMER. Mains input. Output 6-0-6V. 250MA. 90p. P&P 35p. 2 for £2. Post free. 10 for £8.75. Post free.

FERITE RODS. 4" long. 5/16ths diameter. Packs of 10 £1.35. P.P. 50p. 10 packs (100 rods) £10. Carr. £2.50.

BULK BARGAIN TRANSISTOR RADIO/CASSETTE SERVICE PACK. Contains at least £25 worth of new transistor radio and cassette spares. Loads of those hard to obtain components and spares including hardware. Ideal for the radio service engineer. ONLY £6.50. P.P. £1.50. Double Pack £12.75 carr. free.

GENUINE EX-GOVT COLLAPSIBLE AERIALS. A fully adjustable highly efficient whip aerial in 5 sections. Length 1 1/2 metres. Closed 300 mm. Copper plated sections. As used on Ex Govt Manpacks. Brand new in makers boxes. £2.50 each, p.p. 75p. 2 for £5 post free. Aerial bases for same, £2.75, P&P £1.25.

HAVE YOU SEEN THE GREEN CAT? 1000's of new components, radio, electronic, audio at unbelievably low prices. Send 60p for catalogue.

GOVT SURPLUS LIST 60p.
VALVE LIST. Valves from 1925 to 1980. Many obsolete types. Modern TV, radio and transmitting valves. Send 60p. Or £1 (Refundable on purchase) for all three.

WE SELL VALVES OF ALL TYPES. Please send SAE for your requirements.
 Try a **JUMBO PACK.** Contains transistors, resistors, caps, pots, switches, radio and electronic devices. **OVER £50 WORTH FOR £11.00.** Carriage and packing £2.50.

Please add 15% VAT to all orders including carriage and PP.

Myers Electronic Devices

Dept. PW7, 12/14 Harper Street, Leeds LS2 7EA. Tel: (0532) 452045. Retail premises at above address (opposite Corals) 9 to 5 Mon to Sat. Sunday 10 to 1 by appointment. **GOVT. SURPLUS ITEMS ALWAYS IN STOCK.**

TIS 76 CHURCH ST., LARKHALL, LANARKS ML9 1HE
UNIQUE COLLECTION OF SERVICE SHEETS & MANUALS

Manuals from early '30s to latest issues. Copies of out-of-print manuals obtainable nowhere else. We even produce our own service sheets and manuals as well as stocking all other published service sheets. £5,000 video manuals alone in stock. G8, A823, early Autovox or Tyne @ **£7.50 each** (CTVs).

Complete full size sets any published s/sheet £2 + I.s.a.e.
except CTVs and Music Centres from £3 + I.s.a.e.

Sole stockists of all TV and VCR Repair Manuals. Complete inexpensive diagram collections TVs, VCRs, etc. Repair data and circuits almost any named TV or VCR **£8.50.**

Large s.a.e. brings full details our unique technical publications, plus any requested quotations, plus free 50p magazine.

FOR FAST QUOTES - PHONE 0698 883334

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc., £1.25 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

30,000 SERVICE SHEETS IN STOCK
COLOUR MANUALS ALSO AVAILABLE
 TV Monos, Radios, £3.00. Tuners £3.00. Tape Recorders, Record Players £3.00. Transistors £3.00. Car Radio £3.00 + SAE. Stereograms & Music Centres £3.00. Radiograms £3.00. Also Colour Available. State if circuit will do if sheets are not in stock. Circuits £3.00 colour. All TV Sheets are full length 24 x 12 not in Bits & Pieces. All other Data full length. All sheets £3.00 except colour. SAE please. Old Valve Radios £3.00 + SAE 9 x 3.
C. CARANNA,
 71 Beaufort Park, London NW11 6BX. (Mail Order).

Miscellaneous

MORSE CODE PREPARATION

RECEIVING

Cassette A: 1-12 wpm for amateur radio examination.
 Cassette B: 12-25 wpm for professional examination preparation. Each cassette is type C90.
 Price each cassette (including booklets) £4.75.

SENDING

Morse key with separate battery (PP3) - driven solid-state oscillator and sound transducer produces clear tone for sending practice; optional light (solid state) signal included. Price of key with electronic unit £9.75.

Price includes postage etc. Europe only.

MH ELECTRONICS (Dept PW)
 12 Longshore Way, Milton,
 Portsmouth PO4 8LS.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from PVC. Faced steel. Vast range. Competitive prices start at a low £1.50. Punching facilities at very competitive prices. Suppliers only to Industry and the Trade. BAZELLI, (Dept. No. 25), St. Wilfrid's Foundry Lane, Halton, Lancaster LA2 6LT.

AVIATION FREQUENCY LISTS (Europe) 384 pages £5.75 per copy. AOS (PW), West London Building, White Waltham Aerodrome, Maidenhead. SL6 3MJ. Tel. (0628 82) 5362.

THE SCIENTIFIC WIRE COMPANY

811 Forest Road, London E17. Telephone 01-531 1568

ENAMELLED COPPER WIRE

SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	9.09	5.20	2.93	1.97
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.97	2.41	1.39	0.94
----------	------	------	------	------

Fluxcore Solder 5.90 3.25 1.82 0.94

Prices include P&P VAT. Orders under £2 add 20p.

SAE for list of copper and resistance wire.

Dealer enquiries welcome.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

WAVEGUIDE, FLANGES & DISHES. All standard sizes & alloys (new material only) from stock. Special sizes to order. Call EARTH STATIONS, 01-228 7876. 22 Howie Street, London SW11 4AR.

QSL CARDS, printed to your own design on white or coloured gloss card. Send for samples. THE NUTLEY PRESS, 21 Holmehorpe Avenue, Redhill, Surrey RH1 2NB.

RTTY PROGRAM FOR BBC. Split screen, type ahead, cw ident, real time clock. Cassette and instructions £7.50. P. J. HARRIS (G3WHO), 10 Appleby Close, Great Alnc, Alcester, Warwickshire. Tel. (078981) 377.

RARE DX

UNDER QRM? DIG IT OUT with a Tunable Audio Notch Filter, between your receiver and speaker, BOOST your DX/QRM ratio, 40dB notch, hear WEAK DX, **£16.40.**

LOSING DX? Antenna Fault? Check FAST with an Antenna Noise Bridge, MEASURE resonance 1-160MHz and radiation resistance 2-1000 ohms. GET answers - more DX, **£19.60.**

V.L.F.? EXPLORE 10-150KHz, Receiver £21.20.
Each fun-to-build kit includes all parts, printed circuit, case, instructions, by-return postage etc, money back assurance so GET yours NOW.

CAMBRIDGE KITS

45 (PX) Old School Lane, Milton, Cambridge.

ALARMS

FREE CATALOGUE!

OUR GREAT NEW ILLUSTRATED CATALOGUE IS PACKED WITH INFORMATION ON SUPERB QUALITY, PROFESSIONAL BURGLAR ALARM EQUIPMENT

AT UNBEATABLE PRICES!

SEND SAE OR PHONE NOW FOR YOUR COPY

AD. ELECTRONICS
 DEPT. PW
 217 WARBECK MOOR
 AINTREE LIVERPOOL
 L9 0HU/051-523 8440

THIEFCHECK BURGLAR ALARM D-I-Y SYSTEM MAIN DISTRIBUTOR

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address in written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Wireless for
 insertions I enclose Cheque/P.O. for £.....
 (Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Wireless).

NAME

ADDRESS

Send to: Classified Advertisement Dept.,
PRACTICAL WIRELESS
 Classified Advertisement Dept., Rm 2612
 King's Reach Tower, Stamford Street,
 London SE1 9LS Telephone 01-261 5785
 Rate
34p per word, minimum 12 words.
 Box No. **60p** extra.

Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed".

CITY AND GUILDS CERTIFICATES

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Basic Electronic Engineering (C&G/ICS)
Radio Amateurs

CERTIFICATE COURSES

TV & Audio Servicing
TV, Radio and Audio Engineering
Radio & Amplifier Construction
Electronic Engineering*
Computer Electronics*
Industrial Electronics*
Radio Frequency Electronics*
Electrical Engineering*
Electrical Contracting & Installation

*Qualify for IET Associate Membership



Approved by CACC

ICS

Div National Education Corporation



Member of ABCC

POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest _____

Name _____

Address _____

ICS

Dept M276
ICS School of Electronics
160 Stewarts Road
London SW8 4UJ



01 622 9911
(All Hours)

NEOSID LIMITED

FERRITE COMPONENTS : COIL FORMERS :
BOBBINS : INDUCTOR PARTS

Coil Component Kits Include

PW10 - 'Nimbus'	£6.65
PW20 - 'General'	£6.10
PW30 - 'Helford'	£3.95
PW40 - 'Stour'	£10.90
PW50 - RF Noise Bridge	£1.00
PW60 - Time Out Alarm	£1.00

"PW SEVERN"

Coil assys., Toroids,
Beads and Winding
Wire.

PW 70 £4.00

PLUS REF 650 Trimming Tool Kit £1.25
MP 110 Magnet (Various) Kit £4.50

All above prices include P & P. Terms - C.W.O.

Catalogue of standard parts available - S.A.E. please


NEOSID SMALL ORDERS 1982

P.O. Box 86, Welwyn Garden City, Herts. AL7 1AS.

Please allow 10 days for delivery

PLEASE MENTION PRACTICAL WIRELESS WHEN REPLYING TO ADVERTISEMENTS

B.S.R. Single Player Record Decks. 240 volt A/C 2 speed. (No cartridge) £14.75
B.S.R. Automatic Record Decks. 240 volt A/C 3 speed. (No cartridge) £16.75
10 Watt Stereo Amplifier Chassis with vol on/off, balance, treble & bass controls, knobs & fascia. (Req. 15 volt supply) £7
Stereo Cassette Tape Decks with built in pre amps, level indicators, auto stop & mics. 11" x 6". Black with silver trim. Req. 6 & 12V supply £17.50
FM4 Tuners. A complete AM/FM tuner chassis covering L/W, M/W & VHF stereo. (Brand new & boxed) £9.95
Power Supply Kit for all the units above. (15V at 1 amp; 12V at .5A; 6V at 250 M/A) £6

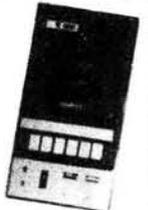

All prices inc. VAT, Post & Packing.

Orders by return of post.

Cheque, P/O, or Access

ISHERWOODS ELECTRONICS

Hozier St., Blackburn, Lancs. England.

Tel. (0254) 57616



SPECIALS

JUST ARRIVED!

CONVERT YOUR JAYBEAM Q6 WITH TWO ELE. ADD-ON (Not Mail Order) £15.00

HB9-CV ANTENNA (2 METRE 2 EL. BEAM) £8.50

AS ABOVE 70cms (BOTH INC. MOUNTING CLAMP) £8.50

EDDYSTONE RE1 MARINE GEN. COV. RECEIVER - FEW ONLY £450
10 MERTON PARK PARADE, KINGSTON ROAD, LONDON, SW19.

ZX81 MORSE TAPE (& SATELLITE TRACKING PROGRAMME) £4.75

MORSE TUTOR TAPE (INC. SIMULATED TESTS) £6.50


FT290R ANTENNA EXTENSION CONVERTS TELESCOPIC AERIAL TO 3/8 WHIP £10.50

30 FOOT TELESCOPIC MAST (Not Mail Order) £28.50



Tel. 01-543 5150
01-543 4212



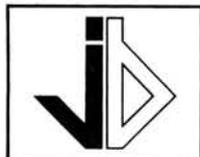

Jaybeam



BRITISH 'QUALITY' AMATEUR ANTENNAS

MECHANICAL QUALITY



VHF
(25 models)

TB3

UHF
(15 models)



ELECTRICAL PERFORMANCE

BRITISH MANUFACTURE

Manufactured in Northampton by experts using modern manufacturing techniques to extremely high mechanical and electrical standards. Made to last — many old timers still using Jaybeam antennae installed in the early 1950's and 60's.

DESIGN LEADERSHIP


Designed by professionals using computer aided technology and over 30 years experience in professional telecommunication and amateur antenna research and development.

STANDARDS AND MEASUREMENTS

The recommendations of the International Electrotechnical Commission (on IEC 128 and 138A) and the IEEE (on revision of 48 IRE252 1965), have been taken into account where technical details are quoted. Both these professional bodies stipulate stringent conditions on the measurement of electrical and mechanical characteristics. All gain figures quoted in our new amateur catalogue are in dBd — gain over 1/2 dipole and are measured at our purpose built test range in Northampton.

WARNING

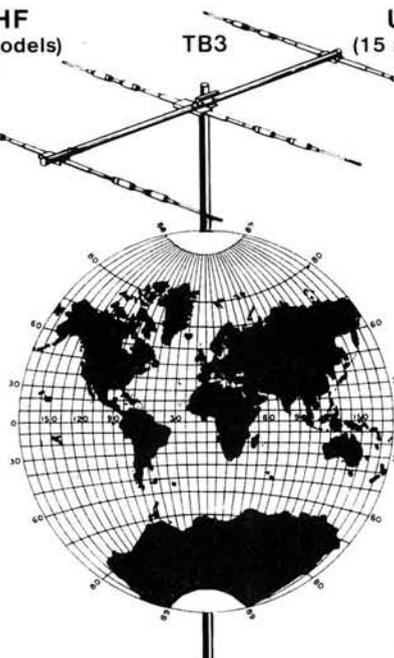Beware of exaggerated gain claims used as a sales aid rather than a measure of the performance of the aerial. Play safe by backing the professionals with over 30 years experience and select a quality Jaybeam antenna with accurate specification.



GUARANTEE AND BACK UP

All Jaybeam aeriels and components are fully guaranteed against faulty materials and workmanship. A full back up of spare parts are readily available at low cost in the event of antennae being accidently damaged.

DISTRIBUTION

Jaybeam antennae are available from a network of distributors throughout the United Kingdom and many overseas countries. A list of stockists is supplied with our amateur catalogue.

NEW PRODUCTS

New TB1 Broad Band Rotary Dipole for 10, 15 and 20 metres available end of July.
New 4Y/6M element Yagi for 50 MHz available end July.
New TB2 Broad Band 2 element Yagi for 10, 15 and 20 metres available August.
New HF Verticals to be announced soon.

For latest catalogue contact your local Jaybeam distributor — or — write enclosing s.a.e. 16p stamp to:



Jaybeam Limited

Kettering Road North,
Northampton NN3 1EZ

INDEX TO ADVERTISERS

A.D. Electronics	92	Garex Electronics	62	Northern Communications	14
A.H. Supplies	90	G2DYM Aerials	93	P.M. Components	88
Amateur Electronics U.K.	8, 9	Gemini Communications	76	Photo Acoustics	14
Amateur Radio Exchange	10, 11	Greatch	90	P.R. Golledge	91
Ambit International	87	Greens Telecom	88	Radio Society of Great Britain	82
Amcomm Services	15	G.T. Technical Services	92	Rapid Results College	96
Ant Products	36	H.A.C. Shortwave Products	93	R.S.T. Valve	10
A.R.R.A. Exhibition	16	I.C.S. Intertext	94	Radio Component Specialists	93
Armon Electronics	76	I.L.P. Electronics	12, 13	Radio Shack Ltd.	25
B. Bamber		Institute of Electronic Learning	93	Radio & T.V. Servicing	36
Bi-Pak	81	Isherwood Electronics	94	Scarab Systems	14
Birkett, J.	76	Jaybeam	95	Scientific Wire Co.	92
Blackstar Ltd.	89	LB Electronics	96	Selectronic	90
B.N.O.S. Electronics	69	Lee Electronics	Cover 3	S.E.M.	70
Bowes, C.	70	Leeds Amateur Radio	89	South Midlands Communications	4, 5
Bredhurst	Cover 2	Lexton, H.	65	Stephens-James Ltd.	36
British National Radio & Electronics School	26, 76	Lowe Electronics	2, 3	Spectrum Communications	90
Cambridge Kits	92	Maplin Electronics	Cover 4	Tandy	85
C-Tec Security	86	Marlborough Electronics	91	Thanet Electronics	6, 7, 89
C.O. Centre	94	Metal Fayre	88	Van Dermolen	87
C.R. Supply Co.	91	M.H. Electronics	92	Ward, Reg	90
Caranna, C.	92	Microwave Modules	26	Waters & Stanton	35
Colomor Electronics	26	Mutek	70	Western Electronics	96, 75
CVS Enterprises	88	Myers Electronics	91	Wood & Douglas	86
Datong Electronics	82	Neosid	94		
Dewsbury Electronics	82	Northampton Communications	86		
Electronics Mail Order	93				
Electrovalue	86				
Enfield Emporium	87				

B. BAMBER ELECTRONICS

Rank Pullin Airport Weapon Detector Type 3 Walkthrough Cabinet. Complete and good working order. **£150 plus VAT.**
 Marconi HF Spectrum Analyser Type OA1094A/S complete with frequency converter type TM644B and mounted on trolley, 0-30 MHz. **£90 plus VAT.**
 Systron Donner Spectrum Analyser Model 805 200 Hz-1.6 MHz. POA. Hewlett Packard SHF Signal Generator Type 620B 1-11 GHz, FM, CW, & Square Wave. **£120 plus VAT.**
 Marconi AM Signal Generator Type TF 801D/8S 10-485 MHz. **£95 plus VAT.**
 Avo Valve Tester Mark IV complete with instruction book. **£45 plus VAT.**
 Tektronix Oscilloscope Type 545A Mainframes. **£65 plus VAT.**
 Tektronix Oscilloscope Type RM45A Rack Mount Mainframes. **£50 plus VAT.**
 Tektronix Oscilloscope Type 551 Mainframes with Power Unit. **£75 plus VAT.**
 Tektronix Oscilloscope Type 555 Mainframes with Power Unit. **£85 plus VAT.**
 Tektronix Sampling Oscilloscope Type 661 fitted with 4S1 plug-in. **£120 plus VAT.**
 Tektronix Plug-In Units Type B, G, H, K, L. **£25 each plus VAT.**
 Avo Transistor Tester Type 2 with battery and mains power units. **£30 plus VAT.**
 Solartron Oscilloscope Type CD 1642.
 Solartron Oscilloscope Type CD 1014.3.
 Tequipment Oscilloscope Type D 61.
 Tequipment Oscilloscope Type D 43 R.
 Tequipment Storage Oscilloscope Type DM 64.
 Solartron RC Oscillator Type CD 1004 10Hz-1MHz. **£25 plus VAT.**
 Advance Oscilloscope Type OS 2100 DC-30MHz. **£185 plus VAT.**
 Radiosonde RS 21 Meteorological Balloon Transmitter with water activated battery. **£5 each plus VAT.**
 Pye Industrial pH Monitor Model 539 complete with technical manual. **£30 plus VAT.**
 Marconi AM/FM Signal Generator Type TF 995A/5. **£250 plus VAT.**
 Meguro Signal Generator Type MG6-16KHz-50MHz. **£125 plus VAT.**
 Philips PAL Colour TV pattern generator type PM 5508. **£185 plus VAT.**

Marconi Signal Generator Type TF 1064B/5, AM/FM covering three ranges: 68-108, 118-185 and 450-470 MHz, good condition with service manual. **£125 plus VAT.**
 Marconi RF Power Meter Type TF 1020A/4M 300 W 75 ohm. **£65 plus VAT.**
 Pye Europa MF5M High Band Sets ideal for 2M. 5 watt output 6Ch. Complete with mike and cradle with circuit diagrams. **£60 each plus VAT.**
 Pye Reporter MF6 AM High Band Sets Single Ch. Complete but less speaker with circuit diagrams. **£60 plus VAT.**
 Pye Motofone MF5AM Mid Band 6 Ch. Good condition with circuit diagram. **£15 plus VAT.**
 Pye Westminster W15AMD Mid Band Single Ch. Complete but less speaker, mike and cradle. **£45 plus VAT.**
 Pye Westminster W15AMD Low and High Band Sets complete but less speaker, mike and cradle. **£50 plus VAT.**
 Pye Westminster W30AM Low Band Sets, Boot Mounted, 30W Output. Complete but less speaker, mike and leads. **£25 plus VAT.**
 Pye Olympic M201 AM High Band, complete but less mike, speaker and cradle. With circuit diagrams. **£40 plus VAT.**
 Pye Cambridge AM10B High Band, few only. **£15 plus VAT.**
 Pye Base Station F27 Low Band, **£40 plus VAT.**
 Pye Base Station F30 High Band, **£180 plus VAT.**
 Pye Base Station F401 High Band, **£220 plus VAT.**
 Pye Base Station F9U UHF. Remote. **£90 plus VAT.**
 Pye RTC Controller units for remotely controlling VHF and UHF fixed station radio telephone over land lines. **£10 plus VAT.**
 Pye PC1 Radiotelephone controller, good condition. **£50 plus VAT.**
 Pye Base Station Tx Type T406 100W Low Band FM. **£150 plus VAT.**
 Pye Base Station Tx Type T100 100W FM 'G' Band 38.6 MHz, ideal for 6M. New condition. **£100 plus VAT.**
 Pye Pocketfone Type PF5, UHF 'T' Band, complete with battery, good condition. **£45 plus VAT.**
 Pye Pocketfone PF5 Battery Charger Type BC16A. **£25 plus VAT.**
 Pye Pocketfone PF1 UHF Receiver, 440-470 MHz, single channel, int. speaker and aerial. Supplied complete with rechargeable battery and service manual. **£6 plus £1 p.p. plus VAT.**

PLEASE NOTE all sets are sold less crystals unless otherwise stated. Carriage on RT equipment-Mobiles £2 each. Base stations £15 each. Red Star available at cost.

SEMICONDUCTORS & VALVES p.p. 50p per order. PLEASE ADD VAT. 1N4148 10 for 25p, 741 4 for £1. 555 4 for £1. 280-P10 £1.85, 280-CTC £1.85, BC108 4 for 50p, BC109 4 for 50p, BC113 4 for 50p, BC148 4 for 50p, BC149 4 for 50p.
 QOV03 - 10 ex-equip. **£1.20**, QOV03 - 10 new **£2.50**, QOV03 - 20a ex-equip. **£5**, QOV06 - 40a **£15.00**, QOV06 - 40a ex-equip. **£10**.
VIDCON SCAN COILS 1" Transistor type but no details, complete with vidcon base. **£3.50 each plus 50p p.p. plus VAT.**
 Mains isolating transformer, 500VA 240V input, 240V C.T. output, housed in metal box. **£15 each plus £6 p.p. plus VAT.**
 Mains isolating transformer, 240V tapped input, 240V input, 240V 3 amp, plus 12V 0.5 amp output. **£20 each plus £6 p.p. plus VAT.**

Ni-Cad Batteris for Pye PF1 r, used but good condition. **£2 each**, PF1 bx batteries **£3 each plus VAT.**
 Garrard Car Cassette Player Mechanisms 12V motor, stereo head, brand new **£2.50 each plus 50p p.p. plus VAT.**
 Cigar Lighter Plug with lead. **£1 each plus 30p p.p. plus VAT.**
 IC test clips, 28 way and 40 way, gold plated **£2 each plus 30p p.p. plus VAT.**
 60 amp alternator and generator noise filters for use in vehicles. **£1 each plus 50p p.p. plus VAT.**
 Computer grade electrolytic capacitors, scw terminals, 25000 mfd., 33 volt, brand new **£1 each plus 50p p.p. plus VAT.**
 Mains Transformers 220V Pri. 36v @ 1.5 amp. Sec. **£1 each plus 50p p.p. plus VAT.**
 BASF chromidioxid video cassette tape for use with Philips N1500/1700 VCR. LVC30+5, 36 min long play. **£5 each plus 50p p.p. plus VAT.**
 Mullard vari-cap tuner Type EL22003, UHF only, removed from brand new TV sets. **£3.50 plus 50p p.p. plus VAT.**
 2N3055 Transistors Brand new 4 for **£1 plus 20p p.p. plus VAT.**
 Beryllium block mounts for CCS1 valves, brand new and boxed. **£10 each plus 50p p.p. plus VAT.**

Good secondhand equipment always wanted for cash

Goods in stock delivery by return

All prices quoted exclude p/p & VAT unless otherwise stated



5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE
PHONE: ELY (0353) 860185



Your Radio Amateurs Exam - our guarantee of success

Pass first time — or up to 4 years' continued tuition at our expense.

RRC's complete tuition service

- Self-contained courses, regularly updated for The City and Guilds Radio Amateurs Exam ● Fully inclusive fees
- No costly, time consuming text books to buy
- Everything you need in booklet lecture form
- Regular tests ensure you are fully prepared ● Enrol at any time ● Timetable to suit you ● Up to 4 years' continued tuition at no extra cost if you don't pass first time.

FREE PROSPECTUS & ADVISORY SERVICE



Write or 'phone today for full details, and a Free copy of our prospectus, without obligation.

THE RAPID RESULTS COLLEGE

Dept. JX10, Tuition House, London SW19 4DS
 Tel: 01-947 7272 (9am-5pm) — or use our 24-hour
 Recordacall Service: 01-946 1102 quoting Dept. JX10

YES Please send me my FREE prospectus right away.

NAME _____ (BLOCK CAPITALS PLEASE)

ADDRESS _____

Postcode _____

My interest is _____



THE RAPID RESULTS COLLEGE

BRAND NEW HAVARD H452

POWER SUPPLY AND NICKEL CHARGER

Output 13 volts at 0.7A (max. 1 amp) 7" x 3" x 3 1/2" approx. Fully cased and boxed.
ONLY £4.95 p/p £1.70

SPECIAL OFFERS

Mullard .2" red LEDs 0.06p, 7805 38p, 7805KC 5 volt 1.5A 75p, 78H05 5V 3A £3.50, 5K 3" multi-turn trim pots 14 for £2.50. P/P 30p.

EPSON FX80 PRINTERS

Brand new and boxed, frustrated export order limited quantity

£350 plus V.A.T. — Carriage £12

TEXTPOOL 24 DIL ZIF SKT (used) £3.95 — P/P 30p

9" Green Phosphor Monitors, brand new and cased, composite video input 18 Mhz band width — £80 plus V.A.T. Carriage £8.

LB ELECTRONICS

11 HERCIES ROAD, HILLINGDON, MIDDLESEX UB10 9LS
 PHONE 0895-55399

BARGAIN CORNER

2M/70CM FM MOBILE EQUIPMENT

Yaesu FT-720RU (70cm) **£209.95**

Yaesu FT-720RV (2m) **£189.00**

also: FP-80 AC PSU **£47.50**

All prices include carriage and VAT.


Goods supplied by return of post

Western Electronics (UK) Ltd

Fairfield Estate, Louth, Lincs. LN11 0JH Tel. Louth (0507) 604955 Telex 56121 WEST G
 Northern Ireland Agents: Tom & Norma Greer G14TGR-G14TBP Drumbo (023 126) 645

Published on approximately the 7th of each month by IPC Magazines Limited, Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon and Gotch (Asia) Ltd.; South Africa - Central News Agency Ltd. Subscriptions INLAND £13 and OVERSEAS £14 payable to IPC Magazines Ltd., "Practical Wireless" Subscription Department, Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. PRACTICAL WIRELESS is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

BROKE? LICENCED? INTERESTED IN FREE HP?

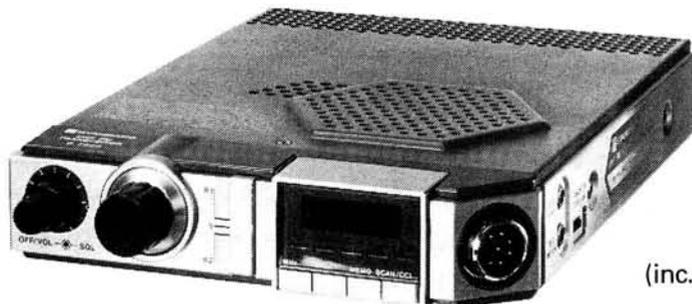

C8900 (2 mtr)

C7900 (70 cm)

**£219/
£239**

(inc. VAT)

These small slim transceivers are ideal for todays compact cars as very little room is required for fitting. The units can be fitted separately or stacked one above the other with the brackets provided. Both units feature tiltable led displays for easy reading when the sets are mounted below the drivers eye level. The sets provide a good 10 watts RF output with excellent performance specification.

s.a.e. for details

NORMAN G4THJ

**2 metre
MULTI-MODE**

The C58 has all the features possible on a portable rig, many of which are absent in mobiles. The optional accessories allow it to be used in the car with a power output of 25W.



C5800

£359

(inc. VAT)

- * 144-146MHz
- * 25W SSB/FM
- * 10 Memories
- * 3 Scan Modes
- * 25/5KHz Steps
- * RIT Control
- * S/Power Meter

**C58
£249** inc. VAT

INSI BARGAINS! BARGAINS! BARGAINS! BARGAINS! BARGAINS!
**PHONE US FOR BARGAINS IN EX-DEMO
 EQUIPMENT + DISCONTINUED
 LINES SUCH AS:-**
**FT101ZD
 FT901
 FT902**

INTEREST FREE H.P.

STANDARD C5800 Cash Price: £359	STANDARD C7900 Cash Price: £239	STANDARD C8900 Cash Price: £219	STANDARD C58 Cash Price: £249
H.P. over 6 months Deposit £72 Repayments ... £47.83 TOTAL £359	H.P. over 6 months Deposit £48 Repayments ... £31.83 TOTAL £239	H.P. over 6 months Deposit £45 Repayments ... £29.00 TOTAL £219	H.P. over 6 months Deposit £51 Repayments ... £33.00 TOTAL £249
H.P. over 12 months Deposit £180 Repayments ... £14.91 TOTAL £359	H.P. over 12 months Deposit £120 Repayments ... £9.91 TOTAL £239	H.P. over 12 months Deposit £111 Repayments ... £9.00 TOTAL £219	H.P. over 12 months Deposit £126 Repayments ... £10.25 TOTAL £249

400 EDGWARE ROAD,
LONDON W2
01-723 5521 Tlx 298765



Normally 24hr despatch
but please allow up to 7
days for delivery.



NEAREST TUBE:
EDGWARE ROAD
PADDINGTON

OPENING TIMES:
9.30am-5.30pm Mon, Tues, Wed, Fri.
9.30am-1pm Thurs.
10am-4.30pm Sat.

100% Satisfaction

MAKE ALL THE RIGHT CONNECTIONS

with a MAPLIN MODEM KIT

Exchange programs with friends, leave or read messages from the various Billboard services, talk to computer bureaux, or place orders and check stock levels on Maplin's Cashtel service. A Maplin Modem will bring a whole new world to your computer and vastly increase its potential.

Now you can exchange data with any other computer using a 300 baud European standard (CCITT) modem and because the Maplin Modem uses this standard, you could talk to any one of tens of thousands of existing users.

Some computers need an interface and we have kits for the ZX81, VIC20/Commodore 64, Dragon and shortly Spectrum and Atari, whilst the BBC needs only a short program which is listed in Projects Book 8.

A Maplin Modem will add a new dimension to your hobby.

Order As LW99H (Modem Kit) excluding case. Price £39.95.
YK62S (Modem Case). Price £9.95.

Full construction details in Projects Book 5.



Maplin's Fantastic Projects



Full details in our project books. Price 70p each.

In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier ● Universal Timer with 18 program times and 4 outputs ● Temperature Gauge ● Six Vero Projects.

In Book 2 (XA02C) Home Security System ● Train Controller for 14 trains on one circuit ● Stopwatch with multiple modes ● Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics ● Stereo 25W MOSFET Amplifier ● Doppler Radar Intruder Detector ● Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions ● Frequency Counter 10Hz to 600 MHz ● Ultrasonic Intruder Detector ● I/O Port for ZX81 ● Car Burglar Alarm ●

Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard ● 100W 240V AC Inverter ● Sounds Generator for ZX81 ● Central Heating Controller ● Panic Button for Home Security System ● Model Train Projects ● Timer for External Sounder.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 ● Module to Bridge two of our MOSFET amps to make a 350W Amp ● ZX81 Sound on your TV ● Scratch Filter ● Damp Meter ● Four Simple Projects.

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20 ● Digital Enlarger Timer/Controller ● DXers Audio Processor ● Sweep Oscillator ● CMOS Crystal Calibrator.

In Book 8* (XA08J) Modem (RS232) Interface for Dragon ● VIC Extensible Board ● Synchime ● Electronic Lock ● Minilab Power Supply ● Logic Probe ● Doorbell for the Deaf.

*Projects for Book 8 were in an advanced state at the time of writing, but contents may change prior to publication (due 13th August 1983).

NEW MAPLIN STORE OPENS IN MANCHESTER

Our new Manchester store offering the full range of Maplin's electronic components, computers and software will be opening 16th August, 1983. Part of the new store will be a self-service area where you can browse around and choose the parts you want. Counter service will be available as well. Upstairs you will find our computer demonstration area with displays of hundreds and hundreds of different software packages for Atari, BBC, Commodore 64, Dragon, Sord M5, Spectrum and VIC20.

You will find us at 8, Oxford Road opposite the BBC, between Piccadilly and the University complex. We're just a few steps from



Manchester's Oxford Road station and about five minutes walk from the city centre. There is excellent parking on meters in the adjacent sideroads and we're about five minutes drive straight in from junction 10 on the M63 at the start of the M56.

Call in and see us soon!

Great Projects From E&MM

Our new book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects.

Order As XH61R. Price £1.

★ 1983 CATALOGUE ★

Over 390 pages packed with data and pictures and all completely revised and including over 1000 new items. On sale in all branches

of W.H. Smith. Price £1.25. Or send £1.50 (including p&p) to our mail-order address.




LEARN ROBOTICS

- with Hero 1: the new robot who sees, hears, speaks and detects movement!

This remarkable microprocessor-controlled robot is the perfect robotics training system for industry, home and schools. Hero 1 can see, hear, speak, detect moving and stationary objects and determine their distance, pick up small objects, move in any direction and can learn from your instructions.

Hero 1 is a superbly documented Heathkit kit.

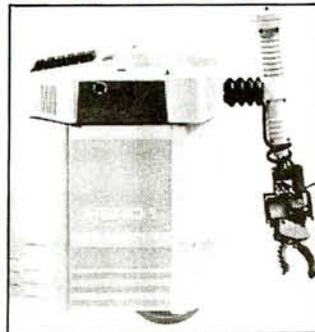Order As HK20W (Robot Kit) Price £1,599.95.



MAPLIN
ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend-on-Sea (0702) 552911.
Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748 0926.
284 London Road, Westcliff-on-Sea, Essex. Tel: (0702) 554000.
Lynton Square, Perry Barr, Birmingham. Tel: 021-356 7292.
8 Oxford Road, Manchester. Tel: 061-236 0281. (Opens 16th Aug. 1983)
All shops closed Mondays.

All prices include VAT & carriage. Please add 50p handling charge if total order value is under £5.