

MAKING AN INEXPENSIVE AERIAL

PRACTICAL TELEVISION

AND TELEVISION TIMES


1/4

EDITOR
F. J. CAMM

A NEWNES PUBLICATION

Vol. 3 No. 25

JUNE 1952

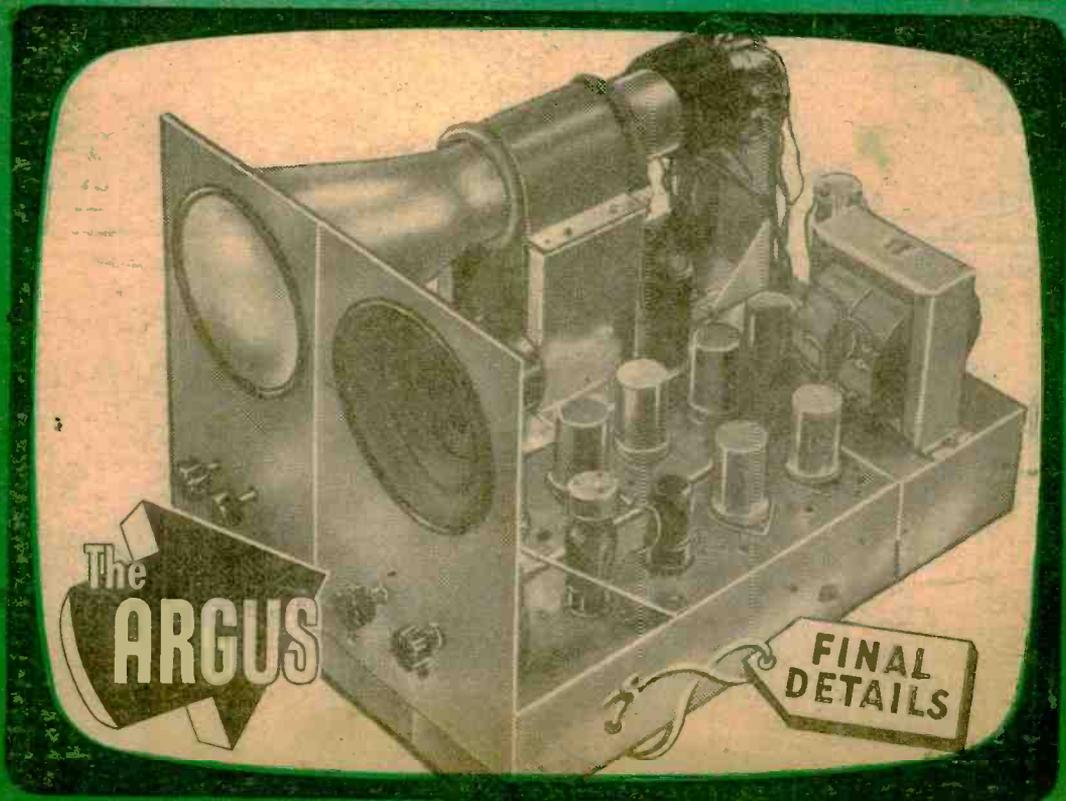


FEATURED IN THIS ISSUE

A Grid Dip Meter and Bar
Generator
Improving Your Video Stage
Sound Rejection

The Northern Radio Show
Line Flyback EHT
Underwater TV
Pioneers of Television

MAGNETIC T.V. TUBES

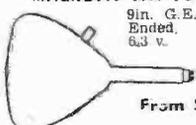

9in. G.E.C. Flat Ended Heater 6.3 v.

From 55/-

These tubes have had very little use and will probably give years of service.

TYPE 2. Have small ion burns otherwise in good condition. Price £315—each.

TYPE 3. Have larger ion burns but are useful as spare or when first testing out a circuit, or doing repairs, etc. Price £215—each.

NOTE: Callers to our Ruislip branch can see these tubes demonstrated but whether you see it or not we guarantee a "working" tube. If not calling please add 7/8 each tube for packing and postage.

"P.T." ARGUS


We have in stock everything necessary for this television. Send for our "ARGUS" List. Complete set of valves as specified, all tested before despatch. Price £51/-, plus 2/6 postage and insurance.

VCR97 (not cut-off type), guaranteed to give full picture. Price £22 6, plus 5/- carr. and insurance.

Post Orders come from our Ruislip depot. To avoid delay address to: E.P.E., Ltd. (Dept. 5), Windmill Hill, Ruislip, Middx. Includes extra 2/8 under £2. 1/9 under £1.


THE TELETRACER

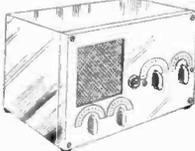This booklet Free. Send 3d. stamp to-day.



with the Teletracer signals can be followed through the T.V. to the tube or Loudspeaker. Similarly, powerful indications can be obtained in and around the sync. separator and time base sections. The Teletracer uses 5 valves and speaker and operates entirely from A.C. and D.C. mains. Send for a free copy of the instruction manual or better still save time by sending £6 10/-, plus 7/6 post and insurance for the complete outfit.

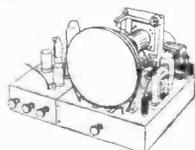
£5 DISCOUNT—TECHNICAL AID—14 DAYS' APPROVAL




You get all these if you buy your "Viewmaster" components through us. Send 7/6 to-day for new printed data and with it we will send a £5 cash voucher and technical aid coupons. You can have this data of 14 days' approval, in other words, if after studying it you doubt your ability to make the Teletracer simply return the data and we will refund your cash, less only 6d. for P. & P.

IDEAL HOLIDAY RECEIVER

The Elpreq "Wotsey" 5 valve A.C./D.C. Superhet has a built-in aerial and is of convenient size and weight to take with you on your holiday. Powerful reception on long, medium and short waves—handsome wooden cabinet—illuminated glass dial with station names—A.V.C. and usual refinements. Size 11in. x 8in. x 7in. with B.V.A. valves. 12 months guarantee. Limited quantity only. deposit and balance over 10 months.

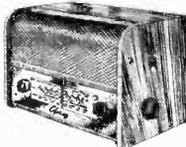


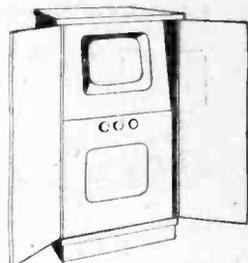£9 5s. 0d. or £2 2s. 6d. carriage and insurance 5/-.



NEW METHOD IMPROVES APPEARANCE

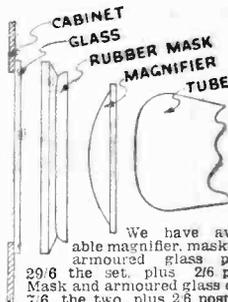This is a 6in. (VCR97) T.V. but by using the method shown in the diagram below the impression of a much larger tube is created.



We have available magnifier mask and armoured glass price 29/6 the set, plus 2/6 post. Mask and armoured glass only 7/6, the two, plus 2/6 post.

WINDMILL HILL, RUISLIP MANOR, MIDDX. and at 152-153, FLEET STREET, E.C.4.



PRECISION EQUIPMENT

RADIO MAIL

4, RALEIGH STREET, NOTTINGHAM

**INTRODUCING
A RESISTANCE-CAPACITY BRIDGE
AT 30/- ONLY**

Note the following points

LESS THAN ONE FIFTH THE COST OF A COMMERCIAL INSTRUMENT OF SIMILAR RANGE.

THREE CAPACITY RANGES. TESTING UP TO 50 MFD. THREE RESISTANCE RANGES. TESTING UP TO 5 MEGOHMS.

EASILY AND QUICKLY ASSEMBLED WITH THE SIMPLE INSTRUCTIONS AND CIRCUIT DETAILS SUPPLIED.

NO CALIBRATING NECESSARY AFTER ASSEMBLY.

ALL CALIBRATIONS. SWITCH RANGE MARKINGS. TERMINAL FUNCTIONS, ETC. READY LAID OUT ON A HANDSOME ESCUTCHEON COVERING THE ENTIRE OPERATING PANEL.

THIS IS THE FIRST TIME THAT AN INSTRUMENT OF THIS CALIBRE HAS BEEN AVAILABLE AT SUCH A LOW PRICE. ORDER NOW WHILE SUPPLIES LAST.

STAMP FOR LIST AND WITH ALL ENQUIRIES PLEASE

The solder for all
**HOME TELEVISION
CONSTRUCTOR SETS**

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60-40 High Tin Television and Radio Alloy. The size 1 Carton contains 37 feet of solder, costs 5/-.



Ersin Multicore Solder

In case of difficulty in obtaining supplies, please write to:
MULTICORE SOLDERS LTD., MULTICORE WORKS, MAYLANDS AVE., NEMEL HEMPSTEAD, HERTS • Boxmoor 3838 (3 lines.)

You're *SURE* to get it at
STERN'S
 ESTABLISHED 25 YEARS

CAN SUPPLY ALL RECOMMENDED COMPONENTS

FOR THE

"VIEWMASTER"

LONDON — SUTTON COLDFIELD — HOLME MOSS
 KIRK o' SHOTTS — WENVOE

Specified Components by :


T.C.C., W.B., Morganite, Bulgin, Westinghouse,
 Belling, Wearite, Mullard, Mazda, G.E.C.,
 Ferranti. Tallon and W.B. Table or Console
 Cabinets are also available.

Send 5/- for the "Viewmaster Envelope," which
 gives a complete description of this Televisor, includ-
 ing Assembly Layouts and Component Price List.



Our NEW STOCK LIST is now available (price 9d.)
 Brief details are given of the various KITS OF PARTS
 we are able to offer for the construction of many types
 of Radio Receivers, Battery Chargers, "Alldry" Battery
 Eliminators, and "hundreds" of Wireless Components.

STERN RADIO LIMITED

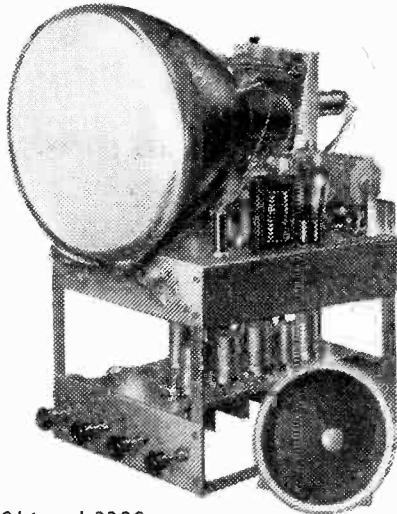109/115 FLEET STREET, E.C.4. Telephone: CENTRAL 5814 and 2280



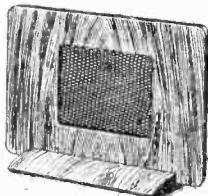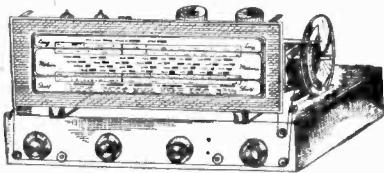SALVAGE RADIO-GRAM CHASSIS. From £7 17/6.
 5 Valve S'Het. 1952 Models. Made to sell at three times this
 price. Latest pin-type Midget Valves (BRA series). Can be
 built into your own cabinet in combination with one of our



EXTENSION SPEAKERS.
 New type in baffle stand, with
 metal frnt. 6in. P.M. 19/9.
 Post 1/-.

VALVES. Large stock in-
 cludes: EB9, EF69, EF91,
 EF92 at 8/9; SV61, EY51,
 FC180, 6AB8 at 11/9; UF41,
 UY41, 8/9; OZA, PEN200A,
 VPT210, VP133, at 6/9.

CONDENSERS.
 Tuning, two-gang,
 from 2/9.

1952 Catalogue available on request (21d. stamp).

TELEVISION COLOUR FILTERS. Make those outdoor
 telecasts look entrancing with one of these new colour
 filters. Adds to your television enjoyment. Brings blue
 sky tints, pink centre colour, and grass green foreground
 to your screen. For 10in. screens, 10/6. For 12in. screens,
 12/6. For 15in. screens, 19/6.

TELEVISION LENSES. Magnifies the picture 1½ times.
 Best quality manufacture. For 11in. and 9in. screens, 55/- ea.
 For 10in. and 12in. screens, 75/-. Tinted a pale blue for Day-
 light and Anti-glare viewing. 5/- extra. Post. and pack, 2/6.

C.W. or
 C.O.D. **DUKE'S** 621, Romford Road, London, E.12. Money
 (Grangewood 6677) Back Guarantee.

B.P.L. SUPER RANGER

1,000 ohms per volt—20,000 ohms per volt.

A precision built instrument of high accuracy equipped with a
 fine 5in. movement in spring loaded sapphires.

Fitted with mirror scale.

The range selector is of sturdy construction, consisting of solid
 silver contacts mounted on a ceramic base. By means of this
 switch all ranges are selected except the A.C. current ranges and
 the 5,000 volts range.

Provided with A.C. current ranges which, in conjunction with the
 other ranges, will cover all ranges to be expected.

LIST PRICE :

£19.19.0. 1,000 ohms per volt.

£22.15.0. 20,000 ohms per volt.

Subject to Trade Discount.

LONDON STOCKIST :

M.R. SUPPLIES LTD., 68,
 NEW OXFORD ST., W.C.1

- Leather carrying handle.
- Captive head terminal con-
 nectors for all ranges.
- Easy to read 2-colour dial.
- 5,000 volts range for A.C. and
 D.C.
- 1,000 ohms per volt and 20,000
 ohms per volt for D.C. and
 A.C.
- Rotary switch selects ranges
 clearly marked.
- 5in. scale meter with mirror
 scale. Movement fitted with
 spring loaded sapphires.
- Built-in 3 range current trans-
 former.



DELIVERY EX-STOCK

BRITISH PHYSICAL LABORATORIES

HOUSEBOAT WORKS, RADLETT, HERTS

Telephone: RADLETT 5674-5-6



CONDENSERS

The abbreviated ranges of two popular types given here are representative of the wide variety of T.C.C. Condensers available.



'Hi-K' 'PEARL' CERAMICS

Capacity pF.*	Wkg. Voltage		Dimensions		Type No.
	D.C.	A.C.	Length	Dia.	
1·0	500	250	3·5 mm. to 7 mm.	5 mm. to 7 mm.	SPG 1
10·0	500	250			SPG 1
33·0	500	250			SPG 1
150	500	250			SPG 1
330	500	250			SPG 1
470	500	250			SPG 1

Hi-K MULTIPLE TUBULAR CERAMICS


Capacity pF.*	Wkg. Voltage		Dimensions		Type No.
	D.C.	A.C.	Length	Dia.	
2 × 500	500	250	10 mm.	4·5 mm.	2CTH 310/W
2 × 1000	500	250	10 mm.	4·5 mm.	2CTH 310/W
2 × 1500	500	250	15 mm.	4·5 mm.	2CTH 315/W
2 × 2200	500	250	22 mm.	6 mm.	2CTH 422/W
3 × 500	500	250	15 mm.	4·5 mm.	3CTH 315/W
3 × 1000	500	250	15 mm.	4·5 mm.	3CTH 315/W
3 × 2200	500	250	22 mm.	6 mm.	3CTH 422/W

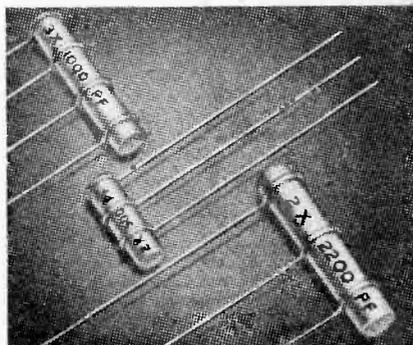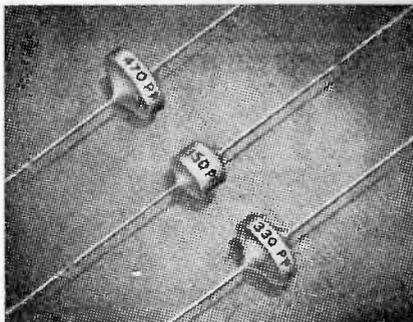* Guaranteed not less than stated values at 25°C.



THE TELEGRAPH CONDENSER CO. LTD.

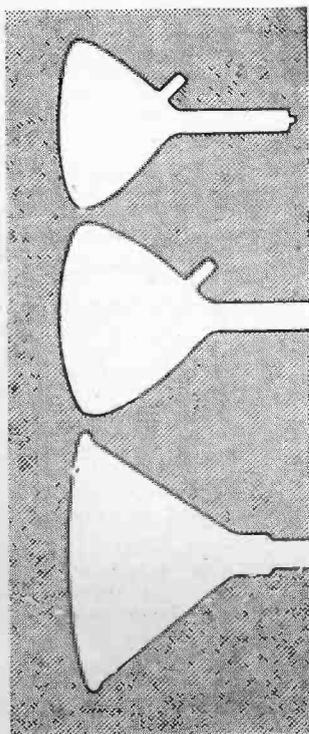Radio Division: North Acton, London, W.3. Tel: Acorn 0061



Your set deserves a Mullard Tube

If you are building a television receiver, leave nothing to chance; choose a Mullard Tube.

Mullard Television Tubes owe their high reputation for performance, reliability and LONG LIFE to the unrivalled facilities for research possessed by Mullard; to the complete control of manufacture from the production of raw materials to the completed product; and, in particular, to the ion-trap, which safeguards the screen from damage by heavy negative ions produced in the region of the cathode.

Tubes available for home construction include:—

- MW22-16 - 9 inch screen
- MW31-16 - 12 inch screen
- MW36-22 - 14 inch rectangular screen
- MW41-1 - 16 inch screen (metal cone)

Tube data and application notes on the above tubes and their associated range of World Series television valves are available on request to the Technical Publications Department at the address below

Mullard

Long Life T/V TUBES



MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2
MVM 192A

PRACTICAL TELEVISION

& "TELEVISION TIMES"

Editor : F. J. CAMM

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 3 No. 25

EVERY MONTH

JUNE, 1952

TelevIEWS

COLOUR TELEVISION

THE announcement by Sir Noel Ashbridge that we shall have colour television in this country in five years' time is encouraging. It is known that considerable progress has been made in this country and in America in the development of colour television. Colour television programmes have been radiated in America for a considerable period, although they have now ceased for no other reason than the rearmament programme. That same reason has prevented the more rapid development of colour television in Great Britain. It is agreed that we are far ahead of the Americans, and those who have visited America and compared their system with ours are convinced that our system is the better.

GERMAN RADIO AND TELEVISION EXHIBITION

AFTER a gap of two years the German Radio and Television Exhibition is to be held at Düsseldorf from August 22nd to August 31st this year. All factories located in the Federal German Republic and in West Berlin which produce wireless sets, television sets, radiogram attachments and phonograph records, as well as accessories, will be represented in full. They will offer a comprehensive exhibition of the new designs in all fields. There will be a large selection of television receivers on view. German developments have quickly made up the ground they lost in this field, for it was only in 1949 that a few German firms made some faltering attempts to carry on the experience which they had gained up to 1939. In 1950 the Nordwestdeutscher Rundfunk began initial test transmissions from a 100-watt transmitter in Hamburg. In the autumn of this year, however, there are to be four or five television transmitters working for three hours daily with a power of up to 10 kilowatts, while a relay system for the transmission of programmes between Hamburg and Munich via Cologne, Frankfurt and Stuttgart is under construction. There are over 40 different German makes of television receivers and samples from each will be located in the show windows of a whole television street. German television operates on 625 lines according to the C.C.I.R. standards and six channels are used between 174 Mc/s and 216 Mc/s.

VISUAL ASPECTS OF TELEVISION

MR. J. L. H. MOSS, at the Southern Optical Congress at Bournemouth, dealt with the extent to which television is affecting eyesight. The Association of Optical Practitioners had previously submitted a questionnaire to a representative sample of opticians in reception areas served by Alexandra Palace, Sutton Coldfield and Holme Moss. Although this is the first investigation of its kind in this country, the replies confirmed the results of similar scientific research in America. It is stated that almost without exception the opticians reported that they had received complaints from their patients of optical discomfort "in some way associated with televiewing. An analysis of the answers makes it seem likely that up to one half of the televiewing public may associate symptoms of eye-strain with the use of television." The conclusion is, however, reached that it would be a mistake to blame television for the symptoms. "A person may have a minor visual defect, but for normal occupations he gets along without noticing it. He may not be a great reader, or very enthusiastic about the cinema; then he acquires a television set and spends hours concentrating on a small screen." Most of the complaints came from viewers over 45 years of age who wanted to see a clearer image rather than seek relief from eye-strain. Other points made in the lecture were: it is inadvisable to look at television in a darkened room; greater comfort for the eyes will be obtained in a reasonably illuminated room with light either above or behind the viewer; the ideal viewing position is directly in front of the screen looking slightly down; the ideal viewing distance is for the viewer to be approximately eight times the diameter of the cathode-ray tube away from the screen—say, 6ft. to 10ft.; television sets in which there is a light-coloured surround to the screen aid visual comfort; the use of filters or black screens is helpful in removing reflections on the surface of the screen. It was reported that 65 per cent. of televiewers are probably using their sets under conditions which could be improved if more attention were paid to lighting, viewing distance, and the proper adjustment of the brightness control. Opticians agreed that once proper glasses had been prescribed subsequent complaints of eye trouble were negligible—F. J. C.

An Inexpensive Aerial

MAKING AN "H" ARRAY FOR LESS THAN £2

By "Erg"

THIS aerial can be readily constructed by the amateur with the aid of a few simple tools, and should cost not more than £2, including the chimney lashings, and possibly the mast. (The price charged for the metal work may vary from district to district.)

Although designed to be an inexpensive unit for use with the "Argus" television, it will function equally as well with other home-built or commercial receivers. Data is supplied for each TV channel.

Fig. 1 gives a general view of the aerial. Although the illustration shows a complete "H" array, those who live within 25 miles of the transmitter can dispense with the reflector portion, mast and chimney lashings, and mount the dipole on the side wall of the house.

The dipole proper consists of two lengths of duralumin tubing $\frac{3}{8}$ in. diameter. They are supported in the junction box in the manner to be described later. The reflector is a straight piece of duralumin of the same diameter; the cross-boom is made from a length of hardwood $\frac{3}{4}$ in. thick and 2 in. wide. The dimensions "A," "B" and "C" will depend upon the channel which the aerial is designed to receive, and will be found in the table.

The cross-boom is mounted upon the mast, and the length and material used for the latter will depend upon the supplies available. Wood can be used, and pitch pine, with minimum diameter of 2 in., will be found to be very suitable. The maximum length should not exceed

10 ft., but the mast can be made up to 16 ft. if the butt end is $2\frac{1}{2}$ in. in diameter.

Even this height can be extended, provided the chimney stack is sound, by coupling the lengths of pole together with iron ferrules, and staying in three directions, each stay at 120 deg. to the next. Pitch pine is a strong wood with a certain amount of flexibility, and is quite light in proportion to its strength.

As an alternative, dural. tubing can be used. In this case the mast will be heavier, and it is unwise to exceed 16 ft. unless the chimney stack is proportionately strong.

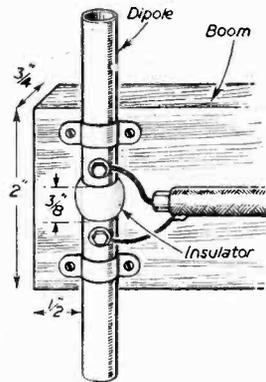


Fig. 2.—Details of fixing the dipole and taking off the lead-in or feeder.

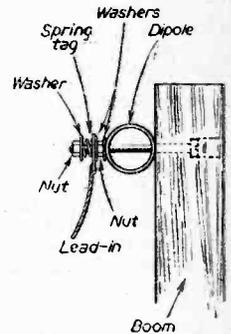


Fig. 3.—Further details of the method of fixing the connecting leads.

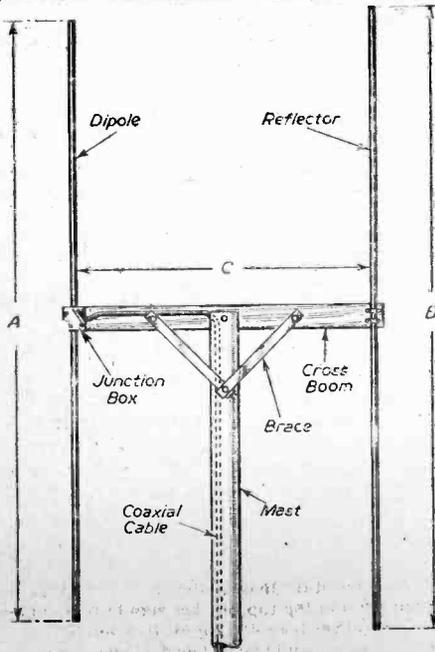


Fig. 1.—The completed aerial with the main parts named. Dimensions are given on page 6.

Its diameter should be 2 in., and it makes a more rigid mast than pitch pine.

The cross-boom is held in position by being bolted in its centre to the mast, and by the provision of two iron braces.

The only difference between the design for the various channels is in the lengths of the elements and the cross-boom. The spacing between the dipole and the reflector has been fixed at $\frac{1}{4}$ wavelength, though this can be reduced to $\frac{1}{8}$ wavelength for those who require greater gain and do not mind the risk of the picture fluttering in a high wind. The figures for the Alexandra Palace transmitter have given the cross-boom as a little under the $\frac{1}{4}$ wavelength so as to avoid the aerial appearing unwieldy.

Constructing the Dipole

Fig. 2 gives the detail for fixing the dipole elements. The insulator is an ordinary glass marble which fixes the gap at $\frac{3}{8}$ in. between the two opposite ends. Buckle-type clips (which can be easily made from sheet aluminium) are used to fasten the rods; their diameter should be slightly less than that of the rods, and they are screwed to the cross-boom. The leads from the coaxial cable should be kept as short as possible; tags should be soldered to their ends and they should be bolted to the ends of the dipole by bolts which go right through the cross-boom.

The bolt heads should be countersunk in the far side

of the boom and the holes filled in with plastic wood firmly tamped in. Spring washers should be used so that there is no possibility of the connections becoming loose. Fig. 3 shows the method used.

The connections to the dipole are totally enclosed in a junction box comprising two wooden side pieces with a top and bottom piece made of 1/4 in. paxolin, and provided with a paxolin lid. Fig. 4 shows the method of constructing the box.

When the box has been made and the work in Fig. 2

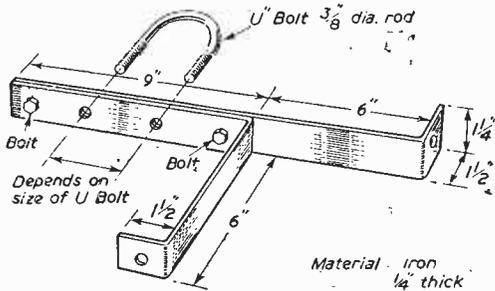


Fig. 7.—Chimney bracket details. Strip-iron is used here.

completed, then, before the lid is fastened on, the box is almost completely filled with molten beeswax (obtainable from a cobbler). The beeswax should completely cover the ends of the dipole and coaxial cable so that they are "sunk" under the wax. When the wax has solidified the lid can be screwed on, using Bostik on the edges to ensure a watertight seal.

Sealing compound should be liberally applied where the dural rods and coaxial cable enter the box. A generous application of Bostik can be used.

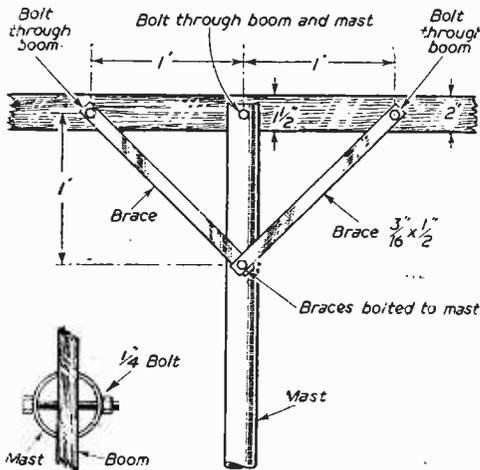


Fig. 6.—Details of the fixing of the cross-boom to the mast.

The open ends of the dipole should be plugged with wooden plugs, but before this is done the rods can be filled with dry, sharp sand, so as to mitigate the humming caused by the rods vibrating in the wind.

Construction of the Reflector

This is a very simple operation, the rod being merely cut to the length required and fastened to the boom

in the manner shown in Fig. 5. Bolts are fitted through the clips and through the boom in a manner similar to that employed with the dipole.

The rod can be filled with sand as explained for the dipole and the ends plugged with wooden plugs.

Fitting the Cross-boom

Fig. 6 shows the method of connecting the cross-boom to the mast, and the same method can be employed

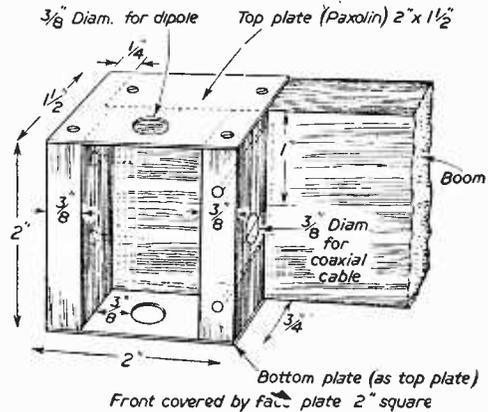


Fig. 4.—Details of the box used to enclose and weather-proof the connecting point

whether a wooden or metal mast is used. The braces should be 17 in. long and 3/8 in. thick. The inset figure shows how the boom should be bolted to the mast.

If the mast is made of metal tubing the coaxial cable can be brought down inside it as shown in Fig. 1. If a wooden mast is used the cable should be cleated neatly down the length of the pole.

Construction of the Chimney Bracket

Strip iron is used to construct the chimney bracket. Fig. 7 shows the construction clearly. Two strips of iron measuring 16 1/2 in. long by 1 1/2 in. wide by 1/4 in. thick are required. The size of the "U" bolt will depend

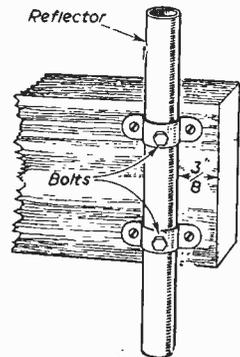


Fig. 5.—Details of the fixing of the reflector. Compare this with Fig. 2, and note that the rod is continuous.

upon the diameter of the mast at the base. Two brackets will be required and the top bracket should be mounted at least three courses from the top of the chimney stack. The second bracket should be fastened as low as possible.

Fig. 8 shows the method of fixing the bracket and the corner pieces; these latter are made of 16- or 14-gauge

sheet iron as shown in Fig. 8. Six of these pieces will be required.

The bracket is bonded to the chimney stack by 7/14 stranded iron wire.

An alternative method of tightening the wire is shown, for use if strainers are not obtainable.

Mounting a Dipole

In areas of high signal strength the "H" array will not be required and the dipole can be mounted by itself

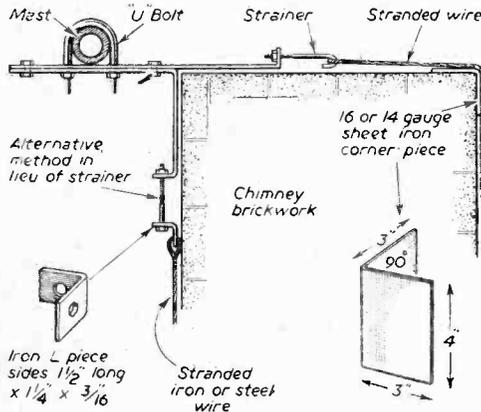


Fig. 8.—Corner bracket and mast-fixing details.

on the side of a wall. Fig. 9 shows how this can be done. The dipole is mounted on an 18in. length of hardwood as described previously and two shelf brackets used to fasten it to the wall. The coaxial cable can be cleated down the wall.

Adding a Director

Where the signal strength is low it may be beneficial to add a director. This should be a rod similar to the reflector but shorter, and it should be mounted in front of the dipole at the same distance from the dipole as is the reflector. The length of the director is given in the table.

Fitting the director will result in a slight mis-match if 75-ohm cable is used, but the mis-match will be small and will be outweighed by the greater gain.

Before fitting the aerial on the chimney it should be given three coats of paint. The whole array should be painted. Battleship grey is a good colour to use as it becomes very inconspicuous when seen against the sky-line.

The brackets should also be painted, and black can be used here. The main thing is to prevent rust.

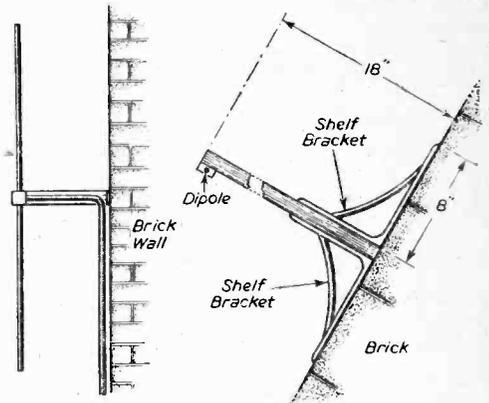


Fig. 9.—Wall-mounting details.

Channel	Dipole Lengths	Reflector	Cross Boom	Director	Station
1	5'-2 1/2"	10'-9"	4'-0"	10'-1"	Alex Palace
2	4'-6"	9'-3"	4'-6"	8'-9"	Holme Moss
3	4'-1 1/2"	8'-6"	4'-1 1/2"	8'-0"	Kirk O Shotts
4	3'-9"	7'-9"	3'-9"	7'-3"	Sutton Coldfield
5	3'-6"	7'-2 1/2"	3'-6"	6'-9"	Wenvoe

Book Review

JOHN BAIRD. By Sidney Moseley. Demy 8vo. 256 pages. 16s. net. Published by Odhams Press, Ltd.

THE author of this book was closely associated for many years with John Logie Baird, who did so much to draw public attention to the possibilities of television. His book sets out to answer some of the questions which have been raised concerning Baird, such as, Why did the BBC adopt another system and reject Baird's? Was Baird badly treated? Did he originate television as we know it to-day? What happened to the million pounds or more which the public subscribed to help Baird develop his invention? The author is certainly well qualified to answer these questions for he was deputy chairman of the Baird Co., and he conducted the secret negotiations with the Gaumont-British Group as well as with the BBC. The book covers Baird's beginning, his early struggles, the financial struggles, the first television programme and discloses many unrevealed secrets of the tragedy as well as the romance of Baird. It is common knowledge to-day that our present television system owes nothing to Baird. It is equally common knowledge that Baird owed much to Paul Nipkow, who as long ago as 1884 demonstrated the possibilities of scanning by means of a spirally

perforated disc. I do not know whether Baird ever acknowledged the source of his original inspiration.

It is beyond all doubt, however, that Baird continued the experiments of Nipkow and brought it to a higher pitch of efficiency. As marketed, however, the Baird receiver and the Baird 30-line low definition transmitting system were foredoomed to failure. The receivers were at best a laboratory experiment, and Baird made the fatal mistake of marketing his receivers long before they were ready for the public. Obviously, the Baird system was not the answer, and it was equally obvious that high definition television would replace it. When the Television Advisory Committee issued their report they recommended that the programmes should be radiated on the Baird and the E.M.I. systems alternately so that the public could judge for themselves. There could be no possible doubt as to the verdict, and I suspect that the suggestion was only made to give Baird one final opportunity of improving his system and making it worthy of public demonstration. That, of course, was scientifically impossible.

Baird undoubtedly drew public attention to the practicability of television and he spent the whole of his life in doing it. The fact that he was the apostle of a lost cause and the victim of a belief in a device which all scientific people knew could never be better than it was, does not detract from his work. It is doubtful whether we would have had television to-day had it not been for his belief in it.

This book is an interesting study of Baird's life and work and it should be read by every viewer.—F.J.C.

Improving Your Video Stage

OBTAINING HIGHER QUALITY PICTURES WITH THE MINIMUM OF MODIFICATION

By W. J. Delaney (G2FMY)

DETAILS have been given in various articles in these pages concerning the importance of the video stage, and it is obvious that the best results are not obtained from many receivers in this particular part of the circuit. It is possible to modify most home-constructed receivers so that a better picture may be obtained—in many cases without making any modification either to the tuning or to the earlier stages of the receiver. There are a few special valves, designed primarily for use in a video stage, the main characteristics of such a valve being a very high slope and a low impedance. One of the most popular valves for this stage, and one which is being used by many constructors, is the EF55, but there is an American valve which is almost equivalent—the 6AG7. Both of these valves are available ex-government, the reference for the former being CV173, and for the latter CV1882. To enable readers to appreciate these two valves we give below the main characteristics of them in tabular form.

	EF55	6AG7
Va	250 v.	300 v.
Ia	40 mA.	30 mA.
Vg1	-4.5 v.	-3 v.
Vg2	250 v.	150 v.
Ig2	5.5 mA.	7 mA.
S mA/v.	12	11
Rk.	100 Ω	81 Ω

The greater efficiency of these valves may be appreciated in many circuits merely by plugging them in in place of an existing stage. For instance, in a receiver employing the popular EF50 in the video stage, the EF55 may be plugged in as a direct replacement without any circuit changes and will give greater gain and a different quality to the picture, but obviously for maximum results certain changes should be made.

Load Resistor

It will be found that the two main features of the video stage are the values of the load resistor and the

distributed self-capacity. In general the lower both of these are, the better the picture quality, but unfortunately there are other factors which have to be taken into consideration. The majority of receivers rely for their picture quality upon cathode or anode compensation in the video stage, such ideas as using a low value cathode by-pass resistor and resonant chokes being very common, and giving to the stage a rising characteristic visible on the majority of receivers in the form of outlining or black-after-white. Although a very small measure of such outlining is not actually detrimental, and does sharpen up the image, it is not desirable for the quality enthusiast, and an attempt should be made to obtain high quality pictures without any "ringing," outlining or other artifice

For maximum detail a low value anode resistor is required, together with a valve having a low impedance such as one of these already mentioned, and it will be found that an EF55, for instance, may be used with a load as low as 1,000 ohms. It might be argued that this will result in loss of volume in view of the small voltage change across the resistor, but it should be remembered that the anode current is quite high and in an ideal state the valve may be operated without bias, relying upon the signal to bias the valve. However, before going into such details, let us consider what may be done to an existing receiver, where there is no excessive current available, but in which an EF50 or similar valve is employed with a medium value of anode load. First, the anode load should be changed for one of lower value, say, about 2k Ω , and the bias by-pass condenser (if one is fitted) removed. The anode resistor will, of course, have to be of the high-wattage type—one of the small green Welwyn ex-government items proving small and capable of standing considerable heat. If an EF55 is now plugged in, in place of the EF50, there should be an obvious improvement in the picture quality, although it may be found that the gain is too great. In this case the Contrast control should be reduced, and if there was much "noise" on the picture this will assist in removing the spots and blemishes and

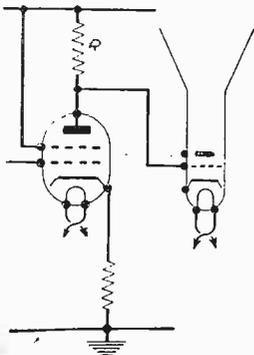


Fig. 1.—Resistance R should be as low as possible.

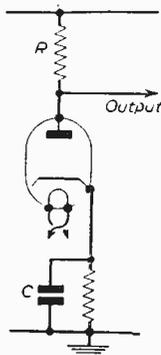


Fig. 2.—Condenser C should be as low as possible or omitted.

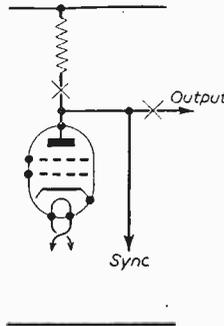


Fig. 3.—If any resonant chokes are used they should be inserted at the points marked "X."

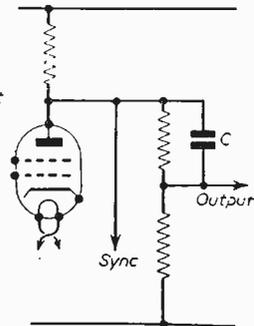


Fig. 4.—To reduce the voltage on grid or cathode of the valve, a voltage divider as shown here may be used.

giving a cleaner picture. It may be found, however, that the whites will be flattened as a result of the removal of the bias by-pass condenser and experiments should then be carried out with different values of bias resistor and by-pass condenser.

Cathode Drive

If the tube is grid modulated, as shown in Fig. 1, it will be preferable to change this to cathode modulation,

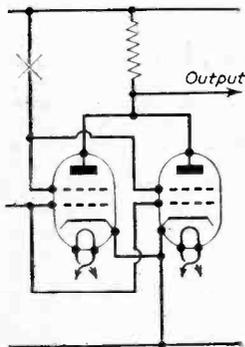


Fig. 5.—Two valves may be paralleled to give improved results, and if the tube is grid-modulated, bias components may be removed entirely.

a procedure which necessitates a reversal of the rectifying diode. The arrangement in Fig. 1 is not ideal as the grid of the picture tube is joined to the H.T. positive line (which is probably 250 volts or more) through the video stage anode resistor, and should the valve fail, there will be no drop across R, which means that the grid of the tube will go immediately 250 volts or so positive, a fact which will not be counteracted by the Brilliance control. In view of the expense of the tube, connecting the cathode to the anode is desirable as should the video stage fail it merely means that the cathode goes more positive, which is the same thing as making the grid more negative and the tube is protected from harm.

Resonant Chokes

In some circuits special chokes will be found in the anode circuit to improve the middle and H.F. response and these should be removed whilst experimenting with a new output valve. If it is subsequently found that slight adjustment of the trimmers in the vision receiver, or adjustment of the bias resistor and anode load do not effect sufficient gain at the higher frequencies, and more "white" is required the chokes may be added one at a time, but they should be inserted only at the points marked with an X in Fig. 3. They are best kept out of the sync circuits, and the effect may be tried of putting them in singly at each of the points marked, and then of using two, if necessary. Generally speaking, if the tuned circuits are properly adjusted it should be quite unnecessary to use these aids.

Tube Feed

One device which may be used without detriment is a tapped output as shown in Fig. 4, to feed the tube. The taking of the tube feed to cathode from the anode direct as shown in Fig. 2, means that the cathode may be at 250 volts or so compared with the heater under "no-signal" conditions. If there is a separate heater winding on the mains transformer this need cause no trouble as the heater winding may be used to feed the tube, and the heater left "in the air," that is, not joined to earth,

whilst a 100 k Ω resistor may be joined between cathode and heater to keep both heater and cathode at the same potential. It will be remembered that the tube makers recommend a heater-cathode potential not in excess of about 150 volts. The arrangement shown in Fig. 4, however, lowers the voltage at the output point, the two resistors between anode and earth being each of 47 k Ω for general use, but again experiments may be carried out with different values here. A condenser C is required across the first resistor and this will affect picture quality. Experiments may be carried out with values from .01 up to 8 μ F for this component, and in general it should be about 1 μ F although its presence does in some way detract from the desired direct coupling. In all the illustrations the suppressor grid has been omitted, as it is connected to earth or is internally joined to the cathode.

B7G Valves

For those who are using the special miniature B7G type of video stage, with special high-slope pentodes such, for instance, as the Z77 or EF42, the experiment may be tried of connecting another similar valve in parallel to simulate the effects previously described for an EF55, etc. The valves are wired directly in parallel—grid to grid, etc. A single anode load resistor of low value as already described may be fitted, and again the bias circuit may be experimented with in an endeavour to use the best value without by-passing. If the picture tube is grid modulated, bias can probably be removed entirely.

The changes described may not result in every receiver being improved and there are certain technical flaws in some of the suggestions mentioned. However, the old axiom holds good that the proof of the pudding is in the eating, and the changes should be made whilst watching either a good Lime Grove transmission or Test Card C, and the effects of the changes may be readily observed. With a properly run video stage, there should be a very wide range of tones visible in the picture and it should be markedly different from the type of picture one associates with the average type of receiver—very similar, in fact, to a comparison between a high-class professionally-made bromide photographic print and an amateur gaslight print. It is a quality which cannot adequately be described in words but which can readily be seen, and it is well worth the trouble of experimenting in this part of the circuit to obtain this improved performance.

G.E.C. Conversion Kits

THE General Electric Co., Ltd., announces its arrangements for the conversion of their existing television receivers for the reception of Kirk o' Shotts and Wenvoe transmissions.

Super Heterodyne Models

For receivers BT 3443, BT 3839 and BT 9144 M, conversion kits are available with full instructions to G.E.C. dealers at a net price of 7s. 6d. each. The modification consists of substituting aerial and oscillator coils, realignment, etc. The kit for the Scottish frequency is BT 42C and for the Western frequency BT 42E.

To convert models BT 1091B, BT 1093 and BT 4640 a conversion kit (also priced 7s. 6d. net to the Trade), BT 42D will be needed to change to the Scottish frequency and a conversion kit BT 42F to change to the Western. It should be noted that models BT 1091A, BT 7092, BT 7094 and BT 9144L cannot be converted for use on single-sideband transmissions.

The Northern Radio Show

A BRIEF REVIEW OF SOME OF THE EXHIBITS AT THIS YEAR'S SHOW AT MANCHESTER

ALTHOUGH obviously on a scale much smaller than the London exhibitions, this year's Northern show gave a good preview of some of the new season's lines in both radio and television. The keynote was viewing and considerable numbers of visitors saw television for the first time, whilst viewers at home had a show practically every night during the exhibition on their screens at home.

The principal manufacturers were showing at Manchester but a few of those whom we always see at Olympia or Earls Court were missing—mainly, we understand, due to the fact that Government contracts have resulted in a reduction of the home-market apparatus and as a result they found it undesirable to exhibit any of their products.

On the opening day the E.M.I. group announced the introduction of a new range of "Highlight" models, pictures of two of which are seen on page 10. On the H.M.V. stand were a table model (No. 1814) and a console model (No. 1816) in each of which special arrangements had been made to improve the quality of the picture by circuit and tube modifications. In these and the new Marconiphone models a 12in. aluminised tube is employed, and the circuits incorporate a five-channel selector so that each model may be set up in any part of the country without difficulty. This device is particularly valuable in fringe areas of more than one station, as it is a simple matter to tune the receiver to each station and ascertain which gives the most satisfactory results in that particular area. It is claimed that the reception is satisfactory in the most remote fringe areas and that good pictures are obtained with inputs as low as 25 microvolts. An inbuilt attenuator takes care of the excessive signal in areas of high signal strength. All that is necessary is to insert the aerial plug in a suitable socket on the receiver, and even the user may carry out this adjustment without difficulty.

Another feature incorporated in these models is a variable picture interference limiter, and this operates in addition to a beam-limiting device embodied in the special C.R. tube which is fitted, and further to add to the enjoyment of the viewer there is an "aeroplane flutter" limiter and special sound channel interference suppressors. Above all the price has been kept at a very low level, the table models costing only 69 gns. including Purchase Tax.

Big Screen

Among the many big-screen models, which included screen-projection models for clubs, schools, etc., there was also the direct-view 21in. metal-tube H.M.V. receiver which was seen at last year's radio show in London. The picture produced on this receiver is approximately 18in. by 14in. Other big-screen receivers exhibited by several firms incorporated the new 16in. metal picture tubes, and illustrated overleaf is the Peto-


Scott model TV168, in which the actual picture size is 14.2in. by 10.8in. This particular receiver is a 19-valve model and has full-length folding doors to protect the tube face.

Components

Space does not permit us to pick out each of the many items which were on show, but mention can be made of such items as the range of television download cables shown by the Telegraph Construction & Maintenance Co., which included both screened twin and coaxial, as well as solid and air-spaced low-loss cables and accessories suitable for operation at frequencies as high as 3,000 Mc/s. For the amateur transmitter there was a new type of 300-ohm feeder, with stable characteristics in varying weather conditions, known as the K.35B tubular twin cable.

The G.E.C., in addition to various television receivers of both table and console types, were showing their special flat-ended glass C.R. tube, in which the end is welded on to the glass "funnel" in a process very similar to that adopted with the metal type of tube.

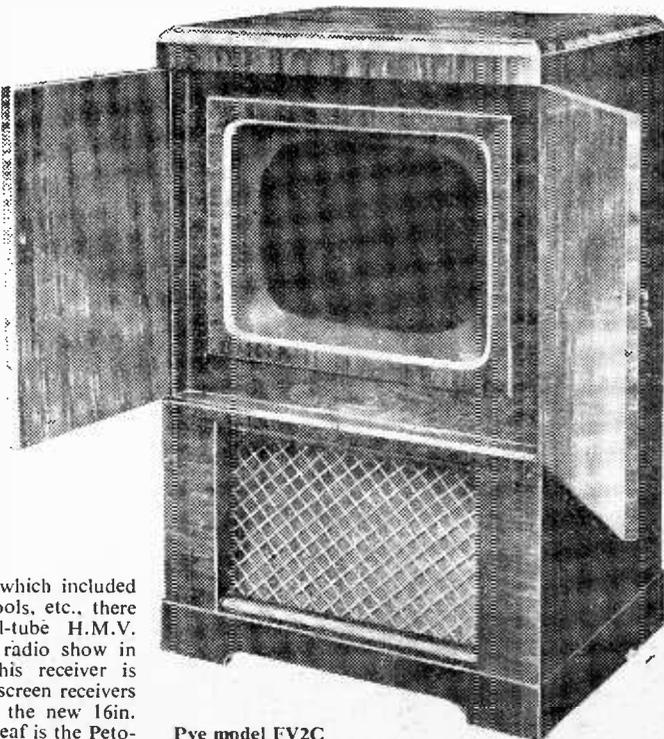The "talking television set" on the Ediswan stand attracted considerable attention and explained to many how the modern receiver functions. Mazda valves and C.R. tubes were also to be seen, together with many small accessories which find their place in a modern television receiver. The Clix valveholders, for instance,



Pye model FV2C

which we have used in some of our receivers, were well displayed and possess many attractive features.

Ekco appeared to be the only firm to be incorporating "spot wobble" in their receivers, although this appears to be used in only two of the Ekcovision receivers. As readers are aware, this aims at removing the "lininess" which a properly functioning receiver displays when viewed at close quarters, and there is considerable difference of opinion as to whether it is worth while. However, the makers have fitted a switch to the receivers so that it is easily switched off, either for comparison or when not needed.

Philips were featuring their "original" projection receiver, and were displaying receivers also of the direct-view type. The largest picture produced by their

and sound, often spoils a programme which would have better entertainment value if the sound could be maintained, as this makes up to some degree for the faded picture. The front of these large 16in. tubes is obviously




Marconiphone model VT59DA at 69 gns.

projection apparatus is 16in. by 12in., and, of course, it produces a flat "back illuminated" picture which may be viewed by a large number of people without difficulty.

Pye "Big Picture"


Among the new Pye models, Model FV2C, shown on page 9, utilises the new 16in. tube in which the picture has been made 13½ by 10¼in. (the average size being 13¼ by 10in.), and upon which the new more or less standard "black screen" has been fitted. This particular model is a 19-valve five-channel A.C./D.C. receiver and costs £93 3s. 2d., plus P.T. A feature found in this model, and which we cannot remember noting in any other television receiver, is the provision of A.V.C. on the sound section, so that this model should prove very useful in fringe areas where it is often found that fading, which affects both picture

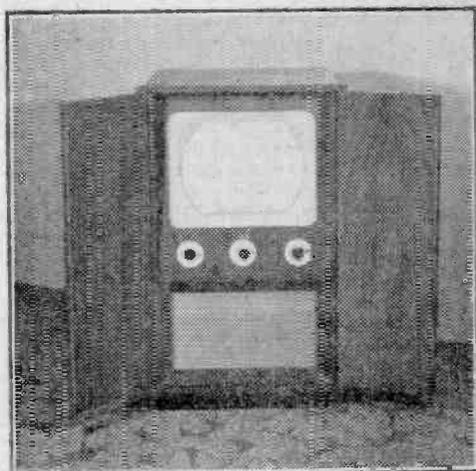

Peto-Scott model TV168.

more in need of protection than the smaller receivers, and folding doors are accordingly fitted to this model.

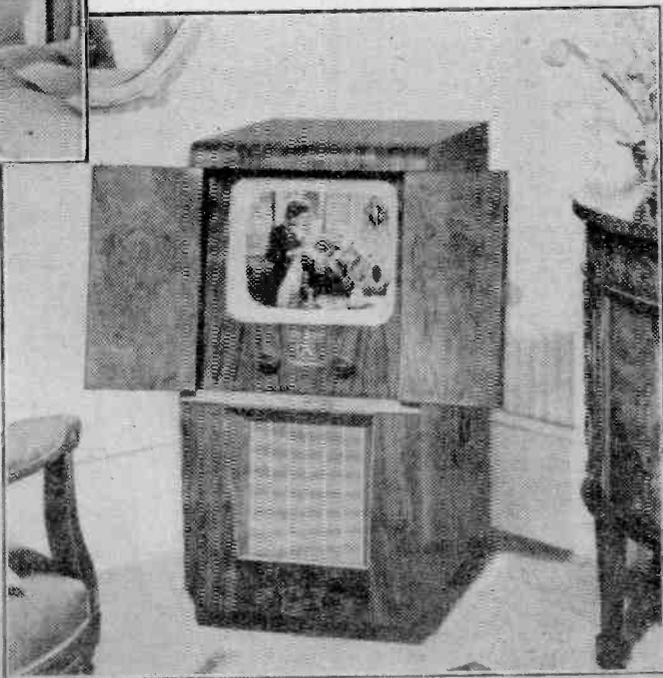Several manufacturers, including Dubilier, were showing miniature condensers, etc., which are now used in many modern television receivers, whilst small valves were seen on the Mullard, G.E.C. and Marconi stands.



HMV model 1815, an AC/DC receiver.

Birth of a Name

HOW "TELEVISION" FIRST ARRIVED

TV! Everyone nowadays recognises this most modern of the many generally accepted technical abbreviations which we all permit ourselves in our written and spoken English. There is no better shortening of "television." It is an abbreviation which, in many respects, has come to stay.

But now comes the interesting question of how, when, where and by whom the expression "television" itself first came to be used? It is, perhaps, not really a very important question, but, curiously, it is one which has never yet been settled fully and authoritatively. Take up your family dictionary. Better still, examine any standard Victorian dictionary. You will fail completely to find therein the now homely and everyday-employed term, "television." This is rather strange, if only for the reason that the Victorians and their immediate successors, the Edwardians, were fond enough of the "teles," as witness the long list of "tele"-prefixed words which give such massive and learned compilations both authority and comprehensiveness.

"Telescope," "telegraph," "telephone" and, perhaps, "telepathy" are all long-used and eminently obvious and respectable "tele"-words. But what, for instance, do you make of *telephonographic*, *teleseme* and *telekinesis*? Or of *telephote*, *telethermographic*, *teleplastic*?—all of which somewhat mysterious looking, high-flown expressions are to be found in any competent dictionary which is fifty years old or more.

Latin and Greek

"Tele," we are told, is a Greek word meaning "distance," "far," "away," and so on. "Video" is a Latin verb for "I see." Clearly, therefore, *television* is fairly self-explanatory, despite that mixing of Latin and Greek words which is so repugnant to classical scholars. But, strangely enough, the early television experimenters seem to have had no idea of how to designate or describe the aims of their various systems. They seem to have been quite satisfied by the use of expressions such as "Seeing by Electricity," "Electric Vision," and so forth. Ultimately, as their experiments developed, they gave us the expressions "electrical telescope," "distancevision," "teletroscope" (with its consequent "teletroscopy"), "electro-magnetic vision," "electrical vision," and, finally, the rather more elegant "telescopy," which latter term was a favourite with the British Patent Office, it being used officially therein as late as 1908.

An Inaccurate Term

Why the first experimenters failed to agree on a simpler term for their experiments is rather a moot point. We are inclined to think that the word "television" should have been obvious to them. Yet, on reflection, it will be seen that this word, used universally as it is at present, is not, in fact, a perfectly accurate one. An astronomer when he regards a distant planet or even the moon through his instrument is not utilising the science of television as we understand it. Yet he is obviously seeing at a distance. The term "television" has become a permanent one in nearly all languages, yet it does not perfectly describe the essentially electrical character of the technique which is employed. One has, of course, yet to hear a professional astronomer describing himself as a pure televisionist, but if such an argument

were to develop it would, strictly speaking, be difficult to disregard the claim.

Hugo Gernsbach, a very popular American magazine editor, writer and publisher, once put in a strong claim to be the first to have made use of the word "television." "This word," he wrote in 1928, "was first coined by myself in an article entitled 'Television and Telephot,' which first appeared in the December, 1909, issue of my *Modern Electrics*."

There is no doubt that H. Gernsbach believed his statement to be correct, but as a matter of fact subsequent investigation has shown that such was not the case. A Frenchman named Perskyi used the word some eight years before Gernsbach.

Perskyi was a literary man. At the beginning of the century he was engaged in making up subject-lists for a publication of the International Congress of Electricity which was held in France during the summer of 1900. Among his published lists of electrical apparatus, projects, inventions, instruments and devices, Perskyi has the word *télévision* which he uses in precisely its modern connotation. The issue of the publication containing Perskyi's *télévision* ("Annexes Congres International d'Electricité") is dated "August 18-25th, 1900."

So far as we know at present this constitutes the world's first use of our modern word. TV, therefore, in its origins, turns out to be a French-devised and applied word, not a British or even an American one. Which is rather a pity because, for the most part, modern television has been, almost exclusively, the product of British and American brains and technical enterprise combined.

New Underwater Television Equipment for Admiralty

AS we close for Press it is announced that new underwater television equipment, incorporating a strong water-tight casing for a modified standard television camera and special lighting, has been developed for the Admiralty by Messrs. Pye.

One complete set has been assembled for immediate delivery to undergo sea trials in the deep-diving vessel *Reclaim* (Lt.-Cdr. J. N. Bathurst, O.B.E., D.S.C., R.N.). A second camera has been ordered for experimental work at the Admiralty Research Laboratory, where a different type of casing is being developed.

Both these cameras will be capable of reaching depths of 1,000ft. They will have built-in facilities for changing lenses, focus and aperture while under water, this being done by remote control. With a maximum visual field of 70 deg. this equipment is of the most advanced design available.

A large fin is fitted to the exterior of the casing to steady the camera and to facilitate its use in difficult tidal conditions. This also serves for mounting the lighting.

The principles of the equipment result from lessons learned by Royal Naval Officers and scientists with the improvised equipment used for the identification of H.M.S. *Affray*, but, with the new equipment, the unwieldy external framework has disappeared. With its neat shape, it is anticipated that it will be easier to handle at sea.

SOUND REJECTION

AN EXPLANATION OF A COMMON TROUBLE AND CIRCUITS FOR ITS REMOVAL

By Gordon J. King, A.M.I.P.R.E.

ALTHOUGH the Pye development of pulse modulation—enabling modulation of sound on the vision carrier to be performed during the 10 micro-second line synchronising pulses—has shown gratifying results, the current method of using two separate channels is, at present, still favoured by the BBC, due, quite probably, to the lack of adjacent channel interference around this part of the spectrum. This state of affairs may not exist for long, however, as with the opening of the new television transmitters, receivers located in certain parts of the country may suffer from interference on the sound channels due to sound breakthrough from an adjacent channel transmitter unless, of course, they have a high high-frequency vision rejection ratio!

Sound on Vision

The problem presented at the present time, however, is one of minimising the vision channel response to the sound frequency, for unless this is satisfactorily achieved, the picture tube will produce the sound modulation in the form of dark lines across the picture varying in sympathy with the modulation content.

The character of the sound and vision transmissions are approximated by the curves of Fig. 1; at (a) the London double sideband transmission is shown, while that at (b) is the single sideband characteristic radiated by the others and potential television transmitters. Observation will show, in either case, that the sound carrier is located at the low-frequency side of the vision signal and that the sound and vision carriers are separated by a frequency of 3.5 Mc/s. Quite a reasonable frequency separation and discrimination between the two channels would not be difficult to secure if the problem was as simple as this, but obviously the vision signal must extend for at least 2.75 Mc/s in the low-frequency direction in order to convey the picture intelligence. This applies equally to the double and single sideband transmissions, for it is the upper sideband which is partially eliminated in the latter case, while the upper sideband of the former extends equally in the high-frequency direction.

It will be seen, therefore, that virtual separation between the sound carrier and the low-frequency side of the vision signal is in the region of 0.75 Mc/s only. This, then, is the factor that creates the sound rejection problem, for unless the response of the vision receiver is such that a sharp cut-off at the low-frequency end is secured, the response of the vision channel will embrace that of the sound—see Fig. 2. This, of course, will result in the vision channel being acceptable to responses at the sound frequency.

One way of overcoming this—with London receivers anyway—is to align the vision channel to the *upper sideband* of the double-sideband signal. This has the effect of shifting the vision channel response away from the sound carrier, as shown by Fig. 3. Obviously, such adjustment is applicable only to channel 1 receivers, but even so, a stage of sound rejection is usually deemed desirable.

Unless an impracticable number of stagger-tuned circuits are employed in the vision channel, the necessary sharp low-frequency cut-off in receiver response is

unobtainable from the selectivity aspect, for it must be remembered that in the interest of picture quality the 2.75 Mc/s bandwidth must be maintained.

The superhet mode of reception helps a little in this respect, especially when transformer-coupled I.F. amplifiers are employed, since then the overall vision channel comprises a larger number of tuned circuits. Further, the sound and vision channels are reduced in frequency (to the intermediate frequency) by the same ratio, and the separation frequency is then not such a small ratio of the carrier frequencies.

Sound Pick-up

Tied up with the problem of sound rejection is the circuitry employed to facilitate sound pick-up from the stages common to both sound and vision. Usually the first two valves are common to both channels. In the case of the superhet the R.F. and mixer stages are invariably common, the two channels being separated in the mixer load.

One method of performing this function is depicted by Fig. 4 (a). Here two coils L1 and L2 constitute the anode load, coil L2 is tuned for the correct vision passband, while the other—if tuned to the sound carrier—produces a trough in the overall response curve as illustrated at (b). Such a trough is desirable if it corresponds to the sound carrier where maximum rejection is needed. It is usual, therefore, not to tune L1 for maximum sound, but to tune it for *minimum sound on vision*. This effect is illustrated at (c), where a point noteworthy to observe is the very slight frequency mutation necessary.

It should be noted, of course, that (c) corresponds to the response curve of the coupling to the vision channel only. The coupling to the sound channel, being much sharper, responds solely to the sound carrier. Therefore it does not follow that when tuning to the trough on the overall response curve one is doing this in the sound channel. As far as this is concerned

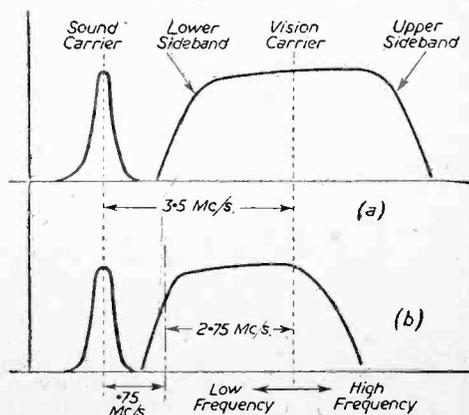


Fig. 1.—The characteristics of sound and vision transmissions, above double sideband (London), and below, single sideband (other channels).

the circuit is being slightly detuned. The sound will, of course, be attenuated due to this, but the extra sound rejection derived far outweighs this loss, which is easily counteracted in proceeding stages.

Other methods of sound pick-up produce the same effect in some degree or other, provided the sound pick-up circuit is tuned to minimum sound on vision and not maximum sound.

Rejector Circuits

The basic rejector circuit can take the form of either (a) or (b) at Fig. 5. The series-tuned (acceptor) circuit of

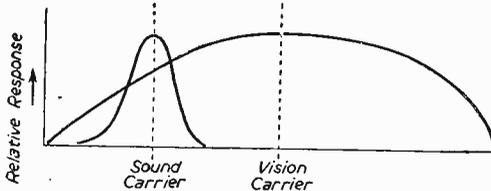


Fig. 2.—Vision channel response without rejector circuits.

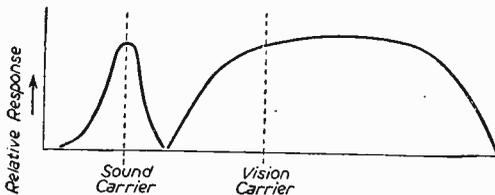


Fig. 3.—The response of a London receiver tuned to the upper sideband.

(a), when resonant, shows, across its terminals x y, a very low impedance to the resonant frequency. While, inversely, the parallel-tuned (rejector) circuit under the same conditions represents an infinitely high impedance.

Now the problem is to introduce a deep and narrow trough at the correct point in the overall response curve without seriously modifying the latter. This has been accomplished to some degree by means of the sound pick-up circuit. Actually—in practice—this circuit produces about a 10 db sound signal rejection. It is desirable, however, in most cases to achieve a sound signal rejection ratio in the order of 40 db (100 : 1 voltage ratio). To this purpose it is therefore necessary to include additional rejection circuits in appropriate sections of the vision channel.

From the foregoing reasoning two methods become obvious. One is to place an acceptor circuit in parallel with the signal path, and another is to insert a rejector circuit in series with the signal path, so that in either case the sound channel is filtered relative to the vision signal.

The principle, therefore, of the series-tuned circuit used for rejection is that at the sound frequency its impedance is so low that it presents a virtual short circuit to the vision coupling it shunts, whereas away from the sound frequency its impedance is so high that it affects very little the vision coupling.

In practice, however, a circuit such as (a) Fig. 5 shunted across one of the tuned couplings of the vision channel would hardly come up to this requirement. Its purpose would be served so far as sound rejection was concerned, but at frequencies above and below the sound rejection frequency it would become respectively inductive and capacitive, and so would tend to reduce or

increase the frequency of the tuned vision coupling. This, of course, would distort the vision response curve and of a consequence would produce the undesirable manifestations on the picture associated with such phenomena.

This effect can be minimised by connecting the rejector to a tapping on the tuned coupling as shown at Fig. 6 (a). A similar effect can also be secured by coupling the rejector coil itself to the vision coupling—see Fig. 6 (b). With this arrangement the coupling between the two coils can be varied to procure a compromise between maximum rejection and minimum effect on the vision response curve.

A circuit which is becoming progressively more popular with designers of commercial receivers is depicted by Fig. 7. Here a series- and parallel-tuned circuit combination is employed. C and L form the parallel arrangement and are chosen to resonate at a frequency corresponding to the lower edge of the vision passband. At this frequency the circuit as a whole subjects a negligible shunt impedance across the coupling coil L1, and so the vision response curve, at this point anyway, is unaffected. The parallel circuit becomes inductive as the frequency is reduced towards the sound carrier, and in association with C1 resonates to form a series circuit of low impedance across the coupling coil L1. A sharp cut-off is, therefore, obtained at the low-frequency side of the vision signal and extends, in the form of a deep trough, to the frequency of the sound carrier, thereby providing the desired sound rejection.

A noteworthy feature of this circuit is that as the frequency extends into the high-frequency side of the vision passband the circuit as a whole becomes capacitive to an extent governed by C1. Usually the value of this is extremely low, and provided it is less than the shunt capacitance of L1 the circuit effect within the vision passband is negligible. A tapping is quite frequently made on L to facilitate the pick-up of sound as previously described.

With component values modified the circuits described are suitable for inclusion in either a superhet or T.R.F. style of circuit. It should be understood, however, that in the former case it is possible for the sound channel

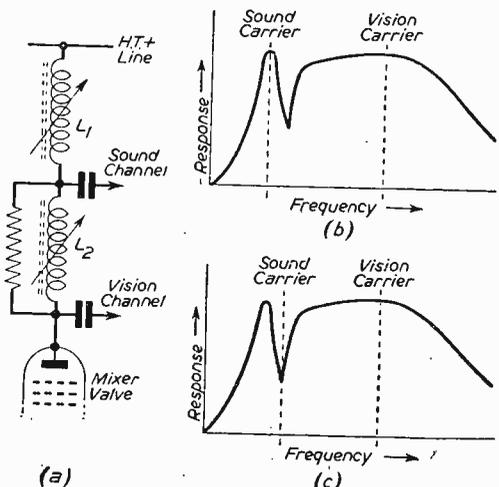


Fig. 4.—A style of sound pick-up at (a) producing a vision response curve at (b) when L1 is tuned to the sound carrier and (c) when L1 is tuned for minimum sound on vision.

—when converted to the intermediate frequency—to be on the high side of the vision passband. This occurs when the frequency of the local oscillator is higher than that of the signals. When this is so it is necessary for the converted vision signal to have a sharp cut-off at

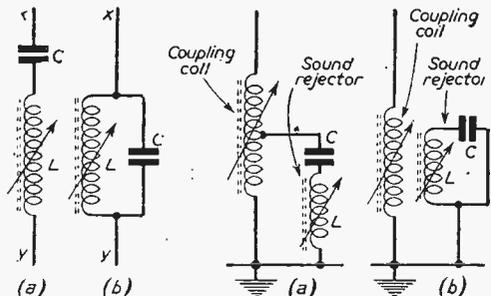


Fig. 5.—An acceptor circuit at (a) and a sound rejector circuit at (b).

Fig. 6.—Two ways of using a series tuned circuit as a sound rejector.

the high-frequency end of the passband, as opposed to the low-frequency end when the local oscillator frequency is lower than the signal frequencies.

While passing it might be of interest to recall that at least one manufacturer of a five-channel receiver has included an adjacent channel rejector to function and give an attenuation of 40 db at the high-frequency end of the vision passband.

Another Method

The parallel-tuned rejector circuit is frequently employed in commercial practice to form a sound rejector circuit in the cathode lead of a vision-amplifying valve. The basic circuit is well known, but for the sake of completeness is depicted by Fig. 8.

The circuit LC is tuned to the sound frequency and at this frequency the impedance of the tuned circuit is solely resistive. This results in heavy negative feedback,

thus reducing the gain of the stage at the sound frequency. Away from this frequency the feedback reduces owing to the fall-off in tuned circuit impedance and the stage resumes its normal gain.

It is usual practice to make the cathode connection via a tapping on the rejector coil. This minimises the load placed on the rejector circuit by the valve circuit and, therefore, enables the circuit to operate at high efficiency.

It is worthy of mention that at frequencies far removed from the sound carrier the circuit is liable to oscillate.

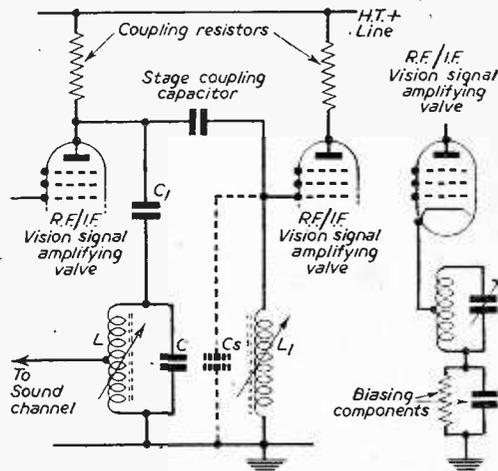


Fig. 7 (left).—A rejection circuit having negligible effect on the vision channel response provided C1 is less than Cs, and Fig. 8 (right).—the cathode circuit rejector unit.

This should be borne in mind by experimenters and service engineers for it tends to complicate the adjustment of this circuit—in fact, it may even be mistaken for a fault elsewhere in the vision channel.

Pioneer's Jubilee

THE first engineer to spend fifty years in the Wireless Industry is Mr. Raymond Dorrington Bangay, of Marconi's Wireless Telegraph Co., Ltd., who celebrated his Jubilee on May 15th.

Born at Lyme Regis in 1883, Mr. Bangay joined the Marconi Company and went to the world's first Wireless College—the Marconi College, at Frinton-on-Sea—in 1902. Later that year he went to America for the Company and, during the next five years, helped to instal many stations, including the first U.S. Coastal Station, at Babylon.

On his return to England in 1907, Mr. Bangay began his now famous study of wireless for military purposes, including the original experiments in air-to-ground communication. He later achieved the distinction of writing the first wireless text book, "The Elementary Principles of Wireless Telegraphy," and was later to follow up with "The Oscillation-Valve."

The experiments and developments he made in the military field led to the establishment, in the Marconi

Company, of a "Field Station Department" and he took it over, as Chief, in 1914.

In 1921, Mr. Bangay was appointed Chief of Designs and, with the knowledge and experience gained during all these years he became the Technical Representative abroad in 1925. His present appointment of Foreign Manager was made in 1935.

There are few countries in the world that Mr. Bangay has not visited and he is well known as a technical authority all over the world.

During his extensive travels it has been inevitable that many adventures have befallen him and, even in his Jubilee Year, Mr. Bangay is maintaining the pace and tremendous scope of his travelling.

During the first three months of 1952 he has already visited Norway (twice), Sweden (twice), Finland, Belgium, Germany and Switzerland. There can be few companions of his schooldays (Epsom College 1896-1899 and Finsbury Technical College 1899-1901) who still maintain the immense vitality and industry of Raymond Dorrington Bangay.

UNDERWATER TELEVISION

FIRST DEMONSTRATIONS OF THE NEW STANDARD EQUIPMENT PROVE HIGHLY SUCCESSFUL

THE use of television under water has been the subject of much research and experiment during recent months. When, 12 months ago, the Admiralty requested the help of Marconi's Wireless Telegraph Company Ltd. in an attempt to find the lost submarine *Affray* with a Marconi television camera chain, a new field of television applications was opened.

Since then the Marconi Company have been investigating this application, and, during the past few months, had the fullest co-operation of Siebe, Gorman and Co. Ltd. in the design of pressure cases and lighting gantries.

A recent demonstration, at the works of Siebe, Gorman's in Tolworth, shows the extreme sensitivity of this camera, and illustrates the importance of this new development. It is of primary importance in any type of underwater work where it would be dangerous for a diver to descend, and for use at depths far greater than a diver's limit.

In major salvage operations one of the greatest drawbacks has so far been the "blindness" of the surface officers directing operations. With the Marconi-Siebe, Gorman underwater television equipment they will now be able to follow the operations, direct movement and technique, and brief relief divers *visually* before they go down to take over. This will lessen the reliance on a diver's verbal report and will be of inestimable help to those in charge on the surface and to the divers themselves.

A television camera can work for far longer periods under water than could a diver; the Image Orthicon pick-up tubes in the Marconi cameras are far more sensitive and accurate than the human eye, a point of particular importance under water where visibility is necessarily bad, and, in matters of interpretation, it allows scientists and experts to see what is below, thus eliminating the discrepancies which must creep into a diver's report—the diver often having no specialised knowledge of the flora, fauna, machinery and geological vista he is sent down to inspect. At great depths pressure has an adverse effect on a diver's judgment, and discrepancies of size and distance become all too frequent.

Another very important advantage is that the television picture received on board a ship from a submerged camera can be filmed and a permanent record obtained.

So far standard Marconi cameras similar to those used by broadcasting authorities all over the world, and used extensively by the British Broadcasting Corporation for outside television broadcasts, have been used. The new camera is fitted with extra facilities designed to allow flexible control from a remote position in lieu of a cameraman.

The full facilities which are required for underwater work with a television camera chain include:

(a) *Remote focus control.* This allows the camera to be focused, while submerged, by the operators aboard ship, and, as indication of setting is shown at the control point, it is possible to estimate the size and distance away of an object with reasonable accuracy.

(b) *Remote iris control.* Remote indication is again provided with this facility. The main advantage of remote iris control is that the lens aperture can be varied to obtain the best possible picture under conditions of considerable light variation. Such variations are present when an object is viewed at 20ft. distance, and then the camera is moved in for a close-up view at 4ft., without varying the light intensity.

(c) *Lighting system.* This must be very flexible to allow for use in waters of various densities and content, and at various depths. The unit provides eight lamps which can be controlled, in pairs, from the surface.


(d) *Mounting facilities.* This must also be a flexible system so that camera and lights can be set up for viewing at various angles, as well as at varying distances.

(e) *Inclinometer.* This gives indications, at the control point, of the unit's angle when submerged.

(f) *Water indicator.* Moisture within the pressure casing, which houses the camera, is extremely detrimental to all the equipment, and this facility detects and warns the operators of any moisture entering the casing.

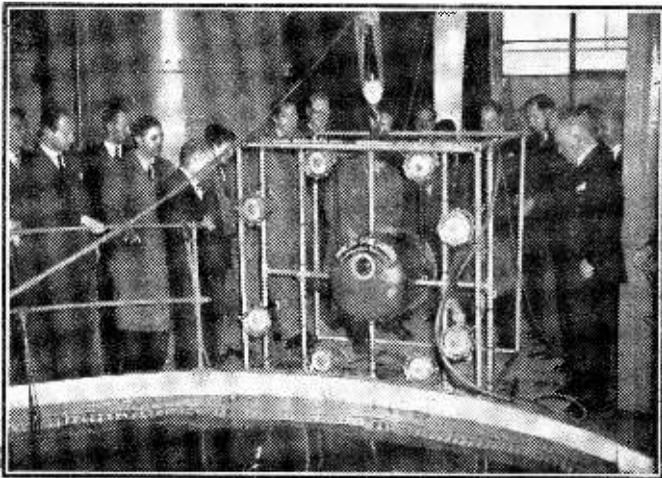(g) *Orientation.* A remote bearing compass to indicate the correct orientation of the camera.

Apart from the experimental side of underwater television the Marconi equipment has already proved highly successful in the finding of the *Affray* at a depth of 280ft.



The underwater television equipment, designed by Marconi's Wireless Telegraph Co., Ltd., was shown to Naval Attaches and Admiralty Officials at the works of Siebe, Gorman and Co. Ltd., who have designed the pressure casing and lighting gantry. The Attaches (representing the Argentine, Brazil, Chile, Denmark, Holland, Italy, Norway, Spain, Sweden, Turkey and Venezuela) together with Admiralty and Scotland Yard Officials saw divers working in murky water through the "eye" of the Marconi-Siebe, Gorman underwater television camera.


Knowledge gained on that occasion is now being put to use and a pressure casing for containing the camera is being designed and produced. These casings will have viewing windows through which the lens of the cameras will "shoot" the underwater scenes. A new type of gland has been devised for the camera cable. The cable is of special construction, and is capable of being operated at depths of over 1,000ft.

The Marconi cameras have been used at varying depths and it has been found that in certain conditions good pictures are obtained as deep as 80ft. without the aid of artificial light.

Tests made under practical conditions at sea show that artificial illumination of the object is of doubtful value when the water is clear, but many more results will have to be compiled and obtained before firm conclusions can be justified. Another interesting point shown by these sea tests is that tungsten lighting appears to give better results than either sodium or mercury vapour light.

Under test conditions some applications have already been thoroughly tried out—study of wrecks, finding of objects, and the investigation of the sea bed—and others which present themselves are the study of fish in their natural surroundings, the investigation

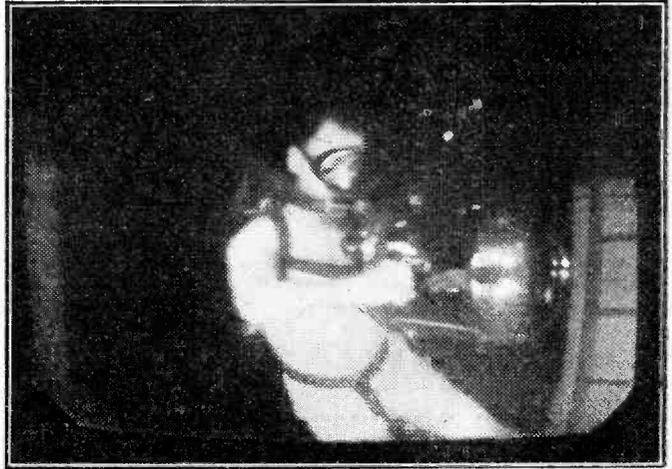of trawl nets under operational conditions, identification and control of oyster and scallop beds, inspection of dock gates and ships below the water line without



A photograph taken of the screen of a television receiver, showing a "frogman" at work below the surface—using a cine camera.

employing divers or using dry docks, and the possibility of undertaking really deep-sea research to depths exceeding 1,000ft.

New Use for Colour : B.S. for Colour Codes

A NEW use for colour television which adds another dimension to biological research was described recently to the Institute of Radio Engineers by three R.C.A. scientists, Dr. V. K. Zworykin, L. E. Flory and R. E. Shrader, of the David Sarnoff Research Centre at Princetown, N.J. They said the use of colour television will enable the biologist to obtain more information about microscopic specimens than with present methods.

The development was made possible by hooking up an R.C.A. tricolour picture tube to a sensitive new ultra-violet vidicon camera, which is mounted over a microscope trained on a specimen. The absorption of ultra-violet light by the tissues of the specimen differs among them. By arbitrarily assigning different colours to the tissues, the biologist can make them emerge with individual clarity. This method supplants the old system of staining the tissues.

The new technique adds colour artificially to cells or tissues by translating different wavelengths of invisible light into electronic energy. This energy is then translated into the three different primary colours on a colour television picture tube.

A specimen or thin slice of tissue which, to the human eye, appears colourless and flat through a microscope then can be viewed on a television screen as a dynamic picture in colour.

It was pointed out that the use of colour television in biological research represents an extension of the television microscope technique which was introduced by R.C.A. last year. This development permitted instantaneous examination of microscopic specimens under ultraviolet light, and represented an advance over the earlier system of filming biological specimens.

A NEW British Standard, B.S. 1852, "Colour code for fixed resistors for telecommunication purposes," sets out what has now become, with one or two minor divergencies, the internationally agreed colour code for resistors of the type commonly used for telecommunication purposes. The colour code has been in use in this country and elsewhere for several years and is based upon that originated by the Radio Manufacturers' Association of America.

Preferred Method

The Standard specifies the colours to be used and describes alternative methods of marking; the coloured band method is given as the preferred method. Tables giving an interpretation of the code are included.

The Standard applies only to resistors for which colour coding is used to indicate resistance value and certain other characteristics, and does not preclude the continued production of resistors on which ratings are indicated in a non-coded form.

Copies of this Standard may be obtained from the British Standards Institution, Sales Branch, 24, Victoria Street, London, S.W.1, price 1s. post free.

NEW EDITION NOW READY

"PRACTICAL WIRELESS" CIRCUITS

15th Edition

6/-, or 6/6 by post from

GEORGE NEWNES LTD.,

Tower House, Southampton Street, Strand, W.C.2

Television Technique as an Aid to Observation

FURTHER EXTRACTS FROM A PAPER BY J. D. MCGEE, M.Sc., Ph.D., A.M.I.E.E., OF E.M.I. RESEARCH LABORATORIES, LTD., READ TO THE ROYAL SOCIETY OF ARTS

(Continued from page 551 May issue)

Televising of Dangerous Processes

THERE are many cases in which it is desirable to watch closely events which are either inherently or potentially dangerous. Thus, in atomic energy work there are operations which must be performed in the presence of intensive and lethal radiation. These have been done by remote controls while observing through a mirror system, which enables the operator to see over an intervening radiation screen, or through 3ft. thick windows of special lead glass. These operations could be watched by television, and possibly with greater facility than by the use of mirrors. The advantage to be gained is the means of keeping the operator well away from the source of dangerous radiation—distance being the best and cheapest form of protection—while by means of remote controls of the camera—focus, iris, lens turret or zoom lens and even direction—he could have greater freedom of observation than when using a mirror system.

It is possible, though by no means certain, that to compete with the mirror system a colour television equipment would be necessary. Insufficient first-hand evidence is available to enable a worthwhile opinion to be given on this point. However, if colour television is necessary this, like operative surgery, is the kind of situation in which it could be applied, since the technical and economic difficulties arising in broadcasting colour television do not arise. Probably the only technical question arising in this application is what effect will such intense penetrating radiation be likely to have on the operation of such a sensitive and temperamental electronic device as a television pick-up tube. Such tests as the author is aware of have shown that the effect is negligible. A C.P.S.₄ Emitron camera was completely unaffected by being exposed to a powerful beam of γ -radiation.

Many other similar applications can be visualised. For example, in the testing of atomic weapons a television camera might be used to give, at a safe distance, a close-up picture of events up to the moment when, presumably, the camera would disintegrate and evaporate in the intense heat of the atomic explosion. Similarly, television cameras could be used to give pictures of the results of such a trial at distances where a human being would, but a camera would not, be damaged by radiation.

Again, it may be necessary to observe closely a new device being tested, or tested to destruction—a process which may involve considerable danger to an observer close at hand. One hypothetical example will be given. It may be desired to test some part of the structure of a new aircraft to the point where it fails. This is a very hazardous thing for a pilot to have to do, since the machine would probably have to be flown at supersonic speeds for the failure to occur, thus making it difficult for him to escape by parachute. However, it would be a comparatively simple technical problem to arrange a television camera to watch the critical point and to

transmit the picture to a receiver on the ground by radio where the experts concerned could watch the failure occur in detail from the safety and comfort of an armchair. The 'plane, of course, would be flown by remote radio control in the ordinary way.

Television Guided Weapons

This is an application that was envisaged at a very early stage in the development of television and has received some publicity in recent years. (See *Time*, May 19th, 1951.) In 1938-39 we, of E.M.I. Research Laboratories, fitted a television camera, control equipment and radio transmitter in an aircraft from which pictures of the ground over which the aircraft was flying were transmitted back to receivers at the laboratories. Ground targets were easily identifiable when the aircraft was 25 or 50 miles away over land and 50 to 100 miles over sea. This immediately led to the proposal to put the camera in the nose of the aircraft, load it with explosive, and fly it by remote control, and directed by the television picture, into the selected target on the ground; the aircraft and camera equipment being treated as expendable. It was hoped that the accuracy of bombing selected targets would compensate for the expenditure of so much equipment.

Quite clearly such a scheme is in principle still a possibility, but to discuss it in more detail is outside the scope of this paper.

X-ray Image Television

Radiologists have been, and still are, very anxious that some device be found, possibly by the utilisation of television technique, by means of which adequately bright X-ray images might be obtained while using less intense X-ray beams. This is important both for the doctor and the patient.

Electromagnetic radiation of very short wavelength, such as X-rays and gamma rays, liberate very few photo-electrons when they fall on a surface such as the photo-sensitive surface of a television pick-up tube. Hence a television signal cannot be obtained by the direct action of these radiations on such a mosaic target.

The only feasible approach to this problem, therefore, was to direct the television camera at the fluorescent screen which is normally viewed directly by the radiologist. However, in this comparison, as noted earlier in the section on the televising of surgical operations, the camera compares badly with the human eye if reasonably rapid movement must be observed.

Television Memory

All television pick-up tubes make use of "memory" to some extent. That is, the effect of the light of liberating photo-electrons, which is instantaneous, is integrated in the form of electric charges on small, highly insulating condensers which can retain or

remember the charge image until they are discharged in rapid succession by a scanning electron beam to produce the picture signal. In normal television, substantially all charges collected on the mosaic during one frame period are discharged at each transit of the scanning beam, otherwise objectionable lag would appear in the picture. Now this capacity of the tube to integrate and store electric charges can be used in various ways, a few of which are now described.

Transmitting Pictures Over a Narrow Frequency Band Circuit

The normal television system requires a 400- to 500-line picture repeated 25 times per second and if good detail is to be reproduced this requires a band width of about 3 Mc/s. To transmit such a picture signal requires a very special and expensive transmission channel. There are cases in which it would be worth while sacrificing something in the picture to enable it to be transmitted over a more or less simple, narrow-band, channel. Picture detail cannot be sacrificed, but rapid reproduction of movement sometimes can. Suppose, then, it is agreed to send only one complete picture per second. This will reduce the frequency bandwidth by a factor of 25 to say 100 kc/s. In the C.P.S. Emitron camera the noise is due to the amplifier and is proportional to the square root of the band-width required. Hence the noise will be reduced by a factor of 5, and so for the same signal to noise ratio, a signal current of only one-fifth is required. The signal current must equal the charging current to the mosaic condensers, which in this case must integrate one-fifth the normal charging current for 25 times the normal frame period. Hence the mosaic capacity must be five times that of the normal C.P.S. Emitron.

If such a picture signal is transmitted over a communication channel, received and used to modulate a cathode ray tube scanning one complete picture per second, the result would be very unsatisfactory to look at because of the violent flicker. A high capacity C.P.S. Emitron type tube can, however, be used to give a steady picture. The reconstituted picture on the receiving cathode ray tube is focused optically on to the mosaic of the high capacity tube, where strong charges are built up by photo-emission. These charges are then scanned off slowly by the scanning beam operating at normal television frame frequency. The picture signals so generated are then reconstituted on a conventional television receiver to give a flicker-free picture. The frame period might be increased to, say, ten seconds with a proportional decrease in the required band-width to 10 kc/s., thus making transmission over communication channels easier. Thus a fixed chart, document, photograph, or even a slowly changing picture such as a radar display could be transmitted over great distances without special wide-band channels.

Stroboscopic Television

The problem sometimes arises of observing closely a moving object at some point of its cyclic path over which it moves too rapidly to be followed accurately by the unaided eye. It is comparatively simple to arrange a mechanism which is triggered by the object at the appropriate point on its path and fires an electrically operated flash lamp which illuminates the object brilliantly for a sufficiently short time to effectively arrest its movement, say, 0.001 second. If a high capacity type C.P.S. Emitron is focused on the object at this point, a brilliant image of it will be formed on the mosaic and a strong charge image of the object will

be built up on the mosaic which is sufficient to give an adequate signal to noise ratio when the tube mosaic is scanned in the normal way at, say, 25 frames per second for the next second or so until another charge image is built up on the mosaic. Thus a rapid succession of pictures of the moving object arrested at any chosen point in its cyclic path will appear on the television display screen.

This kind of investigation has usually been done by cinematographic methods, but these suffer from the disadvantage that some time must elapse before the film can be developed and projected.

Television in Astronomy

If we compare the picture from a modern television camera operating at 25 pictures per second, with a photograph taken with the same effective exposure time of 1/25 sec. using the fastest available commercial film (Super XX) we find that the television camera is the more sensitive by a factor of 5 to 10. Also a television pick-up tube of the C.P.S. Emitron type allows charges produced by very weak light images to be integrated on the mosaic since they are not lost or confused by electrical leakage. When sufficient charges have been accumulated they can be scanned off rapidly by the scanning electron beam to produce a signal picture. In tubes already made such a "time exposure" of a C.P.S. Emitron tube has been continued for several minutes and there seems to be no reason why tubes cannot be made to enable time exposures lasting some hours to be made. Thus there is a good reason to hope that a television pick-up tube might surpass the photographic plate in sensitivity even when used for long time exposures. It is true that the picture reproduced from the storage tube after a long exposure would last for only a few picture frames, but it could be photographed, and there is good reason to hope that it will be possible to reproduce it for quite long periods by use of other storage tube devices.

The most important feature of this possible application is that the photo-electric emission, on which the whole process depends, is strictly proportional to the incident light down to the smallest amounts of light known as quanta. This is not the case with the photographic process which shows a discontinuity at low light intensities, and so cannot be relied upon to give accurate reproduction of very faint images. Thus it is possible that this application of television technique to the recording of very faint light images may both extend the range and improve the fidelity of recorded images.

Space does not permit a detailed description of the type of apparatus envisaged for this application to be given, but the main requirements are:

1. The photo-electric efficiency of conversion of light into electrons must be as high as possible, thus indicating a continuous photocathode rather than a discontinuous mosaic.
2. The integration and storage of these electron charges must be efficient over long periods which requires a storage mosaic with extremely good insulation.
3. The reproduction of the stored charges must be done in such a way as to avoid spurious signals, shading effects and other defects so common in television pictures.
4. The reproduced picture must be recorded for prolonged study in detail.


It seems quite possible that in the not too distant future electron tubes of this general type may be used for recording very faint optical images as, for example, in the large astronomical telescopes.

IT PAYS TO SOLDER

★ WIDEST RANGE TO SUIT EVERY NEED
★ SOLDER TWICE AS FAST AT FAR LESS COST

WITH WOLF

SOLDERGUNS

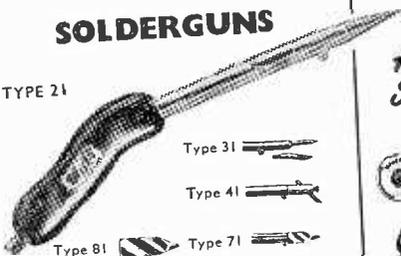

TYPE 21



Type 31



Type 41



Type 71



Type 81

**OFF-STRAIGHT EASY-GRIP HANDLE
PERFECT CONTROL • QUICKER HEAT-UP • LOCALISED HEAT • LOW CURRENT CONSUMPTION • MAINTAINS CORRECT HEAT • MODELS FOR EVERY PURPOSE**


Automatic Soldergun



TYPE 51

The Wolf Automatic Soldergun with its automatic, trigger solder-feed action is indispensable to all modern assembly.

SOLDERING IRONS

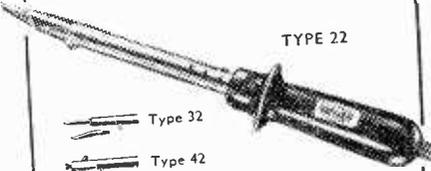

TYPE 22



Type 32



Type 42

For all who, for special reasons, prefer the conventional straight-type handle. Identical as regards elements and bits to Wolf Solderguns, but with round hard wooden handle with heat-deflecting skirt.

★ OBTAINABLE FROM ALL HIGH-CLASS STOCKISTS AND IRONMONGERS
WOLF ELECTRIC TOOLS LTD., PIONEER WORKS, HANGER LANE, LONDON, W.5. TEL. PERIVALE 5631-4

LASKY'S RADIO

FOR TELEVISION COMPONENTS

We stock all the specified Viewmaster components, and you can buy everything separately, or stage by stage. Write for a complete Viewmaster price list.

ELECTRO MAGNETIC FOCUS COIL. fitted to rear tube support. Suitable for 9in. cr. tubes. A few only.
LASKY'S PRICE, 27/6 complete. Postage 2/- extra.

SPECIAL TV CONDENSERS, T.C.C. VISCONOL. .04 mfd. 12.5 Kv. **LASKY'S PRICE, 7/6 each.** 32 + 100 mfd. 450 v.v. **LASKY'S PRICE, 8/6 each.** Postage 6d. per item extra.

DE LUXE TV CONSOLE CABINETS. Beautiful figured walnut veneer. For 12in. c.r. tubes, figured medium walnut finish, with high polish. Fitted with shelf for receiver, glass, speaker baffle and fret, and castors for easy movement. Undrilled. Outside dimensions: 17 1/2in. x 16 1/2in. x 32in. high. Adaptor frames for 9in. and 10in. tubes can be supplied.
LASKY'S PRICE, £8.10.0. Carriage and packing 12/6 extra. Write for illustration.

THE VIEWMASTER
Television for the home constructor at its finest. Send today for The Construction Envelope, a 32 page booklet crammed with top-rate information and all the necessary data, also 3 full size working drawings and stage by stage wiring instructions.
Model A for use in London and Home Counties, B for Sutton Coldfield, C for Holme Moss, D for Kirk o'Shotts, E for Wenvoe.
PRICE, 7/6 per copy. POST FREE.

CATHODE RAY TUBES. All makes, types and sizes in stock. Brand new and fully guaranteed.

9in.	From £13.13.8
10in.	From £15.4.0
12in.	From £18.4.10
15in.	From £22.16.10
16in. M.E.T.	From £24.6.5
14in. Rectangular	From £22.8.5
17in. Rectangular	From £26.19.8

FRAME BLOCKING OSCILLATOR TRANSFORMERS. LASKY'S PRICE, 4/6. Postage 6d. extra.

MULTI RATIO FRAME OUTPUT TRANSFORMERS. Brand new and unused. By Parmeko.
LASKY'S PRICE, 10/6. Postage 1/6 extra

E.H.T. VALVE RECTIFIERS, VU111 and VU120A.
LASKY'S PRICE, 3/6 each. Postage 6d. each extra.

VCR97 CATHODE RAY TUBES. Brand new and unused. In maker's sprung wood case.
LASKY'S PRICE, 40/-. Carriage 5/- extra
6in. SCREEN ENLARGERS. Suitable for use with VCR97's.
LASKY'S PRICE, 22/6. Carriage 3/6 extra
6in. SCREEN ENLARGERS, Filter type, suitable for use with VCR97's.
LASKY'S PRICE, 25/-. Carriage 3/6 extra

SCANNING COILS
Low impedance line and high impedance frame.
LASKY'S PRICE, 14/6 per pair. Low impedance line and frame by Plessey. Suitable for V/M.
LASKY'S PRICE, 29/6 per pair. Postage 1/- per item extra.

LINE OUTPUT TRANSFORMERS. Manufacturer's surplus. For use with ET51 rectifier.
LASKY'S PRICE, 12/6. Postage 1/6 extra
ALLAN LINE OUTPUT TRANSFORMERS. Suitable for V/M.
PRICE, 29/6. Postage 1/6 extra.

LUXURY CONSOLE TV CABINETS. Luxuriant medium walnut veneer finish. For 12in. c.r. tubes. Fitted with shelf for receiver, speaker baffle and fret, also safety glass. Undrilled. Outside dimensions: 17 1/2in. x 17in. x 34in. high. Adaptor frames for 9in. and 10in. c.r. tubes can be supplied.
LASKY'S PRICE, £10.10.0. Carriage 12/6 extra. Send for illustration.

LASKY'S RADIO, 370, HARROW ROAD, PADDINGTON, LONDON, W.9. (Opposite Paddington Hospital.)

(Lasky's (Harrow Road) Ltd.)
Phone: Cunningham 1979 and 7214. Hours: Mon. to Sat., 9.30 a.m. to 6 p.m. Thurs. half-day.
TERMS: Pro Forma, Cash With Order, or C.O.D. on post items only. Postage and packing extra, unless otherwise stated.
All goods fully insured in transit.

T/V TECHNOLOGY



*Home Study will give you
a fuller understanding
of Television problems*

To the enthusiast for whom television is an absorbing interest and who wishes to understand more about it, or to those who are constructing their own sets and want complete knowledge of the theory underlying the constructional details, ICS offer a sound, practical and comprehensive course of instruction. It has given a high level of efficiency to many, who studied in their own time. What about you?

FOR THE ENTHUSIAST OR INTENDING T/V ENGINEER

Course 'A' provides a sound introduction to radio and television principles, deals with the principles of reception and transmission, and includes the preliminary study of Mathematics, Electrotechnics and Radio and Television.

Course 'B' offers a more comprehensive treatment of receiving equipment, deals in detail with modern principles of transmission and reception, and contains the necessary introductory instruction in mathematics, electrotechnology and radio.

The ICS also offer the following Courses in Radio :

Complete Radio Engineering
Radio Service Engineers
Radio Service and Sales
Advanced Short-Wave Radio
Elementary Electronics, Radar and Radio

And the following Radio Examinations :

British Institution of Radio Engineers
P.M.G. Certificates for Wireless Operators
City and Guilds Telecommunications
C. and G. Radio Servicing Certificate (R.T.E.B.)

For FREE BOOKLET and full details of these highly successful courses, fill in and post the coupon below. Fees are moderate and include ALL books required.

Generous Discount to H.M. Forces.
(Dept. 172A, I.C.S. 71, Kingsway, W.C.2.)

CUT HERE
INTERNATIONAL
CORRESPONDENCE SCHOOLS LTD.
(Dept. 172A),

International Buildings, Kingsway, London, W.C.2.

Please send booklet on subject

Name Age

(BLOCK LETTERS PLEASE)

Address

VIEWMASTER

LONDON - MIDLAND - HOLME MOSS
KIRK O'SHOTTS AND WENVOE

A superb quality receiver you can build in 7 easy stages from standard parts.

- ★ Brilliant, high definition picture.
- ★ Uses 9in. or 12in. C.R. Tube.
- ★ Table or Console versions.

A complete constructional envelope is available with 34-page fully illustrated "How to make it" Manual, eight full-size working drawings, alignment and operating details, etc. Model "A" London, "B" and "E" Midlands and Wenvoe, "C" and "D" Holme Moss and Kirk o'Shotts. 7/6 post paid.

Revised price list of Viewmaster components giving details of the 7 easy stages, 2½d. post free.

"VIEWMASTER" KITS IN STAGES—Holme Moss, Kirk o'Shotts : (1) £3.2.3, (2) £2.2.9, (3) £5.1.10, (4) 8/11½, (5) £10.8.3, (6) £7.5.3, (7) £2.13.11. Sutton Coldfield : (1) £3.3.0, (2) £2.2.9, (3) £5.1.4, (4) 8/11½, stages 5-7 as Holme Moss, Wenvoe : (1) £3.3.0, (2) £1.19.0, (3) £5.1.4, (4) 8/11½, stages 5-7 as Holme Moss, London : (1) £3.3.6, (2) £2.1.10, (3) £4.8.3, (4) 6/7½, stages 5-7 as Holme Moss. Kit of coloured sleeving and screened sleeving 5/-, Kit of unspecified bolts and nuts 5/-.

Please include postage on orders under £2.

CATALOGUE No. 8—54 pages, illustrated on fine art paper, containing over 2,000 radio and television lines, 9d. post free

Southern Radio & Electrical Supplies

85, FISHERTON STREET, SALISBURY, WILTS.

Telephone: Salisbury 2108

ARTHURS HAVE IT!

LARGE VALVE STOCKS

TEST METERS IN STOCK

"AVO," "TAYLOR" TEST METERS AND SIGNAL GENERATORS

Leak Point One Amplifiers	£28 7 0
Leak Pre-amplifiers	9 9 0
Leak Tuning Unit	36 17 4
Chapman Tuning Units	17 6 8
Crystal and Moving Coil Microphones.	
Decca Replacement Heads and Pickups.	
Goodman's Axiom 150 Speakers	10 5 6
Partridge Output Transformers for	
Williamson Amplifiers	6 12 0
Cossor Double Beam Oscilloscope { 1035	93 10 0
{ 1049	132 0 0

LATEST VALVE MANUALS

MULLARD, OSRAM & BRIMAR No. 4, 5/- each. MAZDA 2/- each. Postage 6d. extra. TELEVISION SETS, WIRE AND TAPE RECORDERS ALWAYS IN STOCK

Goods offered subject to price alterations and being unsold.

Arthur's first
Est. 1919

PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS : Gray House,
150-152 Charing Cross Road, London, W.C.2

Temple Bar 583314 and 4765 WRITE FOR LISTS
TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."
CABLES—"TELEGRAY, LONDON."

Line Flyback E.H.T.

METHODS OF OBTAINING DIFFERENT VOLTAGES

By P. Dodson

THE high-voltage pulses generated at the anode of the line output valve in a magnetically-deflected receiver make it possible, with the addition of a suitable rectifier, to obtain E.H.T. simply and cheaply. It is a method favoured by the majority of commercial manufacturers. The actual voltage is usually fixed, being determined largely by the amplitude of the pulse. This varies with different line output transformers, type of valve and H.T. potential. These pulses reach an amplitude of 2 to 2.5 kV. above earth and occur at the line frequency of 10,125 cycles per second. They can be stepped up by means of an overwind on the line output transformer, or by a multiplier circuit, then rectified to produce E.H.T. Sometimes it happens that the E.H.T. is not correct if another type of C.R.T.

is to be used, the voltage being either too high or too low.

Should the voltage be too high a bleeder network consisting of half a dozen or so fixed resistors to a total value of, say, 50 megohms may be connected from E.H.T. line to earth (Fig. 1). The correct operating voltage can then be obtained from a point on the network.

If a metal rectifier, such as 36EHT100, is used instead of a valve, it could be connected to either the anode of the line output valve or the transformer. If the transformer ratio is 2 : 1 then the anode connection will give 1½ times instead of double voltage. A valve rectifier cannot be connected to the anode of the line

output valve with an overwound transformer, as the rectifier heater would run at too low a temperature. This is due to the fact that the heater winding has been designed for operating the valve from the overwind on the transformer. A separate heater transformer could, however, be used, but it would need to be highly insulated, as the inverse peak voltage from heater to earth is double the input peak voltage.

When it is desired to fit a modern tube in an old television receiver an increase in E.H.T. will be necessary. There are several ways in which this can be accomplished. If the receiver derives its E.H.T. from the line fly-back, the voltage can be increased by using the pulse at the anode to supply a boost rectifier. The output of this is added to that from the transformer overwinding (Fig. 2). If the ratio is 2 : 1 the increase in E.H.T. will be approx. 1½ times. So, if the original voltage was 6 kV., then the augmented E.H.T. will be 9 kV. If the tube requires a lower voltage a bleeder network can be fitted and the correct operating voltage tapped off.

A booster can also be applied to an existing mains-driven E.H.T. supply (Fig. 3). If the original E.H.T. was, say, 5kV., then the augmented voltage will be approximately 7.5 kV., the additional 2.5 kV. being supplied by the booster circuit from the anode pulse.

Fig. 4 shows a method whereby 4.5 kV. or 6 kV. can be obtained by a multiplier circuit using miniature metal rectifiers on a line output transformer without overwound primary or heater winding. For a 4.5 kV. output omit MR3, C2, C5 and R2.

In addition to the systems outlined a further variation of E.H.T. voltage can be effected by varying the H.T. applied to the anode of the line output valve. This, as mentioned earlier, varies the amplitude of the pulse at

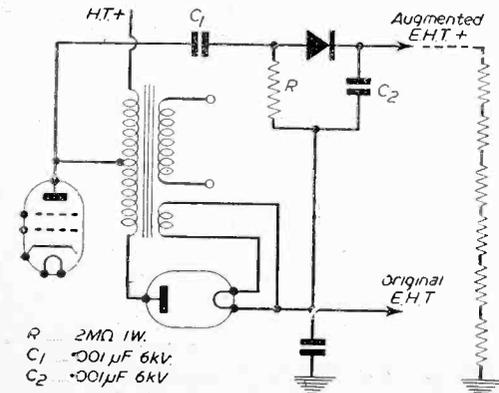


Fig. 2.—Circuit showing booster diode added to a line flyback circuit.

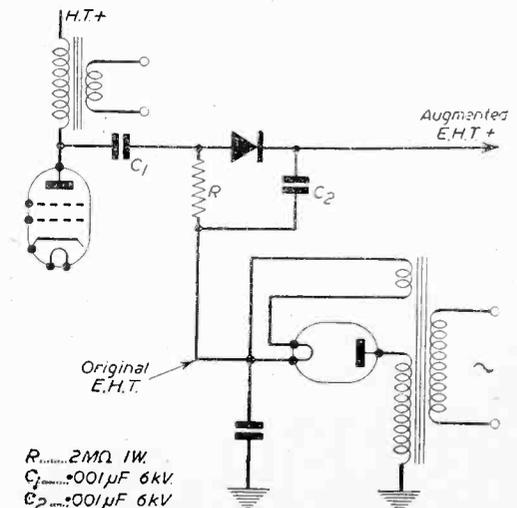


Fig. 3.—A booster added to a mains-driven E.H.T. supply.

the anode. If further control is desired a wirewound variable resistor may be fitted to supply the screen volts. The cathode bias resistor may be made variable and used to alter the amplitude, and this will vary the E.H.T. voltage. For this reason the amplitude (width) control is best placed in the leads to the line coils or across a separate winding on the line transformer.

A Warning

It is as well to repeat here the warning that the efficiency of the line scanning circuits is dependent upon the value of the E.H.T. For instance, if it is thought that more E.H.T. is desirable, and any of the changes mentioned above are made, it will undoubtedly be found that the picture will be reduced in width. Therefore, it must be remembered that increased E.H.T. calls for increased scanning power and vice versa.

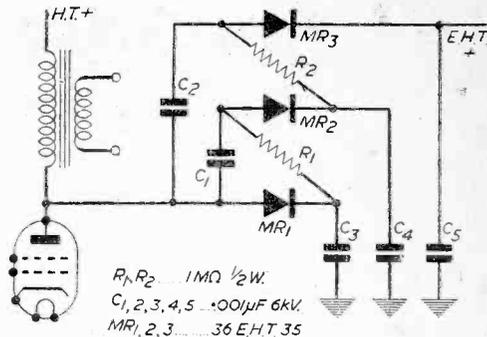


Fig. 4.—Multiplier using metal rectifiers.

Irish Television

By J. Gray

THEY say that the average human is very prone to boasting; and with many long-range television enthusiasts this remark is particularly true. Possibly the Celtic background has something to do with it; for somehow when your video signals reach us in the Ulster hills they have a peculiar way with them. By some they are reflected by the clouds, and by others the reception reasons are due to ground drag. More mystical reasons are given by outer circles of the public, however, so perhaps no more need be said of these.

Somehow the "little folk" seized the writer, and he felt compelled to dabble in the enchantment. His magic box was a 1355 unit, with an RF26 tuner (how these horrible numbers break spells). At first the choice was apparently Sutton Coldfield, and then Holme Moss; but, as the stations drew closer and still no picture materialised, so also did the spirits drop. A detailed study of a map of the British Isles, however, showed that the local Castlereagh Hills (S.E. of Belfast), in the shadow of which the writer lives, were providing an effective screen. Until the Kirk o' Shotts station opened, therefore, it was decided to study receptions in other parts.

Now the spell returns, when visits always bring forth tales of previous wonderful reception. Perhaps it was just the night before, or was it two or three nights ago? My fellow enthusiasts, stout chaps all, will excuse me here. It is all in good fun, and one cannot resist poking a finger of fun now and then. Preserve us from TV bigotry. The main point was that always there was snow, lots of it, more than the North or South Poles ever saw. And then the cars and amateur transmitters, and Radar stations—and cement mixers. Have you ever had your reception spoilt by a cement mixer? Still, all joking aside, there were one or two bright periods, particularly on the high ground north of the city.

At last the hour arrived, and Scotland came on the air. For some weeks there had been a warming-up period, when the tuning signal was transmitted and the clock was duly noted (yes, it was badly out of shape, crushed to one side, and holding badly). Still, if you can do better at 120 miles and 5 kW, you are welcome. There is a certain temptation to sum up the previous receptions by the haughty remark: "Oh, high-ground, you know"; but then look at the distances—220 miles Sutton Coldfield and 180 miles Holme Moss. The reception set-ups

were similar—1355 unit with RF26, and, incidentally, VCR97.

Since those first exciting days Kirk o' Shotts has come on to the regular programme, though still at 5 kW., and results are variable. Sometimes they are fair; but more often there just aren't any. There is certainly nothing entertaining about the reception, and the best that could be said about it is "novelty." Then again there is the ever-present urge to boast, to display that rare thing the TV aerial (this is a three-element array, cut for, and directed towards, Kirk o' Shotts), or to say in that nonchalant way, "yes, I saw it on the TV the other night."

Still, to break through the enchantment, and the blarney, some facts do emerge. First, results improve with temperature and pressure rise. Then reception is usually better after dark. Finally, the sound reception is generally quite good. Before concluding, the author must point out that there is still a vertical black line cutting across his picture three-quarters to the right, and all his spells to date have been unable to remove it.

Practical Wireless — June

The current issue of our companion journal **PRACTICAL WIRELESS** contains preliminary details of a new Radiogram designed for the quality enthusiast who wishes to use any of the various types of gramophone record which are now available. A special auto-changer is employed which enables a stack of standard 78, 33 $\frac{1}{2}$, or 45 r.p.m. discs to be used, and the amplifier is designed for high quality. A radio unit and gramophone pre-amplifier are built in, the former covering three wavebands and utilising a commercial multi-coil unit. The circuit employed is of the superhet type, and the output stage employs two 6V6's in push-pull. The issue also contains articles on a Voice-operated Relay, a Modified Folded "V" beam Aerial and Variable-frequency Oscillators, whilst the amateur transmitter is catered for in a new series on V.F. oscillators which commences in this issue.


between the grid and anode circuits of the triode sufficient to cause strong low-frequency oscillations; the original high-frequency oscillations of the circuit are thus strongly modulated and what is, in effect, a "pulsed" carrier is transmitted. If the one-turn coupling loop is plugged into the output socket this will be found to serve as a sufficient aerial for good signal injection into a nearby televisor, the televisor itself being coupled into a suitable dipole. It is generally preferable to test televisors with a dipole connected into the aerial sockets to give the first tuned circuit correct loading if a properly matched signal or pattern generator is not available.

Since only a low H.T. potential is required (of the order of 150 volts), a simple power pack suffices. That shown in Fig. 1 employs a 250 volts half-wave rectifier (two SenTerCel RM1 units in series), with no reservoir capacitor, the rectifier feeding directly into the smoothing resistor R3. An 8 μ F 350 v.w. capacitor provides adequate smoothing, a slight residual hum on the supply line serving to lock the audio oscillator to a multiple of 50 cycles per second.

In a single valve unit of this description where the H.T. is drawn directly from the A.C. mains there is little purpose in tying up a heater transformer for the valve heater supplies, and a series-capacitor heater circuit is, therefore, employed; a CZI Brimistor being placed in series with the capacitor and valve heater to take up undesirable starting surges which might otherwise overload the valve heater. For the benefit of constructors to whom this method of heater power supply is new it can be said that the regulation of the system is remarkably good so long as the heater load is kept reasonably low—for 0.2 amp. valves regulation is good until the voltage drop across the series heater chain is as high as 100 volts. In the present case where only one valve is in circuit, regulation might be said to be almost perfect—shorting out the Brimistor, for example, once the circuit has risen to operating temperature, gives practically no variation in heater voltage, and mains fluctuations are similarly made ineffective. In the grid-dip meter this is not a point of great advantage, but in some types of test gear, such stability of the heater supply confers considerable benefits.

The value of the capacitance required may be calculated from the formula:
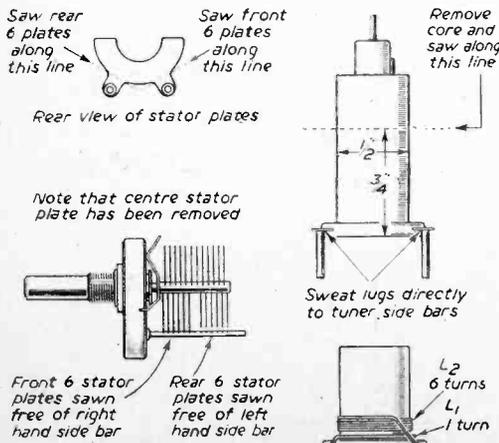
$$C = \frac{I_h \times 10^6}{2\pi f \sqrt{V_s^2 - V_h^2}}$$



Figs. 2 and 3.—Details of the condenser and coil modifications.

where C is the capacitance in microfarads,

I_h is the heater current of the valve chain,

V_s is the mains supply voltage and

V_h is the voltage drop across the heater chain.

The term $2\pi f$ may, for 50 c.p.s. mains, be taken as equal to 314.

In the present case I_h is 0.15 amp. and V_h , taking into account the Brimistor whose final operating resistance is of the order of 100 ohms, is approximately 21 volts (6.3 volts for the valve heater plus approximately 15 volts dropped across the Brimistor. The Brimistor, when cold, has a resistance of about 3,000 ohms, so that when the circuit is first switched on the valve heater draws very little current at all. The Brimistor rapidly heats up, however, its resistance falling as it does so, until the valve is drawing its correct current).

Logarithmic working of the formula gives the value of capacitance required as 2.085 μ F but a 2 μ F capacitor will serve in the present circuit. If possible, the component should be bridge checked, for its value should not be much higher than the calculated figure otherwise the valve heater may be overrun. In the original model the capacitance of the component proved to be rather lower than the 2 μ F marked on the can, so that the valve heater was found to have only 5 volts across it. Nevertheless, the circuit worked well so that no adjustment was made; in this case the low H.T. potential made it possible to underrun the valve heater without bad effects, though it must be remembered that as a general rule underrunning of a valve heater is as bad as overrunning.

The term in the bottom line of the right-hand side of the equation, $\sqrt{V_s^2 - V_h^2}$, gives the R.M.S. voltage across the terminals of the capacitor—in this case practically the full mains supply taking the supply voltage as 230 volts. The capacitor, therefore, must be chosen with care not only from the point of view of correct value, but also for its ability to withstand A.C. operation. The D.C. rating of the component should be at least 500 v.w. and preferably 1,000 v.w. and if there should be any doubt about the component it should be tested in an equivalent circuit for a long run, using a 120 ohms 5 watt resistor in place of the valve heater and Brimistor. The mains supply line to such a test circuit should be well fused. Remember that a paper capacitor MUST be used, never an electrolytic component.

Construction

It was required not only that the unit should be small and compact, but also that it should be cheap to construct, and for that reason no special parts were obtained, everything being drawn from the spares box. The meter movement was taken from an 0.5 amp. thermo-couple meter whose thermo-couple had seen better days. The meter was stripped down, due care being taken with the delicate pointer and bearings in

LIST OF COMPONENTS

- | | |
|---|--|
| L1—1 turn 26 S.W.G. rubber or polystyrene covered wire. | C4—8 μ F 350 v.w. El |
| L2—6 turns 28 S.W.G. enamelled wire, close-wound and touching L1. \dagger Windings on adapted Aladdin $\frac{1}{2}$ in. former. | C5—2 μ F 500 or Paper Mansbridge |
| R.F.C.—40 turns 32 S.W.G. D.S.C. wire, close-wound on Erie Type 8 33 K Ω resistor. | R1—10,000 ohms, $\frac{1}{2}$ W |
| C1—Adapted 100 pF J.B. C804 Air Tune tuner, or normal 50-0.50 pF split stator. See Text. | R2—33,000 ohms, $\frac{1}{2}$ W |
| C2—25 pF S.M. 350 v.w. | R3—4,700 ohms, $\frac{1}{2}$ W |
| C3—220 pF S.M. 350 v.w. | Brimistor—CZI. |
| | Rec. 1, 2—SenTer rectifiers. |
| | T1—Midget 5 : 1 Ω former. See Text. |

order that these should not be knocked, and the thermo-couple was removed from the meter base (the movement being placed under its cover during this operation in order that no dust or metal filings should fall into the gap). The meter movement was then re-mounted on its baseplate, its two leads being taken to the original thermo-couple mounting blocks and sweated to these to connect the movement directly to the external terminals.

The scale was then removed from its mountings, the two limit stops on their screws being handled by tweezers, and a piece of fairly thick white paper was cemented down on the scale face by rubber solution (bicycle tyre repair solution is perfectly satisfactory). When the solution was dry the paper was trimmed round the scale with a very sharp razor blade, the scale then having a new and unmarked surface. On this, with draughtsmen's bows, was drawn in India ink a new scale arc to suit the pointer length, the arc not being calibrated in any way but left blank. Below the arc the scale was lettered "TV Grid-dip Meter" to relieve the plain whiteness of the meter face. The scale was remounted, the limit stops being adjusted for the correct pointer travel, the cover was cleaned and the meter re-assembled, not forgetting a check on the zero-correcting pip before the cover screws were replaced. It remained to check the polarity of the meter terminals and to ascertain the sensitivity of the movement—this was found to be approximately 2 mA.

It would be possible, of course, to employ any meter with a sensitivity of 2 mA or better in this instrument, and many constructors will probably have surplus 1 mA meters which they will wish to use. It will almost certainly be necessary to place a small shunt resistance across a 1 mA meter, if used in this circuit, to bring the pointer off the full-scale stop, but such a shunt can soon be made of a small resistance or length of resistance wire. If the 1 mA meter has a common resistance of 100 ohms or thereabouts, the required shunt need be no more elaborate than a 220 or 150 ohm resistor, chosen by trial and connected directly across the meter terminals. It is repeated that it is only necessary to bring the meter pointer to any convenient position on the scale arc, preferably near the full-scale reading point, so that a dip in the reading can be seen immediately.

A somewhat unelaborate metal case had already been chosen for the instrument, which was to be housed in a large Rowntree's cocoa tin, and it was found that when the power supply components and the meter, together with the two switches, were housed in the tin, little room was left for the oscillator itself. This was accordingly mounted on the lid of the case and connected to the rest of the circuits by leads of sufficient length to allow the lid to be withdrawn well clear of the tin. Remember, when such a form of construction is used, that the lid must be bonded by a length of flex to the main case.

Some little ingenuity was required so far as the split-stator tuning capacitor was concerned. A split-stator component with an earthed rotor was essential for the complete avoidance of hand-capacitance effects, and no component of that type possessed by the writer would fit the available space. Finally a split-stator tuner was made from an ordinary 100 pF ceramic-mounted variable capacitor of the Jackson Bros. Air Tune C804 type, as shown in Fig. 2. In this tuner the stator plates are supported on two side rods and the 100 pF capacitor

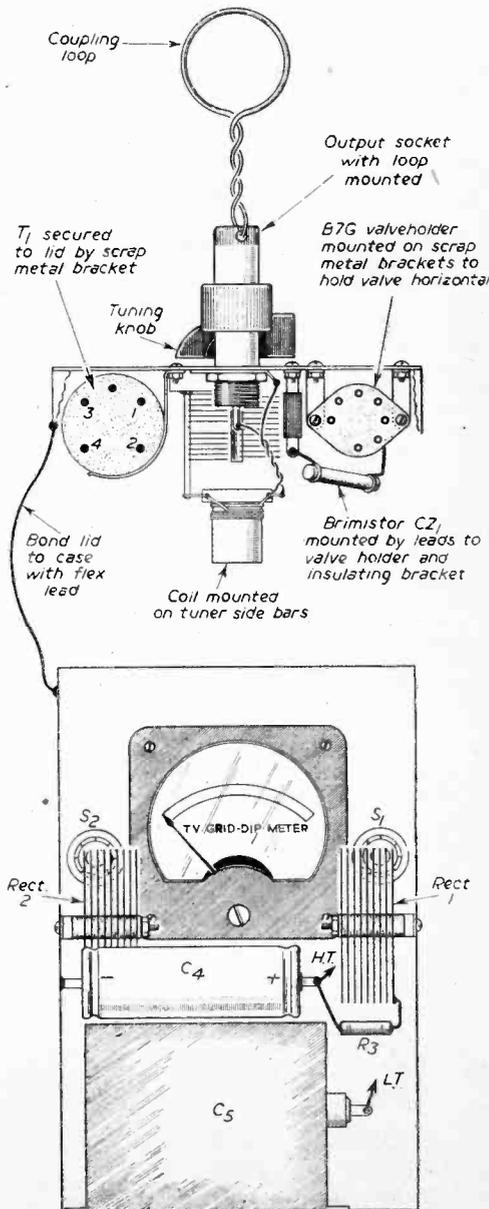



Fig. 4.—Pictorial layout of the unit.

COMPONENTS

- electrolytic. M—2 mA moving coil meter or 1 mA etc.,
- 1,000 volts working. shunted. See Text.
- type. V1—9002 triode.
- 1 watt. 1 B7G valveholder, small size (paxolin
- watt. preferred).
- att. S1, S2—On-off switches, toggle or push.
- Cel RM1 selenium 1 Belling-Lee co-axial socket and plug.
- Insulated wire loop.
- r 2 : 1 audio trans- 1 Pointer knob.
- Case, card, nuts, bolts, etc.

The "ARGUS"

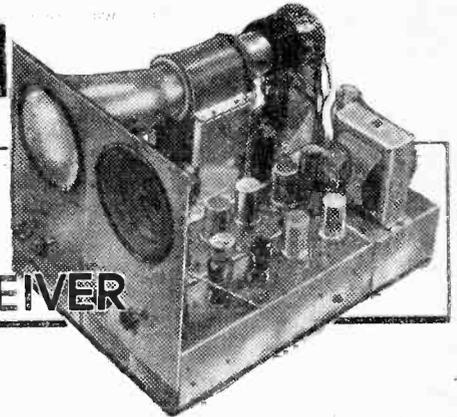BUILDING OUR Free Blueprint TELEVISION RECEIVER



4.—FINAL DETAILS AND A LIST OF SUPPLIERS AND PRICES

NOTE:—Reprints of the Blueprint and instructions are now available for 2/6 each.

AMONG the various queries received on this receiver the most common was undoubtedly, "Can you tell me where I can get the parts for the 'Argus' at the price quoted?" Some readers even went so far as to challenge the cost given in the opening article, and in one case a trader is reported to have said it was impossible to obtain the parts for anything like the price given and suggested that it would cost at least double.

In order to satisfy those readers who are in doubt on this question we give below a full shopping list of the parts which were obtained for the prototype, and it will be seen that the firms are all advertisers in these pages or those of our companion paper *Practical Wireless* and, in fact, most of the items were obtained as a result of their advertisements.

56	100 pF	5½	Alpha Radio
57	100 pF	5½	Alpha Radio
58	0.30 pF	10	Alpha Radio
59	.005 pF	5½	Alpha Radio
60	.01 pF	4½	Alpha Radio
VR4	2 M.	2 0	Willetts, W. Bromwich, Staffs
VR5	2 M.	2 0	Willetts
VR6	25 K., 2 w.	1 0	Alpha Radio
R43	2 w.	1 0	T.R.S., Croydon, Surrey
R47	2 w.	1 0	T.R.S.
6 V holders	at 4d. ea.	2 0	T.R.S.
14 Res.	½ w. at 6d. ea.	7 0	T.R.S.
9 Res.	1 w. at 8d. ea.	6 0	T.R.S.

£1 12 8½

VISION RECEIVER

	£	s.	d.	
7 Coil former.	4	1		Alpha Radio
18 500 pF condensers at 5½d. ea.	8	3		Alpha Radio
8 others at 9d. ea.	6	0		Radioelectron, 22, Frances Street, Scunthorpe.
18 Res. at 6d. ea.	9	0		Alpha Radio
VR1 (2 KΩ in lieu of 2.5 KΩ)	1	0		Alpha Radio
5 V holders	2	6		Alpha Radio
1 V holders (EA50)	4			Alpha Radio
	£1	11	2	

SOUND RECEIVER

	£	s.	d.	
C27	500 pF	5½		Alpha Radio
C28	500 pF	5½		Alpha Radio
C29	500 pF	5½		Alpha Radio
C30	500 pF	5½		Alpha Radio
C31	35 pF	9		Radio Mail
C32	.01 pF	4½		Alpha Radio
C33	.001 pF	4		Radio Mail
C34	25 pF 12 v.	1 3		Alpha Radio
C35	.5 pF	4½		Alpha Radio
C36	.5 pF	4½		Alpha Radio
C37	.05 pF	4½		Alpha Radio
C38	50 pF 25 v.	1 3		Electrolab Radio, Belfast
C39	.001 pF	4½		Radio Mail
12 at ½ w. at 6d. ea.	6	0		T.R.S.
2 at 1 w. at 8d. ea.	1	4		T.R.S.
VR2, 2.5 K (or 2 K.)	1	0		Alpha Radio
VR3 500 K.	1	9		Alpha Radio
Loudspeaker	12	11		Radio Supply
L/S transformer	3	11		Radio Supply
6 V holders at 6d. ea.	3	0		Alpha Radio
1 EA50 V holder	4			Alpha Radio
3 Coil forms. ½ with cover	1	9		Alpha Radio
3 Trimmer, 0.30 pF	2	6		Alpha Radio
	£2	1	9½	

TIME BASE

	£	s.	d.	
C40	.01 pF	4½		Alpha Radio
41	.1 pF	4½		Melluish, Totworth, Surrey
42	.1 pF	4½		Melluish
43	.5 pF	4½		Alpha Radio
44	.05 pF	4½		Alpha Radio
45	.1 pF	4½		Benson, 308, Rathbone Rd., Liverpool
46	8 pF	1 9		Sussex Electrical, Brighton
47	.1 pF	4½		Melluish
48	.1 pF	4½		Melluish
49	.001 pF	4½		Radio Mail
50	.001 pF	4½		Radio Mail
51	.1 pF	4½		Melluish
52	50 pF	9		Radio Electric
53	50 pF	9		Radio Electric
54	.1 pF	4½		Melluish
55	.1 pF	4½		Melluish

C.R.T. NETWORK AND E.H.T.

	£	s.	d.	
C61	.03, 2.5 Kv. (nearest equivalent .02, 5 Kv.)	1	6	Benson
C62	0.1, 2.5 Kv.	2	6	Benson

PREMIER RADIO CO.

(REGD.) B. H. MORRIS & CO. (RADIO) LTD. ESTAB. 40 YEARS

This is our only address : (Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

OPEN TILL 6 P.M. SATURDAYS
 TERMS OF BUSINESS:—CASH WITH ORDER OR C.O.D. OVER £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

BALANCED ARMATURE LOW RESISTANCE HEADPHONES, Type 1, 5/11 pair. Type 2, 8/11 pair.

HIGH RESISTANCE HEADPHONES, 12/6 pair.

LIGHT-WEIGHT HIGH RESISTANCE HEADPHONES, 14/6 pair.

BRAND NEW R1155 RECEIVERS, in original cases, complete with 10 valves, £12/10/0. 7/6 Packing and Carriage.

BATTERY CHARGER KITS. All incorporate metal rectifiers. Transformers are suitable for 200/250 v. A.C. 50 cycle Mains.

Cat. No.
 2002 Charges 6 volt accumulator at 1 amp. Resistance supplied to charge 2 v. accumulator £1 2 6

2003 Charges 12 volt accumulator at 1 amp. £1 7 6

THREE PIECE AERIALS.—Brand New. 12ft.—3 4ft. screw-in sections of copper-plated steel, highly flexible with non-stick screw jts., tapering 1/4in. to 1/8in. Brand new in container. 6/9. Also plug-in type, 3/9. Packing and carriage 1/6. Insulated Base, 2/6.

GERMANIUM CRYSTAL DIODES, wire ends, midjet size. The Ideal Crystal Detector. G.E.C. or B.T.H. 4/6 each.

METAL RECTIFIERS—FULL WAVE, 6 v. 1 amp., 4/-; 12 v. 1 amp., 8/-; E.H.T.

Pencil Type—Output: 650 v. 1 mA., 4/7 each; 1,000 v. 1 mA., 6/- each.

CRYSTAL MICROPHONE
 An entirely insulated crystal microphone which can be safely used on A.C./D.C. amplifiers. High impedance. No background noise, really natural tone. The ideal Mike for tape, wire and disc recording and sound projectors. Price 22/6.

MAINS NOISE ELIMINATOR KIT. Two specially designed chokes with three smoothing condensers, with circuit diagram. Cuts out all mains noise. Can be assembled inside existing receiver. 6/- complete.

T.V. WHITE RUBBER MASKS (CORRECT ASPECT). We can supply a specially designed White Rubber Mask for 6in. C.R. tubes at 18/6 each. 9in. White Masks, 9/6. 12in. White Masks, 16/11. For Round or Flat faced Tube.

BURGONEV SOLDER GUNS, 75/-

V.C.R. 97 C.R. TUBES

We are once again able to offer this famous tube with the usual PREMIER guarantee of a full screen picture, free from cut-off. Every tube is television picture tested before despatch.

£2. 5. 0
 Plus 5/- postage, packing and insurance.

NEW BABY ALARM KIT
 A tremendously improved and re-designed version of the famous Premier Baby Alarm Kit, consisting of a Kit of Parts in Plastic Cabinet to construct a device to enable Baby's cries, or even breathing to be heard in any selected room in the house. Consists of a 2-valve amplifier (A.C. mains-operated 200/250 volts), with a Midget Telephone used as a Microphone. A 3in. Loudspeaker is now incorporated in the kit which together with other improvements in the design have resulted in tremendously improved sensitivity and quality of reproduction. May be left permanently connected. Extra Microphones in different rooms may be used without impairing the efficiency of the Unit.

The lead from Microphone to the Unit may be up to 60 ft. in length. Complete with Valves, Circuit and Instructions. 69/6. Already built and tested. 79/6. plus 2/6 pkg./carr.

PREMIER SUPERHET COILS, 16-50, 180-550, 800-2,000 metres. Set, with circuit, 10/6.

EX-U.S.A. U.H.F. AERIAL, with untuned detector stage consisting of VR92 valve, etc. Brand new in carton, 5/-.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. All parts to construct an eliminator to give an output of 120 volts at 20 mA., and 2 volts to charge an accumulator. Uses metal rectifier. £2.

IMPORTANT ANNOUNCEMENT : We cannot accept responsibility for, or guarantee, any kit or component sold as a Premier product by firms other than ourselves. All prices quoted are those ruling at the time of submitting advertisement copy, and are subject to alteration without notice.

TALLON CABINETS

for the

VIEW MASTER
 ELECTRONIC ENGINEERING &
 PRACTICAL TELEVISION SETS
 MINI-FOUR • ARGUS

In pack-flat kits or assembled cabinets. Radiogram, Radio and Television or combination cabinets made to suit customer's requirements, in quantities or singly. Tape Recorder Cabinets.

Prices and literature on application

JAMES TALLON & SONS LTD.

(Dept. P.T.I.)

MANOR WORKS • MANOR ROAD
 RUGBY

Telephone : RUGBY 2070

faithful reproduction

from 50 c/s to 10 Kc/s at 7½ in/sec using



High-quality recorder reproducers demand high-quality tape to produce results that will satisfy the discriminating listener.

"SCOTCH BOY" MAGNETIC TAPE HAS:

- High, uniform sensitivity
- High fidelity at low speeds
- High signal/noise ratio
- Medium coercivity, easy erasure
- Low distortion and transfer
- Special cellulose acetate base giving strength and durability.

in 1200', 600', 300' reels and other sizes.

If you want advice on any tape-recording problem, our entire technical knowledge is at your disposal.

MINNESOTA MINING & MANUFACTURING Co. Ltd
 167 Strand, London, W.C.2. Telephone: TEMple Bar 6363

**"YOU CAN RELY ON US"
FOR CLEAN COMPONENTS
AT COMPETITIVE PRICES
48 HR. SERVICE AGAIN**

T.V. EHT UNIT

6-9 kv. fully enclosed in louvered metal box, well smoothed, 128V. Coil Only, fully wound on Polystyrene former, 39/-, Leaflet available.

VALVES

CIC	...	10/-	5Z3	...	10/6	77	...	7/6
CV1141	...	5/-	12AT7	...	10/6	12SQ7	...	8/-
DH63	...	12/-	6AG5	...	9/6	954	...	5/-
EA50	...	3/6	6AK6	...	8/6	955	...	8/-
KTZ11	...	7/6	6B8	...	8/-	VU111	...	7/6
EF39	...	10/6	6C4	...	7/6	3525	...	12/6
EF50	...	7/6	6C5m	...	7/6	3524gt	...	12/6
EF54	...	7/6	6C6gt	...	7/-	6K3gt	...	12/6
3D6	...	6/-	6H6m	...	4/6	6B5	...	12/6
EL32	...	8/-	6J5gt	...	6/6	KT61	...	10/6
EL35	...	10/6	6J7G	...	9/-	KT41	...	10/6
KTW61	...	8/6	6K6	...	8/6	KT63	...	10/6
KT33C	...	10/-	6K7 metal	...	8/-	KT66	...	12/6
MS/Pen	...	7/6	6K7G	...	8/-	6J5M	...	7/-
N37	...	10/6	6L7 metal	...	8/6	6ACTM	...	8/6
Pen46	...	8/-	6SA7gt	...	8/-	6BW6	...	15/-
PT25H	...	5/-	6SH7 metal	...	7/6	6AT6	...	10/6
U78	...	10/-	12SF7	...	7/6	50C5	...	13/6
VU120A	...	4/6	12SF7	...	7/-	5130	...	7/6
1Q4	...	8/6	12SC7	...	7/-	12K3	...	9/-
1S4	...	10/6	12SG7	...	6/-	7C5	...	8/6
3A4	...	7/6	12SK7	...	8/-	UB41	...	8/6
3Q5gt	...	8/6	12SR7	...	6/6	VR116	...	3/6
354	...	10/6	78	...	6/-	1W4 350	...	10/-

Postage 6d. any quantity.

2.5 kv. Transformer 5m/A. 2-0.2v. at 4a. 4v. at 2a. New 35/- SWITCHES.—Rotary : 4 pole, 4 way, 3 pole, 3 way, 4/-; 3 pole, 4 way, 4/-; 2 pole, 6 way, 4/-; 6 pole, 3 way, 4/6.

SELENIUM RECTIFIERS.—36EHT50, 22/6. 36EHT45, 20/6. Type 14D36, 10/6. Type 14A86, 18/6. Type 36EHT100, 27/10. WX3, 3/5. WX6, 3/5. 12v. 5 m.a., 1/-; 36EHT40, 20/6A.

EASYBUILT CHASSIS.—Two chassis for the Easybuilt Television, heavy gauge tinplate soldered four sided, 8/6 each. 3in. x 3in. screens, 6d. Ask for complete list of parts.

SPEAKERS.—2in. WB, 17/3. 6in. Elac, 15/-; 3in. Elac, 14/3. 5in. Plessey, 14/9. 5in. P.M. 15/-; Plessey 5in. M.E., 1,000 field, 15/-; Plessey 10in., 21/-.

HAYNES COMPONENTS.—Scanning Coil Units. Type S914, S27, 45/-; S914H, S112, each, 42/-; Transformer TQ135, 17/6. Choke Type LUS6F, 22/-; LUS6L, 16/6. TQ132, 12/-; TK1041, 38/-; Kit Coil Cans, Formers and Wire, 17/6 set of 10.

SPANNERS.—4 B.A., 6d. Five for 2/-; Box type, set of three Flat Type, 2 B.A., 4 B.A., 6 B.A., 1/-.

FILAMENT TRANSFORMERS.—Midget dimensions, finished in green crackle. Primary 210/240 v. to 6.3 v. 1.5 a. 3/6; to 6.3 v. 3 a. 12/6; Multi purpose type for instruments, models, etc., tappings 3 v. to 30 v. at 2 amp., 24/-.

SPEAKER TRANSFORMERS.—Super Midget for personals. DL92, 3S4, 1S4, 5/-; Standard Pentode, 4/6; 60:30:90: to 1, 6.6. 30:1, 4/-; Mains Pentode Midget, 4/-.

COILS.—Wearite "P" Coils 3/-; Wearite Viewmaster coils, per set, London, 20/-; Midland, 28/-; Holme Moss, 30/-; MWLW TTF Matched pair with circuit, 7/6. Weymouth CT3W3, 9/6 pair. CS2W2 11/6 pair. K.O. Coils, 4/9. "H" Coils, 3/3.

I.F. TRANSFORMERS.—RS/GB Semi-Midget 465 kc/s, 12/6 pair. Wearite M800, 21/- pair. Weymouth P4, 15/- pair.

FORMERS.—Aladdin with cores, 1in., 7d.; 1in., 10d.; 1in., 9d. Cores, 1in., 3d.; 1in., 4d.

BOOKS.—Viewmaster Book and Circuits, 5/-; London or Midland Easybuilt Television, 2/6; Portable Television, 3/-; Personal Portables, 2/6.

MISCELLANEOUS.—Bulgin Octal plug, 2/3. Belling-Lee Co-axial plug, 1/6. Socket, 1/6. Connector, 1/6. Bulgin rotary DP Switch 4/3. Bulgin feeder plug, 1/3. Socket, 1/3.

ELECTROLYTICS.—2 mfd. 50v. 1/3. 4 mfd. 350v., 1/6. 16-16 mfd. 450v., 7/6. 8 mfd. 500v., 3/6. 16 mfd. 450v., 4/6. 16 mfd. 350v., 3/-; 25v. 16. 80 mfd. 50v., 2/6. 8 mfd. plus 8 mfd. 500 v., 4/3. 25 mfd.

CHOKES.—First quality Audio Chokes, high impedance, 10/6. 40 m.a. Midget, 5/-; 60 m.a., 6/6. Smoothing Chokes.

MAINS DROPPERS.—3 a. 800 ohm, 5/6. Midget Type, 6/3; 2 a. 950 ohm, 5/6. Midget Type, 6/3.

LINECORD.—3 way 2 a. 100 ohm per foot, 8d. per foot; 3-way 3 a. 60 ohm per foot, 8d. per foot.

Our No. 11 Catalogue, price 6d., Post Free. Postage: Over £2 free, below 10/-, 9d.; £1. 1/-; £2, 1/6.

RADIO SERVICING CO.

444, WANDSWORTH ROAD, CLAPHAM, LONDON, S.W.8.

Telephone MACaulay 4155. 77, 77A, 168, 169, Buses. S.R. Station: Wandsworth Road. Open till 6.30 p.m. 1 o'clock Wednesday.

CLYDESDALE
Bargains in Ex-Services Radio and Electronic Equipment

FOR INEXPENSIVE TELEVISION

THE R.3601 RECEIVER UNIT
A 15 Valve (6V6, WU39A, 4 SP61, 4 EA50, 2 EF54, EF50, EC52, VU111) dual chassis radar receiver for 220 mc/s. with 13 mc/s. I.F. Strip R.F. Section, high cycle power section, antenna switch, relay, etc., etc.. In metal case 18 x 9 x 8 ins.
CLYDESDALE'S £4. 12. 6 CARRIAGE PAID PRICE ONLY

R.3170A RECEIVER UNIT
A 13 Valve (2 EF54, EC52, 8 EF50, 2 EA50, CV189, 5Z4G, VU111) Radar Chassis with 30 mc/s. I.F. Strip, etc., original range about 200 mc/s., suitable for T.V. Conversion. In metal case 18 x 9 x 8 ins.
CLYDESDALE'S £4. 12. 6 CARRIAGE PAID PRICE ONLY

INDICATOR UNIT TYPE 6
In maker's original case. Containing a VCR87 Cathode Ray Tube with mu-metal screen. 4 VR91's (EF50), VR54 (EB34) 3 VR62's (EASO) VR78(D1), various w.w. pots., switches, H.V. Conds., Resistors, etc., built in metal chassis to fit into metal box 18 x 8 1/2 x 7 1/2 ins. All controls are brought to front panel beside viewing screen.
CLYDESDALE'S £4. 9. 6 CARRIAGE PAID PRICE ONLY

NEW LIST OF EX-SERVICE ITEMS No. 511. Now ready. Priced 1/6. Price credited on purchase of 10 - value or over.

70-80 ohm CO-AXIAL CABLE. 5 mm. dia. 7/0076 Centre, polythene insulation, ideal for T.V. Aerials. Minimum order 10 yds. Price.....1/3 per yard. or in 100-yard Coils. Price.....£5 per coil.

THE DATA BOOK No. 4. (Revised and enlarged.) 2/6 each.

Order direct from:
CLYDESDALE SUPPLY CO. LTD.
2, Bridge St., Glasgow, C.5. Phone: SOUTH 2706/9
Visit our Branches in Scotland, England and N. Ireland.



THIS FREE 104 PAGE BROCHURE

describes the Courses of Training offered by E.M.I. Institutes—the only Postal College which is part of a world-famous Industrial Organisation.

- Aero. Eng. • Motor Eng. • Draughtsmanship • Elect. Eng. • Prod. Eng. • Management Languages • Refrigeration Eng. • Civil Service • General Cert. of Education • Radio, TV and Electronics • University Training • Maths. • Mech. Eng. • Heating and Ventilation Eng. • Public Speaking • Police • Telecommunications, etc., etc. • Special Courses for A.M.I.Mech.E., A.M.I.C.E., A.M.I.P.E., A.M. Brit. I.R.E., A.F.R.Ae.S., City & Guilds Examinations, etc.

E.M.I. Institutes
associated with MARCONIPHONE COLUMBIA H.M.V. ETC.

COURSES FROM **£1** PER MONTH

Post this for a FREE copy of "Successful Careers" to E.M.I. Institutes, Dept. 138, 43 Grove Park Road, Chiswick, London, W.4.

Name.....
Address.....
I.C.9

Pioneers of Television

4.—CAMPBELL SWINTON, AND THE PRINCIPLE OF MODERN TELEVISION

IT is a curious fact that the electrical ingenuity of Campbell Swinton, the London experimenter, enabled him to put forward a working scheme for television transmission and reception long before the notion was ever submitted to the test of practical trial. Indeed, Campbell Swinton was in reality a television pioneer, a television inventor who hit upon the idea of a really practical television system without ever going to the trouble of constructing a television set of his own design. And, rather sadly, this pioneer died within a couple of years of the inception of commercial and nation-wide television practice in America.

Readers who have a good reference library available will be able to study Swinton's now historic scheme for television at first hand, and at their leisure if they so desire, for in the issue of *Nature*, dated June 18th, 1908, there appears an important letter, the writer of which makes the suggestion that the problem of electrical vision could be solved by using two cathode-ray tubes, one at the transmitting and the other at the receiving end of the system. The letter continues:

"The real difficulties lie in devising an efficient transmitter, which, under the influence of light and shade, shall sufficiently vary the necessary alterations in the intensity of the cathode beam of the receiver, and, further, in making this transmitter sufficiently rapid in its action to respond to the 160,000 variations per second that are necessary as a minimum.

"Possibly no photo-electric phenomenon at present known will provide what is required in this respect, but should something suitable be discovered, distant electric vision will, I think, come within the region of possibility."

"A. A. Campbell Swinton."

Here, clear enough, we have the first glimmerings of the modern tele-transmitter and televisor, both operating electronically through the agency of cathode-rays.

Prophetic Details

In November, 1911, Campbell Swinton greatly augmented his notions of television possibilities and practicabilities during the course of a Presidential Address which he gave before the members of the London Röntgen Society. This speech may be followed in detail in the pages of Volume VIII of the above society's *Journal* which was issued in the year 1912. It is a remarkable Address, containing, as it does, all the fundamentals and even some of the details inherent in our present-day system of television working. Swinton, at that time a highly-active and utterly indefatigable electrical engineer in business practice, and well known among London technical circles, had actually (and as early as 1908) hit on the notion of a transmitting cathode-ray screen on which the image to be televised was optically projected and rapidly scanned by an ultra-fast moving pencil of cathode-rays, controlled by electro-magnetic influence. Additionally, Swinton had allowed for a similar cathode-ray tube in the television receiving equipment, the cathode-ray beam in the receiving tube being synchronised with that in the transmitting tube and thus giving rise to like variations of light, shade and image-motion on the screen of the receiving tube.

But Campbell Swinton was a more than usually active man at that period. Seemingly, he was quite content to

establish his televisionary schemes on paper and allow others to do the practical and the detailed experimental work. He never attempted to construct for himself a working model of his proposed system. All he said was "It's an idea only. I do not suppose that it could be got to work without a great deal of experiment and probably much modification."

He was, indeed, correct in this assertion. Nearly a quarter of a century had still to elapse before the first cathode-ray television system was successfully operated by Vladimir Zworykin and others in America. Yet Swinton was not alone in his predictions. About the same time a certain Professor Boris Rosing, under whom Dr. Zworykin had originally studied at St. Petersburg, put forward a similar scheme to Campbell Swinton's, although it can now be proved that it was Swinton who was first in the field with his published notion for televising views and images. Thus it must be that Swinton must justifiably be given chronological priority over Rosing in this most important matter of television development.

A London Scotsman

Alan Archibald Campbell Swinton (the surname is not a hyphenated one, although nowadays there is a tendency to designate it as such) may be described as being almost a Londonder, for he spent the whole of his working days in or around London. His father was a Scotsman, one Archibald Campbell Swinton, who was Professor of Civil Law in the University of Edinburgh. The younger Campbell Swinton was born on October 18th, 1863. He was sent to his first school in Edinburgh and from those immature days he invariably showed a strong inclination to experimental and mechanical science. There is in existence an old oil painting of the lad Swinton which was exhibited at the Royal Scottish Academy's Exhibition of 1873, and which was labelled "The Young Engineer." It shows the boy proudly holding up a small but rather complicated steam engine of his own making.

During these Edinburgh days Swinton was fortunate enough to come under the care of a headmaster who was sufficiently enlightened to encourage him in his mechanical tastes and abilities. He allowed the lad to give school magic-lantern exhibitions of his own designing in which he was wont to demonstrate to the assembled audience the then extremely popular art and trick of manifesting on the screen the ingenious system of "dissolving views." Swinton, at this time, took up photography for the purpose of making his own lantern slides. Soon it became a favourite hobby to him, and remained as such throughout the rest of his life.

The First Telephone

Graduating to a more senior school, Swinton encountered unfortunate circumstances. He began to hate the normal routine of school subjects. He disliked his school-fellows, his teachers, his circumstances. In all, it proved to be a period during which he was continuously unhappy. In 1879 he happened to be present at a lecture-demonstration on the subject of the telephone which had been invented a couple of years before. Returning to school, Swinton, within a week, succeeded in constructing "for himself, and with an absolute mini-

num of electrical knowledge, a telephone transmitter and receiver, and he astonished his housemaster by successfully operating it within the school buildings. But the school powers came down severely on him and made him remove the new-fangled invention on the score of its interfering with his classical studies and with his general application to school work, Swinton being some fifteen years of age at this juncture.

Two years later—in 1881—Swinton was sent to Le Havre, in France, to finish his schooling, and, in particular, to study French and mathematics. Whilst in that town he saw for the first time in his life a large dynamo of the then popular De Meritens type, which was producing current for a local lighthouse. The generator was equipped with steel permanent magnets, and the lighthouse-keeper was having trouble with it. Swinton examined the generator and at once detected the cause of the trouble. He remedied it almost instantly, and, in so doing, he resolved to devote his career to the electrical industry, a decision which was soon afterwards confirmed in his mind when he visited the Paris Exhibition of 1881 and became greatly entranced by the numerous electrical exhibits which he was then able to view and to examine at close working quarters.

Five Years an Apprentice

Returning from France in 1882, young Swinton began a five years apprenticeship in the engineering works of Sir W. G. (afterwards Lord) Armstrong at Elswick-on-Tyne. It was, for him, a period of great activity for, on top of his now essentially practical studies, he found time to write a book on "The Principles and Practice of Electric Lighting," which, dealing with an entirely new subject, proved to be unexpectedly successful. The interest shown in this volume brought to him an added enthusiasm for the electrical side of the Armstrong business, and he began to be employed on the major electrical tasks which the firm undertook. Incidentally, it may be recorded that the apprentice Swinton, during those days, was the first to use lead-covered wiring in ships in place of the old silk-wrapped and surface-varnished cable which was then relied on in order to prevent the slow penetration of water.

A Move to London

In 1887, the year of Queen Victoria's golden jubilee, Swinton threw up his job at Armstrong's. Making a bold move, he went to London, convinced of his ability to set up successfully in his own business as an independent electrical consultant and contractor. Electric lighting was just coming into vogue and popularity. Swinton's idea was to commence business by specialising in the necessary wiring of the many country houses and landed properties around London which, at that time, were eagerly "going electric" for the first time in their history. In this work the enthusiastic and energetic Swinton was enormously successful. He added on other electrical aspects to his business, becoming, indeed, one of the very first of the really practical London "electricians."

The First X-ray

One morning, in the early January of 1896, Swinton read over breakfast a newspaper account of Professor Röntgen's discovery of certain new electrical "rays" which enabled an observer, as it were, to look into the flesh of the human or animal body and to see directly the bones thereof. Having in his possession an old Crookes high-vacuum tube, Swinton instantly repeated Röntgen's original experiment, and within a day or two

he was successful in producing an actual "shadow-graph," as he called it, of his hand. It was the first X-ray photograph to be produced in England. At once it was exhibited at the Camera Club in Charing Cross Road, London, and it was reproduced in *Nature* for January 23rd, 1896.

X-rays to Cathode-rays

From X-rays the step to cathode-rays is not a great one. Swinton was not slow to take such a step. Indeed, it was then an age of new electrical "rays" of various kinds, all of which were electronic in nature. Besides the spectacular Röntgen or X-rays there were the Lenard-rays, the Crookes-rays, Hertz-rays, vacuum-rays and, of course, the now well-established cathode-rays. Swinton it was who proved himself to be the British apostle of the cathode-rays, for it was he who experimented with them in a really practical manner and who discovered, among other things, the high-temperature effect set up in a tube by the focusing of these rays or electron-beams. The latter discovery led to a close investigation of the entire phenomenon of "electro-luminescence" or the effect of luminescence which is created on the screen of a cathode-ray tube when building-up the transmitted picture in a television set.

Turbine Development

A more versatile inventor and experimenter than A. A. Campbell Swinton would be hard to imagine. In addition to his many-sided electrical work, he was closely connected with Sir Charles Parsons in the latter's development of the early steam turbine and, in particular, with the design and construction of the first turbine-propelled vessel, the *Turbinia*, a torpedo-boat destroyer of 1897 which attained the then unheard speed of 33½ knots.

It was Campbell Swinton, the electrician, who, in 1896, first introduced a young Italian electrical inventor named Marconi to Sir William Preece, then Chief Engineer to the British Post Office Engineering Department, and who obtained for him permission to conduct certain experiments on signalling without wires which Marconi had enthusiastically in mind.

Not only did Swinton become Britain's first radiographer with his "electrical shadow pictures," but he found much time and energy to encourage and to preside at the introduction of a numerous variety of electrical applications. He was a member of the Institutions of Electrical, Mechanical and Civil Engineers, becoming vice-chairman of the former body. His lasting enthusiasm over the many forms of electrical "rays" brought him, in 1911, the Presidency of the then famous Röntgen Society which specialised in Röntgen or X-ray technology. Lastly, in 1915, the august Royal Society opened its door to him, admitting him as one of its Fellows in that year.

For all his honours and distinctions, academic as well as technological, A. A. Campbell Swinton was a very approachable, kindly and agreeable man. He gave many vital services to scientific endeavours. In a way, too, he was something of a philanthropist. And, when he died, unmarried, at his London residence, 40, Chester Square, on February 9th, 1930, some two years before his erstwhile cathode-ray system of television was first practicalised and tried out in America, the scientific world almost intuitively realised that an original and an intrepid electrical genius had departed, the like of which, for sheer versatility and creative, indefatigable energy, would probably not be available again for many years to come.

HENRY'S

"PYE" 45 MC/S STRIP. Special purchase of M.O.S. Type 3583 Unit, size 15in. x 8in. x 2in. Complete with 45 mc/s Pye Strip, 12 Valves, 10 EF50, EB34 and EA50: Volume controls and a host of Resistors and Condensers. Sound and vision can be incorporated on this chassis with minimum of space. New condition. Price £5, carriage paid.

FOUR SECTION CHASSIS adaptable for the "Argus" Television lay-out, 21" carr. pd.
CATHODE RAY TUBES. VCR97 Brand New. Guaranteed Full Pictures, 45" carriage paid; VCR139A. Brand New. Suitable for Scopes, 35" carriage paid; 3BP1. Brand New. Suitable for Scopes, 25" carriage paid.
9in. ESCUTCHEON. Brown Bakelite. Suitable Plate glass and Mask for 9in. Tube. Price 7/6 each.

INDICATOR UNIT TYPE 1182A. This unit contains VCR517 Cathode Ray 6in. Tube, complete with Mu-Metal screen, 3 EF50, 6 SP61 and 1 5U4G valves, 10 wire-wound volume controls and quantity of resistors and condensers. Suitable either for basis of Television (full picture guaranteed) or Oscilloscope. Offered BRAND NEW (less relay) in original packing case at 79/6. Plus 6/6 carriage.

★ **A COMBINED SIGNAL TRACER AND AUDIO OSCILLATOR** ★

An easy-to-build unit that can be used for I.F. and Audio signal tracing, without any switching or tuning, including variable output oscillator, for amplifier checking. Highly sensitive, responds to signals picked up from an ordinary receiving aerial. The circuit is that of a high-gain 2-stage, resistance-coupled audio frequency amplifier, employing 3 miniature 1.4 valves, with a 3-inch speaker in the output of the Power Amplifier Stage. An added advantage being that as this Unit is "All-Dry" it can be used with safety on A.C. or A.C. D.C. mains and Battery sets. The completed Kit with portable cabinet (size 6in. x 7in. x 6in.) and battery weighs only 4 lbs. We shall be pleased to supply a complete Kit for the construction of the above, right down to the last nut and bolt, including 2-1T4 and 1-1S4 Valves, 3in. Speaker and Portable case and All-Dry Battery for £4/19/6. Concise instructions and circuits supplied. If preferred, circuit and instructions only can be supplied for 1/6. If required this Unit will be assembled and tested for an extra charge of 15/-. This is a highly efficient instrument, and a MUST for every Radio man.

★ **SEND S.A.E. FOR 28**

WIRE WOUND VOLUME CONTROLS. (Colvern, Bakelite Cases). 200, 250, 750, 1,000, 2,000, 5,000, 10,000, 20,000, 25,000, 30,000. All standard 1in. spindle. 4/6 each.
SLIDER POTS. As used in all the latest T.V. sets. A bank of four, comprising two of 10K, 100 ohm and 500 ohm. Easily split up. The set only 6/-.
TELE-COLOR FILTERS. Enjoy the new vogue at a trifling cost. 9in. screens 11/9 and 12in. at 12/6.
RECEIVER UNIT TYPE 159. Containing VR91, VR92, VR65 and 24v. Selector Switch, New condition. 15/- (Post 1/6).
E.H.T. TRANSFORMER for VCR97. Input 230v. Output 2,500v. 4". 2/9.2. 45/-.
WALKIE-TALKIE TYPE 46. Containing 6 Valves, 2 of VP23, HL23/DD, QP25, TP25, ATP4, 2 I.F.T.'s 1.6 Mcs. Mike and Interval Trans. Aerial Rods, etc. Metal case, size 12in. x 6in. x 4in. In new condition but less transmitting components removed by the M.O.S. Price including carriage 35/-. Limited quantity.
GERMANIUM CRYSTAL DIODES, complete with full wiring circuit and diagram. 4/6.
STEWART TELEVISION MAINS TRANSFORMER. 350-0-350 at 250 m.a. 6.3 volts at 8-10 amp. 5 volt at 3 amp. 0-2-6.3 volts at 2 amp. Primary 0-210-230-250. Fully shrouded. FULLY GUARANTEED PRICE £4.
HEAVY DUTY FILAMENT TRANSFORMERS. 6.3 volts at 12/14 amp. Input 230 volts. 27/6d.


5 HARROW ROAD, PADDINGTON, LONDON, N.W.2. TEL: PADDINGTON 100819, 0401.

★ **PAGE CATALOGUE** ★

METAL RECTIFIERS. S.T.C. 300 volts, 75 m.a. 6/-; G.E.C. 6 volts, 1 amp. 4/-; Westinghouse 12 volts, 2 amp. 12/8; Pencil Type E.H.T. 900v, 1 m.a. 4/7; Pencil Type E.H.T. 1,000 v. 1 m.a. 6/-; 12v. 31 amp. 17/6.
G.E.C. 1 ma Meter Rect., 11/6.
EX-GOVT. Valves. THE FOLLOWING ARE BRAND NEW:—EF50 Red Sylvanian. Original Boxes (U.S.A.). 10/- English. Types. Original boxes, 8/6. EF50 Ex Units, Guaranteed, 6/-. At 8/6 each.—EF50, EF51, EF55, CV66, EFR, EFR36, EFR39, EK32, EL32, EBC33, 6K7GT, 6J7GT, 6L7GT, 6SK7GT, 6S7GT, 6B8GT, 6N7GT, 6J5GT, 6C5GT, 6A7GT, 6A7GT, 6S7GT, 6D6, 6C3, 12S7GT, 12S7GT, 12S7GT, 12S7GT, 12C8, 12S7GT, 12S7GT, 12A6GT, 14A7GT, 12Q7GT, 7A7GT, 7C7GT, 7H7GT, 7S7GT, 7B6GT, 41MP, 955, 9001, 9002, 9003, 9004, 1299A, 28D7, 9D2, 4D1, 15D2. RECTIFIERS AT 5/- each.—VU111, VU133, VU120A. At 8/6 each.—6X5, OZ4, 5Z4G, U50, 5Y3G. At 10/- each.—6BT, AC6PEN, MU14, 6AM6, 6V6GT, 5U4G, 6Z7, U52, 6A5, PEN46, 5R4, EFR1, 80. At 12/6 each.—12K8GT, 6K8G, KT3C, 6S7GT, 43, 6J6, 6L6, (1622 Metal), 6S17GT. Also at 11/-—35L6GT, 50L6GT, KT61, DI, 3/6; EAB1, EB34, 3/6; VR65 (SP61), 5/-; RL18, 5/-; 954, 5/-; 6H6, 5/-; S130, 7/6; VR150/30 and VR105, 8/6; PX25, 10/-; MS/PENB, 8/6.
ALL DRY BATTERY VALVES. 3V4, 1C5, 1T4, 1S5, 1R5, 1LN5GT, 1S4, 3S4, all at 10/- each. VP2, TDD2A, VP23, HL23/DD, all at 8/6. 2155G, KT2, PEN220A, 6/-; P2 (Super-power), 4/-; HIVAC HX, 7/6.

The new ARMSTRONG Television Chassis Model T.V.15

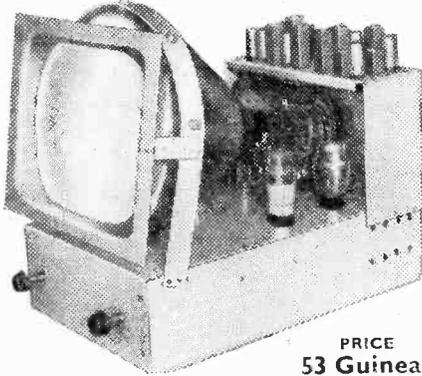incorporating a 12in. C.R.T., is now available for distribution



PRICE
53 Guineas
 TAX PAID

Also in production

The new **ARMSTRONG TELEVISION CHASSIS** Model T.V.17F for Fringe Area Reception (similar in appearance to the T.V.15). Price **£75.15.6 TAX PAID**

Please send for Radiogram and T.V. list, post free.

ARMSTRONG WIRELESS & TELEVISION, CO. LTD.,
 WALTERS ROAD, HOLLOWAY, LONDON, N.7.
 Telephone—NORTH 3213.



Whatever make or size your present Television set, there's a **MAGNAVISTA** Television Lens optically computed to suit it . . . bringing you larger, clearer, sharper pictures, and daylight viewing without turning up the brilliance control.

18 models—from £5.5.0. from your Radio Dealers.



A product of
METRO-PEX LIMITED
 42a DENMARK HILL,
 LONDON, S.E.5

RADIO SUPPLY CO. 15, WELLINGTON ST., LEEDS, 1.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/- charged on orders up to £1; from £1 to £3 add 1/6; over £3 post free. Open to callers 9 a.m. to 5.30 p.m. Saturdays until 1 p.m.

R.S.C. MAINS TRANSFORMERS

Fully Guaranteed, Interleaved, and Impregnated. Primaries 200-230-250v. 50 c/s Screened.

TOP SHROUDED, DROP THROUGH

260-0-260 v. 70 ma., 6.3 v. 2 a., 5 v. 2 a.	15/9
260-0-260 v. 80 ma., 6.3 v. 2 a., 5 v. 2 a.	15/9
260-0-260 v. 90 ma., 6.3 v. 2 a., 5 v. 2 a.	17/6
260-0-260 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a.	19/9
350-0-350 v. 90 ma., 6.3 v. 3 a., 5 v. 2 a.	21/9
260-0-260 v. 100 ma., 6.3 v. 4 a., 5 v. 3 a.	23/11
350-0-350 v. 100 ma., 6.3 v. 4 v. 4 a. C.T.	23/11
0-4-5 v. 3 a.	23/11
350-0-350 v. 120 ma., 6.3 v. 4 a., 5 v. 3 a.	29/11
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a.	29/11
350-0-350 v. 150 ma., 6.3 v. 2 a., 6.3 v. 2 a., 5 v. 3 a.	29/11

CLAMPED UPRIGHT MOUNTING

250-0-250 v. 80 ma., 6.3 v. 3 a., 5 v. 2 a.	18/9
250-0-250 v. 100 ma., 8.3 v. 6 a., 5 v. 3 a.	18/9
for 1355 conversion	26/9
350-0-350 v. 100 ma., 6.3 v. 3 a., 5 v. 3 a.	28/9

FULLY SHROUDED UPRIGHT

250-0-250 v. 80 ma., 6.3 v. 2 a., 5 v. 2 a.	17/6
Midget type 21-3in.	17/6
250-0-250 v. 100 ma., 0-4-6.3 v. 4 a.	25/9
0-4-5 v. 3 a.	25/9
300-0-300 v. 100 ma., 0-4-6.3 v. 3 a.	25/9
0-4-5 v. 3 a.	25/9
350-0-350 v. 70 ma., 6.3 v. 6 a., 4 v. 8 a.	18/9
350-0-350 v. 100 ma., 0-4-6.3 v. 4 a.	25/9
0-4-5 v. 3 a.	25/9
350-0-350 v. 150 ma., 6.3 v. 4 a., 5 v. 3 a.	33/9
350-0-350 v. 250 ma., 6.3 v. 6 a., 4 v. 8 a.	33/9
0-2-5 v. 2 a., 4 v. 3 a. for Electronic Eng. Television	67/6
425-0-425 v. 200 ma., 6.3 v. 4 a., C.T.	67/6
6.3 v. 4 a., C.T., 5 v. 3 a., suitable Williamson Amplifier, etc.	51/-
325-0-325 v. 20 ma., 6.3 v. 0.5 a., 6.3 v. 1.5 a. for Williamson Preamplifier	17/6

FILAMENT TRANSFORMERS

All with 200-250 v. 50 c/s Primaries: 6.3 v. 2 a., 7/6; 0-4-6.3 v. 2 a., 7/9; 12 v. 1 a., 7/11; 6.3 v. 3 a., 10/11; 6.3 v. 6 a., 17/9; 0-2-4-6-3 v. 4 a., 17/9; 12 v. 3 a., or 24 v. 1.5 a. ... 17/9

CHARGER TRANSFORMERS

All with 200-230-250 v. 50 c/s Primaries

0-9-15 v. 1.5 a., 14/9; 0-9-15 v. 3 a., 16/9	
0-9-15 v. 6 a., 22/9; 0-4-9-15-24 v. 3 a., 22/9	
0-9-15-30 v. 3 a., ...	23/9

SMOOTHING CHOKES

250 ma. 8-10 h. 50 ohms	16/9
250 ma. 3 h. 100 ohms	8/9
200 ma. 5 h. 100 ohms	7/6
100 ma. 10 h. 100 ohms	7/6
90 ma. 10 h. 100 ohms	5/9
80 ma. 10 h. 350 ohms	5/6

ELIMINATOR TRANSFORMERS

Primaries 200-250 v. 50 c/s. 120 v. 40 ma.

120-0-120 v. 30 ma., 4 v. 1 a.	7/11
40 ma.	12/9

OUTPUT TRANSFORMERS

Midget Battery, Pentode 66:1 for 354, etc.

Small Pentode, 5,000 ohms to 3 ohms	3/6
Multi ratio 40 ma., 90:1, 45:1, 60:1, 90:1; Class B Push-Pull, 4/9	5/6
Push-Pull 10-12 watts 6V6 to 3 or 15 ohms	15/11
Push-Pull 10-12 watts to match 6L6, 6X4, 6V6, etc. to 3-5-8 or 15 ohms	16/11
Push-Pull 15-18 watts to match 6L6, etc. to 3 or 15 ohm Speaker	22/9

NEW EX-GOV. VALVES, DI, 1/9

EA50, 954, VU120A, 2/9; 12H6 Met., 1/11; 92D, 2/11; 12SCT, Met. 6/5GT, 12SHT Met. 5/9; 6S7 Met. 6S57 Met. 6C5 Met. 12S7 Met. 12SR7 Met. 6/9; 6K7G, 6J7G, KT263, 12A6 MHLDe, 9/6; 5Y3G, EB91, 10/6; 607G, 12A6 Met. ECL80, EP80, 12/11; MSP4, 5/6; 6SL7GT, 11/9.

SPECIAL OFFERS. Mains Trans.

220-240 v. Primary, 6.3 v. 1.5 a., small 5/9
 Ex. Gov. Block Paper 4 mfd. 600 v. 2/9
P.M. SPEAKERS. All 2-3 ohms, 5in.

F.W. 11/9; 5in. Rola with Trans., 15/9; 6in. F.W. 13/11; 8in. Plessey 14/11; 8in. Rola, 17/6; 10in. Goodmans, 27/9; M.E. SPEAKERS, 8in. R.A. (2-3 ohms), Field 600 ohms, 12/9; 10in. Plessey (3 ohms), Field 1,000 ohms, 21/9.

VOL. CONTROLS (standard spindles). All values, less switch, 2/9; with S.P. switch, 3/11.

BROWN BAKELITE CABINETS (PREFMTC). Size approx 12-61-51in. Complete with punched (T.R.F.) Chassis, Coloured Station Named 2 or 3 wave Glass Dial, Drive Drum, Cord Drive Head, Nylon Cord, Spring, and Dial Backplate, 28/6. T.R.F. Coils, Combined L. and M. wave, with circuit, 6/6 pair.

SELENIUM RECTIFIERS Ex. New Equipment, 120 v. 40 ma. (small), 4/9; New 36 v. 50 ma., 11d. Bridge Type, 12 v., 21 a., 15/6.

MISC. ITEMS. Ex-Govt. (Tron) Chokes, 50 ma., 50 h., 1,000 ohms, 4/6; Philips Chokes, 90 ma., 8 h., 100 ohms, 4/6. Pye Coax Plugs and Sockets, 7/6 doz. pairs. W.W. Pots., 5 k., 20 k., 50 k., 2/9 each. Cream Masks, 9in. (slightly soiled), 6/9. Suitable Armour plated glass, 1/11. EF50 Valves (ex. New Equip.) perfect condition, 6/6. EF54, 5/9.

ELECTROLYTICS. Tubular 8 mfd. 350 v. 1/9; 8 mfd. 450 v. 2/3; Can 16 mfd. 450 v. 2/11; 8-8 mfd. 450 v. 4/6; 8-16 mfd. 450 v. 4/6; 12-12 mfd. 350 v. 3/3; 16-16 mfd. 450 v. 5/3; 32 mfd. 350 v. 4/3; 32 mfd. 450 v. 5/9; 32-32 mfd. 350 v. 6/6; 32-32 mfd. 450 v. 6/9; 32-32 mfd. 350 v. plus 25 mfd. 25 v. 5/6; 32-32 mfd. 350 v. 6/6; 50 mfd. 350 v. plus 250 mfd. 12 v. 4/3; 16-32 mfd. 350 v. 3/11.

FULL RANGE OF STANDARD COMPONENTS AVAILABLE AT KEEN PRICES. ALL GOODS GUARANTEED AND NEW, UNLESS OTHERWISE STATED. QUANTITY QUOTATIONS GIVEN FOR STANDARD TYPES OR SPECIALS. S.A.E. PLEASE WITH ALL ENQUIRIES. FULL STOCK LIST 4d. SPECIAL LIST FOR TRADE, 4d.

WENVOE CONVERSION

Type AC4 Converter unit for use with Sutton Coldfield receivers. Optimum picture detail and Sound reception without retuning or alterations. Incorporates power supply unit, R.F. stage and highly successful double mixer stage ensuring freedom from noise and correct reception of the new single side-band transmitters. Also available for Holme Moss on London type receivers. Price, complete with 5 valves, etc., 15 gns. C.O.D. if desired, or by arrangement with your Dealer.

The AC3 neutralized triode PRE-AMPLIFIER. A well designed and proved unit giving the best possible results for 'Fringe' and long distance viewers. Our confidence in the unit is revealed by our 7 days' approval offer. Price complete, 10 gns. C.O.D. if desired, or by arrangement through your Dealer. Illustrated leaflets and details, etc., available on request.

SPENCER WEST

Quay Works, Gt. Yarmouth
 Telephone: Gt. Yarmouth 3009.

NORMAN H. FIELD

68, HURST ST., BIRMINGHAM 5.
 Mail Order Dept.
 64-65, CHURCH LANE,
 WOLVERHAMPTON.

VALVES

At 12/6: 6K3; 6R4G; ECC32; 6SN7. At 11/6: 5Y3/524; 6Q7; KT61; KT66; 6F6; 6K6. At 10/-: 6SQ7; PEN46; 50YG/GT. At 9/-: ARP6; 6X5; KT63; IT4; IS4; 1R5. At 7/6: 12SL7; TR; 77; 6J7; VR150; 606/GT; 7C7; VR119; 6AC7; OZ4; 12A6; 12A7; VR126. At 7/-: 6B8; IG6/GT; IA5/GT; 6K7G; VR53; EF39; EF36; 1616. At 6/6: H66; ARP12; VP23; EF50; VR59. At 5/6: 1235; 6SH7; 3D6; 68S7. At 5/-: 2A3; VUI33; 12SHT; 6J5/GT; 1625; TV51; VS10; PEN20A; VRI18; KT2. At 4/6: SP61; VR65; 12H6; VUI20. At 3/6: RR72; ARP3; 9D2. At 3/3: VRI8; 2155G; VUI11; RK34; 2C34; VUI33. At 2/6: VR21; VR60; P61; VR65A; SP41. At 2/6: VR54; EB34; D1; VR78; CV6.

Kit of VIEWMASTER VALVES
 at HALF PRICE
 £6 : 4 : 0.

E.H.T. TRANSFORMERS.—2,500 v. 5 m/a, 4 v. 2 amps 0-2-4 v. 4 amps 210-250 v. 50 cycles. Completely wax impregnated, 45/- each.

METERS marked OIL and AIR. Moving Coil basic 200 Microamps. Very sensitive. 2 1/2in. square, 7/6.

METERS.—0-1 amp. R.F. Thermo-couple, 2 1/2in. square, 5/6.

All above meters New and Boxed.

ROTARY CONVERTERS.—Approx. 6 volts input and 220 v. at 80 m/a. output, 12/6.

BATTERY AMPLIFIERS.—AL368 with 2 valves 210LF and QP21. 2v. and 120v., 15/- Brand New, plus 1/6 if carrying case required.

Please include something for Postage. Money Back Guarantee.

OPPORTUNITIES IN TELEVISION



144 pages
Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.J.R.E., R.T.E.B., Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS—NO FEE"
 If you are earning less than £14 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

WRITE TODAY!

British Institute of Engineering Technology
 237, Stratford House,
 17-19, Stratford Place,
 London, W.1.

BIET



Pye Television for Switzerland

THE first Swiss television station will be fitted with British equipment manufactured by Pye Ltd., of Cambridge.

As a result of the recent visit to Switzerland of the Pye technical and export directors, Pye cameras will be ready for delivery towards the end of May for transmissions expected to commence towards the middle of this year.

Switzerland is planning an extensive television network with five stations at Zürich, Berne, Geneva, Lausanne and Lugano.

Danish TV to End ?

DENMARK may become the first country in the world to end its television service because people are not interested enough to buy expensive receivers. The Danish State Radio is considering dropping the service for these reasons.

Since television began in Denmark last autumn only 400 sets have been sold, though permission was given for 1,500 to be marketed. The sets cost £195 each.

"Television Topics Quiz"

TELEVISION is no substitute for radio. In television you are going to enjoy a new form of entertainment—one of the finest I know," said Mr. Harold A. Curtis, London, secretary of the R.T.R.A., in Cardiff recently.

He was one of the speakers at a "Television Topics Quiz" organised by the Cardiff centre of the Association, and attended by 500 representatives of all sections of the radio industry, the BBC, G.P.O., the Electricity Board, other organisations and invited members of the public. They came from many parts of South Wales.

Three hundred applications for tickets had to be refused.

Purpose of the meeting was to discuss some of the teething troubles facing television in the area when the Wenvoe station opens in August.

Mobile Unit for Scotland

IT is expected that Scotland will soon have its own mobile television unit.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Four vans, each fitted with a camera and other technical apparatus, will cover events within a radius of

25 miles of the unit headquarters in Glasgow.

Mr. Ian Crawford, publicity officer of the BBC, stated recently that programmes with a Scottish flavour had proved to be quite popular even with English viewers.


Plaque to Baird

IN addition to the memorial plaque to J. L. Baird, unveiled at 22, Frith Street, Soho, last year, another is to be put up at his one-time home at Bexhill, Sussex.

Protest against Mast

THE BBC's proposal to build a television mast at Hessary-Tor, near Princetown and Dartmoor gaol, has met with strong protests from people who believe that any such mast would spoil the moor's natural beauty.

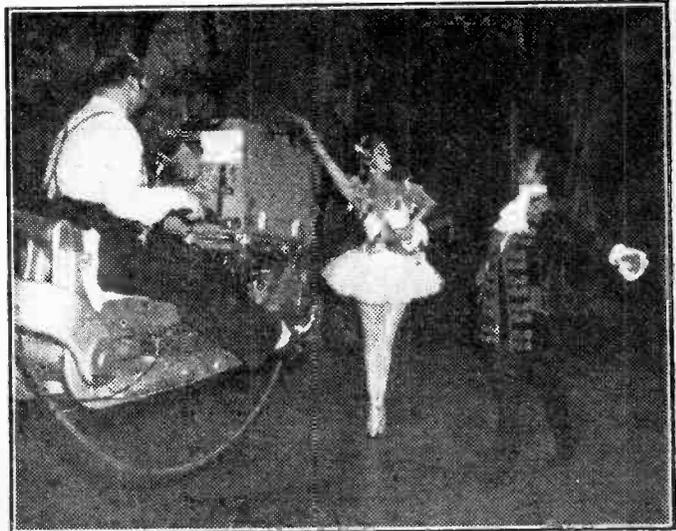Residents of Torquay, Exeter, Paignton, Falmouth and Truro would be within range of the new mast which would mean an additional 900,000 viewers.



Television cameraman Friese-Greene, son of the inventor of moving pictures, photographed "shooting" a scene from the "Sleeping Princess" ballet, seen by viewers recently. This scene, in the woods, shows Harold Turner as Prince Floramund and June Brae as the Lilac Fairy.

Strongest protests are being made by the Dartmoor Preservation Society.

Russian Service

ACCORDING to an article in the Russian press, Moscow now possesses approximately 60,000 receivers, half of which were bought in the past year. The Moscow television headquarters televises from three to four hours daily, six days a week. Programmes consist mainly of music concerts and plays televised from actual theatres.

Reception in Ireland

MR. JAMES McKEOWN had been experimenting for months with his receiver behind his jeweller's shop in Ballymoney, Co. Antrim, but had been unable to obtain a picture from either the Sutton Coldfield or the Holme Moss transmitter. The experiments continued after the opening of the Kirk o' Shotts transmitter until, finally, Mr. McKeown obtained an almost perfect picture on his screen.

He has now placed the set in his shop window.

Cinemas Can Compete

SPEAKING at the Leeds Publicity Club recently, Mr. J. Arthur Rank said that when national sport-

ing events were being televised on the spot cinema takings were likely to be affected, but he believed that the cinema would be able to compete with television "provided we make entertaining pictures."

Television in Canada

THE initial plans for the opening of a television service in Canada are nearing completion. With the aid of a 6,000,000 dollar loan from the Government, the Canadian Broadcasting Corporation is completing an English language station at Toronto and both English and French stations in Montreal. The building of these first stations was delayed for two years by the shortage of materials and equipment owing to the rearmament programme, but closed circuit experiments have taken place since February and it is now expected that public transmissions for about three hours each day will commence in Montreal on August 1st and in Toronto on September 1st.

One in Seven

EVERY seventh householder in Bedfordshire possesses a television receiver.

Announcers' Wardrobes

TELEVISION announcers, by today very much in the public eye, are supplied by the BBC with the clothes which they wear for their screen appearances. The Corporation has, for some time, been considering methods of raising the standards and widening the range of its television announcers' wardrobes.

As a result of discussion with the BBC the London Model House Group, consisting of 13 leading wholesale fashion houses, has agreed to supply television announcers with clothes from their latest collections. The BBC will pay for all clothes supplied by the Group and the clothes will be fitted by the fashion house from which they are bought. The clothes will be selected by the BBC, assisted by members of the London Model House

Group. The announcers themselves will also help in the selection. Arrangements to buy clothes for guest announcers will also be made.

No Outside Aerials in Glasgow

GLASGOW Corporation Housing Sub-committee decided recently that television aerials must not be installed on the outside of their 70,000 council houses.

The tenants of the 35,000 terrace or cottage-type houses may have pole aerials in their back gardens and loft aerials may be fixed by flat occupiers.

Tube Implosion

WHEN Charles Mobely was having a television set installed in his New York City home, the tube imploded, injuring two of his children and wrecking the receiver.

The family was gathered round the set while the installation engineer was instructing them in its method of operation. The set had barely been on five minutes when the tube imploded. The two children were cut by flying glass, and only the fact that Mr. Mobely's coat stopped a lot of the glass prevented further damage.

The cause of the implosion has not yet been determined.

Rise in "Viewmaster" Cost

OWING to increased costs in production, the publishers of the "Viewmaster" envelope have announced that, as from February 15th, the price has been raised to 7s. 6d.


There are three editions: Model "A" for London, Model "B" for Sutton Coldfield, and Model "C" for Holme Moss or Kirk o' Shotts. The increase is the first since the envelope was issued.

Broadcast Receiving Licences

STATEMENT showing the approximate numbers issued during the year ended March 31st, 1952.

Region	Number
London Postal	2,394,000
Home Counties	1,677,000
Midland	1,776,000
North Eastern	1,961,000
North Western	1,660,000
South Western	1,085,000
Welsh and Border Counties	749,000
Total England and Wales	11,302,000
Scotland	1,150,000
Northern Ireland	213,000
Grand Total	12,665,000

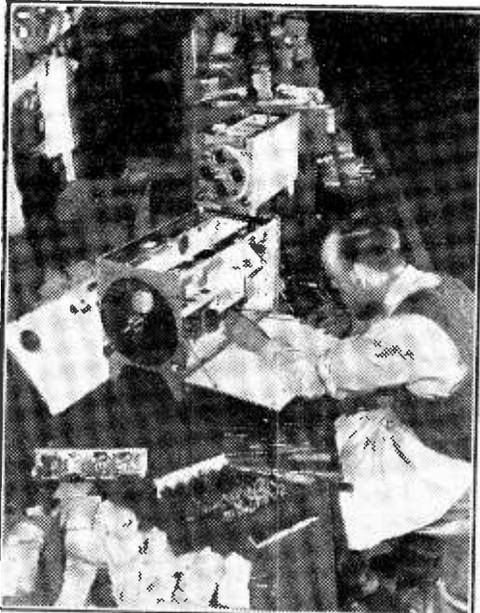The above total includes 1,457,000 for television, an increase of about 71,000 during the month.



A Mark II camera with the rotating lens turret being assembled while the prototype stands complete in the background.

VINER

INDICATOR TYPE 97. New Condition, complete (less Tube and Valves).

10/- ——— 10/-

SLC Receiver, 45/-, R1355, 65/-, Type 6H, 80/-, VCR97 Tubes, 39/-.

TRANSFORMERS

450-450 120 mA. 4 v. 6 Amp., 26/-.
 2.5 Kv., 5 mA., 4 volt, 1 Amp., 2 volt-0.2v. 1 Amp., 39/6.
 Filament Transformers: 4 v. 8 Amp., 10/-; 6.3 v. 8 Amp., 10/-;
 6.3-7 volt, 2 Amp., 5/-; 14 volt and 17.5 volt, 20 Amp., 20/-;
 14 volt and 20 volt 20 Amp., 35/-, Auto-wound Transformer,
 1.6 kva., 110 v., 150 v., 190 v., 230 v., 21/-, Belling Lee 5-pin
 or 7-pin Plug and Socket, complete, 1/6. Micro Switches,
 2/6. Chokes, 10 H. 250 mA., 9/-; 15 H. 100 mA., 9/-; 8.1 H.
 80 mA., 4/-, Electrolytics, 25 mfd. 25 volt, 1/3; 20 mfd.
 40 volt, 1/-; 8 mfd. 600 volt, 3/-, Pye Co-axial Plug and
 Socket, 1/- complete. Co-axial Cable 80 ohm. 1/3 per yd.
 Ex-R.A.F. Mains Suppressors, 5/-, M.C. Meters 300 mA., 6/-;
 500 mA., 6/-.

WE SUPPLY SPARES FOR TX
 1154, 1131, No. 33, No. 12.

Receiver 1155A or B., £11. Brand new condition.

LARGE STOCK OF TRANSMITTER VALVES

26, EAST STREET, MIDDLESBROUGH.

Tel.: 3418 Middlesbrough.

"ADCOLA" SOLDERING INSTRUMENTS

Regd. Trade Mark

FOR WIRELESS AND TELEVISION ASSEMBLY

Regd. Design No. 860302

(British, U.S. and Foreign Patents.)

Simplify your construction with the aid of Adcola Soldering Instruments.

SUPPLIES FOR ALL VOLT RANGES FROM 617 v. to 2301250 v. 3/16in. dia. Bit. Standard Model ... 22/6

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED

SALES OFFICES AND WORKS:

Cranmer Court, Clapham High Street, London, S.W.4 (MACaulay 4272)

QUALITY TELEVISION COMPONENTS
SCANNING COILS
 6/10 kV. R.F., E.H.T. UNITS
 E.H.T. and OUTPUT TRANSFORMERS
 LINE FLY-BACK E.H.T. UNITS

"TELEVISION CIRCUITS"


Third Edition, 64 pages, 2/6

HAYNES RADIO Ltd.,

Queensway, Enfield, Middlesex.

D. COHEN

Radio and Television Components

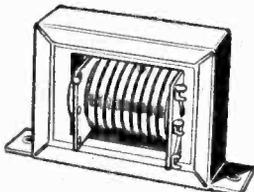

Line and EHT Transformer 5 to 6 Kv. removed from Chassis. Guaranteed. Rectifier £Y51.



Line and Frame Scan Coils. Low Line High Impedance Frame removed from Chassis. Guaranteed.

Both items above **25/-**
 P. & P. 1/6.



Frame oscillator blocking transformer.

4/6
 P. & P. 5d.



Heater transformer Pri. 230-250 volt, Sec. 2 volt 2 amp. **5/-**
 P. & P. 1/-.



Smoothing choke 150 mA 2 Henry, **3/6**
 P. & P. 1/-.

PM Focus Unit. Any 9in. or 12in. tube, except Mazda 12, state tube. Similar to above, with front adjustment, 15/-.

PM Focus Unit for 12in. Mazda ... **15/-**
 Similar to above with front adjustment, 17/6. P. & P. 1/6 each.

MAINS TRANSFORMERS

These transformers are all famous radio manufacturers' surplus and are fully inter-leaved, impregnated and guaranteed.

Primary 200-250 v. P. & P. on each, 1/6 extra.
 300-0-300, 100 mA, 6 volt 3 amp., 5 volt 2 amp., 17/6.
 350-0-350, 70 mA, 6 v. 2.5 amp., 5 v. 2 amp., 14/6.
 280-0-280, 80 mA, 6 v. 3 amp., 4 v. 2 amp., drop-through, 14/-.
 Semi-shrouded, drop-through, 280-0-280 80 mA, 4 v. 6 amp., 4 v. 2 amp., 12/6.

350-0-350, 120 mA, 4 v. 6 amp., 4 v. 3 amp., drop-through, 21/-.
 350-0-350, 100 mA, 4 v. 2 amp., 4 v. 4 amp. Upright or drop-through mounting, 16/-.

Tube supporting Bracket in 18 gauge cadmium plated steel, size 9 1/2 in. x 4 1/2 in., with 3 1/2 in. diameter cut-out complete with 12in. Tube supporting clamps, 2/-, post paid.

Frame output transformer. 10 Henry matching 10-1. 9/6.
 Auto-wound, could be used in the Viewmaster, H.T. 280 volt, 360 mA, 4 volt 3 amp., 4 volt 3 amp., 2 volt 3 amp., 10/-, plus 1/6 post and packing.

9in. White rubber mask with armour-plate glass ... 16/-
 12in. Cream rubber mask with armour-plate glass ... 15/-
 15in. Rubber mask ... 15/-
 12in. Armour-plate glass ... 4/-
 9in. Armour-plate glass ... 3/-
 Heater Transformer Pri. 230-250 v. 6 v. 1 1/2 amp., 6/-; P. & P. each 1/-.

TV. Chassis. Size 9 1/2 x 9 1/2 x 3 1/2. 18 gauge steel cadmium-plated, complete with five coil cans, size 1 1/2 in. x 1 in., with ironed cored former. These are wound for television frequency, 616 P. & P. 1/6. 6 1/2 in. Energised Television Speaker by Plessey. Field resistance 68 ohms with Humbucking coil. Will pass up to 300 ma. Require minimum 200 mA to energise. These are cheaper than a TV choke, 9/6 each, 2 for 18/-.

TERMS OF BUSINESS: CASH WITH ORDER.
 DISPATCH OF GOODS WITHIN 3 DAYS FROM RECEIPT OF ORDER.

Orders under £2 add 2/-. Under £1 add 1/6 post and packing
 All enquiries and lists, stamped addressed envelope

23, HIGH STREET, ACTON, W.3.
 (UXBRIDGE ROAD) Acorn 5901

U.E.I. CORPN.,

THE RADIO CORNER, 138, Gray's Inn Road, London, W.C.1 (Phone TERminus 7937)

THE "ARGUS" TELEVISOR

The following items available ex-stock:

MAINS TRANSFORMER
425-0-425v. 200ma., 6.3v. 4a., 6.3v. 4a., 5v. 3a. (postage 1/6) ... 50/-

E.H.T. TRANSFORMER FOR VC187 TUBE
2,500v. 5ma., 2-0-2v. 1.1a., 2-0-2v. 2a. (post 1/6) ... 37/6

VC187 TUBE
Tested full screen for T.V., with base (carriage paid) ... 45/-

CHOKES
5h. 200ma. (postage 1-) ... 6/-

VALVES
EF50 (VR91) ... 6/6
5U4G ... 10/-
6V6 ... 12/8
EB34 (VR54) ... 3/6
EF35 (VR50) ... 7/6
SP61 (VR65) ... 4/6
EA50 (VR192) ... 3/6

POTENTIOMETERS
Less switch ... 3/-
With switch ... 4/6

VALVEHOLDERS
I.O. or M.O. ... 6d.
EBC ... 10d.
Diode ... 6d.

RESISTORS
1w. ... 4d.
1w. ... 5d.
1w. ... 6d.
2w. ... 9d.
15w., 2.5k. ... 2/-

CONDENSERS
Mica and Silver Mica ... 6d.
Tubulars—
.1mf. ... 9d.
.01mf. ... 9d.
.05mf. ... 9d.
.005mf. ... 9d.
.5mf. ... 2/-
.03mf., 2.5kv. ... 2/6
.1mf., 3kv. (block type only) ... 4/6

ELECTROLYTICS

8mf. 450v. ... 2/6
8 x 8mf. 450v. ... 4/9
16 x 16 mf. 450v. ... 7/-
25mf. 25v. ... 1/6
50mf. 12v. ... 1/6

TRIMMERS 0-30pf. ... 7d.

COIL FORMERS WITH SLUGS
1in. ... 8d.
1in. ... 10d.

P.M. SPEAKERS (less transformer)
5in. Plessey ... 12/6
5in. Rola ... 16/6
8in. Plessey ... 17/6
(Postage 1/6 per speaker)

PENTODE OUTPUT TRANSFORMER ... 5/-

Constructional details with blueprint for the "Argus" Televisor 2/9 post paid.

RDF 1 RECEIVER

The unit reviewed in the October and November issues of this journal and reviewed in a separate article giving SOUND AND VISION ON THE ONE CHASSIS. Complete with 14 valves as follows: 5 of SP61, 2 of P61, 3 of EA50 and 1 each CV63, EB34, EC52, 5Z4c, also a complete reprint of the above review (carriage etc., 5-) ... ONLY 49/6

194 I.F. STRIP

Reviewed in the October issue of this journal. An easily modified I.F. Strip recommended for TV constructors who want good results at moderate costs, or for those who have built televisors, but are having trouble in the Vision or Sound receivers. Can be built into any layout, measuring 1 1/2in. x 5in. x 5in. Complete with valves as follows: 6 of SP61, 1 of EA50, and 1 of EF30 or EF39 (carriage etc., 2/6) ... ONLY 45/-

MAGNIFYING LENS FOR VC187 TUBE

First grade oil filled (postage 2-) ... ONLY 25/-

TRANSFORMERS

Manufactured to our specifications and fully guaranteed. Normal Primaries.
425v. 0-425v. 200ma., 6.3v. 6a., 6.3v. 6a., 5v. 3a., 0-2-0-3.3v. 3a. ... ONLY 72/6
350v. 0-350v. 180ma., 6.3v. 6a., 6.3v. 3a., 5v. 3a. ... ONLY 42/6
250v. 0-250v. 100ma., 6.3v. 6a., 5v. 3a. ... ONLY 32/6
All above are fully shrouded, upright mounting.
Top shrouded, drop through: 260v. 0-260v. 70ma., 6.3v. 3a., 5v. 2a. ... ONLY 16/6
Universal Mounting: 350v. 0-350v. 80ma., 0-4-0.3v. 4a. and 0-4-5v. 2a. ... 18/6
5.5 kv. E.H.T. with 2 windings of 2v. 1a. ... ONLY 72/6
7 kv. E.H.T. with 4v. 1a. ... ONLY 82/6
PLEASE ADD 1/6 POSTAGE FOR EACH TRANSFORMER

CHOKES

20h. 80-120ma. ... 9/6
30h. 100-150ma. (post. ea. choke 1/-) ... 12/6

10 VALVE 1 METRE RECEIVER ZC8931

For long-distance TV results. Valve line-up is 6 of SP61, 2 of EA50, and 1 each EF54 and EC52, and the 12 Mc/s 6-stage I.F. Strip gives tremendous amplification with ample bandwidth of 4 Mc/s. EASILY MODIFIED, full details being supplied (carriage etc., 5-) ONLY 59/6

R.F. UNIT TYPE 24.

For use with the R1355 Receiver, etc. Supplied Complete with 3 valves SP61 and Modification Data for all TV Stations (postage, etc., 2-) ... ONLY 25/-

Cash with order, please, and print name and address clearly.

Open until 1 P.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station), 5 mins. by bus from King's Cross

Come to the
CLASSIC for

"THE CLASSIC SERVICE"

Our Motto is

"NOTHING IS TOO MUCH TROUBLE"

We will ship to any part of the British Isles or Abroad.

TAPE RECORDING EQUIPMENT

Agents for all leading makes.

AMPLIFIERS & HI-FI EQUIPMENT

Agents for: Leak, Quad, Williamson, Decca, Connoisseur, etc.

TELEVISION COMPONENTS

Northern and Scottish readers write to us for details of our special offer of View Master components. Full details sent by return. Special terms available for those wishing to build their own Television receivers. Maximum stocks of valves, tubes and other accessories available for despatch by return.

Send 2d. stamp for List, to:

The Classic Electrical
Co. Ltd.

352-364 LOWER ADDISCOMBE RD.,
CROYDON, SURREY.

Tel.: ADD. 6061-2

Pre-Amplifier Transformer. Prim. 200/250 v., Sec. 230 v. at 30 mA., 6.3 v. at 1.5/2 amps., 23/-.

HS150. 350-0-350 at 150 mA. 6.3 v. 3 amps. C.T. 5 v. 3 amps. Half-shrouded, 30/9.

FS43. 425-0-425 at 200 mA., 6.3 v. 4 amps. C.T., 6.3 v. 4 amps. C.T., 5 v. 3 amps. Fully shrouded, 51/-.

F35X. 350-0-350 v. at 250 mA., 6.3 v 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded, 71/6.

FS160X. 350-0-350 v. 160 mA., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded, 47/6.

FS43X. 425-0-425 v. 250 mA., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded, 69/-.

FS50. 450-0-450 v. 250 mA., 6.3 v. 4 amps. C.T. 6.3 v. 2 amps. C.T. 5 v. 3 amps. Fully shrouded, 75/-.

F36. 250-0-250 v. 100 mA., 6.3 v. C.T. 6 amps. 5 v. 3 amps. Fully shrouded, 32/6.

FS150X. 350-0-350 v. 150 mA. 6.3 v. 2 amps. C.T. 6.3 v. 2 amps. C.T. 5 v. 3 amps. Fully shrouded, 34/9.

F30X. 300-0-300 v. 80 mA., 6.3 v. 7 amps., 5 v. 2 amps. Framed. 31/9. The above have inputs of 200-250 v. C.W.O. (ADD 1/3 in £ for carriage.)

H. ASHWORTH

676, Great Horton Road, Bradford, Yorks. Tel.: Bradford 71916.

G.E.C. & B.T.H. GERMANIUM CRYSTAL DIODES

G.E.C. GLASS TYPE 5/16in. x 3/16in. B.T.H. LATEST TYPE MOULDED IN THERMO-SETTING PLASTIC

Both Wire Ends for Easy Fixing. 416 each, postage 2jd.

SILICON CRYSTAL VALVE
316 each, postage 2jd.
Fixing Brackets 3d. Extra.

Wiring instructions for a cheap, simple but high quality Crystal Set included with each Diode and Crystal Valve.

COPPER INSTRUMENT WIRE ENAMELLED, TINNED, LITZ, COTTON AND SILK COVERED.

Most gauges available.

B.A. SCREWS, NUTS, WASHERS soldering tags, eyelets and rivets.
EBONITE AND BAKELITE PANELS,
TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES,
ALL DIAMETERS.
Latest Radio Publications.

SEND STAMP FOR LISTS.


CRYSTAL SET
INCORPORATING THE SILICON
CRYSTAL VALVE
Adjusted Iron Cored Coil.

RECEPTION GUARANTEED

Polished wood cabinet, 15/-, post 9d.
A REAL CRYSTAL SET, NOT A TOY
POST RADIO SUPPLIES
33 Bourne Gardens, London. E.4

TELEVISION PICK-UPS AND REFLECTIONS

UNDERNEATH THE DIPOLE

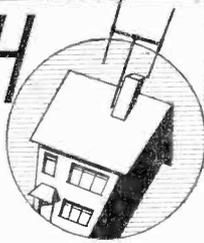

ATTACKS ON TELEVISION

EVERY generation seems to produce its Aunt Sally of entertainment, to be blamed, praised, assailed, extolled and condemned—but never to be ignored. The “vulgar” music-halls of the nineties were succeeded by the equally “wicked” musical comedies of Edwardian days which, in turn, gave way to the supersensations of the silent cinema and the prattling “inanities” of the talkies. Each were frowned upon by the busybodies and meddlers, but rapturously received by the entertainment-hungry public. Each was cited as an example of the decadence of its own particular age, with the sole exception of the sound radio of the twenties (which was blamed for its general level of dullness!). And now comes the great television boom, keeping millions of viewers in their homes instead of patronising the pictures, the pubs, the theatres, the clubs. No wonder the florid impresarios of stage and screen turn pale as they survey rows of empty seats!

THE KNOCKERS

TELEVISION has received its fair share of knocks from busybodies and meddlers, but the biggest knock of all seems to me to come from the BBC's own official survey of the influence of television on British public life and other entertainments. It is apparent that, in spite of much grumbling at the programmes, over 40 per cent. of viewers are at their sets each evening and that no less than 63 per cent. go to the cinema less than they did before. The success of television is so staggering as to be frightening; its tremendous power is almost too great to be left in the hands of a monopoly; conversely, its mission too sacred to be fed to the sponsors! What is to become of it in the New Charter? And what will become of the empty libraries, the ruins of film studios, deserted race tracks, cobwebbed dart boards and the like? The national newspapers send up a wail of woe.

COLOUR AND STARS

BUT all is not lost. Cinemas and theatres have undoubtedly suffered a fall in patronage, but are preparing to fight back. What can

By Iconos

they offer the public to beat the “menace” of television? The answer is—stars and colour. Star names become more important than ever, since major star salaries are normally beyond the purse of the BBC. New stars will be created, groomed, boomed and billed. And some of television's own stars will find their way into the top-bracket classes of stage and screen acting. Already Gilbert Harding has sampled the glare of film studio lights as an alternative to the television lights, and Terry-Thomas heads the bill of a cheerful music-hall road show called “How Do You View!” which I assume is based on the television feature of the same name.


On the technical side, there is a positive rush to colour. Technicolor, Cinecolor, Gevacolor and Ektacolor are in such great demand both in England and America that the printing of hundreds of copies of colour films will become a problem in itself. Since the plant and equipment required to make colour-film prints is about five times as large and ten times as complicated as for black-and-white, it may be two or three

years before all films turn over to colour. But it is quite certain that the end of the black-and-white era of films is at hand—the pace has been forced by TV. Colour, too, will influence the design of stage plays, musical shows and revues. Improved lighting equipments, including coloured fluorescent strips which can be gradually dimmed, will help to put over live shows in a colourful manner.

CELLULOID

THE colossal footage of colour-film prints now required by the film industry does not by any means spell ruin for the manufacturers of black-and-white film. One big American maker of film stock states that they sell five times as much black-and-white film to the American television industry as they ever did to the film industry itself. In England, the film content of BBC TV programmes is high, too, and a growing number of film units are maintained by the BBC in addition to the subcontracting of special subjects to outside producers. It is interesting to note that the BBC have commissioned an outside independent producer, Marcus Cooper, to make a monthly series of films about the stately homes of England. Marcus Cooper made the special morning test film which opened the BBC television after the war.

PROFESSOR BOFFIN

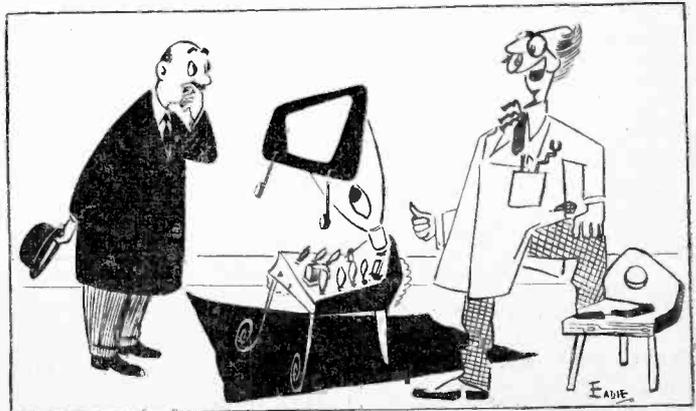

“I feel a different man since I started on television sets for Pablo Picasso!”

Nera Spot Wobbler and EHT Unit

AREN RADIO AND TELEVISION, LTD., have recently

introduced two interesting items for the home constructor, both of which are available either as complete units or in the form of separate parts. The Spot Wobbler measures 1½ in. by 1½ in. by 3½ in. and requires 6.3 volts at .3 amp. and an H.T. supply of 2 to 8 mA. at 200 to 300 volts, which may be obtained from the existing receiver. The wobbler coils slip on the tube neck between the scanning coils and the focus magnet, for which the maximum space needed is ½ in. The coils may however, be compressed into ¼ in., where necessary, without affecting the results. The operating frequency is 10 Mc/s and a trimmer is provided so that the best setting may be obtained free from interference with any of the tuned circuits. The complete unit costs £3, and the individual parts available are a chassis and valve-holder for 2/6; screening can 5/6; coils 6/6; plug and socket for H.T. and L.T. supplies 1/6 and the necessary kit of resistors, condensers, potentiometer, etc., 6/6.

The second item is an R.F. E.H.T. unit which we have had the opportunity of testing. This gives a peak output which may be varied from slightly over 7 kV. to slightly greater than 12 kV. The necessary 6.3 volts at 1 amp. and H.T. at up to 30 mA. may be obtained from the existing receiver, and the unit is screened to prevent interference. The placing of the oscillator valve outside simplifies replacements when necessary, and there is an adjustment by the side of the valve by means of which the output may be regulated. The coil is wound on an "X"-shaped former and the heater winding of the rectifier is not permanently fixed. As the heater supply is R.F. it is, of course, not a simple matter to measure it, and it will vary according to the H.T. applied to the unit. The cover is therefore removed from the unit, and the apparatus connected up ready for use, and the heater of the small U25 rectifier is inspected. For this purpose the unit should be in a somewhat darkened position, and the unit preferably placed on its side so that the end of the heater may be seen. With the unit then switched off, the

TRADE TOPICS

heater winding should be placed closer to or farther away from the main coil until the heater glows a cherry red. If possible,


the valve should be connected to a 2 volt accumulator and the colour of the heater noted, and then the coil adjusted until the same colour is obtained. If the coil is too close the heater will give an orange glow, and if too far away it will be a deep red. The output of the unit, is, of course, dependent upon the heater supply as well as upon the H.T. adjustment. This unit may be used in the PRACTICAL TELEVISION receiver in place of the originally-specified unit which is no longer being manufactured, and the price is £6/10/-, complete. The coil, with the rectifier valve incorporated may be obtained, with a circuit diagram and full instructions for £3/17/6. For those using series-heater operated receivers with H.T. not exceeding 170 volts a specially modified unit may be obtained to give the same output for 7/- extra. The unit may be thoroughly recommended.—Aren (Radio and Television), Ltd., High Street, Guildford, Surrey.

Brimar Teletube Service Depots

STANDARD TELEPHONES AND CABLES, LTD., announce an immediate exchange service for defective Brimar Teletubes, which are *still under guarantee*.

These exchanges will eliminate unnecessary delay while the tubes are being returned to Footscray, and can be made at the following depots: 5, Oldbury Road, Blackheath, Birmingham, Warwickshire; 87, McAlpine Street, Glasgow, C.3.

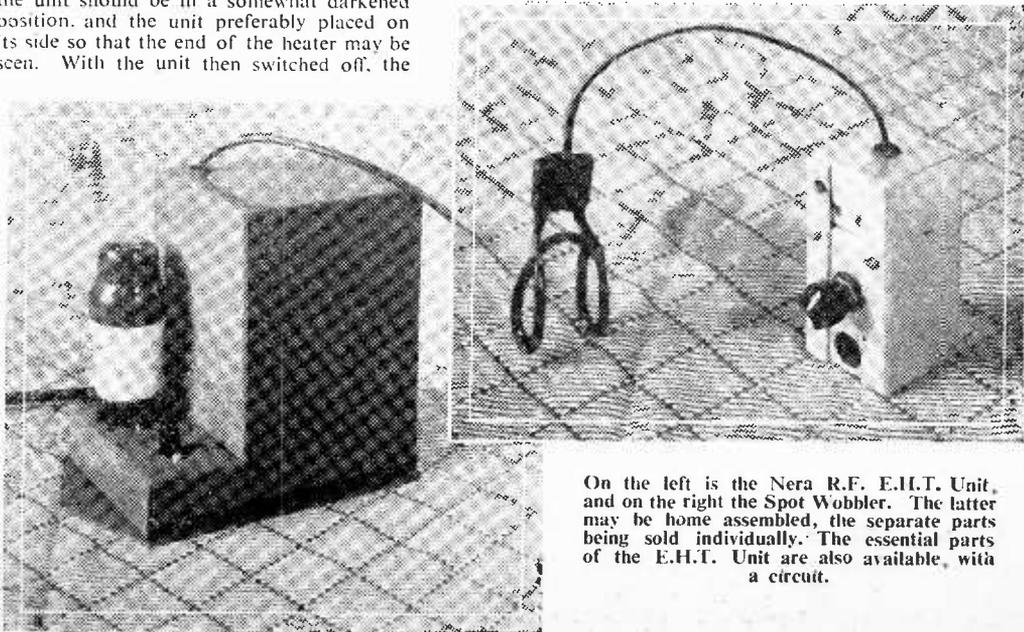All other replacements and orders should be sent, as usual, to the Service or Commercial Departments at Footscray.—Standard Telephones and Cables, Ltd., Footscray, Sidcup, Kent.



On the left is the Nera R.F. E.H.T. Unit, and on the right the Spot Wobbler. The latter may be home assembled, the separate parts being sold individually. The essential parts of the E.H.T. Unit are also available, with a circuit.

ALPHA OFFERS

1 WATT RESISTORS at 6d. each.

100 kΩ, 47 kΩ, 30 kΩ, 150Ω, 33 kΩ, 22 kΩ, 6 kΩ, 250Ω, 39 kΩ, 560 kΩ, 4.7 kΩ, 680Ω, 1 megΩ, 300 kΩ, 40 kΩ, 10 kΩ, 1 kΩ, 5.6 kΩ, 330 kΩ, 330Ω, 0 kΩ, 80 kΩ, 8 kΩ.

MOULDED MICA CONDENSERS

901, 001, 002, 003, 005, 0061, 0002, 0003, 0005, 00022, 00005. All 5.6 doz.

BAKELITE CASE CONDENSERS

25 mfd. 500 v., 02 mfd. 5 kV., .001 mfd. 4 kV., .01 mfd. 4 kV. All 1/- each.

PANEL MOUNTING PRESS SWITCH

2-hole fixing type, 1/3 each.

WIRE-WOUND VOLUME CONTROLS

5Ω, 200Ω, 1 kΩ, 5 kΩ, 15 kΩ, 20 kΩ, 25 kΩ, 35 kΩ, 50 kΩ, 2.9 each.

SPEAKERS

5 1/2" Elec. 3Ω, 13.6; 5" Goodman, 3Ω, 13.6; 5" Plessey, 3Ω, 12.6; 8" Plessey, 3Ω, 14.6; 12" Traves, 57.6; 10" Goodman, 32.6; 10" Rola, 32.6; 9" Goodman, 16/-.

STANDARD CAN CONDENSERS

16 mfd. 500 v., 3/9; 8 mfd. 450 v., 1/11; 24 mfd. 450 v., 4/6; 8 x 8 mfd. 450 v., 4/-; 16 x 8 mfd. 450 v., 4/8; 32 x 32 mfd. 450 v., 7/-.

EX EQUIPMENT VOLUME CONTROLS

All in good condition carbon type, 200 kΩ, 10 kΩ, 1 megΩ, 50 kΩ, 5 kΩ, 500Ω, 20 kΩ, 25 kΩ. 1/- each.

VIEW MASTER ENVELOPES

For Hobbs Moss or Kirk o' Shotts, 5/- each.

VALVES

All Guaranteed
Majority in Maker's Cartons.

024	8/	6160	11/6	DD13	8/9	VR137	5/9
174	9/-	6276T	7/6	EC180	12/6	EL52	7/9
183	9/-	6Q7G	11/6	EB041	11/6	VU111	4/6
184	9/-	6SA7GT	9/6	EL41	11/6	VU120A	4/-
185	9/-	6S67	7/9	E1148	2/-	UX41	10/6
105GT	8/6	6RH7	7/-	FW4500	9/9	UCH42	12/6
243	7/9	6R7	8/6	G6Z5	4/6	DL41	11/6
2158G	4/-	6RK7	7/-	H63	9/6	Y63	9/-
282	6/6	6RN7GT	11/6	KTW61	8/9	W21	9/-
334	9/-	68Q7	9/6	KT66	11/6	E1436	3/9
3D6	8/6	6U7G	9/-	KT263	7/9	7473	3/9
384	10/6	6V6GT	9/6	KT332	11/6	KT91	10/-
42	9/6	6V61	9/6	KTZ41	6/9	734	9/-
314G	9/-	6X5GT	9/-	KT30	11/-	767	9/-
534G	9/6	6AM6	11/6	ML4	8/9	785	9/-
5330T	9/6	6AL5	9/-	ML6	4/-	796	9/-
5Z4M	9/6	6B7	7/9	MH41	7/9	X18	10/-
5Z4H	10/6	7B8	9/6	DI1	4/9	VM84B	12/6
6A07	7/9	7B	8/6	8P2	4/6	EL50	9/6
6B8	7/9	80	9/6	VP41	9/-	6U5	9/6
6C5GT	7/6	954	2/9	DH73M	9/6	APV4	9/6
6C6	7/6	955	5/-	PM2A	7/6	SP2	9/6
6D6	7/6	906	3/3	PM202	7/-	EA30	10/-
6E6M	9/-	902	4/9	EF39	7/6	with	3/-
6E6A	9/-	12A6	7/3	EB34	3/-	Hobler	3/-
6A6A	7/6	12H6	7/3	EP26	7/6	KT32	9/6
6H6	4/6	12K8	9/6	EK32	7/6	807	11/6
6J5GT	5/6	12SH7	7/3	SP61	4/-	UB41	9/-
6J7M	8/6	TP25	8/6	8H41	4/-	EB41	9/-
6J43	7/9	V1P23	8/6	EF50	6/6	CV135	9/-
PE285	8/6	128K7	8/-	RF50 SYL	8/6	DH77	9/-
HL23D10	8/6	1622	11/6	VANIA	8/6	W77	9/-
6K7G	6/6	ACB/PEN	7/9	V872	4/-	U75	9/-
6K7GT	6/6	CV6	2/-	DD14	4/6		
6B86	12/6	CV9	4/-	EP9	7/6		

1/2 WATT RESISTORS AT 31d. each.

10 kΩ, 15 kΩ, 350Ω, 1.8 megΩ, 270Ω, 100 kΩ, 680 kΩ, 1,500Ω, 4.7 kΩ, 47Ω, 470Ω, 470 kΩ, 47 kΩ, 200Ω, 33 kΩ, 35 kΩ, 68 kΩ, 39 kΩ, 8 kΩ, 30 kΩ, 150 kΩ, 20Ω, 330 kΩ, 1 kΩ, 3 kΩ, 1 megΩ, 80Ω, 56 kΩ, 680Ω.

ENAMELLED COPPER WIRE

14 s.w.g. 1/9 per lb.
16 s.w.g. 1/8 " " "
20 s.w.g. 2/9 " " "
40 s.w.g. 3/- " " "

MAINS TRANSFORMERS

Half shrouded drop through type. Prim. 200-250v. Sec. 250-0-250v., 50 ma.
6.3v. 3a., 5v. 2a. N.P. As above. Sec. 350-0-350v., 80 ma/4, 4v. 2a., 5v. 2a., all at 18/6 each.

STANDARD THREE-WAY MOUNTING

Prim. 200/250v. Sec. 350-0-350v., 80 ma A., 0-4v., 5a., 6.3v., 3a., 0-4-5v. 2a., 16 - each.
Chassis mounting type waxed dipped, all leads to a tag board on top. Prim. 200/250v. Sec. 350-0-350v., 80 ma/4. Two 6.3v. 4a. winding 5v. 2a., 25/6 each.
Postage on all mains transformers, 1/6 each.

OUTPUT TRANSFORMERS

GOODMANS STANDARD, 4/9 each.
A.W.F. Power Pentode, 3/11 each.
ROLA MIDGET, 4/6. PERSONAL SET TYPE, 4/3 each.

WAXED TUBULAR CONDENSERS

WIRE ENDS 3 mfd. 500v., 003 mfd. 1,000 v., .01 mfd. 3 kV., 1 mfd. 500v., all 41d. each, 4 - doz.

SPECIAL OFFERS

T.C.C. Micropack 8 mfd. 350v., 1.6 each.
MorganHe 1 meg. v/c with S.P.S., 3/- each.
Erie 1 meg. v/c D.P.S., 4/3 each.
Both with lin. spindles.

TERMS: Cash with order or C.O.D. Full list available. Send 3d. in stamps. Postage: 6d. under 10/-, 1/- under 20/-, 1/6 under 40/-.

ALPHA RADIO SUPPLY CO., 5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS, 1:

DIPOLE AERIALS FOR ALL CHANNELS

These television Dipole Aerials consist of 2 elements of strong 1/2 in. diameter tubing and a heavy bakelite insulator.

Price for all stations, 17/6 each, plus 2/6 Packing & Carriage. Don't be disappointed! Stocks are rapidly drying up and, although your station may not yet be in operation, we recommend that you obtain one of these aerials now!

POLYETHELENE DIPOLE INSULATORS

With moulded in brass stubs to take 1/2 in. iid dia. tubing. 5/- Each, plus 1/6 Packing & Carriage.

Another line that will be unobtainable shortly.

SEND S.A.E. & 3d. IN STAMPS FOR OUR CLEARANCE LIST.

**WALTON'S WIRELESS STORES,
48, STAFFORD STREET, WOLVERHAMPTON.**

VIEW MASTER

SPECIAL OFFER

Complete set of resistors. Every resistor packeted and labelled with the value and position in the set.
London, 26/- All other models, 24/9.

INSTRUCTION BOOKS

View Master instruction books for all Models are available at 5/4, post free. A fully detailed list of View Master Components is available upon request.

WATTS RADIO (WEYBRIDGE) LTD.

8 Baker Street, Weybridge, Surrey.
Telephone: Weybridge 2542

TELEVISION CABINETS

FOR ALL HOME BUILT RECEIVERS. ANY SIZE SCREEN UP TO 17". FITTED WITH FULL LENGTH DOORS AND BEAUTIFULLY DESIGNED. ALSO RADIOGRAM & L.S. CABINETS.

WRITE OR PHONE FOR LEAFLET
H. ASHDOWN, 98, Hertford Rd., Edmonton, N.9.
Tel: TOT 2621

VALVES or COMPONENTS?

VALUE, QUALITY AND EXPRESS SERVICE FROM

COVENTRY RADIO

COMPONENT SPECIALIST SINCE 1925
189, DUNSTABLE ROAD, LUTON, BEDS.
Phone: LUTON 2677

Stop Press! The latest book on the subject and an invaluable guide for all interested in TV—

TELEVISION PRINCIPLES and PRACTICE

by **F. J. CAMM**

(Editor of this journal)

Television Principles and Practice is a fully-illustrated, authoritative and up-to-the-minute work on the underlying principles of television transmission and reception, covering every aspect of this new science, including servicing and installation. An exhaustive dictionary of television terms is included. The book is fully indexed.

Written by one of the leading technical authorities of the day this handbook is a necessity for everyone interested in television—the technician, the student, and the amateur.

25/- net

"The technician and the student will find this book invaluable."

Manchester Daily Dispatch

FROM ALL BOOKSELLERS or in case of difficulty use this handy ORDER FORM

Television Principles and Practice



F. J. CAMM

Please send me C.O.D.

.....copy/copies TELEVISION PRINCIPLES AND PRACTICE
by F. J. Camm (25/- net).

Name

Address

Post this form to **GEORGE NEWNES, LTD.** (Book Dept.), Tower House, Southampton Street, London, W.C.2.

Send no money now—pay the postman on delivery plus normal postal charges.

PT 6/52


CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

DESIGN OF V.F. STAGES

SIR,—I have been reading through the complete series on the design of V.F. stages and am rather puzzled by Fig. 19, in the December issue. After reading the various details I fail to see how the black level or sync pulses are obtained in the illustration and I feel that there must be something wrong in this picture. Could you please confirm that the diagram is correct as I am studying the theory of television receiver design very closely and have gained much valuable information from your various articles. I might mention that I knew nothing of television last summer and have now commenced to build my own receiver, including in it various features which I have been able to understand from the different articles on design in your pages.—G. TRIMBLE (Golders Green).

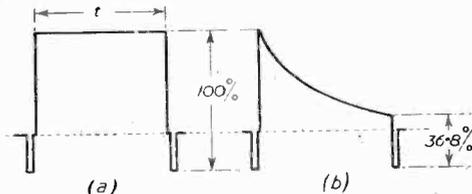[There was a fault in the diagram in question, the figures being indicated as ending on the dotted line, instead of going to the bottom of the complete swing. For the benefit of other readers who may be following the series we give the diagram again below, with the figures correctly marked.—ED.]



(a) Video signal, constant white line; (b) Video signal after C.R. circuit when C.R. is too small (0.0001 secs.).

R.G.D. MODEL 1700

SIR,—Re your advice to E. L. T., of Liverpool, and lack of width on R.G.D. 1700. The usual cause of this is the metal rectifier going low. We find that these often drop 20 to 40 v. in the first few months, and give the same symptoms. Replacement will cure the fault.—M. PRINCE (Pontypool, Mon).

COST OF UPKEEP

SIR,—With reference to your correspondent who has spent £16 4s. in two years on his television set. It is stated that this included one C.R.T. and 12 valves. There is obviously something wrong with this statement, as these items could not be purchased for this sum, even at the old rate of P.T., assuming new valves and not surplus.

There appears to be some inaccuracy in your statement with regard to the guarantee on commercial sets. Surely the position is, six months on the C.R.T., three months on valves, and 12 months on the components. Your observations on this point would be greatly appreciated.

My own receiver has been in constant use for three years (it is home constructed), and so far has cost me 1s. 6d. for a resistor. The total of valves is 24 and although these have been removed from ex-R.A.F. units by me they are still functioning.

A colleague of mine has had the "Premier Radio"

Magnetic Kit working for a little over two years and replacements for this have been nil, with the exception of the C.R.T. which was changed under guarantee, free of charge.

In conclusion I would say that if the manufacturers consider the above-mentioned sum to be normal, the answer seems to be, invest in a subscription to PRACTICAL TELEVISION and "build it yourself."—ERNEST E. FENN (E.12).

SIR,—In your Editorial of the May issue, mention was made of the cost to a reader to maintain his commercial television receiver over the last two years.

Actually the figures quoted were extremely difficult to assess. Surely 12 valves and a C.R.T. costs more than £16 4s.!

Even at the old rate of purchase tax, a 9in. tube costs £11 6s. 10d. Therefore, we can only assume that the 12 valves cost £4 17s. 2d., an average of 8s. each, including purchase tax!

Now, is the answer to it all that several valves or the tube or both, were replaced under guarantee? If not, were surplus valves used as replacements?

Further, too. Who serviced the receiver?

Incidentally the B.V.A. guarantee is for three months only on valves and six months on C.R.T.s.

After all, whatever the true facts are, it must be seen that the cost to maintain an average receiver over say the first three years of its life is near enough to three shillings per week.

This is in keeping with the costs quoted by many dealers for comprehensive maintenance for 9in. tube receiver over a period usually of two years, and in my opinion is a fair price to both parties.

I am a trade engineer, and I maintain hundreds of television receivers every year, and am fully aware of the costings. I would, therefore, like to state that a set owner who does not profess the ability to service his receiver, and is also sensible enough to realise that his set is a highly scientific instrument, and that it will definitely need the attention of a skilled engineer from time to time, would be safe to assess his running costs at say 2s. 6d. to 3s. per week over a period of three years.

I stress that this is an average. A 12in. model would be about 6d. per week more.

A 9in. tube costs around £13 4s., and the average valve costs 25s. This includes purchase tax.

Assuming a new C.R.T. and, say, three valves needed over a period of three years, this not including any other components, this would average about 2s. per week for replacements only. No consideration is yet given to the skilled labour involved, which generally in most trades is the highest expense.

Surely then, any set owner would be extremely glad to pay the very modest sum of 1s. per week for the services of a skilled engineer to maintain his television receiver, and pay for the material himself.

A further check of these figures may well be taken from the rental firms. Comparison with the normal hire-purchase prices, and then allow for the "free" maintenance, will disclose that the figures I have mentioned are very near the mark.

May I, therefore, conclude, and sum up by saying that although I am unable to see how the owner of the set mentioned in the Editorial, arrived at his costings, I do think that the cost even on those figures, is substantially about right.

It is useless to quote isolated examples as these will err on both sides. The average taken from hundreds of receivers can be the only way of arriving at an approxi-

mate price of expectant running costs.—A. B. CHINN (Romford).

TV BLANK SUNDAY

SIR,—I must reply to K. Norton (Surrey), who evidently forgets the Sunday staff which provides him with gas, electricity, transport, etc., etc. There is the obvious staff rotation of free time to provide for these essentials and who will deny the growing importance of TV in our lives?

We have paid now nearly £1,500,000 for TV service and we are entitled to the great extension of time we all urgently demand.

There is no valid reason at all why we could not make Sunday the TV day of the week, with continuous programme from say 2 p.m. to 10.30 p.m.

Surely it is obvious that this period is the whole nation's leisure time of the week.

Hope you keep plugging away for this essential service.—LEO TAYLOR (St. Annes-on-Sea).

7BP7 TUBE

SIR,—May I add some information to the query about the tube 7BP7 on page 523 of "PRACTICAL TELEVISION" April, 1952.

In the R.M.A. nomenclature the fluorescent screen of cathode ray tubes is described by the code P1 to P14, the figures denoting the following properties:

	Colour	Contrast	Persistence	Application
P1	Green	20 : 1	Medium	Oscilloscope (Exp. TV).
P2	Green	20 : 1	Long	Long pers. oscilloscope.
P3	Yellow	20 : 1	Medium	Oscilloscope.
P4	White	30 : 1	Short	TV
P5	Blue	10 : 1	Very short	Transients—60 Kc. oscilloscope photography.
P6	White	30 : 1	Short	TV
P7, β	Yellow	20 : 1	Long	Radar slower 1 scan/sec.
P9	White	30 : 1	Long	High definition radar.
P10	Dark trace for radar	1.2 : 1	Long	Radar slower than 1/5 scan/sec.
P11	Blue	10 : 1	Very short	Photog. of transients—9 kc/s.
P12	Orange	20 : 1	Long	Radar 4-16 scans/sec.
P14	Orange	20 : 1	Long	Radar 1 scan/sec.

Thus while tubes 7BP1 to 7BP11 are electrically similar only the types with screens of short to medium persistence would be satisfactory for television. P7 is a double phosphor screen with a short persistence blue screen actuating the long persistence yellow screen.

This afterglow of over one second might be absorbed by a suitable filter in front of the screen. Since it has been reported that filtering has made this type of tube suitable for amateur flying spot scanning, its application to TV reception might be possible.

The making of deflector coils for similar tubes is discussed in "Cathode ray tube displays," Vol. 22 of the Radiation Lab. Series," McGraw-Hill.

In the hope that this may help Mr. Profaze in his experiments, I remain.—P. LEWIS (N.10).

TIME BASE SYNCHRONISATION

SIR,—Surely your contributor G. J. King is in error in his diagram of integrated line pulses Fig. 1(d) on page 484 of the April issue, where he shows the line pulses used for synchronisation.

He has indicated with an "x" the fourth pulse from the left as being one used to trigger the line oscillator. This pulse is coincident with the onset of the frame pulses as is the third pulse from the left in Fig. 1(c). If, therefore, No. 4 pulse is used as shown, the line oscillator will have to jump half a cycle when the odd frame pulses arrive, frame and line triggering pulses will be in phase and interlacing will be upset. Furthermore, if the line oscillator is adjusted to jump the half cycle as shown, it must of necessity jump all the following half cycles also, and the top of the picture will be distorted. Mr. King himself points out that this is incorrect.

A correct diagram would be one in which Figs. 1(c) and 1(d) are the same. The line oscillator is at all times triggered by pulses placed one line apart and the interlacing achieved by bringing forward the frame pulses by half a line each time. There is no change of line frequency or phase at any time.—R. W. SWABY (Northumberland).

[I wish to thank Mr. Swaby for pointing out the slip in Fig. 1(d) in my article entitled "Time Base Synchronisation."

Under the section *Interlace Problems* I stated that to secure a good interlace the start of a frame scan must coincide with the start of a line scan every other frame only; this condition is shown by Fig. 1(c). Fig. 1(d), however, shows the line pulses formed during the end of the following frame; here my mistake is obvious, for again I have indicated the differentiated pulse formed by the leading edge of the first framing pulse as the one used to "fire" the line generator.

The inclusion of the half line during odd frames successfully ensures that the start of a frame scan is not coincident with the start of a line scan during odd frames. Replacing the two left hand "x" of Fig. 1(d) one pulse to the right will then, of course, satisfy this condition.—G. J. KING]

A.C./D.C. RECEIVERS WITH SAFETY

SIR,—As far as I can see all good commercial TV sets are fitted with a safety device and all home-made sets should definitely be so constructed.

It would indeed be very dangerous to switch on the set with the chassis at mains potential.

To prevent this danger and to give the necessary warning, a small neon bulb is fitted in series with a resistor (about 2 megohm) between the chassis and a well insulated lead taken direct to an earth point.

If the neon bulb lights up when the set is switched on, then the chassis is alive and dangerous to all concerned. If the neon bulb does not light up, it is not live.

If the neon bulb lights up, it is necessary immediately to switch off and reverse the mains plug before switching on again.

On the surface this method appears to be quite satisfactory, but to my mind, it is not quite good enough. Why not remove the danger for good. There is always the danger between the periods of switching on and off with the mains plug the wrong way round on any further occasions.

Why not an eccentric fitting (3 point) plug so that the plug cannot be inserted the wrong way round?

After fitting this type of plug and socket the set can be switched on and if the neon bulb lights up, it is only necessary to reverse the H.T. cables in the mains plug. (The third pin in the plug would be dead) and the danger would be removed for good.—D. KEATING (Bradford).

R.F. UNITS, type 24 and 24mod., 27, 10/- ea. less valves; Midget Carbon Mikes. 2/6; Magnetic Contact Mikes. 3/6; Motor Blowers. 24v. AC DC. 17/6 ea.; Motors. 24v. DC or 100 v AC. 30/- ea.; Condensers, 2g. 0003, 3, 6, 3g. 00015. 3/6; Transformers. 500-0-500, 120ma, 3 x 4v. 4a. 1 x 10v. 1a. 32/6; 120ma chokes to suit, 10/-; heavy duty PP input 1L. 10/-; Ferranti HD intervalve 1L. 10/-; Westcoats. 4/- ea.; metal Recs. 230v. 80ma. 5/9; 200v. 80ma. 4/-; Cintelcel-midgts. 125v. 120ma. 6/6; crystal diodes. 3/6; bank of 20 res. and conds. plus 3 Westcoats. 5/6; 100 new tubular condensers. assorted. 7/6; 100 res. on tag boards. 10/-; Toggle switches, 1/- ea.; Selectors. IP. 9w. 2/6; 5B, IP. 12w. 6/6; Panel lights. clear, 1/- ea.; VCR. 139A. with holder. screen and cover glass. 50/-; Indicator units. brand new. with CR97, less valves. 23. carr. and packing. 8/6; 24in. meters. 0-40v 8/6, 0-20v 8/6, 0-20a 8/6, 50-0-50a 8/6; 31in. 0-100ma. 15/-; all flush type. 6in. dial. AC. 0-300v. 45/-; ditto. 0-50a. AC/DC. 45/-; Sangamo Weston. 6in. dial. 0-150v. 1ma. PSD. 1.000 OPV. oak case. 24/10; hand generators. 230v AC. for bells. etc. 10/-; Valves. most surplus types in stock at current surplus prices. Special offer: soiled VR858. dirty but unused. 18/- doz.; 5H7. original cartons. 6/- ea.; 6H6. 4/-; EF54. slightly soiled. 5/-; Deaf-aid Valves. XH. XL. 5/- ea. new; 9D2. 8D. 6/- ea.; ISD2. 8/6; 4D1. 5/-; 12AG. 7/6; VU39. 9/-; All types plugs and sockets in stock. S.A.E. for lists. Large stocks lenses. etc. and optical gear. H. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

EKCO TS46/1 T.V. London. perfect. less tube. 227/10/-; 6in. T.V. Chassis. Birm. complete. less p. pack. 212/10/-; 3in. Oscilloscope. 27/10/-; 6/12v Car Radio. new (BC46145). 26/-; new Valves. Speakers. Meters. etc. S.E.I.C. "D" Multirange Meter. 27/10/-; R1155 Chassis. 50/- S.A.E. please. DAVIS. 34. High St., High-worth, Wilts.

TV SOUND ADAPTOR receives TV sound on your radio; cheap and simple. For simple and constructional details send P.O. 2/6 to L.T.H. RADIO, 18, Mount St., Wigan.

6 ELEMENT Midland Aerial for sale; 40ft. hinged mast. Write, WHITWAM. 301, Leymoor Rd., Golcar, Huddersfield.

OSCILLOSCOPE, W.W. (May, 1948), from unit 6, complete with circuit. 210. 19, Marley Ave., Bexleyheath Kent.

RADIO AND T.V. Constructors. For Components, Technical Advice, Receiver Alignment, Rewinds, etc. contact GLYNDON RADIO SERVICE, 63, Glyndon Rd., S.E.18. (WOO. 2749.) S.A.E. for list.

FRESH STOCK CONDENSERS, 450v. 8 mid. 2/6; 16. 3/3; 8 x 8. 4/-; 8 x 16. 4/3; 16 x 16. 4/6; 32 x 32. 6/-; 500v. 8 mid. 3/-; 16. 4/-; 1-350v. 6/- doz.; 1-500v. 7/- doz. Co-axial Cable, 1in., 80 Ohm. 1/- rd. Semi-midg. V. controls. 1 sp., 50 K. 4-meg. and 2-meg. 2.3. Rectifiers. 5Z4. 5Y3. 6X5. 9/- each. Special offer. 6KGT in original cartons. 4 for 23/6. List available. D. F. STRANGE. 52, Pendestone Road, London, E.17. (Mail only.)

HOME CONSTRUCTORS, short-wave radio or television. Send for free list components, valves kits, speakers, etc. THE RADIO EQUIPMENT COMPANY (P.T. Dept.), Castor Road, Brixham, Devon.

RATES

3/- per line or part thereof
average five words to line,
minimum 2 lines. Box No.
6d. extra. Advertisements
must be prepaid and addressed
to Advertisement Manager,
"Practical Television," Tower
House, Southampton St.,
Strand, London, W.C.2.

6-12 VOLT AC/DC midget geared Camera Motors, boxed, brand new. 6/-; "Wearite" type Yaxley Ceramic new 3 pole, 4-way Switches. 2/3; "Viewmaster" Edison-Plessey new Scan Coils. 23/6; special octal M pin 913A photo tube new Holders. 1/9; "Sprague" double 1 mfd. 2,000v. working Condensers. 4/-; "Sprague" single tubular television 1 mfd. 800v. working. 1/3; "Sprague" tubular 1 mfd. 600v. working. 1/- and 2 watts. 10/6 per 100; assorted mica and silver mica Condensers. 10/6 per 100. Cash with order; all new goods; post paid. JACK PORTER LTD., "RADIO," 30/31, College Street, Worcester.

PREMIER Magnetic Television; 12in.: new; no cabinet; offers. 7, Henry Rd., Slough, Bucks.

CANNED Cored Formers, 3in. x 2in., 6-eyelitted base and tag panel, 2/3 ea.; Polyesterene 3in. cored, tagged Formers, 1/-; 4p. 3w. new switches, 8/- per doz.; EF42 type Valves from 10/6. BEL, Marlborough Yard, Archway, N.19. (ARC. 5078.)

50 SECONDHAND Televisions always for sale; famous makes. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (Por. 3497.)

40 GERMANIUM Diode Circuits. 3/2. S.A.E. for lists. Also Components. Valves, etc. WESTWOOD RADIO, Westwoodside, Doncaster.

RELIABLE Mail Order Service.—Viewmaster components, instructions. 7/6; engraved Knobs, white 1/6, brown 1/3; Morganite Resistor Kits. 36/3; Perspex colour code free; Potentiometer Kits. 28/6; T.C.C. Condensers. London. 27; others 7 gns.; Console Cabinets. 28/10/-; carriage extra; B.V.A. Valves; Adcola Irons. 22/6. No ex-Government goods. C.T.S. ELECTRONICS, 1, Pitlake, Croydon.

MASTS.—No. 1 is 28ft. in 4 sections of Paxolin tubing, max. diam. 3in. at base tapering to top, rustless metal ferrules. 35/-; No. 2 is 32ft. in 7 sections of 2in. diam. dural tube, only 45/-; either carriage paid. Sorry, no guys available. R. G. FANOURT, Kilburn, Derby.

"VIEWMASTER" Valves, complete set for 26/2/6. Coax Cable. 4in., 80 ohms, 1/- yard. Steel. Cad. Ptd. chassis. 10in. x 8in. x 2 1/2in. 6/6. Electrolytics. 500v. 8 mf. 2/9; 8 x 8. 3/9; 16. 3/6; 450v. 8 mf. 2/6; 16. 3/6; 8 x 8. 3/6; 8 x 16. 4/3; 16 x 16. 4/6; 32 x 32. 6/-; Bias. 25-25. 1/6; 50-50. 2/3. Valves, new, boxed. KT81. 10/6; 5P81. 6/-; E9B1. 8/6; EF91. 9/6; ECL80. 10/6; EF50. 12/6; DCC90. 14/6; 5Z4. 9/6; 6X5GT. 8/-; Hundreds other types in stock. Non-Mag. Spkrs., 5in., 12/6; 8in., 14/6; 10 in., 19/6. New list available, stamp please. RADIO UNLIMITED, Elm Rd., London, E.17. (PHONE: KEY 4813.)

HANNEY OF BATH offers: Viewmaster, complete kit to designer's specification. 231, or may be purchased in stages at prices detailed in our current list. WB200. 18/6; WB101. 6/-; WB102. 18/6; WB103. 42/-; WB104. 15/6; Frame Trans. 35/6; Line Trans. 32/6; Scan Coils. 23/3; Focus Rings. 22/6; Width Control. 10/-; Boost Choke. 5/9. Westinghouse Rectifiers. 36EHT100. 29/5; 36EHT45. 22/6; 36EHT50. 24/10; 14A86. 20/4; 14D36. 11/7; WX3 and WX6. 3/9 each. Bulglin Kit. 13/6; Morganite Resistors. 35/3, or type "T" 6d. each; type "R" 8d. each; type "Q" Pots. 5/- each; 6 Colvern Pots. 22/6; CIR 90. 3/3 each; CLR. 4089. 22. 6/4 each. T.C.C. Condensers, complete kit. 27/7/-, or any single condenser sold separately; price as per instructional manual. Wearite Coils for all channels, including Wenvoe. 30/-, including choke. Constructor's Envelope for all channels. inc. Wenvoe. 7/6. Complete set of BVA valves to specification. 212/10/4. Cathode Ray Tubes. 9in., Mullard MW22-16-17-18 and Mazda CRM92. 213/13/8; GEC 6504A. 214/16/5; 13in. Mullard MW31-16-17-18. 218/4/10; Mazda CRM121A and 121B. 218/4/10; GEC 6705A. 219/7/8. Regret no C.O.D. on Tubes. Wireless World TV Receiver, set of 20 coils, all channels. 45/-; Formers for these coils are also available, also Pots. Resistors and Condensers as specified by the designer. Send for our current list which gives details of Components for "Wireless World," "Electronic Engineering," "Practical Wireless" and "Practical Television" TV Receivers. Take advantage of our large stocks now and save yourself time and trouble. Goods sent C.W.O. or C.O.D.; all goods post free over 22, but 2/- is added to all C.O.D. orders under 25. L. F. HANNEY. 77, Lower Bristol Rd., Bath. (Telephone: 3811.)

80 OHM CO-AX., thin. 10d. yd.; BR55. 3/-; 20 p. 1% sil. mica. 5d. List. OTRIDGE, 21, Southdown Rd., Bath.

6in. TELEVISION CHASSIS; perfect working condition; "X" aerial and feeder. 220, or offers. 60, Albany Rd., Norton, Stockton-on-Tees.

"VIEWMASTER" Valves, as specified; all guaranteed brand new and boxed, comprising 5 EF50. 1 K761. 1 6P25. 1 EBC33. 1 EB91. 2 6K25. 1 6P28. set of 12. 26/9/6; PL38. EY51. 1 6B6. 10C1. 6C9. 157. X78. ECH21. 13/6; ECL80. 10P13. 10LD11. 10F9. 6F15. ECR91. 7C5. 7C6. 7B7. 7H7. 12/6; K761. DAC32. 50LGT. 52-4G. UP41. UBC1. 10/6; AZ31. 7Y4. UY41. U404. U9/10/-; EF91. 6AM6. 6F12. 6V8GT. 9/6; EB91. 6AL5. 9/-; Miniature all-diy Battery types. 155 (DAF91). 1R5 (DK91). 1T4 (DF91). 3V4 (DL94). 8/9 each; EF39. EF50. EF8. KT2. 7/6; 6K7G. HVR2A. 2D4A. G/6; 9D2. 4/6. All valves guaranteed brand new and boxed. C.W.O. Post paid 40/- READERS RADIO. 24, Colberg Place, Stamford Hill, London, N.16.

BUILDING a Signal Generator? We regret delay to earlier clients. Now offer ex. stock our Oscillator units. 100 kcs. to 100 mcs. 1% 59/6; Attenuators. 22/6; Directly Calibrated Scale. 9/6; Pointer. 1/6; Circuit diagrams, etc. incorporating Line-Frame-AF Modulation. 4/6; s.a.e. literature. M.L. 5, Hyde Rd., Maidstone.

WALNUT Console Tele. Cabinets. 12in., fitted doors, fraction of cost; ex. leading manufacturers stock. 27; suit Electronics, Viewmaster, etc. SOUTHERN ELECTRONICS CO., 65, Wyndham Rd., London, S.E.5.

(Continued on page 46)

CLASSIFIED ADVERTISEMENTS

(Continued from page 45)

BARGAINS: Condensers 32/32 mfd. 350v.w./2V; 8/500. 2/6; 50/50. 2/6; 16-8-4-4/500. 7/6; 16-24/350. 5/-; 1/450. 1/9; 5/2.5kV. 3/-; 25/2kV. 2/-; Variables: twin 500pf. 5/6; with trimmers. 6/6; with drive. 6/6; single. 3/6; 4 gang. 7/6; 75pf D.E. 2/-; twin 75 pf. 4/-; single 50pf. 1/3; 25pf. 1/3. L.F. Trans. (for EHT. 2kV). 7/6; Fil. Trans. 2v. 2a. 6/-; IPT's. 0/13mes. canned. new. 1/6; Epicyclic Drives. 1/3; with pointer. 1/6; Spindle couplers. brass. flexible or insulated. 9d. Alladin in. Formers (wound 30mes). cored. 10d. Linecord. 3a 3-way. 1/- yd. Rotary Toggles. 1/-. Pre-amps type 6048. 17/6. less valves. 8/6. Formers. in. pax. slugged. 2in. x in. 4 for 1/3; Valves at 3/6: VU111. CV54. VU120A. 2X2. VR85. VR65A. VR66. VR135. 6H6. VR21. 9004. VS70. 954. 956B; at 5/6: EF51. EF54. EC52. CV66. 6SH7M. 6AC7. EF36. 12SK7. at 2/6: EA50. 7193. EB34. Most parts for "Argosy" in stock. C.W.O., postage extra. Queries s.a.e. pl. W.A. BENSON, 308. Rathbone Rd.. Liverpool, 13.

A FEW Television C.R. Tubes, 9in. made by G.E.C., brand new and tested: bargain, 27/15/6, carr. paid. R. MORTLOCK, Yaxley, Suffolk.

A £1 in the hand—Send me that list of Valves you have for disposal and I will by return post offer you the best price for them. No lot too small or too large. NORMAN H. FIELD, 68, Hurst St., Birmingham, 5.

PREMIER 12in. Televisor (London). less tube and cabinet. £20. ROBINSON, 2, Coteford Close, Loughton, Essex.

RADIO G200 ANNOUNCES

VALVES—NGT1. GDT4c. CV18 RK31/2C34. EI198. VR92. VR78. 3/9. or 6 for £1. KT61. KT86. IA5. 8K7. 6M7. 6S1T. 12SG7. 6SK7G. 12SG7. KT14. EF22. W143. W148. 6J5GT. EF54. EC52. EF36. 9006. 7S7. 7B7. 7H7. 7K7. 7C6. 14S7. 7Y4. 7/9. X61. 6Q7gt. 6R7gt. 6L7. 3B71291. 6B6G. 6CDE. 277. 6AM6. 6F12. 6B9. EF91. HF6. EPC. ECL30. 11/6. 6V6gt. 6AC7. 6K6gt. 6J7. 12AG. Fan6. 2A3. 6B1. 6U9g. 6SG7. 6X5gt. KT41. 7A3. 42MP12. 420T. A70C. APP4B. N41. PT4. VU39. MU14. 12AT7. 12AU7. 12AX7. 9/6. 3A4. DL93. DL92. N17. 354. 3Q4. DL95. N18. N78. ZD17. 1S5. DAF91. W17. 1T4. D91. W77. EF92. 9D6. X17. DK91. 1R5. D77. 6AL5. 6D2. EB91. DH77. 6AQ6. 6AV6. 9/-.

Post 6d. Registered Post. 10d.

ARTHUR HOILE

55, Union Street, Maidstone, Kent

Phone: 2812

VALVES, new and guaranteed: 6J6. 6AK5. EC91. EY51. EL91. X78. 15/-; 6BA6. EF42. 12/6; Z77. EF91. EF92. 11/6; 807. VR105/30. 6P6. CV53. EL35. KT133C. 10/-; EB91. D77. 9/-; 6AG5. 6SP5. VR150/30. 6N7. 8/6; 1L4. 3A4. EF50. EF54. 7/6; 6J7G. 3D6. 6/6; 954. SP61. 4/-; special. 3 EA50 for 6/-; 3 6J5 for 15/-; 3 6L6 for 30/-; Pre-amp Transformers. 200v. 30 ma. 6.3v 1.5a. 10/-; Pre-amp Chassis. 5 1/2in. x 2 1/2in. x 2in., totally enclosed type. 1/3. Ribbon Feeder. 300 ohm. 7/6 doz. yds. Mains Transformers. 425-0-425v. 350 ma. 6.3v 9a. 4v 6a. 45/-; Condensers. .02 mfd. 5,000v. 1/6; 25 mfd. 2,500v. 3/-. Post 9d. under £2. ELECTRAD RADIO. 69, High St., Belfast, N.I.

VIEW MASTER (London). in working order. complete with cabinet. valves, pre-amp S/H tube. £30. or offer. C. M. SHEPARD, Bishop's Sutton, nr. Aylesford, Hants.

T.V. CONSOLE Cabinets. Radio-grams. L.S. Assemblies. etc. All requirements catered for up to the new 16in. tube. Write or phone ASHDOWN, 98, Hertford Rd. Edmon- ton, N.9. (TOT. 2621.)



One coil, 4 circuits. Simple receivers from a crystal set to a 3 valver. Full circuits enclosed. T.R.I. Coil. 5/- P.P. 6d.

HILLFIELDS RADIO
8, BURNHAM ROAD,
WHITLEY, COVENTRY

Learn TELEVISION



Big wages or extra spare time money can be earned in the growing television field. This fully illustrated and up-to-the-minute work covers every aspect of tele-

vision, with special chapters on installation, aeriels, servicing, interference, etc. This practical, easy-to-read book offered on our special 5 days Post Paid 26/- approx terms—money refunded if you do not wish to retain. OR SENT C.O.D.

A. THOMAS & CO. (T)
111, Buchanan Street, Blackpool.

CHASSIS, fitted on/off switch, transformer, choke, condensers and tag board; last few to clear 12/6, post free. R. MORTLOCK, Yaxley, Suffolk.

WANTED

WANTED, Valves, small or large quantities. 6K8. 6V6. 5Z4. 6AC7. 1K5. 1S5. FW4. 500. 6Q7. 12K8. 80. VU39. EBC33. 3S4. etc. etc. Prompt cash. WM. CARVIS, 103, North Street, Leeds, 7.

WANTED, "Practical T.V." Nos. 20 and 21. GIBSON, "Berca," St. John's, Narborough, Leics.

EDUCATIONAL

TELEVISION Servicing and Theoretical (postal) Courses at extremely moderate fees are available from the Institute of Practical Radio Engineers, either for study or as reading matter only. Syllabus post free from the Secretary, I.P.R.E., 23, Fairfield Road, London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the College operated by Britain's largest electronic organisation. Moderate fees. Write to E.M.I. INSTITUTES, Postal Division, Dept. PT28, 43, Grove Park Road, London, W.4. (Chiswick 4417.) Associated with H.M.V.)

COAX. CABLE (Midget) Ediswan. Standard lin. diam. All values. Long 80 ohm. spindle. Guar. 1 yr. Less Sw. 3/- 10d. yd. Sample 3d. S.P. Sw. 4/- D.P. Sw. 4/9.

VALVES—New, boxed and guaranteed. 6K7 7/6 6K8 12/6 1S4 9/6 EP55 13/6 8X5 9/6 6V6 10/6 1S5 9/6 MD4 10/6 5Z4 9/6 6Q7 11/6 1R5 15/6 6J7 9/0 807 12/6 1T4 9/6 3524 11/6

100's of others. Bargain Lists. 3d.

ELECTROLYTICS—Brand New, best makes, all values. 8450 v. B.E.C. 2/6 8+8 450 v. B.E.C. 4-16 450 v. T.C.C. 3/6 8-16 450 v. T.C.C. 5-16+16 450 v. B.E.C. 5/6 25 25 v. B.E.C. 1.9

RESISTORS—1 w. 4d. 1 w. 6d. 1 w. 8d. **SOLDER**—M-core, 60/40 grade, 16 g. 4d. per yd. 1lb. reel 11/6.

SPEAKERS—P.M., less trans. 3in., 12/6. 5in., 13/6. 8in., 14/6. 8in., 15/6. All items P. and P. 6d. extra. £1 orders post free. **T.R.S., 71, MEADVALE ROAD, EAST CROYDON, CROYDON.** Callers: 307, WHITEHORSE RD., WEST, CROYDON. THO 1665.

NOW READY

For the

VIEWMASTER

(KIRK O' SHOTTS)
SETS OF COILS
WIDTH CONTROLS
BOOST CHOKES
RF CHOKES

OLYMPIC RADIO COMPONENTS,

COIL WINDING SPECIALISTS

224, HORNSEY ROAD, HOLLOWAY, N.7

Phone: NORTH 2914.

RADIO EXCHANGE CO.

THE NEW 1355 CONVERSION . . . The now famous self-contained TV receiver. Data for all Five TV channels, 3/- per copy.

MAINS TRANSFORMER, as specified, 52/6.

1355 RECEIVERS in original crates, 55/-

BRAND NEW STROBE UNITS with six EF50 (mostly red), four EA50, 5Z4, dozens of resistors, condensers, pots, etc., 79/6. (Dimensions 18 x 8 1/2 x 7 1/2.)

POWER UNIT 532. Containing 5Z4, VU120 EHT rectifier (5,000 v., 2 v. indirectly heated), two transformers, one smoothing choke, high resistance relay. 1. 2 1/2 kV. condenser, two other condensers, etc., etc., complete with our 50 cps conversion data for EHT or H.T. (approx. 450 v. at 90 mA), 17/6.

9, CAULDWELL STREET, BEDFORD. Phone: 5569.

YOUR Problems SOLVED

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed.

TUBE FAULT

"I have had my Philco television set (model No. T1551) just three months and have been receiving a good black-and-white picture from Holme Moss until recently. Now I find at the commencement of a programme the picture is quite good, but deteriorates after about one hour viewing into a sepia picture. What should be white is a warm cream, and black becomes dark brown. I would be much obliged if you could enlighten me whether this trouble is a fault in the C.R. tube which is fitted with an ion trap."—R. H. C. (Sheffield).

The trouble is almost certainly in the tube itself, as there is nothing else that can possibly affect the colour of the picture apart from a chemical change in the screen phosphors. Apparently there is a change of some sort occurring in the screen materials after an hour's scanning or so. As the receiver and tube are still under guarantee, you should contact your dealer and get the tube replaced as soon as possible.

THE "ARGUS"

"I am constructing the Argus television receiver, and I have an American type 5 $\frac{1}{2}$ in. 5 C.P.I. cathode-ray tube which I would like you to tell me if it would be all right to use.

"Please let me know the voltage for the heater and the anodes for the tube?"—A. J. Evans (E. Croydon).

The 5 C.P.I. can be used but the whole of the C.R.T. network will have to be altered as the tube requires a minimum of 4,000 volts E.H.T. The heater is 6.3 volts. The base connections numbering from the key in a clockwise direction are: 1. Heater. 2. Cathode. 3. Grid. 4. Blank. 5. Anode 2. 6. Blank. 7. Y1. 8. Y2. 9. Anode 1. 10. X1. 11. X2. 12 and 13. Blank. 14. Heater, side connection intensifier.

MODIFICATIONS FOR CHANNEL 2

"I enclose drawings of a Houghton and Osborne television for which the coils are for Sutton Coldfield. As I now want to change them for Holme Moss, I should be glad if you could supply me with the coil data for Holme Moss, as I have already written to the above people but I have never had a reply from them. The set was built in 1950."—F. Naylor (Nr. Wakefield).

You need only modify the turns slightly on your coils to make the set suitable for Holme Moss. For every 5 turns on a coil at present, add another 1 $\frac{1}{2}$ turns; this applies to the sound rejectors as well. The tapping points on these latter is central as before. Nothing else need be modified in the circuit.

NO DANGEROUS RADIATION

"I purchased a 9in. table model television set a few months ago and have found that on the other side of the

wall behind the set the lime which had been put on the pantry wall 12 months before has now turned a vivid yellow in colour in a circle on two walls.

"There is no other explanation to account for this strange fact other than the TV set.

"What I am actually worried about is, if these rays are emitting from the back, are there any rays which come from the front and, if so, are they injurious to health, as we have a very small baby in the house?"

"Have you heard of this before and can you give me an explanation?"—R. Owen (Sheffield).

The discoloration of the pantry walls behind the television set is a rather unusual phenomenon, but it appears to be the result of having the receiver in its present position. No obvious explanation is possible without examination and careful analysis, but there are no rays emitted from the normal television receiver that are injurious to health, either from the back or the front.

VIEWMASTER ON D.C.

"I have recently had the opportunity of watching a 'Viewmaster' television receiver in operation and would like to build such a set for myself, but observe that it is designed for operation on A.C. mains only.

"My home supply is 230 volts D.C. and I was wondering if you could kindly inform me whether it is possible to modify the 'Viewmaster' circuit for operation on this type of mains by arranging for the heater circuits in the usual way, etc.?"—R. C. S. Tugwell (Epsom).

It is not possible to modify the "Viewmaster" for use on D.C. mains since this would involve a complete redesign of the receiver. We can, however, recommend the use of the "Viewmaster" with a converter of either the rotary or vibrator type and have received many excellent reports of reception on D.C. mains. If a vibrator type converter is used, then it is necessary to fit a full-wave rectifier instead of the half-wave rectifier normally specified.

HEATER-CATHODE SHORT-CIRCUIT

"As a reader of your 'Problems Solved' articles, I have not as yet come across a peculiar fault that has developed in my particular set—a commercial one. At times the set will run with a clear picture, but on odd occasions it will suddenly go out of focus with streamers going to the left. This may persist for the whole evening programme. On another occasion this defocusing may only last a minute or so and the picture will snap back clear again; this may occur two or three times. I would like to add that I tested the cathode to the filament of my tube and got a dead short reading on my ohmmeter, but I run the set for five minutes and test straight after switching off and there is no short for about five minutes and then it appears as before. The signal is injected to the cathode on my particular set."—F. Fleetwood (Ilford).

The fault is due to the heater-cathode short on your cathode-ray tube. You must either replace the tube or run its heater from a small separate transformer. If you decide on the latter, let the heater winding float completely, rather than connect the heater and cathode together.

"VIEWMASTER" BOOSTER

"Can you assist me in locating fault of 'Viewmaster' which I have recently finished which is as specified and all new material? It does not give desired width as I have a border each side the screen about $\frac{1}{2}$ in. width, and controls will not move it. I have tried all your instructions to alter same, such as M.R.4 rectifier, scanning coils,

valves, C42 condenser, line transformer, M.R.2 rectifier, which, according to the working of same, is loss of E.H.T. I cannot get boost volts as compared from your instruction book. Hoping you can assist me in this matter and oblige."—N. Green (Darlaston).

We assume from your letter that you are unable to measure any boost volts across C42. If this is the case then very obviously the line scan will be short. If, as you say, there is no fault in the line transformer M.R.2 rectifier, or C42 condenser, then we suggest that there must be a faulty connection somewhere in your line scan circuit, though we are unable to advise as to its exact location. We suggest disconnecting all components around the line transformer, checking each component individually, and carefully re-wiring.

POOR SYNC

"I have made a 'Premier' television set, 'Holme Moss' model, using a VCR97 tube. The sound reception is very good, but I cannot get any satisfactory results from the vision side. The vision signal is present, and I can hear it through a pair of 'phones connected to the end of the coaxial cable to the tube and to earth. When the brilliance is turned down and contrast up the modulation is there on the tube, and a raster at other times when brilliance is at full and contrast down, which completely fills the screen.

"For the first five minutes or so a picture appears but it does not seem to fill the tube, either in height or length, and it keeps moving downwards as if on a revolving drum, and then when the set has got warmed up disappears and on the screen appears a complex pattern of little dots and streaks. I have an idea that it is the timebase that is wrong somewhere. I have checked all the wiring, and moved the valves around, etc., as instructed in the 'Premier' book, and the picture is reduced even further in height and width when these are removed, also I have tested all the condensers but not resistors, having no meter available."—G. Shore (Huddersfield).

The receiver appears to lose synchronism, even though the vision signal is still present. The cause may be, of course, a fault in the vision strip itself which causes the signal strength to fall after a short while and so allows the set to lose synchronism; you should check on the valves in this strip by changing each in turn with one of the sound valves. If there is no improvement, check on the sync separator circuit, as both your line and frame appear to be equally affected. Finally, your H.T. supply may be failing, and, if possible, you should borrow a voltmeter in order to check on this.

VALVE-PIN CONNECTIONS

"I am in the process of building the 'Viewmaster.' There is a point that I am not quite sure about, valvholder No. 4. Are the tags of the holder (Nos. 3 and 6) bent over and soldered to the chassis? It looks as if they are in the drawing, though there are no instructions to this effect. The shop where I bought my kit of parts say they are, but did not seem too sure about it. I should be pleased if you would assure me on this part."—H. E. Barrow (Beckenham).

Tags Nos. 3 and 6 on valvholder V4 are connected to chassis and for convenience may be bent over and soldered direct to chassis or, if preferred, a very short wire may be used.

LINE WHISTLE

"I am having trouble with my Marconi TV and would be grateful for any advice that you can give me. The trouble is that my picture breaks up or moves irregularly across the screen, leaving for a few moments a black strip about 1in. wide at the right of the picture.

"The trouble gets worse during interference, and there is a persistent high-pitched whistle. I have tried correcting the trouble with the pre-set controls, but this only holds the picture for a short time."—E. Hudson (Hendon).

The high-pitched whistle from your receiver is the line time-base output valve circuit, and you will have to screen it with some absorbent material if you wish to eliminate this. You must take care, however, that the heat of the valve can be dissipated away safely. The slipping of the line hold points to a faulty sync separator valve or line oscillator valve, and you should check these by replacement.

E.E. TELEVISOR FOCUS

"I have built an E.E. Televisor, and for some time it has been giving very good results, the picture being very clear. It has, however, developed a fault in the focusing. At first, on switching on, the focus was perfect, but a few moments later the picture became all blurred, and altering the control brought it back, until the control would go no farther; now, it wont focus properly at all. To try and counteract it I have fitted a P.M. in place of the electro, but I can't obtain a spot anywhere on the tube neck where the lines would become clear and distinct. It also now has a tendency to pull what lines there are to the left, making everything pointed. I thought it would be the electro condensers leaking and I replaced these, but they have made no difference. I also replaced the E.H.T. condenser; this didn't alter it any. I have replaced both the line and frame amplifier valves. Hoping you can help."—A. Heaven (N.1).

It is not clear from your description as to whether a fault has developed in the focus circuit itself or in some other section.

If you find that it is now necessary to reduce the value of R.91 to bring the focus in, the fault may be due to a variation in the H.T. supply, in which case the size of picture would vary and it would become smaller, or, if it was due to a fault in the E.H.T. supply causing the E.H.T. to fall, then the picture would become larger.

An indication of the type of fault which is occurring may be obtained by noting whether R.91 has to be reduced in value or increased in value. We suggest checking whether the picture is in fact becoming smaller or larger during those periods that it goes out of focus. If the picture becomes larger, then it is due to a fall in E.H.T., whereas if it becomes smaller it is due to a fall in H.T. If possible, voltage measurements should be carried out from the grid of the cathode-ray tube to chassis to check whether there is any change during the periods when the picture is in focus as compared to the periods it is out of focus.

You mention that there is a tendency to pull the lines to the left, making everything pointed. We are not clear by what is meant by this, but if the left side of the picture is narrower top to bottom than the right side, then it would indicate that a fault has developed in the scanning coils.

THE MODERN BOOK CO.

The Oscilloscope Book, by E. N. Bradley. Price 5s. 0d., postage 3d.
 Television Principles and Practice, by F. J. Camm. Price 25s. 0d., postage 8d.
 Television Receiving Equipment, by W. T. Cocking. Price 18s. 0d., postage 6d.
 Television Engineering, by D. G. Fink. Price 72s. 6d., postage 1s. 0d.
 The Radio Amateur's Handbook, by A.R.R.L. (23th edition, 1952). Price 30s. 0d., postage 1s. 0d.
 Magnetic Tape Recording, by P. A. Tarry. Price 6s. 6d., postage 1d.
 Amplifiers, by N. H. Crowhurst. Price 3s. 6d., postage 3d.
 The De Luxe Home Built Television and Radiogram, by W. I. Flack. Price 6s. 6d., postage 1d.
 Practical Wireless Encyclopaedia, by F. J. Camm. Price 21s. 0d., postage 9d.
 The Principles of Television Reception, by A. W. Keen. Price 30s. 0d., postage 9d.
 Television Explained, by W. E. Miller. Price 5s. 0d., postage 6d.
 The Cathode Ray Oscillograph in Industry, by W. Wilson. Price 18s. 0d., postage 9d.
 Radio Valve Data compiled by Wireless World. Price 3s. 6d., postage 3d.
 The Television Annual for 1952, by K. Bailey (Editor). Price 8s. 6d., postage 6d.
 Radio Television and Electrical Repairs, by R. Norris (Editor). Price 12s. 6d., postage 6d.
 We have the finest selection of British and American Radio books in the Country. Complete list on application.

19-23, PRAED STREET,
 (Dept. T.6) LONDON, W.2
 PADDINGTON 4187

VCR97's !!

Brand new in crates, tested before despatch. Full picture, 39/6; slightly reduced, 28/6. Both types 3/- carriage. Hurry! Limited stock.

AMAZING TRANSFORMER BARGAIN!
 Due to closing well known mail order stores, surplus 300-0-300 80 mA., 6.3 v. 3 a.s. 5 v. 2 a. black compounded, store soiled, but unused and tested. Only 10/9 (L/- post). While they last!


VALVES !!

A—Original cartons. B—Unused and boxed.
 Type A B Type A B Type A B
 6PH6 9/8 — 6K7 7/9 — E134 — 2/6
 6J5 6/9 — 6Q7GT 13/- 11/6 EP33 — 6/3
 6J5GT 6/3 — 6H17 6/9 — Pen. 383 9/9 9/6
 6J7 — 7/- 6V6GT 12/6 10/- 4K34 2/6 3/-
 6K8GT 8/6 — 80 — 8V 11/11 10/-
 6K7GT 6/9 — 8A30 — 3/5 VU111 3/5
 MANY MORE AVAILABLE! Send S.A.E. for full list of bargains of all kinds.

SCREENED CABLE: Single, 10ft., Twin, 1/3 yard.
 CO-AX. CABLE: 1/4 mm. (for T.V.), 1/1 yard.
 VIEWMASTER: Send for price list.
 METAL TUBULAR: 23 mfd. 500 v., 9d., 8/- doz.
 TRIPLE: 1 mfd., metal block (U.S.A.), 9d.
 VALVEHOLDERS: EP30, 6d., 5/6 doz.; 1.0, 9d.
REED & FORD, AINSDALE, SOUTHPORT

When you are planning to use
**ALUMINIUM, LIGHT ALLOYS,
 BRASS, COPPER, BRONZE,**
 remember . . . you have a
 choice of 3,000 stock sizes of
**TUBE, ROD, BAR, SHEET, STRIP,
 WIRE, ANGLE, CHANNEL, TEE**
 at

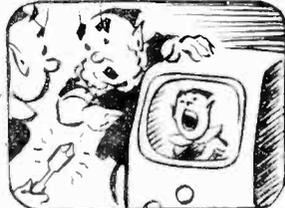H. ROLLET & CO. LTD.
 6, CHESHAM PLACE, LONDON, S.W.1
 Phone: SL Oane 3463
 WORKS:
 32136, ROSEBERY AVENUE, LONDON,
 E.C.1.
 KIRKBY TRADING ESTATE
 LIVERPOOL
 "No Quantity too Small"



The "Fluxite Quins" at Work

"Our 'tele's' gone haywire inside,
 This crooner—his mouth open wide—
 Has been like this all day,
 What's it needing?" cried EH.
 "Some FLUXITE at once," OI replied.

See that FLUXITE is always by you
 —in the house—garage—workshop—
 wherever speedy soldering is needed.
 Used for over 40 years in Govern-
 ment works and by leading engineers
 and manufacturers. Of all ironmongers
 —in tins, from 1/- upwards.
 The FLUXITE GUN puts FLUXITE
 where you want it by a simple
 pressure. Price 2/6, or filled 3/6.

FLUXITE

SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT"
 Soldering and for Leaflets on CASE-
 HARDENING STEEL and TEMPERING
 TOOLS with FLUXITE. Price 1/4 each.
 FLUXITE Ltd., Dept. P.T.
 Bernondsey Street, London, S.E.1

TRANSFORMERS

No. 1. 250-0-250v. 80 ma. 0-4v. 5a. 6.3v.
 3.5a. 0-4-5v. 2a., 17/-
 No. 2. As No. 1 but 350-0-350v. 17/-
 No. 3. 28v. 2.5a. tapped to give almost
 any voltage up to
 28v. Ideal for
 chargers, models,
 W.D. motors, etc.
 16/6.
 No. 4. 4v. 9v. 20v.
 4 amp. For 2, 6 and
 12 volt chargers, 15/-
 No. 5. Auto wound,
 10-0-110-200-230-
 250v. 150 watts.
 For general voltage
 changing, up or
 down, 15/6.
 No. 6. 250-0-250v. 100
 ma. 6.3v. 3.5a. 5v. 2a., 22/-
 No. 7. Television Auto with overwind.
 0-200-230-250-290v. 500 ma. 6.3v. 7 amps,
 0-2-6.3v. 2 amps. 38/6.
 All types upright or drop through. No
 others available. Primaries on 1, 2, 4 and 6
 tapped 200-200-250v. interleaved, im-
 pregnated, Screened, Guaranteed.

Terms: C.W.O., C.O.D. or pro forma.
 Postage 1/6 1 to 3.

HILLFIELDS RADIO, 8, BURNHAM ROAD, WHITLEY, COVENTRY

VIEWMASTER
 Exact specified parts at Shopping List
 prices by return post. H.M., B'ham,
 and Scottish. Also valves and tubes.
H.G. RADIO ELECTRICAL CO.
 1350, Stratford Rd., Birmingham, 28
 *Phone: Springfield 2359. Estb. 25 years

SPEAKERS. 10in. P.M. Celestion, 32/-;
 8in. P.M. Plessey, 14/6; 6 1/2in. P.M.
 Truvox, 13/6; 5in. P.M. Goodman, 13/-;
 3 1/2in. P.M. Elac, 12/6.

CONDENSERS.—B.E.C. 32 x 32, 450
 vw., 6/6; B.E.C. 8 x 16, 450 vw., 4/2;
 Dubilier 32 x 32 x 16, 350 vw., 8/6;
 Dubilier BR 850, 8 mfd., 500 vw., 3/-;
 Dubilier BR 1650, 16 mfd., 500 vw., 3/6;
 B.E.C. Midget 8 mfd., 450 vw., 2/9.

VOLUME CONTROLS. Morganite
 w/s 2 meg., 1 meg., 1/2 meg., 4/4

MICA CONDENSERS. .001-.002, 150
 pF., 430 P.M., 5/- doz.

ADHESIVE TAPE. 1/2 lb. tin, 3/4in., 4/-
 per tin.

CO-AXIAL CABLE. 75 ohm per foot,
 1/2 per yd.

MISC. Push-Pull unit, 6 position, 5/-
 Standard, 2 Gang with Drive, 8/-;
 Bulbs, 6.5, 15, 6/6 per doz. Voltage
 Selector Panel, 7d.

RECTIFIERS. 300 v., 60 mA., 6/6.

KNOBBS. Set of three, "Volume,"
 "Tuning," Waveband. "G.L.M.S.,"
 2/- per set.

Mail Order only.
 Send stamp for catalogue.
 Carriage Paid on orders over 4/-
 All Goods Guaranteed.
 Cash with order or C.O.D.

REX RADIO

37, LOUIS STREET,
 CHAPELTOWN ROAD, LEEDS, 7


TELEVISION COMPONENTS

FOR THE
"Practical Television"
**RECEIVER VIEWMASTER
 AND E. E. TELEVISORS**
IN STOCK

Price lists available on request
Prompt Postal Service

J. T. FILMER
 MAYPOLE ESTATE, BEXLEY, KENT
 TEL. Bexleyheath 7267

We have a limited stock of the following
RESISTORS AND CONDENSERS
 1-watt—100Ω, 330Ω, 470Ω, 2,200Ω, 15kΩ,
 30kΩ, 150kΩ, 220kΩ, 270kΩ, 470kΩ,
 680kΩ, 1MΩ, 3MΩ, 3.3MΩ 8/- per doz.
 1 watt—220Ω, 680Ω, 1kΩ, 10kΩ, 5/6 per doz.
 2 watt—3,200Ω, 47kΩ 1/- each
 3 watt—1kΩ, 2kΩ 1/6 each
 Fixed Wire Wound, 2kΩ, 1 watt 9d. each
 Air Spaced Trimmer, 0-100 1/9 each
 Volume Controls, 200,000 Carbon
 Track, N.S. 1/6 each
 Tubular Paper Condensers—0.001, 450v.
 4- doz.; 0.2, 350v.t., 6/- doz.; 0.25, 350v.t.,
 6/- doz.; 0.5, 350v.t., 8/- doz.
 All Osborn O Range Coils in Stock, 4/- each
 Test Prods fully insulated pencil type, each
 prod fused, 4/3
 C.W.O. Postage 6d. up to 10/-, 1/- under 20/-
J. W. PARKER,
 66, DALSTON LANE,
 DALSTON, LONDON, E.8.

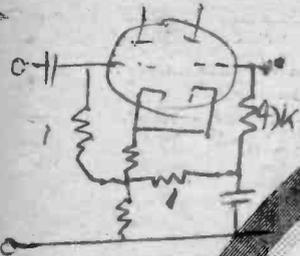


ADVANTAGES OF THE 'ENGLISH ELECTRIC' METAL C.R. TUBES

5. Wide Angle Scanning

The introduction of wide angle scanning has made it necessary to obtain an even higher degree of efficiency in scanning circuits. The requirements of scanning power for the 70° short tube and for higher E.H.T. voltage (14 kV) of which advantage can be taken, mark a considerable departure, as well as an advance in technique, from that necessary for earlier type tubes of 50° deflection angle using lower E.H.T.

By using high Q coils, low loss Ferrite cores, and a "booster-damper" type of circuit, it is now possible to scan fully a 70° tube over the full screen area (Double D) at 14 kV. And it is worth noting that current consumption will be no greater than that required for a resistance-damped scanning circuit driving a narrow angle tube at low E.H.T. voltage.

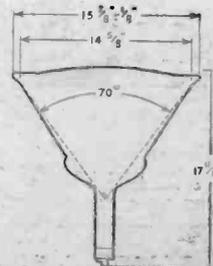High efficiency components are now available for the home constructor, and full technical details concerning them and the scanning circuits may be obtained on application to the address below.



PRICE £24.6.5
Tax Paid

BRITISH MADE BY 'ENGLISH ELECTRIC'

THE ENGLISH ELECTRIC COMPANY LTD., TELEVISION DEPT., QUEEN'S HOUSE, KINGSWAY, LONDON, W.C.2