

OBTAINING A GOOD INTERLACE

PRACTICAL TELEVISION

AND TELEVISION TIMES


1/-

EDITOR
F. J. CAMM

A NEWNES PUBLICATION

Vol. 3 No. 34

MARCH, 1953

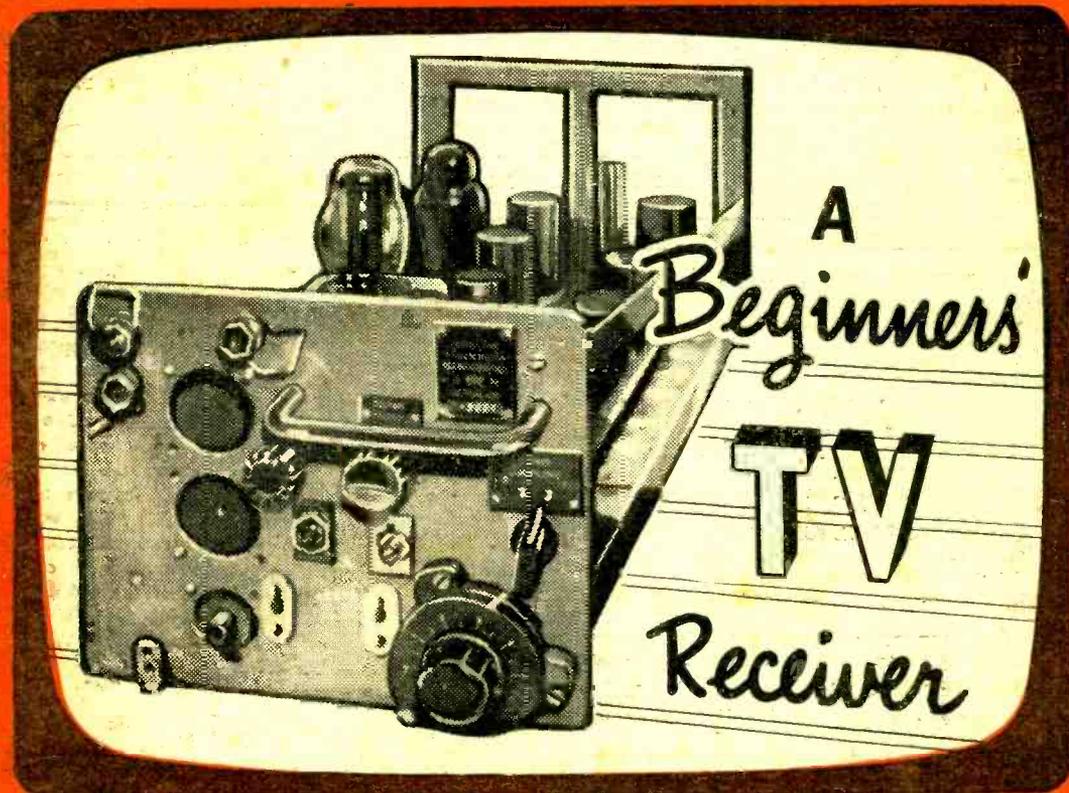

FEATURED IN THIS ISSUE

NTSC Colour System
Hints and Tips on Tuning
TV Society's Exhibition

Making Sound I.F. Transformers
The Wenvoe Transmitter
A Question of Phase

A GENUINE SPECIAL OFFER!

PLESSEY 3-SPEED AUTO CHANGE UNITS
Brand New in maker's cartons, complete with mounting instructions.

£11.19.6

(Normal price is £23/10/0).

- ★ These units will auto change on all three speeds, 7in., 10in. and 12in.
 - ★ They play MIXED 10in. and 12in. records.
 - ★ They have separate sapphires for L.P. and 7 $\frac{1}{2}$ r.p.m., which are moved into position by a simple switch.
 - ★ The size of the unit deck is 14in. x 10in. with 6in. above deck and 2in. below.
- A bulk purchase enables us to offer these **BRAND NEW UNITS** at this exceptional price. Please add 7/6 packing, carriage and insurance.

"PERSONAL SET" BATTERY ELIMINATOR

Complete kit of parts to build a Midget "Alldry" Battery Eliminator, giving approx. 60 volts and 1.4 volts. This is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltage as above or approx. to 60 volts. The kit is easily assembled and is housed in a light aluminium case, size 4 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. Complete kit with easy-to-follow assembly instructions 42/6. We can also offer a similar **COMPLETE KIT** to provide approx. 60 volts and 1.4 volts. Size of assembled Unit 7in. x 2 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. Price 47/6.

COMPLETE BATTERY CHARGER

For charging either 2, 4, 6, or 12 volts at 11 amps. Complete in metal case, and incorporating a limiter resistor. Size 5 $\frac{1}{2}$ in. x 5 $\frac{1}{2}$ in. x 4 $\frac{1}{2}$ in. Complete and ready for use, 52/6.

WE CAN SUPPLY ALL RECOMMENDED COMPONENTS

"VIEWMASTER"


FOR THE

LONDON — SUTTON COLDFIELD — HOLME MOSS
KIRK O' SHOTTS — WENVOE

Specified Components by:—
T.C.C., W.B., Morganite, Bulgin, Westinghouse, Belling, Wearite, Mullard, Mazda, G.E.C., Ferranti, Taiton and W.B. Table or Console Cabinets are also available.

Send 7/6 for the "Viewmaster Envelope," which gives a complete description of this Televisor, including Assembly Layouts and Component Price List.

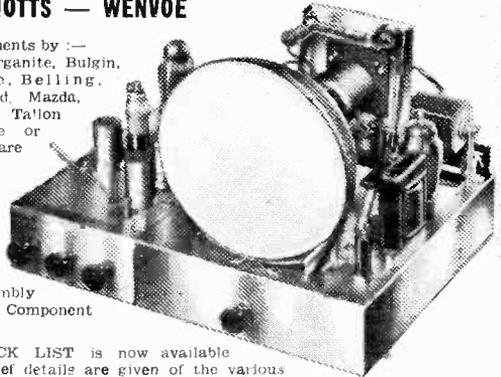Our **NEW STOCK LIST** is now available (price 9d.). Brief details are given of the various **KITS OF PARTS** we are able to offer for the construction of many types of Radio Receivers, Battery Chargers, "Alldry" Battery Eliminators, and "hundreds" of Radio Components.



STERN RADIO LTD.

109/115 FLEET STREET, E.C.4. Telephone: CENTRAL 5812/3/4.

R O M

RIGHT FIRST TIME!

Trial and error is a costly and often disappointing business. For too long the radio amateur has had such methods forced upon him by the high cost of test instruments. The **RADIO MAIL RES/CAP. BRIDGE** has changed all that. For 31/6 he now has at his command an instrument to check each component before use, and ensure 100% results.

THE PRICE OF 31/6 COVERS THE COMPLETE KIT FOR THIS SELF-CONTAINED INSTRUMENT

5 Megohms—50,000 ohms	50 mfd.—2 mfd.
100,000 ohms—1,000 ohms	1 mfd.—.01 mfd.
1,000 ohms—10 ohms	.01 mfd.—.0005 mfd.

NO CALIBRATING


The panel bears six separate scales, one for each range, ready calibrated in ohms and mfd's. for direct reading. Each range is fully variable, covering all intermediate values.

New components, specially selected for accuracy. Instructions and diagrams for easy assembly. Prompt delivery. Cash with order or C.O.D.

**RADIO MAIL, 4, RALEIGH STREET,
NOTTINGHAM**

Stamp with all enquiries, please.

SOLONS FOR ESSENTIAL JOBS!

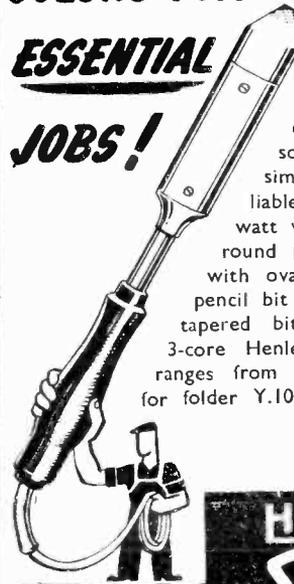


Use **SOLONS** for the jobs that matter—this modern precision tool makes soldering speedier, simpler and more reliable. 5 models: 65 watt with oval tapered and round pencil bit; 125 watt with oval tapered and round pencil bit; 240 watt with oval tapered bit; each with 6 feet 3-core Henley flexible. Voltage ranges from 100 to 250. Write for folder Y.10.

**W. T. HENLEY'S
TELEGRAPH WORKS
CO. LTD.,**
51-53 Hatton Garden,
London, E.C.1.

**HENLEY
SOLON
ELECTRIC**
TRADE MARK
SOLDERING IRONS
FOR INDUSTRIAL USE

SIGNAL GENERATOR TYPE 10

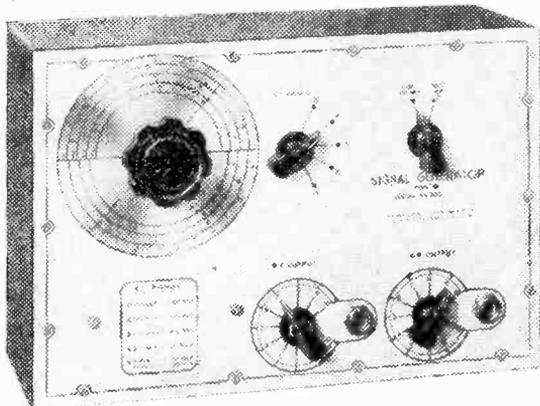

PRICE (U.K. ONLY)

£7-10-0

HOMELAB INSTRUMENTS LTD., 615-617, HIGH ROAD, LEYTON, E.10.
Telephone: LEY 5651

Recently re-designed and embodying many improvements, this is an ideal instrument for constructors and service engineers requiring a thoroughly reliable generator for aligning and testing television and radio receivers.

- COVERAGE 100 KC/S—100 MC/S.
- DIRECTLY CALIBRATED.
- INTERNAL MODULATION 30 per cent.—400 c.p.s.
- C.W. or EXTERNAL MODULATION.
- VARIABLE 400 c.p.s. A.F. SIGNAL.
- ACCURACY \pm 1 per cent.
- A.C. MAINS (double wound transformer tapped 110, 200/230/250 volts).
- GUARANTEED FOR TWELVE MONTHS.
- FULL OPERATING INSTRUCTIONS SUPPLIED.

Illustrated brochure and full details sent on request.

VIEWMASTER

LONDON—MIDLAND—HOLME MOSS
KIRK O'SHOTT—WENVOE & PONTOP PIKE

Still the most popular home constructor design. This is due to the ease of construction—the drilled chassis, full-size diagrams and fully illustrated comprehensive manual for making in 7 easy stages a first-class table or console television for 9in. or 12in. tubes. Send 7 6 now for Constructor Envelope stating for which station. If after examining this you feel that you are not capable of building this receiver we will refund the amount paid in full.

Revised price list of Viewmaster components giving details of the 7 easy stages. 2/6. post free.

"VIEWMASTER" KITS IN STAGES.—Holme Moss, Kirk-o-Shotts: (1) £3 2/3. (2) £2 2/9. (3) £5 2/1. (4) 8 10/4. (5) £10 8/9. (6) £7 5/9. (7) £3 8/7. Sutton Coldfield: (1) £3 3/4. (2) £2 2/9. (3) £5 2/1. (4) 8 10/4. stages 5-7 as Holme Moss. Wenvoe and Pontop Pike: (1) £3 3/4. (2) £1 19/-. (3) £5 2/1. (4) 8 10/4. stages 5-7 as Holme Moss. London: (1) £3 3/6. (2) £2 1/10. (3) £4 9/1. (4) 6 6/4. stages 5-7 as Holme Moss.

MODIFIED WEARITE WENVOE COILS.—We have co-operated with the designer to produce new improved Viewmaster coils for Wenvoe. The latest modified type are now available from stock, price 2/6 - set, postage 6d.

MODIFIED WE FOCUS RINGS.—New improved WB109/3 focus ring for Mazda tubes, 2/6. WB109 2 for Mullard tubes, 2/6.

OUR SERVICE CONTINUES AFTER THE SALE.

ELAC FOCUS RINGS.—R17 for Mullard tubes, 2/-; R20 medium flux for triode tubes, 2/6; R25/6D high flux for triode tubes up to 15 Kv and those difficult to focus. With fine adjuster, 2/6.

Postage extra on orders under £2.

CATALOGUE No. 8.—54 pages, illustrated on fine art paper, containing over 2,000 radio and television lines, 9d., post free.

Southern Radio & Electrical Supplies
85 FISHERTON STREET, SALISBURY, WILTS.

Telephone: Salisbury 2103.

A workshop in your pocket!

FOR ONLY 25/6 POST FREE

THE TELEVISION AND RADIO SERVICE ENGINEER'S MASTER TRIMMER KIT contains:

- 1 End Trimmer
- 1 Side Trimmer
- 1 Yaxley Switch Contact Adjuster
- 1 Low Capacity Trimmer
- 1 Screwdriver
- 1 Set of Feeler Gauges
- 1 Set of six Box Spanners from 1 to 8 B.A.
- 1 Set of Four Spanners from 0 to 8 B.A.
- 1 Durable black crackle finish metal case.



WELDED RADIO CHASSIS

Aluminium Chassis 18 s.w.g., welded corners for added strength. Highest quality manufacture.

- 6" x 4" x 2 1/2", 4 9
- 8" x 6" x 2 1/2", 6 -
- 10" x 7" x 2 1/2", 6 9
- 12" x 8" x 2 1/2", 8 6

Trade Supplied.

J. & S. NEWMAN LTD.
100 HAMPSTEAD ROAD, N.W.1.
Telephone: EUSton 5176/7.



Focus Magnet. With Vernier Control. For any type c.r. tube with 35 mm. diam. neck, 21/6. Less Vernier, 15/-.

Multi-Ratio Frame Output Transformer, 10/6.

Scanning Coils. High impedance frame, low line, 12/6. Plessey. Low impedance line and frame, 25/-.

Line EHT Transformer, with EY51 heater winding, 12/6.

Variable Inductance Width Control, 3/6. Plessey, 6/6.

C.R.T. Rear Neck Protectors, 2/6.

Co-Axial Cable. 70-80 ohms impedance. Single core, 9/- doz. yards. Twin core, 12/- doz. yards. Twin feeder, 6/- doz. yards.

Co-Axial Connectors. For standard 1/4 in. cable, 1/11.

The Latest 12in. Plastic Mask. Incorporating gold finish tube escutcheon, and dark screen filter. Overall dimensions: 13 1/2 in. wide, 10 in. high, 17/6. Post 2/6 extra.

C.R.T. MASKS. Brand new LATEST ASPECT RATIO

- 10in., 7/6
- 12in., 15/-
- 12in. flat face, 15/-
- 14in. rectangular, 21/-
- 16in. Double-D, 30/-
- 17in. rectangular, 27/6.

SOILED OLD ASPECT RATIO

- 9in., 5/-; 12in., 7/6;
- 12in. with fitted armour plate glass (new ratio), 11/6.

ARMOUR PLATE GLASS

- 15in. Actual size 18 1/2 in. x 19 1/2 in. x 3/4 in. 7/11
- 12in. Actual size 13 1/2 in. x 10 1/2 in. x 3/4 in. 4/-
- 9in. Actual size 9 in. x 8 in. x 3/4 in. 3/-

CLOSED FIELD LOUDSPEAKERS

Ideal for television receivers. Less o/trans. 3 ohms. Will not affect your C.R. tube.
6 1/2 in. 15/-
8 in. 17/6

THE TELE-KING

INTRODUCING THE TELE-KING. A laboratory developed, 5 channel, 16in. television receiver for the home constructor.

17. Valve, superhet circuit.

Construction envelope contains full-size wiring diagrams and working drawings together with 32-page instruction book.


All component parts for the Tele-King are standard, and can be supplied separately as and when required.

PRICE PER COPY

6/-

POST FREE

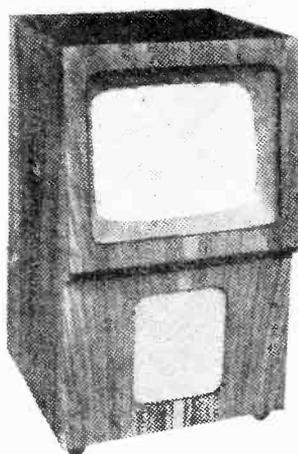Everything now in stock from the Nuts and Bolts to the Cabinet.



LASKY'S RADIO.
LASKY'S (HARROW ROAD), LTD.
370, HARROW ROAD, PADDINGTON, LONDON. W.9.
Telephones: CUNNINGHAM 1979-7214.
MAIL, ORDER AND DISPATCH DEPARTMENTS: 485-497.
HARROW ROAD, PADDINGTON, LONDON, W.10. Telephone: LADbroke 4075.
Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs. half day 1 p.m.
Postage and packing charges (unless otherwise stated); on orders value £1-1s. 0d. extra; 2s.-2s. 0d. extra; £10-3s. 6d. extra; over £10 carriage free. All goods fully insured in transit.

DARK SCREEN FILTERS

Latest Tint

- 12 1/2 in. x 14 1/2 in. for 16 and 17in. c.r. tubes, 25 -
- 11in. x 13 1/2 in. for 9, 10 and 12in. c.r. tubes, 15/-

TALLON CABINETS

for the

VIEW MASTER

ELECTRONIC ENGINEERING & PRACTICAL TELEVISION SETS

MINI-FOUR ● ARGUS P.W. 3-SPEED AUTOGRAM ● CRYSTAL DIODE ● P.M. TAPE RECORDER

"TELE-KING" WITH DOORS

in pack-flat kits or assembled cabinets. Radiogram, Radio and Television or combination cabinets made to suit customer's requirements, in quantities or singly. Tape Recorder Cabinets. Prices and literature on application.

Mini-four Cabinet, Blue Leathercloth, complete with grille and plastic handle ... 14/- incl. postage

JAMES TALLON & SONS LTD.

Consult your dealer or write to:-

(Dept. P.T.I.)

MANOR WORKS MANOR ROAD RUGBY Telephone: RUGBY 2070

TELEVISION COLOUR FILTERS. For 10in. screens, 6/6. For 12in. screens, 8/3. For 15in. screens, 10/9.

TELEVISION LENSES. Magnifies the picture 1 1/2 times. Best quality manufacture. For 8in. and 9in. screens, 5s. ea. For 10in. and 12in. screens, 7s. Tinted a pale blue or Daylight and Anti-glare viewing, 5/- extra. Post and pack., 2/6.

RADIO-GRAM CHASSIS. 5-valve, all-wave, superhet. Tested and guaranteed. Resprayed. Complete with all valves, less speaker. End drive model, £7 17/6. Carr. 5/-. Also brand new and unmarked 1953 radiogram chassis. Export model (six wavebands), £15 15/- Home market model (three waves), £10 17/6. Carr. 5/-.

T.V. TUBES. Any size. £5. Moderate fitting charge. Personal callers only.

TRANSFORMERS. Mains Store soiled. 260-0-260. Two heaters, 6.3v., 3a., and 6.3v. 1.5a. Tapped 240, 210 and 110. Load 80 m/A. Resprayed, tested and guaranteed three months. Wire-ended. New reduced PRICE, 9/8. post 2/-. Also standard O.P. transformers matching to 2-5 ohm speech coil. Bankrupt stock price, 2/9. post 1/3.



CONDENSERS. Two-gang, .0005 mfd. Store soiled. Standard and half size. All tested. Bargain PRICE, 2/9 each, or special offer of three for 7/-, post 6d. Also brand new (boxed) single tuning condensers, .0005 mfd. at 2/9, post 6d.

EXTENSION SPEAKERS. Brand new 5in. P.M. speakers, mounted on latest type polished baffle stand with gold-sprayed metal fret. 19/9, post 1/9. Also available in totally enclosed cabinet type stand at 25/-, post 1/9.

VALVES. Surplus and salvage. At 11/9: 6T1C, PL91, PL82, PL83, PY80, PY82; at 10/9: 6BW6, 6BR7, 6X4, 11A, 50L5, 10M4; at 8/9: EF41, EI41, 3V4, 1S4, JS5, IR5, IT4, 10F1, 6F15; at 6/9: EB91, EF92, KTW61, RK172. Many others.

INSULATING TAPE. Brand new and wrapped. 1 1/2 in. wide. In 1/2 lb. rolls, 1/6, post 6d.

PERSONAL RADIO. 4-valve TRF kit. Excellent reception on Long and Medium bands. Full wiring details and assembly instructions. Plastic or wooden cabinet. Complete for £5.19.6. carriage 3/6. Assembled ready for use, 20/- extra.

Stamp for 1953 List.

C.W.O. or C.O.D. **DUKE'S** 621, Romford Road, London, E.12. (Grangewood 6377) Money Back Guarantee

The **AVO** ELECTRONIC TESTMETER



This instrument has been developed to meet the growing demand for an instrument of laboratory sensitivity built in a robust and portable form, for use in conjunction with electronic and other apparatus where it is imperative that the instrument should present a negligible loading factor upon the circuit under test.

The instrument consists basically of a balanced bridge voltmeter. It incorporates many unique features and a wide set of ranges so that in operation it is as simple to use as a normal multi-range testmeter.

The instrument gives 56 ranges of readings as follows:—

D.C. VOLTS : 5mV. to 250V. (Input Resistance 11.0 megohms.)
25mV. to 10,000V. (Input Resistance 110.0 megohms.)

D.C. CURRENT : 0.5μA. to 1 Amp. (250mV. drop on all ranges.)

A.C. VOLTS : 0.1V. to 2,500V. R.M.S. up to 2 Mc/s. With diode probe external 0.1V. to 250V. R.M.S. Useful measurements can be made up to 200 Mc/s, the applied voltage being limited to 100V. above 50 Mc/s.

A.C. OUTPUT POWER : 5mW to 5 watts in 6 different load resistances from 5 to 5,000 ohms.

DECIBELS : -10db. to +20db.

CAPACITANCE : 0.001μF. to 50μF.

RESISTANCE : 0.2 ohm to 10 megohms.

INSULATION : 0.1 megohm to 1,000 megohms.

£10 Size: 12½ins. x 9ins. x 5½ins.
Weight: 12½lbs.

The instrument operates on A.C. mains, 100-130V. and 200-260V., 50-60c/s

Write for fully descriptive pamphlet.

The instrument is quickly set up for any of the various tests to be undertaken, a single range selector switch automatically removing from the circuit any voltages and controls which are not required for the test in question.

Sole Proprietors and Manufacturers :

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE · DOUGLAS STREET · LONDON · S.W.1 Telephone: VICTORIA 340119

E.T.M.3



For SUCCESSFUL
wide angle scanning
ALLEN DEFLECTOR COILS

70 deg. Scan with minimum deflection defocusing high-efficiency castellated "FERROXCUBE" core. Suits any wide angle C.R.T. up to 27 in. double (d) Scan.

LARGE SCREEN TELEVISION

Only achieved with high efficiency components throughout. ALLEN can supply complete range.

Send 9d. and S.A.E. for circuit diagram of line and Time Base. Write for price list and details of full range of ALLEN components to :


ALLEN

COMPONENTS LIMITED

Crown Works, 197, Lower Richmond Road, Richmond, Surrey. Tel.: Prospect 9013

"WEYRAD"

TELEVISION COMPONENTS

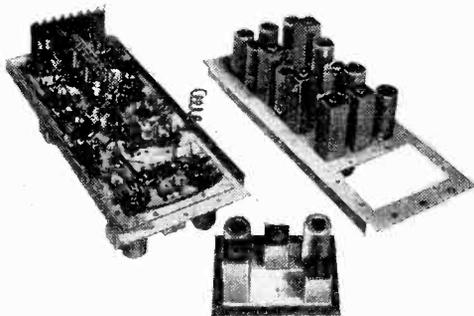

I.F. STRIPS & R.F. INSERTS


Forming a complete superhet sound and vision receiver. Employing 11 B.7.G valves. Excellent fringe area performance provided by 2 R.F. stages. R.F. inserts are available for each of the five Television Channels.

These strips are supplied less valves.

PRICE £10.8.0, including P.T
CIRCUITS & DATA 1/6 per set.
ILLUSTRATED CATALOGUE ... 6d.

WEYMOUTH RADIO MFG. CO., LTD.,
CRESCENT STREET, WEYMOUTH, DORSET

Your set deserves a Mullard Tube

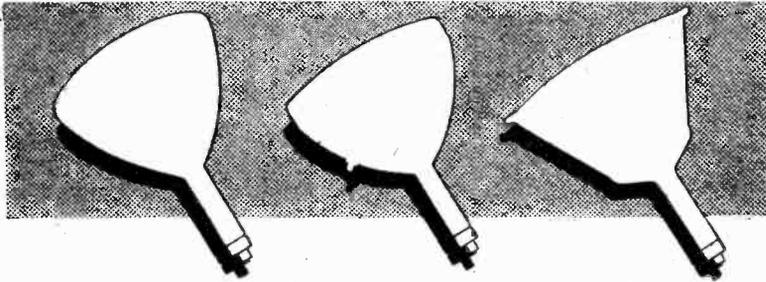

If you are building a television receiver, leave nothing to chance; choose a Mullard Tube. Mullard Television Tubes owe their high reputation for performance, reliability and LONG LIFE to the unrivalled facilities for research possessed by Mullard; to the complete control of manufacture from the production of raw materials to the completed product; and, in particular, to the ion-trap, which safeguards the screen from damage by heavy negative ions produced in the region of the cathode.

Tubes available for home construction include:—

- MW22-16 9 inch screen
- MW36-24 14 inch rectangular screen
- MW31-16 12 inch screen
- MW41-1 16 inch screen (metal cone)

Mullard *Long Life* T/V TUBES



MULLARD, LTD., CENTURY HOUSE, SHAFTESBURY AVENUE, LONDON, W.C.2

MVM 206



ELECTROLYTIC CONDENSERS

These abbreviated ranges of two popular types are representative of the wide variety of T.C.C. Condensers available.


'LECTROPACK' ETCHED FOIL ELECTROLYTICS

Cap. μ F.	Peak Wkg.	Length	Dia.	Type No.
8-32	275	2 $\frac{1}{2}$ in.	1 in.	CE34HE
60-100	350	4 $\frac{1}{2}$ in.	1 $\frac{1}{2}$ in.	CE37LEA
8-16	450	2 $\frac{1}{2}$ in.	1 in.	CE34PEA
32-32	450	4 $\frac{1}{2}$ in.	1 $\frac{1}{2}$ in.	CE37PE
100-100	350	4 $\frac{1}{2}$ in.	1 $\frac{1}{2}$ in.	CE36LEA

'MICROPACK' ELECTROLYTICS All Aluminium Construction

Cap. μ F.	Wkg.	Dimensions		Type
		Length	Dia.	
100	6	1 $\frac{1}{2}$ in.	1 in.	CE32A
25	12	1 $\frac{1}{2}$ in.	1 in.	CE31B
50	25	1 $\frac{1}{2}$ in.	1 in.	CE18C
12	50	1 $\frac{1}{2}$ in.	1 in.	CE32D
32	150	2 $\frac{1}{2}$ in.	1 in.	CE19F
4	200	1 $\frac{1}{2}$ in.	1 in.	CE31G
4	350	1 $\frac{1}{2}$ in.	1 in.	CE18L
8	450	2 $\frac{1}{2}$ in.	1 in.	CE19P
4	500	2 $\frac{1}{2}$ in.	1 in.	CE13P

Regd.

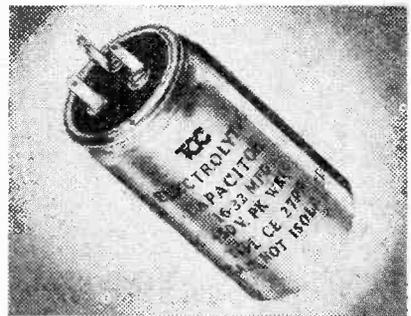

THE TELEGRAPH CONDENSER CO. LTD.

Radio Division: North Acton, London, W.3. Tel: Acorn 0064

PRACTICAL TELEVISION

& "TELEVISION TIMES"

Editor: F. J. CAMM

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363. Telegrams: Newnes, Runt, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 3 No. 34

EVERY MONTH

MARCH, 1953

TELEVISIONS

Recorded Television

THE Chairman of R.C.A., Brigadier-General David Sarnoff, over a year ago issued a challenge to his scientific staff to make two vital contributions to television. He asked them first to produce an electronic amplifier of light that would provide brighter pictures for television which could be projected in the home or theatre on a screen of any desired size. In other words, he was asking for a light amplifier, as with radio we have amplifiers for sound. He coined the word "Magnalux" for the projected system. Everyone is agreed that a true photo amplifier that could produce bigger and brighter pictures in fine detail would greatly enhance television in the home, but it is particularly needed for theatres and industrial purposes. It is equally well known that the present optical system cannot accomplish it. We can enlarge pictures optically, but in the process light is lost and the pictures become dimmer instead of brighter. No news, however, has come from R.C.A. that their scientists have been able to forge one of the two missing links in television.

The second missing link is a television picture recorder that would record the video signal on a tape or disc machine as music and speech are now recorded on a disc or tape. Such recorded television pictures could be reproduced in the home, theatre or elsewhere at any time. That such a videograph must eventually come is beyond all doubt. It would enable recordings of expensive productions to be made for repeat transmissions and save the enormous amount of money now necessary when an expensive production needs to be put on a second time.

To-day when a television programme is recorded the pictures pass from the camera through the television system and are reproduced on a picture tube. Another and special camera, placed in front of the tube, photographs the programme on motion picture film. That, however, is costly, time-consuming and limited in its application, because the pictures pass through all the possible hazards of the television system and suffer all the losses of the photographic process. The recorded picture, therefore, suffers in quality. The instantaneous recording of the actual television signals on tape or discs would be more economical, save processing time and would simplify problems of distribution. Such tapes could be copied in the ordinary way.

It is known that experiments along these lines have been going on in this country for several years with highly promising results.

PROGRESS

HAD such a system been available the showing of the Coronation ceremony on the cinema screens of this country would have been greatly simplified. The BBC is taking this programme as far as Dover for European distribution and we learn that a large European hook-up has been arranged to include Germany and Scandinavia. There is also talk of five new French stations, so that after the Coronation we may expect more frequent continental relays.

It is also known that the BBC is taking delivery of the new telefilm apparatus which is a great improvement on the old. Norman Collins has offered to provide television for the larger towns of this country, probably because he has discovered that there is available a number of 5 kw. transmitters left over from the war.

In Canada more stations are being planned, although they have encountered the difficulty of supplying sufficient quality programmes for a small population. A large percentage of the programmes are quizzes, and the programmes are recorded on telefilm. Four more Canadian stations are being planned with extra studios at Toronto.

Australia is now pressing for television and pressure is being brought to bear on the Australian Government. It will possibly commence with private stations.

From this brief résumé it can be seen that the world has become television conscious and that progress will be accelerated as the known snags are overcome. As reported in previous issues, transistors have already solved some difficulties and they are bound to exert a profound influence on the future of electronics and communications.

Progress has been made in colour television and the development of the tri-colour tube which dispenses with the rotating discs which hitherto have been used.

Within five years it is expected that there will be at least five million television receivers in operation in this country, and that within ten the number of television licences will equal radio licences.—F. J. C.

The NTSC Colour System

THE LATEST DEVELOPMENTS IN COLOUR COMBINE THE BEST FEATURES OF SEVERAL METHODS

By Edward Sieminski

We are indebted to our American contemporary, "Radio Electronics," for permission to publish the following article on the latest colour television developments in the U.S.A.

A YEAR or so ago anyone who expressed a preference for a particular colour TV system was likely to find himself in the centre of a heated argument. Now, at last, time and technical progress are clearing the air, and a new system—NTSC—has emerged out of the confusion.

Named after its sponsor, the National Television System Committee, the new system is the joint development of a broad cross-section of the radio-television industry.

NTSC Background

NTSC was created in 1940 by the Radio-Television Manufacturers Association (then called the RMA) to assist the FCC in developing and formulating a set of standards for black-and-white television. These standards are now the basis of the present American TV system.

The committee was reactivated in the late 40's when the FCC was holding hearings to establish standards for U.S. colour television. Its new purpose was to gather background information on the general problem.

In 1950 the famous "Ad Hoc" (single-purpose) Committee was set up under Dr. W. R. G. Baker for a concentrated study of the state of the art. It examined the work of several laboratories working on various systems of colour transmission with the idea of deciding if one or more of their methods offered promise as a *compatible* colour system. On the basis of the *ad hoc* report, the RTMA reorganised NTSC into nine panels made up of prominent engineers. In the spring of 1951 these panels launched an intensive and extensive programme of organising, selecting, and testing the best features of all colour-television systems. The panels will set up system standards based on the results of these tests, and NTSC is expected to embody these in a formal proposal to the FCC in the near future. The work being done by NTSC has become an outstanding example of engineering co-operation and achievement.

Before going into the complexity of NTSC transmission let us first review the current status of colour TV in the United States.

Field-sequential Colour TV

The present U.S. standard system—the only one permitted for commercial colour-TV transmissions—is the *non-compatible* field-sequential system sponsored by CBS. A programme transmitted by this method cannot be displayed either in monochrome or in colour on a standard television receiver without extensive circuit modifications (especially


in the horizontal and vertical sweep sections). There is practically no audience for these colour programmes. This lack of a large audience discourages sponsors. Lack of sponsors discourages station construction. Without stations, there will be no audience, and without a prospective audience there will be no receiver production. As yet, no way has been found to break this vicious circle.

Engineeringwise the field-sequential system suffers fundamental handicaps. Briefly, it transmits *three* complete pictures in sequence: representing first the red, then the green, then the blue light picked up by the camera televising a colour scene. However, the 6 Mc/s band-width of a regular television channel is just enough to carry only *one* such picture in full detail. The necessity for trimming all three colour signals to crowd them into this meager channel space results in degraded picture detail, objectionable flicker, and colour instability with fast motion.

The field-sequential method *does have* excellent colour rendition and very desirable simplicity. Belabouring it here for its weaknesses is done only to indicate the room for improvement.

NTSC Colour TV

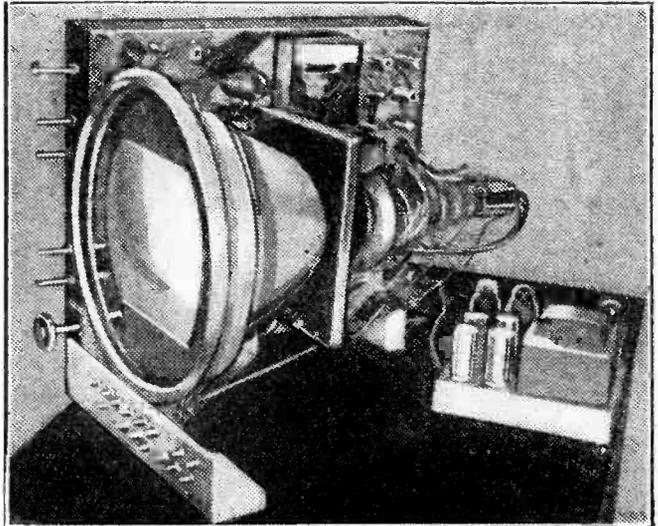NTSC transmission was born in the same ideas that inspired RCA's *dot-sequential* system, but the NTSC system is not sequential. It is a *simultaneous* system, since the three primary colours in the picture are encoded electrically, not one after the other, but *all three continuously*. Many independent laboratories have contributed to its development.



A typical American chassis of a receiver developed for colour reception on the NTSC system.

It is a high-efficiency system, in which the equivalent of a 12-megacycle-wide picture (4 Mc/s for each colour) is transmitted within a 6-megacycle-wide channel, the same bandwidth used for conventional television.

In a nutshell, the new system transmits an ordinary black-and-white television picture, to which is added a modulated sub-carrier signal conveying information about the colouring in the picture. From that viewpoint it could be called "coloured" television. Although a colour receiver is needed to display the coloured picture, the system is compatible; that is, it will reproduce the picture on an ordinary television set in black-and-white (monochrome) without altering the set in any way.

Most of us have been taught that for a circuit to carry more information in a unit time the bandwidth of the circuit must be increased (provided the information is

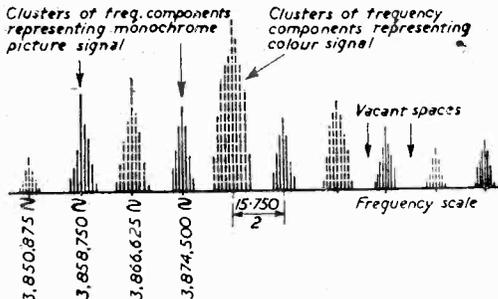


Fig. 1.—Black-and-white TV signal side-bands form clusters, separated by 15,750-cycle gaps. NTSC colour-TV system uses these blank spots to send colour signals.

sent strictly in its original form, as in standard AM broadcasting).

How does the NTSC overcome this rule? Theoretical analysis provides the answer. It shows that any conventional television scene, when translated into a video signal occupying a given channel, does not fill that channel space completely. In fact, there is a regular series of vacant intervals in the transmitted frequency band. If the same theoretical analysis is applied to the colour information of the televised scene, it, too, is revealed as a regular series of discreet frequency components separated by uniform gaps.

Obviously the gaps in the black-and-white picture signal can be utilised for transmitting some other kind of information. Why not the frequency components of the colour signal? The monochrome signal and the colour signal are then said to be "interleaved." Fig. 1 shows a small slice of the frequency band of the channel, indicating how frequency components of the picture signal and of the colour signal are spaced over the same channel bandwidth.

To utilise this method it is necessary only to select a colour sub-carrier frequency which is calculated by multiplying half the horizontal line frequency by any odd number. At the present time the NTSC subcarrier frequency is:

$$\frac{15,750}{2} \times 495 = 3,898,125 \text{ cycles.}$$

On paper the idea may look fine, but does it work in practice? The answer

is that it does—not perfectly, but quite acceptably. A fine grain crawling checkerboard-like pattern is noticeable to anyone standing close to the picture tube and looking for it. The usual viewer does not see it, hence this interference is described as "low-visibility."

There is nothing quite as good as a block diagram for examining a complicated system. Fig. 2 is a simplified outline of the transmitter half of the system.

Colour Encoding

In Fig. 2, the camera supplies electrical signals G, R and B, which correspond to the green, red and blue components of the light in the televised scene. These separate colour-signal voltages are combined in the proportions shown, to make up the luminance signal Y. The proportions of G, R and B are based on the relative sensitivity of the human eye to those colours.

All information about variations in brightness—that is,

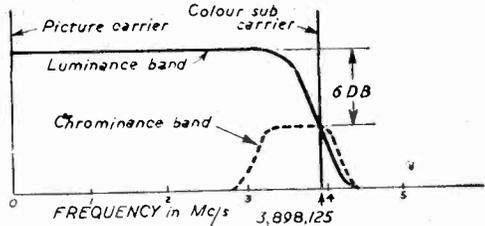


Fig. 3.—Relative positions of the picture carrier and the colour sub-carrier in the upper sideband of transmitted signal. The vestigial lower side-band and the sound carrier have been omitted.

the detail in the televised scene—is wrapped up in the luminance signal. All information concerning the colour in the scene is restricted to the chrominance signal.

Now for the encoding of the colour. (1) The R, G and B voltages are fed through low-pass filters which cut down the bandwidth, passing the equivalent of three degraded single-colour pictures.

(2) Two of these, R and B, are added electrically to the luminance signal Y, whose polarity has been inverted to -Y, thereby creating colour-difference signals R-Y and B-Y. A similar manipulation to obtain G-Y turns out to be superfluous, for the following reasons: G information already exists in the Y signal. We transmit R-Y and B-Y, and can easily extract G-Y from these signals at the receiving end. Therefore there is no

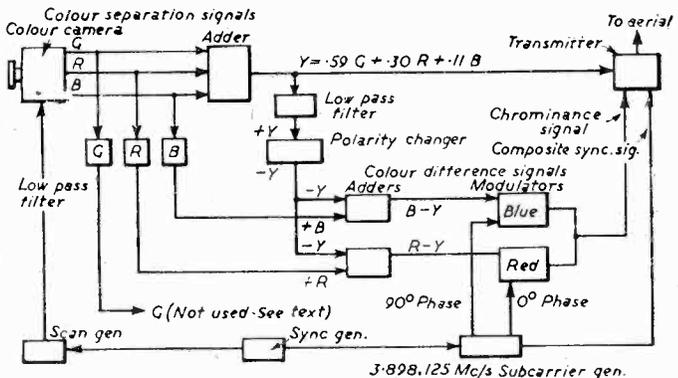


Fig. 2.—Block diagram of the NTSC non-sequential colour-TV transmitter.

point in handling G—Y, since it is already present (although not apparent) in the transmitted intelligence.

(3) Continuing with Fig. 2, R—Y and B—Y modulate two sine-wave voltages which have exactly the same frequency but are 90 deg. out of phase. The combined result, the *chrominance* signal, becomes a two-phase sub-carrier, with each phase amplitude-modulated by picture-colouring information.

Our video signal is now complete, the *luminance* and *chrominance* signals providing all the information needed to reconstruct the colour scene. A station transmitter handles it substantially as it would any normal black-and-white picture. Fig. 3 shows the make-up of the transmitted frequency spectrum.

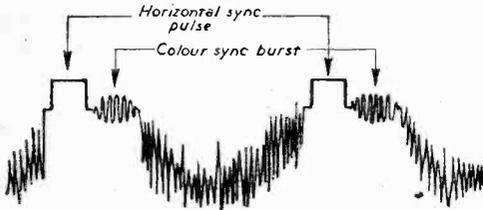


Fig. 4.—Colour-sync bursts consisting of nine cycles of the 3.898125-sub-carrier are sent on the unused "back porch" of each regular horizontal sync pulse.

The synchronising signal is the same as the one used for monochrome television, except that a colour-sync signal is inserted on the "back porch" of each horizontal sync pulse (Fig. 4). In the receiver this burst synchronises the local "colour oscillator," which is used to demodulate the colour signals.

The Receiver

At the receiver (Fig. 5) all circuitry up to the output of the picture detector is conventional.

Let us start with the bandpass filter. This rejects all frequency components of the signal *except* the region containing the *chrominance* signal (see Fig. 3). The output of the bandpass filter feeds separate red and blue *chrominance demodulators*. The colour-difference signals R—Y and B—Y are extracted by reversing the process of sub-carrier modulation at the transmitter. The local *colour oscillator* supplies two sine-wave signals having exactly the same frequency and phase as the sub-carrier which was used for encoding at the transmitter. (These oscillators are synchronised with the colour sub-carrier by

the bursts mentioned above.) The demodulation is a zero-beat form of heterodyning sometimes called "synchronous detection."

In the *matrix-circuit* block the R—Y and B—Y signals are mixed in the pre-determined polarities and proportions to produce the G—Y signal.

Finally, the three decoded *colour-difference* signals are combined with the main *luminance* signal to reproduce the G, R and B colour signals which originally left the camera of Fig. 1. For example, adding R—Y to Y leaves R alone. The R, G and B voltages are applied separately to the tricolour picture tube to recreate the scene.

Colour Reproduction

The great advantage of the NTSC system lies in its economical handling of colour information. In Fig. 1 we noted that the R, G and B signals were each limited to a bandwidth of about 1 Mc/s, implying the transmission of a limited amount of colouring information. The *luminance* information (picture detail) occupies the full 4 Mc/s bandwidth.

This bandwidth relation makes sense when you understand how the eye sees. Visible light produces three separate and distinct sensations: *brightness* (relative intensity or luminance), *hue* (recognition of red, orange, yellow, etc.), and *purity* or *saturation* (the degree to which the colour is off-white, ranging from *zero saturation*, or white, to 100 per cent. *saturation*, meaning a deep, vivid colour, a pure *hue*.) The human eye is extremely sensitive to brightness variations but surprisingly insensitive to changes in hue. The NTSC transmits picture information only to the extent that the human eye appreciates.

One more puzzling question, *colour mixing*, deserves attention. The tricolour picture tube operates on the principle of *additive* colour mixtures. A good example of this is a cluster of partially overlapping coloured lights, as in Fig. 6. The overlapped areas show some examples of *additive* mixing. Mixing coloured paints, or looking through superimposed colour filters are examples of *subtractive* colour mixing.

The phenomenon of colour sensation is in direct contrast to the sense of hearing. Most of us can identify the instruments being played from the general character of the sound, and a trained musician can even recognise the individual notes which make up complex musical tones. The eye has no corresponding ability to recognise the individual components of a colour mixture. The eye perceives only the *overall result* of the mixing. With the proper set of primary colours, such as the red, green and blue used in NTSC, we are able to reproduce practically the entire range of colours.

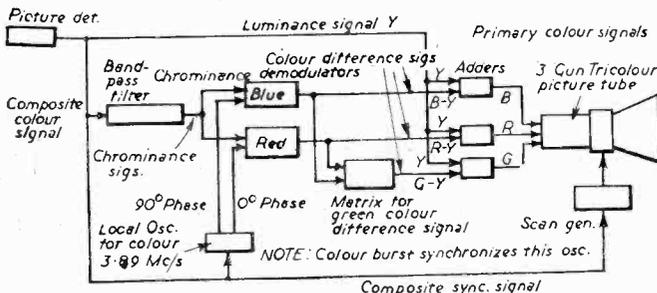


Fig. 5.—Block diagram of the receiver colour circuits. All sections of the receiver in front of the colour unit are conventional.

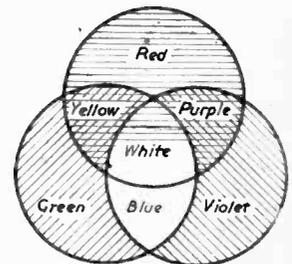


Fig. 6.—Colour combinations produced by blending coloured lights. This is known as *additive mixing*.

Hints and Tips on Tuning

GETTING MAXIMUM RESULTS FROM A HOME-MADE OR COMMERCIAL RECEIVER

By Gordon J. King, A.M.I.P.R.E.

THE final connection has been carefully soldered in position. The continuity—or ought we to say “insulation”—check between the H.T. rail and chassis proves satisfactory; yes, surely quite in order to apply mains. This is, indeed, the moment the home constructor has been fervently working for. Good! The valve heaters are glowing, and the comforting 10 Kc/s whistle indicates that all is well with the line timebase.

Generally speaking, the majority of home-constructed receivers examined by the author produce, on first test, some sort of raster—at least—on the picture-tube screen; although very much unmodulated, quite out of focus, and usually well out of centre—that is to say, large corner shadows appear to give the raster, or the diffused patch of light, a new moon effect. Such a combination of easily remedied (usually) defects can be extremely disconcerting to the constructor, especially if he is new to the art of TV. construction.

Cleaning the Raster

The constructor should take heart, for the cause of the deranged raster is not often as bad as the picture-tube first shows it. It is advisable, first of all, to get the raster in some sort of order, after which the constructor can then concentrate on receiving sound and vision. The aerial taken out, or the Contrast control turned to minimum is the best way to start. Next, the raster should be brought to some form of focus; this will give it a clear edge, and indicate its boundaries so that centring is facilitated.

Receivers primarily designed for home construction may specify either electro-magnetic focusing or, as is more usual, a focusing magnet. In the former case, alteration of the external focusing control should do as it indicates—it may, to a degree, but more than likely hard over on one of its “stops” the raster just starts to focus. Should this occur, all is well, for it simply means that the focus coil is not quite correctly positioned on the tube neck.

The focus coil—or magnet—and the electron beam can be considered analogous to an optical lens and light rays. We all know, for instance, that to focus the sun’s rays to a point of maximum heat on, say, a piece of paper the optimum point, or point of focus, is determined by the position of the lens relative to the paper, and also by the focal length of the lens. A convex lens from a pair of ordinary spectacles will need to be held much farther away from the paper to focus the sun’s rays than, say, a watchmaker’s lens, which has a much shorter focal length than the spectacle lens.

Now, with electro-magnetic focusing we energise the focus coil by passing a certain current through it as determined by the setting of the focusing control. This allows the focus coil to behave with an electron beam as a lens does to light rays; the electron beam is brought to a point of focus on the screen by modifying the focal length of the coil. Clearly, then, the coil must be correctly positioned on the tube neck in the first place so that the approximate midway setting of focusing

control will effect a perfect focus of the electron beam.

Fig. 1(a) and (b) illustrates the general method of focus coil mounting: a circular bracket drilled to take the neck of the picture-tube is secured to the chassis. The bracket carries three threaded bolts, which line up with holes drilled in the focus coil cowling. Three compression springs provide loading for the coil, and three nuts allow its axial movement. With the focusing control set to its midway position, and the coil set as far as possible towards the tube base, the three adjusting nuts should be given equal clockwise turns (about one complete turn at a time) and the raster noted. A position will be reached where the horizontal scanning lines are clearly defined on the tube face, although it is possible that the raster may be well out of centre with its corners cut off.

At this point the picture width and height controls should be adjusted so that the raster occupies about two-thirds of the screen area. It is then an easy matter to centre the raster by slight readjustment of individual nuts, the correct nuts and direction of adjustment being readily found by trial and error. Should it be found that, instead of the raster being wholly in focus, the centre is very sharp, but deteriorates towards the side and corners, correction may be effected by moving the coil very slightly along the neck of the tube towards the screen. The final centring and focusing adjustments must be done with the aid of test card “C” in conjunction with the settings of the horizontal and vertical linearity controls.

With permanent magnet focusing, the field strength along the tube neck, and thus the virtual focal length, is adjustable by means of a soft iron sleeve, which can be made to traverse the tube neck in such a way that it gradually by-passes the focusing field as it enters the magnet. The magnetic gap is sometimes adjustable by three screws, which, apart from focusing the raster, also act as a picture shift. Adjustment of this arrangement may be followed by the method recommended for the focus coil, although the optimum focus adjustment must be performed by this means as no external focusing control is available to facilitate this function.

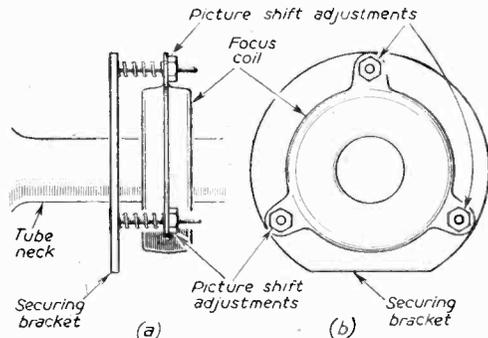


Fig. 1.—Illustrating a method of focus-coil mounting.

Finally, it should be remembered that it is pointless to perform these adjustments, to an optimum limit, if the picture tube is not securely fixed to the chassis, for only a slight alteration in the position of the tube when it is fitted into the cabinet will be sufficient to necessitate further adjustment.

Shadowing

This fault has several variations, since the shadows may be no more than slight shadings at one or more of the corners; or there may be complete blackout of the corners with clearly defined edges. Adjustment of picture shift screws or nuts probably tends to prevent

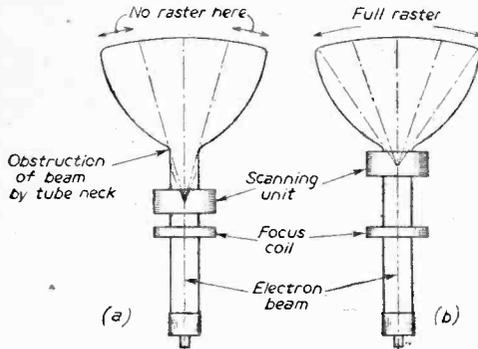


Fig. 2.—Showing how a wrongly positioned scanning unit can cause corner shadow.

shadowing, but only when the raster is well out of centre. In the end the exasperated constructor realises that it appears impossible to have it both ways—no shadowing and a perfectly centred raster—by the mere adjustment of the picture shift screws, so a compromise is usually aimed at.

Little is said in construction manuals about this type of fault, although it can present quite a headache to the builder. The fault is, of course, produced by an obstruction of the electron beam, where the deflection is greatest, by the glass envelope of the tube. Fig. 2(a) clearly illustrates how such a fault could occur. The scanning unit, as will be noticed, is not as far as possible up the tube neck, and deflection is taking place about one third of the way down, resulting in sharply-defined corner shadows. It is, therefore, essential that the scanning unit be well up to the top of the neck of the tube as shown by Fig. 2 (b).

Sometimes the corner shadows are less clearly defined, which generally means that the electron beam is not coming up to centre of the tube. This fault is usually indicative of bad alignment of the tube in relation to the focus unit. The mechanical mounting of the tube should be such that the tube axis passes centrally through both the scanning and focus units. With home-constructed equipment special attention should be given to this very important point.

Slight misplacement of the gun electrodes in the tube itself can be responsible for corner shadowing, and more than one such instance can be remembered by the author. It is frequently possible to avoid shadowing by rotating the tube into a different position, and then re-setting the shift adjustments. Apart from changing the tube—if it is still under guarantee return it to the dealer—little more can be done. Care should be taken if the tube is rotated, to provide adequate clearance between the E.H.T. connector and chassis.

External fields, either electro-static or electro-magnetic, can distort a raster and give rise to corner shadowing. The electro-static charges develop on the tube and associated mask; usually due to slight dampness. A complete dry-out is the answer coupled with a coating of anti-static tube polisher.

Magnetic, or electro-magnetic fields arise mainly from the loudspeaker magnet, transformers, or smoothing chokes which carry a large current, orientation of the offending component is the only real cure, although a degree of success is usually had by reversing the leads on the smoothing choke, and thus reversing the direction of its field.

Hints on Receiving Sound

Having successfully achieved a clean raster our attention must now be focused on obtaining sound and vision. If the receiver is home constructed, then, without much doubt, the construction data will provide adequate circuit alignment instructions. This article will, therefore, mainly concentrate on various snags, which have been known by the author to result during the process of deriving sound and vision, and which are not often included in the instruction book.

It is frequent practice to align, first of all, the sound circuits; but as the constructor rarely possesses accurate instruments, he has to rely on the eye, the ear, and the transmitted signal. The following hints will, therefore, cater for such a constructor.

Constructors located within the fringe area have the benefit of a strong signal for tuning purposes, and tentative adjustment to coils nearest the sound detector should be sufficient to bring in the sound signal. Although at first the sound will be very faint, the chief problem, that of tuning at least one circuit to the sound frequency, will be solved. It now remains to follow up with the rest of the sound coil adjustments for maximum output. Fringe area constructors will find that a pair of 'phones, suitably isolated by coupling capacitors, connected across the loudspeaker, are a boon when first endeavouring to establish the sound frequency.

The threaded iron-dust cores used to tune the coils are often very slack in the formers, which makes it extremely difficult to get the final maximum setting; a piece of elastic—from a thin elastic band—inserted in the former, before the core is fitted, successfully takes up the slack, and allows a solid adjustment.

Instability

As the subsequent tuned circuits are adjusted the sensitivity of the sound channel increases, and there arises a distinct possibility of the channel going unstable. A large percentage of home-constructed receivers adjusted by the author have been prone to this effect. The results being that, everything is progressing satisfactorily when, after a certain coil—usually the one

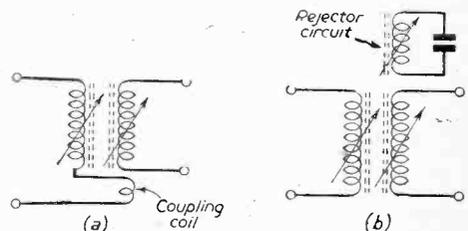


Fig. 3.—(a) Band-pass coupling with separate coupling coil, and (b) coupled rejector circuit.

nearest the aerial—is adjusted a distinct “plop” emits from the loudspeaker and the sound goes completely dead. Readjusting the coil brings the sound back again, but it appears obvious that the circuit is not correctly tuned, because the volume of sound increases as the coil is adjusted up to the point of instability.

Such a fault can be very difficult to trace, but it must be rectified before further alignment is attempted. Special attention should be given to the screening between coils or stages. Mechanically it may be perfectly sound, but from the R.F. point of view, probably, sadly lacking. Frequently, screens and shields of this nature are secured to the main chassis by B.A. nuts and bolts, and so far as R.F. is concerned this method of fixing is totally inadequate. In fact, in certain cases, where the screen is also employed to earth decoupling capacitors, etc., the receiver would probably behave better if the screen were omitted altogether!

This is because R.F. voltages induced into the badly-secured screen are fed back again, via the capacitors, to the valves, and if these voltages are of the right phase conditions for positive feed-back are developed. First of all, then, make absolutely certain that any R.F. shielding is really doing its job—and where possible solder all round any mechanical joint, especially where the shield is making contact with the main chassis—dozens of cases of tricky instability problems have been so cured by the author.

Decoupling capacitors must be returned direct to a common point, for the stage in question, and not to random sections of the chassis as is unfortunately very common practice. The circuit of Fig. 3 illustrates the arrangement which should be adopted. Grid and anode leads must be kept as short as absolutely possible, and it is essential to earth the metal centre portion of the valve base, since this acts as a screen between grid and anode pins of the valve.

Coils not Tuning

It may be found that when tuning for maximum sound—or vision—an optimum point is not apparent on one or more of the coils. Sometimes the core is unscrewed and the sound volume is still on the increase when the core is out as far as possible; taking the core right out of the coil may increase the volume slightly more. If the core is iron-dust, then this effect means that the coil inductance is too great, for taking the core out completely reduces the inductance, but not sufficiently. A reduction in the number of coils turns should correct this, although other factors may be responsible. For instance, should the number of turns on the coil be that stipulated in the construction data, it may be advisable to investigate the other possibilities first.

If the circuit employs a band-pass coupling with an additional one- or two-turn coupling coil, or a coupled rejector circuit, as shown in Fig. 4 (a) and (b), it is possible that the coupling is too tight. A reduction in coupling will result if the coupling coil is moved slightly away from the anode (or grid) end of the main coil—towards the earthy end if the coupling coil is wound on top of the main coil.

Another factor to bear in mind is that of valve capacitance, for it is this in conjunction with the coils, which forms the tuned circuit. Now, the Miller effect determines to a large extent the valve capacitance under working conditions, and this is readily altered with control or suppressor grid bias, or even the screen potential has a certain effect. Clearly, then, a wrong value cathode or screen grid resistor may so modify the capacitance across the coil that, unless its inductance is

modified also, it will not tune to the desired frequency.

It may be that the coil is still not peaked when the core is fully screwed into the former. In this case coil coupling may *not* be tight enough, or incorrect electrode voltages may, again, be the cause. If the tuning appears flat throughout the whole range of core adjustment, a brass rod temporarily inserted into the coil former usually determines whether the inductance is too high—or too low, remembering, of course, that brass reduces the inductance.

Hing on Receiving Vision

In the service area, no doubt, some sort of modulation will appear on the screen with tentative core adjustments and it is usually a straightforward matter to peak the vision coils—making the stipulated adjustments for band-width. In the fringe area, however, the situation is different, and much time can be spent in trying to locate the vision signal. A pair of 'phones, suitably isolated, and connected to the video amplifier anode

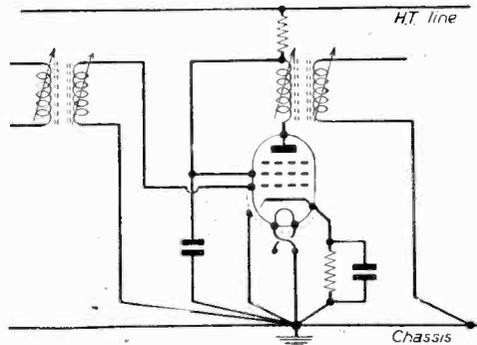


Fig. 4.—Single-point wiring is carried out as shown here.

(picture-tube cathode, or sometimes grid) and chassis can assist considerably.

Very often a faint vision signal can be heard in the 'phones, though not indicated on the picture-tube, even if the cores are well out of adjustment. It is a simple matter to enlarge on this, starting from the vision detector end, and tuning the cores, first one way and then the other, for maximum volume of the vision signal in the 'phones.

Using 'phones so connected is, by the way, very convenient when adjusting the sound rejector circuits. During the latter period of the sound only news transmission, after the vision carrier is switched off, the rejector coils are easily adjusted for *minimum* sound signal in the 'phones.

Pattern Manifestations

Owing to the wider band-width of the vision channel the instability problem is less aggravating in this section; nevertheless, certain home-constructed receivers tend to be very “touchy,” especially as the tuned circuits nearest to the input are brought into resonance, and where the receiver is of single side-band working. Generally speaking, instability in the vision circuits will effect very little the sound reproduction—apart from, perhaps, giving the reproduction a slight edge. The converse is true where instability originates in the sound channel; although it may be noticed that, instead of the picture being built of clearly defined scanning lines, the lines tend to break up, and the picture appears to be composed of a series of dots.

The early stages common to both sound and vision channels are more likely to develop instability than later stages. Both loudspeaker and picture-tube will respond violently to instability here, and in extreme cases a microphonic howl may build up in the loudspeaker accompanied by an uncontrollable brilliant screen. In less severe cases the loudspeaker may go conspicuously quiet, and all valves appear microphonic if gently tapped; at the same time herring-bone or wire netting patterns come and go on the screen, and alter in form as the contrast control is adjusted.

To quickly determine the actual stage which is unstable (oscillating) a valve current check can be taken. A volt-meter connected across the cathode resistor of each valve in turn will indicate an abnormal reading across the resistor of the valve which is oscillating. After locating the unstable stage attention should be focused on its associated wiring, decoupling, and shielding arrangements.

A latter stage connecting lead which has inadvertently been displaced so that it is within coupling distance of a valve or coil in the first stages would almost certainly cause the early stage to go unstable. High-resistance contacts to the valve pins frequently give rise to instability, which can often be started and stopped by wriggling the offending valve in its holder—miniature types and the EF 50 variety are particularly prone to this trouble. The valve pins should be carefully scraped clean, while

the sockets may be beneficially treated with carbon-tetrachloride.

Although non-inductive decoupling capacitors should be employed in the R.F. and I.F. stages, some constructors use ex-Government components of dubious characteristics. In certain parts of the circuit such components may be suitable, but for R.F. or I.F. decoupling they usually do the opposite to what is required of them. A quick way to make an inductive capacitor non-inductive is by shunting it with a 50-100 pF good quality mica capacitor.

The aerial feeder in close proximity to the mains lead has been known to produce conditions for instability. It is, therefore, advisable to keep these two leads as far as possible away from each other, particularly during the process of tuned circuit adjustments.

Little has been said concerning the timebases and synchronising circuits in this article, but as a large majority of constructors follow a tested circuit design, little can go wrong provided he observes stipulated component values. And for constructors who desire to evolve their own circuits many excellent articles in this connection have already been published in this journal. In conclusion, therefore, it is hoped that this article will be of assistance to the many constructors, who, although fully realising the problems associated with radio construction, have so far had little experience with television construction.

The BBC and Films

THE BBC and the British Film Producers Association recently made the following announcements.

An extended report of the meeting between the BBC and the British Film Producers Association, which took place on January 1st, has been drawn up as follows:

A meeting took place at Broadcasting House on January 1st between representatives of the BBC and the British Film Producers Association. Present as observers were representatives of the Association of Specialised Film Producers, Ltd., the Cinematograph Exhibitors Association of Great Britain and Ireland, and Kinematograph Renters Society, Ltd.

The discussion was entirely exploratory and aimed at meeting the request of the film producers for information on the BBC's use of feature and short films and the extent to which the British film industry might be able to produce filmed programmes for television in this country. No offers to supply films were made by the film industry's representatives, nor did the BBC declare that it would be able to meet any particular scale of fees.

The BBC stated that in the past year it had used 66 feature films of old vintage, only four of which had appeared in the evening programmes.

There were also 52 Westerns and serials used in the children's programmes and about 250 shorts at various times.

Asked by the producers to estimate their future requirements of films, the BBC representatives said that if the timing and pattern of the television service remained as at present they would like to have access in 1953 to 12 feature films for evening transmission, 26 features for afternoons, 26 films suitable for children, and shorts at the rate of two a week.

The BBC's interest in films was governed by their age, quality and suitability for television, and by the cost of hiring. The BBC emphasised that higher rates than they were accustomed to pay could only be contemplated if much more modern and better quality films than at

present offered were made available. The BBC's representatives said that it was conceivable that hiring fees in the range of £750 to £1,000 might be considered for feature films which were thought to be particularly suitable for television and which had only recently completed their general release.

No formal offer of any kind whatsoever was made in this connection by the BBC.

The producers asked if the Corporation would be interested in hiring programmes specially produced for television by the film industry. The BBC replied that their policy was to consider films from all available sources, but again had to take account of quality and cost.

Amateur Cinematograph Trophy

A NEW award, the Television Amateur Cinematograph Trophy, will be presented to the maker of the best amateur film on the result of a nation-wide vote by television viewers.

Beginning in April, a number of films chosen by the British Amateur Cinematographers' Central Council will be transmitted in a series of three programmes. Some of these films have already won awards.

This series of programmes is an experiment designed to put television viewers in touch with the country's growing amateur film movement. The installation of 16 mm. film-scanning equipment has made it possible for the BBC to transmit the amateur type of film.

In each programme the films shown will be discussed and voted on by a panel of three judges in the studios. The panel will consist of a chairman, a professional filmmaker, and an amateur film-maker. The chairman, who will have the casting vote, will be Dr. Roger Manvell, film critic and director of the British Film Academy.

The panel's choice of the three or four best films will be repeated in a fourth programme, and at this point viewers will be asked to write to the Television Broadcasting Service of the BBC stating their choice. The film which viewers like best will be awarded the Television Amateur Cinematograph Trophy.

Television Society's Exhibition

THIS YEAR'S PRINCIPAL EXHIBITS BY MEMBERS AND MEMBER FIRMS

THE annual exhibition of equipment related to television design and production, was held this year at 155, Charing Cross Road, on January 23rd and 24th. It was well attended (admission being by ticket only) and the following are brief details of the items which were exhibited. They will serve to give readers some idea of the most interesting lines of development which are being followed, and particular interest was paid to the spot wobbler circuits, A.G.C. and flywheel sync, about which there is so much difference of opinion among the experts.

AERIALITE LTD., Castle Works, Stalybridge, Cheshire. This firm showed a display stand designed to illustrate the most suitable type of aerial for operation at given distances from the transmitter. Other exhibits included R.F. feeders, coaxial plugs, television, broadcast and car aerials.

ALLARD, L. S., of G. E. C. Ltd. Research Laboratories. A demonstration of electron beam plotting in cathode ray tubes—the size and path of an electron beam in a special tube can be noted and deflection defocusing properties of deflection coils assessed from changes in locus of beam focus.

A. J. BALCOMBE, LTD., Tabernacle Street, London, E.C.2. Here was shown one of Alba's latest 17 in. tube receivers operating with an E.H.T. of 17.5 kV., designed for 5-channel operation of A.C. or D.C. A finished production chassis was also on show for inspection purposes.

AREN (RADIO & TELEVISION) LTD., High Street, Guildford. As specialists in the manufacture of projection sets, this company exhibited a 4 ft. x 3 ft. projection console with remote control, and a number of interesting mechanical and electrical features.

BEDFORD CENTRE. Two items of test gear interest were shown.

BELLING & LEE, LTD., Gt. Cambridge Road, Enfield. A television field strength measuring set—utilising the received BBC frame sync pulses for amplitude measurements, thus enabling the "true" directional response of an aerial to be determined even in the presence of "ghost" reflections was exhibited.

BBC TELEVISION. This exhibit consisted of:

1. Representative selection of sketches by television scene designers and artists.

2. A servo-assisted panning head for television cameras. Prototype developed by the BBC's engineering design department to meet the problem of slow, smooth panning at race-courses and similar events.

B.R.E.M.A., 59, Russell Square, London, W.C.1. This was an exhibit designed to illustrate precautions needed to reduce the line timebase radiation to small proportions. Three forms of interference considered are: electrostatic, electromagnetic and mains-borne.

BUSH RADIO LTD., Power Road, Chiswick, W.4. In addition to still pattern signals for 525 and 625 line production testing, a subjective test is secured by mixing BBC's 90 Mc/s. FM and 45 Mc/s. TV signals to produce a negative modulated carrier with FM sound on any television channel for intercarrier receiver testing.

CINEMA TELEVISION LTD., Sydenham, S.E.26.

At this exhibit was seen a selection of tubes for television purposes and a demonstration of measurement of projectile velocity using miniature range and model gun firing a ball. Measurement accuracy of 1 micro-sec. to 0.005%.

DECCA RECORD CO. LTD., Brixton Road, S.W.9. A projection model television receiver giving a picture 4 ft. x 3 ft., was shown here.

EDISWAN ELECTRIC CO. LTD., Charing Cross Road, W.C.2. Three demonstrations were given, using C.R. tubes under working conditions to illustrate (a) the effect of aluminising, (b) the spiral path of a magnetically focused electron beam and (c) the removal of halo by use of a liquid layer.

E. K. COLE, LTD., Southend-on-Sea, Essex. A demonstration of the applications of "spot wobble" to large screen direct-viewed domestic receivers. Two identical receivers were shown, one of which had "spot wobble" in operation.

E.M.I. LTD. & E.M.I. (SALES & SERVICE) LTD., Hayes, Middx. In addition to a range of equipment, including two waveform monitors and production television receivers, the television distribution equipment shown was being used to relay either BBC or local camera signals throughout the exhibition.

FERRANTI LTD., Moston, Manchester. A back projection receiver employing a 2½ in. tube with 25kV. was shown here. Designed for operation on all channels and employing a two-valve paraphase video circuit for maximum contrast range.

GILBERT, J. C. G., Northern Polytechnic. A high intensity monitor developed solely for use under high ambient light conditions, as met with in studio work, was shown here.

DAVIS, C., Hallam, Sleigh & Cheston, Ltd., showed component parts in readily assembled form for unique framework construction for radio communication, test gear and allied equipment.

A. H. HUNT (Capacitors) LTD., Garratt Lane, Wandsworth. In addition to a wide range of capacitors for many uses and conditions of temperature and humidity, this exhibit included a working demonstration of production winding of miniature capacitors.

LELAND INSTRUMENTS, LTD., Millbank, Westminster. A wide range of precision ceramics and precision ceramic capacitors, together with standard laboratory equipment, instrument cases and panels for industrial equipment, were shown.

MARCONI'S WIRELESS TELEGRAPH CO. LTD., Chelmsford. An optical demonstration of (a) the effects of restricted colour definition in colour television systems (photographs by courtesy of Ilford Ltd.), (b) flicker in constant luminance television systems, and (c) working model of "ideal" filters with linear phase shift.

Also shown was a complete working Image Orthicon Camera Channel, capable of operating down to as little as 1 ft. candle incident illumination.

McMULLAN, D., Cambridge University, showed a light meter with current feedback, keeping the photo-

(Continued on page 447.)

The Question of Phase

HOW VARIOUS CIRCUITS CAN DIFFER, AND THE DIFFICULTY OF MAKING CERTAIN COMBINATIONS

By W. J. Delaney (G2FMY)

AN increasing number of inquiries have been received lately asking how a certain portion of one receiver may be used with a section of another. For instance, a number of vision and sound strips have been sold recently as manufacturer's surplus, and some readers have wanted to include these in a receiver which they possess and which is giving unsatisfactory results. We have repeatedly pointed out that unless one is fully aware of the implications and modifications called for in combining sections of different designs it is best not to make the attempt. Provided one knows sufficient about the subject, however, it is quite possible to carry out such modifications, and, therefore, some idea of the difficulties met with will now be given.

First, there is the all-important question as to the method of feeding the heaters of the valves. Obviously all sections of the completed receiver must be fed in the same way—either parallel connected and fed from a transformer winding, or series connected with the necessary modifications made to any series dropping resistor which may be needed due to the different load imposed by the replaced or changed section. There may be other changes called for in the power supply connections, but it will be assumed that the reader is aware of these, which will follow normal radio practice. In a television receiver, however, there is one thing met with which does not worry the radio man. That is the question of phase. You can call this polarity, if you choose, but it is most important in a television receiver that the phase or polarity of the signal is known at every stage after the vision detector.

Audio Signals

In a radio receiver the audio signal is in the form of an alternating current, and this is applied to the reproducer (loudspeaker) which, to explain matters in a simple way, moves backwards and forwards. Now it does not make any difference whether the cone of a speaker is driven backwards or pushed forwards—the ultimate movement of the air will be the same, and, therefore, it does not matter whether we use one L.F. stage or two (or more). But in a television receiver it is most important to know just whether the impulses with which we are dealing are positive-going or negative-going.

In Fig. 1, is shown the normal type of vision diode detector, less the various filters and similar items which

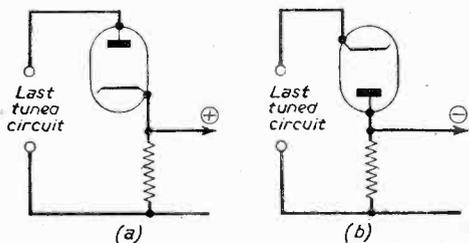


Fig. 1.—The Video detector can produce a positive or negative signal as shown here.

may be associated with it, and which do not concern us at the moment. If the last R.F. coil is connected to the anode of the detector the result will be a positive-going signal at the cathode. Alternatively, if the cathode is connected to the R.F. coil, then the signal will be negative-going. The sync pulses, however, in the present BBC signal are arranged on the carrier in such a manner that they are of opposite polarity to the picture signal, and thus a positive-going picture signal will carry negative-going sync pulses, and vice versa.

Picture Tube Connection

Now when the signal is applied to the grid of the video amplifier the effect is to produce at the anode an outgoing signal of opposite polarity, and this, in fact, applies to all amplifying stages, whether in a straight radio amplifier or in a timebase or other apparatus. Therefore, the connections to the picture tube must be considered in conjunction with the design of the vision strip, i.e., whether the detector delivers a positive or negative-going picture, and whether there is one stage or two of subsequent video amplification. A positive-going picture at the grid of a single video amplifying stage will call for the output to be connected to the cathode of the picture tube, and a negative-going signal at the grid will call for grid modulation of the tube. This is the first point which will have to be considered if a change in vision strips is contemplated.

Sync Pulse

As a negative picture signal is found at the anode of a video stage fed from the cathode of a video diode, this means that positive sync pulses are present, and it is important to remember that the cathode of an amplifying valve is carrying a signal of polarity opposite to that in the anode. Therefore, if negative sync pulses are required in the arrangement just described they could be obtained from the cathode, but it is necessary to bear in mind that they will be very much weaker than the pulses in

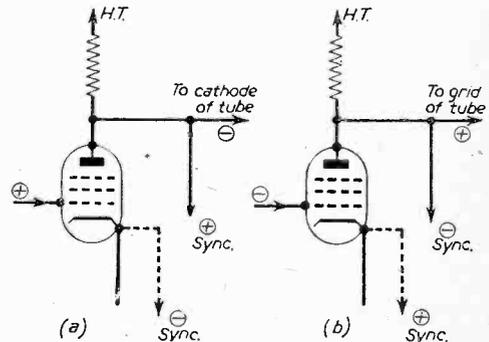


Fig. 2.—The output from the Video stage can be of either polarity, and the tube must be correctly connected.

the anode circuit. It is not proposed to go into the question of the brilliancy control which will, of course, have to be connected to the grid or cathode of the tube according to which electrode is modulated, as this does not come within the scope of "phase," but it may call for some complication, as to maintain the grid negative with respect to the cathode, with the grid fed from the anode of a video stage (making it probably nearly 200 volts positive), this may mean that the brilliancy control will have to be at a very high voltage which may not be obtainable from the normal H.T. rail.

We have now seen that we may have a positive or a negative sync pulse available from our video stage, and before use can be made of it it is necessary to know what arrangements are used in the timebase. The sync separator may be ignored for the moment, but it should be remembered that the phase may be reversed, as already described by passing it through a simple L.F. amplifying stage.

Blocking Oscillator

The blocking oscillator is probably the most common form of circuit met with and has replaced the thyatron in most receivers. If the circuit utilises a thyatron, then usually a positive sync pulse is called for. In the case of a blocking oscillator, however, we can use either a negative or a positive pulse. If the sync pulse is negative it is applied to the anode of the oscillator if this is of the simple triode type. If an H.F. pentode is employed, the pulse may be applied to the screen grid, but it will still have to be of the negative-going form. If the sync pulse is of the

positive-going form it will have to be applied to the grid of the oscillator. These remarks are, of course, generalisations, and some commercial receivers may have modified forms of oscillator to which these general remarks do not apply, but sufficient has been said to show that it is

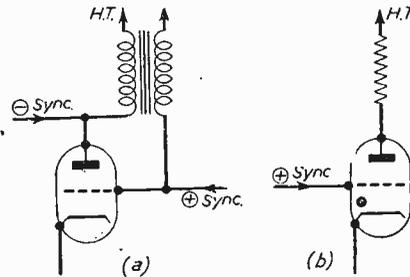


Fig. 3.—The sync pulses are applied to different electrodes, according to their polarity.

impossible for us to be able to inform a reader whether or not a certain tuner can be included in a different receiver without knowing exactly what circuits are employed in both pieces of apparatus, and that it is quite possible that the alterations called for may be so extensive that it would be easier to make up the section which is to be changed. As a general rule such a mixed combination should not be attempted.

Television Society's Exhibition

(Continued from page 445.)

multiplier output current constant for very wide ranges of light intensity. Contrast range greater than 100,000. (10^{-6} to at least 10^{-1} lumens incident on photocathode.)

MULLARD LTD., Century House, Shaftesbury Avenue, W.C.2. This exhibit comprised a selection of cathode ray tubes designed for television purposes, a display of Ferroxcube for scanning and focus applications and a back-projection television receiver.

MURPHY RADIO LTD., Welwyn Garden City, Herts. A V204 receiver was shown specially modified for fringe reception and employing a G.E. 24 in. direct view tube at 17 kV. Extra features in this receiver included slow-acting AGC, anti-flutter, flywheel sync., black spotter and optional spot wobble.

PEACHEY, H. J. Experimental tele-still equipment, designed for the home constructor, were shown.

PHILIPS ELECTRICAL LTD., Century House, W.C.2. Amongst a number of items manufactured by this company the composite pattern generator shown was used with local camera signals to produce a composite television signal at 45 Mc/s. for distribution throughout the Exhibition.

POOLE, R. B., showed an experimentally constructed model showing C.R.T. design.

REGENTONE TELEVISION & RADIO CO. LTD., Romford, Essex. One of a large range of domestic television receivers made by Regentone was on demonstration with local camera and BBC signals. A typical production chassis, detailing the design, was also available for inspection.

STANDARD TELEPHONES & CABLES, LTD., Aldwych, W.C.2. The main exhibit was a large scale contour map showing both cable and radio links, from London to all terminal points. Sections of typical multi-

way cables were exhibited, together with the specialised test equipment used for associated measurements.

TELEGRAPH CONDENSER CO. LTD., Acton, W.3. Here was seen a D.C. ionization detector for testing dielectrics. This apparatus applies a test voltage to the test capacitor, and any ionization discharge is monitored visually and aurally. "Visconol" capacitors were exhibited together with a working model of the "View Master."

TELEQUIPMENT LTD., Whetstone, N.20. A type WG/4 television pattern generator and a Monoscope equipment designed particularly for factory production use were shown.

THORN ELECTRICAL INDUSTRIES, LTD., Ferguson Radio. This exhibit consisted of a receiver, operating alternatively with and without fly-wheel sync under weak signal input conditions, with superimposed artificially generated ignition and C.W. to simulate fringe reception.

TOWNSEND, G. B., of G. E. C. Research Laboratories. A G. E. C. table model receiver employing aluminised 16 in. tube at 12 kV., and incorporating a video diode spot limiter and modulation following suppression on the sound channel, was shown.

T. KILYINGTON, of Post Office Research Dept., showed a television monitor with line broadening effected by modifying the p.m. focusing device to produce an elongated spot instead of a circular spot.

20th CENTURY ELECTRONICS LTD., West Norwood, S.E.27, exhibited a number of single and double gun C.R. tubes with perfectly flat faces, and characterised by extreme precision of electrode alignment during production.

THE TELEVISION SOCIETY. This exhibit consisted of a television transmitter designed for propagation tests at 427 Mc/s, using the standard 405 line video waveform.

The Wenvoe Transmitter

SOME INTERESTING TECHNICAL DATA OF THE LATEST BBC STATION

THE BBC high-power television transmitters at Wenvoe were brought into service on 20th December, 1952 and replaced the medium-power transmitters which have carried the programme since 15th August, 1952.

General

The station is situated on a site of approximately thirty acres close to the Cardiff/Swansea road some five miles to the west of Cardiff. It is 400 feet above sea-level, and the transmitting aerials are located on the top of a 750-foot mast which brings the total height to over 1,100 feet. This is an important factor in securing the greatest possible service area, particularly in the hilly country of South Wales.

The vision transmitter operates on a frequency of 66.75 Mc/s (4.495 metres) and the sound transmitter on 63.25 Mc/s (4.745 metres).

The vision programme is received at the station over the G.P.O. distribution network which consists of a $\frac{3}{4}$ in. tube coaxial cable system from London via Reading, Bath, Bristol and Cardiff.

The sound programme reaches Wenvoe over specially equalised G.P.O. telephone circuits similar to those used for other B.B.C. transmitting stations.

THE NEW TRANSMITTERS

High-power Vision Transmitter

This transmitter, manufactured by Electric and Musical Industries, Ltd., is similar to that installed at the Kirk o' Shotts station. Low level modulation is used, and a block-schematic diagram of the essential units in the new transmitter is shown in Fig. 1.

The design has not only enabled a considerable reduction to be made in the physical size of the transmitter, but it offers increased overall efficiency with a consequent saving in power consumption.

The incoming vision signals are fed from the vision Lines Termination room to the modulation amplifier.

This consists of (a) a three-stage D.C. input amplifier using receiver-type valves exclusively and having a cathode-follower output, (b) a linearity correction amplifier and (c) a pre-modulation v.f. amplifier, also with a cathode-follower output, feeding the grids of the modulated amplifier. The black level is finally clamped at the input to the pre-modulation amplifier. The fact that this clamping has to be separated by a considerable number of stages from the transmitter output could introduce variations in the transmitted black level unless special precautions were taken. This possible difficulty is overcome by the inclusion of a black level r.f. feed-back circuit which monitors the black level at the transmitter output and injects a suitable correcting signal into the vision circuits. A further advantage of this technique is that it tends to reduce any mains hum introduced by the class "B" R.F. amplifiers forming the later stages.

The modulation is applied to the grids of a pair of ACT.27 air-cooled triodes which operate as an earthed grid push-pull modulated amplifier having an output of approximately 600 watts peak white. This stage is preceded by a pre-modulation R.F. amplifier, a frequency multiplier and the crystal oscillator stage.

The modulated amplifier output is fed to a chain consisting of three push-pull earthed-grid class "B" linear wide-band R.F. power amplifiers in series. The first employs a pair of ACT.27 air-cooled triodes and produces an output of 3 kW.; the second is fitted with ACT.26 air-cooled triodes and has an output of 12 kW., whilst the third uses a pair of BW.165 water-cooled triodes. The transmitter will be operated with an output power of 50 kW.

From the outputs of the modulated amplifier, inter-stage couplings of the wide-band three-stage coupled-circuit type are used, and these are so tuned that their pass-band centre frequency is about 0.7 Mc/s below the carrier frequency. The two side bands are thus not symmetrical—the upper one being slightly attenuated—but a filter is used to obtain the final asymmetric side-band condition. A further three-stage coupled circuit is used at the anodes of the output amplifier and this is arranged to change from a balanced to an un-

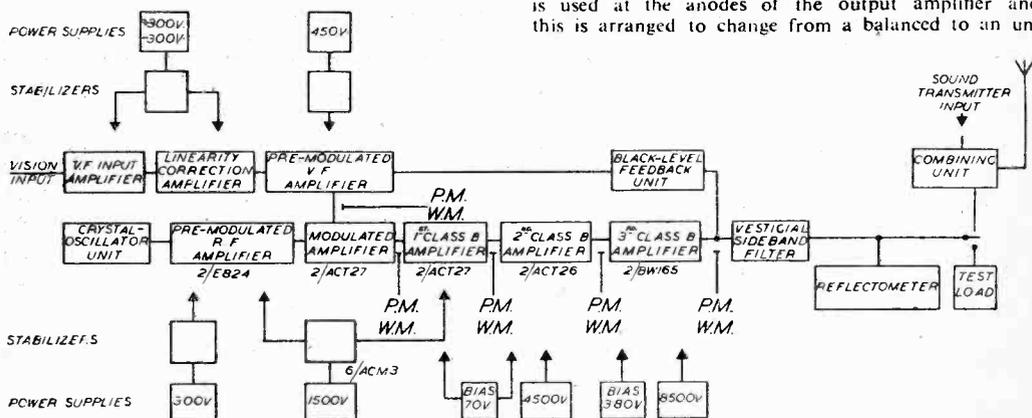


Fig. 1.—Block diagram of the essential units of the new transmitter.

balanced load to feed the coaxial output transmission line.

The high-voltage D.C. supplies for the high-power stages are provided by oil-cooled metal rectifiers; one of the advantages of this type of rectifier is that the control circuits are simpler than those associated with the hot cathode mercury vapour type of rectifier which has been used in previous stations.

Air for cooling the valves in the earlier stages of the transmitter is drawn from outside the building, filtered and blown through the cooling ducts at the rate of 3,000 cubic feet per minute. Two blowers of the centrifugal fan type are used for this purpose, one delivering filtered air to the transmitter and the other exhausting it by suction. By this means the air pressure in the cubicles is equalised and air leakage and noise are considerably reduced. Another improvement in this direction is that the design of the vision transmitter permits the air duct being led in from below; the connecting ducts to the cooler room are therefore run under the floor. The blowers are driven by V-belts at approximately 1,000 r.p.m. and produce an air speed in the main ducts of between 1,500 and 2,000 feet per minute. An arrangement of dampers is incorporated in the system whereby the air, after leaving the valves, can either be exhausted to atmosphere, or circulated in the building for heating purposes.

Distilled water is used for cooling the valves in the final stage. Three tanks are provided, the main tank with a capacity of 50 gallons, a 100-gallon reservoir tank and a 15-gallon expansion tank. The water is circulated by a centrifugal pump from the main water tank through a multi-tube radiator, where it is cooled by means of air from a separate air-blower, to the valve jackets in the transmitter and back to the main tank. Except for the air-blown radiator, the components are mounted together to form a self-contained unit. No ferrous metal is used in the construction of the water-cooling system which operates as a closed circuit to exclude air. Water expansion is taken up by the 15-gallon expansion tank in which the space above water level is filled with nitrogen at approximately 5 pounds per square inch above atmospheric pressure. The normal water flow required to cool a pair of BW.165 valves is 18 gallons per minute. The flow in the system is electrically metered. Contacts are provided in the main inter-lock circuit, to ensure that the transmitter cannot be powered until the water flow is correct. Conversely, a failure of the water-cooling system would close down the transmitter.

High-power Sound Transmitter

The high-power sound transmitter, manufactured by Standard Telephones & Cables, Limited, is of the conventional high-power class "B" modulated type. Modulation is applied at the anodes of both the penultimate and the final R.F. stages. The transmitter uses air-cooled valves throughout and will be operated with a carrier output power of 12 kW. There are five push-pull stages in the A.F. chain, the first two using 4074A double triodes; the third is a class "A" stage and uses a pair of 5C/450A pentodes. This is followed by a cathode-follower-driven stage having a low output

impedance and employing four 5C/450 A pentodes. The final class "B" stage uses two 3J/192E air-cooled triodes. Negative feed-back, derived from the primary of the modulation transformer, is applied over the A.F. chain. The R.F. side of the transmitter is composed of an R.F. exciter comprising a crystal-controlled oscillator followed by a buffer stage, two stages of frequency trebling and an output amplifier. The first stage of the transmitter proper uses a single 4H/180E air-cooled tetrode; the penultimate and final amplifiers each employ a single 3J/261E air-blast-cooled triode. Variable inductive coupling is used between stages. The filaments of the three R.F. power amplifiers and the class "B" modulator valves are supplied with heating current from metal rectifiers equipped with current-limiting reactances to control the current supplied to the filaments when starting. The remaining valve filaments are A.C. heated. The main high-tension supply is derived from a 6 kW, three-phase full-wave bridge-connected rectifier of the hot cathode mercury vapour type. A half-voltage half-wave output is taken between the star point and negative in order to supply the first earthed-grid R.F. amplifier and the A.F. driver stages. The equipment is grid-controlled, giving high-speed overload protection, together with automatic restoration of voltage and smooth increase of output voltage from zero on starting, as well as a substantially constant output voltage between plain carrier and fully modulated conditions.

The main blower of the air cooling system provides 3,300 cubic feet per minute to the base of the power amplifiers. Discharge air is drawn from the tops of the transmitter cabinets by a smaller exhaust blower. All the power equipment is housed in a separate enclosure, one compartment of which contains the power supply and distribution control contactors and protective circuits, whilst the other accommodates the high-tension rectifier and main modulation equipment.

Output and Combining Circuits

The output of the vision transmitter is passed to the vestigial side-band filter which consists of a constant-resistance filter of the transmission line type. It is composed of two complementary networks, the high-pass section being terminated by a constant resistance

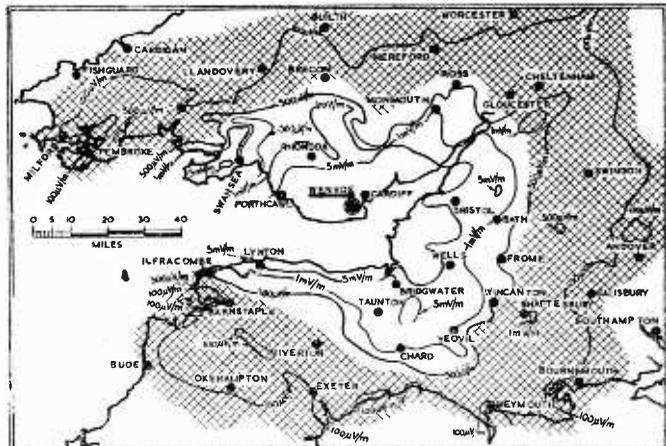


Fig. 2.—Approximate service area of Wenvoe. Considerable fading may be experienced in the shaded area.

absorber load and the low-pass section by the aerial system.

The filter is constructed from coaxial copper tube transmission line having an outer diameter of 5in., but with the diameter of the inner conductor varied to obtain the required impedance for the various stubs: The output of the low-pass section is taken to a change-over switch enabling the shaped output to be fed either to the combining unit and aerial or to the test load.

The combining unit into which the outputs of both the vision and sound transmitters are fed consists of a "sound-pass/vision-stop" filter inserted between the sound transmitter and the common output, and a "vision-pass/sound-stop" filter between this point and the vision transmitter output.

The mechanical construction of these filters is similar to that of the vestigial side-band filter.

Masts, Aerials and Transmission Lines

From the output of the combining unit the signals are fed to the common aerial at the top of the 750-ft. mast. The transmission line used for this purpose is of the coaxial type having an outer conductor of 5in. diameter copper tube and an inner conductor consisting of high conductivity copper wires which form the outer layer of a locked coil steel wire rope. This rope, together with the outer tube, is suspended pendulum fashion from the top of the mast and the rope is connected at the base of the mast to a loading mechanism so arranged as to apply a tensioning force of approximately two tons. Correct location of the inner conductor within the outer tube is effected by small rod insulators, spaced at 120 deg. which project from the inner surface of the tube at suitable intervals. This type of transmission line has a very high degree of electrical uniformity which is a necessary characteristic of lines intended for wide-band television transmission. The method of suspending and loading the transmission line results in its electrical uniformity tending to increase towards the end remote from the transmitter. This is a useful feature, as it reduces the formation of echoes; these have the greatest time-delay when the irregularities producing them are at the greatest distance from the transmitter.

The mast, which is built to the BBC's detailed specification of structural requirements, carries an aerial system designed to accept the full power from the main transmitters. Both the mast and aerial system are generally similar to those already in use at Sutton Coldfield, Holme Moss and Kirk o' Shotts. The supporting lattice-steel mast is 600ft. high and is triangular in section, each face being 9ft. across. This is surmounted by a cylindrical section, 110ft. high, having slots cut in its surface which may eventually form a very-high-frequency aerial for sound broadcasting should this system be installed at Wenvoe in the future. Surmounting the cylindrical section is a 40ft. steel tower carrying the combined sound and vision aerial. This consists of two tiers of four vertical dipoles, each fitted with an electric heater, controlled from the ground, to prevent the formation of ice on the dipoles which would upset their characteristics. The structure is stayed at four levels by sets of three locked coil steel wire ropes spaced equidistantly around the mast. The stays range in circumference from 4½in. to 6in. The longest stay is 860ft. All stays together weigh over 21 tons, and have breaking loads up to 210 tons. The mast is designed to withstand wind velocities of 80 miles an hour at the base, rising to 120 miles an hour at the top, under which conditions the total wind load is 80 tons. With this loading the masthead would move 7ft. 6in. from the

perpendicular. In calculating the loading, allowance has been made for a half-inch thick coating of ice distributed over all members and weighing some 23 tons. The mast weighs 140 tons and the total down-thrust on the concrete base including that due to the stays and ice, is 336 tons.

A separate 150ft. mast carries the emergency aerial system for use in the event of a breakdown of the main aerial or transmission lines. The emergency aerials are separately fed and switches are provided to enable a rapid change-over to be made from the main to the stand-by system.

Power Supply

Power for operating the station is taken from the South Wales Electricity Board's system. Duplicate 500 kVA. transformers fed from a 6,600 volt feeder provide a supply of 415-volts three phase 50 c/s. In addition, a 240-volt single-phase stand-by supply is available to provide mast lighting and other essential services if the E.H.V. feeder has to be disconnected for maintenance purposes. The H.V. switchgear, metering equipment and main L.V. switchgear are located in the annexe building, the transformers being mounted on an adjacent raft.

The Service Area of Wenvoe

The range within which consistently good reception of the programmes broadcast by Wenvoe can be expected depends upon many factors, the chief of these being the presence or absence of high ground between the station and the reception point, the height of the receiving aerial, and the amount of electrical interference. A map is given (Fig. 2) showing the estimated field-strength contours for the 50-kW. high-power transmitter; it will serve as a rough guide to reception conditions in the area, though there will be local variations. Reception is usually possible at a field strength as low as 100 microvolts per metre, although it depends on the degree of local interference, especially that produced by motor-cars.

The 1953 Radio Show

THE provisional dates previously announced for the 20th National Radio Show, Earls Court, London, 1953, are now confirmed.

The Show will be open to the public from Wednesday, September 2nd, to Saturday, September 12th, from 11 a.m. to 10 p.m. daily. The Exhibition will be closed on Sunday, September 6th.

There will be a pre-view on Tuesday, September 1st, from 11 a.m. to 6 p.m. Admission on this day will be by special invitation ticket from the Radio Industry Council, dealer's season ticket or by Press ticket. There will be no public admission on the pre-view day.

The planning of the Radio Show by the Exhibition Organising Committee, Radio Industry Council, is now well advanced. Mr. Ian Jeffcott, A.R.I.B.A., is again the Exhibition Architect and a new lay-out has been approved. BBC participation is assured, and in addition to the usual representative exhibits of radio and television receivers, components and valves, there will be an increased number of electronic demonstrations, an enlarged training exhibit and demonstrations by the Services.

Organisers are the Radio Industry Council, 59, Russell Sq., London, W.C.1 (Secretary, Mr. R. P. Browne; Deputy Secretary, acting for Mr. Browne at present, Mr. G. B. Campbell.)

JUST PUBLISHED! For the Servicing Engineer

**NO MORE WASTED TIME
for want of Circuit Diagrams**

HERE ARE HUNDREDS!

**Servicing data for all these
Radios:—**

Bush, Cossor, Ekco, Etronic, Ever Ready, Ferguson, Ferranti, G.E.C., K-B, Marconiphone, Masteradio, McMichael, Mullard, Murphy, Peto Scott, Philco, Philips, Pilot, Pye, Regentone, R.G.D., Sobell, Ultra, Vidor, etc., etc.

**Servicing data for all these
famous TV's**


Baird, Beethoven, Bush, Cossor, Ekcovision, English Electric, Ferguson, Ferranti, G.E.C., H.M.V., K-B, Marconiphone, Masteradio, McMichael, Mullard, Peto Scott, Philco, Philips, Pilot, Pye, Regentone, R.G.D., Sobell, Ultra, Vidor, White-Ibbotson, etc., etc.

Radio & Television Servicing

RADIO · TELEVISION · RADIOGRAMS · CAR RADIOS

Inspect this practical new work for servicemen—without cost or obligation. It is yours for **7 days** so that you can judge its value as a time and money saver—and **money maker!** Providing full installation and servicing data for the principal makes of Radio and T.V. (London and Sutton Coldfield Transmitters), it assures quicker and more efficient servicing. On the service bench alone it is worth an extra pair of hands! *If you are a service engineer or trainee don't let the opportunity pass—post the coupon now!*

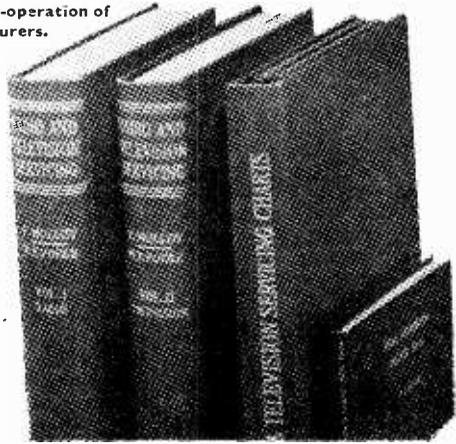Produced with the co-operation of the leading manufacturers.



Yours for 7 days' Free Examination

Study this great new work in the quiet of your own home for 7 days free of charge. You have everything to gain from this preview.

HERE IS WHAT YOU RECEIVE

2 Volumes strongly bound in maroon cloth, each 9½ in. x 6½ in.

1,432 Pages of practical information written by more than 30 skilled engineers, many of them executives of the biggest Radio and TV firms.

1,000 Photographs, explanatory illustrations, circuit, component and chassis layout diagrams, etc.

24 Servicing Charts, each 11½ in. x 16½ in., for popular models and trouble-tracing.

1 Strong Chart Case. Bound in cloth to match the volumes.

FREE! Radio Engineer's Pocket Book (value 5s.). A handy compendium of facts, figures and formulæ, which is presented free to every owner of RADIO AND TELEVISION SERVICING.

FREE! 2 years' Technical Advisory Service on any of the subjects in the work.

Don't miss this opportunity
SEND TO-DAY!

To: **GEORGE NEWNES, LTD., 66-69, GREAT QUEEN STREET, LONDON, W.C.2.**

YES, send me RADIO AND TELEVISION SERVICING. It is understood that I may return the work within eight days. If I keep it I will send a first payment of 10s. 6d. eight days after delivery and 10s. 6d. monthly until £6 6s. 0d. has been paid.

Name

Address

Occupation

Your Signature..... RTV3
(If under 21, your Parent's Signature.)

HOUSEOWNER
or TENANT?
(Strike out one)

Apply on our notepaper if you do not wish to cut this page.

"YOU CAN RELY ON US"

METAL RECTIFIERS.—Westinghouse, 1A86, 20/-; 14D96, 11/-; WX3, WX6, 3/9; 36EHT100, 20/4; LT52 (2v. 11a.), 19/6; 1 m.a. Meter, 12/6; 36EHT40, 21/6; 36EHT45, 23/8; 36EHT50, 26/-; S.T.C. Type K3/100, 14 8/8; K3/45, 9/-; RM1, 4/6; RM2, 5/-; RM3, 6/-.

HAYNES.—Scanning Coils, S914, S914H, S112, 42/-; S27, 45/-; Osc. Trans. TQ132, 13/-; TQ135, 18/6; Feed Chokes LUS5F, 23/-; LUS6L, 18/6; Line Trans. TW6/128, TW5/109, 42/-; Frame Trans. TK10/41, 35/-; E.H.T. Line Trans. T27, 132/6; T34, 50/-; Amp. Control, VL5, 12/6; Tuning Coil Kit, 20/-; P/pull Output Trans., TK12/61, 38/-.

"G-MAX" CUTTERS.—Chassis Punch complete with Key, 4in., 4in., 12/4; 4in., 13/4; 4in., 11in., 11in., 16/-; 11in., 11in., 17/9; 11in., 19/9; 2-3/32in., 31/8; 1in., Square, 24/8.

HUNTS' MIDGET MOLD-SEAL CONDS.—1 mfd. 150v., 1/6; .02 mfd. 150v., 1/6; .005 mfd. 350v., 1/6; .01 mfd. 350v., 1/6; .02 mfd. 600v., 1/2; .001 mfd. 350v., 1/3; .002 mfd. 350v., 1/3; Midget Electrolytics, 32-32 mfd. 250v., 2in. x 1in., 9/-; 16 mfd. 350v., 4/-.

WAX PAPER.—1 mfd. 500v. (543), 1/3; 1 mfd. 750v. (743), 1/6; .05 mfd. 350v., 1/-.

THE "MOTOK" TAPE DECK

After careful inspection we now offer a Tape Deck we can really recommend.

- *Brown Crackle Steel Frame.
- *3 Collaro High Torque Motors (A.C. 250 25v.).
- *High Impedance Twin Track Record and Erase Heads.
- *Heavy Accurately Machined Flywheel.
- *Capstan Machined to Stringent Limits.
- *Tape Speed 7 1/2 in. per Second for Quality. (Using Twin Track, one Spool will give 1 hour's playing.)
- *Rewind and Fast Forward in 1 Minute.
- *Free from "Wow" or "Flutter".

This is a fine "Deck" at a moderate price and will operate well with a 5-valve Amplifier and Oscillator (Circuit supplied).

Price: £15/15/-, Post 5/-; Erase Head, 39/6; Record Head, 39/6; Oscillator Coil, 8/6. Can be supplied separately.

MAINS DROPPERS (New).

—2a. 950 ohms, 3a. 800 ohms, 5v., Midget, 6/8; Linecord, 2a. 100 ohms ft., 3a. 60 ohms ft., 8d. per ft. ADCOLA Pencil Bit Irons, 200-220v., 230-250v., 25/6.

METAL PACKS.—25 mfd. 350 v., 2/8; .5 mfd. 350v., 3/-.

CERAMIC TUBES.—47 Pf., 1/9; 10 Pf., 2/8; 40 Pf., 2 6/8; 2 Pf., 1/-.

MOLDED MICA.—001 mfd., CM20N, 1/6; .001 mfd., MWN, 1/9.

PAPER PACKS.—1 mfd. 350v., 2 mfd. 150v., 10 mfd. 25v., 20 mfd. 12v., 2/6 each.

ELECTROLYTICS.—100 mfd. 350v., 13/6; 250 mfd. 60v., 10/-; 2,500 mfd. 3v., 6/9; 2,000 mfd. 6v., 8/6; 2,000 mfd. 12v., 12/-; 1,000 mfd. 6v., 5/6; 500 mfd. 6v., 4/-; 100 mfd. 25v., 4/-.

T.C.C. CONDENSERS (NEW)

METALMITES.—1 mfd. 200v., 2/4; .1 mfd. 350v., 2/3; .05 mfd. 350 & 500v., 2/-; .005 mfd. 500v., 1/10; .002 mfd. 500v., 1/8; .001 mfd. 500v., 1/6; .01 mfd. 350v., 1/8; .01 mfd. 500v., .105 mfd. 350v., 2/-; .001 mfd. 1,000v., 2/2.

FILAMENT TRANSFORMERS.—200 240v. to 6.3v. at 1 1/2a. (Small), 8/6; 200 240v. to Multi-tap Secondary, 2v. to 30v. at 2a., 2 1/2/-; 6.3v. at 3a., 12/6.

VIBRATOR TRANS.—280-0-280v., 12v. Primary, 23 6/8; Primary 6v., 23/6; 75 m.a. PRIMISTORS, CZ1, 3 6/8; CZ2, 2/6; CZ3, 1/6.

COILS.—All Wearite "P" Coils stocked, 3/- each. All Weymouth Coils stocked. "H", 3/0; "K", 4/9; CF2W2, 10/6 pair; CSW3, 12/6.

ALADDIN FORMERS.—Inn., 7 1/2; 1in., 10 1/2, with Cores. **TRIMMERS.**—50 pF., 9d.; 100 pF., 150 pF., 1/-; 250 pF., 1/7; 500 pF., 2/-; 750 pF., 2 3/8; Twin 50 pF., 1/3.

MULTICORE SOLDER.—60/40 Core Solder, 6d. and 5-carbons.

E.H.T. OSCILLATOR COIL.—8-11 kv. Wound on a Polyester former and of high quality, 39/-; Coil complete with Mazda U25 Valve mounted and wired with anti-corona wire, 67/6; Complete Unit in louvered case, 126/6. Circuit supplied with coil and unit. NEW.

COLVERN PRESET WIRE-WOUND POTS.—100, 250, 500, 1 K., 2 K., 2.5 K., 5 K., 10 K., 20 K., 25 K., 30 K., 3 3/8 each.

MID POINT & B.Y. SWITCHES.—2p. 6w., 3p. 4w., 4p. 3w., 1p. 2v. (New), 4/-; Surplus, 8p. 4w. (4 Bank), 4 6/8; 6p. 3w., 3/6; 1p. 2v., 2/-.

CHOKES.—40 m.a. Midget, 5/6; 50 m.a. 15H., 6/6; 90 m.a. 10H., 14/-; 70 m.a. 1,200 ohms 40H., 17/6; 250 m.a. 5 Hy., 19/6; Surplus, 150 m.a. 5H., 7/6.

R.F. Chokes, TV diode, L9, 2/-; M.W. L.W., 2/6; Audio 5,000 ohms, 10/-.

VIEWMASTER WB PARTS.—Width Control, 10/-; Boost Choke, 5/9; Frame Trans., 25/6; Line Transformer, 32/6; Focus Magnets, 22/6; Vision Chassis, 18/6; Sound and T.V., 18/6; Bracket, 6/-; Scanning Coils, 33/8.

RADIO SERVICING CO.


Our No. 11 Catalogue, price 6d., Post Free. Postage: Over £2 free, below 10/-, 6d.; £1, 9d.; £2, 1/-.

444, WANDSWORTH ROAD, CLAPHAM, LONDON, S.W.8.

77, 77A, 168, 169 Buses, S.R. Station; Wandsworth Road. Open till 6.30 p.m., 2 o'clock Wednesday.

The new ARMSTRONG Television Chassis Model T.V.15

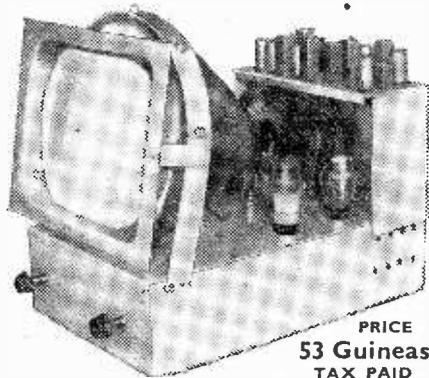incorporating a 12in. C.R.T., is now available for distribution



**PRICE
53 Guineas
TAX PAID**

Also available in a beautifully veneered two-toned walnut
CONSOLE CABINET. 63 GUINEAS Tax Paid.

Installed free.

Comprehensive Maintenance Service available.

Please send for Radiogram and T.V. list, post free.

ARMSTRONG WIRELESS & TELEVISION CO., LTD.,
WALTERS ROAD, HOLLOWAY, LONDON, N.7.
Telephone—NORth 3213.

SAFE, RELIABLE E.H.T



The NERA R.F., E.H.T. unit has been designed to provide a safe and reliable source of D.C. high voltage for all C.R.T.s including the new wide angle and aluminised types. The output is continuously variable between 8 to 12 kV. at approximately 500 microamps.

PRICE £6 · 10 · 0 COMPLETE

The unit is completely wired and tested ready to switch on, requiring only H.T. and L.T. connections. Ample shielding is provided to prevent radiation and interference to Broadcast receivers. The coil with rectifier incorporated may be purchased separately. Full instructions and data supplied.



**COIL & RECTIFIER
PRICE: £3 · 17 · 6**

**WITH THE
NERA R.F., E.H.T. UNIT**

Full details from:
AREN (RADIO & TELEVISION) LTD., HIGH ST., GUILDFORD

Obtaining a Good Interlace

SYNC SEPARATORS AND INTERLACE FILTERS EXPLAINED AND ANALYSED

By M. Lock

A GOOD interlace is not a feature very commonly found in the more popularly-priced commercial receivers, a fact which causes some dismay to amateur constructors, although it is true that the amateur can, with the exercise of a little care, usually produce a superior result since his problem is confined to one set only. It is hardly necessary to dwell upon the importance of good interlace, particularly in the case of a well-focused 12in. picture, which even if not being in the extreme case of giving 202-line picture (100 per cent. pairing) is still very unpleasant to watch if bad pairing or a drifting of interlace is produced. Assuming that these matters need be laboured no further, we must find the most common causes of bad interlace to appreciate what we have to cure.

caused by screen charge on the C.R.T. and an examination of the frame timebase, by means of an oscilloscope, would naturally show interlacing *all* the time!

Having tried to avoid the obstacles, we now come to the real cause, which is line-pulses in any form getting into the frame timebase by any means whatsoever. In fact, as a cut-and-dry method particularly useful in the older types of frame timebases using a thyratron and consequently a very small synchronising pulse, it is often effective to experiment with a 0.1 μ F condenser by trying its effect from the cathode of the frame output valve to earth, the thyratron cathode to earth or even across the H.T. supply actually on the timebase chassis. In this respect, it may be desirable to add a further stage of decoupling to the H.T. supply to the frame timebase to ensure that no line-pulses are being coupled in via the H.T. supply. Again, if a synchronising circuit is being used which relies upon the picture separation taking place due to a large time constant and a diode, the condenser C in Fig. 1 should be of excellent quality (low-leakage), otherwise many synchronising troubles will be experienced.

There are, of course, three main ways in which line-pulses get into the frame:

1. Via the H.T. line (as the H.T. supply acts as a common coupling impedance), or the heater supply.
2. By stray pick-up of pulses at line repetition frequency, generated in the line timebase, and sync valve.
3. True line synchronising pulse or pulses emanating from any heavy discharge pulse in the line oscillator valve finding their way through the synchronising separator to the frame oscillator valve.

The first two causes can be overcome without recourse to much that is special. In case No. 1, if the power supply is A.C./D.C. the smoothing condenser will usually be about 200 μ F, which will be effective so long as it has no appreciable inductance. In cases of doubt, the effect of an extra stage of resistance decoupling to the frame oscillator valve only can be tried as a temporary measure to see if it is necessary (Fig. 2). In the case of normal H.T. supplies, where the voltage rail is of 300/350 volts, it is usually advisable to decouple the whole frame timebase separately. However, in the case of a single receiver problem, it is always worth while trying it out, on the chance that it may be effective.

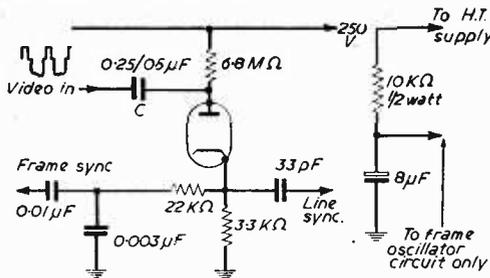


Fig. 1 (left).—Condenser C in this circuit must be of high quality. Fig 2 (right).—Additional decoupling circuit.


Required Accuracy of Synchronising

It is useful to know the minimum standard to which we must work. The author has found that with a 12in. tube closely viewed no disturbance of interlace can be detected unless the time-difference between the start of alternate frame scans is at least between 5 and 10 μ s. Therefore, to aim at closer limits is normally a waste of effort. This still imposes a strict limit on the apparatus, bearing in mind that a single-frame pulse lasts 40 μ s. Of course, we are committed to synchronising on the same frame pulse for every frame scan. This must invariably be the first one of the block; this will be dealt with in detail later.

Causes of Non-interlace

Let us first of all dispose of a common fallacy; stray pick-up of 50 c/s hum, or such hum introduced in any way into the timebase, whether thyratron or hard valve, does not cause interlace trouble. It will, under certain circumstances, cause many other troubles, particularly in regard to odd linearity defects and difficulty in maintaining really solid synchronising, but it will not be the cause of non-interlace.

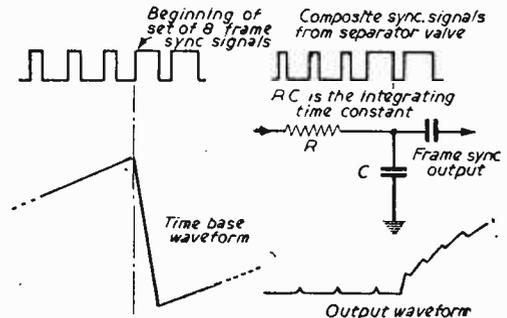Another puzzle that sometimes occurs is of practical importance, but difficult to do much about. That is the effect observed on some picture tubes of interlace changing with the prevailing humidity! This does appear true since breathing on the tube face may cure the pairing which seems to be present, although in fact the trouble is



Figs. 3 & 4.—Frame pulses and waveform from sync separator.

If the frame timebase H.T. supply is obtained from the "boosted H.T. rail" of a line timebase circuit of the efficiency-diode type it may again be necessary to use extra frame oscillator decoupling as in Fig. 2, but in the author's experience this is not often the case. These expedients, however, should always be tried when trouble with interlace is experienced. In the case of the heater supply being suspected as a cause of coupling in the line-pulses, it should suffice to try a 0.1 μ F from one side of heater to earth. This, by the way, is a fairly unusual cause of trouble.

In case No. 2, all that is required is to keep frame components and wiring well away from all parts of the line timebase where large pulses are found, particularly

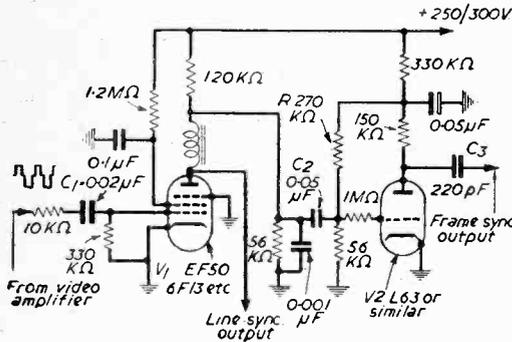


Fig. 5.—Sync separator and triode interlace valve.

the line scan transformer. Also keep the frame synchronising lead short, or pick-up will almost certainly occur. If this cannot be done, the lead carrying the frame synchronising pulse should be screened, as is usual with a gramophone pick-up lead.

Finally, in this respect we must not overlook the possibility of magnetic coupling inducing line frequency pulses into the frame circuit. This can happen most easily if the frame oscillator blocking transformer (where one is used) has been mounted so as to be in the leakage field near the line output or even the line blocking transformer. It may even be necessary, in extreme cases, to screen the frame oscillator transformer if it is too inconvenient to shift it. In this case a high-permeability material such as mu-metal should be used for the screen-

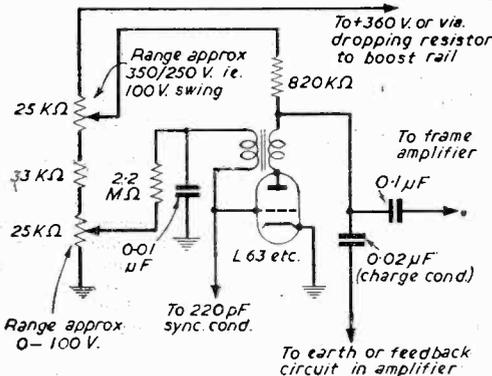


Fig. 7.—Frame blocking oscillator for use with sync circuit of Fig. 5.

ing can. It is even possible, although less likely, that a large loop of wire associated with the frame oscillator circuit may have line-pulse currents induced in it, but this can easily be avoided by more compact wiring, and, above all, keep the frame oscillator circuit well separated from the line output components, then no trouble of this nature will be encountered.

Synchronising Circuits for Good Interlace

Whatever types of timebase circuits are used, even if all the precautions detailed are taken, it is still impossible to achieve the desired result unless the synchronising

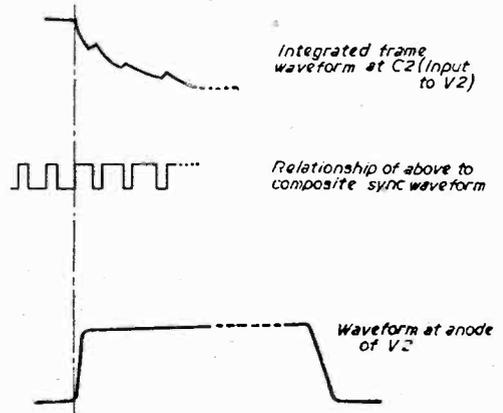


Fig. 6.—Frame pulse as integrated by the Fig. 5 circuit.

circuit is providing accurately timed pulses. This can be done in many ways, but those shown are very effective.

The object is to produce a pulse which will always initiate the discharge of the frame oscillator at the beginning of the block of frame pulses (Fig. 3), and there must be excellent discrimination between line and frame synchronising pulses. It is clearly not easy to obtain accurate timing with the simple integrating circuits which give a slowly rising pulse by integrating all the eight frame pulses, the slope being such that triggering may take place over a much wider time-range than the 5 to 10 μ s, which we have specified, and any alteration in the frame speed controls will certainly alter the interlace (Fig. 4). It is also an advantage to render the valve supplying frame synchronising signals inoperative when only line synchronising pulses are being transmitted. This not only keeps out line synchronising pulses, but all pulses at line frequency generated by the line oscillator which may find their way into the synchronising circuit

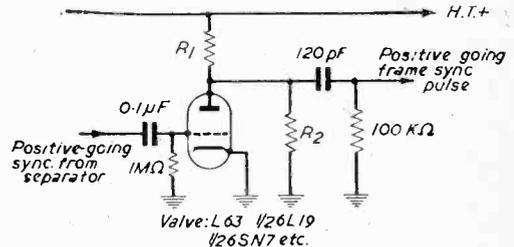


Fig. 8.—Positive pulse producing interlace stage. R1 and R2 depend on valve used.

are likewise prevented from getting through. This can be achieved in the first circuit described.

We require two valves, one for separating synchronising from picture, and the second for separating frame from line and at the same time producing a suitable type of waveform from the frame synchronising signals to fire the timebase.

The exact form which the circuit of the first valve V1 (Fig. 5) takes is not important; its function is to


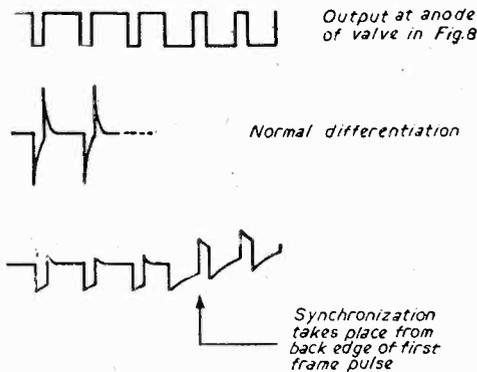


Fig. 9.—Frame pulses in which the back instead of the leading edge is used.

produce synchronising pulses free of all picture, which are passed on to V2 which produces an accurately timed single pulse for the frame and gives no output during the remaining time (i.e., it is "dead" to all line synchronising pulses).

In Fig. 5, the only unusual component is the choke in the anode of V1. It is an advantage to use this circuit in place of the more common resistive load for several reasons, not the least of which is that it prevents a disturbance of line sync amplitude during the frame synchronising period. Such an inductance can readily be constructed by winding between 500 and 1,000 turns of 40 s.w.g. enamelled wire on a small former about

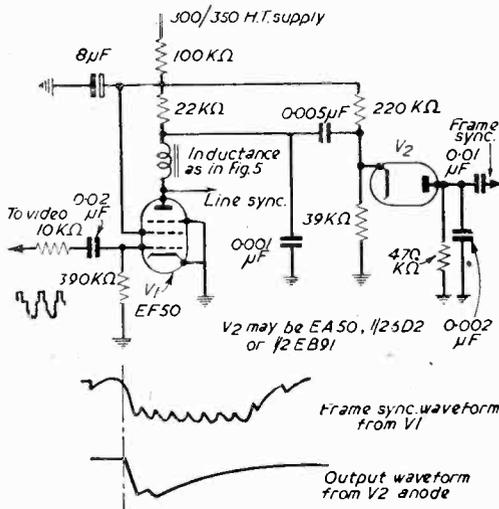

Figs. 11 & 12.—A circuit for producing a negative pulse and the waveforms associated with it.

¼ in. to ½ in. dia., and using mu-metal laminations reclaimed from ex-surplus components (e.g., a small microphone transformer or something similar). The precise inductance is not important. It would also be possible to find a wave-wound single section from an R.F. choke of about the correct number of turns and remove it, if suitable laminations can be found to fit it. The core should be assembled as a transformer, i.e., interleaved and not choke fashion.

The action of V1 is obvious. The valve takes grid current, being fed with positive-going synchronising pulses, and the grid acts as a D.C. restorer, a steady potential being maintained across C1. The valve is operated at very low screen volts so that it has a short grid-base (i.e., a small excursion of voltage in a negative direction will cut off the anode current entirely), and with the grid-current bias used, only a small part of the synchronising pulse is effective in producing anode current. Thus all the picture signal has been suppressed, and since the positive tips of the synchronising pulses cause the grid current to flow (which means, of course, that the grid of V1 presents a very low impedance during that time) the "noise" present on the synchronising pulse tips is removed as well; this gives a clean synchronising output to start with.

We will not consider the line synchronising as it does not come within the scope of this article, but simply

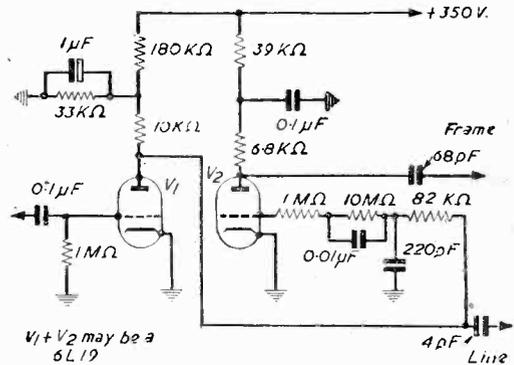


Fig. 10.—Two triodes are used in this positive pulse circuit.

take the frame synchronising signals as they arrive at the grid of V2. This valve is made to pass grid current by connecting the grid to H.T. via a high resistance. When a frame synchronising signal arrives it has already been partially integrated (Fig. 6).

Until the arrival of this frame waveform, the grid current has been flowing and the valve has been conducting, but as soon as the first frame pulse arrives, the grid is carried negative by an amount exceeding its grid-base, and the anode current ceases. As the time-constant of the grid circuit components of V2 is arranged to make each of the eight-frame pulse negative tips reach about the same (negative) level, V2 will remain cut off for the whole of the block of eight frame pulses. As soon afterwards as is permitted by the time-constant of the anode components, current will again flow in the anode of V2 since the large negative signal has been removed from the grid and the connection to H.T. via R is supplying once more a positive bias more than sufficient to overcome any line-pulses arriving at the grid of V2. We now have a waveform whose leading edge may be used to synchronise a blocking oscillator or thyatron b

applying it via C3 to the grid of the oscillator. If desired, in cases where only a very small synchronising pulse is needed and great accuracy of synchronisation required, the waveform obtained may be differentiated and the positive pulse obtained used to fire the timebase. There is, however, a limitation to the use of this circuit in the case of blocking oscillator timebases. It cannot be used if the charge condenser is in the grid circuit, but only when it is in the anode, as is more usual when high H.T. voltages are being used. In A.C./D.C. type sets with H.T. supplies of 160-200 volts only, the charge condenser is usually put in the grid circuit and under such circumstances the circuit just described will give the appearance of slow flyback (i.e., folding over at the top of the picture), due to the 400/ μ s block of frame pulses from the synchronising circuit coming to an end before the grid current pulse of the blocking oscillator, and disturbing the action of the oscillator. The cure is to use the circuit of Fig. 7 at all times when a blocking oscillator is used, and if insufficient H.T. is available due to A.C./D.C. technique then the "boosted H.T." from the efficiency diode circuit, always present in such a low-voltage receiver, will have to be utilised.

The other circuits shown can only be touched upon briefly, and though they may represent slightly less foolproof designs for the home-constructor working without an oscilloscope to see just what is happening, they may readily be adjusted to give good results. Fig. 8 gives the circuit of a frame interlace valve which will give the same polarity of output synchronising pulse, but works off a positive input instead of negative. This apparent contradiction is explained as follows: the frame output pulses at the anode are in fact negative going, but the back edge of the first one is used as the synchronising pulse. This is achieved by employing a partially differentiating output circuit which tilts the waveform. The line pulses do not get tilted much, due to their short duration, but the frame pulses, being longer, are tilted more and have much less time (in between pulses) to sink down again, so they stay up (Fig. 9). The valve may be any triode (L63, 6J5, etc.) or triode-connected pentode.

Next, there is an interesting circuit also giving positive synchronising output (Fig. 10), but using two triodes for the whole synchronising circuit. It may be convenient to use a double triode such as the ECC32, 6L19, 6SL7, etc., or two separate triodes or triode connected EF50's or VR65's.

We need positive-going synchronising signals from the video amplifier which are applied to V1 which has low H.T. and thus a short grid-base. Hence, the picture is removed and only the positive synchronising pulses cause the valve to draw current; in addition the tops of the synchronising pulses are cut off, due to the heavy grid current flow that they cause. V2 acts very much as V2 in the first circuit described (Fig. 5) and is normally conducting. The synchronising waveform at the grid

is likewise affected by a time-constant such that the frame is raised above the line, and the output from the anode is obtained only when the frame pulses arrive. If this result should not be achieved, the H.T. potential at the anode of V1 may be too high, causing the grid base to be too long, which would result in insufficient separation of picture. The second likely need for adjustment would be to the time-constants in the grid circuit of V2, mainly the 82K Ω and 220 pF.

It will be evident from the foregoing that we have described only those circuits which give a very accurately timed synchronising pulse which will ensure that the frame timebase is fired on either the leading or back edge of the first of the eight-frame pulses in the transmitted synchronising waveform. There are many variations of the described circuits, and one in particular must be mentioned. This is commonly used and quite effective when properly adjusted. In contrast to the previous circuits this one gives a negative output pulse and, therefore, if a blocking oscillator is used, the synchronising pulse must be applied to the anode. It is also very useful for Miller-integrator types of circuits. The circuit values of Fig. 11 are given for an EF50 valve in the position of V1, but it will be appreciated that this is essentially the same as V1 in Fig. 5, so that the two may be interchanged. The operation will, therefore, only be mentioned in reference to the diode. The coupling time-constants between V1 and V2 partially differentiate the waveform (the components joined to the diode cathode are those concerned). Two of these components, the 220 K Ω and 39K Ω resistors, bias the diode such that it will not conduct unless the amplitude of the waveform reaching the cathode is greater than that of the line pulses. This means that the diode will only conduct on frame pulses (which have, as with the circuit of Fig. 5, already been raised above the line pulses at the anode of V1). It should also be observed that when the diode conducts, that the anode components are placed in parallel with the cathode components, which causes a slow decay to the frame synchronising pulse. The amplitude of the negative synchronising pulse obtained is approximately 10 volts.

A final word may be useful on the choice of the main separator valve. This is normally a pentode, and for maximum output voltage, easy achievement of separation, and a short rise-time for the output pulses a high-slope, short grid-bias valve, such as an EF50, EF80, 6F12, etc., is desirable. When this is not convenient, the compromise in results caused by using less suitable valves (of the low-slope, audio output type) is by no means disastrous. So long as the screen voltage is kept down to 10 or 15 volts by the use of 1.5 M Ω to 2.2 M Ω screen resistors, and a small amount of experimenting is done with the value of anode load around a value of 100 K Ω or so, perfectly good results are obtainable. These remarks apply, of course, to any of the circuits described.

TELEVISION PRINCIPLES AND PRACTICE

By F. J. GAMM

CONTENTS: The BBC Television System; The Television Camera; From Transmitter to Receiver; Projection Receivers; Stereoscopic and Colour Television; Time Bases; DC Receivers; Aerials; A London-Birmingham Converter; Servicing; Interference; A Pattern Generator; Choosing a Receiver; The Beveridge Report; Dictionary of Television Terms.

Price 25/- or 25/8 by Post. Available from:

GEORGE NEWNES LTD., TOWER HOUSE, SOUTHAMPTON ST., STRAND, W.C.2.

the oscillations set up in the output transformer secondary during flyback; obviates, or reduces, the amount of damping necessary; provides the initial scanning current while the line output valve is cut off, and at the same time sets up a bias voltage which is effectively added to the anode supply of the output valve.

When the E.H.T. output is taken from the overwind on the transformer, using only one K3/100 rectifier, 5/6 kV. is available.

A Multiplier

Shown in dotted lines is a one and a half times multiplier, which should be wired into the circuit when a 8/9 kV. output is desired. The pulse at the anode is used to supply the boost rectifier, the output of which is added to that obtained from the transformer overwind, resulting in an increase of about 40 per cent. in E.H.T. voltage.

The same two metal rectifiers and three .001 μ F condensers may be wired into the circuit, as shown in Fig. 3, to form a voltage doubler, giving an output of 12/13 kV.

The components comprising the booster should be mounted on a small piece of bakelite near the line output valve.

New RCA Tubes

THE RCA Tube Department has announced a small TV camera tube intended for industrial television applications. Its small size and simplicity facilitate the design of the camera and associated equipment as compared with camera equipment required by larger types of camera tubes.

Utilising a photoconductive layer as its light-sensitive element, this new camera tube, designated as the RCA-6198 Vidicon, has a sensitivity which permits televising scenes with 100-200ft. candles of incident illumination on the scene. The photoconductive layer has a spectral response characteristic approaching that of the eye.

The 6198 provides 400-line resolution, employs magnetic focus and magnetic deflection, and operates with relatively low D.C. voltages.

Measuring only about 1in. in diameter and 6½in. in length, the 6198 lends itself to use in light-weight, compact television cameras. The size and location of the photoconductive layer permit a wide choice of commercially available lenses.

A series of components designed especially for use with the 6198 is planned for commercial availability this coming autumn, according to an announcement from the RCA Tube Department. The series will include a deflecting yoke, focusing coil, alignment coil, horizontal-deflection output transformer, and vertical-deflection output transformer.

A technical bulletin on the 6198 can be supplied on request to RCA Photophone Ltd., 36, Woodstock Grove, London, W.12.

RCA-6199 Multiplier Phototube

A new, small, 10-stage multiplier phototube of the head-on type has been recently introduced by the RCA Tube Department. Designated as the RCA-6199, this new multiplier phototube is intended for use in scintillation counters, and in other applications involving low-level, large-area light sources. Because of its small size, the 6199 is especially suited for portable and fixed equipment where space considerations are important.

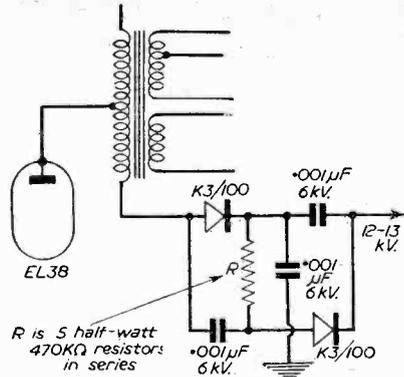


Fig. 3.—In this circuit the same two metal rectifiers are employed as a voltage doubler.

A reduction in E.H.T., with or without multiplier in circuit, may be had by shunting the line coils with a fixed condenser, value 100 to 1,000 μ F.

The spectral response of the 6199 covers the range from about 3,000 to 6,200 angstroms with a peak value at approximately 4,000 angstroms. The 6199, therefore, is highly sensitive to the blue-rich light emitted by excited organic phosphors such as anthracene and inorganic materials, such as thallium-activated sodium iodide.

Design features of the 6199 include a semi-transparent cathode, having a diameter of 1½in. on the inner surface of the face end of the bulb; a face with a flat surface 1in. in diameter to facilitate the mounting of flat phosphor crystals in direct contact with the surface; and 10 electrostatically focused multiplying stages.

The relatively large cathode area permits very efficient collection of light from excited phosphor crystals, such as are employed in scintillation counters.

A technical bulletin on the 6199 can be supplied on request to RCA Photophone Ltd., 36, Woodstock Grove, London, W.12.

MULLARD VALVE DATA

THE popular wall chart and pocket book has been brought completely up to date and now includes data for germanium crystals and the new rectangular picture tubes MW36-22 and MW36-24.

The distinguishing feature of this year's wall chart is the new yellow cover designed by Ronald Ingles, M.S.I.A. Finished in a heavy high-gloss varnish, the cover will withstand the most constant handling and yet remain as conspicuous as ever.

Other Mullard innovations of previous years, such as the "step ladder" presentation of the title pages and the metal hanger inset in the spiral binding, have, of course, been retained.

Other contents of this year's wall chart are shown under the following headings: List Prices; Base Diagrams; Battery Types; Series Operated Types; 4-Volt Types; 6.3-Volt Types; Television Tubes; Stabilisers; Germanium Crystals; Flash Tubes; Photo-cells; Substitutions for Non-current Mullard Valves; Direct Equivalents; Near Equivalents.

Mullard Valve Data is again available in pocket booklet form. Like the wall chart, this year's edition of the pocket book has a bright yellow cover.

A BEGINNER'S RECEIVER

AN EASILY-BUILT SUPERHET CIRCUIT, UTILISING AN EX-GOVERNMENT UNIT—R3170A

By B. L. Morley

IT is generally agreed that at and beyond the fringe areas a superhet is more desirable than the straight receiver by reason of its signal-getting properties. Unfortunately, there are very few superhet circuits which have been designed for the home constructor; it is hoped that the details given here will enable even the novice to enjoy the advantages of this type of circuit.

The set comprises a sound and vision receiver complete with power pack, built together on a single chassis. It is, therefore, entirely self-contained, and can be used with any form of timebase and CRT. The details given here are for a sound and vision receiver only; it is hoped at a later date to produce data for (1) a timebase and CRT network for an electrostatic tube (VCR97) complete with power supplies on a single chassis; (2) a timebase and CRT network for an electromagnetic tube (standard type) complete with power supplies on a single chassis. The completed televisor, whether using VCR97 or normal magnetic tube, will, therefore, occupy two self-contained chassis.

The receiver unit can be operated either horizontally or vertically and can, therefore, be accommodated in a prefabricated cabinet of the types which are available to the amateur constructor.

As the unit is complete in itself it can be used in conjunction with any timebase and CRT unit which the reader may have.

The basis of the receiver is an ex-Government unit—the R3170A, but don't let that fact put you off; as you will see from the photographs, the appearance of the chassis is quite pleasing. Moreover, really detailed instructions are given so that the novice need not hesitate to tackle the job. The more advanced constructor who can quite happily wire up directly from a theoretical diagram is advised which parts of the data he can skip!

We are all interested in costs these days, but the author is not going to fall into the trap of giving a detailed price list; the cost of various components rises and falls with each issue of PRACTICAL TELEVISION, due to the fluctuating supplies, and this is particularly true where ex-Government apparatus is used. Suffice it to say that this combined vision and sound unit can be built for round about £10 and the electrostatic tube unit for about another £10, making £20 in all. If a magnetic tube is used, then the cost will be a total of £30-£35.

In order to assist the constructor two lists

of components have been made; one is the shopping list and will enable the current cost to be easily assessed and at the same time provide an easy reference table, and the other is a complete list of components and values.

There is no difficulty in obtaining the R3170A, which is available from several regular advertisers in this journal.


Although some of the coils must be home-made, they are very simple to construct, detailed instructions being given.

Provided the data is carefully followed, there should be no difficulty in aligning the receiver without the aid of a signal generator; the vision I.F.s need no alignment as this has been arranged in the unit; the bandwidth has been given as 4 Mc/s.—under test the unit enabled the 2.5 Mc/s. lines to be resolved 80 miles from Sutton Coldfield, which is more than sufficient for long-distance reception. For those luckier people nearer the transmitter there is no reason why this cannot be improved upon.

The R3170A

This is the unit on which the complete vision and sound receiver is based. It is a handsome job with a very neat layout and contained in a chassis which measures 7½ in. by 8½ in. by 19 in. overall. Fig. 1 shows a view of the layout.

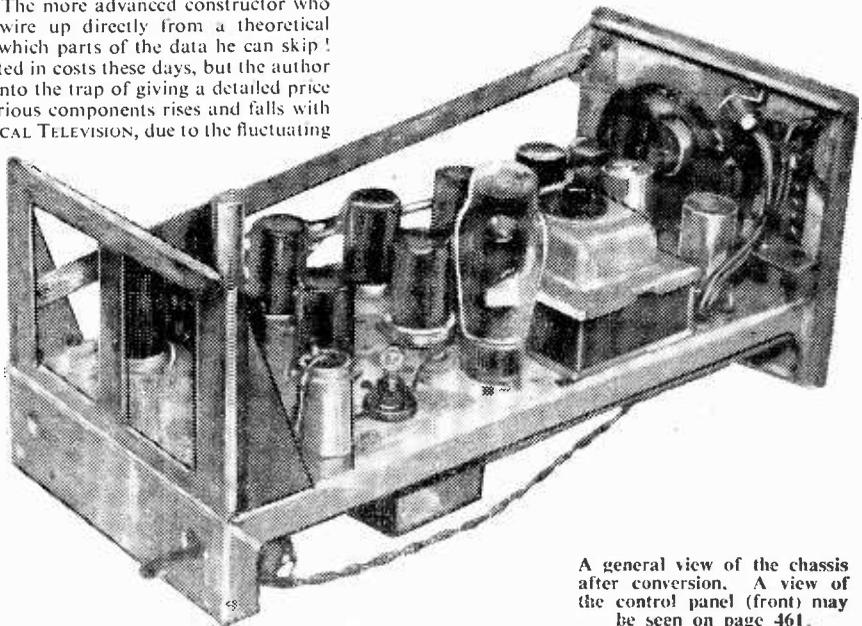The valves supplied with the unit are as follows:—8 of EF50 (red Sylvania type), 2 of CV66 (EC54), 1 of VR137 (EC52), 1 of VU111 (HVR2), 1 of VU39 (MU14), 2 of VR92 (EA50) and 1 of CV118.



A general view of the chassis after conversion. A view of the control panel (front) may be seen on page 461.

Neither the VU111 nor the CV118 is used in the modified version, though the former valve can be used as an EHT rectifier for the VCR97 tube.

An I.F. section at 30 Mc/s. is incorporated, and this portion is used for the vision section.

without having to get up from one's chair to adjust the contrast control.

A manual control is provided to vary the oscillator frequency within certain limits; this enables any frequency drift due to heating effects to be counteracted

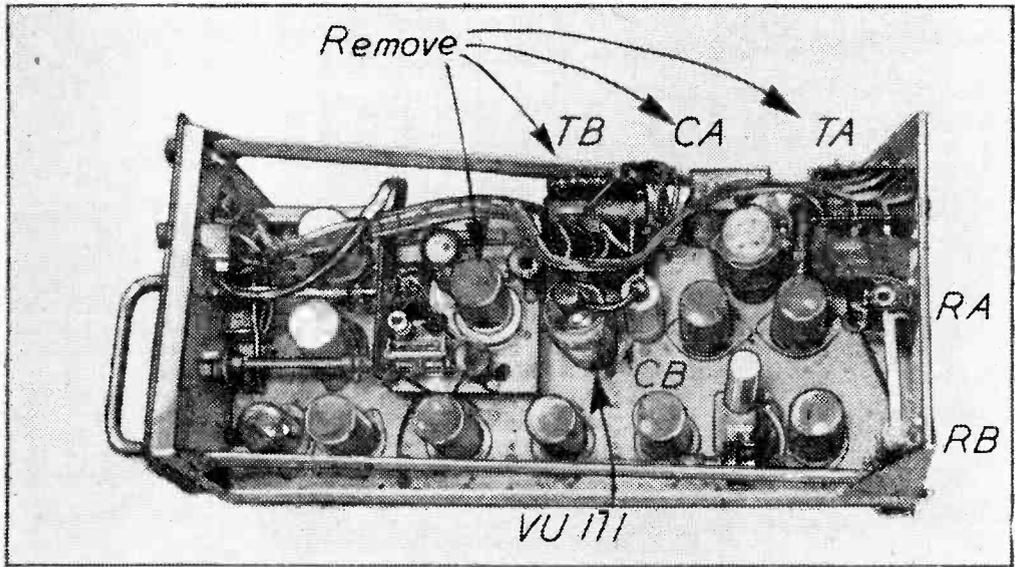


Fig. 1.—General view of the unit as purchased.

Special Features

The completed receiver incorporates several unique features in order to increase its efficiency at extreme ranges.

Variable video coupling is incorporated so that the balance between quality and quantity of the signal can be manually adjusted. A local-distance switch is fitted on the sound section, and the contrast control is supplemented by a jack so that an armchair control can be used. By this method fading can be counteracted

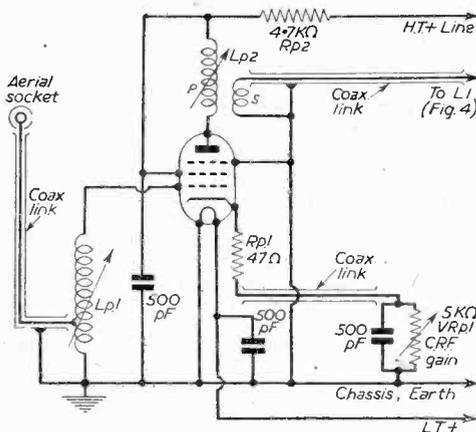


Fig. 3.—The pre-amplifier stage. Coil-winding data will be given next month.

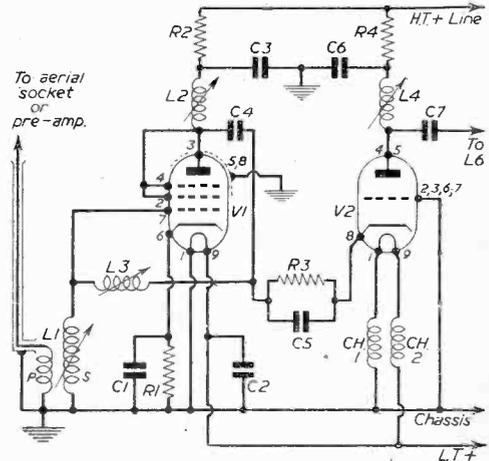


Fig. 4.—The first two R.F. stages.

- | | | |
|------------|------------|------------------|
| R1—150 Ω | C1—500 pF. | C6—500 pF. |
| R2—8.2 Ω | C2—100 pF. | C7—100 pF. |
| R3—100 Ω | C3—500 pF. | |
| R4—2.2 K Ω | C4—100 pF. | V1—EF50 (VR91). |
| | C5—100 pF. | V2—ECS4 (CV66). |
| | | CH1, 2—See text. |

and also enables a greater gain to be obtained on the vision channel on those nights when reception is particularly weak.

Fig. 2 shows a view of the top of the converted chassis.

The Circuit

So that the circuit can be followed easily even by the novice, it has been divided into six sections. They are the pre-amplifier (only required at extreme distances), the R.F. stages, the oscillator, the vision section, the sound section and the power pack.

The Pre-amplifier

This has been freely adapted from that given for the "Argus" in the August issue of PRACTICAL TELEVISION, because of its compactness; it fits into the only space which is available for a pre-amplifier.

It may be found that the pre-amp. is not necessary except in the very remote areas, and the constructor is advised to leave this section until he has tried out the receiver without its aid. If it is then found that extra gain is required the pre-amp. can be constructed and fitted in position.

The circuit is quite straightforward and needs no explanation beyond the arrangement of the cathode circuit. (Fig. 3.) It will be seen that a 5 K Ω variable resistor is used in this position and forms a pre-set gain control; one of the ex-Government pre-set potentiometers can be used in this position. The control is fitted on the front panel. RP1 provides a small degree of negative feedback to assist in counteracting the detuning effect of the gain control.

The valve used is a Mazda 6F12.

Twenty-two s.w.g. wire is used for the coils and for the wiring.

The R.F. Section

The circuit is shown in Fig. 4, and has been freely adapted from the excellent circuit given by A. Thomson in the November issue of PRACTICAL TELEVISION. The reason why this circuit was used is that it has been found very easy to set up and the novice should experience no difficulty with it; also it makes use of one of the CV66's which is already in the unit.

V1 is an EF50 with screened grid, suppressor grid and anode strapped together to form a triode and used in a neutralised triode circuit.

V2 is the CV66 (EC54), a valve especially designed for operation as a grounded-grid triode. As will be seen, the grid (which is actually brought out to four pins at the valve base) is taken directly to earth; the input to the valve is made via the

cathode from the anode of the EF50 and the output is taken directly to the mixer valve.

L3 is the neutralising coil for V1 and will be found quite easy to adjust.

The Oscillator

The circuit is shown in Fig. 5. It employs the existing VR137 though the circuit is different from that used in the original unit. L5 is existing and can be used as it is, for Wenvoe and Sutton Coldfield; for the other channels it is better to wind a new coil.

Tuning is effected by the 0.30 pF condenser C10, which is actually a Pye airspaced concentric type removed from another part of the unit.

C11 forms a vernier control over the frequency of the oscillator to give the facility mentioned in an earlier paragraph. It is an airspaced variable condenser which is removed from the sub-chassis and fitted in this new position.

The output from the oscillator is taken to the grid of the mixer valve via a 2 pF condenser. It is important that this value is adhered to or trouble may be experienced in aligning the receiver.

The Vision Section

This section includes the mixer valve, I.F. stages detector and Video output valve. Fig. 6, shows the circuit.

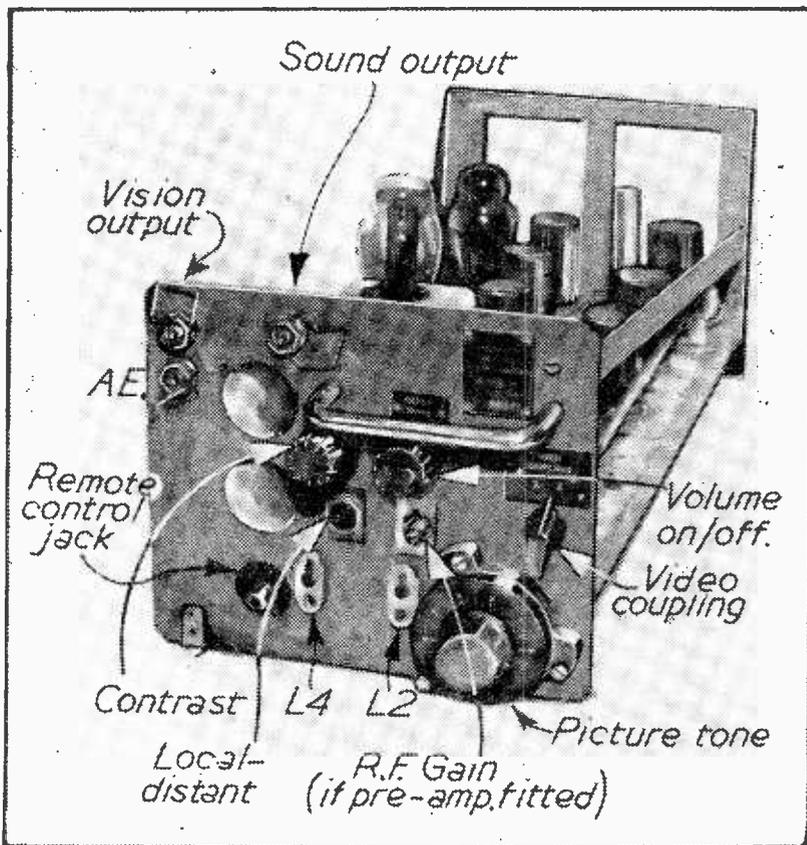


Fig. 2.—View of the front panel with all items identified.

The output from V2 in the R.F. section is fed to the grid of the mixer V4; the output of the oscillator is also fed into the grid. At the anode of the mixer will appear the vision signal at a frequency of 30.75 Mc/s and the sound signal at a frequency of 34.25 Mc/s.

The vision signal is transferred to the first I.F. valve, V5 via the transformer L7, 8. The sound signal is taken from L7 by means of the small coupling coil L7 (a).

Output from V5 is fed via the transformer L9, 10 to V6 and from here to the last I.F. valve V7 via the transformer L11, 12.

From L13, 14 the signal is passed to the detector V8, which is shown connected in the diagram for grid modulation. For cathode modulation the anode and cathode of the EA50 must be reversed.

The video signal is passed to the video output valve V9 which has a correcting choke L17 in its anode circuit. The output shown in the diagram is for grid modulation and can be fed directly into a timebase which caters for this form of circuit; this output could be fed directly into the input of the "Argus" timebase, for example.

It will be noted that the decoupling of the cathode is controlled by the switch S1 which varies the value of capacitance across the bias resistor. The greater the value of this capacitance then the greater will be the gain of the valve though the quality of the picture will be reduced as the correcting effect (due to negative feedback across the cathode resistor) becomes reduced.

The actual setting of the switch is one for personal choice and on nights when the signal strength is good, then the minimum position is suggested as being the best.

No spot limiter circuit is shown in the circuit because use of a small tube such as the VCR97 does not really justify the use of such a device. The usual method of supplying EHT from a mains transformer for this type of tube means that the regulation of the supply is quite good and one does not get the defocusing effect on

interference spots such as is so pronounced with flyback EHT.

Where it is desired to employ cathode modulation, the circuit must be modified slightly. As this is now the

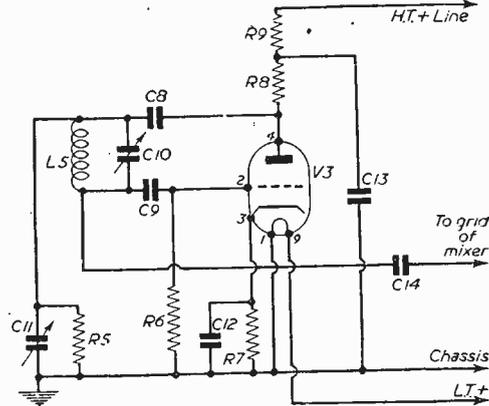


Fig. 5.—The oscillator stage.

- | | | | |
|-------------------|--------------------|-------------|----------|
| R5—100 K Ω | } $\frac{1}{2}$ w. | C8—100 pF | } approx |
| R6—10 K Ω | | C9—8 pF | |
| R7—100 Ω | | C10—0.30 pF | |
| R8—4.7 K Ω | | C11—0.45 pF | |
| R9—47 K Ω | | C12—500 pF | |
| | | C13—500 pF | |
| | | C14—2 pF | |

general method of feeding electromagnetic tubes, the new circuit arrangement (given in Fig. 7) includes a spot limiter. It should be noted that the anode and cathode of the detector valve must be reversed and the bias resistor of V9 must be increased.

(To be continued)

COMPLETE SHOPPING LIST

(This comprises all components which have to be bought)

ONE R3170A UNIT

Four $\frac{1}{2}$ in. coil forms with iron-dust cores.
One International Octal valveholder.

OSCILLATOR SECTION

One 100 Ω , one 150 Ω $\frac{1}{2}$ -watt resistors.
Two 500 pF, one 100 pF, one 2 pF condensers.

V2 CIRCUIT

One 22 K Ω , one 100 Ω $\frac{1}{2}$ -watt resistors.
Three 500 pF condensers.

VISION CIRCUIT

One 0.01 μ F (350 volts wkg. min.).
One 8 μ F Dubilier Drilitic 500 volts.
One jack for remote contrast control if required.
One 5 K Ω potentiometer, ditto.
Additional items if cathode modulation used (see text).
One each of 4.7 K Ω , 150 Ω ($\frac{1}{2}$ -watt) and 5.6 K Ω , 27 K Ω (1 watt).
150 K Ω potentiometer, B.T.H. crystal diode type CG6.

SOUND RECEIVER

Resistors: Three 1 K Ω , two 180 Ω , two 33 K Ω , two 1 M Ω , one 3 M Ω (or one 1 M Ω plus one 2 M Ω , two 470 K Ω (all $\frac{1}{2}$ -watt)). One 500 K Ω with switch; one 4-point tag strip, one 6V6; one EF50.
One B.T.H. crystal diode type CG6.

Condensers: Four 500 pF, one 100 pF, one ~33 (or 35) pF (can be one 25 pF and one 10 pF in parallel), one 300 pF.
250 volt wkg.: 0.1 μ F, 0.01 μ F, 0.05 μ F.
25 volt wkg.: 25 μ F, 50 μ F Dubilier Drilitic.
500 volt wkg.: 8 μ F.

One loudspeaker transformer to suit loudspeaker with pentode output.

POWER SUPPLY

One transformer. Outputs: 6.3 volt 4.5 amp., 5 volt 3 amp, 350-0-350 150 mA, half-shrouded droptrough. (Available Clydesdale Supply Co.)

One smoothing choke type W/B 104 W.E.R.C. 150 mA. (Clydesdale Supply Co.)

One reservoir and smoothing condenser, 16+16 μ F 500 volts (Hunts).


If VU39A used: One $\frac{1}{2}$ Ω 3 watt resistor (see text).

If 5U4G used: One International Octal valveholder; one 5U4G valve.

One resistor 350 Ω , 10 watts minimum.

PRE-AMPLIFIER

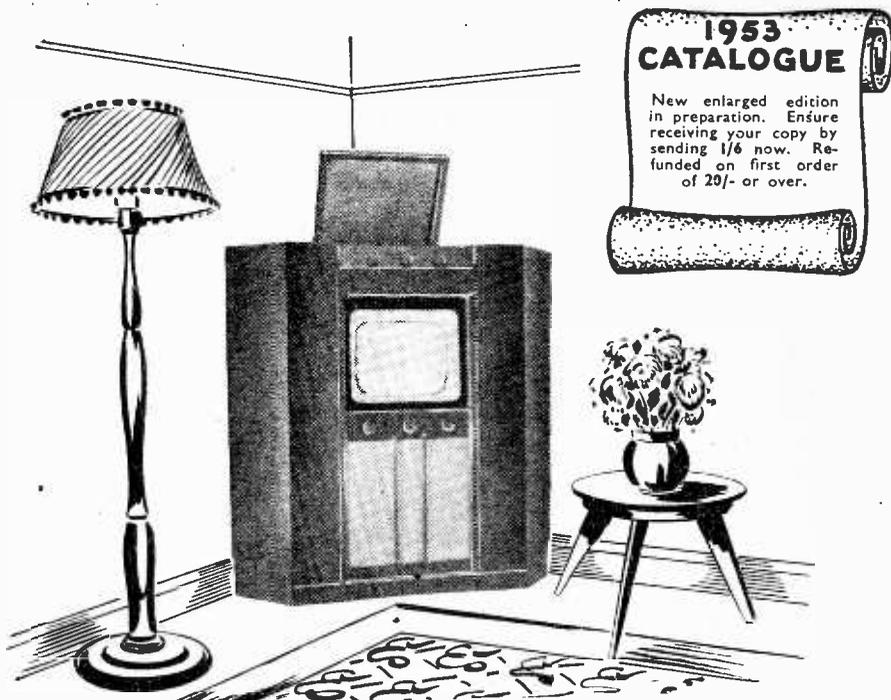One 6F12 valve.
One B8G valveholder.
Two $\frac{1}{2}$ in. diameter coil forms with iron core.
Three 500 pF condensers.
One 4.7 K Ω } $\frac{1}{2}$ -watt resistors.
One 4.7 Ω } $\frac{1}{2}$ -watt resistors.
One 5 K Ω potentiometer.



**1953
CATALOGUE**

New enlarged edition in preparation. Ensure receiving your copy by sending 1/6 now. Refunded on first order of 20/- or over.

THE ELPREQ CORONATION CONSOLE

A combined Radio, Radiogram and 15in. Telesor valued at a shop price of £300-£400 can be yours for about £75 if you adopt our plan. At the time of writing this page, the final details of design have not been completed but are sufficiently advanced to enable us to give approximate prices.

THE T.V. CHASSIS. This incorporates a 15in. Cossor tube and has all the latest features of interference suppression, fly-back E.H.T., etc., etc. Total cost of this, complete with tube, should not exceed £35.

THE RADIO UNIT. A 3-station pre-set superhet with special attention to quality is, we think, the best for the "Console." Such a set is being designed and will not cost more than £8.10.0.

THE RADIOGRAM UNIT. The latest 3-speed Collaro or Garrard autochanger will fit in the top. Cost about £15.

THE CABINET. This handsome corner

fitting piece (47in. wide, 31in. deep to the corner, and 50in. high) has actually been made. We are having it redesigned so that it can be supplied flat for you to screw together. It will be polished, but we feel certain that if you scratch it a little whilst assembling you can get it touched up or repolished by a local man. We have not an actual costing, but are told that it should not be more than £18.

OUR PLAN. As soon as we are ready to send out the parts we will ask you to forward £12.10.0, upon receipt of which we will send you parts for the Telesor

section. From then on you send us 30/- every week and we will send you other sections in the following order: Radio and Audio Chassis, Cabinet, and finally Record Changer unit.

WHAT TO DO FIRST. Constructors' envelopes will be ready early in March, so first send 7/6 for one of these. Upon receipt you can study it, and we feel sure that you will want to make the "Console," but the data will be on 7 days' approval and if you wish you can return it within this period, and providing it is received in clean condition 7/- will be refunded to you.

ELECTRONIC PRECISION EQUIPMENT LTD.

Post Order, please, to our New Warehouse:—
**ELPREQ HOUSE (Dept. 5), HIGH ST.,
WEALDSTONE, MIDDX.**

Personal shoppers must, however, continue to call at:—

**42-46, WINDMILL HILL, RUISLIP,
MIDDX.**

Phone: RUISLIP 5780
(Half-day Wednesday)

152-153, FLEET STREET, E.C.4

Phone: CENTRAL 2833
(Half-day Saturday)



BUILDING THE "ARGUS" ?

Thousands of enthusiasts are building the Practical Television "Argus" Telescor. Why not YOU? Full constructional details with Blue Print sent for only 2.9 post paid. All components available ex stock, as follows:


<p>MAINS TRANSFORMER 425-0-425v. 200ma., 6.3v. 1a., 6.3v. 4a., 5v. 3a. (Postage 1/6) 50/-</p> <p>E.H.T. TRANSFORMER FOR VCR97 TUBE 2.500v. 5ma., 2-0-2v. 1.1a., 2-0-2v. 2a. (post 1/6) 87 S</p> <p>CHOKES 5h. 200ma. (postage 1/-) 6-</p> <p>VALVES EF50 (VR91) 6/6 5U4G 10/6 6V6 10/6 EB34 (VR54) 3/8 EF26 (VR56) 7/6 SP81 (VR65) 4/6 EA50 (VR92) 3/5</p> <p>POTENTIOMETERS Less switch 3/- With switch 4/6</p> <p>VALVE HOLDERS I.O. or M.O. 6d. B9G 10d. Diode 6d.</p> <p>RESISTORS 1w. 4d. 1w. 5d. 1w. 6d. 2w. 9d. 15w. 2.5k. 2/-</p> <p>CONDENSERS Mica and Silver Mica Tubulars— .1mf. 9d. .01mf. 9d. .05mf. 9d. .05mf. 9d. .5mf. 2/- .03mf. 2.5kv. 2/6 .1mf. 2.5kv. 4/6</p>	<p>ELECTROLYTICS 8mf. 450v. 3/6 8 x 8mf. 450v. 4/9 16 x 16mf. 450v. 7/- 25mf. 25v. 1/6 50mf. 12v. 1/6 TRANSFORMERS 0-300p. 7d.</p> <p>COIL FORMERS WITH SLUGS 1in. 8d. 1in. 10d.</p> <p>P.M. SPEAKERS (less trans.) 5in. Rola 16/6 8in. Plessey 17/6 (Postage 1/6 per speaker)</p> <p>TV FAULT FINDING—An 80-page publication giving reasons for various TV troubles, and how to cure them. Profusely illustrated with photographs taken from a Television Screen. Post paid ONLY 5/3</p> <p>INEXPENSIVE TELEVISION—The 48-page book which gives details of TV construction from various ex-TV. Radar Units. Post pd. ONLY 2/9</p> <p>TRANSFORMERS Manufactured to our specifications and fully guaranteed. Normal Primaries. 425v.-0-425v. 200ma., 6.3v. 6a., 6.3v. 6a., 5v. 3a., 0-2-4-6-3v. 3a. ONLY 72/6 350v.-0-350v. 160ma., 6.3v. 5a., 6.3v. 3a., 5v. 3a. ONLY 43/6 250v.-0-250v. 100ma., 6.3v. 6a., 5v. 3a. ONLY 32/6</p> <p>All above are fully shrouded, upright mounting. Universal Mounting : 350v.-0-350v. 80ma., 0-1-6.3v. 4 a., and 0-4-5v. 2a. ONLY 18/6 5.5kV. E.H.T. with 2 windings of 2v. 1a. ONLY 72/6 7kV. E.H.T. with 4v. 1a. ONLY 82/6</p> <p>PLEASE ADD 1/6 POSTAGE FOR EACH TRANSFORMER.</p>	<p>PENODE OUTPUT TRANSFORMER 5/-</p> <p>RDF1 RECEIVER The unit reviewed in the October and November issues of this journal for conversion into a Telescor giving SOUND AND VISION ON THE ONE CHANNELS. Complete with 14 valves as follows: 6 of SP81, 2 of P81, 3 of EA50, and 1 each CV63, EB34, EC52, 5Z4G, also a complete reprint of the above review (carriage, etc., 5/-) ONLY 49/6</p> <p>MAGNIFYING LENS FOR VCR97 TUBE First grade oil-filled (postage, 2/-) ONLY 25/-</p> <p>RECEIVER R.3118 A further supply of the very popular unit we sold out of a few months ago. Ideal for conversion to TV, having a built-in A.C. Mains Power Pack for 180-240 volts. Is tremendously powerful, employing 7 I.F. stages of 12 mc's with 4 mc's bandwidth, and has 15 valves: 6 of VR85, 4 of VR92, 2 of VR136, and 1 each VR137, P81, 5Z4, and Y63 "Magic Eye." In excellent condition (carriage etc., 7/6) ONLY 97/6</p> <p>RF UNITS 26 & 27 As recommended in last month's issue for Long Distance TV Reception in conjunction with the R1355. Are variably tuned and employ 2 valves EF54 and 1 EC52. Type 26 covers 65-50 mc's (3-6 metres), and Type 27 covers 85-65 mc's (3.5-5 metres). BRAND NEW IN MAKERS' CARTONS, each ONLY 59/6 (postage, etc., 2/-)</p>
---	--	--

Cash with order, please, and print name and address clearly.

U.E.I. CORPN., THE RADIO CORNER, 138, Gray's Inn Road, London, W.C.1 (Phone TERminus 7937)
Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station), 5 mins. by bus from King's Cross.

CLYDESDALE

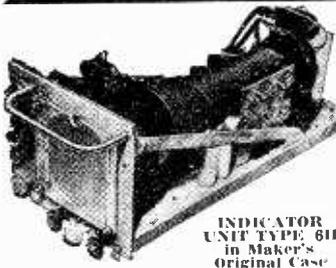Bargains in Ex-Services Radio and Electronic Equipment



INDICATOR UNIT TYPE 611
in Maker's Original Case

Containing a VCR97 Cathode-ray Tube, with mu-metal screen, 4 VR91s (EF50), 3 VR54s (EB34), various w.w. pots, switches, H.V. Conds., Resistors, etc., built in metal chassis to fit into metal box 19 x 8 1/2 x 7 1/2 in. All controls are brought to front panel beside viewing screen.
ASK FOR **£4/9/6** CARRIAGE PAID
No. D'E777

INDICATOR UNIT TYPE 6A

in Transit Case
ASK FOR **£4/9/6** CARRIAGE PAID
No. D H887

BOOKS ON TELEVISION

- Television Explained (Niffe).....5/3
- The Television Receiver Practice.....5/3
- Inexpensive Television (No. 4) (S.W. Press) 2/6
- T.V. Fault Finding (No. 5) (S.W. Press) 5/3
- "Argus" T.V. Receiver Blueprint (PT) 2/6

R3170A Receiver Unit.
ASK FOR **£4/12/6** CARRIAGE PAID
No. D/H402

R3801 Receiver Unit.
ASK FOR **£4/12/6** CARRIAGE PAID
No. D.H493


5 CPI CATHODE RAY TUBE
ASK FOR **35/-** POST PAID
No. D H529

INDICATOR UNIT TYPE 62
in Maker's original case
ASK FOR **£5/9/6** CARRIAGE PAID
No. D H526

Also available, used, good condition
ASK FOR **7/9/6** CARRIAGE PAID
No. D E774

INDICATOR UNIT TYPE 62A
Used, Good Condition.
ASK FOR **£7/19/6** CARRIAGE PAID
No. D H883

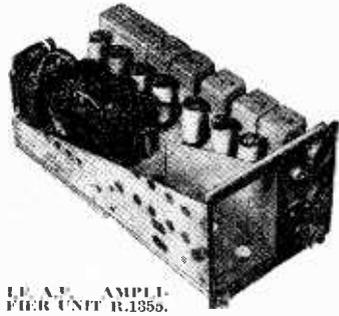DATA FOR USING EX-SERVICE UNITS
REPRINTS FROM "PRACTICAL TELEVISION"—Article by B. L. Morley using Indicator Type 62 1/6 (Components Price List free on request.)



AMPLIFIER UNIT R.3155.

The popular T.V. Sound and/or Vision Unit, 5 I.F. stages, 10 valves 8 VR85 (SP81), 5U4G, VU120A, etc., etc. in metal case 19in. x 8 1/2 in. x 7 1/2 in. Used, good condition. IN ORIGINAL CASE '47/6 CARRIAGE PAID
ASK FOR No. D E770
2nd Grade, in Transit Case, 42/6 Carr. Paid.
3rd Grade, loose stored, 35/- Carr. Paid.

TRANSFORMERS

E.H.T. 55"-, 57 6, 59 6, or 65"- each.
Mains (Morley), 55"-, (Argus), 69/6 each.

NEW 192-PAGE CATALOGUE

Now in the press.
Price 1/6 (credited on first purchase of 10/- or over).

Order direct from :

CLYDESDALE SUPPLY CO., LTD.

2 Bridge Street, Glasgow, C.5. 'Phone : SOUTH 2706/9
Visit our Branches in Scotland, England and N. Ireland



Pages from a TELEVISION ENGINEERS Notebook

3.—DOUBLE-TRIODE MIXERS

IN home-constructed television receivers it is most usual for a mixer stage to consist of a pentode with a separate triode (or strapped pentode) oscillator. Such a system is much preferable to a single valve arrangement employing a triode-hexode of the 6K8 class, but circuits using double-triode valves are not often encountered.

A triode frequency-changer is better than a pentode because it has a lower noise figure, and, in many cases, a higher conversion gain is obtained. A typical circuit of a mixer-oscillator of this type is shown in Fig. 1, and a valve of the 12AT7 class is considered to be employed. The left-hand triode forms the actual mixer, and this section is biased by resistance R_1 , by-passed to earth with C_1 . The input signal appears across the tuned circuit L_1 , either directly from the aerial or, more commonly, from the anode circuit of an R.F. amplifier stage. The anode load of the mixer consists of a damped tuned circuit L_2 and this is resonant at the intermediate frequency; this winding may well be the primary of a coupled-circuit transformer, the secondary of which would be tuned and damped to provide the requisite pass-band.

The right-hand triode of the circuit is the oscillator, and is shown as a Hartley, although variations are many in the actual possible designs. The frequency of the tuned circuit L_3C_4 is adjusted so that it is tuned above (or below) the input signal frequency by the I.F. It is usual to tune below the signal frequency to assist in obtaining more stable operation.

Oscillator Voltage

The oscillator voltage is coupled to the grid of the mixer by condenser C_2 , but in a valve having a common cathode (such as the 6J6) coupling can take place across the cathode load. Mixing results because of the non-linear characteristic of the grid-voltage/anode-current relationship, which is brought about by the biasing voltage across R_1 . This is arranged to bias the valve back close to cut-off.

The efficiency of such a mixer depends upon the amplitude of the oscillator voltage at the mixer grid, the I.F. output increasing as the oscillatory voltage increases. Suitable design values for the various components will now be calculated, together with an outline of the method for setting the oscillator amplitude.

Design Values

Consider Fig. 2. This is the I_a/V_g characteristic for the mixer section of the valve for a particular value of anode current. Let the cut-off bias voltage be $-V_c$

and let the anode current at zero grid voltage be I_0 . If now the valve is normally biased just to cut-off and the oscillator voltage is adjusted so that the peak input just causes an anode current of I_0 to flow, then the average current over a half-period is—

$$\begin{aligned} I_{ave} &= \frac{1}{2\pi} \int_0^\pi I_0 \sin \theta \cdot d\theta \\ &= \frac{1}{2\pi} [I_0 (-\cos \theta)]_0^\pi \\ &= \frac{I_0}{\pi} \end{aligned}$$

The value of the cathode resistance R_1 should therefore be.

$$R_1 = \frac{V_c}{I_{ave}} = \pi \frac{V_c}{I_0}$$

If the valve used is a 12AT7, therefore, working with

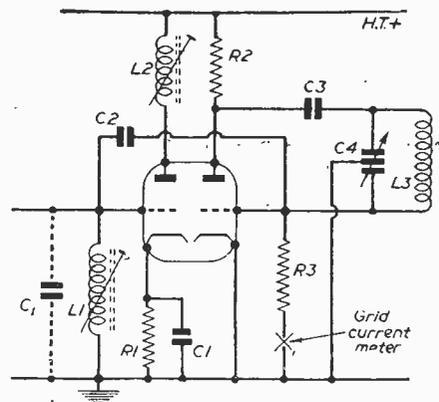


Fig. 1.—The basic double-triode mixer circuit from which design values are calculated.

an anode supply of 200 volts, the maker's figures give an anode current of 22 mA with zero bias. The grid cut-off voltage is about -6 volts. From the above equation, then,

$$R_1 = \pi \frac{6 \times 1,000}{22} = 860 \text{ ohms,}$$

say 820 ohms to take a preferred value.

Further, the anode current (D.C.) is

$$I_a = \frac{I_0}{\pi} = \frac{22 \times 10^{-3}}{\pi} = 7 \text{ mA}$$

and the R.M.S. value of the oscillator voltage is—

$$V_{osc} = 0.707 V_c = 4.25 \text{ volts.}$$

Conversion Gain

The conversion gain of a triode operating essentially close to cut-off is given by the equation :

$$V_{it} = \frac{\mu R V_s}{\pi (R + R_a)}$$

where V_{it} is the I.F. voltage developed, R is the anode load impedance, V_s is the signal voltage, and R_a and μ have their usual meanings.

The 12AT7 operating under the previous conditions has a R_a of 9,800 ohms, and a μ of 55. If the anode load impedance is 2,500 ohms, therefore, the conversion gain will be

$$\frac{V_{it}}{V_s} = \frac{55 \times 2,500}{\pi (2,500 + 9,800)} = 3.5$$

which, is a typical figure.

The value of C_2 , the coupling condenser from the

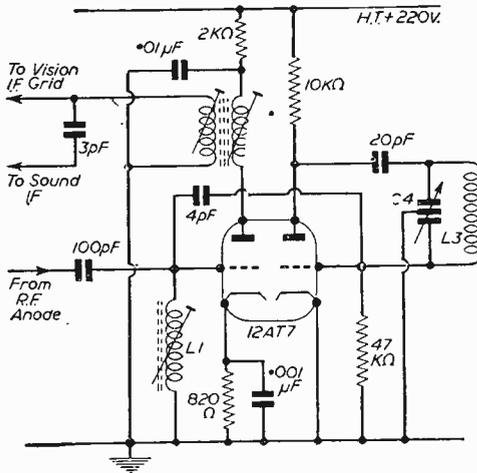


Fig. 3.—A practical mixer circuit.

oscillator to the mixer grids, has not been mentioned. This depends upon the amplitude of the oscillator voltage, the amplitude required at the mixer grid, and the effective input capacity C_1 of the mixer. The value is given by the equation

$$C_2 = \frac{C_1}{\left\{ \frac{V_x}{V_{osc}} \right\} - 1} \text{ (approx.)}$$

where V_{osc} is the voltage across C_2 and V_x is the

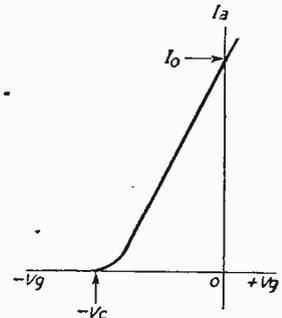


Fig. 2.—This is the operating characteristic of the triode mixer section.

oscillator amplitude. Thus, if $C_1 = 10\text{pF}$, $V_x = 15$ volts, and $V_{osc} = 4.25$ volts as obtained above,

$$C_2 = \frac{10 \times 10^{-12}}{3.5 - 1} = \frac{10^{-11}}{2.5} = 4 \text{ pF}$$

The oscillator amplitude V_x can be readily determined by measuring the change in grid current through the grid resistance R_3 that occurs when the valve passes from a non-oscillating condition to an oscillating condition. In general, the grid current is so small when the valve is not oscillating that it can be ignored, and a measure of the normal oscillating current is sufficient. The grid current in microamperes multiplied by the value of R_3 in megohms gives a figure which is roughly 80 per cent. of the oscillator amplitude. Thus, with a value for R_3 of 47 kΩ (0.047 MΩ), the current must be about 250 μ amps to give the above required amplitude of 15 volts. The amplitude actually obtained depends largely upon the coil L_3 and especially upon its diameter, as well as upon the value of C_3 . This condenser should not be too large, however, and a maximum of 20 pF is a useful design figure. The coil should be wound with 20—22 gauge enamelled wire on a half-inch former and tuned to cover the required frequency band. Adjustment of C_3 will then set the grid current to the approximate value required.

A complete circuit with component values is given in Fig. 3, together with a method of coupling off the sound. An alternative circuit using a 6J6 (ECC91) was described by the author in the July issue of PRACTICAL TELEVISION for 1951.

New Ground Radar Trainer

THE production design of an entirely new type of ground radar trainer designed by the Ministry of Civil Aviation is now being developed by Marconi's Wireless Telegraph Co., Ltd., and manufacture will shortly begin. First models will be ready for delivery to Commonwealth and other overseas countries by the end of 1953.

Stations within range of a busy air route can use as targets civil or military aircraft flying on normal duties. In quieter areas special aircraft have to be flown—when weather permits—often for hours at a time. This new trainer by eliminating the need for special target aircraft is economical in men, machines and expense.

The trainer, by electro-mechanical methods, simulates

the echoes received from genuine target aircraft, i.e., it provides synthetic responses on a radar screen—plan position (PPI) display—identical with those reflected from aircraft within range. It is therefore possible to "fly" two "aircraft" targets independently at once.

As this trainer is capable of being integrated into any existing radar system, it is possible for service training purposes to treat real 'planes as "tactical targets."

Though each trainer is supplied with one unit of two echoes, it is also designed so that there may be as many as 12 units, i.e., 24 "aircraft."


The aircraft may be set by the instructor to fly in any direction with speeds from 150 to 600 knots. The maximum range is 200 nautical miles, the minimum 2 nautical miles at airspeeds of 150-200 knots, and 5 nautical miles at 210-600 knots.

IT PAYS TO SOLDER WITH Wolf

★ WIDEST RANGE TO SUIT EVERY NEED
★ SOLDER TWICE AS FAST AT FAR LESS COST

SOLDERGUNS

TYPE 21

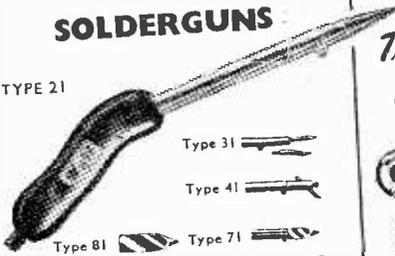

Type 31

Type 41

OFF-STRAIGHT EASY-GRIP HANDLE
PERFECT CONTROL • QUICKER HEAT-UP
• LOCALISED HEAT • LOW CURRENT CONSUMPTION • MAINTAINS CORRECT HEAT • MODELS FOR EVERY PURPOSE

Trigger-Feed Soldergun




TYPE 51

The Wolf Type 51 Soldergun with its trigger-feed action is indispensable to all modern assembly.

SOLDERING IRONS

TYPE 22

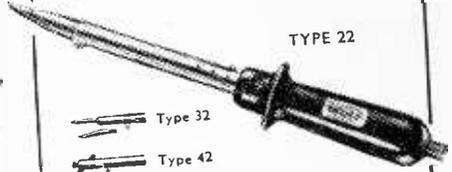

Type 32

Type 42

For all who, for special reasons, prefer the conventional straight-type handle. Identical as regards elements and bits to Wolf Solder-guns, but with round hard wooden handle with heat-deflecting skirt.

★ OBTAINABLE FROM ALL HIGH-CLASS STOCKISTS AND IRONMONGERS

WOLF ELECTRIC TOOLS LTD., PIONEER WORKS, HANGER LANE, LONDON, W.5. TEL. PERIVALE 5631-4

RADIO SUPPLY CO. 15, WELLINGTON ST., LEEDS, 1.

Post Terms C.W.O. or C.O.D. No. C.O.D. under £1. Postage 1/- charged on orders up to £1; from £1 to £3 add 1/6; over £3 post free. Open to orders 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list, 5d.; Trade List, 5d.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v 50 c/s Screened. *

TOP SHROUDED, DROP THROUGH

230-0-230 v 70 ma. 6.3 v 2 a, 5 v 2 a	14.11
260-0-260 v 80 ma. 8.3 v 2 a, 5 v 2 a	15.9
350-0-350 v 80 ma. 6.3 v 2 a, 5 v 2 a	17.6
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a	23.11
350-0-350 v 100 ma. 6.3 v 4 v 4 a C.T.	23.11
0-4.5 v 3 a	23.11
350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a	29.11
350-0-350 v 150 ma. 6.3 v 2 a, 6.3 v 2 a, 5 v 3 a	29.11

CLAMPED UPRIGHT MOUNTING

300-0-300 v 100 ma. 6.3 v 3 a, 5 v 3 a	21.9
350-0-350 v 100 ma. 6.3 v 3 a, 5 v 3 a	23.9

FULLY SHROUDED UPRIGHT

250-0-250 v 60 ma. 6.3 v 2 a, 5 v 2 a	17.6
Midjet type, 21-3-3in.	25.9
250-0-250 v 100 ma. 0-4-5.3 v 4 a, 0-4-5 v 3 a	25.9
250-0-250 v 100 ma. 6.3 v 6 a, 5 v 3 a, for R1355 Conversion	28.9
300-0-300 v 100 ma. 6.3 v 4 v 4 a, C.T.	25.9
350-0-350 v 70 ma. 6.3 v 2 a, 5 v 2 a	18.9
350-0-350 v 100 ma. 6.3 v 4 v 4 a, C.T.	25.9
0-4.5 v 3 a	25.9
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a	33.9
350-0-350 v 160 ma. 6.3 v 6 a, 6.3 v 3 a, 5 v 3 a	45.9
350-0-350 v 250 ma. 6.3 v 6 a, 4 v 8 a, 0-2-6 v 2 a, 4 v 3 a, for Electronic Engineering Television	67.6
425-0-425 v 200 ma. 6.3 v 4 a, C.T. 6.3 v 4 a, C.T., 5 v 3 a, suitable Argus Television, etc.	51-

FILAMENT TRANSFORMERS

All with 200-250 v 50 c/s Primaries; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/9; 0-2-4-5-6-3 v 4 a, 17/9; 12 v 3 a, or 24 v 1.5 a, 17/9

CHARGER TRANSFORMERS

All with 200-250-250 v 50 c/s Primaries:

0-9-15 v 1.5 a, 13/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 6 a, 22/9; 0-4-5-10-24 v 3 a

SMOOTHING CHOKES

250 ma 8-10 h 50 ohms	16.9
200 ma 5 h 50 ohms Potted	9/6
150 ma 10 h 220 ohms Potted	10/9
100 ma 10 h 200 ohms	7/6
90 ma 8 h 100 ohms	5/9
80 ma 10 h 350 ohms	5/6
50 ma 50 h 1,250 ohms Potted	8.11

OUTPUT TRANSFORMERS

Standard Pentode, 5,000 to 3 ohms	4.9
Standard Pentode, 8,000 to 3 ohms	4.9
Push-Pull 10-12 watts 6V6 to 3 or 15 ohms	16.9
Push-Pull 10-12 watts to match, 6V6	16.9
etc., to 3-5-8 or 13 ohms	16.9
Push-Pull 15 watts to match 6L6, etc., to 3 or 15 ohms Speaker	22.9

BATTERY SET CONVERTER KIT. All parts for converting any type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplies 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 v or at 1 a. Price, including circuit, 47s.

BATTERY CHARGER KITS.—For mains input, 200-250 v 50 c/s. To charge 6 v Acc. at 1 amp, 19/11; to charge 6 v or 12 v Acc. at 2 amps, 29/6; to charge 6 v or 12 v Acc. at 4 amps, 45/- Above consist of transformer, F.W. Rectifier, Fuse, Fuscholder, Steel Case, and Circuit.

SPECIAL OFFERS.—Mains Trans., Midjet Type, 21-3-2in. Primary 220/240 v. Secs. 250-0-250 v 60 ma. 6.3 v 2.5 a, 10/9; Small fil. trans. 220-240 v input, 6.3 v 1.5 a output, 5/9; Auto Trans. 50 watts, 0-110-200-210-230-250 v with sep. 6.3 v 1.5 a, 4/9.

P.M. SPEAKERS.—All 2-3 ohms 5in. ELAC, 13/9; 5in. Goodmans, 14/9; 6in. ELAC, 15/9; 8in. Plessey, 15/9; 10in. Plessey, 18.11; 10in. Rola, 3L/-

M.E. SPEAKERS (2-3 ohms). 6in. Rola, 700 ohm Field, 12/9; 8in. R.A., 600 ohm ohm Field, 12/9; 10in. R.A., 800 ohm Field, 23/9.

EX-GOVT. CONDENSERS.—Block Paper (Mansbridge type), 4 mfd 500 v, 1/11; 8 mfd 500 v, 4/9; Bak. Tubular, .02 mfd 5,000 v, 2/9; .05 mfd 3,500 v, 3/6.

NEW VALVES (EX-GOVT.)

IT4	Each	6V6G	Each	EF39	9/6
IS5	8.11	6X5GT	9/9	EF80	12.9
IR5	9/6	7D8	6/9	EF91	11.9
384	8.11	807	10/11	EB91	10/6
5Y3G (U50)	8/6	9D2	2/11	KT44	5/3
5U4G	10/6	8K4	1/11	KT66	11/6
5Z4G	9/6	12K8GT	11/9	MP21	6/9
6J5G	5/9	12Q7GT	10/6	MS/PEN	5.9
6J7G	7/6	12SC7	5/11	SP41	3/9
6K7G	6.11	15D2	6/6	SP61	4/6
6R8G	12.9	1825	5/6	UCH42	10.11
6Q7G	9.11	25A6G	10.9	UF42	10.11
6SN7GT	11/9	35L8GT	9.9	UL41	10/6
6SL7GT	11/9	35Z4GT	10.6	UX1	10/6
6SK7	6.11	D1	1/3	VU120A	2/11
6SV7	6/9	EA50	2.9		

SILVER MICA CONDENSERS.—5, 10, 15, 20, 25, 30, 35, 50, 60, 100, 120, 150, 180, 200, 220, 300, 340, 400, 470, 500, 1,000 (0.01 mfd), 2,000 (0.02 mfd), 5d. each, 3/9 doz. 1 type.

VOL. CONTROLS (standard long spindles). All values, less switch, 2/9; with S.P. switch, 3/11; with D.P. switch, 4/6.

ELECTROLYTICS.—Tubular 8 mfd 450 v, 1/11; 16 mfd 450 v, 2/11; Can 8-8 mfd 450 v, 3/11; 8-16 mfd 450 v, 4/6; 16-16 mfd 450 v, 4.11; 32 mfd 350 v, 2.11; 32 mfd 450 v, 4/11; 32-32 mfd 350 v, 5/6; 32-32 mfd 450 v, 5/11; 16-32 mfd 350 v, 4/6; 16-32 mfd 450 v, 4.11.



OPEN TILL 6 P.M. SATURDAYS

TELEPHONES: AMBASSADOR 4033 & PADDINGTON 3271/2

PREMIER RADIO Company

(REGD.) B. H. MORRIS & CO (RADIO) LTD. EST. 40 YRS.

THIS IS OUR ONLY ADDRESS (Dept. PT) 207 · EDGWARE ROAD · LONDON · W2 (THIS IS OUR ONLY ADDRESS)

PREMIER MAINS TRANSFORMERS

All primaries are tapped for 200-220-250 v. mains 40-100 cycles. All primaries are screened. All LTs are centre tapped.

SP175B, 175-0-175, 50 mA., 4 v. @ 1 a. 4 v. @ 2-3 a.	25
SP250B, 250-0-250, 60 mA., 4 v. @ 1-2 a. 4 v. @ 3-5 a.	25
SP300A, 300-0-300, 60 mA., 6.3 v. @ 2-3 a. 5 v. @ 2 a.	25
SP300B, 300-0-300, 60 mA., 4 v. @ 2-3 a. 4 v. @ 3-5 a. 4 v. @ 1-2 a.	25
SP301A, 300-0-300, 120 mA., 5 v. @ 2-3 a. 6.3 v. @ 3-4 a.	28
SP301B, 300-0-300, 120 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a.	28
SP350A, 250-0-350, 100 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a.	29
SP350B, 350-0-350, 100 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a.	29
SP351, 350-0-350, 150 mA., 4 v. @ 1-2 a. 4 v. @ 2-3 a. 4 v. @ 3-6 a.	38
SP375A, 375-0-375, 250 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-3 a.	39/8
SP375B, 375-0-375, 250 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-6 a.	39/8
SP501, 500-0-500, 150 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 2-2 a. 4 v. @ 3-5 a.	47
SP501A, 500-0-500, 150 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a. 6.3 v. @ 2-2 a.	50
SP425A, 425-0-425, 200 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-5 a.	67/8

RECTIFIERS

E.H.T. Pencil Type S.T.C.	
Type K3/25 650 v. 1 mA.	4/7
.. K3/40 3.2 Kv. 1 mA.	6/-
.. K3/45 3.6 Kv. 1 mA.	8/2
.. K3/50 4 Kv. 1 mA.	8/8
.. K3/100 8 Kv. 1 mA.	14/8
.. K3/160 12 Kv. 1 mA.	21/6
H.T. Type S.T.C.	
Type RM1 125 v. 60 mA.	4/6
.. RM2 125 v. 100 mA.	5/-
.. RM3 125 v. 125 mA.	6/-
.. RM4 250 v. 250 mA.	18/-
L.T. Type G.E.C. Full Wave	
12v. 1 amp.	4/-
12v. 1 amp.	8/-

MOVING COIL METER

A super quality Moving Coil Meter basic movement 2 mA. Scale dimension, 2 1/2 in. Overall dimensions, 2 1/2 in. diam., 1 1/2 in. deep. Bakelite Case projecting type. At present scaled 1 amp. R.F. By removing thermo couple, reversing scale and recalibrating the meter, a high grade test instrument with any range above the basic F.S.D. may be built up. Price 4/0.

AVAILABLE ONCE AGAIN!

A.C.R. I.C.R. TUBES

(DIRECT REPLACEMENT FOR A CR 2X) 5 1/2 in. screen, 4 volt Heater. This Electrostatic Tube is recommended as eminently suitable for Television, 15" plus 2/6 Pkg., Carr. and Ins., Data sheet supplied.

V.C.R. 97 C.R. TUBES

We are once again able to offer this famous tube with the usual PREMIER guarantee of a full screen picture free from cut-off. Every tube is television picture tested before despatch. £2/5/-, post paid.

WHITE RUBBER MASK

for 6in. tube. 8/8

SORBO RUBBER MASKS

Grey Felt finish (new aspect ratio). 9in., 5" ; 12in. 9/6

CORRECT ASPECT WHITE RUBBER MASK

For 12in. Round or Flat-faced Tube 16/11

WEYMOUTH MINIATURE I.F. TRANSFORMERS

485 Kc/s. Iron cored, permeability tuned, 10/6 pair.

WEYMOUTH MINIATURE COIL PACK

Covering Med. Long Short-wave bands. Iron-cored coils. Dimens.: Hght. 1 1/2 in. Length 3 1/2 in. Width 2 1/2 in. Spindle length, 2 in. Price 18/6.

MINIATURE TUNING CONDENSERS

2-gang. .0005 mfd., 6/9.

EX-U.S.A. U.H.F. AERIAL with untuned detector stage consisting of VR92 valve, etc. Brand new in carton, 5/-.

TERMS OF BUSINESS:—CASH WITH ORDER OR C.O.D. OVER £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

Let **ICS** perfect YOUR knowledge of radio and T/V

THOSE who wish to supplement their existing knowledge with a sound technological background or pass qualifying examinations, can do so by means of I.C.S. Home Study Courses. These include T/V TECHNOLOGY · RADIO SERVICE ENGINEERING · RADIO ENGINEERING · ELEMENTARY ELECTRONICS · RADAR · ADVANCED SHORT WAVE RADIO and training for the following

examinations: C. & G. RADIO SERVICING CERT. (R.T.E.B.) · B.I.R.E. · C. & G. TELECOMMUNICATIONS · C. & G. RADIO AMATEURS · P.M.G. CERT. FOR WIRELESS OPERATORS, etc., etc. Students are coached until successful. Fees are moderate and include all books required. **GENEROUS DISCOUNT TO H.M. FORCES.**

Dept. 172C, I.C.S., 71 Kingsway, W.C.2

CUT HERE

WRITE TODAY for FREE BOOKLET describing complete facilities for the successful study of T/V technology and Radio.

INTERNATIONAL CORRESPONDENCE SCHOOLS LTD. Dept. 172C, International Buildings, Kingsway, London, W.C.2

Please send Booklet on subject.....
 Name..... Age.....
 (Block letters please)
 Address

Making Sound I.F. Transformers

CONSTRUCTIONAL DETAILS AND A SUITABLE CIRCUIT IN WHICH THEY MAY BE USED

By Gordon A. Symonds

FOR those constructors who find enjoyment in making components which lend themselves to home-construction, this article deals with the making of I.F. transformers for the sound section of a superhet television receiver. They are extremely simple and require the minimum of skill to make, but are, nevertheless, a very efficient means of intervalve coupling.


There is, of course, nothing new in their design, being merely an H.F. version of the type of I.F. transformer found in most broadcast receivers.

Fig. 1 indicates a suitable circuit for use with these transformers and from it will be seen that they consist of a pair of inductively-coupled coils each shunted by a fixed capacitor and tuned by a dust-iron core. In all, five coils are employed, including the sound input coil, and as can be expected a very high degree of selectivity is obtained, thus preventing any possibility of vision breakthrough. In point of fact, a degree of selectivity much higher than is necessary for this purpose is possible and much more than desirable from other aspects, namely those of local oscillator drift and interference suppression.

Local oscillator drift (which should not be excessive) has the effect of shifting the intermediate frequency by an amount equal to the drift of the oscillator. If, therefore, the drift is greater than the I.F. passband, the sound will be completely lost. A bandwidth of about 200 kc/s is usually sufficient and is obtained by slightly over-coupling the coils. This bandwidth also allows the peakiness of ignition interference to be retained, thus enabling the noise limiter to operate more effectively.

Turning again to Fig. 1, it will be seen that two I.F. amplifiers are employed plus detector, noise limiter and A.V.C. diode. Sufficient output is obtainable from the detector to drive a sensitive output valve such as the KT61, but as constructors will doubtless have their own ideas about the A.F. section, this has been omitted.

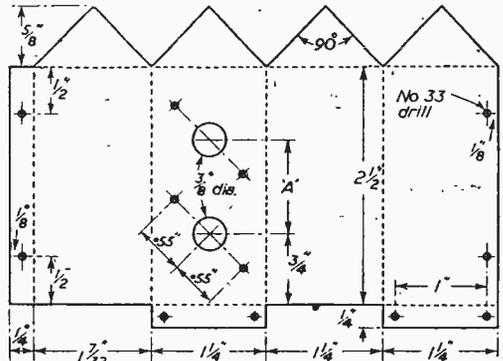The component values given are suitable for such valves as EF50, EF54, SP61, EF91, and equivalents for the pentodes, and EB91, EB34 and equivalents for the detector and noise limiter. The A.V.C. diode can be an



Note: Dimension 'A' is 1" for 1st I.F.T. and 1 5/8" for 2nd I.F.T. Omit bottom coil fixing holes in L1 coil can

Fig. 2.—How to drill and cut the aluminium before bending.

EA50 or a suitable germanium crystal diode. Other pentodes could be used if attention is paid to bias resistors, and screen droppers included if necessary.

Construction

In the interests of stability the coils are placed inside screening cans. The grid coil being mounted at the top so that in the event of a valve with a top cap grid being


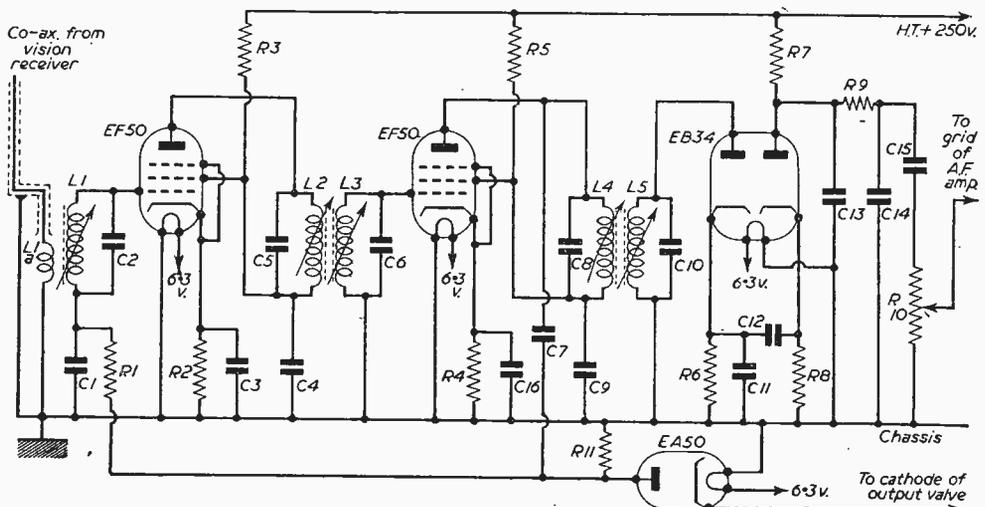
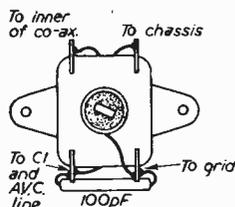


Fig. 1.—Suggested circuit for use with the I.F. transformers.

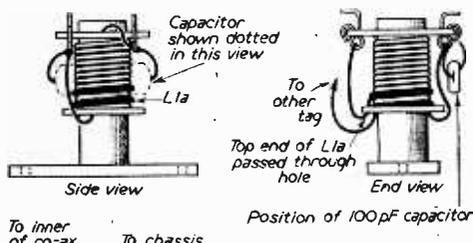used, the grid lead can be conveniently brought out at the top of the can. The transformer cans are made from 22 s.w.g. aluminium cut to the dimensions given in Fig. 2. All holes should be drilled before bending. If a piece of hardwood $1\frac{1}{4}$ in. square is at hand, the cans can be bent around this, greatly facilitating the work. The



*L1 is 13 turns closewound
26 SW.G. enam. wire
L1a is 2 turns interwound
at earthy end*

top of the can is closed by bending over the four triangular shaped pieces and two fixing flanges are bent out at the bottom.

Aladdin formers, type F804 (approximately $\frac{3}{8}$ in. diameter) are used on which to wind the coils. Five of these are needed, one wound as in Fig. 3a and four as in Fig. 3b. The number of turns given is for a frequency of 10 Mc/s, other frequencies being accommodated by suitably altering the number of turns. The simple formula

$$\frac{13 \times 10}{F}$$

(13 and 10 being the number of turns and frequency in Mc/s respectively of the coils described, and F the required frequency) will be found to be sufficiently accurate over the usual range of intermediate frequencies employed in TV sound receivers. The 100 pF capacitors must be used in all cases; 26 s.w.g. enamelled wire is used for all coils, the turns being retained in position by washers made from $\frac{1}{16}$ in. thick paxolin sheet to the details given in Fig. 4. These must be a tight fit on the formers. Soldering anchors on which are mounted the 100 pF capacitors and to which the lead-out wires are connected are provided on the upper washer by passing $\frac{1}{16}$ in. by $\frac{1}{2}$ in. split-pins through holes provided and retained by bending one leg over.

The sound input coil which, incidentally, also serves as a sound rejector coil for the vision I.F. amplifier, is fed with signal from the frequency changer anode coil. A two-turn loop on this coil picks out the signal, which is then carried by a length of co-axial cable to the two-turn loop on the input coil.

Alignment

Although it is easily carried out, the alignment is not quite so straightforward as with critically coupled pairs of coils.

Assuming this sound section has been built into a complete television receiver, the procedure is as follows. Stop the local oscillator by removing the valve or disconnecting its H.T. supply if it is in the same envelope as the mixer. Short to chassis the A.V.C. line, and connect the signal generator across the second I.F. amplifier grid coil. Inject an A.F. modulated signal of 10 Mc/s and tune L4 and L5 to resonance. This should be done with

the volume-control set at maximum and an A.C. voltmeter connected across the loudspeaker speech coil to indicate resonance. Reduce the signal generator output, transfer to grid of first I.F. amplifier, and tune L2 and L3 to resonance. Next, connect a 0.1 milliammeter in series with vision detector load resistor and transfer the signal

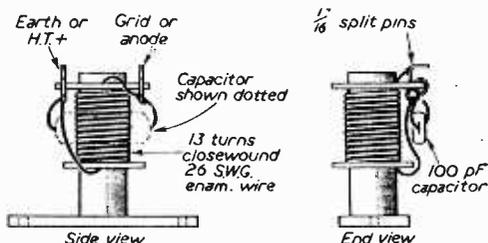


Fig. 3a (left).—Three views of the sound input coil. 3b (above).—Two views of L2-5 inclusive.

generator to the grid circuit of the frequency changer. With the output still at 10 Mc/s, tune L1 to show minimum response on the milliammeter. While doing this it will be found necessary to increase the signal generator output and to turn down the volume-control.

The coils will now be roughly aligned, but the passband will not be symmetrically placed about the intermediate frequency. The coils L2, L3, L4 and L5 should now be re-tuned as follows.

With the signal generator remaining connected across the grid coil of the frequency changer, inject an A.F. modulated 10 Mc/s signal. Connect across L2 a 5 K Ω

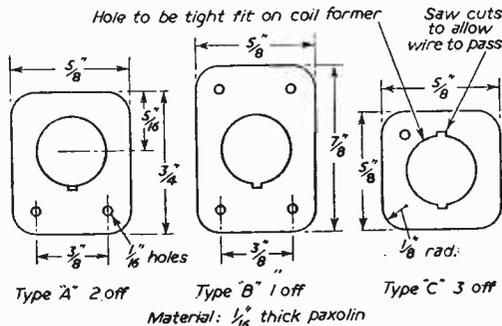


Fig. 4.—Details of paxolin washers.

resistor and tune L3 to resonance. Transfer the resistor L3 and adjust L2. Repeat the procedure with L4 and L5, connecting the resistor across one coil while the other is being tuned. The passband will now be correctly placed and the cores may be sealed with a spot of wax. For frequencies other than 10 Mc/s, substitute the required frequency at all references to 10 Mc/s.

COMPONENT VALUES IN FIG. 1

R1, R11.—5M Ω ($\frac{1}{2}$ w).	C1, C3, C4, C9, C12, C16,—.01 μ F (500v Paper).
R2, R4,—150 Ω ($\frac{1}{2}$ w).	C2, C5, C6, C8, C10,—100pF Silver Mica ($\pm 5\%$).
R3, R5,—3.3K Ω ($\frac{1}{2}$ w).	C7,—10pF (Silver Mica).
R6, R9,—33K Ω ($\frac{1}{2}$ w).	C11,—25pF (Silver Mica).
R7,—2.2M Ω ($\frac{1}{2}$ w).	C13,—300pF (Silver Mica).
R8,—1M Ω ($\frac{1}{2}$ w).	C14,—.001 μ F (Mica).
R10.—5M Ω Volume Control.	C15.—1 μ F (500v Paper).

ARTHURS HAVE IT!

LARGE VALVE STOCKS

TEST METERS IN STOCK
AVO VALVE CHARACTERISTIC METER IN STOCK.
 "AVO," "TAYLOR" TEST METERS AND
 SIGNAL GENERATORS. MEGGERS
AVO. No. 8 IN STOCK

Leak Point One Amplifiers	£28	7	0
Leak Pre-amplifiers	9	9	0
Leak Vari-slope Pre-amp. for Leak Point One	12	12	0
Leak Tuning Unit	38	5	0
Chapman Tuning Units	17	6	8
Connoisseur Two-Speed Motor	22	18	6
Decca Replacement Heads and Pick-ups	35	0	0
Wright & Weaire Tape Deck	93	10	0
Cossor Double Beam Oscilloscope	1035	132	0
	1049		

Woden Output Transformers
 for Williamsons Amplifier 6 10 0

LATEST VALVE MANUALS
 MULLARD, OSRAM, & BRIMAR No. 4, 5/- each.
 MAZDA 2/- each. Postage 6d. each extra.
**TELEVISION SETS, WIRE AND TAPE RECORDERS
 ALWAYS IN STOCK**


TERMS C.O.D. OR CASH with order and subject to price alterations and being unsold.

Arthurs

Est. 1919

PROPS: ARTHUR GRAY, LTD.
 OUR ONLY ADDRESS: Gray House,
 150-152 Charing Cross Road, London, W.C.2
 TEMPLE Bar 5833/4 and 4765
 TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."
 CABLES—"TELEGRAY, LONDON."

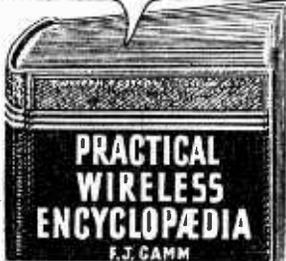How much do you know
 about **RADIO** and
TELEVISION?



This world-famous book contains all latest radio and television developments. Earlier copies sold 300,000; this entirely new volume has 400 pages, 1,440 entries, hundreds of illustrations, covers every aspect of radio; new sections include radar, television, remote control, oscillators, Kirchoff's laws, photo-electric cells, new series of modern circuits

for receivers and amplifiers; automatic station sel., car radio, electron multipliers, fault finding, building television receiver, new colour codes, etc.—contains all the accumulated knowledge of radio science! Examine this grand book on our 5 days' approval terms—if you do not wish to retain it, return and your purchase money is refunded in full.

MAKE SURE OF YOUR COPY—POST COUPON NOW

To: **A. THOMAS & Co. (T4), 111 Buchanan St. BLACKPOOL**
 I enclose 22/- for one copy of above OR Please send C.O.D.
 If I return book in 5 days you refund in full.

Name

Address

D. COHEN

RADIO & TELEVISION COMPONENTS

SMOOTHING CHOKE. Five Henry 250 mA. 50 ohms, 6/6. P. and P. 1/-.
T.V. COILS: wound in Aluminium Can, size 21 x 1, with former and iron dust core, 1/-.
FRAME OSCILLATOR TRANSFORMER. 4/6. P. & P., 9d.
H7G VALVEHOLDER with screening can, 1/8.
HEATER TRANSFORMER.—Pri. 230-250 v. Sec. 2 v. 21 amp., 5/-. Pri. 230-250 v. Sec. 6 v. 11amp. 6/-. P. & P. 1/- Primary 230-250 v. Sec. 2, 4 or 6 v. 2 amp., 7/6. P. & P. 1/-.
SMOOTHING CHOKE.—150 mA. 2 Henry, 3/6. P. & P. 1/-.
P.M. FOCUS UNIT.—Any 9in. or 12in. Tube, except Mazda 12. State Tube, 12/6. with front adjustment, 15/-. For 12in. Mazda, 15/-. Similar to above, with front adjustment, 17/6. P. & P. 1/6 each.

MAINS TRANSFORMERS
 Primary 200-250 v. P. & P. on each, 1/6 extra.
 280-0-280, 80 mA., 6 v. 3 amp., 5 v. 2 amp., semi-shrouded, drop-through, 17/-.
 250-0-250, 60 mA., 6 v. 3 amp., upright mounting, 12/6.
 250-0-250, 80 mA., 6 v. 4 amp., upright mounting, 14/-.
 300-0-300, 100 mA., 6 v. 3 amp., 5 v. 2 amp., 25/-.
 350-0-350, 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.
 Semi-shrouded, drop-through, 290-0-290 80 mA., 4 v. 6 amp., 4 v. 2 amp., 12/6.
 350-0-350, 120 mA., 4 v. 6 amp., 4 v. 3 amp., drop-through, 21/-.
 350-0-350, 100 mA., 4 v. 2 amp., 4 v. 4 amp. Upright or drop-through mounting, 16/-.
 Primary 230 v. Secondary 200-0-200 v. 35 mA. 6 v. 1 amp., 8/6.
 Transformer, Primary 200-250 v. Secondary 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 v. at 2 amps., 13/-.
 220-0-220, 250 mA., 6 v. 6 amp., 5 v. 3 amp., semi-shrouded, drop-through with fuse, P. & P. 3/-. 20/6.
 Tube supporting Bracket in 18 gauge cadmium-plated steel, size 9 1/2 x 4 1/2 in., with 3/16 in. diameter cut-out complete with 12in. Tube supporting clamps, 2/-.
 Frame output transformer, 10 Henry matching 10-1, 9/6.
 Auto-wound, could be used in the Viewmaster. H.T. 280 v. 380 mA. 4 v. 3 amp., 1 v. 3 amp., 2 v. 3 amp., 2 v. 3 amp., 10/-, plus 1/6 post and packing.
 9in. White rubber mask with armour-plate glass, 10/-; 12in. Cream rubber mask with armour-plate glass, 15/-; 15in. Rubber mask, 15/-.
 12in. Armour-plate glass, 4/-; 9in. Armour-plate glass, 3/-.
TV CHASSIS.—Size 9 1/2 x 9 1/2 x 3 1/2. 18 gauge steel cadmium plated, complete with five coil cans, size 1 1/2 in. x 1 1/2 in., with iron cored former. These are wound for television frequency, 4/6. P. & P. 1/6.
6in. ENERGISED TELEVISION SPEAKER by Plessey. Field resistance 68 ohms with Humbucking coil. Will pass up to 300 mA. Require minimum 200 mA. to energise. These are cheaper than a TV choke, 9/6 each, 2 for 18/-.
TV WIDTH CONTROL. 3/6.

Kit of parts for Signal Generator. Coverage 100 Kcs.-300 Kcs., 320 Kcs.-600 Kcs., 900 Kcs.-2.75 Mcs., 2.75 Mcs.-8.5 Mcs., 8.5 Mcs.-20 Mcs. Metal case 10 x 6 1/2 x 4 1/2 in., size of scale 6 1/2 x 3 1/2 in. 2 valves and 1 rectifier valve. A.C. mains 230/250. Internal modulation 400 cps. to a depth 30 per cent. Frequency calibration accuracy plus or minus 1 per cent. Modulated or unmodulated R.F. output continuously variable 100 millivolts. Price £2/10/0. P. & P. 4/-. This includes the return to us for checking and calibration. Point to point and theoretical diagram, 3/6. We will build for 15/- extra.

WATERHOUSE 5in. EXTENSION SPEAKER, complete with volume control, in gold and green, 22/6. P. & P. 1/-.
GERMANIUM DIODE, 2/3 each. Post paid.
COMBINED 12in. MASK AND ESCUTCHEON in lightly-tinted perspex. New aspect edges in brown. Fits on front of cabinet for round face tubes, 17/6. P. & P. 2/-.
E.H.T. INSULATED HEATER TRANSFORMER.—6.3 v. 0.6 amp., and 2 v. 21 amp. Primary 200-250 v., 8/6. P. & P. 1/6.
CONSTRUCTOR'S POLISHED CABINET, size 10 x 6 1/2 x 5 1/2 in. approx., supplied in flat form, grooved and ready to glue together. Complete with plastic front, 3-valve chassis, size 9 1/2 x 4 1/2 in. tuning scale, back-plate and back. Two knobs not supplied, 10/-. P. & P. 1/6.
TWIN-GANG and pair of T.R.F. COILS to suit above, 8/6.
MINIATURE MOULDED WIRE ENDS. .001, 50pF, 100pF, 470 pF and 500pF, 7d. each.
12 YDS. PUSH-BACK CONNECTING WIRE, 1/6 post paid.
P.M. SPEAKERS
 Closed field

	with trans.	less trans.
2 1/2 in.	15/6	
3 1/2 in.	13/6	
5 in.	12/6	
6 1/2 in.	12/6	
8 in.	15/6	
10 in.	25/6	

Post and packing on each of the above, 1/6.
TERMS OF BUSINESS: CASH WITH ORDER.
DISPATCH OF GOODS WITHIN 3 DAYS FROM RECEIPT OF ORDER.
 Orders under £2 add 2/-. Under £1 add 1/6 post and packing.
 All enquiries and lists, stamped, addressed envelope.


23, HIGH ST., ACTON, W.3

(Uxbridge Rd.) Acton 5901.

... picture perfection
with the **DUBLEX**
Aerialite

Because
It Has

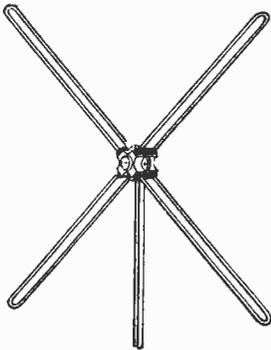
- HIGH GAIN
- BROAD BANDWIDTH
- CORRECT MATCHING
- HIGH MAX/MIN RATIO



these features, PLUS excellent mechanical design, ensure that you get the best performance from your receiver. Moreover, the Dublex is moderately priced at **£4.8.6** (7ft. mast complete with brackets, etc.); **£7.15.0** (10ft. x 2in. mast complete with double lashings, etc.).

... other quality aerials

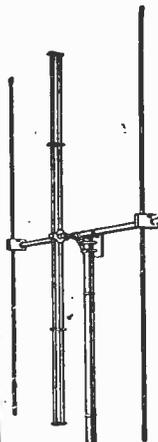in the comprehensive Aerialite range include the AERFRINGE and AERADDOOR models: 8.0dB forward gain, sharp directivity for interference elimination and broad bandwidth for greater detail. Model 63A complete with 10ft. mast, double lashings, etc., price **£13.15.0**. The room-mounting AERADDOOR model 65 has a telescopic top element and is suitable for all channels. Price **£11.12.0** complete.



NEWCASTLE and BELFAST TRANSMITTERS—

the Dublex is available with a special horizontal mounting bracket for reception of these stations and most other Aerialite aerials can be used without modifications.

Aerialite LTD.

CASTLE WORKS STALYBRIDGE CHESHIRE

The solder for all
HOME TELEVISION CONSTRUCTOR SETS

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60/40 High Tin Television and Radio Alloy. The size 1 Carton contains 47 feet of solder, costs 5/-.



Ersin Multicore Solder


In case of difficulty in obtaining supplies, please write to:

MULTICORE SOLDERS LTD. MULTICORE WORKS, MAYLANDS AVE., HEMEL HEMPSTEAD, HERTS. • Boxmoor 3636 (3 lines).

Television at 200 miles

NEW MODEL SC23 TV PRE-AMPS. ALL CHANNELS

- High gain and low noise.
- Customs built to the highest standards.
- Ample bandwidth for good definition.
- Ideal for the "difficult" fringe and ultra fringe areas.
- Each pre-amp. supplied guaranteed to have been "air tested" and to have received both vision and sound at 200 miles using a standard commercial superhet receiver.
- Models SC22 and SC23 have self-contained metal rectifier power supply, 200/250 v. A.C.
- 12 months' guarantee.
- Immediate delivery.

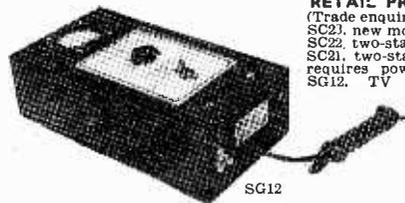

RETAIL PRICE LIST
(Trade enquiries invited)
SC23, new model, **£5.5.0.**
SC22, two-stage, **£9.10.0.**
SC21, two-stage, **£8.6.0.**
requires power supply.
SG12, TV Sig. Gen., **£8.19.6.**
PG12, Patt. Gen., **£19.19.0.**

TELEVISION SIGNAL GENERATOR


- Frequency range 4070 Mc/s.
- Calibration chart for all Television Channels.
- Modulation on sound and vision optional.
- Sensitive meter fitted for use as grid dip oscillator.
- Ideal for service engineer and experimenter.
- Measures coil, aerial frequencies, etc.
- The only one of its kind on the market.
- Self-contained power supply, 200/250 v. A.C.
- 12 months' guarantee.
- Immediate delivery.

J. V. RADIO CO.

25, WILLIAM STREET, PLYMOUTH.

Manufacturers of Television Equipment.

Tel. 4797

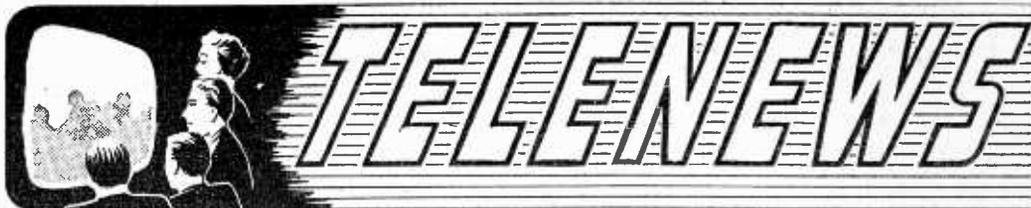

Germans Use British Equipment

PYE, LTD., of Cambridge, announce that the German authorities have decided to use British equipment in the German Television service. Orders have been received for the installation of television cameras and their associated equipment by the Bayerische Rundfunk and the Nordwestdeutscher Rundfunk at Munich and the Nordwestdeutscher Rundfunk at Hamburg.

Cricket Again

THE M.C.C. have decided that the sound and vision broadcasting of Test and county cricket matches will be again permitted during this year's season, but fees may be slightly raised.

Free Baby Sitters

"**WANT** a free night out?" was the title of a publicity campaign launched by J. W. Dargavel Ltd., Glasgow dealers in Ekco radio and television receivers.

The firm offered free transport and a baby sitter to parents wishing to spend an evening out at a TV demonstration, but although the free transport offer was accepted by quite a few no one appeared to require the services of a nursemaid.

Commercial Service

A COMPANY providing a commercial television service for advertising agencies has been formed under the name of Feature Programmes Ltd.

Its staff includes Mr. John MacMillan, ex-deputy to the Controller of the BBC Light Programme, and its main features will be script preparation, casting and direction.

Ediswan Replacement

MR. SIDNEY WEBSTER has taken the place of Mr. A. B. Carnell as specialist radio representative in the Ediswan Birmingham District Office area, covering Warwickshire, Worcestershire, Staffordshire, Herefordshire and Shropshire.

He is thoroughly conversant with all aspects of the radio trade, particularly those concerning valves and cathode-ray tubes.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Cossor Research

MR. B. C. FLEMING-WILLIAMS, Cossor director of research, and Mr. K. E. Harris, research manager, recently left this country by air on a visit to the U.S.A. and

Canada. They will be contacting subsidiary companies in both America and Canada and generally keeping in touch with current electronic developments in the New World. Their visit will last some two months.

Underwater Camera


A NEW underwater television camera, developed by the Bureau of Ships, Department of the U.S. Navy, is being used as a "seeing eye" for Navy divers.

It electronically records a picture which is transmitted to a television screen on the ship. Engineers can either check the scope as it records or a film can be taken of the action and used as a permanent reference. The camera is manipulated entirely by remote control.

Development Down Under

THE Australian Government has given permission for the development of television by private as well as State enterprise.

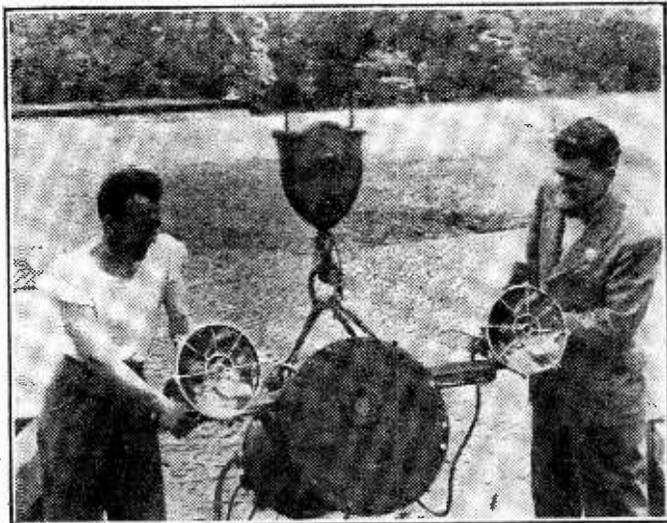The television development plan was halted at one time because of Australia's rearmament programme.



Engineers adjust the floodlights on one of the U.S. Navy's new underwater television cameras before lowering it to the ocean bed.

Television Licences

THE following statement shows the approximate number of television licences issued during the year ended December, 1952. The grand total of sound and television licences was 12,859,473.

Region	Number
London Postal	664,248
Home Counties	222,131
Midland	426,045
North Eastern	199,771
North Western	232,335
South Western	47,750
Welsh and Border	58,529
<hr/>	
Total England and Wales	1,850,809
Scotland	41,699
Northern Ireland	324
<hr/>	
Grand Total	1,892,832

Wales Keener than Scotland

SPEAKING in Aberdeen recently, Sir Ian Jacobs, Director-General of the BBC, said that the number of television licences taken out in South Wales far exceeded the number issued in Scotland, although the Wenvoe transmitter came into operation after the Kirk o' Shotts station.

He said that this was probably due to the natural caution of the Scots concerning the reduction of purchase tax on receivers.

Temporary Station in N. Ireland

THE BBC proposes to instal a temporary low-power television station in N. Ireland before the Coronation. A site has been acquired 2½ miles from the centre of Belfast. The station will be known as Glencairn and will serve the city of Belfast and its immediate surroundings.

Glencairn will share the same frequencies as Alexandra Palace, vision 45.0 Mc/s and sound 41.5 Mc/s. The double side-band system of transmission will be used.

High-Frequency Convention

MR. H. J. FINDEN, M.I.E.E.; of Plessey Ltd., read a paper on Developments in Frequency Synthesis at the High Frequency Measurements Convention in Washington.

It described a development carried out on a British Ministry of Supply contract for Telecommunications Research Establishment. A method of generating any single frequency out of a possible 100,000 in the spectrum 1 kc/s-100 Mc/s locked in

terms of a frequency standard was explained.

Royal Patronage for the Show

THE Radio Industry Council announces that H.M. Queen Mary has graciously consented to be patron of the National Radio Show to be held in London in September. Her Majesty has been patron on each occasion since the war.

Provisional dates for the Radio Show are September 2 to 12, with a pre-view for overseas visitors and other special guests on September 1.

Foottallers Want TV

MR. J. GUTHRIE, 42, Chairman of the Football Players' Union, has asked the BBC for programme time in which professional footballers will be allowed to state their views on the position concerning the televising of soccer matches.

Mr. Guthrie contends that players should be paid a fee of about three or four guineas for each game and would like to have televised a discussion forum between the Football Association, the Football League and club managers under an independent chairman so that viewers might see that the ban is not the fault of the players themselves.

Camera Sites Fixed

WHEN the Coronation is televised in June, viewers will see almost two miles of the Queen's journey to the Abbey.

Cameras will be stationed at the Victoria Memorial, outside Buckingham Palace, on the Colonial Office

overlooking the west door of the Abbey and inside the Abbey itself.

Special "long-range" lenses will enable the cameras to pick up pictures when the procession is a quarter of a mile away, allowing for any kind of weather conditions.

Closed Circuit Only

COMMERCIAL television on a closed circuit only will begin in New Zealand next year.

The transmitter is to be built by a British company

French Tele-clubs

FORTY villages in France have formed "Television Clubs," each village collectively owning a receiver which is installed in the public hall or local school.

Members pay a small admission fee to see an evening's programme, usually 20 francs which goes towards the payment for the set. Chief aim of such clubs is the advance of educational standards as well as providing entertainment.


TV in Workshop

THE *Literary Gazette*, a Russian magazine, states that TV is to be used in Russian factories so that managers can watch progress and developments without their having to leave their office desks.

170 Sacked

ON the grounds of redundancy, 170 employees have been discharged from a Hayes, Middlesex, radio and television factory.

Each was given an extra week's wages.

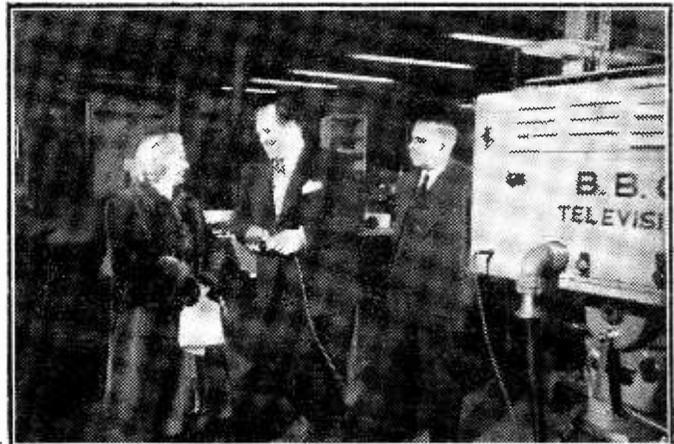

BBC commentator chosen to cover the Coronation for television is Richard Dimbleby, who is seen here in one of his many interviews before the camera.

MAINS TRANSFORMERS

MT1 PRIMARY: 200-220-240 v.
SECONDARIES: 250-0-250 v., 80 m.a.,
 0-4 v.; 5 a.-6.3 v.; 4 a. 0-4 v.-5 v. 2 a.

MT2 as above, but with 350-0-350 H.T. winding ... 17/6 each

ERIE CERAMICONS
 6.8 PF., 5 PF., 12 PF., 50 PF., 180 PF., 5d. each

INDICATOR UNIT TYPE 233
 Complete with 10 valves and VCR97,
 70/- each, carriage 7/6 each.

INDICATOR UNIT TYPE 6
 Very good condition. VCR97 Tube.
 EF50 valves, etc. Wire wound vol.
 controls and a Host of Resistors and
 Condensers. 72/6 each, carriage 7/6.

WIRE WOUND VOL. CONTROLS
 512, 200Ω, 10 kΩ, 20 kΩ, 25 kΩ, ... 2/6 each
 50 kΩ

400Ω, 1 kΩ, 2 kΩ, 5 kΩ, 15 kΩ, ... 2/6 each
 300Ω, 50Ω ... 2/6 each

LOUD SPEAKERS
 All 2 to 3 ohms, these prices are less
 purchase tax. Buy now while stocks last

3in. round type, 12/8 each.
 9in. Elac. square type, 13/6 each.

5in. units by Goodmans, Plessey,
 Waterhouse and Lectrona, all 13/9 each.

6in. units by Elac, Plessey, 14/6 each.
 8in. units by Elac, Plessey, 17/6 each.

10in. Rola, 32/6; 10in. Plessey, 19/6
 each.

Truvox 6in. with output transformer,
 16/6 each.

Goodmans 6in. latest type, 16/-
 Truvox wafer speaker 7in., 25/- each.

Truvox heavy duty 12in., 15 ohms
 speech coil, 26.6.0 each.

P.F. SILVER MICA CONDENSERS
 150, 35, 125, 2, 100, 30, 20, 610, 9, 18, 500, 10,
 300, 120, 375, 680, 15, 25, 370, 27, 39, 330,
 245, 470, 1, 5, 1,600, 750, 1,200, 3, 7.5, 8, 6,
 33, 200, 1,000, 175, 360, 190, 47, 58, 50, 68,
 45, 30, 13d.

**ALPHA RADIO
 SUPPLY CO.**

VALVES

GUARANTEED NEW AND BOXED.
 MAJORITY IN MAKERS CARTONS.

6P25	10/-	6AK5	8/6	6F6G	8/-
6SL7	9/-	6AJ5	8/6	6G6G	7/-
6SN7	10/6	6BA6	8/6	D63	4/6
6V6G/GT	8/6	6AG5	8/6	807	10/-
6AL5	8/6	EL42	11/6	6J5GT	5/6
6AM6	9/6	EF42	10/-	6J5M	6/-
6AT6	10/-	EF41	11/6	6J7G	6/6
6BE6	11/6	UF41	10/6	6KTG-GT	6/6
6C4	8/6	VR136	7/-	6K5G-GT	10/6
6LD20	11/6	VR137	5/9	6L6G	10/8
6L8	11/6	EF50	6/6	12A6	5/9
6L19	11/6	EY51	15/-	12C3	9/8
12A17	10/-	R12	13/6	6S07	9/6
KT61	10/6	ECH42	12/6	6SS7	9/6
N87	10/6	5V4	9/6	KT33C	11/6
20D1	11/6	VU120A	4/-	MS-PEN	5/-
20L1	11/6	VU111	4/6	PEN25	8/6
7S7	8/6	OZ4	7/-	25A6G	9/8
TY4	8/6	IC5GT	8/6	25L8G	9/6
PL82	11/6	IR5	8/6	PEN20A	4/9
AC6/PEN	5/8	IS4	8/6	TH300	8/6
A731	10/-	IS5	8/6	TP25	8/6
10LD11	11/6	IT4	8/6	UR2C	9/6
U22	9/-	3S4	10/-	4D1	4/-
U43	8/6	2X2	5/6	9D2	3/-
UB41	9/-	6Q7G/GT	10/-	8D3	3/-
UCH42	11/6	6SK7	7/-	15D2	4/-
UF41	12/-	4Z	8/6	Y83	9/-
UL41	10/6	5U4G	9/-	ECH21	11/-
EA42	11/6	5Y3G-GT	8/6	12SH7	5/6
EBC11	10/6	5Z1G	8/9	PEN43	8/6
EBC41	11/6	6X5GT	7/9	Z83	5/9
6AK5	8/6	6CS	7/6	VR101	5/6

RESISTORS 1 and 1 watt.

We send whichever rating is available
 at this price:

3.3 kΩ, 1.5 kΩ, 68Ω, 2.2 meg.Ω, 100 Ω,
 12 meg., 330Ω, 10 meg., 27 kΩ, 470 kΩ,
 2.2 kΩ, 22 kΩ, 150 kΩ, 6.8 kΩ, 5.6 kΩ,
 600 Ω, 39 kΩ, 120 kΩ, 1 meg.Ω, 10 kΩ,
 330 kΩ, 15 kΩ, 220 kΩ, 33 kΩ, 5 meg.Ω,
 1 kΩ, 51 kΩ, 90 kΩ, 1.8 meg.Ω, 33Ω,
 20 Ω, 1.8 kΩ, 15-meg.Ω, 270Ω, 220 kΩ,
 350Ω, 40 kΩ, 47 kΩ, 60 kΩ, 100 kΩ,
 18 kΩ, 270 kΩ, 68 kΩ, 680 Ω, 25 kΩ,
 33 kΩ, 5 kΩ, 150 Ω, 200 Ω, 200 Ω, 22 kΩ,
 50 Ω, 4.7 kΩ, 680Ω, 56 kΩ, 56Ω, 470Ω,
 4 kΩ, 47Ω, 50 kΩ, 150Ω. All 31d. each.

RESISTORS 1 watt

1.5 kΩ, 15 kΩ, 6 kΩ, 390 kΩ, 3.3 kΩ,
 620 kΩ, 350 kΩ, 5.6 kΩ, 75Ω, 8.2 kΩ,
 2.5 kΩ, 20 Ω, 680Ω, 1 meg., 5 1/2 Ω, 250Ω,
 100Ω, 40 kΩ, 150Ω, 6.8 kΩ, 9 meg.Ω,
 8 meg.Ω, 7 meg.Ω, 4.7 kΩ. All 6d.

SINGLE P.V.C. COVERED WIRE
 Various colours: Red, Blue, White,
 Green, Yellow, etc. 5/6 per 100 yds.

METAL RECTIFIERS

12 v., i.a., 1/6; 2 to 6 v., i.a., 3/-; 12 v.,
 1 a., 4/9; 250 v. 45 m/a., 6/9; 250 v.,
 75 m/a., 7/6; 12 v., 3 a., 18/6; R.M1,
 4/-; R.M2, 4/6; R.M4, 16/-; 12 v. 2 a.
 10/6 each.

ALLADIN COIL FORMERS

4in. and 8in., complete with iron dust
 cores. 9d. each.

CONDENSERS METAL-CASE TYPE ELECTROLYTIC

8 mfd., 450 v., 1/11 each; 16 mfd., 450 v.,
 3/3 each; 16 x 16 mfd., 450 v., 4/9 each;
 16 x 8 mfd., 450 v., 4/6 each; 8 x 8 mfd.,
 450 v., 4/- each; 25 mfd., 25 v., 1/3 each;
 32 mfd., 350 v., 1/9 each; 32 x 32 mfd.,
 350 v., 25 mfd., 25 v., 5/3 each.

TERMS: Cash with order or C.O.D. **MAIL ORDER ONLY.** Illustrated List available; send 6d. stamp.

Postage, 6d. to 10/-; 1/- to 20/-; 1/6 to 2/-; 2/- to 25. Minimum C.O.D. and postage charge 2d.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS, 1

HOME CONSTRUCTED TELEVISORS



Component Specialists since Broadcasting started,
 can supply all or any of the components specified for the

**"VIEWMASTER"
 "MAGNAVIEV"
 "TELEKING"**

and "Viewmaster" Wide-angle Conversion.

All cabinets, valves, aerials, feeder cable, wire,
 sleeving, solder, nuts and bolts, clips, etc.

Order with confidence c.o.d. or c.w.o. at current
 prices, or send s.a.e. for Price List.

We also invite your inquiries for all other electronic
 components.

H. L. SMITH & CO., LTD.
 287/9 Edgware Road, London, W.2.


Tel.: Paddington 5891. Hours 9 till 6 (Thursday
 1 o'clock).

Near Edgware Road Stations, Metropolitan and Bakerloo.

The British Neon T/V E.H.T. Tester, is the
 very thing for the amateur constructor, does the
 job of an electrostatic voltmeter, and more ...
 at a fraction of the cost.

It measures C. R. T. anode volts from 3-16
 thousand and gives a check on volts at anode of
 line output and deflector coils, and E. H. T.
 rectifier.

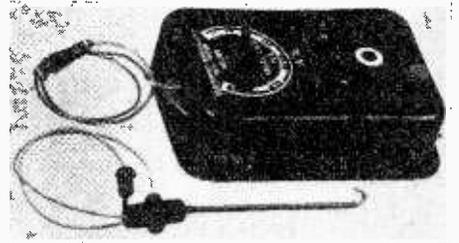Is in use in hundreds of Service Departments
 throughout the British Isles and abroad.



Obtainable direct from the makers:—
 47/6 Post Paid. Cash with Order.
 Guaranteed 12 months.

BRITISH NEON
 Manufacturing Company Ltd.,
 Cottenham, Cambridge.

HENRY'S

INDICATOR UNIT TYPE 182A. This unit contains VCR517 Cathode Ray 6in. Tube, complete with Mu-metal screen, 3 EF50, 4 5P61 and 1 5U4G valves, 9 wire-wound volume controls and quantity of Resistors and Condensers. Suitable either for basis of Television (full picture guaranteed), or Oscilloscope. Offered BRAND NEW (less relay) in original packing case at 79 6. Plus 7/6 carr. "W.W." Circuit supplied Free.

2	Cang.	.0005	Condensers	Midget	5/-
2	"	.0005	"	"	with Trimmers. 6 6.
2	"	.0005	"	"	with 4-way Push-Button. 8 6.

WEARITE MAINS TRANS. Input 110/250v. output. 325-0-325. 80 m.a. 6 v. 2.5 amp., 5 v. 2 amp., £1 1/-.

PLESSEY MIDGET TYPE. 200/250 output. 290-0-290 50 m.a. 6 v., 2.6 amp., 12 6. P.P. 1/-.

I.F.T.S. Wearite. 501A and 502. 465 kc's, 10" pair, P.P. 1/-.
 .. Plessey 465 kc's Permeability, 8 6 pair, P.P. 1/-.

EXCEPTIONAL VALVE OFFER

Ten EF50 Brand New (Ex-Units)	55 - Set
6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G (or KT61)	42 6 ..
1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4)	32 6 ..
TP23, HL23 DD, VP23, PEN25 (or QP25)	27 6 ..
6K8G, 6K7G, 6Q7G, 5Z4AG, 25Z5 or 25Z6G	42 6 ..
12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT or 50L6GT	42 6 ..
12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT or 50L6GT	42 6 ..

Complete set of specified valves for "P.W." Personal Rec. 5 6AM6, 2-6AK5, 1 6J6, 1 6J4, 1 EA30, and 3BP1 C.R. Tube with base. £5 12-6.

PYE 45 Mc's. STRIP. Size 15in. x 8in. x 2in. Complete with 45 mc's Pye Strip, 12 valves, 10 EF50, EB34 and EA50, volume controls and hosts of Resistors and Condenser. Sound and vision can be incorporated on this chassis with minimum spec. New condition. Modification data supplied. Price £5, carriage paid.

BLUE & WHITE VISION

VCR517C Tubes, Brand New and crated. Guaranteed full picture. These Tubes replace the VCR97 and VCR517 without alteration and give a Blue and White picture. 45 - plus 5/- carr.

CATHODE RAY TUBES:

VCR97. Guaranteed full picture, 40"-, carr. 5/-.
 VCR517. Guaranteed full picture, 40"-, carr. 5/-.
 3BP1. Suitable for scopes and Tel. 25 - carr. 3/-.
 MU-METAL SCREEN for VCR97 or 517. 12 6d.
 VCR139A (ACR10), 35 - carr: 3 -.

6in. ENLARGER LENS. 18 6. p.d. 3 -.

45 mc - Two Stage Pre-Amplifier containing 2-VR1. Completely wired. Requires slight modification and coil adjustments for any area. 22 6 complete. 3 - p.p.

P.M. SPEAKERS (Inc. Tax)

Plessey 3in. with Trans.	15 -	Rola 10in. with Trans.	30 -
Celestion 5in. with Trans.	18 -	Goodman's 10in. with Trans.	30 -
Rola 5in. less Trans.	12 6		
Plessey 5in. less Trans.	12 6	Electrona 10in. with Trans.	25/-
Plessey 61 L T	15 -		

Postage and packing 1/- extra.

1355 Complete Brand New in Case. 55/-, RF21, 25, 25/-, RF26 and 27. 59 6.


SEND POSTAGE FOR NEW 1953 COMPREHENSIVE 28 PAGE CATALOGUE.

Open Mon.-Fri. 9-5.30. Sat. 6 p.m. Thurs. 1 p.m.

5, HARROW ROAD, PADDINGTON, LONDON, W.2.

TEL.: PADDINGTON 1008/9, 0401.

FREE

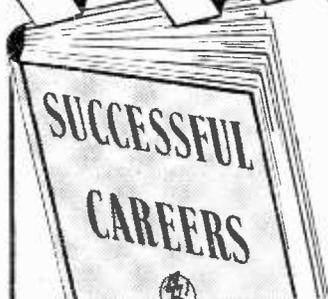

THIS VALUABLE BOOK

which details the wide range of Engineering and Commercial courses of modern training offered by E.M.I. Institutes — the only Postal College which is part of a world-wide Industrial Organisation.

Courses include training for:

City and Guilds Grouped Certificates in Telecommunications; A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio & Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering.

NEW!

- POST NOW -

Please send, without obligation, the FREE book.

E.M.I. Institutes, Dept. 138K
 43 Grove Park Road, Chiswick, London, W.4

Name

Address

EMI INSTITUTES
 associated with
MARCONIPHONE H.M.V.
COLUMBIA &
 (His Master's Voice)

Home Experimental Kits now form part of the following courses: Draughtsmanship, Carpentry, Chemistry, Photography, Commercial Art, Radio and Electronics, etc.

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

THE "MIRACLE"

SIR.—I have a five-year-old model television set which has, unfortunately, been in the hands of service engineers far too often. When one depletes savings to the extent of £100 for purchase, and a further £25 in the next four years it makes one a little canny.

As I have now retired on a small pension, it became necessary to do my own servicing, as far as possible. For the past year, I have been quite successful, with the exception of occasional vertical turns of the picture when warming up. (None of the service engineers has been able to do much about this.)

Last week I determined to have another attempt. On being unbolted, the chassis slides down a slope. I worked it gently forward, because I did not wish to unsolder loudspeaker leads, for complete removal. I turned as an interruption came in the form of a ring on the doorbell. To my amazement, the chassis slid from its grooves and crashed 24in. to the floor. The young lady upstairs came rushing to see what all the noise was about and gasped.

I carefully lifted the chassis and, apart from torn loudspeaker leads, could find no damage. (The chassis weighs about 50lb.) Not one of the 20 or more valves was disturbed. The tinkles heard were valve covers falling off.

On replacing the set and connecting the loudspeaker, I retuned line and frame holds and was overjoyed to find that width and height of the picture were more satisfactory than they had ever been and reproduction was perfect.

But for the witness upstairs I almost feel that this has been a bad dream, from which I must awake and chase those elusive vertical turns. Anyway, I am ensuring that only *one* miracle like this can happen in my lifetime.—CHARLES HASSELL (New Southgate, N.11).

LOW-NOISE PRE-AMPLIFIERS

SIR.—Owing to my enthusiasm to keep a previous letter brief and so conserve your space when it appeared in the December issue, I seem to have fallen into the trap of omitting a qualifying statement when saying that the 6AK5 was not suitable for triode connection. Had I added the words "as shown in the diagram" after "triode connection" in line five, your correspondent Mr. E. D. Frost might not have been moved to question my statement.

However, I did at least explain in the next sentence that a comparatively low-resistance path would be formed across the H.T. supply if the 6AK5 is connected as shown. Mr. Frost seems to have missed the import of this. I cited the EF91 because like the EF50 shown in the diagram it has its suppressor grid isolated; it can, therefore, be connected as shown with anode, screen and suppressor all tied together. Do the same with a 6AK5 and it will cease to function in the triode manner intended by Mr. Thomson, and due to the anode and cathode components being placed directly across the H.T. supply, something is going to get mighty warm! Mr. Frost will, I am sure, agree that the 6AK5 cannot

be triode-connected as shown in the published diagram.

I quite agree with him that the 6AK5 can be triode-connected by strapping screen to anode, and I also concede his point that this valve has a very low-noise factor. Nevertheless I am well satisfied with my ex-Govt. EF91's and their low-noise factor when triode-connected, even in this down-the-drain signal area.

Since we can mutually agree that the EF95 is an exact equivalent to the 6AK5 my remarks above can be applied to both valves.—W. E. THOMPSON (St. Leonards-on-Sea).

CAGE AERIALS

SIR.—I would like to thank Mr. F. R. W. Stafford for writing in support of my views regarding the Cage Aerial controversy. I had, of course, observed "Erg's" assumption that Mr. Stafford's bandwidth figures were purely theoretical, whereas I had been at pains to point out that they had been verified by practical measurements, which showed that in fact they were 15 to 20 per cent. less than the actual bandwidth.

I did not immediately take "Erg" up on this point since I was temporarily blinded by the science displayed in his reply, but I have subsequently discovered the source of his highly-technical dissertation upon bandwidth, and am now somewhat less impressed than I was at first! I, too, have now read the article on page 7 of the Radio Show Edition of "Belling-Lee" Bulletin, and I think it a pity that when quoting therefrom (without any acknowledgment) he did not also quote the penultimate paragraph, which states that any television receiver capable of resolving 3 Mc/s will do so when connected to any "Belling-Lee" television aerial correctly installed. This, surely, answers the suggestion that a rod aerial of normal dimensions is incapable of giving adequate bandwidth.

I would hasten to assure "Erg" that he is not by any means the first to make this suggestion. No less an authority than Dr. Lee de Forest, to whose early work on triode valves we owe so much, recommends the use of iron drain-pipes (of suitable length) to ensure adequate bandwidth, in his "Television To-day and To-morrow," published in 1945!

The only reason for my embarking on this controversy was that I had just read Mr. Stafford's paper prior to reading "Erg's" article, and I was immediately struck by the contradiction. Obviously, the question can only be settled to the satisfaction of the individual by a practical test, and in this connection I warmly support Mr. G. Lee Evans, whose letter in your January number asks why the BBC cannot radiate Test Card C at a time when amateurs who are otherwise engaged on every morning of the week (including Saturdays) can make use of it for bandwidth and linearity tests, which cannot be carried out during a normal programme. Would it not be possible for an approach to be made to the BBC by you, sir, in this matter, in the name of the thousands of amateurs who would welcome such a move?

I must also congratulate "Erg" for his timely article in the January issue, which remedies the shortcomings of his previous article by giving the actual dimensions of aerial elements. This is of real practical value.—H. B. GREGORY. (Birmingham).

[We have approached the BBC on more than one occasion in this connection, but they put forward various reasons why it cannot be done. Perhaps, now, that the main network has been completed, and the band of amateur experimenters reached such large proportions, they will reconsider the matter again.—EDITOR.]

VCR517

SIR,—I wonder if anyone in my part of the world has built a set incorporating a VCR517 tube? If so, then I would very much like to get into touch with him. I myself have just completed a set using such a tube with the Pye 45 Mc/s strip for vision with only moderate results. I am using, roughly, 2.5 kV on the tube, and though the raster is bright enough the picture, alas, is not. Perhaps the fault lies not in the tube, but in the alignment of the vision strip? Anyway, I would like to see what really can be done with this tube. Can anyone oblige, please?—J. B. PHILLIPS (20, Pentlands Close, Mitcham, Surrey).

SIR,—Re my letter on non-focus of VCR517. I must thank all those who wrote to me, and the problem is now solved. For those interested, the voltage on A_1 should be $\frac{2}{3}$ of that on A_3 for correct focus. Incidentally, the base connections are reversed on my tube!

Now I have another problem. Is the heater transformer on the 62 (or 95) unit a 50 c/s model?—B. GILBERT (Bournemouth).

TELEVISION AERIALS

SIR,—The letter signed "Dealer, Bristol" in February issue of P.T. is interesting if only to reveal how the buyers have been "sold."

During 1950 I constructed every conceivable type of TV aerial including a large circle, but never achieved much gain over the conventional "H" type, despite proper matching—at the time I was receiving Sutton Coldfield, approximately 80 miles away, on a Pye TRF receiver.

"Dealer" says: "You are still left with some pretty nasty joints to protect from the weather." Again experiment has proved that the dipole terminals can be left exposed to rain, snow, etc., with no deterioration of signal strength—indeed, my dipole consists of two suitable lengths of dural tube in a 6in. length of paxolin tubing.

Two screws driven through the paxolin and dural act as terminals, to which the 80 ohm twin wire screened feeder is soldered. No weather protection whatsoever and even a covering of snow or ice has no effect on signal strength.—A. ASHCROFT (Ormskirk).

SPOT WOBBLE

SIR,—Some time ago you gave a circuit for a spot wobble unit and I passed this by as being some new "stunt." Later I noted that a well-known manufacturer had introduced this feature and I thought perhaps there may be something in it. I therefore turned up my old copy and made up the unit. When I tried it out I found that it certainly worked, but have spent a number of evenings lately experimenting and I should like to give my opinion as to the results obtained. On most transmissions (except certain Lime Grove ones, such as Café Continental and certain sections of the news-reels) the quality of the picture is so variable that slight defocusing gives just as good results. On the really high-quality transmissions (which are few and far between) when the camera is properly focused, the sharp image which results is spoilt by the spot wobbler or defocusing, and I personally prefer the slightly noticeable line structure. I might mention that I am using a 16in. metal tube, with as near perfect interlace as I can obtain. The unit has been left in position, but is switched off most of the time and the focus is set just off optimum, and this satisfies us and prevents us from noticing too

clearly the variable focus which unfortunately attends most transmissions.—G. WATTS (London, N.W.).

SURPLUS COMPONENTS

SIR,—I know you don't advise using ex-Service parts, but you often specify ex-Service tubes, especially the VCR97, and I should like to add a word of warning about this. I bought one locally and made up a unit as described by you, with very bad results. I had given it up as a loss and actually stopped taking your paper as I thought the circuit had not been tried. One day a friend came in and I happened to mention the set and he looked at it and offered to try to get it working. We went over the circuit together and he brought some meters, etc., and to cut a long story short we finally found the tube was at the root of the trouble. After two or three nights we took a chance and removed the base of the tube and checked the actual leads. We then found that they were joined up all over the place on the base and we managed to sort them out and connect them as shown, when the set worked perfectly. There was nothing wrong with the circuit, but someone had had a game with the tube, and this was probably in the Service before being disposed of. Perhaps some other constructors may experience the same trouble.—G. E. RENDELL (Watford).

TIMEBASE HINT

SIR,—Referring to the article "Timebase Hint," by Mr. G. Williams in your January issue, and being one of the many home constructors who have been disappointed with the Miller timebase, I would like, in addition, to suggest a simple cure for the linearity problem in these timebases, especially the one used in the £9 televisor which I myself use.

I have no doubt also that some home constructors must be using the timebase with non-linearity existing in the frame output.

After arduous experimenting I also evolved a circuit built round the charging condenser which is really split into two components having the same value and the centre connection taken to a potentiometer wired into the discharging network.

The height of the frame also suffered in this timebase and I compensated for this by increasing the capacity of the .003 μ F. condenser in the suppressor grid circuit to .01 μ F.

By this method I produced a *variable* linearity control which opened the lines out alternately on both top and bottom of the frame, having an intermediate effect which was, or near, perfect.—R. CUMMING (Edinburgh 3).

VALVE FAILING

SIR,—I have not seen any hints in your paper on the subject of valve failures. I have had a set now for just over three years, and have replaced six valves. But these have not cost me anything, as I have merely changed them round with others in the set. They were EF50's and were employed in, I think, the sync stage. As I am not aware of the circuit and have never taken the set to pieces, I am not certain and only go by the fact that the trouble which developed resulted in both line and frame slipping. I took out a valve which I thought was the one and changed it with another EF50. By doing this several times I eventually found which was causing the trouble and have done this six or seven times since, each time with an improvement in the trouble. I have now stuck small labels on the valves to indicate which have been used! The hint may perhaps be of use to others.—G. WATT (Shrewsbury).



**Test any
T.V. picture
tube**
without
removing
from cabinet or carton!

with the **Radar** CATHODE RAY TUBE TESTER
REACTIVATOR

Accurately and rapidly check for EMISSION, HEATER CATHODE LEAKAGE, INTER ELECTRODE INSULATION, etc. Measure any component for insulation or resistance up to 50 megohms.

Restores "brightness" to weak tubes
Many tubes which would previously have been discarded because of low emission may now, with this instrument, be reconditioned for a further period of useful service. Invaluable to dealers operating rental or maintenance schemes. Write for fully descriptive leaflet to-day.


PRICE
£21.0.0
NETT TRADE

WAVEFORMS product.

WAVEFORMS LTD., Radar Works, Truro Rd., London, N.22. Tel. BOWes Park 6641-3.

ADCOLA

REGISTERED
(Regd. Trade Mark)

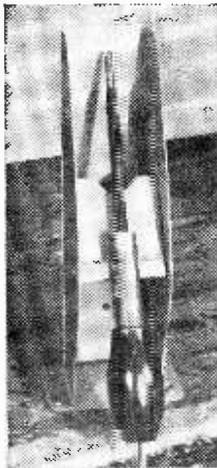

SOLDERING INSTRUMENTS FOR

SUCCESSFUL HOME CONSTRUCTION AND ALL SOUND EQUIPMENT SOLDER JOINTING

"STANDARD MODEL" AS ILLUSTRATED 25/6

Any volt range supplied, 6/7 to 230/250

3/16" dia. bit Standard Model

Equally suited to daily or intermittent use

Made in England
Registered Design
(British, U.S.A., Foreign Patents)

Export Enquiries Invited

Shields as illustrated 10/6 extra.

WRITE DIRECT TO

ADCOLA PRODUCTS LTD.

Sales, Offices & Works: CRANMER COURT, CLAPHAM HIGH ST., LONDON. S.W.4. MACaulay 4272

MAKE YOURS A QUALITY

"VIEWMASTER"

IN TIME FOR THE CORONATION
CASH £32 OR H.P.

Available for purchase stage by stage or H.P. terms by arrangements

ALL ITEMS IN STOCK—SEND FOR LISTS

WB.200 S.V Chassis ...	18 6	TCC Condensers ...	£7 7 0
WB.101 Chassis Supports ...	6 0	Morganite Resistors ...	£1 18 3
WB.102 T.B and P Chassis ...	18 6	Resistances Variable	
WB.103 Mains Transformer ...	£2 2 0	Colvern Pts (Set 6) ...	£1 2 0
WB.103A Auto Transformer ...	£2 12 0	Westinghouse Rectifiers 36/EHT/100 ...	£1 9 5
WB.104 Smoothing Choke ...	15 6	Westinghouse Rectifiers 14/A/85 ...	£1 0 4
WB.105 Loudspeaker	£2 7 6	Westinghouse Rectifiers 14/D/36 ...	11 6
WB.300 Pre-Amplifier chassis ...	17 6	Westinghouse Rectifiers WX.3 ...	3 9
WB.106 Frame Transformer ...	£1 5 6	Westinghouse Rectifiers WX.6 ...	3 9
WB.107 Line Transformer ...	£1 12 6	Westinghouse Rectifiers 36/EHT 45 ...	£1 2 6
WB.108 Scanning Coils ...	£1 13 6	Westinghouse Rectifiers 36/EHT 50 ...	£1 4 6
WB.109 1 Focus Magnet ...	£1 2 6	TCC Condenser Type CP55GO ...	6 8
WB.110 Width Control ...	10 0	TCC Condenser Type CP55VO ...	10 0
WB.111 Boost Choke ...	5 9	TCC Condenser Metal pack CP47N ...	3 6
WB.112 Tube Support 12in. ...	£1 16 0	Wearite R.F. Choke ...	2 0
WB Conversion kit ...	£1 15 0	Bulgin Parts (complete set) ...	15 3
Wearite Coils, H.M. K'SHTS. W.V ...	£1 8 0	Belling Lee Conn. Unit and Fuses ...	10 6

THE CLASSIC ELECTRICAL CO., LTD.

"THE HI-FI TELEVISION SPECIALISTS"

352/364, Lwr. Addiscombe Rd., Croydon, Surrey. Addiscombe 8061/2



The "Fluxite Quins" at Work
 "Fixing an aerial's all right,
 And making it sound with FLUXITE,
 But working in snow
 Is snow joke," bawled OH,
 "It's the third time we've skidded to-
 night."

See that **FLUXITE SOLDERING PASTE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, from 1/- upwards.

FLUXITE

SOLDERING PASTE

A *Staunch Companion to Fluxite Soldering Fluid.*

SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 11d. each.

FLUXITE, Ltd.,
 Bermondsey Street, London, S.E.1.

G.E.C. & B.T.H.

GERMANIUM

CRYSTAL DIODES

G.E.C. GLASS TYPE 5/16in. x 3/16in.
 B.T.H. LATEST TYPE MOULDED IN THERMO-SETTING PLASTIC

Both Wire Ends for Easy Fixing.
 4/6 each, postage 2½d.

SILICON CRYSTAL VALVE

3/6 each, postage 2½d.
 Fixing Brackets 3d. Extra.

Wiring instructions for a cheap, simple but high quality Crystal Set included with each Diode and Crystal Valve.

COPPER INSTRUMENT WIRE

ENAMELLED, TINNED, LITZ,
 COTTON AND SILK COVERED.

Most gauges available.

B.A. SCREWS, NUTS, WASHERS
 soldering tags, eyelets and rivets.
 EBONITE AND BAKELITE PANELS,
 TUFNOL ROD, PAXOLIN TYPE COIL

FORMERS AND TUBES,
 ALL DIAMETERS.

Latest Radio Publications.
 SEND STAMP FOR LISTS.

CRYSTAL SET

INCORPORATING THE SILICON

CRYSTAL VALVE

Adjustable Iron Cored Coil.

RECEPTION GUARANTEED

Polished wood cabinet, 15/-, post 1/-
 A REAL CRYSTAL SET, NOT A TOY

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4

CITY & RURAL

OFFER IMMEDIATE DELIVERY
 FROM STOCK:—

VIEWMASTER

Specified Components. (London—Sutton Coldfield—Holme Moss—Kirk-o-Shotts—Wenvoe—Newcastle—Belfast). Complete Kits, Stage-by-Stage, and Single Components supplied. Send for Stage 1 now—£32.3, post free. Construction Envelopes (all areas), 7/6.

WIDE-ANGLE TV

Wide-Angle Components for Viewmaster, Tele-King and Magnaview.

TV PRE-AMPLIFIERS

Viewmaster Pre-Amp Components for all areas from stock.

CHEAPER TV

See our Current List for Details.

LANE TAPE TABLE

(The new Mk. 3), Three Motors—Fast Forward and Reverse Rewind—Twin Track—High Fidelity—Electromagnetic Erase—Positive Servo Braking. Price £16.10.0, plus 10/- carriage and packing.

TAPE AMPLIFIERS

Lane Tape Recording and Playback Amplifier Kit. (Including valves, and complete down to the last nut and bolt.) Price £13.0.0. Stage-by-stage Construction Envelope 5/-. The Lane Amplifier assembled and tested £15.10.0. Ronette Microphones for use with this Amplifier 52/-.

TRUVOX TAPE DESK MARK III

Three Motors—Drop-in Tape Loading—Push-button Control, Electrically and Mechanically Interlocked—Separate Push-button Brake—Fast Forward and Fast Rewind—Silent Drive—Half-track Working and 2 Tape Speeds—Visual Playing-time Indicator—With a suitable Amplifier, covers a frequency range of 50-10,000 c.p.s. at 7½ inches per second. (Details of an easily-constructed Amplifier supplied free of charge with each desk purchased.) Price £23.2.0, plus 15/- carriage and packing.

For further details of the above equipment, together with details of our range of New and Surplus Valves, Transformers, Coils, Chassis, Cabinets, Chokes, Electrolytics, Manuals, Switches, Meters, Controls, Metal Rectifiers, etc., etc., please send 2½d. stamp for a copy of our Spring Price List.

FOR
 ATTENTION —
 ADVICE —
 SERVICE,
 WRITE

CITY & RURAL RADIO

101, HIGH STREET,
 SWANSEA, GLAM.

Telephone: Swansea 4677

THE MODERN BOOK CO.

The A.R.R.L. Radio Amateur's Handbook, 1953. 30s. 0d., postage 9d.
 Television Engineers' Servicing Manual, by E. Molloy (ed.). 42s. 0d., postage 1s.

Practical Wireless Encyclopedia, by F. J. Camm. 21s. 0d., postage 9d.

Television Receiving Equipment, by W. T. Cocking. 18s. 0d., postage 9d.

Television Fault Finding, compiled by "Radio Constructor." 5s. 0d., postage 3d.

Thermionic Valve Circuits, by E. Williams. 21s. 0d., postage 9d.

Inexpensive Television for the Radio Constructor. 2s. 6d., postage 3d.

Cathode-Ray Oscillographs, by J. H. Reyner. 15s. 0d., postage 6d.

Personal Receivers, by E. N. Bradley. 3s. 6d., postage 3d.

The Radio Amateur Operator's Handbook. 2s. 6d., postage 3d.

Television Explained, by W. E. Miller. 8s. 0d., postage 6d.

Radio Upkeep and Repairs, by A. T. Wills. 12s. 6d., postage 6d.

Radio Valve Data, compiled by "Wireless World." 3s. 6d., postage 3d.

The Williamson Amplifier. 3s. 6d., postage 3d.

We have the finest selection of British and American radio publications in the Country. Complete list on application.

19-23, PRAED STREET,
 (Dept. T.3), LONDON, W.2

PADDINGTON 4185.

YOU can become a well-paid RADIO ENGINEER

Our Home-Study Courses in Radio, Television and Mathematics are a proved success. We train men to earn good money in their spare time, start businesses of their own, or get bigger salaries. Post coupon for free details.

T. & C. RADIO COLLEGE

Post in unsealed envelope, 1½d. postage

To: T. & C. RADIO COLLEGE,
 36, Northfield Road,
 Ringwood, Hants.

NAME.....

ADDRESS.....


T3/53

TRADE NOTES

Aerial for Pontop Pike

A DUBLEX aerial for the new horizontally polarised stations at Pontop Pike and Belfast are announced by Aerialite.

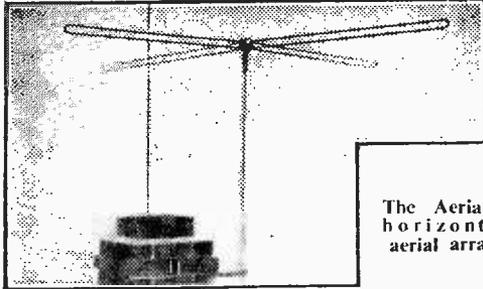The aerial has the features of high gain, excellent maximum/minimum ratio, broad bandwidth. The construction is novel in that the folded elements are cross-connected, giving a highly directional array of robust mechanical construction.



The Aerialite horizontal aerial array.

This model has the advantage that the mast and the aerial can be earthed as a precaution against damage by lightning to the receiver.

The price complete for the Dublex, with a 7ft. mast chimney bracket, etc., is £4 18s. 6d.; other models are available.—Aerialite, Ltd., Castle Works, Stalybridge, Cheshire.

Hunt (Capacitors)—Phone Change

THE telephone number of Messrs. Hunt, at Wandsworth, has been altered to Battersea 1083-7.

New Mullard Double Tetrode

A NEW high-performance double tetrode, especially suitable for use on the new U.H.F. wave-bands, recently allocated for business radio, radar-sonde and television-link equipment, is now being marketed by the Communications and Industrial Valve Department of Mullard, Ltd. It is the QQV03-20, and is intended for wide-band operation as an R.F. Class "C" power amplifier or multiplier in low-power mobile transmitters working at frequencies up to 600 Mc/s. At 200 Mc/s the new valve is capable of providing a power output of 42 watts. Under reduced input conditions, 22 watts can be obtained at 400 Mc/s and approximately 12 watts at 600 Mc/s. As a result of new and important design features the QQV03-20 has the outstanding advantages of high anode efficiency, excellent power gain, low filament consumption and small physical dimensions. In addition, being of the all-glass technique, it does not require the complex circuitry that is normally associated with existing U.H.F. valves of this class. Its small size and low power consumption makes the new valve of particular value for use in compact mobile communications equipment. It is constructed on the B7A base. Technical data is available from Mullard, Ltd., Century House, Shaftesbury Avenue, London, W.C.2.

Magnavita Television Magnifier

METRO PEX announce a new low-price Magnavita oil-filled magnifier. The Magnavita gives perfect enlargement over a wide field of view, and is available in 9in., 12in. or 15in. sizes, clear, or filter at no extra cost.

It is complete with straps enabling it to be easily fitted to any make of television receiver. 12in., 65s.; 9in., 45s.; 15in., 85s.—Metro Pex Ltd., 42a, Denmark Hill, London, S.E.5.

Forrest Picture-tube Transformer

H. W. FORREST, of Shirley, have produced a transformer to overcome cathode-to-heater shorts.

The transformer is for 230 volts input and is available for 2, 4, 6.3, 10 and 13 volts (voltages to be stated when ordering).

The secondary is specially wound to give a small capacity to the primary and core to retain good definition, and special "booster" transformers are also supplied on similar core assemblies, either with or without tag board. Price, 11s. 6d.—H. W. Forrest, 349, Haslucks Green Road, Shirley, Birmingham.

Airmec, Ltd.

WITH reference to the note in our February issue, it should be noted that the name of the company referred to is Airmec, not Airmex.—Airmec, Ltd., High Wycombe, Bucks.

Catalogues and Publications

T.C.C. TECHNICAL BULLETIN

BULLETIN No. 27 deals with Hi-K ceramic receiver condensers which have pure silver electrodes fired on to a ceramic of the barium-titanate group giving high capacity with small physical size. Copies are available on application to the T.C.C. (Radio Division), North Acton, London, W.3.

MULTICORE TECHNICAL SUMMARY M.52

THIS deals only briefly with the many Multicore products, but it contains a large quantity of information generally required by planning and production engineers. In addition to the more well-known Multicore Solders, there is information available on fluxes, fluid solders, solder rings, tape and preforms. The summary is available, free of charge, from Multicore Solders Ltd., Hemel Hempstead, Herts.

KABI TERMINAL BLOCKS

A LEAFLET describing an interesting range of terminal blocks is available from Precision Components (Barnet) Ltd., 13, Byng Road, Barnet, Herts. These blocks range from 2-way to 12-way and are capable of carrying currents up to 30 amps. The mouldings are in phenolic material and the insets and screws are of nickel-plated brass.

HOMELAB INSTRUMENTS

SIGNAL General Type 10, a Checktest and a calibrated variable condenser are described in the latest Homelab leaflet. The Checktest is a collection of resistors and capacitors with a socketed engraved panel by means of which it is possible to obtain over 400 combinations of parallel, series-parallel condensers or resistors or both. A wire-wound resistor calibrated 0-500 ohms and rated at 3 watts is included, as well as an 8 μ F electrolytic condenser for rapid and accurate substitution tests. Copies of the leaflet are available from Homelab Instruments Ltd., 617, High Road, Leyton, London, E.10.

TELEVISION PICK-UPS AND REFLECTIONS

UNDERNEATH THE DIPOLE



By Iconos

BIG SCREEN CORONATION TV

BIG screen television has been a practical proposition in this country for such a long time that M.P.s (and many of their constituents) seem to have taken it for granted. They assumed that the mere granting of permission by the Postmaster-General for public relays would result in the Coronation television being available in hundreds of cinemas, theatres and municipal halls. Readers of this journal are well acquainted with the technical details of big screen TV installations, and are not surprised that the costs of each equipment is in the neighbourhood of £10,000. Unless, therefore, a reasonably frequent service of suitable items is available, either from the BBC or by sponsored TV (or on "wired" TV), the large capital expenditure is scarcely justified.

TWENTY YEARS ON

UNTIL recently there has seemed to be little possibility of any special TV transmission frequencies being available for the cinema circuits or advertising sponsors. Over the last few years manufacturers of big screen TV in Britain have had little to encourage them to market their products and as a result American makers have been slowly catching them up, encouraged by the success of big screen TV for relaying American boxing and other big sporting events to large, paying audiences. The equipments have been expensive, but, in America, have turned out to be worth while. In Britain there have been very few installations made to date, but experimental big screen equipments have been fitted in a few cinemas in London and the provinces, one such installation being as far north as Doncaster. In London, Coronation big screen TV is likely to be available at the Odcon, Leicester Square, and at cinemas in Hammersmith, Temple Fortune and Bromley. Other cinemas may also take part, and I shouldn't be surprised if one of the cinemas in the Victoria district takes part. It was at the Metropole Cinema in Victoria on Derby day, 1932, that the first big-screen relay took place of the finish of the great race—and a packed audience watched Tom Walls's horse, April the Fifth,

romp home to win. That was in the days, long before high-definition television, on the old Baird mechanical system.

"THE GAY LORD QUEX"

THE more I see of television plays the more I am convinced that the most effective technique is that which imitates as little as possible the restless camera movement of the cinema. When the subject matter is taken from a stage play, such as Pinero's comedy, "The Gay Lord Quex," there is little excuse for constant cuts from camera to camera. Economy in camera cuts was the technique used by Royston Morley for his TV production of that play, and I must say that it put over most successfully the famous boudoir-bedroom scene, highlight of so many stage and film versions of this famous old play. At no time was one conscious of the camera, there was no frantic panning and tracking—in fact, the literally "creaking" camera track technique was conspicuous by its absence.


THEATRICAL KNIGHTS

THESE old plays—or some of them—make reasonably good television material, and have the advantage that many of them are free of copyright—known, I believe, as "in the public domain." I am told that the copyright exists until 50 years after the death of the writer, hence the interest of the BBC play producers in the stage plays which were produced in the 'nineties. That was the heyday of the actor managers—Herbert Tree, Cyril Maud, George Alexander, Henry Irving, Squire Bancroft and John Martin Harvey, all of whom received knighthoods. I suppose, in due course, we shall have a few knighthoods arising from television, if not from television plays. At any rate, these theatrical knights always selected plays which had "meaty" parts for themselves and their leading ladies. Some of the plays have "dated," but

Pinero, Henry Arthur Jones, Oscar Wilde, Sardon, Barrie and several others wrote many magnificent stage plays. Only when the plays took on a melodramatic vein have they failed to retain their appeal. The fact of the matter is that well-written dialogue, well delivered, was the essence of a play in the days when actors took pride in the audience hearing every word. Too often, these days, lines are lost through slurry, slipshod diction. In the old days the villain of the melodrama, when he saw the game was up, wrung his hands, gritted his teeth and hissed out "Foiled!". In this day and age, he shrugs his shoulders, offers the detective a cigarette and coshes him without a word.

THE OLD SILENT FILMS

OPPPOSITION of the film trade to early showing of current film releases is understandable. The commercial life of an average film is at least three years, at which period it had "graduated" to the dignity of Sunday night showings. Sometimes, if the film is particularly good, it is re-issued again for general release—and in this case a film might have a revenue-earning life of five years. If the BBC are unable to obtain films newer than five years old, then they should take a leaf out of the book of the National Film Theatre, which is showing programmes of silent films dating up to 40 years old vintage. It seems that the full-blooded melodrama was then in the ascendant, and the lurid titles "The Road to Ruin," "Passions of Men," "Trapped By London Crooks" and "A Message From Mars" were typical top-liners of the pre-Kaiser's war era. If the stage melodramas of the 1900's don't click home on television, these old films should. I have seen "The Road to Ruin" and, aided with a remarkable piano accompaniment, I found it a highly interesting and amusing 50-minute entertainment. The dream of a very elderly undergraduate warns him of the perils of strong drink and gambling, and he passes through a series of adventures remotely reminiscent of Hogarth's "Rake's Progress." If the BBC shows any of these old silent pictures they should be run at the then correct speed—16 frames per second.

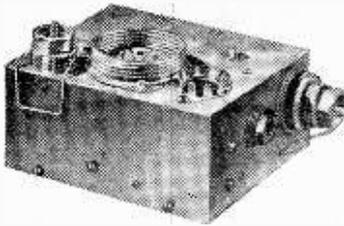

Boost that Signal

Pre-Amps. Ultra S.W. uses EF54s, with Coaxial Input and Output sockets. Power Supply input. Broad Band, Slug-tuned for use on T.V. Frequencies or 10 Metres (Valves to suit available.) 5/- each.

Chokes, smoothing, 20 H. at 60 m.a., 8/6 each. Chokes, 10 H. 60 m.a., Shrouded, 2/6 each. Chokes, L.T. smoothing, 5 ohms, 2/6 each. Twin Screened Cable, Heavy, 1/- yd. Single Screened Cable, Lightweight, 8d. yd. Belling Lee 5-pin Plugs and Sockets, 2/3 pr. Black Bakelite Moulded 4-pin plugs and Sockets, 1/- pr.

NORMAN H. FIELD
Dept. C3, 68, HURST ST., BIRMINGHAM

OPPORTUNITIES IN TELEVISION



Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.D. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS—NO FEE"
If you are earning less than £15 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

WRITE TODAY!

British Institute of Engineering Technology
237, Stratford House,
17-19, Stratford Place,
London, W.1. **BIET**

80 ohm COAX

STANDARD 1/4" diam.
Polythene insulated.
NOT EX GOV.
10d. per yd.
COAX PLUGS, 1/2 each
COAX SOCKETS, 1/2 each
COAX CONNECTORS, 1/2 each

WIDE ANGLE SCANNING.—Full Bruce Allen and Viewmaster Comp. In stock.

RESISTORS.—All Values: 1 w., 4d.; 1 w., 6d.; 1 w., 8d.; 2 w., 1s.

WIRE-WOUND RESISTORS.—Best makes. Minutaire Ceramic Type.—5 w., 15 ohm to 4 K.; 1.9; 10 w., 20 ohm to 6 K., 2.3; 15 w., 30 ohm, to 10 K., 2/9; 5 w. Vitreous, 12 K. to 25 K.; 3/-.

W.W. POTS.—Mini. T.V. Type Pre-Set. Fitted knob is knurled and shotted, 23, 50, 100, 200, 500 ohm, 1 K., 2 K., 3.3 K., 5 K., 10 K., 15 K., 20 K., 25 K. each 3/-.

COILS.—Wearite "P" type, 3/- each. Midget O-mur "Q" type, 4/- each. All ranges.

O.P. TRANSFORMERS.—Tapped small pentode. Universal. Mounting, 250 v., 400 v. or 500 v. L.F. chokes 10 h. 85 ma., 4/6. 20/25 h. 100/150 ma., 12/6. 5 h. 250 ma., 15/-.

MAINS TRANS.—Made in our own workshops to high grade specification. Fully inter-leaved and Impregnated. Standard mains Transformer. Universal. Mounting, 250 v., 400 v. or 500 v. 0-350 v. 80 ma., 6 v. 4 amp., 5 v. 2 amp. From 21/-.

Viewmaster, 35/-; Teiking, 30/-; 6.3 v. 11a. HTR Trans., 7/6. Specials or re-winds to own requirements.

CONDENSERS. new stock best makes.—600 mfd. 6 K.V. T.C.C., 5/6. Ditto, 12.5 K.V., 9/6. 002 Muirhead, 8 K.V., 2/6. .0001, .0003, .0005, .001 mfd., small mica, 6d., .001, .003, .01, .02 mfd. 450 v. Tub., and 1 mfd. 350 v. Tub., 9d., .005, 1 mfd. 450 v. Tub., 1s., .25, .5 mfd. 450 v., 1/9. .01 sprague 1,000 v. short ends, 8d.

VOL. CONTROLS.—Midget Ediswan type. All Values, 10 K. to 2 Meg. Long spindle. Guar. 1 yr. Less sw., 3/-; 8 P. sw., 4/-; D.P. sw., 4/6.

ELECTROLYTICS. ALL TYPES, NEW STOCK
8450 v. B.E.C. 2/6 8416/500 v. Dubilier 5/6
*8500 v. Dubilier 3/6 16/46/450 v. B.E.C. 5/6
848/450 v. B.E.C. 4/- 32/350 v. B.E.C. 4/-
16/450 v. B.E.C. 3/- *32/500 v. Dubilier 5/-
16/450 v. T.C.C. 3/6 *25/25 v. B.E.C. 1/9
16/350 v. Dubilier 3/- 50/50 v. B.E.C. 2/-
*16/500 v. Dubilier 4/- 60 mfd. 350 v. T.C.C. 6/6
8416/450 v. B.E.C. 5/- 250 mfd. 350 v. B.E.C. 8/6

*Ins. Tub. W/E. All others Can Type.

NEW BOXED VALVES GUARANTEED ALL

1R3 ... 9/-	6A17 ... 9/-	EF39 ... 9/-
1R5 ... 9/-	6V6 ... 9/6	6BE6 ... 10/6
1T4 ... 9/6	6X3 ... 9/6	EF50 ... 7/6
384 ... 9/6	Y30 (6U3) ... 9/6	6BA6 ... 10/8
5V4 ... 9/6	787 ... 9/6	EF91 ... 10/6
5Z4 ... 9/-	12K7 ... 10/6	EF92 ... 9/6
6B8 ... 7/6	12K8 ... 10/6	EY51 ... 12/6
6E4 ... 7/6	12Q7 ... 10/6	EY91 ... 8/6
6F6 ... 9/6	33L6 ... 10/8	KT11 ... 10/6
6H6 ... 6/6	33Z4 ... 10/8	MT14 ... 10/6
6H6 ... 3/6	50L6 ... 9/6	3D6 ... 2/6
6J7 ... 8/6	807 ... 10/6	12AX7 ... 10/6
6K4 ... 7/6	8A30 ... 2/-	12EN25 ... 8/6
6AM6 ... 10/6	EB34 ... 1/6	12Z2 ... 9/6
6BG6 ... 12/6	EB91 ... 8/6	6C06 ... 12/6
6K7 ... 6/6	EB33 ... 9/6	GAT6 ... 12/6
6K8 ... 10/6	EC91 ... 7/6	1A7 ... 10/6
6L6 ... 10/6	EC91 ... 12/6	6BA6 ... 9/6
6N7 ... 8/6	EF39 ... 7/6	EF50 ... 10/6
6Q7 ... 10/6	TP25 ... 9/6	1Y92 ... 10/6

SPECIAL PRICE PER SET:
1R3, 1T4, 1R5 and 384 22 6
6K8, 6K7, 6Q7, 6V6, 5Z4 40 6
10EF91 for Pract. Tele. A.C./D.C. TV ... 85/-

VIEWMASTER. Set 12 valves, 26/10/- With T.C.C. 27.
TEIKING.—Set 17 valves, 29 10s.


BARGAIN CORNER.
M'vete solder 60/40, 160., 5 6 1/2 lb.; 10/6 lb.; 4d. yd.; T.C., wire 18 to 22 s.w.g., per yd., 2d.; PVC Connecting wire, various colours. Single or stranded, 2d. yd. Twin (ang Midget 375 mmd.), 7/8; 1190s. semi midget, 6000 mfd. slightly soiled, 5/6. BTG Valveholder and Screening Can, 1/9. V-holders, octal, pax., 4d.; moulded, 6d.; EF50, BTG. HSA. B9A, 1/-; B12A, 1/3; 2 k. 5 w., heavy duty WW Pot. 1in. spindle, 4 6; new and boxed, 1 mfd. 500 v. Sprague and Micamould Tubular Cond., 8/6 doz.

P. and P. 6d. xl orders post free. Lists 5d.

T.R.S. -71, MEADVALE ROAD, EAST CROYDON

Callers: 307, WHITEHOUSE ROAD, WEST CROYDON. THO 1665

COMPACT T.V.

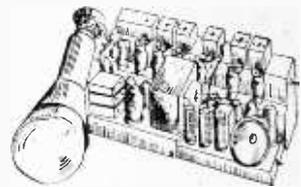

The now famous "New 1355 Conversion" enables you to construct a remarkably compact, self-contained television: Sound, Vision, Time bases, Speaker and power pack on one 1355 chassis—without the use of any expensive RF units.

Data for all five channels, 3/-.

We can supply 1355 receivers, in original makers' cases, complete with 11 valves, 45/-.

Loose stored, 35/-.

INDICATOR UNIT 182A containing VCR517 (6 in. C.R.T.), 4 SP61's, 3 EF50's, 5U4G, dozens of resistors, condensers, etc., 9 WW pots, these contain many of the additional components required for our conversion, or for 'Scope construction. 79 6 in original cases. We can supply a few, less EF50's and 5U4. 50/-.

RADIO EXCHANGE CO.

9 AOLDWELL STREET, BEDFORD
(Phone: 5568)

TELEVISION RECEIVER CONVERSION

The type AC/4 unit permits receivers to be used for reception of other channels without re-tuning or alterations.

Type AC/4KL (New Brighton transmitter or Kirk o'Shotts on London receiver).

Type AC/4WL (Wenvoe on a London receiver).

Type AC/4WB (Wenvoe on a Sutton Coldfield receiver).

Also available for all other conversions. The unit is complete with 5 valves and self-contained power supply unit. Price 15 gns. complete from your Dealer or C.O.D.

Type AC/3 neutralized triode PRE-AMPLIFIER without doubt the best Pre-amplifier available. Price complete, 10 gns. from your Dealer or C.O.D.

Illustrated leaflets, etc., on request.

SPENCER - WEST

Quay Works, Gt. Yarmouth
Phone: 3009. Telegrams: Spencer-West, Gt. Yarmouth.

FIRST-CLASS TELEVISION and RADIO COURSES . . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M.Bric.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc.**, together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER

150,000 SUCCESSES.

**NATIONAL INSTITUTE OF
ENGINEERING**
(Dept. 462), 148, HOLBORN,
LONDON, E.C.1.

Pre-Amplifier Transformer. Prim. 200/250 v., Sec. 230 v. at 30 mA., 6.3 v. at 1.5/2 amps., 23/-.

HS150. 350-0-350 at 150 mA. 6.3 v. 3 amps. C.T. 5 v. 3 amps. Half-shrouded, 30/9.

FS43. 425-0-425 at 200 mA., 6.3 v. 4 amps. C.T., 6.3 v. 4 amps. C.T., 5 v. 3 amps. Fully shrouded, 51/-.

F35X. 350-0-350 v. at 250 mA., 6.3 v. 6 amps., 4 v. 8 amps., 4 v. 3 amps., 0-2-6.3 v. 2 amps. Fully shrouded, 71/6.

FS160 X. 350-0-350 v. 160 mA., 6.3 v. 6 amps., 6.3 v. 3 amps., 5 v. 3 amps. Fully shrouded, 47/6.

FS43X. 425-0-425 v. 250 mA., 6.3 v. 6 amps., 6.3 v. 6 amps., 5 v. 3 amps. Fully shrouded, 69/-.

FS50. 450-0-450 v. 250 mA., 6.3 v. 4 amps. C.T. 6.3 v. 2 amps. C.T. 5 v. 3 amps. Fully shrouded, 75/-.

F36. 250-0-250 v. 100 mA., 6.3 v. C.T. 6 amps. 5 v. 3 amps. Fully shrouded, 32/6.

FS150X. 350-0-350 v. 150 mA. 6.3 v. 2 amps. C.T. 6.3 v. 2 amps. C.T. 5 v. 3 amps. Fully shrouded, 34/9.

F30X. 300-0-300 v. 80 mA., 6.3 v. 7 amps., 5 v. 2 amps. Framed, 31/9. The above have inputs of 200-250 v. C.W.O. (ADD 1/3 in £ for carriage.)

H. ASHWORTH

676, Great Horton Road, Bradford,
Yorks. Tel.: Bradford 71916

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.T.
SHEPHERD'S BUSH, LONDON, W.12.

Telephone: SHEPherd's Bush 1729

RECEIVERS TYPE R1155.—One of the best known and most popular of ex-Government communications receivers. In five switched bands the range covers 20, 40 and 80 metre "Ham" bands as well as the long and medium wave transmissions. Power requirements: 220 v. D.C. approx. at 50 mA for H.T. and 6.3 v. at 3 a. for L.T. Complete with their seven valves in used condition but in good working order. All receivers being aerial tested before despatch, with circuit diagram and data leaflet included. PRICE £6.17.6, carriage 7/6.

POWER PACK/OUTPUT STAGE UNIT.

—Designed to operate the R1155 direct from A.C. mains and to provide for a speaker output. Assembled in neat metal case employing 5Z4 rectifier and 6V8 output valves with built-in moving coil speaker. Plugs direct into receiver for immediate operation. PRICE £5.10.0, carriage 3/6.

POWER UNITS TYPE 87.—Rotary converter units for 24 v. D.C. input and having a twin D.C. output of 250 v. at 50 mA. and 6.5 v. at 2.5 A. Can be operated in reverse from D.C. mains or 6 v. accumulator. Totally enclosed in neat metal case 8 1/2 x 6 1/2 x 4 1/2 in. In good condition and working order. PRICE 9/6, post 2/6.

INDICATOR UNITS TYPE 6.—These units are fitted with a cathode ray tube type VCR37, suitable for scope or TV, 4 VR91's, 3 VR54's, mu-metal screen, wire-wound pots, H.V. condensers, resistors and many other useful components. We can supply data for scope conversion for 9/6 and "Inexpensive TV" for TV data for 2/6. Units are in good condition with C.R.T. TV picture tested to ensure freedom from cut-off. PRICE 65/-, carriage 6/6. (Data only. 3d. extra postage.)

"TYANA"

SOLDERING IRON 16/9

Reg. Design No. 867804

The Perfect Small Soldering Instrument

- Adjustable Bit. ● Easy to Handle. ● Weight approx. 4 ozs. Overall length 11" of the iron and diameter of the bit 3/16". ● Heating Time 3 min. ● 40 Watt economy Consumption. ● Standard Voltage Ranges (other Ratings Available on Request). ● Long Life and Efficiency.

- Replacement Elements and Bits always available. ● Just the Convenient Iron Required for Intricate and Fine Soldering.

Maintenance Service for Industrial users.

British made by :-

KENROY LIMITED

152/297, Upper Street, Islington, London, N.1.

Telephone: Canonbury 4905-4663

Vision and FRINGE AREAS!

..... Sound Strip

Of supreme interest to viewers in the difficult reception areas, this new Unitel product gives reliable reception with first class picture quality in districts where most other receivers function below par.

The superhet vision and sound receiver with triple R.F. amplifiers, can be bought individually like other Unitel products. Plug and socket connection enables anyone to assemble the units in sixty minutes.

The performance is outstanding; send for details to-day!

UNITEL ELECTRIC 18, Avenue Road, Belmont, Surrey.

TELEVISION CABINETS

FOR ALL HOME BUILT RECEIVERS. ANY SIZE SCREEN UP TO 17". FITTED WITH FULL LENGTH DOORS AND BEAUTIFULLY DESIGNED. ALSO RADIOGRAM & L.S. CABINETS.

WRITE OR PHONE FOR LEAFLET

H. ASHDOWN, 98, Hertford Rd., Edmonton, N.9.
Tel: TOT 2621



QUALITY TELEVISION COMPONENTS
SCANNING COILS
6/10 kV. R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS
LINE FLY-BACK E.H.T. UNITS

"TELEVISION CIRCUITS"

Fourth Edition, 96 pages, 3/6

HAYNES RADIO Ltd., Queensway, Enfield,
Middlesex.

YOUR Problems SOLVED

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p.486 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

"VIEW MASTER" VOLTAGE CHECKS

I thank you for your communication of the 12th ult. I have remedied the faults by carrying out your instructions. C.29 seemed to be causing most of the trouble on the sound channel.

I have one other fault with the line time-base, which is non-linear on the right side, causing my picture to be under-scanned by $\frac{1}{4}$ in. The left-hand side is reasonably good, falling short of full scan by less than $\frac{1}{4}$ in.

I have checked the voltage at the output of 14-A-86 MR.4, and it is 259 volts, the mains input voltage at that time being 230 volts. I have measured hoost volts across C.42 to be at 19 volts. I have tried increasing the drive to the line amplifier valve by decreasing R.46, but that did not remedy the fault. Adjustment of width and R.52 does not improve this condition.

Another point—my WB.103 mains heater transformer is, as you know, only tapped for 200, 220 and 240 volts input. I am on a 230-volt supply and am connected to the 240-volt tapping. Do you think this would have any detrimental effect on the operation of my television?

I might add I am situated close to a sub-station and my supply is constant 230 volts. I feel if I were to connect to the 220-volt tapping I should run a risk of overloading my equipment.—A. V. Badman (Bristol).

You are correct in using the 240-volt tapping on your W.B. transformer if your voltage is normally 230 volts. As you are only developing 19 volts across C.42 it would appear that there is a fault in this circuit and we suggest carrying out voltage measurements particularly at the screen G.2 of V.10. Also check wiring of L.14, R.52, C.43 and note whether by shorting out L.14 there is an appreciable increase in amplitude.

CATHODE-HEATER SHORT

In three and a-half years three tubes have gone faulty after approximately 12 months' use, the same fault developing with each tube. Perfect reception for a minute or so and then the picture flicks approximately $\frac{1}{4}$ in. to the left and smudged.

A light tap on the base of tube puts the matter right for a few seconds.

A separate transformer for tube heater stops the flick-over of picture, but gives the impression of a black smoke being blown across the picture.

With a 2 v. accumulator for heater the tube works absolutely satisfactorily.

In your opinion, could any fault on the set be the cause of this tube trouble, or is it just had luck with three tubes?—J. L. Perrie (Nr. Rotherham).

An intermittent heater-to-cathode short in the picture-tube is responsible for the effect. Usually the result is

uncontrollable brilliance, but since the receiver in question employs an isolated winding for supplying power to the heater of the picture-tube, the effect is manifested in the form of picture distortion: This is prompted by attenuation of the higher video frequencies owing to the capacitive effects of the heater winding.

The use of a separate heater transformer—unless a special low capacitance component—yields little assistance. With an accumulator, however, the losses are minimised and good definition results.

The heater voltage and cathode to heater potential on the picture-tube should be checked to make sure that the manufacturer's ratings are not being exceeded.

E.H.T. TRANSFORMER CONNECTIONS

I bought an E.H.T. transformer and there were two secondary leads, one black denoting 0 volts and one red lead denoting +1,000 volts, the black lead being earthed to the transformer.

If I wish to obtain -1,000 volts for a cathode-ray tube, do I connect the +1,000 volts red lead to the E.H.T. rectifier cathode and use the anode as -1,000 volts, leaving the 0 volt black lead earthed, or do I unearth the 0 volt black lead, connect it to the E.H.T. rectifier cathode using the anode as -1,000 volts, and earthing the +1,000 volts red lead?—A. Van Hoof (Blackburn).

It is necessary to apply a positive potential (relative to cathode) to the anode of a cathode-ray tube under any condition. An earthed positive potential for the final anode relative to -1,000 volts at the cathode is normal C.R.O. practice.

In this case, the black secondary wire must be disconnected from the transformer earthing tag, and connected to the negative end of the potentiometer chain which produces the various control potentials. The red wire should be connected to the anode of the rectifier, the cathode of which should be taken to the positive end of the potentiometer network, which should also be earthed.

INTERFERENCE

My receiver was installed three months ago and, I must add, the quality of picture received, when viewing is possible, has been excellent.

Unfortunately, we are on D.C. mains and during a programme five or six 1 in. lines appear on the screen, blotting out the picture.

The G.P.O. has been working trying to find the trouble for several months without success.

The same interference is also being experienced by fifteen other viewers in the same area using different models.

Can you suggest anything to reduce this interference? I have tried, without success, an advertised mains filter—two chokes, decoupled by condensers.—G. W. Hunt (Milford Haven).

From your remarks it appears that interference is arriving at your receiver through the aerial system—mains-borne interference should be minimised by the inclusion of the filter. But since you have not commented on the type of interference—impulsive or R.F.—it is difficult to make suggestions.

Aerial repositioning may help to reduce the magnitude of interference, and give a rough indication of its direction, but the only successful way to obtain complete elimination is by adequate suppression at the source.

D.C. IN SCANNING COILS

In my home-built "Practical Television" receiver, a fault developed in the line scanning circuit which was

located as a short circuit in the line scanning coils. I am using a 12in. C.R. tube at 7 kv. E.H.T.

After asking your advice I decided to change the circuit to that shown in Haynes Technical Publication No. 38 circuit 23 with transformer output but without V3 the efficiency diode. The best results I have been able to get give a raster that is pulled to the left-hand side of the tube, leaving a space of about 2in. on the right-hand side.

No adjustments to the controls will improve the position and I should be grateful if you could advise me what to do.—O. L. Keys (Chester).

You have D.C. in the line coils, which is pulling the raster to one side. Connect a 1 μ F condenser in series with one of the scan coil leads to see if this corrects the matter. You do not state whether you have tried centring the raster with the focusing magnet. This may be severely displaced.

R.F. INTERFERENCE

I have a table model which has given good service since purchasing a year ago, but which has now developed a kind of curtain or grille of black diagonal lines in front of picture, which behind this is good.

By altering the oscillator unit underneath set we almost get rid of them, but the sound goes and the car interference marks become blobs and noisier.

It does occasionally fade out, but only for a matter of seconds and then returns. I had a new E.H.T. fitted a week ago.—E. Ripley (Sedgefield).

The acceptance of radio-frequency interference by the vision channel of the receiver is the most likely cause of the effects. This may be a spurious signal on the same frequency as the vision signal, and can usually be proved by finding out whether other viewers situated nearby are experiencing the same trouble. On the other hand, the interference may be gaining admittance to the receiver via its second channel. In this connection local mobile transmitting services often produce pattern manifestations of the kind you describe.

A quarter-wave stub cut for 90° Mc/s. frequently assists in minimising second channel pick-up. Faulty tuned circuit alignment is prone to give rise to similar effects, but in this case the patterns do not tend to fade.

CIRCULAR AERIAL

I cannot use an outdoor aerial on my TV set, as the only place to put it has overhead cables running very close. I have no attic to use an indoor type.

At present I am using a "Vee'd" piece of flex on the wall, but it is unsightly.

Can I make an aerial with two rods bent into a circle, mounted on swivels for direction, to place on top of the TV? If so, can you tell me the sizes and distances, etc., for it? I am 14 miles from Sutton Coldfield's transmitter and in a very good reception area.

If this type of aerial is not possible, can you suggest anything that I can fit into a room?—Walter Holston (Cannock).

If you make up an aerial of two rods bent into the form of a circle, these should each be about 6ft. in length, the cable connecting in at the bottom of the O, and a small gap being left between the ends at the top. For strength this can be bridged with an insulator. A reasonable signal should be picked up on this arrangement when the aerial O is broadside to the transmitter.

The diameter of the circle will be only a matter of some 4ft. Alternately, a compressed-type dipole can be bought from Messrs. Aerialite which is designed for mounting in small spaces.

LINE LINEARITY

Will you please help me to cure this fault on my home-made television?

The picture is too wide, the left-hand side being behind the mask while the right side just reaches the mask. By reducing the width a black border appears on the right-hand side and any adjustment of the focus magnet only makes matters worse.

I found by accident that by reversing the line connections on the scanning coil this fault was corrected but, of course, the picture was reversed.

Will you also advise me which is the correct position for the ion trap? I have it set for the brightest picture but find that by altering the position of the focus magnet the ion trap must also be altered.—H. Newton (Co. Durham).

A non-linear current change through the line scanning coils is the cause of this common fault. Most receivers—home-constructed and commercial—incorporate a horizontal linearity control, which functions by altering the width of the left-hand side of the picture relative to the right-hand side.

Unless your receiver is so featured obtaining correct linearity will be extremely difficult. Various methods are in current use, but as no mention is made of the type of receiver built little advice can be given.

The ion-trap magnet should be positioned for maximum picture brightness.

FRAME LOCK

I am having trouble with a commercial model which although giving a reasonably steady picture for some time has now developed a frame-slipping antic.

It slowly revolves upwards and, although the speed can be controlled and direction reversed by operation of frame-hold knob, it will not "lock".

By adjusting carefully I think I have achieved this, but after standing still for a minute or two the "flyback" lines appear and slowly the picture slips upwards and continues to do so.

All valves associated with sync separation and frame have been changed but with no improvement.—George Booth (Bradford).

An unsatisfactory frame lock on this receiver is sometimes brought about by a reduction in efficiency of the small rectifier which is shunted by a 2.2 megohm resistor, and located between the anode circuit of the sync separator valve and the pink connecting wire on the frame blocking oscillator transformer. A 0.047 μ F capacitor is also connected in this circuit, which can develop a D.C. leak and give rise to similar trouble.

A substitution test is desirable in this circuit ensuring, of course, that the replacement components are in good condition.

QUERIES COUPON

This Coupon is available until March 18th, 1953, and must accompany all Queries.

PRACTICAL TELEVISION, March, 1953.

VIEWMASTER Valves, complete set of 12, £6/2/6; EY51, 9/-; EF91, 8/6; EB91, 7/6; EBC33, 8/6; 6K7G, 4 for 16/6; SP61, 4 for 19/6; 6V6G, 4 for 30/-; 1T4, 1S4, 1S5, 1R5, 3S4, 3V4, 4 any type, 31/-; V/Conrks, all valves, 3/-; SP/sw, 4/3; Coilpacks, 3-waves, 27/6; Rola 10in. P.M. with trans., 31/6. New list, stamp. WINWOOD, 12, Carnarvon Rd., London, E.10. (Mail only.)

TELEVISION and Radio Valves; guar. brand new, EY51, EF91, EF80, EF50, 185BT, 9/6 each; ECH35, CCH35, PL38, EL38, EL33, PZ30, HVR2, KT33c, PL33, 13 - each; 8D3, 6K7, 6J7, 6K6, EL32, EF39, 6C5, 6C6, 6D6, 6N7, 6SK7, 6SS7, 6V5, 757, 9D6, SP61, D63, all at 6/3 each; CV137, SP135, CV139, CV139, CV136, 4 any type, 22/-; 6CD6, 9/-; 12K7, 12K8, 12Q7, 35L6, 25L6, 35Z4 6SN7, 6V6M, 6V6G, 6Q7, 80, 50L6, 42, CL33, U50, U14, 6J6, all at 9/3 each. "Viewmaster" set of 12, as specified, £6/2 6". "Viewmaster" Coils, complete set, with choke, 17/6. New Valve Component list, stamp please. RADIO UNLIMITED, Elm Rd., London, E.17. (Telephone: KEY. 4813.)

GUARANTEED VALVES: 6K8G 25Z4G, KT61, CL33, PL33, 11/6; 6Q7GT, 6V6GT, 12Q7GT, 12AT7, 12K7GT, 10/-; 5U4G, 80T, 6SN7GT, 6SL7GT, 10/-; 5Z4G, MU14, VU39, 12K8, 50L6GT, 35L6GT, 9/6; 7C5, VP133, VR55, 6U5G, 6X5GT, 8/-; 6C6, 0Z4, 12SH7, 12A6, 1A5, 7/-; 6K7G, 12J5GT, 1LN5, 9D2, VR53, VR56, 6/-; Special offer: 4 6J5GT, or 3D6, or 15/-, postage, 6d. Send 2jd stamp for full list of Components. ELECTRO-SERVICES & CO., 28, Ethelburga St., S.W.11. (Phone: Battersea 2964.)

50 SECONDHAND Televisions always for sale; famous makes. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR. 5497.)

IF YOU REPAIR T/V SETS, send 3d. stamps for our Spares Manual. DIRECT T/V REPLACEMENTS, Dept. P.W., 134-136, Lewisham Way, New Cross, S.E.14. (TIDeway 3696.)

EXPERIMENTER has quantity of apparatus for disposal: IF strip 194 with valves £1/15/-; RP26, £1/15/-; RF25, modified Sutton Sound, £1/5/-; EF50's, 6/- each. No callers. Apply PEPPER, Bibury Rd., Birmingham, 28.

BY RETURN of post. Cream Masks, 12in. 2/6, 9in. 1/6; Scanning Coils by Scanco, Hi Imp. frame 24/6; Mains Trans. WB 103 42/-; 36 EHT 100 kvv Rects., 28/-; P.M. Focus Magnets, R/17, 22/6; Rubber Grommets, 1/6 dz.; Self Tap Screws, 2, 4, 6 BA, assd. lngth., 9d. dz. Few only brand new R/G Chassis, 5v AW, S/Het., complete with valves and 8in. energised spkr., 9 x 5 coloured scale and escutchion, L. and P. Car Battery Chargers, 6/12v, 5/-; Terms, c.v. 9. GSAT, 26, Nightingale Rd., London, N.9. (How. 2527.)

BELFAST'S leading Radio and Television Store offers the following Valve bargains—6AK5, 9/6 each, 3 for 27/-; 6K8, 9/6 each, 3 for 26/-; 6AG5, 6/6 each, 3 for 16/6; 807, 8/6 each, 3 for 24/6; 6L7M, 6/6 each, 3 for 16/6; 6N7M, 6/6 each, 3 for 16/6; 6SF5, 7/6 each, 3 for 21/-; EA50, 2/- each, 3 for 5/-; 3A4, 4/-; 185BT, 12/6; CV286, CV287 (BT stabilisers), 12/6; GS16, GS46 (P.E. Cells), 22/6; 1T4, 7/6; 3Q4, 8/6; GSAT, 8/6; 12SG7, 4/-; 6J6, 12AT7, 10/6. Please add 9d. postage on orders under £2. Send for full valve list. Television components. Full range of components and valves stocked for the "Tele-king," "Viewmaster," "Argus" etc. ELECTRAD RADIO, 69, High St., Belfast, N.I.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines, Box No. 1 - extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

"VIEWMASTER" Valves, exact to specification, guaranteed new and boxed, comprising 5 EF50, 1 6P25, 1 KT61, 1 EBC33, 1 EB91, 2 6K25, 1 6P28, set of 12 £6/2/6 (post and insurance 2/-); "Tele-King" 16in. Receiver, complete set of 17 valves exact to specification, £9/19/6; 6AM6, EF91, 6P12, Z77, 8D3, W77, EF92, 7/9; EB91, 6AL5, 6/9; 6V6G, 6P6, 5Z4G, EBC33, MU14, U22, DH77, 6A16, Pen 46, 1S5, 1R5, 1T4, 3V4, 3S4, 1S4, 8/6; PZ30, PL38, EL38, 17/6; EF51, ECC91, EP42, DK32, 1ATG, UB80, PL81, PL43, U37, R16, 10P1, 20L1, 6F15, 6C9, 12/-; UAF42, 6K8GT, CL33, PL33, PL82, 10F9, 10P13, 11/-; UL41, UBC41, UCH42, EL41, EP41, EZ40, KT61, PY80, PY82, 12AT7, 10/6; 6J6, UY41, UP41, U404, ECH42, DL35, 1C3G, DAC32, 1HS6, 10/-; ECL80, EF80, KTW61, 6SN7GT, 6SL7GT, 6Q7GT, 12Q7GT, 12K7GT, 12K8GT, 9/6; U50, 5Y3G, U78, 80, 25L6GT, 35L6GT, 50L6GT, 35Z4G, 6V6GT, 9/-; EF39, EF8, EF50, 7C5, 7C6, 7E7, 7H7, 757, 7Y4, 7/6; HVR2A, 6K7G, 6/3. All new and boxed; postage 4d. per valve extra. READERS RADIO, 24, Colberg Place, Stamford Hill, London, N.16.

SPARES, Aerial, VCR97, EHT-Trans., etc. PORTER, 25, Mannville Grove, Keighley, Yorks.

COMPONENTS. Our 1953 Catalogue is now available giving full details of our comprehensive range of components. WATTS RADIO, 8, Baker St., Weybridge, Surrey.

COMPLETE VIEW MASTER SERVICE

ALL MODELS ALL AREAS

PRICES. We can save you up to £7 on your View Master. Our very detailed list gives full particulars. Send for your copy now.

SPECIAL OFFERS. Resistor Kit. Every resistor labelled with value and position in set. Please note that no knowledge of the colour code is required with our kit. London, 26/-; Midland, 24/9.

PAYMENT. Cash or C.O.D. H.P. Terms now available.

DELIVERY. All orders are despatched on day of receipt.

INSTRUCTION BOOKS. Any model 7/6 post free.

Watts Radio (Weybridge) Ltd.
8 BAKER STREET, WEYBRIDGE, SURREY. Telephone: Weybridge 2542

S.E. LONDON CONSTRUCTORS
We hold good stocks of new and guaranteed
COMPONENTS AND VALVES
Rewinds, loudspeaker repairs, communication and TV. receiver alignment, etc.
GLYNDON RADIO SERVICE,
68, Wellington St., Woolwich.
WOO 2749.

SERVIO'S NEW CHASSIS SERVICE. Have your chassis made, in all. to your own specifications, cheaper than a ready-made one, e.g., chassis 9 x 5 x 2 1/2in. costs 3/9, normal mfrs. price 7/3. Details: One side any length up to 17in., the other side any length from 4in. to 12in.; depth any size up to 3in.; price 1d. per sq. in. of top surface, ignoring depth, e.g., chassis 10 x 7 x 2 1/2in. = 10 x 7 = 70 sq. in. = 70d. = 5/10. New EHT valve bases for HVR2, VU111, etc., 6d. New amphenol octal bases (int.), 6d. A new book on TV servicing giving actual cets. of 6 mfrs., incl. projection TV, 5/-. Write for our free lists offering valves as free gifts. **SERVIO RADIO,** 156/8, Merton Rd., Wimbledon, S.W.19. (Phone: LIB. 6525.)

SULPLUS 465 kcs iron dust cored aligned and sealed IFTs (marked red, green, yellow, black), perfect + twin 500 per gang condenser, 6/-, post 1/-; American and British resistance boards, 27b, 27c, 27d, 27e, post 1/-. New list of radio bargains (incl. valves) available, s.a.e. **THE RADIO SERVICES,** Lr. Bullingham, Hereford.

VIEWMASTER KITS, new specified parts, less speaker, focus ring, £24/10/-; assembled, £28. **BETTS,** 53, Mirfield Grove, Hull.

GUARANTEED new, 6AM6 8/-, EB91 6/6, EF92 6/3; reg. post 1/-. **MARTIN,** 42, Glengarry Rd., London, S.E.22.

PREMIER Electrostatic TV; working order; polished Console cabinet, built-in magnifier, 22, Pine Rd., Todmorden, Lancs.

BARGAINS. -Auto-trans., 50 cycle, 0-10-230v., 312 V.A., 17/6; I.F.T.s., canned, new, 10/13 each, 1/6; R1355 type (7 mcs), 1/6; diode type 2/-; Generators, hand-driven, geared, 300v and 28v outputs, 9/-; Dynamos, 6v to 250v (soiled), 8/6; R1355, cpte., 35/- (carr. 6/-); RF24 21/-, RF25 25/-, RF27 45/- (2/- carr.); RF monitors with 2/VR91, 1/VR92, 14/-; Power Units, 50 cycle. Outputs 300v 40ma and 12v 3a. DC, 50/-; 1 each 5U4G, 6V6G, VU120, 2/02 8kv. conds. and choke, 3 H 200ma 2V91, Indicators with VCR97, 3 each VR19, VR65, VR54, 2/VR92, 65/- (carr. 5/-), less valves and CRT, 17/6 (carr. 5/-). Stock list and enquiries, s.a.e., please. Terms: C.W.O.; immediate delivery; post extra. W. A. BENSON, 308, Rathbone Rd., Liverpool, 13.

NEW VALVES WANTED, small or large quantities. 3Q4, 6V6, 5Z4, ECL80, EF80, KT66, KT61, 6L6N, VR150, 30, 5R4, 80, etc., etc. Prompt cash. - WM. CARVIS, 103, North Street, Leeds, 7.

EDUCATIONAL

I.P.R.E. Data for constructing TV Aerial-strength Meter, 7/6; 5,500 Alignment Peaks for superhets, 5/9; sample copy "Practical Radio Engineer", 2/-. Membership-examination particulars, 1/-. Syllabus of seven postal courses free and post free. **SECRETARY,** I.P.R.E., 20, Fairfield Rd., London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby enthusiast or for those aiming at the A.M. Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other Professional examinations. Train with the College operated by Britain's largest Electronic organization. Moderate fees. Write to **E.M.I. INSTITUTES,** Postal Division, Dept. PI28, 43, Grove Park Rd., London, W.4. (Associated with H.M.V.)

TECHNICAL BOOK SERVICE

for the Radio Industry



For all your technical books and periodicals you need go no further than the nearest shop or bookstall of W.H.S. Whilst it is not practicable to maintain a big stock of such books at every branch—the Daily Supply Service from Head Office will quickly deliver the books you want to your local branch. We will gladly supply lists of the standard works on any subject and welcome inquiries from students and librarians.

★ Our Postal Service can send technical books and periodicals to any address at Home or Overseas.

W. H. Smith & Son

TECHNICAL BOOK SERVICE

HEAD OFFICE: STRAND HOUSE, LONDON, W.C.2

E.H.T. TRANSFORMER 7/6

(Ex-Government 500 cps.)

2.5 KV — 3.5KV

By putting condenser in series with input and 50 cps mains, secondary gives 2.5 Kv.-3.5 Kv. dependent on the condenser capacitance—2 mfd.—2.5 Kv. 4 mfd.—3.5 Kv. Secondary short does no damage.

New Guaranteed Perfect Transformed

Receiver 161. Chassis. 4 EF50 Valveholders, Electro-Mechanical Selector Switch, 4-position Coil Turret, Valve line-up: 1 CV66, 2 EF54, 1 EC52.

Less Valves, 4/6 each.
Condensers (small), 8 mfd. 500 volt. New. W.E. 2/6.
Torch and Panel Bulbs. 3.5 or 2.5 Volt, 2/- dozen. New.

VALVES

EF50	5/-	EF50 RED	6SK7M	5/-	VU39	9/-
6V6	10/-	(SYL)	954	4/-	KT44	8/6
6K8	12/6	6SH7M	VU111	3/6	6AC7	8/-
KT66	12/6	955	9001	5/6	EB34	2/-
HL2K	3/6	VUI33	ECC31	8/-	EF36	4/6
SG215	3/-	807 (U.S.A.)	SP41	2/6	PEN46	5/-
1625	7/-		8/6	8/6	PEN220	3/6
EL50	7/6	ECC32	EBC33	8/6	1T4	7/6
EA50	2/-	2/6	12F32	7/-	5Z3	7/6
D1	2/-	6J5M	6K7	6/-	VT104	9/-
			956	5/-	50L6	9/-

All Type Valves Stocked. Transmitter, etc.

VINER

24-26, EAST ST., MIDDLESBROUGH

Tel.: (Mid) 3418

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,
IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:

36, ROSEBERY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester, Birmingham.

"No Quantity too Small"

TRANSFORMERS

FOR ALL PURPOSES

SINGLY OR IN QUANTITIES FROM OUR STANDARD RANGE OR TO YOUR SPECIFICATIONS

GOOD DELIVERIES REASONABLE PRICES

We have also a department for rewinds giving you a 24-hour service and a better job. Please label all burnt-outs with your name and address when despatching.

P. HOWORTH

(Dept. P.T.)

51, FOLLARD LANE, BRADFORD

Tel.: 37030

Cinesmith Television of Quality

* DE LUXE T.V. CHASSIS *

* FACTORY-BUILT. * SUPERHET. * B.V.A. VALVES. * ALUMINIZED TUBE. (G.E.C.). * ANY FREQUENCY. * DEFINITION. GRADUATION. FOCUS. BANDWIDTH. UNSURPASSED. * GTD. 12 MONTHS.

* 12" or 15" Prices from £54 *

Chassis absolutely complete ready for fixing into your own furniture or cabinet. Also supplied in handsome table or console cabinets of Walnut Veneer. S.A.E. please for details of 6 models.

CINESMITH PRODUCTS

EST. 1932. BRITANNIC WORKS, Regent St. BARNSELY. Phone 4445

RADIO C200 ANNOUNCES

VALVES, at 2/9: RK34/2C34, VR78, D1, 7193, 954, 2X2, 879. At 4/6: 12H6, 4D1, VU111, GDT4C, NGT1. At 5/6: 12SH7, SP41, VT51/KT2. At 6/9: 6J7gt, 6S7G, 6U5G, 125C7, 125K7, EC52, EF54, VR136, U78, 125L7, CV73. At 7/9: 757, 1619, OZ4, 6AG5, 2A3, 6SK7gt. At 8/6: 7C5, 7Y4, 7H7, PT25H, VT46, 7R7, 1T4, 3A4, 3Q4/N18, DH77, W77, 6AC7, KT44, 6K7gt, 25L6gt, 50L6gt, 6V6gt, 6K6G, KL35, 6C6, 6D6, 6X5gt, EL3. At 9/6: KT61, 1R5, 1S4, 1A5gt, 6B8gt, 6CH6, 5Z4G, 6SL7, 6SN7, 1S5, 3V4, 12AX7, 6B4G, 6G6G, EB91, D77, 6BA6, 6BE6, 6BW6, 50C5, 6AU6, 6BR7, 6X4, 6AM6, 5763. At 10/6: 12K8gt, 6K8gt, 6S07, KT66, 6Q7gt, X79, 6BG6, X76, Z77. At 12/6: 6I7, 8012, 801, 807, CV66, RL18, VS68, STV280/40. Viewmaster and Tele-King Components by return post.

ARTHUR HOILE,

55, Union St., Maidstone, Kent. Tel.: 2812

NUTS, BOLTS, SCREWS AND WASHERS

ALL CADMIUM PLATED

SET 305 (Size 2BA).—Assorted screws and bolts from 5/16in. to 1 1/2in. long, with plain hex. nuts, Pinacle nuts, double anchor nuts, lock washers and plain washers. All rust proof. Average Contents, 400 Pieces, 7/6, plus 11d. post.

SET 306 (Size 4BA).—Assorted screws and bolts from 2in. to 1 1/2in. long, with plain hex. nuts, Simmonds nuts, and plain washers. All rust proof. Average Contents 600 Pieces, 7/6, plus 11d. post.

SET 307 (Size 6BA). Assorted screws from 2in. to 1 1/2in. long, with plain hex. nuts, Simmonds nuts, shake proof washers and 1 plain washers. All rust proof. Average Contents 750 Pieces, 7/6, plus 11d. post. By post, air-freight or ship, anywhere in the world. Overseas post extra.

All sets well packed in compartmented boxes.

BERNARD F. WADE LTD.

ILKLEY, YORKS, ENGLAND

Tel.: Ilkley 1787

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH

CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE

(DEPT. B.)

72-76 Leather Lane, Holborn, E.C.1

Phone: HOLborn 4777

THE PRACTICAL TELEVISION REC

iii

		£	s.	d.
Haynes	Frame Feed Choke	LUS8F	1	3 0
	Line Feed Choke	LUS6L	18	6 6
	Frame Osc. Transformer	TQ135	18	6 0
	Line Osc. Transformer	TQ132	13	0 0
	Scanning Coil Unit	S9141	2	2 0
Hivolt	R.F. EHT Unit 7 Kv.	201	5	19 6
	P.M. Focus Unit	R177	1	8 6
Elac	Mains Transformer	RI30	5	3 6
	L.F. Choke	(C21)	1	19 0
Gardner	10in. Speaker 7,000Ω	S1012T	5	1 6
	Potentiometers 500Ω and 10kΩ		6	6 6
W.B.	Type A. 20 kΩ and 250kΩ		5	0 0
	50kΩ with switch. Variable		6	6 6
Colvern	500kΩ. Variable		5	0 0
	All Values of Erie 8 Resistors		5	8 0
Morganite	Complete set of labelled 1 watt Resistors		1	7 6
	Wirewound resistors		2	0 0
Eric	Formers and Cores	PP5920-5	1	0 0
	B.V.A. as specified at current prices		2	0 0
Aladdin	T'38 modifications in stock		1	0 0
Valves				
Haynes				

T.C.C.			
3PF	35PF	Ceramic	SMWM
	33PF		SMWM
	100PF		CM20N
	220PF		SMWM
	300PF		CM20N
	680PF		SM2N
	401µF		CM20N
	105µF		Type 2045
	42µF		Type 2045
	01µF		Type 346
	06µF		Type 343
	1µF		343
	25µF		343
	5µF		343
	Dubilier		4µF 500v.
8µF 500v.		BR850	4 0
16µF 500v.		BR/C1650	6 6
32µF 500v.		CT3250	10 0
30µF 12v.		BR501	2 6

J. T. FILMER Place these prices in your P.T.R. Booklet or send for latest P.T.R. List. **MAYPOLE ESTATE, BEXLEY, KENT.** Prompt Postal Service. Tel: Bexleyheath 7267

OAK, WALNUT & ORDINARY PLYWOOD CUT TO YOUR SIZES FOR CABINETS, etc.

We will **FREE** Leaflet on French Polishing send you & Plywood List for S.A.E.

We specialise in Plywood for Amateurs and gladly advise on Constructional Problems

THE DERWENT CRAFTS SHOP

BRIDGE GATE, DERBY

Keep this advertisement for future reference

AERIAL MASTS

Again we have been fortunate to secure a limited number of 1 1/2in. WOODEN MASTS, approx. 2in. dia. slight taper and ideal for television chimney masts, etc.

PRICE 7/6 EACH. Carriage 2/6 or IN TONS OF 4 OR OVER 6/- EACH, Carriage 3/-.
T.V. DIPOLE AERIALS. For all channels. Heavy Bakelite Insulator and 2in. dia. elements for inside or outside use. (Please state for which station when ordering.)
15/- EACH, PACKING AND CARRIAGE 2/6.
POLYETHYLENE DIPOLE INSULATORS fitted with 2in. dia. Brass stubs; with your own elements and a small amount of ingenuity a very highly efficient aerial system can be constructed.
PRICE 5/-. postage 1/6.

WALTON'S WIRELESS STORES
48, Stafford Street, WOLVERHAMPTON.
Send s.a.e. and 3d. for latest list.

TRANSFORMERS, 220-250 v. Primary 50 c/s.
A4377S. 5 v 1 amp., 6.3 v, 7 amps.; 6.3 v, 1 amp., auto winding, 300 v 250 m.a., 25-
A4516T1. 6.3 v 7 amps., 6.3 v 1 amp., auto winding, 300 v 250 m.a., 20-
A4867S. 5 v 2 amps., 6.3 v 7 amps., 6.3 v 1 amp., auto winding, 350 v 250 m.a., 27 6.
A4777T. 6.3 v 7 amps., 17 6.
A4814W. 6.3 v 5 amps., 6.3 v, tapped at 4 v 2 amp., 17 6.
A4814T. 6.3 v 3 amps., 300-0-300 80 m.a., 15-
P-123-61. 6.3 v 3 amps., 6.3 v 500 m.a., 250-0-250 100 m.a., 25/-
A4347S. 12 v 3 amps., C.T., 2 v 1.5 amps., 12 6.
A4259T. 6.3 v 3 amps., 5 v 2 amps., 350-0-350 150 m.a., 35/-
A4157W. 5v v tapped at 45, 75, 30, 25, 15 2 amps., 4 v 1 amp., 7 6.
A4479S. 48 v tapped at 37, 30, 24, 18, 13 2 amps., 4 v 1 amp., 7 6.
A4656S. 6.3 v 3 amps., 5 v 2 amps., 250-0-250 80 m.a., 16-
A4673S. 12 v 3 amps., 12 6.
A4840S. 350-0-350 300 m.a., 6.3 v tapped 4 v 2 amps.; 6.3 v tapped 5 v 3 amps.; 6.3 v 10 amps.; E.H.T. rect. fil. 2 v 2 amps.; E.H.T. 6.250 v 5 m.a., 45.
A1250. input 220-210, 220-230, 240-250, 4 v 12 amps., 4 v 4 amps., 4 v 2 amps. C.T., 350-0-350 300 m.a.; E.H.T. rect. fil. 2 v 2 amps.; E.H.T. 5,000 v 5 m.a., 44.
E.H.T.1, E.H.T. 5,000 v 5 m.a.; rect. fil. 2 v 2 amps., pri. 220-250 v, 50-
CHOKES, HEAVY DUTY.
5622B. 45Ω 250 m.a., 10 h., 8-, p. & p., 2 6; 4961S1. 12Ω, 200 m.a., 10 h., 8-, p. & p., 2 6; U25L. 125Ω 150 m.a., 8 h., 8-, p. & p., 2 6; U25S. 300Ω, 80 m.a., 10 h., 6 6; G62. 100Ω, 80 m.a., 5 h., 6-; GU5. 300Ω, 80 m.a., 10 h., 5-; 4073W. 300Ω, 60 m.a., 10 h., 4-; C178. 350Ω, 60 m.a., 10 h., 4-; C115. miniature choke, 200Ω, 60 ma., 6 h., 3 6; 60 m.a., 10 h., 4-; C115. miniature choke, 200Ω, 60 ma., 6 h., 3 6; T15. miniature mic. trans., 250-1, step up, 4-; A4653T. O.P. trans., 2.3 ohms, sec. 3 w., 3 9; KP7911. O.P. trans., 2.3 ohms, sec. 5 w., 4-; A4600R. P.P. O.P. trans., 2.3 ohms, sec. 6 w., 5-.

SCANNING YOKE for 35 m.m. neck tubes, line and frame winding, low imped., 12 6.
FOCUS COILS for 35 m.m. neck tubes, fully shrouded. High impedance (parallel), 22-; low impedance (series), 15-.
VIBRATOR TRANS., 12 v input, 300-0-300 O.P., 80 m.a., 7 6.
VIBRATOR TRANS., 12 I.P., 200-0-200 O.P., 60 m.a., 6-.
VIR. TRANS., M162, 6 v I.P., 150-0-150, O.P., 80 m.a., 6-.
Mail Order Terms, C.W.O. Where p. & p. charge is not stated please add 1/- up to 10/-; 1/6 up to £1; 2/- up to £2. Orders over £2 post free.

AUDIO LTD.

37, HILLSIDE, STONEBRIDGE, LONDON, N.W.10
SATS. 9-6 Phone: ELG. 3644

HANNEY of BATH offers:

STANDARD VIEWMASTER. Constructor's Envelope, 7 6. Complete kit with wire, sleeving, nuts and bolts, less Valves, Tube and Cabinet. GENUINE specified parts only. £31. In Easy Stages: ONE, 62 3; TWO, 62 9 (Wenoco, 39-); THREE, £5 1 3; FOUR, 9 10; FIVE, £10 4; SIX, £7 5 9; SEVEN, 67 8.
Individual Parts (any item sold separately): WB100 sound and vision chassis, 18 6; WB101, 6-; WB102, 18 6; WB103, 42-; WB104, 52 6; WB104 15 6; WB106, 25 6; WB107, 32 6; WB108, 33 3; WB109 1, 2 or 3 (state tube type), 22 6; WB110, 10-; WB111, 5 9; WB112 12in., 21 6; WB Console conversion kit, 35-; WB300 pre-arr. chassis, 17 6. Westinghouse Rectifiers, 14A86, 20 4; 14D36, 11 7; WX3 and WX6, 3 9 each; 36EH100, 20 5; 36EH150, 26 1; 36EH175, 23 8; S.T. & C. equivalents K3 100, 14 8; K3 50, 8 9; K3 45, 8 2; C.C. Condensers: London, £7 1 6; all others, £7 8 6. Any condenser supplied separately, prices as per Constructors Manual, except CP560Q, which is 6- Morganite pots, 5/- each; Fete pots, 4 6 each; Morganite resistor kits: London, 36-; other, 35 2. Resistor kits are also available in the latest type ERLE insulated ceramic tubes at the SAME PRICE. Colvern pots, kit, 22 6; or CLR 601, 3 3 each and CLR 4089 22, 6 4. Belling-Lee L707 connector, 8 9; fuses, 61, each. Wearite coilssets (with 1 1/2in. London, 22-; Wenoco, 28/- All other channels, 30-; Pre-amp. coils for all channels, 4- per pair.
TELEKING. Constructor's Envelope, 6-; Coilssets, 54 3; Complete chassis kit, 70-; T.C.C. condenser kit, £7 5; R.M. rectifier, 21-; Allen Wide Angle components: L10 308, 50-; FO 305, 21-; DC 300, 42-; FC 302, 85-; G7, in and GL 18, 10- each; BT 314, 15-; Se. 312, 22 6; AT 310, 30-; OP.117, 9-. Resistors and Pots, are detailed in our TK supplement.
MAGNAVIEW. Booklet available from Brimar Valves. Denco Coilssets, 41 2; Complete chassis sets, 37 6; Complete kit of Erie resistors, 39 2; Denco Wide Angle Components: WA/DCA1, 43-; WA/FCAl, 31-; WA/LC1, 7 6; WA/WA1, 7 6; WA/FMA1, 21-; WA/LT1, 42-; WA/FBT1, 42-; Condensers and pots, are detailed in our supplement.
ELAC MARK 2 Focus Rings (Thin Lens). R1, 30-; R2, 32 6; W2, 52 6; W25, 57 6.
1 1/2in. ITR and ITR, 5- each.
Please add 9d. postage on all orders over 10/-.
All C.O.D. orders under £5. Send for comprehensive lists now, which contain details of Receivers, recent P.F.W. designs and more.

L. F. W.
77, LOWER

