

SERVICING TV RECEIVERS

PRACTICAL TELEVISION

AND TELEVISION TIMES

A NEWNES PUBLICATION


Vol. 5 No. 49

JUNE, 1954

1/-

**EDITOR
F. J. CAMM**

A New

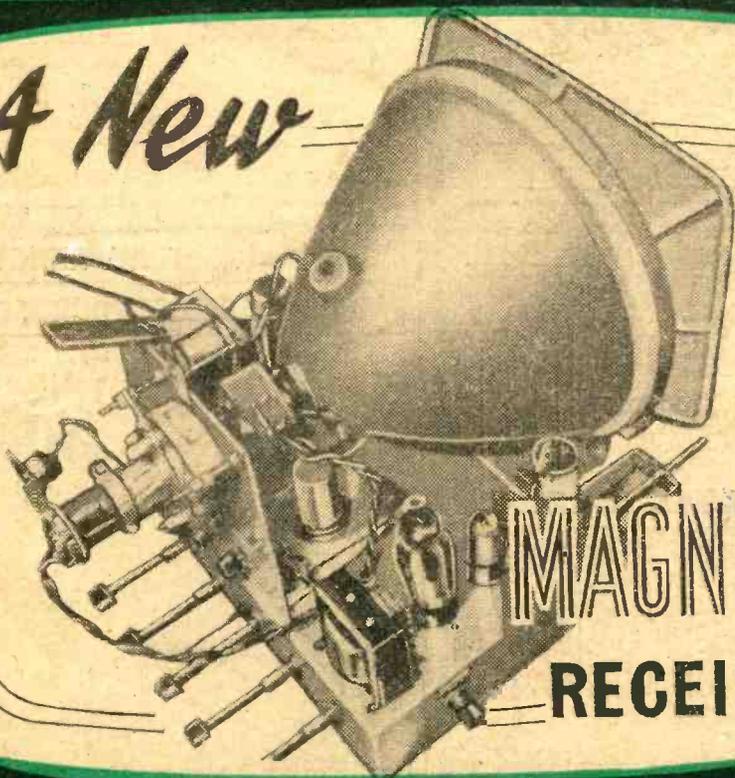


**MAGNETIC
RECEIVER**

FEATURED IN THIS ISSUE

Modifying the R3118
European 8-way Link-up
Pages from an Engineer's
Notebook

Fault Symptoms
A Simple Wobbulator
Problems Solved
News from all Quarters

TABLE TELEVISION CABINETS

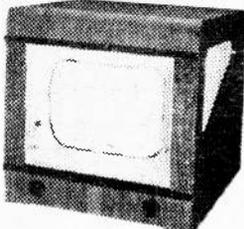

For 12in. and 14in. C.R. tubes. Beautifully finished in polished medium walnut veneer. Complete with mask glass, speaker-fret. Internal dimensions: 15in. wide, 16in. deep, 14in. high. **LASKY'S PRICE... 39/11** Carriage 7 6 extra. Also available in unpolished veneer. **LASKY'S PRICE... 19/11** Carriage 7 6 extra.

DE LUXE T.V. CABINETS—Console model, for 12, 14, 16 and 17 inch C.R. tubes. Finished in beautiful walnut veneer, with high polish. Either light, medium or dark shade. Inside dimensions: 16 1/2 in. deep, 17 in. wide, 24 in. high. Supplied complete with mask, glass, back, speaker baffle and fret. On castors for easy movement. **LASKY'S PRICE, £8.10.0.** Carriage 12 6 extra. State tube size when ordering.

AERIAL ROD SECTIONS. Steel heavily copper plated. Each rod is 1/4 in. diameter and 12in. long. Any number of rods can be fitted together. **LASKY'S PRICE... 2 6 per doz.**

TELEVISION CONSTRUCTOR'S PARCELS

No. 1. Brand new components by Igranite. Comprises E.H.T. line flyback transformer, 7-10 Kv output with ferroxcube core and rectifier heater winding; scanning coils; frame output transformer; Eiaa focus unit with vernier adjuster, U37 E.H.T. rectifier, 12in. mask and glass. **LASKY'S PRICE FOR THE COMPLETE PARCEL, 79 6.** Carriage 3 6 extra.

No. 2. **WIDE ANGLE CONSTRUCTOR'S PARCEL.** Comprises ferroxcube line E.H.T. transformer 9-16 Kv. output, with rectifier heater winding; scanning coils with ferroxcube core; P.M. focus magnet with ferroxcube core OR electro-magnetic focus coil; also frame transformer, linearity and width controls, frame blocking oscillator transformer. **LASKY'S PRICE FOR THE COMPLETE PARCEL, 95 11.** Carriage 3 6 extra.

No. 3. Complete set of metalwork. For 12in. chassis. Comprising main chassis, tube supports and valveholders (less sound-vision chassis). **PRICE, 25 -.** Carriage 3 6 extra.

No. 4. **RESISTANCES.** Half-Watt. 85 resistances your own choice. **PRICE 18 -.** POST FREE.

R.F. OSC. COIL KITS—Consisting of R.F. oscillator E.H.T. coil with EY51 heater winding, EY51 rectifier, 6V6 valve and base. All necessary condensers and resistances. Full circuit and data supplied. 6-9 Kv. **LASKY'S PRICE, 47 6** 9-15Kv. **LASKY'S PRICE, 53 6**

R.F. E.H.T. OSC. COILS—For use with 6V6 valve, and EY51. Circuit and full data supplied. 6-10Kv. **PRICE 19 6** 6-18Kv. **PRICE 25 -**

WESTINGHOUSE MINIATURE RECTIFIERS TYPE WX.6. **PRICE 16 each.**

TELEVISION SELENIUM RECTIFIERS—The very latest "Sentercell" S.T.C. range. K3 40, 3.2 kv 6- K3 45, 3.6 kv 8/2 K3 50, 4.0 kv 8 6 K3 100, 8.0 kv 14 8 K3 160, 12.8 kv 21 6


COLLARO 3-SPEED AUTOMATIC RECORD CHANGERS. Model 3RC 521 / With turn-over crystal head. **LASKY'S PRICE...£9.19.6** CARRIAGE FREE.

FLESSEY 3-SPEED RECORD CHANGERS. Complete with pick-up and crystal head. **LASKY'S PRICE...£9.19.6.** CARRIAGE FREE.

LASKY'S RADIO,

LASKY'S (HARROW ROAD), LTD.,
370, HARROW ROAD, PADDINGTON, LONDON, W.9.
Telephones: CUNningham 1979-7214.
Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs. half day, 1 p.m. Postage and packing charges (unless otherwise stated): on orders value £1-1s. 0d. extra; £5-2s. 0d. extra; £10-3s. 6d. extra; over £10 carriage free. All goods fully insured in transit.

CYCLON 5-CHANNEL SWITCHED TELETUNERS

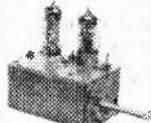

Instant and positive selection of any one of the 5 B.B.C. television channels, by a single control knob. Uses EF.80 R.F. pentode and ECC91 or 12AT7 Double Diode Triode as frequency changer. Tuning is obtained by switching incremental inductances. Size: 4 1/2 x 2 1/2 x 2 1/2 ins. Spindle 2 1/4 in. long, 1/4 in. diameter. I.F. Output 9.5-14 Mc. s. none figure on all channels; better than 10.5dB. I.F. rejection better than 45dB on all channels. Power gain 21dB. **LASKY'S PRICE... 12/6** Postage 2 6 extra.

BRIMISTONS. Type CZ3. **LASKY'S PRICE, 10/4.** each. 9 - per dozen.

CRYSTAL DIODES. Glass type, wire ends. **PRICE 1/6** each.

3-WATT MIDGET A.C. D.C. AMPLIFIER, PUSH PULL, VERY HIGH GAIN

4 valves: 2 U141 in push pull, 1 UCH12 and 1 UAF32. Input voltage 100 110 A.C. D.C. Very easily converted to 230 volts. Supplied with circuit diagram and full details. Size: 9 x 4 x 4 in. Uses 2 metal rectifiers, 1 each RM1 and RM2. Ideal for ships record players, tape recorders, home record players, baby alarms, etc., etc. Supplied complete, fully assembled and wired, with 4 valves, 69/6. Carriage 3 6.

Positively the 2 BEST T/Vs yet built for the Home Constructor!

The STERN'S "TELE-VIEWERS"

5 CHANNEL SUPERHET RECEIVERS

Suitable for any transmitting channel and for which commercial adaptors will be available.

PERFECT PICTURE QUALITY
SIMPLE DIAGRAMS MAKE CONSTRUCTION EASY

PERFECT FRINGE AREA RECEPTION
BETTER RECEPTION AT HALF COMMERCIAL COST

The "WIDE-ANGLE" TELE-VIEWER


* This is the most efficient large screen TV yet offered to constructors.

* Excellent Time Base efficiency producing 15 to 16 Kv with ample scanning power for C.R.T.'s up to 17 inch.


CAN BE COMPLETELY BUILT FOR

£33 - 0 - 0

(Plus cost of C.R.T.)

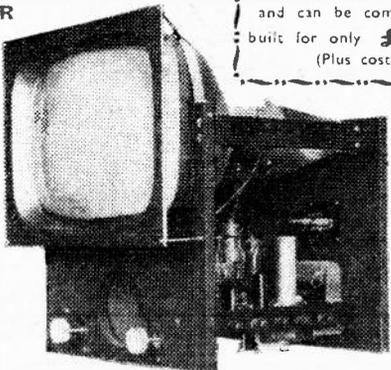

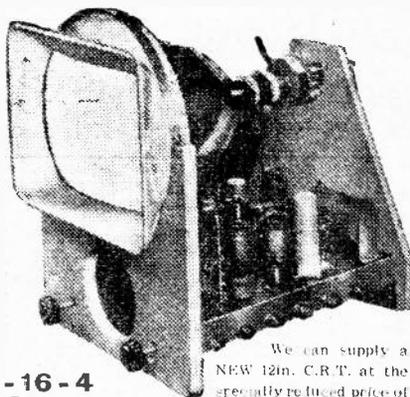This is the 12" **TELE-VIEWER** and can be completely built for only **£28 - 16 - 4** (Plus cost of C.R.T.)



We can supply a NEW 12in. C.R.T. at the specially reduced price of **£12.19.6.** Carr. & Ins. 15 - extra.

The complete set of **ASSEMBLY INSTRUCTIONS** for these T/Vs are available for 5 - each. They include really detailed **PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST.** ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. AN ATTRACTIVE TABLE MODEL CABINET FOR THE 12in. Model IS AVAILABLE FOR **£8.19.6.**

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4.

Tel.: CENTRAL 5812-3-4.

SOLDERING COSTS CAN BE CUT...

Wolf

BEST VALUE FOR MONEY!

★ **SOLDER TWICE AS FAST · AT FAR LESS COST!**

TRIGGER-FEED

SOLDERGUN


The Wolf Type 51 Soldergun with its trigger-feed action is indispensable to all modern assembly.

SOLDERGUNS

Off-straight easy-grip handle · Perfect balance · Solid construction · Low current consumption · Model for every purpose · Rapid constant heat.

SOLDERING IRONS

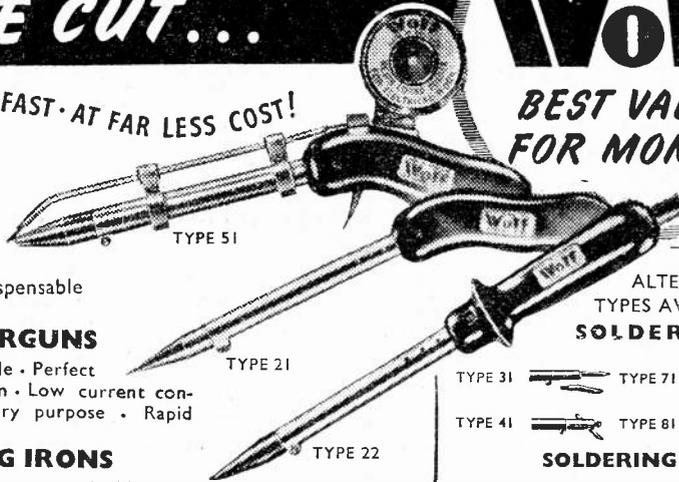Identical as regards elements and bits to Wolf Solderguns but with round hard wooden handle with heat-deflecting skirt.



ALTERNATIVE TYPES AVAILABLE
SOLDERGUNS



★ Obtainable at all high-class stockists and ironmongers

WOLF ELECTRIC SOLDERGUNS AND SOLDERING IRONS

WOLF ELECTRIC TOOLS LTD., PIONEER WORKS, HANGER LANE, LONDON, W.5 - TELEPHONE: PERIVALE 5631-4



Pointers for Designers


AND CONSTRUCTORS

NUMBER ELEVEN

VALVES FOR TAPE RECORDERS

INPUT STAGE Z729


(low noise pentode)

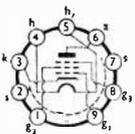

V_h 6.3V
 I_h 0.2A
 V_a 250V
 V_{g2} 140V
 g_m 1.85m/AV
 V_{hum} 1.5 μ V
 R_{g1-k} = 470 Ω
Base B9A


Tone correction and intermediate stages B309

double triode

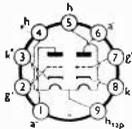


V_h 6.3V
 I_h 0.6A
 V_a 250V
 g_m 5.5 mA/V
 r_a 10 k Ω
Base B9A

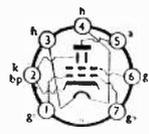Output and bias oscillator N727/6AQ5 or N78



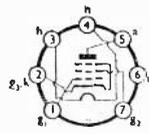
V_h 6.3V
 I_h 0.45A
 V_a 250V
 V_{g2} 250V
 I_k 50 mA
 V_{g1} -12.5V
 P_{out} 4.5W
Base B7G



V_h 6.3V
 I_h 0.64A
 V_a 250V
 V_{g2} 250V
 I_k 40 mA
 V_{g1} -5V
 P_{out} 4W
Base B7G

Rectifier U709

full-wave rectifier

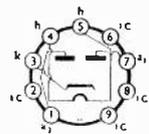

V_h 6.3V
 I_h 0.95A
 V_{h-k} 450V (max.)
 V_{in} 350 rms (max.)
 I_{out} 150 mA
Base B9A

The heater-cathode rating of the U709 permits operation from a common 6.3V heater winding

For further information and full technical data write to: The Osram Valve and Electronics Dept.
THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2

PRACTICAL TELEVISION

& "TELEVISION TIMES"

Editor: F. J. CAMM

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4383.
Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 5 No. 49

EVERY MONTH

JUNE, 1954

TelevIEWS

COLOUR TV ON TAPE

THE Radio Corporation of America recently disclosed that it has developed its own system of recording colour television on magnetic tape. The system records and reproduces pictures in black and white and in colour with no intermediate operations such as film processing. In fact, it eliminates all chemical processing. An official of the company said that the magnetic tape recording of TV signals should make possible a simple means by which TV set owners can make recordings of TV pictures in their own homes. Such recordings can, of course, be played over and over again like a gramophone disc. A demonstration of the system showed the colours in true as distinct from the usually exaggerated reds, blues and greens of the cinema.

The same company has also announced that colour TV sets will be on the market about six months after the Federal Communication Commission approves the new colour system. The method of recording TV on tape corresponds in general principle to that employed for recording sound on tape or wire.

Colour TV can now be received in 35 big cities in the U.S.A. and by the end of this year the range will have increased to take in about 125 TV stations, which will bring colour TV to 75 per cent. of the American population.

Other American experts have been considering the problem from another angle—the tube or screen. Experts at the National Convention of the Institute of Radio Engineers in New York dealt with this in detail. The General Electric Company of America made the suggestion that the TV industry should adopt a single standard electron gun to replace the three types at present being used in America.

AN ATOMIC BATTERY

FROM America also comes the announcement that it is now possible to convert atomic energy, directly and simply, into small but usable quantities of electrical energy sufficient to operate a transistor, by means of an atomic battery. This direct conversion of nuclear energy may prove to be as significant as Edison's con-

version of electricity to light. The battery recently demonstrated to the Press is powered by a minute quantity of long life strontium-90 radio-active isotope, obtained as a by-product of atomic reactor operation. This big stride has been achieved by coupling the battery's radio-active source to a transistor-like wafer which instantaneously releases about 200,000 electrons for each electron it receives.

This may prove to be the beginning of a new chapter in man's effort to utilise some of the enormous untapped energies within the nucleus of the atom for peaceful purposes rather than for the destruction of life. The atomic battery is likely to be applied first to portable and pocket-size radio receivers, hearing aids, signal control and similar devices.

Almost at the same time as the above announcements came the news that the Bell Laboratories have produced a "solar" battery. Made from strips of silicon, it is claimed that this battery is powered from energy radiated by the sun, and that it can deliver power at the rate of 50 watts a square yard of surface. This is approximately 50 million times the power of the atomic battery.


THE RADIO SHOW

SPACE for this year's national Radio Show, to be held at Earls Court from August 25th to September 4th, is already overbooked. The demand has been greater than at any time since the war and this suggests that competition in the radio and TV market is likely to be even more competitive. All of the large firms in radio and TV are among the exhibitors, and all three services are taking space. The BBC are to be allocated more space than ever before.

PRACTICAL TELEVISION and our sister journal *Practical Wireless* will of course, occupy a stand.

INDEXES FOR VOLUME 4

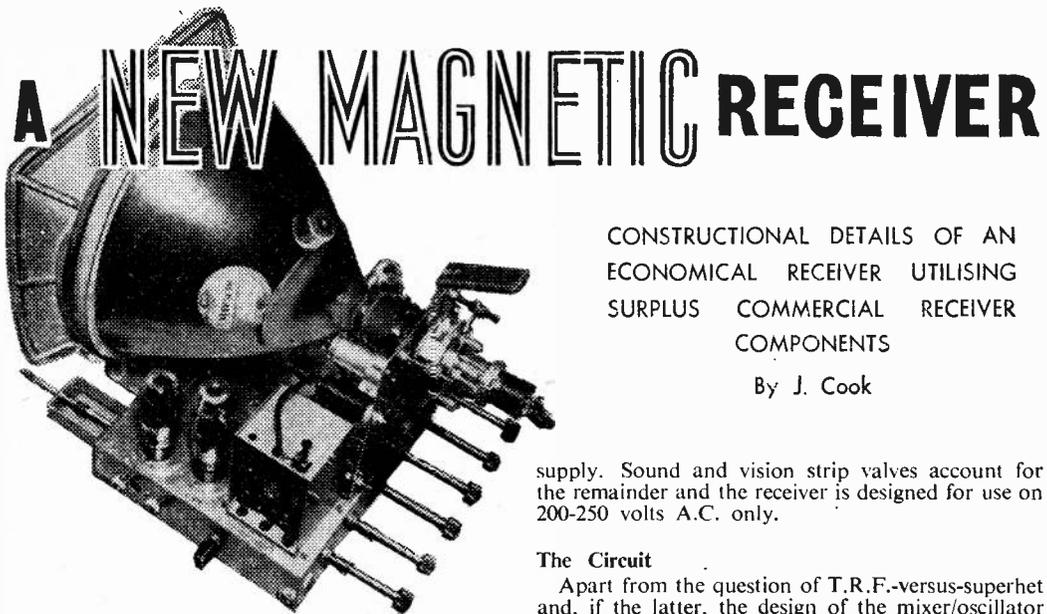INDEXES for Volume 4 are still available at 1s. 1d. each from our publishing department, address as above. Readers are advised, whether they have their copies bound or not, to obtain indexes so that they can rapidly trace articles and information published herein.—F. J. C.



CONSTRUCTIONAL DETAILS OF AN
ECONOMICAL RECEIVER UTILISING
SURPLUS COMMERCIAL RECEIVER
COMPONENTS

By J. Cook

THERE are at present being advertised in these pages 9in., 12in. and 15in. narrow angle tubes and a number of key components at very reasonable prices, and it is a set of these which has been incorporated into the following design. This is not primarily a constructional article, with precise wiring and dimensional instructions, but rather is it intended to take the design section by section and dissect each in turn to show how it functions. Apart from prospective constructors, it may be that some readers will find this description interesting as a design study because some of the features, e.g., the method of D.C. shift controls, may be incorporated into existing equipments—always provided, of course, that underlying principles are appreciated. The warning remarks which appeared in the Editorial of this magazine some months ago concerning the many pitfalls of mixing circuits are most heartily endorsed by the writer.

Balancing cost against desired performance usually means accepting sub-standard results, but whilst the endeavour of this design has been to simplicity and economy of components the receiver maintains a full frequency response, excellent interlace, linearity, etc. Modern circuit techniques are employed, but the older and more cheaply obtained B9G and octal based valves are used. Any C.R.T. with a scanning angle not much greater than 50 deg. may be used and will be fully scanned, with an inch or two to spare, with the E.H.T. of 7 to 8 kV. derived from the line output auto-transformer. Since this is accomplished without an efficiency diode, which is the normal practice, it will be appreciated that the line transformer is quite an efficient component. A further economy in this stage is effected by operating the line output valve as a self oscillator, thus saving at least one valve and several components. The C.R.T. illustrated is the ion-trap type Mullard MW31/16; the more current type being the MW31/74. This is a similar tube but with a grey filter face plate. The equipment uses eight valves for video, timebases and power

supply. Sound and vision strip valves account for the remainder and the receiver is designed for use on 200-250 volts A.C. only.

The Circuit

Apart from the question of T.R.F.-versus-superhet and, if the latter, the design of the mixer/oscillator combination, designs vary but little. Since many suitable vision and sound strips have been described in these pages, the circuitry of the author's receiver is included for interest only because the modified "Pye" strip used on the vision side is suitable for the 45 Mc/s London transmissions only, it being a T.R.F. line-up. In fact, unhappily, the T.R.F. seems to be dying a natural death due to the difficulty of retuning a vast number of tuned circuits when alternative channels are desired. However, if the 45 Mc/s channel is required, the "Pye" strip can hardly be bettered for performance and for ease of adaptation from its service rôle. With five R.F. stages and no less than 10 tuned and one broad-band inductance, the alignment of this strip to get the very best out of the BBC transmissions is a relatively simple matter since the strip is aligned to give at least 4 Mc/s bandwidth as it stands. The input coil has no variable core and is broadly tuned at 45 Mc/s; all the anode coils are peaked at 46.75 Mc/s with the exception of the final (diode) coil, which is peaked at 45 Mc/s; and the grid coils are all at 43.25 Mc/s as aligned at factory. Thus a little judicious stagger tuning, taking care not to overdo it on the sound channel side because of breakthrough, enables a bandwidth of 6 Mc/s for double sideband reception to be obtained without any great difficulty. Principal modifications are associated with the cathode biasing arrangements where a potentiometer controls the gain of the first two R.F. stages and controls picture contrast. Partially unby-passed cathode resistors develop negative feedback to counteract the changes of input capacitance and impedance which would otherwise introduce serious changes of tuning. The contrast control is located on the separate time-base chassis via cabling for the convenience of having all variable controls together. Sound input is extracted from the anode circuit of the second vision R.F. stage and fed thence into the two R.F. sound receiver; the sound output stage with associated gain control is located on the main time-base chassis.

Detector

The diode detector (EA50) is connected in such a manner that a positive-going signal is presented to the following video valve, i.e., the output is taken from the cathode. If the "Pye" strip is used the connections must be reversed to meet this requirement. The R.F. choke (Ch. 1) forms a low-pass filter with

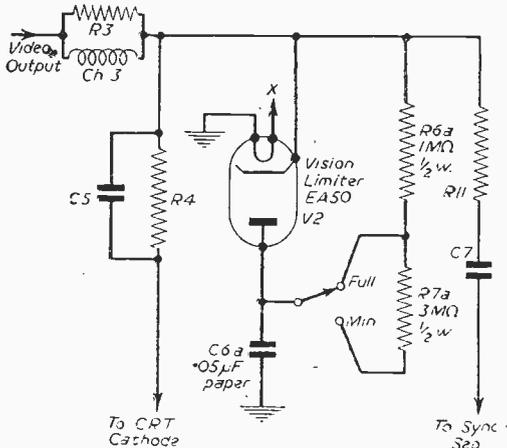


Fig. 2.—An alternative vision interference limiter circuit.


its associated components designed to reject the carrier (T.R.F.) or I.F. and harmonics (superhet). The two chokes used for this purpose in the "Pye" strip add up to about 5 mH., but rather more, some 200-300 mH., will be required in a superhet depending on the intermediate frequency. The load resistor (R1) must be as low as possible to maintain high-frequency response, but high enough to ensure reasonable detector efficiency. A value of 5.6 K Ω has been found a reasonable compromise although lower values may be tried and possibly preferred by some.

Video

The special EF55 valve has been tried in this position (V1), but it was found the "Old Faithful" EF50 when used with a high anode load resistor was capable of fully modulating any normal tube requiring something like 30 volts swing—and with greater economy having regard to the higher current requirements of the former valve. Inductance compensation is used in the anode load to offset the inevitable H.F. loss incurred by the high anode load. Provided that none of the coils in the preceding vision strip is peaked exactly to the resonant frequency of the chokes Ch. 2 and Ch. 3, very little "ringing" should be discernible. It should, perhaps, be explained that "ringing" is visibly apparent by the outlining of all details on the screen by a secondary image. A damping resistor (R3) is to prevent the over-resonance which would cause this effect. Additional H.F. compensation is provided by the by-pass condenser (C3) across the cathode bias resistor (R5). The value of this condenser has a profound effect on picture quality, being quite critical and varying from one set to another due to the different stray capacities associated with the video output lead and

components going to the modulation electrode of the C.R.T. In fact, one TV set manufacturer has recently made the capacity variable and labelled it "Quality Control." What happens is that negative feedback is developed across R5 at low frequencies, when the condenser then has negligible effect. But as the frequency rises, the condenser becomes effective as a by-pass and the gain of the valve increases due to the reduction of negative feedback which provides a degree of correction dependent on the value of C3. Some experiment to determine the best value of this component is well worth while, for upon it depends the quality of the picture.


A 0.001 μ F condenser is a good value to start with and, by increasing the value in steps of, say, 500 pF in parallel, the effect can be observed on the screen until a value is reached when L.F. response suffers and outlining haloes appear at the right-hand edges of images. A value slightly less than this is the correct value. In the author's receiver it was 0.0035 μ F, but this value was probably rather higher than normal due to a long video lead to the tube. This long cable, though not good practice because of the extra capacity introduced affecting H.F. response, is, nevertheless, in order if it is possible by compensation to resolve the full bandwidth adequately. This is fortunate in large screen receivers because, as the tube diameter increases, the distance between tube

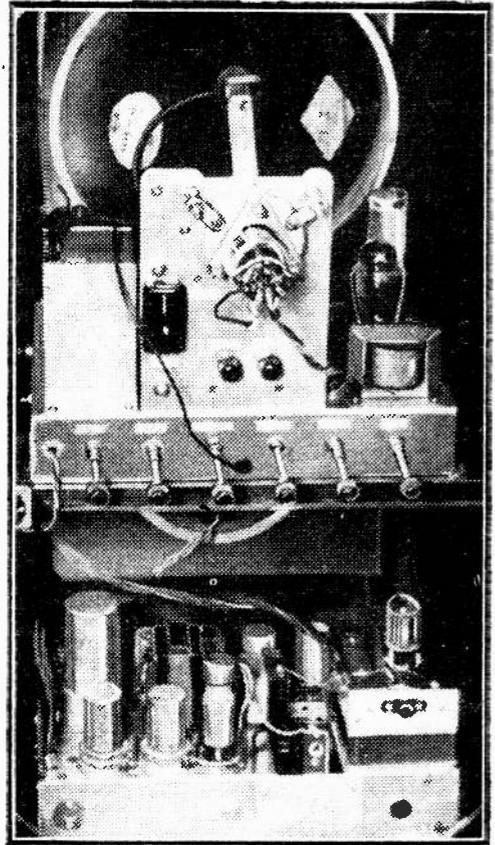

The finished receiver in a console cabinet.

socket and chassis and hence the length of the video lead unavoidably increases also. At all events, the resolution of the 3 Mc/s bars in the test pattern is the final acid test.

Cathode modulation of the C.R.T. is effected through a resistance (R4) and associated by-pass condenser (C5). If a C.R.T. with a tetrode gun is used, the D.C. voltage applied to the cathode is nearly halved by R26 so that the voltage of the first anode may be reasonably low to maintain the required difference of about 250 volts. If a triode gun C.R.T. is used R26 is not necessary and need not be fitted. The feed circuit R4/C5 possesses a long time-constant. This is an arrangement which is finding increasing favour among manufacturers now because moderate changes in D.C. level of the picture, such as those sometimes experienced when going from one camera to another or picture "flutter" due to aircraft, are greatly reduced by this simple arrangement. When a change of D.C. level occurs

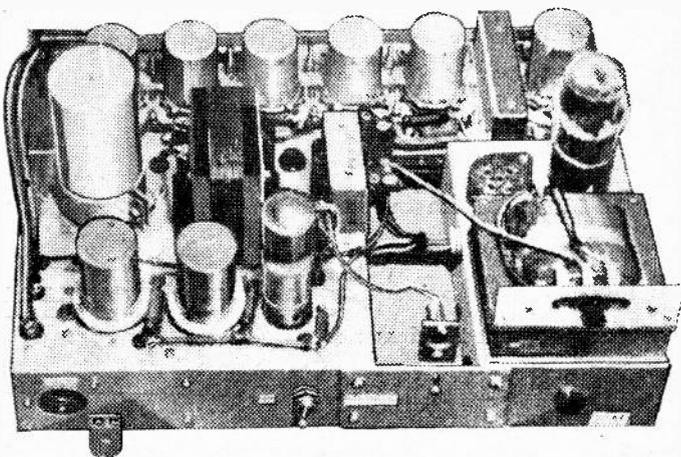

Vision sound strips and power pack. Front left : Sound receiver with main H.T. smoothing components. Front right : Power pack. Rear : Pye vision strip.

causing the beam current to rise, the voltage across R4 increases proportionately. This increase of voltage across R4 biases the tube back.

(To be continued.)

LIST OF COMPONENTS

CONDENSERS

(All condensers have a working voltage rating of 350 volts unless otherwise stated.)

- C1, C2—5 μ F mica
 C3—See text
 C4—32 μ F electrolytic
 C5, 6, 7, 13, 22, 23, 28—0.1 μ F
 C8—16 μ F electrolytic
 C9—200 μ F mica
 C10—0.5 μ F
 C11, 26—0.005 μ F mica
 C12, 18, 31, 35 0.002 μ F mica
 C14—300 μ F mica
 C15—0.001 μ F 12.5 kV (see text)
 C16, 24—1000 μ F electrolytics, 6V (can insulated)**
 C17, 30, 32—0.05 μ F
 C19—0.01 μ F
 C20—100 μ F electrolytic, surge limiting TV type
 C21—64 μ F electrolytic, surge limiting TV type
 C25—100 μ F electrolytic, 50 v.
 C27—0.015 μ F (0.01 plus 0.005 μ F)
 C29—500 μ F mica
 C33, 34—0.01 μ F, 500 v.
 C36—16 μ F electrolytic

RESISTORS

(All resistors $\frac{1}{2}$ watt rating unless otherwise stated.)

- R1, 38—5.6 k Ω R14, 15, 25, 27, 43, 44—
 R2—8.2 k Ω 2W 100 k Ω
 R3, 30, 49—22 k Ω R16—220 Ω 2W
 R4—220 Ω R17—100 Ω variable 3W
 R5—270 Ω R18—1 k Ω variable 3W
 R6, 40, 42—470 k Ω R19—5 k Ω 10W
 R7—100 k Ω variable R20, 28—50 k Ω variable
 R8—27 k Ω R22—6.8 k Ω 10W
 R9—500 Ω 2W R23, 2, 2 k Ω —2.2 k Ω
 R10, 32, 51—1 M Ω R24—10 Ω variable pot.
 R11—10 k Ω $\frac{1}{2}$ W, centre tapped**
 R12—15 k Ω R26—270 k Ω *
 R13, 21, 46—47 k Ω R31—470 Ω

R33, 34—45 Ω 5W

R35—6 Ω variable pot. centre tapped**

R36, 41, 45—1 M Ω variable potentiometers

R37—33 Ω

R39—5 k Ω variable

R48—100 k Ω 1W

R47—1 M Ω 1W R50—200 Ω 1W

TRANSFORMERS AND CHOKES

T1—Plessey line output transformer Type SL7, Part No. CP.72036, 2 or CP.72036 complete with width inductance.

L1, L2 and F1 E2—Deflector coils, low impedance line and frame to match above.

(Both the above manufacturers' surplus items available as a set together with focus coil from Radio Clearance, Ltd., Tottenham Court Road, W.1.)

T2—Multi-ratio frame output transformer (manufacturers' surplus available from Laskys Radio, Harrow Road, W.9)

T3—TV type auto-transformer, input 200 to 250 volts A.C. overwound to 300 volts at 250 mA. Heater windings 6.3 volts 8 amps, 5 volts 3 amps. (Obtainable from Premier Radio, Ltd., Edgware Road, W.2)

T4—Small heater transformer to suit C.R.T. (e.g., 6.3 volts at minimum of 0.3 amp. for MW 31/16)

Ch.1a, Ch.1b—See text

Ch.2, Ch.3—Universal video peaking chokes. Made by Denco

Ch.4—3 to 5 henry 250 mA smoothing choke, 50 ohms D.C. resistance

MISCELLANEOUS

F1, F2—2 amp. fuse

V6—6SN7GT

F3—750 mA fuse

V7—EL33

V1, 3—EF50

V8—5U4G

V2—EA50

W—S.T.C. rectifier

V4—EL38

K3 25 or similar

V5—EY51 or SU61

*See text. **May be omitted if desired.

Modifying the R3118 and the ZC8931

CONVERSION DETAILS FOR A POWERFUL SOUND AND VISION RECEIVER

By B. L. Morley

(Concluded from page 554, May issue)

MODIFICATIONS to the vision stages are very simple. They are as follows:

V5.—Take two brown wires from pin 7 and connect together, clear of the valve. Remove the $0.1 \mu\text{F}$ from pin 7 to earth and short circuit pin 7 to earth.

V6 and 7.—No modifications required.

Contrast Control

This should be fitted on the front panel as given previously; the brown wire previously wired to the centre of the "Gain" socket should be connected to the centre tag of the control and the other tag should be connected to earth. Make certain to reconnect the $50 \mu\text{F}$ condenser.

Detector V8

This valve was originally used for pulse input controlling the suppressor grid of V9.

To modify it disconnect the wire from L8 to the grid of V9 and connect it to the cathode of V8. Disconnect the cathode of V8 from earth. The connection of L8 to the cathode of the diode is most easily arranged by disconnecting the grid V9 wire from the top right-hand tag by the coil, and running a wire from this point through a spare hole in the base of the screening can to the cathode of V8.

Wind the filter coil as per the data.

Remove the 470Ω and $470 \text{K}\Omega$ resistances from pin 7 of V9 and drill a hole in the chassis by the side of pin 7. Fit a small grommet in the hole and run a short piece of flex from the pin to grid of the valve. Fit a $4.7 \text{K}\Omega$ from pin 7 to earth and connect the filter coil from pin 7 to the anode of the detector, and at this point connect a 15pF condenser to earth.

Video Valve

Earth the suppressor grid (pin 5) of the valve; remove the 100Ω cathode resistor and fit 47Ω in lieu. (A value between 47Ω and 68Ω is suitable.)

Connect an $8 \mu\text{F}$ condenser from the screened grid of V9 to earth. The condenser can be mounted on a clip on the side of the chassis. (A condenser of the Drilytic type is most suitable.)

Remove the small resistor panel from L9 can and mount it at the end of the resistor panel containing the $4.7 \text{K}\Omega$ resistors underneath the chassis. The little panel should be fitted at right angles to the existing panel.

Wire up the panel by taking the red wire previously running through the bottom of L9 can to the junction of the $1 \text{K}\Omega$ resistor and the $0.002 \mu\text{F}$ condenser, and the yellow wire to the screened grid of V9 and the other side of the $1 \text{K}\Omega$ resistor. Wire from the $10 \text{K}\Omega$ resistor to the anode of the video valve and connect the other side of the $0.002 \mu\text{F}$ to earth.

Wire the existing screened cable previously going to the "Pulse Input" socket so that one end is connected directly to the anode of the video valve and the other end to the video output socket.

If a magnetic tube is being used, then it is worth

while to replace the screened wire with a short section of coaxial cable.

This completes the vision section. (Fig. 6.)

Cathode Modulation

The circuit arrangements just described are quite suitable for the VCR97 or for a magnetic tube which is connected to a timebase via a cathode follower and uses grid modulation. Where cathode modulation is desired, then the video valve output must be altered in accordance with Fig. 5b, while if direct connection to the grid of the picture tube is desired, then Fig. 5a circuit can be used.

Note that the detector is connected for grid modulation; if cathode modulation is to be used the detector valve must have its anode and cathode reversed, and the bias resistor of V9 must be increased to 220Ω .

The Sound Section

This section requires a little more work than the vision stages.

V10. This becomes the first sound I.F. As the frequency is 9.5 Mc/s the tuning of the coils must be altered. This is carried out simply by connecting an 0.30 pF postage stamp trimmer across each I.F. coil.

The hole which is spare in L9 can is enlarged to take $\frac{1}{4}$ in. diameter coaxial. A similar hole in can L5 is also enlarged. A short section of coaxial cable is now run between the two cans.

Put 2 turns of approximately 22 swg enamelled wire on top of the coil in L5 and earth one end. Take the other end to the centre conductor of the coaxial cable and earth the outer of the cable. Do exactly the same thing in can L9.

The trimmer can be mounted on the upright metal strip which holds the can itself and it should be so

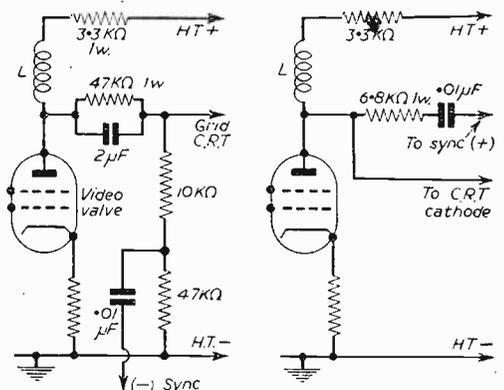


Fig. 5.—Alternative methods of feeding the tube.

Note: L can be 3 Mc/s boost choke as used in "Viewmaster".

arranged that the trimmer can be adjusted when the can is on.

The 2.2 K Ω resistor should be removed from across the coil.

2nd Sound I.F.

Take out the bottom 10 K Ω resistor on the panel in can L10 and fit the trimmer. Disconnect the white wire; remove the 10 K Ω resistor from the cap of V12 and short circuit the tags on the cap. Change the cap lead to the top tag of coil L10.


Now take two yellow wires from tag 4 and insert a 10 K Ω resistor between the yellow wire and tag 4.

The cathode of the valve should now be decoupled with a 0.01 μ F condenser.

Detector and Noise Limiter

Remove the 100 pF from the cathode of V14; strap the cathode of V14 to that of V11, and connect a 35 pF condenser between the cathodes and earth. Disconnect the 2.2 M Ω from the top of L11 can and fit 500 pF in lieu. This 500 pF is one removed from lower down the small tag strip. It is mounted as in the previous can.

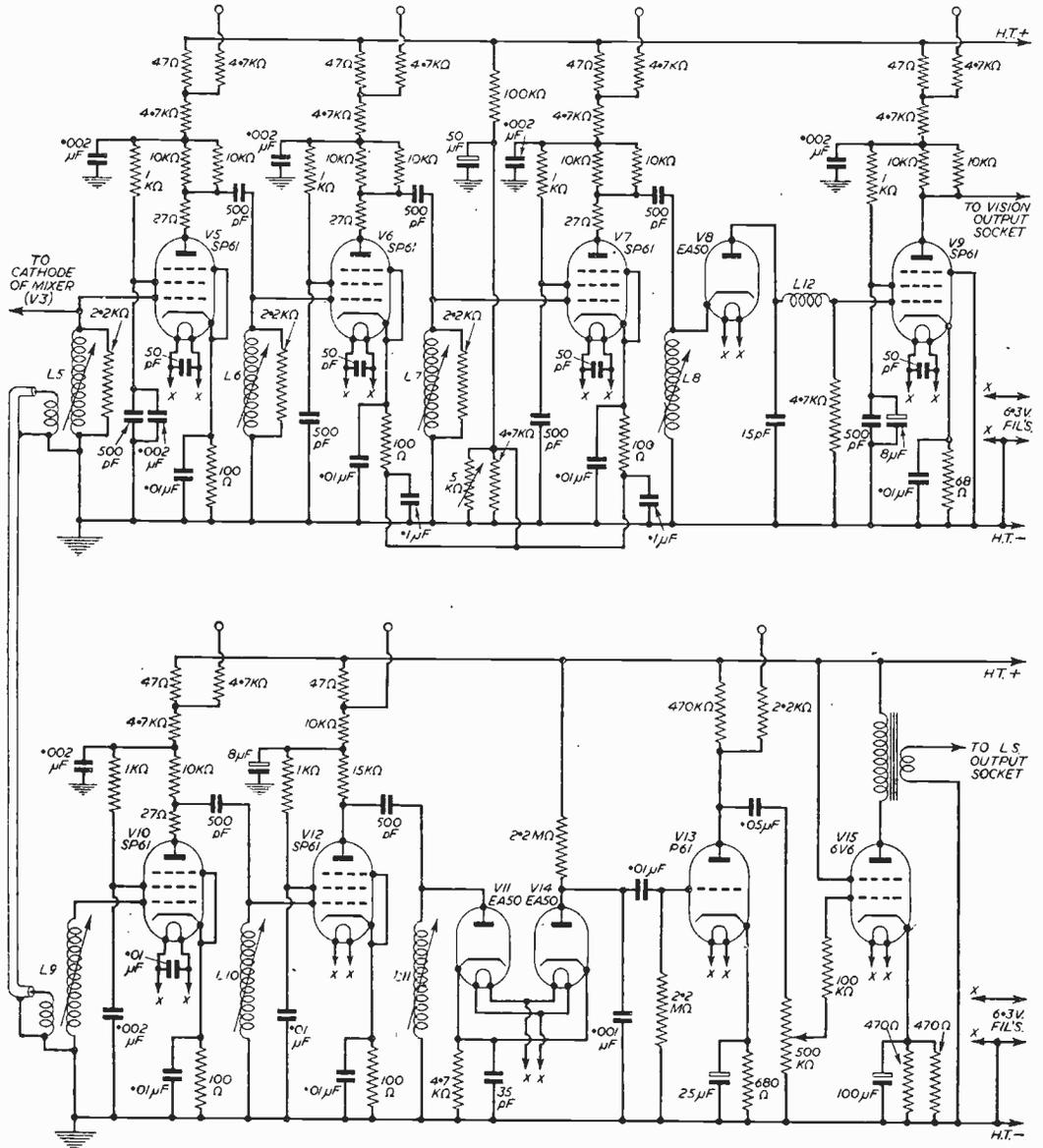Remove the 10 pF from inside L11 can and recover the 100 pF and 4.7 K Ω from the strip by V11. Run



Figs. 6 and 7.—The vision and sound sections.

a wire from can L11 to the anode of V11 and fit the 4.7 KΩ between the cathode of V11 and earth.

Reference to Fig. 7 should make the matter clear.

Remove the 100 KΩ resistor and connect the anode of V14 to the 2.2 MΩ resistor in L11 can and

Connect a 100 KΩ resistor on the component strip by the magic eye and remove the other resistors. This resistor now becomes the grid stopper for the 6V6. The other side of the grid stopper goes to the slider of the volume control.

The green wire on the magic eye is used for the cathode of the 6V6 and underneath the chassis it is diverted to the positive side of the 100 μF condenser. Two 470Ω resistors are connected across the tags of this condenser.

The output transformer is fixed underneath the long metal strip, towards the front end of the chassis, upside-down. It is wired as shown in Fig. 7 and one side of the output is earthed, while the other side is taken to the Pye output socket. (One side of the Pye socket must also be earthed, of course.)

This completes the modifications. Fig. 8 shows the layout at the top of the chassis.

The wiring should now be checked before checking the alignment.

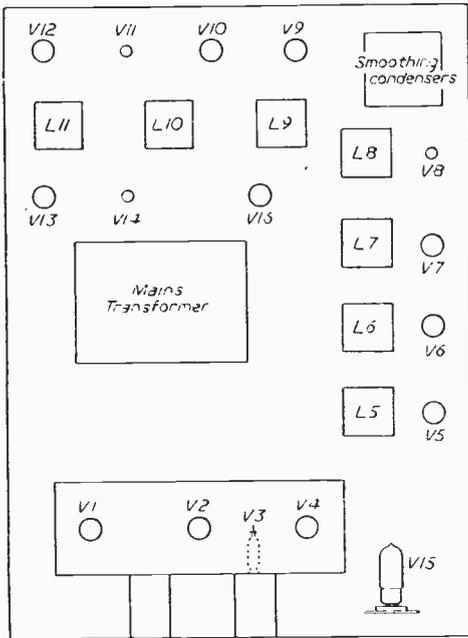


Fig. 8.—Chassis layout.

take the other side of the resistor to H.T. positive line.

Disconnect the red wire running between cans L11 and L10 and divert it to the anode of V12.

First Audio

Remove the 2.2 KΩ cathode resistor from V13 and replace it with one of 680 ohms. Fit a 25 μF 25 volt wkg between the cathode and earth and disconnect the lead going to the 100 μF condenser. Insert a 470 KΩ resistor in the anode circuit of the valve and disconnect the 1 μF paper type condenser; in its place insert an 0.05 μF mounted on the side of the chassis.

Wire the volume control as shown in Fig. 7.

Sound Output

The magic eye should have been removed and the holder is now wired for a 6V6. The red wire is the heater common and the black wire is the earth. The yellow wire goes via the switch operated by opening the tuning panel and the switch should either be removed or the contacts short circuited. This wire now becomes the H.T. positive feed for the 6V6 and should be connected to pin 4.

VOLTAGE READINGS AT TEST PANEL					
V1 ...	1.5	V6 ...	1.5	V10 ...	1.5
V2 ...	1.5	V7 ...	1.2	V12 ...	3.0
V3 ...	1.1	V9 ...	1.25	V13 ...	4.0
V5 ...	1.8			V15 ...	20.0

Alignment

Connect phones or a loudspeaker with its output transformer to the video output socket, via a condenser of about 0.1 μF.

Connect an aerial to the aerial socket and insert the mains plug; switch on and allow the set to warm up. Set the contrast to maximum.

The vision signal should now be tuned in. If the tests given previously have been made there should be no difficulty in getting the signal. The vision signal sounds like a mixture of rough hum and motor-boating.

Note the position of the trimmers and now tune in the sound signal and again note the position of the trimmers.

The loudspeaker (without transformer) should now be connected to the loudspeaker output socket and the oscillator should be swung until the sound signal is heard. Adjust the trimmers to maximum volume, and note the position of the oscillator.

Now reset the oscillator for the vision signal and retrim the sound I.F.s.

Gradually work the oscillator from sound position to the position obtained for vision and when the two readings approach each other go back to the vision stages.

Once again adjust all tuners to maximum vision

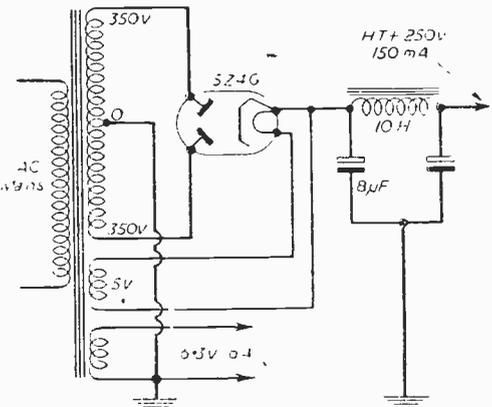


Fig. 9.—Circuit of a suitable mains unit.

signal and then adjust the oscillator until the "volume" of the vision signal is reduced by half. Note the position of the oscillator. Now go back to the sound channel and adjust the oscillator for maximum sound and finally adjust the sound I.F.s for maximum sound.

The position should now be reached where the vision signal is correctly positioned and has plenty of "volume" and the sound has plenty of volume.

Final adjustments to vision and sound are best done when Test Card C is being radiated.

Power Pack

In the case of the ZC unit a power pack will be necessary; this need not be elaborate and a suggested scheme is given in Fig. 9.

Instability

If difficulty with regeneration is experienced then further decoupling can be added by connecting a 500 pF condenser across each 50 pF decoupling condenser.

Increasing the Gain

An increase in gain can be obtained by dis-

connecting the 2.2 K Ω damping resistors from the vision I.F. coils.

Increasing the quality

The band-width of the vision I.F. stages should be ample to provide a signal of good quality. If quality is poor, then the vision I.F. coils can be retuned. It should not be normally necessary to do this, but if it is attempted, then the work should be done on Test Card C so that the result of the operations can be observed.

Test Voltages

One useful feature of the unit is that a small test panel is provided so that valve voltage readings can be checked. A list of those obtained with the prototype is appended.

Pre-Amps

In the remote areas a pre-amplifier can be used and circuits for such pre-amps have been given from time to time in the pages of this journal.

Note that any pre-amp used must be equipped with its own power supply. The existing power supply of the unit is already worked to the limit by using the 6V6 valve.

BBC Station and Studio News

North Hessay Tor

FOLLOWING the Public Enquiry at Exeter in September, 1953, the Minister of Housing and Local Government on January 25, 1954, gave his formal planning permission for the erection of a BBC television station on North Hessay Tor, subject to agreement between the BBC and the Devon County Council as to the exact position of the building and mast. Agreement has been reached on this point. It is, however, alleged that there are commoners' rights affecting North Hessay Tor, of which the present owners of the land have no records. The legal processes involved in disproving the existence of these commoners' rights or alternatively of extinguishing any commoners' rights which may exist on the very small amount of land which the BBC would need to enclose may take several months and may still further delay the television service for Devon and Cornwall. In the meanwhile the BBC is taking all possible steps towards the provision of the transmitters so that any delay may be minimised.

The Meldrum Station

A contract for building work at the new medium-power television transmitting station for North-East Scotland, at Meldrum, Aberdeenshire, has been placed with Alexander Hall & Son (Builders) Ltd., of AberJeen.

The contract covers the provision of the main station building, the drainage system, service roads, and fencing.

Crystal Palace Station

A contract has been placed with British Insulated Callender's Construction Co., Ltd., for the design, supply and erection of a self-supporting tower to carry the aerials for the new London Television Transmitting Station at Crystal Palace.

This new tower, which will be designed and built

to comply with the BBC's specification of structural requirements, will have a height of 640ft. It will be of lattice steel construction, tapering from 120ft. square at the base to 9ft. 6in. square at the 440ft. level. Between 440ft. and 600ft. the tower will have parallel faces 9ft. 6in. across; on this portion will be mounted eight stacks of four dipoles forming the Band I transmitting aerial. Above this there will be a topmast 40ft. high and 2ft. 6in. square.

Provision is made at the 440ft. level for the installation of dish-type receiving aerials for picking up outside broadcast transmissions. There will be a hoist between this level and the ground.

The tower will be equipped with aircraft warning lights to comply with the requirements of the Ministry of Transport and Civil Aviation.

It is expected that the main structure of the tower will be completed by the autumn of 1955.

New Studio Equipment

Contracts have been placed with Marconi's Wireless Telegraph Co., Ltd., Electric and Musical Industries Ltd., and Pye Ltd., for new television cameras, picture monitors and other equipment for studio use.

The Marconi contract covers the provision of 16 cameras using the 4½in. Image Orthicon pick-up tube developed for studio use, the associated camera channel apparatus, six vision mixing and pre-view switching equipments, distribution amplifiers and waveform generators.

The Marconi Image Orthicon Cameras are of the same type which will be used with the four BBC Television Outside Broadcast Vehicles now under construction at Marconi's Chelmsford Works.

The Pye contract covers the provision of 62 picture monitors.

This equipment will be used to re-equip some of the existing television studios and to extend studio facilities in the London area.

A Simple WOBBULATOR

CONSTRUCTIONAL DETAILS OF AN EASILY BUILT INSTRUMENT SUITABLE
FOR ALIGNING TELEVISION RECEIVERS

By S. C. Murison

(Concluded from page 546, May issue.)

THE potentiometer now has a 360 degree travel. During 170 degrees of this the resistance between the wiper and one of the track ends varies linearly. During the remaining 190 degrees the wiper to track end resistance is constant except for a momentary open-circuit at the point where the wiper leaves the end of the foil.

Construction

The form which the instrument takes need not be the same as that shown in the photographs. Changes must not be made to the layout of the oscillator, however, unless the constructor has facilities to ensure that the performance is not impaired by the changes. The layout of the parts in the oscillator can be seen from the photographs. A single earthing point is used at the side of the valve-holder away from C3. The earthing wire from the rotor of C3 should not be forgotten in wiring up.

Fig. 4 gives details of the brackets used on the original. No tools beyond a hack-saw, a hammer, a vice and a drill need be used in making the brackets. Aluminium sheet of 16 s.w.g. was used for the originals. The side flanges on each bracket are present to improve their rigidity and should not be omitted. It is recommended that two flexible couplers in tandem be used to couple the shaft of C3 to that of RV2. This makes their alignment very little trouble.

The only connection to the wavemeter is made by a 3in. length of coaxial cable, which is soldered to the wavemeter before it is fastened in place, because it is not accessible afterwards. The screw used to secure the wavemeter coil to the front panel should be no longer than is necessary to hold the coil firmly. Too great a length of screw projecting into the coil can damp it and by so doing will broaden the appearance of the frequency marker. An ideal solution is to stick the former to the panel with a *really good* adhesive.

If the same oscilloscope is to be used all the time with the wobulator, it may not be necessary to build a power pack into the wobulator. It may be possible to arrange a plug and socket arrangement for the power supply to the internal timebase, so that when the wobulator is used it uses the power which is normally fed to the timebase. If this course is adopted, it is safer to leave L3, C8 and C9 on the wobulator. This improves the decoupling and minimises any tendency for feedback from the oscilloscope to the wobulator. The requirements of the wobulator are 6.3 volts at 0.75 amps and 300 volts at 12 mA.

If a great deal of alignment is to be undertaken and the user does not wish to tie up an oscilloscope

exclusively for this work, a simple unit on the lines of Fig. 5 makes a convenient solution without undue expense. The simple Y-axis amplifier can receive its heater and H.T. supplies from the wobulator via a plug and socket. The same plug and socket can carry the X-axis sweep voltage. It is not recommended that the same cable be used for the mains supply to the monitor unit. A multi-core cable for this purpose can be seen on some of the illustrations.

It should be noted that the Y-axis amplifier used to display the output of the receiver need not have a good high-frequency response. Providing that enough gain at 20 to 30 c/s is available to allow a reasonable vertical deflection to be obtained, there are no complicated requirements for this amplifier.

Setting-up

When the instrument is fully wired, a check to make sure that it is oscillating should be made. At this stage its output frequency will probably be unknown; and consequently the easiest way is to short-circuit C3, while watching the glow in V2. With RV1 fully clockwise, short-circuiting C3 results in the glow in V2 dimming.

The first step in the setting-up process is to make the left-hand end of the trace correspond to the low-frequency end of the wobble. Disconnect one side of the mains going to the motor and tape it or otherwise render it harmless. Slacken off the grub screws

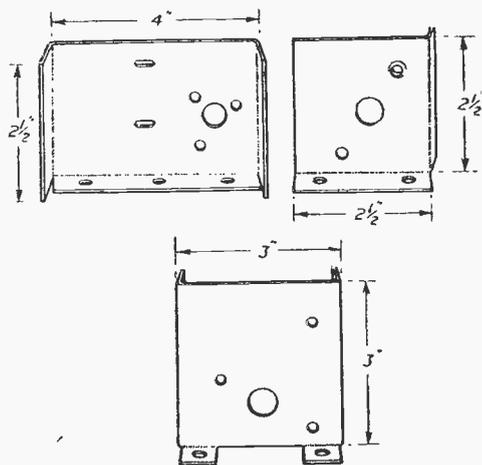


Fig. 4.—Details of the mounting brackets.

in the couplers between C3 and RV2. Connect the wobbulator to the oscilloscope and connect both to mains. By hand, turn the shaft of RV2 until the spot is fully to the left of the screen. Now turn C3 to its maximum capacitance position, and then turn it five degrees towards minimum capacitance in the same direction as the motor will turn it. Tighten up the grub screws on the couplers without disturbing the relative positions of C3 and RV2 shafts. The motor lead should now be connected. *It should be noted that the method given above will only work when there is a direct connection from the wiper of RV2 to the X1 plate.* Even if it is not intended to use the wobbulator with such a connection, it should be employed for setting-up purposes.

The next step is to calibrate the wavemeter. Although easier methods may suggest themselves, the method which follows is recommended because of the accuracy which is possible with it. A detector of some kind is necessary. The simple circuit given in Fig. 6(a) is very suitable. A signal generator covering 40 to 70 Mc/s is necessary. The only important thing required of this generator is good frequency calibration. If a constructor does not have one of his own, he should be able to borrow one by virtue of the happy relationship which always seems to exist between service mechanics and constructors.

Using the arrangement of Fig. 5, tune the signal generator to 70 Mc/s. Set C1 to maximum capacitance. Reduce the value of C2 and unscrew the core of L2 until a pattern like that of Fig. 6(b) appears on the screen. This pattern is produced by a beat between the wobbulator and the signal generator. Now tune C1 until the frequency marker coincides with crest of the beat pattern. If the wavemeter cannot be tuned high enough in frequency, gently

increase the spacing between the turns of L1 until it can tune to 70 Mc/s. When this has been done, paint the turns of L1 with coil dope. Mark the pointer position corresponding to 70 Mc/s.

Tune the signal generator to 65 Mc/s, adjusting the core of L2 and the setting of C2, if necessary, to keep the beat pattern on the screen. Tune the wavemeter to coincide with the new position of the beat pattern. Mark the pointer position for 65 Mc/s. This process is continued down to and including 40 Mc/s.

It is a matter of personal preference how many points on the calibration of the wavemeter should be permanently marked. Probably the best method is to calibrate every 5 Mc/s point in one colour and to mark the extremities of each television channel in another colour. It is worth taking pains in the calibration of the wavemeter, for it will be used throughout the life of the wobbulator as a reference to frequency, not only in making measurements on receivers but also in changing the wobbulator from one channel to another.

When the wavemeter has been calibrated, it only remains to adjust C2 and L2 for the desired channel. To do this a detector is still necessary, but the signal generator is not. As a detector either the arrangement of Fig. 6(a) may be used, or the wobbulator output cable may be fed into the aerial socket of a receiver tuned to the desired channel. If the latter method is used, the Y-axis of the oscilloscope should be fed from the anode of the video amplifier valve. The actual procedure is the same whether C2 and L2 are being set-up for the first time or whether a change of channel is being made.

Set C2 to minimum capacitance. With the wavemeter set to the highest frequency required for the desired channel, adjust the core of L2 until the frequency marker appears on the right-hand side of the trace. Now tune the wavemeter to the lowest required frequency and adjust C2 to bring the frequency marker to the left-hand side of the trace. Re-tune the wavemeter to the highest frequency and readjust the core of L2, if necessary, to bring the frequency marker to the right-hand side of the trace. Return to the lowest frequency of the channel and check the setting of C2. Repeat this process until the ends of the

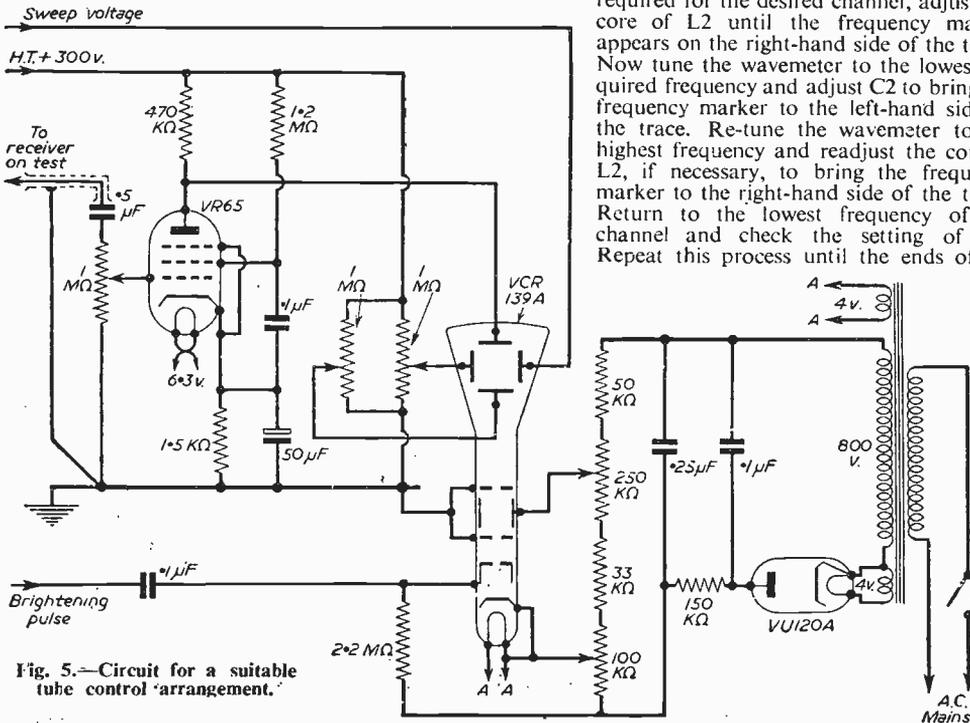


Fig. 5.—Circuit for a suitable tube control arrangement.

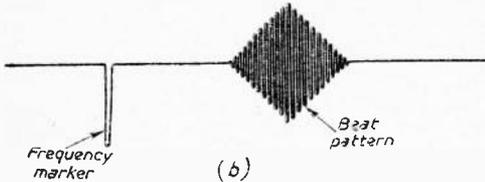
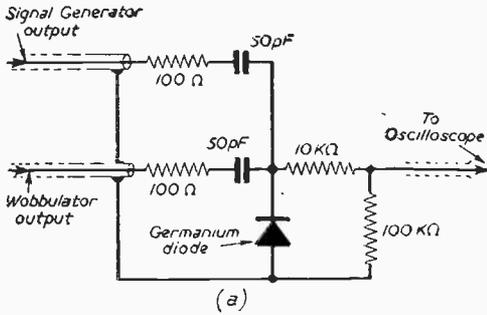


Fig. 6.—A suitable simple circuit for a detector.

horizontal trace correspond to the desired frequency limits required.

Mobile TV Laboratory on the Continent

IN order to extend its information regarding television reception abroad, The General Electric Co. Ltd. has carried out a series of field tests on the Continent. A mobile laboratory, manned by a team drawn jointly from the G.E.C. Research Laboratories at Wembley and the G.E.C. Radio Works Development Laboratory at Coventry, has spent several weeks on the Continent testing receiver chassis developed for use on European transmitting systems. Valuable information has been gained on TV reception generally, which will be particularly useful in the design of G.E.C. export receivers.

Since the European transmitting stations use negative modulation and 625 lines, while their sound is frequency-modulated instead of amplitude modulated, their system is basically different from that used in this country: reception conditions are accordingly quite different, and the information required could only be obtained by field tests on the spot. For example, the use of negative modulation renders Continental synchronising systems much more susceptible to interference, and to obtain the same quality of reception as is achieved on the British system a much more complicated receiver is needed. Again, since the sound on Continental TV is frequency-modulated, inter-carrier systems can be used, and information on these was also obtained.

In addition, the results obtained enabled the performance of the closed line transmitter at the Research

Usually it is only necessary to adjust L2 twice and C3 three times, if one starts from scratch without any idea of where they should be set. After a little experience it is possible to set them up practically without reference to the wavemeter—although they should always be checked by it, of course.

If the wobbulator is to be moved about in cars and vans, it is worthwhile to slip a thin strip of rubber between the core of L2 and the threads in the bore of the former. This prevents the core being moved by vibration, yet leaves it free enough for changing the channel.

Modifications

The instrument as described is well suited to rapid alignment on a chosen channel. Any proposed modification should be well considered. It is not wise to make any change to the circuit of V1 unless the constructor is prepared to embark on a long series of measurements to check the constancy of output voltage over the band. It may be felt that the unused half of V1 is a waste; but any proposed alternative should be carefully checked to ensure its freedom from microphonic effects.

The more ambitious constructor may care to devise a method of panel control for C2 and the core of L2. Providing that no pieces of metal which may be resonant in the band 40 to 70 Mc/s are involved, this would be a slight advantage.

Laboratories, Wembley, to be checked. Photographs of Dutch and Wembley waveforms were compared.

Measurements were made of the signal/noise ratio in various towns, an important factor in designing receivers for general use in a given area. In the course of the expedition, the van was also taken into a part of Holland in which Dutch and German transmissions overlapped; this enabled the team to study the degree of protection obtained with the tuning stages of the G.E.C. test receivers, which proved to be extremely high. Furthermore, additional information was obtained on the reception conditions prevailing on the 200 Mc/s band used in Germany.

The expedition followed naturally on a series of field tests which have been made throughout Great Britain during recent years.



The G.E.C. mobile laboratory out on field tests near Eindhoven.

FAULT SYMPTOMS

THE CAUSES OF COMMON FAULTS, AND METHODS OF CORRECTION

By Gordon J. King, A.M.I.P.R.E.

(Continued from page 549, May issue)

THIS in itself, however, represents a form of interlace checking aid, particularly when such a condition is compared with a non-interlaced picture clearly revealing the total inertness of the line structure and the comparatively wide and empty spaces between. To provide a comparison it is easy to achieve a non-interlace by adjusting the framehold control just off lock so that the picture slips very slowly downwards.

Incidentally it should be noted that the illustration given last month and marked Fig. 45 actually consists of three illustrations, the centre one being 46 and the lower one 47.

Another method is by following the apparent line movement with the eyes, and, after a little practice, as the eyes scan the screen vertically it is possible momentarily to resolve just a single frame of a picture to obtain a comparative mental impression of non-interlace. Should it seem impossible to obtain a fleeting glimpse of a separate frame by this method, however, the indication may be that interlace is not occurring, or it may mean that the requisite art of moving the eyes at the correct speed in a fixed plane has not yet been acquired; practice on a number of receivers is generally desirable before making a definite statement in this respect! To assist, however, the use of a pencil or finger can be employed to trace the line movement mechanically—the eyes, of course, then following the movement of the pencil, while at the same time scanning the screen. Practice is necessary to determine the optimum speed of pencil movement.

Examining the frame flyback lines is another method frequently adopted. Fig. 48(a) reveals how the flyback lines are generally formed when the brightness control is advanced beyond its desirable setting (this, of course, is assuming that no flyback suppression device is embodied in the receiver; this will be considered later). The two vertical columns of short horizontal lines (the two horizontally adjacent short lines tend to resolve into a complete line if the brightness control is advanced too far) are those in which we are mainly interested for this test. The actual number of lines is of no consequence, since the number is a function of the speed of the frame flyback and will vary from receiver to receiver.

We are interested in the spacing between the short lines of one of the columns; it does not matter which column is considered. When the spacing is even—taking into consideration, of course, the fact that the space tends to diminish towards the top of the screen, anyway—it indicates 99 times out of a 100 that interlace is taking place. The 1 per cent. possibility that interlace is not occurring under these conditions embraces

the remote chance that, although the frame timebase is being "fired" at the precise moment each frame to create evenly spaced flyback lines, something unusual may be happening to impair raster interlace.

As compared with a good interlace condition at Fig. 48(a), the diagram at (b) illustrates how the flyback lines generally resolve when the interlace is not so good or when it is not occurring at all.

Faults in a Receiver Which May Affect Interlace

When it is realised that a successful interlace can occur only when the start of a frame scan coincides with the start of a line scan every other frame only, we can clearly understand why a slight disturbance in the frame generator or synchronising circuits is liable severely to impair the interlace performance. If, for instance, the scans start together at every scan they follow the same path and no interlace exists; and it is interesting to note that to do this the frame generator has to be "pulled" only half a line every other frame. As a ratio this works out to something like 50 microseconds in 20 milliseconds, or one part in 400. It has been proved, however, that a minute disturbance in the frame circuits of one part in 2,000 will impair the interlace to a noticeable degree, probably resulting in something like a 40-60 interlace.

About the largest normal disturbance generated in a television receiver is during the line flyback when, as we have already seen, a high potential pulse is developed across the line output transformer and associated inductors. In a large number of cases a poor interlace is the result of this pulse gaining admittance, by some means or other, to the frame timebase sections to "fire" the generator either slightly before or after the "firing" time necessary for a perfect interlace.

In this respect the cause can generally be traced to an undesirable coupling existing between the line timebase and frame generator. This may be due to a defective component in the sync separator, interlace filter (if such a device is incorporated), or in the frame generator circuit itself—sometimes poor insulation in the frame blocking oscillator transformer provokes the symptom, although the frame timebase may be functioning quite normally otherwise.

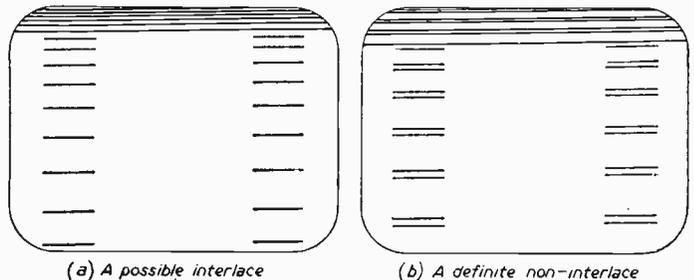


Fig. 48.—The formation of flyback lines, showing possible and non-interlace.

It is also most important to ensure that no screening has been removed from the line timebase and that no associated interconnecting wire has inadvertently been moved near the vision detector, video amplifier, synchronising circuits or frame generator.

Sometimes it happens that the line pulses are not sufficiently isolated from the frame generator by the sync separator, and due to this possible leakage path arrive at the frame generator in a roundabout way. Modern receivers, unless a fault is modifying their performance, are less prone to this kind of trouble, since, generally, an efficient interlace filter acts, apart from its normal function, as a satisfactory "buffer" between the line timebase and the frame generator.

It has been known for line pulses—due to the flyback—to get mixed up in the H.T. circuits, often as the result of poor decoupling, and following a most unorthodox

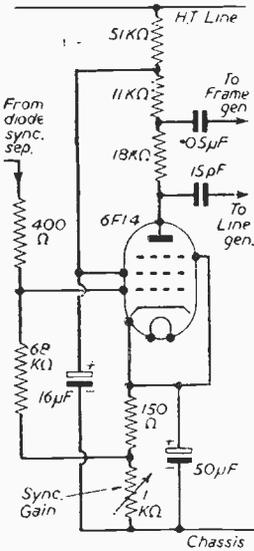


Fig. 49.—The sync amplifier stage of the Decca Projection Model 121.

route find their way to the critical frame circuits. If poor interlacing is suspected to be due to this cause a lot of time is saved by working the frame generator from a

separate power source as a test. If then interlacing is not restored the fault must obviously lie elsewhere. A pair of high resistance headphones can prove most useful as an indicator for tracing line pulse leakage. They should be used connected in series with suitably rated isolating capacitors, and one terminal can be connected to the receiver chassis and the other employed as a wander-lead, allowing quick connection to parts of the frame circuit. Line pulses in the frame generator will, of course, be heard in the phones as a high-pitched whistle.

To make this test successfully it is first desirable to stop the frame generator: In certain receivers this can be done simply by removing the appropriate valve. In other circuits, however, care must be taken owing to the possibility of the valve heaters being wired in series, or that two sections—one section only working as frame generator—may be

embodied in a single valve unit. The ECL80—triode pentode—and the B36—double triode—are typical valves in this category often employed in frame timebase circuits. Killing the H.T. supply by disconnecting a resistor in the anode lead is about the easiest way of tackling the problem in these cases.

Before leaving the symptoms of poor interlacing, it may be instructive to consider two such problems presented to the writer in recent months. One of the receivers was a Decca Projection Model 121. This set employs an amplifier stage solely for the sync pulses, the actual separation being performed by a diode circuit. The sync pulses from the diode are, therefore, directly applied to the control grid of the sync amplifier valve, and the amplified pulses in correct phase appear in the anode circuit. The circuit at Fig. 49 shows the relevant details, in which it will also be seen that a variable resistor is included in the cathode circuit to control the gain of the stage.

The complaint was poor interlacing, coupled with a critical line hold. Usually on this model an optimum interlacing point can be found on the sync gain control. In this case, however, the control had very little effect, and being a projection receiver the fault condition of non-interlace was clearly revealed on the large screen. General circuit analysis soon established that the 50 μF cathode by-pass electrolytic capacitor had lost most of its value. Incidentally, it is always a good point to make an immediate test on any electrolytic capacitor that may form a part of the circuit under suspicion—they have a bad habit of drying up and changing from a capacitor to a resistor.

There are cases when an associated valve develops some obscure fault that, although the general function of the circuit remains unaffected, tends to disturb the interlace performance. This makes it desirable, therefore, particularly if a receiver suddenly develops the symptom of poor interlacing without any unusual accompanying symptom, to try substituting the frame generator and sync separator valves with others known to be well up to standard before anything more serious is contemplated.

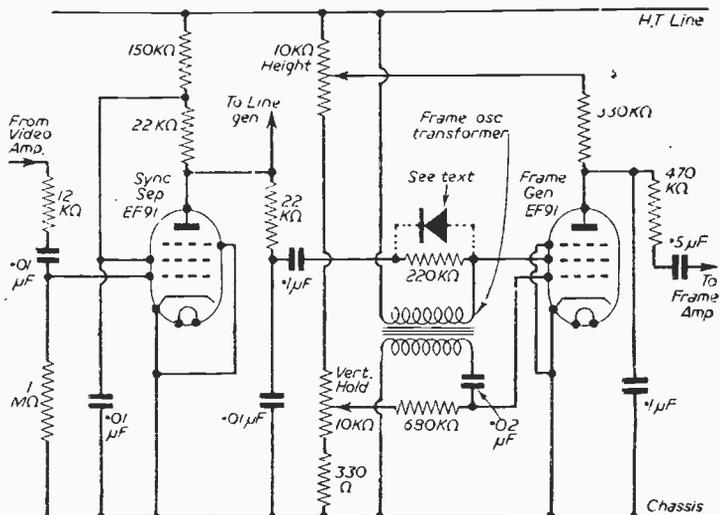


Fig. 50.—The frame synchronising section and frame blocking oscillator of the Ferguson 941T.

The circuit in Ferguson Model 941T tends to suffer in such a way, and in an instance investigated by the writer care was demanded in selecting a *new* replacement valve that gave a good interlace. Fig. 50 illustrates the sync separator and the blocking oscillator section of this receiver. It was discovered that by including a Type W6 Westector rectifier across the frame sync feed resistor, as shown in dotted lines on the diagram, a much improved interlace performance was achieved, and replacing associated valves was then not such a critical process; apart from this, frame lock was made much more solid and was less affected by sudden bursts of interference.

No Raster (E.H.T. O.K.)

We have already considered ways and means of checking E.H.T. and the line timebase circuits with respect to a blank screen being caused by lack of picture-tube final anode potential. Having established that the missing raster is not due to this cause, however, it is still a comparatively simple matter to locate the precise cause and, generally speaking, such a symptom represents one of the less complex faults to diagnose—so far as a direct viewing receiver is concerned.

In the first place it is fairly obvious that, after having established the presence of E.H.T., we will observe the picture-tube in the vicinity of its neck to ensure that the heater is emitting light and, we hope, electrons. Although we can see the heater glowing we can only assume, for the time being, that it is producing the desired quantity of electrons. It is interesting to note, however, that from data gained from observations made by the writer the chance that the glowing heater is not emitting electrons in the correct way for screen illumination is very small indeed.

So far as the picture-tube itself is concerned, something may have happened to the fluorescent quality of the screen to cause our lack of raster. In practice a fault of this nature very rarely—if ever—occurs. Though it should be remembered that as a tube wears the phosphors comprising the screen undergo a chemical change which tends to reduce their light emitting efficiency this effect may be hastened if direct sunlight is allowed to fall on the tube face for any length of time. This must be taken into account when examining a set for a blank screen, but essentially, provided the raster died suddenly, whether during a period when the set was actually operating or whether the symptom was brought to notice when the receiver was switched on, it is safe to be definite that the fluorescent screen is not responsible.

Check the Tube Heater Circuit

Sometimes, mainly for mechanical reasons, the tube "goes down to air." When this occurs, however, the tube heater rapidly burns out—it being very rarely observed alight under these conditions. Furthermore, a white deposit is often seen clinging to the inside of the neck of the tube.

With this reasoning in mind, therefore, we can clearly see that there is little need to express concern over the health of the picture-tube, even though no trace of illumination is displayed on the screen and yet E.H.T. is around in normal quantity; this is, of course, provided the tube heater is glowing.

In certain cases there is still a degree of hope, even with the tube heater cold! Where the valves and tube heaters are connected in series, for instance;

the tube may be O.K.—a valve heater, series resistor or even a fuse may have "blown" to open the tube heater circuit.

Where the tube heater is energised from a winding on the mains transformer the possibility of a dry joint or poor soldering tag connection should always be borne in mind, particularly where a soldering tag carrying heater current is secured in connection with the receiver chassis by means of a rivet or nut and bolt. A bad electrical contact has been known to exist between the tube base heater pin and the heater lead-out wire. A two minute job with a soldering iron focused on the appropriate pin on the tube base saved the day, and a considerable expense. Remember, then, even though an open circuit may be shown across the heater pins on the tube base, do not discard the tube before checking the soldered connections.

Check the Setting of the Ion-trap Magnet

Assuming, then, that the tube still possesses useful life, the missing raster may be caused by the ion-trap magnet, on the neck of the tube, incorrectly positioned. This cause should be suspected if, for instance, the raster disappeared during the time a receiver was being examined for another reason. Some ion-trap magnets are not securely locked to the neck of the tube, and tend to shift easily if touched or inadvertently knocked while, perhaps, some other adjustment is being performed within the set. This possibility is well worth bearing in mind if the receiver embodies a tube with an ion-trap. An ion-trap magnet very rarely moves out of adjustment on its own accord, however, so the sudden disappearance of a raster should not always be associated with this cause.

At this point it may be instructive to consider the correct way of adjusting the ion-trap magnet. We will assume that the magnet is already on the neck of the tube with the arrow pointing towards the screen. The magnet should be carefully rotated until the arrow is immediately over the line marked on the tube neck. On Mullard tubes this line is nearly always in line with the position corresponding to pin number three on the base.

As an initial adjustment the magnet should be moved along the neck of the tube until it is slightly in advance of the tube base, and the following adjustments must be performed while the receiver is switched on, preferably during the transmission of the Test Card. With the brightness control set for screen illumination of *only just* workable intensity the magnet should be moved gradually towards the screen until the focused raster is at maximum brightness. During this operation care must be taken to keep the arrow marked on the magnet over the line on the neck of the tube. Without altering the position of the magnet readjust the brightness and contrast controls to give a picture of correct contrast ratio.

Finally, readjust the magnet along the tube axis for optimum picture brightness, and by means of the picture centring adjustments on the focusing unit ensure that the picture resolves in correct position on the screen. If it is found that the picture cannot be centred correctly by this means it is in order to rotate the magnet slightly to assist in this respect. It is extremely important to ensure, however, that no loss in illumination results by this adjustment; if it is noticed that the illumination is impaired the magnet **MUST NOT** be rotated.

(To be continued.)

Used Mazda C.R.M. 123 cathode heater short aluminized. Complete with rubber mask Elac P.M., focus unit, scan coils, low line, low frame and frame o.p. trans. £5.10.0 P. & P. 7s.

Used Mazda 12in. C.R. Tube 121, 121A and 121B, heater cathode short. £3.7.6. P. & P. 7s. Guaranteed 3 months.

Used Mazda 9in. C.R. Tube, heater cathode short. C.R.M. 91, 92 & 92A. Guaranteed 3 months. 37 6. P. & P. 7s.
Most of the above 9in. with ion burn 27 6. P. & P. 7s.

USED Mullard 12in. with ion burn 50-. P & P 7s.

P.M. SPEAKERS	with trans.	less trans.
3in.	13 6	13 6
5in.	16 6	12 6
6in.	16 6	12 6
8in.	18 6	15 -
10in.	19 6	19 6

Post and packing on each of the above, 1/- extra.

Line and E.H.T. Transformer, 9KVA using ferocart core complete with built-in line and width control. Mounted on Ali-chassis. Overall size 4in. x 1in. EY50 Rec. winding. P. & P. 2.6, 27 6.

Scan coils, low line, low frame, complete with frame o.p. trans. to match above line and E.H.T., 27 6. P. & P. 2.6.

Heater Transformer, Pri. 230-250 v. 6 v. 1 1/2 amp., 6 - 1 2 v. 2 1/2 amp., 5 -. P. & P. each 1 -.

Completely built Signal Generator. Coverage 120 Kc s-320 Kc s., 300 Kc s-900 Kc s., 900 Kc s.-2.75 Mc s., 2.75 Mc s-8.5 Mc s., 8.5 Mc s.-25 Mc s., 17 Mc s.-50 Mc s., 25.5 Mc s.-75 Mc s. Metal case 10 x 6 1/2 x 3 1/2 in., 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black

crackle finished case and white panel. £4.19.6. or 34/- deposit and 12 monthly payments 20-. P. & P. 4 - extra.

R. and A.T.V. energised 6in. Speaker, field coil 175 ohms. Requires minimum 150 mA to energise maximum current 250 mA. P. & P. 2 - 9 3.

Valve Holders, moulded octal Mazda, and octal, 7d, each. Paxolin octal, Mazda and octal, 4d, each. Moulded B7G, B8A and B9A, 7d, each. B7G moulded with screening can. 1 6 each. 32 mfd., 350 wkg., 2 -; 16 x 24 350 wkg., 4 -; 4 mfd., 200 wkg., 1 3; 40 mfd., 450 wkg., 3 6; 16 x 8 mfd., 500 wkg., 4 6; 16 x 16 mfd., 500 wkg., 5 9; 8 x 16 mfd., 450 wkg., 3 9; 32 x 32 mfd., 350 wkg., 4 -; 32 x 32 mfd., 350 wkg. and 13 mfd., 25 wkg., 6 6; 25 mfd., 25 wkg., 11d.; 250 mfd., 02 v. wkg., 1 -; 16 mfd., 500 wkg., wire ends, 3 3; 8 mfd., 500 v. wkg., wire ends, 2 8; 8 mfd., 350 v. wkg., tag ends, 1 6; 50 mfd., 25 v. wkg., wire ends, 1 9; 100 mfd., 350 wkg., 4 -; 100 200 mfd., 350 wkg., 9 6; 16 16 mfd., 350 wkg., 3 3; Ex-Govt. 8 mfd., 500 v. wkg., size 3 x 1 1/2 for 2 6; 60-100 mfd., 200 v. wkg., 7 -; 16 x 32 mfd., 350 wkg., 6 -; 50 mfd., 180 wkg., 1 9; 65 mfd., 220 wkg., 1 6; 8 mfd., 150 wkg., 1 6; 60 10, min., 200 wkg., 8 6; 50 mfd., 12 wkg., 11d.; 32-32 mfd., min., 275 wkg., 4 -; 50 mfd., 50 wkg., 1 9; Miniature wire ends moulded, 100 pt., 500 pt., and .001 ea., 7d.

Combined 12in. Mask and Escutcheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet, 17 6 P. & P. 2 -.

Frame Oscillator Blocking Trans., 4 6.

Smoothing Choke, 250 mA, 5 henry, 8 6; 250 mA., 10 henry, 10 6; 250 mA., 8 henry, 8 6.

P.M. Focus Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15 -. P. & P. 1 6.

P.M. Focus Unit for Mazda, 12in., with Vernier adjustment, 17 6 P. & P. 1 6.

Wide Angle P.M. Focus Units, Vernier adj., state tube, 25 -. P & P 2 -.

Energised Foral Coil, low resistance mounting bracket, 17 6. Plus 2 - P. & P.

Ion Traps for Mullard or English Electric tubes, 5 - post paid

T.V. Coils, moulded former, iron cored, wound for rewinding purposes only. All-in-one 1 1/2 in. x 1/2 in., 1 - each; 2 iron-cores All-in-one 2 1/2 in. x 1/2 in., 1 6 each

Terms of business - cash with order. Dispatch of goods within three days from receipt of order. Where cost and packing charge is not stated, please add 1 1/2 up to 10 -, 2 - up to £1 and 2 6 up to £2. All enquiries S.A.L. Ltd, 5d. each.

D. COHEN


RADIO AND TELEVISION COMPONENTS
23, HIGH STREET, ACTON, W.3.

(Opposite Granada Cinema)

Hours of Business - Saturdays 9-5 p.m. Wednesdays 2-1 p.m.
Other days 9-4.30 p.m.

The Famous
UNEX TELEVISION AERIAL
IS NOW ONLY

74'6"

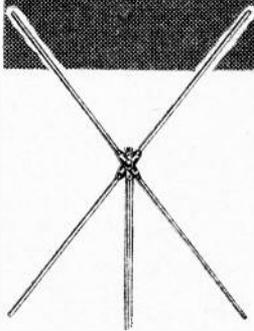

The popularity of the Unex has resulted in increased production which has enabled us to reduce the prices substantially. The outstanding features of the Unex are:-

- Easy fitting.
- Robust construction.
- 100% waterproofing.
- 3 dB forward gain.
- Light weight.

Unex 85S. Complete with 6ft. alloy mast, chimney bracket, etc., £3 14 6.

Unex 83K array only, £2.
Unex 83T complete with 10ft. x 2in. alloy mast, brackets, etc., £6 15 0.

Unex 83F complete with 11ft. x 2in. alloy mast, brackets, etc., £7 12 6.

Unex 83C with cranked arm, chimney brackets, etc., £3 14 6.

Above prices are for all vertical channels and 2 6 extra for horizontal channels.


BAND III

Aerial and downloads will be equally important for Band III reception - we design and manufacture both aerials and cables, so order Aerialite when the time comes.

The **DUBLEX**
High Grade Aerial

The Dublex has the highest gain (6dB) of any aerial in the same price bracket. It has particularly strong mechanical construction with special resilient mounting to prevent element breakage. The Dublex is available with cranked, 7ft., 10ft. or 11ft. chimney mounting masts and brackets.

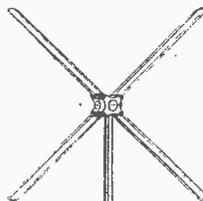
Dublex 77S (complete with 7ft. mast, brackets, etc.), £4 5 6.



Aerialite LTD.

CASTLE WORKS STALYBRIDGE CHESHIRE.

MAINTAINING A REPUTATION

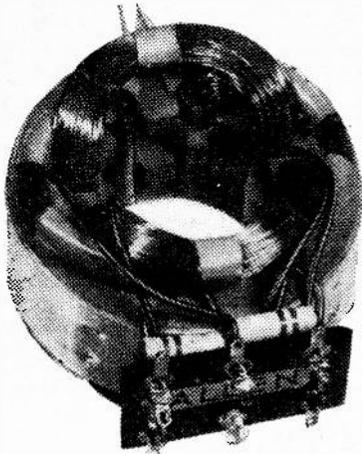

Deflector Coils type DC300/C. As specified for the "Teleging," "Supervisor" and "Magnavision." Conversion circuits for 14in. and 17in. C.R. Tubes available. Send 9d. and S.A.E.

Every day we read the words: "I am ordering Allen Components because they are so highly recommended by my friends."

We are proud of our reputation. Since we pioneered Wide Angle scanning some years ago we naturally carried on our policy of producing components designed to the highest specification and engineered to the closest tolerance. In these days of shortages and lowered standards such a policy is not easy to carry out and it has necessitated unrelaxed attention to detail in all our departments. The result of this care is apparent in all our products, in which good workmanship is combined with high reliability.

May we suggest you ask your friends ?

From all Leading Stockists.

ALLEN COMPONENTS LIMITED

Crown Works, Lower Richmond Rd., Richmond, Surrey

Telephone : Prospect 9013

Send 9d. and S.A.E. for Circuit Diagram


HENRY'S (RADIO LTD.)

We have over 20,000 American and B.V.A. valves in stock.

ALL VALVES NEW AND GUARANTEED.

SETS OF VALVES
 Ten EF50 (Ex-Brand New Units) 5/- each ... 45/- Set
 6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G (or KT61) ... 37/6 ..
 1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4) ... 30/-
 1S1
 TP25, HL23/DD, VP23, PEN25 (or QP25) ... 25/- ..
 6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 or 25Z6G ... 37/3 ..
 12K8GT, 12K7GT, 12Q7GT, 35L6GT or 50L6GT/37/3 ..
 12S17GT, 12SK7GT, 12S17GT, 35Z4GT, 35L6GT or 50L6GT 37/6 ..

CRYSTAL MICROPHONE INSERTS

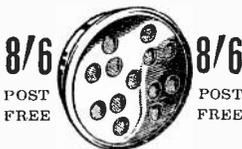

8/6 POST 8/6 POST
 FREE FREE

Ideal for tape recording and amplifiers. No matching transformer required.

RECORDING TAPE G.E.C.

600 feet Reels ... 10/-
 1,200 feet Reels ... 17/6

024A	7/-	6K8G	9/-	12SG7	7/6	EK32	6/6	S130	7/6
1G6	6/6	6K8GT	8/6	12SH7	7/6	EF91	9/-	7475 (VS70)	
1R7	8/-	6L8G	8/6	12SJ7	8/6	EL33	10/-		7/6
1S1	8/-	6U5	7/6	12SK7	8/6	EL42	7/6	CV68	6/-
1S1	8/-	6U5G	7/6	12SR7	7/6	EF50 (Rev. Svl.)	10/-	VR150/30	8/6
1T4	8/-	6L7	7/6	14A7	8/6		8/6	CK510AX	5/-
1C5	8/-	6N7GT	7/6	25Z6GT	8/6	EF50	10/-	D1	2/-
1LN5	8/-	6Q7GT	8/6	25Z5	8/6	SP2	8/6	AC6PEN	6/6
2X2	5/-	6S17GT	8/6	35Z4GT	8/6	VP2	8/6	AC5/PEND	12/6
3V4	8/-	6B7	8/6	25A8	8/6	DDD2A	8/6		12/6
3S4	8/-	6X5G	8/6	35L6	8/6	DK40	9/-	PEN25	6/6
5Z3G	8/6	6SA7GT	8/6	50L3GT	8/6	UL41	9/-	PEN46	7/6
5U4G	8/6	6S4Q7GT	8/6	42	8/6	UY41	9/-	QP25	6/6
5Z4G	8/6	6S97	7/6	43	8/6	4D1	4/-	SP61	4/-
6A7G	8/6	6SHTM	7/6	75	8/6	8D2	4/-	SP41	4/-
6AC7	8/6	6SK7GT	7/6	78	9/6	9D2	4/-	HL23/DD	6/6
6AC5	7/6	6SL7GT	9/-	80	8/6	R3	8/6	VP23	6/6
6A8G	8/6	6SN7GT	9/-	866A	15/-	D41	5/-	VP41	7/6
6AM6	9/-	85C7	10/-	9001	6/-	D42	5/-	U22	8/6
6B8	7/6	85S7	7/6	9002	6/-	D63	5/-	ATP4	4/-
6C4	8/6	6V8GT	7/6	9003	6/-	KT2	5/-	TP22	8/6
6CS5G	5/-	7C5	8/6	9004	6/-	U52	8/6	TH23	10/-
6C8	6/6	7A7	8/6	9005	6/-	U19	10/-	41MP	7/6
6D6	6/6	7C7	8/6	954	6/-	Y63	8/6	42SPT	6/-
6P6G	8/6	7H7	8/6	955	6/-	P2	4/-	21SSG	4/-
6G6G	6/6	7B7	8/6	956	6/-	MU11	8/6	MS/PENB	
6H8GT	5/-	7S7	10/-	1289A	7/6	PX25	12/6		7/6
6H8M	8/6	12A5	7/6	7Z40	37/6	KT33C	10/-	VT501	7/6
635GT	5/-	12C3	7/6	931A	50/-	KT88	12/6	AC/PEN(7)	10/-
6J6	9/-	12H5	8/6	EA50	2/-	GU50	12/6		10/-
6AK5	9/-	12K7GT	8/6	EF54	6/-	XP2V	4/-	PENDD4020	
6J7G	6/6	12K8GT	8/6	EB34	3/6	XH (1.5)	4/-	FC13C	12/6
6J7M	8/6	12Q7GT	8/6	EBC33	8/6	VU11	4/-	VP4(7)	8/6
6K6	9/-	12S4GT	8/6	EF36	6/6	VU133	4/-	ID5	8/6
6K7G	6/6	12S7GT	8/6	EF39	6/6	VU120 A	4/-	4THA	10/-

Brand New R.F. UNITS
 RF24 20-30 mc/s
 RF25 40-50 mc/s 15/- post free
 RF26 50-65 mc/s 19/6 post free
 45/- post free
SLIGHTLY SOLED
 RF24 ... 12/6
 RF25 ... 15/-
 RF26 ... 35/-

62A INDICATOR UNIT
 Complete with 12-EP50, 4-SP61, 3-EA50, 2-EB34 on Double-deck Chassis, V controls, Resistors, etc. In absolute New Condition. 69/6, carr. 7/6.

VCR157 Blue and White 6Pin Tube
 This Tube replaces the VCR97 and VCR157 without alteration and gives a full Blue and White picture. Brand new in original crates, 35/-, carr. free.

"428" CONTROL UNIT
 Containing 4-REDEF50, 2-SP61, 2-EA50, 1-EB34, 2-Single-gang .0005 Condensers, W.W. Vol/controls and Switches, etc. Size: 12in. x 9in. x 5in., 35/-, Carr. 3/-

"182A" INDICATOR UNIT
 - Complete with VCR157 and Screen, 3-EP50, 4-SP61 and 1-5U4G 9 w.w. controls. Ideal for TV or Scope. Brand New (less relay). In original cases. 67/6 plus 7/6 carr.

MORSE PRACTICE BUZZERS
 Morse tapper and 4 volt buzzer complete on baseboard, with battery and headphones. Brand New complete 15/- p.p., or less Headphones and Battery, 6/- post paid.


28-page Catalogue, 3d. Open Mon.-Sat. 9-6. Thurs., 1 p.m.

"Eurovision"—An 8-way Hook-up

SOME INTERESTING DETAILS OF THE INTER-CONTINENTAL RELAYS

DURING the Coronation celebrations last year the BBC made arrangements to provide pictures of the ceremony to viewers on the Continent. As an extension of the idea, and profiting by the experience gained during last year's relays, a more elaborate hook-up has been arranged and the map below shows the vast linkage which has been provided in order that eight countries may interchange programmes during the period from June

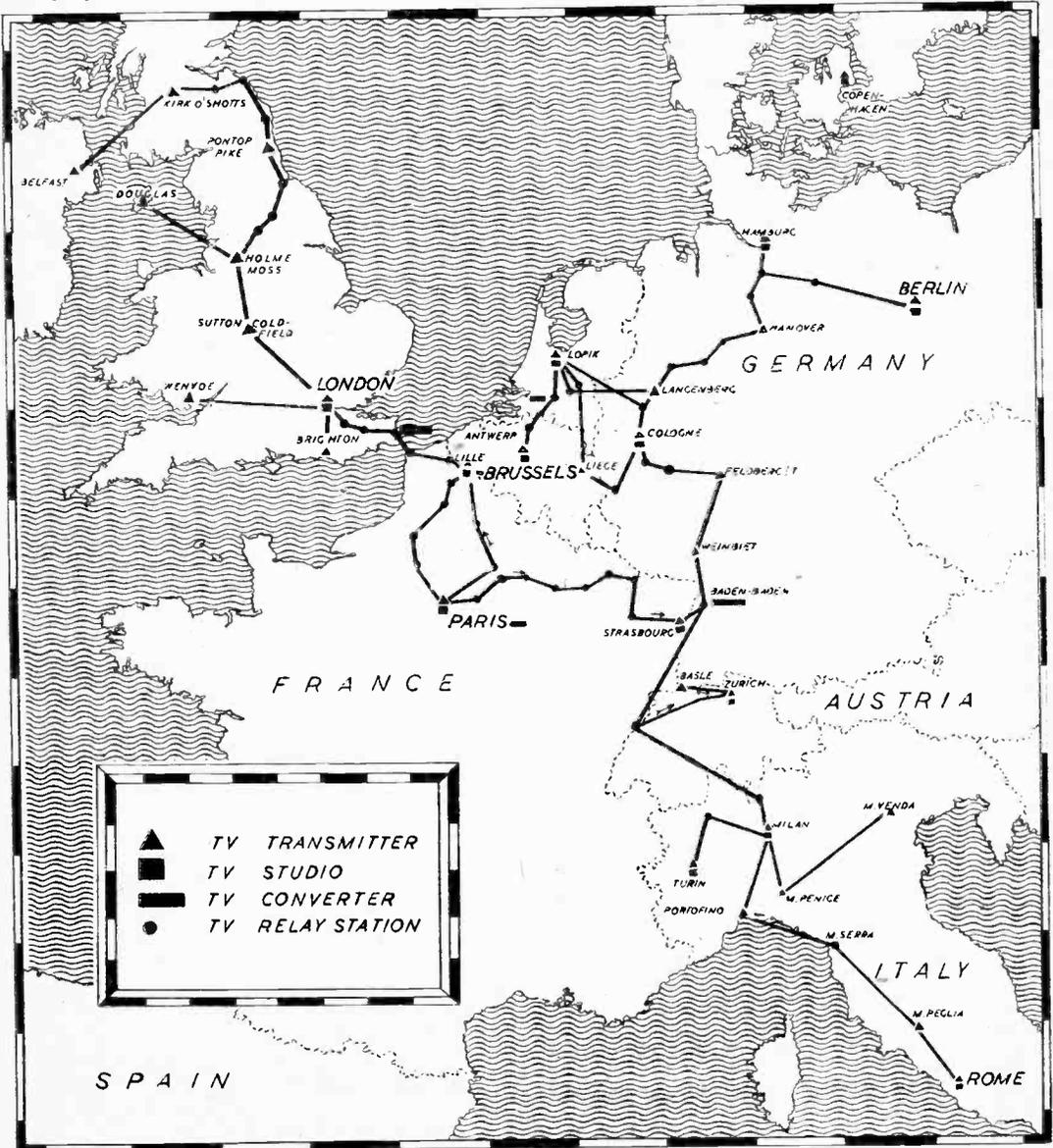6th to July 4th. It will be seen that in addition to those countries which participated in last year's relays there are now Switzerland, Italy and Denmark. The network will cover about 4,000 miles and will incorporate 44 transmitters and 80 relay stations as indicated on the map. Hamburg is now linked to Copenhagen via four relay stations situated on the intervening islands.



The major problem in arranging this interchange of stations is the different systems which are used in the various countries, an arrangement which it was at one time thought would prevent a satisfactory link-up. However, as with many major problems a simple way out was eventually found—consisting, in effect, of merely placing a receiver in front of a transmitting camera and photographing the received picture. Every one of the countries participating in this hook-up will be using some British equipment, and it is stated that the total value of such equipment will approach £2,000,000. This will include transmitters, cameras, studio apparatus, outside broadcast units and vehicles, various radio links, one of which will include a relay station 10,000ft. up on the Jungfrau, forming the link between Italy and Switzerland. In addition to the many items of equipment a large number of British radio engineers will also be employed to instruct foreign technicians in the use of the British equipment and in some cases will be retained to carry out the actual relay work.

M. Jean d'Arcy, the Director of Television Programmes, R.T.F., said: "This is an experiment with all kinds of technical and other difficulties to overcome, but it is the most ambitious undertaking yet in the history of television involving problems not met in the U.S.A. It points the way to a permanent exchange of television programmes in which Great Britain, through the BBC, and France, through the R.T.F., have been joint pioneers.

"In spite of the problems of the commentaries in different languages, television may be more likely than sound radio to make international broadcasting

a reality and to enable 'Nation to speak unto Nation'—in the words of the BBC motto. Our unique conference of eight nations has brought this a little nearer."

TV in Italy

There are centres for the production of programmes in Turin, Milan and Rome and transmitters in Torino-Eremo, Milan—Torre del Parco, Monte Penice, Portofino, Monte Serra, Monte Peglia, Rome—Monte Mario, Florence and Monte Venda. The important dates for Italian TV are September of 1949 when the first transmitter went up in Turin and at the same time a studio and transmitter went up in Milan. In March of 1950 a plan was presented to the Minister of Communications (Post Master General in England) for the organic distribution of the various transmitters and for a national network. In February of 1951 the national council of research asked that Italy should adopt the European standard of 625 lines. In May of 1951 the TV and Radio services were combined. In June of 1951 in Turin the first experimental TV shows were given, and in October of 1951 the first direct transmissions were made on outside sites. In April of 1952 the first real studio was set up in Milan in the Radio Palace, with a complete transmitter, and a micro-wave link between Turin and Milan came into being. In August the direct connection of metric-waves between Milan and Turin took place. In September of 1953 the connection between Milan and Rome was finished and Milan became the centre of Italian TV. On October 3rd, 1953, the large TV studio in Rome was finished.

Ghost Images

ELIMINATING REFLECTED SIGNALS

By S. Edmunds, A.M.T.S.

THE causes and effects of "Ghosts," as the multiple images due to reflected signals are so aptly termed, are well known, but the practical steps necessary to provide a remedy are not such common knowledge, and the purpose of this article is to explain the most effective methods of dealing with this trouble.

Many elaborate anti-ghost arrays have been evolved, and quite fantastic claims made for some of them, but in the writer's experience the most consistently effective is a three- or four-element fringe type consisting of the usual dipole, reflector and one or two directors. One advantage of this type over the double "H" or "X" arrays is that it offers less resistance to the wind and is considerably lighter. An attenuator is often necessary owing to the higher gain.

It is essential to have an assistant watching the receiver screen to notify the effect of movements of the aerial, and if the two are far apart it is well worth while to hook up an "intercom." This is easily improvised from a pair of earphones and a spare loudspeaker used as a microphone, amplified if necessary through the domestic radio receiver. Agreement upon a system of signals before going up to the aerial saves time and unnecessary repetitions of operations.

It helps a lot if the cause of the reflections can be determined first, and to this end a climb to the

highest part of the roof will enable an aerial view to be obtained. Note the direction and distance of any likely cause of reflections and rotate the aerial so that it "points" well away from it. Do not worry about the direction of the transmitter at this stage.

In addition to orientating the aerial about its vertical axis, tilting upwards sometimes helps, and in difficult cases even leaning it over to one side or the other may do the trick. In one particular case near the Truleigh Hill booster, a cure was eventually found by mounting a standard "H" horizontally.

Movement to another chimney stack should not be resorted to until other methods have been tried, as it often means lengthening the feeder as well as re-making the lashings, possibly requiring extra lashing wire or different lashings. Small increases in height are not usually of much avail, but may be helpful in "noisy" areas for reducing interference when, as is sometimes the case, the direction of least reflection is that of strongest interference.

A mismatched feeder can cause a ghost, but it must be very long before the ghost is displaced far enough from the true image to be visible as such. More often it is evident only as a slight blurring of the picture.

The foregoing remarks apply principally to those areas where outdoor aerials are normally used. In districts where an indoor aerial provides sufficient signal strength it should be tried in various positions about the house before a more elaborate outdoor array is resorted to. One of the indoor types with flexible elements is particularly useful for this purpose, or a simple substitute for testing is easily made from flex. The latter is not recommended for permanent use owing to its narrow bandwidth.

Line Circuit

Line oscillations are obtained in a very efficient single-valve transistor circuit. A single transformer is used which is overwound to provide E.H.T. (rectified by V9), and which incorporates its own inductive width control.

The valve used (an EL38) is caused to oscillate by positive feedback from the transformer winding feeding the deflector coils. The feedback is applied to the grid via C28.

The periodicity of the oscillations is controlled by the time constant of the grid circuit via R35, R36, C30 and R40.

Power Supply

The H.T. is obtained directly from the mains using the D.C. principle, the rectifier being connected to the top end of the auto-transformer. Secondaries of the auto-transformer feed the C.R.T. heater and the heaters of the remaining valves in the circuit.

Controls

Two variable controls are set into the front panel. They are the contrast control and the volume on/off control.

There is a sensitivity control fitted at the back of the receiver and which is pre-set. It is R3 and it controls both the sound and the picture. When setting up the television the following procedure is suggested. With the aerial

disconnected, adjust the brilliance control on the back of the receiver until the line-scan appears. Reduce it until the lines are just about visible. Now set contrast to zero and sensitivity to zero and plug in the aerial. Now advance the contrast to about one-third and then advance the sensitivity control until the picture is strong enough. Now adjust contrast and brilliance until the correct value of tones is obtained. Advance the volume control.

If it is found that insufficient volume is obtained, then L1 can be trimmed towards the sound channel, provided it does not spoil the quality of the picture. The sensitivity control can then be adjusted to make up for the loss in picture contrast.

At the rear of the chassis are various controls, as shown in Fig. 2. The line linearity is used for correcting horizontal distortion; the line-hold locks the picture horizontally and it will be found that these


two controls interact to a certain extent. Interaction is also liable to take place with the width control, which is a plunger fitted on the left rear side of the line transformer.

The sensitivity and brightness controls have been mentioned previously.

The vertical (frame) linearity controls the linearity of the vertical scan and should be adjusted in conjunction with the height control to prevent the top becoming elongated.

The vision interference limiter is in the form of a rotary switch. Unless interference is experienced the switch should be left in the minimum position. Where interference is experienced, the switch can be rotated to the second position and, where it is very severe, then it can be switched to the third position. The latter position should not be used if it can be avoided, as it is inclined to cut the peak whites and thereby introduces a certain amount of greyness into the highlights.

Vertical holding is accomplished by the frame (or vertical) hold control. This control also affects the interlace, and its correct positioning is critical. The control should be set while the lines of the picture are closely observed. The optimum position is where the horizontal lines are equidistant, and it will be found that this is on the threshold of picture slip. The lines should not appear in pairs but should

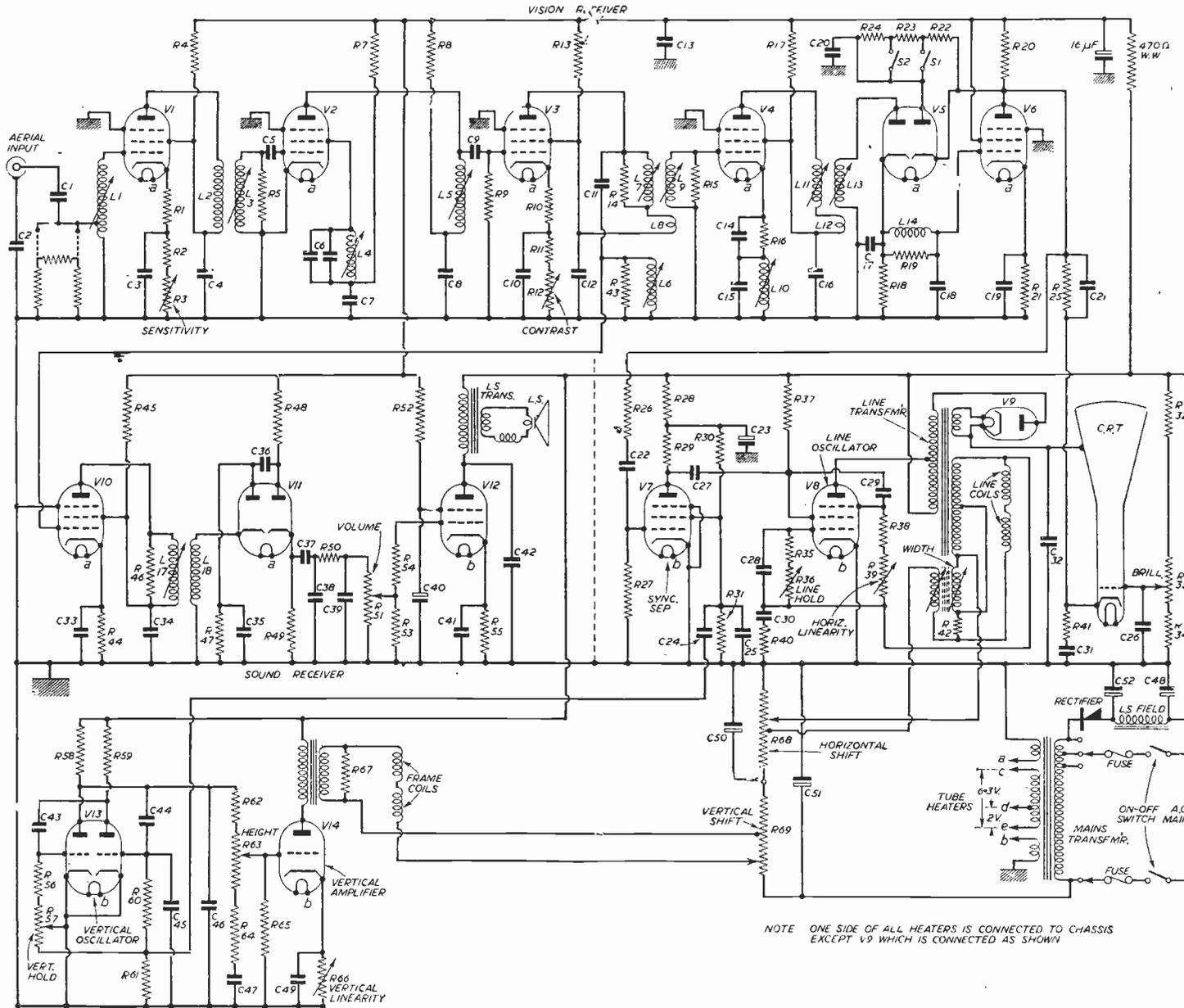

Circuit of the Plessey Mark II Chassis.

COMPONENT VALUES

RESISTANCES	R35—220 Ω
R1—39 Ω	R36—1 K Ω
R2—120 Ω	R37—6.8 K Ω
R3—10 K Ω	R38—47 K Ω
R4—1.5 K Ω	R39—50 K Ω
R5—6.8 K Ω	R40—5 K Ω
R6—22 K Ω	R41—100 K Ω
R7—100 K Ω	R42—2.2 K Ω
R8—1.5 K Ω	R43—68 K Ω
R9—2.2 K Ω	R44—150 Ω
R10—39 Ω	R45—1.5 K Ω
R11—120 Ω	R46—68 K Ω
R12—10 K Ω	R47—68 K Ω
R13—1.5 K Ω	R48—1 M Ω
R14—5.6 K Ω	R49—1.5 M Ω
R15—5.6 K Ω	R50—47 K Ω
R16—150 Ω	R51—2 M Ω
R17—1.5 K Ω	R52—2.2 K Ω
R18—5.03 K Ω	R53—470 K Ω
R19—47 K Ω	R54—10 K Ω
R20—6.8 K Ω	R55—180 Ω
R21—330 Ω	R56—47 K Ω
R22—470 K Ω	R57—1 M Ω
R23—1 M Ω	R58—1.5 M Ω
R24—3.3 M Ω	R59—100 K Ω
R25—330 K Ω	R60—100 K Ω
R26—10 K Ω	R61—100 K Ω
R27—1 M Ω	R62—1 M Ω
R28—47 K Ω	R63—1 M Ω
R29—15 K Ω	R64—470 K Ω
R30—100 K Ω	R65—2.2 M Ω
R31—100 K Ω	R66—5 K Ω
R32—15 K Ω	R67—470 K Ω
R33—50 K Ω	R68—10 Ω
R34—15 K Ω	R69—10 Ω

COMPONENT VALUES

CONDENSERS	C35—50 pF
C1—100 pF	C36—.01 μF
C2—.005 μF	C37—.01 μF
C3—.001 μF	C38—500 pF
C4—.001 μF	C39—500 pF
C5—100 pF	C40—16 μF
C6—30 pF	C41—25 μF
C7—.005 μF	C42—.002 μF
C8—.005 μF	C43—.05 μF
C9—100 pF	C44—500 pF
C10—.005 μF	C45—.002 μF
C11—2 pF	C46—.05 μF
C12—.005 μF	C47—.02 μF
C13—.05 μF	C48—100 μF
C14—.005 μF	C49—100 μF
C15—650 pF	C50—1,000 μF
C16—.005 μF	C51—1,000 μF
C17—5 pF	C52—64 μF
C18—5 pF	C53—.01 μF
C19—750 pF	
C20—.05 μF	VALVES
C21—.1 μF	V1—6F1
C22—.1 μF	V2—6F1
C23—16 μF	V3—6F1
C24—.05 μF	V4—6F1
C25—.005 μF	V5—6D2
C26—.05 μF	V6—6F1
C27—200 pF	V7—6F1
C28—25 μF	V8—EL38
C29—300 pF	V9—EY51
C30—.002 μF	V10—6F1
C31—.1 μF	V11—6D2
C32—.001 μF	V12—6P25
C33—.005 μF	V13—6SN7
C34—.005 μF	V14—6L18



Pages from a TELEVISION ENGINEERS Notebook

17—FREQUENCY CHANGERS

ALTHOUGH the double-triode type of television mixer stage was discussed previously in this series and finds use in many home constructed televisions, there are several other forms of mixer suitable for television superheterodyne receivers which merit attention.

The mixer stage of any superheterodyne is made up of two basic parts: the mixer proper, or modulator which produces the intermediate-frequency output, and the local oscillator. In television techniques particularly, the oscillator must be quite stable in frequency, and must be unaffected by reasonable changes in temperature likely to be experienced in the actual receiver cabinet. A separate oscillator tends to be best from this point of view, and combined valves, such as the triode-hexode, are not so common now as they were before the war. The double-triode is, of course, a combined valve in one sense, but the oscillator is strictly separate and the single glass envelope simply encloses the distinct systems. This article will therefore be mainly concerned with the mixer stage proper, the oscillator being ignored for the time being.

General Principles

Frequency changing is basically the low percentage modulation of the local oscillator frequency by the aerial or signal frequency; the signal frequency may or may not be amplified before reaching the mixer stage, although in television, a single R.F. amplifier is almost invariably employed. One of the resulting sidebands of the modulating process is used as the intermediate frequency, the two sidebands produced, of course, being the signal frequency plus and minus the oscillator frequency. Mixing is carried out in one of three ways: in the type of valve known as the hexode or pentagrid, the signal is placed on one grid and the oscillator output on another; the signal grid may be nearest the cathode, as shown in Fig. 1(a) or it may be a later electrode as shown at (b). In the third form, signal and oscillator frequency are applied to the same electrode such as is shown in Fig. 1(c), and mixing results from the characteristic curvature of the valve. For a fuller explanation of this process, you should refer to Part 3 of the present series. The conversion operation of all three mixer types can be readily analysed from the signal grid to plate transconductance g_m plotted against the oscillator grid voltage curve, and this is true even when combined valves such as triode-hexodes are used.

Such analysis shows that the conversion conductance of a triode with signal and oscillator voltages applied to the grid is equalled only by the hexode connection of Fig. 1(a), although the triode is usually the quieter in operation. If a pentode is used as a mixer with both inputs applied to the control grid, the conversion conductance is about four-fifths of that obtainable from the triode, but the noise is greater, fluctuations in the current distribution between the screen and anode being part of this. The only serious disadvantage of the triode over the pentode is that feedback occurs in the former and must be taken into account. The I.F. tuned circuit in the anode is capacitive at the signal frequency, the input resistance is low at this frequency, and the feedback will tend to step up noise. The input damping will be small, however, if the anode-grid capacity is negligible in comparison with the I.F. tuning capacity, but this is not always the case. If the receiver uses no R.F. stage, the pentode form is probably to be preferred.

The mixer circuit of Fig. 1(b) has a conversion conductance about half that of either the above, but it is difficult to compare this form of circuit with those because there is no direct dependence of the signal-grid characteristics on the cathode and oscillator-grid configuration. Noise is inclined to be greater, but if a suppressor is added (hexode

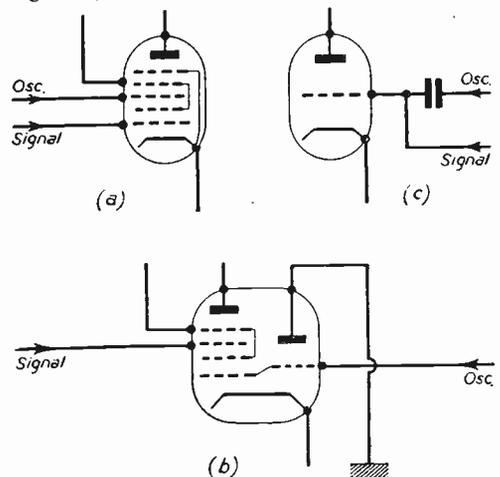


Fig. 1.—Mixer circuits suitable for television receivers.

construction) to eliminate secondary emission, the remaining noise is primarily that of current distribution and is not much worse than that of the pentode form. Loading of the input circuit is negligible with this mixer.

The remaining difficulty with the triode and pentode forms of mixer is that of interaction of the signal and oscillator circuits. This interaction can lead to radiation from the stage, thereby becoming a nuisance to nearby apparatus, and alignment troubles, pulling as this is more generally called.

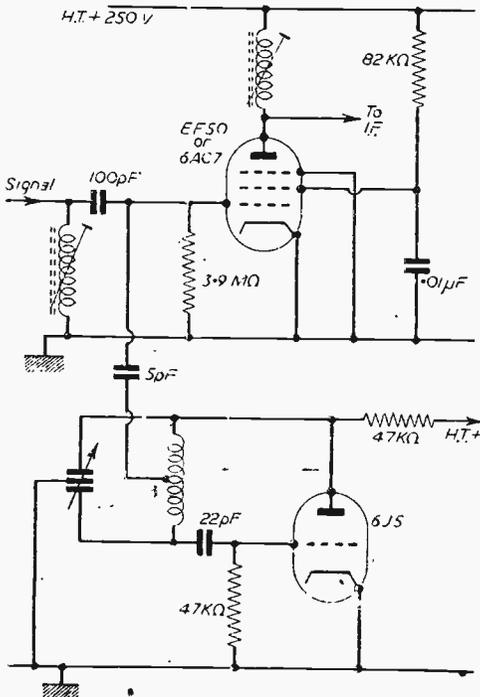


Fig. 2.—A practical mixer circuit using a pentode as a mixer with separate triode oscillator.

Interaction is, of course, greatest when the voltages are applied to the same electrode in the valve: to overcome this difficulty, very loose oscillator coupling has to be employed, but this is no disadvantage in its way, since the oscillator voltage required is generally quite small.

Although, then, none of the forms of mixer discussed meet all the requirements of television practice, the triode or pentode with the signal and oscillator frequencies applied to one electrode will produce the greatest gain and lowest noise figure, and are to be particularly preferred where there is no previous R.F. amplification.

A Practical Design

A practical circuit suitable for the home constructor is shown in Fig. 2, this using a pentode as mixer with a separate triode oscillator. Surplus valve types are employed, as these are most readily available at low cost. A few notes will be given on the design considerations of this circuit.

We note first of all the method of obtaining bias for the pentode, which is by means of a high time-

constant grid C.R. circuit, a 100 pF condenser and a 3.9 MΩ resistance. The point of this form of bias is to make the mixer stage as little dependent as possible upon the amplitude of the oscillator voltage. This applies particularly in receivers having a switched oscillator stage (five-channel models, for example), as variations in oscillator output at the various frequencies is then unavoidable. Further, it is desirable never to let the oscillator voltage swings carry the mixer valve into grid current.

Automatic bias of the type illustrated in Fig. 2 is derived from rectification of the oscillator voltage, the grid being driven negative by an amount depending upon the oscillator amplitude. This steady bias will be removed if the oscillator stops working, however, and so the screen must be fed from a high resistance. This resistance assists even further in the independence of gain with oscillator amplitude, although its presence will increase the noise very slightly.

The actual oscillator is of little importance provided that it is stable with temperature changes, etc., and in the figure the common Hartley is shown. The output is tapped down this coil and fed through a small condenser, thus reducing the possibility of interaction between the circuits. The tapping point can well be about a quarter-way up from the grid end of the coil.

HONOUR FOR PIONEER

ON April 29th the high award of the Faraday Medal of the Institution of Electrical Engineers was presented to Mr. Isaac Shoenberg.

This award has been made to Mr. Shoenberg for his outstanding contributions to the development of television in this country.

The great success of the television Coronation programme last year was to a considerable extent the result of his pioneering work and it was with this in mind that the Council of the Institution decided that it would be appropriate while thoughts of the Coronation were still fresh to award him the Faraday Medal of the Institution.

Mr. Shoenberg led the team of scientists at E.M.I., Hayes, who developed the television system and ancillary equipment adopted by the BBC in 1936.

The Emitron


His development of the electronic picture tube known as the Emitron contributed perhaps more than any other single item to the success of the new system.

Later, in 1937, Mr. Shoenberg was able to offer the Post Office and the BBC transmission equipment including special cables and repeaters which enabled the Coronation Procession of King George VI to be televised.

Since then E.M.I. have supplied the British Broadcasting Corporation with considerable additional television equipment including many Emitron cameras of advanced types, film scanners and other studio equipment, outdoor television apparatus, high power vision transmitters and microwave television links which are facilitating the reception of television broadcasts from various parts of Europe.

The occasion of this award to Mr. Shoenberg is a reminder, too, of the foresight and imaginative investment of considerable capital in these early days by the E.M.I. Company under the late Mr. Alfred Clark.

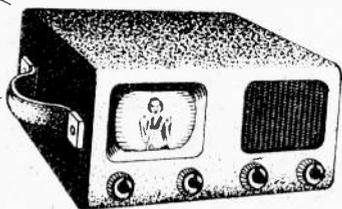MINIATURE PORTABLE T.V. YOUR LAST CHANCE TO MAKE THIS MAGNIFICENT TELEVISOR RADIO & GRAMOPHONE



You can probably think of many other reasons when you may need a midget television, but it will certainly be useful when—

- (a) Someone is ill, or confined to another room.
- (b) Your big T.V. fails.
- (c) You want to alter or adjust your big T.V.
- (d) The commercial programmes start.
- (e) Servicing an aerial installation.

The Elpreq Miniature Television uses standard conventional circuitry, employing a total of 13 valves and 2 crystal diodes. The cathode-ray tube used is a 2 1/2 in. Service type VCR139A, which has a standard equivalent and will therefore always be obtainable. The layout is extremely clean, straightforward and professional. The wiring, whilst naturally being a little more intricate due to miniaturisation, is nevertheless completely accessible, and very good results have been obtained.

The total cost, if you have to buy every part, would come to £16-£17, but you may have many of the components already in stock, as only standard conventional components are used. A carrying case, similar to the artist's illustration above, will be available shortly. Its size will be approximately 9 1/2 in. x 8 in. x 6 in. (internally). Full construction data, layouts, diagrams, templates, etc., running into some 50 sheets, is available, price 5/-, post free.



A circuit for a suitable radio unit to fit into our Coronation Console Cabinet has now been completed and thoroughly tested. All the parts are available. The total cost is £5.19.6. Data is included free with orders for parts, or can be supplied separately. Price 2/6. Note: This radio unit incorporates T.V. control and is also highly suitable for fitting into other televisions. The addition of a radio unit to a television is not only worthwhile but is essential where the television is kept in a room away from the main radio. The Superior 15 Corner Cabinet (illustrated) is also available now in light oak, or medium oak to suit your furnishings,


and it really does look impressive. The price is £18, plus carriage. H.P. terms £6 deposit, balance over 12 months. About the Superior 15 itself, if you have not already ordered your set of parts for this, be advised and do so immediately. We are definitely getting down to the last batch of the 15 in. tubes and once these are gone the Super 15 T.V. cannot be repeated. At £37.10.0 for all the parts (including 15 in. Cosor Tube) this represents the finest value ever offered to the home constructor. If you doubt your ability to make it, then send 7/6 for the data and study this first. Don't forget, we guarantee to help you to get perfect results and, if necessary, for nominal charge, will take in your television, completely check over your work, and return it to you in perfect order.

THE STROLLER




A new booklet for Constructors, shows how to make a sensitive and powerful superhet battery portable, which will be just the thing to take on a day out or on your holidays. The booklet also shows how to make the Picnic Player, a useful battery-driven record player. The price of the booklet is 2/6, which is returnable if component parts are purchased.

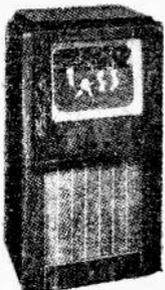YOUR LAST CHANCE TO SECURE A REAL BARGAIN



This cabinet is offered below cost. It is suitable for a television using tube sizes varying from 12 in. to 17 in. its overall dimensions being 31 in. 5 in. high, 1 ft. 4 in. deep, 1 ft. 10 in. wide. It is complete with plywood back and "Bowler Hat." Originally made for a very expensive television and really good quality. Unrepeatable. Offered at £7.5.0, carriage, packing, etc., 12/6. Note: These are cut for 12 in. tubes, but the holes for the controls are not drilled.

7 WAVEBAND ASSEMBLY

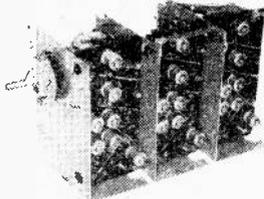


7-wave coil pack for up to 11 meters with R.F. stage, three-gang tuning condenser, slow-motion drive, I.F. transformers and numerous other parts, make a really fine receiver. Price £6, plus 10/- post and insurance.

Note: The above are new. Lut removed from chassis.

TRULY PORTABLE INTRODUCING THE CLEVELAND SPRINGBAT RECORD PLAYER



To be truly portable, a record player must be independent of the mains. Owing to the cost and weight of dry batteries, however, it is not advisable to use a battery motor. Fortunately, at the picnic and other functions, when the player is most needed, there are plenty of willing hands to wind. Therefore a spring motor is no objection. The Cleveland portable Record player combines the true and full response of electronic recording with the convenience of a modern spring-wound motor, hence its name "Springbat" it is also very nicely put together in a handsome carrying case. Price complete ready to work (des. batteries), £13.13.0 or £4.11.0 deposit, carriage free. Batteries, 10/7 the two.

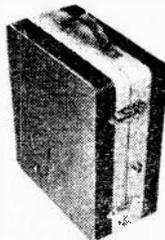

FREE BOOKLET

Our booklet Handy Hints gives tips for Carpenters, Mechanics, Engineers and Gardeners. Fully illustrated, and it is yours for the asking. Send stamp to-day.



ELECTRONIC PRECISION EQUIPMENT, Ltd.

Post Orders should be addressed to: (Dept. 5), ELPREQ HOUSE, HIGH STREET, WEALDSTONE, MIDDLESEX. Personal shoppers, however, should call at any of our following branches: 42/46, WINDMILL HILL, RUISLIP, MIDD. 29, STROUD ROAD, FINSBURY PARK. 151/153, FLEET STREET, LONDON, E.C.4.

TELEVISION PICK-UPS AND REFLECTIONS

UNDERNEATH THE DIPOLE



By Iconos

MOST of us have rather got out of the habit of going to the theatre and seeing real actors ("in person!") appearing in plays. We have all become so used to gazing at their shadows on TV and cinema screens that the flesh-and-blood originals seem to be somewhat smaller than life: sharp-focused coloured characters moving about in permanent long-shots and mumbling incoherently. That, at any rate, is the opinion of the younger generation, brought up in this electronic age of perpetual magnification in entertainment. Poor voice production on the stage could not be tolerated in the days before public address amplification, when singers sang instead of crooning and actors had to pitch their voices so that even the back rows of the gallery could hear every whisper.

"SUCH MEN ARE DANGEROUS"

CHANGING styles of theatrical interpretation are well illustrated when one is able to see old stage plays re-presented on television. The TV version of Ashley Duke's *Such Men are Dangerous* recalled for me a youthful visit to the theatre in the early twenties when I was enthralled by the magnificent portrayal of Count Pahlen by the late Mathieson Lang. This fine actor obtained many of his most dramatic effects by gestures and dialogue delivery which might now be considered by many to be too broad. How wonderful were those theatrical gestures, so typical of a time when actor-managers were the most important men in the London theatres. Then I saw a silent film of the same story, in which Lewis Stone played Pahlen in a rather restrained but most effective manner and, later on, a French talking film in which the dialogue was translated with subtitles. I therefore awaited the TV version with considerable interest—and I was not disappointed. Stephen Murray's interpretation of Pahlen was in keeping with the new medium—restrained, quiet but strong. Theatrical gestures were avoided and close-ups demonstrated the

many shades of meaning which can be conveyed by the eyes alone. Under Rudolph Cartier's polished direction, Mr. Murray's performance was ideally suited to the intimacy of television. Time marches on! Thirty years ago older playgoers sighed over the restrained acting of Mathieson Lang, recalling the robust declamatory manner of Irving and Tree.

LENGTHY PLAYS

Such Men Are Dangerous was a very long play—two hours, including a short interval. If it had faults, the principal one was its great length—though I was myself gripped by it almost all the time. Another costume play, *Beau Brummell*, by Anatole de Grunwald, was half an hour shorter, but, lacking the story value of the Pahlen play, seemed to drag a little in parts. Here again, Peter Cushing's interpretation of the arrogant dandy of Regency days was restrained and intellectual in style, far removed from the romanticism of John Barrymore's portrayal many years ago. I cannot remember the detail of the Barrymore film but it seemed to me that Mr. de Grunwald introduced entirely new characters, especially that of the unfashionable country girl, Georgina Seymour, beautifully played by Daphne Slater. Campbell Logan's production was smooth and the technical values were first class. These costume pieces come over very well indeed and by comparison the more modern TV plays seem to creak with age. *Ambrose Applejohn's Adventure*, for instance, had little shape, form or wit and seemed more suitable as a vehicle for the clowning of a slapstick comedian than the well-known and loved "Housemaster" style of Jack Hulbert. It was difficult to believe that this play ran successfully for many months in

a West End theatre, when Charles Hawtrey played the leading part. I suppose the light comedies of Seymour Hicks, enormously popular in their heyday, would suffer the same fate on TV.

MUSIC ON TV

MOST viewers concede that music, as such, belongs to sound radio, and only on rare occasions do they become enthusiastic about straight presentations on TV of bands and orchestras. The sight of rows of musicians playing *en masse* does not usually excite, even when the blurry long-shots are relieved by odd close-ups of individual instrumentalists or the conductor. There are exceptions, of course, and Vic Oliver's shows and "Music For You," for instance, are admirably handled by the producers. My pet aversions are the jazz-band gentlemen who introduce alleged "funny" gags in between or during their musical numbers. Generally speaking, the less they say, the better. If their bands are really good, they should cut down the patter. *The Glenn Miller Story*, a film in which 22 full musical numbers are admirably put over, was excellent both in its cinema form and in its sound radio excerpts. Here, the chief factor for success was in the varied methods of musical presentation used in one film with introductory dialogue readily adaptable for cueing in musical numbers on sound radio. I realise the difficulty of varying the clothes, settings and even the constitution of a band during a live TV transmission. This difficulty might be overcome by generous use of film for alternate sequences with live transmissions.

OLD CROCKS?

SOUND radio has given a clear exposition of the subtle differences of the adjectives "Veteran," "Vintage" and "Edwardian" as applied by enthusiasts to the extraordinary and rather special automobiles seen on the Brighton runs and other club gatherings. It has occurred to me that these adjectives could be appropriately applied to many of the TV plays we have seen lately, though in some cases one could substitute the

disrespectful description of "old crock." T. W. Robertson's play *Caste* seemed to come into this last category, with its contrived plot, its asides and its exaggerated characterisation. And yet there lingered a great deal of charm in this old play. Unfortunately, museum pieces cannot stay the pace and a running time of one hour 25 minutes was a little too long, despite the good performances of Sarah Lawson and Jill Bennett as the Eccles sisters and Mervyn Johns as their father. It was a play designed for a theatrical age of exaggerated gestures, declamatory speeches and that insinuating device for conveying plot points to the audience—the stage "aside." Too good for burlesquing and too naïve for underplaying in the modern style, *Caste* was played just a little too straight to make the grade. Nevertheless, the bright and vigorous hoydenish performance of Jill Bennett will linger in the memory for a long time.

"JEANNIE"

AIMEE STUART'S play *Jeannie* is not old enough to be a museum piece and yet it seemed to belong to a far-off theatrical era. In the title rôle, Barbara Mullen played the part of a woman from a Scottish village who decides to spend the whole of a small legacy on one grand holiday in Vienna to give her memories to store up for her old age. Her adventures in that gay city with an impecunious count and a Yorkshire business man provide an enchanting series of episodes leading up to an entirely satisfactory and happy ending. Naturally, Eric Portman played the part of Stanley Smith, the blunt but kindly Yorkshireman. It would have been difficult to think of anyone else playing the part after his success as the Yorkshire politician in *His Excellency*. It might well have been difficult to follow the dialogue with Scottish and Yorkshire dialects mingled with the broken English of the continental characters, but David Macdonald and Dennis Vance, director and producer respectively, kept the accents at a reasonable level that could be understood by all. This TV play ran for one hour 30 minutes; still on the long side, but the interest was held by the very fine performances of Barbara Mullen and Eric Portman. Back-projection and other technical devices were used in the train sequences and else-

where to great advantage, and the whole production had a smoothness and polish which put it in the top class. *Jeannie* was a vintage play, worthy of a repeat in a year or two.

FAMILY FARE

MUCH more in the modern "Mrs Dale" or "Archers" family saga style was *It Never Rains*, by Lynne Reid Banks. Once again were we given a regional play set in Yorkshire, with Olga Lindo and Carl Bernard playing the parts of parents of three children having widely differing temperaments, and their personal problems, ambitions and troubles provided an entertainment that lasted for one hour 55 minutes. Again the play was a little too long, in my opinion—especially as the action was restricted to the kitchen of the Boltons' house. Producer Douglas Allen kept the camera on the move with expert handling, emphasising points without too much dependence on cutting from camera to camera. Incidentally, I am puzzled by the fact that this play was handled by a producer only, whereas others seem to call for a director as well as a producer. In film production the director is the man on the studio stage who instructs the actors while the producer sits in an office (or a private theatre) exercising his judgment on the artistic and commercial angles of the script, the selection of artistes, design of settings and editing of the film. In the theatre the producer directs the artistes in their performances and supervises all the technical presentation. Just what is the difference between a TV producer and a TV director? Then, of course, there is that other mysterious executive whose function is signified by the fact that he "presents" this or that TV play or feature. I must say that it conjures up for me a vision of a dominating gentleman behind a large desk mumbling wise and hypnotic words behind a large cigar.

TV PLAY ARCHIVES

I HOPE that photographic records are being made of some of these plays, even if they are only kept in the BBC archives for reference. Both 35 mm. and 16 mm. film recordings are available,

of course, but are expensive if the resultant film record is not used for a public repeat performance. Meanwhile, great progress is being made with magnetic recording of pictures.

MAGNETIC RECORDING OF TV

IT still seems hard to believe it possible that good television pictures can be recorded on magnetic tape. And yet it has been done, and done very well, according to a friend who has seen what has been achieved at the Princeton Laboratories of the R.C.A. Compared with the problems of recording sound on magnetic tape, the demands of picture recording are enormous. For instance, the recording of a 4 megacycle-per-second signal on tape travelling at 30ft. per second results in a wavelength on tape of less than 1/10,000 of an inch. On the other hand a 100-cycle note recorded on the picture magnetic recorder has a wavelength of 4in., whereas on an ordinary 15in. per second sound magnetic recorder the same frequency would have a wavelength of less than 1/10in. This imposes immense problems in the design of recording and reproducing heads, particularly when a recording is intended to be reproduced on an entirely different reproducing machine. Azimuth settings require very fine adjustment to avoid losses in reproducing performance on account of excessive ground noise levels; on low-frequency sounds recorded at this very high speed it has been found desirable to use a high-frequency carrier, modulated in amplitude by the audio-frequency signals. For colour television recording the present R.C.A. standards are a ½in. tape travelling at 30ft. per second carrying five tracks in the following order: blue information; red information; sound; green information; synchronising signals. For black-and-white ½in. tape is used, with one track for picture and one for sound, the latter being recorded with a modulated carrier. Results of pictures from magnetic recordings were practically as good as the direct pictures, both in colour and black-and-white. The cost of recording pictures on tape is claimed to be less than 10 per cent. of the cost of recording on film.

VIEWMASTER

LONDON — MIDLAND — HOLME MOSS — KIRK O'SHOTT'S — WENVOE — PONTOP PIKE — TRULEIGH HILL — ISLE OF MAN — ROWBRIDGE (ISLE OF WIGHT).

Constructional envelope with fully illustrated manual, full size diagrams and operating instructions for building on the ready-drilled chassis with simple tools in 7 easy stages from guaranteed new, as specified, components—a first-class 9in. or 12in. tube television in table or console form, 7/6. Constructional envelope for modifying to 16in. or 17in. big-picture tube, 3/6.

W.B. COMPONENTS.—WB200 Sound and Vision drilled chassis with all valveholders and grommets mounted, 18/6; WB101 Chassis Support, 6/-; WB102 Power Pack drilled chassis with all valveholders mounted, 18/6; WB103 Heater Transformer, 42/-; or WB103A Heater-auto Transformer, 52/6; WB104 Smoothing Choke, 15/6; WB105 Special T.V. type Loudspeaker, 43/6; WB106 Frame Transformer, 23/6; WB107 Line Output Transformer, 32/6; WB108 Scanning Coil, 33/3; WB109/1 Focus Ring for C.R. Tubes, except Mullard and Mazda, 22/6; WB109/2 Focus Ring for Mullard Tubes, 22/6; WB109/3 Focus Ring for Mazda Tubes, 22/6; WB110 Width Control, 7/6; WB111 Boost Choke, 5/9; WB112 C.R. Tube supports, 21/6; WB300 Pre-amp chassis, 17/6; 12in. Console Conversion kit, 35/-.

Wide Angle Components.—WB113 Line Transformer, 48/6; WB114 Frame Transformer, 23/6; WB115 Scanning Coil, 42/-; WB116 Width Control, 7/6; WB117 Linearity Control, 7/6; WB118 Focus Ring, 22/6; WB119 Heater Transformer, 18/6.

WEARITE COMPONENTS.—Complete set of coils and type L9 choke; Model "A," 22/-; Model "B," 30/-; Model "C," 30/-; Model "D," 30/-; Model "E," 28/-.

Pre-amp coils, all models, 4/- pair.

WESTINGHOUSE RECTIFIERS.—14A86, 20/4; 14D36, 11/7; 36EH100, 29/5; 36EH130, 17/6; WX3, 3/9; WX6, 3/9.

ALL OTHER PARTS AVAILABLE. VIEWMASTER LIST FREE ON APPLICATION.

Postage and packing extra on orders under £2. 54-page illustrated Catalogue No. 8, post free.

Southern Radio & Electrical Supplies

SORAD WORKS

REDLYNCH : SALISBURY : WILTSHIRE


Telephone : Downton 207

Armstrong

(Specialists in Chassis manufacture for over 20 years)

11" and 17" Television Chassis for the Amateur Constructor

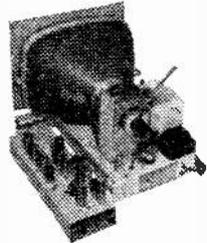PROVISION IS NOW MADE FOR A 13-CHANNEL ADAPTOR WHICH WILL BE AVAILABLE AT A NOMINAL CHARGE WHEN REQUIRED



Incorporating all the very latest in design, these chassis give you a TRUE BLACK AND WHITE PICTURE. Both Models are similar in general specification, having 19 Valve Superheterodyne Circuits with instantaneous 5-channel selector switching and aluminium rectangular, flat-faced Cathode Ray Tubes with tinted filter.

Chassis showing easy removal of "RF & AF" strip

PRICES

T.V.5. 14in. Chassis, £54.0.3. T.V.5.17in. Chassis, £64.15.11. Both prices including Purchase Tax.

Available with or without a loudspeaker. Also available complete in handsome table and console cabinets.

ARMSTRONG WIRELESS & TELEVISION CO. LTD.

WALTERS ROAD, HOLLOWAY, LONDON, N.7.
Telephone : NORTH 3213/4

NEW!

EXPERIMENTAL OUTFITS

LEARN THE PRACTICAL WAY

Specially prepared sets of television parts (which you receive upon enrolment) with which we teach you, in your own home, the working of circuits and bring you easily to the point when you can construct and service a television set. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — this Practical Course is intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM £1 A MONTH

A tutor is available to give individual help and guidance throughout the Course.

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:

I am interested in.....
To: E.M.I. INSTITUTES, Dept. 138X, 43 Grove Park Road, Chiswick, London, W.4.

NAME.....

ADDRESS.....

6/54.....

EXPERIMENTAL OUTFITS:

TELEVISION — Instruction and equipment for building a Television Receiver.


RADIO 1 — A course in basic principles.

RADIO 2 — Instruction and equipment from which you build a Radio Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.

E.M.I. INSTITUTES

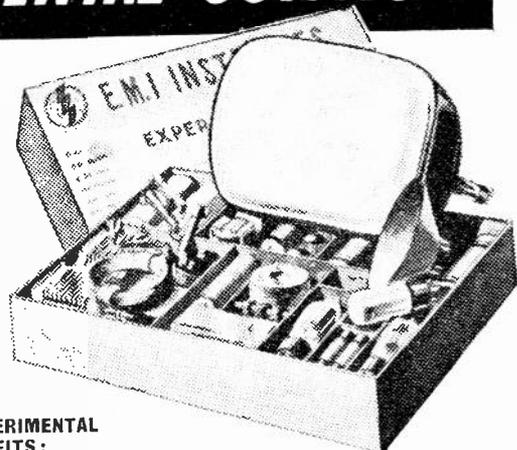The only Postal College which is part of a world-wide Industrial organisation.



BUILDING THE "SIMPLEX"?

Thousands of enthusiasts are building the "Simplex" Television, now being featured in "Practical Television". WHY NOT YOU? CONSTRUCTOR'S ENVELOPE, containing full constructional details and Blue Print, additional notes and suggestions, and Query Service form, sent for ONLY 5/- All components available ex stock as follows:

ALUMINIUM CHASSIS.—13 s.w.g. DRILLED, with screens and tube holder bracket, 27 6. PLAIN, with screens and tube holder bracket, 20 -

TRANSFORMER.—350-3-350 v. 150 ma., 6.3 v. 5 a., 5 v. 3 a., tapped at 4 v., ONLY 32 6. (Postage 2-)

CHOKES.—10 h. 120 ma., 10 6. (Post 1-)

RECTIFIERS.—6AL5 - ea., K3 to 6 - ea. 684 - 7/6

VALVES.—EF50 6 6, SP61 4 - 6, 6SN7 11 6, 6X5 5 6, EB3 3 6, EA50 3 6

VALVE HOLDERS.—395 (EF50) 10 1, I.O. and M.O. 6d., Diode (EA50) 6d., VCR97 2 6.

VCR97 TUBE.—Tested full screen, 42 6

CONDENSERS.—Electrolytics 25 mfd. 25 v. 1 10, 16 x 8 mfd. 150 v. 5 6, 32 x 32 mfd. 330 v. 6 - 1 mfd. 250 v. 4 6, Mica, silver mica, and tubulars, 330 v. 6d. each.

POTENTIOMETERS.—All valves, meter 1/9 each, long spindle 3-, with switch, 4 6.

RESISTORS.—1 watt 4d., 1 watt 5d., 1 watt 6d., 1.5 K 5 watt, 1 6.

COIL FORMERS.—1in. 8d., 1in. 10d.

SPEAKER.—5in. BOLA P.M. with trans. 17/6 (postage 2-)

All Components Brand New and Un-used. Full Price List available on request.

VALVES			
1G5	6/6	7A7	8 8
1G6	6 6	7C5	8 8
1E7	6/6	7F7	8 6
1LH4	8 -	7W7	8/6
1LN5	8 -	12H5	8 6
1L4	7/6	12J5	6 -
2B7	8/6	12A7	12 6
3A4	9 -	12S7	7/6
3B7	8/6	12SK7	8/6
6AG5	7/6	12SR7	7/6
6AK7	9/6	28D7	7/6
6B4	7/6	32	7/6
6B7	7/6	36	7/6
6C3	8 -	50Y3	8 6
6G3	6 8	58	8 6
6H5	5 -	1622	11 -
6K6	9 -	1625	7 6
6L7	7 6	1926	4 6
6N7	7/6	1295A	7 6
6P6	8 6	VR150 30	8 6
6Q5	8/6	VR197	5 9
6V6	10 6	KT41	8 6
6SA7	8 6	KT2	5 -
6SC7	7/6	VP23	6 6
6SH7	7/6	VP23	6 6
6SJ7	8/6	HL23DD	6 6
6SK7	7/6	TP23	8 -
6SL7	9 -	185	8 -
6SS7	7 6	1T4	8 -
IR5	8 -		
SZ1	10 -		
SU4	10 -		
6AC7	6 6		
6K7GT	5 6		
807	7 6		
ECH35	12 6		
EA50	3 6		
EBC33	8 6		
EB34	3 6		
EF36	6 6		
EF39	6 6		
RF50	6 6		
.. Red			
Sylvania	9 6		
EF55	12 6		
EK32	6 6		
EL32	7 6		
SP61	4 -		
MU14	10 6		
RL37	6 -		
VS70	7 6		
954	6 6		
955	6 -		
8 - 9003	6 -		
8 - 9001	6 -		
8 - 331A	50 -		

R.F. UNITS TYPE 26 and 27. For use with the R.1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves EF54 and 1 of EC32. Type 26 covers 65-50 Mc/s (5-6 metres), and Type 27 covers 85-65 Mc/s (3.5-5.0 metres). Complete with valves, and BRAND NEW IN MAKER'S CARTONS. ONLY 45 - each.

R.F. UNIT TYPE 24. Complete with 3 valves SP61 and full details of modification required to cover all TV. Stations, ONLY 15 -

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed Normal Primaries. 425-0-425 v. 200 ma. 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., ONLY 50 -; 350 v.-0-350 v. 150 ma., 6.3 v. 5 a., 6.3 v. 3 a., 5 v. 3 a., ONLY 42 6 -; 250 v.-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., ONLY 32 6. 350 v.-0-350 v., 150 ma., 6.3 v. 5 a., 5 v. 3 a., ONLY 32 6. The above are fully shrouded, upright mounting. 5.5 kV. E.H.T. with 2 windings of 2 v. 1 a. ONLY 72 6 -; 7 kV. E.H.T. with 4 v. 1 a., ONLY 92 6. PLEASE ADD 2 - POSTAGE FOR EACH TRANSFORMER.

E.H.T. TRANSFORMER FOR VCR97 TUBE.—2,500 v. 5 ma., 2-0-2 v. 1.1 a. 2-0-2 v. 2 a. 87 6 (postage 2-)

INDICATOR UNIT 233 chassis, containing VCR97 holder, 11 assorted valve holders, condensers, resistors, etc. NEW CONDITION. ONLY 7 6 (carriage etc. 3 6).

RECEIVER R 1355 chassis, containing 10 assorted valveholders, I.F. transformers, condensers, resistors, etc. NEW CONDITION. ONLY 7 6 (carriage etc. 3 6).

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station), 5 mins. by bus from King's Cross. Cash with order, please, and print name and address clearly. Include postage as specified and on Component Orders under £2.

U.E.I. CORPN. THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1. (Phone TERMINUS 7937.)

IT'S 60% CHEAPER !!

To Construct Your Own Television Aerial
SUMMER TIME IS THE RIGHT TIME TO CONSTRUCT AND ERECT AN AERIAL.
 WE SHALL BE PLEASED TO SUPPLY INFORMATION, IF REQUIRED, ON ELEMENT LENGTHS AND SPACINGS, WITH FULL ASSEMBLY INSTRUCTIONS. ALL WE NEED IS THE CHANNEL NO. AND TYPE OF AERIAL TO BE CONSTRUCTED

All fittings are die-cast, using high quality aluminium and are fully guaranteed.

14ft. 16 s.w.g. 2in. Aluminium Poles.	Inc. Carr.	50/-
1in. 18 s.w.g. D/H Alloy Tubing.	Per ft.	10d.
1in. 18 s.w.g. D/H Alloy Tubing.	Per ft.	1/4d.
INSULATORS. Unbreakable, waterproof (standard 1in. x 1in. fitting).	Each	6/9
INSULATORS. Unbreakable. For "In-line" Aerials, 1in. x 1in. fitting.	Each	8/9
MASTHEAD MOUNTINGS. 2in. Pole fitting, 1in. Cross Boom.	Each	8/6
MASTHEAD MOUNTINGS. 1in. Pole fitting, 1in. Cross Boom.	Each	6/-
REFLECTOR AND DIRECTOR ROD HOLDERS. for 1in. Elements, 1in. Cross Boom.	Each	3/9
BRACKETS. Heavy Duty. 2in. Pole fitting, double lashing.	Set	40/-
BRACKETS. Lightweight. 1in. Pole fitting, single lashing.	Set	25/-

Write for Illustrated Price List. C.W.O. Carriage & Packing 1/6 extra.

Fringevision Ltd.
 ANGEL YARD WORKS, MARLBOROUGH, WILTS.
 Phone 605.


SAFEGUARD YOUR SET ECONOMICALLY

55' FOR 5/-
 AND NOT AN INCH WASTED
ERSIN Multicore SOLDER

The image shows a rectangular box of Ersin Multicore Solder. The box is white with black and red text. At the top, it says 'PULL AT REQUIRED SELF DIAM.' and '3 CORES OF NON-CORROSIVE FLUX'. The main text on the box reads 'ERSIN Multicore SOLDER'. A large price tag is attached to the box, showing '55' FOR 5/-'. The box also indicates it contains 3 cores of non-corrosive flux.

ERSIN MULTICORE SOLDER makes every electrical connection in your equipment a sound, permanent joint. Countless jobs—construction, repair—can be done with one 5 - carton. And, because ERSIN MULTICORE contains 3 cores of extra-active, non-corrosive Ersin Flux to prevent oxidation, 'dry' and H.R. joints, it solders instantly, without trouble, waste or extra flux. Get a carton today.
MULTICORE SOLDERS LTD.
 MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. • BOXMOOR 5636.

TELENEWS

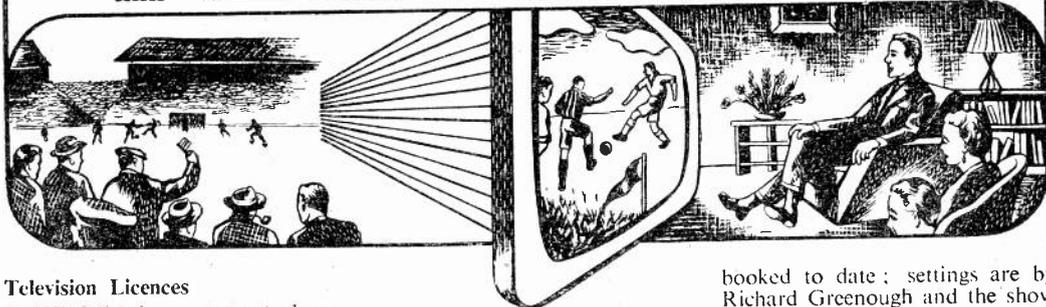

Television Licences

THE following statement shows the approximate number of television licences issued during the year ended March, 1954. The grand total of sound and television licences was 13,436,793.

Region	Number
London Postal ...	936,019
Home Counties ...	351,920
Midland ...	632,117
North Eastern ...	427,072
North Western ...	450,745
South Western ...	138,163
Wales and Border ...	158,230
Total England and Wales ...	3,094,266
Scotland ...	144,273
Northern Ireland ...	10,353
Grand Total ...	3,248,892

World's Tallest Structure

ENGINEERS have commenced work on what will be the highest man-made structure in the world—a 1,572ft. television aerial. The station site is situated in Oklahoma City, U.S.A., and the aerial will exceed the mast on the Empire State Building, New York, by 100ft. Completion is expected by the autumn of this year.

Relay TV for Eastbourne

IN the course of the installation of a television relay network at Eastbourne, recently, Link Relay Vision, Ltd., required a direct cable link between two of their principal stations. Every precaution had to be taken to ensure the least possible distortion of signal and part of the link between the two stations now consists of a special underground precision multicore cable designed by British Insulated Callender's Cables, Ltd., and manufactured in one length of 1,500 yards at their Helsby Works. It runs across a part of the Eastbourne Corporation territory where overhead wiring would have been unsuitable.

"In the News"

THE panel for "In the News" on May 28, will consist of Sir Robert Boothby, M.P., W. J. Brown, Anthony Greenwood, M.P., and Michael Foot, M.P.

The chairman for the programme will be Frank Byers.

Aberdeen Contract

A CONTRACT for the building work on the new medium-power television transmitting station, at Meldrum, Aberdeenshire, has been placed by the BBC with Alexander Hall and Son (Builders) of Aberdeen.

The contract includes the erection of the main building and the provision of a draining system, service roads and fencing.

His First Series

ON May 12 Bob Monkhouse, the well-known BBC script-writer, began his first series of monthly television programmes, in which he is supported by his partner, Denis Goodwin.

Produced by Kenneth Carter, the new series will be a mixture of sketches and music in an intimate style, following no set form or pattern. The Tanner Sisters and Eric Robinson and the Orchestra are among the musical residents

booked to date; settings are by Richard Greenough and the show will come each month from the Television Theatre.

No Plans Yet for Schools

REPLYING on the subject of a television service for schools, Mr. Kenneth Pickthorn, Parliamentary Secretary to the Ministry of Education, said in the House of Commons recently that the BBC were unable to say when such a service would begin.

He added that it would be too costly for educational programmes to start on an experimental basis as



The new Orient liner, "Orsova," is the first ship to have the new Marconi Marine 15in. "Radiolocator" radar. One of the "Orsova's" navigating officers is seen watching the screen of the new radar in the liner's chartroom.

lengthy preparations and heavy demands on studio space and equipment would be involved.

Direct from the States

NEARLY 450 scientific and engineering experts met at the Milan International Samples Fair recently to discuss developments in the field of electronics and television and most were optimistic that television broadcasts could be received soon in Europe direct from America. This would be by means of the trans-Atlantic telephone cable, upon which work has already been started.

British Transmitters for Denmark

SIX television transmitters (three vision and three sound), with associated aerial systems, transmission lines and combining units, are to be manufactured by Marconi's Wireless Telegraph Co., Ltd., for installation in Denmark.

This important export order has been received from Sophus Berendsen, Ltd., the Marconi agents in Denmark, for supply to the Danish P. and T. It was secured for Britain despite severe competition from foreign countries, rival tenders being submitted from America, Germany and Holland.

Television Society Awards

THE Council of the Television Society has announced that the "Electronic Engineering" Premium has been awarded to D. D. Jones for his paper on "Transistors and Other Crystal Valves," and that the "Mervyn" Premium has been awarded to G. J. Hunt and E. W. Elliot, for their paper "An Introduction to the Sine Squared Pulse."

All three authors are employed in the Research Laboratories of The General Electric Co., Ltd.

Fewer Sets Sold

REPORTS from the trade show that the sale of television receivers is on the decline, commercial television being blamed for the gradual decrease. Potential viewers feel that by waiting they

may avoid the expense of converting a normal receiver for commercial programmes.

New sales reports also indicate an increase in the buying of radio sets; figures for February of this year were the highest for that month—a bad one for the trade—since 1951.

Hotel Licences

NEW regulations under the Wireless Telegraphy Act, 1949, which come into force on June 1, will enable the G.P.O. to issue special licences for the reception of television in hotels.

The basic cost of this licence will be £3 plus an additional £3 for every single room to which television is relayed. There is as yet no licence which legalises the charging of an admission fee for the viewing of TV programmes.

"Biggest Gamble"

MR. CECIL MCGIVERN, BBC Television Controller, recently described the plans for the international exchange of television programmes in July as "the biggest gamble that television has ever undertaken."

Top TV Town

ACCORDING to figures just released by the BBC, Walsall would be the chief contender for the position of "Top TV Town" if such a title existed. Walsall, a small Midlands town just north of Birmingham, can boast the total of 27,000 television licences whereas Wolverhampton, with a much larger population, possesses only a thousand

more than little Walsall.

After Hours

THERE are not many workers who, having finished their evening meal, prepare to return to the scene of their day's work for the evening.

This is the case in Ilkeston, Derbyshire, however, where a hosiery firm have provided their employees with TV viewing facilities as part of their welfare scheme.

Aerials on Guernsey

THE States of Guernsey recently granted permission to the BBC to erect three temporary television masts and a hut at Pleinmont Point.

This is still subject to confirmation by the island's natural beauties committee and satisfactory tests will have to be made.



A popular artiste with viewers these days is Joan Regan, resident singer in "Quite Contrary," whose pleasant voice and easy style led to a request appearance in "Well, You've Asked For It."

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

PREMIER RADIO COMPANY

OPEN TILL
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone:
AMBASSADOR 4033
PADDINGTON 3271

PREMIER — MAINS TRANSFORMERS

All primaries are tapped for 200-230-250 v. mains 40-100 cycles. All primaries are screened. All LTs are centre tapped.

SP175B, 170-0-075, 50 mA., 4 v. @ 1a., 4 v. @ 2.5a. 25/-

SP250B, 250-0-250, 60 mA., 4 v. @ 0-2 a., 4 v. @ 3-5 a. 25/-

SP300A, 300-0-300, 60 mA., 6.3 v. @ 2.3 a., 5 v. @ 2 a. 25/-

SP300B, 300-0-300, 60 mA., 4 v. @ 2.3 a., 4 v. @ 3-5 a., 4 v. @ 1-2 a. 25/-

SP350A, 350-0-350, 100 mA., 5 v. @ 2-3 a., 6.3 v. @ 2-3 a. 29/-

SP351, 350-0-350, 150 mA., 4 v. @ 1-2 a., 4 v. @ 2-3 a., 4 v. @ 3-6 a. 38/-

SP375A, 375-0-375, 250 mA., 6.3 v. @ 2-3 a., 6.3 v. @ 3-5 a., 4 v. @ 2-3 a. 55/-

SP501, 500-0-500, 150 mA., 4 v. @ 2-3 a., 4 v. @ 2-3 a., 4 v. @ 2-2 a., 4 v. @ 3-5 a. 47/-

SP425A, 425-0-425, 200 mA., 6.3 v. @ 2-3 a., 6 v. @ 3-5 a., 5 v. @ 2-5 a. 67/6

EHT UPDRA for VCR57 tube, 1750 RMS v., 5 mA., 2-0-2 v., 1a., 2-0-2 v., 2a. 37/6

C.R. TUBES

VCR 517C
6in. picture, this tube is a replacement for the VCR97 and VCR517. Guaranteed full size picture ... **PRICE 35/-**
Plus 2/6 pkg. carr., ins.

VCR 516

9in. Blue picture. Heater volts 4. Anode 4 Kv. In manufacturer's original carton
£3.19.6 Limited Quantity
Plus 5/-pkg. carr., ins.



ALL BRAND NEW

AUTO TRANSFORMER, 50 watts. Input/Output 0-110-210-220-230-240-250 volt. Plus 1/- pkg. & carr., 7/6.

A.C.R.I. C.R. TUBES

(DIRECT REPLACEMENT FOR A C.R. 2X)
5in. screen, 4 volt Heater. This Electrostatic Tube is recommended as eminently suitable for Television, 15/-, plus 2/6 Pkg., Carr. and Ins. Data sheet supplied.

RECTIFIERS

E.H.T. Pencil Type	S.T.C.	S.T.C.	
Type K3 25	650 v.	1 mA.	4/7
.. K3 40	3.2 kV.	1 mA.	6/-
.. K3 45	3.6 kV.	1 mA.	8/2
.. K3 50	4 kV.	1 mA.	8/8
.. K3/160	12kV.	1 mA.	21/6

LT. Type	S.T.C.	
Type RM1	125 v.	60 mA.
.. RM2	125 v.	100 mA.
.. RM3	125 v.	125 mA.
.. RM4	250 v.	150 mA.

LT. Type	Full Wave.	
6 v. 1 amp.	...	4/-
12 v. 1 amp.	...	8/-
12 v. 2 amp.	...	10/9
12 v. 4 amp.	...	15/-

T.V. WHITE RUBBER MASKS (CORRECT ASPECT). We can supply a specially designed White Rubber Mask for 6in. C.R. tubes at 8/6 each. 9in. White Masks, 9/6. 12in. White Masks, 16/11. For Round or Flat-faced Tube.

THE NEW PREMIER TELEVISION

Wide Angle Scanning, for 14in. or 17in. Tubes may be used with a 12in. Tube with minor modification.
Tunable from 40-58 Mcs without coil or core changing, completely isolated from the mains.
The New Time Base may be used with existing Premier Televisors to convert them to the latest type of picture tubes. All the individual components may be purchased for a total cost of £31/19/7 (less tube).
Data booklet, 3/6 post paid.

SPECIAL OFFER

CRYSTAL HAND MICROPHONE



High Impedance. Excellent frequency response light weight gives very high quality results when used with tape recorder, amplifiers for any type of P.A. equipment. Complete with screen lead and plug. 29/6 Plus 1/6 pkg. and carr.

Ex. W.D. STEEL AERIALS

Also ideal for fishing rods—**BRAND NEW** 12ft. 3 4 ft. sections of copper-plated steel, highly flexible, tapering in to tin. Brand new in container. Plug-in type, 6/9; Screw-in type, 7/9. Packing and carriage, 1/6. Insulated Base 3/-; Webbing waterproof carry-in; case with shoulder-sling, 2/6.

TERMS OF BUSINESS:—CASH WITH ORDER OR C.O.D. OVER £1
Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

HANNEY OF BATH offers:—

EDDYSTONE 740 RECEIVER, ex-stock at £42/15/-. Send for illustrated brochure. NEW Eddystone catalogue 1/2 post free.

M.K.S.—Acos Mic. 2/2, 84/-; Mic. 30. 50/-; Mic. 33.1, 50/-; Mic. 35.1, 25/-; Rothermel 2AD56, 63/-.

LOUDSPEAKERS—Goodmans Audiom 60, £9/12/6; Axiom 150 Mk. II, £10/5/6. W.B. HIGH FIDELITY 3 n coil, H.F.610, 6in. 50/6; H.F.810 8in., 60/6; H.F.912, 9in., 67/-; H.F.1012, 10in., 73/6; (15in. available at 73/6).

COILS—(State range required)—Osmor Q, 4/-; Weymouth H. 3/9; Wearite P, 3/-; Denco C TRF, 8/- pr.; Denco Maxi-Q std. or miniature, 3/11, with reaction, 4/9; R.E.P. dual range high gain, 4/-; OSMOR Q Coilpacks, Type HO, 48/-; LM, 40/-; Batt., 50/-; TRF, 40/-; ETA 4 Station Tuning pack, 43/8.

I.F. TRANS. (465 kc.s.) Denco I.F.T. 11, 12, 13, 4/-; I.F.T. 6, 18/4 pr.; Wearite M, 800, 21/- pr.; Weymouth P, 4, 15/- pr.; P.5, 8/6 each; P.5A, 10/- each.

OUTPUT TRANSFORMERS—50 watt POTTED de Luxe type to suit single or push-pull PX4, 6V6, 6L6 and KP66 valves. Optimum leads 4,000Ω to 10,000Ω. Eleven ratios 15:1 to 78:1, 47/8. Elstone MR/T 4 w. multi-ratio, 8/9; Elstone MR/7, 7-10 w. multi-ratio, 15/9; MR.15 15 w. multi, 41/6; MR.30, 30 w. multi, 49/6. Woden Williamson, Potted, WOT25, 17Ω sec., £6/10/-; WOT26, 3.5 Ω sec., £6/16/6.

P.W. CORONETS—JB. SL8 Drive, 27/6; E.2 V-Condenser, 14/-; W.B. 8in. H.F.810 L.S. (less trans.), 60/6; All resistors and condensers as per our General List.

TELEKING—Constructors' Envelope, 6/-; Coilsets, 44/6; Chassis kit, 50/-; T.C.C. kit, £7 4/3; RM4 rectifier, 21/-; Allen Components, LO306, 40/-; PO305, 21/-; DC300, 39/6; FC302, 31/-; GL16 and GL13, 7/6 each; BT314, 15/-; SC312, 21/-; AT310, 30/-; OP117, 9/6; Duplicator Resistor pot. kit, 81/6.

P.T. SUPER VISOR
T.C.C. Condenser kit, £8 6/4; Erie resistor kit, 54/4; 4 w w pots, 26/-; 7 Erie carbon pots, 35/-; Allen coilsets, 44/6; Allen CD 300 39/6; GL.18 and GL.18, 7/6 each; SC.312, 21/-; FC.302, 31/-; OP.117 output trans., 9/-; Denco WA FMA1, 21/-; WA LOT1, 42/-; Denco chassis kit, 51/6; Westinghouse WX.6, 9/10; WG.4, 7/6; LW.7, 26/9; English electric polystyrene mask, 45/8; perspex filter, 32/8; anti-corona ring, 6/8; Tube sheath, 6/2; T.901 tube, inc. carriage and insurance, £22 14/10; Inlac IT8 ion trap, 5/-.

WIDE ANGLE VIEWMASTER—Instruction Envelope, 3/6. Priced parts list available on request.

CATHODE RAY TUBES—Magna CRM.12B, £18 13/8; CRM.123, £17/14/6; Mullard MW31-74, £18 13/8; MW36-22 & 24, £19 9/3; MW43-74, £23/12/8. Ion traps for all tubes, 5/- each. Please add 10/- carriage and insurance on all tubes, any excess being refunded. Send 6d. in stamps for our GENERAL LIST, which contains details of components for Viewmaster, Teleking, Magnaview, Super Visor. Universal large Screen Television, by Mullards, Coronet Four, Williamson Amplifier, Soundmaster, etc., etc. Please add postage to orders under £2.

L. F. HANNEY 77, LOWER BRISTOL ROAD, BATH Tel.: 3811

Forrest

REPLACEMENT LINE OUTPUT TRANSFORMERS (ETRONIC TYPE)

Retail 37/6. Trade 25/-

FRAME OUTPUT TRANSFORMERS (multi-ratio) for service replacements.

Retail 18/9. Trade 12/6

BLOCKING OSCILLATOR TRANSFORMERS. Ratio 1 : 1, 1 : 2, 1 : 3.

Retail 12/9. Trade 8/6

COMBINED ISOLATING AND BOOSTER TRANSFORMERS. All voltages from 2-13.3 volt.

Retail 18/9. Trade 12/6

MAINS TRANSFORMERS. Primary: 200 v., 230 v., 250 v. Secondary: 6.3 & 4 v., 2.5 a., 4 v. & 5 v., 2.5 a, 350-0-350 80/100 ma.

Retail 35/3. Trade 23/6

All types of Rewinding. Lists on application.

H. W. FORREST,

349, HASLUCKS GREEN ROAD,

SHIRLEY, BIRMINGHAM.

Volume Controls

Midget Edison type. Long spindles. Guaranteed 1 year.

ALL VALUES. 5,000 ohms to 5 Megohms.

BALANCED TWIN FEEDER per rd. 8d. **TWIN SCREENED COAX FEEDER** per rd. 1-Johns 50 OHM COAX CABLE, 60 per yd.

TRIMMERS. Ceramic, 30, 70 pf., 9d.; 100 pf., 150 pf., 1.3; 250 values; 1 w., 4d.; 1 w., 8d.; 1 w., 8d.; 2 w., 1.1; 1 w., 1.2; 1 w., 8d.; 1 w., 8d.

WIRE-WOUND RESISTORS. Best Makes Miniature Ceramite Type—5 w., 15 ohm to 4 K.; 1.9; 10 w., 20 ohm to 6 K.; 2.3; 15 w., 30 ohm to 10 K.; 2.9; 5 w. Vitrores, 12 K. to 25 K., 3.3.

WIRE-WOUND POTS, 3 WATT, FAMOUS MAKES Present Min. TV Type. 1 Standard Size Pot—2 1/2" Knurled Slotted Knob, Spindle. High Grade. All values 25 ohms to 200 K. All values, 100 ohms to 200 K., 3 w., 50 K., 4 w., Ditto Carbon Track, 50 K., 2 to 2 Meg., 3 w.

O/P TRANSFORMERS. Tapped solid pentode, 3.9. Heavy duty 70 ma., 4.8. Ditto, trioded, 4.9. L.F. CHOKES 10 h. 65 ma., 4.8. 20 h., 150 ma., 12.6. 15 h. 100 ma., 10.6. **LYNX.** 3 h. 250 ma., 13.6. **SIMPLEX** 10 h. 150 ma., 10.6.

MAINS TRANS. Made in our own workshops to high grade specification. Fully iron-bleaded and impregnated. Heater Trans., tapped, 10-200 v., 250 v., 6.3 v., 13 amp., 7.8. 12 v., 25 amp., 7.8. 6.3 v., 3 a., 10.6. 250-0-250, 80 ma., 6.3 a., 4 amp., 5 v., 2 w., ditto 300-0-300 ditto 250-0-250, 21 w. Viewmaster, auto type, 35 w. Telexing, 30 w. Lynx, 30 w. Caromet, 30 w. Simplex (modified), 35 w.

TV. AERIALS. Aerolite etc. all grades all channels in stock. Indoor loft type Inv. T. 13.6 etc. etc.

TYANA. Midget Soldering Iron. 200-220 v., 220-250 v., 14 1/2. Triple Three mod. w/5 detachable bench stand, 19.6. Soton Midget Iron, 19.3.

TAG STRIPS.—2 or 3-way, 2d., 4 or 5-way, 3d.; 6-way, 4d.; 8 or 10-way, 6d.; 2-way, 1.3.

GOODMANS. Latest Wide Angle Illuminer Type. Focus Unit. Variable Focus and adjustable Picture Shift, 35 w. ELAC.—(R.F. Ion Traps, 2.6).

ENAMEL OR T.C. WIRE.—1 lb., 14 to 20 s.w.g., 2.1; 22 to 28 s.w.g., 2.6; 30 to 40 s.w.g., 3.9.

80 OHM COAX

STANDARD (In. diam. Polythene Insulated. Grade "A" Not Ex Govt., 8d. yd. **COAX PLUGS,** 1-2 each. **SOCKETS,** 1-2 each. **LINE CONNECTOR, 1.2.** **OUTLET BOXES, 4.8.**

NEW BOXED VALVES

1A3	5/8	6PF12	9/-	12A6	7/6	EP50	7/8
1A5	3/-	6H6	3/6	1V127	Pen	EP50	9/-
18Y	8/-	6J5	7/6	46	9/-	EP50	Equip
191	9/-	6J7	8/6	12AX7	10/6		5/6
184	8/-	6K6	7/8	12AT7	10/6	British	7/6
344	9/-	6K7	6/6	12BK7	10/6	Sylvania	
384	8/-	6K8	9/-	12K8	10/6	Red	10/6
2X2	5/8	EP50	10/6	12M7	10/6	EP50	9/-
20Y	2/8	6L6	10/6	6L6	10/6	EP50	9/6
214	10/6	6P25	15/-	6V6	10/6	EP50	9/6
224	9/-	6Q7	9/6	50L6	9/6	RV34	12/6
6X4	7/6	6SA7	8/6	50Y7	10/6	HV82	7/6
6AU5	7/6	6SH7	6/6	50Y8	5/6	PV80	11/6
6AM6	9/-	6SL7	9/-	9001	7/6	PV81	11/6
6AV5	10/6	6SR7	11/-	9006	7/6	PV82	10/6
6BS	7/6	6T5	6/6	6X5	3/6	6V6	9/6
6B34	10/6	6V6	9/-	6X18	6/6	12	9/6
6B4	10/6	6V8	9/-	6X50	2	VR11	6/6
6C4	7/6	6X4	10/6	EB91	7/6	EP50	12/6
6C6	7/6	787	9/6	EB92	9/6	25L5	10/6
6C8	9/6	8D8	9/-	EB91	7/6	6Z82	15/-

Huge Stock B.V.A. Valves at BGL low tax prices.

P. and P. Ltd. All orders post free. Lists in ALL TRANS. P. & P. 1 extra please.

T.R.S. RADIO COMPONENTS SPECIALISTS

307, Whitehorse Road, West Croydon.

SIMPLEX TELEVISION

Detailed price list available. **STAGE 1, VISION AND SOUND**

7 Valves	30/-
12 Resistors	3/-
16 Condensers	9/-
2 Potentiometers	6/-
7 Coilformers with cores	9/6
7 Valveholders	4/6
Sundries (with undrilled chassis)	22/6

STAGE 2—TIME BASE

6 Valves	29/-
20 Resistors	9/6
15 Condensers	15/6
5 Potentiometers	12/6
8 Valveholders	2/6
Sundries	1/6

extra with KIT OR VCR97 TUBE TESTED & GUAR. 22. (1" and p. 2.)

STAGE 3—POWER SUPPLY

2 Rectifiers	2/-
5 S.T.C. Rectifiers	27/6
3 Condensers	23/6
1 Choke	10/6
1 Mains Trans Tapped 4 v. and 5 v.	35/-

STAGE 4—C.R.T. NET WORK

9 Resistors	4/-
1 Condenser	6d.
4 Potentiometers	10/6
Sundries	3/6

COMPLETE SIMPLEX KIT (less tube) 12 gns. Chassis, 17/6, or 10/-

NEW WORK.

COMPLETE SIMPLEX KIT (less tube) 12 gns. Chassis, 17/6, or 10/-

STAGE 1. VCR97 TUBE TESTED & GUAR. 22. (1" and p. 2.)

C.R.T. HEATER ISOLATION TRANSFORMER.

Low leakage winding with 25% sec. boost. 2 w. 10.6; 4 v., 10.6; 4 v., 9.3; 12 v., 10.6. **BRIMISTORS.**—(Z1) 3 a., 9.6; (Z2) 15 a., 9.6. **CRYSTAL DIODE.**—Very sensitive. G.E.C., 3/6. H.R. PHONES (S.G. Brown), 15/6 pr.

CONDENSERS.—New stock best makes, 500 (old) 6KV, T.C.C., 5/6. Ditto, 12.5 KV., 9.6; 2 pf. to 500 pf., 8d.; 301, 300, 301, T.C.C. 500 v., 01 Sprague 500 v., 02 N.S.P. 500 v., 1 (old), 350 v. Micamold Tube, 9d.; Hums Multised 500 v., 05 (old) and 1 (old), 11.2; 25 (old), 1.6; Tubular (old), 550 v., 1.9. **SILVER MICRA CONDENSERS.**—10/6.

5 pf. to 500 pf., 1-; 600 pf. to 5,000 pf., 1.3. **DITTO 1/6, cv stock.** 1.5 pf. to 500 pf., 1.9; 515 pf. to 1,600 pf., 2/-.

ELECTROLYTIC ALL TYPES NEW STOCK.

Tubular Wire ends	
2 450 v. B.E.C.	2/3
4 500 v. Hums	2/-
8 450 v. B.E.C.	2/3
8 450 v. T.C.C.	2/9
8 500 v. Dullier	2/9
16 500 v. Dullier	4/-
8 500 v. Dullier	4/8
32 500 v. Dullier	4/-
32 500 v. Dullier	5/-
32 500 v. Dullier	5/6
50 12 v. B.E.C.	1/9
50 25 v. Plessey	1/9
50 50 v. Plessey	2/-
6,000 5 v. B.E.C.	5/6

16 (old), 700 v. Hums, 9/6

SENTERCEL RECTIFIERS.—EHT Type. Tube-bank Voltage.—K3 25.2 Kv.; 4.3; K3-40.2 Kv. 6; K3-15.35 Kv., 6.6; K3-20.4 Kv., 7.3; K3-100.8 Kv. 12.6; K3-160.14 Kv., 18. **MAINS TYPE.**—RM1 125 v., 60 ma., 4.2; RM2, 100 ma., 4.9; RM3, 120 ma., 5.8; RM4, 250 v., 275 ma., 10/6.

KNOB GOLD ENGRAVED.—Walnut or Ivory. 1 in. diam., 1.8 each. Not engraved, 1/- each.

LOUDSPEAKERS P.M., 3 OHM.—3in. Geometry 12.6. 3in. Goodmans, 13.6; 6in. GOODMANS, 14.6. 5in. R. & A., 17.6. 10in. Plessey, 25/-.

SLEEVING.—Various colours, 1, 2 mm., 2d.; 3, 4 mm., 3d. yd., 6 mm., 5d. yd. **TOGGLE SWITCHES**

EX-GOV.—On-On, 8d. Grain M cone solder, 0.10. 10 v. or 18 v., 5.6; 11 v., PWC connecting wire, 10 colours. Single or Stranded 2d. yd. **TRF Valveholder and Screening Can, 1.8; V holders, octal, 12s., 4d.; moulded, 6d.; EP50, B7G, moulded, 9d.; ceramic, 1/-; BSA, B9A, 1/-; B12A (CRT), 1/3; VCR97 moulded holders, 2.6. ALADDIN FORMERS and core, 1in., 8d.; 3in., 10d.**

HOME BUILT TV

Full HP Facilities • Return Post Service

SIMPLEX

Stage 1, £53/- Stage 2, £44/- Stage 3, £6/- Stage 4 (less C.R.T.), 14/6. Sundries Kit, 13/-

All items available separately. Send for list.

VIEW MASTER

We have fully detailed lists available for all versions of the View Master. Any of these will be sent free upon request.

INSTRUCTION MANUALS

Standard set. For 9in. or 12in. tube, 7/6. Wide Angle Conversion, 16in. and 17in. tube, 3/6.

WATTS RADIO (Weybridge) LTD.

8, Baker Street, Weybridge, Surrey

'Phone: Weybridge 2542

INTRODUCING . . .

"NURAY"

REGD. TRADE MARK.

A HEATER BOOSTER UNIT THAT JUST PLUGS IN. IT GIVES LOW EMISSION C.R.T.s A NEW RAY.

1. You can fit "Nuray" in 3 minutes.
2. With the special clamp provided drilling is not necessary.
3. No soldering.
4. High, medium and low boost on the one unit.
5. Can be re-used many times.
6. Instructions clearly printed on each unit.
7. Booster results can be demonstrated to customers without involving costly labour.



You will improve your service if each of your engineers has a "Nuray" in his kit. The "Nuray" is available for 2-volt tubes in parallel heater circuits. (Other types to order.)

OBTAINABLE AT 27/6 RETAIL, PLUS 1/6 PKG. & POST.

Trade enquiries welcome.

DIRECT FROM

direct TV REPLACEMENTS

134-136, LEWISHAM WAY, NEW CROSS, S.E.14

TIDeway 3696-2330.

C.W.O. OR C.O.D. PLEASE ADD 1/6 PKG. AND POST.

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

"H" VERSUS THE MULTI-ELEMENT ARRAY

SIR,—Reference Mr. A. Hale's notes in the March issue on the subject "'H' Versus the Multi-element Array," he infers that aerials can be compared to within 1 db by observation of pictures. The only way to compare two aerials by this method is by observing the difference in signal-to-noise ratio. Ability to detect 1 db change in modulation depth does not imply ability to detect 1 db difference in signal-to-noise ratio; in fact, there is no connection between the two parameters.

Mr. Hale, by including the cost of a 12ft. mast and chimney lashings, managed to obtain a very low ratio between the prices of the two types of aerials, but I must admit that even with the exclusion of these items my ratio of 5/1 is still slightly high, at least so far as Belling and Lee's prices are concerned.

By the way, whilst I was searching through my Belling and Lee catalogue in order to check the prices I came across the following statement in praise of the "H" aerial:

"Research proves that the improvement in signal obtained by the addition of one element is not worth the cost, even though many people feel they must be better."

Perhaps the most serious mis-statement of facts is made by Mr. West when he refers to galactic noise.

In *Nature*, 158 (1946), curves are given showing the magnitude of galactic noise and at normal television frequencies up to about 70 mc/s, this type of noise is seen to be much greater than valve noise.

In a well-designed receiver at 45 mc/s, the valve equivalent noise temperature is only a few hundred degrees Kelvin, but the aerial noise temperature is several thousand degrees Kelvin. This means that the noise power in the aerial is many times greater than the valve noise, and it is this noise which causes the "snow" one sees on the screen. The fact that the aerial noise is predominant accounts for the disappointing results obtained when low noise pre-amps are tried.

At Band III frequencies galactic noise is much less than valve noise as seen from the curves and a low noise pre-amp will give a definite improvement. Also at these frequencies the broad band matching difficulties of multi-arrays will disappear, because the band width of the aerial will require to be much less compared with the centre frequency. The required bandwidth at normal television frequencies is about one tenth of the centre frequency, but at Band III frequencies the ratio is reduced to one fortieth. For these two reasons, multi-arrays (or Yagis as they are called), will be superior at the much higher frequencies.

The same reasoning applies to the use of Yagis at radar frequencies, which are much higher than normal television frequencies.

In answer to Mr. Wilson, I would like to say that my figures were obtained from a report on a survey of the service area of Sutton Coldfield, which appeared in Proc. I.E.E. Pt. III, 1951. The disagreement with

his figures may be due to the use of different reference levels.—M. R. HARKNETT (author of "'H' versus the Multi-element Array") (E. Southsea).

FOCUSING—85K TUBE

SIR,—I have read with sympathetic interest W. Herring's query in your feature "Your Problems solved" in the March PRACTICAL TELEVISION concerning the focusing of the Cosor 85K tube. I might well have written an identical letter, but have now just managed to obtain a good focus with this type of tube myself, and the following information might, therefore, be of assistance.

It would seem to me that Mr. Herring has purchased the 85K V.M. Kit as displayed by an advertiser. If so, then the mask supplied in this kit offers the maximum 4:3 ratio picture dimensions that this size tube can give: in consequence, the corners of the picture are made up in part of the corner radius of the tube bulb. This corner radius is obviously much sharper than the radius of the tube face and the effect of this difference, to me, is that in assuming the centre and major part of the tube face to be flat in one plane "A," then the corners of the picture verge into a plane "B," which gradually assume an angle of nearly 90 degrees from plane "A." In these circumstances it can hardly be expected that the electron beam will remain in focus when having to turn corners. However, since very little picture detail is usually contained in the corners, the small amount of defocusing that occurs in these areas does not detract from the general quality obtainable, for otherwise I have found the 85K will positively focus over a very high proportion of the screen.

The suppliers of this surplus tube recommend the WB 109/1 or the Elac 17/4 Focus Magnet, but these recommendations only hold good when using 6-7 kV E.H.T. In applying the full permitted 9 kV resulting in an increased beam velocity the low flux density of the above two magnets might not allow a satisfactory focus to be obtained.

I am using an Elac R20 Focus Ring, but as I am operating the 85K on the original View Master 6kV E.H.T., this magnet tends to be rather too strong, as the gap has to be nearly fully closed before any focus is obtained.

My main trouble was not so much in the overall focusing, but in the correct centring of the picture within the mask. Repeated efforts failed to get the raster to extend fully to the right-hand side. It was found that the ion trap would give a false centring of the picture, but only with a dangerous reduction in the overall brilliance of the raster.

After much trial and error it was found that the very critical positioning of the focus magnet along the neck of the tube solved the trouble. The picture now centres easily, and whereas previously picture shift could be obtained only in a general leftward direction shift can be made now in all directions. Focusing is good all over, except for the corners, as mentioned above. Incidentally, the ion trap remains in its Optimum Brilliance position and has not been moved in any way to obtain focusing or centring.

The manufacturers of the tube recommend that the focus magnet should be fitted approximately 3in. from the end of the glass of the tube neck. I have found this to be rather confusing, as in my case the gap in the magnet is 4in. from the end of the glass.

The measurement I find most concrete is this: the distance between the extreme rear edge of the scanning coils to the leading edge of the vernier adjustment plate or front plate of the focus magnet is 2½ in. I would also point out that this measurement checks with that on the 15 in. TV Kit marketed by the same firm (verified by measurement on one model at one of their branches). Nevertheless, it has been my experience that up to a ¼ in. either way of this 2½ in. can make or mar the correct focusing and positioning.

Another final point Mr. Herring might consider is in checking the position of the focus magnet in relation to the axis of the tube neck. Given the focus unit is uniform in flux density, tilting too far up or down or sideways could possibly cause defocusing in parts of the picture. On the other hand, if the magnet is faulty to some degree, then tilting might well assist in obtaining focus. Finally, he might try swinging the focus magnet through 120 degrees either way around the neck to see whether this helps.

As a matter of interest, it is my opinion that there does not appear any necessity in raising the E.H.T. to 9 kV with this tube. I obtain quite good pictures using only 6 kV and can even, on occasion, use a tinted filter in front of the screen and still get sufficient brightness whilst retaining focus.—L. H. MILLER (London, N.17).

COST OF COMPONENTS

SIR,—Whilst I heartily agree with H. Telford, with regard to the exorbitant price of large-size cathode ray tubes, I find it difficult to imagine how they can be serviced except by their respective manufacturers. However, a prominent manufacturer does, in effect, repair your tube for you, if of their manufacture, by supplying you with a new tube at half price, and repairing your tube equal to new.

But in my view a more serious shortcoming of TV is the low quality of reproduction presented by the majority of receivers. We who are interested in TV do occasionally note, with appreciation, a solitary model which can resolve a picture up to 3 Mc/s, with good linearity, contrast, interlace, etc., but for one set which can do this there must be thousands that will not.

This suggests to me immense possibilities, for some manufacturer who will dare to claim in advertising his wares: that "every set which leaves his works will resolve Test Card C with no visible imperfection." Providing no second-rate sets were ever allowed to leave his works that manufacturer would be firmly set on the road followed by the famous motor-car manufacturers. A position which, at the present time, cannot fairly be filled by any of the better-known TV manufacturers.

But unlike H. Telford, regarding what he calls unitisation, I feel my manufacturer as outlined above could with advantage, exchange, complete electrical elements as distinct from cabinets, of their TV sets at a fixed fee to keep them always up to standard, and so maintain his reputation.—G. METCALFE (Skipton).

BRIGHTENING VCR97

SIR,—Although my experiments are now over, using VCR97, I have been tempted many times to write of a tip I used for brightening the tube considerably, in fact in my case when the tube got a

little old made the difference of a picture or no picture at all.

I do not feel it possible that I am original in this idea as to me it seems obvious what happens.

Here is the tip in a few words but first you will need a permanent magnet from an old loudspeaker.

There are two positions for it, under the tube at the front or in a reversed position at the back. I used to keep mine on the table in front as my heap of equipment never got to the stage of being fitted to a cabinet. It seems pretty obvious to me what happens, the beam is pulled or pushed to the tube face, according to the position of the magnet.

I should be very interested to know how other readers fare as I only tried it with one tube and feel certain that my experience was not unique.

Of course, the position of the magnet is fairly critical and needs to be found by experiment.—P. R. MOUNTER (Langport).

TUBE REPLACEMENTS

SIR,—With reference to the May, 1954, issue, page 580, "Your Problems Solved," we would offer the following information regarding the answer given to the query from G. O. Ware, Enfield.

The MW22-16 is a tetrode tube incorporating an ion trap and before recommending this tube as a replacement for earlier non-ion trap tubes, it is necessary to ensure that it is possible to do this, for the following reasons:

1. Insufficient room for the adjustment of the ion trap magnet (a space of approximately 30 mm. of the glass neck next to the base is usually required).
2. Ferrous rear tubes supports which will cause a deterioration in the field strength of the ion trap magnet.

In the case of the Invicta T101, we do not recommend the MW22-16 as a replacement as there is insufficient room on the neck of the tube to adjust the ion trap magnet. We normally recommend our type MW22-18, which is a non-ion trap tube. When substituting it is necessary to change the base to a B12A type and earth the external conductive coating.—I. A. REID (Mullard, Ltd.).

A NEW HANDBOOK

"PRACTICAL TELEVISION CIRCUITS"

288 pages.

156 illustrations.

15/- net.

CONTENTS

The "Argus"
 A £9 Television Receiver
 A 3-inch Midget Television
 A Compact Television
 An A.C.-D.C. Television Receiver
 A Combined Television and Broadcast Receiver
 The "Argus" Pre-amplifier
 Low Noise Factor Pre-amplifier
 Two-valve Pre-amplifier
 A "Spot-wobbler"
 A Black Spotter
 A Variable E.H.T. Generator
 A Portable E.H.T. Generator
 An Alignment Aid
 The Grid-dip Meter and Bar Generator
 A Pattern Generator
 The Telasquare
 The Practical Television "Lynx"
 The Practical Television "Super-visor"
 Aerial Data

Prices slashed at Clydesdale

INDICATOR UNIT "ASB" SERIES. (U.S.A.)

Contains 5B11 C.R.T., with mu-metal screen 3/8H9's, 2.65H7's, 6AC7, 6AC7, plus H.V. conds. etc. Metal case 18 1/2 in. x 8 1/2 in. x 8 in. All controls brought to front panel beside viewing screen.
ASK FOR **69/6** each. CARRIAGE PAID D/E776

INDICATOR UNIT TYPE 62

In original wood case.
ASK FOR **£3.19.6** each. CARRIAGE PAID D/H526

INDICATOR UNIT TYPE 62

Used, good condition.
ASK FOR **£2.9.6** each. CARRIAGE PAID D/E774

INDICATOR UNIT TYPE 305

BRAND NEW REF. 10QB.6504
Contains VCR524A-VCR325, 7 EF50's
ASK FOR **£3.19.6** each. CARRIAGE PAID D/H493

POWER UNIT TYPE 285

Ready made for T.V.
A.C. Mains. Input 230 v. 50 c.p.s. Outputs E.H.T. 2 Kv., 5 m.a., H.T. 250 v, 150 m.s., L.T. 6.3 v. 10 a. and 6.3 v. 5 a. Fully smoothed and rectified with valves VU120; 5U4G, VR91 (EF50), plus cond., resistors, etc.
ASK FOR **£4.19.6** each. CARRIAGE PAID D/H547

REPRINTS FROM "PRACTICAL TELEVISION"

Components Price List Free on Request.
The "Beginner's Receiver," modifying the R3170A ... 1/6
April to July ... 1/6
The "Beginner's Timebase" ... 1/8
Economy Television, modifying Ind. 62 ... 1/6
Argus Televisor, data and blue-print ... 2/6

INDICATOR UNIT TYPE 6

In original wood case.
ASK FOR **£2.19.6** each. CARRIAGE PAID D/H524

BEGINNER'S T.V.

Mains Transformer ... 32/6 each
Smoothing Choke ... 15/6 each
Output Transformer ... 9/9 each
Crystal Diodes ... 5/3 each

THE BEGINNER'S TIMEBASE

Mains Transformer ... 20/- each
E.H.T. Transformers ... 50/- & 45/- each
Smoothing Choke ... 15/6 each

INDICATOR UNIT TYPE 6H

In original wood case.
ASK FOR **£9/6** each. CARRIAGE PAID D/E777

CIRCUITS AVAILABLE AT 1/3. ASB35.7 or 8, type 62, R1355, R.F., 24, 25, 27, and R3601.

ION TRAP MAGNET ASSEMBLY

Mfg. Surplus.
Type IT/6 by Elac for 35 mm. tube neck.
ASK FOR **2/6** each. POST PAID. EXTRA D/H919

IF/AF AMPLIFIER UNIT R1355

In Transit Case.
With valves, I.P. frequency 7.5 mc/s Dim. : 18 x 8 1/2 x 7 1/2 in. Used, good condition.
ASK FOR **32/6** each. CARRIAGE PAID D/E770A

R.F. UNIT TYPE 24

In original carton.
Switched tuning 20-30 mc/s with valves, etc.
ASK FOR **15/-** each. POST PAID. EXTRA D/H580

R.F. UNIT TYPE 25

In original carton.
Switched tuning 40-50 mc/s with valves, etc.
ASK FOR **19/6** each. POST PAID. EXTRA D/H847

R.F. UNIT TYPE 27

With broken dial.
Variable tuning 65-85 mc/s with valves, etc. Used, good condition.
ASK FOR **29/6** each. POST PAID. EXTRA D/E771

RECEIVER UNIT R3601

Ref. 10DB6037.
ASK FOR **39/6** each. CARRIAGE PAID D/H493

PLEASE NOTE.—Carriage and Postal charges refer to the U.K. only. Overseas freight, etc. Extra.

Order direct from:

CLYDESDALE SUPPLY CO. LTD.

2, BRIDGE ST., GLASGOW, C.S.

'Phone: SOUTH 2706/9

TV. BARGAINS—

COLVERN PRE-SET WIREWOUND POTENTIOMETERS
—100 ohms to 30 k., 3/2 each. Carbon pots, 2/6, with switch, 4/-, 1/2 w. resistors, 4d. each; 1 w., 8d. All preferred values stock.

VALVE CANS
B7G or B9A Moulded Holder and Can, 1.6. I.O. Can (3 piece), 1.6. E.H.T. (OILS. 6-9 kv., 15/-; 6-18 kv., 25/-; with circuits. 4/-).

SWITCHES
New Midget Type, 2 p. 2 w., 2 p. 3-way, 2.6. 1 p. 12 w., 2 p. 6-way, 3 p. 4 w., 4 p. 3-way, 3.6. Yaxley Standard (two bank), 2 p. 11-way, 6 p. 3-way, 4 p. 5 w., 8 p. 2 w., 7.6.

MISCELLANEOUS
Pair of Best Quality Test Prods, 1.9 pair. Adcola Soldering Iron, 25.6, with detachable bit, 3.6. Stand, 10.6. Henley's New Instrument Iron, 18.9. Pyana, 14.11. Multicoore 18 s.w.g. Solder, 5/- per carton. Flux, 1.6. 2 v., 6 v. or 12 v. at 2 a. Charging Transformer, 19.6. 4 a. Type, 22.6. Ellison 60 ma. 250-0-250 v. 6.3 v. and 5 v. fully shrouded Midget Mains Transformer, 21.6. A.E., L.S. or P.U. Socket Strips, 6d. each; 5/- doz. Volts Adjustment Panels, 1.2.

TV. TRANSFORMERS
350-0-350, 250 ma. 6.3 v. 8 a., 5 v. 3 a., 6.3 v. tapped 2 v., fully shrouded, 67/6. Denco Wide Angle Line Trans., 42-. Allen, 40-. Haynes Frame Blocking Trans., TQ135, 18.6. 120 ma. 250-0-250 v. 6.3 v. 5 a., 5 v. 5 a., fully shrouded, 39/6. Allen TV. Auto AT310, 30/-.

HIGH STABILITY 2% 1/2 W. RESISTORS
All values (preferable 100 ohms to 2 meg., 1/8 each. 5% wirewound up to 7 watt, 2/3. 10 w., 2.9. 40 ohms to 10 k.

BOOKS
"How to Make Electronic Gadgets," 3.6. "TV. Faults," 5/-. "TV. Fault Finding," 5/-. "Radio Servicing Instruments," 4.6. "Viewmaster Plans," 7.6. "Soundmaster," 6.6. "Teletking," 6/-. "Personal Portables," 2.6. "The Oscilloscope Book," 5/-. "World Valve Manual," 3.6. "Brimar," 5/-. "T.R.F. and Superhet Tuner Unit Plans," 2.6.

CONDENSERS
.01 5,000 v., 2/9 (oil filled), .5 400 v., 8d., 5/- doz., .01, .1, .001, .002, .02, .05, 6d., 5/- doz., .0016 kv., 6/-. .0012 kv., 10/- or 15 kv., 10/-. .016 kv., 7.6. .1 7 kv., 20/- (all T.C.C. Visconol).

VALVES
6U5 Magic Eye, 7/-, AC6PEN, 5/-. HVRA2, 4.6. KT241 (7 pin 4 v.), 5/-. 12SC7 D Triode, 4.6. 6N1, 6.6. 6BW6, 7.6. 6AT6, 7.6. 6X4, 7.6. KT36, 8/6. All available BVA types.

ODDS AND ENDS
1/2 in. Polystyrene Spindle Extensions with 1/2 in. Panel Bush, 4in., 1 10. 8in., 2.3. Brass Couplers, 8d., 1/2 in. Alladin Formers and Cores, 7d. 1/2 in., 10d. Denco Maxi "Q" Formers, 1/8 each.

All Coils Stocked: Osborn, Denco, Weymouth, Wearite, S.A.E. for List or Quote.
Post 6d. up to 5/-, 1/- up to £1. 1/6 to £2. C.O.D. over £1/-.

RADIO SERVICING CO., 82, SOUTH EALING ROAD, EALING 5737. Next to South Ealing Tube Station

SOLDERING - SAFE - SIMPLE - SPEEDY

with the sensational



PRIMAX —★

BALANCED GRIP SOLDERING GUN

The PRIMAX-SOLDERER is the ideal tool for any RADIO-TV-TELEPHONE mechanic or amateur. Just the tool for service calls and small jobs on the bench. The Primax-Solderer works on a different principle from that of commonly known soldering irons. A current of high amperage produced in the transformer will heat the soldering tip within 6 seconds. 220/250v. A.C., 50/60 cycles (60w.). One year guarantee.

Specially designed for easy soldering on hard-to-reach jobs. TRIGGER CONTROL.

- ★ EXCLUSIVE ALLOY TIP—never needs re-tinning, lasts indefinitely under normal use.
- ★ INSTANT HEATING—Ready for soldering in 6 seconds.
- ★ COMPACT LIGHTWEIGHT—slips into your pocket or tool kit, weighs only 23 ounces.

Sole Distributors:—
S. KEMPNER, 19 Ebury Street, London, S.W.1
Tel. SLOANE 3586 Through wholesalers; and retailers

TALLON CABINETS

for television, radio and gramms, polished, ready for assembly in packed flat kits or factory assembled.

TELE-KING cabinets with space for radio or tape recorder with or without doors, for 15", 16", or 17"

VIEW MASTER cabinets, console or table, 12 and 17in.

P.W. 3-SPEED AUTO-GRAM CABINET.

LYNX CABINET.

ARGUS CABINET.

RADIOGRAM, RADIO AND SPECIAL CABINETS TO CUSTOMERS' DESIGNS. SOUNDMASTER TAPE RECORDER CABINETS

MINI-FOUR AND CRYSTAL DIODE cases at 14/- each, including postage.

Consult your local dealer or write to:
(DEPT. P.T.I.)

JAMES TALLON & SONS LTD.

MANOR WORKS, MANOR ROAD
RUGBY Telephone: RUGBY 2070

MONEY BACK
GUARANTEE

DUKE & CO

Tele: GRA 6677

CWO
or
COD

621 ROMFORD RD. LONDON. E.12.

12"

£5

TV TUBES

3 MONTHS
GUARANTEE

MAZDA CRM121-A-B, and a few other types and makes. Picture shown to callers. Not Ex-W.D. Carriage and insurance 15/6 extra. No catch. Special offer of tubes with burns for testing and spares at 30/- each.

SALVAGE VALVE CLEARANCE SALE

8-9	6/9	5/9	3/9
6F15	1A5	3V4	1LD5
6BE6	1T4	12Y4	1LN5
6BW6	1S4	210VPT	4D1
6BA6	1S5	77	6AB7
6V6	6K7	E1436	37
8D3	EL91	KTW61	CV6
6F1	6AM5	OZ4A	UM4 (M. eye)
			SP2 (5 pin)

Postage on valves 1/- up to 6.

RECTIFIERS

Selenium type, 180 volt at 40 mA., 3/9. Metal recs., 300 v. 200 mA. Also 200 v. 80mA.; either at 8/9. T.V. type, new, 300 v. 200 mA., 12/9. P. & P. on rec., 1/-.

P.M. 12" 10" SPEAKERS 8" 6"


12in. Truvov, 47/6; 10in. 25/9; 8in., 18/6; 6½in., 14/9; 5in., 13/9. All 3 ohms. Best makes. P. & P. 1/9.

SPOTLIGHTS.—8/9 Butlers, new but ex-W.D. 7½in. dia., 6½in. deep. These lights are similar to those sold for £3-£5, but finished Black. The lamp fitting is of the pre-focus type, this can be easily changed by fitting a holder from side light (1/9). Also a chrome screw is required to cover hole in centre of glass. Post 1/3.

SIDELIGHTS.—1/9. Infra-red glass. Ideal tail lamps. New ex-W.D. Post 9d.

INTERFERENCE & NOISE SUPPRESSOR.—5/9. Cuts out frig., hair drier, etc., interference. Post 1/3.

STAMP ONLY FOR 1954 CATALOGUE.

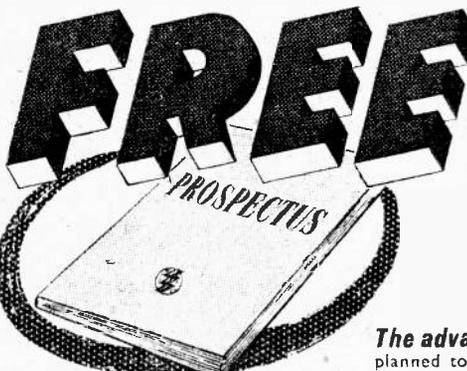

POST THE COUPON TODAY FOR OUR
BROCHURE ON THE LATEST METHODS
OF HOME TRAINING FOR OVER
150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME

City and Guilds Grouped Certificates in Telecommunications; A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY.

With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Courses from
£1 per month

POST THIS COUPON TODAY

Send without obligation your FREE book.
E.M.I. INSTITUTES, Dept. 138K
43 Grove Park Road, London, W.4.
Phone: Chiswick 4417/8.

NAME

ADDRESS

SUBJECT(S) OF INTEREST

EMI INSTITUTES

The only Postal College which is part of
a world-wide Industrial Organisation.

YOUR Problems SOLVED

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 47 must be attached to all Queries, and if a post. reply is required a stamped and addressed envelope must be enclosed.

LACK OF WIDTH

Could you help me with a fault on my "View Master"? My width control only opens out full to a 9in. tube and not a bit over; after that just one side opens out and that is on the linearity side, and the other side remains stationary. I have always had the picture wider on that side and I cannot overcome it. Would you kindly help me?—F. J. Morley (S. E.14).

Insufficient line width may be due to the voltages in the V10 stage being on the low side and we suggest that this should be measured and, if necessary, corrected; also ensure that the correct boost volts are obtained across C42, if necessary replacing MR2 and V10.

REPLACING BRIMISTOR

Could you inform me as to the correct value for a 1 watt resistor, in series with the heaters and heater voltage dropper resistor, in the Ferguson Model 998T, 12in.?

The resistance in question must have suffered from a dry joint, as the increase in resistance caused severe thermal agitation, resulting in the colour code being burned off.—R. G. Stevens (Nr. Loughborough).

A 1-watt resistor is not used in the heater circuit of the Ferguson type 998T. We feel that you may be referring to the Brimistor type CZ1A; this is connected between the heater of the H.T. rectifier (PY82) and the mains dropper. In certain sets a thermistance is used instead of a Brimistor. When a Brimistor is employed, however, a 350Ω 5-watt wire-wound resistor is connected in parallel. It should be mentioned that it is quite normal for these components to work at a very high temperature.

CHANGING A TUBE

The Emiscope tube of my H.M.V. 1949 No. 1804 10in. tube, type 3/4 has just blown. As I have always wanted a larger picture, can you give me any details as to the possibility of putting in a 12in. tube without too much modification?—D. G. Lewis (Romford).

Your model set is not readily adaptable to cater for a current type 12in. picture-tube. There is an older style 14in. tube, however—Emiscope type 3/5—that could be used in the receiver without any electrical modification of any kind. This tube is now generally available for replacement purposes only.

I.F. COIL DATA

I have a Sobell Model T91 which has recently

developed trouble which I have localised to the T4 sound transformer (9.5 Mc/s?). Unfortunately, the fault destroyed the turns on this component and I would like to rewind it. The component is now obsolete with the makers. Could you please provide me with the turns, spacing, etc., required to perform this operation?—C. J. Hurley (Tylorstown).

This data is not available and is not issued by the manufacturers. You should be able to deduce the approximate number of turns required and the mode of winding by examining the adjacent transformer in the sound channel. It may be necessary to modify the number of turns slightly to obtain the optimum tuning point.

IMPERFECT FOCUSING

I have recently fitted an "Elac" Duomag focaliser, type No. FD14/9 medium flux to my "View Master," which uses a Mullard tube MW 31-16 (12in.), and find it totally unsuitable.

It was specified that a "tetrode" tube was being used, and my dealer, although I think in some doubt, recommended medium flux.

I find that the brightness of the spot is affected, and no matter how I move the focaliser, either towards or away from the deflection coils, I cannot get even a rough focus.

I should therefore appreciate it very much if you could let me have your remarks and recommendations at your earliest convenience.—Alan Lewis (Selby).

From your description it is quite evident that your focusing arrangement is unsuitable. It is probable that the focus flux is excessive for a tetrode tube, and, in addition, it is possible that it is too large physically, causing a variation in the magnetic field of the ion trap magnet. Hence there will be a variation in brightness when adjusting focusing. As this type of focus magnet is an unspecified type, we have no operating experience with it on this particular receiver.

FAULTY TUBE

I have an Ultra TV model W470, 9in. tube. I have had three service engineers overhaul it within one month but still cannot get a satisfactory performance for more than 1½ hours' continuous viewing. The I.F. chassis has been sent to the makers for check-up and was returned fitted with a new oscillator coil and two new valves. They diagnosed "frequency creep." These replacements have not made any difference to the performance.

These are the symptoms: After warming up for 10 minutes, the picture comes up quite good with contrast, focus and definition quite good. After about 90 minutes' viewing the picture slowly darkens with a falling of contrast and high-lights until the whole picture becomes milky. Any further adjustment of the contrast control makes the picture fade to almost a plain milky screen.

I shall be glad if you will diagnose the trouble and tell me what the fault or faults may be.—T. W. Bond (S.E.10).

On the face of it, this symptom would seem to be the result of a defective picture-tube. Many unusual effects are caused by a picture-tube that deteriorates in efficiency and alters in characteristics after it has been working for a while. Unfortunately, a fault of this nature can be proved only by substituting the suspected component.

RESISTOR VALUE CHANGE

On my television receiver Pye FCI the line hold control has got gradually more critical.

Looking at the back of the receiver the control knob has to be turned fully anti-clockwise to prevent the picture tearing. I have tried different EF80 valves, but there is no improvement.—W. Paterson (Hambleton).

This symptom on the Pye series is nearly always caused by an alteration in value of a resistor directly associated with the line hold circuit. If you examine this section, two resistors will be observed connected to the line hold potentiometer: the one connected to the slider of the control should measure 150,000 Ω and the one connected to the high potential side of the control should measure 39,000 Ω . These resistors should be checked for value and replaced if necessary.

POOR INTERLACE

I would welcome your advice regarding my "View Master," constructed for double-deck working, using a 12in. Mullard 31-17 tube.

I have recently noticed that a fault has developed with the interlacing—it appears to be pairing on lines. I have checked wiring, changed valves, but cannot locate the fault. I will also mention that to obtain a reasonable line hold I can only do so by doubling the value of the resistor in series with the variable line hold.

I trust that you will be able to assist me with the mentioned faults.—G. A. Wright (Orpington).

To improve interlacing it is probably only necessary slightly to reduce the value of R57.

The increase in the value of R44 can have no connection with difficulty in interlacing, and in any case will cause no harm.

LOW E.H.T.

I have a Cossor television set, model No. 926.

For 18 months it has given perfect results, but now on switching on the picture height is extended considerably and the focus is very bad. The focus can be brought back by turning the control fully over (focus control R77).

After about 10 to 15 minutes the picture height has shrunk to normal and the focus control has to be readjusted, then picture is perfect until next switch-on.

Can you give me a lead to the fault?—A. H. March (New Malden).

The main cause of this trouble is low E.H.T. voltage, which gradually increases nearly to normal after the set has been in operation for a while. This in a large number of cases is due to a defect in the E.H.T. rectifier valve, which results in low emission after the valve commences to conduct, but gradually returns to something like normal after the cathode has been emitting for a while. The valve concerned in your set is an SU61, and is positioned underneath the removable metal top of the line output transformer can.

FAULTY RECTIFIER VALVE

Could you help me rectify a fault which has developed in my "Ultra" TV model VA7216? On switching on screen fully lights up, then after about one minute it suddenly cuts right out, leaving the screen blank and leaving a spot in the centre of tube, which also dies out. If I switch on after a short period again it comes on with loud hum and remains O.K. for rest of programme. This trouble happens regularly.—A. Woodroffe (Birmingham, 18).

The effect you describe is often caused by an intermittent defect in a section of the U801 valve. This is positioned behind a metal shield at the right-hand side of the chassis when viewing from the rear of the cabinet.

MAINS TRANSFORMER FAULT

I shall be much obliged if you will assist me in locating some trouble I am experiencing with my "View Master" television on which I use a 12in. G.E.C. aluminised tube type 6705A and E.H.T. boost.

On most occasions on switching on the neon warning lamp glows and the valve heaters and C.R.T. remain dead, although the mains plug is properly connected. On the occasions when the neon lamp remains dead, the valve heaters function, but after the normal heating-up time the tube face becomes very bright with the flyback lines showing and the picture hardly noticeable behind the brightness. On reducing the gain, the usual point is reached where line slip occurs, but on increasing the gain no noticeable change takes place and the brightness control has no effect on the screen. The sound is as normal.—W. Cameron (Glasgow, S.4).

There appear to be two quite separate faults in your receiver. In the first place, if your neon lights but the heaters do not, it must merely indicate a disconnection to your mains transformer, possibly due to a faulty mains switch. When your receiver is operating and the brightness is excessive, it may be due to a fault in your C.R.T., a fault in the brightness control circuit, though this should be shown up by a voltage measurement and, possibly, by a failure in the operating conditions of V5, such as a short-circuit across R70, which may prevent sufficient bias being developed.

SOUND ON VISION

I have a Philco model T1412. It is two years old. When test card is on the centre ring appears to be moving round, and when raster is on the black vertical band seems to be flowing down. It is a good picture, but when anyone is singing loudly waves start to move up the screen.

I would be very grateful if you could determine the fault for me.—J. Derbyshire (Newton-le-Willows).

This is the symptom of sound interference on vision. Several factors could cause the effect, but in the main you should carefully check the following: general alignment of the tuned circuits; excessive aerial signal—this would be evidenced by little or no setting of contrast to resolve a picture; a microphonic valve associated with the frame timebase (in this case the effect would be displayed in more severe form as the volume control is turned up).

REPLACING A RESISTOR

On switching my Pye BV30 TV there was a crack; the sound was on, but no picture. I took the set out and under the PZ30 and PL38 valves I found a wirewound resistor burnt out; it is the only wire resistor in the set. Could you help me by telling me the value of it?—Benison (Workshop).

The wirewound resistor to which you refer is probably the line-output valve screen feed. This has a value of 1,500 ohms, but before replacing check the insulation of the 0.1 microfarad capacitor which is connected between one side of the resistor and chassis. The capacitor generally short-circuits to cause the resistor to burn out.

RADIO UNLIMITED offer: Valves, new/boxed, 5/- each; 1L4, 3A4, EB91, 6K7, 6B8, 12J5, 6J5M, 6CS, D63, LP2, EF50, SP41, SP61, ARP12, AR8, 6K6, 6H6M; at 6/6 each, 6J7M, 6V6, 6P6, EL32, 6X5, 12SL7, VR101, 6SK7, EF91, EF92; at 8/6 each, 5Z4, U14, 6BE6, 6BA6, 6BW6, 12AT7, 6AT6; at 7/6 each, 1T4, 1S4, 1S5, 1R5, 3S4, 3V4; c/plate sets, 5Z4, 6V6, 6K7, 6Q7, 6K8, 35/-; Viewmaster set of 12, £26/2/6; Viewmaster Coils, 17/6 set, incl. choke; Iso. Trans., 2v. 4v or 6v, 6/6; V/master Fil. Trans., 35/-; Coilpacks, 1. med., short, 24/6; Heater Trans., 200/240v, 6.3v at 1.5a, 5/6; Chokes, 100-65ma, 5/-; Co-ax. Cable, 7/6 doz. Vds.; Corod Solder, 16oz. ctn., 8/9. New lists available. **RADIO UNLIMITED**, Elm Road, London, E.17. (KEY 4183.)

VIEWMASTER (Sutton Coldfield) completed 12in. Console chassis, valves, tube with cathode heater short, speaker, pre-amp; offer nearest £25. **OWEN**, "Northdown," Beech Street, Highley, nr. Kidderminster.

T.V. AND RADIO Service Sheets. 2/3. Sales/loan list, 1/-; s.a.c. **RATEL**, 171, Norris St., Preston.

TELEVISION.—All home-built TV Coil Sets; 3in. TV Canned Formers. 2/3; Commercial Converters, £15. **BEL**, Marlborough Yard, N.19. (ARC. 5078.)

SENSATIONAL AMPLIFIER, fully isolated A.C., 3 int. oct. valves, vol. and neg. fedbk. controls, dual input, 2 ohm out; no ex-Govt. components; newly wired and tested; 79/6. **E. K. ELPHEE**, 47, Arksey Lane, Bentley, Doncaster.

SUPPRESS THAT APPLIANCE with the First Lead Suppressor for med., short and T.V. bands combined. **Belling Lee** 799 for 2 or 3 core, 17/6, d.p. 6d.

For T.V. only use our Midget Iron Dust Chokes and Button Condensers, specially designed for small spaces. 3/6 set of 4, p.p. 3d.; state 1 amp or 2 amp. **SERVIO RADIO**, 156-8, Merton Rd., Wimbledon, S.W.19. (Liberty 6525.)

ELECTRONIC TESTER required for fault tracing and repairs on miniature audio equipment including work on transistor circuits. Please write with details of experience and wages required to **PERSONNEL OFFICER**, Fortiphone Ltd., 22-27, Addington Square, S.E.5.

STORAGE BATTERIES, 12v, 75AH heavy duty, 19 plates, separate cells in hardwood cases; finest possible specification. £5/17/6, 9/6 delivery; 12v, 22AH, almost similar specification, surprisingly powerful. £2/14/-, delivery 5/6; 6v, 90 AH, 15 plates, hard rubber Cells, also suitable for cars, tractors, lorries, etc. £3/7/6, delivery 7/6; 6v, 150 AH, extra heavy duty, 25 plates, separate cells in hardwood cases, £5/7/6, delivery 8/6. **TEDDINGTON ENGINEERING CO. LTD.**, Dept. "C," High St., Teddington, Middx. (KINGston 1193-4.)

MESSRS. JASSOY & HAYES, F.V.I., A.A.L.P.A., Agents to the Radio/Television Trades, can offer several businesses for sale as going concerns to those enthusiasts wishing to branch out on their own. Write and give particulars of requirements. **JASSOY & HAYES (P.T. Dept.)**, 23, Leinster Terrace, London, W.2. (AMB. 9575.)

RATES

4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

"VIEWMASTER" Valves, exact to specification, guaranteed new and boxed, set of 12, £5/15/-, post free; "Tele-King" 17in. Receiver, complete set of 17 valves, exact to specification, £8/19/6, post free; 6AM6, EP91, 6F12, 277, EB91, 6AL5, 6AM5, EL91, any 8 for 50/-, post 1/6; 1.4v miniatures, 1S5, 1R5, 1T4, 3V4, 3S4, 1S4, DK92, any 4 for 27/6, post 1/-. All guaranteed brand new and boxed. For individual prices and other types, see displayed advert., p. 48. **READERS RADIO**, 24, Colberg Place, Stamford Hill, London, N.16. (STA 4587.)

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Bullingdon Rd., Oxford.

ELECTRONIC COMPONENTS. Send stamp for interesting comprehensive bargain list. **A. J. S. McMILLAN**, 5, Oakfield Rd., Bristol, 8.

VCR511A 12in. Electrostatic Tube, £5. Write: **R. HALLETT**, 30, Denholme Rd., W.9.

TRANSFORMERS: EMI. Input, 110/245v, outputs 350/0/350v, 120ma, 6v. 4a; 2v, 2a, Dropthrn., 18/-, 1p, paid; Meters: 2in. sq., 5 or 100ma, 7/-; 2in. rd. 4a, AC, 8/6; 2in. rd. fl., 100, 200 or 20ma, 8/-; 15v. a.c., 10/6; 130v. AC/DC (1ma FSD), 15/6. Pots, w/w. 29 k. 10w, 3in. dia., 3/6. Condensers, 5 2.5kVw block, 4/6; 500 or 750pF. Ceramic, 15kVw, pair 5/6; 8mfd, 500v block, 4/6; R.F. Units: 24, 25, 15/-; 26, 27, 35/-, with valves. Dynamotors, soiled cases, input 6 or 12v), output 250v, 80ma approx., 8/6 (p.p. 2/-). LT/HT Filter for these, 2/6, c.w.o., post extra; immediate despatch. S.A.E. for List/Inquiries. **W. A. BENSON**, 308, Rathbone Rd., Liverpool, 13.

MANUFACTURER'S SURPLUS STOCK.—Telefridge Service, 193, Mare Street, Hackney, have pleasure in announcing the opening of a special department solely for the convenience of the home constructor and radio enthusiasts everywhere. Electronic spares and service sheets a speciality. Send 2ld. stamp for free list. Personal callers welcomed. (Amherst 4426.)

AMERICAN MAGAZINES.—One-year "Audio Engineering," 28/6, specimen copy, 3/-; "High Fidelity," 50/-, specimen copy, 4/6; "Popular Science," 28/6. Free booklet quoting others. **WILLEN LTD.** (Dept. 23), 101, Fleet Street, London, E.C.4.

HIGH GAIN 4W 230-250 AC Audio Amplifier, suitable mike or gram., with tone control; chassis 3in. x 6in. or 9in. x 4in., price £5/14/-, complete with valves and fully wired. Controls, less switch, 3in. spindle, 1/8 each pre-set 25K (miniature); 2 Meg Spindle, 1in. long (min.); pre-set 20K (1 1/2in. dia.); 2K spindle, 3in. long (1 1/2in. dia.); Alum. alloy tube, 3in. dia., 18SWG, 9d. ft.; 1 1/2in. dia. for cross arm, 2/- ft.; cast mast-head Bracket for 2in. pole, 8/6 (with 4 "U" bolts); 2in. dia. high tensile Poles, 10ft., 32/6, 12ft. 30/-, 20ft. 65/-; double Chimney Lashings, complete, 30/-, single 25/-; please add a little for carriage. **GLADSTONE RADIO**, Gladstone Place, Newton Abbot, Devon.

SIMPLEX T.V. 18 swg. Chassis with screens and valve punched 17/6, post 1/6; fully-wound Coil Sets 15/-, post 1/6; Lynx wound Coil Sets, 35/-, post 1/6; Super-Visor and Tele-King Coil Sets 37/6, post 1/6; 3in. square Cans, Former, Side Wires, etc., 1/9 each; Simplex Mains Transformers, 27/6, post 1/6. **C. O. PRESTON & SON**, Healey Lane, Batley, Yorks.

ALL YOUR T.V. COMPONENTS. Valves, Books and Transformer Rewinds can now be obtained from one source. Send 9d. stamps for new "Replacement and Rewind Manual." "DIRECT T.V. REPLACEMENTS," 134-136, Lewisham Way, New Cross, S.E.14. (Tideway 3696, 2330.)

50 SECONDHAND Televisions always for sale; famous makes. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

BOOKLETS: "How to use ex-Gov. Lenses and Prisms." Nos. 1 and 2, price 2/6. Ex-Gov. Optical lists free for s.a.e. **H. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

SELLING UP quantity of Radio/TV Components. Send s.a.e. for details. Box 169, c/o PRACTICAL TELEVISION.

WANTED

NEW VALVES WANTED, small or large quantities, 3Q4, 6V6, 5Z4, ECL80, EF80, EY51, PL81, PY82, KT61, 6L6N, VR150/30, 5R4, 80, etc., etc. Prompt cash. **WM. CARVIS**, 103, North Street, Leeds, 7.

EDUCATIONAL

I.P.R.E. Data for constructing TV Aerial-strength Meter, 7/6; 5,500 Alignment Peaks for superhets, 5/9; sample copy "Practical Radio Engineer," 2/-, Membership-examination particulars, 1/-. Syllabus of seven postal courses free and post free. **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast, or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest electronic organisation; moderate fees. Write to **E.M.I. INSTITUTES**, Postal Division, Dept. PT28, 43, Grove Park Road, London, W.4. (Associated with H.M.V.)

S.R.S.

HOME CONSTRUCTORS

"VIEW" THESE PRICES !!

TELEKING COMPONENTS

Chassis parts. 50 : T.C.C. Condenser Kit. £7 4 2 : Valve-holders-plugs. 24 6 : Resistor Kit. 40 9 : FK1-9 Coil Kit. 44 6 : LO308 Line Scan Trans. 40 : DC300C Deflector Coil. 39 6 : FC302 Focus Coil. 31 : FC305 Frame O P Trans. 21 : GL18 Width Control. 7 6 : GL16 Linearity Control. 7 6 : BT314 Frame Blocking Trans. 15 : SC312 Smoothing Choke. 21 : OP117 Sound O P Trans. 15 :
SEND FOR CONSTRUCTION ENVELOPE. PRICE 6.

SUPERVISOR COMPONENTS
 Most of the above T.K. Wide Angle Scanning Components are specified for use in construction of the P.T. Supervisor.

"SIMPLEX"

ALL COMPONENTS BRAND NEW

PUNCHED ALUMINIUM CHASSIS.—Complete with screens and bracket, 20 :.

RECTIFIERS.—Sen-ter-sel RM3 at 5 9 : pencil type K3 40, 7 : VALVES.—EF50, 7 6 : SP61, 4 6 : 6SN7, 12 6 : 6J5, 5 9 : EB34, 3 9 : EA50, 3 9.

VALVE HOLDERS.—EF50, ceramic, 1 - : inter.octal. 6d. : Mazda/octal. 6d. : diode. 6d.

CONDENSERS.—25 mfd. 25 v. 1 6 : 16 x 16 mfd. 450 v. 6 8 : 32 x 32 mfd. 450 v. 7 : 1 mfd. 2,500 v. 4 6 : .001 mfd. 500 v. 8d. : .005 mfd. 500 v. 8d. : .01 mfd. 350 v. 8p. : 1 mfd. 500 v. 10d. Silver micas (all values), 6d.

RESISTORS.—1 watt. 4d. : 1 watt. 5d. : 1 watt. 6d. : 5 watt. 1/6.

COIL FORMERS.—1in., 8d. : 1in., 10d.

T.C.C. "VISCONE" E.H.T. CONDENSERS

.0005 mfd. 15 kv. D.C. Type CP56W0. Price, 5/6 each. 500 pf. 10 kv. D.C. Type CP55T0. Price, 3 6 each.

SEND FOR S.R. RADIO & TV CATALOGUE

which gives detailed descriptions and illustrations of all types of Radio and Television Components in stock : Radio Chassis. Cabinets, Autochangers, Amplifiers, Tape-decks, Condensers, Resistors, etc. Price, 6d., post free.

TERMS.—Cash With Order or C.O.D. Extra charge for C.O.D. Please add postage. Open 9 a.m.-6 p.m. Monday to Saturday, 1 p.m. Thursday.

SUPERIOR RADIO SUPPLIES


37, HILLSIDE, STONEBRIDGE, N.W.10
 Phone : ELGar 3644

THIS IS "BIB"
The NEW wire cutter and stripper

ONLY


3/9

post paid

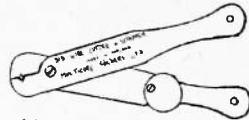

Easily strips insulation without nicking wire. Adjustable to different sizes of wire. Cuts and splits wire and twin flexes. Individually boxed with full instructions. Manufactured by Multicore Solders, Ltd. and obtainable from HOME RADIO. You will wonder how you ever managed without one of these fine little tools. Size 5in. long.

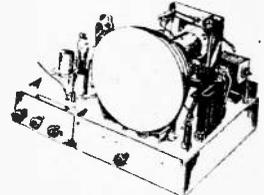"VIEWMASTER"
or "SIMPLEX"
COMPONENT
PARTS BY RETURN



Simplex mains transformer	£2/4/-	(2/- post)
.. choke	15/-	(1/6 post)
.. all chassis 15in. x 18in. x 2 1/2in.	15/-	(1/- post)
EF50 (VR91), ea.	6/-	...
EA50 (VR92) "	2/6	SP61 (CV118) ... 4/3
6H6	4/-	6J5GT ... 5/-
3in. Alladin formers with slug	6SN7GT ... 10/-
1in.	10d
S.A.E. for full "SIMPLEX" price list.	8d.

Goods despatched by return. C.W.O. or C.O.D. Please add postage under £1.

Obtainable direct from :—

HOME RADIO 187, LONDON ROAD, MITCHAM, SURREY.

MIT 3282. (Open until 6.30 p.m. every day. Weds. 1 p.m.)

TELEVISION RECEIVER CONVERSION

The type AC/4 unit permits receivers to be used for reception of other channels without re-tuning or alterations.

Type AC/4KL (New Brighton transmitter or Kirk o'Shotts on a London receiver).

Type AC/4WL (Wenvoe on a London receiver).

Type AC/4WB (Wenvoe on a Sutton Coldfield receiver).

Also available for all other conversions. The unit is complete with 5 valves and self-contained power supply unit. Price 15 gns. complete from your Dealer or C.O.D.

Type AC/3 neutralized triode PRE-AMPLIFIER without doubt the best Pre-amplifier available. Price complete, 10 gns. from your Dealer or C.O.D.

Illustrated leaflets, etc., on request.

SPENCER - WEST

Quay Works, Gt. Yarmouth

Phone : 3009. Telegrams : Spencer-West, Gt. Yarmouth.

OPPORTUNITIES IN TELEVISION

144 pages

Free!



Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointment Dept.

We Guarantee "NO PASS—NO FEE"

If you are earning less than £15 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

WRITE TODAY!

British Institute of Engineering Technology
 237, College House,
 29-31, Wright's Lane,
 Kensington, W.8.

BIET

COVENTRY RADIO

189, DUNSTABLE ROAD, LUTON

Tel : Luton 2677

COMPONENT SPECIALISTS SINCE 1925

All B.V.A. and Tungram Valves in Stock.

EDDYSTONE COMMUNICATION SETS AND COMPONENTS

Short Wave Components Catalogue 1/-, plus 3d. postage.

We are preparing an entirely new Components Catalogue 1954, which will be interesting and helpful, ready shortly. Price 1 -.

Our No. 1 and No. 2 Circuits, 5 Valve Superhet and 4 Watt Amplifier, 1 -, plus postage.

Special quotations on kits of parts or large orders.

News from the Trade

TWO NEW TELEVIDOR RECEIVERS HAVE CONVERTOR UNIT SOCKETS

TWO new television receivers have been added to the Vidor range. Both have a socket for a multi-channel convertor unit giving second and third programmes. Model CN 4220 has a 14in. flat, daylight viewing tube and retails at 65 guineas including purchase tax. The 17in. TeleVidor—CN 4221—is priced at 74 guineas including tax.

The convertor unit socket embodied in the new TeleVidors provides for an input at the intermediate frequency, thus eliminating the interference from Band I stations.

The socket also enables the heater and H.T. power to be fed to the convertor from the receiver chassis, thus dispensing with the need for a separate power supply. By adopting this system Vidor hope to provide in due course a suitable convertor at minimum cost.

All TeleVidor receivers are superheterodynes and have no special circuitry which would complicate their adaptation for use with any standard convertor.

Manufacture of the TeleVidor 12in. receiver—model CN 4216—will continue, and the price remain unchanged at 56 guineas with tax.—Vidor-Burndept, 18, Abbey House, Victoria Street, S.W.1.

WOLSEY ADDITIONS

A FURTHER addition to the range of Wolsey "Quick-Fix" aeriels, the "Deltex," introduced for the first time at the 1954 R.E.C.M.F. Exhibition, is an X-shaped aerial with the added advantage of delta matching which, by ensuring correct matching of aerial to feeder, results in marked gain and performance over similar aeriels that are not matched.

The "Deltex" is supplied completely pre-assembled for speedy erection, the $\frac{1}{2}$ in. dia. 18 s.w.g. elements being swivelled into position and firmly clamped by one bolt only, the clamp being of very robust



This is the "Nuray" heater booster unit which was described in this section in last month's issue. It is available from Direct TV Replacements, 134-136, Lewisham Way, S.E.14.

construction in corrosion-resisting alloy. The matching stubs complete with junction box are attached at one end and when swung into position are clamped at the other by the insertion of one bolt and tightening of a wing nut. The diecast junction box is specially sealed to prevent entry of moisture and designed for ease of making connections. Available for all channels, suitable for wall mounting, mast mounting or chimney lashing.

Price of the DX/L kit comprising the "Deltex" aerial, 6ft. by $1\frac{1}{2}$ in. duralumin stand-off arm and complete set of chimney lashings with aluminium diecast chimney bracket is 77s. 6d. retail.

With a view to assisting the engineer, and for providing the most efficient contact, Wolsey have introduced the new solderless co-axial plug. This can be quickly and easily assembled, and obviates the necessity for soldering. The dimensions of the cable of which it will accept are from .2in. to .312in., and by the action of the collet ensures a firm grip on the cable. The plug is manufactured of brass, nickel finish and is nylon insulated, price 1s. 2d. retail.

Wolsey Television, Ltd., 43-45, Knights Hill, West Norwood, S.E.27.

TRICOLOR PICTURE TUBE

RECENTLY made commercially available by the RCA tube department, the 15GP22 is a directly viewed picture tube of the glass-envelope type for use in colour television receivers. It is capable of producing either a full-colour or a black-and-white picture $11\frac{1}{2}$ in. by $8\frac{3}{4}$ in. with rounded sides (double-D).

The 15GP22 utilises three electrostatic-focus guns spaced 120 deg. apart with axes parallel to the tube axis; magnetic deflection; electrostatic convergence; and an assembly consisting of a shadow mask and a plane, tricolour, filterglass phosphor-dot (screen) plate located between the shadow mask and a clear-glass faceplate.

The tricolor phosphor-dot plate, which serves as the directly viewed screen, carries an orderly array of small, closely spaced phosphor-dots arranged in triangular groups (trios). Each trio consists of a green-emitting dot, a red-emitting dot, and a blue-emitting dot. The phosphor-dot plate has approximately 195,000 dot trios or 585,000 dots and is metalised after application of the phosphor-dots to give increased light output and contrast, as well as to prevent ion-spot blemish.

The metal shadow mask, interposed between the electron-gun structure and the phosphor-dot plate, contains round holes equal in number to and centred with respect to the dot trios.

A technical bulletin for the 15GP22 may be obtained from RCA Photophone, Ltd., 36, Woodstock Grove, Shepherds Bush, London, W.12.

QUERIES COUPON

This Coupon is available until June 21st, 1954, and must accompany all Queries.

PRACTICAL TELEVISION, June, 1954.

RADIO SUPPLY CO. (Leeds)

LTD.

Dept. N.

32, THE CALLS, LEEDS, 2.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/1 charged on orders up to £1. From £1 to £3 add 2/0; over £3 post free. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 5d.; Trade List, 5d.

R.S.C. MAINS TRANSFORMERS

(Fully Guaranteed)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s Screened.

TOP SHROUDED, DROP THROUGH

250-0-250 v 70 ma. 6.3 v 2.5 a	12 11
250-0-250 v 70 ma. 6.3 v 2 a, 5 v 2 a	14 11
350-0-350 v 80 ma. 6.3 v 4 a, 5 v 3 a	17 6
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a	23 11
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a	23 11
350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a	29 11

FULLY SHROUDED UPRIGHT

250-0-250 v 60 ma. 6.3 v 2 a, 5 v 2 a, Midget type, 21-3 in.	16 9
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a	25 9
250-0-250 v 100 ma. 6.3 v 6 a, 5 v 3 a, for R1335 Conversion	31 6
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a	25 9
350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a	33 9
350-0-350 v 250 ma. 6.3 v 6 a, 4 v 3 a, 0-2 v 2 a, 4 v 3 a, for Electronic Engineering Television	67 6
425-0-425 v 200 ma. 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a, suitable Argus Television, etc.	49 9

FILAMENT TRANSFORMERS

All with 200-250 v 50 c/s Primaries: 6.3 v 1.3 a, 5.9 v 0.3 v 2 a, 7.6 v 0.4-5.3 v 2 a, 7.9 v 1.2 v 1 a, 7.11 v 5.3 v 3 a, 9.11 v 6.3 v 6 a, 17.9.

CHARGER TRANSFORMERS

All with 200-230-250 v 50 c/s Primaries: 0.9-1.5 v 1.5 a, 1.3 v 3 a; 0.9-1.5 v 3 a, 1.6 v 3 a; 0.9-1.5 v 6 a, 2.2 v 9 a; 0.9-1.5-3.0 v 3 a, 23.9.

E.H.T. TRANSFORMERS

5,000 v 5 ma, 2 v 2 a ... 39/6

SMOOTHING CHOKES

230 ma 7-10 h 200 ohms, Fully Shrouded 18/9
100 ma 10 h 150 ohms ... 7/8
80 ma 10 h 350 ohms ... 5/6
50 ma 40 h 1,000 ohms Potted... 8/11

BATTERY SET CONVERTER KIT

All parts for converting any type of Battery Receiver to A.C. mains 200-230 v 50 c/s. Supplied 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 at 0.4 to 1 a. Price, including circuit, 45/9. Or ready for use, 8/9 extra.

BATTERY CHARGER KITS.

For mains input, 200-250 v 50 c/s. To charge 6 v Acc. at 2 amps, 26/9; to charge 6 v or 12 v Acc. at 2 amps, 31/9; to charge 6 v or 12 v Acc. at 4 amps, 49/9. Above consist of transformer, F. W. Rectifier, Fuse, Fuseholder, Louvered, Blister Crackle, Steel Case and Circuit. Or ready for use, 6/9 extra.

EX-GOV'T. BLOCK PAPER CONDENSERS.

—1 mfd. 500 v. 2.9; 4 mfd 1,500 v. 5.9; 10 mfd 1,500 v. 7.9; 11.7 mfd 500 v. 7.9; 0.1 mfd plus 0.1 mfd 8,000 v, common negative isolated, 11/9.

EX-GOV'T. SMOOTHING CHOKES

100 ma 10 h 150 ohms Tropicalised ... 6/8
150 ma 10 h 150 ohms Tropicalised ... 6/9
250 ma 3 h 50 ohms Potted ... 7/11
250 ma 15 h 250 ohms ... 14/9
250 ma 10 h 100 ohms ... 16/9

EX-GOV'T. E.H.T. SMOOTHERS

.92 mfd 8 Kv. 1 1/1; 0.1 mfd 2,000 v. 1 1/1; 0.25 mfd 5,000 v. 3/9; 0.5 mfd 3,500 v. 3/6.

R.F. UNITS TYPES 26.

—Brand new. Cartoned. 39/6 plus carr. 2/6.

ELECTROLYTICS.

—Tubular 8 mfd 450 v. 1 1/1; 16 mfd 450 v. 2 1/1; Can 8-3 mfd 450 v. 3 1/1; 8-16 mfd 450 v. 2 1/1; 16-16 mfd 450 v. 4 1/1; 32 mfd 350 v. 2 1/1; 32 mfd 450 v. 4 1/1; 32-32 mfd 350 v. 5 1/1; 32-32 mfd 450 v. 5 1/1; 61 mfd 450 v. 4/9; 60-100 mfd 450 v. 7/9; 50-50 mfd 350 v. 3/9.

SPECIAL OFFER.

—Midget Mains Trans., 230 v input, 275-0-275 v 70 ma. 6.3 v 2 a, 10 1/1.

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.T., SHEPHERD'S BUSH, LONDON, W.12.

Telephone: SHEPherd's Bush 1729

ALUMINIUM CONTAINERS.—A useful item for storage of small parts, for picnics to hold food, for holidays in which to pack your shaving and tooth brushes, soap, etc. Two sizes available, both with screw-on lids and 2 in. dia. Size "A" is 4 1/2 in. tall. PRICE, 6 for 7-. Size "B" 6 in. tall. PRICE, 6 for 8 6. 3 each "A" and "B", 7.9. or 12 your choice, 12 6.

SMALL ELECTRIC MOTORS.—Size 2 1/2 in. dia. x 4 in. long with 5 1/2 in. dia. spindle providing 1/4 in. Operate from 21 v. D.C. or A.C. or at reduced speed on 12 v. D.C. PRICE, 10 6. or with blower fan attached, 12 6. Postage each type, 1 1/3.

2 MFD. HIGH VOLTAGE CONDENSERS.—Working 5,000 v. D.C. Test 10,000 v. D.C. Overall size 1 1/4 x 9 x 6 in. PRICE 15-, carriage 5-.

A.C. METERS.—Switchboard M.I. Types, 0.39 amps. flush mounting, 3 1/2 in. dia. PRICE, 25-. 0.15 amps projection type, mtg. 4 in. dia. PRICE 25-. Voltmeters, calibrated 90-150 v. flush mtg. 3 1/2 in. dia. PRICE, 17 6.

THIS MONTH'S SPECIAL BARGAIN.—TYPE 6 INDICATOR UNITS.—Less valves, fitted with casted ray tube, type VCR97 (TV picture tested to ensure in good order) with holder, condensers, resistors, pots., extension spindles and couplers and many other useful parts. In good condition. PRICE ONLY 42 6. carriage 6-.

RECORDING TAPE.—Plastic base, by well-known manufacturer. An unrepeatable bargain. Buy now whilst the opportunity exists. 1,000ft. reels, only 18-.

W. B. SUPPLIES

100, OLDHAM ST., MANCHESTER, 4.

Terms. Cash with order. Orders under 20/- add 6d. postage. Orders over 20/- add 1/- postage. Goods dispatched same day.

price quote Ref. No. 7.

HIGH VOLTAGE Rect. Valves: VU120, 2 v. 1.5 a. 5 kv., 4-. E90, 4-; 3 for 10/9. SP81, 3-. EF55, 8 6. 6V6GT, 6 11. 12 v. Voltage Stabiliser, 2-. G.E.C. Germanium Diodes, 1.9 ea.; 2 for 3-.

MAGNETIC HEADS for VCR97, etc. Magni-4, 5/6. **YANLEY TYPE SWITCHES.** 2-pole 6 way (2 Bank), 2.3. 5 K. wire-wound potentiometers, 1-.

STANDARD COAXIAL CABLE 9d. yd.; 3- doz. yds. (Not surplus).

SPEAKER PAPER. Woven Fabric 12 in. x 12 in., 2 6; 12 in. x 18 in., 3 9; Expanded Metal, gold, 12 in. x 12 in., 4 6; 12 in. x 18 in., 6 11.

HIGH VOLTAGE TUBULAR CONDENSERS. .01 mfd. 4 kv., .02 mfd. 5 kv., .03 mfd. 2.5 kv., .05 mfd. 3.5 kv., 2- each.

CHOKES. 20 Hys. 80 mls., 2-. H.F. Chokes, 6d. Bostik, sticks almost anything, 2- tube.

PERMEATING OIL, for removing those rusted nuts and bolts, 2 6 can, with brush.

CAR AERIALS, 5ft., stainless, complete with insulators, 12 6.

MAGNETIC PICKUPS, made for export by well-known maker. Brand New, 28 11.

TV. LOFT AERIALS, adjustable V. Holme Moss or 12 6. Coil Formers, 1 in. with feet, complete with cores, 9d. each, 6 6 dozen, 1 in. Brass cores only, 6d. each.

TELEVISION PICTURE FAULTS. The book everyone should have, contains 150 illustrations, 3/9, post free.

CONTROL UNIT TYPE 4A, with 16 dial lamps, 8 press buttons, with release. Volume control and Send Receive switch, complete with 10ft. 85 core cable, brand new 12 6 plus 2 6 carriage.

RHOFASTS suitable for battery chargers, train sets, etc., complete with knob and pointer, 5-.

SPECIAL OFFER. Midget I.P. Transformers 400 kc.s., manufacturers surplus, cannot be repeated 7 6 pair.

TELEVISION ENGINEER'S POCKET BOOK

Edited by E. MOLLOY & J. P. HAWKER

Reference data and formulae for television engineers, dealers and service men as well as practical information on installing, fault-tracing and alignment. A comprehensive section listing valve complement and other valuable information is included. 10s. 6d. postage 6d.

Television Receiver Servicing: Vol. 1—Time-Base Circuits, by E. A. W. Spreddy, 21s. Postage 9d.

TV Fault Finding: Data Book No. 5, 5s. 0d. Postage 3d.

The Radio Amateur's Handbook: 1954, by "A.R.R.L." 30s. 0d. Postage 1s. 0d.

Television Test Equipment, by E. N. Bradley, 5s. 0d. Postage 3d.

Radio Valve Data, compiled by "Wireless World," 3s. 6d. Postage 3d.

Please write or call for new catalogue.

THE MODERN BOOK CO.,

BRITAIN'S LARGEST STOCKIST OF BRITISH & AMERICAN TECHNICAL BOOKS

19-23 PRAED STREET, LONDON, W.2. (Dept. T.6)

Phone: PADDington 4185. Open all day Saturday.

GUARANTEED NEW BOXED VALVES

Same Day Service

1A7GT 15-	6U4GT	50L6GT	6Z32 15/-
1C5GT 7/9			8 6 HVR2A
1H5CT	6V6G 7/6	80 8 6	KT3C 6/9
1N5CT	12- 6V6GT 7/6	80 7	8 6 KT3C
	6X4	8 6 AC VPI	12/-
	12- 6X5GT 8/6	AZ11	13 6 KT63 7/6
1R5	7/6 7B7	7/6 AZ31	12- M14 8/9
1S4	7/6 7C5	7/6 CY12	12- N78 15/-
1S5	7/6 7C6	7/6 DAC32	PL38 22/6
1T4	7/6 7H7	7/6	12- PL81 11/-
3A4	5/6 757	7/6 DF33	12- PL82 11/-
3Q5GT	7/6 774	6 6 DK15	9- PY80 10/-
	12- 8D3	8 6 DK32	15- PY81 11/-
3S4	7/6 10C1	12 6 DK92	7/6 PY82 9/6
3V4	7/6 10C2	12 6 DL33	12- PZ30 17/-
5U4G	10/6 10F1	10 6 DL35	7 9 R10 10/6
5Y3CT	7 9 10F9	10 6 EAC93	9- R19 13/6
5Z4C	8 6 10LDD1	10 6 EAF42	SP41 4/3
6A7	10/6	10	10 6 U22 7/6
6A8G	9- 10P13	10 6 EB91	6 9 U25 13/6
6AL5	6 9 12AT7	9- EB3C3	7 6 U50 7/6
6AM5	7 9 12AU7	10 6 EB41	7 6 U78 8/9
6AM6	6 9	10 6	10 6 U84 9/-
6AT8	9- 12AX7	9- EPB80	10 6 U80 13/6
6BA6	7 6 12KGT		12 6 UB1 10/-
6BE6	7 6	9- EC91	7 6 UCB4 10/-
6BW3	7 6 12K8GT	10 6 ECCR1	9- UB1 10/-
6BW7	9- 10 6	10 6 ECCR1	10 6 UCB1 10/-
6CH6	8 6 12Q7GT		12- UCH21 12/6
6C4	7 9	9- ECH42	10 6 UCH21 12/6
6F1	10/6 20D1	8 6 ECL80	
6FG	7 6 25A6G		10 6 UCH42 12/6
6F12	6 9	10 6 EF39	7 9 UF41 10/6
6F15	10 6 25L6CT	8 6 EF50	10 6 UF41 10/6
6G6	8 6	8 6 EF80	10 6 UF42 10/6
6J7GT	25Z4G	9- EF90	10 6 UF42 10/6
6KTG	7 6 25Z5	8 6 EF91	6 9 13/6
6K7CT	8- 25Z6CT	EF92	5 6 UL41 9/-
6K8G	9- 27S5	8 6 EN31	11- UY41 9/-
6K8CT	9- 35L6CT	EL41	10 6 U08 17/-
6LD20	9 6	8 6 EL91	7 9 U09 9/-
6P25	15- 35Z4GT	8 6 EY31	11- UY41 9/-
6QCT	9- 35Z5CT	8 6 EY31	12- UY77 5/6
6SN7CT	35Z5CT	8 6 EZ40	9- X66 11/-
	9- 8 6	8 6 EZ41	10- Z77 6 9

Postage 4d. per valve extra. See Special Offer in classified advert, page 45. READERS RADIO 24, Colshire P ace, Stamford Hill, London, N.16.



QUALITY TELEVISION COMPONENTS
 SCANNING COILS
 6/10 kV. R.F., E.H.T. UNITS
 E.H.T. and OUTPUT TRANSFORMERS
 LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

Introducing the:— **TYANA TRIPLE THREE**



Reg. Design No. 867804

MAKE SOLDERING A PLEASURE
SMALL SOLDERING IRON

Complete with detachable BENCH STAND 19/6
 The smallest high-power soldering iron. Length only 8" ; adjustable long bit dia. 3/16" ; mains voltages 100/110, 200/220, 230/250.

The "STANDARD" Popular Soldering Iron now reduced to 14/11.

Replacement Elements and Bits for both types always available.

KENROY LIMITED
 152/297 UPPER ST., ISLINGTON, LONDON, N.1.
 Telephone: Canonbury 4905-4663

TELEVISION COMPONENTS

always in stock for the
P.T. LYNX, TELEKING
P.T. SUPER-VISOR

THE E.E. TELEVISOR
AND VIEWMASTER

Viewmaster wide angle conversion instructions 3/6d. List available.

SOUND MASTER and
CORONET FOUR
 components also in stock

Separate price lists available on request.

J. T. FILMER,
 Maypole Estate, Bexley, Kent
 Tel.: Bexleyheath 7267

IMMEDIATE DELIVERY

RADIO & TV SPARES

Transformers, Timebase Components, Wirewound Controls, Electrolytics, Chokes, Coils, Coil Magnets, Scanning Components, Focus Magnets, Condensers, Resistors, Specified Components for "View Master" and "Sound Master", Tape Recording Accessories, 3-, 5-, 8- and 12-watt Amplifiers, Tone Controls and Radio Feeder Units, Microphones, Quality Loudspeakers, etc., etc.

MONTHLY PRICE SUPPLEMENTS.

SPECIAL.—Miniature Mains Transformers for use in Pre-amps, Tone Controls, etc. Input 230/240 v. Output 0.250 v. at 30 mA. 6.3 v. at 1 A. New and Guaranteed. 14/9, plus 1/- postage and packing.

Solon Miniature Soldering Irons, 19/8. Ronette "Coronation" Microphones, 52/-.

Scotch Boy 1,200 ft. Recording Tape. 35/-.

Lane Bias and Erase Generators (complete), 70/-.

"Quality" Amplifiers, from £10/10/-.

SERVICE & SPEED

CITY & RURAL RADIO

101, HIGH STREET, SWANSEA
 Telephone: 4677

FIRST-CLASS TELEVISION and RADIO COURSES . . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship** (all branches) etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER

150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH
 CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE

(DEPT. B)

72-76 Leather Lane,
 Holborn, E.C.1

Phone: CHAncery 6791/2

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
 SLOane 3463

Works:

36, ROSEBERY AVE., LONDON, E.C.1.
 Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small"

BENTLEY ACOUSTIC CORP. LTD.
 38, Chateauf Road, N.W.1. *PRIMROSE 9080.*

6BA6	7/-	6SN7	8.6	12BE6	7-
6BE6	7/-	6V6	7-	6B41	5.6
6BJ6	7/-	7C5	7/-	6CC33	10-
6BW6	7/-	7C6	7/-	6CC35	9-
6J5G	5/-	7S7	7/-	6CC81	8-
6KTG	5/-	783	5/6	6F39	6-
6K8	8/-	807	7.6	6UB121	13-
6L7	6/-	12AT7	7-	6UCH21	13-
6N7	7/-	12AU7	10-	6VR41	2-
6SL7	7.6	12AX7	7-	6VRL36	5.6

Post extra. 24 hr. C.O.D. Service. Refund Guarantee. S.A.E. Free List.

James H. Martin & Co. for

"VIEWMASTER," "TELEKING," "SOUNDMASTER," "TRUVOX TAPE DESKS," Components, Valves, Cabinets, etc.

Mail Order ONLY, Easy Terms available.

FINSTHWAITE, NEWBY BRIDGE, ULVERSTON. LANCs.

HIGH GRADE TRANSFORMERS

FOR ALL PURPOSES
SINGLY OR IN QUANTITIES
TO YOUR SPECIFICATION

VARNISH IMPREGNATED
 BAKED WINDINGS
 WITH OR WITHOUT TAG PANELS
GOOD DELIVERIES

Our rewind dept. will handle your repairs promptly and efficiently.
 S.A.E. with enquiries please.

P. HOWORTH

(Dept. P.T.)
 51 POLLARD LANE, BRADFORD
 Tel.: 37C30

Line and frame scanning All information required by the home-constructor has been put together in this leaflet. If you are building a new set or converting with an 'ENGLISH ELECTRIC' metal C.R. tube, please let us know and we will gladly send you a copy.



'ENGLISH ELECTRIC' T901A

BRITISH MADE LONG LIFE 16-INCH METAL C.R. TUBE

The tube around which the 'Tele-King', 'Magnaview' and 'Super-Visor' circuits and 'View-Master' conversion circuits were designed.

* The T901A is a suitable replacement for 16in. wide angle metal C.R. tubes used in A.C. and D.C. sets, without modification.

The ENGLISH ELECTRIC Company Ltd. Television Department, Queens House, Kingsway, London, W.C.2.