

BAND III PROBLEMS

PRACTICAL TELEVISION

AND TELEVISION TIMES


A NEWNES PUBLICATION

Vol. 5 No. 54

NOVEMBER, 1954

1/4

EDITOR
F. J. CAMM

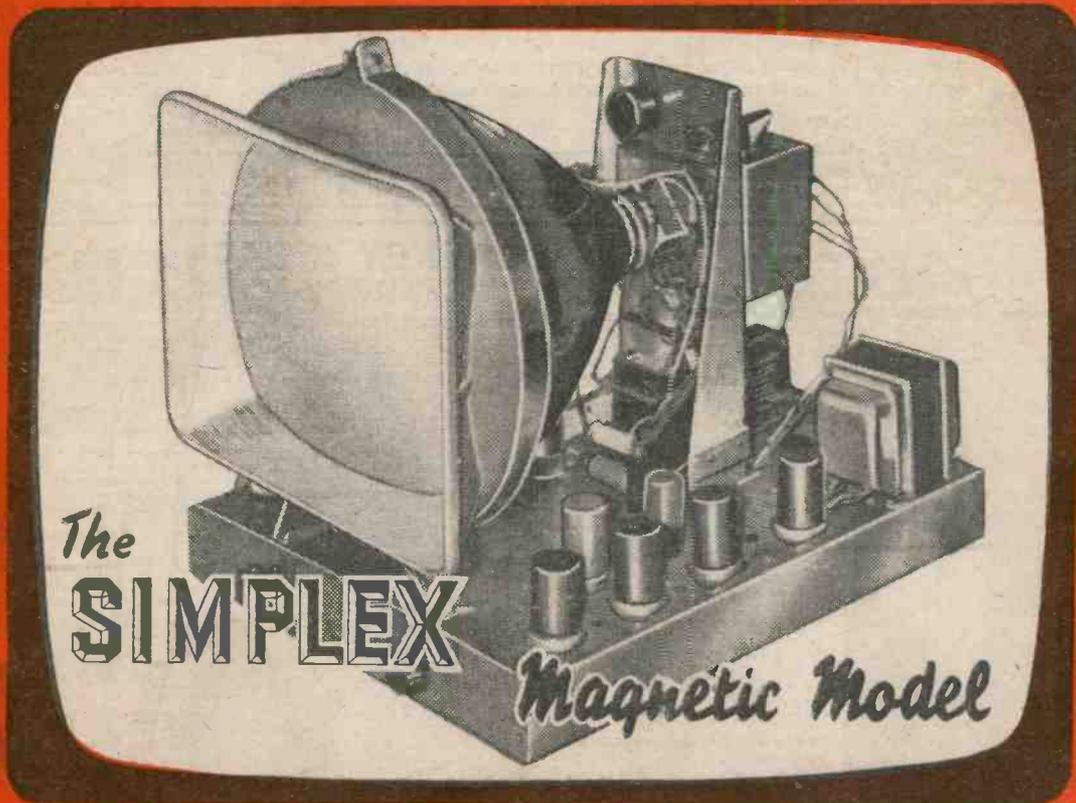

FEATURED IN THIS ISSUE

Ghost Reception
Fault Symptoms
Servicing Receivers

The 931A Cell
A TV Engineer's Notebook
Final Thoughts on the Show

The



ELECTRONIC TESTMETER

This instrument has been developed to meet the growing demand for an instrument of laboratory sensitivity built in a robust and portable form, for use in conjunction with electronic and other apparatus where it is imperative that the instrument should present a negligible loading factor upon the circuit under test.

The instrument consists basically of a balanced bridge voltmeter. It incorporates many unique features and a wide set of ranges so that in operation it is as simple to use as a normal multi-range testmeter.

The instrument gives 56 ranges of readings as follows:—

D.C. VOLTS: 5mV. to 250V. (Input Resistance 11.0 megohms.)
25mV. to 10,000V. (Input Resistance 110.0 megohms.)

D.C. CURRENT: 0.5 μ A. to 1 Amp. (250mV. drop on all ranges.)

A.C. VOLTS: 0.1V. to 2,500V. R.M.S. up to 2 Mc/s. With diode probe external 0.1V. to 250V. R.M.S. Useful measurements can be made up to 200 Mc/s. the applied voltage being limited to 100V. above 50 Mc/s.

A.C. OUTPUT POWER: 5mW to 5 watts in 6 different load resistances from 5 to 5,000 ohms.

DECIBELS: -10db. to +20db.

CAPACITANCE: .0001 μ F. to 50 μ F.

RESISTANCE: 0.2 ohm to 10 megohms.

INSULATION: 0.1 megohm to 1,000 megohms.



£40 Size: 12 $\frac{1}{2}$ ins. x 9 ins. x 5 $\frac{1}{2}$ ins.
Weight: 12 $\frac{1}{2}$ lbs.

The instrument operates on A.C. mains, 100-130V. and 200-260V., 50-60c/s

Write for fully descriptive pamphlet.

The instrument is quickly set up for any of the various tests to be undertaken, a single range selector switch automatically removing from the circuit any voltages and controls which are not required for the test in question.

Sole Proprietors and Manufacturers:


The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.

WINDER HOUSE • DOUGLAS STREET • LONDON • S.W.1 Telephone: VICTORIA 3404/9

E.T.M.3

ADCOLA

(Regd. Trade Mark)

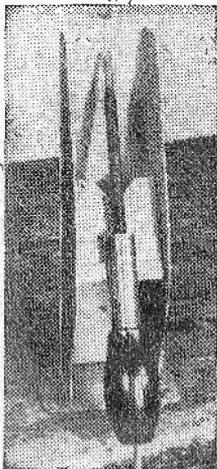

SOLDERING INSTRUMENTS

FOR

SUCCESSFUL HOME CONSTRUCTION AND ALL SOUND EQUIPMENT SOLDER JOINTING

"STANDARD MODEL," as ILLUSTRATED, 25/6

Any volt range supplied, 6/7 to 230/250.

3/16" dia. bit Standard Model

Equally suited to daily or intermittent use

Made in England

Registered Design

(British, U.S.A., Foreign Patents)

Export Enquiries Invited

Shields as illustrated 10/6 extra.

WRITE DIRECT TO

ADCOLA PRODUCTS LTD.

Sales, Offices & Works: CRANMER COURT, CLAPHAM HIGH ST., LONDON, S.W.4. MACaulay 4272

HANNEY of BATH offers:—

ALL COMPONENTS for: OSRAM 812 AMPLIFIER and MULLARD 5 VALVE 10WATT HIGH QUALITY AMPLIFIER

Send for priced parts list.

WILLIAMSON AMPLIFIER. Woden bottled components. Output trans. WOT.25 (1.7 0), 130/-; P1M. 14 a. mains trans., 87/6; PCF.12 150 mA. choke, 44/-; PCF.22 30 H. 20 mA. choke, 30/-; P1M. 23 (mains trans. for pre-amp.), 47/6. Resistor (RK and Condenser kits CK) available, RK, main amplifier, 29/6; RK figs. J3 and 27, 12/6; RK fig. 15, 25/9; RK fig. 19, 36/-; RK fig. 29, 29/6; CK fig. 13, 15/-; CK fig. 15, 47/-; CK fig. 19, 54/6; CK fig. 27, 19/-; CK fig. 29, 54/6. 121% silver micas (fig. 19), 15/-; 75% 7/-; Elstone output trans., 90/-; mains trans., 57/6; 1 OH 150 mA. choke, 20/-; 20 H. 20 mA. choke, 10/-.

FREQUENCY MODULATION. For Wrotham high fidelity transmissions. Denco technical bulletin giving circuit and point to point wiring diagram for building an F.M. Feeder unit, 1/6. We have all components available. Priced parts list on application. W.B. STENFORIAN. High fidelity Speakers. HF610, 50/6; HF610, 60/6; HF612, 67/-; HF612 (3 or 15 Ω), 73/6; ACOS Hi-Fi. Pick-ups. HGP 20-1 std., or LP, 65/8. Heads only, std. or LP, 42/3.

COILPACKS. Denco, CP 4/L and CP 4/M, 33/4; CP 3/370 pf. and CP 3/500 pf., 42/8. OSMOR "Q" HO, 48/-; LM, 40/-; Batt., 50/-; TRF, 40/-; HF stage for HO pack, 20/-; ETA 4-station pack, 43/8. We stock COILS by Weymouth, Osamor, Wearite, Denco, Teletron and R.E.P.

VIEWMASTER. WIDE ANGLE VIEWMASTER CONVERTER. Complete set of parts for converting existing Viewmaster to W.A., less valves, tube and mask, 114/18/6. W.A. Conversion instructions, 3/6; WB113, 49/6; WB114, 123/6; WB115, 42/-; WB116 and WB117, 7/6 each; WB118, 22/6; WB119, 26/9; WB121, 3/6; WB124, 10/6; Westinghouse 36/EHT/130, 17/-; Plus condensers and resistors as per our general list.

MULLARD. UNIVERSAL. LARGE SCREEN A.C./D.C. TELEVISOR. Denco drilled chassis with all mechanical parts, 53/8; ED12/4, duomax focaliser, 37/6; 14A/342, rectifiers, 37/2; Goldsman droppers DK37/6, 8/9; DK35/6, 7/6; VA1008 varrite res., 4/6. Other Denco parts, please see below.

WIDE ANGLE COMPONENTS. ALLEN. Teleting Chassis, 50/-; Coilssets (FK and Super-Visor), 42/6; LO 308, 40/-; FO 305, 32/-; DC 302, 30/6; TCC 301, 31/-; GE 19 and 18, 7/6 each; SC 312, 21/-; AT 310, 30/-; OP 117, 9/-; BT 314, 15/-; Denco Chassis Magnaview, 37/6; Chassis, Super-Visor, 51/8; Coilssets, Magnaview, 41/2; WA/DCAL, 43/-; WA/FCA, 31/-; WA/LCI and WCI, 7/6 each; WA/MA, 31/4; WA/LOTI, 42/-; WA/FBTI, 15/-.

Send 6d. stamps for our General List of components for Viewmaster, Viewmaster, Williamson Amplifier, Teleting, Magnaview (Brimar and English Electric large screen TV), Super-Visor, Mullard Universal, Glass tolerance, Silver Micas, etc., etc. Please add 1/- postage to orders under 42.

L. F. HANNEY, 77 Lower Bristol Road, Bath. Tel: 3911

HENRY'S

(RADIO LTD.)

We have over 20,000 American and B.V.A. valves in stock.
ALL VALVES NEW AND GUARANTEED.

1R5	7/6	6U5	7/6	3SL6GT	8/6	EF90	10/8	VR150/30	8/6
1S4	7/6	6UGG	7/6	30L6GT	8/6	ECL80	10/6	CR510AX	5/-
1S5	7/6	6N7GT	7/6	42	8/6	PCC81	12/8	DI	2/6
1T4	7/6	6Q7GT	8/6	43	8/6	PCF82	12/6	AC8PEN	6/6
1C5	8/-	6S7GT	8/6	75	8/6	UY41	9/-	PEN25	2/6
3A4	9/-	6X5G	8/6	80	8/6	4D1	4/-	PEN46	7/6
3V4	7/6	6S4GT	8/6	868A	15/-	3D2	4/-	QP25	6/6
3S4	7/6	6S2GT	8/6	T240	37/6	9D2	4/-	SP81	4/-
5Z3G	8/6	6S6GT	7/6	931A	50/-	D41	5/-	SP41	4/-
5U4G	8/6	6SK7GT	7/6	EA50	2/-	KT2	5/-	HL23/DD	6/6
5Z4G	8/6	6SL7GT	9/-	ECH35	12/-	U52	6/6	VP23	6/6
6A7G	8/6	6S7GT	9/-	EF54	6/-	U19	10/-	VP41	7/6
6A7	6/6	6S7GT	9/-	EB34	3/6	Y83	8/6	U22	8/6
6A8C	8/6	6V8GT	7/6	EBC33	8/6	MU14	8/6	ATP4	4/-
6AM6	9/-	6AG7	12/6	EF36	6/6	PL81	11/-	TP22	8/6
6B8	7/6	12A6	7/6	EF39	6/6	PL82	10/-	TR23	10/-
6C5GT	5/-	12K7GT	8/6	EY51	12/-	PX25	12/6	41MP	7/6
6C6	6/6	12K8GT	8/6	EK32	6/6	PY31	10/-	42SPT	6/-
6D6	6/6	12Q7GT	8/6	EP61	9/-	PY32	8/6	21SSG	4/-
6F6G	8/6	12S4GT	8/6	EL33	10/-	KT33C	10/-	MS/PEN	7/6
6G6G	6/6	12S7GT	8/6	EL32	7/6	KT66	12/6	MS/PENB	6/6
6H6GT	5/-	12S7	8/6	EP50	10/-	GU50	12/6		7/6
6J5GT	5/-	12SK7	8/6	Red Svl.	10/-	XP25	4/-	VT501	7/6
6J8	9/-	12SR7	7/6	EP50	5/-	XH(1.5)	4/-	AC/PENCT	7/6
6AK5	9/-	25Z6GT	8/6	SP2	8/6	VU11	4/-	or 5-pin	10/-
6J7G	6/6	25Z5	8/6	VP2	8/6	VU133	4/-	PENDD4020	10/-
6K7G	6/6	3S24GT	8/6	TDD2A	8/6	VU120A	4/-		12/6
6K8G	9/-	3S25GT	8/6	DK40	9/-	QP230	8/-	FC13C	10/8
6L6G	10/-	25A6	8/6	UL41	9/-	VR105/30	8/6	VP4(7)	8/6

INDICATOR UNIT TYPE 182A

This unit contains VCR517 Cathode Ray 8in. tube, complete with Mu-metal screen, 3 EF50, 4 SP81 and 15U4G valves, W/W volume controls, resistors and condensers. Suitable either for basis of T/V or Oscilloscope. "Radio Constructor" Scope constructional circuit included. 67/6 (plus 7/6 carr.).

CATHODE RAY TUBES

(Brand New)
VCR97 (slight cut-off) 15/-
VCR97, guaranteed full TV Picture ... 40/-
VCR517C, guaranteed full TV Picture ... 35/-
VCR139A, guaranteed full TV Picture ... 35/-
3BT1, guaranteed full TV Picture ... 30/-
Carr. & packing on all tubes, 2/-.

DENCO F.M. FEEDER UNIT

Finest Audio available. Complete kit of parts, including drilled chassis. 5 valves - types 6AM6, 12AH6, E191 and 2 6AB6. Also complete circuit and wiring diagram. 68/7/6. Or assembled and aligned, 68/10/-. Alignment only, 10/-.

SETS OF VALVES

Ten EF50 (Ex-Brand New Units), 5/- each ... 45/- Set

6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G ... 37/6 ..

1R5, 1S5, 1T4, 1S4, or (3S4 or 3V4) ... 27/6 ..

TP25, HL23/DD, VP23, PEN25 (or QP25) ... 25/- ..

6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 or 25Z6G ... 37/6 ..

12K8GT, 12K7GT, 12Q7GT, 3S24GT, 35L6GT or 50L6GT 37/6 ..

12A7GT, 12SK7GT, 12S7GT, 3S24GT, 35L6GT or 50L6GT 37/6 ..

CRYSTAL MICROPHONE INSERTS



Ideal for tape recording and amplifiers. No matching transformer required.

Brand New R.F. UNITS

RF24 20-30 mc/s 15/- post free

RF25 40-50 mc/s 19/6 post free

RF26 50-65 mc/s 35/- post free

RF27 60-80 mc/s 35/- post free

MORSE PRACTICE BUZZER

Complete with tapper and 4 volt buzzer on baseboard. 6/-, brand new. Post paid.

R.F. OSCILLATOR COIL UNIT

6-18 kv., including EY51 valve. 37/-.

CRYSTALS

200 kc/s, 2-pin (U.S.A.) ... 10/-
465 kc/s, 2 pin (U.S.A.) ... 10/-
500 kc/s, 2-pin (British) ... 15/-

T.C.C. 1 57,000 v. wkr.

Type CP58Q0. Bakelite Case. 7/6 each.

28-page Catalogue, 3d. Open Mon.-Sat. 9-6. Thurs. 1 p.m.

5, HARROW ROAD, PADDINGTON, LONDON, W.2 TEL: PADDINGTON 1008/9, 0401.

Positively the 2 BEST T/Vs yet built for the Home Constructor!

The STERN'S "TELE-VIEWERS"


5 CHANNEL SUPERHET RECEIVERS

Suitable for any transmitting channel and for which commercial adaptors will be available.

- PERFECT PICTURE QUALITY
- SIMPLE DIAGRAMS MAKE CONSTRUCTION EASY
- PERFECT FRINGE AREA RECEPTION
- BETTER RECEPTION AT HALF COMMERCIAL COST


The "WIDE-ANGLE" TELE-VIEWER

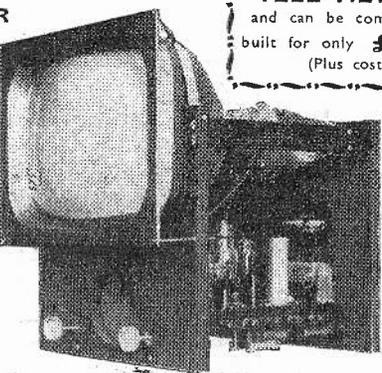- This is the most efficient large screen TV yet offered to constructors.
- Excellent Time Base efficiency producing 15 to 16 Kv with ample scanning power for C.R.T.'s up to 17 inch.



CAN BE COMPLETELY BUILT FOR
£33 - 0 - 0
(Plus cost of C.R.T.)

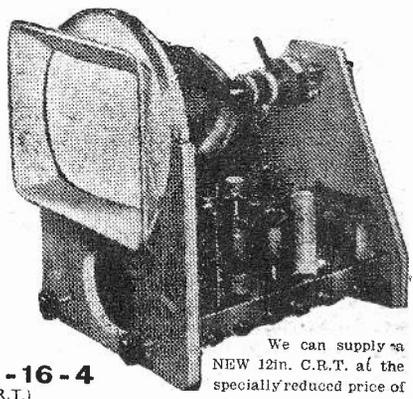This is the 12" TELE-VIEWER and can be completely built for only **£28 - 16 - 4** (Plus cost of C.R.T.)



We can supply a NEW 12in. C.R.T. at the specially reduced price of £12.19.6. (Carr. & Ins., 15/- extra.)

The complete set of ASSEMBLY INSTRUCTIONS for these T/Vs are available for 5/- each. They include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. AN ATTRACTIVE TABLE MODEL CABINET FOR THE 12in. Model IS AVAILABLE FOR £6.19.6.

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4.
Tel.: CENTRAL 5812-3-4.


Your set deserves a Mullard

LONG=LIFE TV TUBE

If you are building a television receiver, leave nothing to chance: choose a Mullard Tube. Mullard Television Tubes owe their high reputation for performance, reliability and LONG LIFE to the unrivalled facilities for research possessed by Mullard and to the complete control of manufacture from the production of raw materials to the finished product. For practical evidence of performance and reliability, ask the people who use them.

MULLARD LONG LIFE TUBES FOR HOME CONSTRUCTORS

- MW22-16 9 inch circular screen.
- MW31-74 12 inch circular grey-glass screen.
- MW36-24 14 inch rectangular grey-glass screen.
- MW41-1 16 inch circular screen. Metal cone.
- MW43-64 17 inch rectangular grey-glass screen.

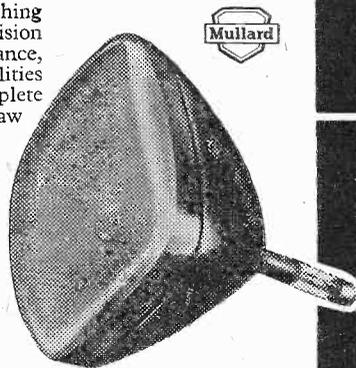

MW43-64



MW22-16



MW31-74



MW36-24



MW41-1


MULLARD LTD · CENTURY HOUSE · SHAFTESBURY AVENUE · LONDON W.C.2

MVM290

For super tropical service 'METALPACK' PAPER CONDENSERS

This range has been developed for operation in high humidities and high temperatures. Their ability to withstand variations from -40°C . to $+100^{\circ}\text{C}$. makes them the obvious choice for the most stringent conditions. Internal construction follows the well-proved T.C.C. technique of winding non-inductively two or more layers of paper dielectric to each layer of solid aluminium foil, all impregnated under vacuum, and finally hermetically sealed in aluminium tubes.

Cap. μF	Wkg. Volts D.C.		Dimns. inches		Type No.	List Price Each
	At 70°C .	At 100°C .	L	D		
.005	1,000	750	$1\frac{1}{2}$.375	CP45W	1/10
.01	1,000	750	$1\frac{1}{2}$		CP45W	1/10
.02	750	600	$1\frac{1}{2}$		CP45U	1/10
.05	500	350	$1\frac{1}{2}$		CP45S	2/1
.1	500	350	2		CP46S	2/2
.1	1,000	600	$2\frac{1}{4}$		CP47W	2/6
.25	350	200	2		CP48N	2/8
.5	350	200	$2\frac{1}{4}$		CP47N	3/-
.5	500	350	$2\frac{1}{4}$		CP91S	3/10
1.0	350	200	$2\frac{1}{4}$		CP91N	4/-

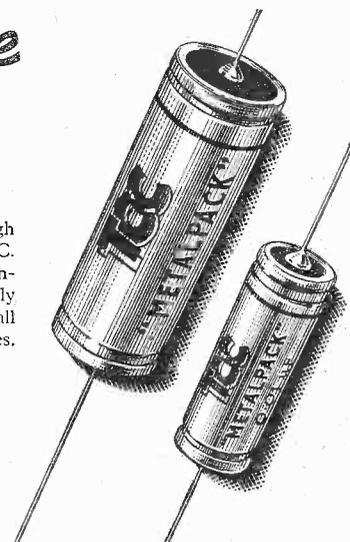


DETAILS OF COMPLETE RANGES AVAILABLE ON REQUEST



THE TELEGRAPH CONDENSER CO. LTD

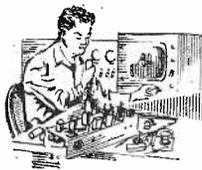RADIO DIVISION: NORTH ACTON · LONDON · W.3 · Telephone: ACOrrn 0061



Practical Television



& TELEVISION TIMES

Editor : F. J. CAMM

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. 'Phone: Temple Bar 4383. Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 5 No. 54

EVERY MONTH

NOVEMBER, 1954

TelevIEWS

TUBE SIZE

TH**E**RE is one feature of receiver specification which is causing great confusion in the public mind. It is the manufacturers' method of designating tube size. We will give a case in point, but it is typical of all makers. The manufacturer's catalogue deals with a 17in. rectangular face tube. An examination of a scale drawing of the tube shows that the overall dimensions are 15.375in. and 10.75in. respectively, the screen diagonal being 15.375in. Screen sizes are now given in relation to the *diagonal*. Why? It is utterly misleading and gives the public the impression that it is obtaining a larger tube than is actually the case. In any case, in the example which we have quoted *no dimension equals 17in.* We suggest that the B.V.A. rationalises tube size nomenclature, and stipulates that its members advertise their tubes according to their rectangular width and depth. To designate a tube according to its diagonal, especially when even that figure is incorrect, is ridiculous and cannot be supported on any logical grounds.

COMMERCIAL TELEVISION

IN view of the confusion in the minds of some members of the public, caused by various statements regarding modifications to sets necessary to receive commercial TV, the Radio and Television Retailers' Association state that the simple position is that the sets intended to receive additional programmes will need to have additional components included. This means additional cost whether the set is manufactured to include the additional part or whether the additional components are supplied in the form of an adaptor for fixing to existing sets.

It is important to remember that commercial TV will only cover a small part of the country during the first few years of its existence, and those about to purchase a receiver should enquire whether they are within the TV commercial service area and if not how soon it will be before they are. If it is likely to be some years they may

save themselves some money by purchasing a receiver not adapted to receive the additional programme. A nation-wide commercial TV coverage will not occur for several years, and even in London where the first commercial TV station is to be put into operation, it must not be assumed that the range of the station will be that of the BBC. It will probably be less.

The association adds that "Whilst this Association supports competitive television, and feels the public will wish to have alternative programmes when possible, it is of the opinion that it is not fair to the public upon whom the industry depends, to sell only sets which will receive commercial stations, because to do so would, in very many cases, be compelling the public to buy sets only part of which would be usable. It is, therefore, stressed that the public will be at no disadvantage by buying sets which can be altered if and when required."

THE DETECTOR CAR

ACCORDING to a statement from the General Post Office, results of the efforts of nine new television detector cars, seeking persons operating sets without a licence, have been "astonishing." In the first four days, 522 television licences and 388 sound licences were taken out and 371 sound licences were exchanged for television, a total of 1,281 against a normal week of 60. The presence of these cars should have a stimulating effect in Birmingham, where the number of wireless licences bought in the first week was doubled, and Brighton, Reading, Hastings and Luton reported an increase of 100 per cent.

The North-East region reported that licences taken out in three days exceeded those taken out during three days the previous week at Newcastle upon Tyne by 240, at Leeds by 259, at Sheffield by 86, and at Middlesbrough by 261. The South-Western region reported that in seven towns 200 licences more than usual were issued during the week.—F. J. C.

BAND III PROBLEMS

A DISCUSSION OF SOME OF THE DIFFICULTIES LIKELY TO BE ENCOUNTERED

By A. Thompson

WHEN we come to consider the requirements for the R.F. stages in TV receivers for the proposed Band III frequencies, it is essential that a low-noise factor and a high gain are obtainable. In Band III, which covers frequencies from 174 to 216 Mc/s, two channels 8 and 9 have been made available between 186 and 208 Mc/s.

Very little noise is contributed by the aerial circuits at these frequencies. The main noise contribution is supplied by the first valve, and it is to this circuit that we must pay particular attention.

In R.F. circuits for Band I (40 to 68 Mc/s) we use an R.F. pentode, but the use of a pentode in Band III will give a rather high noise level due to partition effect, that is, the noise caused by the random division of the electron stream between the screen grid and the anode. Valve noise is, therefore, a very important factor in the first stages of a V.H.F. receiver. The signal voltages in this stage, which are not as yet amplified, have come direct from the aerial system and are, therefore, of magnitudes comparable with the noise voltages. Therefore, it can be seen that any noise introduced in the first stage will be amplified by the following stages. It is essential that noise be kept to a minimum in these first stages.

As all radio experimenters know it is impossible to eliminate noise altogether, even a standard resistor introducing noise owing to thermal vibration of its electrons. (This is one of the reasons we use high-stability resistors in high-gain amplifiers such as for magnetic tape recorders, etc.)

A valve has a heated cathode which emits electrons. These electrons arrive at the grid and anode in a more or less random fashion and not as a continuous stream. The arrival of these electrons at the anode causes a current to flow. The anode current is referred to as a steady current but this really means an average current. So, in effect, each electron arrives individually at the grid or anode. We can almost liken it to pebbles being tipped from a cart, they don't fall to the ground as one, they fall individually.

The noise which is created by these electrons has no definite frequency, as the electrons arrive completely in random fashion and, therefore, their noise extends practically over all frequencies. A wide-band receiver such as a TV set is inherently more noisy than one having narrow band working. "Shot effect" is the term applied to this type of noise and it is rather fortunate that it is masked by the space charge, which forms a cloud around the cathode, this space charge acting as a sort of electron reservoir and buffer. This type of noise is always present and it is the noise that is left after all other sources of noise have been eliminated. There is no known remedy for this type.

When we were discussing the pentode we referred to "parti-

tion noise," and this is one type of noise which we can take steps to reduce. This is done mainly by mutual alignment of the grids, particularly, the control and screen grid; thus the electron stream, is directed through the spaces between the grid wires, and it is only the stray electrons which ever reach the screen grid

R.F. pentodes specially designed for use in the first stages of TV receivers, such as the EF80 and the EF95, made it possible to obtain a high gain coupled with stability. Therefore, the use of these pentodes for Band I receivers was ideal, but the pentode set a limit to the sensitivity of the receiver.

As we are bringing more services into the V.H.F. bands, and this is the TV expansion area also FM broadcasting, we must use techniques which are suited to these V.H.F. bands. Components for use in the R.F. and frequency changer stages have to be specially designed, capacitors and inductors must possess as little as possible of the properties of each other. In the end, it is the valve which is the limiting factor. In Band I many problems were created but they were overcome, and a great deal of the credit must go to the valve manufacturers who gave us specialised valves. Now we go to Band III for TV, and meet frequencies in the region of 200 Mc/s and a totally different set of conditions regarding the design of the R.F. stages, but once again the valve manufacturers have given us specialised valves for the job, such as the Mullard PCC84 and PCF82.

Triodes

A much lower noise level can be obtained by using a triode valve, but due to internal feedback that takes

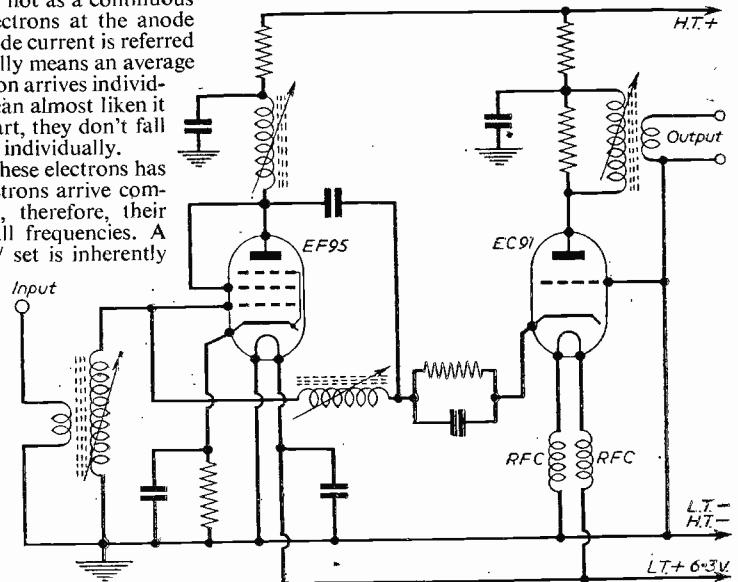


Fig. 1.—A Low-noise Cascode pre-amplifier.

place via the anode to grid capacitance of the valve, the gain of the stage is seriously reduced. Therefore, we must depart from the conventional triode circuit and look for other types of circuit in which we can take full advantage of the triode valve.

In V.H.F. work a circuit often employed uses the grounded grid technique, and this type of circuit operates most efficiently to high up in the frequency spectrum. An example of earthed grid circuitry is shown in Figs. 1 and 2. It is also being used a great deal for FM broadcast receiver design as it allows an efficient R.F. stage with a low noise level. By earthing the grid and allowing the cathode potential to vary according to the input signal we have in effect a screen between cathode and anode. From this it will be gathered that the capacitance between anode and cathode is very small, but what is more important is that the anode voltage is in phase with the cathode voltage, so that such "Miller effect" as exists tends to reduce the input capacitance rather than to increase it. It is this fact, and also the inherent possibility of reducing transit time effects in a triode much more than in a pentode, that makes the earthed grid triode an amplifier of great use in V.H.F. work. The valve manufacturers have given us special triodes for use in earthed grid circuits and this valve is shown in Fig. 1 where it is used in a low noise pre-amplifier for TV work. The latest valve for this type of work is the PCC84, which is shown in Fig. 2 in the R.F. stages of a multi-band TV receiver. The PCC84 has a high mutual conductance, very thorough internal screening between triodes, low inter-electrode capacities, etc., and designers of V.H.F. equipment have not been lacking in employing these valves for Band III TV receivers. Another valve worthy of note here is the ECC85 and the 12AT7 which are being used extensively as earthed grid R.F. amplifiers in the FM broadcast receivers.

Cascode

Fig. 1 shows a type of circuit that has been developed over the past few years and is known as the "Cascode" amplifier. This type of amplifier has been used extensively on Band I television, and also on 144 Mc/s by our colleagues in the amateur radio field. The EF95 is strapped as a neutralised triode, and the EC91 as a grounded grid amplifier. This type of circuit has the advantage of a low noise level and a high gain, thus giving the low noise level of a triode with the high gain and stability of a pentode.

Fig. 2 shows a cascode amplifier as developed for Band III TV receivers. It will be noted that the H.T. voltage is applied across the two sections in series, therefore each triode is running at half the total H.T. supply voltage. The average H.T. rail in the modern TV receiver is approximately 180 volts which means that only 90 volts is applied to each anode. However, despite this low anode voltage which is the result of series working, the mutual conductance of each triode is 6.0 ma/V (with a grid voltage of -1.5 volts). It will be seen from this circuit that the first triode in the D.C. series connected cascode circuit is a neutralised grounded cathode amplifier. The second triode is a grounded grid amplifier with the grid earthed capacitively by means of a lead-through capacitor. It can be shown that the noise factor of this arrangement is virtually that of the first triode alone, the noise contribution of the second triode being negligible.

It should always be remembered when constructing or designing the R.F. stages of a V.H.F. receiver,

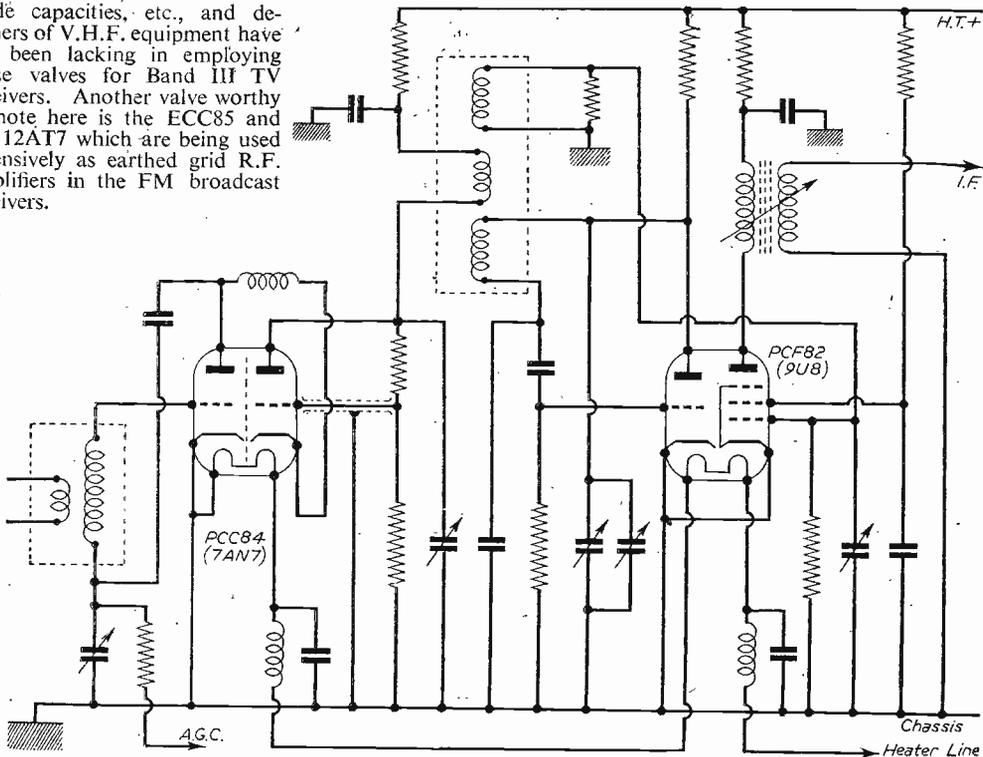


Fig. 2.—The cascode circuit as used in the latest KB receivers.

whether it be for TV or FM, that one must take into account the invisible factors or components which are formed by the stray capacities, the self-capacity and inductances of coils and condensers. The physical layout, lengths of wiring, placement of components, etc., all affect performance. It is therefore essential that once a layout has been found that is stable it should not be altered. This is evident in some of the latest 12-channel TV receivers employing rotary turrets. The final adjustment of alignment for each channel is done by altering the end turns of the coils and if these are mishandled it follows that the set will be put out of alignment on that channel.

Frequency Changer

Another valve which has been developed for specific use in the front ends of multi-channel TV receivers is the Mullard PCF82 and the circuit employed for frequency changer is shown in Fig. 2. The triode section of the PCF82 is employed as the local oscillator working in a Colpitts circuit. It will be noted that the triode and pentode sections are not internally connected in any way. It is recommended that inductive coupling be employed for the injection of the local oscillator; however, many manufacturers seem to favour capacitive coupling and both methods appear to function very well. When capacitive coupling is employed it is necessary to arrange alternative capacitors for different frequency bands. There is a danger with capacitive coupling that a value of capacitance may be chosen to give optimum drive at a low frequency, and when the set is tuned to a higher frequency there may be serious overdrive. On the other hand, in inductive coupling which is employed in practically all turret-type tuners, each coupling coil is adjusted to give the best value of mixer drive on each frequency band, also making the whole of the oscillator coil available for the induction of an oscillator voltage into the grid circuit.

One of the greatest factors in any V.H.F. receiver is the stability of the oscillator circuits and from this point of view the PCF82 is very stable when used under the recommended operating conditions. Most of the local oscillator circuits in the multi-band TV receivers make use of negative temperature coefficient condensers, and it is essential that should these condensers require replacement during servicing that they are replaced with exact types.

As only channels 8 and 9 have so far been allocated for alternative TV programmes, most of the turret type tuners are fitted with coils for these channels. When other channels are announced, coils for fitting to these tuners will be made available by the respective manufacturers. The local oscillator coil is fitted with a brass slug and this enables the oscillator to be tuned. Also, in most cases, a trimmer is fitted for fine tuning of the oscillator circuit. The turret is well screened and access to these slugs is usually via a hole in the front of the turret. Once again it must be stressed that the spacing between turns on the coils must not be altered, as this will affect the alignment of the receiver.

Intermediate Frequency

It appears that most manufacturers seem to favour an I.F. of 35 Mc/s for vision and 38.5 Mc/s for sound. The number of I.F. stages has been increased in many instances to three and practically all sets have some form of A.G.C. or picture control. For

sets used within the service areas of a powerful transmitter this A.G.C. takes the form of a sampling of average picture brightness. In the special fringe area versions, a more elaborate system using gated controls is employed.

A greater signal strength will, of course, be required for Band III than is required on Band I. If a Band I receiver has a sensitivity of, say, 20 micro-volts for vision and 15 micro-volts for sound, then when used on Band III with the same I.F. stages, etc., the sensitivity will now be approx. 60 micro-volts for vision and 45 micro-volts for sound. Studying these sensitivity figures it will be seen that we require three times the signal strength for Band III as we do for Band I, and therefore we must pay due care and attention to the aerial system. Where at present we are using two and three element arrays for the alternative programmes we may have to use four, five or six element arrays; also, as the overall size will be smaller than Band I aerials, it is likely that a great many stacked arrays will be seen in the fringe areas. A good many examples of Band III aerials were shown at the National Radio Show ranging from multi Yagi types to a slot aerial.

As there are something like three million TV receivers in use that are not fitted for receiving Band III transmissions, it is not surprising that a great many inquiries are coming in as to what can be done to make these sets suitable for the new transmissions in Band III. Most of the manufacturers are catering for their own models and it seems that most sets will be catered for in this respect. Where we have a "single channel only" set, it seems that the easiest plan is to make a converter that will use the channel of the set as an I.F. The trouble with this method is that we have two oscillators and they set up patterning. Also, it is possible that the station on one channel will also break through and cause further trouble from pattern effects. It seems that the only real satisfactory answer is to make a complete tuner unit incorporating Band I and Band III and feed this straight into the receiver I.F. stages. By using this method we can get away from the patterning effect and all the complication of having two oscillators functioning at once.

Many manufacturers are supplying these tuner units now for adding to present sets when a station opens near the viewer, and the cost of these units appears to be approximately 6 guineas.

JOIN THE PRACTICAL GROUP

Edited by F. J. CAMM

PRACTICAL WIRELESS	1/-
Every Month.	
PRACTICAL MECHANICS	1/-
Every Month.	
Devoted to Mechanics, Science and Invention.	
PRACTICAL ENGINEERING	6d.
Every Friday.	
For Engineers, Mechanics, Designers and Works Managers.	
PRACTICAL MOTORIST & MOTOR CYCLIST	1/-
Every Month.	



NEW SERIES

Servicing TELEVISION RECEIVERS

No. 3.—BUSH MODELS TV22 AND T24

By L. Lawry-Johns

and E.H.T. with it, suspended safely away from any near-by chassis member.

The faults mentioned are due to overloading of the timebase, not to its non-operation, which may be caused by a leaky coupling condenser to the control grid of the line output valve, an open circuited resistor in series with the line hold control or failure of the valve itself.

Variable Gain

A frequent fault is variations in the gain of both sound and vision, and this is usually due to the 50 μ F, 25 volt electrolytic condenser which is across the contrast control. It is a metal-cased type, and no difficulty should be found in locating it. A small drop in its efficiency causes large variations of gain. Another fault encountered several times on this model is a defective 100 pF coupling condenser on to the grid of V2 the mixer EF91. Depending upon the extent of the leak the symptoms may vary from a ragged picture with a small leak, to "snow storm" effects as the leak gets worse. When the condenser shorts out completely the picture vanishes with the mixer ceasing to operate. The position in the circuit is shown in the diagram and is marked with a star.

Other Models

Some variation may be found in these notes and in the circuit diagrams as they are designed to encompass the TV22a, TV24a and the console variants. Most variation will be found in the line timebase and the types of valve fitted, e.g. PL81 for PL38, etc., but there is little variation in the actual circuit of the supply and sound/vision strips.

A hum on these sets has often been traced to a loose 4 B.A. nut and bolt on the rear of the chassis. This holds the earthing clip of the audio output stage and also the tag to which the main fuse is earthed.

THESE are very reliable receivers but nevertheless still have their "usual" faults, fortunately comparatively few in number. The first is undoubtedly the PZ30; this is located in the screening box on the "top deck" chassis right-hand side.


The first thing to remember is that this valve is not only used as the H.T. rectifier, but one half is used as a booster diode; hence a defective valve can give some rather misleading symptoms. Those possessing a receiver of this type are advised to keep a spare PZ30. If, after the failure of one of these valves and when a new one has been fitted, a slight hum is present on sound, especially in the "minimum" position, and there is evidence of frame non-linearity, the 38 ohm resistor, in series with the reservoir capacitor, should be examined. The reason for this is, in the event of an internal short in the PZ30, A.C. is present on this capacitor, causing a heavy flow of current through it, thus burning out the series resistor.

When the "going off" of one of these sets is accompanied by a trace of smoke, or by a smell of burning, this is what has happened, and a new PZ30 and a new resistor will normally be the "size" of the repair.

The diagram will show clearly the position of this resistor in the circuit.

Line Output Transformer

The line output transformer is another source of likely trouble. However, failure of the line timebase is not the signal for a new transformer to be fitted. A defective PZ30 could also cause it, and the following points should also be suspected. A leaky C20 470 pF condenser (linearity correcting) wired across the T4 transformer (see diagram) will result in (a) no raster, (b) very small spark at anode of the EY51 (the valve not lighting up at all) and very weak line whistle. An internal short in the EY51 or an internal short (may be intermittent) in the tube. To check the tube remove the E.H.T. cap from the tube anode and check the operation of the timebase

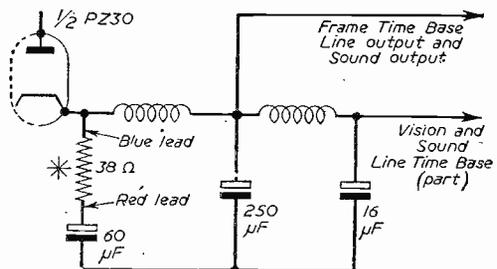

* This resistor is mounted on the end of a paxolin panel on the left side of the upper chassis.

Fig. 1.—Showing how the series resistor and the 60 μ F condenser are wired direct to the PZ30 cathode.

It is situated just under the fuse-holder and should be inspected for tightness should hum be present. The first time this fault came in, it caused some heartaches and shows how the most baffling problems have the most simple answers sometimes.

If, after having repaired some fault on the receiver, and upon switching on no picture or a very weak

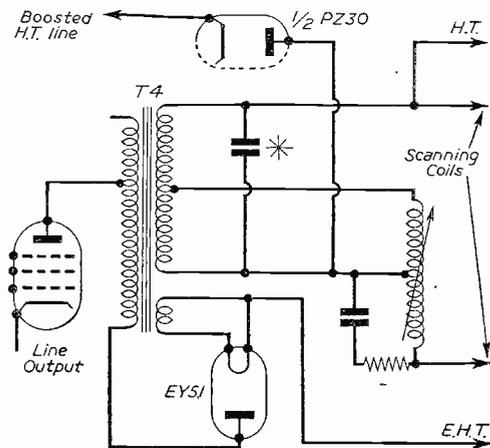


Fig. 2.—The condenser marked * is 470pF and is C20 referred to in the article.

raster is obtained, or the tube shows every sign of having lost its emission, remember the ion trap. The way these little items can work loose or be accidentally moved and cause momentary confusion is remarkable. Once again look for the simple things.

Advances in Colour TV

THREE new major developments in colour television were recently demonstrated by the Radio Corporation of America, opening the way to early mass production of colour television sets at costs within the reach of the consuming public.

Described as milestones in the march toward commercial colour television, the three new developments were:—

1. A new 21in. R.C.A. colour picture tube with 250 square inches of viewing area—22 per cent. more than any other colour tube yet produced.

2. A magnetic field equaliser called the "Colour Equaliser." This is a significant new R.C.A. invention—not previously announced—which guarantees improved colour set performance and makes possible a reduction in manufacturing costs.

3. A new simplified colour television receiver, which reduces circuitry by one-third and enables a substantial reduction in production costs to be effected.

Each of these developments represents "years of scientific and engineering endeavour telescoped into a memorable few months," according to E. C. Anderson, Executive Vice-President, R.C.A. Commercial Department.

R.C.A. Timetable for Production of Tubes and Sets

"The R.C.A. timetable," Mr. Anderson continued, "calls for industry sampling of the 21in. colour tube starting on November 1st, and for the

Further Notes on the HMV 1807 and Pye B18T

If the tube face of the HMV or Marconi receivers, dealt with in the first article in this series, shows hum bars, i.e. no picture with wide dark and light bands, the trouble can usually be located in the D77 video detector valve. This is the last in the vision strip and is located at the rear of the chassis in the most accessible position. The valve will probably have a heater-to-cathode leak or short-circuit and should be replaced.

If on the Pye a rather more "contrasty" picture, accompanied by intermittent or complete loss of sync is experienced, the trouble will almost certainly be the 12 μ F video anode decoupling condenser having

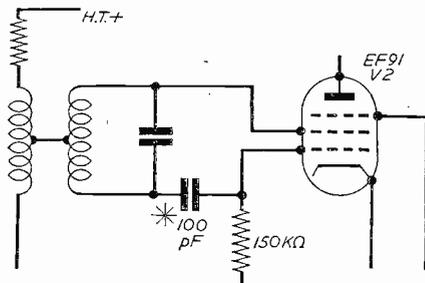


Fig. 3.—Frequency changer V2. This diagram shows how a leak in the 100 pF condenser can cause the symptoms described.

gone O.C. This is located under the chassis at the rear. It is connected to the junction of two 1 watt resistors and is of the white cardboard covered type. Usually the frame sync is affected most, the line may only "zip" occasionally.

appearance in the market of our first 21in. colour sets before the end of this year, with production in quantity by early 1955.

"While we have not yet established a suggested retail price for our 21in. colour set, I can tell you to-day that it will be between \$800 and \$900."

At a special Press showing, which preceded demonstrations for representatives of virtually the entire television manufacturing industry, Mr. Anderson said, "When R.C.A. first tackled colour television, we were aware of the importance of creating an entire system, not just isolated elements of one. . . ."

The 21in. Colour Tube

"The 21in. tube, which holds the spotlight to-day, was only eight short months ago in our development laboratories. But the progress we had made with it was so good that we determined not to go ahead with our 19in. tube. We concentrated our efforts on a 21in. colour tube—the preferred size—without introducing any intermediate smaller sizes. . . ."

Receiver Circuitry is Simplified

"We have also given much attention to reducing the cost and increasing the stability of colour receiver circuitry and components. Approximately a one-third reduction in receiver circuitry has been achieved, without any loss of performance. Substantial cost savings are inherent in the results of this work.

"While the simplified circuit receiver uses 11 tubes less than the modified receiver, nevertheless their performance is the same."



Ghost Reception

SOME NOTES ON ITS CAUSES, EFFECTS, AND SOME SUGGESTED CURES

By B. L. Morley

THE appearance of a ghost picture on the screen often spoils what would otherwise be a very good picture; it occurs in the fringe area and also well within the service area of the transmitter and there are certain spots in Britain covered by the high-powered stations in which reception is almost impossible due to ghost troubles.

A ghost picture is actually a second picture, usually fainter than the main picture but displaced to the right of it. The amount of displacement will vary according to the origin of the ghost and it is possible to receive one which is practically on top of the main picture and hardly distinguishable as such, or to have one which is well separated from the main image.

Fig. 1 shows a typical case and it will be observed that the clock is repeated just to the right of the main image.

A ghost can be negative or positive. A negative ghost is one in which the blacks and whites of the picture are reversed like a photographic negative, while a positive ghost has the same relationship of black and white as the main image.

It is possible to have more than one ghost—in fact in bad areas a whole host of them can be present on the screen with some providing a positive image and some a negative image.

Ghosts which occur almost on top of the original picture are very difficult to diagnose as the only symptom may be a slightly blurred image although the raster lines are clearly focused. This fault can be confused with lack of bandwidth in the vision receiver which gives a similar effect.

Causes of Ghost Images

There are two main causes of ghost images; the

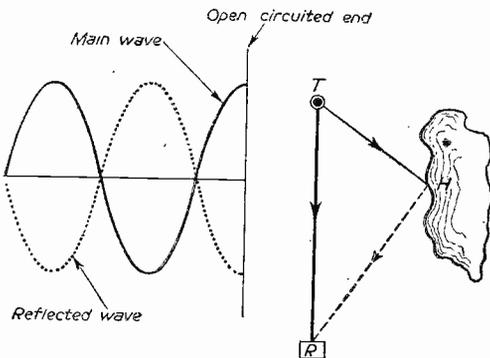


Fig. 2.—The reflected wave. Fig. 3.—Reception of one ghost.

first is due to reflections in the feeder line from the aerial, and the second due to reflections from surrounding objects such as hillsides, steel-framed buildings, etc.

There is another source of ghosts which is not often encountered and this is within the television itself. It is caused by certain of the tuned circuits "ringing" and is more often observed in badly adjusted superhets than in straight receivers.

Feeder Reflections

If the feeder from the aerial to the television is very badly matched at either end it is possible to have reflections taking place throughout its length. The trouble is more likely to occur with long feeders than with short ones though the writer has observed

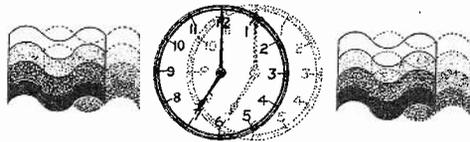


Fig. 1.—A ghost shown on the Tuning Signal.

a series of ghosts (five in all) caused by severe mismatch in a feeder only 60ft. long!

The reason for the reflection is not difficult to understand. Imagine a case where the end of the feeder line is open-circuited, the current wave will travel down the line until it comes to the end; at this point it can travel no farther and will collapse to zero. The consequent collapsing magnetic field associated with the current will induce a current and voltage in the opposite direction which will then travel back to the source.

When the returning wave reaches its originating point an out-of-balance condition will result as it will not be in phase with the waves originating from the source. It will, so to speak, be turned back on itself and will, therefore, return to the far end of the line.

On each journey a certain amount of power is consumed due to the impedance of the line and a certain amount of power is also dissipated in radiation so that after a few journeys up and down the line the current is reduced to zero. Nevertheless the waves will "stand" upon the line and the transmitting engineer usually refers to them as standing waves.

The same principles apply if the line is short-circuited at its distant end. In this case the current wave reaching the short-circuit will suddenly increase to a maximum; the voltage will obviously fall to zero and the consequent sudden change in the magnetic field will induce currents and voltages in the opposite direction which will travel back to the source.

It is not strictly necessary to have a completely

short-circuited or open-circuited line; the termination can be of any value between these two extremes and reflection will take place. No reflection will take place if the line is terminated with its characteristic impedance; for example, if an 80-ohm TV coaxial cable is terminated with an impedance of 80 ohms no reflection will take place. A terminating value other than that of the characteristic impedance will

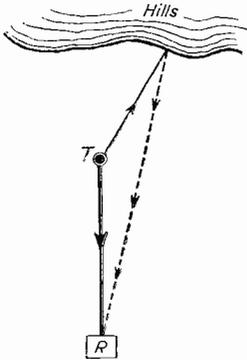


Fig. 4.—Diagram illustrating the result of reflection from an object behind the actual transmitter.


cause reflection, the amount of reflection depending upon the deviation from that impedance.

Note the characteristic impedance of a line is the impedance which the line would have if it were extended to infinity. In all transmission work where power is sent along a line it is necessary to terminate each end with the line's characteristic impedance in order to keep down the losses and to avoid reflections.

It will be seen how necessary it is to ensure that the line is correctly matched. At the television end a transformer is used to ensure that the input impedance of the television is made the same as that of the line.

Note that a transformer will not only transform voltage and current, it will also transform impedance. In transmission of audio frequencies transformers are frequently used solely for this purpose.

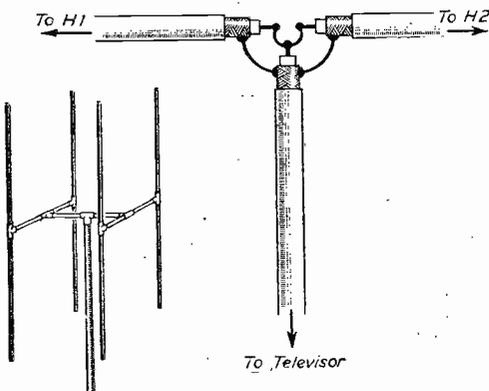The turns ratio of a transformer has a direct relation to the impedance ratio. The voltage ratio of a transformer is the same as the turns ratio; a transformer having a turns ratio of 1 : 3 will therefore have a voltage ratio of 1 : 3; the voltage at the output will be three times that of the input.



Figs. 6 and 7.—A double "H" aerial and the cable connections for a double "H."

The impedance ratio of a transformer is the square of the turns ratio. A transformer with a turns ratio of 1 : 3 will therefore have an impedance ratio of $1 : 3^2 = 1 : 9$. This means that the impedance of the output will be nine times the impedance of the input.

This explains the reasons why it is possible to match correctly an 80-ohm feeder line into the television input circuit, by the use of a small coupling coil or a tap on the main coil.

It will be obvious that not only must the feeder match into the television input but it must also match the aerial output. A small amount of mismatch is allowable and because of this it is possible to use an H aerial with a centre impedance of about 60 ohms with a coaxial line of about 80 ohms. If the mismatch is greater than this then reflections may occur with the production of ghost images.

It is important, therefore, that where a high gain aerial is used in the fringe areas, correct matching is employed not only to ensure the greatest transfer of signals but also to avoid the production of ghost signals.

Reflections from Solid Objects

The very high frequencies employed in TV can be reflected by solid objects such as hills, tall buildings,

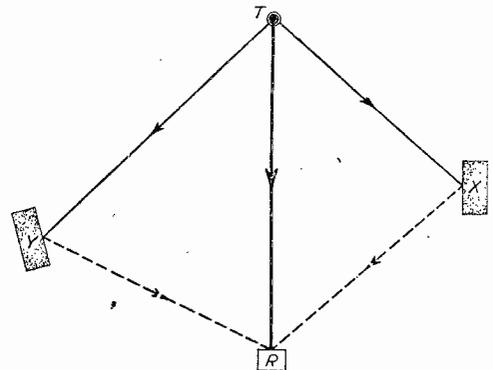


Fig. 5.—Reflection from two sources.

gasometers, etc. Fig. 3 shows typical conditions where reflection can take place.

At the receiving point R a direct signal is received from the transmitter at T. This is the main signal and provides the picture. The electromagnetic waves radiate from the transmitter in all directions and some of them will strike the side of the steep hill at H. Here a certain amount of absorption will take place, but a large percentage of the signal will be reflected towards the receiving point and will therefore be picked up by the aerial at R.

It will be appreciated that the distance from T to R is much shorter than from T through H to R; the signals from the second path will therefore arrive a short time after the signal from the main path; in the meantime the spot on the C.R.T. has moved from the left towards the right and the second signal will therefore show itself on the screen a little to the right of the main image.

Clearly the longer the path of the reflected image, then the greater will be the displacement to the right of the ghost image.

It is possible for the point of reflection to be at such a distance that the reflected image only just

commences on the extreme right of the tube and is continued on the left.

The reflection may be positive or negative according to the reflecting medium and the time of arrival. It is possible for the arrival time to be such that a complete reversal of phase takes place and the whites and blacks are reversed.

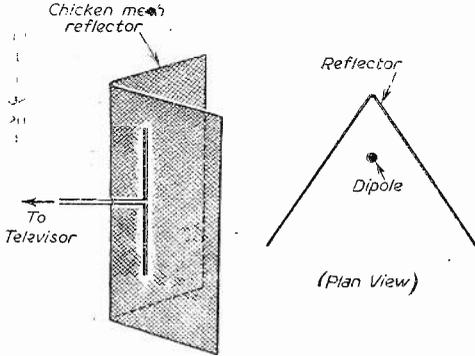


Fig. 8.—The corner reflector.

It is not necessary for the reflecting medium to be placed at one side as shown in the diagram, it can be at the rear of the receiving point and can even be in front of the receiving point. A typical case of the latter is shown in Fig. 4. The main signal reaches the aerial direct and the ghost image is received by reflection from hills behind the transmitter. This type of reflection is the most difficult to cure.

It is possible to have more than one reflection. Fig. 5 shows a typical case of the reception of two reflected images. First, we have the main signal from *T* to *R*, then a reflected image from *T* through *X* to *R*, and then a second reflection from *T* through *Y* to *R*.

The path *T, X, R* is rather shorter than *T, Y, R* and therefore the image from the latter will be displaced more to the right than the image from the former.

In very bad areas a large number of reflections takes place and we have certain notorious localities such as Hebden Bridge, certain areas of Bath and the Welsh valleys working on Wenvoe.

The reception of a double or multiple image is not the only bad effect caused by reflections, but where the reflection is quite strong then it is possible for the sync pulses contained in the reflected signal to trigger the timebases and lead to loss of or intermittent operation of synchronisation.

Before leaving the subject of causes of ghosts, it should be mentioned that it is possible to have reflected images which sometimes entirely disappear. Cases have been reported where ghost images are received for a few days only every week, and the trouble has usually been traced to reflection from a nearby gasometer, the height of the container being considerably reduced when the gas supply was low!

In some cases it is possible to have a variation between summer and winter due to reflections taking place from belts of trees which shed their leaves during the winter.

Band III

The higher the frequency of the electromagnetic wave the more does its behaviour resemble that of

light, and the rather high frequencies which will be employed on Band III are likely to be reflected to a greater degree than those on Band I. This will be especially true in built-up areas where tall, steel-framed buildings are common, and the installation engineer will have to devote considerable attention to the layout of the aerial system.

The Cure of Ghosts

The most obvious answer to the ghost problem is to shield the receiving aerial from the reflecting source. In the simple case an *H* type of aerial will be of appreciable assistance; this aerial operates over quite a wide arc with little fall in the strength of the signal picked up. It is possible to move it over an arc of ± 30 to 40 degrees without decreasing the signal strength too much. It can therefore be aligned so that the point of minimum pick-up—the rear of the aerial—is pointed in the direction of the reflected signals and while there may be some small loss in forward gain the ratio of direct signal to reflected signal is greatly increased; the contrast control can be adjusted so that the ghost is not then visible on the screen.

Where reflection takes place from more than one source then matters are a little more difficult. It is beneficial in these cases to use a high gain aerial because of its directional properties. A high gain array has a narrow pick-up area and the strength of signals falls off rapidly either side of the forward direction.

It is possible that such an array will pick up too great a signal and the first stages of the receiver may be overloaded. It is possible to overcome this defect by using attenuators before the first R.F. valve.

One disadvantage of highly directional arrays is that the radiation pattern may contain subsidiary lobes, so that there is appreciable pick-up at certain definite angles, and if this should coincide with the direction of the reflection, then no benefit will result.

Another solution to the problem is to use a double

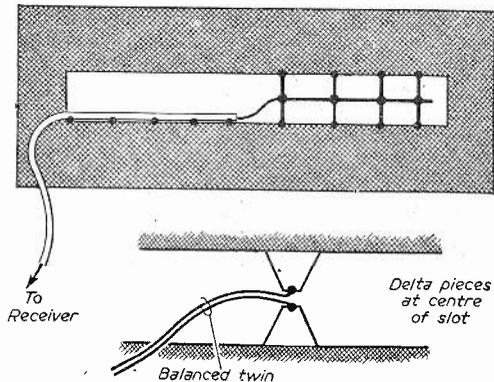


Fig. 9.—Details of the slot aerial.

array and it will be found that a double *H* aerial is generally satisfactory.

The double *H* does not have twice the gain of a single *H*; it is more than a single *H*, however, and what is more important, it has a high front-to-back ratio. It has proved very successful where ghost reception is troublesome.

Fig. 6 shows the scheme. The two *H* aerials are

mounted in parallel with each other $\frac{1}{2}\lambda$ apart. It is important to note that the feeder from each H must be exactly the same length. The simplest method of connection is to run a coaxial lead from the dipole of one H to the crossboom where it joins the supporting mast; an identical length of cable is then run from this point to the other dipole. The feeder down to the television is taken to the same central point and all three cables are connected in parallel as shown in Fig. 7.

If 80-ohm cable is used for each dipole and the feeder is 50-ohm cable there will be a certain amount of mismatch, but not a serious amount. If the connections are made sound and enclosed so as to be weatherproof, then no trouble should be experienced.

Corner Reflector

Where space allows it and it is found that the reflection occurs mostly from the rear, then a corner reflector is worth while. It has an extremely high front-to-back ratio and is not affected by signals arriving from the rear.

Fig. 8 shows the scheme. The reflector can be made of chicken-wire netting of about $\frac{1}{2}$ in. mesh supported on a wooden or metal cage. The centre impedance of the dipole falls rather low in this arrangement and it is necessary to fit some form of matching device. Perhaps the best matching method is to fold the dipole.

An aerial in this form not only has a high front-to-back ratio, but it has a good forward gain and gains in the region of 10-12 db. can be expected.

The Slot Aerial

Perhaps the most successful aerial to combat ghost trouble is the slot aerial; it has been proved very successful in all sorts of difficult localities.

It is easy to construct, is very inexpensive and can be mounted in a loft which has very little headroom.

Chicken wire netting can be used for its construction and a mesh of $\frac{1}{2}$ in. is recommended.

It can be supported in the loft by strings tied to the rafters and should face in the direction of the transmitter.

Fig. 9 shows the arrangement and the method of feeding with coaxial cable.

Balanced twin cable can be used if desired and if the television is designed for this type of input. In

this case the cable is connected to the centre of the slot by means of delta-shaped pieces. (100 Ω cable.)

The slot should be about 1ft. wide and the length should be that of the complementary dipole for the particular channel it is desired to receive.

The width of the netting should be a minimum of 0.2λ for successful operation.

A reflector can be fitted if desired and this can be either a slot reflector or a straight reflector of chicken wire netting.

It is important to realise that the slot aerial must be mounted in the reverse position to the ordinary dipole. Where the transmissions are vertically polarised the slot aerial must be mounted horizontally and where the transmissions are horizontally polarised the slot aerial must be mounted vertically.

The reason for this is to counteract the change in electric and magnetic fields which takes place in the slot aerial.

Where a slot reflector is used it must be mounted in a similar manner to the aerial proper, but if a plain reflector is employed then it should be mounted in the vertical direction for vertically polarised transmissions and horizontally for horizontally polarised transmissions.

When fitting an aerial of this description in the loft it is advisable to keep it as clear as possible of the surrounding objects, paying particular attention to the proximity of electric wiring which may be carrying interference.

Conclusion

In the foregoing paragraphs we have endeavoured to outline the main causes of ghost reception and to suggest a cure. It is not possible to cater for every situation and there are bound to be certain areas where complete elimination is not possible.

One factor which should be remembered is that it is possible for the ghost signal to be stronger than the original and the aerial can be oriented so that it is pointed towards the reflecting source rather than towards the transmitter. This is not always successful, however, for it is possible for the reflected image to become distorted so as to be useless, but it is worth while trying.

Each case must be decided on its merits and the home constructor is advised to experiment for himself with the suggested methods so as to arrive at the best solution for his own particular locality.

BOOK RECEIVED

"Radio Laboratory Handbook," by M. G. Scroggie, B.Sc., M.I.E.E., sixth edition. Published on 23rd August, 1954, at 25s. net (postage 1s. 3d.), for "Wireless World," by Iliffe & Sons Ltd. Size 8 $\frac{1}{2}$ in. x 5 $\frac{1}{2}$ in. 436 pages, 299 illustrations. Cloth bound with jacket.

THIS standard reference book on laboratory electronic techniques, written by a well-known consulting engineer, is intended for both professional engineers and amateurs. It first describes the layout and furnishing of an up-to-date laboratory, and then the various types of apparatus available. Both commercial instruments and improvised equipment are covered. Later chapters deal in detail with methods of making measurements and tests of every kind. Finally, a large section is devoted to general

principles and reference material of everyday use to the radio engineer.

The large amount of information contained in the volume has been presented as concisely as possible and made easily accessible by the very comprehensive system of cross-references, table of contents and index. A special feature is the many carefully selected references to further information.

"Radio Laboratory Handbook" was originally published in 1938, and quickly gained recognition as a lucid and not-too-solemn practical manual filling the gap between "popular" home experimenters' literature and the advanced professional textbooks. In the intervening period, there have been extensive developments in techniques and equipment, with which subsequent editions have kept pace. This sixth edition has been almost entirely rewritten and greatly enlarged and is now presented in a new format. The usefulness of the text is enhanced by some 300 photographs, drawings and circuit diagrams.

The 931A Photomultiplier Cell

SOME INTERESTING DATA FOR THE AMATEUR TELEVISION TRANSMITTER

By C. Grant Dixon

THE 931A is an extremely sensitive photoelectric cell which achieves its sensitivity by electron multiplication. Consider an ordinary photocell; when light is incident on the cathode, electrons are liberated and these are collected by the anode, the entire current through the cell is due to these photoelectrons. In the 931A the electrons emitted by the cathode are caused to strike an electrode called a dynode, which has a special coating that favours secondary emission; this means that each electron striking the dynode may cause the emission of two or more electrons. This process of electron multiplication is repeated as the electrons bounce from one dynode to another and the final current is collected at the anode. Each dynode is kept at a higher potential than the preceding one and this means that the electrons are caused to follow a zig-zag path around the tube as shown in Fig. 4.


The sensitivity of the cell is enormous, being about 10 mA. per lumen when the potential between dynodes is 50 volts, and about 1 amp per lumen when operated at its maximum rating of 100 volts between the dynodes. This may be compared with a figure of 70 μ A. per lumen for a typical cell with no electron multiplication. It should be clearly understood, however, that these are sensitivity figures and the actual current flowing through the cell is much less; the cathode current, in fact, should not exceed 10 μ A. To ensure that this condition is observed, it is essential to operate the cell with comparatively low illumina-

tion when the voltages are applied to the electrodes.

As will be seen from the diagrams, the dynodes are supplied from a tapped potentiometer across the E.H.T. supply. This usually takes the form of a chain of equal resistors, soldered from pin to pin of the special 11-pin socket. These resistors can be $\frac{1}{2}$ or even $\frac{1}{4}$ watt and any value between 10 K and 50 K will be satisfactory, provided they are all equal. A convenient way of controlling the gain of the cell is by varying the total potential across the resistor chain, and this can easily be done by connecting a 2 M potentiometer in series with the chain as shown in the diagrams.

Noise

The 931A is usually employed to feed an amplifier and there are several suitable input circuits depending on whether positive or negative E.H.T. supply is available. As there are 10 stages of multiplication and each requires up to 100 volts, this might seem to imply a total E.H.T. of 1,000 volts, but for most purposes about half this value is sufficient and it is found that there is less "noise" if the cell is worked at a lower voltage. The most satisfactory arrangement is to half-wave rectify one H.T. secondary winding of the mains transformer to give an H.T. line, which is negative with respect to earth, and use the potential difference between this line and the usual H.T. positive line. For the sake of completeness, circuits are also given for those cases where a separate high voltage supply is available.

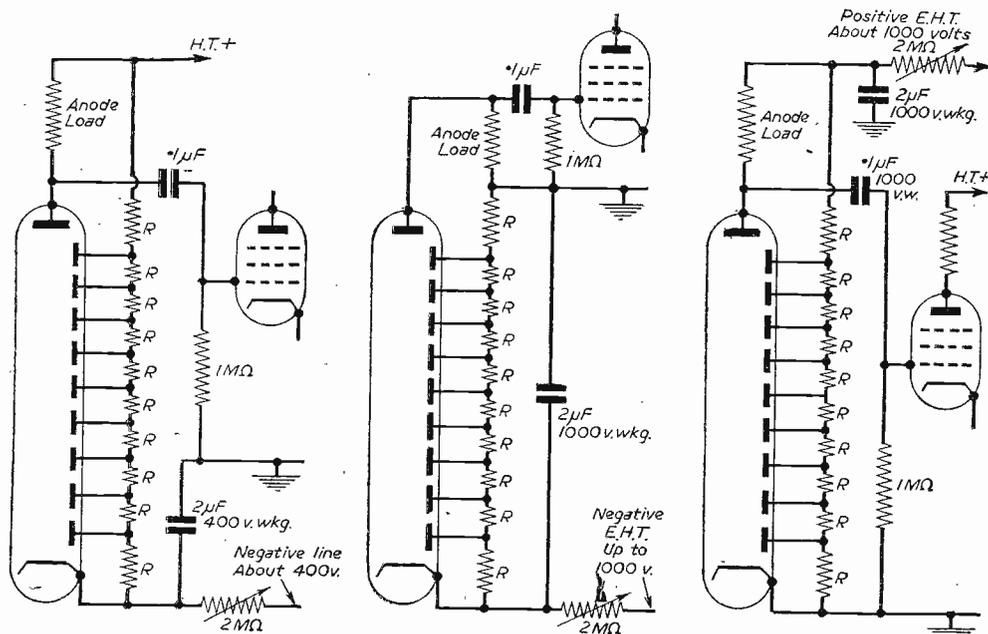

Figs. 1, 2 and 3.—Circuits for the 931A. In these diagrams the cell has been shown elongated for convenience in showing the voltage supplies to the dynodes.

Small Current

As the current drawn from the E.H.T. supply is small, there is not likely to be any trouble with hum or ripple and the $2\mu\text{F}$. condenser shown in the diagrams should be sufficient. It should never be necessary to decouple the dynodes, and stabilisation of the cell voltage is only undertaken where the cell is used for precision measurement as in a photometer. As the electrons are directed on their path by means of electrostatic fields, it is obviously important to keep out stray electrostatic fields by efficient screening. The line timebase of a scanning tube has been known to cause trouble in this way.

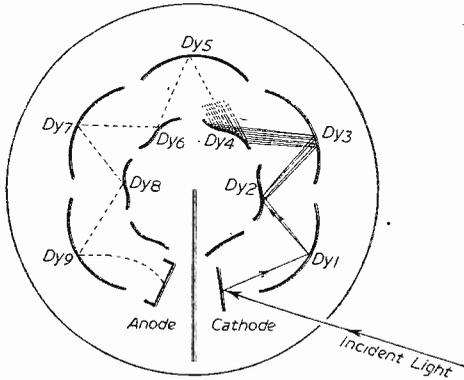


Fig. 4.—Diagram of the electrode structure of the 931A showing electron multiplication and the approximate path of the electrons through the tube.


The 931A has become very popular as a pick-up tube from a flying spot scanner. (See previous article in PRACTICAL TELEVISION, July, 1954.) It has a markedly greater response in the blue region of the spectrum and with a scanning tube such as the 5FP7 this is an advantage. In order to obtain the frequency response desirable for television transmission, the anode load should be kept to a low value and in some circuits 1 K has been specified, though the writer has obtained good results with a 6.8 K load with a suitable peaking inductance. The video amplifier should always be fed from a very low impedance power supply; preferably one using electronic stabilisation with a series valve, or alternatively a smoothing condenser, having a value in the region of $150\ \mu\text{F}$ may be used. If this is not done, some trouble may be experienced with very low frequency oscillation.

An Experiment

Whilst on the subject of the 931A and amateur television applications, the following suggestion is offered as it may interest some readers who are looking for something unusual to do. If a couple of old 30-line scanning discs and motors can be obtained it is a comparatively easy matter to rig one up as a "live" camera and the other as a monitor. Of course, 30-line pictures are of historic rather than of practical value, but it is very satisfying to build up one's own TV. camera, of whatever definition. The scene to be televised is focused on the rotating disc and a lens gathers in the light and concentrates it on the 931A. The frequency response need not exceed 20 kc/s if the old 30-line standards are adhered to, and this means that a comparatively simple amplifier will

serve to modulate the neon tube behind the receiver disc. Of course, there will be many readers to whom the last few sentences convey nothing, they are those who have missed the days of real pioneer TV reception, but the principles of 30-line reception can be easily

Fig. 5.—Base connections for the 931A cell.

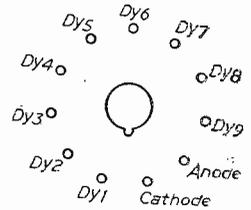

grasped by reference to books and magazines of the 1930-35 period.

Another use for the 931A is the measurement, or rather the comparison, of the "D.C." value of very low light levels as in a spectrophotometer. For this purpose a toothed wheel is interposed between the light and the 931A to convert the steady light into a varying one. This "chopped" light beam, when incident on the 931A, gives rise to an alternating voltage across the load and this is usually amplified by a narrow bandwidth, tuned, amplifier and, after rectification, is used to give an indication on a sensitive milliammeter. For this application "noise" is of little importance and the cell can be worked at its maximum voltage with a high anode load, thus giving an extremely sensitive device.

In conclusion it should be pointed out that the 931A shows its superiority over the conventional photocell only when dealing with very low light levels, and it is interesting to note that photo-multiplier cells of more advanced design are becoming increasingly used for detecting the scintillations produced by alpha particles.

" PRACTICAL " SUGGESTIONS FOR CHRISTMAS !

This year, why not solve your Christmas gift problems by sending Gift Subscriptions for one of the famous "Practical" magazines edited by F. J. Camm? Most of your friends are sure to be delighted with a year's subscription for one of them—and the copies, arriving regularly, month by month or week by week, will serve as constant reminders of your good wishes from the beginning of the year till the end.

It's very simple to arrange—just write to the Subscription Manager (G.I.), "PRACTICAL MAGAZINES," Tower House, Southampton Street, Strand, London, W.C.2, enclosing the names and addresses of your friends, the titles of the magazines you wish to be sent, and remittance to cover. We will arrange for attractive greetings cards to be despatched, in your name, announcing your gifts in good time for Christmas.

A year's subscription to PRACTICAL MECHANICS and PRACTICAL MOTORIST & MOTOR CYCLIST costs 14s. (Canada 13s.), including postage to any part of the world, to PRACTICAL TELEVISION and PRACTICAL WIRELESS 13s. 6d. (Canada 13s.), and to PRACTICAL ENGINEERING £1 12s. 6d. (Canada £1 10s. 4d.).

Final Thoughts on the Show

A VISITOR REVIEWS SOME OF THE EXHIBITS

By The Marquis of Donegall

THE National Radio and Television Show came of age this year and proved highly worthy of adult status.

Before touring the Earls Court exhibition let us mention a few highlights that struck the visitor.

On the whole prices have not come down since last year, but this is compensated for by the fact that general improvement in performance has necessitated more complicated—and in some cases more costly—insides. Better value for much the same money was, I would say, the keynote of the show.

The word novelty best describes the demonstration on a closed circuit of 3-D television by Messrs. Pye. The effect of depth is achieved by throwing two images on to a screen, but I refuse to be unduly impressed by any process, either in cinema or television, that requires the use of spectacles by the audience. At least this experimental 3-D television is viewed on a flat screen and not—a scientific absurdity—by trying to make a flat surface out of the curved wrong-end of a cathode-ray tube.

Condemned as we still are to the optical gymnastics of direct viewing by the overwhelming majority of manufacturers, the 17in. picture rules the day as opposed to the 14in. picture in the majority last year. I shed a metaphorical tear for the death and burial of the 9in. tube: it was such a conveniently portable little set and one unkind critic remarked on its passing that 9in. was, if anything, too big a picture for most of our television programmes. Contrariwise, the portable gramophone that you wind up with a handle is still selling in incredible quantities.

E.M.I. announced with deafening fanfare that the ever-patient public may now buy copies of master-tapes from which the gramophone records of the group are made. I tried the Menuhin and Joe Loss tapes on my own tape recorder and it must be admitted that the reproduction from the speaker placed at the top of my staircase to the living room downstairs was quite uncanny in fidelity. Ever patient, however, is the operative word so far as the public is concerned because, 17 years ago, I undertook to demonstrate in my home a "radiogram" which played tape instead of records. It was never marketed because the interested parties were unable to find sufficient well-known artistes and orchestras that were not under contract to the various gramophone companies.

Appearance

The outside appearance of radio and television sets having just about reached the zenith of craftsmanship, design and material, there is little to be said that contrasts with last year except that there was even greater variety and, surely, a set to suit every taste, from that of Madame de Pompadour to that of Diogenes. (As a matter of fact, there was a radio-controlled beer-barrel—appropriately just outside the Press Room—that rolled itself about and dispensed beer to the multitude.)

The outstanding major development emerging at this year's show concerns the opening of the BBC's

V.H.F./F.M. broadcasting stations next year. Although they are not yet available there were some radiograms and TV sets capable of receiving these new stations which are of special interest to those living in bad reception areas and within 50 miles range.

Sundry historic exhibits were fascinating. These included Marconi's diary and the set that enabled Crippen to be apprehended in mid-Atlantic.

On the Baird stand they showed the earliest television set that first functioned in 1932. But the first tube to produce colour television had special interest for me. It was in December, 1940, that Baird asked me to bring something red or blue to his house near the Crystal Palace and I arrived with Miss Paddie Naismith, a flaming redhead, dressed in bright blue. Paddie was duly televised in colour from Baird's house to an outhouse some 50 yards away on a 3ft. x 4ft. screen. The quality of the colour reproduction astounded Baird's guests—14 years ago.

The Royal Navy showed under-water television and included among its exhibits the TV camera which they used to find the Comet that disintegrated near the island of Elba.


The Army provided a look into the future by demonstrating battlefield television, which it has not so far used.

The Royal Air Force demonstrated most lucidly the important part played by radio in forecasting the weather. There was a typical Meteorological Forecasting Office with Radio Sonde and Sferic Radio Director Finder that tracks down thunderstorms in remote places.

Contrasts

Now for a few contrasts. Vidor's "Lady Margaret"—8in. by 4in., weighing 6½lb.—was said to be the smallest battery set. And the largest TV screen in the world, measuring 21ft. by 16ft., was a Cintel installation in the BBC arena.

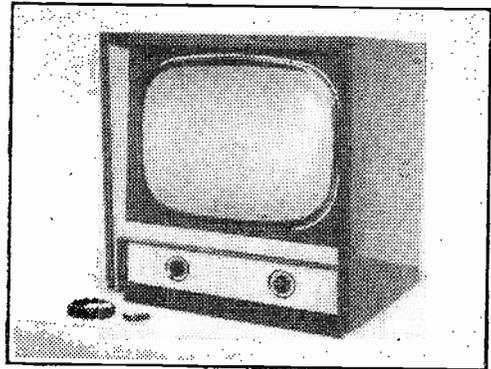The smallest TV camera was to be seen on the Pye stand. It is an industrial type-of which one was recently installed in a whaling ship. As a gadget



The Murphy V250 Table Model.

maniac I was, of course, delighted with the H.M.V., Philips and Ekco novelty radios that put you to sleep, wake you up, cook your breakfast, switch your light on and, for all I know, take the dog for a walk!

Champion have produced table-radiograms at 42 and 33 guineas. The most expensive radiogram that I found was on the R.G.D. stand at £611.

The smallest three-wave mains receiver, 8in. by 4½in. by 4½in., was shown by Alba; and Roberts, whose portables I have long regarded as among the finest in the world, have produced a "baby" at 15 guineas. It is a battery set for medium and long wave with a 5in.-moving coil loudspeaker having a field flux density of 11,000 gauss.

The H.M.V. portable radiogram (model 2001), priced at 22 guineas, is a very neat job that copes with all sizes of records and all three speeds. It has a rotatable dual-headed pick-up and a 10½in. elliptical loudspeaker. In this field Decca compete with their Deccamatic II with a Collaro turnover pick-up at 19 guineas. Personally I use a Deccalian of which the new model is numbered 81 and is priced at £34 18s. 10d. On the Deccalian, Decca still favour interchangeable ferr magnetic pick-up heads with sapphire styli. Their technicians unequivocally assert that comparable fidelity cannot be achieved with a rotatable pick-up head.

Innumerable makers show record-players to cope with all speeds and sizes of records through existing radios or radiograms. Twelve guineas seemed to be an average price for these.

My American friends never cease to be amazed when they see my Decca projection set in operation and generally begin by mistaking the picture on my screen for home-movies.

"We don't have that in the United States," they usually remark. And I refrain from pointing out that neither did they have a television service at all in 1936. The new projection model costs £165, including the screen, of which I can tell you from experience the 3ft. by 2ft. is by far the most suitable for the average sitting-room.

This year's exhibition brought home the fact that it is now possible to buy TV sets that will receive

the commercial programme when it becomes available.

Television receivers working on one of the frequencies to be allotted to the Independent Television Authority were demonstrated by superimposing a Band III signal from a special transmitter in the R.I.C. control-room so that it was possible to switch from the BBC band to the other. This alternative "programme" was obviously not designed for entertainment. It consisted of fish swimming in an aquarium with the caption "This receiver is now operating on an alternative programme wavelength." Other firms showed TV sets that at present can only receive the BBC, but are readily convertible. What it amounts to is that these cost 5 or 6 guineas less and you pay that sum when the time comes to have the set adapted to commercial TV.

Turret Tuning

Most firms have adopted the 12-position turret tuner. This gives tuning to any of the five BBC Band I channels and to the two channels so far allocated to commercial TV in Band III. Bush, however, use a two-position band switch plus two continuously variable tuning-knobs, each tuning over one of the bands. And Regentone use a two-band switch system combined with continuous tuning. The band switch is operated automatically by the tuning-knob. Nearly every set is designed for the easy addition of a tuner. For instance, the Vidor 14in. and 17in. models already provide the necessary space and fixing studs. The English Electric "Rotomatic" can also be adapted by using only one's bare hands.

To sum up on TV, focus at the edges of the screen has improved and I would say that the "scan" is more uniform. Interference suppression circuits are often adjustable to local conditions. The all-round result is sharper, steadier and brighter pictures. Much attention has been concentrated on catering for the fringe areas.


Finally, Ferguson found their "Halo Light," which is a luminous screen surround that produces the illusion of a larger picture, such a success that they have now incorporated it on four new models. Some makers, of which one is Ekco (TC209), provide frequency-modulated sound reception. It is noteworthy that few TV sets incorporate a radio. The Philco A1718 is an exception and the price is 106 guineas.

The Ferrite rod aerial of Pilot and Champion sets was a novelty to me, as was the incorporation of a built-in aerial in an Invicta receiver.

The 21in. rectangular tube—Kolster-Brandes table model, Philco and Ferguson consoles—was also a novelty; but the H.M.V. 1820 has a round 21in. tube.


Twelve-inch speakers, notably by Goodman, make their appearance in several radiograms, including the Ferranti 1045 and the Regentone ARG88. Philco have produced a push-button short-wave converter that can be added to any make of car radio. They also make two six-valve and two eight-valve car radios.

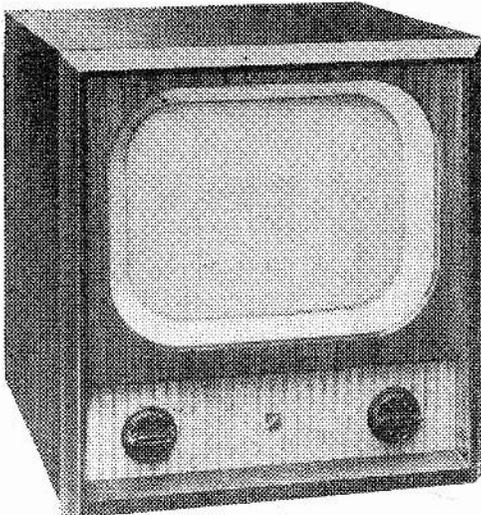Let me end this little account of a highly impressive and thoroughly enjoyable 21st birthday National Radio and Television Exhibition by saying, as did Sir Miles Thomas in his opening speech, that this year's show was "a striking testimony to the achievements of a great industry."



This is the Alba Model T321—a 14in. tunable receiver.

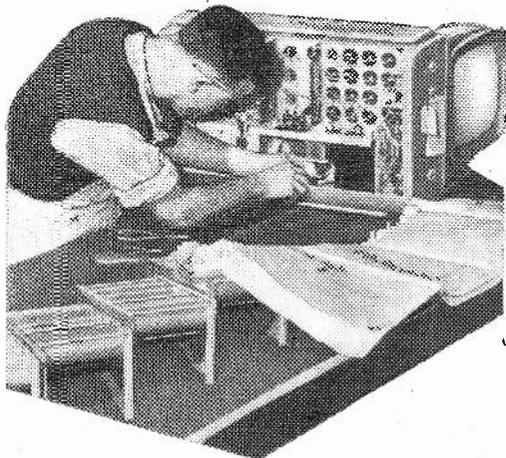PAGES FROM A TELEVISION ENGINEER'S NOTEBOOK



22.—FURTHER SWEEP CIRCUITS

directly proportional to the depth of penetration, and consequently the frequency will now be inversely proportional to the square root of the penetration, which again is assumed to vary linearly. Both systems, therefore, give a non-linear variation of frequency with electrode displacement, and to a similar degree. The result is obviously unaffected by any fixed capacity shunting the mechanical system. This is added to amplify the remarks of last month on mechanical systems, and must be borne in mind

As we have already seen, it is not possible to get a linear frequency change with a linear motion on either the rotating condenser or coaxial plunger tuning systems. On the basis of a lumped circuit for the oscillator tuning elements, the frequency is inversely proportional to the square root of the total capacity; if this capacity is in the form of a parallel plate condenser, it will be inversely proportional to the separation of the plates, so that the frequency will then be directly proportional to the square root of the plate separation which is assumed to be varied linearly by the mechanical drive.

If the capacity is made up of the form of a coaxial condenser with a reciprocating plunger, it will be

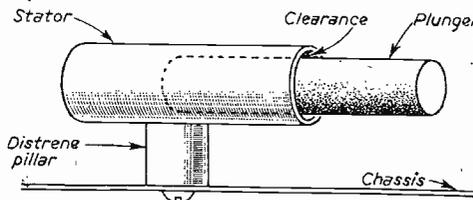


Fig. 1.—Mounting of a co-axial tuning system. The stator is best split to form a split-stator condenser.

by the experimenter who is working on mechanical systems. For true frequency linearity, more complex condenser arrangements are necessary. The coaxial form has, however, the property that the rate of change of capacity with penetration is independent of the initial depth (which is equivalent to a fixed shunting capacity) and is therefore unaffected by mechanical distortions arising from the motions imparted to the plunger. This system is the better for the experimenter, but usually calls for better engineering from a mechanical point of view than the rotating condenser form.

Practical Hints

As was outlined last month, a plunger form of condenser can be operated from an old loudspeaker cone movement, but the exact form the set-up will take obviously depends upon the constructor. Referring to Fig. 1, the important points are the mounting of the fixed tube (stator) and the clearance between it and the plunger (moving plate). The tube can be readily mounted off the chassis on a distrene pillar, which must be without shake, however; but

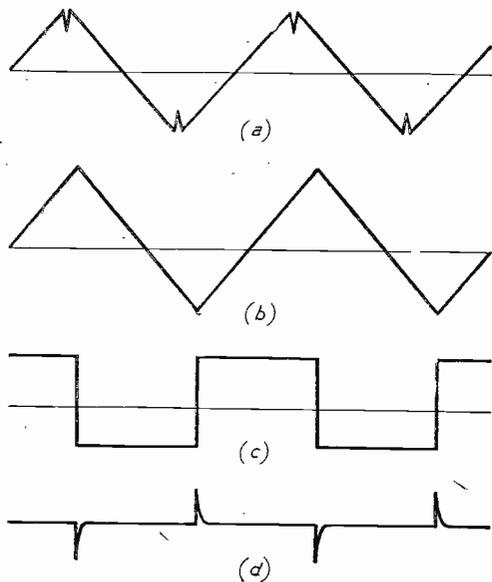


Fig. 2.—Waveforms associated with a plunger driven by a speaker cone adaption.



Fig. 4.—Appearance of marker pip from signal generator.

the fitting of the plunger to the speaker cone movement, or cam associated with a small motor, will have to be tackled in a way best dictated by the shape and size, etc., of the actual pieces being used.

The clearance cannot be very small unless very precise work can be undertaken and the proper tools are to hand, but normally a spacing of 1/16in. is quite reasonable from this point of view, and also allows a

scope with which the circuit is to be used must be triggered in synchronism with the capacity change. Normally, a switch system can be readily set up for this, the beam being blanked off during the return trace at the same time.

V₃ is a mixer with V₄ as the variable oscillator. V₄ is tunable over the range 115 to 185 Mc/s; and details of the coils, etc., are given in the figure. Mixing takes place in the cathode of V₃, and the output at the anode is taken to the set under examination. A simple attenuator may be inserted at this point if necessary.

If a signal generator c.w. output is applied to the output simultaneously (as shown), a pip will appear on the response curve as depicted in Fig. 4. A ready means of determining frequency, read from the signal generator, is then available. The signal generator output should be adjusted so that the pip is small.

The valves may be double triodes such as ECC81's.

Electronic Sweeping:

Electronic sweeping may appeal more to the home experimenter than the mechanical systems just discussed, and a basic circuit is shown in Fig. 5. Here the valve V takes the place of the mechanical tuning set up, the remainder of the circuit being similar to that of Fig. 4.

A linear sawtooth is applied from the timebase to potentiometer R₁, and a portion of this is therefore applied to the grid

of the reactance valve V. This alters the mutual conductance of the stage and also the apparent capacity which is wired across the first oscillator circuit.

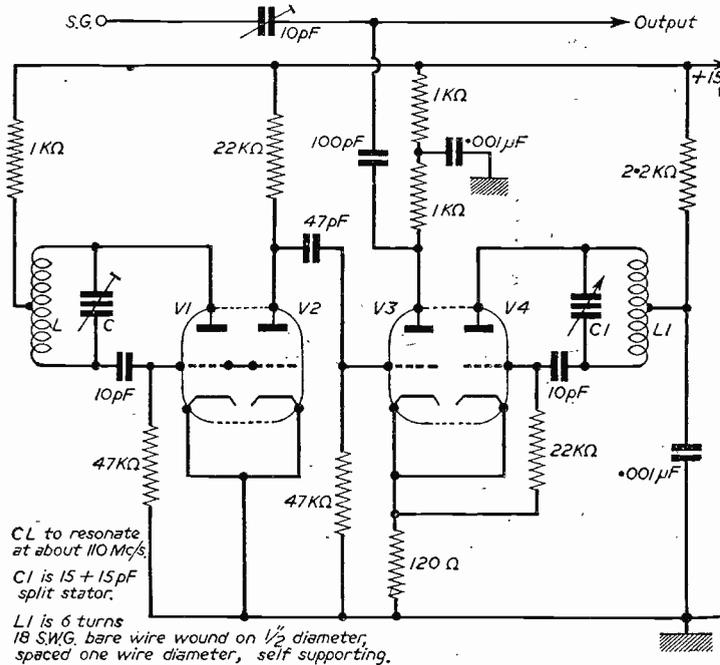


Fig. 3. — A simple sweep circuit.

reasonable capacity change to be obtained without a very long plunger movement, a thing to be avoided. A 3/16in. plunger moving in a 1/4in. tube has a capacity change of about 0.5 pF per 1/8in. movement. At 100 Mc/s a change of 2 pF is normally sufficient to give a frequency change of 6 Mc/s with the proper inductance and fixed tuning values, and when used in a mixer system, as outlined in the previous article, will provide this sweep of frequency over the television bands.

To get a linear backward and forward motion on the plunger when operated from a speaker system, it is necessary to produce a driving current in the speech coil that is shaped as shown in Fig. 2(a). The actual motion will then be as shown at (b). Such a waveform can be derived from a square wave, which is first integrated into a triangular wave and also differentiated (see (c) and (d)). A combination of these two waveforms will then produce that of (a).

Simple Circuit

A simple circuit is shown in Fig. 3. Here the oscillator V₁ operates at 110 Mc/s by the tuned circuit LC. C is mechanically operated to give a change of 3 Mc/s on either side of 110 Mc/s, the resultant output being buffered and amplified by V₂. The exact form of the mechanical control matters little provided this change is achieved, but the timebase of the oscillo-


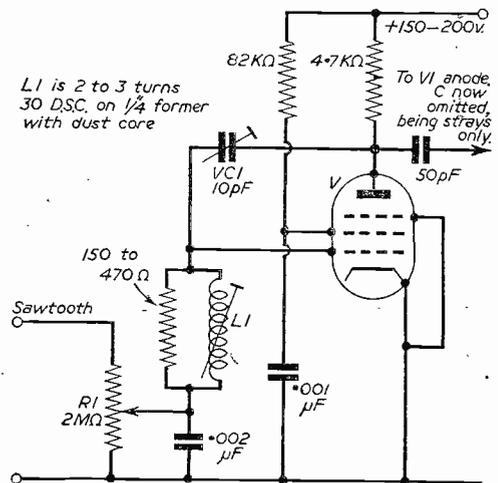


Fig. 5. — Electronic equivalent of the mechanical tuning systems.

Smith's for Technical Books

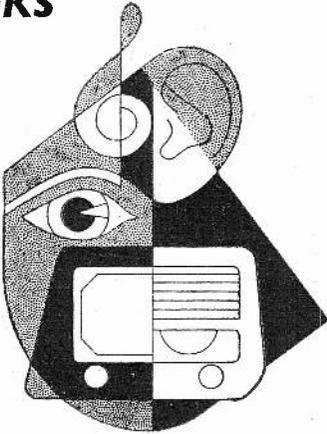

Books on the theory and practice of electronics, new developments, circuit design, and other specialized subjects can be quickly supplied through your local Smith's shop or bookstall.

Your copies of *PRACTICAL TELEVISION* can be bound into attractive volumes; and all your stationery and printed matter supplied through our local branch.

W. H. Smith & Son

for SPECIALIST BOOKS

Head Office: Strand House, London, W.C.2

Used Mazda C.R.M. 123 Cathode heater short aluminized. Complete with rubber mask Elac P.M. focus unit, scan coils, low line, low frame and frame o.p. trans., £5.10.0. P. & P. 7/6.

Used Mazda 12in. C.R. Tube 121, 121A heater cathode short. £3.7.6. P. & P. 7/6. Guaranteed 3 months.

Used Mazda 9in. C.R. Tube, heater cathode short. C.R.M. 91 92 & 92A. Guaranteed 3 months. 37/6. P. & P. 7/6.

Most of the above 9in. with ion burn 17/6 post paid.

9in. T.V. Cabinet in polished walnut, complete with chassis, 20/- post paid.

USED 9' TUBE with ion burn 17/6 post paid.

USED Mullard 12in. with ion burn 50/-. P. & P. 7/6.

Line and E.H.T. Transformer, 9KV_A using ferocart core complete with built-in line and width control. Mounted on All-chassis. Overall size 4 1/2 in. x 1 1/2 in. EY51 Rec. winding. P. & P. 2/6. 27/6.

Scan coils, low line, low frame, complete with frame o.p. trans. to match above line and E.H.T. 27/6. P. & P. 2/6.

Heater Transformer, Pri. 230-250 v. 6v. 1 1/2 amp. 6/- ; 2 v. 2 1/2 amp. 5/-. P. & P. each 1/-.

Completely built Signal Generator.

Coverage
120 Kc/s-320 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8.5 Mc/s-25 Mc/s, 17 Mc/s-50 Mc/s, 25.5 Mc/s-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black

crackle finished case and white panel. £4.19.6, or 34/- deposit and 3 monthly payments 25/-. P. & P. 4/- extra.

Pattern Generator, 40-70 Mc/s direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits, and vision channel band width. Silver plated coils, black crackle finished case, 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 200-250 volts. This instrument will align any T.V. receiver. Cash price £3.19.6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/- extra.

T.V. Converter for the new commercial stations complete with 2 valves. Frequency : can be set to any channel within the 186-196 Mc/s band. I.F. : will work into any existing T.V. receiver designed to work between 42-68 Mc/s. Sensitivity 10 MuV with any normal T.V. set. Input : arranged for 300 ohm feeder. 80 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF80 as local oscillator. ECC81 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier 10 db. Required power supply of 200 v. D.C. at 25 mA. 6.3 v. A.C. at 0.6 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2.10.0. P. & P. 2/6.

Line & E.H.T. transformer, 9KV, ferocart core. EY51 heater winding, complete with scan coils and frame output transformer and line and width control. P. & P. 3/-. £2.5.0.

T.V. Filter in lightly tinted perspex size 1 1/2 x 1 1/2 x 3/16 in., 4/6. Metal rectifier, 250 v. 250 mA, 12/6. Used metal rectifier 250 v. 150 mA, 6/6.

R. and A.T.V. energised 6in. Speaker, field coil 175 ohms. Requires minimum 150 mA to energise maximum current 250 mA. P. & P. 2/-. 9/6.

Valve Holders, moulded octal Mazda, and loctal, 7d. each. Paxolin octal. Mazda and loctal, 4d. each. Moulded B7G, B8A and B9A, 7d. each. EY3 moulded with screening can, 1/6 each.

Combined 12in. Mask and Escutecheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet. 12/6. As above for 15in. tube, 17/6.

Frame Oscillator Blocking Trans., 4/6.

Smoothing Choke, 250 mA 5 henry, 8/6 ; 250 mA, 10 henry, 10/6 ; 250 mA, 8 henry, 8/6.

P.M. Focus Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15/-. **P.M. Focus Unit** for Mazda, 12in., with Vernier adjustment, 17/6. **Wide Angle P.M. Focus Unit** Vernier adj., state tube, 25/-.

Energised Focal Coil, low resistance mounting bracket, 17/6. **Ion Traps** for Mullard or English Electric tubes, 5/- post paid.

T.V. Coils, moulded former, iron cored, wound for rewinding purposes only. All-can 1 1/2 in. x 1 in., 1/- each ; 2 iron-cores All-can, 2 1/2 in. x 1 in., 1/6 each.

Dubilier .001 10kV, working, 3/6.

Cydon 5 channel T.V. tuner 12/6 post paid.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquires S.A.E. Lists 5d. each.

D. COHEN

RADIO AND TELEVISION COMPONENTS

23, HIGH STREET, ACTON, W.3.

(Opposite Granada Cinema)

14 DAYS' FREE TRIAL

Send only £1 deposit—refunded if tool not approved.

1in. DRILL

Robust tool with trigger switch and self-centring chuck. Drills, sands, polishes, grinds, sharpens. Also, with attachments, drives: lathe, saw bench, rise and fall, grinder, buffer, etc.

Price £5. 19. 6 cash, or 20/- deposit. Carriage and Packing 2/6.



Horizontal Stand
17/6, post 1/6

Vertical Bench Stand
£3.7.6, post 2/6.

Lathe Stand

£5. 5. 0, or 20/- deposit. Carriage and Packing 5/-.

The four items £15. 9. 6, or £3 deposit.

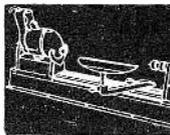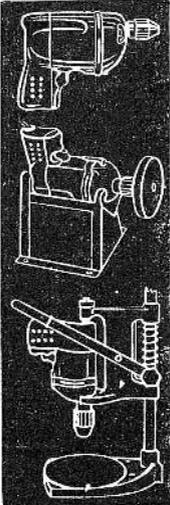

HANDY BATTERY THREE

Constructional data showing how to make useful portable loudspeaker set (total cost 70/-, including cabinet) is available. Price 1/6.




MULTI-METER KIT

The Multi-meter illustrated measures D.C. volts, D.C. m/amps and ohms. It has a sensitivity of 500 ohms per volt and is equally suitable for the keen experimenter, service engineer or student. All the essential parts including 1in. moving coil meter, selected resistors, wire for shunts, 8-point range selector, calibrated scale, stick on range indicator and full instructions for making are available as a kit, price 15/- plus 9d. post and packing.

MAKE A RADIO


Using our parts in one evening you can make an all mains 4 valve radio with bakelite case, then you will be giving a £12 present which costs you only £5.15.0, or £2 deposit. (Carr. and insurance 5/-.) Data book 1/6.

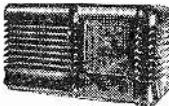

BEETHOVEN 5-VALVE SUPERHET

Complete with valves and Rola loudspeaker ready to work off A.C. mains—three waves (L. M. and S.)—large dial, slow motion drive, dust coated coils, etc. £8. 17. 6, or £2 deposit (balance over 12 months), carr. 7/6.

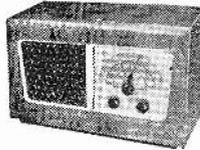Fine walnut veneered and polished cabinet to take the Beethoven 5-valve Superhet with 6in. loudspeaker, thus making a really excellent table model—worth £18-£20. Price 49/6, carr. and packing 5/- extra. If bought with the Beethoven chassis, the hire purchase deposit is £3. carr. 10/-.



THE SUPERIOR 15in.

up to the minute big picture TV for only £37. 10. 0. A 20-valve televisor for the amateur constructor, all components, valves and 15in. Cosmor Cathode Ray Tube costs £37.10.0, plus £1 carriage and insurance or £12. 10. 0 deposit and 12 monthly payments of £2. 11. 6. Constructor's envelope giving full details and blueprint, 7/6. Returnable within 14 days if you think you cannot make the set.




MAINS MIDGET RADIO

This is an excellent little radio in an attractive cabinet to which can be affixed transfers, thus making it extra suitable for nursery or child's bedroom. The circuit is a T.R.F. for A.C. mains operation. All the parts—bakelite cabinet, valves, knobs, back—in fact everything will cost you only £3.15.0, plus 2/6 postage. Construction data free with the parts or available separately at 1/6.


REBUILT T.V. TUBES

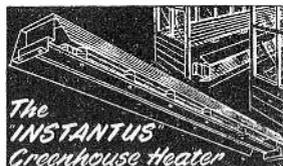All sizes completely rebuilt as new. Cost approx. half-price. Call or write for list of types in stock.



4ft. long made from heavy gauge sheet steel (galvanised), 1 kW. suitable A.C. or D.C. Price £2, or with thermostat £3.15.0. Note: The thermostat mounts separately and will control up to three heaters.

CLEVELAND CAR BATTERY CHARGER

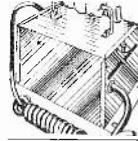

Gives 14 amp. charge—uses everlasting metal rectifier and robust double wound mains transformer—in metal carrying case with leads and croc. clips. Price, 6 volt 29/8, 6 to 12 volts, 39/8, post. 2/6.

ELECTRIC CLOTHES HORSE

Warms room as it dries clothes, towels, etc.—stove enamelled rails—A.C. or D.C. 650 watts. Size 3ft. x 3ft. x 3in. Made to sell at 12 gns., fully guaranteed only £3. 19. 6, carr. 7/6.



Complete kit comprises battery control unit, starter lamp, lamp holders clips and wiring diagram. Price less tube 22/6, plus 1/6 post, with tube 30/-, carriage and insurance 3/6. Tubes 7/6 each carr. free, minimum quantity 6.

CONSTRUCTOR'S PARCEL



3 colour, 3 wave band scale covering standard Long, Medium, and Short wavebands, scale punched for standard 5 valve superhet, pulley, driving head, springs, etc., to suit. Scale size 14 1/2in. x 3 1/2in. Chassis size, 15in. x 5in. x 2in. deep. Price 15/-, plus 1/6 post. Note: We have a really excellent walnut veneered cabinet for this, price only 37/6.

AUTO RADIOGRAM

From 25 gns.

Good assortment of cabinets, chassis, and auto changers, available at all branches—total cost from 25 gns.



ADJUSTABLE THERMOSTAT

250 v. heavy silver contacts can be adjusted to operate between 70 deg.-300 deg. F. These are suitable for aquarium heaters, electric blankets, etc., etc. 1 Amp. Model, 3/6. 2 Amp. Model, 5/6. 5 Amp Model, 8/6. Post, etc., 6d. extra.



CONNECTING WIRE SNIP

P.V.C. insulated 23 s.w.g. copper wire in 100ft. coils, 2/9 each. Colours available: Black, Brown, Red, Orange, Pink, Yellow, White. Transparent. 4 coils for 10/-.

Another Address for Personal Shoppers

We are pleased to announce that we have taken premises in the Kilburn district. The address is:—


249, KILBURN HIGH ROAD, KILBURN, OPENING SHORTLY LONDON, N.W.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 5, RUISLIP.

Personal shoppers, however, can call at:

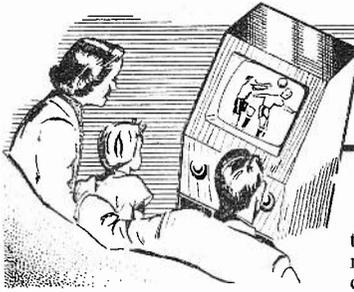42-46, Windmill Hill, 152-3, Fleet Street, 29, Stroud Green Road, Ruislip, Middx., E.C.4, Finsbury Park, N.4.
Phone: RUISLIP 5780 Phone: CENTRAL 2833 Phone: ARCHWAY 1049
Half day, Wednesday. Half day, Saturday. Half day, Thursday.



UNDERNEATH THE DIPOLE

By Iconos

THE I.T.A.

THE passing of the Act which gave birth to the Independent Television Authority has by no means ended the most popular controversy of 1953—sponsored television programmes: to be or not to be. Many viewers, members of the radio industry and newspaper commentators watched with misgivings the gradual formation of a compromise solution which seemed to them to combine the weakest features of both nationalisation and private enterprise, tied together with a full measure of red tape. Their apprehensions were increased when the names of the members of the governing council were announced: worthy and well-meaning individuals who, for the most part, excelled in their own particular non-television fields. Sections of the national press began to be alarmed and dubbed the I.T.A. as being neither fish, fowl nor good red-herring. Then came the appointments of Sir Kenneth Clarke and Sir Robert Brown Fraser as Chairman and Director-General, respectively, and their dismay began to turn to anger. "Good men—but bad appointments" wailed one critic. "A political appointment" wrote another, "for which the Postmaster-General deserves severe censure." The radio industry, grateful for relaxation of the hire-purchase restrictions, pressed on with the production of more and more TV sets; but at the same time prepared themselves for a long, long wait for sponsored programmes to be produced with a cultural background of Arts Council, Whitehall and a tug-of-war between the political parties.

Let us hope that Sir Kenneth and Sir Robert will confound the dismal prophesies of the critics. Otherwise, the only people they will please will be the moguls of the theatre and film worlds—together with the TV Executives of

their rivals, the BBC. It is well to remember that the I.T.A.'s principal practical function is to own and operate a chain of TV transmitting stations, leaving the programme arrangement and organisation to others. That being the case, one would have thought that the I.T.A.'s chief executives would have some kind of engineering background. When the original British Broadcasting Company Limited was formed, the Board (under Lord Gainsford) looked to engineering for its chief executives and selected J. C. W. (now Lord) Reith and P. P. Eckersley, both of them engineers as well as administrators. This valuable precedent has been ignored.

TV STARS

THE power of TV as a star-maker increases week by week. Already we have Gilbert Harding, Elizabeth Allen, Benny Hill, David Nixon and scores of others who are now well established and top bills at variety houses, feature in films or perform on political platforms in brains trusts. Two or three successful TV appearances—and their names are made! It is just as simple as that. "What's My Line" and its variations have already created more star names in Britain than a couple of decades of sound radio or fifty years of music hall. Latest passengers on the BBC's star-making wagon are Eunice Gayson, another "What's My Line"-er, and Peter Cushing, actor in TV costume plays—followed up by Helen Bailey, a new expert panellist, whose gentle charm is allied to a brilliant brain.

NEW STYLE OPERA

I MUST admit that self-conscious arty-crafty entertainment leaves me stone cold. I don't just dislike it; I despise it. Therefore, the idea of "Three's Company," an opera with three singers and one piano, with a musical score by a new young composer, Antony Hopkins, did not attract me very much. However, I decided to get

"into training" for a typical example of what some people allege sponsored TV will give us—and I enjoyed it. This was not the usual hotch-potch of cheap gibes at established customs. "Three's Company" had all the wit and sparkle that West-End theatregoers glean from half-a-dozen intimate revues—caviar for the sophisticates and honest British humour for everyman. The music, written and played by Antony Hopkins revealed an unusual coherency in this age of obscure impressionistic musical composition. It gave admirable point to Michael Flander's libretto. The basic plot of this surprise packet was enacted in flash-back form and concerned the rivalry of two business men for their secretary. Mr. Three (Eric Shilling) is the sharp business man who rules the firm belonging to his dullard partner Mr. Love (Stephen Manton) under the terms of Mr. Lowe senior's will. Miss Honey (Elizabeth Boyd) is the woman in the case. The musical treatment on highly original lines intermingled arias of the traditional Verdi or Puccini flavour, but in Latin-American tempo, with Flanagan and Allen-type duets and an impressive baritone solo in a blues idiom. The outstanding artist was Stephen Manton, well-known on sound radio as a tenor of distinction but now revealed as a new singing clown whose mime and sense of timing are first rate. "Three's Company" was an enjoyable experiment for a late night spot—all the more enjoyable for confounding my gloomy expectations.

RIVERSIDE STUDIOS

THE rumours about the acquisition of the Riverside Studios, Hammersmith, by the BBC for television have been persistent during the last few weeks, and if negotiations are finalised, valuable stage space and facilities will have been tied up in the face of probable I.T.A. competition. These studios are situated on the

bank of the Thames, near Hammer-smith Bridge, and actually possess a quay where barges can be moored. It comprises two main stages 105ft. x 75ft. and 80ft. x 60ft., a musical scoring stage large enough to hold a symphony orchestra, excellent plaster, carpenters and other workshops, theatres and dressing-room accommodation. The sound recording installation by R.C.A. is first-class, comprising several optical and magnetic recorders of the latest type. Mitchell and Newall cameras and Mole-Richardson lighting are used, together with back-projection and other devices for trick photography. There is a 250kw. motor generator set for providing direct current for arc lights plus alternating current for "inkies." The Riverside Studios were originally the warehouse of a large motor accessory firm. It became a film studio in about 1933, when it was run by the Triumph Film Company. Two or three years later it was taken over by the Twickenham Studios, after a fire at the latter had destroyed one of its stages. But, it was not until

after the war that films of any real consequence were made at Riverside, the most successful being "The Seventh Veil" and "Reluctant Heroes." It is interesting to note that this studio plant, originally improvised out of a warehouse, was so well planned in the structural alterations of 1933 as to lend itself readily to additions to plant and premises, without becoming a rabbit warren like Lime Grove.

FILMING TV SHOWS IN U.S.A.

THE proportion of live TV shows in America continues to decrease. Photographing and recording of all special features and plays is now the rule rather than the exception and the standard half-hour television feature is shot in two or three days. The McCadden Corporation, which makes the weekly Burns and Allen show as well as the Jack Benny and Bing Crosby TV shows, has evolved a system of working which enables one of these programmes to be completely photographed and

recorded in one eight-hour day. Phil Tannura, a lighting cameraman who photographed many British films some years ago, has developed a system of lighting, coupled with a layout of sets on one stage and the introduction of specialised equipment, which makes this possible. A new type of lighting unit, known as the "cone" is used. This consists of a large cone-shaped housing in which is mounted a 5 kw. incandescent lamp behind a baffle which reflects the light back toward the white reflecting surface of the interior of the lamp. This surface is a soft matt white and the indirect light so reflected gives a non-shadow producing quality similar to natural north light. This reduces troublesome shadows from one artiste to another, from set props and from suspended microphones. Other special gadgets include a silent all-ways camera dolly and variable resistance controls of all banks of lamps. The lighting can be varied during lengthy shots. Some of these ideas will shortly be in use over here.

A Diamond Aerial

By R. Pinkney

THE usual requirements of a television aerial are that it is easy to make, easy to erect, gives satisfactory results and does not cost too much. I think the Diamond fulfils all these.

Its performance is better than either the "H" or the "X" and it is more directional.


It has an impedance of about 70 ohms and matches into the ordinary coaxial cable.

Constructional Details

Rods can be used to make this aerial, but I found flexible, multi-strand copper aerial wire of the type used for ordinary broadcast reception, twisted double, was easier to work with and gave adequate bandwidth. One quarter sound wavelength from the top of a wood or metal pole a spreader, one half sound wavelength long, is secured by its centre at right angles to the pole. A piece of wood, 1in. wide by $\frac{1}{2}$ in. thick, should do as it has to take little strain. A metal spreader can be used.

At the dipole end, which is the end pointing towards the television station, fasten a small block of Paxolin about 2in. square with a hole at the top and bottom for securing the inner ends of the dipole. From the top hole, one half of the dipole, one quarter vision wavelength long, is stretched towards the top of the pole, where it is secured to an insulator which in turn is secured to the top of the pole by a piece of strong cord. The lower half of the dipole stretches from the block towards a point one quarter sound wavelength below the centre of the spreader and secured to the pole by insulator and cord. The inner core of the feeder is connected to the top half

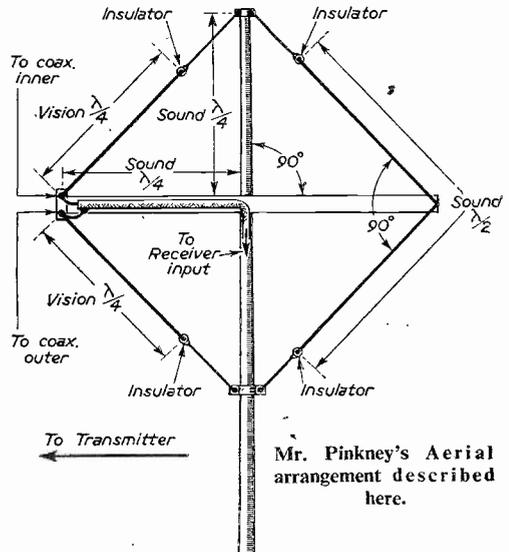
of the dipole at the insulating block and the outer screen to the lower half. The feeder is taken along the spreader to the centre and then down the pole.



The copper wire reflector is taken from an insulator at the top of the pole over the rear end of the spreader and secured to an insulator at the same point as the lower end of the dipole cord. The reflector should be one half sound wavelength long. The whole thing should now be diamond shaped.

There is very little weight in the aerial itself and only a lightweight pole is required.

The SIMPLEX

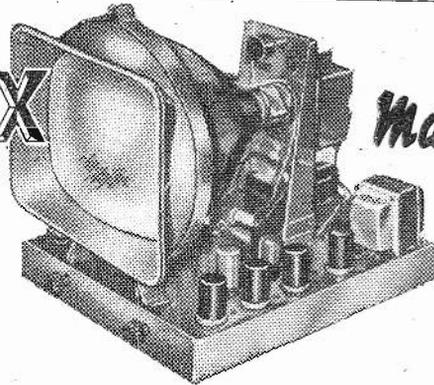

Magnetic Model

WHEN we published the first details of our £16 television receiver—the Simplex—we stated that a long-term view had been taken with the design so that the televisor could be converted from the smaller electrostatic C.R.T. to a larger tube at a later stage.

The reason for this is that many home constructors get their first introduction to television by building a television receiver using one of the small ex-Govt. cathode-ray tubes, and after a year or so feel they would like to change over to a larger tube.

The original intention was to produce the data for the conversion at a rather later date; however, we have received so many requests for the data that the design was put on hand and is therefore now published at a much earlier date than was originally anticipated.

Those Simplex owners who do not wish to change at the present time can keep the data for use at a later date.

There are many problems in such a conversion; it often means the wholesale scrapping of the original timebase. We have avoided this and but for a few modifications the Simplex timebase has been retained, the outputs being fed into an amplifying stage for direct application to the C.R.T.

Two extra valves only are required, and one rectifier.

Design Features

It should be emphasised at the outset that this is not a purely magnetic receiver; it is *conversion data* to change from an electrostatic tube to a magnetic tube and, therefore, contains several features which would not normally be found in a televisor designed originally for magnetic working. As an example, instead of having one main power supply there are two supplies and this has been arranged so that the present Simplex owner does not have to scrap his existing power supply.

We have retained as many of the original parts as possible. There are bound to be some items which are used in electrostatic working which are not suitable for magnetic working such as the C.R.T. holder, bleeder network, E.H.T. condensers, etc., but most of the existing timebase has been retained.

The method of working in stages has been adhered to. In order to cater for those who will be converting their televisors and also those who will be building this model directly, two shopping lists have been prepared. The first list is for the additional items required for the conversion of the existing timebase, and the second is for the total number of items required for timebase and C.R.T. network.

DETAILS FOR CONVERTING THE SIMPLEX TO MAGNETIC TUBE

The concluding article will appear next month

Another important feature of the design is that we have adhered to standard components which are available in the normal market. It would have been possible to reduce the overall cost by employing some of those surplus parts which become available from time to time such as line output transformers, etc., but as such supplies are very irregular their use has not been contemplated.

The new circuit can be used with either a 12in. or 9in. C.R.T. There are available on the market from time to time cathode-ray tubes with cathode-heater shorts. These tubes have had some use but generally have a fairly useful life left, but due to short circuits developing between cathode and heater they have become unworkable in many commercially designed receivers. By employing grid modulation these tubes can be used in the new Simplex model without recourse to special low-capacity heater transformers. A considerable saving can be effected in cost by this method.

If the constructor should purchase such a tube it is advisable to test it immediately. Some of them have a rather low emission and are useless. Do not buy a tube which has been "reconditioned" as the life

COMPLETE LIST OF CONDENSERS, RESISTANCES, ETC.

(This list comprises those items of the new model which are not listed in the original data in the April, 1954, issue of "Practical Television.")

Resistances :

All $\frac{1}{2}$ watt unless stated otherwise
 RM1—2M Ω
 RM2—1M Ω
 RM3—100 K Ω 2w.
 RM4—330 ohms 1w.
 RM5—47K Ω 1w.
 RM6—220 ohms
 RM7—330 K Ω
 RM8—4.7 K Ω 2w.
 RM9—100 ohms 1w.
 RM10—47 K Ω 1w.
 RM11—15 K Ω 1w.
 RM12—470 K Ω
 RM13—330 K Ω
 RM14—100 K Ω
 RM15—5 K Ω 10w.
 RM16—2.2 K Ω 2w.
 RM17—470 ohms.

Condensers :

All 350 v. wkg. unless stated otherwise
 CM1—.005 μ F
 CM2—100 pF
 CM3—.002 μ F
 CM4—.1 μ F
 CM5—.1 μ F
 CM6—25 μ F 25v.
 CM7—.01 μ F
 CM8—.001 μ F 6-7 Kv.
 CM9—.01 μ F
 CM10—.02 μ F
 CM11—25 μ F 50 v. wkg.
 CM12—4 μ F
 CM13—32 μ F tubular
 CM14a 8 μ F } both
 CM14b 16 μ F } 450 v.
 } tubular
 CM15—.01 μ F 450 v.
 CM16—.01 μ F 450 v.
 CM17—.002 μ F

Potentiometers (pre-set)

VRM1—2 K w.w.
 VRM2—1 M
 VRM3—250 K
 VRM4—2 K w.w.
 VRM5—25 K

Valves :

V14—EL38
 V15—6V6
 V16—5U4G

cannot be expected to be more than a few months. (We are not referring here, of course, to the scheme of the English Electric Company which have an exchange service for their 16in. tubes.)

In conversion design there are two rather important problems which have to be considered. The first is that the usual Miller Integrator and Transistron oscillator such as has been used in the original Simplex is not suitable for direct amplification in the line timebase as it is negative-going on scan. A positive-going sawtooth waveform is required for correct operation of the line amplifier and a phase reversal stage must therefore be inserted. This is accomplished by employing the original V13 line amplifier as a phase reversal stage.

The problem does not arise in the frame circuit as the flyback period is so very much longer and the extremely high flyback voltages generated in the line circuit are absent in the frame amplifier. Direct amplification can therefore be used providing the biasing conditions of the amplifier are adjusted accordingly.

In the frame circuit the main problem is that at the low frequency for frame operation the Miller circuit does not have the excellent linearity which it possesses at the higher line frequency; further, the flyback is inclined to be rather prolonged and this is likely to affect the few top lines of the picture.

A simple solution to the problem would be to redesign the oscillator as a blocking oscillator but as this would entail drastic alterations in the original design and the scrapping of some useful components it was decided to adhere to the original scheme and to apply correction in the following amplifier circuit.

Under working conditions the linearity is quite satisfactory; the clock in the tuning-in signal can be made perfectly round and the only criticism is that unless the linearity controls are very carefully

set there is a tendency for the top three or four lines to fold over.

We mentioned earlier that the new design caters for both those who wish to convert their existing televisions and for those who wish to build the present version from scratch. The method to be followed in each case follows.

To convert the original Simplex to the new one obtain the new components. Convert the existing timebase by following the details given in the paragraphs under the heading "Conversion Details." After this, parts for Stage IV (M), V (M) and VI (M) should be purchased and the various stages completed. Each stage can be built separately and the parts for that stage bought separately.

To build the magnetic Simplex version directly the original Simplex data will be required. Stage I is built, followed by Stage II (M), III (M), IV (M), V (M) and VI (M). The original Stages 2, 3 and 4 are not built.

It will be noted that Stages IV (M), V (M) and VI (M) are common to both constructions.

Circuit Description

The circuit diagram of the timebase amplifiers and C.R.T. network is given in Fig. 1: The vision and sound sections have been given previously in the original Simplex, but in order to assist constructors a complete circuit diagram of the new version has been prepared.

The output from the frame oscillator is fed into V15 and the coupling condenser and the resistance network RM12, VRM2, RM13 add correction. Further correction is obtained from the feedback circuit via CM10, VRM3 and RM14. VRM being made variable allows control over linearity to be

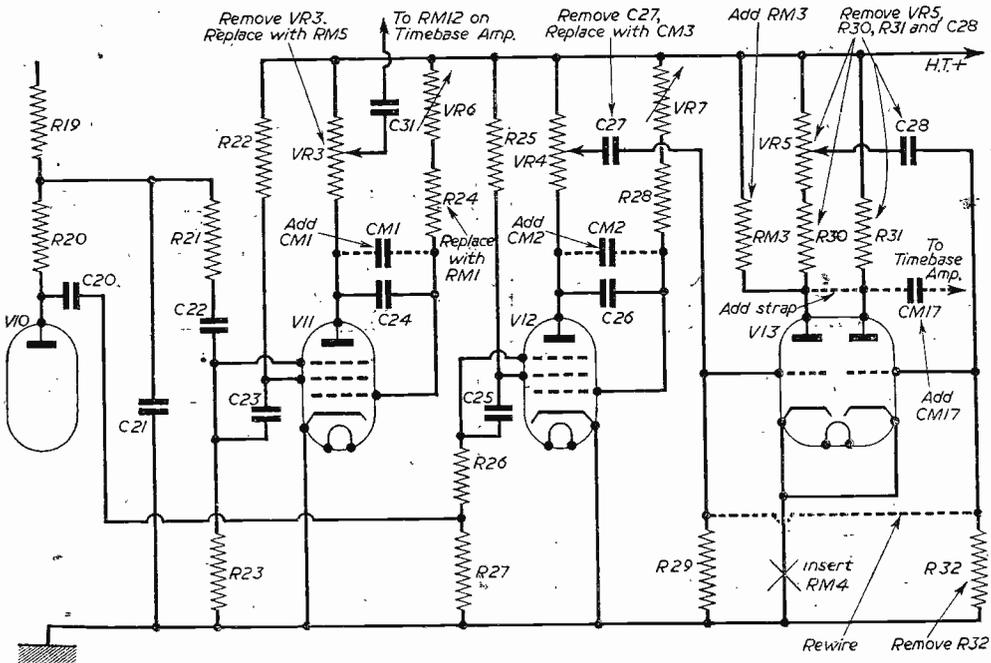


Fig. 2.— Modifying the existing timebase: R28 is replaced by RM2.

exercised and this control will be found to affect mainly the top portion of the picture.

It will be noted that the biasing resistor of the 6V6 frame amplifier is made variable; this ensures that the valve works over the correct portion of its curve and it will be found that the control varies the linearity at the bottom of the picture.

Output from the frame amplifier is fed to the frame output transformer via an R.C. network comprising RM15 and CM13. The use of this method applies a certain amount of correction to the waveform and also obviates having to feed D.C. through the primary of the coupling transformer.

CM13 should be of the tubular type (Hunts or Drilytic) and the can must *not* be earthed.

Damping of the frame flyback is accomplished by RM17.

The Line Amplifier

V13 of the original circuit is converted to a phase reversal stage and its output is fed into the line amplifier an EL38.

Sufficient drive is obtained to overscan a 12in. tube with adequate E.H.T. The width of the scan is controlled by the variable inductance in series with the scan coils, the advantage being that the width becomes separated from the main drive and does not therefore affect E.H.T.

Linearity at the extreme left is controlled by VRM1 and CM7.

The original width control has been left and it becomes a further linearity control.

An efficiency diode circuit using a metal rectifier RM6 has been included to provide additional power to the scan and to ensure efficient absorption of the flyback.

E.H.T. is derived from the step-up of voltages

from the flyback pulse in the overwinding of the transformer. The voltage is rectified by two K3/40 rectifiers in series, which were used in the original E.H.T. circuit.

Note that it is important to connect CM6, MR6 and the width control correctly and care must be taken to ensure that the Z and Y terminal connections are as given in the diagram.

Although the tube is grid modulated the coupling is obtained from the phase splitter V9 of the original timebase, and it is therefore practically at earth potential. The difficulties associated with providing sufficient positive voltage on the cathode for adequate control of brilliance is thereby avoided, and the simple potential divider RM10, VRM5 and RM11 is sufficient.

Power Supply

A standard type of transformer has been employed in an orthodox full-wave rectifying circuit. It was considered that the use of the transformer was justified so that the difficulties associated with a "live" chassis could be avoided.

One important feature is the provision of a filter network in the mains supply.

The object of the network is two-fold. Firstly, it assists in keeping mains-borne interference from the television, and equally important it prevents re-radiation of the line frequency via the mains.

This is the first time, to our knowledge, that such an arrangement has been incorporated in a home-constructed television and we hope that other designers will follow our lead. Television receiver owners suffer appreciably from unsuppressed electrical apparatus and car ignition circuits and appeals are made from time to time for owners to fit suppression devices. It is only fair that we in turn suppress our

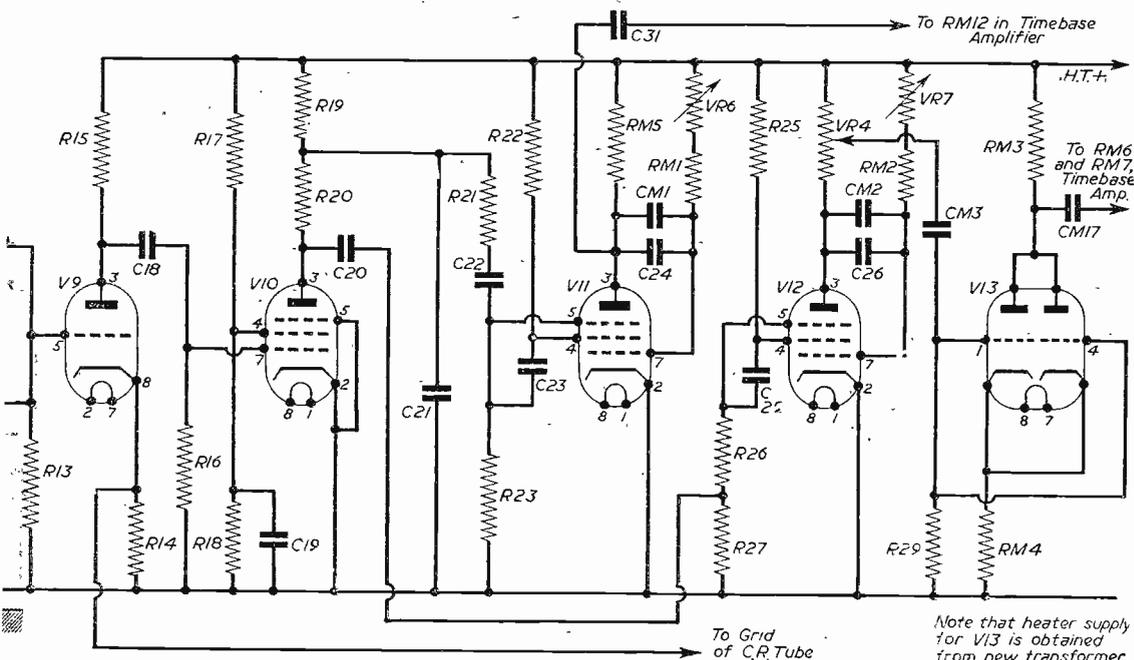


Fig. 3.—The complete existing timebase as modified Stage II (M).

own televisions to prevent re-radiation. In many localities it has become impossible to listen to the light programme on the long wavelength due to the whistle produced from television receivers.

A great deal of the radiation takes place over the mains and the use of the suppression circuit effectively reduces this source. When the television is completed it should be put into a cabinet and we recommend that the sides, top and bottom and back of the cabinet be covered with copper mesh, which is earthed.

It is suggested that a three-pin plug and socket be used even if the normal household sockets are two-pin, so that effective earthing can be made.

CONVERSION DETAILS

This section should be studied by those who are converting the original model into the magnetic. Those who are building the latter version directly should build Stage I as given in the original data

and then study Stage II (M) and Stage III (M) given later.

Mechanical Arrangements

The following items should be removed from the chassis in the order mentioned :

Front C.R.T. mounting; rear C.R.T. mounting with R40, 41; MR1, 2 and C34; R38, 39, C39; C29, 30, 31 (C31 can be used in its original circuit position but placed under the chassis later); VR8, 9, R34, 35, 33, 36, 37, 32, 30, 31, C28; C27 is replaced with an 0.002 μ F.

On the rear of the chassis there should now be the original width control, the line-hold control, the frame-hold control, and on its panel above the brilliance and focus controls; these latter can now be removed.

The timebase should be almost complete (except for the slight modifications to follow) up to the grid of V13.

(To be continued.)


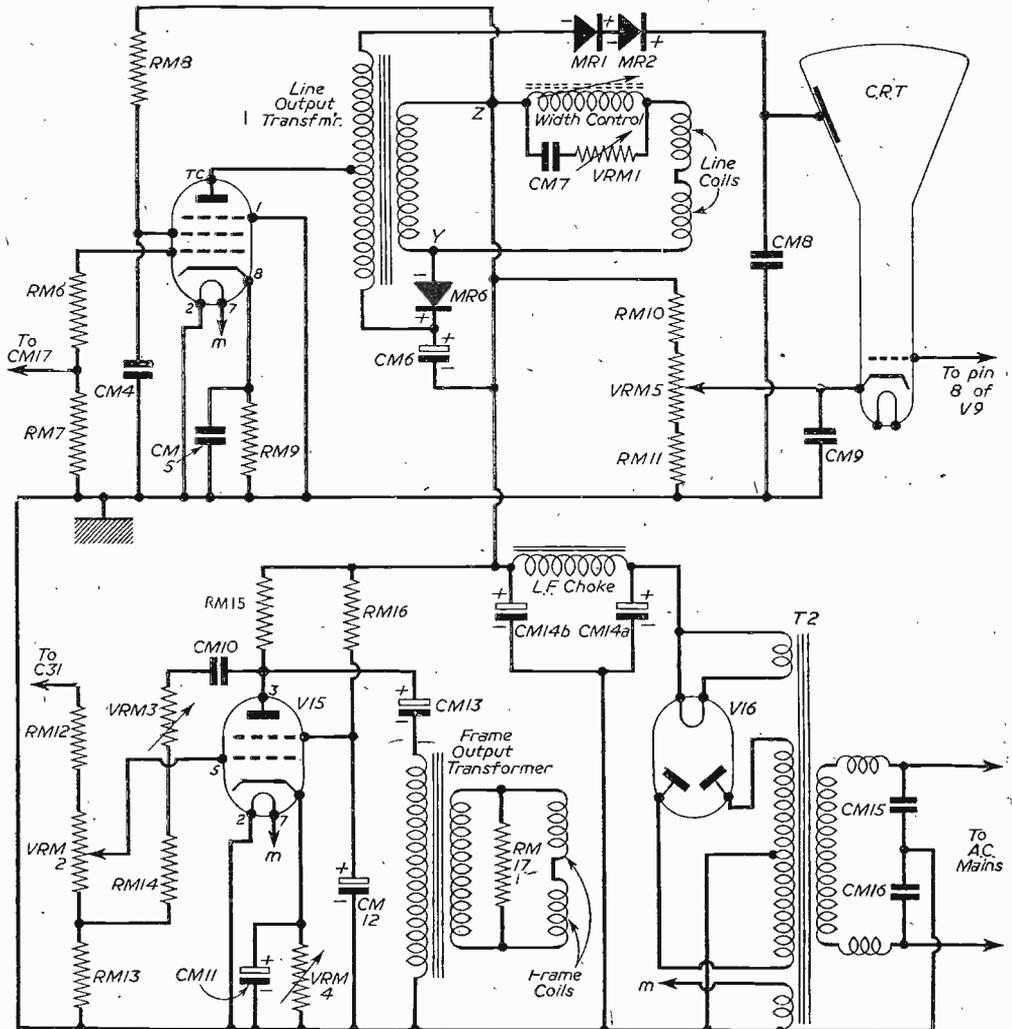


Fig. 1.—The timebase amplifier.

Fault Symptoms

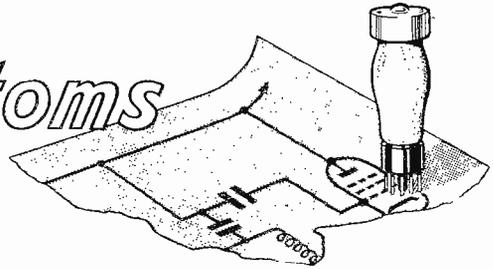

THE CAUSES OF COMMON FAULTS, AND METHODS OF CORRECTION

By Gordon J. King, A.M.I.P.R.E.

(Continued from page 201, October issue.)

The Vision Interference Limiter

FIGURE 67 depicts a typical vision interference limiter—or spotter—circuit. This in itself is quite simple and straightforward to follow, for essentially it boils down to a diode (sometimes a crystal diode is used) the potentials on which are arranged to hold it just off conduction at the potential corresponding to a peak-white picture signal. Any spurious impulsive signals exceeding this level are, therefore, suppressed, or partially damped, by reason of the diode becoming conductive.

The potential at the diode cathode follows the pattern of the vision signal since this electrode is in direct connection with the cathode of the picture-tube. We must remember, of course, that the picture signal voltage here is working in a less positive direction; this means that the cathode potential falls less positive corresponding to the white content of the picture.

The anode of the diode is maintained at a pre-determined positive potential, and, so far as the circuit of Fig. 67 is concerned, this is achieved by the potential divider comprising R1 and R2. Under normal operating conditions the diode cathode is slightly more positive than the anode, and when the fluctuating potential at the cathode falls to that representing a peak-white picture element, the potential at the cathode equals that at the anode.

Now impulsive interference—such as that created by the ignition system of petrol engines—picked-up and accepted by the receiver in the usual way takes the form of a sharp pulse which sits on the top of the vision signal waveform as illustrated by Fig. 67 (b). Clearly, then, since an interference pulse of this nature causes the diode cathode potential to fall below that induced by a peak-white picture signal, the cathode becomes less positive than the anode; or, in other words, during a burst of interference the anode of the diode is more positive than the cathode. This, of course, causes the diode to conduct and limit the interference voltage applied to the picture-tube.

Although we are still looking at the signal applied to the tube from the cathode aspect, we must always bear in mind when considering a transient reduction in tube cathode potential, that the potential from the viewpoint of the tube grid is a mirror image of that at the cathode, but rising—going more positive—in value, instead of falling more negative. Looking at the problem in this light enables us to realise more readily that, without the inclusion of an interference limiter circuit, an interference pulse can drive the tube grid extremely positive. This may result in excessive beam current, coupled with a probable drop in E.H.T. volts, and it is such a combination which provokes the display of the relatively large defocused spots of light on the picture corresponding to the interference pulses.

From this reasoning, therefore, we can better understand why a simple spotter circuit does not eliminate the interference effect completely, but at best reduces the size of the spots and keeps them in focus by reason of preventing the tube grid from swinging any more positive than allowed by a peak-white picture element.

Undesirable Operation of the Vision Interference Limiter

During the normal life of a tube the brilliance of the picture or raster gradually diminishes until a stage is reached when the tube is considered no longer serviceable (see “Dim Picture” symptom). Flyback lines generally become prominent towards the end of

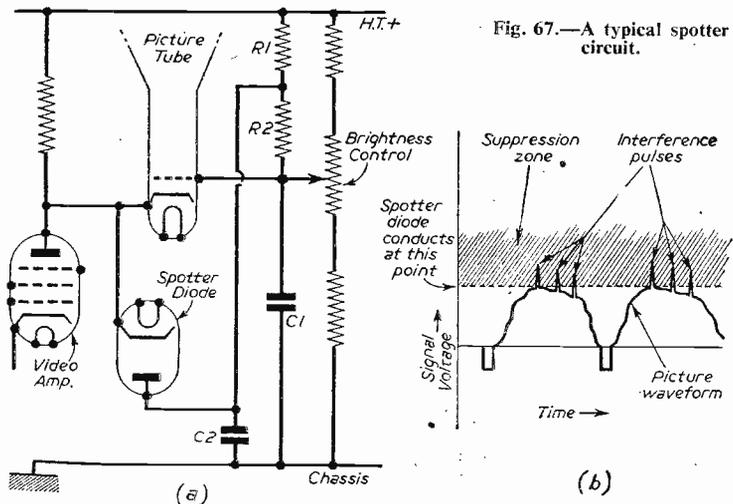


Fig. 67.—A typical spotter circuit.

its useful life, and quite probably it is found that viewing can be done successfully only in total darkness. One is very often tempted, when using a tube in this condition, to exceed the optimum brightness control setting in an endeavour to combat ambient

to the slider of the brightness control, and this means that as the brightness control is advanced, the diode anode will go even more positive, thereby assisting further diode conduction during a potential level corresponding to peak-white picture signals or less.

This reasoning clearly illustrates how the action of the vision interference limiter often exaggerates the symptom of an ageing tube, for since both factors are of a synonymous nature it can readily be seen that the overall effect will possibly be stimulated. When a tube begins to wear in this way, and excessive drive is necessary to resolve an image of viewable brightness, it is often desirable to disconnect the limiter circuit, and let the tube itself perform the limiting function!

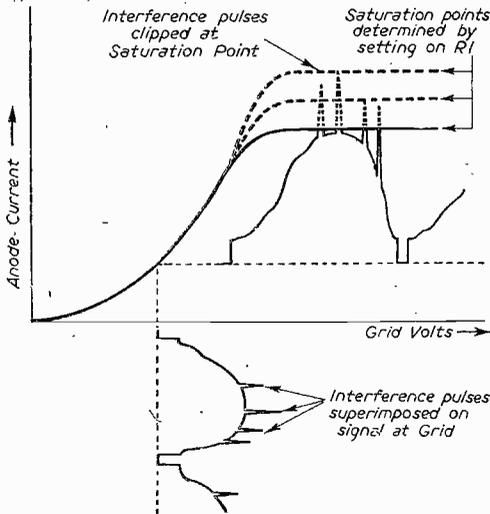


Fig. 68.—Grid volts—anode current characteristics of video amplifier in Fig. 69. Note how the valve is run into saturation current during interference pulses above peak-white, while the peak-white signal is just below the saturation level.

illumination falling on the screen. This procedure is, of course, incorrect, but since the brightness of the picture reduces very gradually a progressively advanced setting on the brightness control is usually unwittingly performed. Apart from exaggerating the display of flyback lines, defocusing on whites and the symptoms of poor E.H.T. regulation become apparent, due to the increased load across the E.H.T. system. As revealed by our Query Service, many experimenters are under the impression that such effects are symptomatic of E.H.T. circuit defects. They might be so in certain cases, though in a large number of instances tube replacement has solved all the problems!

In order to maintain correct contrast balance on a worn tube, the increase in brightness control setting demands more tube drive, or a higher contrast setting, and as the tube continues to decline in brightness a point is reached when it is severely over-driven. This is often indicated by the picture appearing "flat," or—in severe cases—in negative form. This undesirable symptom is often aggravated—when a tube is dying—due to the vision interference limiter diode conducting during a peak-white signal level. Premature diode conduction is, of course, provoked by the heavy outbalancing video signal applied to the tube and diode cathodes, and is often little alleviated, under this condition, by retarding the limiter control, if one happens to be fitted.

Fixed limiting is shown in the circuit of Fig. 67, but sometimes R2 is made adjustable, and labelled "limiter control"; this allows—within a fixed limit—an adjustable bias potential to be applied to the diode anode, and thus determines its conduction level.

It will also be seen that the resistor R2 is returned

Limiting in the Video Amplifier

It must always be borne in mind that unless the video amplifier stage is capable of providing the extra drive demanded by a worn tube, the associated valve may give rise to a limiting action, for a state is bound to occur when further drive has little effect on the valve anode current. In the case of a cathode modulated tube, for instance, a positive going signal is applied from the vision detector to the signal-grid of the valve, and if we consider this in relation to the grid-volts/anode-current characteristic (Fig. 68), we can clearly see how an excessive grid signal would readily run the video valve into saturation current during peak-white signal components.

As a form of artifice this is, in fact, used for the purpose of suppressing impulse interferences in

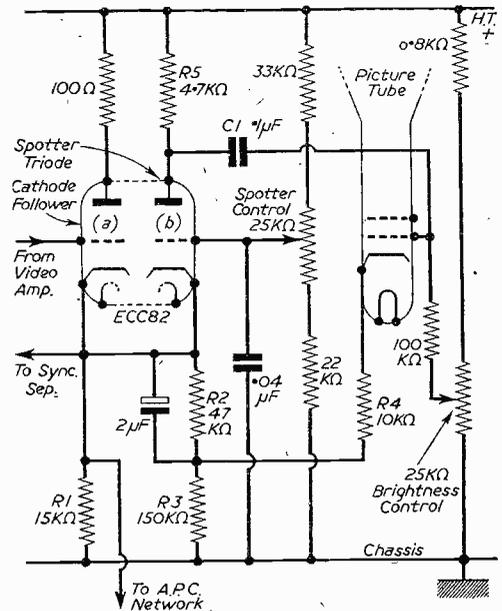


Fig. 70.—Circuit of white spot suppressor as used in the Pye V4 series.

the Philips 1100U series receivers. Fig. 69 depicts the relevant circuit details, from which it will be seen that fundamentally the system relies on the variable potential at the suppressor grid. This potential is picked up between the H.T. line and a negative potential in the frame timebase circuit, and is developed

SPEED UP your SOLDERING

WITH
Wolf
Electric
SOLDERGUNS
AND
SOLDERING IRONS

TYPE 21
TYPE 41
TYPE 31
TYPE 71
TYPE 81
TYPE 22
TYPE 32
TYPE 42

TRIGGER FEED SOLDERGUN

Type No. 51 is designed specially for all assembly operations. Solder is fed automatically with trigger-action and two reels are supplied—one 15 ft. acid-cored and one 15 ft. resin-cored.

Unbeatable from every point of view, well able to withstand hard workshop treatment and ideal for continuous use. Features include rapid constant localised heat—solid sturdy construction—low current consumption—perfect balance—absolute dependability. A type and bit for every purpose from fine instrument to heavy industrial work. Each tool includes 5 feet tough rubber 3-core cable.

Obtainable from all leading tool merchants and factors. Fully descriptive Brochure on request

WOLF ELECTRIC TOOLS LTD · PIONEER WORKS · HANGER LANE · LONDON · W.5
Tel: PERIVALE 5631-4 Branches: BIRMINGHAM · MANCHESTER · LEEDS · BRISTOL · NEWCASTLE · GLASGOW

Osram 912

**a modern high quality
amplifier & reproducer
for the home constructor**

BUILD THIS HIGH QUALITY AMPLIFIER

- Every part specified and readily obtainable from your Radio dealer.
- Every stage in construction clearly explained with step-by-step wiring, in instruction book.
- Rock-like stability in performance — no hum, no microphony, wide frequency response (9 octaves), low harmonic distortion at full power (12 watts) and ensured reliability, with Osram valves specified.
- Full control on frequency characteristics to introduce "art" into listening.
- Unparalleled clarity of both speech and music when used in conjunction with G.E.C. Metal Cone Loud-speaker in octagonal loaded-port cabinet.

Overall frequency response of the complete equipment, comprising L.P. record, specified pick-up, Osram 912 amplifier and G.E.C. Metal Cone Loudspeaker in octagonal loaded-port cabinet.

How to build the Osram 912

A book giving full constructional details is obtainable from your dealer, or by post (3d. extra) from The Osram Valve and Electronics Dept. **PRICE 3/6**

Volume Controls

Midget Bobsman type. Long spindles. Guaranteed 1 year. S. P. Sw. No Sw. 3/- D.P. Sw. 4/6. ALL VALUES.—10,000 ohms to 2 Megohms.

80 ohm CABLE COAX

STANDARD 4 in. diam. Polythene insulated. Grade "A" Not Ex Govt. 8d. yd. COAX PLUGS, 1/2 each. SOCKETS, 1/- each. LINE CONNECTOR, 1/2. OUTLET BOXES, 4/6.

BALANCED TWIN FEEDER per yd. 6d. TWIN SCREENED COAX FEEDER per yd. 1/- j ohms 50 OHM COAX CABLE 8d. per yd. TRIMMERS, Ceramic, 30, 70 pf., 9d.; 100 pf. 150 pf., 1/3; 250 pf., 1/8; 600 pf., 1/9. RESISTORS.—All values: 1/4 w., 15 m., 150 m., 1 k., 2 k., 2 w., 1/-; 1/2 w., 1/2, 2/6.

WIRE-WOUND RESISTORS.—Best Makes Miniature Ceramic Type—5 w., 15 ohms to 4 k., 1/9; 10 w., 20 ohms to 6 k., 2/3; 15 w., 30 ohms to 10 k., 2/9; 5 w. Vitreous, 12 k. to 25 k., 3/-. WIRE-WOUND POTS. 3 WATT. FAMOUS MAKES Pre-Set Min. TV. Type. Standard Size Pots. 2 1/2 in. Knurled Stotted Knob. Spindle. High Grade. All values 25 ohms to 30 k., 3/- ea. 50 k., 4/-. 10 to Carbon Track 50k. to 2 Meg., 3/-. O.P. TRANSFORMERS.—Heavy duty 70 ma., 4/6. Tapped small pentode, 3/9.

L.F. CHOKES 10 h. 65 ma., 5/-; 20 h., 150 ma., 12/6. 15 h. 100 ma., 10/6. LYNX. 3 h. 250 ma., 13/6. SIMPLEX 10 h., 130 ma., 10/6. MAINS TRANS.—Made in our own workshops to high grade specification. Fully inter-leaved and impregnated. Heater Trans., tapped pent., 6-300 v./250 v. 6.3 v. 11 amp., 7/6. 12 v. 75 amp., 7/6. 6.3 v. 3 a., 10/6. 350-0-350, 80 ma., 5.5 v. 4 a., 5 v. 2 a., ditto 300-0-300 ditto 250-0-250, 21/-.

VIEWMASTER, auto type, 35/-. Telexing, 30/-. LYNX, 30/-. CORONET, 30/-. SIMPLEX (modified with 4 v. tap), 35/-. TV AERIALS.—Acerials etc. full range all channels in stock. Indoor loft type Inv. T., 13/6 etc. etc. TYANA.—Midget Soldering Iron, 200/220 v. or 230/250 v., 14/11. Triple Three mod. with detachable bench stand, 19/6. Solon Midget Iron, 19/6. TAG STRIPS.—2 or 3-way, 2d.; 4 or 5-way, 3d.; 7-way, 4d.; 9 or 10-way, 6d.; 28-way, 1/3.

GOODMANS.—Latest Wide Angle Duomagn type. Focus Unit. Verner Focus and adjustable Picture Shift. 35/-. ELAC.—C.R.T. Ion Trap, 2/6. ENAMEL OR T.C. WIRE.—1 lb. 14 to 20 s.w.g., 2/-; 22 to 28 s.w.g., 2/6; 30 to 40 s.w.g., 3/3. XTAL DIODE.—Sensitive G.E.C. type, 3/6. H.R. THONS (S. G. Brown) or H-grade Amer., 15/6 pair.

SIMPLEX TELEVISION

Table listing electronic components and their prices. Includes sections for Stage 1 Vision and Sound, Stage 2 Time Base, Stage 3 Power Supply, and C.R.T. Network. Items include valves, resistors, condensers, potentiometers, and chassis.

Table listing various electronic valves and their prices. Includes sections for New Boxed Values and All Values Guaranteed. Items include 6X5, 6X4, 6X3, 6X2, 6X1, 6Y5, 6Y4, 6Y3, 6Y2, 6Y1, 6E5, 6E4, 6E3, 6E2, 6E1, 6F5, 6F4, 6F3, 6F2, 6F1, 6G5, 6G4, 6G3, 6G2, 6G1, 6H5, 6H4, 6H3, 6H2, 6H1, 6J5, 6J4, 6J3, 6J2, 6J1, 6K5, 6K4, 6K3, 6K2, 6K1, 6L5, 6L4, 6L3, 6L2, 6L1, 6M5, 6M4, 6M3, 6M2, 6M1, 6N5, 6N4, 6N3, 6N2, 6N1, 6O5, 6O4, 6O3, 6O2, 6O1, 6P5, 6P4, 6P3, 6P2, 6P1, 6Q5, 6Q4, 6Q3, 6Q2, 6Q1, 6R5, 6R4, 6R3, 6R2, 6R1, 6S5, 6S4, 6S3, 6S2, 6S1, 6T5, 6T4, 6T3, 6T2, 6T1, 6U5, 6U4, 6U3, 6U2, 6U1, 6V5, 6V4, 6V3, 6V2, 6V1, 6W5, 6W4, 6W3, 6W2, 6W1, 6X5, 6X4, 6X3, 6X2, 6X1, 6Y5, 6Y4, 6Y3, 6Y2, 6Y1, 6Z5, 6Z4, 6Z3, 6Z2, 6Z1.

TV. PRE-AMP.—Channel 1, easily modified to other channels or converter use. Midget chassis 6 in. x 3 in. x 1 1/2 in. Complete with coax. lead, plug and EP42 valve. Brand new (boxed). Listed £3/13/-. Special clearance, 27/8, h/p, 1/6.

P. and P., 6d. £1 orders post free. Lists 3d. ALL TRANS. P. & P. 1/- extra please. T.R.S. RADIO COMPONENTS 178, THE 1665 SPECIALISTS 307, Whitehorse Road, West Croydon.

C.R.T. HEATER ISOLATION TRANSFORMER.

Low leakage winding with 25% sec. boost, 2-10/6; 4 v., 10/6; 6.3 v., 10/6; 12 v., 10/6. BRIMISTONS.—CZ1 3 a., 3/6. CZ2 15 a., 2/6. CONDENSERS.—New stock. .001 mfd., 10 kV, T.C.C., 5/6. 100 pF., 12.5 kV., 9/6. 2 pF. to 500 pF., Micas, 6d.; .001 Mica or Tub. T.C.C. 500 v., .01. Sprague 500 v., .02 N.S.F. 500 v. 1 mfd. 350 v. Micamould Tub. 9d.; Hunts Moldcaul 500 v., .005, .01, 9d.; .05 mfd. and 1 mfd., 1/-; .25 mfd.; 1/6. Tubular 5 mfd., 350 v., 1/9.


SILVER MICA CONDENSERS.—10%, 5 pF. to 500 pF., 1/-; 600 pF. to 3,000 pF., 1/3. DITTO 1%, ex Stock 1.5 pF. to 500 pF., 1/9; 515 pF. to 1,000 pF., 2/-. ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends Can Type, Clips, 3d. ea. 2/450 v. B.E.C. 2/3 16/450 v. Plessey 3/6 4/500 v. Hunts 2/- 60/350 v. T.C.C. 6/6 8/450 v. B.E.C. 2/3 250/350 v. B.E.C. 8/6 8/450 v. T.C.C. 2/9 8+16/450 v. B.E.C. 5/- 8/500 v. Dubilier 2/9 8+16/500 v. Dubilier 5/8 16/600 v. Dubilier 4/- 10+16/450 v. B.E.C. 5/6 8+8/500 v. Dubilier 4/6 8+16/500 v. Dubilier 4/6 32+32/275 v. B.E.C. 4/8 16+16/500 v. Dub. 6/- 32+32/450 v. B.E.C. 6/6 32/500 v. Dubilier 5/- 60+100/350 v. Hunts. 11/6 32+32/350 v. Dub. 5/6 100+200/275 v. B.E.C. 12/6 50/50 v. Plessey 2/-

SPECIALS.—500 mfd. 12 v., 3.0, 1500 mfd. 6 v., 4.6, 6000 mfd. 6 v., 5/6, 1000+1000 mfd. 4 v., 6/6. CENTERLOCK RECTIFIERS.—BILT Type. Fly-back Voltage.—K3/25 2 kV., 4/3; K4/40 3.2 kV., 6/-; K5/45 3.6 kV., 6/6; K3/50 4 kV., 7/3; K3/100 8 kV., 12/6; K4/150 14 kV., 18/-. MAINS TYPE.—RM, 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3, 120 ma., 5/9; RM4, 250 v., 275 ma., 16/-.

KNOBBS, GOLD ENGRAVED.—Walnut or Ivory, 1 1/2 in. diam., 1/6 each. Not engraved, 1/- each. LOUDSPEAKERS P.M., 3 OHM.—3 in. Plessey, 12/6; Goodmans, 4 in. square, 15/6; 5 in., 14/6; 6 in., 16/-; 8 in. R. & A., 17/6; 7 in. Elliptical, 13/6; 10 in. R. & A., 25/-.

SLEEVEING—Various colours, 1, 2 min., 2d.; 3, 4 min., 3d. yd.; 6 min., 5d. yd. TOGGLE SWITCHES EX-GOV'T.—On-Off, 9d. Brim Mica solder, 60/40. 16 g. or 18 g., 4d. yd., 5/8 lb.; PVC Connecting wire, 10 colours, Single or Stranded 2d. yd. V.HOLDERS.—Pax: 10, 4d.; EF50, EA50, 6d.; B12A CRT, 1/3. Moulded: 10, 6d.; B7G, 9d.; with screening can, 1/6; B8A, B8G, B9A, 1/-; Ceramic: EF50, B7G, 1/-. All English, 3, 7, 9 pin and U.S.A. UX types, 1/-; VCR97 moulded holders, 2/6. ALADDIN FORMERS and core, 1 in., 8d.; 3 in., 10d.

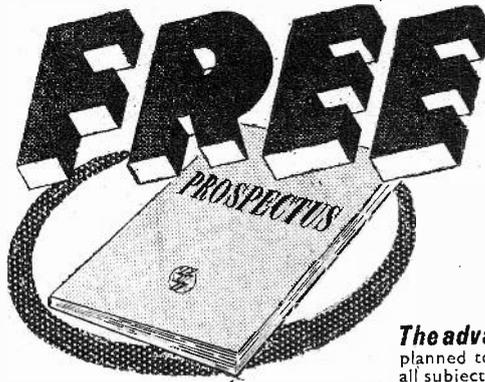

POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME City and Guilds Grouped Certificates in Telecommunications: A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY. COURSES WITH EQUIPMENT. With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Equipment supplied upon enrolment and remains your property. Courses from 15/- per month

POST THIS COUPON TODAY. Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 138K, 43 Grove Park Road, London, W.4.

EMI INSTITUTES The only Postal College which is part of a world-wide Industrial Organisation.

NAME _____ ADDRESS _____ SUBJECT(S) OF INTEREST _____

sound output valve control grid, and an increasing magnitude of sound emits from the loudspeaker. Not so well known, however, is the fact that the contrast control performs a very similar function so far as the vision, or video, signal is concerned. As this control is turned from minimum towards maximum so an increasing video signal is applied to the picture-tube. This, of course, creates a greater ratio of voltage change represented by picture signals between black and peak-white, and in this way has a direct bearing on the contrast (black:white) ratio of the picture.

It is usual practice to position the volume control so that it provides variable attenuation to the sound signal *after* it has been demodulated by the detector. From the vision aspect, only one or two manufacturers adopt this scheme; mainly, the video drive is controlled through the medium of a variable R.F. or I.F. attenuator. This latter method renders circuit design less critical in maintaining a low level of frequency distortion unaffected by the setting of the contrast control.

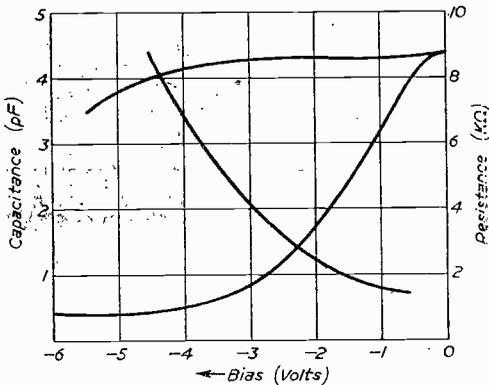


Fig. 71. — Curves (a) and (b) respectively show how the input capacitance and resistance change with grid bias potential. Curve (c) shows how the capacitance change is reduced when both control and suppressor grids are biased.

It is accepted practice to provide a means of altering the bias potential on the R.F. and/or I.F. valves, and in this way institute variable gain over the associated stages. Owing to the fact that a variation in control grid potential also provokes a variation in the valve's input capacitance and resistance, it is essential to arrange the circuit in such a way as to provide a sufficient degree of attenuation without severely modifying the circuit constants.

For let it be remembered that the input capacitance of an R.F. or I.F. amplifier valve represents a large proportion of the grid-circuit tuning capacitance, which, if happened to alter while adjustments were being made to the picture contrast, would obviously present a very undesirable feature.

Furthermore, the valve's input resistance is a contributory constant to the tuned-circuit damping and has a marked controlling effect on the bandwidth of the circuit associated with the valve. It would certainly be most disturbing if, apart from an alteration in picture definition, certain tuned circuits went out of alignment every time the contrast control was adjusted!

Fortunately it is quite a straightforward matter to reduce these undesirable effects simply by arranging the contrast circuit to bias negative both the control

and suppressor grids. This artifice will not severely modify the desirable change in the valve's mutual-conductance (a factor associated with gain), but it will reduce drastically the change in input capacitance.

This is brought to light in Fig. 71 which shows at curve (a) the change of control-grid capacitance and curve (b) the change of input resistance with bias. Curve (c) illustrates how the change in capacitance is reduced when both control and suppressor grids are biased.

In practice it is found that the suppressor grid needs approximately 12 times as much bias as the control grid. This, again, is readily catered for as will be realised by studying the typical contrast control circuit at Fig. 72. Here the variable resistor (contrast control) R1 passes the cathode current of the valve and thus gives rise to a voltage drop—making the cathode positive with respect to chassis—according to the current and resistance values.

This volts drop is applied across the potential divider R2 R3, the junction of which is in direct contact with the control grid through L1. Now, since the suppressor grid (grid 3) of the valve is returned direct to chassis, the full voltage (VR1) existing across R1 will bias grid 3 negatively (this is so because the cathode of the valve is VR1 positive with respect to grid 3, which, of course, is exactly the same thing as grid 3 being VR1 negative with respect to cathode). The negative potential at the control grid (grid 1) is something less than VR1,

depending on the ratio $\frac{R2}{R3}$. The precise value being equivalent to $\frac{R3 \times VR1}{R3 \times R2}$.

Control of a single valve does not generally permit sufficient range of contrast adjustment, and for this reason it is customary to control 2, or sometimes 3, stages. Even so, the inclusion of an aerial attenuator is often demanded in areas of high signal strength.

Some sets also embody an independent gain control—generally known as a sensitivity control. Such a facility may be found to obviate the need of an aerial attenuator, that is provided it is possible to achieve a picture of correct contrast ratio by adjusting the sensitivity control when the contrast control is approximately two-thirds on—if, under this condition, the sensitivity control is fully off, then an aerial attenuator should be used.

Another point worth mentioning here, and one which often provokes the TV owner to contact our Query Department, is that contrast control adjustment—on certain sets—will also affect the volume of sound. The same applies so far as sensitivity control adjustment is concerned. This is quite normal and should cause no alarm; it simply means that the contrast control operates the gain of a stage that is common to both sound and vision.

(To be continued.)

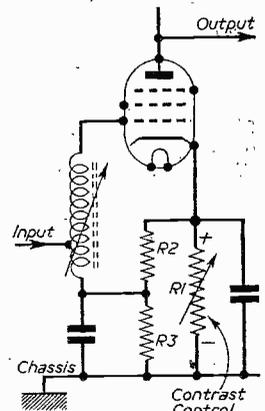


Fig. 72.—A typical contrast control circuit.

ALPHA VALVES

GUARANTEED NEW AND BOXED
MAJORITY IN MAKERS' CARTONS

1C5GT	8/- 6P6M	8/673	10/- 33W4	10/- SP220	6/9
1FD9	9/- 6F8G	7/- 177	8/- 33Z4GT	8/6 TP26	9/-
1L4	7/6 6P15	11/680	8/6 30L8GT	8/6 U10	9/-
1LD5	6/9 6C6G	6/6807	7/6 AC/P	6/9 C16	15/-
1R3	7/6 6H6	3/6 81D2	2/9 AC6/PEN	6/6 U17	10/6
1S4	7/6 6J5G	5/- 9001	5/6 ATP4	6/0 U22	8/-
1R5	7/6 6J5GT	5/6 9002	5/6 CV71	1/- U25	14/6
1T4	7/6 6J3M	6/6 9003	5/6 CV73	1/0 U81	10/-
1U5	8/- 6J6	8/- 9004	6/6 CV28	7/6 U281	16/6
2X2	5/- 6J7G	8/6 9006	6/6 DH7M	10/- U403	10/-
3A4	8/- 6K6GT	6/6 954	2/- EB41	11/- U801	14/6
3Q4	9/- 6K7G	6/6 955	4/9 EB41	11/- U6	10/-
3Q45	10/- 6K7GT	6/6 956	3/6 EBF80	11/6 UAF42	12/-
3D6	5/- 6K7M	6/6 10P1	9/- EB41	9/- UB41	9/-
3S4	8/6 6K8G	8/6 10LD11	10/- ECH33	12/6 UB41	11/-
3V4	8/- 6K8GT	9/6 10P13	11/6 ECH35	12/6 CH42	11/-
4D1	3/- 6L6G	9/- 10P14	10/6 ECH42	10/6 VR53	6/6
42	8/- 6L7M	7/6 12A6	6/6 ECL80	11/6 VR34	2/-
5R4	9/6 6L8	11/- 12A85	11/6 EP41	10/- VR55	7/6
5U4	8/6 6N7	7/6 12A77	9/- EP80	13/6 VR56	6/6
5Y3GT	8/6 6Q7G	9/- 12A77	6/6 EL2	12/6 VR37	8/-
5Z3	8/6 6Q7GT	9/- 12AX7	10/- EL31	10/6 VR65	3/6
5Z4G	8/6 6R7G	8/- 12C8	8/- EL35	10/6 VR65A	3/6
6A5G	9/6 6S47GT	8/- 12D16	5/- EL41	11/6 VR66	3/6
6AC7	6/6 6S67	7/6 12E75	6/- EL42	11/6 VR91	6/-
6A45	7/6 6S87	6/6 12K7	9/- EB41	9/- VR31	8/-
6A5	9/- 6S47GT	8/- 12K8GT	9/- EB51	13/6 VR92	2/-
6A55	9/- 6S47GT	6/3 12Q7GT	9/- EB40	10/- VR105/30	9/-
6A57	7/6 6S18	8/- 12SC7	7/6 EB41	11/- VR116	4/-
6AM5	7/6 6S87GT	9/- 12SH7	5/6 EI149	2/- VR119	4/-
6AM6	7/6 6S87	9/- 12S47	8/6 FN4500	10/- VR123	6/6
6AQ5	8/6 6S87	8/- 12SK7	6/6 H109	8/- VR136	7/-
6AT6	6/- 6S77	7/6 12SL7	9/- H43	7/9 VR137	6/3
6B4	6/- 6UGG	8/6 12SQ7	8/6 KTS2	12/- VR130/30	9/-
6B9G	4/- 6U7G	9/- 12R47	7/6 H132DD	7/6 VP23	8/-
6B46	8/- 6V9G	7/6 29D1	10/6 PEN46	8/6 VT52	8/-
6B9E	8/- 6V9GT	7/6 29D2	12/6 PEN220A	4/- VT501	8/6
6BR7	9/6 6X4	8/- 20P1	15/- PLS1	13/6 VU39	8/6
6BW6	8/6 6X3GT	7/9 25A6G	9/- PLS2	11/6 VU64	8/6
6C4	8/- 7B7	8/6 25L6GT	8/6 PLS3	13/- VU111	3/6
6C5GT	7/6 7C5	8/6 25V4GT	12/- PM12M	10/- VU120A	3/-
6C9	6/6 7C6	8/6 25V5	8/- PY30	11/- W77	8/6
6C9	8/- 7H7	8/6 25V3G	11/- W81	11/6 W1	10/-
6A'D6G	15/- 7Q7	8/- 25Z4G	9/- PY2	10/6 X18	9/-
6D3	7/6 7R7	8/6 25Z5	9/- PX25	15/- X65	10/-
6D8	7/3 7S7	8/6 25Z6GT	8/6 QP21	7/6 X66	11/6
6F6G	7/6 7Y4	8/6 35L6GT	8/9 8128	8/6 Y63	9/-

TRANSFORMERS FOR BATTERY CHARGERS

230 v. Input Tapped 6-12 v. 1 amp.	13/6 each
230 v. Input Tapped 6-12 v. 3 amp.	18/- each
Both with tap on Primary for 2.5 v. Pilot light	

MAINS TRANSFORMERS 3 WAY MOUNTING TYPE

MT1	
Primary : 200-220-240 v.	
Secondaries : 275-0-275 v. 80 M/A 0-6.3 v. 4 amp. 0.5 v. 2 amp.	
Both tapped at 4 v.	17/6 each
MT2	
Primary : 200-220-240 v.	
Secondaries : 350-0-350 v. 80 M/A 0-6.3 v. 4 amp. 0.5 v. 2 amp.	
Both tapped at 4 v.	17/6 each
MT3	
Primary : 200-220-240 v.	
Secondary : 30 v. 2 amps. Taps at 3 v., 4 v., 3 v., 6 v., 3 v., 9 v., 14 v., 12 v., 15 v., 18 v., 20 v., 24 v.	17/6 each

A FEW ONLY
Collaro AC37 Gramophone motors. Suitable for 100/125 v. 200/250 v. Governor controlled with turntable chrome edge covered with Blue cloth. 50/- each. Post 2/6.

AERIAL RODS

Copper Plated Tubular Rods 12in. long ... 3d. each
Will Plug into one another to make any length Rod Aerials.

TELEROD AERIALS

Indoor TV Aerials Complete with Co-Axial Lead for Kirk-o-Shotts frequency. Price 29/6
Our Price ... 19/11 each

BALL DRIVES

Epicyclic Friction Drive Ratio 8-1 ... 1/6 each
Epicyclic Friction Drive with Brass Drum. For use with Steel Dial.
Drive Wire ... 1/9 each

WIRE WOUND RESISTORS

Available in the following values: 25Ω, 50Ω, 100Ω, 150Ω, 200Ω, 250Ω, 300Ω, 500Ω, 1,000Ω, 1,500Ω, 2,000Ω, 2,500Ω, 3,500Ω, 5,000Ω, 6,800Ω, 10,000Ω. Tolerance + 10%. Ratings 3 watt 1 1/2 ea., 10 watt 1/3 ea., 15 watt 1/9 ea.

FILAMENT TRANSFORMER

Primary 200/250v. Secondary 6.3 volt 1.5 amps./tapped at 4 v. and 2 v. 7/6 ea.
Mallory 1 mid. 600 v. Condensers. 1/- ea.
Pentode Output Transformer, 2/9 ea.

HEATER TRANSFORMERS

230 v. Input	2 volt .5 amp.	4/6
230 v. Input	2 volt 3.0 amp.	7/9
230 v. Input	4 volt 1.5 amp.	5/-
230 v. Input	4 volt 3.0 amp.	10/-
230 v. Input	5 volt 2.0 amp.	10/-
230 v. Input	6.3 volt .5 amp.	5/-
230 v. Input	6.3 volt 1.5 amp.	6/-
230 v. Input	6.3 volt 3.0 amp.	9/-
230 v. Input	12 volt .75 amp.	5/-

OUTPUT TRANSFORMERS

Multi Ratio suitable for all ordinary receivers giving six single ratios ... 6/6 each
SPECIAL OFFER. Pentode Output Transformer, 2/9 each.

LATEST TYPE PRE-AMPLIFIER

Well known maker. Chassis size 4 1/2 x 2 1/2 x 1. Co-axial input and output. With valve EF42. 14/- each. Post 1/6.



MIDGET RADIO CABINETS

Size 10in. x 5 1/2in. x 7in. complete with chassis and back. (Bakelite case.) To clear at 15/- each.
This well known cabinet of which thousands have been sold is ideal for every constructor. Complete with chassis, dial, bakelite, cord drive, pointer and dial drum. Price 27/6 each.

TECHNICAL PUBLICATIONS


Radio Calculations Manual ...	2/6 each
Television Servicing Manual ...	4/6 each
Power Pack Manual ...	4/6 each
Radio Data Book ...	1/6 each
40 Circuits Using Germanium Diodes ...	3/- each

MAINS DROPPERS

Dubbilier type HY 71228, 1,350Ω with 5 taps, 2/6 ea.
945Ω Dropper with 5 taps, 2/6 ea.
Vibrator Clips, 4d. ea.
Dubbilier Nitrogen Condensers, 12 mid. 350 v. D.C., 5/- ea.
TVC Condenser, type CE3TPE 100 mid. 450 v., 4/- ea.

THE COMPACT TELEVISION AERIAL BY ANTIFERENCE LTD.

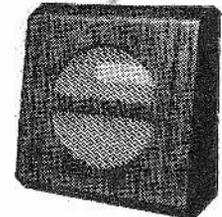Supplied complete with universal mounting and backplate in neutral brown finish. Overall length 3ft. 6ins. Packed in carton 3ft. 4in. long. Complete with full instructions. Cat. No. CDA. List price, 50/- Our price, 12/6 each. Postage 2/6.



LOUDSPEAKER CABINETS

This attractive walnut finished cabinet is available for 61in. or 8in. speaker units. Metal speaker fret, complete with back and rubber feet.

61in. type :

Measures 8 1/2in. x 8 1/2in. x 4 1/2in. at base. Price 15/6 each.

8in. type :

Measures 10 1/2in. x 10 1/2in. x 5 1/2in. at base. Price 19/6 each.
We can also supply a Baffle type cabinet, with the same excellent finish for 8in. speaker units only. The price is 17/6 each.

LOUDSPEAKER UNITS

PLESSEY 3in. Round type for personal portables 2 to 3 ohm	12/9
ELAC 4in. Square type 4/02, 2 to 3 ohm	13/6
PLESSEY 5in. Latest type	13/6
GOODMAN'S 6 1/2in. Round type	15/11
ELAC 6 1/2in. Type 6/19, 2 to 3 ohm	15/6
TRUVOX 6 1/2in. Water type, 1 1/2in. deep, 2 to 3 ohm	20/-
R. & A. 8in. Lightweight, 2 to 3 ohms	16/11
PLESSEY 6 1/2in. Mains Energised 650 ohms field	17/6
ELECTRONA 8in. PM 2 to 3 ohms	16/6
ELAC 8in. PM 2 to 3 ohms	17/6

THE LATEST ELAC 4in. x 7in. ELLIPTICAL UNIT, 19/10 each.

ELAC 10in. Units 2 to 3 ohms	25/6
PLESSEY 10in. Lightweight	19/6
TRUVOX BX11 12in. Lightweight	49/6

JUST A FEW LEFT

Goodmans 10in. Units. With Transformer, 28/6. Less Transformer, 25/6.

TERMS : Cash with order or C.O.D. Postage to be added to orders as follows : 9d. up to 10/- ; 1/- up to 20/- ; 1/6 up to 40/- ; 2/- up to £5. MAIL ORDER ONLY : Send 6d. in stamps for illus. catalogue.

WHEN ORDERING PLEASE QUOTE "DEPT. P.T."

ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

PREMIER RADIO COMPANY


OPEN TILL
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone :
AMBASSADOR 4033
PADDINGTON 3271

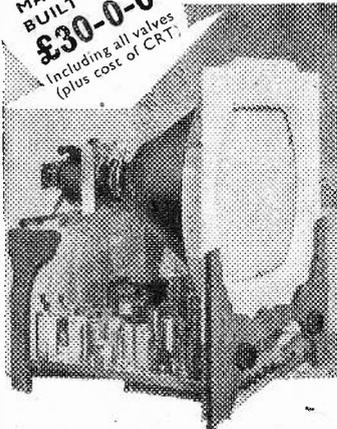MAY BE
BUILT FOR
£30-0-0
Including all valves
(plus cost of CRT)



THE COMPLETE TELEVISOR IS SAFE TO HANDLE, BEING COMPLETELY ISOLATED FROM THE MAINS BY A DOUBLE WOUND MAINS TRANSFORMER. ALL PRESET CONTROLS CAN BE ADJUSTED FROM THE FRONT, MAKING SETTING UP VERY SIMPLE.

The NEW PREMIER TELEVISOR

USING THE ENGLISH ELECTRIC CATHODE RAY TUBE T901

Brief Technical Details are as follows :

20 valves (plus tube) Superhet Receiver, tunable from 40-68 Mc/s without coil or core changing. Wide angle scanning Flyback EHT giving 14 kV, Duomag Focalliser, permanent magnet focussing with simple picture centring adjustments, suitable for any wide angle Tube, may also be used with a 12 in. Tube with very minor modifications.

VISION CIRCUIT. Common RF Amplifier, single valve frequency changer, two IF stages, Video Detector and Noise Limiter followed by special type of Video Output Valve. ALL COILS PRE-TUNED ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.

SOUND CIRCUIT. Coupling from anode of frequency changer, two IF stages, Double Diode Triode detector and first LF Amplifier, Diode Noise Limiter and Beam type Output Valve, feeding a 10in. Speaker. ALL COILS PRE-TUNED.

TIME BASES. 2 valve sync. Separator, giving very firm lock and excellent interlace. **LINE TIME BASE.** Blocking Oscillator using a pentode driving a high efficiency output stage comprising Ferroxcube Cored Output Transformer with Booster Diode.

FRAME TIME BASE. Blocking Oscillator driving a Beam Output Valve coupled through a Transformer to the high efficiency FERROXCUBE Cored Scanning Coils.

POWER PACK. Double wound Mains Transformer supplying all L.T. and H.T. using two full-wave Rectifiers.

The Televisor may be constructed in 5 easy stages : (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnet-c Televisors for use with modern wide angle tubes. All components are individually priced.

Instruction book 3/6, Post Free.

Console Cabinets in figured walnut can be supplied for the above receiver at a cost of £13/10/-, plus 21/- pkg. & Carr. H.P. Terms for cabinet on request.

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.s.

AVO METERS IN STOCK

Avo Model 7	—	—	—	—	£19	10	0
Avo Model 8	—	—	—	—	23	10	0
Electronic Test Unit	—	—	—	—	27	10	0
Electronic Test Meter	—	—	—	—	40	0	0
Valve Characteristics Meter	—	—	—	—	60	0	0
* Cossor Oscilloscopes Models 1052	—	—	—	—	104	0	0
"	"	"	"	"	1049	—	132 0 0

Full range Taylors Meters. List on request.

Leak—TL/10 Amplifier and "Point One"	—	—	—	—	28	7	0
Pre-amplifier	—	—	—	—	Complete	28	7 0
					Specification on request.		
Leak Tuning Unit	—	—	—	—	35	6	3
Chapman Tuning Units	—	—	—	—	from 17	6	8

LATEST VALVE MANUALS

MULLARD, OSRAM, & BRIMAR No. 5, 5/- each, MAZDA 2/- each.

SCOPE SOLDERING IRON A.C.D.C. HEATING

TIME : 4 v. 6 sec. 6 v. 4 sec. 39/6

Postage 6d. each extra.

Terms C.O.D. OR CASH with order and subject to price alterations and being unsold.

Arthur's Est. 1919

PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS: Gray House,

150-152 Charing Cross Road, London, W.C.2

TELEPHONE: Temple Bar 5833/4 and 4765.

TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."

CABLES—"TELEGRAY, LONDON."

TV EYE STRAIN REMOVED BY POLARISATION

(Brit. Pat. App. 12107/53)

The only sun glasses with all the year round use are the SEARLE 3 D-2 D Polarising spectacles. They are based on the scientific fact that only polarisation will remove glare without destroying contrast or spoiling definition. The lenses are adjustable, rendering the glasses ideal for:

TELEVISION. Prevents eyestrain due to screen glare aggravated by sun glare during the day.

DRIVING AND FISHING. Maximum cut out of road and water and sky glare, irrespective of the position of sun relative to wearer.

PHOTOGRAPHY. Essential for best results when using polarising filter on camera in cloud and water studies, with artistic perfection.

3 D FILM VIEWING. Glass lenses with high light transmission for clearest vision. Adjustment enables wearer to view the 3 D film as a flat film, if eye strain is experienced.

Price £2.2.0, case 4/6 extra, inc. P. Tax. Post Free. Gent's black and brown. Ladies' mother of pearl, cream and blue mottle. All models shaped eye, latest styles.

These Spectacles have been tested and acclaimed by following journals—THE CINEMA, Aug. and Sept. '53. MANUFACTURING OPTICIAN, November, '53. BRITISH JOURNAL OF PHOTOGRAPHY, Sept. '53. AMATEUR PHOTOGRAPHER, March, '54. THE AUTOCAR, May, '54. MOTOR TRADER, July, '54. PRACTICAL MOTORIST AND MOTOR CYCLIST, Sept. '54. THE GARAGE AND MOTOR AGENT, Sept., '54.

DENNIS SEARLE

626, Brighton Road, South Croydon, Surrey

TELENEWS

Education in Stockport

THE Stockport Borough Council decided recently to go ahead with plans to install TV in Stockport schools.

Television Licences

THE following statement shows the approximate number of television licences issued during the year ended August, 1954. The grand total of sound and television licences was 13,421,629.

Region	Number
London Postal	973,090
Home Counties	378,498
Midland	679,707
North Eastern	485,465
North Western	502,682
South Western	157,437
Wales and Border Counties	178,588
<hr/>	
Total England & Wales	3,355,467
Scotland	164,407
Northern Ireland	13,824
<hr/>	
Grand Total	3,533,698

Top Priority

AT the recent annual conference of the National Association of Women's Clubs held in London, Miss Rosalind Chambers, a lecturer in sociology, said that most of the tenants of houses on a new estate had told her that they regarded a television set just as necessary as the daily supply of milk.

The average wage earned on the estate was £7 a week. "We discovered," she said, "that the ambition of everyone was to have a TV set."

TV v. Cinema

MR. J. ARTHUR RANK, head of the Rank Organisation, believes that, after a bitter three-year struggle, the cinema's battle against TV is nearing an end and that "the menace has been beaten off." Patrons, even though most of them own a TV receiver, are coming back to the cinema not only because films are better but because they have finished paying for their sets.

"Television is no longer a

bogy for us," states Mr. Rank. "We have got its measure—it is no longer the threat it was."

Licence Scare

WHEN a G.P.O. radio detector van toured the streets of St. John's Wood and Marylebone, London, recently local inhabitants thought that the big chase had at last reached the area. Post offices in the district soon reported a substantial increase in applications for television licences.

It was later revealed by an official, however, that the detector van was not in working condition but was merely on the road for tests. There certainly seems to be something in the theory that the vans are worth a lot in "scare value."

Russian TV Station

A SOVIET news agency has reported that construction of a very large TV transmitting station at Kharkov is completed and that it is expected to begin operating almost immediately.

Eric Barker

MR. ERIC BARKER, star of TV and radio, thinks that it would be too great a demand on

his material and his talents for him to appear on television more than six times a year and refuses to exceed that number.

For Darker Evenings

WE learn from Scotland that many dealers, there are extremely thankful now that the clocks have been put back an hour and the evenings are closing in by teatime. They hope that when turning their thoughts to the dreary winter months that lie ahead people will decide that television is the best home entertainment value for their money.

Summer sales figures are down on last year. In June and July only 3,997 new licences were taken out at Scottish post offices compared with 12,780 in the same period last year. The July total this year of 1,550 was the lowest monthly figure for two years.

I.T.A. Order Television Transmitters

THE Independent Television Authority has placed an order for six television transmitters, three vision and three sound, with Marconi's Wireless Telegraph Company Limited.



A line-up of the G.P.O. detector vans visiting different parts of the country in an effort to round up "television pirates." In the foreground is the Scottish Region van and next to it the one serving Northern Ireland.

The vision transmitters have an output power of 10 kW. and the sound transmitters, which are amplitude modulated, an output power of 2½ kW. These transmitters are generally similar to those produced by Marconi's for export, but modified to suit the transmission standards peculiar to the U.K. They will operate in the Frequency Band III.

Illuminations Rendered Harmless

THE Sunderland Corporation, following a complaint of TV interference, fitted suppressors to the lighting strips that were part

room of the house opposite. Evidently, the only "interference" met with is the occasional drawing of the blinds.

British Firms in Baghdad

TELEVISION was demonstrated for the first time in Baghdad last month when twelve prominent British companies, supported by the British Radio Equipment Manufacturers' Association, sent exhibits to the British Fair.

A transmitter was supplied by Pye Limited and King Feisal was televised as he declared the exhibition open. Receivers were set up in

Contact with Files

A BRIGHTON firm has equipped its filing rooms with a television system so that records may be examined speedily even though the main offices are three miles away.

New Mobile Unit

THE Midland Region is to have its own mobile TV unit next March. At present, the area is forced to share a unit with the Northern Region.

Tubes on H.P.

IT has been announced from the trade that cathode ray tubes are to be made available on hire-purchase terms.

Less Fiction Read

IN 1953-54 the number of fiction books borrowed from Lancashire county libraries dropped by more than 174,000. The county library report blames the decrease on the growth of television-watching.

Export to Italy

ANOTHER contract for television equipment has been placed by Radio Audizione Italiana through Marconi Italiana for two further TV outside broadcast units, the equipping of another two-camera studio and a large quantity of monitoring apparatus.

Peterborough Exhibition

THE Peterborough Radio and Scientific Society recently held its eighth television and radio exhibition in the Town Hall. The show was open to the public for three days.

Quick Detection

FIFTY minutes after Mr. Leslie Crook, of Brixton, had bought his television, two G.P.O. detector van officials knocked at his door demanding to see his licence.

American Sales

TELEVISION retail sales in the United States reached a record level in July.



"In the News," an unrehearsed discussion on topics of the week, returned to the TV screen in October. This picture was taken during one of the final sessions in the last series. Noel Annan is seen in the rôle of Chairman.

of the Seaburn illuminations this year. They stretched along eight miles of sea front.

New Form of "Piracy"

WE hear of a new kind of TV "pirate" who manages to view television programmes regularly without paying out a penny.

He is a Londoner who uses a strong pair of field glasses to peer across the road, focusing them on the set in the drawing-

room of the house opposite. Evidently, the only "interference" met with is the occasional drawing of the blinds.

Most Sets in Midlands

AT a Press conference in Birmingham recently, Mr. H. J. Dunkerley, controller of the Midland Region of the BBC, said that there is a higher proportion of TV sets in the Midlands than in any other area in the country.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

BUILDING THE "SIMPLEX"?

Thousands of enthusiasts are building the "Simplex" Television, now being featured in "Practical Television." WHY NOT YOU? CONSTRUCTOR'S ENVELOPE containing full constructional details and Blue Print, additional notes and suggestions, and Query Service form, sent for ONLY 5/- All components available ex stock as follows:

ALUMINIUM CHASSIS.—18 s.w.g. DRILLED, with screens and tube holder bracket, 27/6. **PLAIN**, with screens and tube holder bracket, 20/-.

TRANSFORMER.—350-0-350 v. 150 m.a. 6.3 v. 5 a., 5 v. 3 a. tapped at 4 in., ONLY 32/6. (Postage 2/-).

CHOKE.—10 h. 120 ma., 10/6. (Post 1/-).

RECTIFIERS.—RM3 5/- ea., K3/40 6/- ea. **VALVES**.—EF50 6/6, SP61 4/-, 6SN7 9/-, 6X5 5/6, EB34 3/6, EA50 3/6.

VALVE HOLDERS.—B9G(EF50) 10d., I.O. and M.O. 6d., Diode (EA50) 6d., VCR97 2/6.

VCR97 TUBE.—Tested full screen, 42/6. **CONDENSERS**.—Electrolytics 25 mfd. 25 v. 1/10, 16 x 8 mfd., 450 v. 5/6, 32 x 32 mfd. 450 v. 6/-, 1 mfd. 2,500 v. 4/6. Mica, silver mica, and tubular, 350 v. 6d., each.

POTENTIOMETERS.—All values, pre-set 1/8 each, long spindle 3/-, with switch, 4/6.

RESISTORS.—1 watt 4d., 1/2 watt 5d., 1/4 watt 6d., 1.5 K. 5 watt, 1/6.

COIL FORMERS.—1 in. 3d., 1 in. 10d. **SPEAKER**.—8 in. ROLA P.M. with trans. 17/6 (postage 2/-).

All Components Brand New and Unused. Full Price List available on request.

VALVES

1G6	6/6	7A7	8/6	524	10/-
1E7	6/6	7C5	8/6	5U4	10/-
1LH4	8/-	7F7	8/6	6AC7	6/6
1LN5	8/-	7W7	8/6	6K7GT	5/6
1L4	7/6	12H6	8/6	807	7/6
2B7	8/6	12J5	6/-	ECH35	12/6
3A4	8/6	12A7	12/6	EA50	3/6
3B7	8/6	12SG7	7/6	EB34	3/6
6AG5	7/6	12SK7	8/6	EBC33	8/6
6AK7	9/6	12SR6	7/6	EBC32	3/6
6B4	7/6	2BD7	7/6	EF36	6/6
6B8	7/6	32	7/6	EF39	6/6
6C3	8/-	36	7/6	EF50	6/6
6C6	6/6	50Y6	8/6	.. Red	
6H8	5/-	58	8/6	Sylvania 8/6	
6K6	9/-	1622	11/-	EP91	12/6
6L7	7/6	1626	4/-	EY51	15/-
6N7	7/6	1299A	7/6	EK32	6/6
6R6	8/6	VR150/50	8/6	EL32	7/6
6U5	8/6	VR137	5/9	SP61	4/-
6V6	8/6	KT44	8/6	MU14	10/6
6V6GT	7/6	KT2	5/-	RL37	6/-
6SA7	8/6	VP23	6/6	VS70	7/6
6SC7	7/6	HL23DD	6/6	854	6/-
6SH7	7/6	TP25	8/-	955	6/-
6SJ7	8/6	1S5	8/-	9003	6/-
6SK7	7/6	1T4	8/-	9004	6/-
6SL7	9/-	1R5	8/-	931A	50/-
6SS7	7/6				

R.F. UNITS TYPE 26 and 27. For use with the R.1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves EF34 and 1 of EC52: Type 26 covers 65-50 Mc/s (5-6 metres), and Type 27 covers 85-65 Mc/s (3.5-5.0 metres). Complete with valves, and BRAND NEW IN MAKER'S CARTONS. ONLY 35/- each.

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed Normal Primaries. 425-0-425 v. 200 ma. 0.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., ONLY 50/-; 350 v. 0-350 v. 160 ma. 6.3 v. 3 a., 6.3 v. 3 a., 5 v. 3 a., ONLY 42/6; 250 v. 0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., ONLY 32/6; 350 v. 0-350 v., 150 ma. 6.3 v. 5 a., 5 v. 3 a., ONLY 32/6. The above are fully shrouded upright mounting. 5.5 kv. E.H.T. with 2 windings of 2 v. 1 a. ONLY 72/6; 7 kv. E.H.T. with 4 v. 1 a. ONLY 82/6. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

E.H.T. TRANSFORMER FOR VCR97 TUBE.—2,500 v. 5 ma., 2-0-2 v. 1.1 a. 2-0-2 v. 2 a. 37/6 (postage 2/-).

INDICATOR UNITS, TYPE 6.—Contain VCR97 Tube with mu-metal screen. 4 valves; EF50 and 2 of EB34. NEW CONDITION. ONLY 59/6 (carriage, etc. 7/6).

INDICATOR UNIT, TYPE 95.—Exactly the same as the Type 62, but for 60-cycle operation. Built on a two-deck chassis, it contains VCR97 Tube with mu-metal screen, 16 valves SP61, 2 of EB34 and 4 of EA50, also shafts of components. A snip at ONLY 58/6 (carriage, 7/6).

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station), 5 mins. by bus from King's Cross. Cash with order, please, and print name and address clearly. Include postage as specified and on Component Orders under £2.

U.E.I. CORPN.

THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1 (Phone TERMINUS 7937.)

Prices slashed at Clydesdale

INDICATOR UNIT TYPE 166
With VCR-97 tube and valves, 7 VR91 (EF50), 4 VR54 (EB34), 1 VR116, 1 VR92 (EA50), etc. Dim. 20in. x 18in. x 9 1/2in. Used good condition.
ASK FOR **£3.19.6** each CARRIAGE D/H885 PAID

INDICATOR UNIT TYPE 166
As above, but less tube and valves.
ASK FOR **£1.12.6** each CARRIAGE D/H885A PAID

INDICATOR UNIT TYPE 62
With VCR-97 tube and valves, 16-VR65-CV118 (SP61), 2-VR54 (EB34), 2-VR92 (EA50), etc. Dim. 18in. x 18in. x 11 1/2in. Wgt. 42 lbs. In original wood case.
ASK FOR **£3.19.6** each CARRIAGE D/H526 PAID

INDICATOR UNIT TYPE 62
As above, but in used, good condition. Loose stored.
ASK FOR **£2.9.6** each CARRIAGE D/E774 PAID

INDICATOR UNIT TYPE 62
As D/E774, but less VCR-97 tube.
ASK FOR **19/6** each CARRIAGE D/E774A PAID

INDICATOR UNIT TYPE 305
BRAND NEW. REF. 100B/6504. With tubes VCR-524A, VCR-525 and valves 7-VR91 (EF50), 2-VR54 (EB34), 6-VR92 (EA50). Dim. 12in. x 7in. x 18in. Wgt. 30 lbs.
ASK FOR **£3.19.6** each CARRIAGE D/H493 PAID

INDICATOR UNIT "A.S.E." SERIES (U.S.A.)
Contains 5BP1 C.R.T. With mu-metal screen 3-6H0's, 2-6SH7's, 6A1G7, plus H.V. conds, etc., metal case 18in. x 8in. x 8in. All controls brought to front panel beside viewing screen.
ASK FOR **£3.19.6** each CARRIAGE D/E776 PAID

INDICATOR UNIT TYPE 6
With VCR-97 Tube and valves 4-VR91 (EF50), VR54 (EB34), 3-VR92 (EA50), VR78 (D1), etc. Dim. 18in. x 8 1/2in. x 7 1/2in. Wgt. 21 lbs. In original wood case.
ASK FOR **£2.19.6** each CARRIAGE D/H524 PAID

INDICATOR UNIT TYPE 6H
With VCR-97 Tube and valves 4-VR91 (EF50), 3-VR54 (EB34). Dim. 18in. x 8 1/2in. x 7 1/2in. Wgt. 22 lbs. In original wood case.
ASK FOR **£4.9.6** each CARRIAGE D/E777 PAID

POWER UNIT TYPE 285
Ready made for T.V. A.C. Mains. Input 230 v. 50 cps. Outputs, E.H.T. 2 kv. 5 ma., H.T. 250 v. 150 ma., L.T. 633 v. 10 a. and 6.3 v. 5 a. Fully smoothed and rectified with valves VU120, 5U4G, VR91 (EF50), plus con., resistors, etc.
ASK FOR **£4.19.6** each CARRIAGE D/H947 PAID

ALSO AVAILABLE: POWER UNIT TYPE 285
As above, less valves. Slight internal damage, Transformers O.K.
ASK FOR **£1.19.6** each CARRIAGE H947A PAID

R.F. UNIT TYPE 24
In Original carton. With valves 3-VR65 (SP61), etc. Range 20-30 mc/s., switched tuning. Dim. 9in. x 7 1/2in. x 4 1/2in. Wgt. 7 lbs.
ASK FOR **15/-** each POST 1/6 D/H850 EXTRA

R.F. UNIT TYPE 25
In Original Carton. Range 40-50 mc/s., otherwise as R.F. 24.
ASK FOR **19/6** each POST 1/6 D/H874 EXTRA

R.F. UNIT TYPE 27
With Broken Dial. Range 65-85 mc/s., valves 2/VR135 (EF54), VR137 (EC52), etc. Dim. and Wgt. as R.F. 24.
ASK FOR **£1.9.6** each POST 1/6 D/E771 EXTRA

RECEIVER UNIT R3601
Ref. 10DB/6037. With valves 2 VR136 (EF54), VR137 (EC52), 5 VR65 (SP61), 4 VR92 (EA50), VR91 (EF50), 6V6G, VU39A (R3), etc. I.F. 13mc/s. Dim. 18in. x 9in. x 8in. Wgt. 38 lbs.
ASK FOR **39/6** each CARRIAGE D/H493 PAID

ION TRAP MAGNET ASSEMBLY
Mfg. Surplus. Type 1D/6 by Elac for 35 mm. tube neck.
ASK FOR **2/6** each POST 3d. D/H919 EXTRA

CO-AXIAL CABLE
Any length 52 ohms, 12 mm. dia. Price 5/- per yard. Minimum 12 yds. at 5/-, post 1/- extra.
ASK FOR D/E987.

REPRINTS FROM "PRACTICAL TELEVISION"
Components Price List Free on Request. The "Beginner's Receiver," modified by the R3170A 1/6 April to July 1/6 The "Beginner's Timebase" 1/6 Argus Television, data and blueprint ... 2/6 **CIRCUITS AVAILABLE** at 1/3 each. ASB3/5/7 or 8, type 62, R1355, R.F. 24, 25, 27 and R3601.
PLEASE NOTE.—Carriage and Postal Charges refer to the U.K. only. Overseas freight, etc., extra.

Order direct from:

CLYDESDALE SUPPLY CO. LTD.

2, BRIDGE ST., GLASGOW, C.S. Phone: SOUTH 2706/

RADIO SUPPLY CO. (LEEDS) LTD.

Dept. N.,
32, THE GALLS, LEEDS, 2.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/- extra under 10/- 1/6 extra under £1; 2/- under £3. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 5d.; Trade List 5d.

R.S.C. MAINS TRANSFORMERS (GUARANTEED) FULLY Interleaved and Impregnated. Primaries 200-230-250 v 50 c/s Screened.

250-0-250 v 70 ma, 6.3 v 2.5 a	12/11
250-0-250 v 70 ma, 6.3 v 2 a, 5 v 2 a	14/11
350-0-350 v 80 ma, 6.3 v 3 a, 4 v 2.5 a	15/11
350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a	17/6
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a	21/9
300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a	21/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a	21/9
350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a	27/9

FULLY SHROUDED UPRIGHT

250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a	16/9
Midget type, 21-9-3in.	23/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a	23/9
250-0-250 v 100 ma, 6.3 v 6 a, 5 v 3 a, for R1335 Conversion	29/9
300-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a	23/9
350-0-350 v 70 ma, 6.3 v 2 a, 5 v 2 a	18/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a	23/9
350-0-350 v 150 ma, 6.3 v 4 a, 0-4-5 v 3 a	29/11
350-0-350 v 250 ma, 6.3 v 6 a, 4 v 8 a, 0-2-6 v 2 a, 4 v 3 a, for Electronic Engineering Television	69/6
425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v 4 a, C.T., 5 v 3 a	47/9
450-0-450 v 250 ma, 6.3 v 6 a, 6.3 v 6 a, 5 v 3 a	69/6

FILAMENT TRANSFORMERS

All with 200-250 v 50 c/s Primaries; 6.3 v 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/9;

CHARGER TRANSFORMERS

200-250 v 0-9-15 v 1 a, 11/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 4 a, 18/9; 0-9-15 v 6 a, 22/9.

OUTPUT TRANSFORMERS

Standard Pentode 5000 to 3 ohms	4/9
Standard Pentode 73000 to 3 ohms	4/9
Standard Pentode 10,000 to 3 ohms	2/11
Small Pentode 6000 to 3 ohms	3/9

E.I.T. TRANSFORMERS 200-230-250 v

2,500 v 5 ma, 2-0-2 v 1.1 a, 2-0-2 v 1.1 a, for VCR97, VCR517	36/6
---	------

SMOOTHING CHOKES

250 ma 3 h 100 ohms	11/9
100 ma 10 h 200 ohms Potted	8/9
80 ma 10 h 350 ohms	5/6
60 ma 10 h 400 ohms	4/11

CO-AXIAL CABLE 1in. 7d yd
75 ohm 14/36 (Coils of 20 yds., 10/-) ... 7d yd
Twin Screened Feeder ... 10d yd
TV. PRE-AMPLIFIER.—For Fringe Areas Brand New. Complete With 6F13 valve. Only 22/6.

SELENIUM METAL RECTIFIERS
RM2 125 v 100 ma, 4/9; RM4 250 v 250 ma, 11/9; RM3 125 v 120 ma, 5/9; G.E.C. 300 v 250 ma, 12/9; 120 v 40 ma, 3/9; 6/12 v 1 a F.W., 5/9; 250 v 50 ma, 5/9; 6/12 v 2 a F.W., 9/9; 250 v 80 ma, 7/9; 6/12 v 4 a F.W., 14/9.

BATTERY SET CONVERTER KIT
All parts for converting any type of Battery Receiver to A.C. mains 203-250 v 50 c/s. Supplied 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 v at 0.4 a to 1 a. Price including circuit 48/9. Or ready for use 8/9 extra.

ALL DRY RECEIVER BATTERY SUPERSOLDER KIT—All parts for the construction of a unit (housed in metal case 5-4-4in.) to supply 90 v 10 ma, and 1.5 v 250 ma. Fully smoothed. From 200-250 v 50 c/s mains. For 4-valve receivers. Price inc. point-to-point wiring diagrams, 35/9. Supplied assembled and tested, at 42/6.

SILVER MIC.A. CONDENSERS. Most values 5d. ea., 3/9 doz. one type.

VOL. CONTROLS (standard long spindles) All values, less switch, 2/9; with S.P. switch, 3/9; with D.P. switch, 4/6.

ELECTROLYTICS.—Tubular 8 mfd 450 v, 1/11; 16 mfd 450 v, 2/11; Can 8-8 mfd 450 v, 3/11; 8-16 mfd 450 v, 3/11; 16-16 mfd 450 v, 4/11; 32 mfd 350 v, 2/11; 32 mfd 450 v, 4/11; 32-32 mfd 350 v, 5/6; 32-32 mfd 450 v, 5/11; 64 mfd 450 v, 4/9; 60-100 mfd 350 v, 7/6.

EX-GOVT. BLOCK PAPER CONDENSERS.—4 mfd 500 v, 2/9; 4 mfd 750 v, 3/9; 4 mfd 1,500 v, 5/9; 4 mfd 2000 v, 7/9; 8-8 mfd 500 v, 7/9; 0.1 mfd plus 0.1 mfd 8,000 v. common negative isolated, 11/9; 0.5 mfd 2500 v 2/11; 1.5 mfd 4000 v, 5/9

EX-GOVT. SMOOTHING CHOKES

50 ma 5-10 h	2/9
100 ma 10 h 150 ohms Tropicalised	5/9
150 ma 10 h 150 ohms	11/9
250 ma 10 h 150 ohms	16/9
250 ma 10 h 50 ohms	14/9

EX-GOVT. MAINS TRANSFORMERS
Primaries 230/250 v 50 c/s 4 v 2.5 a, 4/9; 4 v 6 a (High Ins.), 7/9; 48 v 1 a, 9/9; 250-0-250 v 40 ma 6.3 v 2 a, 5 v 2 a, 9/11; 400 v C.T. 150 ma 4 v 6 a, 6.3 v 6 a, 6.3 v 6 a, 4 v 6 a, 4 v 3 a, 4 v 3 a, 4 v 3 a, 5 v 2 a, 22/9; 300-0-300 v 120 ma 4 v 1 a, 17/6; 865-775-690-0-690-775-865 v 500 ma, 29/6; 610-0-610 v 150 ma, 300-0-300 v 150 ma, 1220 v 350 ma, 29/6; 460 v 200 ma, 6.3 v 5 a, 29/6; 460 v 200 ma, 6.3 v 5 a, 29/6.

EX-GOVT. AUTO TRANSFORMERS
0-110-190-250 v 1400 watts, 49/6; Double Wound 10-0-200-220-240 v to 10-0-275-295-315 v 1800 watts, 69/6; Double Wound 230 v to 230 v (tapped every 11 volts) 5kVa, 68/15/-.

EX-GOVT. E.H.T. SMOOTHERS
0.02 mfd 8000 v, 1/11; .25 mfd 4000 v (Block), 4/9; .5 mfd 3500 v, 3/3.

"SIMPLEX" PARTS
7 valves for Vision and Sound Section 29/6
7 valveholders for above ... 4/-
2 Electrolytics H.T. Smoothing ... 9/-
1 Smoothing Choke 150 ma 10 h ... 11/9
6 Valves for Time Base ... 25/-
6 Valveholders for above ... 1/10
5 Selenium rectifiers ... 27/6
Mains transformer 350-0-350 v 150 ma, 8.3 v 4 a, 0-4-5 v 3 a ... 29/11
Most other components available at low prices.

R.F. UNITS TYPE 26.—Brand new. Cartonned, 39/6, plus carr., 2/6.

BATTERY CHARGERS.—For mains 200-250 v, 50 c/s. Outputs for charging 6 v or 12 v at 1 amp. In strong metal case. Only 19/9.

NEW! EXPERIMENTAL OUTFITS

LEARN THE PRACTICAL WAY
Specially prepared sets of television parts (which you receive upon enrolment) with which we teach you, in your own home, the working of circuits and bring you easily to the point when you can construct and service a television set. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — this Practical Course is intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM 15/- A MONTH
A tutor is available to give individual help and guidance throughout the Course

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:


I am interested in.....

To: E.M.I. INSTITUTES, Dept. 138X, 43 Grove Park Road, Chiswick, London, WY.4.

NAME.....

ADDRESS.....

NOVEMBER..... IC-3

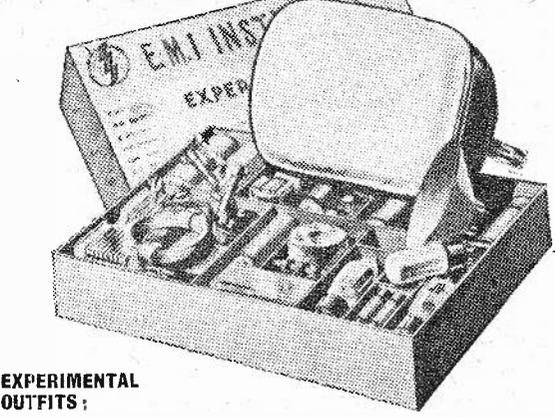

EXPERIMENTAL OUTFITS:
TELEVISION — Instruction and equipment for building a Television Receiver.
RADIO 1 — A course in basic principles.
RADIO 2 — Instruction and equipment from which you build a Radio Receiver.
Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.
E.M.I. INSTITUTES The only Postal College which is part of a world-wide Industrial organisation.

News From the Trade

SUB-MINIATURE VALVE MOUNTINGS

TWO new mounting devices suitable for certain types of sub-miniature valves have been developed by the Plessey Co., Ltd. One of these is a simple universal clip available in two sizes for pentodes and diodes. While occupying very little space it is designed to give constant spring tension without being too severe on the valve envelope and allows for any variations in size found in subminiature valves.

The pentode clip is made of 0.010in. and the diode clip of .006in. beryllium copper, heat treated to spring temper and finished in oxidised matt black. This finish, together with the intimate contact between the valve and clip, results in very favourable heat radiation characteristics and some degree of screening. Small projections are provided which may be used as earthing points to facilitate wiring. The pentode clip as supplied holds two valves, but can easily be divided into two separate clips by snapping along a tool impression mark provided for that purpose, whereas the diode clip is available in two forms to hold either one or two valves.

In the other mounting device the valve is held in a small spring clip attached to the chassis by means of a support with a very high copper content which acts as an excellent thermal conductor. A base ring made of P.T.F.E. or high grade bonded phenol resin in which tags are moulded is fixed into the chassis beneath the clip. The wire leads of the valve are soldered directly to the tags.


It has been the experience of many production engineers that, especially in sub-miniature equipment, the use of semi-skilled labour may give rise to circuit faults, particularly in intermediate stages of assembly. Much of the expense of fault location in finished equipment can be avoided by this mounting. This connection method also offers an advantage in that a contact point is available for intermediate testing of equipment prior to the installation of valves.

In addition to its electrical advantages this system also offers a rational form of chassis layout in assembly, and allows valves to be removed without disturbing the circuit. It has the further obvious advantage in that it combines the reliability of the wired-in circuit with conventional chassis construction.

It will be found that this device makes it easier to replace valves which fail in service, as well as facilitating and quickening line assembly processes. —Plessey Co., Ltd., Ilford, Essex.

CORE LOCKING MATERIAL

ONE of the major difficulties met with by the home- constructor of TV coils is fixing the small powder-iron cores. Elastic string is available but tends to twist up, and furthermore, is easily lost if the cores are removed. Vibration can result in shifting of the cores with the necessity for retuning. These troubles are overcome by using some form of adhesive, but ordinary paints, cellulose and similar materials, often advised for the purpose, may affect

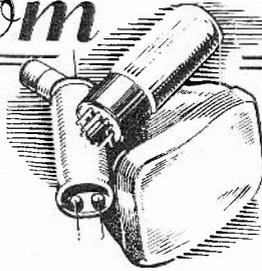


the properties of the core, and in many cases will prevent subsequent removal without breaking the cores or the formers. A special adhesive has been produced, however, known as 8G Core Locking Material. It is supplied in a small collapsible tube with a long tapering nozzle which just fits inside the standard coil formers,

and to use it the core is removed, the nozzle inserted in the former, and the tube pressed slightly. A few seconds should be allowed to elapse before the tube is removed, as the material is rather thick and takes a moment or two to leave the tube. On withdrawal a "blob" of the material should be inside the former and when the core is inserted it will spread and hold the core very firmly. It does not harden and remains firm and tacky almost indefinitely. The price is 4s. 6d. a tube, plus 3d. postage.—TV Replacements, 134-136, Lewisham Way, New Cross, S.E.14.

DECADE CAPACITOR BOX

FACED with the problem of considerable expenditure on decade capacitor boxes for a large research and development programme, two development engineers at Winston Electronics, Ltd., investigated the design of these instruments.

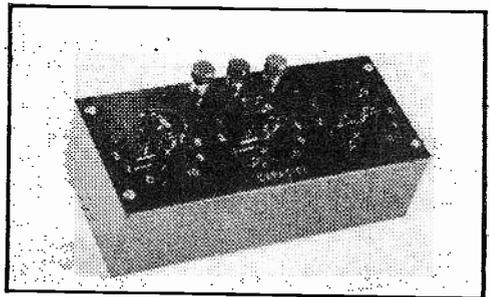By designing a new type of eleven-position switch—now patented—a great saving in bulk and manufacturing costs was made. An instrument, which can



The Winston Decade Capacitor Box.

be sold at a lower price than the cost of constructing home-made apparatus in either the factory or laboratory resulted, and is now being marketed.

Already the Decade Capacitor Box has proved useful in servicing deaf aids; but it should find wide application in electronic circuit designing and building, production control and testing, research and technical laboratories.

The service engineer in electronics, television or radio, will find this small size, extremely light and portable instrument particularly useful.

Technical Specification

Range : 0.001 μ F to 1.11 μ F in 0.001 μ F steps.

Stray Capacitance : Less than 15 pF per decade.

Working Potentials : 500 volts D.C., except the 0.1 μ F range, where it is 350 volts D.C.

Switching : Positive and firm. No play.

Controls : Firm, finger-ready.

Finish : Facia Panel : Photo-etched. Box : Steel, grey hammer-tone enamel.

Dimensions : 8in. x 3½in. x 3in. (20.3cm. x 8.4cm. x 7.6cm.).


Weight : 32 ozs. (0.9 kilos). *Price* : £10 15s. Winstone Electronics Ltd., Park Road, Hampton Hill, Middx.

TWO-BAND PATTERN GENERATOR

VARIOUS aids to the lining-up of television receivers are available, and one of the most useful which we have seen is the WG/44 Telequipment Unit. This is designed for use on both Band I and Band III and gives a choice of five patterns. When connected to a receiver it will modulate the frame giving a horizontal pattern with five levels of brightness from black to peak white, upon which may be superimposed, if desired, a fine ruled grating locked to the line timebase. This enables picture gradation, height, width, line and frame linearity, ringing, pulse response and other factors to be examined in the set under test. Alternatively, the raster may be made to provide a regular cross-hatch pattern for checking astigmatism, and this pattern may be opened by means of a small pre-set adjustment in the centre of the panel (with the aid of a screwdriver) so that other forms of line distortion may be checked. A strip running up the centre of the screen may be made to produce, with a grey back-ground over the rest of the raster, definition bars of 1.5, 2, 2.5 or 3 Mc/s detail for checking frequency response and ringing. The output is continuously variable from 10 μ V to mV and the instrument is extremely compact—measuring 11½in. x 8in. x 5½in. The price is £62.—Telequipment Ltd., 1319A, High Rd., Whetstone, N.20.

3D-2D SUNGLASS SPECTACLES

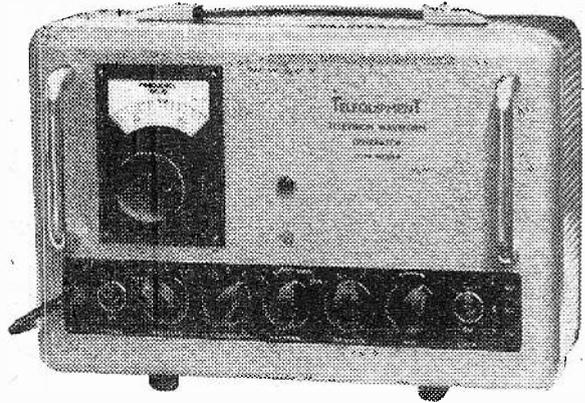UNDER this name, Dennis Searle of Croydon has produced a pair of spectacles made from a polarised material with movable lenses. In use they



The Telequipment two-band pattern generator.

may be employed for watching 3D films, or the lenses may be rotated so that they are both polarised in the same direction, when they may be used as anti-dazzle sunglasses or for reducing eye strain when viewing television. The lenses are made from laminated safety glass, not plastic, and they will find many uses—even returning a 3D film to 2D without blurring if one gets tired of the three-dimensional effect. The price is 2 gns. from D. Searle, 626, Brighton Road, South Croydon, Surrey.

The British Amateur TV Club

THE club was founded in 1949 to co-ordinate the activities of amateur radio enthusiasts experimenting with television transmission, and to liaise with other enthusiasts overseas similarly engaged. The club is affiliated to the Radio Society of Great Britain.

Experiments carried out by B.A.T.C. members have been mainly in two directions, viz., video and R.F. Very few members have the resources to build both sorts of equipment. On the video side, the standards recommended are such that any normal BBC television receiver can be used as a monitor, i.e., 200-line 50 pictures per second sequential, or 405-line 25 pictures per second double interlaced, positive modulation, and waveform similar to that of the BBC. For interchangeability, club members are recommended to arrange all outputs at the one-volt level, low-impedance picture positive, syncs negative. Belling-Lee plugs and sockets are preferred.

On the radio side, the experimenter must hold a G.P.O. amateur vision licence, costing £2 per annum, under which the holder may now transmit messages by telephony or morse without a separate licence, provided that these messages are concerned with the technical matter of the visual transmission. Operation is permitted in the 70 cm. amateur band and on shorter wavelengths. Full details can be obtained


from the G.P.O. To date some eight stations have been on the air in this country.

For a camera, the only tube available at the moment is a Vidicon type, rejected by the manufacturer for minor blemishes and costing £25. Occasionally, other types of tube become available also; Monoscopes are available at £7 10s., but these offers are only valid for members resident in the United Kingdom. Very satisfactory results can be obtained with much less costly equipment; a flying spot scanner using a 5FP7 scanner and 931A photocell can be built for as little as £10, with a resolution of 2.5 Mc/s. Such units can also be easily converted for telecine work.

There is very little literature of value to the amateur, and so the club issues a quarterly magazine, "CQ-TV," free to members, containing circuits and notes not to be found elsewhere. A few back copies are available at 1s. 6d. each. Also available are headed notepaper, membership certificates, QSL cards and lapel badges. Loans of equipment, films, posters, photos, tapes and lecture notes can be arranged for demonstration purposes.

Membership costs 5s. per annum, payable on the first of January. New members are asked to enclose 6d. per month remaining of the old year plus 5s. for the following year. Further details are available from the Hon. Secretary, B.A.T.C., 56, Burlington Gardens, Chadwell Heath, Essex (Seven Kings 1051).

A LARGE PICTURE TV.

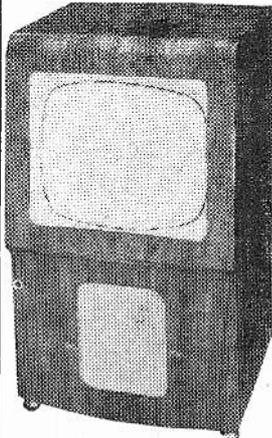

CABINET for THE TELE KING

As illustrated here. Pleasing design, strongly constructed, finished in walnut veneer, light, medium or dark shade. Including 14, 16 or 17 inch mask and glass.

Lasky's Price £8.10.0d.
Carriage 12/6.

14, 16 or 17 inch

FOR **£29.10.0**

Including valves.

Only cabinet and cathode ray tube extra.

THE TELE KING


This well-tried and famous home constructor television receiver, can be built with ease from the comprehensive construction envelope. Complete instructions, including 32-page booklet, point to point wiring diagrams and theoretical circuits.

PRICE **6/-** POST FREE.

LASKY'S RADIO, LASKY'S (HARROW ROAD), LTD.,

370, HARROW ROAD, PADDINGTON, LONDON, W.9.
Telephones: CUNNINGHAM 1979-7214.

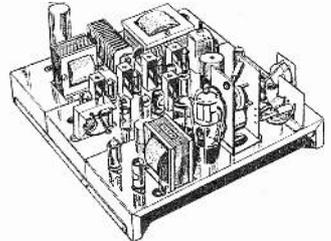Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs. half day, 1 p.m. Postage and packing charges (unless otherwise stated): on orders value £1-1s. 0d. extra; £5-2s. 0d. extra; £10-3s. 6d. extra; over £10 carriage free. All goods fully insured in transit.



CATHODE RAY TUBES

For Use with The Tele King.

- 14 Inch. Mullard. MW30-24. £19 9s. 3d.
 - Brimar. C14FM.
 - 16 Inch. English Electric. T.301. £20 10s. 1d.
 - Mullard. MW43-64. £22 4s. 10d.
 - 17 Inch. Mullard. MW43-64. £23 12s. 6d.
 - Brimar. C17FM. £24 13s. 6d.
- Carriage and insurance 15/- per tube extra.

VIEW MASTER

Complete Standard or Wide Angle; Wide Angle Conversion

Return of Post Service

PRICES: We can save you money on your View Master. Full details in our lists.

RESISTOR KITS. Our special kits have every Resistor marked with value and position in set.

HIRE PURCHASE. Complete or part kits can be supplied on Hire Purchase. Ask for details. Deposit only 2/- in the £.

INSTRUCTION BOOKS. Standard, 7/6. Wide Angle 11/-. Wide Angle conversion, 3/6. Please state model required and your local transmitter.

PRICE LISTS. Our very detailed price lists give full details for all models. Sent free upon request.

Any item supplied separately.

WATTS RADIO

8, Apple Market, Kingston on Thames, Surrey.

Phone: KINGSTON 4099

TALLON CABINETS

for television, radio and grams, polished, ready for assembly in packed flat kits or factory assembled.

TELE-KING cabinets with space for radio or tape recorder with or without doors, for 12", 15", 16" or 17"

VIEW MASTER cabinets, console, or table, 12 and 17in.

P.W. 3-SPEED AUTO-GRAM CABINET.
LYNX CABINET.
ARGUS CABINET.

RADIOGRAM, RADIO AND SPECIAL CABINETS TO CUSTOMERS' DESIGNS. SUPER CABINETS FOR SOUNDMASTER. MINI-FOUR AND CRYSTAL DIODE cases at 14/6 each, including postage.

Consult your local dealer or write to:
(DEPT. P.T.I.)

JAMES TALLON & SONS LTD.

MANOR WORKS, MANOR ROAD
RUGBY Telephone: RUGBY 2070

THE THREE-IN-ONE TOOL FOR ALL RADIO ENTHUSIASTS

Bib Wire Stripper and Cutter



CUTS wire cleanly

STRIPS insulation

SPLITS plastic extruded flex

Adjustable to most wire thicknesses.
No more fiddling with razor blades or pen-knives whenever you make a joint. Here's the tool that strips, cuts and splits flex in half the time, with half the trouble—and does it more efficiently. Nickel plated and packed in cartons with full instructions. Bib wire strippers are available at ironmongers and electrical shops. Get one today.

In case of difficulty, write to:
MULTICORE SOLDERS LTD.,
Multicore Works, Hemel Hempstead, Herts. (Boxmoor 3636)

3/6

WE SPECIALISE ONLY IN RADIO COMPONENTS—

LET US QUOTE YOU BY
RETURN FOR ANY RADIO
VALVES OR PARTS YOU
REQUIRE

HIRE PURCHASE TERMS ON KITS,
INSTRUMENTS, ETC.

Goods Sent C.O.D. or Cash
With Order

SURPLUS BOOKLET 6d. QUOTES S.A.E.

RADIO SERVICING COMPANY

82 SOUTH EALING ROAD
LONDON W.5 EAL. 5737

NEXT DOOR SOUTH EALING TUBE STATION (TURN LEFT)

MONEY BACK GUARANTEE

DUKE & CO

621 ROMFORD RD. LONDON, E.12.

3

12" £5 TV TUBES 3 MONTHS' GUARANTEE

MAZDA CRM121-A-B, and a few other types and makes. Picture shown to callers. Not ex-W.D. Carriage and insurance 15/6 extra. No catch.

SPECIAL OFFER of tubes with burns or Cathode to heater short. 30/- each, plus carr.

AMPLIFIERS. 7/6. Push-pull. 4 valve and rec. Full tone range, variable. Output 3-7.15 ohms matching. A.C. or Universal. Post 2/6.

AMPLIFIERS. 5/7.6.
4 watts, 3 valves.
Switched tone range
2-5 ohms output. Good
quality. A.C. or A.C./
D.C. Post 2/6.

AMPLIFIERS. 9/6.
X.W.D. with one valve
EF36. Complete with
FREE drawings.
Post 1/6.

**100 MICRO-AMP
METERS.** 12/9. Full
scale reading, 2 1/2 in.
square dial. Drawings supplied. Post 1/6.

EXTENSION SPEAKERS. 19/9. 5in. speaker on polished baffle. 3ft. lead ready connected. Post 1/9.

8/9. 700 MICRO-AMP METERS, and movement (radiator). Post 1/3.

REAR LIGHTS. 1/9. Ideal tail or side lights. Infra red glass, easily changed. Post 9d.


SPOTLIGHTS.—8/9 Butlers, new but ex-W.D. 7 1/2 in. dia. 6 1/2 in. deep. Pre-focus type. Post 1/3.

BULBS.—For above now in stock, 6 volt, 36 watt, 12 volt, 48 watt, 4/6 each.

INERT CELLS.—3 volt twin cells G.E.C. Post 9d.

H.T. BATTERIES.—1/9 Aldry min. : 40 volts and L.T. 1 1/2 v. 60 volt + 1 1/2 v. at 3/9. 87 1/2 volt personal portable type at 3/9. 60 volt at 3/9. 90 volt + 1 1/2 v. at 6/9. 90 volt new Ever Ready at 7/9. Post on all H.T. batts. 1/9 each. All batts. tested before despatch.

Send 2d. stamp for Catalogue.

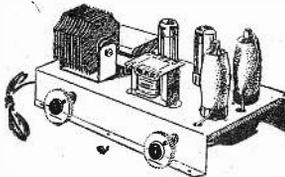

LINE E.H.T. TRANSFORMERS REWOUND PROMPTLY

Our 30 years' experience of winding and wave-winding enables us to provide the finest service in the Country for all types of TELEVISION COMPONENTS.

We repair or manufacture all types of transformers singly or in quantity, and welcome your enquiries.

Catalogue on request.

H. W. FORREST

349, HASLUCKS GREEN ROAD,
SHIRLEY, BIRMINGHAM.

Telephone : SH1 2483.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 287 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

FAULTY SOUND

A friend of mine has a Raymond television (table model) F.60, Ref. A/C No. A13257, which has the peculiar habit after a short period of use of dropping in volume to a very low level of sound.

It is noticeable that if the contrast control is over-advanced it generally corrects it for a further short period.

The PL.83 was found to be low and replaced, but this trouble still persists on sound only, as the vision is remarkably excellent in quality.—E. J. Wall (Coventry).

This symptom frequently indicates a resistor or capacitor defect in the sound detector/noise limiter or sound output stages. You should endeavour to prove whether the fault occurs in the output stages or in the detector stage by listening to the sound signal in a pair of headphones connected to the control grid of the sound output valve and chassis. If, when the symptom becomes evident from the loudspeaker, the signal in the phones remains constant, the fault must lie in the output stage where normal testing methods should soon reveal the defective part.

TYPE 26 UNIT

I would be greatly obliged if you could help solve a problem I have come up against. I am using a 1355 I.F. unit for vision and since replacing the R.F. unit type 25 with type 26 the fly-back lines are unduly prominent and there is sometimes a white vertical band down the screen near the centre. The half-lines at the bottom are shaped more like matchsticks with blobs on the end, otherwise I get a splendid picture. The tube is the VCR97.—W. Farrell (Blackburn).

The use of the RF26 as against the RF25 should make no difference to the appearance of the raster. The RF unit is more powerful than its predecessor and that is all.

If the actual raster is the same as before then it is possible that you have a fault in the video output stage and we suggest you check the biasing arrangements on the valve, paying particular attention to the decoupling condenser.

The receiver should always be operated with the brilliance reduced so that when no picture is being transmitted no raster is seen on the screen.

DETAILS OF VCR511

I shall be most grateful if you can give me the following information on VCR511, an ex-Government cathode ray tube :

- (a) Base connections.
- (b) Filament voltage and current.
- (c) Final anode voltage.
- (d) Deflection voltage for full width of screen.—J. R. Crane (Bell Heath, Worcs).

(a) The base connections are as for VCR97 but grid and cathode are reversed.

(b) The heater voltage is 4 at a current of about 1.2 amp.

(c) The maximum final anode voltage is 5 kV.

(d) Deflection voltage for line is 1.170 volts and for frame 887 volts.

"SIMPLEX"—SOUND OUTPUT STAGE

I am making up your "Simplex" TV. In the sound section I see you use a Pen 45. I have a transformer where I could use 6V6. Can this be used? If so, what are the modifications for this valve? What is the object of Pen 45? Thanking you for a reply.—A. E. Wareham (Portsmouth).

The reason for using the Pen 45 was simply that it has a 4-volt heater and a 4-volt potential was available from the same supply on the mains transformer as the C.R.T. It was not possible to use a 6.3-volt valve as the existing 6.3-volt line is fully loaded without the power valve.

You can use the 6-volt valve provided you have a suitable winding on the transformer.

The following modification is recommended: Remove RS5 and place it in RS2 position; move VR2 to RS5 position, taking the slider to the grid of the output valve; connect the now free end of RS1 to chassis and the free end of C15 to pin 6 of the EBC33.

FAULTY MAINS TRANSFORMER?

I have a TV set, Ekco TS46, which has worked well for over five years.

It was working well until I went on holiday for a fortnight, but on returning I switched on the set and after about 30 seconds a distinct smell of burning came from the back with slight smoke.

I instantly switched off and removed back.

On switching on again I noted that the filaments of valves came on but again after about 30 seconds I noted smoke coming from the mains transformer immediately behind the E.H.T. screened section. It was hot to the touch.

I switched off at once in case of further damage.

It appears that as the valve filaments glow, the transformer appears in order and I'd be grateful if you can tell me what other component can be at fault? I have no instruments for testing.—B. W. Himes (S.E.9).

The fact that the valve heaters light up does not conclusively indicate that the mains transformer is free from defect. Indeed, since it has actually been burning it is now almost certainly in need of replacement. The H.T. secondary winding has probably overheated either as a result of insulation failure

or due to a short-circuit on the H.T. line—the chief cause in this respect being electrolytic smoothing capacitor failure.

EKCO T.161 LINE FAULT

My television set, which was bought in November, 1951, is an Ekco table model, Type T.161.

We have had perfect reception until a week ago, when two pairs of black wavy lines appeared across the screen, these flickered up and down the screen for a few seconds and then the picture became blank and, although sound remains perfect, no picture comes at all. Up till the moment of the lines appearing the picture was perfect.

The screen went completely blank, suddenly, no fading of the picture or any changing, and the receding bright spot which we have always seen when turning off the set was not present.—F. J. Burch (Keston).

We feel certain that the cause of the symptom described lies in the line timebase section. It is a typical symptom of a sudden failure of the line output transformer—probably a collapse of the winding insulation.

In the first place, we would advise that you check for E.H.T. pulse voltage at the anode of the U25 E.H.T. rectifier valve—holding the blade of an adequately insulated screwdriver close to the anode lead should result in an arc at least $\frac{1}{4}$ in. long.

You will probably discover that this will not occur, but before contemplating transformer replacement, it may be a good idea to have the emission of the 20P1 line output valve tested.

Incidentally, if you are able to draw an arc from the E.H.T. valve anode lead you should suspect the U25 for low emission or open-circuit heater.

TESTING BEAM CURRENT

Would you advise me how I can test the beam current in C.R.T., both for tetrode and triode tubes?

The points which I should most like clarified are—Is beam current taken with modulation on tube—and what should be the setting of the brightness control?—N. Rego (Harrogate).

The actual value of beam current varies widely from tube to tube, and is also dependent on the value of grid bias. In turn, the value of grid bias is, of course, set by reason of the brightness control itself.

The cathode current can be measured by inserting a microammeter in series with the lead to the tube cathode pin, and adjusting the grid voltage according to the figures given in the tube makers' data sheet to give an expected beam current of 20-30 μ A. If the tube is in order and the ion-trap magnet is correctly set, a raster should be obtained on the screen under these conditions.

Beam current is not normally taken with the tube working under signal conditions.

R1355 AND SIMPLEX

I am already converting a 1355 plus RF25 to sound and vision. It will consist of 9 VR65, 1 VR92, 1 6V6 and 1 VR55 valves.

What I wish to know is, can I get the power supply from the "Simplex" power supply, and use the "Simplex" timebase and "Simplex" cathode-ray tube circuit as laid down in your articles?

I want to save myself the expense of building three separate power packs.—H. Calladine (Manchester).

It is not possible to employ the method of power supply which you suggest as the heater current is far too heavy. It is possible to construct a single power supply for the whole television, but the difficulty is in the supply of a transformer with sufficient heater current. The most economical method is to use a transformer giving the necessary H.T. and to supplement this with a heater transformer, feeding the heaters on split loading.

BUSH TV24A—WIDTH TROUBLE

I have a Bush TV24A (12in. screen). A few weeks ago I discovered that the width control did not travel its full course. I found that the 30 K Ω variable resistor had overheated to such an extent that the plastic casing had melted and locked the spindle. I replaced the resistor and the same thing has happened again. The resistor does not burn right out but only gets very hot—the resulting deformation of the casing, of course, locks the spindle and prevents any adjustment.

I would be grateful if you could suggest a remedy for this fault.—J. Howe (S.E.26).

The resistor to which you refer, together with an .80 pF 5,000 volt working capacitor connected in series, forms a damping circuit across the deflector coil output. Considerable line pulse energy is thus dissipated across the resistor in the form of heat—this is quite normal. We assume that your replacement resistor is of the correct type and wattage rating—this is most important, of course.

If the trouble persists, however, you may find it advisable to use a control rated slightly higher than the original.

VIDOR CN4216—VISION INSTABILITY

I have a Vidor 12in. TV, model CN4216 and it has developed an intermittent fault and would like your help to try to rectify this fault.

Its symptoms are as follows: after the set has been on about 30 minutes, a pattern rather like a honeycomb comes over the whole screen, this lasts for a second or two and then the whole picture breaks up with the effect of faulty horizontal hold control, this lasts for about three or four seconds and then returns to normal. The whole process repeats after a few minutes. The foregoing effect lasted throughout one evening's viewing and on switching off and being left to cool down, after switching on again, it took about seven minutes for the fault to develop.

After the evening referred to, there was no further trouble for four or five weeks. The second time the fault developed in much the same way, but with an interval between of about 30 minutes.

I would like you to give me an indication where to look for the fault and would mention that I have the service sheet for the set.—J. Thompson (Glasgow).

Since you mention that the vision disturbance can be temporarily corrected by letting the receiver cool-off, and since your remarks indicate that the sound is unaffected, we feel that one of the valves associated with the vision channel may develop a fault to provoke instability. You should endeavour to prove this possibility by substituting, in turn, the valves concerned. A valve for this purpose can probably be obtained from the sound channel provided it is of the same type, which should, of course, be replaced with one of the valves in the vision channel. You should make a note of the original valve positions, for it is not desirable to interchange valves permanently, even though they are of the same type.

COMPLETE T.V. AERIALS with chimney lashings, "H" type, £3; single dipole, £2; 3-element folded dipole with 10ft. pole, £5/15/-; all prices carr. pd. **GLADSTONE RADIO**, Gladstone Place, Newton Abbot, Devon.

A BIG ADVANTAGE of using our rewind service is that in most cases a stock replacement can be supplied. We have the most complete T/V component replacement service in Great Britain. Have you tried "Nurray" the heater booster isolator that just plugs in? "DIRECT T/V REPLACEMENTS," 134-136, Lewisham Way, New Cross, S.E.14. (Tideway 3696-2330.)

THE CHEAPEST Blank Ali. Chassis, made in bright 18g. ali, with sides and narrow end tinned in and down in. for maximum strength and rigidity.

7 x 4 x 2, 3/4 9 x 5 x 2, 4/-
10 x 6 x 2, 4/6 10 x 8 x 2, 5/-
12 x 8 x 2, 5/6 12 x 9 x 2, 6/-
14 x 9 x 2, 6/6 15 x 9 x 2, 6/9
16 x 8 x 2, 6/9 16 x 10 x 2, 7/3
17 x 9 x 2, 7/3 17 x 12 x 2, 8/6
Other sizes made to specification. Any length up to 17in., any width up to 12in., any depth up to 3in. Cost 1d. per sq. in. of the top surface only, ignoring depth. e.g., 10 x 7 x 2 = 10 x 7 = 70 sq. in. = 70d. = 5/10. **SERVIO RADIO**, 156/83, Merton Rd., Wimbledon, S.W.19. (Liberty 6525.)

SIMPLEX T.V. 18 swg. Chassis with screens and valve punched 17/6, post 1/6; fully-wound Coil Sets 15/-, post 1/-; Lynx wound Coil Sets, 35/-, post 1/-; Super-Visor and Tele-King Coil Sets, 37/6, post 1/-; 3in. square Cans, Former, Side Wires, etc., 1/9 each; Simplex Mains Transformers, 27/6, post 1/6. **C. O. PRESTON YORKSHIRE**, Healey Lane, Batley, Yorks.

POWER UNIT 285. 230v. 50c input; outputs D.C. 2kV. 5ma. 350v. 150ma; A.C. 6.3v. 15a. 3 valves, new, 85/-, carr. paid inland. Transformers, new, std. mains input; 250-0-250v. 70ma. tapped 200v. 6.3v. 3a. 4v. 2a; 10/6; 600v. H.W. 6.3v. 3a. 4v. 2a; 10/6; 230v. to 6.3v. 5a and 10a. 15/-; 2kV. 5ma. 2v. 2a. 25/-; 350-0-350v. 150ma. 5v. 2a. 25/-; 55v. 30ma (twice), 6.3v. 3.2a. 9/-; 220-0-220v. 33ma. 7.1v. 8a. 8.4v. 10a. 5v. 3a each C.T. 15/6; 740-0-740v. 165va. 470-0-470v. 220va. 4v. 8a. C.T. (twice), 40/- (carr. 5/-). Postage 2/- each. List and enquiries, s.a.e. please. Terms: Cash with order. Postage extra. Immediate despatch. **W. A. BENSON**, 308, Rathbone Rd., Liverpool, 13.

LATEST BRIMAR MANUAL, 248 pages of circuits, formulae, valve techniques. 5/-, post 8d. **BENTLEY LTD.**, 38, Chalcot Road, N.W.1. (PRImrose 9090.)

511A—12in. Tube and rubber Mask, 45. **R. HALLETT**, 30, Demholme Rd., W.9.

VIEWMASTER:—Assembled, tested, and aligned Sound/Vision Chassis £4/12/6 to £7/18/6. Amazing value, stamp for details. Half Price Offers: Guaranteed brand new specified Viewmaster parts, Line Tran, 16/-; Mains Tran, 23/6; Frame O/V. Tran, 13/-; Scan Coils, 16/6; P.M. Focus Ring (Mullard), 12/6; Width Cont., 5/-; Power/TB Chas., 10/-; L707 5/-; Q257/1. 4/6; WB101. 3/-; 12in. Tube Supports 11/6. Postage extra. **R. MASSEY**, 58, Wakefield Ave., Hull.

COILSETS for PT. Argus, Simplex, 21/- complete. Other sets to order. Commercial Convertors £8. **BEL**, Marlborough Yard, Archway, N.19. (ARC 5078.)

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Bullingdon Rd., Oxford.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

RADIO UNLIMITED offer new, boxed Valves, SP41, SP61, 2/6 ea.; 9D2, 8D2, 4D1, 3/6 ea.; 6K7M, 1L4, 3A4, EF50, EF36, 5/- ea.; 6AL5, 6AM6, 6V6, 6P6, 12A6, EF39, EL32, 1R5, 1S5, 1T4, 3S4, 3V4, 7/- ea.; 6L6G, 5Z4, 5U4, 6SN7, 6SL7, PL82, PY82, UY41, EP41, W77, X78, EBC41, 8/- ea. V/hdrs., all types, 8d.; Hunts, 1-500v. 7/6 doz. Bargain list free. **RADIO UNLIMITED**, Elm Rd., London, E.17. (KEY 4813.)

WINWOOD FOR VALUE.—3-wave Coilpacks, L, M, and S 24/6; V/master Coils, any area, 17/6 set; 6AM6 and 6AL5 Valves, 6/-; Iso/trans., 2v. 4v. or 6v. 25% boost, 6/6; Fil/trans., 200-240v. 6.3v at 1.5a. 5/6; W.W. Cntrs., 5K and 25K, 3-watt, 3/6; V/master Pre-sets, 2/9 each. Dubilier, 8mf-500v. 2/3; 8 x 8-500v. 3/8; 16 x 16-500v. 4/6; Cored Solder, 8oz. reel, 4/6; Elliptical Spkrs. 7in. x 4in. closed field, 17/9; SP41 and SP61 Valves, 24/- dozen. **WINWOOD**, 12, Carnarvon Rd., Leyton, E.10. (Mail only.)

AMERICAN MAGAZINES.—One-year "Audio Engineering," 35/-, specimen copy, 3/6; "High Fidelity," 50/-, specimen copy, 4/6; "Popular Science," 28/6. Free booklet quoting others. **WILLEY LTD.** (Dept. 23), 101, Fleet Street, London, E.C.4.

R.F. UNITS, types 26 at 32/6, 25 at 16/6, 24 at 12/6, brand new in original cartons with valves; postage 2/4. **E.W.S. CO.**, 69, Church Rd., Moseley, Birmingham.

"VIEWMASTER" Valves, exact to specification; guaranteed new and boxed, set of 12, £5/15/-; "Tele-King" 17in. Receiver, complete set of 17 valves exact to specification, £8/19/6; 6AM6, EP91, 6P12, Z77, EB91, 6AL5, 6AM5, EL91, any 8 for 50/-, post 1/6; 1.4v. miniatures, 1S5, 1R5, 1T4, 3V4, 3Q4, N18, 3S4, 1S4, DK92, any 4 for 27/6, post 1/-; all guaranteed new and boxed. For individual prices and other types see displayed advert., p. 288. **READERS RADIO**, 24, Colingb. Place, Stamford Hill, London, N.16. (STA 4587.)

SERVICE SHEETS for Radio and Television, over 2,000 models. S.A.E. enquiries. **W. GILBERT**, 24, Frithville Gardens, London, W.12.

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempt from the provisions of the Notification of Vacancies Order, 1952.

HIGHLY QUALIFIED GLASS TECHNICIAN required by The English Electric Valve Co. Ltd., Chelmsford, for small laboratory production of special glasses. Some years' experience in actual manufacture of glass as well as academic qualifications. Apply, quoting Ref. 497J. to Dept. C.P.S. 336/7, Strand, W.C.2.

RADIO AND TELEVISION COMPONENTS

All parts in stock for: **VIEWMASTER, SOUNDMASTER, TELEKING, ETC.**
Easy Terms Available.
Stamp for list, NOT S.A.E.
JAMES H. MARTIN & CO.
Finsthwaite, Newby Bridge,
Ulverston, Lancs.

ELECTRONIC ENGINEER is required for work in the research laboratory of a progressive East Midlands firm on the design and development of electronic measuring instruments and of circuits for automatic control systems, etc. The post should prove most attractive to a man aged 25/30 who has obtained a good degree and has had some experience in servo systems, electronic motor control and/or magnetic amplifiers. A salary up to £700 depending on qualifications is offered. The post is pensionable. Please write, stating age, experience etc., to Box 23 39848 A. K. ADVG., 212a, Shaftesbury Ave., London, W.C.2.

TELEVISION AND RADIO MAINTENANCE ENGINEERS WANTED

Good remuneration, conditions and prospects for capable men.

Apply to Clydesdale Supply Co., Ltd., 2, Bridge St., Glasgow, C.5, or contact the Manager at our branch nearest to you.

SCOTLAND. Alloa, Aberdeen, Arbroath, Ayr, Cambuslang, Clydebank, Coatbridge, Cowdenbeath, Dumbar, Dumfries, Dunfermline, Dundee, Edinburgh, Falkirk, Glasgow, Greenock, Irvine, Kirkcaldy, Kilmarnock, Motherwell, Paisley, Perth, Renfrew, Stirling.

ENGLAND. Birmingham, Bromsgrove, Darlington, Doncaster, Dudley, Gloucester, Middlesbrough, Newcastle-on-Tyne, Stockton-on-Tees, Walsall, York.

NORTHERN IRELAND. Ballymena, Belfast.

TELEVISION AND RADIO ENGINEER is required for the design and development of components including small power transformers. Ability to engineer these components for mass production essential. The post carries a salary of £600/800 p.a. and is pensionable. Please apply, stating age, experience etc., to Box 23 39850 A. K. ADVG., 212a, Shaftesbury Ave., London, W.C.2.

WANTED

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcot Road, N.W.1. (PRImrose 9090.)

NEW VALVES WANTED, small or large quantities. PL81, EY51, KT61, 5Z4G, 5R4, 5U4, 3Q5, all television; prompt cash. **WM. CARVIS LTD.**, 103, North St., Leeds, 7.


EDUCATIONAL

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest electronic organisation; moderate fees. Write to Dept. PT28, E.M.I. INSTITUTES, London, W.4.

YOU CAN become a first-class Radio Engineer. Our Postal Courses will teach you to earn more money or start a spare-time business of your own. Write now for free details. **T. & C. RADIO COLLEGE**, 36, Northfield Rd., Ringwood, Hants.

30/-

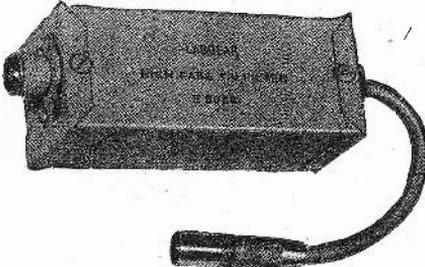FOR FREEDOM FROM TV SWAMPING INTERFERENCE FROM NEARBY TRANSMITTERS



If the interfering station operates at 30 Mc/s. or lower, use model E.5028. If it operates at 70 Mc/s. or higher, use model E.5031. Relieves interference from the following classes of stations:—Broadcast, Press, Radar, Beacon, Amateur, Aircraft, Taxis, Ambulance, Fire, Shipping, etc., etc.

AS SUPPLIED TO THE G.P.O.

Labgear (Cambridge) Ltd.
WILLOW PLACE, CAMBRIDGE Tel. 2494—2 lines

VALVES

TV. ≡ ALL GUARANTEED ≡ RADIO

4/- ≡ EF50 ≡ 4/-

SP61 2/6	BF39 7/-	EL32 7/-	EF91 7/6
EF36 4/6	EC64 4/6	6K8 11/-	EL33 12/-
EBC32 5/-	6K7 4/6	6SN7 9/-	6J5 5/-
EBC33 7/6	6SK7 5/-	6BW6 8/-	6N7 8/-
6J5 (M) 6/-	6AG5 7/-	12A6 6/6	6BW7 8/6
6AM6 7/6	6AL5 6/-	6SJ7 6/-	12J5 5/-
9BW8 9/-	2X2 4/-	1T4 7/-	6SA7 8/-
6Q7 8/6	6H6 4/-	3S4 8/-	154 7/-
6B4 5/6	1R5 7/-	6SH7 (M) 5/-	3A4 7/-
1S5 7/6	P2 6/-	6X5 7/6	5Z3 8/6
3V4 7/6	5U4 8/6	Pen223 3/-	35L3 9/-
5Z4 8/6	35Z4 9/-	Pen46 5/6	HL2 8/-
50L6 9/-	SG215 3/-	U22 7/-	807 6/-
LF210 2/6	VU39 8/6	PT15 7/-	MU2 7/-
6V6 8/6	ML4 4/6	6S10 5/6	832 17/-
TZ40 10/6	VT501 6/-	VU133 3/-	CV288 7/-
EF8 7/-	CV201 6/-	VT62 9/-	VU111 8/-
GV287 7/-	CV73 4/-	EB34 2/-	CV19 11
D1 2/-	EA50 2/-		
SP41 2/6	EF54 5/-		

U.S.A. RADAR RECEIVER CHASSIS RB9/APN4.—Less valves. Brand new. £1

CONDENSERS.—Electrolytic, B.E.C. 450 v. wkg. 8 mfd., 2/6. 8+8 mfd., 3/9. 16+16 mfd., 4/6. Dubilier, 500 v. wkg. 20 mfd., 3/-, 32 mfd., 5/-. T.C.C., etc., 5 mfd., .01, .001. Metal min., 7/- dozen. Mica, 15, 25, 100, 200, 500, .001, 6/- dozen.

POTENTIOMETERS.—Less switch, all values, 2/6 each; with switch, 1, 1.1, 2 meg., 4/- each.

RESISTORS.—Ass'd, our selection, 12/6 per 100.

CONDENSERS.—Ass'd, our selection, £1 per 100.

VINER'S (Middlesbrough)
Radio Government Surplus **Electrical**
26, EAST STREET, MIDDLESBROUGH
Telephone: MID 3418

OPPORTUNITIES IN TELEVISION



144 pages
Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointment Dept.

We Guarantee "NO PASS—NO FEE"

If you are earning less than £15 a week you must read this enlightening book.


Send for your copy NOW—FREE and without obligation.

WRITE TODAY!

British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane,
Kensington, W.8. **BIET**

MAST HEAD UNITS

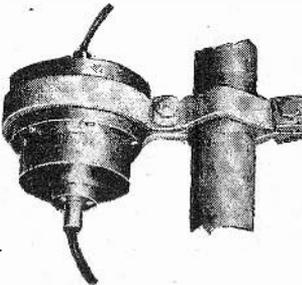(Gain approximately 15dBs. Noise factor approximately 2dBs.)



Beautifully designed and engineered. Incorporating a Cascode connected amplifier and suitable for use with all types of aerials. Supplied complete with Power supply unit and mounting bracket as illustrated. Descriptive leaflet on request.

Price complete with 40ft. £19-0-0 of special low loss feeder...

(sent carriage and packing free or available from your Dealer).

SPENCER - WEST
Quay Works, Gt. Yarmouth

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.T., SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEPherds Bush 1729

POWER UNITS. Type R7.—Rotary converter units for 24 v. D.C. input and having a twin D.C. output of 6.3 v. at 2.5 A. and 250 v. at 50 mA. Can be operated in reverse from 6 v. accumulator or D.C. mains. Totally enclosed in neat metal cases, 8 1/2 x 6 1/2 x 4 1/2 ins. in good condition and working order. PRICE: 9/6. post 2/6. or ROTARY CONVERTER only, PRICE 5/4. post 2/-.

L.T. RECTIFIERS.—Full wave bridge type. 6/12 v. 1 amp. PRICE 7/6. 6/12 v. 3 amp. PRICE 12/6. 6/12 v. 4 amp. PRICE 14/6.

L.T. TRANSFORMERS.—Primary 200/250 v. A.C. 50 cps. mains. Secondary, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 or 30 v. at 2 amp. Excellent for accumulator charging, model railways, experimental work, etc. Brand new and guaranteed, all connections clearly marked. PRICE only 18/6. post 1/6.

RECEIVERS. Type R.1155.—One of the best known and most popular of ex Government receivers. Frequency range includes 20, 40 and 80 metre "Ham" bands and Long and Medium wave transmissions. With 100 to 1 slow-motion drive, B.F.O., A.V.C., etc., and with seven valves carefully aerial tested before despatch. In good new condition and supplied in makers' transit case. PRICE £10/17/6. carriage 7/6.

R.1155 A.C. POWER PACK/OUTPUT-STAGE UNITS.—Designed to operate the R.1155 direct from A.C. mains 200/250 v. and to provide for a speaker output. Fitted with rectifier 5Z4 and 6V6 output valves and connector which plugs straight into receiver for immediate use. PRICE £3/19/6. carriage 3/6.

SPARE VALVES FOR R.1155.—Types VR30, VR100 and VR101. PRICE 8/6 each, post 6d.

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

SERVICING—HMV1807

SIR,—I was interested in your new item "Servicing TV Receivers."

A few additional points occur to me with respect to the "1807" and I wonder if it might not help to get a better coverage if other authors were invited to contribute comments in advance, the lot being collated together as an article, which would be more complete and therefore of even more value. For the "1807," for example, I could add, among others, the following:

(1) The queer effects of an intermittent O/C line hold slider (and also notes on the necessity to handle the sliders with great care).

(2) The cure of sound on vision.

(3) Although you cover the fault of the sync separator screen resistor going "high," the makers advise its replacement with a 1 watt, not a $\frac{1}{2}$ watt.

(4) Hum from H/K leaks in Z77 valves.

(5) Mention that the EA50 is replaced by a metal rectifier in many sets.

(6) Varying focus and width is often due to the .001 μ F condenser from the end of the .33 M Ω in the grid circuit of the line oscillator going slightly leaky.—D. E. WALDRONS (Gravesend).

THE SIMPLEX—AMATEUR RESULTS

SIR,—I notice in the September issue of PRACTICAL TELEVISION that Mr. J. Ward, of Southampton, is contemplating building the Simplex, but being a novice is wondering whether his efforts will be successful. May I be allowed to help to set his mind at rest?

I also am a novice, never having built even a wireless, but I have now built the Simplex and am very pleased with the results. As a matter of fact, the set is working at the present time with a single dipole aerial just propped up against my living-room wall, until I get a length of co-ax. long enough to reach to the roof.

I did have a spot of trouble getting the picture centralised on the screen, but I wrote to you and you suggested altering the values of a resistor and condenser, and that cured it.

If Mr. Ward wishes to contact me I will be only too pleased to give him any information that I can, and I hope he gets as much pleasure out of building his own TV as I have.—JAMES F. PILLING (Bury).

ENGINEER'S NOTEBOOK—A.C./D.C. HEATER WIRING

SIR,—In looking through your August edition of PRACTICAL TELEVISION I see that in your article on "Heater Wiring in A.C./D.C. Receivers," page 107, in Fig. 3 a heater chain of 10P14, 10P14, 10F1, 10F1, and U801, 20P1, 20L1, 20D1, 20D1 are put down as 150 mA valves, whereas the 10P14 and 10F1 valves are .1 amp. valves and the U801, 20P1, 20D1 are of the .2 amp. type. I suggest that if these

valves were used with the suggested currents of 150 mA, serious damage will be done to the valves.

Although the total heater current of these chains if run under correct conditions will pass .3 amp., this is suitable for running the 12AT7.—CHAS. R. BOCKING (Enfield).

(The author states: "The error here is entirely mine. The ratings of the individual valve strips are, as Mr. Bocking points out, 0.1 amp. and 0.2 amp. respectively, and the error arose through carelessly referring to a rough sketch of the system before current values were inserted.

No damage would result to an actual set-up, of course, as the dropper values given are quite correct. The 12AT7 current at 0.3 amp. is unaffected.)

MODIFYING THE R3118 AND ZC8931

SIR,—I read with great interest in the September issue of PRACTICAL TELEVISION Mr. George Twist's letter on the ZC8931. From his description of the above unit, also the fact that the code APW 4790 appears on it, I should say that it is the same unit as the Admiralty pattern W4790A responder unit Design A.

A careful study of the R3118 circuit up to the fourth IF stage, and the W4790A unit will reveal that they are similar, but various condensers and resistors are of different values, and only one R.F. stage.

I have a W4790A unit which at present I am modifying on the lines of B. L. Morley's articles on the R3118 up to the fourth IF. From that I am trying out circuitry to suit the unit, and am certain this will prove a most useful unit to the experimenter.—WM. ROBERTSON (Fife).

SIR,—Your correspondent George Twist of Liverpool, whose letter appears in the September PRACTICAL TELEVISION, is quite right regarding the ZC8931. I have two of these sets and they have not the circuit of the R3118 you published. In my sets there are 10 valves each and the description of Mr. Twist's tallics with mine. I purchased these from a firm who supplied modification data.

The sets are extremely powerful and I can receive a strong signal on an indoor cage aerial with them. However, my picture has never been sharp and I have been hoping that PRACTICAL TELEVISION would publish an article on it.

I have the modification data as supplied with the unit. I am using one for vision and one for sound.—F. J. BUSH (Exmouth).

QUERIES COUPON

This coupon is available until Nov. 21st, 1954, and must accompany all Queries.

PRACTICAL TELEVISION, Nov., 1954.

VALVES *Same Day Service*

All Guaranteed New and Boxed

1A7GT	6K8GT	9/	25Z4G	9/6	EL91	7/9
1S4	11/66K25	11/	25Z6G	9/6	EM34	11/
1C5GT	7/61D20	9/6	35L6GT	8/6	EY51	12/
1H5GT	8P25	13/6		8/6	EZ41	8/6
	11/66P28	17/	35Z4GT	8/6	EZ41	9/
1N5GT	6Q7GT	9/	35Z5GT	8/6	FW4/500	
	11/66S28GT					14/6
1R5	7/3	8/6	50L6GT	8/6	CZ32	14/6
1S5	7/3	8/6	KT63	7/8	KT63	7/8
1T4	7/3	17/		8/6	MU14	8/6
3Q4	7/3	8V6GT	7/6	80	Pen45	15/
3Q5GT	6X4	7/6	AZ31	10/	N78	15/
	10/66X5GT	6/9	CL33	11/6	PL38	22/6
3S4	7/3	7B7	DAC32	7/6	PL81	10/
3V4	7/3	7C5		11/6	PL83	12/6
5Y3GT	7/9	7C6	DF33	11/6	PY80	9/6
5Z4G	8/6	7H7	DH77	8/6	PY81	10/
6A7	10/6	7S7	DK32	11/6	PY82	7/9
6A15	6/9	7Y4	DK32	7/6	PZ30	17/
6AM3	7/9	10C1	DL33	11/6	RL12	15/
6AM6	6/9	10F1	DL35	7/8	T41	13/
6AT7	7/9	10LD11	EB91	6/9	U22	7/6
6BA5	6/6	10/	EBC33	7/6	U21	17/6
6BH6	6/6	10P13	EBC41	10/	U25	12/
6BF6	6/6	10P14	10/	U50	7/9	
6B7E	6/6	12A6	EBF80	10/	U78	8/6
6BW6	7/6	12AH8	10/	0404	9/	
6BW7	9/6	12AT7	9/	ECC81	9/	U801
6CH6	8/6	12AU6	7/6	ECH42	9/	UBC41
6C9	7/9	12AU7	10/	10/	UBF80	
6C9	7/9	12AU7	10/	10/	UBF80	10/6
6F1	10/6	12K7GT	ECL80	9/	U24	10/6
6F6G	7/6	9/	EF37A	9/		
6F12	6/9	12K8GT	EF39	6/6	UF41	9/
6F13	11/6	10/6	EF41	9/	UF42	13/6
6F15	10/6	12Q7GT	EF50	7/6	UL41	9/
6J6	8/6	9/	EF80	10/	UR3	18/
6J7GT	7/6	20D1	EF91	6/9	UY41	9/
6K7G	6/	20F2	EF92	5/6	W77	5/6
6K7GT	6/	25L6GT	EL38	22/6	X78	13/6
6K9G	8/6	8/6	EL41	9/6	Z77	6/9

Postage 4d. per valve extra. See special offer in classified advert., p. 235.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA 4587

The OSRAM

NINE - ONE - TWO

Amplifier Instruction Book and Highest Quality Components

Available from Coventry Radio

189 Dunstable Road, LUTON. Phone 2677

Book 3/6d. plus 3d. postage. Our 1954-5 Component Catalogue 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

UNIT CONSTRUCTED TV RECEIVERS

by E. N. Bradley
Full details for building units which make into complete local or long-range receivers to suit all areas, using any size tube from 3in. to 15in. Operating and fault-finding data are included. 6s. 0d., postage 4d.

The Oscilloscope and Its Applications, compiled by "Philips Electrical" Ltd. 5s. 0d., postage 6d.

Television Receiver Servicing: Vol. I—Time-Base Circuits, by E. A. W. Spreadbury. 21s. 0d., postage 9d.

Transistors and Crystal Diodes: What they are and How to Use Them, by B. R. Bettridge. 5s. 0d., postage 3d.

Mullard 5 Valve 10 Watt High Quality Amplifier Circuit. 2s. 6d., postage 3d.

Television Test Equipment, by E. N. Bradley. 5s. 0d., postage 3d.

Radio Valve Data: NEW EDITION, compiled by "Wireless World." 3s. 6d., postage 3d.

Osram 912. 3s. 6d., postage 3d.

Please write or call for our catalogue.
19-23 PRAED STREET (Dept. T.11), LONDON, W.2
Phone: PAddington 4185.
Open all day Saturday.

FIRST-CLASS TELEVISION and RADIO COURSES . . . GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE
The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M. Brit. I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ., London B.Sc. (Eng.), A.M. I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc.,** together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE
Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES.
NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

W. B. SUPPLIES

100, OLDHAM ST., MANCHESTER, 4
Tel.: Central 4246.

TERMS.—Cash with order. Orders under 20/- add 6d., over 20/- add 1/- postage. Orders despatched same day. Quote Ref. No. 21.

STRONG MAGNETERS for 6in. tubes (VCR97, etc.). 17/6.

HIGH VOLTAGE CONDENSERS, bakelite case, .003 mfd. 4 kV., .01 mfd. 4 kV., .02 mfd. 5 kV., .03 mfd. 2.5 kV., 2/- each.

TUBULAR CONDENSERS, wire ends, 1,500 volts test, non-leak, .001, .005, .05, .02, .01, .1 mfd., all at 1/- each.

SLEEPING to suit 20 s.w.g. wire, 2/- dozen yards.

YAXLEY TYPE SWITCHES,—2 pole, 6 way (2 bank), 2/3; 4 pole 3 way midgeet, 1/6; 4 pole 2 way, 2/8.

MIDGET SILVER MICA Condensers, new stock, 5, 30, 1,000 pF., 6d. each.

RESISTORS,—25 assorted in packet, 2/-.

NEON SCREWDRIVERS,—110 volts to 350 volts, 7/6.

FX BYE DARK SCREEN Filters for daylight viewing, 12in. tubes only, 13 1/2in. x 10 1/2in. x 3/8 in. perspex, 7/6. Limited quantity only.

"ELPICO" DARK SCREEN Filters for 15in. or 16in. tubes, 8/11.

E.H.T. TRANSFORMERS for VCR97, etc., 2.5 kV., 5 Mis., 2 v.-0-2 v., 2 v.-0-2 v., made to specification, 37/6.

SPEAK. FRET—Woven 12in. x 12in., 2/6; 13in. x 12in., 3/9. Expanded metal (gold), 12in. x 12in., 4/6; 18in. x 12in., 6/9.

SPEAKER TRANSFORMERS, limited quantity, 3/6 each.

RECTIFIERS,—RML, 4/-; RM2, 4/9; RM3, 5/9; 250 volts, 7s Mo/s., 7/6; Brimston CZ1, 3/6.

TIN SNIPS, 3/11. Side Cuts, 4/11. Peeler Gauges (10 Blades), 3/6. 6T. Steel Pocket Tapes, 1/6. Paddocks, 1/-. Engineers' 2ft. Folding Steel Rules, 2/6.

SELECTOR UNITS, rotary action, with relay, 3/6.


BENTLEY ACOUSTIC Corp., Ltd.,

38, Chalcot Road, N.W.1. PRImrose 9090.

024	6/	6SN7	8/6/57	8/6	ILL1920	6/6
1A3	6/	6L6 (UX7)	7/1-58	8/6	ILL192A	8/6
1D6	8/6	6U7	8/6	7/2	4/6	KP35
1G6	6/6	6V6g	7/	7/6	7/	KT2
1L4	6/	6X4	7/6	7/7	8/6	KTW62
1LD5	4/6	6X5	7/	8/3	8/	KTW63
1N35	4/6	6Z4	10/	8/6A2	10/	KZ63
1N37	7/	7C5	7/6	8/6	7/6	KT66
1S5	7/	7C6	7/6	9/55	5/	MH4
1T4	7/	7D8	6/	8/763	9/	Mspen
2D13c	4/	7H7	7/6	9/002	6/	Mvspen
2X2	4/6	7Q7	8/6	9/003	6/6	N77
3C3	4/	7RT	9/6	ACT2P	9/6	N78
3C3	10/8	7S7	7/6	ACT23	10/6	OM5
5U4	8/	8D2	2/6	AL60	4/6	PEN46
5Y3	7/6	9D2	3/	AP24	7/6	PL38
5X4	8/6	10P1	10/6	ATP4	3/	PL81
6A7	8/	10P13	10/6	BL35	7/6	PL82
6AB7	6/	11D3	6/	OB11	17/6	PM12
6AC7	6/6	12A6	6/6	LD33	8/	PM12M
6AK5	7/6	12AH7	6/6	EA50	1/6	PY80
6AM6	6/6	12AT7	7/	EAC91	9/	PY82
6AQ5	9/	12AU7	10/	EB34	1/6	Q1250
6AV6	6/	12AX7	7/	EB37	6/	Q1250
6B4B	7/	12BE6	6/6	EB38	7/6	QV47
6B56	7/	12C8	7/6	EB91	7/	RM4
6B7E	7/	12EL1	30/	ECC35	9/	SE4
6BV6	7/6	12H6	3/	ECC35	9/	SP61
6C9	6/6	12J5	6/6	ECC37	8/6	SP62
6C9B	6/6	12K3	8/6	ECC91	7/8	SP41
6D6	6/6	12N37	7/	EJ35	12/	TP22
6F1	10/6	12SK7	6/6	EJ38	10/6	UF42
6F17	9/6	12SQ7	6/6	EP36	4/6	UB121
6F93	9/6	12SR7	7/6	EP39	6/6	UF41
6H6g	2/6	12Z5	8/6	EP91	6/6	UR3
6J5	5/	13D1	8/	EP91A	3/	UR3
6J6	7/6	14H7	10/6	EP54	6/	UY4
6J7g	5/	14R7	10/6	EP80	10/	UY41
6K6g	7/	15D2	4/	EJ2	12/6	U403
6K7g	5/	18	8/	EJ32	8/6	VP2
6K8g	3/	19H1	10/	EP91	6/6	VP2B
6L5	7/6	19H4	35/	EJ38	20/	VP4
6N7g	6/6	12N37	6/6	EJL91	6/6	VP23
6Q7g	8/6	20	7/6	EM34	10/	VP41
6R7g	8/	35L6	8/	EP31	11/	VR53
6S47	8/6	48	7/6	EP91	7/6	VR50
6S17	6/	42Mpt	15/	FC2	10/6	VT501
6SK7	6/6	42	8/6	FC13	9/	X24
6SL7	8/	50V6	8/6	H30	7/6	X56

Post 6d. each. 24 hour G.O.D. service. All guaranteed. Complete list free S.A.E.

An OPPORTUNITY

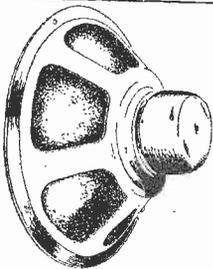

to secure a super quality TRUVOX BX.11 12in. moving coil permanent magnet loudspeaker at a bargain price. Brand new in maker's carton. Available in 3 ohm speech coil only. Limited quantity at the special price while stocks last of

ONLY 50/- carriage paid.

Our full list of loudspeakers will be sent on receipt of your name and address and 2½d. stamp.

HOME RADIO OF MITCHAM

187, London Rd., Mitcham, Surrey MIT 3282



QUALITY TELEVISION COMPONENTS

SCANNING COILS
6/10 kV. R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS
LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

IT'S 60% CHEAPER!! to construct your own aerial, whether TELEVISION or YAGI

Write for our catalogue, illustrating all fittings, prices, etc. Included in the range we offer Alloy Masts, Insulators, Reflector and Director rod holders, Mast head fittings, together with formulae, useful construction hints for designing your own aerial, etc.

Send 9d. in stamps to cover the cost of postage and catalogue to —

Fringevision Ltd.

MARLBOROUGH, WILTS.

Phone : 605.

Introducing the — TYANA TRIPLE THREE



Reg. Design No. 867804

MAKE SOLDERING A PLEASURE
SMALL SOLDERING IRON

Complete with detachable BENCH STAND 19/6

The smallest high-power soldering iron. Length only 8 1/2"; adjustable long bit dia. 3/16"; mains voltages 100/110, 200/220, 230/250.

The "STANDARD" Popular Soldering Iron now reduced to 14/11.

Replacement Elements and Bits for both types always available.

KENROY LIMITED

152/297 UPPER ST., ISLINGTON, LONDON, N.1.
Telephone : Canonbury 4905-4663.

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH
CALL OR SEND DRAWINGS
FOR QUOTATION

B. KOSKIE

(DEPT. B)

72-76 Leather Lane,
Holborn, E.C.1

Phone : CHAncery 6791/2

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP,
WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:

36, ROSEBURY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester,
Birmingham, Leeds.

"No Quantity too Small"

TELEVISION COMPONENTS

always in stock for the
P.T. LYNX, TELE-KING
P.T. SUPER-VISOR
THE E.E. TELEVISOR
AND VIEWMASTER

Separate price lists available.

**NEW! RADIO AND
TELEVISION
COMPONENT CATALOGUE**
available on request to

J. T. FILMER,

Maypole Estate, Bexley, Kent
Tel.: Bexleyheath 7267

HIGH GRADE TRANSFORMERS

FOR ALL PURPOSES
SINGLY OR IN QUANTITIES
TO YOUR SPECIFICATION
VARNISH IMPREGNATED
BAKED WINDINGS
WITH OR WITHOUT TAG PANELS
GOOD DELIVERIES

Our rewind dept. will handle your
Repairs promptly and efficiently.
S.A.E. with enquiries please.

P. HOWORTH

(Dept. P.T.)

51 POLLARD LANE - BRADFORD
Tel.: 37030

TELEKIT SUPPLY

MAIL ORDER DEPT.


Chantry Lane Works, Chantry Lane,
Bromley, Kent. Phone: Rav. 5245.

Please mention P.W. and enclose 6d. postage
VALVES, NEW & SURPLUS, GUARANTEED.

OZ4	4/-	6BA6	6/6	9D6	6/6
1L4	5/6	6BE6	6/6	11D3	6/-
1LN5(soiled)	5/-	6BR7	7/6	12A6 1299	
1S5	6/-	6BS7	7/6	(soiled)	5/-
1Y4	6/6	6BW6	6/6	12BE6	7/-
1U5	6/-	6CH6	6/6	6SH7(soiled)	5/-
3Q4	7/6	6J5	5/-		5/-
3V4	8/6	6V6	7/-	15D2	4/-
5Y3	8/6	6X4	6/6	19AQ5	10/-
6AB	8/6	6X5	7/6	AL60	4/6
6AL5	7/6	7D5	6/6	CM401	6/6
6AM6	6/-	7D8	6/6	EP50	5/6
6AT6	7/6	7H7	6/6	VR21	3/6
6B8	8/6	7S7	6/6	W77	6/6
		9D2	5/-	1B24	50/-

BECKENHAM, KENT

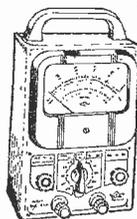THE SHOP FOR THE CONSTRUCTOR
NOW OPEN AT 104, HIGH STREET.



PULLIN
SERIES 100
TEST METER
AC/DC 10,000 μV
21 RANGES
100 μA to 1000 V
COMPLETE IN DIE-CAST
CASE WITH TEST LEADS
CLIPS AND PRODS
FULLY GUARANTEED

SENT POST FREE FOR £2.10s.
DEPOSIT AND TEN FURTHER MONTHLY
PAYMENTS OF £1. CASH PRICE 11GNS

Frith
RADIOCRAFT Ltd
69-71 CHURCH GATE LEICESTER
PHONE 58927

If you can't build a set yourself . . .

Why not take advantage of the manufacturing experience of the people who supply radio and television equipment to more than one hundred countries of the world and buy yourself an 'English Electric' receiver?

New models include 17in. rectangular screen Rotomatic 12-channel turret type tuning, in a circuit design that you could not better.

You can see a full range of models at your local 'English Electric' dealers, or we will gladly supply full spec and sample Hire Purchase terms on request. Write to :

ENGLISH ELECTRIC

Bringing you Better Living

The ENGLISH ELECTRIC Company Limited,
Domestic Appliance and Television Division, East Lancashire Road, Liverpool, 10.