

THE "SIMPLEX" MAGNETIC MODEL

PRACTICAL TELEVISION

AND TELEVISION TIMES


A NEWNES PUBLICATION

Vol. 5 No. 56

JANUARY, 1955

1/-

EDITOR
F. J. CAMM

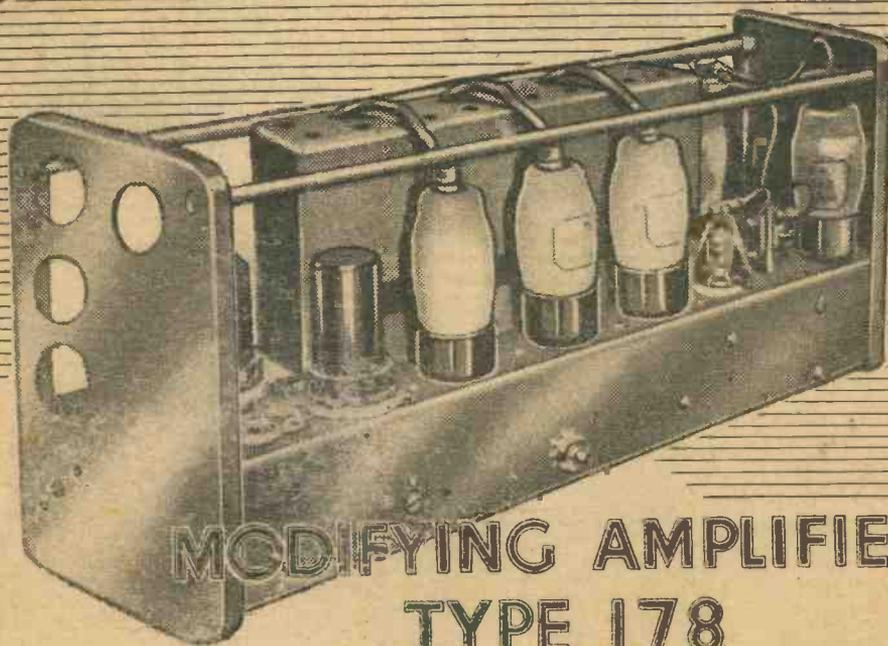

MODIFYING AMPLIFIER
TYPE 178

FEATURED IN THIS ISSUE

Changing to the New
Stations
Positive or Negative ?
Using the Responder Unit

Making TV Coils
Fault Symptoms
Interference on Band III
Your Problems Solved

THE COMPACT TELEVISION AERIAL BY ANTIFERRENC LTD.

Supplied complete with universal mounting and backplate in neutral brown finish. Overall length 5ft. 6in. Packed in carton 3ft. 4in. long. Complete with full instructions. Cat. No. C24. Original price 50/-.


CHOKES

20H, 250 Ohm, 60 mA. Clamp construction... 6/- ca. 10H, 200 Ohm, 30 mA. Clamp construction... 9/3 ca. 5H, 250 mA., 200 Ohm. Fully shrouded... 18/3 ca.

TRANSFORMERS FOR BATTERY CHARGER

230 v. Input Tapped 0-12 v. 1 amp... 13/6 ca. 230 v. Input Tapped 0-12 v. 3 amp... 18/- ca. (Both with tap on Primary for 2.5 v. Pilot light.)

LOUDSPEAKER CABINETS

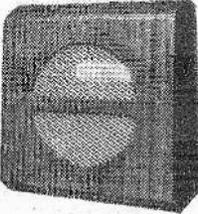

This attractive walnut finished cabinet is available for 8 1/2 in. or 9 in. speaker units. Metal speaker feet, complete with back and rubber feet. 6 1/2 in. type: Measures 8 1/2 in. x 8 1/2 in. x 4 1/2 in. at base. Price 15/6 each. 8 in. type: Measures 10 1/2 in. x 10 1/2 in. x 5 in. at base. Price 18/6 each.

CARRYING CASE

Suitable for use as a processor or recording case, size 7 1/2 in. x 9 1/2 in. x 3 1/2 in. Internal dimensions: 1 1/2 in. long, 1 1/2 in. deep, 3 1/2 in. front Ht., 8 1/2 in. rear Ht. With a black rexine finish. Weight 8 1/2 lb. Post and packing 2/6. 13/6 ca.

"CLEM" Travelling Iron with Asbestos Stand.

Size 4in. x 2in. x 2 1/2 in., including handle, complete with lead and switch to enable it to be used on any voltage between 110 and 250 v. A.B.C. adaptor is fitted on the lead. (Colour as available: Blue, Green, etc.)... 17/6 ca.

SENTERCEL RECTIFIERS

RM1, 3/9 ea.; RM2, 4/2 ea.; RM3, 7/- ea.; RM4, 16/- ea.

METAL RECTIFIERS

12 v. 1 amp, 3/6 ea.; 12 v. 1 amp, 4/6 ea.; 2 v. 1 amp, 3/6 ea.; 250 v. 45 mA., 6/3 ea.; 250 v. 75 mA., 7/6 ea.; 300 v. 60 mA., 7/6 ea.

TERMS: Cash with order or C.O.D. Postage to be added to orders as follows: 9d. up to 10/-; 1/- up to 20/-; 1/6 up to 40/-; 2/- up to £5. MAIL ORDER ONLY: Send 6d. in stamps for illus. catalogue. When ordering please quote "Dept. P.T.V."

ALPHA FOR VALVES

GUARANTEED NEW AND BOXED.

Table listing various vacuum tube types and their prices. Columns include tube type, price, and other specifications.

CONDENSERS MOULDED NICA

.0001 .0002 .0003 .0004 .0005 .0007 .0008 .001 .002 .003 .005 01 50 PF. All 4d. each.

CONDENSERS

The following is a selection from our stocks of manufacturers' surplus condensers all by well-known makers, DUBILIER, B.T., BCC (BIRSWAN), SPRAGUE, etc.

Table listing various capacitor types and their prices. Columns include capacitor type and price.

Table listing various capacitor ranges and their prices. Columns include capacitor range and price.

Table listing various tag boards and their prices. Columns include tag board type and price.

Table listing various group tag boards and their prices. Columns include group tag board type and price.

Table listing various mains transformers and their prices. Columns include mains transformer type and price.

Table listing various 3-way mounting type MT1 primary and secondary transformers and their prices.

"ALPHA" FOR SETS OF VALVES

Ten V1R1 (EF50) Valves Ex. Brand new units, 6/- each, 45/- set. 6K84, 6K74, 6Q7G, 5Z4G, 6V6G, 37/6 set. 1R3, 1S5, 1T4, 1S4, or 3V4 or 3S4, 30/- set. 6K8C, 6K7G 9Q7G, 25A0C, 25Z4G, 37/6 set. 12K6G, 12K7G, 12Q7G, 35Z4GT, 35L6GT, or 50L6GT, 37/6 set. Ten 6AM6 (6E91), 75/- set. 7B7, 7B7, 7C5, 7C5, 7Y4, 42/- per set. ECH42, EF41, ER04, EL41, LZ40, 50/- per set. LCH22, LF41, EB04, EL41, UC41, 36/- per set.

MAINS DROPPING RESISTORS

72 Ohm Welwyn 2 section 40 Ohm 32 Ohm ... 1/9 ea. 72 Ohm Erie tap at 600 Ohm ... 1/6 ea. 650 Ohm taps at 375 Ohm 500 Ohm 3 Ohm 30 Ohm ... 2/6 ea. 770 Ohm Mains Dropper for Midget Radios with a tap at 125 Ohm size 3in. long x 1in. dia. ... 1/3 ea. Dagleo Mains Dropper 3A, cement coated with 2 sliders ... 3/6 ea. 2 amp. as above 1,200 Ohm ... 3/9 ea. Green, Vitreous Mains Dropper 1,200 Ohm 2 taps ... 1/3 ea. Zenith Mains Dropper 910 Ohm ... 2/- ea.

SOLDERING IRONS

Solon type 964 Fitted Oval Bit ... 19/11 ea. Solon type 968 Fitted Pencil Bit ... 19/11 ea. Both 5 pips are complete with approx. 6ft. of Henley 3-core cable and are suitable for 230/240 v.

PANELS, etc.

Resistor and Condenser Panels, over 50 items guaranteed, including wire wound resistors ... 4/- ea. Resistor and Condenser Panels, over 36 items guaranteed ... 2/6 ea. Tagboard, latest type vertical mounting, with resistors and condensers ... 1/- ea. Tagboard, containing 2 watt Resistors, wire wound resistors and condensers ... 2/- ea.

ALPHA RADIO SUPPLY CO. 5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.

HENRY'S

(RADIO LTD.)

We have over 20,000 American and B.V.A. valves in stock.
ALL VALVES NEW AND GUARANTEED.

SETS OF VALVES
Ten EF50 (Ex-Brand New Units), 5/- each ... 45/- Set
6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G ... 37/6 ..
1R5, 1S5, 1T4, 1S4, or (8S4 or 3V4) ... 26/6 ..
TP25, HL23/DD, VP23, PEN25 (or QP25) ... 25/- ..
6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 or 25Z6G ... 37/6 ..
12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT or 50L6GT 37/6 ..
12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35L6GT or 50L6GT 37/6 ..

1D8GT	10/-	6AM6	9/-	12SA7GT	8/6	EF36	6/6	ISP41	4/-
1A7GT	12/6	42	8/6	12SQ7GT	8/6	EF39	6/6	D11	5/-
1H5GT	10/-	43	8/6	12S7GT	8/6	EK32	6/6	VP23	6/6
1NSGT	10/-	75	8/6	12SK7GT	8/6	EL32	7/6	HL23DD	6/6
1CSGT	10/-	89	8/6	12SRT	7/6	EF50 (Red)	7/6	TP25	8/-
1Q5GT	10/-	6L6G	10/-	6D6	6/6	Syl.)	10/-	PEN25	6/6
1ASGT	10/-	6Q7GT	8/6	6C6	6/6	HL2	3/6	QP25	6/6
1S5	7/6	6S07GT	8/6	6A7G	8/6	LP2	5/-	QP21	8/-
1S4	7/6	6S7GT	6/6	6A8G	8/6	KT2	4/-	TP22	8/6
1T4	7/6	6S7GT	8/6	1Z40	37/6	VP2	8/6	ATP4	4/-
1R5	7/6	6SNTGT	8/6	0Z4	7/-	5F2	8/6	MS/PENB	7/6
334	7/6	6SNTGT	9/-	25Z6G	8/6	TDD2A	8/6		
3V4	7/6	6SL7GT	9/-	25Z6G	8/6	VP2E	8/6	MS/PEN	7/6
1LN5	8/-	6SCT	10/-	35Z4GT	8/6	215SG	4/-	VP4 (5 or 7)	7/6
1LD5	8/-	6V6G	7/6	35Z5GT	8/6	889A	15/-		8/6
5U4G	8/6	6V8GT	7/6	35L6GT	8/6	354V	5/-	AC/PEN	
5Z4G	8/6	6F6C	7/6	50L6GT	8/6	1D1	4/6	(5 or 7) 10/-	
6Z3G	8/6	6AC7	6/6	25A6G	8/6	8D2	4/-	FC13C	10/-
MU14	8/6	6AG7	12/6	KT39C	10/-	8D2	4/-	FC13s/c	10/-
6B8	7/6	6CSGT	5/-	KT86	12/6	PEN46	7/6	AC/PEN	6/6
6K8G	9/-	6J5GT	5/-	EBC33	8/6	AC/PEN	6/6	PENDD4023	6/6
6K7G	6/6	12A6	7/6	EF34	6/-	VP41	7/6		12/6
6V7G	6/6	12K7GT	8/6	EB34	3/6	TH233	10/-		12/6
6V7GT	7/6	12K8GT	8/6	EA50	2/-	4IMP	7/6	VT501	7/6
6L7	7/6	12Q7GT	8/6	D1	2/-	5P51	4/-	U19	10/-

CRYSTAL MICROPHONE INSERTS



8/6 POST FREE

Ideal for tape recording and amplifiers. No matching transformer required.

Brand New R.F. UNITS
RF24 20-30 mc/s 15/- post free
RF25 40-50 mc/s 19/6 post free
RF26 50-65 mc/s 35/- post free
RF27 60-80 mc/s 35/- post free

INDICATOR UNIT TYPE 182A
This unit contains VCR517 Cathode Ray 6in. tube, complete with Mu-metal screen, 3 EF50, 4 5P61 and 1 5U4G valves, W/W volume controls, resistors and condensers. Suitable either for basis of TV or Oscilloscope. Radio Constructor's Scope constructional circuit included. 67/6 (plus 7/6 carr.).

CATHODE RAY TUBES (Brand New)
VCR97 (slight cut-off) 15/-
VCR97, guaranteed full TV Picture ... 40/-
VCR17C, guaranteed full TV Picture ... 35/-
VCR139A, guaranteed full TV Picture ... 35/-
3BP1 guaranteed full TV Picture... 30/-
Carr. & Packing on all tubes, 2/-


DENCO F.M. FEEDER UNIT
Finest Audio available. Complete kit of parts, including drilled chassis, 5 valves - types 6AM6, 12AB3, EB91 and 2 6AB6. Also complete circuit and wiring diagram. 28/7/6. Or assembled and aligned, 48/10/- Alignment only, 10/-.

INDICATOR UNIT BC929A
Complete with 3BP1 and 7 valves: 2-6SNTGT; 2-6E46, 6X5GT; 2X2 & 6G5. Black crackle case 14in. x 9in. x 9in., 65/-, Carr. 5/-. In absolute new condition.

931A PHOTO-CELLS
as described in "P/T" Nov. issue. 50/- each. Data supplied. Equivalent to Mazda 27M/2.

28-page Catalogue, 3d. Open Mon.-Sat. 9-6. Thurs. 1 p.m.

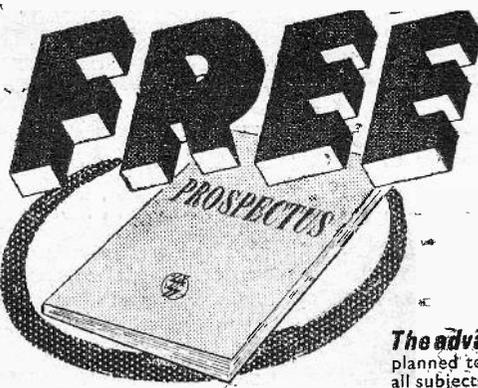5, HARROW ROAD, PADDINGTON, LONDON, W.2 TEL.: PADDINGTON 1008/9, 0401.



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME
City and Guilds Grouped Certificates in Telecommunications; A.M.Brit.I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY. COURSES WITH EQUIPMENT
With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Equipment supplied upon enrolment and remains your property.
Courses from 15/- per month

POST THIS COUPON TODAY

Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 138K, 43 Grove Park Road, London, W.4.

NAME _____
ADDRESS _____
1/5P SUBJECT(S) OF INTEREST _____

EMI INSTITUTES
The only Postal College which is part of a world-wide Industrial Organisation.


BUILD THIS HIGH QUALITY LOW COST AMPLIFIER

★ Circuit designed by Mullard research engineers.

★ Specified components available from most radio dealers.



Here's an entirely new amplifier circuit which brings high quality sound reproduction within the reach of thousands more enthusiasts. It has been designed by Mullard research engineers with special regard for easy construction and low cost. Full details of the circuit are included in the 2/6 book which is obtainable from radio dealers or direct from Mullard Ltd. Valve Sales Department—2/10 post free. Get your copy now.

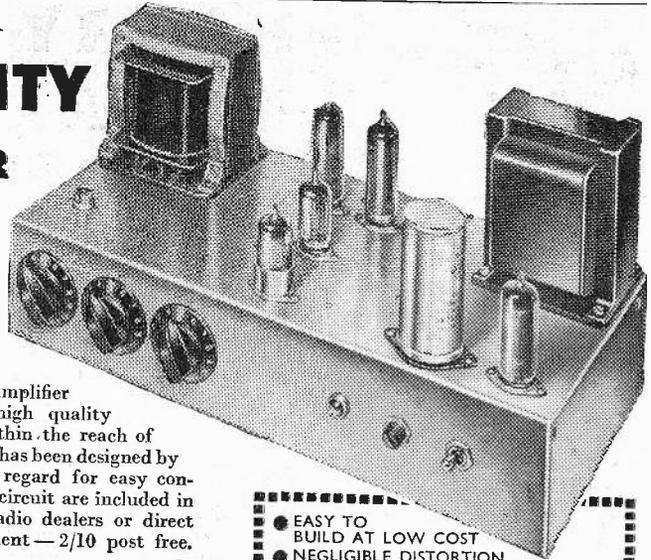

- EASY TO BUILD AT LOW COST
- NEGLIGIBLE DISTORTION AT ALL OUTPUT LEVELS
- UNIFORM FREQUENCY RESPONSE IN AUDIBLE RANGE
- GOOD TRANSIENT RESPONSE
- LOW OUTPUT RESISTANCE
- LOW HUM AND NOISE
- DESIGNED ROUND 5 MULLARD MASTER VALVES — EF86, ECC83
2 x EL84, GZ30 or EZ80

Mullard



MULLARD LTD., CENTURY HOUSE, SHAFESBURY AVENUE, LONDON, W.C.2

MVM308A

Supreme in Service

'MICROMITE'

DRY ELECTROLYTIC CONDENSERS


These small but high quality electrolytics have proved so popular that the range has been greatly extended. The use of high-gain etched foil electrodes keeps size and weight down, making the condensers suitable for suspension wiring. Conservatively rated; long shelf life ensured; green plastic insulating sleeving prevents short-circuits.

Capacity in μ F.	Peak Wkg. Volts	Surge Volts	Dimns. in Ins.		Type No.	List Price Each
			Length	Diam.		
50	12	5	1 1/8	3/8	CE87B	2/9
25	50	60	1 1/8	3/8	CE88DE	3/-
1	350	400	1 1/8	3/8	CE86L	2/6
8	350	400	1 1/8	3/8	CE99LE	3/3
16	350	400	2 1/8	3/8	CE91LE	4/-
32	350	400	2 1/8	3/8	CE93LE	6/-
4	450	550	1 1/8	3/8	CE99PE	3/3
8	450	550	1 1/8	3/8	CE90PE	3/6
16	450	550	1 1/8	3/8	CE92PE	5/-
32	450	550	2 1/8	3/8	CE94PE	7/6




THE TELEGRAPH CONDENSER CO. LTD

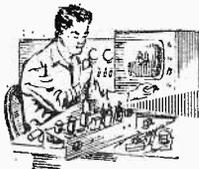RADIO DIVISION: NORTH ACTON · LONDON · W.3 · Telephone: ACOrn 0061



Practical Television

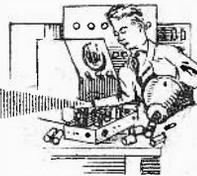

& TELEVISION TIMES

Editor: F. J. CAMM

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363.
Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 5 No. 56

EVERY MONTH

JANUARY, 1955

TelevIEWS

TV RECEIVER INTERMEDIATE FREQUENCY

AS a result of investigations, made by B.R.E.M.A. in consultation with the G.P.O., an announcement of a recommended intermediate frequency for television receivers of 34.65 Mc/s with a high oscillator has been made. It is the subject of a report prepared for the industry by a B.R.E.M.A. panel formed specially for the purpose.

The TV industry in general have endorsed the recommendations which have received the approval of the G.P.O. It should, however, be made clear that the choice of an intermediate frequency must rest solely with the individual receiver manufacturer, who must have the same liberty in design as he has in the selection of a particular circuit. The designer naturally bases his circuitry in accord with a number of technical and economic factors, not the least of which is that it must satisfy public need.

Too much significance should not therefore be attached to the B.R.E.M.A. recommendations. Indeed, it would be misleading to do so. Members of the public may safely continue to choose their TV receivers without reference to the I.F. used. A great deal of confusion over this matter has been caused by a G.P.O. statement on the protection of amateur wavebands, and it has led some members of the public to believe that the incidence of interference from amateurs is high.

The truth is that hundreds of thousands of television receivers in use to-day have an I.F. in the vicinity of the amateur waveband and are operating quite satisfactorily without interference from that source. It is pointed out that provided the designer's receiver is satisfactory, and amateurs keep their harmonics within the prescribed limits, there is no reason to expect such interference.

The B.R.E.M.A. report therefore means that 34.65 Mc/s is a preferred frequency towards which designers should veer in future development. Some manufacturers are making receivers

to this frequency, and no doubt in the course of a few years such an I.F. will become standard.

WEAK COMMERCIAL TV ?

COMMERCIAL TV is to make its debut next autumn, and it is thought in some circles that the signals will be so weak that only a small percentage of present televiewers will be able to receive the alternative programme. It is suggested that commercial TV will be restricted to an area of about 35 miles radius of the transmitter. When the Manchester station opens which will radiate programmes via the BBC Holme Moss transmitter, it is doubtful whether Blackpool, Southport or any other north-west coastal resort will be able to receive the programmes. Liverpool and Preston are in the fringe area, where reception cannot be guaranteed, and Chester will be out of range. On the other hand, most of the industrial areas of Lancashire will be able to watch I.T.V., but only half of Cheshire, a small part of Yorkshire and less than half of Derbyshire.

The suggested reason for the weakness of the signals as compared with those radiated by the BBC from the same mast is that the BBC works on Band 1, while I.T.V. has been relegated to the much less satisfactory Band 2. In its early days, at least, commercial television may not be able to employ the equivalent power of the latest BBC transmitters—100 kW.


When the three stations—Manchester, Birmingham and London—are operating at full strength, it is expected that I.T.V. programmes will reach an area of population of 30 millions, which is about 50 per cent. of the BBC's coverage.

In the meantime, political controversy still rages around this thorny subject in the House of Commons.

The Postmaster-General is satisfied about the power of I.T.V. But politics itself has extended its influence into radio, which we have always considered to be a retrograde step.—F. J. C.

The SIMPLEX

Magnetic Model

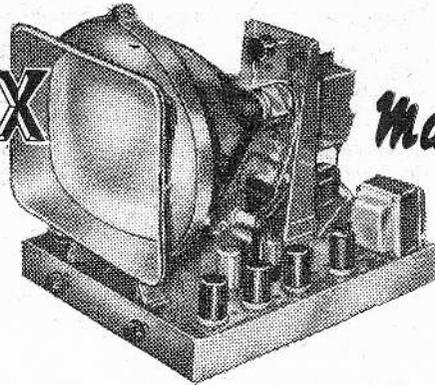

A FOUR-WAY tag strip is mounted on the tube holder for terminating the scanning coils and another one-way is used for mounting the width control.

On the other side of the holder a one-way tag strip is fitted to hold R43.

The periphery of the holes cut for the neck of the C.R.T. should be bound with plastic tubing slit down the centre. The outer covering of a piece of coaxial cable is very suitable for this purpose.

Under no circumstances should the edge of the bar metal come into direct contact with the glass of the tube.

MR6 and CM6 are mounted directly on the base of the transformer.

MR1 and MR2 are mounted at right angles to each other and soldered directly between the line transformer and CM8. If mounted in this manner they are well protected and accidental contact during the preliminary running-in period is thereby avoided.

Soldered connections in the E.H.T. stages should be made very carefully and the joints finished with well rounded blobs of solder. No sharp points should exist as these will set up corona discharges.

VRM1 with CM7 and the width control are mounted on the tube rear support.

The wiring can now be completed and then carefully checked before proceeding to Stage VI.

STAGE VI (M)

The final stage has now been attained and it is very short. The mains transformer and smoothing choke should be mounted in their positions and the rectifier holder wired in. R43 can be fitted in position (this belongs, of course, to the original power pack).

Separate tubular condensers have been used for smoothing so they can be conveniently mounted beneath the chassis.

The transformer input is connected in parallel with the vision mains transformer input and the mains supply taken via the filter to the switch.

After this work is completed the scanning coils can be wired in to the tag strip on the tube support using flexible leads.

The tube can be wired using a valveholder to suit type of tube...

DETAILS FOR CONVERTING THE SIMPLEX TO MAGNETIC TUBE

(Continued from page 295 December issue)

C.R.T. Heater

C.R.T.s fall into three main classes so far, as the heaters are concerned; they are 2 volt, 4 volt and 6.3 volt. Some tubes are designed to be used on A.C./D.C. receivers and have larger voltage ratings, but we are not concerned with them here.

If a 4-volt tube is used the supply can be obtained from the transformer. T1 using the spare 4-volt winding. This winding can

also supply the sound output stage where fitted. If the tube has a cathode-heater short a separate transformer is not required.

When a 6.3-volt tube is used then the heater supply can be taken from the normal 6.3-volt line of the time-base amplifier from T2 mains transformer. If the tube has a cathode-heater short then a separate transformer must be used and this can be a heater-to-heater type or a mains type.

A 2-volt tube requires a separate transformer either of the heater-to-heater (type 6.3 volt to 2 volt) or a direct mains type. It does not matter if a cathode-heater short exists in this case.

If a heater transformer is required it can be mounted on the rear support of the tube above the smoothing choke.

Note that V13 is wired in the heater chain from

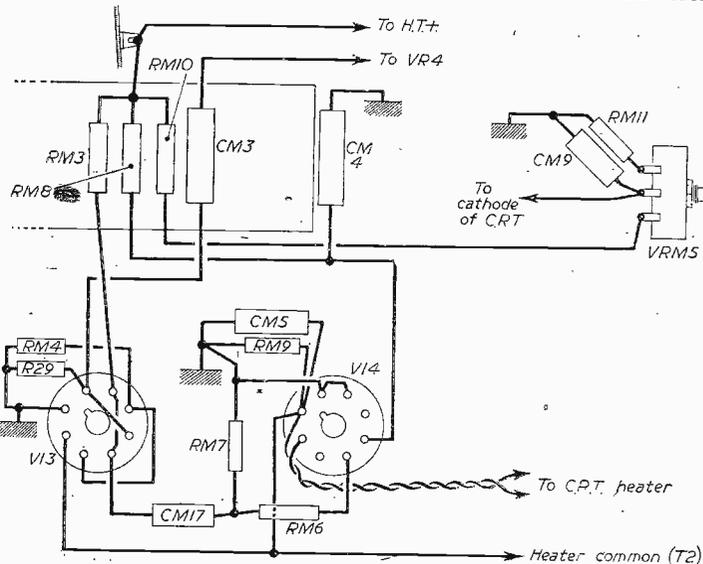


Fig. 12.—Under-chassis wiring of line amplifier and brilliance control.

Positive or Negative?

THE ADVANTAGES OF BOTH FORMS OF E.H.T. SUPPLY

By S. A. Money

THE polarity of the E.H.T. supply must be decided upon before any piece of equipment using a cathode-ray tube is built. Why bother to use a negative supply at all? As a matter of fact it is possible to use positive E.H.T. almost every time, but in some cases it is much more convenient to use a negative supply. Consideration of the advantages and disadvantages of the two types of supply will make it easier to decide which polarity will be best for any particular circuit.

First, let us look at the negative supply. There are two points regarding negative supplies which might well be clarified. Some people may get the impression that because negative supplies are so called they are less dangerous than the positive variety. That is not true. A shock from a negative supply can be just as painful as one from a positive supply. It is the voltage that does the damage, and it makes no difference whether it is positive or negative with respect to earth.

Another point that some people cannot, at first, understand, is how a cathode-ray tube can work when its anode is earthed. The explanation is that the operating voltages on the tube are always referred to the cathode of the tube. If the anode voltage is stated as 2,000 volts then the anode must be made 2,000 volts positive to the cathode. If the anode is at earth then the cathode will have to be 2,000 volts negative to earth. Under those conditions the tube will work normally.

Negative

Negative E.H.T. is most useful in those circuits where signals are applied to the deflector plates of an electrostatic cathode-ray tube. These deflector plates are normally held at or near the anode voltage, which in this case is earth potential. The coupling condensers to the plates need only be of low working voltage. This point becomes increasingly important as the frequency of the signals is reduced and the value of the coupling capacity is increased. It is much easier to obtain a large capacity at low working volts than one which will withstand several thousand volts.

In some applications, such as low speed oscilloscopes where the sweep may last for several seconds, it is often necessary to use direct coupling to the plates. This only becomes practicable if the plates are at or near earth. Direct coupling is often used when measurements of voltage have to be made on circuits where a normal voltmeter would give false readings due to its shunting effect.

A Disadvantage

One disadvantage of using a negative supply is that it is necessary to use an isolated supply for the tube heater. The heater-to-cathode insulation is usually only rated at about 100 volts. Because of this one side of the heater is generally tied to the cathode through a high value resistor. The heater transformer supplying the tube must, therefore, be capable of withstanding the full value of the E.H.T. voltage. Such transformers tend to be large and expensive, their cost rising rapidly as the E.H.T. voltage is increased.

Since the tube grid is connected to the E.H.T. line at the negative end there is quite a high resistance between it and earth. This allows a certain amount of stray signal to be picked up on the grid. This stray signal shows up as variations in the brilliance of the trace. If another signal is being applied to the grid such pick-up can be very troublesome.

It should be remembered when designing the chassis that the focus and brilliance controls are at or near the E.H.T. potential. Therefore, it becomes necessary to mount them on insulated brackets and to insulate the control spindles from the earthed chassis.

When signals are applied to the tube grid it is sometimes necessary to make use of a D.C. restoring diode. If a valve is used its heater supply must be isolated from earth in the same way as the tube heater. In most cases it is possible to run the two heaters from the same winding by choosing a diode having the same heater voltage as the tube.

Positive

Positive E.H.T. is generally used in those circuits where it is an advantage or a necessity that the cathode of the tube should be at or near earth potential. This arrangement is invariably used with tubes of the magnetically deflected type such as those used in television receivers. These tubes have only two electrodes to which signals can be applied. These are the grid and cathode. It becomes much easier to apply the signals to these electrodes if they are near earth than if they are at some high voltage.

Another advantage of an earthy cathode is that the heater supply can also be earthed without fear of a breakdown between the heater and cathode. This removes the need for a special isolating transformer since the tube heater can be operated from the common heater line of the set.

In television work the video signals are often directly coupled from the anode of the video amplifier to the tube cathode. By doing this the D.C. component of the signal is retained and no D.C. restoration is necessary. In order to do this the cathode must be made about the same voltage as the anode of the video valve. This can only be done if the E.H.T. supply is made positive.

Summarising we see that positive E.H.T. is generally used for television receivers, especially those where a magnetic tube is used. Negative E.H.T. is generally used in oscilloscopes since it makes the coupling of signals to the deflector plates relatively easy. For television receivers using electrostatic tubes either polarity can be used, the choice depending on the components to hand or personal preference.

A NEW HANDBOOK

"PRACTICAL TELEVISION CIRCUITS"

288 pages, 156 illustrations

15/- net or 15/6 by post from:


GEO. NEWNES, LTD.,

Tower House, Southampton Street, Strand, W.C.2.

NEW SERIES

Servicing

TELEVISION RECEIVERS

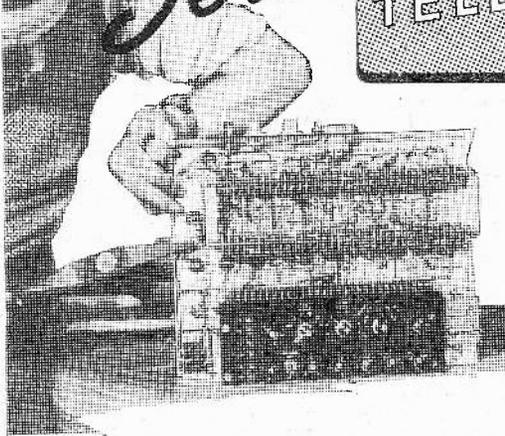

No. 5.—H.M.V. 1803-4, 1805-6,
2806, ETC.

By L. Lawry-Johns


E.H.T. Smoothing

THE 1803 15in. console was built soon after the war and contained an essentially pre-war chassis with the addition of the Z66 and other valves. The chassis was also used in the 1804 table model with a 10in. tube and re-distributed controls. The main cause of trouble in these sets is undoubtedly the frequent failure of the Z66 valves, but once a good set has been installed, quite long periods of trouble-free operation can confidently be expected. These valve troubles are usually quite obvious and need not be considered further.

If the owner of one of these sets has not had a new tube since the original, a word about this could be of value, as the original type of tube is no longer supplied, and has not been for a considerable time. The replacement tube for the 1803 is a TA15J. Now the J is rather important as it concerns the shape of the bulb of the tube. In addition, a small modification is necessary, and the J type tube carton should contain the small kit of parts and instructions. These items are necessary owing to the altered position of the focus coil assembly, the tube base, springs, etc.

The 1804 replacement is the TA10 and the fact that both this and the TA15 are tetrode tubes must be remembered, and the extra supply taken from the focus coil tag to the first anode of the new tube base. It may be thought that the E.H.T. of the set which is under 4 kV. would not be sufficient for the proper working of aluminised replacement tubes which normally require 7 kV. However, the picture obtainable with this low voltage is as good as that with the original tube and unless extensive re-designing of the line timebase is carried out no attempt at boosting the E.H.T. should be made.

One fault that regularly occurs with these sets (and any others that employ transformer E.H.T. circuits) is the appearance of a band of bright illumination along the bottom of the raster. This may come and go at irregular intervals, or may appear and remain. This is due to the E.H.T. smoothing condensers becoming defective and the following suggestion should be considered before purchasing new ones. The condensers fitted are two .03 μ F 4 kV. mounted on the top of the chassis on the left side and are both fixed to a common plate. It is the writer's opinion that more reliable operation of this circuit is achieved by the use of a single .1 μ F condenser of 5-7 kV. rating. This should be secured by a suitable clip in place of the unit, leaving a space for the E.H.T. cable to be passed through the chassis. This cable may be connected to the top of the E.H.T. bleeder resistor tube leaving the smoothing resistors in the circuit, and incidentally whilst this operation is being carried out the bleeder resistors should be tested to ensure that they are still fulfilling their purpose of discharging the condenser when the set is switched off. *Never* touch the E.H.T. components until this condenser(s) has been discharged to chassis with a screwdriver, the handle of which is well insulated. This is necessary as the bleeder network often goes OC leaving the condenser

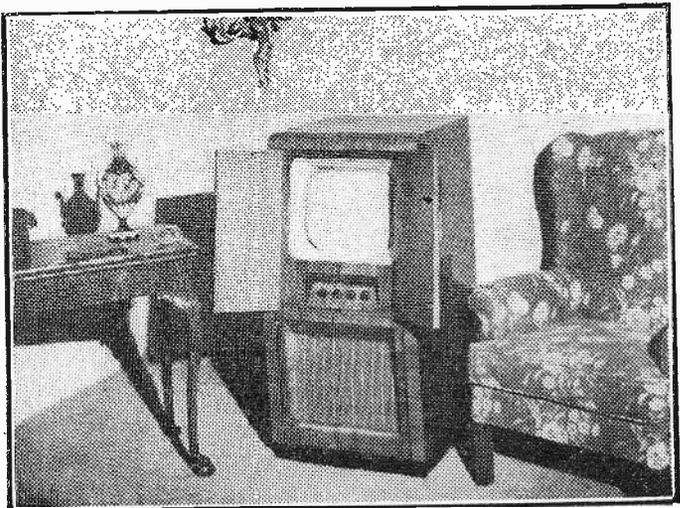

An H.M.V. receiver, model 1806.

charged and *lethal*. Defective condensers in this position may also show themselves by "snowstorm" effects on the screen most often with a crackling on the sound.


Other effects although less usual include that of the raster taking on a wedge-shaped appearance. This of course in more up-to-date sets is usually an indication of leaky scan coils. A "snowstorm" effect may also be caused by a resistor in the bleeder chain breaking down. All these effects of faulty E.H.T. components may in some circumstances be affected by the operation of the contrast and brightness controls.

1805, 2805, 1806, 2806, Etc.

These receivers employ a rather more up-to-date circuit using Z77 vision and sound amplifiers with the exception of the video which is a Z66 and the audio which has an L63 and KT61 sound output. The detectors and limiters are D77 double diodes and the sync. sep. line oscillator and frame oscillator employ Z66 valves which with the video amplifier make a total of four valves of this type used in this receiver.

The E.H.T. circuit is similar in design to the previous 1803 with the exception of the higher voltage, 7 kV, to supply the TA10 in the 1805 and TA15 in the 1806.

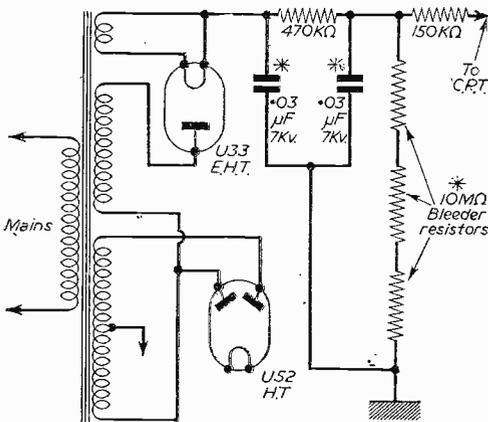The same E.H.T. faults may be expected and the modification of fitting a single condenser in place of the two .03 μ F can be adopted if trouble comes, remembering that the .1 μ F fitted must be rated at 7 kV. or over.



Components likely to be faulty are marked thus *

Fig. 1.—E.H.T. circuit of the 1805 model which may be used as a guide for the 1803.

The diagram of the circuit shows that one end of the E.H.T. winding is connected to the high side of one H.T. secondary winding on the mains transformer. This circuit may be used in following the design of the 1803 with the exception of the type of E.H.T. rectifier fitted and the voltage ratings of the condensers. Trouble with the line or frame timebases can nearly always be traced to a defective Z66 valve and sometimes a valve in this position can be changed for the central sync. separator as this is already operating under limited conditions and a slightly low

oscillator valve may operate quite adequately as a sync. separator.

Dark hum bars across the raster may often be caused by a heater-to-cathode leak in the Z66 video amplifier. If this is the case it may be changed with one of the oscillators or the sync. sep. As these valves have their cathodes strapped to chassis a leak does not affect them. When replacing either of the Z66 oscillator valves it will be found that the new valve, if recently purchased, has a metal base. In the case of the frame oscillator, the valve base is mounted so

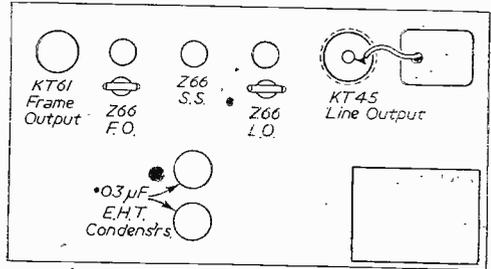


Fig. 2.—Plan view of lower chassis of the 1805 model, showing the position of components mentioned in the text.

close to the blocking oscillator transformer that one of the tags of this touches the base of the valve. As this is an H.T. tag, the reason for these words is obvious. Either the valve may be changed for the sync. sep. or the video amp., or the metal base must be covered with insulating tape. In the former case, it is assumed of course that the valves concerned do not have metal bases!

It is suggested that the tubes be rotated a little at, say, six monthly intervals to compensate for heater sag. This of course applies to most receivers and a useful length of life may be added to a tube by this means. The idea is that with a tube in a permanent position the wires that feed the heater do sag downwards after a lengthy period and many cause trouble, but by periodic rotation of the tube the risk is minimised. As the E.H.T. supply on these receivers is transformer supplied from the mains no variation of picture size or flaring should occur with varying brightness levels. If this does happen it points to a defective U33 E.H.T. rectifier, although flaring at high brightness level, or contrast, may indicate a failing tube.

As the latest 266 valves have plastic bases the necessity of insulating the metal is obviated when replacing these valves in the timebase of the 1805-6.

Eighth Edition

WIRELESS TRANSMISSION

By F. J. CAMM
6/-, by post 6/4

From
**GEORGE NEWNES, LTD., Tower House,
Southampton Street, Strand, W.C.2.**

Using the Responder Unit

HINTS ON ADAPTING A POPULAR EX-GOVERNMENT UNIT FOR BAND I
AND BAND III RECEPTION

By R. E. Jones

(Continued from page 313, December issue)

IF it is intended to build a separate timebase chassis, L5 and R59 can be fitted on the outside of the receiver chassis. R40, R58, C43, C63 were used in the author's case for a 12in. electromagnetic tube. R58 and C63 feed the sync-separator and can therefore be on the timebase chassis. C43 and R40 were in the lead to the cathode of the C.R.T. and were fitted across the C.R.T. base.

Sound Rejectors

The rejection provided by the sound take-off coil proved sufficient, but if further rejection is found necessary the most suitable place to fit rejectors is in the cathode circuits of V5 and V6.

Contrast Control

It will be found that the cathode circuits of the I.F. valves have 100 ohm bias resistors across the valve bases. Those on the sound channel are already earthed. Those on the vision channel, however, are "commoned" and should at this stage be "floating," having been left so when the "gain" socket was removed. The "commoned" ends of these three bias resistors should be wired to the conventional type of contrast control. As this gives control of three stages, VR1 should be of low value (say 500 ohms). Alternatively, the first stage only can be controlled, the cathode resistors of the other two stages being earthed. In this case VR1 should be 2 k. It might be found that slight instability occurs at the maximum setting of the contrast control. This can be overcome by increasing slightly one of the fixed bias resistors.

The Sound Channel

A sound input coil has to be fitted. A small Haynes type coil can fit neatly in close proximity to V7. A hole should be drilled in the top of the can to allow exit for the wire to the top cap of V7. Details of the coil (L6) are given in the separate table. Tuning of L6 is by the iron-dust slug. In setting up the sound channel it may be necessary to make C48 variable. The frequency of the sound channel is to be approximately 10 Mc/s. In theory it is necessary to shunt the other two I.F. coils by extra capacitance in order to lower the frequency to $3\frac{1}{2}$ Mc/s less than the vision I.F. In practice, however, it was found that one coil could be adjusted on the iron core without the need for a capacitor. On the other coil a 20 pF capacitor was necessary. Sufficient gain was obtained by removing the tuned circuit damping resistors. Further gain can be obtained, if required, by removing one of the two 10 k load resistors in each can.

To utilise valves which were to hand, it was decided to use a DH63 and a 6V6 for the audio stages. This meant changing the valve bases of V10 and V11 from MO to IO type. The simplest procedure here is to recover all wiring and completely

COIL WINDING DETAILS

L1.— $\frac{1}{2}$ in. diam. Aladdin former. Winding length, $\frac{1}{4}$ in. Wire gauge unimportant.

Channel	No. of turns	Tapped from earthy end
1	8 $\frac{1}{2}$	1 $\frac{1}{2}$
2	7 $\frac{1}{2}$	1 $\frac{1}{2}$
3	6 $\frac{1}{2}$	1 $\frac{1}{2}$
4	5 $\frac{1}{2}$	1
5	5	1

L2.— $\frac{1}{4}$ in. diam. Aladdin former. Winding length $\frac{1}{4}$ in. Wire gauge unimportant.

Channel	No. of turns
1	9
2	8
3	7
4	6
5	5

L3.— $\frac{3}{8}$ in. diam. Polythene o. Paxolin. 20 s.w.g. enam. close wound.

Channel	No. of turns	Oscillator frequency
1	15	32
2	10	38.75
3	9	43.75
4	8	48.75
5	6	53.75

L4.— $\frac{1}{2}$ in. diam. Paxolin tube, 200 turns, 40 s.w.g. enam. winding length, $1\frac{1}{4}$ in.

L5.— $\frac{1}{2}$ in. diam. Paxolin tube, 180 turns, 40 s.w.g. enam. Winding length, $1\frac{1}{4}$ in.

L6.—Haynes type former (with can). Approx. diam. 0.3in., 25 turns, 32 s.w.g. enam. Winding length, $\frac{3}{8}$ in.

rewire. If economy is of importance, however, the existing valve bases can be left in place and the spare P61 and SP61 can be used in these stages.

Owing to the physical layout of the components it was found that the most suitable circuit for the audio and output stages was one similar to that used in the Lynx receiver. This allows the DH63 diode load and filter to be fitted inside the last I.F. can, and a short lead out of the top of this can connects to the top cap grid of the DH63. The existing EA50 was used as a noise limiter and its position in the circuit is following the DH63.

R.F. Unit for Band I

This was built up on a small aluminium sub-chassis, 3in. wide and equal in length to the depth

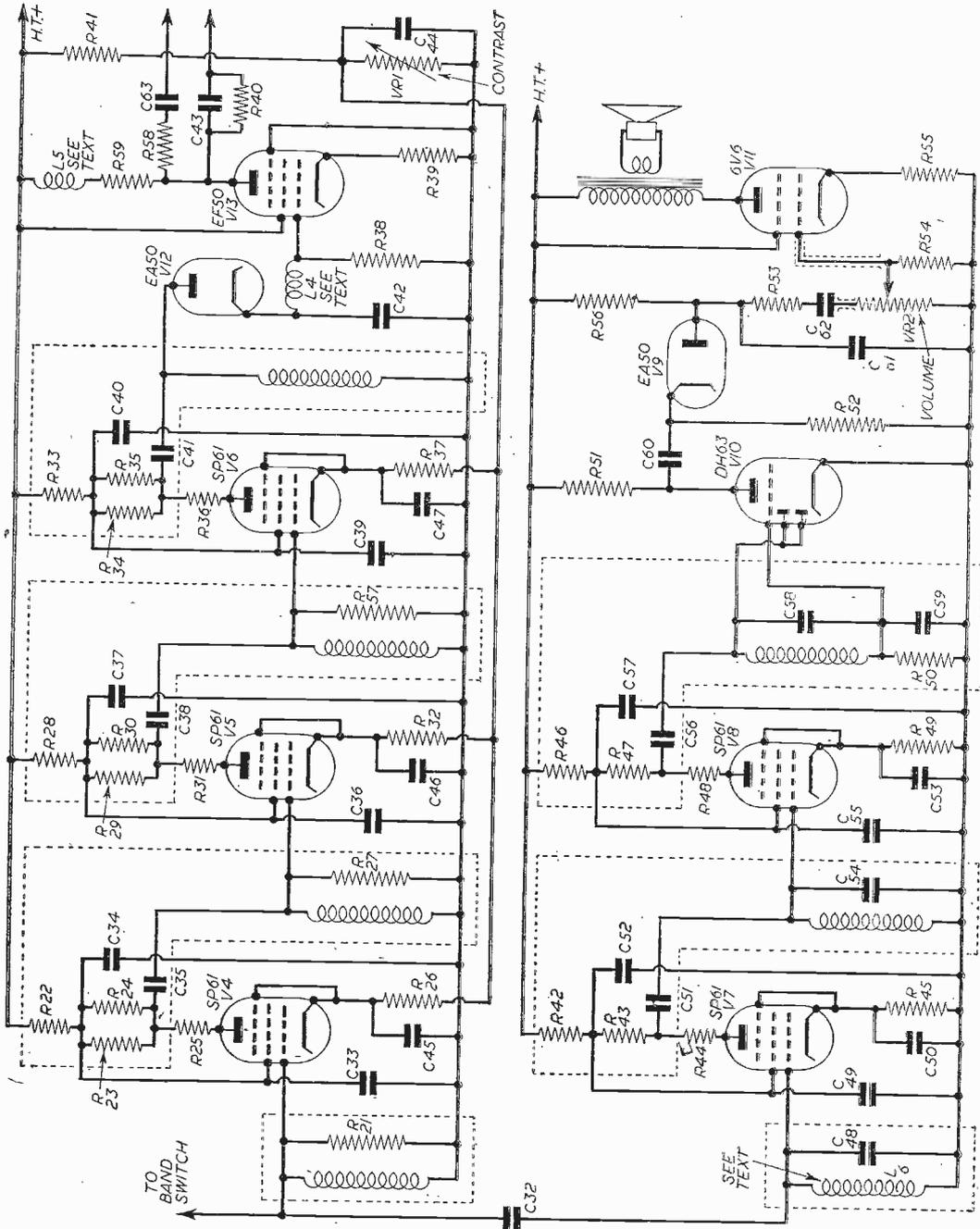


Fig. 6 — The completed, modified, video and sound receivers. The input marked "To Band Switch" is connected to the switch through condenser C63. A complete list of values was given in last month's issue.

of the unit. It consists of an R.F. amplifier (EF54), mixer (EF54) and oscillator (EC52) in line along the chassis. The oscillator valve is arranged to be at the front of the chassis and the R.F. amplifier at the rear. This allows the oscillator tuning control to appear at the front of the receiver similar to the three Band III tuning controls. The idea is, eventually, to have a flap in the front of the cabinet so that these controls are easily accessible. The circuit is shown in Fig. 5. The coils L1 and L2 are wound on $\frac{1}{4}$ in. diam.

Aladdin formers in small aluminium cans. Owing to the screening of the cans, no further screening was found necessary. The connection between the oscillator grid and the mixer grid (via C19) was taken in a few inches of coaxial cable, C19 being fitted at the V15 end of the cable.

An alternative to building the R.F. unit would be to use one of the surplus "Cydon" 5-channel tuners now advertised. This has not been tried by the writer, but no difficulties are foreseen in its use.

The Rowridge Transmitting Station

THE new Rowridge transmitting station operates on Channel 3 (Vision 56.75 Mc/s, Sound 53.25 Mc/s).

Built on a 26-acre site 470 ft. above sea level and $3\frac{1}{2}$ miles west-south-west of Newport near the Calbourne road, Rowridge, is the first of the five medium-power stations to be equipped with permanent transmitters. It is part of the BBC's 18-station plan to provide a television service for 97 per cent. of the population of the United Kingdom. Initially, Rowridge uses a temporary mast and aerial, and its service area will be somewhat less than that expected when the permanent mast and aerial system are brought into use next autumn. Nevertheless, it is expected to provide a reliable service to approximately two million people.

Vision Transmitter

The main vision transmitter, manufactured by Marconi's Wireless Telegraph Co. Ltd., is of the low-level modulated type with a peak white output of 5 kW. Modulation is carried out at the 500 watt level and the signals are then amplified by two class "B" wide-band linear R.F. amplifiers each using a pair of forced-air-cooled triodes, type BR191, made by the English Electric Company. The appropriate shaping of the vestigial side-band signals radiated by the vision transmitter is carried out entirely by its own tuned circuits, and not by a separate vestigial side-band filter. The valve filaments are A.C. heated, with the exception of those in the modulated amplifier and the linear amplifiers, which derive their supply from metal rectifiers. The transmitter H.T. supplies are obtained from hot-cathode mercury-vapour rectifiers, which provide a maximum of 3,000 volts for the anodes of the linear class "B" amplifier stages.

Sound Transmitter

The sound transmitter, also manufactured by Marconi's Wireless Telegraph Co. Ltd., is of the conventional class "B" modulated type and is rated at 2 kW output. The output power will be adjusted to 1.25 kW to maintain the standard ratio of 4:1 in terms of vision to sound power. All valve filaments are A.C. heated. As in the case of the vision transmitter, the crystal-controlled drive and the power-conversion equipment are built as an integral part of the transmitter.

Both transmitters are contained in similar sheet steel cubicles mounted side by side, and so present a single continuous front in the transmitter hall.

The air blast cooling equipment and combining filter are mounted behind the transmitter cubicles which are built into a sound-proof partition wall so as to isolate the noise of the air blowers from the control desk situated in front of the transmitters.

Controls

The two transmitters are controlled and monitored from this desk, which incorporates a built-in waveform monitor and two picture monitors in addition to the conventional controls and meters. The provision of the two picture monitors enables the incoming signals to be compared with those radiated. Programme switching for both sound and vision circuits is accomplished at this desk. The controls of each transmitter are sequence interlocked to ensure that the various supplies are applied in the correct order and, where necessary, with the appropriate time interval between each. Adjacent to the control desk are the vision and sound programme input equipment bays, and the test waveform generating equipment which provides a variety of signals for testing, lining up and maintaining the characteristics and performance of the vision transmitter.

The low-power standby transmitters operate on the same frequencies as the main transmitter and have a rated power output of 500 watts vision and 125 watts sound. These are manufactured by Standard Telephones and Cables Ltd.

Links

The vision programme reaches Rowridge from London via a Post Office repeater station at Alton in Hampshire. Here, special receivers intercept the vision signal radiated from Alexandra Palace. The signal is then re-radiated by a microwave link transmitter and is received by Post Office equipment installed at Rowridge. From this the video signal is passed to the BBC vision input equipment.


Ultimately two microwave links will be available, one normally acting as spare to the other, and they will be reversible so that outside broadcasts from the Isle of Wight may be relayed to the mainland for connection to the main television distribution network.

The sound programme travels to Rowridge over special G.P.O. telephone circuits including a submarine cable between Southampton and the island.

Aerial

The receiving aerial and reflector for the Alton-Rowridge microwave vision link are located at the 60ft. level on the temporary 200ft. self-supporting tower. This tower also carries the two dipoles forming a simple two-stack array which serves as the temporary vision and sound transmitting aerial for Rowridge pending completion of the permanent mast and aerial system. These are mounted at the 175ft. level, whilst at the very top are located aerials for receiving the television programmes from the high-power transmitter at Wenvoe should the normal programme route fail.

Fault Symptoms

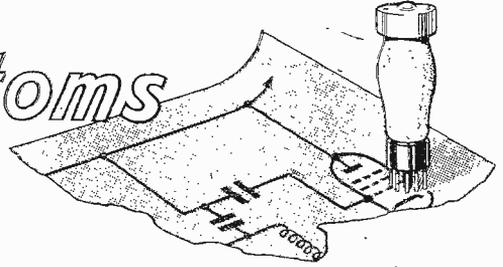

THE CAUSES OF COMMON FAULTS, AND METHODS OF CORRECTION

By Gordon J. King, A.M.I.P.R.E.

(Continued from page 320, December issue.)

Instability

TO revert back to the rectified oscillation potential across the detector load resistor; this potential is, of course, directly coupled to the control grid of the video amplifier valve, which is thus driven heavily positive. As a result a large anode current flows in the valve and associated video amplifier load resistor, causing the video amplifier anode potential to fall considerably. This reduction in potential is reflected directly to the cathode of the picture-tube (assuming cathode modulation) and looks to the tube very much like a peak-white picture signal.

As a consequence the tube lights up very brightly as the potential at its grid is probably slightly more positive than the potential at its cathode, meaning that, in certain cases, screen illumination may be in evidence even at minimum setting on the brightness control.

Apart from the more obvious symptom of excessive tube brightness and lack of picture, internal examination will often reveal the video amplifier valve anode load resistor to be operating very hot; this, of course, is due to the large anode current.

One stage oscillating only slightly—in the vision channel, for instance—may not wipe the picture out completely, but frequently causes the display of

pattern interference that cannot be attributed to any external source, and that can be made to alter in form by adjusting the contrast control. Nevertheless, even slight instability will register at the vision detector to give rise to a mean D.C. potential due to the oscillation, and this, as we have already seen, arrives at the control grid of the video amplifier valve as a positive potential. Although of insufficient magnitude to over-drive the picture-tube, this oscillation potential is almost bound to outbalance the grid bias on the video amplifier valve with a consequent loss in picture contrast ratio.

Sometimes slight oscillation occurs in the vision channel at a frequency removed from the vision carrier frequency or sound I.F. so that heterodyne patterns, normally associated with slight instability, are not displayed.

In a case like this what generally happens is that the operating point of the video amplifier valve is shifted slightly—due to the bias neutralising effect of the oscillation potential—and the picture tends to resolve somewhat "flat"—as though the vision noise limiter is adjusted to "clip" on peak-whites.

We would point out that this symptom can readily deceive unless one happens to be well versed in the characteristics of the receiver concerned, for it might well be thought that the effect could be caused by more or less anything *but* instability!

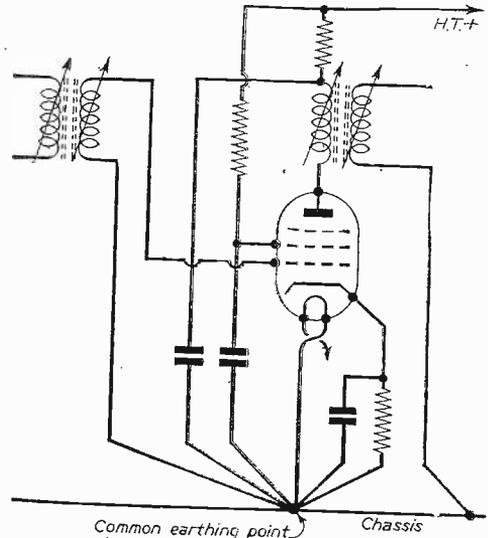
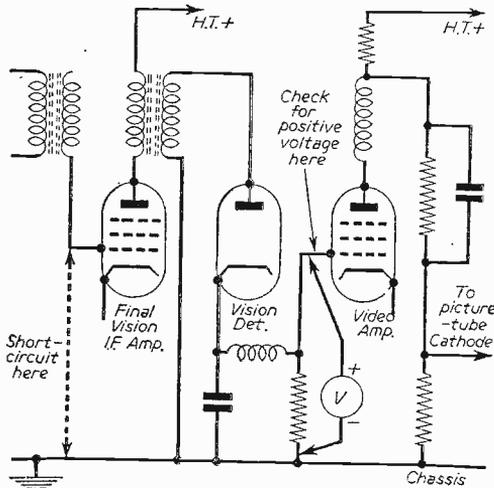


Fig. 79 (left).—A test for instability. Fig. 80 (right).—When replacing decoupling capacitors, ensure that they are returned to the common earthing point.

A Test

A quick test to prove whether the vision R.F./I.F. channel is oscillating is by measuring the potential across the vision detector load resistor, or at the control grid of the video amplifier valve—relative to chassis—with a high resistance voltmeter. If there is any tendency for the meter needle to swing in a positive direction, the control grid of the final vision I.F. amplifier valve should be short-circuited to

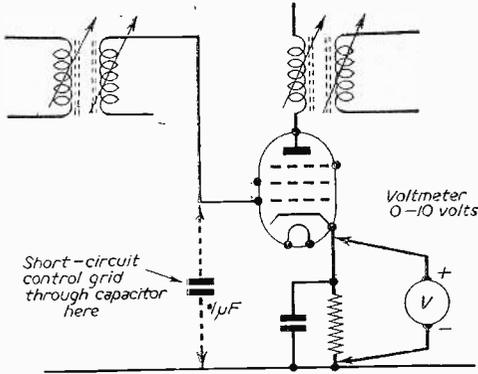


Fig. 81.—A method to prove which stage is oscillating.

chassis whilst observing the voltmeter reading (see Fig. 80). If, by suppressing oscillation by this means, this results in the needle swinging back to zero, then, almost certainly instability is occurring in the vision channel.

To prevent any spurious needle deflection due to picture signal, and to avoid any alteration in receiver characteristics that may occur by removing the aerial, it is often desirable to perform this test when the BBC is off the air.

The Ferguson 991T receivers would appear prone to this trouble, and in a large number of cases it is due to a defective EF80 valve operating in the vision I.F. channel. On several occasions, however, a similar symptom has been caused by deterioration in a decoupling capacitor associated with the vision I.F. channel. Also, in this particular receiver, the crystal diode employed as vision detector (located within the final I.F. can) sometimes develops a fault

that is conducive to the symptom of a "flat" picture without severely detracting from the overall definition—which means, therefore, that extra special care may be demanded in establishing the actual cause, since the two symptoms are more or less of the same character.

Some receivers are much more prone to instability than others. The old Invicta T101 series, for instance, often exhibit the effect when the contrast control is advanced beyond a certain critical point. To maintain good stability on this receiver it is essential to ensure that the general alignment is kept up to standard, and this applies particularly as the R.F. valves age, and after valve replacement.

It is also most important to make certain that the copper screens underneath the chassis are making good electrical contact to the chassis, and that all the screws are used to secure the screens in position—an elusive bout of instability on one of these receivers was eventually traced to one loose screen securing screw!

There are times when both the sound and vision channels go unstable. This generally occurs when the stages common to both services turn into an oscillator. In such cases the set might well remain perfectly stable at a low contrast control setting, or if the sensitivity control is somewhat retarded. This fault would appear to be more in evidence in areas of low signal strength where a high or maximum contrast/sensitivity setting is demanded. Apart from the instability effect on a picture, as the gain of the set is advanced a "plop" is heard from the loud-speaker and the sound signal disappears completely. Under these conditions the contrast and/or sensitivity control performs a function analogous to the old-time reaction control; indeed, the same effect results in both cases.

Receivers which have a tendency to go unstable easily usually demand that the aerial feeder and aerial system possesses an excellent impedance match to the aerial terminals, particularly where high gain working is necessary. In fringe areas, where a receiver might be working "flat-out," a gradual tendency towards instability is sometimes provoked by deterioration in the aerial and feeder systems. A fault of this nature is immediately revealed when the set stability holds on a different aerial system.

As previously intimated, an alteration in the characteristics of a valve—or valves—can often be

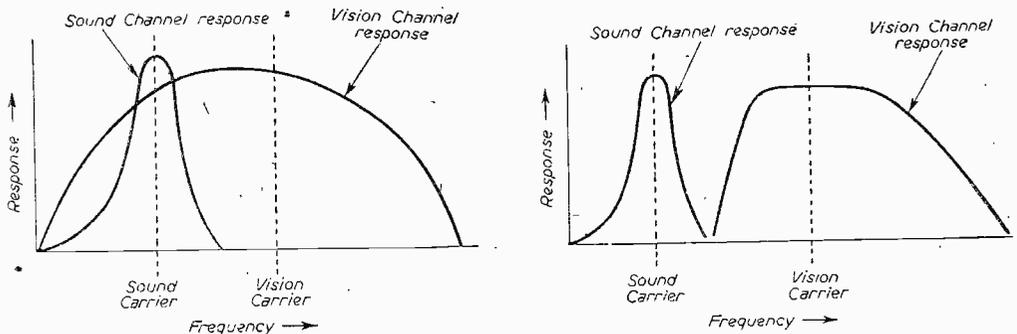


Fig. 82 (left). —Diagram showing how the vision channel response is liable to embrace the sound frequency and cause sound interference on vision. Fig. 83 (right). —The employment of a sound rejector provides a sharp cut-off at the low-frequency side of the vision channel response.

proved responsible for unstable operation. Sometimes an actual defect occurs in a valve to incite conditions for instability, whereas, in other cases, it is the alteration in valve characteristics which tends to modify the frequency of an associated tuned circuit, and thus disturb the overall alignment.

Special care must be taken to avoid misplacing circuit wiring and components appertaining to the R.F./I.F. stages during the process of repairs and general adjustments. Such inadvertent circuit disturbances might well be sufficient to induce positive feed-back in the high frequency section of a receiver that tends to be critical from the stability aspect.

Often an experimenter clears a certain fault in a television receiver, only to find on test that another fault has somehow or other been introduced unwittingly. After consulting our "Query Service" in despair, the experimenter eventually establishes that the second fault—which is often instability or low sensitivity—was instigated during the course of the original repair, when, for instance, it was necessary to disturb the R.F./I.F. wiring to permit easy replacement of a defective part—all would have been well if the experimenter had made a special point of rearranging the wiring.

Check Dubious Connections

After a receiver has been operating for several years without attention the symptom of intermittent instability may develop. This can often be stopped and started by gently tapping the cabinet. Removing the back of the cabinet and wiggling each valve in turn in its holder will nearly always prove the trouble

caused by poor connections between the valve pins and the valve holder sockets and, in some cases, aggravated also by poorly fitting valve screening cans. (To be continued.)


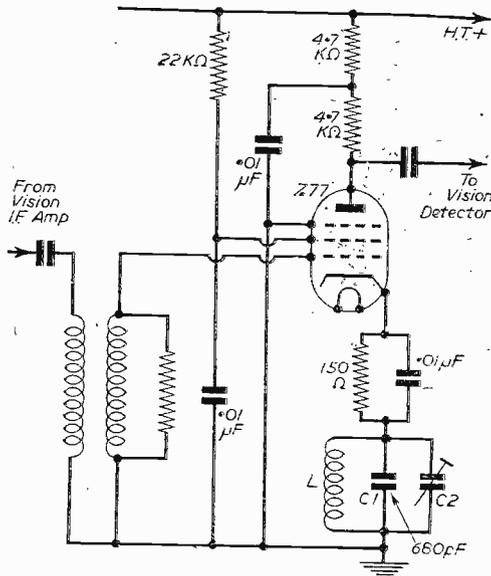


Fig. 84.—A cathode sound rejector circuit as used in G.E.C. BT1091 series receivers.

Further Notes on the Diamond Aerial

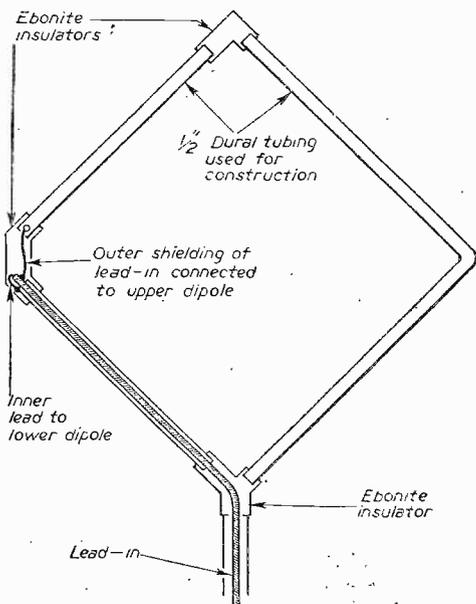THE "Diamond Television Aerial" in November's issue of PRACTICAL TELEVISION, has drawn a deal



The self-supporting "Diamond" aerial.

of correspondence. One of the most common queries was the correct length to make the dipole and reflector.

The lengths and angles were worked out to give, as near as possible, an impedance of 70 ohms at a frequency between vision and sound, so that the standard coaxial feeder can be connected straight to the aerial. If the lengths are kept the same and the angle reduced from 45 degrees to 40 degrees, to the vertical, the aerial impedance is also reduced to about 60 ohms. If the angle is further reduced to 35 degrees, the impedance goes down to between 40 and 50 ohms. The length of the spreader being reduced accordingly, of course. This is as far as the angle can be altered without reducing the efficiency of the aerial considerably.

The average "H" aerial has an impedance of about 50 ohms and the 70-ohm feeder is normally connected directly to the aerial; so the non-technical reader will see some mismatch is acceptable.

The correct lengths to cut the "diamond" for different channels are as follows:


	Each Half of Dipole	Reflector
Channel 1 (London) ...	5ft. 5in.11ft. 10in
Channel 2 (Holme Moss) 4ft. 6in.9ft. 6in.
Channel 3 (Kirk o' Shotts) 4ft. 2in.8ft. 10in.
Channel 4 (Sutton Coldfield) ...	3ft. 9in.8ft.
Channel 5 (Wenvoe) ...	3ft. 6in.7ft. 5in.

A Spalding reader who has made this self-supporting "Diamond" aerial, claims very satisfactory results from it.—R. PINKNEY (Fareham).

Making TV Coils

HINTS ON PRACTICAL METHODS OF WINDING COILS FOR
ALL TYPES OF TV RECEIVERS

By W. J. Delaney

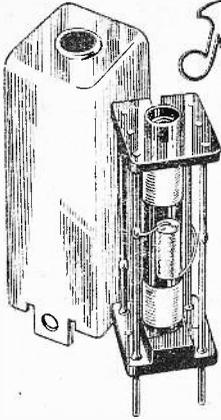



MOST home-made receivers call for the construction of the necessary coils, and constructors appear to find difficulty in either interpreting the instructions or in actually carrying out the constructional work. Many experimenters, too, fail to make full use of the equipment which they have available owing to the difficulty of obtaining suitable coils. A number of samples of coils and home-made receivers which we have seen have given poor results, simply because the coils have been badly made. There is nothing really difficult in making these components, and, in fact, they can be made by the beginner to be every bit as efficient as those which are produced by commercial firms, provided certain details are borne in mind.

Firstly, let us consider the materials which may be used. Popular with the cheaper and simpler types of receiver are the Aladdin small formers shown in the group on page 352. These merely need two fixing screws and a clearance hole for the core. They will, however, only accommodate a single core and therefore the range of coils and control is restricted. Ex-government coil formers of the clear polystyrene type, with a single core attached to an adjusting screw may also be used, but suffer from the single core restriction. Undoubtedly the most satisfactory type of former is the large component seen in the group, which is available with screening can. This type of coil is available in two lengths, but it is a fairly simple matter to cut down the long former if desired—although even if a single short coil is wound, there is no need to reduce the size of the former. The screening can is provided with two lugs, which, if bent inwards, enable the can to be attached to the chassis by the same screws which hold the coil former in position. The drawback to this is that if the can is to be removed in order to make some change in the contents, the entire coil will be loosened. The lugs may therefore be bent outwards and then the former may be left rigidly held whilst changes are made in the windings or other parts. A further, and most important advantage of these coil formers, is that the windings may be rigidly and simply attached by means of the side wires, and coupling condensers, parallel resistors, etc., may be placed inside the can, enabling a much more stable receiver to be constructed. A typical coil of this type is seen in the illustration. Modern receiver designs often call for coupled coils giving a type of band-pass characteristic with sharply peaked resonance points, but covering a fairly wide frequency band—say a full 3 Mc/s. This often means that there must be a primary and a secondary, one or both of which must be shunted by a resistor to obtain the necessary flattening of the

response, plus a coupling coil. Constant coupling may be required, irrespective of the tuning of the two coils, and with the type of long former mentioned, the primary and secondary may be wound at the extreme ends, separate cores used for peaking, and the coupling winding placed at some point between them where the core will not provide any additional modification to the coupling. The resistors are mounted on the side wires, together with a coupling condenser, if needed, and the whole totally screened.

Windings

So far as the actual windings are concerned, the term "spaced" windings appears to offer some difficulties, especially to the newcomer. As a general rule it means that the turns of wire are spaced from each other by a space equivalent to the thickness of the actual wire used for the coil. The simplest way of obtaining the desired effect is to take a former of the required size and very roughly wind round the number of turns called for, hold the end of the wire and then let it slip off. In this way you will have a rough idea of the length of wire which will be needed. Cut two such lengths. Lay these side by side and wind both on together, attaching the ends as required—either with wax, cement or by soldering to the side wires. At the end, or when the cement is dry, remove one of these windings, and this will leave a neatly spaced coil as called for. As an alternative, the large formers shown are provided with an internal thread for the cores which is exactly OBA. If, therefore, a length of OBA rod is mounted on a support and one of these coil formers is threaded on to the rod, a length of wire may be anchored into position, and by holding this with one hand in a fixed position, and rotating the coil former with the other, the wire will be laid on with a spacing equivalent to the thread

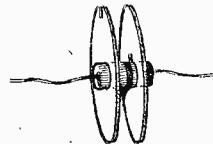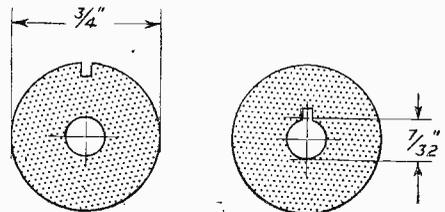

Details of Construction of Video Peaking Chokes. The cheeks are made from card or paxolin, and mounted on a resistor.

of the OBA rod. Provided the wire is fine, this will be quite satisfactory, but obviously the thicker the wire the smaller the spacing between adjacent turns.

The Wire

So far as concerns the actual wire to use, in spite of the fact that the television transmissions are on the very high frequencies, it is not necessary to use heavy gauge wire. At signal frequencies it will be found that with the number of turns which are required there will be little measurable difference between 18 s.w.g. and 30. An aerial coupling winding, for instance, may be made of wire as heavy as the internal lead of the coaxial feeder or the twin feeder, there being no object in making it thicker. All other windings may be carried out in about 30 or 32 s.w.g. The covering should be single or double-silk (the latter preferably as there will be less risk of shorted turns in a close-wound component), and this will be found to take the necessary fixing dope most readily. This should be polystyrene cement which is readily available under various proprietary names. Do not use cellulose paint except, perhaps, for a temporary type of coil. Cellulose, too, should not be used for locking the cores, as it will probably cause the core to disintegrate, or lock it so securely that it cannot be removed. The characteristics of the sound-trap coil may enable a thick tinned bare copper wire to be employed, but this depends upon the design.


The direction in which the windings are laid on (clockwise or anti-clockwise) is quite immaterial, provided that where two coils are used on a single former, they are both wound in the same direction—unless the designer has stated that they are to be in opposition. The question of whether or not the winding should be space-wound, may be settled if a particular design is being followed. The core proceeds into the coil as it is turned, its rate of forward movement being dependent upon the thread which is provided inside the coil former. If the coil is close wound, one turn of the core will result in the core moving through three or four turns of the coil, and consequently this will have a much greater effect than in a space-wound coil, where the same movement of the core will only result in the core moving through a single turn. The final tuning point with both types of coil will be more or less identical (depending upon the place in the circuit and the associated stray capacities, etc.).

An iron core gives a similar effect to that of adding turns to the coil (increasing the inductance), whilst a core of brass acts in the same manner as reducing the number of turns. If, therefore, it is found that a given coil does not peak when an iron core is fully withdrawn, it indicates that there are too many turns on the coil, and instead of removing one or two, a brass core may be inserted.

Video Chokes

Special chokes for peaking in the video stage, may be made in either of two ways. Small lengths of $\frac{1}{16}$ in.

paxolin or similar formers may be employed, with the coils wound in the same manner as standard tuning coils, or they may be pile-wound on a small former which may conveniently be a $\frac{1}{4}$ watt Erie ceramic type resistor. In each case about 200 turns will be required, and 40 s.w.g. wire may be used here. Two discs or thick card as shown on page 351 may be cut and slipped on to the resistor, which

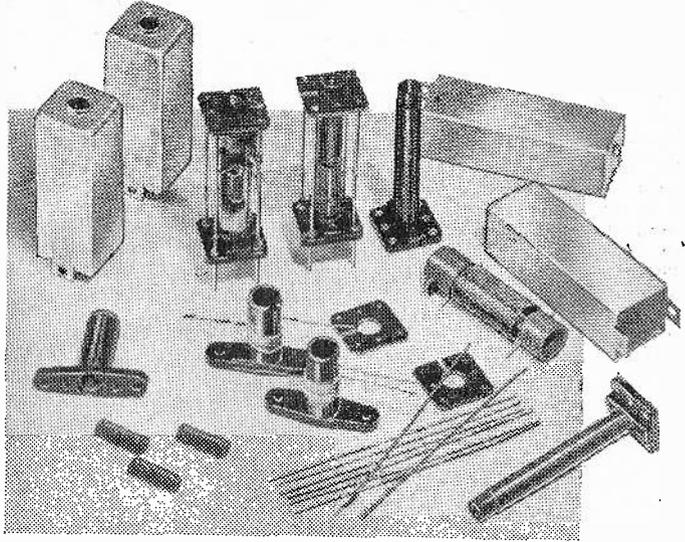

A Group of Coil Components and some finished Coils.

should have a value of $1 M\Omega$, and the 200 turns wound haphazardly inside the cheeks. This will give a result somewhat similar to a wave-wound commercial coil, and the ends of the coil are soldered to the two end wires of the resistor, which will provide the necessary flattening effect and prevent sharp peaking which may lead to oscillation. As an alternative, such a coil, especially where used between the video detector and the video amplifier stage, may conveniently be wound on one of the formers already described and the entire unit, consisting of coil, detector load resistor and filter condensers, etc., totally screened.

Polytechnic Courses for Senior Engineers

IN September the Northern Polytechnic started some special classes dealing with Band III television and F.M. broadcasting for the benefit of service engineers.

Two groups of classes started: (a) one full day per week and (b) evening classes. The one day per week group finished their course at Christmas, whereas the evening class will terminate at the Easter recess.

In view of the interest in these classes it has been decided to commence a second one day per week course as from the 10th January next. The class will take place each Monday from 9.30 a.m. to 4.30 p.m. and prospective students can obtain full details of the course on application to the secretary of the department, Holloway, London, N.7.

CHANGING TO THE NEW STATIONS

SOME DETAILS FOR MODIFYING RECEIVERS AND AERIALS FOR THE NEW TV STATIONS

By "Erg"

PART I THE ISLE OF WIGHT

TWO new transmitters are opening in the southern half of England, and should provide good service to many new viewers. The Southern Counties have a new transmitter situated on the Isle of Wight while viewers in the south-west have a new transmitter at Hessary Tor.

In the service area of the Hessary Tor transmitter most existing televisions are tuned to Channel 5 for the Wenvoe transmitter; in the area served by the Isle of Wight, however, some viewers are tuned to London while others are tuned to Wenvoe. The I.O.W. transmitter itself is operating on the Kirk o' Shotts frequency in Channel 3.

There will be many people who come within the service area with existing receivers and aerials designed for other frequencies than those of the local channel, and it is in order to assist them in changing over to the new station with the least expense, that this article is written.

Most modern televisions are equipped for five-channel operation, and it is only necessary to alter the trimming or switching, as detailed in the instructions accompanying the television, to receive the new station. The aerial is not quite so simple to deal with and we shall discuss that problem later.

Converting the Superhet

Where five-channel switching is not incorporated within the television it will be necessary to modify the coils. It is only necessary to modify the first stages; the I.F. stages work at a fixed frequency and can remain so. In fact, it is rather important that they are not tampered with, as once alignment of I.F. stages is lost, it is extremely difficult to re-align without the aid of specialised instruments, not normally possessed by the amateur.

The normal arrangement of the tuning stages of a superhet are shown in the block diagram in Fig. 1. The aerial is fed into the first amplifying stage which amplifies at signal frequency; from this point the signal is fed into the mixer stage, which also has an input from the local oscillator stage. In the mixer the signal frequency is changed to another frequency which is the value of the sound I.F. and the vision I.F. No modifications are necessary beyond this point.

Fig. 2 shows the general coil arrangement. The dipole feeds into the R.F. stage via a coil L1, the dipole actually being coupled to the coil by a smaller primary coil. This coil must be modified.

From the R.F. stage the signal passes through another coil L2, which sometimes has two windings, as shown in the figure, and other times has a single winding. This coil must be modified.

The mixer stage also takes the output from the oscillator coil L3, and this, too, must be modified. The oscillator coil can usually be easily distinguished by the fact that it generally has no coil former, and is made of rather stout wire, self-supporting.

It is not possible to give exact data for every type of receiver, but we can provide some general information to furnish a guide. The coils will require extra turns when changing from Wenvoe to Kirk o' Shotts, and will require some turns taken off when changing from London to Kirk o' Shotts. (The Kirk o' Shotts channel is, of course, the new channel used by the I.O.W. transmitter.)

Channel 5 to Channel 3

In the case of L1 (p) one turn should be added. Wire of the same type already on the coil form should be used. The larger winding on the coil L1 (s) should have two extra turns added.

If L2 is a single wound coil then two turns should be added, but if it is double wound (i.e., it actually consists of two coils), then two turns should be added to each coil.

L3 need not have any turns added. It may be possible to find a position with the core where the I.O.W. transmitter can be received, but if this is not the case then a 25 pF condenser can be added across it.

Channel 1 to Channel 3

The conversion here follows exactly the same lines as the foregoing excepting the fact that two turns must be *taken away* from the existing coils, and if it is found that the oscillator will not trim to the channel then one turn can be taken from it. Otherwise, the procedure given above should be followed and alignment made as given below.

Alignment

Set the cores level with the tops of the formers and connect the aerial (modified). Now turn the oscillator until a signal is received on the sound and vision, but if the normal trimmer will not bring in the signal try varying the value of the added condenser. Repeated operations will bring in the signal, and L1 and L2 can be adjusted for maximum signal.

Adjust all coils so that the vision is at its maximum and then adjust the oscillator so that sound is at maximum; the effect on the screen should be ignored while this is being done.

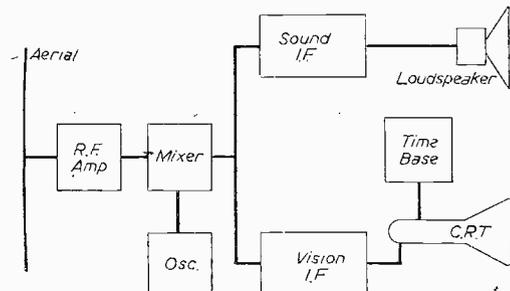


Fig. 1—Block diagram of a TV superhet.

Finally adjust L1 and L2 to give the best quality picture combined with adequate sound.

Straight Receivers

Most amateur-constructed televisions are of the straight type, and the modifications while being quite simple are a little more laborious.

Each R.F. coil should have two turns added to the grid coils, and to the sound rejector coils as well. London receivers should have two turns taken off and sound rejectors fitted; these should duplicate existing sound coils. If trimmers are not fitted all ready, then they can be fitted now instead of altering the windings. Trimmers of 0-30 pF can be used.

Note that this applies only to the sound section and not to the vision receiver.

Alignment

The alignment procedure given in the original data should be followed but if it is found that a particular coil does not peak then a turn can be added or subtracted as given in the section dealing with the superhet, provided that that coil was operated in peak position previously.

In some televisions it is not intended that each coil should peak, so that stagger tuning can be applied to increase the quality of the picture.

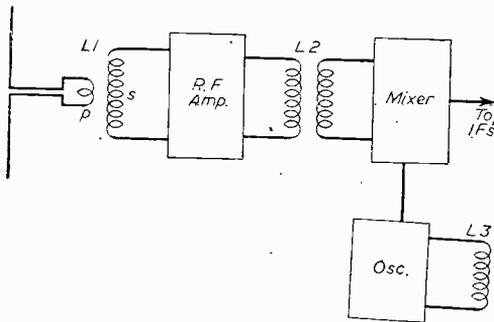


Fig. 2—Details of coil arrangements.

As a general guide the aim should be to get the core into approximately the same position it occupied previously.

The Aerial

The aerial which was used previously can be employed again if it is suitably modified.

Where an aerial for the London transmitter was employed then it will be necessary to shorten the rods. Dipoles should be shortened by cutting 1ft. 2in. from each end. The open ends of the tubing should be resealed by inserting of wooden plugs.

Many commercial aerials use rods filled with some substance (such as finely ground cork granules) in order to damp down vibration and, therefore, care should be exercised when cutting to avoid loss of this substance.

The reflector should be shortened by 1ft. 1½in. at each end, taking the same precautions as explained for the dipole.

Directors should be shortened by 1ft. 1in. for the first director and 1ft. 0½in. for the second director (if fitted). Note that this amount must be cut from each end of the rods.

It is not normally practicable to alter the spacing

between the elements, and experience has shown that it is not really necessary unless one is at the fringe; in that case it is hardly worth while to change from one fringe to another.

There will be many cases where a much simpler aerial system can be used. In localities close to the new transmitter it will be possible to convert from a high-gain array to a simple dipole, or even an "H" type of aerial.

Converting Wenvoe Aerials

Those who are at the moment using Wenvoe aerials can alter them for the new station by adding sections on to the end.

Dipoles should have an additional 14in., i.e., 7in. should be added to each end of the dipole as shown in Fig. 3 (a). The added section is shown as "A." A length of duralumin tubing of the same diameter as the existing dipole rod should be cut 10in. long, and then a slit 3in. long should be made with the blade of a hacksaw, at one end. This portion fits over the end of the dipole rod. Rivets can be applied to keep the extensions in position.

A reflector should have similar extensions but they should be 8½in. long.

Directors should be dealt with similarly but the length of the extensions should be 6in. for the director nearest to the dipole and 5½in. for the second director.

Note that it may not be necessary to alter the aerial in any way other than re-orienting it towards the new transmitter. It is advised that the aerial be tried out first using Test Card "C" as a guide and if the full bandwidth is displayed then there is no need to make alterations. It may be that if this plan is adopted the signal will be too strong and in that case a simple attenuator can be fitted. A "T" type of attenuator giving about 20 db. attenuation is shown in Fig. 4 and this is suitable for coaxial cable. A "Pi" type of attenuator giving about 10 db. attenuation suitable for balanced twin cables is also given.

Types of Aerial

It is not possible to specify what type of aerial should be used in which locality. As a general guide when the station is on full power a normal dipole should be sufficient up to a radius of about 25 miles under average conditions. Up to 50 miles an "H" or "X" aerial must be used, and beyond this a Yagi array will be necessary.

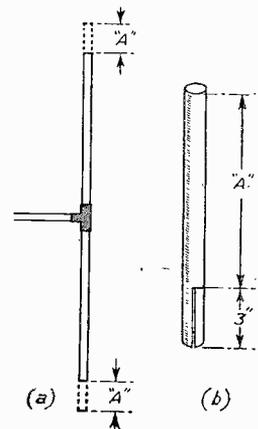


Fig. 3—Details of a standard dipole, and method of increasing its overall length by adding a further length of tubing.

Specially useful for Television Work . . .

The



WIDE-RANGE

SIGNAL GENERATOR

A Signal Generator of wide range and accuracy of performance, designed to cope with modern radio and television work. Turret coil switching provides six frequency ranges covering 50 Kc/s—80 Mc/s.

50 Kc/s—150 Kc/s
150 Kc/s—500 Kc/s
500 Kc/s—1.5 Mc/s

1.5 Mc/s—5.5 Mc/s
5.5 Mc/s—20 Mc/s
20 Mc/s—80 Mc/s

Stray field less than $1\mu\text{V}$ per metre at a distance of 1 metre from instrument.
General level of R.F. harmonic content of order of 1%.

Direct calibration upon fundamental frequencies throughout range, accuracy being better than 1% of scale reading. 45 inches of directly calibrated frequency scales with unique illuminated band selection, giving particularly good discrimination when tuning television "staggered" circuits.

Of pleasing external appearance with robust internal mechanical construction

using cast aluminium screening, careful attention having been devoted to layout of components with subsidiary screening to reduce the minimum signal to negligible level even at 80 Mc/s.

Four continuously attenuated ranges using well-designed double attenuator system.

Force output 0.5 volts.

Internal modulation at 400 c/s, modulation depth 30% with variable L.F. signal available for external use.

Mains input, 100-130 V. and 200-260 V. 50-60 c/s. A.C.



MAINS MODEL, as specified, or BATTERY MODEL, covering 50 Kc/s to 70 Mc/s, powered by easily obtainable batteries **£30**

Fully descriptive Pamphlet available on application to the Sole Proprietors and Manufacturers

The AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.
WINDER HOUSE • DOUGLAS STREET • LONDON • S.W.1 Telephone: VICTORIA 340419

S.G.1.

Osram

AUDIO VALVES

The following valves are outstanding in the current range of Osram audio valves and offer unsurpassed performance, reliability and long life to the discriminating user.

★ **Z729** 1st stage voltage amplifying amplifier pentode. The valve which has set the standard in its class where minimum hum and microphony are essential.

★ **B309 (12AT7)** Double triode voltage amplifiers.
B329 (12AU7)

★ **N709** The high output pentode for all domestic amplifier purposes.

KT66 The world famous beam tetrode specified for the Williamson amplifier. The standard output valve for all medium power high quality amplifiers.

KT61 An efficient output beam tetrode for domestic receivers and small amplifiers.

KT33C An efficient output beam tetrode for DC/AC equipment.

PX4 The popular directly heated power triode which made true high quality sound available to the home constructor.

DA42 A new indirectly heated high power Class B triode for industrial amplifiers.

★ Specified for the OSRAM 912 high quality amplifier.

Write to the Osram Valve and Electronics Department for full technical information, circuit and application data.

THE GENERAL ELECTRIC COMPANY LIMITED, MAGNET HOUSE, KINGSWAY, W.C.2.

PREMIER RADIO COMPANY


(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone: **AMBADGATOR 4033**
ABBASSINOR 3271

OPEN TILL
6 P.M. SATURDAYS

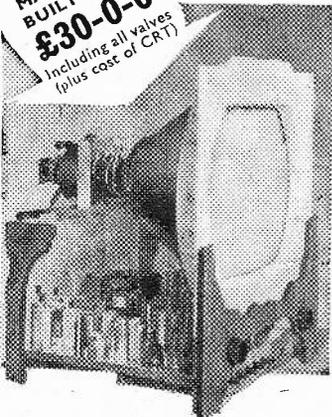MAY BE
BUILT FOR
£30-0-0
Including all valves
(plus cost of CRT)



THE COMPLETE TELEVISOR IS SAFE TO HANDLE, BEING COMPLETELY ISOLATED FROM THE MAINS BY A DOUBLE WOUND MAINS TRANSFORMER. ALL PRESET CONTROLS CAN BE ADJUSTED FROM THE FRONT, MAKING SETTING UP VERY SIMPLE.

The NEW PREMIER TELEVISOR

USING THE ENGLISH ELECTRIC CATHODE RAY TUBE T901

Brief Technical Details are as follows:

20 valves (plus tube) Superhet Receiver, tunable from 40-68 Mc/s without coil or core changing. Wide angle scanning Flyback EHT giving 14 kV, Duomag Focalliser, permanent magnet focussing with simple picture centring adjustments, suitable for any wide angle Tube, may also be used with a 12 in. Tube with very minor modifications.

VISION CIRCUIT. Common RF Amplifier, single valve frequency changer, two IF stages, Video Detector and Noise Limiter followed by special type of Video Output Valve. ALL COILS PRE-TUNED ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.

SOUND CIRCUIT. Coupling from anode of frequency changer, two IF stages, Double Diode Triode detector and first LF Amplifier, Diode Noise Limiter and Beam type Output Valve, feeding a 10in. Speaker. ALL COILS PRE-TUNED.

TIME BASES. 2 valve sync. Separator, giving very firm lock and excellent interlace.

LINE TIME BASE. Blocking Oscillator using a pentode driving a high efficiency output stage comprising Ferroxcube Cored Output Transformer with Booster Diode.

FRAME TIME BASE. Blocking Oscillator driving a Beam Output Valve coupled through a Transformer to the high efficiency FERROXCUBE Cored Scanning Coils.

POWER PACK. Double wound Mains Transformer supplying all L.T. and H.T. using two full-wave Rectifiers.

The Televisor may be constructed in 5 easy stages: (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced.

Instruction book 3/6, Post Free.

Console Cabinets in figured walnut can be supplied for the above receiver at a cost of £13/10/-, plus 21/- pkg. & Carr. H.P. Terms for cabinet on request.

Volume Controls

Midget Edison type. Long spindles. Guaranteed 1 year. All values 10,000 ohms to 2 Meg-ohms.
No Sw. S.P.Sw. D.P.Sw. 3/- 4/- 4/6
COAX PLUGS ... 1/2
SOCKETS ... 1/8
LINE CONNECTOR 1/2
OUTLET BOXES ... 1/8

BALANCED TWIN FEEDER per yd. 6d. 80
TWIN SCREENED COAX FEEDER per yd. 1/- 150 ohms
50 OHM COAX CABLE, 8d. per yd.
TRIMMERS, Ceramic, 30, 70 pf., 9d.; 100 pf. 1.50 pf. 1/3; 250 pf. 1/6; 500 pf. 1/9.
RESISTORS—All values: 1 w., 4d.; 1 w., 6d.; 1 w., 8d.; 2 w., 1/-; 1 w., 15d., 2/-.

WIRE-WOUND RESISTORS—Best Makes Miniature Ceramic Type—5 w., 15 ohms to 4 K., 1/9; 10 w., 20 ohms to 6 K., 2/3; 15 w., 30 ohms to 10 K., 2/9; 5 w. Vitreous, 12 K. to 25 K., 3/-.

WIRE-WOUND POTS 5 WATT FAMOUS MAKES
Pre-set Min. T.V. Type. Standard size Pots, 21in. Knurled Slotted Knob. Spindles. High Grade. All values 25 ohms to 30 K., 3/- ea. 50 K., 4/-; 50 K., 5/6; 100 K., 6/8. Ditto Carbon Track 50K.

O/P TRANSFORMERS—Heavy duty 70 ma., 4/6. Ditto, tapped primary, 4/9. Tapped small pentode, 3/9.

L.F. CHOKES 10 h. 65 ma., 5/-; 20 h., 150 ma., 12/6; 15 h. 100 ma., 10/6; SIMPLEX 10 h. 150 ma., 10/6.

MAINS TRANS.—Made in our own workshops to high grade specification. Fully inter-leaved and impregnated. Heater Trans. tapped primary, 0-200 v./250 v. 6.3 v. 11 amp., 7/6. 12 v. 7.5 amp., 7/6. 6.3 v. 3 a., 10/6. 350-0-350, 80 ma., 6.3 v. 4 a., 5 v. 2 a., 4/10. 300-0-300 ditto 250-0-250, 21/-.

VIEWMASTER, auto type, 35/-; (Modelling, 30/-; Lyux, 30/-; Coronet, 30/-; Simplex (telediff with 4 v. tap), 35/-; T.V. AERIALS. Aerial type etc. full range all channels in stock. Indoor loop type Inv. T., 13/8 etc. etc.

FLYAN.—Midget Soldering Iron. 200/220 v. or 230/250 v., 14/11. Triple Electro mud. with detachable bench stand, 19/6. Floor Midget Iron, 19/6.

TAG STRIPS—2- or 3-way, 2d.; 4- or 3-way, 3d.; 6-way, 4d.; 9- or 10-way, 6d.; 28-way, 1/3.

ENAMEL OR T.C. WIRE—1 lb., 14 to 20 s.w.g., 3/4; 2/-; 22 to 28 s.w.g., 2/6; 30 to 40 s.w.g., 3/9.

XTAL DIODE—Sensitive G.E.C. type, 3/6. H.R. Phones (S. G. Brown) or Hi-grade Amer., 15/6 pair.

80 ohm COAX

STANDARD 1in. diam. Polythene insulated. GRADE "A" ONLY

8d. yd.
SPECIAL—Semi-air spaced polythene, 80 ohm Coax 1in. diam. Stranded core. Losses out 50% (just released), 9d. yd.

30 TWIN SCREENED COAX FEEDER per yd. 1/- 150 ohms
50 OHM COAX CABLE, 8d. per yd.
TRIMMERS, Ceramic, 30, 70 pf., 9d.; 100 pf. 1.50 pf. 1/3; 250 pf. 1/6; 500 pf. 1/9.
RESISTORS—All values: 1 w., 4d.; 1 w., 6d.; 1 w., 8d.; 2 w., 1/-; 1 w., 15d., 2/-.

WIRE-WOUND RESISTORS—Best Makes Miniature Ceramic Type—5 w., 15 ohms to 4 K., 1/9; 10 w., 20 ohms to 6 K., 2/3; 15 w., 30 ohms to 10 K., 2/9; 5 w. Vitreous, 12 K. to 25 K., 3/-.

WIRE-WOUND POTS 5 WATT FAMOUS MAKES
Pre-set Min. T.V. Type. Standard size Pots, 21in. Knurled Slotted Knob. Spindles. High Grade. All values 25 ohms to 30 K., 3/- ea. 50 K., 4/-; 50 K., 5/6; 100 K., 6/8. Ditto Carbon Track 50K.

O/P TRANSFORMERS—Heavy duty 70 ma., 4/6. Ditto, tapped primary, 4/9. Tapped small pentode, 3/9.

L.F. CHOKES 10 h. 65 ma., 5/-; 20 h., 150 ma., 12/6; 15 h. 100 ma., 10/6; SIMPLEX 10 h. 150 ma., 10/6.

MAINS TRANS.—Made in our own workshops to high grade specification. Fully inter-leaved and impregnated. Heater Trans. tapped primary, 0-200 v./250 v. 6.3 v. 11 amp., 7/6. 12 v. 7.5 amp., 7/6. 6.3 v. 3 a., 10/6. 350-0-350, 80 ma., 6.3 v. 4 a., 5 v. 2 a., 4/10. 300-0-300 ditto 250-0-250, 21/-.

VIEWMASTER, auto type, 35/-; (Modelling, 30/-; Lyux, 30/-; Coronet, 30/-; Simplex (telediff with 4 v. tap), 35/-; T.V. AERIALS. Aerial type etc. full range all channels in stock. Indoor loop type Inv. T., 13/8 etc. etc.

FLYAN.—Midget Soldering Iron. 200/220 v. or 230/250 v., 14/11. Triple Electro mud. with detachable bench stand, 19/6. Floor Midget Iron, 19/6.

TAG STRIPS—2- or 3-way, 2d.; 4- or 3-way, 3d.; 6-way, 4d.; 9- or 10-way, 6d.; 28-way, 1/3.

ENAMEL OR T.C. WIRE—1 lb., 14 to 20 s.w.g., 3/4; 2/-; 22 to 28 s.w.g., 2/6; 30 to 40 s.w.g., 3/9.

XTAL DIODE—Sensitive G.E.C. type, 3/6. H.R. Phones (S. G. Brown) or Hi-grade Amer., 15/6 pair.

SIMPLEX TELEVISION

Detailed price list available.

STAGE 1. VISION AND SOUND
7 Valves ... 30/-
12 Resistors ... 3/-
16 Condensers ... 9/-
2 Potentiometers 6/-
7 Coil formers with cores ... 4/6
7 Valveholders ... 3/6
Sundries (with drilled chassis) ... 22/6
STAGE 2.—TIME BASE.
6 Valves ... 28/-
20 Resistors ... 8/6
15 Condensers ... 15/6
5 Potentiometers 12/6
6 Valveholders ... 2/6
Sundries ... 1/6

STAGE 3.—POWER SUPPLY
2 Resistors ... 2/-
5 S.T.C. Rectifiers ... 27/6
5 Condensers ... 23/6
1 Choke ... 10/9
1 Mains Trans. Tapped 4 v. and 5 v. ... 55/-
STAGE 4.—C.R.T. NETWORK
6 Resistors ... 4d.
1 Condenser ... 6d.
4 Potentiometers ... 10/-
Sundries ... 3/6
COMPLETE SIMPLEX KIT (less tube) 12 gns. Drilled Chassis, Screens etc., 17/8, or 10/- extra with KIT or Sundries (Stage 1).

VCR97 TUBE TESTED & GUAR., 22 (P. & p., 2/-).

NEW VALVES GUARANTEED

1R5 8/-6R3 9/-6AC7 8/6 8F01 9/-
1S5 8/-6BG6 12/6 6C9 12/6 6Y1 12/6
1T4 8/-6P25 15/-35L6 10/6 6L81 13/6
1S4 8/-807 9/6 80 9/-PY80 11/6
2S 4/-6SL7 9/-EA50 2/-SP81 8/6
3V4 8/-6SN7 11/-EA50 2/-SP81 8/6
2X2 5/6 6U5(Y63S) EB01 7/6 U29 9/6
5Y4 10/6 6V6 8/-6BC33 9/6 6CL80 12/6
6Z4 9/-6X5 9/-6E30 9/-6F80 10/6
6AL6 10/6 6V127 (Pen EBY) 12AX7 10/6
6AM6 9/-V127 (Pen EBY) 12AX7 10/6
6HM6 3/6 12A17 10/6 British 7/6 MU14 9/6
6J5 7/6 U25 12/6 6Y1 Red 10/6 6BF55 12/6

Huge Stock B.V.A. Valves at 1951 low tax prices.

TV. PRE-AMP.—Channel 1, easily modified to other channels or converter use. Midget chassis 6in. x 3in. x 1 1/2in. Complete with core, lead, plug and EP43 valve. Brand new (boxed). Listed £3/15/-. Special clearance, 27/6, p/p. 1/6.

P. and P., 6d. £1 orders post free. Lists 3d.
RADIO COMPONENT SPECIALISTS
307, Whitehorse Road, West Croydon.
TEO 1865

C.R.T. HEATER ISOLATION TRANS.

Ratio 1:1.25 Low leakage winding with 25% sec. boost, 2 v. 10/6; 3 v. 10/6; 6.3 v., 10/8; 12 v., 10/6.
10/6; 3 v., 10/6; 6.3 v., 3/6. C22 15 a., 2/6.
BRIMISTORS—CZ1, 3 a., 3/6. C01 mid. 8 kV.
CONDENSERS—New stock. .001 mid. 8 kV. T.C.C., 5/6. Ditto, 12.5 kV., 9/8; 2 pf. to 300 pf. Micās, 6d.; .001 Mica or Tub. T.C.C. 200 v., .01. Sprague 500 v., .02 N.S.F. 500 v., 1 mid. 250 v. Micromol Tub. 8d.; Hunts Midceal 500 v., .005, .01, 9d.; .05 mid. and .1 mid.; .25 mid., 1/6. 5 mid., 350 v., 1/9; 1 mid., 1,500 v., 9 C.C., 3/6.
SILVER MICA CONDENSERS—10%, 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/8. DITTO 1% ex Stock 1.5 pf. to 300 pf., 1/9; 515 pf. to 1,000 pf., 2/-.

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Wads Can Type, Clips, 6d. ea.
2/450 v. B.E.C. 2/3 8+8500 v. T.C.C. 4/6
4/500 v. Hunts 2/3 16/450 v. T.C.C. 3/6
8/450 v. B.E.C. 2/3 60/350 v. T.C.C. 6/6
8/450 v. T.C.C. 2/3 250/350 v. B.E.C. 8/6
8/500 v. Dubilier 2/9 8+16/450 v. B.E.C. 5/6
16/500 v. Dubilier 4/8 8+16/500 v. Dubilier 5/8
8+8/500 v. Dubilier 4/8 16+16/450 v. B.E.C. 5/6
16+16/500 v. Dub. 6/8 16+16/500 v. T.C.C. 6/8
32/500 v. Dubilier 5/8 32+32/275 v. B.E.C. 4/6
92+24/350 v. Dub. 5/8 32+32/450 v. B.E.C. 6/6
25/25 v. Hunts. 1/9 25/25 v. Dubilier 4/8
50/12 v. B.E.C. 1/9 60+100/350 v. 11/6
50/50 v. Plessey 2/- 100+200/275 v. 12/6

SPECIALS—500 mfd. 12 v., 3/-, 1,500 mfd. 6 v., 4/6, 6000 mfd 6 v., 5/6, 1000+1000 mfd. 6 v., 6/6.

SENSECEL RECTIFIERS—EHT Type. Fly-back Valve, K925 2 kV., 1 mid. K3246 1 kV., 6/-; K345, 3.6 kV., 6/6; K350 4 kV., 7/8; K3/100 8 kV., 12/6; K3/160 14 kV., 18/-; MAINS TYPE.—RM1, 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3, 120 ma., 5/9; RM4, 250 v., 275 ma., 16/-.

KNOBES, GOLD ENGRAVED.—Walnut or Ivory.

1 1/2in. diam., 1/6 each. Not engraved, 1/2 each.
LOUDSPEAKERS P.M., 3 OHM.—3in. Plessey 12/6; Goodmans, 4in. square, 15/6; 3in., 14/6; 6 1/2in. 16 v. Sin. R. & A., 17/8; 7in. Elliptical, 19/6; 7in. R. & A., 25/-; 6 1/2in. with trans., 19/6.

SLEEVING—Various colours, 1, 2 mm., 2d.; 3 mm., 3d. yd.; 6 mm., 5d. yd. **TOGGLE SWITCHES EX-GOV'T.** "On-Off", 4d. Erskin M.c.c. solder, 00/40, 16 g. or 18 g., 4d. yd., 5/6 1 lb. 1PC Connecting wire, 10 colours. Single or Stranded 2d. yd.

WELDERS—Pax: 10, 4d.; 25/50, 15/6, 6d.; 30/60, 15/6, 6d.; 40/80, 15/6, 6d.; B12A CRT, 1/5. Mounted, 10, 6d.; B7G, 9d.; with screening can, 1/6; BSA, BSG, B9A, 1/2; Ceramic; EF50, B7G, 1/-; All England, 5, 7, 9 pin and U.S.A. UX types, 1/-; VCR97 moulded holders, 2/6.

ALADDIN FOREMERS and core, 1in., 3d.; 1 1/2in., 4d.; 2in., 5d.; 3in., 6d.; 4in., 99d.; 97in., 100d.

OPTICAL CABLE PLUG (5-in.) with cover, 1/8.

Orientation

In many cases, by reason of the improved signal it will not be necessary to align the aerial directly on the transmitter. As a general rule, where signal strength is adequate the aerial should be arranged so that local interference is least. As an example, if the transmitter is almost in line with the main road fronting the house it is often beneficial to arrange an "H" or "X" aerial at right angles so that the rear points towards the road.

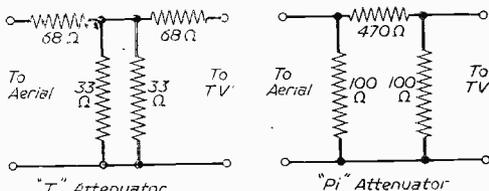


Fig. 4—Two simple types of signal attenuator.

**PART II
HESSARY TOR**

The opening of the new transmitter at Hessary Tor, in Devonshire, extends the service area of the BBC Television to an area which is notoriously ill-served even by the normal broadcast service.

Although it is not possible to forecast the actual results likely to be obtained it is thought that in the extreme south-west high-gain Yagi aerials will have to be fitted—a rather difficult operation in some areas swept by the winter gales!

In the districts around Plymouth some stalwarts have been using television receivers aligned on Wenvoe and a surprisingly large number of high-gain aerials are visible in the remote areas almost as far as Land's End. It is hoped that this section will enable them to convert to the new transmitter at the least expense.

The Hessary Tor transmitter will provide vertically polarised signal using Channel 2, which is the channel used by the high-powered station at Holme Moss. Wenvoe which has been serving the area up to the present time operates on Channel 5 and it is regrettably much easier to convert from a lower channel to a higher one than *vice versa*.

Those who possess a modern television receiver equipped for five-channel operation can convert their sets quite easily by simply following the instructions accompanying the televisor. The aerial can be modified in the manner given in the case of the I.O.W. transmitter and details will be given later in the article.

Converting the Superhet

Most commercial televisors are of the superhet type and it will be necessary to alter the windings on the R.F. and mixer coils, and to vary the frequency of the oscillator by adding a variable condenser across the coil.

The method given in the previous section dealing with conversion from Wenvoe to Channel 3 should be employed the only difference being that three turns should be added to the R.F. coil and three turns to the mixer coil. The data given in the previous section should be studied in relation to Figs. 1 and 2 and there should be no difficulty in arranging the alteration.

It is important to follow the alignment procedure

so that maximum quality of picture is obtained and under no circumstances must the I.F. stages of the vision or sound I.F. stages be disturbed as it is rather difficult to re-align these stages accurately.

Should it be found impossible to obtain a peak on the respective coils then a turn can be added or subtracted to enable a peak to be found.

Straight Receivers

In this case the previous section relating to conversion from Wenvoe to Channel 3 should be followed except that the number of added turns should be three per grid coil. For the sound section 0.30 pF trimmers can be added where trimmers are not fitted at present, and it will not then be necessary to alter the sound coils.

Do not omit to adjust the sound rejectors.

Aerials

The existing aerials in this area are tuned to Wenvoe and it will be necessary to alter the tuning to Channel 2 by adding sections to the dipole as given in Fig. 3.

The dipole should have an additional 13in. added at each end using a short length of duralumin tubing of the same diameter as the existing dipole rod.

A reflector should have similar extensions added but in this case the extra length required will be 13½in.

Directors should be dealt with in a similar manner. The first director will require an extension of 12in. and the second an extension of 11½in. Note the previous remarks concerning riveting of the extension pieces.

Orientation

The remarks concerning orientation given in the preceding section should be studied as it is often beneficial to arrange the aerial to pick up the minimum interference rather than the largest signal.

Ghosts

Due to the rather rugged nature of the Devon and Cornwall countryside it may be possible that ghost reception will be troublesome. A ghost is a second or even third image on the screen slightly displaced to the right of the main image. It is caused by reflections from hillsides, etc.

In these cases a directional aerial should be employed and it would be wise to study the article on this subject given in the November issue of PRACTICAL TELEVISION.

It should be noted that sometimes it is possible to get a better signal from the reflection itself than from the main source of signal, and pointing the aerial towards the source of the ghost may provide a worthwhile picture.

JOIN THE PRACTICAL GROUP
Edited by F. J. GAMM

PRACTICAL WIRELESS 1/-
<small>Every Month.</small>	
PRACTICAL MECHANICS 1/-
<small>Every Month. Devoted to Mechanics, Science and Invention.</small>	
PRACTICAL ENGINEERING 6d.
<small>Every Friday. For Engineers, Mechanics, Designers and Works Managers.</small>	
PRACTICAL MOTORIST & MOTOR CYCLIST 1/-
<small>Every Month.</small>	

1954

By "Omega"

1936

Now and Then

OUR CRITIC REVIEWS STUDIO METHODS AND CONDITIONS OVER THE PAST 18 YEARS

WHEN the first television programmes in the world began at Alexandra Palace in 1936 the producers of those days were not fettered by any conventions. There were no precedents to follow. The producers came from the theatre, films and radio and all soon agreed that nothing they had done before would, by itself, be sufficient for this new electronic baby which they hoped to rear to manhood.

In those early months two types of equipment were used. One the E.M.I., which is still giving faithful service in certain programmes, and the other Baird, which recorded on film that was developed and transmitted less than a minute later.

Two Systems

The Baird system, which, incidentally, called for the most fiendish make-up ever devised, was discarded after a time, but how enjoyable it would be if some of the films made by it were available and suitable for showing to-day. Would some of those early programmes still appear as wonderful as we then thought them to be, or would they seem to us as comic as those early silent films we are treated to from time to time?

The equipment in the pre-war days suffered from several handicaps which have now largely been removed. The cameras had one lens only, so that for any close-ups the mountain of the camera had to track forward to the Mohammed of the artiste. Having got there, the depth of focus was only a few inches, so that if any close-ups involved two artistes, inevitably one was in sharp focus and the other seen through a gentle mist. It was the rule always to focus on the nearer object and the cameraman saw his picture upside down in his viewfinder.

At the present time only O.B. cameras are fitted with "zoom" lenses. Possibly in time to come studio cameras will be fitted with them too. Another pre-war handicap removed after the resumption of television was the inability to "cut" from one picture to another. A "mix" took several seconds and rendered impossible any snappy camera work.

Television is a medium demanding and receiving full co-operation between the technical and programme sides. Although few, if any, producers could trace an electric circuit, all of them, by the nature of their work, have to learn and respect the capabilities of the equipment they use. The old-timers learnt by trial and error in a period of intense enthusiasm and co-operation amongst themselves. Their mistakes did not matter so very much in the beginning because, after all, there were only some 7,000 viewers to be considered and the novelty of getting a picture on their screens lasted a long time. But any mistakes by the designers of the first equipment would have mattered very much indeed. They, too, had no precedents to guide them and it is, to say the least, remarkable that their equipment has stood the test of time so well. A suggestion has been made that when the new studios at the White City are built a place of honour should be kept for one of the

first E.M.I. cameras, to remind future generations of the great pioneering work it typifies.

Lighting Engineers

A class of engineers whose work is largely taken for granted is the lighting engineers. Light in great quantities had to be used at Alexandra Palace, much to the dismay of some artistes and all cooks, who found their ingredients behaving as if in a tropical country. Less light is needed in the Lime Grove Studios owing to the greater sensitivity of present-day cameras. Apart from quantities of light there is great skill in lighting a television production, which is generally appreciated most by visiting lighting cameramen from film studios. The film men achieve a quality of lighting which is seldom approached in television, but, as they themselves point out, they can concentrate on a comparatively small area for a shot which may last a few seconds only. The television lighting engineer has so to light a set that continuous well-illuminated action is possible in any part of it. The resulting pictures are not as consistently good as those seen in films, but fortunately they do not have to be, as the demands of the small television screen are less exacting than the large screen in the cinema. As time passes the engineers place more equipment at the disposal of the producers. There is now "inlay" and "overlay," permitting a shot of a princess in the studio to appear in the top window of a castle 100ft. high. Back projection gives wings to studio actions in photographed pictures of the authentic places where the action is set.

More and more refinements will doubtless continue to come. What of the producers in the midst of all these aids to their craft? The majority to-day have passed the time of what is sometimes called "new boys'" disease. This can be described as an irresistible impulse to use all the gadgets available to him. When a singer is performing happily to one camera, he suddenly cuts to another and so causes her to sing to someone else on her left or right; or to use superimpositions without proper cause. The whole tendency amongst experienced producers is towards greater simplicity and the avoiding of stunts unless strictly necessary.

Looking Back in 1973

How interesting it would be if producers and engineers could see their efforts of years ago. Perfection has not been reached and never will be reached. The passing years will see continuing experiments in all directions in search of the unattainable and in this way television will remain vital, although few viewers may be able to point the reasons accurately. But it is a safe prophecy that just as we would be amused or possibly shocked could we see again those programmes of 18 years ago, so in another 18 years' time the viewers then, probably taking for granted their coloured stereoscopic pictures, will see the tele-records of to-day and be amused, and possibly shocked.

only, leaving the other ends free. Fit the screens either by nuts and bolts or, if tin plate is used, by sweating to the chassis which is also tin plate. Fit tags 1, 2

straightforward; however, it is possible to obtain satisfactory results with a test oscillator and an A.C. voltmeter.

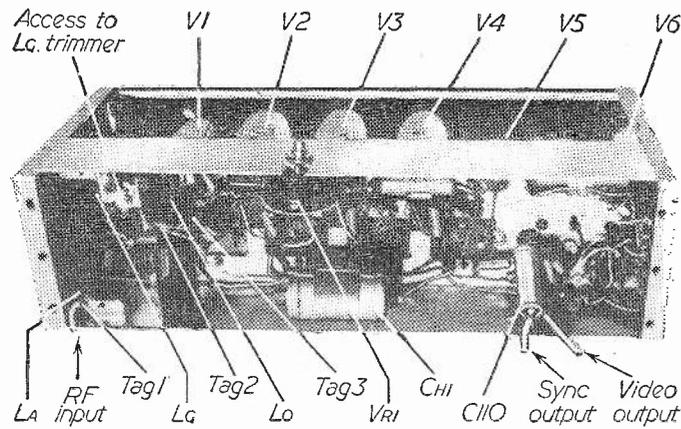


Fig. 5 (a)—View of the unit with various parts identified, after modification.

and 3 and brackets for coil LG. Fit and wire coil LG. Connect one end of R104 to tag 2 and the other end to the junction of R103, R105 and C102. Secure earthy ends of C102, C101 and C108. Fit coil LO and connect between pin six on V1 and tag three (see Fig. 6), fit C107, C105, R106 and connect tag two to H.T. rail. The modification is now complete and the receiver can be lined up.

Setting Up

With a signal generator, valve-voltmeter and oscilloscope the setting-up procedure is

With the A.C. voltmeter set on the 100 v. range, connect across V8 cathode. Inject a modulated signal of 12 Mc/s into V1 grid with LO short-circuited.

The I.F. coils will not require much tuning. Swing test oscillator output between 10 and 14 Mc/s. Note the two frequencies that give an output of 70 per cent.

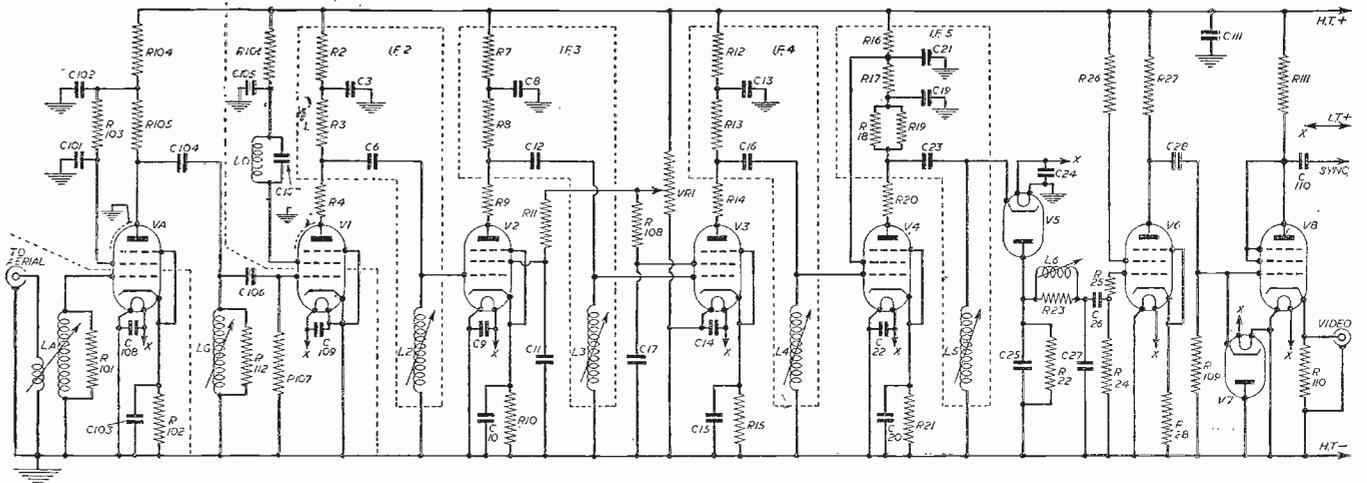


Fig. 3.—Complete circuit of the modified unit.

COMPONENT LIST

RESISTORS :	10 K 1/2 w. R23 and 25	CONDENSERS :	0.1 μF C110, 27 and 28
27 Ω 1/2 w. R4, 9, 14 and 20	*10 K 1/2 w. R110 and R111	10 pF Ceramic C107	16 μF C111.
100 Ω 1/2 w. R10, 15 and 21	12 K 2 w. R27	20 pF Ceramic C106	
220 Ω 1/2 w. R28	15 K 1/2 w. R18 and 19	25 pF C26	VALVES :
1 K 1/2 w. R102, 103, 104, 108,	20 K 1/2 w. R106	40 pF C25	6AC7, V4 and V1
2, 7, 11, 12, 16, 17 and 26	22 K 1/2 w. R107	50 pF C108, 109, 9, 14 and 22	EA50 V5 and V7
3.3 K 1/2 w. R3	1 m 1/2 w. R109 and 24	100 pF Ceramic C104	VR65 V2, 3, 4, 6 and 8
3.9 K 1/2 w. R22	100 K wirewound potentiometer VR1.	200 pF C6, 12, 16 and 23	2 Ceramic I.O. valve holders
4.7 K 1/2 w. R8, and 13		500 pF C101 and 102	1 B3G valveholder
4.7 K 1/2 w. R112		0.001 μF C103 and C105	3 1/2 in. Aladdin formers
5.6 K 1/2 w. R101		0.01 μF C3, 8, 10, 11, 13, 15 17,	3 insulated soldering tags.
5.6 K 1/2 w. R105		19, 20, 21 and 24	

* See Text. Resistors R2 to R28 and condensers C3 to C28 are already in position in original amplifier.

of maximum, if the difference is not 3 Mc/s adjust the tuning slugs of L2 to L5 until this is so. If the television receiver is to use a 6in. C.R.T. 3 Mc/s is more than adequate and greater sensitivity without appreciable loss of definition will be achieved if the I.F. coils are peaked until the bandwidth is reduced to 2.5 or even 2 Mc/s.

Transfer the test oscillator to the aerial input, inject an R.F. of suitable frequency, remove short circuit from LO and tune oscillator for maximum output as indicated by the voltmeter. Tune LA and LG then

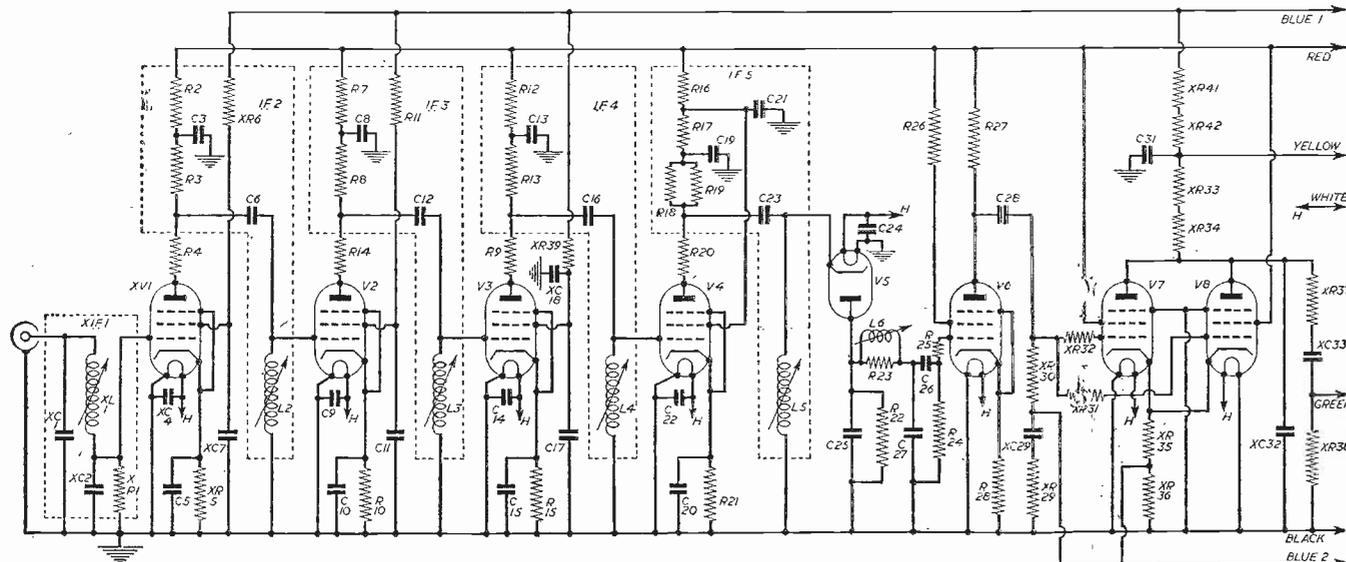


Fig. 2.—Complete circuit showing components, prefixed by "X," which have to be removed.

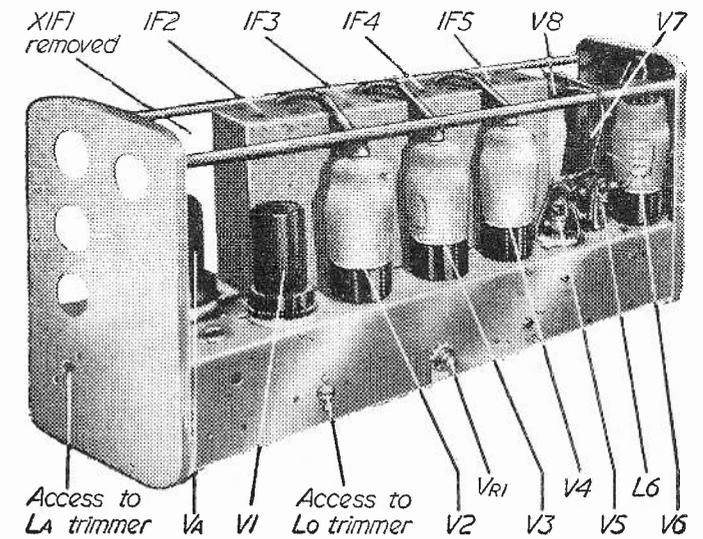


Fig. 5 (b)—Another view of the modified unit with further identifications.

readjust LO. The tuning of LA and LG is fairly flat but LO is sharp enough to give complete separation between sound and vision.

Note that the value of R111 and of R110 is critical and that the optimum value is affected by load conditions. It is advisable to fit a 10 K variable resistance in the place of R110 and a 15 K variable resistance in the place of R111. Various combinations

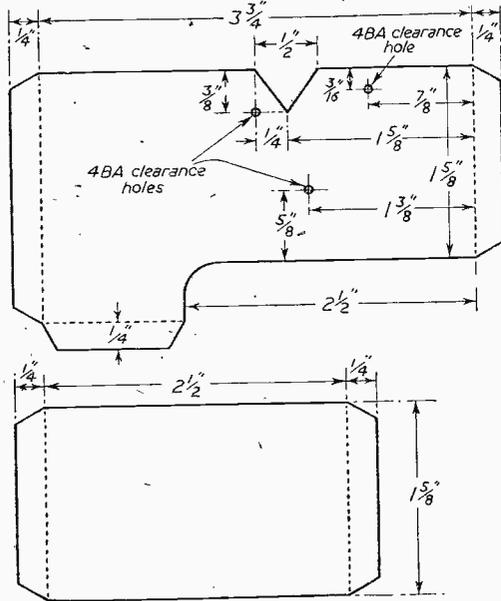


Fig. 4.—Details of the screen.

of these two components can be tried until the most suitable positions are found under load conditions. Fixed resistances can then be fitted of values equal to the measured values of the variable resistances.

It should be pointed out that, as with all ex-service equipment, individual samples of apparatus may differ, due to their having been modified or put to some special use whilst in the Services, and therefore correspondence cannot be entered into with regard to individual departures from standard.

Aberdeen Exhibition Planned

PLANS are in hand for a radio and television exhibition to be run by the north-east branch of the Scottish Radio Retailers' Association next October.

It is hoped that this exhibition will coincide with the opening of the permanent TV transmitter at Corehill, Oldmeldrum.

No Rent, No Viewing

THE rural council of Wainford, Suffolk, intends to refuse permission for the erection of a TV aerial to all council tenants who do not pay their rent.

HERE AND THERE

500 Prosecuted

THE G.P.O. visit to Leicester recently with detector vans resulted in prosecutions for 500 TV "pirates."

"What's My Line?"

"WHAT'S My Line?" is to continue through the first quarter of this year with the same team and chairman. The producer of the show will be Leslie Jackson who was responsible for the production of some earlier editions in this series.

Some Advertising

THE Belgian Government is expected to charge a licence fee soon to its viewers who have so far been enjoying a free service. Some programmes may be allowed containing a little advertising.

Park Committee's Refusal

MANY angry protests were registered recently by North Pembrokeshire residents when the national Park Committee decided to deny permission for the erection of a television relay station at Foel Eryr in the Prescelly mountains.

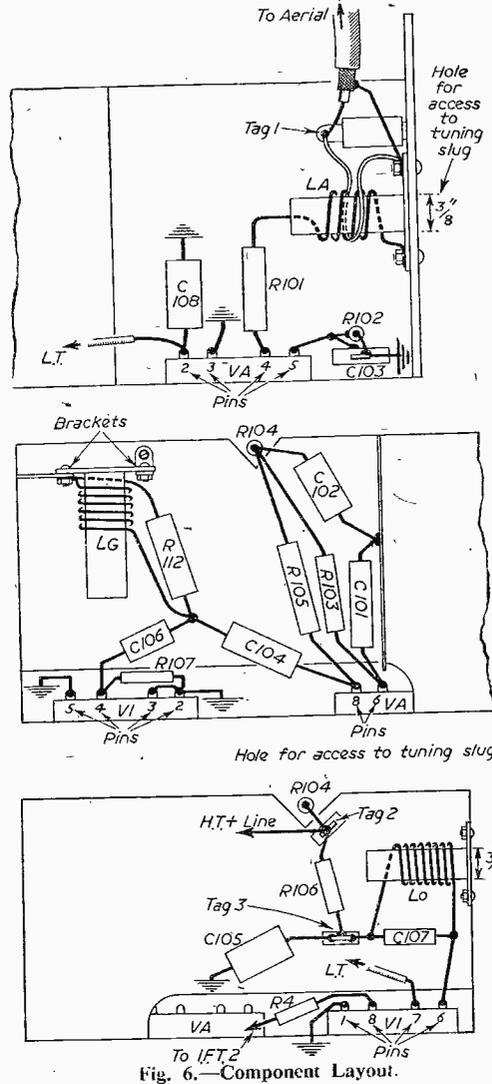


Fig. 6.—Component Layout.

Modifying the Amplifier Type 178

DETAILS OF CONVERSION OF ANOTHER POPULAR EX-SERVICE RADIO UNIT

By F. J. Shipgood, A.M.I.P.R.E.

FROM time to time there appears on the market various Government surplus I.F. and R.F. amplifiers. Their attractiveness lies in the saving in expense and in the ease of modification. From these two viewpoints alone the amplifier makes a "good buy." In addition, the completed amplifier compares favourably with its commercial counterpart.

It is possible to convert the amplifier into a TV receiver, giving both sound and vision outputs, but it was decided to concentrate on the vision side alone. The following specification shows this to have been worthwhile. An input of 35 μ V at 65 Mc/s modulated 30 per cent. by 1,000 c/s gave an undistorted output of 50 v. A.C. (measured peak-to-peak) at the phase-splitter cathode and 35 v. at the anode. To obtain the same output with 70 per cent. modulation only 17 μ V input is required. The bandwidth is 3 Mc/s, this being more than ample for receivers employing average diameter picture tubes.

Fig. 1 shows a block diagram of the amplifier (a) before and (b) after modification.

With reference to Fig. 1 (b) and Fig. 3, the circuit of the complete receiver is described as follows. The received signal is applied from the aerial to an R.F. amplifier (VA) via the R.F. transformer LA. This valve is resistance-capacity coupled to V1, a tuned-grid, tuned-screen frequency changer. The next three stages, V2, V3 and V4, are I.F. amplifiers with grid coils slug-tuned to or near 12 Mc/s. The H.T. supply to V2 and V3 screens may be varied in order to control the gain. The I.F. voltage developed across L5 is rectified by the diode V5, filtered by L6 and C27 and the resulting video applied to V6, a video amplifier. This valve has its cathode resistor unby-passed to provide negative feedback. V8 is a phase-splitter with a D.C. restoring diode V7 in its grid circuit. The picture content is available at the cathode of V8 and synchronising pulses at the anode.

Modification Procedure

The modification procedure is as follows: Referring to Fig. 2, remove all components preceded by an X. Start by removing X1F1, the first I.F. can which contains XC1, XC2, XR1 and XL1. Next remove XR6 which is in I.F. can, number two, then XR5, XC4, XC7, XC18, XC29 to XC33 and XR29 to XR42. Remove the coaxial input socket and its bracket.

At this stage it is advisable to check and replace where necessary all paper type condensers. Some of these will be found in the I.F. cans.

Now the new circuit as shown in Fig. 3 may be built up. In order to retain the old valve numbers as

Channel	Coil LA		Coil LG	Coil LO
	Primary	Secondary		
1	1	8	8	10
2	1	7	7	9
3	1	6 1/2	6 1/2	8
4	1	5 1/2	5 1/2	7 1/2
5	1	5	5	6 1/2

Figures indicate number of turns of 26 s.w.g. enamelled copper wire required for each channel. LA primary is covered in 1 mm. diameter PVC sleeving. All formers are 1/4 in. Aladdin type.

indicated on the chassis the first valve is numbered VA. This valve is fitted in the space previously occupied by the first I.F. can. The holder of the old V7 may be removed or left in to serve as a convenient anchoring point for L.T. and H.T. supplies. Above this holder and fitted to the side of the chassis is the B3G holder for the D.C. restoring diode, the new V7. Other

valve holders to be fitted are, as previously mentioned, VA which is a ceramic International Octal, and V1—here the British Octal holder is removed and another International Octal fitted. Wire up all these holders for L.T. and earth all pins where indicated in the circuit. Fit the wire-wound potentiometer, VR1, to the chassis and complete the wiring to the screens of V2 and V3. The circuit of V4, V5 and V6 requires no modification and part of the wiring of the old valves V7 and V8 can be utilised when wiring up the D.C. restorer and the phase-splitter.

There now remains the R.F. amplifier and frequency changer circuit. Table 1 gives the coil data, Fig. 4 details of screens, and Figs. 5 and 6 component layout. First check that heater and earth wiring is complete then wire in VA cathode components. Fit coil LA and complete VA grid circuit, as in Fig. 6 (a). Wire in C104, C106, R107 and R112. Connect C101, R103 and R105, at the valve pin side

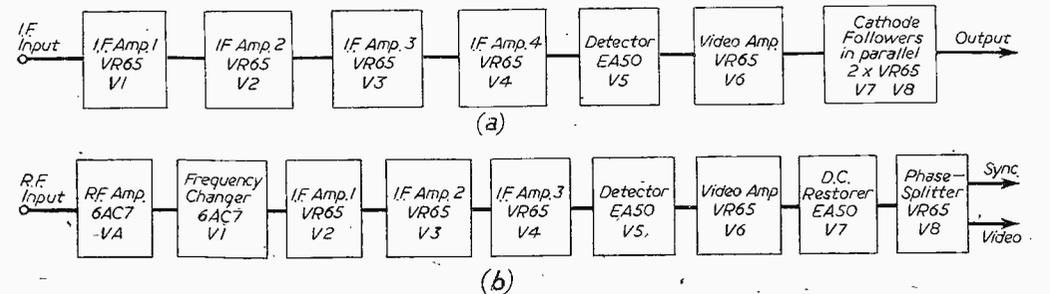


Fig. 1.—Block Diagram (a) before modification and (b) after modification.

INTERFERENCE ON BAND III

By A. E. LOFTING

NOW that Band III is well on the way, it is as well to consider what interference is to be expected, and what measures will be necessary to reduce it. The much higher frequencies of Band III require special treatment. The higher the frequency the more difficult is its suppression. This is because of the greater ease with which high frequencies leave conductors. Thus a length of wire having negligible radiation at 45 Mc/s will radiate like a charm at 200 Mc/s. With this in mind one can realise the extra difficulties involved, and the uselessness of present suppressors at these frequencies. Much work will have to be done to eliminate as far as possible the radiation of Band III frequencies, and the first "interfering agent" to be investigated will doubtless be the fractional horse power motor. First let us consider the few points on which we, the home constructor, have some control. These are: the careful choice of motor, and correct brush adjustment.

Brushes of commutator machines are the source from which our trouble flows. Each tiny spark produced, as the copper segment of the armature moves away from the brush, being responsible for a wide range of frequencies. Fig. 1 shows a diagrammatic representation of a brush and its neighbouring commutator segments. It will be seen that as the armature rotates there will be one or two coils short circuited beneath the brush, the number depending on the width of the brush. As these coils have an induced voltage within them, a current will flow. When the segment moves past the brush the circuit is interrupted, then a spark is formed. The intensity of this spark, and consequently the R.F. energy radiated, will depend mainly on the initial current flowing and coil inductance. The initial short-circuit current is proportional to circuit resistance and coil voltage. To reduce this current we must either increase the closed circuit resistance and/or reduce the coil voltage. Coils necessarily have a low resistance, only a fraction of an ohm; therefore, in practice the brushes are designed to have a high resistance. To reduce the coil voltage the number of turns for each coil must be reduced. But at the same revolutions per minute this will result in lower available torque, unless more coils are used. From this it follows that for a motor of a given size, the one having more coils and therefore more commutator segments will produce less interference. More coils for a given output also has the desirable effect of reducing coil inductance.


Bedding-in Brushes

Intermittent contact between brush and commutator can cause serious interference. This occurs if the brush is not "bedded in," or shaped to fit the commutator, and if the copper segments are rough and burned. To bed-in a new set of brushes is an easy matter, and can produce worthwhile results. First remove the brushes and place a narrow strip of the finest emery paper around the commutator, rough side outwards. Replace one brush to touch the paper and rock the armature to and fro until, on removing the brush, it has assumed the correct shape. Note carefully the positioning of the brush in its

holder, so that it may be replaced the same way. After grinding both brushes it is as well to remove dirt and dust from the segments. A glass hairbrush is the best tool, it does not scratch the soft copper. For bad marks use carbon-tetrachloride on a rag.

In addition to these points there are the basic precautions necessary for all interference suppression. The most important of these being effective screening and earthing. Screening of a small motor is best achieved by using its own metal frame, this frame extending well over the ends of the motor and brushes. Good bonding between the three (usually)

Fig. 1—A brush and its neighbouring commutator segments.

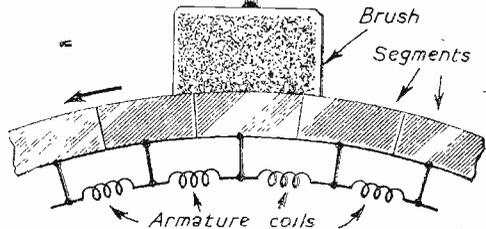

pieces forming the frame and case is essential. Unfortunately not all small motors have a metallic frame, and it is sometimes inconvenient and cumbersome to place a frame around the motor. In this respect the manufacturers must provide some answer. One remedy applicable with a bakelite casing is to coat the inside of the case with a conducting film, a relatively simple matter for the manufacturer. Now a metallic screen is provided to be the point at which electrostatic lines of force (interference lines) terminate. For this the screen must be well bonded to earth. The interfering lines finishing at the screen then do no further harm. However, we still have two leads supplying power to the motor, and these can, and do, lead away interference currents to be radiated from the cable. As mentioned earlier only a small length of conductor is sufficient to radiate considerable interference. At 200 Mc/s 1 or 2 in. is a lot! Therefore any suppressor we may design must be connected closer than 1 in. to the screen to be effective. The best mounting for such a suppressor is through the screen.

Conventional suppressors having lumped capacitance and inductance will not be suitable. A suppressor quite satisfactory at broadcast, medium wave bands is shown in Fig. 2, though at 200 Mc/s it would be of little use. This is mainly because the interfering currents flowing along the input to the inductance and capacitance will radiate in so doing. For this reason it is expected that tuned suppressors will be of great importance.

Practical Data

I mentioned these briefly in the May P.T. for use on present TV frequencies. However, the higher frequency of Band III permits the use of another arrangement to provide a resonant rejector circuit.

Inductors can be wound to specified dimensions to have a predetermined value of self-capacitance, this self-capacitance, together with the coil inductance, forming the tuned circuit, Fig. 3. If this circuit be arranged to resonate at the TV channel frequency, it will form an effective barrier to this frequency. This insertion loss will be very high, depending on the circuit Q. Self-capacitance of inductors can be calculated from a variety of formulae, as can the inductance. These formulae are obtainable for many types of coil windings in good radio reference books,

the lamp has only one apparent electrode it can, and does, emit amplitude- and frequency-modulated V.H.F., due to an interesting effect investigated by Barkhausen and Kurz, after whom the oscillation has been named. More modern lamps sometimes give rise to interference, caused by arcing across tiny fissures in the filament, usually when nearing failure. A simple remedy in either case is to renew the lamp.

Unfortunately the majority of us suffer from interference of someone else's manufacture. Interference over which we have very little control. Event-

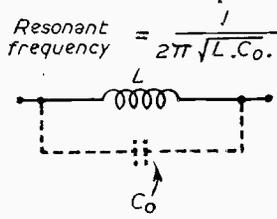
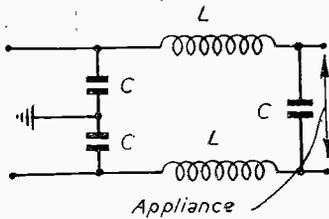


Fig. 2 (left)—A simple suppressor circuit. Fig. 3 (right)—The essential components of a suppressor.

TABLE I

l/d	H	l/d	H
10	1.32	1.5	0.47
9	1.22	1.0	0.46
8	1.12	0.9	0.46
7	1.01	0.8	0.46
6	0.92	0.7	0.47
5	0.81	0.6	0.48
4	0.72	0.5	0.50
3	0.61	—	—
2.5	0.56	—	—
2.0	0.50	—	—

giving accuracy to practically any degree. But for general work the following formulae will be useful for single layer coils:

$$C_0 = Hd \text{ pF. Where } d \approx \text{diameter in cms.}$$

H = constant depending on ratio l/d, where l is the coil length. Given in Table I.

$$L = \frac{d^2 n^2}{18d + 40 \times l} \text{ n = diameter, inches. l = coil length, inches.}$$

Armed with these formulae the enthusiast will have useful weapons to wield against interference.

Among the rarer cases of interference are the oscillations of old carbon filament lamps. Though

usually all appliances sold will be suppressed for Band III, but that still leaves a lot of apparatus working today which will create plenty of 200 Mc/s interference. Also manufacturers have yet to develop effective and cheap suppressors for their products, or provide other means of preventing interference, i.e., prevention rather than cure. One interesting possibility is the design of motors having balanced to earth layout. We all know the effect of twisting valve heater wires, and of keeping them of approximately the same length. This basically is the idea with motors, to produce "balanced" interference whose net result is zero.

New Mullard Voltage Stabilisers

ALMOST every piece of industrial, military, and commercial electronic equipment incorporates a source of stable voltage. Mullard gas-filled stabilisers and voltage reference tubes such as the 90C1 and 85A2 are widely used in such equipments because of their extremely long life, freedom from voltage "jumps," and close tolerance burning voltages. Samples of Special Quality versions of these tubes are now being made available by the Communications and Industrial Valve Department of Mullard, Ltd. These combine the good qualities, of normal types with the ability to operate satisfactorily under severe conditions of shock and vibration such as are encountered in aircraft, ships, vehicles, and in industry. They are tested to withstand impacts of 500g. and vibrations of 6g. at 175 cycles per second.

The new tubes are electrically equivalent to the 85A2, the 90C1, and the 150B2. They are available in two forms, one with pins and one with flying leads. Flying leads are desirable because, since they can be soldered firmly in place, variations in contact resistance such as are encountered when plug-in types are subjected to vibration are eliminated. Such variations give rise to noise and minute voltage fluctuations which degrade the high performance of a voltage reference tube. The fact that replacement is more difficult mechanically than with plug-in types is of little importance in view of the long life of these tubes.


Extending Mast Vehicle

THE BBC recently introduced a new prototype extending mast vehicle. This vehicle, which has been produced for use with television outside broadcasts, is unique in performance and provides means whereby the radio link transmitting or receiving aerials, and associated electronic equipment, can be elevated to a height of just over 60ft., in order to clear obstructions that might otherwise impede the transmission or reception of signals. The aerial, consisting of a 4ft. diameter paraboloid which is mounted on top of this mast, has to be accurately set to within approximately ± one deg., and a system of remote control has been devised whereby this can be readily achieved. The aerial can be rotated continuously through 360 deg. in the horizontal plane.

The mast is erected from the horizontal position on the vehicle to the vertical position on the ground by a system of hydraulic rams. A similar system is then used to extend it to its full height of approximately 60ft. In this position the mast is self-supporting, but provision has been made for stay wires to be fitted should it be necessary for the mast to be left erected in strong winds.

The remote control system employed enables a pre-set bearing to be determined and set up to within ± half deg. On bringing the remote control into operation the paraboloids will adjust themselves to the position indicated.

CLEVELAND CAR BATTERY CHARGER

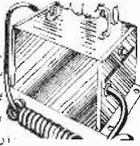

gives 11 amps. charge over a 500 g. metal rectifier and robust double-wound transformer in metal carrying case with leads and croc. clips.

Price 6 volts, 29/6; 6 to 12 volts, 39/6. Post 2/6.

INFRAY LAMP

Means real comfort in bed as it emits Infra Red Rays which warm and keep you healthy.


- Economical.
- Costs only 1d. per hour (elec. at 1d. per unit).
- Absolutely safe, no health or fire risk.
- Ideal for many other uses--over pet's basket, rearing pup, chicks, over desk, work bench, etc.
- All complete and ready to work.

Price 36/-
Post & Pack. 2/-



CONNECTING WIRE SNIP

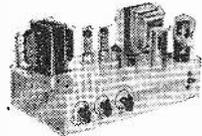
P.V.C. insulated 23 s.w.g. copper wire in 100ft. coils, 2/9 each. Colours available: Black, Brown, Red, Orange, Pink, Yellow, White. Transparent. 4 coils for 10/-.



MULLARD AMPLIFIER

A high Quality Amplifier designed by Mullard engineers. Robust, high fidelity, with a power output exceeding 10 watts and a harmonic distortion less than 4% at 10 watts. Its frequency response is extremely wide and level being almost flat from 10 to 20,000 C.F.S.—three controls are provided and the whole unit is very suitable for use with the Collaro Studio and most other good pick ups. The total cost of the amplifier is around £11. For 30/- extra a unit completely made up and tested can be supplied. Carriage in either case is 10/- extra.

SOMWEAVE

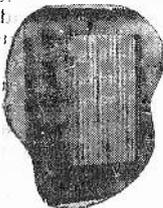


This really lovely loud-speaker fabric we offer at approximately a third of today's cost. It is 42in. wide and our price is 12/- per yard or panels 12in. x 12in. 1/9 each.

This is also very suitable for covering plain wooden cases, for portable radio amplifiers, etc.

COMPONENT SNIP

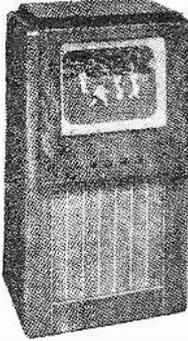50 assorted 1 and 1/2 watt resistors, ranging between 10 ohm and 10 meg. ohm. (Our selection.) Price 5/- pikt.



A FEW REMAIN


This cabinet is offered below cost. It is suitable for a television using tube sizes varying from 12in. to 17in., its overall dimensions being 34.5in. high, 1ft. 4in. deep, 1ft. 10in. wide. It is complete with plywood back and "Bowler Hat." Originally made for a very expensive television and really good quality. Unrepeatable. Offered at £6.19.6 carriage, packing, etc. 12/6. Note: These are cut for 12in. tubes, but the holes for the controls are not drilled.

TUBES ALL SIZES

All makes repaired at a little over half price—SIX MONTHS' GUAR.

We Wish All Our Readers of "Practical Television" a Merry Xmas and a Prosperous New Year.


MINIATURE PORTABLE T.V.

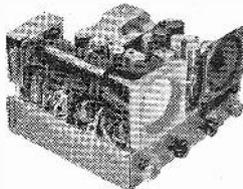

The Elpreq Miniature Television uses standard conventional circuitry, employing a total of 13 valves and 2 crystal diodes. The cathode-ray tube used is a 21in. Service type VCR139A, which has a standard equivalent and will therefore always be obtainable. The layout is extremely clean, straight-forward and professional. The wiring, whilst naturally being a little more intricate due to miniaturisation, is nevertheless completely accessible. The total cost comes to £16-£17. Its size will be approximately 9 1/2in. x 6in. x 6in. Full construction data, layouts, diagrams, templates, etc., running into some 50 sheets is available, price 5/-, post free.

THE ELPREQ E.H.T. GENERATOR

This is a made up unit working on the blocking oscillator/over-wound amplifying stage principle. It is of moderate power consumption (6.3 volt .8 amp. filament and approx. 59 mA. H.T.) and contains three EVA valves. Output obtainable ranges from 6kV to 9kV with normal H.T. rail input but somewhat higher outputs can be obtained with higher H.T. supply. Valve rectification is employed in the output stage. The dimensions are 6 1/2 x 4 1/2 x 7 1/2. Price 69/6, post, packing, etc., 5/-.

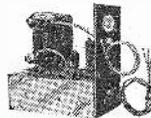

MULTI-METER KIT



The Multi-meter illustrated measures D.C. volts, D.C. m/amps and ohms. It has a sensitivity of 200 ohms per volt and is equally suitable for the keen experimenter, service engineer or student. All the essential parts, including 2in. moving coil meter, selected resistors, wire for shunts, 8-point range selector, calibrated scale, stick-on range indicator and full instructions for making are available as a kit, price 15/-, plus 9d. post and packing.

1in. MICROMETER




Exceptional purchase enables us to offer a 1in. precision micrometer at the very low price of 10/-. A micrometer is an essential part of an engineer's equipment. You will have found the need for one on many occasions in the past for measuring wire gauges, etc. If you act quickly you can now acquire this precision instrument at the remarkably low price of 10/-, post free.

THE F.M. FEEDER UNIT



All the parts necessary to make the Denco F.M. Unit are now available. The unit gives an A.F. output suitable for feeding in at the pickup sockets of any standard broadcasting receiver and superior results can be expected. The full constructional details are available—price technicians are available—price 1/6, post free. Alternatively, they will be given free to those ordering all the parts which come to £6.7.6. plus 2/6 post and packing. Note: four valves and everything including a prepared metal chassis is supplied. Approximate chassis measurements are 6 x 6 x 1 1/2.

THE PROJECTOR

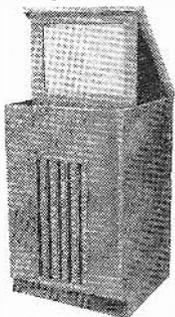

An impressive cabinet, originally designed for T.V. but slight modification makes it into an unusual but most dignified radiogram or amplifier. Size 23in. wide, 22in. deep, 37 1/2in. high. Price £8.15.0. or £2.18.4 deposit. Carriage and ins. £1.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 7, RUISLIP.

Personal shoppers, however, can call at:

- | | | | |
|---------------------------------------|-----------------------------|---|--------------------------|
| 42-46, Windmill Hill, Ruislip, Middx. | 152-3, Fleet Street, E.C.4. | 29, Strand Green Road, Kingsbury Park, N.4. | 249, High Road, Kilburn. |
| Phone: RUISLIP 5780 | Phone: CENTRAL 2833 | Phone: ARCHWAY 1099 | (Now Open) |
| Half day, Wednesday. | Half day, Saturday. | Half day, Thursday. | |

RADIO SUPPLY CO. (LEEDS) LTD.

Dept. N., 32, THE GALLS, LEEDS, 2.

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/- extra under 10/- 1/6 extra under £1; 2/- under £3. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 5d.

R.S.C. MAINS TRANSFORMERS (GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v 50 c/s Screened.

TOP SHROUDED, DROP THROUGH
 250-0-250 v 70 ma, 6.3 v 2.5 a ... 12/11
 260-0-260 v 70 ma, 6.3 v 2.5 v 2 a ... 14/11
 350-0-350 v 80 ma, 6.3 v 3 a, 4 v 2.5 a ... 15/11
 350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 17/6
 250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 21/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 21/9
 350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 27/9

FULLY SHROUDED UPRIGHT
 250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a
 Midget type, 21-3-in. ... 15/9
 250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 250-0-250 v 100 ma, 6.3 v 6 a, 5 v 3 a, for
 R135 Converters ... 29/9
 300-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 150 ma, 6.3 v 4 a, 0-4.5 v 3 a
 425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v
 4 a, C.T. 5 a ... 47/9
 450-0-450 v 250 ma, 6.3 v 6 a, 6.3 v 6 a,
 5 v 3 a ... 69/6

FILAMENT TRANSFORMERS
 All with 200-250 v 50 c/s Primaries: 6.3 v
 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9;
 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/9.

CHARGER TRANSFORMERS
 200-250 v 0-9-15 v 1 a, 11/9; 0-9-15 v 3 a, 16/9;
 0-9-15 v 4 a, 18/9; 0-9-15 v 6 a, 22/9.

OUTPUT TRANSFORMERS
 Standard Pentode 5,000 to 3 ohms ... 4/9
 Standard Pentode 7,800 to 3 ohms ... 4/9
 Standard Pentode 10,000 to 3 ohms ... 2/11
 Small Pentode 5,000 to 3 ohms ... 3/9

E.H.T. TRANSFORMERS 200-230-250 v
 2,500 v 5 ma, 2-0-2 v 1.1 a, 2-0-2 v 1.1 a,
 for VCR37, VCR517 ... 36/6

SPECIAL OFFERS—Midget Mains
 Trans. Primary 220/240 v 50 c/s. Secs. 275-
 0-275 v 70 ma, 6.3 v 3 a, 11/9. Output Trans.
 5,000 to 3 ohms, 2/9.

SMOOTHING CHOKES
 250 ma 3 h 100 ohms ... 11/9
 100 ma 10 h 200 ohms Potted ... 5/6
 80 ma 10 h 350 ohms ... 5/6
 60 ma 10 h 400 ohms ... 4/11

CO-AXIAL CABLE (in.)
 75 ohm 14/36 ... 7d yd
 Twin-Screened Feeder ... 10d yd

TV. PREAMPLIFIER—For Fringe
 Areas—Brand New. Complete with 6F13
 valve. Only 22/6.

SELENIUM METAL RECTIFIERS
 RM2 125 v 100 ma, 4/9; RM4 250 v 250 ma,
 11/9; RM3 125 v 120 ma, 5/9; G.E.C. 300 v
 250 ma, 12/9; 120 v 40 ma, 3/9; 612 v 1 a
 F.W., 5/9; 240 v 50 ma, 3/9; 612 v 2 a F.W.,
 9/9; 250 v 80 ma, 7/9; 612 v 4 a F.W., 14/9.

BATTERY SET CONVERTER KIT
 All parts for converting any type of Battery
 Receiver to A.C. mains 200-250 v 50
 c/s. Supplied 120 v 90 v or 60 v at 40 ma.
 Fully smoothed and fully smoothed L.T.
 of 2 v at 0.4 a to 1 a. Price including circuit
 48/9. Or ready for use 8/9 extra.

**ALL DRY RECEIVER BATTERY
 SUPERSEDER KIT**—All parts for the
 construction of a unit (housed in metal
 case 5-4-1 in.) to supply 90 v 10 ma, and 1.5
 v 250 ma. Fully smoothed. From 200-250 v
 50 c/s mains. For 4-valve receivers. Price
 inc. point-to-point wiring diagrams, 35/9.
 Supplied assembled and tested, at 42/6.

HYPER MICA CONDENSERS. Most
 values 5d. ea. 3/9 doz. one type

VOL. CONTROLS (standard long spindles).
 All values, less switch, 2/9; with
 S.P. switch, 3/9; with D.P. switch, 4/6.
ELECTROLYTICS.—Tubular 8 mfd 450 v,
 1/11; 16 mfd 450 v, 2/11; Can 8-mfd 450 v,
 3/11; 8-16 mfd 450 v, 3/11; 16-16 mfd 450 v,
 3/11; 32 mfd 350 v, 2/11; 32 mfd 450 v,
 4/11; 32-32 mfd 350 v, 5/6; 32-32 mfd 450 v,
 5/11; 64 mfd 450 v, 3/9; 60-100 mfd 350 v,
 7/6.

EX-GOV'T. SMOOTHING CHOKES—
 50 ma 5-10 h ... 2/9
 100 ma 10 h 150 ohms Tropicalised ... 6/9
 150 ma 10 h 150 ohms ... 11/9
 250 ma 10 h 150 ohms ... 14/9
 250 ma 10 h 50 ohms ... 14/9

EX-GOV'T. MAINS TRANSFORMERS
 Primaries 230/250 v 50 c/s 4 v 2.5 a, 4/9;
 4 v 6 a (High Ins.), 7/9; 48 v 1 a, 9/9; 400 v,
 C.T. 150 ma 4 v 6 a, 6.3 v 6 a, 6.3 v 0.6 a, 4 v
 6 a, 4 v 3 a, 5 v 3 a, 4 v 3 a, 22/9; 300-0-
 300 v 120 ma 4 v 1 a, 17/6; 350-75-300-0-300-
 75-300 v 500 ma, 29/6; 610-0-610 v 150 ma,
 300-0-300 v 150 ma, 122 v 350 ma, 29/6; 460
 v 200 ma, 6.3 v 5 a, 29/6; 460 v 200 ma, 6.3 v
 5 a, 29/6.

EX-GOV'T. E.H.T. SMOOTHERS
 .02 mfd 8,000 v, 1/11; .25 mfd 4,000 v (Block).
 4/9; .5 mfd 3,500 v, 3/9.
R.F. UNITS TYPE 26—Brand new. Carton-
 d, 39/6, plus cart., 2/6.

BATTERY CHARGER KITS—Consist-
 ing of attractive Green Crackle Case,
 Transformer, F.W. Rectifier, Fuse, Fuse-
 holder, Tag strip, Grommets, and Circuit.
 For mains input 200-230-250 v 50 c/s 6 v 2 a,
 25/9; 6 v or 12 v, 3 a, 31/6; 6 v or 12 v, 4 a,
 6/9 extra.

R.S.C. 6v or 12v BATTERY CHARGER

For normal A.C. mains input 200-230-250 v, 50 c/s. Selector panel for 6 v or 12 v charging. Variable charge rate of up to 4 A.M.P.s. Fused, and with 5 amp meter. Well ventilated metal case with attractive crackle finish. Guaranteed for 12 months, 69/6. Carr. 2/6.



BATTERY CHARGERS—For mains 200-250 v 50 c/s. Outputs for charging 6 v or 12 v at 1 amp. In strong metal case. Only 19/9. Above can also be used for electric train power supply.

BUILDING THE "SIMPLEX"?

Thousands of enthusiasts are building the "Simplex" Television, now being featured in "Practical Television". WHY NOT YOU? CONSTRUCTOR'S ENVELOPE containing full constructional details and Blue Print, additional notes and suggestions, and Query Service form, sent for ONLY 5/-. All components available ex stock as follows:

ALUMINIUM CHASSIS.—18 s.w.g. DRILLED, with screens and tube holder bracket, 27/6. PLAIN, with screens and tube holder bracket, 29/-.
TRANSFORMER.—350-0-350 v, 150 ma, 6.3 v, 5 a., 5 v, 3 a., tapped at 4 v., ONLY 32/6. (Postage 2/-).
CHOKES.—10 h, 120 ma, 10/6. (Post 1/).
RECTIFIERS.—RM3 3/2 ea., K3/40 6/ ea.
VALVES.—EF50 6/6, 5F61 4/6, 6SN7 9/6, 6J5 5/6, 6B3 3/6, EA50 3/6.
VALVEHOLDER.—89G (EF50) 10d., I.O. and M.O. 6d., Diode (EA50) 6d., VCR97 2/6.

VCR97 TUBE.—Tested full screen, 42/6.
CONDENSERS.—Electrolytics 25 mfd, 25 v, 1/10, 16 x 8 mfd, 450 v, 5/6; 32 x 32 mfd, 450 v, 6/7. Mica, silver mica, and tubulars, 350 v, 6d. each.
POTENTIOMETERS.—All values, pre-set 1/9 each, long spindle 3/1, with switch, 4/6.

RESISTORS.—1 watt 4d., 1 watt 5d., 1 watt 6d., 1.5 k, 5 watt, 1/6.
COIL FORMERS.—(in. 8d., (in. 10d.)
SPEAKER.—6 (in. ROLA P.M. with trans. 17/6 (postage 2/-).

All Components Brand New and Unused. Full Price List available on request.

VALVES

1G6	6/6	7A7	3/6	5Z4	10/-
1E7	6/6	7C5	3/6	5U4	10/-
1LH4	8/-	7F7	3/6	6AC7	6/6
1LN5	8/-	7W7	3/6	6KTGT	5/6
1L4	7/6	12H6	3/6	807	7/6
2B7	8/6	12J5	6/-	ECH35	12/6
3A4	9/-	12AHT	12/6	EA50	3/6
3B7	8/6	12SG7	7/6	EBC33	3/6
6AG5	7/6	12SK7	3/6	EB34	3/6
6AK7	9/6	12SR7	7/6	EF36	6/6
6B4	7/6	28D7	7/6	EF38	6/6
6B8	7/6	32	7/6	EF50	6/6
6C8	8/-	36	7/6		Red
6C6	6/6	50Y6	3/6	Sylvania 8/6	
6H6	5/-	58	3/6	EF91	12/6
6K6	9/-	1622	11/-	EY51	15/-
6L7	7/6	1626	4/-	EK32	6/6
6N7	7/6	1299A	7/6	EL32	7/6
6U5	3/6	VR150/30 8/6	SP61	4/-	
6V6	3/6	VR137	5/9	MU14	10/6
6V6GT	7/6	KT44	3/6	RL37	6/6
6S47	3/6	KT2	5/-	VS70	7/6
6SG7	7/6	VP23	6/6	954	6/6
6SH7	7/6	HL23DD	6/6	955	6/6
6SJ7	3/6	TP25	3/-	9003	6/6
6SK7	7/6	1S5	3/-	9004	6/6
6SL7	9/-	1T4	3/-	931A	50/-
6SS7	7/6	1R5	3/-		

R.F. UNITS TYPE 26 and 27. For use with the R.1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves EF54 and 1 of EC52. Type 26 covers 65-50 Mc/s 6 metres to 27 covers 30-65 Mc/s (3.5-5 metres). Complete with valves, and BRAND NEW IN MAKER'S CARTONS. ONLY 35/- each.

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed Normal Primaries. 425-0-425 v, 200 ma., 6.3 v, 4 a., 6.3 v, 4 a., 5 v, 3 a., ONLY 50/-; 350 v, 0-350 v, 160 ma., 6.3 v, 5 a., 6.3 v, 3 a., 5 v, 3 a., ONLY 42/6; 250 v, 0-250 v, 100 ma., 6.3 v, 6 a., 5 v, 3 a., ONLY 32/6; 350v-0-350 v., 150 ma, 6.3 v, 5 a., 5 v, 3 a., ONLY 32/6, 250-0-250 v, 60 ma., 6.3 v, 3 a., 5 v, 2 a., ONLY 21/-. The above are fully shrouded, upright mounting, 5.5 kv. E.H.T. with 2 windings of 2 v, 1 a., ONLY 32/6. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

E.H.T. TRANSFORMER FOR VCR97 TUBE.—2,500 v, 5 ma., 2-0-2 v, 1.1 a., 2-0-2 v, 2 a., 37/6 (postage 2/-).

PYE 45 mc/s I.F. STRIPS.—The strip this is made for the London Vision Channel. Complete with 6 valves EF50 and 1 of EA50. BRAND NEW. ONLY 70/-.


CHASSIS OF INDICATOR 233.—Contains VCR97, C.R.T. holder, 11 valve holders, resistors, condensers, etc., etc. BRAND NEW. ONLY 10/- (carriage, etc., 5/-).

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station), 5 mins. by Bus from King's Cross. Cash with order, please, and print name and address clearly. Include postage as specified and on Component Orders under £2.

U.E.I. CORPN.

THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.I. (Phone TERminus 7937.)

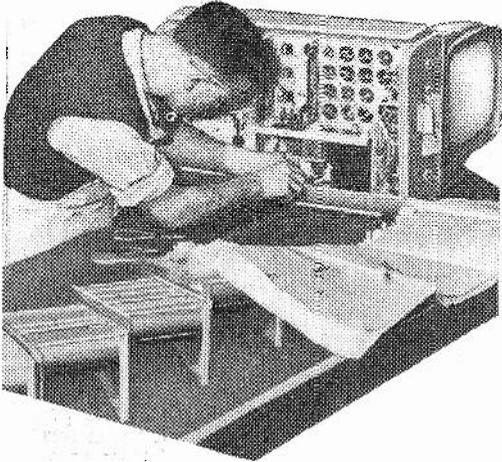PAGES FROM A TELEVISION ENGINEER'S NOTEBOOK



24.—OSCILLOSCOPES

The Time Base

THE choice of a time base for an oscilloscope often presents several difficulties. There is the necessity of keeping the number of valves at a minimum, especially when a compact, portable design is the aim, and this restriction usually leads to a comparatively narrow range of sweep frequencies. A thyatron time base can be made up using a single valve but the frequency is then restricted to a maximum of some 20 to 30 Kc/s at the high-frequency end

and it is not always simple to get good linearity below some 20 cycles at the low-frequency end.

Thyatrions are made to have good high-frequency performances, but in the present design these were dropped in favour of a conventional hard-valve type of generator used in conjunction with one other valve (omitting a clipper diode) to give push-pull deflection. A frequency range of some 5 cycles to 50 Kc/s with good linearity is easily obtained in five switched and overlapping steps, and flyback suppression and the introduction of external synchronising is readily achieved.

The circuit is shown in Fig. 1 and the valves used are type Z77, or equivalents, and an EA50 diode.

Readers will see at once that the circuit is a Miller transitron with switched condenser feedback between anode and control grid. Coupling is also provided through C16 from screen to suppressor, the valve then providing its own triggering and so becoming a free-running generator. The square wave at the screen is clipped by the diode at a level determined by the voltage across R25.

One output is taken to X1 plate from the anode of the transitron, while another is fed via VR6 to the grid of the parphase amplifier V3. There is

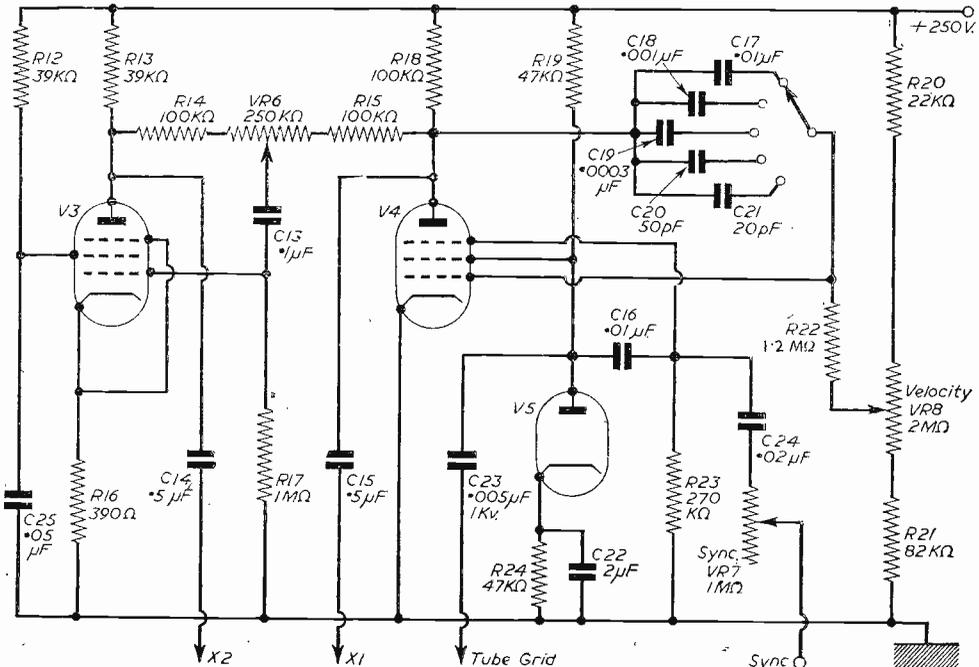


Fig. 1.—Time base circuit. All resistors are 1/2 watt and condensers paper, 350v. working, except C23.

negative feedback between the anodes of the two valves and the gain of V3 is unity, the output at the anode being an inverted but equal version of that at the anode of V4. This is fed via C14 to the other X plate of the C.R.T. and push-pull deflection is obtained. This prevents defocusing at the extremities of the trace and results in a sharply defined image.

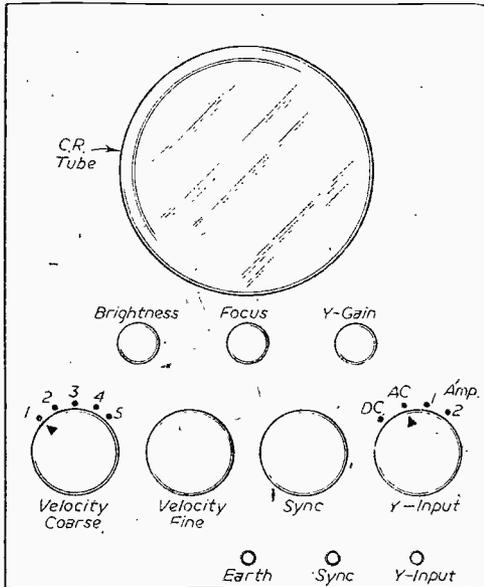


Fig. 2.—A suggested panel layout of knobs and input terminals.

External synchronising is applied through VR7, the sync control, and C24 to the suppressor of the transistor, and so lock the trace to the work signal. A voltage of 15 is necessary for stable lock under normal conditions.

Constructional Notes

A rough layout of the chassis was indicated in last month's article, and this should be followed in main outlines. The total chassis length need not exceed that of the tube and mains transformer combined and, with a width of some 6in., the other valves can be easily mounted along the side of the tube. There are no special precautions necessary, apart from that of mounting the Y-amplifier close to the panel input socket and switch. A suitable control layout is shown in Fig. 2.

A small screen may be well fitted around the Y-amplifier section and the leads to the Y-plates should be kept short and well clear of other leads, especially those carrying A.C. Screening will tend to reduce the bandwidth (on the wide range) of the amplifier, but up to a foot of low-capacity screening may normally be used for the Y1 input without serious effect. The correction choke of 125 μ H is wound on a $\frac{1}{2}$ in. paxolin former from 36 s.w.g. enamelled wire, 95 turns close wound being required.

Use of the Instrument

Normally, the first check on the design is to ensure that the timebase is functioning on all switch posi-

tions and that proper brightness and focus control is obtained. The setting of VR6 is not very critical and it will normally be about two-thirds turned towards the anode of V4. An improper setting will show itself up as a thickening and slight kinking of the trace at one end or other of the scan. This control is, of course, a pre-set and is not mounted on the panel. The H.T. rail voltage should be 250 volts, and R1 may be adjusted if necessary to bring it roughly to this figure should any large change be noticed, provided this is not due to a fault.

Work signal inputs are applied to the input terminal and the amplifier switch is set according to whether an amplified or straight input to the Y-plate is required. Normally, the A.C. position will be used for unamplified conditions of input, particularly on signals where a D.C. component is present, as when investigating ripple on H.T. points of a receiver. With amplified conditions, the narrow band position is most generally useful as a large gain is possible without overloading; a trace amplitude on the screen of roughly 2in. can be obtained without distortion in this position. For video work and other high-frequency set-ups, however, wide-band working will be necessary and here a reduced gain must be tolerated. A maximum undistorted trace amplitude of about $\frac{1}{2}$ in. is obtainable in this switch position. Both the above conditions are with the gain control at maximum setting; there will be some restriction of the high-frequency response, on wide-band working, when the control is used at very low settings and it is always advisable to work it as far advanced as possible. The sync control is normally set fully anti-clockwise (resistance fully in circuit), and only advanced far enough to ensure locking when a sync signal is applied, otherwise distortion will occur.

The base connections of the two tubes mentioned in the previous article are given below.

ECR30

Pin 1 2 3 4 5 6 7 8 9 10 11 12

K G H HA2—Y2 X2 A3 X1 Y1 —

(A2 is focus anode, A3 final anode, internally joined to A1).

DG7-5

Pin 1 2 3 4 5 6 7 8 9

H-K Y1 Y2 A2 X2 X1 A1 G H

(A1 is focus anode, A2 final anode and coating). It should be noted that the ECR30 has a 4 volt 1 amp. heater whilst the DG7-5 has a 6.3 volt 0.3 amp. heater. The recommended transformer is wound for either type of heater.

PRACTICAL WIRELESS

The current issue of PRACTICAL WIRELESS, now on sale, contains constructional details of the new A.C. Fury Four and further notes on the construction of a valve tester.

The first of a new series dealing with the use of test instruments, notes on amplifier design, Low-cost Hi-fi, Programme Pointers, Oscillatory Circuits, Surplus Bolometer Indicators, the 6CH6 for Audio, in addition to regular features such as the Beginner's Guide to Radio, Transmitting Topics, Short-wave Section, complete the issue.

MANUFACTURERS' SURPLUS T.V. COMPONENT BARGAINS

WIDE ANGLE 38 mm.	STANDARD 35 mm.
Line E.H.T. trans., ferroxcube core. 9-16 kV. ... 25/-	Line Output Transformers No. E.H.T. ... 12/6
Scanning Coils, low imp. line and frame ... 25/-	Line Output Transformers 6-9 kV. E.H.T. and 6.3 v. winding. Ferroxcube ... 19/6
Frame Output Transformer ... 10/6	Scanning Coils. Low imp. line and frame ... 12/6
Scanning Coils low imp. line and frame ... 17/6	Scanning Coils. Low imp. line and frame, by Igranic ... 14/6
Frame blocking osc. transformer ... 4/6	Line blocking oscillator transformer ... 4/6
Line Blocking osc. transformer, caslam cored ... 4/6	Frame blocking oscillator transformer ... 4/6
Focus Magnets Ferroxcube ... 25/-	


VIEWMASTER LARGE SCREEN CONVERSION

Enjoy a 14, 16 or 17 inch screen on your Viewmaster. All W/B Components as specified.

- | | |
|---------------------------------|------------------------|
| 1 Line transformer. W/B 113. | 1 Ion trap (Optional). |
| 1 Frame transformer. W/B 114. | 1 B.12.A Base. |
| 1 Pair Scanning coils. W/B 115. | 1K3/100 rectifier. |
| 1 Width control. W/B 116. | 1 K3/40 rectifier. |
| 1 Linearity control. W/B 117. | 1 6C06 Valve. |
| 1 Heater transformer. W/B 119. | 1 6U4 Valve. |
| 1 Focus magnet. W/B 118. | 3 Sundry resistances. |
| | 9 Sundry condensers. |

THE COMPLETE PARCEL Including VALVES
£9 . 3 . 8d. Carriage 3/6d. extra.

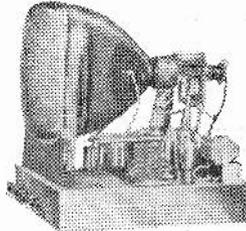Viewmaster Wide Angle Conversion booklet and full details
Price 3/6 Post Free



MAGNIFICENT T.V. CABINET

Complete with full-length doors. Walnut veneer. Outside dimensions: 41ins. high, 23ins. wide, 24ins. deep. The front panel finished in sycamore veneer. Originally designed for use with projection receivers.




THE FINEST VALUE EVER OFFERED IN T.V. CABINETS.
LASKY'S PRICE, £14.10.0. PERSONAL CALLERS ONLY.

THE TELE KING

5 Channel 16 or 17 inch SUPERHET RECEIVER

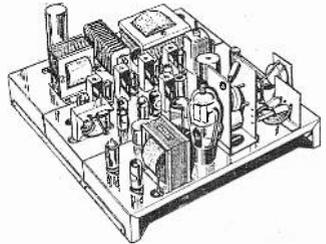This famous and well tried home constructor set can now be built for



£29/10/-.

Only tube and cabinet extra.

EVERY COMPONENT CAN BE SUPPLIED SEPARATELY.

Full constructional data, wiring diagrams and circuits.

Price 6/- POST FREE

WRITE NOW FOR OUR NEW TELE KING PRICE LIST. WE CAN SAVE YOU MONEY.

LASKY'S RADIO (New Branch), 42, Tottenham Court Road, London, W.1.

Telephone: MUSeum 2605.
ONE MINUTE FROM TOTTENHAM COURT ROAD AND GOODGE STREET UNDERGROUND STATIONS.

All our usual lines, plus everything for the serviceman, ham and home constructor. Radio, Television, Hi-Fi, Electronics, P.A. Equipment, Recorders, etc.



Wharfedale, Stentorian, Goodmans, Baker's, Leak, Cosmocord, Vitavox, Hunts, T.C.C., Dubilier, Grundig, Wearite, Acos, Garrard, G.E.C., W/B, etc., etc.

WE HAVE PLEASURE IN OFFERING YOU HIRE PURCHASE TERMS ON CERTAIN ITEMS. Down payments can be arranged to suit yourself. Send us details of your requirements.

SPECIAL OPENING OFFER FOR PERSONAL CALLERS ONLY:
Moving Coil Microphone. Switch incorporated. Listed at £5.5.0.
LASKY'S PRICE.....59/6

NOW OPEN. SAVE MONEY AT LASKY'S

CABINET for THE TELE KING and THE VIEWMASTER

Illustrations available on request. Pleasing design, strongly constructed, finished in walnut veneer. Light, medium or dark shade. Including 14, 16 or 17 inch mask and glass.

Lasky's Price £8.10.0d.
Carriage 12/6.

LASKY'S RADIO,

LASKY'S (HARROW ROAD) LTD.

370, HARROW ROAD, PADDINGTON, LONDON, W.9.

Telephones: CUNningham 1979-7214.

ALL POST ORDERS TO HARROW ROAD.

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs., half day, 1 p.m.

Postage and packing charges (unless otherwise stated): on orders value £1 - 1s. 0d. extra; £5 - 2s. 0d. extra; £10 - 3s. 6d. extra; over £10 carriage free. All goods fully insured in transit.

CATHODE RAY TUBES

For Use with The Tele King and the Viewmaster

- 14 Inch. Mullard. MW36-24. £19 9s. 3d. Brimar. C14FM. £20 10s. 1d.
 - 16 Inch. English Electric. T.301. £22 4s. 10d.
 - 17 Inch. Mullard. MW43-64. £23 12s. 8d. Brimar. C17FM. £24 13s. 6d.
- Carriage and insurance 15/- per tube extra.

Used Mazda C.R.M. 123 Cathode heater short aluminized. Complete with rubber mask Elap P.M. focus unit, scan coils, low line, low frame and frame o.p. trans., £5.10.0. P. & P. 7/6.

Used Mazda 12in. C.R. Tube 121, 121A heater cathode short. £3.7.6. P. & P. 7/8. Guaranteed 3 months.

Used Mazda 9in. C.R. Tube, heater cathode short. C.R.M. 91 92 & 92A. Guaranteed 3 months. 37/6. P. & P. 7/6. Most of the above 9in. with ion burn, 17/6 post paid.

Heater T.V. Cabinet in polished walnut, complete with chassis, 20/- post paid.

USED 9in. TUBE with ion burn, 17/6 post paid.


USED Mullard 12in. with ion burn, 50/- P. & P. 7/6.

Line and E.H.T. Transformer, 9KVA using ferocart core complete with built-in line and width control. Mounted on All-chassis. Overall size 4 1/2 in. x 1 1/2 in., EY51 Rec. winding. P. & P. 2/6. 27/6.

Scan coils, low line, low frame, complete with frame o.p. trans. to match above line and E.H.T., 27/6. P. & P. 2/6.

Heater Transformer, Pri. 220-250 v. 6v. 1 1/2 amp., 6/-; 2 v. 2 1/2 amp. 5/- P. & P. each 1/-.

Completely built Signal Generator. Coverage 120 Kc/s-322 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8.5 Mc/s-25 Mc/s, 17 Mc/s-50 Mc/s, 25.5 Mc/s-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated. R.F. output continuously variable 100 milli volts. C.V. and modulator, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. £4.19.6. or 34/- deposit and 3 monthly payments 25/-. P. & P. 4/- extra.

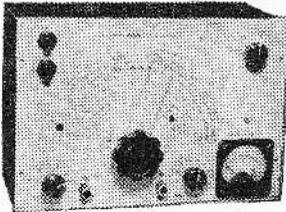

crackle finished case and white panel. £4.19.6. or 34/- deposit and 3 monthly payments 25/-. P. & P. 4/- extra.

Pattern Generator. 40-70 Mc/s direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound rejection circuits, and vision channel band width. Silver plated coils, black crackle finished case, 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 200-250 volts. This instrument will align any T.V. receiver. Cash price £3.19.6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/- extra.

T.V. Converter for the new commercial stations complete with 2 valves. Frequency: can be set to any channel within the 199-198 Mc/s band. I.F.: will work into any existing T.V. receiver designed to work between 42-58 Mc/s. Sensitivity 10 MuV with any normal T.V. set. Input: arranged for 300 ohm feeder. 80 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF80 as local oscillator. ECC91 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier 10 db. Required power supply of 200 v. D.C. at 25 mA. 6.3 v. A.C. at 0.8 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2.10.0. P. & P. 2/6.

Line and E.H.T. transformer, 9KV, ferocart core. EY51 heater winding, complete with scan coils and frame output transformer and line and width control. P. & P. 3/- £2-5.0.

T.V. Filter in lightly tinted perspex size 13 1/2 x 11 x 3/16 in., 4/6. Metal rectifier, 250 v. 250 mA, 12/6. Used metal rectifier 250 v. 150 mA, 6/6.

R. and A.T.V. energised 6in. Speaker, field coil 175 ohms. Requires minimum 150 mA to energise maximum current 250 mA. P. & P. 2/- 9/6.

Valve Holders, moulded octal Mazda, and octal, 74c. each. Paxolin octal, Mazda and octal, 44c. each. Moulded BTG, B8A and B9A, 74c. each. B79 moulded with screening can, 1/6 each.

Combined 12in. Mask and Escutcheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet. 12/6. As above for 15in. tube, 17/6.

Frame Oscillator Blocking Trans., 4/6.

Smoothing Choke, 250 mA 5 henry, 8/6; 250 mA, 10 henry, 10/6; 250 mA, 8 henry, 8/6.

P.M. Focus Unit for any 9 or 12in. tube except Mazda 12in., with Vernier adjustment, 15/-. P.M. Focus Unit for Mazda, 12in. with Vernier adjustment, 17/6. Wide Angle P.M. Focus Unit Vernier adj., etc. tube, 25/-.

Energised Focal Coil, low resistance mounting bracket, 17/6.

Ion Traps for Mullard or English Electric tubes, 5/- post paid.

T.V. Coils, moulded former, iron cored, wound for rewinding purposes only. All-can 14in. x 1in., 1/- each; 2 iron-cores All-can, 24in. x 1in., 1/6 each.

Dubiter .001 10kV, working, 3/6.

Cyclon 5 channel T.V. tuner, 12/6 post paid.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

D. COHEN

RADIO AND TELEVISION COMPONENTS

23, HIGH STREET, ACTON, W.3.

(Opposite Granada Cinema)

SIMPLEX and VIEW MASTER

We can supply all items needed for all versions. Our fully detailed lists are available free upon request.

Full Hire Purchase Facilities

WATTS RADIO 8, Apple Market, Kingston on Thames, SURREY.



QUALITY TELEVISION COMPONENTS
SCANNING COILS
6/10 kV, R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS
LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

SOLDER THE "PRIMAX" WAX FOR 3/7 DEPOSIT and 8 monthly payments of 8/7. (CASH PRICE 70/-)

(Instant Heating—ready for use in 6 seconds, and weighs only 23 oz.)

OTHER SOLDERING EQUIPMENT AS FOLLOWS:

HENLEY SOLON TYPE 625, 19/8 CASH OR 2/6 deposit and 8 monthly payments of 2/6. 65 WATT TYPES, OVAL BITS; 23/8 CASH OR 2/11 and 8 x 2/11. 125 WATT TYPES (OVAL BITS) 40/4 or 4/11 and 8 x 4/11. 240 WATT TYPES (OVAL BITS ONLY) 66/- or 8/1 and 8 x 8/1.

SOLO SOLDER TOOL ready to be run off a 6-volt battery (car or motorcycle battery) 37/6 CASH or 4/7 deposit and 8 x 4/7. The transformer is available to enable the tool to be run off 220-230 v. A.C. mains at an additional 28/3 or 3/6 and 8 x 3/6. A combined De Luxe unit consisting of the Tool and Transformer permanently mounted and wired, in handsomely finished cartons, 35/- or 10/5 and 8 x 10/5. (Send stamp for leaflet.)

ADCOLA, 25/6 or 3/2 deposit and 8 monthly payments of 2/2. Also Handyman's tools as follows: B. & D. 4in. Electric Drill 13/11 deposit and 8 monthly payments of 13/11 (£5.19.6 CASH). 1in. Electric Drill Kit 27/11 and 8 x 27/11 (£11.17.6). Craftsman Lathe, 12/3 and 8 x 12/3 (£5.5.0). 5in. Sander Polisher Kit 27/6 and 8 x 23/- (£9.17.6). (This list is not complete.)

We also stock Wolf, Bridges, Burgess products, etc. Send stamp for leaflet. If you have any particular item in mind, please let us know, we can probably obtain for you and quote our terms.

LAFCO COMPOUNDS Ltd., Desk 103, 8, Corbetts Passage, Roth-

emithie New Rd., London, S.E.16.

BER 4341 (Ext. 1).

IT'S 60% CHEAPER!!

to construct your own aerial, whether
TELEVISION or YAGI


Write for our catalogue, illustrating all fittings, prices, etc. included in the range we offer Alloy Masts, Insulators, Reflector and Director rod holders, Mast head fittings, together with formulae, useful construction hints for designing your own aerial, etc.

Send 9d. in stamps to cover the cost of postage and catalogue to:—

Fringlevision Ltd.

MARLBOROUGH, WILTS.

Phone: 605.

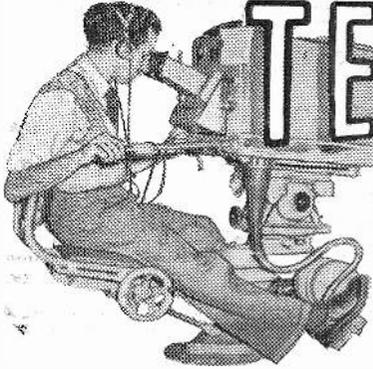

TELENEWS



Soccer in the Cinema

WHEN England played Germany at Wembley on December 1st, TV transmissions of the match were shown on cinema screens in eight cities and towns including London, Doncaster, Leeds and Manchester.

Members of the public were charged for admission.

missions to begin from July, 1956, to serve the interests of "culture, national education, the community and the home."

Nera Ceiling Projectors

FOUR Nera Ceiling Projectors have been permanently installed by the BBC in the Television Theatre at Shepherd's Bush.

These large-screen projection receivers, which were first used by the BBC at the 1952 National Radio Show, provide an audience with "double vision," enabling them to see both the action on the studio floor and the transmitted picture on the receiver screen.

Programme Check Before Cuts

IN future, the North-Eastern Electricity Board intends to refer to the BBC before making power cuts so that the "blacking out" of programmes of national importance can be avoided.

Heated Protest

MR. T. LEONARD, a cafe proprietor, was so disgusted with the standard of BBC programmes that he threw both his radio and television receivers on to a public bonfire in Shepperton on Guy Fawkes night.

Boom in Germany

THE Eurovision link-up between West European countries has caused sales of television sets in Germany to double. The average number sold each month before July, 1954, was 3,000. Now, with more and more programmes being shared internationally, the average is 6,000.

Not Completely Abandoned

"COIN-IN-THE-SLOT" TV, where the viewer inserts money into his set and selects a film he wishes to see, has been dropped in Palm Springs, California, where the system was in its experimental stage. Its backers insist, however, that the scheme has not been completely abandoned.

By February

MR. L. D. GAMMANS, Assistant Postmaster-General, announced in the House of Commons recently that the new television transmitter at Talcolneston would be ready to serve central Norfolk by February.

Tower Inquiry

AN inquiry has been made, it is learned, into the possibility of using Blackpool Tower as a relay station for commercial TV.

Car Ignition Tester

TECALEMIT, LTD., are to market a car ignition tester designed by the English Electric Company, following an agreement recently concluded between the companies.

The tester is comprised of a small cathode ray tube which gives the car owner a complete picture of his ignition system, enabling him to detect and rectify faults with ease.

State TV Service in Sweden


A TELEVISION committee has recommended the Swedish Government not to introduce a commercial television service but to keep it under the auspices of the National Broadcasting Corporation. The committee calls for television trans-

Ghosts from the School ?

RESIDENTS in the Eltham district of south-east London complain of "ghost" television reception which, it is claimed, is caused by steel girders in the new giant Kings Park Comprehensive School built by the L.C.C. Some viewers in the area report that a mixture of BBC and French programmes is sometimes received while others are bothered by background voices in French or German.

Television Licences

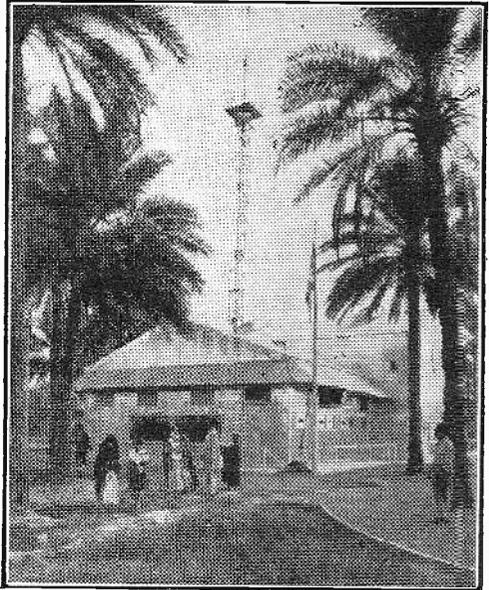THE following statement shows the approximate number of television licences issued during the year ended October, 1954.



The Pye television studio at Baghdad Fair, showing the 408 aerial which transmitted pictures to sets installed in different parts of Baghdad, including the King's Palace.



Bob Hope, Maura Lister and Maurice Chevalier rehearsing a scene for the film made recently at the TV theatre, Shepherd's Bush, for screening on American television.

The grand total of sound and television licences was 13,701,205.

Region	Number
London Postal	1,026,658
Home Counties	407,577
Midland	731,950
North Eastern	538,612
North Western	551,220
South Western	176,616
Wales and Border Counties	201,152
Total England and Wales	3,633,785
Scotland	190,838
Northern Ireland	17,045
Grand total	3,841,668

Bob Hope TV Shows

WHEN he visited this country in November, American comedian Bob Hope had to film his weekly TV programme which is received in about 50,000,000 homes in the U.S.A. The film was made here to keep up the continuity of the series and may be shown later in this country.

This Year's Show

THE Radio Industry Council has announced that the next National Radio Show will be held at Earls Court, London, from August 24th to September 3rd, 1955, with a preview for overseas and other special visitors on August 23rd.

This period is approximately the same as in 1954.

Mr. Peter Dimmock

MR. PETER DIMMOCK, Assistant Head of the Outside Broadcasts Department of the BBC Television Service, and recently Acting Head, has been appointed Head of the department.

Commercial "Plugs"

IT is reported that commercial television in this country will attract an audience of 10,000,000 each evening, and that all the advertising spots will be on film so that planners will be able to time programmes to the split-second.

Newsreel Application

MR. JACK DAVIS, managing-director of the Monseigneur News Theatres and of British Newsreels has applied to the I.T.A. for a contract to supply the newsreel for the national network.

"Keeping Up with the Schmidts"

POST OFFICE officials checking on television licences in a small West German town found that 170 residents, although having an "H" aerial on top of the roof, really had no set at all but just wanted to impress neighbours.

No Swiss TV Yet

THERE is still no regular television service in Switzerland, although test programmes are transmitted on six evenings each week from Geneva and Zurich. These test transmissions are composed entirely of films, however, as Switzerland does not yet possess any TV cameras.

When a television service is eventually inaugurated, it will be run by the State without advertising.

Simplicity the Keynote

SPEAKING to members of the Publicity Club of the Cotswolds in Gloucester recently, Mr. Neal Arden said that when commercial television begins in this country, the keynote of most programmes will be simplicity.

He described how he had helped in the making of a half-hour film which had been shown to the Independent Television Authority as an example of the way commercial shows would be presented.

Sewing Machines Come First

IT is learned from Italy that television receivers cost so much in comparison with wages that the average Italian finds TV beyond his means. "The average household," a report states, "as soon as it has a little money set aside, first buys a sewing machine and then a midget motor-cycle. A long way after comes a TV set."

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

HANNEY OF BATH offers:—

VIEWMASTER.—Constructor's Envelope, 7/6. Stage 1, 62/3; two, 43/3; three, 25/1/8; four, 9/10; five, 41/0/4; six, 27/7/3; seven, 64/-. Complete pre-amp kit (less valve), 32/2. WB100 (sound and vision chassis), 18/6; WB101, 6/-; WB102, 18/6; WB103, 42/-; WB103A, 52/6; WB104, 15/6; WB105, 47/2; WB106, 25/6; WB107, 32/6; WB108, 33/3; WB109/1, 2 or 3 (state tube type), 22/6; WB110, 7/6; WB112, 21/6; WB113 Console conversion kit, 35/-; WB300 pre-amp chassis, 17/6; Westinghouse Rectifiers, 14A36, 20/4; 14D36, 11/2; WX3 and WX6, 3/9 each; 36EHT100, 29/5; 36 EHT50, 28/1; 36EHT45, 23/8; K3/100, 14/8; K3/50, 8/9; K3/45, 8/2. T.C.C. Condensers, 27/10/- (any condenser supplied separately). Morganite pots, 5/- each; Morganite resistors, 35/3. Colvern pots, 22/6; or CLR201, 3/3 each and CLR409/22, 6/4. Belling-Lee L707, 3/9. Fuses, 6d. each. Wearite Coilsets (with L9), L don and Belfast, 22/-; Wenvoe and Pontop Pike, 23/-; H. Moss, K.O.S., B'ham and Brighton, 30/-. Pre-amp coils, 4/- pr. (any channel).

TELEKING.—Constructor's Envelope, 6/-; Coilsets, 44/6; Chassis kit, 50/-; T.C.C. kit, 37/4/8; RM4 rectifier, 21/-; Allen Components, LO308, 40/-; FC305, 21/-; DC309C, 39/6; FC302, 31/-; GL18 and GL18, 7/6 each; BT314, 15/-; SC312, 21/-; AT310, 30/-; OP117, 9/-; Dubilier Resistor/pot. kit, 81/6.

P.T. SUPER VISOR.—T.C.C. Condenser kit, 28/6/4; Erie resistor kit, 54/4; 4 w/v pots, 20/-; 7 Erie carbon pots, 35/-; Allen coils, 44/6; Allen DC300C, 39/6; GL18 and GL18, 7/6 each; SC312, 21/-; FC302, 31/-; OP117 output trans., 9/-; Denco WA/FM1, 21/-; WA/LOT1, 42/-; Denco chassis kit, 51/6; Westinghouse WX.6, 3/10; WG1A, 7/6; LW.7, 26/8; English Electric polystyrene mask, 45/8; perspex filter, 32/8; anti-corona ring, 6/8; Tube sheath, 6/2; 1/501 tube, inc. carriage and insurance, 222/14/10; Elac IT3 ion trap, 5/-.

OSRAM 912 Erie resistor-pot. kit with ceramic tube resistors, very highly recommended, 29/6; Lab. resistor kit, 32/4; T.C.C. condensers, 55/-; **PARTIDGE** Components, with loose lead terminations, Mains trans., 44/-; Smoothing Choke, 25/6; Output trans., 76/9. Price includes Partridge carriage packing charge. Printed panel, 14/6. W.B. chassis, 28/6. Send for complete list.


MULLARD 5 VALVE, 10 WATT AMPLIFIER. T.C.C. Condensers, 45/-; Erie resistor-pot. kit, 37/6; Elstone Mains trans., 38/-; Elstone Output trans., 45/- (both types); Denco chassis, 12/6. Small parts as per our list. Matched pairs of valves are available for both the above designs.

Send 6d. in stamps for our complete list.

L. F. HANNEY, 77 Lower Bristol Road, Bath.

Tel: 3811

Smith's for Technical Books

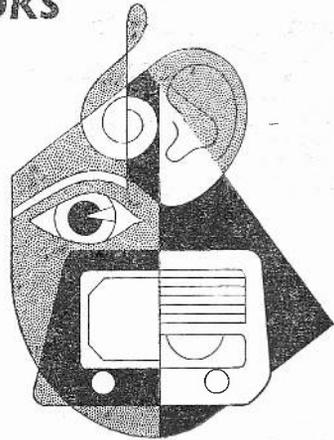

Books on the theory and practice of electronics, new developments, circuit design, and other specialized subjects can be quickly supplied through your local Smith's shop or bookstall.

Your copies of *PRACTICAL TELEVISION* can be bound into attractive volumes; and all your stationery and printed matter supplied through our local branch.

W. H. Smith & Son

for SPECIALIST BOOKS

Head Office: Strand House, London, W.C.2

SIMPLEX MAGNETIC MODEL COMPONENTS

WRITE FOR QUOTATION
RESISTORS, CONDENSERS, VALVES, ETC.

VALVES

EF50	4/-	VP41	2/-	6SL7	7/6	D1	2/-
EC54	9/-	6SN7	9/-	6X7	3/6	UJ4C	8/6
IT4	7/6	1S5	7/6	1LN5	7/-	1299A	7/-
APT4	6/-	6SJ7	4/6	6K7	6/-	6U7	6/-
EBC33	7/6	PT15	6/6	VU111	3/-	VU39	8/6
6AM6	7/6	6BW6	8/6	PEN46	4/6	35L6	9/-
SP81	2/6	EA50	2/-	EP54	5/-	EP39	7/-
6X3	7/6	6J5(M)	6/-	6J5	6/-	EP36	4/-
1R5	7/6	354	7/6	1LD5	7/-	AR8	6/6
6SK7	4/-	6N7	7/-	EL32	7/-	ML6	4/-
VU133	3/-	PEN220	2/6	6AT6	7/6	9BW7	9/6
35Z4	9/-	SP41	2/6	EB94	2/-	EC52	5/-
2X2	2/6	3Z4(M)	3/6	5Z4G	8/6	RK34	2/-
154	7/6	3A4	7/-	3D6	5/-	ARF12	5/6
6SA7	6/6	607	3/6	ECC31	7/6	JT11	6/6
955	5/-	VU120	3/-	HL2	2/6	6AL5	6/-
6K8	11/-	6H6(M)	3/-	807	6/-	6B4	4/-

CONDENSERS.—Elec. Dubilier 500 volt wkg. 20 mfd., 3/-; 22 mfd., 5/-; B.E.C., 450 volt wkg. 3 mfd., 2/-; 8+8 mfd., 3/9; 16+16 mfd., 4/6; 32+32 mfd., 6/-; Bias, 25+25 volt, 50/50 volt, 2/- each. Tubular and mica as last month's list.

RECTIFIERS.—RMO, 5/9. K3/40, 6/9. K3/45, 8/-; CROKER-10, 120 mA (50), 12/- each.

POTENTIOMETERS, 2/6 all valves to 2 meg. 4/- with Switch. Mixed. Our Selection, 1/1 dozen.

COAX CABLE, 1/1m. 80 ohms, any length, 8d. yd.

VINER'S (Middlesbrough)

Radio Government Surplus Electrical

26, EAST STREET, MIDDLESBROUGH

Telephone: MID 3418

Solder with

LIFE SOLD
 THE
**LIGHTWEIGHT
 CHAMPION**
**NO TRANSFORMER NECESSARY.
 FOR MAINS OR LOW VOLTAGES.**
 Sole Manufacturers and Distributors:
LIGHT SOLDERING DEVELOPMENTS LTD.,
 106, GEORGE ST., CROYDON, SURREY. Tel. CR0ydon 8589

Rapid Heating — Extreme
 Lightness — Eight different
 models — Bit sizes, $\frac{1}{8}$, $\frac{1}{4}$, $\frac{3}{8}$,
 $\frac{1}{2}$, $\frac{5}{8}$ — Prices from 19/6.
 A precision instrument for
 discerning craftsmen.

Details of full range in folder
 No. S.11 sent on request.

SPECIAL OFFERS


Dubilier miniature pots, 100K	...	2/6
Dubilier miniature pots, 5K	...	2/6
75 pf air spaced variable trimmers	...	1/3
EF50 valveholders paxolin	...	6d.
Metal rectifiers, 500 v. 150 mA.	...	7/6
6,170 pf. Silver mica 2% condensers	...	6d.
5 mfd. 350 v. single hole fixing	...	2/-
30K 10 watt wire wound resistors	...	1/-
Neon tester and screwdriver combined	...	6/-
Bank of 3—50 pf. trimmers	...	1/-
Bank of 5—50 pf. trimmers	...	1/3

Dealers and bona fide radio service engineers, send for our trade list of resistors and condensers.

Obtainable direct from
HOME RADIO OF MITCHAM
 187, London Road, Mitcham, Surrey. MIT. 3282.
 Open until 6.30 p.m. including Saturdays. (Wed. 1.0 p.m.)

W. B. SUPPLIES

100, OLDHAM ST., MANCHESTER, 4
TERMS.—Cash with order. Orders under 20/- add 6d.; over 20/- add 1/- postage.
CREAM RUBBER MASKS.—For VCR97 etc., correct aspect, 10/6.
STRONG MAGNIFIERS for 6in. Tubes, 17/6.
STANDARD COAXIAL CABLE.—22ft. lengths, 3/11.
HIGH VOLTAGE CONDENSERS.—01 mfd. 4 kV., 02 mfd. 5 kV., .001 mfd. 4 kV., 2/- each.
VALVES.—EF55, 8/6; EF50 Sylvania, 8/- All fully tested.
METERS.—Dual Range, moving coil, 0-20 volts, 0-200 volts, with leads, 10/6.
YANLEY TYPE SWITCHES.—2 pole 6-way (2 Bank), 2/3; 4-pole 3-way midgets, 1/6; 5K Wire-wound Pots, short spindle, 1/-; H.F. Chokes, 8d.
SPEAKER PRET.—Expanded metal (gold) 12in. x 12in., 4/6; 18in. x 12in., 6/9; Woven cloth 12in. x 12in., 2/6; 18in. x 12in., 3/9; other sizes to order.
SPEAKER PRET.—Expanded metal (gold) 12in. x 12in., 4/6; 18in. x 12in., 6/9; Woven cloth 12in. x 12in., 2/6; 18in. x 12in., 3/9; other sizes to order.
RESISTORS.—25 assorted, 2/- packet.
TUBULAR CONDENSERS.—Wire ends, guaranteed non-leak, all at 1500 volts test. .001, .002, .005, .05, .02, .01, 1 mfd., 1/- each, 10/6 dozen.
PENCIL RECTIFIERS.—3.2 kV., 7/6; 3.6 kV., 8/6; 4 kV., 9/-; 8 kV., 14/8.
VIEWMASTER CABINETS.—Complete set of sections in walnut veneer (unpolished) to build 12in. table model cabinet, easily assembled, 45/- set.
JUST PUBLISHED! "Practical Transistors and Transistor Circuits," the latest book on Transistors. 3/9 post paid.
3in. POLYSTYRENE COIL FORMERS with cores, 9d. each, 8/6 dozen. 3in. Bakelite with cores, 9d. each, 6/6 dozen.
"Valve Equivalents Manual." Latest publication giving equivalents for Govt. Surplus and Commercial valves. 5/3 post paid.

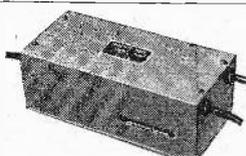

CONVERTOR TYPE 26.
 For conversion from channel 3 to channel 1, complete with self contained power supply unit and totally enclosed in a handsome well finished steel case. Price complete £11-17-0

Also available in chassis form less H.T. supply but including mains operated heater supply for inclusion in receivers. Price complete £8-0-0

CONVERTOR TYPE AC/4
 For weak signal areas. Price complete £15-15-0

(Leaflets on request)

SPENCER-WEST
QUAY WORKS,
Gt. YARMOUTH.
 Tel. : 3009. 'Grams : Spencer-West, Gt. Yarmouth.

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. M.T.
 SHEPHERDS BUSH, LONDON, W.12.
 Telephone: SHEpherds Bush 1729

2 RANGE POCKET VOLTMETERS.—Moving coil, 345 ohms per volt, 2 1/2 ins. dia., calibrated 0-15 v. and 0-250 v. D.C. Fitted with test lead and prods. An accurate meter as new in maker's carton. PRICE ONLY 12/6, post 1/3.

CATHODE-RAY TUBES TYPE VCR97.—Brand new and unused in maker's special transit cases. Television picture tested to ensure freedom from cut-off. PRICE 39/6, carriage 3/6.

AMMETERS.—Switch board mounting projection pattern 4 1/2 ins. dia. Moving iron type calibrated 0-14 amps. A.C. or D.C. First grade meter in maker's carton, as new at the SPECIAL PRICE OF ONLY 12/6, post 1/3.

SPECIAL BARGAIN in VR91's. These are dirty and marked externally but all are tested before despatch and guaranteed electrically perfect. PRICE ONLY 3 for 10/6; 6 for 19/6; 12 for 35/-. Post paid.

SPEAKER GRILLE.—Woven metal with smart gold sprayed finish. Approx. size 15 x 12ins. PRICE 8/6, post paid.

TEST SETS TYPE 102.—Mains operated, emitting synchronising pulses of 25 and 50 cps. Amplitude calibrated 0.2 to 1.4 watts for output lamp. Provision is made for a comparison of outputs by means of a photometer type comparator. Housed in smart metal instrument cases 11 x 10 x 9ins. and fitted with A.C. mains 50 cps. power pack using transformer Pri., 200/250 v. Sec., 6.3 v., 12 v., and 300 v., 1/2 wave selenium rectifier, double triode valve CV18 and valve type 6J5, 1 spare lamp, etc. In good condition with circuit diagram. PRICE ONLY, 32/6, carriage 4/6.

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH
 CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE
 (DEPT. B)
 72-76 Leather Lane,
 Holborn, E.C.1
 Phone: CHAncery 6791/2

20
CIRCUITS

In our "Home Constructor*" Handbook, with full constructional details for building a superhet coil pack, a car radio and a variety of receivers, loads of information, data, etc., and a comprehensive illustrated catalogue.

ALL FOR **2/6** ONLY

* "The Most Helpful Book in the Trade"


SEND FOR YOUR COPY TODAY TO
SUPACOILS (Dept. T.1)
 21, Markhouse Road,
 London, E.17.

TELEVISION COMPONENTS

always in stock for the
**P.T. LYNX, TELE-KING
 P.T. SUPER-VISOR
 THE E.E. TELEVISOR
 AND VIEWMASTER**

Separate price lists available.

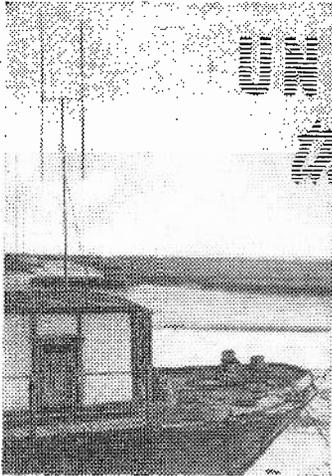NEW 48-PAGE
**RADIO AND TELEVISION
 COMPONENT CATALOGUE**
 available free on request to
J. T. FILMER,
 Maypole Estate, Bexley, Kent
 Tel. Bexleyheath 7267



UNDERNEATH *the* DIPOLE

TELEVISION PICK-UPS AND
REFLECTIONS

By *Icons*

BACK PROJECTION

THE use of back projection in BBC studios varies a great deal in the quality of the results. The equipment for film or still photograph slides has reached a high standard of performance. The uneven results we see, I am told, are largely due to over-confidence on the part of the BBC producers. A film cameraman or a still photographer is despatched to obtain specified background scenes at the docks or an airport—and the weather is bad. Nevertheless, the backgrounds are wanted against time and the producer has perforce to accept photographic backgrounds obtained from flat and dull negatives. The technicians cannot be blamed for this. A first requirement of this particular process, and of the “inlay” and “overlay” matte process is an absolutely first-class photographic negative for the proposed trick background. In America, the use of studio back projection has reached a new peak with the N.B.C. production of *Richard II*, when a screen 15ft. high and 60ft. long was used. This was illuminated by two 90 amp. arc slide projectors using 4in. by 5in. slides made on heat-resisting glass. A new type of screen made of a blue latex rubber has been found to give a better diffusing quality than previous types of screen. It is stated that the picture can be viewed at an angle of 45 deg. to this screen with no noticeable difference in illumination from that observed at the perpendicular. This means that there is less “hot spot” effect in the centre of the screen, a common fault, and a greater flexibility for

the television camera in the use of angle shots from widely spaced camera positions. Incidentally, there were no less than 250 additional television stations brought into operation in the U.S.A. during the 12 months to June, 1954, many of them with 25 kW. and 50 kW. transmitters. It is this intense progress which has forced the American motion picture industry to develop CinemaScope and other wide screen techniques for colour pictures with an aspect of 2.5:1, otherwise the cash customers at the cinemas are inclined to say “We could have seen that on our TV sets.”

STORY TELLING

THE art of story telling on TV is not an easy one. The late Algernon Blackwood could hold one's attention by means of this highly stylised technique. No special props or assistants were necessary; he just sat back in an armchair and talked quietly to the television camera. His marvellous sense of timing and his expressive vocal delivery made every point on sound radio. The addition of picture broadened his technique by enabling us to watch the many slight changes of expression on his face and above all to come under the spell of his almost hypnotic eyes. No one has yet replaced him. Joseph Tomely made a fine attempt when relating Guy de Maupassant's short story, “The Necklace.” The Producer, Tony Richardson, presented him in character of a jeweller in a shop setting with a customer at the other side of the counter. This automatically made the viewer a third party, listening to a story told by the jeweller to his customer. In this way, the personal contact with the viewer was not so close as the simpler and more direct story telling of Blackwood. However, it was a most

enjoyable little feature and I look forward to hearing more stories from Joseph Tomely.

“WAR IN THE AIR”

IN setting out to tell in a TV film the story of air power and its impact on the world during the past 20 years, the BBC set itself a pretty stiff task. “Victory at Sea,” the American documentary TV film, produced by Henry Salomon, reached an extremely high standard in the expert handling of film material from many sources and is still well remembered by viewers. Here was a most professional job of film editing, with a wide variety of material skillfully knitted together with commentary, music and sound effects. Could the BBC match it with their documentary, “War In The Air”? Having seen several episodes, I would say that the BBC has achieved its task most triumphantly. Philip Dorté, who launched and directed the project, assembled a fine team of producers, editors and technicians to tackle the job and the result has been a series of documentaries which have set a new standard. Each episode had its basic background story line, each its build-up of historic sequences smoothly linked with music and commentary, Churchill's war speeches and a cautious use of diagrams. Few viewers could have failed to have been moved by this re-creation of the atmosphere of the terrible days of the Battle of Britain or the stupendous efforts to get the convoys through.

GREAT TEAMWORK

A SPECIAL word of praise must be given to John Elliot, the producer, for his brilliant script and also to John Byers for his excellent sound recording. Philip Dorté, the director of the series, is to be congratulated on what must be his last major undertaking before leaving the BBC for sponsored TV. His next opus will probably appear in due course under the flag of his old chief, Norman Collins, radiated from I.T.A. aerials.

NEWS AND NEWSREEL

THE departure of Philip Dorté from the BBC indirectly focuses attention on the TV News and Newsreel, for it was Dorté who organised the original BBC Television Newsreel and ran it until about a year ago. Since that time, the influence of the sound news side of the BBC has turned it

from being a smooth, slick and entertaining feature into a shapeless, halting mixture of lantern slides, diagrams, and announcements eked out with a few flashes of the old newsreel style. News and Newsreel in its present form is a most unsatisfactory mixture of styles of presentation and its conception is one of the few mistakes of Sir George Barnes. He would be well advised to abandon the "hotch-potch" and adopt once more the conventional cinema newsreel style or the somewhat slower tempo of the original TV newsreel.

"WAITING FOR GILLIAN"

NIGEL BALCHIN'S novel, "A Way Through The Wood," has been read by many thousands who were interested to see just how a TV play could be adapted from it. However, Ronald Miller is a playwright and film scenario writer of high reputation and we were entitled to expect a skilled transfer of the somewhat rambling though absorbing story into the newer medium. Mr. Miller did not disappoint us. He divided the plot into several separate sequences, in the manner of the theatre, interpolated with exterior film sequences and montages worthy of his best film scripts, and an ending in the traditional cinema style. Having said this, it will be appreciated that the ending of the TV play is completely different from the book! However, under the skilled direction of Alvin Rakoff and with a distinguished cast, including Anne Crawford, Patrick Barr and Michael Denison, the play held one's interest for the full ninety minutes of its playing time. The most memorable performance, I thought, was the polished acting of Michael Denison as the Hon. William Bule, in which character he had the advantage of the brittle dialogue traditionally spoken by the theatrical cad.

"THE FAST BUCK"

HALF-HOUR features are the main-stay of American TV. There is a lot to be said for limiting TV plays to this playing time, though such an assertion must not be read as a reflection on the merits of "Waiting For Gillian." Not many TV plays have the weight of story or characterisation to sustain ninety minutes, and "The Fast Buck," a short story in one scene, fitted its twenty-eight minutes, plus titles, to the last second. Here was an amusing little sketch of a couple of confidence tricksters

outwitting a master confidence trickster. A twist ending, in the manner of Maugham, was to be expected and duly turned up. This play was well cast, but the major part of the interest was centred on the interplay between a couple of picturesque crooks, played by John McCallum and Alexander Gauge. Both of these artists once more demonstrated their mastery of television acting technique, under the experienced and smooth direction of Dennis Vance. Praise must also be given to the technicians for first class photographic and sound presentation.


MAGNETIC RECORDING

IN America, magnetic recording for TV and in the film studios is carried out on a multitude of different widths of film and tape, at various speeds. Recordings are made on 35 mm., 17.5 mm. and 16 mm. perforated magnetic film running at 90 to 45 feet per minute, and also on tape running at 7½ and 15 in. per second. Sound chiefs of British film studios, sitting on a technical committee of the British Film Producers Association, have got together to avoid a repetition of this multitude of standards and have decided to standardise on 35 mm. magnetic film running at 90 feet per minute and tape at 15 in. per second. Manufacturers of sound equipment and engineer representatives of the BBC

were invited to attend the deliberations of this Sound Committee, an act of co-operation suggested in this column some months ago. These decisions are well-timed, for photographic recording is on the way out and magnetic is "in."

ARSENIC AND OLD LACE

THE Projection of Britain," a series of three episodes purporting to describe the growth and influence of the British documentary film carried with it a curious atmosphere of arsenic and old lace. The first instalment perpetuated the myth that "Drifters," an interesting film of the herring fisheries of Scotland, launched the documentary film upon an eager public and initiated a new field of information and instruction. Mention of such monumental documentary films as Ponging's "With Captain Scott in the Antarctic" and "With Cobham to the Cape," or other films which preceded "Drifters" was conspicuous by its absence, though excerpts of these films were shown on TV some time ago. Proceeding with excerpts from various odd films from the Empire Marketing Board, the Post Office Film Unit and the C.O.I., most of the films seemed to strike the same note, with the exception of a very fine sequence from Harry Watt's "North Sea," which had the story and tension demanded by audiences.

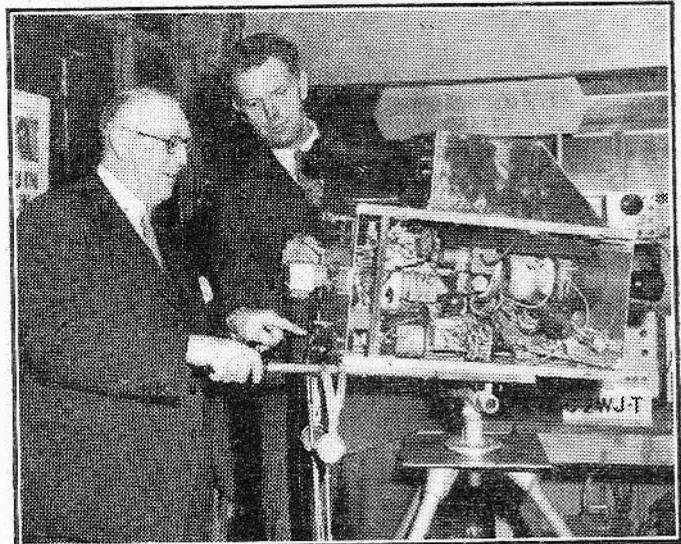

One of the exhibits at the Eighth Annual Amateur Radio Exhibition, organised by the R.S.G.B., was the first British regularly-operated amateur TV station which was built two years ago by Mr. Ralph Royle and his son Jeremy, age 21. Mr. Royle is seen showing the camera he and his son used to Mr. H. Faulkner, C.M.G., B.Sc.

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.s.

AVO METERS IN STOCK

Avo Model 7	—	—	—	£19	10	0
Avo Model 8	—	—	—	23	10	0
Electronic Test Unit	—	—	—	27	10	0
Electronic Test Meter	—	—	—	40	0	0
Valve Characteristics Meter	—	—	—	60	0	0
* Cossor Oscilloscopes Models	1052	—	—	104	0	0
"	"	1049	—	132	0	0

Full range Taylors Meters. List on request.

Leak—TL/10 Amplifier and "Point One"
 Pre-amplifier — — Complete 28 7 3
 F.M. Kit of parts £5 less valves. Ref. Radio Constructor
 July, 1954.
 Chapman Tuning Units — — from 17 6 8

LATEST VALVE MANUALS

MULLARD, OSRAM, & BRIMAR No. 5. 5/- each,
 MAZDA 2/- each.

SCOPE SOLDERING IRON A.C.D.C. HEATING

TIME: 4 v. 6 sec. 6 v. 4 sec. 39/6

Postage 6d, each extra.

Terms C.O.D. OR CASH with order and subject to price alterations and being unsold.

Arthur's Est. 1912

PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS: Gray House,

150-152 Charing Cross Road, London, W.C.2

TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."

CABLES—"TELEGRAY, LONDON."

VIEW MASTER

IMPROVED SOUND NOISE LIMITER

In response to many requests we have introduced a modification to the View Master which will give a much better degree of Sound Noise suppression than the original circuit.

This we call

THE NOISE MASTER

All items needed to incorporate it in your View Master, together with detailed instructions, are available in kit form.

PRICE **26/-** post free.

Sent by return of post.


See Editorial Review on page 335 of the December issue.

WATTS RADIO

8, Apple Market, Kingston on Thames,
 SURREY.

Telephone: KINGston 4099

For HIGH SPEED SOLDERING

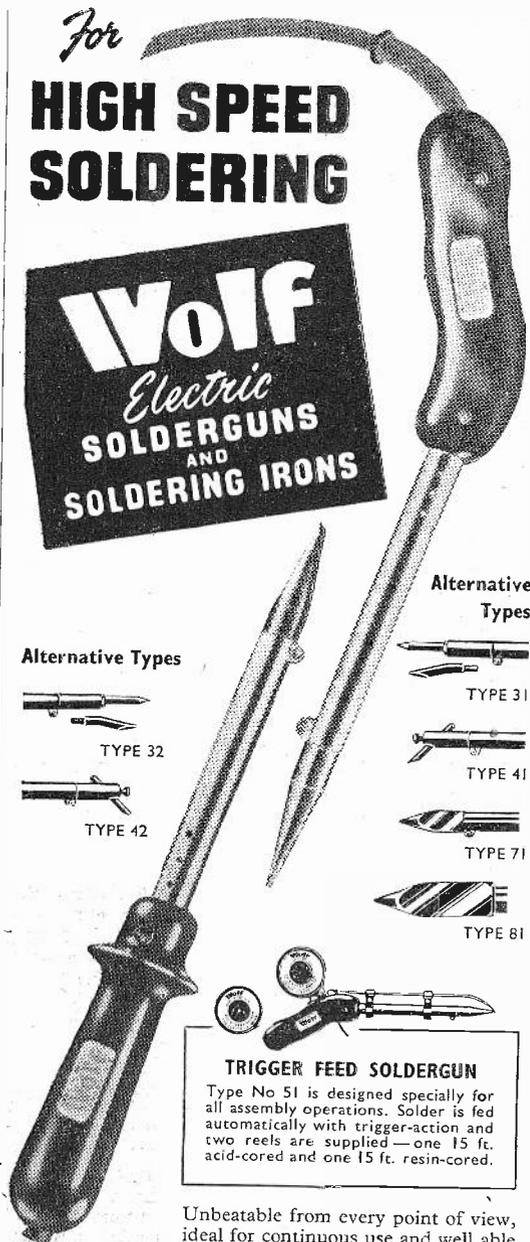

Alternative Types



TYPE 32



TYPE 42

Alternative Types



TYPE 31



TYPE 41



TYPE 71



TYPE 81



TRIGGER FEED SOLDERGUN

Type No 51 is designed specially for all assembly operations. Solder is fed automatically with trigger-action and two reels are supplied—one 15 ft. acid-cored and one 15 ft. resin-cored.

Unbeatable from every point of view, ideal for continuous use and well able to withstand hard workshop treatment. Features include rapid constant localised heat—solid sturdy construction—low current consumption—perfect balance—absolute dependability. A type and bit for every purpose from fine instrument to heavy industrial work. Each tool includes 5 feet tough rubber 3-core cable.

Obtainable from all leading tool merchants and factors. Fully descriptive Brochure free on request.

WOLF ELECTRIC TOOLS LIMITED

PIONEER WORKS · HANGER LANE · LONDON W.5

Telephone: PERIVALE 5631/4

Branches: Birmingham Bristol Glasgow Leeds Manchester Newcastle

BENTLEY ACOUSTIC Corp., Ltd.,

38, Chalcot Road, N.W.1. PRImrose 9090.

024	6/4	6SH7	5/0	83	8/1	K122	5/1
1A3	8/6	6S7	8/1	85A2	10/6	K1W65	5/1
1A5	6/4	6K7	6/1	807	7/6	K1W63	6/8
1D6	8/6	6SN7	8/6	8763	8/1	K1Z63	6/8
1O6	6/6	6U6(UX)	7/1	9004	6/6	K1T65	12/6
1L4	8/1	6U7	8/6	9002	5/6	MH4	5/6
11L5	4/6	6V6Gg	7/1	9003	5/6	Mspen	5/6
1LN3	4/6	6X4	7/6	9006	6/6	Mspen	7/6
1R3	7/1	6X5	7/1	AC23	10/6	N77	6/6
1S5	7/1	6Z4	6/1	AP4	7/6	N78	10/6
1T4	6/6	7C3	7/6	AT4	3/1	OD3	8/6
1921	8/6	7C6	7/6	BL63	7/6	PPCS4	12/6
2X2	4/6	7D3	6/1	DAP0	6/6	PPCS0	12/6
3D6	2/6	7H7	7/6	DH77	8/1	PPN46	7/6
305	10/1	7Q7	8/1	DL72	9/6	PL81	10/1
50C5	10/6	7R7	8/6	DL83	8/1	PL82	10/1
5U4	8/1	787	7/6	EA30	1/6	PM12	4/1
5Y3	7/6	8D2	2/6	EAT6	10/1	PM12M	7/6
5X4	8/6	9D2	3/1	EAC91	9/1	PY80	10/1
6A7	8/6	10LD11	10/1	EB34	1/6	PY81	10/1
6AB7	6/1	12A6	6/6	EB91	6/6	PY85	8/8
6AC7	6/6	12AH7	12/6	EC33	7/6	QY20	5/1
6AG5	6/6	12AT6	10/6	EBC41	10/6	RM4	12/1
6AK5	7/6	12AT7	7/1	EC91	7/1	SP4	7/6
6AM6	6/6	12AU7	9/1	ECC33	9/1	SP41	2/6
6AQ6	9/1	12AX7	7/1	ECC35	9/1	SP31	2/6
6AT6	8/1	12BA6	9/6	EC82	10/6	ST22	8/6
6BA6	6/6	12BE6	6/6	ECC91	7/6	U78	8/6
6BE6	6/6	12EL1	30/1	ECH42	10/1	U929	10/6
6BJ6	6/6	12K8	8/6	ECL80	10/1	UAF42	12/1
6BW6	7/6	12S7	7/1	EF36	4/6	UBC41	10/6
6BX6	10/6	12SK7	6/6	EF39	6/6	UB121	12/6
6C4	7/6	12SO7	8/1	EF80	10/1	UGH42	10/6
6CH6	6/6	12SR7	7/6	EF42	10/1	UP41	9/1
6F12	6/6	14H7	10/6	EP50E	5/1	U441	9/1
6P17	9/6	14R7	10/6	EP50A	8/1	U46	10/1
6P22	6/1	15D2	4/1	EF54	5/1	U441	9/1
6P33	8/6	15OA2	10/6	EF73	10/1	V12	5/6
6H6g	2/6	18	8/1	EP80	10/1	VP2B	10/6
6J5g	5/1	19H1	10/1	EP91	6/6	VP4	8/6
6J6	7/6	19H4	35/1	EL22	6/6	VP22	6/6
6J7g	5/1	20L1	11/6	EL91	6/6	VP41	7/6
6K6g	6/6	20L6	8/6	EM34	10/6	VR33	5/6
6K7g	5/1	30L1	11/6	EV91	7/6	VT501	6/6
6K8g	8/1	35L6	8/1	EZ40	8/6	W77	5/6
6L7g	7/6	42	8/1	PC2	10/6	X24	10/6
6N7g	7/6	43	8/6	H30	5/1	X66	7/6
6H7g	8/1	72	4/6	HLL320	6/1	Z77	6/6
6SA7	8/6	77	8/1	KF35	8/6	Z719	10/1

Post 6d. each. 24 hour C.O.D. service. All boxed and guaranteed. Complete list free S.A.E.

The OSRAM NINE - ONE - TWO

Amplifier Instruction Book and Highest Quality Components

Available from **Coventry Radio**

189 Dunstable Road, LUTON. Phone 2677

Book 3/6d. plus 3d. postage. Our 1954-5 Component Catalogue 1/-

VALVES SAME DAY SERVICE All Guaranteed New and Boxed

1A7GT	6K3G	8/6	25Z8	9/6	EL91	7/9	
1CSGT	6K2CT	9/1	35L6GT	8/6	EY51	12/1	
1HSCT	9/6	6K25	11/6	6/6	EZ40	8/6	
	6L20	9/6	35Z4GT	8/6	EZ41	9/6	
1NSGT	11/6	6P25	14/6	8/6	FW1/500		
	6P28	17/1	35Z6GT			12/6	
	6Q7GT	9/1		9/6	CZ32	16/5	
1R5	7/3	6SN7GT		50L6GT	KT63	7/6	
1S4	7/3				MU14	8/6	
1S5	7/3	6U4GT	8/6		Pen45	15/1	
1T4	7/3		17/1	807	PL81	10/1	
3Q4	7/6	6V6G	7/6	AZ31	11/6	EZ42	9/6
3Q5GT	7/6	6V6GT	7/6	D77	6/9	PL83	12/6
	11/6	6X4	7/6	DAC32		PY30	9/6
3S4	7/3	6X5GT	6/9		11/6	PY81	10/1
5U4C	8/6	7C5	7/6	DH73	11/6	PY82	7/9
5Y3GT	7/9	7C6	7/6	DK32	11/6	R12	15/1
5Z4G	9/1	7H7	7/6	DK92	7/6	T41	15/1
6A7	10/6	7S7	7/6	DL33	11/6	U14	8/6
6AL5	6/6	7Y4	8/6	DL35	9/6	U22	7/6
6AM5	7/9	10C1	12/6	EB91	6/9	U24	17/6
6AM6	7/9	10F1	10/1	EBC33	7/6	U25	12/1
6AT6	8/6	10LD11		EB41	10/1	U50	7/9
6BA6	6/6			EBF80		U78	8/6
6BE6	6/6	10P13	10/1		10/6	U84	9/1
6BH6	6/6	10P14	11/6	EC91	7/6	U801	14/6
6BJ6	6/6	12AH8	10/1	ECC81	9/1	UBC41	9/1
6BW6	7/6	12AT7	9/1	ECH35		UBF80	
6BW7	9/6	12AU6	7/6		11/9		10/6
6CH8	8/6	12AU7		ECH42		UCH42	
6C4	7/9		10/6				11/6
6C9	8/6	12J7GT		ECL80		UF41	9/1
6F6G	7/6		10/6		10/1	UF42	13/6
6F12	7/6	12K7GT		EF37A		UL41	11/6
6F13	13/6			EF39	17/1	UL9	16/1
6F14	13/6	12K8GT		EF39	6/6	UY41	9/1
6F15	10/6		10/6	EF41	9/1	VP4B	12/6
6J6	8/6	12J7GT		EF50	7/6	W77	5/6
6J7GT	7/6			EF80	10/1	X78	13/6
6K7G	6/1	20D1	9/1	EF91	7/9	Y63	7/6
6K7GT	6/1	25Z4G	8/1	EF92	5/6	Z77	7/9

Postage 4d. per valve extra. T.A. 587.

READERS RADIO 24, Colberg Place, Stamford Hill, London, N.16.

JUST PUBLISHED Radio and Television Engineers' Reference Book

Edited by E. MOLLOY & W. E. PANNETT
Broadcasting · Communications · Navigation · Servicing, etc.
36 specialist contributors. Over 1600 pages Over 1860 diagrams
70s. 0d. post free

The Oscilloscope at Work, by A. Haas & R. W. Hallows. 15s. 0d., postage 8d.
Television Receiver Servicing: Vol. I - Time-base Circuits by E. A. W. Spaldbury. 21s. 0d., postage 9d.
Television: 2nd edn., 1954, by V. K. Zworykin & G. A. Morton. 140s. 0d., postage free.
Unit Constructed TV Receivers, by E. N. Bradley. 6s. 0d., postage 3d.
Television Engineers' Pocket Book, edited by E. Molloy & J. P. Hawker. 10s. 6d., postage 4d.
Radio Valve Data: 4th edn., compiled by "Wireless World." 3s. 6d., postage 3d.
Please write or call for our catalogue.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS OF British and American Technical Books.
19-23, PRAED STREET, (Dept. T.1) LONDON, W.2.
Phone: PADDINGTON 4185
Open all day Saturday

OPPORTUNITIES IN TELEVISION

144 pages 8/6 **Free!**

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS—NO FEE"
If you are earning less than 15 a week you must read this enlightening book. Send for your copy NOW—FREE and without obligation.

WRITE TODAY!
British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane, **BIET**
Kensington, W.8.

RADIO AND TELEVISION COMPONENTS

All parts in stock for: VIEWMASTER, SOUNDMASTER, TELEKING, ETC.
Easy Terms Available. Stamp for list, NOT S.A.E.
JAMES H. MARTIN & CO.
Finsthwaite, Newby Bridge, Ulverston, Lancs.

INDICATOR UNIT TYPE 233, with VCR97 and 8 valves. Ideal for Simplex. Only 42/6.
MICROAMP METERS, 100µA. 2 1/2 in. proj. min-max. scale, 27/6. 500µA 1 1/2 in. rd. fl. 0-10 scale, 8/6. Amps. 20, 0, 20, M/c. 50, F.L. 2in., 2/6. CERAMIC rotary switches. 3 for 1. Metal rescs. 300 v. 80 mA, 6/-. 300 v. 120 mA, 7/6. EF50 bases, 6d. Cer. 807 cer., 1/- Aladdin coils wound for R1155s. 4d. 1/-. with core. 4d. H1 res. earpieces, 1,620/0. 3/1. 100 K WVV POTS, 3in. DIA, canned, 6/6. 100 K, car. sp., 1/-. Fixed WVV res. 100Ω 200 watt. vit., 4/-. 20Ω, 30Ω 5 K, vit., 3/1. 9d. 100K, 5K, 10 W, vit., 1/-. Tog. sws., bak. sp. dt., Dp., st., 9d. 250 v. 10 amp. 1/6. Chokes, 20H, 30 mA. Ex-equip. 4/6. Twin chassis. mnt. fuseholders, 6d. LR headers, 7/-. Std. off. insu. fin. high. 6d. Res. 1 w. 3d. 1 w. 4d. 1 w. 6d. Valves. Bulgin panel lamps, red or green, 2/-. Terminal strips, 4-way, 4 for 1/-. EF50 Bases, Ex-equip. 3 for 1/-. 100 pF mica, 3d. ea. 500 pF mica, 4/-. 5P41, Ex-equip. 1/3. 4K, 20K, 25K, vit. res., at 20 wt., 2/-. ea. 2,600 pF, 5,600 pF, S, M, 1 Kvv, 3 for 1/-. ARP12, VP23, 4/-. 5K, 5w, ww Pots., 2/-. ea. H, R, Headers, 3,000Ω, 7/6. 1in. Iron Dust Cores, 2/8 doz. Post Extra, Ex-equip only if stated. S.A.E. for lists.

BATES SURPLUS STORE
49, IVY ST., BIRKENHEAD, CHESHIRE

Your problems solved



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p. 383 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

ADJACENT CHANNEL INTERFERENCE

I have a Pye V4 in conjunction with a J-beam acria (four element) and have changed over from Holme Moss to the Isle of Man. I get a much better, far more reliable picture but with the following defect.

The picture is crossed by horizontal lines, sometimes about $\frac{1}{4}$ in. apart and sometimes perhaps 1 in. and these are sometimes hardly noticeable and at others are most distracting. They are continually on the move and change from going up to going down most erratically. I rather suspect that the set is not at fault as others get the same result, but is there anything that I can do to counteract it? None of the ordinary controls has any effect. I might say that in the intervals when there are no such lines the raster looks rather like fine linen with vertical, somewhat irregular lines running vertically. But still, Isle of Man is the best we can get on this Cumberland coast!—W. A. Henderson (Whitehaven).

The picture disturbance described is almost certainly the result of external spurious signals adjacent to the vision frequency of the Isle of Man transmitter. They are most likely originating from the local oscillator of neighbouring receivers tuned to a different channel. Unfortunately, there is little that can be done at the affected receiver to alleviate the effect. It is generally a matter of completely screening the offending set, or installing wave-traps in the associated aerial system. The G.P.O. interference investigation department should be able to give you assistance in this connection.

SOUND ON VISION

I have an Ultra television model V8ULF with J-type aerial and could you please help me with the following? I have a hum all the time but more pronounced during transmissions from the studio, namely, announcements, weather and also during the showing of test card "C." This hum can be cured by the following:

(a) Tuning selectivity back in an anti-clockwise direction.

(b) Reducing contrast with selectivity adjustment.

By doing either of these till hum disappears I get in return a very poor picture, "white-washy" and blurred. I have had the set 18 months and this hum has gradually crept in during the last three months. The set is tuned to Brighton, about 40 miles distant.—C. J. Petter (Chichester).

This effect is known as vision interference on

sound and it is, in fact, caused by the vision signal gaining admittance to the sound section. Since you mention that the disturbance has appeared gradually during the last three months, we feel that it is the result of a drift in the alignment of the tuned circuits. If you cannot cut it out entirely by adjusting the local oscillator trimmer for maximum sound, consistent with minimum *sound interference on vision*, your set may have to go to your Ultra dealer for complete realignment.

H.T. RECTIFIER FAILING

I am having trouble with my G.E.C. TV, model BT454, which is 12 months old and has had three KT36 and one Z77 valves.

For some time now the width has been closing in towards the centre of the screen. My width control fails to operate on the outward, or the width, to give me a full picture or mask and leaves the black line $\frac{1}{4}$ in. to $\frac{1}{2}$ in. each side. My horizontal form is all right. But the width will take the picture in, but not out. It is not possible to get test card C at width by well over $\frac{1}{2}$ in. each side.

My picture fades out and the only thing which will bring the picture back is to ease back the brightness control to focus again.

This does not happen on every picture.—J. S. Whitehead (Stoke-on-Trent).

The lack of full picture width on your set is almost certainly caused by wear in the metal H.T. rectifier. We would advise, therefore, that you have this part checked for efficiency and replace it if necessary.

A certain degree of defocusing is normal on your set when the overall brightness of a picture suddenly increases—such as during a newsreel programme. We would mention, however, that the effect is aggravated somewhat by a low emission E.H.T. rectifier valve.

A slightly misplaced aerial would have no bearing at all on the above defects.

LOW E.H.T.

I am still having some trouble with my Simplex. The cause of it all is the E.H.T. which is very low—700 volt. But if I disconnect VR9 from the circuit I can get 1,000 volt reading on my electrostatic meter. I have replaced VR9 and also re-checked my circuit, but it is still the same.—R. Avery (Coventry).

Lack of E.H.T. may be due to faulty rectifiers, faulty smoothing condensers (they should be tested at full working voltage), faulty E.H.T. network due to leakage direct to chassis by corona discharge, and finally by too low a value for C34.

These points should be checked.

VIEWMASTER FRAME AMPLITUDE

I have recently converted my Viewmaster to take the Cossor 15in. tube. In doing this I have increased the E.H.T. and scanning amplitude of both line and frame line bases.

Before fitting the line and frame moderator I found the picture width was $\frac{1}{2}$ in. short on the right-hand side, and the height and depth suffered the same.

The frame moderator gave me more height but caused a foldover at the bottom and cramping at the top. I have altered C49 to 0.025 μ F; this has nearly corrected the foldover but has slightly affected the height. I have tried decreasing R56 to 220 k. but without effect.

The line moderator, even with the 1 M Ω resistor in parallel with R46 removed, still gives me a bright line on the right of the picture.—D. Brooks (Princes Risborough).

To increase frame amplitude even further we suggest the following modification.

Connect a 1 μ F condenser between the top of R60 and the junction of R57 and C48, reduce the value of R66 to 220 Ω , connect a 1,000 Ω resistor in parallel with R65, delete R67, then adjust R64 and R65.

To remove the bright line on the left of the picture it should only be necessary slightly to increase the value of R46, the best way being to connect a variable resistor in series with it; at the same time connect a 500pF condenser across the line scanning coils tags L1, L2.

INCREASING E.H.T.

I have an Ekco TS46 which has recently been thoroughly overhauled by a qualified dealer.

Although the picture is good as far as brilliance and contrast are concerned, the general focus is not all that it should be. When the centre is in focus the corners are slightly out, and about $\frac{1}{16}$ in. of the right-hand edge is quite appreciably out of focus.

I have heard that by increasing the E.H.T. to the maximum allowed by the makers (in this case 6,000 volts) it is possible to overcome this fault. Can you tell me how this is achieved?

There is another fault and that is that when the set is first switched on the picture is broken up linearly, but as the set warms up this slowly corrects itself from the bottom upwards until the picture is fully held. This takes about 10 minutes. If the line hold is adjusted when the set is switched on the picture breaks up after about 10 minutes.—K. A. Noll (London).

The E.H.T. potential in your receiver is 6,000 volts, and it is not readily possible to increase it above this value. Uneven focus generally indicates that the focus unit has been shifted relative to the neck of the tube. You should try the effect of adjusting this in your case. The line hold defect is almost certainly caused by a worn line oscillator valve.

USING THREE-CHANNEL TUNER

I wish to replace the front end of my Magnaview receiver with a commercial three-channel tuner, being particularly interested in the "Pilot" as it has means of a slight oscillator adjustment by means of a ring round the selector knob. Could you tell me if this unit would be suitable, or if not could you suggest any other make that would do? The vision I.F. in the Magnaview is 19.75 Mc/s, and sound 23.25 Mc/s, as you probably know. I have plenty of heater and H.T. current to spare.—J. Williams (Manchester).

As a potential aid to minimise possible interference

in Band III due to local oscillator radiation, Band 1-3 (13 channel) front-end adaptors are designed to have an I.F. output in the region of 35 Mc/s. For this reason, therefore, they would not be suitable for use with your receiver in its present form.

LINE FOLDOVER

I would be very grateful if you could give me any advice with my problem of "foldover." The set is a Marconi VT73DA, and the foldover is on left, accompanied by a bright band about $\frac{1}{2}$ in. from left-hand edge of mask.

I have tried to cure by replacing main rectifier and also cathode bias resistor of line output valve KT36, but without success.

At its most the foldover is about $\frac{1}{2}$ in., although this varies at different times.—H. Morris (West Bromwich).

Make sure that the U31 efficiency diode and the associated 2 μ F electrolytic capacitor are well up to standard. Check the 0.01 μ F capacitor coupling the line generator to the KT36 for insulation—if a slight leak is evidenced the capacitor should be replaced. Suspect the line output transformer and/or line scan coils for short-circuited turns.

INCREASING E.H.T. VOLTAGE

In my Masteradio Model T412 I have altered the tube to a C12B with P.M. focusing. The E.H.T. is insufficient to give me a good picture and I would like to add a 5 Kv R.F. unit in series, to make 10 Kv. Can this be done? I can add an efficiency diode for the consequent non-linearity which will result, or decrease the E.H.T. on the R.F. unit.—P. C. Whittingham (St. Albans).

We do not advocate the modification you suggest. It is, of course, feasible to raise the E.H.T. potential by means of an R.F. E.H.T. generator, though extreme care would have to be taken to achieve correct potential distribution throughout the series network. Another method is by rectifying the pulse potential existing at the anode of the line output valve during the line flyback, and adding the so-derived D.C. in series with the existing E.H.T. supply. The main trouble that will almost certainly arise in both of these cases is the unavailability of sufficient scanning power.

H.T. RECTIFIER FAULTY

I have an Invicta T105 about which I would be most grateful for advice.

With the line amplitude plunger at maximum, on first switching on, the line timebase fails to reach the mask both left-hand and right-hand sides of the screen by $\frac{1}{16}$ in. to $\frac{1}{8}$ in., but after the set has been running about 30 minutes the amplitude creeps until mask is just filled.

I have renewed line generator EF50 and amplifier PL38M with no effect or fault at all. Frame timebase has no fault.—R. Wellis (Alton).

Yours may be due to H.T. rectifier trouble. Two metal rectifiers are used in your set for this purpose, and they often reduce in efficiency to provoke the symptom described. You should check the H.T. line voltage over the period of time it takes for the effect to correct itself; if the voltage rises gradually you should have the rectifiers tested for efficiency. The normal H.T. line potential in your set is 245 volts, and the total H.T. current ranges between 220 to 240 mA.

NEW BOOKS for the constructor, "Unit Constructed TV Receivers," by Bradley, everything from 3in. ex-Gov. tubes to 15in. magnetic, 6/- each; "TV Circuit Refinements," by Banthorpe, telling you how to improve your set, 5/-; "TV Faults," by Stevens giving actual circuits of six leading manfr., 5/-; "TV Fault Finding," the ideal book for the beginner, 5/-; "TV Picture Faults," 3/6 each; "TV Test Equipment," by Bradley, describing the construction of all the instruments you need, 5/-; "The Oscilloscope Book," by Bradley, 5/-; "Transistors and Crystal Diodes," by Bettridge, what they are and how to use them, 5/- Send stamp for free list if you are not already on our mailing list. **SERVIO RADIO**, 156-8, Merton Rd., Wimbledon, S.W.19. (LlBerty 625.)

BARGAINS. R.F. Units 26 or 27, 27/6; 24 at 12/6 brand new, with valves; 25 soiled 12/6, post 2/4 each; EHT trans., 2,000v. 5ma, and 2v, 24, 25/-; 250v. 30ma HW and 6.3v, 1.5a, 9/-; Eliminator trans. 110v 30ma and 6.3v, 3.2a, 8/6; 350-0-350v 200ma and 5v, 3a, 25/-; all 230v input, post 2/-; Metal rectifiers, 270v 80ma 6/-; 600v 30ma 6/-; 480v 80ma 6/6; 240v 30ma 4/-; List and enquiries s.a.e. please. Cash with order, immediate delivery. **W. A. BENSON**, 308, Rathbone Rd., Liverpool, 13.

SERVICE AIDS: Nuts, Bolts, etc., Solder, Instrument Wires, Sleeving, Coils, Formers, Trimmers, etc., etc. In fact, all the O's and S's you can't do without. Free list for the asking. Return post service. **RADIO UNLIMITED '50**, Hoe St., Walthamstow, E.17. (LAR 6377.)

NEW 9in rubber masks 3/- p. pd.; E.H.T., 001 10Kv 3/6 ea.; stamp for details. Band 3 converter, compl., with 2 valves 47/6 p. pd. **E.K.E.**, 47, Arksey Lane, Bentley, Doncaster.

R.F. UNITS, types 26 at 27/6, 25 at 15/-, 24 at 11/-; brand new in original cartons, with valves; postage 2/6. **E.W.S. CO.**, 69, Church Rd., Moseley, Birmingham.

JIM'S RADIO COMPONENTS, 23, Alexandra Rd., Sleaford, Lincs. Send s.a.e. for free price list and order forms.

VIEWMASTER (Wenvoe) 12in.; good working order. **W. STARR**, Yew Tree Farm, Westham, Wedmore, Som.

IN GOOD ORDER, 9in. Mullard, table model, £15; 9in. Pye, table model, £17; Sphere Signal Generator, as new, £8/10/-; require attention, 12in. Marconi Console, £15; 15in. Electronic Console, £18/10/-; **POLLARD** 5279, after 6 o'clock.

LONDON ARGUS with enlarger; cheap; needs slight attention; amateur can't get working. 39, Percy Road, Finchley.

1st P.R.E. Data for constructing "TV Aerial-strength Meter" 7/6; 5,500 Alignment Peaks for superhets, 5/6; sample copy "Practical Radio Engineer", 2/-; Membership-examination particulars, 1/-; Syllabus of seven postal courses free and post free. **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest electronic organisation; moderate fees. Write to Dept. PT28, E.M.I. INSTITUTES, London, W.4.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

PREMIER 1951 12in. Console, (less C.R.T.) needs adjustment, £10. **F. C. SMITH**, 28, Warwick Road, Wandstead, E.11.

ALL TV. COIL SETS made to order; many stocked; commercial TV. Converters; High Fidelity Feeder Units from £7/5/-; **BEL**, Marlborough Yard, N.19. (ARChway 5078.)

A BIG ADVANTAGE of using our boxed service is that in most cases a stock replacement can be supplied. We have the most complete I/V component replacement service in Great Britain. Have you tried "Nuray" the heater booster isolator that just plugs in? "DIRECT TV REPLACEMENTS," 134-136, Lewisham Way, New Cross, S.E.14. (Tideway 3996-2320.)

BOOKLETS: "How to use ex-Gov. Lenses and Prisms," Nos. 1 and 2, price 2/6. Ex-Gov. Optical lists free for s.a.e. **H. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

TV WITHOUT MAINS.—Absolutely first-class picture, plus DC circuit for lighting; as supplied to the B.E.C. Special AC/DC "Chorehorse" Generators, self-starting, compact, and complete. AC 220/250 volts, 50/60 cycles, 250/350 watts AVC. Will run radios, vacuum cleaners, small tools, etc. £47/10/-, plus 10/- delivery Below.

STORAGE BATTERIES, 12v, 75AH heavy duty, 19 plates, separate cells in hardwood cases; finest possible specification. £5/17/6, 9/6 delivery; 12v, 22AH, almost similar specification, surprisingly powerful, £2/14/-, delivery 5/6. **TEDDINGTON ENGINEERING CO. LTD.**, Dept. "C," High St., Teddington, Middx. (KINGston 1193-4.)

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.

A MANAGER is required to take charge of the radio components division of an electrical engineering Group in the East Midlands. In addition to the control and expansion of the sales organisation, the post carries the responsibility for co-ordinating all other considerations such as design, production and estimating etc. Applicants must have a sound knowledge of the radio components business and its potentialities and should have initiative and drive to open up new markets. The post, which carries a salary of not less than £1,500 p.a. is permanent and pensionable. Please write stating age, qualifications etc., to Box 2.J.L 7393 A.K. ADVG., 212a, Shaftesbury Ave., London, W.C.2.

LEADING VALVE and Cathode Ray Tube Manufacturers require statistical clerk. Should have good knowledge of simple statistics, or mathematics to matriculation standard, with interest in Radio/Television. Must have completed National Service. Salary £400 approx. Excellent future prospects; pension scheme. Box No. 300. **DORLAND ADVERTISING LTD.**, 18/20, Regent Street, London, S.W.1.

AMERICAN MAGAZINES.—One-year "Audio Engineering," 35/-, specimen copy, 3/6; "High Fidelity," 50/-, specimen copy, 4/6; "Popular Science," 28/6. Free booklet quoting others. **WILLEN LTD.** (Dept. 23), 101, Fleet Street, London, E.C.4.

SIMPLEX T.V. 18 swg. Chassis with screens and valve punched 17/6, post 1/6; fully-wound Coil Sets 15/-, post 1/-; Lynx wound Coil Sets, 35/-, post 1/-; Super-visor and Tele-King Coil Sets, 37/6, post 1/-; 3in. square Cans, Former, Side Wires, etc., 1/9 each; Simplex Mains Transformers, 27/6, post 1/6. **C. O. PRESTON YORKSHIRE**, Healey Lane, Batley, Yorks.

WINWOOD FOR VALUE. New, Boxed Valves: EB91, EF91, 6/6; 6K8G, 6V6M, 6SN7, 6SL7, 6F6G, 5U4, 807, 7/6 each; ECL80, 8/9; EF37a, 10/-; EP36, EF39, EBC33, EL32, 7/6 ea.; 6BE6, 6BA6, 6AT6, 6BW6, R19, 6/6 ea.; SP61, SP41, 9D2, 8D2, 4D1, 3/- ea.; 1A7, 9/-; 6K7M, 5/-; 13,000 Valves in stock; stamp list. Co-ax Cable, 8/20z yds.; C/diodes, 1/6; Loft Aerial, 18/6; W.W. Pots, 3-watt, 5K, 3/9; CR Isolation Trans., 2v, 4v, or 6v types, 25% boost, 6/9; Heater Trans., 200/240v, 6.3 at 1.5A, 5/6; STC Res., RMI 3/6, RM2 3/9, RM3 4/9, RM4 13/6. **WINWOOD**, 12, Carnarvon Rd., Leyton, E.10. (Mail only.)

RADIO UNLIMITED offer new, up-to-the-minute Valve and Component Catalogue. Your every requirement at really keen prices. Special this month 6V6, 6K7, 6K8, EBC33 524, 29/- set; 6SN7, 6SL7, 807, 6V6M, 7/- each; EP36 2/6, EBC33 7/6; SP41 and SP61, 5/6 each. Comprehensive range, Nuts, Bolts, Washers, etc., in fact, all the very essential O's and S's. Write to-day for your bargain list. **RADIO UNLIMITED**, Elm Rd., London, E.17. (KEY 4813.) New branch at 50, Hoe St., Walthamstow, E.17. (LAR 6377.)

"VIEWMASTER" valves, exact to specification, guaranteed new and boxed, set of 12 £5/15/-; "Tele-King," complete set of 17, £8/19/6; "Supervisor," complete set of 20, £10/2/6, all exact to specification. 14v. miniatures: 1S5, DAF91, IR5, DK91, 1T4, DF91, 3S4, DL92, 3V4, DL94, 1S4, 3Q4, N18, DK92, any 4 for 27/6, post 1/- all new and boxed. For individual prices and other types see displayed advert., page 378. **READERS RADIO**, 24, Colberg Place, Stamford Hill, London, N.16. (STA 4587.)

WANTED VALVES, 5Z4, ECL80, EY51, EF80, KT68, 6U4CT, KT61, and all TV. types, also P.M. Speaker Units, 3in., 5in., 6in., 8in., 10in.; prompt cash. **WM. CARVIS LTD.**, 103, North Street, Leeds, 7.

GUARANTEED Valves. All boxed: 1E7 6/6, RK34 2/-, 4D1 3/-, 5Z4 8/6, 6AL5, 6/-, 6C8 8/6, 6P7 6/6, 6P8 7/-, 6C6 6/6, 6SL7 8/-, 12SC7 7/6, 39/44 7/6, 215SG 4/-, 220VSG 7/6, 717A 8/6, 813 70/-, 1629 7/-, 7193 2/-, 7475 7/6, ACP4 15/-, AC/DD 4/-, CV73 4/6, E1148 1/6, EF37 10/6, EL2 12/6, HL23DD 6/6, KTZ41 8/6, PEN25 6/6, PEN26 16/-, PEN1340 6/-, TP2623 17/6, Y63 7/6. See also advt. on page 378. **BENTLEY LTD.**, 38, Chalcot Rd., N.W.1.

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcot Road, N.W.1. (PRImrose 9090.)

VALVES WANTED. EB91, EF80, ECL80, PL81, EY51 and all TV. types, 5Z4G, 6Q7, etc., etc., Brand new only, prompt cash. Send us your offers. **RADIO HAM SHACK LTD.**, 155, Swan Arcade, Bradford, 1.

Prices slashed at Clydesdale

INDICATOR UNIT TYPE 62
With VCR-97 tube and valves. 16-VR65-CV118 (SP61), 2-VR54 (EB34), 2-VR92 (EA50), etc. Dim.: 18in. x 18in. x 11in. Wgt. 42 lbs. In used, good condition. Loose stored.
ASK FOR D/E774 **39/6** each 5/- EXTRA

INDICATOR UNIT TYPE 6
With VCR-97 tube and valves 4-VR91 (EF50), VR-54 (EB34), 3-VR92 (EA50), VR78 (D1), etc. Dim.: 18in. x 8in. x 7in. Wgt. 21 lbs. In original wood case.
ASK FOR D/H524 **45/-** each CARRIAGE 5/- EXTRA

INDICATOR UNIT TYPE 6H
With VCR-97 tube and valves 4-VR91 (EF50), 3-VR54 (EB34). Dim. 18in. x 8in. x 7in. Wgt. 22 lbs. In original wood case.
ASK FOR D/E777 **59/6** each CARRIAGE 5/- EXTRA

POWER UNIT TYPE 285
Ready made for T.V.
A.C. Mains. Input 230 v. 50 cps. Outputs E.H.T. 2 kV, 5 mA., H.T. 250 v. 150 ma. L.T. 633 v. 10 a. and 6.2 v. 5 a. Fully smoothed and rectified with valves VU120, 5U4G, VR91 (EF50), plus con. resistors, etc.
ASK FOR S/H947 **£4.19.6** each PAID

POWER UNIT TYPE 285
ALSO AVAILABLE
As above less valves. Slight internal damage. Transformers O.K.
ASK FOR H/947A **£1.19.6** each 7/6 EXTRA

R.F. UNIT TYPE 24
In original Carton.
With valves 3-VR65 (SP61), etc. Range 20-30 mc/s., switched tuning. Dim.: 9in. x 7in. x 4in. Wgt. 7 lbs.
ASK FOR D/H850 **10/-** each POST 1/6 EXTRA

R.F. UNIT 25
In original Carton.
Range 40-50 mc/s., otherwise as R.F.24.
ASK FOR D/H874 **12/6** each POST 1/6 EXTRA

R.F. UNIT TYPE 27
With Broken Dial Variable Tuning. Range 65-65 mc/s., valves 2/VR135 (EF54), VR137 (EC52), etc. Dim. and Wgt. as R.F.24.
ASK FOR D/E771 **£1.9.6** each POST 1/6 EXTRA

RECEIVER UNIT R3601
Ref.: 10D/6037
With valves 2 VR136 (EF54), VR137 (EC52), 5 VR65 (SP61), 4 VR92 (EA50), VR91 (EF50), 8V6G, VU39A (R3), etc. I.F. 13 mc/s. Dim.: 18in. x 9in. x 8in. Wgt. 36 lbs.
ASK FOR D/H493 **39/6** each CARRIAGE 5/- EXTRA

ION TRAP MAGNET ASSEMBLY
Mfg. Surplus.
Type 1T/6 by Elac for 35 mm. tube neck.
D/H919 **2/6** each POST 3d. EXTRA

REPRINTS FROM "PRACTICAL TELEVISION"
Components Price List Free on request.
The "Beginner's Receiver," modified (the R3170A)... .. 1/6
April to July :
The "Beginner's Timebase" 1/6
Argus Telesvisor, data and blueprint 2/6
CIRCUITS AVAILABLE at 1/3 each.
ASB35/7 or 8, type 62 R1365 R.F. 24, 25, 27 and R3601.

E.H.T. TRANSFORMER
For the P.T.T.V. Receivers (VCR-97)
Pri. tapped 230-250 v. Sec. (1) 3,000 3 mA. tapped at 2,500 v. (2) 4 v. 1 amp. (3) 4 v. 1 amp. tapped at 2 and 2.5 v. Dim.: 4in. x 3in. x 5in. Upright mtg. 4 hole fixing, 4in. x 1in. between centres. Weight 4 lbs.
ASK FOR D/H735 **15/-** each POST 2/6

E.H.T. TRANSFORMER
Pri. tapped 230-250 v. Sec. (1) 3,000 v. tapped at 2,500 v. (2) 4 v. 1 amp. C.T. (3) 4 v. 1 amp. tapped at 2.5 v. Dim.: 4in. x 4in. x 3in. Upright mounting. 4 hole fixing, 3in. x 2in. between centres.
ASK FOR D/H834 **35/-** each POST 2/6

E.H.T. TRANSFORMER
Pri. tapped 230-250 v. Sec. (1) 3,000 v. tapped at 2,500 v. (2) 4 v. 1 amp. C.T. (3) 4 v. 1 amp. tapped at 2.5 v. Dim.: 4in. x 3in. x 3in. Upright mounting. 4 hole fixing, 2in. x 1in. between centres.
ASK FOR D/H834 **19/6** each POST 2/6

E.H.T. TRANSFORMER
Pri. tapped 230-250 v. Sec. (1) 3,000 v. tapped at 2,500 v. (2) 4 v. 1 amp. C.T. (3) 4 v. 1 amp. tapped at 2.5 v. Dim.: 3in. x 3in. x 3in. Upright mounting. 4 hole fixing, 2in. x 2in. between centres.
ASK FOR D/H835 **37/6** each POST 2/6

MAINS TRANSFORMER
For the P.T.T. Argus T.V. Receiver.
Pri. tapped 230-250 v. Sec. (1) 425-0-425 v. 200 mA. (2) 6.3 v. 4 amps. (3) 6.3 v. 4 amps. (4) 5 v. 3 amps. Upright Mtg. Dim.: 5in. x 4in. x 4in. 4 hole fixing, 4in. x 2in. between centres. Wgt. 8 1/2 lbs.
ASK FOR D/H933 **30/-** each POST 2/6
PLEASE NOTE.—Carriage and Postal Charges refer to the U.K. only. Overseas freight, etc., extra.

Order direct from:

CLYDESDALE SUPPLY CO. LTD.


2, BRIDGE ST., GLASGOW, C.S. Phone: SOUTH 2706/9

TELEKIT SUPPLY

MAIL ORDER DEPT.
Chantry Lane Works, Chantry Lane, Bromley, Kent. Phone: Rav. 5845.
Please mention P.W. and enclose 6d. postage

VALVES, NEW & SURPLUS, GUARANTEED			
0Z4	4/-	6BE6	6/6
IL4	5/6	6BR7	8/6
ILN5 (soiled)	6BS7	7/-	(soiled) 5/-
IS5	5/-	6BW6	6/6
IT4	6/-	6CH6	6/5
IT5	6/-	6CJ5	5/6
3V4	6/6	6V5	7/6
5Y63	8/-	6X4	6/6
6A8	8/-	6X5	7/6
6AL5	7/6	7D5	6/-
6AM6	6/-	7D6	6/-
6AT6	7/6	7D7	6/-
6B8	6/-	7H7	6/-
6BA6	6/6	9D2	5/6
		9D6	6/-
		11D3	6/-
		12A6	12/9
		12BE6	7/-
		6SH7 (soiled)	5/6
		15D2	4/-
		19AQ5	10/-
		AL60	4/6
		EF50	5/-
		VR21	3/-
		W77	6/6
		1B24	50/-

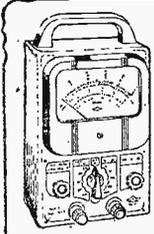BECKENHAM, KENT
THE SHOP FOR THE CONSTRUCTOR
NOW OPEN AT 104, HIGH STREET.
BECKENHAM 3720



PULLIN
SERIES 100
TEST METER
AC/DC 10,000 A/V
21 RANGES
100µA to 1000V
COMPLETE IN DIE-CAST CASE WITH TEST LEADS
CLIPS AND PRODS FULLY GUARANTEED

SENT POST FREE FOR **£2.10s.**
DEPOSIT AND TEN FURTHER MONTHLY PAYMENTS OF **£1.** CASH PRICE 11/6s

Frith
RADIOCRAFT Ltd
69-71 CHURCH GATE LEICESTER

FIRST-CLASS TELEVISION and RADIO COURSES . . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification or learn Servicing and Theory. Let us show you how!

—FREE GUIDE—

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M. Brit. I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ., London, B.Sc. (Eng.), A.M. I.P.E., A.M.I. Mech.E., Draughtsmanship** (all branches), etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES.

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

HIGH GRADE TRANSFORMERS

FOR ALL PURPOSES
SINGLY OR IN QUANTITIES
TO YOUR SPECIFICATION
VARNISH IMPREGNATED
BAKED WINDINGS
WITH OR WITHOUT TAG PANELS
GOOD DELIVERIES
Our rewind dept. will handle your repairs promptly and efficiently.
S.A.E. with enquiries please.

P. HOWORTH

(Dept. P.T.)
51 POLLARD LANE - BRADFORD
Tel: 37030

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,
IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:
36, ROSEBURY AVE., LONDON, E.C.1.
Branches at Liverpool, Manchester, Birmingham, Leeds.
"No Quantity too Small!"

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

R1355 AND R.F. UNIT FOR BAND III

SIR,—With Commercial Television always coming nearer, many of us who are using R1355 and the associated R.F. units for our respective Band I transmitters, would like to be given a circuit for conversion of an R.F. unit to Band III, using the present I.F.s of the R1355. It would mean completely breaking down an R.F. unit and rebuilding it for Band III, but it wouldn't require more than a few seconds to change a Band I R.F. unit for a Band III unit when one desired to switch over to another programme.—**J. RODGER (Reverend) (Oldmeldrum).**

BAND I CONVERTER RESULTS

SIR,—While at Robin Hood's Bay, which is on the north-east coast of Yorkshire, last week, I built the Band I Converter Unit as in the October issue of PRACTICAL TELEVISION.

I found that by using Aladdin $\frac{3}{4}$ in. coil formers with dust cores for the two oscillator coils, I was able to receive very good vision and sound from Holme Moss on a H.M.V. 1807 London fixed tuned receiver, using a cross type aerial (forward gain 6dB).

I should point out that Robin Hood's Bay is 85 miles from Holme Moss. Also, if trouble is found in getting the two 18pF condensers, 20 pF will work just as well.

I hope you will publish the above, as I am sure there are many who have a London fixed tuned receiver wishing to use them in the coverage of Holme Moss transmitter.—**GORDON R. BUSSEY (A.M.I.E.T.) (Coulsdon).**

TUBE DATA—ACR10 AND VCR139A

SIR,—It appears that for some time the cathode-ray tube ACR10 has been sold by many firms as a VCR139A.

According to my reference books these tubes are far from direct equivalents, the only similarity being the base connections, and I am sure that this has misled many experimenters.

The following are the figures quoted in one of my reference manuals:

		ACR10					
Diam.	1h	Vh	Va ₁	Va ₂	Vg ₁	Sensitivity	
2.5in.	1.1	4	800	120	12	.217 mm/v	
						(Both axes)	
Va ₃ = 800							

		VCR139A										
Diam.	1h	Vh	Va ₂	Va ₃	Vg ₁	Sensitivity						
2.75in.	1.1	4	100	450	10	.11 mm/v						
						(Both axes)						
Bases:	1	2	3	4	5	6	7	8	9	10	11	12
	k	g	h	h	a ²	—	y"	x"	a ¹ × 3	x'	y'	—

—**H. D. FORD (Fleet).**

SERVICING ARTICLES

SIR,—I read Mr. Waldron's letter in the November issue with great interest. It is a good idea to gather information from many quarters to form the basis of an article on servicing.

The sliders on the 1807 chassis are troublesome, but as the defect, or rather the source of it, is nearly always evident (I said nearly) upon operating these controls I did not deem it necessary to include this fault in the article; however, for readers' information they are 25K sliders made by either Colvern or E.M.I., the two makes being of different size. Take a sample when buying! The fact that the valve noise limiter is often replaced by a metal rectifier was mentioned in the caption beneath the diagram on this subject. It is rare that an EA50 is fitted and the metal type will nearly always be encountered.

I expected plenty of comment in the correspondence column regarding why this fault or that was not included, but the original aim was to help readers to service their own sets; and whether all available information is included or not, the fact is that the ball has been set rolling, and I know that the great interest of readers on this subject will ensure that the maximum information will be forthcoming whether from my pen or not. Mr. Editor, I have a feeling that the subject will not end here.—**L. LAWRY-JOHNS (Gravesend).**

TUNABLE TV

SIR,—Re your articles on a communication receiver, Ediswan have just introduced a 12-band turret tuner for TV, with replaceable coil units.

Why not a similar job for 12-band radio, —2RF + FC? Surely this would be the "dream come true" for amateurs!

Suggestion (1) Cathode sensitivity control (manual); (2) screen A.G.C.; (3) variable selectivity; (4) B.F.D.; (5) initial valves of latest type for U.S.W.

What do other readers think?—**E. T. BATLMAN (Southampton).**

"CANNED SOUND"

SIR,—It is with great misgiving that I learned recently that many commercial programmes will be on film. "Canned vision" means "canned sound" and one has only to see and hear the "Amos 'n Andy" editions to realise how badly recorded sound tracks come over to the viewer. Only "live" sound can be easily received on the ear, and the sponsors will find this a sore point when they are trying to give the public the best in entertainment in order to sell their goods. Film sound tracks can only be amplified over a cinema sound system if good reproduction is desired.—**B. COOK (Charlton).**


QUERIES COUPON

This coupon is available until Jan. 21st, 1955, and must accompany all Queries.

PRACTICAL TELEVISION, JAN., 1955.

ADCOLA

REGISTERED
(Regd. Trade Mark)

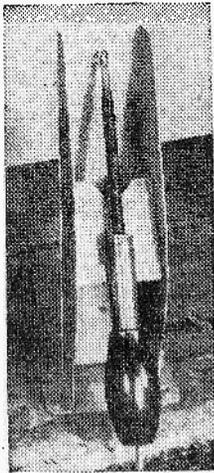

Shields as illustrated
10/6 extra.

SOLDERING INSTRUMENTS

FOR

SUCCESSFUL HOME CONSTRUCTION AND ALL SOUND EQUIPMENT SOLDER JOINTING

"STANDARD MODEL," as ILLUSTRATED, 25/6

Any volt range supplied. 6/7 to 230/250.

3/16" dia. bit Standard Model

Equally suited to daily or intermittent use

Made in England
Registered Design
(British, U.S.A., Foreign Patents)
Export Enquiries Invited

WRITE DIRECT TO

ADCOLA PRODUCTS LTD.

Sales, Offices & Works: CRANMER COURT, CLAPHAM HIGH ST., LONDON, S.W.4. *MACaulay 4272*

PRACTICAL TV AERIAL MANUAL FOR BANDS I AND III

R. Laidlaw.

72 pages. 72 diagrams 4/6

This book describes nearly every type of TV aerial of practical use, with full instructions for construction and erection. The theory of transmission and reception of electromagnetic waves is given in a clear and almost non-mathematical manner. There are details of aerials designed to give the best possible results in any particular location. Deals with the latest developments in aerials for Band III and the construction of tried and tested types.

UNIT CONSTRUCTED TV RECEIVERS

E. N. Bradley.

92 pages. 50 diagrams and half-tones. 6s.

Complete details are given in this book for building units which make up into local or long-range receivers to suit all areas, using any tube size from 3in. to 15in. Operating and fault-finding data are included.

TRANSISTORS AND CRYSTAL DIODES

B. R. Bettridge.

(Osram Valve and Electronics Dept. of the General Electric Co., Ltd.)

72 pages. 53 diagrams and half-tones. 5s.

An explanation of what these devices are and how to use them. There are many practical and fully tested circuits.

NORMAN PRICE (PUBLISHERS) LTD.,
283, City Road, London, E.C.1.

TALLON CABINETS

for television, radio and grams, polished; ready for assembly in packed flat kits or factory assembled.

TELE-KING cabinets with space for radio or tape recorder with or without doors, for 12", 15", 16" or 17".

VIEW MASTER cabinets; console, or table, 12 and 17in.

P.W. 3-SPEED AUTO-GRAM CABINET.
LYNX CABINET.
ARGUS CABINET.

RADIOGRAM, RADIO AND SPECIAL CABINETS TO CUSTOMERS' DESIGNS. SUPER CABINETS FOR SOUNDMASTER. MINI-FOUR AND CRYSTAL DIODE cases at 14/6 each, including postage:

Consult your local dealer or write to:
(DEPT. P.T.I.)

JAMES TALLON & SONS LTD.

MANOR WORKS, MANOR ROAD
RUGBY Telephone: RUGBY 2070

WE SPECIALISE ONLY IN

RADIO COMPONENTS—

LET US QUOTE YOU BY RETURN FOR ANY RADIO VALVES OR PARTS YOU REQUIRE

HIRE PURCHASE TERMS ON KITS, INSTRUMENTS, ETC.

Osram "912" and Mullard "510" Amplifier Parts in Stock.


NEW CATALOGUE WITH H.P. TERMS 6d. QUOTES S.A.E.

RADIO SERVICING COMPANY

82 SOUTH EALING ROAD
LONDON W.5 EAL. 5737
NEXT DOOR SOUTH EALING TUBE STATION (TURN LEFT)

30/-

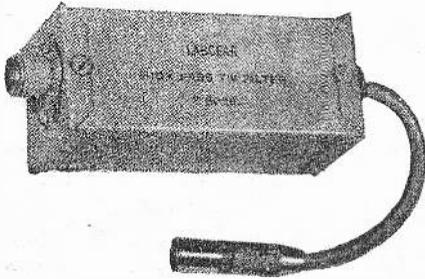FOR FREEDOM FROM TV SWAMPING INTERFERENCE FROM NEARBY TRANSMITTERS



If the interfering station operates at 30 Mc/s. or lower, use model E.5028. If it operates at 70 Mc/s. or higher, use model E.5031. Relieves interference from the following classes of stations:—Broadcast, Press, Radar, Beacon, Amateur, Aircraft, Taxis, Ambulance, Fire, Shipping, Military, Police, etc.

AS SUPPLIED TO THE G.P.O.
SEND S.A.E. FOR FREE LEAFLET

Labgear (Cambridge) Ltd.
WILLOW PLACE, CAMBRIDGE Tel. 2494—2 lines

Finest Soldering! Always specify **ERSIN MULTICORE** to be precise

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SIZE 1 CARTON
4 specifications for radio enthusiasts.

5/-



HANDYMAN'S CARTON
Sufficient for 200 average joints. **6d.**

TAPE SOLDER

MELTS WITH A MATCH!
Real tinlead solder containing cores of Ersin Flux. Needs no sold. ring iron or extra flux.

1/- PER CARD



BIB WIRE STRIPPER AND CUTTER
The 3 in 1 tool. For stripping insulation without nicking wire, cutting without leaving rough edges and splitting extruded flex. **3/6 EACH**

MANUFACTURERS ARE INVITED TO WRITE FOR DETAILS OF BULK PACKS AT BULK PRICES

MULTICORE SOLDERS LTD.

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS (BOXMOOR 3636)

Forrest

Combined ISOLATING BOOSTER Transformers

Enable your old CRT to have many more months of useful life. Acknowledged by ALL the leading service organisations and Maintenance Companies to be by far the most effective Transformer for this purpose on the market. PRICE 18/9.

LINE E.H.T. REWINDING SERVICE

The original repair firm for all types of winding. Wave winding, etc. New Transformers to your requirements. 2-3 days delivery.

ALL PW AND PT DESIGNS

Established over 30 years.

H. W. FORREST,

349, HASLUCKS GREEN ROAD, SHIRLEY, BIRMINGHAM.

MONEY BACK GUARANTEE **DUKE ECo** CWO OR COD
621 ROMFORD RD. LONDON, E.12. Tel: GRA 6677

£5. TV Tubes, guaranteed for 3 months. 12 inch.

Mazda CRM21—A, or B.—A few other types available. As we have been selling for the last three years. Picture shown to callers. INSU-Carr. and Packing 15/6 extra.

TEST TUBES £1.—Most makes and types, all work Perfectly, but have Cathode to Heater shorts or slight burn, ideal for testing or spares. Insured Carriage 15/6.

AMPLIFIERS, 77/6. Push-pull, 4 valve and rec. Full tone range, variable. Output 3-7-15 ohms matching. A.C. or Universal. Post 2/6.


AMPLIFIERS, 57/6. 4 watts, 3 valves. Switched tone range 2-5 ohms output. Good quality, A.C. or A.C./D.C. Post 2/6.

AMPLIFIERS, 7/6. X, W.D. Less valve. Complete with FREE Drawings. Post 1/6.

LADIES ONLY.—Treat the lady and yourself to a heated blanket for the home. 37/6 brings a complete heater kit that a lady can fit by herself unaided—with free drawings.

FIRESIDE "RIPPINGHILLS" HEATER, 77/6. For the home, works or office. Although these are used ex W.D. they have all been overhauled and work perfectly (paraffin). Carriage 2/6.

H.T. BATTERY BARGAINS, 1/9.—All 6ry L.T. 1.5 and H.T. minimum 40 volt tested. 3/9 : 60 volt +1.5 L.T. All-Dry, 3/9 ; 671 volt H.T. Personal Portable type, 3/9 ; 60 volt H.T., 5/9 ; 671 volt +64.5 volt +41 volt, size 9in. x 4 1/2in. square, 3/9. Inert cells, G.E.C. 3 volt twins, 1/4 ; 41 volt New Ever Ready L.T. or Bell, list price, 3/6. P. & P. 1/9 on H.T., 9d. on L.T. and cells. Plugs for Batts., 6d. each. Send 21d. stamp for Catalogue.

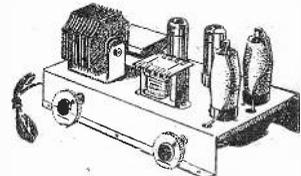

NEW!

**EXPERIMENTAL KITS
in Radio, T.V. etc**

**LEARN THE
PRACTICAL
WAY**


Specially prepared sets of radio parts from which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at a Very Moderate Cost.

EASY TERMS FROM 15/- A MONTH
With these outfits, which you receive upon enrolment, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to complete Radio and Television Receiver Testing and Servicing.



TELEVISION — With this equipment you are instructed in the design, construction, servicing and testing of a modern high quality Television Receiver.

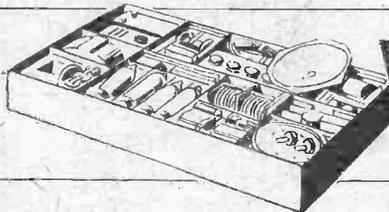**ALL EQUIPMENT SUPPLIED
IMMEDIATELY AND REMAINS
YOUR PROPERTY**




BEGINNER'S RADIO OUTFITS

— For carrying out basic practical work in Radio and Electronics, from first principles and leading to the design and building of simple Receivers.

ADVANCED RADIO OUTFITS

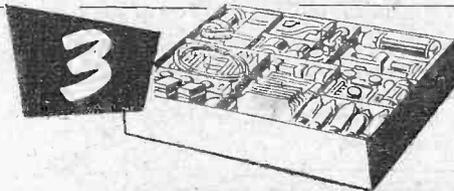— With this equipment, you are instructed in the design, construction, testing and servicing of a complete modern T.R.F. and Superhet Radio Receiver.



OTHER COURSES WITH OUTFITS INCLUDE:

**MECHANICS • ELECTRICITY
CHEMISTRY • PHOTOGRAPHY
CARPENTRY**

**ALSO DRAUGHTSMANSHIP • COMMERCIAL ART
AMATEUR S.W. RADIO • LANGUAGES • ETC.**

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses: I am interested in Television
Radio: Beginners , Advanced
Other subjects (Please indicate item(s) required)
To: E.M.I. INSTITUTES, Dept. 138x, Grove Park Road, London, W.4.

NAME

ADDRESS



E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation