

Whitney
A BAND III CONVERTER

PRACTICAL TELEVISION

AND TELEVISION TIMES

1/4

EDITOR
F. J. CAMM

A NEWNES PUBLICATION

Vol. 6 No. 63

AUGUST, 1955




**TIMEBASE
TESTING**
with the

'SCOPE'


FEATURED IN THIS ISSUE

Receiving the ITA
Picture Tube Developments
Underneath the Dipole
Your Problems Solved

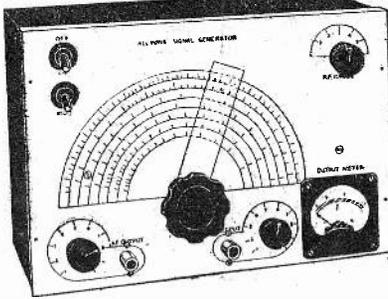Amateur Chassis Construction
Servicing the Pye V4, V7, VT4
and VT7
A TV Engineer's Notebook



T.V. CONVERTER
for the new commercial stations, complete with 2 valves. Frequency can be set to any channel within the 186-196 Mc/s band. I.F. will work into any existing T.V. receiver between 42-68 Mc/s. Input arranged for 80 ohm feeder. EF80 as RF amplifier, ECC81 as local oscillator and mixer. The gain of the first stage, RF amplifier 10dB. Required power supply of 200 D.C. at 25mA, 6.3v A.C. at 0.6 amp. Input filter ensuring freedom from unwanted signals. Simple adjustments only, no instruments required for trimming. Will work into any T.R.F. or superbet. Size 4 1/2 x 2 1/2 x 2 1/2 in. P. & P. 2/6, £2.19.6.

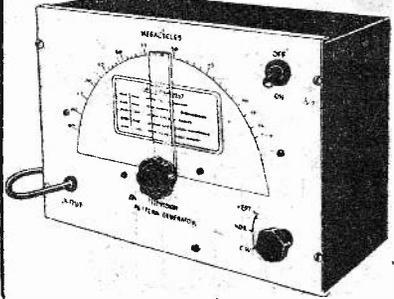


BOTH GENERATORS GUARANTEED FOR 12 MONTHS

COMPLETELY BUILT SIGNAL GENERATOR

Coverage 120 Kc/s-320 Kc/s, 300 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8.5 Mc/s-25 Mc/s, 17 Mc/s-50 Mc/s, 25.5 Mc/s-75 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated, R.F. output continuously variable 100 milli volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel. Accuracy plus or minus 2%, £4/19/6, or 34/- deposit and 3 monthly payments 25/- P. & P. 4/- extra.

PERMEABILITY TUNED T.V. UNIT

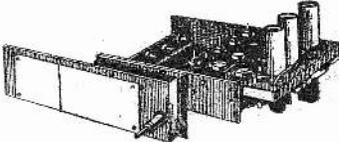

Input 300 ohm balanced line, coverage 54 Mc/s-89 Mc/s and 174 Mc/s-217 Mc/s. Vision I.F. -45 Mc/s, sound 40.5 Mc/s. Uses 6AK5 RF valve, 6AK5 as mixer, and 6C4 oscillator. Provision for auto-gain control. Dimensions 9in. wide, 6 1/2 in. deep, 4 1/2 in. high, 9in. blank-scale. Width including scale-overlap 1 1/2 in. Four stages permeability tuned. Complete with 3 valves, P. & P. 3/-, £2.19.6. Used Mazda C.T.M. 123 Cathode heater, short aluminiumised. Complete with rubber mask. Elac P.M. focus unit, scan coils, low line, low frame and frame O/P trans., £5.10.0, P. & P. 7/6. **USED 9in. TUBE 22/14C** with ion burn, 17/6. Post paid. Mazda CRM 92A, used with heater cathode short, guaranteed for 3 months. P. & P. 7/6, £2.17.6. Used Mullard 9in. tube 22/16 & 17 ion burn. 25/- post paid, 40 watt Fluorescent kit A.C. mains 230/240. Comprising choke, power-factor condenser, 2 tube holders, starter, and starter-holder. P. & P. 3/-, 17/6. 20 watt A.C. or D.C. 230/250v Fluorescent kit, comprising trough in white stove enamel, 2 tube holders, starter, starter-holder and barretter. P. & P. 1/6, 12/6.

Three speed automatic changer by a very famous manufacturer, current model. Will take 7in., 10in. or 12in. records mixed. Turnover crystal head.
VERY LIMITED QUANTITY.
A.C. Mains 230/250. £7.19.6. P. & P. 4/6.

Line and E.H.T. Transformer. 9Kv. Ferrocort core. EY51 heater winding, complete with scan coils and frame output transformer and line and width control. £2.5.0. P. & P. 3/-.
As above but complete with line and frame blocking transformers, 5 Henry 250 mA. choke, 100 mid. and 150 mid. 350 wkg., 380 mA. A.C. ripple. £2.19.6. P. & P. 3/-.
Standard wave-change Switches. 4-pole 3-way, 1/9; 5-pole 3-way, 1/9; 3-pole 3-way, 1/9; 9-pole 3-way, 3/6; Miniature type, long spindle 3-pole 4-way, 4-pole 3-way and 4-pole 2-way, 2/6 each. 2-pole 11-way twin wafers, 5/-; 1-pole 12-way single wafers, 5/- P. & P. 3/6.
Scaler Cell RM4B 300 mA. 250 v. 15/-.
USED metal rectifier, 250 v. 150 mA. 6.6.
R. and A.T.V. energised 6in. Speaker with O/P Trans., field coil 175 ohms. Requires minimum 150 mA. to energise maximum current 250 mA. P. & P. 2/6.
R. and A.M.E. 6in. with O/P Trans., 440 ohms field, 10/6 plus 2/6 P. & P.
Combined 12in. Mask and Escutcheon in lightly tinted perspex. New aspect, edged in brown. Fits on front of cabinet. 12/6. As above for 15in. tube, 17/6.

R. & T.V. COMPONENTS (ACTON) LTD.
23 HIGH STREET, ACTON, LONDON, W.3
(UXBRIDGE ROAD) Telephone: ACORn 5901

PATTERN GENERATOR

40-70 Mc/s direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and section circuits and vision channel band width. Silver plated coils, black crackle finished case, 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 230/250 volts. This instrument will align any T.V. receiver, accuracy plus or minus 1%. Cash price £3.19.6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/- extra.

Line or Frame Oscillator Blocking Transformers, 4/6 each. Smoothing Choke, 250 mA., 5 Henry, 8/6; 250 mA., 10 Henry, 10/6; Wide Angle P.M. Focus Unit, Vernier adj. state tube, 15/-; Ion Taps for Mullard or English Electric tubes, 5/-; Post paid. T.V. Coils, moulded former, iron core, wound for rewinding purposes only. Ali-can 1 1/2 in. x 1/2 in., 1/- each; 2 iron-cores Ali-can, 2 1/2 in. x 1/2 in., 1/6 each.
Dubilier .001 10kV. working, 3/6.
Primary, 200-250 v. P. & P. 2/-.
350-0-350, 100 mA., 6 v. 3 amp., 5 v. 2 amp., 22/6.
Drop thro' 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6.
Drop thro' 250-0-250 v. 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.
280-0-280, drop through, 80 mA., 6 v. 3 amp., 5 v. 2 amp., 14/6.
250-0-250 80 mA., 6 v. 4 amp., 14/-.
Drop thro' 270-0-270 80 mA., 6 v. 3 amp., 4 v. 1.5 amp., 13/6.
Drop thro' 270-0-270 80 mA., 6 v. 3 amp., 11/6.
250 v. 350 mA., 6.3 v. 4 a., twice 2 v. 2 a., 10/6.
Semi-shrouded drop-through 380-0-380 100 mA., 6.3 v. 3 amp., 5 v. 2 amp., 25/-.

Auto-trans. Input 200/250, H.T. 500 v., 250 mA., 6 v. 4 a., twice 2 v. 2 a., 19/6.
250-0-250, 80 mA., 6.3 v. 1.5 a., 0.5-6.3 v. 1.5 a., 10/6.
Auto Trans. Input 200/250, H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 1 1/2 amp., 5 v. 3 amp., 25/- P. & P. 3/-.
Heater Transformer, Pri 230/250 v. 6 v. 1.4 amp., 6/-; 2v. 2 1/2 amp./5/-
Input 210, 220, 230, 240. Sec. 350-0-350 100 mA., with separate heater transformer. Pri. 210, 220, 230, 240. Sec. 6.3 v. 2 amp., 6.3 v. 3 amp., 4 v. 6 amp., and 5 v. 2 amp. 30/- P. & P. 5/-.
350-0-350 75 mA., 6.3 v. 3 a., 4 v. 6.3 v. 1.5 amp., 13/6.
500-0-500 125 mA., 4 v. C.T. 4 a., 4 v. C.T. 1 a., 4 v. C.T. 2.5 a., 27/6.
500-0-500 250 mA., 4 v. C.T. 5 a., 4 v. C.T. 5 a., 4 v. C.T. 4 a., 39/6.
Chassis mounting or drop thro'. Pri. 110/250 v. Sec. 350-0-350 250 mA., 6.3 v. 7 amp., 6.3 v. 0.5 amp., 5 v. C.T. 0.5 amp., 4 v. 4 amp., 32/6. P. & P. 3/6.

R.F. E.H.T. Oscillator Coil. 6-9 Kv. with EY61 rectifier winding, and circuit diagram, 15/-.
As above, but complete with 6V6, EY51 and associated resistors and condensers. Circuit diagram, 37/6.
As above, but complete with line O.P. transformer, scan coils and frame O.P. transformer, £2.19.6. P. & P. 3/-.
Polishing Attachment for electric drills, 1/6. Spindle, chromium plated 5in. brush, 3 polishing cloths and one sheepskin mop mounted on a 3in. rubber cup. Post & pkg. 1/6, 12/6. Spare sheepskin mops, 2/6 each.

Used AC mains 230/250 volts, 4 valve plus metal rectifier, medium wave superhet in polished walnut cabinet, size 14 x 9 x 7 1/2 in., complete with valves 6X3, 6X7, 6C7 and 6T6. 6in. PM speaker. Fully guaranteed. P. & P. 7/6, £3.15.0.

Valve Holders, moulded octal Mazda and octal, 74, each.	8 mfd., 500v. wkg., wire ends 2/6
Faxolin, local Mazda and octal, 4d. each. Moulded BTG, B8A and B9A, 7d. each.	8 mfd., 350 v. wkg., tag ends 1/6
BTG moulded with screening cap, 1/6 each.	50 mfd., 25 v. wkg., wire ends 1/6
32 mfd., 350 wkg. ... 2/-	100 mfd., 450 v. wkg., 280 mA., A.C. ripple ... 3/11
16 x 24, 350 wkg. ... 4/-	150 mfd., 350 v. wkg., 280 mA., A.C. ripple ... 4/6
4 mfd., 200 wkg. ... 1/3	100 + 200 mfd., 275 wkg. ... 7/6
40 mfd., 450 wkg. ... 3/6	16 + 16 mfd., 350 wkg. ... 3/3
16 x 8 mfd., 500 wkg. ... 4/6	50 mfd., 180 wkg. ... 1/9
16 x 16 mfd., 450 wkg. ... 4/6	65 mfd., 220 wkg. ... 1/6
16 x 16 mfd., 450 wkg. ... 5/9	8 mfd., 150 wkg. ... 1/6
32 x 32 mfd., 350 wkg. ... 4/-	60 + 100 mfd., 280 wkg. ... 7/6
25 mfd., 25 wkg. ... 11d	50 mfd., 12 wkg. ... 11d
250 mfd., 12 v. wkg. ... 1/-	50 mfd., 50 wkg. ... 1/9
16 mfd., 500 wkg. ... 3/3	Miniature wire ends moulded, 100 pf., 500 pf., and .001 ea., ... 7d.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.



Get your new

BRIMAR MANUAL

The
LATEST EDITION
has
272 Pages
of **VALVE and**
TELETUBE DATA
CIRCUITRY
& SPECIAL
COMPONENTS

- SUMMARY OF CONTENTS**
- Valve ratings and base connection symbols.
 - Classified lists of nearly 300 valves, teletubes and selenium rectifiers.
 - Germanium diode section including ratings in various circuits.
 - Brimaristors section.
 - Radio engineering formulae and NEW circuits.
 - Brimarize section. Valves and teletubes.
 - Up-to-date substitution list of American types.
 - Equivalents and C.V. numbers.
 - Details of Trustworthy types.
 - Valuable information on Transistors.


still only **5/-**

Send 5/- for your copy to: Publicity Dept.

Standard Telephones and Cables Limited **FOOTSCRAY SIDCUP KENT Footscray 3333**

LASKY'S RADIO

**12
CHANNEL
TV.
TUNER**

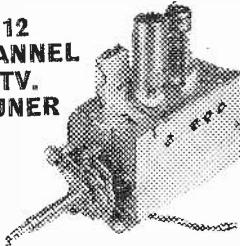

Famous make. Covers Bands I and III. Complete with valves EF90 and ECC81. Ceramic valveholders, finest quality components, precision made. Switch and fine tuning. I.F. output 20-25 Mc/s. Freq. coverage 50-87.75 Mc/s and 175.75-215.75 Mc/s. Supplied with full details and circuit diagram.


LASKY'S PRICE 89/6
Post 3/6.

Knobs, 2/9 extra.

TELETRON BAND III CONVERTER COIL SET.—For use with T.R.F. and superhet Band I receivers. Uses two Z119. Circuit, practical wiring diagram, alignments, full details with each set. 15/-. Post 1/6.


THE HANDSOME "ROTHESAY" CABINET

Absolutely rigid construction with finest laminated woods, veneered in walnut, polished light, medium or dark shade. Fitted gold anodised speaker grille. The C.R.T. aperture frame is detachable, supplied to order to suit any size tube.
Outside dim. 34 1/2 in. high, 21 in. wide, 21 in. deep. Inside 18 1/2 in. wide, 19 1/2 in. deep. Size of top 22 in. x 21 in.
LASKY'S PRICE £9. 19. 6
Carriage 15/- extra. With full length doors, £14.9.5.
Available on H.P. terms.

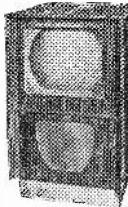

"THE UNVERTER"—FOR BAND III CONVERSION OF BAND I RECEIVERS

Send for this new book just published, giving full details of a new Band III Converter for any TV receiver, home constructed or factory made. All components and valves in stock, prices on request. Also available as a complete unit. Uses two 6AM6, one 12AT7, one 6X4. Contains its own power supplies. **THE BOOK**, containing full circuit diagram, wiring instructions and component lists, 3/6 post free.

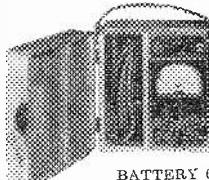

MULTI-TEST METERS

1,000 ohms per volt.
Basic movement 400 micro-amp. 3 in. AC/DC
0-5,000 v. 0-1 amp. 11 switched ranges: 100,000-ohms and 1 meg., also decibel range. In wood carrying case (6 x 6 1/4 x 4 in. closed).
95/-
Post, 3/6.

BATTERY 6d. TEST LEADS, 3/6.

LASKY'S (HARROW RD.) LTD.,

370, HARROW ROAD, PADDINGTON, W.9.
Telephone: GUNNINGHAM 1970-7244.
42, BOTTENHAM COURT ROAD, W.1.
Telephone: MUSEUM 2695.

Open all day Saturday. Half Day: Thursday. ALL MAIL ORDERS TO HARROW ROAD, PLEASE.

MAKERS' SURPLUS COMPONENT BARGAINS

WIDE ANGLE 38 mm.

- Line E.H.T. trans., ferro-cube core, 9-16 kv ... 25/-
- Scanning Coils, low imp. line and frame ... 25/-
- Frame Output Transformer Scanning Coils low imp. line and frame ... 10/6
- Frame or line blocking oscillator transformer ... 4/6
- Focus Magnets Ferro-cube ... 25/-
- P.M. Focus Magnets, Iron Cored ... 19/6
- Duomag Focalisers ... 29/6
- 300 m/a. Smoothing chokes ... 15/-
- Electromagnetic focus coil, with combined scan coils ... 25/-

STANDARD 35 mm.

- Line Output Transformers. No E.H.T. ... 12/6
- Line Output Transformers 6-9 kv. E.H.T. and 6.3v. winding. Ferro-cube ... 19/6
- Scanning coils. Low imp. line and frame ... 12/6
- 14/6
- Frame or line blocking oscillator transformer ... 4/6
- Frame output transformer ... 7/6
- Focus Magnets: Without Vernier ... 12/6
- With Vernier ... 17/6
- Focus Coils. Electro-magnetic ... 12/6
- 200 m/a. Smoothing chokes ... 10/6

SPECIAL PURCHASE OF 16in. C.R. TUBES. Famous make offered at nearly Half-Price. Metal cone, 3 amp. heater, c.h.t. required 10-14 Kv. Limited quantity only.
LASKY'S PRICE £12.19.6
Car. & Ins. 2/6 ex.


Your set deserves a Mullard

LONG-LIFE TV TUBE

If you are building a television receiver, leave nothing to chance: choose a Mullard Tube. Mullard Television Tubes owe their high reputation for performance, reliability and LONG LIFE to the unrivalled facilities for research possessed by Mullard and to the complete control of manufacture from the production of raw materials to the finished product. For practical evidence of performance and reliability, ask the people who use them.

MULLARD LONG LIFE TUBES FOR HOME CONSTRUCTORS

MW22-16	9 inch circular screen.
MW31-74	12 inch circular grey-glass screen.
MW36-24	14 inch rectangular grey-glass screen.
MW41-1	16 inch circular screen. Metal cone.
MW43-64	17 inch rectangular grey-glass screen.

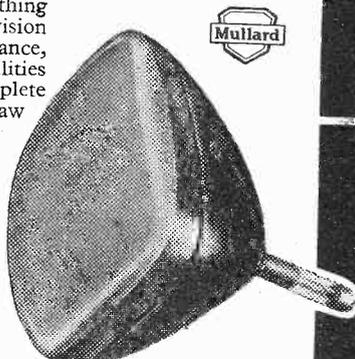

MW43-64



MW22-16



MW31-74



MW36-24



MW41-1

MVM290

MULLARD LTD · CENTURY HOUSE · SHAFTESBURY AVENUE · LONDON W.C.2

PREMIER RADIO COMPANY


OPEN TILL
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone:
AMBASSADOR 4033
PADDINGTON 3271

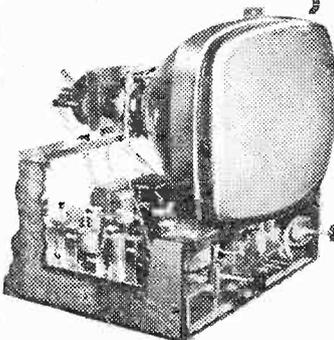★ **Band Three** (Commercial)
For the Home Constructor



Instruction Book 3/6. Post Free. Includes details of both designs.



THE NEW PREMIER TELEVISOR

13 CHANNEL DESIGN


SUITABLE FOR USE WITH ANY POPULAR WIDE ANGLE TUBE

DESIGN 1. Includes a Multi-Channel Tuner (Channels 1-13) continuously variable 40 — 100 Mc/s and 170-225 Mc/s. The Tuner is supplied wired and tested and is complete with Valves, all connecting leads and fixing brackets.
THIS DESIGN MAY BE BUILT FOR **£34. 9. 7** (plus cost of C.R.T.).


DESIGN 2. Channels 1-5, tunable from 40-68 Mc/s.
THIS DESIGN MAY BE BUILT FOR **£30** (plus cost of C.R.T.).

- ★ Constructors who have built Design 2 (5 Channels) may convert their Receivers to Design 1 for £6; this price includes Multi-Channel Tuner, New Vision Input Coil and full instructions.
- ★ All Coils supplied for these two Superhet Receivers are PRE-TUNED, ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.
- ★ Duomag permanent magnet focusing with simple picture centring adjustment.
- ★ Exceptionally good picture "hold" and interlace. ★Noise suppression on both Sound and Vision.

The Televisor may be constructed in 5 easy stages: (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced.

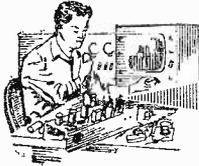

Practical Television

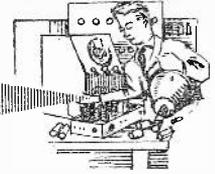

& TELEVISION TIMES

Editor : F. J. CAMM

Editorial and Advertisement Offices : " Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone : Temple Bar 4363. Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 6 No. 63

EVERY MONTH

AUGUST, 1955

TelevIEWS

THE EVE OF I.T.A.

SOON viewers will have a choice between the BBC and the ITA programmes. The advent of the rival programme has had the beneficial effect of stimulating the BBC, who are busy not only in their efforts to improve their programmes so that they compare favourably with their rival, but also in signing up on contract the best personnel, both on the technical and the entertaining side. The new service has provided the best possible answer to those who feel that the BBC monopoly was a good thing. The moves they are at present making would not have taken place and the old attitude of take it or leave it as far as the programmes are concerned would have remained.

Commercial interests will be able undoubtedly to afford higher fees for artists and technicians and unquestionably will have to pay higher fees if they are to attract good personnel away from the BBC. It will remain to be seen whether an artist who serves one master will also be allowed to serve both. Will the BBC taboo those artists who work for commercial television? There is not an excess of first-class entertaining material, indeed, insufficient to provide a good daily programme seven days a week. That is why so many of the programmes are padded out with silly parlour games and other matter of desultory and purely transitory interest. The BBC has excelled itself on the technical side, but we suggest that there is immediate need for a complete overhaul of its methods of programme production and selection of programme material and particularly of plays. In making this criticism we acknowledge that the BBC plans have been tied for lack of capital, but, at the same time, had they husbanded their resources and kept a wiser guard over expenditure, they would have had sufficient to produce first-class programmes all the time. There are far too many water-tight compartments, there is considerable over-staffing and overlapping. A select committee is needed headed by efficiency experts to examine the BBC methods both on radio and on television. There is far too much free-lance work about the BBC and those

responsible for picking programmes are not subject to sufficient surveillance.

As far as commercial television is concerned, it now enters its first testing period. Those responsible for it know that unless the material is first class advertisers will not buy programme time at its present costly rate. It is beyond all doubt, however, that viewers will benefit by the new service, even if they do not wish to view the ITA programmes.

INTERFERENCE

ALTHOUGH the new Act relating to the fitting of suppressors is a move in the right direction it does not go far enough. Interference caused by aircraft, power stations and electric vehicles is still a major cause of TV interference and it should be the concern of the Postmaster-General to seek early powers to put a stop to it. The present Act strains at a gnat and swallows a camel. Let the P.M.G. deal with major causes of interference and deal with the smaller fry later.

Of course, the problems of suppressing power stations, electric trains and aeroplanes is an involved and difficult problem, and it may be that it will only be solved by set manufacturers. It is, however, a problem which is the cause of widespread complaint and it should be tackled now.


BUILD-IT-YOURSELF

IN this do-it-yourself age more and more people are building TV receivers rather than purchasing the commercial product. In this respect they are finding our " Practical Television Circuits," which costs 15s., or 15s. 6d. by post, of great service. This valuable book describes construction of a number of cheap receivers, deals with aerials and test apparatus. The circuits range from a receiver costing under £10 to more elaborate receivers, designed for quality rather than low price. Those wishing to study the fundamentals will find " Television Principles and Practice " a practical help in their studies. It costs 25s., or 25s. 8d. by post.—F. J. C.

TIMEBASE TESTING with the OSCILLOSCOPE

OBTAINING MAXIMUM EFFICIENCY WHERE RESPONSE
CURVES ARE AVAILABLE

By Gordon J. King, A.M.I.P.R.E.

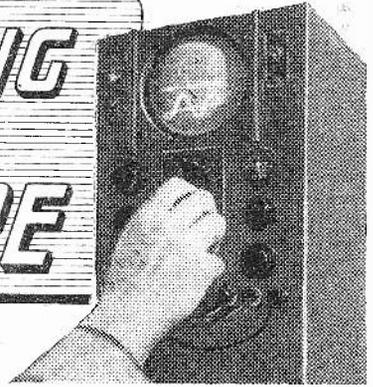

THE oscilloscope is invaluable in tracing faults in the timebase circuits of a television receiver. Properly applied it permits rapid tracing of elusive faults which might well take hours in locating without a means of observing the various waveforms. Receiver manufacturers, realising the asset of an oscilloscope in practical servicing, are now starting to include a selection of timebase (and other) waveforms in their service manuals.

Such specimen waveforms are essential in tracking down faults which provoke poor linearity, insufficient amplitude of scan, and other symptoms which demand a pattern waveform as a comparison. For example, apart from the shape of the waveform, which may or may not indicate that a certain section of the timebase circuit is responsible for impaired linearity, it is desirable to have a voltage comparison, so that one can quickly establish whether a fault, such as reduced scan amplitude, lies in the timebase generator or in the output stage. If the stipulated amplitude of drive is being applied to the output valve, then there is little object in extensively analysing the timebase generator circuits—that is, of course, so far as the symptom of reduced scan amplitude is concerned.

Moreover it is desirable to have some idea of the repetition frequency of the 'scope's timebase, for then it will be possible quickly to determine the frequency of the receiver timebase and thus expedite the location of time-constant faults.

It is often general practice to adjust empirically the timebase of the 'scope to suit the frequency of the waveform under examination, but such practice might well mislead the operator into concluding that the receiver timebase is at least running at the correct frequency. One can only be conclusive in this respect by knowing definitely that the 'scope timebase is running at a certain submultiple of the correct frequency of the receiver timebase. For example, if the 'scope timebase controls are marked and calibrated at, say, 25 and just over 5,000 c.p.s., the correct frame and line scanning speeds in the receiver itself will be revealed by the display of two complete cycles on the screen.

In order to use the 'scope to full advantage in timebase analysis, specimens and amplitudes of waveforms to be expected at various points in the particular receiver under examination will need to be available. Unfortunately, there are no waveforms

which can be illustrated as "standard," since they vary so considerably with various receivers and their diverse circuit arrangements.

Nevertheless, in order to provide the experimenter with an idea of the kind of waveforms to be expected at various points, a frame timebase circuit complete with oscillograms is shown at Fig. 1. The low-value resistor R (about 20 ohms) shown inserted in series with the deflecting coils enables a voltage reflection of the current in the coils to be applied to the oscilloscope, for it must always be remembered that the C.R.T. is a voltage operated device.

If the timebase circuit has failed completely a few rapid 'scope tests will soon show up the faulty part. The correct procedure, of course, is to work backwards through the circuit, towards the generator, until a signal is located. For example, if waveform 4 is present, it would almost certainly mean that the deflecting coils are short-circuited, and that resistor R is acting as a load for the amplifier.

A signal present at the anode of V2 (oscillogram 3), but lacking across R is an indication of an open-circuited deflecting coil. In the line amplifier, it is not a good idea to make the 'scope connection direct to the anode of the line amplifier valve owing to the presence of large voltages which occur during the line flyback. The test is best made via a small value capacitor—a crocodile clip fastened to the insulation of the wire carrying the current will in most cases provide sufficient coupling.

The presence of a signal at the grid of V2 (oscillogram 2) but not at the anode will indicate a fault somewhere in the amplifier, and this should take little time to find by employing normal testing techniques. A signal at the anode of V1 (oscillogram 1) but not at the grid of V2 will obviously indicate a fault in the coupling circuit between the oscillator and the amplifier.

If no sign of a trace can be obtained at the anode or grid of the oscillator valve, the valve itself or an associated component is undoubtedly to blame. The ease with which a signal can be traced in any equipment without the necessity of disturbing the wiring or making numerous unsoldering and resoldering operations is one of the chief merits of the oscilloscope.

Poor linearity of either vertical or horizontal scan is generally a very difficult fault to trace by using conventional testing methods; with a 'scope, however, it is a simple matter to check the waveform

at various points and then compare it with specimen waveforms given in the servicing data. The action of the negative feedback voltage in timebase linearity correcting networks can also be observed on the screen, and if a pattern is at hand it does not take long to find out whether or not this circuit is operating properly. In some cases it is necessary to follow up 'scope tests with routine voltage tests in order to find the faulty part, but in many cases correct use of the 'scope reveals the defect right up to the responsible component.

Application in the Sync Circuits

In the sync separator circuit of a TV receiver waveform analysis most certainly aids in hunting out a fault. This is revealed in Fig. 2, which depicts a typical sync separator stage and frame pulse filter (the diode). Oscillogram (1) shows the composite picture and sync pulses; oscillogram (2) illustrates the appearance of the line sync pulses after the picture content has been removed by the limiting action of the pentode sync separator valve. Complete frames with frame sync pulses are depicted in oscillogram (3), while oscillogram (4) satisfactorily indicates a clear frame sync pulse free of line sync pulses as the result of the filter action of the diode.

A picture which tends to pull and creep about the screen as its content and brightness level changes is nearly always caused by some of the picture signal finding its way into the line timebase. A 'scope test on the anode of the sync separator would quickly establish this, for then, instead of the line sync pulse being clear-cut, it would reveal slight traces of picture signal.

This, of course, is a clear indication that the sync separator valve is not limiting as it should do, and is

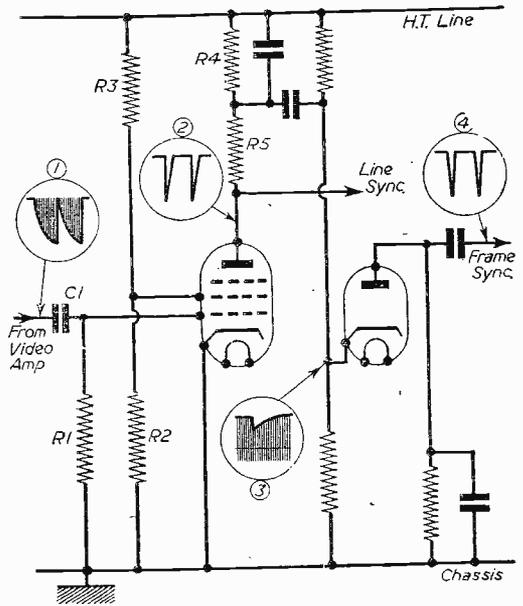


Fig. 2.—Circuit diagram of a sync separator showing the oscillograms which may be expected at various points.

essentially the result of an alteration in the value of a resistor associated with the anode or screen circuits.

A similar 'scope symptom may result in pulling on whites, in which case the time-constant components in the pentode control grid circuit should be examined for value—it is often discovered that either C1 or R1 has altered in value, or that C1 has become very slightly leaky, and is thus transmitting a positive potential from the anode of the video amplifier valve to the control grid of the sync separator valve, causing a considerable alteration to the biasing of this valve.

When making tests of this kind or, in fact, any tests with a 'scope, it should be noted that the waveform may be displayed inverted as compared with a textbook illustration of a similar waveform. This is because the C.R.T. cannot say which way up a curve is, as it depends on which way round the voltage is applied to the "Y" plates.

For example, between grid and anode of a valve a complete phase shift occurs, so that if a spikey waveform is shown positive-going (this

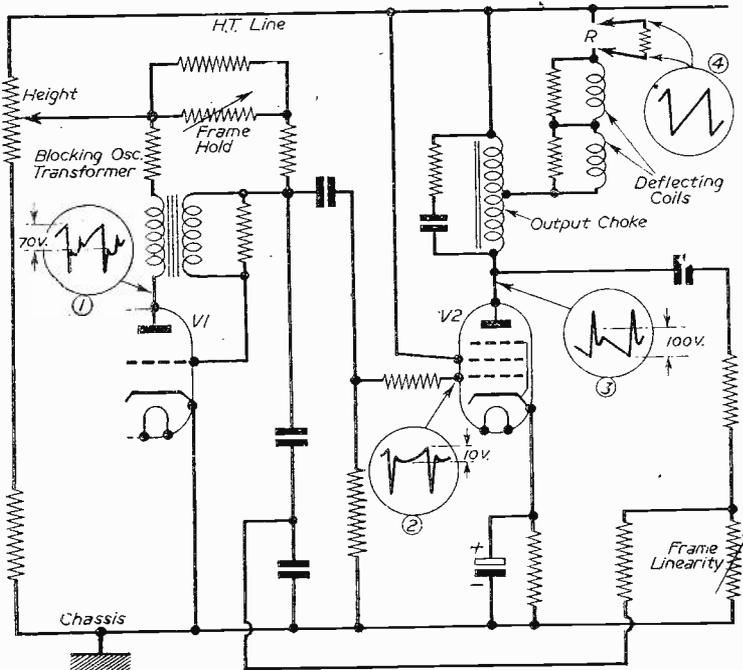


Fig. 1.—Circuit diagram of a frame timebase showing the oscillograms which may be expected at various points.

is with the spikes pointing to the top of the screen) on the grid of a valve, it will be displayed in inverted form on the anode of the same valve—a phase shift is, of course, occurring between oscillograms (1) and (2) on Fig. 2. A 380-degree phase shift will occur over two normal stages, so that the waveform will appear the right way up again.

A scope is a very useful instrument to have available during the process of adjusting the circuits of a home-built TV receiver. For example, the sync

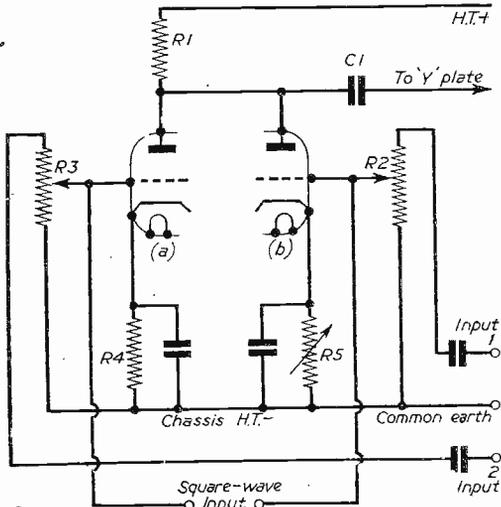


Fig. 3.—Illustrating the principle of electronic beam switching.

separator valve can be adjusted for optimum limiting while actually observing the output waveforms at the anode. It is a good idea to perform adjustments of this nature when the stage is in receipt of a constant-vision signal, such as that produced by Test Card "C."

Electronic Beam Switching

It is often advantageous to view two entirely different waveforms simultaneously, particularly if it is required to obtain a comparison. Special double-beam C.R.T.s, made primarily by Mullard, Ltd., are available for this purpose.

It is not generally known, however, that an ordinary oscilloscope can be made to produce a pair of separately controllable traces in the "Y" direction. The problem is not very difficult, and simply demands an electronic switch or gating circuit arranged to switch alternately on and off two "Y" amplifiers.

Fig. 3 shows two triode amplifiers connected to a common load resistor R1, and the voltage output developed across this conveyed through C1 to the scope "Y" plate. The two examination voltages are fed to the grids of the triode amplifiers via the variable controls R2 and R3. Normally, the valves are slightly over-biased and are also in receipt of a square-wave voltage. Now, on the positive impulse of the square-wave the corresponding valve is pushed into correct class "A" operation, and the applied examination signal is thus amplified and properly presented on the screen.


At the same time, however, the other triode receives a negative potential due to the square-wave, which virtually switches the valve off due to excessive

over-biasing. The examination signal on the grid of this valve does not, therefore, record on the screen. At the next instant, depending on the square-wave repetition frequency, the conditions are reversed and a continuous changeover from one amplifier (or channel) to the other automatically takes place.


Each waveform is thus produced as a series of spots or dashes, and provided the change-over is sufficiently rapid in relation to the timebase speed, each display appears to consist of a continuous line. By altering the cathode bias on one of the triodes relative to the other, i.e., by means of R5, it is possible to separate the two traces.

Co-axial Ends

THERE is apparently a problem in terminating the ends of co-axial cable, whether for use as connections between various points, or in use in actual aeriels. Correspondence in these columns recently (*Inexpensive Indoor Aerial*, July) shows that there is some difference of opinion concerning the best way of making "pigtails" for use as earthing connections. Whilst the method described in the letter referred to is very quick and easy to carry out, it is not, in the opinion of the writer, the best method. I always maintain the braiding *intact* which, I think, is the best plan, and the practice of trying to untwist the braiding is almost certain to lead to one or more strands being broken. The only precaution in the method illustrated here is that the penknife is not pressed too hard so that it cuts the braiding, and that the sharp pricker used to lift the braiding and open it as shown in Fig. 4 is not used too vigorously. Beyond this, it is perfect. To assist in following the sketches the details are as follows: bare about 2in. of the braiding, double the lead back on itself, and

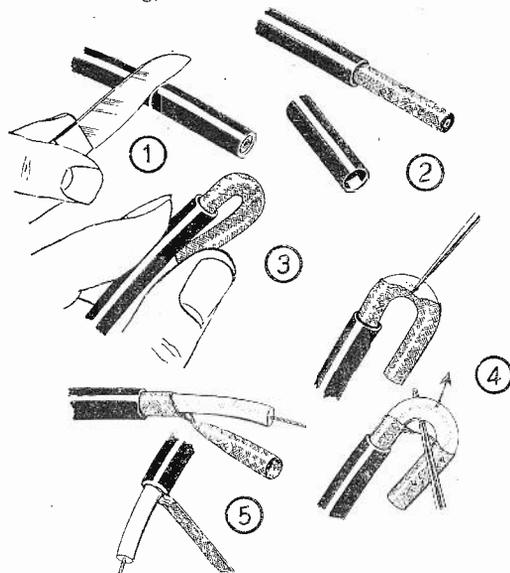

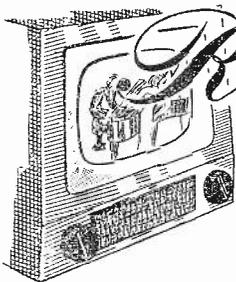then with a pointed implement *open* the braiding so that the polythene projects, when it may be pulled up and the end of the lead withdrawn through the bared space. The braiding, freed from the polythene but otherwise intact, is then twisted in the fingers and used as the anchoring piece.—W. J. D.



Receiving the I.T.A.

THE SECOND IN A SHORT SERIES ON THE PROBLEMS INVOLVED IN THE RECEPTION OF COMMERCIAL PROGRAMMES ON BAND III

By Gordon J. King, A.M.I.P.R.E.

AFTER last month's discussion of the somewhat abstract—though nevertheless, important—factors associated with reception in the V.H.F. Band, we should now be in a position to appreciate the more practical problems relating to TV reception in this Band.

It does not seem very long ago that a considerable demand existed for converters enabling single-channel receivers to respond to the wavelength of the BBC's local TV station. With the advent of new high- and low-power transmitters in Band I many viewers discovered that a picture of enhanced quality could be obtained from their new local station, but that it was operating on a wavelength (channel) removed from that of the more distant station.

In order to obtain the better picture, therefore, it was necessary for these viewers either to alter their receivers to correspond to the new wavelength or to fit a channel converter to the front of the receiver so that the new wavelength could be altered to correspond to the receiver.

Viewers possessing receivers which could be tuned to any of the five channels in Band I had little trouble in receiving the new station, for the main problem involved was simply that of altering the aerial. Less fortunate viewers with fixed channel receivers either altered the coils and realigned the circuits or made use of a channel converter.

The necessity of conversions of this nature is now diminishing since most current television receivers embody facilities for readily selecting any one of the five channels operating in Band I.

Instead, however, a demand is existing for converters or adaptors to enable five-channel receivers (and fixed-channel receivers) to tune to Band III. It will also be required of the receiver to tune to the BBC stations in Band I, and for this reason—apart from other technical reasons—it is not feasible to alter the tuned circuits as could be done to change channel in Band I.

With this in mind, then, there exists two methods by which existing Band I receivers (whether five-channel or otherwise) can be arranged for the reception of the I.T.A. programmes.

One method makes use of a superhet converter designed to respond to, and convert, the relatively high frequency signals in Band III so that they are acceptable by the input circuits of a Band I receiver.

The other method is to use an adaptor—such as a Band I/Band III tuner-unit—which, by means of switched coils, responds either to any channel in Band I and any channel in Band III and converts the accepted signals to the intermediate frequency of the receiver itself. This arrangement is featured in present-day two-band receivers and proves to be quite successful.

A similar method employs a Band III tuning adaptor which can be plugged into a Band I receiver—of special design—and by switching arrangements the entire existing R.F. and frequency changer section appertaining to Band I can be switched in or out of circuit at will thereby permitting Band I/Band III changeover.

The Band Converter

There are on the commercial market at the present time several designs of band converter units, most of which are self-powered from the mains and incorporate a switch facilitating changeover from a Band I station to one (or in some cases more) station in Band III. Converters of this kind are extremely easy to install as it is only necessary to connect the converter to the receiver through a short coaxial connecting link, connect both the Band I and the Band III aerials to sockets on the converter, and connect the converter to the mains supply.

The band changeover switch is accessibly positioned on the converter control panel, and on some units a master mains on/off switch is incorporated which enables both the receiver and the converter to be connected or disconnected from the power supply. In this case, apart from the mains lead from the converter, an extra lead is taken from the on/off switch to carry power to the receiver, and the receiver on/off switch is usually left in the "on" position.

The wiring and switching arrangements relating to this type unit are illustrated in the block diagram at Fig. 4. From this it may be seen that when the converter is switched to the "Band I" position, the signal in the Band I aerial is conveyed through the converter wiring and changeover switch, and on through the converter-receiver coaxial link so that it arrives at the Band I receiver aerial terminals in the usual way.

When the switch is set to the "Band III" position, however, the signal in the Band III aerial is taken, via a filter, to the grid circuit of the converter R.F. amplifier valve; the signal in the feeder of the Band I aerial is short-circuited, and the converted Band III signal in the converter mixer anode circuit goes by way of the I.F.T. and band changeover switch, and on through the coaxial link, again to the Band I receiver aerial terminals.

The converter, then, simply performs the function of changing the frequency of the Band III sound and vision signals so that they correspond to the tuned frequency (channel) of the Band I receiver. For example, if we consider the Midland area case, the Band III channel 8 sound and vision signals—186.25 Mc/s and 189.75 Mc/s respectively—are changed in frequency to correspond to the co-sited

Band I channel 4 station—sound 58.25 Mc/s and vision 61.75 Mc/s.

In order to maintain the correct frequency relationship between the converted Band III sound and vision signals it is necessary to use an oscillator frequency equal to the incoming Band III signal minus the tuned frequency of the Band I receiver. For example, if we consider this from the point-of-view of the sound signal in Channel 4 and Channel 8, we find that the oscillator frequency will need to be 186.25 Mc/s minus 58.25 Mc/s, or 128 Mc/s. In either band a

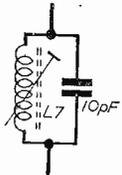


Fig. 6.—Circuit of a Band I Filter.

frequency of 3.5 Mc/s separates the sound and vision carriers, so it automatically follows that provided the converter oscillator is adjusted for maximum sound, the converted Band III vision signal will be presented to the Band I receiver in correct form.

We should add a qualification here, however, and that is when the converter is tuned for maximum sound, the converted Band III vision signal will have a single-sideband characteristic. This is, of course, because, as is common with the BBC's Band I transmissions in Channels 2 to 5, all Band III vision transmission are of the single-sideband mode.

So far as the Midland area is concerned, this is just what is required, since Sutton Coldfield in Channel 4 radiates a single-sideband signal and all the receivers in this area are adjusted for the reception of such a signal; the same applies to all stations operating in Channels 2, 3 and 5, which means that in the corresponding reception areas the converted Band III vision signal will be of ideal form for the receivers in use.

This may not be the case with all receivers in the London area (Channel 1), however, for here the BBC is radiating a double-sideband signal, and if a receiver is adjusted to respond fully to this kind of signal a certain degree of vision distortion will be evidenced on the application of a single-sideband vision signal—such as that obtained from a converted Band III vision signal.

Let us consider the London area problem in a little more detail. From the aspect of the sound signal a London Band III converter will need to use an oscillator frequency of 149.75 Mc/s (191.25 Mc/s : Channel 9 sound—minus 41.5 Mc/s—Channel 1 sound); therefore the Channel 9 vision carrier frequency—194.75 Mc/s—will be preproduced at the output of the converter at 45 Mc/s

(the vision carrier frequency of Channel 1). On the face of it, this would appear quite in order, but, unfortunately, this is not so, because the ideal response of the vision channel of a single-sideband receiver is 6 db down at the vision carrier frequency, and this does not hold good on a receiver which is adjusted for double-sideband operation.

It is estimated that quite a number of Band I receivers in the London area will respond satisfactorily to a converted Band III vision signal, particularly the less vintage type. The older models, however, may not be suitable for one hundred per cent. conversion by this means, and certain receivers may demand realignment of the vision channel, especially those which are tuned to the higher sideband of the Channel 1 vision signal.

If a receiver does not possess the correct response characteristic for a single-sideband transmission, the lower vision modulation frequencies will tend to be over-emphasised and streaking of the picture will result. It may be found, however, that the effect may be alleviated by detuning the converter oscillator slightly off the maximum sound position.

Converter Design

Apart from the circuit, two of the most critical features relating to the design of any V.H.F. converter are mechanical stability and shortness of wiring associated with the tuned-circuits—a converter would be of little success if its frequency shifted several megacycles when subjected to vibration or slight pressure, and not much good would come from a converter whose coil-connecting wires were longer than the length of wire used for the actual coil.

It is essential, therefore, to build any V.H.F.

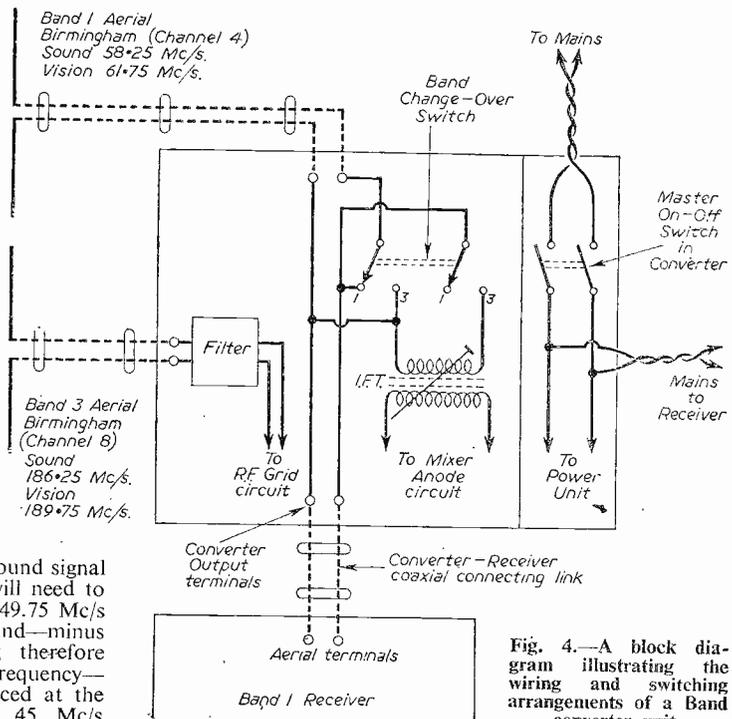


Fig. 4.—A block diagram illustrating the wiring and switching arrangements of a Band converter unit.

device on a really rigid chassis, and to arrange the coil's in relation to the tags on the valveholders so that the shortest possible wiring can be used.

The decoupling resistors and capacitors should be of non-inductive type and, as is common with the R.F./I.F. sections of television receivers, a common earthing point should be fixed for each separate circuit.

Converter Circuits

A rather interesting converter circuit which employs a pair of EF80 valves is shown at Fig. 5. The first valve V1 operates as an R.F. amplifier, while V2 performs the function of a self-oscillating frequency changer.

The Band III signals are coupled by L1 and tuned by L2 and thus arrive at the signal grid of V1. The amplified signals are developed across L3 and fed through the 10 pF capacitor to the signal grid of V2. The screen grid circuit of V2 in conjunction with L4 is arranged to oscillate at the frequency difference between the incoming Band III signals and the frequency at which the Band I receiver is tuned.

The difference frequency due to heterodyning of the oscillator and the Band III signals is thus in Band I, and is developed in the anode circuit of V2 across the I.F. transformer L5, L6. This signal goes by way of S1A—when in the "Band III" position—to the converter output socket and from this, via the coaxial link, to the aerial terminals of the Band I receiver.

With all converters of this kind there exists a possibility of interference occurring on Band III as the result of breakthrough of the local Band I station. This arises mainly when a receiver is operated in a Band I "swamp" area where the signal strength is very high.

In order to avoid pattern interference from this

cause it is essential that the coaxial link be restricted to, say, 3in. to 4in., and only best quality close-braided cable be used. The fact that the Band I feeder signal is shorted by S1B also assists in this respect.

Moreover, it is possible that some Band I signal may gain admittance to the receiver, via the Band III aerial and converter. If this happens the resulting pattern interference may be virtually eliminated by introducing a simple filter circuit (Fig. 6) in the input circuits of the converter.

Owing to the small power requirements of a two-valve converter a simple powerpack after the style of that shown in Fig. 5 is all that is generally necessary. The mains can be totally isolated from the converter chassis by using a small mains transformer with a H.T. secondary winding, but if the method shown in Fig. 5 is adopted, care should be taken to ensure that the chassis is connected to the neutral side of the mains supply.

Coil Winding Data

All coils wound on Aladdin low-loss 1/4 in. dust-cored formers.

- L1.—1 turn p.v.c. covered wire spaced 1/2 in. from L2.
- L2.—2 turns 20 s.w.g. spaced 1/2 in.
- L3.—2 turns, wire and spacing as for L2.
- L4.—4 turns, wire and spacing as for L2 and L3, tapped at 2 turns.
- L5.—22 turns 26 s.w.g. insulated, close-spaced.
- L6.—2 turns p.v.c. covered wire, spaced 1/2 in. from L5.
- L7.—12 turns, wire and spacing as for L5.

The Coils

As the wiring capacitances represent a considerable factor governing the frequency of the tuned-circuits, the coil winding data should be treated mainly as a

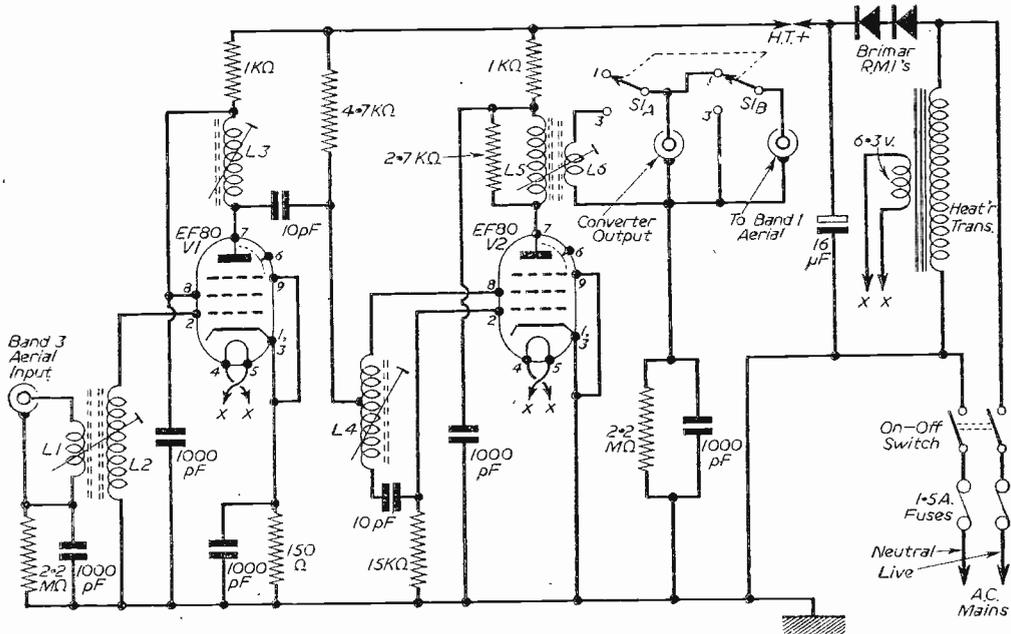


Fig. 5.—A Band III Converter Circuit employing Pentode valves. Coil Data will be found above.

guide. In most cases, however, it will be found that Channels 8 and 9 will be within the range of adjustment of the cores in coils L1/2, L3 and L4. If this does not resolve in practice, due to abnormal wiring capacitances, the desired range will almost certainly be found by altering the spacing between the turns on the coils—this applies particularly to coils L1/2 and L3, and most particularly to coil L4 (the oscillator).

Coils L5/6 and L7 are much less critical since they are tuned to a considerably lower frequency.

Tuning in the I.T.A. Signals

With the converter connected to the Band I receiver and with contrast and volume controls at maximum, L4 should be very slowly adjusted until the sound signal is heard. The core in L5/6 should then be

adjusted for maximum sound. L1/2 and L3 should next be adjusted for maximum sound, and at this stage the brightness control should be advanced slightly for it should now be possible to discern a picture.

L4 should be re-adjusted for maximum sound, consistent with optimum picture quality, and the remaining coils should be re-adjusted for a correct balance between sound and vision.

If any of the coils commence peaking with the core fully in, the turns spacing should be *reduced*, whilst the spacing should be *increased* if peaking commences as the core is coming out.

Next month a circuit employing the new type valves in a "cascode" circuit will be considered.


(To be continued)

An Aerial Mounting

By "Serviceman"

THIS aerial was originally mounted on the house chimney in the usual way and was quite satisfactory except for one big fault—it could not be maintained easily. Not many householders possess the necessary ladders or the head for heights which is an essential for such work. During the winter months the repair bills have been costly. Broken aerial sections and snapped coaxial cable have figured prominently.

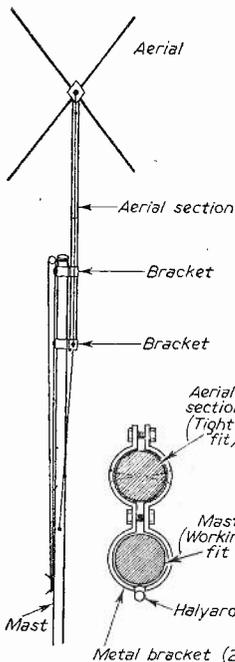For one who prides himself upon being able to do all the electrical repairs in the house, including the radio and television (with the valuable assistance of the "Practical Group"), this state of affairs was intolerable, so when the last repair became necessary, the aerial was taken



An illustration of the aerial mounting described.

off the chimney for re-erection elsewhere.

Though the overall size of it was surprising, the weight was negligible, so a 35ft. length of 2in. steel pipe was used for a mast. One end was sunk about 5ft. into very hard ground (it is surprising how hard it becomes

when deeper than 3ft.). The aerial was mounted on a 10ft. length of round wood, tapered at the end which goes hard into the pipe to a depth of a foot or so. Erecting this mast with aerial proved quite a job, but was successfully accomplished with the aid of

friends. It stands quite steady without guys, though three are used as additional supports. The picture was certainly improved and full advantage of the directional properties of the "X" type aerial could now be utilised by rotating the mast.

However, a month later the coaxial cable broke at the upper end (it had to be at the top, of course) though how it could have done so without outside aid was a mystery, as it was neither tight nor loose and was clipped securely to the wooden section. The mast had to be unstepped for the repair and then re-erected. Later, an aerial section became bent, nearly horizontal, and the mast had to be taken down again. (Eight large birds were responsible for this.) Two repairs in three months was not so bad, but the cost was not a great deal cheaper after all.

Two months later the well-known snowstorm effect became evident on the screen and the aerial was again suspect after the receiver had been checked O.K. The coaxial cable was checked for continuity as far up as possible, by sticking pins right through and testing with an ohmmeter from the plug end. All was well there, so a bad connection was suspected at the top (as usual). The mast was taken down once more and the aerial removed from it. The tapered portion of the wooden section could not be drawn out so was sawn off, leaving the end of the pipe well plugged.

A strong steel halyard and pulley block were purchased. The halyard being long enough to form a continuous loop. The pulley block was bolted to the top of the mast and the halyard passed through it before jointing. The mast was then erected without the aerial. Two metal brackets were made to go round the mast—a good working fit. These brackets are 2in. wide and form runners. They are screwed to the wooden section which supports the aerial—2ft. apart and 1/2in. from the mast. The double halyard is fixed to both brackets and pulled tight. The aerial rises until the upper bracket rests hard against the pulley block.

There is no tendency to swing as the halyard holds the aerial fast. It can now be lowered easily for any repairs, though none have been necessary during the past two months.

Aerials that are out of reach have always been suspect whenever trouble is experienced such as snowstorms, crackling, weak picture, etc. It's grand being able to start testing from the aerial whenever things go wrong. A TV aerial which can be lowered for repairs seems to be a novelty and an extremely handy one.

GROUND-PLANE AERIALS FOR TELEVISION

SOME EXPERIMENTAL AERIAL IDEAS


FOR THE AMATEUR

By S. A. Money

THE usual form of television aerial, such as the H or X type, is based on the use of a half-wave dipole as the active element. Among other possible arrangements there is the ground-plane type of aerial. This makes use of a quarter-wave vertical rod instead of a dipole. This type of aerial, though not frequently used for television, does have some advantage over the others, since it is much less sensitive to signals which come up to the aerial from the ground. Since most man-made interference comes from ground level this property of the aerial is extremely useful in those areas where such interference is prevalent.

The ground-plane aerial consists simply of a vertical rod a quarter of a wavelength long which is provided with its own earthed screen. This earthed screen often consists of four rods, known as radials, arranged to form a horizontal cross as shown in Fig. 1. This form of construction is generally used when the aerial is made for short-wave working. For the television frequencies, where the dimensions of the aerial are much smaller, it would probably be an advantage to use an earthed screen made of wire mesh. This would provide more efficient screening of the aerial from interference reaching it from the ground.

Fig. 1—The ground-plane aerial

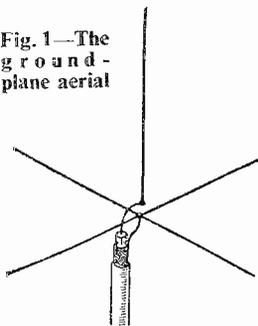

aerial, one for the vertical plane and another for the horizontal plane.

The vertical and horizontal polar diagrams for a half-wave vertical dipole are shown in Figs. 5a and 5b respectively. It will be seen that in the horizontal plane the aerial receives equally well from all directions. In the vertical plane the maximum sensitivity is in the direction broadside on to the aerial, whilst the sensitivity is very low off the ends of the aerial.

Suppose now the lower half of the dipole were to be removed, leaving a quarter-wave vertical rod.

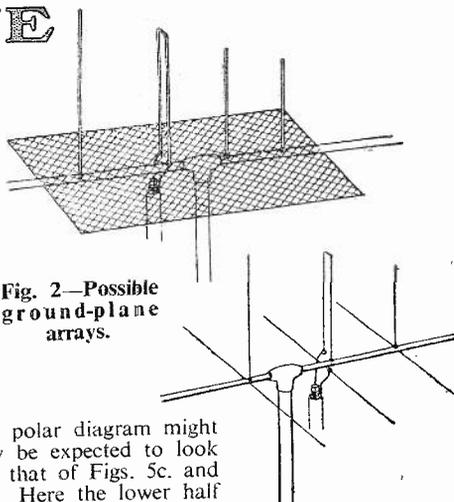


Fig. 2—Possible ground-plane arrays.

The polar diagram might now be expected to look like that of Figs. 5c. and 5d. Here the lower half of the lobe in the vertical plane has been removed. In actual fact the polar diagram would not be cut off so sharply, but the curve would be more likely to follow the dotted line as shown.

Let us now go a little further and place an earthed screen under the quarter-wave rod to form a ground-plane aerial. The polar diagrams will now be as shown in Figs. 5e and 5f. It will be noticed that although the pattern in the horizontal plane is still the same as for a half-wave dipole, the vertical pattern is considerably altered. It will be seen that the vertical pattern is now a fairly sharp lobe inclined at about twenty to thirty degrees to the horizontal. The sensitivity to signals coming from below the level of the aerial would ideally be zero, but in practice the screen is not perfect so that a small amount of signal is received from this direction.

Power Gain

Another important property to be considered for television aerials is their relative power gain. This is the ratio of the power picked up by the aerial in question to that picked up by a half-wave dipole when the field strength of the signal is the same for both aerials. This is usually expressed in decibels. In general the greater the directional properties of the aerial the greater will be its power gain.

For the ground plane aerial the power gain relative to a half-wave dipole is about 5 to 6 decibels. It is interesting to note that this has been achieved without sacrificing the omni-directional properties of the aerial in the horizontal plane.

Impedance

The characteristic impedance of the aerial is a factor which must be considered when we come to feeding the signals from the aerial to the receiver. In the case of the ground-plane aerial the characteristic impedance usually lies between 35 and 40 ohms, approximately half that of the half-wave dipole.

The actual value of the impedance is altered if the radials are not horizontal. If the radials are set at an angle of greater than 90 degrees to the vertical rod, as shown in Fig. 3, the impedance becomes greater. As the radials are lowered the impedance increases

until it becomes the same as for a dipole when they are in line with the vertical rod. At this stage the aerial is in fact a dipole. The properties of the aerial will vary from those of a ground-plane to those of a dipole as the radials are lowered.

In order to transfer the maximum signal from the aerial to the receiver it becomes necessary to make the characteristic impedance of the feeder cable, and the input impedance of the receiver, as nearly as possible equal to the characteristic impedance of the aerial. The normal input impedance of a British television receiver is about 70 to 80 ohms and the most popular feeder cable is the 70 to 80 ohm coaxial type. Hence, the best value for aerial impedance would be about 80 ohms. The ground-plane, however, has an impedance of only 40 ohms, so it is obvious that some form of matching device will be needed to match the aerial to the cable and the receiver.

Matching

When the aerial is being used fairly close to the transmitter, the amount of mismatching caused by using an 80-ohm cable can generally be neglected. The interference rejection properties are reduced by the mismatch, however, since the cable itself tends to pick up signals. In order to obtain a better match to the aerial, a 40-ohm cable could be used. The receiver matching being broader than that at the aerial end would produce very little loss of signal. If no 40-ohm cable is obtainable it is easy to make an equivalent cable by using two lengths of 80-ohm cable and connecting them in parallel.

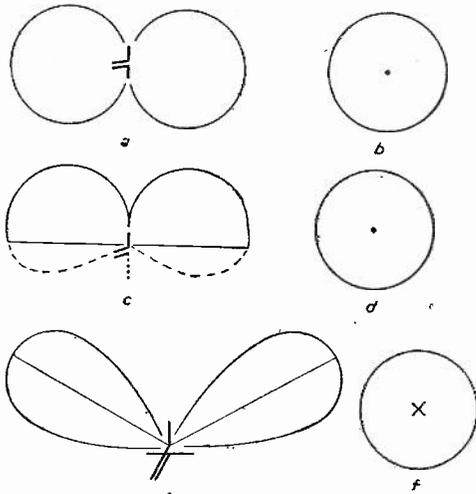


Fig. 5—Polar diagrams

In order to obtain a better match, 80-ohm cable is used for the feeder, so as to match at the receiver end, and it is matched at the aerial end by means of a quarter-wave matching section. This matching section consists of an electrical quarter-wavelength of cable of an impedance different from the feeder cable. The characteristic impedance of the matching cable can be found from the formula :

$$Z_q = \sqrt{Z_a \cdot Z_f}$$

where Z_q = Impedance of quarter-wave section.

Z_a = Impedance of the aerial.

Z_f = Impedance of the feeder cable.

In order to find the length of an electrical quarter-wave we can use the formula :

$$\text{Length in ft.} = \frac{246}{f \text{ Mc/s}} \times \text{V.F.}$$

where V.F. is the Velocity Factor of the cable, and this usually has a value of about 0.65 for coaxial cables.

For fringe area locations it is possible to make use of an aerial preamplifier for matching purposes. In this case a perfect match can be obtained and also any effects due to pick-up on the cable itself can be ignored.

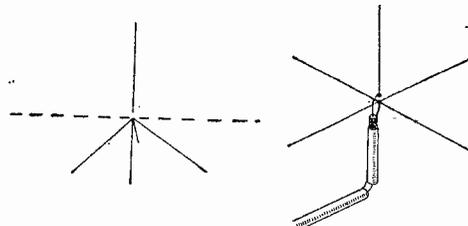


Fig. 3—(left) Lowered radials. Fig. 4 (right)—Matching section

Construction

Now let us consider the practical details of construction of ground-plane aerials. The vertical rod should be 0.24 of a wavelength long and each of the radials should be at least 0.28 of a wavelength long. If a wire mesh screen is used it should be at least 0.28 of a wavelength radius. The dimensions of the elements for the various television channels is given in the table. Also included in this table are the lengths for the matching section required. If an 80-ohm feeder cable is used, the characteristic impedance of the matching section should be about 50 ohms. A reasonably good match would be obtained by using two lengths of 80-ohm cable connected in parallel. This matching section is then connected in series between the aerial and the cable, as shown in Fig. 4.

Channel	Rod length	Radial length	Matching Section length
	ft. in.	ft. in.	ft. in.
Alexandra			
Palace ...	5 4	6 5	5 7
Holme Moss ...	4 7	5 7	5 0
Kirk o'Shotts ...	4 3	5 0	4 7
Sutton			
Coldfield ...	3 11	4 7	4 2
Wenvoe... ..	3 7	4 4	3 10
Croydon I.T.A.	1 2	1 5	1 3

In order to retain a bandwidth wide enough for television purposes, it is necessary to use elements which are at least 3/8 in. in diameter.

To obtain a higher impedance at the aerial terminals, the technique of folding the active element may be used. By connecting a second element in parallel with the main element, the impedance is increased by a factor of four. The impedance goes up as the square of the number of elements used. Thus, three elements gives an impedance nine times as great. The folded ground-plane has a wider bandwidth than the simple type and is useful if two channels are to be covered.



Servicing TELEVISION RECEIVERS

No. 12.—PYE V4, V7, VT4 AND VT7

By L. Lawry-Johns

THESE receivers exhibit several "usual" faults, some of which may be rapidly cleared due to their obvious nature, and others which are not so easily dealt with owing to their more confusing symptoms. The difference between the V models and the VT is, of course, the addition of the Band III tuner unit. This difference affects only the early parts of the receiver up to V2.

The faults likely to be encountered are: no raster due to no E.H.T.; raster but no modulation (picture); horizontal tearing; unsteady frame scan; faint picture with weak sync.

The chassis is quite easily withdrawn for servicing purposes, leaving the tube mounted in the cabinet. In the V4 it is only necessary to remove the two fixing screws from the rear flange of the chassis, the right-hand one being visible, the left is concealed below the cardboard covers of the control panels. Next, slacken the screws retaining the aerial socket at the top right-hand side of the cabinet and remove the small panel. The E.H.T. lead to the tube anode may be removed until the chassis is free of the cabinet and the multi-cable form held clear whilst this is being done. The chassis may now be handled into the desired position, replacing the E.H.T. clip and ensuring that the aerial panel is not touching any H.T. points. A frequent fault encountered is that the line hold control is at the end of its travel and the picture still not locking. Normally this is due to the line oscillator ECL80 losing its emission, and a change of valve rights the trouble. On this receiver there are two line hold adjustments to cater for variations which may occur between different ECL80 valves. The normal line hold control is, of course, on the left-hand side at the rear of the chassis, but the other is a pre-set condenser mounted beneath the chassis as shown in Fig. 2. The correct method of adjustment is as follows: rotate normal line hold to centre of its travel and then adjust the preset control to obtain picture lock.

There is a resistor in the line hold circuit which may affect the adjustment and make a positive lock difficult. It is a $1M\Omega$ resistor and is shown in

Fig. 2 next to the preset line drive control. If no raster can be obtained at all, i.e., the brilliance control does not cause any illumination of the screen, the presence of E.H.T. should be checked. If no spark is obtained at the tube anode clip, check the EY51 on the top of the line output transformer; the screening cover will have to be removed (one screw fixing) to gain access to it. The cover, when it is removed will reveal the EY51 on top of the transformer and the PL81 and PY81 line output and efficiency diode. If the EY51 is not lighting up, the single wire end of the valve, i.e., the ring further away, should be tested for the presence of E.H.T. by means of a screwdriver blade. If a spark—a healthy blue one, not a faint tiny pinprick—is drawn off, the EY51 may safely be replaced, taking care to make the soldered connections properly:

If, however, with the EY51 not lighting up and with no healthy spark available at the anode, it is safe to assume that the fault is either in the line oscillator or output stages.

If no audible whistle is present at all, the fault should be looked for in the oscillator stage, but should a faint whistle be heard which varies with rotation of the line hold control, it may be assumed that the oscillator stage is in order and that the output is at fault.

The most common cause of the output stage failing to operate properly is the failure of the PL81 output valve. After this has been cleared as a possible cause, the PY81 should be suspected. If this valve is in order the next most common cause of non-operation of the line output stage, is a defect in the line output transformer.

Replacement is the only sure method of checking this, but before doing so the following components should be checked. The $.5\mu F$ condenser marked C106 in Fig. 2: this may cause heavy damping of the line output stage, resulting in low E.H.T., if it is leaky, as well as a complete failure of the stage. The width and linearity coils should be measured, or at least their continuity established. These are the two coils which partially obscure the PY81 when viewed from the rear, L23 and L24. As well as testing these for continuity, it should be ensured that they are not too close, as this may cause sparking between the two, and line "tearing" if not a complete cessation of operation of the output stage.

Line Drive Control

If these points are checked it is reasonably safe to replace the line output transformer, as this is almost sure to be the culprit.

As in most modern receivers, a line drive pre-set condenser is fitted and is marked C101 in Fig. 2. C97 is the pre-set horizontal hold already referred to. It is evident from many readers' letters that the function and adjustment of this line drive condenser

This receiver features automatic contrast control and the bias applied to the vision section is obtained via the line output stage. Therefore a device is necessary which will limit the signal applied to the video amplifier to avoid overloading whilst the PY81 takes its time to reach operating level. The device employed is known as the "overload diode" and is a crystal diode connected between the grid of V8 (video amp) and the cathode of V27 (PL81 line output). Thus, the grid of the video amplifier is virtually earthed until V27 becomes operative and the cathode voltage of this valve renders the diode inoperative.

Obviously a fault in this diode will result in a weak picture and sync due to the signal being shunted to chassis from the grid of the video amplifier. Replacement of the overload crystal diode is the only reliable test although as a rough guide the diode should measure a few hundred ohms one way and approximately 4 M Ω the other.

Negative Picture with Hum Bars

This may be caused by a heater to cathode leak in the ECC82 signal sampler (V12B). A negative picture is so termed because the blacks tend to turn white and the whites black, this of course being also a symptom of a failing C.R.T. when the contrast is well advanced. On this receiver the presence of hum bars (wide bands of light and dark across the tube face) completes the diagnosis and directs suspicion to the ECC82.

This ECC82 (V12) is a double triode, the other triode section being used as the local oscillator on the V4, V7 models, and is rendered inoperative on Models VT4 and VT7. Although referred to as the signal sampler, V12 is actually the amplifier part of the circuit, the actual signal sampling being done by V13 (EB91).

Raster with no Modulation

By this is meant that the brilliance control may be advanced to show the blank illumination, but no picture on the tube face. This may, most often, be caused by the failure of emission of an EF80 valve. If no sound is received valves 1 and 2 should be substituted. If, however, sound is being received valves 4 and 5 should receive attention first, then V8 video amp. The cathode of the tube is signal fed from the cathode of one triode section of an ECC82 (V9), the other section is the white spot suppressor, this, therefore, is a cathode follower. The point being that the tube receives its modulation from V9 and not from the anode of the video amplifier as is normal practice. V3 is a crystal diode (CG6E) interference suppressor which limits the interference level to .5 volt, thus preventing V4 from being overloaded.

V6 is a CG5E crystal diode which operates as the vision detector, whilst V7 is the before-mentioned overload diode. Lack of both vision and sound may, of course, be due to the failure of the

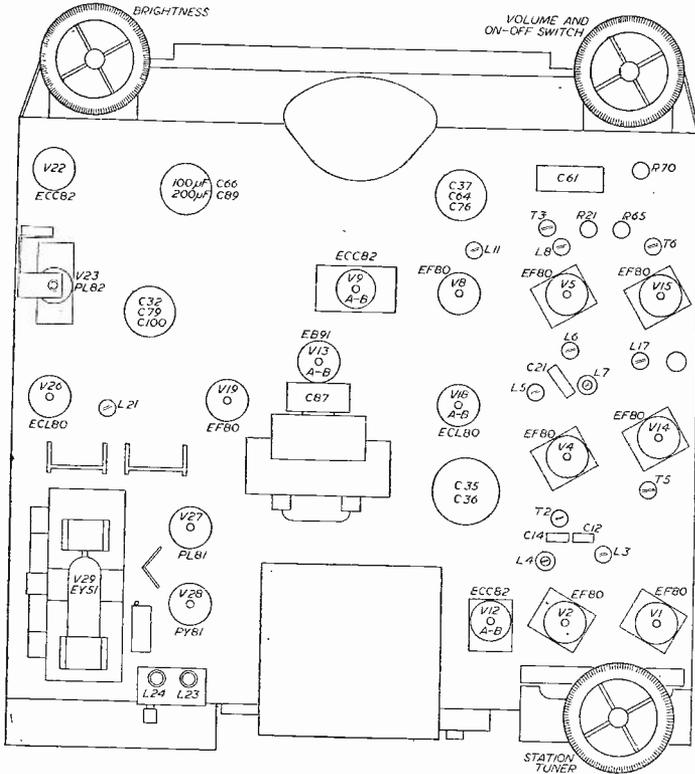


Fig. 1.—Note position of EY51, L24, L23 and V26 line oscillator. This illustration shows the screening cover of the line output stage removed.

is not clearly understood. It has a profound effect upon the operation of the line output valve and the correct adjustment is essential both from a viewing standpoint and the working life of the line output valve. With a voltmeter connected from the cathode of the PL81 (pin 3) and chassis, the control should be adjusted for *minimum reading on the meter*. Before this point is reached kinks or a bright white line will be observed to the left of the screen. Hence many queries.

Before leaving the line timebase, a few points may be noted. The core of L21 marked in Fig. 1 must *not* be adjusted. This is the coil control of the *auto-sync* circuit, and synchronisation will be affected if this is disturbed.

The PY81 has ceramic insulation between the heater and cathode and, therefore, takes longer than is normal to reach operating efficiency. Two to three minutes is usual. The ECL80 (V26) line oscillator is used as a multivibrator and thus uses no blocking transformer. The small transformer mounted beneath the chassis under the line output transformer is the *auto-sync* transformer and is usually trouble free. The 250 mA fuse at the rear of the receiver is in series with the H.T. feed to the line output stage.

local oscillator (one section V12) ECC82, but normally this is less suspect than the EF80 stages. Should the valves prove faultless, lack of vision only is often due to the vision detector V6, crystal diode CG5E, developing a fault. Again substitution is the only reliable check. The position of this diode is indicated in Fig. 2. Should the signal still be lacking, the other crystal diodes referred to should be checked for short-circuit, V3 and V7. The majority of this fault location applies to the V and the VT models, but there are several variations such as the triode section oscillator of V12 not being in use on the VT models, the oscillator being the triode section of the PCF80 in the channel selector unit. The pentode section of this valve serves as the mixer, and the other valve in the unit is a PCC84 double triode connected as a cascode R.F. amplifier. The output of the mixer is fed to the grid of what is termed V2 in the V models, and which was used as the mixer in these, this then becoming the first common I.F. amplifier.

Vision Defect on VT Models

This usually shows as ringing, a black or white second image on the picture, and is nearly always due to the fine tuner being out of adjustment. The position of this fine tuner is rather critical and some patience may be required to obtain good definition with freedom from ringing and good sound.

Sound Channel

V14 and V15 are the two sound I.F. amplifiers and both are EF80 valves. V16 is the sound detector and is a crystal diode CG6E. The signal then passes through V17, which is a WX6 interference limiter, to the triode section of V18, an ECL80. The pentode section is used as the sound output to the speaker.

On several occasions a rather peculiar fault has developed, which takes the form of a hum on the sound accompanied by distortion of the frame scan.

In each case this has been found due to an internal leak in the 100+200µF condenser can C66/C89 marked in Fig. 1. These condensers are the bias decouplers of the ECL80 sound output and PL82 frame output valves.

Obviously a leak between the two sections of this condenser can will result in an amount of interaction between the circuits. The sound channel is reasonably trouble free. Lack of sound should direct attention to V14, V15 and V18 first, and then the crystal diode. Distortion may usually be tracked down to the interference suppressor or its load resistor (2.2 MΩ). If distortion is not located here the diode detector should be suspected and if this proves good, the ECL80 sound A.F. and output V18 will most likely be at fault. This, of course, may be checked first.

These faults are not listed with the easiest to check placed first, but in order of the most likely cause.

Frame Timebase

This part of the circuit consists of an ECC82 double triode V22, which functions as a multi-vibrator. This being followed by the PL82 frame output V23. The ECC82 is pulse fed from an interlace circuit consisting of two WX6 rectifiers which ensure that the circuit is triggered at the right instant. Loss of frame hold may be due to several factors depending upon the symptoms. The frame hold (vertical hold) control will enable the fault to be localised. If the picture is rolling one way and as the control is rotated the rolling slows down and then commences to roll in the opposite direction, it may be assumed that the fault is lack of adequate frame pulses and not a fault in the timebase itself. Check the sync separator V19 (EF80) and then the interlace diodes (WX6) previously referred to. If, however, the picture roll is in one direction whatever the position of the hold control, the ECC82 should be substituted and if this does not cure the fault check the series resistor from the slider of the hold control (820 KΩ) coloured grey, red, yellow.

Poor linearity, that is uneven spacing of the scanning lines leading to vertical picture distortion which cannot be corrected by adjusting the frame (vertical) linearity control, should direct attention to the ECC82 and then the PL82. If no improvement

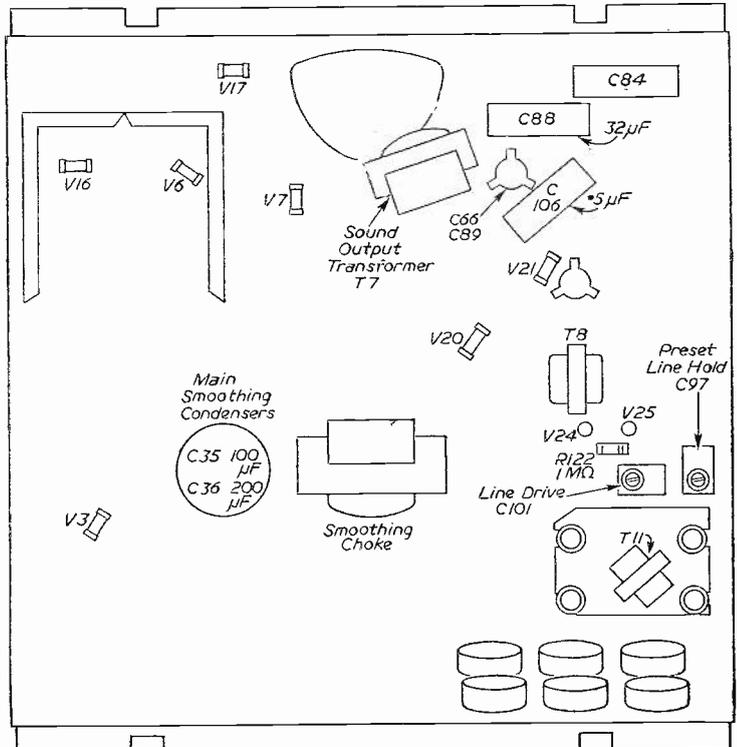


Fig. 2.—Showing the position of line timebase pre-set condensers. The various crystal and metal rectifiers and components mentioned in the text are simplified so that they may be seen more clearly.

is apparent by replacing these valves, and the poor linearity is accompanied by decreased height, check the screen decoupling condenser of the PL82, C88

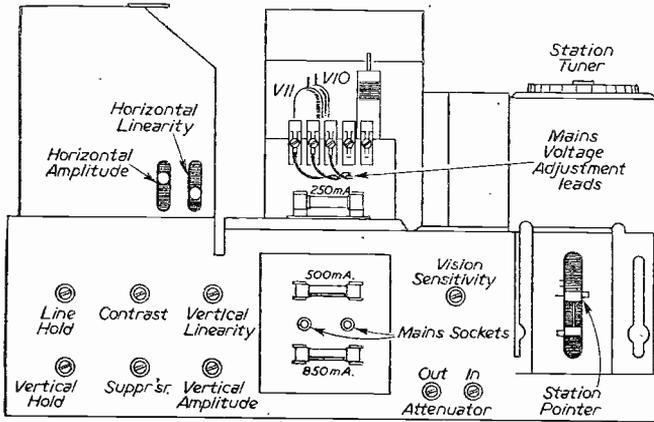


Fig. 3.—Rear view of V4 and V7 models.

(32 μ F) and the previously mentioned C89 cathode bypass.

Weak Sync

If no sync pulses line or frame are being received, and this is shown by inability to lock either the frame or line timebases properly, first check V19 (EF80), then its 12 μ F screen decoupling condenser and then the vision detector crystal diode, peculiar though this may seem. This presupposes that a reasonably strong modulation is being displayed on the tube face even if it is scrambled.

If the modulation is weak, however, and of very poor contrast, valve replacement having no effect, the overload diode should be suspected, and the vision detector diode if the overload seems to be up to standard.

Power Supplies

H.T. is obtained from two PY82 rectifiers which give very little trouble, a 30 ohm surge limiting resistor is in series with each cathode, the centre point of the two being taken to the reservoir capacitor and smoothing choke and thence to the H.T. line. All valves, plus C.R.T., have their heaters connected in one chain so that the failure of one will render the others inoperative.

Fuses

Three are fitted, one in the chassis side of the mains supply rated at 850 mA anti-surge.

Another is fitted between the mains selector resistors and the valve heater chain and is rated at 500 mA. The 250 mA fuse has already been referred to as being in the H.T. supply to the line output stage.

Final Notes

The VT models operate satisfactorily on Band III, using "sprigs" (clip-on elements) fitted to an existing well sited, H or X aerial up to 20 miles from the transmitter, depending upon the locality. Beyond this distance, and sometimes inside this distance, a multi-element array is essential. In this case both aerial leads are taken to a junction box from which one lead is taken to the receiver.

The V models are converted by a specially made adaptor, made by Pye for easy fitting. It will have been gathered from the above remarks that these receivers are rather complicated, and unless the function of the various components is understood, second thoughts should be indulged in before any involved servicing is undertaken.

It would appear that there is some confusion about the correct method of centring the picture on the screen. Viewed from the rear of the tube, the first component on the tube neck is the ion-trap, this is always adjusted for maximum brilliance as described many times in these pages.

The next item is the focus magnet with its lefthand control lever. Behind this will be found two metal plates with small finger-grip extensions. These are the centring plates, and each varies the vertical or horizontal position of the picture upon rotation. In front of these again is the scan coil unit with the thumb screw at the top giving a tilt adjustment, i.e., adjustment will slightly rotate the picture. A drawing is provided in case these directions are not understood.

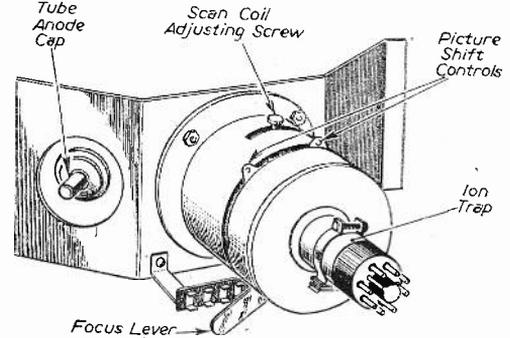


Fig. 4.—Rear view of the tube assembly.

I.T.A. PROGRESS REPORT

TWO further contracts with ARTV and Granada were signed recently. All contracts are for 10 years, but it is unlikely that their contents will be published.

Good progress has been made regarding the siting of transmitters. The ITA received planning permission for Winter Hill (near Bolton), where a station, sited 1,450ft. above sea-level, will serve the Lancashire area. The architects expect building to begin shortly, so that the station can transmit by the spring of '56. From an initial signal strength of 100 kW., power will be stepped up to about 200 kW.

Coverage will extend to Barrow-in-Furness, Lancaster and Settle in the north; Stoke-on-Trent, Crewe and Wrexham in the south; Liverpool and Colwyn Bay to the west; and points inward from Rochdale to the east. In all, the potential audience equals the population of London, i.e., 7 million people.

Midlands.—The Midland transmitter now being tested at Cambridge should be ready for the opening of a Birmingham station at the turn of the year. It is the first Band III station to be built by Pye.

THE NATIONAL

August 24th to
September 3rd

RADIO SHOW

List of Principal Exhibitors
in Alphabetical Order,
with Stand Numbers

Name	Address	Stand No.	Name	Address	Stand No.
Aerialite, Ltd. ...	Castle Wks., Stalybridge, Cheshire	33	E.M.I. Sales & Service, Ltd.	Hayes, Middx.	215
Airmec, Ltd. ...	High Wycombe, Bucks.	108	Edison Swan Electric Co., Ltd.	155, Charing Cross Rd., W.C.2	58
Antiference, Ltd.	Bicester Rd., Aylesbury, Bucks.	64	Electric Audio Reproducers, Ltd.	17, Little St. Leonards, S.W.14	216
Argosy Radio-vision, Ltd.	Argosy Wks., Hertford Rd., Barking, Essex	35	English Elec. Co., Ltd.	Marconi House, 336-7, Strand, W.C.2	31
Arrell Electrical Accessories, Ltd.	Vincent Wks., New Islington, Manchester, 4	111	Ever Ready Co. (G.B.), Ltd.	Hercules Place, Holloway, N.7	54
Assimil (England), Ltd.	10, Pembridge Sq., W.2	312	Ferguson Radio Corp., Ltd.	105-109, Judd St., W.C.1	14 & 103
Automatic Coil Winder & Elec. Equip. Co., Ltd.	"Avocet Hse.," 92-96, Vauxhall Bridge Rd., S.W.1	116	Ferranti, Ltd. ...	Hollinwood, Lancs.	13 & 120
Balcombe, Ltd., A. J.	52-58, Tabernacle St., E.C.2	21	Garrard Eng. & Mfg. Co., Ltd.	Newcastle St., Swindon, Wilts.	47
Belling & Lee, Ltd.	Gt. Cambridge Rd., Enfield, Middx.	46	General Elec. Co., Ltd.	Magnet Hse., Kingsway, W.C.2	37
British Communications Corporation, Ltd.	Second Way, Exhibition Grounds, Wembley, Middx.	217	Gibbs, Ltd., Herbert, E.	First Avenue, Montague Rd., Edmonton, N.18	209
Bulgin & Co., Ltd., A. F.	By-Pass Rd., Barking, Essex	59	Goodmans Industries, Ltd.	Axiom Wks., Wembley, Middx.	20
Bush Radio, Ltd.	Power Rd., Chiswick, W.4	22 & 57	Gramophone Co., Ltd.	Hayes, Middx.	48 & 49
Champion Elec. Corp., Ltd.	Champion Wks., Drove Rd., Newhaven, Sussex	62	Hart & Co., Ltd., Alfred	249, Upper St., N.1	210
Channel Electronic Industries, Ltd.	Princess St., Burnham-on-Sea, Somerset	212	Hartley Baird, Ltd.	Princess Wks., Brighouse, Yorks.	52
Cole, Ltd., E. K....	Ekco Wks., Southend-on-Sea, Essex	12 & 121	Hunt (Capacitors), Ltd., A. H.	Bendon Valley, Garratt Lane, Wandsworth, S.W.18	8
Collaro, Ltd. ...	Ripple Wks., By-Pass Rd., Barking, Essex	39	Hiffe & Sons, Ltd.	Dorset Hse., Stamford St., S.E.1	202
Co-operative Wholesale Society, Ltd.	1, Balloon St., Manchester	60	Invicta Radio, Ltd.	100, Gt. Portland St., W.1	53
Cosmocord, Ltd.	700, Gt. Cambridge Rd., Enfield, Middx.	201	J. B. Mfg. Co. (Cabinets), Ltd.	86, Palmerston Rd., E.17	219
Cossor, Ltd., A. C.	Cossor Hse., Highbury Grove, N.5	23	J. Beam Aerials, Ltd.	Weedon Rd. Estate, Northampton	104
Cossor Instruments, Ltd.	Cossor Hse., Highbury Grove, N.5	114	Kolster-Brandes, Ltd.	Footscray, Sidcup, Kent	16
Decca Record Co., Ltd.	1-3, Brixton Rd., S.W.9	32	Labgear (Cambridge), Ltd.	Willow Place, Cambridge	204
Domain Products, Ltd.	Domain Wks., Barnby St., N.W.1	305	McMichael Radio, Ltd.	190, Strand, W.C.2	40
Dubilief Condenser Co. (1925), Ltd.	Ducon Wks., Victoria Rd., North Acton, W.3	221	Marconiphone Co., Ltd.	Hayes, Middx.	50
Dynatron Radio, Ltd.	"The Firs," Castle Hill, Maidenhead, Berks.	24	Masteradio, Ltd.	10-20, Fitzroy Place, N.W.1	36
E. A. P. (Tape Recorders), Ltd.	546, Kingsland Rd., E.8	303	Matthews (Radio & TV), Ltd.	419, Old Ford Rd., Bow, E.3	211
E.M.I. Institute, Ltd.	10, Pembridge Sq., W.2	311	Mullard, Ltd. ...	Century Hse., Shaftesbury Ave., W.C.2	18

Name	Address	Stand No.	Name	Address	Stand No.
Multicore Solders, Ltd.	Maylands Ave., Hemel Hempstead, Herts.	63	Sapphire Bearings, Ltd.	96a, Mount St., W.1	304
Murphy Radio, Ltd.	Welwyn Garden City, Herts.	29	Simon Equipment, Ltd.	Recorder Hse., 48-50, George St., W.1	10
NEWNES, LTD., GEORGE	Tower Hse., Southampton Street, W.C.2	107	Slingsby, Ltd., H. C.	89, 95/7, Kingsway, W.C.2	112
Pañ (Radio & T/V) Ltd.	295, Regent St., W.1	61	Sobell, Industries, Ltd.	Langley Park, Slough, Bucks.	19
Pamphonic Reproducers, Ltd.	17, Stratton St., W.1	34	Specto, Ltd. ...	Vale Rd., Windsor, Berks.	206
Permanoid, Ltd.	Vincent Wks., New Islington, Manchester, 4	111	Standard Tel. & Cables (Brimar), Ltd.	Brimar Vale Division, Footscraë, Sidcup, Kent	1
Peto Scott Elec. Instruments, Ltd.	Weybridge Trading Estate, Surrey	55	Standard Tel. & Cables, Ltd. (SenTerCel)	Connaught Hse., Aldwych, W.C.2	119
Philco (Overseas), Ltd.	Romford Rd., Chigwell, Essex	15	Stella Radio & Tel. Co. Ltd.	Oxford Hse., 9-15, Oxford St., W.1	51
Philips Elec., Ltd.	Century Hse., Shaftesbury Ave., W.C.2	27 & 43	Tape Recorders (Electronics) Ltd.	3, Fitzroy St., W.1	66
Pilot Radio Ltd. ...	Park Royal Rd., N.W.10	56	Taylor Electrical Instruments, Ltd.	Montrose Ave., Slough, Bucks.	6
Plessey Co., Ltd. ...	Vicarage Lane, Ilford, Essex	122	Telegraph Condenser Co., Ltd.	North Acton, W.3	45
Portogram Radio Elec. Ind., Ltd.	Preil Wks., St. Rule St., S.W.8	65	Telerection, Ltd. ...	Antenna Wks., St. Paul's, Cheltenham	7
Pye, Ltd. ...	Radio Wks., Cambridge	30	Telequipment, Ltd.	1319a, High Rd., Whetstone, N.20	105
RCA Photophone, Ltd.	36, Woodstock Grove, Shepherds Bush, W.12	110	Television Society	164, Shaftesbury Ave., W.C.2	315
" PRACTICAL WIRELESS " AND " PRACTICAL TELEVISION " STAND NO. 107					
RadioGramophone Dev. Co., Ltd.	Eastern Av. West, Mawneys, Romford, Essex	11	Ultra Elec. Ltd. ...	Western Ave., Acton, W.3	41
Radio Society of Great Britain	New Ruskin Hse., Little Russell St., W.C.1	310	Valradio, Ltd. ...	New Chapel Rd., Feltham, Middx.	118
Radio & T/V Retailers' Assn., Ltd.	26, Fitzroy Sq., W.1	302	Vidor, Ltd. ...	West St., Erith, Kent	28
Regentone Radio & Tel. Ltd.	Eastern Avenue West, Mawneys, Romford, Essex	38	Westinghouse Brake & Signal Co., Ltd.	82, York Way, King's Cross, N.1	101
Roberts' Radio Co., Ltd.	Creek Rd., East Molesey, Surrey	117	Whiteley Elec. Radio Co., Ltd.	Mansfield, Notts.	25
Rola Celestion, Ltd.	Ferry Wks., Thames Ditton, Surrey	17	Wolsey Television, Ltd.	43-45, Knight's Hill, S.E.27	5
Rudman, Darlington (Electronics), Ltd.	Wednesfield, Staffs.	208	Wright & Weaire, Ltd.	131, Sloane St., S.W.1	218

Marconi TV Centre

THE Broadcasting Division of Marconi's Wireless Telegraph Co., Ltd., have established at St. Mary Abbot's Place, London, W.8, the first fully equipped television training studio of its type in Britain.

The advent of Commercial Television has posed serious problems to the many organisations, throughout Britain, interested in the television medium. To all such, the Marconi Television Centre offers the following facilities:—

A complete training course in the operation and maintenance of television studio equipment is undertaken by the Marconi College.

The Centre is available to any organisation wishing

to use the equipment for training their own studio and production staffs.


It can be used by any organisation, large or small, for rehearsals or auditions under true operational conditions. Telecine equipment is available for those wishing to appraise filmed programmes on television. A complete mobile Outside Broadcasting Unit is attached to the Centre and can be used.

Arrangements can be made for live broadcasts to be originated from the Centre, which has a stage of approximately 2,000 sq. ft.

The Marconi Television Centre, which has been in operation since June 2nd, has already proved to be an unqualified success in the training of personnel upon the latest equipment. Among those already making extensive use of the facilities are Associated-Rediffusion, Ltd.

SUMMER SALE — Special Prices This Month

THIS MONTH'S SNIP

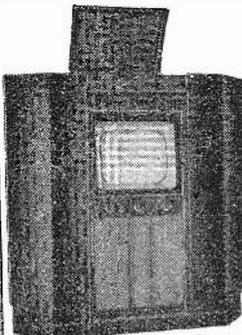

Corner Console. A massive cabinet but being corner fitted is not out of place even in a modern small living-room. Overall dimensions of this cabinet are 47in. wide x 31in. (deep to corner) x 50in. high. Made to house "15" Television, Radio Unit, Amplifier, Tape Deck, etc. Originally £18—our price, £10, plus 30/- carriage.

12/6

Post 1/-

CONSTRUCTOR'S PARCEL

Five valve superhet chassis—size 15 x 5 x 2in. with three waveband glass scale, pulley, driving head, etc.

Also **TABLE CABINET** Veneered and polished—takes the above chassis. 39/6. Post 2/6.




59/6

Post 3/6.

THREE-SPEED GRAM MOTOR
200-240 A.C. mains-operated, complete with turntable—plays 33, 45 and 78 r.p.m. records.


2/6

Post 9d.

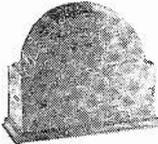

INSTRUMENT CASE

Veneered and polished—un-drilled.

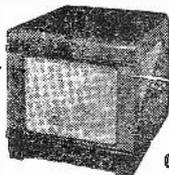


17/6

Carr. 3/6.

12" TELE-CABINET

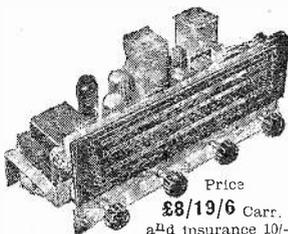Veneered and Polished—Perfect. New and unused.




Price
£8/19/6 Carr.
a^d insurance 10/- Cabinet to suit, 37/6.

5 VALVE SUPERHET

5-valve superhet, long, medium and short. Fine clear dial. Latest local valves. Ready to operate. Chassis size 15in. x 6in. x 6in.

T.V. BAND III NEWS ADD-ITA

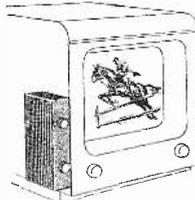

This is a ready-to-work adaptor which fixes to the side or back of your T.V. and will give you the new commercial station by the flick of a switch. You do nothing to your set, just plug in mains and aerial leads. Suitable for any T.V. Price £8/10/- or 30/- deposit and six payments of £1.

3 INSTRUMENTS FOR 25/-

THE "ELPREQ" Band III SIGNAL GENERATOR is very efficient and it:—

1. Will provide the signal for tuning to any Band III station.

2. Can be used as a grid-dip meter for checking the frequency of Band III T.V. aerials. Coils, etc.

3. Can be made to give a pattern on T.V. Receiver screen. It can be accurately calibrated with included equipment.


All the parts including valves, tuning condenser and metal chassis are available as a Kit at 25/- post free. Constructional data free with Kit or available separately price 2/6.

BUILD YOUR OWN CONVERTER

The Elpreq Band III Converter has given very satisfactory results from the experimental Beulah Hill station. It uses 2 valves, is not at all difficult to make and can be lined up with the simple 25/- instrument described above. Price for all the components, including constructional data, is £3/10/-—data available separately price 2/6.

3 SPEED RECORD PLAYER

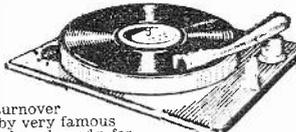3-speed record player with pick-up using the famous Acos "H G" turnover crystal—motor also by very famous maker. All on unit board ready for installation. A wonderful bargain at £5/10/-, plus 5/- carriage.



NOVELTY RADIO

Complete tunable M/L Radio with room for 3in. speaker in base. Needs only valves, speaker and batteries.



29/6

Post 2/6.

SPECIAL BARGAINS FOR CALLERS AT ALL BRANCHES

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 5, Bourne Hse., Grove Rd., Eastbourne.

42-46, Windmill Hill, Ruislip, Middx. Phone: RUISLIP 5730 Half day, Wednesday.

152-3, Fleet Street, E.C.4. Phone: CENTRAL 2833 Half day, Saturday.


89, Stroud Green Rd., Fin-bury Park, N.4. Phone: ARCHWAY 1049 Half day, Thursday.

249, Kibbura High Road, Kibbura, MAIDA VALE 4921.

10/-

Carr.

3/6.

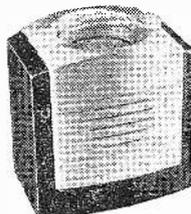

BAKELITE CABINET

Two tone with built-in handle. Note.—All have slight imperfections but these are hardly noticeable and will not affect the soundness of the set.

3/6

Post 1/-.

ALTIMETER (imperfect).


These contain aneroid barometer movement.



14/6

Post

2/6.

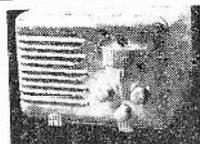

CONSTRUCTOR'S PARCEL

Bakelite cabinet, complete with dial, metal chassis and back, and plans of T.R.F.

BEETHOVEN CHASSIS

Chassis size approx. 9 1/2 x 8 1/2. First-class components. A.C. mains operation. Three wave (medium and two shorts). Complete with five valves, ready to work. Special cash-with-order price this month, £5/19/6, carriage and insurance 7/3

2/6

100ft.

Post

free.



CONNECTING WIRE

P.V.C. covered in 100 ft. coils—most colours—four coils, different colours. 9/-.

CARBON RESISTORS

50 assorted 1 and 1/2 watt resistors. Ranging between 10 ohms and 10 meg. ohms. (Our Selection.) Price 5/- pckt. 50 at 1 watt. 7/6.



BUILDING THE "SIMPLEX"?

Thousands of enthusiasts are building the "Simplex" Television, now being featured in "Practical Television." WHY NOT YOU? CONSTRUCTOR'S ENVELOPE containing full constructional details and Blue Print, additional notes and suggestions, and Query Service form, sent for ONLY 5/-. All components available ex stock as follows:

ALUMINIUM CHASSIS.—18 s.w.g. DRILLED, for VCR97 version with screens and tube holder bracket, 22/6.

TRANSFORMER.—350-0-350 v. 150 ma. 6.3 v. 5 a., 5 v. 3 a. tapped at 4 v., ONLY 37/6. (Postage 2/-)

CHOKE.—10 h. 120 ma., 10/6. (Post 1/-)

RECTIFIERS.—RM3 5/- ea., K3/40 6/- ea. VALVES.—EF50 6/6, SP61 4/-, 6SN7 9/-, 6X5 5/6, EB34 3/6, EA50 3/6.

VALVEHOLDERS.—B9G(EF50) 10d., I.O. and M.O. 6d., Diode (EA50) 6d., VCR97 2/6.

VCR97 TUBE.—Tested full screen, 42/6.

CONDENSERS.—Electrolytics 25 mfd. 25 v. 110, 16 x 8 mfd. 450 v. 5/6, 32 x 32 mfd. 450 v. 6/-, Mica, silver mica, and tubulars, 350 v. 6d. each.

POTENTIOMETERS.—All values, pre-set 1.9 each, long spindle 3/-, with switch, 4/6.

RESISTORS.—1 watt 4d., 1 watt 5d., 1 watt 6d., 1.5 k. 5 watt. 1/6.

COIL FORMERS.—1in. 8d., 1in. 10d. **SPEAKER.**—3 in. P.M. less trans., 16/6 (postage 2/-).

O/P TRANSFORMER. 5/-.
All Components Brand New and Unused. Full Price List available on request.

U.E.I. CORPN.

VALVES

1G3	6/6	7A7	8/6	5Z4	10/-
1E7	6/6	7C5	8/6	5U4	10/-
1LH4	8/-	7F7	8/6	6AC7	6/6
1LN5	8/-	7W7	8/6	6K7GT	6/6
1L4	7/6	12H8	8/6	807	7/6
2B7	8/6	12A5	6/-	ECH35	12/6
3A4	9/-	12AH7	12/6	EA50	3/6
3B7	8/6	12SG7	7/6	EBC33	8/6
6AG5	7/6	12SK7	8/6	EB34	3/6
6AK7	9/6	12SR7	7/6	EP36	6/6
6B4	7/6	28D7	7/6	EP39	6/6
6B8	7/6	32	7/6	EP50	6/6
6C8	8/-	36	7/6	Red	
6G6	6/6	50Y6	8/6	Sylvania	8/6
6H6	5/-	58	8/6	EF91	12/6
6K6	9/-	1622	11/-	EF51	15/-
6L7	7/6	1626	4/-	EK32	6/6
6N7	7/6	129A	7/6	EK32	6/6
6R5	8/6	VR150/30	8/6	EL32	7/6
6U5	8/6	VR137	5/9	EP61	4/6
6V6	8/6	KT4	8/6	MU14	10/-
6V6GT	7/6	KT2	5/-	RL37	7/6
6SA7	8/6	VP23	6/6	V870	6/6
6SG7	7/6	HL23DD	6/6	954	6/-
6SH7	7/6	TP25	8/-	955	6/-
6SJ7	8/6	IS5	8/-	9003	6/-
6SK7	7/6	IS5	8/-	9004	6/-
6SL7	9/-	1T4	8/-	931A	50/-
6SS7	7/6	1R5	8/-		

R.F. UNITS TYPE 26 and 27. For use with the R.1355 or any receiver with a 6.3 v. supply. These are the variable tuning units which use 2 valves EF54 and 1 of EC52. Type 26 covers 65-50 Mc/s (5-6 metres), and Type 27 covers 85-65 Mc/s (3.5-5.0 metres). Complete with valves, and BRAND NEW IN MAKEUP'S CARTONS. ONLY 29/6 each.

AMPLIFIER TYPE 223A, or 208A, as described in the July issue of "Practical Television" for making a TV CONVERTER. Complete with valves. ONLY 15/- (Postage, etc., 1/6).

CHASSIS OF INDICATOR 233.—Contains VCR97 C.R. Tube Holder, 11 valveholders, resistors, condensers, etc., etc. BRAND NEW. ONLY 10/- (Carriage, etc., 5/-).

POCKET VOLTMETERS.—Not ex-Govt. Read 0-15 v. and 0-300 v. A.C. or D.C. BRAND NEW & UNUSED. ONLY 18/6.

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed. Normal Primaries. 425-0-425 v., 200 ma. 6.3 v. 4 a., 6.3 v. 4 a., 5 v. 3 a., ONLY 65/-; 350 v.-0-350 v. 150 ma., 6.3 v. 5 a., 6.3 v. 3 a., 5 v. 3 a., ONLY 47/6; 250 v.-0-250 v. 100 ma., 6.3 v. 6 a., 5 v. 3 a., ONLY 37/6; 350 v.-0-350 v., 150 ma., 6.3 v. 5 a., 5 v. 3 a., ONLY 37/6; 250-0-250 v. 60 ma., 6.3 v. 3 a., 5 v. 2 a., ONLY 21/-. The above are fully shrouded, upright mounting. 5.5 kv. E.H.T. with 2 windings of 2 v. 1 a., ONLY 79/6; 7 kv. E.H.T. with 4 v. 1 a., ONLY 89/6. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

PYE 45 mc/s I.F. STRIPS.—The strip that is ready made for the London Vision Channel. Complete with 6 valves EF50 and 1 of EA50. BRAND NEW. ONLY 59/6.

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station) 5 mins. by bus from King's Cross. Cash with order, please, and print name and address clearly. Include postage as specified and on Component Orders under £2.

THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1. (Phone TERminus 7937.)

NEW!


EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY

Specially prepared sets of television parts (which you receive upon enrolment) with which we teach you, in your own home, the working of circuits and bring you easily to the point when you can construct and service a television set. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — this Practical Course is intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM 15/- A MONTH

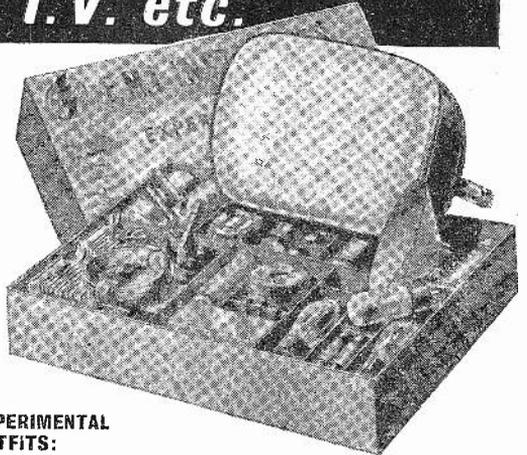A tutor is available to give individual help and guidance throughout the Course.



EXPERIMENTAL OUTFITS:

TELEVISION — Instruction and equipment for building a Television Receiver.

BEGINNER'S RADIO OUTFITS — A course in basic principles.

ADVANCED RADIO OUTFITS — Instruction and equipment from which you build a Radio Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation.

POST THIS COUPON TODAY


Please send me your FREE book on Practical Courses:
To: E.M.I. INSTITUTES, Dept. 138X, Grove Park Road, London, W.4.

NAME.....

ADDRESS.....

SUBJECT(S)..... AUG. 1

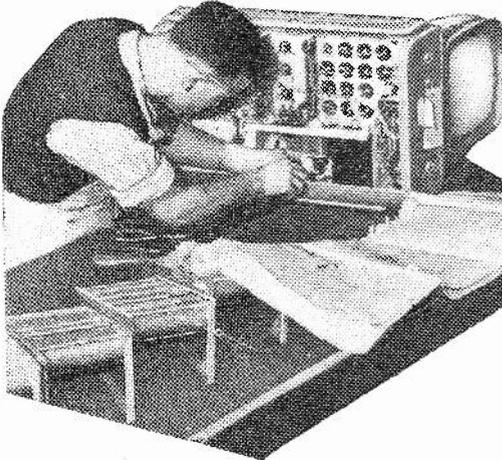PAGES FROM A TELEVISION ENGINEER'S NOTEBOOK



EFFICIENCY DIODE SYSTEMS

the secondary winding and the feed to the anode of the amplifier V1 is, therefore, by way of the secondary winding, the efficiency diode, the linearity coil L1 and the transformer primary winding, in that order: In practice the secondary of the transformer is wired so that it provides a reversed polarity to that generated by the primary flux; the anode current which flows in both windings does not, therefore, saturate the core to the extent it would if the magnetising currents were in phase.

Equivalent Circuit

Before considering the action of the efficiency diode it is best to visualise the circuit conditions at the scan coils in the absence of the valve. The scanning coils can be considered as a simple parallel-tuned circuit as shown in Fig. 2, where the resistance R of the windings is drawn in series with the inductance L, and the wiring capacity is represented as a parallel capacity C. The switch S replaces the output amplifier valve and the battery E the normal H.T. supply line. If the switch has been closed for some appreciable time, a steady D.C. will be flowing in the circuit having a value of I amp; nothing will upset this condition until the switch is opened, which in practice is equivalent to suddenly cutting off the output valve by a heavy bias.

It is fairly easy to show that the current in the circuit does not then fall evenly to zero as it would in the case of a pure resistance in place of L, C and R, but oscill-

ALTHOUGH almost universally used in the present-day television receiver, the working principles of the efficiency, or booster diode circuit, are not clear to all constructors and servicemen. When the working is understood, many obscure faults such as horizontal non-linearity, vertical shaded bands and the various forms of picture "kinking" can be remedied without great difficulty.

Consider Fig. 1 where a typical double-wound type of line transformer is used in an efficiency circuit. Although the auto-transformer method of connection is now quite common where the scan coils are fed across a section of a single winding instead of a separate secondary coil, the working principles to be discussed are, of course, unaltered. In the figure the anode of the output amplifier valve V1 is connected to one end of the primary winding of the transformer, the other end of this section being returned to the H.T. rail through a condenser C1. From the operating point of view this condenser might just as well be considered as returning to earth, and in many practical circuits it is so connected. The overwind portion of the "primary" winding is wired to the anode of the E.H.T. rectifier diode V3, whose filament is lighted from a separate, highly-insulated winding of a few turns.

The main secondary winding connects to the scan coils through a blocking condenser C3, which keeps the D.C. from passing through the windings, and a series variable inductance L2 generally referred to as the width control. The efficiency diode V2 is wired between one side of the secondary and a further condenser C2 returned to the H.T. line (or earth).

The anode voltage supply is fed in on the other side of

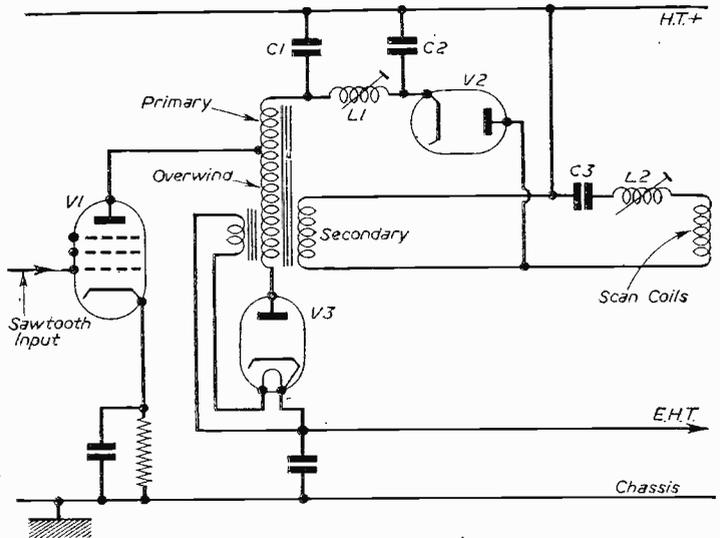


Fig. 1.—A typical efficiency diode line output circuit.

lates backwards and forwards around the circuit at a frequency given roughly by the familiar formula of

the tuned circuit, $f = \frac{1}{2\pi\sqrt{LC}}$. The oscillation is, of course, damped out quite quickly by the resistive losses and consequently appears as shown in Fig. 3(a),

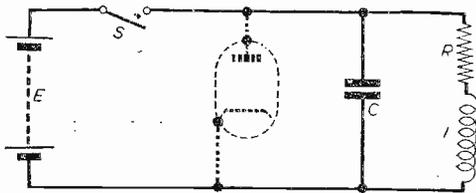


Fig. 2.—Equivalent circuit of scan coils.

becoming negligible after a very few cycles.

Over the same period the current in the inductive arm is very similar in waveform, being displaced by 90 deg. from the oscillation mentioned above, and falling over a few cycles of damped oscillation from the normal steady current value I to a very small figure. This is shown in the figure at (b). The conclusions drawn from an inspection of these two waveforms are, therefore, that when the circuit is suddenly opened: (a) the voltage across the scan coils builds up to a very high value and oscillates sinusoidally until damped out by the resistive component; (b) the current falls from its initial value of I and oscillates at the same frequency as the voltage, but leading the latter by 90 deg.; (c) the greatest negative excursion of the current occurs at the same instant as the voltage wave passes through zero on its negative swing. This point is shown at π in the figure.

If now a diode is introduced into the circuit of Fig. 2 as shown in the broken lines, wired in such a way that it becomes non-conducting for positive-going voltage, its action in the practical circuit should be quite clear. When the scan coil current swings from its initial positive value I to its maximum negative value (slightly less than I), the diode is cut off and has no effect on the circuit; when the current tries to swing upwards on the next half-cycle, however,

the diode conducts and effectively shunts the circuit with a very low resistance. The oscillation is therefore immediately absorbed.

As the switching cycle is actually identified with the flyback period of the normal scan, the scan coil current and voltage conditions in the working circuit are therefore as shown in Fig. 4, the sine and cosine "sections" of the appropriate waveforms of Fig. 3 having been transferred there. If the oscillations are not damped out at once at the end of the flyback period, a ringing occurs at the front of the next line-scan and the picture is marked into vertical bars on the left-hand side. By a proper design of the damping conditions all of the oscillation should have been damped out in the flyback period.

The capacity C of the scan coil windings may be neglected provided the resistance of both the windings and the efficiency diode are very small. The effective load resistance of the diode can be adjusted by L.I. to

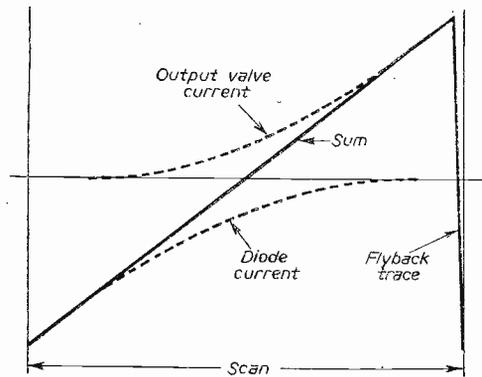


Fig. 5.—Change-over conditions during the scan.

allow the proper rate of fall of the current to match to the rise of current in the coils towards the middle of the trace which is provided by the output amplifier itself as conduction re-commences. Fig. 5 shows the take-over conditions, the output valve being brought

(Concluded on page 124)



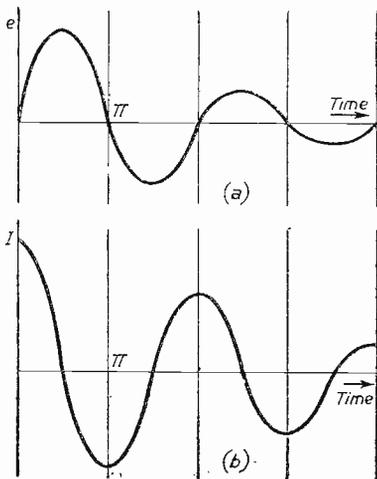


Fig. 3 (Left).—Oscillatory conditions in the scan coils in an undamped circuit. Fig. 4 (Right).—Scan coil current and voltage conditions over one scan period.

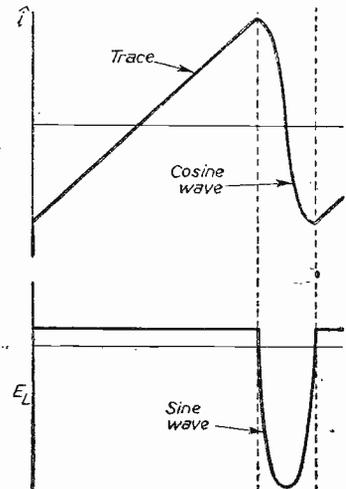

CONVERTERS

FOR BAND III

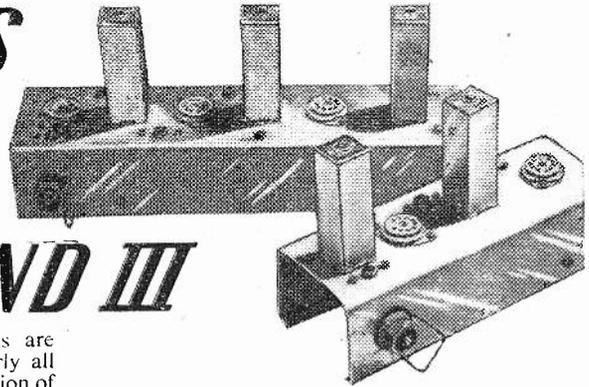

THE FIRST OF A SERIES OF CONVERTER UNITS FOR THE RECEPTION OF THE ITA

COMPLETE Band I-Band III tuner units are available commercially, but they nearly all use an intermediate frequency in the region of 35 Mc/s with the oscillator working high (that is, above the signal frequency), so that the sound I.F. is higher in frequency than the vision I.F. This mode of operation was advised by the British Radio Equipment Manufacturers' Association (B.R.E.M.A.) and the G.P.O. as a means of reducing TV and F.M. interference, which is otherwise liable to occur as the result of oscillator radiation and second-channel pick-up.

Therefore, as the older style receivers use I.F.'s of considerably lower frequency (in the order of 14 to 19 Mc/s), and in some cases use a lower than signal frequency oscillator, so that the vision I.F. is higher than the sound I.F., it is not feasible to adapt such receivers to cater for a two band tuner-unit.

The Band Converter

There is still a way left open to the would-be Band III viewer who is the owner of either a Band I superhet or T.R.F. receiver, however. That is by making use of a band converter which operates by converting the frequency of the Band III signal to the frequency of the Band I receiver. It is, of course, necessary to arrange the conversion so that the sound and vision signals are altered in frequency in their right relationship.

The block diagram at Fig. 1 shows how this may be achieved. Here it will be seen that the signals from the Band III aerial are first amplified and then fed to a mixer stage which is also in receipt of a signal produced by an internal oscillator. The frequency of the oscillator is chosen so that when the two signals are mixed a heterodyne signal equal in frequency to the difference between the incoming Band III signals and the oscillator is produced which corresponds to the acceptance frequency of the Band I receiver. In order to maintain correct relationship between the sound and vision signals the oscillator must be lower in frequency than the incoming signals. If, for example, the oscillator were made higher in frequency the converted sound signal would have a higher frequency than the converted vision signal and both would not be accepted simultaneously by the Band I receiver.

A band converter of this kind

(units which convert the Band III signals to an intermediate frequency are generally known as adaptors) operates quite successfully in practice, but it has limitations which are as well to bear in mind. Its chief shortcoming is that when used in an area of high Band I signal strength it is extremely difficult, and in some cases almost impossible, to eliminate breakthrough of the Band I signals on the Band III programme.

How true this can be may be realised readily by some viewers who find that they are well able to receive the BBC signals—and a reasonable picture—by removing the aerial from the receiver. The signal, being so high in such areas, is picked up directly by the wiring and first stages of the set itself!

It is, therefore, fairly obvious that a simple switch in the converter which disconnects and short-circuits the Band I aerial when switched to Band III is not going to be wholly successful in eliminating completely Band I breakthrough. In extreme cases of this kind it may be essential to alter the channel of the Band I receiver when using a converter.

Another source of Band I interference is due to pick up of the signals by the Band III aerial and conveyance of them through the converter. This presents much less of a problem, however, for a simple filter interposed in the Band III aerial feeder is all that is generally required. A filter of this style is shown in Fig. 2. Preferably it should be built into a thoroughly screened box and mounted as close as feasible to the converter Band III input. Its trimmer should be adjusted for minimum Band I breakthrough

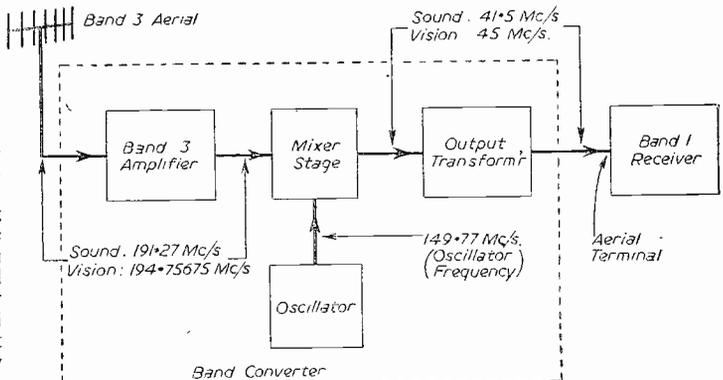


Fig. 1.—Block diagram showing arrangement of a converter.

on the Band III programme; in this respect vision breakthrough is the more troublesome as it causes patterning on the picture.

It is interesting to note, however, that extensive experiments relating to Band I breakthrough reveal that the main source is after the converter and that very little Band I signal actually gets through the converter itself.

We propose to describe the construction of four or five different models of converter so that every type of reader will be covered and at least one model should be found to suit any individual preference.

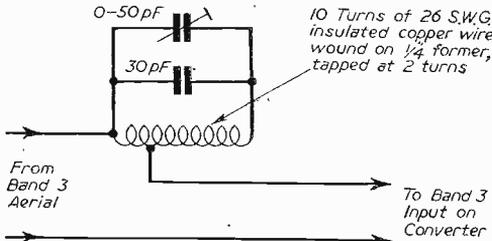


Fig. 2.—Band 1 aerial filter

It has been found that the incorporation of a power pack complicates the design unnecessarily, and accordingly these models rely for their power supply on the receiver with which they are employed, but as the H.T. requirement is quite small and most receivers have sufficient heater power available this should present no difficulty. Alternatively, a separate power pack may be used, and its construction will be described.

Band III Coils

At the outset channels 8 and 9 will be employed and coil winding details given will cover both channels

with some further spread on each side. The coils are not at all difficult to make and explicit instructions will be given for their construction.

Alignment

The Band III coils cover a wide bandwidth and there should be no difficulty with the alignment. So that the best results can be obtained detailed instructions are given for the alignment of each model and if these instructions are followed carefully no difficulties should be experienced.

SERVICE AREA MODEL No. 1

Circuit Description

Fig. 3 shows the circuit of the service area model. This model is intended for use where there is an adequate signal. This will not necessarily correspond to the same areas as the Band I transmitters; by reason of the greater attenuation of the Band III signal the service area will be much smaller and many viewers who are at the moment within the normal service area of the Band I station will find themselves in the fringe area of the Band III transmitter.

If the constructor is in any doubt as to whether or not he is in the fringe area, then he is advised to build a fringe model.

In all cases a good aerial system is recommended. This should be as efficient as possible.

The aerial circuit (Fig. 3) is designed for normal 80 ohm coaxial cable input, the feeder being fed directly into the first R.F. coil L1, which is tapped to effect matching. The tap is arranged at half a turn up the coil. If the aerial employed uses a 300 ohm balanced twin cable, then a separate coil of one complete turn must be used to terminate the feeder cable.


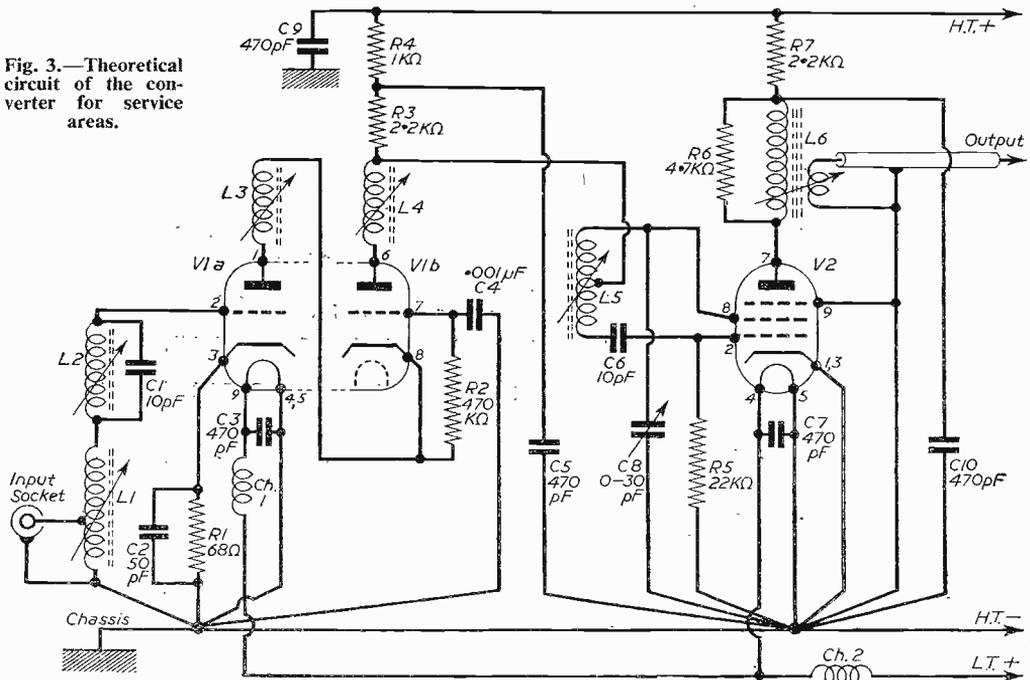


Fig. 3.—Theoretical circuit of the converter for service areas.

L2 is simply a wavetrapp tuned to the local Band I transmitter. The signal is fed to the grid of V1a, which is the first section of the ECC81 or double triode.

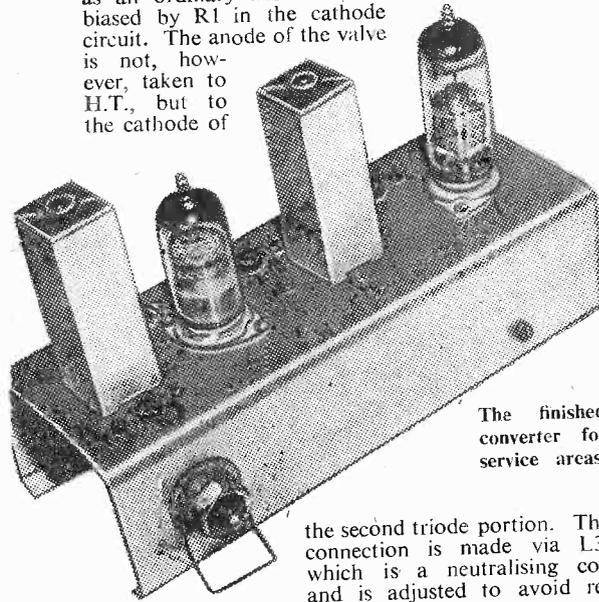It will be seen that this section of the valve acts as an ordinary triode and is biased by R1 in the cathode circuit. The anode of the valve is not, however, taken to H.T., but to the cathode of



The finished converter for service areas.

the second triode portion. The connection is made via L3, which is a neutralising coil and is adjusted to avoid re-generation.

The grid of V1b is grounded via the large capacity condenser C4, and the output of the valve is fed to the mixer via the centre tap of the oscillator coil L5. L4 is tuned to the local station and will be found to be fairly sensitive.

V2 (an EF80) is the combined oscillator and mixer. The screened grid is used in a conventional Colpits circuit, the core being tuned by an iron dust core,

C8 acting as an auxiliary. It would have been possible to have used the core solely for the tuning, but the arrangement of the circuit with additional capacitative tuning materially assists in the avoidance of oscillator drift.

The output of the mixer is taken to the I.F. coil L6, which also acts as a step-down transformer to take the output of the converter to the input of the television. This coil is made from a Haynes coil unit to obtain the greatest efficiency and screening.

It will be noted that the theoretical diagram shows the earthy end of components going to single earthing points. This feature is carried out in practice as common earthing connections do much to prevent losses and to improve stability.

The "live" side of the heaters has been decoupled by the use of small chokes and decoupling condensers.

Construction


The first step in construction is to make the chassis. This is quite a simple job as it can be made from a single aluminium sheet.

Fig. 4 shows the main dimensions of the chassis. The valve holes and holes for aerial socket and coils should be drilled before the chassis is bent into shape. The holes for the Haynes coils should be drilled as given in the diagram. Two holes are needed for the retaining bolts and the other holes for the connections.

Having drilled the holes, then the chassis can be bent into shape. This is best done by bending over the edge of a block of wood, using a second piece of wood to force the metal.

The next step is to insert the valveholders and care should be taken to ensure that they are correctly positioned so far as the pins are concerned; a tag should be inserted under the retaining bolt for the common earthing.

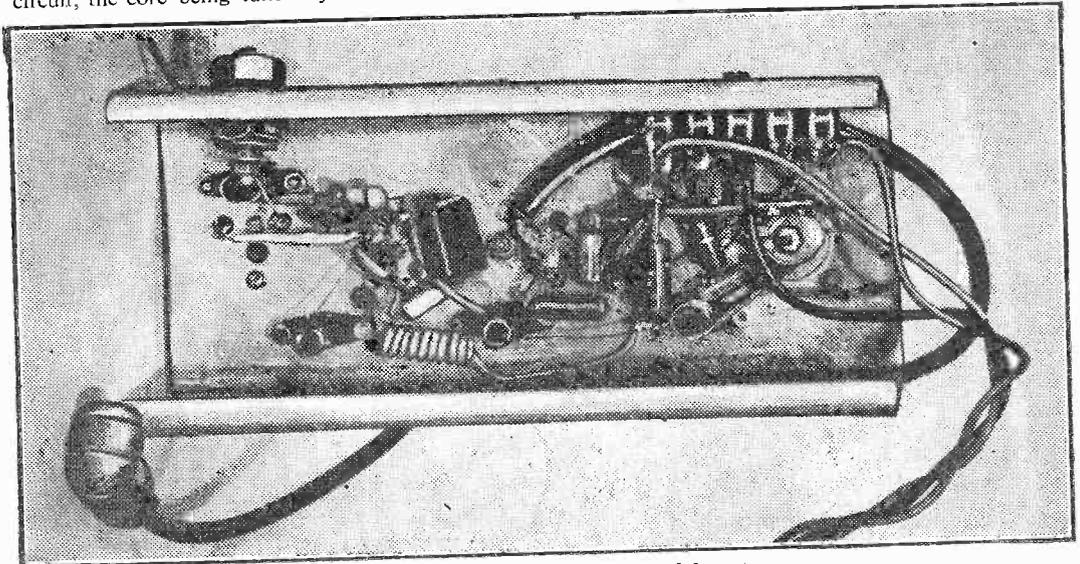After the valveholders have been fitted the formers for L1, L3, L4 and L5 should be placed in position, and the tag strip at the end of the chassis. The coils are not wound at this stage.



Underside view showing wiring and layout.

It may be necessary to reduce slightly the height of L1 coil form so that it comes directly under the input socket.

Pye aerial sockets were used in the prototype as they are inexpensive and easy to obtain; the more modern type of socket can be used if desired. The output plug for plugging into the television receiver should be of the same type already fitted.

Heater Chokes

The first step in the wiring is to wire in the heater chokes. These are very simply made by wiring 10 turns of insulated wire about 22 s.w.g. on to a former about 1/4 in. in diameter. When the coil is taken off the former the natural springiness of the wire will increase the diameter. The turns should be wound on the former so that adjacent turns touch.

Anything can be used as a temporary former, such as a knitting needle. Fig. 5 shows the method.

A long "tail" should be left on the coil and the short end wired directly to the valveholder of V1, the other end of the long tail being wired to the valveholder of V2. The second choke has the short

strip, cores, screened can and mounting screws.

L2 is a filter coil and is wound at the bottom end of the coil form. The wire used should be about 28 s.w.g., enamelled, or insulated with silk or cotton. The number of turns should be according to the frequency of the local channel. Table 1 gives the number of turns for each channel.

To make up the coil first slightly roughen the coil form where the windings are to be mounted with

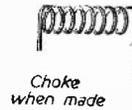
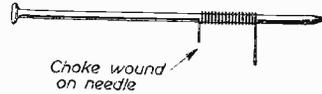


Fig. 5.—Details of the heater circuit chokes.

TABLE I.

Coil Data.				
Channel 1	11 turns
Channel 2	9 turns
Channel 3	8 turns
Channel 4	7 turns
Channel 5	6 turns

COMPONENT LIST

- Half-watt resistors and ceramic miniature condensers as in Fig. 3. Additional components :
- Two B9A valveholders.
- Four 1/4 in. diameter coil forms with cores.
- Two Haynes coil forms and cans.
- One Coaxial aerial socket.
- Chassis as in Fig. 4.
- One 5-way tag strip.
- One ECC81 valve.
- One EF80 valve.

end wired to V2 and is stood vertically underneath the tag strip.

The Haynes Coils

The Haynes coils can be wound next. Each coil unit consists of coil former, side wires, top paxolin

some fine sandpaper. This will assist in keeping the wires in position.

If the enamelled wire is used bare the end of the wire with emery and slip it through one of the small holes in the bottom of the mounting adjacent to the side wire eyelet. Wind on the required number of turns, making adjacent turns touch one another and take the other end of the wire to another convenient hole. Coil dope of the polythene variety can be used, if desired, to keep the turns neatly in position.

Now fit the top paxolin holder and mount the side wires. These are kept in position by a spot of solder at the base eyelet. Do not allow a lot of solder to accumulate on the other side of the eyelet or there may be danger of contact with the chassis.

In the case of L1 two side wires only are required: after they are in position the ends of the coil should be soldered to them so that the coil is held firmly in position.

C1 is now soldered to the side wires. It will be found that, if the condenser is mounted on the slant it will be possible to solder it directly to the side wires without it fouling the can when placed in position.

The coil form can now be fitted in position and the can bolted on.

(To be continued)

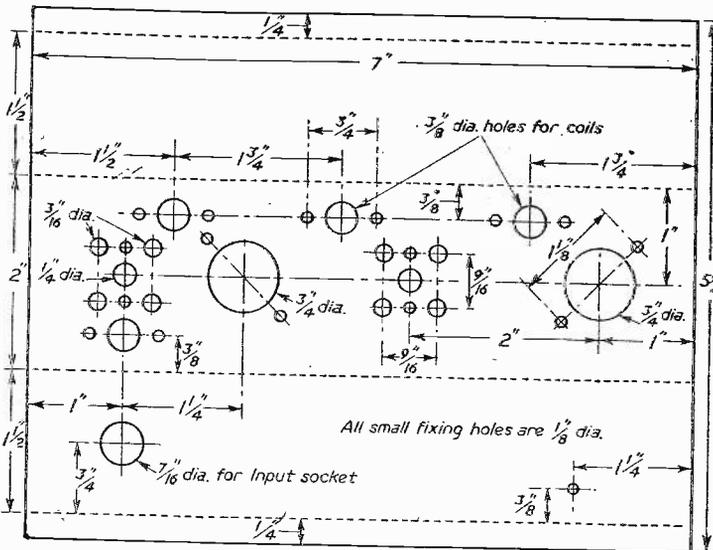


Fig. 4.—Chassis drilling and cutting data.

Amateur Chassis Construction

THE IMPORTANCE OF RIGIDITY AND SOME SUGGESTIONS FOR THE CONSTRUCTOR

By P. Green


UNDoubtedly now that commercial TV is about to commence, more home-built receivers will be used, and a few hints on one of the most important parts of a TV receiver, and one which generally gets the least consideration, i.e., the chassis, would be of assistance to many amateur constructors.

Experience has shown that in many amateur-built receivers the rigidity of the framework supporting the chassis has been neglected, and this weakness brings annoying troubles when finally setting up the receiver. With two-tier construction it is especially important to make the framework perfectly rigid, and this must be able to support the timebase, and sound and vision chassis without causing distortion to them when moved from bench to cabinet.

The chassis themselves should be free from warping due to heat. They should not be too thin, and, if possible, be reinforced on the edges. The simplest way of doing this is by bending down the edges. The bolting-down feet are best bolted to the frame independently, and made adjustable by means of slotted holes. This avoids any distortion of the frame if the mounting position is uneven.

Any distortion of the chassis would disturb the wiring and coils, and this must be avoided at all costs with short-wave receivers, as this causes trimming troubles. Therefore, be sure to make the frame and chassis strong and rigid.

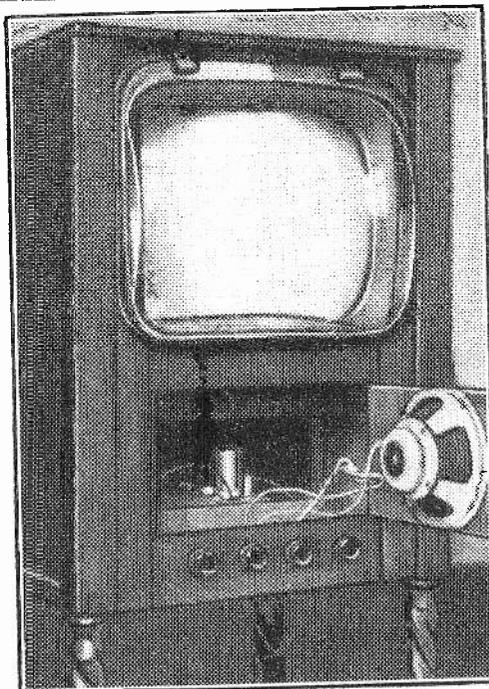Servicing of the receiver will be required at some future date. Therefore leave plenty of space, and make removable ends to boxed-in assemblies, so



that it will be possible to reach all component parts easily. A little planning at the beginning will save time if trouble starts.

Example

A good example of frame construction is shown in Fig. 1. This assembly was used for the "View Master," and it consists of $\frac{3}{4}$ in. \times $\frac{3}{4}$ in. \times $\frac{1}{8}$ in. angle uprights, tied together securely both top and bottom by removable end pieces.

The timebase chassis at the top is made from $\frac{1}{16}$ in. thick dural, and is wired up before placing in position. The removable end pieces allow for any servicing that would be required in the future.

Both the front and rear supports at the bottom, for mounting the sound and vision chassis, are $\frac{1}{16}$ in.

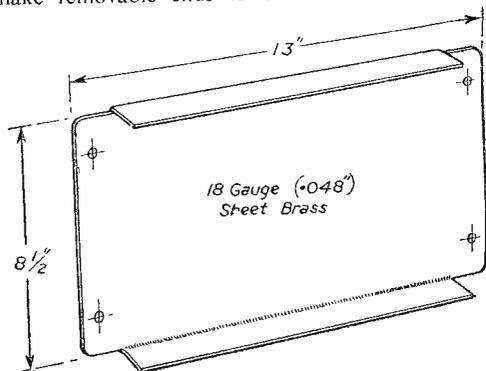


Fig. 1.—Sound and vision chassis showing edges bent down.

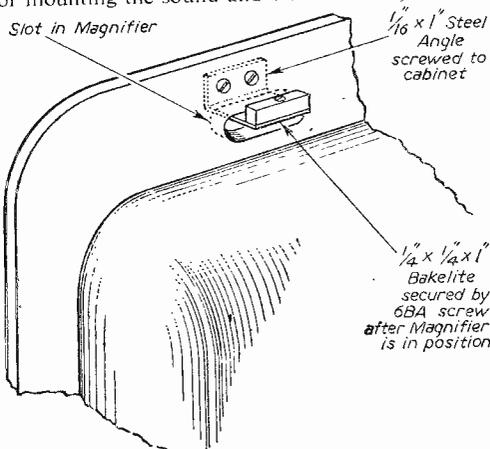


Fig. 2.—A method of hinging a magnifier.

thick dural, and on these are mounted the various controls. The removable bolting-down feet are clearly shown, and these may be mounted on either side of the cross-pieces.

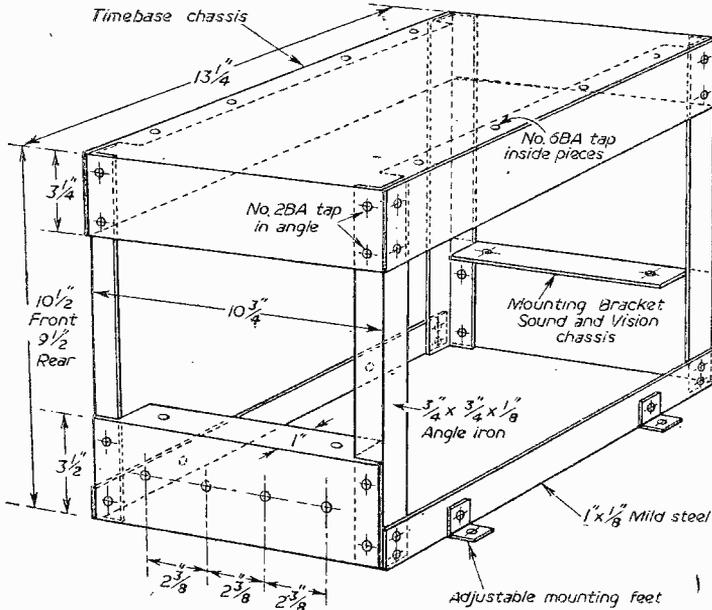


Fig. 3.—An example of frame construction.

Fig. 1 shows the sound and vision chassis, made from not less than 18 g. (048) thick brass sheet; the edges are shown bent over to give added strength. A good point is to rivet, or bolt, in various positions on the chassis, copper soldering tags, as it is easier to solder a connection to a tag than direct on to the chassis. This prevents dry joints. Soldering tags must always be securely fixed to aluminium chassis.

EFFICIENCY DIODE SYSTEMS

(Concluded from page 118)

back into conduction by proper grid-voltage control, at about one-third along the forward scan period. The grid input sawtooth is, therefore, arranged to carry the valve into conduction about one-third along the slope.

In a practical circuit, the efficiency diode does not simply shunt the coils as shown in Fig. 2, but is wired effectively in series with the anode voltage supply to the output amplifier. This connection consequently adds the diode voltage to that available on the H.T. rail proper, and increases of 100 to 200 volts are easily possible over the normal supply.

The E.H.T. for the tube anode is derived from rectification of the inductive kick which occurs when the primary current in the transformer is suddenly interrupted by the cut-off of the amplifier valve. The overwinding acts as a step-up auto-transformer in the usual way (a ratio of some 3 to 1 is usual) and a very high voltage pulse is produced at the outer end of the coil. As the pulses are sharp, the peak inverse voltage across the rectifier is barely 10 per cent. or so in excess of the D.C. developed at the cathode.

The photograph shows a "View Master" constructed with a frame and chassis as described, and has proved very successful. As will be seen, this set is fitted with a magnifier. The fixing straps were removed, and a hinged arrangement was made: a constructional view is shown in Fig. 2. This is an excellent idea, since there is no safety-glass in front of the tube, and the magnifier and tube can easily be kept free from dust. This saves periodic dismantling for cleaning, with all its hazards and disadvantages. A front opening door has been provided, and on this the speaker has been mounted. Through this door opening final adjustments can easily be made. From the speaker terminals, additional leads are taken to a jack socket, mounted on the bottom of the cabinet. To this may be connected a phone for a deaf person, or connections may be made to a tape-recorder.

An alternative housing arrangement would be to include the television receiver in a larger cabinet housing a high-quality amplifier used for record and radio reproduction. The sound side of the television set would, in this case, terminate at the sound detector, and this point would be taken to a change-over switch. The radio and pre-amp for gramophone would also go to the switch and a simple operation would then give the highest quality on radio or television or records. The only difficulty here would be in the avoidance of interaction resulting from the long leads, but I have found that standard coaxial is ideal, as well as lending itself ideally to coaxial plugs and sockets which are vibration proof.

It should be stressed again here, for the benefit of those who are not familiar with this part of the circuit, that no attempt should be made to measure the voltage on the anode of either the line timebase output valve or the efficiency diode. Although it is possible to do this with special apparatus the ordinary type of voltmeter will be destroyed, as well as the user running the risk of a severe shock from the back E.M.F. kick which arises and which is of the order of kV.

"PRACTICAL WIRELESS" AUGUST ISSUE

Now on Sale, Price 1/-

The August issue of *Practical Wireless* contains constructional details of an economical A.C. high-gain sensitive two-valve for receiving local stations.

The issue also includes "A Pre-amplifier with Scratch Filter and Tone Control," "A Crystal Marker for Communication Receivers," "Improving Amplifier Performance," "A Resistance Ratio Board," "Using Test Instruments," "Tuning the Link Coil" and "The Phase-splitting Valve."

The third article in the series on "Servicing Radio Receivers" deals with the Ferguson 325 and 326 series and the first of a short series describing the home construction of air-cored R.F. coils appears in this issue, in addition to features on world radio news and trade topics.



Whatever the pleasure
Player's complete it

*Player's
Please*

[NCC 910Q]

RADIO SUPPLY CO. (LEEDS) LTD.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/- extra under 10/-; 1/6 extra under £1; 2/- under £2. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 5d.; Trade List 6d.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v. 50 c/s Screened.

TOP SHROUDED, DROP THROUGH

- 260-0-260 v 70 ma. 6.3 v 2 a, 5 v 2 a... 16/9
- 350-0-350 v 80 ma. 6.3 v 2 a, 5 v 2 a... 18/9
- 250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a 23/9
- 350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a 23/9
- 350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a 28/9

FULLY SHROUDED UPRIGHT

- 250-0-250 v 60 ma. 6.3 v 2 a, 5 v 2 a Midget type, 21-3-3in. ... 17/6
- 250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a 26/9
- 250-0-250 v 100 ma. 6.3 v 6 a, 5 v 3 a, for HI335 Conversion ... 31/-

HI335 Conversion

- 300-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a 27/9
- 350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a 27/9
- 350-0-350 v 150 ma. 6.3 v 4 a, 0-4-5 v 3 a 31/6
- 425-0-425 v 200 ma. 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a 49/9

FILAMENT TRANSFORMERS

- All with 200-250 v 50 c/s Primaries; 6.3 v 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 9/11; 6.3 v 6 a, 17/9.

CHARGER TRANSFORMERS

- 200-250 v 0-9-15 v 11 a, 11/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 4 a, 19/9; 0-9-15 v 6 a, 22/9.

OUTPUT TRANSFORMERS

- Standard Pentode 3,000 to 3 ohms ... 4/9
- Standard Pentode 7/8,000 to 3 ohms 4/9
- Small Pentode 5,000 to 3 ohms ... 3/9

E.H.T. TRANSFORMERS 200-230-250 v

- 2,500 v 5 ma, 2-0-2 v 1.1 a, 2-0-2 v 1.1 a For VCR37, VCR37 ... 37/6

SMOOTHING CHOKES

- 250 ma 3 h 100 ohms ... 11/9
- 100 ma 10 h 200 ohms Potted ... 8/9
- 80 ma 10 h 350 ohms ... 5/6
- 60 ma 10 h 400 ohms ... 4/11

BATTERY SET CONVERTER KIT

All parts for converting any type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplied 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2V at 0.4 a to 1 a. Price including circuit 45/9. Or ready for use 8/9 extra.

TV. PREAMPLIFIER.—For Fringe Areas. Brand New. Complete with 6F13 valve. Only 22/6.

SELENIUM METAL RECTIFIERS

- DN 250 v 250 ma, 11/9; G.E.C. 300 v 250 ma, 12/9; 120 v 40 ma, 3/9; 6/12 v 1 a F.W., 5/9; 240 v 50 ma, 5/9; 6/12 v 2 a F.W., 9/9; 250 v 80 ma, 7/9.

ALL DRY RECEIVER BATTERY SUPERNEDED KIT

All parts for the construction of a unit (metal case 5 1/4" x 1 1/2") to supply Battery Portable receivers requiring 90 v. and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagram, 33/9. Or assembled and tested at 45/6.

R.S.C. 25 WATT AMPLIFIER

Push Pull Output. Quality comparable with the best in amplifiers. Includes 7 valves. Preamplifier and Tone Control Unit is incorporated. Separate Bass and Treble controls. Two separately controlled inputs for Mike and Gram, or Tape and Radio. Sensitivity is very high, making the unit suitable for use with any type of pick-up and microphone. IDEAL FOR DANCE HALLS, CLUBS, SCHOOLS, HOMES, OR LARGE AUDITORIUMS, FOR ELECTRONIC ORGAN OR GUITAR. For operation on normal Mains 200/250 v 50 c/s. Outputs 2 and 15 ohm speakers. Available in Kit form with point to point wiring diagrams and instructions at the amazingly low price of..... 9 GNS.

(Cap. 10/- Or supplied ready for use for 50/- extra, 12 months guarantee (Valves 3 months). Suitable speakers, mikes, etc. available H.P. TERMS on assembled units: Deposit 26/- and 12 mthly. p'ments. 20/-

Dept. N.,
32, THE CALLS, LEEDS, 2.

CO-AXIAL CABLE (in.)

- 75 ohms 14/36 ... 7d yd
- Twin-Screened Feeder ... 10d yd

EX-GOVT. SMOOTHING CHOKES.—

- 50 ma 5-10 h ... 8/9
- 100 ma 10 h 500 ohms Tropicalised ... 6/9
- 150 ma 10 h 150 ohms ... 11/9
- 250 ma 10 h 150 ohms ... 14/9
- 250 ma 10 h 60 ohms ... 14/9

EX-GOVT. MAINS TRANSFORMERS

- Primaries 230/250 v 50 c/s, 48 v 1 a, 9/9; 400 v C.T. 150 ma 4 v 6 a, 6.3 v 6 a, 6.3 v 0.5 a, 4 v 6 a, 4 v 3 a, 5 v 3 a, 5 v 2 a, 22/9; 300-0-300 v 120 ma 4 v 1 a, 17/6.

EX-GOVT. E.H.T. SMOOTHERS


- .02 mfd 8,000 v, 1111; .25 mfd 4,000 v (Block), 4/9; .5 mfd 3,500 v, 3/6.

BATTERY CHARGER KITS.—Consist-

ing of attractive Green Crackle Case, Transformer, F.W. Rectifier, Fuse, Fuseholder, Tag strip, Grommets, and Circuit. For mains input 200-230-250 v, 50 c/s 6 2 a, 25/9; 6 v or 12 v 2 a, 31/6; 6 v or 12 v, 4 a, 49/9; Any type assembled and tested for 6/9 extra.

R.S.C. 6v or 12v BATTERY CHARGER

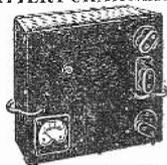For normal A.C. mains input 200-230-250 v, 50 c/s. Selector panel for 6v or 12v charging. Variable charge rate of up to 4 AMPS, Fused, and with 5 amp meter. Well ventilated metal case with attractive crackle finish. Guaranteed for 12 months, 69/6. Carr. 2/6.



BATTERY CHARGERS.—For mains

200-250 v 50 c/s. Output for charging 6 v or 12 v at 1 amp. In strong metal case. Only 19/9. Above can also be used for electric train power supply.

R.F. UNIT TYPE 26.—Brand new. Cartonned, 39/6, plus carr. 2/6.




ALL WAVE RADIOGRAM CHASSIS

THREE WAVEBANDS LATEST MULLARD
 S.W. 16 m.—50 m. ECH42, EPI4, EBC41
 M.W. 200 m.—550 m. EL41, E240.
 L.W. 500 m.—2,000 m. EL41, E240.
 12 month Guarantee, with 10in. P.M. Speaker,
 A.C. 200/250 v. W/c Switch, Short-Medium-Long-
 Grain, A.V.C. and Negative feedback, 4.2 watts.
 Chassis 13 1/2 x 5 1/2 x 2 1/2in. Glass Dial—10in. x 4 1/2in.,
 horizontal or vertical available. 3 Pilot Lamps.
 Four Knobs. Walnut or Ivory aligned and cali-
 brated Chassis isolated from mains. PRICE £10/15/0.
 Without 10in. Speaker, £9/15/0. Carr. & Ins. 4/6.
CONDENSERS.—New stock. .001 mfd. 7 kV.
 T.C.C. 5/6. 10k/0, 12.5 kV., 9/6; 2 pf. to 500 pf.
 Micra. 6d.; Tubular 500 v. .001 to .01 mfd., 9d.;
 .05, 1/1; .25, 1/6; .5, 1/9; .1/550 v., 9d.;
 .1/600 v., 1/3; .1/1,500 v., 3/8.
CERAMIC CONDENSERS.—500 v., .3 pf. to .01
 mfd., 1/-.

SILVER MICA CONDENSERS—10%, 5 pf. to 500
 pf., 1/-; 600 pf. to 3,000 pf., 1/3. DITTO 1%
 1.5 pf. to 500 pf., 1/8; 515 pf. to 1,000 pf., 2/-.
TUBULAR CAN TYPES CAN TYPES
 2/450 v. 2/3 16/500 v. 4/- 8+16/450 v. 5/-
 8/450 v. 2/3 500/12 v. 3/- 33+32/350 v. 4/6
 16/500 v. 4/- SCREW BASE 22+32/450 v. 6/8
 25/25 v. 1/9 TYPE 512 98+100/350 v. 11/6
 50/50 v. 2/- 8/500 v. 3/- 1,000+1,000/6r. 6/8
 100/25 v. 2/- 16/500 v. 4/- 1,800/6 v. 4/6
C.R.T. LOW LEAKAGE ISOLATION TRANS. Ratio
 1:1.25, 25% boost, 2 v., 10/6; 4 v., 10/8; 6.3 v.,
 10/6; 10.8 v., 10/8; 15.3 v., 10/6. Ditto mains
 primary 12/6. MAINS TYPE Multi-Output, 2-24,
 24, 24, 3 v. 2 amp., 17/6. MAINS TYPE Multi Out-
 put, 3, 4, 6.3 v., 7.3 v., 10 v., 13 v., two taps
 boost output 25% or 50%, 21/-.

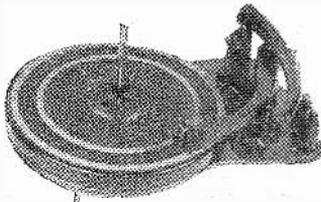COMMERCIAL T.V. CONVERTOR, BAND III.
 With Self-contained power pack, just plug in,
 full instructions supplied. An Aerialite
 Rainbow product, £9/10/-.



Brand new Plessey 3-speed Autochanger Mixer Unit
 for 7, 10 and 12in. Records. Twin Hi-Fi Xtal Head
 with Duo-point sapphire stylus. Plays 4,000 records.
 Spring mounting. Baseboard required, 15 1/2in. x
 12 1/2in. Height 5 1/2in. Depth 2in. Superb Quality.
 Bargain Price, 91 gns. post free.
SIMILAR MODEL.—3 speed Single Record unit
 with Acos 37 Turnover Head, each Sapphire Stylus
 plays 2,000 records. Starting Switch Automatically
 places Pick-up on records, 7in., 10in. or 12in. Auto
 Stop. Baseplate 12in. x 8 1/2in. Height 2 1/2in. Depth
 1 1/2in. Price £7/15/6, post free.

T.V. PRE-AMP.—Channel 1, easily modified to
 other channels or converter use. Midget chassis
 6in. x 3in. x 4 1/2in. Complete with coax. lead,
 plug and RF42 or GF13 valve. Brand new
 (boxed). Listed £3/15/- special clearance, 21/-.

SIMPLEX T.V. 12 gns. COMPLETE KIT
 of parts with punched and drilled chassis
 screens and tube supports to build 6in.
ELECTROSTATIC MODEL (less tube). All
 parts available. Separately detailed list S.A.E.
 6in. VCR97 Tested full picture, 22.

WIRE-WOUND POTS, 3 WATT. FAMOUS MAKES
 Pre-Set 5 1/2in. T.V. Type. Standard Size Pots, 2 1/2in.
 All values 25 ohms to 30 Spindle. 100 ohms to
 1K, 3/- ea. 60 K., 4/- 50 K., 5/6; 100 K., 6/6.

RADIO COMPONENT SPECIALISTS
 48 Hour Mail Order Service
 307, Whitehorse Road, West Croydon.
 Open all day. THO 1865, Wed. 1 p.m.
 Post Gilt. £1 orders post free. C.O.D. 1/6. Lists s.a.e.

7/6 VALVE SALE 7/6
 New boxed. All guaranteed
 1R5, 1R5, 1T4, 1R4, 3V4, 6AN6, 6P12,
 6BE6, 6BW6, 6K7M, 6K8, 6SA7, 6SL7, 6V6,
 6X4, 6X5, 787, 8D3, 12AX7, 807, EC91,
 6F9, 6F91, 6F92, EL32, HVK2A, PEN25,
 12Z, 17F41, AT 8/6; 5U4, 5Z4, 6AK3, 6AT6,
 6C9, 6L6, 6Q7, 6SN7, 80 ECH42, Sylvania
 6F50, MU4, AT 10/6; ECL90, 6F89, EL41.

Volume Controls 80 ohm CABLE COAX
 Long spindles. Guaranteed 1 year. All values
 Semi-air spaced Poly-
 theme insulated. 2in. dia.
 Stranded core. 4
 10,000 ohms to 2 Meg.
 No Sw. S.P.S.W. D.P.S.W.
 3/- 4/- 4/9
 EXT. SPKR. TYPE 3/-
 1in. Coax. 7d. yd.

COAX PLUGS ... 1/- **DOUBLE SOCKET** 1/-
SOCKETS ... 1/- **OUTLET BOXES** ... 3/8
BALANCED TWIN FEEDER, yd. 6d., 50 or 300 ohms.
DITTO SCREENED per yd. 9d., 80 ohms.
50 OHM COAX CABLE, 9d. per yd.
TRIMMERS.—Midget, 30, 70 pf., 9d.; 100 pf.,
 150 pf., 1/3; 250 pf., 1/6; 600 pf., 1/9.
TYANA.—Midget Soldering Iron. 200/220 v. or
 230/250 v., 14/11. Triple Three mod. with detach-
 able bench stand, 19/-. Soton 31dget Iron, 22/-.
RESISTORS.—All values: 10 ohms to 10 meg.,
 1 w., 4d.; 1 w., 6d.; 1 w., 6d.; 2 w., 1/-.
HIGH STABILITY.—1 w., 1/3; 2 w., 1/6. Preferred values
 10 ohms to 10 Meg.

B.S.E. MONARCH 3-SPEED MIXER
CHANGERS. ACOS GP37 XTAL HEADS.—
 Baseboard, 14in. x 12in. Height 5 1/2in. Brand
 New in Maker's Boxes, £9/19/6, post free.

ALADDIN FORMERS and core, 4in., 6d.; 4in., 10d.
SENTEREL RECTIFIERS.—BHT Type. Fly-
 back Voltage.—K3/25, 2 kV., 4/3; K3/40, 3.2 kV., 6/-
 K3/45, 3.6 kV., 6/6; K3/50, 4 kV., 7/3; K3/100, 8 kV.,
 12/6; K3/160, 14 kV., 18/-. MAINS TYPE.—RM
 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3,
 120 ma., 5/9; RM4, 250 v., 275 ma., 16/-.

£5/15/- CONVERT YOUR RADIO. Playing
 desk 13in. x 22in. x 7in. Walnut finish, drawer
 front with 78 r.p.m. motor, turntable and
 pick up. Press lever start places pick up on
 records 10in. or 12in. Auto Stop. Brand
 New. £5/15/-, carr. free.

T.V. AERIALS.—All channels. Indoor Inv. T., 13/6.
RECORDING TAPE. Exclusive Bargain, 1,200 ft.
 reels, High Coercitivity. Brand new, 17/6.

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.s.
AVO METERS IN STOCK
 Avo Model 7 — — — — — £19 10 0
 Avo Model 8 — — — — — 23 10 0
 Electronic Test Unit — — — — — 27 10 0
 Electronic Test Meter — — — — — 40 0 0
 AC/DC Minor — — — — — 10 10 0
 ★Cossor Oscilloscopes Model 1052 — — — — — 104 0 0
 " " " " " 1035 — — — — — 120 0 0

Full range Taylors Meters. List on request.
 Leak—TL/10 Amplifier and "Point One"
 Pre-Amplifier — — — Complete 28 7 0
 F.M. Kit of parts £5 less valves. Ref. Radio Constructor
 July, 1954.
 Jason F.M. Tuner Unit and Power Pack — — — 19 7 0
 Chapman Tuning Units — — — from 15 0 0
 Aerialite Band 3 Unit — — — — — 9 10 0

LATEST VALVE MANUALS
MULLARD, OSRAM, & BRIMAR No. 6, 5/- each,
MAZDA 2/- ea. OSRAM Part 2, 10/-, Post, 6d. ea. ex.
SCOPE SOLDERING IRON A.C./D.C. HEATING
TIME: 4 v. 6 sec. 6 v. 4 sec. 39/6.
TRANSFORMER for 200/230 v. 37/6.
 Terms C.O.D. OR CASH with order and subject to price
 alterations and being unsold.

Arthur's Est. 1919
 PROPS. ARTHUR GRAY LTD.
 OUR ONLY ADDRESS: Gray House,
 150-152 Charing Cross Road, London, W.C.2
 Temple Bar 5833/4 and 4765.
 TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."
 CABLES—"TELEGRAY, LONDON."

P.T. SIGNAL GENERATOR

Mains Transformer to specification
 21/-, post free.
 Oscillator Coil 81 kc/s
 8/6, post free.

Specialists for over 30 years in Design and
 Manufacture of all types of Radio and Television
 Transformers.

ALL MAKES REWOUND
Forrest
H. W. FORREST (TRANSFORMERS)
LTD.
 349, HASLUCKS GREEN RD., SHIRLEY,
 BIRMINGHAM. Tel.: SH1 2483.

Picture Tube Developments

SOME INTERESTING INFORMATION CONCERNING THE LATEST PICTURE TUBE PROCESSES


By "Physicist"

EXCEPT for an increase in the screen size, there has been very little change in the design and construction of television picture tubes for several years. Recently, however, some interesting developments have been disclosed which may lead to the production of better picture tubes. Some of these developments are described below.

The Flat Picture Tube

The normal television picture tube is a bulky, awkwardly shaped object which calls for a large cabinet in which to house it. How often would experimenters have wished to have a large screen picture tube of not more than a few inches in depth? It is not difficult to imagine the changes in television receiver cabinet design which such a tube would bring about: the receiver proper could then be housed in a small cabinet, and the picture tube separately housed and hung on a wall in the same manner as a picture or painting.

Impossible? The Electronics Division of Willys Motors—an American company—has, in fact, developed just such a tube, consisting of a fluorescent screen mounted between two flat glass plates which are arranged to form a shallow rectangular box (see Fig. 1). The gun which provides the electron beam is located at one corner of the box and the whole of the interior of the box is completely evacuated. To date, these new picture tubes have been

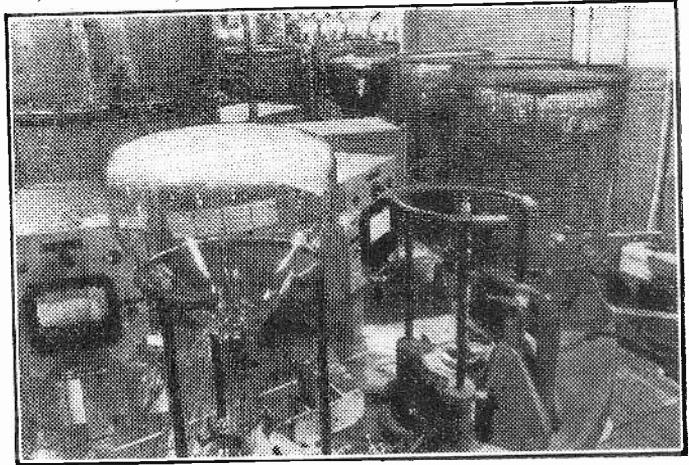

projected horizontally from the electron gun and passes immediately below a series of deflector plates, D, near the top of the box. By applying suitable voltages to these plates, the electron beam can be deflected along any one of a number of vertical paths. Another set of transparent deflector plates, D2, are mounted horizontally behind the fluorescent screen, and by adjusting the voltages on these the beam can again be deflected, this time so that it moves in a horizontal direction and impinges on the fluorescent screen. A raster can therefore be produced on the fluorescent screen by varying the voltages on the two sets of plates in a regular manner.

In addition to the improvement in the shape of the picture tube, it is also said to give a very fine spot, which makes it an ideal tube for high-definition television systems (a 2,000-line raster is claimed as a possibility). The small spot size is also advantageous for purposes in which an optical enlargement of the picture is desirable.

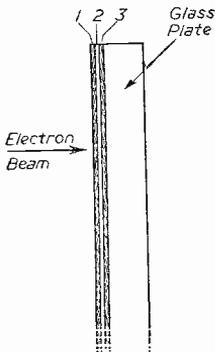


Fig. 2.—The structure of a colour television screen; 1, 2 and 3 are insulated transparent layers, each of a different colour phosphor. The depth of penetration of the electron beam is controlled by varying the potentials on the three layers.

Flat Tube Colour TV

The flat picture tube has been suggested for use in colour TV systems. For this application, the single phosphor fluorescent screen would be replaced by multilayer screen comprising three separate layers of transparent colour phosphors (see Fig. 2). The three colour layers would be electrically insulated from each other, and the three separate colour rasters which go to make up the picture would then be obtained by applying different potentials to the individual phosphor layers.

Flat Tube for Aircraft Navigation

It is also intended to use the flat picture tube in U.S. naval aircraft. Two such tubes are to be employed to provide the pilot with information re air speed, wind velocity, altitudes, etc., by displaying these figures visibly on one tube, whilst the other will show a radar map of the ground over which the aircraft is passing.

produced with a picture area equivalent to that of a normal 24in. tube, and even at this screen size the overall depth of the box is no more than 3in.!

Reference to Fig. 1 will help to make the principle of operation of this tube clear. An electron beam is

The Light Amplifier

In television picture tubes, light is produced when a beam of high velocity electrons impinges on a phosphor-coated screen. The light output from the tube is very small, so much so that it is impossible to project an image from, say, a 12in. screen on to a wall, and thus obtain a reasonably sized picture.

the phenomenon is rather obscure, but it has been suggested that a photo electric effect within the insulating layer of phosphor produces many more photons than were present in the light incident on the glass plate. Even when the potential difference across the electrodes is only 100 volts, 10 times more light is emitted than was incident on the plate.

Possibly, future television tubes might have such a light amplifier incorporated within them and in this way intense images, suitable for projection, may result. Additionally, since the device is remarkably simple in its construction and does not require a source of extra-high tension, uses such as slave screens can be envisaged. Thus, provided some light of the right wavelength from the master picture tube screen in the television set proper, can be directed on to faces of several light amplifiers, a reasonable image should be obtained from each of these (see Fig. 4).

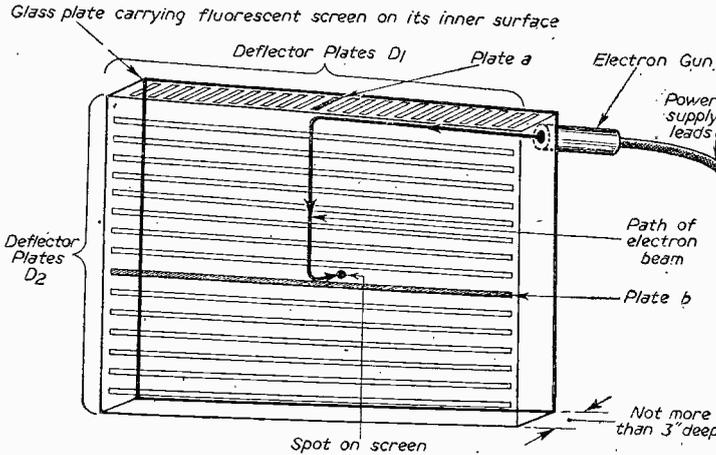


Fig. 1.—The flat picture tube. The voltages on the two sets of deflector plates, D1 and D2, are derived from timebases; the path of the beam of electrons is shown in continuous line. The two shaded deflector plates, a and b, are those which would be largely responsible for bending the beam as shown.

R.C.A. Single Screen Colour Television Tube

A new 21in. picture tube, 21AXP22, now has the phosphor dot screen deposited on the surface of the glass face instead of on a plate mounted within the envelope. Another interesting point about this tube is that the three electron beams which go to make up the colour picture are directed on to the same group of three phosphor dots each of a different colour, by three ferro-magnetic pole pieces which are built in the electron gun assembly. These internal pole pieces are energised via external pole pieces which are magnetically linked to adjustable permanent magnets. Correct colour registration is achieved by adjusting the magnets. The correct convergence of the three beams is maintained over the whole picture area by correction coils mounted on the external pole pieces and energised with a varying current derived from the scanning systems associated with the tube (see Fig. 5).

Admittedly, some progress in the direction of projection television has been made by using specially corrected lens systems and projection tubes, but the high cost of this equipment and the inferior quality of the picture that often results, does much to mitigate against its widespread adoption.

An apparatus recently demonstrated by the General Electric Research Laboratory in America might go a long way towards solving the light intensity problem in TV receiver tubes. The apparatus, known as the light amplification cell, consists essentially of a glass plate upon which a thin, transparent, electrically conducting film of titanium dioxide is evaporated (see Fig. 3). A thin insulating layer of zinc sulphide-phosphor, activated with manganese, is deposited on top of the first layer and this in turn is covered by a thick conducting layer of silver. Reference to Fig. 3 will show that the arrangement thus obtained is equivalent to a parallel plate condenser having the transparent conducting film of titanium dioxide and the layer of silver as plates and the insulating zinc sulphide layer as the dielectric.

Whenever a weak source of ultraviolet light falls on the glass plate, a faint yellow image is obtained. If, now, a D.C. potential be applied across the two conducting layers and slowly increased from a small value, the image will become many times more bright. The precise mechanism underlying

phosphor dot screen deposited on the surface of the glass face instead of on a plate mounted within the envelope. Another interesting point about this tube is that the three electron beams which go to make up the colour picture are directed on to the same group of three phosphor dots each of a different colour, by three ferro-magnetic pole pieces which are built in the electron gun assembly. These internal pole pieces are energised via external pole pieces which are magnetically linked to adjustable permanent magnets. Correct colour registration is achieved by adjusting the magnets. The correct convergence of the three beams is maintained over the whole picture area by correction coils mounted on the external pole pieces and energised with a varying current derived from the scanning systems associated with the tube (see Fig. 5).

Some idea of the composition of the colour phosphors that are used in the R.C.A. single screen system can be obtained from the information divulged in the recently published British Patent 728,179. The red emitting element is stated to be zinc selenide or zinc-cadmium selenide in which there are at least eight parts by weight of zinc to one part by weight of

(Concluded on page 131)

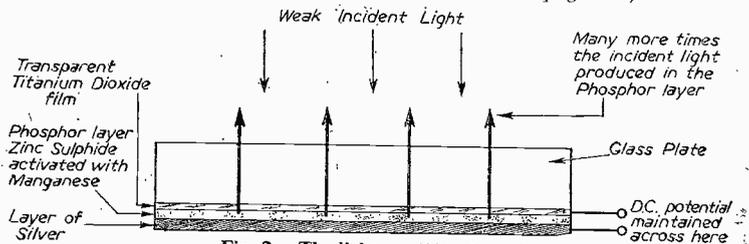


Fig. 3.—The light amplification cell.

BAND 3 T/V CONVERTER—186 Mc/s-196 Mc/s.

Complete Kit of Parts to build this most successful Unit (Mod. W/W Circuit), with drilled chassis, 2 BVA miniature valves, wound coils, and all components down to last nut and bolt for only

Supply voltages required 250 v.
20 mA H.T. 6.3 v. 1 a. l.f.

£2 5s. post free.

Power Pack Comps. To fit chassis, 30/- extra.

Prepare for Commercial T/V now. Come and see this Unit in operation. Suitable for all types T/V sets TRF or Superhet and all channels 42 Mc/s—68 Mc/s. Blueprint and circuit details, 1/6, post free.

Volume Controls

Midget Edison type. Long spindles. Guaranteed 1 year. All values 10,000 ohms to 2 Meg-ohms.
No. Sw. S.P.Sw. D.P.Sw. 3/- 4/- 4/9
COAX PLUGS ... 1/2
SOCKETS ... 1/-
COUPLER ... 1/3
OUTLET BOXES ... 4/6

80 ohm COAX CABLE

STANDARD 1/4 in. diam. Polythene insulated. GRADUATED "A" ONLY

8d. yd.

SPECIAL—Semi-air spaced polythene, 20 ohm Coax 1/4 in. diam. Stranded core. Losses cut 50%.

9d. yd.

12 yds. 8/9.

BALANCED TWIN FEEDER per yd. 6d. } 80 ohms
TWIN SCREENED FEEDER per yd. 1/0 } 80 ohms
50 OHM COAX CABLE per yd. 4in. dia.
TRIMMERS. Ceramic, 4 pt.—70 pf., 9d. 100 pf. 150 pf., 1/3; 250 pf., 1/6; 600 pf., 1/9. PHILIPS Bechive Type—2 to 8 pf. or 3 to 30 pf. 1/3 each.
RESISTORS.—Pref. values 10 ohms to 10 megohms.

CARBON WIRE WOUND

20% Type. 1/2 w. 3d. } 5 w. 25 ohms 1/3
1/2 w. 5d. } 10 w. 10,000 ohms 1/6
7 w. 9d. }
10% Type. 1/2 w. 9d. } 5 w. 15,000—
5% Type. 1/2 w. 1/- } 15 w. 33,000 1/9
1% Hi-Stab. 1/2 w. 2/- } 10 w. 10 ohms 2/3
WIRE-WOUND POT. 3w. LAB COILVERN, Etc.


Pre-set Min. T.V. Type. Knurled Slotted Knob. All values 25 ohms to 100 K. 3/- ea. 50 K. 4/- Ditto Carbon Track 50 K. to 2 Meg. 3/-.

MAINS TRANSFORMERS.—Made in our own Workshops to Top Grade spec. Fully insulated and impregnated. RADIO AND AMPLIFIER TYPE.—250 v. 30 Hz. P.W. sec. 5 v. or 6.3 v. 1 a rect. 6.3 v. 2.5 a. set Hftrs. 21/-, etc. C.R.T. HTR. ISOLATION TYPE.—Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1:1.25, 2 v. 10/6; 4 v. 10/6; 6.3 v. 10/6; 13.5 v. 10/6. Specials to order. SPECIAL TYPES.—To designers spec. simplex, 35/-; Viewmaster, 35/-; Lynx, 30/-; P/W Tape Deck, 22/6; Soundmaster, 35/-; Mullard Amp., 35/-; Osram 912, 35/-; HEATER TRANS.—Prim. 200/250 v. 6.3 v. 1 a. or v. 2.2 a. or 12 v. 15 a.; 7/6; 6.3 v. 3 a. or 5 v. 3 a. or 4 v. 4 a. 10/6.

L.F. CHOKES.—10 H. 65 ma., 5/-; 15 H. 100 ma., 10/6; 10 H. 120 ma., 10/6; 20 H. 150 ma., 15/6; Simplex, 10/6; Soundmaster, 10/6; 1/2 w. Q.R. gram., 13/6. OUTPUT TRANS.—Soundmaster 6/6; P/W TUBE CRANK, 25/-; Osram 912 sectionalised windings, 4/6; 10.0 Mftr. surplus types, standard pentode, 4/6; ditto triode, 4/6; small pentode, 3/9; Midget battery pentode (15A, 3V4, etc.), 4/6.

SOLDER SOLDERING IRONS (200-220 v. or 230-250 v.) 25 watt, instrument type, 18/6; 65 watt, Pentil 1st Type, 25/-; 65 watt, Oval Bit Type, 23/-; Comprehensive stock of spares available.
CRYSTAL DIODE.—Very sensitive. G.L.C. 2/-; VOLDERS.—Pax: 1st. Oct., 4d.; 2nd. EP50, EA50, 6d.; ENG. and AMER. 7/-; 10-pipe, Oct. 7/-; B1A CRT. 1/3. Moulded: 1st. Oct. 7d. B74, 9d.; with screening can, 1/6; B8A, B8G, B9A, 1/-; VCR87, 2/6. Ceramic: EF50, B7G, 1/-.
TAG STRIPS.—2-, or 3-way, 2d.; 4- or 5-way, 3d.; 6-way, 4d.; 8- or 10-way, 6d. etc.
TOGGLE SWITCHES EX-GOV'T.—"On-off," 9d. Esmat M core solder 60/40, 16 ad., 1d.; 18 g., 3d. yd., 3/- per lb. T.C. wire, 4s. to 22 s.w.g., 2d. yd., P.V.C. Connecting wire, 10 colours. Single or Stranded, 2d. yd.

SLEEVING.—Various colours, 1 mm. and 2 mm., 2d. yd., 3 mm. and 4 mm., 3d. yd., 6 mm., 5d. yd. NUTS, BOLTS AND WASHERS in packets 1 doz. ea. 4BA, 6HA or 8BA, 1/4 in. length, 1/- packet. Comprehensive stock all kinds bolts PK screws, Holder Tags, Grommets, etc.
FUSES.—1/4 in. all values 60 ma. to 10 a., 4d. ALUMINUM FORMERS and cores, 1/4 in., 5d.; 1/4 in., 10d. SLOW MOTION DRIVES.—Epicyclic ratio 6:1, 2/3.

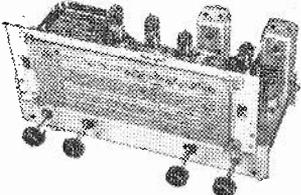

ALL WAVE RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES
S.W. 16 m.—550 m. / LATEST MIDGET
M.W. 200 m.—500 m. B.A. B.A.
L.W. 800 m.—2,400 m. SERIES.
Brand New and Guaranteed, A.C. 200/250 v. Four-Position Wavechange Switch. Short-Medium-Long-Gram. Slow Motion Tuning. Speaker and Pick-up connections. High Q iron-dust core coils, 465 kc/s I.F. Latest circuit technique, delayed A.V.C. and Negative feedback. Output approx. 4 watts. 3 ohm output transformer on chassis. Chassis size 13 1/2 x 5 1/2 x 2 1/2 in., Glass Dial—10in. x 4 1/2 in. horizontal or vertical type available, lit by 2 Pilot Lamps. Colour Black Station names, L.W. Green, M.W. Red, S.W. White. Four Knobs supplied. Walnut or Ivory to choice, aligned and calibrated. Cabinet isolated from mains. PRICE **£9.15.0**
Carriage and Insurance, 4/6.
Sin. or 10in. speakers to match available.

BARGAIN VALUE IN RECORD CHANGERS

Recommended for above chassis
B.S.R. MONARCH.—Latest Model 3 sp. Auto-Changer Mixer Unit. Famous Magidisc, 7, 10 and 12in. Record Selector. Modern Cream Styling Dual Xtal Cartridge Stylus for Hi-Fi reproduction. As used by leading manufacturers. Bargain Price.
9 1/2 Gns. post free.

NEW BOXED VALVES GUARANTEED ALL

1R5	7/6	6Q7	8/6	EP41	10/6	MU4	8/6
1R5	7/6	6SN7	9/-	EP50	11/6	PC84	12/6
1T4	7/6	6V6	7/6	Mullard	10/-	PC80	12/6
1R4	7/6	6X1	8/6	EP50	11/6	PC82	12/6
354	8/-	6X3	8/-	EP80	10/6	PL81	12/6
3V4	8/-	6X5	8/-	EP80	10/6	PL82	10/-
3D6	3/6	EA50	2/-	EP86	12/6	PL83	12/6
5Z4	8/6	EB3C1	10/6	EP91	8/6	PY80	11/-
6AM6	8/6	EB91	7/6	EL41	11/6	PY81	12/6
6AT6	8/6	EB3C3	8/6	EL84	12/6	PY82	10/-
6C610	10/6	ECC83	12/6	EM80	12/6	SP41	6/6
6HM6	3/6	EH42	10/6	EM80	12/6	SP41	6/6
6K7	6/6	ECL80	12/6	EY51	12/6	U22	8/6
6K8	9/-	EP39	7/6	EZ40	10/6	U22	12/6

SPECIAL PRICE PER SET

1R5, 1T4, 1R5 and 354 or 3V4 27/6
6K6, 6K7, 6Q7, 6V6, 5Z4 or 6X5 25/-
SPEAKER PRET.—Expanded Bronze anodised metal 8in. x 8in., 2/3; 12in. x 8in., 3/-; 12in. x 12in., 4/3; 12in. x 16in., 6/-; 24in. x 12in., 8/6, etc.
TYGAN FRET (Murphy pattern)—12in. x 12in., 2/-; 12in. x 16in., 3/-; 12in. x 24in., 4/-; etc., etc.
P.W. TUNER-UNIT (87 mc/s—105 mc/s), by Jason. —As tested and approved by Radio Constructor. Complete Kit of parts to build this modern highly successful unit, drilled chassis and J.B. dial, and all components extra, for only **£6.10.0** post free. SUPERIOR TYPE GLASS—Calibrated in Mc/s and edge lit by 2 pilot lamps, 12/6 extra. Illustrated handbook with full details, 2/-, post free.

WAVECHANGE SWITCHES.—Midget type, single wafers, 2 pole, 2-way; 3 pole 2-way, 2/6 ea.; 1 pole 4-way, 2 pole 4-way, 3 pole 4-way, 3/6 ea.; 4 pole 2-way, 4 pole 3-way, 3/6 ea. 2 WAFER TYPE.—5 pole 4-way, 6/9. SOUNDMASTER.—Set of 3 specified switches, 25/-.

CONDENSERS.—Mica, S. Mica, Ceramics. All pre-values. 3 pf. to 680 pf., 6d. ea., 5/- doz. Tubulars: 450 v. Hunts and T.C.C. 0085, 001, 005, 011, 02 ea., 1/- 350 v. 9d., 05, 1.500 v. Hunts Mold-lead, 1/-, 25 Hunts, 1/6. 5 Hunts, 1/9. 1.1,500 v. T.C.C. (Simplex), 3/6. 001, 6 v. T.C.C., 5/6. 001 12.5 kV. T.C.C., 9/6.

SILVER MICA CONDENSERS.—10%. 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3. 1% 1.5 pf. to 500 pf., 1/9. 515 pf. to 3,000 pf., 2/-.

ELECTROLYTICS ALL TYPES NEW STOCK
Tubular Wire ends 8-18/450 v. Hunts 5/-
25/25 v., 50/12 v. 1/9 8-16/500 v. B.H.C. 5/6
50/50 v., 4/500 v. 2/- 16-16/450 v. B.H.C. 5/6
8/500 v. Dub. 2/6 16-16/500 v. Dub. 6/-
8-8 500 v. Dub. 4/6 32/350 v. B.H.C. 4/-
8-8 450 v. Hunts 5/- 32-32/450 v. B.H.C. 6/6
16/450 v. B.H.C. 3/6 60/350 v. B.H.C. 6/6
16-16/450 v. T.C.C. 5/6 60-100/450 v. 11/6
25/500 v. B.H.C. 4/- 60-200/275 v. 12/6
22-22/350 v. B.H.C. 5/6 100-200/275 v. B.H.C. 12/6
32-32/500 v. Dub. 5/6 1500/6 v. B.H.C. 4/6
32-32/500 v. Dub. 5/6 1000-1000/6 v. B.H.C. 4/6
Can Types, Chps. 3d. ea. 8-8/450 v. T.C.C., 4/6 500 mfd. 12 v. 3/-

SEMI-CONDUCTOR RECTIFIERS. B.H.T. TYPE FLY-BACK VOLTAGES.—K3/25 2 kV., 4/3; K3/40 3.2 kV., 6/-; K3/45 3.6 kV., 6/6; K3/50 4 kV., 7/3; K3/100 8 kV., 12/6; K3/160 14 kV., 18/-; MAINS TYPE.—RM1, 125 v., 60 ma., 4/-; RM2, 100 ma., 4/9; RM3, 120 ma., 5/9; RM4, 250 v. 275 ma., 16/-.

ENGRAVED CONTROL KNOBS for 1/4 in. Spindles, 1 1/2 in. diam. Walnut or Ivory. Gold Filled. Standard engravings, 1/6. Plain knobs to match above, 1/4 in., 10d. ea., 1 1/2 in. dia., 8d. ea. Superior Unmarked Knobs with Gold Ring. Very stylish and becoming highly popular. Walnut or Ivory, 1 1/2 in., 1/- ea.; 1 in., 9d. ea. Pointer Knobs. Black with White Line. 6/6.

WRITE UP TYPE COILS. All ranges. 1 to 7. 2/8 ea. Osamor Q Series Coils. Slug tuned. All ranges from 3/6. Full range popular Coil Packs.

REACTION COIL.—0001, 0008, 0006 mfd., 3/6 ea. MAINS DROPPERS.—Silicone coated, with 2 slider clips. 15 amp, 1,500 ohms, 4/9; 2 amp, 1,000 ohms, 4/3; 3 amp, 1,000 ohms, 4/9; 5 amp, 700 ohms non-coated, 4/6.

LINE COIL.—250 ohms, 60 ohms per foot, 2 amp, 100 ohms per foot, 2 way, 6d. ft.; 3 way 7d. ft.

I.F. TRANSF.—465 kc/s Plessey Semi Midget HI-Q, only 6/9 pair. BERNARDS RADIO HAND-BOOKS. Comprehensive Range from 1/6 ea.

ALUMINIUM CHASSIS.—18 s.w.g. Plain, undrilled, folded 4 sides and riveted corners lattice fixing holes. Strong and soundly constructed with 2 1/2 in. slides, 1 1/2 in. x 5 in., 5/9; 1 1/2 in. x 7 in., 8/9; 1 1/2 in. x 8 in., 10/6; 1 1/2 in. x 10 in., 14/6; and 1 1/2 in. x 13 in., 16/6.

CARBON MIKE INSERT.—Superior quality type 2 1/2 in. x 1 in. Brand new and boxed only 3/6 each.

BRIMMERS.—CMI for 3a heater chassis, 3/6. CMI for 15 a., or 2 a., 2/6; C23 (Pilot Lamp), 1/6. COPPER ENAMEL WIRE.—1 lb. 1/- to 20 s.w.g., 2/-; 25 to 28 s.w.g., 2/3; 30 to 40 s.w.g., 3/6.

SWITCH CLEANER Fluid, squirt spout, 9/9 tin. TWIN GANG TUNING CONDENSERS.—375 pf., Midget, 6/6; ditto, with dust cover and trimmers, 8/6, 0005 mfd. Standard size with feet, 8/6; ditto, with trimmers, 9/6.

RECORDING TAPE.—Switch Box 1,200 ft. reels, 30/- each. Spool, 5in., 3/8; 7in., 4/3. LOSSPEAKERS P.M., 3 OHM.

Richard Allen, 5in., 16/6; 6in., Goodmans, 17/6; 7 x 4 in. Elliptical, 18/6; Sin. Goodmans, 18/6; 8in. Blac., 20/-; 10in. Plessey, 25/-; 10in. 1 a., 25/-; 12in. Plessey, 37/6.

T.R.S. RADIO COMPONENT SPECIALISTS (THO. 2188)

Now at 70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY
BIGGER PREMISES PLEASE NOTE OUR NEW AND ONLY ADDRESS BETTER BARGAINS

Buses 130A, 133, 159, 166 & 190 Send 3d. stamp for Bargain Lists Hours: 9 a.m.—6 p.m. 1 p.m. Wed. OPEN ALL DAY SAT.

N.B.—Terms C.W.O. or C.O.D. Post/Packing up to 1 lb. 6d., 1 lb. 1/-, 3 lb. 1/6, 5 lb. 2/-, 10 lb. 2/6.

HENRY'S

(RADIO LTD.)

CRYSTAL MICROPHONE INSERTS



Ideal for tape recording and amplifiers. No matching transformer required.

SPECIAL REDUCTION

1A7GT, 1N5GT	
1H5GT, 1A5GT	
(1C5GT or 1Q5GT) 40/- Set	
10 EF50 (Ex-Brand New Units) 5/- each	45/-
6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G	37/6
1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4)	27/6
TP25, HL23/DD, VP23, PEN25 (or QP25)	25/-
6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 (or 25Z6G)	37/6
12K9GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50L6GT)	37/6
12S4GT, 12SK7GT, 12SG7GT, 35Z4GT, 35L6GT (or 50L6GT)	37/6

PACKARD BELL AMPLIFIER
Brand new complete with 2817 and 6SL7GT and instruction book. 12/6. P. & P. 2/-.

CATHODE RAY TUBES
(Brand New)

VCR37 (slight cut-off) 15/-	
VCR37 guaranteed full T/V Picture ...	40/-
VCR517C, guaranteed full T/V Picture ...	35/-
VCR139A, guaranteed T/V Picture ...	35/-
3BP1, guaranteed full T/V Picture ...	30/-

Carr. & packing on all tubes. 2/-.

B.S.R. 3-SPEED AUTO-CHANGERS
These are brand new in original cartons. Plays mixed records. Cream finish. List price £16.10.0 Our Price £9.19.6.

WALKIE-TALKIE SETS TYPE 38
We are able to offer the above "38" sets complete with 5 valves, 4 VP23 and ATP4. Throat Microphone, Junction Box and Whip Aerial, all in good condition. All sets air tested and guaranteed. 50/6, carr. 5/-. (Suitable new batteries and leads, £1.2.6 set).

All Items sold separately.

"RF 26" F.M. CONVERTER UNIT 88/100 Mc/s
This well-known RF26 Unit is now adaptable for P.M. reception using 2 IF, stages and separate local Oscillator and tuned by a Muirhead graduated. Ver-

COMPONENTS OFFERED TO COMPLETE F.M. UNIT

New RF26 UNIT WITH THREE VALVES — VR137, EF54, EF54, Chassis stamped out for easy conversion	£1.15.0
--	---------

COMPLETE SET OF ALL COMPONENTS FOR CONVERSION including 2-6BA6 and EB91, tuning condenser, I.F.T's and OSC. coils, resistors and fixed condensers, plugs, wire and tag strips £4.12.5

INSTRUCTION BOOK with technical circuit and complete layout 1/6

SPECIAL OFFER OF ALL ABOVE ITEMS, INCLUDING RF26 and book £6. 5.0

postage ... 3/-

CHARGE FOR ALIGNMENT WHEN COMPLETED ... 7/6

COMPLETE SET as above and 6 valves — Aligned and ready for use £8.10.0


N.B. VOLTAGE REQUIRED 250v. 50 mA. and 6.5v. 2 amps.

VALVES — VALVES — VALVES
WE HAVE OVER 50,000 AMERICAN AND ENGLISH VALVES IN STOCK AT VERY LOW PRICES. SEND 3d. FOR 28-PAGE ILLUSTRATED CATALOGUE.

TR1196 RECEIVER
Receiver 27/73. This is a six-valve superhet receiver with 465 kc/s I.F.'s. Complete with all valves—2 EF39, 2 EK32, 2 EF38, 1 EB33. In brand new condition with full conversion data. SPECIAL OFFER 27/6 (plus 2/6 carriage.)

5, HARROW ROAD, PADDINGTON, LONDON, W.2

TEL.: PADDINGTON 1008/9, 0401.

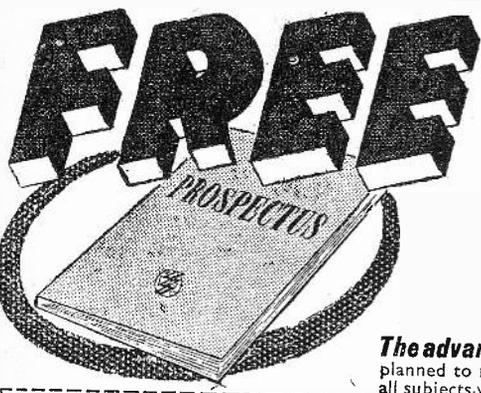

POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME
City and Guilds Grouped Certificates in Telecommunications: A.M.Brit.I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

NEW LEARN THE PRACTICAL WAY. COURSES WITH EQUIPMENT
With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

Equipment supplied upon enrolment and remains your property.
Courses from 15/- per month

POST THIS COUPON TODAY

Send without obligation your FREE book. E.M.I. INSTITUTES, Dept. 138K, 43 Grove Park Road, London, W.4.

NAME _____


ADDRESS _____

8/55 SUBJECT(S) OF INTEREST _____

EMI INSTITUTES
The only Postal College which is part of a world-wide industrial Organisation.

cadmium, plus 0.003 per cent. to 0.03 per cent. by weight of copper activator. The blue emitting phosphor is either zinc sulphide or zinc selenium


Fig. 4.—A possible arrangement of light amplifiers working as slave screens from a single master screen. There does not appear to be any reason why the amplifiers should not be housed in different rooms provided light from the master screen can be formed into an image on each slave screen.

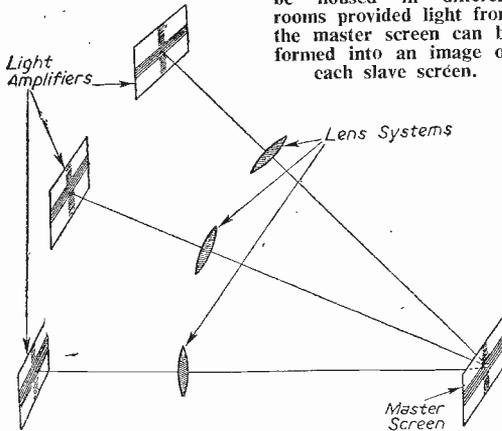

sulphide in which there are eight parts by weight of zinc to one part by weight of selenium, plus 0.005 per cent. to 0.025 per cent. by weight of a silver activator.

The green emitting phosphor is zinc silicate with 0.1 per cent. to 1.0 per cent. by weight of a manganese activator.

Fig. 5.—Schematic diagram of beam convergence adjustment on a R.C.A. tri-colour screen tube, type 21AXP22. A.—Internal pole pieces of ferromagnetic material. B.—External pole pieces assembled to correspond with the internal pole pieces. C.—permanent magnet which is adjusted as shown to give the correct beam convergence. D.—Coils energised from scanning circuits to maintain the right convergence all over the picture area. E.—Electron beam from one colour. There are three such set-ups in and around the tube neck, one for each primary colour of the picture. F.—Glass envelope.

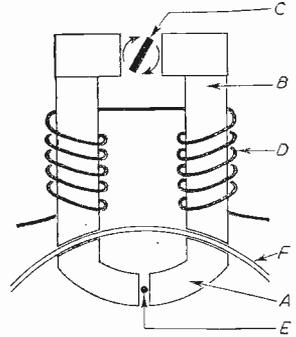

The information disclosed in this patent gives some idea of the high purity materials which must be used in the preparation of the phosphors and emphasises the small amount of activator that is usually necessary to produce fluorescence.

The information disclosed in this patent gives some idea of the high purity materials which must be used in the preparation of the phosphors and emphasises the small amount of activator that is usually necessary to produce fluorescence.

Colour TV Progress

ACCORDING to the American Industrial Correspondent of the *Financial Times*, innovations in colour television were demonstrated by leading U.S. manufacturers of TV studio equipment and receivers at the recent trade show of the National Association of Radio and Television Broadcasters. The new equipment evidenced further progress in the direction of lower-cost colour telecasting.

Chief attraction at the show was the "Vitascan" equipment made by the Allen B. Du Mont Laboratories, Inc. This permits television broadcasting in colour of live studio shows without the use of television cameras.

The Vitascan equipment emits light from a cathode-ray tube instead of a conventional lens. The beam of light from the tube scans people and objects in the studio. The light reflected from these is picked up by multiplier phototubes. The phototubes convert the light into an electric signal, which can be passed on to a regular TV transmitter.

Du Mont states that the new equipment can be operated by one person, and can also be used with regular black-and-white telecasting. It is engineered to complement the company's "Multi-Scanner," already widely in use in the United States for producing pictures in black and white or colour from films, slides or photos.

Vitascan equipment alone costs a little over \$9,000, the company states. Complete with Multi-Scanner equipment, the price is around \$32,500. Du Mont points out that the Vitascan is not adapted to use out of doors, or indoors with programmes involving a great deal of movement. For other types of pro-

grammes, it eliminates the high expenses usually associated with colour telecasts, it is claimed.

R.C.A. Transmitter

At the same show, the Radio Corporation of America unveiled a new transmitter for colour as well as black-and-white broadcasting on ultra-high-frequency channels, which costs about 25 per cent. less than similar equipment previously offered by the company.

This is a 25-kilowatt transmitter capable of a million-watt effective. It takes up no more space than a 12½-kilowatt transmitter, uses many fewer electron tubes than previous models, and offers savings of up to \$20,000 annually in studio costs, the company states.

R.C.A. states that the new equipment will be available commercially this year.

A Standard Work

TELEVISION PRINCIPLES AND PRACTICE

2nd Edition

By **F. J. CANN**

Price 25/- By post 25/8.

From **GEORGE NEWNES, LTD., Tower House, Southampton Street, Strand, W.C.2.**

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

AERIAL CONSTRUCTION HINT

SIR,—You helped me about 18 months ago with a home-made "X" aerial described in PRACTICAL TELEVISION, using a four-way by $\frac{3}{8}$ in. electric junction box. It was very satisfactory. It was, however, difficult to fix the rods tightly in the sockets, owing to the good fit of the rubber sleeves. I got over this by slitting the tubes and squeezing them in a vice, to a smaller diameter, and then expanding to full size after putting in the short metal tubes and rubber sleeves—by driving a $\frac{3}{8}$ in. dowel rod into the end of aluminium tubes, for about 6 in. This also stiffens tube. I also used rubber walking stick ferrules to protect and insulate joints.—S. RANDELL (Purley).

FOREIGN TRANSMISSIONS

SIR,—I can assure G. Little (PRACTICAL TELEVISION, July) that the interference during May definitely was French television. It was received clearly here on many evenings in May and June, when it completely blocked out the Belfast TV. station at Glencairn.

I received a steady, clean picture, with powerful sound on a Pye FVI. One evening of particularly high field strength the programme viewed was the newsreel, including helicopter ascent of Mt. Blanc and a cycle race, followed by "Magazin Feminin."

I might add that Glencairn is very weak here, but doubtless the new station with its better positioned aerial and greatly increased power, will provide more opposition in the future.—N. GRAHAM (Co. Derry).

T.R.F. RECEIVERS

SIR,—I was glad to see in the June issue that T.R.F. receivers will still be useful when commercial starts. I had been "reliably" informed by a dealer that I would have to scrap the set and it would not be possible to convert it. Reading the article, I see that you give confidence to those of us who have old sets, and you may be interested to hear that during July a neighbour built himself a converter and after telling me of his results on the test transmission, he brought it in to me to see if it would give the same good results on my set. It was connected (it has its own power supply), and with no trouble at all the Saturday morning test picture was adequate and compared with the BBC signal, with good sound and no interference or trouble whatsoever. I do not know what it will be like during the dark periods in the winter, but obviously it will not be difficult to make any slight adjustments to make up for any increased signal gain.—K. R. HARDCASTLE (Stanmore).

VIEWING IN THE DARK

SIR,—I do not agree with Mr. Dunn concerning the best way of viewing modern TV. Leaving aside all questions of eye strain, there is a very important psychological effect. First, the picture is too small to be used as any attempt at "reality." One has, therefore, to reconcile oneself to the fact that one is looking at a picture, which is a "live" reproduction of something, on the lines of the cinema screen. That being so I feel that it is best to make some attempt to make the screen look what it is, in the same manner that the cinema decorates the screen with an ornamental proscenium. One manu-

facturer attacked this problem last year, and following the idea used there I have sunk the tube face of my set about $1\frac{1}{2}$ in. behind the cabinet front, and surrounded the space between tube and cabinet front with a piece of theatrical lighting coloured plastic (deep orange). On each side of the screen I have a 15 watt pygmy bulb joined to the input to the set. When switched on these light up and give a deep orange halo to the tube and flood slightly forward. I think this makes the picture crisper and more "black and white," and at the same time gives sufficient light in the room to enable one to move about comfortably. Unfortunately, the summer months call for complete blacking out of the room.—G. F. R. TUNNEY (S.W.3).

NO MARATHON COMMENTARY


SIR,—The television broadcasts from Wimbledon this year have been extremely well handled by the BBC and all praise to them, except for one small yet annoying point.

Richard Dumbleby showed us on election night and the day after how it is possible for one man to act as compere or commentator on a TV programme for almost 24 hours practically non-stop. His was a superb piece of TV commentating, which brings me to that small, annoying point concerning the outside broadcasts from Wimbledon. Why do we have to put up with commentators who, after about 20 minutes only of occasionally coming out with remarks like: "Set point now to the Australians" or "Now it's Miss Hart to serve to Hoad," tell viewers triumphantly, "And now I am handing over to Roy So-and-so for a further commentary"? One would think theirs had been another Dumbleby marathon by the way they continually pass the microphone backwards and forwards to each other. One commentator, please, for a whole afternoon's broadcast.—H. JAMES (Bromley).

WIDER TV SCREENS

SIR,—The cinema industry began many years ago with a rectangular screen of a 4:3 ratio. A couple of years ago it was forced to alter this ratio to produce a more spectacular effect and possibly bring back the customers to the cinema. This has greatly improved motion pictures, in my opinion, and I do not see why the TV back-room boys could not develop a screen of the same ratio as that which takes films in CinemaScope. This would be advantageous in many respects. We should see more continuous play in sports broadcasts such as soccer and cricket and bigger and more enterprising plays. Of course, the old ratio screen could still be employed where necessary, just as in the cinema; tennis, for instance, would come over better on the 4:3 ratio due to the shape of the court. Indeed, one could even fit curtains to the edges of one's C.R.T. to be adjusted according to the ratio being used for each broadcast. Can you imagine Sylvia Peters saying the following: "That is the end of our tennis broadcast from Wimbledon and we are now going over to Lord's to see play in the first Test Match. As this transmission will be in Wide-screen, viewers are now advised to adjust their curtains to the full length, accordingly"? Perhaps I am looking much too far ahead.—K. N. CHANT (Hounslow).

LAFCO "E. PAYMENT" CORNER

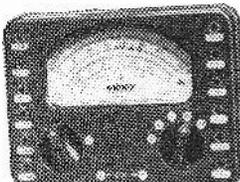


THE "METRIX" MODEL 410

—19 ranges with a sensitivity of 100 ohms per volt from 75-750 volts. A.C. and D.C. Volts 15-75-150-300-750. Resistance 0-100 ohms. Weight: 1 lb. 5 ozs. Cash Price £14.6.4 or 24/6 deposit and 8 monthly payments of 24/6.

THE "METRIX" MULTIMETER 460

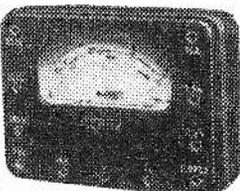with 28 ranges. Internal resistance 10,000 ohms per volt A.C. and D.C. Volts: 3-7.5-30-75-150-300-750 v. A.C. and D.C. Resistance from 0 to 2 megohms in two ranges. Dimensions: 5 1/2 in. x 4 1/4 in. x 1 1/2 in. Weight: 1 lb. 5 ozs. Cash Price £14.6.4 or 35/- deposit and 8 monthly payments of 35/-.



There is a "Metrix" Meter for YOUR needs

MODEL 400 TRANSLIP.—Currents can be measured without any volts drop. All voltages (A.C.) up to 600 v. may be measured. A.C. currents 0-10, 30, 100, 300A. Accuracy ± 5% F.S.D. £17.8.0 cash or 42/7 deposit and 8 by 42/7.
MODEL 422F.—Sensitivity 5,000 ohms per volt. A.C. and D.C. volts 1.5-5-15-50-150-500-1,500. A.C. and D.C. currents 1.5-5-15-50-150-500 mA. 1.5-5 amps. resistance, 0-2 meg. in 2 ranges. Accuracy 1.5% on D.C. 2.5% on A.C. Weighs 2 1/2 lbs., £22-14.10 cash or 55/7 deposit and 8 by 55/7.

Send stamp for leaflets of the *Metrix* range, all of which are available on easy terms.

"LAFCO" (Desk 211)

3, Corbetts Passage, Rotherhithe New Road, London, S.E.16. Telephone: BERmondsey 4341. Ext. 1.

HANNEY of BATH offers:—

VIEWMASTER.—Constructor's Envelope, 7/6; WB.103, 42/-; WB.103A, 52/6; WB.104, 15/6; WB.105, 43/6; WB.106, 25/6; WB.107, 32/6; WB.109, 33/3; WB.109.1, 2 or 3, 22/6; WB.110, 7/6; WB.111, 5/9. Westinghouse rectifiers: 14A86, 20/4; 14D36, 11/7; WX.3 and WX.6, 3/10 each; 35EH100, 29/5; 36EH150, 23/1; 30EH145, 23/6. SerrPencil Rectifiers: K3/103, 14/8; K3/50, 8/9; K3/45, 8/2. Wearite Coilssets with L.9, 30/-; Pre-amp coils, 4/- pr. State channel.

TELEKING.—Constructor's Envelope, 6/-; Coilssets, 44/6; Chassis kit, 50/-; T.C.C. kit, 47/4/3; RMA rectifier, 21/-; Allen Components, L0308, 40/-; F0395, 21/-; DC390C, 39/6; FC302, 31/-; GL16 and GL18, 7/6 each; BT314, 15/-; SC312, 21/-; AT310, 30/-; OP117, 9/-.

P.T. SUPER VISOR.—T.C.C. Condenser kit, £8/6/4; Erie resistor kit, 54/4; 5 w/v pots, 26/-; 7 Erie carbon pots, 35/-; Allen coils sets, 44/6; Allen DC/300C, 39/6; GL16 and GL18, 7/6 each; SC.312, 21/-; FC.302, 31/-; OP.117 output trans., 9/-; Denco WA/FMAI, 21/-; WA/LOT1, 42/-; Denco chassis kit, 51/6; Westinghouse WX.6, 3/10; WG4A, 7/6; LW.7, 26/8; English Electric polystyrene mask, 45/8; perspex filter, 32/8; anti-coronal ring 6/8; Tube sheath, 6/2; T.501 tube, inc. carriage and insurance, £22/14/10; Elac I78 ion trap, 5/-.

MAXI-Q (Deneco) F.M. FEEDER UNIT.—Constructor's Technical Bulletin, 1/9. P. Free. Chassis set, 7/6; Coilsset, 11/9; 10.7 Mc/s IP's, 6/- each; Ratio discrim. trans., 12/6; Phase discrim. trans., 9/-.

SUNDRIES.—1st Quality 70/80 ohm co-axial cable, by famous maker, stranded core, 9d. yard, 8/9 doz. yds. post paid. Pre-set controls, 3 watt wire-wound, all values, 10p to 30 KΩ, 3/- each; ditto, 4 watt carbon, all values 50 KΩ to 2 MΩ, 3/- each. Denco MTO.1 Test Oscillator, with valve, 75/-; Denco TPA.1 TV pre-amp with valve, 29/6; Elac ion traps, all types, 5/-; ALSO, over 100 values in close tolerance Silver Micas in stock from 1.5 Pf. to 5,000 Pf. 20,000 Erie resistors ex-stock in all preferred values and wattage.

Send S.A.E. for list. Please add 2/- postage to all orders under £3 (any excess refunded).

L. F. HANNEY,

77 LOWER BRISTOL ROAD, BATH

Tel.: 3811

VIDEO ELECTRONICS

Head office: 27, Bacon Street, London, E.1.
 Works: 16/22, Bacon Street, E.1.
 Telephones: Bishopsgate 0419/0410.

T.V. Tubes

Cheap, reliable high grade seconds and reconditioned C.R.T's, as supplied to the trade and leading Television Insurance Companies, prices from £3.

Valves

Send at once for our useful list of cheap valves which will save money, we are the cheapest in the trade.

Condensers

Electrolytics, bias, coupling, etc., etc., at giveaway prices. All types stocked.

Resistors

A fine stock of these at very low prices.

Radiograms

A few brand new salvaged table Radiograms, modern all wave, single player at £9. Cannot be repeated.

Send for stock list of speakers, valves, components and T.V. and Radio Spares.

All goods are guaranteed.

NEW-MAX ELECTRONICS LTD.

307, EDGWARE ROAD (JUST PAST THE MET.)

Tel.: PAD 5607

London's Best T.V. and Radio Bargain Store

Special Offer: T.V. Tubes—All Sizes: 9in., £4; 12in., from £4/10/-; 14in., £6; 15in., £7; 17in. from £9/10/-.

Every tube guaranteed.

Callers can see picture before purchase.

We have just completed a large purchase of used and H.P. repossessed T.V. sets—all types and all sizes—to be sold at knock-out prices. Special item: 1807 H.M.V. 10in. chassis adapted to be used with Mazda 12in. tube, £19/10/-, including tube. These chassis are very easily tuned to the Thersary Tor transmitter. Also large selection of used radios, gram chassis, instruments, amplifiers, tape recorders, etc.

BAND III CONVERTOR KIT

We can now supply a set of ready wound coils complete with circuit diagram, point to point wiring diagram, parts list, for a suitable Band III convertor for any television set.

Price 15/- post paid.

We also stock the VALRADIO and CHANNEL Band III convertors and a full range of aerials. Don't miss the start of this new exciting television service, convert your set NOW.

HOME RADIO OF MITCHAM

187, London Road, Mitcham, Surrey. MIT 3282.

"The quality component specialists."

BUILD THIS FOR 49/6



Build this exceptionally sensitive twin-fringe radio. Uses unique assembly system and can be built by anyone without any radio knowledge whatever in 45 minutes. Handsome black-crackle steel case with specially made black and gold dial with stations printed. Size of radio only 6 1/2 in. x 5 in. x 3 in. Covers all Medium and Loag waves—uses one only aldry battery which costs 7s. 9d. and lasts many months, as H.T. consumption is only 1 to 1.5 mA. Ideal for Bedroom, Garden, Holidays, etc. Many unsolicited testimonials. Mr. Norton, of Oxford, writes: *Yesterday evening on the Medium waveband, I counted 32 separate stations. I am very pleased with the set, which is well worth the money.* Sent by return. Complete Kit, 49s. 6d., post free, with full set of clear, easy-to-follow plans, or parts sold separately. C.O.D. Is. 6d. extra. Note: We stock complete range of components and valves, orders despatched C.O.D. by return. Overseas orders welcomed—Regret No C.O.D. abroad.

BRIGHTON RADIO CO. (PTD.)
69, Preston Street, Brighton, 1.


THE VALVE SPECIALISTS

Bentley Acoustic Corp. Ltd.

38, CHALCOT ROAD, N.W.1.
PRImrose 9090

1st GRADE GOODS ONLY. NO SECONDS OR REJECTS.

0Z4	6-16V6G	7-1103	2/8-KT7A1	6/8
1A3	6-16V6GT	7/8-9001	5/8-KT233	6/8
1K7	6/8-6X4	7/6-9002	5/8-LP2	4/6
1G6	6/8-6X5	6/8-9003	5/8-MH4	5/6
1H4	6-16V6	10-9006	5/8-M14	6/8
1L15	6-16V6T	15-AC/HL	6/8-M16	6/8
1LN5	6-10Z4/84	8-AC/HA	6/8-M12	6/8
1R5	7-7A7	3/8-ACVP1(7)	8-871	7/6
185	7-7AN7	11-10/6	8-N78	11/6
1T4	7-7B7	7/6-AP4	7/6-OM5	7/6
6X50	4-7C5	3-ARP3(A)	5-OM5A	10/8
2D2L	8/6-7C6	6-ATP4	3-OC5	10/8
2X2	4/6-7D8	9-ATP4	9-OD3	8/6
3A4	7/6-7H7	7/6-B309	9-OD3	8/6
3D6	2/6-7Q7	8-B319	11-PCC84	11/6
3Q5	9/6-7R7	8/8-BL63	7/6-PCP80	11/6
3S4	7-7T7	9/8-C105	6/8-PC183	12/6
3V4	7-7A8	11-CK322	6/8-PC45	6/8
4D1	3-8D2	2/6-CK525	6/8-Pen 46	7/6
5U4	8-10D1	4/6-D77	6-Pen 1340	9/6
5V4	10-10LD11	10-DA90	8/6	6/6
5X4	10-12A6	6/8-DAP91	7/6-PL81	10/6
5Y3	7/6-12AT7	13/6-D81	7/6-PL82	9/6
5Y4	10-12AT6	10/D92	6/8-PL83	12/6
5Z3	8/6-12AT7	8-D830	15/6-PM12	4/6
5Z4	8/6-12AUX7	9-DH177	8-PM12M	6/6
6A3	10/6-12AX7	9-DH142	10-PM256	6/6
6AB7	6/8-13BE6	6/8-DE150	10-PP225	7/6
6AC8	6/8-12AT7	12/6-DK32	7-PT30	9/6
6AC7	6/8-12E1	3/8-DL72	7-PS1	12/6
6AC5	6/8-12BE6	3- DL93	7/8-PS82	7/6
6AC7	12/6-12J5	6-DL94	7-QP21	7/6
6AK5	7/8-13K8	6/8-DL810	10/8-Q866/10	10/8
6AL5	6-12SC7	7/8-EL148	2- Q875/9	10/8
6AM5	6/8-12SG7	7/8-EA50	2- Q875/9	10/8
6AM6	6/8-12SJ7	8- EA76	9/8	10/8
6AQ5	6/8-12SK7	8- EAC91	9- Q8150/13	10/8
6AT6	8-12SR7	8/8-EB34	2- QV04/7	10/8
6B4	7/6-14R7	7/8-EB91	6/8-RL57	9/6
6BA6	7/8-14R7	10/6-EB41	10-RL90	9/6
6B3C	4-16A5	9/8-EC53	5/8-S16	7/6
6B4M	4/6-17Z3	10-EC70	10/6-SP47	9/6
6B55	6/8-19H1	10-EC91	7/8-SP61	2/6
6B73	6/8-19F3	8/8-EC32	10/8-TP22	3/6
6BQ4	11/6-25A6	3/8-EC33	6/8-U16	12/6
6BR7	9-25L6	8/8-ECC35	8/8-U25	12/6
6BW6	7/6-20	7/8-ECC31	9-U31	8/6
6BW7	10-33L6	8-EC32	10/6-U50	7/6
6BX6	10/6-33V4	10-EC33	10/8-U52	3/6
6C4	3/8-33Z4	3/8-EC91	7/8-U76	7/6
6C6	6/8-42	8/8-ECH42	10-U142	9/6
6C10	10-45	8/8-ECL80	10-U150	9/6
6CH6	6/8-60C5	10-EF22	9-U155	10/6
6D8	6/8-50L6	8-EP36	4/8-U154	3/6
6E6M	8-50V6	8/8-EP37A	10-U401	9/6
6E8	8-50V7	8/8-EP37	6/8-U804	9/6
6P12	6/8-38	8/8-EP41	9-UCH42	9/6
6P17	9/6-61BT	12/6-EP50(A)	8-UCH81	12/6
6P32	3/8-61RPT	15-EP50(E)	5-UP41	3/6
6P33	9/6-623DPT	10-EP54	5-UP85	12/6
6R6	6/8-62TH	10-EP71	10/8-U141	9/6
6H6G	2/6-62VP	9-EP80	10-U146	11/6
6H6M	3/8-64ML6	10/6-EP91	6/8-U19	9/6
6J5G	5-66KC	9-RL32	6/8-UY41	9/6
6J5M	6-67PT	10/6-EL41	10/8-V986	6/6
6J6	7/6-72	4/8-EL84	11-V1367	2/6
6J7C	8-73	3/8-EL91	6/8-VLS492A	2/8
6JGT	5/6-76	7-EM34	10/6	9/6
6K6	7-77	8-EP51	11-VMP40	10/6
6K7E	5-78	8/8-EP86	12-VP27	8/6
6K74T	5/8-80	8/8-EP91	7/8-VP47	8/6
6K77	8-83	8/8-EP91	9-VP18K	8/6
6K8G	8-83A2	10/6-KZ41	9-VP25	8/6
6K8GT	8/8-121VP	9-EP30	5-VR52	5/6
6L7	7/6-141TH	10-HL2	3-VP501	6/6
6N7	7/8-210LF	3-HL3C	7/8-VT111	3/6
6N7M	8-135G	4-HL25	5/8-VT133	4/6
6O7	7/6-301	10-HL25D1	10/8	11/6
6R7	8-451PT	10/6	6/8-W150	9/6
68A7	8-80L	7/6-HL41	7/8-X66	7/6
68C7	10/8-808	25-HL120	6/8-X142	9/6
68G7	6/8-822	25-VR2	7/8-X50	10/6
68H7	8-85	10/8-VR2A	7/8-NPW10	6/8
68J7	8-956	3/8-KBC32	8/8-NPY10	6/8
68K7	9-1203	7/6-KP25	9-XPY12	6/6
68L7	8-162A	7-RL25	9-KH1.5	4/6
68M7	8-2051	10/8-KT2	5/8	6/6
68N7	8/8-4022AR	3/8-KT41	7-X841.5	4/6
68S7	7/6-4033X	7/8-KT74	12/6	7/6
615G(UK)	7/6-4074B	2/8-KTW61	7-777	6/6
615G(U)	7/6-5763	9/8-KTW62	5-2713	10/6

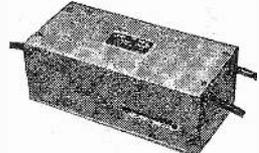

CONVERTOR TYPE 26.
For conversion from channel 3 to channel 1, complete with self contained power supply unit and totally enclosed in a handsome, well finished steel case. Price complete£11-17-0

Also available in chassis form less H.T. supply but including mains operated heater supply for inclusion in receivers. Price complete£8-0-0

CONVERTOR TYPE AC/4
For weak signal areas. Price complete£15-15-0

(Leaflets on request)

SPENCER-WEST
QUAY WORKS,
Gt. YARMOUTH.
Tel. : 3009. Grams : Spencer-West, Gt. Yarmouth.

LYONS RADIO Ltd.

3, GOLDHAWK ROAD, Dept. M.T., SHEPHERDS BUSH, LONDON, W.12.
Telephone : SHEpherds Bush 1792

POWER UNITS TYPE 285. These will make a fine TV. and general purpose power pack. Input 230 v. 50 cps. A.C. mains. At Output: F.H.T. 2,000 v. smoothed D.C. at 5 mA. H.T. 350 v. smoothed D.C. at 150 mA. I.T. 6.3 v. at 5 A. and 6.3 v. at 10 A. Soudly constructed with fully impregnated transformers and chokes, metal cased paper condensers. (No electrolytics), etc. Fitted with valves VR91, 5U8 and VU39. Input/output plugs, fuse holders and on/off switch fitted to front panel. Supplied with circuit diagram, in good condition and working order. PRICE ONLY 69/6.

RESIN CORED SOLDER. By famous maker, we have purchased a large quantity of this 6-cored radio solder which enables us to offer it at greatly reduced prices. Sold in economical coils of 4 ozs. at 3/9; 8 ozs., at 7/-; 1 lb. at 12/9 post paid.

VIBRATORS. Standard 4-pin non sync. type. For 12 v. operation, 8/6. For 24 v. operation, 5/-.

POWER UNITS TYPE 16. Contain rotary converter with separately wound field. Input 24 v. D.C. Output: 300 v. D.C. at 200 mA. 150 v. D.C. at 15 mA. and 14.5 v. D.C. at 4.9 A. Fitted with input and output filters, carbon pile voltage regulator, starter relay, etc. Can be operated from 12 v. D.C. applied to 14.5 v. section and with field windg. connected. Output voltages rather a little lower than rated. Housed in metal cases 12 x 8 x 5 ins. In used good condition. PRICE ONLY 12/6, carriage 6/-.

OPPORTUNITIES IN TELEVISION

144 pages
Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.


We Guarantee "NO PASS—NO FEE"
If you are earning less than £15 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

WRITE TODAY!
British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane,
Kensington, W.8.



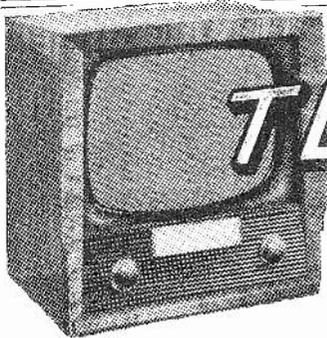Crystal Diodes. CG68, GEX4, M1, OAT7, 7/- each. All boxed and guaranteed. Post 6d. each. Same day service. Shop hours 8.30 to 5.30, Sats. 1 pm. Write not 'phone or wire that urgent order for immediate despatch C.O.D. ?



TELENEWS

Television Licences

THE following statement shows the approximate number of television licences in force at the end of May, 1955. The grand total of sound and television licences was 14,000,795.

Region	Number
London Postal	1,139,192
Home Counties	504,271
Midland	839,939
North Eastern	674,495
North Western	674,603
South Western	260,298
Wales and Border Counties	252,827
Total England and Wales	4,345,625
Scotland	253,328
Northern Ireland	24,964
Grand Total	4,623,917

Commercial Equipment Order

ASSOCIATED-REDIFFUSION, LTD., have ordered most of their studio and outside broadcast equipment from Marconi's Wireless Telegraph Co., Ltd., through their technical advisers, Central Rediffusion Services, Ltd.

Complete installations for three three-camera studios, one two-camera studio and two complete three-camera TV outside broadcast vehicles are included in the initial order.

TV Production Increase

THE General Electric Co., Ltd., is to transfer production of domestic radio sets from its Spon Street works to another Coventry factory so that the whole of the space previously occupied can be devoted to the manufacture of television receivers.

It is calculated that potential output will be increased by more than 50 per cent. in this way.

BBC Reorganisation

MR. H. J. G. GRISEWOOD has been designated Chief Assistant to the Director-General, with the personal rank of Director. The

post of Director of the Spoken Word has been abolished and the Talks Division now comes under the Director of Sound Broadcasting.

Blaen Plwy Aerial

THE BBC has placed a contract with the J. L. Eve Construction Co., Ltd., of London, S.W.19, for the design, supply and erection of the 560ft. stayed mast for the television and V.H.F. station to be built at Blaen Plwy, Cardiganshire, to serve the coastal areas of West Wales.

Mullard Reference Book

MULLARD dealers have been issued with a 36-page booklet entitled "Television Receivers Equipped with Mullard Valves." This booklet contains a table giving lists of receivers grouped according to the makers' names. Against each receiver is given its valve complement. Another set of tables lists Mullard valves and tubes and against each type is given a list of the sets in which it is used.

Industrial Television

MARCONI industrial television equipment was demonstrated recently to officials of the British Electricity Authority at the BEA power station, Little Barford, Hunts.

Three cameras were applied to give close-up viewing of furnace flame conditions, a boiler water-level gauge and a feed pump.


Alternative Service's Opening

THE ITA has confirmed that its London transmitter at South Norwood Hill, Croydon, will start high-power test transmissions during the first half of September and regular service will begin on Thursday, September 22nd.


Colour on Tape

A RECORDING on tape of a colour television broadcast was transmitted for the first time in America recently.

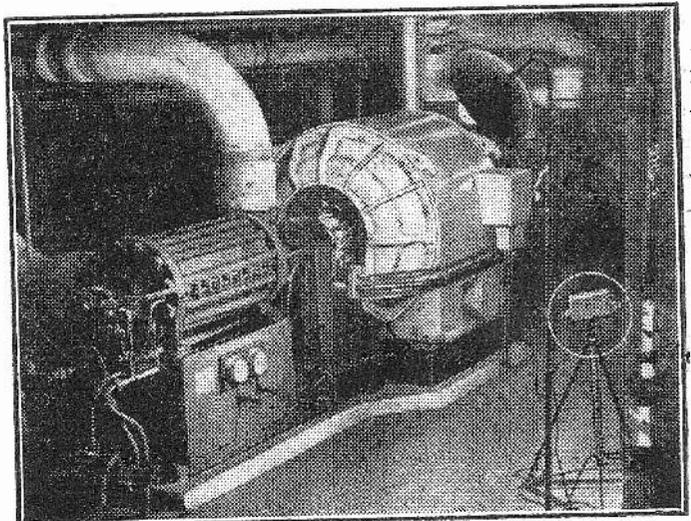The transmission originated from the N.B.C. studios in New York and was relayed over a closed circuit to St. Paul, Minnesota.



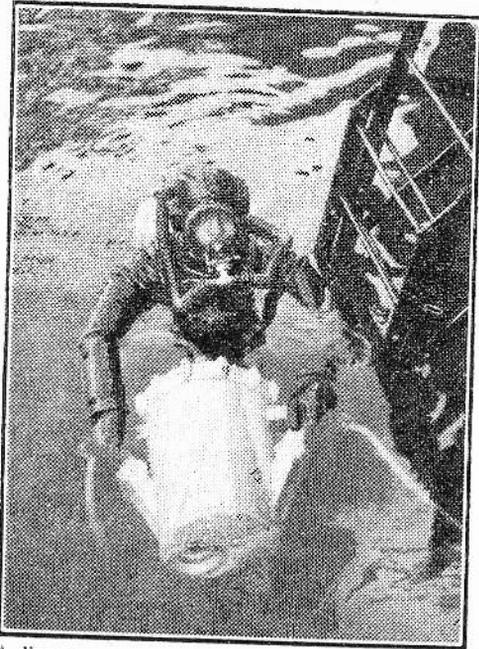A white circle indicates the small camera (right) mounted for observing a feed-pump at the B.E.A. power station. (See "Industrial Television.")



A diver prepares to submerge to test equipment to be used on the Arctic patrol. (See "Underwater Television.")

Suppressors to be Fitted

FLUORESCENT street lighting in Crawley, Sussex, is causing interference to radio and television reception in the town.

Following complaints, suppressors are to be fitted to the lamps.

Link With Europe

THE G.P.O. has informed the BBC that the first section of the permanent vision link between London and the Continent, ordered last January, will be completed in September.

This section consists of a two-way coaxial cable circuit between London and St. Margarets Bay.

Sweden Begin Service

SWEDEN expects to commence operating her own television service on July 1st, 1956, with approximately 50 transmitting stations.

The television committee plan-

ning the service anticipates that within 14 years of the inauguration of a regular service there will be nearly a million licence-holders.

Interference Danger

IN his inaugural speech as president of the Radio Industries' Club, Mr. Harold Bishop, director of BBC Technical Services, emphasised the danger in over-simplifying the design of television receivers. This could result in interference from line timebases, he explained.

Advertising Shorts

JACK TRAIN is making a series of short advertising films for Currys radio shops.

advertising films for Currys radio shops.

Underwater Television

WHEN the Canadian Navy Arctic patrol vessel *Labrador* begins northern operations this summer in the sub-Arctic she will use the first underwater television equipment ever used in Canada.

The gear will be employed for surveys and underwater beach approaches, as well as for the study of the behaviour of divers in the cold waters of the Arctic region.

Name Change

IT is learned that products previously sold under the names of E.M.I. Factories, Ltd., E.M.I. Engineering Development, Ltd., and E.M.I. Research Laboratories, Ltd., are now being handled by E.M.I. Electronics, Ltd., of Blyth Road, Hayes, Middlesex.

Advertising by Post

IN an effort to boost the popularity of television in Belgium, the postal authorities are having letters franked with a stamp which reads: "Be Televiewers."

From Effects to Producing

FEW viewers who saw the third edition of "The Ted Ray Show" on July 16th will realise that the show's producer, George Inns, was responsible for the sound effects in the first play ever to be televised—"The Man with a Flower in his Mouth."

Theatre Purchased

GRAMADA LIMITED, one of the contractors for commercial television, has bought the Embassy Theatre, Swiss Cottage, London.

After redecoration and repairs Granada will probably use the premises for theatrical productions, and dramas may also be filmed there for transmission from the Granada Northern TV station.

Sir Alexander Korda

FOR its first showing in America Sir Alexander Korda's film, "Richard III," will earn for him a fee of 500,000 dollars.

The National Broadcasting Company is to pay this amount to show the film on television.

Colour Demonstration

STUDENTS at Bradford Technical College recently attended a demonstration of large-screen colour television. This was incorporated in the last lecture in a series entitled "Modern Developments in Radio and Television."

Isle of Man Broadcasting

THE BBC has been in consultation with His Excellency the Lieutenant-Governor of the Isle of Man and the Lt.-Governor's Advisory Committee on Broadcasting concerning the development of television and sound broadcasting for the island but, as yet, no definite plans have been announced.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.



QUALITY TELEVISION COMPONENTS

SCANNING COILS
6/10 kV. R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS
LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

VALVES

SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. midget. 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, 7/3; any 4 for 26/6.

1A7GT 6K25 11/9 35Z5GT EL31 6/6

1C5GT 6L6G 10/8 6EY8 12/6

1D5 11/6 6P25 14/6 80 8/6 F22 9/6

1H5GT 6Q7GT 9/6 1B36 16/6 KT63 7/6

1N5GT 11/6 6SN7GT CL33 12/6 KT66 11/6

1R5 7/6 6U4GT 8/6 D1 3/6 MUI4 8/6

1S5 7/3 6V6G 7/6 17- DAC32 P61 3/6

1T4 7/3 6V6GT 7/6 DCC9010 6 PCF80 10/6

3A5 10/6 6X4 7/6 DF33 11/6 PL33 11/6

3Q5GT 11/6 6X5GT 6/9 DH77 8/6 PL41 11/6

3S4 7/3 7B7 8/6 DK32 11/6 PL32 9/6

3V4 7/6 7C5 8/6 DK92 7/6 PL83 12/6

5U4G 8/6 7C8 8/6 DL33 11/6 PY80 9/6

5Y3GT 7/9 7H7 7/6 DL35 11/6 PY81 10/6

5Z4G 9/6 7S7 8/6 EB91 6/9 PY32 7/9

6AB8 7/6 7Y4 8/6 EPC33 7/6 PZ30 17/6

6AL5 6/9 10C1 12/6 EBC41 10/6 T41 13/6

6AM5 6/6 10F1 10/6 EBF80 U24 17/6

6AM6 6/3 10P13 10/6 U25 12/6

6AT6 8/6 10P14 12/6 ECC81 9/6 U50 7/9

6BA6 8/6 12AT7 9/6 ECC83 12/6

6BE6 6/6 12AU7 9/6 U281 10/6

6BH6 6/6 12J7GT 9/6 ECC91 7/6 U404 9/6

6BW6 6/6 10/6 ECH35 UBC41 9/6

6GB6 7/6 12K7GT 9/6 UBF80 10/6

6BW7 7/6 9/6 ECH42 10/6 UCH42 9/6

6BX6 7/6 12K6GT 9/6 ECH81 10/6 U41 8/6

6C4 7/6 10/6 ECL30 9/6 UF41 8/6

6C9 8/6 12Q7GT 9/6 EP39 6/6 UF42 13/6

6FG6 7/6 9/6 EP41 8/6 UL41 9/9

6F14 12/6 12Z3 7/6 EP50 7/6 U06 10/6

6J6 7/6 20P2 11/6 EP80 10/6 U08 17/6

6J7GT 7/6 20P1 15/6 EP86 17/6 UY41 9/6

6K7C 6/6 25Z4G 9/6 EP91 6/3 W77 5/6

6K7GT 6/6 25Z5 8/6 EP92 5/6 Y63 7/6

6K8G 8/6 35L6GT8 6/6 EL38 22/6 Z66 21/6

6K8GT 9/6 35Z4GT8 6/6 EL41 11/6 Z77 6/3

Postage 4d. per valve extra.

READERS RADIO
24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

IT'S 60% CHEAPER!!
to construct your own aerial, whether
TELEVISION or YAGI

Write for our catalogue, illustrating all fittings, prices, etc. Included in the range we offer Alloy Masts, Insulators, Reflector and Director rod holders, Mast head fittings, together with formulae, useful construction hints for designing your own aerial, etc.

Send 9d. in stamps to cover the cost of postage and catalogue to :-



FIRST-CLASS TELEVISION and RADIO COURSES . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M. Brit. I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.C. (Eng.), A. M. I. P. E., A. M. I. Mech. E., Draughtsmanship (all branches),** etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER

150,000 SUCCESSES.

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

COVENTRY RADIO

189, DUNSTABLE ROAD LUTON, BEDS.

Phone : Luton 2677

The Quality Component Specialists offer you Kits of Parts for the following :-

- Osram "912" Amplifier ... 3/6
- Mullard 10-watt Amplifier ... 2/6

- The Coventry
 - 2-watt Amplifier ... 1/-
 - 4-watt Amplifier ... 1/-
 - 6-watt Quality Amplifier ... 1/-
- The Coventry A.M. Tuner Unit 1/-
- Denco F.M. Tuner Unit ... 1/6

Complete Component Price Lists will be supplied with each Manual.

Have you had a copy of our 1954/5 60-page illustrated Component Catalogue, price 1/- plus 3d. postage?

TELEKIT SUPPLY

MAIL ORDER DEPT.
Chantry Lane, Bromley, Kent.
Please mention P.T.V. and enclose 6d. postage

VALVES GUARANTEED

OZ4	4/-	6BW6	6/6	15D2	4/-
ILN5 (soiled)	3/-	6CH6	6/6	EP50	5/-
		6J5	5/-	W77	5/-
I55	6/-	6V6	7/-	1B24	35/-
10U5	6/-	6X4	6/6	6AK6	6/6
5763	8/-	6X5	7/-	6AQ5	8/-
6A8	8/-	7D5	6/-	6U5	6/-
6AL5	6/-	7D8	6/-	12AT6	7/6
6AM6	6/-	7H7	6/-	60C5	8/-
6AT6	7/6	9D2	5/-	TTII	6/-
6B8	6/-	11D3	6/-	12BH7	7/-
6BA6	6/-	12BE6	6/6	6BH6	6/-
6BE6	6/-	12AG 1299	6/6	6K7G	5/-
6BT7	8/6	(soiled) 5/-		7B6	9/-

COMPONENTS FOR F.M., RADIO, T.V., RADIO CONTROL, ETC., AVAILABLE AT 104, HIGH ST., BECKENHAM, KENT BEC 3720


RADIO AND TELEVISION COMPONENTS

All parts in stock for: **Viewmaster, Soundmaster, Teleking, etc.** Easy Terms available. 2d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO.
FINSTHWAITHE, NEWBY BRIDGE, ULVERSTON, LANCs.

R.F. OSC. E.H.T. COILS

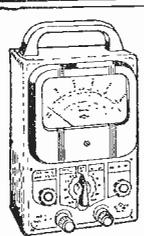TYPE "D" 2-9 kV 25/- WITH RECTIFIER ASSEMBLED 54/-
TYPE "F" 9-14 kV 30/- WITH RECTIFIER ASSEMBLED 59/-
For use with valve or metal rectifier. Current available, 1-2 mA. Ideal for oscilloscopes and television. Dimensions 3 1/2" x 1 1/2" dia. Wave wound winding. Complete with circuit. Terms: C.W.O. Post orders only.
THE WATSON WATCH CO.,
29, LEIGH ROAD LONDON, N.5



PULLIN SERIES 100 TEST METER

AC/DC 10,000 A/V

21 RANGES

100µA to 1000V

COMPLETE IN DIE-CAST CASE WITH TEST LEADS

CLIPS AND PRODS

FULLY GUARANTEED

SENT POST FREE FOR £2.10s. DEPOSIT AND ELEVEN FURTHER MONTHLY PAYMENTS OF £1. CASH PRICE £12.7s.

Frith Radiocraft Ltd
69-71 CHURCH GATE LEICESTER
PHONE 58927

NEW!

"FROM THE ELECTRON TO THE SUPERHET"

700 pages. 733 illus. and diagrams. A simplified radio course consisting of 42 lessons each dealing with a specific subject specially based on radio service practice.

PRICE 55/- POSTAGE 1/6.

Practical TV Aerial Manual for Bands I and III, by R. Laidlaw, 4s. 6d. postage 3d.

TV Fault Finding, a Data Publication, 5s. 0d. postage 3d.

Television Engineers' Pocket Book, by E. Molloy and J. P. Hawker, 10s. 6d. postage 4d.

Television Test Equipment, by E. N. Bradley, 5s. 0d. postage 3d.

Basic Television, Principles and Servicing, by Bernard Grob, 45s. 0d. postage 1/-.

The Oscilloscope and its Applications, by Phillips, 5s. 0d. postage 6d.

Radio Valve Data, compiled by "Wireless World," 8s. 6d. postage 3d.

THE MODERN BOOK CO.

Britain's Largest Stockists of British and American Technical Books. Please write or call for our catalogue.

19-23, PRAED STREET

(Dept. W.6.)
LONDON, W.2.

Phone: PADdington 4185.
Open 6 days 9-6 p.m.

RADIO & TELEVISION COMPONENTS

Brand new and guaranteed by the leading makers. Orders dealt with by return.

VIEWMASTER, TELE-KING, ETC.
Constructional manuals: Viewmaster, 7/6. Viewmaster Wide Angle Conversion, 3/6. Tele-King, 6/- Mullard 5 valve 10 watt amplifier, 2/6. Osram 912 12 watt amplifier, 3/6.

FREE CATALOGUE.

56 page illustrated on fine art paper.

SOUTHERN RADIO & ELECTRICAL SUPPLIES
SORAD WORKS, REDLYNCH, SALISBURY

Telephone: Downton 207.

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:

36, ROSEBURY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small!"

GLADSTONE RADIO

DARK SCREEN 14½" x 11½" x 3/16" Perspex ... 6/-

VALVEHOLDERS:

B7G ceramic ... 9d.

B9A moulded ... 7d.

YAXLEY type switch 5 position ... 2/-

SPEAKER 5" P.M. 2-3 ohm ... 17/-

FORMERS, polystyrene ½" dia. ... 6d.

VALVES, new: EF80 ... 12/-

EF91 ... 12/-

2-GANG 500 pf. Variable ... 6/-

3-SPEED autochangers cream:

B.S.R. Monarch ... £10. 5.0

Collaro RC54 ... £10.15.0

BLOCK CONDENSER, small size: .1 mf 2,500 v.w. Simplex ... 5/-

SILVERED MICA condensers:

4 pf to 470 pf ... 5d.

560 pf to 2,700 pf ... 6d.

3,300 pf to 8,200 pf ... 1/-

POTENTIOMETER, 2K,

W.W. pre-set ... 1/-

PART 7v. chassis, bargain, 50 components ... 7/6

4v. I.F. chassis, 40 components ... 7/-

"H" AERIALS WITH LASHINGS ... 50/-

All items carr. pd.

57 EAST STREET, NEWTON ABBOT, DEVON

PROVE ITS VALUE WITHOUT COST—

FREE FOR 7 DAYS

RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK

Broadcasting . Communications . Navigation . Servicing, etc.

Here is a great opportunity for Radio men—examine this new work in your own home for 7 days without cost or obligation. It is essential to all engaged in installation, servicing, design and manufacture. Forty-five self-contained sections provide all the practical data and theory, formulae and technical information you need and which you cannot readily obtain elsewhere. For you—the technical man and executive-to-be—it is indispensable! Claim a copy NOW on coupon below.

GEORGE NEWNES, LTD., 66-69 Great Queen Street, London, W.C.2. Please send me Newnes RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK. It is understood that I may return the work within eight days. If I keep it I will send a first payment of 7s. 6d. eight days after delivery, and 10s. 0d. monthly thereafter, until the sum of £3 17s. 6d. has been paid. Cash price within eight days is £3 12s. 0d.

Name

Address

Occupation

Your Signature

(Or your Parent's Signature if under 21)

Place X where it applies

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

RTRB31


YOU WILL RECEIVE:—

1,600 PAGES

45 SECTIONS.

1,860 diagrams tables, standard formulae, measurements, etc.

2,500 Index entries.

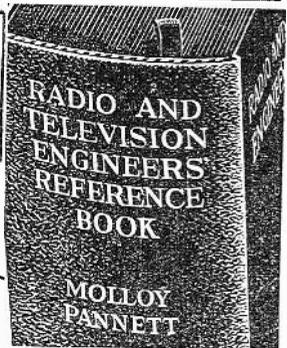

THE MOST UP-TO-DATE WORK OF ITS KIND.

Written by

36 SPECIALISTS


Formulae. Calculations. Transmitter power plant. Aerials. Amateur radio equipment. Wave-guides. V.H.F. Transmitter-receiver equipment. Industrial TV. Interference. Installation and servicing. Projection TV. Units and symbols, etc.

It is impossible to list above more than a very small fraction of the contents—so seize this opportunity of free examination and judge for yourself! Post coupon on left to-day!

UNDERNEATH the DIPOLE

TELEVISION PICK-UPS AND
REFLECTIONS

By **Iconos**

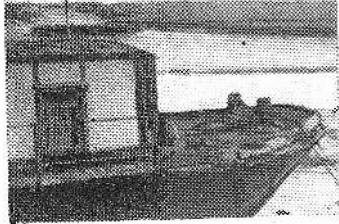

EFFECTS OF COMPETITION

NEW faces, changed routines, more technical gimmicks, new concepts—all of these symptoms are indications of the internal revolution of ideas which is going on at Lime Grove and other BBC television centres. The competition of sponsored TV has to be faced in the autumn and the prospect is having the healthy astringent effect of getting BBC producers and technicians out of the groove.

TV's NEW LOOK

TELEVISION drama progresses slowly but steadily, establishing and consolidating a set of stagecraft conventions which lie midway between stage and screen. It is the "feature" type of programme which enables the creative boys (and girls) to try out their new ideas, and the engineers to display their electronic virtuosity. Take the Jack Payne *Off The Record* programme for example. Here is a type of feature programme which, a year or so ago, would have been put over on routine, conventional lines, somewhat in the style of *Café Continental*, and would have amused without causing much enthusiasm. The mounting of that long-running TV feature was of secondary consideration to the talent of the artistes and yet the fussy setting, the crowd players and the balloons did bring some sense of warmth and audience participation to what was really nothing more than a variety parade, principally featuring Continental artistes. To-day, under the skilled direction of Francis Essex and Claude Whatham, disc recording

stars and personalities are introduced with avuncular charm by Jack Payne and paraded with all the technical aids of inlay, overlay, back-projection and stylised settings. Ruby Murray, the attractive youngster with the fine recording voice, was seen putting over a number with a real sea background (probably either film back-projection or electronic inlay) instead of being draped in front of some palms from the property room.

The avuncular link has also been exploited by J. B. Priestley in his series, *You Know What People Are*, in which he comperes a series of satirical sketches. These are in the style of the intimate revues, such as "Airs on a Shoe String" and the Globe and Lyric revues, but again put over with every possible technical gadget from the BBC engineering bag of tricks. If it is true to say that the series has been a little uneven, the same can be said of even the finest West End theatre intimate revues; satirical humour has a highly selective appeal, and different items in the same show appeal to different members of the audience.

One of the most attractive features of this series is the incidental music of Roberto Gerhard, though the highly stylised decor of Bruce Angrave also contributes much to its success. The sketches are an amusing comment on the contemporary scene, put over with verve and pace by Clive Morton, Frances Rowe, Natasha Parry and John Stratton—sometimes with so much speed that it is a relief to return to the more measured tones of Uncle Jack Priestley himself.

AUTUMN PARADE

CHRIStIAN SIMPSON has often been mentioned in this column for his stylised direction in ballet and musical presentations. His handling of tableaux, group

movements and pictorial design has always been outstanding. The preview of autumn fashions by the Apparel and Fashion Industries Association might have been just another routine mannequin display of somewhat restricted appeal had not the keen choreographic direction of Christian Simpson added that special indescribable polish to the show. Even a mere male will sit through the verbal technical jargon of tulle, broderie Anglaise and triple-ninon (whatever that is!) if he can watch beautiful women display these things attractively, both individually and in groups, in a manner which suggests that the models actually enjoy what they are doing.

THE RETURN OF THE CLOWN

THE red-nosed comic and the musical clown, popular in the music-hall and circus years ago, seem to be on their way back. Grock, Noni and Partner and Barton, the tramp who nearly rode a bicycle, were top-liners years ago. Then came the period of the evening dress comedian, whose possibilities have now been almost exhausted by TV and radio. Hal Monty made a big success on television when he completely changed his style and reverted to a dumb red-nosed clown act, relying upon physical comedy and a variety of musical instruments. This act has been booked up by the music-hall people and Hal Monty is now cutting out all patter and repeating his TV clown act, topping bills in the No. 1 provincial music-halls. Hal has found that silence is golden—thanks to TV.

THE COMMERCIAL DRIVE

THE ITA has commenced a big drive to induce London viewers to have their sets converted and fit new aerials capable of receiving the sponsored TV programmes from Croydon. Extensive advertising in the London Tube stations and evening papers features the names of Bob Hope, Gracie Fields, Norman Wisdom, Orson Welles and Sir John Barbirolli on posters in the style of a variety bill. The ITA seems to be determined to open up to a full audience of viewers which, of course, is essential for the advertisers who put up the money. Some viewers are still taking a poor view of the prospect of being subjected to advertising plugs. Yet the same viewers cheerfully pay their money to see cinema

programmes which likewise contain a small quota of advertising plugs for next week's films, for local shops and for a couple of nationally sold products such as soap flakes and chocolate. Nobody seems to object to this 10 or 15 minutes extra to the programmes—in fact, to be really effective, the advertising "short" must be entertaining and attractive.

A TV SCHOOL

ASSOCIATED REDIFFUSION seems to be way ahead of all the sponsored TV films in getting prepared for the autumn opening. Not only is the preparation of Wembley Studios and the Granville TV Theatre, Waltham Green, well in hand, but TV films have been made at Shepperton, Barnes and other film studios to form a stock-pile of entertainment for next winter's sponsored TV. In addition, the small but very well equipped Viking Studios at Kensington have been taken over as a school for potential producers and technicians, who are trained in the use of both film and Marconi TV equipment. After a five weeks' initial course at Kensington the successful trainees pass on to the Granville TV Theatre, where they receive a further five weeks' training. The first course is timed to end there on August 27th, when the graduates will be ready to proceed to the Wembley Studios in time for the start of commercial TV on September 22nd. This all seems to be first-class planning in the D-Day style.

THE ELECTRONICAM

NOT long after the appearance in American TV studios of the Video-Film camera (recently described in this column), a similar type of camera has been announced under the name of Electronicam. Like the Video-Film camera, the Electronicam comprises a television camera and a motion picture camera mounted side by side on the same base and utilising a common lens system. However, unlike the Video-Film camera, which uses a prismatic beam-splitter for sharing proportions of the rays between a vidicon tube and a motion picture film gate, the Electronicam tackles the problem differently. When the motion picture film is being pulled down to the next frame (which occurs 24 times a second) a shutter interrupts the light path in the normal way. The

front of this shutter is polished and reflects the image into the optical path of the image orthocon tube of a TV camera. The Electronicam can be thus used for direct film recording while a high quality television signal is being simultaneously broadcast. Alternatively, the TV side can be used purely for control, monitoring and production purposes, enabling a TV film director to stop and start cameras and generally direct (via headphone intercom.) their movement in the approved TV manner, thus attaining the speed of production for films equal to pure electronic methods.

TITLE GIMMICKS

THE BBC producers spend a lot of time thinking about titles, backgrounds to titling and mechanical devices for changing the wording. A great deal of ingenuity is used by both art and engineering departments, who bend over backwards in their attempts to be original. I think it can be said that they now surpass the film trailer makers, whose adjectives have loomed up on the cinema screens until we have become almost stunned. The BBC television titling is now of a very high standard, excepting when the original old routine "roll up" titling is used. This mechanical device is frequently unsteady and jerky and has improved very little since the early days at the Alexandra Palace. The sponsored TV people are tackling the problem with a simple motorised device. A rotary drier of the type used in photographic works for glossing and drying prints is used. The titles are printed on long strips of paper which are fixed with adhesive tape to the cloth belt of the drier. The title strip will then move up with the belt in front of the TV camera, the speed of travel being regulated by the normal control resistance. In this manner, a steady flow of titles is ensured, including the all-important cast, directional credits and "The End."

TV LIGHTING

LATELY there seems to have been considerable deterioration in the lighting and camera work at the Lime Grove Studios. Some shows have suffered severely. Celia Lipton was lit most unbecomingly in Richard Afton's *Saturday Night Date*, and other shows have been subject to poor camera movements, tracks and

panoramas. Perhaps there has been a thinning of the ranks of the experienced TV camera operators at the BBC since the sponsored TV companies started getting into operation. At any rate, some of the most elementary rules of camera operation are broken time after time. These rules are: for normal camera panning, camera movement should be motivated by the artiste being televised; the actor should make the first move (such as an exit towards a door) and then be followed by the camera, with only a slight lag. The anticipation by the camera of such moves by actors is extremely bad technique. Similarly, the sudden tracking-in of a camera in anticipation of a movement by an actor is not good. The producers are, of course, partly to blame for these faults. An example of the camera handling at its very best was the transmission of the Cup Final. Precision following of the game with long-focus lenses, zoom lenses and long shots was all carried out most expertly. The combination of absolutely first-class camera operation coupled with beautifully timed cutting from shot to shot was an example of what can be done by first-class technicians who no longer require an "L" plate!

MORE STUDIOS

ENORMOUS studio premises are to be erected in Manchester by the Granada TV organisation. These will take many months to plan and build. The construction is to be on the lines of the elaborate American TV centres and an American expert is acting as consultant. In the meantime other sponsored TV companies have opened studios converted from other uses. The Vandyke Cinema and Café at Barnes has been reconstructed into a TV film studio with three stages with respective dimensions of 75ft. by 42ft., 48ft. by 32ft. and 25ft. by 18ft. (for trick work), together with dressing rooms, offices and workshops. Several TV features have already been made there with success. Motion picture cameras are used in conjunction with RCA recording equipment. The speed of shooting is 24 frames per second, as compared with 25 frames used by the BBC. Most studios making TV films have ignored this slight difference in film travel speed which affects the pitch of music by a semi-tone.

BRAND NEW R.F. Units, types 26 or 27/27/6, 24/10/- (postage 2/6); RF25, soiled, 10/-; I.F. Amplifier, type 178, brand new, 22/6. Relays, small, 6v, 2 br. 1m. 1/6. Dynamotors, D.C. (approx. 250v, 80ma, at 6v), 8/6; 12v input, 250v, 60 ma, and 6.3v outputs, P.M. field, 7/6; Filters for these 2/6; Eddystone, cased, smoothed, 12v, D.C., to 190v. 75ma, 15/-; 12v to 300v, 200ma, 17/6 (carr. 5/-); Hallicrafter, 12v to 250v. 75ma, (vibrapack) and 300v, 165ma dyn., on one cased chassis, smoothed, new, 50/- (carr. 7/6). Transformers, new, std. mains input, 6.3v, 3a (twice), tapped, 4v and 5v, 9/6; 230v to 6.3v, 5a and 10a, 17/6; 2kv, 5ma, 2v, 2a, 17/6; 740-0-740v, 165va, C.T. 470-0-470v, 220va, 4v, 8a. C.T. (twice), 30/- (carr. 6/-); 350-0-350v, 120ma, 6.3v, 4a, 4v, 35/- (post 2/- each). RX161, valves, 2/EF54, 1/EC52, 1/CX166, VHF with rotary coil selector, 17/6. List and enquires, s.a.e., please! Cash with order; postage extra; immediate despatch. Closed 25 July-1 Aug. W. A. BENSON, 308, Rathbone Rd., Liverpool, 13.

T.V. TIME BASES, 10/6, complete with Scanning coil, focus unit, line trans., 10 controls, etc.; drawing free; post 2/6. DUKE & CO., 621, Romford Road, Manor Park, E.12.

COIL PACKS, 3/9 (two wave), including IFs, also 3 wave with 465 k/c/s IFs at 7/9; free drawing; money back guaranteed. IFs only 2/- pair; p.p. 1/3. DUKE & CO., 621, Romford Road, E.12. (GRA 6677.)

DENCO RADIO-GRAM CHASSIS, £5/17/6, 4-wave turret coils, modern octal valves included, front controls; carr. 4/6. P.M. Speaker, 8in., with O.P. Transformer, 12/9 extra with order; limited quantity. DUKE & CO., 621, Romford Road, E.12. (GRA 6677.)

T.V. TUBES, 6 months' guarantee, Mullard 12in. at £5, 14in. at £8/10/-, 17in. at £12/10/-; Mazda 12in. at £5, 3 mths.' guarantee; 15/6 insured carr. on each tube. DUKE & CO., 621, Romford Road, Manor Park, E.12.

V.H.F. 1124 RECEIVER, 17/6, complete with 6 valves, ex-W.D., good condition, 6-channel switching, receives T.V. sound; drawings and conversion data free with order; post 2/6. DUKE & CO., 621, Romford Road, Manor Park, E.12.

1125 V.H.F. RECEIVER, 7/9, complete with 2 valves, new and boxed; requires modification to put into service; post 2/6. DUKE & CO., 621, Romford Road, Manor Park, E.12.

R.F. 24 UNIT, 10/6, new and packed, tubes 20-30 m/cs, including 3 valves; post 2/6. DUKE & CO., 621, Romford Road, Manor Park, E.12.

SPEAKERS, 10/9, Standard P.M. 8in.; unrepeatable offer; post 1/9. DUKE & CO., 621, Romford Road, Manor Park, E.12.

DIRECT T.V. REPLACEMENTS offer the most complete Handbook of T.V. Components and Rewinds, price 1/-; T.V. Components for all kit sets in stock. "Nurray" heater booster isolator for 2-volt C.R.T.s. just plugs in, 27/6, plus 2/- packing and postage. 134-136, Lewisham Way, S.E.14. (TIDeway 3696-2330.)

R.F. UNITS, Types 26 at 27/6, 25 at 12/6, 24 at 11/-; brand new with valves; post 2/6. E.W.S. CO., 69, Church Road, Moseley, Birmingham.

SIMPLEX T.V. 18 swg Chassis, with screens and valve punched, 17/6, post 1/6; fully wound Coil Sets, 15/-, post 1/-; Simplex Mains Transformer, 27/6, post 2/-; Magnetic Chassis and Screens, 22/6; 0.1 of 2.5 kv wkg., 7/6; Rectifiers, RM3, 5/9; 3K/40, 6/-; 4-way Tag Boards, 2/-. List for other items, Lynx-wound Coil Sets, 35/-, post 1/-. C.O.P.Y. WINDINGS, Healey Lane, Batley, Yorks.

RATES: 4/- per line or part thereof, average five words to line; minimum 2 lines. Box No. 11-extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television", Tower House, Southampton St., Strand, London, W.C.2.

T.V. WITHOUT MAINS.—Absolutely first-class picture, plus DC circuit for lighting; as supplied to the B.B.C. Special AC/DC "Chorehorse" Generators, self-starting, compact, and complete. AC 220/250 volts. 50/60 cycles, 250/350 watts AVC. Will run radios, vacuum cleaners, small tools, etc. £47/10/-, plus 10/- delivery. Below:—

STORAGE BATTERIES, 12v, 75AH heavy duty, 19 plates, separate cells in hardwood cases; finest possible specification. £5/17/6, 9/6 delivery; 12v, 22AH, almost similar specification, surprisingly powerful, £2/14/-, delivery 5/6. TEDDINGTON ENGINEERING CO., LTD., Dept. "C", High St., Teddington, Middx. (KINGSTON 1193-4.)

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets "How to Use Ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive lists of lenses, optical, radio and scientific gear free for s.a.e. H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.

TELEVISION AERIALS, half cost, ex-demonstration as new, 1 Belling multi-rod Channel 3 £10, 1 Double J-Fair Channel 3 £15, 1 Belling Junior Multi-rod Horizontal Channel 4 £5; also 36ft. x 2in. Alloy Masting, 6ft. lengths, £9, or offers. Box No. 178, c/o PRACTICAL TELEVISION.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

T/V, PERFECT WORKING ORDER, All makes; Pye, 9in., £15; Murphy 9in., £16; Murphy 9in., £17/10/-; G.E.C. 9in., £15; G.E.C. 12in., £25; Ekco, 9in., £27/10/-; Murphy Console, £30; many others. List sent on request. Service manuals loaned with sets supplied by ourselves. T/V needing attention from £7. Multi-channel Converters supplied with instructions for fitting from £6. Please enclose s.a.e. HIGH STREET RADIO, 284-6, High Street, Croydon, Surrey. (Tel.: CROYDON 8099.)

VIEWMASTER COILS, 13 Coils, plus choke, for K/O/Shorts, Wenvoe, Midlands, H/Moss, 12/6 set; Iso Trans., 2v, 4v or 6v type, all with 25% boost. 5/9; Htr./trans., 200/240v, 6v at 1.5a, 5/6; W/W Cntrls., 5K-3 watt, 3/-; Band 3 Converter Coilset, 15/-; Diagrams, 6d.; Band 3 Aerials, 45/-; Conversion for single dipole, 7/6, post 1/-. New list available: WINWOOD, 12, Carnarvon Road, Leyton, E.10. (Mail only.)

RADIO UNLIMITED. First in the field with the Band 3 Converter Coilset. For use with TRF or S/hel Band 1 Receivers. Complete precision Coilset, with circuits and point-to-point diagrams, 15/-, post free. Circuit and Data only 6d. RADIO UNLIMITED, Elm Road, London, E.17; also at 50, Hoe Street, E.17. (Telephone: LAR 6377.)

VALVES

WANTED, Valves 6F13, 6F15, 6U4, EY51, 5Z4, ECL80, KT61, 25A6, etc.; prompt cash. WM. CARVIS LTD., 103, North Street, Leeds, 7.

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. RADIO FACILITIES LTD., 38, Chalcot Road, N.W.1. (PRINROSE 9090.)

VALVES, SP61, 3/6; 5U4, 7/6; 6SN7, 7/6; EB333, 7/6; EF39, 7/6; EF50-Red, 7/6; 13,000 Valves actually in stock. Write for free list. RADIO UNLIMITED, Elm Road, London, E.17. New branch now open at 50, Hoe Street, London, E.17. (Telephone LAR 6377.)

GUARANTEED BOXED VALVES: PCC84, PCF80, U25, 20P3, 20P4, 40/-; PL81, 20F2, 10C1, U282, 9/-; EF80, ECL80, EBF80, U281, UJ6, 10C2, 10P1, PY81, 6K8, 8/6; 6SN7, ECC81, 6X5, 6V6, 7/6. W. FEWELL, 19, Mapledene Rd., Dalston, London, E.8.

WANTED

WANTED, large or small quantities of new Valves Loudspeakers, Components, Receivers, etc.; prompt cash paid. R.H.S. LTD., 155, Swan Arcade, Bradford, 1.

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.

PYE TELECOMMUNICATIONS LTD., Dilton Works, Cambridge, offer excellent opportunities for Junior and Senior Development Engineers in the electronics and communications field. Duties include development work on H.F., V.H.F., microwave and recording equipments. Applications from persons possessing B.Sc., Higher National or Ordinary National Certificates are especially welcomed. Good facilities are available, however, to keen young men wishing to train and study in these fields. Pleasant working conditions in modern factory. Single accommodation available. Write, giving fullest details, to Personnel Manager.

ALL DISTRICTS. An opportunity exists for Television Technicians to establish a business of their own. The business can be commenced in first instance in spare-time, showing an all the year round increasing income. Write, giving particulars of age, training, and equipment, experience, to TELEPATROL LTD., Federation House, Epsom.

EDUCATIONAL

COVENTRY TECHNICAL COLLEGE. Session 1955-56. Electronic Engineering Applications invited for entry to next three-year full-time course commencing September, 1955, from those requiring comprehensive training to an advanced level in Electronic Engineering, qualifying for technical posts in radio, telecommunications, television and industrial electronics. Syllabus will cover requirements of City and Guilds, Brit.I.R.E., and I.E.E. examinations. Entry age 16 or over. Application forms and further information from PRINCIPAL, Coventry Technical College, Educational Office, Council House, Coventry.

FREE! Brochure giving details of Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, -R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest electronic organisation; moderate fees. Write to Dept. PT28, E.M.I. INSTITUTES, London, W.4.

BUILD YOUR OWN T/V and learn about its operation, maintenance and servicing. Qualified engineer-tutor available while you are learning and building. Free Brochure from E.M.I. INSTITUTES, Dept. PT.58, London, W.4. (Associated with H.M.V.)

News From the Trade

NEW 2-BAND TELEVISION RECEIVERS BY MARCONIPHONE

TWO completely new television receivers—a 14in. and 17in. table model respectively—are now released by Marconiphone.

Specifically designed for first-class reception of Band I and Band III programmes, these new models incorporate a tuner unit of the incremental inductance type with built-in coils for all 13 channels. This is an integral part of the chassis and therefore permits the channel selector and the fine tuning control to be mounted in the logical and most convenient position—on the front of the cabinet.

Further simplification for the user is afforded by the single co-axial aerial socket, catering for a combined Band I and III feeder.

Circuit features include: flat-faced aluminised Emiscope picture tube with in-built dark screen and special non-reflecting mask; frame fly-back suppressor enabling full use to be made of the extended brightness range, stable pre-set permanent magnet focusing system, "sync cancelled" vision A.G.C. to counteract fading, aircraft flutter and differences in signal strength between Band I and Band III signals. This obviates major adjustments by the user when the set is switched from one band to the other.

Interference is effectively dealt with in three ways. Impulsive interference on vision is drastically reduced by a very efficient adjustable "black spotter" type of limiter. An automatic suppressor circuit takes care of sound interference. For diathermy and similar kinds of interference there is a wide-range tunable filter which can be connected at will via alternative sockets for the feeder cable.


H.T. supply is from two rectifier valves instead of metal rectifiers.

The 17-valve circuit has a high degree of sensitivity, designed to provide the best possible reception on both bands. Easily accessible controls for picture



shift, squaring, linearity, etc., make for quick initial setting-up of the receiver.

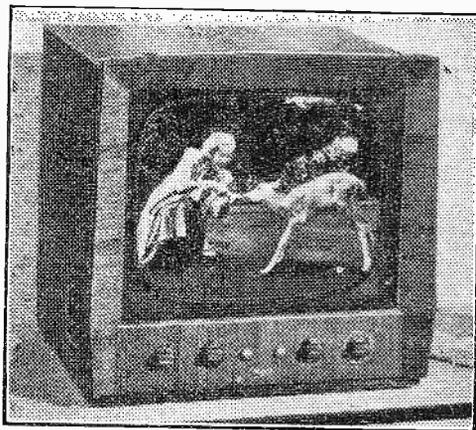Well-tried components are used throughout, but the servicing aspect has not been overlooked. The tube is carried on the chassis and this can be easily removed as a complete unit if necessary. A number of test points have been provided



Marconiphone Model VT69DA.

and brought out to the back of the chassis for servicing measurements *in situ*.


These receivers operate on D.C. mains voltages from 195 to 255 volts, or 50 cycle A.C. mains of similar voltages. Consumption is approximately 130 watts.

Both models are housed in cabinets in highly-finished walnut veneers. Prices: Model VT68DA (14in.), 66 gns. (tax paid); Model VT69DA (17in.), 79 gns. (tax paid).—The Marconiphone Co., Ltd., Hayes, Middx.

VENDOMA SCREEN MASK

TO avoid difficulties due to light from windows or room lights, a shade round the screen is very useful and a novel type of screen is now available and shown here. Made from stout card, with the inside covered with sprayed black felt, this is very simply attached with the aid of suction cups and an adjustable elastic band. The set will not be marked in any way, and the material lends itself well to adaptation in the case of special cabinets, as it may readily be cut. Models are available at present for 12in., 14in., 15in. and 17in. screens and the retail prices are as follows (free of Purchase Tax): 12in. and 14in., 17s. 9d.; 15in., 18s. 6d.; 17in., 19s. 6d.

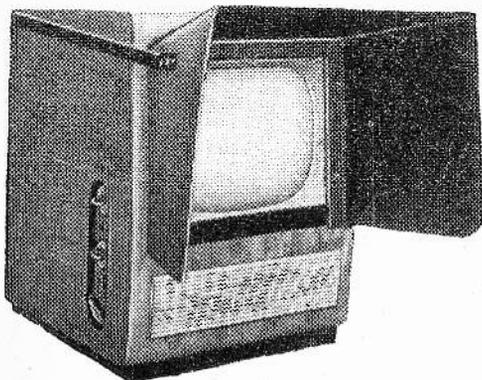The makers are Vendoma (TV), Ltd., Station Buildings, Preston Park, Brighton.



The Vendoma Television Screen Mask.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 144 must be attached to all queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

VIEW MASTER

My "View Master" TV is fitted with a Mazda CRM 121B C.R.T. and in order to get the full benefit from it I have increased the E.H.T. from approximately 6 kV to 9 kV. Since I increased the E.H.T. the picture will not fill the screen at the top and bottom.

By reducing the E.H.T. to 6 kV, again the picture fills the screen, but the quality is not so good.

I have been told that now I have boosted the E.H.T. I will have to increase the frame and line scan outputs. If this is so could you please give me details of the necessary modifications.—P. Blamire (Stafford).

You are correct in assuming that if the E.H.T. is increased it would be necessary also to increase the scan amplitudes and frame timebases. As you say that the height is short we suggest that you make the following modifications.

In the first place check that the voltages in the V11 and V12 stages are exactly as specified as this is essential. Break the connection between the top of R60 and the junction of R57 and C48 and connect a 1 μ F condenser across these points; reduce the value of R66 to 220 Ω , connect a 1,000 Ω resistor in parallel with R65. Delete R67, then readjust R64 and R65. If necessary, connect a 330 pF condenser across the line scan coils, tags L1, L2.

SIMPLEX

I have recently completed the Simplex televisor and have obtained a picture. The trouble is that the vision is slightly blurred, more especially objects that are at the back of the picture. I have modified the video amp. by connecting another valve in parallel with the existing video valve and tried staggering the coils, but although there is some improvement the blurr is still there. I cured the frame linearity distortion which was very apparent by connecting a 2.5 kV. condenser, of .1 μ F capacity between number 10 connection on the tube and chassis. The line hold is extremely critical and I have to make frequent adjustments to preserve sync, and the frame seems to tremble when I advance the contrast beyond a certain point. I suspected oscillation in one of the R.F. stages so I spent quite a time making certain that this trouble did not exist. I have tried three

VR97 tubes and there seems little difference between them. I find I can stop the frame tremble by touching the top cap of the sync separator.—G. Cook (Southampton).

The first thing to ascertain is that the horizontal lines focus correctly. If this is so then the fault lies in the tuning of the vision receiver; if this is not the case then a resistor in the bleeder network has altered in value; each one must be checked preferably by substitution.

It must be remembered that the studio cameras do not keep everything in exact focus; this is particularly noticeable in close-ups.

The frame trouble may be cured by doubling the value of C24.

To secure better line hold add a 50 pF condenser across C20.

K/B. KV35

After renewing a fuse which had blown, the picture is very dull. It cannot be seen in daylight.

Having an Avometer Model 7 and service chart, I measured all the volts between the valve sockets and chassis, I found them all normal except two. The voltage on screen of valve 50CD6G was 140 volts instead of 95 volts as on service chart. The voltage on first anode cathode-ray tube (C14FM) was 75 volts instead of 330 volts as on service chart.

I replaced the 1 meg. resistor on the lead to the first anode of tube and it still gives 75 volts. The reading on the other side of this resistor was 400 volts.

Would the drop from 330 volts to 75 volts be the cause of the dull picture? If so, how can I rectify this?—R. J. McClure (Belfast).

We feel that the low voltage reading on the picture-tube first anode is the result of the measurement being taken on a relatively low-resistance meter—a valve-voltmeter or a very high-resistance meter is essential to obtain an accurate reading at this point.

The trouble you describe is either caused by a low emission picture-tube, or misplacement of the ion-trap magnet on the neck of the tube. You should check these possibilities.

EKCO TSC91

The framhold slips many times during the evening, necessitating frequent readjustment of the framhold control. I am not certain whether this has occurred as a result of fitting a new valve, or whether it is just a coincidence. The slipping is often triggered off by a change in the picture transmitted, and is bound up with the black and white relation to the sides of the picture.

I would much appreciate any guidance you can give me on tracing and curing this trouble.—F. A. Chappell (Kingston-on-Thames).

The new valve may be defective and should be substituted before going any further.

Should the picture continue to roll intermittently, the resistors in the T41 circuit should be suspected of changing their value as the temperature of the set varies. This may also cause a condenser in this part of the circuit to vary in capacity. A hot soldering-iron placed near to, but not touching, the suspected component may provoke the symptom and give a definite lead.

The electrolytic condensers in the video-amplifier valve circuit should receive attention. The sync separator circuit and the valve itself should be checked to ensure correct working.

ARGUS

I have searched through your issues for two years back to find some reference to a fault that has developed in my "Argus." Perhaps you will be kind enough to enlighten me.

When I turn down the brilliance control to fade out the raster, it fades out—but at the same time the complete raster moves sideways off the screen and no raster is obtainable.—F. Nicholls (Whitley Bay).

Movement of the raster with operation of brilliance is due to leaky condensers connecting the deflecting plates to the timebase valves. Check C54, 55.

PHILIPS 12IN. MODEL

I have a Philips 12in. television set and have been getting excellent reception, both vision and sound, but for quite a while now I have been troubled by a very loud hum. I have had a service engineer and he has examined it to see if it is a mains hum, but apparently it is not. It is possible to reduce it by altering the attenuators at the back of the set, but this means a consequent loss in vision. A friend suggests it may need tuning. Could you be so kind as to give me your opinion?—N. Millar (Everton).

It is not stated whether the hum is present when no vision signal is being received. Assuming it is only present when the vision signal is "on," it can be put down to vision on sound.

The cure for this is to change the setting of the oscillator, probably a concentric trimmer mounted on the top of the chassis adjacent to V2. No precise instructions can be given as the model number is not supplied. Tune the trimmer to maximum sound by rotating it to find its best position.

If the trouble happens again after a short period (say, a week), change the UF42 oscillator-mixer valve. This is a common failing (drift).

K/B. HF40

Your help would be appreciated on the following: After the set has been on for about 10 minutes, the picture folds up for about half an inch at the bottom. I have changed the frame output valve with another in the set but the trouble still persists.—P. F. Harrington (E.11).

The valve with which you substituted may also be slightly defective and while working without trouble in another section of the receiver, the defect may show, in the form you describe, when used as frame amplifier. You should, if possible, prove this possibility by checking with a valve of known goodness. You would also be advised to check the condition of the frame generator valve.

Once you have proved conclusively that valve trouble is not responsible, you should investigate in the frame timebase circuits for a resistor which alters in value as it increases in temperature.

LOOSE ELECTRODE ASSEMBLY

After moving my set the other day to another part of the room I noticed that, when it was reconnected up, on switching off the spot that remained was enlarged and very blurred, and when viewed in a dark room with no raster on screen (aerial disconnected), a red glow could be seen in the centre of the screen

and it was possible to see through it and see the electrode system in the neck. I assumed that the tube must be at fault as no other part of the set had been touched, so I moved the tube round to another position and noticed that the spot this time was a little better and nearly normal on switching off. Could this be a faulty electrode in the tube as when it is moved to another position the effect on the spot is changed, and it is possible to see through the coating on the tube? There is no heater cathode short and control of brilliance is perfect and emission appears O.K. Is there any way of curing this, what appears to be a loose connection in the electrodes which only affects it when any vibration is caused to it? I would appreciate details of any process on rejuvenating tubes apart from fitting the low-loss transformer to heaters.—N. Shaw (Salford).

It is possible that the electrode assembly in your tube is loose, and if this is the case, unfortunately, nothing can be done by way of rejuvenation. Under certain conditions it is quite normal to observe slight illumination from the tube heater through the screen. This should only occur, however, when the tube is viewed in a darkened room with the brightness control fully retarded—it should not be visible when the screen is illuminated by a picture or raster. If it does, then we feel that the emission of the tube is somewhat impaired.

NOISE SUPPRESSION

Can you help me as regards this problem? I am using a U.H.F. unit, 2 RF. and def., described some years ago in "Practical Wireless." Used with a three-stage amplifier it gives me good reception of TV sound, the only snag is car interference, living, as I do, on a main road. I have been trying various noise limiter circuits as used in modern TV sets, the basis of which is a double-diode valve, but they do not reduce the noise even a little bit. I even built up the D.X. aid described in the current "Practical Wireless," but all it did was to drop considerable volume and distort the output. Maybe I am experimenting on the wrong lines and I cannot claim to understand the way these noise suppression circuits work, so perhaps you can suggest a possible line of experiment.

As this area is on the fringe for F.M. reception, car interference again will be a serious drawback. Aircraft causing sound flutter is another snag, but that has no remedy—it will just have to be endured it seems! —F. V. Trent (Bognor Regis).

The essential requirement of any sound unit in which a limiter is incorporated is that it should possess a reasonably wide bandwidth, 100 kc/s is usual.

This is because the original shape (spikes) of interference pulses must be preserved in order for the time constant of the limiter to be effective.

Interference on F.M. receivers does not cause trouble because of the limiter circuit which "levels" the response before discrimination. A.G.C. applied to the sound stages should limit aircraft flutter.

QUERIES COUPON

This coupon is available until AUGUST 21st, 1955, and must accompany all Queries.

PRACTICAL TELEVISION, AUGUST, 1955.

Finest Soldering? Always specify ERSIN MULTICORE to be precise

Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SIZE 1 CARTON

4 specifications for radio enthusiasts.

5/-



**HANDYMAN'S
CARTON**
Sufficient for
200 average
joints. **6d.**



TAPE SOLDER

**MELTS WITH
A MATCH!**
Real tin/lead solder
containing
cores of Ersin
Flux. Needs no
soldering iron
or extra flux.

1/-

PER CARD



**Bib RECORDING
TAPE SPLICER**
These nickel-plated brass
Splicers enable recording tape
to be jointed easily and accurately so that
no breaks or "clicks" occur in the recording. A comprehensive
leaflet is supplied with every splicer. 18/6 each (subject).

MANUFACTURERS ARE INVITED TO

WRITE FOR DETAILS OF BULK PACKS AT BULK PRICES

MULTICORE SOLDERS LTD.

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS (BOXMOOR 3656)

TV Tubes, guaranteed 6 months

14" WIDE ANGLE. £7.10.0. Picture shown to callers. 6 month guarantee.

17" WIDE ANGLE. £12.10.0. Guaranteed 6 months. Picture shown to callers.

12" MULLARD TUBES. £5. 6 month guarantee. 3 months on other makes. As we have been selling for the past 4 years. 15/6 ins. carr. on all tubes.

12" T.V. CHASSIS. 9/6. Complete chassis by well-known mfr. R.F. E.H.T. unit included. Drawing FREE. Easily fitted to table or consol model, owing to this chassis being in 3 separate units. (Power, sound & vision, timebase) interconnected. THIS CHASSIS IS LESS VALVES & TUBE. Our £5 Mazda tube fits this chassis. Carr. 5/- London, 10/- Provinces.

T.V. TIMEBASE. 10/6. Complete with scanning coil, focus unit, line transformer, 10 controls, 8 valveholders, electrolytics, conds., resist., etc. Famous mfr. Drawing FREE. Post 2/6.

DENCO R/GRAM CHASSIS. £5.17.6. Complete with valves (Int. Octal) dial, etc.; in full working order, 8" P.M. speaker with O.P. Transformer 12/9 extra. Carr. 4/6.

1124. V.H.F. RECEIVER. 17/6. Complete with 6 valves. X.W.D. 6 channel switching. Receives T.V. sound. Tunes 30.5-40 mc/s. I.F.s 7 mc/s. Post 2/6. Drawings & conversion data 1/- or FREE with each set.

V.H.F. 1125 SET. 7/9. New X.W.D. and boxed. Complete with valves. Requires modification to put it into service. Post 2/6.

R.F. 24 UNIT. 10/6. Complete with 3 SP6I valves. New X.W.D. & boxed tuning 20-30 mc/s. Post 2/6.

SPEAKERS. 10/9. Standard P.M. 2-5 ohms. 8" and 5". Tested and guaranteed. Post 1/9.

SPEAKERS. 2/9. Mains energised. 8". Field 1K, 1½K, 2K and 4½K. ohms. Post 1/9.

O.P. TRANSFORMERS. 1/9. For above. Salvage guaranteed. If bought separate, 9d. post.

MONEY BACK GUARANTEE **DUKE & CO** Tel: GRA 6677 CWO or COD!
621 ROMFORD RD. LONDON, E.12.

VIEWMASTER AND SIMPLEX KITS

ON EXTENDED PAYMENTS

Only 3/- in the £ Deposit

★ SIMPLEX ★

Six-inch kit, less tube. Deposit £2.11.0 and 12 monthly payments of £1.5.9.

Conversion to Twelve-inch kit, less tube. Deposit £2.6.0 and 12 monthly payments of £1.4.1.

Twelve-inch kit, less tube. Deposit £4.10.0 and 12 monthly payments of £2.5.10.

★ VIEWMASTER ★

Nine- or Twelve-inch kit, less tube. Deposit £5.8.6 and 12 monthly payments of £2.15.10.

Wide Angle Model, less tube. Deposit £6.6.0 and 12 monthly payments of £3.5.6.

Full details of these Kits are given in our lists which will be sent free upon request.

WATTS RADIO

8, Apple Market, Kingston-on-Thames, Surrey.

Telephone: KINGSTON 4099.

"You can rely on Us"

BARGAIN LINES

8 mfd. 500 v. Cardboard Block B.1., 2/6; 3 for 6/6. 16 mfd. 350 v. Aluminium Can, 2/-; 3 for 5/-. 16 mfd. 500 v. 4/- each; 3 for 10/6. 6 Assorted Vol./Controls, Long Spindle, 10/6. 6 Assorted Vol./Controls, with Switch, 18/6. 60 m/a Smoothing Chokes, 4/3 ea.; 6 for 24/-. 25 mfd. x 25 mfd. at 12 v., 1/-; 6 for 5/-. Paper Tubulars; all popular values, 6d. each; 6 for 2/6. Switches, 8 p. 4-way, 3/9; 4 p. 8-way, with Screens between Wafers, 3/9; 1 p. 12-way, 3/6; 2 p. 6-way, 3/6; 4 p. 3-way, 3/-; 3 p. 4-way, 3/-. Six Assorted New Wirewound Preset Pots., 10/6. 24 Assorted Ceramic and Silver Mica Condensers, 7/6. .01 mfd. 5,000 v. Dubilier, 2/6. 6 Assorted Radio Books, 10/-. Band III Multi Aerials (Loft Type), 30/-, carriage 2/6. Air Drying Crackle Paint, Brown, Green or Black, 3/-; Bib Tape Splicer, 18/6. Puretone Tape, 1200ft., 20/-.

VALVES

R19	7/-	6BW6	6/-	6AM6	6/-	6BE6	6/-
12BE6	6/-	9BW6	6/-	3ABCT	2/6	AC6PEN	3/6
12SC7	4/6	6K7GT	6/-	6AT6	6/-	EM34	7/6
25Z4	9/-	12AT7	7/-	12AU7	7/-	6CH6	6/6
EF80	8/-	13D3	3/6	PL82	8/6	6AG5	5/6
6SH7	5/6	KTZ41	5/-	6K7G	6/-	6BW7	7/6

VALVE MANUALS

Osram, 7/6. Brimar, 5/-. Mullard, 5/-. Valve Data Book, 5/- Equivalent and Ex. Gov., 5/-.
Post on any order, 9d.

Radio Servicing Co.,

82, SOUTH EALING ROAD, LONDON, W.5. Eal. 5737.

ALPHA FOR VALVES

GUARANTEED NEW AND BOXED

Table listing various vacuum tube types and their specifications, including AC/PC, 6X4, 6X5, etc.

CHASSIS

Aluminum Un drilled with Reinforced Covers. Available in the following sizes: 6in. x 4in. x 2 1/2in. 4/6 ea.

SENTRELEC RECTIFIERS

RM1, 8/9 ea.; RM2, 4/2 ea.; RM3, 5/- ea.; RM4, 12/ ea.

METAL RECTIFIERS

12 v. 1 amp., 1/6 ea.; 12 v. 1 amp., 4/8 ea.; 2 v. 1 amp., 3/- ea.; 250 v. 45 mA., 6/3 ea.; 250 v. 75 mA., 7/6 ea.; 300 v. 60 mA., 7/6 ea.

GOLDRING PICK-UP HEADS

Pick-up head type No. 112 (2,000 ohms), complete with lead. Price 17/6 each.

NYLON DRIVE COIL

25 yard reel nylon drive coil on wooden reel, 2/9 ea.

BI CONDENSERS

Waxed carious, with drying leads, 4 mfd., 500 v., 1/8 ea.; 4 v. mfd., 500 v., 3/4 ea.

METERS

0-50 ma. Milliammeter by Perranti. Panel Mounting, 7/6 each.

SPECIAL OFFER

1 Pair 866A VALVES. 12/6 PAIR. POST 1/6.

MAINS TRANSFORMERS 3-WAY MOUNTING TYPE

MT1 Primary: 200-220-240 v. Secondaries: 250-0-250 v. 80 m.t. 0-6-3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. 17/6 ea.

TERMS

Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; £5 add 2/- unless otherwise stated. Minimum C.O.D. fee and postage 2/3.

MAIL ORDER ONLY

WHEN ORDERING PLEASE QUOTE "DEPT. P.T."

LOUDSPEAKER UNITS

R. & A. 10in. unit. 25/6 ea. Plessey 5 1/2in. lightweight unit. 16/6 ea. Rola 6 1/2in. standard type. 17/6 ea.

CRYSTAL DIODES

Plastic case, wire ends, 2 for 2/1. K/25, 5/8; K/40, 7/6; K/45, 8/2; K/50, 8/8; K/50, 9/6; K/100, 14/8.

JUNCTION BOXES

Type 5X/2234-20 Way, 1/6 each. OSOMOR COIL PACKS Type H.O., 48/- each. Type I.M., 40/- each. Type T.B., 50/- each. Type TRP, 40/- each.

OSMOR COIL PACKS

.05 mfd., 500 v.; .01 mfd., 1,000 v.; .1 mfd., 350 v.; .02 mfd., 750 v. All 9/- doz.

SPECIAL OFFER

VR07 TUBES PICTURE TESTED. 20/- EACH. CARRIAGE 3/6.

HEATER TRANSFORMERS

230 v. Input 2 volt 5 amp. 4/6 230 v. Input 2 volt 3.5 amp. 7/9 230 v. Input 4 volt 1.5 amp. 5/- 230 v. Input 4 volt 3.5 amp. 10/- 230 v. Input 5 volt 2.5 amp. 10/- 230 v. Input 6.3 volt 5 amp. 15/- 230 v. Input 6.3 volt 1.5 amp. 6/- 230 v. Input 6.3 volt 3.0 amp. 9/- 230 v. Input 12 volt 7.5 amp. 5/-

L.E.M. Silver Mica, 1,000 PF, 10%, 31d. ea. L.E.M. Silver Mica, 100 PF, 5%, 31d. ea. L.E.M. Silver Mica, 50 PF, 10%, 31d. ea. L.E.M. Silver Mica, 500 PF, 10%, 31d. ea. Hunts Silver Mica, 374 PF, 1%, 31d. ea. L.E.M. Silver Mica, 330 PF, 10%, 31d. ea. L.E.M. Silver Mica, 25 PF, 20%, 31d. ea. L.E.M. Silver Mica, 50 PF, 10%, 31d. ea. Tubular Condenser, 500 mfd., 50 v., 6d. ea. Yaxley Switch, 1 pole, 8 way, 1/9 ea. Spindle 1/9 ea. Arrow Toggle Slotted Dolly S.P., 1/9 ea. Sturge Screed Cable 8d. yd.

CONDENSERS

8 x 8 mfd. 450 v. 4/- ea. 8 x 16 mfd. 450 v. 4/- ea. 8 x 24 mfd. 450 v. 4/- ea. 8 x 32 mfd. 450 v. 4/- ea. 12 x 4 mfd. 450 v. 2/- ea. 16 mfd. 450 v. 3/- ea. 10 x 8 mfd. 350 v. 4/- ea. 16 x 16 mfd. 350 v. 4/9 ea. 20 x 20 mfd. 400 v. 3/6 ea. 24 mfd. 450 v. 2/9 ea. 24 x 16 mfd. 350 v. 3/6 ea. 22 mfd. 350 v. 3/- ea. 32 x 8 mfd. 350 v. 3/6 ea. 32 x 16 mfd. 350 v. 4/6 ea. 32 x 32 mfd. 450 v. 9/11 ea. 32 x 32 x 8 mfd. 350 v. 5/6 ea. 32 x 32 mfd. 350 v. 25 25 mfd. 25 v. 5/9 ea.

DUBILIER (R.R. Range)

60 mfd. 450 v. 2/9 ea. 64 mfd. 350 v. 2/- ea. BR. 850 8 mfd. 500 v. 2/9 ea. BR. 1650 16 mfd. 500 v. 3/3 ea. BR. 2050 20 mfd. 500 v. 3/6 ea. 8 x 8 mfd. 500 v. 4/6 ea. BR. 501 50 mfd. 12 v. 1/9 ea. BR. 2 16 mfd. 500 v. 5/6 ea. 16 x 8 mfd. 500 v. 4/9 ea.

PERSPEX IMPLOSION GUARDS

Incorporating acetone bath and filter. 12in. type, 11/6 ea.; 16in. type, 14/6 ea.


U.S.A. INDICATOR UNIT

Type B.C.420A at £3.19.6.

B.S.R. MONARCH AUTOMATIC RECORD CHANGER

Model U46, fitted H.P.37 Cartridge, 3 speeds; 33 r.p.m.; 48 r.p.m.; 78 r.p.m. Complete with full instructions, £9.19.6. Carriage 2/6.

LOUDSPEAKER CABINETS

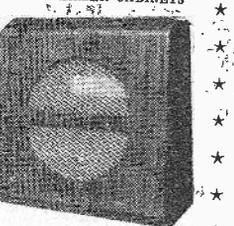

This attractive walnut finished cabinet is available for 6 1/2in. of 8in. speaker units. Metal speaker front, complete with back and rubber feet. 6 1/2in. type, 2 Measures 8 1/2in. x 8 1/2in. x 4 1/2in. at base. Price 16/6 each. Post 1/6. 8in. type, 2 Measures 10 1/2in. x 10 1/2in. x 5 1/2in. at base. Price 20/6 each. Post 1/6.



ALPHA RADIO SUPPLY CO.

5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.