


Timebases Simply Explained


Practical Television 1's

JUNE 1956

AND TELEVISION TIMES

EDITOR: F.J. CAMM

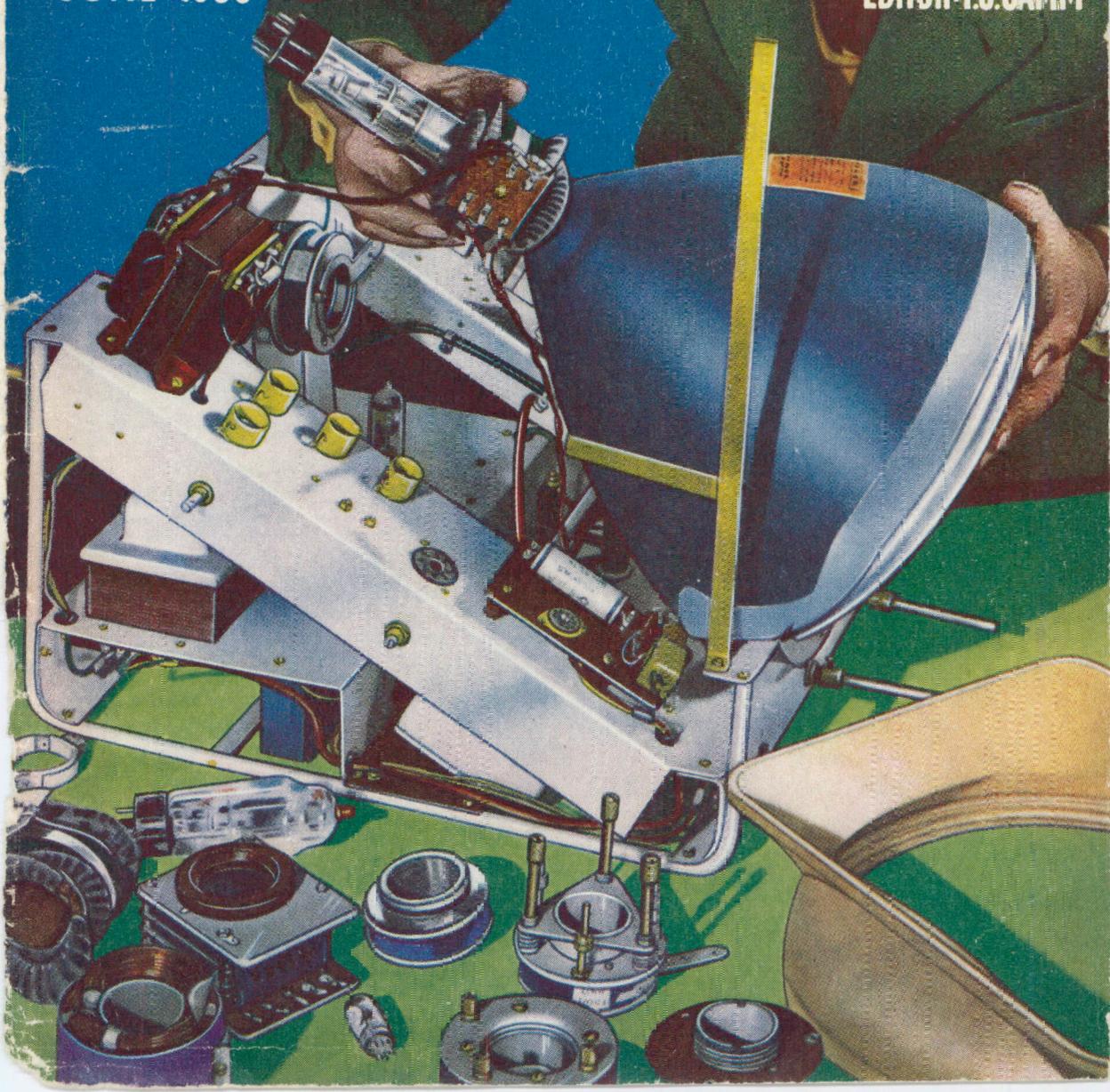

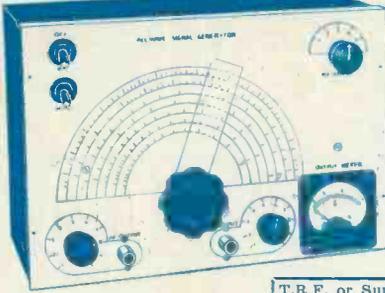


COMPLETELY BUILT SIGNAL GENERATOR

Completely built Signal Generator, coverage 120 Kc/s-320 Kc/s, 100 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8 Mc/s-28 Mc/s, 16 Mc/s-56 Mc/s, 24 Mc/s-84 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle-finished case and white panel. Accuracy plus or minus 2%. £4.19.6 & 34/- deposit and 3 monthly payments 25/- P. & P. 4/6 extra.

BOTH GENERATORS GUARANTEED FOR 12 MONTHS

COMPLETELY BUILT T.V. CONVERTER

for the new commercial stations, complete with 2 valves. Frequency can be set to any channel within the 186-196 Mc/s band. I.F. will work into any existing T.V. receiver between 42-68 Mc/s. Input arranged for 80 ohm feeder, EF80 as RF amplifier. ECC81 as local oscillator and mixer. The gain of the first stage, RF amplifier 10DB. Required power supply of 200 D.C. at 25mA. 6.3 v. A.C. at 0.6 amp. Input filter ensuring freedom from unwanted signals. Simple adjustments only, no instruments required for trimming. Will work into any

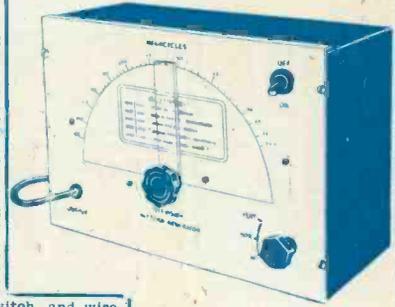

PATTERN GENERATOR

Completely built Signal Generator, coverage 120 Kc/s-320 Kc/s, 100 Kc/s-900 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8 Mc/s-28 Mc/s, 16 Mc/s-56 Mc/s, 24 Mc/s-84 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent. modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle-finished case and white panel. Accuracy plus or minus 2%. £4.19.6 & 34/- deposit and 3 monthly payments 25/- P. & P. 4/6 extra.

40-70 Mc/s direct calibration, checks frame and line time base frequency and linearity, vision channel alignment, sound channel and sound rejection circuits and vision channel band width. Silver plated coils, black crackle-finished case 10 x 6 1/2 x 4 1/2 in. and white front panel. A.C. mains 200-250 volts. This instrument will align any T.V. receiver, accuracy plus or minus 1%. Cash price £9.19.6 or 29/- deposit and 3 monthly payments of £1. P. & P. 4/6 extra.
Line or Frame oscillator Blocking Transformers, 4/6 each. Smoothing Choke, 250 mA. 5 henry, 8 6 ; 250 mA. 10 henry, 10/6.

3-speed TRANSCRIPTION MOTOR BY FAMOUS MANUFACTURER

Complete Kit of parts comprising accurately balanced precision made, heavy turntable with rubber mat, large constant speed condenser, starting motor, base plate. Can be assembled in half-an-hour. A.C. Mains 200/250 v. Fully guaranteed. **£6.19.6** Post Paid. Parts sold separately.



A.C. mains 230/240 Comprising choke, power-factor condenser, 2 tube holders, starter, and starter-holder. (No tube or metal work supplied.) P. & P. 3/- **17/6**

40 watt A.C. or D.C. 200/250 v. Fluorescent kit, comprising trough in white stove enamel, 2 tube holders, starter, starter-holder and barretter. (No tube.) P. & P. 1/6. **12/6**

Three speed automatic changer by B.S.R. MONARCH current model. Will take 7 in., 10 in., or 12 in. records mixed. Turnover crystal head. Cream finish. BRAND NEW. VERY LIMITED QUANTITY. A.C. Mains 200, 250. £7-15-0. P. & P. 3/6

Line and E.H.T. Transformer, 9kV. Ferrocort core. EY51 heater winding, complete with scan coils and frame output transformer and line and width control. 95/- P. & P. 3/-

As above but complete with line and frame blocking transformers, 4 henry 250 mA. choke, 100 mfd. 350 wkg., 380 mA. A.C. ripple. £2-9-6. P. & P. 3/-

Standard wave-chance Switches. 4-pole 3-way; 5-pole 3-way; 3-pole 3-way, 1/9 each; 9-pole 3-way 3/6; Miniature type, long spindle, 4-pole 3-way and 4-pole 2-way 2/6 each. 2-pole 11-way twin wafers, 5/-; 1-pole 12-way 5/6. P. & P. 3d.

USED metal rectifier, 250 v. 150 mA., 6/8.

Combined 12 in. Mask and Escutcheon perspex. New aspect, edged in brown. Fits on front of cabinet. 12/6. As above for 15 in. tubes, 17/6.

Polishing Attachment for electric drills. 1 in. spindle, chromium plated 5 in. brush, 3 polishing cloths and one sheepskin mop mounted on a 3 in. rubber cup. Post & pkg. 1/6. 12/6. Spare sheepskin mops, 2/6 each.

16in. TUBE BY FAMOUS MANUFACTURER

Brand new E.H.T. 14 Kv. Heater. 6.3 volts, 0.6 amp., guaranteed 3 months. £9.19.6, post packing and insurance 22/6. H.P. terms available. E.H.T. and scanning components available.

Wide Angle P.M. Focus Unit, Vernier adj., state tube, 15-P.M. Focus Unit for Mullard tubes with vernier adjustment, 15/-

Ion Traps for Mullard or English Electric tubes, 5/-. Post paid. T.V. Coils, moulded former, iron core, wound for rewinding purposes only. All-can 1 1/2 in. x 1 1/2 in., 1/- each; 2 iron-cores All-can, 2 1/2 in. x 1 in., 1/6 each. These coil formers are suitable for the Prac. T.V. Converter.

Dubitter .001 10kV. working, 3/6

Primary, 200-250 v. P. & P. 2-300-300, 100 mA. 6 v. 3 amp., 5 v. 2 amp., 22/6.

Drop thro' 350-0-350 v. 70 mA. 6 v. 2.5 amp., 5 v. 2 amp., 14/6

Drop thro' 250-0-250 v. 80 mA. 6 v. 3 amp., 5 v. 2 amp., 14/6. 280-0-280, drop through, 80 mA. 6 v. 3 amp., 5 v. 2 amp., 14/6.

GARRARD RC/110 3-SPEED AUTOMATIC CHANGER

10 Records, turnover crystal head. BRAND NEW, A.C. Mains, 100 250 v. **£8.19.6** P. & P. LIST PRICE £14.10.0. 5/-

Drop thro' 270-0-270 60 mA. 6 v. 3 amp., 11/6. 250 v. 350 mA. 6.3 v. 4 a., twice 2 v. 2 a., 19/6.

Semi-shrouded drop-through 380-0-380 120 mA. 6.3 v. 3 amp., 5 v. 2 amp., 25/- Auto Trans., Input 200/250 H.T. 500 v., 250 mA., 6 v. 4 a., twice 2 v. 2 a., 19/6.

Auto Trans. Input 200/250, H.T. 350 v. 350 mA. Separate L.T. 6.3 v. 7 a., 6.3 v. 11 amp., 5 v. 3 amp., 25/- P. & P. 3/-

Heater Transformer, Pri 230/250 v. 6 v. 11 amp., 6/-, 350-0-350 75 mA. 6.3 v. 3 a. tap, 4 v. 6.3 v. 1 a., 13/6 each extra. 500-0-500 125 mA. 4 v. C.T. 4 a., 4 v. C.T. 4 a., 4 v. C.T. 2.5 a., 27/6. 500-0-500 250 mA. 4 v. C.T. 5 a., 4 v. C.T. 5 a., 4 v. C.T. 4 a., 39/6. Chassis mounting or drop-thro. Pri. 110-250 v. Sec. 350-0-350 250 mA. 6.3 v. 7 amp., 6.3 v. 0.5 amp., 5 v. C.T. 0.5 amp., 4 v. 4 amp., 32/6. P. & P. 3/6.

P.M. Speakers, closed field 3 ohm speech coil 12 in., 25/-; 10 in. 25/-; 8 in., 20/6; 6 in., 18/6; 5 in., 18/6. P. & P. each extra. 1,200 ft. High impedance recording tape on aluminium spool, 12/6 post paid.

Wave Holders, moulded octal Mazda and octal, 7/6 each. Faxolin, octal Mazda and octal, 4/6 each. Moulded B7G, B8A and B9A, 7/6 each.

Where cost and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1 and 2/6 up to £2. All enquiries, please add 1/6 up to 10/-.

R. & T.V. COMPONENTS (ACTON) LTD.
23 HIGH STREET, ACTON, LONDON, W.3

BAND III CONVERTER.

Coil kit by TELETRON, with circuit and wiring details, etc. For use with TRF or Superhet TV Receivers. **ONLY 15/-**. Cascade coil kit 17/6. Drilled chassis 3/9, or slightly larger to hold power pack components, 6/- (postage on either 6d.). Instruction leaflet only, 6d.

INDICATOR UNIT TYPE 6.—Contains VCR 97 tube with mu-metal screen, 4 valves EF50 and 2 of EB34, valveholders, CRT holder, condensers, resistors, etc. **NEW CONDITION. ONLY 39/6** (carriage, etc., 7/6).

AMPLIFIER TYPE 293A or 208A—As described in July, 1955, issue of *Practical Television*, for making a TV CONVERTER. Complete with 2 valves EF50. **ONLY 10/-** (post, etc., 2/-).

PYE 45 MC S.F. STRIPS.—Ready-made for London Vision Channel. Complete with 6 valves EF50 and 1 of EA50, and details of very slight mod. required. **BRAND NEW. ONLY 49/6** (post, etc., 2/6).

I.F. STRIP 194.—Another easily modified strip for TV. Complete with 6 valves SP81, 1 of EA50, and 1 of EF36; also mod. data. **ONLY 29/6** (post, etc., 2/6).

RECEIVER UNIT 159.—Contains 4 valves, 1 each EF50, EA50, SP81, IU35 and 24 v. Selector switch. **ONLY 7/6** (post, etc., 2/-).

R.F. UNITS TYPE 26.—Complete with 2 valves EF54 and 1 of BC52, this is the variable tuning unit covering 65-50 mc.s 6-6 metres. **BRAND NEW IN MAKER'S CARTONS. ONLY 27/6**.

POCKET VOLTMETERS.—Read 0-15 and 0-300 v. A.C. or D.C. **BRAND NEW. ONLY 18/6**.

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station) 5 mins. by bus from King's Cross. Cash with order, please, and print name and address clearly. Include postage and carriage on all items.

U.E.I. CORPN. THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1
(Phone TERminus 7937.)

COMMAND RECEIVERS.—Huge purchase from the Air Ministry. These famous compact American receivers which can be used for a variety of purposes are offered at ridiculously low prices while stocks last. Complete with six metal type valves, one each of 12K8, 12SR7, 12A6 and 3 of 12SK7, in aluminium case, size 11in. x 5 1/2in. x 3in. Used, but in good condition. Choice of models, BC 455 (6.9 Mc/s), 25 -, BC 454 (3.6 Mc/s), 27.6, BC 453 (190-550 kc/s), 59.6, and a few of the 1.5-3 Mc/s model, 65. - (Postage on all models 3/-).

COLLINS TRANSMITTERS.—The renowned American TCS models covering 1.5-12 Mc.s in 3 bands. Complete with 7 valves, employing 2 of 1625 in P.A. stage, one of 1625 in each of buffer and modulator stages, and 3 of 12A6 in oscillator stage. Provision for V.F.O. or crystal control for 4 Xial positions. Incorporates plate and aerial current meters. In Brand New Condition. **ONLY £12.10.0** (Carriage, etc., 15/-).

COLLINS RECEIVERS.—Matches the above transmitter and is exactly the same size, 11in. x 13in. x 1 1/2in. Has same coverage, and is complete with 7 valves, 1 each of 12SA7, and 12SQ7, 2 of 12A6, and 3 of 12SK7. Also has provision for Xial control. A really terrific receiver for the serious operator. In Brand New Condition. **ONLY £8.10.0** (Carriage, etc., 15/-). **OR THE TRANSMITTER AND THE RECEIVER TOGETHER, £20.0.0.** (Plus Carriage, as above).

L.T. HEAVY DUTY TRANSFORMER.—EX Admiralty. Has 3 separate windings of 5v.-0-5v. at 5 amps. and by using combinations will give various voltages at high current. **BRAND NEW. ONLY 29/6** (post, etc., 2/6).


MODEL MAKERS MOTOR.—Reversible poles. Only 2in. long and 1 1/2in. diameter, with 1in. long spindle. Will operate on 4, 6, 12 or 24 volts D.C. **ONLY 10/6** (post, etc., 1/-).

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed. Normal Primaries. 425-0-425 v., 200 ma., 8.3 v., 4 a., 6.3 v., 4 a., 5 v., 3 a. **ONLY 65/-**; 350 v.-0-350 v., 160 ma., 6.3 v., 5 a., 6.3 v., 3 a., 5 v., 3 a., **ONLY 47/6**; 250 v.-0-250 v., 100 ma., 6.3 v., 6 a., 5 v., 3 a., **ONLY 37/6**; 350 v.-0-350 v., 150 ma., 6.3 v., 5 a., 5 v., 3 a., **ONLY 37/6**; 250-0-250 v., 60 ma., 6.3 v., 3 a., 5 v., 2 a., **ONLY 21/-**. The above are fully shrouded, upright mounting, 5.5 kV. E.H.T. with 2 windings of 2 v., 1 a., **ONLY 79/6**; 7 kV. E.H.T. with 4 v., 1 a., **ONLY 89/6**. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

E.H.T. TRANSFORMER FOR VCR97 TUBE.—2,500 v., 5 ma., 2-0-2 v., 1.1 a., 2-0-2 v., 2 a., 42/6 (postage 2/-).

SPEAKERS.—P.M. 6in. less trans., 19/6; 8in. less trans., 16/6; 16in. with trans., 27/6 (post 2/-).

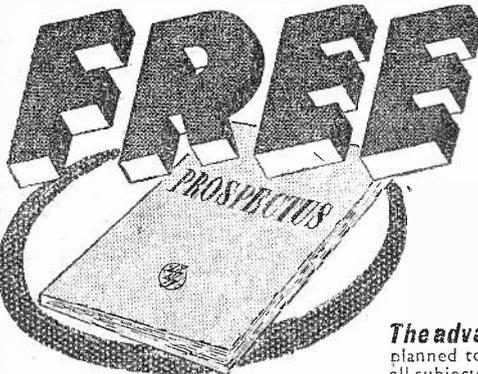CHOKES.—10H 60 mA., 4/-; 5H 200 mA., 7/6 (post 1/-).



POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME
City and Guilds Grouped Certificates in Telecommunications; A.M.Brit.I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering and Commerce.

The advantages of E.M.I. training. ★ The teaching methods are planned to meet modern industrial requirements. ★ We offer training in all subjects which provide lucrative jobs or interesting hobbies. ★ A tutor is personally allotted by name to ensure private and individual tuition. ★ Free advice covering all aspects of training is given to students before and after enrolling with us.

Equipment supplied upon enrolment and remains your property.

Courses from 15/- per month

POST THIS COUPON TODAY

Send without obligation your FREE book, E.M.I. INSTITUTES, Dept. 138K, 43 Grove Park Road, London, W.4.

NAME _____

ADDRESS _____

6/56 SUBJECT(S) OF INTEREST _____

NEW LEARN THE PRACTICAL WAY. COURSES WITH EQUIPMENT
With many of our courses we supply actual equipment thus combining theory and practice in the correct educational sequence. Courses include: Radio, Television, Electronics, Draughtsmanship, Carpentry, Photography, and Commercial Art, etc.

EMI INSTITUTES
The only Postal College which is part of a world-wide Industrial Organisation.



Get your new

BRIMAR MANUAL

The **LATEST EDITION** has **272 Pages** of **VALVE and TELETUBE DATA** **CIRCUITRY & SPECIAL COMPONENTS**

- SUMMARY OF CONTENTS**
- Valve ratings and base connection symbols.
 - Classified lists of nearly 300 valves, teletubes and selenium rectifiers.
 - Germanium diode section including ratings in various circuits.
 - Brimaristors section.
 - Radio engineering formulae and NEW circuits.
 - Brimarize section. Valves and teletubes.
 - Up-to-date substitution list of American types.
 - Equivalents and C.V. numbers.
 - Details of Trustworthy types.
 - Valuable information on Transistors.

still only 5/-

Send 5/- for your copy to: Publicity Dept.

Standard Telephones and Cables Limited FOOTSCRAY SIDCUP KENT Footscray 3333

LASKY'S RADIO

3-WATT MIDGET AMPLIFIER

A.C./D.C., very high gain. 4 valves: 2 UL41 (p.p.), UCH42, UAF42. Input voltage 100/100, easily converted to 230v. Ideal for record players, recorders, baby alarms, etc. Fully assembled, with valves and circuit diagram. **REDUCED TO Carr. 5/- 50/-**

COMPLETE 5-VALVE RADIO CHASSIS

Brand new and unused. A.C./D.C. 200/250 volts. I.F. 465 kc/s A.V.C., 4 watts output, 3-station pre-set, frame aerial fully aligned, chassis 10 x 5 1/2 in. max. height 5 1/2 in. Completely wired and ready for use, with the addition of a speaker and output transformer. Two controls, volume and station switch. Valves used: 10C1, 10F9 or UF41, 10LD11, 10P14, U404 or UY41. **LASKY'S PRICE 52/6** less valves. Post 3/6 extra.

METER BARGAINS


2 1/2 in. Moving Coil. Brand new Microammeters F.S.D. 0-750 micro/amps. 15 ohms rest. ... **21/-**

T.O. CRYSTAL P.U. CARTRIDGES. ACOS HI/G type HGF 37 as used in latest radiograms. L.P. and standard, with styl. **22/-** Post 1/-.

B.S.R. Crystal Cartridges 18/6, post 1/-.


SPECIAL OFFER! GARRARD RC.110 3-SPEED AUTO-CHANGERS

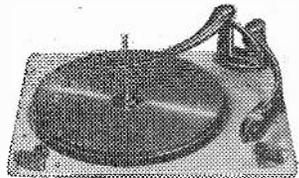Brand new in maker's cartons. Complete with turnover crystal pick-up. Incorporates automatic record size selection (mixer). Cabinet space required: 14in. x 12 1/2in. x 4 9/16in. above and 2 1/2in. below motor board. Cream and Brown enamel finish. Limited quantity only. List £14.13.0. **LASKY'S PRICE £8.19.6** Carr. 5/-. Cabinets available.



BIGGEST BARGAIN EVER OFFERED IN TV CATHODE RAY TUBES

Limited number only

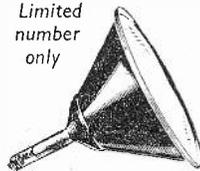

LASKY'S PRICE £9. 19. 6

Carr. & Insur. 22/6 extra.

Big Picture TV at a Price You Can Afford! **16" METAL CONE C.R.T.**

6.3 v. heater, Ion trap, 14 Kv. E.H.T., wide angle 70°, standard 38 m.m. neck, duodecal base, magnetic focus and deflection. Length 17 11/16in.

Gives large black and white picture size 11in. x 14 1/2in. Unused in original cartons. Guaranteed by us 3 months. Full data, connections and suggested time bases supplied with every Tube.

THE TUBE YOU HAVE BEEN WAITING FOR!

MUCH LESS THAN HALF PRICE!

LISTED AT £23. 9. 10

Masks, Anti-Corona Rings, Bases and Ion Traps available.

B.S.R. MONARCH 3-SPD. AUTO-CHANGERS

£7.19.6 Carr. 3/6.

PLEASE ADDRESS ALL MAIL ORDERS TO HARROW ROAD


Open all day SAT. Half day Thurs.

LASKY'S (HARROW ROAD) LTD. 42, TOTTENHAM COURT ROAD, W.1. Telephone: MUScum 2865.

270, HARROW ROAD, PADDINGTON, W.9: LADbroke 4075 and CUNningham 1379.



Practical Television

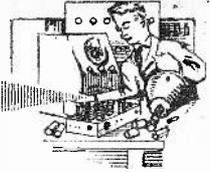

& TELEVISION TIMES

Editor: F. J. CANN

Editorial and Advertisement Offices: "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4363. Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by Canadian Magazine Post.

Vol. 6 No. 71

EVERY MONTH

JUNE, 1956

Televiews

C.R. TUBES—A NEW PRINCIPLE

DOCTOR D. GABOR, of the Department of Electrical Engineering, Imperial College, has (as noted elsewhere in this issue) developed an entirely new form of cathode-ray tube which must, eventually, give rise to a fundamental change in the design and layout of TV receivers. Although the tube has a 21in. screen, it can be as short as 4in. in length, by virtue of the fact that the electron gun is situated at the top of the tube and projects an electron beam vertically to the bottom of the tube, where it is bent by means of an electrostatic lens through an angle of 180 degrees. The beam is then tipped by means of an electrostatic deflecting field so that it impinges on the side of the tube where the fluorescent screen is located. Aberration, both spherical and otherwise, is pre-corrected before the beam arrives at the lens. Any line required for a television picture can thus be traced on the screen. The line is provided by the deflection of the beam, and the frame by the adjustment of the electrostatic field.

One of the disadvantages of the present C.R. tube is that the receiver is of an unwieldy depth to accommodate its length. It is true that the introduction of the wide-angle tube has provided some shortening, but there are limits to which this can go. The new tube is obviously the answer, and so within a few years we may expect TV receivers of a "flatness" making it possible to suspend them on a wall like a picture.

The new tube has distinct possibilities in connection with colour television, for three separate beams can be propagated in the manner described. These beams will, of course, be deflected through different angles when passing through the electrostatic field, but the actual separation, as viewed on the screen, will be small. The system makes it possible to overcome, at least partially, the register difficulty experienced.

COLOUR TELEVISION

SIR IAN JACOB, in an address to members of the International Radio Consultative

Committee, reviewing the position of colour television in this country as far as it relates to the BBC, pointed out that the BBC is using all the five channels in Band I, and that 97 per cent. of the population will be within reach of their television service by the end of this summer. There are at present nearly six million television receivers in use, which means that about 40 per cent. of the total population have television receivers. This leaves us eight million short of saturation point, which is considered to be 14 million. The BBC, whilst desirous of starting a second television network in Band III, is not able to do so because of economic reasons. The Government is not disposed to sanction a second television programme by the BBC or anybody else, but proposes to reconsider the matter in two years' time, when we shall be able to see much more clearly how colour TV can be woven into BBC plans.

The BBC has conducted and still is conducting a series of technical tests on colour TV, and they have been demonstrated in the research laboratories. The NTSC system of colour television, developed by the American radio industry and adopted by the Federal Communications Commission for public use in the United States, has been adapted to the British 405-line television standards and is being employed in the tests. The object of the tests is to determine whether this system gives a satisfactory colour picture without degrading to any noticeable extent the black-and-white picture which will be picked up on an existing receiver. In fact, the tests should show whether or not a compatible colour system could be introduced into Band I and similarly into Band III. Later experiments may be made with other systems, because the BBC is in no way committed to any particular one.


If the tests show that a system on 405 lines is satisfactory, it will mean that programmes in colour could be transmitted over the whole of the existing network. If the tests do not prove this, then there may not be an alternative solution suitable for adoption in Bands I and III.—F. J. C.

A Beginner's Guide to Television

A NEW SERIES

3.—THE TIMEBASE

By F. J. Camm

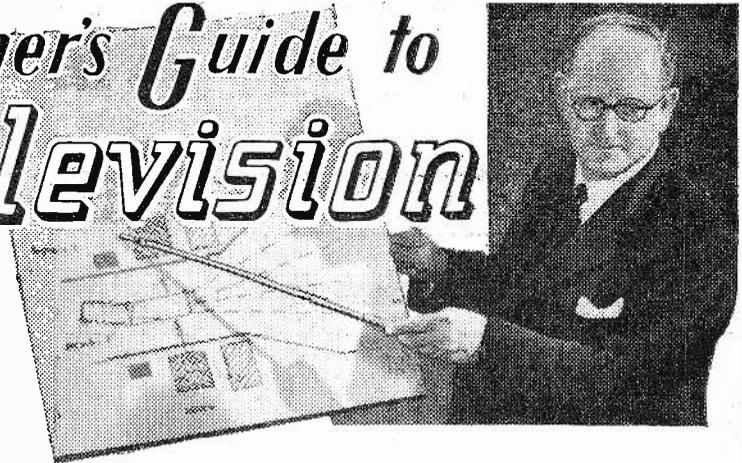

IN the previous article it was explained that timebases were employed in a TV receiver to produce the saw-tooth wave-form. It is important to state that with electro-static deflection a saw tooth voltage wave is required, and a saw-tooth current wave with electro-magnetic deflection.

The deflection of an electron beam of a cathode-ray tube is dependent on the magnitude of the current flowing in the deflector coils, and for electro-magnetic scanning it is necessary, as we have seen, to produce a saw-tooth current wave-form. Now the deflector coil possesses inductance as well as resistance, and therefore when a saw-tooth wave-form is applied to the deflector coils, the saw-tooth effect is destroyed by distortion, and to correct this, the wave-form must be such that when it is applied to the deflector coils the required saw-tooth form is produced. Let me briefly explain how the scanning spot is caused to scan the fluorescent screen by a combination of horizontal and vertical timebase systems and (refer to Fig. 11) commencing with the spot in the top left-hand corner of the tube a saw-tooth wave-form is applied to the horizontal deflector plates, with a frequency equal to the number of lines required per frame, multiplied by the number of frames per second, and a saw-tooth current wave-form is passed through the vertical deflecting coils at a frequency equal to the number of frames required per second.

The lined area on the end of the tube on which the picture appears is called the raster.

The triggering of each timebase in synchronism with the scanning of the transmitter will be dealt with later on.

Now the image received on the end of a cathode-ray tube is the counterpart of the pulses (line and frame synchronising) produced by the scanning system at the transmitting end. When received they control the scanning devices so that the spot on the

frame of the received image is in precisely the same position as the picture element being scanned at the transmitter. There are many methods of generating synchronising pulses, but that most frequently employed is a control multi-vibrator associated with the scanning system of the television camera. No matter what system is employed, however, its purpose is to mark the end of each line and each frame. The frame pulse is, of course, of longer duration, so that it is possible to distinguish between them, and the receiver separates them by this difference in duration. They are transmitted with the vision signal.

When the receiver picks up the combined signal

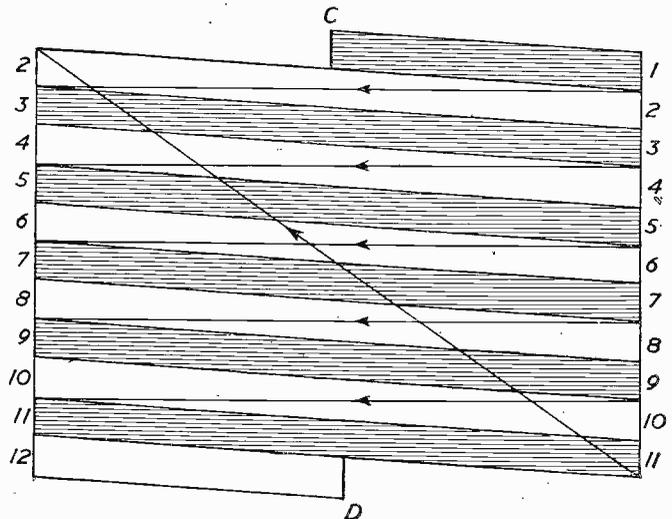


Fig. 11.—The spot movement during a complete frame scan. The spot starts at point C and traverses the lines shown shaded—that is, the odd numbers. At the end of the single scan, or first part of the interlace, when the spot arrives at the end of the line marked 11, it flies back to the point indicated by the beginning of line 2. It then scans the unshaded line, the even numbers, until it arrives at point D, when it flies back to point C, and the sequence commences again. There are, of course, considerably more than 12 lines, but the small number has been used to make the procedure clear.

and synchronising pulses it must separate them, and this is done by taking advantage of what is known as a difference in amplitude. This means that a valve is biased beyond cut-off to provide maximum signal current, and the synchronising pulses, being of greater amplitude than the signal current, raise the bias enough to permit the valve to conduct and to pass to the anode circuit free from signal variations. The pulses are then passed to a network separating the line and frame pulses.

Of course, timebases are not only used in connection with television; they are used in connection with oscilloscopes and other electronic measuring devices, and the simplest timebase of all is that which makes use of a neon tube. A neon tube timebase consists of only a capacitor, resistor, neon lamp, and a source of direct current. The principle of this simple timebase is the same as that of the more complex valve-driven circuits. It operates by virtue of the fact that if the voltage across a neon tube is gradually increased from a low value, a point will be reached when the lamp suddenly lights and passes a heavy current. This is known as the striking voltage, and if this voltage is now reduced the tube will remain alight until at some considerably lower value it suddenly goes out. This is known as the extinguishing voltage.

Suppose that a condenser C is discharged and that D.C. is applied to the input terminal of the circuit and the condenser begins to charge up through a resistance. When the E.M.F. or voltage across the condenser reaches the striking value, the neon lights and conducts heavily, thus placing a virtual short-circuit across the condenser, which discharges rapidly through the lamp, causing the voltage across it to fall rapidly. When the extinguishing voltage is reached, the lamp will go out and cease to conduct, thus removing the short-circuit from across the condenser which commences to charge again. This cycle of operations is repeated, and the frequency of repetition depends upon all the circuit constants, but in practice is usually controlled by altering the

value of the resistance or the condenser; both of which govern the rate of charge.

The amplitude of the output voltage depends upon the characteristics of the neon, and will be equal to the difference between the striking voltage and the extinguishing voltage.

The Thyatron

In what is known as the thyatron timebase, a gas-filled triode or thyatron is used, and it has certain characteristics similar to those of the neon lamp. For instance, if the anode volts are increased from a low value, a point is reached where the valve suddenly conducts heavily. This is called the firing point, and if the anode volts are decreased from this value, a point is reached when the valve, as with the neon, stops conducting. The thyatron, however, has some advantages over the neon lamp. The firing point can be varied by changing the negative bias on its grid. Also, once conduction has started, it remains until the anode volts have dropped to a very low value, say between 10 and 20 volts; whereas the neon lamp stops conducting at 100 volts, approximately. This means, in essence, that a much higher output can be obtained from a thyatron. When connected in circuit, the action of the thyatron is precisely the same as for a neon.

Thyatron, like neons, are not generally used today in connection with TV receivers.

The Puckle timebase is a well-known system still much in use. Its action is as follows. When the condenser is beginning to charge up through the charging resistor, there is only a small voltage across it, and it follows that nearly all of the H.T. voltage is across the resistance. Therefore, the filament of the valve which is connected with a junction of the condenser and resistance will be near the H.T. positive line. At

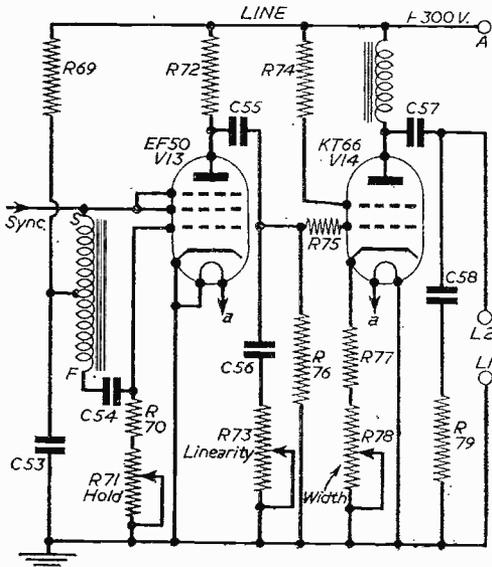


Fig. 12.—Typical simple form of line timebase.

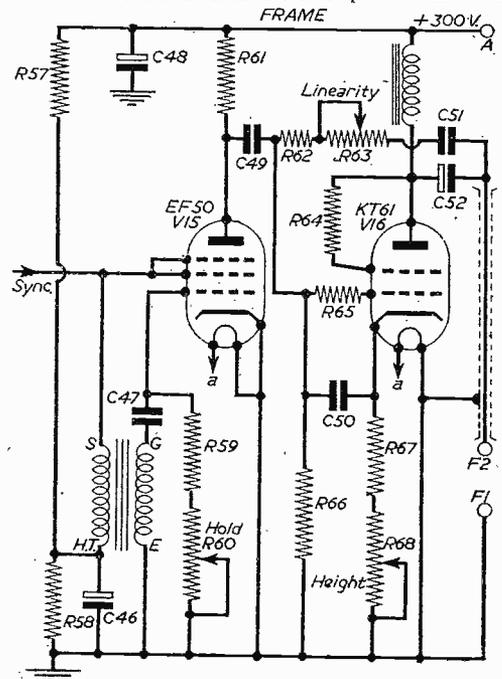


Fig. 13.—A simple frame timebase.

the same time another valve is conducting heavily and, therefore, its anode together with the grid of the first valve is near earth. Thus, the grid of V1 is very negative with respect to its cathode and the valve is at cut off point; but as the condenser charges up, the voltage across it increases, giving rise to an equivalent voltage decrease across the resistance. When the two electrodes are nearly at the same potential the first valve begins to conduct, and the consequent voltage drop across the second resistance appears as a negative pulse causing V2 to be less conductive.

Consequently, the plate of the second valve begins to rise towards the H.T. positive line, and this rise is communicated as a positive-going pulse directly to the grid of the first valve, which thus is made to conduct more heavily. In turn, this makes the plate of the first valve fall still nearer to earth potential, and the suppressor of the second valve more negative and, therefore, still less conductive. This drives the first valve grid even more positive and so on until it is conducting heavily, and V2 is driven to cut off. There are many other timebases in use to-day, but the foregoing briefly explains the operating cycle of them all.

Summarising then, a timebase is simply an oscillator in which a condenser is arranged to charge up slowly and discharge rapidly, or in some cases to charge up rapidly and discharge slowly. The resultant voltage output taken from across the condenser and applied to the plates or deflection coils of the tube causes the spot to be drawn slowly across the screen and then to return rapidly to the beginning of its stroke, when the cycle is repeated. The terms "slowly" and "rapidly" are only used here in a comparative sense. They mean that while one part of the cycle is very slow compared with the other, the whole action takes place in a minute fraction of a second. The actual time, in fact, is determined by the constants of the circuit, and can be arranged to give a repetition frequency of from a few cycles per second up to 250 k/cs or more.

The Complete Scan

In the complete receiving and transmitting system, first the image is scanned by the television camera, producing a series of varying currents which are the counterparts of the changes in light intensity along the scanning line. These varying currents are fed to a video-frequency amplifier, the output from which is passed to a limiter and pulse-generating system. The purpose of the limiter is to obviate the overloading of later stages and to limit the peak amplitudes of the combined signal and synchronising pulses to about 50 per cent. more than black. The triggering impulses are provided by the pulse generator, and it also superimposes the synchronising pulses on the signal currents, proceeding from the first video amplifier. Further amplification takes place after the limiter stage and the currents are then used to modulate the carrier wave generated by the oscillator. The modulated carrier is passed on to the aerial arrays by means of a radio-frequency power amplifier.

The aerial system picks up the signals from the transmitter and they are passed through a series of radio-frequency stages which are heavily damped in order to handle the necessary frequency band. The output is mixed with that of a local oscillator, and the intermediate frequency which results is then amplified by a series of I.F. stages of from 8 to 10 Mc/s. The I.F. stages are sometimes stagger-tuned.

By this is meant that each stage is tuned a megacycle or so above and below the actual I.F. to obtain the desired response over the wide range being handled.

We have already seen that in order to comply with the principle of persistence of vision, which gives the appearance of moving pictures, the television screen must be scanned a regular number of times every second. If the frequency of this scanning is not sufficiently high, flicker will result as in some of the early cinematograph pictures. As is well-known with the cinematograph about 24 frames per second, sometimes many more, are projected on to the screen. This does

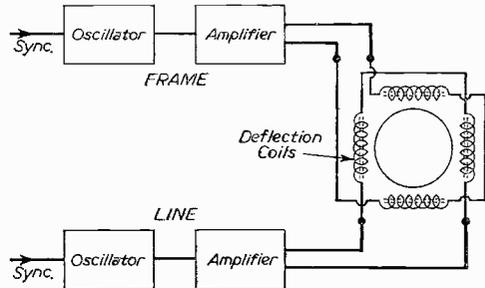


Fig. 14.—This block diagram shows how the two timebases are connected to the scanning or deflection coils in order to move the spot in two directions.

not entirely avoid flicker. The purpose of the shutter system in the cinematograph is two-fold—to cut off the light between frames and to obscure the middle period of each frame. In the result there are two distinct light projections for each frame, giving the illusion of 48 frames per second.

A repetition frequency of about 48 frames per second is also necessary with television if flicker is to be reduced to the minimum. This repetition frequency is also necessary to avoid, as far as possible, frame-ripple caused by stray fields created by the power circuits of the receiver and associated apparatus. If the frame frequency is not an exact sub-multiple of the mains frequency this trouble is likely to occur, manifesting itself in the form of irritating ripples upon the viewing screen. If a frame frequency, in the case of 50-cycle mains, of about 25 is employed, ripple is considerably reduced. On 50-cycle power systems it is theoretically necessary to employ at least 50 frames per second to reduce flicker and mains ripple. This is, indeed, a high frame frequency calling for a wide frequency band during transmission and from this point of view alone it is undesirable.

(To be continued)

A Standard Work TELEVISION PRINCIPLES AND PRACTICE

2nd Edition

By F. J. CANN

Price 25/-. By post 25/8.

From GEORGE NEWNES, LTD., Tower House,
Southampton Street, Strand, W.C.2.

Long-distance Band III Reception

PRACTICAL HINTS ON OUT-OF-AREA
RECEPTION

By B. L. Morley

THE ITA on Band III has been received at some phenomenal distances, phenomenal because they were so completely unexpected prior to the opening up of the transmitter. The reports received have encouraged many amateurs to attempt reception far beyond the normal accepted range of the transmitter; in some cases good results have been obtained, whilst in others results have been very disappointing.

Band III signals differ from Band I only in the fact that they are radiated at a much higher frequency. Under normal conditions for a given transmitter power the coverage of a Band III signal is much less than that of a Band I.

The reason for this is that the higher frequencies are not refracted so much by the atmosphere as the lower ones. It is a well-known fact that signals at TV frequencies normally radiate in straight lines from the transmitting aerial, and under theoretical conditions it is possible to receive the signals at points that are within sight of the transmitter. These are termed "line-of-sight" conditions.

Fortunately, the radiations are affected to some extent by atmospheric conditions, and a certain amount of bending of them takes place. The result is a slight tendency for the waves to follow the curvature of the earth, and so it is possible to receive them at points beyond the horizon.

The amount of refraction depends mainly upon two things; the first is the atmospheric conditions obtaining at the time, and the second is the frequency of the radiated signals.

Atmospheric conditions vary, especially in the United Kingdom! And the result is a variation in the distance from the transmitter, at which reception is possible.

On Band I it has been observed that unsettled

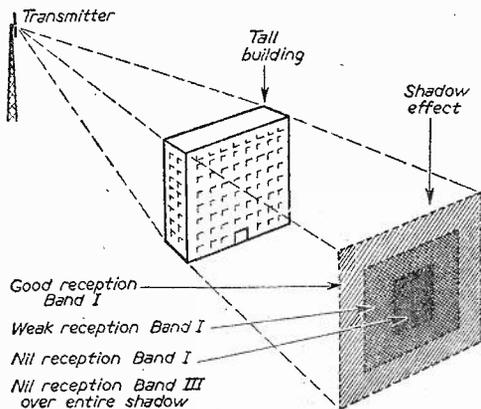


Fig. 1.—An illustration of the shadow effect.

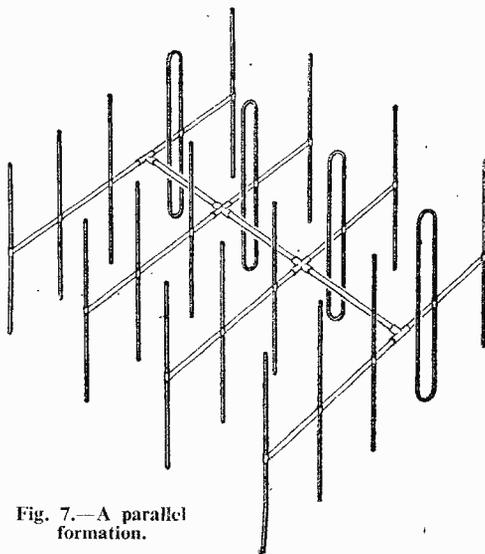


Fig. 7.—A parallel formation.

stormy weather during the summer period enhances fringe reception, while an anticyclone giving settled, calm weather will result in poor reception in the distant areas. This appears contrary to what would normally be accepted.

A curious fact is that during the winter period settled, calm conditions giving rise to fog, etc., means enhanced reception in the fringe, and the very best conditions obtain when fog stretches from the transmitter to the receiving point. Stormy weather during the winter, however, results in Band I fringe reception being below par.

The Band I conditions during winter, i.e., good reception during calm, poor reception during storm, is what should be the normal reception conditions in summer or winter. This fact is found to be true in the case of Band III, and good reception at long distances depends very greatly upon calm, settled weather.

We have been blessed during the autumn and early winter with very settled periods of weather and this has given rise to a false promise—that Band III signals reach out further than Band I. It is not argued that such could not be the case—it is an improbability; and until observations have been made over an extended period it will not be possible to say what the true conditions are likely to be.

A second factor which distinguishes Band III reception against Band I is that, by reason of the higher frequencies used, absorption is much greater. By absorption we mean that the signals appear to be absorbed by surrounding objects making up the local terrain much more than is the case with Band I. This factor tells against long-distance reception of Band III.

A third factor which is closely linked to the above is that the higher frequencies of Band III are much more prone to reflection than those of Band I and "shadow" effects are much greater. The higher the frequencies, the more nearly do they conform with the conditions obtaining with light, and shadows become very distinctive.

The effect is shown in Fig. 1. The shadow thrown by the tall building is much less defined in the case of Band I and there is a spreading of signal round the object. At a certain distance from the object there

may be only a small area where the reception is nil, and this will be surrounded by a large area where reception is possible though rather weak. This will be surrounded by a still larger area where reception, though not first class, is quite good.

The thickness and material of the structure materially affects these conditions. A few brick walls

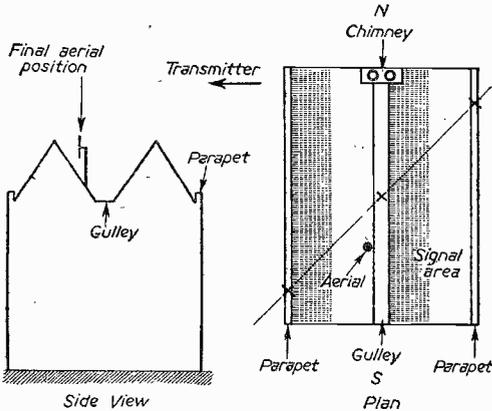


Fig. 2.—Illustrating the final positioning of an aerial.

like those of an average house will not have as much effect as a wide multi-storeyed building built of thick reinforced concrete.

In the case of Band III the "stopping" effect of the building is much greater as shown by the diagram. Because of this, it is possible to be within a very short distance of the transmitter and yet be unable to obtain signals. The shadowing is very marked indeed at some points, and where reception does not come up to expected standards, it is a good idea to probe the area with the aerial in an effort to find a better spot.

A Practical Case

An example of this shadow effect was recently encountered. The position where the TV receiver was to go was well known as a poor area, though well within the service range of the transmitter. An elaborate aerial comprising two directors, folded dipole and reflector was erected on the chimney on a 16ft. mast (Fig. 2). The result was no signals at all.

Fortunately, the house, which was an old one, was admirably designed for probing tests. It had a parapeit followed by a sloping roof running down to a gully in the centre of the roof area, followed by a second roof to a second parapeit.

A large hill lay between the house and the transmitter, the base of the hill being a matter of a few hundred yards away.

A dipole aerial was used as a probe. It was found that a usable signal could be picked up on the south end of the house and when the dipole was moved towards the north end the signal disappeared. The points of disappearance are marked in the figure by "X." A line drawn through these points gave the dividing line between signal and no signal areas. The division was distinctive and it was obvious that the choice of the original aerial site on the chimney was the worst position!

Repeated tests eventually proved that a simple dipole erected in the position indicated (most of the aerial elements being actually below the apex of the roof) gave the very best signal.

It will be seen that by careful experiment it is actually possible to plot the shadow thrown by a large object, in the path of the signal.

At the fringe, where the Band III signals are naturally weaker, the effect of shadow is likely to be much greater and must be taken into consideration when endeavouring reception.

Tropospheric Reception

Some mention was made of this type of reception in a previous article (TV DX). Briefly it can be said that certain atmospheric conditions favour the formation of "ducts" in the upper atmosphere which will carry the signals far beyond their normal range. It is undoubtedly due to these ducts that reception of Band III signals at phenomenal range have been reported. Often it is worthwhile attempting reception in what may be considered impossible condition in the hope that duct reception is possible.

Where duct reception is obtainable really remarkable results have been obtained, and the author has seen the Test Card of the I.T.A. from London at 120 miles distance received equally as well as Test Card C from the local transmitter!

Admitting the possibility of reception of the I.T.A. at good distances from the transmitter there are several points which must be observed in order to enhance the chances of success. These may be classified as the aerial system, the feeder system, and the receiver.

Aerials

Band III aerials are shorter than Band I aerials and therefore present a smaller "front" to the signals. The pick up of a similar type of aerial is therefore likely to be less on Band I than on Band III.

Against this must be set the fact that because of

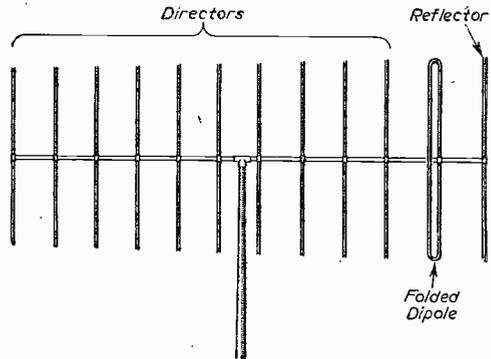


Fig. 3.—A 12-element array.

the smaller dimensions far more elements can be arranged in a Band II system than is physically possible in Band I.

For Band III an aerial with 10 directors is a practical proposition and the spacing for optimum results 0.2 wavelength can be employed (Fig. 3).

One defect of such an arrangement is the resistance given to winds at right angles to the array. For this reason an array using less elements, but doubled is often favoured. One type is increasing in popularity is the five element array comprising three directors, dipole and reflector (Fig. 4).

The gain of this array is about 10 dB. An extra

3 dB can be obtained by simply doubling the array, i.e., to use two such arrays side by side. The scheme is shown in Fig. 5.

Several commercial firms have designed aerials on this principle and it is possible to buy units and to build them up if the necessity arises.

One ingenious arrangement is two five-element arrays arranged with a slot aerial in skeleton form being used to couple the two dipoles and to effect matching.

Matching arrangements are very important and the matching must be reasonably accurate or the increased gain obtained by the use of extra elements will be more than offset by the losses due to mismatch.

These double arrays can be again "doubled up" to improve signal pick up. In Fig. 6 we have such an array, the two doubled sections are arranged one above the other, the spacing between the crossbars being a quarter of a wavelength. In Fig. 7 a parallel formation is shown. The latter has been known to give better results than that in Fig. 6, possibly because all elements are at the same height above the ground. Under practical working conditions the array in Fig. 7 was found to give about 3 dB greater gain than that of Fig. 6.

In the parallel array each section was mounted at a quarter wavelength from its predecessor. All arrays mounted in line makes the overall horizontal length of the array equal to one wavelength, which at Band III frequencies is nowhere near as bulky as may be thought; at the lowest frequencies the length is only about 5ft.

In all cases the aerial must be mounted at a very good height, and it is better to endeavour to attain

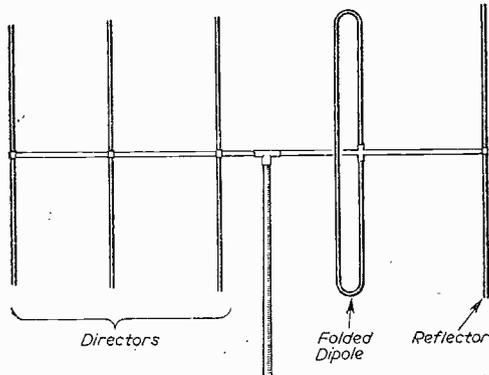


Fig. 4.—A five-element array.

a greater height than is the practice with Band I arrays. The smaller elements and hence the lightness of the array makes this more practicable than is the case with Band I.

It will be remembered that the refraction of the Band III signals is much less than that of Band I and they therefore follow a much smaller curvature of the earth. Receiving points situated at a high level therefore stand a much greater chance of obtaining satisfactory reception.

The receiving point mentioned previously 120 miles from the transmitter is situated at about 350ft. above sea level. At a point a mile away standing only 50ft. above sea level no trace of signal could be obtained.

This is a general rule and it will be found that

those reports of reception of programmes which are of entertainment value are mostly from places situated on high ground. This natural feature coupled with a good aerial system, is the main ingredient of success.

The Feeder

The feeder from the aerial to the receiver plays a very important part in long distance reception. A few figures will show this.

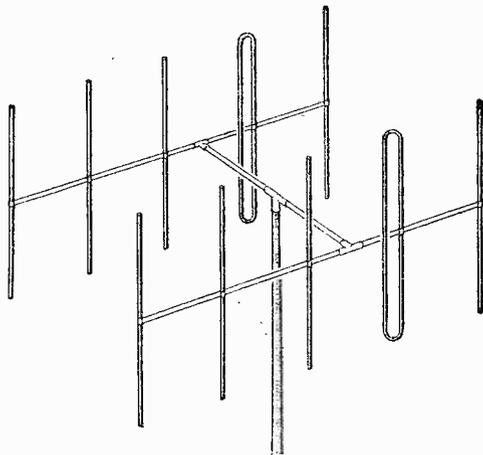


Fig. 5.—A double array.

A typical manufacturer's coaxial cable has a loss of 2.5dB per 100ft. at 45 Mc/s (note all losses will be quoted as for 100ft.). At 60 Mc/s (channel 4 approx.) the loss has increased to 3.1 dB but at 200 Mc/s (in Band III) the loss has increased to 6.2 dB. This is an appreciable figure and represents a considerable loss.

Previously we stated a case for making the aerial system as high as possible and this naturally entails a long feeder. It is quite usual therefore, to have cases where 100ft. of coaxial feeder cable is a necessity. The losses become real.

The case for balanced twin cable is even worse. A typical balanced twin cable will give a loss of 3.8 dB at 45 Mc/s, of 4.35 dB at 65 Mc/s while the loss at 200 Mc/s is 8.0 dB.

Where screened feeder of the balanced twin variety is used to overcome interference effects then, the losses are greater, typical figures being 4.5 dB at 45 Mc/s, 5.4 dB at 65 Mc/s and 10.0 dB at 200 Mc/s.

When it is realised that a change in signal strength of 1 dB can be seen on the screen then it is obvious that losses must be kept as low as possible.

Fortunately there are special low-loss cables available some of which have been especially developed because of Band III conditions.

Some typical figures for this low-loss cable are 1.2 dB at 45 Mc/s, 1.5 dB at 60 Mc/s and 2.6 dB at 200 Mc/s.

These figures are for coaxial cable with a semi-airspaced core. Note that for this cable the loss is 2.6 dB against 6.2 dB, for ordinary coaxial.

The cost of this type of cable is rather more than that of ordinary coaxial, but this is well worth while when it is considered that the gain obtained by a double array, an extra 3 dB, can be more than lost by use of ordinary coaxial cable.

Matching

Another important point in connection with feeders is that matching must be such that the standing-wave ratio on the feeder is not more than 3 : 1. This means that the mismatch of impedance values between aerial and feeder must not exceed 2 : 1.

To effect matching it is common practice to insert a quarter-wave matching section between aerial and feeder. The methods of calculating the impedance of the matching section have been dealt with before in these pages. It is sufficient to point out here that matching section in the region of 100 ohms are quite common and low-loss cable of this impedance can be bought from most dealers.

Where balanced twin cable is called for then low-loss types can be obtained. There is also available a cable of 100 ohms impedance and also a low-loss cable of 300 ohms balanced-twin, where the receiver calls for this class of cable.

Diplexers

Matching units for combining aerials of Band I and Band III into a single cable are available under various trade names such as a Diplexer etc. These units effect impedance matching between the two types of aerials but they usually introduce some loss

and for fringe area reception it is considered better to employ an entirely separate cable.

It should be noted that it is often possible to use a Band III aerial on Band I and this is better practice for the fringe Band III area where there is a local Band I transmitter, than to attempt to use a Band I aerial for Band III reception.

One point which should not be overlooked is that the radiation pattern is probably changed with the frequency, and it may be found that this practice causes undue interference pick-up on Band I.

Practical Feeder Arrangements

Where low-loss feeders are used it is important to realise that the cable is a lot more fragile than ordinary coaxial. In the latter case the polythene core is solid and the cable will withstand quite a deal of bending; in the case of the low-loss feeder, however, the core is largely of air and if the cable is bent sharply then the air spaces will be crushed. This means that the actual characteristic impedance may be altered at the point of crushing and the cable will exhibit losses and reflections from the point of damage. Sharp bends should be avoided and the cable should be treated with the greatest of care. It should be kept clear of drain pipes, etc., and any overhead wiring, electrical or telephone.

The Receiver

Practical experience has suggested that, at the moment, receivers fitted with channel changing facilities integral as part of the receiver give better results at long distance on Band III than most convertor arrangements. The latter are generally spoiled by excessive noise.

Receivers themselves vary from one to another, and some will be found to give quite exceptional results. Both home-constructed and commercially built convertors have been tried and they all seem to fail more or less, in this respect. A good turret-tuned model takes some beating!

Pre-amplifiers

It has been proved that the signal can be boosted by the use of pre-amps and those of the low-noise type are generally favoured.

Where conditions are really difficult because of noisy local man-made static then a high aerial system with a masthead pre-amplifier has much to recommend it. Pre-amplifiers using R.F. pentodes are not generally favoured, but quite a good combination is a pre-amp comprising a cascade stage followed by a R.F. pentode stage. The advantage of the R.F. stage with the pentode is that it prevents re-radiation at intermediate frequency, this can be really troublesome where convertors are used.

Weather

It has been noticed that at extreme ranges, a really good signal can be enjoyed for a considerable period but the first few drops of rain will cause the signal to vanish without trace! If no results are obtained at first then wait for more favourable weather conditions.

Although it is unwise to be dogmatic about the subject it does appear that it is the local weather conditions which have the greatest effect. A rain-storm at the transmitter area will have but little effect at the fringe but those few drops of rain at the fringe exert a tremendous effect.

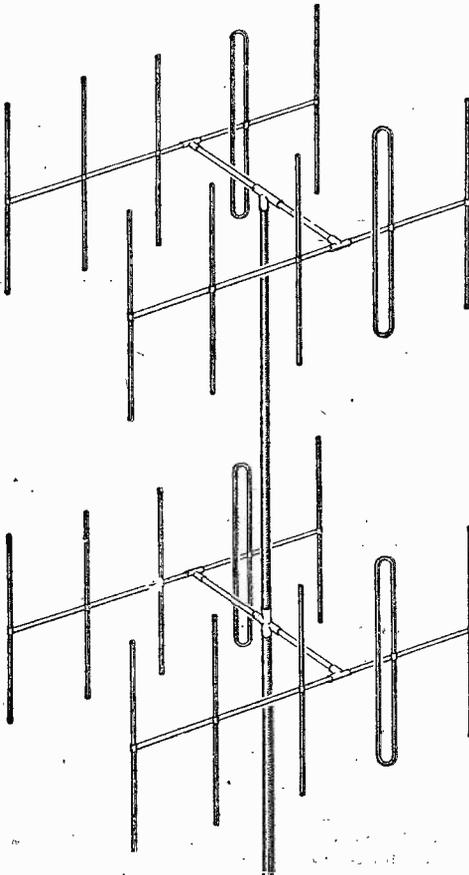


Fig. 6.—A doubled-up array.

COLOUR TELEVISION

THE SECOND OF A NEW SERIES DEALING WITH THE PRINCIPLES AND PRACTICE
OF MODERN TELEVISION IN COLOUR

2.—THE VARIOUS SYSTEMS

By C. Grant Dixon, M.A.

IT was in 1926 that J. L. Baird first gave a demonstration of the transmission of a living image by television. Few people realise that only two short years later, in 1928, he also demonstrated television in colour to a meeting of the British Association. Of course, the definition was poor, but it is a striking tribute to the advanced outlook of this television pioneer. The system which he employed depends on the fact that the eye blends together images which are presented in rapid succession. This effect is called persistence of vision and is, of course, the means whereby we can view a normal television image. It will be recalled that to transmit a coloured television image it is necessary to transmit colour information in each of the three primary colours: red, green and blue. Baird transmitted a complete image in each of these colours in rapid succession, a process known as frame sequential scanning. In those early days scanning was performed by means of a rotating Nipkow disc, and Baird's colour disc had three sets of spirally placed holes with appropriate colour filters mounted over them (Fig. 1). Each revolution of the disc caused the picture to be scanned three times, once for each colour, and at the receiver a similar disc built up a coloured image.

Frame Sequential System

Subsequent work on colour television followed Baird's early experiments and as the television image became better in quality due to the use of an increased number of lines, so the colour image became better, too. In 1938 Baird demonstrated colour pictures in a London theatre on a screen 12ft. by 9ft. A 120-line picture was used and the scanning was effected by means of a combination of a mirror drum with a slotted disc. In the post-war period the CBS in America developed a frame sequential system which was provisionally adopted by the FCC, but which was later rejected in favour of an all-electronic system. The CBS system transmitted 24 complete colour pictures a second using a 405-line interlaced raster similar to that used in this country. The frame timebase was set to run at 144 cycles/sec., two vertical scans produced a fully interlaced picture, and this was repeated three times to produce a complete colour picture. The colour change took place 144 times a second, however, so the scanning sequence was as follows:

- 1st frame : Odd lines scanned in red.
- 2nd frame : Even lines scanned in blue.
- 3rd frame : Odd lines scanned in green.
- 4th frame : Even lines scanned in red.
- 5th frame : Odd lines scanned in blue.
- 6th frame : Even lines scanned in green.

The camera for this system was a normal television camera with modified timebases and a disc of colour filters mounted immediately in front of the photocathode. This disc was driven by a motor whose speed was controlled by the frame timebase. At the

receiving end, a similar disc was rotated in front of the screen of a normal television set (Fig. 2) and maintained in exact synchronism with the camera disc by a system of electronic control of the motor speed. Thus, when the red filter was in front of the camera, a signal corresponding to the red component of the picture was transmitted and actually viewed as red light through the receiver filter. This use of an electric motor was obviously not a very satisfactory solution to the problem of colour television for the home viewer, but for closed circuit industrial television it has proved useful, and Messrs. Pye, of Cambridge, have developed the same system in this country and demonstrated it both here and on the Continent. The system is capable of giving very good quality pictures, but it suffers from the disadvantage that rapidly moving objects occupy successive positions which are laterally displaced and this gives an annoying colour-fringing effect. In the U.S.A. care had to be taken with the elimination of hum as the frame frequency was not related to the frame frequency of 60 cycles per second. In this country Messrs. Pye used a frame frequency of 150 cycles per second, which could be locked to the British 50 cycle mains, but, even so, the presence of any hum on the raster would have given a similar colour-fringing to that mentioned above and careful magnetic shielding was necessary.

Line Sequential System

Another process was developed in the United States by Color Television Inc., in which the colour elements were lines, and the system is usually called the line sequential system. Clearly, the mechanical

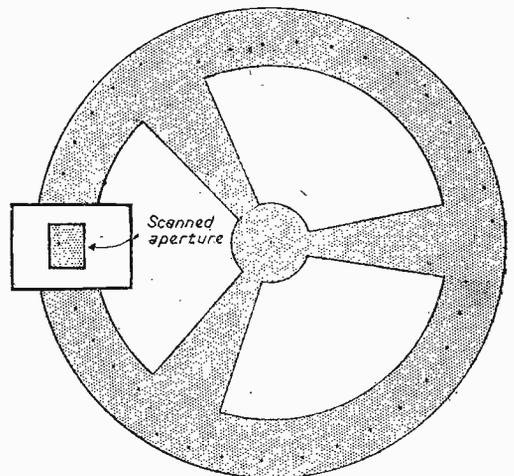


Fig. 1.—Showing the principle of Baird's original colour disc scanner which used three spiral sets of holes, one set for each colour.

movement of filters at line speed is out of the question, so this system is entirely electronic. At the transmitting end the camera lens has a group of mirrors behind it which produces three images side by side on the camera photocathode (Fig. 3). By using special mirrors known as dichroic filters, which reflect light of one colour and transmit all other colours, it is possible to get the three images in the three primary colours. If the camera photocathode is now scanned from one side to the other, the spot will traverse one line of the red image, one of the green image, and one of the blue image before it reaches the other side. The camera line frequency must, therefore, be a third of its normal value, and if this reduced line frequency is used at the receiver three images will be formed side by side on the cathode-ray tube. These images may be given the three primary colours by the use of suitable filters or by making a cathode-ray tube the screen of which will fluoresce in the three colours in adjacent areas. Of course, three images are no good as they stand and they must be combined optically to form a complete coloured image; this is usually done by using three projection lenses and projecting on to a translucent screen. It should be noted that in the frame sequential system both the line frequency and the frame frequency have to be raised, but in the line sequential system the frame frequency remains the same as for black and white. This is because the green image has a much higher luminosity than the red or blue, and a flicker is produced at the reception rate of the green. In the frame sequential system, therefore, it is necessary to ensure that the repetition rate of the green frames is sufficiently high to avoid this flicker. In the line sequential system the repetition rate is already very high and the question does not arise in this form; the luminosity of the green lines gives rise, however, to an annoying line-crawl. Another disadvantage of the system is the difficulty of registration of the three images which demands almost 100 per cent. linearity in the line timebase both in the camera and in the receiver.

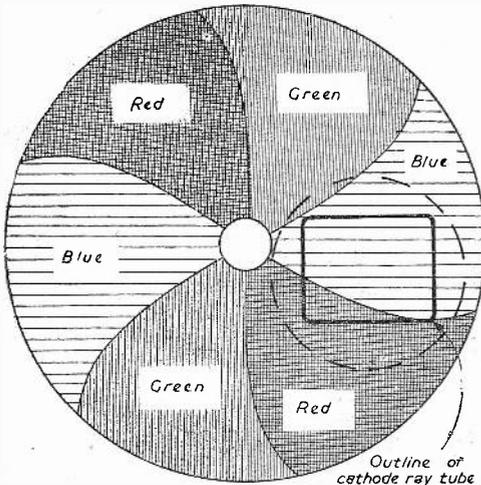


Fig. 2.—The actual shape of the colour filter disc used in the CBS frame sequential system depends on its position with respect to the cathode-ray tube. It must be over twice the diameter of the tube, and projection tubes were often employed on account of their small size.

Dot Sequential System

A third system was proposed by the RCA in which the colour sampling rate was increased to about 3.58 Mc/s, thus giving a dot sequential system. Flicker was eliminated by the use of this high frequency, and with the problem of flicker solved it became possible to consider much brighter pictures at the receiving end. A number of difficulties were introduced by the choice of this very high rate of

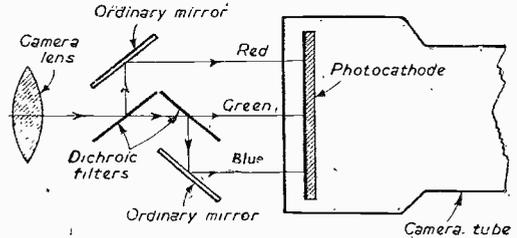


Fig. 3.—Showing how the three images are produced side by side for the line sequential system.


colour sampling, not the least of which was the synchronism of the receiver sampling circuits with those at the transmitter. Several important features of this system have been carried over into the present American system, so it is not proposed to discuss the dot sequential system in detail.

Compatible Systems

In 1949 and 1950 the American FCC held an inquiry into the various colour television systems with a view to giving official approval to one system which would then be adopted nationally. After hearing the claims of the three systems outlined above, the FCC licensed the CBS frame sequential system, which undoubtedly was the simplest from the technical point of view and was capable of giving very good pictures. Nevertheless, it was felt in many quarters that it was an unwise decision for two reasons: first, an all-electronic system would be preferable; and second, a compatible system would be preferable. The phrase "compatible system" implies that the colour system must transmit pictures which can be resolved as black and white pictures on a normal receiver. The line and frame timebases must be run at the same frequencies as for black and white reception, and the colour information has to be transmitted by some means or other leaving the luminance signal to give a black and white picture. Thus it was that in less than two years the FCC had withdrawn its licence and called for a complete shut-down to all colour television production. Following this, as a result of co-operation amongst the radio and television manufacturers, a new system was evolved in which the chrominance signal was sorted from the luminance signal and transmitted on a special subcarrier within the same channel as the normal black and white television. This simultaneous system was approved by the FCC and is now the standard colour television system in the U.S.A. A modification of this system has been developed in this country to fit in with the British 405-line picture and the BBC have been making engineering tests of this modified system as was reported in the February issue of PRACTICAL TELEVISION.

(To be continued)

Servicing TELEVISION RECEIVERS

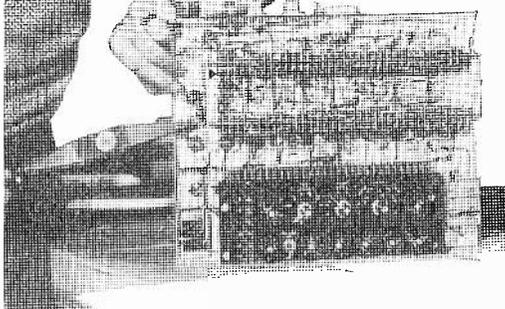

No. 19.—FURTHER NOTES ON CATHODE-RAY TUBES

By L. Lawry-Johns

IN the January issue we itemised some of the faults which occur in cathode-ray tubes and gave some practical means of overcoming the more common of these defects. A reader has taken us to task for not being more comprehensive and for making a misleading statement. This was in reference to a fault which often happens on Mullard tubes in particular, where an internal short produces a "no raster, no E.H.T." condition.

We said that in the event of an internal breakdown there was little which could be done and that the tube would have to be replaced. In some cases this is quite true, and, indeed, some time ago it was so in nearly every case. This particular defect, happily, does not seem to occur so frequently now, however, and in the majority of cases the tube can be saved. It should be understood that the following procedure is applicable to Tetrode and Pentode tubes, as shown in Fig. 1, and not to triode tubes at all, for obvious reasons.

Usually, the defect shows in the receiver as an E.H.T. fault where no spark is available from the anode cap of the C.R.T. or from the E.H.T. rectifier heater. However, when the anode cap is removed from the tube, the E.H.T. immediately comes to life and vigorous sparking results when the cap approaches any metallic body or human body! It should be understood that an upset in the receiver circuits could cause this condition. If the grid voltage is in excess or even is slightly under that of the cathode, in some cases the effect is simulated. In the majority of cases, however, it will be found that the fault is usually met where a tetrode or pentode tube is employed, and the usual cause is a leak or short between the cathode and grid of the tube.

The base holder is usually of the duodecal type, and the connections are shown in Fig. 2.

The valve pins are numbered from the spigot in a clockwise direction. Thus pin 1 is a heater, pin 2 is the control grid. Now on some bases only half of the base is used so that it appears semi-circular. Base tags are still numbered the same, 1 and 2 to the left of the spigot, 12, 11 and 10 to the right. This represents a tetrode base and all up-to-date bases

employ the complete circle of tags as pin 7 may be required for a pentode tube. In some cases this may be found shorted to pin 11 (cathode) and in others a separate lead may be taken to it. Even where a tetrode tube is in use, pin 7 may be shorted to 11 to provide for the fitting of a pentode tube at a later date. Taking an example, a PAM 14in. model was examined for a "No Picture" fault. The customer stated that the picture would appear at odd intervals, and then vanish again. The set was switched on, allowed its usual three minutes to warm up, and the fact that the line timebase whistle was not of-normal pitch was noted.

No EHT was present at the tube anode.

The EHT connection was removed and immediately the line timebase whistle became normal and the

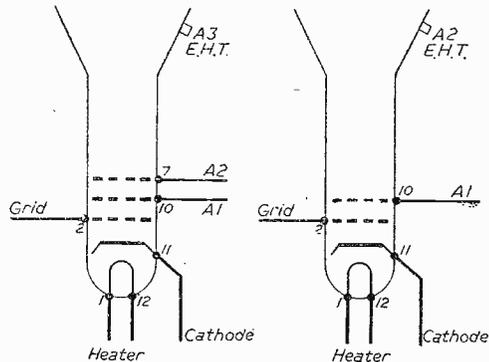


Fig. 1.—Showing pentode base and internal connections. Fig. 1a.—Showing tetrode base and internal connections.

EHT sprang to life, with healthy sparks and the usual "unconnected" hiss. Upon replacing the connection, the screen lit up momentarily and the EHT once more disappeared.

The tube was a tetrode with tag 11 shorted across to tag 7 which was, in this case, an unconnected pin. The shorting lead was removed from tag 7 and connected to tag 2. The lead to tag 2 was then removed and placed on to tag 10. The usual A1 connection was removed from tag 10 and taped up. The set was tried again and the customer could detect no difference between the displayed picture and the original with the A1 lead connected. The writer noticed a fall off of "attack" and general brilliance but the result was extremely gratifying and a really good test card could be resolved.

The customer was particularly pleased as he could now advance his brilliance control without the picture losing width and focus upon approaching maximum. This was, of course, due to the emission of the tube being lower and thus it was not tending to overload the EHT supply at excessive brilliance.

This was a case where a cathode-to-grid short in a tetrode tube was overcome by using the A1 grid as the control grid and strapping the cathode to the control grid permanently. The A1 supply lead was left disconnected.

In another case the receiver was a Ferranti 17K5. Similar symptoms were noted and the tube base showed that tag 10 was strapped to tag 7. Pin 7 was actually in use, the tube being of the pentode type. In this case, the strap was removed from between 7 and 10, the lead to 10 was taken to 7 and the grid lead to 2 was taken to 10. Then a shorting lead was wired across from 11 to 2. The result was that the tube functioned in every way as good as before the short occurred.

In this case the wiring had been arranged so that the tube continued to operate as a tetrode.

It is stressed that the emission of the tube must be basically good if a reasonable picture is to be resolved on a tetrode tube, such as an MW31/74 and others in the 14in. and 17in. range as the loss of voltage on the first anode is considerable, and the tube is really functioning as a triode which it was never intended to be.

An example of what is meant was the case of a small Bush TV22. The picture had been quite satisfactory until it became uncontrollably brilliant and failed altogether. The tube was an MW22/16. A

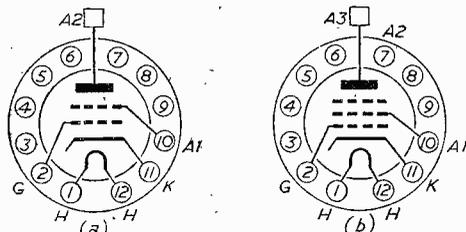


Fig. 2.—Showing tetrode base (a) and pentode base (b).

grid-to-cathode short was diagnosed and the tag wiring was duly modified. The result was an extremely poor picture: A new tube was fitted, using the base holder still wired for the fault condition, and a very reasonable picture was obtained. The point having been made, the proper wiring was restored and the picture was still further improved. Thus, before the letters commence to pour in! A worn tube is unlikely to operate satisfactorily with rearranged base wiring, unless it is of the pentode type and is rewired as a tetrode. Another tube fault which was touched upon in the January issue but which merits further comment is that of a partially shorted heater. When a tube suddenly displays symptoms which indicate a soft or low emission condition the receiver being of the A.C./D.C. type, a glance at the rear of the tube neck will often show that the heater is glowing a dull red rather than the more usual healthy yellow. A voltage check with a meter will indicate that the volts drop across the heater pins is approximately half of what it should be. Another point which may be noticed is that the tube is of the Ion Trap type, where a small magnet

is employed to straighten out the electron beam.

Now the effect of this magnet upon the tube heater is not generally realised.

If the tube neck is examined, a painted line will be seen which indicates the approximate position for the Ion Trap magnet's initial alignment. Also on the magnet itself is a small arrow. When the magnet is aligned with the arrow toward the tube face it will be approximately on the line. If the magnet is rotated 180 deg. to the other side of the tube neck the tube will not illuminate due to the electron beam being thrown completely out of line.

If, however, the Ion Trap is reversed so that the arrow points to the rear, correct operating conditions are obtained with the magnet on the opposite side of the neck to the line.

This may be very elementary stuff for many of the readers, but it is none the less essential for the not-so-well-informed to be clearly briefed upon this point.

This is the reason: in a large number of cases where a partially shorted heater exists, movement of the Ion Trap magnet will cause the fault to clear and recur as the magnet rotates about its optimum setting.

Quite often, by completely reversing the position of the Ion Trap magnet, i.e., so that it is rotated through 180 deg. and the direction of the arrow is reversed, a fault condition can be cleared. If possible, rotation of the tube itself may help initially to clear the short although a slight tap on the neck of the tube will often perform the same function.

In an earlier article in this series it was mentioned that rotation of a tube is often beneficial. This is particularly valuable where an internal short exists and it is not convenient to install an isolating transformer.

In a large number of cases a heater-to-cathode short can be cleared by this means, at least temporarily. Also, before leaving this heater-to-cathode short subject, the fault condition of no EHT can quite easily be caused by this defect. If a tube heater is in an A.C./D.C. chain, and is the last heater to chassis, as is usual, an internal short will result in the cathode being virtually taken to chassis potential, leaving the grid biased positive. Thus the condition of heavy beam current is provoked and the EHT supply may be overloaded.

The golden rule, therefore, is to check the tube base voltages before taking any action.

COMMERCIAL TELEVISION IN THE NORTH


ON May 3rd Winter Hill, the Independent Television Authority's first station in the North of England, came into programme service.

This marked the climax to seven months' intensive work by Marconi's Wireless Telegraph Co., Ltd., who have been responsible for building the entire station.

Some idea of the task involved may be gathered from the fact that before constructional work could begin a layer of peat of up to 7ft. in depth had to be removed before a solid foundation was reached. The severity of the past winter was an additional handicap.

The Marconi vision and sound transmitters installed are $7\frac{1}{2}$ kW and 2 kW respectively. The outputs from these are combined and fed to a 16-stack aerial, producing an effective radiated power (vision) of 100 kilowatts (see illustration on page 515).

The aerial tower is 445ft. in height and the station is sited at a height of 1,440ft. above sea level.

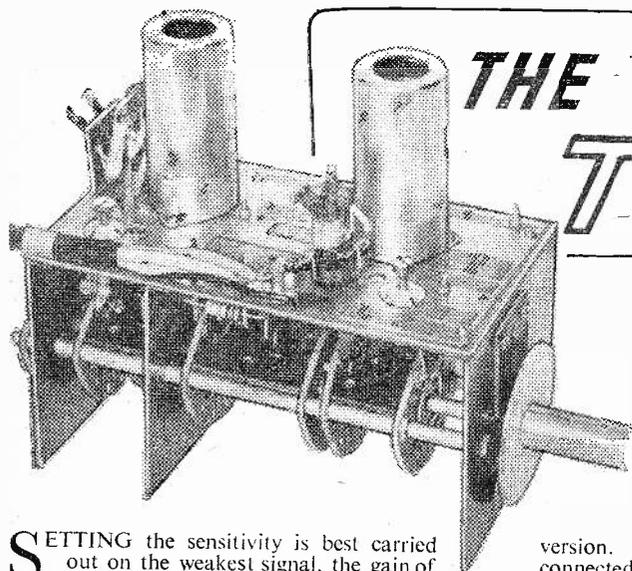

THE V.M. TV Tuner

DETAILS OF A 3-STATION TUNER
DESIGNED FOR THE VIEW MASTER,
BUT WHICH MAY BE USED WITH
OTHER RECEIVERS

(Concluded from page 442 May issue)

SETTING the sensitivity is best carried out on the weakest signal, the gain of the tuner being at maximum when C5 is connected to chassis and the I.F. amplifier gain control adjusted to give a picture having the correct degree of contrast. If now the tuner is switched to another channel with a stronger signal the variable resistor connected to SW5 is then readjusted, in which case the gain of the I.F. amplifier is reduced and the picture contrast remains constant. This is the preferred arrangement where the receiver is located anywhere but in a transmitter swamp area.

An Alternative

An alternative arrangement where the receiver is located close to a transmitter is to set the I.F. amplifier contrast control to the correct setting on the weakest signal with SW5 connected to C5 on the tuner and then taken direct to chassis so as to obtain the maximum sensitivity on the tuner. Then switch to the alternative channel which will be the strongest and adjust the variable resistor which will be connected to C5 via SW5 to give the correct gain and contrast. Switching from one channel to another should now enable a picture having satisfactory sensitivity to be obtained without necessitating further readjustment.

Models for Channels 2-5


Some confusion appears to have arisen in the minds of those View Master owners whose receivers operate on Channels 2-5 as they appear to be under the impression that the modification details given in the December, 1955, issue relate only to the Channel 1 View Master intended for reception of Alexandra Palace.

The instructions which were published did, of course, relate to all View Masters irrespective of the Channel for which they were originally designed, but on those receivers operating on Channels 2-5 it will now be necessary to remove the existing sound rejector circuits as they are no longer required. The modified bridge "T" rejector being used instead.

The one other point leading to confusion is condenser C6 shown on Fig. 4, page 296 of the December issue, as this condenser only appears in the Channel 1

version. C6 has a capacity of 2 pF and must be connected as shown from the anode of V1 direct to the grid of V6. The grid coil of V6 is specified as having $9\frac{1}{2}$ turns, and in parallel there must be a 10 pF condenser. The combination of the two condensers and one inductance thus operates to "suck off" the sound I.F. from the combined sound vision output to V1.

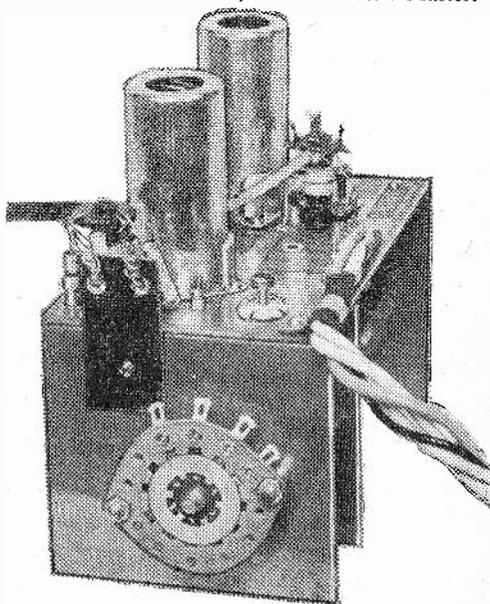Finally, it may be repeated that, although referred to as the View Master Tuner, and it was, in fact, designed primarily for that particular receiver, it may be used with any I.F. strip designed for 34.65 Mc/s vision, and 38.15 Mc/s sound. The only point to note is that the input arrangements should follow similar lines to those adopted in the View Master.



This rear view of the V.M. Tuner clearly shows switch SW5, referred to last month.

The New London Transmitter

ADJUSTING TELEVISION RECEIVERS TO THE NEW SYSTEM

By "Erg"

THE London television transmitter at Alexandra Palace was the first television transmitter in the whole world to radiate regular television programmes. Since its opening in 1936, new techniques have been evolved and advantage is being taken of these developments, in the opening of the replacing transmitter at Croydon.

The London transmitter operated on principles similar to those used in normal broadcasting. Amplitude modulation was employed and each sideband was used—termed double sideband modulation.

With present-day techniques it has been found practical to radiate on one sideband only, and this is the common method employed to-day. But for this system we should not be able to accommodate so many transmitters within the frequency spectrum allotted to television.

Although the system is quite often commonly referred to as single sideband this is not a true description; the more correct term is vestigial sideband.

The Two Systems

Fig. 1 shows the double sideband method of transmission such as has been used from Alexandra Palace. The vision carrier is set at 45 Mc/s and radiation takes place for 3 Mc/s each side of the carrier to cater for the full vision signal. The sound transmitter is radiated on a carrier 3.5 Mc/s from the carrier, i.e., at 41.5 Mc/s.

In the case of transmissions as shown in Fig. 1, the method used at the receiver was to adjust the R.F. and I.F. stages to receive both sidebands;

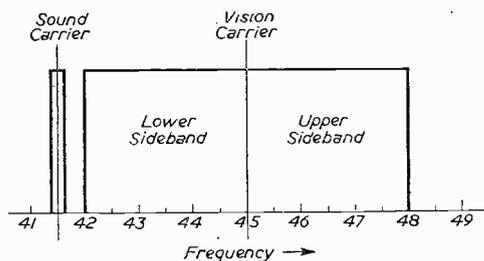


Fig. 1.—The double sideband.

thus the R.F.^e and I.F. sections needed a bandwidth of 6 Mc/s.

The vestigial sideband method is shown in Fig. 2. The sound is set on its carrier at the same position as before but the vision has part of the upper sideband suppressed. It is not practicable completely to suppress the upper sideband—a small proportion remains unsuppressed and this is transmitted.

In practice the upper sideband is transmitted up to 0.75 Mc/s.

Now it is obvious that it is not practicable to effect transmissions which cut off dead as shown by the straight vertical lines in Fig. 2. Actually severe attenuation takes place above 0.75 Mc/s above the carrier and at 2.75 Mc/s below the carrier and the result is more like that shown in Fig. 3.

Further inspection of Fig. 3 shows that this will not give a true result as, although correct response will be obtained for the higher frequencies, at the lower frequencies we still have double sidebands. This means that if our receiver was adjusted in this manner the output of the lower frequencies would be doubled.

The effect on the screen is over-emphasis of the lower frequencies and the picture would appear smeary especially in the blacks, black portions having long tails to the right of them.

To overcome the problem, the response of the receiver should be such that the carrier is set at half-way down the slope (6db down). The detector will now respond correctly and the small portion of double sideband will be added to that attenuated below the carrier and correct conditions will be obtained.

It is important therefore to ensure that the response of the receiver is adjusted so that it is 6db down on the carrier.

Classes of Receivers

Sutton Coldfield transmitter was the first of the single sideband television transmitters to be constructed in this country and at this time a change-over began to take place in the design of receivers. Until the advent of Sutton Coldfield most receivers were of the "straight" type R.F. amplification being used throughout. A superhet was something of a rarity.

These straight receivers built for the London transmitter were mostly tuned so that both side-

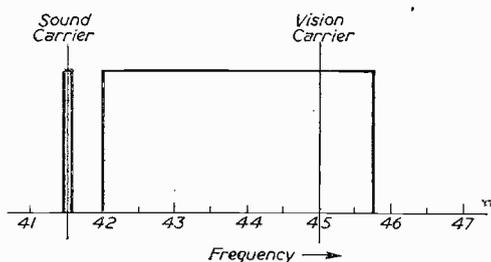


Fig. 2.—Vestigial sideband.

bands were covered. The superhets began to become more prominent mainly because of manufacturing processes.

A straight receiver was quite efficient but where different channels were being used, a different receiver had to be built for each channel. To avoid a lot of duplication and to ease production difficulties, superhets came to the fore and these were mostly designed for lower sideband operation.

At first two classes of superhets were made, some designed for Sutton Coldfield and some for London. For the Midland transmitter single sideband operation was required and this was effected in the I.F. stages, rejector coils being fitted to cut the sound channel from interfering with the vision.

The London receivers were either double sideband, or in some cases, upper sideband reception for vision. This latter method enabled the receivers to be operated without the need for rejectors on the vision strip, to cut the sound from the vision.

Nowadays, with multi-channel receivers, all commercial receivers are arranged to operate on the lower sideband.

Straight Receivers

Where straight receivers are employed, then two troubles may arise from the new transmitter. The first is sound on vision, and the second is a deterioration in quality of the received image, the pictures appearing less sharp.

To remedy the first trouble two or more sound rejectors may be required. These can be made quite easily by winding about 9 turns of wire on a $\frac{1}{2}$ in. diameter coil form and tuning with an 0.30pF condenser. In some cases a 22pF condenser can be connected across the coil and the coil tuned by using the core.

There are two methods of connecting the rejector. One is by grid insertion and this is shown in Fig. 4. The coil is tapped at two turns up from the bottom as shown and connected in the grid circuit.

The second method is by cathode insertion and this is shown in Fig. 5. The coil is connected directly in series with the cathode of the R.F. valve.

The placement of the coils will be determined by the number of R.F. stages and where the sound is tapped from the R.F. circuits. As a guide, a four valve I.F. strip (4 I.F. valves) could have one rejector at valve 2 and one rejector at valve 4.

Under normal circumstances two rejectors should be sufficient especially if they are made high-Q using 22 s.w.g. wire and low-loss coil forms.

The best method of adjustment would be to retune all R.F. stages to peak to the vision signal and then to adjust the rejectors so that there is minimum sound breakthrough. Having done this then the R.F. circuits should be stagger tuned for the best possible quality, and this is best done on Test Card C.

By careful adjustment it should be possible to get a picture of the same quality that was obtained previously from Alexandra Palace.

Double Sideband Superhets

In the case of a double sideband superhet somewhat similar results may be noticed. This is some interference from sound, and some loss of picture quality. (The sound interference will not, of course become noticeable until the alteration of the television to single sideband is attempted.)

To cut the sound from the vision will require two or more rejectors which should operate at sound I.F. As the I.F. of receivers vary there may be some necessity to experiment. As a guide an I.F. of about 9.5 Mc/s can be used and a coil comprising about 22 turns 34 s.w.g. enamelled wire on a $\frac{3}{8}$ in. diameter coil form, tuned with an 0.30 pF trimmer, should work in most circuits.

Great care must be exercised in placing these rejectors; they must be screened and must not cause loss of quality through destruction of the existing pass band.

To tune the receiver it will be necessary to retune the R.F. sections to the lower sideband; if instruments are not available much care and patience will be required.

Having done this then the rejectors should be tuned to cut the sound on vision effects but the quality of the picture must be guarded. Some variation of the oscillator is permissible, but this is best done on Test Card C.

If it is found that the use of the traps seriously affects the quality of the picture, then the coupling between the traps and the circuits can be loosened. In the case of a grid rejector this is most easily done by inserting a small condenser of say 5 pF between the coil tap and the grid of the valve.

Upper Sideband Superhets

Some superhets have been made to operate on the London Frequency on the upper sideband. This was to ensure that no sound interference was experienced and the object was accomplished without the use of sound rejectors.

These receivers are those which are particularly difficult to get working in Band III with the aid of converters.

One important point is that it is still possible to get a picture through without modification in some cases, because there is still 0.75 Mc/s of the upper sideband included in vestigial sideband transmission. The quality of the picture will, however, be rather on the poor side.

The alteration of such receivers should not be undertaken lightly; the success of the operation will depend much upon the skill and knowledge of the person doing the job.

For success a signal generator is almost essential and this is not the equipment of the average amateur.

Failing the use of such an instrument, some patience is called for.

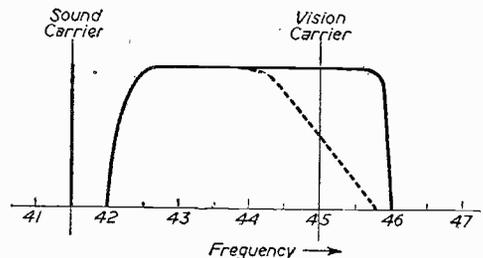


Fig. 3.—Typical response curves.

The first step is to retune the R.F. stages to the lower sideband, and then to make and insert the rejectors: If sound on vision is not experienced the rejectors can be left to later if desired.

The oscillator should be tuned for maximum sound and then the vision I.F. stages must be tuned for maximum vision, without altering the oscillator from maximum sound position. Ignore the sound on vision to start with and continue tuning for maximum picture.

When this stage is reached the sound rejectors can be inserted so as to cut the sound from the vision.

Now detune the oscillator towards the vision, away from the sound and then retune the vision stages to maximum picture. Retrim the oscillator to the sound channel and note the loss of picture. The aim is to adjust the vision I.F. stages so that when the oscillator is swung to maximum sound the "volume" of the picture signal is cut by half. This

gives the correct position for the oscillator, which is 6db down on the vision carrier.

The remainder of the work is best carried out by using Test Card C and the vision I.F.'s should be very carefully adjusted for maximum quality. The

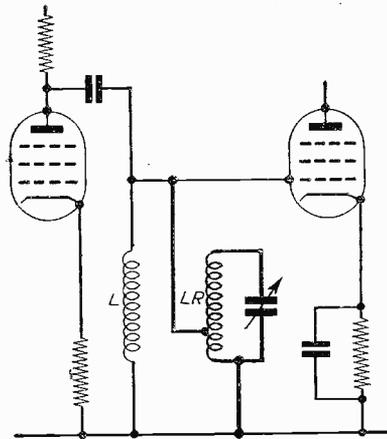


Fig. 4.—A grid rejector.

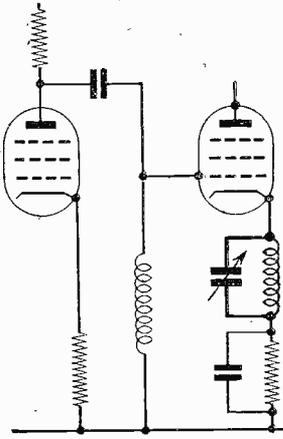


Fig. 5.—A cathode rejector.

oscillator should not be moved from the position obtained by the previous process or the whole alignment will be upset.

However, by very careful and patient work it should be possible to obtain quite good results.

Another important point to note about this process is that it can be applied to receivers which have not worked with Band III converters. Indeed, when a receiver has been adjusted for the new transmitter then it should be capable of being worked with most of the Band III converters which are available on the present market.

One point which must not be overlooked is that in very many cases the I.F. coils will be found to have the cores practically sealed in position by some method. Great care must be exercised when dealing

with these cores so as not to break them; a spot of methylated spirit is often of value.

All trimming must be done with an insulated trimmer. A metal trimmer such as the blade of a screwdriver will give false results.

Aerials

There should be no need to alter the aerial systems except where highly directional arrays are employed. In these cases it may be found necessary to alter their direction somewhat.

Where the receiver is located near the new transmitter it may be found that the signal is too strong. In this case attenuators can be fitted in the aerial circuit. A simple attenuator is shown in Fig. 6.

A simple attenuator of this kind should be found suitable for most cases, and can be wired directly into the aerial circuit within the receiver chassis.

A point worth observing is that it is generally better to fit an attenuator to the aerial system, than to reduce the efficiency of the aerial by replacing it with one of lower quality. A poorer aerial will reduce the signal to noise ratio—an attenuator still retains that ratio.

When the new transmitter gets into its stride many people will feel the benefit of its increased range and power.

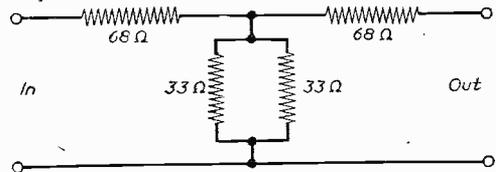


Fig. 6.—Circuit of an attenuator.

L. C. Jesty Honoured by I.R.E.

THE Institute of Radio Engineers, New York, has honoured Mr. L. C. Jesty, of Marconi's Wireless Telegraph Co. Ltd., by electing him a Fellow of the Institute. The citation reads:—



Mr. L. C. JESTY

“For leadership and personal contributions in the development and evaluation of television systems.”

L. C. Jesty, B.Sc., M.I.E.E., F.Inst.R.E., F.T.S., F.B.K.S., is Chief of the Television Research Group at the Marconi Research Laboratories, Great Baddow, in which capacity he joined the company in 1949. In recent years he has been closely connected with research into, and evaluation of,

colour television systems, and has done much pioneer work on Anglicised versions of the N.T.S.C. system, with one of which the BBC is now conducting experimental transmissions.

First Radar Tube

Mr. Jesty, after graduating from University College, Southampton, was appointed to the staff of the G.E.C. Research Laboratories at Wembley, Middlesex, in 1927, and was for some time engaged in research on electric lamps. In 1933, however, he started and built up a cathode ray tube research group. He was responsible, among other things, for developing the “safe” bulb shape (which made large tubes possible), and the rigid concentric electron gun assembly, which subsequently satisfied airborne radar requirements in withstanding vibration, so contributing materially to the first radar tube to be used in aircraft—the VCR97.

In 1938 he commenced specialist work on radar applications of cathode ray tubes. Wartime radar personnel will recall the VCR84, the first 12in. tube with a double-layer long-afterglow screen, for which his team was responsible. In 1944 he was promoted to the leading scientific staff of the laboratories.

C.R.T. ISOLATION TRANSFORMER
 Type A. Low leakage windings. Ratio 1: 1.55 giving a 25% boost on Secondary. 2 v., 10.6 v., 4 v., 10.6 v.; 6.3 v., 10.6 v.; 10.5 v., 10.6 v.; 13.3 v., 10.6 v.
 Ditto with mains primaries. 12.6 each.
 Type B. Mains Input 220/240 volts. Multi Output 2, 4, 6.3, 7.5, 10 and 13 volts. Input has two taps, which increase output volts by 25% and 50% respectively. Low capacity, suitable for most Cathode Ray Tubes. With Tag Panel, 21/- each.
 Type C. Low capacity wound transformer for use with 3 volt Tubes with falling emission. Input 230/240 volts. Output 2-21, 21-23 volts at 2 amps. With Tag Panel, 17/6 each.
NOTE.—It is essential to use mains primary types with T.V. receivers having series-connected heaters.

TRIMMERS. Ceramic. 30, 50, 70 pf., 9d., 10d. per 150 pf.; 1/3; 250 pf. 1/6; 500 pf. 750 pf. 1/9.
RESISTORS. All values. 10 ohms to 10 meg., 1/2 w., 4d.; 1/4 w., 6d.; 1 w., 8d.; 2 w., 1/-.
HIGH STABILITY. 1/2 w., 1/2, 2/-. Preferred values 100 ohms to 10 meg.
WIRE-WOUND RESISTORS 1/3 10 watt } 25 ohms—10,000 ohms 1/6
 15 watt } 25 ohms—10,000 ohms 2/-
 15,000 ohms—30,000 ohms, 5 w., 1/9; 10 w., 2/3.
KNOBS, GOLD ENGRAVED.—Walnut or Ivory, 1 1/2 in. diam., 1/6 each. Not engraved, 1/4 each.

PURETONE RECORDING TAPE
 1,200 ft. on standard fitting 7" Plastic reels. Brand new boxed 17/6.

O.P. TRANSFORMERS. Heavy Duty 50 mA., 4/6. Ditto, tapped primary, 4/9. Multifunction, push-pull, 6/6. Tapped small, peroxide, 3/9.
L.P. CHOKES 15/10 H. 60/65 mA., 5/-; 10 H. 120 mA., 10/6; 15 H. 150 mA., 12/6.
MAINS TRANS. 250-0-250, 30 mA., 6.3 v. tapped 4 v., 4.5 v., 5 v., tapped 4 v., 2 v., ditto 250-0-250, 21/-.
HEATER TRANS. Tapped prim., 200/240 v., 6.3 v., 1 1/2 amp., 7/6; tapped sec., 2, 4, 6.3 v., 1 1/2 amp., 8/6.
VC97 TESTED FULL PICTURE, 32.
COFFER PLATED AERIAL RODS. 1/4 x 12 in. push fitting, 3/-; 1/2 x 12 in., Aeriatec Earth rods, 4/-.
ALADIN FORMERS and core, 1 in., 8d.; 1 in., 10d.; 1 1/2 in. FORMERS with Cans and Core, 2 in. sq. x 1 1/2 in. and 1 in. sq. x 2 1/2 in., 2/- ea.
TYAMA.—Midjet Soldering Iron, 200/220 v. or 230/250 v., 12/11. Selson Midjet Iron, 24/-.
MIKE TRANS. Ratio 50:1, 3/9 ea.
MAINS DROPPERS. 3 x 1 1/2 in. Adj. Sliders, 3 amp., 750 ohms, 4/3. 2 amp., 1,000 ohms, 4/3.
LINE CORE. 3 amp., 60 ohms per foot, 3 amp., 100 ohms per foot, 2 way, 6d. per foot, 3 way, 7d. per foot.
LOUDSPEAKERS P.M. 3 OHM.
 5 in. Goodmans, 17/6. 7 1/2 x 4 in. Goodmans, 21/-; 5 in. x 4 in. Rola, 19/6. 10 in. R. G. S., 22/6.
 6 1/2 in. Goodmans, 17/6. 10 in. R. G. A. 30/-; 5 in. M.B. 2.5 v. or 6d. tapped 4 v. trans, 24/6.
CRYSTAL DIODE, G.E.C. 2/-; Circuit Book, 1/-.
HIGH RESISTANCE PHONES. 4,000 ohms, 17/6 pr.


GARRARD 3 SPEED AUTOCHANGERS
 Hi-Fi model 75 BRAND NEW.
 Our price £8-19-6, carriage 5/6.

SWITCH CLEANER Fluid, squirt spout, 4/3 tin.
TWIN GANG TUNING CONDENSERS. .0005 mfd. midget with trimmers, 8/6; 375 pf. midjet, less trimmer, 6/6. .0005 Standard size with trimmers and feet, 9/-; less trimmers, 8/-; ditto, coated, 2/8.
SPEAKER FRET. Woven Plastic T.Y.G.A.N. Walnut tone. 12 in. wide, 2/- per foot. Expanded metal, Gold 9 1/2 x 12 in., Silver, 15 1/2 x 9 1/2 in., 2/- each.

VALVES
 A SMALL SELECTION FROM OUR STOCKS


All Boxed	1/6	New & Guaranteed
8/6	5/6	EA50 8/6 10/6
1R5	6/8	6A15 6/2 7/4
1T4	9/2	2X2 6/5 12A7
1S5	1E50	1E148 6/6 EBC41
384	Equip.	EB34 6K7G BIP780
3V4	8P1	3/6 EB91 ECH35
5Y4	8F41	3/6 HV72 ECT30
6AM6	EP92	3/6 (near) ECR42
6AT6		6H6M 4F41
647	7/8	7/6 EF80
6K8	6B6E	6V6G 7L32 EI41
6SL7	6B6E	6X4 HV2A EZ40
6SN7	6P6	6X4 HV2A KT33
6VGGT	6K7GT	6X5 PEN25 MU14
EB33	6G6M	807 U22 MU14
EP50	68A7	EP39 VP23 EY51

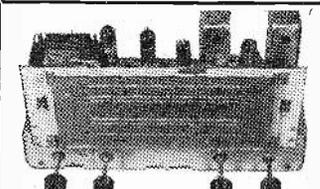Sylv. Ref. 12K 8, 12K7, 12K7, 35L6, 35Z4 6/7
 EP91 Special Price—37/6—The Set. X79



ALL WAVE RADIOGRAM CHASSIS
THREE WAVEBANDS FIVE VALVES
 S.W. 16 m.—50 m. LATEST MULLARD
 M.W. 200 m.—530 m. BC142, TP41, EB341,
 L.W. 800 m.—2,000 m. EI41, EZ40.
 12 month Guarantee.
 A.C. 200/250 v. 4-way Switch; Short-Medium-Long-Gram. A.V.C. and Negative feedback. 4.2 watts. Chassis 13 x 5 1/2 x 2 1/2 in. Glass Dial 10 x 4 1/2 in. horizontal or vertical available. 2 Pilot Lamps, Four Knobs, Walnut or Ivory. Aligned and calibrated. Chassis isolated from mains. **10 gns.** Carr. & Ins., 4/0.
MATCHED SPEAKERS FOR ABOVE CHASSIS
 8 in., 19/6; 10 in., 25/-; 12 in., 30/-.

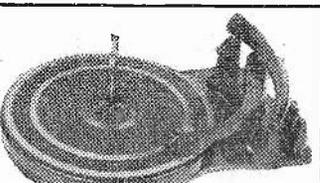RCS SCOOP
 Collaro Auto-changer RC531 for 78 r.p.m. 10 in. and 12 in. records. Brand new in maker's boxes! High impedance lightweight Pick-up with sapphire needle, will match any Amplifier or Radio. Less than half price. **£5.19.6.** carr. and ins. 5/6.



£8-19-6 Post Free.
 Brand new Plessey 3-speed Autochanger Mixer Unit for 7, 10 and 12 in. Records. Twin Hi-Fi Xial Head with Dupoint sapphire stylus. Plays 4,000 records. Spring mounting. Base-board required 15 1/2 x 12 in. Height 5 in. Depth 2 in. Super Quality. 200/250 V. A.C. vs Walnut Veneered Playing Desk cut out ready for Plessey, only sold complete with Changer 10/6 extra.

AMPLION. 3-speed Single Record unit with Acos 37 Turnover Head, each Sapphire Stylus plays 2,000 records. Starting Switch Automatically places Pick-up on records, 7 in., 10 in. or 12 in. Auto Stop. Baseplate 12 x 8 in. Height 2 1/2 in. Depth 1 1/2 in. Price £7.15.6, post free.

B.S.R. MONARCH. 3-speed Motor and Turntable with selecting switch for 33, 45 and 78 r.p.m. records. 100-120 v. and 200-250 v. A.C. 50 cps. Also B.S.R. MONARCH Lightweight Pick-up with Acos Xial turnover head, separate Sapphire stylus for L.P. and Standard records. **SPECIAL OFFER, THE TWO: 1 £4.15.6, post 2/6.**

T.V. PRE-AMP. (McMICHAEL). Tunable Channels 1 to 5. (With Amplify Output of your Band 3 Converter). Midjet size. High Gain. Fringe Model, B.V.A. Valve, Full instructions. Ready for use. (H.T. 200 v. L.T. 6.3 v., 3 amp. mains). **BRAND NEW, 25/- each. SPECIAL MAINS POWER PACK** for above, 25/- extra.

F.M. TUNER COIL KIT. 22/8. H.P. coil, Aerial coil, Oscillator Coil, 20 v. I.F. Transformers 10.7 Mc/s. Detector transformer and heater choke. With circuit and component list, using four 6AM6, Chassis and Dial, 19/6.

TELETRON BAND III CONVERTER
 For London, Midland and Northern Transmissions.
 Suitable all T.V. makes. T.R.F. or Superhet. Ready wound coils, two RF50 valves, all component, punched chassis, circuit diagram, wiring plans. **COMPLETE KIT** for mains operation 200-250 v. A.C. £2.10.0.
 AS ABOVE: LESS POWER PACK. Requires 200 v. 20 ma. H.T. 6.3 v. 6 a. L.T. £2.5.0. Mains Transformer to above Spec. ... 10/6
 Min. Westinghouse Rect. ditto ... 8/6
 B.B.C. T.A. crossover unit ... 7/6
 Punched and drilled chassis ... 3/9
 Larger chassis for Mains Model ... 6/7
 Teletron Coilset with plans ... 15/-
 Full plans and circuit details ... 6d.

Volume Controls 80 ohm COAX
 Thin spindles. Guaranteed. Semi-air spaced. Poly-ethylene insulated. 1 in. dia. 10,000 ohms to 2 Meg. Stranded core. No Sw. R.P.S. No. 111.8. Losses cut 50%. 3/- 4/- 4/9
STANHARD 1 in. Coax. 8d. yd.

COAX PLUGS ... 1- DOUBLE SOCKET ... 1/3
SOCKETS ... 1- OUTLET BOXES ... 4/6
WOUND TWIN FEEDER, yd. 6d. 80 or 300 ohms.
DITTO SCREENED per yd. 1/-, 80 ohms only.
WIRE-WOUND POTS. 3 WATT. Pre-Set Min. T.V. Type. All values 25 ohms to 30 K., 3/- ea. 50 K., 4/-; Carbon 50 K. to 2 m., 3/-.
WIRE-WOUND 4 WATT. Pots, 2 1/2 in. Spindle. Values, 100 ohms to 30 K., 5/6; 100 K., 9/6.
CERAMIC CONDS. New stock. .001 mfd., 7 K.T. T.C.C. 5/8. Ditto, 10 KV. 9/6; 100 pf. to 500 pf. Micas, 6d.; Tubular 500 v. .001 to .01 mfd., 9d.; .05, .1, .1, .2, 1, 2, 3, 1, 9; .1 (350 v., 9d.); .1 (900 v., 1/3); .1 (1,000 v., 2/6) to .01 mfd., 10d.
SILVER MICA CONDENSERS. 500 pf. to .01 mfd., 10d. 1 pf., 1/6; 600 pf. to 3,000 pf., 1/3. **DITTO** 1/2, 1.5 pf. to 500 pf., 1/9; 515 pf. to 1,000 pf., 2/-.

I.F. TRANSFORMERS 7/6 pair
 485 Kc/s Stag Tuning Miniature Can, 2 1/2 in. x 4 in. x 1 in. High and good bandwidth. By Pyle Radio. Data sheet supplied.

NEW ELECTROLYTICS. FAMOUS MAKES

TUBULAR	TUBULAR	TUBULAR	CAN TYPES
1/275 v. 2/-	100/25 v. 2/-	8-16/450 v. 5/6	16/450 v. 5/6
2/450 v. 2/3	8-200 v. 4/6	16-120/350 v. 4/8	16-24/350 v. 4/8
4/450 v. 2/-	16-16/300 v. 1/6	32-32/350 v. 4/6	32-32/350 v. 4/6
8/450 v. 2/3	32-32/350 v. 4/6	64-32/350 v. 7/6	64-32/350 v. 7/6
8/300 v. 2/3	32-32/350 v. 4/6	128-120/350 v. 11/6	128-120/350 v. 11/6
16/450 v. 3/6	64-32/350 v. 4/6	100-200/275 v. 1/6	100-200/275 v. 1/6
16/300 v. 5/6	128-120/350 v. 4/6	1,000-1,000/0 v. 6/6	1,000-1,000/0 v. 6/6
32/300 v. 5/6	250-250/0 v. 5/6	1,000-1,000/0 v. 6/6	1,000-1,000/0 v. 6/6
50/25 v. 1/9	500-250/0 v. 5/6	1,000-1,000/0 v. 6/6	1,000-1,000/0 v. 6/6
50/25 v. 1/9	500-250/0 v. 5/6	1,000-1,000/0 v. 6/6	1,000-1,000/0 v. 6/6
50/25 v. 1/9	500-250/0 v. 5/6	1,000-1,000/0 v. 6/6	1,000-1,000/0 v. 6/6
50/25 v. 1/9	500-250/0 v. 5/6	1,000-1,000/0 v. 6/6	1,000-1,000/0 v. 6/6


Screw Base Type 512, 8,500 v. 3/-; 16,500 v. 4/-.
ALUMINIUM CHASSIS. E.H.T. TYPE FLY LEAD BACK VOLTAGES. K33/2 2.4, 4.3; K34/0 3.2 kv., 6/-; K34/5 3.6 kv., 6/6; K3/50 4 kv., 7/3; K3/100 8 kv., 12/6; MAINS TYPE, RMI, 125 v., 60 mA., 4/-; RMD, 100 mA., 4/9; RMD, 120 mA., 5/9; RMD, 250 v., 275 mA., 16/-.
COILS Weatite, "P" type, 3/- each. Osamor Midjet, "Q" type, dust core, 4/- each. All ranges.
H.F. CHOKES, iron cored, 14 M.H., 3/- each.

ALUMINIUM CHASSIS. 18 s.w.g. undrilled. With 4 sides, riveted corners and lattice fixing holes, 2 1/2 in. sides, 7 x 4 in., 4/6; 9 x 6 in., 5/9; 11 x 7 in., 6/9; 14 x 9 in., 8/6; 14 x 11 in., 10/6; 15 x 14 in., 12/6; 18 x 10 x 8 in., 16/8.

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 2.6 or 12 v. 1 1/2 amp., 8/9; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amp., 13/6; 4 amp., 21/-.
AL BERNARDS boxes in stock.
VALVE MANUALS I & II, 5/- ea. part.
VALVE and TV TUBE equivalent 5/-.
ACID HYDROMETER. New Ec Govt. Unbreakable. Packed in metal case 7 x 1 1/2 in. dia., 4/6.
WAVECHANGING SWITCHES.
 5 p. 4-way 2 water, long spindle ... 6/6
 2 p. 2-way, 3 p. 2-way, short spindle ... 2/6
 2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle 3/6
 3 p. 4-way, 1 p. 12-way, long spindle ... 3/6
VALVEHOLDERS. Fax. Int. Oct. ad., EP50, EA50, 6d. B12A, CRT. 3. Eng. and Amer. 4.5, 5, 6, 7, 9 pin. 1/-.
MOULDED Mazda and Inet. Oct. 6d., B7G, B8A, B8G, B9A, 9d., B7G with can 1/6.
VC97 2/6. B8A with can 2/6.
CERAMIC, EP50, B7G, B9A. Int. Oct. 1/-.
B7G with can 1/3.
BLACK CRACKLE PAINT, air drying, 3/- tin.
Orders correctly as below.
OPEN ALL DAY—(Wed. 1 p.m.) 10 page list 3d.

RADIO COMPONENT SPECIALISTS 307 WHITEHORSE RD., WEST CROYDON
 OPEN ALL DAY—(Wed. 1 p.m.) 10 page list 3d.
 Tel. TH01655. Buses 133 or 69 pass door. 48-hour postal Service. P. & P., 1/-; £2 orders post free. (Export Extra) C.O.D. Service 1/6


F.M. TUNER

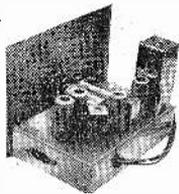

This tuner is based upon the very successful circuit published by Data Publications. We have made up models at all branches and will gladly demonstrate. Stability is extremely good and making and aligning most simple. Cost of all parts including valves, prepared metal chassis, wound coils and stove enamelled scale, slow-motion drive, pointer, tuning knob, in fact everything needed is £6.12.6. Data is included free with the parts or is available separately, price 2/-. Extra for fringe area model, 20/-.


THE CLEVELAND ORGANONE

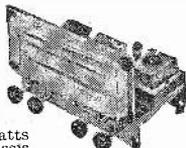5 valve 3 waveband superhet covering Long, Medium and Short waves Osmar miniature valves—low loss iron coils — permeability-tuned I.F.S.—full A.V.C.—variable negative feed-back—gram. position—4 watts output—particularly fine tone. Chassis size 7in. x 7in. x 7in. approx. Tested in difficult areas, where exceptional results have been obtained. Price £11.10/0 Carriage and ins. 10/-.



THIS MONTH'S SNIP 14" T.V. CABINET

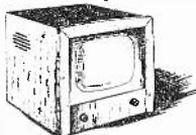
14in. T.V. cabinet of the latest styling made for one of our most famous firms—beautifully veneered and polished—limited quantity—19/6 each. Carriage and packing 3/6 extra.



ELECTRONIC PRECISION EQUIPMENT LTD.

See page 513 for address

AM/FM RADIOGRAM CHASSIS

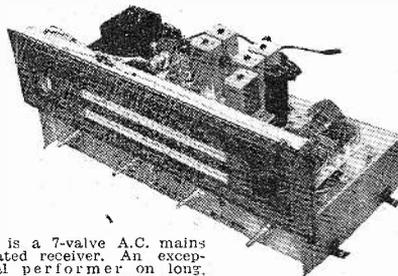


This is a 7-valve A.C. mains operated receiver. An exceptional performer on long, medium and short A.M. bands and on the new V.H.F. band. It is an ideal unit for a quality radiogram. Special features include magic eye tuning indicator, extra long scale and pointer travel—latest circuitry employing full A.V.C. feed-back, etc., etc. Undoubtedly one of the finest AM/FM chassis available today. Chassis size 17in. x 6in. x 7in. Price £23.17/6, carriage, packing and insurance 20/- extra.

RECORD PLAYER £4.10/0

3-speed

Gramophone Motor

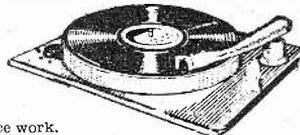Latest rim drive 3-speed motor with metal turn-table and rubber mat. Small mod. makes speed easily variable for special effects and dance work.



Hi-Fi Pick-Up


Using famous Cosmocondor Hi-G turn-over crystal. Separate sapphire for each speed. Neat bakelite case with pressure adjustment.

Special Snip Offer This Month

The two units for £4.10/-, plus 5/- post and insurance, or made up on board as illustrated, £5.10/0, plus 5/- post.

BAND 3 T.V. CONVERTER

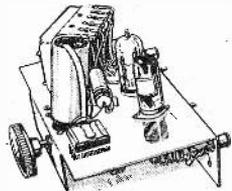FOR THE NEW STATIONS: LONDON, BIRMINGHAM, MANCHESTER



42/6
(2/6 Post)

Complete kit of parts, including ECC85 and EF80, with punched chassis 6½in. x 4½in. x 2in. (200 v. at 25 ma. and 6.3 v. 1 A. required). Power pack components to wire on chassis, 20/-.

WIRED, with power pack, ready for use, £4 (2/6 post). Suitable for superhet and T.R.F. State I.F. or local station.

Interference pattern ELIMINATOR, 8/6 (9d. post). Does away with the herringbone pattern due to BBC break-through. State local station. Guaranteed to work or money back.

3-speed mixer autochangers. B.S.R., £7.19.6. Collaro, £9.9.0, carr. 5/- on each. 4d. for full list of bargains.

GLADSTONE RADIO

P. O. BOX 8, CAMBERLEY, SURREY

“You can rely on US” for . . .

ALL RADIO and ELECTRONIC COMPONENTS

One of Britain's Largest Stockists of all Leading Makes: Hunts, T.C.C., Haynes, Allen, Denco, Osmor, Weymouth, Morganite, Bulgin, Belling Lee, Teletron, R.E.P., Scotch Boy, Ellison, Elstone, Partridge, Wynall, Westinghouse, S.T.C., AVO, Taylor, Goodmans, J.B., Wharfedale, Wearite, Acos, etc.

Suppliers to: Ministries, Development Laboratories, Education Authorities, etc.

Some of the more difficult parts you may not be able to acquire:

Tapped Vol. Control, Linear C.T. ¼ mg., ½ mg., 1 mg., 7/6. Linear ¼ mg., ½ mg., 1 mg., 6/6. Post 6d.
2 High Stab. ½ w. Resistors. 2% Range, 100Ω to 2 meg., 1/6 each. 1% Silver Micas up to 100 pf., 1/-, 280 pf., 1/2. 500 pf., 1/4. 1,000-5,000, 2/6. Post 6d.
Teletron-Band III Converter—Punched Chassis, 4/- Post 6d. Set of Coils and Circuit, 15/- Band III Loft Aerials, 30/- plus 2/- carriage.

Thousands of Valves, Condensers, Resistors—Can We Help You?

MULLARD 510 and GEC 912 all specified parts and lists available.

Catalogue, Book Lists, S.A.E.

RADIO SERVICING CO.,

82, SOUTH EALING ROAD, LONDON, W.5.

Tel.: EAL 5737. Next Stn. Ealing Tube, 65 Bus. 1 p.m. Wed.

A 'View Master' Conversion

HOW TO MODIFY THIS POPULAR RECEIVER FOR SINGLE SIDEBAND WORKING

By L. D. Stuart

IT is now fairly common knowledge that all British television is now transmitted using a single sideband. The London BBC transmission on its transfer to the Crystal Palace fell into line with other stations and now operates on the lower portion only of the band which it previously employed.

This subject has been adequately treated in articles in PRACTICAL TELEVISION, the most recent being that entitled "Alignment of T.V. Receivers" in the November and December issues of 1955. It is only necessary here, therefore, to emphasise how the change affects the performance of the London version of the View Master.

This stalwart, estimated (see PRACTICAL TELEVISION, November, 1955) to number 10,000, was designed to receive vision on the upper sideband. That is, on the half of the double sideband which has now been lost to us. The consequences of this are two-fold. In the first case, many converter units are designed for insertion between aerial and set to render it capable of receiving ITA transmissions without further modification. These will not perform properly on a View Master tuned to the upper sideband. Secondly, an unmodified View Master will no longer receive vision satisfactorily.

I took the opportunity of making a few quite simple modifications and this article describes my not unsuccessful efforts at conversion to single sideband working by re-tuning after adding a few simple components.

Not unsuccessful, because the receiver has returned to the custody of a small son who blithely selects either the BBC or the ITA programme as the fancy takes him. I am at present using a commercial version of the "R.F. pentode followed by a self-oscillating pentode mixer" type. The converter with cascode R.F. stage described on page 120 of the

August, 1955, issue of PRACTICAL TELEVISION works equally well and has higher gain, which has advantages in certain circumstances to which I will refer later, while the PRACTICAL TELEVISION converter should be suitable at greater distances. Separate H.T. and L.T. supply for the converter is desirable—the View Master has none to spare, as we all know.

Details

It was obvious that the original design chose upper sideband working in order to dispense with the complication of sound traps, and that tuning the coils down to the lower vision sideband would necessitate the employment of one or more traps. Previous successful experience in another connection inclined me towards using the very effective method described by J. S. Hopwood in the September, 1953, issue of PRACTICAL TELEVISION. This applies traps to the "grid" ends of the grid coils of an R.F. amplifier.

Inspection of the View Master circuit diagram (usually depicted as in Fig. 1) was encouraging in that these "grid" ends seemed to be unencumbered. Inspection of the actual vision strip soon dispelled this idea. The R.F. grid connections on the actual receiver (which I built to the wiring instructions—and so, I expect, did you) proved to be not a bit like the published circuit diagram. The coupling turns to the preceding anode coils are in the "grid" ends of the grid coils of the second and third R.F. valves (not the "earthy" ends), and are adjacent to the "anode" ends of the primary windings. Rather like Fig. 2, in fact.

This makes the employment of Mr. Hopwood's method difficult, but we can see that it would be simple to add sound traps coupled to the anode coils, which are automatically effectively coupled

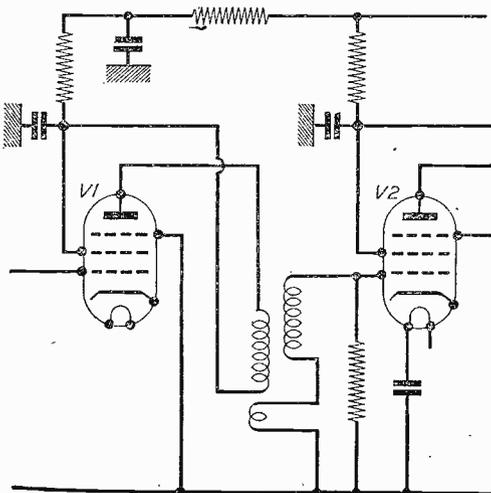


Fig. 1.—Circuit of the I.F. coil as originally published.

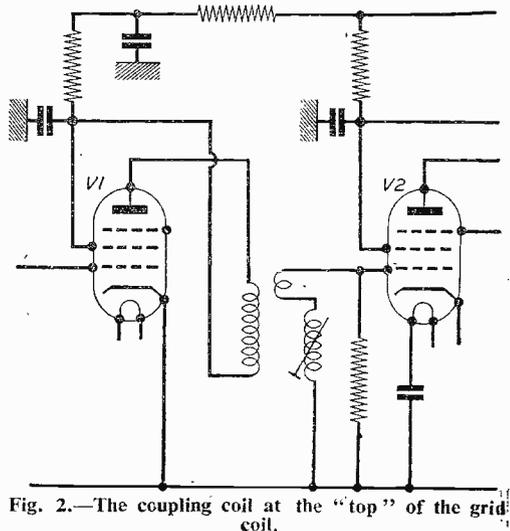


Fig. 2.—The coupling coil at the "top" of the grid coil.

to the "grid" ends of the following grid coils. It would simply mean winding the coupling turns of the sound traps round the tops of the anode-coil formers. (Note: "tops" here refers to the ends remote from the chassis-deck—we are inspecting from below).

These trap coils can be similar to that designated L11 in the original circuit. The tuning capacity required is, however, greater—there is no EF50 grid-cathode capacity to assist. Two traps are necessary, but I have added a third which serves to make the tuning of the first trap less critical with advantages to be described later. One notes, however, that the coupling turns of the diode input coil are, in fact, in the "earthy" end. This is probably why the tuning of the third trap is uncritical.

The location of the three trap coils, together with the number of coupling turns is shown in Figs. 3 and 4. A simple modification of the input circuit, to adapt it for co-axial feeder, is also shown. This modification is not necessary if only the BBC programme is desired: but is probably essential if the receiver is to be used with an ITA converter not specially adapted for balanced output. The diagram also shows the sound coupling where the 2 pF coupling condenser in the original receiver is dispensed with in favour of a simple link coupling, consisting of a single turn of 5 amp. fuse wire between the first trap and L11.

A Warning

These conversion instructions will not suffice to make a bad View Master into a good one. A prerequisite is that the receiver be carefully aligned according to the View Master book, particularly as to the vision R.F. grid coils which should be peaked at 45 Mc/s. That is, to maximum brightness of

picture. There should be two positions of the tuning slugs producing maximum brightness—with darkness each side of each position. If this is not so the inductance of the non-co-operative coil (or coils) is too high, and shorter slugs should be obtained and fitted or the bottom turn loosened, or (as in my own set) removed entirely, thus shortening the winding by one turn. If your coil formers are of the type having an internal lip preventing the slug from projecting at


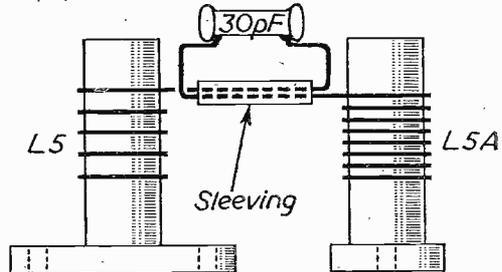


Fig. 5.—How the coupling condenser between L5 and L5A is arranged.

the end remote from the coil base the second tuning position may not be attainable even though the coil is correctly sized. Make sure the slug is not exactly central when at maximum picture brightness.

Alignment

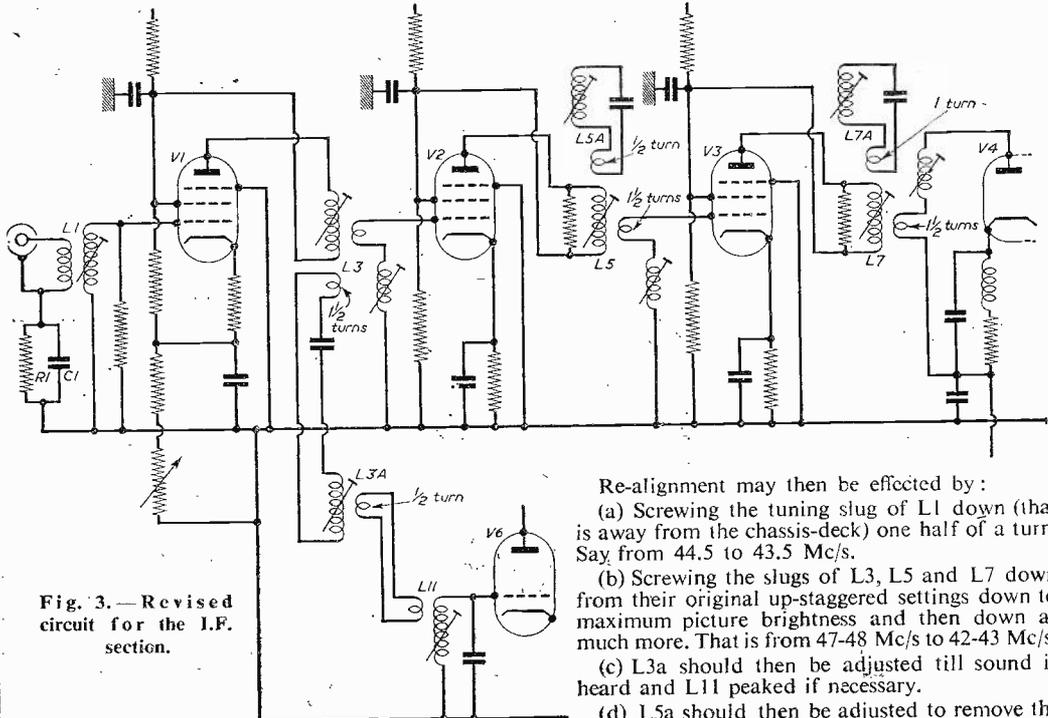With this tuning, and that of the sound strip completed, the traps may be fitted in the positions shown using, if you are lucky enough to have them, holes intended for coils used in the provincial versions of the View Master.



- Re-alignment may then be effected by:
- (a) Screwing the tuning slug of L1 down (that is away from the chassis-deck) one half of a turn. Say from 44.5 to 43.5 Mc/s.
 - (b) Screwing the slugs of L3, L5 and L7 down from their original up-staggered settings down to maximum picture brightness and then down as much more. That is from 47-48 Mc/s to 42-43 Mc/s.
 - (c) L3a should then be adjusted till sound is heard and L11 peaked if necessary.
 - (d) L5a should then be adjusted to remove the

CONTINUING the constructional data, connections to the C.R.T. holder are by means of ordinary single flex, and the condenser C9 and resistor R13 are mounted direct on the Perspex holder by drilling small holes to allow their wires to pass through and support them.


Rubber grommets are used for all wires passing through the chassis. A slot is cut in the C.R.T. bracket to allow the coaxial leads to pass through easily.

The L.F. choke is mounted on the back panel underneath the mains transformer. The fuse-holders are mounted close beside the 2-pin main input socket. All heater wiring is run away from other wiring and kept close to the chassis, and the chassis is used as a return wire.

The circuit diagram is pasted inside the bottom plate for reference.

Operating Details

After checking all the wiring, switch on the brilliance control and wait for a few seconds. Then advance this control until a spot or a trace is seen on the screen. Use the focus control to get the sharpest image at the centre of the screen; defocusing may be noticed at the edges, but the centre is the main thing to get in focus. Make sure the X and Y shift controls work smoothly, shifting the trace smoothly from left to right and up and down; one should be able to put the spot anywhere on the screen by means of these controls.

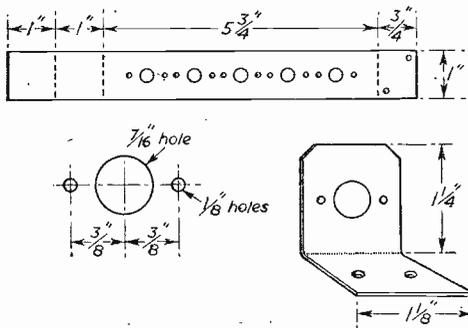


Figs. 14 and 15.—Details of the potentiometer bracket.

Next connect a lead from 50~ test to Y out socket, and with coarse frequency switch at Range 1, beam blanking hard, beam switch on Y amp. low, sync int. and X int., a trace should now appear on the screen if the Y amp. is advanced enough. The trace will probably be moving rapidly, but by operating the fine frequency control a point will be found where it moves slowly. Now advance the sync control until the trace remains stationary. The length of the trace can now be adjusted by the X amp. control.

To set the beam-blanking adjust preset R2 until the flyback lines just blank out. The lengths of the traces on the various ranges can be adjusted by means of the presets R19, 20, 21, 22, 23.

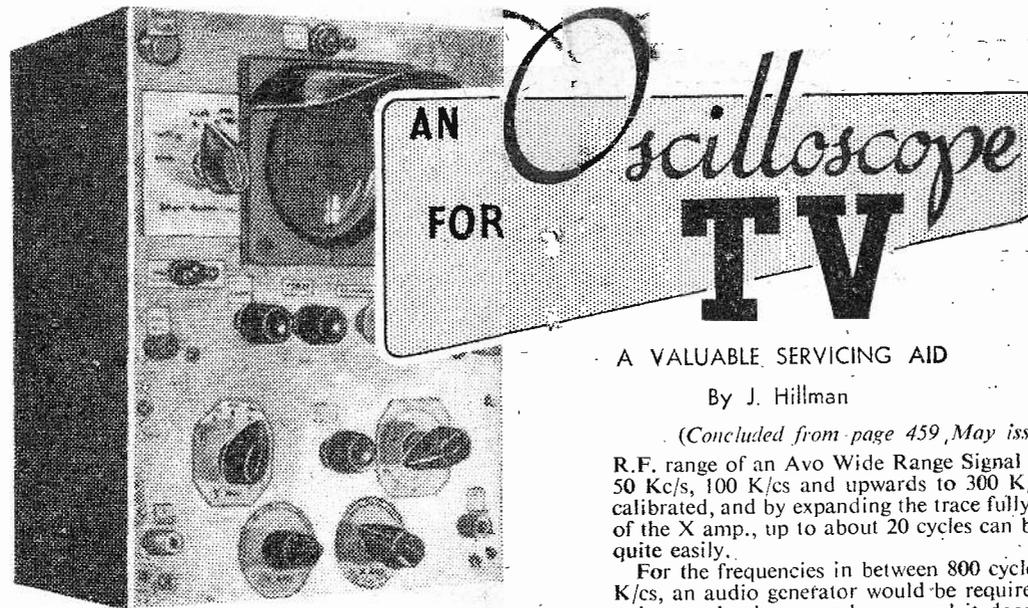The linearity control R26 is set up on Range 1, and by adjusting the fine frequency control until about 5 cycles are shown then by adjusting R26 and R23 the 5 cycles can be made equal to each other. This control R26 only affects Range 1 as the time-base is linear on the other ranges. One word of



A VALUABLE SERVICING AID

By J. Hillman

(Concluded from page 459, May issue)

R.F. range of an Avo Wide Range Signal generator 50 Kc/s, 100 Kc/s and upwards to 300 Kc/s can be calibrated, and by expanding the trace fully by means of the X amp., up to about 20 cycles can be counted quite easily.

For the frequencies in between 800 cycles and 2.5 Kc/s, an audio generator would be required and the writer used a home-made one and it does not need to be very accurate. The 100 cycles can be calibrated, and then, leaving the oscilloscope set at 100 cycles, a wave of 800 cycles or more can be reset on the audio generator; this can be carried out again at 1,600 cycles and will thus cover the gap.

Line Transformer Testing

First a lead is connected between the line output test socket and the Y output socket. Next, a test

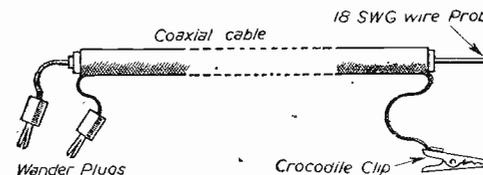


Fig. 20.—Details of the test lead.

lead is connected from the Y output socket and earth socket to the primary of the line output transformer under test. Usually the easiest points to connect the leads to are between the top cap of the line output valve and chassis.

Now set sync control at zero, Y amp. switch to high, Y amp. about one third from off and X amp. about half-way, range switch at 3, fine frequency about a third.

A trace should now appear on the screen as in Fig. 23A if transformer is all right, and B if trans-

forming regarding the use of the sync control: If this is advanced too much it will distort the trace, so only advance it sufficiently just to lock the trace.

To calibrate the controls, roughly stick squares of paper under the knobs and mark off in 10 divisions

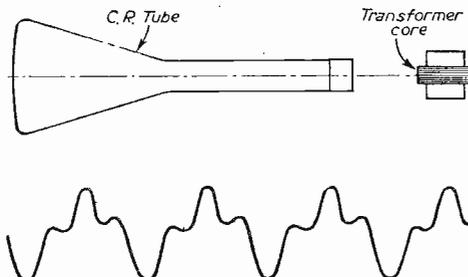


Fig. 21 (Top).—Positioning the transformer and tube base.

Fig. 22 (Bottom).—The trace, affected by radiation.

using Indian ink, and use the 50~ test socket to get the position for 50~. That will be when one complete cycle is seen on the screen. Similarly, 2 cycles on the screen will indicate 25 cycles frequency.


Other Frequencies

Similarly, by using a 300 or 400 cycles audio test signal from a signal generator, further calibration points can be obtained up to 800 cycles, and by using the

MISCELLANEOUS PARTS

- | | | |
|--------------------------------------|------------------------------|---|
| 14 metal wander plug sockets | 6 Int. octal valveholders | Coaxial cable—as required (7/.036 type) |
| 6 insulated wander plug sockets | 1 B36 valveholder | Nuts and bolts as required |
| 1 socket and wander plug combined | 1 B5 valveholder | Solder tags 4BA as required |
| 3 Wander plugs | 1 twin fuseholder | Wire and sleeving as required |
| 1 crocodile clip | 2 500 mA fuses | 2 group panels |
| 1 grid cap Int. octal | 7 small round coloured knobs | Polystyrene rod as required |
| 1 two-pin plug and-socket, polarised | 3 small pointer knobs | Rubber grommets as required |

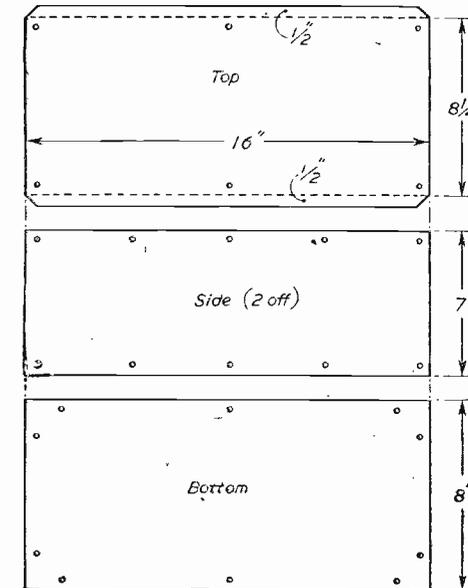former has any shorted turns. A point to note, however, when trace B is obtained is that it can also be due to faults in any other coils in that part of the circuit, e.g. scan coils or width coil, so that a further



Figs. 17, 18 and 19.—Top, sides and bottom of chassis.

check must then be made by disconnecting these coils one by one.

The oscilloscope can also be used to check heater/cathode leaks in valves.

First set up the controls to give a 50-cycle trace on the screen, then with the probe touch the cathode of the valves one by one and any leakage will show

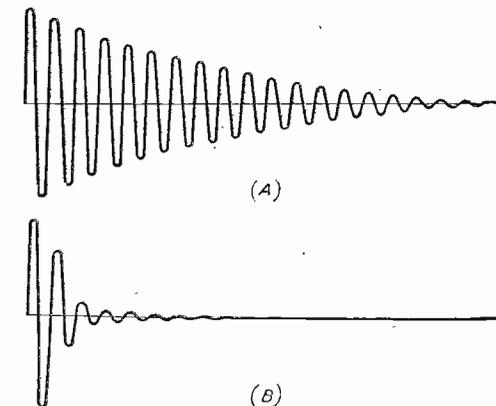


Fig. 23 (A and B).—Response curves with sound and faulty line transformers.

up as a 50-cycle trace. The action of the sync separator can also be checked by first getting a trace from the video input to the sync valve and then checking at the anode or screen where the sync pulses are taken off and no trace of the picture context should be present, just the sync pulses.

Radio Components Show

DETAILS OF SOME OF THE MOST IMPORTANT TELEVISION EXHIBITS

THE most noticeable feature of this year's show was the large expansion of the use of printed circuit technique. This has resulted in the introduction of many new components designed expressly for the use of this type of circuit, and as a result not only has the overall size been reduced, but different fixing methods have been introduced. For instance, as readers who have followed the details of the new tuner for the View Master in these pages will have seen, the valveholders are now supplied ready for direct insertion in the printed circuit plate, the projecting lugs of the sockets being soldered on the underside to the copper coating.

Among many examples of printed circuits shown by T.C.C. was a complete "front-end" of a TV set, with a tuner for Bands I and III, an F.M. tuner, a portable radio set with self-contained battery, several hi-fi amplifiers and transistor computer panels.

B7G, B8A and B9A stand-off type valveholders for printed circuits made of moulded woodflower or natural nylon-loaded P.F. with pen-nib contacts and optional skirts for screening cans were shown by McMurdo Instrument Company.

B9A and B7G holders in high-grade phenolic mouldings designed for rapid and reliable dip soldering were exhibited by Carr Fastener Company.

Egen Electric showed special resistors for printed circuitry and Electro-Methods had connectors suitable for 1/16th cards up to a maximum of 22 ways moulded in melamine with U-shape sockets of gold-plated phosphor bronze.

Capacitors

Miniature electrolytic condensers, specially designed for printed circuits were shown by Daly Condensers Ltd., Plessey, T.C.C., L.E.M., Dubilier, Hunt, etc.

Special type condensers are also made for fluorescent lighting, photo-flash equipment and mine exploders.

Sub-miniature polystyrene capacitors, measuring only 10 mm. x 4 mm. varying in capacity from 5-330 pF and designed to work up to 125 volts D.C. were shown by Suffix.

For automatic assembly in printed circuit production, Plessey miniature capacitors are mounted on a paper strip wound on a drum.

Test Instruments

New test instruments included a TV waveform generator, combined with an A.M. and F.M. signal generator and sweep oscillator, suitable for use on British, American and C.C.I.R. systems (Taylor Electrical Industries).

An F.M./A.M. signal generator covering a range of 10-470 Mc/s in five bands with a tuning system allowing small frequency changes to be read from a directly calibrated meter suitable for all carrier frequencies (Marconi Instruments Ltd.). A portable D.C. voltmeter, made by British Physical Laboratories, had a resistance of 1 megohm per volt. It covers nine ranges up to 500 volts.

Avo models 7 and 8 are now available in pan-climatic versions. These instruments have passed

Government tests for use in tropical climates. They will withstand high temperature, humidity and the cases are fungus resistant.

Valves and C.R.T.s

The G.E.C. type KT55 tetrode is a new beam type output valve for D.C./A.C. equipment with the limited H.T. available from 220 volts D.C. mains. Two of these new valves in push-pull will give an output of 25 watts—double that hitherto obtained from British valves.

New valves introduced by Edison Swan include a range of 12 types of 0.3 amp TV valves for series heater connection and also a variable mu H.F. valve for F.M. sets. The CRM93 is a 9in. cathode ray tube incorporating all the latest developments and suitable for the new portable TV sets. It is also thought that it might be welcomed for use in receivers designed to reduce the hire purchase deposit.

For the first time Ferranti were showing a range of ceramic valves.

Resistors

Egen Electric have produced an inexpensive version of sub-miniature potentiometer of the pre-set type in three forms. One is for chassis mounting with tag connectors; another has wire terminations and the third type is of the plug-in variety for use in printed circuits.

A new development, known as Pin Assembly Circuits, was shown by Erie. Designed to replace the conventional components with a tangle of wiring, the P.A.C. units are in such compact form that 15 components occupy only one square inch of chassis space. These are particularly suitable for printed circuits and other methods of automatic assembly.

The P.A.C. units consist of resistance and capacity elements 1/8in. diameter and 5/8in. long, varying in number from 3 to 4 to 90—and all connections are embodied in the moulded assembly. These elements terminate in special spill-type pins for insertion in the holes or eyelets of printed circuits ready for dip soldering.

The same firm is showing a hi-fi output transformer for use with G.E.C. KT66 valves in "Ultra Linear" connection and handles an audio power of 25 watts in the frequency range of 25 cps to 25,000 cps.

For the "distributed load" version of the Mullard 5-10 amplifier there is a new Partridge hi-fi "C" core output transformer.

Aerials

Many types of aerials, including arrays with up to 10 elements for V.H.F. and TV Bands I and III, in both indoor and outdoor forms, were shown by Antiference. A printed circuit is used in the "Y" connector box which enables a single aerial feature cable to be used with aerials for both bands.

Belling and Lee showed types for Bands I, II and III.

The Aerialite "Multiway" aerial elements can be arranged in 18 different ways through angles varying from 0 degrees to 350 degrees.

sound-on-vision ripple which should now be seen on the tube. This tuning should be commenced with the slug at the bottom of its coil—bottom being the end remote from the chassis-deck in this instance. A "bright picture" position will be passed through en route to the correct position.

Residual ripple may be removed by adjustment of the third trap L7a but this may be deferred till later.

These are initial settings only and may be effected on a normal transmission. As with the original View Master, close adjustments are made on Test Card "C," and the making of these is a matter of individual experiment (and experience). The adjustment of L3a is critical as regards resolution of the higher frequency line-squares. Where critical adjustment introduces sound ripple, adjustment of L7a will clear it. *The use of a signal generator is not necessary!*

Referring to the statement that the conversion cannot make a bad set into a good one it may, however, be stated that if your receiver resolved, say, the 2.5 Mc/s lines before adaptation, it will do so

rather more easily afterwards. It was the experience of most of us that the tuning of an upper sideband View Master was a "throw-away" technique whereby gain was sacrificed for definition, the limit being reached when line-tearing commenced. With lower sideband tuning staggering may be continued till the vertical lines on Test Card "C" suffer without the exhibition of weak sync and line slip which would have resulted before adaptation. One can also use "better" EF50's than an upper sideband View Master will carry without instability. My own set will just resolve the 3 Mc/s lines though this may be in part due to some other minor modifications which I may perhaps have an opportunity of describing at a later date. I was not able to achieve this with the original circuit.

Apart from the conventional Parts List and some notes on the mounting of the coils and condensers

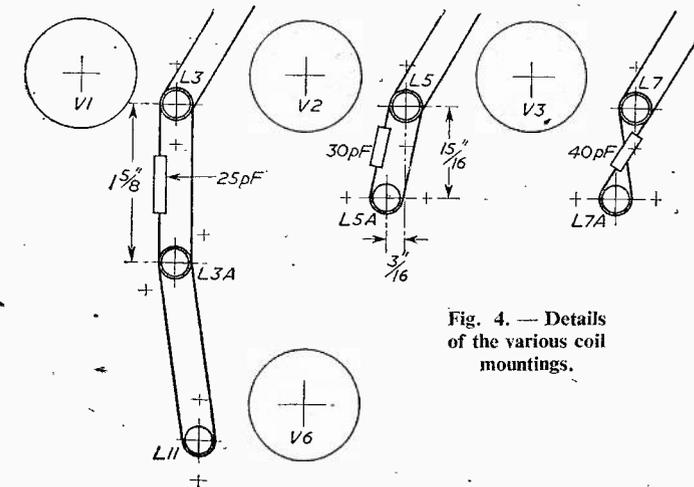


Fig. 4. — Details of the various coil mountings.

there is little more to add. Two friends of whom one has been abroad a year since last handling a View Master found no difficulty in "lining" my set.

Method of Mounting Coils

If your vision chassis is of the universal type with lots of extra holes intended for use with other channels you may be able to fix L3a, L5a and L7a without drilling. If this is not the case the positions may be marked out from the dimensions given in Fig. 4 which serve to locate the centres of the coils.

With the coils in position take the free lower end of L3a and wind it counter-clockwise round the lower end of L3 for 1 1/2 turns. This involves threading

the wire between the L3/L4 coupling turns and chassis. Thread on a 3/16in. length of sleeving, draw tight, and secure the coupling turns with a spot of shellac varnish. (Don't use cellulose or polystyrene cement—it is apt to soften the coil former.)

L5a is coupled to L5 in a somewhat similar manner, but a half turn only is taken round L5 and it can be at the top of L5.

L7a is coupled to L7 in the same way except that, to achieve a single turn, the turn round 7a is reverse wound and the finish crosses the start.

Mounting the Condensers

This is shown in Fig. 5. The method is unscientific, contrary to all the best teachings of R.F. circuitry, but entirely satisfactory. It consists in threading the free ends of each coil through the short length of sleeving already passed over the other end, turning each end up after drawing tight, then baring and scraping the wires and soldering the appropriate condenser in position. In particular, it permits the condenser to be changed or added to without disturbing the coupling.

Sound Take-off

This consists in a single turn of 5 amp fusewire wound round the centres of L3a and L11 on top of a protecting strip of plastic tape wrapped round the existing winding of each coil. This constitutes a simple link with a half turn around each former. The ends of the bare wire should be twisted together and touched with solder.

OUR
COMPANION JOURNAL

PRACTICAL
WIRELESS

1/3 Every Month

IMPROVING IFA CONVERTERS

ADDING A FURTHER TUNED CIRCUIT TO IMPROVE SELECTIVITY AND GAIN

By P. J. Evans

MANY readers living outside the primary service area of their local Band III transmitter, or in areas of poor reception, will have found that some increase in the gain of certain converters would be an advantage. This

of inductive coupling as well. Some increase in gain can also be achieved by modifying the turns on the aerial input coil, as well as by experiment with the value of the capacitor in the bottom or earthy end of the neutralising bridge network.

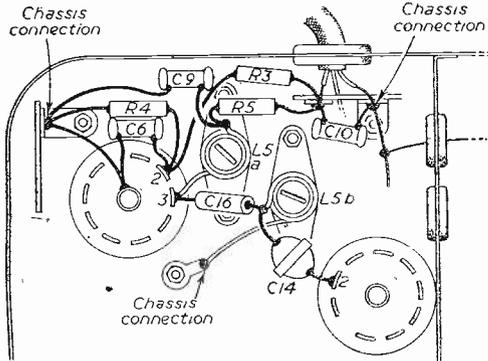


Fig. 1.—Location of the new coil L5a and new position of existing components in the P.T. Converter.

relates particularly to the P.T. and similar designs. In fact, any constructor who feels that more gain is desirable will find that the following modifications will be well worth the time spent in making the changes. In the result, the bandwidth is more than adequate; there is even less noise; breakthrough patterning from the Band I transmitter is reduced to negligible proportions; and at the same time the overall gain is increased by some 5 dB.

In one particular case with the original circuit it was necessary to turn the contrast control right up to produce an acceptable Band III picture—even then it was difficult to obtain sufficient sound. But with the modified arrangement the same control can be turned down hard against its stop with ample sound and better results on the screen than before.

The fundamental change is made in the coupling between the two valves. Instead of the single tuned-anode coil in the second cascode triode, a band-pass coupling circuit is incorporated with top-capacitive coupling. In addition to the capacitive coupling the coils are physically spaced so that there is a useful degree

Modifications

To make the coupling changes the following procedure is recommended, the details relating specifically to the October blueprint design. An additional coil former has to be provided between V1 and the existing coil L5; in order to make space for the new former, the screen between V1 and V2 must be removed. To do this, the earth busbar running through the screen from the central earthing point of V1 to the 3-way tag strip in compartment B should be taken out. Condenser C6 is earthed to the common point on V1; C10 is reconnected to earth on the tag strip; and C9 can be removed completely for the time being.

The connection from pin 2 on V1 valveholder to the junction of R3 and R4 is removed, and the other end of R4 is disconnected from the tag strip in compartment A and pulled through the screen. C14 is unsoldered from L5, and L5 disconnected from pin 3 of V1.

The screen can now be removed and discarded. At this stage it simplifies matters if coil L5 is removed

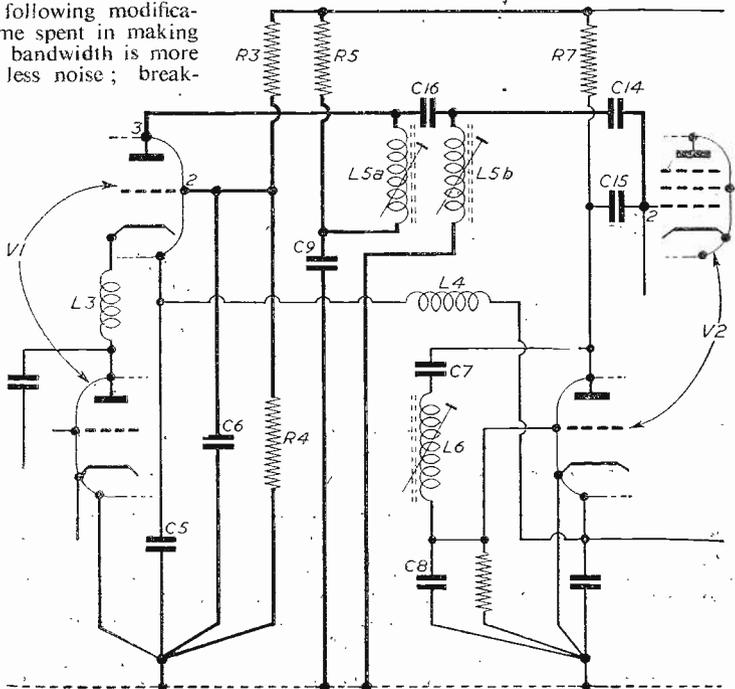


Fig. 2.—Modifications to the P.T. Converter shown in heavy lines.

from its former and its feed resistor R5 is also taken out of the chassis.

There should now be plenty of room for mounting the additional coil former between the L5 former and the valvholder of V1. Its precise location is not critical except that the centres of the two formers should be about $\frac{3}{8}$ in. apart. No drilling dimensions are specified as it is easier to mark out the holes direct from the coil former after determining the

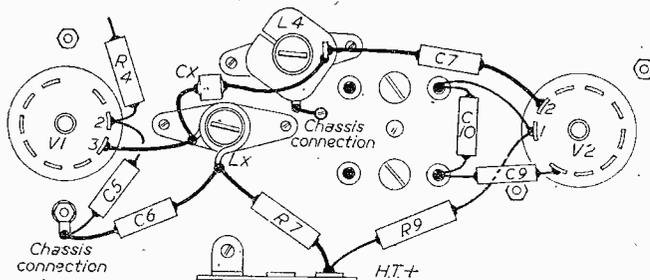


Fig. 3.—Modifications to the Teletron Converter. Note new position of L4.

best position. A former that mounts completely under the deck is preferable to the type that projects partly through the chassis—otherwise difficulty may be encountered because of the projection fouling the valvholder.

Resistors R3 and R4 can be repositioned and connected as shown in the diagram, Fig. 1.

The new coil L5a consists of $3\frac{1}{2}$ turns of 18-gauge tinned copper wire with the turns spaced approximately twice the diameter of the wire. This is placed on the new former and the bottom of the coil goes to pin 3 of V1. The top is connected to H.T. through a 1 K Ω resistor (use R5) and decoupled by a 1,000 pF condenser C9, as shown in Fig. 2.

On the former used for the original coil (L5) is wound a new coil of $4\frac{1}{2}$ turns similar to L5a. The new coil is designated L5b. It is important that both L5a and L5b are wound in the same direction and it is advisable to wind them in anti-clockwise direction, as shown in the diagram.

The bottom of L5b (the end nearest the chassis) is earthed at the nearest convenient place—a tag under the adjacent fixing screw of V1 valvholder is probably best—and the top end is connected to pin 2 of V2 through C14 (10 pF). The top end capacitive coupling between the two coils is arranged by connecting a small condenser from the top of L5b to pin 3 of V1. A ceramic type is recommended for this new condenser which need not be greater than about 2 pF.

Neutralising

In the author's case, an increase in value of the condenser in the bottom end of the aerial input coil (C2) resulted in a useful increase of signal output. It was necessary to increase the value to 17 pF for maximum gain.

Aerial Input Coil

This was changed to four turns of 20 s.w.g. tinned copper wire spaced approximately twice the diameter of the wire with two turns of 24 s.w.g. double-cotton covered for an aerial coupling coil wound on at the earthy end.

Other Designs

This simple modification to the form of coupling the two valves appears to be applicable to other similar circuits. In the case of the Teletron Mk. II arrangement for instance, the same useful increase in gain can be achieved. The changes for the Teletron are somewhat simpler to incorporate as ample room already exists under the chassis for the additional components.

The revised chassis layout showing the new arrangement is shown in Fig. 3 and the theoretical circuit is given in Fig. 4.

Here again the spacing between the coupling coils L4 and Lx can be about $\frac{3}{8}$ in. to $\frac{1}{2}$ in. L4 supplied in the coil kit is used as the grid coil and a new coil Lx is connected in the anode circuit of V1. Lx consists

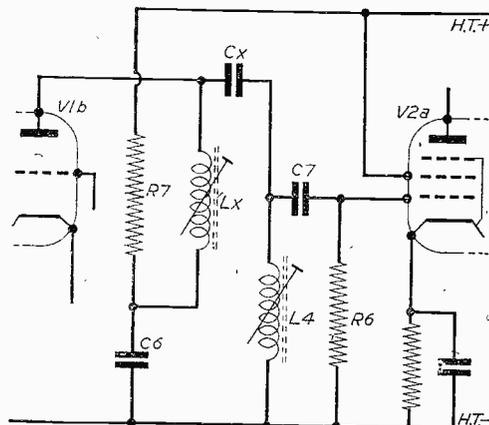


Fig. 4.—Circuit of the modifications to the Teletron Converter. Cx is 2 pF, and Lx consists of three turns widely spaced.

of three turns of 18 s.w.g. tinned copper wire with considerable spacing between the turns so that the coil occupies the whole of the former.

PRACTICAL WIRELESS JUNE ISSUE NOW ON SALE PRICE 1/3

The current issue of our companion paper "Practical Wireless," now on sale features the construction of a car radio from an ex-Government unit (the R1124). This is a complete constructional article and the actual work of modifying the set will be found well within the capabilities of the average amateur.

A Hi-Gain Pre-selector is another constructional feature in this issue, and it consists of a two R.F. pentode stage with a self-contained coil pack. There are some further constructional details of the "Seven-Five" Superhet, and amongst the other articles will be found a simple Bench Supply giving a stabilised high voltage output, details of various Tone Controls, Using Test Instruments, a further article in the series on Practical Amplifier Design, Transmitting Topics, Valves for Battery Portables, Short-Wave Notes, and the usual features. The Servicing Notes this month are on the G.E.C. BC5246 Series.



FOR VALVES—GUARANTEED NEW AND BOXED

074	6/-	6F11	13/-
1A3	6/-	6F13	14/-
1A5GT	6/6	6F15	14/-
1A7	11/6	6G64	4/-
105GT	9/6	6H6	3/6
1H5GT	10/6	6J5	5/6
1N5GT	10/6	6J5GT	5/6
1L4	8/6	6J5M	6/6
1L4S	6/9	6J6	7/6
1R5	8/-	6J7G	6/6
1R5	7/6	6K6GT	6/6
1T4	7/6	6K7G	5/6
1U5	8/-	6L7GT	5/6
2X3	4/-	6K7	6/9
3A4	7/-	6K8	8/9
3Q4	9/6	6K8GT	9/6
3Q5	10/-	6L6G	9/6
3D6	5/6	6L7G	7/6
3R4	8/6	6M7	7/-
3V4	8/6	6Q7G/GT	7/-
4D1	3/-	6S1	9/-
42	8/-	6SA7GT	8/-
514G	8/6	6S7	7/6
5Y3GT	8/6	6S7	6/-
5Z4	8/6	6S7GT	8/-
5Z4G	8/9	6S7	5/6
6A8G/GT	10/6	6S7	8/6
6AC7	6/6	6S7	9/3
6AM5	6/6	6S7	8/6
6AL5	7/-	6U3G	15/-
6AM5	5/-	6U7G	9/-
6AM6	7/6	6V6G/GT	9/6
6AQ5	9/-	6X4	7/6
6AT6	8/9	6X4	8/-
6B4	5/-	6X5GT	7/6
6B8	4/-	7B6	9/6
6BA6	8/-	7B7	9/6
6B8B	8/-	7C5	8/6
6B9B	8/6	7C9	9/6
6C4	7/-	7B7	8/6
6C8	4/-	7Q7	8/6
6C5GT	7/6	7R7	8/6
6C6	6/6	7S7	9/6
6C9	10/-	7Y4	8/6
6D6	7/6	75	10/6
6F6	7/6	80	8/6
6F6M	8/6	80	10/6

807	2/6	EBP80	11/6	PL82	11/6
8D2	6/6	EC91	9/6	PL83	13/-
9D2	3/6	ECC31	8/6	PP225	5/-
9001	5/6	EC94	12/6	PP25	13/6
9003	5/6	EC135	13/6	PS80	10/-
9004	5/6	EC142	10/6	PS81	11/6
9006	6/-	EC181	13/6	PS82	10/6
954	2/6	EC190	10/6	QP21	7/6
955	4/6	EP22	9/6	SP22	6/6
956	3/6	EP41	11/6	SP220	6/9
1062	12/6	EP42	13/6	TP22	8/-
1071	12/6	EP89	10/-	UB29	13/6
1079	12/6	EP86	13/6	U403	10/-
10713	11/6	EL41	11/6	UB41	9/-
12A6	6/9	EL84	12/-	UBC41	11/-
12AH7	6/9	EM34	11/6	UCH42	11/-
12AT7	9/6	EM80	12/6	UF41	11/6
12AT7G	9/6	EY51	13/6	UL41	11/6
12BA6	10/-	EY86	13/6	UY41	10/6
12BB6	10/-	EZ40	10/-	VR21	3/-
12H6	5/-	EZ41	11/-	VR83	6/6
12J5	6/6	EZ80	12/6	VR84	2/-
12K7	9/6	FL148	2/-	VR55	7/6
12K7	9/6	EY91	7/-	VR56	6/6
12K8	11/-	FW4/500	7/-	VR57	8/-
12Q7	9/6	GZ32	12/6	VR65A	3/3
12RC7	7/6	H30	5/-	VR66	3/6
12RG7	7/6	HL23DD	7/6	VR91	5/6
12SH7	5/6	IP211C	6/9	VR91YL	7/6
12S7	8/6	HP4101	7/-	VR92	2/-
12SK7	6/6	KL35	8/6	VR105/30	7/6
12SQ7	8/6	KT2	5/-	VR118	4/6
12R87	7/6	KT5	12/6	VR119	4/6
20D1	10/6	KT66	12/6	VR119	4/6
20L1	12/6	KT66	12/6	VR136	7/6
25L6GT	9/6	KT67	8/6	VR137	5/6
25U4GT/10	10/-	KTZ41	6/6	VR150/30	9/6
25Y3G	11/6	LP220	6/9	VR150/30	8/6
25Z4G	9/6	MH4	5/6	VP23	8/6
25Z6GT	9/6	MPEN5	12/6	VS70	3/6
35L6GT	9/6	N78	12/6	VT32	8/6
35V4	10/-	P41	9/6	VT50	6/6
35Z4GT	9/6	P215	5/6	VU39	8/9
50L6GT	9/6	PEN25	6/6	VU41	9/6
AC6P/8N	8/6	PEN46	8/6	VU42	9/6
ATP4	6/6	PK8220A	8/6	VU121A	3/6
D173M	10/-	PC84	13/6	W77	8/6
DM70	10/6	PC180	13/6	W61	8/6
EAB80/13/6	13/6	PC182	12/6	X65	10/6
EAC91	10/6	PC183	12/6	X66	11/6
EAP42	12/6	PC182	12/6	X63	9/6
EBC41	9/-	PC183	12/6	Y87	2/6
ER41	11/6	PL81	13/6	5R4CY	9/6

MAINS DROPPING RESISTANCES

725 ohms Eric tap at 600 ohms	1/6
650 ohms taps at 375 ohms, 500 ohms, 3 ohms, 50 ohms	2/6
770 ohms Mains Dropper for Miglet Radios with a tap at 125 ohms, size 3in. long x 3/16 in. dia.	1/3
Dazole Mains Dropper 3A, cement coated with 2 sliders	3/9
2 amp. as above, 1,200 ohms	3/9
Green Vitreous Mains Dropper, 1,328 ohms, 2 taps	1/3
Zenith Mains Dropper, 910 ohms	2/6

CRT ISOLATION TRANSFORMERS

NR9A, 2 volt. NR9B, 4 volt. NR9C, 6.3 v. NR9D, 10.8 v. NR9E, 13.3 v. Price 10/6 each, all for use on receivers with own transformer.	
NR11. Input 230/240 v., output 2.2-2.2-2.3 volts at 2 amps. 17/6 each.	
NR12. Input 220/240 v. Multi output 0-2.4-6-3.7-3-10-13 volts, 25% and 50% BOOST. 21/- each.	
NR13. Input 220/240 v. Output 0.3 v. with 25% and 50% BOOST. Price 17/6 each.	

TYANA SOLDERING IRON

Lightweight 40 watt iron with easily replaceable elements and lites. 200/250 v. Price 16/9 each.

PURETONE TAPE

1,200ft. Reels, Plastic Spool. 17/6 each.

WIRE WOUND CONTROLS

By Colvern, etc. All with 1/16 in. Spindle.

5 ohms, 100 ohms, 200 ohms, 250 ohms, 500 ohms, 1K ohms, 3K ohms, 10K ohms, 20K ohms, 25K ohms and 50 K ohms. All 2/6 each.	
---	--

OUTPUT TRANSFORMERS

Multi Ratio Type	6/6
Miglet for 354 Output	4/6
Standard 5,000 ohms	4/6
Standard 10,000 ohms	4/6
Ironcore Jack Plug and Socket	2/6
Belling Lee 7-Pin Plug and Socket	1/6

SPECIAL PURCHASE!

G.E.C. Cabinet Loudspeakers, Cat. No. BG1935, 8in. P.M. Moving Coil Loudspeaker Unit, 2/4 ohms, with Volume Control. Price 52/6 each.

PHIFCO ALL-IN-ONE RADIO METER

Tests L.T. 0-6 v. A.C./D.C., H.T. 0-240 v., A.C./D.C., M/A 0-30. Black Bakelite Case. Internal Battery for Circuit Testing. Price 32/6 each.

VARIABLE CONDENSERS

3 gang .00075 mfd.	5/6
2 gang .00035 mfd.	5/9
2 gang .0005 mfd. with feet and trimmers	7/6
2 gang Miglet with dust cover .00025 mfd. with trimmers	8/6
2 gang Miglet .0005 mfd.	7/6

STC RECTIFIERS

RM 1 ... 4/-	RM 3 ... 5/6
RM 2 ... 4/8	RM 4 ... 16/-

SMALL SUB-CHASSIS

With 2 valveholders for 95A, 955 type of valves ... 5/- each

PENCIL RECTIFIERS


K 3/25 ... 5/8	K 3/50 ... 8/8
K 3/40 ... 7/6	K 3/75 ... 9/8
K 3/45 ... 8/2	K 3/100 ... 14/8

HEATER TRANSFORMER

Primary 230 v.

Available:

2 volt 1 amp.	4/6
4 volt 1.5 amp.	5/-
5 volt 2 amp.	10/-
6.3 volt 1 amp.	6/-
2 volt 3 amp.	7/9
4 volt 3 amp.	10/-
6.3 volt 3 amp.	5/-
6.3 volt 3 amp.	9/-
12 volt .75 amp.	5/-

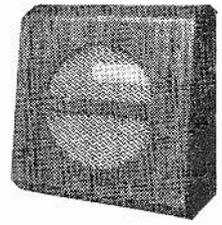

LOUDSPEAKER CABINETS

This attractive walnut finished cabinet is available for 6in. or 8in. speaker units. Metal speaker fret, complete with back and rubber feet.

6in. type: Measures 8 1/2 in. x 8 1/2 in. x 4 1/2 in. at base. Price 16/6 each.

8in. type: Measures 10 1/2 in. x 10 1/2 in. x 5 in. at base. Price 20/6 each.

5in. type: Measures 6 1/2 in. x 4 1/2 in. x 7 1/2 in. 16/6

LOUDSPEAKER UNITS

all 2/4 ohm 5in. types by Goodmans, Elec. Lectra, Baffle, etc., all 17/6 each.

6in. types by Goodmans, R. & A., Plessey, etc., all 18/6 each.

8in. types by Goodmans, Plessey, R. & A., etc., all 18/6 each.

10in. types by Celestion, R. & A., Plessey, etc., all 25/6 each.

12in. types by Plessey Lightweight unit, 35/- each.

Goodmans 4in. x 7in. Elliptical speaker, 19/6 each.

8in. units with output transformer by Goodmans & Lectra, 22/6 each

MAINS ENERGISED TYPES

8in. 600 ohm field, 21/- 6in. 600 ohm field, 17/6. Postage on all above, 1/6 extra.

TRANSFORMER MT6

Small mains transformer suitable for TV converters, etc. Primary, 250 v. Secondary, 250 v. 40 mA and 6.3 v. 1.5 A. Price 15/6 each. Postage 1/6.

CONDENSERS

BEC 100 MFD 25 v.	1/9
BAC 500 MFD 12 v.	1/9
TCC 25 MFD 25 v.	1/3
DUBILIER 100 mfd. 12 v.	1/9
BEC 50 MFD 50 v.	2/-
TCC 25 MFD 50 v.	1/9
TCC 50 MFD 25 v.	1/9
TKS 250 MFD 12 v.	1/6
BEC 250 MFD 25 v.	1/6
TCC 12 MFD 50 v.	1/-
TCC 50 MFD 12 v.	1/9
BEC 250-250 MFD 6 v.	1/6
DUBILIER 50-12 MFD 12 v.	1/9

CHARGER RECTIFIERS—All Full Wave

12 volt 1 amp.	5/3
12 volt 2 amp.	8/6
12 volt 3 amp.	13/6

VOLUME CONTROLS

Type with Single Pole Switch.

5K ohms; 10K ohms; 20K ohms; 50K ohms; 100K ohms; 1 meg.; 2 meg.; 5 meg.	
--	--


All 2/6 each.

DUAL VOLUME CONTROL

With Double Pole Switch 500K ohms and 500K ohms. Price 6/9 each.

VALVE HOLDERS

B7G, 9BA, B9G, etc., Moulded Types	9d.
B7G with Screening Cans	1/6
Ceramic International Octal	1/-
Duolect Paxolin	9d.

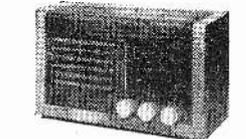

★ Easy to Build.
★ Valves 6J7, 6K7, 6V6GT with metal rectifier.
★ Walnut cabinet.

Full instructions, point to point wiring diagram, Circuit diagram, and full shopping list 1/-. All components may be purchased separately.

Build this Excellent Kit for Yourself!

Alpha 3 valve T.R.F. Kit

£5. 10. 0

T.S.L. FERRO-MAGNETIC AERIAL ROD

A length of Ferrite rod with full instructions for winding Medium or Long and Long Wave internal aerials. 6/- each.

WHEN ORDERING PLEASE QUOTE "DEPT. P.T."

ALPHA

RADIO SUPPLY COLUMN

5/6 VINCES CHAMBERS

VICTORIA SQUARE

LEEDS.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra, as follows: Orders value 10/- add 9d.; 20/- add 1/-; 40/- add 1/6; £5 add 2/- unless otherwise stated. Minimum C.O.D. fee and postage 2/3.

MAIL ORDER ONLY

RADIO SUPPLY CO. (LEEDS) LTD.

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/- extra under 10/-; 1/6 extra under £1; 2/- under £3. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d.; Trade list 5d.

R.S.C. TRANSFORMERS

Fully Guaranteed.
Interleaved and Impregnated.
Primaries 200-230-250 v. 50 c/s screened
TOP SHROUDED DROP THROUGH
260-0-260 v 70 ma. 6.3 v 2 a, 5 v 2 a ... 16/9
350-0-350 v 80 ma. 6.3 v 2 a, 5 v 2 a ... 18/9
350-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a ... 29/9
FULLY SHROUDED UPRIGHT
250-0-250 v 60 ma. 6.3 v 2 a, 5 v 2 a
Midgett type, 2i-3-3in. ... 17/6
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 26/9
250-0-250 v 100 ma. 6.3 v 6 a, 5 v 3 a
for R1335 Conversion ... 31/-
300-0-300 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 26/9
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 150 ma. 6.3 v 4 a, 0-4-5 v 3 a 31/6
425-0-425 v 200 ma. 6.3 v 4 a, C.T. 6.3 v
4 a, C.T. 5 v 3 a ... 49/9

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s Primaries: 6.3 v
1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9;
12 v 1 a, 7/11; 6.3 v 3 a, 8/11; 6.3 v 6 a, 17/9

CHARGER TRANSFORMERS
200-250 v 0-9-15 v 1 a, 11/9; 0-9-15 v 3 a, 16/9
0-9-15 v 5 a, 19/9; 0-9-15 v 6 a, 22/9

OUTPUT TRANSFORMERS
Standard Pentode 5,000 to 3 ohms ... 4/9
Small Pentode 5,000 to 3 ohms ... 3/9
E.H.T. TRANSFORMERS 200-230-250 v
2,500 v 5 ma. 2-0-2 v 1.1 a, 2-0-2 v 1.1 a
for VCR27, VCR57 ... 36/6

SMOOTHING CHOKES
250 ma 5 h 50 ohms ... 11/9
100 ma 10 h 250 ohms ... 8/9
80 ma 10 h 350 ohms ... 5/6
80 ma 10 h 400 ohms ... 4/11
SELENIUM METAL RECTIFIERS
G.E.C. 300 v 250 ma. 12/9; 120 v 40 ma. 3/9;
6.12 v 1 a F.W. 5/9; 240 v 30 ma 5/9; 6.12
v 2 a F.W. 8/9; 6.12 v 4 a. 16/9; 250 v 80
ma. 7/9; 6.12 v 6 a F.W. 19/9; 6.12 v 10 a,
29/9.

BATTERY SET CONVERTER KIT
All parts for converting any normal type
of Battery Receiver to A.C. mains 200-250 v
50 c/s. Supplies 120 v 90 v or 60 v at 30 ma.
Fully smoothed and fully smoothed 1.1
of 2v at 0.4 a to 1 a. Price including circuit
49/9. Or ready for use, 9/9 extra.

**ALL DRY RECEIVER BATTERY
ELIMINATOR KIT**—All parts for the
construction of a unit (metal-case
5 1/4-2in.) to supply Battery Portable
receivers requiring 9v and 1.5 v. Fully
smoothed. From 200-250 v 50 c/s mains.
Price, inc. point-to-point wiring dia-
grams, 39/9. Or assembled and tested
at 46/9.

**R.S.C. TAI HIGH QUALITY TAPE
DECK AMPLIFIER**. For All Tape
Decks with High Impedance Playback
and Erase Heads, such as Lane, Truxo
Adjustment to type of deck Ready for
made by alteration of a Use ONLY
resistor. For A.C. Mains
200-250 v. 50 c/s. Positive
compensated identification of
recording level given by Magic
Eye. Recording facilities for 15. 7 1/2 or
3 1/2 in. per sec. Automatic equalisation at
the turn of a knob. Linear frequency
response of ± 3db., 50-11,000 c.p.s. Negative
feed-back equalisation. Minimum
microphony and hum. High output with
completely effective erasure and dis-
tortionless reproduction. Sensitivity is
15 millivolts so that any kind of crystal
microphone is suitable. Provision is
made for feeding a P.A. amplifier. Unit
can also be used as a gram-amplifier
requiring input of 0.75 v R.M.S. Carriage
7/6. Illustrated leaflet 6d.
EX-GOVT. UNIT RDP1—Brand new.
cottoned. Complete with 12 valves,
including 5Z4G. Also mains trans., F.
choke rectifier, etc., etc. Only 28/9.
Carr. 7/9.

11 GNS

Dept., N. 32, THE CALLS, LEEDS 2.

SMALL POTTED MAINS TRANSF.
Removed from New Ex-Govt. units.
Primary 0-200-230-250 v Secs. 250-0-
250 v 60 ma. 6.3 v 2 a, 5 v 2 a 11/9
Size 3 1/2 x 4 1/2 x 3 in.

CO-AXIAL CABLE 1in.
75 ohms 14/6
Twin-Screened Feeder ... 11d. yd.
EX-GOVT. SMOOTHING CHOKES.—
100 ma 10 h 250 ohms Tropicalised ... 3/11
150 ma 6-10 h 150 ohms ... 6/9
150 ma 10 h 150 ohms ... 11/9
250 ma 10 h 50 ohms ... 14/9

E.H.T. SMOOTHERS
.5 mid 3,500 v can, 3/6; .5 mid 2,500 v
Blocks (ex-Govt.), 2/11.
BATTERY CHARGER KITS.—Consist-
ing of attractive Green Crackle Case,
Transformer, F.W. Rectifier, Fuse, Fuse-
holder, Tag strip, Grommets, and Circuit.
For mains input 200-230-250 v 50 c/s, 6 v 2 a,
25/9; 6 v or 12 v 2 a, 31/6; 6 v or 12 v 4 a,
49/9. Any type assembled and tested for
6/9 extra.

**R.S.C. 6 v or 12 v
BATTERY CHARGER**
For normal A.C. mains
input 200-230-250 v 50 c/s.
Selector panel for 6 v or
12 v charging. Variable
charge rate of up to 4
AMPS. Fused, and with
meter. Well ventilated
case with attractive
hammer finish. Guar-
anteed for 12 months.
69/8. Carr. 2/6.



TV. CONSOLE CABINETS
Handsome well constructed with beautiful
figured walnut veneer finish. Size 40in.
high, 24 1/2 in. wide, 20in. deep. For 15in. or
17in. Tube. Limited number at only 9gns
Above for callers only.
Table Model types with doors, 4 gns. 6/6
carr. Table Model. 12in. Tube, 29/9.5/- carr.
BATTERY CHARGERS.—For mains
200-250 v 50 c/s. Output for charging 6 v or
12 v at 1 amp. In strong metal case. Only
25/9. Above can also be used for electric
train power supply.

VIDEO ELECTRONICS

(LONDON) LTD.
(DEPT. PT.)

Head office: 27. Bacon Street, London, E.1.
Works: 16/22, Bacon Street, E.1.
Telephones: Bishopsgate 0419/0410.

T.V. Tubes

Cheap, reliable high grade seconds and recon-
ditioned C.R.T.s, as supplied to the trade and
leading Television Insurance Companies, prices
from £3.

Valves

Send at once for our useful list of cheap valves
which will save money, we are the cheapest in
the trade.

Condensers

Electrolytics, bias, coupling, etc., etc., at give-
away prices. All types stocked.

Resistors

A fine stock of these at very low prices.

T.V. & Radio Cabinets

A few 17" Table cabinets, new, ex famous
manufacturer, and about 500 very handsome
radio cabinets made for export.


Send for stock list of speakers, valves, components
and T.V. and Radio Spares.

All our goods are guaranteed.

COMMERCIAL TV FOR YOUR VIEWMASTER

All parts in stock.

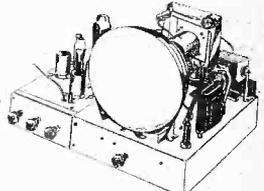DENCO ready wound
modification coil set. Price 20/-
DENCO 3 station tuner
coils and screens. Price 30/-



DENCO Switch kit, fine tuner, and coil modification plates, 27/-
T.C.C. Complete kit of condensers printed circuits and
special valveholders. £2-3-0.
LAB. Complete set of resistors as specified. 5/-
Coaxial plugs, 1/3. Sockets, 1/3.
VALVES. PCC84 and PCF80, 10/6 ea.
TRANSFORMER. Special 16 volt, 10/6.

This is THE conversion for Viewmaster, no patterning, no
breakthrough, full definition.


Please add postage on all orders under £2.

HOME RADIO OF MITCHAM

187, LONDON ROAD, MITCHAM, SURREY.

Telephone: MITcham 3282.

TELENEWS

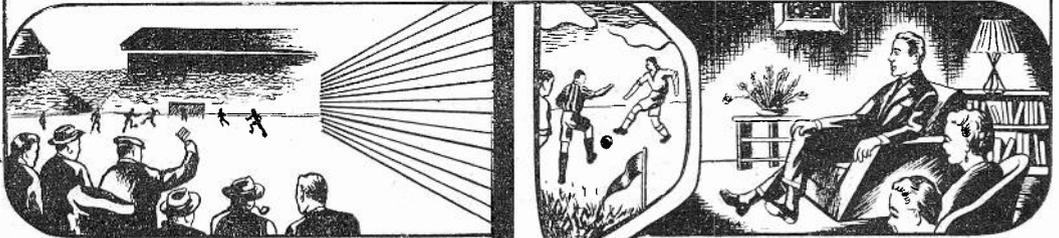

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of March, 1956, in respect of receiving stations situated within the various postal regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,296,020
Home Counties	654,174
Midland	993,223
North Eastern	873,564
North Western	830,161
South Western	381,627
Wales and Border Counties	320,466
Total England and Wales	5,349,235
Scotland	348,152
Northern Ireland	42,206

Grand Total 5,739,593
 During March the number of television licences increased by 90,327.

14,261,551 broadcast receiving licences, including 5,739,593 for television and 293,459 for sets fitted in cars, were current in Great Britain and Northern Ireland at the end of March, 1956.

U.S. Set Replacements

AN interesting sidelight on American policy is revealed by some recent figures of set replacements. The G.E.C.'s tube market research manager stated that sets are scrapped when they need tube replacements, and a boom is expected in set replacements this year. It is suggested that nearly all of the 3,533,000 sets sold in 1948-49 will be eligible for replacement this year. In 1954 1,630,000 sets were scrapped, and in 1955 2,370,000 were replaced.

Television Band III Converters

THE Post Office has found that in some cases where Band III television programmes are taken by means of a "converter" added to a Band I set, viewers are liable to cause interference to others.

It is a condition of the receiving licence that the set shall not cause interference to other wireless (including television) users. Having

consulted the British Radio Equipment Manufacturers Association the Post Office advises users of Band III converters which cause interference to ask their radio dealers about the most suitable steps which should be taken to stop the interference. The Post Office regrets that it cannot itself undertake the work of curing the interference.

Air-to-ground TV Tests

REPRESENTATIVES of Scotland Yard and senior Army officers recently watched a demonstration in Bristol of air-to-ground television by means of a helicopter. The system could be used by police in manhunts or for traffic control.

A helicopter took off from Filton and flew at heights of 500ft. to 1,000ft. A camera mounted in the plane transmitted pictures to a screen on the ground. Tests lasted half an hour.

New BBC Transmitter

THE contract for building work for the new Scottish Television Transmitting Station at Rosemarkie, about 12 miles N.N.E. of Inverness, has been placed with Alexander Hall & Son (Builders) Ltd., of Granitehill Road, Northfield, Aberdeen.


The contract includes the construction of the transmitting station building and of the access road.

Work on site will start almost immediately and it is expected that the building will be sufficiently far advanced for the installation of plant to begin during the late summer this year.

Croydon ITA Station

IT is reported from ITA's London television station at Croydon, that up to December 28th the Marconi vision and sound transmitters installed there had been radiating for a total of 1,333 hours, of which 700 hours had been taken up by programme time.

During the whole of this period

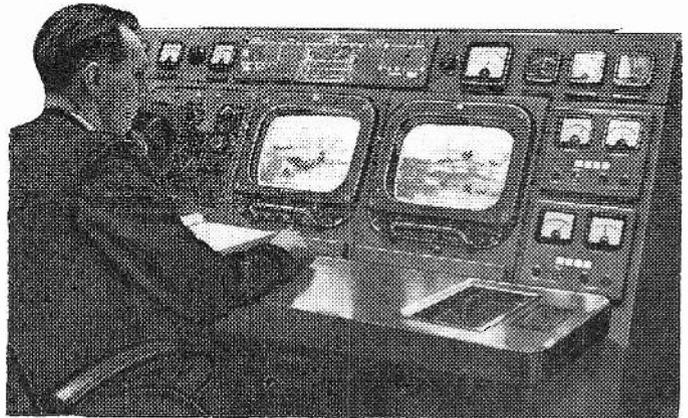

Mr. Cutler, of Norbury, at the main control desk of the new BBC transmitter at Crystal Palace. Only a temporary Mast Aerial is being used for the time being. The permanent Tower will come into use later in the year.

the vision transmitter has been "off the air" due to breakdown for only 23 minutes 13 seconds, and the sound transmitter for 12 minutes 40 seconds.

Expressed as a percentage, vision transmitter breakdowns amount to only .029 per cent. of the total hours of radiation, while sound transmitter breakdowns represent .016 per cent.

Colour TV Award

FROM Philadelphia comes news that English-born Frank Bingley has been awarded the 1956 Vladimir K. Zworykin Television Prize for outstanding contributions to the development of colour television. The annual winner is selected by the Institute of Radio Engineers and the award is made at the annual meeting of the I.R.E. in March.

Mr. Bingley, Executive Engineer of Philco Research Laboratories, received the award for his exhaustive and penetrating study of the relationship between the science of colourimetry and the compatible colour television signal developed by the National Television System Committee and approved by the Federal Communications Commission.

Born in England where he was graduated from the University of London, he joined the Philco Research Laboratories in 1931, where he has since been engaged in the development of electronic transmitting and receiving equipment, as well as television-systems engineering. At the moment he is actively engaged on Philco's intensive research programme on research on colour TV.

Behind the Scenes

VIEWERS of the BBC Television programme "Science Review" on April 4th had a "behind the scenes" view of how the most important component in their TV set is made.

During the programme a filmed sequence of some interesting aspects of the production of cathode ray tubes was featured. What to the viewer is a flattish, oblong screen

was seen to be just part of a highly complex piece of scientific apparatus.

The film sequences were adapted by Norman MacQueen—who produces the programme jointly with James McCloy—from the Mullard film "Made for Life."

Pye Atomic Camera Authority

AFTER demonstrating industrial television to the Atomic Energy Authority last year Pye Limited were given a contract to design a special camera capable of being used inside an atomic reactor at the Authority's Cumberland factory. This has now been completed and has been delivered to Harwell for tests prior to its use at Calder Hall.


The camera, which is based on Pye's normal industrial television equipment, has had to conform to certain very rigid specifications, and as a result of the experiments which were carried out at the Authority's premises it was found that special materials had to be used. The work which has been done by the engineers can be regarded as a triumph of mechanical engineering, particularly in view of the complex problems of design. For ease of manipulation the camera carries its own source of illumination, consisting of a series of four small but powerful bulbs grouped around the camera's lens.

As the camera is liable to be exposed to temperatures of up to 200 deg. C., the control cables leading to the camera head are enclosed in a flexible hose through which carbon dioxide is pumped to cool the cables and camera. Radio-

active dust can be removed from the camera, after its withdrawal from the reactor, by washing down.

Russia Buys British

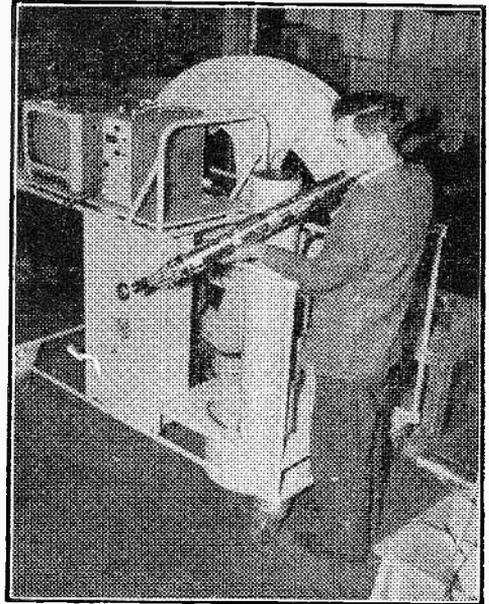MARCONI'S WIRELESS TELEGRAPH CO., LTD., are to supply the U.S.S.R. with a



View of the atomic camera which is held by Mr. W. L. Cruickshank, Development Engineer, with the controls and receiving set—mounted on a portable trolley.

large quantity of television equipment. Amongst the main items in the order are included two three-camera television outside-broadcast vehicles, two mobile petrol-electric trailer power units and a comprehensive supply of spares.

Marconi Mk. III cameras fitted with 4½ in. English Electric Image Orthicon pick-up tubes are incorporated in the O.B. vehicles. Facilities in the latter include sound and vision mixing equipment, duplicated synchronising generators and comprehensive inter-communication and commentators' panels.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.


Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.


MISCELLANEOUS BARGAINS

Valves.—Most types available, many at really bargain prices.
 Coaxial Cable.—Cellular polythene—super low loss for Band III—11d. per yard.
 200 m.a. Chokes, 8.6.
 Mu-Metal Screens for V.C.R.97, etc., 8/6 per pair.
 Resistors.— $\frac{1}{2}$ and 1 watt, 5d.; 1 watt, 6d.
 American Microphone Inserts.—4/6 each.
 .1 mfd. 350 v. Metal Case Condensers.—3/- per dozen.
 1,000 pF. Ceramic Condensers.—1/- per dozen.
 Extra High Voltage Test Condensers. .001 mfd. 28,000 volt test (20,000 volt) working at 8/6 each.
 Silver Mica Condensers.—50 assorted containing (3 of each) values from 2 pf. to 2,000 pf. 10/-, 100 assorted containing (3 of each) values from 2 pf. to 2,000 pf., 17/6.
 Metal Rectifier, 250 volt, 250 milliamps, 12/6 each.
 S.P. 61 Valves, brand new, and perfect, 4/6 each, 43/- per doz.
 Potted E.H.T. transformer, 1500 v. at 5 m.a. and 2 v. at 2 a. 12/6, 4 mfd. 400 volt block condenser, 19/- per doz.
 Miniature American relays double pole, 4.6 each.

FINE TUNERS

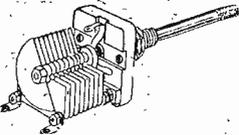

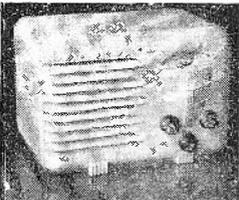Ceramic trimmers all with in. spindles and 1/8 in. caps, 10, 15, 30, P.F. all 2/3 each or 24/- per dozen.



MAINS-MIN

Uses high-efficiency coils, covers long and medium wavebands and fits into the neat white or brown bakelite cabinet—limited quantity only. All the parts, including cabinet, valves, in fact, everything, £4 10.0, plus 3/6 post. Constructional data free with the parts, or available separately 1/6.


INTERFERENCE FILTER

To eliminate patterning and other interferences. Two models—one high-pass cuts out frequencies above 45 m.c. the other low-pass cuts out frequencies below. Price 2/7.6 each, postage 2/6.


TRANSFORMER SNIP

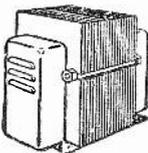11.6 Post 2/-

Fully shrouded—standard 200-250 v. primary 280-0-280 at 80 m.a. 6.3 v. at 3 amp. 5 v. at 2 amp.



THE "CRISPIAN" BATTERY PORTABLE

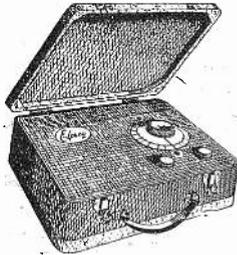

A 4-valve truly portable battery set with very many good features as follows: Ferrite rod aerials. Low consumption valves. Superhet circuit with A.V.C. Ready built and aligned chassis if required. Beautiful two-tone cabinet covered with I.C.I. Rexine and Tygan. Guaranteed results on long and medium waves anywhere. All parts, including speaker and cabinet, are available separately or if all ordered together, the price is £7/15/0 complete ready built chassis, 30/- extra. Instruction booklet free with parts or available separately, price 1/6.

ADDDITA—BAND III CONVERTER

Any television receiver, whether superhet or straight, home constructed or factory built, which at present will receive B.B.C. will also receive I.T.A. if this converter is added. No modifications at all are necessary to the receiver. Simply plug in the aerial leads and connect to A.C. mains. The converter is in a neat metal case with provision for fixing to the side or the back of the set. Price £6/10/-, or H.P. terms available on request if required.


BUILD YOUR OWN CONVERTER

You can save at least £2 on the above if you build the converter yourself. Price of all components including stove enamelled case and even transfer for the front is £3 10/0 or £4/10/0 if mains components also required. Data are included free with the parts or available separately price 2/6. State whether Midlands or London.




OFFICE TELEPHONES

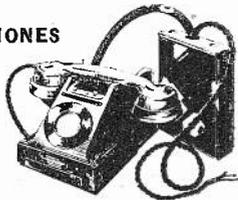New G.P.O. telephone sets with internal bell and push button switch easily connected together to form office intercom. Price £2/10.0 each. Post, etc., 2/6.




HIGH VOLTAGE TESTER

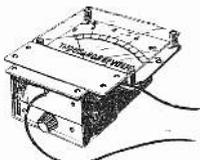


An instrument that will measure voltages up to 10,000 but which draws no current from the source, will probably be a valuable addition to your workshop equipment. It can be made entirely from odds and ends. Booklet giving full instructions, plans, etc., 2/6 post free.

THE CASCODER

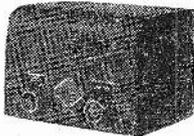Of the several circuits used for Band III conversion at aerial frequencies, undoubtedly the most popular is the Cascode circuit. We can offer a very good converter suitable for any Band I to any Band III station, in a very neat, polished cabinet with fine tuning, on/off mains. Band I-III contrast switches. Price £7/10/0, post and packing 2/6.



GRAMOPHONE AUTO-CHANGERS

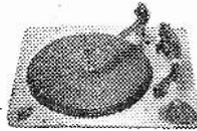


The latest models by very famous manufacturers. 3-speed with crystal turn-over pick-up, brand new and perfect, in original cartons. Choice of four from £7/15/0, carriage, ins., etc., 7/6.

BAND III PRE-AMP



In difficult areas it will be necessary to increase the signal level and this is the ideal unit for this purpose. It is A.C. mains operated and is fitted with input and output coax plugs. Price £4, post and packing 5/6.

THE ELPREQ E.H.T. GENERATOR

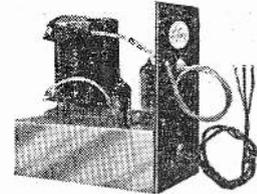

This unit contains three BVA valves. Output from 6 kv to 0 kv rectified with normal H.T. rail input but somewhat higher outputs can be obtained with higher H.T. supply. Dimensions are 6 1/2 x 4 1/2 x 7 1/2. Price 69.6, post packing, etc., 5/-.

CIRCUITS W.D.

Diagrams and other information extracted from official manuals. All 1/6 per copy, 12 for 15/-.

American	R.109
Service Sheets	78 receiver
A.1134	76 receiver
BC.348	R28 ARCS
BC.312	R1116 A
R.103A	RA-1B
B.C.342	AR88D
RA-1B	AN, APA-1
R-209	78
R-1155	76
R-1124A	R.T.18
R-1132A, R-1481	CAY-46-AAM-
R-1147	RADAR
R-1224A	A.S.B.-3
R-1082	Indicator 62A
R-1355	Indicator A.S.B.3
B.C.1200-A B	Indicator 62
B-455-A (or-B)	Indicator 6K
B-454-A (or-B)	R.F. unit 24
B-453-A (or-B)	R.F. unit 25
Transmitter	R.F. unit 25
T1154 B.D.J.N.	R.F. unit 27
Fifty-eight	Wireless set No.
walkie-talkie	19
Frequency	Demobbed valves
meter B.C.221	

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to E.P.E., LTD., Dept. 5, 123, Terminus Road, Eastbourne. Personal shoppers to one of these addresses please.

42-46, Windmill Hill, Epsom, Middx.	152-3, Fleet Street, E.C.4	29, Stroud Green Rd., Finchbury Park, N.4	249, Kilburn High Road, Kilburn, MAIda Vale 4921.
Phone: RUISLIP 5780	Phone: FLEET 2833	Phone: ARCHWAY 1049	
Half day, Wednesday.	Half day, Saturday.	Half day, Thursday.	

HERE IT IS!

THE NEW 1956 EDITION

NEWNES

Radio and Television Servicing

FREE for 7 DAYS

THIS is the most complete collection of models ever assembled—it provides all the data, circuit diagrams and component layouts you need to service over 1,550 different models. The work covers Multi-channel T.V. receivers, Band III converters, Radios, Radiograms, VHF/FM receivers and adaptors, Portables, Car radios—and can pay for itself within a week of receiving it. Prove this by claiming Free Examination NOW!

1,550 POPULAR MODELS including LATEST RADIO SHOW MODELS

TELEVISION

SERVICING DATA for—
 Ace, Alba, Ambassador, Argosy, Baird, Banner, Beethoven, Bush, Champion, Cossor, Decca, Defiant, Ekcovision, E.M.I., English Electric, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Mullard, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Rainbow, Raymond, Regentone, R.G.D., Sobell, Stella, Ultra, Valradio, Vidor.

RADIO

SERVICING DATA for—
 Ace, Ambassador, Banner, Beethoven, Bush, Champion, Cossor, Decca, Denco, Defiant, Eddystone, Ekco, Etronic, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Mullard, Murphy, Pam, Peto Scott, Philco, Philips, Pilot, Pye, Rainbow, Raymond, Regentone, R.G.D., Roberts Radio, Sobell, Strad, Ultra, Vidor.

**6 VOLUMES.
 3,150 PAGES.
 3,000 CIRCUIT, COMPONENT AND CHASSIS LAYOUT DIAGRAMS.
 FREE 2 YEARS' ADVISORY SERVICE.**

Owners said the last edition was worth a fortune! This New Edition is even more valuable. Prove it yourself by sending for Free Examination—no cost or obligation.

DON'T MISS THIS GREAT OPPORTUNITY

To: George Newnes, Ltd., 66-69 Great Queen St., London, W.C.2.

Send me Newnes RADIO AND TELEVISION SERVICING. I will either return it in 8 days or send 9s. deposit 8 days after delivery, then 10s. monthly, paying £9 9s. in all. Cash price in eight days £9.

Name.....

Address.....

Occupation.....

Signature.....
 (Parent's Signature if under 21)

Place X where it applies

HouseOWNER	
Householder	
Living with Parents	
Lodging Address	

RTV 119

ADCOLA
 PRODUCTS LIMITED
 (Regd. Trade Mark)

SOLDERING INSTRUMENTS

Sound jointing for the Home Radio Engineer

Protective Shield (List No. 68)
 $\frac{3}{16}$ " Detachable Bit Model (List No. 64)

Supplied for all volt ranges with no extra cost for low voltages. Bit sizes $\frac{3}{8}$ " to $\frac{1}{4}$ ".

Apply Catalogues:

Sole Proprietors & Manufacturers

HEAD OFFICE SALES AND SERVICE
ADCOLA PRODUCTS LTD.
 GAUDEN RD., CLAPHAM HIGH ST., LONDON, S.W.4. Tel: MACaulay 3101-4272.

17" TV TUBES 14"

*** 6 MONTHS' GUARANTEE ***

- 17" £7. 10. 0 RECTANGULAR. Tetodes and Triodes All popular makes and types. Ins. and carr. 15/6.
- 14" £5. 10. 0 RECTANGULAR. Latest types on all makes available. Ins. and carr. 15/6.
- 12" £5 ROUND. State make and type required. If possible state equivalent second choice. Due to very heavy demand for some makes. Ins. and carr. 15/6. 6 mth. Mullard, 3 mth. other types.


SPRING CLEARANCE OF GUARANTEED BARGAINS

- 9" 16/6 Types 22/18, 22/14C with slight burn. FREE post.
- 12" 50/- Types T12/72, T12/44. Tested, guaranteed 3 months. Ins. and carr. 15/6.
- 12" 12/6 Types 121K, 12XP4, 31/14C. Slight burn. Ins. and carr. 15/6.
- 14" £5 Types CRM 141, 142. Round Mazda's, 3 month guarantee. Ins. and carr. 15/6.
- 15" £5 Types CRM 151, 152A or B. Round, 3 month guarantee. Ins. and carr. 15/6.
- 16" £5 Types 41/1. 3 month guarantee. Ins. and carr. 15/6.

As we have been selling for the past 5 years. All enquiries welcomed. Please send cash with order.

Send 2d. stamp for FREE Catalogue.

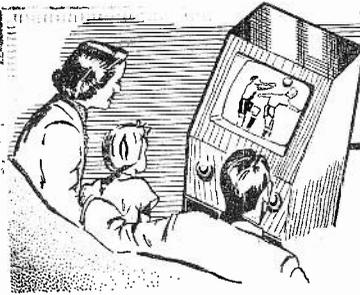100% MONEY BACK GUARANTEE **DUKE & CO** Tel: GRA 6677 CWO1 OF COD1
 621 ROMFORD RD. LONDON, E.12.



UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

TV NEWS AND NEWSREELS


EVER since the BBC abandoned their original newsreel format viewers have taken less and less interest in the news items on TV. At one time most viewers took care to switch on for the newsreel, and if they missed any special item looked forward to the weekend hour's newsreel saga of events of the week. This was produced in the well-tryed cinema newsreel style, with musical background almost throughout, sub-titles to sequences—and commentary when required. The sound-only repeat of the radio service news bulletin at the end of the TV programme seemed to be quite adequate. Then came the revised system of "News and Newsreel," which changed the style from cinema "magazine" presentation to the factual documentary stuff with newsreaders, diagrams, stills, short film sequences and other odds and ends. It was a thorough mess, at first, and the editorial board still seem unable to strike a format which interests viewers. The ITA have made the same mistake, and in addition make much use of speedily processed 16 mm. film sequences which are of poor quality. It was only natural that ABC-TV, with all the newsreel resources of the Pathé organisation behind them, should hesitate before taking IT News items which had probably been adequately covered by the 35 mm. cameraman of the Pathé Newsreel, in any case. This storm will probably die down and, in due course, the IT News will take a new shape, presented in an entertaining manner and not as a pale imitation of the evening doses of news put out by the BBC. Viewers prefer their news pills to be sugar coated! The advertisers on ITA quickly found that the BBC's News and Newsreel, even in its much improved form, had not cured the viewers of switching off!

MOVIE MUSEUM

ONE of the most interesting film series put on for a long time by the BBC is "Movie Museum," an American series which presents entertainingly some of the early efforts of film-making by D. W. Griffiths and other giants of the silent days of the cinema. Incidentally, the photographic values of some of these early films seemed to be very good, in spite of the fact that the print must have been made from a "dupe" negative—certainly not from the original negative. Perhaps the American film laboratory which processed this film specially for television has corrected some of the imperfections. By the way, this accurate judgment of TV print requirements is seen in many other American film importations, such as the "Burns and Allen Show," "I Love Lucy" and "Inner Sanctum," though the last named series is sometimes marred by poor sound.

SOUND ON TV

I SOMETIMES think that the golden rule for TV producers is to look after the picture and let the sound take care of itself. This especially seems to apply to many of the "commercials," which have good ideas and pictorial presentation but badly recorded or badly spoken dialogue or music. Advertisers would be well advised to make use of 35 mm. film for picture with magnetic sound. Occasionally, the ITA's telefilm sound apparatus is at fault and the optical scanning light can be heard scanning the edges of the film perforations. This results in a faint "harmony" 100-cycle buzz. Careful checks and tests should take care of this trouble and in the meantime the possibilities of using a magnetic strip for carrying the sound in the normal sound track position should be investigated. An alternative is to use entirely separate magnetic film, electrically interlocked with the picture film.

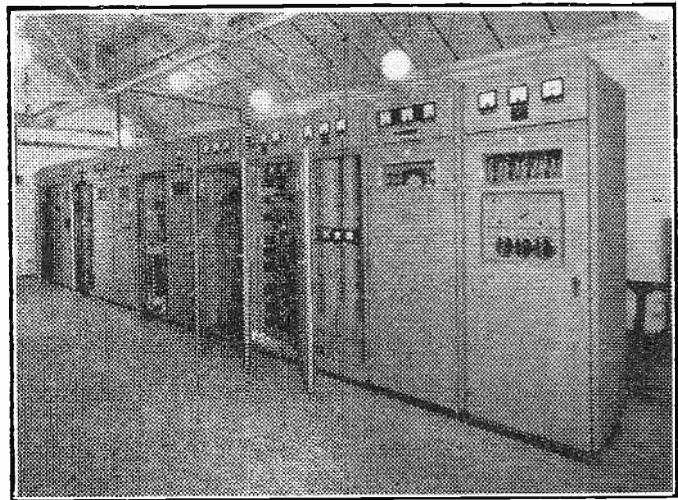

Marconi Vision and Sound Transmitters as used at ITA London and Winter Hill. The $7\frac{1}{2}$ kW vision transmitter occupies the first seven panels from the right; the $2\frac{1}{2}$ kW sound transmitter the remainder.

Live TV sound is also occasionally below par. This is often due to bad microphone placing or sound mixing. Dialogue is frequently drowned by music or effects. Too often are actors allowed to clatter tea cups or slam doors as they say their lines, thereby covering important key words with the extraneous noise. Close-ups of instrumentalists in orchestras are shown—with the sound of the particular

instrument faintly heard or not heard at all. I must say that this criticism does not apply to the transmissions of the Hallé Orchestra by AR-TV. This is usually excellent from the sound point of view, but not always as regards picture quality. Once again, Image Orthicon cameras demonstrate their crisp ability to add ten years to the age of Sir John Barbirolli and every member of his orchestra. When these TV cameras are good they are very, very good, but when they are bad they are horrid!

BBC STUDIOS

AT one time the sole BBC sound studio in London was a smallish room on the top floor of Marconi House, next to the 2LO transmitter. Every single item was sent out from this studio, from news announcements to orchestral concerts, the latter frequently performed under suffocating conditions. Two or three crude solid-back Post Office type carbon microphones were used. After a few months the BBC studio premises were removed across the Strand, to 2, Savoy Hill, where three sound studios sufficed for a very long time, supplemented by enterprising outside broadcasts from the adjoining Savoy ballrooms! Then came a rapid expansion of facilities, first at Savoy Hill, then at Broadcasting House and

BBC REAL ESTATE

THE same geometric progression of real estate and leasing operations seems now to be taking place in the television field. The primitive facilities which did duty for such a long time at the Alexandra Palace have been superseded by a growing list of fully equipped and sound-proofed TV studios, with specialised stages for plays, talks, music, filmed features and shows with audiences. Including the two

Palace (which are still in use), the BBC now have sixteen permanent TV (or TV film) studios in London, plus two television theatres and numerous rehearsal rooms. Some of these premises have taken months from the date of acquisition to their recommissioning and fitting out for TV purposes. Major structural alterations, refitting, rewiring and replumbing seems to have been the rule before BBC operations could start. Two or three of the stages are still not in operational use. This was not the case, however, with the acquisition of the Ealing Studios premises, which was carried out with lightning rapidity. The last scenes of Ealing's feature film "The Long Arm," starring Jack Hawkins, were shot on Friday, 20th January. There was an auction sale of surplus equipment and furniture on the following Tuesday and Wednesday. The BBC officially took over the premises on the Saturday of the same week and on Monday, 30th January, they actually commenced shooting their own films there. On this day alone—their first day—they shot sixteen camera set-ups for film sequences in "Jesus of Nazareth," the series part-live and part-filmed, which has been so beautifully and reverently treated by the producers and actors. The BBC had wisely purchased a great deal of the Ealing film equipment, including power plant, lighting, camera and sound equipment, stage "props," some of the furnishings and even a large "street" open air set on the lot, which had been used in "The Ladykillers" and "Who Done It?" the Benny Hill film. Needless to say, the speedy transference of the premises was made possible by the close co-operation of BBC and Ealing executives, assisted by their respective technicians. Within a few days theatres were changed over to the 25 frames per second speed necessary in British television work, while Ealing carried on for a time with the final dubbing and editing of their last films made at that studio in their final "beach-head," the sound-recording block. Operation "Walpole Park Studios" had been painlessly carried out and the Ealing Films banner had been hoisted at the M.G.M. British Studios, Elstree. Congratulations all round!




Destined to be known as "The Thing," this mobile hydraulic platform, mounted on a Bedford chassis, can raise a cameraman and camera up to heights of 40ft. or more. It is an Associated Rediffusion requirement. Its main advantage is that it obviates the necessity for erecting scaffolding when a high angle camera position is needed.

'Practical Television Circuits'
288 pages, 156 illus. 15/- net or 15/6 by post from
GEO. NEWNES, LTD.,
Tower House, Southampton Street, Strand, W.O.2.

BAND 3 T/V CONVERTER — 183 Mc/s-196 Mc/s

£2-5-0 post free.

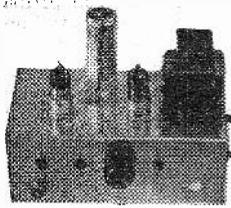Suitable for London, Sutton Coldfield and Northern Transmission.



This Unit, comprising drilled chassis, 7in. x 4in. x 2½in., two miniature valves and met. rect., wound coils, res., cond., etc., is a slightly modified version incorporating variable oscillation tuning of the circuit shown in *Wireless World*, May, 1954. It has proved itself highly successful—over 4,000 sets have already been sold to buyers all over England. We invite you to visit us and see it in operation for yourselves. Suitable for most types of T/V Sets. T.R.F. or Superhet. Blueprint and circuit

details will be sent on application by return of post, 1/6, post free. Supply voltages required 200-250 v., 20 ma H.T. 6.3 v. 1 a. L.T. Power pack components to fit chassis as illustrated, 30/- extra. Complete set wired, tested and aligned ready for use 20/- extra. Band 1, Band 3 Ae switching can now be added, switch kit, 6/6. Full range of Band 3 aerials in stock. Adaptors for 7/6 per set, dipoles—indoor 6/6, outdoor with cable 13/9. Band 1-Band 3 Cross-over filter unit, from 10/6. B.B.C. pattern rejection, 8/6.

B.B.C. BREAK-THROUGH FILTER. Tunable filter unit for B.B.C. pattern rejection, 8/6.


Volume Controls

Midget Ediswan type Long Spindles. Guaranteed 1 year. All values 10,000 ohms to 2 Meg. ohms.
 No Sw. S.P. Sw. D.P. Sw.
 3/- 4/- 4/9
COAX PLUGS ... 1/2
SOCKETS ... 1/-
COUPLER ... 1/3
COUPLER BOXES ... 4/6

80 ohm COAX

STANDARD ½in. diam. Polythene insulated. GRADE "A" ONLY.

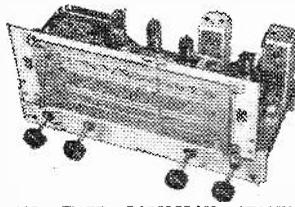8d. yd.
 SPECIAL — Semi-air spaced polythene, 80 ohm Coax ½in. diam. Stranded core. Losses cut 50%
9d. yd.



ALL WAVE RADIOGRAM CHASSIS
THREE WAVEBANDS. FIVE VALVES.
 S.W. 26 m.—50 m. LATEST MIDGET
 M.W. 200 m.—550 m. B.V.A.
 L.W. 800 m.—2,000 m. SERIES.

Brand new and guaranteed. A.C. 200/250 v. 4 pos. W/C sw. 8 Med. L.Gram. P.U. connections. High Q dust core coils. Latest circuit technique, delayed A.N.C. and Neg. feedback. Output approx. 4 watts. Chassis 1½in. x 5½in. x 2½in. Glass Dial—10in. x 4½in. horizontal or vertical type available, lit by 2 Pilot Lamps. 4 knobs supplied, walnut or ivory to choice. Aligned and calibrated ready for use. Chassis isolated from mains. PRICE **£9. 15. 0** Carriage and Insurance, 4/6.
 8in. or 10in. speakers to match available.
 New Available. **DE LUXE 7 VALVE** push-pull version of above chassis, £12.10.0, carr. ins. 5/-.

ELECTROLYTICS ALL TYPE'S NEW STOCK

Tubular Wire Ends	1/8	Can Types, Clipp., 3d. ea.
8+8/450 v. T.C.C.	4/6	8+8/450 v. T.C.C.
50/550 v. 4/500 v.	2/0	8+16/450 v. Hunts
100/25 v.	2/-	16+16+8/550 v. 5/6
S/500 v. Dub.	2/6	16+16/450 v. B.E.C. 6/6
8+8, 500 v. Dub.	4/6	16+16/450 v. Dub. 6/6
8+16 450 v. Hunts	5/6	32/350 v. B.E.C.
16/450 v. B.E.C.	3/6	32+32/450 v. B.E.C. 6/6
16/500 v. Dub.	4/-	60/250 v. B.E.C.
16+16/450 v. T.C.C.	5/6	60+100/550 v.
32/350 v. B.E.C.	4/-	60+250/275 v.
32/500 v. Dub.	5/-	64+120/275 v.
32+32/350 v. B.E.C.	5/6	100+200/275 v. B.E.C.

SENTERCEL RECTIFIERS. E.H.T. TYPE FLYBACK VOLTAGES.—K3/25 2 kv., 4/3; K3/40 3.2 kv., 7/-; K3/45, 3.6 kv., 6/6; K3/50 4 kv., 7/3
 K3/100 8 kv., 12/6; MAINS TYPE.—RM1, 125 v., 6/6 ma., 4/-; RM2, 100 ma., 4/9; RM3, 120 ma., 5/9; RM4 types, 250 v., 2/5 ma., 16/-.

ENGRAVED CONTROL KNOBS for 1in. Spindle, 1½in. diam. Walnut or Ivory. Gold filled, 16 Standard engravings, 1/6 ea. Plain knobs to match above, 1½in. dia. ea., 1½in. dia., 8d. ea. Walnut or Ivory, 1½in., 1/- ea., 1in. 8d. ea. Pointer Knobs Black with White Line 8d.

WEARITE 2 P TYPE COILS. All ranges, 1 to 7, 2in. x 2in. Gsmor Q series Coils. Ring tuned. All ranges from 2/6. Full range popular Coil Packs.

I.F. TRANSFORMERS — 465 k/cs

Brand new ex-manufacturer's midge I.F.T., size 2½ x 1½ x 1½, dust core tuning, Litz wound coils, High Q—Bargain offer, 7/6 pair.

MAINS TRANSFORMERS.—Made in our own Workshops to Top Grade spec. Fully interleaved and impregnated. **RADIO AND AMPLIFIER TYPE.**—250 v. 0 ma. F.V. sec., 5 v. or 1.5 v. 1 a. net, 6.3 v. 2.5 a. sec HTRs. 2½/-, etc. C.R.T. HTR. **ISOLATION TYPE.**—Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1:25, 2 v., 10/6; 4 v. 10/6; 6.3 v., 10/6; 12.5 v., 10/6. Dito with mains primaries 200/250 v., 12/6. Specials to order.

L.F. CHOKES.—10 H. 6.5 ma., 5/-; 15 H. 100 ma., 10/6; 10 H. 120 ma., 10/6; 20 H. 150 ma., 15/6; Simplex, 10/6; Soundmaster, 10/6.
ERSIN MULTICORE SOLDER 60/40. 18g., 3d. per yd.; 16g. 4d. per yd.; 1½/2/6.
LOUDSPEAKERS P.M. 3 OHM. 5in. Celest., 17/6; 6in. Celest., 18/6; 7 x 4in. Goodmans Elliptical, 18/6; 8in. Elec., 20/-; 8in. Goodmans special, 21/6; 10in. R. and A. 25/-; 12in. Plessey, 35/-; Sin. M.E. 2 k. ohm field, tapped O.P. Stens, 24/6.
RECORDING TAPE.—1,200ft. reels, Scotch boy, 30/-; good quality paper tape on standard plastic reels, 12/6.

F.M. TUNER-UNIT (87 mc/s—105 mc/s) by Jason.—As tested and approved by Radio Constructor. Complete Kit of parts to build this modern highly successful unit, drilled chassis and J.B. dial, coils and cans. 4 B.V.A. miniature valves and all components, etc., for only £8.10.0, post free. **SUPERIOR TYPE GLASS DIAL.**—Calibrated in Mc/s and edge lit by 2 pilot lamps, 12/6 extra. Illustrated handbook with full details, 2/- post free.

TWIN FEEDER, 80 ohms, 6d. yd., 300 ohms, 8d. yd. TWIN SCREEN FEEDER, 80 ohms, 1/- yd. 50 OHM COAX CABLE 8d. per yd., ½in. dia.

TRIMMERS, Ceramic, 4 pf.—70 pf., 9d. 100 pf. 150 pf., 1/3; 250 pf., 1/6; 600 pf., 1/3. PHILIPS Resistor Type—2 to 5 pf. or 10 to 30 pf., 1/3 each. 50 RESISTORS.—Tret. values 10 ohms 30 megohms.

WIRE WOUND
 20% Type, 1 w., 3d.; 1 w., 5d.; 1 w., 6d.; 2 w., 9d.
 10% Type, 1 w., 9d.; 1 w., 1/0; 1 w., 1/1; 1 w., 1/2.

WIRE-WOUND P.O.S. Free-Set Min. T.V. Type. Knurled Slotted Knob. All values 25 ohms to 30 K., 3/- ea. 50 K., 4/-; Ditto Carbon Track 50 K. to 2 Meg., 3/-.

CONDENSERS.—Mica or S. Mica. All pref. values, 3 pf. to 650 pf., 6d. each. Ceramic types, 2.2-5, 600 pf. as available, 8d. each. **Tubular, 450 v. Hunts and T.C.C., .0005, .001, .005, .01, .02 and 1.550 v., .01, .05, 1.550 v. Hunts Moidesal, 1/-, .25 Hunts, 1/3, .1 1.550 v. T.C.C. (Stimples), 3/6, .001, 6kV., T.C.C., 3/6, .001 12.5kV., T.C.C. 9/6.**

SILVER MICA CONDENSERS.—10%. 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3, 1.5 pf. to 500 pf., 1/9. 515 pf. to 5,000 pf., 2/-.

ALUMINIUM CHASSIS.—18 s.w.g. Plain, undrilled, folded 4 sides and riveted corners lattice fixing holes. Strong and soundly constructed with 2½in. sides. 7in. x 4in., 4/6; 9in. x 6in., 5/9; 11in. x 7in., 6/9; 13in. x 8in., 8/6; 14in. x 11in., 10/-; and 18in. x 18in. x 3in., 18/6.

CARBON MIKE INSERT.—Superior quality types 2½in. x 1in. Brand new and boxed only, 3/3 each.

BRIMSTONS.—CZ1 for 3A heater chains, 3/6. CZ2 for 15 a., or 2 a., 2/6. CZ3 (Pilot Lamp), 1/5.

COPPER ENAMEL WIRE.—1 lb. 14 to 29 s.w.g., 2/-; 22 to 28 s.w.g., 2/6; 30 to 40 s.w.g., 3/3.

SWITCH CLEANER Fluid, squirt spout, 3/9 1in.

TWIN GANG TUNING CONDENSERS.—375 pf. Midge, 6/6; ditto, with dust cover and trimmers, 8/6, .0005 mid. Standard size with feet, 8/8.

QUALITY FLUORESCENT FITTINGS

Ideal for home or workshop. 4 ft., 20-250 v., complete with tube, ballast unit, etc., ready for use. Famous manufacturer's surplus offered at approx. half price. Starter switch type, 42/-. Quick start type, 47/6. Carr. and ins. 7/6 extra.

NEW VALVES GUARANTEED ALL BOXED

1R5	7/6	6Q7	8/6	6CH81	12/6	6EY51	12/6
1R5	7/6	6SN7	9/-	6ECL80	12/6	6E40	10/-
1F4	7/6	6V6	7/6	6E39	7/6	6MU11	8/6
194	7/6	6X4	8/6	6E741	10/6	6PC84	12/6
384	8/-	6X5	8/-	6E739	10/6	6CF80	12/6
5V4	8/-	6A50	2/-	6SY6	10/6	6PF82	12/6
306	3/6	6ABC80	12/6	6E750	10/6	6PL81	12/6
524	8/6	6B81	7/6	6E619	5/6	6PL82	10/-
6AM6	8/6	6BC63	8/6	6E780	10/6	6PL83	12/6
6AT6	8/6	6BC44	10/4	6E786	12/6	6PY80	11/6
6C16	10/6	6BF80	12/6	6E791	8/6	6PY81	12/6
6H6M	5/6	6ECC83	12/6	6E141	11/6	6PY81	12/6
6K7	8/6	6ECH35	12/6	6E134	12/6	6PY82	10/6
6K8	9/-	6E142	10/6	6E850	12/6	6SP41	6/6

SPECIAL PRICE PER SET
 1R5, 1F4, 1R5 and 584 or 5V4 27/6
 6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5 35/-
SPEAKER FRET. Expanded Bronze anodised metal 8in. x 8in., 2/3; 12in. x 8in., 3/-; 12in. x 12in., 4/3; 12in. x 16in., 6/4; 24in. x 12in., 8/6, etc. **TIGAN FRET** (Murphy pattern).—12in. x 12in., 2/-; 12in. x 18in., 3/-; 12in. x 24in., 4/-; etc., etc.

3 VALVE AMPLIFIER
 With variable Tone and Volume controls, 3 Midget P.V.A. valves, 4 watts output. Neg. feedback. Chassis isolated from Mains. A.C. 200/250 v. A quality amplifier at an economical price of £3.19.8. Carr. 2/6. Wired and tested, 15/- extra. Circuit and instr., 1/6, free with kit.

TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)



50 yards Thornton Heath Station. Buses: 130A, 133, 159, 165 & 190
 Listed above are only a few items; from our very large stock. Send 3d. stamp today for Complete Bargain List.
 Hours: 9 a.m.—6 p.m., 1 p.m. Wed. OPEN ALL DAY SAT.

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc. payable to T.R.S. Post/Packing up to ½lb. 7.11, 11s. 1/11, 35s. 1/6, 35s. 2/-, 10lb. 2/9

HANNEY of BATH offers:—

MULLARD 3-VALVE 3-WATT AMPLIFIER
Gison Output trans., 25/6; Mains trans., 35/-; Resistor pot kit, 25/-; Condenser, 20/-. Send for full list.

WIRELESS WORLD F.M. TUNER (May 1955)
Osmor coilset with IF's and RDT, 58/6; J.B. type U.102 variable, 14/6; ERIE condenser and resistor kits, low-loss valveholders and valves. Full list available.

MULLARD F.M. TUNER UNIT
Denco drilled chassis, 16/6; coilset with IF's etc., complete, 46/-; J.B. U.101 variable, 10/9; J.B. SL.15 dial drive assembly, 25/6; condenser and resistor kits, valves, etc. Full list available.

OSRAM 912 F.M. TUNER UNIT
Denco chassis with dial assembly, 37/6; Denco coilset IF's and RDT, 44/9; 2 gang variable, 17/6. Condenser and resistor kits, valves, etc. Full list available.

MAXI-Q DENCO F.M. TUNER UNIT
Chassis set, 7/6; Coilset, 11/9; 10.7 Mc/s IF's, 6/- each; Ratio discrimin. trans., 12/6; Phase discrimin. trans., 9/-; Technical Bulletin giving circuit, point-to-point wiring, etc., 1/9 P.F.

COILPACKS, DENCO CP 4 L and CP 4/M, 35/-; CP 3/370 pf. and CP 3/500 pf., 44/9; OSMOR "Q" HO, 50/5; LM, 40/-; Batt., 50/-; TRF, 40/-; HF stage for HO pack, 20/-. We stock COILS by Weymouth, Osmor, Wearite, Denco and R.E.P.

OSRAM 912 PLUS AMPLIFIER
Erie resistor kit, 17/4; Erie 1 meg. pots, 4/6 each; TCC condenser kit, 55/-; PARTRIDGE components with loose lead terminations (includes packing charge), Mains trans., 65/6; choke, 34/6; output trans., 35/6; W.B. components, Choke, 18/9; output trans., 32/-; Denco drilled chassis, 14/6; Denco 912 Plus printed panel, 7/6; pre-amp or passive chassis, 6/-; Full list available.

MULLARD 510 AMPLIFIER
ERIE resistor kits, 27/-; TCC condensers, 45/-; Elstone mains trans., 36/-; Elstone output trans. (state 6,000 or 8,000 ohms), 45/-; Partridge components (loose leads), Mains trans., 65/6; output trans. type PPO (state 8,000 or 8,000 ohms), 85/6; smaller version type P.867, 55/6; Denco drilled chassis, 19/6; Denco printed panel, 6/6. Full list available.

DENCO WIDE ANGLE COMPONENTS. Magnaview chassis set, 37/6; Supervisor chassis, 51/6; Magnaview coilset, 41/2; scan coils WA/DCAL, 43/-; focus coil WA/FOAL, 31/-; width and line/lin. controls WA/WCL and WA/LCL, 7/6 each; frame trans. WA/FMAL 21/-; line trans. WA/LOT1, 42/-; frame blocking osc. trans. WA/FBTL, 16/-; Send stamp for lists. Please add postage 2/- to all orders under £3. (Excess refunded).

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

VIEW MASTER CONVERTER

All items for the View Master Converter as described in "Practical Television" can be supplied from stock. Full details are given in our special list which is available free upon request.

COIL SET AND METAL PARTS. Denco. Includes a ready wound set of coils, switch screens and metal cover. 30/-.

SWITCH ASSEMBLY. Denco. Complete switch with fine tuner and coil platforms. 27/-.

CONDENSER AND PRINTED CIRCUIT KIT. TCC. Contains all the condensers, printed circuit and valve holders. 43/-.

RESISTOR KIT. We make up this kit with the specified LAB resistors. All labelled with value and position. 8/-.

GAIN CONTROLS. Colvern CLR901 5,000 ohms. Three required. 3/3 each. Panel for mounting three controls, 1/-.

VALVE SCREENS. Carr Fastner. Skirt and screen. Two required. 1/3 each.

CO-AXIAL PLUG AND SOCKET. Belling Lee. L604S Socket. 1/3. L734P Plug. 1/3.

SOLDER. Ersin Multicore. Special for printed circuits. 2/6.

VALVES. Mullard PCC84 24/4. Surplus 13/6. Mullard PCF80 25/9. Surplus 13/6.

KNOB. Pointed knob for switch. 1/-.

SUNDRIES KIT. Contains all nuts and bolts, flex, wire co-axial cable, copper foil and spring wire. 8/-.

COMPLETE KITS. All above items supplied at one time.

KIT A. With new Mullard valves. £9.4.0. Credit Terms: Deposit £1.6.9 and seven monthly payments of £1.6.9.

KIT B. With surplus valves. £8.2.0. Credit Terms: Deposit £1.4.0 and seven monthly payments of £1.4.0.

PLEASE NOTE. These kits do not include the items needed for conversion of the View Master Sound/Vision Chassis. We can supply the chassis conversion kit for £2.0.0. Full details in our list.

SET OF TWIST DRILLS. Complete set of the correct size twist drill for drilling the Printed Circuit Panel. 10/-.

WATTS RADIO

8 Apple Market, Kingston-on-Thames, Surrey.
Telephone: KINGSTON 4099.

NEW!

EXPERIMENTAL KITS in Radio, T.V. etc.

LEARN THE PRACTICAL WAY

Specialy prepared sets of television parts (which you receive upon enrolment) with which we teach you, in your own home, the working of circuits and bring you easily to the point when you can construct and service a television set. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — this Practical Course is intended for YOU — and may be yours at very moderate cost.

EASY TERMS FROM 15/- A MONTH

A tutor is available to give individual help and guidance throughout the Course.

POST THIS COUPON TODAY

Please send me your FREE book on Practical Courses:
To: E.M.I. INSTITUTES, Dept. 138X, Grove Park
Road, London, W.4.

NAME

ADDRESS

SUBJECT(S) JUNE



EXPERIMENTAL OUTFITS:

TELEVISION — Instruction and equipment for building a Television Receiver.

BEGINNER'S RADIO OUTFITS — A course in basic principles.

ADVANCED RADIO OUTFITS — Instruction and equipment from which you build a Radio Receiver.

Also for Mechanics, Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S. W. Radio, Languages.

E.M.I. INSTITUTES

The only Postal College which is part of a world-wide Industrial Organisation.

A TEN-ELEMENT BEAM

A LIGHTWEIGHT AERIAL FOR THE NEW TRANSMISSIONS ON BAND III


By E. H. Trowell, G2HKU

HAVING built a Band III Channel 9 converter and discovered that aerials suitable for this Band were in short supply and unobtainable locally, the writer decided to make a temporary lightweight beam for erection in the loft. The results obtained 50 miles from London with this aerial have proved extremely satisfactory over the past month, so much so that the idea of buying a ready-made aerial has been dropped. In case it is thought that the writer's house has a good location, it may prove of interest to state that it is located 6ft. below sea-level—the aerial being 22ft. above sea-level.

All elements are made from 12-gauge copper wire and the general layout may be seen in Fig. 1. A bamboo cane, as straight as possible, is drilled to take the elements, each of which is secured and joined to its neighbour as in Fig. 2.

Connecting the Feeder

The folded dipole aerial is not, of course, joined to any of the directors or the single reflector. The directors C to J should be mounted and wired together, as in Fig. 2, and then the folded dipole constructed and mounted on its Perspex or Polythene block, shown in Fig. 3. The feeder connections are provided by bending the ends of the dipole at right-angles and passing them through the Perspex block; the feeder then being soldered to the protruding

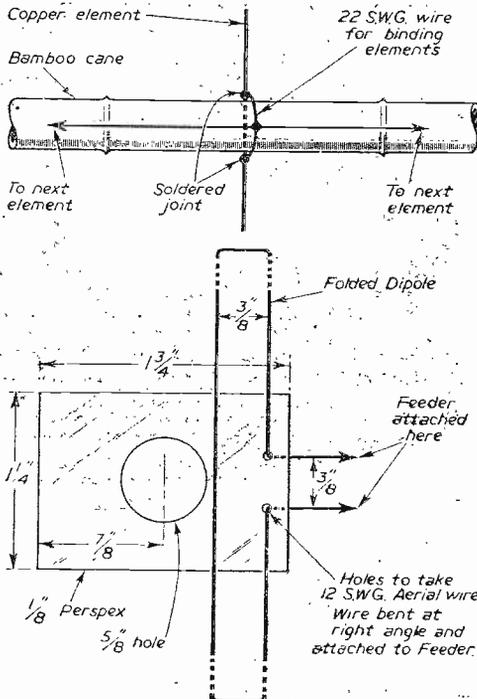

Figs. 2 and 3.—Method of connecting up the elements, and the folded dipole mounting block.

ends. The block should then be pushed over the bamboo cane and set in position with Perspex cement 6in. from director C, as shown in Fig. 1.

Reflector A should then be mounted and con-

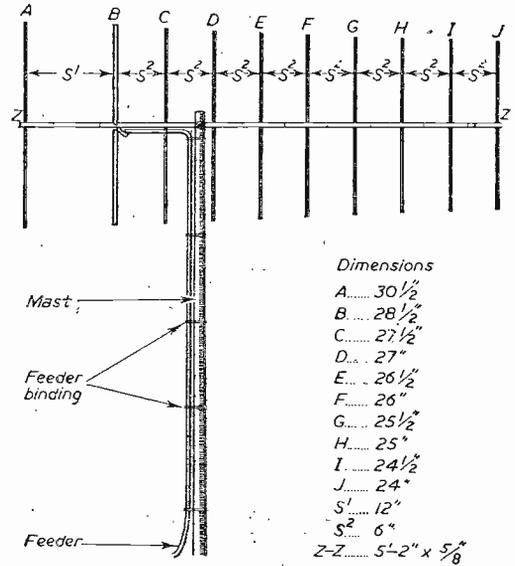


Fig. 1.—Details of the 10-element beam aerial described here.

ected by the common wire, as shown in Fig. 2, to the directors.

Mounting

The method of mounting on a mast is left to the individual constructor, since force of circumstances, such as loft space and proximity of any electrical wiring or water storage tanks, will be the deciding factors. The Beam could, of course, be suspended from the roof supports or, as in the writer's case, attached to a paxolin tube which was lashed to a rafter. Due to its extreme lightness no special precautions are required in mounting, and since it is not exposed to the weather there is no fear of damage, either to the aerial or property.

The high gain of this aerial gives an acceptance angle of only a few degrees at short distances. In other words, at a long range it will be necessary to position the aerial with accuracy, preferably whilst the television receiver is receiving a signal. An inch either way will make a good deal of difference to the picture at extreme range.

NEWNES SHORT-WAVE MANUAL
7th Edition
6/-, or 6/6 by post from
GEORGE NEWNES, LTD : : Tower House, Southampton Street, London, W.C.2.

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

TUBE "SALVAGE"

SIR,—L. Lawry-Johns, in your January edition under "Servicing Television Receivers," states that tubes such as the MW31/16, MW31/74, etc., having grid to cathode shorts, would have to be scrapped and new tubes bought to replace them. This is not quite true, as these tubes can be given a fresh lease of life by connecting them as triodes. The first thing to do is to join the grid and cathode together at the base, then remove the first anode connection. Disconnect the grid connection and reconnect to the first anode. (These connections are for negative drive; for grid drive reverse the order.) The first anode lead is then taped back and put out of the way. Under this system I have, as a service engineer, cleared many a tube trouble and saved customers the price of a new tube.—S. W. INGRAM (Ilford).

THE CINEMA AND TELEVISION

SIR,—As a regular reader of PRACTICAL TELEVISION herewith some observations for what they may be worth.

In view of the opposing interests which exist between the cinema and television perhaps it would be possible for cinemas to be wired up to houses on the slot meter principle; this might well be compared to the public call box and the private telephone. All advertising could then be confined to its rightful place in the cinema, and the BBC operating their own and the present ITV on the basis of a "Home" and "Light" programme which appears to be becoming badly needed.

The above could possibly lead to the present cinema being used half for those who do not wish to stay at home for their "recreational entertainment" and half for "educational entertainment," the latter being really what the "below average" youth may be looking for, but for want of it is finding an outlet in the "Teddy" approach.—J. I. SOMERS (Portsmouth).

TEST CARD C

SIR,—I would like to draw your attention to the test card on TV. Like thousands of amateurs interested in TV I will have to give up this interesting hobby because of the time of the test card, 10 a.m. to 1 p.m.; us chaps who are away working all day cannot test out our home-made sets when we come home in the evening because we are interfering with other people's viewing. Is it not possible to have a test card, say, after the day's viewing, from about 11 p.m. to 1 a.m. to give us amateurs a chance. If there is nothing done I am afraid thousands of amateurs will have to give up this hobby.—ALEX BARTON (Glasgow, C.5).

COLOUR EFFECT

SIR,—G. F. Remmett asks, in your December issue, for an explanation of the multicolour effects seen on his VCR97 tube. If Mr. Remmett reads a book entitled "The Living Brain," by Dr. Grey Walter, he may well find his question answered in the chapter dealing with the effects of flickering light on the human brain.

Mr. Remmett noticed in a particular television programme that the images of revolving planets

appeared in various colours. This is exactly what one might expect given the right circumstances, and for the following reasons:

The brain itself produces complex electrical waveforms which under harmonic analysis are found to consist mainly of basic frequencies varying from 1 to 36 cycles per second. Flickering light is sometimes used experimentally to stimulate by resonance individual brain frequencies, the flicker being a bright electronic flash of variable repetition rate. At certain frequencies of flicker which differ from one person to another, the most brilliant colours and changing patterns are seen. These are not due to the light itself, but are evoked solely by the flicker frequency.

These conditions would be closely simulated by your correspondent's viewing conditions for that particular programme where the only light would be the spot images of the planets recurring at the television frame frequency. If this frequency happens to coincide with Mr. Remmett's own critical frequency for the colour-from-flicker effect, he would most certainly expect to see coloration effects.

An interesting point is that brain frequencies of the order of 10 to 14 per second are definitely related to human vision since they disappear when the eyes are opened and return strongly when the eyes are closed. It is possible that these brain waveforms are part of a scanning system by which human vision is accomplished.—A. W. ELPHICK (Bath).

"VIEW MASTER" IMPROVEMENTS

SIR,—With reference to your contributor's article on "View Master" improvements in the May issue, I too have quarrelled with C55. It is not, however, necessary to use such a large component, as a resistor can be inserted between the negative side of resistor R70 (C53, transformer, etc., junction) and C55 negative. Values of 10 k. for the resistor and 4 μ F for C55 are suitable, although any values giving a similar minimum time constant can be used. I wrote to "View Master" on this point in May, 1952, and they agreed with this measure, but stated that on their prototypes some variation in brilliance was noted on first switching on, "hence the present arrangement was adopted." Nevertheless I have never noticed any adverse effect.

The one major change I have incorporated in my receiver—or at least the one with the major effect—concerns the coupling between L107 and L108. Some two years ago when re-lining, I noted that slight pressure with the time-honoured filed knitting needle resulted in marked variations in brilliance. This proved to be due, not to stray capacity but to the mechanical position of the coils which must be critical. Instead of moving the coils I added a turn to the coupling winding on L107 former and the result was an increase in gain, greater in fact than that obtained by adding the pre-amplifier. Consequently it was possible to align the tuned circuits for maximum quality—with no consideration for gain—and connect V5 cathode to earth via a non by-passed resistor of 68 ohms. The latter may help picture quality; it reduces the loading on the detector and assists the expectation of life of V5 which was previously about a year.—E. C. DYSON (Beeston).

HENRY'S

(RADIO LTD.)

CATHODE RAY TUBES

(Brand New)
 VCR97 (slight cut-off) 15/-
 VCR97 guaranteed full T.V. Picture ... 40/-
 VCR517C, guaranteed full T.V. Picture ... 35/-
 VCR139A, guaranteed T.V. Picture ... 35/-
 VCR139A (with Screen) ... 35/-
 3EP1, guaranteed full T.V. Picture ... 30/-
 Carr. & Packing on all tubes, 2/-.

"38" WALKIE-TALKIE SETS

Special offer of above set, complete with 5 valves, 4 AR12 and 10P4, with circuit. Range 7.4 to 9 mc s. These sets are not guaranteed but are serviceable. 25/-
 Junction box 2/6 extra.

PYE 45 MC/S STRIP TYPE 3583 UNITS

Complete with 45 Mc s Pye Strip. 12 valves, 10 EF50, EB34 and EA50, volume controls, and hosts of resistors and condensers. New conditions of satisfaction data supplied. Price 69/6, carriage paid.

62A INDICATOR UNIT

Containing VCR97 with Mu-metal screen. 21 valves: 10 EF50, 4 SF61, 3 EA50, 2 EB34, 10P4, 10P5, switches, H.V. cond., resistors, MuHred 5 M dial, double deck chassis and crystal. BRAND NEW ORIGINAL CASES, 67/6, carriage 7/6.

INDICATOR UNIT TYPE 182A

Unit contains VCR517 Cathode Ray 6in. tube, complete with Mu-metal screen, 3 EF50, 4 SF61 and 1 5U4G valves, 9 wire-wound volume controls and quantity of resistors and condensers. Offered BRAND NEW (less relay) at 67/6 plus 7/6 carr. Radio Constructor scope circuit included.

VR91A The Selected EF50. Brand New Red Sylvania original cartons. 10/- each, 90/- for ten.

U.S.A. INDICATOR UNIT TYPE BC929A

In black cracked G cabinet 14in. x 9in. x 9in. Complete with 3BP1 C.R. Tube, shield and holder, 2 6SN7GT, 2 6H6GT, 1 6X5GT, 1 2X2, 1 6G6, Vcontrols, condensers, etc. Ideal for scope. Brand new, 65/-, carriage paid.

MINIATURE I.F. STRIP TYPE "373" 9-72 MEG.

Brand new miniature I.F. Strip size 10in. x 2 1/2in. x 3in. high. Valve line-up: 2 EF92, 3 EF91 and EB91. With Circuit. Pae (less valves), 7/6. P.P. 1/6.

We have over 50,000 American and B.V.A. valves in Stock. LATEST TYPES NOW IN STOCK

EBC41 10/-	UBC41 10/-	PL52 10/-	12AT7 9/-	EF85 10/6	DL96 10/-
EV51 11/-	DK40 10/-	PY81 10/-	12AU6 9/-	EF89 10/-	DAF96
EF41 11/-	EF90 10/6	EM90 10/-	12BA6 9/-	ECF82 15/-	DF96 10/-
EZ40 10/-	EABC80	6X4 8/-	12BE6 10/-	PABC80	ECC84 15/-
EM34 10/-	ECC85 10/-	PCCF82	12AH8 12/6	15/-	6A45 10/-
UL41 11/-	EF80 10/-	PCF82	35W4 8/6	6AU6 9/6	PCL82
UF41 11/-	ECL80	12/6	PCF80 15/-	117Z3 8/6	12/6
UCH42	12/6	12AU7 9/-	EBF80	12AX7 10/-	ECH42
	12/6	PL31 12/6	12AT6 8/-	11/6	DK96 10/-

LP2 3/6	VP2 8/6	FW4/500	TDD2A 8/6	U10	8 625PT 6/-
210LF 3/6	SF2 8/6	10/-	FC13C 10/-	DDL4 5/-	254V 5/-
P2 4/-	VP2B 8/6	FC13S/C	MS/PEN	PENDD	ML4 7/6
215SG 4/-	TP22 8/-	10/-	7/6	4020 12/6	MU14 8/6

SPECIAL REDUCTION FOR SETS OF VALVES

1A7GT, 1N5GT, 1H5GT, 1A5GT (or 1Q5GT or 3Q5GT) ... 40/-Set
 10 EF50 (Ex-Brand New Units), 5/- each ... 45/-
 10 EF50 (Red Sylvania ex-new units), 5/- each ... 45/-
 6K9G, 6K7G, 6Q7G, 5Z4G, 6V6G ... 37/6 ... 27/6
 1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4) ... 27/6

SEND 3d. for 28-PAGE ILLUSTRATED CATALOGUE

CRYSTAL MICROPHONE INSERTS



Ideal for tape recording and amplifiers. No matching transformer required.

QUARTZ CRYSTALS

Type PT243 Fundamental Frequencies, 2-pin pin. Spacing, 120 Types: 5675 Kc/s to 8650 Kc/s (Channel 270,369). (In steps of 25 Kc/s). 40 Types: 5706.667 Kc/s to 8340 Kc/s. (Channel 079). (In steps of 33.333 Kc/s.).

BRAND NEW AND GUARANTEED, 10- each Complete sets of 80 and 120 Crystals available.

Type FT241A '54th Harmonic

21-Pin pin. Spacing
 21.1 Mc s. 23.2 Mc s.
 21.2 Mc s. 23.4 Mc s.
 21.4 Mc s. 24.4 Mc s.
 21.5 Mc s. 26.0 Mc s.
 22.0 Mc s. 28.1 Mc s.
 22.8 Mc s. 29.4 Mc s.
 22.9 Mc s. 27.0 Mc s.

BRAND NEW AND GUARANTEED, 7/6 each.


Complete Sets of 80 Crystals Channel 079 available.
 200 Kc/s. 10- each. CRYSTAL HOLDERS, 1/3 each 10/- Discount on all orders of 25/-.

5, HARROW ROAD, PADDINGTON, LONDON, W.2 TEL.: PADDINGTON 1098-9, 0401

RADIO CHASSIS

39/6

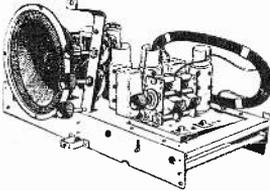3 w/band & gram. Extra speaker sockets, 5 valves international aet. Built-in portable aerial. Optional 4 knob control. A.C. or universal. Less valves (see our cheap list). 8" P.M. speaker 7/9 with order. Set of knobs 2/-. Chassis 15 1/2 x 7 x 9" (when speaker is fitted). Carr. 4/6.



12" T.V. CHASSIS 97/6

Easily adapted to Band 3 (ITV). Drawing 2/6 or FREE with order. Complete chassis by famous manfr. R.F. E.H.T. unit included. Owing to this chassis being in 3 separate units (power, t-base and vision inter-connected), it is easily fitted to table or console model. State BBC channel. This chassis is less valves and tube. Ins. and carr. London 5/-. Provinces, 10/-

RADIOGRAM CHASSIS, 29/9. Including 8" speaker, dial and knobs. 5 valve s het. 3 w/band. A.C. mains. Complete. Guar. tested. Less valves. Ins. and carr. 4/6.

POWER TRANSFORMERS, 15/9. 325-0-325 v. mains. 6 v. at 5 A., 4 v. at 5 A., 4 v. at 5 A. Extra isolated windings for 2 or 4 v. tubular. Also similar trans. with 6 v. at 5 A., 6 v. at 5 A., 22 v. at 11 A. Both are 250 mA. Plus post 2/-.

MAINS TRANSFORMERS, 5/9. Heaters 6 v. and 5 v., 350-0-350 v., primary 200-250 v. Post 2/-.

MAINS TRANSFORMERS, 3/9. 350-0-350 v. heaters 12 and 4 v. primary 100-250 v. Ideal auto-trans. Post 2/-.

MAINS TRANSFORMERS, 5/9. 350-0-350 v. heaters 4 and 4 v. primary 200-250 v. Post 2/-.

MAINS POWER PACK UNIT, 28/9. 5 kv. E.H.T. 325 v. 250 mA. Smoothed h.t. heaters, 6 v. at 5 A., 4 v. at 5 A., 4 v. at 5 A. and 4v centre tapped. Carr. 4/6.

MONEY BACK GUARANTEE

Tele: GRA 6677
DUKE & Co

CWO
 COD

621 RIMFORD RD. LONDON, E.12.

TECHNICAL TRADING CO.

SPECIAL GUARANTEED SNIPS

WIDE ANGLE TRANSFORMER KITS.

- Original wrappings consisting of:
- (a) Line Output Transformer 14 Kv. ceramic base, EY51 mountings, ferroxiide core, 17/8 with instructions, post 1/-.
 - (b) Frame Output Transformer, large efficient type giving ample output from ECL80, 9/6, post 1/3.
 - (c) 250 ma 5 H standard Smoothing chokes, 3-way mounting, 7/8, post 1/3.

COMPLETE KIT AS ABOVE.—Shnp price for 3 items, 30/-, post 2/6.

ION TRAP MAGNETS.—Best quality with brass outer rings, 3/6, post 4d. 1in. Aladdin Formers with Slug, 4/- doz.

DEFLECTION COILS.—Standard low impedance 35 mm., iron cored, 9/6. Width Coils, 4/-. Linearity Coils, 4/-. 6in. and 8in. SPEAKERS.—Best makes, slightly soiled, guaranteed perfect, 10/-, post 1/6.

TV TABLE CABINETS.—14in., 19", 17in., 22 1/2. Ditto, with Mask and Glass, 14in., 29/-; 17in., 39/-; All 7/6 Carr.

CYLDON 13 Ch. Tuners with Valves. Boxed, 24.

RES (CR100) CONVERTERS, £12-10. Cossor D.B. Scopes, £17-10

AVO Valve Testers, 28.

WIREWOUND PRESET POTS. 500Ω 2.5K, 10K, 2.6 ea.

AMPHENOL V.H.S.—Octal, Noval, B7G, B9G, 7/- doz.; B9G W/Screen, 1/6 ea.

12 volt 10/20 w. AMPLIFIERS.—Inbuilt motor gen., compact, ideal outdoor work, push pull 6L6, and 2 douck triodes, cost approx. £30, good cond. untested, £5.10, carr. 10/-.

1 MEG. POTS D.P. SWITCH.—1in. spindle, small type, only 3/6, post 4d. .001 18 kv. Visconal, 4/9, post 9d.

MIDGET CERAMIC CONDENSERS, 10, 20, 50, 300, 1,000, 3,000 pF, 6/- doz.; 18+16 350v., 3/-; 8" 250 v., 1/-; 100 x 6 v., 1/-; 80+100 350 v., 6/-.

THROAT MICS. British, boxed with jack plug, 3/6, post 6d. Single L.R. earphones with headband, 3/6.

RADIO VALVES GUARANTEED PERFECT

6AK5	6.6/6F33	8.6/12AX7	8/-EF92	4/6SP61	3/6
6AG5	5.6/6J66	6/6813	50/-EL91	5/6SP219	3/6
6AL5	5.6-6J7G	4/6	EB34	2/-E235	8/-U22
6C4	6.6/6J5G	4/6	EB34	2/-E235	8/6
6P6G	6.6/6K7G	6/-	ECC31	8/-PY31	8/-UR150 30 6/-

1,000 OTHER BARGAINS TO CALLERS AT

PORTSMOUTH'S RADIO, TV AND TOOL SHOP
 350/352, FRATTON ROAD, PORTSMOUTH

TALLON CABINETS

for RADIOGRAM, TELEVISION and RADIO

- Radiograms.** Contemporary light oak.
Walnut Standard.
Walnut Bureau.
- Television.** Teleking suitable 12", 15", 16", 17". Console with or without doors. Viewmaster 12" or 17", Table or Console.
Lynx 15".
Argus.
- Tape Recorder.** Super Cabinets for Soundmaster.
- Radio.** Portable. } 15/-
Mini-Four. }
Crystal Diode. }

JAMES TALLON & SONS LTD.
MANOR WORKS, MANOR ROAD
RUGBY Telephone : 2070 Rugby

direct TV REPLACEMENTS

The largest stock of T.V. Components in Great Britain—all from one source

All Time-base components, Rectifiers, Controls for Home Constructors and Set Manufacturers. Universal Frame Output Transformer with 9 different ratios from 80:1 to 8:1. 30/- plus 2/- p.p.

SAME DAY DESPATCH

"NURAY" Mk II

Regd. Trade Mark

A HEATER-BOOSTER & ISOLATOR UNIT

—that just plugs in!

- ★ Gives low emission C.R.T. a new ray.
- ★ Remedy for tubes with cathode heater short.



For 4 and 2 volt Tubes.
27.6 p.p. 2/-

direct TV REPLACEMENTS

Terms of business—C.W.O., C.O.D. or Pro forma.

134/136 LEWISHAM WAY, NEW CROSS, S.E.14.
Tel.: TIDewey 3696/2330. Grams : Flibak, London, S.E.14.

TELETRON COILSETS FOR VIEWMASTER CONVERSION

(P.T., Dec., '55-Jan. '56)

Bands I and III. Coilsets as specified.

—Comprising—

Tuner kit, metal screens and cover, and I.F. coil kit. Coded coil formers for easy reference.

London version for Channels 1, 2 and 9. Midlands version for Channels 3, 4, 5 and 8.

Complete Tuner and I.F. Coilsets, 49/6.

THE TELETRON CO., LTD.,
266, Nightingale Road,
London, N.9
HOW 2527.

FIRST-CLASS TELEVISION and RADIO COURSES

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M.Bric.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc.,** together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

VALVES SAME DAY SERVICE

All Guaranteed New and Boxed

14v. midget.	1R5	1S5	1U5	1T4	3S4	DAF91		
	DF91	DK91	DL92	DL94				
1A7GT	11.6	6Q7GT	9.6	DH77	8.6	GZ32	15.6	
	12.6	6SN7GT		DK32	12.6	HVR2A	7.6	
1C5GT	11.6		8.6	DK32	7.6	KT33C		
1D5	11.6	6U1GT	11.5	DL33	11.6		10.6	
1H5GT		6V6G	7.6	DL35	11.6	KT63	7.6	
	11.6	6V6GT	7.6	EABC809		MU14	9.6	
1N5GT		6X4	7.6	EB91	6.9	PE1	5.6	
	11.6	6X5GT	6.9	EBC33	7.6	PCC84	10.6	
1R5	8.6	7B7	8.6	EB41	10.6			
1S5	7.3	7C5	8.6	EBP8010	6.6	PCF80	9.6	
1T4	7.3	7Cs	8.6	ECC40		PCF82		
1U5	7.3	7H7	7.6		15.6		11.6	
3A5	9.6	7S7	9.6	ECC81	10.6	PEN4516		
3Q5GT	11.6	7T4	8.6	ECC8310	6.6	PEN46	7.6	
3S4	7.6	10C1	13.6	ECC81	6.6	PL38	23.9	
3V4	8.6	10C2	10.6	ECP80	15.6	PL81	11.9	
5U4C	8.6	10F1	10.6	ECH35		PL82	9.6	
5Y3GT	7.9	10LD11			11.9	PL83	12.6	
5Z4G	9.6	12A7	10.6	ECH42		PY80	10.6	
6AT5	6.9	12A7	9.6		10.6	PY81	10.6	
6AL5	6.9	12A7	8.6	ECH81	9.6	PY82	9.6	
6AM5	5.6	12J7GT		ECL60	10.6	PZ30	18.6	
6AM6	7.6		10.6	EF97A		U22	10.6	
6AQ5	7.6	12K7GT	9.6	EP90	10.6	U25	18.6	
6AT5	8.6	12K8GT		EP90	6.6	U26	15.6	
6BA6	7.9		12.6	EP91	17.6	U60	7.9	
6BE6	7.6	12Q7GT		EP41	10.6	U78	7.6	
6BW6	7.9		9.6	EP42	14.6	U404	9.6	
6BN6	7.6	12Z3	7.6	DF50	7.6	UAF42		
6C9	10.6	14S7	15.6	EF80	10.6		11.9	
6F1	13.6	20L1	10.9	EP83	11.6	UBCA1	9.6	
6F6G	7.6	25L6GT	6.6	EP86	13.6	UCH42		
6F15	13.6	25Z4G	9.6	EP91	7.6		10.9	
6J6	6.6	35L9GT	9.6	EP92	5.6	UF41	9.6	
6J7GT	7.6	35Z4GT	6.6	EL32	6.6	UL41	10.9	
6K7C	6.6	35Z6GT	9.6	EL33	23.9	UU7	11.6	
6K7GT	6.6	50L6GT	9.6	EL41	11.6	UY41	9.6	
6K8G	8.6	D15	7.6	EL84	11.6	W77	5.6	
6K8GT	9.6	DAC3211	6.6	EY51	12.6	X79	12.6	
6L8	10.6	DCC90	9.6	EZ40	8.6	Y63	7.6	
6LD20	9.6	DF33	11.6	EZ80	9.6	Z77	7.6	

Postage 3d. per valve extra.
READERS RADIO
24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4537



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p. 527 must be attached to all queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

K.B. EV30B

The height control will not control the picture, which closes up from the bottom. On operation of this control, the picture then extends to the top and bottom, which tops and tails the characters on the screen. Can you tell me what the cause can be?—V. Moore (Bristol, 3).

If the frame linearity control does not correct this fault (this should be adjusted in conjunction with the height control), then a fault should be suspected in either the 6SN7GT oscillator valve or the 6V6G frame amplifier valve. If these valves prove to be up to standard, however, check the components related to the linearity control and, if possible, substitute the frame blocking oscillator transformer with one of known goodness.

MURPHY V.150

I would be glad if you could help me with Band III conversion.

I wish to build the "Practical Television" Converter and would be glad if you can tell me if the U.801 rectifier on this set will stand the extra load, if I connect H.T. as Fig. 25, page 264, November issue.

Also, since this model uses A.C./D.C. technique, in that a heater chain is used, I wish to use a separate heater transformer, with a separate mains switch to same, to conserve current to the convertor when it is not in use.—L. Wilton (Tamworth).

Your set is working fairly heavy under normal conditions and we would not advocate that you feed a Band III converter from its power section. Your best plan would be to build a small power unit, using an RM3 metal rectifier and small mains transformer with a separate 6.3 volt heater winding; in this way you will also be able to energise the valve heaters, which is quite in order.

G.E.C. BC7092

I have a G.E.C. BC7092 combined television and radio set, the radio side of which is perfectly all right, but the picture at intervals of about five minutes suddenly has a white flash across it and the picture

almost immediately blacks out. If left alone it will right itself in about one minute. The picture can be restored at once by use of the brilliance control, although then the control has to be backed off over about one minute to compensate for increase of brilliance. This fault can be simulated by switching the room light on or off. Could you please help me, as my local dealer has refused to service this set on the grounds of overwork.—A. D. Marchant (Farnborough).

The fault described is caused by an electrical connection somewhere in the vision section which is intermittently defective at radio-frequencies. Often the fault lies in a coupling or decoupling capacitor, or even in a coil, but sometimes a poor connection between a valve pin and the corresponding socket on the valveholder provokes the effect. In this case, the effect can usually be stopped and started by moving the offending valve in its holder.

H.M.V. 2807

I could not get the frame hold to lock in my receiver. I changed V7 (B36) and the transformer; also R55. The voltages and condensers in this circuit appear to be O.K.

Now, with height and framhold controls at maximum I get a steady picture, but the height is an enormous length. Slight movement from maximum of the height control reduces the picture to about 2in.—width O.K. In order, therefore, to reduce the amplitude I changed cathode resistor in the frame amplifier V15 (KT33C) to 5,000 Ω , still keeping height control at maximum. This helped to close up the picture, but head and shoulders are normal, legs twice their normal length. Your advice to correct this would be greatly appreciated.—C. Blundell (North Kensington, W.11).

First put the circuit back to normal, and then check the condition of R54 and C36. Almost certainly you will find that one or other of these components has altered in value.

MARCONIPHONE VT53DA

At present the picture is lacking in height (in short top and bottom of screen) and any attempt to increase same by means of the height control sends the picture "flying" vertically (not a slow roll) and as the vertical hold is at the end of its tether, the only way I can obtain a steady picture is by decreasing the height control. This has been going on for some time, but I have to adjust the height control periodically with a consequent further reduction in picture height.

I have, in turn, replaced B36, KT33C and Z63 valves, also reduced the values of R32 and R47.

I should mention that the mains voltage here is low, 200 volts, and I am using a transformer (outside the set) to step the voltage to 230, but as I am getting full width I do not think it can be lack of H.T.—F. Sullivan (Bayswater).

Change R41, 3.3 M Ω frame hold series resistor. This is located under the chassis on the long tag strip near the B36 and KT33C valve bases. It is concealed by a flat type .0039 μ F capacitor.

PHILIPS 1700A

My Philips projection model has just commenced to give trouble with frame slip. I have renewed the frame oscillator and output valves, also the blocking transformer and resistors R106 and R101, which put matters right for a few days, after which it started to slip again, and I found the fault in the R101 resistor, which I

renewed, and which put matters right for about a week, then it went again. In all I have renewed this resistor about three times. Is there anything else that will cause this resistor to keep going high, or have I got a poor lot of resistors, which I got all at the same time?—J. Riley (Oldham).

There is no reason why R101 (1.5M Ω) should require frequent replacement if when the receiver is working the frame scan is reasonably linear. You have not stated the wattage of the resistors used. We should recommend $\frac{1}{2}$ watt. It is possible that long storage under unsuitable conditions may have effected a deterioration in the group of resistors which you purchased. Therefore it would be advisable to purchase a new one from a dealer's new stock.

PHILCO BT1410/B

I have a Philco BT1410/B converted to Holme Moss, which has been working on this station for five years.

However, six months ago the receiver stopped working suddenly and I tested all the valves and voltages and condensers and found them O.K. Still no signals, so I started to substitute all valves in turn and condensers, but still no signals.

Having no signal or pattern generator I was lost, so by accident I tried the coupling condensers from R.F. transformers L2 and L3 to V2. However, when I tried C5 100pF in parallel with the other condenser in circuit signals came through and reception was, as before, very good; so I tried the condenser in place of the old one, but no signals. This was queer as I saw on the service data that it is 100pF, so I put two 100pF in parallel and the receiver worked satisfactorily and still does. The receiver is a Plessey Mark I chassis.

The reason for asking you why this receiver is working O.K. in this condition is that I have tried several Band III converters and cannot receive any signals of sound or vision. I have tried multi-arrays, checked cable E.T.C., but no results. The latest 13-channel receivers receive the Band III channel 8 and 9 O.K.—D. G. Johnson (Cheshire).

We would suggest you check the following points:

That R6 is 22K Ω .

That, with C5 at 100 pF, L3 is properly tuned.

That R7 is 100K Ω and R8 1.5 K Ω .

It would appear that a minimum signal of a certain amplitude is necessary in order to operate the V2 mixer/oscillator. Therefore if C5 and R6 are correct and L3 is properly aligned, suspect the V2 stage, R7 and R8 being suspected in the first stage of the fault finding.

BAIRD T165

I recently bought a Baird portable, secondhand.

On switching it on some sparks flew out, so I dismantled it and found the picture width control burnt out, also the one next to it, that is, the horizontal hold. I replaced these; now I get a resistor at the base of valve 20P1 very hot, also a 10F1 valve all aglow at the base. May I state that previous to the 10F1 glowing I got a rather good picture, but now I get no picture, but horizontal rasters.

I have had plenty of experience in radio, but nothing much in television; also I am unable to get a service sheet.—E. Mayers (Oldham).

It would help us if you could let us know to which tag of the 20P1 valve base the resistor which is overheating is connected. We are inclined to think that you mean the screen dropping resistor, which normally

does run rather warm, but will overheat if the line time-base is not functioning properly. Also we would like to know which 10F1 is "aglow." The video amplifier will do this if the contrast control is advanced beyond its normal setting so that excessive signal strength results.

Again oscillation in the vision stages will cause the effect and thus the decoupling arrangements should be checked.

FERGUSON 988T

My problem is that I cannot view my set in daylight because I cannot get the picture bright enough.

It gives a good picture with a 60 watt table lamp on the top of the set in a dark room with these exceptions: not quite full width (about $\frac{1}{4}$ in. each side) and faint dark lines $\frac{1}{2}$ in. thick with half-normal picture in between (four in all).

I have a new tube fitted, a 12XP4, in place of the old one because it was four years old.

When I turn up the brilliance control the whites go whiter and the blacks just gradually fade out as it is advanced.

The sound is normal and clear, and I am miles off the road as to interference.—R. W. Marjoram (Norwich).

Check the condition of the vision detector. This is a germanium diode type CG5 situated inside the final vision I.F. transformer can. Also check the condition of the 220K resistor and 0.01 μ F capacitor in the first anode circuit of the picture tube. Check the video amplifier valve EF80 and associated components.

EKCO TS114

My set is an EKCO, type TS114, 12in., and is developing signs of trouble with frame slip (vertical). I have no circuit diagram and should, therefore, appreciate particulars of the valve controlling the "frame hold" and its position in the set. The control is adjusted as far as possible.—F. C. Vincent (Uxbridge).

The 6K25 (there is only one on the chassis) is the frame oscillator valve, in the cathode circuit of which is the frame hold control. Connected between the control grid and cathode is a 2.2K resistor; ensure that this is of correct value. Also check the condition of the valve and the 500pF capacitor which is connected between the grid circuit (pin 5), via a 5.6K resistor, and the anode circuit of the sync separator valve (SP61).

P.T. BAND III CONVERTER

I have carried out the suggestions made by you, but still find that the only way I can receive a picture is by shorting L2 to earth. I have not been able to check V1 as I do not possess a valve tester, but the voltages are O.K.

I would be satisfied with the picture as it is if only I could get a bit more strength as I cannot get rid of the fly-back lines.—E. Gubbins (Hampton Hill).

It is obvious that the first section of the double-triode valve is not tuning properly. This, as we have already suggested, may be caused by a faulty associated capacitor. If you are unable to get these tested or check them by substitution remove C3 from the circuit and short-circuit C2. If the unit now functions normally the capacitors concerned should come under suspicion.

Make certain that L2 has the shortest possible lengths of wire to connect it in circuit, and also make sure that the bottom end (that is normally C2) is connected to a common earthing point as shown on the circuit diagram.

RX159, 160/220 mc/s. with 1/VR91, 1/VR65; 1/CV66, 12/6; I.F. Amplified 178 (for this), 16.5 mc/s. with valves. 15/6 (postage 2/6 each).
R1355, new improved type, 37/6 (carr. 7/6). Condensers, Bak. tubular, 0.1/1.2 kV; 5/800 v.; 25/800 v.; 9d. each; 03/2.5 kV; 05/3.5 kV; 25/1.5 kV; 1/1. each. Responder, RDP1, new, 160/220 mc/s. 12 valves. 15/1 (carr. 7/6) or ZC3931, 9 valves. 25/- (carr. 6/-). Relays, 6v. 2 break. 1/6. R1355 I.F. Strips only, complete new with valves, 25/-; less valves, 12/6 (post 2/6). R.F. Units, Types 26 or 27. 27/6 (postage 2/6); RP24, RF25, soiled, 10/6. Motors, synch. 3,000 r.p.m., 10 VA, 100 v. 50 c.c. new. 10/-. I.F.T.'s 10/13 mc/s. canned, new, 1/3. Power Pack, new 200/260 v., A.C. input, outputs 250 v. D.C. 80 mA.; 6.3v., 3A and 24 v. 1A, D.C. 40/-. (carr. 2/9). Receivers, miniature, 100/145 mc/s. Valves, 3/EF91, 2/EL91, I.F. 9/72 mc/s. new, 37/6; less valves 7/6 (post 2/9). Vibrapacks, Jefferson-Travers, 12v. input. 22/6. List and enquiries. S.A.E. please! Terms, c.w.o. Postage extra. Immediate despatch. W. A. BENSON (PT), 308, Rathbone Rd., Liverpool, 13. (STO 1604.)

DIRECT T/V REPLACEMENTS offer the most complete Handbook of T/V Components and Rewinds, price 1/- T/V Components for all kit sets in stock. "Nuray" heater booster isolator for 2-volt C.R.T.'s, just plugs in, 27/6, plus 2/- packing and postage. 134-136, Lewisham Way, S.E.14. (Tideway 3696-2330.)

B.S.R. MONARCH 3-speed auto-change units; new in maker's sealed carton; guarantee; complete with instructions, template, suspension springs, 29/15/1, carriage paid; immediate delivery. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

TELEVISION, 9in. models, 26/10/-; 12in. models, 25/15; all makes; working; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

GUARANTEED TELEVISION, 12in. models, first-class picture, 5-channel, 23/0 each, carriage paid. THE GRAMOPHONE SHOP, 19-21, Brockley Rise, Forest Hill, S.E.23.

R.F. UNITS, Types 27 or 26, 25/-; 25 or 24, 10/-; brand new with valves; post 2/6. E.W.S. CO., 69, Church Rd., Moseley, Birmingham.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

"RADIO AND TELEVISION SERVICING", 5 volumes, untouched, 26, 113, ORANGE HILL RD., Edgware, Middx.

ALL DISTRICTS. An opportunity exists for Television Technicians to establish a business of their own. The business can be commenced in first instance in spare-time, showing an all the year round increasing income. Write, giving particulars of age, training, test equipment, experience, to TELEPATROL LTD., Federation House, Epsom.

SERVICE SHEETS for hire, Radio, T.V. Components, Valves, etc., supplied. Send stamp for list. M. FOY, 6, Wykebeck Gardens, Leeds, 9.

TELEVISION COMPONENTS

in stock for the

P.T. SUPER-VISOR, TELE-KING, VIEWMASTER, E.E. TELEVISOR and BAND III and wide angle modifications

Price lists available on request to:

J. T. FILMER, Maypole Estate, Bexley, Kent.
 Tel.: Bexleyheath 7267

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

T/V IN PERFECT WORKING ORDER from £14, carriage paid; all makes; many sets suitable use anywhere. Impossible to show complete stocks here. Send s.a.e. for lists of latest bargains. 10in. Marconi £14, 9in. Ekco £15, 12in. Ekco £22/10/-, 12in. Ferguson £24. THIS IS A GENUINE OFFER - NOT A "CATCH". 100's SOLD EVERY WEEK. Callers welcomed. HIGH STREET RADIO, 284-6, High Street, Croydon, Surrey. (Phone: CROydon 9015.)

SEVERAL EARLY MODELS 9in. Television, complete, and mostly working, 25/5/- each; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets "How to Use Ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive list of lenses, optical, radio and scientific gear free for s.a.e. H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.

TELEVISION INTERFERENCE. Receiver Filters, High-Pass E.5037, 30/-; Low-Pass E.5031, 30/-; Composite Band I/III, 49/6; Transmitter Filter E.5034-80dB, 1kw, 26. LABGEAR (CAMBRIDGE) LTD., Willow Place, Cambridge.

SUPER-TONIC SUN-RAY LAMPS. Ultra-violet Infra-red combined. Superb therapeutic quality. controlled output, automatic exposure. All mains. Listed 27/10/-, our price 20/- S.A.B. illustrated brochure. Dept 16. SCIENTIFIC PRODUCTS, Cleveleys, Lancs.

F.M. RECEIVERS and Complete Kits from 25. BEL, Marlborough Yard, Archway, N.19. (ARC 5078.)

SERVICE SHEETS, 4,000 models; new lists, 1/- (incl stamps). TELRAY, 11, Maudland Bk., Preston.

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP, WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
 SLOane 3463

Works:

36, ROSEBERY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small"

OSMOR CONVERTERS

LONDON. BIRMINGHAM. MIDLANDS Simple, efficient for all TV (including TRF). Guaranteed no break-through of Band I or re-radiation. Approx. 1 hr. to build. Will convert any Band III channel to any Band I channel. AC or AC/DC. Kit, £3.5.0. Ready wired, £4.0.0. Post free. Terms: C.W.O. Post orders only. THE ELECTRONIC SUPPLY CO. 29, Leigh Rd., Highbury, London, N.5

ENGRAVING.—Amateurs and trade surplus can be undertaken by getting in touch with A. G. ENGRAVING, now at 292, Earlsfield Road, London, S.W.18. (Tel.: BAT 9897.) (Engravers to well-known makers of Electronic Equipment used by the Aircraft Industry, A.W.R.E. etc.)

INVENTIONS. Letters Patent, a manuscript of 4,000 words tells how to obtain full protection for only £1 (government stamp). Manuscript from J. BLAIR, 21, Aberdeen Road, Bristol, 6.

SERVICE SHEETS, T.V. and Radio, over 2,000 models, sale or hire. Valves and Components. S.A.E. with enquiries. W. J. GILBERT, 24, Frithville Gardens, London, W.12.

"PREMIER" 12in. Birmingham Console, £20, o.n.o.; C12B tube almost new. Box No. 185, c/o PRACTICAL TELEVISION.

T.V. TUBES. We have a large selection of reclaimed or used but perfect CR. Tubes with 2 months' guarantee. High emission and picture shown on sale. 9in. 60/-/70/-, 12in. 24/10/-/25/10/-, 14in/17in. 26/27/10/-; post, packing and insur. 7/6. DELAWAR LTD., 77, Praed Street, London, W.2. (AMB 5465.)

BANISH THAT GHOST. Ghost pictures caused by mismatch and standing waves in aerial lead can be tuned out with special Tunable Matching Stub. Just plug in set and tunc. 15/6, post 9d. State channel. R.M.S., 60, Portway, Warminster.

WANTED

ALL TYPES of new radio valves wanted, small or large quantities; cash payment. R. H. S. LTD. (T), 159, Swan Arcade, Bradford, 1.

WANTED, Cossor 15in. TV Mod. 901, WALKER, Parsfield, Pucklechurch, Glos.

WANTED, Valves 6F13, 6F15, 6U4, 6Y51, 5Z4, ECL80, KT61, 25A6, etc.; prompt cash. WM. CARVIS LTD., 103, North Street, Leeds, 7.

EDUCATIONAL

BUILD YOUR OWN TV and learn about its operation, maintenance and servicing. Qualified engineer-tutor available while you are learning and building. Free brochure from E.M.I. INSTITUTES, Dept. PT.58, London, W.4. (Associated with H.M.V.)

I.P.R.E. Data for constructing TV Aerial-strength Meter, 7/6; 5,500 Alignment Peaks for superhets, 5/9; sample copy "Practical Radio Engineer," 2/-. Membership-examination particulars, 1/-. Syllabus of seven postal courses free and post free. SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.E.I., I.R.E., City and Guilds, R.T.E.B. and other professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to E.M.I. INSTITUTES, Dept. PT.28, London, W.4.

ALL DISTRICTS

A Permanent and Increasing Income TECHNICAL AGENTS REQUIRED

For Servicing:

T.V. Insurance and T.V. Rentals Must own Test Equipment. Retailers' Enquiries Welcomed.

Write:

TELEPATROL LTD., WEST STREET, EPSOM.
 Tel.: Epsom 4700.

"VIEWMASTER"

T.V. TUNER COMPONENTS

- 6 wafer Switch assembly ... 20/-
- Fine Tuner ... 4/-
- 3 Coil platforms ... 1/-
- Set of three metal brackets... 7/6
- Screen complete ... 5/-

All prices include postage

Send for complete list of radio and T.V. components. POST FREE.

Components for the ARGONAUT A.M./F.M. RECEIVER available from stock.

AUDIO LTD.,

Tower Road, London, N.W.10.

NEW-MAX ELECTRONICS LTD.

220, Edgware Rd., London, W.2
Tel. PAD. 5607

Come and visit us. The Largest Electronic Bargains Store in London. We have large stocks of H.P. repossessed T.V. and Radio Sets, Radiograms, Reclaimed and guaranteed C.R. Tubes, 12in. £5, 14in. £6/10/-, 15in., £7/10/-, 17in. £9/10/-, p. and p. 10/-; Tubes with Heater Cathode Short, 12in. £2/10/-, 14in. £3/10/-, 15in. £4/10/-, 17in. £5/10/-, p. and p. 10/-. Surplus Valves, Components and Test Equipment, etc. etc. Also available all types and makes of new CR Tubes at list prices. Part exchanges welcomed! 12in. T.V. Set to suit any BBC channel £28 inclusive carriage. Also Wanted: Electronic Equipment of Every Description. Best Prices Given. Phone, Write or Call.

RADIO AND TELEVISION COMPONENTS

All parts in stock for:
Viewmaster, Soundmaster, Teleking; etc.
Easy Terms available,
2d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO.
FINSTHWAITHE, NEWBY BRIDGE,
ULVERSTON, LANCs.

THE VALVE SPECIALISTS

Benley Acoustic Corp. Ltd.

38, CHALGOT ROAD, N.W.1
PRImrose 9090

1st grade goods only. No seconds or rejects.

024	6/-	617	8/6	9003	5/6	HL123	10/6
LAB	8/6	6VGG	7/-	9006	7/6	HL123D16	6/6
LA5	6/-	6VGGT	7/6	AC1RL	7/6	HL41	7/6
106	8/6	6X4	7/6	DDD	15/-	HL41D10	7/6
115	11/-	6Z4S4	8/6	AC1P6a	6/6	HL123D12	6/6
114	7/6	6Z5	12/6	AC1P4	8/-	HL123D12	6/6
1135	7/6	7A7	12/6	ACV11	10/6	KBC32	8/-
11N5	5/-	7B7	8/6	AP4	7/6	KF35	9/-
1N5	11/-	7C5	8/-	ATP4	8/6	KL25	9/-
1R5	9/-	7G6	8/-	AZ1	10/6	KT2	5/-
185	7/6	7H7	8/-	B309	9/-	KT33C	10/-
171	7/6	7Q7	12/6	B119	12/6	KTW61	7/-
175	7/6	7T7	8/6	BL63	7/6	KTW62	7/-
2A3	12/6	7Y4	8/6	CK323	6/6	KTZ41	6/6
2026	4/-	8A8	12/6	CK325	6/6	L63	6/-
201C	7/6	10C2	10/6	CV35	12/6	LN309	12/6
2X2	4/6	10D1	7/6	F11	3/6	LN310	9/6
2A1	7/6	10F1	11/-	10G3	5/6	LZ119	12/6
2A5	8/6	12A6	6/6	DAF96	9/6	M14	5/6
307	8/6	12A8	15/-	DCC90	8/6	M14	7/6
306	2/6	12A17	12/6	DF96	9/6	M44B	8/6
305	9/6	12A77	9/-	DH77	8/6	M112	8/6
284	7/6	12A17	8/-	D92	9/6	OC3	9/-
2V4	8/6	12AKT	10/6	DK96	9/6	OV3	8/6
544	8/-	12BA6	9/-	DI2	15/-	OM6	7/6
5V4	10/-	12BE10	10/-	DL35	11/-	P22	10/6
5X1	10/-	12E1	30/-	DL46	9/6	PABC015	7/6
5V3	8/-	12H6	3/-	DL410	10/6	PC84	10/6
374	10/-	1235GT	6/-	DL14	2/-	PC86	10/6
3267	8/6	1237	9/6	EAG0	2/-	PCL83	12/6
5Z4	8/6	12K7	9/6	EADCS0		Pen25	6/6
6A37	8/-	12U64	7/6			Pen16	7/-
6A85	11/-	128A7	8/6	EAF42	12/6	PL81	12/6
6A7	6/6	128C7	7/6	EB41	7/6	PL82	10/6
6A7	5/6	128C7	5/6	EB41	6/6	PL85	12/6
6A47	12/6	128H7	7/6	EB91	6/6	PM12	4/6
6A38	10/-	128J7	8/-	EB93	12/6	PM12M	6/6
6AK5	6/6	128K7	6/6	EBC33	7/6	PM2B	12/6
6AK8	10/-	128Q7	8/6	EBU41	10/-	PY81	10/6
6AL5	6/6	128A7	7/6	EBF39	11/-	PY81	10/6
6AG5	7/6	128PA	10/6	EC32	7/6	PY82	10/6
6A7	10/-	13VTA	8/6	EC34	6/6	PY83	10/6
6AT6	8/6	14R7	10/6	ECC32	10/6	Q21	7/6
6B4	6/-	16A5	10/-	ECC33	8/6	Q22B	12/6
6B7	10/6	17Z3	10/-	ECC35	8/6	Q25	6/6
6BA9	7/6	19H1	10/-	ECX40	15/-	QS1501	11/-
6B5	4/-	19Y3	10/6	ECH1	9/-	Q25	10/6
6B8M	4/6	20L1	12/6	ECC82	10/6	SD6	7/6
6BE6	8/-	20P3	12/6	ECC83	10/6	SP27	8/6
6B46	12/6	25Z4	9/-	ECC84	12/6	SP47	8/6
6B36	8/-	25Z5	8/6	ECC85	10/-	SP41	8/6
6BW6	8/6	27	7/6	ECX41	6/6	SP21506	8/6
6B47	10/6	28D7	7/6	ECH2	15/-		7/6
6BX6	10/6	30	7/6	ECH35	11/6	TD2A	8/6
6BY7	10/-	31	7/6	ECH42	10/6	FD23	10/6
6C1	7/6	30C1	12/6	ECH81	10/-	TP22	10/6
6C9	6/6	30L1	12/6	ECJ30	11/-	U16	12/-
6C8	8/-	33L9	9/-	EP6	10/6	U17	7/6
6C16	9/6	35Z4	8/6	EP9	12/6	U22	10/6
6D6	6/6	35Z5	8/6	EP36	4/6	U31	9/-
6D6A	7/6	35Z1	12/6	EP7A	10/6	U30	8/-
6D6CT	8/-	31MP	12/6	EP39	6/6	U32	8/-
6E7	10/6	41MCL	7/6	EP40	17/-	V28	7/6
6E8	10/6	43Z5	12/6	EP41	11/-	U25	12/6
6E7	9/6	30C5	7/6	EP42	12/6	EAB42	13/6
6E32	6/-	50L6	8/6	EP50(A)	8/-	UB41	10/-
6E33	9/6	57	8/6	EP50(B)	5/6	UB12	11/-
6G6	6/6	58	8/6	EP54	5/6	VP41	10/6
6H6C	2/6	61ET	12/6	EP80	10/-	VP42	13/-
6H6M	3/6	61EP	10/6	EP83	10/6	VP41	10/6
6L5	5/-	61SPT	15/-	EP86	12/6	UL46	11/6
6L54C	5/6	62TH	10/-	EP89	10/6	U74	10/6
6A6	6/-	62VP	9/-	EP91	9/-	V1507	5/6
6G74	6/-	72	6/6	EP92	7/6	V18492A	2/6
6K6	7/6	73	7/-	EL32	6/6	V1840	10/6
6K7	6/6	77	8/6	EL41	10/6	V1848	10/6
6K8A	8/-	78	8/6	EL42	13/-	V247	8/6
6K8CT	8/6	80	10/6	EL81	15/-	VP47	8/6
6L64	9/-	83	8/6	EL84	11/-	VP23	6/6
6L67	7/6	150B2	12/6	EL91	6/6	VP41	7/6
6M7	7/6	210L7	3/-	EM34	10/6	VP33	10/6
6M7	8/6	240QP	8/6	EM31	11/6	VP33	8/6
6Q7GT	9/-	807	7/6	EP86	12/-	VT501	6/6
6R7	8/6	808	25/-	EZ40	10/-	X66	10/6
68A7	8/-	86G4	12/6	EZ41	11/-	XFW10	6/6
68G7	6/6	883	10/6	EZ90	10/-	XPY2	6/6
68H7	6/6	850	3/6	FC13	12/6	XH15	4/-
68I7	8/-	1203	7/6	FC30	8/-	XSC15	5/-
68K7	6/-	3763	12/6	H63	12/6	Y63	7/6
68L7	8/-	17193	2/6	HK90	10/-	V65	10/6
68N7	8/6	7475	7/6	HL2	8/-	Z77	9/6
6887	7/6	9003	5/6	HL130	7/6	Z79	10/6

CRYSTAL DIODES.—617L, GEX34, CUG6, M1, CG10B, all 7/- each.
All boxed. Full maker's guarantee. Post 6d. each. Insurance (optional) 6d. per order. Shop hours 9.30 to 5.30, Sat. 1 p.m. Why not 'phone or wire that urgent order for immediate despatch C.O.D. 7/12d and conditions of sale S.A.E.



THE SPENCER - WEST PATTERNING REMOVAL UNIT TYPE 54

works with any Band III convertor unit and completely removes patterning caused by Band I breakthrough. Results are guaranteed

PRICE 25/- Complete

Full instructions for simple fitting supplied. We will send a unit on approval for 7 days against cash on receipt of order, or from your Dealer.

SPENCER - WEST LTD. QUAY WORKS GT. YARMOUTH

Phones : 4794 and 3009
Grams : Spencer-West, Great Yarmouth

OPPORTUNITIES IN TELEVISION

144 pages
Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M.Brit.I.R.E., R.T.E.B. Cert., City and Guilds. Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 144-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

We Guarantee "NO PASS-NO FEE"

If you are earning less than £15 a week you must read this enlightening book.


Send for your copy NOW—FREE and without obligation.

WRITE TODAY!
British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane, **BIET**
Kensington, W.8.

News From the Trade

NEW MULLARD LINE OUTPUT PENTODE


THE Mullard PL36 is an output pentode primarily designed for the line timebases of television receivers using picture tubes with a deflection angle of 90 deg., and 16 kV. E.H.T. The new valve is octal based, and has a 25 v., 0.3 A. heater, suitable for series operation. A new half-wave power rectifier valve for use in television receivers with series-connected heaters has also been produced and is known as the PY32. The valve has a maximum rated output current of 275 mA., a typical D.C. output voltage being 190 v. when the valve is supplied direct from A.C. mains, 200 v.—Mullard, Ltd., Century House, Shaftesbury Avenue, W.C.2.

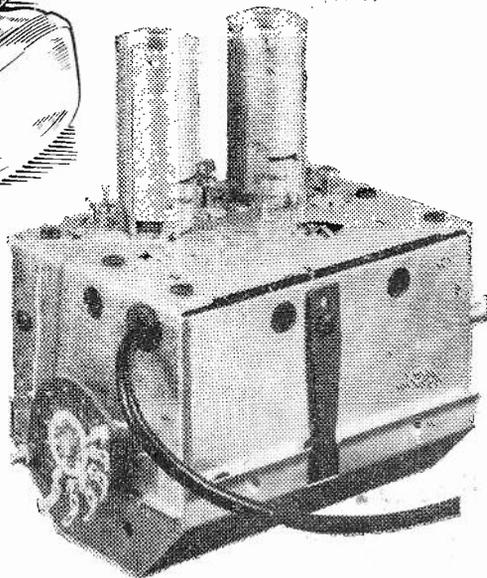

Plessey's 12-channel Tuner

OSMOR ATTENUATOR

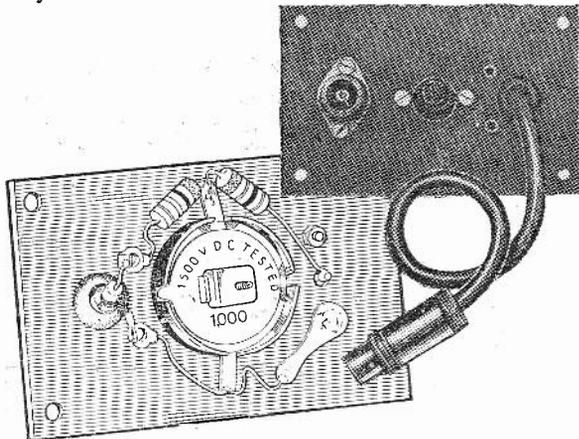WHAT is claimed to be the only attenuator of the constantly variable type is now available from Osmor and is illustrated below. Designed for an 80-ohm input, and with a constant output impedance over the complete attenuation range, this component has a variable adjustment from 2 to 1 to 10 to 1 by single control. The price is 15s.—Osmor Radio Products, Ltd., 418, Brighton Road, S. Croydon, Surrey.



The New Osmor Attenuator

PLESSEY TUNER

A NEW 12-channel tuner unit is being manufactured by The Plessey Co., Ltd., for domestic television receivers.

This tuner is constructed on the turret principle. Each channel is pre-set by a set of coils designed for optimum performance at that particular frequency. These coil circuits are all mounted within a drum which can be rotated for frequency selection by a simple switch.

In addition to its prime function as a tuner for new sets now in production, the unit can be used to replace the input circuit of a receiver designed for Band I only, and will give peak performance on both Band I and Band III by use of the latest low-noise valves. It may be connected to the frequency changer circuit of the receiver, in which case the frequency changer serves as an extra I.F. amplifier, and power supplies for the converter may be obtained from this valve socket or that of the now redundant R.F. stage. Alternatively, the converter may be connected to the first I.F. stage of the receiver.

The tuner unit can be provided for any of the normal I.F. frequencies, i.e., 10.5 to 14 Mc/s, 16 to 19.5 Mc/s, 34.5 to 38 Mc/s. If required the unit can be supplied with a wafer switch ganged to the main spindle to enable selection of alternative gain controls for Band I and Band III to be made.

Where less than 12 channels are required, the units can be modified accordingly—a fact that will be appreciated where economy is a consideration.—Plessey Co., Ltd., Ilford, Essex.

QUERIES COUPON

This coupon is available until JUNE 21st, 1955, and must accompany all Queries.

PRACTICAL TELEVISION, JUNE, 1955



QUALITY TELEVISION COMPONENTS

SCANNING COILS, 6/10 kv. R.F., E.H.T. UNITS, E.H.T. and OUTPUT TRANSFORMERS, LINE FLY-BACK E.H.T. UNITS

Write for illustrated list (Publication 75)

Coil Kit of two for Aug "P.T." Band III Converter 5/-
Kit of three 7/6. Kit of four for October Band III Converter 6/-.

HAYNES RADIO Ltd., Queensway, Enfield,
Middlesex.

AERIAL FITTINGS

FOR

Band III, Band I and Radio F/M.

Our increased range of Diecast Alloy Fittings include Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "In-line" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc., together with useful Formulæ and Hints for constructing your own aerial quickly and cheaply. Send 1/- P.O. to cover the cost of catalogue and postage to:

FRINGEVISION LTD.

MARLBOROUGH, WILTS.

Phone : 657/8

WHY WASTE TIME

Give that set its best chance
FIT QUALITY COMPONENTS

Catalogue 1/-.

Parts for the following :—

Manual

Osram "912" plus Amplifier 4/-

Mullard 10-watt Amplifier 3/6

The Coventry

2-watt Amplifier ...)

4-watt Amplifier ...) 1/-

6-watt Quality Amplifier ...)

The Coventry A.M. Tuner

Unit 1/-

Denco F.M. Tuner Unit ... 1/6

Complete Component Price Lists
will be supplied with each Manual.

COVENTRY RADIO

EST. 1925

189, DUNSTABLE ROAD,
LUTON, BEDS.

Phone : Luton 2677

CASCADE TYPE T/V PRE-AMPS

BBC & ITV

Manufactured specially to suit fringe and ultra-fringe conditions. Band I models in use 140 miles north of Kirk O' Shotts (check our position), and in many other distant locations and difficult areas.


Complete in crackled steel case with built-in powerpack for 200-250 v. A.C.

£5/5/- P. & P.
2/-

State channel used, or send 6d. stamp for illustrated details and some interesting fringe data.

ELECTRO-Acoustic LABS.
TAIN-ROSS-SHIRE-SCOTLAND

PARKER'S SHEET METAL FOLDING MACHINES

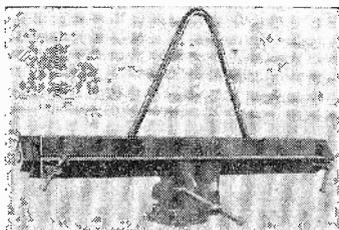

Heavy Vice Models. 18 gauge mild steel x 2 ft. wide and 18 gauge MS x 18 in. wide. Form angles and channels. End folding attachments for radio chassis. Tray or box making.

Price 55/- each. Attachments 1/6 per ft.

Carriage 4", if with attachments 5/6.

Send for details of 3 ft. model, also sheet metal hack-sawing machine.

**A. B. PARKER WHEATCROFT
WORKS**
WELLINGTON STREET, BATLEY,
YORKS. Telephone 426

"VIEW MASTER"

ENTHUSIASTS!

If your supplier has any difficulty in obtaining "View-Master" modification and converter kits for you, get him to contact the foremost component wholesalers:—



**UNCLES, BLISS
OF CROYDON**

All Denco and T.C.C. kits and circuits
in stock. Trade enquiries only.

INTERNATIONAL TUBE

Handbook 15/- Post 9d
(MK BUIZEN)

TELEVISION TIMEBASE CIRCUITS PRINCIPLES AND PRACTICE. By C. H. Banthorpe. 5s. 0d. Postage 4d.

THE RADIO AMATEUR'S HANDBOOK, 1956. By A.R.R.L. 30s. 0d. Postage 1/6.

TELEVISION CIRCUITS AND SERVICE DATA. No. 1. By C. H. Banthorpe. 9s. 6d. Postage 9d.

TELEVISION ENGINEERS' POCKET BOOK. By E. Molloy and J. P. Hawker. 10s. 6d. Postage 6d.

T.V. FAULT FINDING, a Data Book, No. 5. 5s. 0d. Postage 4d.

TELEVISION RECEIVER SERVICING Receiver and Power Supply Circuits, Vol. 2. By E. A. W. Spreadbury. 21s. 0d. Postage 1/2.

PRACTICAL T.V. AERIAL MANUAL for Bands I and III. By R. Laidlaw. 4s. 6d. Postage 4d.

The MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British and American Books

19-23, PRAED ST., LONDON, W.2

Phone : PADDington 4185

Open 6 days 9-6 p.m.

DISC CERAMIC CAPACITORS

The modern decoupling capacitor. Midget size, non-inductive with excellent dielectric insulation. Ideal for T.V., etc. 500 v. D.C. (300 v. A.C.) working : 470 pF., .001 μ F 5/16 in. dia., .002 μ F, .003 μ F, $\frac{1}{2}$ in. dia., .005 μ F, $\frac{3}{8}$ in. dia. Each 9d.

Minimum postage 6d. on orders under £2.

**SOUTHERN RADIO &
ELECTRICAL SUPPLIES**
SORAD WORKS, REDLYNCH
SALISBURY

Telephone : Downton 207

TELEVISION TUBES

MULLARD ...	12in. £6.10.0	14in. £7.10.0	17in. £10.0.0	} Ex Stock
COSSOR ...	12in. £6.10.0	14in. £7.10.0	17in. £10.0.0	
EMITRON ...	12in. £6.10.0	14in. £7.10.0	17in. £10.0.0	

MAZDA. 12in. only £6.10.0. 14 Days Delivery.

All Tubes plus 12/6 carriage and insurance.

SIX MONTHS' GUARANTEE

Converter M.1. Midlands area, high gain, own power supply, built in crossover unit £9.9.0

Converter M.2. Midland fringe area, own power supply £9.18.0

Crossover Box. Low loss 12/6

Finished in Stove Enamelled Steel Case.

Terms to the Trade.

RE-VIEW (LONDON) LTD.

81, HIGH STREET : : MERTON, S.W.19

Telephone: CHERRYWOOD 3255

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES AND C.R.T.'S.
AVO METERS IN STOCK

Avo Model 7	—	—	—	£19 10 0
Avo Model 8	—	—	—	23 10 0
Electronic Test Unit	—	—	—	27 10 0
Electronic Test Meter	—	—	—	40 0 0
AC/DC Minor	—	—	—	10 10 0
*Cossor Oscilloscopes Model 1052	—	—	—	104 0 0
" " " 1935	—	—	—	120 0 0

Full range Taylors Meters. List on request.

LEAK Pick-up Arm	—	—	P.T. ...	2 15 0
" Long Play or Standard Heads With Diamond Stylus	—	—	—	1 3 1
" Matching Transformer	—	—	P.T. ...	5 15 0
	—	—	—	2 8 4
	—	—	—	1 15 0

Leaflets on Request

JASON AF/FM Tuner, complete with valves and automatic frequency control, also cascade input — £28 13 0

LATEST VALVE MANUALS

MULLARD, 10/6, OSRAM & BRIMAR No. 6, 5/- each, OSRAM Part 2, 10/-. Post 9d. each extra. TRANSFORMER for 200/230 v., 37/6.

Terms C.O.D. OR CASH with order and subject to price alterations and being unsold.

Est. 1919

Arthur's


PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS: Gray House

150-152 Charing Cross Road, London W.C.2

TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."

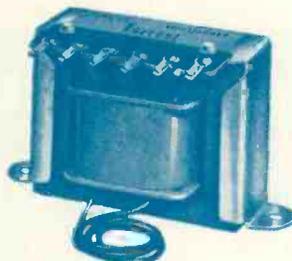TELEGRAMS—"TELEGRAY, WESTCENT, LONDON." CABLES—"TELEGRAY, LONDON."



Forrest COMBINED BOOSTER

AND ISOLATING TRANSFORMERS

Cheap and easy to fit to any Receiver, they enable Tubes with low emission or with Cathode-Heater short to be used again. Supplied in any voltage from 2v.—13.3v.

OPTIONAL BOOST (12½% and 25%).

Price 21/- (Retail)

H. W. FORREST (TRANSFORMERS) LTD.

349 HASLUCKS GREEN ROAD SHIRLEY, BIRMINGHAM. SHI. 2483

PREMIER RADIO COMPANY


OPEN TILL
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2

Telephone :
AMBASSADOR 4033
PADDINGTON 3271

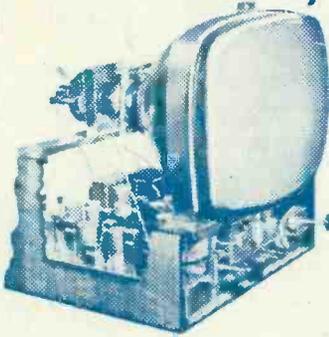★ **Band Three (Commercial)**
For the Home Constructor



Instruction Book 3/6. Post
Free. Includes details of
both designs.



The Televisor may be constructed in 5 easy stages : (1) Vision, (2) Time Base, (3) Sound, (4) Power Pack, (5) Final Assembly. Each stage is fully covered in the Instruction Book, which includes layout, circuit diagrams and point-to-point wiring instructions. The Instruction Book also includes full details for converting existing Premier Magnetic Televisors for use with modern wide angle tubes. All components are individually priced

THE NEW PREMIER TELEVISOR 13 CHANNEL DESIGN

SUITABLE FOR USE WITH ANY POPULAR WIDE ANGLE TUBE

DESIGN 1. Includes a Multi-Channel Tuner (Channels 1-13) continuously variable 40-100 Mc/s and 170-225 Mc/s. The Tuner is supplied wired and tested and is complete with Valves, all connecting leads and fixing brackets.

THIS DESIGN MAY
BE BUILT FOR **£31. 12. 2** (plus cost of
C.R.T.)

DESIGN 2. Channels 1-5, tunable from 40-68 Mc/s.

THIS DESIGN MAY
BE BUILT FOR **£26. 12. 2** (plus cost of
C.R.T.)

- ★ Constructors who have built Design 2 (5 Channels) may convert their Receivers to Design 1 for £6 ; this price includes Multi-Channel Tuner, New Vision Input Coil and full instructions.
- ★ All Coils supplied for these two Superhet Receivers are PRE-TUNED, ASSURING ACCURATE ALIGNMENT AND EXCELLENT BANDWIDTH.
- ★ Duomag permanent magnet focusing with simple picture centring adjustment.
- ★ Exceptionally good picture "hold" and interlace. ★ Noise suppression on both Sound and Vision.

S.E.C. ALUMINISED C. R. TUBES



7203A, 14"

The G.E.C. 14in. Cathode Ray Tube type 7203A has the following attractive features:—

- (1) Improved tube life and reliability.
- (2) A narrow beam angle triode gun giving:—
 - (a) Uniform focus over the entire screen area.
 - (b) Small spot size. (c) Freedom from astigmatism.
- (3) A high reflectance aluminium backing to the fluorescent screen giving:—
 - (a) 70% increase in picture brightness. (b) High contrast daylight viewing. (c) Complete elimination of ion burn from both positive and negative ions.

Price
£14. 15. 0
P. Tax **£6. 18. 1**

THE GENERAL ELECTRIC CO. LTD MAGNET HOUSE, KINGSWAY, LONDON W.C.2

Handwritten signature