

• PORTABLE TV RECEIVERS •

# Practical Television 13

NOVEMBER, 1956


AND TELEVISION TIMES

EDITOR: F.J. CAMM





# LASKY'S RADIO

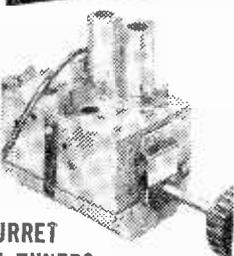

## TURRET TV TUNERS

Complete with 12 coil sets. Covers all Channels Band I and III, London and Birmingham. Valves used: PCC84, R.F. double triode, cascade R.F. amplifier, PCF80, triode pentode i.c. and mixer, I.F. output 33-33 Mc.s, easily modified to other I.F. outputs. With full instructions and circuit diagram. Knobs, 3/6. **99/6.** Post 2/6.

## BIGGEST BARGAIN EVER IN TV CATHODE RAY TUBES



### BRAND NEW, PERFECT 16" METAL CONE C.R.T.

First specification: 6.3 v. heater, Ion trap, 11 kV. E.H.T., wide angle 70 degrees, standard 33 mm. neck, duodecal base, magnetic focus and deflection. Length 17 1/16 in. Gives large black and white picture 11 x 11 in. Unused in original cartons. GUARANTEED BY US FOR 3 MONTHS. Full data, connections and suggested time bases supplied with every Tube.

LISTED AT £23.9.10

LASKY'S PRICE £8.9.6.

Carr. & Insur. 2/6 extra.

Masks, Anti-Corona, Bases and Ion Traps available.

## 5-Valve RADIO CHASSIS

Ideally suitable as radio receiver for inclusion in a TV set. Brand new and unused. A.C. D.C. 200 250 v. I.F. 465 kc.s. A.V.C., 4 watts output, 3-station pre-set, frame aerial, fully aligned, chassis 10 x 5 1/2 in., max. height 5 1/2 in. Completely wired and ready for use with the addition of a speaker and output transformer. Two controls, volume and station switch. Valves used: 10C1, 10T9 or 1P11, 10L11, 10P14, U401 or UX11.

LASKY'S PRICE 52/6

## GARRARD RC.110 3-SPEED MIXER AUTO-CHANGERS

Complete with crystal pick-up. Brand new in maker's cartons with instruction book. Cream brown enamel finish. List £11.13.0.

LASKY'S PRICE £7.19.6. Carr. 3/6. Suitable Cases available.

## MAKERS' SURPLUS COMPONENT BARGAINS

- WIDE ANGLE 38 mm. Line E.H.T. trans., Ferro-cube core, 0-16 kV. 25/- Scanning Coils, low Imp. line and frame. 25/- Ferro-cube cored scanning Coils and Line Output Trans., 10-15 kV. EY51, winding Line Trans., incorporates width and linearity control. Complete with circuit diagram, the pair. 50/- Frame Output Transformer Scanning Coils low Imp. line and frame. 17/6 Frame or Imp. block osc. transformer. 4/6 For us Magnets Ferro-cube P.M. Focus Magnets, Iron Cored. 19/6 Duomag Magnets. 22/6 300 m.a. Smoothing Chokes. 15/- Electromagnetic focus coil, with combined scan coils. 25/-
- STANDARD 35 mm. Line Output Transformers, No E.H.T. 12/6 Line Output Transformers, winding, E.H.T. and 6.3 v. 19/6 Scanning coils, Low Imp. line and frame. 12/6 Ditto by Igranite. 14/6 Frame of line blocking oscillator transformer. 4/6 Frame output transformer. 7/6 Focus Magnets: Without Vernier. 12/6 With Vernier. 17/6 Focus coils, Electromag. 12/6 200 m.a. Smoothing Chokes 10/6

## LASKY'S (HARROW ROAD) LTD.

Both Addresses Open All Day Saturday. Early Closing, Thursday.

42, TOTTENHAM COURT ROAD, W.1. Telephone: MUSEUM 2905.

370, HARROW ROAD, PADDINGTON, W.9. LADbroke 4075 and CUNNINGHAM 1979.

All Mail Orders to Harrow Road, please SEND FOR OUR NEW LIST enclosing 3d. in stamps

## BAND III CONVERTER.

Kit kit by TELETRON, with circuit and wiring details, etc. For use with TRF or Superhet TV Receivers. ONLY 12/-. Drilled chassis 3/-. Instruction leaflet only, 6d.

**INDICATOR UNIT TYPE 6.**—Contains VCR 197 tube with mu-metal screen, 4 valves EF50 and 2 of EB34, valveholders, CRT holder, condensers, resistors, etc. NEW CONDITION. ONLY 39/6 (carriage, etc., 7/6).

**AMPLIFIER TYPE 233A or 208A.**—As described in July, 1955, issue of *Practical Television*, for making a TV CONVERTER. Complete with 2 valves EF50. ONLY 10/- (post, etc., 2/-).

**PYE 45 MC S.F. STRIPS.**—Ready-made for London Vision Channel. Complete with 6 valves EF50 and 1 of EA50, and details of very slight mods. required. BRAND NEW. ONLY 49/3 (post, etc., 2/6).

**I.F. STRIP 194.**—Another easily modified strip for T.V. Complete with 6 valves SP61, 1 of EA50, and 1 of EF50; also mod. data. ONLY 29/6 (post, etc., 2/6).

**RECEIVER UNIT 159.**—Contains 4 valves, 1 ea h EF50, EA50, SP61, RI.37 and 24 v. Selector switch. ONLY 7/6 (post, etc., 2/-).

**R.F. UNITS TYPE 26.**—Complete with 2 valves EF51 and 1 of EC52, this is the variable tuning unit covering 65-50 mc/s (5-6 metres). BRAND NEW IN MAKER'S CARTONS. ONLY 27/6.

**POCKET VOLTMETERS.**—Read 0-15 and 0-500 v. A.C. or D.C. BRAND NEW. ONLY 18/6

**COMMAND RECEIVERS.**—Huge purchase from the Air Ministry. These famous compact American receivers which can be used for a variety of purposes are offered at ridiculously low prices while stocks last. Complete with six metal type valves, one each of 12K8, 12SR7, 12A6 and 3 of 12S-7, in aluminium case, size 1 1/2 in. x 5 1/2 in. x 5 in. Used, but in good condition. Choice of models, BC 455 (6-4 Mc/s), 25/-, BC 454 (3-6 Mc/s), 27/6, BC 453 (190-550 kc/s), 59/6, and a few of the 1.5-3 Mc/s model 65-/. (Postage on all models 3/-. Circuits supplied).

**COLLINS TRANSmitters.**—The renowned American TCS model, covering 1.5-12 Mc/s in 3 bands. Complete with 7 valves, employing 2 of 16Z5 in P.A. stage, one of 16Z5 in each of buffer and modulator stages and 3 of 12A6 in oscillator stage. Provision for O.P.O. or crystal control for 4 Xtal positions. Incorporates plate and aerial current meters. In Brand New Condition. ONLY £12.10.0 (Carriage, etc., 15/-).

**COLLINS RECEIVERS.**—Matches the above transmitter and is exactly the same size, 1 1/2 in. x 1 3/4 in. Has same coverage, and is complete with 7 valves, 1 each of 12S-7, and 12SQ7, 2 of 12A6, and 3 of 12SK7. Also has provision for Xtal control. A really terrific receiver for the serious operator. In Brand New Condition. ONLY £9.10.0 (Carriage, etc., 15/-) OR THE TRANSMITTER AND THE RECEIVER TOGETHER. £20.0.0 (Plus Carriage, as above).

**L.T. HEAVY DUTY TRANSFORMER.**—EX Admiralty. Has 3 separate windings of 5v.-0-5v. at 5 amps, and by using combinations will give various voltages at high current. BRAND NEW. ONLY 29/6 (post, etc., 2/6).

**MODEL MAKERS MOTOR.**—Reversible poles. Only 2 in. long and 1 1/2 in. diameter, with 1/4 in. long spindle. Will operate on 4, 6, 12 or 24 volt D.C. ONLY 10/6 (post, etc., 1/-).

**TRANSFORMERS.**—Manufactured to our specifications and fully guaranteed. Normal Primaries, 425-0-425 v., 200 ma., 6.3 v., 4 a., 6.3 v., 4 a., 5 v. 3 a., ONLY 65/- 250-0-250 v., 100 ma., 6.3 v. 3 a., 5 v. 3 a., ONLY 37/6 350 v.-0-350 v., 130 ma., 6.3 v. 5 a., 5 v. 3 a., ONLY 37/6 250-0-250 v., 60 ma., 6.3 v. 3 a., 5 v. 2 a., ONLY 21/-. The above are full shrouded, upright mounting, 5.5 kv. E.H.T. with 2 windings of 2 v. 1 a., ONLY 79/6 7 kv. E.H.T. with 4 v. 1 a., ONLY 89/6. PLEASE ADD 2/- POSTAGE FOR EACH TRANSFORMER.

**E.H.T. TRANSFORMER FOR VCR97 TUBE.**—2,500 v. 5 ma., 2-0-2 v., 1.1 a. 2-0-2 v., 2 a., 42/6 (postage 2/-).

**SPEAKERS.**—P.M. 6" or 6 1/2" trans., 19/6; 8 in., less trans., 10/6

**CHOKES.**—10H 60 m.A., 4/-; 5H 200 m.A., 7/6 (post 1/-).

Open until 11 p.m., Saturdays, we are 2 mins. from High Holborn (Chancery Lane Station) 5 mins. by bus from King's Cross. Cash with order, please, and print name and address clearly. Includes postage and carriage on all items

**U.E.I. CORPN. THE RADIO CORNER, 138, GRAY'S INN ROAD, LONDON, W.C.1 (Phone TERminus 7937.)**

The



## ELECTRONIC TESTMETER

This instrument has been developed to meet the growing demand for an instrument of laboratory sensitivity built in a robust and portable form, for use in conjunction with electronic and other apparatus where it is imperative that the instrument should present a negligible loading factor upon the circuit under test.

The instrument consists basically of a balanced bridge voltmeter. It incorporates many unique features and a wide set of ranges so that in operation it is as simple to use as a normal multi-range testmeter.

The instrument gives 56 ranges of readings as follows:—

**D.C. VOLTS :** 2.5mV. to 250 V. (Input Resistance 11.0 megohms.)  
25mV. to 10,000V. (Input Resistance 110.0 megohms.)

**D.C. CURRENT :** 0.5 $\mu$ A. to 1 Amp. (250mV. drop on all ranges.)

**A.C. VOLTS :** 0.1V. to 2,500V. R.M.S. up to 2 Mc/s. With diode probe external 0.1V. to 250V. R.M.S. Useful measurements can be made up to 200 Mc/s, the applied voltage being limited to 100V. above 50 Mc/s.

**A.C. OUTPUT POWER :** 5mW to 5 watts in 6 different load resistances from 5 to 5,000 ohms.

**DECIBELS :** -10db. to +20db.

**CAPACITANCE :** .0001 $\mu$ F. to 50 $\mu$ F.

**RESISTANCE :** 0.2 ohm to 10 megohms.

**INDUCTION :** 0.1 megohm to 1,000 megohms.



List Price:

**£10** Size 12 $\frac{1}{2}$ ins. x 9ins. x 5 $\frac{1}{2}$ ins.  
Weight: 12 $\frac{1}{2}$ lbs.

The instrument operates on A.C. mains, 100-130V. and 200-260V., 50-60c/s

Write for fully descriptive pamphlet.

The instrument is quickly set up for any of the various tests to be undertaken, a single range selector switch automatically removing from the circuit any voltages and controls which are not required for the test in question.

Sole Proprietors and Manufacturers:

### THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. Ltd.

Avocet House, 92-96, Vauxhall Bridge Road, London, S.W.1

Phone: VIctoria 3404-9

E.T.M.3

## OSMOR VARIABLE Band I ATTENUATOR

Enables reception of ITA and BBC in all areas and avoids constant adjustment of controls. The Osmor is the only variable attenuator that will reduce the signal exactly to the required level. Easily Fitted—just plug in. Reduction ratios variable 2-1 to 10-1. An Essential with all types of Band III Converters. 10/-, plus 9d. p. & p. From your Dealer—or direct.



## BAND I FILTER

Rejects BBC from ITA aerial and improves picture. Suitable for all makes. Fitted in 2 minutes. 10/-, plus 6d. p. & p. including instructions.

## ITA CONVERTERS LONDON · LICHFIELD · MANCHESTER

A very efficient Band III Converter for all TV sets of any age (including TRF). Approximately one hour to build! Guaranteed no breakthrough of Band I. Will convert any Band III Channel to any Band I Channel. Station switching. A.C. or A.C./D.C. Size 4 $\frac{3}{4}$ in. x 2 $\frac{1}{2}$ in. x 3in. Circuits, Wiring Diagrams and full constructional information, ready to fit inside your TV cabinet.

Complete Kit **65/-** Completely wired **80/-**  
Both plus 2/- post and packing.

**FREE** We keep right up to date in building the latest circuits published in "Practical Wireless," "Wireless World" and "Radio Constructor" and we stock the components specified. Send 7 $\frac{1}{2}$ d. in stamps for circuits, fully descriptive literature together with coil and coilpack leaflets, component lists, chassis drawings and templates.


## ITA Band III CONVERTER KIT

Complete with all components, including power unit, for construction of an efficient Band III converter. Nothing else to buy. Circuit, wiring diagram, chassis templates and complete instructions, **£6.19.0.**

plus 2 6 p. & p.

**OSMOR RADIO PRODUCTS LTD.** 418 Brighton Road, South Croydon, Surrey. Croydon 5148-9

Dept. PT4.

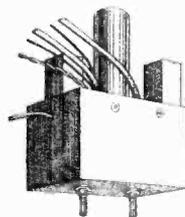

**NEW!**

**EXPERIMENTAL KITS**  
*in Radio, T.V. etc*

**LEARN THE PRACTICAL WAY**

Specially prepared sets of radio parts from which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at a Very Moderate Cost.


**EASY TERMS FROM 15/- A MONTH**

With these outfits, which you receive upon enrolment, you are instructed how to build basic Electronic Circuits (Amplifiers, Oscillators, Power Units, etc.) leading to complete Radio and Television Receiver Testing and Servicing.



**TELEVISION**—With this equipment you are instructed in the design, construction, servicing and testing of a modern high quality Television Receiver.

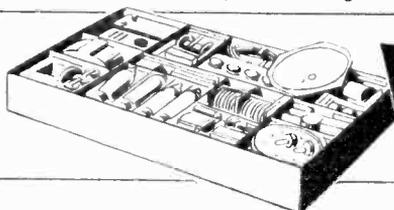**ALL EQUIPMENT SUPPLIED IMMEDIATELY AND REMAINS YOUR PROPERTY**




**BEGINNER'S RADIO OUTFITS**

— For carrying out basic practical work in Radio and Electronics, from first principles and leading to the design and building of simple Receivers.

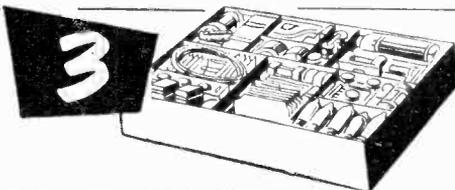**ADVANCED RADIO OUTFITS**

— With this equipment, you are instructed in the design, construction, testing and servicing of a complete modern T.R.F. and Superhet Radio Receiver.



**OTHER COURSES WITH OUTFITS INCLUDE:**

**MECHANICS • ELECTRICITY  
CHEMISTRY • PHOTOGRAPHY  
CARPENTRY**

**ALSO DRAUGHTSMANSHIP • COMMERCIAL ART  
AMATEUR S.W. RADIO • LANGUAGES • ETC.**

**POST THIS COUPON TODAY**

Please send me your FREE book on Practical Courses: I am interested in Television , Radio: Beginners , Advanced , Other subjects

(Please indicate Item(s) required)

To: E.M.I. INSTITUTES, Dept. 138x, Grove Park Road, London, W.4.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_



NOV.

**E.M.I. INSTITUTES**

The only Postal College which is part of a world-wide Industrial Organisation

# CERAMICS

## for all electronic applications

Silvered Ceramic Condensers cover a variety of useful shapes, including Pearls, Discs, Beads and Tubes, and have many applications in R.F. circuits — particularly where ultra-high frequencies are present, when their low inductance and excellent power factor are of special advantage. A wide choice of negative and positive temperature co-efficients permits the temperature compensation of other components, and frequency stabilisation of tuned circuits.

### Hi-K CERAMIC DISCS

for decoupling purposes in T.V. and spark suppression in small electrical apparatus—extremely low inductances. Up to 10,000 pF at 500 v. D.C. working. Finished in a moisture-resisting compound that does not soften or crack up to 100°C.

### LOW-K TUBULARS


with the choice of four temperature co-efficients and a wide range of capacity values, serve many purposes in general circuitry.

### Hi-K TUBULARS

combine high capacity with small physical size: used widely as by-pass condensers in T.V. and other H.F. receivers where low inductance is of special value.
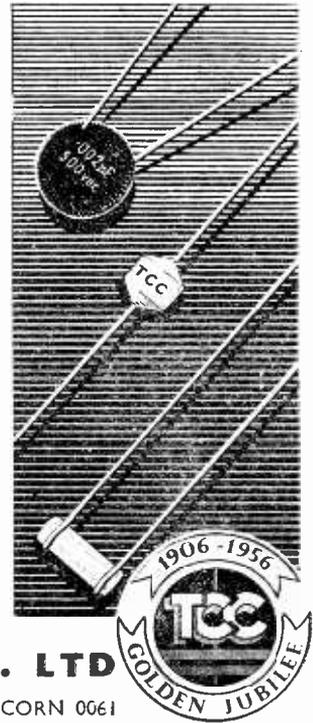
### LOW-K PEARLS

of up to 10 pF capacity and **LOW-K DISCS** of up to 50 pF. with high negative temperature co-efficient permitting compensation of other components and frequency stabilisation in tuned circuits.



## THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION: NORTH ACTON • LONDON • W.3 • Telephone: ACORN 0061

## PREMIER RADIO COMPANY

OPEN TILL  
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.) 207, EDGWARE ROAD, LONDON, W.2



Telephone :  
AMBASSADOR 4033  
PADDINGTON 3271

# SAFETY FIRST!

Build these PREMIER TELEVISORS

WHICH GIVE  
COMPLETE SAFETY  
TO THE CONSTRUCTOR

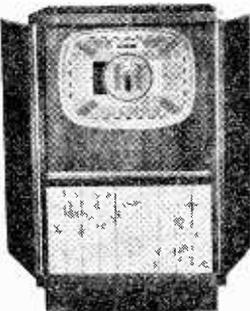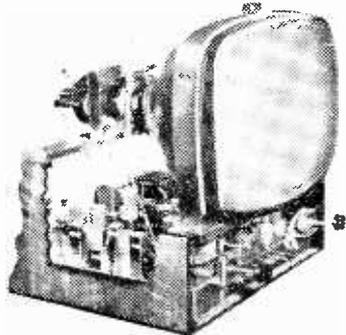These Televisors use a double wound mains transformer which gives you complete safety from contact with the mains supply when handling the chassis or controls.



★ ALL CHANNELS BBC & I.T.A. DESIGN NO. 1. MAY BE BUILT FOR £32.7.11 PLUS COST OF C.R.T.

★ 5 CHANNELS BBC DESIGN NO. 2. MAY BE BUILT FOR £27.9.4 PLUS COST OF C.R.T.

CONSOLE CABINETS with full length doors for 14in., 16in. and 17in. tubes. PRICE £14.14.0. H.P. Terms: Deposit £7.7.6 and 9 monthly payments of 18/6. CONSOLE CABINETS, half door, still available at £12.12.0. H.P. Terms: Deposit £6.6.0 and 8 monthly payments of 18/3.

On above cabinets add 21/- for pkg. and carr.

BUILD IN 5 EASY STAGES. FULL CONSTRUCTION DETAILS AVAILABLE INSTRUCTION BOOK 3/6 POST FREE INCLUDES BOTH DESIGNS.



# Practical Television



## & TELEVISION TIMES

Editor : F. J. CAMM

Editorial and Advertisement Offices : " Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2, 'Phone : Temple Bar 4363. Telegrams : Newnes, Rand, London.  
*Registered at the G.P.O. for transmission by Canadian Magazine Post.*

Vol. 7 No. 76

EVERY MONTH

NOVEMBER, 1956

## TelevIEWS

### THAT VACANT TV HOUR

**T**HERE are no TV programmes, either BBC or I.T.V., between the hours of six and seven in the evening. The official reason given is that Children's Hour finishes at six o'clock and the hour before programmes start again gives parents the time to put their children to bed. This shows how out of touch the authorities are with modern times. Children may have been put to bed 50 years ago, when children were expected to be seen and not heard, but children are certainly not put to bed nowadays at the absurd hour of six o'clock, excepting, of course, very young children, who would not be interested in TV anyway. Presuming, however, that parents are still so Victorian as to send their children to bed at six o'clock, that is no reason why the programmes should cease, if parental control means anything at all.

Not so long ago the complaint was made that TV programmes were interfering with children's homework. Most children to-day do their homework in the evening and after six o'clock. We suggest that this vacant hour should be made use of.

### PROJECTION TV

**T**HE Radio Show this year showed a marked decline in the number of projection receivers on show. It would be a pity if this type of receiver disappeared from the market, for it has undoubted advantages which more than outweigh the main disadvantage that the picture must be viewed "square on," and presents a blurred image if viewed at an angle. The public is demanding a larger picture, and the C.R.T. has already, in our view, reached a practical limit. As the Bell Laboratories have claimed to have invented a method of amplifying light, perhaps a fresh fillip will be given to

projection TV, on which at present brilliance is reduced as the size of the picture is increased.

### TV IN TRAINS

**F**OR the first time in the history of TV it has been installed in a train. Two excursion trains from Glasgow to Oban were so equipped with a closed-circuit TV system, the guard's van being turned into a studio feeding two 17in. TV receivers in every 64-seater carriage. This was on September 24th. The studio was equipped with a miniature industrial TV camera, which from time to time televised the Highland scenery, whilst a commentator pointed out landmarks of particular interest. The passengers on the return journey changed trains so that they could see the alternative programme.

### " UNSIGHTLY " TV AERIALS

**T**HE Town Planning Committee of the London County Council is concerned at the unsightly appearance of television aerials in residential areas. It adds the rider that " at this stage, public opinion would not be favourable to the council's seeking new powers of control over their erection on private property." On the contrary, we think that the power should be taken away from all councils to interfere in this matter or to make regulations concerning it. It would be a further unwarranted interference with the liberty of the subject.

### I.T.V. IN YORKSHIRE

**T**HE new I.T.V. station at Emley Moor will commence broadcasting regular programmes on November 3rd, and it will make I.T.V. available to about 5,000,000 people in Yorkshire, Lincolnshire, Nottinghamshire and Derbyshire. Although I.T.V. at the present time is losing money, there can be no doubt that more and more viewers are deserting the BBC programmes for I.T.V. — F. J. C.


**OUR NEXT ISSUE, DATED DECEMBER, WILL BE ON SALE ON THURSDAY, NOVEMBER 22nd.**

# A Beginner's Guide to Television

A NEW SERIES

8.—COLOUR TELEVISION

By F. J. Camm

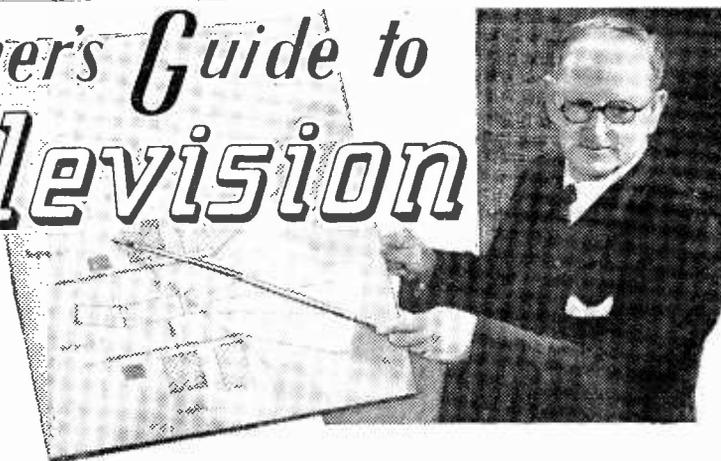

ALTHOUGH it may be some years before we have a regular colour television service in this country colour TV technique is well advanced. The exact date of the commencement of such a service is dependent not so much upon technical development as upon finance and trade policy. Naturally, manufacturers of monochrome TV receivers are not anxious to disturb production by encouraging the public to believe that colour TV is imminent. Nonetheless, it is well that we should understand something about it in readiness for the day when TV emulates the films.

Now before we can understand colour TV it is necessary to know something about the spectrum. In Fig. 31 I have shown a diagram of the visible and invisible spectrum with corresponding types of rays and approximate wavelengths. We all know that we only see anything by virtue of the light which it reflects and that it is impossible, even for a cat, to see in complete darkness. The commonly held belief that a cat can see in the dark cannot be substantiated, although it is possible that it can see better in a darkened room than a human being. The source of all natural light is the sun, and the emissions from the sun are considered as white light, and by this is meant the colour of light which does not appear as any of the colours in the visible spectrum, such as the colours seen in a rainbow. It was Newton who demonstrated that when a beam of white light is projected through a glass prism, and the light which has passed through is projected on to a white screen, a series of coloured bands appears on the screen and they appear in this order: red, yellow, green, blue-green, blue, and violet. These are, indeed, the colours of the rainbow. Each of these colours has a certain frequency and wavelength, and they therefore have electro-magnetic energy. It may be said, to put it another way, that each band of colour embraces a band of frequencies and wavelengths. To be more specific, the blue band, which, of course, includes violet and some of the blue-green, extends from 400 to 510 millimicrons approximately, and the green band, inclusive also of some of the blue-green, extends from 510 to 580 millimicrons, whilst the yellow band extends from approximately 580 to 600 millimicrons. Finally, the red band, including the orange, extends from 600 to the practical limit of 700 millimicrons. Beyond the red at one end there are, however, the infra-red rays,

and beyond the violet the ultra-violet rays. These are rays beyond the scope of the retina of the human eye, just as certain sounds are beyond the aural frequency of the human ear.

The separation of these colours by means of a prism is due to the phenomenon known as refraction, and the refraction will, of course, depend upon the substance. In the case of glass, for example, which is a solid, if light strikes a surface at right angles (90 deg.), the light will be slowed down at each edge of the ray and the direction of the light is not affected. At any other angle, however, the ray is bent. This is because the right-hand edge of the ray strikes the surface before the left-hand edge. The glass, therefore, slows down the right-hand edge and this portion of the ray can travel only a certain distance, whilst the left edge in air will travel a greater distance.

It will thus easily be seen that by the time the whole ray has penetrated the solid material what may be termed the wavefront of the ray is bent, and a similar state of affairs exists when the ray leaves the material, but the bending in this case is in the reverse direction, because the ray is proceeding from solid to air instead of from air to solid. What may be termed the departing ray can be bent or deflected in relation to the entering ray by using a prism of triangular section. As a result of the different angles of the surfaces of a prism, the ray is bent the same way in both cases, but it is important to note that the ray is always bent towards the normal in entering the solid and away from the normal when it is departing.

The greater the ratio of the velocity in air to

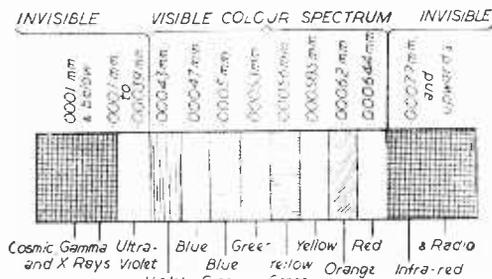


Fig. 31.—The visible and invisible spectrum with approximate wavelengths in mm.

velocity in the solid, the greater will be the bending and the deviation, and this velocity ratio for a particular solid and for a given light wavelength is known as the index of refraction, a term you will often see quoted in books on telescropy, microscopy, optics and spectroscopy.

The important thing to remember, however, is that each colour has a different index of refraction in relation to a particular solid, and light rays of different colours which enter a solid at the same angle will depart at different angles.

Light, as we have seen earlier, is a combination of the light of different colours, or wavelengths, and when these enter the prism at the correct angle the light of each different colour will leave the prism at a different angle.

We have all at some time spun a disc containing the colours blue, red and yellow, and found that when spun they appear white. An examination of the visible spectrum shows that blue, green and red occupy by far the greatest part of it, and that blue-green, yellow and orange form a comparatively small region of the spectrum.

From this basic fact emerges the basis for colour television. For colour television the spectrum may be simplified and considered as extending from blue, through blue-green, green, orange-yellow to red, embracing the band of frequencies from 400 to 700 millimicrons. It would be practically impossible to devise a TV colour system which would embrace the whole of the visible spectrum. As with colour films, which will never look quite the same as the natural objects shown, so with TV. It cannot be expected because of the limitations to which I have referred that the pictures will be represented in really natural colours. Newton demonstrated that he could produce white light by reversing the prism procedure. He passed the visible spectrum through one prism, through a second prism and thus was able to show a band of white light on the screen.

Now, due to the optical limitations of the human eye, the sensation of white light can be created in the

mind of the viewer by a sort of mental illusion. That is, by combining only three colours in the proper proportion. These are blue, green and red lights, which are the TV primary colours.

We know that by combining these three primary

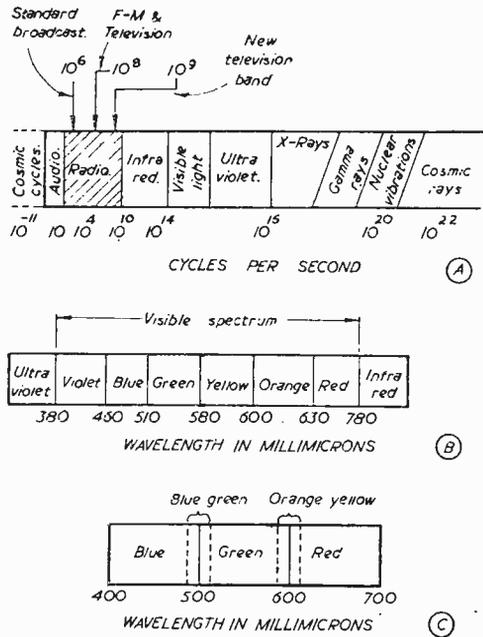


Fig. 32.—The complete electromagnetic spectrum (a); the visible spectrum (b) and (c) simplification for colour television.

colours in other than equal proportions, or indeed, any two of them, a much wider variety of other colours can be seen by the viewer. It is, then, the colours of blue, green and red which are used in the colour television system in use to-day.

To give a technical name to it, the phenomenon that a particular colour can be matched by a proper combination of the three primary colours is known as trichromatic vision. Opticians tell us, although there is some doubt about it, that within the mechanism of the eye there are three receiving devices and each is capable of responding to the colours of all wavelengths, and one of these devices is more responsive to blue, another to green and the third to red; and when the eye sees a particular colour, these three devices respond according to the colour value—or the respective wavelengths to which it is responsive. I have mentioned earlier that we see all objects by the reflection of light and we see all coloured objects by reflection of the colour rays and also by the projection of them. A simple experiment will demonstrate what is meant. If all the colours of the rainbow are projected on to a screen and a piece of red cloth is held in front, it will appear to the eye as black or brown, except when it is placed in front of the red colour area of the projected spectrum. This is because the red cloth is only reflecting the red colour radiations in the light that impinges on it, but is absorbing the radiations of the other colours.

Now when the piece of cloth appears brown to the eye it is because of the reflection of the colour radiations

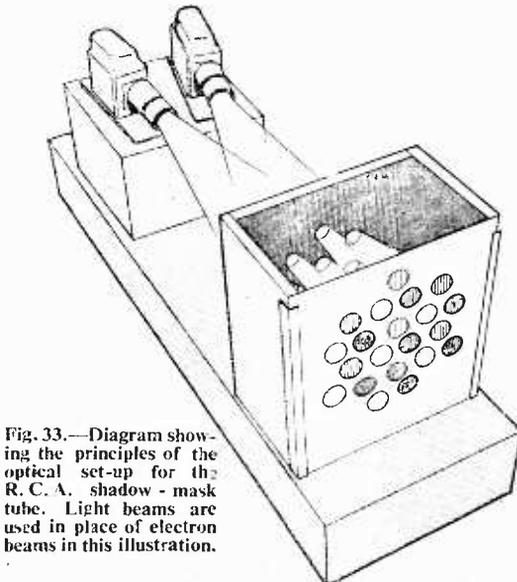


Fig. 33.—Diagram showing the principles of the optical set-up for the R. C. A. shadow-mask tube. Light beams are used in place of electron beams in this illustration.

tions which, to the eye create the colour sensation of brown. It is for these reasons that colour matching should never be undertaken in artificial light.

Another important fact. A white object appears white to the human eye only when it is viewed in a pure white light. In those circumstances it reflects all of the wavelengths radiated by the light source, but when viewed in a light which does not contain the full range of colours in the visible spectrum any white object will appear as the colour corresponding to the wavelengths present in the source of light radiation. This does not apply, of course, to black, which appears as black under white light and, indeed, will remain black under all colours of light. This is because black objects absorb all visible light rays, but do not reflect any of them. Black, therefore, may be said to be due to the absence of reflected light rays. Many systems of projecting colour TV pictures have been tried from the time that Baird first demonstrated that colour TV was possible. One method which has been successfully demonstrated is to generate radiations corresponding to certain wavelengths and, therefore, of certain colours from self-luminant sources. Sodium vapour light is one such source and it produces a yellow light. The argon tube, when the cathode is connected to a source of electrical energy, will produce a blue or purple light, and there are many other different kinds of gases which are capable of radiating wavelengths which correspond to different colours. Neon will radiate an orange colour, but it must be appreciated that the band of wavelengths in radiations from these sources is quite limited.

The tricolour picture tube is, in effect, a generator of colour. Its screen contains red, green and blue phosphors, and these are excited as with ordinary monochrome TV by the electron beam. Each of the phosphors will radiate light of its own colour. The quantity of light radiated from each of the phosphors is electronically controlled so that the emitted light in combination forms the composite colour of the object being scanned in the television studio.

Another system of colour projection makes use of a white light source, in turn followed by a colour filter.

In colour photography, filters are used in front of the lens so that only the light which passes through the filter is impressed on the negative, and each filter will allow only the desired colour to pass through it, absorbing all the other colours. Indeed, the traffic lights of red, amber and green are simple examples of the use of colour filters. The source of light in

each case is white, but the motorist only sees the light which passes through the filter or coloured glass, and it absorbs all the other colours. One system of colour television which may be considered as a mechanical system makes use of filters, but it has not been found successful. The system which has most favour and appears, to be the one most likely to be used makes use of three cameras for red, green and blue respectively which separate the colours reflected from the object being scanned into the three primary colours. As with ordinary TV each camera will deliver its own signal voltage, corresponding to the colour passed by its filter, and these signals pass through the TV network in the ordinary way.

I said earlier that the three primary colours are red, blue and yellow, but in TV they must be considered as red, green and blue. The R.C.A. colour television system which is used in America and is likely to be used over here, is shown diagrammatically in Fig. 34. As shown in the diagram, light coming from the scene being televised passes into the R.C.A. colour camera and then through a series of mirrors to the camera tubes. These mirrors have the property of "splitting" the light from the scene into three components—blue, green and red. Each mirror reflects one of the components of the light, while passing the other components, thus separating the light into three colours.

Each primary colour is directed to one of the camera tubes. The pictures are then simultaneously scanned by electron beams, a process in which each image is dissected into 525 horizontal lines. This scanning procedure is repeated 30 times a second. The output from the camera consists of three simultaneous high-definition television picture signals—each representing one of the three colours.

The signals leaving the camera are made up of elements representing both black-and-white and colour pictures. The black-and-white portion of these signals represents the very fine detail of the scene being televised. At the same instant the three colour signals are processed electronically to make it possible for them to be transmitted in the standard television channel. Once this has been done to the colour signals the black-and-white picture is added and the result is a video signal which is in full colour and high in picture detail.

The video signal is sent to a standard television transmitter which is the same kind of transmitter used for standard black-and-white television broad-

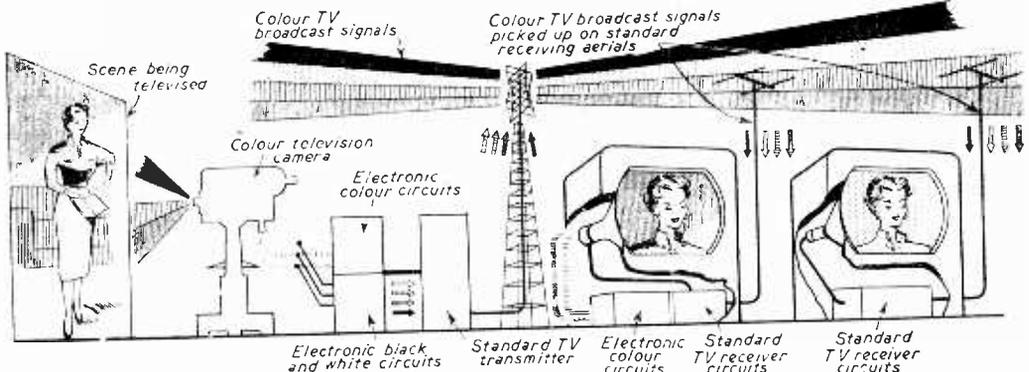


Fig. 34.—How the colour system used by R.C.A. is used to pick up a signal and reproduce it in either colour or black and white.

casts. The signal is then broadcast for reception in the regular manner. The channel width—6 Mc/s—is the same as the standard black-and-white television channel. Hence, the standard television channel may be used to transmit either black-and-white television or R.C.A. colour television.

R.C.A. colour television signals can be received in one of three ways: 1, they can be received in colour on colour television receivers; 2, they can be received in colour on converted black-and-white receivers; or, 3, they can be received as standard high-quality black-and-white pictures on ordinary receivers without any modification. In each case all-electronic equipment is used throughout. Fig. 34 shows how R.C.A. colour television signals are reproduced in black and white on a standard unmodified black-and-white television receiver. This illustrates the compatibility of the system.

Fig. 34 also illustrates how R.C.A. colour television signals are reproduced in colour. This applies

to both a colour television receiver and a black-and-white receiver converted for colour. As shown in the diagram, the incoming television signal passes through standard television receiver circuits and then through colour circuits to the tricolour picture tube on which a full-colour high-definition picture is reproduced. As in black-and-white television, the size of the picture is determined by the size of the tube. The R.C.A. colour system can use any size picture tube.

Several development models of R.C.A. colour television receivers have been produced and demonstrated. One model uses the 16in. R.C.A. direct-view tricolour kinescope. Another modulates a 21in. tube. The screen of the colour picture tube is composed of hundreds of thousands of dots of red, green and blue light-producing phosphors. These dots are arranged in groups of three and so positioned that the electrons from each of the three electron guns always hit the dots of their own colour. The phosphor dot groups are so small and so close together that

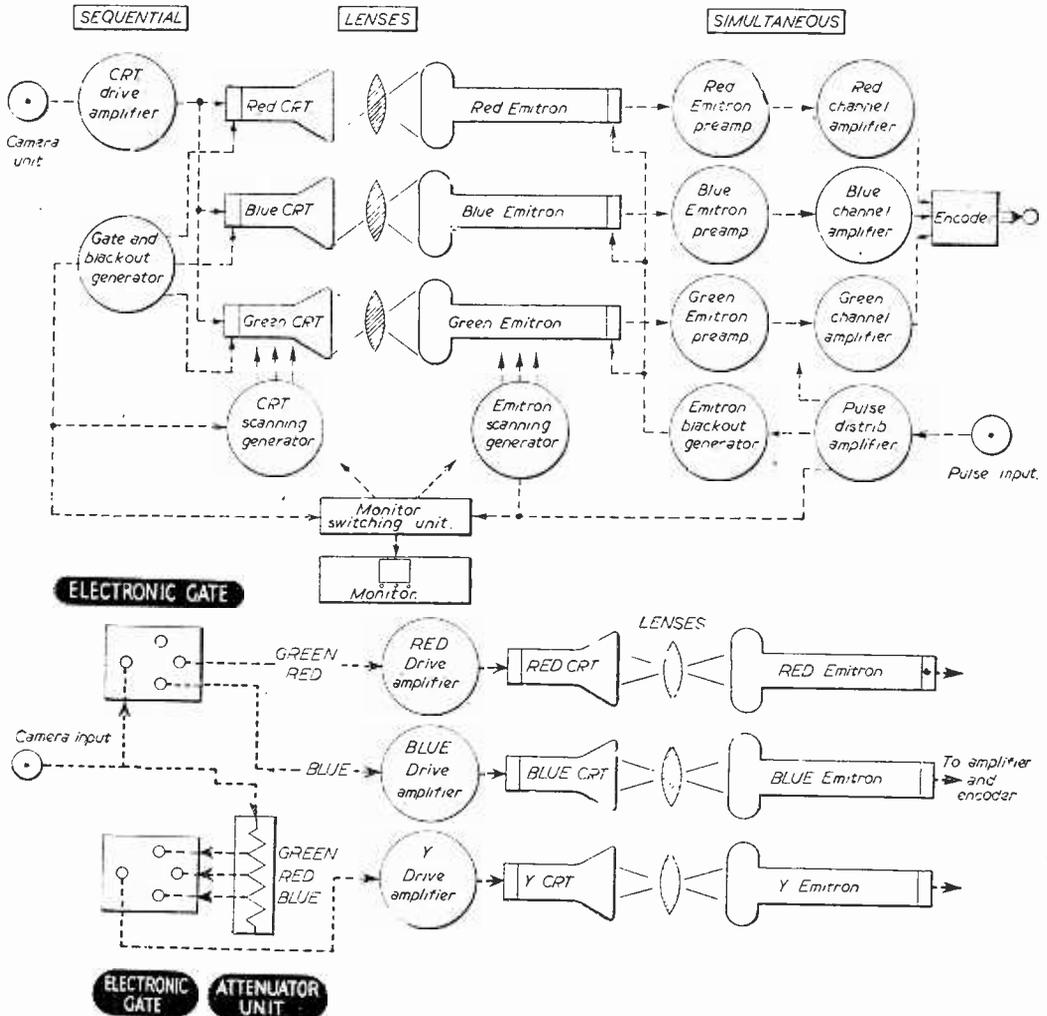


Fig. 35. — Schematic layout of the E.M.I. chromacoder, and below the modified R.Y.B. colour scheme.

when activated by the electron streams they present a continuous smooth full-colour picture.

The reception in colour on a converted black-and-white receiver is identical with the foregoing. In this case the colour television tube is used instead of a

and they must make use of scanning rates which are not the same as those used in black-and-white television and such pictures cannot be received on standard black-and-white receivers unless costly alterations are made to the set. Even then the

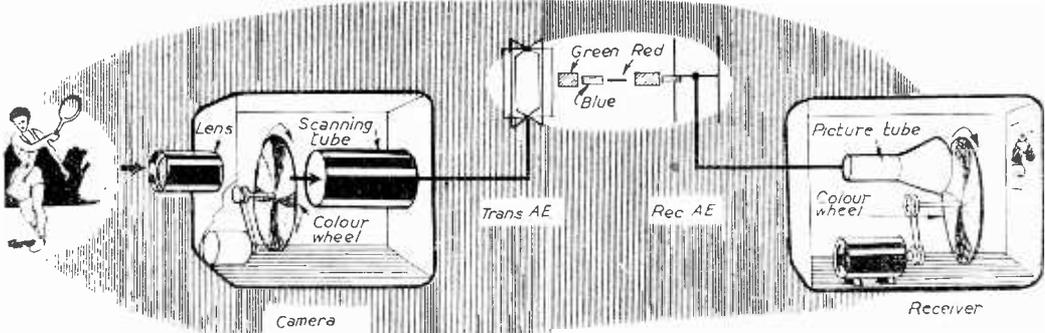


Fig. 36.—A disc colour system as used by the C.B.S. of America.

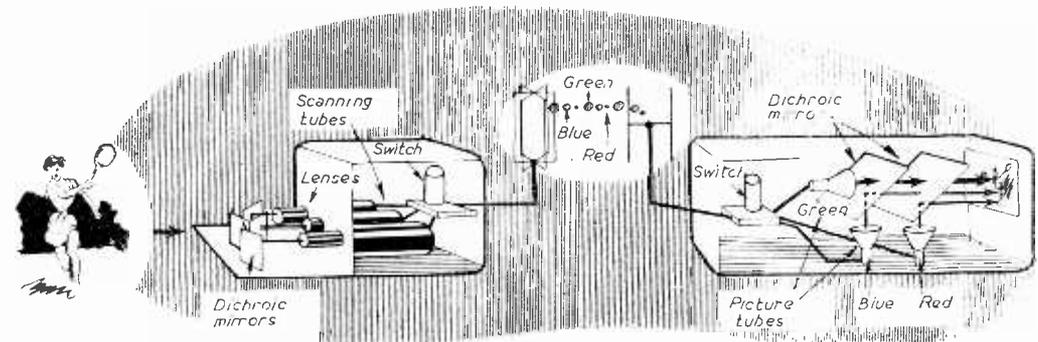



Fig. 37.—The dichroic mirror system of the R.C.A.

black-and-white C.R.T. The necessary circuits are added to the black-and-white receiver. After a set has been converted to colour black-and-white television pictures can still be received from those stations transmitting in black and white and viewed on the tricolour tube as high-quality black-and-white pictures (Fig. 33).

Other systems produce pictures with poor detail

picture has less than half the detail or sharpness of the present black and white. The system just described, however, provides a picture of the same detail as the standard black-and-white picture. It can use the same scanning rates as in black-and-white television and it will give a high-quality black-and-white picture on standard television receivers without any modification. (To be continued)

Fig. 38.—Diagrammatic representation of the R.C.A. single screen system of television. The screen is built up from a mosaic of dots of three phosphors, viz. (1) zinc orthophosphate activated with manganese which gives a red colour, (2) Zinc sulphide activated with silver, which gives a blue colour, (3) Zinc orthosilicate activated with manganese, which gives a green colour, are assembled in such a manner that the beam from each falls only on the dots of one phosphor throughout each complete scan.

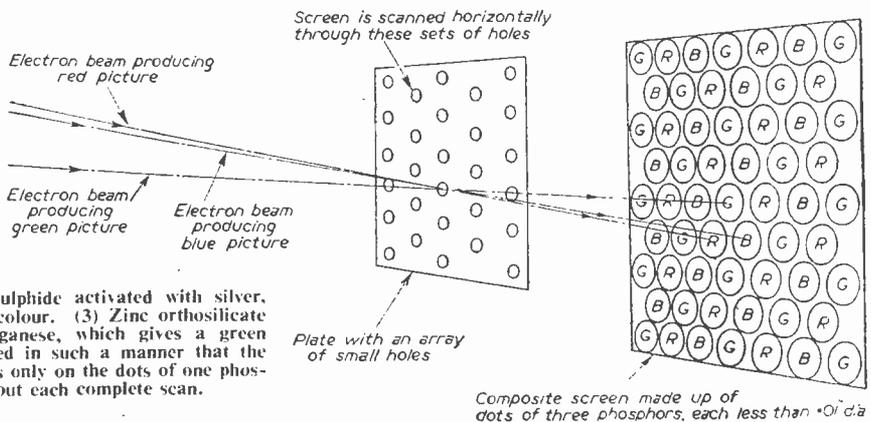

# HOW TO USE AN OSCILLOSCOPE

## HOW TO UNDERSTAND AND EMPLOY THIS VALUABLE SERVICING ACCESSORY

By J. Hillman

(Continued from page 118 October issue)

### Sensitivity

**T**HE sensitivity of all British C.R.T.s is given as mm/VA3 and in the case of the VCRI39A this is 170 mm/VA3. VA3 is the final anode voltage, and unless this is accurately known the exact sensitivity figures given by the makers cannot be checked. However, to the service engineer, the main thing to know is what voltage input will produce a given height of trace. First set up circuit as Fig. 17. Where V is an A.C. voltmeter or multimeter switched to its A.C. range. Connect output terminals A and B to the Y output terminals of the oscilloscope; set Y amp switch to direct; timebase off, i.e., range 6; sync S.W. to ext. Set VR1 to give 50 volts on A.C. meter, and measure height of trace which will be a vertical line. In my oscilloscope this was 47 mm, and sensitivity is 50 volts for 47 mm. However, this voltage is the R.M.S. voltage and the oscilloscope measures peak to peak voltage, and so it is desirable to work with this value. With 50 volts R.M.S. the peak voltage is  $\sqrt{2} \times 50$  peak volts, and  $2 \times \sqrt{2} \times 50$  peak to peak volts which is  $2 \times 50 \times 1.414 = 141.4$  volts. The sensitivity is then 47 divided by 141.4 or 0.33 mm/V. If this is checked at 20 volts, the line is 21 mm, giving  $2 \times 20 \times 1.414$  or 56.5 peak to peak volts and this gives sensitivity as 21 divided by 56.5 or 0.37 mm/V.

Similarly for 60 volts line is 55 mm giving  $60 \times 2 \times 1.414$  or 170 P.P. volts and sensitivity is then 55 divided by 170 or 0.32 mm/V. You will notice that the sensitivity values seem to vary for different voltages. This is due to errors in the voltmeter, and it is best to use the highest range of the meter and to get the reading near the full scale reading in order to ensure accuracy. It is best to take several readings and take the average figure as the sensitivity of the tube. Now connect A and B to the X output socket and measure the sensitivity of the horizontal plates. With this test it is better to connect direct to the X plates, and for this purpose my oscilloscope has a socket fitted on top of the C.R.T. partition, and a 0.5  $\mu$ F condenser connects this to pin 7 of the C.R.T. The sensitivity should be approximately the same

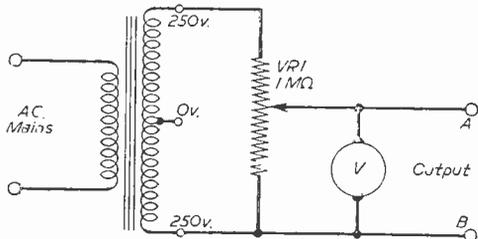


Fig. 17.—Circuit for sensitivity checking.



On the right is the 'scope which was described in our May and June issues.

for both X and Y plates. The X amplifier can be checked by first measuring the sensitivity of the direct X connection and then changing to the X ext. socket and putting the X amp control to maximum, and the amplification should be just over eight times. A point of interest in regard to the published figures of sensitivity of C.R. tubes is the relation between


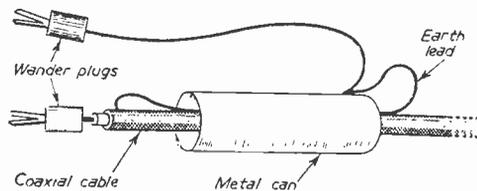


Fig. 18.—Simple screened connector.

the sensitivity and the final anode voltage. The formula used by British manufacturers is  $S=K$  divided by VA3. Where S is the sensitivity and VA3 is the final anode voltage whilst K is a constant. From this it will be seen that the higher the anode voltage the less sensitive the tube becomes, so that for service work it is preferable to keep the anode voltage as low as possible and so get a more sensitive oscilloscope. Of course, there is a limit to the voltage, as the brightness of the trace depends on this voltage. Another advantage of using a low anode voltage is that the life of the tube is increased.
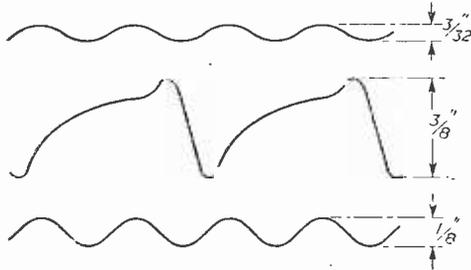
### Checking Hum


First check the hum level with the coaxial lead not connected to the set and with the Y amp switch at high; range 1; Y amp maximum; X amp 4;



Figs. 19, 20 and 21.—Oscillograms referred to on page 160.

X and sync switches int.; beam blanking hard. There should be no trace of hum, and the trace should be a straight line, but as the amplification of the oscilloscope is high some precautions need to be taken in the lead used. The connections at the oscilloscope end are by means of wander plugs and some hum pick-up can occur unless the plug is screened completely as Fig. 18.

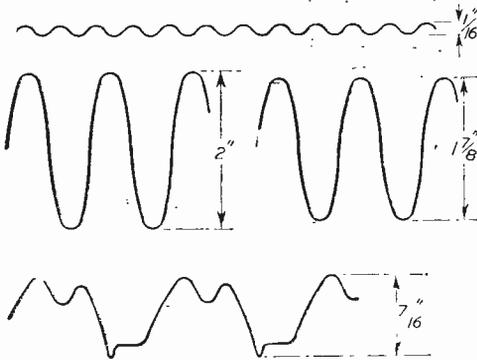The metal case can be made from the top of an



Figs. 22, 23, 24 and 25.—Further Oscillograms.

old pen torch and the metal braid of the coaxial cable is soldered to a lead which passes through the case, allowing sufficient slack for tube to slide far enough back to connect the wander plugs. This lead is then soldered to the case, together with another lead terminating in a wander plug. In checking hum level in TV sets connect Y out to cathode of C.R.T. or grid, whichever is being modulated and earthed to chassis, and in radio sets connect Y out to L.S. and earth lead to chassis, and with controls set as previously stated line of trace should be fairly straight. With a PAM751 model the line was as Fig. 19, and no hum was visible on the screen of the set. With a G.E.C. BC5442 trace was practically a straight line, and very faint hum could be heard in background, whilst with the scope connected to the reservoir condenser and controls set range 1, Y amp low, Y amp 3, X amp 4 fine frequency 25 cps, the trace was as Fig. 20. With a Columbia C301 A.C. radio

the trace was as Fig. 21 when connection was made to H.T. + with controls set as follows: Range 1, I amp high, Y amp max., X amp 4. With the same settings but with the lead connected to reservoir condenser trace was as Fig. 22. The hum was audible in the set and, after replacing the two condensers, the trace was as Fig. 23. For H.T. +, and as Fig. 24 for reservoir condenser, and hum was not audible now.

#### Sound Waves

Sound waves can be seen if a microphone is connected to the Y out socket and earth, and with Y amp max., Y amp high, X amp 4, range 1. Fine frequency 7. X and sync int. beam blanking hard;

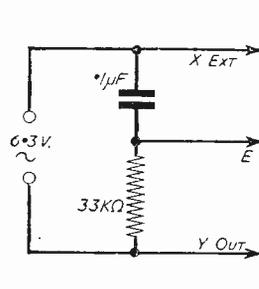


Fig. 26.—Circuit for checking phase displacement.

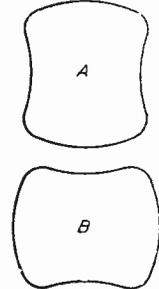


Fig. 27.—Oscillograms showing phase displacement.

on speaking into the microphone vibrations will appear on the trace. If the sound is a pure note a single trace will appear, but if harmonics are present there will be several traces. The audio note from a signal generator will appear as Fig. 25.

#### Phase Displacement

Using an external 6.3 volt A.C. source connect up circuit as Fig. 26, and set controls as follows: Range 6; X ext.; Y amp high; Y amp 4; X amp 6; beam blanking hard; sync int. Trace A Fig. 27 should now appear. Now reverse connections E and Y out, and trace should appear as B Fig. 27, showing a 90 deg. displacement.

(To be concluded)

## Syria Sees Live TV

**A**FTER three weeks' concentrated work in building and installing equipment into a specially constructed studio, Pye Limited of Cambridge, England, have transmitted the first "live" television programmes to be seen in Syria. The first pictures were seen during the evening of the 1st September, when the President formally opened the Fair.

A considerable number of receivers, belonging not only to Pye, but also to manufacturers from several other countries, had been installed in different parts of Damascus, as well as in Pavilions at the Fair. Among those which had been distributed by Pye were sets for leading Government officials, hotels, clubs, shop windows, bazaars and cafés.

The first programme to be transmitted was a press conference and reception for Damascus journalists, televised from the studio. At it, the journalists were encouraged to ask questions of a general nature


on the subject of television which they thought would be of interest to the public watching the conference. This was followed by a cabaret by Syrian artists.

The most up-to-date equipment had been installed in the Damascus studio and it incorporated all the latest modern developments. There were three television cameras, as well as a unit of telecine capable of transmitting either 35 or 16 mm. films. An outside broadcasts van, completely air-conditioned, acted as a control room and was parked immediately outside the studio with a connecting window for the producer to see into the studio. The outside broadcasts van was chosen so that the maximum mobility could be achieved in producing programmes away from the studio.

The aerial mast for the station was over 100ft. high and dominated the entrance to the British Pavilion and all the other Pavilions at the Fair. In addition to the large studio, forty-foot square, there were office and dressing-room facilities for artists taking part in the "live" programmes.

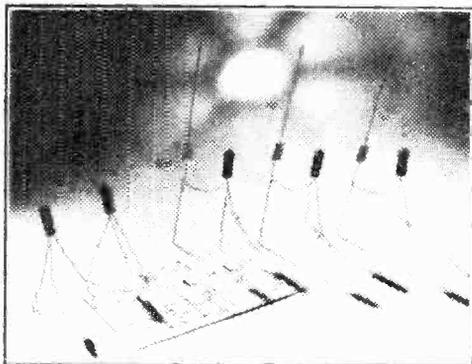
# THE TRANSISTOR STORY

A REVIEW OF THE MODERN TRANSISTOR IN PICTORIAL FORM BY MULLARDS



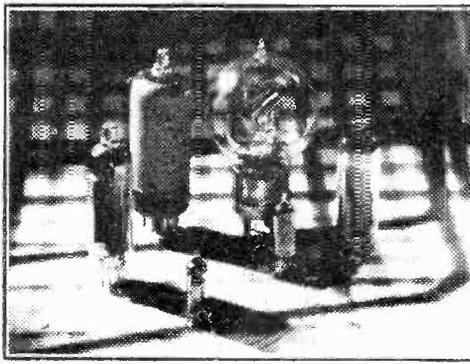
### THE STORY SO FAR . . .


Latest products of Free Space evolution; the diminutive Semicons have increased their numbers so much that they plan to take over more living space. This means trouble for the Trons . . .



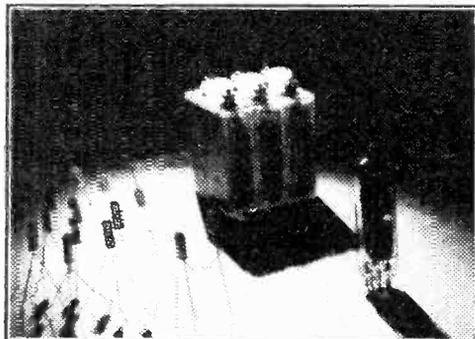
. . . who have been Lords of Free Space from the earliest times.



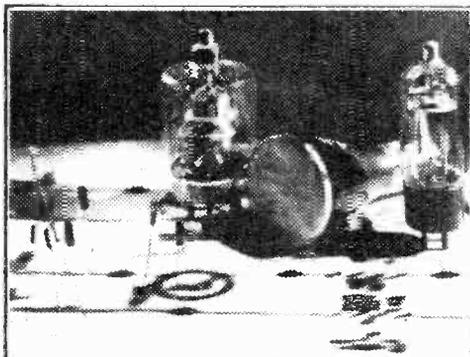
The Semicons are small, but active. More than 100 of them can keep going on the supplies needed by a single Tron.



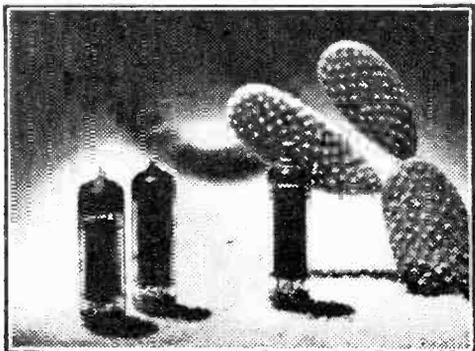Overwhelmed by armies of Semicons, some of the Trons are forced to retreat. Others are too powerful. A truce is arranged. They live together in a state of uneasy peace.



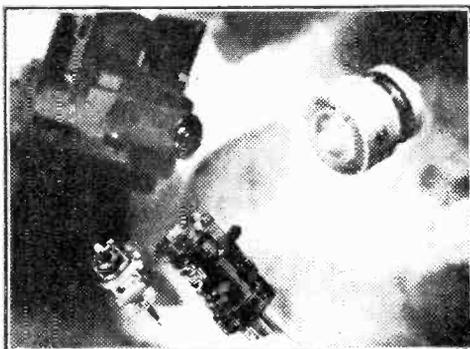
The heat of the equatorial regions is too much for the Semicons. There the Trons still reign supreme.



In the higher regions of space, too, the Semicons are no match for the specialised types of Tron which have evolved there.

READ NEXT YEAR'S THRILLING INSTALMENT

# Serviceing TELEVISION RECEIVERS

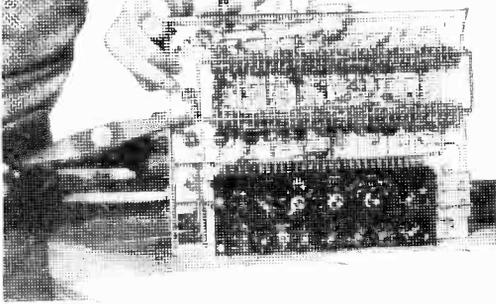

## No. 24.—THE REGENTONE 14T AND SIMILAR MODELS

By L. Lawry-Johns

AS this receiver uses a standard Plessey chassis these notes may be used in the servicing of several other receivers, including the Marconi VT63DA and various others in the De'nant, R.G.D., Argosy and Decca ranges. These are 14in. table models using a superhet circuit easily tunable with the adjustment on the rear right side of the chassis. Models marked S, L, M, W, or with no marking at all, have a vision I.F. of 14 Mc/s and a sound I.F. of 10.5 Mc/s. Models marked N (north) HM or KS have 15 Mc/s vision and 11.5 Mc/s sound I.F. tuning. Some variation may be found between various models and the focus magnet assembly may differ from our drawing. Most models are fitted with facilities for the line and frame shift, although this is not shown in the timebase drawings.

The aerial input is intended for 75 ohm coaxial cable, an attenuator being fitted in the aerial circuit marked "Distant" and "Local."

The contrast control operates on valves V1 and V3, thus its operation affects the sound volume as well as the vision. V1 is an EF80 operated as a conventional R.F. amplifier feeding vision and sound signals at R.F. to the V2 EF80 mixer-oscillator. The oscillator coil is wired in the screen grid circuit of this valve and the R.F. signals at the control grid are mixed with the screen oscillatory voltages to produce the signals at the anode at the required I.F. frequencies of sound and vision. These are tuned by the first I.F. transformer and passed to the control grid of V3 EF80, which again is common to

both sound and vision. These signals are separated at the anode circuit of this valve, the sound being fed to V6 EB180 via a 2 pF capacitor, whilst the vision signals are tuned by the vision I.F. transformer and passed to V4 EF80 control grid. Included in this circuit is the sound rejector coil which shunts signals at sound I.F. to chassis. The clear vision I.F. signals appearing at the anode of V4 are passed via the third vision I.F. transformer to the detector, which is one section of V12 EB91. The other diode section functions as the vision interference limiter. The detector diode section is that wired at pins 2 (anode) and 5 (cathode), whilst the anode and cathode of the limiter are pins 7 and 1 respectively. The detected vision signal voltages are developed across a 5.6 K and a 1 K resistor, which are wired in series from pin 5 to chassis. A test point is provided at the junction of these resistors to enable a meter to be connected across the 1 K resistor. The developed signals are passed via a resistor-capacitor filter to the control grid of V5 EF80, which is the video amplifier. Although the anode circuit of this valve is quite conventional, a single 6.8 K resistor

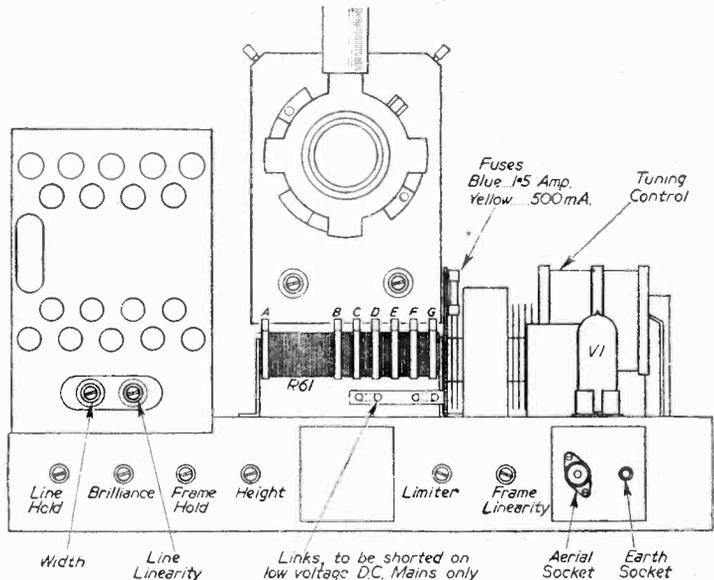


Fig. 2.—A rear chassis view.

being used as a load, the cathode circuit requires some description. Pin 1 and 3 are the common cathode connections at the valve base. From here a 2,000 pF capacitor is wired in series with chassis, whilst a 150Ω resistor is wired in series with a 180Ω to chassis with a 250 μF electrolytic shunted across the 180Ω.

The circuit is shown in Fig. 3 and it should be realised that a severe loss of vision response and sync will result if this capacitor becomes defective.

At the anode of V5 signals are fed to the C.R.T. cathode to the sync separator control grid via a 10 K resistor and a .05μF capacitor and also to the limiter diode V12B. The limiter control operates upon the anode of this diode, varying the H.T. applied to its anode. As the H.T. applied becomes greater and approaches that of the cathode, the valve becomes conductive and this flattens the white content of the picture. The correct setting for the control is found by advancing it until the whites tend to flatten and then retard it until this effect no longer occurs. This ensures that all interfering signals which have a greater magnitude than peak white are attenuated by the diode.

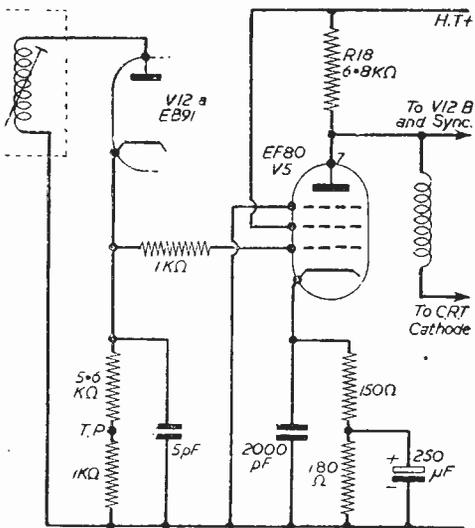


Fig. 3.—Detector and video amplifier circuit.

**The Sound Circuit**

Signals at sound I.F. are applied as previously.

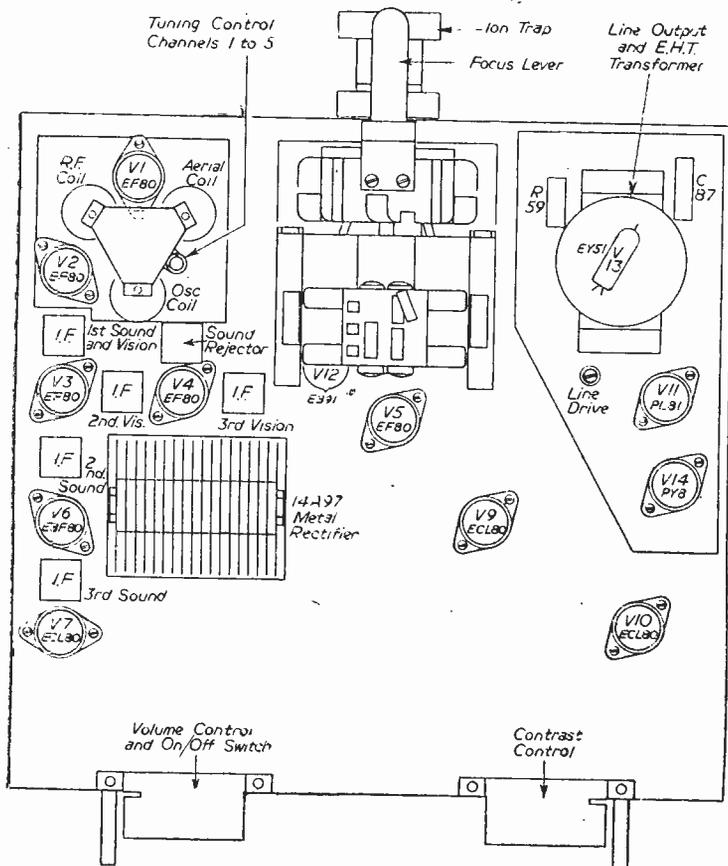


Fig. 1.—Above chassis view of the main parts.

stated to the control grid of V6 EBF80, being tuned by the second sound I.F. transformer. Signals appearing at the anode circuit are tuned by the third sound I.F. transformer and are passed to a diode section of the same valve. Signals developed across a .68 KΩ resistor are applied via a .01μF capacitor to a WX6 sound interference limiter rectifier. Fig. 7 shows the circuit, and in the event of low and distorted sound the marked 2.2 M resistor (red, red-green) is to be suspected.

Other sound troubles can usually be overcome, either by the replacement of V6 or V7. Quite often a loud hum may develop due to one of these two valves developing a heater-cathode leak or short, and in this respect V7 is usually the offender.

**The Line Timebase**

The triode section of V9 functions as a blocking oscillator, the frequency being controlled by the line hold control.

If this control has to be at the end of its travel in order to lock the picture horizontally, suspect V9; and if a replacement does not produce a cure the 150 K resistor, which is in series with the centre tag or slider, should be inspected, as this had a tendency to rise in value. The line oscillations are fed to the V11 line



replacement of V10, although loss of hold can be due to several factors. If the hold control is at one end of its travel, suspect R47 330K. If the control works normally, i.e., will make the picture roll both upward and downward but will not lock it, suspect the interlace diode, R41 (2.2M sync separator screen resistor), R37 or R38. R37 is a 220K and R38 a 1.5M. If weak frame sync (picture will not lock) is accompanied by critical or weak line sync, check V9 and R41, and if the picture seems under contrast at the same time, check C63 video amplifier 250  $\mu$ F cathode capacitor.

**C.R.T. Type and Wiring**

In the Regentone, the tube fitted is usually a Mullard MW36-24 or an Emitron 14KPH. These are tetrode tubes with a duodecal base wired as follows. Pins 1 and 12—heaters; Pin 2—control grid; Pin 10—1st anode; Pin 11—cathode. The EHT supplied to the final anode is some 12-13KV and this, of course, is derived from the EY51 mounted on the line output transformer. As is well known, a common fault to develop on these tubes is a cathode to grid short, which causes the beam current to become excessive, thus overloading the EY51 and the line output stage. If no picture is obtainable, and inspection reveals that the EY51 heater is not glowing, listen for the line timebase whistle. If it is present, connect tag 10 of the tubebase to chassis. Due to the 2.2M resistor this will cause no harm. If now the EY51 heater lights up and the EHT voltage is present at the tube anode, try connecting a 2.2M resistor from tag 10 to tag 12 of the tubebase. In all probability the picture will be quite presentable, and due

to the decreased A1 voltage the short should clear. A little experimenting with the value of the additional resistor, say up to 4.7M, may brighten the picture and still "hold off" the original short. If this procedure fails, use the tube as a triode, strapping

APPROXIMATE VALVE VOLTAGES			
	Anode	Screen	Cathode
V1 ... ..	175	175	3-35 (contrast)
V2 ... ..	180	40	—
V3 ... ..	175	175	3-35 (contrast)
V4 ... ..	175	175	2.2
V5 ... ..	140	215	3.3
V6 ... ..	205	100	3.75
V7 triode ...	60	—	7
V7 pentode	200	200	7
V9 triode ...	205	—	—
V9 pentode	140	5-10	—
V10 triode ...	200	—	—
V10 pentode	200	200	—
V11 ... ..	*	155	1.3
V13 ... ..	—	—	12 kV
V14 ... ..	215	—	*

\* No test advisable.

tag 2 to tag 11 and connecting the lead to tag 2 in the place of tag 10, which should become redundant. If however no line timebase whistle is audible, check valves 9, 11 and 14. Uncontrollable brilliance, or a raster which is brilliant at minimum brilliance setting and vanishes as the control is advanced, indicates usually a cathode to heater short. If the set is used on A.C. mains, the fitting of a 6.3 volt isolating

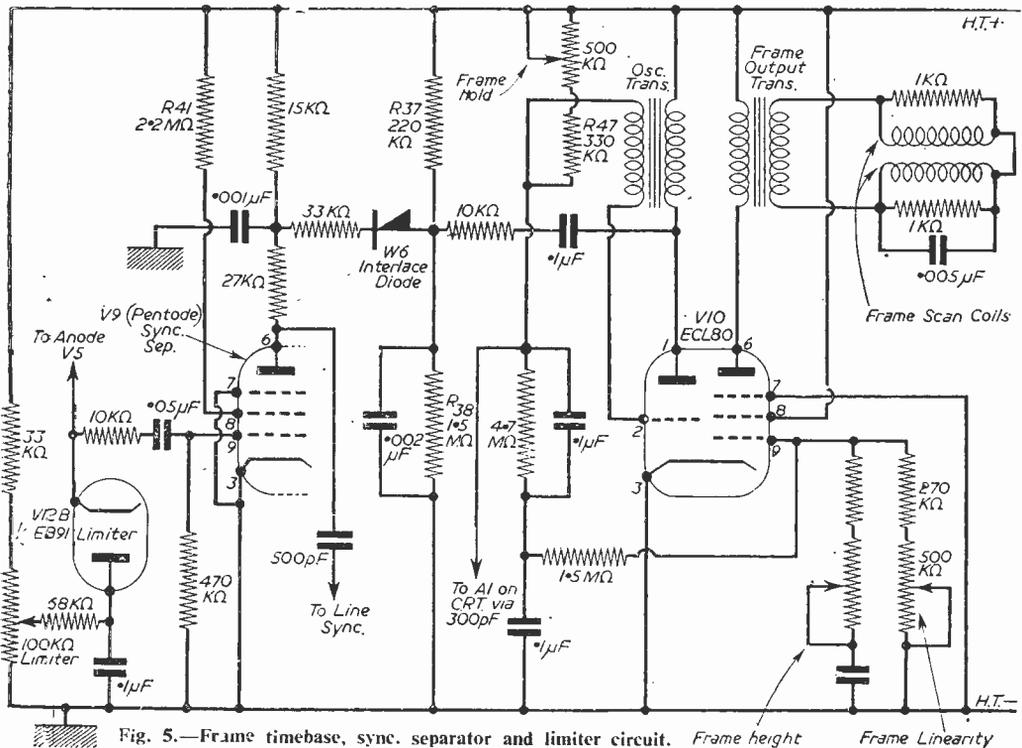


Fig. 5.—Frame timebase, sync separator and limiter circuit. Frame height Frame Linearity

heater transformer presents no difficulty. It should be realised that in the event of a short occurring between the cathode is at chassis potential.

Therefore the 6.8 K video amplifier load resistor is effectively connected from H.T. to chassis and a certain amount of overheating is bound to occur. If,

correspond with those given in this article. In place of the EF80 valves, 6BX6s may be found. 6AB8s in place of ECL80s and the PL81 may be replaced by a 21A6, the PY81 by a 1723, the EB91 by a 6AL5 and the EY51 by a 6W2.

On the Decca D14 receiver a Ferranti T14/2 triode

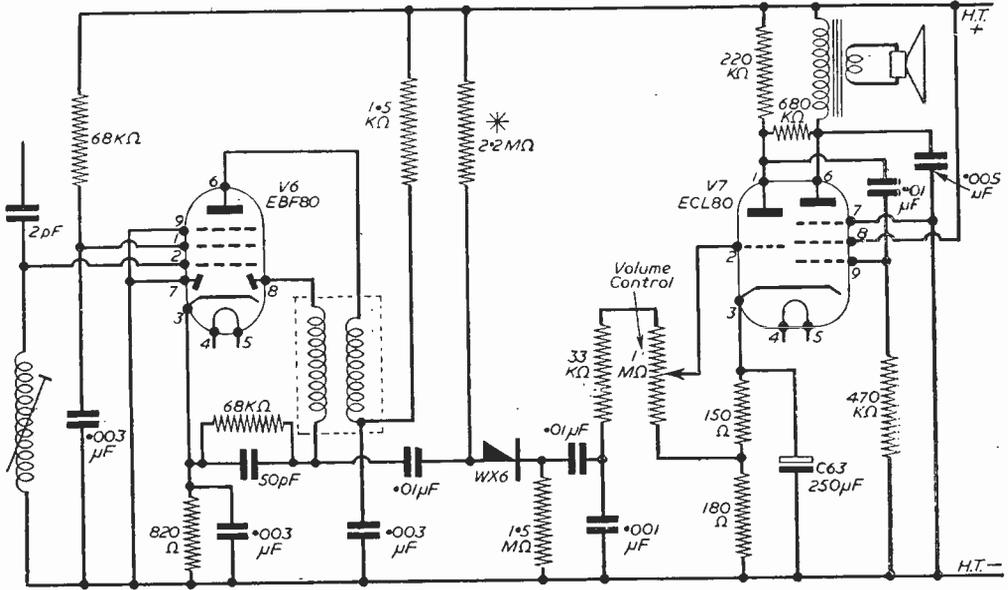


Fig. 7.—Sound I.F., detector, limiter and output circuit.

after fitting an isolating transformer, results are not as expected, check this resistor (R18) to ensure its value is correct. The heater voltage of the tube is 6.3 and if it is desired to fit a resistor in the heater chain to take the place of the tube heater when a transformer is fitted, a value of 20Ω at 3-5 watts will be in order. Alternatively, the leads to tags 1 and 12 may be connected together (after removal from the tube base of course) and the green leads of the main supply voltage selector placed on the next tag to the left.

As the receiver is designed for connection to A.C. or D.C. mains, the valve heaters are wired in series and are therefore all of the same heater current rating, i.e., .3 amp. Two fuses are provided. The 1 or 1.5 amp. is coloured blue and is in series with the mains supply. The 500 mA is coloured yellow and is in series with the main H.T. supply from the metal rectifier.

The mains supply is applied to the metal rectifier via R61, the actual tapping depending upon the mains voltage. The D.C. output of the rectifier is applied to the reservoir capacitor (200 μF) which maintains the voltage at this point fairly smooth, despite mains ripple and varying current demands. The current is further ironed out by the 30 Ω and 60 Ω resistors and is finally smoothed by the 500 μF section. The link beneath the voltage adjustment must only be made when the mains input is D.C. and the effect of this link is to short out one section of the metal rectifier to minimise the voltage drop across it and to remove the 60 Ω resistor.

It may be found that the valve numbers do not

tube is fitted, and in this case the tube wiring and circuit values are slightly different.

**PRACTICAL WIRELESS NOVEMBER ISSUE NOW ON SALE PRICE 1s. 3d.**

The current issue of our companion paper, PRACTICAL WIRELESS, which is now on sale, contains a special article for the newcomer to Short Wave working. This consists of a constructional feature on an A.C. mains-operated Short-Wave three—two stages plus a valve rectifier for the mains section. It uses plug-in coils and is simple to construct and operate.


An interesting contemporary design for a radiogram cabinet forms the subject of another constructional feature, whilst transistor enthusiasts are catered for this month by a constructional article on a small square-wave generator housed in a fountain-pen cap. Other practical articles cover a Signal Tracer and Amplifier, the use of 807s in Class A.B2—with special reference to a transmitter modulator, a Simple "S" Indicator using a worn-out Magic eye. Other articles cover the conclusion of the series on Push-Pull and a Novel Baby Alarm, and model control enthusiasts are told how to make a single valve Model Control Transmitter. An electrostatic loudspeaker is described, whilst for Tape Recorder fans there is an article on modifying the Sound-Master and one on the fitting of an automatic switch for Tape Recorders. The Servicing article this month deals with the Marconiphone T24DAB.

# Portable TV Receivers

SOME INTERESTING DETAILS OF PORTABLES NOW AVAILABLE, AND THE FACTORS WHICH GOVERN DESIGN

WITH the increasing popularity of television as a form of home entertainment, there has arisen a need for a "second set." This may be so that certain members of the family may view one station, whilst others may have the alternative programme, or one set may be placed in a bedroom in a case of sickness, etc. There is also the possibility of wanting to use a receiver in the open on picnics or other outings, although due to the brightness of the light satisfactory reception may be difficult to obtain. These facts have led to the development by a few manufacturers of small receivers intended for what might be termed portable use, although, of course, they are by no means as light in weight as a portable radio receiver.

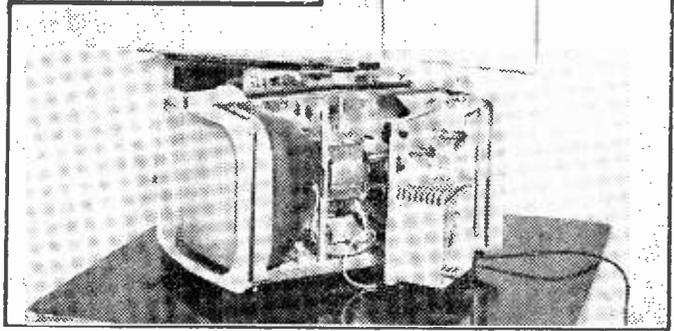Now that the 17in. or 20in. screen is accepted as the more or less standard domestic size, the old 9in. tube has become obsolescent, but it is ideal for a



The Pye Portable, with frame aerial in position.

portable receiver. The picture is large enough to offer satisfactory viewing, and in fact many homes are still using the older 9in. sets. The tube, therefore, forms the main part and governs the dimensions of the set. It is interesting to see how the various manufacturers have tackled the problem of reducing size and weight in this type of equipment and in this article four models which were shown at this year's Radio Show are illustrated.


## Pye

At the top of this page is the Pye, removed from its case to show the general method of assembly. In this model the front of the cabinet forms the tube mask and there are no controls or anything else to increase the overall frontal area. As this model utilises a 14in. screen, the frontal dimensions are 13 $\frac{1}{2}$ in. by 11 $\frac{1}{2}$ in., and all the remaining equipment is housed in the length, making this measurement 19 $\frac{1}{2}$ in. The elliptical speaker (6 $\frac{1}{2}$ in. by 4in.) is on the side of the assembly, and in this particular model a frame aerial is provided for areas of good signal strength. The number of valves used in these portables may be reduced by the employment of diodes for certain functions, and double types of valves can also be used in places so that the number of actual stages is not much reduced. In the Pye, for instance, there are 17 valves, 5 selenium diodes and 3 germanium diodes, and in addition there is a 13 channel tuner.

The cabinet for this model is in aluminium, and the side portions are made removable for easy access to components, whilst the chassis swings out for easy servicing. The overall weight of this model is 40 lbs.
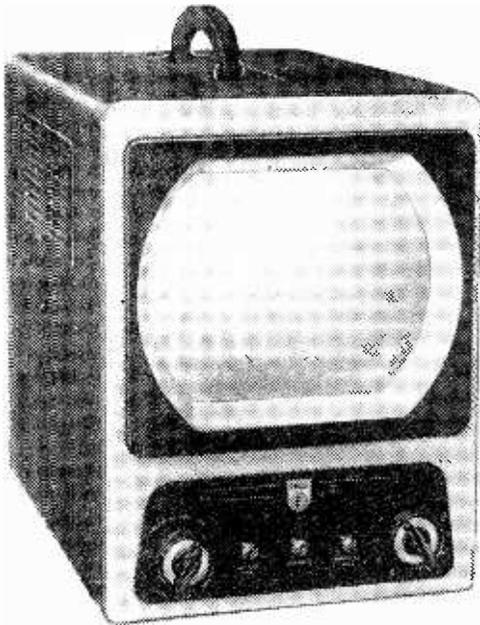
## Ekco

The Ekco is designed on different lines, and is intended for use with a normal mains power supply, or a 12-volt D.C. supply. In this manner it may be used with a normal car battery and, unlike other portables, it may be taken out into the country in a



This is the Ekco Portable.

car and then, by merely plugging into the car lighting circuit, it can be brought into operation. The load on the battery is 7 amps, and the necessary mains or power switching is automatic, the action of plugging in the appropriate connecting lead automatically selecting mains rectifier or D.C. supply. In this model a 9in. aluminised tube is fitted and the front of the cabinet, as may be seen from the illustration at the foot of page 167, carries also the various volume, tuner and essential controls. This brings the frontal area in this model to 13½in. by 10½in., whilst the depth has been kept to 15½in. The weight is 5 lbs. less than the Pye (35 lbs.), and it will be noted that the "double-D" type of mask is employed to offer a slightly increased picture area, compared with the normal "5 by 4" rectangular picture on a 9in. tube. Again an elliptical speaker is fitted (7in. by 4in.), and the case is of aluminium covered with leather-cloth.


#### Spencer-West

The Spencer-West "Teevy" also incorporates a 9in. tube, and although no details are available concerning the circuitry, etc., the case is finished in various forms according to the particular use to which the receiver is to be put. One form is shown above, and another has the cabinet finished with interesting nursery pictures where it is intended that the receiver shall be a "second set" in the nursery. The general lines of design may be seen from the illustration and the general size should not be much different from the Pye.
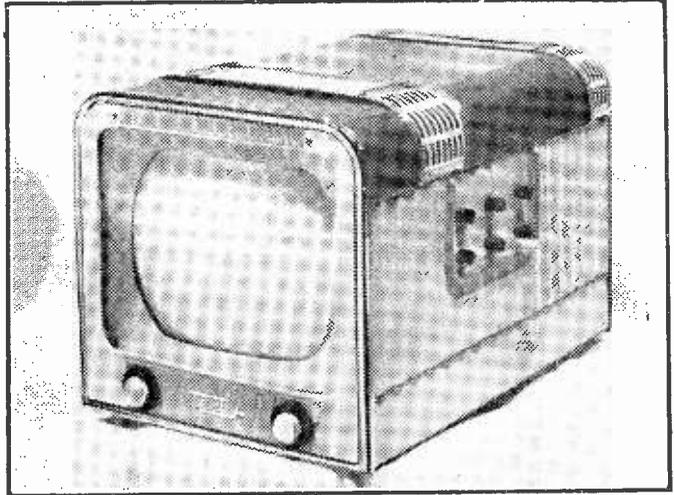
#### Murphy


In the Murphy model, shown below, a 12in. tube has been fitted, but apart from other interesting features of design the containing case follows novel

lines. Again the frontal area is "all picture," the controls being recessed into the sides. Instead of metal, the makers here have used a fibre-form material which is moulded in two halves—after the manner of a chocolate Easter egg. When placed together, the two halves are held by a die-cast



The Spencer-West "Teevy."

aluminium fitting which holds the receiver in a vertical plane. To take the weight of the set when it is placed down the set stands on feet which form part of the chassis—not the case. The latter is therefore merely a shell and as such protects the interior from damage rather than the more customary utility use to which the cabinet is put. The overall dimensions of this set are 14½in. by 14in. for the front, with an overall depth of 17½in. and the weight has been kept down to 28 lbs. The layout of the interior may be seen from the illustration from which it will be noted that a form of assembly has been adopted which does not appear to have found much favour in this country, although quite popular on the Continent. In this, the chassis upon which the main receiver is assembled carries a central hole to which the scanning coils, etc., are fixed, and the tube neck is inserted into this hole so that the set is arranged round the tube. There are a number of advantages in this form of assembly, although all the valves then become horizontal and need retaining springs or screens. The turret tuner may be seen in the lower left of the picture, whilst one of the metal feet upon which the set stands may be seen on the right. The loudspeaker in this model lies on its back and points upwards through the carrying handle, and this may be seen above the looped EHT lead to the tube cap. Much of the mechanical design of this receiver was influenced by the cabinet shape.

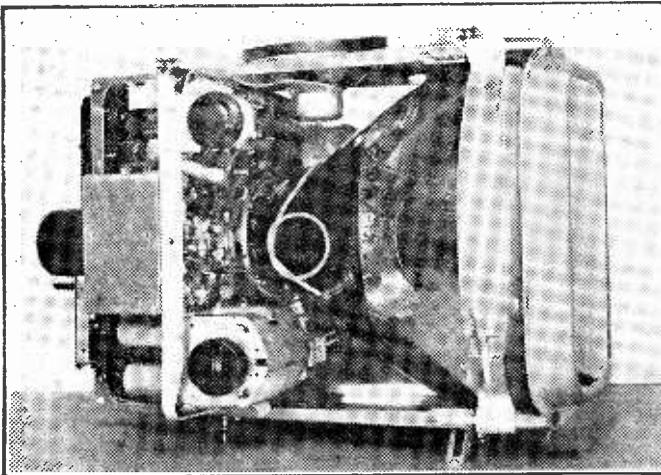

An inside view of the Murphy Portable.



**FOR VALVES**  
**GUARANTEED**  
**ALL TESTED**  
**BEFORE**  
**DESPATCH**

6Z1	5/6	6U5G	8/6	6CH81	11/-
1A7	3/6	1U5	8/6	6E80	10/-
1A5GT	6/-	6U7G	8/6	6E22	8 8
1A7	11/6	6V8G	7/-	6L80	10/6
1C2	9/6	6Y9GT	7/6	6L41	11/-
1C5GT	9/6	6X4	7/6	6E86	12/6
115GT	10/6	6X5G	7/6	6E89	12/6
1L4	6/6	6X5GT	7/6	6L2	12/6
1L15	5/-	7B6	9/6	6L32	6 6
1N3	10/6	7B7	8/6	6L44	10/6
1J5	8/-	7C5	8/-	6L42	11/6
1S1	9/6	7C6	8/-	6L84	11/-
1S5	7/6	7H7	9/-	6M31	10 -
1P1	7/6	7Q7	9/-	6M80	11/-
115	7/6	7A7	9/6	6V51	11/6
2X2	4/6	7A1	10/6	6V86	12 -
3A1	7/-	75	10/6	6V91	6/-
316	5/-	77	8/-	6Z40	10/-
5Q1	9/6	80	8/6	6Z41	11/-
3Q5	9/6	807	6/6	6Z90	10/-
3M4	7/6	812	2/6	6L148	3/-
3V1	8/6	9D2	3/6	6V1500	10/-
411	3/-	9001	5/6	6Z82	12/6
42	8/-	9003	5/6	6H0	5/-
6R41V	9/6	9001	5/6	6H2	5/-
6L4C	8/-	9006	5/6	6L1320	4/-
6Y3G	8/-	901	2/6	6K35	12/6
6Y3GT	8/-	955	4/6	6K2	5/-
6Z15	8/9	956	3/6	6T33C	10/-
6A7	11/6	10C1	12/6	6T6W1	7/-
6ACG	6/6	10C2	10/6	6M80	8/6
6AC7	6/6	10P1	11/6	6Z41	6/-
6AG5	6/6	10F9	11/6	6P229	6/9
6AK5	6/6	10P13	11/6	6M/PEN	5/-
6AL5	6/6	10P14	13/6	6P1	3/9
6AM5	5/-	12A6	6/6	6P25	5/9
6AM5	7/6	12A7	8/-	6P825	5/-
6AQ5	7/6	12A7T	9/-	6P846	7/-
6AT8	6/6	12A17	9/6	6P820A	4/-
6H8	4/-	12A7X	10/-	6PC84	10/-
6H36	7/6	12B39	10/-	6P880	9/-
6H63	8/-	12B8	7/6	6P882	12/6
6H16	8/6	12H6	3/-	6C185	12/6
6BW7	10/-	12J3	4/6	6P181	12/6
6C4	7/-	12J7	9/6	6P182	12/6
6CGT	6/6	12K7	9/6	6P183	12/-
6C6	6/6	12Q7	7/6	6P225	5/-
6C9	10/6	12M7	2/6	6Y80	10/-
6CH6	7/6	12S67	7/6	6Y81	10/-
6D6	6/6	12H17	5/6	6Y82	8/-
6F1	12/6	12S47	8/-	6R19	13/6
6F60	7/6	12S87	8/6	6P220	6/9
6F8	7/6	12S87	8/6	6H0	9/-
6P12	14/-	12M87	7/6	6U2	8/-
6P14	12/6	20D1	10/6	6U5	13/6
6P15	14/-	20F2	13/6	6U4	11/6
6G6G	4/6	20L1	12/6	6AF42	11/6
6H6	2/6	25L6GT	9/6	6U41	9/-
6J50	5/6	25U4GT	10/-	6U41	10/-
6J5GT	5/6	25Y5	9/6	6U42	11/-
6J5M	6/6	25Z4G	9/-	6U41	10/-
6J6	6/-	25Z6GT	9/6	6U41	11/-
6J7G	6/-	33L6GT	9/6	6V41	10/-
6K64	7/-	33W4	9/-	6V21	8/-
6K74	5/9	33Z4GT	8/6	6V52 (6F29)	6/6
6K7M	6/9	33Z5	8/6	6V52	6/6
6K80	8/9	50L6GT	8/6	6V54 (6B24)	8/6
6K81	8/9	A30/PEN	6/6	6V54	8/6
6L6G	9/-	ATP4	5/-	6V55 (6B32)	8/6
6L7	7/6	DH73M	10/-	6V56 (6F26)	7/6
6N7	7/-	EABC80	10/-	6V56	6/6
6Q7GT	9/-	EAF42	12/6	6V57 (6K22)	8/6
6S47GT	8/-	EB41	9/-	6V57	8/6
6S47	7/6	EB41	10/-	6V65 (6P61)	8/6
6S47	6/-	EBF80	11/-	6V65A (6P11)	8/6
6S47	8/-	EC91	9/6	6V66 (P61)	3/-
6S47	8/-	EC84	12/6	6V66A (6P11)	3/-
6S17	8/6	EC85	10/-	6V66 (P61)	3/9
6S87	8/6	EC89	14/6	6V61 (6F50)	4/-
6S97	9/6	ECF82	15/6		
6S87	8/6	ECH35	11/6		
6U1GT	15/-	ECH42	10/6		

Packing and Postage—6d. per valv.  
 SAME DAY SERVICE

# ARE YOU BUILDING THIS POPULAR KIT ?

Modern Portable. A.C./D.C. Mains/Battery Receiver. Four valves, DK96, DL96, etc. 2 Waveband Superhet. In an attractive Lizard Grey Case, size 8 1/2 in. x 8 1/2 in. x 4 1/2 in. Full Kit of Parts down to last nut and bolt.

**£9.9.0**



Or if you prefer you can build the battery version first for £7/17/6 and add the mains components later. Post extra on Kit 3/-.

Full Circuit Diagram, Shopping List, and Point-to-Point Wiring Diagram, 2/6.

## MAINS TRANSFORMERS—3-way Mounting Type

<b>MT1:</b>	Primary: 200-220-240 v. Secondaries: 250-0-250 v. 80 m/a 0/6.3 v. 4 amp. 0-4 v. 2 amp. Both tapped at 4 v. ... each	18/4
<b>MT2:</b>	Primary: 200-220-240 v. Secondaries: 320-0-320 v. 80 m/a 0/6.3 v. 4 amp. 0-5 v. 2 amp. Both tapped at 4 v. ... each	19/8
<b>MT3:</b>	Primary: 200-220-240 v. Secondary: 50 v. 2 amps. Taps at 3 v., 4 v., 6 v., 8 v., 9 v., 10 v., 15 v., 18 v., 20 v., 24 v. ... each	19/3

Please add 2/- per transformer post and packing.

### SPECIAL OFFER

Anti-Interference Aerial Type CD4 Indoor ... with full instructions, etc. 13/6 each. Carriage Paid.

Aerialite Band III Aerials 5 element, 792 x 17. An array with universal lin.-2in. masthead bracket, suitable channels 8, 9 and 10. Price 41/-, carriage 4/6.  
 Aerialite Coaxial outlet boxes at 4/6 each.  
 Aerialite Coaxial plugs and sockets at 1/1 each.  
 Transformers T1154X, 25/- each. Transformers T1154H, 37/- each. Transformers T1151 in tough condition, 15/- each.  
 Carriage and postage on above transformers is 12/6.  
 Meters 0-100 m/a., panel mounting, 7/6 each.  
 Meters 0-5 amp. R.F. panel mounting, 7/6 ea.

### CRT ISOLATION TRANSFORMERS

NR9A 2 v.; NR9B 4 v.; NR9C 6.3 v.; NR21 10.8 v.; NR5E 13.3 v. 1rce 10 6 each, all for use on receivers with own transformer.  
 NR14 Input 230/240 v., output 2-21-23-25 volts at 2 amps. 17/6 each.  
 NR12 Input 220-240 v. Multi output 0-2-4-6-8-7-10-13 volts 25% and 50%. BOOST. 21/- each.  
 NR15 Input 220-240 v. Output 6.3 v., with 25% and 50% BOOST. Price 17 6 each.

**OUR NEW 1956-57 48-PAGE ILLUSTRATED CATALOGUE IS NOW AVAILABLE**  
 Send 1/- for your copy to-day.

## LOUD SPEAKERS

### All PM Types less Transformers

3 1/2" square type	Each	18 6
4in. Types by Blac. Lectrona, Celestian, etc.	17/3	
6 1/2in. Types by Goodmans, Roia, H. & A.	18 3	
5in. Types by Goodmans, Plessey, R. & A.	19 3	
10in. Types by R. & A., Celestian, etc.	25 3	
6 1/2in. Wafer Speaker by Truvox, suitable for Car Radio, etc.	26 -	
12in. Plessey Lightweight	35 -	
Elliptical Speakers, Goodmans, 4in. x 7in.	19 8	



### OUTPUT TRANSFORMERS

Multi Ratio Type, each	6/6
Midget for 254 Output, each	4/6
Standard 5,000 ohms, each	4/6
Standard 10,000 ohms, each	4/8

### CHARGER RECTIFIERS—All Full Wave

12 volt 1 amp., each	5/3
12 volt 2 amp., each	8 3
12 volt 3 amp., each	13 3

WHEN ORDERING PLEASE QUOTE DEPT. "PT."



**5/6 VINCES CHAMBERS**  
**VICTORIA SQUARE**  
**LEEDS 1.**


**TERMS:** Cash with order or C.O.D. Postage and Packing charges extra, as follows:  
 Orders value 10/- add 1/-;  
 20/- add 1/6; 40/- add 2/-; £5 add 3/- unless otherwise stated, Minimum C.O.D. fee and postage 3/-. All single valves postage 6d.

**MAIL ORDER ONLY**

**ADCOLA**  
PRODUCTS LIMITED  
 (Regd. Trade Mark)
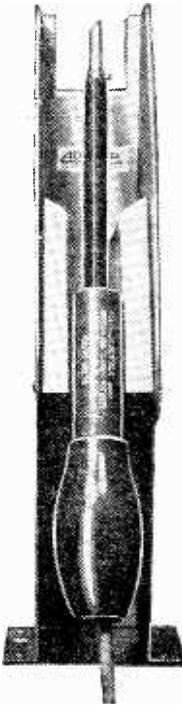
# SOLDERING INSTRUMENTS

Sound jointing for the  
Home Radio Engineer



Illustrated  
Protective  
Shield  
(List No. 68)

$\frac{3}{16}$ " Detachable  
Bit Model  
(List No. 64)

Supplied for  
all volt  
ranges with  
no extra cost  
for low volt-  
ages.

Bit sizes  $\frac{3}{8}$ "  
to  $\frac{1}{4}$ "

Apply Catalogues:

*Sole Proprietors & Manufacturers*

HEAD OFFICE SALES AND SERVICE  
**ADCOLA PRODUCTS LTD.**

GAUDEN RD., CLAPHAM HIGH ST.,  
LONDON, S.W.4.

Tel: MACauley 3101-4272.

17" **RECTANGULAR** 14"  
**£7.10. T.V. TUBES** £5.10.  
SIX MONTHS GUARANTEE.  
16" 15" 14" ROUND £5  
THREE MONTHS GUARANTEE.

Please Note: A 15in. or 14in. T.V. tube can be fitted in place of 9in. or 12in. with little or no alteration. 15/6 ins. carr. on each tube. 12in. Round Type and smaller sizes please enquire and give alternative if possible, as heavy ordering may cause delay in delivery.

## T.V. CHASSIS 97/6

Complete chassis by famous manufacturer R.F. E.H.T. Unit included. Drawing FREE. Easily fitted to Table or Console model, owing to this chassis being in three separate units (Power, Sound and Vision. Timebase) inter-connected.

**T H I S**

**CHASSIS**

**IS LESS**

**VALVES**

**AND TUBE.**

but see our catalogue for cheap valves. Our £5 Tube fits this Chassis. List of valves by request. Carr. 5- London, 10/- Provinces.

CHANNELS 1-3 or 4-5. Many clients have successfully converted to 14in., 15in. and 17in. tubes. I.F.s are 17.25-19.25 mc/s vision. I.T.V. Channel 7-13 easily converted.

REMEMBER: SATURDAY OPEN ALL DAY.

MONEY BACK  
GUARANTEE

**DUKE** Tele: GRA 6677  
G-Geo

CWO  
OR  
COD

621 ROMFORD RD. LONDON, E.12.

## VIDEO ELECTRONICS (LONDON) LTD. (Dept. P.T.)

Head Office: 27, Bacon Street, London, E.1.

Works: 16/22, Bacon Street, E.1.

Telephones: Bishopsgate 0419/0410.

**T.V. Tubes (17in. £8, 14in. £6, 12in. £5, etc.)**

Cheap, reliable high grade seconds and reconditioned C.R.T.s, as supplied to the trade and leading Television Insurance Companies, prices from £3.

### Valves

Send at once for our useful list of cheap valves which will save money, we are the cheapest in the trade.

### Condensers

Electrolytics, bias, coupling, etc., etc., at giveaway prices. All types stocked.

### Resistors

A fine stock of these at very low prices.

### T.V. & Radio Cabinets

A few 17in. Table cabinets, new, ex famous manufacturer, and about 500 very handsome radio cabinets.

Send for stock list of speakers, valves, components and T.V. and Radio Spares.

All our goods are guaranteed.



"ICONOS" VISITS  
MANCHESTER'S NEWEST  
ITV ESTABLISHMENT

## Centre

### The Main Stage

Most of the studio transmissions originate from the main No. 1 Studio, 48ft. x 84ft., which is equipped with a new system of mechanical light placement. The incandescent lamps, spots and floods are suspended from the overhead grid on telescopic supports, and may be raised or lowered or slid along the R.S.J. supports on


MANCHESTER is a great city—centre of a thriving industrial area, hub of the cotton trade and a great port. Historians think of it as the cradle of the Manchester school of political theory, where Mill and Cobden expounded their ideas of economics, Free Trade and the individualist. Thanks to the constant wisecracks of music hall comedians, however, the name of Manchester has become associated in the minds of most viewers with rain—steady rain.

I am not quite sure whether it is by intention or coincidence that the Granada TV Network have selected an umbrella-shaped dipole as their symbol or trade mark, appearing before each transmission. This seems most appropriate. But like everything else at the Granada TV Centre, Quay Street, Manchester, it has been carefully thought out and planned, right from the zoom lenses on the cameras to the buttons of the commissionaires' uniforms.

The Granada TV plant is not of huge dimensions, judging by BBC standards or even by the aggregate space taken up by the scattered components of, say, Associated Rediffusion in London. It is compact: an admirable mixture of brand new buildings and adapted old ones situated 50 yards or so from Deansgate, in the heart of the city. There are actually two sites. The one in Quay Street contains all the production plant, workshops, production offices, dressing rooms and four stages, with ample space for extensions and garages for the outside broadcasting trucks (known here as "Travelling Eyes"), radio link vans and other vehicles. The second site, in Water Street, houses the accounts and other administrative departments, the film editing and handling sections and viewing theatres. All the premises, whether built up completely new, or re-built old, have been decorated in a pleasing contemporary style slightly reminiscent of the Royal Festival Hall, London. The cleanliness of the floors and corridors was almost clinical. I noticed that the muddy foot-marks I had made in the entrance hall were magically removed when I passed it by, 20 minutes later, in the company of Simon Kershaw, the genial general manager of the Centre.

runners. This latter movement, however, is limited to some extent by the supporting girders. It is possible for an electrician to walk about on the closely placed lighting grid and make very speedy alterations to lamp positions below. The lamps, all of which are of the normal incandescent type (mostly by Mole Richardson), are supplied with alternating current through an organ-like lighting console (by Strand Electric) which controls remote contactors and dimmers situated in the roof. Two hundred and fifty amps at 115 volts is the maximum requirement with the sensitive cameras used. Direct current for arcs from a rectifier is also available but has not so far been used.

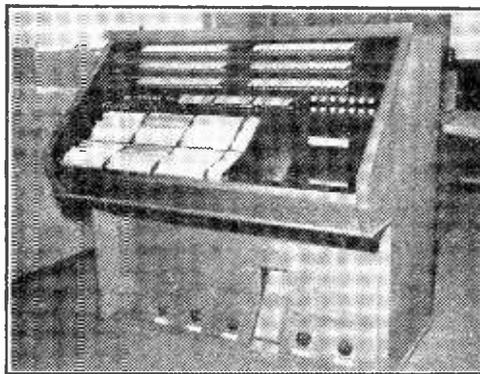
The studio is equipped with 4½ in. Image Orthicon cameras (Marconi) of which three are in use and a fourth is standing by in permanent readiness. These are linked with the studio vision control apparatus, which enables the producers to make the usual cuts, fades and lap dissolves. The cameras are mounted on Houston-Fearless pedestals, with the



The lighting console in the vision control room. It is from here that the lighting operator controls the intricate lighting system.

exception of one, which is usually mounted on a Vinten Pathfinder crane.

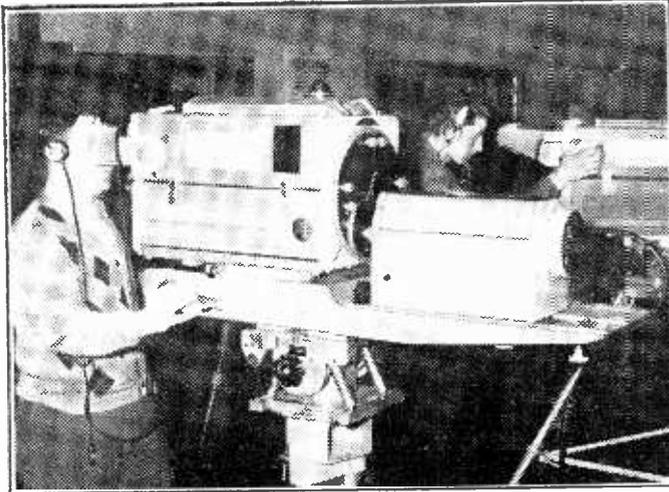Adjacent to this main stage and separated from it by a large plate glass window is a small "Interview" Studio, No. 2. This has been found to be especially useful for parlour game transmissions and the cameras are sometimes required to shoot through the glass from one stage to the other. Studios 3 and 4 were not fully completed at the time of my visit, though partly operational.



One of the Granada O.B. cameras fitted with a zoom lens.

### Ventilation

Heating and ventilation of TV studio premises is always a problem, especially as regards the elimination of noise in both studios and control rooms. The Granada engineers have tackled this problem in a very thorough manner. Precautions have included flexible couplings between sections of the ventilation ducts and, in some places, the lining of the interior of the ducts with sound-absorbing material. The incoming air is filtered and heated but is not washed. After three months of operation in Manchester atmosphere it was necessary to replace the filters!

### Telecine Facilities

The telecine equipment consists of two E.M.I. Flying Spot scanners of the latest type, capable of handling 35 and 16 mm. film with optical or magnetic sound tracks. These machines have produced some of the finest film reproductions seen on television. There are also two Vidicon telecine machines which each includes a slide projector and also 35 and 16 mm. film mechanisms. An unusual item is a special Telejector slide handling equipment, which gives remote control of slide changing, handling 12 slides at one loading and providing an automatic lap dissolve. There are no facilities at present for telerecording, but these are under consideration.


### Co-axial Links

There is a special cable between the Granada TV Centre and the G.P.O.'s Telephone House, Manchester, which provides six vision circuits, of which five are in use at the moment. Two outgoing

circuits link the Centre with the Winter Hill transmitter in Lancashire and—shortly—the Emley Moor transmitter in Yorkshire. One incoming line handles the I.T.A. networked programmes and two incoming lines are set aside for outside broadcasts. Either of these two can be used for feeding from the Capitol, Didsbury, the A.B.C.-TV television theatre for the Manchester area. The sound and control line arrangements are orthodox.
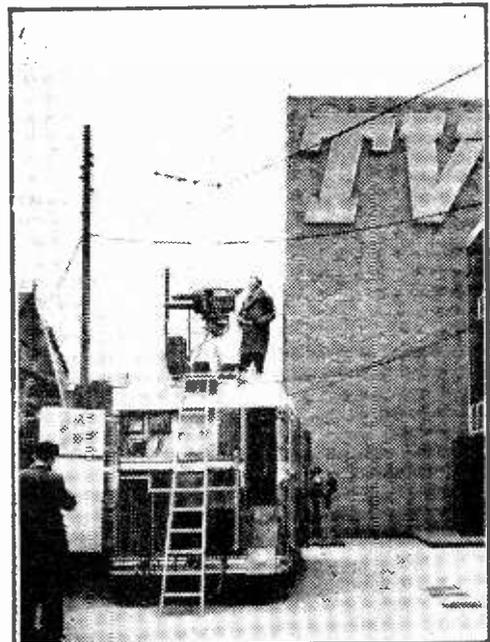
### Travelling Eyes

Granada's two outside television trucks, their "Travelling Eyes," are extremely well equipped. Each truck has a Pye three-channel system and a complete monitoring, sound mixing and gramophone reproducing desk. In addition, there are two radio link vans which can be used as radio-control rooms, and two special tender vehicles for the transporting of outside broadcast equipment. The latter are fitted with ramps to facilitate the loading of camera dollies and similar wheeled equipment. The technical planning and operation of the equipment comes under the supervision of the Chief Engineer, Reginald Hammand, who was with the International Marine Radio Co., Ltd., from 1930-35. In 1935 he joined the BBC Engineering Division, where he stayed until joining Granada in April of last year. Hedley Gower, Assistant Chief Engineer, also came from the BBC,




A "Travelling Eye" truck being tested outside the Granada TV centre.

where he was in the Planning and Installation Department. Leonard Holt, Second Planning Engineer, specialised in lines and communications at the BBC, including the designing of equipment used in Eurovision. These three engineers and their staff are to be congratulated upon the excellent layout and smooth technical operation of the Granada transmissions, the fine results of which I heard much from viewers in Manchester, Lancaster, Morecambe and Blackpool during my northern trip.
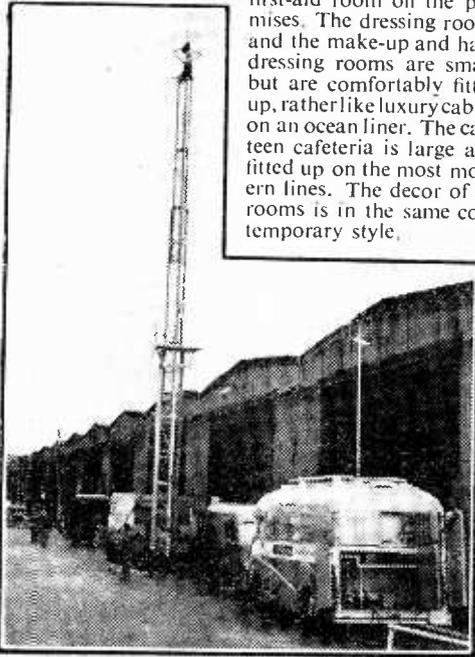
#### Ancillary Workshops and Premises

The same care and thought has been applied to the important ancillary servicing departments as was given to the electronic side. George Speller, Construction Manager, ex-Ealing Film Studios, where he was well known for his many ingenious time-saving gadgets, has laid out a fine series of workshops equipped with various types of woodworking machinery for making scenery, sets and properties. Mr. Speller, with several other leading personnel, together with Simon Kershaw, are all exiles from the Ealing Studios who seem to have settled down comfortably in their new surroundings. They have been joined by Ealing's Sister Ross, who is in charge of the

first-aid room on the premises. The dressing rooms and the make-up and hair-dressing rooms are small, but are comfortably fitted up, rather like luxury cabins on an ocean liner. The canteen cafeteria is large and fitted up on the most modern lines. The decor of all rooms is in the same contemporary style.



An O.B. control room (to the right of the picture), with an Eagle Tower which enables the mobile mast to be raised to 60ft.

#### Granada Programmes


The principal object of this article is to report upon the premises and engineering facilities of the Granada Television Centre. But I must also refer to the programmes side, under the control of Denis Forman, who was formerly Director of the British Film Institute, and to Eddie Pola, who handles the variety programmes. The live programmes which originate from both the studio and from the

"Travelling Eyes" have been very favourably received by viewers in the Lancashire area and elsewhere. Granada has paid special attention to the need for programmes which are serious and informative but, at the same time, not pompous or boring. I seemed to sense that the spirit of Cobden—suitably streamlined—emerged in some of these. The proportion of programmes originating at this studio is likely to increase in the future. At present, the number of live transmission hours in an average week is about 25, plus nine hours of film. These figures include, of course, programmes from other sources and the National ITV network.

#### Commercials

Split-second timing of programmes is the rule here, as at other ITV centres. The mixture of local announcements with or without local picture, followed by, perhaps, an ITV network outside broadcast, intercut with local announcements and commercials on a variety of films or slides, is positively bewildering. At Manchester this intricate jig-saw of precision switching may be even more complicated if and when different commercials are inserted in the same programmes for transmitting respectively and simultaneously from Winter Hill and Emley Moor. Some of the advertising boys have strong

(Concluded on page 186)

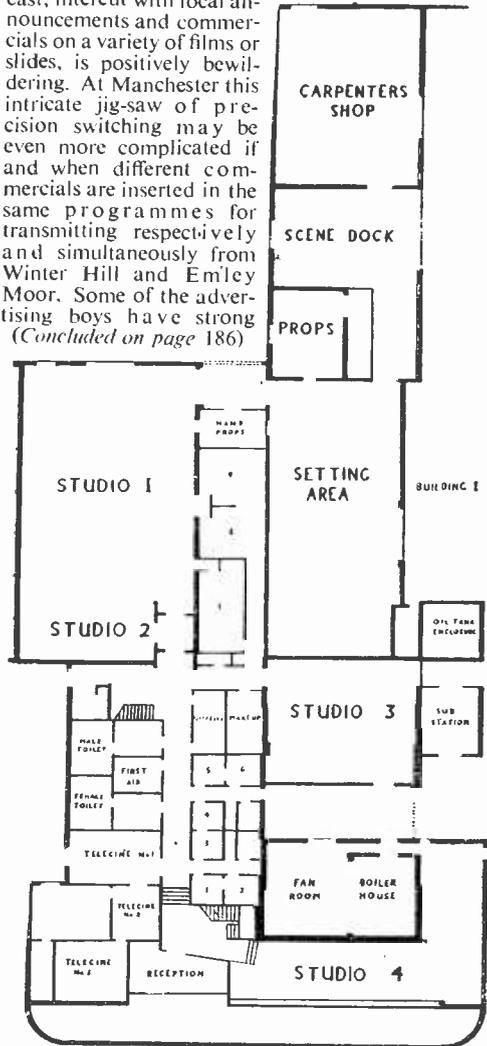

Ground plan of the Granada centre.

THE device to be described measures, in conjunction with a 1 mA meter and suitable power supplies, A.C. signals between 10 c/s and 60 Kc/s, of amplitudes between 0.1 and 10 volts. It has an input impedance of 0.5 megohm, so that it does not appreciably load the circuit under test.

It can be used for checking test equipment, audio and supersonic voltages, measuring gain, feedback factor and output power.

The voltmeter consists of an input attenuator, acting as a range switch, followed by a two-stage resistance-capacity coupled amplifier which drives a 1 mA meter via a full-wave bridge rectifier. A total

The minimum frequency is governed by the values of C3 and C4, and is about 10 c/s.

The second stage feeds into a very low load impedance, and to give high gain without distortion a high-slope low impedance valve is desirable. Consequently a 12A17 double triode is used.

The attenuator consists of high-stability resistors with a total resistance of nearly 0.5 megohm. This is a somewhat low value for a valve voltmeter, but it is the best that can be achieved without the use of a cathode follower. Even with the values specified, on the 1 volt range where the resistance feeding the first stage is highest, stray capacitances cause the meter to read 5 per cent. low at 25 Kc/s. On other ranges the maximum frequency is 60 Kc/s.

The external

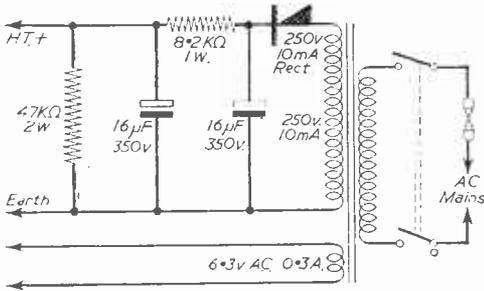
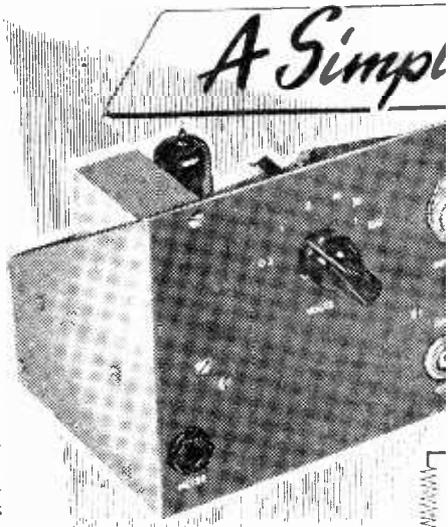


Fig. 3. A mains power supply unit.

of 30 db's feedback is provided by unby-passed cathode resistors in both stages, and by overall current feedback from the output to the first valve cathode. This gives a feedback voltage proportional to the output current, eliminating much of the non-linearity associated with meter rectifiers. The amount of this feedback, and consequently the gain of the amplifier, is adjusted by the wirewound potentiometer RV1. C2 and R7 reduce the feedback at high frequencies to compensate for the fall in amplifier gain due to stray capacitances.

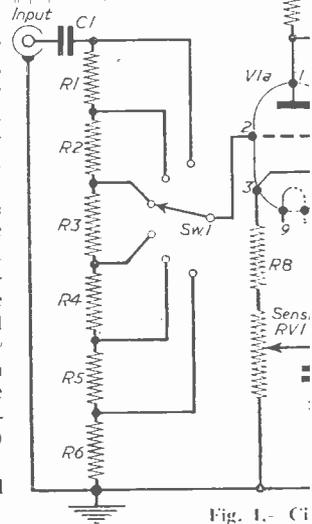


Fig. 1.- C1


LIST OF C

Capacitors -

- C1 - 0.5 µF 350 volts working 25 per cent. Paper
- C2 - 0.001 µF 350 volts working 25 per cent. Paper
- C3 - 0.005 µF 350 volts working 25 per cent. Paper
- C4 - 2 µF 350 volts working 25 per cent. Paper

Resistors -

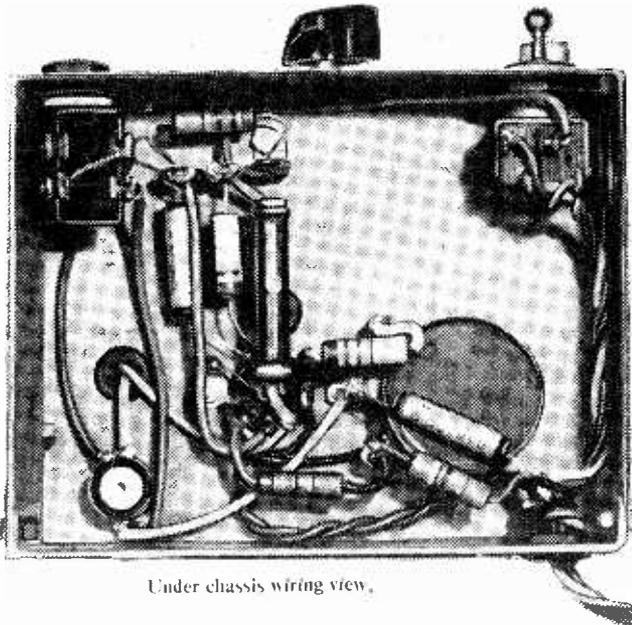- R1 to R6 are attenuator resistors and must be of high stability. The table on page 176 lists these and at the same time shows the voltage readings which those values will give.
- R7 - 3.9 K ½ w, 10 per cent. Carbon
- R8 - 150 ohm ½ w, 10 per cent. Carbon
- R9 - 100 K ½ w, 10 per cent. Carbon



Under chassis wiring view.

# 2 Valve Voltmeter

AN A.C. MEASURING DEVICE WHICH IS EASY AND INEXPENSIVE TO CONSTRUCT  
By R. C. Marshall

power supplies required are 220 to 320 volts D.C. at 3 to 5 mA, and 6.3 volts A.C. at 0.3 amps. If it is desired to make the instrument self-contained, a larger chassis may be used to provide space for the power pack and 1 mA meter beside the unit described in detail. A suitable supply unit is shown in Fig. 3.

It is recommended that the layout shown in the photographs be adhered to, or modification to the values of R7 and C2 may be required. Chassis details are given in Fig. 2.

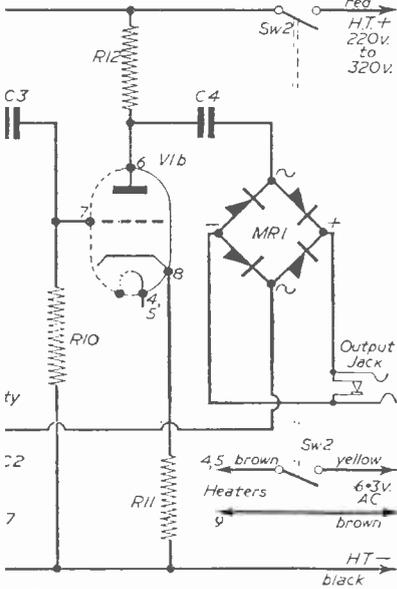


Fig. 1. Circuit diagram of the valve voltmeter.

## COMPONENTS

- R10— 1 M  $\frac{1}{2}$  w. 10 per cent. Carbon
- R11— 680 ohm  $\frac{1}{2}$  w. 10 per cent. Carbon.
- R12— 68 K 1 w. 10 per cent. Carbon.

## MISCELLANEOUS

- MR1— 1 mA Meter Rectifier
- VI— 12AT7
- SW1— 1 pole 6 way Wafer Switch
- SW2— DPST Toggle Switch
- RV1— 500 ohm Wirewound Potentiometer
- Closed-circuit Jack Socket
- Belling-Lee Coaxial Socket L.604S
- B9A Valveholder
- Aluminium (18 s.w.g.), nuts, bolts, solder tags, tag strips, grommets, wire, sleeving, knob.

unit and then assemble the chassis and all those components which are bolted to it. Next wire up the power cable and on/off switch SW2, and connect the attenuator to pin 2 of the valve. Lastly, the remaining connections should be made, and the wire-ended components fixed. The meter should be connected by


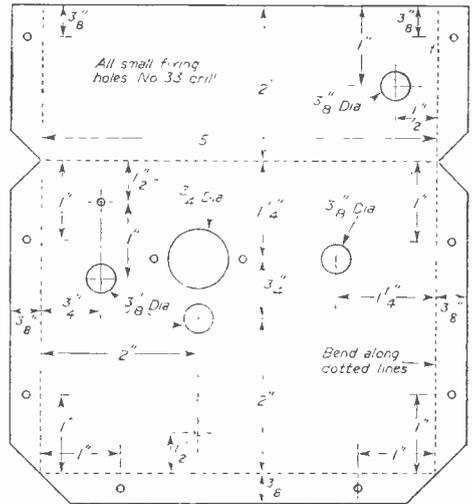


Fig. 2. Chassis bending and drilling details.
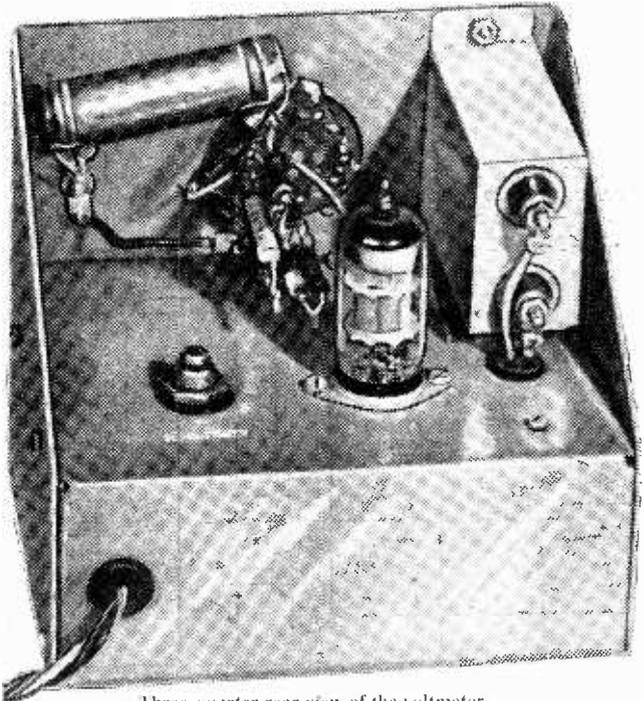
## Wiring

First wire up the attenuator as a separate

the wires supplied, as soldering directly to its tags will cause damage. Note that neither side of the meter is earthed; make sure that the jack used does not introduce such an earth.



Three-quarter rear view of the voltmeter.

**Calibration**

The meter should be initially calibrated against a standard, which may be any accurate A.C. meter. This may conveniently be done at 50 c/s. The comparison should be made on as many ranges as possible, to check the attenuator. The meter sensitivity is

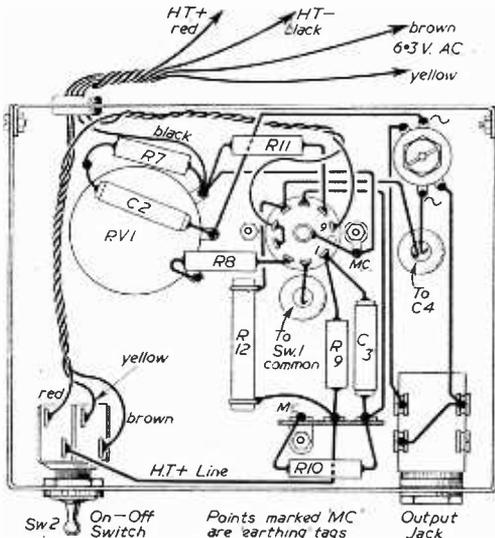


Fig. 4.—Under chassis wiring scheme.

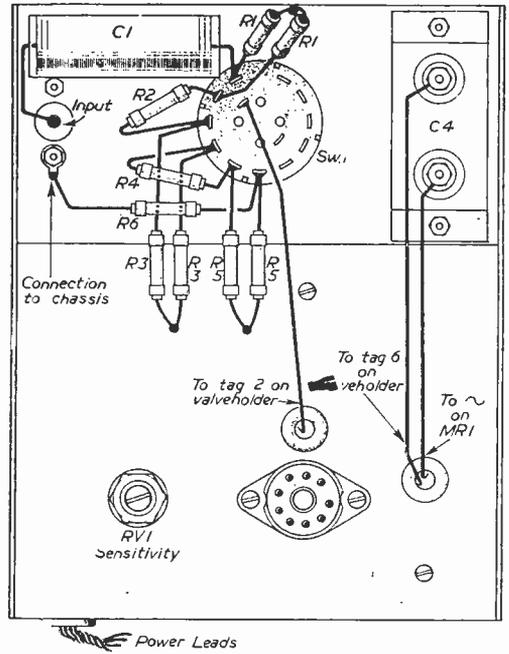


Fig. 5.—Above chassis and panel wiring details.

adjusted by RV1. As a check on open-loop gain, turn RV1 to the position of maximum sensitivity and check that the meter is 7 to 10 times as sensitive as it was when correctly adjusted.

When correctly adjusted the meter reading is unlikely to be in error by more than +1 per cent. or -4 per cent. over any of the operating ranges speci-

**ATTENUATOR RESISTORS**  
(All Welwyn 1/4 watt High-Stability)

R1—700 K, i.e. 200 + 500 K  
 R2—200 K  
 R3—70 K, i.e. 20 K + 50 K  
 R4—20 K  
 R5—7 K, i.e. 2 K + 5 K  
 R6—3 K, i.e. 2 K + 1 K

With these resistors, ranges are :

1—300 mV  
 2—1 V  
 3—3 V  
 4—10 V  
 5—30 V  
 6—100 V

fied above. Changing valves may introduce up to 2 per cent. variation, so recalibration is desirable but not essential.

When the meter is used with speech or music signals, it must be remembered that whilst calibration is in terms of r.m.s. voltage this is only true for sinusoidal inputs, as the meter actually measures average voltage.


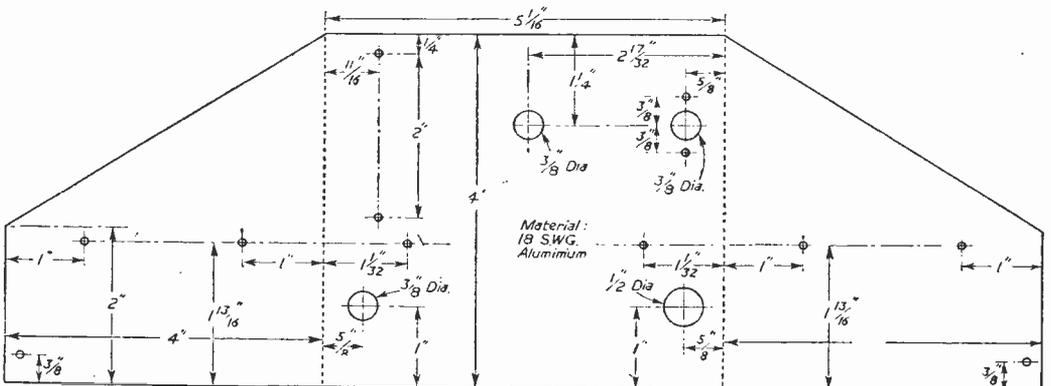


Fig. 6.—Case bending and drilling details.

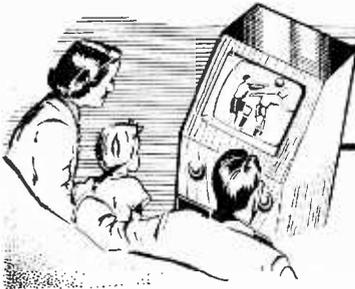

## UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

### NEWSREELS

**N**EWSSREELS have been with us in one form or another for many years. The life of a cinema newsreel used to be about six weeks, descending during this time from the glittering presentation of the West End theatres to the flickery projection of the small town and fairground fit-ups. TV has outmoded the smaller cinemas, and the life of the newsreel is now little more than one week. TV newsreels and film sequences have the ephemeral life of one day, after which they shed their aura of topicality and are relegated to the junk bin or the film vaults. From the junk bin they go to the processors who recover various ingredients from the film base and the photographic emulsion, and the silver from the latter possibly goes to making more photographic emulsions and, perhaps, more TV newsreels. The silver photographic image of Sir Anthony Eden of to-day might, in fact, be the chemical reincarnation of Lloyd George or Mr. Asquith of years ago. More interesting is what happens to the film which is stored away in the film vaults, for use again—but when?

### FILM ARCHIVES

**T**HE BBC has been building up a library of picture and sound records of this day and age for some considerable time. Like the Pathé, Movietone and other newsreels, they have accumulated huge footages of all the national events together with many other filmed features, for future use. Tele-filmed plays are occasionally brought out for reissue or prints are made for export. In the vaults, too, are thousands of useful shots of rough seas, huge crowds, big fires, aerial views, animals, sunsets, snowstorms, etc. etc., any of which can be produced and used for the film sequences in dramatic or documentary live TV subjects. The historic items are

used from time to time in the popular scrap-book features. Television consumes large footages of these items week by week and the calls upon the resources of the film libraries maintained by the BBC and also by all the I-TV companies are constant. For many specialised shots, the assistance of the film studios' film libraries is sought, and many a spectacular shot of arctic wastes or sun-baked veldt, previously seen in some super-film, is now finding its way into the complicated pattern of live TV presentation by both BBC and I.T.A. These special shots, frequently only 3ft. or 4ft. long, are usually quite expensive to buy and are, in fact, leased for use in one named subject only; after use, they must be returned to the owner-library or destroyed. Nevertheless, it is far cheaper to pay £10 or £20 or more for such a shot than to attempt to film it afresh. Library shots are usually leased at so much per foot, but the footage of individual shots is quite small. There is a good deal of interchange between the various libraries and a special organisation has sprung up to standardise on procedure, charges, descriptions and filing systems. Physically, the problem of actual storage of film has been eased considerably with the introduction of safety-base film. Until about two or three years ago the highly inflammable nitrate film base was used, and film vaults had to be fitted with elaborate and expensive sprinkler systems. Now, film vaults merely have to be brick-built and generally convenient, with iron shelves; sprinklers are not required. Storage space for film libraries has expanded enormously as a result.

### "LE MANS"

**O**NE of the very best filmed items put out by the BBC was the "special" they made of the 1956 Le Mans car race. In record time there was presented a docu-

mentary record of the event, edited with the smoothness and slickness of a feature film, complete with commentary, sound effects and a little music. The highlight of this particular film was a trial run around the course by Mike Hawthorn, which was filmed with a camera mounted on the tail of the car, looking over Mike's shoulder. A microphone was strapped to his face and the viewer was able to hear as well as see just what goes on at all points of this exciting course: his commentary was characteristic and crisp, and added to the thrill of this epic shot.

I understand that a Newman Sinclair camera was used for the picture and a portable tape recorder for sound, the recording subsequently being transferred to magnetic sound-on-film for transmission purposes. Here is an item that well deserves to go into the BBC archives for future reference! It has been selected by the British Kinematograph Society for showing at one of the coming season's meetings, as an example of "outstanding filmcraft." The Shell-Mex film of the 1954 Le Mans race was very fine, compiled from dozens of cameras, painstakingly edited together and served up with typical French accordion music. But the latest BBC film has a supercharged zip even more in tune with the roar of the hotted-up racing engines.

### "WHO GOES THERE!"

**T**HE rapidly changing taste of the viewers for comedy is having an amazing effect upon the impact of the older stage comedies when they are presented on TV. *Who Goes There* was one of the comedy successes of 1951 when it was put on by Henry Sherek at the Vaudeville Theatre. And yet in 1956, this comedy by John Dighton seemed to be very much dated, with dialogue and situations which failed to arouse much mirth, and with presentation which seemed

to be almost static. It seems to me that we have become accustomed—or possibly drugged—to expect the pace and high-speed quips of the Burns and Allen Show and *I Love Lucy*, or the crazy nonsense of the Goons. Comedies which rely upon situations alone have less appeal, unless played with expert "character" interpretations. This, however, requires the presence of actors of the calibre of Alec Guinness, Peter Ustinov or Cecil Parker.

### GOONATICS

THE short seasons we have had of the Goons on *Idiot's Weekly*—*Price Twopence* and *A Show Called Fred* started a new era in crazy humour, which seems to be breaking out in various other programmes, particularly on commercial TV. Harry Secombe has left the gang, but Harry himself, Peter Sellers, Spike Milligan and others seem to bob up in all kinds of shows to provide the quota of new style comedy. Peter Sellers appeared as a phoney operatic singer and performed a riotous duet with Dicky Valentine in his own TV Show. Dicky co-operated with engaging good humour and even took part in an amusing simultaneous dance with Peter Sellers. The song was "I'm walking backwards for Christmas," a burlesque of the sentimental ballads of which we hear so many. The crazy goon song has become quite a best-selling gramophone record, and this in itself has increased the public taste for goonatic humour.

### "RATS TO YOU!"

THE series of vaudeville programmes specially arranged for the BBC by that unique organisation, the Grand Order of Water Rats, has come to a dismal end, carrying with it evidence of the troubles and trials which beset its organisation. It started off hopefully, but not too successfully, with the veteran music hall star Wee Georgie Wood looking after the interests of the Water Rats, supported by a committee of fellow music hall artists. Following a few bad press notices of the first show there was considerable bad feeling about the choice of artists and the general production arrangements and Georgie Wood was asked to hand the reins elsewhere. The internal strife was made public in the theatrical newspapers and many artists weren't too keen in taking part, and the

show degenerated into a conventional cabaret show of a type which is now considered by viewers to be of the "corny" variety. This is a pity, because there is an enormous range of talent available in the Water Rats fellowship of music hall artists, and their Rats Revel Shows for charity given at theatres or at banquets at the big hotels have always sparkled with fun, even if that fun was what might be termed "robust." Most of these shows have been produced by Wee Georgie Wood whose knowledge of the business and whose flair for giving scope for such famous "ad-libbers" as Tommy Trinder, Bud Flanagan and the Crazy Gang has been an enormous asset. Let us hope that the BBC appoint someone to take the show thoroughly in hand before the next series commences, making use also of the people who made contributions in ideas, scripting and production which were such a bright feature of the Rats Revels.


### AMERICAN TV FILMS

THERE is no official quota for British TV films or British live TV features on commercial television. In the cinema, the quota calls for 25 per cent. of the films shown to be of British origin. In commercial TV the I.T.A. have the delicate responsibility of maintaining a "reasonable" proportion of items, filmed and live, which is of British origin. This seems to work out at about 85 per cent. of the total transmission hours. In other

words, the screen time of foreign (mostly American) features which is transmitted seems to be about 15 per cent. This American material looms prominently because it is the cream of the items considered suitable for British TV audiences and it achieves peak viewing times here. If the percentage of imported material grows greater, I have no doubt that the trade unions will nudge Sir Robert Fraser's arm as a reminder. All the same, a little more latitude in this matter would give all TV organisations—both I.T.A. and BBC—a much needed relief, creatively and financially. The consumption of new ideas is prodigious. No wonder there is a tendency to fall back upon amateur talent shows and parlour games.
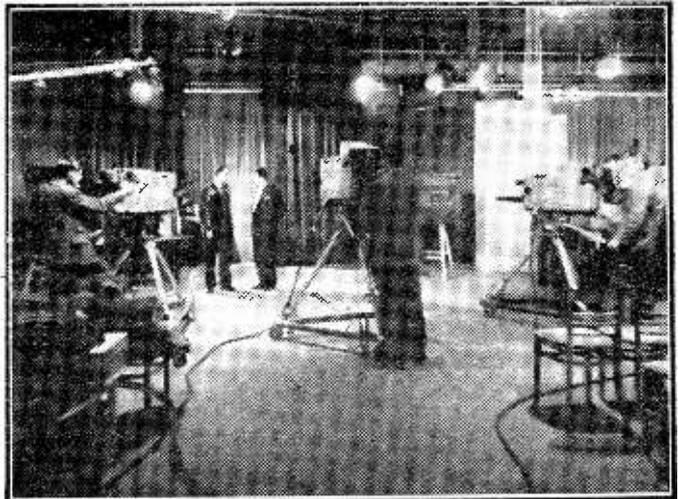
### "THE LAST ENEMY"


ANOTHER outstanding TV play, this time from AR-TV, was *The Last Enemy*, a dramatisation of Richard Hillary's wartime biography. Technically, this was a very skilled mixture of filmed and live television. For the plane sequences and montages, official and newsreel sources must have been drawn upon in a big way. All fitted in perfectly with the narrative, spoken by Peter Murray, who also portrayed Hillary. Of all of the TV plays or features which have depicted the lives of pilots who took part in the Battle of Britain, this, I thought, was the most moving: Peter Murray is a young actor who should be watched—here is another TV star.




Shooting a live scene on No. 1 stage of the Granada centre, a description of which will be found on pages 171 to 173.

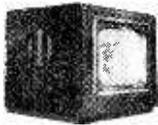**12in. TV. CABINET—15/-**

We are offering these at not much more than the cost of the plywood they contain. If not wanted for TV, many useful items can be made—record storage cabinet, H.P. loud-speaker case, book case, etc. Price 15/-, carriage 3/6.



**"SNIPERSCOPE"**

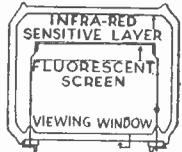

"Cats eye" used for seeing in the dark. Will work burglar alarms, counting circuits, smoke detectors and the hundred and one other devices as will the simpler type of photo cell. Price 5/- each. Post and ins. 1/-. Data will be supplied with coils if requested.

**WESTINGHOUSE (U.S.A.) METERS**



All flush mounting type, outside diameter of face 3 1/2 in.

- 0-500 v. D.C. .... 25/-
- 0-1.5 kV D.C. external multiplier supplied..... 35/-
- 0-2.5 kV D.C. external multiplier supplied..... 35/-
- 0-15 v. A.C. moving iron..... 30/-
- 0-1 mA. .... 25/-
- 0-50 mA. .... 25/-
- 0-100 mA. .... 25/-
- 0-150 mA. .... 25/-
- 0-250 mA. .... 25/-
- 0-500 mA. .... 25/-


**CONNECTING WIRE**

P.V.C. covered in 100ft.coils—29 a coil or four coils different colours, 10/- post free.

**W.D. CIRCUIT DETAILS**

- Diagrams and other information extracted from official manuals. All 1/6 per copy, 12 for 15/-.
- American Ser-78 receiver vice Sheets 76 Receiver R23 ARC 5
  - A-134 R1116 A
  - BC-348 RA-1B
  - BC-312 AR88D
  - R-103A AN.A.PA-1
  - R.C.342 78
  - PA-1B 78
  - R-208 R.T.18
  - R-1155 CAY-46-AAM-
  - R-1124A RADAR
  - R-1132A, R-1481 A.S.B.-3
  - R-147 Indicator 62A
  - R-1224A Indicator
  - R-1062 A.S.B.3
  - R-1375 Indicator 62
  - B.C.1206-A B Indicator 62
  - B-455-A (or -B) R.F. unit 24
  - B-454-A (or -B) R.F. unit 24
  - R-453-A (or-B) R.F. unit 26
  - Transmitter R.F. unit 25
  - T1154 R.F. unit 27
  - Pfity-eight Wireless set No. 49
  - walkie talkie valves
  - Frequency meter B.C.221
  - R.109

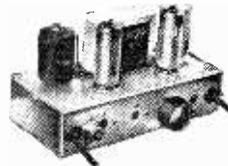**PRODUCTION INCREASED—CIRCUIT IMPROVED—PRICE REDUCED**




Today's best value in Band III converters suitable for your T.V. or money refunded. Complete ready to operate. 49 6 mains, post a n d insurance, 3/6.

**T.R.F. CONVERTOR**

New this month is a convertor for T.R.F. Set Viewmaster-Electronic Engineering, etc. Small model to the T.V. are necessary as this must be turned into a superhet to stop re-radiating. Price complete with two valves £6.10.0 assembled—ready Oct. Nov.

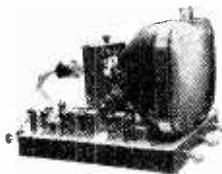**THE UNI—T.V.**

Undoubtedly the most up-to-date television for the home constructor. You can build all or only part and the set when finished will be equal to a factory-made equivalent. What other constructor T.V. has all these features? ★Made up units if required.



- ★ All miniature valves.
  - ★ Metal rectifier.
  - ★ No expensive transformers.
  - ★ 13-channel circuitry.
  - ★ Multi-vibrator time bases.
  - ★ Ferrucube, E.H.T. and scan coils.
  - ★ 34/38 Mcs I.F.
  - ★ Suitable for any modern 12, 14 or 17" tube.
  - ★ Modern contemporary cabinet if required.
- The building cost (less tube) is only £29.10.0, plus 10-carriage and insurance. All parts guaranteed 12 months. Full information and data free with parts or available separately price 3/6.

**THE "CRISPAN" PORTABLE RADIO**



A 4-valve truly portable battery set with very many good features as follows: Ferrite rod aerials, low consumption valves, superhet circuit with A.V.C. ready - built and aligned chassis if required, beautiful two-tone cabinet covered with I.C.I. Rexine and Tygan. Guaranteed results on long and medium waves anywhere.

All parts, including speaker and cabinet, are available separately or if all ordered together the price is £7.15 complete, post and ins. 3/6, ready-built chassis 30/- extra. Instruction booklet free with parts or available separately price 1/6.

**THE REALITE**



This is a complete fluorescent, fitting, stove enamelled white with starter and ballast all ready to install. Price 25/-, plus 4/6 carriage and packing. 40-watt tube. 10/-, no extra for backing if ordered with fitting.

**CROYDON BRANCH OPENING**

We have taken the Lease of 268, London Road, Croydon, and hope to open this month.

**ELECTRONIC PRECISION EQUIPMENT, LTD.**


Post orders should be addressed to E.P.E., LTD., Dept. 5, Sutton Road, Eastbourne. Personal shoppers to one of these addresses please.

42-46, Windmill Hill, 152-3, Fleet Street, 29, Strand Green Rd., 249, Kilburn High Road, Kilburn, E.C.4. Phone: ARChway 1049 MAIda Vale 421.

Half day, Wednesday. Half day, Saturday. Half day, Thursday.


**THE SKYSEARCHER**

An all mains set for 19 6

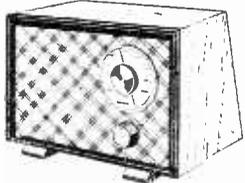

This is a 2-valve plus-metal rectifier set for beginners, also makes a first second set for the bedroom, workshop, etc. All parts, less cabinet, chassis and speaker, 19 6. Post & ins. 2/6. Data free with parts or available separately 1/6.

**THERMOSTATS**

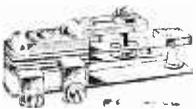


Useful for the control of appliances such as convector, blue-prints, vulcanisers, hot plates, etc. Adjustable to operate over the temperature range 50-550 deg. F. 3 amp. 3 6 ; 5 amp. 8 6 ; 2 amp. QMB. 5 6 ; 5 amp. QMB. 15 -




**MULLARD AMPLIFIER "510"**

A Quality Amplifier designed by Mullard. Power output exceeds 10 watts. Frequency response almost flat from 10 to 20,000 C/P.S. For use with the Acos "High G" and other good pick-ups. Made up and ready to work for £12 10/- or 85/- deposit, plus 10-carriage and insurance.

**MAINS-MINI**

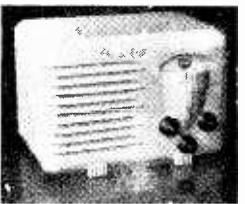

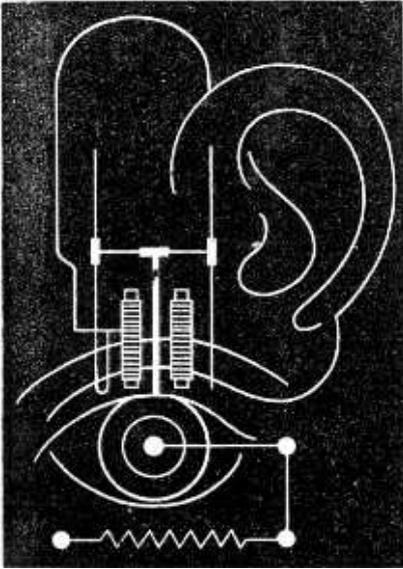Uses high-efficiency coils, covers long and medium wavebands and fits into the neat white or brown bakelite cabinet—limited quantities only. All the parts, including cabinet, valves, in fact, everything. £4.10/-, plus 3/6 post. Constructional data, free with the parts, or available separately 1/6.



# SMITH'S FOR TECHNICAL BOOKS

Books on radio theory, practice and maintenance for the beginner and books on new developments in circuit design, new components, methods of application, and the established text books can be obtained through your local Smith's shop or book-stall. Books not in stock at the branch can be quickly obtained from Head Office.

★ *Your stationery and printed matter can also be supplied through our local branch.*

## W. H. SMITH & SON FOR BOOKS ON ELECTRONICS

Head Office: STRAND HOUSE, LONDON, W.C.2

### VIEW MASTER CONVERTER

All items for the View Master Converter as described in "Practical Television" are available from stock and can be supplied by return of post. Full details are given in our lists, which are available free.

#### FULL INSTRUCTIONS NOW AVAILABLE

We can supply the special "Practical Television" booklet giving construction information from stock. Price 2/6, plus 3d. postage.

#### COMPLETE KITS

Complete Kits are available as follows :

KIT A.—All specified components with new Mullard Valves. **£8.18.0.**

KIT B.—All specified components with alternative valves. **£8.2.0.**

Remember that our kits are really complete.

#### CREDIT TERMS

Credit Terms are available on the above kits.

KIT A.—Deposit **£1.6.0** and seven monthly payments of **£1.6.0.**

KIT B.—**£1.4.0** deposit and seven monthly payments of **£1.4.0.**

### WATTS RADIO

8, Apple Market, Kingston-on-Thames, Surrey

Telephone : KINgston 4099.

### ARTHURS HAVE IT!

#### LARGE STOCKS OF VALVES AND C.R.T.s.

##### AVO METERS IN STOCK

Avo Model 7	—	—	—	—	£19 10 0
Avo Model 8	—	—	—	—	23 10 0
Electronic Test Unit	—	—	—	—	27 15 0
Electronic Test Meter	—	—	—	—	40 0 0
AC/DC Minor	—	—	—	—	12 0 0
* Cossor Oscilloscopes Model 1052	—	—	—	—	104 0 0
" " " 1035	—	—	—	—	120 0 0

##### Full range Taylors Meters. List on request.

LEAK Pick-up Arm	—	—	—	—	2 15 0
" Long Play or Standard Heads With Diamond Stylus	—	—	—	P.T. ...	1 3 1
" Matching Transformer	—	—	—	—	5 15 0
				P.T. ...	2 8 4
					1 15 0

Leaflets on Request  
**JASON AF/FM Tuner**, complete with valves and automatic frequency control, also cascade input — — — — — **£28 13 0**

**LATEST VALVE MANUALS**  
**MULLARD, 10/6, OSRAM & BRIMAR No. 6, 5/- each,**  
**OSRAM Part 2, 10/-.** Post 9d. each extra.  
**TRANSFORMER for 200/230 v., 37/6.**


Terms C.O.D. OR CASH with order and subject to price alterations and being unsold.

*Est. 1919*  
**Arthurs**

PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS: **Gray House**  
**150-152 Charing Cross Road, London, W.C.2**

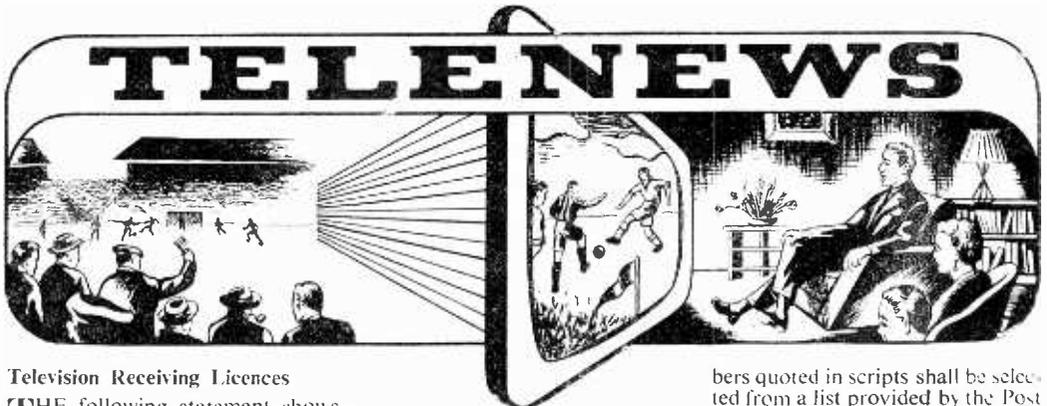TEMPLE Bar 5833/4 and 4765  
 TELEGRAMS—"TELEGRAY, WESTCENT, LONDON."  
 CABLES—"TELEGRAY, LONDON."



### Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of August, 1956, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal ... ..	1,344,110
Horn Counties ... ..	695,058
Midland ... ..	1,038,454
North Eastern ... ..	923,138
North Western ... ..	868,436
South Western ... ..	413,773
Wales and Border Counties ... ..	336,689
Total England and Wales ... ..	5,619,658
Scotland ... ..	377,446
Northern Ireland ... ..	47,226
Grand Total ... ..	6,044,330

### I.T.A. Lichfield Station

THE I.T.A. announces that, in association with Pye Radio Ltd., they have been able, by arranging for the simultaneous parallel operation of the two existing transmitters, to increase the power of their Lichfield station from 50 to 100 kW.e.r.p. This is an interim measure and it is expected that it will result in a more even and homogeneous pattern of reception within their Midland service area. It remains the Authority's intention to increase the power to 200 kW.e.r.p. as soon as possible, probably in the autumn.

### BBC TV Service in the Channel Islands

THE BBC announces that its Channel Islands Television Service from the transmitting station at Les Platons, Jersey, which has been in operation experimentally since October last year, is now working on a permanent basis.

The service was started on an experimental basis because the television programme for re-trans-

mission in the Channel Islands had to be received by radio from the temporary low-power transmitter at North Hessary Tor in South Devon, or alternatively from the station at Wenvoe in Wales. Because of the distances involved the quality of the picture was not at times up to the required standard, but the arrangement enabled transmissions to be started in the Channel Islands earlier than would otherwise have been possible. The recent completion of the permanent station at North Hessary Tor and the increase in its radiated power has made possible reliable reception of the television programmes for re-transmission by the Les Platons station, which now joins the BBC's network of television stations providing a regular service.

### Telephone Numbers in Radio Plays


TELEPHONE numbers are frequently used in plays broadcast by the BBC and I.T.V. In the past some listeners and viewers when they have heard a telephone number have themselves called that number out of curiosity. To avoid any embarrassment that might follow from a live number being accidentally selected, arrangements have been made that in future all telephone num-

bers quoted in scripts shall be selected from a list provided by the Post Office. These are of two kinds, numbers which have not yet been issued to the public and the numerical equivalent of TIM and other fee-paying services. Thus, no embarrassment will be caused to private subscribers, and if one of the latter numbers is chosen, callers will at least get something for their money.

### Temporary Station at Sandale

THE BBC announces that it is hoped to have a temporary television station in operation before the end of the year at Sandale, some 14 miles south-west of Carlisle.

The temporary station, compris-

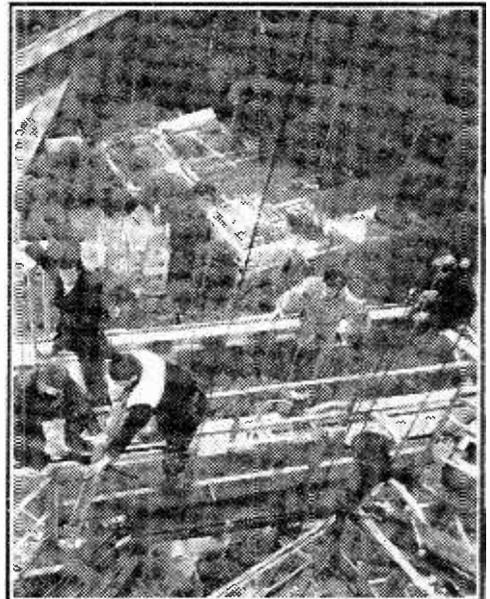

At work on the BBC television mast at Crystal Palace (440ft. high).

ing low-power vision and sound-transmitting equipment installed in portable buildings, mobile power plant, and a temporary 100ft. mast to carry the aerials, is being provided so that television can be made available in Cumberland at a much earlier date than would otherwise have been possible. It will continue in service until the permanent medium-power station with its 500ft. mast, to be built on the same site, can be completed, which it is hoped will be before the end of next year.

Because of its lower power the coverage of the temporary transmitter will not be as great as that to be provided by the permanent station, but it is expected to include Carlisle, Wigton and Maryport. In favourable conditions reception may also be satisfactory in Penrith, Cockermouth and Workington.

The temporary station will operate on the same frequencies as those which are to be used by the permanent station so that receivers and aerials set up for reception of the temporary station will not have to be changed when the permanent station comes into operation. The technical details of the transmissions are as follows:

Vision frequency : 61.75 Mc/s  
Sound frequency : 58.25 Mc/s  
Polarisation : Horizontal.

#### Television from a Helicopter

ON Thursday, September 20th, Pye Ltd., in conjunction with Bristol Aircraft Ltd., held a series of demonstrations to show the possibilities of airborne television.

The demonstrations, which were held in Cambridge, were attended by air-attachés from many countries, including the U.S.S.R., high-ranking officers from County Police Forces, Scotland Yard, and the three Services, and officials from the Home Office and the BBC.

A Bristol "Sycamore" helicopter, installed with a complete television transmission system specially developed by Pye, broadcast pictures of Cambridge, and also of instruments inside the aircraft, to several 21in. TV monitors at an hotel in the centre of Cambridge. Permission was granted for the helicopter to land on Parker's Piece, which is a famous recreation ground adjoining the hotel in which the receivers were installed.

The camera system used was a miniature Pye industrial unit, the

transmitter having been specially constructed for experimental work. All the TV equipment was adapted to work from the 24-volt power supply of the helicopter. The aircraft was fitted with a new type of aerial that has been designed to avoid TV interference from the rotor blades.

#### TV Developments in Hungary

BUDAPEST television station, which has been broadcasting test film transmissions on low power for more than a year, plans to go over to its new 30-kilowatt transmitter by next April.

The transmitter has been bought from East Germany.

A mobile outside-broadcast unit has been bought from Britain and an additional one is being made by Hungarian technicians at the Ikarus factory.

Studio programmes will come from studios now being constructed in the city's Lenin Institute. These will be relayed to the Szécsenyi Hill transmitting station overlooking the city, which with aerial has a height of 340ft.

In 1958, a five-kilowatt station is to be installed at the northern city of Miskolc, and the following year another station will be erected on a site yet to be chosen to serve the western part of Hungary.

Then work will begin on a chain of relay stations to link Hungary with Prague, Vienna and Berlin—and later, probably, with Moscow.

#### Yorkshire Press and Publicity

##### Manager

MR. TOM BENTLEY has been appointed Press and publicity manager for A.B.C.-TV's Yorkshire station.

Mr. Bentley joins A.B.C.-TV from a Bradford advertising agency, Charles Walls & Partners Ltd., where he has been Public Relations Officer and Television Executive for the last two years. Before this he was Public Relations Officer at

Nevin D. Hirst (Advertising) Ltd., Leeds and London, and Tattersall Advertising Ltd., Harrogate.

Mr. Bentley has a wide experience as a journalist and Public Relations Officer. He was P.R.O. for the Central Institute of Art and Design and the National Gallery in London for 18 months, and has lectured extensively for the Central Office of Information in South Africa.

#### Over 6,000,000 on TV

DURING August the number of television licences increased by 64,820 to 6,044,330.

14,389,474 broadcast receiving



A scene during recent U.S. Army trials of the use of TV in relaying to command forces at the rear, scenes at a battle-head. The chain consists of three field cameras, an airborne camera, and an Iconoscope film chain.

licences, including 6,044,330 for television, and 307,082 for sets fitted in cars, were current in Great Britain and Northern Ireland at the end of August, 1956.

#### I.T.A.'s Croydon Transmitter Power

THE experiments carried out by the Independent Television Authority in association with Marconi's Wireless Telegraph Company to increase the power of the Croydon station have been successful, and as from September 8th, the power was raised from 60 to 120 k W.e.r.p.

**G.R.T. ISOLATION TRANSFORMER**

Type A. Low leakage windings. Ratio 1:1.25 giving a 25% boost on secondary. 2 v., 10.6; 4 v., 10.6; 6.3 v., 10.6; 10.8 v., 10.6; 13.3 v., 10.6.

Type B. With main primaries, 12.6 each. Type B. Mains Input 220-240 volts. Multi Output 2, 4, 6.3, 7.5, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50% respectively. Low capacity, suitable for most Cathode Ray Tubes. With Tap Panel, 21s. each.

Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 220/240 volts. Output 2-21-21-21-3 volts at 2 amps. With Tap Panel, 17.6 each. NOTE.—It is essential to use main primary taps with T.V. receivers having series-connected heaters.

TRIMMERS, Ceramic, 30, 50, 70 pf., 6d., 100 pf., 150 pf., 1.3; 250 pf., 1.6; 500 pf., 750 pf., 1.9. RESISTORS. All values, 10 ohms to 10 meg., 4 w., 4d.; 1 w., 6d.; 1 w., 8d.; 2 w., 1s. HIGH STABILITY, 1/2 w., 1s., 2s. Preferred values 100 ohms to 10 meg., 1/2 w., 1s., 2s.

WIRE-WOUND RESISTORS 1/3 16 watt, 25 ohms—10,000 ohms ..... 1.6 16 watt, 25 ohms—10,000 ohms ..... 2/1 16,000 ohms—50,000 ohms, 5 w., 1.9; 10 w., 2.3. **KNOB, GOLD ENGRAVED.**—Walnut or Ivory, 1/2 in. diam., 1/8 each. Not engraved, 1s. each.

**12/6 PURETONE RECORDING TAPE**

1,200 ft. on standard fitting 7" Plastic reels. Brand new, boxed, 12.6. Spools 5" metal, 1/6, 7" plastic, 4/3.

OP TRANSFORMERS. Heavy Duty 50 mA., 4.6. Multitap, push-pull 6.6, Tapped small pentode, 3.9. L.F. CHOKES 15 10 H. 60/65 mA., 5-; 10 11. 150 mA., 10.6; 15 H. 150 mA., 12.6.

MAINS TRANS. 330-350, 80 mA., 6.3 v. Tapped 4 v., 4 s.; Tapped 4 v., 2 s.; DITTO 21 v., 21 v. HEATER TRANS. Tapped prim., 200/250 v., 6.3. 11 amp., 7/6; Tapped sec., 2, 4, 6.3 v., 11 amp., 8/6. VCR97 TESTER FULL PICTURE, 82.

COPPER PLATED AERIAL RODS. 1 x 12 in. push fitting, 3/4 doz. p.p., 1 p. 1/2.

ALADDIN FORMERS 21 in. core, 1 in., 8d.; 2 in., 10s. FORMERS 58378 and Cans TV1.2, 2 in. 8d. x 2 in. and 1 in. sq. x 1 1/2 in., 2s. ea. with cores.

TYANA.—Midget Soldering Iron, 200-240 v. or 250-250 v., 18.9. Solon Instrument Iron, 24s.

MIKE TRANSF. Ratio 50:1, 3/8 sec.; 100:1, 10/8. MAINS DROPPERS. 3 x 1 1/2 in. Adj. Sliders, 3 amp., 750 ohms, 4.3; 2 amp., 1,000 ohms, 4.3. LINE CORD. 3 amp., 60 ohms per foot, 2 amp., 100 ohms per foot, 2 way, 6d. per foot, 3 way, 7d. per foot.

LOUDSPEAKERS 2 P. 3 OEM. 5 in. Hoodlams, 17/6. 7 in. x 4 in. Goodman, 21s. 3 1/2 in. square, Elac., 21s. 5 in. Elac., 21s. 6 in. Goodman, 18/6. 10 in. R. & A., 30s.

7SL Tweeter, LSH73, 12.8. 12 in. Plessey, 30s. 5 in. M.E. 25 K or 2 K. Heil, taped O.P. trans., 24.6. CRYSTAL DIODE, G.E.C., 2s. Crystal Books, 1s. GEX34, 4d., Handbook of Germanium Circuits, 2.6. HIGH RESISTANCE PHONES. 4,000 ohms, 1/2 p.

CRYSTAL MIKE INSERT by Aeos, precision engineered. Size only 1 1/4 x 3/16 in. Bargain Price 6/6. No transformer required.


SWITCH CLEANER Fluid, squirt spout, 4.3 tin. TWIN GANG TUNING CONDENSERS. .0005 mid. midget, less trimmers, 6/6; .0005 Standard size with trimmers, 9s.; less trimmers, 8s.; ditto, sealed, 2/6; .001 mid. 3-gang, 7/6.

SPEAKER FRIT. Expanded metal. Silver, 15 1/2 in. x 9 1/2 in., 2s. each. TAPEMASTER RECORD PLAY HEAD, 45s.

**VALVES**

A SMALL SELECTION FROM OUR STOCKS

All Boxed	New & Guaranteed
8/6	5/6
145	95A
171	912
185	EF50
384	Equip.
374	8F61
514	8F4
AM6	EF92
6AT6	3/6
6J7	6H6M
6K8	7/6
6SL7	6V6G
6SN7	6BW6
6X6GT	6F6
EB33	6K7M
EF59	6K7M
8y.v. Red	11/6
8F91	EY51
	U25
	PL51
	6/6
	10/6
	5/24
	12AT7
	EB41
	EBB80
	6Y1435
	EB34
	6YR2
	EP412
	EL41
	EL41
	EL40
	KT34C
	MF11
	PL81
	PL81
	12AT7
	3574
	6U7

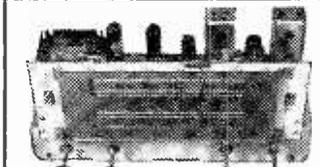

**ALL WAVE RADIOGRAM CHASSIS**

THREE WAVEBANDS FIVE VALVES  
S.W. 16 w.—50 m. LATEST MULLARD  
M.W. 200 m.—550 m. EH42, EF41, EB44,  
L.W. 800 m.—2,400 m. EL41, EZ40.

12 month Guarantee.  
A.C. 200-250 v. 4-way Switch; Short-Medium-Long-Gram. A.V.C. and Negative feedback 4.2 watts. Chassis 13 1/2 x 5 1/2 x 2 1/2 in. Glass Dial 4 1/2 x 4 1/2 in. horizontal or vertical available. 2 Pilot Lamps, Four Knobs, Walnut or Ivory. Aligned and calibrated. Chassis isolated from mains. T.S.L. Tweeter Supplied Free!


**10 gns.** Carr. & Ins. 4/6.

TERMS: Deposit £5.50 and six monthly payments of £1.

MATCHED SPEAKERS FOR ABOVE CHASSIS  
5 in., 19.6; 10 in., 25s.; 12 in., 30s.

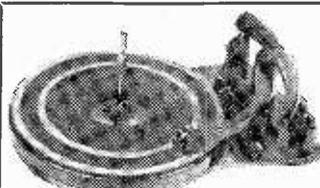**R.C.S. SCOOP**

Collaro Auto-change RC531 for 78 r.p.m. 10 in. and 12 in. records. Brand new in maker's boxes! High impedance lightweight Pick-up with sapphire needle, will match any Amplifier or Radio. Less than half price.  
**£5.19.6** Carr. & Ins. 5/6.



**£7-19-6** Post Free.

TERMS: Deposit £4 and six monthly payments of 15s.

Brand new Plessey 3-speed Autochanger Xtal. Head with Dupont sapphire stylus, 30 ops. Also B.S.R. MONARCH Lightweight Pick-up with Walnut mounted on baseplate. Auto-stop fitted.  
WALNUT VENEERED PLAYING DESK 10/6 extra.

**EXCEPTIONAL OPPORTUNITY**

COLLARO 4-speed Single Record Player, including heavyweight turntable and lightweight Pick-up with turnover Xtal mounted on baseplate. Auto-stop fitted.  
**OUR PRICE, 6 gns.** carriage 4/-.

**ALLDRY UNIT POWER PACK**

Replaces Battery B114, etc., 63 v. plus 1 1/2 v. Size 4 1/2 in. x 3 1/2 in. x 4 1/2 in. 4-pin socket. Same as battery. ONLY 1s. a year to run on A.C. 200/250 v. FAMOUS MAKE. LIST PRICE, 65s. OUR PRICE, 39/6. Ready for use.

B.S.R. MONARCH. 3-speed Motor and Turntable with selecting switch for 33, 45 and 78 r.p.m. records. Input 200 v. at 200/250 v. A.C. ONLY 1s. a year to run on A.C. 200/250 v. LIGHTWEIGHT Pick-up with Aeos Xtal turnover head, separate Sapphire stylus for L.P. and Standard records. SPECIAL OFFER, THE TWO: £4.12.6, post 2/6.

T.V. PRE-AMP (McMICHAEL). Tunable Channels 1 to 5. (Will Amplify Output of your Band 3 Converter.) Midget size. High Gain Fringe Model. B.A.T. Valve. Full Instructions. Ready for use. (H.T. 200 v., L.T. 6.3 v., 3 amp. required.) BRAND NEW, 25s. extra.

MAINS POWER PACK for above, 25s. extra. SUPERHERT COIL PACK, 27.6. Miniature size 2 1/2 in. x 2 1/2 in. x 1 1/2 in. High v. O.T. Dust Cored Coils, Short, Medium, Long, Beam Switching. Single hole fixing. Complete with connection diagram, and circuit.

**TELETRON BAND 3 CONVERTER**

For London, Midland and Northern Transmissions.

Ready all T.V. makes. T.R.F. or Superhet. Ready wound coils, two EB90 valves, all components, punched chassis, circuit diagram, wiring plans, COMPLETE KIT for mains operation 200-250 v. A.C. £33.00.  
AS ABOVE, LESS POWER PACK. Requires 200 v. 20 mA. H.T. 6.3 v. 50 mA. L.T. £25.0. Mains Transformers to above Spec. ... 10.6 Min. Workinghouse Rect. ditto ... 8/6 B.H.C. T.V. Aerial crossover unit ... 7/6 Pinch and drilled chassis ... 8/6 Larger chassis for Mains Model ... 6/- Television Cabinet with plans ... 15/- Full plans and circuit details ... 6d.

**Volume Controls**

80 ohm CABLE COAX Long spindles. Guaranteed. Semi-car spaced. Polystyrene insulated. 1 in. dia. 1000 ohms to 200,000. Stranded core. 6.3 v. No Sw. S.P.S. D.P.S.W. Losses cut 50% 3/- 4/- 4-9 STANFORD 8d. yd 1 in. of Low Tracks. 1in. Coax. 8d. yd

COAX PLUGS — 1- DOUBLE SOCKET ... 1.3 SOCKETS ... 1- OUTLET BOXES ... 4.6

BALANCED TWIN FEEDER, yd. 6d. 80 or 300 ohms. DITTO SCREENED per chassis ... 80 ohms only. WIRE-WOUND POTS. 3 WATT. Pre-set Min. T.V. Type. All values 25 ohms to 30 K, 3-4, 50 K, 4/-; Carbon 50 K, 2 to 20, 2/-

WIRE-WOUND 4 WATT. Pots. 2 1/2 in. Spindle Values, 100 ohms to 50 K, 5/6; 100 K, 6/6 CONDENSERS. New stock. 400 mfd., 7 K.V. T.C.C. 5.6. Ditto, 20 K.V. 9.6; 100 pf. to 500 pf. Micaf. 6d.; Tubular 500 v., 500 to 0.01 mfd., 9d. .05, 1.1, 2.5, 1.6; mfd., 1.9; 1.500 v., 9d.; 3000 v., 1.3; 1 mfd., 2.900 volts, 4/-

CERAMIC CONDENSERS. 10s., 5 pf. to 500 pf., 1-; 500 pf. to 3,000 pf., 3/6. DITTO 1s., 1.5 pf. to 500 pf., 1.9; 515 pf. to 5,000 pf., 2/-

**I.F. TRANSFORMERS 7/6 pair**

465 Kc x Stup tuning Miniature Can., 2 1/2 in. x 1 1/2 in. High Q and good bandwidth. By Pye Radio. Data sheet supplied.

**NEW ELECTROLYTIC, FAMOUS MAKES**

TUBULAR TUBULAR CAN TYPES  
1275 v. 2- 100 25 v. 2/- 3- 16500 v. 5.6  
2 450 v. 2 1/2 8 500 v. 4.6 16 16500 v. 6/-  
4 450 v. 2- 15 16500 v. 5.6 25 120450 v. 5.6  
8 450 v. 2- 3 15 6/- 32 4 22500 v. 4.6  
8 500 v. 2- 3 CAN TYPES 32/450 v. 6.6  
16/450 v. 3.6 Clips 3d. 50 500 250 v. 7-  
16500 v. 4. 16 450 v. 3/6 164 4 120 275 v. 7.6  
32500 v. 5.6 32 350 v. 4/- 100 4 200 275 v. 7-  
325 v. 1.9 64 350 v. 4/- 100 4 200 275 v. 12.6  
70 25 v. 1.9 500 12 v. 3- 1,000 4 1,000 v. 5-  
50 50 v. 2- 8 16 450 v. 5/- 6.6

Screw Base Type 512, 8 500 v. 3/- 16500 v. 4/-  
SENTECEL RECTIFIERS, P.H.T. TYPE PLY-BASED VOLTAGES. 8V. 25. 3 K.V. 4.5 40 3.2 K.V. 6- K.V.45 3.5 K.V. 6/6; K/300 4 K.V. 7.3; K/100 8 K.V. 12.6; MAINS TYPE, R.M.I. 125 v., 60 mA., 5-; R.M.2, 100 mA., 6-; R.M.3, 120 mA., 8-; R.M.4, 200 v., 275 mA., 16-

PANEL LAMPS (New). L40, 250 v., A.C. D.C., 3.6. PANEL WARDEN, 300 v., 25 v., 3 each. Osmer Midget "O" type all. dist. core, 4- each. All ranges.

TELETRON, L. A. Med. T.R.F. with reaction, 3.6. FERRITE RODS, M.W., 8/9; M.A. L. 12.6. T.R.F. COILS A.H.F. 7/- pair.

H.F. CHOKES, iron core, 14 M.H., 3s. each

ALUMINIUM CHASSIS. 18 swg. modified. With 4 sides, riveted corners and lattice fixing holes, 2 1/2 in. x 3 1/2 in., 4.6; 3 x 6 in., 5.6; 4 x 7 in., 6.6; 4 1/2 x 9 in., 8.6; 4 x 11 in., 10.6; 5 1/2 x 14 in., 12.6; 18 x 16 x 3/4 in., 16/6.

FULL WAVE BRIDGE SELENIUM RECTIFIERS. 2.6 or 12 v., 11 amp., 8.9; 2 amp., 11/3; 1.4, 17.6. CHARGE TRANSFORMERS. Tapped input 200/250 v. for charging at 2.6 or 12 v., 11 amp., 13.6; 4 amp., 21s.

BERNARDS VALVE MANUALS I & II, 5/- ea. part. VALVE and TV TUBE equivalents books, 5-; ACID HYDROMETER. New Ex. cert. Unbreakable. Packed in metal case 7 x 1 1/2 in. dia., 4.6. WAVECHANGING SWITCHES.

5- 4-way 2 waffer, long spindle ... 6.6  
2 p. 2-way, 3 p. 2-way, short spindle ... 2.6  
2 p. 6-way, 4 p. 2-way, 4 p. 3-way, long spindle ... 3.6  
3 p. 4-way, 1 p. 12-way, long spindle ... 2.6

VALVE HOLDERS. Pax. Int. Oct. 4d., EF50, EA50, 6D, B12A, CRT, 1 Enc. 10s. 8, 5, 6, 7 and 9 pin, 1/-; SHOULDED Mazda and Int. Oct. 6d. B76, B8A, B8G, B9A, 9d., B76 with can, 1.6. VCR97 2.6, B9A with can 2.6. CERMIC, EF50, B76, B9A, Int. Oct. 1-; B76 with can 1.9.

BLACK CRACKLE PAINT, air drying, 3/- tin.

We have no connection with any other firm. Please address all Mail Orders correctly as below.

**RADIO COMPONENT SPECIALISTS 307 WHITEHORSE RD., WEST CROYDON**

OPEN ALL DAY—(Wed. 1 p.m.) 10 page list 3d.


Tel. THO 1665, Buses 133 or 68 pass door. 48-hour postal Service. P. & P., 1/-; £2 orders post free. (Export Extra.) C.O.D. Service 1/6

# Unfailingly fresh

Tobacco at its best. Player's Medium Navy Cut is once again supplied in the familiar pocket tin, vacuum sealed, which means that absolute freshness is retained and enjoyment assured whenever you buy it.

2 oz. tin 9/7d.

## PLAYER'S MEDIUM NAVY CUT TOBACCO

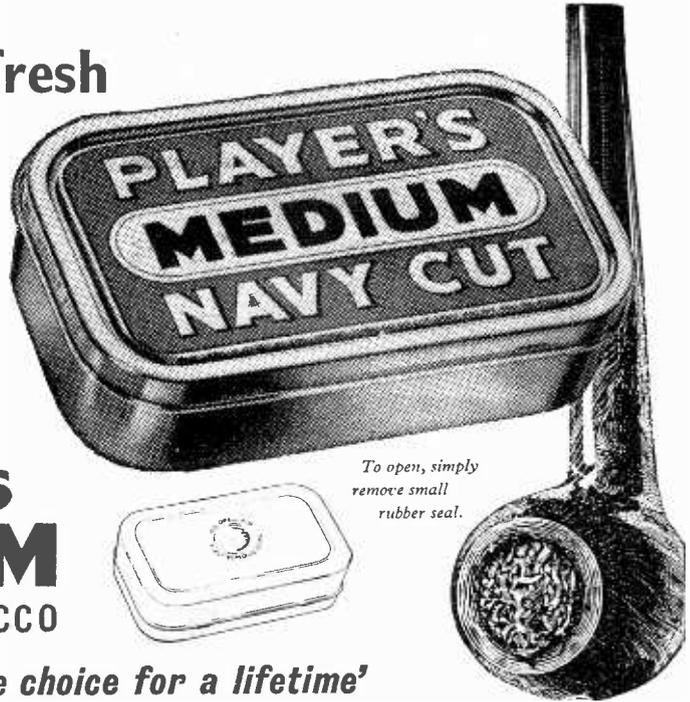

*'The choice for a lifetime'*

[NCT 94M]

# BENTLEY ACOUSTIC CORPORATION LTD.

EXPRESS SERVICE!!! C.O.D. ORDERS RECEIVED BY 3.30 P.M. EITHER BY LETTER, PHONE, OR WIRE, DESPATCHED SAME AFTERNOON. THE VALVE SPECIALISTS 38 CHALCOT RD., LONDON, N.W.1 PRImrose 9090 UNIQUE OFFER ANY PARCEL INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6d. EXTRA. SAVES TIME IN CLAIMS AND WORRY!

0Z4	6/-	6AC7	8/6	6P15	11/8	6X4	7/-	12K7	9/-	64M6	10/-	DA62	11/-	ECU82	10/6	FC13	12/6	N150	10/8	RD6	7/8	UY41	8/6
1A3	6/-	6AG5	8/6	6P17	9/6	6X4T	6/8	12Q7	8/6	72	4/6	DA91	7/6	ECU85	9/6	FC230	8/6	N152	10/6	SP(7)	8/6	V1507	5/-
1A5	6/-	6AG7	12/6	6P17	12/6	6Z4.84	12/6	12SA7	8/6	76	7/-	DA99	9/6	ECU84	12/6	GC22	12/6	N154	9/6	SP(7)	12/6	V1507A	£3
1C2	8/-	6AJ8	10/-	6P52	10/6	6Z7	12/6	12SG7	7/6	77	8/-	DC90	7/-	ECU85	10/-	GC24	14/-	N309	12/-	SP(1)	3/6	VMS4B	15/-
1D6	8/6	6AK5	5/-	6F23	12/6	7A7	12/6	12SG7	7/6	78	8/6	DF33	11/-	ECU91	6/-	H3	5/-	N329	9/6	TDD2A	8/6	VP(7)	8/6
1H5	11/-	6AK8	10/-	6G6	6/8	7B7	8/6	12SH7	5/6	80	8/6	DP97	9/6	ECF80	12/6	H63	12/6	N339	10/6	TH23	12/6	VP(7)	12/6
1L4	6/6	6AL5	6/6	6HG6	2/6	7C5	8/-	12SH7	8/-	83	8/6	DH4	8/6	ECF82	14/6	HK30	10/-	N709	10/6	TH30C	25/-	VP(7)	7/-
1L45	5/-	6AM5	5/-	6HM6	3/6	7C8	8/-	12SK7	6/-	85A2	12/6	DH76	9/-	ECH35	10/6	H12	3/-	OC3	9/-	VP22	10/6	VP23	6/6
1N5	5/-	6AM6	9/-	6J50	5/-	7H7	8/-	12SK7	8/6	150B2	12/6	DH77	8/6	ECH42	10/-	HL13C	7/6	OD3	9/-	U19	8/6	VP41	7/6
1N5	11/-	6AQ5	7/6	6J6	6/-	7Q7	8/-	12S47	7/6	210LF	3/-	DH12	9/-	ECR81	9/-	HL23	10/6	PABC80	U16	U12	8/6	VP33	10/6
1R5	8/6	6AQ8	10/-	6J7C	8/-	7S7	9/-	12U5G	7/6	807	8/6	DK91	8/6	ECI80	10/-	HL41	7/6	U15	U17	12/6	VP51	8/-	
1S5	7/6	6AT6	8/6	6J34TG	5/8	7T7	8/6	12V4	10/6	808	25/-	DK92	8/-	EP6	10/6	HL4DD	12/6	PC84	8/-	U22	7/6	W7	8/-
1T4	7/6	6B4	8/-	6J30PM	6/-	7Y4	8/6	18VPA	10/6	813	7/6	DK93	9/6	EP66	4/6	HL2	12/6	PCF80	8/-	U25	12/6	W7	6/6
1U5	7/-	6B7	10/6	6K7G	5/-	8A8	10/-	14R7	10/6	866A	12/6	D12	15/-	EP27A	9/-	HVR2A	7/6	PCF80	8/-	U31	9/6	W142	9/6
2A3	12/6	6B8G	4/-	6K9G	8/-	8I2	2/6	19H1	10/-	885	10/6	D133	9/6	EP39	6/-	KBC32	8/6	PCF82	11/-	U59	7/6	W150	9/6
2C26	4/-	6B8M	4/6	6K9GT	8/6	8I3	9/-	20L1	10/6	953	3/-	D192	7/6	EP40	11/6	KF35	9/-	PC138	12/6	U52	8/-	W142	11/-
2D18C	7/6	6BA6	7/6	6L1G	10/-	9I2	3/-	20P3	12/6	1203	7/6	D194	8/6	EP41	9/6	KL35	8/6	PCN25	6/6	U76	8/-	X61	10/6
2X2	4/6	6E26	7/6	6L6G	9/-	10E2	10/-	25Y3	8/6	573	12/6	D136	9/6	EP42	12/6	K72	5/-	PCN40D	U78	7/-	X65	10/6	
3A4	7/-	6B36G	12/6	6I7	7/6	10D1	7/6	25Z4	9/-	7I93	2/6	D1816	10/6	EP50(A)	7/-	K73C	10/6	25/-	U192	8/6	X66	10/6	
3A5	7/-	6B3E	8/-	6N7	7/-	10F9	9/6	25Z5	8/6	7475	7/6	EL148	2/-	EP50(B)	5/-	K763	7/6	PEN46	6/6	U150	8/6	X142	10/6
3B7	8/6	6B3W	7/6	6Q7G	8/6	10L13	9/-	27	7/6	9002	5/6	EA50	2/-	EP54	5/-	K771	8/6	PL81	10/6	U152	9/6	X150	10/6
3D6	2/6	6B3W	7/6	6Q7GT	9/6	10P13	11/-	28I7	7/-	9003	5/6	EA76	9/6	EP58	9/6	KTW61	7/6	P82	9/-	U153	10/-	XPM10	6/6
3Q4	9/-	6B3X	9/6	6RTG	9/6	11D3	15/-	30	7/6	9006	6/-	EA80	8/6	EP65	8/6	KTW92	7/6	P833	11/6	U154	7/6	XFY1	6/6
3Q5	9/6	6B3Y	10/-	6S47	8/-	1246	6/6	30C1	10/-	AC8PEN	6/6	EA42	11/-	EP68	11/6	KTW63	7/6	PM2B	12/6	U251	12/6	XH(1.5)	4/-
3A4	7/6	6C4	7/-	6S67	6/6	12ANGT15	30L1	10/-	AC/HL	7/6	EB34	2/-	EP65	10/-	KT24	6/6	PM12	4/-	U319	7/6	XH(1.5)	4/-	
3V4	8/6	6C6	8/6	6S87	8/-	12AR7	12/6	31	7/6	DDD	15/-	EB41	8/-	EP91	9/-	KT263	6/6	PM12M	8/6	U329	12/6		4/-
3U4	8/-	6C8	8/-	6S87	8/-	12AH8	12/6	35S1	12/6	AC/PA	4/-	EB91	6/6	EP92	8/6	L63	8/6	P889	9/-	U404	8/6	Y63	7/6
5V4	10/-	6C10	10/6	6S87	5/6	12AT7	8/6	35L9	9/-	ATA	7/6	EB93	12/6	EP92	8/6	LN132	10/6	P874	9/-	U404	11/-	Y65	10/6
5X4	10/-	6C16	7/6	6S17GT	8/-	12AAT	8/-	35Z4	8/-	ATP4	3/6	EB93	7/6	EL41	10/6	LN309	12/6	P882	7/6	U404	8/6	Z63	6/-
5Y3	7/6	6D6	6/6	6S87GT	7/6	12AX7	10/-	35Z5	8/6	AZ31	12/6	EB94	10/-	EL42	13/-	LZ319	10/6	PY83	10/6	U404	10/-	Z77	9/-
5Y4	10/-	6P1	12/6	6S87	7/6	12BA6	9/-	41MP	12/6	B399	9/6	EBF80	10/-	EL41	15/-	MH4	5/6	Q221	7/6	U41	9/-	Z142	13/6
5Z3	8/6	6P6G	7/6	6U44T	14/6	12BE6	10/-	41MTL	7/6	B329	10/6	10/-	EL84	10/6	MH4	7/6	Q222	12/6	UP42	13/6	U150	12/6	
5Z4	8/6	6P7	10/6	6U5G	7/6	12C1	30/-	42Z3	12/6	BL63	7/6	EC32	5/6	EL91	5/-	M84B	15/-	Q225	6/6	U141	10/-	Z152	8/6
6A7	10/-	6P8	10/6	6U7	8/6	12D4M	3/-	50C5	10/-	CK23	6/6	EC34	6/-	EM54	10/6	MU14	8/6	Q8130/15	U146	12/6	Z16	10/6	
6A17	8/-	6P12	9/-	6V6G	7/-	12E5GT	4/-	50L6	8/6	CK525	6/6	EC31	15/-	EV51	10/6	N77	5/-	10/6	U15	8/6	Z29	12/6	
6A8	10/-	6P13	12/6	6V6GT	7/-	12J7	9/6	57	8/6	CV85	12/6	EC32	10/6	EY46	12/-	N142	10/6	R12	10/6	U19	8/-	ZD152	10/-

Terms of business:—Cash with order or C.O.D. only. Orders value £3 or more sent post packing free. Orders below £3 please add 6d. per valve. C.O.D. orders 7d. minimum fee, including post and packing. 3/- We are open for personal shoppers, Mon.-Fri. 8.30-5.30. Sat. 8.20-1 p.m.

CRYSTAL DIODES (1st Grade OA71, GEX34, CG6E, M1, CG10E, all 7/- each.

All valves new, boxed, tax paid, and subject to makers' guarantee. First grade goods only, no seconds or rejects. All orders received by first post despatched same day. S.A.E. for free complete list, with terms of guarantee and conditions of sale.

# CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## COAXIAL TIP

**S**IR,—I have recently noted the coaxial tips which you have published, and I think it is about time that many of these types of hint were given. For instance, there are two or three coaxial plugs on the market, and although I have managed to fit these to my aerials and converters from time to time, the work was most involved. When the plug is taken to pieces, in one case, there are five separate pieces, and how do you start? The first time I tried I found that the single lead inside the coaxial has twisted off in screwing on the plug and there was no connection to the inner part of the plug. Another time the projecting "claws" of the plug cut clean through the insulated covering of the aerial into the inner flex lead. Surely, after all this time, manufacturers could agree on a standard type of plug or socket and the fitment could be standardised. Also, what about a plug or socket which did not call for soldering? Quite a number of listeners no doubt break off the aerial lead in moving a set about in the house, and that means they have to make a very poor repair job if they can't solder, or call in the service engineer and he surely has enough to do without going out to solder an aerial plug on.—G. YOUNG (Bexley Heath).

## USING A 'SCOPE

**S**IR,—I had just written to you to ask whether there was any book on the subject of using a 'scope. I had been interested in the tester you described a few months ago, and wanted to build this up but postponed the event as I did not know how to make full use of it. I find this often happens with us amateurs. We see a nice bit of test gear in your pages, or in your companion paper, and on working out the cost this proves very cheap and it would no doubt be a useful acquisition, but we don't know how to use it. The 'scope seems to be a very good case in point, and as there is such a lot you can do with it, I was wondering when you would tell us. When the present series is finished, could you let us have some more on connecting it to a typical television set and working out what is wrong by the pictures which you get on the 'scope? I recently saw an outside unit of the I.T.A. at work near our home and I got near the camera man and there was a monitor set working with a picture on it, and in the corner a small 2in. tube face with the oscillogram of the signal on it (green) and it was fascinating to watch how the patterns changed, and I would like to do this. I spoke to one of the men and he said the black level was jumping or something and I should like to know how to see this, for instance, as I have read that this is a most critical adjustment in a set to get the proper graduations of tone. What do other readers do in cases such as mine?—G. F. RAISTRICK (Manchester).

## AERIAL DESIGN

**S**IR,—Whilst I am deeply interested in Mr. Burton's letter in your October issue, I feel that there is another point which should receive the attention of the experts. I refer to the general question of outdoor aerials. At present, if one is at all "radio-minded" one will have on one's roof the most shocking array of old metal that one could think of. There will be a Band I, a Band III, an F.M. and a normal broadcast aerial. All of these take on various different forms, and although one might say there is little weight there as the majority of the material is aluminium tubing, there is the question of the wind resistance and also the unsightliness. Why can't all of these be incorporated in one *simple* design? I

am by no means a technician, but I have seen a combined Band I and Band III aerial in which the Band I element was folded and it was therefore very little larger than the Band III arrangement. At the other extreme, I saw near Southend a Band III system with 8 elements, on top of which was a Band I

with three directors—and the whole thing was leaning heavily, no doubt due to the wind having loosened the moorings. One day it's going to fall on somebody, and surely it is unnecessary. I wonder if technicians do not attempt to research into unexplored avenues, or do they all plough along known lines, with the result that very little new materialises.—F. ARNOLD (S.W.4).

## PERSONAL TELEVISOR

**S**IR,—Re the "Personal Televisor" as published in your November, 1952, issue. The series-connected R.F. amplifiers were recommended to be valves type EF95 (Mullard). The "Mullard" published data for this valve type, however, gives a maximum heater-cathode potential of 90 v. which is somewhat exceeded by the valve occupying position  $V_2$ . It may be of interest to others to know that the EF95s tried in this circuit have all withstood the extra h-k voltage, and it would appear safe to run these continuously under these conditions.—R. T. IRISH (Carshalton).

## AMATEUR TELEVISION CONVENTION

**S**IR,—I wonder if you would draw readers' attention to the fact that this year's Convention of the British Amateur Television Club will be held at the Bonnington Hotel, Southampton Row, W.C.1, from 10 a.m. till 7 p.m. on Saturday, October 27th.

In addition to demonstrations of the equipment owned by some of the members, there will be a film show and other interesting displays.

The prices of admission (which do not include the price of lunch) are as follows: Members, 3s. 6d.; Non-members, 5s.

Tickets will be on sale at the door, or may be obtained in advance from the writer.—D. S. RUD (4, Bishop Road, Chelmsford).

## SPECIAL NOTE

Will readers please note that we are unable to supply Service Sheets or Circuits of ex-government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

**STRANGE SIGNAL PICK-UP**

**SIR.**—Seeing the letter from Mr. Maguire, I should like to report that I also have had some peculiar signals from time to time on my television receiver. I have heard faint snatches of conversation behind the broadcast, but never loud enough to be able to distinguish what was being said. I have often switched on during periods of no transmission, but the set is then perfectly quiet. The background is not radio or television signals, I am sure, as the conversation always appears to be between two people, and I never hear music or singing. I might add that I have no telephone, and there is no phone near my house. Is it possible to hear neighbours through coupling between aërials, I wonder?—J. K. SIMS (Barnet).

**BBC VERSUS I.T.A.**

**SIR.**—It would be interesting if some really independent body could analyse the number of viewers on both existing channels. I notice recently that after a statement by the I.T.A. chief the BBC came out with a disclaimer that the figures were inaccurate. It appears, however, that the body which at present gives the analysis for I.T.A. has made its check on people who have a set which receives both systems, whilst the BBC figures are based on the number of viewers throughout the country. Of course, thousands cannot pick up an alternative, as there is no station in their locality, so the number of viewers of the BBC there must be in the majority. I have made a rough tally amongst my work and domestic circle, and it would appear that the majority view for the greater part of the time to the I.T.A. The news-reels on the BBC still have a great following, but many people prefer a longer play than the I.T.A. generally gives. There are arguments for both sides, but it would be interesting if a really true comparison of viewing figures could be made.—G. F. DE LISLE (W.4).

**INCREASING EHT**

**SIR.**—I notice in the October issue Mr. Engelen raises the question of increasing the EHT to obtain a better picture. I had the same problem,

feeling that my picture was too dark and finding the EHT was only about 9 kV whilst the tube was rated at 11 kV. I tried increasing the EHT by using a Cockcroft circuit and although I got 2 or 3 kV more the picture was worse. I found that not only was the scanning inadequate, but the modulation produced by the existing video stage (peak to peak swing) was not adequate to give good modulation at the higher EHT. I then *reduced* the 9 kV to just over 7 kV and found that I had a much better, more contrasty picture. True it was overall dimmer and the room lights needed screening, but when the lighting arrangements are suitable the picture is very much better than with the original 9 kV and there is better contrast. I don't know whether it is imagination, but it seems that the regulation and steadiness of the picture are also greatly improved.—J. HART (Reading).

**CONVERTER PROBLEM**

**SIR.**—Now that the alternative programme has been available for some time I feel it is time that a really good alternative station selector was available. I have tried out several commercial sets (built for the two stations) and in my own case have tried out several converters with my home-made set. In all cases it is not possible to *switch* from one station to another. A fine tuner, trimmer or similar gadget has to be operated each time one changes, and although in one of my home-built converters I got very nearly the desired results the drift on Band III is such that the trimmer has to be actuated now and again. I wonder if other readers have experienced this trouble and whether anyone has found a circuit which does away with the necessity for trimming on one or other of the bands? In one commercial set I found that the setting held good, but the advantage was offset by the fact that the control was ganged with the on/off switch, and to retain the advantages of switching direct from one to another without retrimming one had to use the mains power plug switch to switch the set on and off and thus avoid upsetting the control setting.—G. TURNBULL (Finchley).

**THE GRANADA TV CENTRE**

(Continued from page 173)

ideas of framing different styles of commercials to appeal to the differing tastes of Lancashire and Yorkshire.

**Overall Control**

The overall control of the Granada TV Network has the very personal attention of Sidney L. Bernstein, the managing director, who is also the head of the progressive Granada cinema circuit. The general manager of the Network Company is Victor Peers, for many years a film production executive. These two very live showmen head a fine team which is capturing a high percentage of TV audiences to the Granada fold. And to remind their team that they are all still in show business, each office has a small picture on the wall—not of the chief—but of P. T. Barnum, the greatest showman of all time.

As I left the Granada premises, I wondered just what Barnum would have thought about this television business—"travelling eyes," telecines, parlour games, brass-buttons and commercials. But that would make quite a Gulliver's Travels type of TV play in itself.

**SOMETHING DIFFERENT IN CHRISTMAS GIFTS**

*Send your friends who are TV enthusiasts an original and really acceptable Christmas present this year—send a year's subscription for PRACTICAL TELEVISION. For twelve whole months your gift will bring them repeated pleasure, and each new issue will be a renewed reminder of your good wishes.*

*And no gift could be easier to arrange! Just send your friends' names and addresses with your own and remittance to cover (an annual subscription for PRACTICAL TELEVISION—12 issues, including postage—costs 17s. 6d.) to Subscription Manager, (G.I.), George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. We will despatch first copies to arrive in good time for Christmas, together with an attractive Christmas Card, made out in your name, to announce your gift.*

**RF26 F.M. CONVERTER UNIT 88 100 Mcs**

This well-known RF26 Unit is now adaptable for F.M. reception using 2 I.F. stages and separate local oscillator and tuned by a Muirhead graduated vernier drive. Can be converted at low cost of 92 6. Send 16 for 8-page descriptive booklet containing full wiring instructions, circuits and layout diagrams.

**5-V ALAE 3-WAVEBAND SUPERHET**

16-50 Metres, Short-Wave, 187-550 Metres, Medium-Wave, 900-2,000 Metres, Long-Wave.  
Flywheel Tuning.  
Negative Feed Back.  
Valves : 6BE6, 6A7G, 6BW6, 6X4.  
Wave Change and Gram.  
Chassis 11 x 7, x 8!  
£9 5-  
Manufactured by well-known Manufacturers.  
Absolute Unrepeatable Bargain.

**U.S.A. INDICATOR UNIT RC929A**

Complete with 3BP1 C.R. tube and screen. 7 valves - 2-6SN7GT, 2-6H6GT, 6C6, 2S2, 6X5G, volume controls, condensers, etc. Ideal for portable scope. In black crank case size 15 1/2 in. 9 in. 9 in. BRAND NEW. 65 - carr. FREE.

**62A INDICATOR UNIT**

Containing VC975 with Mu-Metal Screen, 21 Valves - 12-EF50, 4-SP61, 3-EA50, 2-EB34. Plus Pots, Switches, H.V. Cond., Resistors, Muirhead S.M. Dial, Double Deck Chassis and Crystal. BRAND NEW ORIGINAL CASES. 67 6. Carr. free.

**PYE 45 Mcs STRIP TYPE 3583 UNITS**

Size 15in. 8in. 2in. Complete with 45 Mcs. Pye Strip, 12 valves, 10 EF50, EB34 and EA50, volume controls, and hosts of Resistors and Condensers. New condition. Modification data supplied. Price 69.6. Carriage paid.

**INDICATOR UNIT TYPE 182A**

Unit contains VC977 Cathode Ray 6in. tube, complete with Mu-Metal screen, 3-EF50, 4-SP61 and 1-5C4G valves, 9 wire-wound volume controls and quantity of resistors and condensers. Offered BRAND NEW (less relay) at 67 6. Plus 7 6 carr. Radio - Constructor's scope circuit included.

**WE HAVE OVER 50,000 BRITISH AND AMERICAN VALVES AVAILABLE AT VERY LOW PRICES - SEND FOR LISTS**

**TRANSISTORS**

**JUNCTION TYPE (Red-Spot) OFFERED AT LESS THAN HALF-PRICE**

Designed for A.F. application up to 800 Kcs and are suitable for use in amplifiers, Signal Tracers, Local Station Receivers, Radio Control, Oscillators, Transistor Voltmeters, Baby Alarms, Microphone Pre-Amplifiers, etc.

**10/- EACH**

(Tested and complete with Data & Circuits)

N.B. These Transistors may be used in place of Mullard OC71 or similar Transistors.

**R.F. TRANSISTORS (BLUE SPOT) 1.6 Mcs 15 - each**

"TELETRON" PORTABLE TRANSISTOR SUPERHET  
We offer all the Components, including 4 Transistors, I.F.T.'s, Trans., 2 Gang miniature Condenser, Ferrite Rod, 3in. P.M. Speaker, V.C and resistors and condensers to build this receiver for 66 10-  
Or as above with Push-Pull Output, 6 Transistors and 6 4 elliptical Speaker 49 --  
Or with matched pair Mullard DC72's and latest type high resistance P.P. Elliptical speaker, output 200 milliwatts 110 10-  
Call and hear demonstration models working.

**TRANSISTOR SIGNAL TRACER**

This circuit is designed for Audio, R.F. and I.F. Frequency and is ideal for the Serviceman for checking all types of sets including T.V. Powered by 6-volt dry battery. Miniature in construction. Complete Kit with 2 Transistors, Components and Phones with Circuit. 42 6.

**TRANSISTOR-PUSH-PULL AUDIO AMPLIFIER (100 MILLIWATTS OUTPUT)**

Build this Push-Pull Amplifier which is ideal for Crystal or Magnetic Pick-up Amplification, Baby Alarm, Microphone Amplifier, etc. Powered by 6-volt Dry Battery lasting for months. Complete Kit of Parts including 4 Transistors and all Components with Circuit (less speaker), 44 10-

**TRANSISTOR SQUARE WAVE GENERATOR**

This arrangement comprises an emitter-coupled multi-vibrator, and provides a square waveform with excellent transient characteristics. The output provides two basic tones and a large number of harmonics - spreading through the A.F. spectrum. Ideal for signal tracing. Complete Kit with 2 Transistors and Components and Circuit. 25 -

**QUARTZ CRYSTALS**

**TYPE FT243** fundamental frequencies, 2 pin (in. spacing).  
**120 TYPES.** 5675 Kcs., to 8950 (in steps of 25 Kcs.), 33-933 Kcs.).  
**ALL BRAND NEW 10 - each.**  
**TYPE FT241A** 54th harmonic Crystals, 2 pin (in. spacing).  
**80 TYPES** 20 Mcs. - 27.9 Mcs.  
(in steps of 100 Kcs.)  
**ALL BRAND NEW 7 6 each.**  
FT241A 200 Kcs. 10 - each.  
Crystal Holders for both Types 1 3 each.

**SPECIAL REDUCTION FOR SETS OF VALVES**

1A7GT, 1N5GT, 1H5GT, 1A5GT (or 1Q5GT or 3Q5GT)	37 6 Set
10 EF50 (Ex-Brand New Units) 5 - each	45 - "
10 EF50 (Red Sylvania, ex-new units) 6 - each	55 - "
6K8G, 6K7G, 6Q7G, 5Z4G, 6V8G	35 - "
1R5, 1S5, 1T4, 1S4 (or 3R4 or 3V4)	27 6 - "
TP25, VP23, HL23 DD, PEN25 (or QP25)	25 - "
DK96, DF96, DAF96, DL96	32 6 - "
6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 (or 25Z6G)	37 6 - "
12K8GT, 12K7GT, 12Q7GT, 35Z4GT, 35L6GT (or 50L6GT)	37 6 - "
12S4GT, 12S6GT, 12S8GT, 35Z4GT, 35L6GT or 50L6GT	35 - "

**TRANSMITTER RECEIVER SCR 522**

Comprising the well-known BC625 and BC624A. Units complete with 17 valves types : 2-832, 3-12A6, 3-12S6T, 3-9003, 9002, 6C6G, 12J5GT, 12AH7GT, 12C6, 68S1. The complete unit is in very good condition having very useful parts including Relays, Transformers, Condensers, etc. With valves, 67 10 - carr. paid. Less valves, 63 10 - carr. paid.

Send Stamps for new 1956 28-page catalogue.

**HENRY'S**  
(RADIO LTD.)

**CRYSTAL MICROPHONE INSERTS**



Ideal for Tape Recording, Gramophone Amplifier, etc. Very sensitive. Guaranteed and Tested. 5/- (ex-nits), or 8 6 Brand new and boxed.

**1355 RECEIVER**

Complete with 11 valves - 8-SP61, 5-1G, VC123, VP2. As specified for inexpensive T.V. In absolute new condition. 27 6. Carr. 5-  
R.F. 2 - 10 - R.P. 25 12 6.  
R.P. 30 25 - Brand new with valves, carr. 2 8.

**CATHODE RAY TUBES**

VC138A WITH SCREEN	£1 15-
VC139A	25/-
C.R. Tube Brand new in original cartons (each)	£1-15-
VC197, Guaranteed full TV picture (each)	£2 --
VC197C, Guaranteed full TV picture	£2 --
MULTI-TAL SCREENS for VC905 or 517, P.P. 16	£1 15-
6in. ENLARGER for VC905 or 517, P.P. 16	10-
VC187, slight-cut-off Carr. 2	17 6
3BP1, Brand new	£1 10-

**GARRARD 3-SPEED MINOR AUTO-CHANGING Model RC110**

As 200 250. List price £14 15. Brand New. **£7 19 6** P. & P. 3 6

**R.S.I. 4-SPEED RECORD CHANGERS**

Very latest type 4-speed with HGP37 crystal turn-over pick-up. Plays mixed records. £9 15 - P.P. 3 6.

**MINIATURE TRANSMITTING STRIP TYPE "81"**

Size 7 1/2 in. 6 in. 3 in. Complete with Valves Type CV115, CV709, 2-6A6B, 2-719 and QUARTZ Crystal, 4,800 Kcs. Fully wired with circuit. £4 10 - complete.

**MINIATURE I.F. STRIP TYPE "973" 9-72 MEG.**


Brand new miniature I.F. Strip size 10 1/2 in. 2 1/2 in. 3 in. high. Valve line-up 2-EP92, 3-EF91 and EB91. With circuit. With valves, 45/- (less valves 8 - Post free). This I.F. Strip is part of above equipment.

*For a regular  
smooth response curve*

**You need a PHILIPS**

**dual-cone  
loudspeaker**


Made in Holland

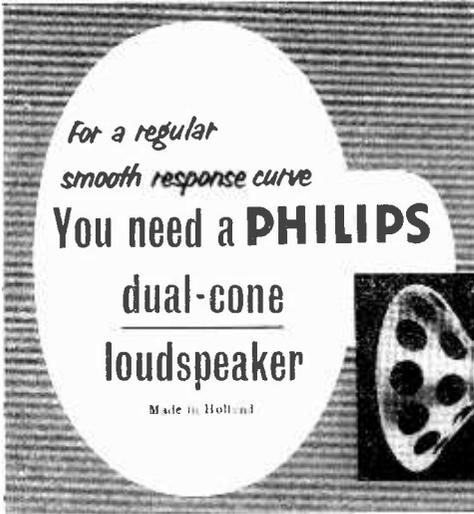

A special dual-cone design distinguishes Philips high fidelity speakers, resulting in energy transmissions almost independent of frequency. This ensures that, in an ordinary room, sound pressure within an angle of 90 degrees varies by not more than six decibels; while the excellent spatial distribution of acoustic energy — even at the highest frequencies — is obtained by Philips choice of coupling factor between high-range and low-range cones.



The small cone acts as a high note radiator for frequencies above 10,000 cycles and as a diffuser for frequencies below 10,000 cycles from the large cone. The large cone itself acts as a low note radiator below 10,000 cycles, and as a reflector for the high notes above this frequency. The distribution of sound over the entire frequency range is thus much wider than on a normal loudspeaker. These loudspeakers have a very smooth response curve combined with a low resonance frequency.

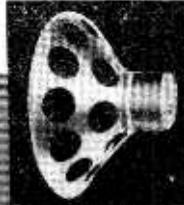

The Philips dual-cone loudspeaker comes in two sizes: 8" and 12", price 6½ gns. (tax paid) and 10 gns. respectively. There is also a single-cone loudspeaker, available in the same two sizes: price £6.2s. 6d. (tax paid) and £10.0s. 0d. respectively.

N.B. Any of these speakers may be used on their own or with another suitable loudspeaker using a crossover unit.


For full details write to:



**PHILIPS ELECTRICAL LTD**  
Musical Equipment Dept. • Century House  
Shaftesbury Avenue • London • WC2  
(PR436)

**BAND III CONVERTERS**

**800 ONLY AT 49/-**  
(C.O.D. 1/-)

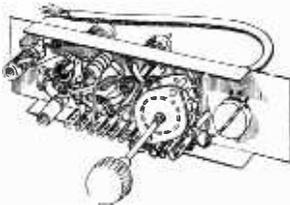

For internal conversions — fully wired chassis, approx. 9in. x 2½in. x 2in. deep. Complete with 2 valves EF91, contrast control, aerial and band switching. Co-

axial plug and one knob supplied. Suits 6.3 v .3 A. and 12.6 v .15 A. heater chains. ALL NEW COMPONENTS and VALVES. For complete converters see advert., page 200.

50 mixed new resistors 9/- (post 1/-). 40 of ½ and ¼ W. and 10 of 1 and 2 W., all standard values Dubilier, Erie, Morgan.

40 mixed new silv. mica and ceramic condensers 9/- (post 1/-), standard values ½ pf. to 6,000 pf. Lemco, T.C.C., etc.

Pre-amplifiers less power pack, with EF80 valve 20/-. With power pack in metal case 40/- (post 2/-). When used with converter, also amplifies Band 3 signal.

**GLADSTONE RADIO**  
P.O. BOX 8, CAMBERLEY, SURREY

**SOLDERING ?**

**HENLEY  
SOLON**  
TRADE MARK  
**ELECTRIC  
SOLDERING IRONS**

*for 25 years  
the best*



A model for every purpose

Leaflets on request from

25 watt Instrument Model

**W. T. HENLEY'S TELEGRAPH  
WORKS CO. LTD.**

51-53 Hatton Garden, London, E.C.1 Tel CHAncery 6822

# Bandwidth

SOME NOTES INTENDED TO HELP THE BEGINNER TO APPRECIATE THE SIGNIFICANCE OF THIS TERM

By S. C. Murison, A.M.Brit.I.R.E.

**M**OST beginners can see the significance of a waveform and can understand its dimensions. The illustration shows a pulse and most newcomers could say what its amplitude, duration, time of rise and time of fall are just by looking at it. When it comes to considering bandwidth, what is involved is usually less clear in the beginner's mind.

The bandwidth of a system (say, the video amplifier in a television set) is usually taken to mean the *difference* between the two frequencies at which it starts and finishes to perform its function (amplifying, in our example). For a typical video amplifier in a 405-line television set, the bandwidth (as defined above) would be about 2.5 Mc/s. Such an amplifier

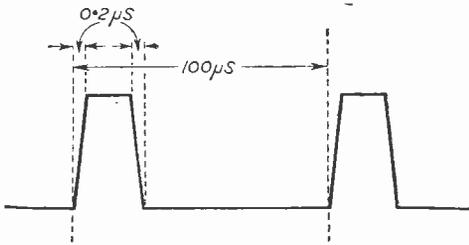


Fig. 1.—An example waveform.

often provides amplifications from D.C. up to about 2.5 Mc/s, so the *difference* between the two frequencies is the same as the upper frequency, in this example. For the sound channel of a typical amplitude modulation television set, the bandwidth provided is often about 300 kc/s or 400 kc/s. In this example, the lower frequency at which the channel starts to respond might be 41.2 Mc/s and the upper frequency 41.7 Mc/s. (The example chosen here is for the Channel 1 frequencies.) The bandwidth provided by such a sound channel is wider than is needed. An amplitude modulated transmitter radiates a band of frequencies on each side of the carrier frequency. The band of frequencies is usually thought of as being in two *sidebands*; the one which is on the low frequency of the carrier is called the *lower sideband*, the one on the high frequency being the *upper sideband*. How this effect arises need not concern us here. What is of interest to us here is how wide this band of frequencies is. The lower sideband extends below the carrier frequency by the frequency of the modulating wave; and the upper extends above the carrier by the same

amount. Thus, if a sound of frequency 15 kc/s is being transmitted, the sidebands occupy a band of frequencies 30 kc/s wide centred on the carrier frequency. The highest frequency which can be heard by young people is about 18 kc/s, with older people tending to be unable to hear such high frequencies. Consequently, a bandwidth of 36 kc/s would be adequate for even the most exacting need. The extra bandwidth is provided in most sound channels because to make it any less would introduce extra components and would also mean that the tuning of the channel would have to be more stable.

So far we have only considered bandwidth in terms of frequency; it is often more helpful in seeing what is involved, to think of it as a proportion of the centre frequency. Suppose that we required to transmit the pulse shown on the left. If the time between pulses is 100 micro-seconds, the repetition rate is 10 kc/s. Then the lowest frequency which would be used for modulation would be 10 kc/s, because nothing in the waveform occurs at a slower rate. What is the highest modulating frequency? This question is the same as asking what part of the waveform changes in the least time and how fast is this change. Obviously, the leading and trailing edges are the fastest parts of the waveform: what we need to know is what sort of frequency they represent. Both the leading and trailing edges take the same time to happen—0.2 micro-seconds each. We can think of both the leading and trailing edges as being a part taken from a sine wave. A slope which takes 0.2 micro-seconds to happen is rather like one-quarter of a cycle of a sine wave having a frequency

Source of Modulation	Modulation Frequencies	Carrier Frequency	Approximate Fractional Bandwidth
Teleprinter	5—100 c/s	2,000 c/s	0.098
Speech	300—3,000 c/s	1,000 kc/s	0.0054
Speech	300—3,000 c/s	50 Mc/s	0.0011
Speech	300—3,000 c/s	200 Mc/s	0.0003
Music	20 c/s—18 kc/s	1,000 kc/s	0.036
Music	20 c/s—18 kc/s	50 Mc/s	0.0072
Music	20 c/s—18 kc/s	200 Mc/s	0.0018
Television			
Camera	25 c/s—2.75 Mc/s	10 Mc/s*	0.55
Television			
Camera	25 c/s—2.75 Mc/s	35 Mc/s*	0.157
Television			
Camera	25 c/s—2.75 Mc/s	50 Mc/s	0.11
Television			
Camera	25 c/s—2.75 Mc/s	200 Mc/s	0.027

\* Representative of intermediate frequencies.

of 1.2 Mc/s. A sine wave having a frequency of 1.2 Mc/s takes 0.8 micro-seconds for a whole cycle ; so one-quarter of a cycle takes 0.2 micro-seconds. So we now have a reasonable answer to the question of what is the highest frequency in the waveform on Fig. 1. We now know that we must be able to modulate with frequencies between 10 kc/s and 1.2 Mc/s to be able to transmit such a waveform.

If we modulate a transmitter of frequency 20 Mc/s with our pulse, the sidebands will extend from 18.8 Mc/s to 21.2 Mc/s and the bandwidth is 2.4 Mc/s. With a 60 Mc/s transmitter, the bandwidth remains 2.4 Mc/s, but as a proportion it is less—three times less in simple proportion. Sometimes simple proportion is not used to express the bandwidth as a fraction of the carrier frequency. The geometric mean of the upper and lower frequencies can be taken and used as the denominator of a fraction whose numerator is the bandwidth. The term "geometric mean" need not cause any concern ; all that is involved is multiplying the two frequencies together and taking the square root of the answer.


Applying this to the two examples above, we get : For the 20 Mc/s carrier, a geometric mean of  $\sqrt{18.8 \times 21.2}$ , which is almost exactly 19.95. Using this as a denominator of a fraction, whose numerator is the bandwidth, we get  $\frac{2.4}{19.95}$  or about 0.12.

Doing the same thing for the 60 Mc/s carrier, we get a geometric mean of  $\sqrt{58.8 \times 61.2}$ , which is 59.99 Mc/s. The fractional bandwidth then becomes  $\frac{2.4}{59.99}$  or about 0.04.

All of these results are in close agreement with those obtained by using the carrier frequency rather than the geometric mean of the outer sideband frequencies, and the reader will see that an appreciation of what is involved can be had by using simple proportion. The table shows some typical fractional bandwidths occupied by the sidebands of various carrier frequencies when amplitude modulated by various sources. The fractional bandwidth shown in the table assumes that both sidebands have to be accommodated.
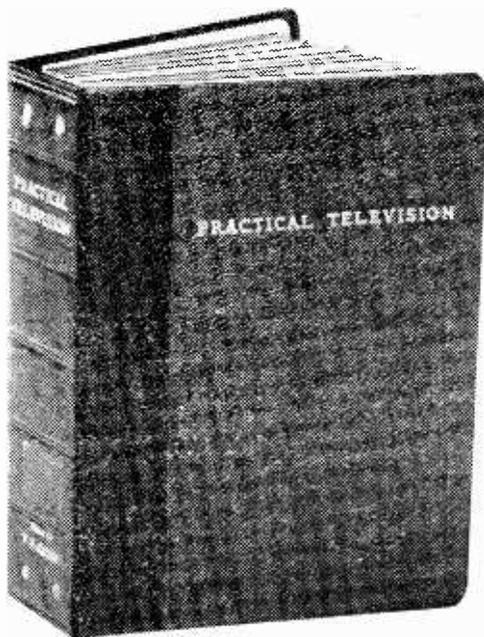
### Two Examples

It is not the purpose of this article to do more than familiarise the reader with the term bandwidth ; design techniques for obtaining bandwidth are outside the scope of the article. However, it may be of interest to conclude by considering two numerical examples of tuned circuits. The bandwidth of a tuned circuit depends on the ratio of the reactance of either the inductor or capacitor and the losses. Below about 20 Mc/s almost all the losses are due to the resistance of the inductor's wire. This ratio is called Q. The bandwidth of the circuit is arrived at by dividing the resonant frequency by the value of Q. A typical value of Q for a medium-wave coil is 100, although higher values are attainable. At 1 Mc/s a tuned circuit using such an inductor would have a bandwidth of about 10 kc/s. Typical tuning inductors for television sets have values of Q (before any damping resistors are connected) of between 100 and 200. Assuming a Q of 150 for an inductor used in a tuned circuit resonant at 45 Mc/s, the bandwidth would be 300 kc/s.



## Self-Binders FOR "PRACTICAL TELEVISION"

AS a service to our readers we have arranged for self-binders to be supplied in which they may preserve the copies of this journal. Copies can be inserted as received, and you do not, therefore, have to wait for the completion of the volume. You secure the same all-time protection as with ordinary binding. The self-binders are in black, waterproof and greaseproof cloth, attractively lettered in gold. This system avoids copies becoming damaged or mislaid. The Easibinder opens flat at any page of any separate edition and gives quick reference facilities. When the volume is complete our annual index published at 1s. 3d. should be inserted.

Binders cost 10s. post free. Orders should be sent to "Practical Television" (Binding Dept.), George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.



# BAND 3 T/V CONVERTER—185 Mc/s - 199 Mc/s

Suitable for London, Birmingham and Northern Transmissions

£2-5-0 post free.

A highly successful unit (B' World circuit), incorporating variable oscillator tuning, Midget BVA valves, etc. Chassis size 7 x 4 x 2 1/2 in. Thousands already in use. Suitable for most types of T/V sets. TRF or Superhet. Kit of parts 45/- . Blueprint 1/6. Power pack kit 30/- . Switch kit (Band 1—Band 3 Ae switching),

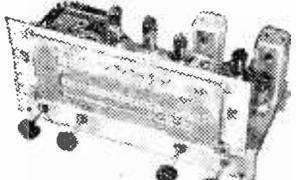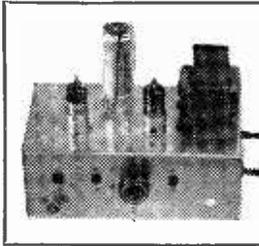6/6—all Post Free. Wiring and aligning of above 20/- extra. Full range of Band 3 aerials in stock. Adaptors for 7.6 per set. Indoor dipoles, 6/6. Outdoor with cable 13/9. Band 1—Band 3 cross-over filter unit, 7/6. Variable attenuators 6 db—36 db, 7/6. BBC Break-through Filter, suitable for BBC pattern rejection, 8/6.



## Volume Controls

Log ratios, 10,000 ohms - 2 Megohms. Long - 100 Ohms. 1 Year guarantee. Midget Edition Type. No. Sw. A.P. Sw. D.P. Sw. 3/- 4/- 4/9  
Linear Ratio, 10,000 ohms—2 Meg ohms. Less switch, 4/- each. Coax plugs, 1/2. Coax sockets 1/-. Couplers 1/-. Outlet boxes, 4/6.

## 80 ohm COAX

STANDARD 1/4 in. diam. Polythene insulated. GRADE "A" ONLY

8d. yd.

SPECIAL — Semi-air spaced polythene. 80 ohm. Coax 1/4 in. diam. Stranded core. Losses cut 50%

9d. yd.

TWIN FEEDER, 80 ohms, 8d. yd.; 500 ohms, 8d. yd.  
TWIN SCREEN FEEDER, 80 ohms, 13 1/2 yd.  
50 OHM COAX CABLE 8d. per yd. 2 1/2 in. dia.  
TRIMMERS, Ceramic, 4 pf.—70 pf., 9d. 100 pf. 150 pf., 1/3; 250 pf., 1/6; 500 pf., 1/6. PHILIPS Resitive Type—2 to 8 pf. or 3 to 50 pf., 1/3 each.  
RESISTORS—Pref. values 10 ohms to 10 megohms.

## CARBON

20% Type. 1/2 w., 3d.; 1 w., 5d.; 1 w., 6d.; 2 w., 9d.  
10% Type. 1/2 w., 9d.; 1 w., 1/2; 1 w., 1/2; 1 w., 2/-

## WIRE WOUND

25 ohms 1/3; 10w., 10,000 1/6; 15w., 2/-; 15,000 2/-; 33,000 2/6; 10w., 2/6

## WIRE-WOUND POTS

Pre-Set, Min. T.V. Type Knotted, Slotted Knobs. All values 25 ohms to 50 K., 3/- ea. 50 K., 4/- Ditto Carbon Track 50 K. to 2 Meg., 3/-

## CONDENSERS

Mica or P. Mica. All pref. values. 7.6 to 680 pf., 6d. Ceramic types 2.2 pf. to 50,000 pf. as available, 9d. each. Tubulars, 150 v. Hints and T.C.C., 0.005, 0.01, 0.05, .01 and 1/320 v., 9d., .02, .05, 1/500 v. Hints, T.C.C., 1/2, .25 Hints, 1/6. 1/2 Hints, 1/9. 1/3 250 v. T.C.C. (Simplex), 3/6. 250 v. T.C.C., 5/6. 500 to 20 KV. T.C.C., 9/6.

## SILVER MICA CONDENSERS

100 v. 3 pf. to 500 pf., 1/9. 500 pf. to 5,000 pf., 1/3. 1/2, 1/2 pf. to 500 pf., 1/9. 515 pf. to 5,000 pf., 2/6.

## STANDARD 3 WAVEBAND COIL PACK

Size 2 1/2 in. x 1 1/2 in. depth, 4 pos. switching. Long, Mid., Short, Gram. Dust-core coils prealigned for 465 Kcs I.F. Complete with trimmer, ready to use. A very sensitive and efficient coil pack.

## Manufacturer's Surplus. Barkan Offer, 27/6.

ALUMINIUM CHASSIS.—18 x 5 x 5 in. Plain, undrilled, folded 4 sides and riveted corners lattice finish holes. Strong and soundly constructed with 2 1/2 in. sides. 7 in. x 4 in., 4/6; 9 in. x 6 in., 5/9; 11 in. x 7 in., 6/9; 13 in. x 8 in., 8/6; 14 in. x 11 in., 10/6; and 18 in. x 13 in., 18/6.

## SPECIAL OFFER.—Goodmans 12 in. P.M. Speaker

Autium 50, Brand new, boxed and guaranteed. PEW ONLY, 24/10/-, Carr. 2/-

## BRIMISTORS.—CZ1 for 3A heater chains, 3/6.

CZ2 for 15 a, or 2 a, 2/6. CZ3 (Pilot Lamp), 1/6. COPPER ENAMEL WIRE.—1/2 lb. 11 to 20 swg., 1/2; 22 to 28 swg., 2/6; 30 to 40 swg., 3/6. SWITCH CLEANER Fluid.—10 oz. tin 3/6.

## ALL WAVE RADIOGRAM CHASSIS

3 WAVEBANDS, 5 VALVES LATEST MIDGET M.W. 20 in. x 10 in. BVA Brand new and gear, A.C. 200-250 v. 1 pos. W/C sw. short-nothing-longer run, P.I. socket. High Q. dist. cond. Lastest circuit including delay, AVC and neg. feedback. 0-1 P. 4 watts. Chassis size, 13 1/2 x 5 1/2 x 2 1/2 in. Dial 10 in. x 4 in. Hor. or vert. station names. Walnut or ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost. Double wound motor-trans. BARGAIN £9.150 Carr. and ins., 4/6. 8 or 10 in. speakers to match, from 2/6.

## 7 Valve De Luxe, push-pull version

7 watt output, £12.10.0. Carr. & ins., 5/- BARGAIN VALUE IN AUTO CHANGERS 2 speed auto change movers for 7 in., 10 in., & 12 in. records. Lightweight Metal P.T. with turnover. Dipoint magnetic stylus for Hi-Fi reproduction. Latest models—Modern styling. All brand new, boxed and gear. A.C. 200-250 v. only. PHENIXY, £8 10/- BSH MONARCH, 81 gns. GARRARD, H.C.H., £8 18/6 COLLARD, R/34, £10 10/- All suitable for above Radiogram chassis.



## QUALITY FLUORESCENT FITTINGS

Ideal for home or workshop. 4ft., 220-250 v., complete with tube, ballast unit, etc., ready for use. Famous manufacturer's surplus offered at approx. half price. Starter switch type, 42/- . Quick start type, 47/6. Carr. and ins., 7/6 extra. PEW ONLY NOW LEFT.

## NEW BOXED VALVES GUARANTEED ALL TYPES

115	174	6	1A P36	10	1A P38	12	1A P40	10/-	
185	184	7	1D36	10	1E120	12	1E200	10/-	
354	3V4	8	1K36	10	1E41	10/8	1M14	8/6	
524	8	6	1D36	10	1E30	10/-	1PCC84	12/6	
64T6	8	6	1E50	2	1E50	10/-	1P380	12/6	
6H16	10	6	1E31	7	6	1E31	1P382	12/6	
6H40	3	6	1E31	10	6	1E31	1P382	12/6	
6K7	6	6	1E33	8	6	1E33	1P381	12/6	
6K8	9	6	1E33	12	6	1E33	1P382	10/-	
6Q7	8	6	1E34	13	6	1E34	1P383	12/6	
6N7	9	6	1E35	13	6	1E35	1P381	11/-	
6V5	7	6	1P38	12	6	1E41	11/6	1P381	12/6
6X4	8	6	1E32	13	6	1E34	12/6	1P382	10/-
6X5	8	6	1E42	10	6	1E51	12/6	1E25	12/6

## SPECIAL PRICE PER SET

115, 174, 185 and 354 or 3V4 ... .. 27/6  
6K8, 6K7, 6Q7, 6V5, 6Z4 or 6X5 ... .. 35/-  
SPEAKER FRET.—Expanded Bronze anodized metal 8 in. x 8 in., 2/3; 12 in. x 8 in., 3/-; 15 in. x 12 in., 4/3; 12 in. x 16 in., 6/-; 24 in. x 12 in., 8/6 etc.

## ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	32	32/350 v. B.I.P.	5
25 25 v., 50 12 v.,	1 9	Can Types, Chips, 3d. ea.	6
1/2 v., 6 v., 8 v., 12 v.,	2	8 v. x 450 v. T.C.C.	4 8
100 25 v., 2 450 v.,	2	8 v. x 450 v. Hints	5
8 450 v. B.I.P.,	2 3	16 16 1/8 250 v.	5 6
5 500 v. Dab,	2 6	16—16 450 v. T.C.C.	5 6
8 500 v. Dab,	4 6	16—32 350 v. B.I.P.	5 6
8 16 450 v. T.C.C.,	5	32 350 v. Hints	4
16 450 v. B.I.P.,	3 6	32—32 450 v. T.C.C.	6 6
16 500 v. Hints,	4	60 250 v. T.C.C.	6 6
16 16 450 v. T.C.C.	5 6	60—100 450 v.	11 6
32 250 v. Hints,	4	60—250 275 v.	12 6
32 500 v. Hints,	5	100—200 275 v.	12 6
50 50 450 v. B.I.P.	6 6	6,000 mfd. 5 v.	3 9

## SENTERLOC RECTIFIERS. E.H.T. TYPE FLY-BACK VOLTAGES

K/25 2 KV., 4/3; K/30 2 KV., 5/6; K/35 2 KV., 6/8; K/50 2 KV., 7/3; K/100 2 KV., 12/8; MAINS TYPE.—RM1, 125 v., 60 mA., 4/-; RM2, 100 mA., 4/9; RM3, 120 mA., 5/9; RM4 type, 250 v., 275 mA., 16/-

## ENGRAVED CONTROL KNOBS

1 1/2 in. diam. Walnut or Ivory. Gold plated. Do Standard engravings, 1 1/2 in. dia. Plain knobs to match above, from 10d. 1 1/2 in. dia. 8d. ea. Walnut or Ivory, 12/6. 1 1/2 in. dia. 9d. ea. Pointer Knobs Black with White Line, 9d.

## WEARITE "P" TYPE COILS

All ranges, 1 to 7, 2/6 ea. Dens. Q Series Coils. Slug tuned. All ranges from 3/6. Full range popular Coil Packs

## I.F. TRANSFORMERS—465 kc/s

Brand new manufacturer's midget I.F.T. size 2 1/2 in. x 1 1/2 in. dust core tuning. Latz wound coils, High Q. Bargain offer, 7/6 pair.

## MAINS TRANSFORMERS—Made in our own

Workshops to Top Grade spec. Fully corrected and Impregnated. RADIO AND AMPLIFIER TYPE. 250 v., 50 ma. P.W. sec. 5 v. or 6 1/2 v. 1 a. rect. 6 1/2 v. 2 1/2 a. set Hints, 21/- ea. C.R.T. HTR. ISOLATION TYPE. Low leakage with or without 25% sec. boost voltage. Ratio 1:1 or 1:25, 2/6; 10/8; 4 v. 10/6; 6 1/2 v. 10/6; 12 1/2 v. 10/6. Ditto with mains primaries 200/250 v., 12/6. Specials to order.

## L.F. CHOKES—10 H., 65 ma., 5/-; 15 H., 100 ma.

10/6; 10 H., 120 ma., 10/6; 20 H., 150 ma., 15/6; 30 H., 10/6; 30 H., 200 ma., 10/6. Paper type, each quality 1/2000, 12/6. Reels only, 5 in., 3/8; 7 in., 4/3

## TWIN GAIN TUNING CONDENSERS—355 pf.,

Midget, 8/6; ditto, with dust cover and trimmers, 8/6. .0005 mfd. standard size with feet, 8/6

## TYGON FRET (3 mm) pattern.—12 in. x 12 in., 2/-.

12 in. x 18 in., 3/6; 12 in. x 24 in., 4/3 etc. etc.

## F.M. TUNER UNIT .87 mc/s—105 mc/s by

Jason. As tested and approved by Radio Constructor. Complete kit of parts to build this modern highly successful unit, drilled chassis and J. H. dial, coils and caps. 4 BVA miniature valves and all components, etc., for only £6.10.0 post free. SUPERIOR VARI GLASS DIAL. Calibrated in Mc/s and color lit by 2 pilot lamps, 12/6 extra. Illustrated handbook with full details, 2/- post free.



## TRS RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Buses 130A, 133, 159, 166 & 190.

Listed above are only a few items from our very large stock.

Send 3d. stamp today for Complete Barkan List.

Hours: 9 a.m.—6 p.m., 1 p.m. Wed.

OPEN ALL DAY SAT.

Please write to C.O.D. kindly make cheque, P.O.S. etc., payable to T.R.S. Post Packings up to 5/7.50, 10/1, 15/1, 20/1, 2610/1, 2

# RADIO SUPPLY CO. (LEEDS) LTD.

Dept. N,  
32, THE CALLS, LEEDS 2.

Post Terms C.W.O. or C.O.D. under £1. Postage 1/9 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d.; Trade list 5/1.

## R.S.C. TRANSFORMERS

Fully Guaranteed.

Interleaved and Impregnated.

Primaries 200-230-250 v. 50 c/s screened

**TOP SHROUDED DECO THROGH**

260-0-260 v 70 ma. 6.3 v 2 a. 5 v 2 a ... 16/9

350-0-350 v 80 ma. 6.3 v 2 a. 5 v 2 a ... 18/9

200-0-250 v 100 ma. 6.3 v 4 a. 5 v 3 a ... 23/9

350-0-350 v 100 ma. 6.3 v 4 a. 5 v 3 a ... 23/9

350-0-350 v 150 ma. 6.3 v 4 a. 5 v 3 a ... 29/9

**FULLY SHROUDED UPRIGHT**

250-0-250 v 60 ma. 6.3 v 2 a. 5 v 2 a

Midset type. 21-3-3in. ... 17/6

250-0-250 v 100 ma. 6.3 v 4 a. 5 v 3 a ... 26/9

250-0-250 v 100 ma. 6.3 v 6 a. 5 v 3 a ... 31/-

for R1335 Conversion ... 23/9

350-0-350 v 100 ma. 6.3 v 4 a. 5 v 3 a ... 23/9

350-0-350 v 150 ma. 6.3 v 4 a. 0.4-5 v 3 a 31/6

425-0-425 v 200 ma. 6.3 v 4 a. C.T. 6.3 v 4a. C.T. 5 v 3 a ... 49/9

**FILAMENT TRANSFORMERS**

All with 200-250 v 50 c/s Primaries: 6.3 v 1.5 a 5/9; 6.3 v 2 a. 7/6; 0-4-6.3 v 2 a. 7/9; 12 v 1 a. 7/11; 6.3 v 3 a. 8/11; 6.3 v 6 a. 17/9.

**CHARGER TRANSFORMERS**

200-250 v 0-9-15 v 11a. 11/9; 0-9-15 v 3a. 16/9; 0-9-15 v 5 a. 19/9; 0-9-15 v 6 a. 22/9.

**OUTPUT TRANSFORMERS**

Standard Pentode 5,000 to 3 ohms ... 4/9

Small Pentode 5,000 to 3 ohms ... 3/9

**E.H.T. TRANSFORMERS** 200-230-250 v. 2,500 v 5 ma. 2-0-2 v 1.1a. 2-0-2 v 1.1 a for VC897, VC857 ... 38/6

**SMOOTHING CHOKES**

250 ma 5 h 50 ohms ... 11/9

100 ma 10 h 250 ohms ... 8/9

80 ma 10 h 350 ohms ... 5/6

60 ma 10 h 400 ohms ... 4/11

**SELENIUM METAL RECTIFIERS**

G.E.C. 300 v 250 ma. 12/9; 120 v 40 ma. 3/9; 6/12 v 1 a F.W.. 5/9; 240 v 50 ma. 5/9. 6/12 v 2 a F.W.. 8/9; 6/12 v 4 a. 16/9; 250 v 80 ma. 7/9; 6/12 v 6 a F.W.. 19/9; 6/12 v 10 a. 29/9.

**BATTERY SET CONVERTER KIT**

All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplies 120 v 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. of 2 v at 0.4 a to 1 a. Price including circuit 49/9. Or ready for use, 9/9 extra.

**ALL DRY RECEIVER BATTERY ELIMINATOR KIT**—All parts for the construction of a unit (metal-case 51-41-2in.) to supply Battery Portable receivers requiring 90 v and 1/5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or assembled and tested at 46/9.

**R.S.C. TAI HIGH QUALITY TAPE DECK AMPLIFIER.** For ALL Tape Decks with High Impedance. Playback and Erase Heads, such as Lenc. Truxox. Adjustment to type of deck. Ready for made by alteration of a Use ONLY resistor. For A.C. Mains 200-250 v. 50 c/s. Positive compensated identification of recording level given by Magic Eye. Recording facilities for 15, 7 1/2 or 3 1/2 in. per sec. Automatic equalisation at the turn of a knob. Linear frequency response of ± 2db. 50-11,000 c.p.s. Negative feed-back equalisation. Minimum microphony and hum. High output with completely effective erasure and distortionless reproduction. Sensitivity is 15 millivolts so that any kind of crystal microphone is suitable. Provision is made for feeding a P.A. amplifier. Unit can also be used as a gram-amplifier requiring input of 0.75 v. R.M.S. Carriage 7/6. Illustrated leaflet 6d.

**EX-GOVT. UNIT RDF1**—Brand new, cartoned. Complete with 14 valves, including 5Z4G. Also mains trans. L.F. choke, rectifier, etc., etc. Only 29/6. Carr. 7/8.

11 GNS

**SMALL POTTED MAINS TRANSF.**  
Removed from New Ex-Govt. units.  
Primary 0-200-230-250 v Secs 250-0-250 v 60 ma. 6.3 v 2 a. 5 v 2 a. Size 3 1/4 x 1 1/8 in. **11/9**

**CO-AXIAL CABLE** lin. ... 8d. yd.  
Twin-screened Feeder ... 11d. yd.

**EX-GOVT. SMOOTHING CHOKES**—  
100 ma 5 h 100 ohms Tropicalised ... 3/11  
150 ma 6-10 h 150 ohms ... 6/9  
150 ma 10 h 150 ohms ... 11/9  
250 ma 5 h 50 ohms ... 12/9

**E.H.T. SMOOTHERS**  
5 mfd 2,500 v Blocks (ex-Govt.). 2/11.

**BATTERY CHARGER KITS**—Consisting of attractive Green Crackle Case. Transformer, F.W. Rectifier, Fuse, Fuseholder, Tag strip, Grommets and Circuits. For mains input 200-230-250 v 50 c/s. 6 v 2 a. 25/9; 6 v or 12 v 2 a. 31/6; 6 v or 12 v. 4 a. 49/9. Any type assembled and tested for 6/9 extra.

**R.S.C. 6 v. or 12 v. BATTERY CHARGER**  
For normal A.C. mains input 200-230-250 v 50 c/s. Selector panel for 6 v or 12 v charging. Variable charge rate of up to 4 AMPs. Fused, and with meter. Well ventilated case with attractive hammer finish. Guaranteed for 12 months. 89/9. Carr. 3/6.



**TV. CABINETS**  
Handsome well-constructed with walnut veneer 18in. high, 20in. wide, 13in. deep. Size of aperture 17in. 13 1/2 in. Fitted Doors. For 15in. or 17in. Tube. Limited number at only **79/6** Plus 7/6 carr.

Table Model. 12in. Tube. 29/9. 5/- carr.

**BATTERY CHARGERS**—For mains 200-250 v 50 c/s. Output for charging 6 v or 12 v at 1 amp. In strong metal case. Only 25/9. Above can also be used for electric train power supply.

## WHY WASTE TIME

Give that set its best chance  
**FIT QUALITY COMPONENTS**

Catalogue 1/-.

Parts for the following:—

- Manual
- Osram "912" plus Amplifier 4/-
- Mullard 10-watt Amplifier 3/6
- The Coventry
- 2-watt Amplifier ...)
- 4-watt Amplifier ... 1/-
- 6-watt Quality Amplifier)
- The Coventry A.M. Tuner
- Unit ... 1/-
- Denco F.M. Tuner Unit ... 1/6

Complete Component Price Lists will be supplied with each Manual.

## COVENTRY RADIO

EST. 1925

189, DUNSTABLE ROAD, LUTON, BEDS.

Phone: Luton 2677

## FIRST-CLASS TELEVISION and RADIO COURSES

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

### FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M. Brit. I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams, Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc.,** together with particulars of our remarkable Guarantee of

### SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER

150,000 SUCCESSSES

**NATIONAL INSTITUTE OF ENGINEERING**  
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

## VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

- 1.4v. midset. 1R5, 1S5, 1T4, 1U5, 3S4, DAF91, DF91, DK91, DL92, DL94, any 4 for 27/6.
- 1A7GT12/6 6V6G 7/- DH77 8/6 EY51 10/6
- 1C5GT11/- 6V6GT 7/- DK32 12/6 EZ40 8/-
- 1H5GT 6X4 7/6 DK92 8/6 EZ41 8/-
- 11/6 6X5GT 6/9 DK96 8/6 EZ40 8/6
- 1N5GT 7B7 8/- DL33 11/6 FW4500
- 11/6 7C5 6/9
- 1R5 8/6 7C6 8/- DL96 8/6 GZ32 12/6
- 1S5 7/3 7H7 8/- EABC80 KT33C 10/-
- 1T4 7/3 7S7 9/- 7/9 KT63 7/6
- 1U5 7/3 7Y4 8/- EAF4210/6 MC14 8/6
- 3A5 6/6 10CL 12/6 EBF3 6/9 N76 14/6
- 3Q5GT11/6 10F1 10/- EBC3 7/6 PC84 8/6
- 3S4 7/6 10LD11 10/- EBC41 10/- PCF80 8/6
- 3V4 8/6 11/6 EBF80 9/6 PCF8211/6
- 504G 8/- 10P14 13/6 ECC4012/6 PEN36C
- 5Y3GT 7/6 12AT7 8/6 ECC81 9/- PEN45 16/-
- 5Z4G 9/- 12AT7 7/6 ECC81 9/- PEN45 16/-
- 6AR5 5/- 12J7GT ECC91 6/- PEN46 6/6
- 6AL5 6/9 9/6 ECF9012/6 PL81 11/9
- 6AM6 7/6 12K7GT ECF8213/6 PL82 9/-
- 6AQ5 7/6 8/6 ECH3510/3 PL83 11/9
- 6AT6 8/6 12K8GT ECH312 6/- PY30 10/-
- 6BA6 7/8 14/6 10/- PY81 9/-
- 6BE6 7/6 12Q7GT ECH31 8/6 PY82 7/9
- 6BW6 7/6 8/6 ECL8010/0 PZ30 18/-
- 6C9 10/- 14S7 14/6 EF37A U25 12/6
- 6F1 13/- 20L1 18/9 EF39 9/- U50 7/6
- 6F6G 6/6 20P1 18/9 EF39 9/- U78 7/6
- 6F13 13/- 25L6GT EF40 12/- UAF42
- 6F15 13/- 9/6 EF42 11/- UAF41
- 6J6 6/- 25Z4G 9/6 EF42 12/- UBC41 8/9
- 6K7C 5/- 35L6GT 9/6 EF50 7/6 UCH42
- 6K8GT 9/- 35Z4CT 9/- EF90 9/- W7 10/3
- 6K8C 7/9 50L6CT 9/6 EF85 8/6 UF41 9/-
- 6K8CT 9/6 B36 15/6 EF86 12/6 UL41 10/-
- 6L8 11/6 CL33 14/- EF91 7/6 UU7 11/6
- 6Q7GT 9/6 DAC3211/6 EF92 6/6 UY41 8/6
- 6SN7GT 0.4F6G 8/6 EL32 6/- W7 6/6
- 6V6GT 7/9 DCC90 6/6 EL41 10/6 YX79 12/6
- 6U4GT DF33 11/6 EL84 10/6 Y63 7/6
- 14/6 DF96 8/6 EM34 10/- Z77 7/6

Postage 5d. per valve extra.

## READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587



*Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 197 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.*

#### MARCONIPHONE VC69DA

When I switch on the picture does not fill the screen — there is a gap at the top and bottom of about 5in. ; after about 15 minutes it will fill the screen completely, but there are lines flashing across for most of the evening's viewing. I have looked through past editions of "Practical Television" and in the July, 1955, issue I see an article on servicing the H.M.V. 1814-16, but I cannot find my symptoms described.—J. Barlow (Bolton).

This is a fault in the LN152 frame timebase valve. This is situated approximately in the centre of the chassis, underneath the envelope of the picture tube. Preferably, it should be checked by substitution.

#### H.M.V. 1828

Suddenly, for no apparent reason, the width of the picture is reduced and is now only about 3in. wide on a 14in. screen. Altering the width control has a little effect, but not much; height of picture is O.K. and so is the sound. I have changed over the Z77 valves, but to no effect. Could you please give me some directions as to the positions of components I should test?—R. G. Lacey (Niton).

Suspect a short in the line output transformer. Check the N339 and the U329 valves. Low H.T. voltage often causes this symptom, due to a faulty metal H.T. rectifier, though the effect is gradual, as distinct from the sudden occurrence in your case.

#### EKCO T161

My Ekco television set model T161, which I purchased in 1952, has developed a fault in sound. The sound output is at the highest and control knob will not lessen its volume. The picture is quite in order.—J. T. Hope (Cheshire).

The volume control is actually a gain control fitted in the cathode circuit of the first sound (10F1) I.F. amplifier valve. This is the centre valve of the three on the right side of the chassis. The control is a 25 K $\Omega$  wire wound, which should be inspected; this would be rendered inoperative if the .003  $\mu$ F capacitor which is wired from cathode to chassis were to become short circuited.

#### BUSH TV43

I have a Bush TV43 which every time I switch on is off tune on the I.T.A. I have changed the two valves on the converter side, but this has no effect.—A. D. Banks (Birmingham).

A certain amount of tuning drift occurs on most sets on Band III. The purpose of the fine tuner is to correct this easily. If the effect is excessive in your case, though, a capacitor may be at fault in the tuner unit. You would be advised to let your dealer investigate the trouble for you and, if necessary, remove the tuner for examination at the factory.

#### I.T.A. CONVERSION

I would be grateful if you could suggest a cure for the fault I have come across in converting my set for I.T.A.

The converter I am using is the Teletron Mark II cascade, which has been modified for band pass coupling as suggested in "Practical Television."

The set is a G.E.C. B.T.4541 T.R.F., which has been realigned to try to check the fault.

On aligning the converter, I found that I could get good sound, or vision, on rocking the oscillator core half a turn, but cannot get sound and vision together.—A. H. W. (Cambridge).

For correct conversion it is necessary for the converter's oscillator to work below the signal frequency. In your case it would appear that the oscillator is working above the signal frequency. This, of course, provides sound or vision conversion, but not simultaneous conversion of both sound and vision.

#### MARCONIPHONE VT53DA

I am endeavouring to service a Marconiphone VT53DA of which I have the circuit diagram. The trouble appears to be in the frame timebase as the raster is sharply divided. The upper half has clear line structure and answers to brilliance control, but the lower half remains bright all the time and is very blurred and milky. I have not attempted lining up for picture until I get a good raster. The frame oscillator and O.P. valves are O.K. I would be extremely obliged if you could give me a clue as to which defective components are likely to produce this symptom.—J. H. B. (S.E.17).

Hum in the vision channel is a very likely cause of this trouble. Check the picture tube for heater to cathode leakage, and also the valves in the vision channel, particularly the vision interference limiter diode and the video amplifier. Check the smoothing electrolytics.

#### FERRANTI 14T4

I get a thin line to a 2in. patchwork picture in the middle across the screen. The whistle seems to be extra strong, and does not always work. Touching base sets it going. I also get a kind of flash in neck of tube screen; it will flash (not big), then screen gets brighter. I have changed P181, ECL80, PV81, without effect. I have a chart.—G. P. (Hayes).

We are not clear on the symptom. It would help if you let us have a rough sketch of it, also indicating whether the sound channel is affected.

The flash in the tube almost certainly indicates that the tube is faulty and in need of replacement. We would not recommend replacement with a 17in. tube.

**FERGUSON 996T**

The trouble is no picture, blank screen. EHT seems O.K., line whistle present, but when set is on for a few minutes PL81 line output valve gets hot and grid and plate of this valve go red. I have replaced this valve with new one, but still same results. If anode connection from tube is disconnected, valve goes back to normal. I have checked line and frame output transformer and these seem O.K.—T. L. H. (Liverpool 5).

Try making the following modification to the tube base wiring. Tube pins numbered 1-12 (counting absent pins) from locating spigot clockwise. Remove lead from pin 2. Disconnect strap from tag 7 and connect to tag 2, i.e., tag 2 is now strapped to tag 11. Remove lead from tag 10 and place on tag 7. Connect original lead from tag 2 to tag 10.

**MARCONIPHONE VC55**

I wish to convert Model VC55 to I.T.A., and would like your advice on the matter, as being a regular reader of your journal I realise that a "turret tuner" is the best way of doing this; so could you let me know if there is one made for this model, or is there an alternative that could be fitted, and could you give me some information on how it could be done?—F. C. (E.16).

Yours is a superhet type receiver having a vision I.F. of 14 Mc/s and a sound I.F. of 10.5 Mc/s, with the oscillator below the signal frequency. A turret tuner is not available for this model; a superhet type add-on converter is generally favoured, for example, the Aerialite Type MC. Alternatively, the Valradio Type TP adaptor is suitable; this has an output at I.F. When ordering this latter type the I.F.s must be stipulated. Instructions for fitting are supplied.

**ULTRA VA72**

After the set has warmed up, there appear on the left hand side of screen four white vertical lines which appear to be wavy, otherwise picture quality seems to be quite good. Can you advise how to correct fault?—E. C. (Stratford).

This may be caused by flashover in the line output transformer during the line flyback period. This is most likely if the vertical lines are composed of short irregular horizontal lines in columns. If the lines are clear cut, however, ringing in the line amplifier may be responsible. In this case you should check the condition of the reclaim diode (part of PZ30). Also check the condition of associated capacitors.

**EKCO TS146**

My set is an Ekco TS146. It has run trouble free for 10 years but for four days I had the following failing. When I first switched it on I had a perfect, bright, clear picture, good enough for daylight viewing. After approximately six or seven minutes the picture would commence to go darker, very gradually, till finally, inside half-an-hour, very little was distinguishable of the picture and the screen was almost black. Sound, focus, line hold and frame hold, all continued normal. I could not advance the contrast beyond a certain point or the picture went negative in a very dull way. I have switched all the vision 6F13s to the sound strip one at a time, and on switching No. 6 valve I advanced the contrast a little when the picture was

going dark, and after approximately 10 to 15 seconds the brightness seemed to flow back like a valve heater getting hot. I have had no further trouble since, but I would like to know the cause. P61 and U22 + UU8—have all been time-tested O.K. I cannot think the No. 6 valve is faulty as it now works very well on sound. Could you please localise the fault for me?—R. H. (Slough).

Your description is that of an intermittent heater short in the picture tube. You do not mention how long the present tube has been in service, but if it is the original it has, indeed, done very well.

**MURPHY V118C**

When switching the set on one 500 mA fuse blows (top one). I have replaced the smoothing condenser 32/F and UU8 rectifying valve, also I have checked H.T. volts, these appear normal. The H.T. smoothing choke has a resistance of 75 ohms, the two 75 ohms resistors in series with the H.T. windings are O.K. When the 500 mA blows the UU8 rectifying valve goes fluorescent.—P. D. (Hillingdon).

Your description indicates conclusively that a short-circuit exists on the cathode side of the UU8—this may be of an intermittent nature. Make sure that the replacement valve is in good order, for it has been known for new ones to possess an internal short. If the valve is in good condition, then you will have to check systematically the H.T. line with an ohmmeter with respect to chassis, in an endeavour to locate the source of the short, bearing in mind, of course, that it may actually be in a transformer or coil.

**ETRONIC ETV1536**

The fault was some weeks ago; the Brimistor was broken and it had two 1-watt resistors in parallel with it. These had gone o/c. I couldn't tell what they should be so I put a 500 $\Omega$  3-watt and a Brimar CZ1 in. The set then worked all right for about six weeks. Then the fuse blew. On checking I found the PZ30 faulty. Pins 1 and 7 o/c, but pins 5, 6 and 7 shorted internally. Replaced valve and fuse and set then worked at full contrast and nearly full brilliance. If I turn any of these controls down severe sparking occurs in the line transformer from the EHT filament winding to the windings, and this sometimes sparks also into the PZ30. Also, when transmission is on and I take the aerial out sparking will occur without touching the controls. Turning the R.F. gain down also causes the sparking. I have checked the EHT and it is 7 kV, but rises when I turn the brilliance control down and then it sparks. I have the circuit but it doesn't give any voltages and any ohms readings for the transformer. I have changed 470K R31 in EHT line as it was high resistance and also C31 .5 $\mu$ F condenser. I also have a loud hum on sound at full volume only. I have tried replacing the ECL80 sound output and line drive valve, PL38 line output, EBC41 sound detector and bias rectifier.—J. H. (Hove).

The EHT sparking may be due to inefficient soldered connections and these should be inspected and, if necessary, remade with well-rounded blobs. Also it may be necessary to reposition the EY51. The inclusion of a 7 kV metrosil "bleeder" resistor in the EHT circuit would help matters. The loud hum on sound at maximum volume is probably due to inefficient screening of the A.F. cables or of the control itself and due to this the circuit is picking up the frame timebase hum frequency.

## TELEVISION SETS

**TELEVISION.** 9in. models, £6/10/-; 12in. models, £15/-; all makes; working; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**SEVERAL EARLY MODELS** 9in. Television, complete and mostly working, £5/5/- each; carriage paid. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

**GUARANTEED TELEVISION,** 12in. models, first-class picture, 5-channel, £30 each, carriage paid. THE GRAMOPHONE SHOP, 19-21, Brockley Rise, Forest Hill, S.E.23.

**TELEVISION,** 12in., 5 channel, tunable anywhere models, £28 each, carriage paid; guaranteed perfect. RYAN, 4, Ewcliffe Road, Forest Hill, London, S.E.23.

## COMPONENTS

**RADIO UNLIMITED,** offer Teletron converter kits 52/6, with p.p. 65/-; Goodmans (Audion 50) 12 in. P.M. 15 Ohm Spkrs. at 84/-, plus 5/- p.p. charges. Valves, SP41, SP01, 6K7, EL32, 6J5M, all at 3/6 each. ECL80, EF80, 9/-, EY51, 10/6. Valves and spares for any make of Television. Quotation by return. **RADIO UNLIMITED,** (M.O. Office), 50, Hoe Street, London, E.17.

**BAND III CONVERSION** easily carried out with Spencer-West Type 66 printed circuit Converter. Price, complete with valves and change-over switch, £2. **SPENCER-WEST LTD.,** Quay Works, Great Yarmouth.

**B.S.R. MONARCH** 3-speed auto-change units; new in maker's sealed carton; guarantee; complete with instructions, template, suspension springs, £9/15/1, carriage paid; immediate delivery. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**DIRECT T/V REPLACEMENTS** offer the most complete Handbook of T/V Components and Rewinds, price 1/-; T/V Components for all kit sets in stock. "Nuray" heater booster isolator for 2-volt C.R.T.s, just plugs in, 27/6, plus 2/- packing and postage. 134-136, Lewisham Way, S.E.14. (TDeway 3696-2330.)

**LOUDSPEAKERS** repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

**TELEVISION INTERFERENCE.** Receiver Filters, High-Pass E.5037, 30/-; Low-Pass E.5031, 30/-; Composite Band I/III, 49/6; Transmitter Filter E.5043-80dB, 1kW. £6. **LABGEAR (CAMBRIDGE) LTD.,** Willow Place, Cambridge.

## WANTED

**WANTED,** Valves 6F13, 6F15, 6T4, EY51, 5Z4, ECL80, KT61, 25A6, etc.; prompt cash. **WM. CARVIS LTD.,** 103, North Street, Leeds, 7.

**ALL TYPES OF VALVES REQUIRED** for cash. State quantity and condition. **RADIO FACILITIES LTD.,** 38, Chalcot Road, N.W.1. (PRIMrose 9090.)

**ALL TYPES** of new radio valves wanted, small or large quantities; cash payment. **R. H. S. LTD. (T),** 155, Swan Arcade, Bradford, 1.

## VALVES

**VALVES.**—Vast range obsolete types, British, U.S., etc., from 5/- to 15/-; send s.a.c. with requirements. Also large range latest types: EB91, 6/6; EF91, 7/6; EF80, 9/-; ECL80, 9/6; KT66, 10/-. **LAWRENCE,** 131, Waddington Ave., Coulsdon, Surrey.

**RATES:** 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

## FOR SALE

**EX A.M. HIGH TENSION BATTERIES.** All perfect and guaranteed. Hundreds of satisfied customers to date: 90 x 7 1/2 x 5.6, 60 x 1 1/2 x 2 1/2, 90/14 High Cap. 10/6, 64 x 86 x 4 1/2 10/6. Special offer due to further bulk purchase. Plenty to go at Midget 120v 2/3, 6 for 11/-, 12 for 20/-; 22 1/2, 2/- ea., 8 for 10/-, 18 1/2 doz.; 6 1/2 v (BIO), 4/-, 6 for 20/-, 30/- doz.; 30v, 1/9, 6 for 8/-, 14/- doz. All inc. p. & p.; s.a.c. for list. **DIGGINS,** 129, Radnor St., Hulme, Manchester, 15.

**SALE:** Premier 9 in. Telescor (London); working, £10; best offer accepted. "Phone BOW 1817."

**£20.** O.N.O. 12in. Viewmaster; expertly built to specification; 2 years old; working order. **H. MOSS,** 5, Station Road, Brompton-on-Saave, Yorks.

**TELEVISION AND TUBE BARGAINS.** 12in. 5-Channel Ferguson, tunable anywhere, M/No. 988, £25 each. Reclaimed and guaranteed C.R. Tubes, 9in. £3/15/-, 12in. £5, 14in. £5, 15in. £5/10/-, 17in. £6/10/-, plus 5/- carriage. All makes in stock. Phone Ladbroke 1734, or call 1070, Harrow Road, London, N.W.10.

## FOR HIRE

**USE OF WORKSHOP.** Holborn district, suitable for T.V. servicing or experimenter. Small weekly rental. **BRICE,** (HOL 8622.)

## MISCELLANEOUS

**EXPERIMENTAL BARGAIN.** 100 Mica, Silver Mica, Ceramic Condensers, Resistors. Ex. new receivers, short ends, but all usable values. 10.- lot. **H. JAMES,** 240, Queens Rd., E.17.

**TAN IN 24 HOURS.**—Super-tonic Sunray Lamps, ultra-violet infra-red combined; automatic exposure; controlled emission; all mains; listed £7/10/-, our price 80/-, S.A.E. brochure. Dept. 16. **SCIENTIFIC PRODUCTS,** Cleveleys, Lancs.

**CAR CIGARETTE LIGHTERS,** 6 or 12 volt, 7/6, post free. **WHITSAM ELECTRICAL PRODUCTS,** 18, Woodrow Close, Perivale, Middlesex.

**MAKING YOUR OWN?** Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets "How to Use Ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D without Viewers," price 7/6. Comprehensive list of lenses, optical, radio and scientific gear free for s.a.c. **H. W. ENGLISH,** Rayleigh Road, Hutton, Brentwood, Essex.

## TELEVISION COMPONENTS

in stock for the

**P.T. SUPER-VISOR, TELE-KING, VIEWMASTER, E.E. TELEVISOR AND BAND III** and wide angle modifications

Price lists available on request to:

**J. T. FILMER,** Maypole Estate, Bexley, Kent.  
Tel.: Bexleyheath 7267

**KEYS,** Morse, large, covered, 10/6; small, 2/6. Switches, Knife, large, DPCO, 15/-, Command RXS5, 1.5-3.0 mc/s, brand new, with valves, 55/-; BC454, 3-6 mc/s., 45/- (post 3/-). Condensers, var. spindled, ceramic, 15, 25 or 50 pfs., 1/3; 75 pfs., 1/6; butterfly 25 pfs., 1/6. Speakers, new 8 in. in round grey metal case, 27/6 (p.p. 3/-). Eddystone RXS.P40 (S450.85), 95 mc/s., 1.F29 mc/s., 10 valves, 25/- (post 3/-). RXS.112 114 (TR1987), with 3/EP91, 2/EL91, 5 gang tuner, new, 37/6, less valves, 7/6. Circuit, 1/-, Indicators, type 6L, new, 45/- (curr. 7/6). Suppressors, Radio interference, ex-A.M., 5/6 (post 2/-). Brand new RF28, 27/6 (postage 2/6). RF24, RF25, 10/6. Dynamotors, D.C., 5v input, 250v 80mA output, 11/6. Filters for these, 2/6; 12v to 250v 65mA, and 6.3v, 2.5A, 10/6. Eddystone 12v to 190v, 74mA, cased, 15/- (post 3/-); 11v to 300v 200mA, cased, 13/6 (curr. 8/6). Throat Mics, U.S.A., new, 2/6. Metal Rectifiers: 600 v 30mA, 6/-; 500v 500mA, 10/6; 1,000v 30mA, 7/6. R1355 T.F. strips only, new, with valves, 25/-; less valves, 12/6 post 2/6. Wafer Switches, 1 pole 11-way, 2 Bank, 3/6; 4 P 3 W, 4 P 2 W, 1 P 6 W, 5 B, 2/6. I.F. Amplifier 178, 13.0 mc/s., with valves, 15/6 (postage 2/6 each) Relays, 6v 2 break, 1/6. I.F.T.s 1013 mc/s., cased, new, 1/3. List and enquire s.a.c. please! Terms: C.W.O., postage extra. Immediate despatch. **W. A. BENSON (PT),** 136, Rathbone Road, Liverpool, 15. (SEP 685.)

**ENGRAVING.**—Amateurs and trade surplus can be undertaken by getting in touch with A. G. ENGRAVING, now at 292, Earlsfort Road, London, S.W.18. (Tel.: BAT 9897.) Engravers to well-known makers of Electronic Equipment used by the Aircraft industry. A.W.R.E., etc.)

**SERVICE MANUALS SHEETS,** Tel. Radio for hire, sale and wanted. S.A.E. enquiries, **W. J. GILBERT (P.T.),** 24, Fritville Gardens, London, W.12.

**PATENTS** Consultant, qualified, service. **C. L. BROWNE,** 114, Greenhays Ave., Banstead, Surrey.

## EDUCATIONAL

**BUILD YOUR OWN TV** and learn about its operation, maintenance and servicing. Qualified engineer-tutor available while you are learning and building. Free brochure from **E.M.I. INSTITUTES,** Dept. P.T.58, London, W.4. (Associated with H.M.V.)

**INCORPORATED** Practical Radio Engineers home study course of Radio and TV Engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. "The Practical Radio Engineer" journal, sample copy 2/-. 6,000 Allment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet, 1/-, All post free from the **SECRETARY, I.P.R.E.,** 20, Fairfield Road, London, N.8.


**FREE!** Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M. Brit.I.R.E., City and Guilds, R.T.E.B., and other professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees. Write to **E.M.I. INSTITUTES,** Dept. P.T.28, London, W.4.



— FROM E.M.I. INSTITUTES  
**BROCHURE ON THE LATEST  
 METHODS OF HOME TRAINING**

**CAREERS — HOBBIES — NEW INTERESTS**  
**PRIVATE AND INDIVIDUAL TUITION IN YOUR OWN HOME**

**OUR  
 BACKGROUND!**

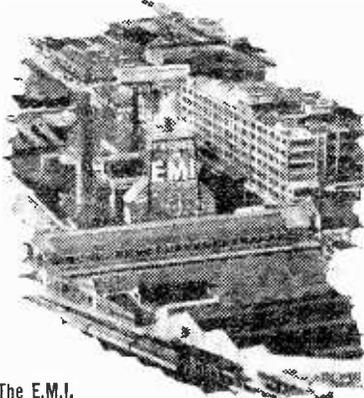

The E.M.I.  
 Factories at  
 Hayes, England:

**The only Home Study College  
 operated by a world-wide  
 manufacturing organisation**

**Over 150 Courses including:—**

- |                          |                       |                     |                     |
|--------------------------|-----------------------|---------------------|---------------------|
| Accountancy              | Draughtsmanship       | Marine Engineering  | Refrigeration       |
| Advertising              | Economics             | Mathematics         | Retail Shop         |
| Automobile Eng.          | Electrical            | M.C.A. Licences     | Management          |
| Banking                  | Engineering           | Mechanical Eng.     | Salesmanship        |
| Book-keeping             | Electrical            | Metallurgy          | Secretaryship       |
| Building                 | Installations         | Motor Engineering   | Shorthand & Typing  |
| Business                 | Electronics           | Photography         | Short Story Writing |
| Management               | Engineering Drawing   | P.M.G. Licences     | Short Wave Radio    |
| Carpentry                | Heating & Ventilation | Police              | Sound Recording     |
| Chemistry                | Engineering           | Production Eng.     | Telecommunications  |
| Civil Service            | High Speed Oil        | Production Planning | Television          |
| Commercial               | Subjects              | Radar               | Time & Motion Study |
| Commercial Art & Drawing | Industrial Admin.     | Radio Amateurs      | Tracing             |
| Customs & Excise Officer | Jig & Tool Design     | Certificate         | Welding             |
|                          | Journalism            | Radio & Television  | Workshop Practice   |
|                          | Languages             | Servicing           | Works Management    |
|                          |                       | Radio Engineering   | and many others.    |


Also courses for University Degrees, General Certificate of Education, B.Sc.Eng., A.M.I.Mech.E., L.I.O.B., A.C.C.A., A.C.I.S., A.M.Brit.I.R.E., A.M.I.I.A., A.F.R.Ae.S., A.M.I.M.I., A.C.W.A., A.M.I.E.D., City & Guilds Examinations, R.S.A. Certificates, R.T.E.B. Serv. Cert., etc.

**NEW! LEARN THE PRACTICAL WAY  
 HOME COURSES—WITH EQUIPMENT**

Whether you are a student for an examination, starting a new hobby, intent upon a career in industry or running your own business — these Practical Courses are intended for YOU.

With these outfits, which you receive upon enrolment, you are given instructions that teach you the basic principles in the subject concerned.

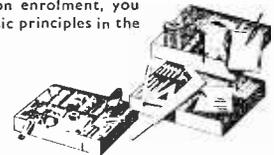**COURSES WITH PRACTICAL EQUIPMENT INCLUDE: RADIO** (Elementary and Advanced) · **TEL. VISION** · **MECHANICS** · **ELECTRICITY** · **CHEMISTRY** · **PHOTOGRAPHY** · **CARPENTRY**. Also Draughtsmanship · Commercial Art · Amateur S.W. Radio · Languages.



Courses from 15/- per month

**POST THIS COUPON TODAY**

Please send without obligation your FREE brochure.  
 E.M.I. INSTITUTES, Dept. 138, 43 Grove Park Road, London, W.4.

NAME ..... [BLOCK CAPS PLEASE]

ADDRESS .....

SUBJECT(S) OF INTEREST .....

November (We shall not worry you with personal visits) I C.75A

**EMI INSTITUTES**

An Educational Establishment associated with the E.M.I. group of Companies including 'HIS MASTER'S VOICE', MARCONIPHONE, etc.

# News From the Trade

## Signal and Pattern Generator

**R**ADIO and TV Components of Acton announce a new Generator which is illustrated below. The frequency coverage is from 7.6 to 210 Mc/s in five switched ranges. Modulation is at 400 c.p.s., 81 kc/s or the output may be used unmodulated. The audio voltage is available at a separate output socket. The single attenuator controls both the R.F. and the A.F. output. The front panel contains the mains on/off switch, the audio output socket, and




Other features of this new component include easily accessible screw terminals, cable clamps gripping both the insulation and braiding of cables, and inductances wound on nylon formers with factory pre-set cores. The Triplexer is finished in attractive "hammer-bronze" enamel. Egen Electric Ltd., Chaffleet Industrial Estate, Canvey Island, Essex.
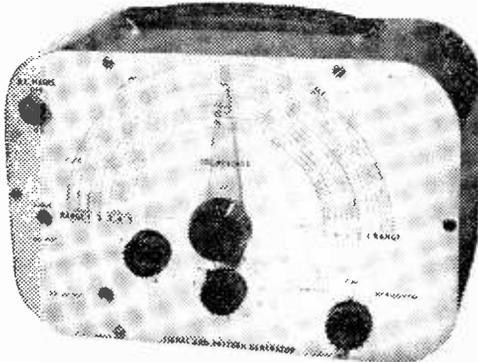
## New Grade of Plessey Magnetic Material

**T**HE range of "Caslox" magnetic materials, manufactured by The Plessey Company Limited for use in television receiver focusing magnets, has been extended by the introduction of a new type known as "Caslox" Grade III.

Basically, this material, like earlier "Caslox" grades is a non-metallic magnetic ferrite for use in geometrical configurations where metallic magnets are unsuitable. It has a high stability which results from a high value of coercivity and a permeability only slightly greater than unity.




The Radio and TV pattern and signal generator.

the R.F. output socket. The frequency range switch is marked 1 to 5 to correspond with the scale markings and the output attenuator is marked 0-10. The modulation switch selects the frequency of modulation, and in the "vertical" position the signal is modulated at 81 kc/s and will show eight vertical lines on the screen of a TV receiver which should be evenly spaced if the receiver is correctly adjusted. In the "horizontal" position (400 c.p.s.) eight horizontal bars will show. The lower range from 7.6 Mc/s upwards may, of course, be used for aligning I.F. stages and F.M. receivers. The case is finished in grey and the price is £6 19s. 6d. (plus 5/6 for post and packing).—Radio and TV Components (Acton) Ltd., 23, High Street, Acton, W.3.
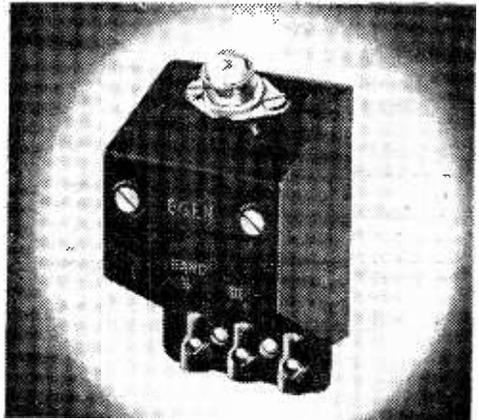
## Egen Aerial Triplexer

**A** NEW Aerial Triplexer, Type 163, has been introduced by Egen Electric Ltd. to combine or separate aerial signals in Bands I, II and III as required in almost any arrangement of aerials and television and V.H.F. radio receiver sockets.

In addition to providing all the known advantages of the conventional Band I/III diplexer, the Egen Triplexer also covers Band II, allowing signals from separate Band I, II and III aerials to be fed to a TV/V.H.F. radio receiver with a single aerial socket, or signals from a combined Band I, II and III aerial to be fed to separate sockets.



The Egen "Triplexer."

It consists of a powered magnetic ferrite which is bonded into the shapes desired by the addition of a small quantity of resinous binder. This technique enables tolerances of  $\pm 0.005$  in. to be achieved.

A wide range of different shapes can be produced. When "Caslox" is used in scanning coils and ion traps, the magnets can be very compact, featuring high magneto-motive force and very low-leakage flux.—The Plessey Co. Ltd., Ilford, Essex.

## QUERIES COUPON


This coupon is available until NOVEMBER 21st, 1956, and must accompany all Queries.

PRACTICAL TELEVISION, NOVEMBER, 1956.

**DARK EVENINGS AHEAD . . . .**

Start building the

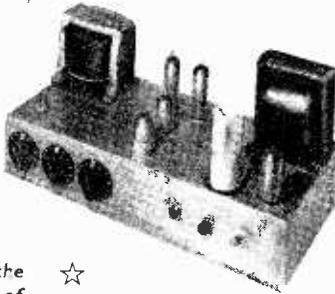**MULLARD FIVE-TEN HIGH QUALITY AMPLIFIER**



and enjoy the thrill of really Hi Fi radio and gram reproduction.

All parts in stock and detailed price list available. Full constructional details including FM tuner with wiring diagrams, etc., are contained in "High Quality Sound Reproduction," price 3/6. Get yours today—and have fun this winter.

We also stock all parts for "912-PLUS," Jason and Mullard FM tuners, and a full range of WB Stentorian, Goodmans and Wharfedale speakers.

**HOME RADIO (Mitchem) LTD.**

187, LONDON ROAD, MITCHAM, SURREY. MIT 3282

**"You can rely on US" for . . .**

**ALL RADIO and ELECTRONIC COMPONENTS**

One of Britain's Largest Stockists of all Leading Makes : Hunts, T.C.C., Haynes, Allen, Denco, Osmor, Weymouth, Morganite, Bulgin, Belling Lec, Teletron, R.E.P., Scotch Boy, Ellison, Elstone, Partridge, Wynall, Westinghouse, S.T.C., AVO, Taylor, Goodmans, J.B., Wharfedale, Wearite, Acos, etc.

Suppliers to : Ministries, Development Laboratories, Education Authorities, etc.

Some of the more difficult parts you may not be able to acquire :

Tapped Vol. Control, Linear C.T.  $\frac{1}{2}$  mg.,  $\frac{1}{4}$  mg., 1 mg., 7/6. Linear  $\frac{1}{2}$  mg.,  $\frac{1}{4}$  mg., 1 mg., 6/6. Post 6d.  
High Stab.  $\frac{1}{2}$  w. Resistors. 2% Range, 100 $\Omega$  to 2 mg., 1/6 each. 1% Silver Micas up to 100 pf., 1', 280 pf., 1/2. 500 pf., 1/4. 1,000-5,000, 2/6. Post 6d.  
Now a full range of  $\frac{1}{2}$  w. 1% High Stab. resistors 100 Ohms to 2.2 mg., 2 - each.

Thousands of Valves, Condensers, Resistors—Can We Help You?

MULLARD 510 and GEC 912 all specified parts and lists available.

Catalogue, Book Lists, S.A.E.

**RADIO SERVICING CO.,**

82, SOUTH EALING ROAD, LONDON, W.5.

Tel. : EAL 5737. Next Sth. Ealing Tube, 65 Bus. 1 p.m. Wed.

**SPENCER-WEST TYPE 50 BAND III CONVERTER**



Ask for Leaflet Ref. 2356 which gives full technical details of this wonderful new unit.

Perfect results with any receiver. From your dealer or on 7 days' approval from :

**SPENCER-WEST, LTD.**

Quay Works, Great Yarmouth

Phones : 4794 & 3009

**!! RECORDERS !!**

We are London's largest stockist of tape recorders. All makes and types available from stock.

We also have a large quantity of used and H.P. reprocessed Guaranteed machines at Bargain Prices for the personal shopper.

Recorders bought, sold, repaired and part exchanged.

Collaro 3-speed tapedeck £20.10.0 good selection of surplus valves, speakers and components.

No Lists.

**JACKSON RADIO**

163, Edgware Road, London, W.2

Telephone : PAD 0537

OPEN ALL DAY SATURDAY.

**RADIO AND TELEVISION COMPONENTS**

All parts in stock for : Viewmaster, Soundmaster, Telexing, etc. Easy Terms available. 24d. stamp (only) for Catalogue.

**JAMES H. MARTIN & CO.**  
FINSTHWAITE, NEWBY BRIDGE,  
ULVERSTON, LANCs.

AIR-SPACED CO-AXIAL CABLE, 75 90 ohms, 7/36 new. 9d. per yd.  
MIDGET VOLUME CONTROLS. Long spindles, new, boxed. 10k-2 meg. Less switch, 2/10 S.P., 4-; D.P., 4/4.

CONDENSERS. Fully tropicalised, all at 500 volt working. Prices per dozen. Not less than 1 dozen supplied. 100 pF., 4/6 ; 250 pF., 5- ; 500 pF., 5- ; 1,000 pF., 5/6 ; 2,500 pF., 6- ; 5,000 pF., 7- ; .01 mfd., 7/6 ; .025 mfd., 8/6 ; .05 mfd., 9- ; 1 mfd., 12- ; 25 mfd., 14/6 ; 5 mfd., 18/6.

These condensers are new and of current manufacture—not to be confused with inferior types, or old stock.

WALNUT EXTENSION SPEAKER CABINETS, 6in., 14/6 ; 8in., 18-.

TELEVISION AERIALS. 3 Element Band III, 28/6 ; 5 Element, 39/6 ; B.B.C. "H" 70- ; B.B.C. "X" 74/6. Also many other types in stock. Send us your requirements and we will quote by return. No rubbish.

Wolsey, Aerialite, Lumex, etc.

CONDENSER BARGAIN. 8+8 mfd. 350 volt Dubilier, 2/6 each. 2 amp. Mains Droppers, 7/7 ohms tapped at 600 ohms. 2 - each.

2 Gang Tuning Condensers, .0005 with trimmers with feet for fixing. Brand new, made by "J.B." 8/6 each. Postage 1/3.

**GUARANTEED VALVES**

OZ4	5/8	6U5C	7-	25L6	7-	DF96	9/6	
1A5	5/-	6CD6	19/6	807	6/-	DAF96	10/-	
11LN5	4/6	6V6C	7/6	1623	6-	DL96	9/6	
11LD5	5/-	6U7	6/6	PEN46	6/6	UCH42	8/6	
1A7	13/10	6J5	5/6	EC180		UBC11	8/-	
1R5	8/6	6AQ5	7/6			1110	14/9	
1T1	7/-	6AT5	7/6	ECF82	13-	Y81	10/6	
1S5	7/-	6BW6	7/6	EC84		Y82	7/3	
2P	8/6	7A7	6/-			12/6	EB91	7-
2X2	5/-	7Q7	6/-	EY51	11/3	PL81	13-	
5Y3	8/-	7Y4	8/-	PCC84		PL82	10-	
5Z4	8-	12A6	8-			12/6	ET90	9/6
5U4	8-	12AT7	7-	EL84	9-	ECH81		
6K7	7-	12S7J	7/6	DK96	9/6	KT36	10/6	
6K8	8/6	12C8	7/6				19/6	

Terms : C.W.O. or C.O.D. Postage and packing : Under £2. 1/3 ; Under £3, 1/9 ; £4 and over goods sent post free.

**ELECTRO-SERVICES & CO.**

221, BATTERSEA PARK RD., LONDON, S.W.11. MAC. 8155.

# FREQUENCY MODULATED RADIO

By K. R. Sturley.  
45/- Postage 9d.

**TRANSISTORS IN RADIO AND TELEVISION.** By M. S. Kiver. 37s. 6d. Postage 1/-.

**RADIO VOLUME 3.** By J. D. Tucker & D. Wilkinson. 12s. 6d. Postage 6d.

**V.H.F. TELEVISION TUNERS.** By F. H. Fisher. 21s. Postage 9d.

**RADIO VALVE DATA,** compiled by "Wireless World," New 5th. edit. 4s. 6d. Postage 6d.

**CORRECTING TELEVISION PICTURE FAULTS.** By J. Cura & L. Stanley. 3s. 6d. Postage 4d.

**FREQUENCY MODULATION RECEIVERS.** By J. D. Jones. 17s. 6d. Postage 9d.

**HANDBOOK OF LINE COMMUNICATION VOL. 1.** The Royal Signals. 30s. Postage 1s. 3d.

## The MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23, PRAED ST., LONDON, W.2

Write or call for our catalogue.  
Phone: PADDINGTON 4185.  
Open 6 days 9-6 p.m.

# VALVES

By return post  
All NEW and BOXED

1R5	8/-	6K8G	8/-	ECL80	10/-
1T4	7/-	6Q7GT	9/-	EF80	9/6
1S5	7/-	6K7G	5/6		
3B4	7/3	6V6G	7/3	SP61	3/-
3Y4	8/-	6V6GT	7/3		
3Q4	8/6	6F6G	7/-	12K8	11/-
6X4	8/-	6X5G	7/-	12K7	9/6
DK92	8/-	6SN7GT	8/-	12Q7	9/-
DAF96	9/-	6S17GT	8/-	35L6	9/-
DF96	8/6	6L6G	10/-	50L6	9/6
D196	8/6	5U4C	8/3	35Z4	8/-
		5Z4G	9/-	RT11	3/-
7B7	9/3	5Y3G	8/-	25Z4	9/-
7B7	8/6	80G	8/-	25L6	10/-
7CG	8/6	6BE6	9/-	MU14	8/-
7C5	8/6	6BA6	9/-		
7Y4	8/6	6AC6	9/-	ECH42	10/-
		6BW6	9/-	EF41	9/-
ECH81	9/3	6N4	8/-	EBC41	10/-
EABC80	9/-	6AL5	9/-	EL41	10/-
EBP80	10/-			EZ40	8/-
EM80	10/-	PY80	9/6	EZ41	9/-
EZ80	8/6	PY81	9/6	EAF42	8/-
EP85	9/-	PY92	9/6		
EL81	11/-			UCH42	10/6
				UP41	9/-
ECC81	9/6	PCF80	8/6	UC41	9/-
ECC82	10/6	PCF82	11/6	UA41	11/-
ECC83	10/-	PCC84	9/-	UL41	9/3
ECC84	12/-	PCC85	12/6	UY41	9/3
ECC85	10/-	PL83	12/6	UBP80	10/-
ECF82	12/6			10P1	10/-
EP86	12/-	PL81	10/6	U35	19/-
EV51	11/-	PL82	9/6	20L1	10/6
EV86	12/-	PL83	12/-		

Postage 5d. per box per valve.

## MARTIN PRODUCTS

UPPER DICKER, HAILSHAM,  
SUSSEX, ENGLAND

# "VIEWMASTER"

Printed Circuit Converter

No Patterning  
or Breakthrough

We can supply the complete kit of parts including valves, **£5.0.0**

Send for detailed list of this kit and others, **POST FREE.**

Set of coils for conversion of Viewmaster receiver, **£1.15.0**

## AUDIO LTD., Tower Road, London, N.W.10



**PULLIN**  
SERIES 100  
TEST METER  
AC/DC 10,000µV  
21 RANGES  
100µA to 10000µV  
FULLY GUARANTEED

SENT POST FREE FOR **£2.10s.** DEPOSIT AND NINE FURTHER MONTHLY PAYMENTS OF **£1.1s.** CASH PRICE **£12.7s.**

### FRITH RADIOCRAFT LTD

69-71 CHURCH GATE LEICESTER  
& 28 HIGH ST NEWPORT PAGNELL Bucks

### OSMOR CONVERTERS

LONDON, BIRMINGHAM, MIDLANDS. Simple, efficient for all TV (including TRF). Guaranteed no break-through of Band I or re-radiation. Approx. 1 hr. to build. Will convert any Band III channel to any Band I channel. AC or AC/DC. Kit, £25.0. Ready wired, £40.0. Post free. Terms: C.W.O. Post orders only. **THE ELECTRONIC SUPPLY CO.** 29, Leigh Rd., Highbury, London, N.5

### RES/CAP. BRIDGE 35/-

Post Paid  
Checks all types of resistors and condensers

Easy to Build Up Easy to Use  
**READY CALIBRATED**

Stamp for details of this and other kits.  
**RADIO MAIL, 6 Raleigh St., Nottingham**

### ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP,  
WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

### H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.  
SLOane 3463

Works at:

36, ROSEBERY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small"



### QUALITY TELEVISION COMPONENTS

SCANNING COILS, 6 10 kv. R.F., E.H.T. UNITS, E.H.T. and OUTPUT TRANSFORMERS, LINE FLY-BACK E.H.T. UNITS.

COIL KITS FOR "P.T." BAND III CONVERTERS

Write for illustrated list (Publication 75)

**HAYNES RADIO Ltd.,** Queensway, Enfield, Middlesex.

### NEW-MAX ELECTRONICS LTD.

220, Edgware Rd., London, W.2 Tel. PAD. 5607

Come and visit us. The largest Electronic Bargains Store in London. We have 500 Repossessed T.V.s, all sizes always in stock, also Radio Sets, Radiograms, Reclaimed and guaranteed C.R. Tubes, 12in. £5, 14in. £6 10/-, 15in. £7 10/-, 17in. £8 -/-, p. and p. 10 -/- Tubes with Heater Cathode Short, 14in. £3 10/-, 15in. £4 10/-, 17in. £5 -/-, p. and p. 10 -/-. Surplus Valves, Components and Test Equipment, etc., etc. Also available all types and makes of new C.R. Tubes at list prices. Part exchanges welcomed!


### SPECIAL OFFER

Projection T.V. Unit. Complete optical projection box with focus and frame coil, usual cost £30 our price £6 -/- incl. p. and p. Any set can be converted to large screen T.V. with this unit by increasing E.H.T. (to approx. 15-20 kv).
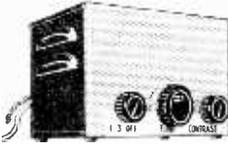
# BAND III T.V. CONVERTER

12 months' guarantee all items.

FOR I.T.A. LONDON, BIRMINGHAM, MANCHESTER, YORKS, GLASGOW. For superhet or T.R.F. State B.B.C. station. Fully wired with power pack, aerial switching, tested and ready for use.



## £4-10-0


Post Free  
C.O.D. fee 1/6 extra

with valves EF91 and 12AT7 (ECC81) and metal rectifier. NO ALTERATION TO YOUR SET. OR in walnut cabinet, 3 knobs, 2 valves 12AT7, and metal rectifier. £5. (C.O.D. 1/6.) OR in chassis form with power pack, £4.2.6. BAND I aerials: Telection "X" with pole and lashing, 55/- . "H" aerial with lashing, 50/- . Co-axial cable. 7d. yd. Low loss, 9d.

Filter eliminating Band I pattern on I.T.A., 8/-, 1,000 pf, 2,000 pf, 3,000 pf ceramics, 4/6 doz. 0.5 pf, 3.3, 4.7, 6.8, 20, 22, 30, 35 pf, 4/- doz. Part 7-v. T.V. strip with famous mnfr. (over 50 ceramics and resistors) with drawing, 10/-.

## GLADSTONE RADIO

P.O. BOX 8, CAMBERLEY, SURREY

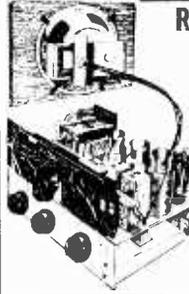

## RADIO - GRAM CHASSIS 29/9

including 8in. Speaker, Dial and Knobs, 5 Valve 8 Hot, 3 Wave Band, A.C. Mains. Complete, tested, guaranteed. Less Valves. Post and Packing, 4/6.

## CHRISTMAS PRESENTS! P.M. SPEAKERS—8"—8/9

Ideal Xmas Gift, if fitted in small cabinet. Treat the lady at home. Fit one in kitchen or cupboard door. Let her follow that T.V. or Radio Programme. At this price you can have one in every room. Post 1/9.

## CANDELABRUM—19/9


3 Light Lounge Fitting, with flex and lamp holders and 3 shades in glass or plastic. Special purchase makes us able to sell at this very cheap price. P. & P., 2/6.

## MIDGET RADIOS—7/6

A.C. S. Het., 4 valve and rec., ready to use. In Walnut Cabinet. P. & P., 4/6.
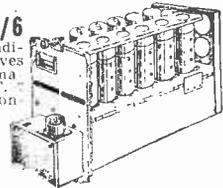
## V.H.F. 1466 RECEIVER, 27/6

with 6 valves, ex-W.D., new condition, 6 channel tuning. Receives T.V. sound, police, fire and amateurs, 30.5 m/cs to 40 m/cs. I.F. m/cs. Post 2/6. Drawings and Conversion data free with each set. (Similar to 1124 set but with slow motion dial.)



REMEMBER, SATURDAY  
OPEN ALL DAY.

# DUKE & CO.

621, Romford Road, Manor Park, London, E.12  
GRA 6677-8

## TECHNICAL TRADING CO.

SPECIAL BARGAIN 12 V. 4 AMP RECTS. 9 6 EA., £5 Doz. Iron Selection, Full Wave, heavy, compact. No. 18 WALKIE-TALKIES. 69/- . WIDE ANGLE TRANSFORMER KITS, boxed, one-thing: (a) Line Transformer 14 Kv., recumbent base, RYJ1 mounting, ferrocore core, 17/6 with instructions. (b) Frame Transformer, large efficient for RCL50, 9 6. (c) 250 ma 7 H Smoothing Chokes, 3 way mounting, 7 6. COMPLETE KIT AS ABOVE. Strip Price for 3 items, 30/- . Width coils to match above, 4 - ea. ION TRAP MAKERS. Best quality, 9 6. ALADDIN FORMERS 12s. with slug, 4 - doz. VISCONOL CONDS., 300 mf., 18 Kv., 4 9. DEFLECTION COILS, standard 35 mm., iron core, 9 6. 5 CHANNEL TUNERS. Complete classic, famous make, for EF50 and ECC81 (less valves), 12 6. BOWLER HATS, 1 - . FOCUS MAGNET HANDLES, 6 6. LOUDSPEAKERS, Top make, 7 x 4 elliptical, 17 6. (A) P.M., 10 - 8in. P.M., 12 6. (B) 8in. P.M.P.T., 7 6. THROAT MIKES, British, 20 6. Single I.R. earphones with headband, 2 6. TV TABLE CABINETS. Top make, brand new, boxed, beautiful appearance, latest designs. 14in., 19 - ; 17in., 22 6. ditto with mask and glass, 14in., 29 - ; all 7 6. corr. COSBOR D.B. 'SCOPES, £18. WIREWOUND PRE-SET POTS, 500Ω, 1 K, 2.5 K, 5 K, 10 K, 20 K, 25 K, 50 K, 2 - ea. MARGONY VALVE VOLT-METERS, £10. AMPHENOL HOLDERS, Gerol, Mazda, Sovat, BTG, B93, 6 - doz. Rac W Screw, 1 6 ea. Tube Holders, total, 6d. Diodeval, 1 - . 1 MEG POTS D.P. SWITCH, 3 6in. spindle, small type, 3 6. Ditto, 1in. spindle, 2 6. RESISTANCES ASSORTED. 1-5 w., 47Ω-10 MΩ, 2 - doz., 10s-100s. AVO VALVE TESTERS. K.V., 1000 Ω, transit case, 29. MIDGET CERAMIC CONDENSERS. 10, 20, 200, 500, 1000, 3000, 6 - doz. 16, 16 250 v., 3 - . Midget 22, 22, 250 v., 2 6. Midget 8 x 250 v., 1 - . Midget 100 tad x 6 v., 1 - . 60 - 100 250 v., 6 - . ORGANTONE RADIOGRAM CHASSIS, 28. F.M. CHASSIS. Drilled 6 valve receiver, hammered finish, 1 6. F.M. RECEIVERS, 5 valve, speaker, heavy case, listed £20, £11. CHASSIS, 2 - 4 x 11, 2 9. 6 v. 41 x 21, 3 - . 8 x 5 x 21, 3 6. 8 x 6 x 21, 4 9. 8 x 10 x 21, 5 9. All best quality heavy aluminium sheet. 5H 250 mA CHOKES. Compact type, special shop, 4 6 ea. INDICATORS TYPE 95. 16 valves, V.I.R.T., complete, 39 - . curr. 5 - . AMERICAN SCR528 TRANCEIVERS. Complete, 522 valves, £4, curr. 6 - . TEN 5-CHANNEL COILS. 5 - tunable, 71 1/2" and resistors. Nos. 9 - set. DISTRESS TRANSMITTERS. 4 - . Atlatx with valve dipole telescopic aerial. Weight 1 lb., 12 8. 29 WAY DOUBLE TAG STRIPS, 16. EARTHING STRINGS, 4d. VOLTAGE ADJUSTER PANELS. Complete, 6d. DOUBLE FUSEHOLDERS. With 5 amp. plug, 9d.

### RADIO VALVES GUARANTEED PERFECT

6AK5	4 -	6J6	5 -	12AT7	8 8	6F92	5 -	6P61A	2 6
6AC5	5 -	6J70	5 -	807	5 6	6E09	5 6	6P210	3 6
6C4	6 6	6L6	4 -	6X4	5 6	6E25	8 -	12A2	3 6
6E41	6 6	6K6	6 6	6R4	1 6	6E25	5 -	VR150	30 -
6E43	9 6	6K7M	6 -	ECC81	8 -	6P61	3 -		6 -

Postage 1/- in 21. (1 9 in 21) Speakers Trans. minimum 9d. No C.O.D.

### 1,000 OTHER BARGAINS TO CALLERS AT

350/352, FRATTON ROAD, PORTSMOUTH

PORTSMOUTH'S RADIO, TV AND TOOL SHOP

## HANNEY of BATH offers:—

ERIE RESISTORS, all values from 10Ω to 10MΩ. Type 9 (1 watt), 6d. ; Type 8 (1 watt), 8d. 10 watt 512ct, wire-wound resistors, all values 10Ω to 10 KΩ, 2 - each.

SILVER MICA CONDENSERS, top quality, close tolerance up to 33 pF 11 pF, from 33 pF up to 1.5 pF, 1.5 pF to 30 pF, 1 - each ; 316 pF to 815 pF, 1 3 each ; 1,000, 1,500, 1,800 and 5,000 pF, 2 - each.

SILVER CERAMIC CONDENSERS, 3 pF to 500 pF, 1 - each. Hi-K Midget Ceramics, 500, 630, 1,000, 1,500, 2,200, 3,000, 5,000 and 10,000 pF, 1 - each.

COILS, Osborn "O." full range, 4 - each ; Weymouth "H" type, full range, 3 9 each ; Weymouth CT2W2 coils, TRF, 10 3 pr. ; Denco Type "C" TRF, 9 - pr. ; REP Crystal set coils, 2 6 ; Single TRF, 4 - ; Matched pr. TRF, 8 - . Denco 465 Kcs a midget 1.F.s, 12 - pr. ; Weymouth, ditto, 15 - pr.

COILPACKS, Osborn Type HO, 50 5 ; H.F. stage for HO, 21 - ; Osborn TRF (L. and M.W. only), 42 - ; Denco CP.3 370 and CP.3 500, 44 9 each ; CP.4L and CP.4M, 55 - ea. h. ; CP.4L G and CP.4M G, 43 5 each.

FERRITE ROD AERIALS, M. and L.W., 12 6 each by Denco, REP and Teletron.

TRANSISTORS, MULLARD OC.50, OC.51, OC.72, 30 - each ; OC.70, 21 - ; OC.71, 24 - . BRIMAR, 3X100N, 3X101N and 3X300N, 40 - each ; 3X301N, 45 - ; 3X302N, 50 - .

GERMANIUM DIODES, BRIMAR GD3, GD4 and GD5, 7 6 each. MULLARD OA70, 5 - . OA71, 6 - . G.E.C. 6EX34 and 6EX35, 4 - each.

METAL RECTIFIERS, Full range of the popular types of Westinghouse and Brimar available.

ALL COMPONENTS and PRICED PARTS LIST ARE AVAILABLE for:

Osram 912 AMPLIFIER, Passive Unit and Pre-Amplifier. MULLARD 510, 20 watt, 3 watt Amplifiers and Pre-Amplifiers. MULLARD, OSRAM, WIRELESS WORLD, DENCO and TSL, F.M. UNITS, HIGHWAYMAN, VIEWMASTER, V-MASTER 3 STATION TUNER CONVERTER, TELEKING, MACNAVINE, etc., etc. Send 21d. stamp for lists required. Please add sufficient postage to orders under £3.

## L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

# TELEVISION TUBES

MULLARD ...	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0	} Ex Stock
COSSOR ...	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0	
EMITRON ...	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0	

MAZDA. 12in. only £6.10.0. 14 Weeks Delivery.

All Tubes plus 12/6 carriage and insurance.

## SIX MONTHS' GUARANTEE

Converter M.1.	Midlands area, high gain, own power supply, built in crossover unit	£9.9.0
Converter M.2.	Midland fringe area, own power supply	£9.18.0
Crossover Box.	Low loss	12/6

Finished in Stove Enamelled Steel Case.

Terms to the Trade.

## RE-VIEW (LONDON) LTD.

81, HIGH STREET . . . . . MERTON. S.W.19

Telephone : CHERRYWOOD 3255

## MAKE SOUND JOINTS SIMPLY BY USING Multicore

### ERSIN MULTICORE

Contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON

5/-

HANDYMAN'S CARTON

Suitable for 200 average joints. 6d.



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

### ARAX MULTICORE

FOR METAL FABRICATION

(Not wire-to-tag joints)

Contains 2 cores of Arax flux. Flux residue is easily removed with water.

SIZE 8 CARTON

5/-

Handymans Carton 6d.



### HOME CONSTRUCTORS 2 1/2 PACK

In addition to the well-known Home Constructors Pack (containing 19ft. of 18 s.w.g. 60/40 alloy) a similar pack is now available containing 40ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits



### BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire. cuts wire cleanly, splits extruded flex 3/8 each



## BAND III AERIALS OR FITTINGS

Whether you are contemplating the construction of a Band III aerial or purchasing one complete it will be well worth your while to write to us who, as manufacturers, can offer you real

### VALUE FOR MONEY

THE FOLLOWING IS A CROSS SECTION OF ITEMS TAKEN FROM OUR NEW COMPREHENSIVE CATALOGUE.

- \* 10 Element Band III Aerial, 77/6.
- \* 8 Element Band III Aerial, 62/6.
- \* 6 Element Band III Aerial, 47/6.

### FITTINGS

- \* Universal Band III Clamp-on Fitting.
- \* Band III Insulator, complete with folded dipole.
- \* Director and Reflector Rod Holders for Bands I, II, and III.
- \* Straight and Cranked Masts (all sizes).
- \* Chimney and Wall Brackets. Alloy Tubing, etc. etc.

Send 1/- P.O. for the NEW MULTI-PAGE illustrated Catalogue (together with element and boom measurements (all Bands) to help the constructor) to :

**FRINGEVISION LTD.** MARLBOROUGH, WILTS. Phone 657/8

### MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3635)

# 2 'musts'

## for the home constructor



### THE G.E.C. 'nine-one-two PLUS'

The publication contains step by step wiring instructions for this high quality Amplifier together with many additional features of exceptional interest to the Home Constructor.

PRICE **4/-** from your dealer or by post—5d. extra—from the G.E.C. Valve and Electronics Dept.

### THE "FM PLUS" TUNER

The "FM PLUS" Tuner is ideal for use with the 'nine-one-two PLUS' Amplifier and the publication gives constructional details and suggests circuits for inter-station noise suppression and a 'magic eye' tuning indicator.

PRICE **2/6** from your dealer or by post—5d. extra—from the G.E.C. Valve and Electronics Dept

**G.E.C.**  
*Valves*

THE GENERAL ELECTRIC CO. LTD · MAGNET HOUSE · KINGSWAY · LONDON WC2