

A TUBE TESTER & REJUVENATOR

Practical Television '13

DECEMBER:1957

AND TELEVISION TIMES

EDITOR:F.J.CAMM



CONTENTS

- SIMPLIFIED TV SOUND RECEIVERS
- FLYWHEEL SYNC SCANNING AND SYNCHRONISATION
- SIMPLIFIED TV SERVICING YOUR PROBLEMS SOLVED
- Etc. Etc Etc.

THE

MULTIMINOR

The "Avo" tradition of pioneering enterprise again finds expression in a new multi-range meter of compact size, robust construction, and thoroughly sound design.

It is a rectifier/moving coil instrument, simple to use, easy and quick to read. A single rotary switch selects any one of the 19 ranges. One pair of connection sockets deals with any measurement. One scale is provided for current and voltage readings and another for resistance.

Sensitivity :
10,000 Ω/V on D.C. voltage ranges.
1,000 " " A.C. " " " "

Accuracy :
On D.C. 3% of full scale value.
On A.C. 4% " " " "

Designed and Manufactured by

AVO Ltd.

19 RANGES

D.C. Voltage	A.C. Voltage
0—100 mV.	0—10 V.
0—2.5 V.	0—25 V.
0—10 V.	0—100 V.
0—25 V.	0—250 V.
0—100 V.	0—1,000 V.
0—250 V.	
0—1,000 V.	D.C. Current
	0—100 μ A
	0—1 mA
Resistance	0—10 mA
0—20,000 Ω	0—100 mA
0—2 M Ω	0—1 A

List Price :

£9' 10s.

complete with Test Leads and Clips

AVOGET HOUSE · 92-96 VAUXHALL BRIDGE RD. · LONDON · S.W.1



Pocket size: 5 3/8" x 3 3/8" x 1 1/2" ins.
Weight: 1 lb. approx.




Leather Case if required 32/6

a Great little Instrument



Telephone : VICtoria 3404 (9 lines)

Build your own Aerials...

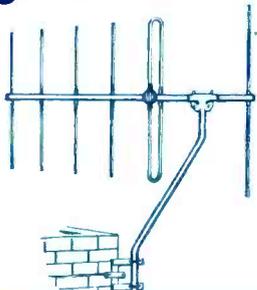

AT HOME


AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.
Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above to :-

Fringelevision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

NEW! THE PRACTICAL WAY

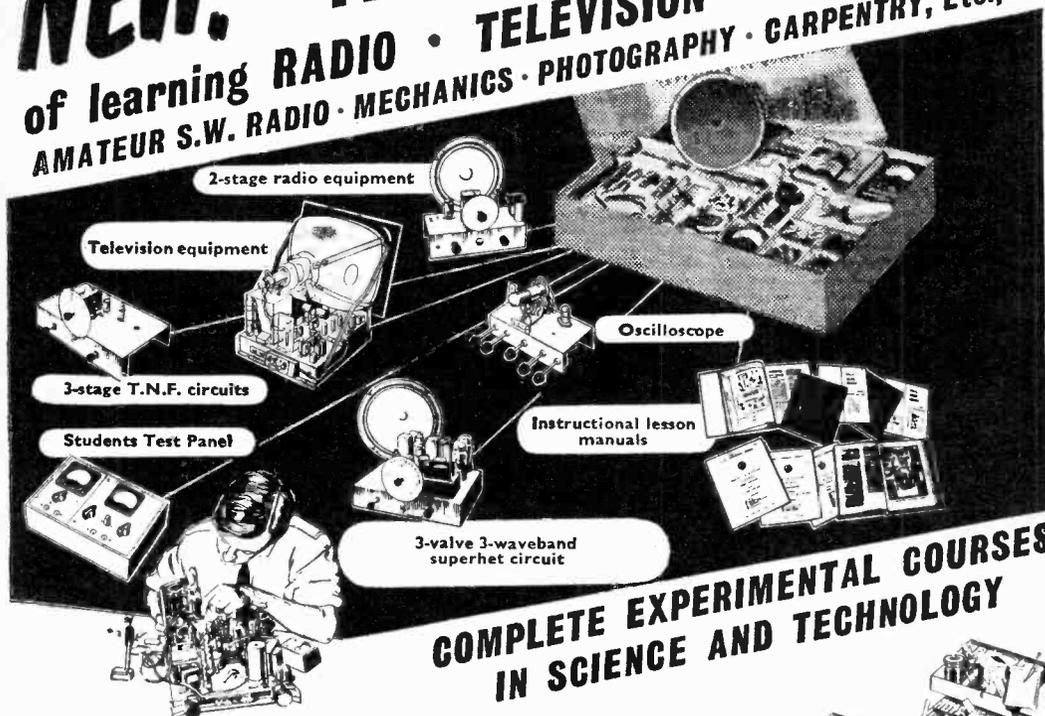of learning **RADIO · TELEVISION · ELECTRONICS**
AMATEUR S.W. RADIO · MECHANICS · PHOTOGRAPHY · CARPENTRY, Etc., Etc.



2-stage radio equipment

Television equipment

3-stage T.N.F. circuits

Students Test Panel

Oscilloscope

Instructional lesson manuals

3-valve 3-waveband superhet circuit


COMPLETE EXPERIMENTAL COURSES IN SCIENCE AND TECHNOLOGY

NEW... Completely up-to-date method of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teachers.

NEW... Experimental outfits and lesson manuals sent on enrolment remain the student's property. Tutor allotted to each student for personal and individual tuition throughout the course. Radio and television courses, with which specially prepared components are supplied, teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern radio and T/V receivers. If you are studying for an examination, wanting a new hobby, commencing a career in industry or running your own part-time business, these practical courses are ideal and may be yours for moderate cost. Fill in the coupon to-day for a free Brochure. There is no obligation whatsoever.

SUBJECTS

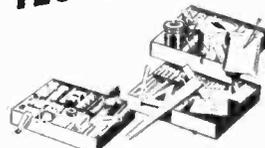- INCLUDE:—**
- RADIO · SHORT WAVE RADIO**
 - TELEVISION · MECHANICS · CHEMISTRY**
 - PHOTOGRAPHY · ELECTRICITY · CARPENTRY**
 - ELECTRICAL WIRING · DRAUGHTSMANSHIP**
 - ART, ETC.**



**COURSES FROM
15/- PER MONTH**

FILL IN COUPON
FOR
FREE
PROSPECTUS



E.M.I. INSTITUTES, Dept. 138x
LONDON, W.4

NAME _____ AGE _____
 (If under 21) BLOCK CAPS PLEASE

ADDRESS _____
 I am interested in the following subject(s) with/without equipment

DEC./57 (We shall not worry you with personal visits) IC.85

The only Home Study
College run by
a world-wide
Industrial
organisation



E.M.I.
Factories
at Hayes,
England

EMI INSTITUTES

- Part of "His Master's Voice", Marconiphone, etc, etc.

TOP QUALITY FULLY GUARANTEED VALVES BELOW MANUFACTURERS' PRICES

EXPRESS SERVICE !!!

C.O.D. ORDERS RECEIVED BY 3.30 P.M. EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON. ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY

FOR ONLY 6d. EXTRA PER ORDER WE WILL INSURE YOUR VALVES AGAINST DAMAGE IN TRANSIT. ALL UNINSURED PARCELS AT CUSTOMER'S RISK.

0Z4	6/-16AQ5	7/6	6L6G	9/6	12AH8	10/6	33A/158M	CV85	12/6	ECC33	8/6	EZ35	6/6	PCF80	12/6	UBC41	8/6	
1A3	3/-6AT6	8/6	6L7M	8/-	12AT6	10/6	30/-	CV271	10/6	ECC35	8/6	EZ40	8/-	PCF82	12/6	UBF80	9/6	
1A5	6/-6AU6	10/6	6L18	13/-	12AT7	8/6	35/51	CV428	30/-	ECC40	15/-	EZ41	10/6	PCL82	12/6	UBF89	10/6	
1A7	15/-6B4G	6/6	6N7	8/-	12AU7	7/6	35A5	D1	3/-	ECC81	8/6	EZ80	8/6	PCL83	12/6	UCC85	10/6	
1D6	10/6 6B7	10/6	6Q7G	8/6	12AX7	9/-	35L6GT	D2	10/6	ECC82	7/6	EZ81	10/6	PEN40DD	10/6	UCH42	10/6	
1H5	11/-6BB8	4/-	6Q7GT	9/-	12BA6	9/-	35W4	D63	5/-	ECC83	9/-	GZ30	10/6	PEN45	25/-	UCH81	11/6	
1L4	6/6 6BBM	5/-	6R7G	8/6	12BE6	10/-	35Z3	D77	6/6	ECC84	10/-	GZ32	12/6	PEN46	19/6	UCH82	13/6	
1LD5	5/-6BA6	7/6	6S47GT	8/6	12E1	30/-	35Z4GT	DAC32	11/-	ECC85	9/6	GZ34	14/6	PLB1	7/6	UF41	9/-	
1LN5	5/-6BE6	7/6	6S7GT	7/6	12J5GT	4/6	35Z5GT	DAF91	8/-	ECC91	5/6	H30	5/-	PLB2	15/6	UF80	10/6	
1N5	11/-6B6	8/-	6SH7	6/-	12J7GT	10/6	41MTL	DAF96	10/6	ECCF80	12/6	H63	12/6	PLB3	11/6	UF85	10/6	
1R5	8/6 6BR7	11/6	6S17	8/-	12K7GT	7/6	50C5	DF33	11/-	ECCF82	12/6	HABC80		PM2B	12/6	UF89	10/6	
1S5	8/-6BW6	8/6	6SK7GT	6/-	12K8GT	9/6	50L6GT	DF91	7/-	ECH35	9/6			PM12	4/-	UL41	10/6	
1T4	7/-6BW7	9/-	6SL7GT	7/6		14/-	61BT	DF96	10/-	ECH42	10/-			PM12M	6/6	UL46	15/6	
1U5	7/-6BX6	8/6	6SN7GT	8/-	12Q7GT	7/6	61SPT	DH63	8/6	ECH81	8/-	HU23	10/6	PM12M	6/6	UL84	11/6	
2A3	12/6 6C4	7/-	6S57	7/6	12SA7	8/6	72	DH76	7/6	ECL80	10/-	HU41	12/6	PY80	9/-	UY41	8/6	
2A7	10/6 6C5	8/6	6G4GT	14/-	12SC7	7/6	77	DH77	8/6	ECL82	13/6	HU133DD		PY81	9/-	UY85	10/6	
2C26	4/- 6C6	6/6	6U5G	7/6	12SG7	7/6	78	DK32	15/-	EF36	6/-			PY82	9/-	VI507	5/6	
2D13C	7/6 6C8	12/6	6U7	8/6	12SH7	5/6	80	DK91	8/6	EF37A	9/-	HVR2	20/-	PY83	9/6	VLS492A	£3	
2X2	4/6 6C9	12/6	6V6G	7/-	12S17	8/-	83V	DK92	12/6	EF39	6/-	HVR2A	6/-	QP21	7/-	VMP4G	£5	
3A4	7/-6C10	12/6	6V6GT	7/6	12SK7	6/-	85A2	DK96	10/6	EF40	15/-	KL35	8/6	QP25	15/-	VP2(7)	12/6	
3A5	12/6 6C16	7/6	6X4	7/-	12SQ7	8/6	150B2	DL2	15/-	EF41	9/6			QS150/15	15/-	VP4(7)	15/-	
3B7	8/6 6D6	6/6	6X5GT	6/6	12SR7	8/6	807	DL33	9/6	EF42	12/6	KT33C	10/6			VP13C	7/6	
3D6	5/-6E5	12/6	6Z4/84	12/6	12Y4	10/6	866A	DL92	8/-	EF50(A)	7/6	KT44	7/-	QVO47	10/6	VP23	6/6	
3Q4	9/-6F1	15/-	6Z5	12/6	14R7	10/6	956	DL94	9/-	EF50(E)	5/-	KT63	6/6			VP41	7/6	
3Q5GT	9/6 6F4GT	8/-	6/30L2	12/6	14S7	14/-	1203	DL96	10/-	EF54	5/-	KTW61	6/6			VR105/30	9/6	
354	8/-6F8	12/6	7A7	12/6	19AQ5	11/-	4033L	DLS10	10/6	EF73	10/6	KTW62	8/-			VR150/30	9/6	
3V4	9/-6F12	9/-	7B7	8/-	19H1	10/-	5763	DM70	8/6	EF80	8/6	KTW63	8/-	SP41	3/6	VT61A	5/-	
5U4	8/6 6F13	13/-	7C5	8/-	20D1	16/-	7193	EA50	2/-	EF85	7/6	KTZ41	6/-	SP42	12/6	VT501	5/6	
5V4	12/6 6F16	9/6	7C6	8/-	20L1	13/6	7475	EA76	9/6	EF86	14/6	KTZ63	10/6	SP61	3/6	W76	8/6	
5X4	10/-6F17	12/6	7H7	8/-	25L6GT	10/-	9002	EABC80	10/6	EF89	10/6	L63	6/-	TP22	15/-	X61	12/6	
5Y3G	8/-6F32	10/6	7O7	9/-	25Y5	10/6	9003	EAC91	7/6	EF91	9/-	MH4	7/-	U16	12/-	X65	12/6	
5Y3GT	8/6 6F33	7/6	7V7	8/6	25Y5G	9/6	9006	EAF42	10/6	EF92	6/6	MHL4	7/6	U22	8/-	X66	12/6	
5Y4	10/-6G6	6/6	7Y7	8/6	25Z4G	9/6	AC/HL	EB34	2/-	EL32	5/6	MHLD6	12/6	U25	13/6	X79	12/6	
5Z3	12/6 6H6M	3/6	8D2	3/6	25Z5	10/6	AC/HL	EB41	8/6	EL41	11/-	ML6	6/6	U31	9/6	XD(1.5)	4/-	
5Z4G	10/6 6J5G	5/-	8D3	3/6	25Z6G	9/6	AC/P4	EB41	8/6	EL42	11/-	MU14	8/6	U50	8/-	XFW10	6/6	
6A8	10/-6J5GTG	5/6	9D2	3/6	28D7	7/6	AC/P4	EBC33	7/6	EL81	15/-	OA10	12/6	U52	8/6	XY12	6/6	
6A87	8/-6J5GTM	6/-	10C1	15/-	30	7/6	AP4	EBC33	7/6	EL84	10/6	OA70	5/-	U76	8/-	XH(1.5)	4/-	
6A88	9/-6J6	5/6	10F1	11/6	30C1	12/6	ATP4	EBF89	9/6	EL91	5/-	OA71	5/-	U78	7/-	XSG(1.5)	4/-	
6AC7	6/6 6J7G	4/6	10F9	11/6	30F5	12/6	AZ31	EBF89	9/6	EM34	10/6	OC72	30/-	U251	15/-	Y63	7/6	
6AG5	6/6 6J7GT	10/6	10F18	12/6	30FL1	12/6	B329	EC52	5/6	EM80	10/6	P61	3/6	U404	10/6	Z66	10/6	
6AG7	12/6 6K7G	5/-	10LD3	8/6	30LL1	12/6	BL63	EC54	6/-	EY51	12/6	PABC80		UABC80		Z67	20/-	
6AJ8	8/-6K7GT	6/-	10P13	17/6	30P4	15/-	CK505	EC70	12/6	(Small)	12/6			U766	10/6	Z77	9/-	
6AK5	5/-6K8G	8/-	11E3	15/6	30P12	13/6	CK506	ECC31	15/-	EY51		PCC84	8/-	UAF42	10/6	Z719	12/6	
6AL5	6/6 6K8GT	6/6	12A6	6/6	30P16	10/6	CK523	ECC32	10/6	(Large)	12/6	PCC85	12/6	UB41	12/7	Z729	14/6	
6AM6	9/-	11/-	12AH7	8/-	31	7/6	CV63											

TERMS OF BUSINESS :-CASH WITH ORDER OR C.O.D. ONLY. ORDERS VALUE £3 OR MORE SENT POST/PACKING FREE. ORDERS BELOW £3 PLEASE ADD 6d PER VALVE C.O.D. ORDERS :-MINIMUM FEE, INCLUDING POST AND PACKING, 3/-. WE ARE OPEN FOR PERSONAL SHOPPERS. MON.-FRI. 8.30-5.30. SATS. 8.30-1 p.m.

ALL VALVES NEW, BOXED, TAX PAID, AND SUBJECT TO MAKERS' GUARANTEE. FIRST GRADE GOODS ONLY, NO SECONDS OR REJECTS. GOODS ARE ONLY SOLD SUBJECT TO OUR TERMS OF BUSINESS. OBTAINABLE FREE ON REQUEST. CATALOGUE OF OVER 1,000 DIFFERENT VALVES 3d.

We specialise in VALVES—of every kind and description—serving the industry for years. More than 2,000 different types in stock for IMMEDIATE DELIVERY—including hard-to-get and discontinued numbers. All valves exhaustively tested in our fully equipped laboratories, and re-tested at time of despatch. FULL NINETY DAY GUARANTEE. All valves individually boxed.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS

38 CHALCOT ROAD, LONDON, N.W.1

PRimrose 9090

PLEASE ENQUIRE FOR ANY VALVE NOT LISTED. 3d. STAMP, PLEASE.

PREMIER RADIO CO.

OPEN TILL
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.
(Dept. P.T.12) 207, EDGWARE ROAD, LONDON, W.2


Telephone:
AMBASSADOR 4033
PADDDINGTON 3271

Build the NEW "MAYFAIR" TELEVISOR which gives complete SAFETY to the constructor!

These Televisors use a double wound mains transformer which gives you complete safety from contact with the mains supply when handling the chassis or controls.

★ **B.B.C. & I.T.A. DESIGN** With New Turret Tuner may be built for **£33.7.11** plus cost of C.R.T.

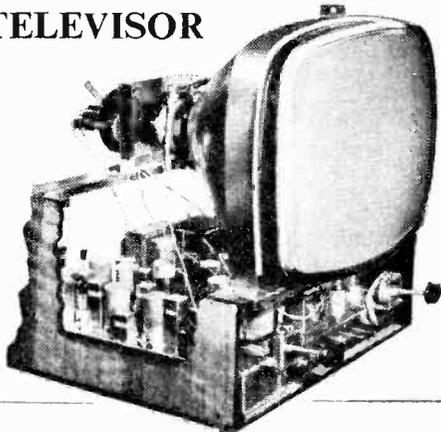Build in 5 easy stages. Full Construction details available. Instruction Book, 3/5 Post Free.
Console Cabinets with full length doors for 14in., 16in., and 17in. tubes. Price £14.14.0.
H.P. Terms: Deposit £7.6 and 9 monthly payments of 18/6. Console Cabinets. Half door £12.12.0.
H.P. Terms: Deposit £6.5.0 and 8 monthly payments of 18/3. On above cabinets add 21/- for pkg. and carr.



The "Petite" PORTABLE

MAY BE BUILT FOR **£7.7.0**
plus 3/- post & packing.



- ★ Size only 8in. x 8in. x 4 1/2in.
- ★ Weight, including batteries, 5 1/2 lb.
- ★ 4 valves of the economy type.
- ★ Medium and longwave superhet circuit.
- ★ High Q frame aerials.
- ★ High sensitivity on both wavebands.
- ★ Prealigned IF transformers.
- ★ 5in. speaker of the latest type.
- ★ Automatic on/off switch operated by lid.
- ★ Designed in our own laboratory.
- ★ Backed by an up-to-date Technical Information Department.
- ★ Components available separately if desired.
- ★ Simple to construct, using normal soldering methods.
- ★ Instruction Book 1/6.

Batteries extra.

HT 10/- (Type B126) or equivalent.
LT 1/6 (Type AD 35) or equivalent.

Battery eliminator now available for 37/5.

B.S.R. TU8

3 speed record player
£3.19.6.

plus 2/6 postage & packing.

8-WATT AMPLIFIER

This design includes 5 miniature Valves of the latest types, an Ultralinear Output Transformer suitable for Speakers of 3 and 15 ohms and a very attractive Perspex front panel with gold lettering, complete set of parts, **£8.8.0.**
Postage & Packing, 5/- extra.
Instruction Book 1/6.

WHY buy surplus or reconditioned tubes when these Fully Guaranteed Wide Angle Tubes are available? The latest type 17in. Rectangular Tube MW43/64 by Telefunken at £17 (inc. tax) post and packing 21/- extra. Also 14in. Rectangular Tube type 14 LPA £13.17.6 (inc. tax) pkg. & carr. 15/- extra.

The New De-Luxe

TAPE RECORDER TR 3

for
£6.5.0

DEPOSIT &
8 MONTHLY
PAYMENTS
OF £5.17.11

OR CASH 45 GNS.
plus 21/- post & pkg.




Write for details of the New PREMIER TAPE RECORDER KIT for £38.15.0.

Case finished in Red and Cream with gilt styling and fittings. Size 18 1/2 in. x 15 in. x 9 in. for A.C. Mains 200/250 v. 50 cycles. **TRADE ENQUIRIES WELCOMED**

NEW F.M. TUNER

for the Home
Constructor

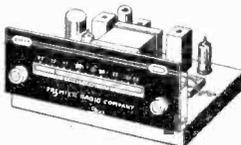


A new design using the latest circuit techniques. Includes 4 valves plus magic eye tuning indicator, permeability tuning and an integral power supply. Two controls only, a gear driven slow motion tuning control and an output volume control with on/off switch. Suitable for fringe area reception.

All components may be purchased for **£8.15.0**, plus postage and packing 3/6.
OR less Mains Transformer & Rectifier £7.12.5, plus postage and packing 3/-.
Power requirements H.T. 230 v. 50 mA., L.T. 6.3 v. 1.5 A. Dial size 3 1/2 in. x 1 1/2 in., overall size 1 1/2 in. long, 5 1/2 in. deep, 4 1/2 in. high. Instruction Book 1/6.

BRIMAR 6BQ7A

The Brimar 6BQ7A is a double triode consisting of two independent high slope sections with similar characteristics. The valve is particularly useful as a cascode R.F. amplifier for television receivers and also as a combined oscillator and mixer for frequency modulation receivers. It can, of course, be used wherever high slope triodes are required, and features low interaction between the sections as an internal screen is provided which is brought out to a separate base pin.

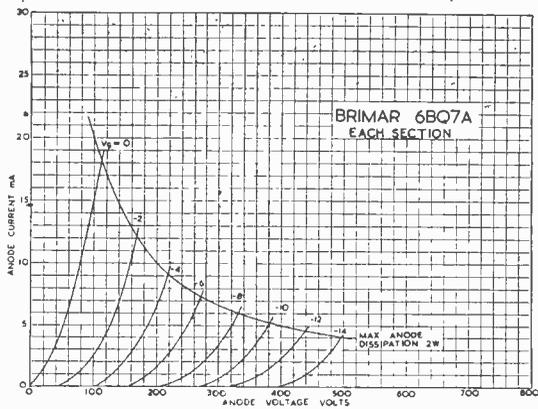


TYPICAL CHARACTERISTICS

Heater voltage.....	6.3 volts
Heater current.....	0.4 amp
Anode voltage.....	150 volts
Cathode bias resistor.....	220 ohms
Anode current.....	9 mA
Mutual conductance.....	6.4 mA/V
Amplification factor.....	39
Anode resistance.....	6,100 ohms
Grid cut-off voltage ($I_a=10\mu A$).....	—10 volts approx.

Write to the Publicity Department for a data sheet.

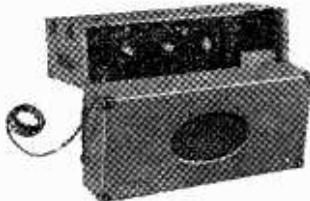Standard Telephones and Cables Limited **FOOTSCRAY SIDCUP KENT** Footscray 3333



GUITAR AMPLIFIER !

5-6 watts output. For use on A.C. Mains 200-250 v. Complete with 4 valves, speaker, all controls, neon level indicator, gram and mike inputs. Speaker in lid, but movable to any position by using lead supplied. In smart case with carrying handle, size closed 8½ in. x 8½ in. x 19 in. long. Brand new and unused.

LASKY'S PRICE, absolutely complete **£10.19.6** Carr. & Pkg. 5/-

Available as Amplifier without Case and Speaker, **£6.19.6**. Carr. & Pkg. 5/-.

NOTE: Can also be used as tape-recording amplifier (pre-amplifier and erase).

TURRET TUNERS. All types in stock—Valradio, Cyldon, Telente, etc. Write us make and model of your Set: we will quote for the Tuner you need. Prices from 79/6.

BAND III CONVERTERS with own power supplies in attractive Cases. Leading makes from **£5.19.6**.

17in. C.R. TUBES. Few only. Brand new and unused. Rectangular, aluminised or ion trap, 0.3 heater.



LASKY'S PRICE
£12.19.6
Carr. & Ins. 22/6.



COLLARO 4-SPEED AUTO-CHANGER

Mixer Model RC.456, with Studio crystal pick-up. List **£13/17/0**

LASKY'S PRICE, **£8/19/6** Post 3/6.

MAKER'S SURPLUS COMPONENT BARGAINS

WIDE ANGLE 38 mm.

- Line E.H.T. trans. Ferro-cube core, 8-16 kV..... 25/-
- Scanning Coils, low imp. line and frame..... 25/-
- Ferro-cube cored Scanning Coils and Line Output Trans. 10-15 kV. EY51 winding Line Trans. Complete with circuit diagram, the pair..... 50/-
- Frame Output Transformer Scanning Coils low imp. line and frame..... 6/6
- Frame or line block osc. transformer..... 17/6
- Focus Magnets Ferro-dure P.M. Focus Magnets, Iron Cored..... 19/6
- Duomag Focalisers..... 22/6
- 300 mA Smoothing Chokes... 15/-
- Electromagnetic focus coil, with combined scan coils... 25/-

STANDARD 35 mm.


- Line Output Transformers, No E.H.T..... 12/6
- Line Output Transformers, 6.9 kV. E.H.T. and 6.3 v. winding. Ferro-cube..... 19/6
- Scanning coils, Low imp. line, and frame..... 12/6
- Ditto by Igranic..... 14/9
- Frame or line blocking oscillator transformer..... 4/6
- Frame output transformer... 7/6
- Focus Magnets Without Vernier..... 12/6
- With Vernier..... 17/6
- Focus coils, Electromag..... 12/6
- 200 mA Smoothing Chokes... 10/6

LASKY'S (HARROW ROAD) LTD.

Open All Day Saturday. Early Closing Thurs. Mail Orders to Harrow Rd. 42, TOTTENHAM COURT ROAD, W.1. 370, HARROW ROAD, PADDINGTON, W.9. Telephone: MUSeum 2605. LADbroke 4075 and CUNningham 1979.



Practical Television

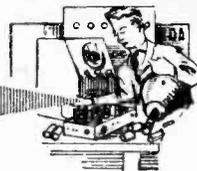

& TELEVISION TIMES

Editor : F. J. CAMM

Vol. 8 No. 89

EVERY MONTH

DECEMBER, 1957

TELEVISIONS

AUDIENCE RESEARCH

THE BBC has admitted that its viewing audience is much less than I.T.V. It says that of the possible viewing public, 28 per cent. look in to the BBC programmes and 72 per cent. to I.T.V. The systems adopted by TAM and the BBC in order to arrive at these figures are very dissimilar, yet they seem to give somewhat comparable results. Under one such system, a gadget attached to the set affords them a means of measuring the time spent looking at I.T.V. or BBC and must give a reasonably accurate result. The BBC, however, depend upon interviewing what is considered to be a cross-section of the public. The director of BBC television, Mr. Gerald Beadle, in a later statement, said that on the question of programme ratings and preferences, the BBC's average audience in TV areas is greater than that of I.T.V. He was possibly taking account here of the number of unconverted sets.

COLOUR TV TRANSMISSIONS

THE BBC started a further series of experimental colour transmissions on October 7th, as a continuation of the experiments for studying the problems of producing, transmitting and receiving TV pictures in colour.

The first experimental transmission was in October 1955. They are being made in co-operation with the radio industry, and in agreement with the Television Advisory Committee, which is to report to the Postmaster General on the whole field of colour television. The experiments do not mean that the BBC is committed to the adoption of the system used in the experiments or of any other system of colour television. The decision rests with the Postmaster General. The experiments take place outside normal programme times and will continue for about six months, and are transmitted from the Crystal Palace station on Channel 1 (vision 45 mc/s, sound 41.5 mc/s).

BBC TV COMES OF AGE.

AT 3.30 p.m. on the afternoon on Monday, November 2nd, 1936, the first regular TV programme of the BBC went on the air. Thus, this year, it celebrates its 21st birthday.

We join with the Radio Industry in wishing it many happy returns of the day.

" PRACTICAL HOME MONEY MAKER "

THE third issue of our new companion "practical"—" PRACTICAL HOME MONEY MAKER"—is now on sale, and it bristles with money-making ideas for the home worker. Our new companion monthly is performing work of national importance, and I hope you will join its ranks.—F.J.C.

Our next issue dated January will be published on December 20th.

Editorial and Advertisement Offices :

PRACTICAL TELEVISION

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1957.

Phone : Temple Bar 4363.

Telegrams : Newnes, Rand, London.

Registered at the G.P.O. for transmission
by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - 19s. per annum

Abroad - - 17s. 6d. per annum

Canada - - - 16s. per annum

CONTENTS :

	Page
Editorial	201
A Switched TV/F.M. Receiver An Improved Band III Converter	202
BBC U.H.F. Transmissions	207
Simplified Sound TV Receivers	210
Scanning and Synchronisation	211
Flywheel Sync. and A.G.C.	213
C.R.T. Tester	215
Simplified TV Servicing	221
Telenews	225
Underneath the Dipole	229
Correspondence	233
Your Problems Solved	237

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

A SWITCHED TV/F.M. RECEIVER

A COMBINED TV AND BAND II SOUND RECEIVER

By R. Shatwell

(Continued from page 173 November issue)

THE tuner is the heart of the set and provides the F.M./A.M. switching of the detector as well as the station selection. Fig. 1 in last month's issue gives the theoretical circuit of the tuner and to cut down variations to a minimum a point to point drawing of the top plate with the precise location of every item is given in Fig. 4b. The work involved should be done in the following order:—

1. Make up the top plate (Fig. 4a), front panel (Fig. 5a) and two partitions (Fig. 5b).

2. Modify switch plates to take coil platforms (Fig. 6a).

3. Make up coil platforms (Fig. 7).

4. Assemble switch wafers, platforms, front panel and partitions (Fig. 7).


5. Make and fit fine tuner.

6. Wire top plate, check no shorts when in position on switch assembly.

7. Insert Band I and II coils, wire to switch plates, bolt to top plate and complete wiring between the two.

The first stage is amply covered by the diagrams. The top plate is 18 s.w.g. aluminium. The partitions can be 18 or 20 s.w.g. Note that only one partition needs the cut-out to avoid components, and this will also need coil platform supporting holes drilling at a later stage. The other partition has a hole for the bias lead to the signal balancing switch plate.


Fig. 6A shows the modifications to the switch

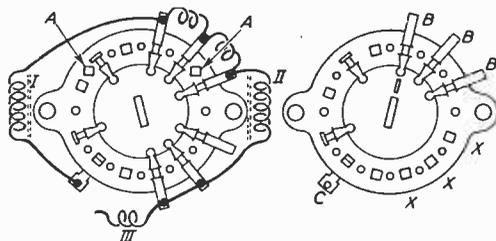

(a) Tuner Wafer
Modified for platforms
and coil connections.
A...Holes enlarged to
take coil platforms

(b) Tube Heater Wafer
X...Contacts removed
B...Contacts linked and
to Tube heater tag
strip.
C...Tube heater supply

Fig. 6(a), (b) and (c). Details of the switch wafer modifications.

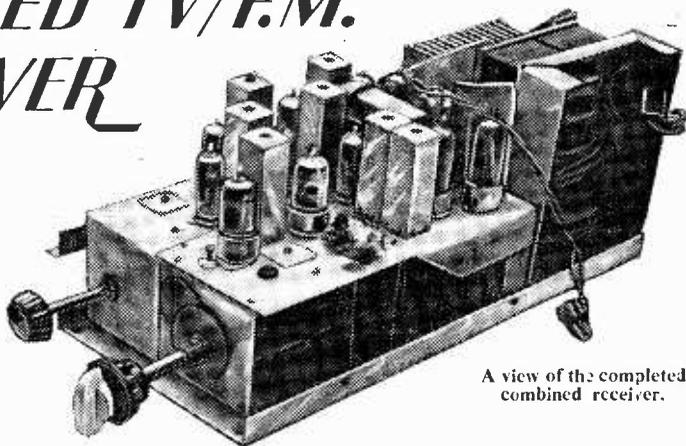

A view of the completed combined receiver.

plates necessary to accommodate the coil platforms, the existing small hole at "A" being enlarged to 1/16in. square in an upward direction on plate 1, downward on plate 3, symmetrically on plate 4, and also on plate 2, but in this case to 1/16in. \times 1/4in. to accommodate two platforms. This latter operation calls for careful work and a fretsaw was used by the author.

The coil platforms can be made up from the details on Fig. 7. The supporting lugs are 1/16in. wide and 1/4in. long. Again a fretsaw is a useful aid. The centres of the coil-former holes must be not less than 1/4in. from the centre, to avoid the switch actuating bar touching the coils. One 8 BA bolt on the outer hole secures the coil formers, as these are inserted through a 1/4in. hole in the platforms. It is therefore a simple matter to remove any coil for modification even in the completed set.

Assembly of the switch is the main work involved. Fig 6a gives the wafer layout, and it will be seen that there are two fixed contacts without soldering tabs and these do not normally take any part in the switching. These are made use of in the modified switch wafer 9. Although nine wafers are used ten are necessary, as an extra contact must be inserted in this modified wafer. The tuner incorporates seven of the nine, and although switch specialists will no doubt make up the assembly to order, it can be made up for a few shillings from two surplus switches as sold by Messrs. W. A. Benson, 136, Rathbone Road, Liverpool. This firm sell a 1P 6W 5B switch at a very low price, and if two are obtained then the ten wafers are obtained, also the copper foil links, and by careful use of the


(c) Video and Time Base Heater Wafer

X...Contacts removed
D Contact inserted
D and E contacts all linked and to tag strip.
G...Moving contacts.
Existing one repositioned and extra one inserted.
F...6.3v. supply

spacers very little modification to these is necessary. The only difficulty is the short spindle, as the fine tuner prevents the use of an ordinary extension coupler. The author used this switch and pinned and soldered a $\frac{3}{16}$ in. extension to the spindle (Fig. 8). A precise horizontal joint can be obtained by lying the pinned joint in a piece of angle aluminium when soldering with a gas or small blow lamp jet. A steel shaft is used on the switch and either spirit flux or the special cored solder will be necessary. After the joint is cleaned up it should be protected with a sleeve of $\frac{1}{4}$ in. ID tube until the fine tuner is fitted.

Fig. 7 gives the spacer lengths, the critical dimensions being the position of the partitions, and it is essential that these be checked. The wafers face to the rear and the moving contact lug is at the top for wafers 1 to 6, and bottom

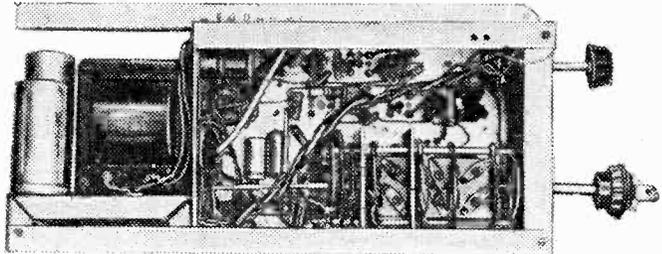for wafer 7, where the L.F. signal is taken off. The front panel is secured only by the switch fixing nut and the top plate. At least $\frac{1}{4}$ in. of the actuating rod must protrude beyond wafer 7, for ganging purposes. The copper foil links bridge the wafers and ensure the effective electrical return of the



This view shows the switch assembly

distance pieces to the chassis. The assembly should then be positioned on the top plate and the 8 B.A. holes drilled through from the top plate into the front panel and partition flanges.

The fine tuner fixed plate should now be fitted. This is made up on a $1\frac{1}{4}$ in. paxolin disc with a countersunk hole at the centre. This hole should be made by using a $\frac{1}{4}$ in. drill to make a countersink, but completing the breakthrough with a pin, and it coincides with the $\frac{1}{4}$ in. dia. centre of the elongated hole in the front panel. Another $1/16$ in. dia. hole is made to coincide with the $5/16$ in. dia. centre. A piece of tinned 36 s.w.g. wire is threaded through one and back

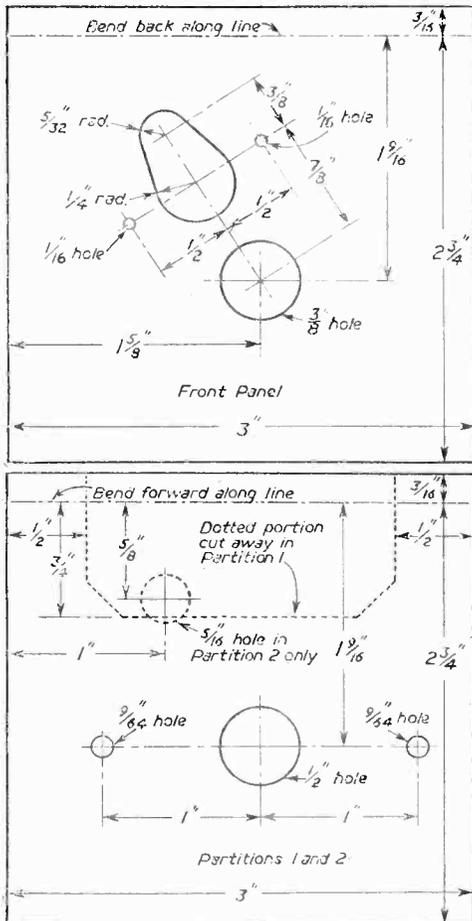


Fig. 5(a) (above), details of the panel, and 5(b) (below), the partitions, two of which are needed.


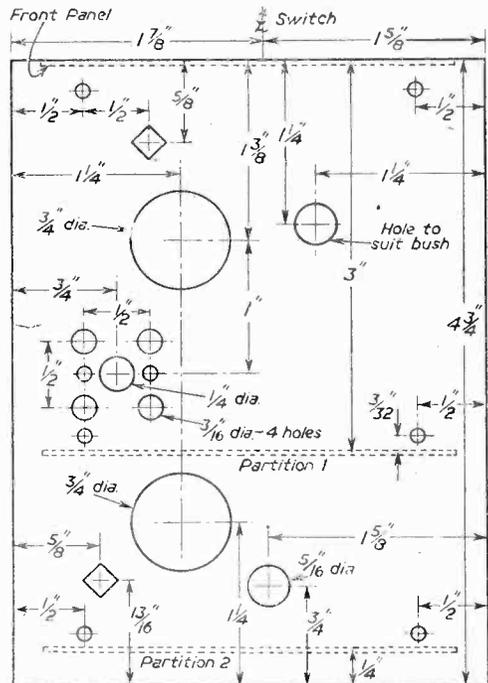


Fig. 4(a).—The top plate drilling data.

through the other and twisted and soldered behind, being left 2 in. long. The countersink on the front is filled with solder until a raised

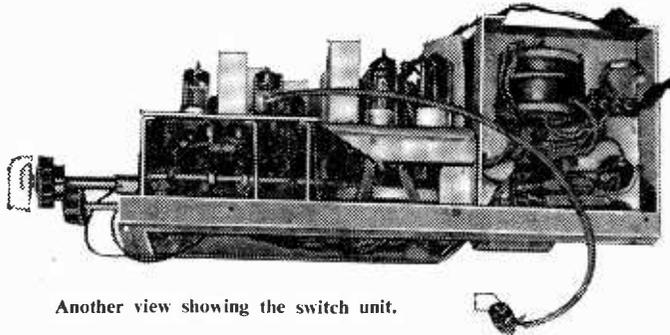and to avoid failures at a later date $\frac{1}{4}$ w. are specified wherever anything higher than bias volts are involved. Leave about $\frac{1}{4}$ in. of wire protruding



Another view showing the switch unit.

$\frac{1}{4}$ in. dia. blob adheres to the wire (Fig. 9b). This is filed to a flat raised disc, and the paxolin then secured to the front panel by two 8 B.A. bolts, a strip of springy brass $\frac{3}{16}$ in. wide being held by one of these bolts to press against the moving plate.

The moving plate is shown in Fig. 9a. Its capacity change is obtained by the cam shape augmented slightly by its closing air gap. Maximum capacity should be obtained in about 270° rotation when the threads of the bush and nut butt tightly. The tab on the outer edge is bent down to form a stop in the minimum capacity position. The plate is of 22 s.w.g. copper, soldered to a nut to suit the switch thread, and this to an inch of $\frac{3}{8}$ in. I.D. copper tube into the end of which is soldered a length of $\frac{1}{4}$ in. I.D. tube to form the fine tuner shaft, the inner shaft to protrude $\frac{3}{8}$ in. beyond this. This soldering operation is best done by tinning all surfaces and then completing the whole jointing in one operation with a small jet. Check that the moving and fixed plates cannot short at any position but arrange them to be as close as possible.

Components

The top plate can now be wired and a small type iron is essential for this. Use of the heavier type $\frac{1}{4}$ in. bit will almost certainly damage some components. Ceramic tubular condensers are used throughout and in no case is there more than $\frac{1}{4}$ in. of wire from the condenser to its fixing point and a pair of pointed-nosed pliers should be used as a "heat shunt." All resistances are $\frac{1}{4}$ watt unless otherwise specified,

and to avoid failures at a later date $\frac{1}{4}$ w. are specified wherever anything higher than bias volts are involved. Leave about $\frac{1}{4}$ in. of wire protruding at all points requiring connection to Band III coils or switch points. The test point is for lining up the I.F.s. Leave the aerial input transformer connections long on the top side of the plate. Wire to the theoretical diagram only, using Fig. 4b as a guide to location of components.

This completed and checked try the switch assembly in position and ensure there are no shorts between components and this assembly. If not, the Band I and II coils can be inserted and

wired to the switch. On wafers 1, 2, 3 and 4 the soldering lugs are cut off the fixed contact points, and connections are made to the contacts at the level of the paxoline. Links are made at the back of the wafers, and damping resistors.

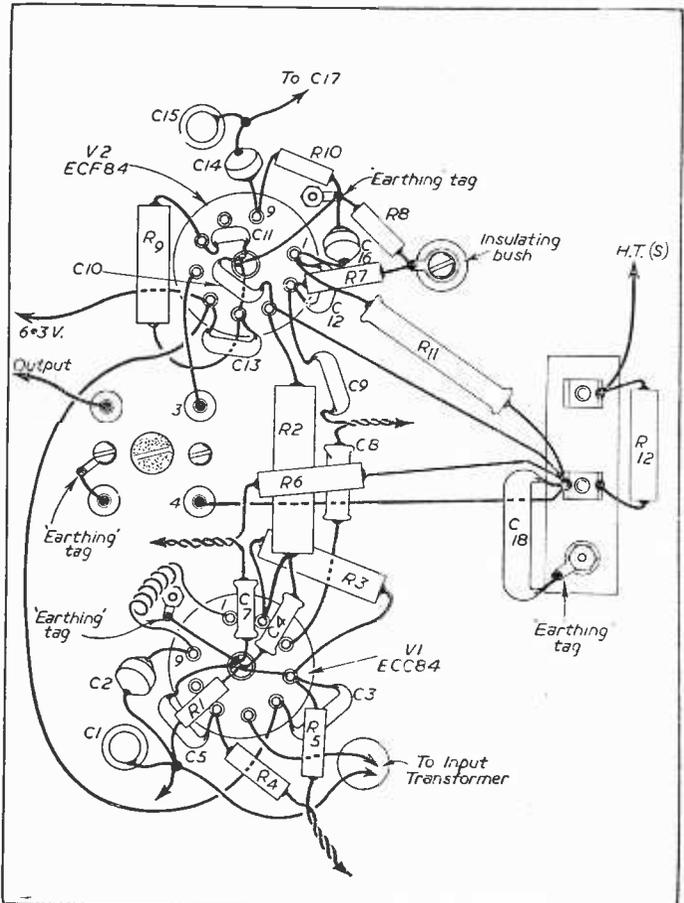


Fig. 4(b).—Wiring diagram of the tuner.

if used, can likewise be accommodated here. The Band III coil L13 does not go to any anchor point on the top plate and can be inserted at this stage the free end passing through the small hole alongside the contact, and tinned ready for C8

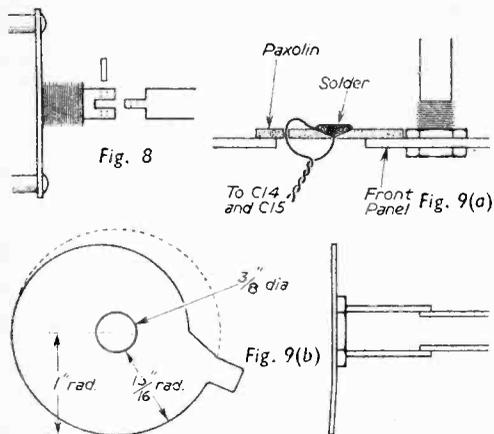


Fig. 8 (above).—Modification to the fine tuner spindle. Fig. 9(a) and (b).—Further fine tuner details.

and 9 to be connected. Note that no connection is made to the Band I position, as this coincides with all coils being in circuit. Fig. 6a shows the coil connections to the wafers. The top plate and switch assembly can now be bolted together and the necessary links made and Band III coils inserted. Those links consist of fine tuner to wafer 1 and C14, 15; L19 from wafer 1 to V2, pin 2; wafer 2 to V2 chassis return; C8, C9 to L13 as prepared; R6, C7 to wafer 3; L7 from

wafer 3 to V1, pin 3; R4, R5 to wafer 5; C1, R1, C2 to wafer 4; L1 from wafer 4 to V1, pin 6. Fit the aerial transformer on the top plate near the grommet hole, with a two-way tag strip nearby and connect to prepared leads and wire C19, C20 to tag strip and T1. Connect a convenient length of 70-80 ohm coaxial suitably terminated for aerial plug used. Wafer 5 can have all fixed contacts taken to chassis at this stage. Wafers 6 and 7 have the three TV positions linked and the three F.M. positions also linked. This completes work on the tuner.

Coil Data

Coil data is given in sets for each coil position as being more convenient to use. At this stage the oscillator F.M. positions, 3, 4, 5 and 6 (wafer 1) can be linked at the back with a short piece of 28 s.w.g. The interval coupling transformers are best made up by anchoring two lengths of 39 s.w.g. to the fixing holes in the Aladdin formers and then laying the wires up opposite sides of the former and taking two or three turns of thread tightly around the former at the start of the winding and tying securely. After winding bifilar fashion finish each wire on the same side as it began and another two or three turns of thread will anchor these. If necessary move the

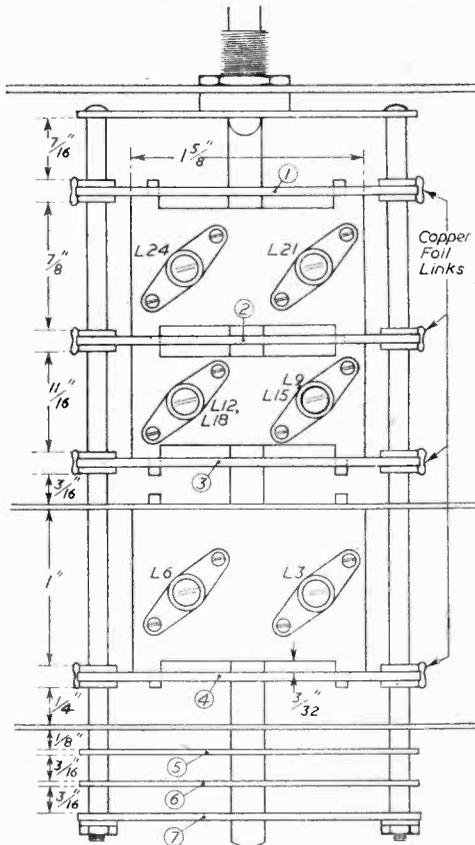


Fig. 7.—Details of the main switching assembly.

TUNER COILS BAND III

	Position 1	Position 2	
L1	4T	Link	All coils clean 18 s.w.g. wound on .2in. former, removed and opened slightly.
L7	5 1/2 T	"	
L13	4T	"	
L19	3T	"	

BAND II

	Position 4		
L3	7T	20 s.w.g. enam.	Aladdin former.
L9	5T	39 DSC bifilar wound-spaced to fill .5 inch	
L15	5T		
L21	3T	20 s.w.g. enam.	

Position 5 and 6—2T throughout, wound as Band III coils. See text for oscillator links.

BAND I

Channel		
Position 1 & 2	Position 3, 4, & 5	
L6	7T	32 s.w.g. Closewound.
L12	8T	Bifilar wound, spaced to fill 6 in.—39 D.S.C.
L18	8T	
L24	4T	32 D.S.C.—to all in.

Aerial input transformer—20T 32 D.S.C. PRI. 1 1/2 T sec. interwound earthy end.


L25 8 turns 22 s.w.g. enam. 1/4 in. diam.

wires to even out the spacing and take a strip of Sellotape completely around the former to protect the winding. Free the wire from the fixing holes and the coil is complete.

Main Chassis

The main chassis can now be made up. This is 9in. X 6in. X 2½in. deep. This may be made up from a sheet of 18 s.w.g. aluminium. Next month we will show details of the wiring and chassis data.

(To be continued)

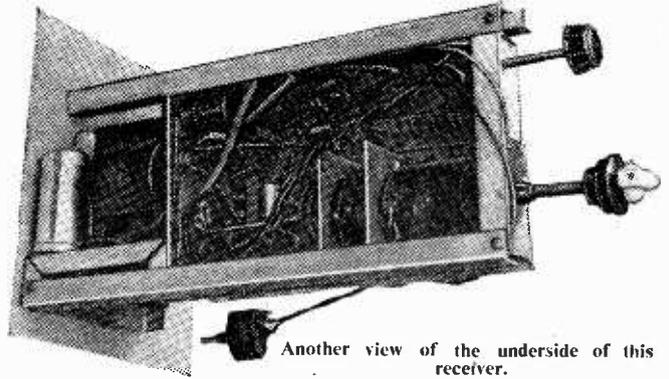


I.F. COIL DATA							
		Pin No.	Turns	S.w.g.	End of winding T=Top B=Bottom	Wire spacing	Other data
T2	A	3	9	28 DSC	T	Close wound	Sec. on PRI. Tissue interleave.
	HT	4			B		
	E	6	B				
	G	1	T				
T3	A	4	11	"	T		
	HT	3			B		
	E	6	B				
	G	1	T				
T7	A	4	16	"	T	"	1½in. between coils.
	HT	3			B		
	E	2 Junction of C47-48		B			
	G	1	15	B			
	Rejector	6		T			
L26		13½ Centre tapped		28 DSC			Aladdin former.
T8	A	4	15	38 EW	T	To cover .45in.	Bifilar wound
	HT	3			B		
	Diode	6	B				
	E	1	T				
T4	A	4	13½	28DSC	T	Close Wound	¾in. between windings.
	HT	3			B		
	E	6	13½	T			
	G	1	"	B			
T5	A	4	13½	28 DSC	T	"	"
	HT	6			B		
	E	1	13½	T			
	Diode	3	"	B			
T6	A	4	9	39 DSC	B	To cover .375in. .5in. Close	3/16in. between windings. Interwound 1 turn with top of primary.
	HT	6			T		
	HT	1	7+7	B			
	HT	3		T			
	Tert	2	3	T			
	All coils wound in same sense.				"		
L27			108	38 enam.		Close	Formers 1½in. long, ½in. dia. paper tube. Start winding ¼in. from top of former. Winding length ½in.
L28			108	"		"	Former 1½in. x ½in. dia. paper tube. Start winding 3/16in. from top. Winding length 13/16in.
L29			200	40 enam.		"	

An Improved BAND III Converter

This Article is Written to Help Readers Who are Having Difficulty in Obtaining Satisfactory Reception on Band III with EF50 and EF80 Valves

By "Diadem"

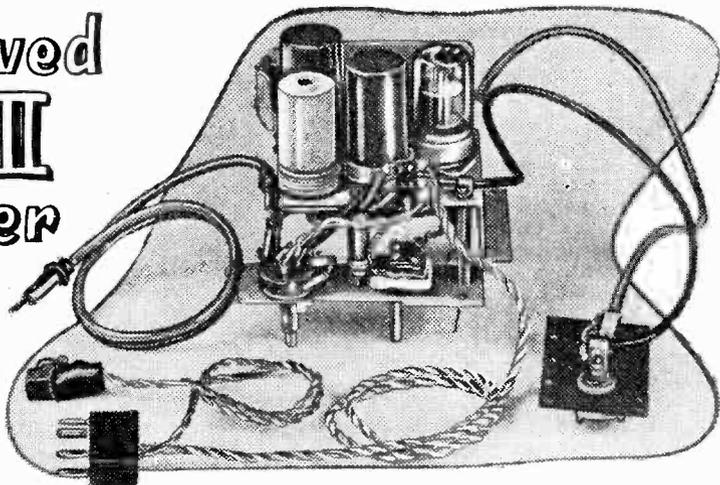


(Continued from page 154, November issue)

THE converted output is taken from the I.F. transformer secondary in the anode of V2, and after switching is fed into the receiver.

The 330pF decoupling condensers were found to be adequate. Larger ones up to 1,000pF were tried and can be used without affecting performance. All other condenser and resistor values must remain as stated. Nothing is to be gained by altering these, many combinations of resistors and condensers were tried and those given were found to be the best. "Red" Sylvania EF50s were found to be much better than the "silver" type and more stable, and gave better contact, especially the spigot which is of different metal and does not oxidise so rapidly.

Valveholder Troubles

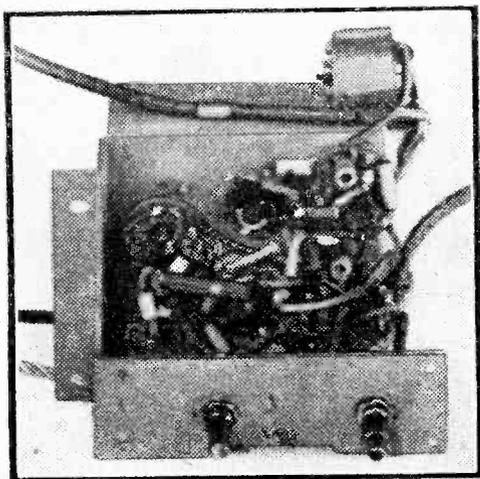Ceramic valveholders were used for low loss. The sockets are silvered and turn black. Some of this can be removed with carbon tetrachloride, and a flat nail file very lightly passed up and



View of the underside of the unit.

down the sockets a few times removes the rest. Do not forget the centre spigot hole, and pinch the spigot contacts together. Clean all valve pins the same way and make sure the aluminium ring on the valve base which holds the spigot is making good contact with the valve can, as both these parts film over with age.

Use spring type ring retainers. The worst type of retainer is the two coiled spring type with the disc on top, although the spigot is "earthed" the top of the valve can is earthed through the disc and the two expanding springs. The disc and the top of the valve can are usually filmed over, the springs make bad contact at both ends and at V.H. frequencies it plays havoc with stability, especially in the first stage where it upsets alignment of I.2. and the gain drops considerably. I hope this explanation will save much hair tearing by the constructor.

At the start all the stages were screened from one another and screens were also placed across the valveholders. All this screening was removed piece by piece and now only coils L1 and L4 are "canned," with no ill effect on performance.

The valveholder bolts are longer than usual and through this bolt on top of the chassis passes the valve retainer ring, the valveholder collar. Then comes the chassis, and underneath the solder tag, nut, Aladdin coil former, washer and nut. This enables the coils to be as near as possible to the valves. On coils L2, L3, L5, only one bolt was sufficient when the thick wire was soldered in place. No holes were drilled through the chassis for the cores as these were not found to be necessary. Coils L1, L4 were held by two bolts each and screened to prevent BBC pick-up.

The formers are $\frac{1}{4}$ in. Aladdin with purple cores. When the converter is working satisfactorily the cores can be removed and a thin piece of elastic inserted down the inside of the former and the cores put back. This is necessary, especially if cores L2, L5 rock about.

Wind the coils on $\frac{1}{4}$ in. control spindle and press on formers: as the formers are slightly over $\frac{1}{4}$ in. the coil makes a tight fit.

The heater chokes are wound on a fat knitting

needle (plastic); this needle is also used for trimming purposes when filed to a screwdriver tip.
 In weak signal areas increase R9 across L4 to 6 K Ω or cut out altogether. It should be left in wherever possible.

Patterning

BBC and I.T.A. co-ax cables running side by side from the aerials have not been found to be the cause of patterning on the I.T.A. unless the cables have been cut or joined or extended. If the BBC cable is cut or extended use a proper cable joiner, not tape, as the cable inner must be screened. The Band I co-ax must always be shorted out when receiving the I.T.A., or pronounced patterning will result. Switching the inner co-ax out of circuit or removing the plug is not effective.

Keep the output leads from the converter away from A.C. wiring in the power pack and mains wiring.

The filter coil L1 will overcome patterning from the BBC being fed into the unit. If patterning is experienced on the BBC fit switch in H.T. lead from the converter power supply or in the mains lead. This is usually switched out automatically when the band switch is operated.

Although an ordinary 3-pole 3-way band switch was used without screening no trouble was experienced through patterning if co-ax is used liberally. Connect co-ax screening to nearest possible points on chassis or solder them to the

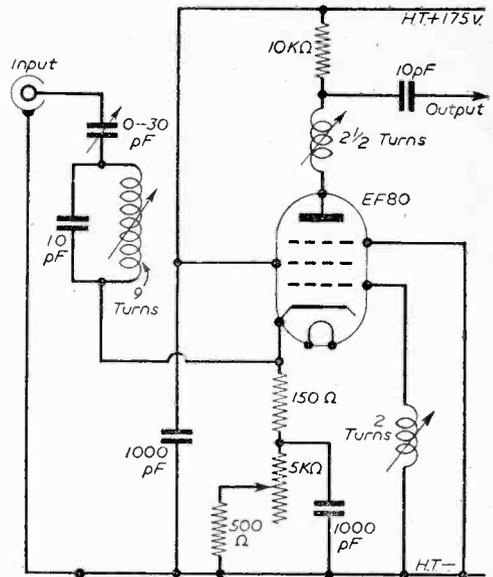


Fig. 7. An alternative circuit.

metal pillars on the switch framework. In the writer's case the converter was fixed inside the front of a console cabinet and the Band I co-ax from the change-over switch was in one continuous length to the back of the cabinet, where it terminated in a Pye socket fixed to a square of paxolin, alongside the

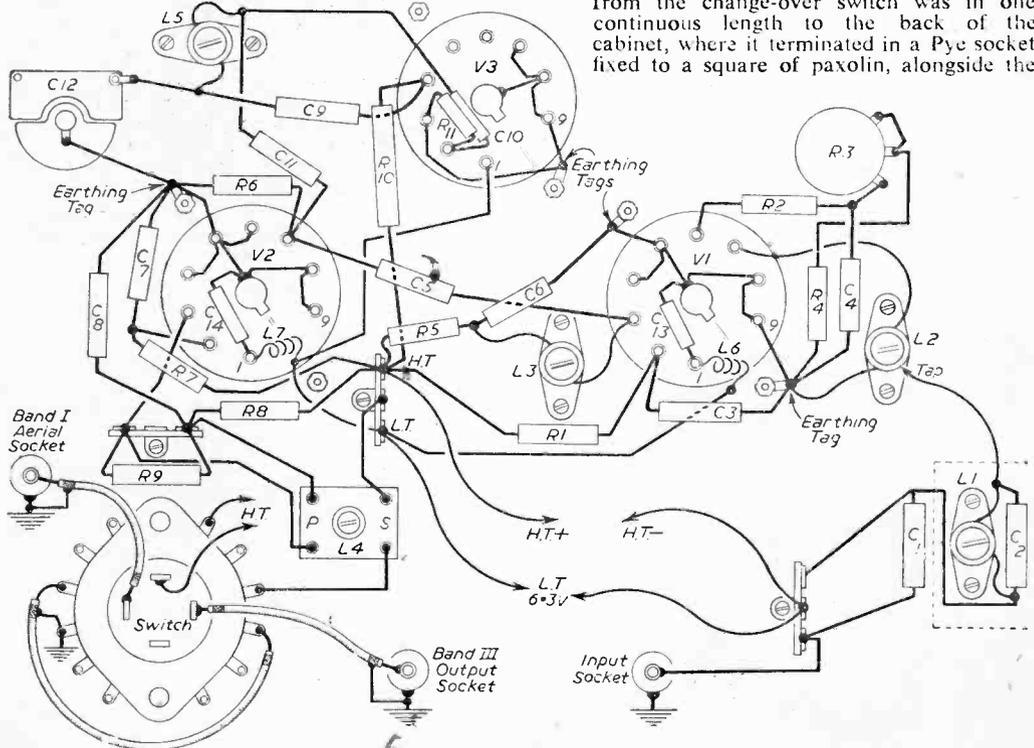


Fig. 8. Wiring diagram of the converter.

I.T.A. socket from which it was screened. This is mentioned because if you are contemplating fixing the Band I socket on the converter chassis, unless the co-ax is taken right up to the

EF80 it works exceptionally well on low voltages (Fig. 5). About 10pF seemed about right for matching in the aerial lead; a postage stamp trimmer was used.

This matching was found to be very important for this valve, as the impedance of the valve is altered and mismatching takes place when the aerial is taken to the cathode. The EF50 requires 1,000pF aerial condenser, or vary to suit individual requirements.

The band change switch contacts were smeared with Vaseline, not oil. This prevents it getting "noisy" after a few months' wear, and an additional refinement which I have found to be worth while to keep the dust out and prevent losses and delay any oxidation is to make a hole $\frac{1}{16}$ in. in the bottom of a small polythene bag, drop the band switch in spindle

COIL DATA

Channel	L1	L2	L3	L4	L5	L6	L7
1	11	2	2 $\frac{1}{2}$	Pri. 11	Sec. 3	5	10
2	10	2	2 $\frac{1}{2}$	10	3	5	10
3	9	2	2 $\frac{1}{2}$	9	2	5	10
4	8	2	2 $\frac{1}{2}$	8	2	5	10
5	7	2	2 $\frac{1}{2}$	7	2	5	10
	Close wound 28 s.w.g. s.c.	Space diam. wire tapped $\frac{1}{2}$ turn earthy end 22 s.w.g. enamel	Space diam. wire 22 s.w.g. enamel	Close wound 28 s.w.g. s.c.	Close wound 28 s.w.g. spaced $\frac{1}{2}$ from primary	Close wound 26 s.w.g. enamel self-supporting	Same as L6

$\frac{1}{16}$ in. Aladdin formers with purple cores.

socket and the socket screened. patterning will be experienced on the I.T.A.


Wiring

Keep it short, wire components right up to the valvholder where possible, especially V1. When "earthing" V1 spigot, solder wire at the bottom of the spigot tag nearest the valvholder, keep R2 off the chassis at least $\frac{1}{16}$ in.

Alignment

Turn down gain control at least quarter of the way and leave alone. Switch on converter, place Band I aerial on grid of V2 mixer and tune L4 for maximum vision. Remove aerial, plug in Band III aerial and set C12 and cores of L1, L2, L3 all midway and L5 on a level with the former top. Tune L5 slowly and rock C12. Vision may be received at two places on L5, but only one where sound and vision is received together, this is the correct one. Tune for maximum sound, tune L2, this may be a little sharper than usual for this position, and if the gain is set too near maximum the removal of this core or the aerial may cause V1 to oscillate with a bright plain raster, and no signal will be received. Keep tuning L2 and L5, and when a signal is received tune L3 for maximum vision. This tunes rather broadly. Now tune L4 for maximum vision, and turn core slightly towards the sound if necessary and increase gain with R3. Now tune L1 if patterning is experienced: this may not seem to have much effect, as it tunes broadly, but it removes BBC patterns. Finally set C12 oscillator trimmer for maximum sound.

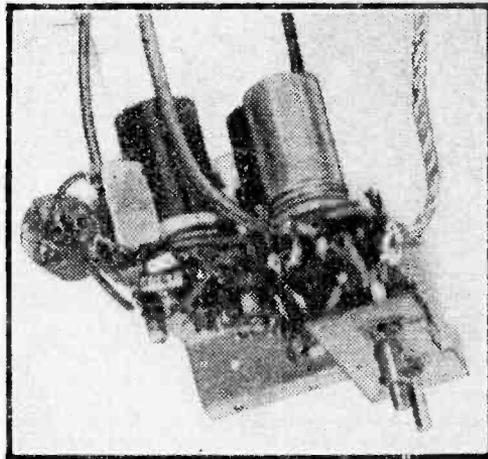The gain control was a 300 Ω W/W midget, as it was to hand, but it can be 500 Ω or up to 1K Ω , but then R4 is omitted, the slider being taken direct to chassis. If a wire-wound control is used Vaseline the track. For those who like to experiment, the circuit in Fig. 2 with EF50 valves, has slightly less gain. L2 tunes rather flatter. Do not omit the condenser in the aerial lead. With the



A view of the complete converter.

first, pull spindle through the hole and fix to chassis in the usual way; bunch the top of the bag together and hold together with Sellotape.

Chassis

Any type of chassis will do provided it is rigid. The chassis used was the two-valve platform from the 3170A unit. The tuner and band switch are under the chassis, built on a smaller platform so as to be near the wiring.

"PRACTICAL TELEVISION CIRCUITS"

288 pages, 156 illustrations

15/- net or 15/6 by post from :

GEO. NEWNES LTD.
Tower House, Southampton Street, Strand, W.C.2

BBC U.H.F. Transmissions

DETAILS OF THE LATEST EXPERIMENTS FOR TV

THIS month, November, the BBC will begin a series of test transmissions on 654.25 Mc/s to collect propagation data relating to the U.H.F. bands (Bands IV and V) which were allocated to television at the International Radio Conference at Atlantic City, 1947, but are not so far used for this purpose.

Following earlier laboratory work, the BBC embarked on its first series of U.H.F. propagation measurements in 1955. These were directed towards the investigation of propagation on frequencies between 470 and 960 Mc/s over distances representing a normal service area, and over longer distances to obtain data necessary for the evaluation of co-channel interference. The initial tests were for the latter purpose and employed transmitters, modulated by square waves, manufactured for the BBC by Mullard Electronic Products Ltd. The transmitters were installed at various television transmitting stations, the aerials being erected high up on the television masts. Regular field-strength measurements were made over long periods at various locations, some as far away as the Shetland Islands. These transmissions are still in progress.

The long-distance tests were followed in 1956 by a series to determine propagation conditions within a typical service area using a transmitter at the Crystal Palace, working into a Yagi aerial and radiating a peak power of 1kW over a fairly narrow beam when modulated with square waves; pulse modulation was also used for some of the tests. The bearing of the aerial, which was at a height of 440ft., was changed from time to time so that field-strengths could be measured over the whole circle from Crystal Palace. These measurements have been completed and the resulting information concerning field-strength contours and an assessment of shadow and echo effects are now being studied.

The information collected in this way was, however, insufficient to determine fully the suitability or otherwise of Bands IV and V for television broadcasting, and at the request of the Television Advisory Committee the BBC decided earlier this year to embark on a more ambitious series of experiments using a high-power transmitter and radiating full television signals, initially on 405 lines and later on 625 lines (C.C.I.R. standards). These tests have been planned by the BBC in co-operation with the committee and the radio industry.

New Equipment

The BBC has installed at the Crystal Palace a 10kW peak-white U.H.F. vision transmitter and a 2½kW carrier power sound transmitter manufactured by E.M.I. Electronics Ltd., the vision frequency being 654.25 Mc/s. The equipment is low-power modulated on both sound and vision channels and employs Eimac 3K5000LF klystrons in both audio and video final stages. These

klystrons use three external cavity resonators and operate as linear amplifiers with a power gain of approximately 100. They are driven by a modulated amplifier stage operating with a cathode modulated circuit. The output of the transmitters is combined in a circuit of the filter bridge type constructed in rectangular section waveguide. The combined output is then conveyed to the aerial by an elliptical waveguide having dimensions of 12in × 6in. The elliptical waveguide is made of 99.5 per cent. aluminium in 12ft. lengths. At the top of the television mast the waveguide is transformed into a 5in. concentric feeder to take power to the four driving points of the helical aerial, the pole supporting the aerial being arranged to form the outer of the concentric feeder.

The helical aerial made of ½in. diameter copper rod comprises four bays, mounted one above the other on the same vertical axis, each having a linear height of five wavelengths. Each bay is fed at the centre, the helix being wound from the centre point of the bay in opposing directions to cancel the vertical component of radiation. In the four bays there is a total of 48 turns, each turn being approximately two wavelengths long. The aerial is mounted at the summit of the Crystal Palace tower, the top of the 6½in. diameter pole supporting the aerial being 707ft. above the ground, while the centre line of the aerial is 691ft. above the ground. The aerial has a power gain of 20 and after allowing for losses in the feeder and waveguide system, the effective radiated power of the vision signal is of the order of 125kW peak-white in the horizontal plane. Provision is made for de-icing the aerial by electrical heating.

When put into use, the transmitter will be in use for several hours a day radiating pictures on the 405-line standard. The pictures will be the same as those radiated by the Band I transmitter installed in the same building. Later on, the pictures on 625 lines will be produced at Lime Grove from flying spot telecine equipment supplied by Cinema-Television Ltd., and sent over a specially equipped coaxial cable to the Crystal Palace.

Change in March, 1958

The tests on 405 lines will continue until about March, 1958, when there will be an interval for the transmitter to be adjusted to radiate on 625 lines. A second series of tests will then begin and will continue for a period not yet decided. For these latter tests, the programme will usually be different from that being radiated by the Band I transmitter, but at certain times duplicate copies of films scanned on the two systems will be radiated by the two transmitters simultaneously.

The BBC, the radio industry, the Post Office, the D.S.I.R., and the I.T.A. are organising comprehensive studies of the received pictures. The receivers themselves will be of various types.

Simplified Sound TV Receivers

PICK UP SOUND ONLY ON THESE SIMPLE CIRCUITS

By F. G. Rayer

A RECEIVER for the reception of the sound signal only can be very easily made, and can prove more useful than might at first be supposed. A fair number of TV programmes, such as orchestral items, are satisfactory without the visual component, and the improved reception is worth while in areas where the usual medium-wave transmitters suffer from interference and where no F.M. receiver is available. Other programmes remain intelligible and interesting with sound only, though naturally a fair number

depend so much on the visual element that they are not satisfactory for listening only. If an amplifier is available, a single valve will suffice in the sound receiver. Such an arrangement (detector followed by two-stage amplifier) has been found to give ample volume at some 40 miles from a transmitter, without any need for a conventional TV type aerial. However, range naturally depends upon local conditions. The popular 954 V.H.F. acorn pentode operates well on these frequencies, and pin connections for it are shown in Fig. 1. The elongated end carries the anode pin. This valve has a 6.3V. 15A. heater, and can be operated from the 6.3V. supply of an amplifier. Maximum anode and S.G. voltages are 250V. and 100V. respectively. A ring holder, with clips, may be used for the

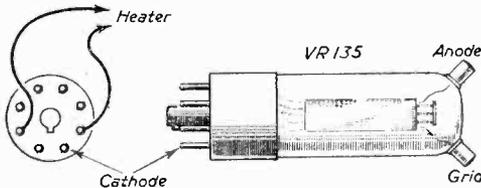


Fig. 2.—Twin cap V.H.F. triode.

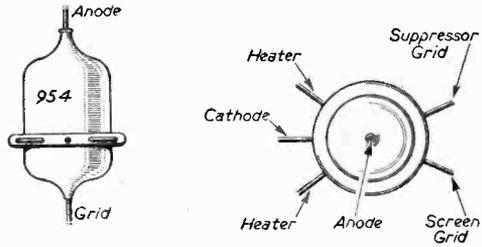


Fig. 1.—Connections for 954 V.H.F. pentode.

depend so much on the visual element that they are not satisfactory for listening only.

If an amplifier is available, a single valve will suffice in the sound receiver. Such an arrangement (detector followed by two-stage amplifier) has been found to give ample volume at some 40 miles from a transmitter, without any need for a conventional TV type aerial. However, range naturally depends upon local conditions.

The popular 954 V.H.F. acorn pentode operates well on these frequencies, and pin connections for it are shown in Fig. 1. The elongated end carries the anode pin. This valve has a 6.3V. 15A. heater, and can be operated from the 6.3V. supply of an amplifier. Maximum anode and S.G. voltages are 250V. and 100V. respectively.

A ring holder, with clips, may be used for the

One-valve Receiver

This will operate phones with a 90V. to 120V. battery H.T. supply, and 6V. heater supply. Or it can be employed to feed an amplifier, as mentioned. The circuit is shown in Fig. 3. Super-regenerative circuits are not recommended, because they may so easily cause interference. Nor should an ordinary regenerative detector be operated at oscillation point for this reason. If this is remembered, no interference can be caused.

A compact layout, with short wiring, is necessary, and the circuit will readily tune from 40 to 70 Mc/s. or about 7.5 to 4.25 metres. Other transmitters (such as Amateurs) within the band tuned will, of course, be heard also. To reach the higher frequencies stray capacity must be kept very low, or a coil with fewer turns will be required.

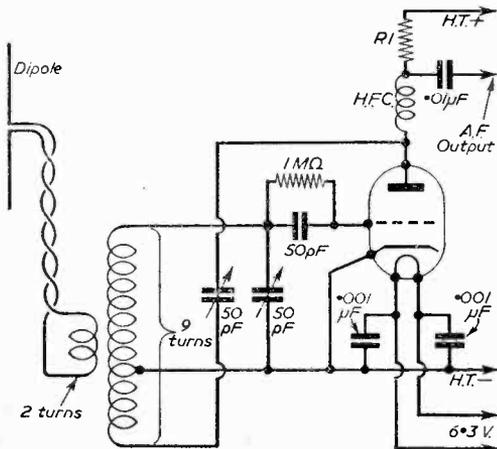


Fig. 3.—The detector circuit.

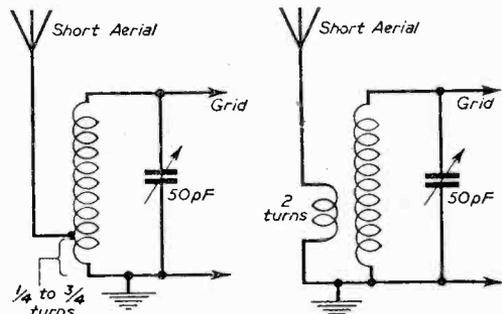


Fig. 4.—Alternative aerial couplings.

R1 may be 50K. for a H.T. line of 175V. to 200V. For 350V. supplies a larger value is required, or a dropping resistor in the amplifier. The 954 may be used as a triode by strapping

coupled to the receiver by either of the methods shown in Fig. 4. Tight aerial couplings should not be used, or adequate reaction will be impossible. The aerial wire may be indoors (except in metal buildings) and may be cut one $\frac{1}{2}$ -wave long.

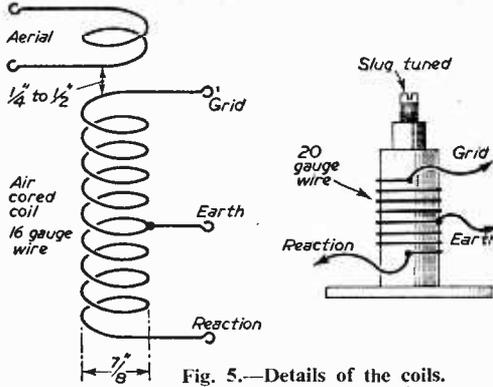


Fig. 5.—Details of the coils.

anode and screen grid, suppressor being returned to cathode. Excessive anode voltages must be avoided, or reaction will be difficult to control.

A simple wire dipole, using a few feet of conductor for each element, is satisfactory. If circumstances result in poor volume, signal strength can be increased by cutting the dipole to suit the station, or by using an improved form of aerial. The distance between aerial coupling winding and tuned winding will considerably influence results. With very weak signals, reaction is also quite critical.

In many areas a single vertical wire a few feet long will be sufficient. This may be

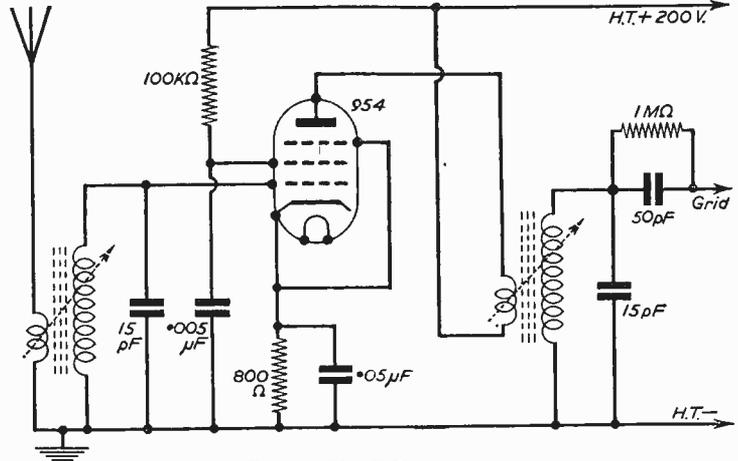


Fig. 6.—The R.F. stage.

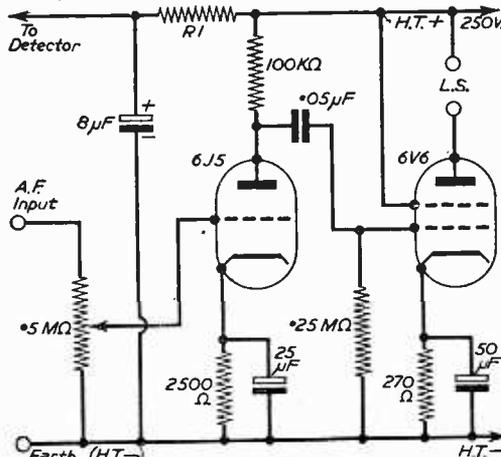


Fig. 7.—A simple amplifier.

to gang with other tuned circuits, modification of the number of turns is a simple matter, until the station is found. Between four and eight turns on the tuned section will normally suffice with a $\frac{3}{8}$ in. or similar former. Slightly fewer turns are used on the reaction section. The band covered may also be modified by changing the parallel capacity, and a pre-set can be used here.

Adding an R.F. Stage

An R.F. stage will improve volume, and a circuit for this is shown in Fig. 6. Slug tuning will be simplest, to avoid two tuning condensers or possible instability associated with continuous tuning with a ganged condenser. If any difficulty arises in aligning, the R.F. coil may be temporarily disconnected, a H.F. choke or .25 megohm grid load being provided. The detector coil can then be tuned, as for the one-valve circuit. The aerial coil can then be replaced in circuit, and tuned.

Scanning & Synchronisation

4.—FRAME SCANNING CIRCUITS (2)

By G. K. Fairfield

High-impedance Coils

IN an attempt to dispense with an output transformer and its attendant disadvantages, high-impedance coils have been used for the frame scanning circuit. A simplified arrangement used for the output stage is shown in Fig. 25. An isolating capacitor C is necessary to prevent direct current from flowing through coils Ry, included in the anode circuit. A resistor R1 is

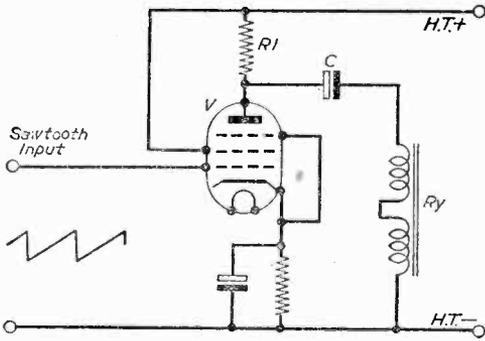


Fig. 25.—Frame scanning output stage for high impedance coils.

connected between anode and H.T. rail and will inevitably absorb some of the output current and result in a fairly low efficiency for the circuit. The limiting factors for scan distortion will now be the reactance of the coupling capacitor C and value of the load resistance and it can be shown that the percentage scan distortion produced by the circuit is given by:

$$\% \text{ distortion} = \frac{1.9}{C \cdot (R - R_y)}$$

where R is the resistance of the parallel combination of R1 and the valve anode impedance Ra. The value of Ry is governed by the practical difficulties of winding a suitable deflection coil and the most one can hope for is a figure of around 2,000Ω. The resistance R1 cannot be too large or the anode will "bottom" at the peak of the sawtooth current swing. Let R1 be 6,800Ω using a valve of Ra=5,000Ω, then for a maximum of 5 per cent. distortion a capacity value of about 80μF is required. This is not an unreasonable figure, although the cost of such a capacitor—at a working potential of 200 to 250 volts—together with the practical difficulties of coil construction (a subject to which it is hoped to return later in this series) will have to be balanced against the cost of a transformer circuit. A further point to consider is the power dissipated in R1. In the example given about 20 per cent. of that supplied by V will not reach the scanning coils, and whilst this low efficiency

may be tolerated for the older 53 deg. scanning-angle tubes, it would be difficult to justify for the wide-angled tubes in use to-day.

Sawtooth Current Generators

The third class of scanning circuits mentioned in the introductory article (part 1) were those which generated a sawtooth current directly without the need for first producing a controlling sawtooth potential. The inductive transistron circuit to be described below is of this type and is suitable for scanning a 12in. tube with an applied EHT of 10kV. This circuit has several points of difference with the Miller transistron used for electrostatic timebases and before describing these it is as well briefly to run over the working of this latter circuit.

Referring to Fig. 26, the transistron can be regarded as a means of periodically short-circuiting the capacitor C between intervals of slow charging via a large resistor R from the H.T. supply. Thus it resembles the sawtooth generators described in an earlier article (part 2) although, in this case, the positive feedback necessary for repetitive action is obtained between screen and suppressor grid via coupling capacitor C1.

Consider the sawtooth cycle to commence with C fully charged and with g3 at zero potential. Screen-grid current Ig2 is at minimum and allows the screen-grid voltage Vg2 to take up its maximum potential. As C discharges linearly through R the grid g1 becomes less negative, allowing Ig2 to increase slightly; Vg2 falls gradually until the "knee" of the pentode characteristic is reached, when anode current ia begins to decrease. This causes a sharper reduction in Vg2 which is communicated to g3, causing this electrode to be biased negatively and ia is now rapidly decreased until the anode current is cut off. g3 is now left with a large negative bias and g2 is drawing

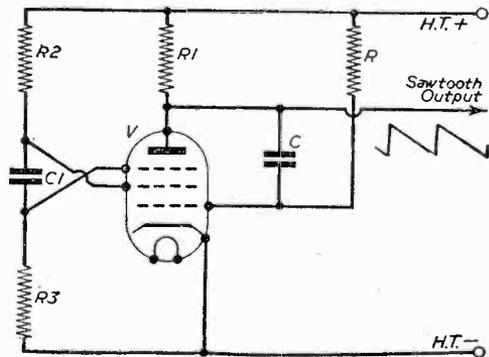


Fig. 26.—Miller transistron sawtooth voltage generator.

all the cathode current. With no drop across R1 and the capacitor now almost completely discharged, g1 assumes a positive potential and C is rapidly charged by grid current via R1. This tends to increase g2 current and reduces vg2 still further causing g3 to become yet more negative. When C is nearly fully charged, vg1 becomes nearly zero potential and Ig2 is reduced. Vg3 rises and allows anode current to flow once more. The cycle then repeats with C discharging gradually through R once more. This rather complicated sequence of events will be made clearer by reference to Fig. 27, which shows the waveforms experienced at the different electrodes during the sawtooth cycle.

The modified transatron circuit for EM scanning is shown in Fig. 28. An output transformer takes the place of R1 and low-impedance coils are connected across the secondary circuit. Correction for the distortion introduced by the transformer is obtained by feedback from the primary circuit to g1 via C2R4, and R4 is made variable to provide a linearity adjustment. Some compression at the top of the picture may be experienced and is due to the small inductive component of the deflection coils. This may be removed by suitable choice of R5 inserted in series with the charging capacitor C. Sawtooth amplitude is best adjusted by variation of total H.T. supply, in order to have as little effect on the operating frequency as possible. R6 achieves this and is bypassed by a decoupling capacitor C3.

The transformer used can follow the general lines of that described in the previous article with the turns ratio adjusted to:

- primary: 3,900 turns .0092 en. copper wire
 - secondary: 420 turns .018 en. copper wire.
- This will then be suitable for matching 26Ω coils

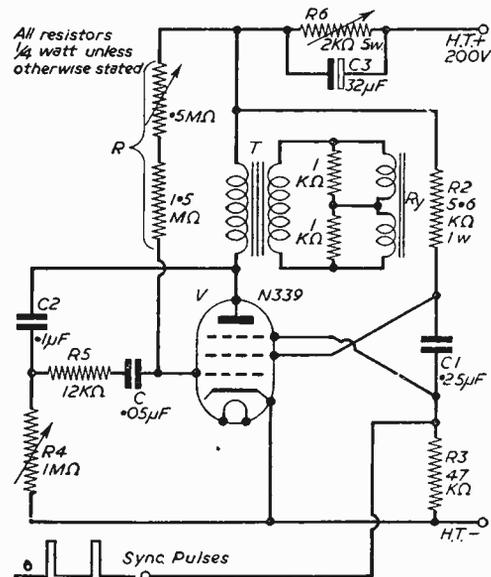


Fig. 28.—Inductive Miller transatron frame scanning circuit.

and later in this series will be described the construction of a suitable set of coils.

90 Deg. Scanning

To complete this section on frame circuits let us now consider the latest of frame scanning problems: that of beam-deflection in the new

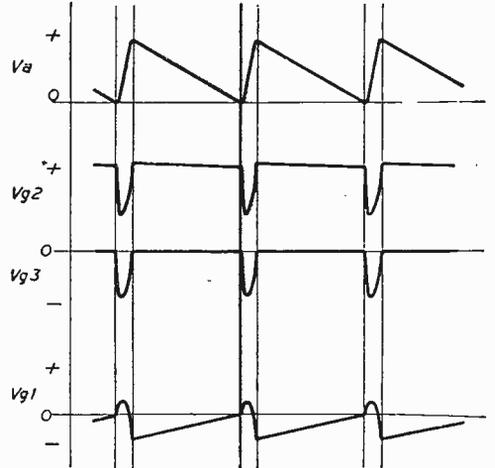


Fig. 27.—Waveforms at the various valve electrodes of the transatron circuit.

90 deg. scanning-angle tubes now appearing on the British market.

As the cathode-ray tube neck diameter in these new tubes is unchanged (35mm.) a decrease in the deflector coil sensitivity can be expected due to the necessity to avoid beam cut-off or "shadowing" of the picture. Even with an unchanged sensitivity, a 20 per cent. increase in scanning current will be required, so that the design must be capable of delivering, say, 30 per cent. more scanning current than a 70 deg. circuit. Fortunately the increase in mean anode current

(Continued on page 238)

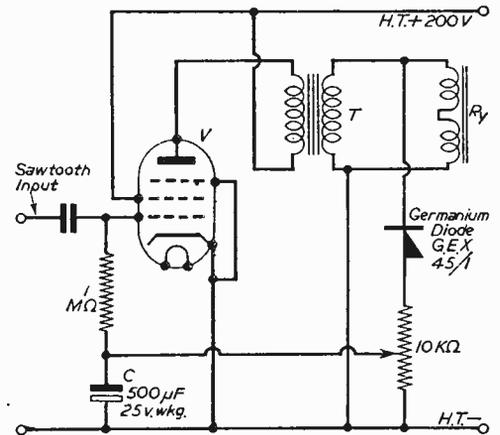


Fig. 29.—Method of obtaining bias supply in a frame scanning output stage.

FLYWHEEL SYNC. & A.G.C.

AN EXPLANATION OF THESE CIRCUITS, AND METHODS OF INCLUDING OR ELIMINATING THEM IN EXISTING RECEIVER CIRCUITS

By H. Peters

TWO blessings have been bestowed upon the manufacturer by his designer to make his set "elastic," and these are "Flywheel Sync." and "A.G.C.," and although these are usually accorded separate paragraphs in the manual they are almost Siamese twins in the set, as engineers sometimes discover when things go wrong. The purpose of these notes is to attempt to break up the circuits physically and diagrammatically so that fault finding can be done in logical progression. In addition suggestions will be made to help those who wish to remove either or both, and details are given to enable both types of control to be fitted to receivers without them.

In order to establish how the two systems are linked Fig. 1 (a) is a block diagram and (b) waveforms. They do not relate to any particular set, but form the basis of most systems used.

Beginning at the left-hand side there is the sync. separator, which is similar to the type employed in non-flywheel receivers. At its grid there is a composite video waveform which is inverted to feed the C.R.T. cathode, and at its anode there is available an amplified upright (negative going) line sync. pulse.

This is passed on to the discriminating device, but may be inverted or amplified—or both—on the way. Here the sync pulses are compared with a reference waveform, usually derived from the line amplifier, and a resultant D.C. voltage, whose amplitude and polarity is according to the difference, is used to vary the speed of the line timebase by means of a control device.

The "flywheeling" of the line sync. system is due to a smoothing device at the discriminator output, shown as a box labelled "Time Constant." This ensures that the control only varies according to the average of the difference between the sync. and the reference pulse, and not to individual pulses.

Whilst all this is going on the inverted video waveform at the sync. separator grid is quietly

passed to the box marked "gate," where the short period of black level which follows the line sync. pulse is measured and the output voltage so derived is used as A.G.C. to control the gain of the R.F. and I.F. valves. If everything from the camera to the video detector is working right this "back porch" of black level corresponds to the strength of the received signal and will produce an accurate control of gain regardless of picture content. The last box in the bottom row is labelled "protection" and covers the devices incorporated in the set to prevent overloading of the video stage before the A.G.C. system warms up, and at other odd times.

The bonds which link these two systems, and which make servicing awkward at times, are the reference pulses which are derived from the line timebase stage, and which for manufacturing convenience can even be one and the same pulse.

The state of affairs can be better visualised by a study of Fig. 1 (b), where the composite video waveform (i) is shown in register with the idealised waveforms required to work the flywheel sync. (ii) and the A.G.C. (iii).

As far as the flywheel sync. is concerned the middle of the line flyback (m) should come halfway between the end of the picture on one line (e) and the beginning of the picture on the next (b). This centres the picture electrically in the raster and prevents foldover, and as can be seen in the drawing, the line (m) is to the right of the centre of the sync. pulse itself. In actual practice slight variations from the ideal do occur, but they do not materially affect the action of the control.

The A.G.C. gating pulse (iii) has to be positioned in the centre of the back porch, and it can be seen that it also coincides with the end

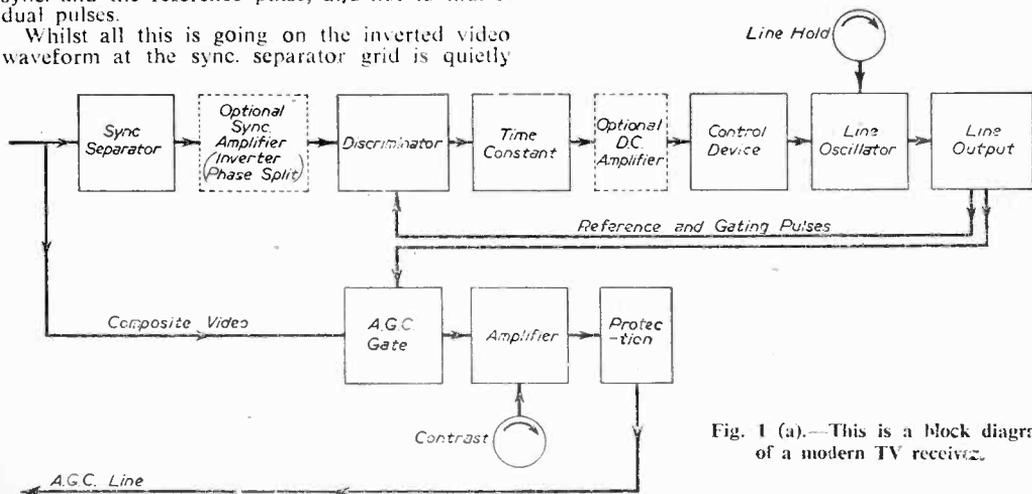


Fig. 1 (a).—This is a block diagram of a modern TV receiver.

of the flyback line, which provides the clue as to why the two systems are sometimes fed with the same pulse and how faults in one can affect the other. Consider, for example, a fault in the line timebase which causes the picture to move slightly to the right; the gating pulse (iii) for the A.G.C. will then occur at the end of the sync. pulse and

and the two effects may be sometimes seen together when hum gets into the line oscillator, causing bent verticals. Where the picture is bent to the right it will brighten up, and where it bends to the left it will darken, giving the appearance of a hum bar. A variety of interesting faults can arise from this association, and in order to set about them logically it is usually desirable to disconnect the one whilst working on the other. This can be done at various points and these will come to light as the circuits are analysed.

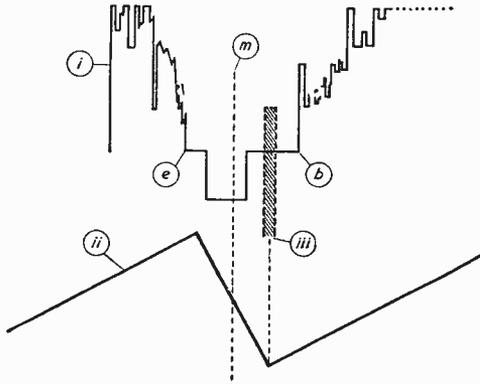


Fig. 1 (b).—The ideal waveforms to be expected in a receiver.

no voltage will be developed at the output of the gate. The set will then run at maximum gain and probably produce a negative picture. If the phase of the line oscillator was such that the picture shifted the other way, to the left, that is, the gating pulse would sample the picture instead of the back porch, and the voltage at the output of the gate would increase and thus black out the picture.

Discriminator Flywheel Sync. System

The circuit in Fig. 2 (a) represents the commonest type of flywheel timebase. It is by no means the original in this country, where the honours go to English Electric's Synchrophase, but is representative of the systems used by Bush, Ekco, Murphy, Pye, Philips, Philco and others. V1, the sync. separator, is a conventional pentode, cumulatively biased back to cut off the negative-going picture input and to amplify only the positive going sync. pulses. Its anode load is the transformer T1, which may be augmented by a resistor to develop a larger frame pulse. The secondary of this transformer is centre tapped and feeds equal and opposite pulses of about 20 volts amplitude to the rectifiers D1 and D2. The sense of these pulses is shown in the diagram, and it will be seen that the two diodes conduct at the same time, developing equal and opposite voltages across R1 and R2, and leaving their junction, from which the output is taken to V2, at zero.

The other ends of the two diodes are joined, and at this point is fed a sawtooth waveform (3) from the line output stage. This is an A.C. waveform and therefore balances about its middle

These two examples serve to illustrate the dependence of the A.G.C. on the line timebase,

(Continued on page 219)


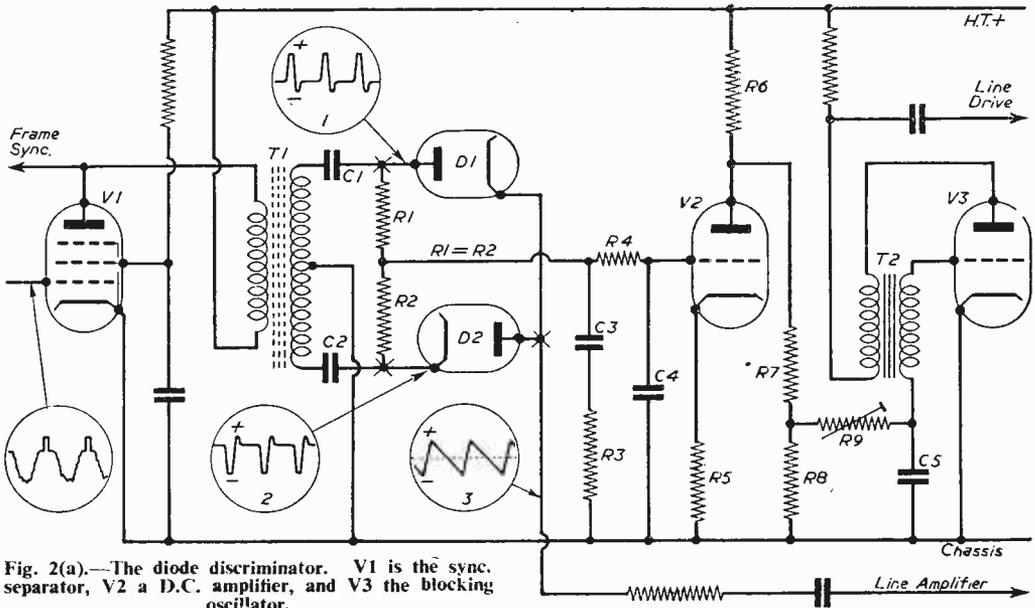


Fig. 2(a).—The diode discriminator. V1 is the sync. separator, V2 a D.C. amplifier, and V3 the blocking oscillator.

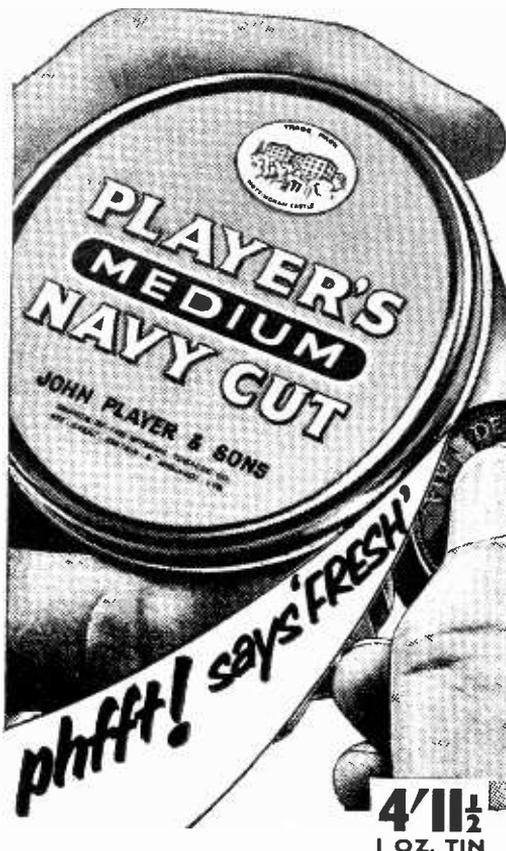

Quality says 'PLAYER'S'

You can buy your favourite PLAYER'S NAVY CUT anywhere in attractive 1 oz. vacuum tins. It comes to your pipe as fresh and full of flavour as the day it leaves PLAYER'S, and stays that way — to the very last shred — in the special air-tight container.

ALL IN ONE OUNCE VACUUM SEALED TINS



4/3½d

4/7d

4/11½d


5/0½d

**PLAYER'S
NAVY CUT TOBACCOS**

[NCT 101U]

COMMERCIAL TV

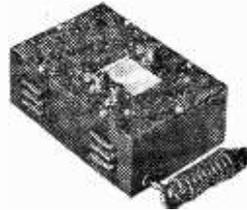DON'T GIVE UP BEFORE YOU HAVE TRIED OUR BAND III PRE-AMP



Separate coaxial inputs for Band I and III Aerial Downloads. No changing of Aerial leads. No Diplexor required. Attractive black crackle finished case fitted with non-scratch rubber feet. Easily installed—just plug in mains and aerial leads.

A sensitive unit complete with built-in power supply specially designed for use in ultra-fringe areas. High signal to noise ratio. Will produce excellent results in localities where the signal is normally unusable.

Dimensions 6in. x 4in. x 2½in. Will fit inside most receiver cabinets. 200-50 v. A.C.

PRICE £6.6.8. C.W.O. OR C.O.D.
(Fly Lead 3/6 extra.)

"AIRVISION"

(Electronic Equipment Manufacturers)
14 Boulton Road, SOUTHSEA

BAND III CONVERTOR

for ANY SET in ANY AREA

This unit has been widely used since I.T.A. Transmissions began to convert all types of sets, Superhet and T.R.F., to receive on Band III.

Unlike many other convertors this unit is small enough to be fitted inside your cabinet, enabling the job to appear finished and perfectly safe for all to use.

The wiring is simple to follow, and alignment is not difficult.

- ★ IT will convert any set, any age, T.R.F. or Superhet.
- ★ IT includes station switching.
- ★ IT provides pre-set contrast balancing.
- ★ IT uses only one aerial input for both bands
- ★ IT provides manual tuning on Band III.
- ★ IT is totally screened.
- ★ IT completely rejects unwanted signals.
- ★ IT requires no additional power supply where either 6.3 v. or .3 amp. heater line is available.

CONVERTOR wired and aligned with fitting instructions £3 10 6
KIT complete in every detail, less knobs £2 10 6
KNOBS each 1 0
CIRCUIT and instructions in detail (free with kit) 1 6
KITS made up by customers checked and aligned, including post 12 6

When ordering please state present B.B.C. Station and I.T.A. Orders over £2 post free.

C. & G. KITS

285, LOWER ADDISCOMBE ROAD,
ADDISCOMBE, CROYDON, SURREY

Phone: ADDISCOMBE 5262

as seen in oscillogram (3). D2 conducts for the portion of the waveform above the line and D1 for the portion below the line; and although R1 and R2 are charged up on alternate half cycles the voltage at their junction over a period of time averages zero.

Now provided that the sync. pulses are fed in at the same time as the sawtooth waveform passes across the zero line the voltage at the junction of R1 and R2 will still be zero. Such a moment occurs halfway through the flyback period and as we saw in Fig. 1 (b) this is just when we want it to be. If the sync. pulses arrive at that instant the line oscillator is running at the right speed and all is well.

What if the line oscillator tries to go fast? The flyback period will have passed by the time the two balanced sync. pulses get to the diodes and

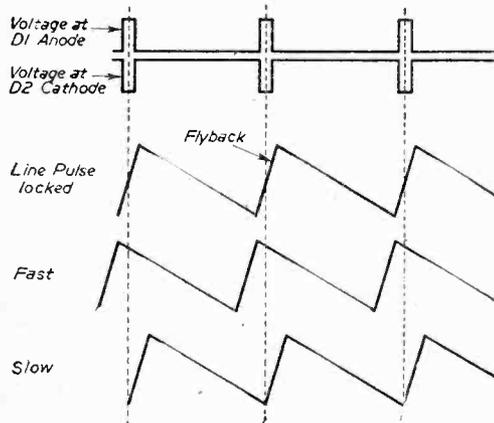


Fig. 2 (b).—Waveforms out of sync. and locked.

the sawtooth waveform will be causing D2 to conduct heavily and at the same time lift the cathode of D1 positive, cutting it well off. Thus the negative going sync. pulse to D2 adds itself to the current passing through the diode and makes the charge at the bottom end of R2 more positive. (If you find this confusing, remember that a negative voltage applied to the cathode of a diode causes conduction just as much as a positive one applied at the anode.)

At D1 conditions are rather different; the diode is biased beyond cut-off by the positive pulse at its cathode, and because the amplitude of the positive sync. pulse is less in value it cannot overcome this bias and D1 remains cut off. So the voltage at the top end of R1 becomes less negative than before.

It follows from this that the voltage at their junction—which hitherto was zero—will now be positive by an amount equal to half the voltage at the bottom end of R2, and will ultimately be used to control the line speed.

The reverse happens if the timebase runs slow. In this instance the sync. pulse arrives before the flyback period, and D1 will be approaching the peak of its conduction. Thus the positive pulse applied to D1 anode will cause the diode to conduct all the more and build up a greater negative charge at the top of R1. D2 will this time be

cut off and the negative sync. pulse, being of less amplitude than the cut-off voltage, is ineffective. So the bottom of R2 remains at zero and the junction voltage is now negative by an amount equal to half the voltage at the top of R1.

We now have available a control voltage which is positive when the timebase runs fast, and negative when the timebase runs slow. It is still responsive to random noise and interference, but can easily be smoothed out to present a reasonably clean D.C. This is done by C3, R4 and C4, with R3 thrown in to provide a fixed delay time, and this section corresponds to the box in Fig. 1 marked "Time Constant."

Horizontal Hold Control

We jump ahead a bit to the blocking oscillator V3, which generates the line scan, and which is conventional except for the horizontal hold control. It is common practice to use a potentiometer across the H.T. supply to perform this function, the higher the voltage on the slider the faster the timebase and vice versa. This enables R9 to be a high stability type, for it is the value of this resistor and C5 which determines the repetition frequency of the scanning voltage. In our case R9 is made variable, and the potential divider across the H.T. supply comprises 3 fixed resistors, R6, R7, R8. If the voltage at the junction of R7, R8 was to rise, the timebase would run faster, and this could be done by applying the D.C. which is available at the end of R4, but unfortunately it is of the wrong polarity. V2, the D.C. amplifier, is therefore interposed between the two, and this not only inverts the sense of the control voltage, but amplifies it as well, thus increasing the "pull-in" range. R6 not only happens to be the top resistor in the blocking oscillator potential divider, but is also the anode load for V2.

Variations on the above circuit are manifold. Pye and Bush use a multivibrator line oscillator and dispense with the D.C. amplifier, and although this would be expected to reduce the pull-in range, it does not in practice appear to do so. This is partly because of the greater stability of the multivibrator as a sawtooth oscillator and partly due to greater control voltages being made available from the discriminator.

In some instances the sense of the control voltage is reversed by inverting the applied sawtooth, and it is instructive to permute the possible combinations, available by inverting the sync. pulses, reversing the sense of the diodes, applying the sawtooth at the other side of them.

Fault-finding

Faults in the flywheel system are usually difficult to locate because they seldom stop the set from working altogether. Drift in the oscillator will not show itself until it exceeds the pull-out range of the discriminator or until the transmission breaks momentarily, when sync. is lost and the horizontal hold has to be reset. Unfortunately similar symptoms can arise if the pull-in range is low due to a fault in the control device or discriminator. To settle which half of the circuit is at fault, the line oscillator can be made free running by disconnecting the "flywheel."

A suitable way in Fig. 2 (a) is to ground the grid of V2, or disconnect its anode from the junction of R6, R7.

In the case of multivibrators, or where no D.C. amplifier is used, it is better to disconnect right back at the discriminator at the points marked X. In strong signal areas where conventional sync. is quite adequate this can then be fitted and, if desired, left permanently in the circuit. In Fig. 2 (a) this would be done by connecting a 5pF condenser between the anode of V1 and the anode of V3. A similar link can be fitted from the same point to other types of timebase. In the case of multivibrators it is best to try it on both anodes and grids in turn, as although the sync. pulse will lock the oscillator almost anywhere, it can, if applied at the wrong electrode, give

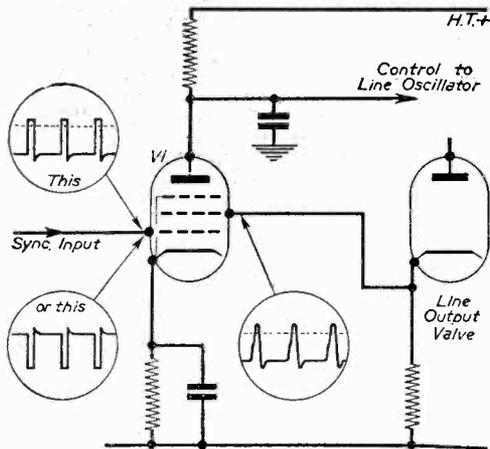


Fig. 3.—A pentode coincidence detector. The screen is tied down to the line output valve cathode.

rise to false lock when the set warms up (i.e., blanking pulse appears down the centre of tube).

The time constant section can give rise to short pull-in or erratic behaviour. C3 is usually in the order of 1.0 μ F (paper) and is likely to leak, and although this will not have much effect in the circuit as shown, if its bottom end is returned to a positive potential, as in the Pye, it can cause intermittent oscillator drift.

If C3 loses its capacity, ragged edges may result, or even "hunting," which is a continual over-correction of the system and which produces oscillating verticals and a corrugated picture.

Bent verticals normally indicate mains hum in the timebase, and in Fig. 2 (a) will usually be picked up in the grid of V2, perhaps on R4. A hint here is to reverse the polarity of the mains supply. If the verticals bend the other way the cause is due to mains; if they do not, the frame timebase should be suspected.

Trouble in the discriminator can be caused if the diodes have unequal emission. If this is the case, and the unbalance due to it is within the pull-in range of the system, it will be corrected automatically, but will result in the free-running speed of the oscillator being offset from normal by an amount due to the voltage required to correct the discriminator's unbalance. The symp-

oms to the user are that the horizontal hold control is over to one end and the picture often warms up out of sync. This sort of trouble is more likely to crop up where semi-conductors are used, and fortunately these can be checked by an ohms test both ways round.

The Coincidence Detector (Fig. 3)

This circuit, which is about the simplest type of flywheel sync., is centred around a valve, usually a pentode, which is biased beyond cut-off on two electrodes, in our case on the control and screen grids. Positive going sync. pulses are fed to the grid at an amplitude sufficient to lift it above cut-off on the peaks and positive line flyback pulses are fed to the screen, which in turn raise it to sufficient a potential to enable the valve to conduct.

It can be seen that the valve will only pass current when the grid pulses and screen pulses arrive at the same time, and that the amount of current passed will be greatest when they overlap exactly. At this point the anode voltage will be at its lowest and it is this "dip" which is used to control the line timebase speed. A disadvantage of this system is that if the timebase runs either fast or slow it will cause the anode voltage to rise, and so the pull-in only works one way. For this reason the free-running speed of the timebase is offset from the correct one, usually on the high side, so that the circuit is held on lock when the pulses only partly coincide. By this means the device can pull-in both ways. Another disadvantage is that the pull-in range is small compared with the previous system, and this can lead to the hold control requiring resetting every time the receiver is switched on. This can be overcome by designing the line oscillator to warm up slowly and pass through 10,125 c.p.s. on its way to its slightly offset free running speed. Provided it does so slower than the time constant circuits can smooth out its effect the coincidence detector will "latch on" to the timebase and hold its speed steady. (To be continued.)

PRACTICAL WIRELESS DEC. ISSUE NOW ON SALE PRICE 1s. 3d.

A small push-pull 3-stage Gramophone Amplifier for A.C. mains operation is the main constructional feature in the December issue of our companion paper *PRACTICAL WIRELESS* which is now on sale.

There is also an article on making a Coil and Transformer winder which is invaluable to the keen experimenter.

The Applications of the OCP71 deals with the Phototransistor, whilst the article which forms the subject of this month's stage in the *Beginner's Constructional Course* deals with the addition of a transistor and of a Long Wave winding for the coils.


Other articles deal with the Tape Recorder Dictation Switch, Transistors in Practice, a Transistorised Pulse Generator, Component Faults and Testing, Microphones and further notes on the conversion of the Command Receiver. The usual features on Transmission, Programme Notes, etc., complete the issue.

A C.R.T. Tester and Rejuvenator

A HANDY UNIT FOR THE SERVICE WORKSHOP AND THE KEEN EXPERIMENTER

By J. Hillman

IN TV servicing one of the great problems is whether the tube is at fault or whether the fault lies in the video circuit. In most cases it is difficult to decide which is the trouble, and extensive testing is necessary before a definite conclusion can be reached. This, of course, takes time and adds to the cost of any repairs, so this tester was designed to overcome these difficulties. With this tester the tube can be tested at its correct heater voltages and its emission checked, any leakage between cathode and heater, cathode and anode, grid and anode being located. All these tests can be carried out without removing the tube or having the set on, and, of course, this can be done at a customer's home. Another advantage is that new tubes can be tested without

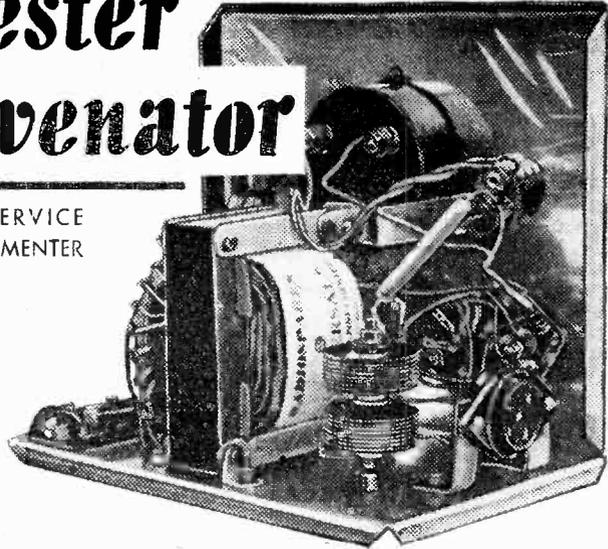

taking them out of their cartons and thus time is saved, for it has been known for new tubes to be faulty and the fault only becomes apparent when it has been fitted to a set. The operation of the tester is quite simple and consists of applying a low H.T. voltage between cathode and grid and checking the reading on a meter. The right heater voltage is selected by means of a switch and the test is selected by means of another switch. Adaptors are used to suit the particular tube to be tested and thus any make of tube can be tested. The reason for using a low H.T. voltage is to avoid breaking down the insulation between electrodes and thus creating faults. The tester can also be used to rejuvenate old tubes by applying the H.T. between the cathode and grid and gradually increasing the heater voltage by means of the variable resistor and heater switch until the emission current rises as far as possible.

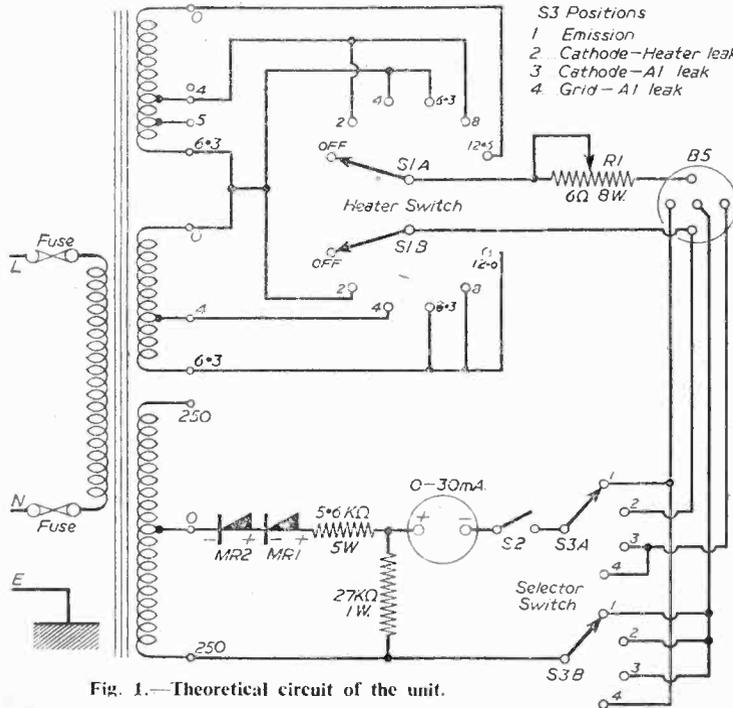


Fig. 1.—Theoretical circuit of the unit.

Construction

First mark off on a sheet of aluminium as in Fig. 6 and cut off the shaded portions, then bend up the 1/4 in. sides. Note that the one edge has no 1/4 in. side and this is the bottom of the front panel. Next mark off as in Fig. 2 and drill and file holes as shown, the

hole marked A is first drilled $\frac{3}{16}$ in. and then filed larger to suit the size of toggle switch used. The hole marked B may be $\frac{3}{16}$ in. or $\frac{1}{4}$ in. according to the type of variable resistor used. Now mark off and cut out the chassis, as Fig. 3. and bend up the $\frac{1}{4}$ in sides and mark out and drill as Fig. 4. The front panel and chassis may now be placed together, and by marking through the centre $\frac{3}{16}$ in. hole and drilling through the chassis the panel can be secured temporarily with a 6BA screw whilst the other two holes are then drilled and secured with 6BA screws. Now fit the mains transformer, using 4BA screws, then the rectifier, twin fuseholder, 3 switches, resistor and meter. In fitting the meter place it in the hole and get it level and then mark through the holes on to the panel and drill $\frac{3}{16}$ in. holes securing with 6BA screws. Make up the bracket as in Fig. 5 and bend the two ends at right angles so that it appears as in Fig. 7. It will be seen that one end of the

top and secure with a self tapping screw, 6BA. Then get cover to fit properly and drill one hole at a time, securing with a self tap screw each time.

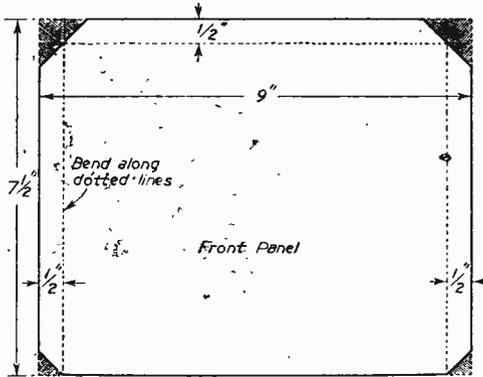


Fig. 8.—The front panel details.

bracket is secured to a bracket on the mains transformer whilst the other end is fastened to the front panel with 4BA screws. The object of this bracket is first to strengthen the support of the panel and second to provide a position for a dial bulb bracket. The cover can now be made as Fig. 6, bending the two 7 in. sides first, then the $\frac{1}{2}$ in. sides and finally the remaining 7 in. side. Now drill holes marked A in Fig. 6 and secure with 6 BA screws. Next mount the valveholder by means of two suitable brackets, as Fig. 10 in position as Fig. 7. Place cover in position and mark and drill a $\frac{3}{32}$ in. hole in the centre of the

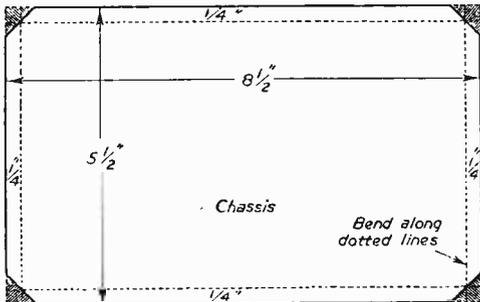


Fig. 3.—Details of the top of chassis.

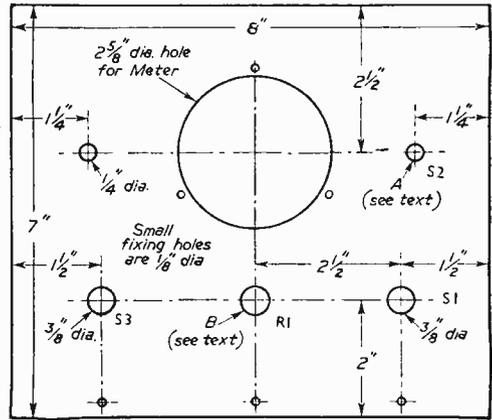


Fig. 2.—Drilling details for the panel.

The holes in the bottom of the cover where they go through the chassis are secured with 6BA screws. Finally remove cover and mark off position of a suitable hole to allow access to the valveholder and cut out the hole.

Wiring

Wire up the heaters, first using 20 s.w.g. T.C. wire and cover with sleeving. It may happen that the mains transformer heater windings are phased differently from that shown in Fig. 1; if so, then the circuit will be as Fig. 11. A check should be

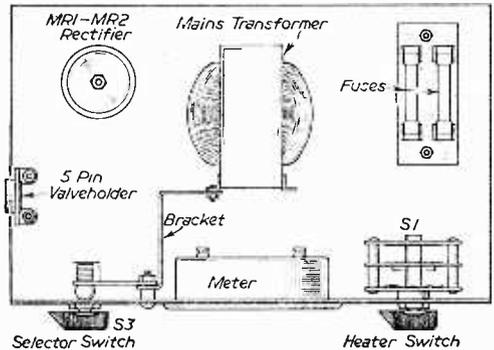


Fig. 7.—The layout.

made with an A.C. voltmeter across the two windings in series and if the voltage is about 13 volts then the two windings are phased correctly. If, on the other hand, the voltage is very low, then they are out of phase and the connections will need to be altered. Now complete the rest of the wiring, taking note of the correct polarity on the rectifiers and on the meter. The adaptors are made up, using an old valve 5-pin type with the glass envelope removed and the wires unsoldered from the pins and 7/33 coloured flex used to make a lead 3ft. long. Three adaptors are sufficient to cover most C.R.T.s. one with a

B12 valveholder, the other two a Mazda and an International octal valveholder. These are wired up as in Fig. 9.

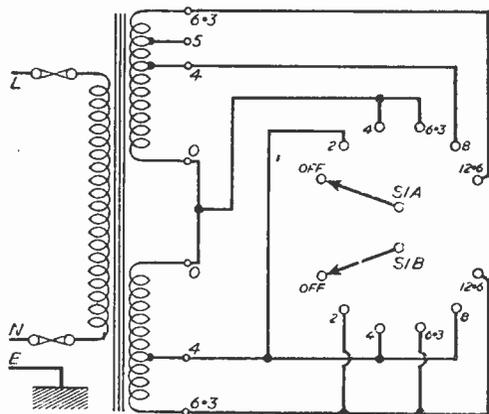


Fig. 11.—Alternative switch circuit.


Testing

Before testing C.R.T.s check all the voltages at the adaptors with different settings of the switches and R1. The voltages should be as follows: H.T. volts off load between cathode and grid 90 volts, and on load 15 volts; H.T. current off load is 3.5mA; the heater voltage on 12.6 position of S1 off load will be about 14 volts; on load voltage on 6.3v. range with resistor R1 at max. volts is 6.5v. and with resistor at min. volts is 4.75v.; on the 8 volt range resistor at max volts is 8.4v. and at min. volts at 6.5v. Having made sure that all the voltages and adaptors are correct a C.R.T. may now be tested. First put S2 to off, next

on position. 3 the cathode/A1 leakage is checked, and on this it is quite in order for the meter to read slightly, providing it does not read more than the first division of the meter. Finally, on position 4 the grid/A1 leakage is read, and this should be zero for a good tube.

Rejuvenation

This is carried out by first running the tube at its correct heater voltage and then putting R1 to min. volts position (i.e., with all resistance in circuit) and switching S1 to the next highest heater range and gradually increasing the heater voltage by means of R1 until the meter reading will not increase any more or until it reads 15mA. To take an example, say a 6.3v. C.R.T. First switch S1 to 6.3v. and advance R1 to max. volts and allow C.R.T. to heat up, then put R1 to min. volts and switch S1 to 8v., allow C.R.T. to heat

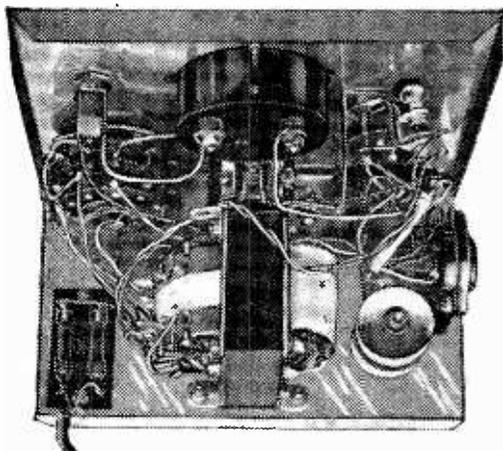

A view of the layout and wiring.

up and watch meter until current will not rise any more. Then advance R1 until current rises again, leave until current stops rising, and then increase R1 again and continue like this until

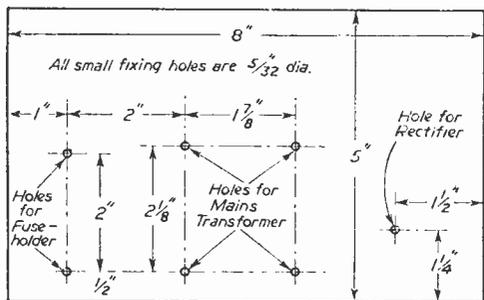


Fig. 4.—Drilling details for the chassis.

select the correct heater voltage to suit the tube to be tested, plug on the adaptor to suit the tube after first removing its holder. Now plug in to the mains and allow the heater to warm up, and then with S3 in position 1 switch on S2 and read off the value on the meter. This should be around 15mA for a new tube and will be below 5mA for a tube that has lost its emission, whilst for a complete loss of emission the meter will read zero. Having read the emission the switch S3 is put to position 2 and the cathode/heater leakage will be shown if the meter reads at all. A good tube will have a zero reading. Similarly,

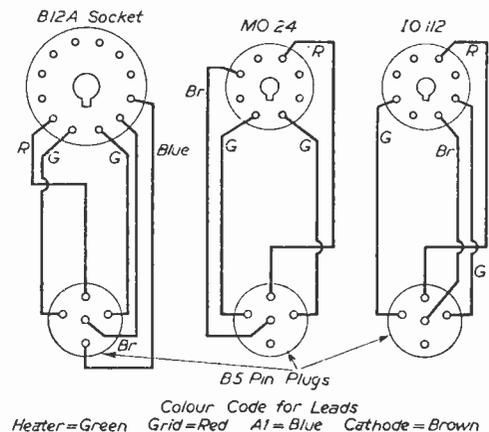


Fig. 9.—Tube base connections.

current ceases or meter reaches 15mA. Not all tubes will respond to this treatment, but a good proportion will have their useful life extended.


CRM92A, CRM121, CRM121A, CRM121B, CRM123 and CRM151 all call for the Mazda Octal base.

Tube Data

It is a good idea to type out a list of the tubes covered by the adaptors and to give their heater voltages, and then to glue this to the top cover of the tester. This will avoid the danger of putting the wrong voltage on a C.R.T. when checking at customer's house, and no data is available normally.

An examination of the various tube makers' catalogues will show that various tubes come under the different categories of bases. For instance, the majority of 6.3 volt tubes, with the exception of certain G.E.C. models, have the duodecal base and will therefore call for the B12A adaptor. The G.E.C. tubes 6501, 6502, 6504, 6504A, 6506A, 6703A, 6705A, 6802A, 6801A, 7101A and 6102A, although having 6.3 volt heaters, utilise the International Octal base. The Ferranti 8v. tubes, types T12/71U, T12/81U and T12/82U also require the Octal base.

The Mazda tubes C9A, C12A, CRM91, CRM92.

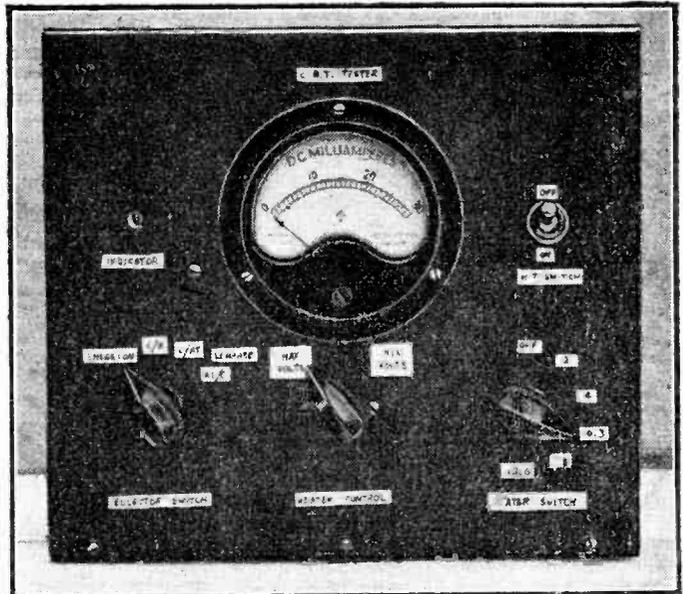

A front view of the panel.

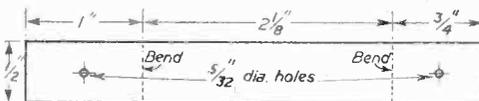


Fig. 5.—Bracket for bulbs.

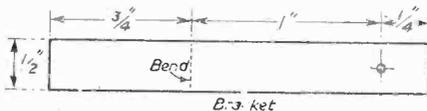


Fig. 10.—Valveholder brackets (two needed)

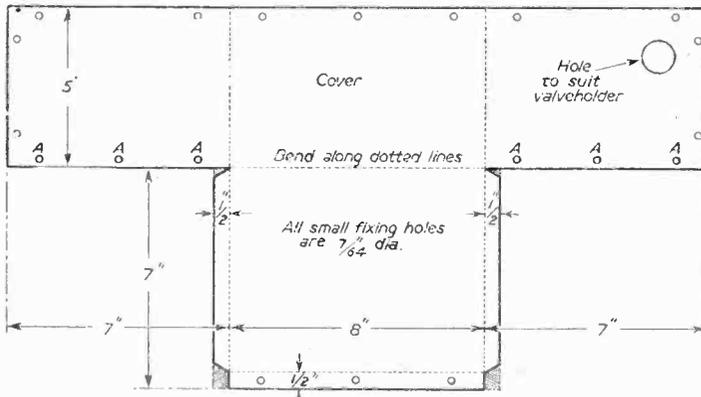


Fig. 6.—Details of the chassis cover.

Radio-telegraph Reception

IN telecommunications circles it is well known that errors can occur in messages transmitted by radio-telegraphy. Consequently, some messages, or parts of them, have to be re-transmitted so that the errors can be eliminated before the message is delivered.

In a new technique, developed by the G.P.O., frequency-shift keying is still used, but whereas in conventional equipment used for the reception of such signals a limiter and discriminator are employed, the new method makes use of the fact that all the signalling intelligence is impressed both on the marking and spacing frequencies. In other words, the information in the mark-channel duplicates that in the space-channel. Consequently, if all the available intelligence is derived independently from each frequency and then combined, a double-diversity arrangement is obtained. Frequency selective fading conditions often cause trouble on R.-T. circuits, but using the new arrangement they can be turned to advantage—if the signal on the marking frequency has faded, there is a second chance of obtaining the required information from the spacing frequency.

SIMPLIFIED TV SERVICING

3.—SETS USING R.F. OSCILLATORS FOR EHT

(Continued from page 160 November issue)

ALTHOUGH the general practice nowadays is to provide EHT by the line flyback method, there are still many sets of about the time T.V. broadcasting restarted, which use the R.F. oscillator method for obtaining EHT for the picture tube. In present-day sets it will only be found in projection models where about 25Kv is required on the tube. Fig. 9 gives a circuit showing a typical R.F. oscillator. Fig. 10 shows a line output stage used with it. It will be noticed that with this type of set the failure of the line output stage does not stop the EHT so that it is necessary in a set where the line fails to keep the brilliance control well down; otherwise damage will be caused to the C.R.T. In the larger projection sets this is covered by electronic circuits which disconnect the EHT from the C.R.T. should either the line or frame circuits fail. This is very necessary in these sets owing to the very high EHT provided. The oscillation frequency varies according to make and will be between 85 Kc/s and 300 Kc/s. The oscillator valve is generally a beam tetrode. Troubles that can arise here are mostly either faulty valves or shorting or arcing across the coil. Replacements are about the only solution.

Sets With EHT Supplied from Mains Transformer

This type of set, which is the earliest type of television set of which there are still some in use, used a mains transformer for supplying EHT. The C.R.T.s were nearly all electrostatic and a circuit is given in Fig. 11. The main

trouble on this section of these sets was generally the EHT secondary of the transformer going O.C. or shorting to the core. Valve trouble was not so common. As replacement transformers are very difficult to obtain it is best, if the job is required to be done, to have them rewound. The 1 μ F EHT smoothing condensers should always be checked. Be careful to short them out before

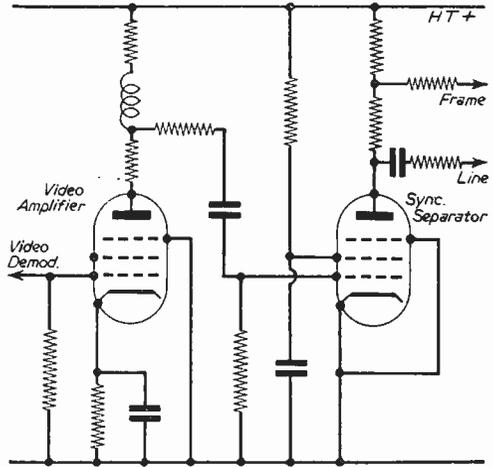


Fig. 12.—Simple sync separator.

checking. They can retain a very hefty charge for quite a time.

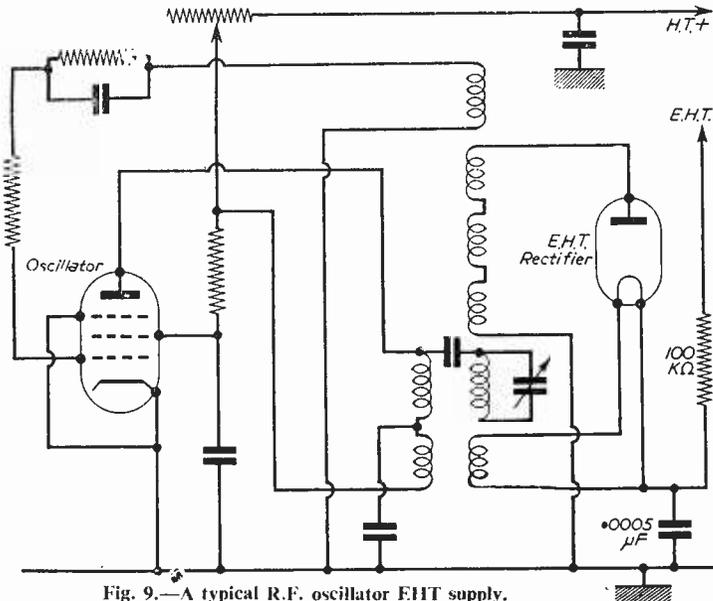


Fig. 9.—A typical R.F. oscillator EHT supply.

Set With Synchronising Faults

The sync separator stage is between the video system and the horizontal and vertical timebases. Any fault in this section will nearly always cause both the frame and line timebases to fall out of

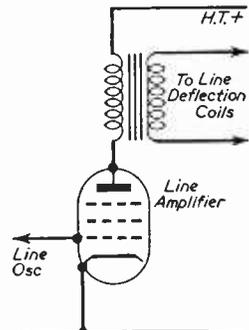


Fig. 10.—A line output stage for use with Fig. 9.

sync. The fault will be shown as a continually rolling picture (frame) or a torn-up picture (line). Sometimes it will be found that one can lock the picture but it will soon fall out of sync again. With only a meter to assist you here, it is difficult to trace a fault, but after valve checking the following should be carried out. Fig. 12 shows a simple sync separator. Fig. 13 shows another

If the video amplifier circuit becomes completely inoperative, there will, of course, be no picture on the screen, but if there are any faults in this stage they will be indicated by the picture shown. The following faults may occur. A faulty low frequency network, a faulty high frequency network or incorrect voltages on the valve electrodes. Should the first occur, a "smeary" picture will be noticed.

In this case check coupling and bypass condensers, grid resistors. It could also be due to overloading the video amplifier. Check the grid leak. The second fault will appear as ghost lines after any sharply defined line and especially noticeable on test card. Check the peaking coils in anode circuit of video amplifier and especially any resistors paralleled across them.

Sets With Two-stage Video Amplifiers

Many of present-day sets are now using two-stage video amplifiers. Some of these utilise the cathode follower technique. There are no more troubles to be expected here than from an ordinary video amplifier stage. If necessary the cathode follower could be isolated if trouble is met.

A circuit of a typical cathode follower stage and some further details will be given in our next issue.

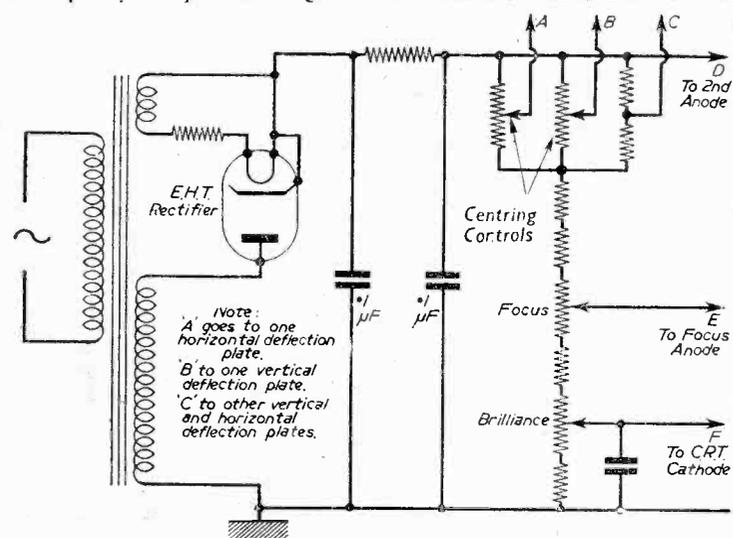


Fig. 11.—An A.C. mains-fed EHT supply.

type. Condensers and resistors from the sync separator to the line and frame circuits should be carefully checked. In the case of condensers, replacement is the best method, but be careful to use the correct value, as given in the service sheet. Do not forget to take voltages on the sync separator valve electrodes. It should be realised that faulty synchronisation of frame and line timebases does not necessarily mean that the trouble lies in the sync stage. Check the timebase circuits first. If, having checked the timebase circuits and the sync stage, trouble is still apparent, then it can possibly be due to compression or limiting of the sync pulses. This can be caused by a fault in the set anywhere in front of the sync stage. A faulty valve, a defective A.G.C. system, too strong a signal or any change in component values can be responsible.

Sets With Faulty or Poor Picture

Faults of this description can be in many cases due to the video amplifier circuit. Fig. 14 gives a typical video amplifier stage.

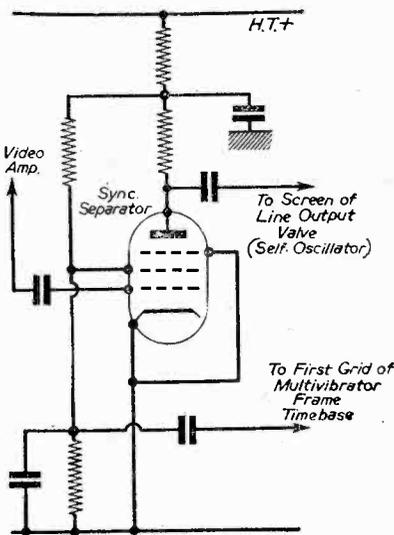


Fig. 13.—Another type of sync separator.

(To be continued)

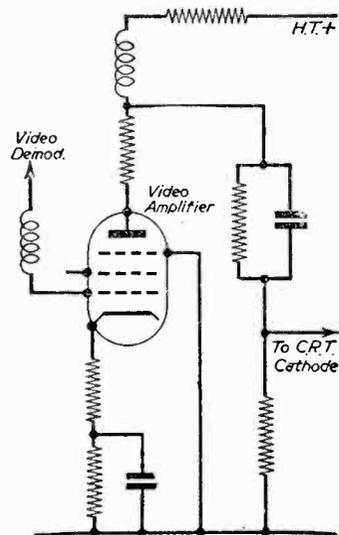


Fig. 44.—A typical video output stage.

DON'T STUMBLE IN THE DARK



Install 2-way switches. Our outfit comprises: 30 yards Multi-core cable, two 2-way switches, two wood blocks. Full instructions—19/6 each (post and insurance 2/6).

MAINS-MINI



Uses high-efficiency coils, covers long and medium wavebands and fits into the neat white or brown bakelite cabinet—limited quantity only. All the parts, including cabinet, valves, in fact everything, £4.10.0, plus 4/6 post & ins. Constructional data free with the parts, or available separately 1/6.

DON'T BE CAUGHT LIKE THIS




CAR STARTER CHARGER KIT

All parts to build 6- and 12-volt charger which can be connected to a "flat" battery and will enable the car to be started instantly. Kit comprising the following:

- Mains transformer..... 22/6
 - 5-amp. rectifier..... 17/6
 - Regulator Stud Switch..... 3/6
 - Resistance Wire..... 2/-
 - Resistance Former..... 2/6
 - Mains on/off Switch..... 2/6
 - 0.5 amp. Moving Coil Meter... 12/6
 - Construction Data..... 1/6
- or if bought all together price is 52/6, plus 3/6 post and packings.

Waterproof P.V.C. covered Heating Element, 16 ohms per foot. 1/- per yard.

BUILD THIS IN AN EVENING

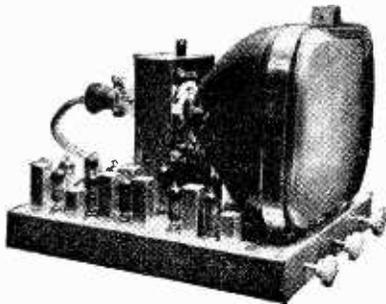

Undoubtedly the most up-to-date television for the home constructor. You can build it in an evening and the set when finished will be equal to a factory-made equivalent. What other constructor T.V. has all these features?

- ★ No technical knowledge required.
- ★ All miniature valves.
- ★ Metal rectifier.
- ★ Turret Tuner.
- ★ 12-channel circuitry.
- ★ Multi-vibrator time bases.
- ★ Ferruxcube, E.H.T. and scan coils.
- ★ 34.38 Mc's I.F.
- ★ Suitable for any modern 12, 14 or 17" tube.

The building cost (less tube) is only £20.10.0, plus 10/- carriage and insurance, or 4/6 deposit & 12 monthly payments of 27/-. All parts guaranteed 12 months. Full information and data, price 3/6.

THIS MONTH'S SNIP

TAPE DECK.—Made by the famous Truvox Company. This contains exactly the same essentials as the current model. Only the styling is different. It also takes the stereophonic head. Specification: 3 B.T.H. shaded pole motors with silent friction drive eliminating wow and flutter. Push-button controls, electrically and mechanically interlocked. Patented electric type push-button controlled brake. Tape loading on the drop-in principle, accommodation for reels of 7" diameter. Tracking sense to British and American standards. Playing times: up to 3 hours with L.P. Tape or 2 hours with Standard Tapes. Two tracks side by side with safety gap. Positive Azimuth adjustment of Record/Player head. High Impedance Heads. Overall size 14" x 12" x 5" approx. 120 only of these fine decks offered at non-repeatable price of £17.10.0 or £3.10.0 down and eight monthly payments of £2. Non-callers add 10/- carriage and insurance.

MULLARD AMPLIFIER "510"

YOURS FOR 30/- DOWN



A Quality Amplifier designed by Mullard. Power output exceeds 10 watts. Frequency response almost flat from 10 to 20,000 C.P.S. For use with the Aeos "Hi G" and other good pick-ups. Made up and ready to work. £12.10.0 or £1.10.0 down and 8 payments of £1.10.0, plus 10/- carriage and insurance.

MULLARD PRE-AMPLIFIER

For extra gain and fidelity this unit gives ideal results. It is arranged to plug into the amplifier and has two switches to provide compensation of radio, microphone, L.P., and 78 records. Complete with valve, made up ready to work. £4. Post and insurance 3/6, or 10/- deposit and eight monthly payments of 10/-.

OUR 19/6 COLUMN



THE SKYSEARCHER

This is a 2-valve plus-metal receiver set useful as an educational set for beginners, also makes a fine second set for the bedroom, workshop, etc. All parts, less cabinet, chassis and speaker, 19/6. Post and ins. 2/6. Data free with parts or available separately 1/6. 3-valve battery version also available at the same price.

ALL-MAINS AMPLIFIER



Powerful three-valve Mains amplifier ideal for dances, parties, etc. Complete less chassis, cabinet and speaker (available if required)—data 1/6 (free with parts). Price 19/6, plus 2/6 post and insurance.

"CHIME LITE" 19/6



It is a hall light as well as a double chime and you can make it in a couple of evenings for the total cost of only 19/6 including instructions, post 2/-—data available separately price 2/-.

Simple Transistor Kit



Makes ideal bedroom radio, uses one transistor and one crystal diode. Complete less case 19/6, case 5/- extra, post and ins., 1/6.

A.C./D.C. Multimeter Kit

Measures A.C./D.C. volts and ohms. All the essential parts including metal case, 2in. moving coil meter, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions. price 19/6 plus 19 post and insurance.



ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to E.P.E., Ltd., Dept. 5, 66, Grove Road, Eastbourne.


Personal shoppers to one of these addresses, please.

266, London Road, Crystal Palace, London S.E.19
Phone: CRO 6558
Half day, Wednesday

42-46, Windmill Hill, Rush, Bucks.
Phone: RU1SLIP 5780
Half day, Wednesday

152-3, Fleet Street, E.C.4.
Phone: FLEET 2833
Half day, Saturday

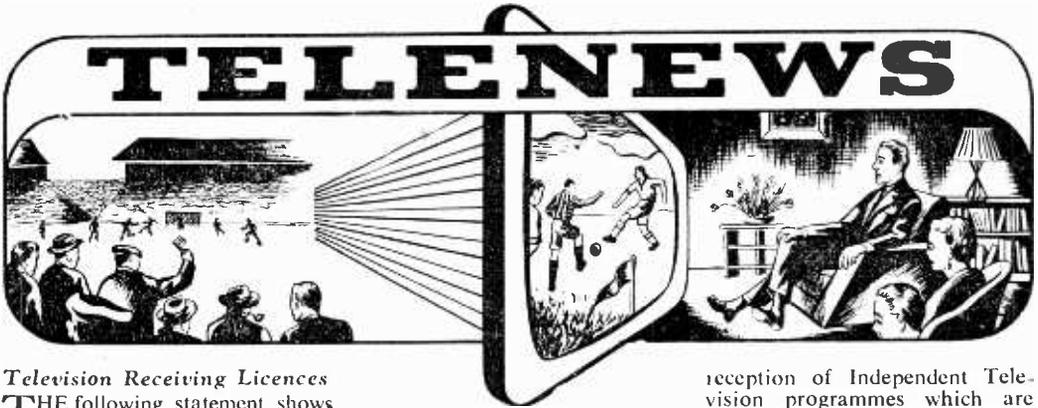29, Stroud Green Road, Finsbury Park, N.4.
Phone: ARChway 1049
Half day, Thursday



Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of September, 1957, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,516,535
Home Counties	889,325
Midland	1,212,406
North Eastern	1,170,335
North Western	1,048,311
South Western	548,611
Wales and Border Counties	415,574
Total England and Wales	6,801,097
Scotland	526,015
Northern Ireland	71,073
Grand Total	7,398,185

Television Really Comes of Age

WHILE definite figures will not be available until after we go to Press, it is now pretty certain that the number of combined sound and TV-Wireless licences now exceeds that for sound radio only.

In 1935 when the figure for sound receiving licences reached 7¼ million—approximately the same as the number of licences for combined sound and television now issued—there was no licence for television. Introduced on June 1st, 1946, for the post-war opening of the service from Alexandra Palace, there were then only 1,343 TV licences.

In little over 11 years, however, users of both sound and television have caught up with sound-only enthusiasts, who took 13 years—1922 to 1935—to reach the 7¼ million figure.

Chillerton Down, Isle of Wight
CHILLERTON DOWN, on the Isle of Wight, I.T.A. station will operate on Channel

11, and the precise frequencies will be: vision 204.75 Mc/s, sound 201.25 Mc/s. Signals will be vertically polarised.

This station will serve an area roughly semi-circular in shape stretching along its base from Weymouth through Ventnor to Brighton and reaching to Newbury in the north. Lying in the service area will be Hampshire and the Isle of Wight, almost the whole of Dorset, West Sussex, the south-eastern part of Wiltshire and the south-western part of Surrey. The Independent Television Authority hopes to bring the station into service next summer.

An approach road to the site is now under construction and the Authority plans to begin work on the building in October.


I.T.A. in the West

FROM September 2nd onwards low power test signals have been radiated from the site of the Independent Television Authority's new transmitting station at St. Hilary in Glamorganshire. The purpose of these test signals is to enable viewers to have their sets adjusted and Channel 10 aerials fitted in time for the

reception of Independent Television programmes which are planned to start before Christmas. Lying in the area which will be served by St. Hilary when it is operating on full power will be the South of Pembrokeshire, the South of Carmarthenshire, Glamorganshire, Monmouthshire, the South of Gloucestershire, Somerset and the North of Devonshire.

Construction work on the permanent station is proceeding extremely rapidly. The mast has been completed and transmission equipment is now being installed.

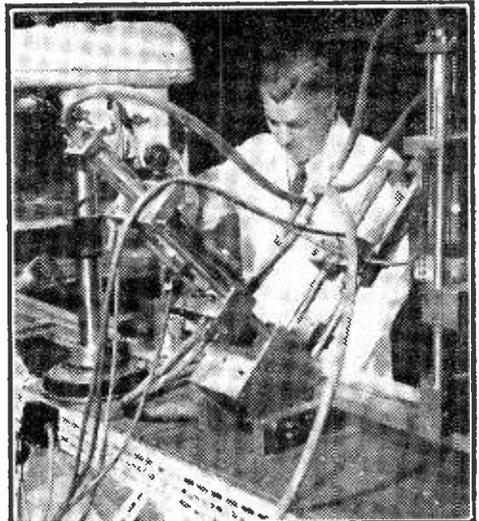The St. Hilary transmitting station will be the sixth to be opened by the Independent Television Authority and test transmission have commenced.



This picture of a J. Beam Aerials operative making aerials was exhibited at the exhibition of professional photographers recently.

Transmissions from Black Hill
SINCE the start of high power test transmissions from the I.T.A.'s Black Hill station, it has been found that in some localities outside the primary service area a strong horizontally polarised signal has been received. In consequence, some dealers have been able to secure better pictures by mounting aerials horizontally instead of vertically.

The cause of this unforeseen

date originally announced as December 17th.

This delay is due to unforeseen technical defects in the aerial system which would lead to inferior reception in some areas so that the general technical quality of the service would not be good enough.

Hungary Makes O.B. TV Unit

HUNGARY'S first outside broadcast television unit has been completed in the Postal

to link it with studios in various parts of Budapest. It can also be used for long-distance calls to the studios from outside of the capital.

Peterborough and Orkney Stations

NEW BBC television stations are to be built, with the approval of the Postmaster-General, near Peterborough and in Orkney. The Orkney station will in addition carry sound broadcasts on V.H.F.

The Peterborough station will serve about 11,000 people and the Orkney station 30,000. No dates can yet be given for the completion of the stations.


Delay at Black Hill

HIGH power test transmissions from the Black Hill (Central Scotland) transmitting station of the Independent Television Authority were delayed.

Due to weather conditions, difficulties occurred in making the final adjustments to the transmitting aerial.

Radio Show, 1958

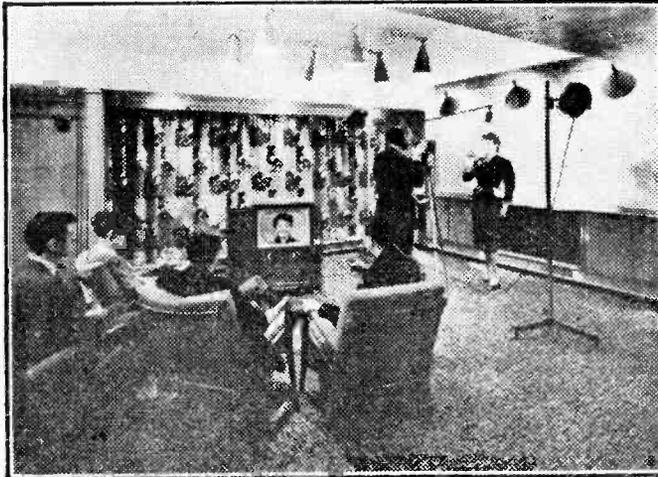THE RADIO INDUSTRY COUNCIL announces that the 25th National Radio and Television Exhibition will be held at Earls Court, London, from Wednesday, August 27th, to Saturday, September 6th, with a preview on Tuesday, August 26th.



The producer and his staff watching a rehearsal for an advertising TV system which has been recently introduced.

development is now being investigated and it is hoped that the trouble can soon be corrected in order that a uniform vertically polarised signal will be available throughout the service area.

In these circumstances dealers are strongly advised to proceed with their installation work in the normal way, mounting all aerials vertically, and deferring installation where the vertical signal is not at present sufficient for reasonable reception.

I.T.A. Opening Delay

THE Independent Television Authority regrets to announce that the opening of its transmissions in South Wales and the West must be postponed to a date now expected to be between the middle of January and the middle of February, 1958, involving a delay of four to eight weeks in the opening

Research Institute. Plans were drawn up by 15 young engineers who experimented until every piece of the unit was made in Hungary.

An institute spokesman told the newspaper *Népszavart*: "After trial tests the unit is operating to perfection and surpasses the one bought from Britain last year from many points of view. The Hungarian-made cameras proved to be faultless."

The television car is equipped with a telephone

LAST-MINUTE CHRISTMAS GIFTS

There's still time to send your friends who are TV enthusiasts the ideal Christmas gift . . . a year's subscription for PRACTICAL TELEVISION. All through the year your gift will bring them repeated pleasure . . . every new issue, reminding them of your good wishes.

But hurry! You must send now to make sure that first copies arrive in time for Christmas. Simply send your friends' names and addresses, together with your own, and remittance to cover each subscription to Subscription Manager (G.2), George Newnes, Ltd., Tower House, Southampton Street, Strand, London, W.C.2. An attractive Christmas Greetings Card will be sent in your name to announce each gift.*

***RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES): U.K. 19s. 0d., OVERSEAS 17s. 6d., CANADA 16s. 0d., U.S. \$2.50.**

C.R.T. ISOLATION TRANSFORMER
 Type A. Low leakage windings. Ratio 1:1.25 giving a 25% boost on secondary.
 2 v. 10/8; 4 v. 10/8; 6.3 v. 10/8; 10.8 v. 10/8; 13.3 v. 10/8.
 Ditto with mains primaries, 12/8 each.
 Type B. Mains input 220/240 volts. Full Output 2, 4, 6.3, 7.3, 10 and 13 volts. Input has two taps which increase output volts by 25% and 50% respectively. Low capacity suitable for most Cathode Ray Tubes, 22/0. Ditto for 6 v. C.R. Tubes only, 17/8.
 Type C. Low capacity wound transformer for use with 2 volt Tubes with falling emission. Input 220, 240 volts. Output 2-24/24/23/3 volts at 2 amps. With Tag No. 17, 6 each.
NOTE.—It is essential to use mains primary types with T.V. receivers having series-connected heaters.

TRIMMERS. Ceramic, 30, 50, 70 pf., 8d.; 100 pf., 1/3; 250 pf., 1/6; 500 pf., 750 pf., 1/1.
RESISTORS. Preferred values, 10 ohms to 10 meg. 1 v. 4d.; 1 v., 4d.; 1 v., 6d.; 1 v., 8d.; 2 v., 1 s. 7.
HIGH STABILITY. 1 w., 1 s., 2 s. Preferred values 100 ohms to 10 meg. 6d.
WIRE-WOUND POT. 13 10 watt 25 ohms—19,000 ohms 1/6
 15 watt 2
 15,000 ohms—50,000 ohms, 5 w., 1 s., 1/9; 10 w., 2 s.

1/2 6 PURETONE RECORDING TAPE
 1,200 ft. on standard 7" Metal reels—Spools 5" metal, 1/6; 7" metal, 2/3—FERROVOICE 1,200ft. Plastic Tape 25/- on Plastic Spools.


Q.P. TRANSFORMERS. Heavy Duty 50 mA., 4.8. Multitap, push-pull, 7/8. Miniature, 2s.4, etc. 4.8.
L.F. CHOKES 15-10 H. 60/65 mA., 5 v., 10 H. 80 mA., 8/8; 10 H. 150 mA., 12/6.
MAINS TRANS. 350-0-350, 80 mA., 6.3 v. tapped 4 v., 4 w., 5 v. tapped 4 v., 2 s., ditto 250-0-250, 22.6. Bargain 200-0-200 mA., 6 v., 4 s., 4 v., 2 s., 15 v.
HEATER TRANS. Tapped prim., 200, 250 v. 6.3 v. 14 amp., 7/6; tapped sec., 2, 4, 6.3 v., 14 amp., 8/6; prim., 230 v., Sec. 6.3 v. 3 amp., 10/6.
ALADDIN FORMERS and core, 10 in., 8d.; 1 in., 10d. 0.3 in. FORMER S5987/8 and Cans TV1, 12, 3 in., 8d. 0.3 in. and 1 in., 50 v., 1 1/2 in., 2 s. each, with core.
TYANO.—Midget Soldering Iron, 200/220 v. or 220/250 v., 18/9. Solon Instrument Iron, 24/-.
MAINS DROPPERS. 3 in. x 1 1/2 in. Adj. Sliders, 3 amp., 750 ohms, 4/3. 2 amp., 1,000 ohms, 4/3.
LINE CORD. 5 amp., 60 ohms per foot, 2 amp., 100 ohms per foot, 2-way, 6d. per foot, 3-way, 7d. per foot.
LOUDSPEAKER, P.M. 3 OHM. 2 1/2 in., square, 17/6. 5 in. Goodman, 17/6. 7 in. x 4 in. Goodman, 21/-. 3 1/2 in. square, Elac., 21/-. 8 in. Plessey, 19/6. 8 in. Goodman, 18/6. 10 in. R. & A., 30/-. T-81 Tweeter, 120/65 mA., 8/8. 3 s. Plessey, 30/-. 8 in. M.E. 2.5k field, tapped O.P. trans., 24/6. 15 ohm Plessey 10 wt. 12 in. with Tweeter, 97/6.
CRYSTAL DIODE (G.E.C. 2/-). GEX34, 4/-.
HIGH RESISTANCE PHONES. 4,000 ohms, 16/8 pr. **MIKE TRANS.** 50, 1.5, 2, 3, 4, 5, 10, 15, 20, 30, 40, 50, 100, 200, 500 pf., 1 s. 10, 15, 20, 30, 40, 50, 100, 200, 500 pf., 1 s.
SWITCH CLEANER Fluid, spirit spray, 4/3 tin.
TWIN GANG TUNING CONDENSERS. 365 pf. miniature 1 in. x 1 1/2 in., 10/-, .0005 Standard with trimmers, 9/-; less trimmers, 8/-; midget, 7/6; single, 50 pF., 2/6; 50 pF., 7/6; 150 pF., 8/6; solid dielectric, 100, 300 pF., 3/6.
SPEAKER FRET. Expanded Metal Silver, 16 1/2 in. x 9 1/2 in., 2/- each.
GOLD COLIC. 17 in. x 2 1/2 in., 5/-; 25 in. x 2 1/2 in., 10/-.
Tyran 41. 6 in. wide, 10/- ft.; 2 1/2 in. wide, 5/- ft.

All Boxed VALVES New & Guaranteed

1R5	8/6	6K8	8/6	6B91	8/6	61148	1/6
1A5	8/6	6H5	10/6	6E33	3/6	HVC80	8/6
1Y3	8/6	6Q7	10/6	6E1C	10/6		12/6
2X2	3/6	68A7	7/6	6E7F80	8/6	HVR2A	7/6
3A4	8/6	68E7	8/6	6ECC4	12/6	MU14	10/6
3V4	8/6	6V80	7/6	6ECP80	10/6	PA1	6/6
5C4	8/6	6V80GT	8/6	6ECP82	10/6	PCP84	12/6
6X3	8/6	6X3	7/6	6E4H42	10/6	PCP80	10/6
6Z4	10/6	6X3	7/6	6ECL80	8/6	PCP82	10/6
6AM6	8/6	12A6	7/6	6ECL82	12/6	PCP82L	10/6
6BR8	5/6	12AH8	10/6	6ECP39	7/6	PCN25	6/6
6BE6	7/6	12AT7	10/6	6E34	10/6	PL82	10/6
6BH6	10/6	12AX7	10/6	6E30	5/6	PSY8	10/6
6BW4	8/6	12AX7	10/6	6E60P	PSY8	10/6	
6BW7	8/6	12BE6	10/6	6E7F50	5/6	PSY8	10/6
6C16	10/6	12BH7	10/6	6E7F50	5/6	SP61	5/6
6D6	7/6	12K7	8/6	6E7F80	10/6	UB41	8/6
6E6	7/6	12Q7	8/6	6E7F92	5/6	UC42	8/6
6H5	3/6	6Z574	10/6	6E132	5/6	UF41	8/6
6J5	6/6			6E184	5/6	UL41	8/6
6J6	7/6	6J4	1/6	6E731	11/6	UY11	8/6
6J7	8/6	6J4	1/6	6E731	11/6	UY11	8/6
6K6	6/6	EA50	1/6	6E740	10/6	U22	10/6
6K7	5/6	EA8C80	8/6	E281	11/6	X79	10/6

A MERRY CHRISTMAS TO ALL READERS OF PRACTICAL TELEVISION
 Please post Christmas orders by Wednesday 17th December.

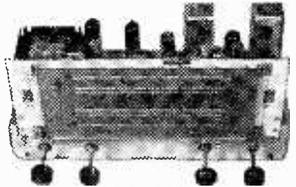RADIO COMPONENT SPECIALISTS
 337 WHITEHORSE RD., WEST CROYDON
 Shop closed 25th, 26th, 27th December.
 OPEN ALL DAY (Wed. 1 p.m.) Catalogue 6d.
 Tel. THO 1665. Buses 133 or 63 pass door. 48-hour postal services. P.&P. 1/-, or 2/- post free. (Export Extra.) C.O.D. Service 1/6



1557 RADIOGRAM CHASSIS
 THREE WAVEBANDS. FIVE VALVES
 S.W. 16 m.—50 m. LAF847 MULLARD
 M.W. 200 m.—550 m. E1424, EF41, EB41,
 L.W. 800 m.—2,000 m. EL41, EZ40,
 12 month guarantee.
 A.C. 200, 250 v. 4-way Switch; Short-Medium-
 Long-Gang. A.V.C. and Negative feedback
 4.2 watts. Chassis 12 1/2 x 5 1/2 x 2 1/2 in. Glass Dial
 10 x 4 1/2 in., horizontal or vertical available.
 2 Pilot Lamps, Four Knobs, Walnut or Ivory.
 Agreed and calibrated. Chassis isolated from
 mains.

10 gns. Carr. & Ins. 4/6.
 TERMS: Deposit £5.50 and six monthly
 payments of £1.
MATCHED SPEAKERS FOR ABOVE CHASSIS.
 8 in., 17/6; 10 in., 25/-; 12 in., 30/-.

RECOMMENDED FOR ABOVE CHASSIS
 ★ COLLARO ★
HIGH-FIDELITY AUTOCHANGER
 1957 Model RC456
 7 in., 10 in., 12 in. Records
 16, 33, 45, 79 r.p.m.
 4 SPEEDS—10 RECORDS
 With Studio "A" pick-up
BRAND NEW IN MAKER'S BOXES

OUR PRICE £9.15.0 post free
TERMS: Deposit £5.50 and six
 monthly payments of £1.
 Space required 14 in. x 12 in. 5 in.
 above and 3 in. below. Cut Out board, 6/-.

GARRARD 4-SPEED RECORD CHANGERS RC120/4H 1957 MODELS
 Brand new and fully guaranteed 12 months.

AUDIO PERFECTION
 Designed to play 16, 33, 45, 79 r.p.m. Records.
 7 in., 10 in., 12 in. Lightweight Xal pick-up,
 turnover head, two separate sapphire styli,
 for Standard and L.P., each plays 2,000 records
 Voltage 200 250 A.C.

OUR PRICE £10.15.0 each. Post Free.
 TERMS: Deposit £6 and 6 monthly payments
 of £1. Space required 14 in. x 12 in., 5 in.
 above and 3 in. below. Cut Out board, 6/-.

AMPLIFIER—RECORD PLAYER CABINETS.
 Cabinet size 18 1/2 x 13 1/2 in. 8 1/2 in. with
 motor board 14 x 12 1/2 in., £3.3.0, post 5/-.

ALUMINIUM CHASSIS. 18 s.w.g. multi-holed
 with 4 sides, riveted corners and lattice fixing
 holes, 2 1/2 in. sides, 7 x 4 in., 4.6; 3 x 6 in., 5/9;
 1 1/2 x 7 in., 6/8; 1 1/2 x 9 in., 8/6; 1 1/2 x 11 in., 10/6;
 1 1/2 x 14 in., 12/6. 18 x 6 x 3 in., 16/6.

TRANSISTORS. Audio, 10/-, R.F. 2/6 Mols.
 21 - Mullard OC71, 20/-.

SUPHRET COIL PACK. 27/8. Miniature
 size 2 1/2 in. x 2 in. x 1 1/2 in. High "Q" Dust
 coated Coils. Short, Medium, Long, Gang
 switching. Single hole fixing with connection
 diagram and circuit. 465 Kc s.f.P.

COLLARO. 4-speed Motor and Turntable
 with selecting switch for 16, 33, 45, 79
 r.p.m. records, 200-250 v. A.C. 50 cps. Also
HIGH FIDELITY Lightweight Pick-up Accu
 Xtal turnover head, separate sapphire styli
 or L.P. and Standard records. **SPECIAL**
OFFER THE TWO! £4.12.6, post 2/6.
 Cut Out Board, 14 x 12 1/2 in., 6/-.

SUITABLE AMPLIFIER-PLAYER CABINET.
 Ready cut out for above. 45/-.

CRYSTAL MIKE INSERT by Acos, precision
 engineered, size only 1 1/2 x 3/16 in. Bargain
 Price 6/6. No transformer required.

CHAMPION VHF (FM) TUNER,
 88-96 mc/s.
 5 Mullard valves and superb tuning head.
 Marsson and cream receiver styled cabinet
 12 x 6 x 6 in. Features: This is a self-powered
 200, 250 v. A.C. VHF (FM) Adaptor with
 operating and servicing data and a screened
 lead for connection to pick-up sockets of any
 radio, radiogram, or amplifier.
 Brand new with 12 months guarantee. List
 price, 16 gns. Our price, **10 gns.**, carr. 4/6.

Volume Controls 80 ohm **COAX**
 Long spindles. Guaranteed spaced Polyt-
 ethene year. Midget. 100,000 ohms to 2 Meg.
 No Sw. S.P.S.W. D.P.S.W. 9d. yd.
 3 - 4 - 4 - 9
 Linear or Log Tracks. Fringe quality, 1/6 yd.

COAX PLUGS ... 1 - DOUBLE SOCKET 1 yd
SOCKETS ... 1 - OUTLET BOXES ... 4/6
BALANCED TWIN FEEDER yd. 6d. 80 ohms yd.
DITTO SCREENED per yd. 1 - 80 ohms yd.
WIRE-WOUND POTS. 3 WATT. Pre-Ket Min.
 T.V. Type. All values 25 ohms to 30 K, 3 - ca.
 50 K, 4 - Carbon 50 K to 2 m., 3 -)
WIRE-WOUND 4 WATT. Pots 2 1/2 in. Spindle.
 Value, 100 ohms to 50 K, 5/6; 100 K, 6/6.
CONDENSERS. Neon stacks, 400 mfd., 5 v.
 T.C.C. 5/6; Ditto, 20 kV, 8/6; 100 pf. to 500 pf.
 Micas 6d.; Tubular 500 v., .001 to .01 mfd., 8d.;
 .05, .1, 1 - 25, 1.8; .5 350 v., 1/9; 1.350 v., 9d.;
 3.600 v., 1/3; .1 mfd., 2,000 volts, 3/6.
CERAMIC COND. 500 v., .3 pf. to .01 mfd., 10d.
SILVER MICA CONDENSERS. 10% 5 pf. to 500
 pf., 1 - 600 pf. to 3,000 pf., 1/3. Close tolerance
 (± 1 pF.) 1.5 pF. to 47 pF., 1/6. Ditto, 1% 50 pF.
 to 815 pF., 1/9; 1,000 pf. to 5,000 pF., 2/-.

I.F. TRANSFORMERS 7/6 pair
 465 Kc Suf tuning Miniature Can, 2 1/2 in. x
 1 in. x 1 in. High Q and good bandwidth
 By Pye Radio. Data sheet supplied.
 Wearise M800 If 465 Kc/s 12.6 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES
TUBULAR TUBULAR CAN TYPES
 1 350 v. 2 - 100, 25 v. 2/- 8 + 16,500 v. 5/6
 2 450 v. 2 3/8 + 5,300 v. 4/6 4 + 16,500 v. 6/6
 4 450 v. 2 - 16 + 16,500 v. 25 + 20,450 v. 5/6
 8 450 v. 2 3/8 6/- 32 + 32,350 v. 4/6
 8 500 v. 2 8 CAN TYPES 32 + 32,450 v. 6/6
 16 450 v. 3 8 (4 types) 32, 50 + 20,350 v. 7/-
 16 500 v. 4 16 450 v. 2 600 + 100,350 v. 11/6
 32 450 v. 6 32 350 v. 4/6 100 + 200,275 v. 11/6
 25 25 v. 1/9 64 350 v. 5/6
 50 25 v. 1/4 500 12 v. 3/- 1,000 + 1,000/6 v. 12/6
 50 50 v. 2 - 8 + 16 450 v. 5/- 6/6

**SENTERCEL RECTIFIERS. E.H.T. TYPE FLY-
 BACK VOLTAGES.** K4 25 kV, 5 -; K3/40 32
 K, 4 -; K3/45, 3.5 kV, 2 -; K3/50 4 kV, 8 -;
 K3/100 kV, 14/6. 50 p-amp. voltage, 30% of above.
MAINS TYPE CONTACT COILED 250 v. 50 mA., 8/6;
 250 v., 83 mA., 9/6. COILS Wearise, "P" type, 3 -
 each. Onoid Midget "Q" type adj. dust core, from
 4. All ranges, 12.6. **TELEPHONE COILS.** T.R.F.,
CHARGER TRANSFORMERS. Tapped input 200,
 8/9; M & L, 12/8. T.R.F. COILS A/B 7/- pair.
H.F. CHOKES 2/6. FERRITE ROD 8 in. x 3/8 in. dia.,
 2/6

JASON F.M. TUNER COIL SET. 28/-, H.F. coil,
 aerial coil, Oscillator coil, 2 I.F. trans-
 formers 10.7 Mc/s. Detector transformer and
 heater choke. Circuit book using four 6AM6,
 2/-, J.B. chassis and Dial, 18/6.
 Complete Jason P.M. Kit, £5.15.8.
 With Jason superior calibrated dial, £8.15.0

FULL WAVE BRIDGE SERVO MOTOR RECTIFIERS.
 2, 6 or 12 v. 1 1/2 amp., 8/9 2 amp., 11/3; 4 amp., 17/6.
CHARGER TRANSFORMERS. Tapped input 200,
 250 v. for charging at 2, 6 or 12 v., 1 amp., 15/6;
 2 amp., 17/6; 4 amp., 22/6.
VALVE and T.V. TUBE EQUIV. valves, 5/-,
TOGGLE SWITCHES. S.P. 2 - A.P. 3/6. D.P. D.T. 4 -
WAVECHANGING SWITCHES.
 5 p. 4-way 2 waf. long spindle 6/6
 2 p. 2-way 3 p. 2-way short spindle 2/6
 2 p. 6-way 4 p. 2-way 4 p. 3-way long spindle 3/6
 3 p. 4-way, 1 p. 12-way, long spindle 3/6
VALVE HOLDERS. Fax. Int. Oct. 4d. EF50, EA50,
 6d. B2A, CRT. 1.3. Enc. and Amer. 4, 5, 6, 7, and
 8 pin, 1/2 MOULDED Mazda and Int. Oct. 6d.
 6R7, 8BA, 8B6, 8A, 9d. 87G with can, 1/6.
 VC87, 2/6, 8B6 with can, 2/6. CERAMIC EF50,
 6R7, 8A, Int. Oct. 1/-, 87G with can, 1/9.
 ELACK CRACKLE PAINT, air drying, 3/- tin.

TELEVISION TUBES

MULLARD	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0
COSSOR	12in. £6.10.0	14in. £6.10.0	17in. £8.10.0
EMITRON	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0

MULLARD. 12in. now 6 weeks delivery. All other types ex-stock.

MONTHLY CLEARANCE REDUCTIONS

MAZDA	14in. £5.10.0	17in. £7.0.0
CATHODEON	14in. £6.0.0	17in. £7.0.0

All Tubes plus 12/6 carriage and insurance.

SIX MONTHS' GUARANTEE

Terms to the Trade.

RE-VIEW (LONDON) LTD.

81, HIGH STREET . . . MERTON S.W.19

Telephone : CHERRYWOOD 3255

VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. midget. 1R5, 1S5, 1T4, 3S1, DAF81, DF91, DK91, DL92, DK92, DL94; ANY 1 for 27.6.

1A7GT 12/6	6L18 19/6	CL33 18/9	EP42 10/6	PCL82 10/-
1C5GT 15/6	8Q7GT 9/6	EF50 3/-	PF50 9/6	PCL83 9/6
1H5GT 11/-	6SN7GT 7/6	D77 6/-	SYL 8/6	PEN46 6/6
1N5GT 11/-	6U4GT 11/-	DAC32 11/-	EP55 9/6	PL33 22/-
1R5 8/-	6V6GT 7/-	DAF96 8/6	EP80 8/-	PL81 12/6
1S5 7/6	6Y6GT 7/6	DF33 11/-	EP85 7/6	PL82 9/-
1T4 7/3	6X4 7/-	DF96 8/6	EP88 11/6	PL83 10/6
3Q4 8/-	6X5GT 6/6	DH76 7/6	EP89 9/6	PY80 8/-
3Q5GT 9/6	7B7 8/-	DH77 8/-	EP91 6/-	PY81 8/-
3S4 7/6	7C5 8/-	DK32 12/6	EP92 5/6	PY82 7/-
3V4 8/-	7C8 8/-	DK32 8/-	EL32 5/6	PY83 9/6
5U4G 8/-	7HT 8/-	DK96 9/6	EL33 22/-	PZ30 18/-
5V4G 11/9	7S7 9/-	DL33 9/6	EL41 9/-	SP41 3/6
5Y3GT 7/6	7Y4 8/-	DL35 15/6	EL42 10/6	SP61 3/6
5Z4G 9/6	12AH3 9/6	DL96 8/6	EL44 9/-	U25 12/6
6AB8 7/6	12AT7 8/-	EABC80 7/9	EM34 10/-	U26 2/6
6AK5 4/6	12AU7 7/6	EAF42 10/6	EM80 9/6	U50 7/6
6AL5 6/-	12AXT 8/-	EB91 6/-	EX51 9/9	U76 7/6
6AM5 5/-	12BA6 8/-	EBC33 7/6	EX86 10/6	U78 7/6
6AM6 6/-	12J7GT 10/6	EBC41 9/6	EZ40 7/9	UABC80 9/6
6AQ5 7/6	12K7GT 7/6	EBF80 8/6	EZ41 9/6	UAF42 10/6
6AT6 8/-	12K8GT 14/-	EBF89 9/-	EZ89 7/6	UBC41 8/6
6BA6 7/6	12Q7GT 7/6	ECB31 8/-	EZ81 9/6	UBR90 9/-
6BE6 7/6	12Z3 7/6	ECC82 7/6	FWA500 13/6	UCH42 8/-
6BJ6 7/-	25L6GT 9/-	ECC83 8/-	GZ32 11/6	UP41 8/-
6BR7 8/6	25Z4G 9/6	ECC84 10/6	KT33C 8/6	UP89 10/-
6BW6 7/6	25Z6GT 9/6	ECC85 9/6	KT41 6/6	UT41 8/6
6BW7 9/6	35L6GT 9/6	ECF80 10/6	KT63 6/6	UL84 9/-
6CH6 7/-	35Z3 9/6	ECF82 11/-	KTW61 6/-	UY21 15/6
6F1 15/-	35Z4GT 7/6	ECH21 14/9	KTW61 6/-	UY41 7/6
6F6G 6/6	35Z5GT 9/-	ECH35 9/6	MH1 6/-	UY85 7/-
6F12 6/-	43 13/6	ECH42 8/6	MU14 8/6	VP41 7/-
6F13 13/-	50L6GT 8/6	ECH61 8/6	N18 8/-	VP1321 21/-
6F15 14/9	50L8GT 8/6	ECL80 8/6	N78 11/6	W76 7/6
6J6 5/6	AC/TP 20/-	EF37A 8/6	PCC84 8/-	W77 5/6
6K7G 4/6	ACZ1 11/6	EF39 6/-	PCC80 10/6	W77 5/6
6K7GT 6/-	B36 20/-	EF41 9/6	PCP82 10/6	Y83 6/-
6K8G 7/9				Z77 6/-

Postage 6d. per valve extra.

Any Parcel Insured Against Damage In Transit 6d. Extra.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587

JASON FM SWITCHED TUNERS

All BBC Programmes at the turn of a switch **MERCURY KIT.** Includes front-end unit already built and aligned. **£9.19.0** Post Free.

Credit Terms : Deposit **£1.10.0** and seven monthly payments of **£1.7.0.**

Instruction Book 2/3 post free. Included in kit. Fully detailed price list free.

PREFECT TUNER. A ready-built unit. Less power supply. **£15.12.6.** Credit Terms : Deposit **£2.4.6** and seven monthly payments of **£2.2.0.** Illustrated leaflet free.

Both these tuners incorporate a good A.F.C. system which ensures freedom from drift.

NEW AVO MULTIMINOR

A brand new test instrument at a very attractive price. A.C. and D.C. Volts. D.C. Current. Two ohms ranges. Movement is 100 microamps (10,000 ohms per volt). **£9.10.0.** Credit Terms : Deposit **£1.8.0** and seven monthly payments of **£1.6.0.** Illustrated leaflet available.

WATTS RADIO (Mail Orders), LTD.,
54, Church Street, Weybridge, Surrey.

Telephone : Weybridge 4556.

PLEASE NOTE : Post orders only to this address.



UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

RIVERSIDE LIGHTING

THE fine new lighting equipment at the BBC's Riverside studios has been admired by all the I.T.A. engineers, especially the new lightweight 1,000 watt lighting units by G.E.C., which weigh only 56lb. each as compared with the more normal weight of about 84lb. The ease with which these lights can be manipulated mechanically has surprised everyone. The amount of capital invested by the BBC in TV premises and equipment must be enormous. The I.T.A. companies now have plenty of money coming in, and both their producers and engineers look with envy at the plushy BBC facilities. Let us hope that this envy doesn't lead to rashness. Pounds can be profitably invested in Personalities as well as Premises.

THE DISTORTION DRUG

THESE Hi-Fi demonstrations of sound radio and records do bring you down to earth and make you realise the shortcomings of your sound radio. Time marches on and valves get tired, but so slowly that one does not notice the slow deterioration in quality. In fact, one becomes drugged to accept quite serious distortion. The same applies to TV reproduction, unless one makes regular use of the transmitted test cards. The BBC clock is a constant reminder of horizontal or vertical egg-shaped distortions, but even these tend to become accepted. When I visit friends' houses and see their TV in operation, I am often shocked by the obvious distortions which are quite happily tolerated. Constant fiddling with the controls—"meggling," they call it in Lancashire—is apt to annoy one's family. But they should be trained to accept at least part of one evening a month for devoting to a routine check up.

"THE PIER"

A.B.C.'s Armchair Theatre has not had a very even run of plays up to now, but surely the most creaky armchair it has ever turned out was *The Pier*. The producer and writer of this play tried to put over a story about Teddy boys (and girls) with a background of a seaside resort and its pier. Presented with a new style of production technique. Breaking almost every rule of theatrical, film and television conventions, the continuity of *The Pier* jerked inconsequentially from scene to scene, scattering close-ups without meaning amidst a farrago of partially inaudible dialogue. If

pretentious nonsense of this kind qualifies for recognition as "new art," then I will be proud to call myself a Philistine! Still, A.B.C.-television deserves a pat on the back for daring to experiment. Even the best of experimental rockets sometimes turns out to be a damp squib.

THOSE ANGRY YOUNG MEN

I HAVE an idea that A.B.C.-television intended *The Pier* to be another offering in the idiom of the angry young men, who are the current symptoms of indigestion in modern art. I suppose that 1957 will go down in history as



Behind the scenes at a TV broadcast. Note the microphone arrangements, and the orchestra being directed by Eric Robinson who follows the singer through headphones.

the year when the Russian satellite and the angry young men of the British theatre both started bleeping. John Osborne set the ball rolling with his provocative play, *Look Back in Anger*, which achieved a great deal of success through the shock effect of its wild attacks upon conventions, traditions and constitutions. Anger being contagious amongst authors, especially when it pays off well, there has been something of a spate of angry young men frantically looking for targets to aim at in their plays for theatre, television and films. Come to think of it, Gilbert Harding must really have started the "anger" cult, with Malcolm Muggeridge following him up with his own special style of attack. Both achieved immediate public attention when their anger was assisted by the combined sound-and-sight impact of television. Fortunately, television has a way of dealing with such repetitions of exhibitionism. The wiser ones, like Gilbert Harding, modify or vary their techniques before the television viewing public gets too angry. I may be wrong, but I have formed the opinion that the mass audience television now commands has no real liking for irresponsible intellectuals. The advertisers on I.T.A. certainly don't love them!

COMMERCIALS IN THE WEST

IT was a good idea to invite potential advertisers on the T.W.W. channel to a preview of various types of filmed commercial, local and national, which will be transmitted from the I.T.A. station at St. Hilary Down. With a probable viewing public of three million, the T.W.W. organisation claims that the relative prices to be charged for advertising space are lower than any other I.T.A. programme contractor. But a friend who was present at the preview, which was held at a local cinema, tell me that the ideas and execution of many of the local advertising commercials was poor and amateurish, not in the same street as some of the nationally advertised products. Still, the local men will soon settle down to work, first to acquire experience in the difficult art of animation draughts-

manship and then to find the ideas which catch public attention. Have you noticed the growing importance of "character" voices in television advertising? I think it was the husky cockney voice of the "one for the—er—pot" tea advertisement which started this craze.

TECHNAMATION

THE latest gadget for putting over animated diagrams clearly, simply and cheaply (it is claimed) is the Technamation system, recently imported from America. This is a mechanical device in which several layers of clear plastic material can be moved separately. Each plastic sheet carries a part of the diagram to be animated. The mechanical movements can be pre-set. Apparently Technamation scored a big success on the Columbia Broadcasting system when it was used with great effect to demonstrate the working of an automobile suspension system. It sounds to me to be a wonderful toy, with immense possibilities in the specialised fields of machinery demonstrations or any kind of repetitive movement. Makers of commercials might find this useful.

MAGNETIC PICTURE RECORDING

PROGRESS continues to be made in U.S.A. with the recording of television pictures on magnetic tape, which is now known as "Video Tape Recording" or V.T.R. V.T.R. machines have been in regular operation on the Columbia Broadcasting system since November, 1956. Valuable experience has been gained in their operation, which, to date, has shown little or no economy as compared with telerecording or, as they call it in U.S.A., Kinescoping. The Ampex video tape recorders scan the tape with four heads, and sixteen television lines are recorded for each sweep of a head across the tape. Since the scanning lines are interlaced, a total of 32 lines per picture field are affected when one head or its associated amplifiers goes out of adjustment. It has been found almost essential to reserve the particular set of heads used for a


recording until that recording is reproduced. Otherwise, the wear on the heads (if used for other recordings in the meantime) will change the characteristic of the pick-up and give bad distortion when the tape is played off. If the V.T.R. recording is sent elsewhere, the magnetic heads have to go with it. The tape has to be very carefully coated to standards infinitely higher than those which are quite satisfactory for sound recording. Nevertheless, steady improvements are being made and already some excellent results have been obtained by Columbia in their regular programme schedules. The V.T.R. system is used for the time delay of a programme for different time zones from coast to coast, and there is no doubt that it will eventually supersede the telefilm recording methods, when used within the same organisation. For picture recordings to be exchanged between networks, or exported abroad, telefilm recording is likely to be used for many years to come.

SOUND QUALITY

ON many occasions I have mentioned the question of poor sound quality on television plays, the I.T.A. companies being the principal offenders. Plays or spectacles from the television theatres, such as the Wood Green Empire (A-T.V.) or the Palace, Chelsea (Granada), often suffer on the sound side when the local loudspeakers for the audience in the auditorium are turned up slightly too high, on the verge of oscillation through feed back. This is a case where an acoustic sound delay system such as that developed by B.T.H. would help matters, both for the transmitted sound quality and for the intelligibility on the auditorium loudspeakers. An acoustic or electronic delay system is adjusted critically so that the sound on the local loudspeaker synchronises with the arrival of the same sound through the air from the stage. In a very large theatre this delay might be half a second for some distant loudspeakers, or even more for a Cathedral. The resultant improvement in intelligibility is quite remarkable.


SIGNAL GENERATOR

Coverage 120 Kc/s-230 Kc/s, 300 Kc/s-600 Kc/s, 900 Kc/s-2.75 Mc/s, 2.75 Mc/s-8.5 Mc/s, 8 Mc/s-28 Mc/s, 16 Mc/s-64 Mc/s, 24 Mc/s-84 Mc/s. Metal case 10in. x 6in. x 4in. Size of scale, 6in. x 3in. 2 valves and resonator. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30 per cent., modulated or unmodulated R.F. output continuously variable 100 milli-volts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%. **£4.13.6** or 34/- deposit and 3 monthly payments 25/-. P. & P. 4/6 extra.

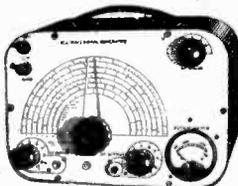


SIGNAL & PATTERN GENERATOR

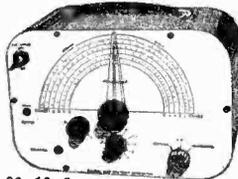Coverage 7 Mc/s-210 Mc/s in five bands, all on fundamentals, slow-motion tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy $\pm 1\%$. A.C. mains 200-250 v. **£6. 19. 6.** Or £2 deposit and 4mthly. pymts of 27/6. P. & P. 5/6.



COMMERCIAL TELEVISION CONVERTER SUITABLE ANY T.V. EXCEPT Philips WITHIN 35 MILES OF I.T.A. TRANSMITTER. ALL CHANNELS NO ALTERATIONS TO SET.

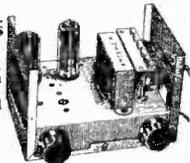Complete with built-in power supply 230-250 v. A.C. mains. Crackle finish case 5in. long, 3in. wide, 4in. high. Incorporating gain control and band switch. Illus. with cover removed. **£3. 19. 6** Plus P. & P. 2/6.



3 element folded dipole I.T.A. loft AERIAL, 15/-. P. & P. 2/-. Co-ax cable, 8d. yard. **H.F. TERMS AVAILABLE**

AC/DC MULTI-METER KIT



Comprising 2in. moving coil meter, scale calibrated in AC DC volts, ohms and milli-amps. Voltage range AC/DC 0-10, 0-100 and 0-500. Milli-amps 0-10, 0-100. Ohms 0-1,000 and 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero setting), two toggle switches, resistors and metal rectifier. In grey hammer finish case. **19/6** Plus P. & P. 1/6.

Point to point wiring diagram 1/-, free with kit.

4 VALVE ALL-DRY SUPERNET PORTABLE KIT

incorporating Ferrite rod aerial Medium and long waves. In grey leatherette. Size 9in. x 7in. x 6in. Valve line-up 174, 1K5, 1S6, 3V4. Complete kit of parts (Gess batteries).

£5. 19. 6 Plus Post & Packing 3/6



COMPLETELY BUILT PORTABLE AMPLIFIER approx. size 6in. x 2in. incorporating 2 valves, contact-cooled metal rectifier, bass and treble lift controls **39/6** Plus P. & P. 3/6. 5in. P.M. SPEAKER & O.P. TRANSFORMER, if purchased with the above. 18/6. Plus P. & P. 1/6.

COLLARO 4-SPEED AUTOMATIC CHANGER

Model 456 (suitable for use with above amplifier). A.C. mains. 200-250 v., turnover crystal head. **£8. 19. 6** Plus Brand new, fully guaranteed. P. & P. 5/-. Or £3 deposit plus P. & P. 5/- and 6 mthly. payments of £1.4.0.

RADIO & T.V. COMPONENTS (Acton) LTD.
23, HIGH STREET, ACTON, LONDON, W.3
GOODS NOT DESPATCHED OUTSIDE U.K.

TRANSISTORS

JUNCTION TYPE P-N-P

(British Manufacture)

RED-SPOT 800 Kc/s Audio Frequency.....	10/-
BLUE-SPOT 1.6 Mc/s Mixer and Frequency Changer.....	15/-
WHITE-SPOT 2.5 Mc/s R.F. and I.F. Amp.....	20/-

All Transistors are Tested and Guaranteed.
N.B. The Red Spot is similar to Mullard OC71.

The New "TRANSISTOR-8"

Push-Pull Portable Superhet **£11/10/-**
Can be built for

This Portable 8 Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set. Simplified construction enables this set to be built easily and quickly into an attractive lightweight cabinet supplied.

TEN STAR FEATURES

- ★ 8 Specially Selected Transistors
 - ★ 250 Milliwatts Output Push-Pull
 - ★ Medium and Long Waves
 - ★ Internal Ferrite Rod Aerial
 - ★ 7x4 Elliptical High Resistance Speaker
 - ★ Drilled Plastic Chassis 8 1/2 x 2 1/2in.
 - ★ Point to Point wiring and practical layout.
 - ★ Economical. Powered by 7 1/2 v. battery
 - ★ Highly sensitive
 - ★ Attractive lightweight contemporary case
- N.B. Pair of Matched OC72's or equiv. Supplied at additional cost of 40/-.**

We can supply all these items including Cabinet for **£11 10/-**. All parts sold separately.

Send for circuit diagrams, assembly data, illustrations and instructions, and full shopping list. **1/6.**

Call and hear demonstration model.

"EAVESDROPPER"

THREE TRANSISTOR POCKET RADIO
(No Aerial or Earth required)

Variable Tuning. Total cost, as specified including Transistors, Transformers, Coils, Condensers and Battery etc. with circuit and plastic case. **77/6** POST FREE

All items sold separately. With single phone. 82/5. With Acos Mike, 90/-, With Min. Hearing Aid 92/6.

MINI-TWO

TWO-TRANSISTOR MINIATURE POCKET RADIO
The smallest Transistor set offered on the market. Variable Tuning, Drilled Chassis, Plastic Case size 3in. x 2in. x 2in., Miniature Hearing Aid, 2 Transistors and all components including 1 1/2 volt battery. Circuits and full practical layout diagrams.

Total Cost **49/6** Complete

TRANSISTOR SIGNAL TRACER
Complete Kit with 2 Transistors, Components, Phones, with Circuit and plastic case. **42/6.**

TRANSISTOR SQUARE WAVE GENERATOR
Complete Kit with 2 Transistors, Components, Circuit and plastic case. **25/-.**

QUARTZ CRYSTALS
5/- each
Send for Lists.

"HOMELIGHT" 2-TRANSISTOR PERSONAL PORTABLE
Variable Tuning
We can supply all components including 2 Transistors Diode, Resistors, Condensers and Miniature Hearing Aid and Plastic Case size 4 1/2 x 2 1/2 x 1 1/2in. and 1 1/2 v. Battery. **FOR 52/6**
All items sold separately

6 v. VIBRATOR PACKS
Output 120 v. 40 mA., 12/6. Brand new.

R.F. 21, 10/-, R.F. 25, 12/6. R.F. 28 25/- Brand new with valves, carr. 2/6.

SEND 6d. STAMPS FOR NEW 1958 28-PAGE CATALOGUE OPEN MONDAY to SAT. 9-5. THURS. 1 o'clock.

HENRY'S RADIO LTD.
5 HARROW ROAD, EDGWARE ROAD, LONDON, W.2
TEL.: PADDINGTON 1008-7

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

SIMPLIFIED SERVICING

SIR,—Articles on testing without elaborate test gear are always interesting, and there is one part of a modern receiver which I think gives rise to more troubles than any other. I refer to the sync. separator so far as it is tied up with the frame timebase. We often hear of bad interlacing, or failure to interlace, but how many amateurs can tell whether the set is interlacing or not? My picture looks as good as most others, yet a friend who comes to see me from time to time always tells me the set is not interlacing. When I ask him how he can tell, all he can say is "You get to know. I can just see that it isn't," and he can't tell me how I can tell. What is the secret, and if it is possible to tell others, how can one really check it and make improvements without a scope or something equally unintelligible to the amateur? Perhaps one of your more experienced readers will lend a helping hand to those of us, and I am sure there are literally hundreds, who are lost in this particular wilderness.—J. Y. TIMMINS (Kensington).

SPECIAL NOTE

Will readers please note that we are unable to supply Service Sheets or Circuits of ex-government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

SOME USEFUL AERIAL DEVICES

SIR,—May I, with all due respect, submit a correction to the article by J. Brown—"Some Useful Aerial Devices"—in your August issue.

The Star Delta Theorem used to find the value of resistor for equally dividing the output of a TV aerial between any number of receivers is as follows:

$$R = Z_a \frac{n-1}{n+1}$$

where Z_a is the impedance of feeder,
 n is the number of outlets.

For 75Ω and 3 outlets:

$$R = 75 \times \frac{2}{4} = 37\Omega \text{ approximately.}$$

For 75Ω and 2 outlets:

$$R = \frac{75}{3} = 25\Omega$$

The circuit would be then as shown.

It is seen quite simply that the impedance presented to us at A, B or C is 75Ω ,

$$\text{i.e., } 25\Omega + \frac{(25\Omega + 75\Omega)}{2}$$

These notes should also apply to the splitter/combiner unit in Fig. 3 of the same article.—D. C. EMMERSON (Northampton).

DABBLERS

SIR.—The recent remarks on "dabblers" were most interesting, especially as I am what might be classed as one. I am a lecturer on

radio at a well-known institute, was a signals officer in the R.A.F. at a fairly high rank during the war, and consider I am fairly well up in most techniques in modern radio and television. Yet, when I wrote to a well-known firm recently for a service manual for *my own* set, not one I was servicing for someone else and for which I might have been accused of doing a service man out of a job, I was told that I couldn't have it—in spite of having listed my qualifications. I agree with the amateur who suggested that manufacturers treat those who ask for a service manual as though they were asking for a working drawing of a guided missile. What is so secret about a set, anyway? The circuit can be traced out by anyone with the slightest knowledge and one's own circuit prepared, but why have to go to all this trouble

when you have spent £60 to £80 on the set? I would venture to suggest that in many cases manufacturers are ashamed of some of the arrangements, not jealous that someone will steal their ideas. I remember, before the war, one judged the quality of a radio set by the size of the service department it had. The bigger the service section, the worse the sets. I think I am correct in saying that one of the big firms had *no* service section at all—the number of faults was so small that local men could put them right and they did not have to go back to the makers. Let us hope that the correspondence and remarks which have been made under this heading will give the manufacturers food for thought and maybe these manuals will be more freely available, even if a slight charge is made for printing, etc.—G. P. RAILTON (Manchester).

SIR.—I am 100 per cent. in agreement with the letter from R. Purdey, of Brighton, in your November issue.

When, as an electrical engineer in a position of responsibility, I have installed complex equipment, a wiring diagram, etc., has been asked for and readily obtained.

Indeed, why not for TV sets, as this writer remarks? £100 spent surely merits full information, if only for the use of the serviceman called in.

I submit that if you must buy, before you buy demand a service sheet. If not given, don't buy and try elsewhere.

I recall a "superior" serviceman attending to my own vacuum cleaner, and impressively grinding out on a megger to prove the said vacuum cleaner was finished. He gleefully anticipated commission on the sale of a new one.

He didn't notice, as I did, a little blue spark busily buzzing brightly to frame. He left sadly as

I refused to buy a new one. The old vacuum cleaner is still singing soothingly.—E. B. DOUGHTY (Bearsden).

SIR,—I, too, would like to add a note or two on "dabblers."

Being a dabbler myself, I have done quite a few jobs on TV sets which have been returned from incompetent radio dealers with small shops and radio service departments. Many of these so-called dealers seem quite unable to diagnose tube faults as such, and when a customer calls him in he blithely tells the customer his tube is done, while all the time all that is required is a new H.T. valve. I do think that the radio dealer should try to be fair in his dealings with a very gullible public, and, to further my argument, I enclose a copy of a letter from an old man of 82 years of age who had similar dealings with a "service engineer" on "the make." This same old man is a cripple with only a pension. I did the job free of charge.

MULTUM IN PARVO

The other day, with much regret, they took my television set.

Not for lack of payment—no!

But just the darned thing wouldn't go.

Some weeks ago it lost its sound, "a new valve needed" the expert found.

As he twiddled knobs and scanned the view he said, "Is this the best the set will do?"

"Your screen should be just twice as bright, a new tube's wanted here, all right."

"I'll fix the lot for 20 quid and make it just like new, no kid."

With gleaming eyes he grabbed the set; a voice within me said not yet.

This man thinks you are a boob, I'm sure it doesn't need a tube.

I said "I think I'll let it stay and send for you another day."

And so, fearing that the set would burst, another expert called, to do his worst.

Then to my extreme delight, he found another valve won't light.

And upon replacement was found, to wit, it worked like new, yes, every bit.

The valve cost six and twenty bob, I guess that expert knew his job.

The moral of this I hope you'll take.

Be sure your man's not on the make.

R. E. WOODALL (Hove).

USING A CONVERTER

SIR,—I would like to pass on a little hint which I think may not be familiar to many viewers. It concerns the addition of a converter which gives rise to patterning on the set, not on those of neighbours. In trying to overcome this trouble I was told of an arrangement which in my case and those of several of my friends really worked. Round an ordinary lead pencil wind 10 turns of the coaxial normally used. A piece of Sellotape will keep the turns together and then the ends are cut to reach from the normal aerial terminal to the set. The position of the converter should be such that there are

1½ in. or 2 in. left between the coil and the converter and set. In other words, the connection between the converter and the set consists of a short length of coaxial, 10 turns, and then another short piece. This acts as a sort of wavetrap and, as already mentioned, works very effectively.—G. H. RANSOME (Woolwich).

PECULIAR FAULTS

SIR,—With reference to recent notes on peculiar faults, I thought you would be interested to see the attached newspaper cutting relating to the new transmissions in Scotland. I think it is extremely cute. No doubt some of your "expert" readers would be able to explain it! —G. FORSYTH (Edinburgh).

[The cutting related that during the experimental tests on the new Band III station dealers erected aerials for viewers in a vertical position instead of horizontal, with the result that the pictures which were received were lying on their side. When the complaints started coming in, the aerials were turned to suit horizontal polarisation, and the pictures were then the right way up!—ED.]

PROJECTION SCREEN

SIR,—I have a small cinema screen which has a beaded surface apparently painted on. This works very well and I would like to paint a similar screen for my projection receiver. I have been unable to find any firm who can supply a suitable paint and wondered if any reader could help me in this direction.—G. M. WORTHINGTON (Burslem).

SCANNING AND SYNCHRONISATION

(Continued from page 214)

required for the output valve will be within the maximum ratings for the type of valve found in 70 deg. practice, e.g., N329, PL82, etc., and the additional scanning current can be obtained with the type of circuit described in part 3 of this series, merely by increasing the H.T. potential to the output stage.

With the low-voltage line obtained with direct half-wave rectification of the supply mains this cannot easily be done and a useful way of providing an overall increase in anode-cathode potential for the output valve is shown in Fig. 5. The cathode bias required for this valve is normally of about 12 to 16 volts. If this could be applied separately as negative grid bias then an effective increase in H.T. potential would be realised. This is obtained in Fig. 5 by rectifying the sawtooth potential across the transformer secondary and applying this as negative bias to the grid. As extremely little grid current flows a point-contact germanium diode can be used. A large capacitor C is necessary to smooth the bias supply, which if insufficiently smoothed will cause a pronounced modulation of the sawtooth waveform.

(To be continued)

Wanted!

QUALIFIED MEN AND WOMEN

Industry & Commerce offer their best posts to those with the necessary qualifications—such posts that will bring personal satisfaction, happiness, good money and security. As part of a modern industrial organisation, we have skilled knowledge of what is required in industry to-day and the best means of training personnel for its present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed below. Make your own choice and write to us to-day for further information. There is no obligation of any kind.



OUR BACKGROUND!

The E.M.I. Factories at Hayes, England.

The only Home Study College operated by a world-wide manufacturing organisation

EMI

INSTITUTES

PERSONAL & INDIVIDUAL TRAINING IN—

- | | | | |
|---------------------------------------|---|---|--|
| Accountancy | Customs Officer | Languages | Refrigeration |
| Advertising | Draughtsmanship | Management | Sales Management |
| Aeronautical Eng. | Economics | Maintenance Eng. | Sanitary Engineering |
| A.R.B. Licences | Electrical Eng. | Mathematics | Salesmanship |
| Art (Fashion, Illustrating, Humorous) | Electrical Installations | M.C.A. Licences | Secretaryship |
| Automobile Eng. | Electronics | Mechanical Eng. | Shorthand & Typing |
| Banking | Draughtsmanship | Metallurgy | Short Story Writing |
| Book-keeping | Eng. Drawing | Motor Eng. | Short Wave Radio |
| Building | Export Heating & Ventilation Eng. | Painting & Decorating | Sound Recording |
| Business Management | High Speed Oil Engines | Photography & Reproduction | & Telecommunications |
| Carpentry | Exams Industrial Admin. Jig & Tool Design | P.M.G. Certs. | Television Time & Motion |
| Chemistry | Subjects | Police Production Eng. Production Planning | Tracing Study |
| City & Guilds | Commercial Art & Drawing | Radar Radio Amateurs (C&G) Licence Radio & Television Servicing | Welding Workshop Practice Works M'gement and many others |

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.AoS., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Examinations, R.T.E.B. Serv. Cert., R.S.A. Certificates, etc.

NEW! Courses with PRACTICAL EQUIPMENT

in RADIO · TELEVISION · MECHANICS CHEMISTRY · ELECTRICITY DRAUGHTSMANSHIP · PHOTOGRAPHY etc., etc.



COURSES FROM 15/- PER MONTH

POST THIS TODAY

E.M.I. INSTITUTES, Dept. 138K, London, W.4

NAME _____ AGE _____
(if under 21)

ADDRESS _____

Subject(s) with/without equipment _____

DEC. 57

We shall not worry you with personal visits



BLOCK CUPS PLEASE

IC 92

—Part of "His Master's Voice", Marconiophone, etc. etc.

BAND 3 T.V. CONVERTERS BY RETURN OF POST

ALL with 12 months' guarantee (B.V.A. valves, 3 months' guarantee). All 3/- each, extra postage. All 2/- C.O.D.

For all I.T.A. stations and all sets except Philips (see next column).

Pattern rejector fitted. All fully wired, aligned and ready for use. All with power pack, knobs, aerial switching, metal rectifier and 2 valves ECC81. Direct switching from B.B.C. to I.T.A. Fine tuning on front. No drift. State B.B.C.



£4.7.6

With metal cabinet as illustrated. Stove enamel grey hammer finish.

Or Walnut cabinet,

£4.17.6. Lizard Rexine, £4.12.6.

Or chassis, i.e., less cabinet, £3.17.6 (p. & p. 2/6).

Variable attenuator, 7/6 (p. & p. 1/-).

Aerial Splitter, 8/- (p. & p. 1/2).

Band III Aerials, mast mounting: Carr. Paid

3-element, 27/-; 5-element, 35/-; 8-element, 55/-.

Our aerials are suitable for loft mounting.

Low-loss Co-axial, 8d. yard.


External Crossover unit, 7.6 (post 1/6).

Belling Lee 6-element Loft Band III aerial, 30/-.

POST ORDERS TO CAMBERLEY PLEASE.

HIGHLY SUCCESSFUL 13-CHANNEL CONVERTER

Designed and made by a world-famous organisation regardless of expense. Tunable over the whole of Band I and Band III to give one Band I and two Band III stations at the turn of the switch. Acts as Two-valve Pre-amplifier on Band I. Valves PCC84 and PCF.80. No drift. In Moulded Bakelite Cabinet, 8 1/2 in. x 4 1/2 in. x 6 in. high. With full operating instructions. Built-in Power Pack added by us. Separate gain controls for I.T.A. and B.B.C.

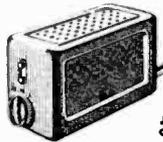

£5-5-0

CONVERTER available for Philips' receivers, to above specification complete with built-in power pack, at £5.5.0.

AUTOMATIC RECORD

CHANGERS are in short supply. Collaro RC456

Studio turnover crystal pick-up. 4-speed mixer.

A.C. mains 200-250 v., see illus.

ALSO Collaro single player AC3/554, 3-speed,

turnover crystal pick-up with "T" head, £6/16/6

(3/6 p. & p.).



£8/16/6 (5/- p. & p.).

GLADSTONE RADIO

3, CHURCH RD., REDFIELD, BRISTOL and 82B, HIGH ST., CAMBERLEY, SURREY

1957 EDITION TV FAULT FINDING

New, enlarged and completely revised edition, covering both BBC and ITA. Data Publication.

5/- Postage 6d.

RAPID TV REPAIR. By G. W. Heath. 23/-. Postage 1/-.

TELEVISION RECEIVING EQUIPMENT. By W. T. Cocking. 30/-. Postage 1/6.

TELEVISION EXPLAINED. By W. E. Miller and revised by E. A. W. Spreadbury. 12/6. Postage 1/-.

F.M. RADIO SERVICING HANDBOOK. By G. J. King. 25/-. Postage 1/3.

UNDERSTANDING HI-FI CIRCUITS. By N. H. Crowhurst. 23/-. Postage 1/-.

THE OSCILLOSCOPE AT WORK. By A. Haas and R. W. Hallows. 15/-. Postage 9d.

RADIO VALVE DATA. Compiled by "WW." 5/-. Postage 9d.

The MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET
LONDON, W.2

Complete catalogue 6d.
Phone: Paddington 4185.
Open 6 days 9-6 p.m.

OPPORTUNITIES IN TELEVISION



148 pages

Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for **A.M. Brit. I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc.** are given in our 148-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointments Dept.

**We Guarantee
"NO PASS—NO FEE"**

If you are earning less than £18 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

WRITE TO-DAY!

British Institute of Engineering Technology
237, College House,
29-31, Wright's Lane,
Kensington, W.8.

BIET

COVENTRY RADIO

Component Specialists
since 1925

We have now trebled the size of our premises in order to supply a larger range of Components, Amplifiers and Hi-Fi Equipment

Send your enquiries to:

189-191 Dunstable Road,
Luton, Beds.

New Telephone No.:
LUTON 7388-9



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 245 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

FERRANTI 17K3

For about 12 months, the operation of width control, on narrowing of the picture, produces a "wickerwork" pattern at the top of the tube face. Further operation of this control produces multiple images; by returning the width control to almost fully clockwise a good picture can be obtained, except that the picture seems to "blow" slightly and clips detail at the sides. Height and frame hold work correctly.

Operating the line hold away from fully anti-clockwise results in a complete break up of the picture, and one position of the line hold produces loss of line scan, i.e., a ragged vertical line only. Could this be a faulty potentiometer.—D. T. White (Ely).

We would advise you to change the 1M Ω horizontal hold control, and also to check the parallel 100K and 150K which are wired in series with it.

R.G.D. 1755T

This set has been in use for about 12 months. The set had not been in use for a week due to holidays. On returning back home I tried the set and it appeared to be O.K. The following day the set appeared to have developed a fault, i.e., the raster was O.K. and slight hum from the speaker, but no sound or picture. I suspected the F.C. stage as the most likely suspect. A friend fitted a new PCC84; the set then seemed to function. The line linearity and width controls were also adjusted. The trouble appears from here on. The aerial is a dipole. The picture now appears slightly blurred. The focus control used to make the picture sharp but it is not as good now. The white content of the picture at times appears as a glare, turning down the brilliance makes the black content lifeless and devoid of detail.

I find that by advancing the brilliance slightly the picture is flat, just as though the interference limiter had been adjusted. The interference

limiter is turned out as far as possible so as not to limit the maximum whites.—K. Holding (Liverpool).

We are rather inclined to suspect the PL81 line output valve of failing, but the symptoms described could be misleading. The V12 ECL80 sig. cathode follower/A.P.C. output valve could be at fault or the 39K1 (MR2) A.P.C. rectifier could be defective. If the contrast cannot be controlled properly this would appear to be extremely likely.

PHILIPS MODEL 1115U

Line hold is very unstable, the slightest drop in volts on the mains causes the picture to slip from the right. This takes place every day, and has been so ever since I bought the set. The engineer put all the blame on the mains, but I could not help thinking that it was a case of 50-50. Last week the supply company fitted an extra transformer on to the supply; this has made a big difference to the supply; we now only get about 5V. drop on peak load, but the line hold still slips.

The ECL80 line oscillator has been changed with other ECL80s in the set, but makes no difference. This change over took place in the first week when the valves were new. The set is now three years old and has given no other trouble. The frame only slips when there is a big drop on the mains, by that time the picture is not worth looking at. I have service sheet for this model.—J. Blake (Bridgwater).

We would advise you to change the 220K Ω (red. red. yellow.) load resistor of the 2nd line sync clipper. Reduce the value to 150K Ω if necessary.

FERGUSON 306T

The set is six months old. In that time I have had to replace E.H.T. rectifier (EY86) four times. Can you please tell me where to look for the trouble? I have a "Avominor" test instrument and service sheet.—J. Ford (Willenhall).

The EY86 heater connections should be examined to ensure that the 4.7 Ω resistor, which should be wired in series with the heater, is actually included in the circuit. If no resistor is found your dealer should be consulted. If the resistor is in the circuit it may be necessary to increase its value to prevent overrunning the EY86 heater.

P.T. BAND III CONVERTER

I wonder if you will be good enough to kindly advise me on the following:

1. Can it be connected to my set, Philips 1100U, by simply plugging the output into the aerial input?

2. My channels are: Band I Channel 5 and Band III, Channel 10. Will the coils as shown be O.K.?

3. Is there sufficient H.T. and L.T. available to energise it from my set? Can the converter heaters be linked into the set chain? Where will I take my 200V. H.T. from?

4. This set, as you know, is fed with a balanced twin feeder. Can twin feeder and its sockets be used in place of the coax and its

fittings on the converter?—G. G. D. Evans (Swansea).

1. Although your receiver uses a balanced aerial input circuit, provided the signal due to the local Band I station is not unduly high in your area, a short length of coaxial feeder can be used successfully to connect the converter to the receiver in the usual manner. If the Band I signal is high, however, trouble will be experienced with Band I breakthrough.

2. L7 should be wound with eight turns of wire of the kind indicated. L6 may also require alteration by increasing the turns spacing or winding with four turns of wire, instead of 4½ turns.

3. A separate power pack should be used in your case.

4. Yes. See 1 above.

PYE LV51

The picture keeps tumbling around and only halts for short periods, even with the control (frame hold) at its maximum. I also note that the position is worsened when an electric fire is switched on.—W. M. Thompson (Radlett).

We would advise you to replace the 470kΩ resistor (yellow, violet, yellow) which is wired in series with the centre tag of the frame hold control.

FERRANTI MODEL T1325

My problem is that, on switching on in the evening, the picture is perfect but the brilliance control is almost fully retarded. After about two hours' viewing the brilliance has increased to such a degree that I cannot reduce it on the control any further and, although the picture itself is perfect, flyback lines are clearly visible and, of course, it is most uncomfortable to watch. If the set is switched off for about three or four hours it then becomes normal for a time but gradually the brilliance increases again.

Can you advise me what to look for? I suspect a resistor is working above load and gradually altering in value. I have no service sheet for this set.—H. I. Toms (Banbury).

Since the picture quality remains good, the increasing brilliance must be due to a rise in potential applied to the grid of the C.R.T. This could well be due to leakage through the .1μF capacitor connected from pin 5 of the C.R.T. to the H.T. line. This capacitor should be changed and the associated 470kΩ resistor (yellow, violet, yellow) checked.

BUSH DAC90A

My Bush has developed a hum which is getting unbearable when trying to listen to a programme. Directly I switch on, the set hums and keeps on all the time it is switched on. I have looked to see if any connections to earth have come unsoldered but there does not seem to be anything wrong. I am only a novice so perhaps with your valuable knowledge you could enlighten me where else to look for the trouble. The set is four years old.—A. Pring (Kew).

If the hum is present when the volume control is turned right down then the trouble is probably

caused by a defective electrolytic smoothing capacitor. A dual 32+16μF unit is used in your model, and both sections should be tested or substituted with a part known to be in good order. Also check the condition of the CL33 output valve.

ULTRA V7116

I would like to know if this model is suitable for conversion to Band III, if so what would be the best to fit, a converter or a channel tuner?—Norman Dewey (Bourne).

Since the oscillator in this model is working below the signal frequency, giving a sound I.F. of 16 Mc/s and a vision I.F. of 19.5 Mc/s, it is not possible to employ a turret converter as these are made only for sets using an oscillator working above the signal frequency.

A simple add-on type Band III converter will need to be used in your case, therefore, such as the Spencer West Type 80 unit.

REPLACING A TUBE

I have replaced a burned out tube, G.E.C. 6706A, with a Mazda CRM122, which the dealer said would fit in. The picture is quite bright, but there is very little contrast, and the raster cannot be cut off with the brightness control at minimum.

Is this a sign of a faulty tube, or is it something in the set which does not agree with the tube ratings?—R. Bailey (Beeston).

Is the tube base connected correctly? The base connections of the G.E.C. tube do not conform with the connections of the Mazda tube. The connections on the Mazda tube are as follows: pins 1 and 8, heater; pin 3, cathode; pin 5, grid; while the connections on the G.E.C. tube are: pins 2 and 7, heater; pin 5, grid; pin 8, cathode. If the base connections are correct, uncontrollable brightness may be caused by a defect in the tube.

RAYMOND 14in.

The vision went completely off, the sound being O.K. At the same time smoke came from the rear of the set. On inspection I found that the smoke was coming from the 1K resistor situated in the E.H.T. section. The resistor is R72 on the service sheet which I have.

The 10 Kc/s whistle is present and the E.H.T. rectifier I had tested and found O.K.

I would be very grateful if you could help me locate the trouble. I do not have any test equipment.—R. M. Ball (Wallasey).

This trouble is almost certainly caused either by a fault in the line deflector coils or in the line output transformer.

PYE MODEL T18

I am trying to modify my Pye to a 14in. I have got a CRM142 tube which has the same size neck as the 9in. tube had (the latter had become quite worn out, hence the idea of trying to adapt a 14in. instead of buying another 9in. tube). I have altered the base connections and fitted a 12 volt filament transformer, raised the tube support and focusing coils and fitted the tube.

(Continued on page 245)

SETS & COMPONENTS

TEST SETS: 74A with 10 valves. VCR. 139a and 50-cycle power pack; fair condition. 50/- (carr. 8/6). Transformers: 21. 50v. 50c. to 10/15/20 25.30/50v. 2A, 7/6 (post 2/6). "C" core: 230v. in: outputs: 315-0-315v. 60 mA. 5v. 2a. 6.3v. 1.5a. 25/- (p.p. 3/6). Input 200/250v. Outputs: 12v., 3a. and 5v., 3A, 12/6; 300-0-300v. 200mA. and 4v. twice. 17/6. Indicator Units, new. with VCR97, 3/VR91, 2/2CV18, 2/VR54, 24/- (carr. 7/-). Responder ZCR931, 160/190 mcs., with valves, 15/- (carr. 7/6). Brand new RF.25, 27, 25/- (post 3/-); RF.25, 10/6. Metal Rectifiers: 240v. 100mA, 4/-; 240v. 30 mA, 3/8; 1,000v., 30 mA, 7/6. Chokes, L.F. 10H, 120 mA, screened, 7/6; 10H, 50 mA, 5/6; 5H, 200 mA, 4/6. List and enquiries s.a.e., please! Terms c.w.o. Postage extra. Immediate despatch. W. A. BENSON (P.T.), 136, Rathbone Road, Liverpool, 15.

GUARANTEED TELEVISION. 12in. 5-Channel models, first-class picture. £25 each, carriage paid. THE GRAMOPHONE SHOP, 19-21, Brockley Rise, London, S.E.23.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Buntingford Rd., Oxford.

I.T.V. CONVERTERS from £3/19/6, self-contained, guaranteed. H.P. without fuss. Aerials from 14/6. Trade enquiries invited. G. A. STRANGE, Dept. P., North Wraxall, Chippenham, Wilts.

TELEVISIONS. 9in. models £7/10/-, 12in. models £13/10/-, 12in. 5-Channel models £19/10/- each; all working; carriage paid. Send for list. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

Elstone Transformers from M. FOY.

BUILD YOUR I.T.A. AERIAL from our machined parts. Supplied with folded dipole already made with insulator fitted, and cranked arm with clamp for any size of existing mast or wall bracket. (State which when ordering.) Only a screwdriver needed to complete a rigid, waterproof array. 3 Element, 32/6; 5 Element, 42/6; 8 Element, 55/-; post free. Lashing Kit if required, 15/- extra. Special Offers.—F.M. Indoor Dipole, complete on mast and base, 12/6. 4 B.A. Steel Screws, 1in. or 3in. long and 6 B.A. Steel Screws, 7/16in. long, all at 1/9 gross, post paid. Polythene Insulators for jin. rods, 4/- each, post paid. Illustrated lists of all Aerial Fittings, with Technical Data for Aerial Construction, all bands, 1/- P.O. All goods post free. Write for details. SKYLINE WORKS, Burnsall Rd., Coventry. (Tel.: 60418.)

DO YOU EVER repair Radios and T.V.s? Then you require a Service Sheet. We have 1,000s and 1,000s of the actual ones used by the Trade, for sale or hire; s.a.e. with enquiry. You also require our new, larger Catalogue, packed with exact replacement and servicing components, price 1/-. M. FOY, 6, Wykebeck Gardens, Leeds, 9.

New, Larger Catalogue from M. FOY.

5-CHANNEL TELEVISIONS: 12in. screen Ferguson 988, Ekco 161, etc. £22 each. A good selection of 12in. T.V.s (London), 100% condition, from £12; 9in. from £7, also 12in. T.V.s, slight faults, from £5; 9in. from £3. TYLER TELEVISION, 63, Lee High Rd., Lewisham, S.E.13. (LEE 5979.)

RATES: 4/- per line or part thereof, average five words to line. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

TRANSISTOR KIT, complete. £4/19/6, post and ins. 2/6. **TRANSISTORS**, tested and guaranteed. A.F. (Red Spot), 8/6. Mixer and F.C. (Blue Spot), 14/8. R.F. and I.F. Amp. (White Spot) 17/6. P.P. 6d. MULLARD Germanium Diodes, 0A74, 8s., P.P. 6d. The R.A.B.A.R. KILVOULTER, Range 3-30 kV. Measures E.H.T. volts. £3/15/0, post/ins. 2/6. The famous BRAY-HEAD 12-Channel Turret Tuner. State set make and model No. £6/19/6, post/ins. 2/6. Send 3d. stamp for lists.

WESTWAY RADIO

5 Westward Way, Harrow, Middx.
Replacement Components from M. FOY

TELEVISIONS, NEEDING ATTENTION. 9in.-10in. models £4/10/- each. 12in. models £6/6/- each. 15in. models and Philips Projection models £11/10/- each; immediate despatch; carriage paid. BARKERS, 325, Brockley Road, S.E.4. (TID 5752.)

TELEVISION TUBES. Good quality reclaimed and guaranteed for 6 months, as supplied to the trade throughout the British Isles: 14-15, 16-in. £5; 17in. £6; c.w.o. or pro-forma carriage 15/-. (Smaller sizes available, but in short supply.) TELEVISIONS, 34 and 18, Market Parade, Rye Lane, Peckham, S.E.15. (Tel.: New Cross 4551.)

T.V. TUBES as new; re-evacuated; all makes; 6 months straight guarantee; 12in. £5, 14in. £5/10/-, 17in. £7/10/-; carriage and insurance 12/6. U.K. Free delivery Greater London. VIDIO REPLACEMENT CO., Hales St., Deptford High St., London, S.E.8. (Tideway 4506.)

T/V TUBES

All Types and Sizes in Stock.
First-class picture guaranteed.

All Sizes, £6 each.

With 6 months' Full Guarantee.

Terms C.W.O. or C.O.D.

All orders dispatched within
3 days.

GRANTS

104 Church Rd., Tranmere
Birkenhead

12IN. T.V., out of order. £5; working O.K., £10; 12in., 5-channel, £15; 14in. from £18. Auto/Radiograms from £15. Callers only. JOHN GILBERT TELEVISION (SHE 8441), 1B, Shepherds Bush Rd., London, W.6.

TRANSFORMERS, built to specification, up to 10kVA; singly or quantities; 2 years' guarantee; quick service. NOTTINGHAM TRANSFORMER SERVICE, 179, Wollaton St., Nottm. (Tel.: 41992.)

TELEVISIONS. 12in., 5 channel, £14; 14in., £18; 17in., £27; Faulty Sets from £2. WILKINSON'S, 146, Goldhawk Rd., W.12. (SHE 4379.) Callers only.

TELEVISIONS, all sizes and channels, at lowest prices ever! Also a few tubes. Trade supplied. HYNES, 9, Cumberland St., Victoria, S.W.1. (TAT 9140.)

UNREPEATABLE OFFER.—12in., 5 channel T.V., £15; 14in., £22; good working order. C. EDWARDS, 1070, Harrow Rd., London, N.W.10. (Phone: LADbroke 1734.)

13-CHANNEL 12in. turret-tuned Sets, suitable any transmitter, £25, plus carriage; 14in., £30; many others from £8. C.C.W. No. 12 Dockhead, S.E.1. (BER 3756.)

"TELEVISIONS," 12in., 5 channel, tunable anywhere, models from £19/10/- each; carriage paid; satisfaction guaranteed. RYAN ELECTRICS, 134, Acre Lane, Brixton, London, S.W.2. (BRI 4533.)

CATHODE RAY TUBES, used, but in good working order, and with 3 months' guarantee. All 12in. to 17in. Mazda, Mullard and Emitron types at £4/10/- each, plus 13/6 carriage. Orders and enquiries by letter only to: BHP DISTRIBUTORS, 379, Staines Road, Hounslow, Middlesex.

R.F. UNITS. Types 27 or 26, 22/-; 25 or 24, 9/-; brand new, with valves; post, 3/-. E.W.S. CO., 69, Church Rd., Moseley, Birmingham.

DIPOLE INSULATORS, 1in. boom, 1in. elements, suitable T.V. or F.M. Dipoles, 5/-. P.O. with order. C. & H., 2a, Mona Street, Liverpool, 7.

NEW AND USED VALVES and Components at low prices; all guaranteed, s.a.e. lists. Service Sheets, s.a.e. enquiries. Reconditioned Radios and T.V.s from £2, for callers. J. PALMER (P.T.), 32, Neasden Lane, N.W.10.

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets "How to Use ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive list of lenses, optical radio and scientific gear free for s.a.e. H. W. ENGLISH, Rayleigh Road, Hutton, Brentwood, Essex.

ELECTRADIO.—Dual Wave Coil 2/6 with circuit, ditto, plus Reaction 4/-, Tuning Condenser 3/10, Crystal Diode 1/6 tested 4 Transistor Set Circuit, 1/3. All Transistor Components stocked. Post free. 18, Broadlands Av., Keynsham, Somerset.

PCF80s, 5/6, post paid; sorry no other types; all first class; mail only; posted Sats. Please don't cross P.O. G. EDWARDS (PT1), 38, Crawford Street, W.1.

FOR SALE

AERIAL CURRENT METERS, reading in micro-amps, render decibels obsolete. HOBLEY, 109, The Drive, Wellingborough.

VALVE CARTONS. Miniatures 10/6, "GT's" 12/-, "G's" 44/- per s.d.00 plus 2/- p. & p. RHS, 155, Swan Arcade, Bradford, 1. Lists free.

T.V. CONSOLE CABINET, 43/64 tube, megger, etc.; all brand new; half-price. S.A.E. Box No. 196, c/o PRACTICAL TELEVISION.

SUPERTONIC SUNLAMPS, listed £7/10/-; 80/-, S.A.E. SCIENTIFIC PRODUCTS CO., Cleveleys, Lancs.

SITUATIONS VACANT

PART TIME Television Service Engineer; Essex area; own transport required. CHA. 8493.

SERVICE SHEETS

TELEVISION and Radio Sheets for sale; not reprints; going cheap. Box No. 198, c/o PRACTICAL TELEVISION.

SERVICE SHEETS FROM M. FOY.

SERVICE MANUALS/Sheets Tel/Radio for hire. Sale and wanted. Mixed Manuals and Sheets. 12 for 10/-; s.a.e. enquiries W. J. GILBERT P.T. 1, 24, Frithville Gdns., London. W 12

WANTED

NEW VALVES WANTED. EY51, EY86, PCF80, PL81, 5Z4G, U25, or what have you? Prompt cash. RHS, 155, Swan Arcade, Bradford. 1

WANTED VALVES

All types for prompt cash. Must be new. State quantity.

WILLIAM CARVIS LTD.
103, North Street, Leeds, 7.

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. **RADIO FACILITIES LTD.** 38, Chalcot Road, N.W.1. (PRImrose 9090.)

WANTED, reconditioned Cathode Ray T.V. Tubes. Please state makes, sizes and prices. Box No. 197, c/o PRACTICAL TELEVISION.

EDUCATIONAL

FREE! Brochure giving details of Home Study Training in Radio, Television and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit. I.R.E., City and Guilds, R.T.E.B., and other professional examinations. Train with college operated by Britain's largest electronics organisation. Moderate fees. Write to E.M.I. INSTITUTES, Dept. PF28, London. W.4.

A.M.I.P.R.E.—For details of suitable study courses (only a limited number of students accepted) send for free Syllabus of Instructional Text. I.P.R.E. Conditions of membership booklet 1/-; "The Practical Radio Engineer" journal, sample copy, 2/3; 6,000 alignment peaks for Superhets, 6/-. All post free from SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

BUILD YOUR OWN T/V and learn about its operation, maintenance and servicing. Qualified engineer-tutor available while you are learning and building. Free Brochure from E.M.I. INSTITUTES, Dept. PF58, London. W.4. (Associated with H.M.V.)

11 + EXAMINATION.

Write for **FREE 20-page GUIDE** and Test, stating age of child to: **THE REGISTRAR** (Dept. MT), Mercer's Correspondence College, 69, Wimpole St., London, W.1.

OSMOR CONVERTERS

ALL CHANNELS

Simple, efficient for all TV (including TRF). Guaranteed no break-through of Band I or re-radiation. Approx. 1 hr. to build. Will convert any Band III channel to any Band I channel. A.C. or A.C./D.C. Kit. £3.5.0. Ready wired. £4.0.0. Post free. Terms: C.W.O. Post orders only. **THE ELECTRONIC SUPPLY CO.** 29 Leigh Rd., Highbury, London, N.5

A WONDERFUL MONEY-SAVING OPPORTUNITY FOR READERS OF PRACTICAL TELEVISION!



Now's the time to join the SCIENTIFIC BOOK CLUB

You **BUY** Books published at 10/6, 12/6 and more—for **ONLY 4/-**

**FULL LENGTH
FULL SIZE**

The Scientific Book Club is owned and controlled by Foyles, the world-famous booksellers.

LOOK AT THESE GREAT TITLES!

Recent and forthcoming selections include:

INSIDE THE ATOM

By Isaac Asimov
Published at 12s. 6d.
4s. TO MEMBERS

AUTOMATION: ITS PURPOSE & FUTURE

By Magnus Pyke
Published at 16s.
4s. TO MEMBERS

WINDOW IN THE SEA

By Ralph Nading-Hill
Published at 18s.
4s. TO MEMBERS

SCIENCE UNFOLDS THE FUTURE

By J. G. Crowther
Published at 18s.
4s. TO MEMBERS

Each month, the Scientific Book Club brings to its members the fascinating story of the march of modern science, told in thoroughly dependable books by the front-rank scientific writers of our time—vivid, vital, constructive contributions to Man's unceasing struggle to solve the problems of the Universe. And although the ordinary editions of these books are sold to the general public at 10/6, 12/6 15/-, or more, THE PRICE TO MEMBERS OF THE SCIENTIFIC BOOK CLUB IS ONLY 4/-. Remember, too, that Scientific Book Club selections are full-length and unabridged. They are printed on good quality paper, well bound, with an attractive picture jacket. These are, we say with certainty, books that you will be glad to read, proud to own. The Scientific Book Club brings these great books to you each month; helping you to build up, at remarkably low cost, a first-class collection of scientific books. Now is the time to join!

FREE! You can obtain the famous **CONCISE OXFORD DICTIONARY** (published at 18s.) FREE if you enrol a friend in the Club. Send your friend's name and address with 5s. (4s. plus 1s. postage) for first book, mentioning this offer, and your gift will be sent to you.

-----FILL IN THIS ENROLMENT FORM TO-DAY!-----

To The Scientific Book Club, 121 Charing Cross Road, London, W.C.2

I wish to join the Scientific Book Club, and agree to purchase the book issued each month to members at a cost of 4s. (postage 1s.). I agree to continue my membership for a minimum of six books and thereafter until countermanded.

Prac. Television/Dec. '57.

- ★ I will pay for selections on receipt.
Or if you wish to save time, postage and postal order costs you may send an advance subscription. 6 months 30s.; 12 months 60s.
- ★ I enclose 30s., 60s. (Strike out amount not applicable.)
★ Place ✓ in the space above, as required.

NAME
(Block letters, please)

ADDRESS

Overseas enrolments (prices as for inland) should be accompanied by an advance subscription.

When I tried it out the sound is still O.K. and all the valves appear to light up O.K.—that is the glass ones—but all I get on the tube is a bright horizontal band about $\frac{3}{4}$ in. wide which is unaltered by any of the controls. Only movement of the ion trap either widens or narrows it within limits. The people who supplied the tube did warn me that I might need more E.H.T. Do you think this is what is wrong? The E.H.T. that is fitted is a cylindrical affair with a Paxolin tube that slides up and down which gives a very slight adjustment to the picture—or rather did do—and two leads—a long one to the C.R.T. and a short one to the top cap of a PL38 valve.—S. L. F. Seares (Letchworth).

Modern wide-angle picture tubes require greater scanning power, E.H.T. voltage and video drive than your 9 in. chassis is capable of supplying. Some form of picture should be obtained, however, and from your description of the symptom we feel that a fault has developed in the frame timebase circuits. Make sure that you have not damaged or disconnected any wires or windings associated with the scanning coils.

EKCO TC185N

My set was converted for Band III, using a Clydon Turret Tuner. My trouble on the set is a varying white line or edging on the bottom of the picture. Adjustment on the frame linearity and height controls, plus the C.R.T. adjustments, removes it to some extent, but still leaves me a gap at the bottom. On some occasions the line seems to disappear on its own accord.

A month ago I had trouble with the picture width but a new 20L1 valve rectified it. Checking over recently I found that on switching on occasionally the U801 H.T. rectifier would flash a little or show a blue tint.

Could this valve or the frame oscillator have any effect with the white line? Also on one occasion I heard a gentle plop in the set and wondered if you could explain this to me.—S. Flox (Leeds).

The flashes around the U801 (and the "plops" probably) are due to small emissive particles flaking off the cathode. One day one of these will lodge between cathode and anode and the valve will need replacing. Your foldover could be due to a low emission frame output valve, which is a 6L18 in some sets and a 10P13 in others. Failing this check the 4,700pF feedback condenser from the anode of the output valve to the linearity control.

MURPHY V114 9in. TV

The lower half of the picture is marred by black or white lines (horizontal) and these usually start at the very bottom and run up to half way and then disappear. Picture quality is excellent. Close investigation of the picture was made and it appears that the spot misses some six or more horizontal traces and then carries on normally

until it repeats itself. This causes this part of the picture to "jump up and down" because of the displacement. Sometimes the trace piles up on itself, causing a white line. Frame hold and other frame controls will not correct this.

Frame output valve (Pen45) checked O.K. Thyatron oscillator (T41) interchanged with line timebase valve. No change. Sync sep. (DD41) interchanged with sound section valve. No change. Frame output transformer windings checked with ohmmeter. O.K. Video output valve replaced with new valve (6F12). No change. C52 (32 μ F) electrolytic shows signs of "bulging" on its end but "kicks" the meter O.K. H.T. voltage O.K. Various resistors associated with frame timebase valves and controls checked and appear to be O.K.—D. Goodey (Farnborough).

The trouble you are having could either be oscillation of the frame output valve or a breakdown in the frame output transformer. As neither of these troubles would show on a tester the only sure way to check is to replace.

A fairly large cored audio transformer will do as a makeshift frame output transformer. It almost certainly will not match, or produce a full linear scan, but it should suffice to enable you to check the original.

MASTERADIO TG7T

The trouble is that, after the set has been switched on, the picture always comes on in broken horizontal lines, with a vertical line down the centre, and dull, and turning up the brightness control does not make much difference. By turning the line hold control I can get two or more dull pictures side by side, and after manipulating the controls for some time the screen will brighten suddenly, and by turning the line hold control I can get a picture which will immediately go dull and break up again. After about half an hour I may finally get a steady picture which may last half to one hour when it will break into two pictures with a wide vertical black band in the middle. Sometimes the picture can be restored by turning the line hold or it may right itself, and may last for an hour or two. The frame hold and contrast controls seem to work all right. I have fitted a new line output valve, 50CD6G, but it did not cure the trouble.—P. F. Wilson (Walthamstow).

Make sure that the aerial is supplying a good signal to the receiver. If all is well here, suspect trouble in the line sync circuits. Change the capacitor between pins 1 and 6 on V11 for one valued 22pF. This will improve the line lock. Line drift may be caused by trouble in V11 itself, and this is best checked by substitution.

QUERIES COUPON

This coupon is available until DECEMBER 21st, 1957, and must accompany all Queries sent in accord with the notice on page 241.

PRACTICAL TELEVISION, DECEMBER, 1957

RADIO SUPPLY CO. (LEEDS) LTD.

Dept. N.
32, THE CALLS, LEEDS 2.

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/0 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d. Trade list 5d.

R.S.C. TRANSFORMERS

Fully Guaranteed.

Interleaved and Impregnated.

Primaries 200-250 v 50 c/s screened
TOP SHROUDED DROP THROUGH
260-0-260 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 16/9
350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9

FULLY SHROUDED BRIDGE
250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a
Midget type 21-33in. ... 17/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 26/9
250-0-250 v 100 ma, 6.3 v 6 a, 5 v 3 a

For R1335 Conversion ... 31/-
300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 150 ma, 6.3 v 4 a, 0.4-5 v 3 a ... 33/9
425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a ... 49/9

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s Primaries: 6.3 v 1.5 a, 5/9; 6.3 v 2 a, 7/6; 0.4-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 8/11; 6.3 v 6 a, 17/9

CHARIER TRANSFORMERS
200-250 v 0.9-15 v 11 a, 11/9; 0.9-15 v 3 a, 16/9; 0.9-15 v 5 a, 19/9; 0.9-15 v 6 a, 22/9.

OUTPUT TRANSFORMERS
Standard Pentode 5,000 to 3 ohms ... 4/9
Small Pentode 5,000 to 3 ohms ... 3/9

SMOOTHING CHOKES
250 ma 5 h 50 ohms ... 11/9
100 ma 10 h 250 ohms ... 8/9
80 ma 10 h 350 ohms ... 5/11
60 ma 10 h 400 ohms ... 4/6

SELENIUM METAL RECTIFIERS
C.E.C. 300 v 250 ma, 12/9; 120 v 40 ma, 3/9;
6.12 v 1 a F.W. 4.11; 240 v 50 ma, 4.11;
6.12 v 2 a F.W. 8.91; 6.12 v 4 a, 14.9; 250 v 80 ma, 7.9; 6.12 v 6 a F.W. 19.9; 6.12 v 70 ma, 25.9; 6.12 v 15 a, 35.9; 24 v 2 a, 14.9.

CO-AXIAL CABLE (In.)
75 ohms 14/36 ... 8d. yd.
Twin-screened Feeder ... 11d. yd.

BATTERY SET CONVERTER KIT

All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma. Fully smoothed and fully smoothed L.T. 1.2 v at 0.4 a to 1 a. Price including circuit 49/9. Or ready for use, 9/9 extra.

ALL DRY RECEIVER BATTERY ELIMINATOR KIT

All parts for the construction of a unit (metal-case 51-41-2in.) to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or ready for use, 46/9.

EX-GOVT. DOUBLE WOUND STEP UP STEP DOWN TRANSFORMERS

10-0-100-200-220-240 v to 5-0-75-115-135 v or REVERSE. 80/100 watts. Only 11/9 plus 2/9 post. 10-0-100-200-220-240 v to 6-0-110-122-136-148 v or REVERSE. 200 watts, 35/9 plus 7/6 carr. Both 50 c.p.s.

EX-GOVT. CASES. Well ventilated black crackle finished, undrilled cover. Size 14 x 10 x 8 1/2 in. high. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE. OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9 plus 2/9 postage. Size 13 1/2 x 8 1/2 x 6 1/2 in. with undrilled perforated cover finished stoved grey enamel, 7/9 plus 2/9 post.

EX-GOVT. VALVES (NEW)

1F4	7/9	6X7G	3/9	6AT6	7/9
1SS	7/9	6X5GT	7/9	EBH1	8/9
2Z1	8/9	6L6GT	11/9	EP80	8/9
6X6G	9/9	807	7/9	EF35	4/9
6ST1GT	6/9	12A6	7/9	EL32	3/9
EF39	5/9	15D2	4/9	EL61	5/9
6V6GT	7/9	23Z4G	8/9	KR95	11/9
6J5C	3/9	6X4	4/9	SP61	2/9

EX-GOVT. MAINS TRANSF.
Removed from New ex-Govt. units.
Primary 0-200-100-250 v Secs 275-0-275 v 100 ma, 6.3 v 7 a, 5 v 3 a ... 19/9

EX-GOVT. SMOOTHING CHOKES

80 ma 10 h 150 ohms ... 3/11
100 ma 5 h 100 ohms Parmalco ... 3/11
100 ma 6-10 h 100 ohms Parko ... 6/-
120 ma 12 h 100 ohms ... 9/-
150 ma 6-10 h 150 ohms Trop. ... 6/9
150 ma 10 h 150 ohms ... 11/9
250 ma 5 h 50 ohms ... 12/9
300 ma 20 h 200 ohms ... 19/9

EX-GOVT. SMOOTHERS

62 mfd. 5,000 v Cans (ex-Govt.). 2/11

BATTERY CHARGER KITS

Consisting of attractive Blue Hammer Case, Transformer, F.W. Rectifier, Fuse, Fuseholder, Tag Strip Grommets and Circuits. For mains input 200-230-250 v 50 c/s, 6 v 2 a, 25/9; 6 v or 12 v 2 a, 31/6; 6 v or 12 v 4 a 59/9. Any type assembled and tested for 6/9 extra.

N.S.C. 6 v. or 12 v. 4 a. BATTERY CHARGER

For normal A.C. mains input 200-230-250 v 50 c/s Selenium panel for 6 v or 12 v charging. Variable charge rate of up to 4 AMPS. Fuse, and with meter. Well ventilated case with attractive hammer finish. Guaranteed for 12 months. 75/- Carr. 3/6.

BATTERY CHARGERS


For normal A.C. mains input 200-230-250 v 50 c/s Selenium panel for 6 v or 12 v at 1 amp. In strong metal case. Only 27/9. Above can also be used for electric train power supply.

D.C. SUPPLY KIT

Suitable for Electric Trains. Consists of mains trans. 200-250 v 50 c.p.s. A.C., 12 v 1 a. Selenium F.W. Bridge Rectifier, 2 Fuseholders, 2 Fuses, Change Direction Switch, Variable Speed Regulator, Partially drilled Steel Case, and Circuit. 29/9



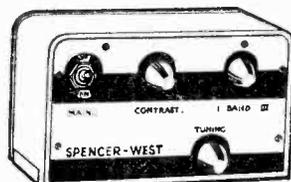A SPENCER-WEST BAND III CONVERTER FOR £6.5.0



The Type 80 with printed circuits, panel controls for Band switch and fine tuning and a performance which ensures enthusiastic satisfaction. Handsomely designed and finished to stand on your receiver with its self-contained power supply it just plugs straight in. Full descriptive leaflet on request. Available from all good dealers or post free direct from the manufacturers if any difficulty.

SPENCER-WEST LTD.,
Quay Works, Great Yarmouth, Norfolk.

Phones: Works 4794; Sales 3009
Grams: Spencer-West, Great Yarmouth.

Air-spaced Coaxial Cable, 75/80 ohms, new, 9d. per yd. 70/- per 100 yds. Meters, 500 microamps. F.S.D., marked 15,600 v., 2in. dial, 15/-, 12in. Plessey P.M. Speakers, new, 27/6. Television Aerials, Band III Channels 8.9, 10, 3-element, 28/6; 5-element, 38/6; 6-element, 58/6; Band I all channels, H, 77/6; X, 74/6. Combined Aerials from 25/-. Why not send S.A.E. with your aerial enquiry and we will reply by return. We only stock the well-known guaranteed made aerials, thereby giving better value for money. Pico All-in-one Radiometer, A.C. D.C. ranges 0.6-240 volts, 0.30 ma, also continuity and valve filament tester. 32/6. F.M. Feeder Cable, new, standard 300 ohms, 6d. per yd. Volume Controls, special offer 1/6 each 5/P. Lone spindle, 3/-. Volume Controls, D.P. 5/6; L.S. 3/6; Pre-set, 4/-; R.M.1. 4/6; R.M.2. 5/6; R.M.3. 7/6; R.M.4. 16/6; R.M.5. 25/-. Ion-Trap Magnets, 5/-. Chrome Car Aerial, 37/6. Fidelity 4-speed Autochange Amplified Record Player, new and guaranteed, 18 gns. Pico Electrical Blankets, new, Single, 67/6; Double, 87/6.

GUARANTEED VALVES

OZ1	5/-	6K8	9/-	6B8	19/6	PCC81	9/9
1A5	3/-	6Q7	9/-	EB91	5/-	12/6	
11N5	3/-	6AT6	8/-	EL84	10/8	UBC41	8/6
2X2	4/-	6AQ5	8/6	ECL80	10/8	UCH42	8/6
3D3	2/6	6SL7	8/-		12/6	UL41	10/-
4D4	3/6	6A7	10/-	EY51	12/6	WR1	13/6
5Z4	9/6	6BW6	8/-	PY82	8/-	9/9	12/8
6U4	9/6	6BC6G	8/-				
6U7	6/6	19/6	PY80	9/-	ECC81	9/6	

MAIL ORDER ONLY.
NO CALLERS.

Terms: C.W.O. or C.O.D. Minimum C.O.D. charge 3/6. Postage and packing per valve 8d. Under £2, 1/9; £4, 2/3. All Aerials 2/6 carriage.

ELECTRO-SERVICES & Co.
221 BATTERSEA PARK ROAD,
LONDON, S.W.11. **MAG 8155**

FIRST-CLASS TELEVISION and RADIO COURSES . . .

GET A CERTIFICATE!

After brief, intensely interesting study undertaken at home in your spare time—YOU can secure your professional qualification or learn Science and Theory. Let us show you how!

FREE GUIDE

- The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.B.R.I., I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of


SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

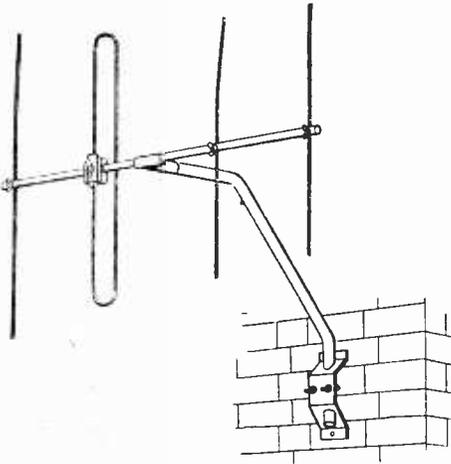AMAZING OFFER IN COMMERCIAL TELEVISION AERIALS



4 element Aerials, array only, for mounting to 1½ in. mast.

LIMITED NUMBER only 25/-.

Double 4 element Aerials, array only, complete with Cross-over-unit. Matching Stubs wired to folded dipoles. Few only 79/6.

Co-axial Plugs 7½d.

Cellular Polythene Co-axial Cable at 8d. per yard.

Aluminium Masts 1½" diam. 10' long 30/-.

Double lashing kit for same 30/-.

This powerful 4-element, pre-assembled, wide-spaced Band III beam Aerial by a leading manufacturer. Supplied complete with cranked pole and wall fixing bracket can also be loft mounted. Listed at 55/6. OUR PRICE, BRAND NEW, in maker's sealed carton, 39/6.

Terms : Cash with order or C.O.D. Carriage on aerials 2/6 extra.

MAIL ORDER ONLY.

G. C. EQUIPMENT CO. LTD., 2, Park Row, Leeds, 1.

EDDY'S (Nottm.) LTD.

(DEPT. P.T.)

172, ALFRETON ROAD, NOTTINGHAM

THIS MONTH'S SPECIAL OFFERS

RECORDING TAPE. 1,200ft. reels 9/11 each, post, etc. 1/- extra.

GERMANIUM DIODES. New and Guaranteed 1/- each. 10/- a dozen, post extra 3d.

MIDGET BATTERY ELIMINATORS. To convert all low consumption portables for mains operation. Mains output 220/240 v. A.C. H.T. Output 85 v. 10 mA. L.T. output 1.3 v. 125 mA. Size 3.7 in. x 2.5 in. Actually smaller than H.T. battery alone! Amazing price of 55/-, plus 2/6 extra post and packing. ALL NEW AND GUARANTEED.

Any parcel insured against damage in transit. **SURPLUS. New & Guaranteed** **VALVES** Postage and Packing 6d. per Valve. **ALL TESTED BEFORE DESPATCH.** extra. Over £2 Free.

1R5	7/6	6Q7C	8/3	35A5	11/6	ECC81	8/-	EZ80	8/-
1R5	7/6	6Q7GT	8/11	35L6GT	8/11	ECC82	8/-	EZ81	9/6
1T4	7/6	6U4GT	13/11	35Z4GT	8/-	ECC83	8/6	GZ32	12/6
9Q4	9/-	6V6GT	5/11	35W4	7/6	ECC84	9/11	GZ34	14/-
354	8/-	6X4	6/6	80	8/6	ECC85	9/3	MU14	8/6
3V4	8/-	6X5GT	6/6	807	6/6	ECH35	9/6	PCC84	7/11
5Y3GT	7/6	7B7	8/-	954	1/6	ECH42	9/6	PCF80	9/11
6B8G	3/11	7C5	8/-	955	4/6	ECH81	8/6	PY80	8/3
6BA6	6/6	7C6	8/-	956	2/6	ECC80	8/11	PY81	8/-
6B36	7/-	7H7	6/6	958	9/11	EP41	9/-	PY82	8/6
6F1	13/6	7S7	8/-	DF96	9/6	EF80	8/3	U25	12/6
6F15	14/-	7Y4	7/11	DK96	9/6	EF86	12/6	UBC41	8/6
6J5GT	3/11	10F1	12/6	DL96	9/6	EF89	9/11	UBF80	9/6
6K7G	2/11	10F9	11/8	DM70	7/11	EF91	6/11	UCH42	8/-
6KR6	7/9	14S7	13/8	EABC80	7/6	EL32	3/11	UF41	8/-
6L6G	7/11	25L6GT	9/-	EB01	6/6	(4-pin)		UT41	8/11
6E28	15/-	25Z4G	9/-	EBC41	9/3	EL84	8/11	UY41	7/6

NO LISTS. TRADE ENQUIRIES INVITED. C.O.D. or C.A.V.O. ONLY.

TELEVISION TUBES

GUARANTEED FOR THREE MONTHS. EX-CHASSIS AND PICTURE TESTED.

MAZDA, EMISCOPE, G.E.C., FERRANTI, COSSOR, EMITRON, BRIMAR, MULLARD

12" £6-0-0

14" £5-5-0

15" £7-5-0

17" £7-5-0

USED VALVES

Ex-chassis, tested, all types for television sets. 5/6

SPECIAL :

MAZDA REBUILT 12" £9-0-0

Guaranteed for six months.

Cash with order for prompt delivery : write

E. B. ELECTRONICS (TUBE DEPT. T.)

28 PEMBRIDGE ROAD, LONDON, W.11

or phone BAY 9262.

All prices include post and packing.

We Regret No Personal Callers for Next 3 Months

TELEVISION TUBES

RECLAIMED GUARANTEED:

12"—£6 14"—£5 17"—£7.10.0

FULLY GUARANTEED HIGH QUALITY
REBUILT:

12"—£9 14"—£11.10.0 15"—£12 17"—£13.10.0

CARRIAGE AND INSURANCE 15/6 EACH TUBE

MAIL ORDER ONLY

PRIME ELECTRICS

36 QUEENSDALE ROAD, W.11.



QUALITY TELEVISION COMPONENTS

SCANNING COILS, 6/10 kV. and 13/15 kV., R.F.,
E.H.T. UNITS, E.H.T. and OUTPUT TRANSFORMERS,
LINE FLYBACK E.H.T. UNITS.

COIL KITS FOR "P.T." BAND III CONVERTERS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd.,

Queensway, Enfield,
Middlesex.

"VIEWMASTER"

Printed Circuit Converter

No Patterning
or Breakthrough

We can supply the complete
kit of parts including valves,
£5 0 0.

Send for detailed list
of this kit and others,
POST FREE.

Set of coils for conversion
of Viewmaster receiver,
£1 0 0.

PLEASE NOTE NEW ADDRESS

AUDIO LTD.

162 Gray's Inn Rd., London, W.C.1

Telephone TERminus 0228-9.

60 PAGES OF SPARES IN NEW CATALOGUE

81 exact replacement V/CS. 37 Mains
droppers. Line output transformers,
Condensers, Resistors, Tools. Everything
for the engineer or amateur. Price 1/-.

M. FOY

6, Wykebeck Gdns., Leeds, 9.

RES/CAP. BRIDGE 35/-

p. & p. 1/6
Checks all types of resistors and
condensers

Easy to Build Up Easy to Use

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. Z)

Raleigh Mews, Raleigh Street, Nottingham

TELEVISION COMPONENT SERVICE

Replacement components available for
the popular home constructor designs.
Catalogue available on request.

J. T. FILMER 82, Dartford Road,
Dartford, Kent.

Tel.: Dartford 4057

RADIO AND TELEVISION COMPONENTS

All parts in stock for:

Viewmaster, Soundmaster, Teleking, etc.

Easy Terms available.

3d. stamp (only) for Catalogue

JAMES H. MARTIN & CO.

FINSTHWATE, NEWBY BRIDGE,
ULVERSTON, LANC.

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP
WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:

36, ROSEBERY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester,
Birmingham, Leeds.

"No Quantity too Small."

CERAMIC CAPACITORS

Non-inductive Hi-k midget tubular
ceramic, 500 v. d.c. wkg. Ideal
for T.V., etc. —.0005 μ F, .001 μ F,
.0015 μ F, .002 μ F, .003 μ F, 10 $\frac{1}{2}$ d.
each; .005 μ F and .01 μ F, 1/- each.
Minimum postage 9d. on orders
under £3.

**SOUTHERN RADIO &
ELECTRICAL SUPPLIES
SORAD WORKS
REDLYNCH, SALISBURY**

TECHNICAL TRADING CO.

RECTANGULAR TV TUBES. 12 MONTH Guarantee. 14in..
£4 15/- : 17in., £6 15/- Carr. & ins., 15/-.
RED SPOT TRANSISTORS up to 800 kc/s. 7/-.
WHITE SPOT TRANSISTORS up to 2.5 mc/s. 14/-.
GERMANIUM NTAL DIODES, 9d., 8/- doz.

13-CHANNEL CONVERTERS

Unrepeatable opportunity. complete.
instructions, makers' sealed cases, no
extra coils required, easily adapted most
sets, beautiful Bakelite cabinet or internal
mounting models, each, £3/15/-.

ATTRACTIVE 14in. TABLE T.V. CABINETS. Size 17in. x
18in. x 16in. mask glass, 7 x 4 front speaker baffle, 29.-, post 6/-.

S.A.E FREE LIST 400 AMAZING SNIPS

Including: EF50, 2/6; EF91, 7/-; W.A. Focus Magnets, 9/-;
Screened Slugged Alladin Coils, 6/- doz. Etc., etc.

10,000 OTHER BARGAINS TO CALLERS AT:—

350/352 FRATTON ROAD, PORTSMOUTH

LINE OUTPUT TRANSFORMERS

Most types available. State Make and Model
Number of Receiver when ordering.

S.A.E. please with all enquiries.

HOWORTH

51 POLLARD LANE, BRADFORD, 2, YORKS

Tel. 37030

TV TUBES

All types
Seen working

Guaranteed

£5 - £7

Plus 10/- carriage

**26 BRISTOL ROAD,
BRIGHTON** Tel. 28440

ADCOLA

PRODUCTS LIMITED
(Regd. Trade Mark)

SOLDERING EQUIPMENT

ILLUSTRATED

$\frac{3}{16}$ " Detachable
bit type (List
No. 64)

Protective Shield
(List No. 68)

Catalogues sent
FREE

Telephones :
MACaulay 4272
& 3101



British and
Foreign Pats.


Reg. Desigs,
etc.

Head Office, Sales :

**ADCOLA
PRODUCTS
LTD.**


Gauden Road,
Clapham High
St., London,
S.W.4

TRANSISTOR TRANSFORMERS

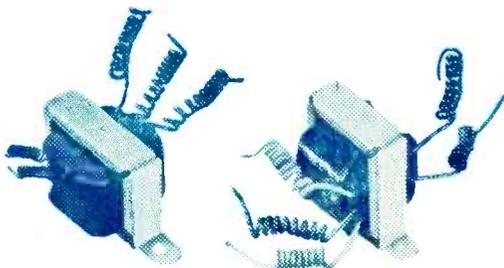

... two examples—a Driver and an Output type—from our miniature lightweight range.

150 mW Range	Size	Weight	Frequency	Price
Driver	1.11.32"x13.16"x13/16"	1oz.	120 c/s-17 Kc/s	13/-
Output	do.	do.	100 c/s-17 Kc/s	8/6
250 mW Range				
Driver	1.3/4"x13.16"x1.1/8"	2oz.	50 c/s-16 Kc/s	14/6
Output	do.	do.	50 c/s-16 Kc/s	9/3

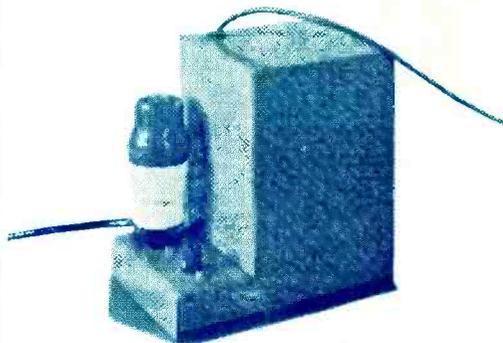

The NERA R.F. E.H.T. UNIT

... designed to provide a safe and reliable source of D.C. high voltage for all C.R.T.'s including the new wide angle aluminised types. Output is continuously variable between 8-12 kV at approximately 500 μ A. Power supplies necessary are 6.3 v. at 1 amp., and 250/350 v. at 40 mA. Ample shielding prevents radiation and interference to broadcast receivers.

Price : £7 . 10 . 0

Coil and rectifier assembly only : £4 . 10 . 0

P.A.M Ltd MERROW · GUILDFORD
SURREY
Tel. Guildford 2211

(One of the group of companies associated with the
Southern Areas Electric Corporation Ltd.)

PERFORMANCE ASSURANCE WITH



COSSOR

PRINTED CIRCUITS

**AN INSTRUMENT RANGE
IN KIT FORM**

- Q.** *Why has Cossor Instruments decided upon this innovation?*
- A.** To make available a range of first-class measuring instruments at a considerable saving in cost to the Buyer.
- Q.** *Are Kit instruments inferior in performance to their Factory-built equivalents?*
- A.** Certainly not. If assembled and wired exactly in accordance with the Manual of Instructions.
- Q.** *A certain skill must, surely, be required to build these instruments?*
- A.** None beyond the ability to use a small soldering iron.
- Q.** *How can a performance specification be maintained without setting up with test equipment?*
- A.** Largely by the use of PRINTED CIRCUITS which allow no interference with the layout of critical parts of the circuit.
- Q.** *How many Kit instruments are at present available?*
- A.** Three. Two Oscilloscopes, a Single-Beam and a Double-Beam, and a Valve Voltmeter. Others will follow shortly.
- Q.** *Could I have more information on these interesting instruments?*
- A.** With the greatest of pleasure. Just write to:

*Model 1071K Double Beam Kit Oscilloscope.
List Price £69-0-0.
Five Purchase Facilities.
Trade terms on application*

COSSOR INSTRUMENTS LIMITED

The Instrument Company of the Cossor Group

COSSOR HOUSE · HIGHBURY GROVE · LONDON, N.5.

Telephone: CANonbury 1234 (33 lines) Telegrams: Cossor. "Norphone," London Cables: Cossor. London

718