

MAKING A VALVE-VOLTMETER

Practical Television 13

JANUARY, 1958

AND TELEVISION TIMES


EDITOR: F.J. CAMM



CONTENTS

- A SWITCHED TV/F.M. RECEIVER
- SIMPLIFIED SERVICING
- SCANNING AND SYNCHRONISATION
- YOUR PROBLEMS SOLVED
- LETTERS FROM READERS
- Etc. Etc. Etc.

Build your own Aerials...

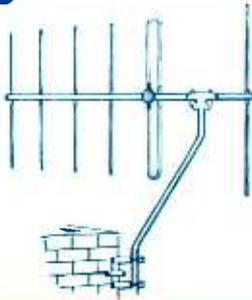

Fringevision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F.M.
Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above to —

SABIR

Voltage Regulator

**MAINS FLUCTUATION OF
150 — 300 V**

will have no observable effect on the performance of your TV set if this revolutionary new Automatic A.C. Mains Regulator is fitted. At the same time, the complete elimination of surges will greatly lengthen the life of all components, especially of tube and valves.
Price £11.15.3. Write now for illustrated technical leaflet, giving full specifications.



MERCIA ENTERPRISES LTD.
Godiva House · Allesley Old Road · Coventry

COMMERCIAL TV

**DON'T GIVE UP BEFORE YOU HAVE
TRIED OUR BAND III PRE-AMP**



Separate coaxial inputs for Band I and III Aerial Downloads. No changing of Aerial leads. No Diplexor required. Attractive black crackle finished case fitted with non-scratch rubber feet. Easily installed—just plug in mains and aerial leads.

A sensitive unit complete with built-in power supply specially designed for use in ultra-fringe areas. High signal to noise ratio. Will produce excellent results in localities where the signal is normally unusable.

Dimensions 6in. x 4in. x 2½in. Will fit inside most receiver cabinets. 200-50 v. A.C.

PRICE £6.6.8. C.W.O. OR C.O.D.
(Fly Lead 3/6 extra.)


"AIRVISION"

(Electronic Equipment Manufacturers)

14 Boulton Road, SOUTHSEA

NEW! THE PRACTICAL WAY

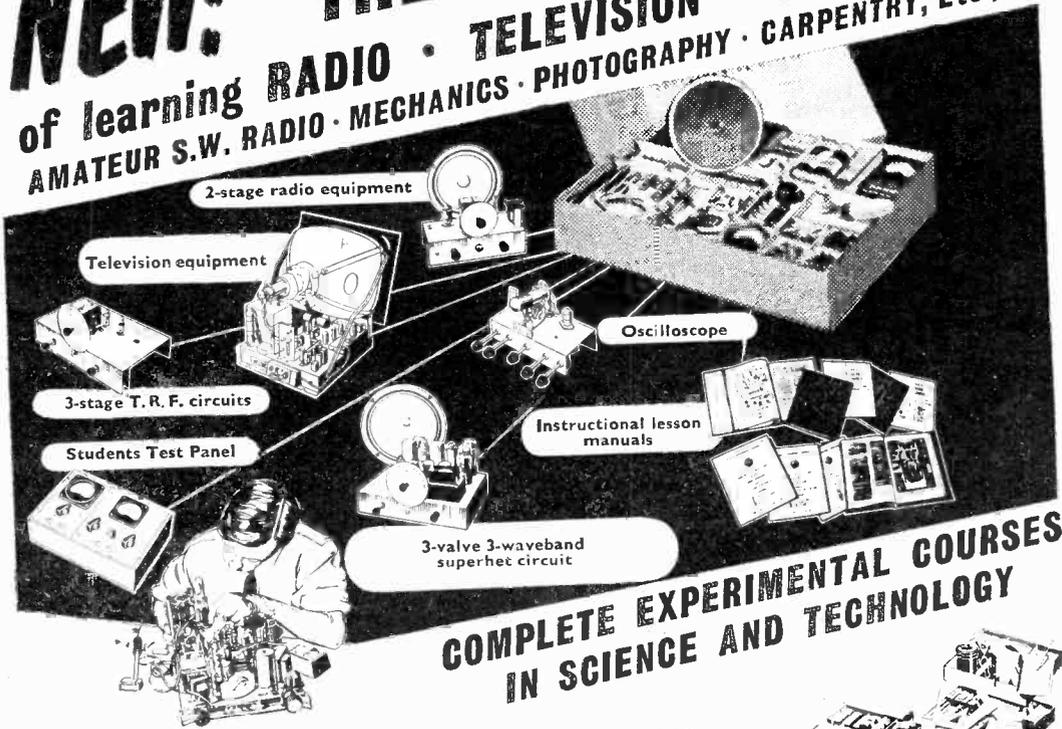of learning **RADIO • TELEVISION • ELECTRONICS**
AMATEUR S.W. RADIO • MECHANICS • PHOTOGRAPHY • CARPENTRY, Etc., Etc.



COMPLETE EXPERIMENTAL COURSES IN SCIENCE AND TECHNOLOGY

NEW... Completely up-to-date method of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teachers.

NEW... Experimental outfits and lesson manuals sent on enrolment remain the student's property. Tutor allotted to each student for personal and individual tuition throughout the course. Radio and television courses, with which specially prepared components are supplied, teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern radio and T.V. receivers. If you are studying for an examination, wanting a new hobby, commencing a career in industry or running your own part-time business, these practical courses are ideal and may be yours for moderate cost. Fill in the coupon to-day for a free Brochure. There is no obligation whatsoever.

The only Home Study
College run by
a world-wide
Industrial
organisation



E.M.I.
Factories
at Hayes,
England

EMI INSTITUTES

- Part of "His Master's Voice" Marconiphone, etc., etc.

SUBJECTS INCLUDE:—

- RADIO • SHORT WAVE RADIO**
- TELEVISION • MECHANICS • CHEMISTRY**
- PHOTOGRAPHY • ELECTRICITY • CARPENTRY**
- ELECTRICAL WIRING • DRAUGHTSMANSHIP**
- ART, ETC.**

COURSES FROM
15/- PER MONTH



E.M.I. INSTITUTES, Dept. 138x
LONDON, W.4

NAME _____ AGE _____) BLOCK
 (if under 21)) CAPS
 ADDRESS _____) PLEASE

I am interested in the following subject(s) with/without equipment

JAN. '58 (We shall not worry you with personal visits) IC.35

TOP QUALITY FULLY GUARANTEED VALVES

ALL GOODS LISTED ARE ACTUALLY IN STOCK

EXPRESS SERVICE !!!

C.O.D. ORDERS RECEIVED BY 3.30 P.M. EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON. ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY

FOR ONLY 6d. EXTRA PER ORDER WE WILL INSURE YOUR VALVES AGAINST DAMAGE IN TRANSIT. ALL UNINSURED PARCELS AT CUSTOMER'S RISK.

OZ4	6/- 6AM6	9/- 6K7GT	6/- 10LD3	8/6 30L1	12/6 CK506	6/6 EC70	12/6 EY51		PCCB4	8/- UAF42	10/6
IA3	3/- 6A05	7/6 6K8G	8/- 10P13	17/6 30P4	15/- CK523	6/6 ECC31	15/- (Large)	12/6 PCCB5	12/6 UBF41	12/7	
IA5	6/- 6AT6	8/6 6K8GT	G 1IE3	15/- 30P12	13/6 CV63	10/6 ECC32	10/6 EZ35	6/6 PCF80	14/- UBC41	8/6	
IA7	15/- 6AU6	10/6	11/- 12A6	6/6 31	7/6 CV85	12/6 ECC33	8/6 EZ40	8/- PCF82	12/6 UBF80	9/6	
ID6	10/6 6B4G	6/6 6L6G	9/6 12AH7	8/- 33A, 158M	30/- CV271	10/6 ECC35	8/6 EZ41	10/6 PCL83	14/- UBF89	10/6	
IH5	11/- 6B7	10/6 6L7M	8/- 12AH8	10/6	30/- CV428	30/- ECC81	8/6 EZ80	9/6 PCL83	14/- UCH42	10/6	
IL4	6/6 6BBG	4/6 6L18	13/- 12AT6	10/6 35/51	12/6 D1	3/- ECC82	8/6 EZ81	10/- PEN40DD	UCH42	10/6	
ILD5	5/- 6BBM	5/- 6N7	8/- 12AT7	8/6 35A5	11/- D42	10/6 ECC83	9/- GZ30	10/6			
ILN5	5/- 6BA6	7/6 6Q7G	8/6 12AU7	7/6 35L6GT	10/- D63	5/- ECC84	10/- GZ32	12/6			
IN5	11/- 6BE6	7/6 6Q7GT	9/- 12AX7	9/- 35W4	8/6 D77	6/6 ECC85	9/6 H30	14/-			
IR5	8/6 6B16	8/- 6R7G	8/6 12BA6	9/- 35Z3	10/6 DAC32	11/- ECC91	5/6 H33	5/-			
IS5	8/6 6BR7	11/6 6SA7GT	8/6 12BE6	10/- 35Z4GT	8/- DAF91	8/- ECC92	13/6 H63	12/6			
IT4	7/- 6BW6	8/6 6SG7GT	7/6 12E1	30/- 35Z5GT	9/- DAF96	10/- EC82	13/6 HABC80	12/6			
IU5	7/- 6BW7	14/- 6SH7	6/- 12J5GT	4/6 41MTL	8/- DF33	11/- EC835	9/6	13/6			
ZA3	12/6 6BX6	14/- 6S17	8/- 12J7GT	10/6 50C5	12/6 DF91	7/- ECH42	10/- HK90	10/-			
2A7	10/6 6C4	7/- 6SK7GT	6/- 12K7GT	7/6 50L6GT	9/6 DF96	10/- ECH81	8/- HL23	10/6			
2C26	4/- 6C5	6/6 6SL7GT	8/- 12K8GT	6/6 61BT	15/- DH63	8/6 ECL80	14/- HL41	12/6			
2D13C	7/6 6C6	6/6 6SN7GT	7/6	14/- 61SPT	15/- DH76	7/6 ECL82	14/- HL133DD	12/6			
2X2	4/6 6C8	12/6 6S57	7/6 12Q7GT	7/6 72	4/6 DH77	8/6 EF36	6/-	12/6			
3A4	7/- 6C9	12/6 6U4GT	14/- 12SA7	8/6 77	8/- DK32	15/- EF37A	9/- HVR2	20/-			
3A5	12/6 6C10	12/6 6U5G	7/6 12SC7	7/6 78	8/6 DK91	8/6 EF39	6/- HVR2A	6/6			
3L7	8/6 6CH6	7/6 6U7	8/6 12SG7	7/6 80	9/- DK92	12/6 EF40	15/- LK35	8/6			
3D6	5/- 6D6	6/6 6V6G	7/- 12SH7	5/6 83V	12/6 DK96	10/- EF41	9/6 KT2	5/-			
3Q4	9/- 6E5	12/6 6V6GT	7/- 12SJ7	8/- 85A2	15/- DL2	15/- EF42	12/6 KT33C	10/-			
3Q5GT	9/6 6E1	15/- 6X4	7/- 12SK7	6/- 150B2	15/- DL33	9/6 EF50(A)	7/- KT44	7/-			
3S4	8/- 6F6G	7/- 6X5GT	6/6 12SQ7	8/6 807	7/6 DL92	8/- EF50(E)	7/- KT67	7/-			
3V4	9/- 6F6GT	8/- 6Z4/84	12/6 12SR7	8/6 866A	13/6 DL94	9/- EF54	5/- KTW61	6/6			
5U4	8/6 6F8	12/6 6Z5	12/6 12Y4	10/6 956	3/- DL96	10/- EF73	10/6 KTW62	8/-			
5V4	12/6 6F12	9/- 6J30L2	12/6 14R7	10/6 1203	7/- DLS10	10/6 EF80	14/- KTW63	8/-			
EX4	10/- 6F13	13/- 7A7	12/6 14S7	14/- 4033L	12/6 DM70	8/6 EF85	7/6 KTZ41	6/6			
EY3G	8/- 6F16	9/6 7B7	8/- 19AQ5	11/- 5763	12/6 EA50	2/- EF86	14/6 KTZ63	10/6			
5Y3GT	8/6 6F17	12/6 7C5	8/- 19H1	10/- 7193	5/- EA76	9/6 EF89	10/- L63	6/-			
5Y4	10/- 6F32	10/6 7C6	8/- 20D1	16/- 7475	7/6 EABC80	8/- EF91	9/- LN152	14/-			
5Z3	12/6 6F33	7/6 7H7	8/- 20L1	13/6 9002	5/6 EAC91	7/6 EF92	6/6 MH4	7/-			
5Z4G	10/6 6G6	6/6 7Q7	9/- 25L6GT	10/- 9003	5/6 EACF42	10/6 EL32	5/6 MHL4	7/6			
5Z4GT	12/6 6H6GT	G 757	9/6 25Y5	10/6 9006	6/- EB34	2/6 EL41	11/- MHL6	12/6			
6A8	10/-	3/- 7V7	8/6 25Y5G	9/6 AC6PEN	7/6 EB41	8/6 EL42	11/- ML4	12/6			
6A87	8/- 6H6M	3/6 7Y4	8/- 25Z4G	9/6 AC/HL	EB91	6/6 EL81	15/- ML6	6/6			
6A88	14/- 6J5G	5/- 8D2	3/6 25Z5	10/6 DDD	15/- EBC33	7/6 EL84	10/6 MU14	10/-			
6AC7	6/6 6J5GTG	5/6 8D3	9/- 25Z6G	9/6 AC/P4	8/- EBC41	10/- EL91	5/- OA10	12/6			
6AG5	6/6 6J5GTM	6/- 9D2	4/- 28D7	7/- AP4	7/6 EBF80	9/6 EP134	10/- OA71	5/-			
6AG7	12/6 6I6	5/6 10C1	15/- 30I	7/6 ATP4	4/- EBF89	9/6 EP134	10/- OA71	5/-			
6AIB	8/- 6I7G	6/6 10F1	15/- 30C1	14/- AZ31	12/6 EBF89	9/6 EP134	10/- OA71	5/-			
6AK5	5/- 6I7GT	10/6 10F9	11/6 30F5	14/- BL63	7/6 EC52	5/6 EY51	10/6 OC72	30/-			
6AL5	6/6 6K7G	5/- 10F18	12/6 30FL1	12/6 CK505	6/6 EC54	6/- (Small)	12/6 PABC80	15/-			
									10/6 2729	14/6	

TERMS OF BUSINESS :-CASH WITH ORDER OR C.O.D. ONLY. ORDERS VALUE £3 OR MORE SENT POST/PACKING FREE. ORDERS BELOW £3 PLEASE ADD 6d. PER VALVE. C.O.D. ORDERS:-MINIMUM FEE, INCLUDING POST AND PACKING, 3/-. WE ARE OPEN FOR PERSONAL SHOPPERS. MON-FRI. 8.30-5.30. SATS. 8.30-1 p.m.

ALL VALVES NEW, BOXED, TAX PAID, AND SUBJECT TO MAKERS' GUARANTEE. FIRST GRADE GOODS ONLY, NO SECONDS OR REJECTS. GOODS ARE ONLY SOLD SUBJECT TO OUR TERMS OF BUSINESS, OBTAINABLE FREE ON REQUEST. CATALOGUE OF OVER 1,000 DIFFERENT VALVES 3d.

When comparing our prices, remember just what we offer. Bentley valves are not only "GUARANTEED NEW AND BOXED," and "GUARANTEED TESTED AT TIME OF DESPATCH," Bentley valves are NEW, BOXED, AND SUBJECT TO THE MAKERS' STANDARD GUARANTEE AS WELL. Only our enormous turnover enables us to select the products of the world's finest manufacturers at lowest prices and pass the benefits on to YOU.

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS

38 CHALCOT ROAD, LONDON, N.W.1

PRImrose 9090

PLEASE ENQUIRE FOR ANY VALVE NOT LISTED. 3d. STAMP, PLEASE.

PREMIER RADIO CO.

OPEN TILL
6 P.M. SATURDAYS

(Regd.) B. H. MORRIS & CO. (RADIO) LTD.

(Dept. P.T.1) 207, EDGWARE ROAD, LONDON, W.2

Telephones:
AMBASSADOR 4033
PADDINGTON 3271

Build the NEW "MAYFAIR" TELEVISOR which gives complete SAFETY to the constructor!

These Televisors use a double wound mains transformer which gives you complete safety from contact with the mains supply when handling the chassis or controls.


★ **B.B.C. & I.T.A. DESIGN** With New
Turret Tuner may be built for **£33.7.11** plus cost
of C.R.T.

Build in 5 easy stages. Full Construction details available.
Instruction Book, 3/6 Post Free.

Console Cabinets with full length doors for 14in., 16in., and
17in. tubes. Price **£14.14.0**.

H.P. Terms: Deposit **£7.7.6** and 9 monthly payments of 18/5.
Console Cabinets. Half door **£12.12.0**.

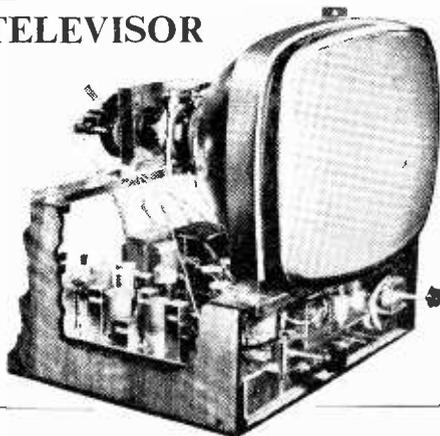H.P. Terms: Deposit **£6.6.0** and 8 monthly payments of 18/3.
On above cabinets add 21/- for pkg. and carr.



The "Petite" PORTABLE MAY BE BUILT FOR

£7.7.0

plus 3/- post & packing.

★ Size only 8in. x 8in. x 4 1/2in.



Batteries extra.

HT 10/- (Type B126) or
equivalent.

LT 1/6 (Type AD 35) or
equivalent.

Battery eliminator now
available for 37/6.

RECORD CHANGERS

Collaro RC456 — **£9.15.0**
Dep. **£1.5.0** & 8 monthly
payments of **£1.5.9**.

Staar Galaxy — **£9.15.0**
Dep. **£1.5.0** & 8 monthly
payments of **£1.5.9**.

RECORD PLAYERS

Collaro 4/554 — **£7.7.0**

Collaro Junior — **£4.14.6**

B.S.R. TU8

3 speed record player

£3.19.6.

plus 2/6 postage &
packing.

8-WATT AMPLIFIER

This design includes 5 miniature
Valves of the latest types, an
Ultralinear Output Trans-
former suitable for Speakers
of 3 and 15 ohms and a very
attractive Perspex front panel
with gold lettering, complete
set of parts, **£8.8.0**.
Postage & Packing, 5/- extra.
Instruction Book 1/5.

The New De-Luxe

TAPE RECORDER TR 3




for **£6.5.0**
DEPOSIT &
8 MONTHLY
PAYMENTS
OF £5.17.11
OR CASH 45 GNS.
plus 21/- post & pkz.

Write for
details of the
New PREMIER
TAPE RECORDER
KIT for **£33.15.0**.

Case finished in Red and Cream with gilt styling and fittings.
Size 18 1/2 in. x 15 in. x 9 in. for A.C. Mains 200/250 v. 50 cycles.
TRADE ENQUIRIES WELCOMED

NEW F.M. TUNER

for the Home
Constructor

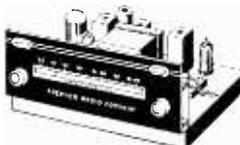

A new design using the latest
circuit techniques. Includes
4 valves plus magic eye tuning
indicator, permeability tuning
and an integral power supply. Two controls only, a gear driven
slow motion tuning control and an output volume control
with on/off switch. Suitable for fringe area reception.

All components may be purchased for **£8.15.0**, plus postage
and packing 3/6.

OR less Mains Transformer & Rectifier **£7.12.5**, plus postage
and packing 3/6.

Power requirements H.T. 230 v. 50 mA., L.T. 6.3 v. 1.5 A.
Dial size 3 1/2 in. x 1 1/2 in., overall size 1 1/2 in. long, 5 1/2 in. deep,
4 1/2 in. high. Instruction Book 1/6.

WHY buy surplus or reconditioned tubes when these Fully
Guaranteed Wide Angle Tubes are available? The
latest type 17in. Rectangular Tube MW43/64 by Telefunken at **£17**
(inc. tax) post and packing 2/- extra. Also 14in. Rectangular
Tube type 14 LPA **£13.17.6** (inc. tax) pkg. & carr. 15/- extra.



**T.C.C. SCREENED
HIGH-PASS FILTER,
TYPE C263.**



THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION · NORTH ACTON · LONDON · W.3 · Tel: ACOrn 0061

**DO YOU SUFFER
FROM THIS TYPE
OF INTERFERENCE?**

This filter has been designed to eliminate the principal causes of I.F. interference; R. F. Heating Equipment, Diathermy Equipment, Industrial and Medical Equipment, Local Oscillators, Forward Scatter Transmissions.


Type C.263 is supplied in an aluminium can, having a co-axial socket mounted at one end and a short length of co-axial feeder, suitably terminated with a plug, at the other end. The filter is connected directly in series with the aerial feeder of a T.V. receiver and no further adjustments would be necessary.

The Unit offers very high attenuation at frequencies of 38 m/cs. and below, and thereby prevents pick-up of the interfering signal by the I.F. Amplifier circuits.

This unit has been approved by and supplied to the G.P.O.

Dimensions of the can: 4½" x 1½" diameter together with a co-axial lead 9" long.

LIST PRICE 29/6 EACH

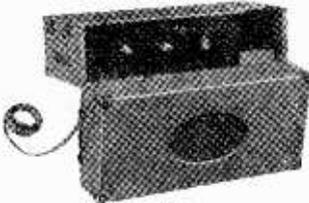

GUITAR AMPLIFIER !

5-6 watts output. For use on A.C. Mains 200-250 v. Complete with 4 valves, speaker, all controls, neon level indicator, gram and mike inputs. Speaker in lid, but movable to any position by using lead supplied. In smart case with carrying handle, size closed 8½ in. x 8½ in. x 19 in. long. Brand new and unused.

LASKY'S PRICE, absolutely complete £10.19.6 Carr. & Pkg. 5/-

Available as Amplifier without Case and Speaker, £6.19.6. Carr. & Pkg. 5/-
NOTE: Can also be used as tape-recording amplifier (pre-amplifier and erase).

TURRET TUNERS.

All types in stock—Cydion, Brayhead, Telenge and Valradio. Write us make and model of your Set; we will quote for the Tuner you need. Prices from **79/6**

BAND III CONVERTERS

with own power supplies, in attractive Cases. Leading makes from **£5.19.6**

17in. C.R. TUBES.

Few only. Brand new and unused. Rectangular, aluminised or ion trap, 0.3 heater.

**LASKY'S
PRICE
£12.19.6**

Carr. & Ins. 22/6.



**COLLARO
4-SPEED
AUTO-CHANGER**

Mixer Model RC.456, with Studio crystal pick-up. List £13/17/0

LASKY'S PRICE, £8/19/6
Post 5/-.

**MAKER'S SURPLUS
COMPONENT BARGAINS**

WIDE ANGLE 38 mm.

- Line E.H.T. trans., Ferroxcube core, 9-16 kV..... 25/-
- Scanning Coils, low imp. line and frame..... 35/-
- Ferroxcube cored Scanning Coils and Line Output Trans., 10-15 kV. EY51 winding Line Trans. Complete with circuit diagram, the pair..... 50/-
- Frame Output Transformer 6.8 Scanning Coils low imp. line and frame..... 17/6
- Frame or line block osc. transformer..... 4/6
- Focus Magnets Ferroxcube 18.6 P.M. Focus Magnets, Iron Cored..... 19/6
- Duomag Focallisers..... 22/6
- 300 ma Smoothing Chokes... 15/-
- Electromagnetic focus coil, with combined scan coils... 25/-

STANDARD 35 mm.

- Line Output Transformers, No E.H.T..... 12/6
- Line Output Transformers, 6.9 kV. E.H.T. and 6.3 v. winding, Ferroxcube..... 19/6
- Scanning coils, Low imp. line, and frame..... 12/6
- Ditto by Itronic..... 14/9
- Frame or line blocking oscillator transformer..... 4/6
- Frame output transformer... 7/6
- Focus Magnets: Without Vernier..... 12/6
- With Vernier..... 17/6
- Focus coils, Electromag... 12/6
- 200 ma Smoothing Chokes... 10/6




LASKY'S (HARROW ROAD) LTD.

Open All Day Saturday, Early Closing Thurs. Mail Orders to Harrow Rd., 42, TOTTENHAM COURT ROAD, W.1. 370, HARROW ROAD, PADDINGTON, W.9. Telephone: MUSWan 2805. LADbroke 1075 and CUNningham 1979.



Practical Television

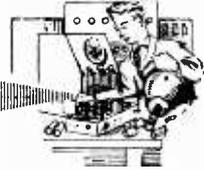

& TELEVISION TIMES

Editor : F. J. C.A.M.M

Vol. 8 No. 90

EVERY MONTH

JANUARY, 1958

TELEVIEWS

Editorial and Advertisement Offices :
PRACTICAL TELEVISION
George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.
© George Newnes Ltd., 1957.

Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - 19s. per annum
Abroad - - 17s. 6d. per annum
Canada - - - 16s. per annum

CONTENTS :

	Page
Televiews	253
Simplified TV Servicing	254
How Many Viewers ...	257
Switched TV F.M. Receiver	260
Flywheel Sync. and A.G.C.	264
Servicing Television Receiv- ers, Ultra VT917 and WT917	267
A Simple Valve Voltmeter ...	273
Scanning and Synchronisation	277
Telenews	281
Underneath the Dipole ...	285
Correspondence	289
Your Problems Solved ...	293

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to : The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

LIMIT ON ADVERTISING

THE Independent Television Authority has instructed commercial television programme contractors to limit advertising to eight minutes in the hour, and that the average must remain at six minutes in the hour. Although the Authority has previously stipulated an average of six minutes advertising in the hour, spot advertising rose by 60 per cent. last autumn. The conclusion to be drawn from this is that the Authority has decided not to draw on the Government grant of £100,000 in the new financial year, which was intended to assist in obtaining a proper balance in programmes. This Government offer, it will be recalled, is part of the £750,000 a year mentioned in the Television Act. It has already been rejected by four of the programme companies as being too small and unrealistic. The final decision whether to accept or reject could only be made by the Authority. In the third Annual Report it is stated that "As the year drew to an end, the Authority could not fail to recognise that the atmosphere in which it had been found necessary to press for a grant had been greatly changed by the marked improvement in the companies' advertisement revenues." Sir Robert Fraser, Director General of the I.T.A., said that next year Independent Television intends to make a further effort to cater for those who love the arts. He did not explain nor expound upon this theme. We can only hope that programme time is not wasted on those arty-crafty programmes which have been so severely criticised when the BBC put them out. The report shows an average operating income of £1,702,152 and that no further sums have been drawn from the Government.

Sir Robert made a passing reference to the speech by Mr. Gerald Beadle, BBC Television Director, by stating that in recent weeks ancestral voices had been putting Independent Television firmly in its place, awarding it a sort of second-class moral status, the innuendo being that I.T.A. is lower in character and aim than the BBC programmes. "To both services, the sound of applause is sweet, and the louder the sweeter. Both want the 'house full' signs out, not the shutters up. The conventional characters of Good BBC and Bad I.T.A. belong to the land of myth and fable. Already in news, politics, public affairs and religion, the I.T.A. has more regular programmes than the BBC." He went on to claim that the I.T.A. Political Discussion Programme "Free Speech," has an audience seven times bigger than the BBC Brains Trust and that the magazine "This Week" had twice as big an audience as the comparable BBC programme, "Panorama." "We do not talk about the taste of the mob, we talk about what ordinary people like. What some regard as the herd, we respect as the human family." These are sound words.—F. J. C.

Our next issue, dated February, will be published on January 22nd.

sections of the set. They are generally means of adjusting the position of the slug in the coils. In the case of sets for the five channels of Band 1, there is often a cursor marked with the appropriate channels. This is naturally not dead accurate, but is only a guide, but it will generally be found that only a slight alteration is needed from the marked cursor.

Troubles here in this section will be applicable to no vision, no sound. Valves as usual should be checked, and in the case of the frequency changer, a known good one should be substituted. Coils should be checked for continuity, and also any controls, such as "sensitivity" or contrast, where it should be checked that the moving arm or slider is making good contact. In checking continuity of these controls, it is best to remove one end connection as in some cases there is a parallel circuit across, which will cause a wrong reading to be given on the meter.

Sets With Sound on Vision

This is a very common fault and it can be generally stated to be due either to too large a signal input, wrong adjustment of oscillator or sound rejector trimmer incorrectly adjusted.

In dealing with the first, it should be investigated if the sensitivity or contrast controls are in position where too much signal is being applied to the receiver. In the case of the second, the oscillator trimmer will need a slight adjustment. In adjusting this, it will be found that as one sweeps across the frequency width of the receiver, firstly vision on sound will occur (this is manifest as a low hum), then the correct position is reached and further on occurs sound on vision. In some sets the position of the oscillator will be

found very critical. Pains should be taken to set this correctly, if good viewing is desired. As regards the last, most sets have a sound rejector circuit, which eliminates any residual sound being passed on in the vision circuit. A good method of adjusting this is as follows. Adjust line hold until it is nearly slipping then if there is sound on vision it will appear as a ragged edge. Adjust sound rejector trimmer until the ragged edge disappears. A slight adjustment of oscillator after this may be necessary. There is one other fault that may cause sound on vision, this is a microphonic valve. This can generally be cleared when sound volume is reduced. By the way, microphonic valves do not generally show up on a valve tester, so substitution is the best cure for this.

Sets With Vision on Sound

This is a fault similar to previous one, but which can be mistaken for ordinary hum, due to lack of smoothing. However, it can be checked, as if it is vision on sound, the hum will disappear when picture transmission ceases, whereas if it is ordinary hum it will still be there whether the programme is on or not. Causes can be, firstly, too strong a signal input, or faulty adjustment of oscillator, or faulty video valve or mismatched aerial and/or transmission line.

R.F. and Video Strip of T.R.F. Receiver

Although this type of receiver is obsolescent there are still many in use. Fig. 17 gives a typical circuit. It will be noticed that in this typical circuit only two valves are concerned with both sound and vision. Thus any fault that affects both sound and vision will be in the circuits of

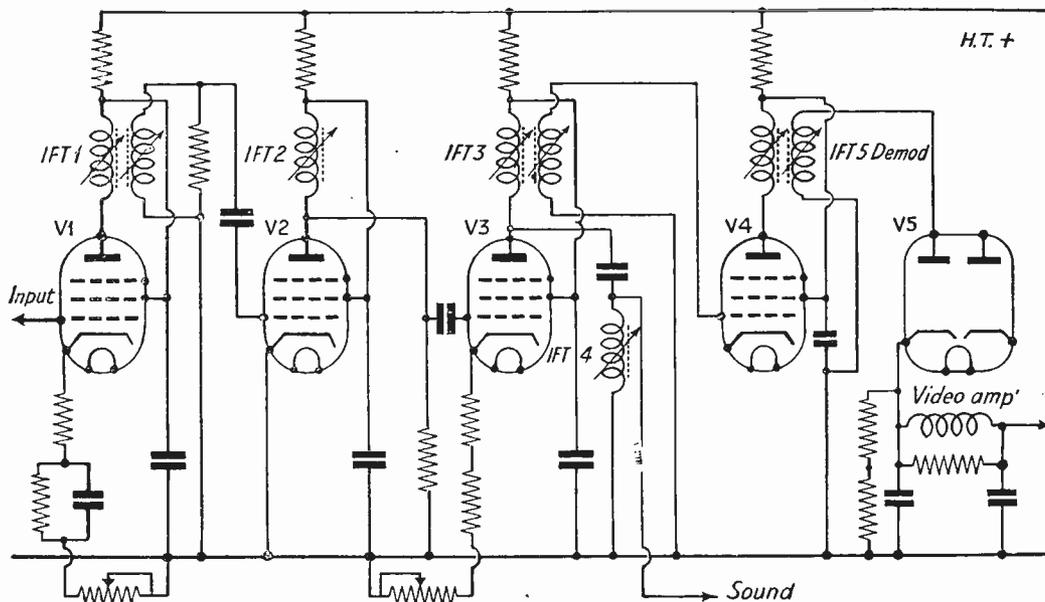


Fig. 16.—Typical S.Het. diagram. V1 is the R.F. amp., V2 the frequency changer, V3 1st I.F. (vision and sound), V4 second vision I.F., and V5 video demodulator.

these two valves, that is if all other things such as H.T. and heater supplies are O.K. The same procedure should be adopted as with a superhet. Check valves first and then components. The contrast control in the circuit given is in the cathode circuit of V1 and acts as a gain control for that valve. In some circuits it may be across the cathodes of the first two valves. Coils should be checked for continuity and particular attention paid to the cathode decoupling condensers. Voltages should be taken whilst varying contrast control.

Sound on Vision in T.R.F. Sets

This is generally caused by either too big a signal input, or mis-alignment, or incorrect setting of sound rejector.

Alteration of Trimmers

The same warning applies as with a superhet. All these radio frequency transformers are aligned on a different frequency to give the correct bandwidth and indiscriminate altering unless the necessary instruments are available will result in either no signals or poor signals with insufficient bandwidth. The only two trimmers that it is really safe to alter are the grid circuit of V1—R.F.T.I. and the sound rejector trimmer. Again non-metallic trimming tools must be used.

Vision on Sound in T.R.F. Sets

This is nearly always due to mis-alignment although too strong an input signal can cause it. In very bad cases a slight movement of R.F.T.2 towards sound may cure the trouble.

Thirteen Channel Sets

These sets include those with a tuner unit built

into the set and those with an attached tuner unit or a converter

Taking the first type the receiver is very much the same as an ordinary superhet with the exception that the aerial, R.F. and oscillator circuits can be tuned to, or are pre-set tuned to any of the thirteen channels. The valves used are in most cases a double diode used as a cascade amplifier and a triode pentode frequency changer. This last valve changes the incoming frequency to the I.F. frequency of the set. Troubles here will generally be found to be valves, although as the channels are switched, trouble may be expected with switch contacts. Use a proprietary switch cleaner to do this job, rotating switch whilst applying. *Warning:* A lot of makers seal their tuning units and will not accept them for servicing if the seal is broken. My advice in this case is to send a faulty unit back to makers.

Sets With Converters

The most frequent of these is the type where the higher frequency channels are converted to the lower frequency Band I channel that the set is tuned to. Some have a power pack incorporated, and in others the H.T. and heater current is taken from the receiver. Here again, valve trouble or switch trouble will be the most likely cause of faults, although a check of components, and also the input and output circuits and connectors, should not be missed. In all these note that the frequency changer valve may show O.K. on a valve tester but is still not satisfactory in the set. This may be because the valve will oscillate perfectly at the lower frequencies but will not do so at frequencies of the higher channels.

(To be continued)

H.T. +


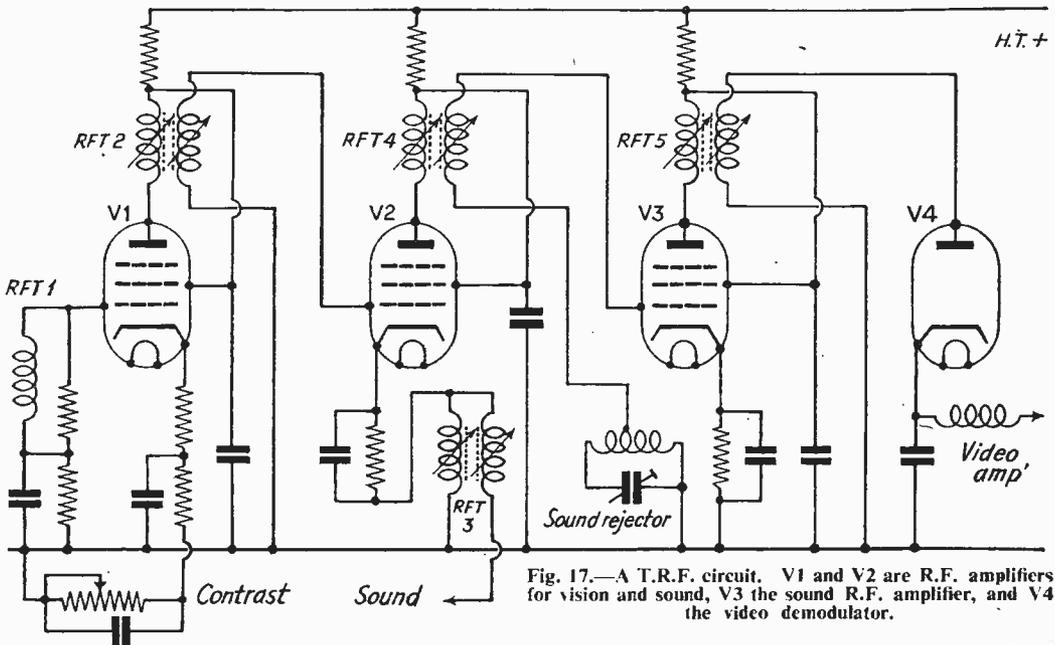


Fig. 17.—A T.R.F. circuit. V1 and V2 are R.F. amplifiers for vision and sound, V3 the sound R.F. amplifier, and V4 the video demodulator.

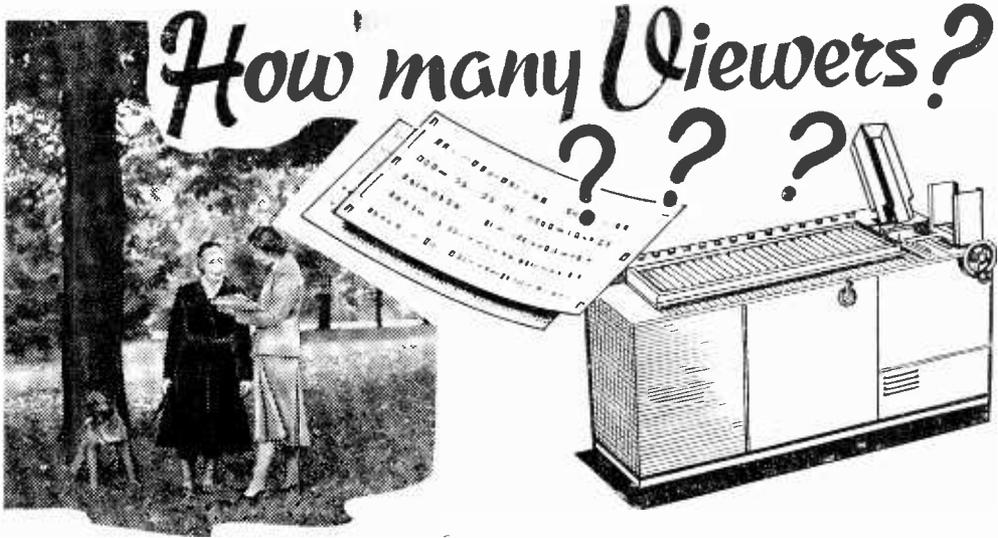

A BRIEF ACCOUNT OF THE METHODS OF ASSESSING THE SIZE OF AUDIENCES
AS USED BY THE BBC AND I.T.A.

FROM time to time one reads in the daily press that a certain programme was watched by so many viewers to I.T.A. to the detriment of an alternative programme on BBC, only to see a few days later a contradiction by the BBC. At the annual meeting of the I.T.A. recently Sir Robert Fraser, for instance, said, *inter alia*, that "in homes able to choose between them, 'Free Speech' has an audience seven times bigger than the 'Brains Trust,' 'Youth Wants to Know' twice as big as 'Press Conference,' 'This Week' twice as big as 'Panorama.'"

Three or four days later the BBC issued a statement in which it said, "The BBC did not understand figures issued by Sir Robert Fraser in his press conference . . . in fact the audiences for 'This Week' and 'Panorama' are fairly equal, with rather more viewing 'Panorama' on the average than view 'This Week.' Again . . . Sir Robert is reported as saying that I.T.V.'s 'Roving Report' has a larger audience in homes with a choice than the BBC's 'Hancock's Half Hour.' But a recent week—quite typical—shows 7 per cent. of the audience viewing 'Roving Report' and 17 per cent. viewing 'Hancock's Half Hour.' Sir Robert Fraser says Alan Taylor's last lecture was delivered to more people than saw 'It's Magic'—again, presumably in homes with a choice. The figures were: 4 per cent. of those homes heard Alan Taylor's lecture and 18 per cent. say 'It's Magic.'"

How do the respective authorities arrive at their figures? In the case of the BBC, personal interviewers are employed as will be described later, whilst the independent company use reports from an organisation known as Television Audience Measurement, who employ what may be termed mechanical methods. We therefore

think readers would be interested in an explanation of these two systems, although such explanation must necessarily be brief. They can then draw their own conclusions as to the reliability of the statements.

The BBC System

Every day a cross section of the public are asked about their previous day's listening (or viewing). Every Sunday people are questioned about Saturday, every Monday about Sunday, every Tuesday about Monday, and so on. In this way every day's broadcasting is covered.

Sampling the Population

It is unnecessary to question more than a cross section of the population because, as has been proved time and again, a properly chosen "sample" can be a reliable guide. The survey samples the population by questioning about 2,800 people each day, and as they are different people every day this means that getting on for 1,000,000 people are questioned in the course of the year. But the question is always the same, "what programmes did you listen to (or view) yesterday?"

The questioning is done by BBC interviewers scattered all over the United Kingdom who record the answers they receive on special "log sheets" on which all the programmes broadcast are printed. It is the interviewer's job to see that the person being asked recalls his listening and viewing accurately. Each interviewer is told to question a certain number of people daily, and he is told the kind of people they must be—so many men, so many women, for example, so many of each age group, so many occupied people and so many unoccupied, etc. This is extremely

important, for the 2,800 or so people questioned each day must be a representative cross-section of the whole adult population.

Result of the Survey

As soon as each day's "log sheets" come back to the head office, the number of people recorded as listening or viewing is counted, broadcast by broadcast. These figures are then expressed as percentages of the number of people questioned. Thus, one broadcaster may have a "listening figure," as it is called, of 5 per cent., another of 10 per cent., or another of 20 per cent. But, thanks to the laws of sampling, these figures can be taken to apply to the whole adult population so that it is fair to say that a broadcast which has a listening figure of, say, 10 per cent., was in fact heard by about 10 per cent. of the entire adult population of the United Kingdom.


In addition there is a viewers panel which is a voluntary body, and consists of viewers of all kinds. It is organised on a "family basis," its membership consisting of 600 viewing families, each serving on the panel for three months. They complete questionnaires sent to them weekly.

The TAM Method

According to Television Audience Measurement Ltd. audiences need to be measured scientifically, on a minute-to-minute basis. This is done by means of a Tammeter, an electro-mechanical measuring device designed by them. This is, to

all outward appearances an ordinary but attractive looking clock, suitable for use in the sitting-room or elsewhere. It has, however, a precision built movement and, connected to the back of the television set by a lead, it can be placed wherever required in the room.

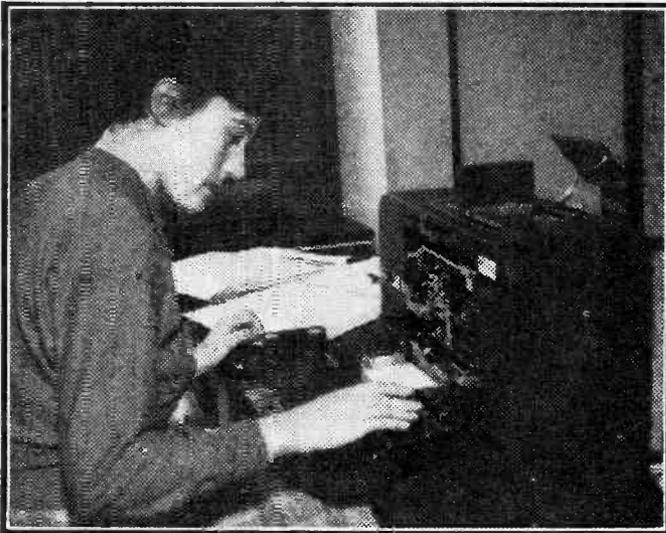At the back of the clock face and enclosed in



Transferring the information received by interviewers to punched cards ready for the sorting machine.

a locked cabinet to which the householder does not have access is a specially designed tape which is fitted in conjunction with the mechanism of the clock. The mechanism is so designed that when the set is switched on, the particular channel to which it is tuned is recorded on the tape.

Tammeter tapes are collected and replaced each week by field workers. When the used tape is removed from the Tammeter, the field worker checks the time of the clock with a chronometer. The clock is wound and a new tape, marked with a datum line showing the time it is put in, is inserted.

Analysis of Tammeter Tapes

The analysis of Tammeter tapes is done at the TAM Operations Centre at Berkhamsted, Hertfordshire. As tapes arrive from each I.T.V. area at the centre they are booked in on a Kardex system indicating the breakdown of the household, its social class, the number of children, the number in family, and the age of the housewife.


The tapes are then analysed on a Tamalyser, an electro-mechanical machine with a clock face and hands. The clock is set



A BBC interviewer, with a complete list of the previous day's programmes, asks a visitor to London which, if any, had been seen or heard.

to the time at which the tape was installed in the Tammeter and the datum line marked on the tape is set at the appropriate position on the Tamalyser. The tape is wound through and the Tamalyser gives an exact reading of the true time of when the television set was on and to which station it was tuned.

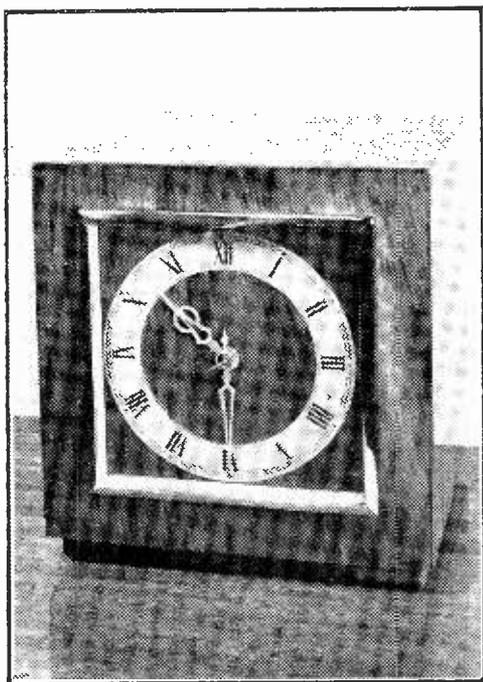The information on the tapes is then transferred, together with the panel number, to punched cards, which are then passed through a verifying machine to bring to light any errors which may have occurred during this process.



The Tammeter, which looks just like a simple clock.

The punched cards are then placed into a mechanical sorter which places them in correct order, day-by-day and minute-by-minute. Next, they are transferred to a tabulation machine which produces a sheet recording, for each minute, the number of sets tuned (a) to BBC and (b) to I.T.V.

This sheet is used for the computation of comparative ratings known as Tamratings for (a) each fifteen-minute period (b) each complete programme, and (c) for the plotting of graphs in the weekly report.

These Tamratings are an arithmetical average of the minute-by-minute percentage of homes viewing in each fifteen minute period or watching a specific programme as the case may be.

Commercials

Tamratings are also prepared for each commercial. Where the commercials are less than sixty seconds the Tamrating represents the percentage of homes viewing for the particular minute in which the whole or greater part of the commercial falls. Where they last over sixty seconds, they

are calculated on an arithmetical average as above.

Since a figure for the total number of homes able to receive I.T.V. is known from the random survey, Tamratings can be converted into homes viewing. So far as commercial Tamratings are concerned this enables the cost per thirty seconds per 1,000 homes reached to be calculated.

All relevant figures resulting from the analysis of Tammeter tapes are presented in weekly Tamratings reports.

Audience Composition

In addition to minute-by-minute programme and commercial Tamratings, it is important to know the actual composition of the audiences by persons. This information, too, is provided by Tam and is compiled from a sample of homes equipped with Tameters and Tamlogs. Members of these households record individually in the Tamlog, which is connected to the Tammeter and is fitted with an electric reminder device, whether they have viewed during each fifteen minute period.

The completed Tamlogs enable Tam to measure the percentage of housewives and other members of each family on the Tamlog panel viewing at any particular time. This percentage figure is then applied to the number of housewives, children, etc., in those homes in which the Tameters show the sets to have been switched on at that particular time.

By this means an accurate indication of audience composition broken down into the number of men, women, housewives and children, together with age groups for adults, is obtained. The panels who have the Tameters were selected as follows:

How Panels Were Selected

The panel in the London I.T.V. area was established from the surveying of a series of large random samples of homes throughout the area. The first sample taken was in June, 1955, when 3,000 homes throughout the area were surveyed. In addition, in order to gain a complete picture of homes throughout the whole area able to receive I.T.V. programmes, a further 2,000 homes in the outer regions were surveyed.

It was important that the field work for these random samples should be carried out scientifically and for this reason investigators entrusted with this work were previously trained to recognise the various types of television sets, adaptors, convertors and aerials, and to assess the quality of reception. It was their task to discover which homes in the samples had television; to examine TV sets found in the households visited, in order to determine whether the set was able to receive I.T.V. transmissions; and to assess, by having the set switched on, the quality of BBC and—when transmissions had begun—I.T.V. reception. To ensure that the households visited matched as nearly as possible the theoretically perfect sample which was selected in advance, up to six or seven calls were often made to make sure of contacting all the households selected.

A SWITCHED TV/F.M. RECEIVER

A COMBINED TV AND BAND II
SOUND RECEIVER


By R. Shatwell

(Continued from page 206, December issue.)

THE I.F. cans used throughout the set are somewhat taller than usual and were obtained from Radio Clearance in sets of three, wound for 34 Mc/s I.F. Seven are needed, but three sets were obtained. It will be found that if the connections to the side wires are unsoldered it is possible to force the existing windings along the former, and the sound I.F.s can be made up by so doing and removing a few turns as necessary. Other I.F. transformers can be made up using part of one winding, and the wire carefully removed from the other and used for the secondary. Only the discriminator transformer T6 and diode transformer T8 actually need a new start. These taller cans are not necessary in all cases, but their height protects the valves and enables the T bridge sound rejector to be in a common can with its input coil. The two spare cans will no doubt prove a useful addition to the spares box. T7 contains C44, C47 and C48 and care is necessary to avoid shorts to the can. Fig. 11 gives the position of the base pins and the cans are 2½ in. high. The pin 2 position used in T6 and T7 necessitates the insertion of a wire in this position.

The coil table gives the pin connection, top and bottom of winding, and all necessary data, but Fig. 12 gives additional data necessary for the discriminator. The tertiary and centre tap of the secondary are joined inside the can. The pass band of the transformer is broader than good quality necessitates, as is the whole sound channel, to simply switch tuning.

The sound input may appear unusual in that no tuned circuit is used at V4 grid. There are several reasons for this. Firstly, two I.F. stages after the common I.F. provide ample output. Secondly, as the switching necessitates a fair amount of switching at I.F., a tuned input must be heavily damped to avoid instability. Lastly, even a damped input circuit increases sound channel selectivity to a degree that makes tuning critical. If the set is to be used by the household it must be accepted that it will invariably be turned to the switch position desired and the fine tuner normally ignored. The present circuit makes this possible, particularly on F.M., without the average listener noticing any ill effect, even though a slight movement of the fine tuner may be necessary for exact tuning. The circuit also has negligible effect on the video channel.

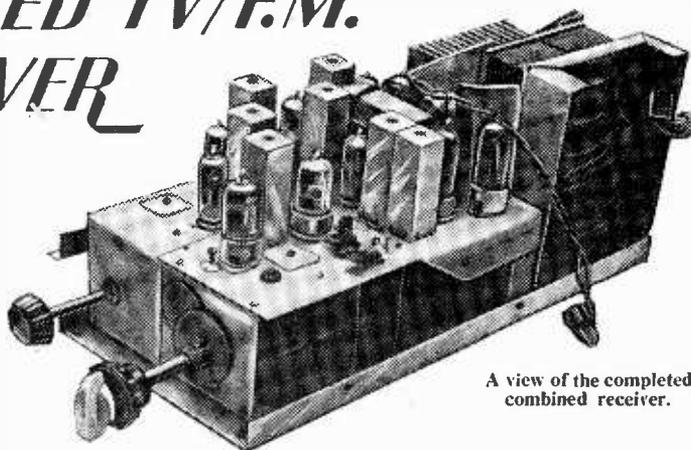

A view of the completed combined receiver.

Before any I.F. cans are fitted it is advisable to bolt down the tuner with 8 B.A. bolts, and then from the spare switch a length of actuating rod is cut, sufficient to extend from the existing rod to the rear of the chassis. Position a switch plate in alignment on the rear of the chassis, facing forward. Make certain that the contacts are in alignment throughout the full range and mark through the fixing holes, which should be at the position shown in Fig. 10.

The two wafers here need simple modification as shown in Fig. 6 (B and C) for wafers 8 and 9 respectively. Wafer 8 needs the contacts removing at the F.M. positions, this being neater than leaving them blank. Wafer 9 switches the heater line to video and timebases, and it was with some trepidation that a trial was made of the capabilities of a single contact. It was found that that would make, break, and carry 5 amp. at 6.3v. without heating or measurable voltage drop. To provide a good margin this wafer was modified to provide two contacts at all TV positions, making use of the stabilising contacts previously mentioned. This involves removing three contacts, refitting one in a new position, and moving the rotating contact to a new position, at the same time inserting another taken from the spare wafer. These can be removed and repositioned by slightly lifting the securing plates at the back of the switch. Removal of the spare one from the tenth wafer will make the process obvious. The fixed contacts are then all linked with 22 s.w.g. wire. Spacing between these wafers, and to chassis, is 3/16 in. The linking of the actuating rod is made by a simple thin metal sleeve, bent about the joint and squeezed tight. No mechanical strain is involved. In all sketches the wafers are shown in the first TV position, the apparent change in the position of the actuating slot is caused by the fact that whilst wafers 1-7 face the rear, wafers 8 and 9 face forward.

Wiring

The I.F. cans, tag strips, and other fixed components can now be fitted and the heaters wired, sound and tuner to the input to wafer 9 and

video to the output from this wafer. Similarly the H.T. parts can be taken to the appropriate tag at the chassis rear. After the cathodes and all decoupling condensers have been wired in, along with the H.T. resistances to each valve, the general wiring can be completed. Note that C32 is repeated at T5 and T6. The tuner takes its H.T. and 6.3v from V3 and its adjacent tag strip.

The photos show the output transformer secured on top of the chassis between the video and sound stages, and it will be found that there is room here for a standard-sized component. No "tone correction" is fitted and quality is good, being nicely balanced and quite up to commercial standards.

This chassis completed the tuner unit should be bolted down and wired in. The interconnection consists of H.T. and 6.3v lines. V3 grid to T2, V5 anode, T5 and T6, and three connections to wafer 7. R27, R28 and C38 are wired between the wafer and the main chassis. The volume control is mounted on the main chassis and is ganged with the on/off switch. This is the only practical arrangement as this is the only control operative on both TV and F.M. The introduction of hum is avoided by screening the leads and by introducing the control after the L.F. stage. The switch leads should be of twisted flex taken with the screened leads in a straight line to keep them clear of the F.M. detector.

Power Supply

This follows standard practice, using a heater transformer but taking its H.T. direct from the mains via an RM4 metal rectifier. The transformer can be purchased or made up to the following data. Fig. 13 gives the laminations used but so long as the core area and winding space is correct use can be made of other types:—

Secondary watts 10×6.3 70 w
 1×6.3

Efficiency 80 per cent., therefore primary watts 87 w.

Core area 1.75 sq. in. or 1.4in. stack of 1.25in. centre limb.

T.P.V. 4.5.

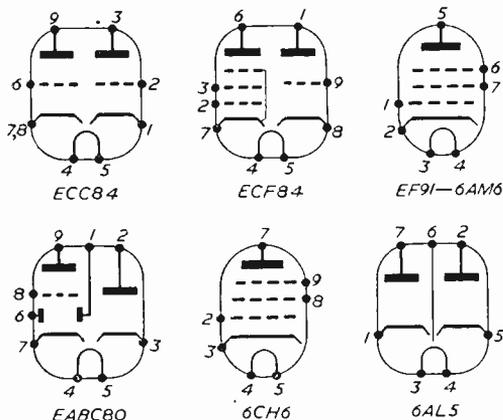



Fig. 14.—Valve base connections.

Primary 1025 of 28 s.w.g. enam. layer wound with tissue interleaving.

Secondary (1) 30T of 2×16 s.w.g. enam.

Secondary (2) 30T of 22 s.w.g. enam.

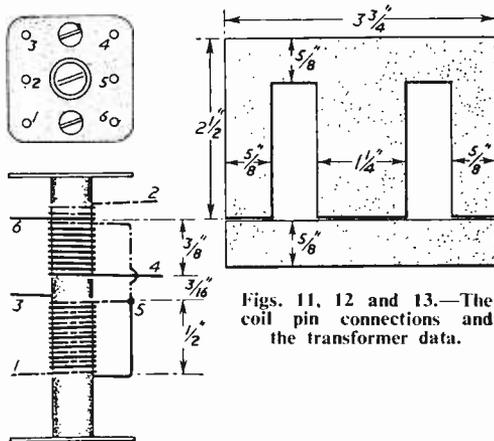Primary and secondary turns are compensated for voltage drop and wire gauges assume home winding, which is rather less compact than the commercially-made transformer, and hence runs somewhat cooler. The 2×16 s.w.g. winding is simply wound, bifilar fashion, the ends being joined externally and is used to avoid cumbersome wire gauges.



Figs. 11, 12 and 13.—The coil pin connections and the transformer data.

Fig. 4 gives the circuit and Fig. 15 the under chassis layout. The choke is on the chassis top. RS, RV and RTB are small 5 watt types and should be adjusted so that HT(s) is about 180-190v. H.T. (v) 200v, and H.T. (TB) 190v. This is normally obtained with all three resistors about 350 ohm, but varies with the mains voltage and also with the condition of the rectifier used. Assuming a new rectifier and 240v. mains, 350 ohms will suit practically all cases.

18 s.w.g. aluminium is suitable for the chassis, and after the receiver and power supply are bolted together, the whole is made rigid by angle aluminium as shown in the photos. The fixing bolts for switch plates 8 and 9 pass through both chassis and the grommet holes must similarly be continued through each. The heater chassis connection from the transformer secondary should be made to a bolt passing through both chassis. The RM4 is secured to brackets on the transformer as shown in the photos. Note that its orientation is such that it is correctly ventilated in either horizontal or vertical use of the receiver. The only other point worthy of mention is that if possible the large capacity condensers should be reformed before use by being placed in series with a meter and about 150v. until the current flow has settled at a minimum, usually in about 15-30 minutes. If the voltage can be increased gradually to the working voltage so much the better. Although most condensers are now date stamped, it is surprising how heavy a current can be drawn if the full voltage is applied and storage conditions have not been good. All electrolytics, including bias condensers, etc., were obtained with the coil

cans from a dealer in surplus, and would have been quite safe to use directly, as reforming was completed in a matter of minutes, but the practice is still a safeguard.

When heater and H.T. lines are connected the set is ready for testing and the signal balancing wafer should have all fixed contacts earthed for the time being. At this stage it is advisable to insert a meter in the rectified H.T. before CR. Assuming no timebases are connected the current will be 90-110 mA approximately. If no cause for alarm and no untoward symptoms after a few minutes, remove meter and insert in video H.T. line. If this is in order, remove the meter and alignment may be started.

Alignment

This should be started with the sound channel as this is the channel used to establish the signal. For the sake of the household in general the speaker should be disconnected and the volume control turned down, lining up being done by phones connected across the volume control, isolated by two .1 uF condensers. Set the tuner to position 2. Inject 38.15 Mc/s at high level to V5 grid and align T5, move to V4 grid and align T4, reducing input as necessary, and again peaking T5. Repeat with generator at V3 grid. T3 should also be tuned to this frequency at present.

The phones should now be transferred to the video output (C57) isolated as before. Inject 36.65 Mc/s at V9 grid and peak T8. Move to V8 grid and peak T7 primary at 37.5 Mc/s, T7 secondary to minimum at 38.15 Mc/s and L26 to maximum at 35 Mc/s. Transfer generator to tuner test point and adjust T2 to maximum at 36.65 and T3 at 35 Mc/s. If necessary, short R7 for this operation. With generator still connected here repeat alignment throughout, starting at T8.

Again move phones to the sound channel and check alignment here. Switch tuner to position 5. Leave modulation on and adjust T6PR1 for maximum output and secondary for null point. This should be sharply defined, output increasing as it is approached then dipping, to increase again as it is passed. Repeat the lining up of this transformer until no improvement can be obtained. A more precise alignment can be made if a high resistance voltmeter on 10v. range is connected across C37 and T6 primary adjusted for maximum output. Transfer

the meter to the junction of R.25, 26 and of R27, C39, and adjust secondary until meter gives a "nil" reading. Further adjustment will send the meter pointer backwards. For this method of lining up the generator must give an unmodulated output. The whole sequence should be repeated to ensure accuracy, as the cores may interact to a slight extent.

The phones should be left on the sound channel and the Band III signal should now be sought. Procedure here will assume the actual signal is to be used, and a flexible insulated lead should be connected to the aerial lead-in (inner conductor), and terminated in a prod of about 22 s.w.g. clean wire, hooked to enable it to be connected as necessary, and insulated with a sleeve up to the hook. The outer braid of the aerial lead can be connected to chassis, but at all times ensure that the chassis is neutral and not live to earth. If one channel is available on Band III it should be tuned on the second switch position, if two are available the highest channel should be on position 1, but it will be necessary to line up initially on the strongest available signal. The only other accessory needed is a "tuning wand" of insulated sleeving with a piece of iron dust core inserted in one end and a piece of brass in the other.

Connect the aerial hook to C⁸ C⁹ junction and adjust C15 for sound output, which should be within its range. If the harsh modulation of the vision channel is heard C15 needs closing
(To be concluded next month)

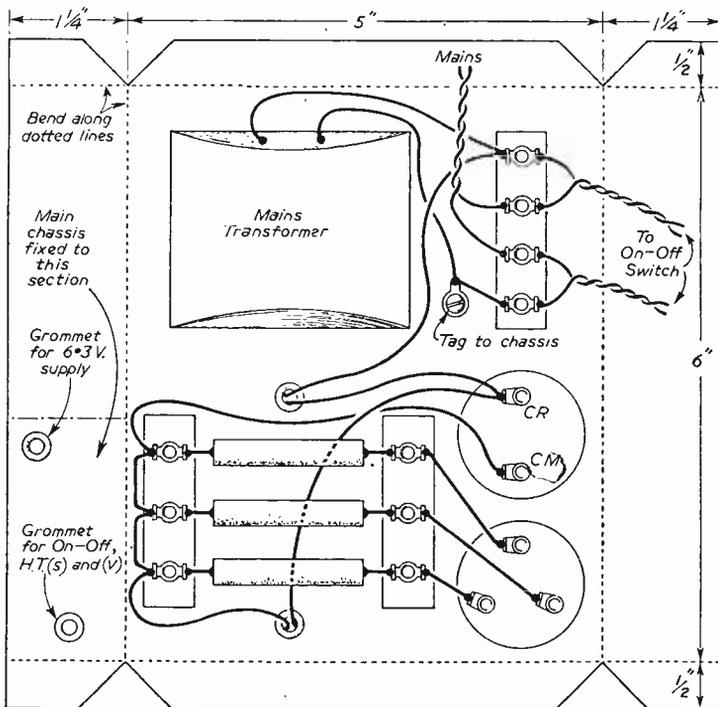


Fig. 15.—Wiring diagram of the Power Pack. The circuit appeared in the November issue.

FLYWHEEL SYNC. & A.G.C.

AN EXPLANATION OF THESE CIRCUITS, AND METHODS OF INCLUDING OR ELIMINATING THEM IN EXISTING RECEIVER CIRCUITS (2)

By H. Peters

FAULT finding in the Fig. 3 circuit given last month follows the general lines of the double diode type, but it should be noted that the sync. pulse is required to be positive going and so a stage of line sync. amplification is usually provided to get it the right way round. When disconnecting this type of discriminator it is better to take the 10pF sync. feed straight from the anode of the sync. separator proper, and to ensure that the coincidence detector does not have any effect on the line oscillator the link which transfers the control voltage to the oscillator should be disconnected. This may alter the range of the line oscillator, and the anode load of the coincidence detector may be required to be transferred as well to offset this effect and provide a steady potential at this point.

The explanation given for this system specifies positive going sync. pulses at the grid. In some receivers it is more convenient to feed in negative pulses, and it should be noted that the circuit works in a similar manner except that the sense of the control voltage at the anode is reversed.

Sinewave Oscillator Systems.

These are the true "flywheel" sync. systems, as the others already mentioned are more accurately called automatic phase control. Ideally the "flywheel" is a resonant circuit which almost oscillates at its natural frequency of 10,125 c.p.s., and which is shock excited into oscillation upon the arrival of the sync. pulses. One sync. pulse absent here and there will make little difference to the oscillation frequency, and the output of the "flywheel" can then be distorted until it is a square wave. This square wave is fed to the line oscillator as a sync. pulse instead of the one received from the transmitter.

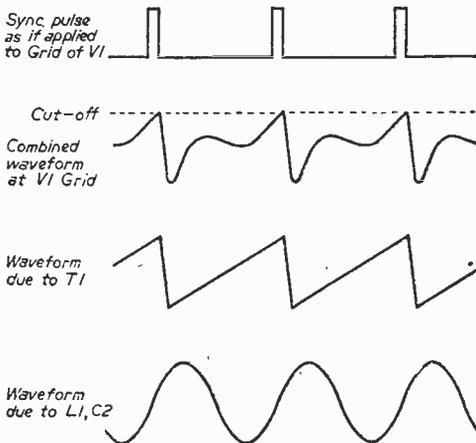


Fig. 6.—The waveforms of the circuit in Fig. 5 on page 266.

This sounds so simple that there must be a catch in it somewhere, and there is. To prevent wavy pictures or "strobing" the transmitted system is locked to the National Grid by a counting system which is a kind of flywheel sync. system of its own. The frame sync. pulses (which are two to a line and thus twice line speed) or 20,250 c.p.s. are divided by 405, and the answer is 50 c.p.s., which is the nominal mains frequency.

If the National Grid is one cycle fast or slow the counting system automatically alters its sum to $20,655 \div 405 = 51$ or $19,845 \div 405 = 49$, and so the line frequency becomes $10,327\frac{1}{2}$ or $9,922\frac{1}{2}$ cycles per second.

A flywheel system sharply resonant at 10,125 c.p.s. would not be able to cope with these variations and so has little practical use. Another snag is that even if it was a working proposition there is no guarantee that the phase of the line time-base would coincide with the phase of the picture and this would cause the famous picture-cut-in; no effect known as "false lock." A practical circuit using a sinewave oscillator is given in Fig. 4.

On the face of it there is a marked resemblance to Fig. 2, but a closer look reveals at the outset that D1 and D2 both face the same way. Negative going sync. pulses are fed to the cathodes via $\frac{1}{2} L1$, causing each diode to conduct equally to build up equal and opposite voltages across R1 and R2 (which are also equal). So in the absence of any other influence, points X and Y are at the same potential and the junction of R1, R2 is zero. These sync. pulses are not integrated, in fact they arrive from the sync. separator through a large enough condenser to keep them substantially square in shape. T1 is the sine wave oscillator. It is cathode coupled and uses the screen, grid and cathode of V2 as its triode. L2 and C1 tune the circuit to line frequency and the sine wave output is fed in push-pull to the pair of diodes by L1. In the absence of sync. pulses the diodes conduct equally and alternately, causing points X and Y to wag alternately positive and negative equally and in opposition. The average voltage at these points is zero and so is the average potential difference between X and Y.

If we now quietly introduce the sync. pulses at the instant when the sine wave oscillator is passing through zero (i.e., in synchronism) the voltage between X and Y is the sum of the voltage due to the sine wave oscillator (zero), and that due to the sync. pulse (zero)—which is zero. Should the sync. pulses arrive slightly later one of the diodes, say D1, will be conducting and D2 will be cut off.

The pulse on the cathode of D1 will add to its total current, whilst the other one will get nowhere. D2 being cut off. The average voltage at X will thus become negative with respect to Y and can be used as a control voltage for the

system. If the sync. pulses arrive earlier than zero potential, D2 will be the conducting diode and Y will then be negative with respect to X.

In the diagram point X is tied down to a fixed bias and therefore Y varies up and down to provide the control voltage.

This is passed through the usual time constant filter, which is really the "flywheel" device (not T1, as one would suppose) to V1, which is a reactance valve, arranged so that a change of grid voltage produces a change of anode capacity. This variable capacity is effectively across L2, C1 and will vary the resonant frequency by small amounts to correct the difference between the line and sync. frequencies. The pentode section of V2 is designed to distort the sine wave produced between cathode, grid and screen, so that it approximates to a square wave with a sharp leading edge which is suitable for synchronising the line oscillator.

Horizontal hold is controlled in this circuit by varying the negative bias to point X, about which the reference voltage varies, and this is sometimes done by a control inserted in the grid leak of the line output valve. This can be mistaken on a circuit for the reference pulse fed back in A.P.C. systems and may at first give a wrong impression of the type of flywheel sync. employed. It will be noticed that the sine wave at D1 and D2 passes twice through zero each cycle, and this would appear to give the system a choice of two operating conditions 180 deg. apart.

Fortunately this is not so, as at only one of these points will the correction voltage work the right way. At the other one the D.C. developed

will be in the wrong sense and will push the line oscillator off tune instead of locking it in.

The phase of the output waveform can be varied against the sync. input by adjusting the core of L1, and this has the effect of moving the picture sideways in the raster. The setting up drill is therefore important and is given here in preference to individual fault-finding tips.

First remove all trace of signal and with the width reduced, centre the blank raster magnetically on the screen with equal amounts of black edge all round. Restore the signal and make a bright under-contrasting picture. Remove the sync. pulses by shorting down point Z to chassis, and with the horizontal hold control set at midway adjust the core of L2 until the picture slowly runs through lock. Remove the short from Z and adjust the locked-in picture until it is in the centre of the raster by means of core in L1.

To change this type to pulsed sync. is not as simple as it looks; it is not sufficient to transfer the sync. lead from point Z to the anode of V2 and stop the sinewave oscillator, as the amplitude of the generated squarewave is great enough to be classified as "drive" to the line timebase.

In the Ferguson system the top half of V2 is indeed the left-hand valve of a multivibrator arrangement, and its free-running speed with T1 inoperative is very low and very harsh. Rather than set about redesigning the stage it may be better to increase the pull-in range by reducing C2 in the time constant circuit, or to permit T1 to oscillate at its natural frequency and to apply the sync. feed to the grid or cathode of V2 instead.

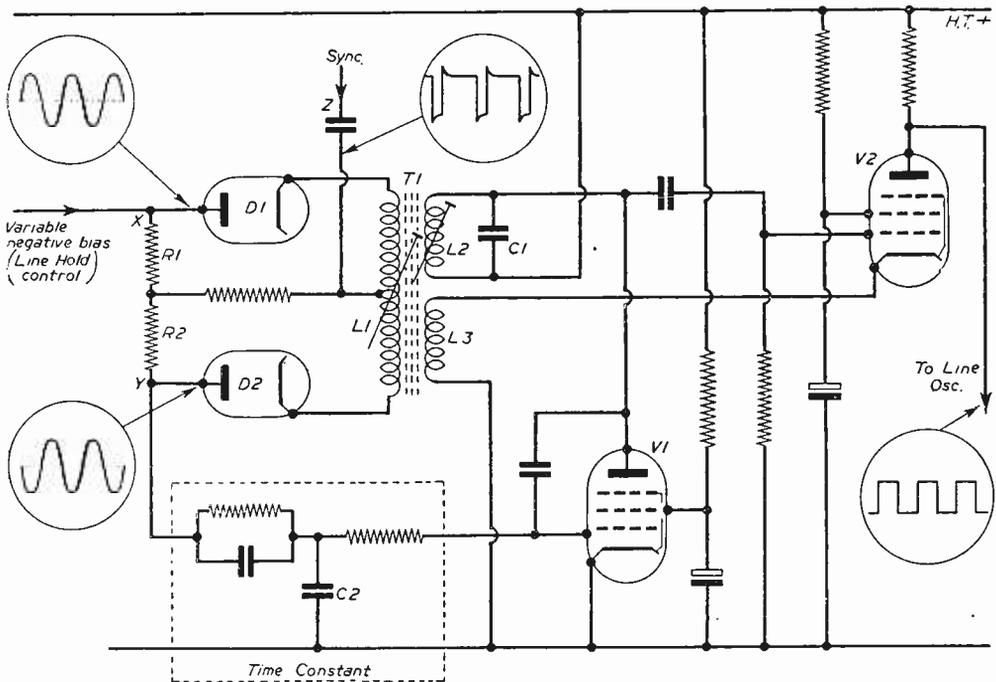


Fig. 4.—A sinewave system. V1 is a reactance valve, and V2 a cathode coupled sinewave oscillator, and pulse shaper.

Synchroguide System

The system shown in Fig. 5a has been developed by the Plessey Company, Limited, and is being fitted increasingly into British sets. Its virtues are simplicity, cheapness, and reliability, and in future years may well become the standard system.

V2 is a blocking oscillator using transformer T1 with C1, C3, R1, R2 in a conventional arrangement. V1 is a coincidence detector behaving similarly to the one in Fig. 3, except that it is a triode and the control voltage is taken from its cathode. The two waveforms are applied to the grid and cathode.

L1 C2 is a tuned circuit resonating at line frequency which is shocked into damped oscillations by the output of T1. A combined sine-sawtooth waveform is fed through R3 to V1 grid, and its composition is illustrated in Fig. 6 with its two components drawn immediately below. Notice that the sawtooth and sine wave are added in a way that produces a sharply rising spike at the end of the line scan, and since V1 is biased well back by R3 R5 only the tip of this spike rises above cut-off.

V1 is thus quiescent except at that period, and even then cannot conduct fully. Incoming sync pulses are shown on the same diagram (Fig. 6) as positive going and are assumed applied at the grid. In practice they are negative and applied at the cathode, which you will recall, amounts to the same thing but saves manufacturers an

inverting valve. The pulses are kept as square as possible and the free running speed of T1 is adjusted so that they coincide with the middle of the flyback time for correct locking. When the timebase runs below the sync. pulses will slide up the flyback line and more of them will appear above the cut-off line, causing V1 to pass more current and increase the voltage across R2 R4. This increase is filtered by the usual time constant or "anti-hunt" circuit to V2 grid, where the rise in voltage will speed up the timebase and correct the error. You are invited to work out the case for the fast-running timebase yourself, assured that it behaves in an opposite manner, producing a negative change at V2 grid.

The Line Hold Control

The line hold control varies the anode voltage of V1, which alters the standing voltage across cathode resistors R2 and R4. This variation is used to control V2 grid in the same way as the correction voltage.

The saw tooth voltage to drive the line output stage is taken from the top of C3, which is the discharge condenser of the blocking oscillator. This keeps the drive free of the sinewave due to L1 C2, and as the anode load is taken to the boost rail, the saw tooth amplitude is sufficient for wide angle scanning and the timebase works on a reasonably linear portion of the discharge curve.

(To be continued)


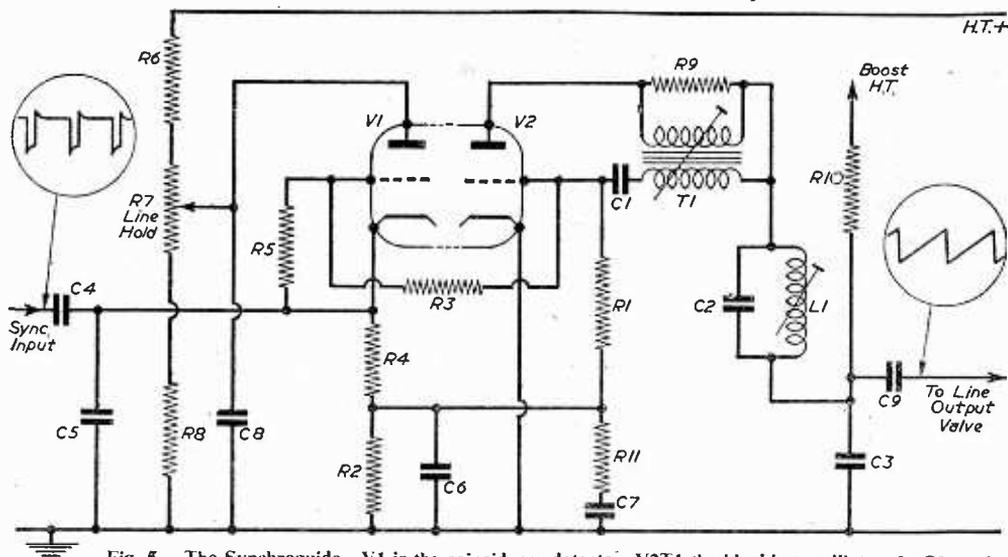


Fig. 5.—The Synchroguide. V1 is the coincidence detector, V2/T1 the blocking oscillator, L1/C2 produces damped sinewave at line frequency. (Courtesy of the Plessey Company Limited.)

LIST OF PARTS FOR FIG. 5

C1—560 pF	C6—.01 μ F.	R3—270 K.	R8—27 K.
C2—.015 μ F.	C7—.5 μ F.	R4—120 K.	R9—47 K.
C3—1,200 pF.	C8—.1 μ F.	R5—470 K.	R10—68 K.
C4—100 pF.	R1—150 K.	R6—33K.	R11—4.7 K.
C5—330 pF.	R2—100 K.	R7—100 K.	V1 and V2—ECC82 (or equiv.).

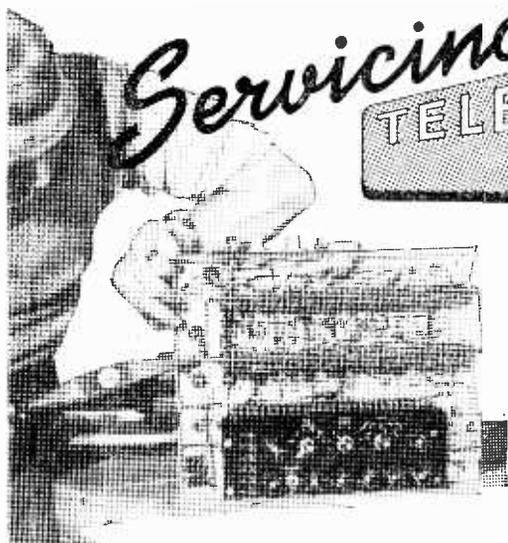

Servicing TELEVISION RECEIVERS

No. 34.—THE ULTRA VT917 AND WT917 (WITH NOTES ON THE ULTRA TUNER UNIT)

By L. Lawry-Johns

confusing at first sight, but a short explanation, together with a close study of the diagram, should leave little doubt as to the part played by each section.


Early models had provision for an additional I.F. amplifier for fringe working, and where this was fitted resistors R15 and R18 are deleted. In later versions this I.F. stage is fitted as standard and therefore the resistors are not fitted, and pin 1 of socket A is now taken to pin 3, i.e., the connection between V15 heater and pin 1 of socket A is now taken to pin 3.

THE VT917 is a table model tunable to any of the five BBC channels and to two Band III channels. The WT917 is the same receiver in a console presentation. Both incorporate a separate tuner unit which is connected to the main chassis by two plugs (A and B, as shown in the diagrams). The C.R.T. is a 17in. Mazda CRM171. A similar receiver, the 915, employs a CRM142 14in. round tube.

These receivers are suitable for connection to either A.C. or D.C. mains, 200-250 volts, employing various types and ratings of valve heaters in a series parallel arrangement such as was mentioned in the last article on the K.B.

The heater circuit diagram may tend to appear

Inspection of the diagram shows a complete .2 amp series of valves 13-16 wired from R61-R62 to Y which point is the cathode (pin 1) of V16, the sound detector, which, from a heater current point of view, is at chassis potential. All the "20" series of valves are in this chain which, apart from the mains dropper, is independent of the other valve heaters. V11 is the first valve of the other composite chain. This valve (U329) has a .3 amp heater and this current is split into three .1 amp channels to supply the "10" series valves before application to the tuner unit

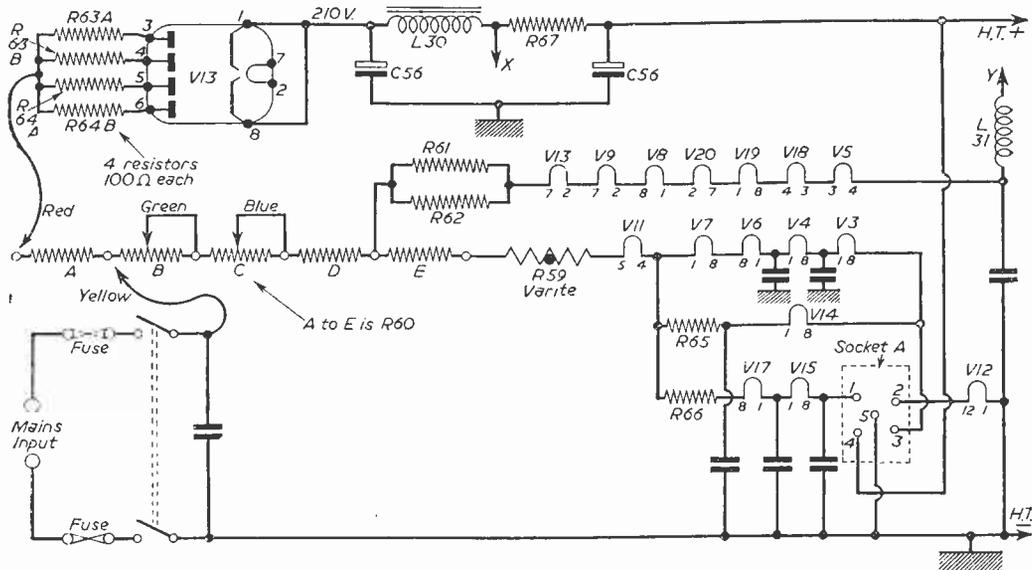

Power Pack heater circuit is completed when plug A of the tuner unit is inserted. L31 is joined to heater of V16.

THE MULTIMINOR

This splendid new AVO Instrument has been developed to meet a definite demand for a sturdy pocket-size multi-range test meter at a modest price, suitable for use on modern electronic apparatus as well as for radio and television receivers, motor vehicles, and all kinds of domestic appliances and workshop equipment.

Readings are obtainable quickly and easily on a very open scale, and range selection is by means of a robust clearly marked rotary switch of the characteristic AvoMeter type. Measurements of A.C. and D.C. Voltage, D.C. Current, and Resistance are made by means of only two connection sockets.

Designed and Manufactured by

AVO Ltd.

19 RANGES

D.C. Voltage	A.C. Voltage
0—100mV.	0—10 V.
0—2.5V.	0—25 V.
0—10 V.	0—100 V.
0—25 V.	0—250 V.
0—100 V.	0—1,000 V.
0—250 V.	
0—1,000 V.	
	D.C. Current
	0—100μA
	0—1mA
Resistance	0—10MΩ
0—20,000 Ω	0—100mA
0—2M Ω	0—1 A

List Price :

£9' 10s.

complete with Test Leads and Clips.

AVOCET HOUSE · 92-96 VAUXHALL BRIDGE RD. · LONDON · S.W.1



Leather Case if required 32/6

Pocket size : 5½ x 3½ x 1½ ins.
Weight : 1 lb. approx.

Sensitivity :
10,000 Ω/V on D.C. voltage ranges.
1,000 " " A.C. " "

Accuracy :
3% of full scale value on D.C.
4% " " " " " A.C.



Telephone : VICTORIA 3404 (9 lines)

M.M.2.


HIGH GAIN BAND 3 T.V. CONVERTERS

NO ALTERATIONS REQUIRED TO YOUR SET

RETURN OF POST SERVICE. All new goods.

Posted orders to Camberley, please. All 3/- each extra post (4/- for 2), 2/- extra C.O.D.

Following apply to all converters : full instructions supplied. Can be fitted in 10 mins. ; free from drift ; fitted with co-axial plug ; fully wired ready for use ; with power pack, including metal rectifier ; double wound transformer ; 2 valves ; mains on-off switch ; fine tuner ; B.B.C. to I.T.A. at turn of switch ; 12 months' guarantee (B.V.A. valves 90 days) ; Terms available, one-third down and balance plus 7/6 in four equal monthly payments ; postage with first payment. **FOR ALL SETS EXCEPT EARLY PHILIPS.**

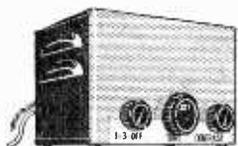

£4.7.6

With metal cabinet as illustrated. Stove enamel grey hammer finish. 5in. x 7½in. x 4½in.

Pattern rejector fitted. State local B.B.C. station. Walnut wood cabinet, £4/17.6. Chassis less cabinet, £3/17.6. Variable attenuator, 7 6 (l.-p. & p.). Aerial splitter, 8 - (l.-p. & p.). External crossover unit, 7/6 (post 1/6). Genuine low-loss co-axial, 8d. yd.

Postal charges in brackets.

Ex-U.S. Army Valves 6K6 GT/G 5 6 (9d.)
I.F. Transformers by Gorler AM, FM (10.7 Mc and 465 Kc), 15/- pair (l.-).
Screens for T.V. PERSPEX, tinted, 14in. x 11in., 5/- (2'-);
White 14½in. x 11in., 5/- (2'-); 17½in. x 15in., 7.6 (2.6).
LAMINATED GLASS, tinted, 14½in. x 11in., 5/- (3.-); 17in. x 13½in., 7/6 (3.6).
Battery eliminator for 4 low consumption valves 90v. 15 ma. and 1.4v. 125 ma., 35/- (2.6).

13 CHANNEL CONVERTER

Switch positions, off-I.T.A.-B.B.C. Valves PCF80 and PCC84. Moulded cabinet 8½in. x 4½in. x 6in.

Don't confuse with similar article being offered without power pack.



£4.15.0

Robust Band 3 AERIALS, for 1in. to 2in. diam. mast or for loft. 3-element, 27/-; 5-element, 35/-; 9-element, 55/-; carr. pd. Belling-Lee 6-el., 37/6.

AUTOMATIC RECORD

CHANGERS are in short supply. Collaro RC456 Studio turnover crystal pick-up. 4-speed mixer. A.C. mains 200-250 v., see illus. ALSO Collaro single player AC3/554. 3-speed, turnover crystal, pick-up with "T" head. £6/16.6 (3.6 p. & p.).




£8/16.6 (5/- p. & p.)

GLADSTONE RADIO

82B, High Street, Camberley, Surrey. 3, Church Road, Redfield, Bristol. Tel. 51207.


is improper contact between the coil studs and the springs in the tuner unit. This shows as intermittent signals which vary in strength and which are temporarily restored by operating the channel switch. This should not be confused with incorrect alignment which is artificially corrected by setting the switch at a "between" position. The springs may be adjusted but this is not advised unless it is really necessary since it is quite easy to distort the springs with the result that no signals will be received at all. If it is necessary, the tuner lid and bottom cover should be removed in the following manner.

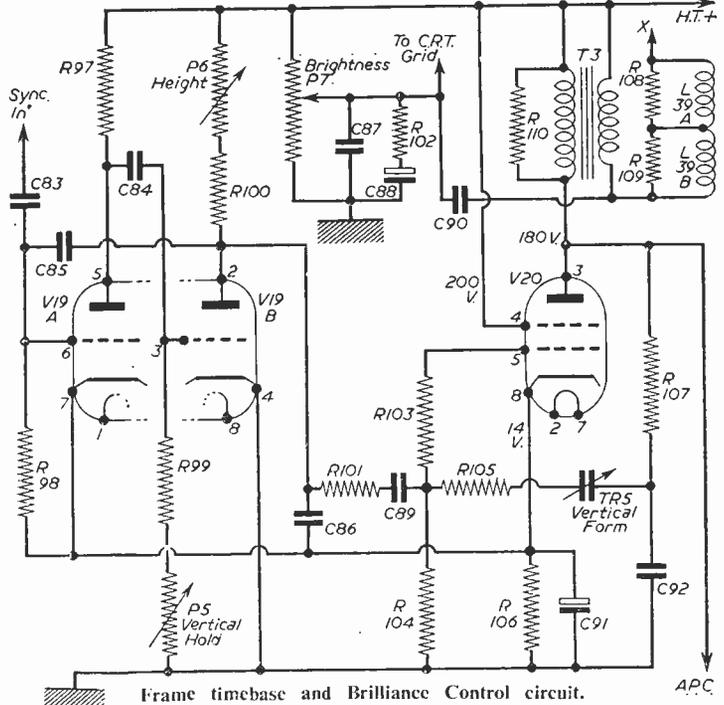Remove channel switch and fine tuner knob. Remove the plugs "A" and "B" and the three knurled nuts holding the unit to the side of the cabinet. To facilitate this, the tuner lid should be unsprung from the side and lifted off. This makes the removal of the upper rear nut easier. The bottom cover is removed by unscrewing the P.K. screws along one side and the front of the unit.



Frame timebase and Brilliance Control circuit.

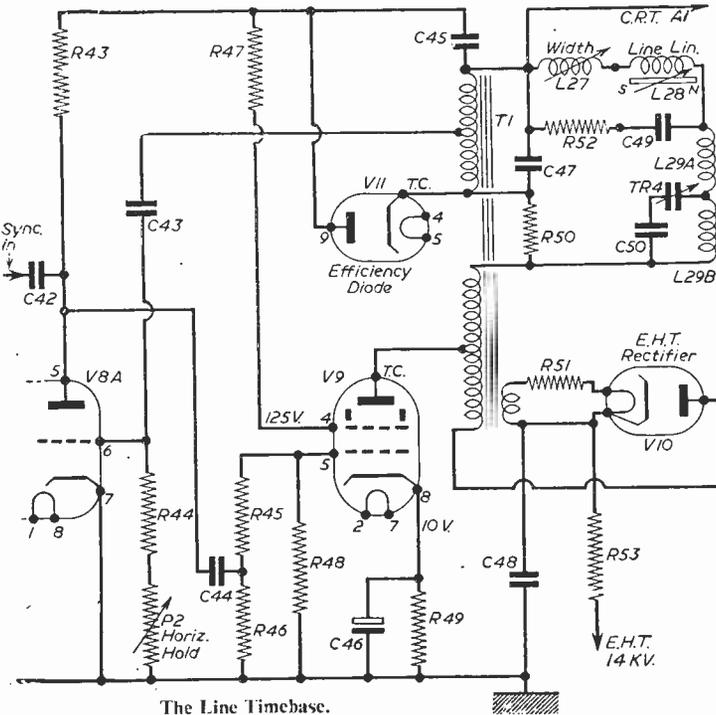No attempt should be made to adjust the springs until the coil carriage has been removed.



The Line Timebase.

On the top front end of the unit is a P.K. screw securing a small plate which limits the travel of the carriage. Remove the plate and unspring the BBC (upright) oscillator coils. These are the coils with the three coloured tuning knobs. The carriage cannot be pushed to the rear far enough for the cutouts to engage in studs unless the coil bank is removed and the switch lever is disengaged (slacken screw and move lever along spindle). The switch lever is located under the unit and is attached to the switch spindle. Having removed the carriage carefully inspect the springs, clean and adjust slightly by increasing the bow of the spring if necessary. On no account must the springs be made too proud as this will cause the carriage to foul them and result in permanent damage. When the carriage is replaced, move it over the springs carefully to check this point before replacing the switch lever, etc. To

replace the BBC coil turret, engage the top and bottom retaining springs on the inside of the carriage first, push against these and clip into the other side slot.

To retune the coils, adjust the Band III section first. With the tuner connected and the top cover off, switch on the receiver and allow a good 10 minutes to warm up.

Switch to the desired channel, set the fine tuner to midway and adjust the oscillator coil core (whichever is in contact with the springs) marked X on the tuner diagram for maximum sound, with TR3 set so that its stem is some $\frac{1}{8}$ in. above chassis. If signals are not up to standard, adjust TR1, TR2 and TR3 for optimum sound and vision. Note that the cores marked X are the oscillator coil cores Band III Channels 8 and 9. The other end of the same former carries the R.F. coils and thus the brass slugs at this end are for R.F. tuning complemented by TR2 and TR3. It is, therefore, not likely that these cores will require adjustment unless both Channel 8 and 9 are required, or if both coils are required to be set for the same channel. Band I tuning is somewhat simpler. Switch to BBC, set fine tuner midway, adjust red knob for maximum sound, yellow midway between maximum sound and vision, blue knob to maximum sound and the white knob to maximum vision. Before leaving the tuner unit it is pointed out that the two resistors at the rear of early versions are R15 and R18 which are not fitted to later models. It is normal for these resistors to run warm. A spare PCC84 should be kept as a slight deterioration in V1 can cause excess noise (picture grain) and weak signals, especially on Band III.

Circuit Description

Signals are fed from the aerial socket to the


aerial coils and to V1 where they are amplified in a cascade circuit. They are then passed via the R.F. coils to the V2 pentode mixer grid together with the triode section (oscillator) signal, the resultant signals appearing at I.F. at the pentode anode of V2, tuned by L10 and passed via plug B to the main receiver. The vision I.F. signals are passed via L13/L15, V3 (10F1), L16/L17, V4 (10F1), L20/L21 to V5 (20D1) for detection. L18/L19, L22 and L23 are sound rejectors. The sound I.F. signals are picked off by L14, applied via L32/L33 to V14 (10F1), L34/L35 to V15 (10F1), L36/L37 to V16 (20D1) for detection. Video signals are taken from pin 1 of V5 via L24 and L25 and are developed across R32 (4.7K Ω) in the grid circuit of V6 (10F1), the video amplifier. Video signals are developed across R35/R36 and are applied via C95/R54 to the C.R.T. cathode. The composite video waveform is also passed via R37/C40 to the sync. separator V7 (10F1) and also is directly coupled to the cathode of the interference limiter (V5B), the anode of which is "held off" by the limiter control P1.


A three position plug is incorporated in the cathode circuit of V6 and is located on the rear centre of the chassis. The correct setting is that which offers the best definition consistent with picture noise, grain, etc., i.e., local conditions.

A.P.C.

The automatic picture control circuit used depends upon the signal obtained from the control grid of the video amplifier, which, of course, varies with the picture content, and another obtained from the anode of the frame output valve. This latter pulse is of constant amplitude being that of the frame flyback.

(To be continued.)

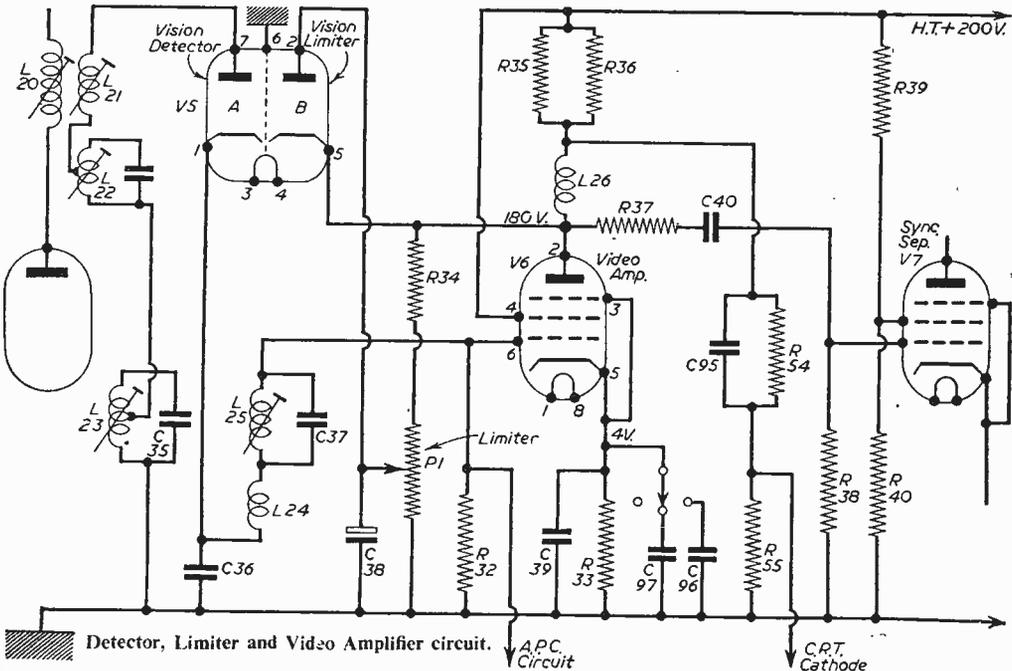

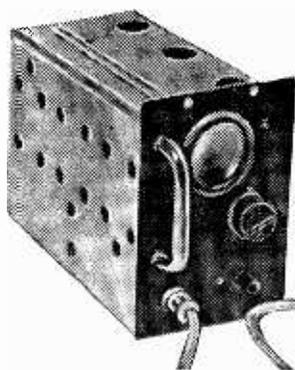

A Simple Valve Voltmeter

AN EXPERIMENTER'S UNIT BUILT IN AN RF26 CASE

By R. I. Jenkins (GW3DVG)

THE little instrument about to be described has proved to be a most useful addition to the test gear used for experiments, and is particularly useful to the TV experimenter. It is not elaborate, but it will be found to cover most of the useful measurements required by the amateur. One special advantage which attracted the attention of the writer to the circuit is the reversing switch to measure either negative or positive quantities. This facility has not been found in the simpler type of valve-voltmeter circuits which have been studied before this one was finally chosen for construction, and chiefly from a constructional angle the writer wishes to continue. No originality whatever is claimed for the circuit which is used, it is simple and completely self-contained.

The Circuit


The circuit is shown in Fig. 1. Resistors R1-R7 must be \pm one per cent, and one watt types were used for reliability over a long period. Switch S1

and the valvholder should be ceramic, again for the same reasons. VR1 is the zero setting control, and is mounted on the front panel, while VR2 is used to calibrate the full-scale reading, and is mounted on the chassis, because it should be unnecessary to move this again after calibration for long periods (e.g., after change of valve).


Construction

Looking around for a chassis for this instrument, a considerably "cannibalized" RF26 unit was found in the spares box, and this proved ideal for the job in hand. Firstly, the unit was completely stripped of all components, leaving only the screen running along one side and back-end of chassis. A hole was cut in the front panel to mount the meter, using an adjustable tank cutter. This proved to be the most difficult item of work, because two layers of metal had to be cut through.

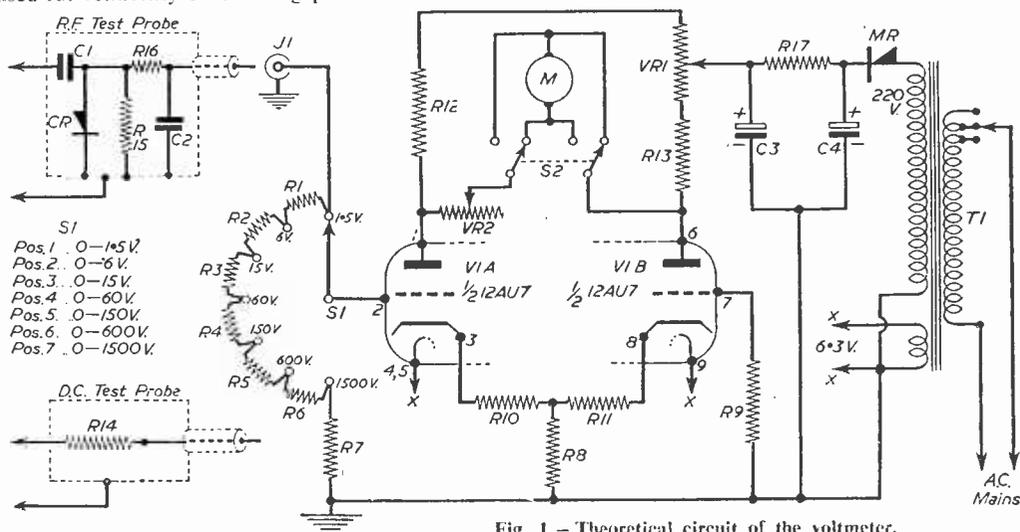The valvholder for the 12AU7 was mounted on a valve adaptor plate, and this plate mounted over the centre valvholder hole in the chassis. The resistor VR2 was mounted in the rear valvholder hole on chassis in a similar manner. An extension spindle was fitted to this control, and owing to the proximity of the rectifier (see illustrations), this was made of 1/4 in. round wood.



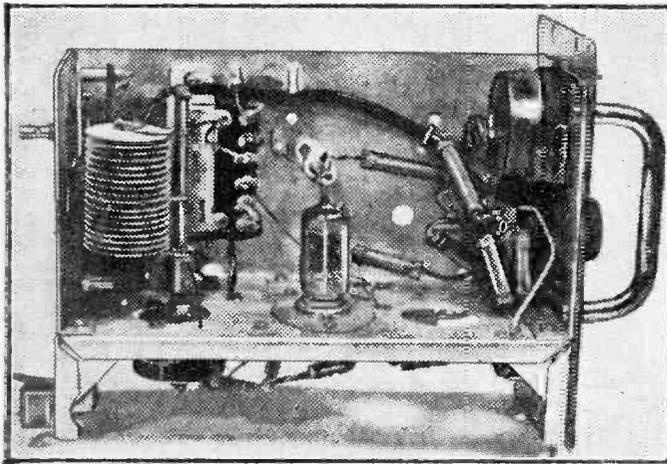Ebonite, or any similar material, could be used, as available. This spindle was made long enough to be level with top edge of screen and could be manipulated by finger and thumb without any risk of contact with the mains rectifier.




General layout of the chassis.


VR1 was mounted below chassis, on the front panel, and needs to be a small type of potentiometer, because of the limited space available. S2 was mounted on the back screen plate, behind the mains transformer, also the metal rectifier. Some of the resistors, R1-R7, were soldered to S1 before it was mounted on panel. R1 was made up

of 2-5 M Ω resistors in series, and it was found advisable to support the central connection of these two on a ceramic stand-off insulator, to prevent them sagging and coming into contact with other resistors in the chain. (This also can be seen in the illustrations). The small mains transformer was mounted on the side screen plate near S2. The Jones' plug was completely removed from rear of chassis and a flex led in through space left, direct to mains transformer, no mains switch being provided as adequate sockets are available in the shack for plugging in various test instruments, the plugs being withdrawn when instruments are no longer required. J1 is a normal coax socket mounted

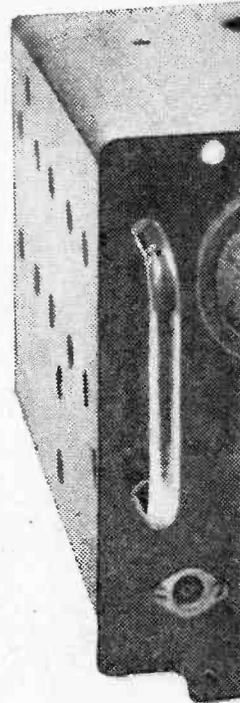on front panel. Insulated tag pillars were mounted where necessary below chassis to hold the components in position. Wiring was in no way difficult, no special precautions being found necessary.



The panel

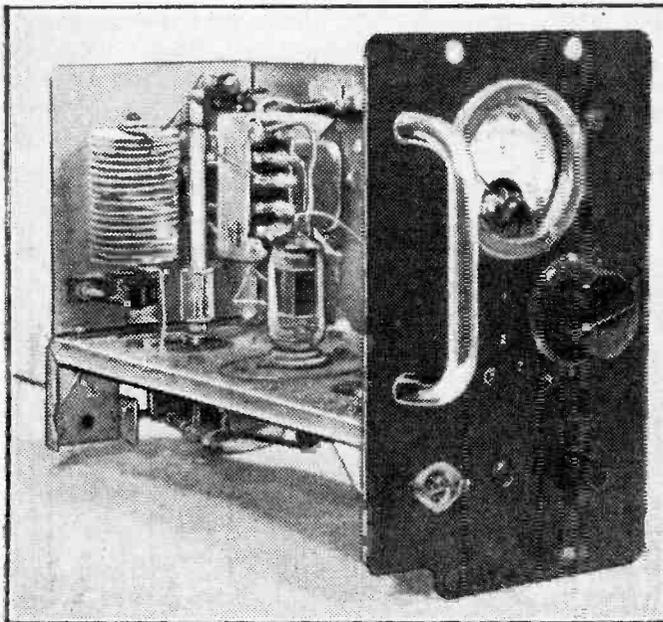

View showing layout and panel.

The Probes

The external leads were of quarter-inch coax, about 2ft. long, with coax plug at one end.

R14 was fitted inside a discarded bakelite shaving-soap holder, and the probe was made of a length of threaded rod, three or four inches long, mounted on the base of the holder. This was filed to a point and a length of tightly-fitting sleeving slipped over it.

LIST OF

C1—0.0001 μ F 2,500 v.w.	VR
C2—0.001 μ F.	VR
C3}	2—
C4} 16 μ F electrolytics.	3—
CR—Germanium diode.	M—
MR—Selenium rectifier replacement type for mains portables.	R1
T1—Mains transformer, instrument type.	R2
	R3
	R4
	R5
S1—Single-pole seven-way ceramic switch.	R6
	R7
S2—Two-pole two-way switch Yaxley type.	R8
	R9

For the R.F. probe, an aluminium case was found, identical in shape and size to the shaving soap case, and with a screw-on lid. A probe was similarly fitted to the lid of this, but insulating washers were necessary to isolate the probe from the case, which is at earth potential. The rest of the components in the probe circuit were neatly wired

and spindle of S2. A knob can be fitted to S2 after cover has been replaced.


It was found that when the probe was placed

and folded together, and the body of the case, with a lining of insulating material inside, and a hole drilled in base to take the coax, was passed over the coax lead and screwed up tight, a coax plug being fitted at the other end of lead.

Calibration

To calibrate the instrument, allow it to warm up for fifteen minutes or so, then short-circuit the tip of the D.C. probe to chassis, and with S2 in the D.C. position, adjust R1 for zero deflection on the meter. Remove the tip of probe from the chassis and place probe across a 1.5 volt cell, which should preferably be a new cell, and adjust VR2 for full scale reading on meter, with S1 in the 1.5 volt position (position 1). Reverse S2 and check for negative readings with probe. A considerable difference between positive and negative readings of the cell will indicate out of balance between the two triodes and a change of valve could be tried.

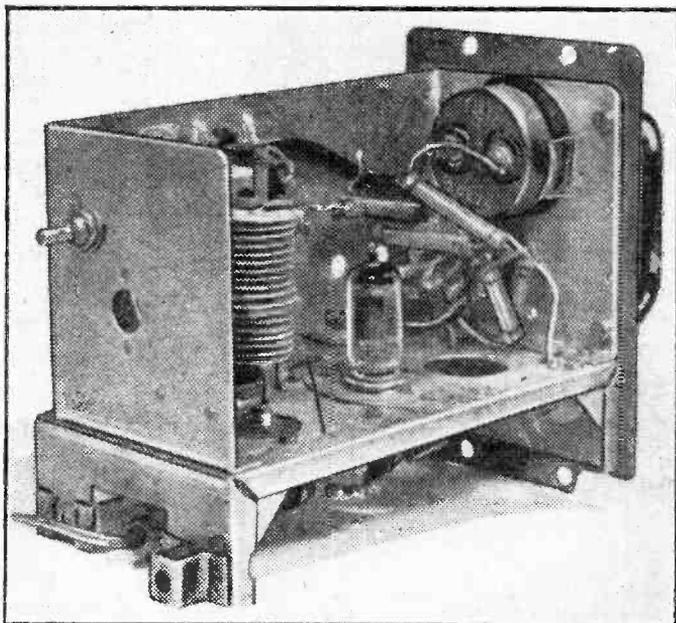The cover of the unit can now be replaced, first drilling a hole in the rear of it to clear the locknut




General view of the chassis.


in contact with certain parts of equipment, the meter pointer vibrated rather heavily against the back stop, though S2 was in correct position. It was discovered that this happened when the earth connection was omitted from voltmeter chassis. Connecting earth completely stopped this. It could be an advantage to use a three-core flex cable for mains connection, with three-pin plug, and make sure that all three-pin sockets have their earth sockets well and truly earthed; this should be a *must* in all shacks, in any case!

Using the Meter

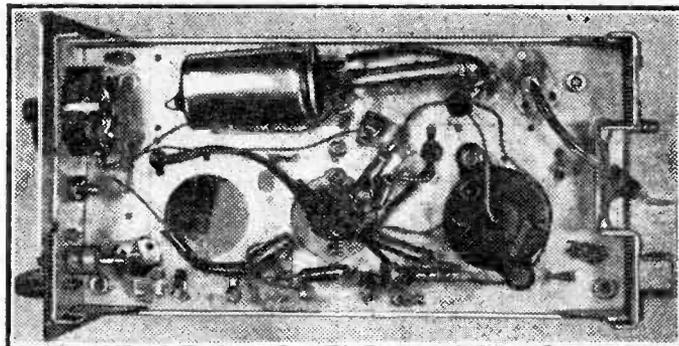In case there are any readers who are uncertain as to the reason for using a valve type of



Underside view of the "deck."

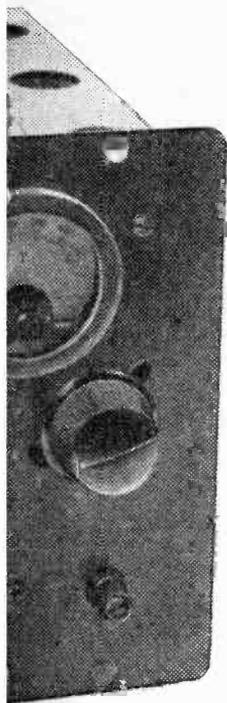


layout.

PARTS


- 10K potentiometer small type (see Text).
- 25K potentiometer.
- five adaptor plates.
- 100 μ A meter.
- 0 megohms.
- 1 megohms
- 1 megohm
- 100K.
- 100K.
- 10K.
- 3 K.
- 1 K.
- 1 megohm.

- R10) 100 ohms.
- R11) 100 ohms.
- R12) 22 K.
- R13) 1
- R14 -1 megohm.
- R15 -68 K.
- R16 -1 megohm.
- R17 -3.6 K.

that is obtained will actually be lower than it is when the test meter is removed. Thus some rather erratic faults may be difficult to locate, simply because the voltage readings obtained are inaccurate. The valve voltmeter, on the other hand, does not consume any current from the apparatus to which it is connected and by its use one can, therefore, locate some of the reasons for the more mysterious types of fault which are experienced in television receivers. It is not essential to use the RF26 cabinet shown in the illustrations, but if it is not employed the instrument should be housed in a metal case of some kind so that it is completely screened and free from extraneous influences.

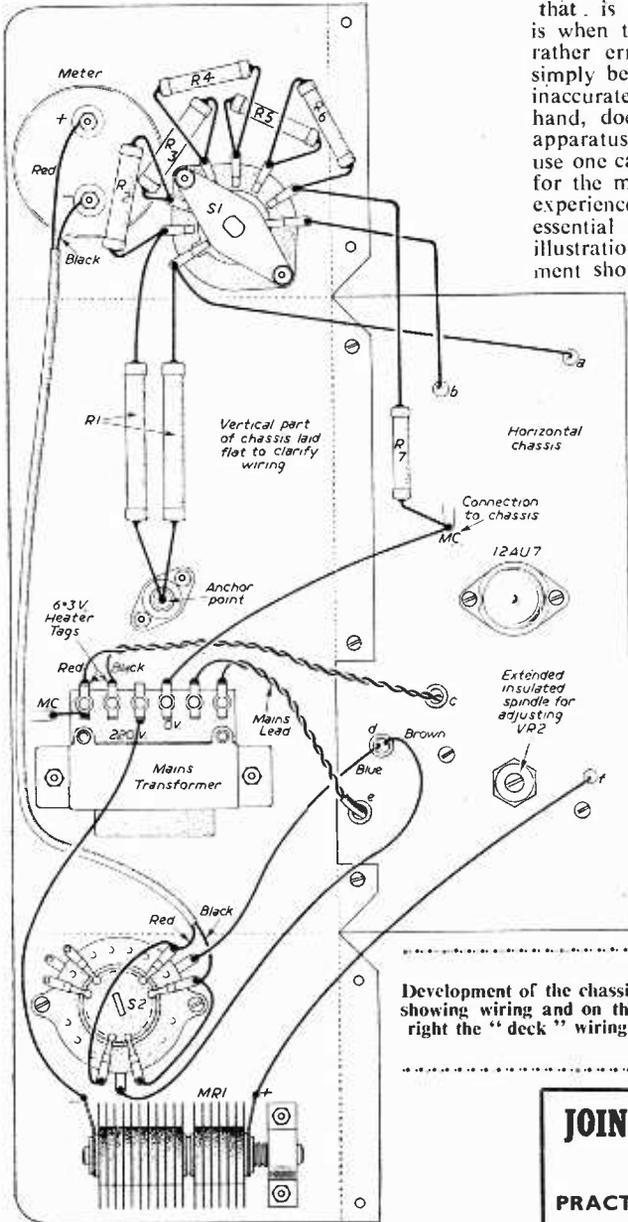

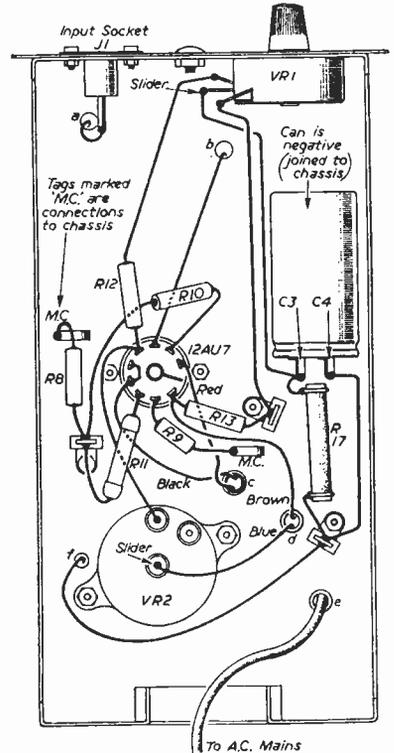Development of the chassis showing wiring and on the right the "deck" wiring.



voltmeter, it may be stated that the ordinary simple type of instrument usually employed by the amateur is definitely unsuitable for certain voltage measurements, either in a television receiver or in an ordinary radio set. To put it in simple words, a standard type of meter takes current, and therefore if it is connected across some part of a circuit where an extremely low current is flowing, the additional current taken by the meter will result in a voltage drop across the circuit as a result of which the reading

JOIN THE PRACTICAL GROUP

Edited by F. J. CAMM

- PRACTICAL HOME MONEY MAKER 1/3
- PRACTICAL WIRELESS 1/3
- PRACTICAL TELEVISION 1/3
- PRACTICAL HOUSEHOLDER 1/3
- PRACTICAL MECHANICS 1/3
- PRACTICAL MOTORIST & MOTOR CYCLIST 1/3

They are all published monthly

Scanning & Synchronisation

5.-LINE SCANNING CIRCUITS (1)

By G. K. Fairfield

LINE scanning systems used for deflecting 53 deg. scanning-angle tubes at relatively low E.H.T. potentials could afford to be quite inefficient and so wasteful of scanning power were they that they have become known as "Brute Force" methods. An E to I conversion stage was used in which the energy stored in the magnetic field at the end of the scan was dissipated in large-wattage resistors connected across the scanning coil. This was necessary to prevent resonances from being set up in the scanning coils and distorting the scanning waveform. It was shown in the first of this series that this could lead to very large current demands

L. represents the scanning coils and C the stray and self capacitance associated with these coils. The resistance of the coils is shown as r. Consider the sequence of events when the switch S is closed. Current I will flow through Lr and increase exponentially, at a rate governed by the L/r time-constant. As mentioned earlier, if the rise is only a small fraction of the maximum current $I_{max} = E/r$ then it can be considered as a linear increase of current with time. After a short interval t1 (see Fig. 31) the switch is opened and this current rise ceases, after reaching a maximum value +I amps (small compared with I max.). Energy has, however, been stored in the inductance L and causes current to flow out of L into the capacitance C during time t2. The direction of current through L has now been reversed and when it has reached a value of -I amps., then switch S is closed once more. The charge acquired by C during time t2 is now used to charge the battery E, whilst the current in L gradually reduces to zero during a time t3, again with a time-constant L/r.

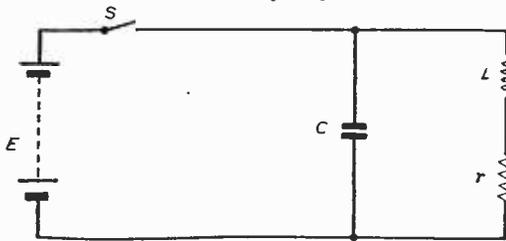


Fig. 30.—Efficiency-diode scanning. Simple equivalent circuit.

when used for wide-angle tubes at large E.H.T. potentials.

The efficiency-diode scanning circuit is inherently more efficient by conserving, instead of dissipating, the stored energy.

Theory of Efficiency-diode Action

The best way to understand this circuit is to get down to fundamentals and consider the simple equivalent circuit of Fig. 30. Here the inductance

Now if no losses are present in the circuit (i.e. $r = 0!$) then the charge lost by the battery during t1 is put back into it during t3 and a linear rise of current in L obtained in the process. In a practical circuit the switch is replaced by two valves, one of which (a pentode V1) conducts during the period t1, and the other (a diode V2) conducting during period t3 (Fig. 32). It will be noticed that a capacitor C1 has been added to the circuit. This will be in series with V2 during its conduction period and will receive the charge shown going to the battery in Fig. 30. The potential developed across C1 (the boost volts Eb) will be added to the H.T. and provide V1 with a bigger supply potential.

This simplified circuit is given practical form in Fig. 35 which is a typical efficiency-diode circuit, with a controlling sawtooth potential applied to V1, the amplitude of which is such that this valve conducts only during period t1. The transformer T performs the dual function of matching both the diode and pentode impedances to that of the scanning coils during their respective conduction periods.

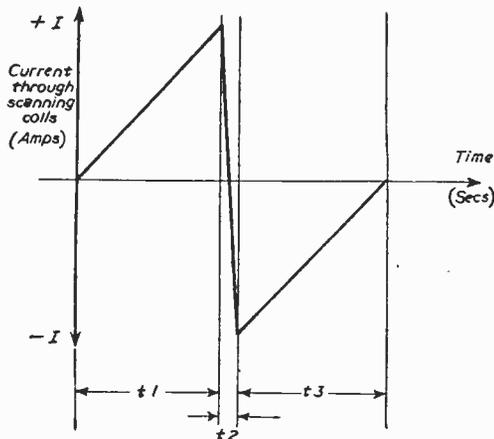


Fig. 31.—Variation of current through L with time.

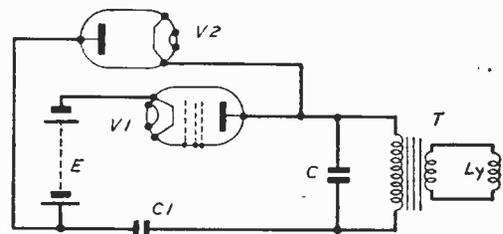


Fig. 32.—Switch S of Fig. 30 replaced by two valves.

Transformer Design and Construction

This is the most important single item in the circuit of Fig. 35 and has several rather special features which render its construction different from, say, a frame output transformer. These can be summarised as problems of bandwidth, potential gradient, and coupling factor.

A transformer handling a sawtooth of repetition frequency 10 kC/s must be capable of passing, without relative attenuation, frequencies up to at least 100 kC/s; consequently the transformer core losses assume some importance. As the circuit can be loosely considered as a push-pull arrangement there is less risk of core saturation by a constant D.C. through the windings and the use of nickel-iron alloys, e.g., radiometal,

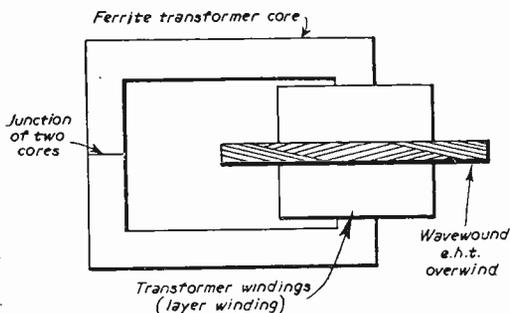


Fig. 34.—Auto-transformer constructional method to obtain a good potential gradient.

rhometal, mumetal, etc., is permissible. However, due to the low losses at high frequencies and the high permeability of ferrite materials, these have now replaced metal stampings for line transformer service. Now that these materials are becoming available to the amateur constructor it is proposed to limit the design details given in this series to their use.

It was mentioned in the first article of this series how a large pulse voltage is developed across the deflection coils during the retrace period. This voltage is stepped-up by transformer action to some 4 to 7 kV at the pentode anode connection. Naturally this leads to special valve construction and, of course, good transformer insulation. By winding an additional coil over the transformer shown in Fig. 35 this pulse voltage can be further increased until 10 to 20 kV is available, and which, after rectification can be used as E.H.T. for the cathode-ray tube. The secret of success with transformer construction of this nature is to ensure a constant potential gradient across the winding and a low self-capacity for the E.H.T. winding. This had led to the type of construction shown in Fig. 34. Here a pair of U-shaped ferrite cores are used and the transformer windings wound on one limb, commencing with the deflection coil winding. A narrow wavewound coil is placed over this and serves to increase the E.H.T. pulse to the required amplitude. By winding the coil in this manner the large number of turns required can be obtained without unduly increasing the self-capacitance. Going outwards from the innermost windings the peak potential will thus be seen to

increase gradually until a maximum is reached at the outer connection of the E.H.T. winding. A good potential gradient is consequently obtained at minimum breakdown risk.

A practical application of the theory and trans- efficiency of the transformer if maximum scanning current is to be transferred to the deflection coils. A high coupling factor is necessary between the winding matching diode and pentode to the coils. Fortunately this is easily assured by the auto-transformer connections shown in Fig. 35, and also by high permeability of the core material, and using Mullard ferrite known under the trade

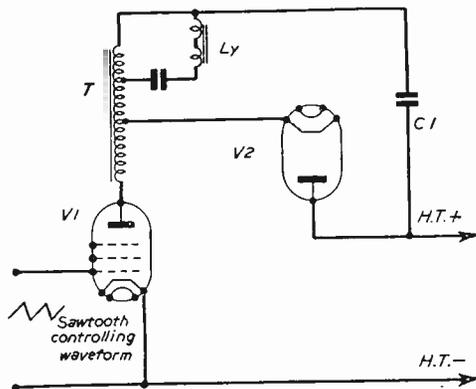


Fig. 35.—Practical efficiency-diode circuit.

name of "ferroxcube," coupling factors of over 0.99 are obtainable.

A practical application of the theory and transformer construction discussed in this article will be given next month in the description of a complete line scanning circuit, when methods of linearization and scan width variation will also be described.

(To be continued)

PRACTICAL WIRELESS JAN. ISSUE NOW ON SALE PRICE 1/3

The constructor is well catered for in the January issue of our companion paper, *PRACTICAL WIRELESS*, which is now on sale. In addition to the main feature, which is a C.R.L. Bridge, there are constructional articles on a Beginner's 200 to 1,600 metre Superhet, a Transistor Square Wave Generator, a Microphone Amplifier using a Transistor, and the final stage of the Beginner's Constructional Course.

The interest in the Russian Satellites has resulted in enquiries on how to find and track them, and there is an article in this issue on this subject. Entitled *Observe the Satellites*, this first article describes the principles of reception and judgment of speed, whilst another article gives details of the Mullard Observatory at Cambridge which has been featured in the news in connection with its tracking of the satellites.

Other articles deal with Choke and Transformer Winding, Transistors in Practice, Transmitting Topics, and the usual Features.

BARGAINS TO CLEAR

A.C. Superhet 5-Valve Chassis. Medium and two short, unused, but less valves and mains transformer. Uses standard Octal range. 27/6. (Again, coil pack worth much more.) Non-callers add 6/6.
A.C. Superhet 7 v. 5-Waveband Chassis. H.F. stage. Unused. Less valves and power pack. Slightly soiled. Coil pack worth twice as much. Circuit diagram supplied. £2/15/-, carriage and insurance 7/6.
A.C. 4-Valve Superhet, complete with valves, but less scale and pointer, unused. 39/6 plus 3/6 post & insurance.

Note that the above three chassis, although unused, will need checking. On account of low price no guarantee is given. Nor, we regret, can technical assistance be given.

.1 mfd. 350 v. Small Tubular Metal-cased Condensers. Made by Dubilier. 2/6 doz and ins. 2/6.
Germanium Diodes, B.T.H. with wire ends. 10d, each or 9/- dozen.
Midget I.F. Coils. Dust cored, size 13 x 1in., 465 Kcs. 4/6 pair.
Standard size I.F. Coil. Dust cored, 465 mc/s. 4/6 pair.
Coil Pack for Superhet. 465 Kc s I.F. Medium and 2 short waves. 9/6.
Bakelite 5 Amp. Electric Wall Switch. "Hicraft," 9d, each, or 8/- per dozen.
Series, parallel and off-circuit wall switch made by Crabtree. Price 1/3 each, or 13/6 per doz.

NOTE: Additional Technical Data is not available on these bargain items.

Amplifier, ex-Government unit 11/4 contains one double triode and one triode. 6/6, post and ins. 2/6.
Connecting Wire, P.V.C. covered 24 s.w.g. copper. 2/6 per 100 ft., or 5 coils, different colours, for 10/-.
Scanning Coils by very good maker. New and unused. 4/6 complete.
Choke, 20 mA. first class. Made for Services. New 6/6, post 1/6.
10 v. Superhet, 11 metre. Ex-Govt. but unused. Complete with valves. Easily converted for Band III. 39/6, carriage and packing 7/6.
Mains Transformer. 250-0-250, 60-80 mA. 6.3 v. standard mains input. Half-shrouded. 12/6, post and insurance 7/6.
R.F. 25 Tuning Unit. New, unused and complete with valves. 9/6, post 2/6.
Cathode-Ray Tube, VCR517. 8/6 each, carriage 4/6.
Mains Leads. Metal screened to stop interference. 9d, yard.
Thermocouple, mounted on valve base. Useful for experiments and schools. 6/6 each.
Midget Push-pull Input Transformer and push-pull output transformer to match. 8/- the pair.

NOTE: Orders for small components over £2 are post free, otherwise please add sufficient.


BAND III CONVERTER

Suitable London, Midlands, North, Scotland, etc. All the parts including 2 valves, coils, fine tuner, contrast control, condensers, and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately 1/6.

BUILD THIS IN AN EVENING

Yours for £1.10.0 Down

17" T.V.

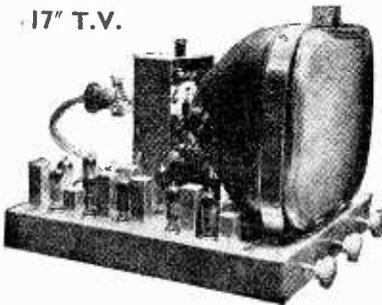


Undoubtedly the most up-to-date televisor for the home constructor. You can build it in an evening and the set when finished will be equal to a factory-made equivalent. What other constructor T.V. has all these features?

- ★ No technical knowledge required.
- ★ All miniature valves.
- ★ Metal rectifier.
- ★ Turret Tuner.
- ★ 12-channel circuitry.
- ★ Multi-vibrator time bases.
- ★ Ferrucube, E.H.T. and scan coils.
- ★ 34.38 Mc.s I.F.
- ★ Suitable for any modern 12, 14 or 17" tube.

The building cost (less tube) is only £29 10 0, plus 10/- carriage and insurance, or £15 deposit & 12 monthly payments of 27/- . All parts guaranteed 12 months. Full information and data, price 3/6.

MAINS ISOLATION TRANSFORMER

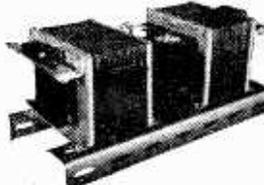

Makes servicing safe, also makes the adjustment for differences in mains voltages very simple. Input tapped 200-250 v., output 250 v., output tapped 200-250 v. Contains in a housing rated at 500 watts, intermittent rating 2,000 watts. Cable entry by terminal blocks. Two separate screens for suppressing mains interference. Size approximately 14 in. x 6 in. x 6 in., weight approximately 40 lbs. Price £5/12/6. Carriage and insurance 7/6 (up to 250 miles).

14" T.V. CABINET


14in. T.V. cabinet of the latest styling made for one of our most famous firms—beautifully veneered and polished—limited quantity—19/6 each. Carriage and packing 3/6 extra.



THIS MONTH'S SNIP INDICATOR No. 95




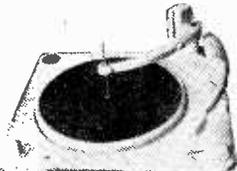Contains many hundreds of very valuable spares including no less than 12 potentiometers. This indicator unit will take the VCR57 or the VCR57 and with relatively simple modifications can be turned into an Oscilloscope. Limited quantity offered at the extremely low price of 10/- each, carriage and packing 4/6 up to 250 miles, beyond this distance at cost.



The latest most up-to-date Record Player made by the famous B.S.R. company. Using Hi-Fi Crystal Pick Up and fitted with every modern device. Definitely a record changer which will give years of trouble-free music. Not surplus but the current model. Price £9.10/- or £1/10/- deposit and 8 monthly payments of £1, carriage and insurance 5/-.

FLUORESCENT LIGHTS

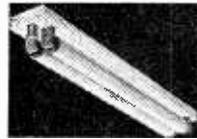

These are complete fluorescent lighting fittings. Built-in ballast and starters—stove enamelled white and ready to work. Ideal for the kitchen, over the work-bench and in similar locations.

Single 40. 4 ft. 3 in. long, uses a 40 watt tube.

Twin 20. Uses 2 20-watt standard tubes.

Price for either type 39/6, with tubes.

Carriage and ins. up to 150 miles 5/6, up to 250 miles 7/6.

SPEAKER BARGAIN



12in. Hi-fidelity loudspeaker. High Flux. Permanent magnet type with standard 3 Ohm speech coil. Will handle up to 12 watts. Brand new by famous maker. Price 32/6, plus 3/6 post and insurance.

CAR STARTER CHARGER KIT

All parts to build 6- and 12-volt charger which can be connected to a "flat" battery and will enable the car to be started instantly. Kit comprising the following:

Mains transformer.....	22/6
5-amp. rectifier.....	17/6
Regulator Stud Switch.....	3/6
Resistance Wire.....	2/6
Resistance Former.....	2/6
Mains on/off Switch.....	2/6
0.5 amp. Moving Coil Meter.....	12/6
Construction Data.....	1/6

or if bought all together price is 52.6 plus 3/6 post and packing.

Waterproof P.V.C. covered Heating Element, 16 ohms per foot. 1/- per yard.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to E.P.E., Ltd., Dept. 5, 66, Grove Road, Eastbourne

Personal shoppers to one of these addresses, please.

266, London Road,
Croydon,
Phone: CRO 6558.
Half day, Wednesday.


42-46, Windmill Hill,
Ruislip, Middx.,
Phone: RUISLIP 5780
Half day, Wednesday.

152-3, Fleet Street,
E.C.4.
Phone: FLEET 2633
Half day, Saturday.

29, Strand Green Road,
Finsbury Park, N.4.
Phone: ARCHWAY 1049
Half day, Thursday.


SIGNAL GENERATOR

Coverage 120 Kc's-230 Kc's.
300 Kc's-900 Kc's. 900 Kc's-
2.75 Mc/s. 2.75 Mc/s-8.5 Mc/s.
8 Mc/s-28 Mc/s. 16 Mc/s-56
Mc/s. 24 Mc/s-84 Mc/s. Metal
case 10in. x 6in. x 4in.
Size of scale, 6in. x 3in. 2
valves and rectifier. A.C.
mains 230-250 v. Internal
modulation of 400 c.p.s. to a
depth of 30 per cent., modu-
lated or unmodulated R.F.
output continuously variable
100 milli-volts. C.W. and
mod. switch, variable A.F. output and moving coil output meter.
Grey hammer finished case and white panel. Accuracy plus or
minus 2%. £4.19.6 or 34/- deposit and 3 monthly payments 25/-
P. & P. 4/6 extra.

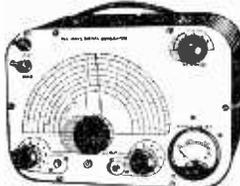

SIGNAL & PATTERN GENERATOR

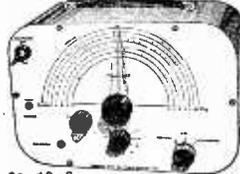Coverage 7.6 Mc/s-210 Mc/s
In five bands, all on funda-
mentals, slow-motion tun-
ing, audio output, 8 vertical
and horizontal bars, logging
scale. In grey hammer
finished case with carrying
handle. Accuracy ± 1%.
A.C. mains 200-250 v.




£6. 19. 6.
Or £2 deposit and 4 mthly. pymts
of 27/6. P. & P. 5/6.

COMMERCIAL TELEVISION CONVERTER SUITABLE

ANY TV. (Except Philips)
WITHIN 35 MILES OF I.T.A.
TRANSMITTER. ALL CHANNELS
NO ALTERATIONS TO SET.

Complete with built-in power supply.
200-250 v. A.C. mains. Crackle finish
case 5in. long, 3in. wide, 4in. high.
Incorporating gain control and band
switch. Illus. with cover removed.
Complete with Wolsey 3 element
I.T.A. outside or loft aerial, 36 ft.
I.T.A. lead and 2 plugs. (Wolsey 4
element 5 - extra). 25/- deposit, plus P. & P. 5/-, and 4
monthly payments of £1.5.6. Cash £5.17.0 plus P. & P. 5/-.
Converter only £3.19.6. plus P. & P. 2/6.

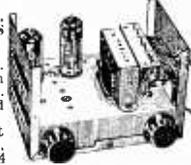

AC/DC MULTI-METER KIT

Comprising 2in. moving coil meter,
scale calibrated in AC/DC volts,
ohms and milli-amps. Voltage range
AC/DC 0-10, 0-100 and 0-500. Milli-amps
0-10, 0-100. Ohms 0-1,000 and 0-10,000.
Front panel, range switch, wire-
wound pot (for ohms zero setting),
two toggle switches, resistors and
metal rectifier. In grey hammer-
finish case. 19/6 P. & P. 1/6.

Point to point wiring diagram 1/- free with kit.

4 VALVE ALL-DRY SUPERHET PORTABLE KIT

Incorporating Ferrite rod aerial
Medium and long waves. In grey
leatherette. Size 9in. x 7in. x 6in.
Valve line-up: IT4. 1R5. 1S5.
3V4. Complete kit of parts (less
batteries).

£5. 19. 6 Plus Post & Packing 3/6



COMPLETELY BUILT PORTABLE AMPLIFIER
approx. size 6in. x 2in. incorporating 2 valves, contact-cooled
metal rectifier, bass and treble lift controls 39/6 P. & P. 3/6.
Plus
and double wound mains transformer 230-250 v. P. & P. 3/6.
5in. P.M. SPEAKER & O.P. TRANSFORMER, if purchased
with the above, 18/6. Plus P. & P. 1/6.

COLLARO 4-SPEED AUTOMATIC CHANGER

Model 456 (suitable for use with above amplifier). A.C. mains.
200-250 v., turnover crystal head. £8. 19. 6 Plus
Brand new, fully guaranteed. P. & P. 5/-.
Or 25/- deposit and 7 monthly payments of £1.5.0.

RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3
GOODS NOT DESPATCHED OUTSIDE U.K.

BOOKS for the T.V. enthusiast . . .

T.V. CONVERSION FOR I.T.A. by C. E. Lotcho

A practical guide giving details of converter units and full information for fitting them to a wide range of receivers, produced by nearly 30 television manufacturers. Over 100 illustrations and circuit diagrams. 25s. (26s. 3d. by post)

PRACTICAL TELEVISION CIRCUITS by F. J. Camm

Full constructional details of a wide variety of television receivers plus chapters on the construction of test and auxiliary apparatus including a spot wobbler and telescope. The circuits range from a receiver costing as little as £20. 15s. (16s. by post)

INDUSTRIAL TELEVISION by H. A. McGhee, Grad.I.E.E.

Discusses the design and application of television equipment and covers television pick-up devices; design of equipment; underwater television; television microscopy; television telescopes; stereoscopic television. 15s. net (16s. by post)

TELEVISION PRINCIPLES & PRACTICE by F. J. Camm

The underlying principles of television transmission and reception, covering every aspect of this new science, including servicing and installation. An exhaustive dictionary of television terms is included. 2nd Edition. 25s. (26s. 3d. by post)

FROM ALL BOOKSELLERS

... or in case of difficulty at post rates from GEORGE NEWNES LTD., Tower House, Southampton Street, London, W.C.2.

NEWNES

POST VIEW & CO. 17, High Street, CARDIFF

Telephone: C.ARDIFF 26527


Television Tubes

- Mullard 14" - £6.10.0
- Mullard 17" - £7.10.0
- Cossor 14" - £6.10.0
- Cossor 17" - £7.10.0
- Mazda 14" - £6.10.0
- Mazda 15" - £7. 0.0
- Mazda 17" - £7.10.0

3 months' guarantee

ALL TUBES PLUS 12/6 carriage and insurance

TELENEWS

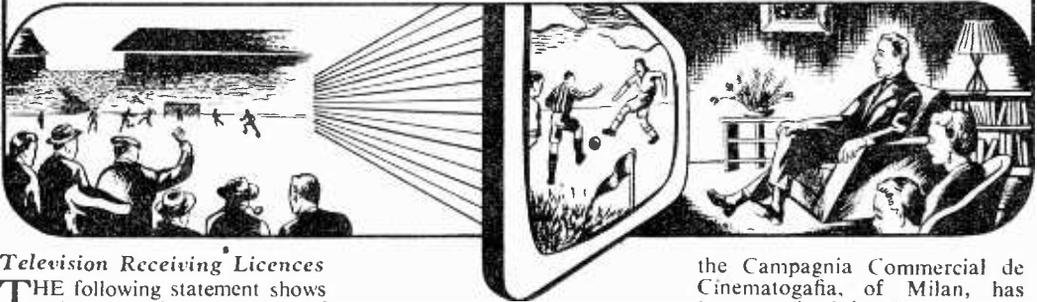

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of October, 1957, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,529,083
Home Counties	908,227
Midland	1,229,644
North Eastern	1,195,137
North Western	1,063,766
South Western	562,096
Wales and Border Counties	422,734
Total England and Wales	6,910,687
Scotland	540,786
Northern Ireland	72,598
Grand Total	7,524,071

Marconi Activities in South America

DESPITE the keenly contested nature of the Latin-American electronics market, Marconi's are having considerable success in this field. Recent orders from Venezuela include one for a complete Band III television station and one for a medium-frequency sound broadcasting transmitter.

The television station, which has been purchased by Radio Valencia, comprises a 2kW vision transmitter Type BD. 357A, a 1kW sound transmitter Type BD.305, programme input equipment, a quadrant aerial array, a vidicon telecine unit, vision and sound links, a 3-camera outside broadcasting unit and studio lighting equipment.

B.I.R.E. Award to Cossor Director

THE British Institution of Radio Engineers has announced the award of the 1956 Brabazon premium for the most outstanding contribution on radio and electronic devices for

aircraft safety to Mr. K. E. Harris, Technical Director of Cossor Radar & Electronics Limited, for his paper, "Some problems of secondary surveillance radar systems."

This is the second such award in three years as the 1954 Brabazon premium was given for a paper on "A high definition general-purpose radar" by four Cossor engineers. Messrs. Jenkins, Evans, Chambers and Wallace.


£10,000 Worth of Ediswan Tubes for Italy

AN order value £10,000 for Ediswan 21in. rectangular television cathode ray tubes for

the Campagna Commercial de Cinematografia, of Milan, has been received by Siemens Edison Swan Ltd. These tubes are being sent to Italy for incorporation in television receiver chassis made by Messrs. E. K. Cole, Ltd., which will be housed in cabinets of Italian manufacture.

Closed-circuit Television Aids Radiation Treatment

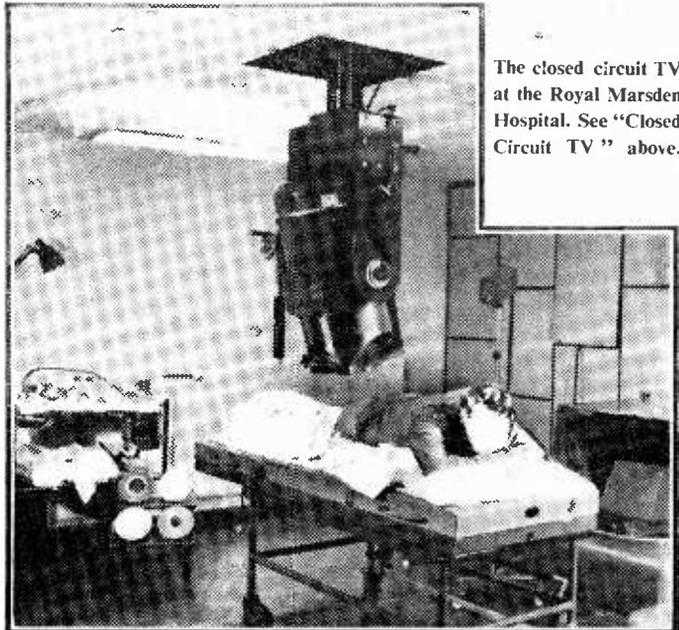MARCONI closed-circuit television is being used in a London hospital to assist in the deep therapy radiation treatment of patients. The equipment is used in conjunction with a Telecaesium Ray Treatment unit at the Royal Marsden Hospital, and permits the treatment to be car-



The closed circuit TV at the Royal Marsden Hospital. See "Closed Circuit TV" above.

ried out by remote observation. In this way doctors and radiographers are safeguarded against excess radiation, which can produce harmful effects.


Observation of the patient is necessary during this type of treatment since a beam of gamma rays is accurately directed into the affected region. It is therefore important that this region be kept in a fixed position relative to the beam, since a centimetre's movement in any

The transmitter is to send out experimental programmes up to January 1st. "Naturally, we cannot ask for money for these programmes, but when regular programmes commence television licences will have to be paid for in the same way as radio licences." Mr. Kövesi, deputy managing director of the Hungarian Post Office, said.

Plans have been made for a TV hook-up and exchange of programmes with Bratislava in

station will have an effective radiated power of about 100 kilowatts and a 750ft. mast will be used.

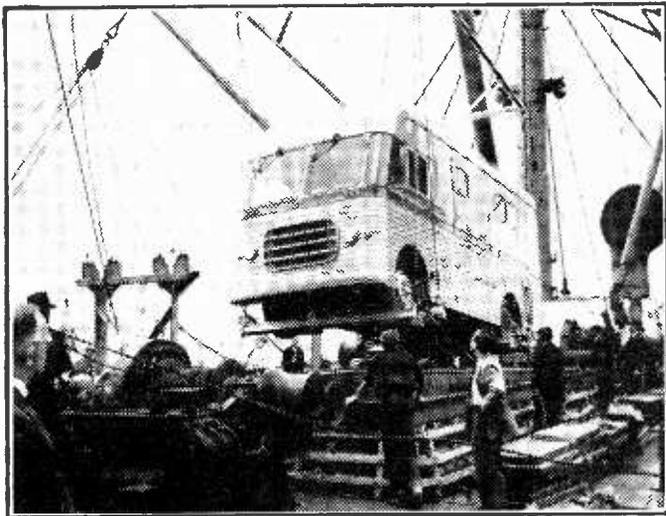This will be the eighth transmitting station on the Authority's network. It will bring another 2,500,000 people within reach of independent television, making a total, including those that will by then be served from the St. Hilary and Chillerton Down stations, of over 43 millions—a coverage of about 85 per cent. of the total population of the United Kingdom.



A Marconi TV van being shipped to Venezuela. See page 281.

direction would render the treatment useless.

By keeping the patient under constant supervision during the irradiation treatment any movement is immediately observed. The treatment is then discontinued while the patient is repositioned. In this way the specialist knows that the equipment is being used at maximum efficiency and in the most economical manner.

New TV Transmitter in Hungary

BUDAPEST'S television station plans to go over to its new 30 kilowatt transmitter by the middle of this month. The television station stands on Liberty Hill overlooking the capital.

The transmitter, bought from East Germany, was due to go into service in April of this year, but plans were delayed.

the first half of next year. Four "bouncer" stations will be built to relay the transmissions.

I.T.V. in the North East

THE Independent Television Authority has invited applications for the contract to provide television programmes for its transmissions in the North East of England.

The Authority's station will be built at Burnhope, about five miles south-east of Consett. It is hoped to open the service late next year.

The coverage of the station is predicted as a rough crescent running from Alnwick in the north, through Middleton in Teesdale in the east, and nearly to Whitby in the south. The highly concentrated populations of Newcastle, Sunderland, Middlesbrough and South Shields will all lie well within the service area. The Burnhope

New Scottish TV Weather Service

A NEW TV weather service for Scottish viewers will be in operation this winter. By agreement with Scottish Television Ltd., the Automobile Association will provide special charts showing prevailing road conditions whenever snow, ice, fog or floods affect roads in Scotland.

Up-to-the-minute reports of road conditions, received by radio and telephone from A.A. patrols covering important roads throughout Scotland, will be collated in the operations room of the A.A. headquarters in Glasgow, and specially drawn charts prepared for showing in the S.T.V. news at 1.30 p.m. and 6.40 p.m.

The object of the charts is to give a general indication of the state of the roads to intending travellers. More detailed information can be obtained from A.A. offices.

America Receives BBC TV

BBBC television direct from London has been received for the first time on several successive days in New York—a distance of over 3,000 miles.

The pictures, seen on a standard British receiver, included the David Nixon show "It's Magic," and were picked up at the Baldwin, Long Island, receiving station of Press Wireless, Inc. First reception was on November 1st, and later reports said that pictures had been received on six occasions in seven days.

This is the first time that such pictures have been seen since 1937, when American TV engineers briefly received a picture.

TELEVISION TUBES



12 MONTHS' GUARANTEE
17" £7.10.0 14" £5.10.0

RECTANGULAR T.V. TUBES

6 months full replacement, 6 months progressive. Made possible by the high quality of our tubes. Terms or Cash. 15/6 Ins. Carr. **CONVERT YOUR 9in., 10in., 12in. to 14in., 15in., 16in.** Our pamphlet is FREE and on many sets costs only the tube to give you these giant pictures.

SPECIAL OFFER, 14in., 15in., 16in. T.V. Tubes £5. Perfect, see them working. 3 means guarantee. Ins. carr. 15/6.
12in. T.V. TUBES, £8. 3 months guarantee. Ins. Carr. 15/6.
T.V. TUBES, 30/-. With cathode to heater shorts. 15/- with burns. State type and size required.

ELECTRIC CONVECTOR HEATER, 99.8.

Cleaner, cheaper, safer than paraffin. A.C./D.C. Switched for 1 or 2 kW. Illuminated grille. Ins. carr. 19/3.



ELECTRIC FIRES, 17/3. Hammered finish. A.C./D.C. 200-250 volt 750 watt. Post 3/6.

MIDGET EVERREADY BATTERYMAX 1/9

"B" type battery. 22½ v. No. B155. Ideal for Midget or Personal radio. Hearing Aid. or Photography Flash. Size 1in. x 2in. 1 for 1/9. Post 3d. 6 for 7/-. Post 6d. 12 for 12/-. Post 9d.




CANDELABRUM, 19/9. 3 light lounge fitting. Complete with lamp holders, flex and shades.

CAR AERIALS, 6/9. Whip antennae, 50in. long collapsible to 11in., one-hole fixing. Post 1/-.

HEADPHONES 1/9

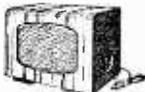HEADPHONES, 1/9. Single earphone and head-band. C.L.R. Ideal for crystal sets, extension on radio etc. P. & P. 1/3.
INSULATING TAPE, 1/6 (75ft. x 1in. wide) finest quality adhesive, in sealed container. Post 9d.



EXTENSION SPEAKERS, 29/9. Complete, fitted with 8in. P.M. Speaker, "W.B." or "Goodmans," of the highest quality. Standard matching to any receiver (2-5 ohms.) Flex and switch included. Unrepeatable at this price. Money refunded if not completely satisfied. Ins. carr. 3/6.

8in. P.M. SPEAKERS, 8/9. Let the lady of the house listen to that T.V. or radio programme. Complete with O.P. trans. 10/- P. & P. 2/8.

P.M. SPEAKERS, 12/9. Elac or Goodmans. High quality. 2-5 ohms. Complete with O.P. trans., 14/- P. & P. 2/9.

MAINS TRANSFORMERS

350-2-350 v. 80 mA. 4 v.-4 v. heaters. 200-250 v. Prim. ... 3/9
 350-0-350 v. 80 mA. 12 v.-4 v. heaters. 200-250 v. Prim. ... 2/9
 250-0-250 v. 80 mA. 6 v., 4 v., 4 v. 200-250 v. Prim. ... 5/9

Drop through type. Half shrouded. All above 2 3 post. ... 5/9
 425-0-425 v. at 250 mA. 5 v. 6 a., 6.3 v. 12 a., 6.3 v. 6 a., 200-250 v. 17/6. Screened primary. P. & P. 2/6.

O.P. TRANSFORMERS, 1/3. Standard size (2-5 ohms). Post 1/-.
 2 for 2/1. P. & P. 2/0 on 2/5/6.

SELF-FEED SOLDERING TOL, 19/6. 6-12 volt. 110-125 volt. Made for the American market. Car Battery or mains, export quality. Complete in light carrying case. Reel of solder and spare parts. P. & P. 2/9. A few of the above in 6-12 volt. 200-210 volt. 35/6.

T.V. AERIALS, 25/6. For all I.T.A. and F.M. channels. For outdoor or loft. 3 elements. Famous manufacturer, At half the normal price. Post 2/6.

T.V. MASKS, 7/9. 17in. Grey plastic. Brand new. Post 2/-.

T.V. MASKS, 14/9. 17in. Halo lighting. New. 2/-.

T.V. MASKS, 10/9. 17in. White plastic. New. 2/- Postage.

5 VALVE MIDGET RADIO, 79/6. Superhet Octal valves: 12X6, 12X7, 12X7, 35L6 & 35Z4. 5in. speaker included. 2 wave bands (L & M). 3 control knobs. 100-240 volts. Universal supply. Wooden cabinet, size 17in. x 8in. x 6in. Ins. carr. 3/6.

TORCH LANTERNS, 6d. each. X.W.D. Includes 2 bulbs, uses 800 battery. P. & P. 1/-. Crate of 48 with 22 bulbs extra 22/- (118 bulbs in all.) Ins. carr. 10/-.

Liverpool St.—Manor Park Stn.—10 minutes.

Send for our FREE 1958 catalogue.


Open all day Saturday.

DUKE & CO. (Dept. 2), 621/3 Romford Road, Manor Park, E.12.

Tel.: ILFord 6001-3

17" T.V. CHASSIS £19.19.6


Latest improved circuits. Higher E.H.T. (brilliant picture). Improved sensitivity (for greater range). Chassis easily adapted to any cabinet. 17in. rectangular tube on adapted chassis. All channels. Turret Tuner 50/- extra. Less valves. With five valves £21.19.6. With all valves £25.19.6. Valve line-up: (5 valves): 2 6D2, SN7C, 6P25, EL33, Others: 7 6F5, EL33, 6L13. 12 months' guarantee on tube, 3 months' guarantee on valves and chassis. Ins. carr. 25/- (incl. tube). State B.B.C. channel and I.T.A. if turret required.

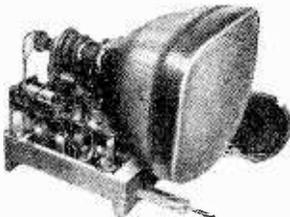

14" T.V. CHASSIS. TUBE. SPEAKER. £13.19.6.

As above, with 14in. round tube. Less valves. Guaranteed 3 months. With 5 valves £15.19.6. With all valves £19.19.5. Turret tuner 50/- extra, ins. carr. 25/- (incl. tube).

POPULAR RADIO OR R/GRAM CHASSIS 39/6

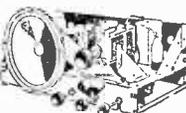

3 w/band and gram Superhet, 5-valve. International. Octal. Ideal table gram, but still giving high quality output. 4-knob control 8in. P.M. Speaker, 7/9 extra. Set of knobs, 2/-, Chassis size: 12in. x 6in. x 9in. Less valves. Ins. carr. 4/6.

12in. T.V. CHASSIS & SPEAKER, 59/6. These chassis can be adapted to take 14in., 15in. or 17in. tubes. Complete chassis by famous manufacturer. R.F. E.H.T. unit included, also 8in. P.M. Speaker. Chassis is in 3 separate units (power, s/vision and timebase inter-connected). These chassis can easily be fitted into existing console cabinets. Less valves and tube. Channels 1-2, 3-5, I.F.S. 16-19.5 Mc/s. Easily converted to I.T.A. channel. Ins. carr. 10/6.

TERMS AVAILABLE

DENCO RADIOGRAM CHASSIS 97/6

3 and 4 waveband turret tuned. Superhet. A.C. D.C. chassis, with 6in. or 8in. speaker. Size 8in. x 10in. x 12in. Valve line-up: 6C135, E739, EBC33, CL33 and CY31. (C10 dropper). Ins. carr. 7/6.

SUPER CHASSIS 99/6

5-valve superhet chassis including an 8in. speaker. 4 control knobs (Tone, Volume, Tuning, W.C. switch); 4 waveband, with position for gram. P.U. and for extension speaker. A.C./D.C. P. & P. 5/6.



CONSTRUCTOR T.V. CHASSIS UNITS

SOUND & VISION STRIP, 19/6. S/het. 10 valve holders (EF91, etc.) Less valves. P. & P. 2/6.

TIME BASE, 7/9. Containing scanning coil, focus unit, line trans., etc. Less valves. Ins. carr. 2/6.

POWER PACK & AMPLIFIER, 19/6. O.P. stage 6V6 with O.P. trans. Smoothed H.T. 350 v. 250 mA., 6.3 v. 5 a., 22 v. 3 a., 6.3 v. 4 a., 4 v. centre tapped. Less valves. Free drawing. Ins. carr. 5/6.

CHASSIS 1- each, 6 or 8 valve. Latest type midget valve design for A.M. and F.M. New cadmium plated on s.w.g. steel. 12in. x 7in. x 2in. P. & P. 1/6. Post on 4/3-. 12 for 10/-, Carr. 3/-.

Boxed VALVES 3 month guarantee

1S5	4/9	77	3/9	ECC81	8/9	PP225	3/9
6AH6	7/9	21OLF	3/9	EF41	8/9	PEN45	12/6
6H6M	1/9	210VPF	5/9	EL32	6/9	RL37	1/9
6N7GT	4/9	7193	3/9	KTW61	5/9	VR21	1/9
6B8G	3/9	AR6(2V)	1/9	L410	1/9	VR91	2/9
6S6T	3/9	CV183	3/9	LP23	1/9	VW49	6/9
8D2	3/9	EB31	1/9	DF66(CV210)	1/9	EF37	4/9
12BE6	6/9	ECH42	8/9	PEN220	3/9	EF37A	4/9



The Bennett College can make you an expert TV technician

- IN YOUR OWN HOME !

Here's your big chance! The Bennett College, famous the world over for its first-class postal tuition, now offers you a course in Television Servicing. Right away you can start adding to your knowledge of television repairs and maintenance, increasing your technical ability—and making a sound investment for your future.

Studying with The Bennett College is a pleasure. You work in your own home, as quickly—or as slowly—as you like. Your personal tutor at the College sends you your lessons—and gives you his friendly help based on years of teaching experience. The College guarantees to continue teaching you until you reach the standard you wish—and all your text-books are provided free of charge.

To: **THE BENNETT COLLEGE (Dept. A 55), SHEFFIELD.**
Please send me free of charge and without obligation, a copy of your prospectus on _____ (subject/s)

NAME _____

ADDRESS _____

Age (if under 21) _____ Please write in block letters.



Send for a free prospectus today! *Just fill in the coupon opposite and post it off—The Bennett College will send you a prospectus free of charge and without obligation.*

EXCELLENT COURSES in the following subjects are also offered by The Bennett College. Write on your coupon the course that interests you.

- ELECTRICAL ENGINEERING
- RADIO ENGINEERING
- ELECTRICAL WIRING
- TELECOMMUNICATIONS
- POWER STATION ENGINEERING

TELEVISION TUBES

**GUARANTEED FOR THREE MONTHS.
EX-CHASSIS AND PICTURE TESTED.**

MAZDA, EMISCOPE, FERRANTI, COSSOR,

EMITRON, BRIMAR, MULLARD

**12" £6-0-0 14" £5-5-0
15" £7-5-0 17" £7-5-0**

SPECIAL :

MAZDA REBUILT 12" £9-0-0

Guaranteed for six months.

Cash with order for prompt delivery: write

E. B. ELECTRONICS (TUBE DEPT. T.)
28 PEMBRIDGE ROAD,
LONDON, W.11

or phone BAY 9262.

All prices include post and packing.

We Regret No Personal Callers for Next 3 Months

VALVES • SAME DAY SERVICE

All Guaranteed New and Boxed

1.4v. midget, 1R5, 1S5, 1T4, 3S4, DAF91, DF91, DK91, DL92, DK92, DL94: Any 4 for 27/6.

1A7GT	13/6	6U4GT	11/6	D77	6/-	EF50	6/-	PCL82	10/-
1C5GT	15/6	6V6G	7/-	DAC32	11/-	EF55	9/6	PCL83	9/6
1H5GT	11/-	6V6GT	7/6	DAF95	8/6	EF80	9/6	PEN46	6/6
1N5GT	11/-	6X4	7/-	DF33	11/-	EF81	8/6	PL38	22/6
1R5	8/-	6X5GT	6/6	DF96	8/6	EF83	7/6	PL81	20/-
1S5	7/6	7B7	8/-	DH76	7/6	EF86	11/6	PL82	9/-
1T4	7/6	7C5	8/-	DH77	8/-	EF89	9/6	PL83	10/6
3Q4	9/-	7C6	8/-	DK32	13/6	EF91	6/-	PY80	8/-
3Q5GT	9/6	7H7	8/-	DK92	8/-	EF92	5/6	PY81	8/-
3S4	7/6	7S7	9/-	DK96	9/6	EL32	5/6	PY82	7/-
3V4	8/-	7V4	8/-	DL33	9/6	EL49	22/6	PY83	9/-
5U4G	8/-	12AH8	9/-	DL35	15/6	EL41	9/-	PZ30	18/6
5V4G	11/9	12AT7	8/-	DL96	8/6	EL42	10/6	SP41	3/6
5Y3GT	7/6	12AU7	8/-	EABC80	7/9	EL84	9/-	SP61	3/6
5Z4G	9/6	12AX7	8/-	EAF42	10/6	EM34	10/-	TH41	17/6
6AK5	4/6	12BA6	8/-	ED91	6/-	EM80	10/-	U25	14/6
6AL5	4/6	12J7GT	10/6	EBB33	7/6	EY51	12/6	U25	13/6
6AM5	5/-	12K7GT	7/6	EBC41	9/6	EY86	17/6	U50	7/6
6AM6	6/-	12K8GT	14/-	EBF80	9/6	EZ40	7/9	U76	7/6
6AQ5	7/6	12Q7GT	7/6	EBF89	9/-	EZ41	9/6	U78	7/-
6AT8	9/-	12Z3	7/6	ECC81	8/-	EZ80	7/6	UABC80	9/6
6BA8	7/6	1AS7	12/-	ECC82	8/-	EZ81	9/6	UAF42	10/6
6BE6	7/6	25L6GT	9/-	ECC83	8/-	FW4500	9/6	UBC41	3/6
6BJ6	7/6	25Z4C	9/6	ECC84	10/6			UBP80	9/6
6BR7	8/6	25Z8GT	15/-	ECC85	9/6	GZ32	11/6	UCH42	8/-
6BW6	7/6	35L9GT	9/6	ECP80	10/6	KT39C	8/6	UF41	8/-
6BW7	9/6	35Z9	9/6	ECP82	11/-	KT41	6/6	UF89	10/-
6E1	15/-	35Z1GT	7/6	ECH21	14/9	KT63	6/6	UL41	9/6
6F6G	6/6	35Z5GT	9/-	ECH35	9/6	KTW61	6/-	UL84	9/6
6F12	6/-	43	13/6	ECH42	8/6	MH4	6/-	UY21	15/6
6F13	15/-	50L6GT	3/6	ECH81	8/-	MU14	8/6	UY41	7/6
6J6	5/6	80	3/6	ECL89	9/-	N18	8/-	UY85	7/-
6K7G	4/6	AC/TP	20/-	ECL91	14/9	VP41	12/6	VP41	9/6
6K7GT	6/-	AZ31	11/6	EF37A	8/6	P81	3/6	VP1321	21/-
6K8G	7/9	B36	20/-	EF39	6/-	PCC84	9/-	W76	7/6
6L18	12/6	CL33	16/9	EF41	9/6	PCF80	10/-	W77	5/6
6Q7GT	9/6	D1	3/-	EF42	10/6	PCF82	10/-	Y63	6/-
6SN7GT	7/6					Z77		Z77	6/-

Any Parcel Insured Against Damage In Transit 6d. extra.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL,
LONDON, N.16 STA. 4587



UNDERNEATH THE DIPOLE

TELEVISION PICK-UPS AND REFLECTIONS

By Iconos

Library Shots

ALMOST every television play on BBC or I.T.A. channels has film sequences. These are essential for real exterior scenes, for montages indicating the passage of time or for linking shots specifically introduced to allow the actors to change their costumes. When the principal characters in the play figure in any of these filmed sequences, the job has to be specially filmed for that particular play. General shots without actors, such as long shots of streets, factories, sunsets or rough seas, are used again and again in different

plays, selected from the rapidly growing collections of "stock shots" held in the film library vaults of the BBC, the I.T.A. (including the I.T.-News) and the old established film companies. Some idea of the rapid expansion in this field is shown by the large stocks now held by the BBC Film Library, which have grown from one vault and a staff of two in 1948 (when the Television Newsreel started) to 60 vaults and a staff of 14 in 1957. Many historic tele-recordings are stored here, including such items as Oxford

1951 Boat Race, Bannister's first four-minute mile, numerous public speeches by Sir Winston Churchill, and Sir Anthony Eden's Suez broadcast. Both the historic tele-recordings and the general stock shots are all carefully indexed and documented, in many cases having single sample film frames readily accessible in card index cabinets, so that television play producers can select their film sequence shots with the minimum of delay. There is a considerable amount of exchanges of library shots between the different organisations, facilitated by standardised ordering procedures, fixed search fees and agreed royalties for using the shots. An important branch is that dealing with back-projection shots, such as moving views from trains or cars, rough sea shots and the like. All the earliest films, made using the highly inflammable nitrate film base, have had to be duplicated on to modern safety film stock. Sound film and tape library, built up over many years of sound radio, has also expanded considerably. The use of 1/2 in. tape helps the problem of storage.

Advertising Space

THE tide has certainly turned for the I.T.A. programme contractors. Once there was a time when it appeared to be difficult for the authority to find "takers," and one or two of the pioneer major companies "obliged" by accepting the responsibility of providing programmes for more than one area. Now, with success assured and advertising space for commercials sold for months ahead, there is a rush for securing the concessions for the smaller and less important areas remaining.

North Eastern Area I.T.A.

THE North Eastern I.T.A. station, with studio premises to be based on Newcastle, is the battleground of many contestants for the N.E. area commercial programmes. Applications have been received from several newspaper interests, including the *News Chronicle*, the *Manchester Guardian*, *Reynolds News* and *The Scotsman*. Let us hope that the launching of the Newcastle area I.T.A. station will be a little more smooth than has been the fate of the T.W.W. station at Cardiff. Major difficulties with the



Such is the accuracy required in the floor level of a modern television studio that tests, such as this picture shows, must be made before the floor can be declared "ready for action." A slide projector, mounted on a mobile pedestal, casts a beam of light on to a line drawn round the walls of the studio at a standard height from the ground, and the light should remain on this line as the pedestal is tracked round the studio.

aerial system at the St. Hilary transmitter has delayed the opening of this station from 17th December until some time in January or February. Naturally, there has been much local gnashing of teeth and people have been asking who would make up the consequential loss.

Teething Troubles

PERSONALLY, I think that the I.T.A. Engineering Department, under Mr. P. A. T. Bevan, has done a first-class and speedy job to date, and a hitch of the type that has happened at Cardiff was bound to occur sooner or later. After all, there are precedents for last-moment panics with aerial systems! Years ago, when the BBC changed their 2ZY broadcast transmitter from the Metro-Vickers works at Old Trafford, Manchester, to a warehouse in the centre of the city, radiation from the new site with triple the power was less than from the original experimental station. Bad earthing system, due to the subsoil, was the principal difficulty, and a counterpoise earth had to be hurriedly rigged. The same thing happened at Edinburgh, where the relay station transmitter was located in the University buildings—on rock. At Swansea the mast blew down. But somehow or another each of these BBC transmitters were got going on time with improvised rigs. Captain Eckersley, BBC's then chief engineer, upheld the showman's motto: "The show must go on." It is very much more difficult, however, with transmitting aerials on the commercial television channels. Pressing ahead with all possible speed, someone on I.T.A. had not allowed enough leeway for coping with hidden snags. The T.W.W. programme company can at least console itself with the fact that they have already sold 75 per cent. to 80 per cent. of their advertising time for the first twelve months of operation—which is more than could be said for Rediffusion and A-TV when they first started.

Expansion


WITH a huge revenue now assured, both Rediffusion and A-TV are now considering various forms of expansion in

London: in premises, in equipment, in star values and in ideas. I have heard that very large and valuable sites are being considered by A-TV, whose present technical headquarters is little better than a compact telephone exchange in Foley Street. More filmed programmes are under consideration—either filmed direct or by telerecording—with the object of increasing the sale of programme material to television stations in the Commonwealth and abroad. What will happen when another channel is to be operated in the London area by the BBC or I.T.A.? That will start a veritable gold-rush of world-be programme contractors for the I.T.A. second London area channel concession if that ever materialises. It would also probably result in a general lowering of programme standards to the most puerile levels. This, I am told, is the way to attract the mass television audience!

I.O.W.


THE South Coast I.T.A. transmitter on the Isle of Wight, with a mast at Chillerton Down shared with the BBC, will have programmes provided by Southern Television Ltd., the capital of which was subscribed in equal proportions by the Rank Organisation, the Amalgamated Press and Associated Newspapers Ltd. The headquarters will be in Southampton, where the main studios will be built or converted from existing premises. Little else is known yet of the intentions of Southern Television, but it is not difficult to make a few forecasts. Southampton is a fine progressive town, but it does not rank very high in its support

of the live theatre or music. Therefore, apart from the nationally networked I.T.A. programmes, unless talent is systematically imported into the town for the local programmes—and for the rehearsals—there will have to be a high proportion of outside broadcasts from the nearest main entertainment centres, Bournemouth, Brighton and London. I would have thought it would be worth while to establish branch studios at Brighton, which could be as important to Southern Television as Blackpool is to ABC-TV, Granada

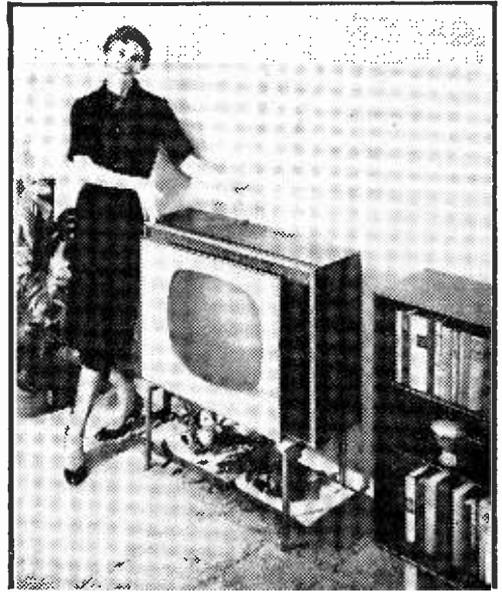

The latest from U.S.A.—the Sylvania Sylouette, a 21in. television console, has a cabinet depth of only 10in. "Floating picture" concept, with picture tube and Halo Light mask extending out 4in. from cabinet, gives a third dimensional effect to the design. The control panel is concealed beneath the top section of the cabinet which slides back for channel selection through "Magic Touch" tuning.

and the BBC. The fame of the Municipal Orchestra at Bournemouth and the Southern Philharmonic Orchestra at Brighton could be enhanced. The latter orchestra is particularly in need of support since the Arts Council decided to support visiting orchestras only. The first-class repertory companies at Worthing, Bognor and Eastbourne should also be able to provide good television material for the programmes to be put out from the I.O.W. transmitter.

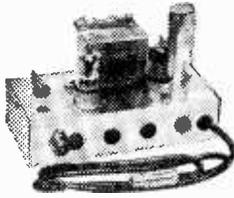

BAND 3 T/V CONVERTER
185 Mc/s—199 Mc/s

Suitable London, Birmingham, Northern and Scottish IFA Transmissions

Mk. 2 Model, as illustrated. Latest double circuit using BUN4 and 6E80 valves giving improved sensitivity (12 db) over standard circuits, built-in Power Supply A.C. 200-250 v. Dimensions only 6 1/2 in. x 4 in. Htn. Single and easy to fit—only external plug-in connections. Wired, aligned and tested ready for use. State Channel required. Guar. Bargain Offer good results or full refund, only **£3.19.6.** Carr. & Pkz. 2/6.

Mk. 1 Model. Using 2 814s or 1F40s. Full constructor's kit of parts including drilled chassis 7 in. x 4 in. x 2 1/2 in., blueprint, valves and all components, etc., excluding Power Supplies to modified W.W. design. Many 100% in satisfactory use. Bargain Offer only 2 gns. P. & P. 2/6. Power Supply Kit, complete, 20/-, P. & P. 1/6. Band 1-Band 3 Switch Kit, 6/6.

CONVERTER ACCESSORIES. Band 1-Band 3 Cross-over Unit, 7/6. Var. Attenuators 60s-300s, 6/9. BNC Pattern Filter, 8/6. Band 3 Aerials—outside single dipole with 4 yds. coax, 12/9. 3 element Beam, 27/6. 5 element, 35/-, etc., etc.

Volume Controls 80 ohm COAX
Loz. ratios, 10,000 ohms
—2 Megohms. Long
spindles. 1 year
Guarantee. Midget Edis-
wan type.
No. sw. S.P. Sw. D.P. Sw.
3/- 4/- 4/9

Linear Ratio, 10,000
ohms — 2 Megohms.
Less switch, 3/- each.
Coax plugs, 12/-. Coax
sockets, 1/-, Comps 1/-
1/3. Outlet boxes, 4/6.

TWIN FEEDER, 80 ohms, 6d. yd.; 300 ohms, 8d. yd.
TWIN SCREEN FEEDER, 80 ohms, 1/3 yd.
50 OHM CABLE, 8d. per yd., 1/4 in. dia.

TRIMMERS, Ceramic, 4 pf.-70 pf., 9d. 100 pf., 150 pf., 1/3; 250 pf., 1/6; 400 pf., 1/9. PHILIPS
Beehive Type—2 to 8 pf. or 3 to 30 pf., 1/- each.
RESISTORS.—Pref. values 10 ohms to 10 megohms.


CARBON
20% Type, 1 w., 8d.;
1 w., 6d.; 1 w., 6d.;
1 w., 9d.
10% Type, 1 w., 9d.;
5% Type, 1 w., 1/-;
1/2 Hi-Stab, 1 w., 2/-

WIRE-WOUND POTS.
Pre-set Min. T.V. Type
Knurled Stotted Knob.
All values 25 ohms to 30
K. 3/- ea. 50 K., 4/-.
Ditto Carbon Type,
50 K. to 2 Meg., 3/-.

SOLO SOLDERING IRONS (200-220 v. or 250-250 v.)
25 watt Instrument Type, 21/6; 65 watt
Pencil Bit Type, 26/6; 65 watt Dual Bit Type,
25/-.
Comprehensive stock of spares available.

SPEAKER FRET.—Expanded Bronze anodised
metal 8 x in., 2/3; 12 x in., 3/-; 12 x 12 in., 4/6;
12 x 16 in., 6/-; 24 x 12 in., 9/-, etc.
TYGAN FRET (Murry pattern) 12 in. x 12 in., 2/-;
12 x 18 in., 3/-; 12 x 24 in., 4/-, etc.

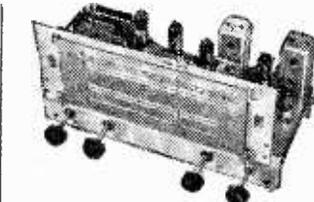8" P.M. SPEAKER (3 ohms)
Ex Mfrs. Units: Rola, W.B., Celestion, etc.
All reconditioned and guaranteed. Ideal Ext.
Unit. Bargain, 7/6. Carr. 1/6. Ditto with
O.P. Trans., 9/6.



ALL WAVE RADIOGRAM CHASSIS
3 WAVEBANDS
5 VALVES

LATEST MIDGET
BVA
SERIES

Brand new and extra. A.C. 200-250 v. 4 pos. W.W. sw. Short-Midium-Long-Gram. P.U. socket. High Q dust core coils. Latest circuit technique, delayed AVC and neg. feedback. O.P. 4 watts. Chassis size, 13 1/2 x 5 1/2 x 2 1/2 in. Dial, 10 in. x 4 in. Hor. or vert. station names. Walnut or ivory knobs to choice. Aligned and calibrated ready for use. Sensitivity and Quality at Low Cost.

Double sound main trans. **BARGAIN 01 gns.**
Carr. and ins., 4/6.
8 or 10in. speaker to match, 20/- and 25/-.
7 Valve De Luxe, push-pull EL41 version, 7 watt. outfit with H. Dyna Trans. £12.10.0. Carr. & Ins., 5/-.

RECORD PLAYER BARGAINS
SINGLE PLAYERS—LATEST MODELS.

- 4 Speed BSR (Model T.U.C.O.) 99.6
- 4 Speed COLLARO (Junior), 5 gns.
- 4 Speed GARRARD (48.F.) £7.10.0

Carriage and Insurance, 3/6.
AUTOCHANGERS—LATEST MODELS.
4 speed BSR (Model U.S.S.) £215.0.

4 speed COLLARO (RC45), etc., £9.15.0.
4 speed GARRARD (RC4 129H), 94 gns.
Carriage and Insurance, 4/9.

All above models Brand New and Gnar.
Fitted latest style I weight Xtal. P.U. with
turnover head and twin sapphire stylus.



RECORD PLAYER CABINETS

Contemporary style rexine covered cabinet in
mottled red with cream interior. Size 18 1/2 x 13 1/2 x ht.
8 1/2 in., fitted with all accessories, including speaker
baffle board and plastic fret. Space available for all
modern amplifiers and autochangers, etc. Uncut
record player mounting board 14 x 13 in. Cut mounting
boards available.

Cabinet Price, **£3.3.0.** Carr. and ins. 3/6.

2 VALVE AMPLIFIER (to fit above cabinet),
modern circuit with EL41 output, ready built, with
6in. speaker and output transformer, £3.12.6,
carr. and ins. 2/6.

SCOTCH BOY, EMITAPE, etc., 1,200ft., 27/-. Long
playing, 1,800ft. reels, 45/- Paper tape, good
quality, 1,200ft., 12/6. Reels only, 3in., 3/-; 5 in.
3/8; 5 1/2 in., 4/-; 7 in., 4/3.

I.F. TRANSFORMER—465 kc/s.
Brand new ex-manufacturer's midget I.F.T.
size 2 1/2 in. x 1 1/2 in. dust core tuning. Litz
wound coils, High Q. Bargain offer, 7/6 pair.

CONDENSERS.—Mica or S. Mica. All pref. values.
3 pf. to 680 pf., 6d. ea. Ceramic types, 2.2 pf. to 5,000
pf., 9d. each. Tubulars, 450 v. Hunts and T.C.C.
0.005, .001, .005, .01 and 1, 350 v. 9d. .002, 5s,
1, 500v. Hunts, T.C.C. 1, .25 Hunts, 1.5 Hunts,
1.9, 1, 1,500 v. T.C.C. (Simplex), 3.8, .001 6 kv.
T.C.C., 5/6. .001 25 kv. T.C.C., 9/6.

SILVER MICA CONDENSERS—
10% 5 pf. to 500 pf., 1/-, 600 pf. to 3,000 pf., 1/-,
15% 1.5 pf. to 300 pf., 1/8. 315 pf. to 5,000 pf., 2/3.
SPEAKERS.—PM 3 ohm, 2 1/2 in. Blac., 16/8; 3 1/2 in.
Goodmans, 18/6; 5 in. R.A., 17/6; 6 in. Celestion,
18/6; 7 x 4 Goodmans, 18/6; 5 in. Elac, 20/-;
10 in. R.A., 25/-; 12 in. Plessey, 35/-.

JASON F.M. TUNER UNIT (87 mc/s-103 mc/s).
As described in Radio Constructor. Designer
Approved Kit of parts to build this modern highly
successful unit, drilled chassis and superior type
illuminated glass dial, coils, cans and all quality
components, etc., for only 5 gns., post free. Set of
4 specified Miniature Valves, 30/-, post free.
Illustrated handbook with full details, 2/-, post free
2-DAY ALIGNMENT SERVICE NOW AVAILABLE.

NEW BOXED VALVES ALL GUARANTEED

1R5, 1F17 6 DAF95	9/-	ECU40	10/6	1P1453	12/6
1R5, 1R7 6 D903	7/6	ELF41	10/6	1P1452	10/-
34A, 3V4 6S-DK96	9/-	EF40	12/6	1P1451	8/6
3Z4	9/6	EDL96	9/-	EF46	12/6
6AT7	8/6	EL35L	10/6	EF41	8/6
6AT7	6/6	EABCS9	9/6	EL41	10/6
6K4	8/6	EB01	6/6	EL44	14/6
6K7	8/6	EB41	10/6	EL52	11/6
6BN7	8/6	BC38	9/6	EL240	8/6
6V6	7/6	EC84	12/6	EL240	8/6
6X4	7/6	EC90	12/6	EL14	9/6
6X5	7/6	EF42	12/6	EL94	10/6
6Y5	8/6	EL42	10/6	EL94	10/6
7Y4	8/6	EL44	10/6	EL94	10/6

SPECIAL PRICE PER SET

1R5, 1F14, 1R5, 3M or 3V4	...	27/6
1R5, 1R7, 1P96, 1P496	...	35/-
DK9, 6K7, 6V7, 6V6, 3Z4 or 6X5	...	35/-

ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	Cat. Type	Clips	3d. ea.
25 25 v., 50 12 v.	1/9	8, 450 v.	2/6
50 25 v., 4 250 v.	2/-	8, 450 v. T.C.C.	4/6
100 25 v., 2 450 v.	2/-	8, 450 v. Hunts, 5	6
8 450 v. B.E.C.	2/3	16, 450 v. T.C.C.	5/6
8 500 v. Dub.	2/9	32 350 v.	4/6
8 500 v. Dub.	4/6	32-32 450 v. Hunts	4/6
16 450 v. T.C.C.	5/-	32-32 450 v. T.C.C.	6/6
16 450 v. B.E.C.	3/6	250 350 v. B.E.C.	8/6
16 500 v. Dub.	4/-	60 350 v. T.C.C.	6/6
16 450 v. T.C.C.	5/6	60 100 350 v.	11/6
32 350 v. Dub.	4/6	64 120 275 v.	11/6
32 500 v. Dub.	4/6	60 250 275 v.	12/6
50-50 350 v. B.E.C.	6/6	100 200 275 v.	12/6
32-32 350 v. B.E.C.	5/6	3,000 mfd. 5 v.	3/6

TRANSISTOR.—Midget electronics, 2 mfd.
1 mfd., 8 mfd., 6 v., 3/6. 6 mfd., 10 mfd., 10 mfd.,
3 v., 3/6. 32 mfd., 1 1/2 v., 3/6.

**SENTERCEL RECTIFIERS. E.B.T. TYPE FLY-
BACK VOLTAGES.**—K3 25 2 kv., 5/-; K3 30
2 kv., 6/9; K3 45 3.6 kv., 7/3; K3 50 4 kv.,
7/8; K3 100 8 kv., 12/6.

MAINS TYPES.—RM1 125 v., 60 mA., 4/9; RM2
125 v. 100 mA., 5/6; RM3 125 v. 120 mA., 7/6;
RM4 250 v., 250 mA., 18/-; RM4B Type 270 mA.,
17/6. RM5, 250 v. 300 mA. 21/-.

MAINS TRANSFORMERS.—Made in our own
Workshops to Top Grade specs. Fully interleaved
and Impregnated. **RADIO AND AMPLIFIER**
Type.—250 v. 60 mA., F.W. sec. 5 v. or 6.3 v. I.a.
rect. 6.3 v. 2.5 a. set HTR., 22/6, etc. C.R.T. HTR.
ISOLATION TYPE.—Low leakage with or without
25% sec. boost voltage. Ratio 1:1 or 1:25. 2/6,
10/6; 4 v., 10/6; 6.3 v., 10/6; 13.3 v., 10/6.
Ditto with mains primary, 200 25 v. v., 12/6.

SPECIAL TRANS.—Wound to your requirements.

TRANSISTORS

Mfrs. surplus PNP Junction type.
A.P. Type, 800 kc/s., 250 m.w., 9/6
R.F. and L.O. Mixer Type, 25 Mc/s., 19/6.

All tested and guaranteed.
Transformer Components.—Midget I.F. transf.
315 kc/s. 5/-; Ferrite Mlab Aerial (dual range),
13/6; M. and L.W. Osc. and 1st I.F., 11/8;
Push Pull Instrument transf., 8/6; Push
Pull output transf., 8/-;
M.Coil Earpiece, 2in. diam., 150 ohm, 4/9.
Bal. Arm. Phone Insert, 11in., 50 ohm, 3/9.

TRS RADIO COMPONENT SPECIALISTS (Est. 1946)
270 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Listed above are only a few items from our very large
stock. Send 3d. stamp today for Complete Bargain
List.

Hours: 9 a.m.—6 p.m., 1 p.m. Wed.

Terms: C.W.O. or C.O.D. kindly make cheques, P.O.O. or payable to T.R.S. Post, Packing up to 30s. Tax, 10s. 1/1, 30s. 1/5, 50s. 2/6, 100s. 5/6.



TRANSFORMER AND COIL WINDING CAPACITY
AVAILABLE FOR PROTOTYPES AND SMALL RUNS

OPEN ALL DAY SAT.

TRANSISTORS

JUNCTION TYPE P-N-P

(British Manufacture)

RED-SPOT 800 kc s Audio Frequency.....	10-
BLUE-SPOT 1.6 Mc s Mixer and Frequency Changer.....	15-
WHITE-SPOT 2.5 Mc s R.F. and I.F. Amp.....	20-

All Transistors are Tested and Guaranteed.
N.B. The Red Spot is similar to Mullard OC71.

"TRANSISTOR—8"

Push-Pull Portable Superhet
Can be built for **£11/10/-**.

This Portable 8 Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set. Simplified construction enables this set to be built easily and quickly into an attractive lightweight cabinet supplied.

TEN STAR FEATURES

- * 8 Specially Selected Transistors
- * 250 Milliwatts Output Push-Pull
- * Medium and Long Waves
- * Internal Ferrite Rod Aerial
- * 7 x 4 Elliptical Speaker
- * Drilled Plastic Chassis 8½ x 2½ in.
- * Point to Point wiring and practical layout
- * Economical. Powered by 7½ v. battery
- * Highly sensitive
- * Attractive lightweight contemporary case
- * N.B. Pair of Matched OC72's or equiv. Supplied at additional cost of 40/-.

We can supply all these items including Cabinet for **£11/10/-**. All parts sold separately.

Send for circuit diagrams, assembly data, illustrations and instructions, and full shopping list, 3d. in stamps.

Call and hear demonstration model.

"EAVESDROPPER"

THREE TRANSISTOR POCKET RADIO
(No Aerial or Earth required)

Variable Tuning. Total cost, as specified including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit and plastic case. **77/6** POST FREE.
All items sold separately.
With single phone. **82/6**. With Acos Mike. **80/-**. With Min. Hearing Aid. **90/-**.

MINI-TWO

TWO-TRANSISTOR MINIATURE POCKET RADIO

The smallest Transistor set offered on the market. Variable Tuning, Drilled Chassis, Plastic Case size 3in. x 2in. x 1in., Miniature Hearing Aid, 2 Transistors and all components including 1½ volt Battery. Circuits and full practical layout diagrams.

Total Cost **49/6** Complete

"HOMELIGHT" 2-TRANSISTOR PERSONAL PORTABLE

Variable Tuning

We can supply all components including 2 Transistors, Diode, Resistors, Condensers and Miniature Hearing Aid and Plastic Case size 4½ x 2½ x 1½ in. and 1½ v. Battery FOR 52/6. All items sold separately.

R.F.25, 12 6. R.F.26, 25-
Brand new with valves, cart.
2/6.

6 v. VIBRATOR PACKS
Output 120 v. 40 mA., 12 6.
Brand new.

373 MINIATURE I.F. STRIP 9.72 Mc/s

The ideal F.M. conversion unit as described in P.W. April May, 1957. Complete with 6 valves, two EF91's, two EF92's and one EB91, I.F.T.'s, etc., in absolutely new condition. With circuit 12/6 (less valves). **42/6** (with valves). Postage & Packing 2/6 (either type).

SEND STAMPS FOR NEW 1958 28-PAGE CATALOGUE
OPEN MONDAY to SAT. 9-6. THURS. 1 o'clock.

HENRY'S RADIO LTD.

5 HARROW ROAD, EDGWARE ROAD, LONDON, W.2
TEL.: PADDINGTON 1003-9

TELEVISION TUBES

RECLAIMED GUARANTEED:

12"—£6 14"—£5 17"—£7.10.0

FULLY GUARANTEED HIGH QUALITY
REBUILT:

12"—£9 14"—£11.10.0 15"—£12 17"—£13.10.0

CARRIAGE AND INSURANCE 15/6 EACH TUBE

MAIL ORDER ONLY

Orders and enquiries to:

PRIME ELECTRICS

36 QUEENSDALE ROAD, W.11

THE HOME CONSTRUCTOR'S FIRST OPPORTUNITY

Make Your Own Integral 30in.
Projection Television Set!

Every component necessary, full wiring
diagrams and working chart supplied.

Complete Kit ... **£40.**

CABINET AVAILABLE, AT **£15.**

SEND STAMPED ADDRESSED ENVELOPE
FOR FULL DETAILS AND LIST OF COM-
PONENTS WHICH MAY BE ORDERED
SEPARATELY

TO

J. S. FIELDEN (DEVON) LTD.

BRANSCOMBE, SEATON, DEVON.

Telephone: BRANSCOMBE 371, 2, 3

LINE OUTPUT TRANSFORMERS

Most types available. State Make and Model
Number of Receiver when ordering.

S.A.E. please with all enquiries.

HOWORTH

51 POLLARD LANE, BRADFORD, 2, YORKS

Tel. 37030

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

A WARNING

SIR,—I should like to recount an experience of mine which I hope will serve as a warning to others. I had a set given to me for servicing and I removed it as far as it would come from the cabinet. It was so constructed that it would not come right out. I then made some checks with a voltmeter/ohm-meter, and at one point found a very low reading. Checking back to the service sheet showed that the reading should have been much higher, so I located a resistor at that point, unsoldered it, replaced it with one which came from my "good spares box" and again made a check.

To my surprise the same original reading was obtained. I traced through the wiring and there were no shorts or leaks apparent, and after disconnecting each end of the complete circuit wire at this point I put both prods of the test-meter across the ends and everything was as it should be. Soldering one end of the circuit back I made another check and everything was all right. I then connected the remaining end and made a check as at first, and everything was again all right. I sat and thought over this and it suddenly dawned on me what had happened. Owing to the rather awkward part in the chassis where the test was being made I was using one probe on the actual component or wiring, one clipped to the chassis and my other hand was supporting the chassis. The lead clipped on to the chassis was making a poor connection due to dirt and corrosion, and the actual test-meter circuit was being completed through my body, as I was holding the test probe. I repeated the "fault" several times to make sure of this, and my warning is: make sure the clip of such a tester is in good contact with the chassis or "earthy" side by making use of a soldered contact somewhere in the wiring, and *do not touch the chassis*, even though the set may not be connected to the mains.—G. H. FERRENT (N.4).

DABLERS

SIR,—Having read the various letters on "dabblers" and "anti-dabblers" in your correspondence columns, I should like to quote you an incident that happened to me.

Some seven months ago an acquaintance of mine purchased a secondhand TV set, quite cheap, and took it to a dealer for an overhaul and to have it converted to Rediffusion (wired TV). The dealer informed the owner that it needed new smoothing condensers, a sync separator valve and a frame amplifier valve. He also told him he'd tried the set both on aerial and Rediffusion input and that it received a perfect picture on

BBC, but was no good on I.T.A., and that a new tube was required to get I.T.A. The owner thought that having got so far he might as well have the new tube—another £18. The set was duly delivered and installed. At the top of the picture was a black line about 1½ in. down from the top of the mask. The dealer said this couldn't be removed because there was a fillet in the top corner of the cabinet and that he couldn't get the tube up enough without removing the fillet. The line hold was very critical and the dealer put this down to the fact that it was an old set (my estimation 4-5 years), and that he couldn't do any more.

The owner took it for granted and paid up. Over £30 altogether for tube and conversion. All this time he has endured a picture of which he could never see the bottom and which was constantly breaking up.

Then he asked me if I would look at it, knowing that I had built my own set and I knew a little bit about them. I found a faulty coupling condenser from sync to line oscillator which cleared the line hold trouble. The picture height control I set correctly and shifted the focus magnet, which removed the black line and brought the picture up to its proper position. I also found four valves had been removed from the now inoperative vision unit. The owner couldn't thank me enough, and says now it's a treat to watch a decent programme.

This may sound fantastic to you, as it did to me when the owner told me, but I can assure you it is absolutely true. I am only an amateur, but I think it's a disgrace the way some of these so-called professionals prey on the innocent public.—"CONTRAST" (Name and address supplied.)

AERIAL DESIGN

SIR,—I am a service engineer and have been surprised at some of the misconceptions which exist as to aerial design. A simple dipole for television is dimensioned to be resonant at about 1.5 Mc/s below the vision carrier frequency. This is done so that the television signal will be spread evenly on either side of resonance. When, however, additional elements are added to the aerial this band width decreases. With an H-type dipole it will not decrease sufficiently to be noticeable, but with multi-element arrays it can be serious. In fringe areas this has, unfortunately, to be tolerated, as picture resolution is the most important point. In other areas, therefore, it is best not to use more directors on the aerial than are absolutely necessary for good picture resolution.—R. BROWN (Sidcup).


SPECIAL NOTE

Will readers please note that we are unable to supply Service Sheets or Circuits of ex-government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

News From the Trade

New Wolsey Lines

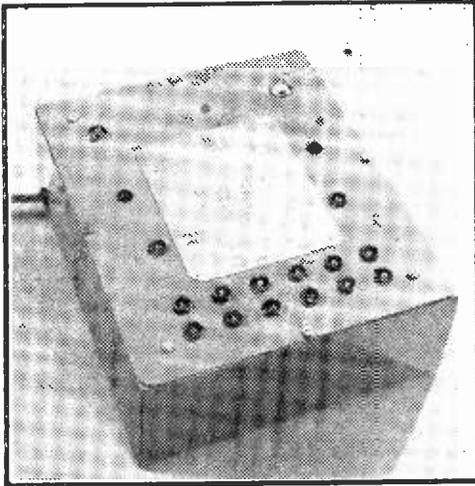TWO new products are announced by Wolsey Electronics and one is shown below. The first is a wide spaced, wide stacked double array aerial for long range reception. This is to be known as the "Interceptor 5" and will be available in four types. Model 360/DY5 is the double array only and costs £5 15s., whilst DY5L is the



The New Wolsey Distribution Box.

same with the inclusion of a 4ft. 6in. crank mast, and chimney lashing equipment. This costs £7 6s. 6d. Model ADY5M is the aerial with a 9ft. \times 1½in. mast and BDY5M is the aerial with a 12ft. \times 2in. mast, these costing £9 7s. 6d. and £11 5s. respectively.

The other item is a Distribution Unit, type D.S.14. This has been designed to meet the demand for feeding multiple television units from a single aerial system. It provides 12 outlets each having a Band I and a Band III signal. The outlets have an isolation figure better than 20dB. A gain control is available on each channel so as to balance the Band I and Band III signals. The units may be connected in cascade if more than 12 outlets are required. The unit measures 10in. \times 8½in. \times 3½in. and weighs 6lb. Finished in green and gold and with a 9ft. three-core lead the price is £15 15s.—Wolsey Electronics Ltd., Cray Avenue, St. Mary Cray, Orpington, Kent.

Beethoven Model B.106

THE latest Beethoven model is shown here mounted on legs, which are an optional item available separately at 2 gns. This new receiver is a 17in. rectangular set with unbreakable window plate which may be removed easily for cleaning. A special high-efficiency video stage provides a contrasty picture which has resulted in the makers referring to the "black

magic contrast," whilst the tuner with R.F. stage is known as the "miracle tuner." A.P.C. is fitted and also a circuit arrangement known as automatic focusing. With all-channel tuning, and designed for A.C./D.C. mains operation this receiver is listed at 68 gns. inclusive of purchase tax.—Beethoven Electric Equipment Ltd., 89, Reddish Lane, Gorton, Manchester 18.


New J-Beam Aerial Range

J-BEAM AERIALS LTD., of Northampton, have just released a new range of aerials which are thought to be ideal for all locations due to their no compromise features and absence of side and rear pick-up.

The Double Beam series is based on the skeleton slot principle which not only gives optimum gain and bandwidth on Band III, but excellent matching properties improving Band I performance.

The Double Beam range has been proved, by means of measured polar diagrams, to be completely free from compromise resulting in perfect performance on all bands.

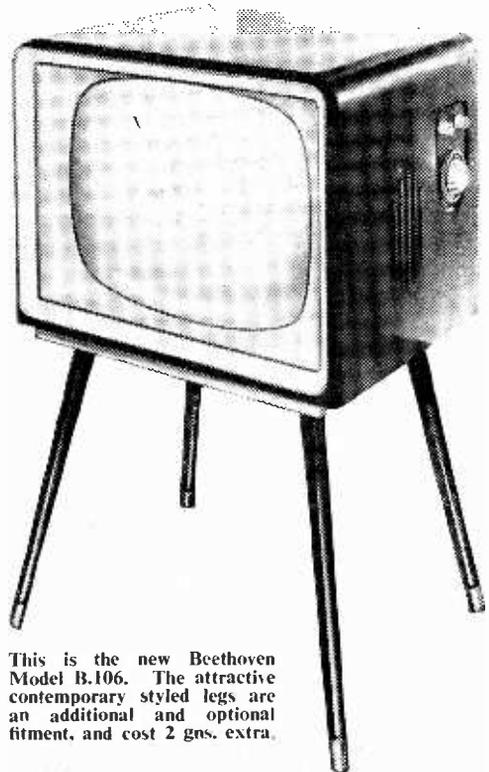Band II may be added with no derogatory effect to the TV channels, as each Band is completely isolated by the use of coaxial sections.—J-Beam Aerials Ltd., Northampton.




This is the new Beethoven Model B.106. The attractive contemporary styled legs are an additional and optional fitment, and cost 2 gns. extra.

Wanted!

QUALIFIED MEN AND WOMEN

Industry & Commerce offer their best posts to those with the necessary qualifications—such posts that will bring personal satisfaction, happiness, good money and security. As part of a modern industrial organisation, we have skilled knowledge of what is required in industry to-day and the best means of training personnel for its present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed below. Make your own choice and write to us to-day for further information. There is no obligation of any kind.

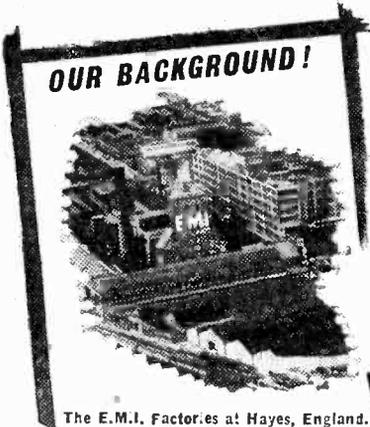

The E.M.I. Factories at Hayes, England.

The only Home Study College operated by a world-wide manufacturing organisation

EMI

INSTITUTES

PERSONAL & INDIVIDUAL TRAINING IN—

- | | | | |
|---------------------------------------|-----------------------------------|------------------------------------|-----------------------------------|
| Accountancy | Customs Officer | Languages | Refrigeration |
| Advertising | Draughtsmanship | Management | Sales Management |
| Aeronautical Eng. | Economics | Maintenance Eng. | Sanitary Engineering |
| A.R.B. Licences | Electrical Eng. | Mathematics | Salesmanship |
| Art (Fashion, Illustrating, Humorous) | Electrical Installations | M.C.A. Licences | Secretaryship |
| Automobile Eng. | Electronics | Mechanical Eng. | Shorthand & Typing |
| Banking | Electronic | Metallurgy | Short Story Writing |
| Book-keeping | Draughtsmanship | Motor Eng. | Short Wave Radio |
| Building | Eng. Drawing | Painting & Decorating | Sound Recording |
| Business Management | Export Heating & Ventilation Eng. | Photography P.M.G. Certs. | & Reproduction Telecommunications |
| Carpentry | High Speed Oil Engines | Police Production Eng. | Television Time & Motion Study |
| Chemistry City & Guilds Exams | Industrial Admin. | Production Planning | Tracing |
| Civil Service Management | Jig & Tool Design | Radar Radio Amateurs (C&G) Licence | Welding |
| Commercial Subjects | Journalism | Radio & Television Servicing | Workshop Practice |
| Commercial Art & Drawing | | | Works M'gmt and many others |

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Examinations, R.T.E.B. Serv. Cert., R.S.A. Certificates, etc.

NEW! Courses with PRACTICAL EQUIPMENT

in RADIO · TELEVISION · MECHANICS
CHEMISTRY · ELECTRICITY
DRAUGHTSMANSHIP · PHOTOGRAPHY etc., etc.



COURSES FROM 15/- PER MONTH

POST THIS TODAY

E.M.I. INSTITUTES, Dept. 136K, London, W.4

NAME _____ AGE _____
(if under 21)

ADDRESS _____

Subject(s) with/without equipment _____

JAN. 58

We shall not worry you with personal visits



BLOCK CAPS PLEASE

IC 92

-Part of "His Master's Voice", Marconiphone, etc. etc.

RADIO SUPPLY CO. (LEEDS) LTD.

Dept. N.
32, THE CALLS, LEEDS 2.

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/9 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. S.A.E. with enquiries, please. Full list 6d.; Trade list 5d.

R.S.C. TRANSFORMERS
Fully Guaranteed
Interleaved and Impregnated.
Primaries 200-230-250 v. 50 c/s screened
TOP SHROUDED DROP THROUGH
250-0-250 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 16/9
350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 29/9

FULLY SHROUDED UPRIGHT
250-0-250 v 90 ma, 6.3 v 2 a, 5 v 2 a
Midjet type 21-3-in. ... 17/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 26/9
250-0-250 v 100 ma, 6.3 v 6 a, 5 v 3 a
for R1355 Conversion ... 31/-
300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
350-0-350 v 150 ma, 6.3 v 4 a, 0-4-5 v 3 a ... 33/9
425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v
4 a, C.T. 5 v 3 a ... 49/9

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s Primaries : 6.3 v
1.5 a, 5/9 ; 6.3 v 2 a, 7/6 ; 0-4-5 v 2 a, 7/9
12 v 1 a, 7/11 ; 6.3 v 3 a, 8/11 ; 6.3 v 6 a, 17/9.

CHARGER TRANSFORMERS
200-250 v 0-9-15 v 1 a, 11/9 ; 0-9-15 v 3 a, 16/9 ;
0-9-15 v 5 a, 19/9 ; 0-9-15 v 6 a, 22/9.

OUTPUT TRANSFORMERS
Standard Pentode 5,000 to 3 ohms ... 4/9
Small Pentode 6,000 to 3 ohms ... 3/9

SMOOTHING CHOKES
250 ma 5 h 50 ohms ... 11/9
100 ma 10 h 250 ohms ... 8/9
80 ma 10 h 350 ohms ... 8/9
60 ma 10 h 400 ohms ... 4/11

SELECTION METAL RECTIFIERS
R.E.C. 300 v 250 ma, 12/9 ; 120 v 50 ma, 3/9 ;
6/12 v 1 a F.W., 4/11 ; 240 v 50 ma, 4/11 ;
12 v 2 a F.W., 8/9 ; 6/12 v 4 a, 14/9 ; 250 v
80 ma, 7/9 ; 6/12 v 6 a F.W., 19/9 ; 6/12 v
10 a, 25/9 ; 6/12 v 15 a, 35/9 ; 24 v 2 a, 14/9
C-O-N-I-A-L Cable 1in. ... 8d. yd.
75 ohms 14/36 ... 11d. yd.
Thin-screened Feeder ... 11d. yd.

BATTERY SET CONVERTER KIT
All parts for converting any normal type
of Battery Receiver to A.C. mains 200-250 v
50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma.
Fully smoothed and fully smoothed L.T.
of 2 v at 0.4 a to 1 a. Price including circuit
49/8. Or ready for use, 9/9 extra.

**ALL DRY RECEIVER BATTERY
ELIMINATOR KIT**--All parts for the
construction of a unit (metal-case
5 1/4-2in.) to supply Battery Portable
receivers requiring 90 v and 1.5 v. Fully
smoothed. From 200-250 v 50 c/s mains.
Price, inc. point-to-point wiring dia-
grams, 39/9. Or ready for use, 46/9.

**EX-GOVT. DOUBLE WOUND STEP
UP-STEP DOWN TRANSFORMERS**
10-0-100-200-220-240 v to 0-5-7.5-11.5-13.5 v
or REVERSE. 80-100 watts. Only 11/9,
plus 2/9 post. 10-0-100-200-220-240 v to
9-0-110-122-136-148 v or Reverse. 200
watts. 35/9, plus 7/6 carr. Both 50 c.p.s.

EX-GOVT. CASES. Well ventilated black
crackle finished, undrilled cover. Size 14
x 10 x 8 in. high. IDEAL FOR BATTERY
CHARGER OR INSTRUMENT CASE.
OR COVER COULD BE USED FOR
AMPLIFIER. Only 9/9, plus 2/9 postage.
Size 13 1/2 x 8 1/2 x 6 1/2 in. with undrilled perforated
cover finished stoved grey enamel.
7/9, plus 2/9 post.

EX-GOVT. VALVES (NEW)

1T4	7/9	6J6	4/9	6AT3	7/9
1S5	7/9	6KTG	3/9	EB91	8/9
3S4	8/9	6X5GT	7/9	ECC91	4/6
5Y3G	7/9	6SN7GT	8/9	EF80	8/9
6J5G	4/9	6L6G	11/9	EF35	4/9
6K8G	9/9	807	7/9	EL32	3/9
6STJGT	6/9	12A6	7/9	EL34	10/6
EF39	5/9	2574G	9/9	EL91	5/9
6V6G	7/9	35Z4	6/9	KT66	11/9
6U5G	3/9	MH4	4/9	SP61	2/9

EX-GOVT. MAINS TRANSF.
Removed from New ex-Govt. units.
Primary 0-200-130-250 v Scss 275-0-275
v 100 ma, 6.3 v 7 a, 5 v 3 a ... 19/9

EX-GOVT. SMOOTHING CHOKES--
80 ma 10 h 150 ohms ... 3/11
100 ma 5 h 100 ohms Tropicalised ... 3/11
100 ma 8-10 h 100 ohms Parmeko ... 6/-
120 ma 12 h 100 ohms ... 9/9
150 ma 6-10 h 150 ohms Trop. ... 6/9
150 ma 10 h 150 ohms ... 11/9
250 ma 5 h 50 ohms ... 12/9
100 ma 20 h 200 ohms ... 19/9

E.H.T. SMOOTHERS
0.2 mfd. 5,000 v Cans (ex-Govt.), 2 1/11.
BATTERY CHARGER KIT--Consisting
of attractive Blue Hammer Case,
Transformer, F.W. Rectifier, Fuse, Fuse-
holder, Tag Strip Grommets and Circuits.
For mains input 200-230-250 v 50 c/s, 6 v 2 a,
25/9 ; 6 v or 12 v 2 a, 31/6 ; 6 v or 12 v 4 a,
35/9. Any type assembled and tested for
6/9 extra.

**R.S.C. 6 v or 12 v 4 a
BATTERY CHARGER**
For normal A.C. mains
input 200-230-250 v 50 c/s
Selector panel for 6 v or
12 v charging. Variable
change rate of up to 4
A.M.P.s. Fuse, and with
meter. Well ventilated
case with attractive
hammer finish. Guaranteed
for 12 months.
75/- Carr. 3/6



BATTERY CHARGERS--For mains
200-250 v 50 c/s. Output for charging 6 v or
12 v at 1 amp. In strong metal case. Only
27/9. Above can also be used for electric
train power supply.

D.C. SUPPLY KIT--Suitable for Elec-
tric Trains. Consists of mains trans.
200-250 v 50 c.p.s. A.C., 12 v 1 a Selenium
F.W. Bridge Rectifier, 2 Fuseholders, 2
Fuses, Change Direction Switch, Variable
Speed Regulator. Partially
drilled Steel Case, and Circuit. 29/9

NEW-MAX ELECTRONICS LTD.

For London's Finest Bargains in
electronics, television and radio
equipment.

500 REPOSSESSED AND SHOP SOILED
T.V. SETS IN STOCK. ALSO LARGE
SELECTION OF TAPE RECORDERS
ALL GUARANTEED.

T.V. TUBES
RECLAIMED & GUARANTEED
12in., 16 ; 14in., 15 ; 15in., and 17in.,
27.10.0.

REBUILT TUBES with 6 mths. guaran-
tee, 10in., £8.10.0 ; 12in., £9 ; 14in.,
£11.10.0 ; 15in., £12.10.0 ; 17in., £14
Regret one month waiting list for
MAZDA 12" tubes.

BRAND NEW FULLY GUARANTEED
14in. M.W. 36-24 tubes, £16.10.0.
17in. M.W. 43-64 tubes, £17.10.0.
P.P. & Insurance on all tubes, 15/-.
Gram. Amplifier and 4-station radio
combined, £8.10.0.

RECORDING TAPE
Well-known. British made
Brand new. 1,200ft. lengths. List 35/-.
Our Price, 22/6 plus 1/6 P. & P.

RECORD CHANGERS--Brand New
Collaro R.C. 54-3 speed, £7.15.0
" R.C. 456 4-speed, £8.10.0
" R.C. 457 4-speed, £9. 0.0
B.S.R. Monarch 4-speed, £8.15.0.

STAR GALAXY
The world's most advanced 4 speed
auto-charger with ultra lightweight
pick-up. List price £12.16.3. Our price :
£9.15.0.

COLLARO JUNIOR
4 speed non-auto gram motor with
pick-up, £4.12.6.
B.S.R.
3 speed gram motor, non-auto with
pick-up, £3.19.0.
Post & Pkg. on record changers is 5/-.
Orders and Callers to :
NEW-MAX ELECTRONICS LTD.
220 Edgware Road, London, W.2.
PAD 5807

"VIEWMASTER"

Printed Circuit Converter
No Patterning
or Breakthrough

We can supply the complete
kit of parts including
valves, £5.0.0.

Send for detailed list
of this kit and others,
POST FREE.

Set of coils for conversion
of Viewmaster
receiver, £1.0.0.

PLEASE NOTE NEW ADDRESS

AUDIO LTD.
162 Gray's Inn Rd., London, W.C.1
Telephone TERMINUS 0228-9.

TELEVISION

RECEIVER SERVICING
Vol. 1
TIME-BASE CIRCUITS
By E. A. W. Spreadbury. 21s. Postage
1/-.

RAPID TV REPAIR. By G. W. Heath.
23s. Postage 9d.

IMPROVE YOUR RECEPTION.
By J. Cura & L. Stanley. 5s. Postage
4d.

CLOSED-CIRCUIT AND INDUS-
TRIAL TELEVISION. By E. M.
Noll. 34s. 6d. Postage 9d.

PRACTICAL TV AERIAL
MANUAL for BANDS 1 & 3. By
R. Laidlaw. 5s. Postage 6d.

A BEGINNER'S GUIDE TO
RADIO. By F. J. Camm. 7s. 6d.
Postage 6d.

TRANSISTOR TECHNIQUES. 12s.
Postage 8d.

RADIO VALVE DATA. Compiled
by "WW". 5s. Postage 8d.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS
of British and American Technical Books

19-23 PRAED STREET,
LONDON, W.2
Complete catalogue 6d.
Phone : PADdington 4185
Open 6 days 9-6 p.m.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 297 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

PYE CW17

The picture is perfect until the set has been in operation for 30/45 minutes, distortion then becomes noticeable at the top of the screen to a depth of 1in. approx. The scan lines appear to spread apart, and they seem to be "pairing," the picture content in this area stretches upwards, and the verticals, bend off to the left. I have the circuit sheets for the set.—H. Finlock (Hythe).

We suggest you replace the PCF80 situated behind the mains input plug and the PL83 mounted on the right side of the chassis (V25 and V21).

BUSH TUG12A

The picture has collapsed to about 2in. wide. Unlike the reader whose letter you answered in May '57 issue the picture does not fade and disappear on advancing the brilliance control. When the width control is advanced a vertical bright line appears down the centre of the 2in. strip. I have had all valves in the line timebase tested and are O.K. I have no service sheet and only a small Pifco voltmeter. Can you help me by suggesting what tests to make and possible faults. I have made spark tests with an insulated screwdriver on the tube anode, EY51 both ends and top cap of line output valve and get satisfactory sparks. Also the width control appears O.K.—A. F. Hartland (Dagenham).

We would advise you to replace the $2\mu\text{F}$ capacitor wired in series with the line scanning coils.

FERGUSON 308T

I get what seems like a bad mains hum and off it goes. Sometimes it can be got back by operating the fine tuner or by turning the channel selector. When this fails it has to be switched off for a time. I have changed the PCL83 and EF80 but it remains the same. The picture is not affected by this fault.—G. R. Gray (Ilford).

We would suggest you test the PCC84 and

PCF 80 valves in the tuner unit by substitution. We assume the PCL83 replaced is the left side upper sound A.F. and output valve. The right side PCL83 is, of course, the frame timebase part generator and output.

MURPHY TYPE V202C

During programmes the picture will suddenly disappear completely, leaving a thin line of very bright light across the centre of the screen. The fault can be remedied by quickly switching off and on again but the cure is not lasting. Could you please give me some indication of the cause of the trouble and possible means of correction?—R. J. Webb (E.12).

The frame timebase, which is your faulty section, is on the top left-hand wing as you look in from the back. The most likely components to check are the frame output valve 6P25, which is the largest valve on this deck, and the 6L1 frame oscillator, which is the uppermost valve on the rear edge. The coupling condenser gives a lot of trouble, too. This is a $.25\mu\text{F}$ paper condenser which shares the same clip as the electrolytic which decouples the section and is underneath the 6P25.

PYE CONTINENTAL

At certain intervals line hold completely fails and cannot be locked by manipulation of line hold control. I have changed V24 horizontal osc. PCF80 and this has effected a lock though the picture still tends to pull to the right-hand side, and the line hold control is at the extreme end of its travel. Any slight rotation from this position gives a picture break up. I would be glad of any suggestion you may be able to give that will enable a good solid lock to be obtained. W. H. Hill (Wednesfield).

Check the condition of the M3 metal rectifiers which are employed in the discriminator circuit associated with the line synchronising circuits. It should be noted that the line hold control should be adjusted critically until a setting is established when the picture jumps quickly into line sync on removing and replacing the aerial.

PYE VT4

Picture and sound very good, but have to keep switching off set due to crackling and sparks from a resistor in the lead attached to the side of the tube.—James Unwin (Manchester).

The $82\text{K}\Omega$ resistor (value not critical) should be inspected, replaced if necessary and the connections remade. It is possible that the sparking may be caused by an internal short in the tube but this is, of course, only a possibility.

FERGUSON MODEL 306T

For periods of two to three weeks I get a good picture from Granada Channel 10, then for a similar period I receive just a shadow or wavy lines. The aerial is standard for this area, being an eight-element array. My BBC aerial is a flat "H" for Channel 5.

My neighbour has the same set and aerial, he receives a perfect picture for 90 per cent. of his

viewing time and has never completely lost the picture as I have. I have tried my set on his aerial during a bad period and received a very good picture (our aerials are on the same chimney).

I have one lead from the aerial to my set, my neighbour has two, with a box on the window sill to change over. Can this be the reason? I see from your article, "I.T.A. in the West," duplexers can be used where signals are strong; as we are on the fringe would you advise changing over to a double feeder?—Mr. S. Clark (Birmingham).

If a good crossover filter is used, such as the Belling & Lee "Diplexer," the loss is so small that it can be ignored. It often happens that the signal conditions fluctuate differently in fringe areas from one aerial to the next, even though they may be closely spaced; this is particularly true so far as Band III is concerned. We would suggest that you move your aerial to another chimney stack or as far as possible away from your neighbour's array. Height of the aerial above ground must not be lost, however, as this is one of the most important factors in fringe areas.

MURPHY V178C

My tube went and I put another in (CRM123), but since putting the tube in I can only get a light on the screen in the centre.

I have put a new EL38, a new U281 and a new U25 in the line transformer. I can get sound and line whistle.

On the top of my line transformer there are five tappings, three on one side and two on the other, but on the side with three tappings I can only get a reading on the two end ones. There is nothing on the middle one. Does this indicate something wrong in the line transformer? I cannot get any scan lines or a raster.—John Balderstone (Burnley).

The fact that you have light on your screen indicates that the line timebase is working and producing E.H.T. The centre tap on the top of the transformer should show 86 ohms to the EL38 anode, the other two are the scancoil winding.

We suggest you look for your fault in the scancoil assembly or the wiring leading thereto.

FERGUSON 978T

I followed your advice and had valve ECL80 checked (dealer says its O.K.), and replaced 470K resistor. The trouble still persists only now when switched on, the picture is very tall (not touching sides of screen), it then closes down leaving a gap top and bottom $\frac{3}{4}$ in. and spreads out sideways filling the screen horizontally. The height and vertical hold controls still working together critically (height opened fully).

Should appreciate your further advice about this. I have checked the mains and the set is on the correct tapping.—E. Camball (Leamington Spa).

It is possible that the PZ30 rectifier is failing and this should be checked. A valve tester will not always reveal a faulty valve and substitution

is sometimes the only reliable check, this also applying to the ECL80 valves.

If the bottom cramping persists, check the linearity components associated with the frame output ECL80 and if necessary change the 150 K Ω resistor to 75 K or even 50 K Ω .

EKCOVISION T221

The symptoms, a very dim picture which turns negative as brilliance is advanced. A well focused raster is obtainable though dim. I tried a 13.3v. transformer with 20 per cent. boost on tube without any real difference. EHT as near as a screwdriver can tell seems to be well up, jumped almost $\frac{1}{2}$ in., and picture does not swell out. Tried moving ion trap magnet, disconnected A.G.C. lead and moving limiter plug without any difference. High reading on tube A1 but low on K and G. I have not got the service sheet yet.—C. F. Prior (Englefield Green).

The trouble you are having is undoubtedly your tube, which is one of those which cannot be improved by boosting. Before discarding it you may like to check the setting of your ion trap magnet, which may give you more light if moved from its present position.

We have in some cases slowly increased the heater voltage to as much as 30 volts in an attempt to burn off the contamination on the cathode. This is sometimes successful if done slowly with the set cold and a positive voltage applied to the grid (10v.), but there is a risk of blowing the filament so should not be tried until you are resigned to replacing your present tube.

FERGUSON 17in. TV MODEL 604T

Sound is normal. Picture rolls and vertical lock hold has little effect. Picture can be held by adjusting height control but is then two frames, and flickers. PCF80 sync separator and part frame oscillator and PCL83 part frame oscillator and frame output have been replaced with no effect.—L. V. Cahill (Co. Antrim).

Replace the OA71 frame sync shaper crystal diode which is probably defective. This is wired to pin 2 of the PCL83.

MURPHY CONSOLE

I have a Murphy built on the circular chassis principle (model number not known), and should be glad of your assistance.

At the present time the picture has good contrast but is very dull and will not fill the 12in. tube. Adjustment of the brightness brings up the raster with consequent loss of contrast and picture detail, and it is impossible to resolve a good black and white image at this degree of brightness. Only when the brightness is turned down can a very dull picture be obtained, with sufficient contrast.

I have recently replaced a faulty line control and also the line output valve (tested and found to have very little emission). I am of the opinion that the tube is running low, or failing altogether, and possibly you could help me by indicating what further tests I should make in order to

(Continued on page 297)

SETS & COMPONENTS

BUILD YOUR I.T.A. AERIAL from our machined parts. Supplied with folded dipole already made with insulator fitted, and cranked arm with clamp for any size of existing mast, or wall bracket. (State which when ordering.) Only a screwdriver needed to complete a rigid, waterproof array. 3 Element, 32/6; 5 Element, 42/6; 8 Element, 55/-; post free. Lashing Kit if required, 15/- extra. Special Offers—F.M. Indoor Dipole, complete on mast and base, 12/6. 4 B.A. Steel Screws, 1in. or 1 1/2in. long and 6 B.A. Steel Screws, 7/16in. long, all at 1/9 gross, post paid. Polythene Insulators for 1/2in. rods, 4/- each, post paid. Illustrated list of all Aerial Fittings, with Technical Data for Aerial Construction, all bands, 1/- P.O. All goods post free. Write for details. **SKYLINE WORKS**, Burnshall Rd., Coventry. (Tel.: 60418.)

TELEVISIONS, 9in. models, £7/10/-, 12in. models £13/10/-, 12in. 5-Channel models, £19/10/- each; all working; carriage paid. Send for list. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23. (FOR 5497.)

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Bullington Rd., Oxford.

GUARANTEED TELEVISION, 12in. 5-Channel models; first-class picture £25 each, carriage paid. **T H E GRAMOPHONE SHOP**, 19-21, Brockley Rise, London, S.E.23.

5-CHANNEL TELEVISIONS: 12in. screen Ferguson 988, Ekco 161, etc. £22 each. A good selection of 12in. T.V.s (London), 100% condition, from £12; 9in. from £7, also 12in. T.V.s, slight faults, from £5; 9in. from £3. **TYLER TELEVISION**, 63, Lee High Rd., Lewisham, S.E.13. (LEE 5979.)

TELEVISIONS, NEEDING ATTENTION, 9in.-10in. models £4/10/- each, 12in. models £6/6/- each, 15in. models and Philips's Projection models £11/10/- each; immediate despatch; carriage paid. **BARKERS**, 625, Brockley Road, S.E.4. (TID 375.)

TELEVISION TUBES. Good quality reclaimed and guaranteed for 6 months, as supplied to the trade throughout the British Isles, 14-15 10in. £5; 17in. £6; c.w.o. or proforma carriage, 15/-. (Smaller sizes available, but in short supply. **TELETUBES**, 34 and 18, Market Parade, Rye Lane, Peckham, S.E.15. (Tel.: New Cross 4551.)

12IN. T.V., out of order, £5; working O.K., £10; 12in., 5-channel, £15; 14in. from £18. Auto/Radiograms from £15. Callers only. **JOHN GILBERT TELEVISION** (SHE 8441). 1B, Shepherds Bush Rd., London, W.6.

TELEVISIONS, 12in. 5 channel £14; 14in., £18; 17in., £27; Faulty Sets from £2. **WILKINSON'S**, 146, Goldhawk Rd., W.12. (SHE 4379.) Callers only.

TELEVISIONS, all sizes and channels, at lowest prices ever! Also a few tubes. Trade supplied. **HYNES**, 9, Cumberland St., Victoria, S.W.1. (TAT 9140.)

DIPLOLE INSULATORS, 1in. boom, 1in. elements, suitable T.V. or F.M. Dipoles, 5/-. P.O. with order. **C. & H.**, 2a, Mona Street, Liverpool, 7.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

SIGNAL GENERATOR
Coverage 120 kc/s—84 Mc/s. A.F. modulation or unmod. R.F. Accuracy, ±2%. A.C. Mains 230/250 v. Complete £4-19-6. P.P. 4/6.
SIGNAL AND PATTERN GENERATOR. 7.6 Mc/s. 0-210 Mc/s in five bands (fundamentals). Accuracy +1%. A.C. Mains 200/250 v. Complete £6-19-6. P.Ins. 6/-.
The RADAR KILOVOLTAGE, Range 3-30 kV. Measures E.P. volts. £3-15-0. P.Ins. 2/6. The famous **BRAYHEAD** 12-Channel Turret Tuner. State set make and model No. £6-19-6. P.Ins. 2/6. Send 3d. stamps for lists.—**WESTWAY RADIO**, 5, Westward Way, Harrow, Middx.

MAKING YOUR OWN? Telescopes, Enlargers, Binoculars, Microscopes, Projectors, or, in fact, anything that needs lenses. Then get our booklets "How to Use ex-Gov. Lenses & Prisms," Nos. 1 & 2, price 2/6 ea. Also our stereo book, "3-D Without Viewers," price 7/6. Comprehensive list of lenses, optical, radio and scientific gear free for s.a.e. **H. W. ENGLISH**, Rayleigh Road, Hatton, Brentwood, Essex.

UNREPEATABLE OFFER—12in., 5 channel T.V., £15; 14in., £22; good working order. **C. EDWARDS**, 1070, Harrow Rd., London, N.W.10. (Phone: LADbroke 1734.)

"TELEVISIONS", 12in., 5 channel, tunable anywhere, models from £19/10/- each; carriage paid; satisfaction guaranteed. **RYAN ELECTRONICS**, 134, Acre Lane, Brixton, London, S.W.2. (BRI 4533.)

R.F. UNITS, Types 27 or 26, 22/-; 25 or 24, 9/-; brand new, with valves; post, 3/-. **E.W.S. CO.**, 69, Church Rd., Moseley, Birmingham.

NEW AND USED VALVES and Components at low prices; all guaranteed, s.a.e. lists. Service Sheets, s.a.e. enquiries. Reconditioned Radios and T.V.s from £2, for callers. **J. PALMER** (PT), 32, Neasden Lane, N.W.10.

ELECTRADIO—Dual Wave Coil 2/6 with circuit, ditto, plus Reaction 4/-. Tuning Condenser 3/10, Crystal Diode 1/6, tested 4 Transistor Set Circuit, 1/3. All Transistor Components stocked. Post free. 18, Broadlands Av., Keynsham, Somerset.

EFFICIENT AERIALS—Make sure with Aerial Current Meter, tests, compares. **HOBBLEY**, 109, The Drive, Wellingborough.

RECLAIMED TUBES, 12in., 14in., 17in., all at £5 each, guaranteed; 100 (5 channel) T.V., Ekco 161, Ferguson 988, £15 each. **C. EDWARDS**, 1070, Harrow Rd. (Phone: LADbroke 1734.)

TEST METER, scaled ohms, volts, m.a., 25/-; Xtal. Mic., 25/-; 4v., A.C. Radio Chassis, 45/-; all new. 28, Jewel Rd., London, E.17.

CATHODE RAY TUBES, used, but in good working order, and with 3 months' guarantee. All 12in. to 17in. Mazda, Mullard and Emtron types at £4/10/- each, plus 13/6 carriage. Orders and enquiries by letter only to: **BHP DISTRIBUTORS**, 379, Staines Road, Hounslow, Middlesex.

T.V. TUBES as new; revacuumed; all makes, 6 months' straight guarantee. 12 in. £25, 14in. £5/10/-, 17in. £7/10/-; carriage and insurance 12/6. **U.K. Free delivery Greater London VIDIO REPLACEMENT CO.** Hales St., Deptford High St., London, S.E.8. (Tideway 4506.)

TYPE 373 I.F. Amplifiers, with valves, brand new, 42/6. Meters: 4 x 4 x 2 1/2in. Read D.C. 1.5 and 3v. 6) m.A. and 5 k. ohms. Bakelite case, new, 12/6. Formers, 1in., 1 1/2in. dust-cores, can 2 x lin. dia., 6d. Test Sets: 744 with 9 valves, VCR 139a, 220-240v. power pack; (a): condition, 59/- (carr. 8/6). Indicator Units, new, with VCR97, 3/VR91, 2/CV18, 2/VR54, 24/- (carr. 7/-). Responder ZC931, 160-190 mc/s. new, with valves, 15/- (carr. 7/6). Brand new R.F. 26, 27, 25/- (post 3/-); RF25, 10/6; RF26, 27, good cond., 20/-. Metal Rectifiers: 240v. 100 mA., 4/-; 240v. 30 mA., 3/6; 1,000v. 30 mA., 7/6. Chokes, L.F. 10H, 120 mA., screened, 7/6; SH, 200 mA., 4/6. Transformers: 230v. in.; 6v. 7 times (total 15 A.), outputs, 25/-. Small, upright (a) 110-250v input; outputs 325v, 20 mA., and 6.3v. 1a., 9/6; (b) outputs 6.5v. at 1a., and 3a., 8/6. Input 200-250v. Outputs: 12v. 3a., and 5v. 3a., 12/6; 300-0-300v., 20) mA., and 4v. twice, 17/6. VHF Amplifier, valves 2/CV66, 1/VR136, with 50 c. power unit, 40/- (p.p. 3/6). LF Multi-choke: 12 H/45 mA., 60 H/10 mA., 35 H/20 mA., 12/6 (post 2/6 min.). Lists and enquiries, s.a.e., please. Terms: c.w.o.; postage extra; immediate despatch. **W. A. BENSON** (P/T), 136, Rathbone Rd., Liverpool, 15.

SITUATIONS VACANT

AEROPLANE AND ARMAMENT EXPERIMENTAL ESTABLISHMENT BOSCOMBE DOWN

requires
SKILLED men to serve as—
INSTRUMENT and ELECTRICAL CRAFTSMEN for laboratory and Aircraft installations work.
RADIO/RADAR and ELECTRONIC CRAFTSMEN for laboratory and Aircraft installations work.
AIRFRAME and ENGINE FITTERS for aircraft servicing and fitting of special equipment.
INSTRUMENT MAKERS and PRECISION MACHINISTS.
Rate of pay for 44 hour 5 day week 182/4 plus 10/- merit lead or 182/4 plus 38/- merit lead according to experience. Prospects of re-assessment of rate within three months, any increase backdated to date of entry. **MERIT LEAD CAN RISE TO 70/-**. **TWO WEEKS (88 hours) PAID ANNUAL LEAVE**. **PAID SICK LEAVE SCHEME**.
Apply giving details of apprenticeship and experience to Air Commodore (Civilian Administration Office), (PT), A. & A.E.E., Boscombe Down, Amesbury, Wiltshire.

AGENTS REQUIRED to sell I.T.V. Converters, Aerials, etc.; s.a.e. for details. **G. A. STRANGE**, N. Wraxall, Chippenham, Wilts.

WANTED

ALL TYPES OF VALVES REQUIRED for cash. State quantity and condition. **RADIO FACILITIES LTD.**, 38, Chalcoet Road, N.W.1 (PRIMrose 9090.)

NEW VALVES WANTED. EY51, EY86, PCF80, PL81, 524G, U25, or what have you? Prompt cash. **RHS**, 155, Swan Arcade, Bradford 1

SERVICE SHEETS

SERVICE MANUALS/Sheets Tel/Radio for hire. Sale and wanted. Mixed Manuals and Sheets, 12 for 10/-; s.a.e. enquiries. W. J. GILBERT (P.T.), 24, Frithville Gdns., London. W.12.

SERVICE SHEETS, Radio, T.V., 5,000 models. Lists 1/-. S.A.E. enquiries. TELRAY, 11, Maudland Bk., Preston.

FOR SALE

T.V. TUBES, used but guaranteed. 12in., £5/10/-; 14in., £5/10/-; 17in., £7/10/-; carriage and insurance 12/6 extra on all tubes. Turret Converters made by Brayhead, no soldering, uses adaptor, just plug in and convert your set. Models available for over 600 sets. Send for details: COTSWOLD ELECTRONIC SERVICE, 5, Windsor Rd., Tetbury, Glos.

SUPERTONIC SUNLAMPS, listed £7/10/-, 80/-. S.A.E. SCIENTIFIC PRODUCTS CO., Cleveleys, Lanes.

VALVE CARTONS, Miniatures 10/6. "GT's" 12/-. "G's" 14/- per 100 plus 2/- p. & p. RHS, 155, Swan Arcade, Bradford, 1, Lists free.

NEW SHOP IN LEEDS.—We are stocking Spares for Radios and T.V.s. New and surplus Valves. Bring this ad. for free valve testing this month. We have plenty of reduced Aerials and Converters in stock for callers only. T.V. SPARES, 41, Call Lane, Leeds, 1.

EDUCATIONAL

A.M.I.P.R.E.—For details of suitable study courses (only a limited number of students accepted) send for free Syllabus of Instructional Text, I.P.R.E. Conditions of membership booklet 1/-. "The Practical Radio Engineer," journal, sample copy, 2/3; 6,000 alignment peaks for Superhets, 6/-. All post free from SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

EXAMINATION.

Write for FREE 20-page GUIDE and Test, stating age of child to: THE REGISTRAR (Dept. M7), Mercer's Correspondence College, 69, Wimpole St., London, W.1.

FREE! Brochure giving details of Home Study Training in Radio, Television and all branches of Electronics. Courses for the Hobby Enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B. and other Professional examinations. Train with college operated by Britain's largest Electronics organisation. Moderate fees. Write to E.M.I. INSTITUTES, Dept. PT23, London, W.4.

LEARN IT as you do it—we provide practical equipment combined with instruction in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to E.M.I. INSTITUTES, Dept. PT47, London, W.4.

BUILD YOUR OWN T/V and learn about its operation, maintenance and servicing. Qualified engineer-tutor available while you are learning and building. Free Brochure from E.M.I. INSTITUTES, Dept. PT58, London, W.4. (Associated with H.M.V.)

COVENTRY RADIO

Component Specialists since 1925

We have now trebled the size of our premises in order to supply a larger range of Components, Amplifiers and Hi-Fi Equipment

Send your enquiries to:
189-191 Dunstable Road,
Luton, Beds.
New Telephone No.:
LUTON 7388-9

Air-spaced Coaxial Cable, 75/80 ohms, new. 9d. per yd., 70/- per 100 yds. Meters, 500 microamps. F.S.D., marked 15/600 v. 2in. dial. 15/-. 12in. Plessey P.M. Speaker, new. 27/6. Television Aerials, Band III Channels 9/9/10, 3-element, 25/6; 5-element, 38/6; 8-element, 58/6; Band I all channels. "H." 7/6; "X." 7/6. Combined Aerials from 25/-. Why not send S.A.E. with your aerial enquiry and we will reply by return. We only stock the well-known guaranteed made aerials, thereby giving better value for money. Pifco All-in-one Radiometer, A.C. D.C. ranges 0-6-240 volts, 0-30 m/a, also continuity and valve filament tester, 32/6. F.M. Feeder Cable, new, standard 300 ohms. 6d. per yd. Volume Controls, special offer 1 meg. S/P. Long spindle, 3/-. Volume Controls, D/P 5/6; L/S 3/6; Pre-set, 4/-. R.M.1. 4/6; R.M.2. 5/6; R.M.3. 7/6; R.M.4. 10/6; R.M.5. 25/-. Ion-Trap Magnets, 5/-. Chrome Car Aerial, 37/6. Fidelity 4-speed Autochange Amplified Record Players, new and guaranteed. 12 gns. Pifco Electrical Blankets, new, Single, 67/6; Double, 87/6.

GUARANTEED VALVES


OZ4	5/-	6K8	9/-	6B6	19/6	PCC84	
1A5	3/-	6Q7	9/-	EB91	5/-		12/6
1LN5	3/-	6AT6	8/-	EL84	10/6	UBC41	8/6
2X2	2/-	6AQ5	8/6	ECL80		UCH42	9/6
3D6	2/6	6SL7	8/-			UL41	10/-
4D1	3/6	6A7	10/-	EY51	12/6	W81	18/6
5Z4	9/6	6BW6	8/-	PY82	8/-	W75	10/6
5U4	9/-	6BG6G				80	12/6
6U7	6/6		19/6	PY80	9/-	ECC81	9/6

MAIL ORDER ONLY.
NO CALLERS.

Terms: C.W.O. or C.O.D. Minlmum C.O.D. charge 3/6. Postage and packing per valve 8d. Under £2, 1/9; £4, 2/3. All Aerials 2/6 carriage.

ELECTRO-SERVICES & Co.
221 BATTERSEA PARK ROAD,
LONDON, S.W.11. MAG 8155

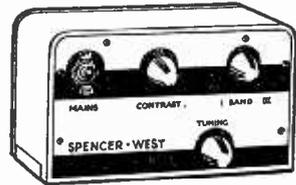A SPENCER-WEST BAND III CONVERTER FOR £6.5 0



The Type 80 with printed circuits, panel controls for Band switch and fine tuning and a performance which ensures enthusiastic satisfaction. Handsomely designed and finished to stand on your receiver with its self-contained power supply it just plugs straight in.

Full descriptive leaflet on request. Available from all good dealers or post free direct from the manufacturers if any difficulty.

SPENCER-WEST LTD.,
Quay Works, Great Yarmouth,
Norfolk.

Phones: Works 4794; Sales 3009
Grams: Spencer-West, Great Yarmouth.

FIRST-CLASS TELEVISION and RADIO COURSES . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

- The New Free Guide contains 132
- pages of information of the greatest
- importance to those seeking such
- success compelling qualifications as
- A.M.Brit.I.R.E., City and Guilds
- Final Radio, P.M.G. Radio
- Amateurs' Exams., Gen. Cert.
- of Educ., London B.Sc. (Eng.),
- A.M.I.P.E., A.M.I.Mech.E.,
- Draughtsmanship (all branches),
- etc., together with particulars of
- our remarkable Guarantee of

SUCCESS OR NO FEE

- Write now for your copy of this
- invaluable publication. It may well
- prove to be the turning point in your
- career.

FOUNDED 1885—OVER
.....150,000 SUCCESSES.....

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN,
LONDON, E.C.1.

restore the picture to its original brilliance. The tube is an Ediswan and is about five years old.—G. Alan Holt (Sheffield).

Your set is the V210C, and apart from your tube being low emission we suggest you have a faulty metal rectifier type RM4. This should deliver about 230v. D.C. from the same A.C. input and give an H.T. rail voltage of 205v.

The heater voltage to your tube can be increased by removing the wire feeding mains to the 2 volt transformer from the 200 volt tag of the voltage panel and connecting it to the rotating contact in the centre (assuming that your mains is 220v. or more).

K.B. MK100

The channel switch has become faulty, the picture flickers on and off, appearing like a loose connection as the switch is altered. I understand the trouble is caused by a loose spring in the channel switch. Could I make the adjustment so as to avoid a long wait for workshop service?—E. Sowerbutts (Bristol).

The tuner springs may be retensioned quite simply by slightly (and carefully) increasing the bow. This of course necessitates the removal of the bottom cover of the tuner unit. To increase the bow, insert a thin screwdriver blade between the end of the spring and the wall of the unit and very carefully apply pressure.

EKCO T310

A line-fault has appeared about one-third from the bottom of the picture, as though two lines had merged together and fluctuates up and down that third of picture.—John Tait (Glasgow).

Your line bunching is due to B-K oscillations in the frame output stage. This can normally be cured by changing the valve, which is a 30PL1 located just below the scancoils against the seam which joins the timebase chassis to the I.F. strip. There is another 30PL1 working as sound output, and the two can be interchanged as an initial step in checking your set's performance.

ULTRA W721

When the set is first switched on the picture is good and bright. After about 30 minutes the picture goes dull and flat. Advancing the brightness control produces an upward flare on all the light spots on the screen. I have tried turning the aerial to reduce the flare without success.

Also a bright horizontal line appears on the bottom of the screen when the set has been on for 15 minutes or so.

I have a "Pifco" radiometer available and have very little experience of TV servicing but can follow a circuit diagram.—J. A. Moran (Morecambe).

From your description we would say that you have a low emission cathode ray tube, although it is unusual for this sort of tube to start bright and go dull. We suggest you measure the filament

volts, which should be 2v., both when the set is working right and when it has gone faulty, as you may have a dry joint in the wiring which reduces the supply when warm. The horizontal line at the bottom of the screen can usually be cured by changing the UL46 frame output valve which is located just behind the line output stage cover.

PHILIPS 1100U

Would you please tell me what is wrong as the picture keeps on rolling? It does not matter which EC180 valve I change (which I have about half a dozen), the rolling still persists, with about three pictures with flyback lines in the frame. It makes no difference which way I turn the frame hold.—D. J. Jones (Glam.).

You should replace the 2.2 megohm resistor wired in series with the hold control. This is located behind the socket on the side wall of the timebase chassis. If the picture tends to be flat, check also the 5.6 megohm associated with the vision limiter control.

EKCO MODEL T284

I should be pleased if you could give me any details, etc., to assist me in cleaning the tube of my set?—G. P. Elsworth (Carlisle).

First remove the chassis by disconnecting the leads to scancoils, tube base, loudspeaker assembly, and E.H.T. condenser, removing circlip and metal shields on knobs, plastic panel covering three side knobs and two screws holding rear flange of chassis to the wood. Chassis then withdraws backwards.

Lay cabinet on its face and undo four long 2BA nuts at the tube corners (mind you do not break the metrosil). Tube cradle then withdraws by a series of angular movements (lift, slide down, tilt out from top, slide up, rest on top of fixing bolts, tilt sideways, lift clear. Undo 4 X 4BA bolts holding glass and mask to tube cradle and lift tube cradle clear. (Clean and reassemble in reverse order, carefully re-fitting plastic strip around the mask join to exclude all air.)

K.B. MV30

No line osc. whistle so no EHT. Voltage tests O.K., also valve O.K. (12AU7). Could the fault be in sync sep. 12AX7?—R. Graham (Millom).

The sync separator would not be responsible. You should have the 6U4GT valve tested and if this is in order the 6CD6G. We are not sure what you mean by "voltage tests O.K.," and would like a more detailed report before offering further advice.

QUERIES COUPON

This coupon is available until JANUARY 21st, 1958, and must accompany all Queries sent in accord with the notice on page 293.

PRACTICAL TELEVISION, JANUARY, 1958

JASON FM SWITCHED TUNERS

All BBC Programmes at the turn of a switch **MERCURY KIT**. Includes front-end unit already built and aligned. **£9.19.0** Post Free.

Credit Terms: Deposit **£1.10.0** and seven monthly payments of **£1.7.0**.

Instruction Book 2/3 post free. Included in kit. Fully detailed price list free.

PREFECT TUNER. A ready-built unit. Less power supply. **£15.12.6**. Credit Terms: Deposit **£2.4.6** and seven monthly payments of **£2.2.0**. Illustrated leaflet free.

Both these tuners incorporate a good A.F.C. system which ensures freedom from drift.

NEW AVO MULTIMINOR

A brand new test instrument at a very attractive price. A.C. and D.C. Volts. D.C. Current. Two ohms ranges. Movement is 100 microamps (10,000 ohms per volt). **£9.10.0**. Credit Terms: Deposit **£1.8.0** and seven monthly payments of **£1.6.0**. Illustrated leaflet available.

WATTS RADIO (Mail Orders), LTD.,
54, Church Street, Weybridge, Surrey.

Telephone: Weybridge 4556.

PLEASE NOTE: Post orders only to this address.

St. Mary's Electronics

(Tel.: AMBassador 9795)

18, PRAED STREET, LONDON, W.2

T/V TUBES

	12 in.	14 in.	17 in.
MULLARD ...	£5	£6	£7
MAZDA ...	£5	£6	£7
EMITRON ...	£5	£6	£7

12" MAZDA TUBES 30 DAYS' DELIVERY.

ALL OTHER TYPES EX-STOCK.

TERMS: 3 MONTHS' GUARANTEE. P.P. INS. 10/- C.W.O.

REBUILT TUBES

	12 in.	14 in.	17 in.
MAZDA ...	£9	£11	£12.10.0
MULLARD ...	£9	£11	£12.10.0

ALL PRICES INC. P.P. & INS.

ALL REBUILT TUBES ARE GUARANTEED
SIX MONTHS

PLEASE SEND S.A.E. FOR ANY ENQUIRIES



QUALITY TELEVISION COMPONENTS

SCANNING COILS, 6/10 kV. and 13/15 kV., R.F., E.H.T. UNITS, E.H.T. and OUTPUT TRANSFORMERS, LINE FLYBACK E.H.T. UNITS.

COIL KITS FOR "P.T." BAND III CONVERTERS

Write for illustrated list (Publication 75)

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

TECHNICAL TRADING CO.

TV TUBES. 12 MONTH Guarantee. 12in. (MW 3L-74 Type), **£4.10.0**. 14in. Rectangular **£4.15**. Carr. & ins. 15/-. **WIDE ANGLE FOCUS MAGNETS** with centring. 8/6. Double magnet. 12/6.

13 CHANNEL CONVERTORS

For T.R.F. or Superhet Receivers. Famous Make. 3 position Switch, Fine Tuner, and 9 Quick Set Trimmers. Give any 3 Channels. T.R.F. Band I, Superhet Band III, Output direct to Aerial Socket. Beautiful Bakelite Case, with PCC 84, PCF 80. **£3.15.0**.

AS ABOVE but with built-in power pack, listed **£10.17.6**. continuous tuning channel. 6/3, hammered gold finish, no alterations just plug in. **£7.10.0**.

ATTRACTIVE 14in. TABLE TV CABINETS. Size 17in. x 16in. x 16in. mask, glass, 7 x 4 front speaker baffle. 29/-, post 6/-.

S.A.E. FREE LIST 400 AMAZING SNIPS

Including EF50, 2 6; EF91, 7 6; plus 100 other valves, 250 mA. T.V.. L.F. chokes, 4/6; 100+200 mfd. 275 v.w.. 5/-, etc.

10,000 OTHER BARGAINS AND TELEVISION SETS AT:—

50/352 FRATTON ROAD, PORTSMOUTH

MAKE SOUND JOINTS SIMPLY BY USING Multicore

ERSIN MULTICORE

Contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON

5/-

HANDYMAN'S
CARTON

Suitable for 200 6d. average joints.



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

ARAX MULTICORE

FOR METAL FABRICATION

(Not wire-to-tag joints)

Contains 2 cores of Arax flux. Flux residue is easily removed with water.

SIZE 8 CARTON

5/-

Handymans Carton 6d.



HOME CONSTRUCTORS
2/3 PACK

In addition to the well-known Home Constructors Pack (containing 19ft. of 18 s.w.g. 60/40 alloy) a similar pack is now available containing 40ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits.



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruded flex 3/8 each



MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3639)

BAND III CONVERTOR

for ANY SET in ANY AREA

This unit has been widely used since I.T.A. Transmissions began to convert all types of sets, Superhet and T.R.F., to receive on Band III.

Unlike many other convertors this unit is small enough to be fitted inside your cabinet, enabling the job to appear finished and perfectly safe for all to use.

The wiring is simple to follow, and alignment is not difficult.

- ★ IT will convert any set, any age, T.R.F. or Superhet.
- ★ IT includes station switching.
- ★ IT provides pre-set contrast balancing.
- ★ IT uses only one aerial input for both bands
- ★ IT provides manual tuning on Band III.
- ★ IT is totally screened.
- ★ IT completely rejects unwanted signals.
- ★ IT requires no additional power supply where either 6.3 or 3 amp. heater line is available.

CONVERTOR wired and aligned with fitting instructions	£3 10 6
KIT complete in every detail, less knobs	£2 10 6
KNOBS each	1 6
CIRCUIT and instructions in detail (free with kit)	1 6
KITS made up by customers checked and aligned, including post	12 6

When ordering please state present B.B.C. Station and I.T.A. Orders over £2 post free.

C. & G. KITS

285, LOWER ADDISCOMBE ROAD, ADDISCOMBE, CROYDON, SURREY

Phone: ADDISCOMBE 5262

ARTHURS HAVE IT!

LARGE STOCKS OF VALVES, METERS, Avo, Advance, Taylor and Philips Service Pattern Generators. Oscilloscopes, Cossor and Philips. AMPLIFIERS, Leak, Trix & Quad. GRAM UNITS, Garrard & Collaro.

LOUDSPEAKERS, Goodmans, Wharfedale, WB, Tannoy and leading makes. PICK-UPS and STYLI of most makes. TAPE RECORDERS, Grundig, Philips, Truvox, Playtime & Ferragraph.

LATEST VALVE MANUALS

Mullard 10/6, Osram Revised 7/6, Brimar No. 7 6/-

POST AND PACKING 9d. EACH.

CASH WITH ORDER.

Arthurs

Est. 1919

PROPS: ARTHUR GRAY, LTD.

OUR ONLY ADDRESS: Gray House,

150-152 Charing Cross Road, London, W.C.2

TEmpLe Bar 5833'4 and 4765

TELEGRAMS—TELEGRAY, WESTCENT, LONDON.

CABLES—TELEGRAY, LONDON.



FOR VALVES GUARANTEED ALL TESTED BEFORE DESPATCH

6Z1	5/8	6AK5	6/8	6K7A	5/-	6Q7	9/-	6U1	10/6	6U142	10/-
6AR	3/6	6AL5	6/6	6K7C	7/-	6U2	9/-	6U11	13/6	6U181	9/-
6AS6T	6/-	6AM5	9/-	6K7M	6/9	6U4	8/-	6U15	13/6	6U180	9/6
6AT	12/6	6AV5	7/6	6K8A	9/-	6U5	11/6	6U12	10/6	6U182	13/6
6B2	9/6	6AV6	8/6	6K8T	9/6	6U7	8/6	6U16	9/9	6U188	8/6
6B6T	10/6	6AV5	10/6	6K8T	9/6	6U8	8/6	6U17	9/6	6U190	8/6
6D1	6/6	6B4	5/-	6L7	7/6	6U9	2/9	6U18	9/6	6U191	9/6
6D5	10/6	6B4	4/-	6L8	11/6	6U10	5/6	6U19	12/6	6U192	10/6
6E1	10/6	6B4	7/6	6L7	7/6	6U11	12/6	6U20	12/6	6U193	10/6
6E2	7/6	6B5	8/-	6L8	13/6	6U12	11/6	6U21	12/6	6U194	10/6
6E3	7/6	6B5	10/6	6L9	9/6	6U13	11/6	6U22	12/6	6U195	10/6
6E4	7/6	6B5	11/6	6L9	9/6	6U14	11/6	6U23	12/6	6U196	10/6
6E5	8/-	6B5	12/6	6L9	9/6	6U15	11/6	6U24	12/6	6U197	10/6
6E6	8/-	6B5	13/6	6L9	9/6	6U16	11/6	6U25	12/6	6U198	10/6
6E7	8/-	6B5	14/6	6L9	9/6	6U17	11/6	6U26	12/6	6U199	10/6
6E89	8/-	6B5	96/6	6L9	9/6	6U99	11/6	6U108	12/6	6U281	10/6
6E90	8/-	6B5	97/6								

EDDY'S (NOTTINGHAM) LTD. (DEPT.)

This Month's Special Offers


TRIPLETONE AMPLIFIERS. List price £6/19/6. Our Price £5/19/6, plus 2/6 postage, etc. 200-250 v. A.C. 4 watts, matched output for 2-3 ohms. Size only 8 in. x 4 in. x 4 1/2 in. high. Valves—6S7GT, 6V6GT, 6XSGT. Special feature of treble, middle and bass controls. **ALL NEW AND GUARANTEED.**

SINGLE PIECE THROAT MIKES. 1/- each, post. etc., 3d. each. Could be used for electrifying musical instruments.

MIDGET BATTERY ELIMINATORS. To convert all low consumption portables for mains operation. Mains input 200/240 v. A.C. H.T. output 85 v. 10 m.a., L.T. output 1.3 v. 125 m.a. Size 3.7 in. x 2.5 in. Actually smaller than H.T. battery alone. Special price of 55/-, plus 2/6 post, etc. **NEW AND GUARANTEED.**

Any parcel insured against damage in transit 6d. extra		SURPLUS, NEW AND GUARANTEED VALVES		Post, etc., 6d. per valve extra. Over £2 post free					
All tested before dispatch									
DAF96	0/6	EF89	9/11	UF41	8/-	3V4	8/-	10F9	11/6
DF96	0/6	EF91	6/11	UL41	9/11	6Y9GT	7/6	12A17	7/6
DK96	0/6	EL32	3/11	UCH42	8/-	6Z1G	9/6	12K7G	7/6
DL96	0/6	EL84	9/-	UL84	11/6	6B8C	3/11	12Q7G	7/6
DM70	7/11	EY51	11/6	U25	13/6	6BA6	6/6	14S7	13/6
DH76	7/6	EZ89	8/-	UY41	7/6	6B36	7/-	35L6CT	9/-
EABC80	1/2	EZ81	9/6	U76	7/6	6F1	13/6	25Z4G	9/-
FB91	7/6	GZ32	12/6	W73	7/6	6F15	14/9	35A5	11/6
ECC83	8/6	MU14	8/11	1C5G	10/6	6C9	12/6	35W4	7/6
ECC84	10/-	PCC84	8/-	1H5G	10/6	6K7C	2/11	35Z4G	7/6
ECC85	9/6	PLC83	11/6	1N5G	10/6	6L8C	7/11		
ECH35	8/6		13/11	1R5	7/6	6Q7G	8/3	907	1/6
ECL80		PY80	8/3	1S5	7/6	6Q7G	8/3	907	6/6
EF41	8/11	PY81	8/6	1T4	7/-		8/11	657	3/11
EF80	8/3	PY31	11/6	3Q1	9/-	6V6GT	5/11	856	2/6
EF86	12/6	PL36	17/6	3S4	9/6		8/-	10T1	14/11
								958	2/11

AMAZING OFFER

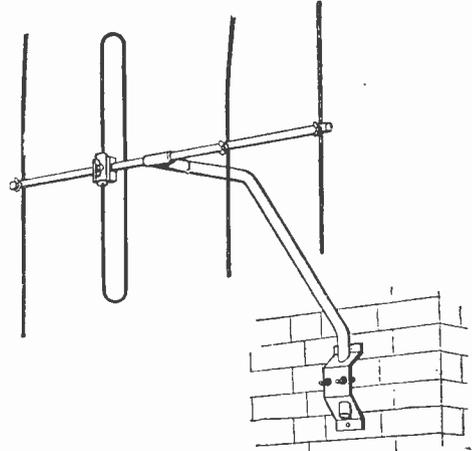

This powerful 4-element, pre-assembled, wide spaced Band III beam Aerial by a leading manufacturer. Supplied complete with cranked pole and wall fixing brackets, can also be loft mounted. Listed at 55/6.

Our price, Brand New, in maker's sealed carton, 39/6. 4-element Aerials, array only, for mounting on 1 1/2 in. diameter mast, 25/-.
Cellular polythene Co-axial Cable at 8d. per yard supplied if required.

Terms: Cash with Order or C.O.D. Carriage 2/6 extra. Mail order only.

G. C. EQUIPMENT CO., LTD.
2, PARK ROW, LEEDS, 1

172, ALFRETON RD., NOTTINGHAM

OPPORTUNITIES IN TELEVISION

148 pages

Free!

Television offers unlimited scope to the technically qualified. Details of the easiest way to study for A.M., Brit. I.R.E., R.T.E.B. Cert., City and Guilds, Television, Television Servicing, Sound Film Projection, Radio Diploma Courses, etc., are given in our 148-page Handbook "ENGINEERING OPPORTUNITIES" which also explains the benefits of our Appointment Dept.

We Guarantee "NO PASS—NO FEE"

If you are earning less than £20 a week you must read this enlightening book.

Send for your copy NOW—FREE and without obligation.

WRITE TO-DAY!

British Institute of Engineering Technology
237, Colsons House,
29-31, Wright's Lane, **BIET**
Kensington, W.8.

TRANSFORMERS?

CONTACT **Forrest** FIRST!

Rewinding and manufacture of all types for Television Radio and Electronic Application.

FORREST (TRANSFORMERS) LTD.,
Shirley, Solihull, Warwickshire.
Phone: SH1. 2483. Est. 34 years.

RADIO AND TELEVISION COMPONENTS

All parts in stock for:
Viewmaster, Soundmaster, Telexing, etc.
Easy Terms available.
3d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO.
FINSTHWAYTE, NEWBY BRIDGE,
CLVERSTON, LANCs.

CSMR CONVERTERS

ALL CHANNELS
Simple, efficient for all TV (including TRF). Guaranteed no break-through of Band I or re-radiation. Approx. 3 hrs. to build. Will convert any Band II channel to any Band I channel. A.C. or A.C./D.C. Kit. £3.5.0. Ready wired. £4.0.0. Post free. Terms: C.W.O. Post orders only.
THE ELECTRONIC SUPPLY CO.
29 Leigh Rd., Highbury, London, N.5

NEW SHOP IN LEEDS 1

Components and Valves for Radios and T.V.s. Hi-Fi equipment.

T. V. SPARES
41 Call Lane, Leeds, 1

TEST GEAR GOING CHEAP!

ITEMS FROM 32/6

Don't wait—Send stamp for lists—NOW

RADIO MAIL (Dept. W)
Raleigh Mews, Raleigh St., Nottingham

ALUMINIUM, LIGHT ALLOYS, BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP WIRE, ANGLE, CHANNEL, TEE

3000 STANDARD STOCK SIZES

H. ROLLET & CO., LTD.

6, CHESHAM PLACE, LONDON, S.W.1.
SLOane 3463

Works:

36, ROSEBERRY AVE., LONDON, E.C.1.

Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small"

TELEVISION COMPONENT SERVICE

Replacement components available for the popular home constructor designs. Catalogue available on request.

J. T. FILMER 82, Dartford Road, Dartford, Kent.

Tel.: Dartford 4057

TELEVISION TUBES

MULLARD	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0
COSSOR	12in. £6.10.0	14in. £6.10.0	17in. £8.10.0
EMITRON	12in. £6.10.0	14in. £7.0.0	17in. £8.10.0

MULLARD. 12in. now 6 weeks delivery. All other types ex-stock.

MONTHLY CLEARANCE REDUCTIONS

MAZDA	14in. £5.10.0	17in. £7.0.0
CATHODEON	14in. £6.0.0	17in. £7.0.0

All Tubes plus 12/6 carriage and insurance.

SIX MONTHS' GUARANTEE


Terms to the Trade.

RE-VIEW (LONDON) LTD.

81, HIGH STREET . . . MERTON S.W.19

Telephone : CHERRYWOOD 3255

T/V INTERFERENCE BANISHED IN SECONDS!

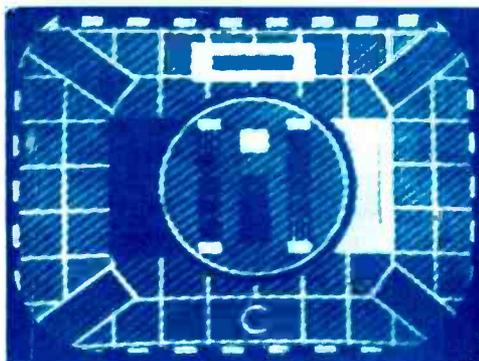

with *Labgear* PRINTED
CIRCUIT FILTERS



PATTERNS LIKE THAT ILLUSTRATED ABOVE RUIN T/V RECEPTION, BUT THANKS TO THE NEW LABGEAR PRINTED CIRCUIT FILTERS CAN USUALLY BE CLEARED INSTANTLY. SEND FOR EXPLANATORY LEAFLET WHICH TELLS YOU WHICH OF OUR 3 MODELS YOU SHOULD EMPLOY. **MONEY BACK OFFER.** Any Labgear filter purchased as a result of this advertisement will be accepted back for cash refund if returned in new condition within 14 days of delivery. This offer is valid for 2 months only, so write to-day for further details to :

Labgear Ltd., **WILLOW PLACE, CAMBRIDGE.**
'Phone 2494/5. 'Grams. Labgear, Cambridge.

PERFORMANCE ASSURANCE WITH



COSSOR

PRINTED CIRCUITS

AN INSTRUMENT RANGE IN KIT FORM

- Q.** *Why has Cossor Instruments decided upon this innovation?*
- A.** To make available a range of first-class measuring instruments at a considerable saving in cost to the Buyer.
- Q.** *Are Kit instruments inferior in performance to their Factory-built equivalents?*
- A.** Certainly not. If assembled and wired exactly in accordance with the Manual of Instructions.
- Q.** *A certain skill must, surely, be required to build these instruments?*
- A.** None beyond the ability to use a small soldering iron.
- Q.** *How can a performance specification be maintained without setting up with test equipment?*
- A.** Largely by the use of PRINTED CIRCUITS which allow no interference with the layout of critical parts of the circuit.
- Q.** *How many Kit instruments are at present available?*
- A.** Three. Two Oscilloscopes, a Single-Beam and a Double-Beam, and a Valve Voltmeter. Others will follow shortly.
- Q.** *Could I have more information on these interesting instruments?*
- A.** With the greatest of pleasure. Just write to:

*Model 1071K Double Beam Kit Oscilloscope.
List Price £69-0-0.
Hire Purchase Facilities.
Trade terms on application*

COSSOR INSTRUMENTS LIMITED

The Instrument Company of the Cossor Group

COSSOR HOUSE • HIGHBURY GROVE • LONDON, N.5.

Telephone: CANonbury 1234 (33 lines) Telegrams: Cossor, "Norphone," London Cables: Cossor, London