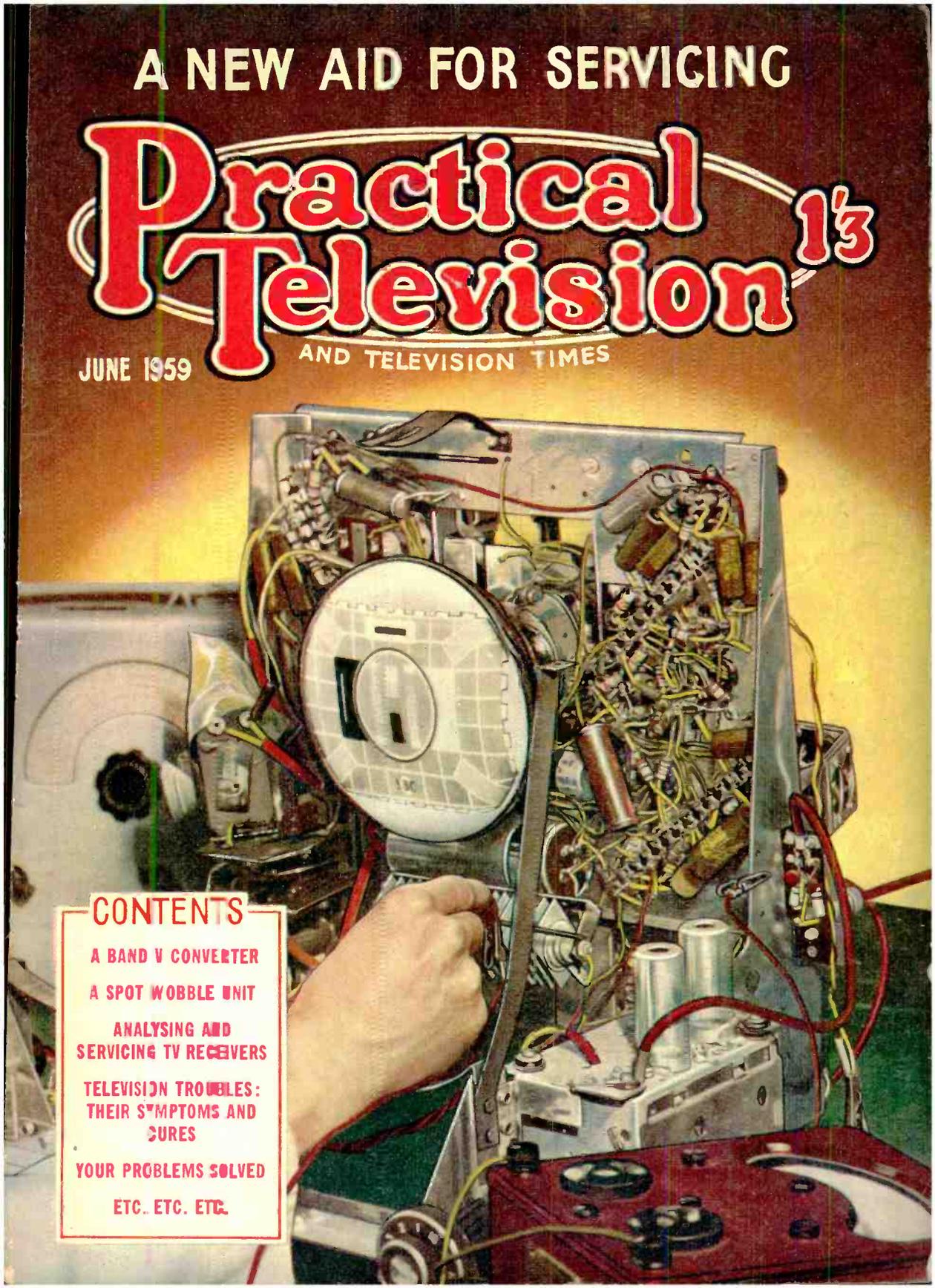


A NEW AID FOR SERVICING

# Practical Television '13

JUNE 1959

AND TELEVISION TIMES



## CONTENTS

A BAND V CONVERTER

A SPOT WOBBLE UNIT

ANALYSING AND  
SERVICING TV RECEIVERS

TELEVISION TROUBLES:  
THEIR SYMPTOMS AND  
CURES

YOUR PROBLEMS SOLVED

ETC. ETC. ETC.

## ● ADVISORY SERVICE

We offer a complete before and after sales service. Our advice is ALWAYS available and freely given, BUYING or NOT! Whether expert or novice, let our extensive experience ensure your success.

## ● AERIALS

An even wider range. We select the ever-popular I.T.V. add-ons to illustrate our bargains.  
**5 ELEMENT.** Complete with universal clamp and stand-off arm. Still unbeatable, 39/6. Also at 45/-.  
**8 ELEMENT.** As above. 51/6. Also at 62/6.  
**Easifix.** All aerials pre-assembled and collapsed for transit.  
**Easimad.** All single aerials can be modified to "double" arrays if desired.  
**Takiteats!** DO be careful on the roof. DON'T wear crêpe soles in wet weather. (Better still, wait for good weather.)  
**NOTE.**—Efficiency and gain of aerials depends on number of elements, spacing, siting, etc., and hardly varies with PRICE which concerns finish, long-term durability and patent assembly methods. DO write us for aerial advice if in doubt.

## ● CABLE & ACCESSORIES

**CO-AXIAL.** Hi-grade, low loss, suitable all normal purposes. Expanded polythene type. 8d. per yd. any length.  
**SEMI-AIRSPACED.** A "must" for long runs in fringe areas ("Don't spoil the ship," etc.) 1/6 per yd. any length.  
**DIPLEXERS** (Junction boxes). Indoor type, 10/3. Outdoor type, 13/-.  
**IF-IN-DOUBT.** Use a separate downlead for I.T.V. with a skirting board "diplexer" if necessary.

## ● I.T.V. CONVERTERS

**WE ARE CONVERSION SPECIALISTS.** Our supplementary advice ensures success. Many appreciative letters from all parts.  
 Still available: CYLDON, BRAYHEAD and CHANNEL converters and turret-tuners at VERY FAVOURABLE PRICES. Write for advice and quote, giving make, model no. and local channels.

## BARGAIN OF THE MONTH

**VALVES:** Types PCC84, PCF80, ECC84, ECF80. Per pair, new, boxed, Mullard or Brimar. £1 post free.

## ● C.R.T. "RE-NU" KITS

Give that ageing tube a new lease of life! Reactivate as per our simple advice. Booster available but not always needed. 18 months of good extra viewing quite common. Complete kit, with reactivation advice and multi-purpose transformer, leads, etc.. 37/6, pkg./postage 2/6.  
**BETTER THAN BRUTE-FORCE BOOSTING!**

## ● RADIO KITS (F.M./V.H.F.)

Our DO-IT-YOURSELF radio. Again, after many tests, we have selected the famous Cossor 701K. Everything except the cabinet for a 6-valve V.H.F./F.M. radio. Pre-aligned R.F. and I.F. stages. (Expensive test gear not required).  
 10in. Elliptical loudspeaker.  
 Illustrated construction manual plus our Supplementary Advice. £15.15.0 tax paid.

## ● VALVE KITS FOR YOUR TV

Save hours of fault-finding. Clear 90% faults. One off, each type. Guaranteed valves, tested prior to despatch and very carefully packed. Complete with TV Fault-finding Guide and advice on your TV. Standard Kits: £5.0.0 post free. (If non-standard, favourable quote by return.) Why pay repair bills? (State make and model number.)

## ● TERMS OF BUSINESS

Cash with order or C.O.D. (2/6 extra).  
 Extended credit on more expensive items. Write to us in confidence.  
 Packing and carriage 1/6. Above £5 free, except aerials (5eL, 2/6; 8eL, 3/6; Others, 5/-).  
 If in doubt or if needing advice WRITE US FIRST.

# WILSON

48, CATHAY, BRISTOL, 1  
 TEL. 57819 or 26242

# ADCOLA

(Regd. Trade Mark)

## SOLDERING EQUIPMENT

THE INSTRUMENTS CREATED FOR THE DISCRIMINATING USER.

British & Foreign Pats., Regd. Designs, etc.

### ILLUSTRATED

Protective Shield  
(Cat. No. 68)

Instrument  $\frac{1}{8}$ " Bit  
(Cat. No. 70)

The ideal combination for transistor and other intricate work.

Apply direct for catalogues:—

**ADCOLA PRODUCTS LTD.,**  
**GAUDEN RD.,**  
**CLAPHAM HIGH ST.,**  
**LONDON, S.W.4.**

Telephones  
 MACaulay 4272 and 3101



# TELEVISION TUBES REBUILT

12 MONTHS' GUARANTEE

12"	-	-	-	-	£6. 0.0
14"	-	-	-	-	£6. 10.0
17"	-	-	-	-	£7. 10.0

Carriage and insurance 12/6 extra.

Customers are requested to send their old tubes for rebuilding. We offer 48 hr. service. In the case of 12" MAZDA tubes please confirm before sending.

## MARSHALLS for TELEVISION

131 St. Ann's Road, Tottenham,  
 London, N.15.

Telephone: STAmford Hill 3267

# BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090.

**EXPRESS SERVICE! C.O.D. ORDERS RECEIVED BY 3.30 P.M., EITHER BY LETTER, PHONE OR WIRE, DESPATCHED THE SAME AFTERNOON, ALL ORDERS RECEIVED BY FIRST POST DESPATCHED SAME DAY.**


**ANY ORDER UP TO £10 INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6d. EXTRA. ORDERS OVER £10 INSURED FREE.**

0B2	17/6	6C6	6/6	6X4	7/6	19H1	10/6	7475	7/6	DL66	15/6	EL32	5/6	KTZ41	8/6	PY81	9/6	UCC84	20/6
OZ4	6/6	6C8	12/6	6X5GT	6/6	20D1	15/3	9002	5/6	DL68	15/6	EL33	12/6	KTZ63	10/6	PY82	9/6	UCC85	10/6
IA3	3/6	6C9	12/6	6/30L2	10/6	20F2	26/6	9006	6/6	DL92	7/6	EL34	17/6	L63	6/6	PY83	9/6	UCF80	22/6
IA5	6/6	6C10	12/6	7A7	12/6	20L1	26/6	AC/PEN	5/6	DL94	9/6	EL38	26/8	LN152	12/6	PZ30	20/6	UCH21	23/6
IA7GT	22/6	6CD6G	30/6	7B6	19/3	20P1	26/6	or 7 pin	23/4	DL96	10/6	EL41	11/6	LZ319	9/6	QP21	7/6	UCH42	41/6
IC5	12/6	6CH6	12/6	7B7	8/6	20P3	23/3	AC2PEN		DL510	10/6	EL42	11/6	MH4	7/6	QP25	15/6	UCL81	11/6
ID5	16/8	6D3	20/6	7C5	8/6	20P4	26/6		23/3	DM70	8/6	EL81	15/6	MHL4	7/6	QS150/15		UCL82	15/6
ID6	10/6	6D6	6/6	7C6	8/6	20P5	23/3	AC2PEN/		EAS50	2/6	EL84	10/6	MHLD6	12/6		10/6	UCL83	24/8
IH5GT	11/6	6E5	12/6	7D5	23/4	25A6G	19/3	DD	26/8	EAT76	9/6	EL91	5/6	ML4	12/6	R12	10/6	UF41	9/6
IL4	6/6	6F1	26/8	7H7	8/6	25L6GT	10/6	AC4PEN		EABC80	9/6	EL95	10/6	ML6	6/6	R18	17/6	UF42	18/8
ILD5	5/6	6F6G	7/6	7R7	12/6	25Y5	10/6		26/8	EAC91	7/6	EM34	10/6	MPT4	5/6	R19	20/6	UF80	10/6
ILN5	5/6	6F6GTM	8/6	757	10/6	25Y5G	10/6	ACSPEN		EAF42	10/6	EM71	23/4	7 pin	23/4	SD6	12/6	UF85	10/6
IN5GT	11/6	6F8	12/6	7V7	8/6	25Z5	10/6		23/4	EB34	2/6	EM80	10/6	MU14	10/6	SP4(7)	15/6	UF86	23/4
IR5	8/6	6F11	17/4	7Y4	8/6	25Z4G	10/6	AC6PEN	7/6	EB41	8/6	EM81	10/6	MX40	26/8	SP41	3/6	UF69	10/6
IS5	8/6	6F12	7/6	8D2	3/6	25Z6G	10/6	AC/HL/		EB91	6/6	EN31	37/6	N37	20/6	SP42	12/6	UL41	10/6
IT4	6/6	6F13	12/6	8D3	7/6	25Z6GT		DDD	15/6	EB33	7/6	EY51	10/6	N78	20/6	SP61	3/6	UL44	26/8
IU5	10/6	6F14	26/8	9D2	4/6		16/7	AC/P4	8/6	EB41	10/6	EY83	16/8	N108	18/8	SU25	26/8	UL46	15/6
2A7	10/6	6F15	15/4	9BW6	5/4	27SU	19/11	AC/TP	33/4	EB31	14/6	EY86	14/6	N308	20/8	SU61	10/6	UL84	11/6
2C26	4/6	6F16	9/6	10C1	15/6	28D7	7/6	AC/VP1		EBF80	10/6	EZ35	6/6	N339	26/8	T41	23/4	UM4	17/4
2D13C	7/6	6F17	12/6	10C2	26/8	30C1	9/6		15/6	EBF89	9/6	EZ40	8/6	OA70	5/6	TDD4	24/8	UR16	16/8
2P	26/8	6F32	10/6	10D2	12/6	30F5	8/6	AC/VP2		EBL21	23/4	EZ41	10/6	OA71/81	6/6	TH4B	26/8	UU6	20/6
2X2	4/6	6F33	7/6	10F1	19/6	30FL1	10/6		23/4	EBL31	23/4	EZ80	9/6	OC72	30/6	TH41	26/8	UU8	26/8
3A4	7/6	6G6	6/6	10F9	11/6	30L1	9/6	ATP4	5/6	EC52	5/6	EZ81	9/6	P61	3/6	TH233	33/4	UY1N	16/8
3A5	12/6	6HG6GT	3/6	10LD3	10/6	30P12	8/6	AZ1	16/8	EC54	6/6	FC2A	24/8	PABC80		TH2321	20/6	UY21	16/8
3B7	12/6	6HG6TM	3/6	10LD11	16/8	30P16	8/6	AZ31	10/6	EC70	12/6	FC4	26/8			TP22	15/6	UY41	8/6
3D6	5/6	6J5G	5/6	10D13	17/6	30PL1	12/6	AZ14	14/6	EC31	15/6	FC13	26/8	PCC84	9/6	TP25	19/6	UY85	10/6
3Q4	7/6	6J5GTG	5/6	10P14	19/4	31	7/6	B36	24/8	EC32	10/6	FC13C	26/8	PCC85	12/6	TP2620	33/4	VMP4G	15/6
3Q5GT	9/6	6J5GTM	6/6	11D3	24/8	33A/158M		BL63	7/6	EC33	8/6	FW4/500		PCC89	30/6	TR86F	20/6	VP2(7)	12/6
3S4	7/6	6J6	5/6	12A6	6/6			CI	12/6	EC34	24/8		10/6	PCF80	9/6	U12/14	12/6	VP4(7)	15/6
3V4	9/6	6J7G	6/6	12AC6	5/4	35/51	12/6	CIC	12/6	EC35	8/6	FW4/800		PCF82	12/6	U16	12/6	VP4B	23/4
5R4Y	17/6	6J7GT	10/6	12AD6	17/4	35A5	19/3	CB11	26/8	EC40	23/4		10/6	PCL82	12/6	U18/20	10/6	VP13C	7/6
5U4G	8/6	6K6GT	8/6	12AE6	14/6	35L6GT	9/6	CB131	23/4	EC81	8/6	GZ30	10/6	PCL83	12/6	U22	8/6	VP23	6/6
5V4G	11/6	6K7G	5/6	12AH7	8/6	35W4	8/6	CCH35	23/4	EC82	7/6	GZ32	12/6	PCL84	22/6	U24	30/6	VP41	6/6
5X4G	12/6	6K7GT	6/6	12AH8	10/6	35Z3	10/6	CK506	6/6	EC83	10/6	GZ34	14/6	PEN4DD		U25	18/6	VR105/30	
5Y3G	8/6	6K3G	8/6	12AT6	10/6	35Z4	7/6	CL33	19/4	EC84	10/6	H30	5/6		26/8	U26	12/6		9/6
5Y3GT	8/6	6K8GT/G		12AT7	8/6	35Z5GT	9/6	CV63	10/6	EC85	9/6	H63	12/6	PEN25	20/6	U31	10/6	VR150/30	
5Y4	12/6		12/6	12AU6	23/4	41MTL	8/6	CV85	12/6	EC91	5/6	HABC80		PEN36C		U33	26/8		9/6
5Z3	12/6	6K25	20/6	12AU7	7/6	42	23/3	CV271	10/6	ECF80	13/6		13/6		10/6	U35	26/8	VT61A	5/6
5Z4G	10/6	6L1	23/4	12AX7	10/6	43	23/3	CV428	30/6	ECF82	13/6	HL133DD		PEN40DD		U37	26/8	VT501	5/6
5Z4GT	12/6	6L6G	9/6	12BA6	9/6	50C5	12/6	CY1	16/8	EC83	26/8		12/6		25/6	U43	10/6	W61M	26/8
6A7	26/8	6L7GT	12/6	12BE6	10/6	50CD6G		CY31	16/8	ECH21	23/4	HL23	10/6	PEN44		U45	10/6	W76	7/6
6A8	10/6	6L18	13/6	12BH7	21/4		29/10	D1	3/6	ECH35	9/6	HL23DD			26/8	U50	8/6	W81M	6/6
6A87	8/6	6L19	23/4	12C8	15/6	50L6GT	9/6	D15	10/6	ECH42	9/6		17/4	PEN45	19/6	U52	8/6	W107	12/6
6A88	12/6	6LD20	16/6	12E1	30/6	53KU	16/6	D42	10/6	ECH81	9/6	HL41	12/6	PEN45DD		U56	7/6	W729	18/8
6AC7	6/6	6N7	8/6	12J5GT	4/6	72	4/6	D63	5/6	ECL80	12/6	HL41DD			26/8	U78	7/6	X31	26/8
6AG5	6/6	6P1	19/4	12J7GT	10/6	75	24/7	D77	6/6	ECL82	12/6		19/4	PEN46	7/6	U107	16/8	X41	26/8
6AK5	8/6	6P25	12/6	12K5	18/6	77	8/6	DAC32	11/6	ECL83	24/8	HL42DD		PEN383	23/4	U191	16/8	X42	26/8
6AL5	6/6	6P28	26/8	12K7GT	7/6	78	8/6	DAF91	8/6	EF9	23/4		19/4	PEN45DD		U251	15/6	X61	12/6
6AM6	7/6	6Q7G	10/6	12K8GT		80	9/6	DAF96	10/6	EF22	14/6	HN309	24/8		33/4	U281	20/6	X61M	26/8
6AQ5	8/6	6Q7GT	11/6		14/6	83	15/6	DD41	14/6	EF36	6/6	HVR2	20/6	PEN/DD		U282	22/4	X63	10/6
6AT6	8/6	6R7G	10/6	12Q7GT	7/6	83V	12/6	DDT4	24/8	EF37A	8/6	HVR2A	6/6	4020	33/4	U301	23/4	X65	12/6
6AU6	10/6	6SA7GT	8/6	12SA7	8/6	85A2	15/6	DF33	11/6	EF39	6/6	KF35	8/6	PL33	19/4	U329	15/6	X66	12/6
6B7	10/6	6S5C	10/6	12S5C	8/6	150B2	15/6	DF91	6/6	EF40	15/6	KL32	22/6	PL36	15/6	U339	16/8	X76M	14/6
6B8G	4/6	6S7GT	8/6	12S7G	8/6	185B7	33/2	DF96	10/6	EF41	9/6	KL35	8/6	PL38	26/8	U403	16/8	X78	21/4
6B8GTM	5/6	6S7H	8/6	12SH7	8/6	185B7A	33/2	DH63	10/6	EF42	12/6	KLL32	24/8	PL81	16/6	U404	10/6	X79	21/4
6BA6	7/6	6S17	8/6	12S17	8/6	203THA		DH63(M)		EF50(A)	7/6	KT2	5/6	PL82	8/6	U401	30/6	X109	17/4
6BE6	7/6	6S7GT	8/6	12S7K	8/6		26/6		17/6	EF50(E)	5/6	KT33C	10/6	PL83	11/6	U4020	16/8	XD(1.5)	6/6
6BG6G	23/4	6S17GT	8/6	12S7Q	12/6	220TH	24/7	DH76	7/6	EF54	7/6	KT36	30/6	PM2B	12/6	UABC80		XFG1	18/6
6BH6	9/6	6S7GT	7/6	12S7R	8/6	30S	10/6	DH77	8/6	EF73	10/6	KT41	26/8	PM12	6/6		10/6	XH(1.5)	6/6
6B16	7/6	6S7GT	8/6	12Y4	10/6	402PEN		DH107	14/6	EF80	8/6	KT44	15/6	PM12M	6/6	UAF42	10/6	XSG(1.5)	6/6
6BR7	23/4	6S7T	8/6	1457	23/3		23/3	DK32	22/6	EF85	7/6	KT61	12/6	PM24M	21/4	UB41	12/6	Y63	7/6
6BW6	9/6	6U4GT	12/6	15D1	26/8	807	7/6	DK40	21/4	EF86	14/6	KT63	7/6	PX4	33/4	UBC41	10/6	Z63	10/6
6BW7	8/6	6U5G	7/6	18	23/4	956	3/6	DK91	8/6	EF89	10/6	KT66	15/6	PX25	60/6	UBC81	14/6	Z66	20/6
6BX6	8/6	6U7G	8/6	19AQ5	11/6	1821	16/7	DK92	10/6	EF91	7/6	KTW61	8/6	PY31	16/8	UBF80	9/6	Z77	7/6
6C4	7/6	6V6G	7/6	19BG6G	5/6	1821	12/6	DK96	10/6	EF92	5/6	KTW62	8/6	PY32	20/6	UBF89	10/6	Z719	8/6
6C5G	6/6	6V6GTG	8/6		23/4	7193	5/6	DL33	9/6	EK32	8/6	KTW63	8/6	PY80	8/6	UBL21	23/4	Z729	14/6

## NEW METAL RECTIFIERS—FULLY GUARANTEED


DRM-1B	15/4	RM-2	9/6	WX3	3/6	14A100	27/6	14R4	1-2-8-2	19/6	16R2	2-1-8-1	8/6
DRM-2B	16/2	RM-4	9/6	WX4	3/6	14A124	28/6	14R4	1-2-8-3	23/6	18R4	1-1-8-1	4/6
DRM-3B	23/3	RM-3	18/6	WX6	3/6	14A163	38/6	14R4	2-1-16-1	21/6	18R4	1-1-16-1	6/6
LMW	22/6	RM-5	24/6	14A86	18/6	14B130	35/6	16R4	1-1-16-1	8/6	18R4	1-2-8-1	11/6
RM-O	7/11	W4	3/6	14A97	25/6	14B261	11/6						

## DUKE & CO. FOR REAL VALUE

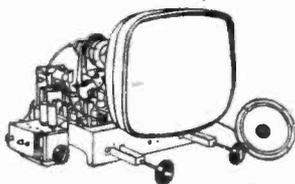
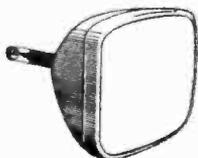
### 17" T/V CHASSIS TUBE and SPEAKER 16 GNS.

17in. Rectangular Tube on modified chassis. Supplied as single channel chassis covering B.B.C. channels 1-5, or, incorporating Turret Tuner, which can be added as an extra, at our special price to chassis purchasers of 50/-, giving choice of any 2 channels (B.B.C. & I.T.A.). Extra channels can be supplied at 7/6 each. Chassis size 12 in. x 14½ in. x 11in. less valves. Similar chassis are used by well known companies because of their stability and reliability. With Tube and Speaker (less valves) 16 guineas. Complete and working with valves and Turret Tuner 24 guineas. 12 months guarantee on the Tubes. 3 months guarantee on the valves and chassis. Ins. carr. (incl. Tube), 25/-.



### REPLACEMENT REBUILT T/V TUBES

**£8/10/-**


12 MONTHS FULL  
GUARANTEE

All sizes and types except 10 in. Rebuilt to the high standard required to give long picture life, quality, and value. Carriage and insurance 15/6.

We are also able to offer attractive terms on the above as follows: 8/6 initial payment, and 19 weekly repayments of 8/6.
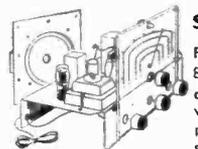
### ★ EXPRESS DESPATCH SERVICE ★

Please phone to confirm Tube in stock. Send Telegraph Money Order. Tube despatched Passenger Train same day. This service only available with remittance by a Telegraph Money Order.



### SUPER CHASSIS, 79/6

Five-valve superhet chassis including Bin. P.M. Speaker and valves. Four control knobs (tone, volume, tuning w/change switch). Four w/bands with position for gram. p.u. and extension speaker. A.C. Ins. carr. 5/6.

### SOUND/VISION & I.F. STRIP, 5/9

Salvaged. Complete sound & vision strip. 8 valve holders. Less valves. I.F.s 16-19.5 Mc/s. Size 8½ in. x 4½ in. x 4½ in. Drawings free with order. P. & P. 2/6.

### TIMEBASE 4/9

Containing scanning coils, focus unit, line transformer, etc., less valves. Drawings free with order. P. & P. 2/6.

### POWER PACK & AMPLIFIER, 9/9

Output stage PEN45, O.P. trans choke. Smoothed H.T. 325 volt at 250 m.a. 4 v. at 5 a.m.p., 6.3 v. at 5 amp. 4 v. at 5 amp. centre tapped. Valve base for rectifier. Octal or 4 pin. Output is taken from standard plugs. Less valves. Ins. carr. 5/6.

### SOLO SOLDERING TOOL, 12/6

110 v., 6 v., or 12 v. (special adaptor for 200/240 v. 10/- extra). Automatic solder feed including a 20 ft. reel or Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 2/9.



### ★ RECORD PLAYER CABINET RP.3 79/6

A delightful-looking cabinet 14½ in. x 17 in. x 8½ in. in 2-tone leatherette. Will take a B.S.R. Monarch 4-speed autochanger and 6½ in. round speaker. Carr. & Ins. 4/6.



### B.S.R. MONARCH UA8 4-SPEED AUTOCHANGER

Incorporating auto and manual control complete with turnover crystal p.u. and sapphire stylus, P/P & Ins. 5/6. **£6/19/6**

LATEST B.S.R. MONARCH UA12 4-SPEED MIXER, P. & P. 5/6. **£8/9/6**

T.U.9. B.S.R. 4-SPEED SINGLE PLAYER, P. & P. 5/6. **£4/9/6**

B.S.R. MONARCH 4-SPEED STEREO AUTOCHANGER, P. & P. 5/6. **£9/19/6**

COLLARO CONQUEST 4-SPEED AUTOCHANGERS, P. & P. 5/6. **£6/19/6**

COLLARO CONQUEST STEREO II GNS. AUTOCHANGERS, P. & P. 5/6.

### ★ AMPLIFIERS ★


12 MONTHS GUARANTEE

### STEREOPHONIC AMPLIFIER, £7/19/6

Beautifully made for portable stereophonic record players. Latest design with printed circuit. Dimensions 3 in. x 5½ in. x 9½ in. A.C. only. Mains isolated. Twin amplifiers each side giving 3-4 watts output. Incorporating ECL82 triode-pentode valve. Full tone, volume and balance controls. Complete and ready to fit. Knobs 3/6 per set extra. P/P & Ins. 4/6.
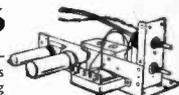
### PORTABLE AMPLIFIER 79/6 MARK D.2.

Printed circuit. Latest design. Dimensions 7 in. x 2½ in. x 5 in. A.C. only. Mains isolated 3-4 watts output. Incorporating the latest ECL82 triode-pentode output valve giving higher undistorted output. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.




### ★ IDEAL FOR STEREOPHONIC SOUND ★

8in. P.M. SPEAKER, 8/9. With O.P. trans. fitted, 10/-.  
6½ in. P.M. SPEAKER, 12/6. 4in. x 7in. Elliptical speakers, 19/6.  
8in. x 5in. ELLIPTICAL SPEAKERS, 19/6. P. & P. 2/9.
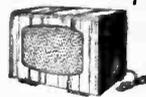
### EXTENSION SPEAKERS,

Polished oak cabinet of attractive appearance. Fitted with 8in. P.M. Speaker, W.B. or Goodmans, of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins. Carr. 3/6. **19/9**



## DUKE & CO.

(DEPT. E.6),

621/3, ROMFORD RD., MANOR PARK,  
E.12. Tel.: ILF. 6001/3.

TERMS AVAILABLE. Send for FREE Catalogue.

# RADIO SUPPLY CO.

(LEEDS) LTD., Dept. N, 5/7 COUNTY ARCADE, BRIGGATE, LEEDS, 1

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/6 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 6 p.m. Wednesdays until 1 p.m. S.A.E. with enquiries, please. Full list 6d. Trade supplied.

## R.S.C. TRANSFORMERS

Fully Guaranteed

Interleaved and Impregnated  
Primaries 200-230-250 v. 50 c/s screened  
**TOP SHROUDED DROP THROUGH**  
260-0-260 v 70 ma. 6.3 v 2 a, 5 v 2 a ... 16/9  
350-0-350 v 80 ma. 6.3 v 2 a, 5 v 2 a ... 18/9  
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9  
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9  
350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a ... 29/9

**FULLY SHROUDED UPRIGHT**  
250-0-250 v 60 ma. 6.3 v 2 a, 5 v 2 a ... 17/9  
Midget type 21-3in  
250-0-250 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9  
300-0-300 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9  
350-0-350 v 100 ma. 6.3 v 4 a, 5 v 3 a ... 23/9  
350-0-350 v 150 ma. 6.3 v 4 a, 5 v 3 a ... 33/9  
425-0-425 v 200 ma. 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a ... 49/9

**FILAMENT TRANSFORMERS**  
All with 200-250 v 50 c/s Primaries : 6.3 v 1.5 a, 5/9 : 6.3 v 2 a, 7/6 : 0.4-6.3 v 2 a, 7/9 : 12 v 1 a, 7/11 : 5.3 v 3 a, 8/11 : 6.3 v 6 a, 17/8.

**CHARGER TRANSFORMERS**  
200-250 v 0-0-15 v 1 a, 11/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 5 a, 19/9; 0-9-15 v 6 a, 23/9.

**OUTPUT TRANSFORMERS**  
Standard Pentode 5,000 to 3 ohms ... 4/9  
Small Pentode 5,000 to 3 ohms ... 3/9  
Standard Pentode, 78,000 to 3 ohms ... 4/9  
Standard Pentode 10,000 to 3 ohms ... 4/9  
Push-Pull EL34 to 3 or 15 ohms ... 16/9  
Push-Pull 10-12 watts 6V6 to 3 or 15 ohms ... 15/9  
Push-Pull 10-12 watts 6V6 to 3, 5, 8 or 15 ohms ... 16/9

**SMOOTHING CHOKES**  
100 ma 10 h 250 ohms ... 8/9  
80 ma 10 h 450 ohms ... 5/6  
60 ma 10 h 400 ohms ... 4/11

**SELENIUM METAL RECTIFIERS**  
250 v 250 ma. 11/9; 250 v 80 ma. 7/9; 250 v 50 ma. 4/11; 120 v 40 ma. 3/9; 24 v 2 a, 11/9; 6.12 v 1 a F.W., 3/11; 6.12 v 2 a F.W., 6/11; 6.12 v 3 a, 9/9; 6.12 v 4 a, 12/3; 6.12 v 5 a, 14/6; 6.12 v 6 a F.W., 15/6; 6.12 v 10 a, 25/9; 6.12 v 15 a, 35/9. Heavy duty type 24 v 15 amp F.W. Bridge with large square alum. coolers, 27/9 each!

**CO-AXIAL CABLE** lin.  
75 ohms 14/3s  
Twin-screened Feeder ... 11d. yd.  
**STANDARD JACK PLUGS**, with 4ft. screened lead, 1/11.  
**STANDARD JACK SOCKETS** (moulded), 2/9.

**5-CORED FLEX.** Rubber insulated 14/3s, 1/3 yd.; 50/- 50 yds.; £4 100 yds.

**BATTERY SET CONVERTER KIT**  
All parts for converting any normal type of Battery Receiver to A.C. mains 200-250v 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma, fully smoothed and fully smoothed L.T. of 2 v at 0.4 a to 1 a. Price including circuit, 49/9. Or ready for use, 9/9 extra.

**ALL DRY RECEIVER BATTERY ELIMINATOR KIT.**—All parts for the construction of a unit (metal-case 5 1/4-1 1/2 in.) to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or ready for use, 46/9.

**D.C. SUPPLY KIT.**—Suitable for Electric Trains. Consists of mains trans. 200-250 v 50 c/s, A.C. 12 v 1 a Selenium F.W. Bridge Rectifier, 2 Fuseholders, 2 Fuses, Change Direction Switch, Variable Speed Regulator. Partially drilled Steel Case, and Circuit. 29/9

**EX-GOVT. CASES.** Well ventilated, black crackle finished, undrilled cover. Size 14 x 10 x 8 1/2 in. high. IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER. Only 9/9, plus 2/9 postage.

**TELEVISION RECTIFIERS**  
250 v 200 ma. Size 3 x 1 1/2 in. Brand New, 6/9.

**HI-FI 8-WATT AMPLIFIER.** Special purchase due to cancelled export orders. £4 19/9. Carr. 7/6. For 200-250 v A.C. A limited number is available of these highly sensitive push/pull units guaranteed brand new and in working order and with separately controlled inputs for mike and gram., etc. etc. Latest B.V.A. valves. Excellent performance.

## EX-GOVT. MAINS TRANSFORMERS

All 200-250 v 50 c/s input.  
Removed from New ex-Govt. units. 22/9  
275-0-275 v 100 ma. 6.3 v 7 a, 5 v 2 a ... 11/9  
250-0-250 v 80 ma. 12.6 v, 1.5 a, 5 v 2 a ... 11/9  
250-0-250 v 150 ma. 5 v 3 a ... 18/9  
350-0-350 v 160 ma. 6.3 v 5 a, 5 v 3 a ... 27/9  
400-0-400 v 250 ma. 5 v 2 a, 5 v 2 a ... 18/9  
450-0-450 v 250 ma. 6.3 v 3 a, 6.3 v 1 a, 5 v 6 a ... 49/9  
12.5 v 3 a, 5 v 3 a ... 12/9

**EX-GOVT. SMOOTHING CHOKES**—  
60 ma 5-10 h 250 ohms ... 2/11  
80 ma 10 h 150 ohms ... 6/9  
100 ma 5 h 100 ohms Tropicalised ... 3/11  
100 ma 8-10 h 100 ohms Parmeko ... 6/9  
120 ma 12 h 100 ohms ... 8/9  
150 ma 6-10 h 150 ohms Trop. ... 6/9  
150 ma 10 h 150 ohms ... 9/9  
200 ma 3-5 h 100 ohms Parmeko ... 7/9  
250 ma 20 h 200 ohms ... 19/9  
£3683 NITW. Comprising chassis with strong cover 17 x 10 x 8 ins. Over 60 resistors (many high stability) and condensers, w/holders, I.F.T.'s, co-ax sockets., controls, fuse-holders, tabboards, etc., etc. Excep. value at only 12/6 carr. paid.

## ELECTROLYTICS (NEW)

Tubular		Can type	
8 mfd 450 v	1/9	8-8 mfd 450 v	2/11
16 mfd 450 v	2/9	8-16 mfd 450 v	3/11
8-16 mfd 500 v	4/11	16-16 mfd 450 v	4/11
25 mfd 25 v	1/3	32-32 mfd 350 v	4/9
50 mfd 12 v	1/3	32-32 mfd 450 v	5/9
100 mfd 50 v	1/9	150 mfd 450 v	5/9
100 mfd 25 v	2/3	100-100 mfd 350v	5/9
3,000 mfd 6 v	3/9	100-200 mfd 275 v	6/11
6,000 mfd 6 v	3/11		

## BATTERY CHARGERS

For 200/250 v 50 c/s A.C. mains. 12 months guarantee. Attractive, well ventilated, hammer finished cases, 6 v or 12 v 4 amp, with meter and variable charge rate selector, as illustrated. 75/- carr. 4/6  
6 v or 12 v 1 amp type. Also suitable for electric train power supply. Only 27/9. post 2/9.



## NEW STOCK 24 HOUR SERVICE

# VALVES ALL GUARANTEED

Postage:—Up to 3 6d.; 4-6 9d. Upwards of 6 see our normal terms.

IAB6	6/9	6D2	6/9	7AN7	7/9	54KU	11/9	EB34	2/3	EY86	13/9	PL38	16/9	UAF42	10/6
1A14	6/9	8D6	7/9	757	9/9	62DDT	8/9	EB41	7/6	EZ80	8/9	PL81	13/9	UB41	11/9
1C1EM	6/9	8P1	11/9	7Y4	7/9	62V	7/9	EB91	5/9	EZ81	8/11	PL82	9/9	UBC41	9/9
1C3	6/9	8P12	6/9	8D3	6/9	63ME	8/9	EBC33	6/9	EZ90	6/9	PL83	10/9	UBF80	9/6
1T4	5/11	8P13	11/9	8D2	3/3	141TH	8/9	EBC41	9/9	FW4/500	9/9	PY31	11/9	UCH85	10/6
1AH5	6/9	8P11	11/9	807	7/6	17DDP	8/9	EBC90	11/9	GZ33	11/9	PY80	11/9	UCH42	10/9
1FD9	6/9	8P15	11/9	9D2	3/9	311SU	8/9	EBCF80	9/9	GZ32	10/9	PY81	8/9	UCL82	14/9
1FD1	6/9	8S5	4/9	954	1/9	451PT	7/9	EBCF89	9/6	GZ34	13/9	PY82	8/9	UF42	8/9
1F1	6/9	835G	4/9	10C1	13/9	ACFEN	5/9	EBC81	7/9	HL41DD		PY83	8/9	UF89	9/9
1F2	6/9	838	4/9	10F1	17/9	AC HL	8/9	ECC72	7/9	KT44	14/9	PZ30	16/9	UL41	9/9
1F1	6/9	837L	5/9	10LD3	7/9	B36	8/9	ECC83	9/9	KT45	9/9	SP42	11/9	UL46	14/9
1P10	6/9	8K7G	4/9	10LD12	15/9	B152	8/9	ECC84	9/9	KT61	11/9	SP61	2/9	U8785	10/6
1S5	7/9	8K7MET	5/9	10LD14	15/9	B308	8/9	ECC85	9/6	KT62	9/9	SP64	8/9	VU120A	3/9
1R5	7/9	8K9T	8/9	10P18	9/9	B310	8/9	ECC81	8/9	KT63	9/9	SU61	9/9	VS110	3/9
1R4	6/9	8L1	8/9	12A6	8/9	B322	8/9	ECC80	12/9	KT64	9/9	T41	16/9	WT19	9/9
1A4	6/9	6LD3	9/9	12AT7	7/9	B719	8/9	ECCF82	12/9	KT65	9/9	U22	7/9	W150	9/9
1C4	6/9	6LD12	9/9	12AU6	7/9	CCH35	7/9	ECL80	10/9	KTW63	9/9	U27	7/9	WD706	9/9
1B4	7/3	6LD20	8/9	12AU7	6/9	D1	2/3	ECL82	11/9	KTZ41	7/9	U24	7/9	WD142	9/9
1V4	6/9	6L12	11/9	12AX7	9/9	DAF61	7/9	EF39	5/9	L63	4/9	U25	7/9	X17	9/9
1U4	6/9	6L13	11/9	12SN7GT	9/9	DAF96	9/9	EF41	8/11	LH152	9/9	U31	9/9	X78	10/6
1Y3G	7/9	6L19	11/9	15A6	6/9	DF96	9/9	EF45	4/9	MH4	9/9	U35	9/9	XZ1	9/9
1Z4G	9/9	6Q7G	9/9	16A5	6/9	DF92	9/9	EF80	7/9	LN14	9/9	U43	9/9	Y63	5/9
1AC7	5/9	6P2B	9/9	16A8	7/9	H77	7/9	EF85	7/3	MU14	9/9	U46	9/9	XZ7	9/9
1AM6	6/9	6N6	8/9	16AR	7/9	D152	8/9	EF86	16/9	N19	9/9	U50	8/9	Y63	5/9
1AL5	6/9	6N8	8/9	17Z3	9/9	DD41	8/9	EF89	9/9	N37	18/9	U78	9/9	Z63	8/9
1AT6	7/9	6SN7GT	9/9	8/9	8/9	DH19	8/9	EF91	9/9	N152	9/9	U151	9/9	Z66	8/9
1AQ5	7/9	6U5C	6/9	19X3	9/9	DH719	8/9	EF93	9/9	N154	9/9	U152	9/9	Z77	7/9
1AQ8	7/9	6U4CT	12/9	20L1	9/9	DH150	8/9	EK90	9/9	N329	9/9	U153	9/9	Z86	8/9
1AK8	8/9	6U6	4/9	20D1	14/9	DH142	8/9	EL32	4/9	N727	9/9	U159	9/9	Z77	7/9
1AB8	1/9	6V8GT	9/9	20P1	12/9	DK51	7/9	EL34	16/9	OA71	4/9	U142	9/9	Z142	9/9
6B8	3/11	6V6G	9/9	20F2	8/9	DK38	9/9	EL38	9/9	OC72	25/-	U403	9/9	Z145	9/9
6BG6G	18/9	6X4	8/9	21A6	8/9	DL92	7/3	EL41	10/9	P61	2/9	U154	9/9	Z152	5/9
6BY7	7/9	6X2	6/9	25L6	9/9	DL94	8/9	EL40	9/9	PL33	9/9	U262	9/9	Z719	5/9
6BX6	8/9	6X5	5/11	30P16	8/9	DL96	9/9	EL91	4/9	PCL82	12/6	U381	9/9	Z729	16/9
1C9	11/9	7C6	7/9	35Z4	9/9	EAF0	1/9	EL90	9/9	PEN46	6/9	U281	9/9	ZD17	9/9
6CD6G	7/9	7C6	7/9	53KU	10/9	EAF42	8/9	EY51	11/9	PEN383	8/9	UABC80	10/6	ZD152	5/9

# LASKY'S RADIO



## C.R. TUBES NEW, UNUSED & GUARANTEED

16in. Metal Cone, famous make, Type T901/B. 6 volt .3 amp. heater, ion trap, 12-14 kv. E.H.T., wide angle, standard 38 mm. neck. LIST £16

**LASKY'S PRICE £6.9.6**

Carr. & Insur., 21/-.

Masks, Anti-Corona, Bases and Ion Traps available.  
Ferranti 9in., T9/3, 4 v. heater, triode, octal base, standard deflection. LIST £9.

**LASKY'S PRICE 59/6**

Ferranti 12in., T12/44 and T12/54. (LIST £12), 99/6. Carr. & Insur., 12/6.

Also other famous makes :  
17in., ion trap, £9.19.6.  
17in., aluminised, 10 Gns.  
14in., £7.19.6. 21in., £12.19.6.  
Carr. & Insur., 15/-.



## SPECIAL OFFER! MULTI-TEST METERS

**FAMOUS MAKE, NEW AND UNUSED**  
AN/27. Accurate, highly sensitive 27-range Test Meter. 5,000 ohms per volt A.C. and D.C. In black leatherette-covered wood case. 7½ x 9½ x 3½ in., with carrying handle and ample room for small tools as well as leads. LIST 15 Gns.

**LASKY'S PRICE £11.19.6**

Post 5/- Leads 7/6 extra. AVAILABLE ON EASY TERMS.

## BARGAIN OFFERS OF TURRET TUNERS

By Cyldon and other well-known makers. New and unused in maker's cartons. List price, 7 gns. A few examples :

P.10.L. (series heaters), I.F. 9-14 mc/s. 59/6.  
P.16.H. (series heaters), I.F. 16-19 mc/s. 99/6.  
E.10.L. (parallel htrs.), I.F. 9-14 mc/s. £5/19/6.

Post 3/6. All other types in stock. List on request.



AN/20. Pocket size 18-range multi-test meter for amateur or service engineer. 5,000 ohms per volt A.C. and D.C. with accurate linear scales for the lower A.C. ranges. In black leatherette-covered case, 3½ x 3½ x 1½ in. deep. LIST 9 Gns.

**LASKY'S PRICE £5.19.6**

Post 3/6. Leads 3/9 extra.

## "STIRLING" BAND III CONVERTER

Very efficient, tunable over all 13 channels, incorporates own power supply for 200-250 v. A.C. Brown metal case, 4in. wide, 7in. deep, 2in. high.

**CASH PRICE 6 GNS.** Post 2/6.

21/- deposit and 5 monthly payments of 21/-.

## MAKER'S SURPLUS COMPONENT BARGAINS

WIDE ANGLE 38 mm. and STANDARD 35 mm.

Large stocks. See our previous advert or send for list.

### LASKY'S (Harrow Road) LTD.

Open All Day Saturday. Early Closing, Thurs. Mail Orders to Harrow Rd.

42, TOTTENHAM COURT ROAD, W.1. 370, HARROW ROAD, PADDINGTON, W.9.  
Telephone: MUSeum 2605. LADbroke 4075 and CUNningham 1979.

## Now... in your own home, LEARN

NO PREVIOUS TECHNICAL EXPERIENCE NEEDED!

**PRACTICAL EQUIPMENT (INCLUDING TOOLS) GIVES YOU A REAL LABORATORY TRAINING**

# RADIO - TELEVISION - ELECTRONICS

"The trained electronics engineer has a great career ahead of him."

Valuable FREE Book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the trained man—high pay, a prosperous future—or if you prefer it— independence in your own business. If you are trained at home by E.M.I. you will be in the hands of specialists who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

Practical Radio and Television Servicing  
Practical Electronics  
Electronics Engineering Automation  
Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc.  
A.M. Brit.I.R.E., City & Guilds Radio Amateurs' Exam.  
R.T.E.B. Certificate  
P.M.G. Certificate  
"NO PASS—NO FEE"

We Definitely Guarantee "NO PASS—NO FEE"

Full details of the Courses, Practical Equipment, convenient monthly payments, our Employment and Advisory Depts., and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. There is no obligation and the book will be sent to you quite free of charge.

### FREE BOOK - POST NOW!

Please send me a free copy of your Guide to Careers in Electronics.

NAME .....

ADDRESS .....

Subject or Exam .....




## E.M.I. INSTITUTES

# SCHOOL OF ELECTRONICS

The Specialist Electronics Division of the British Institute of Engineering Technology.  
(DEPT. SE/20), COLLEGE HOUSE, 29-31, WRIGHT'S LANE, KENSINGTON, LONDON, W.8.



# Practical Television

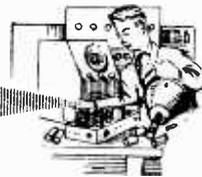

## & TELEVISION TIMES

Vol. 9 No. 107

EVERY MONTH

JUNE, 1959

### TELEVIEWS

Editorial and Advertisement Offices :  
**PRACTICAL TELEVISION**  
George Newnes, Ltd., Tower House,  
Southampton Street, Strand, W.C.2.  
© George Newnes Ltd., 1959.

Phone : Temple Bar 4363.  
Telegrams : Newnes, Rand, London.  
Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

#### SUBSCRIPTION RATES

including postage for one year

Inland - - - 19s. per annum  
Abroad - - - 17s. 6d. per annum  
Canada - - - 16s. per annum

#### CONTENTS :

	Page
Editorial	537
A New Aid for Servicing	538
Analysing and Servicing TV Receivers	539
Transistors in TV Receivers	542
Telenews	545
The Problem of Interlace	547
Television Troubles	549
Servicing Television Receivers	553
A Band V Converter	556
Building a Spot-wobble Unit	560
Correspondence	562
R.E.C.M.F. Exhibition	563
Underneath the Dipole	567
Your Problems Solved	571

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

#### REPLACEMENT C.R. TUBES

**I**N our Editorial in the April issue we pointed out that if cathode ray tubes were rebuilt, Purchase Tax had to be paid by the customer unless his own tube was rebuilt and returned to him. We showed that if P.T. were paid on a rebuilt tube, then, since tax had already been paid when it was new, H.M. Customs and Excise would have received tax twice.

This anomaly was removed in the recent Budget. There is now no purchase tax on any replacement cathode ray tube. This means that tubes being rebuilt need not retain their identity throughout the process. There is no doubt that but for the tax on replacement tubes many viewers would not have put up with inferior quality pictures.

The Chancellor said in his statement: "I propose to free replacement TV tubes from tax. This tax has been suggested to me as being unduly burdensome, and technical developments in the reconditioning of tubes have made it difficult to administer the tax with equity.

"I must, of course, take care that the concession does not give an opportunity for tax avoidance on the sets themselves, and a Treasury Order to safeguard this point will be laid before the House."

This Treasury Order became effective on April 8th, and means that TV receivers (whether or not in a cabinet) which are complete or substantially complete, except that they lack a cathode ray tube at the time when they become the subject of a chargeable transaction, are to be treated for tax purposes as if a C.R. tube formed part of the receiver, and the value of a new tube of appropriate size and character is to be included in the full value of the receiver upon which tax is to be charged.

Thus, tax cannot be evaded by marketing TV sets without tubes. Kits of parts for building receivers are, however, exempt from the Order.

#### OUR QUERY SERVICE

**W**E must once again remind readers that, whilst we are always pleased to help them with their technical difficulties, they must provide evidence of their readership by enclosing with their query the "Queries Coupon" from the current issue (to be found on the last page of "Your Problems Solved"). A stamped, addressed envelope must also be enclosed.

We cannot supply diagrams or provide instructions for modifying surplus equipment unless a relevant article has appeared in PRACTICAL TELEVISION and then only if copies of the issue concerned are available for sale.

We are receiving so many letters from those who are obviously not readers of the paper that we are compelled to insist upon rigid adherence to our rules.

Our next issue, dated July, will be published on June 19th

# A New Aid for Servicing

DETAILS OF A SPECIALLY-DEVELOPED CATHODE-RAY TUBE AS A SERVICING ACCESSORY

**I**n pursuance of our policy of keeping readers informed of the latest developments, we now have much pleasure in giving details of an entirely new approach to the servicing problem.

As most readers will know, the servicing of television receivers can be one of the most difficult of the serviceman's tasks. Apart from the many different sections of the complete circuit which may have to be tested, and perhaps rewired, one has first to gain access to the wiring. In many receivers this is underneath a chassis which can be of quite large dimensions, and to add to the serviceman's difficulties, there is probably an elaborate structure mounted on the top of the chassis into which is firmly mounted the picture tube. If it is a receiver of the console type it may be found that the tube is firmly attached to the front of the cabinet, and the chassis may be removed a short distance only, not sufficient to enable the wiring to be made accessible until the tube has been detached from the cabinet.

Several methods of simplifying the task have been proposed and, in fact, one manufacturer now makes the chassis in vertical form, hinged on one side so that it may be swung back (after the back of the cabinet has been removed) and there is no need to disconnect any leads. All parts of the wiring may thus be checked. Another manufacturer constructed the assembly on metal tubing with the various sections disposed round the tubing which carried, in the centre, the picture tube. The entire unit could then be placed on the bench, and it could be rolled and turned very easily to permit any section to be tested.

The G.E.C. have, however, attacked this problem from a different angle and have produced a special picture tube, which they call a "setting-up" tube. This is a 6in. unit with magnetic focusing, and it is claimed that not only does it facilitate the servicing of receivers but, as a result, the work is more economical and should thus reduce the overall cost of service work.

## Advantages and Applications


The new tube will plug into the majority of television receivers which use a 14in., 17in. or 21in. rectangular tube, and it operates directly from the available supplies. The small size and weight compared with the standard picture tubes makes this an extremely useful accessory for setting-up or checking a receiver either on the test bench or in a customer's own home.

Typical advantages and applications are:

1. The avoidance of unnecessary handling of heavy and bulky picture tubes during any test of a receiver.
2. The use in cases where a large picture tube is suspect to ascertain quickly and easily whether the fault is in the picture tube or elsewhere.
3. In sets in which the picture tube is fixed tube to service the set. The risk of damage to the large and expensive picture tube is therefore avoided.

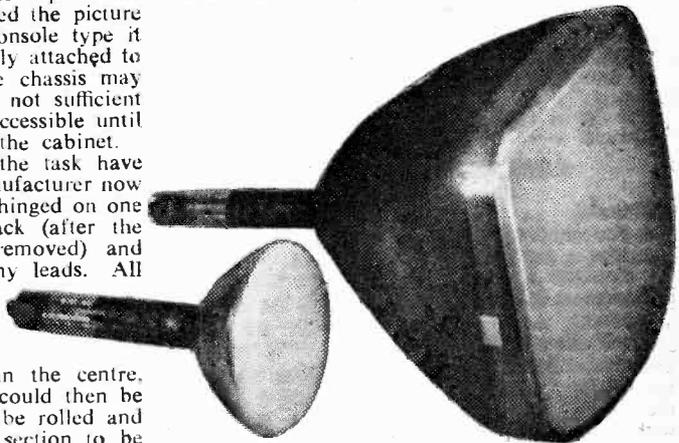4. In sets in which the picture tube is fixed to the chassis, the small size of this "setting-up" tube increases the accessibility of the components on the chassis.

This new tube will normally not require any special mounting arrangements, the focus magnet or deflection coil mountings sufficing to hold it in position. An electrostatic model is also available, and the reference type numbers are 1668VMM for the magnetic model and 1668VTM to the cabinet, there is no need to remove the for the electrostatic model. The standard duodecal base is fitted (B12A) and the side contact for the anode is of the CT8 type. The price of



The new tube (on the left) with a standard tube, showing its small overall size.

this tube is £7 10s. nett to the trade, and a specially designed wooden carrying and storage case is available.


## International Transistor Exhibition and Convention 21-27 May, 1959, Earls Court, London

**F**INAL details for receiving convention delegates and exhibition visitors have now been resolved, and tickets for admission to the exhibition are now available.

Both convention and exhibition are being promoted by the Electronics and Communications Section of The Institution of Electrical Engineers. Some 2,000 delegates from all over the world are expected to attend the convention, very ably organised by the I.E.E.

Visitors to the exhibition will include scientists and engineers representing all developments and applications of transistors and semiconductor devices, and also science students from schools, technical colleges and universities.

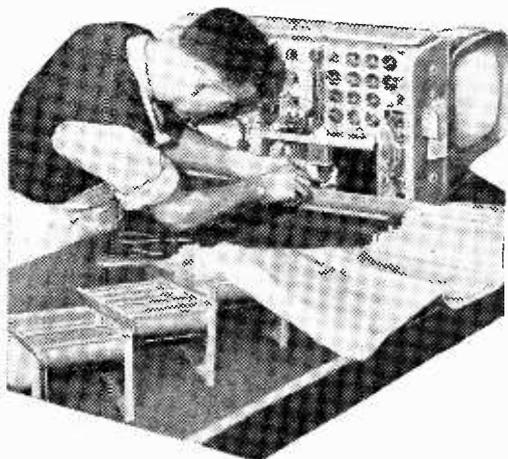Application for exhibition tickets, whether from individuals, scientific bodies, engineering companies, government departments, or from universities, technical colleges and schools, may therefore be sent to: Industrial and Trade Fairs Ltd., Drury House, Russell Street, London, W.C.2.



# Analysing and Servicing TV Receivers

No. 7.—THE EHT SUPPLY

By "Diadem"

anode V2. bringing the voltage on this anode to 350 v. This enables a larger line scan to be obtained than would be possible with only 200 v. As a large flyback pulse (up to 4 kV) appears between the cathode and heater of V3, a special type of rectifier is employed with much greater insulation than is normally required.

### The "Overwind"

The EHT voltage is obtained from the rapid flyback pulse developed across the scan coils, this maximum to minimum change causes a high voltage pulse to be induced in the line transformer. By extending the winding (points 1 and 2), sometimes referred to as an "overwind," and by connecting the end of this winding to a suitable rectifier, this pulse may be rectified to supply a steady voltage of 10 kV or more to the tube. The smoothing condenser is C4.

### Rectifier Heater Supply

The heater supply for V4 is obtained by induction; a winding consisting of a few turns of wire is placed near the high potential winding. Providing the line circuit is working correctly the

**L**INE flyback EHT.—Fig. 26. Although we are only to discuss different methods of obtaining EHT it will do no harm to diagnose briefly the whole circuit in Fig. 26 as it is all tied up with the high voltage supply. The scan coil circuit is coupled back to the grid of the oscillator, V1, by C2; this enables part of the output of V2 to be fed back into the oscillator, V1. This pulse is clipped by the triode V1, its phase is reversed and the output from V1 anode is fed into the grid of V2 through the coupling condenser C1. The frequency of the oscillator is controlled by the sync pulses at the end of each line. These pulses are fed into the anode of V1 thereby enabling the repetition frequency of the timebase to keep in step with the transmitted line frequency of 10.125 c/s. The line transformer is auto-wound. This gives it much greater efficiency than if it were a double wound type. The output of V2 is passed through the auto transformer to feed the scan coils.

### Boosted H.T.

In the older type of television receiver the power generated during the line flyback was wasted in a series condenser and resistor arrangement shunted across the scan coils, this was done to improve the waveform, prevent ringing and to give a more linear scan. A large amount of power was wasted in this damping resistor. To-day this power is reclaimed and rectified by the efficiency diode V3 and smoothed by C3, about 150 v. extra being achieved by this method. The H.T. line voltage is added to this and then passed to the line amplifier

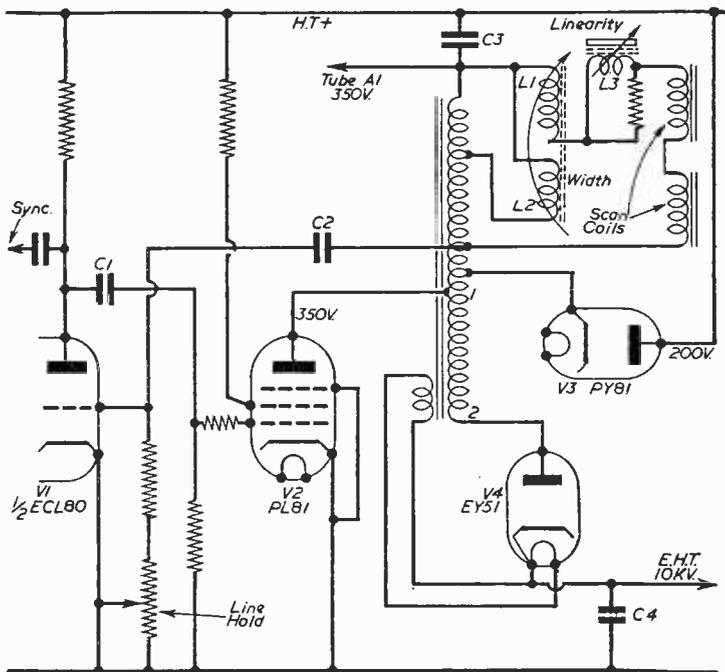


Fig. 26.—Circuit for line flyback EHT.

correct heater voltage will be supplied to V4. Although the voltage on V2 anode is stated to be 350V, readers are advised not to take a voltage reading at this point as a pulse of several kV is present. The width is controlled by sliding a

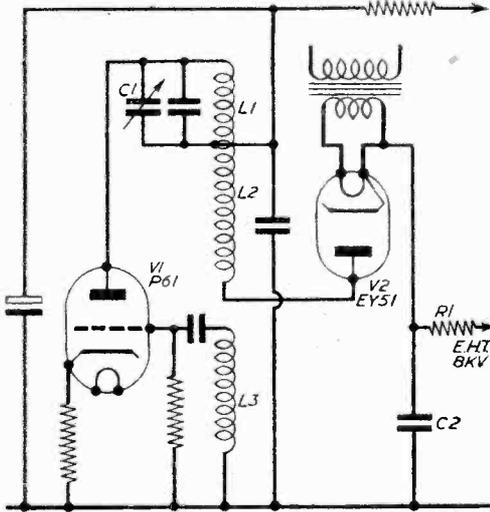


Fig. 27.—R.F. EHT supply.

territe rod through coils L1 and L2. This method does not affect the linearity or the EHT potential. L3 is the linearity coil and the core is also a ferrite rod. The correction of the waveform is carried out by adjusting a magnet with respect to the core.

**R.F. Oscillator**

Fig. 27.—EHT is obtained by means of an R.F. oscillator V1. The coil L1 is a tuned anode winding inductively coupled to the grid winding L3. The frequency of the oscillations is controlled by the variable trimmer C1. The oscillating voltage formed across L1 is fed to L2, the EHT winding; this voltage is stepped up by L2; rectified by V2 and smoothed by C2 and R1. The EY51 heater voltage can be obtained by a separate winding on the R.F. coil as in the case of the flyback system. By adjusting C1 it is possible to alter the EHT output by several kV. This might cause a greater voltage to be induced across the heater winding and "blow" the rectifier heater. This trouble can be overcome as

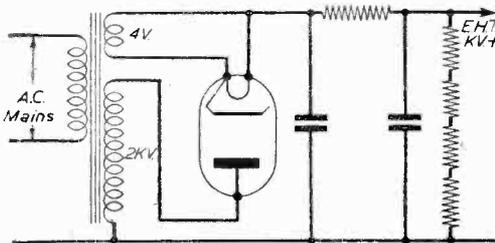


Fig. 28.—Mains driven EHT (positive supply).

shown by using a separate heater transformer of high insulation.

Figs. 28 and 29.—These diagrams show two methods of obtaining EHT from a mains transformer. These two types of supply are dangerous and more costly than other forms of EHT generation already described and are not used by manufacturers to-day for television receivers. No explanation of the circuits is given as they work in the same way as a normal H.T. supply.

Fig. 30.—This diagram shows another form of EHT supply known as the ringing choke. A sawtooth drive is derived from a separate oscillator and the EHT output can be varied by reducing the output from the oscillator by means of variable control R1. For a working description of the remaining circuit refer to the notes already given on flyback EHT.

**EHT Faults**

**No EHT.**—Where line flyback is used, lack of EHT can be caused by a faulty line generator or amplifier, line transformer, rectifier, tube or booster diode. A faulty transformer or line valve will prevent the rectifier from lighting up. Rotate the line hold control and listen for the whistle varying in pitch. Check the line valve top cap for a small spark. If a spark is present, turn down the brilliance control. If the rectifier lights up orange-red check for a large spark at its anode and a small spark or fizzy sound at its cathode. If the spark at the cathode diminishes or cuts out when the brilliance control is advanced suspect low emission of rectifier. If there is no spark with the brilliance at minimum remove the cap from the tube and test the cap for a spark. If

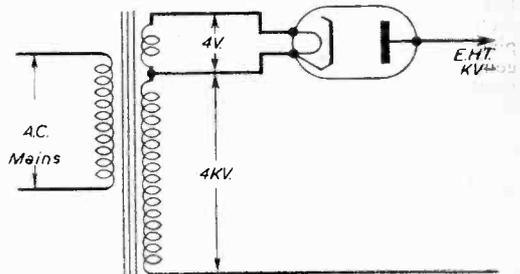


Fig. 29.—Mains driven EHT (negative supply).

a spark is present, suspect a faulty tube. Check the voltage on its grid and cathode and if it is a tetrode or pentode tube check A1 for a short. The tube may be soft or consuming excessive current. If there is still no spark disconnect the rectifier anode from the transformer; try the anode tag for a spark. If there is one suspect the rectifier for an internal short or filament winding leakage. Examine the EHT smoothing condenser and its resistor if one is fitted. The condenser can be disconnected temporarily. If the rectifier does not light examine the line valve and its components and if found to be in order suspect a shorted turn on the line transformer EHT overwind, or open circuit of the heater winding.

**EHT rectifier glows blue.**—The valve is "soft" or overloaded. Check its smoothing components

and "Metrosil" if fitted. Check the C.R.T. and for leakage across transformer windings.

Picture expands on whites and defocuses or "blows up" on advancement of the brilliance control. This is poor EHT regulation and low EHT. Check the rectifier for low emission. If the heater is dim check the line output valve.

Inability to obtain raster with aerial connected, and on removal of the aerial the raster becomes visible. Check for very low EHT rectifier.

### R.F. EHT Supplies

The faults occurring in this type of supply are few. The oscillator valve may cease working as its emission drops. Replace the valve or see if it is oscillating. In some circuits the current consumption will rise considerably and almost double in some cases and the valve temperature will be high when oscillation ceases. Check the trimmer across the coil and resistors and condensers for faults, also test for spark as given in the earlier paragraph on flyback EHT. Finally, suspect breakdown or leakage across oscillator coil transformer. These units are very reliable and safe to handle as the EHT drops to a low value if the supply leads are accidentally touched. Therefore if there is a leakage occurring across any components in the unit, oscillation may cease altogether.

### Ringed Choke EHT

This particular method is very similar to the flyback system except in this case the line output valve deals with the scanning only and a separate EHT generator supplies the tube voltage after rectification. Sometimes the EHT unit is complete with its own sawtooth generator, EHT generator and rectifier, and in others the sawtooth drive to the EHT generator is supplied by the line output valve, and if the line time-base breaks down there will be no EHT. Fault tracing and spark tests on the lines of flyback EHT can be employed.

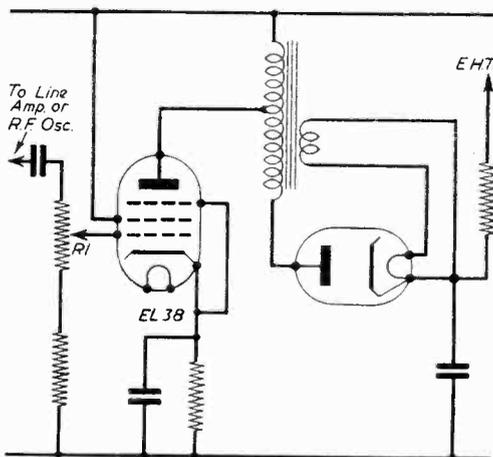


Fig. 30.—Ringed choke EHT.

### Mains-driven EHT

In this method the main faults are insulation breakdown in the transformer windings and this usually means replacement. To prevent breakdown between windings and the core, always insulate the core from the chassis and in cases where one side of the secondary is connected to the core, this wire must be removed and the connection taken to chassis. The transformer should not be operated without a load, and bleeder resistor chain across the EHT supply should be carefully checked for open circuit. This type of supply can be lethal and great care should be taken when handling it. If the bleeder chain goes open circuit the smoothing condensers will remain charged up and these can hold a very dangerous charge for some time after the set is switched off. Intermittent arcing in the transformer, condensers or resistor chain will be noticeable on sound as a clicking noise and on vision as interference spots or "snow."

(To be continued)

## E.M.I. Colour TV

WHEN the Anatomical Society held a symposium recently at the Department of Anatomy's lecture theatre. University College, London, E.M.I. Electronics Ltd.'s new colour television equipment was used to give the capacity audience a close-up view on a 4ft. X 3ft. screen of experiments being carried out under a microscope in a small laboratory several floors away.

The lecturer demonstrated how to prepare biological specimens for use in an electron microscope. As thin sections of tissue vary in colour, when viewed in reflected light according to the thickness of the slice, colour was the most important factor to be conveyed to the screen. The E.M.I. colour TV camera was connected to the optical microscope under which the tissue was being cut.

This is believed to be the first time in this country that this technique has been televised in colour.

## Insulated Instrument Wire

SIEMENS-EDISWAN P.T.F.E. instrument wire for use in electrical instruments is now available from them. Initially, two types are available; for use at voltages up to 500 volts r.m.s. and 1,000 volts r.m.s.

The wire, for use where conductor temperatures of between  $-75$  deg. C. and  $250$  deg. C. are experienced, has either single or stranded annealed copper wires each silver plated to a radial thickness of not less than  $0.00003$ in. The P.T.F.E. is extruded, which permits a high degree of concentricity to be obtained. Whilst the insulation is not loose, it can be cleanly stripped for connections. Electrically, P.T.F.E. has high dielectric strength and low power factor. It offers complete chemical resistance to all known solvents except molten sodium and fluorine gas. The wire is non-chafing owing to the low coefficient of friction; it is highly flexible, and will not harden or perish.



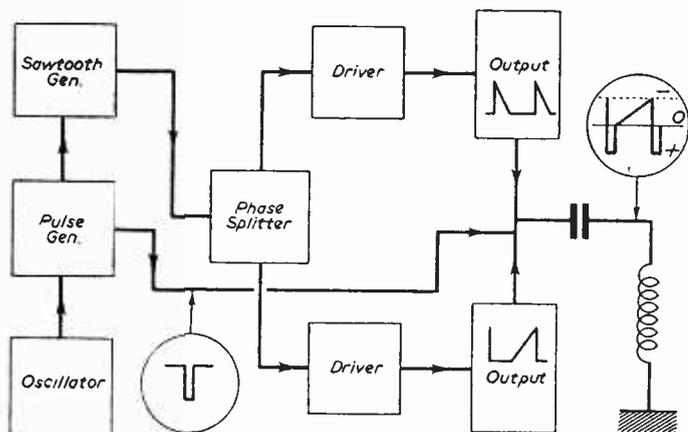


Fig. 25 (a).—A block schematic of the circuit.

system and also a bright picture with a limited video drive. Thus, the EHT generator presented a problem not covered by the existing literature on the subject of D.C. converters.

A circuit which gives the required performance is shown in Fig. 26. The heart of the generator is a square wave oscillator employing a saturating-core transformer (T4) and two transistors (Tr45 and Tr46). A further winding on the transformer, connected to a voltage doubler circuit (D22, D23, C110, C111) produces the EHT potential. Valve rectifiers are used for convenience. Their heater windings and a further winding to supply a 70 v. H.T. supply for the video stage are also on the transformer T4, but

they are not shown in the diagram.

Tr39 which is the upper of the two output transistors. Adjustment for cross-over distortion is made by setting the bias of the output stages via their respective drivers with the resistors RV11 and RV13.

**EHT Generation**

The EHT potential must be stabilised against change in beam current and against change in battery potential within  $\pm 0.3$  per cent, if focus is to be retained with the scan magnification system. Furthermore, it had been decided to operate the picture tube at an ultor potential of 18 kV as this eased the problems of achieving a good spot size with the scan magnification

they are not shown in the diagram.

The essence of the stabilising system is to maintain constant the H.T. potential at point A (the supply to the square wave oscillator) using a Zener diode D17 as a reference. A change of potential at point A appears at point B owing to the high output impedance of the transistor, Tr44. The potential at B is compared with that across the Zener diode D17 by means of the long-tailed pair Tr40 and Tr41. The resulting change of potential at the collector of transistor Tr41 controls the series transistor Tr43 via the emitter follower Tr42 thus completing the feedback loop.

The inherent output impedance of the EHT unit, for constant potential at point A, is approxi-

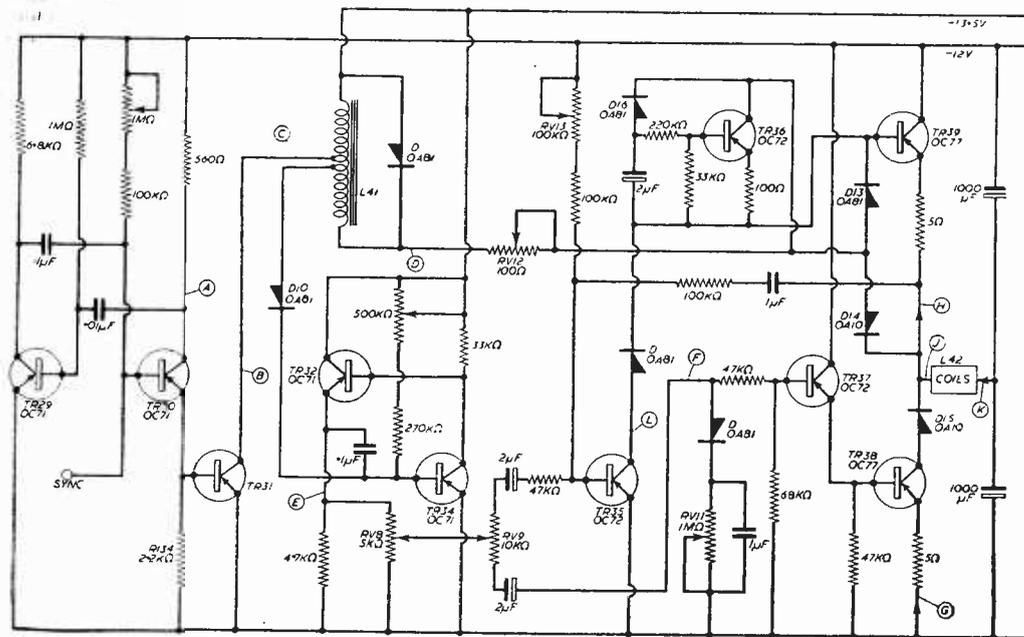


Fig. 25 (b).—The circuit of the field timebase.

mately 3 MΩ over the range 60 to 360 μA. (At lower currents the switching transients produce much higher output potentials. Hence, a bleed resistor (R130), (actually voltage dependent) is used to maintain a minimum drain of 60 μA.) This output impedance is reduced by direct control of the feedback loop previously described with the EHT output current. The earthy end of the EHT winding is connected to chassis via the base bias network (R125, etc.) of the transistor Tr44. An increase of EHT current causes point C to move negative, point B to go positive, point D to go negative and so the potential at point A to go more negative also.

**Pre-set Control**

The pre-set control RV15 is primarily used to adjust the EHT source impedance to zero, but it does interact with the main "Set EHT" control RV16. Some care has been taken in stabilising this circuit against temperature changes (e.g., use of a long tailed pair, very low resistance base circuits throughout) and a good long term stability is expected.

The emitter follower Tr42 requires, for proper

operation, H.T. potentials in excess of that of the main H.T. line. At present a -22 v. supply derived from the output stage (rectifiers, D20 and D21) and an extra 1.5 v. battery are used. Further development of this stage will depend on the answers to the questions posed earlier (under line timebase), but if a separate unit is required then some simplification of the present circuit is desirable. The following points require study.

With such a large power handling capacity a fault may have disastrous effects on other parts of the circuit. Hence, the effects of various faults must be investigated and every effort made to confine the damage done by the more likely dangers such as short circuit of the output terminals.

At present the operating frequency is low (400 c/s) and the final smoothing (required to achieve straight vertical edges to the picture) involves very large smoothing capacitors.

For the mean current being used with the presently available video drive the EHT unit is very inefficient. A unit matched more accurately to the requirements of the rest of the receiver would reduce the battery consumption considerably. More fundamentally, the sources of the losses need to be analysed and attacked.

**Power Supply**

The main H.T. supply of (Continued on page 548)


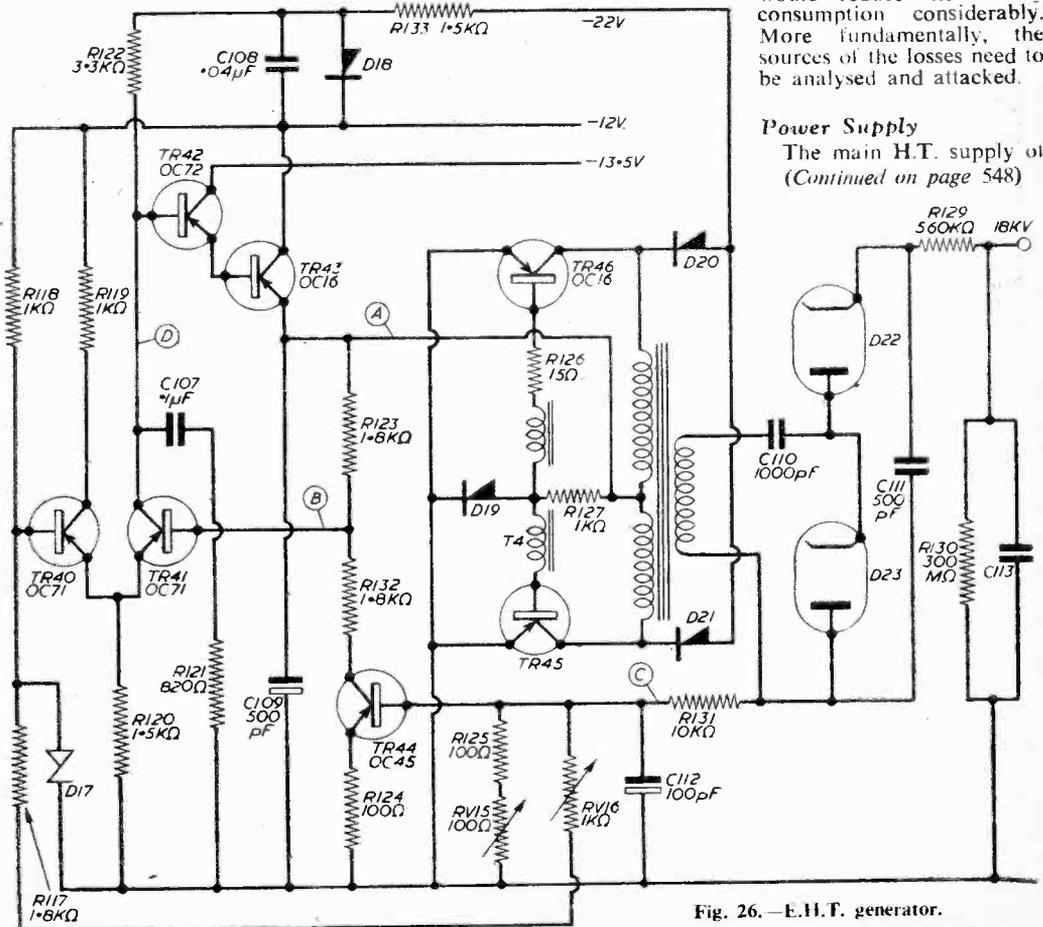


Fig. 26. — E.H.T. generator.

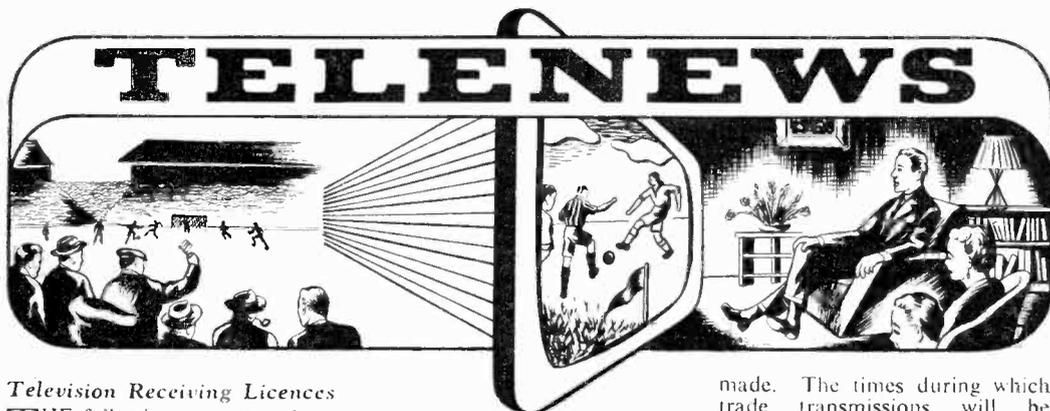

**Television Receiving Licences**

THE following statement shows the approximate number of Television Receiving Licences in force at the end of March, 1959, in respect of receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal...	1,690,174
Home Counties ...	1,192,030
Midland...	1,430,911
North Eastern ...	1,508,696
North Western...	1,270,377
South Western...	756,447
Wales and Border Counties ...	549,308
Total England and Wales ...	8,397,943
Scotland ...	750,891
Northern Ireland ...	106,588
Grand Total ...	9,255,422

**North-Eastern Electronic Exhibition**

THE North-eastern Electronic Exhibition will be held at the Rutherford College of Technology, Newcastle, on May 27th to 29th.

**Closed Circuit Television**

THE importance of advertising, and in particular television advertising, to the British economy, received official acknowledgment in February last when the President of the Board of Trade, Sir David Eccles, inaugurated the closed circuit television and telecine system at the new Headquarters of L.P.E. Television Ltd., in St. Martin's Lane, London. The system, one of the most modern and extensive of its kind, was designed and installed by Marconi's Wireless Telegraph Co., Ltd.

The system enables any executive to audition artistes without leaving his office. The audition is televised by a camera

in the viewing theatre and studio in the basement and the signals conveyed by cables to the receivers in the various offices. The executive has only to switch on to see the artistes exactly as they would appear in a TV advertisement.


**Trade Transmissions to be Interrupted**

TRADE transmissions from the Lichfield, Winter Hill, Emley Moor, St. Hilary and Croydon stations of the Independent Television Authority are in future to be interrupted for a short period each day to enable carrier frequency measurements to be

made. The times during which trade transmissions will be interrupted have been agreed with the R.T.R.A. and will be as follows:—Lichfield, 13.30-14.00; Winter Hill, 13.35-13.45; Emley Moor, 13.35-13.45; St. Hilary, 13.45-13.55; and Croydon, 13.45-13.55.

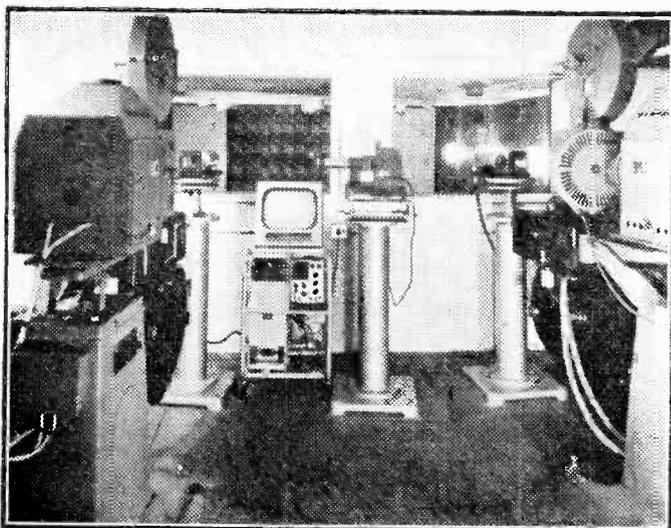**Programme Arrangements for S.E. England**

PROGRAMMES from the I.T.A.'s station near Dover are, subject to contract, to be provided by Southern Television Limited. This station will serve an area stretching from the Medway towns to Beachy Head and it is planned to bring it into operation either late this year or early 1960. The area is contiguous to that in



The projection room of L.P.E. Television Ltd., with two Marconi BD871 television cameras mounted on pedestals for telecine work. (See "Closed Circuit Television".)

which Southern Television are already operating.

Southern Television have undertaken to cater for the tastes and interests of the area and intend to open a studio there. They propose to invite prominent people in the area to associate with them. This appointment follows upon the Authority's decision announced last November to make the Dover transmitter the first of a number of satellite stations to serve areas which do not require or make financially possible the operation of independent companies.

### Solartron Traps the Transient

TO arrest transient phenomena and be able to study it at leisure by a trouble-free method has long been a need of scientists and engineers in almost every field of scientific research, development and industry. The new Solartron Infinite Persistence Oscilloscope, type QD.910 enables this to be done by "freezing" non-recurrent waveforms and other types of curves on an oscilloscope screen for as long as may be desired.

This oscilloscope employs a "Memotron" storage cathode-ray tube which gives an infinite trace persistence. The trace is immediately erasable after each investigation is completed. The QD.910 is a dual-channel instrument, each channel having a bandwidth of D.C. to 1 Mc/s.

### Silver Medal for Benny Hill


THE Television Society's Silver Medal, awarded annually for an outstanding contribution to television as an educative or entertainment medium, was this year presented to comedian Benny Hill.

The medal was presented at the society's annual dinner at the Dorchester Hotel, Park Lane, on April 17th, when the Postmaster-General was present. Among the guests were Sir Ivone Kirkpatrick (chairman of I.T.A.), Sir Arthur florde (chairman of the BBC), Mr. Sydney Bernstein (chairman of Granada TV Network), Dr. J. Bronowski, and many other television personalities.

Last year the society's medal was presented to Mr. Cliff Michelmore. It was instituted

in 1948, and is the first of any such awards to be made in Britain.

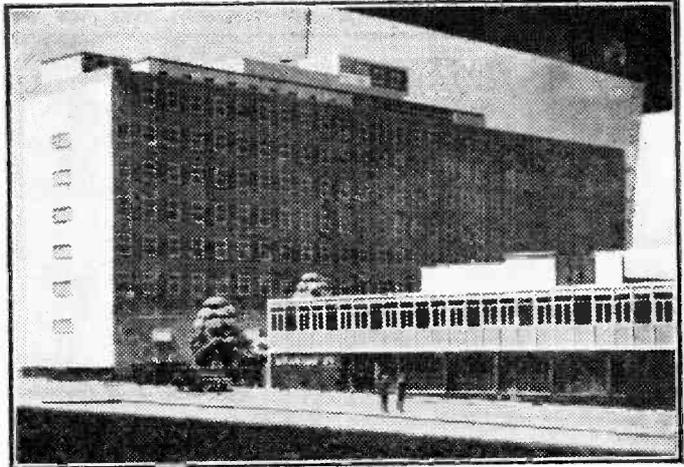in Pontypridd who had been run over by a steam roller. The original print order of 15,000



A model of the new extension to the Granada TV studios in Manchester.

### BBC's Election Broadcasts

IN view of doubts that have been expressed about the legality of the arrangements which were announced on March 18 for broadcasting during the next General Election, the Corporation wishes to make its position clear.

The purpose of all the BBC's Election broadcasts will be to help the public to cast their votes with as clear an understanding of the issues involved in the Election as the broadcasts may be capable of presenting. It will be no part of the BBC's intention to promote or procure the election of a particular candidate in any constituency. Candidates taking part in Election broadcasts will be asked to refrain from dealing with any point at issue in terms of their own, or any other individual's candidature.

### Twenty-five Thousand Transistor Radios

WHEN Gilbert Davey finished his series, how to build a pocket transistor radio set, in the BBC Children's Television programme "Focus," 25,521 applications had been received for the pamphlet which accompanied the programmes. The writers ranged from a 78-year-old who wanted to make the set in his spare time, to a little boy

pamphlets had to be increased, first by 10,000, and then by 5,000. Applications, as we go to Press, are still arriving at the rate of 100 a day along with requests from young viewers for further technical information about the pocket size transistor set, about 1in. X 3in. X 5in. which works a hearing aid ear-piece and costs about 45s. to make.

### Videotape Recorder

AMPEX CORPORATION of America has developed a prototype modification to the firm's standard VR-1000 Videotape recorder permitting one machine to record television programmes on any two, three or all four of the television standards used throughout the world. Previously, television programmes could not be exchanged electronically between Europe and North America, for example, or between England, France and the rest of the European continent. With the Ampex "Inter-switch" modification, however, a Videotape recorder in Hollywood can record a television programme for American television, using 525-line cameras, and then switch to the 405-line system, for instance, to record the same programme with 405-line cameras for British television viewers.

# The Problem of

By D. R. Bowman

# Interlace

IMPROVING PICTURE QUALITY

(Concluded from page 508 of the May issue)

As explained last month line sync pulses are not long enough to allow the flip-flop action to take place; the valve remains cut-off, and only very small line pulses appear in the anode circuit. These are due to feed-through via valve capacitances.

### Suppressor Driven Negative

When a 40  $\mu$ s pulse appears on the control grid, however, the valve is cut-on for 40  $\mu$ s. During this time the transistor has time to operate; not only is the suppressor driven negative (which has no effect on the anode current cut-off condition), but also there is enough time for C1 to recharge. As seen before, this will eventually cause the anode to draw current, and a steep-fronted pulse appears at the anode. At the end of the 40  $\mu$ s pulse, the valve is again completely cut-off and the operation ceases until the next 40  $\mu$ s pulse appears on the control grid.

### Critical Time Constant

Thus it can be seen that every frame pulse gives a square wave at the anode, and what is more, identical waves on odd or even frames. Everything depends on the time-constant C1.R3 being adjusted to the correct working point greater than 10  $\mu$ s and less than 40  $\mu$ s. The values of C1 and R3 given in the diagram are thus suitable, and adjustment is made by varying R3 until proper interlace is obtained.

This circuit gives negative-going frame pulses at the anode and negative-going line pulses at the screen: both are at low impedance and are suitable for synchronising multivibrator timebase generators.

A very suitable valve is the EF50; the more modern 6F33 is also excellent in this circuit. Other pentodes do not have their suppressor grid characteristics constant enough in manufacture for valves to be readily interchangeable, and some experiment with R1 may be needed if such valves as the EF91 are used.

### Patchett's Separator

This separator requires a pentode and also a double diode, and is thus not as economical in the use of components as the foregoing. It gives excellent results, however, and is used by the author in preference to any other. Once set up, it is impossible not to get perfect interlace

on both scan and flyback, and the line structure produced on the tube face is exceedingly rigid. The photographs reproduced (on page 508, May issue, and overleaf) were each of three minutes exposure and show the interlace on scan and flyback respectively. It will be noted that the duration of exposure is such that no picture is visible at all, only variations of density, owing to the moving picture. The height of the picture where interlace on scan is shown has been much increased, so as to separate the lines clearly. The distorted appearance of the picture showing interlace on flyback is due to the presence of a temporary loudspeaker with considerable field.

### Action of the Circuit

Fig. 7 shows the circuit diagram, and it will be easily understood that the basic device is a Miller integrator. The action is as follows:

A negative-going video signal (sync pulses positive) is fed to the suppressor grid of a pentode connected as a Miller integrator. The capacitor between anode and control grid is characteristic. This video signal is D.C. restored either by a separate diode (or crystal diode) or, if the pentode is a 6F33, by the diode internally strapped to the suppressor grid; the whole waveform is negative and the video part of the signal is cut off by the suppressor base.

During the period between pulses, the suppressor is sufficiently negative to cut off anode current, assuming pulses of about 6 volts or a little more


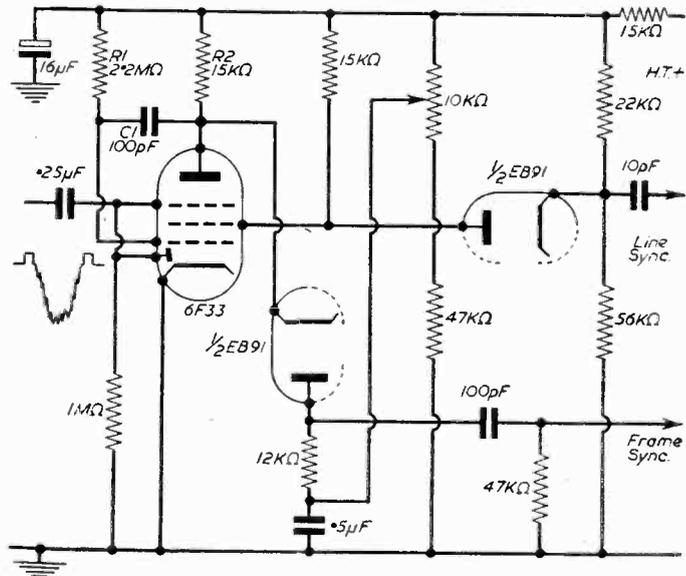


Fig. 7.—Patchett's sync separator.

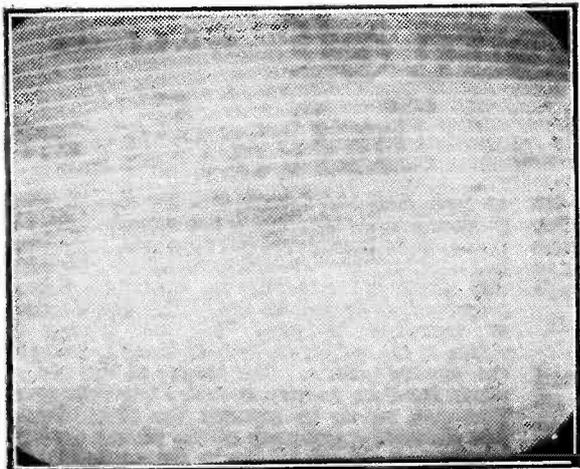

Patchett's separator—interlace on flyback.

are present. The anode rises to H.T. voltage and the "Miller" capacitor C1 between anode and grid is charged up fully by the flow of grid current—the grid is returned to H.T. and does not interfere with this because the coupling resistor is 2.2M. During a pulse, the suppressor grid rises to nearly zero voltage and anode current begins to flow. Anode potential drops and drives the control grid negative via the Miller capacitor, and this tends to reduce anode current; and equilibrium is soon achieved. The Miller capacitor now begins to discharge through R1 and R2 according to the usual "Miller" run-down" effect. At the end of the pulse on the suppressor, the suppressor again goes negative; and anode current is cut off and C1 again re-charges.

#### Proportional Voltages

Since the Miller run-down is linear it is clear that the anode voltage falls four times as much

during 40  $\mu$ s frame pulses as during 10  $\mu$ s line pulses. Thus, pulses differing in duration are converted into voltages differing in exact proportion.

The smaller 10  $\mu$ s line pulses are clipped off by the suitably biased diode, leaving triangular pulses at the frame output terminal. These are differentiated by the 47 k $\Omega$  resistor and 100 pF capacitor to give exceedingly sharp pulses to synchronise the frame timebase generator.

Since the control grid is driven negative during pulses, line sync pulses are available from the screen grid. Owing to capacitance between suppressor and screen, some video signal also appears at the screen and this is clipped off by the suitably biased diode before the line sync pulse is passed to the line timebase generator.

#### Polarity

Positive-going pulses are obtained from this circuit. These may be used direct to synchronise thyratrons, blocking oscillators and some multivibrators, though not all. If the pulses are of incorrect polarity, an amplifier of unit gain can be interposed. A 6J6 is hardly suitable, but an ECC81, with separate cathodes each connected via 150 $\Omega$  to chassis (unbypassed) and anode load resistors of 1k $\Omega$ , will prove effective without much pulse distortion.

Three very reliable sync separators have been described, at least one of which will be suitable to every experimenter's requirements. Each is, however, subject to noise, and this applies to all circuits. It may well be that in some cases, where fringe area reception is obtained, the very sharp pulse fronts that these circuits give are rendered less effective by the presence of noise. In such cases, the old-fashioned integrator may prove superior—just because its sloping pulse front is less affected by noise.

## TRANSISTORS IN TV RECEIVERS

(Continued from page 544)

the experimental receiver is 12 v. The current consumptions of the different stages in the receiver are as follow (in mA):

	12 v.	13.5 v.	70 v.
Converter...	6		
R.F. (full gain) Mixer ...	4		
Sound I.F. ...	6		
Vision I.F. ...	6		
Audio (typical) ...	15		
Video Synchronizing ...	2.5		7.5-30
Line ...	32		
Field ...	31		
E.H.T. ...	550-900	18-35	
	(200 $\mu$ A)		
Tube heater ...	150		


A triode picture tube is being used, hence no first anode supply is required. This would be no problem if required but could readily be provided from a tap on the EHT generator transformer. The video stage supply is part of the

EHT generator though its power consumption is listed separately above. The EHT unit and the frame timebase require extra H.T. lines (20 v. and 13.5V.). The 20V. supply again is part of the EHT unit but the 13.5 volt line is provided by an extra 1.5V. rechargeable cell.

Clearly future development will lie in the direction of more efficient EHT generators and the elimination of "special" H.T. supplies. In the view of the heavy power consumption inherent in a television receiver it does not seem that a portable television receiver will be fitted with expendable batteries unless some startling new advance in technique is realised.

The 12 volt supply of the experimental receiver is a Venner H705 silver-zinc rechargeable cell. It weighs 2½lb. and has a capacity of 7.5 Ah at a 1A discharge rate. Such a battery could be recharged at home from the mains after a day on the beach or in the country enjoying television. Something along these lines seems the obvious answer to the problem of power supply if portable television comes in the immediate future.

# TELEVISION TROUBLES

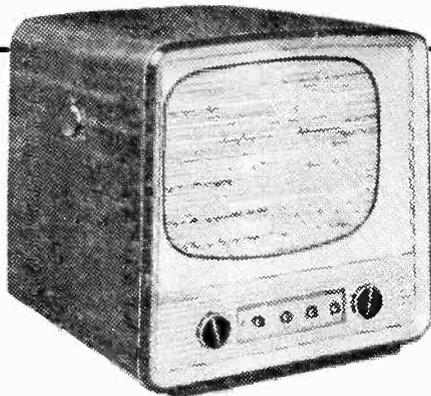

## Their Symptoms and How They May be cured—10 By G. J. King

This may have decreased considerably in value or gone open-circuit.

### Gradual Loss of Picture Width

After making the usual valve tests and the symptom still persists, a check of the value of the 470 k resistor in the anode circuit of the line oscillator is well worth while. This is often found to be high in value.

### Intermittent Breaking-up of the Picture Horizontally

This can prove to be a difficult fault to pinpoint, and often demands the replacement of a number of components to facilitate location of the culprit.

However, in the majority of cases the trouble can be eliminated by replacing the 270 k (R75) resistor connected to the grid of the L63 (V18).

### Horizontal Non-linearity

If the left-hand side of the picture is very much extended, with the right-hand side contracted and a bright, vertical line is present at the cramped side of the picture, attention should first be directed to the two 2,500 ohm resistors (R7) which are both mounted on the top of the rear control panel, and accessible for inspection. In the makers' service data, these are R73 and R74.

**T**HIS month attention is focused on various models in the G.E.C. range of receivers, keeping to the usual pattern in this series of concentrating on timebase and synchronising faults.

### Model BT1091

Although this model is of eight-year vintage it is still maintained in use by a large number of enthusiastic experimenters, as indicated by "Your Problems Solved" correspondence.

### No Frame Scan

Sudden frame failure on this model, resulting in a bright, horizontal line across the screen, should lead first to a check of the negative feedback capacitor in the frame timebase. This capacitor, shown as C60 in Fig. 1, is valued at 0.005  $\mu$ F and rated at 500 v. Owing to the relatively high peak inverse voltage to which it is subjected, it is often found to be short-circuit, resulting in the symptom mentioned.

It pays to make a replacement with a component of the same value, but rated at 1,000 v.

### Out of Balance Line Hold Control

If, in order to secure horizontal lock of the picture, the hold control requires to be hard over against one of the stops (even then there may be a tendency for the picture to "tear"). The trouble is invariably caused by value increase of the 270 k resistor (R75) connected in series with the line hold control. A resistor of reasonably good tolerance should be used as a replacement.

### Poor Line Hold

The lock is by no means definite, although it may tend to occur somewhere within reasonable balance of the hold control. It often happens that a change of camera or a distinct variation in picture content will result in the picture wriggling out of line lock. The first check should be of the 25  $\mu$ F electrolytic capacitor connected to the cathode (pin 2) of the 277 video amplifier valve.

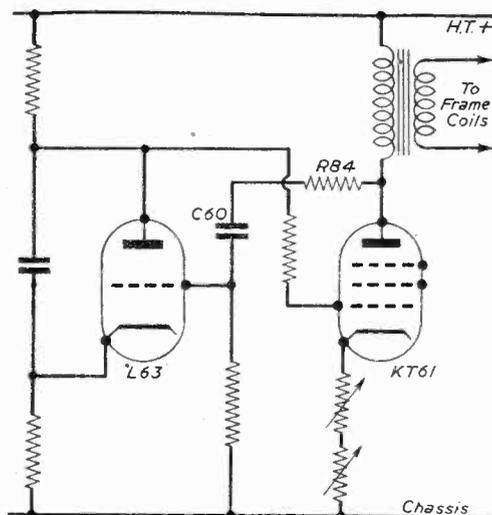


Fig. 1.—Frame timebase of the BT1091. C60 is prone to failure.

and when this symptom is present open-circuit of these components should be suspected. The trouble is also accompanied by failure of the horizontal form control.

### Unstable Line Hold

Instability of the line hold with changes in picture content often means that the 1 M $\Omega$  resistor (R44) between the grid (pin 1) and chassis of the Z77 sync separator valve (V9) has gone high in

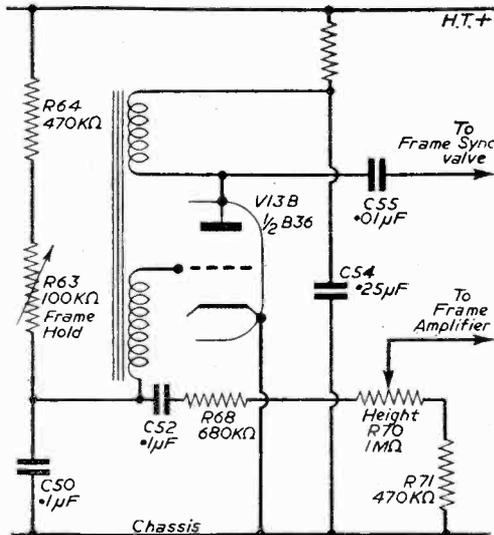


Fig. 2.—The frame oscillator section of the BT2147.

value. Replacement should be made with a  $\frac{1}{2}$  W type.

### Wedge-shaped Raster

Full width at the bottom of the screen, gradually decreasing towards the top of the screen is the symptom typical of shorting turns in one of the line scanning coils. This can be proved by measuring the frame timebase volts across one frame coil section and then comparing the reading with the volts obtained across the other section. Under normal conditions equal voltage readings should be obtained. If they differ, however, replacement scanning coils are usually required, but in some instances the original coils can be kept in service by removing them from the tube, applying insulating varnish in generous proportion so that it seeps well into the windings and then bake them in a very low oven for an hour or so. After this process they should be re-installed on the tube neck.

### Model 2147—White Vertical Band

If the symptom is a vertical series of short, irregular white lines across the left-hand side of the picture, which may be persistent or come and go in a random manner, the trouble is invariably caused by intermittent flashover between the windings in the line output transformer.

Unfortunately, there is little that can be done to alleviate the effect, apart from replacing the

transformer. The winter months tend to aggravate the trouble, particularly if the set is switched on from cold, along with the heating, in a room which has been left unheated for most of the day. Condensation is the responsible element initially, but once a flashover of this nature occurs it rapidly destroys the winding insulation.

On very early models of this series, corona discharge was troublesome between the studs on the line output transformer to which the EHT rectifier valve wires are soldered. In extreme cases, the insulation burns out completely, but where the trouble is less severe impregnating the insulation material with a good quality wax is helpful. Anti-corona grease can also be tried.

### Weak Frame Hold

Value increase of the 0.01 $\mu$ F frame sync coupling capacitor (C55 in Fig. 2) is one cause of this symptom, but if this component appears to be in good order and the frame "tries" to lock near mid-position of the frame hold control, attention should be directed to the diode interlace filter circuit (V11B).

If the frame hold control, on the other hand, is hard towards one side of its travel, the trouble is almost certainly caused by value increase of R64 in Fig. 2. A good tolerance resistor must be used for replacement, otherwise it will be found necessary to try a number of resistors and select one which gives a reasonable balance of the control.

Characteristic alteration of the B36 (V13B) is another cause of the effect, and to save a valve replacement it is permissible slightly to adjust the value of R64, away from the stipulated 470 k ohms, in an endeavour to secure frame hold control balance.

The best frame lock is obtained on this series

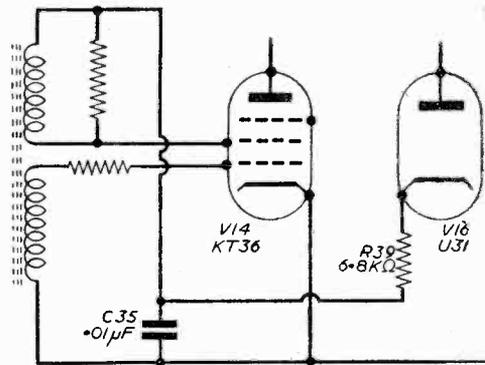


Fig. 3.—Basic circuit of the line amplifier of the BT5145.

by adjusting the hold control until the picture slips slowly downwards and then carefully re-adjusting the control until the picture just locks.

### Model 5144 and Series—Frame Bounce

This model uses the same circuit as the BT2147 for the frame timebase. If frame bounce is accompanied with intermittent decrease in height, the frame timebase coupling capacitor (C52 in

(Continued on page 561)

## BRAND NEW A.M.-F.M. CHASSIS AT £13.6.8 (P. & P. 10/-)




Why buy a F.M. Tuner at the same price? Tapped input 200-225 v. and 226-250 v. A.C. ONLY. Chassis size 15" x 6 $\frac{3}{4}$ " x 5 $\frac{1}{2}$ " high. New manufacture. Dial 14 $\frac{1}{2}$ " x 4" in gold, red and deep brown. Pick-up. Extension speaker, Ae. E. and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gran' Aligned and tested. With valves tone control. Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s. Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit, polished with back, 67/6. 8" x 5" ELLIPTICAL SPEAKER 20/-.

TERMS:—(Chassis) £4.16.8 dep. + 10/- carr. and 6 Mthly. Payments of 30/-, or with Cabinet and Speaker £5.9.2. dep. + 10/- carr. and 7 Mthly Payments of 35/-.

We are specialists in I.T.A. Converters. All our converters give direct switching I.T.A. to B.B.C., have internal power pack, metal rectifier, co-axial plug, can be fitted in 5-10 mins., and need no alteration to your set. ALL AREAS, ALL SETS, ALL CHANNELS 12 months' guarantee (3 months on valves).
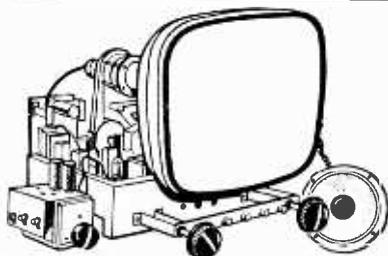
### "READY TO USE" I.T.A. CONVERTER


Separate gain controls. Valves PCF80 and PCC84. Switch positions I.T.A. (1) — I.T.A. (2) — B.B.C. Bakelite moulded cabinet 8 $\frac{1}{2}$ " x 4" x 6". £5.5.0 P. & P. 3/-.



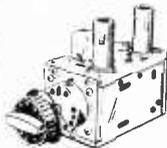
### UNUSED 14in. TV CHASSIS WITH 6 $\frac{1}{2}$ in. SPEAKER AND RECTANGULAR TUBE

TV chassis in working order. 16-19 Mc/s Tunes Channels 1-5 B.B.C. and I.T.A. 8-11. When tuned for local reception only switching is necessary for I.T.A. or B.B.C. To convert to 13 Channel set, special price of 60/- for suitable Cyldon Turret Tuner to customers purchasing this chassis. Includes 2 sets of coils. Carr. and Ins. 20/- extra.


Cabinet for either size with mask and perspex, 60/-, 6 months' guarantee on tube, 3 months' on valves. COMPLETE £30 (17in. tube, £36).



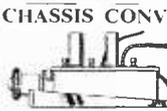**INCREMENTAL TURRET TUNER** by famous manufacturer for 35 Mc/s only; with knobs. Valves PCC84 and PCF80. ONLY 77.6. post free. or valves UCC84 and UCF80.



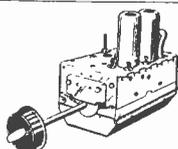
**CHASSIS CONVERTER INTERNAL MOUNTING** Specification as Plinth Converter above; with leads for power supply, etc. Size 9" x 2" x 5" high. PRICE £2.17.6 (2/6 post). Power pack, fully wired with connection instructions 25/- extra.



**CYLDON 16 Mc/s and 19 Mc/s TURRET TUNER** with two sets coils (state B.B.C. & I.T.A. channels). Extra pair of coils, 5/- pr. With knobs. ONLY 77/6 (2/6 post). Valves PCC84 and PCF80 included, or valves UCC84 and UCF80.

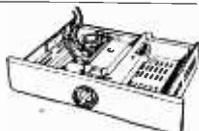
### NOVEL "PLINTH" CONVERTER

Your set stands on this converter giving neat appearance. Size 16 $\frac{1}{2}$ " x 14 $\frac{1}{2}$ " x 3". Valves PCF80 and PCC84. Switch positions I.T.A. (1)—I.T.A. (2)—B.B.C. Separate gain controls. PRICE only £4.15.0 (3/- post), or without power pack £3.3.0, post free.


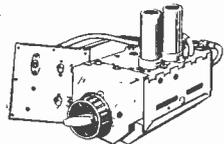
### THE BRAYHEAD TURRET TUNER, £7.7.0, post free.

Complete with booklet and fitting instructions. State set and model no. when ordering.



**NEW SILVERED MICA CONDENSERS.** 50 different values, 10/-, post paid.

**RESISTORS.** 50 different values.  $\frac{1}{4}$  watt to 1 watt. 5/-, post paid.

**I.T.A. AERIALS** clipping to existing mast 1-2" dia. 3-element, 27/-; 5-el., 35/-; 9-el., 55/-; Loft mountg. 3-el., 20/-; 5-el., 27/6; Combined single B.B.C. and 5-el. I.T.A., 75/- with chimney lashings; Co-axial cable semi-air-spaced, 8d. yd. or 20 yds., 12/6; aerial and cable prices carr. pd.

SEND 6d. FOR CATALOGUE.


**BATTERY ELIMINATOR.** Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK96 range). 90 v. 15 mA. and 1.4v. 125 mA., 42.6 (2/6 post). 200-250 v. A.C. Size 5 $\frac{3}{4}$ " x 3 $\frac{3}{4}$ " x 2". Also for 250 mA. 1.4 v. and 90 v. 15 mA. at same price. Please specify which, or state valves.

**PERSPEX UNSCRATCHED**, post 2/- each size. 6 post free; sizes in ins. 16 x 14 x 3/16 clear, 7/-; 15 x 12 x  $\frac{1}{8}$  tinted, 6/-; 17 x 13 $\frac{1}{2}$  x 3/16 clear, 7/-.

Posted Orders to Worthing, please. Delivery by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra.) These terms are applicable to all items except A.M.-F.M. chassis.

All goods are new unless otherwise stated.

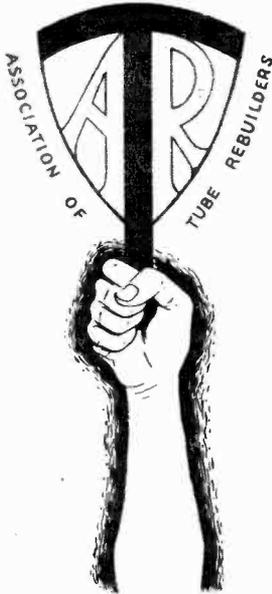**GLADSTONE RADIO**, 25 WORDSWORTH ROAD, WORTHING. Tel.: 235  
58a High Street, Camberley, Surrey. Tel.: 2633; and 3, Church Road, Redfield, Bristol. Tel.: 51207



# SUFFOLK REBUILT TV TUBES

**NOW COST LESS THAN EVER.**

All prices of Suffolk rebuilt C.R.T.'s have now been substantially reduced. New price lists are now available and will be sent on request. For quality ..

*Your Guarantee is this Symbol*

Each rebuilt Tube is fitted with complete new Gun Unit—Immediate delivery—U.K. Carriage FREE and,

**STILL GUARANTEED FOR 7 MONTHS.**

## SUFFOLK TUBES LTD

Write or call for full details :

LONDON'S LARGEST INDEPENDENT TUBE REBUILDERS.

**SUFFOLK HALL, 1-3, UPPER RICHMOND ROAD, PUTNEY, S.W.15. Telephone: VAN 4304, 5267**

**VALVES AND SERVICE SPARES BY RETURN POST SERVICE**

5in. P.M. Loudspeaker Units by Goodmans or Plessey, 17/6 ea. ★ Miniature I.F. Transformers 465 Kc/s. 9/- pair ★ Henley Solon Instrument Irons 25 watts 220/240v., 24/- ea.

★ Aco's Microphone Type 39-1 Pencil Stick, listed 105/-, our price 59/6 ★ Coaxial Plugs and Sockets, 7/d. each part ★ High Resistance Headphones Type CHR, 13/6 pair ★ Cylidon Aerial and Oscillator Coils (All Channels—all Frequencies), 7/6 pair.

★ B.S.R. Monarch UA8 4-speed automatic record changer, £8.19.6 ★ Wafer Switches 3 pole 4-way, 1 pole 12-way, 2 pole 6-way, etc., 3/- each ★ Empty Tape Spools 3in., 3/-, 5in., 3/6, 5 1/2in., 3/9, 7in., 4/3 ★ Vestinghouse Metal Rectifiers, 14A96, 14A97, 14A100 all 17/6 each ★ Philips Receive Trimmers 0/30 pF, 10d. each ★ Belling Lee 7-pin Flexible Plug Fixed Socket, 2/- ★ B7G B9A Anpenol Valveholders with or without skirt, 9d. each ★

Screening Cans, 6d. each ★ Crocodile Clips, 3d. each ★ Heater Transformers Mains Primary 6.3v. 11 amp., 6/9, 6.3v. 3 amp., 10/- ★ 2 Gang 500 pF Condensers Standard or Midret, 7/6 each ★ Solid Dielectric Tuning Condensers 300 pF or 500 pF, 4/6 each.

Coaxial Cable semi-airspaced 75 ohms, 6d. yard ★ Headphones CLR Low Resistance, 7/6 pair ★ Paper based Recording Tape 1.200ft. on plastic spool, 12/6 ★ TRF Kit complete in every detail, £5.10.0, circuit and shopping list 1/- ★ STC Rectifiers RM1, 5/6, RM2, 6/9, RM3, 7/6, RM4, 16/6.

**TERMS:** Cash with order or C.O.D. Postage and Packing charges extra, as follows : Order value 10/- add 1/3 ; 20/- add 1/9 ; 40/- add 2/6 ; 25 and over 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue.

Persons! Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

**103 LEEDS TERRACE, WINTOUN STREET, LEEDS, 7.**

## ALPHA RADIO SUPPLY CO.

**VALVES GUARANTEED ALL TESTED BEFORE DISPATCH**

CY31	16/7	KT66	17/6	5U4	8/-
DL33	13/6	KTW61	8/-	5Y3GT	8/-
DF96	10/6	N78	19/11	5Z4	11/-
DF96	10/6	OZ4	5/6	6A7	13/-
DK96	10/6	PCC84	10/-	6AL5	6/6
DL96	10/6	PCF80	13/6	6AM6	9/-
EB33	7/6	PL81	16/-	6P6G	7/6
EB34	10/-	PL82	8/6	6F1	14/-
EBF80	10/6	PX25	12/6	6P13	14/-
ECC84	10/4	PY80	9/-	6P15	14/-
ECC95	9/6	PY81	10/-	6KTG	5/-
ECH42	10/6	PY82	9/-	6R3G	8/6
ECH81	11/-	PEN4VA	15/-	6L6G	9/-
ECL80	13/6	PEN25	6/-	6L18	15/-
ECL83	14/6	PEN4A	15/-	6Q7G	9/-
EF39	7/6	SP41	3/-	6SN7	7/6
EF40	14/6	SP61	9/-	6SL7	8/-
EF41	9/9	TP25	26/6	6U4	14/-
EF42	14/-	U14	8/6	6V6G	7/6
EF50	4/-	U25	14/6	6V8GT	7/6
EF80	9/-	U191	11/6	6X5G	7/-
EF86	14/6	UCH42	10/6	12AT7	9/-
EL41	11/-	UL41	10/-	12AU7	8/-
EL42	12/-	VU39	8/9	12AX7	9/-
EL84	10/6	X78	15/6	12C8	9/-
EM80	10/6	1C5	12/6	25A6	11/6
EY51	13/6	1H5	10/6	25L6	10/-
EY86	13/6	1N5	10/6	25Y5	9/-
EZ40	9/-	1R5	8/6	35L6	9/6
EZ80	8/9	1S5	7/6	35Z4	8/-
GZ32	12/-	1T4	7/-	35Z4	8/-
HL23DD	8/6	384	8/-	42	8/-
KT33C	10/-	3V4	9/-	40	8/6

**OUR 1959 FULLY ILLUSTRATED CATALOGUE** of components and accessories—invaluable for enthusiasts and engineers—is now available. Send 1/- in stamps for your copy.

T.R.S. Circular flexible, 20/- coil ★

Crystal Diodes, 1/- each ★ Aco's Mic. 33-1 Desk or Hand Microphone, listed 50/-, brand new and boxed, 29/6 ★ TRF Coils aerial and HF coil with circuit, 7/- pair ★ Pointer Knobs available cream, white, black or maroon, 9d. each ★ Elliptical Speakers, 7in. x 4in. by Plessey, 10/6 each ★ Multi-ratio Output Transformer Optimum loads 3.000 to 12.000 ohms, 5.9 each.

5in. Loudspeaker Unit 3 ohms impedance with a Matching Output Transformer suitable for 6V3, brand new but soiled, offered at a Special Price of 11/6 each ★ American Type T30 Throat Microphone complete with strap and plug, 3/- ★ Monarch UA12, the DeLuxe 4-speed automatic record changer, £9.9.0 ★ Yama Soldering Iron, Instrument Model 230/270, 40 watts, 16/9 ★ Garrard 4-speed Single Player fitted with the GC2 cartridge, £6.19.6 ★ Charger Rectifiers Bridge type 12v. 1 amp., 4/3, 2 amp., 7/-, 3 amp., 10/-, 4 amp., 12/6, 6 amp., 15/9 ★ Charger Transformers, Universal Primary Secondary 2, 6 and 12v., 2 amp. version.


Celestion 8in. x 5in. Elliptical Loudspeaker Hi-Flux Model, 25/6 ★ Plessey 10in. x 6in. Loudspeaker Unit, 25/6.

**LINE OUTPUT TRANSFORMERS**

Type	Used in	Price
No.	Model Nos.	
L04	Pye V4-V7-VT4-VT7, Pam 906-909 852-853-858, Invicta 118-119 120	55 2
L024	Cossor 927-932-929	58 8
L017	Alba T372, T472, T732B, T392, T492-9872B, TR9872, U1253	43 2

Value 10/- add 1/3 ; 20/- add 1/9 ; 40/- add 2/6 ; 25 and over 3/6.

# Servicing Television Receivers

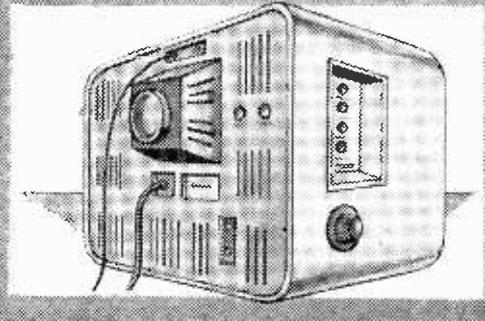

No. 47.—THE FERGUSON 306T AND 308T

By L. Lawry-Johns

THE 306T is a 17in. table model with a Mullard MW43-69 tube. The 308T is a 21in. model with a Mullard MW53-20 tube. They are not intended for use in the extreme fringe areas. The chassis are identical using a turret tuner and A.G.C. derived from the sync-separator input.

### Line Linearity and Width

There are several features which require explanation. One is the width adjustment which also controls the line linearity. This lever is situated on the upper right-hand side. Width is adjusted by moving the lever forward or backward about its pivot. Linearity is adjusted by moving the lever vertically so that the pivot is moved up and down. The adjustments are necessarily interdependent. The picture quality control is provided to vary the video response of V5 as in certain areas, especially in Scotland and Wales, the Band I signals require extra video compensation to avoid smearing and lack of detail. The method employed is simply to increase or decrease by plug and socket adjustment the amount of capacity in the video amplifier cathode circuit.

### Frame Linearity

There are two frame linearity controls. Normally only the lower will need adjustment as this affects the overall linearity, i.e., even spacing of scanning lines over the whole of the picture. The upper pre-set control only affects the extreme top of the picture and will not normally require adjustment.

The turret tuner is not quite so conventional as may be thought. To remove the outer channel selector and inner fine tuner knobs, the centre screw must be removed. Hold the fine tuner knob while doing this to prevent pressure being transferred to the "works." Once the centre shank is unscrewed the outer knob may be pulled off. If it is found that this outer knob when turned does

not rotate the turret, a new spring clip will be required. As the turret tension is considerable the clip often breaks leaving the knob to revolve on the spindle without actuating it.

### Gain Control

The gain control varies the cathode bias of the PCC84 valve and while this control is being adjusted, it is normal for signs of instability to be evident and this must not be regarded as a fault.

The rear cover continues under the cabinet and slides in grooves. It is secured to the rear by sliding clips, not by the screws, which only secure the clips. The screws should only be slackened, not removed when the rear cover is taken off.

### Cabinet Construction

The cabinet itself is in two sections; a base-board upon which the chassis is mounted and a cabinet shell which is removable. This is detached from the baseboard by first removing the rear and bottom cover, unplugging the speaker

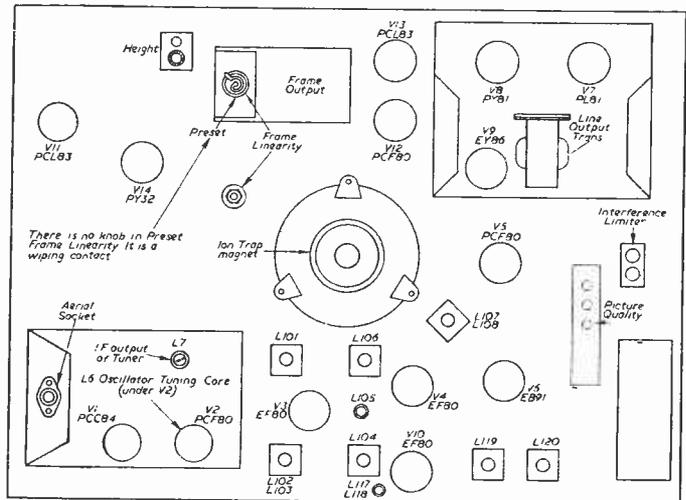


Fig. 1.—Rear view of chassis.



Check V13. If the lower part of the picture is folded up check C158 (.1  $\mu$ F).

Where the top is compressed and the linearity controls do not correct, check C158 (.1  $\mu$ F) and linearity circuit components.

### No Picture, Sound Good

Advance brilliance. If there is no illumination or raster check the upper right side EHT section. Test for spark at EY86 top cap. If there is a healthy sizzling spark, change EY86. If the EY86 fails often, use a TY86F which has a different heater characteristic.

If the symptoms remain, or the line timebase whistle is ragged and the EY86 anode spark subdued, suspect a short in the tube itself and remove the anode clip or if more convenient remove the base socket and short pins 1 and 12 to preserve heater continuity. If now the EY86 lights up and the anode sparks normally with a smooth timebase whistle, rewire C.R.T. base for tetrode working.

If there is no spark and the line whistle is absent, check PL81 valve, then V5 PCF80.

### Isolating Transformer

If a raster (bright) can only be resolved at *minimum* brilliance, check C.R.T. for heater-cathode short and instal 6.3 heater isolating transformer, removing the existing leads to pins 1 and 12 and shorting these leads together to preserve heater chain continuity. Where the brilliance control works up to a point and then causes the picture to balloon out and fade, suspect failing EY86 (or TY86F), but bear in mind that a misplaced ion trap magnet on the rear of the tube neck can produce exactly the same effects.

### Ion Trap Magnet

This may require explanation. The function of the ion trap magnet is to direct the electron beam through a small hole in the anode plate. If it is displaced, the electron beam will collide with the anode causing a heavy flow of current without the screen being fully illuminated. The EHT rectifier (EY86) is still expected to pass this current although the majority of it is not exciting the screen at all. Therefore, an abnormal current has to flow in order to provide some illumination and the EY86 and its supply are not designed to cope with it. Thus a displaced magnet can give rise to the symptoms normally attributed to a weak EY86. This, of course, is true of any other receiver employing an ion trap tube.

### Lack of Width

Where the above symptoms are accompanied by a lack of width, however, the cause is different. If the width is lacking at normal or low brilliance, check the PL81, PY32, PY81 and the 2.2 k $\Omega$  resistor to pin 8 of the PL81 in that order.

The previous symptoms can be added, as the EY86 will be inadequately supplied and will not be capable of operating correctly.

### No Picture, No Sound

Raster resolved when brilliance is advanced. Check tuner valves PCF80 and PCC84 (in that

order), then the EF80 to the right. The PCF80 should also be suspected when BBC can be received but not ITV, i.e., Channels 1-5 quite normal and nothing on Band III. When the Band III signals become seriously detuned so that the fine tuner will not bring in the sound or alternatively the picture, replace the PCF80. Where the detuning is slight so that sound on vision is experienced and the fine tuner is at one end of its travel, check the alignment of L6, the oscillator coil core, adjusted from beneath the tuner, roughly under the PCF80.

### Hum on Sound, Sound on Vision, or Both

Reduce the gain control setting or instal aerial input attenuator. These symptoms only occur normally in areas of high signal strength.

Advancing contrast, gain or brilliance causes a silken effect on highlights with whites at a uniform grey. Suspect tube emission and change tube. Send it for rebuilding or try a boost voltage on the heater which may help matters for a limited time.


Where the picture signal is weak, but the raster resolves quite brightly, check valves and 10 k $\Omega$  2 watt anode load resistor of V5 (video amplifier section), if it is known that the aerial input is in order and a good picture has previously been received. Also check the OA70 vision detector crystal diode contained in the L107/L108 I.F. transformer.

Coil L101 is the adjacent channel rejector. L105 is the sound I.F. rejector. L101 is adjusted to reject 33.15 Mc/s (min. vision) and L105 to reject 38.15 Mc/s (min. vision).

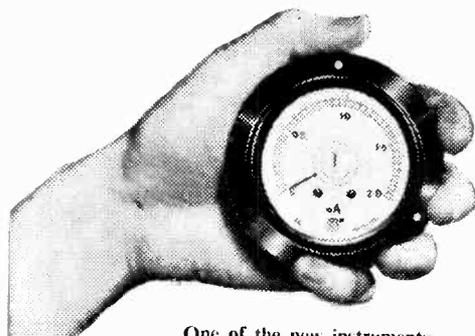
## New Miniature Instruments

A RANGE of panel mounting 240 deg. scale miniature instruments with 2in. and 2½in. dials, is announced by Crompton Parkinson Ltd. The instruments have a limit of inaccuracy of 1 per cent, and have twice the scale length of 90-100 deg. short scale instruments of similar dial diameter. Nine of the 3¼in. scale (2in. dial) instruments can be mounted in a 6½in. square panel space.

They are available in either moulded plastic or sealed die-cast metal cases. Supplied in the metal case form, the instruments withstand the Admiralty 200g shock test. (Crompton Parkinson Ltd., Crompton House, Aldwych, London, W.C.2.)



One of the new instruments.

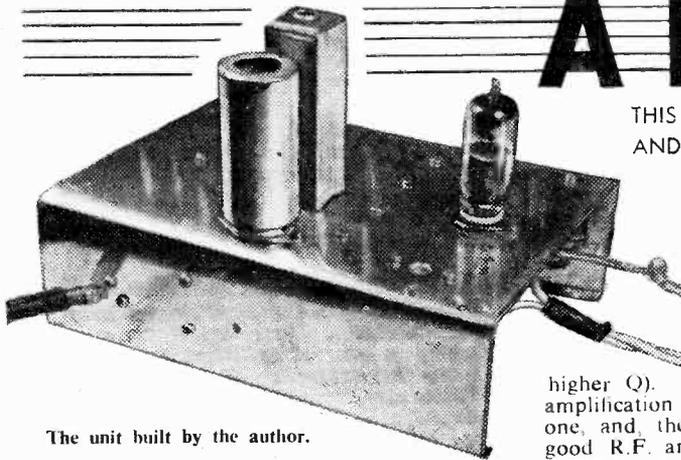

The unit built by the author.

**A**LTHOUGH at present there are no experimental test transmissions on Band V, the construction of this converter will give the amateur valuable experience in operation at frequencies of the order of 600 Mc/s. It is hoped to publish another article in the near future describing a suitable signal generator for Band V frequencies which will enable testing to be carried out in the absence of experimental transmissions.

#### Noise

The first consideration, at 650 Mc/s, is to minimise noise. The usual method, in conventional receivers, is to employ a stage of R.F. amplification—sometimes more than one stage—before the frequency changer. The reason for this is that since the mixer operates necessarily at a lower conversion conductance than the same valve used as an amplifier (the value is usually less than one third gm) for a given output at I.F. the noise is proportionately greater. For example, measurements at 200 Mc/s with a 955 valve show an equivalent noise resistance of 1,360 ohms,  $gm = 2 \text{ mA/V}$  when used as an R.F. amplifier. The same valve, used as a triode mixer at 200 Mc/s had a conversion conductance of  $625 \mu\text{A/V}$  and an equivalent noise resistance of 6,700 ohms. The noise had gone up by 4.9 times and the mutual conductance had decreased by a factor of 3.3.

At high frequencies, such as are encountered in Band V, the figure is much worse. Experiments conducted at 600 Mc/s show that unless the gain of the R.F. amplifier before the mixer stage is at least six, more noise than signals is introduced and it is actually disadvantageous in most circumstances to use such an R.F. stage at all.

#### R.F. Amplification

With the above in mind, measurements were carried out to see whether enough R.F. amplification could be achieved with easily-obtainable valves. The 955 was again the obvious choice, though some doubt was felt at the outset about

# A Band V

THIS UNIT IS INTENDED AS AN EXPERIMENTAL  
AND A SILICON DIODE

its capabilities. From experience with a 600 Mc/s oscillator it was apparent that though it was possible for a selected 955 to oscillate at 670 Mc/s this was the upper limit; even with silver-plated Lecher wires (which have high Q) or a silver-plated coaxial assembly (which has an even higher Q). In other words, at 670 Mc/s, the amplification had dropped to only a little over one, and, therefore, it was unlikely to make a good R.F. amplifier at such frequencies.


There was, however, the possibility that by using the triode in a grounded-grid circuit useful gain could be achieved. This also was found to be useless: the measured gain at 600 Mc/s was 2.2—far too low to be of any use from the point of view of noise-reduction. The 955 was regretfully given up.

Experiments are still continuing, however, using other valves, and it may be possible to report progress at a later date. Meanwhile, the R.F. front end described here is usable in the optical line of sight from the transmitter, with reasonable results.
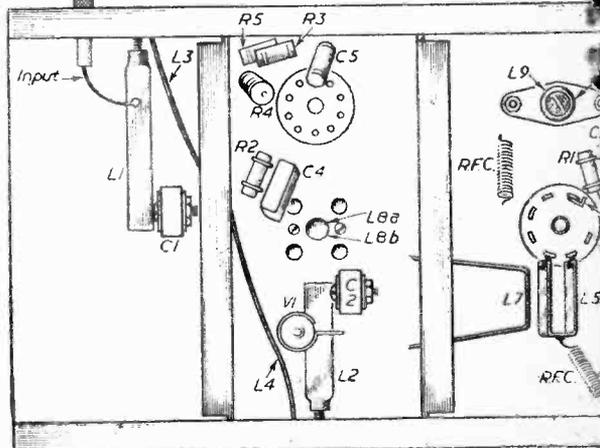
#### The Input Circuits

The writer has experience of the difficulty of obtaining suitable components designed exclusively for the ultra-high frequencies, and has, therefore, attempted to use more conventional ones wherever possible. This has necessarily involved some artifices here and there and these will be mentioned in due course.

Not only must the input circuits resonate without much loss to the U.H.F. frequencies received, but also they must prevent, as far as possible, radiation from the



# Converter

TAL FRONT-END AND USES TWO VALVES

By R. B. Archer

oscillator. For this reason, a filter input circuit has been used. It is not exceedingly efficient, but improves matters to a worth-while extent, while causing little loss in signal strength.

### The Crystal Mixer

Essentially the crystal, whether of silicon or germanium, operates as a mixer by introducing non-linearity into the wave-forms imposed on it. In this it resembles a pentode, operated under non-linear conditions, as, for example, when both signal and locally generated oscillations are


reasons. First, a large crystal current—derived, of course, chiefly from the rectification of the local oscillator output—causes a large D.C. bias across the crystal and this tends to cause a serious increase of noise. Secondly, too small a current causes a large loss of signal—"conversion loss." The correct compromise is usually about 0.2 to 0.4 mA. This, fortunately, is relatively easy to arrange.

### The I.F. Amplifier

Because there is no amplification before the I.F. amplifier, it is essential that a low-noise first I.F. stage is employed. The oscillator and crystal introduce some noise; this cannot be avoided altogether. The I.F. amplifier must, therefore, introduce as little as possible, and the usual pentode is not good enough. For this reason, a cascode stage of simple design has been incorporated. Such a stage introduces almost as little noise as a triode. While in this circuit it is a necessity; in more usual TV practice a cascode stage is not needed in the I.F. amplifier. For the R.F. stage it is, however, quite rightly very popular. Fig. 1 shows the theoretical diagram, which is of conventional appearance because the usual symbols for inductance, capacitance and so on have been employed. The actual construction is, however, far from conventional in appearance, as the diagram of the underside of the chassis shows. The reason is simply that, at Band V frequencies, the inductances reduce to flat strips of copper or plain lengths of wire. Actually, L6 disappears from view almost completely—reduced to the length of the contacts in the valveholder.
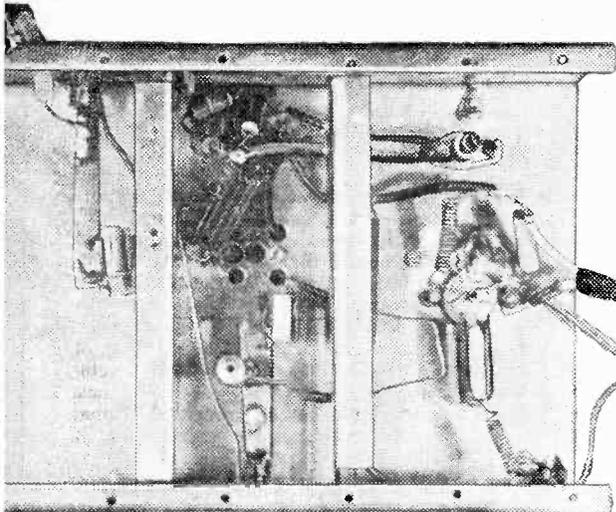
### Circuit

The mixer, oscillator and first I.F. stage together comprise the "converter," which is designed to feed into a suitable sound/vision double I.F. amplifier. The oscillator consists of a tuned-anode, tuned-grid stage, using a 6J6 operating at about 620 Mc/s. This gives vision and sound I.F.'s of 34.25 Mc/s and 39.75 Mc/s respectively, which feed nicely into a modern I.F. amplifier, retuned somewhat as necessary. The 6J6 is operating near its limit at 620 Mc/s



Underchassis view of the converter. (Below)—Diagram for the identification of parts shown in the illustration above.

impressed simultaneously on its grid—the usual practice in television and V.H.F. technique. The crystal, of course, does not amplify—there is actually a loss. Both crystal and pentode introduce noise. With the valve, however, the input and output impedances are relatively large, although at very high frequencies the input impedance does tend to diminish very appreciably. The crystal, however, has relatively a very low impedance, and behaves more like a transistor than a vacuum valve. For this reason it is necessary to match the circuit to the crystal so that correct impedance is presented by the circuit connected to it. Matching is usually accomplished by some kind of transformer; in the circuit described here an auto-transformer is used.

It is also important in using a crystal to ensure that the crystal current is of the right order of magnitude. This is not only to prevent damage by excessive current but also for the following

COMPONENTS LIST	
V1—Silicon crystal diode.	V3—PCC84.
V2—6J6.	R4—100 K.
R1—22 K.	R5—100 K.
R2—100Ω.	
R3—0.22 M.	
L1 to L9—See text.	
C1—5 pF max. trimmer.	
C2—5 pF max. trimmer.	
C3—5 pF Erie ceramic N750 K.	
C4—	
C5—	
	.01 pF Mica or ceramic.

and consumes 24 mA at 200 volts; for this reason it is mounted so that good ventilation is assured and it is not enclosed in a screening can. The rating of the valve is 3 watts anode dissipation, and it is undoubtedly overrun. It seems, however, to show no signs of distress. This valve was selected as being easily available cheaply.

With the tuned-anode tuned-grid circuit used here, the valve capacitances (which limit the maximum frequency obtainable) are in series with each other. Moreover, the cathode does not carry R.F. and so cathode lead inductance is not a limiting factor.

### Inductances

Fig. 2 shows the details of the circuit. L5 consists of a strip of silver-plated copper, 22 s.w.g., 1.5 cm wide and 2.6 cm in length, folded into a "hairpin," the sides of which are 0.6 cm apart internally. It is soldered direct to the two anode pins of a P.T.F.E. or ceramic valve-holder and is self-supporting 1.0 cm above the chassis. The mid-point of the "hairpin" is connected direct to the R.F. choke which consists of 17 turns of 22 s.w.g. tinned copper wire, spaced wire diameter, wound on the shank of an  $\frac{1}{4}$  in. drill as a temporary former. From the H.T. end of the choke a mica condenser of capacity 100 pF is taken to chassis by the shortest route (this is not shown on the circuit or chassis diagrams, but can be seen in the illustration of the chassis).

The inductance L6 consists only of the valve pins and the sockets in the valve-holder. A piece of 22 s.w.g. wire is soldered across the socket tags as near the valve-holder as possible, and the R.C. network C3R1 is attached between its mid-point and chassis by the shortest route.

### Input Filter

For the signal input filter the inductances L1 and L2 each consist of a strip of silver-plated

copper 22 s.w.g. 0.6 cm wide and length 5.6 cm from the C1 or C2 end to the chassis, where they are secured by means of a brass screw and nut. C1 and C2 are preferably of the miniature type. The author, however, used a couple of Government surplus ceramic mounted air-spaced variable trimmers, each reduced to two moving and one fixed plates. The capacitance should be about 0.2 to 4.0 pF.

The aerial input coaxial lead is brought direct through the chassis, no socket being used, otherwise its capacitance (which is rather large) will have to be tuned out. (If a socket is used, a 3 cm length of 22 s.w.g. wire will have to be connected, so as to appear to short-circuit the input.) The coaxial inner conductor is soldered to L1 at a distance of 2.8 cm from the chassis end, and the "outer" of the coaxial cable soldered to the chassis end of L1.

L3 and L4, together with the connecting link consist of a piece of 18 s.w.g. silver-plated copper wire soldered to the chassis ends of L1 and L2. The wire is run close to L1 and L2 for a short distance—the adjustment is made so as to obtain best signal-to-noise ratio in use—and the wire passes through a B7G size hole in the screening partition wall. The fixing must be rigid, and the wire is then self-supporting.

### Mixer

V1 consists of a silicon crystal diode, preferably a "low-noise" type—the author bought a surplus CV291 for 2s. 6d. Clips are fashioned from brass strip, silver-plated, to hold this diode. One clip is soldered to L2 at a distance of 3.7 cm from the chassis end; this gives best matching for the CV291, but some adjustment may be needed if other types are used.

Inductance L7 consists of a piece of wire connected to the other crystal clip, brought through the screening partition and run close to L5 before passing into the I.F. transformer can. L8a consists of 9 turns of 28 s.w.g. enamelled wire, close wound directly on top of L8b. The latter is of 16 turns 28 s.w.g. enamelled wire on a 0.3 in. former, with purple-coded dust core. The reader may have suitable I.F. coils by him; if so, a matching winding of about one half the turns is about right, but may need some adjustments for the type of crystal used. Since no tuning for the oscillator is provided, it may well be necessary to modify the I.F. amplifier to tune to whatever I.F. is produced. If the oscillator frequency is determined by means of a two-wire transmission line, the I.F. can be forecast to a

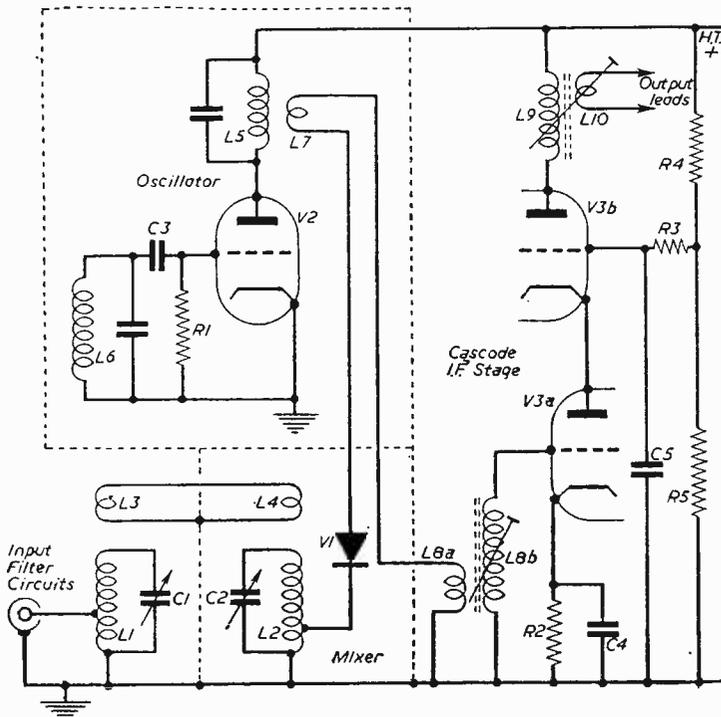


Fig. 1.—Circuit diagram of the converter.

megacycle or two: the I.F. amplifier can then be tuned to suit. A small adjustment of oscillator frequency can be made by judicious alteration of the position of L5 relative to the chassis, as this affects the capacitance of the anode circuit.

**Setting Up the Circuit**

The following adjustments will have to be made to bring the circuit into alignment. (a) L1 and L2 will have to be tuned, each by its capacitor

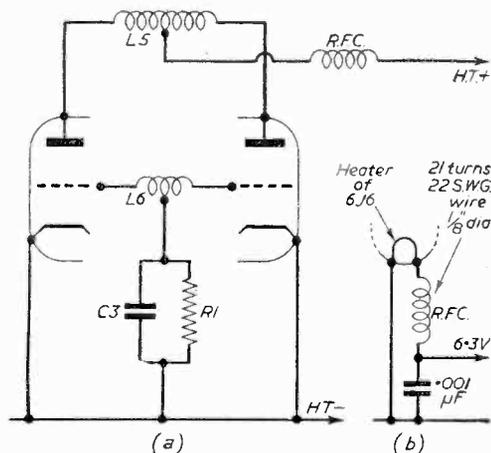


Fig. 2(a) (Left)—Tuned-anode, tuned-grid oscillator circuit.

Fig. 2(b) (Right)—The heater supply circuit.

(C1 and C2); (b) the oscillator frequency may need slight adjustment; (c) the tapping-point of the aerial input on L1 may need altering; (d) the coupling arrangements L3 and L4 will need adjustment for best results; (e) the crystal tapping point on L2 will need slight alteration; (f) the tuning of L8 and L9 will have to be made to correspond with that of the I.F. amplifier in use. This is not dealt with here, as it is thought that an experimenter capable of tackling U.H.F. circuits will be able to manage that for himself. It should be noted that in the underchassis illustrations L10 (output coupling coil) is not shown, as the constructor may wish to vary it for his own use. The inductance L9 is the same as L8b, except that it is not screened. About three turns tightly coupled to the coil—over-wound on the H.T. + end will match the coil to 80 ohm coaxial cable. (g) The position of L7 relative to L5 will need to be varied to get good "conversion" without undue noise. The minimum coupling should be aimed at as this assists in ensuring good oscillator stability.

**Alignment**


First of all, the input circuits

should be aligned. For this, an oscillator working at about the right frequency is needed, and this is not a simple matter to arrange. The stray radiation from an oscillator working on Channel 8 may be found useful—the third harmonic will be at 673.2 Mc/s. This applies to television receivers having I.F. of 34.65 Mc/s (vision). For sets with an I.F. of about 16 Mc/s, the third harmonic of the Channel 10 oscillator (about 64.8 Mc/s) may also be used. It would be better, however, to construct a separate oscillator operating on 657 Mc/s or, more practicably, on 328 Mc/s. This may be a simple Lecher-line oscillator. The distance between the minima on the transmission lines should be 45.7 cm and for constructional purposes the anode and grid lines could start off at 25 cm each, gradually reducing the length until the exact frequency is achieved. The "acorn" works well at this frequency and a strong second harmonic is radiated, which is easily picked up.

It will be seen from the photograph that holes to secure a cover plate are provided: it is fixed by a large number of self-tapping screws. This cover plate should be on for the adjustment of C1 and C2; the latter condenser is reached by way of a hole in the screening partition. When the input circuits have been adjusted for best results, the aerial tapping point may then be altered for maximum signal strength.

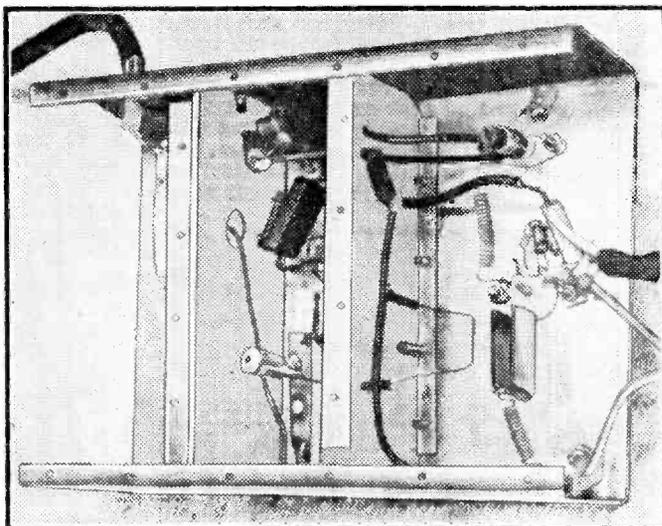**Crystal Tapping Point**

Next, the crystal tapping point may be adjusted; each variation in position may need readjustment of C2 and at the same time, the position of L7 should be brought to the optimum. Variation of the placing of L7 will alter the oscillator frequency a little, and the position of L5 relative to the chassis must then be changed until the signal is back in tune. It may be realised that these adjustments require patience; nevertheless, it will be found straightforward enough.



Another view of the underchassis which shows more clearly the wiring of V3.

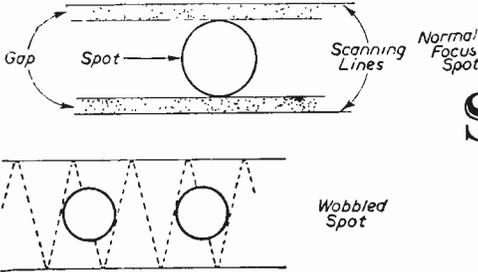


Fig. 1.—With a normally focused spot, there are gaps between the scanning lines. If the spot is “wobbled,” the gaps are filled.

READERS who have not tried out a spot wobble unit may like to experiment with the one described here. Any TV R.F. pentode can be used, such as the 6F1, 6F13, 6BW7, EF91, EF80, EF50 (VR91), or triodes such as 6L18, EC52 (VR137), etc. When using the

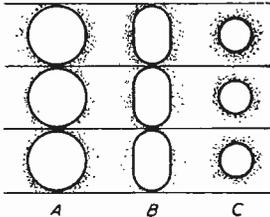


Fig. 2(a).—If the spot is defocused, the gaps disappear, but definition is impaired. (b) Improving horizontal definition. (c) A correctly focused spot leaves gaps.

unit, definition is slightly impaired, just as it is when a filmed telerecording is shown, as this usually is spot wobbled before photographing.

**Operation**

As is well known, a spot moves across the screen from left to right, and as the tube fluorescence has a medium persistence (afterglow) horizontal lines are traced. When the spot is small and the trace is sharply focused, gaps will appear between the lines. If an alternating current, at a frequency greater than the line frequency, is applied to a pair of coils on the tube neck, the spot is made to move rapidly in a vertical direction, as well as horizontally, thereby filling up the gaps between the lines (Fig. 1). The ideal spot size for an inconspicuous line structure is one

# Building a Spot-wobble Unit

FILL IN THE GAPS BETWEEN SCANNING LINES WITH THIS ONE-VALVE UNIT

that fills the gap completely in a vertical plane (Fig. 2(a)), but with this size and type of spot, definition would be below standard. If good definition is required in the horizontal plane, the spot should be small in horizontal diameter (Fig. 2(b)). When the spot is correctly focused for the best definition the spot is reduced in size both vertically and horizontally and the inevitable gap appears between the lines (Fig. 2(c)).

Before attempting to vibrate the spot in a

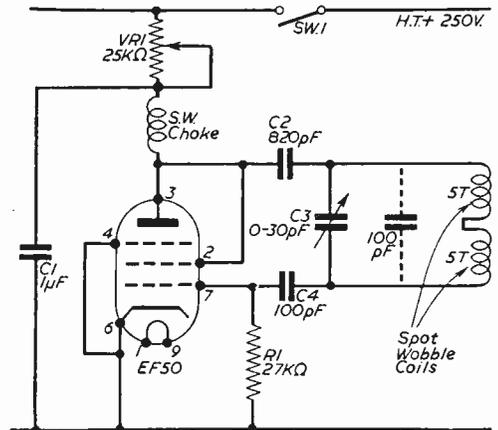


Fig. 3.—Circuit of the oscillator using an EF50.

vertical direction, particular attention must be paid to the picture definition. If this is as perfect as possible, the slight deterioration in picture quality caused by the vibrating spot will be quite bearable.

**Defocusing**

It has been said that deliberately defocusing the spot will fill the gap between the lines and have the same effect as a spot wobbler. However, defocusing with older tubes completely spoils the definition at the sides of the picture. In any case, it is not possible to defocus some of the latest models as no external control is provided.

Low EHT enlarges the spot size, so if the picture is overscanned or dull, or has an exaggerated expansion on operating the brilliance control, it would be wise to check over the line timebase valves and voltages.

**Interlace**

Prominent line structure is sometimes caused by poor interlacing and may be another reason

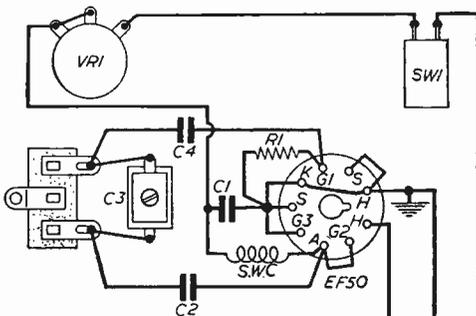


Fig. 4.—Wiring diagram. Note: Earth the valve holder spigot. LT+ HT- H.T. LT- +

for wanting to fit a spot wobble unit. There is no point in fitting the unit if interlacing is bad. The article, "The Problem of Interlace," which began on page 506 of the May issue and which is concluded in this issue, will be of assistance if it is considered necessary to improve the interlace.

### The Circuit

The spot wobble unit (Figs. 3 and 4) consists of a triode-connected pentode oscillator, the output of which is fed to a pair of deflector coils mounted on the tube neck adjacent to and at the rear of the existing line and frame scan coils. As these deflector coils are fitted between the scan coils and the focus magnet, it would be wise to check that there is sufficient space before building the unit. In some cases it may be necessary to fit the coils partly inside the focus magnet and picture centring assembly. As the coils lie flat and take up a very small space it is usually possible to do this.

The frequency at which the oscillator works is important; it must be at least 9 Mc/s, as if it is less, a wavy pattern will be present on the line

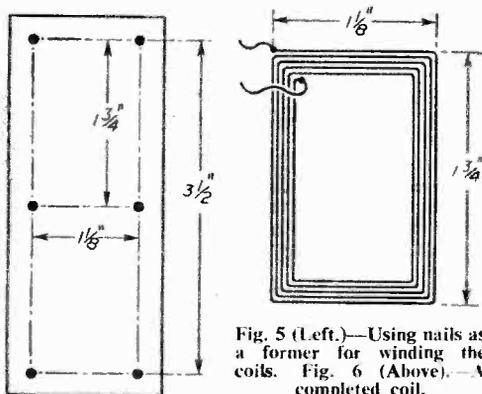


Fig. 5 (Left).—Using nails as a former for winding the coils. Fig. 6 (Above).—A completed coil.

structure when the raster is correctly focused. There is also the problem of seeing that the oscillator frequency or its harmonics do not fall within the receiver's R.F. or I.F. channel. These problems could be forgotten if a frequency greater than 39 Mc/s were used, but then the frequency losses would be much greater and would affect the efficiency of the unit, which is designed to oscillate around 12 Mc/s (25 metres). Trimmer C3 across the spot wobble coils will allow the frequency to be varied so avoiding any frequency beating which may occur in individual receivers. The TV screen should be watched while setting this trimmer.

The potentiometer VRI is rotated to a position where the lines just merge; any further increase will spoil the definition. The switch SW1 is a necessity and allows the unit to be switched off so that the focus control can be correctly set for best definition.

### The Coils

The quickest way to wind the coils is to make a rectangular former, consisting of a small piece

of wood with four shoe nails hammered in about  $\frac{1}{8}$  in. (Fig. 5). The nail heads should be snipped off and the measurement round the outside of the nails should be  $1\frac{1}{8}$  in.  $\times$   $1\frac{3}{4}$  in. The two coils require five turns each of 26 or 28 s.w.g. enamelled wire and are both wound in the same direction (Fig. 6). The five turns are wound carefully side by side and before slipping them off the nails a small band of transparent tape should be stuck to each of the four sides to keep the turns in place. The tape should be wound round once only, as bulk must be kept to a minimum for ease of fitting.

The coils are shaped by pressing them round the tube neck with the  $1\frac{1}{8}$  in. dimensions parallel with the tube axis. In other words, the  $1\frac{1}{8}$  in. measurements lie across the "top" and "bottom" of the tube neck and the  $1\frac{3}{4}$  in. is at the "side" of the neck. If the spot wobble effect cannot be obtained, reverse the connections to one set of coils. Start and finish the windings with both ends at one corner, the corner nearest to the scan coils at the top, as part of the coils will no doubt have to slide inside the focus magnet when they are fitted.

(To be concluded)

## TELEVISION TROUBLES

(Continued from page 550)

Fig. 2) should first come under suspicion. It is as well to be on the safe side and replace this component, since it is difficult to apply an artificial test which is anyway comparable with the operating stress to which the component is subjected.

### Model 5145 and Series—Narrow Line Scan, Possibly Intermittent

Either the B36 or KT36 valve may be to blame, and an emission test of these is first desirable. If they both appear to be reasonably normal, the 47 k resistor in the grid circuit of the KT36 warrants examination. This often increases in value and causes the symptom, and in some cases it tends to become intermittently open-circuit and results in an intermittent reduction in line scan amplitude.

### Hum in Line Timebase

The symptom here often resolves as a raster of considerably reduced width with S-shaped vertical edges; the typical symptom of hum accompanied by suppressed line scan and defocusing.

If the smoothing appears to be normal, indicated by a freedom of hum in the sound channel, the KT36 should be checked for heater-to-cathode insulation and a screen-to-heater short. If this proves to be the case, but a replacement valve fails to provide any horizontal scan at all, attention should immediately be directed to the 6.8 k 1 W. resistor feeding the screen of the KT36 (R39 in Fig. 3).

This will probably be found in a charred condition due to an overload. Replacement of this component, along with the valve will clear the trouble.

(To be continued)

# CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

## 9in. PYE MODIFICATION

**SIR.**—In reply to correspondent C. W. Brooks (see the March issue). I modified an Ekco 9in. TV (TSC30) a few years back. In my case the 50 c/s EHT transformer was burnt out but H.T. transformers (two in number) were O.K. I only modified for EHT off the flyback thus:

Discarded U22 rectifier but retained the M.O. valveholder; removed burnt-out EHT transformer; fitted line EHT Ferroxcube transformer 6.9 kV, costing 19s. 6d. (advertised at 17s. 6d. March issue) and a Govt. surplus VT127 (9s.) which is the Mazda PEN46. I removed the two  $.1\ \mu\text{F}$  EHT smoothing condensers and fitted one  $.001\ \mu\text{F}$  10 kV. The heater and screen supplies were taken from suitable points to take this extra load and the grid of VT127 was tapped into the damping circuit across the line scan coil. The EHT rectifier was a Westinghouse 36 EHT 100, but an EY51 could be used as a heater winding on EHT transformer. —E. BULL (Walthamstow).

## REPLACEMENT DROPPER RESISTANCE

**SIR.**—Your correspondent, J. H. Pope, London N.W.10 (Your Problems Solved, April, 1959) who has been troubled with barretter type 305 burning out in his G.E.C. BT1252, and other owners of G.E.C. sets using the 305, may be interested to know that Messrs. G.E.C. have produced a replacement dropper resistance which can be screwed into the existing 305 holder in a number of their TV models, thus curing this particular trouble.—A. SILVESTRI (Elgin).

## EARLY TV RECORDINGS

**SIR.**—I wonder whether any reader remembers the records of 30-line television pictures which could once be bought. I have often wished that I had bought one when they were offered for sale at that time for 7s. so that I could demonstrate the crude pictures that were obtainable. I wonder whether anyone can suggest a source of supply of a tape-recording of one of these records, as I do not suppose an actual record could now be bought.

I remember that even though pictures were crude, it was possible to recognise faces, although the only one I can recollect now was Lupino Lane. I have appeared once myself on the other side of the cameras at Alexandra Palace in 1948, the programme being "Inventors' Club." There seemed a very cheerful atmosphere in the studios and quite a lot of leg-pulling between the camera operators and our announcer Macdonald Hobley.

I am still using the timebase section of a Baird T26, designed in 1938, with the scanning coil yoke extended beneath the chassis. Most of the original valves are still working, including sound

output, but with a different vision unit and EHT supply and a PRACTICAL TELEVISION Band III converter.—W. E. ANSON (Northfleet, Kent).

## COLOUR TELEVISION DEMONSTRATION

**SIR.**—With reference to a letter from a correspondent, published in your April issue, regarding a demonstration of colour television given at the Radio Hobbies exhibition last November, I feel that there are so many mistakes I must put them right.


Firstly, the colour TV demonstration was not put on by the British Amateur Television Society as your correspondent stated, but by Dr. Moss and his associate Mr. Rodgers of the Bush Colour TV laboratory at Kew.

Secondly, R.C.A. did not supply the line output components; these were manufactured by Dr. Moss at his laboratories and were of original design.

Thirdly, a price figure of £300 was certainly not quoted by anybody in authority. It is very difficult, if not impossible, to price an apparatus of this type at this stage. It must be appreciated that the cost of components is itself no guide,
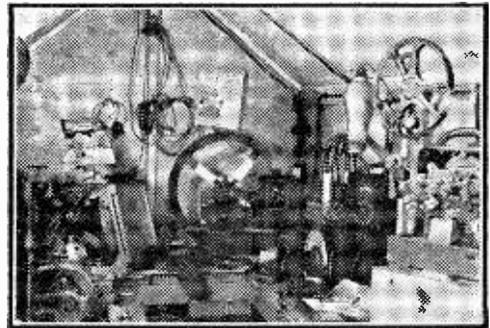
## SPECIAL NOTE

Will readers please note that we are unable to supply Service Sheets or Circuits of ex-government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.



Mr. W. E. Anson's den showing some early TV apparatus. (See "Early TV Recordings.")

since the bulk of the price is made up of development costs. It will suffice to remark, however, that R.C.A. market a 21in. table receiver in the U.S.A. for about £188.

Fourthly, colour TV tubes and components are readily available over here to anybody interested. As an agent for all U.S. tube companies, with the exception of R.C.A. and Sylvania (the latter can, however, be supplied to order) I should be happy to arrange supplies to any interested parties.—B. C. TERRELL (14, Southgate Street, Bath, Somerset).

# Radio and Electronic Component Show

NEW TUBES AND AERIALS WERE THE MAIN TV FEATURES OF THE EXHIBITION HELD IN LONDON FROM APRIL 6th TO 9th

**I**MPROVED components which will lead to increased reliability of all electronic equipment, from television and radio sets to missile guidance systems, were seen at this year's exhibition of the Radio and Electronic Component Manufacturers' Federation. This was the last show of the series to be held at Grosvenor House. Next year there will be no components show, and commencing in 1961 the exhibition will be staged every two years at Olympia. It will then take place in the third week in May.

More compact electronic assemblies are made possible by the use of very small components


Mullard showed a new H.F. cascode double triode for use in television tuners, particularly for fringe area reception. It has frame grid construction and, it is claimed, a very much higher stage gain than previous types as well as an improved noise factor.

A Ferranti valve which was shown entirely eliminates the use of glass. It is of ceramic construction and is claimed to be of particular value where reliability and size are important considerations. This, the UL11, is an R.F. oscillator/amplifier capable of operating at 1,000 Mc/s. with a maximum peak power of 15 kW.

A range of Ferranti cathode ray tubes has been produced to present radar displays of sufficient brightness to be viewed under conditions of high ambient lighting.

Several new valves were shown by the M.O. Valve Company, including the KLS2, a new three-cavity S-band amplifier, giving a C.W. output of 1.7 kW with a power gain of 40 dB. A new convection-cooled travelling wave tube, the TWC 4, for use in the 5,000-8,200 Mc/s range gives an output of 2 watts with a power gain of 40 dB.

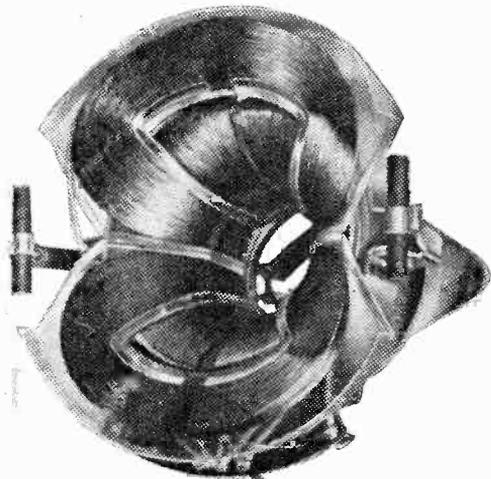The use of silicon rectifiers for television power supplies was featured by several firms, including S. T. and C., Westinghouse and Mullard.



This 110° scanning coil assembly by Elac incorporates a new Ferroxcube core enabling a "pull-back" of 4mm. to be achieved without loss of sensitivity.

which now retain the same reliability as their larger counterparts.

Several exhibitors were showing equipment that foreshadows the opening of new television channels. Turret tuners, for instance, have facilities for switching to the so far unused UHF bands. (Plessey, Brayhead).

## New Tubes


Several firms featured the new 110 deg. television tubes which enable a big-picture television set to be considerably reduced in back-to-front depth. The Mullard 21in. 110 deg. tube shows a saving of more than 8½in. in length compared with the 70 deg. counterpart and 5in. saving over the 90 deg. tube. Siemens Edison Swan and Standard Telephones (Valve Division) were among the other exhibitors of this kind of tube.

The latter also exhibited the PCC89 a high-sloped vari-mu double triode and the PL84, recommended for 110 deg. frame output stages.
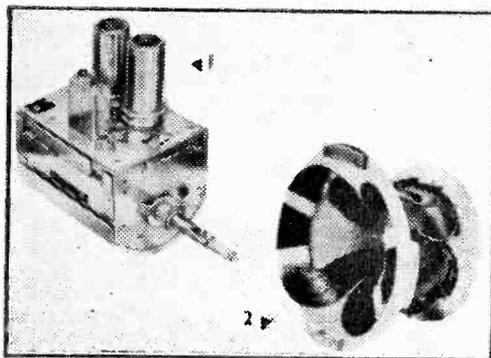
## All-purpose Aerials

There were some particularly interesting developments to be seen in aerials. Antiference Ltd., have redesigned their aerials to reduce the weight and wind-frontage of the arrays, yet without reducing robustness. Elements that automatically click into positions of correct alignment were featured.

A completely new aerial design for operation on Bands I, II and III, with independent directivity and with the facility of adjusting the




An 18 channel Tuner and a 110° scanning coil assembly were among the Plessey exhibits.

Band I signal pick-up to match that of Band III, was introduced by Kimber-Allen Ltd.

Another new aerial introduction comes from Labgear, who exhibited a range of high-gain, small-size dual band aerials which, they say, function on a principle never before used commercially.

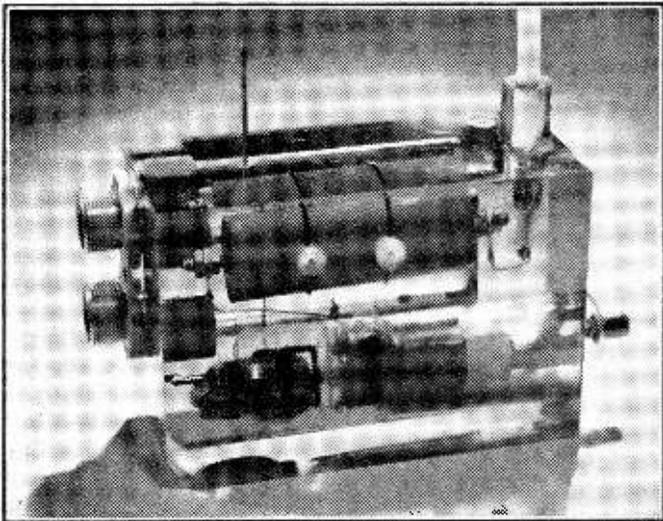J-Beam Aerials Ltd. (who announce price reductions) are one of the firms to show aerials



An E.H.T. block encapsulated in Araldite epoxy resin, shown by Ekco.

with wide-band characteristics, capable of being used at all frequencies in Band III, so providing aerial facilities for a possible third television programme.

The use of common aerials for both television services and V.H.F. radio has called for triplexers, to combine the inputs of the aerials into one coaxial lead and to separate the outputs at the receiver end. Wolsey Electronics, amongst others, showed a triplexer that is equally suitable for use inside or outside.

#### Improved Instruments

There was a wide range of electronic instruments to be seen. A cathode-ray tube

## A Transistor Exhibit

AT the Transistor Exhibition, Messrs. Siemens Edison Swan will show an experimental small-scale crystal growing apparatus enabling very thin base layers to be produced so that the transistors will operate at higher frequencies. Experiments are carried out using as little as 25 grams in the melt and under conditions that permit very good visual observation of the process. A p.n.p. crystal produced by the wafer dip method in this furnace will be shown, a wafer of P type germanium having been used as a seed and a melt prepared containing antimony, gallium and indium. Whilst the crystal was being grown the antimony diffused into the original slice and formed a thin N type layer.

Special properties of the symmetrical transistor

rejuvenator, shown by Labgear Ltd., is of value to television service departments. It measures the cathode emission and applies a controllable excess heater voltage to re-activate the cathode, a meter indicating when the rejuvenation process has been completed.

British Physical Laboratories showed a Megohmmeter (Model RM 185) which has been developed to measure insulation resistance up to 400 million megohms ( $4 \times 10^{11}$  ohms). Dawe Instruments exhibited a "True R.M.S." valve voltmeter which measures the effective value of waveforms other than sinusoidal, giving accurate R.M.S. readings of voltages or currents associated with non-linear circuits.

Whitely Electrical Radio introduced a transistorised field cable test set which enables an operator to locate a break in a multi-wire cable by running a capacitive probe along the outside of the cable. An inductive probe can be substituted for locating shorts between conductors.

An electronic thermometer was the main feature of the Wayne Kerr exhibit. A temperature-sensitive probe is connected by cable to a small battery-operated D.C. bridge measuring circuit. The probe can be positioned some distance from the indicating apparatus. A prototype is now with a geological party operating in New Zealand, who are using the probe for earth temperature measurements at the end of a 1,000ft. cable.

An instrument that quickly and accurately determines the temperature of soldering iron bit or the solder in a solder bath was shown by Multicore Solders Ltd. It is claimed to be particularly useful in work with printed circuits. Known as the BIB solder thermometer it comprises a meter movement connected to a thermocouple, giving direct temperature reading in Centigrade and Fahrenheit, up to 400 deg. C (752 deg. F).

type XS101 have enabled an improved form of modulator to be developed. Considerably less power is required than with diodes, resulting in a lower level of carrier leak. The impedance of the transistor is much lower and no special matching or selection of transistors is required.

Digital circuits operating at 1 Mc/s have been designed for data processing operations. The circuits use an experimental alloy junction transistor with an alpha cut-off frequency exceeding 10 Mc/s and an experimental aluminium-bonded diode.

Production of a germanium p.n.p.n. switch will be demonstrated. Elsewhere applications of the p.n.p.n. switching diode are to be shown, this device having very low resistance in the forward direction and high reverse resistance: such applications include electronic telephony.



# TELEVISION SPARES

**All Makes**

**All Models**

**By return of post**

LINE OUTPUT TRANSFORMERS      FRAME OUTPUT TRANSFORMERS  
DEFLECTOR COILS

LINE AND FRAME BLOCKING OSCILLATOR TRANSFORMERS

ALL POTENTIOMETER AND SLIDER CONTROLS

MAINS DROPPERS

METAL RECTIFIERS

GERMANIUM DIODES

FOCUS MAGNETS

ION TRAPS

E.H.T. CONDENSERS

Our Range of Spares is probably the most extensive in the country and includes all Spares for Tape Recorders, Radio and Record Player Units.

Technical Advice Free. Service Manuals supplied on loan.

Terms: C.W.O. or C.O.D. All Components are supplied at list prices, plus 2/6 p.p.

*Please enclose S.A.E. with all enquiries.*

## NEWBURY RADIO

272, ROMFORD ROAD, FOREST GATE, LONDON, E.7.

MARyland 3100

# YOUR C.R.T. completely FACTORY REBUILT

*New heater and Cathode assembly*

**9 months'  
Guarantee**

COMPARE OUR PRICES

★ 12 in. **£3.0.0**      ★ 14 in. **£4.0.0**


(Money back if not completely satisfied)

★ 17 in. **£5.0.0**      ★ 21 in. **£7.0.0**

*Carriage and Insurance add 12'6*

All Mullard and Mazda Types Rebuilt—Fast Service  
Send your Tube now—Terms C.W.O. or C.O.D.

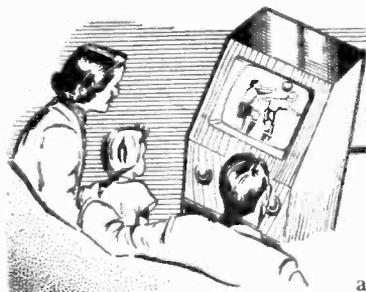**KING'S TELE SERVICE CO.,**  
101-111, DAWES ROAD      ::      FULHAM, S.W.6



## UNDERNEATH THE DIPOLE

A MONTHLY COMMENTARY

By Icons

THE swing of the pendulum applies most appropriately to the relative quality and appeal of the BBC and I.T.A. television programmes.

I seem to swing in my personal preference from one service to the other every five or six months. Just at the moment it puzzles me why the viewing public continues to like I.T.A. programmes so very much better than those of the BBC. According to various public opinion research organisations more than twice as many of the viewers who can pick up both programmes tune to I.T.A. To me this would have been perfectly understandable six months ago, but the fierce competition has forced the BBC programme organisers to try to improve their programmes which they have done in no uncertain manner in my personal opinion. Not only are the BBC comedy programmes on the whole brighter and more original, but the interest features, live and filmed, are of a higher standard. The technical qualities of the BBC pictures are more consistent and considerably more flattering in the reproduction of the faces of actors and actresses. Sometimes, the I.T.A. cameras put years on their apparent age by way of rings under the eyes and lines on their faces.

### BBC Ahead?

OF course, there are occasional I.T.A. programmes which register very well indeed, but in my opinion the BBC programmes have, albeit momentarily, overtaken them. Yet the public as a whole prefers to remain tuned in to I.T.A. What can be the reason? It may be due to sheer laziness, or it may be that they enjoy the advertisements. This, I think, is the real reason. Some of the brightest


and most amusing moments in the television programmes are the really good advertising film-lets, which are the product of first-class craftsmanship. Slick and witty, the best of them provide an admirable thirty-second diversion. Sadly, this high standard is not maintained throughout, and many will agree when I say that.

### Transmitter Sites

I HAVE long admired the names of the BBC television transmitter sites. They always seemed so appropriate. *Kirk o' Shotts* immediately suggests the skirl of pipes and the swing of the kilt. *Pontop Pike* has a rugged sound appropriate to the Pennines. *Wenvoe* has the atmosphere of the rolling West Country and *North Hessary Tor* immediately conjures up the stark landscapes that are the

backbone of the pleasant counties of Devon and Cornwall.

The I.T.A. have not been quite so lucky with their site names, though *Mendlesham* has a distinct Suffolk flavour and *Limley Moor* has the atmosphere of the Brönte county. *Winter Hill* and *Black Hill* are excellent sites with discouraging names. *Burnhope* sounds like the name of a music hall act of 25 years ago—Burr and Hope—while *Croydon* recalls the old London Airport and the earliest aircraft radio telephony network, on

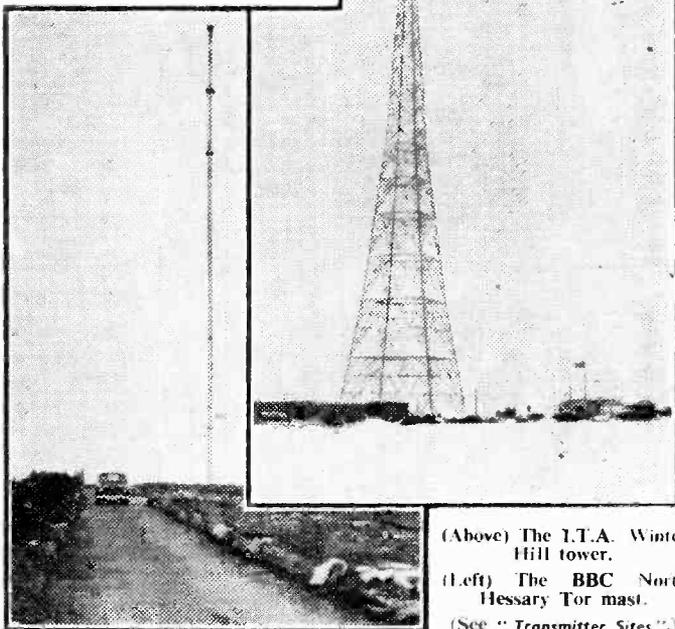

(Above) The I.T.A. Winter Hill tower.

(Left) The BBC North Hessary Tor mast.

(See "Transmitter Sites".)

900 metres. It will be interesting to see what names turn up for the I.T.A. transmitters for Devon, Cornwall, Carlisle and North-east Scotland. The I.T.A. have yet to obtain approval for the sites by various authorities. Up to now, the I.T.A. have scored full marks in their choice of sites, and the designers of their transmitter aerial arrays have included some daring directional designs.

#### TV and the Election

THE BBC, I.T.A. and the various contracting programme companies all have their ideas of how the General Election should be put over to viewers. The impact of television has been recognised by the two great parties, who have spent quite a lot of money on equipment and personnel to groom their speakers for live appearances. This is all to the good and provided the organisations keep the intrusion of politics well under control, as has happened in the last two or three General Elections, the viewers will not be overwhelmed or bored. The suggestion by Granada that all candidates in their area might be given the freedom of the microphone and TV camera is fraught with danger. I remember some incidents in *Under Fire* which accidentally got out of hand and might well have broken the conditions of the licence. Far better for the I.T.A. companies not to play with fire nor to risk annoying at least half of their customers. The BBC handle these things so much better than I.T.A., and their treatment of the results on election night is always absolutely first rate.

#### Lighting Progress

A VERY comprehensive survey of past, present and future lighting equipment for film and television studios was recently given before the British Kinematograph Society in the lecture hall of the Royal Society of Arts. T. E. Knight (Pinewood Studios) and Mr. R. de B. McCullough (BBC) read papers on their own particular spheres and B. Honri dealt with lighting in silent film days and forecasts of types of studio lighting of the future. Into this

last category came 150 and 500 watt, internally silvered reflector, spot and flood lamps of very high efficiency; motorised lamps which can be moved by remote control; very low voltage incandescent bulbs giving a bright and hard spotlight beam; and a new type of xenon arc, which is instant starting and does not require water cooling. The internally silvered reflector lamp has been in use for some time for shop window lighting. In its latest, highly efficient form, it should become a useful and popular lamp in both film and television studios. Not so popular, though, with the lamp-housing manufacturers. Studio lamps usually collect peculiar slang names, such as "foo-foos," "inky-dinkies," "bashers," and so forth, and as the reflector lamp is virtually its own lamp-house, an ideal slang term springs to mind—"snail."

#### "Canned" Entertainment

AS an example of the use of "canned" goods take a recent evening when ITV offered *Song Parade*, *Double Your Money*, *The Cyril Fletcher Show*, *Variety Jubilee* and *The West Warlock Time Capsule*. The last two mentioned were films, the first two presumably telerecorded. On the face of it, a good evening's entertainment. I like Hughie Green very much, but the mixture for this show is "as before." But does Hughie Green have to look so much older than he really is? *The Cyril Fletcher Show* was completely ruined by the most phoney

sounding laughter and applause interpolations I have ever heard. But this kind of dubbing butchery is murder on the work of any comedian, and Cyril Fletcher, of "Odd Ode" fame, deserved better treatment.

*The West Warlock Time Capsule* was preceded by one of those lengthy, uninspired introductions and explanations by Alfred Hitchcock, which is usually the cue for the family to make a cup of tea. *Variety Jubilee*, a film made about 1934, proved to be the best I.T.A. entertainment of the evening for me, with remarkably good technical values, good songs and the sight of George Robey, Florrie Forde, Gus Elen and other music hall favourites of twenty-five years ago. Why didn't I turn over to the BBC? On this particular evening, something was temporarily wrong with my BBC aerial circuit, giving a weak and fuzzy picture. So I missed Cliff Michelmore, Vera Lynn, amateur boxing and *Nina and Frederik*, all reported to have been first class in their different ways.


#### I.T.A. N.I. Coverage

A MAP issued by the Independent Television Authority shows that in the area to be served by its new station at Black Mountain, near Belfast, there is a population of over one million. Practically all these people will be in the primary service area where most viewers, unless they happen to be situated in particularly unfavourable positions, should receive a consistently satisfactory service.

## PRACTICAL WIRELESS CHIEF CONTENTS OF JUNE ISSUE
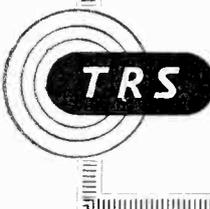
### NOW ON SALE, 1/3

- SIMPLE TONE CONTROLS
- MAKING A SET ANALYSER
- A SIX-VALVE CAR RADIO
- A MINIATURE MAINS SET
- A NOVEL VOLT/OHM-METER
- SERVICING RADIO RECEIVERS
- A RECORD PLAYER AUTO-STOP
- SHIPPING BAND FOUR-VALVER
- A BEGINNERS' MAINS 2-VALVER
- A DIRECT-COUPLED TRANSISTOR RECEIVER
- TRANSMITTING TOPICS
- ETC. ETC. ETC.




## REGUNDED TV TUBES

NEW REDUCED PRICES!

12in.....	£6	17in.....	£8. 10. 0
14in.....	£7	21in.....	£10. 10. 0
15in.....	£7. 10. 0	Carr. and Insur.	10/-

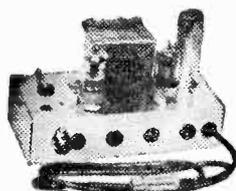All tubes Rebuilt with new Heater. Cathode and Gun Assembly—reconditioned *virtually as new!* Full 6 months' unconditional Guarantee. As used by our own Service Dept. Regret only Mullard and Mazda at present. 10/- part exchange allowance on your old tube.



BAND 3 TV CONVERTER

All channels 7-13 (190-295 Mc/s).  
**Mk. 2 Model.** Latest cascade circuit using 6X4 and 6F80 valves, 18db gain over standard circuits. Built-in Power Supply 200-250 v. A.C. Size 4 1/2" x 3 1/2" x 4 1/2". Simple to fit—only external plug-in connections. Wired and aligned ready to use. Only 29/8. p. & p. 2/6.  
 B1-33 changeover Sw. and BBC Aerial Socket (included) and wired, 8/- extra.  
**Band 3 Aerials.** Single Dipole with 4 yds. cable, 13/9. 5 Element Beam, 25/-, 5 Element, 32/8, etc. B1-B3 Crossover Units, 7/8.

### CYCLON BAND 1-BAND 3 TURRET TUNER

**BRAND NEW—UNUSED—EX-MANUF.**  
 I.F. 9-14 Mc/s (PIOL) 3A SERIES HTRs. Complete with valves and knobs, etc. Listed 7 gns. Bargain 59/8. p. & p. 2/6. *State channel required.*

**ACCESSORIES.** Wired B1-B3 Aerial socket panel and gain control, and output leads wired to B3A valve plugs. 12/6 extra.

### TRANSISTOR 'ONE-WATT' AMPL.

6 v. Battery Operated  
 Latest Push-Pull 4 Transistor circuit giving full 1 watt output using standard 2 ohm speaker. Good sensitivity (approx. 10 mV) and improved frequency response. Neg. feedback volume and tone controls. Chassis size 6 1/2" x 3 1/2" x 1 1/2". Current consumption 10 mA. quiescent—250 mA. at 1 watt.  
 2 matched GEC 4BT15 Transistors ..... 42/- pt.  
 2 GEC 4BT3 Transistors ..... 21/- pt.  
 Driver Trans. .... 8/6  
 Output Trans. (to 3 ohms) ..... 10/6  
 Complete kit of parts incl. 99/6 P. & P. 2/6  
 circuit, etc., less speaker, only  
 Recommended Tin x 4in. speaker 18/6. P. & P. 1/6.

### STAAR 45 r.p.m. SINGLE RECORD PLAYER

6 v. Battery operated. Lightweight Xtal Pickup with Twin Sapphire Stylus (one spare). Auto stop. Mounting 7 1/2" x 6in. Attractive Continental styling. Ideal companion unit to above Transistor Amplifier.  
**RECOMMENDED BARGAIN** 92/6 P. & P. 3/6.

### RECORD PLAYER CABINETS

Contemporary Cabinet  
 striped, resin covered cabinet in two-tone fawn and brown. Carr. and Ins. 3/6.  
 or mottled red with white polka dots. Size 18 1/2" x 12 1/2" x 8 1/2". fitted with all accessories, including baffle board and anodised metal feet. Space available for all modern amplifiers and autochangers, etc. Unmet record player mounting board 14 x 13in. supplied.  
**£3.3.0.**



### 2-valve AMPLIFIER Mk 2

Latest developed circuit giving a higher fidelity response and greater output (2-3 watts) using twin stage valve ECL22 and neg. feedback Tone Control. Complete with knobs wired and tested with 6in. Speaker, etc., ready to fit in above cabinet. Only 23.19.6. Carr. 2/6.

### RECORD PLAYER BARGAINS

ALL NEW 4-SPEED MODELS

**SINGLE PLAYERS** BSR (TU9), 92/6. COLLARO (4/504), 6 gns. GARRARD (48P), 27.15.0, carr. 3/6. GARRARD (TA Mk. II) 29.5.0, carr. 3/6.

**AUTOCHANGERS** BSR (UA8) 26.18.6. BSR (UA12) with stereo/mono pln. 10 gns. COLLARO CONQUEST, 27.19.6. GARRARD RC121/D Mk. II. Plug-in head, stereo adapted, 10 gns., carr. 4/6.

**FINEST SELECTION AVAILABLE ALL BRAND NEW & GUARANTEED**

Listed above are only a few items from our very large stock. Sent 5d. stamp today for Complete Bargain List.

### NEW BOXED VALVES

1R5, 1T4	7/8	DF99	9/-	EF41	10/6	PCF82	10/6
1R5	7/8	DK96	9/-	EF80	10/6	PCL83	12/6
384, 3V4	8/-	DL96	9/-	EF86	14/6	PL81	14/6
3Z4	9/6	35LG	10/6	EF91	9/6	PL82	10/-
6AT6	8/6	EABC80	9/6	EL41	10/6	PL83	11/6
6K7	6/6	EB30	6/6	EL84	11/6	PY90	9/6
6K8	8/6	EC41	10/6	EM85	21/6	PY91	9/6
6Q7	8/6	EC83	9/6	EV31	12/6	PY82	8/6
6N87	8/6	EC84	12/6	EV80	14/6	PY83	10/6
6V6	7/6	ECF80	12/6	EZ40	8/6	U25	13/6
6X4	7/6	ECF82	12/6	EZ80	8/6	UCH2	10/6
6X5	7/6	ECI42	10/6	EL251	8/6	UF41	10/-
7C5	9/-	ECI81	10/6	EM14	9/6	UF41	10/-
7V4	8/6	ECL80	12/6	PCC84	10/6	UL41	10/6
DAF96	9/-	ECL82	12/6	PCF80	10/6	UY41	8/6

**SPECIAL PRICE PER SET**  
 1R5, 1T4, 1R5 or 384, or 3V4 ..... 27/6  
 DK96, DF96, DAF96, DL96 ..... 35/-  
 6K8, 6K7, 6Q7, 6V5, 5Z4 or 6X5 ..... 35/-

### VOLUME CONTROLS

10,000 ohms—2 Megohms. All long spindles. Morganite Midget type. 1 1/2in. diameter. Gain 1 way. Log. or Lin. Ratios. Less Sw. 3/6. D.P. Sw. 4/9. Twin Control controls, 1 meg., 1 meg., 1 meg., less Sw. 8/9 ea.

### ELECTROLYTICS ALL TYPES NEW STOCK

Tubular Wire Ends	32+32/350 v. H.E.C.	5/6
25.25 v. 50/12 v.	1.5 Ohm Types, Clips 3d.	ea.
25.50 v. T.C.C.	2/- 8/500 v. Dub.	3/-
50.50 v., 4500 v.	2/- 8+16/450 v. T.C.C.	4/6
100/25 v., 2450 v.	2/- 8+16/450 v. Hmts	5/6
8.450 v. T.C.C.	2/3 16+16/450 v. T.C.C.	5/-
8+8.450 v. B.E.C.	4/6 32/350 v. B.E.C.	4/6
8+10/450 v. T.C.C.	5/- 32+32/275 v. Hmts	4/-
16/450 v. B.E.C.	3/6 32+32/450 v. T.C.C.	6/6
16/500 v. Dub.	4/- 250/350 v. B.E.C.	8/8
16+16.450 v. T.C.C.	5/6 600/350 v. T.C.C.	6/6
32/350 v. B.E.C.	4/- 60+100/350 v. B.E.C.	11/6
32/300 v. Dub.	5/- 60+250/275 v. B.E.C.	12/6
50+50/350 v. B.E.C.	6/6 100+200/275 v. B.E.C.	12/6

**SENTERCEL RECTIFIERS.** E.H.T. Type Fly-back Voltages. K3/25 2 kV. 5/-; K3/40 3.2 kV. 6/8; K3/45 3.6 kV. 7/8; K3/50 4 kV. 7/8; K3/100 8 kV. 13/6. **MAINS TYPES.**—RM1, 125 v. 60 mA., 4/9; RM2 125 v. 100 mA., 5/8; RM3 125 v. 120 mA., 7/8; RM4 250 v. 250 mA., 16/-; RM4B type 270 mA., 17/6; RM5, 250 v. 300 mA., 21/-.

**SPEAKER FRET.**—Expanded Bronze anodised metal 8 x 8in., 2/8; 12 x 8in., 3/-; 12 x 12in., 4/6; 12 x 15in., 6/-; 24 x 12in., 9/-, etc.

**TYGAN FRET** (Murphy pattern) 12 x 12in., 2/-; 12 x 16in., 2/-; 12 x 24in., 4/-, etc.

**SPEAKERS P.M.** 3 ohm 2 1/2in. Elec. 16/6. 3 1/2in. Goodmans 18/6. 5in. R. & A., 17/6. 6in. Celestion, 18/6. 7 x 4in. G-manus, 18/6. 8in. Rohn, 20/-, 8in. Special Cone G-manus, 21/6. 10in. R. & A., 25/-.

### Another T.R.S. Record Player Winner

1. LATEST 4-SPEED BSR Player Unit (Model TU9) and 'Full-P' pickup, 24.12.6, carriage 3/6.
2. 2-VALVE AMPLIFIER wired complete with speaker, etc., on mounting board, 23.5.0, carr. 2/6.
3. CONTEMPORARY STYLED LIGHT-WEIGHT CASE in maroon and grey, size 7 1/2" x 1 1/2" x 8in., 21.7.8, carr. 2/6.

SPECIAL OFFER.

**ALL 3 UNITS ONLY 29 Carr. 4.6.**

### COAX 80 OHM CABLE

1 1/2in. diam. Low Loss Semi-Air Speed Aerials. **SPECIAL REDUCED PRICES**  
 20 yds. 12/6. p. & p. 1/6; 60 yds 32/6. p. & p. 3/-; 40 yds. 22/6. p. & p. 2/6; All other lengths 8d. per yard.  
 Coax Plug 1/-, Sockets 1/-, Couplers 1/3. Cable End Sockets 1/8, Outlet Boxes 4/8.

### C.R.T. Heater Isolation Transformers

**New Improved types—mains prim. 200/250 v. tapped.**  
 All Isolation Transformers now supplied with alternative no boost plus 25%, and plus 50% boost taps, at no extra charge.  
 2 v. 2A type 12/6 (P. & P. 1/6)  
 6.3 v. 6A .. 12/6 ..  
 10.5 v. 3A .. 12/6 ..  
 13 v. 2A .. 12/6 ..  
 Other voltages in course of production.  
 Small size and tag terminated for easy fitting.

### NOW! The TOURIST Portable

4 valve, Med. & L.W., 1 1/2 weight battery Radio. Size only 8in. x 3 1/2in. x 4in. Weight 3 1/2lb. with battery. Complete receiver component kit 56/6. p. & p. 1/6. Set 4 miniature valves (96 series) 35/- p. & p. 9/6. 5in. Speaker & O/P Trans. .... 21/- p. & p. 1/6. Cabinet, Dial and Knobs, etc. .... 19/6. p. & p. 2/-  
**Complete kit—BARGAIN—only 68.8.6.**

Latest circuitry, delayed AVC and A.F. Neg. feedback. Instruction Booklet 1/6 free with kit.  
**Terrific performance—**

**Remarkable size—**  
**Staggering value**  
 Send for Booklet NOW!

**MAINS TRANSFORMER WINDING CAPACITY AVAILABLE PROTOTYPES & SMALL RUNS**

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 10/4d. 11b. 1/1, 31b. 1/6, 51b. 2/6, 101b. 5/8. Hours: 9 a.m.—6 p.m. 1 p.m. Wed. Open all day Saturday.




## TRR RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Buses: 130A, 133, 159, 166 and 190

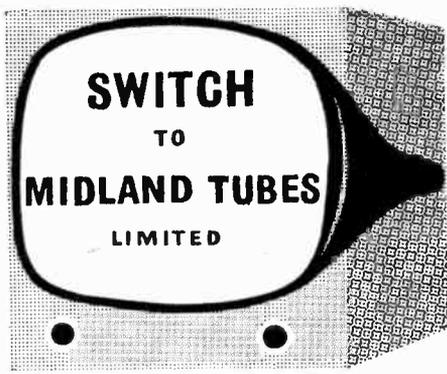

# for SERVICE and PEAK QUALITY in REBUILT T.V. TUBES

## NOW AT LOWEST EVER PRICES

Midland offer you the best value in rebuilt television tubes, please write or call for completely revised price lists.

New Electron Gun Units fitted to all tubes and a seven-months' Guarantee from the Invoice date.

Free, immediate delivery in the U.K.

FOR COMPLETE INFORMATION PLEASE CONTACT:

### MIDLAND TUBES LTD.

37 GEORGE STREET, MANCHESTER. 1.

Telephone: CEN. 4568



# VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS		1R5 1S5 1T4 3S4 3V4 DAF91 DF91 DK91 DK92 DL92 DL94 any 4 for 27/6		DAF96 DF96 DK96 DL96 4 for 32/6		6K7G 6K8G 6Q7G 6V6G 6X5G or 5Y3G 5 for 27/-					
1A7GT	14/6	6Q7GT	8/6	30L1	8/-	EBC41	9/6	EZ80	7/9	U25	13/3
1D5	9/6	6SL7GT	7/-	35L6GT	10/-	EBC42	9/6	EZ81	8/6	U26	12/6
1H5GT	10/-	6SN7GT	6/6	35Z4GT	8/6	EBF89	8/9	FW4500	9/6	U50	7/6
1N5GT	10/-	6U4GT	11/-	35Z5GT	8/6	EBL21	20/6	GZ32	9/-	U52	6/6
1R5	7/6	6V6G	8/6	43	12/6	ECC81	8/-	KT33C	7/-	U76	8/6
1S5	7/6	6V6GT	7/6	50CD8G	26/9	ECC82	7/6	KT41	14/6	U78	6/9
1T4	6/3	6X4	6/9	50L6GT	9/9	ECC83	8/-	KT63	6/6	UABC80	9/-
3A5	10/6	6X5G	8/-	AZ31	9/6	ECC84	9/6	KT71	12/8	UAF42	9/6
3Q4	8/6	6X5GT	8/-	B36	15/6	ECC85	9/6	KTW61	6/-	UBC41	8/8
3S4	7/6	7B7	8/-	CCH35	20/6	ECP80	11/6	LM152	10/8	UBP80	9/8
3V4	8/-	7C5	8/-	CL33	15/9	FCF82	11/6	MH4	6/-	UBP89	8/6
5U4C	6/6	7C6	8/-	CY31	12/6	ECH21	17/8	MU14	9/-	UBL21	20/6
5V4C	11/-	7H7	8/-	D77	5/6	ECH35	6/9	MX40	12/8	UCR84	12/6
5Y3GT	7/6	7S7	9/9	DAC32	10/-	ECH42	9/6	N18	8/6	UCR85	9/-
5Z4C	9/6	7Y4	8/-	DAF91	7/6	ECH81	8/6	PCC94	15/-	UCF80	18/6
6AL5	5/6	10C1	14/6	DAF96	8/6	ECL80	10/6	PCC89	17/8	UCH21	20/6
6AM5	6/6	10C2	17/6	DCC90	10/6	ECL82	11/6	PCF80	8/-	UCH42	9/6
6A6G	5/3	10F1	17/6	DF33	10/-	EF39	5/8	PCF82	10/6	UCH81	9/6
6A25	7/3	10F9	10/6	DF91	6/3	EF41	9/6	PCI82	10/6	UCL82	13/-
6A76	7/3	10P13	15/9	DF96	8/6	EF42	11/6	PCL83	12/6	UCL83	14/3
6BA6	7/6	12A1T	8/-	DH76	6/6	EF80	8/6	PCL84	15/-	UF41	9/3
6BB6	7/-	12A1U	7/6	DH77	7/3	EF86	12/-	PEN4A	11/-	UP89	9/-
6B96	7/-	12A2X	9/-	DK32	14/6	EF89	9/-	PEN36C	9/6	UL41	9/3
6B76	7/-	12BA6	8/-	DK40	16/-	EF91	6/3	PEN45	12/6	UL44	21/6
6B77	7/-	12K7GT	6/6	DK91	7/6	EF92	5/6	PEN46	6/-	UL84	8/6
6CD6	26/9	12K8GT	12/6	DK92	8/6	EL33	10/-	PL36	14/-	UR1C	9/6
6F1	14/6	12TGT	6/6	DK96	8/6	EL38	21/6	PL38	21/6	UY6	10/6
6F9G	6/6	17Z3	7/6	DL33	9/-	EL41	9/6	PL81	12/6	UY1N	10/6
6F13	12/6	19AQ5	7/6	DL35	12/3	EL42	10/6	PL82	8/6	UY21	14/-
6V14	17/6	19Y3	8/6	DL92	7/6	EL84	8/9	PL83	9/6	UY41	7/-
6K7G	3/9	20F2	17/6	DL94	8/6	EM80	9/8	PY32	16/-	UY85	7/6
6K7GT	6/9	20L1	17/6	DL96	8/6	EM81	9/6	PY30	8/-	VP4B	9/6
6K8G	6/9	21A6	13/6	EA8C	7/9	EM84	13/6	PY81	7/6	VP41	6/-
6K8G	6/9	25A6G	11/-	EAC91	5/6	EY51	10/6	PY82	8/6	W76	6/6
6L1	16/9	25Z4C	9/-	EAF42	9/6	EY96	11/6	PY83	8/6	W77	5/-
6L18	12/3	25Z6GT	9/6	EB91	5/6	EZ40	7/6	PZ30	17/-	Z77	6/3
6Q7G	8/-	30C1	8/-	EBC33	7/-	EZ41	8/6	SP61	3/6		

# FIRST-CLASS TELEVISION and RADIO COURSES . .

## GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

## FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A.M.I.Mech.E., Draughtsmanship (all branches),** etc., together with particulars of our remarkable Guarantee of

## SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER 150,000 SUCCESSSES.**

**NATIONAL INSTITUTE OF ENGINEERING**  
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg.  
Australia: P.O. Box 4570, Melbourne.

# READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

Postage 6d. per valve extra.  
Any Parcel insured Against Damage in Transit 6d. extra.  
Any C.O.D. Parcel 2/6 extra.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. **WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE.** The coupon from p. 574 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

#### ULTRA V817

During the past two years I have had seven 6K25 valves fitted in this set, and approximately every three to four months this valve fails, producing a horizontal line across the screen, which indicates timebase failure. I am wondering if you could give me any information that will enable me to eliminate this trouble. Is this defect caused by resistors associated with this valve, or is it possible there is a defective preceding valve?—M. England (Pontyclun, Glam).

The rapid failure of the 6K25 indicates that its heater is overrun. This is normally the result of the mains transformer being set to operate upon a voltage lower than is actually applied. Raise the setting to 236-250. If still troublesome, run 6K25 from separate 6.3 v. transformer (rather than replace the mains transformer).

#### DERWENT RT5126

This set is about 1951 vintage which I have converted from 9in. to 12in. Unfortunately the metal H.T. rectifier (4DQ of unknown make) is disconnected. There appear to be two loose leads, one from the top of the transformer and one going to the red tag on the 100 $\mu$ F-100 $\mu$ F smoothing condenser. I believe it should be connected up as half-wave, i.e., transformer lead to green end of rectifier and condenser lead to the other end of the rectifier. As there is also a rectifier centre tap I would welcome your guidance on connecting up.—P. J. Wild (Plymouth, Devon).

If the rectifier has almost square fins or plates, wire transformer to the centre tag, strap the outer plates together and connect to H.T. (smoothing capacitor). The rectifier should be a Westinghouse 14A100, connected as above.

#### COLUMBIA 12in.

My set has been working perfectly for five years, but recently it started to give trouble. When I switch on all is well, but if I switch off for a time and switch on again it is dead. If I

leave it till the next day, it comes on all right and continues till I switch off. I took it to a dealer but all the time he had it, it would not go wrong, so I brought it home and tried it, and now it is dead again.—W. R. Gilbert (Sheffield, 7).

We would advise you to replace the (Z) thermistor. This is wired in series with the valve heaters and is almost certainly cracked. It is wired from the mains dropping resistor to the first heater in the valve chain.

#### EKCO T217

This set went off with a crack. After inserting two new fuses in the set, and switching on, the rectifying valve, U801, comes to a purple glow then flashes, after this has happened twice the fuses blow in the set. There is no sound or picture.—J. Wesley (Sheffield).

Your fault is almost certainly the U801 itself, although if replacement fails to cure the fault suspect a short to chassis from the U282 filament winding of the mains transformer.

#### BUSH 53

The line-hold on the above set has become very erratic, mostly when the power is low. Also, at the base of the screen, there is a  $\frac{1}{2}$ in. wide bar which develops after the set has been running for a while. Adjusting the height control distorts the picture.—J. Nichols (West Lothian).

You should replace the ECC82 valve situated on the right-hand side of the chassis, behind the PY81. You will have to remove the metal screen (two P.K. screws) to gain access. The frame cramping can be corrected by means of the vertical form control, on a bracket on the same chassis under the tube. Alternatively, the PCL83 valve, near this control, may be failing.

#### G.E.C. BT1846

The above set is tuned to Channel 5, Band I, and Channels 8 and 9, Band III. Could you please advise me on how to tune it to Channel 10?—T. E. Davies (Cwmbran, Mon).

Tilt the set slightly, so that trimmers on the tuner unit are accessible. Set the contrast, sensitivity, and volume to maximum, and switch to one of the Band III ranges. Adjust the oscillator trimmer for maximum sound; aerial and R.F. for maximum picture brightness. Re-adjust the oscillator for minimum sound on vision, and re-adjust aerial and R.F. for best picture quality. During these operations, it may be necessary to reduce both sensitivity and volume.

#### PHILIPS 485U15

The frame lock is very critical—picture rolls badly when the hold control is moved, and also when the contrast control is moved. Flyback lines are visible all the time, and there is considerable "pulling on whites."—W. K. Buckley (Manchester).

The symptoms suggest that an electrolytic capacitor associated with the UL46 video amplifier (on the left of the tube) has become open circuited. Two 5  $\mu$ F and one 50  $\mu$ F are concerned (white cardboard covered).

**ULTRA W817**

I am having a great deal of trouble with lack of height and frame jitter. I have tried checking condensers, resistors, etc., as you advised another reader with similar trouble, but in my case the only cure seems to be a new 6K25 frame oscillator. Would it be possible to alter the circuit to enable the use of a hard valve frame oscillator?—D. Brown (Staines).

Ensure that the mains voltage is correctly set, so that the valves receive their correct current and no more. The .001  $\mu$ F line pulse filter capacitor (junction of 100 K and 500 pF to chassis in 20LI-6K25 circuit) should be checked. Normally, the 6K25 is not troublesome, and a change to a blocking oscillator circuit hardly seems warranted.

**FERGUSON 988T**

Could you please help me cure sound distortion, also picture and sound fading?—L. C. Lee (Waltham Cross).

For sound distortion, check front left-hand side ECL80 valve and resistors associated with the front right-hand side EB91. For fading, check seating of EF80 valves in their sockets, the rear three EF80 valves by substitution, and the resistors, etc., associated with the bases.

**PYE LV51/F**

The picture shimmers and is often too big for the screen and the frame hold needs constant readjustment. The picture inclines to the left, and adjustment does not rectify this. The contrast control is not very good, and tends to act as brilliance control. The sound crackles slightly now and then. All the valves are O.K. Do you think a new choke is required?—P. J. Edwards (Stretford, Lancs).

We do not think so. If it runs hot, an excessive current flow is indicated. This could be due to leaky electrolytic capacitors, and these should be checked. Check the frame timebase ECL80 (jitter and frame hold), and hold control series resistor. Check the EY51 by replacement (picture too big). Check and clean volume control and inspect contact. Centre the picture by means of the shift plates on the front of the focus magnet.

**FERRANTI T1505**

Ten minutes after switching the set on, the left half of the screen goes blank, while the right half breaks up into horizontal lines. After 30 minutes, the whole screen is covered by these lines, with one big vertical white line in the centre.—J. Hupton (Leigh, Lancs).

Inside the top of the line output transformer is a large resistor, probably charred. Its value should be 120 K $\Omega$ . Check this and replace if necessary. Check EL38 valve and 5.6 K $\Omega$  resistor, 8-watt wire wound, to pin 4 of EL38. The "shedded" appearance of this, and nearby resistors does not, however, indicate that they are faulty.

**EKCOVISION T217**

Recently, the picture has become very blurred. If the brightness is advanced, the picture goes off, but if the contrast is turned down at the same time, the picture improves slightly. I have fitted

a new U801 and U282, also a new 20PI without success.—C. Orrah (Sheffield).

You should replace the EHT rectifier, type U25. This is the small glass valve with a single soldered connection at one end and two at the other. The soldered connection must be left well rounded, with no sharp edges (use a hot iron), which could promote corona and arcing.

**COSSOR 937**

After the above set has been on for about half an hour, the picture starts to get smaller from the top and bottom, till it disappears altogether. After switching off for about half an hour, the picture is restored to normal for a while, and then the process repeats itself.—T. Walker (Billingham).

If, when the picture fails, a white line is left horizontally across the tube face, replace the right-hand 6AB8 (ECL80) on the main deck. If, however, the picture fades completely, leaving nothing on the screen, replace the .1  $\mu$ F capacitor, which decouples the first anode supply to pin 10 of the tube base, and .001  $\mu$ F, which decouples the height control.

**MURPHY V350AD**

Upon switching on, the picture is very blurred and the width is not sufficient to fill the screen. As the set warms up this slowly corrects itself until after about 15 minutes a perfectly satisfactory picture is obtained.—W. Prewett (Salisbury).

We advise you to check the two valves inside the screened compartment, as one of them is obviously slow in heating. The most likely one is the efficiency diode type U251 (U301 on earlier sets), but the 20P4 can also cause the symptoms you describe.

**SOBELL TS17**

My set is fitted with a Mullard MW43-64 tube. The picture just disappears and does not reappear for days. There are no inter-electrode shorts and the tube appears to be in order. All valves light up, and movement of the ion-trap magnet has no effect. The sound is perfect and controls are O.K., but there is no raster.—D. Provan (Carnock, Stirling).

Assuming that you have tested for EHT and found it present whether the fault is existent or not, we would say that the cause is an intermittent break in the C.R.T. cathode connection (usually inside the tube). Check for dry joints around the tube base and also short the grid and cathode pins of the tube. If all is in order this should produce an uncontrollably bright raster.

**RAYMOND F89**

When the set is switched on, the frame hold has to be reset, and again as the set warms up. There is considerable frame jitter present. I have replaced three valves, and most of the condensers and resistors in the frame timebase.—J. H. Wilson (St. Helens, Lancs).

We advise you to replace resistor R54, and capacitor C60, as these are most likely to be at fault. If you suspect CV3, remove it, wire a

(Continued on page 574)

(DEPT. T.6.)



**COMPONENTS LTD.**

219, ILFORD LANE, ILFORD,  
ESSEX. Tel.: ILF 0295.

**FOCUS MAGNETS AND T/V SPARES**

9/9. Brand new, 38 mm. Incorporating picture shift controls. P. & P. 1/3.  
 3/9. Frame o.p. Trans. to match low imp coils. P. & P. 1/3.  
 12/9. Elac. Brand new, 35-38 mm. P. & P. 1/3.  
 3/9. Plessey. 35 mm. Permanent magnet. Salvage. P. & P. 1/9.  
**SCANNING COILS, 10/6.** Low impedance. 38 mm. Brand new. P. & P. 1/3.

**SPECIAL OFFER**

**T.V. SLIDER CONTROLS.**

5/- for panel of 5 sliders. 1 K., 5 K., 10 K. and 2 at 50 K. ohms. Complete with knobs. P. & P. 1/-.  
 17in. T.V. MASKS, 7/9. Brand new. Good quality. Grey or white plastic. P. & P. 2/3.  
 12in. T.V. MASKS, 1/9. White rubber. Slightly soiled. Easily cleaned. P. & P. 2/3.

★ **TRANSFORMERS** ★

**MAINS POWER TRANS., 12/6.** 350-0-350 v. at 250 m/a. 22 v. 3 a., 4 v. 3 a., 6.3 v. 4 a., 6.3 v. 4 a., 4 v. centre-tapped. Prim. 200/250 v. Drop thro' type. P. & P. 3/9.  
**MAINS POWER TRANS., 12/6.** 350-0-350 v., at 250 m/a. 6.3 v. 5 a., 4 v. 4 a., 4 v. 7 a., 4 v. centre-tapped. Drop thro' type. Prim. 200/250 v. P. & P. 3/9.  
**HEATER TRANS., 1/9.** 4 volt-6 volt at 3 amp. Ideal auto trans. P. & P. 1/-.  
**O.P. TRANS., 1/3.** Standard size, 2-5 ohms. P. & P. 1/- 20 for £1. Carr. 5/6.  
**VISCONAL CONDENSERS, 5/9.** 0.1 µF at 7kV. working and 0.001 µF at 12.5 kV. working. Post 1/-.  
**V/CONTROLS, 2/6 doz.** Assorted volume and tone controls stripped from working chassis. Post 2/-.  
**CO-AX. CABLE, 6d. yd.** Good quality. Cut to any length. Post on 20 yds. 1/6. 45/- per 100 yds. P. & P. 3/6.  
**RECTIFIERS, 2/9.** Westinghouse. 250 v. 100 m/a. Full or half-wave. Salvage guaranteed. P. & P. 1/3.

**COIL PACKS, 3/9.** 3-gang. Incl. pair 465 i.f.s., 2-gang cond., paper dial. P. & P. 2/3.

**COIL PACKS.** Press button, 10/6. 3 w/band F.M. and gram. P. & P. 1/6.

**2 GANG CONDS.** Miniature 2/6. 500 500 and 30 : 30. P. & P. 1/3.

**TUNING CONDS., 2/6.** Regentone. New, std. size. 500 : 400. P. & P. 1/3.

**2 GANG CONDS., 2/6.** Plessey. A.M./F.M. Std. size. P. & P. 1/3.

**GANG CONDS., 1/9.** Std. size. 2 and 3 gang .0005. Salvage guaranteed. P. & P. 1/3.

**RELAYS, 2/9.** Double pole, D/throw. 12 volt. P. & P. 1/-.

**RELAYS, 5/6.** Double throw. four pole. 12 volt. P. & P. 1/-.

**U.S.A. TYPE VALVES. ALL AT 3/9.** 18-42-75-77-78-80-83-6A7-ID6. P. & P. 1/6 on half doz.

**SPEAKERS 8" P.M. 5/9** Limited quantity of these modern type speakers. All tested and "money back guarantee." They have a slight cone fault that is repaired. Not affecting the quality. Post on 1, 2/6; 2, 3/6.



**SPEAKERS 8" P.M. 8/9.** Ideal for extension in kitchen or bedroom. With o.p. transformer, 10/- P. & P. 2/9. Suitable for stereo.

**6 1/2" SPEAKER, 12/6.** Standard matching to any receiver. 2-5 ohms. P. & P. 2/6.

**ELLIPTICAL SPEAKER, 19/6.** Brand new. 4 in. x 7 in. P. & P. 2/6.

**SOLDER REELS, 1/6.** 20 ft. 3-core ERSIN solder. 60/40. P. & P. 4d.

**INSULATING TAPE, 1/6.** Finest quality tape. 75 ft. x 1/2 in. wide. In sealed metal tins. Post on 1 tin 9d., on 6 tins 2/-.



**T.V. AERIALS, 25 6.** For all I.T.A. channels, including Channel XI. For outdoor or loft. 3 elements. Sold half normal price. P. & P. 2/6.

**T.V. AERIALS, 7/9.** Fitted with 9 ft. co-ax. cable. Suitable for door rod or loft. Extra co-ax. can be supplied at 6d. yd. P. & P. 1/3.


**I.T.A., 18/6. IN-DOOR.** Folded Dipole with 12 ft. co-ax. cable fitted. Aluminium. P. & P. 2/-.

**B.B.C., 15/6. IN-DOOR.** Folded Dipole with 12 ft. co-ax. cable fitted. Gold finish. P. & P. 1/9.

**CAR AERIALS, 6/9.** Plated. Whip antennae. 50in. long. Collapsing to 11 in. One hole fixing. P. & P. 1/-.

Send 3d. stamp for CATALOGUE. Regret U.K. ONLY.

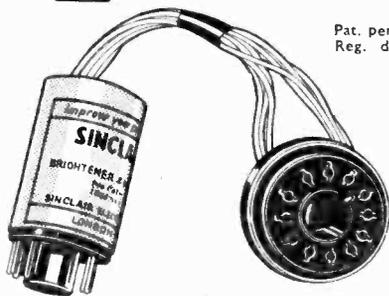**IS YOUR T.V. TUBE DIMMING? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE**



Pat. pending.  
Reg. design.

PRICE **30'**

Package & Postage 2/6.  
(Postal Orders, C.W.O. C.O.D.)

- NO SOLDERING
- NO WIRING
- JUST PLUG IN
- IT'S AUTOMATIC
- IT'S GUARANTEED!

One of the most common T.V. Tube faults is low emission, resulting in loss of brightness, contrast, definition and focus. The Sinclair Unit restores the cathode emission and corrects the above faults for a very low cost. Applicable to all sets operating off A.C. mains.

**IMPORTANT.** State make and model No. of set and tube in block capitals, please. Money refunded if not satisfied.

**SINCLAIR ELECTRONICS,**  
18, NEWPORT COURT, CHARING CROSS ROAD, W.C.2. Phone: REGent 5520

**NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS**

*You LEARN while you BUILD...*

SIMPLE...PRACTICAL...FASCINATING...

**ANNOUNCING**—after years of successful operating in other countries—the latest system in home training in electronics introduced by a new British training organisation. **AT LAST**—a simple way of learning — by practical means—the 'how and why' of electronics with the minimum of theory and no mathematics! **YOU LEARN WHILST BUILDING** actual equipment with the components and parts which we send you — and you really have fun whilst learning!

And afterwards—you have a first rate piece of home equipment plus the knowledge of how it works and how it can be serviced. **THIS NEW SYSTEM** brings an exciting new opportunity and is very moderate in cost. Post the coupon now without any obligation for full details.



**LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!**

**No Mathematics!**

**FREE**  
**POST TODAY**

To: **RADIOSTRUCTOR** (Dept G29)  
46 Market Place, Reading, Berks.  
Please send brochure without obligation to:

Name \_\_\_\_\_  
Address \_\_\_\_\_  
(807) \_\_\_\_\_

**RADIOSTRUCTOR**  
BRITAIN'S LEADING ELECTRONIC TRAINING ORGANISATION

fixed capacitor of .002  $\mu$ F across C52 on tag panel, disconnect white lead from one end. also R54. Connect white lead tag in its place, then instal a 2 M $\Omega$  variable resistor in place of CV3. Use a pre-set control with 2-screw fixing.

#### COSSOR 937A

Recently, a black line has developed on the right side of the screen. At times, this pulls over to the left, forming a wavering line. On other occasions, the whole screen shimmers and none of the controls will stop it, though it settles itself after a few moments.—R. W. Farrow (Redhill, Surrey).

We suggest you change the 6AB8 situated on the main deck, left-hand side, viewed from the rear. If the trouble continues, check the 12AU7, farther to the left, and then check the components associated with the 6AB8 valve base. The 21A6 and 17Z3 on the near left side (with top caps), should also be tested.

#### FERGUSON 203T

Will you please give me instructions for cleaning the front of my tube, and also behind the safety glass. What cleaning medium do you recommend?—J. B. Wilson (Workington, Cumberland).

Pull off the front control knobs; remove the rear cover and turn the cabinet on to its side. Remove the bottom cover, and bottom chassis fixing screws. Pull the speaker lead plugs from their sockets. Turn the cabinet upright and remove centre screw from the side control panels and take out panels. Now slide the chassis carefully out of the cabinet. The screen should be cleaned if possible with an anti-static screen cleaner, but if this is not readily available, household window-cleaning fluid will do the job.

#### PYE LV30

The frame scan in my set has failed, and only a bar appears across the screen, varying from  $\frac{1}{2}$  in. to 4 in. high when the height control is adjusted. I interchanged V14 (frame output valve) and V12 (sound output), and also interchanged the two EB91s without any improvement. While the set was working, I noticed intermittent high-pitched squeaking noises coming from the timebase. When this noise was heard, a slight blue flashing was seen inside the frame output valve (ECL80). As the height of the scan is varied by the height control, I suspect either the frame output transformer, or the blocking oscillator transformer.—C. H. Pugh (Haileybury, Herts).

The frame oscillator transformer of the B18T may be used, and it is possible that this is at fault. Check the frame hold control and the 470k $\Omega$  series resistor, also the 12 $\mu$ F and 50 $\mu$ F capacitors.

#### MURPHY V214

Just before Christmas, I fitted a booster to this set. For a time, all was well, but now I find that the picture is blown up, and any attempt to

increase brightness results in the picture enlarging still further and disappearing altogether.—R. M. Clark (Mexborough, Yorks).

Your present fault should clear up if you replace the U25 EHT rectifier. Be sure to round off all soldered joints, using a really hot iron, or corona will result. Check also the ion trap magnet inside the focus dome. This should be set for maximum brightness.

#### AERIALS—HOLME MOSS AND SUTTON COLDFIELD

Could you please tell me the dimensions of an "X" aerial for these two stations?—M. L. Piercey (Cymmau, Wrexham).

For Holme Moss the aerial should be 9ft. and the director 8ft. 4in. and for Sutton Coldfield the aerial should be 7ft. 7in. and the director 7ft.

#### PYE V4

The sound on the above is working all right, but I cannot get a picture. The EHT rectifier valve (EY51) was not lighting up, so I replaced it, but it made no difference. Then I found that the 250 mA fuse had blown. I renewed this, but it fused again at once.—R. Looker (Waterhouses, Co. Durham).

You should have the PL81 and PY81 valves tested. One of these almost certainly has an internal short, but if this is not the case, the timebase will have to be checked with a meter for shorts.

#### COSSOR 946

When I increase brightness, the picture enlarges and fades out. Also, when I switch the set off, white spots appear on the tube.—J. H. Pritchard (Bethesda, Caernarvonshire).

Your symptoms are those of a displaced ion-trap magnet, and this should be set for maximum brilliance. If this does not improve your picture, we suggest you change the SU61 EHT rectifier, which is inside the aluminium case on the left of the set as viewed from the rear.

#### AERIAL—ST. HILLARY

I am interested in making an ITV aerial for St. Hillary. Could you please tell me the dimensions and spacings for this?—T. H. Kernick (Dawlish, Devon).

The transmitter in question operates on Channel 10, and the dipole should consist of 1ft. 1 $\frac{3}{4}$ in. each half, the reflector 2ft. 5in. and the directors 2ft. 3in. each. The spacing should be 1ft. 1in., which might be reducible to 10in.

### QUERIES COUPON

This coupon is available until JUNE 22nd, 1959, and must accompany all Queries sent in accord with the notice on page 571.

PRACTICAL TELEVISION, JUNE, 1959.

# We offer a . . . Unique Service

Immediate Delivery of New  
Re-built Tubes

with . .

12 MONTHS FULL GUARANTEE

## RETAIL PRICES

12" & 14" - - - £6 5 0

15" 16" & 17" - - - £7 10 0

21" - - - - - £11 5 0

TWO OR MORE AT 20% DISCOUNT

Full details from . .

## THE EXPRESS ELECTRONIC & CONSTRUCTION CO. LTD.

281 Parliamentary Road, Glasgow C.4

Telephone: BEL 4569

## RST

MAIL ORDER DEPARTMENT

211 Streatham Road, Mitcham, Surrey.

ALL VALVES LISTED ARE NEW STOCK

• Terms C.W.O. or C.O.D. Postage 3d. per valve.

MITCHAM 6201.

AZ31 10/6	EP85 7/6	N153 11/3	UCL31	6K7 4/6
B55 8/6	EP86 12/-	N154 11/3	6K7GT10/-	6K8GT10/-
DAF91 9/-	EP89 10/-	N727 8/6	UF41 9/-	6K9GT 12/3
DD62010/6	EP91 8/6	PCC8411/6	UF89 10/-	6L1 17/6
DF91 8/6	EP95 14/-	PCF80	UL41 9/6	6L6G 7/6
DH19 9/6	EL42 10/-	PCF82 12/6	UL84 9/-	6L18 15/6
DE31 9/-	EL44 9/-	PCF88 11/6	UY41 7/6	6L19 21/-
EABC80 9/6	EM80 10/-	PCL82 11/6	UY85 8/-	6N7G/GT 8/-
EM81 11/6	EM81 11/6	PCL83 12/6	VP4B 17/6	6N7GT 7/6
EAF4210/-	EY81 10/-	PCL84 15/6	WB1M 8/6	6S17GT 8/6
EB91 5/9	EY84 13/-	PEN41 11/6	W142 9/-	6S21GT 8/6
EB41 9/3	EY86 14/6	PEN44V 11/6	W19 8/6	6S27GT 8/6
EBF80 8/6	EY91 9/-	PEN4VA X78 19/-	W27 8/6	6S28GT 8/6
EBF89 9/6	EZ35 8/6	X79 17/-	X78 19/-	6S29GT 8/6
EC91 8/9	EZ40 8/-	Z21 10/6	X79 17/-	6S30GT 8/6
ECC33 8/6	EZ41 10/6	Z136 15/-	Z17 10/6	6S31GT 8/6
ECC38 8/6	EZ42 10/6	PL81 17/6	Z177 10/6	6S32GT 8/6
ECC83 9/-	EZ81 8/-	PL82 10/-	Z152 8/6	6S33GT 8/6
ECC84 10/-	FC2 14/6	PL83 14/-	Z152 8/6	6S34GT 8/6
ECC85 10/-	FC4 23/6	PL83 14/-	Z152 8/6	6S35GT 8/6
ECC86 10/-	FC13 14/6	PY82 8/6	Z152 8/6	6S36GT 8/6
ECF80 12/6	FC13C19/6	PY83 8/6	Z152 8/6	6S37GT 8/6
ECF82 12/6	GZ32 13/6	PY83 8/6	Z152 8/6	6S38GT 8/6
ECH35 12/6	H30 4/9	R10 22/-	Z152 8/6	6S39GT 8/6
ECH42 12/6	H63 10/-	R19 19/-	Z152 8/6	6S40GT 8/6
ECH81 9/6	HBC90 8/9	TD4 15/-	Z152 8/6	6S41GT 8/6
ECL80 12/6	HL52 11/6	TD4 15/-	Z152 8/6	6S42GT 8/6
ECL82 12/6	HL133D 11/6	U142 8/6	Z152 8/6	6S43GT 8/6
ECL84 13/6	KT33C 12/6	U147 9/9	Z152 8/6	6S44GT 8/6
EP37A 10/3	KT36 16/6	U153 9/6	Z152 8/6	6S45GT 8/6
EP40 15/-	LZ319 12/6	UABC80 10/-	Z152 8/6	6S46GT 8/6
EP41 9/6	MKT45 (or 7) 21/-	UAF4210/-	Z152 8/6	6S47GT 8/6
EP42 13/-	ML4 12/6	UBC41 8/6	Z152 8/6	6S48GT 8/6
EP50A 4/6	MSP4 15/-	UBF80 9/6	Z152 8/6	6S49GT 8/6
EP80 8/-	MX40 15/-	UCH42 10/-	Z152 8/6	6S50GT 8/6
	N142 9/6	UCH81 10/6	Z152 8/6	6S51GT 8/6

Quotations given for any types not listed. Obsolete and old types a speciality.


## COMPLETELY BUILT 8 WATT PUSH AMPLIFIER



Or 35/- deposit plus P. & P. 7/6 & 3 monthly payments of 25/-.

Complete with Crystal Mike and 8" Loudspeaker A.C. Mains 110/250 v. Size 10 1/2 in. x 6 1/2 in. x 2 1/2 in. Incorporating 6 valves. H.F. pen. 2 triodes, 2 output pens. and rectifier. For use with all makes and types of pick-up and mike. Negative feed back. Two inputs, mike and gram, and controls for same. Separate controls for Bass and Treble lit. For use with Std. or L.P. records, musical instruments such as Guitars, etc. £4.19.6 Plus P. & P. 7/6

## SIGNAL GENERATOR

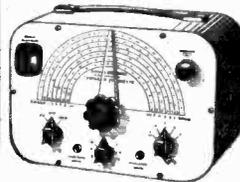


C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 1%.

£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kcs-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 1/2 in. x 6 1/2 in. x 5 1/2 in. Grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal Modulation of 400 c.p.s. to a depth of 30% modulated or unmodulated H.F. output continuously variable. 100 milli-volts.

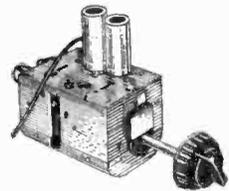
## FAMOUS MAKE "TELETUNER"

Covers all Channels, Bands I and III. Valves used: PCC84, R.F. double triode, cascade R.F. amplifier, PCF80, triode pentode, F.C. and mixer, I.F. output 33-38 Mc/s. Post 2/6 59/6 Knobs 3/6 per set extra.



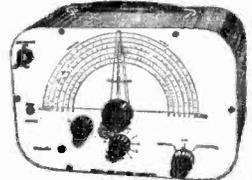
## SIGNAL & PATTERN GENERATOR

25/- deposit plus P. & P. 5/- and 6 monthly payments at 21/6. Cash £6.19.6 plus P. & P. 5/-. Coverage 1.6 Mc/s-210 Mc/s in five bands, all on fundamentals, slow-motion tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1% A.C. mains 200-250 v.



## AC/DC POCKET MULTI-METER KIT

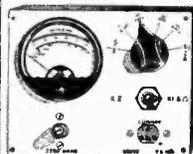

Comprising 2in. moving coil meter scale calibrated in AC/DC volts, ohms and milli-amps. Voltage range AC/DC 0-50, 0-100, 0-250, C 00, milli-amps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wire-wound pot (for ohms zero-setting), toggle switch, resistor and rectifier. Basic movement case. 2 mA. In grey hammer finished case.

19/6 Plus P. & P. 1/6. Built and tested 7/6 extra.

Point to point wiring diagram 1/-, free with kit.

## F.M. TUNER UNIT

Permeability tuned, by famous German manufacturer. Coverage 88-100 Kcs. Complete with ECC85, size 4 1/2 in. x 2 1/2 in.

25/- P. & P. 1/6.

## RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

**EDUCATIONAL**

**"HOW AND WHY"** of Radio and Electronics made easy by a new, non-maths, practical way. Postal instruction based on hosts of experiments and equipment building carried out at home. New Courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept. P.T.12, RADIO-STRUCTOR, 46, Market Place, Reading, Berks.

**INCORPORATED** Practical Radio Engineers home study courses of radio and T.V. engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text free. "The Practical Radio Engineer" journal, sample copy 2/-, 6,000 Alignment Peaks for Superhets. 5/9. Membership and Entry Conditions booklet 1/-. all post free from the SECRETARY, I.P.R.E., 20, Fairchild Road, London, N.8.

**STUDY RADIO, TELEVISION AND ELECTRONICS** with the world's largest home study organisation—I.C.S. Courses for the enthusiast and for those seeking examination qualification. Brit.I.R.E., City and Guilds, R.T.E.B., etc. Build your own equipment with Practical Radio Course. Write to-day for free book. INTERNATIONAL CORRESPONDENCE SCHOOLS. 71, Kingsway (Dept. 516), London, W.C.2.

**BUILD YOUR OWN HIFI** at home! At last, for reasonable cost—the chance to make your own quality HIFI Audio Equipment and to gain the knowledge to service and maintain it. Free brochure from: Dept. P.T.20, RADIO-STRUCTOR, 46, Market Place, Reading, Berks.

**EASY MATHEMATICS**.—Course 21/ for Radio/TV. Write: TUTORIALS, 200, Buchanan St., Glasgow, C.1.

**SETS & COMPONENTS**

**TELEVISION BARGAINS**, 12in. from £9, 14in. from £18, 17in. from £25. TYLER TELEVISION, 63, Lee High Rd., Lewisham, S.E.13. (Lee 5979.)

**MAKE YOUR OWN AERIALS** with our fully machined parts. Example: full kit of ready to assemble parts for 5-element array, plus 3ft. mast and universal clip, 35/-. post paid. Get our full lists and Aerial Data Chart for 1/- postal order, SKYLINE WORKS, Burnshall Rd., Coventry.

**LINE OUTPUT TRANSFORMERS**

**DIRECT REPLACEMENTS** for 500 sets. State make and model No. (3d. stamp).

**BRAYHEAD TURRET TUNER** for ANY AREA. The best converter! State Channels, set make, model No. £6.15.0, post, etc., 2/6.

**WESTWAY RADIO**

5 Westward Way, Harrow, Middx.

**RATES:** 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television", Tower House, Southampton St., Strand, London, W.C.2.

**SETS & COMPONENTS (continued)**

**SALVAGED VALVES**

All at 2/6 each

EF91	PCF90	U309
DH77	PCC94	B36
Z77	PCL83	KT39C
EB91	PY91	KT36
	U329	& Many Others

Minimum Order £1. S.A.E. for List. All Valves Tested on Mullard High Speed Valve Tester. C.W.O. to—

**ARION TELEVISION, 4 Macted Rd., S.E.15.**

**T.V. TUBES**, rebuilt, 12in., £6; 14in. and 17in., £7; 6 months' guarantee. Send for list. Dealers supplied. Aerials and Co-ax. cheap. H. CLAYTON & CO., 1, High St., Chalvey, Slough. (Tel.: 21860.)

**RF27 OR 26, 17/6; 24, 14/6**, brand new, p.p. 3/6; Bendix Receivers RA-10, 4-band superhet, 150 kc/s-10 mc/s, complete, good condition. £3/15/-. p.p. 10/-. E.W.S. CO., 69, Church Rd., Moseley, Birmingham.

**H.M.V. 15IN.** English Electric 15in., Ultra. etc. Televisions not working, originally £175 each. £5/10/-. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**BREAKING MANY TELEVISIONS**

**ALL SIZES ALL MAKES**

L.O.P.T. for most Sets from	£1. 5.0
F.O.P.T. " " " " "	12.6
S.O.P.T. " " " " "	3.0
Focus Mags. " " " " "	12.6
Scanning Coils " " " " "	15.0
Loudspeakers " " " " "	12.6 each
Condensers and Resistors, in large quantities only, at Special prices.	

The above quoted prices are average on most makes, but vary on late model sets. We can also supply new parts to order.

**TUBES**

Regunned, with 6 month guarantee. P.T. paid.	
12in. ... ..	£7.10.0
14in. ... ..	£8. 0.0
17in. ... ..	£9. 0.0
3 Hand T.V. Tubes. £3.10.0. No Guarantee.	

**TELEVISIONS**

Tunable any B.B.C. Programme.	
12in. ... ..	£12.10.0
14in. ... ..	£18. 0.0
17in. ... ..	£25. 0.0
12-Channel at £5.0.0 extra. Inc. Carr. & Ins.	
WASHING MACHINES, SPIN DRYERS, REFRIGERATORS AT KNOCK OUT PRICES	

**VALVES**

EP90, 5/-; PL38, 7/6; PL81, 10/6. All types in Stock, used, tested, all cheap. Send 8d. for Lists. C.W.O. or C.O.D. Despatched Immediately

ADDRESS :

**SPARES DEPT. 240D,**  
124/126, HAYDONS ROAD,  
LONDON, S.W.19.

Phone : CHE 2673.

TRADE ENQUIRIES WELCOMED

**SETS & COMPONENTS (continued)**

**TELEVISIONS**, 12in. to 17in., absolute bargains for home constructors. Some O.K. others require attention. From £3/10/-, carriage paid. Send for list. BERNISSON & CO. (BLACKPOOL) LTD., 69, Bond St., Blackpool.

**FIX IT YOURSELF AERIALS!** For high gain fit a 'PARABOLIC' Aerial. Excellent for anti-ghosting, equal to tube 6, 99%. Loft 3EL, 24" x Wall 5EL, 32/6; Clip on 5EL, 28" x BEL, 40" x Dipole + 5 Chimney Kit, 73" x Double 5 array, 72/6. VHF add on rods, 12/6. Indoor flexible, 11/6. Fringe Area super low loss co-axial, 1/3 vd. Standard low loss 71d. 3d. Diplexers, 10/- BRAYHEAD TURRET TUNER for any area. Will convert over 600 models, 135/- State model and channel. All items carriage paid. C.W.O. S.A.E. For Free List of Aerials, enquiries invited for full range of TV, Radio, Valves and Elect. Spares.

**HASE SUPPLIES**

34 Prince Street, Bristol (Dept. PD).

**THOUSANDS OF SPARES:** Transformers, Coils, Valves, Tubes, cheap, from dismantled radio, television sets, 1938-1958. We may have what you need, 9-19in Projection Tubes, 30/-; 12-14in., £3/10/-; 17in., £5. All picture tested! EF80, EF91, EB91, 3/6. Obsolete sets our speciality. Write, phone, call "ST. JOHN'S RADIO," 156, St. John's Hill, S.W.11 (BATtersea 9838.)

Save 30% on all outdoor aerials and fittings. Example: Double Five Array costs only 70/-. Self-contained Band III Pre-amplifiers only 60/-. Converters 100/- complete. Turret Tuners 94/- complete. Fringe Area Super Low Loss Co-axial, 1/4 yard. T.V. Tubes Rebuilt at keenest prices. Free Passenger Train Delivery all parts U.K. Also Revacuumed ones at lowest prices, all ex-stock. Tubes delivered in 24 hours all parts U.K. S.A.E. for Full Lists.

**G. A. STRANGE** North Wrexall, Nr. Chippenham, Wilts. Tel.: Marshfield 236.

**SEND DUD TUBE** for re-vac. o/c heater repairs (under 3 years old), 12in. and 14in., £3; 17in. and 21in., £4. Save money on spares and equipment; s.a.e., state requirements for reduced quote by return. Examples: Turret Tuner (new and guaranteed), 6 gns.; Factory Re-guns, 17in., £11/5/-. 61, Stanley Ave., Dagenham, Essex.

**CATHODE RAY TUBES** repaired and distributed by B.H.P. DISTRIBUTORS (LONDON) LTD., 379, Staines Rd, Hounslow, Middx. 12in.-17in., £7; 21in., £10/13/4; all tubes carry a 9 months' written guarantee. Trade discount 25%.

**TELEVISION TUBES**

NEW TV TUBES	£	s.	d.
12" MW 31-74	7	10	0
14" MW 36-24	8	0	0
14" AW 36-21	9	0	0
17" MW 43-64	10	0	0
17" MW 43-66	10	0	0
21" MW 53-80	15	0	0

FULLY Rebuilt TV Tubes	£	s.	d.
12" MW 31-74	4	0	0
14" MW 36-24	4	10	0
17" MW 43-64	5	0	0
21" MW 53-80	7	15	0
12" CRM 123	5	0	0
14" CRM 142	5	10	0
15" CRM 152	6	0	0
17" CRM 171	7	0	0
21" CRM 212	7	15	0

Carriage on all tubes 10/-

**CATHODE-RAY TUBE SERVICE**

35, Broomwood Road, St. Paul's Cray, Orpington 21265.

**SETS & COMPONENTS (continued)**

Television repossessions to be cleared by large company. All wide angle scanner. 14" upwards mainly 13 channel. Most makes. Prices ranging £60.00 to £120.00. Reduction for quantity. Personal callers only. Phone Portsmouth 32972 or call.

**LONDON TELEVISION**  
4 Henderson Road, Eastney, Portsmouth.

**TRANSFORMERS:** Audio 4k ohm CT to 700 ohm impedance. 12 watts. 12/6; input 230v. outputs 750-0-750v. 95 mA. 6.3v. and 5v. 15/-; 230v. to 0-4-5-6.3v. twice at 3 amps. 8/6; 110/230v. to 0-30-32v. 1A. 12/6; 230v. to 280-0-280v. 120 mA. 6.3v. 7A. 5v. 3A. 15/- (post 3/6). Relays. 12/24 v. coil; 4 make, 4 break contacts (10 amp. rated) by magnetic devices. 7/6. U.S.A. semi-rotary action. DPDT heavy silver contacts; SPDT and SPST lesser contacts. 6/37. 7/6. Switches, toggle. U.S.A. DPDT. 1/6. I.P. Strip 373. new with valves. 37/6. Vibrators, Mallory G634C. 12v. 4-pin. 7/6. R.F. 26, R.F. 27. good cond. 18/- (p.p. 3/6). Dynamotors (post 3/6). 12v. to 250v., 60 mA. and 6.3v. 2.5A., 11/6; 6v. to 250v., 60 mA. 10/6. Metal Rectifiers: 240v., 100 mA. 4/-; 250v., 80 mA. 5/6; 240v., 30 mA. 3/6; 1,000v., 30 mA. 7/6; R50. 3/6; J176. 7/6. Chokes. L.P. 10H. 120 mA. screened. 7/6. 5H. 200 mA. 4/6. R1155B new condition, tested, with handbook. £7/10/- (rail 10/-). SCR522 modulator or driver trans. either. 7/6. Indicators with C.R.T.s. VCR517 and VCR139A. 5 valves, etc. 50/- (rail 8/6); Single 6 1/2 in. C.R.T., 10 valves. 30/- (rail 7/6). Converters (rotary), 24v. D.C. to 50v. A.C. 4A. 40/- (rail 7/6). Mic Inserts, G.P.O., carbon. 2/6. Ear-pieces, inserts, bal. armature type. 2/6. Morse Trainer Set with buzzer and key, wired for 4v. battery. 3/6. Drives: slow-motion. Admiralty. 200:1 ratio, scaled 0-100. 5/6. R1155 S.M. "N" type, new. 10/6. Vibrapak. 6v. D.C. to 250v., 60 mA. smoothed case. 22/6; 12v. to 250v., 80 mA. 17/6 (p.p. 6/-). Meters, contain 2 separate microamp. movements and 2 neon. new. 8/6. Crossover Needle. 1 mA. x 2. 8/6. 2in. round flush. M.C. 100. 200. 300 mA. each. 8/6; 1 mA. 17/6; 4 1/2 in. mA. (40 ohm). 55/-; 4 1/2 in. Iron Flush. 250v.. M.I. 500 cycles. 10/-; Valveholders. U.S.A. Octal. doz. 4/-; Potentiometers, 100 k. or 500 k. new. doz. 5/-; Preset w/w pots. 1 k. or 2 k. miniature. 1/3. Trimmers. 2-12 pf. air-spaced, ceramic. 1/3. List and enquiries: s.a.e. please! Terms: c.w.o. Postage extra. Immediate despatch. W. A. BENSON (PT), 136. Rathbone Rd., Liverpool. 15.

**C. EDWARDS**

1070 HARROW ROAD,  
LONDON, N.W.10  
LADBROKE 1734

Offers  
S/H T.V. in  
First-class  
Condition  
12in. £8. 0. 0.  
14in. £12. 0. 0.  
17in. £17. 10. 0.  
(all 5 channel)  
-10/- carriage



Guaranteed tubes, all sizes. 12" 14" 17" £5 ea.  
in stock: **PYE, FERGUSON, EKCO**  
CASH ONLY. 10/- Carriage.  
Trade Enquiries Welcome.

**SETS & COMPONENTS (continued)**

**CALLING** 9in. Television owners. Brand new, factory fresh. 9in. Ferranti Tubes, originally £14/10/-, will replace Mazda. Brimar, G.E.C., etc. £4/10/- each, 6 months' guarantee. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**T.V. TUBES.** factory reconditioned. 6 months' guarantee. 12in. and 14in. Mullard and Mazda. £4; 16in. and 17in. Mullard and Mazda. £5; c.w.o. carriage and ins. 10/- RAYVAC TUBE CO., 7, Oakfield Ave. Manchester. 16. (Phone: Moss Side 2611.)

**BRAND NEW TUBES**

Now available with 12 months' guarantee at the following prices. 12in. £8.5.0, 14in. Rectangular or Round £9.10.0, 15in. £10.10.0, 17in. £11.10.0, 21in. £14.0.0. These cover Mazda and Mullard types or equivalents only, but we can offer any other type not covered by these as a completely rebuilt tube with new screen and new gun. These are virtually new tubes and carry a 9 months' guarantee. Same prices as above. All prices include carriage and insurance. S.A.E. with all enquiries.

**A.E.R. SERVICES**

36a, York Street, St. Helens, Lancs.  
Telephone: St. Helens 7947.

**CRM 121 "MAZDA" TUBE,** brand new and unused. 1 only, bought in error, complete in maker's carton and guaranteed. Price £11/10/-, carriage paid; insured. (Listed at £18/14/1.) R. W. BEAVEN, 29, Pettibone Rd., Witney, Oxon.

**YOUR GUARANTEE TO CHEAPER VIEWING**

Renfrew Electronics, Anderson Drive, Renfrew.

- 17 Mazda Tube with new American Gun-mount ... £7.15.0
- 14 Mazda Tube with new American Gun-mount ... £8.10.0
- 17 Mullard Tube with new American Gun-mount ... £7.15.0
- 14 Mullard Tube with new American Gun-mount ... £8.10.0
- For the First Time available from us:
- 17 Mullard Tube with new Mullard Gun-mount ... £8. 5.0
- 14 Mullard Tube with new Mullard Gun-mount ... £7. 5.0

One year's Guarantee.  
Cash with Order: 7/6 allowed on old tube returned in carton supplied. Dealers' Inquiries invited.

**FOR SALE**

**100 BAYS** of brand new adjustable steel Shelving. 72in. high x 34in. wide x 12in. deep, stove enamelled dark green; sent unassembled, 6-shelf bay, £3/15/-; sample delivered free; quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. (Tel.: 69018.)

**ASTOUNDING VALUE.**—9in. Televisions. £9/10/-; 12in. Televisions. 10/-; 14in. £9/10/-; 15in. £5/10/-; 17in. £14. Complete but not guaranteed working; as received in part exchange. TOMLINS, 127, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available; carriage 7/6.

**FOR SALE (continued)**

**VALVE CARTONS** at keen prices. Send 1/- for samples and list. J. & A. BOXMAKERS, 75a, Godwin St., Bradford, I.

**1,000 TELEVISIONS,** all makes, from £3 working, 10/- not callers only 9 till 6, including Sats. 39, Whitehorse Lane, Stepney, London.

**MAKING YOUR OWN TELESCOPES,** Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc. then our booklets "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2. 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. H. W. ENGLISH, Rayleigh Rd., Hutton, Brentwood, Essex.

**SPECIAL OFFER.**—Famous Pye Invicta 12in. 13 channel Television (without tubes or valves) £2 15/-, otherwise complete. Each one with walnut cabinet and Pye 13-channel turret. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**VALVES,** Condensers, Record Changers and Players, Cabinets, Amplifiers, Speakers, etc., etc. Send for free list to: H. F. JAMES, 21, Claremont Rd., Twickenham, Middx.

**RECLAIMED VALVES,** tested and perfect. Huge stock, all types, price 5/- plus 6d. postage each; delivery by return. LEWIS, 57, Chalfont Walk, Woodford Green, Essex.

**ASSORTED RESISTANCES** 10-gr., your choice 12/- gr., 1/6 p. and p. Send for list of components available. LEDSHAM TRADING CO., Ledsham, Wirral.

**TEST EQUIPMENT BARGAINS.**—45A and 45B Taylor Valve Testers, with modern adaptors and valve charts, £8 and £11 respectively. American Genometer, Model TV.50 Signal Generator (110v. AC) £10. 77A Taylor Multimeter, 20,000 o.p.v. in new condition. £9. 88A Taylor Universal Multimeter, 20,000 o.p.v. in new condition. £12/10/-. G.E.C. Frequency Meter 40-75 kc/s. £6. 260A Taylor TV Wobbulator, combined with scope, practically new. £18/10/-. 120A Taylor Multimeter. £4/10/-. All instruments in perfect working condition, supplied with instruction manuals. E. STRAUSS, 9, Keble Rd., Maidenhead, Berkshire.

**SATISFACTION ASSURED.**—12in. Televisions. £9/10/-; 14in. £16; 17in. £19/10/-; Write for quotation, stating requirements. We guarantee satisfaction. TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

**TELEVISIONS.** 12in., 14in., 17in. and Projection. Require attention. From £3.10.0, carriage paid. In working order—12in. B.B.C. from £8; 17in. B.B.C./I.T.A. from £25. Send us your requirements.

**CADMAN'S**

Service Department Bryan Street, Hanley, S.O.T.

(Continued overleaf)

**WANTED**

**ALL TYPES OF VALVES WANTED.** EL81, ECL80, EY51, U25, PCF80, PZ30, U801, etc., etc. Best cash price by return. **STAN WILLETTS, 43, Spon Lane, West Bromwich, Staffs.** (Tel.: WES 2392.)

**A PROMPT CASH OFFER** for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S. 155, Swan Arcade, Bradford. 1

**IMPORTANT!** New Valves and Metal Rectifiers wanted, state price. Same day payment. **ROBERT A.14, Whitefoot Lane, Bromley, Kent.**

**NEW VALVES WANTED.** EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. **DURHAM SUPPLIES, 175, Durham Rd., Bradford, 8, Yorks.**

**SITUATIONS VACANT**

**RADIO/TELEVISION SERVICEMAN** required in Nigeria to service domestic radio/television receivers and tape recorders sold by a large retail organisation. Must be capable of controlling a workshop and supervising and training local mechanics. Contract of 24 months at a salary of £1,250 p.a. with possibility of further contracts. Free passages, free fully furnished accommodation and family allowances with gratuity on satisfactory completion of contract.

Apply stating age, qualifications and experience to: Box 18, c/o PRACTICAL TELEVISION.



**A career on good pay in a skilled, expanding trade**

## RADAR OR WIRELESS MECHANIC in the Royal Air Force

Immediate vacancies; full training for suitable applicants in skilled radar and wireless maintenance, etc., full allowances and all found; month's leave a year; chance to travel, plus all the wider interests of Service life. Call or write for details to: Central Recruiting Office, Dept. PTN 525, Victory House, Kingsway, London, W.C.2.

**SERVICE SHEETS**

**SERVICE SHEETS.**—1 working day delivery. T.V., 4/- ea. Radio. Domestic Electrical Equipment and ex-Government Equipment, 3/- ea. plus postage. Faultfinder Files on all makes and types, 2/- ea. plus postage. Manuals for hire and sale List 1/-; s.a.e. with inquiries, please. **SULTAN RADIO, 23b, Albert St., Tunbridge Wells, Kent.**

**SERVICE SHEETS.**—We have the largest stock of Radio and T.V. Service Sheets in the country for sale at 4/- each. Why tolerate delay in obtaining Service Sheets when we will despatch by return? List 1/-; s.a.e. with enquiries, please. **S.P. DISTRIBUTORS, 11, Old Bond St., London, W.1.**

**SERVICE SHEETS** and Manuals for sale from 1/- ea.; Radio and Television. List 1/-; s.a.e. with inquiries, please. **GLOBE SUPPLIES, BCM/ Electricque, London, W.C.1.**

**TELEVISION SERVICE SHEETS,** over 100 sheets covering 330 popular models, 18/6, post free. Send for full details. All types of Service Sheets for sale and hire. Radio Television, Electronics Books, Television Servicing, 5/-; Radio Servicing, 4/-. List free. **HAMILTON RADIO, BCM/ DATA3, London, W.C.1.**

## SPECIAL VALVE OFFER FOR LIMITED PERIOD

EF80	6/-	PY82	6/6	6P28	7/6
10F1	7/-	PL82	6/6	EB34	1/6
6F1	7/-	PL83	6/6	7C5	5/6
EB91	4/6	6P25	7/6	7Y4	5/6
EF91	5/-	KT33C	7/-	3D6	2/-
ECL80	8/6	EY83	7/6	1625	5/-
DH77	6/-	UCH42	8/6	807	4/-
UL46	8/6	SP61	3/-	4D1	2/6
6F13	6/6	SP41	3/-	EB41	7/-
6F14	6/6	Z63	6/-	6L18	9/6
6F15	6/6	Z66	6/-	N37	9/-
6L1	7/6	B36	7/-	20LD20	9/-
20L1	7/6	L63	5/-	UF42	8/-
20F2	7/-	65N7GT	5/6	UF42	8/-
PY80	6/6	20P1	7/6	6F6G	6/6

Postage 6d. per Valve.

Air-Spaced Coaxial Cable 75 ohms, 8d. per yard; Ion Traps, 5/-; F.M. Twin Feeder, 4d. per yard; T/V Aerials, Band III, 3 E1., 23/6; 8 E1., 57/6; F.M. Aerials, Single Dipole Wall Fixing, 29/6.

**MAIL ORDER ONLY—NO CALLERS.**

Terms: C.W.O. or C.O.D. Minimum C.O.D. charge 3/6. Postage and Packing other than valves: Under £2, 1/6; Under £5, 2/-; Aerials, 2/6 Carriage.

## ELECTRO-SERVICES & Co.

**221 BATTERSEA PARK ROAD, LONDON, S.W.11. MAC 8155**

### MAZDA TRIODES RE-BUILT

We specialise in Mazda 2 volt tube re-builds. No mass production, individual attention to each tube. 152, 27; 121, 123, 25, 10, 0. Mullard 12in. and 14in., 25; 17in., 25. Carriage and packing 7/6. You must supply a tube either in exchange or your own re-built. We do not handle any other types. Send by rail only.

### SONCO ELECTRIC

**19, ALLEN ROAD, WEDNESBURY, STAFFS.** Phone: Wednesbury 1165



## The Royal Air Force

### PILOTS, NAVIGATORS AND AIR ELECTRONICS OFFICERS COMMISSIONS IN THE GENERAL DUTIES BRANCH

Vacancies now exist for fit young men of character and good education and who are capable of taking responsibility, to train as pilots, navigators or air electronics officers in the general duties branch of the Royal Air Force.

#### Methods of Entry

**University Entry**—University graduates may enter on permanent or four-year short-service commissions. Permanent commissions carry an ante-date. University students may be accepted subject to graduation. Age limits: 19 to 24. (26 for short-service commissions.)

**Direct Commissions**—The direct commission scheme offers the choice of a permanent career leading to a pension, or a twelve-year commission with the option of leaving after eight years. Age limits: 17½ to 25.

**Short-Service Commissions**—The short-service commission is for

five years and there are opportunities for transfer to either form of direct commission. Age limits: 17½ to 21.

**Pay and Gratuities**—Pay is high and terminal gratuities are generous. For example, a Flight Lieutenant of 25 can earn, with full allowances, nearly £1,700 a year. The tax-free gratuity paid at the end of a twelve-year commission is £4,000.

Write for further details, stating age and education, and the method of entry in which you are interested to the Air Ministry, Dept. PTN526, Adastral House, London, W.C.1.

# Quality in Tubes

**NOW AT GREATLY REDUCED PRICES**



New price lists for Vidio rebuilt C.R. Tubes are now available on request. All tubes fitted with new Electron Gun Units and delivered immediately, carriage free in the U.K.

**7 MONTHS GUARANTEE**

For full details write or call :

**VIDIO REPLACEMENT CO.**

HALES STREET, DEPTFORD HIGH STREET, LONDON, S.E.8.

Telephone : TIDeway 4506

## SUPER-VISION LIMITED

Every Item Brand New and Guaranteed at Low Prices.

### VALVE HOLDERS

Int. Octal 4d. each. B7G 4d. each. B9A 6d. each. CER. B9A with screen 1/9 each.

### CONDENSERS

2 to 100 pF. 5d. each. 220-5,000 pF. 7d. each. .01 to .1 8d. each.

### RESISTANCES

Variable T/V type pots. 3K 5K 25K and 1M 2/6 each.

### EGEN SLIDER TYPE

3K 5K and 25K 1/9 each.

### VOLUME CONTROLS

.5M 2/9 each. 5.M with DPS switch, 4/3 each.

### ELECTROLYTICS

60/100 mfd., 5/6 each. 32+32+16 mfd., 350 v., 3/6 each.

Clips, 3d. each. 50 mfd., 12 v., 8d. each.

### AUTO TRANSFORMERS

50 w. to 1,000 w., from £1.10.0 to £9.0.0.

D.C./A.C. CONVERTERS for operating shavers, radio and tape recorders from 6 and 12 v. car batteries.

6 v. D.C. to 230 v. A.C. 20 w. shaver converter, £2.15.0

6 v. D.C.—230 v. A.C. 30 w. converter for radio, etc., £4.5.0

12 v. D.C.—230 v. A.C. 20 w. shaver converter, £3.18.0

12 v. D.C.—230 v. A.C. 40 w. converter for radio, etc., £6.10.0

12 v. D.C.—230 v. A.C. 80 w. converter for tape recorder, £12.15.0

Other types available. Send for List. Please include sufficient to cover Postage.

## SUPER-VISION LIMITED

136 High Street, Teddington, Middlesex. KINgston 4393

## TELEVISION SERVICING

Vol. 4.

### PRACTICAL SERVICING AND FAULT-FINDING

More than 400 faults on a typical receiver have been considered, a large number of which have been placed on the receiver to obtain static and dynamic readings and oscillograph records.

The circuit has been divided into the various sections which are contained in fold-out pages at the ends of the book, and so can be viewed clear of the text.

By G. N. Patchett.

7/6.

6d. Postage.

### TELEVISION ENGINEER'S POCKET BOOK, by J. P. Hawker, 12/6. Postage 8d.

### THE OSCILLOSCOPE AT WORK, by A. Haas and R. W. Hallows, 15/-.

### A BEGINNER'S GUIDE TO TELEVISION, by F. J. Camm, 7/6.

### THE RADIO AMATEUR'S HANDBOOK, by A. R. R. L., 1959 ed., 32/6. Postage 1/9.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET, LONDON, W.2.

Complete catalogue 6d. Phone : PADdington 4185. Open 6 days 9-6 p.m.

## TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

Rewinds to all makes.

**H.W. FORREST (Transformers) Ltd.**

Shirley, Solihull, Warwickshire

Tel. : Shirley 2483

## QUALITY REBUILT TUBES

Mullard and Mazda types only, 12in., £7.10.0; 14in., 25; 17in., 29. Fully guaranteed 6 months plus additional 6 months conditional guarantee, 48 hr. Service. C.W.O. or C.O.D. All tubes plus 10/- carriage and insurance.

## B.B.C.-I.T.V.-F.M. AERIALS



B.B.C. (BAND 1). Telescopic loft, 19/8. External, S/D. 26/3.

I.T.V. (BAND 3). 3 Element loft array, 24/5. Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. I.T.V. Loft 1+3 Element, 41/3. 1-5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element 63/8. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H", 28/-, 3 Element loft, 52/6. S/D loft, 12/6. External S/D 26/3. State channel when ordering. C.W.O. or C.O.D. P.F. 2/6. Coaxial cable, 8ft. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept. T.P.)**

3B, GODSTONE ROAD, KENLEY, SURREY

## COVENTRY RADIO LTD.

189/191, Dunstable Road, Luton

If you are unable to visit us at Luton, why not send for one of our

"HI-FI" CATALOGUES?

Price 1/-, plus 6d. postage.

70 pages and listing over 300 items.

Also now on sale: "THE GRUNDIG BOOK."

Price 12/6, plus 1/- postage.

The owner of any make of tape recorder will find this book an essential for successful recording.

## LUTON'S HI-FI CENTRE

Telephone : Luton 7388/9.

## EDDY'S (Nottm.) LTD.

DEPT. P.T.  
172 ALFRETON ROAD  
NOTTINGHAM

**TRANSISTORS.** Yellow/Green Spot, 6/11. R.F. Yellow/Red, 13/11. Post 4d.  
**SUB-MINIATURE TRANSISTOR CONDENSERS.** 1.6 mfd., 5 mfd., 8 mfd., 10 mfd., 16 mfd., 32 mfd. 2/6 each. Post 4d.  
**THROAT MIKES.** 1/- each. Post 6d.  
Can be used for electrifying musical instruments.

**NEON MAINS TESTER/SCREW-DRIVERS.** 4/6 each. Post 6d.  
**JACK PLUGS.** Standard type, I/11. Post 6d.

**GERMANIUM CRYSTAL DIODES.** 1/- each, 10/- dozen. Post 4d.

**MORSE TAPPERS PLATED CONTACTS.** Adjustable gaps, heavy duty, 3/6. Post 9d.

**CONDENSERS TUBULAR WIRE END.** (Not Ex-Govt.) 8 mfd. 450 v., 1/9; 8-8 mfd. 450 v., 2/9; 16-16 mfd. 450 v., 3/9; 16-8 mfd. 450 v., 4/-; 32 mfd. 450 v., 3/9; 32-32 mfd. 450 v., 4/-, Post 9d.

**ACOS CRYSTAL TURNOVER PICK-UPS** (2 Sapphire Stylus) 29/11. Post 2/6.  
**GUITAR PICK-UP "THE ELECTRO."** Super Hi-Fi. Non-acoustical universal fitting. 3in. x 1 1/2in. x 1/2in. High output. Complete with lead and plug. Full and easy instructions. 39/11. Post 1/6.

**RECTIFIERS.** Contact cooled, 250 v. 60 m.a., 9/6. Post 1/6.  
**ROTARY CONVERTER** for Electric Trains, etc. Converts 200 v. D.C. to 12 v. D.C. 19/11. Post 2/6.

**25 x 25 mfd. CONDENSERS.** Size lin. 1/3. Post 6d.

**CONDENSERS (METAL).** 50-50 mfd. 400 v. D.C. 5/6. Post 1/6.  
**NIFE ACCUMULATORS.** Midget single unit. Size 3in. x 2 1/2in. x 3/4in. 1/11. Post 1/6.

**DYNAMOTORS.** 200 volts D.C. to 12 v. D.C. Ideal for train sets for D.C. mains. 19/11. Post 2/6.


**B.S.R. MONARCH 4-SPEED AUTOMATIC RECORD CHANGER.** Type UAB, complete with Hi-Fi turnover head. Capacity of 10 records. 100-200 volts A.C. £6.19.6. Carriage 5/-.

All above are new and guaranteed.

Surplus, New and Guaranteed Valves			
1D5	9/6	6Q7G	8/6 954
1R5	7/6	6SA7M	5/- 955 3/11
1SS	7/6	6SK7GT	4/11 956 2/11
1T4	5/11	6SG7M	5/- AZI 12/6
5U4G	6/6	6SN7GT	5/- AZ31 9/6
5Y3GT	8/-		CY31 12/11
6AG5	5/-	6V6G	5/11 DAF96 8/6
6BA6	7/6	6V6GT	6/6 DF96 8/6
6B8E	7/6	6X5GT	5/11 DL96 8/6
6B8G	2/11	6Z4/84	11/6 DK96 8/6
6C4	4/6	7B7	8/- EF36 2/6
6CH6	10/6	7C5	8/- EF37 4/6
6D6	5/-	7C6	7/9 EF50 2/9
6F1	9/-	7H7	8/- EF50(R) 4/-
6F6M	7/6	757	9/6 EF80 7/6
6F13	9/-	10F1	9/- EF86 13/6
6F15	11/-	12AH8	9/6 EF91 5/-
6F33	6/6	12AT6	9/6 GTIC 7/6
6H6M	2/6	12AT7	6/- L63 3/-
6J5G	2/11	12AU7	7/6 PCC84 8/6
6J5GT	3/11	20P1	14/- PCF80 9/-
6J5M	4/6	25A6G	9/6 PZ30 9/6
6J6	4/6	90AV	7/6 VR/150/130 7/6
6K7G	2/6	807(B)	3/9
6K8G	6/11	807(USA)	
6P28	11/-		Z66 9/6

**ALL TESTED BEFORE DESPATCH**  
C.W.O. or C.O.D. only. Postage and packing 6d. extra per valve. Over £3 free. S.A.E. with enquiries.  
Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk. Trade Enquiries invited.

## 59 Gns.—'17'

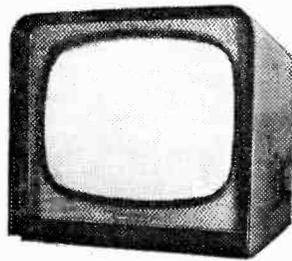

A full specification 17in. Television Receiver to Spencer-West standards now available at your Dealers. Remarkable performance and priced at 59 Gns. only, complete.

For Leaflet apply to:—

**SPENCER-WEST LTD.**  
Quay Works, Great Yarmouth  
Norfolk

Phones: Works 4794; Sales 3009  
Grams: Spencer-West, Great Yarmouth

## LINE OUTPUT TRANSFORMERS

Most types available. State Make and Model Number of Receiver when ordering.

S.A.E. please with all enquiries.

**HOWORTH**  
51 POLLARD LANE,  
BRADFORD, 2, YORKS  
Tel. 37030

## CHASSIS

18 swg Aluminium. Strengthened corners. 6" x 4" x 2 1/2" 4/- 11 1/2" x 7 1/2" x 2 1/2" 7/6 7 1/2" x 5 1/2" x 2 1/2" 5/6 12" x 8" x 2 1/2" 8/- 10" x 7 1/2" x 2 1/2" 6/6 14" x 8" x 2 1/2" 11/- Prompt service. Add 1/- post and pack. Orders over £1 post free. Punching and drilling to your requirements. Chassis for all Mullard circuits available.  
**Sweetnam & Bradley Ltd. Dept. AX**  
BRISTOL ROAD, MALMESBURY, WILTS.

## GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

**WESTINGHOUSE J.50.** Pencil Recs. 500 v. 5 mA. 5/- each.  
**PRE-SET POTS.** New. 1 K. to 2 meg. assorted, 15/- doz.  
**METERS.** 0-1 mA. 2 in. diam., 20/- each. 500-0-500 microamp. 3 1/2 in. diam., 37/6 each.  
**HI-FI CRYSTAL CARTRIDGES.** Turn-over type for Garrard and B.S.R., 16/6 each.  
**I.T.A. AERIALS.** New and Boxed. 3 element, 22/6. 5 element, 27/6. **CABLES.** 6d. per yd. **AIR SPACED.** 9d.  
**NIFE CELLS.** 3 x 2 1/2 x 1 1/2 in. Unused. 5/- ea., 48/- doz.  
**GERMANIUM CRYSTAL DIODES.** 1/- per doz.  
**HEADPHONES.** Moving iron, low impedance. 6/-, high, 9/- . Balanced armature, low, 10/-, high, 15/- . Moving coil, low only, 10/- per pair.  
**GLASS FUSES.** 1 1/2 in., 2 and 10 amp. only. 5 for 1/- .  
**MASS POWER PACKS.** 250 v. 80 m.amp. or stabilised 150 v. 80 m.amp. with 6.3 v. winding. 30/- .  
**RELAYS.** High speed, 1,000-1,000 ohms. plat. cont., 7/6.  
**VALVES.** All valves tested before despatch on MULLARD'S latest ELECTRONIC TESTER.

1L4	5/- 6J5	6/- 12AT7	7/6 EF37A	9/-
1T4	6/6 6J6	6/- 12AU7	7/- EF39	5/6
1U4	6/- 6J7	6/- 12AX7	8/6 EF80	8/6
1A4	6/- 6K7	4/6 12BH7	10/- EF91	7/-
5Z4	9/6 6L6	6/6 12SH7	6/- EF92	8/-
4D1	4/- 6SA7	7/- 12SJ7	7/6 EL32	5/-
6AG5	5/- 6SC7	4/6 12SK7	6/- EL91	5/6
6AL5	5/6 6S7	6/- 15D2	6/- EY51	6/-
6AM5	5/- 6SN7	5/- 50C5	10/- EY51	9/-
6AM6	7/6 6SL7	7/- 30T	8/- P81	4/-
6AQ5	7/6 6SN7	7/6 EA50	1/6 Pen46	7/-
6AU6	8/- 6U5	7/6 EABC80	SP61	4/-
6BA6	8/- 6V6	6/6	VR150.30	
6BE6	7/- 6X4	7/- EB41	7/6	5/-
6B16	5/- 6X5	7/- EB91	5/6 UL84	9/-
6C4	6/6 8D2	4/6 ECH42	10/- VCR37	15/-
6C4	6/- 9D2	5/- ECL80	10/- VCR138A	
6D2	6/- 10P1	7/6 EF36	6/-	25/-
6P6	7/- 12A6	7/6 EF50	3/6 VCR139A	
6P13	7/6 12AH8	8/- EF50	5/-	25/-

OBsolete TYPES. LARGE STOCKS. ENQUIRIES INVITED.

SECONDHAND VALVES. YOUR CHOICE. £1.00 for EIGHT. PL81, ECL80, 6C4, 6AM6, 6AG5, 6J6, EF50, 6BE6, 3A4, PCF80, EF80, SP61, P61, 6J5.

**HUGGETT'S LIMITED**  
2-4 PAWSONS ROAD,  
WEST CROYDON


**RES/CAP. BRIDGE 37/-**  
p. & p. 2/-  
Checks all types of resistors, condensers 6 RANGES  
Built in 1 hour. Direct reading  
**READY CALIBRATED**  
Stamp for details of this and other kits.  
**RADIO MAIL (Dept. VO)**  
Raleigh Mews, Raleigh Street, Nottingham

## RADIO AND TELEVISION COMPONENTS

We operate a prompt and efficient MAIL-ORDER Service. 3d. stamp (only) for Catalogue.

**JAMES H. MARTIN & CO.**  
FINSTHWAITE, NEWBY BRIDGE,  
ULVERSTON, LANCs.

# Build your own Aerials...

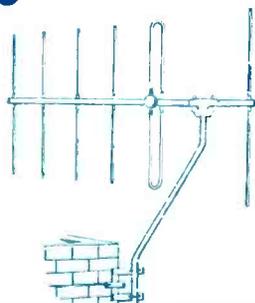

## AT HOME

**AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.**  
 Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above to :-

*Fringevision Ltd.*

MARLBOROUGH, WILTS. Phone : 657/8

Save £££

12 Months' Guarantee

# FACTORY REBUILT... TELEVISION TUBES

Immediate delivery

Double the guaranteed life of a new tube

### TYPES

MW31-74	- 12 in.	<b>£5 . 12 . 6</b>	MW36-24/44	14 in.	<b>£5 . 17 . 6</b>
MW43-64/69	17 in.	<b>£7 . 0 . 0</b>	MW53-20/80	21 in.	<b>£9 . 10 . 0</b>
CRM141	- 14 in.	<b>£5 . 17 . 6</b>	CRM152-153	- 15 in.	<b>£6 . 5 . 0</b>
CRM171	- 17 in.	<b>£7 . 0 . 0</b>			

TERMS TO  
THE TRADE

Plus 10% carriage and insurance.  
Cash with order or C.O.D.

**RE-VIEW (LONDON) LTD.**  
 81, High Street - - - Merton, S.W.19

Telephone: Cherrywood 3255

**C.R.T. ISOLATION TRANSFORMERS**  
TAPPED MAINS PRIMARIES  
TYPE A. OPTIONAL 25% and 50% BOOST.  
2 v. OR 4 v. OR 6.3 v. OR 10.8 v. OR  
13.3 v. 12/6.

**OUR LATEST SUPERIOR PRODUCT**  
TYPE A2. HIGH QUALITY, LOW CAPACITY.  
10 to 15 pF. OPTIONAL BOOST 25%, 50%  
or 75%. 16/6 EACH.  
TYPE B. MAINS INPUT, MULTI OUTPUT 2,  
4, 6.3, 7.3, 10 AND 13 VOLTS. BOOST 25%,  
AND 50%. LOW CAPACITY. 21/-

**TRIMMERS.** Ceramic. 30, 50, 70 pF. 9d. 100 pF.  
150 pF. 13/- 250 pF. 16/- 500 pF. 250 pF. 19/-  
RESISTORS, Preferred values. 10 ohms to 10 meg.  
1 w. 4d. 1/2 w. 4d. 1 w. 8d. 1 1/2 w. 2s. 1/2 w.  
10 w. 10 pF. 100 pF. 1000 pF. 500 pF. 0.9d.  
5 watt. WIRE-WOUND RESISTORS 1/3  
10 watt. 25 ohms -10,000 ohms 1/6  
15 watt. 25 ohms -10,000 ohms 1/2  
15,000 ohms -10,000 ohms. 5 w. 19/- 10 w. 2/3

**GEVAERT GEVASONOR**  
50% extra long play plastic tape. 1,700 ft. 7in.  
Reel. 35/-; 850ft. 5in. reel. 21/-  
**SUPERIOR 1,200 ft. Plastic Tape on 7" Plastic**  
Reels. Quality Guaranteed. 21/-  
**SPARE REELS. ALL SIZES. 8/-**  
\*Instant\* Bulk Tape Eraser, 200 250 v. A.C.  
for any make or size of tape. 27/6

**O.P. TRANSFORMERS.** Heavy Duty 50 mA., 4/6  
Multitap, push-pull, 7/6. Miniature, 38/- etc., 4/6  
**L.F. CHOKES** 100 mA. 6.3 v. 5/-; 10 H.  
85 mA. 10/8; 10 H. 150 mA. 14/-

**MAINS TRANSFORMERS 200/250 v. A.C.**  
STANDARD. 250-250, 80 mA. 1.3, 2.5, 5, 10, 15, 20, 25, 30, 40, 50, 60, 70, 80, 90, 100, 110, 120, 130, 140, 150, 160, 170, 180, 190, 200, 210, 220, 230, 240, 250, 260, 270, 280, 290, 300, 310, 320, 330, 340, 350, 360, 370, 380, 390, 400, 410, 420, 430, 440, 450, 460, 470, 480, 490, 500, 510, 520, 530, 540, 550, 560, 570, 580, 590, 600, 610, 620, 630, 640, 650, 660, 670, 680, 690, 700, 710, 720, 730, 740, 750, 760, 770, 780, 790, 800, 810, 820, 830, 840, 850, 860, 870, 880, 890, 900, 910, 920, 930, 940, 950, 960, 970, 980, 990, 1000, 1100, 1200, 1300, 1400, 1500, 1600, 1700, 1800, 1900, 2000, 2100, 2200, 2300, 2400, 2500, 2600, 2700, 2800, 2900, 3000, 3100, 3200, 3300, 3400, 3500, 3600, 3700, 3800, 3900, 4000, 4100, 4200, 4300, 4400, 4500, 4600, 4700, 4800, 4900, 5000, 5100, 5200, 5300, 5400, 5500, 5600, 5700, 5800, 5900, 6000, 6100, 6200, 6300, 6400, 6500, 6600, 6700, 6800, 6900, 7000, 7100, 7200, 7300, 7400, 7500, 7600, 7700, 7800, 7900, 8000, 8100, 8200, 8300, 8400, 8500, 8600, 8700, 8800, 8900, 9000, 9100, 9200, 9300, 9400, 9500, 9600, 9700, 9800, 9900, 10000, 11000, 12000, 13000, 14000, 15000, 16000, 17000, 18000, 19000, 20000, 21000, 22000, 23000, 24000, 25000, 26000, 27000, 28000, 29000, 30000, 31000, 32000, 33000, 34000, 35000, 36000, 37000, 38000, 39000, 40000, 41000, 42000, 43000, 44000, 45000, 46000, 47000, 48000, 49000, 50000, 51000, 52000, 53000, 54000, 55000, 56000, 57000, 58000, 59000, 60000, 61000, 62000, 63000, 64000, 65000, 66000, 67000, 68000, 69000, 70000, 71000, 72000, 73000, 74000, 75000, 76000, 77000, 78000, 79000, 80000, 81000, 82000, 83000, 84000, 85000, 86000, 87000, 88000, 89000, 90000, 91000, 92000, 93000, 94000, 95000, 96000, 97000, 98000, 99000, 100000, 110000, 120000, 130000, 140000, 150000, 160000, 170000, 180000, 190000, 200000, 210000, 220000, 230000, 240000, 250000, 260000, 270000, 280000, 290000, 300000, 310000, 320000, 330000, 340000, 350000, 360000, 370000, 380000, 390000, 400000, 410000, 420000, 430000, 440000, 450000, 460000, 470000, 480000, 490000, 500000, 510000, 520000, 530000, 540000, 550000, 560000, 570000, 580000, 590000, 600000, 610000, 620000, 630000, 640000, 650000, 660000, 670000, 680000, 690000, 700000, 710000, 720000, 730000, 740000, 750000, 760000, 770000, 780000, 790000, 800000, 810000, 820000, 830000, 840000, 850000, 860000, 870000, 880000, 890000, 900000, 910000, 920000, 930000, 940000, 950000, 960000, 970000, 980000, 990000, 1000000, 1100000, 1200000, 1300000, 1400000, 1500000, 1600000, 1700000, 1800000, 1900000, 2000000, 2100000, 2200000, 2300000, 2400000, 2500000, 2600000, 2700000, 2800000, 2900000, 3000000, 3100000, 3200000, 3300000, 3400000, 3500000, 3600000, 3700000, 3800000, 3900000, 4000000, 4100000, 4200000, 4300000, 4400000, 4500000, 4600000, 4700000, 4800000, 4900000, 5000000, 5100000, 5200000, 5300000, 5400000, 5500000, 5600000, 5700000, 5800000, 5900000, 6000000, 6100000, 6200000, 6300000, 6400000, 6500000, 6600000, 6700000, 6800000, 6900000, 7000000, 7100000, 7200000, 7300000, 7400000, 7500000, 7600000, 7700000, 7800000, 7900000, 8000000, 8100000, 8200000, 8300000, 8400000, 8500000, 8600000, 8700000, 8800000, 8900000, 9000000, 9100000, 9200000, 9300000, 9400000, 9500000, 9600000, 9700000, 9800000, 9900000, 10000000, 11000000, 12000000, 13000000, 14000000, 15000000, 16000000, 17000000, 18000000, 19000000, 20000000, 21000000, 22000000, 23000000, 24000000, 25000000, 26000000, 27000000, 28000000, 29000000, 30000000, 31000000, 32000000, 33000000, 34000000, 35000000, 36000000, 37000000, 38000000, 39000000, 40000000, 41000000, 42000000, 43000000, 44000000, 45000000, 46000000, 47000000, 48000000, 49000000, 50000000, 51000000, 52000000, 53000000, 54000000, 55000000, 56000000, 57000000, 58000000, 59000000, 60000000, 61000000, 62000000, 63000000, 64000000, 65000000, 66000000, 67000000, 68000000, 69000000, 70000000, 71000000, 72000000, 73000000, 74000000, 75000000, 76000000, 77000000, 78000000, 79000000, 80000000, 81000000, 82000000, 83000000, 84000000, 85000000, 86000000, 87000000, 88000000, 89000000, 90000000, 91000000, 92000000, 93000000, 94000000, 95000000, 96000000, 97000000, 98000000, 99000000, 100000000, 110000000, 120000000, 130000000, 140000000, 150000000, 160000000, 170000000, 180000000, 190000000, 200000000, 210000000, 220000000, 230000000, 240000000, 250000000, 260000000, 270000000, 280000000, 290000000, 300000000, 310000000, 320000000, 330000000, 340000000, 350000000, 360000000, 370000000, 380000000, 390000000, 400000000, 410000000, 420000000, 430000000, 440000000, 450000000, 460000000, 470000000, 480000000, 490000000, 500000000, 510000000, 520000000, 530000000, 540000000, 550000000, 560000000, 570000000, 580000000, 590000000, 600000000, 610000000, 620000000, 630000000, 640000000, 650000000, 660000000, 670000000, 680000000, 690000000, 700000000, 710000000, 720000000, 730000000, 740000000, 750000000, 760000000, 770000000, 780000000, 790000000, 800000000, 810000000, 820000000, 830000000, 840000000, 850000000, 860000000, 870000000, 880000000, 890000000, 900000000, 910000000, 920000000, 930000000, 940000000, 950000000, 960000000, 970000000, 980000000, 990000000, 1000000000, 1100000000, 1200000000, 1300000000, 1400000000, 1500000000, 1600000000, 1700000000, 1800000000, 1900000000, 2000000000, 2100000000, 2200000000, 2300000000, 2400000000, 2500000000, 2600000000, 2700000000, 2800000000, 2900000000, 3000000000, 3100000000, 3200000000, 3300000000, 3400000000, 3500000000, 3600000000, 3700000000, 3800000000, 3900000000, 4000000000, 4100000000, 4200000000, 4300000000, 4400000000, 4500000000, 4600000000, 4700000000, 4800000000, 4900000000, 5000000000, 5100000000, 5200000000, 5300000000, 5400000000, 5500000000, 5600000000, 5700000000, 5800000000, 5900000000, 6000000000, 6100000000, 6200000000, 6300000000, 6400000000, 6500000000, 6600000000, 6700000000, 6800000000, 6900000000, 7000000000, 7100000000, 7200000000, 7300000000, 7400000000, 7500000000, 7600000000, 7700000000, 7800000000, 7900000000, 8000000000, 8100000000, 8200000000, 8300000000, 8400000000, 8500000000, 8600000000, 8700000000, 8800000000, 8900000000, 9000000000, 9100000000, 9200000000, 9300000000, 9400000000, 9500000000, 9600000000, 9700000000, 9800000000, 9900000000, 10000000000, 11000000000, 12000000000, 13000000000, 14000000000, 15000000000, 16000000000, 17000000000, 18000000000, 19000000000, 20000000000, 21000000000, 22000000000, 23000000000, 24000000000, 25000000000, 26000000000, 27000000000, 28000000000, 29000000000, 30000000000, 31000000000, 32000000000, 33000000000, 34000000000, 35000000000, 36000000000, 37000000000, 38000000000, 39000000000, 40000000000, 41000000000, 42000000000, 43000000000, 44000000000, 45000000000, 46000000000, 47000000000, 48000000000, 49000000000, 50000000000, 51000000000, 52000000000, 53000000000, 54000000000, 55000000000, 56000000000, 57000000000, 58000000000, 59000000000, 60000000000, 61000000000, 62000000000, 63000000000, 64000000000, 65000000000, 66000000000, 67000000000, 68000000000, 69000000000, 70000000000, 71000000000, 72000000000, 73000000000, 74000000000, 75000000000, 76000000000, 77000000000, 78000000000, 79000000000, 80000000000, 81000000000, 82000000000, 83000000000, 84000000000, 85000000000, 86000000000, 87000000000, 88000000000, 89000000000, 90000000000, 91000000000, 92000000000, 93000000000, 94000000000, 95000000000, 96000000000, 97000000000, 98000000000, 99000000000, 100000000000, 110000000000, 120000000000, 130000000000, 140000000000, 150000000000, 160000000000, 170000000000, 180000000000, 190000000000, 200000000000, 210000000000, 220000000000, 230000000000, 240000000000, 250000000000, 260000000000, 270000000000, 280000000000, 290000000000, 300000000000, 310000000000, 320000000000, 330000000000, 340000000000, 350000000000, 360000000000, 370000000000, 380000000000, 390000000000, 400000000000, 410000000000, 420000000000, 430000000000, 440000000000, 450000000000, 460000000000, 470000000000, 480000000000, 490000000000, 500000000000, 510000000000, 520000000000, 530000000000, 540000000000, 550000000000, 560000000000, 570000000000, 580000000000, 590000000000, 600000000000, 610000000000, 620000000000, 630000000000, 640000000000, 650000000000, 660000000000, 670000000000, 680000000000, 690000000000, 700000000000, 710000000000, 720000000000, 730000000000, 740000000000, 750000000000, 760000000000, 770000000000, 780000000000, 790000000000, 800000000000, 810000000000, 820000000000, 830000000000, 840000000000, 850000000000, 860000000000, 870000000000, 880000000000, 890000000000, 900000000000, 910000000000, 920000000000, 930000000000, 940000000000, 950000000000, 960000000000, 970000000000, 980000000000, 990000000000, 1000000000000, 1100000000000, 1200000000000, 1300000000000, 1400000000000, 1500000000000, 1600000000000, 1700000000000, 1800000000000, 1900000000000, 2000000000000, 2100000000000, 2200000000000, 2300000000000, 2400000000000, 2500000000000, 2600000000000, 2700000000000, 2800000000000, 2900000000000, 3000000000000, 3100000000000, 3200000000000, 3300000000000, 3400000000000, 3500000000000, 3600000000000, 3700000000000, 3800000000000, 3900000000000, 4000000000000, 4100000000000, 4200000000000, 4300000000000, 4400000000000, 4500000000000, 4600000000000, 4700000000000, 4800000000000, 4900000000000, 5000000000000, 5100000000000, 5200000000000, 5300000000000, 5400000000000, 5500000000000, 5600000000000, 5700000000000, 5800000000000, 5900000000000, 6000000000000, 6100000000000, 6200000000000, 6300000000000, 6400000000000, 6500000000000, 6600000000000, 6700000000000, 6800000000000, 6900000000000, 7000000000000, 7100000000000, 7200000000000, 7300000000000, 7400000000000, 7500000000000, 7600000000000, 7700000000000, 7800000000000, 7900000000000, 8000000000000, 8100000000000, 8200000000000, 8300000000000, 8400000000000, 8500000000000, 8600000000000, 8700000000000, 8800000000000, 8900000000000, 9000000000000, 9100000000000, 9200000000000, 9300000000000, 9400000000000, 9500000000000, 9600000000000, 9700000000000, 9800000000000, 9900000000000, 10000000000000, 11000000000000, 12000000000000, 13000000000000, 14000000000000, 15000000000000, 16000000000000, 17000000000000, 18000000000000, 19000000000000, 20000000000000, 21000000000000, 22000000000000, 23000000000000, 24000000000000, 25000000000000, 26000000000000, 27000000000000, 28000000000000, 29000000000000, 30000000000000, 31000000000000, 32000000000000, 33000000000000, 34000000000000, 35000000000000, 36000000000000, 37000000000000, 38000000000000, 39000000000000, 40000000000000, 41000000000000, 42000000000000, 43000000000000, 44000000000000, 45000000000000, 46000000000000, 47000000000000, 48000000000000, 49000000000000, 50000000000000, 51000000000000, 52000000000000, 53000000000000, 54000000000000, 55000000000000, 56000000000000, 57000000000000, 58000000000000, 59000000000000, 60000000000000, 61000000000000, 62000000000000, 63000000000000, 64000000000000, 65000000000000, 66000000000000, 67000000000000, 68000000000000, 69000000000000, 70000000000000, 71000000000000, 72000000000000, 73000000000000, 74000000000000, 75000000000000, 76000000000000, 77000000000000, 78000000000000, 79000000000000, 80000000000000, 81000000000000, 82000000000000, 83000000000000, 84000000000000, 85000000000000, 86000000000000, 87000000000000, 88000000000000, 89000000000000, 90000000000000, 91000000000000, 9