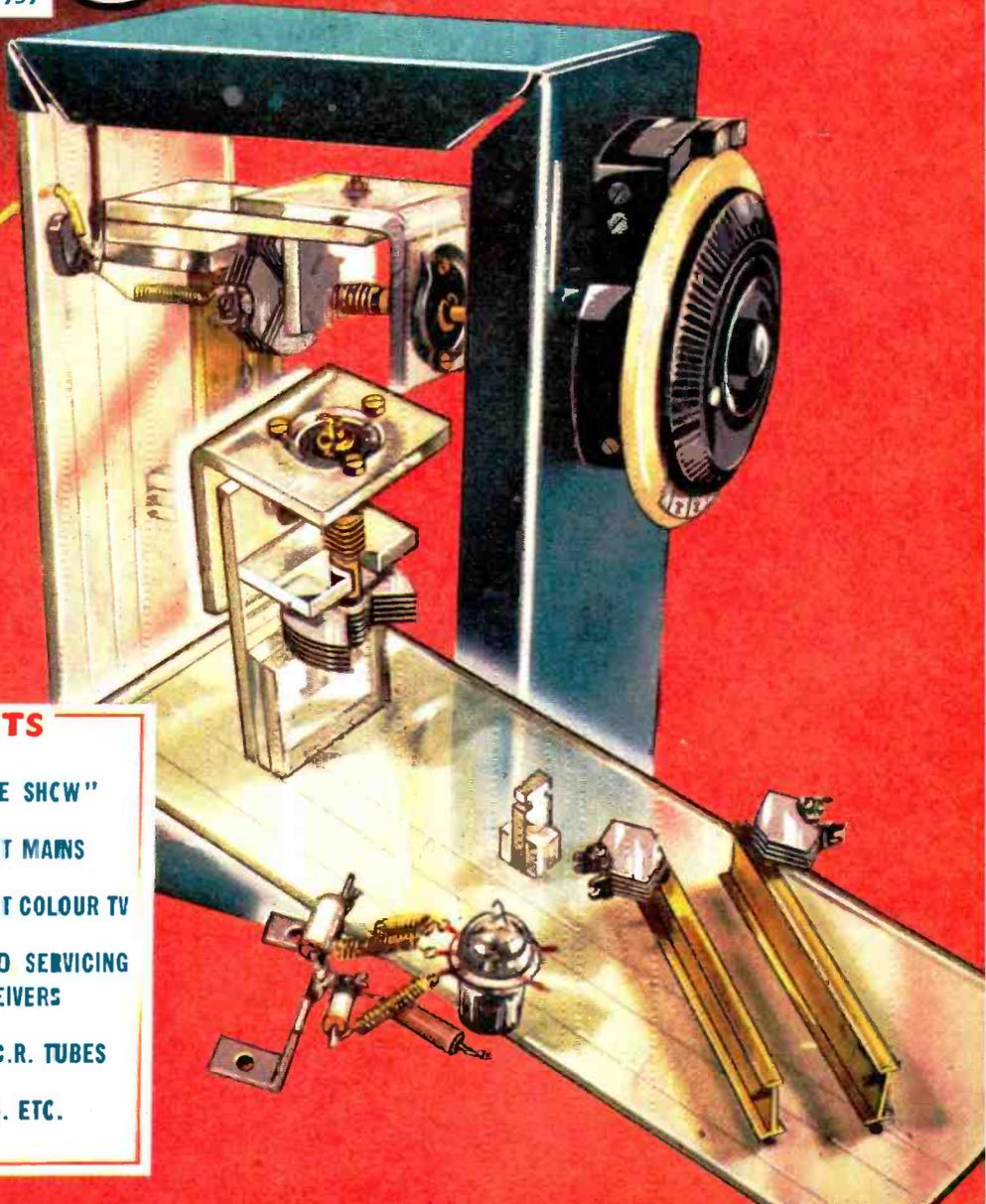


A BAND V SIGNAL GENERATOR

Practical Television 13

OCTOBER 1959

AND TELEVISION TIMES



CONTENTS

TV AT "THE SHCW"

TV WITHOUT MAINS

CLOSED-CIRCUIT COLOUR TV

ANALYSING AND SERVICING
TV RECEIVERS

REPLACING C.R. TUBES

ETC. ETC. ETC.

D.C. OSCILLOSCOPE

A.C. MAINS 200-250 VOLTS



SIMPLIFIED SERVICING PROBLEMS WHEN USING THE 'TESTGEAR' SCOPE
3in. D.C. OSCILLOSCOPE

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable differential provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transmitter operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking T.V. Line O.P. Transformers, etc.; Provision for external X.F.P. and CRT Brightness Modulation. Size 10in. high, 6in. wide, 9in. deep. Wgt. 11 lbs. £15.15.0. plus P. & P. 6/6, or 30/- deposit, plus P. & P. 6/6 and 12 months' payments of 2/6.

FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE.

WOLSEY 3-ELEMENT FOLDED DIPOLE
I.T.V. Aerial less mounting bracket, complete with 12 yds. of coaxial cable; 15/-; 4 element, 17/6; 5 element, 25/-; P. & P. on above 3/6.

E.H.T. Smoothing Condenser 500 p.f., 18 KV. D.C. 1/6. working.

LINE E.H.T. TRANSFORMER

By famous manufacturer, 14 Kv. Complete with built-in line and width controls. Winding for EY51 Rectifier. 19/6 Plus P. & P. 2/6.

13 CHANNEL TUNER

34 to 39 Mc/s complete with PCF80 and PCC84. These have been removed from chassis.

23/- complete with knobs. P. & P. 3/6 extra.

16-19 Mc/s complete with knobs less valves. 13/- Plus P. & P. 2/6.



SIGNAL GENERATOR



£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6in. x 5in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier, A.C. Mains 200/250. Internal Modulation of 40% c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 100 milli-volts.


C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

F.M. TUNER UNIT

Permeability tuned, by famous German manufacturer. Coverage 88-100 Kc/s. Complete with ECC85, size 4in. x 2in. x 2in.

25/- P. & P. 1/6.

SIGNAL & PATTERN GENERATOR

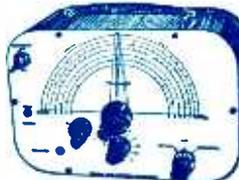

25/- deposit plus P. & P. 5/- and 6 monthly payments of 21/6. Cash £6.19.6 plus P. & P. 5/-. Coverage 7.6 Mc/s-210 Mc/s in five bands, all on fundamentals, slow-motion tuning, audio output, 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1% A.C. mains 200-250 v.

RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

ADCOLA

PRODUCTS LIMITED
(Regd. Trade Mark)

SOLDERING EQUIPMENT

ILLUSTRATED

3" Detachable bit type (List No. 64)

Protective Shield (List No. 68)

Catalogues sent FREE

Telephones :
MACaulay 4272 & 3101



British and Foreign Pat.

Reg. Designs, etc.

Head Office, Sales :

ADCOLA PRODUCTS LTD.

Gauden Road, Clapham High St., London, S.W.4

TELEVISION TUBES REBUILT

BUY DIRECT FROM THE FACTORY!

12 MONTHS' GUARANTEE

12" - - - - £5. 0.0

14" - - - - £5.10.0

17" - - - - £6.10.0

Carriage and insurance 12/6 extra.

MARSHALLS for TELEVISION

131 St. Ann's Road, Tottenham, London, N.15.

Telephone: STAmford Hill 3267

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9693

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. C.O.D. ORDERS BY PHONE OR WIRE ACCEPTED UP TO 3.30 P.M. FOR IMMEDIATE DESPATCH.

ANY ORDER		INSURED		AGAINST		DAMAGE IN		TRANSIT		FOR ONLY 6d. EXTRA.		
0B2	17/6 6CB	12/6 6X4	6/6 20D1	15/3 AC/PEN	DL510	10/6 EL38	26/6 LN152	10/6 R12	9/6 UF41	9/-		
0Z4	6/- 6C9	12/6 6X5GT	6/- 20F2	26/6 5-pin 23/3	DM70	7/6 EL41	9/- MH4(C)	7/- R18	14/- UF42	12/6		
1A3	3/- 6C10	10/6 6/30L2	10/- 20L1	26/6 7-pin 15/-	EAS0	2/- EL42	13/11 MHL4	7/6 R19	19/11 UF80	10/6		
1A5	6/- 6CD6G	7A7	12/6 20P1	26/6 AC/PEN	EABC80	9/- EL81	12/6 MHL6	12/6 SD6	12/- UF85	10/6		
1A7GT		29/10 7B6	19/3 20P3	23/3	23/3 EAC91	7/6 EL84	8/6 ML4	12/6 SP4(7)	15/- UF86	17/11		
	21/11 6CH6	12/6 7B7	8/6 20P5	23/3 AC/PEN/	IEAF42	9/6 EL85	13/11 MU14	9/- SP41	3/6 UF89	9/-		
1C5	12/6 6D3	19/11 7C5	8/- 25A6G	11/- DD	26/6 EB34	2/6 EL91	5/- MX40	15/- SP42	12/6 UL41	9/-		
1D6	10/6 6D6	6/6 7C6	8/- 25L6GT	10/- AC/PEN	EB41	8/6 EL95	10/6 N37	19/11 SP61	3/6 UL44	26/6		
1H5GT	11/- 6E5	12/6 7D8	23/3 25Y5	10/6	26/6 EB91	5/6 EM34	10/- N78	19/11 SU25	26/6 UL46	14/6		
1L4	6/- 6F1	26/6 7H7	8/- 25Y5G	10/- AC/PEN	EBC3	23/3 EM71	23/3 N108	19/11 SU61	9/6 UL84	8/6		
1LD5	5/- 6F6G	7/- 7R7	12/6 25Z4G	9/6	23/3 EBC33	7/- EM80	9/6 N308	20/7 T41	23/3 UM4	17/3		
1LN5	5/- 6F6GTM	8/- 757	10/6 25Z5	10/6 AC/PEN 7/6	EBC41	8/6 EM81	9/6 N339	19/11 TDD4	24/7 URIC	9/-		
1NSGT	11/- 6F8	12/6 7V7	8/6 25Z6G	10/- AC/P4	8/- EBC81	8/- EM84	10/6 OA70	4/- TH4B	15/- UU6	19/11		
1R5	7/6 6F11	17/3 7Y4	8/- 25Z6GT	8/6 AC/TP	33/2 EBF80	10/- EN31	37/- OA71/81	4/- TH41	26/6 U07	16/7		
1S4	9/- 6F12	5/6 7Z4	18/7	16/7 AC/VP1	EBF83	13/11 EY51	9/6 OC72	17/- TH233	33/2 U08	26/6		
1S5	7/6 6F13	11/6 8D2	3/6 27SU	19/11 7 pin 15/-	EBF89	9/6 EY83	16/7 P61	3/6 TH2321	20/- U09	7/6		
1T4	6/- 6F14	26/6 8D3	5/6 28D7	7/- AC/VP2	23/3 EBL21	23/3 EY84	14/- PABC80	TP22	15/- UY1N	18/7		
1U5	10/- 6F15	15/3 9D2	4/- 30C1	8/- ATP4	5/- EBL31	23/3 EY86	10/-	13/11 TP25	19/6 UY21	16/6		
2A7	10/6 6F16	9/6 9BWC	15/3 30F5	7/- AZ1	18/7 EC52	5/6 EZ35	6/- PCC84	8/- TP2620	33/2 UY41	7/6		
2P	26/6 6F17	12/6 10C1	12/6 30FL1	10/- AZ31	10/- EC54	6/- EZ40	7/6 PCC85	9/6 TP86F	13/3 UY85	7/-		
2X2	4/6 6F32	10/6 10C2	26/6 30L1	8/- AZ41	13/11 EC70	12/6 EZ41	7/6 PCC88	23/11 U12,14	12/- VMP4	15/-		
3A4	7/- 6F33	7/6 10D2	12/- 30P12	8/- B36	24/7 EC92	13/3 EZ80	7/- PCC89	14/11 U16	12/- VP2(7)	12/6		
3A5	10/6 6G6	6/6 10F1	17/6 30P16	8/- BL63	7/6 ECC32	10/6 EZ81	7/- PCC80	8/- U18/20	9/- VP4(7)	15/-		
3B7	12/6 6H6GTG	3/- 10F9	10/6 30PL1	11/6 C1	12/6 ECC33	8/6 FC2A	24/7 PCF82	11/6 U22	8/- VP2B	14/6		
3D6	5/- 6H6GTM	3/6 10LD3	8/6 31	7/6 C1C	12/6 ECC34	24/7 FC4	15/- PCL82	12/6 U24	29/6 VP4B	23/3		
3Q4	7/6 6J5G	5/6 10LD11	33A/158M	CBL1	26/6 ECC35	8/6 FC13	26/6 PCL83	11/6 U25	12/- VP13C	7/-		
3Q5GT	9/6 6J5GTG	5/6	15/11	30/- CBL31	23/3 ECC40	23/3 FC13C	26/6 PCL84	12/6 U26	10/- VP23	6/6		
3S4	7/6 6J5GTM	6/- 10P13	15/6 35/51	12/6 CHH35	23/3 ECC81	8/-	FW4/500	PEN4DD	U31	9/6 VP41	6/6	
3R4	7/6 6J6	5/6 10P14	19/3 35A5	21/3 CK506	6/6 ECC82	7/6			26/6 U33	26/6 VR75/30		
3V4G	17/6 6J7G	6/- 11D3	24/7 35L6GT	9/6 CL33	19/3 ECC83	8/-			PEN25 19/11 U35	26/6 VR105/30	17/6	
3Y4G	10/6 6J8G	12/6 12A6	26/6 35W4	7/6 CV63	10/6 ECC84	9/6	FW4/800		PEN36C	U37	26/6	
5V4G	11/- 6K6GT	8/- 12AC6	15/3 35Z3	10/6 CV85	12/6 ECC85	8/6 G230	10/6	10/6 U43	9/6	VR150/30	9/-	
5X4G	12/6 6K7G	5/- 12AD6	17/3 35Z4	6/6 CV428	30/- ECC91	5/6 G232	12/-	PEN4DD	U45	9/6		
5Y3G	8/- 6K7GT	8/- 12AE6	13/11 35Z5GT	9/- CY1	18/7 ECF80	11/6 G234	14/-		U50	8/6		
5Y3GT	7/6 6K8G	8/- 12AH7	8/- 41MTL	8/- CY31	16/7 ECF82	10/6 H30	5/-	PEN44 26/6 U52	8/6 VT61A	5/-		
5Y4	12/6 6K8GTG	12A8H	12/6 42	23/3 D1	3/- ECH3	26/6 H63	12/6	PEN45 19/6 U76	6/5 VT501	5/-		
5Z3	12/6	12/6 12AT6	7/6 43	12/6 D15	10/6 ECH21	23/3 HABC80		PEN45DD	U78	6/6 W61M	26/6	
5Z4G	10/6 6K25	19/11 12AT7	8/- 50C5	12/6 D63	5/- ECH35	9/6	13/6	26/6 U107	16/7 W76	6/6		
5Z4GT	12/6 6L1	23/3 12AU6	23/3 50CD6G	D77	5/6 ECH42	10/6 HL23	10/6	PEN46 7/6 U91	16/7 W81M	6/-		
6A7	26/6 6L6G	6/6 12AU7	7/6	29/10 DAC32	11/- ECH81	9/-	HL23DD	PEN383 23/3 U251	14/- W107	15/3		
6A8	10/- 6L6M	12/6 12AX7	8/- 50L6GT	9/6 DAF91	7/6 ECH83	13/11		PEN453DD	U281	19/11 W729	18/7	
6AB7	8/- 6L7GT	12/6 12BA6	8/- 53KU. 19/11	DAF96	9/- ECL80	10/6	HL41	12/6	33/2 U282	27/2 X24M	24/7	
6AB8	10/6 6L18	13/3 12BE6	10/- 72	4/6 DC90	13/11 ECL82	10/6	HL41DD	PEN/DD	U301	23/3 X31	26/6	
6AC7	6/6 6L19	23/3 12BH7	21/3 75	24/7 DD41	13/11 ECL83	19/3	19/3 4020	33/2 U329	14/- X41	15/-		
6AG5	6/6 6L3D	8/6 12E1	30/- 77	8/- DDT4	24/7 EF9	23/3	HL42DD	PL33	19/3 U339	16/7 X42	15/-	
6AK5	8/- 6LD20	15/11 12J5GT	4/6 78	8/6 DF33	11/- EF22	14/-		19/3 PL36	14/- U403	16/7 X61(C)	12/6	
6AL5	5/6 6N7	8/- 12J7GT	10/6 80	9/- DF66	15/- EF36	6/-	HN309 24/7	PL38	26/6 U404	8/6 X61M	26/6	
6AM6	5/6 6P1	19/3 12K5	17/11 83	15/- DF70	15/- EF37A	8/-	HVR2	20/- PL81	12/6 U801	19/10 X63	10/6	
6AQ5	8/6 6P25	12/6 12K7GT	6/6 83V	12/6 DF91	6/- EF39	5/6	HVR2A	6/- PL82	8/- U4020	7/6 X65	12/6	
6AT6	8/6 6P28	26/6 12K8GT	14/- 85A2	15/- DF96	9/- EF40	15/-	KF35	8/6 PL83	9/- UABCJ	X66	12/6	
6AU6	10/6 6Q7G	8/- 12Q7GT	6/6 150B2	15/- DF97	9/- EF41	9/6	KK32	21/11 PL820	18/7	9/- X76M	14/6	
6AV6	12/7 6Q7GT	11/- 12SA7	8/6 185BT	33/2 DH63	8/- EF42	11/6	KL35	8/6 PM2B	12/6 UAF42	9/6 X78	21/3	
6B7	10/6 6R7G	10/- 12SC7	8/6 185BTA	33/2 DH63(Msc)	EF50(A)	7/-	KLL32	24/7 PM12	6/6 U841	12/- X79	21/3	
6BBG	4/6 6SA7GT	8/6 12SG7	8/6 203THA	17/6 EF50(E)	5/-	KT2	5/-	PM12M	6/6 U8C41	8/6 X81(M)	46/5	
6B8GT	5/- 6SC7	10/6 12SH7	8/6	26/6 DH76	6/6 EF54	5/-	KT33C	10/-	PM24M	21/3 U8C81	8/6 X109	17/3
6BA6	7/6 6S7GT	8/- 12S17	8/6 220TH	24/7 DH77	8/6 EF73	10/6	KT36	29/10 PX4	26/6 U8F80	9/6 XDF(1.5)	6/6	
6BE6	7/6 6S7GT	8/- 12S7K	8/6 30A4	10/6 DH107	13/11 EF80	7/-	KT41	26/6 PX25	16/7 U8187	9/6 XFF34	18/6	
6BG6G	23/3 6S7GT	8/- 12SQ7	12/6 305	10/6 DK32	21/11 EF85	7/-	KT44	15/- PY31	11/6 U8L21	23/3 XH(1.5)	6/6	
6BH6	9/- 6S7GT	8/- 12SR7	8/6 402PenA	DK40	21/3 EF86	12/6	KT61	12/6 PY32	11/6 UCC91	14/7 XSG(1.5)	6/6	
6BH6	7/6 6S7GT	8/- 12Y4	10/6	23/3 DK91	7/6 EF89	9/-	KT63	7/6 PY80	9/- UCC85	9/-		
6BQ7A	15/- 6SN7GT	6/6 14H7	23/3 807	7/6 DK92	10/6 EF91	5/6	KT66	15/- PY81	9/- UCC85	9/-		
6BR7	23/3 6SQ7GT	9/- 1457	27/10 956	3/- DK96	9/- EF92	5/6	KT88	22/6 PY82	7/6 UCFD	16/7 Y63	7/6	
6BW6	10/6 6S57GT	8/- 15D1	26/6 1821	16/7 DL33	9/6 EF97	13/3	KTW61	8/- PY83	9/6 UCFD	23/3 Z63	10/6	
6BW7	7/6 6U4GT	12/6 18	23/3 5763	12/6 DL66	15/- EF98	13/3	KTW62	8/- PZ30	19/11 UCH42	9/6 Z66	20/-	
6BX6	7/6 6U5GT	7/6 19AQ5	10/6 7193	5/- DL68	15/- EK32	8/6	KTW63	8/- QP21	7/- UCHP1	9/6 Z77	5/6	
6C4	7/6 6U7G	8/6 19AG6G	7475	7/6 DL92	7/6 EL32	5/6	KTZ41	8/- QP25	15/- UCL82	11/6 Z719	7/-	
6C5G	6/6 6V6G	7/-	23/3 9006	5/6 DL94	7/6 EL33	12/6	KTZ63	10/6 QS150/15	10/6 UCL83	19/3 Z729	12/6	
6C6	6/6 6V6GTG	8/- 19H1	10/- 9006	6/- DL96	9/- EL34	15/-	L63	6/-				

NEW METAL RECTIFIERS—FULLY GUARANTEED

DRM-18	15/4	RM-2	9/-	WX3	3/6	14A100	27/-	14RA 1-2-8-2	19/-	16RE 2-1-8-1	8/6
DRM-28	16/2	RM-3	9/6	WX4	3/6	14A124	28/-	14RA 1-2-8-3	23/6	18RA 1-1-8-1	4/6
DRM-38	23/3	RM-4	18/-	WX6	3/6	14A163	38/-	14RA 2-1-16-1	21/-	18RA 1-1-16-1	6/6
LW7	22/6	RM-5	24/-	14A88	18/-	14B130	35/-	16RC 1-1-16-1	8/6	18RA 1-2-8-1	11/-
RM-0	7/11	W4	3/6	14A97	25/-	14B261	11/6	16RD 2-2-8-1	12/-	18RD 2-2-8-1	15/-
RM-1	7/-	W6	3/6								

Technical leaflet on Metal Rectifiers free on receipt of S.A.E.

VOLUME CONTROLS

All with long spindle and double-pole switch, 4/6 each. 32 x 10K, 25K, 50K, 100K, 64 x 1 meg., 1 meg., 1 meg. 2 meg. 60 x 250 mfd., 275 v. 9/6 100 x 200 mfd., 275 v. 9/6 32 mfd., 450 v. 5/9 100 mfd., 275 v. 2/6 8/3 200 mfd., 275 v. 3/6 16 mfd., 450 v. 2/9 32 x 32 mfd., 350 v. 4/- 1 meg., 1 meg., 1 meg. 2 meg. 60 x 250 mfd., 275 v. 9/6 100 x 200 mfd., 275 v. 9/6 32 mfd., 450 v. 3/9 8 x 16 mfd., 450 v. 3/9

TERMS OF BUSINESS: CASH WITH ORDER OR C.O.D. ONLY. POST PACKING CHARGES 6d. PER ITEM. ORDERS VALUE 25 OR MORE POST FREE. C.O.D. EXTRA. SHOP HOURS 8.00-5.30. SAT. HOURS 1 P.M. ALL VALUES BONDED, TAX PAID, AND SUBJECT TO MAKERS' GUARANTEE. FIRST GRADE GOODS ONLY. NO SECOND HANDS OR REJECTS. CATALOGUE OF OVER 1,000 DIFFERENT VALVES, WITH FULL TERMS OF BUSINESS, PRICE 6d. PLEASE ENQUIRE FOR ANY VALVE NOT LISTED. 3d. STAMP, PLEASE.

ELECTROLYTIC CONDENSERS

100 x 400 mfd., 275 v. 12/6 Wire-ended Jubular 8 x 8 mfd., 450 v. 3/- 2/6 8 mfd., 450 v. 1/9 16 x 16 mfd., 450 v. 4/- 3/6 16 mfd., 450 v. 2/9 32 x 32 mfd., 350 v. 4/-

TECHNICAL TRAINING

*in Radio, Television
& Electronics Engineering*

WITH ICS

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

These are the Courses ICS offer :

Radio and Television Engineering—Radio and TV Servicing—Radio Service and Sales—Electronics—VHF/FM Engineering—

. . . and the Examinations

A.M.BRIT.I.R.E., City and Guilds Telecommunication, Radio Servicing; P.M.G. Radio Amateurs Cert.

plus

**Learn-as-you-Build
Practical Radio Course**

A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester. *Other Learn-as-you-Build radio courses are also available.*

Other ICS Courses include :

MECHANICAL ENGINEERING—MOTOR ENGINEERING—FIRE ENGINEERING—CHEMICAL ENGINEERING—WOODWORKING—SALESMANSHIP AND SALES MANAGEMENT—PHOTOGRAPHY—ARCHITECTURE—ART—AGRICULTURE—HORTICULTURE, etc. etc.

If subject not shown state on coupon.

Post this Coupon TODAY

For FREE book on Careers in Radio & Television, etc., and giving details of other ICS Courses.

International Correspondence Schools
(Dept. 164A), Intertext House, Parkgate Road,
London, S.W.11.

Please send book on (Subject)

Name and Address

Age

Occupation.....IO.59

INTERNATIONAL CORRESPONDENCE SCHOOLS

BRAND NU GUN BRAND NU LIFE T/V TUBES

12 MONTHS' GUARANTEE

£7.10.0 CASH

or 20 WEEKS at 8/6 weekly

E. E. & C. Co., Ltd.

**281, Parliamentary Road
Glasgow, C4**

BEL 4569.

RST MAIL ORDER DEPARTMENT

211 Streatham Road, Mitcham, Surrey.
ALL VALVES LISTED ARE NEW STOCK
• Terms C.W.O. or C.O.D. Postage 3d. per valve.

MILGRAM 6201.			
AZ31 10/6	EF92 5/3	PCF82 12/6	UY38 8/-
B65 8/6	EL42 10/-	VF43 17/6	6REB 7/6
DAF91 8/6	EL84 9/6	W81M 5/9	6K8GT 12/6
DAF96 9/6	EL90 8/6	W142 9/-	(T1 15/6
DF91 5/-	EM80 10/-	W179 7/6	8L6G 7/6
DH719 7/6	EM81 10/6	W727 7/6	8L18 12/6
DK91 9/-	EY81 10/6	X78 21/-	8L19 12/6
EABC90 7/6	EY84 10/6	X79 21/-	6N7G/GT 7/6
RAF42 10/-	EY86 14/-	Z21 12/6	Z77 5/6
EB91 6/-	EY91 9/-	PL36 16/-	Z152 7/6
EB91 6/-	EZ35 7/-	PL61 14/6	Z719 7/6
EB91 6/-	EZ40 9/-	PL82 10/-	1R5 9/6
EBF90 9/6	EZ41 8/6	PL83 11/6	5U4G 7/6
EBF89 9/-	EZ80 8/-	PL83 11/6	5V4G 9/6
EC91 9/6	EZ81 8/-	PY80 8/6	5V4G 9/6
ECC93 8/-	FC2 21/-	PY81 9/-	5X5GT 5/6
ECC81 8/6	FC3 17/6	PY82 8/-	5Y3GT 9/6
ECC83 9/6	FC13 17/6	PY83 8/6	3Z4G 10/-
ECC84 9/6	FCL3C 21/-	R10 21/-	6A3GT 10/-
ECC85 9/6	GZ32 11/6	R19 19/6	6A15 10/-
ECF80 12/6	H30 9/6	TDD1 17/6	6A3M 5/6
ECF82 12/6	HBC90 9/6	TP22 17/6	6A3B 7/6
EH35 9/-	HL22 6/6	U142 8/6	6AQ5 8/6
ECH42 10/-	HL133D 10/-	U147 7/-	6BA6 7/6
ECH41 9/-	KT33C 10/-	U153 8/-	6BE6 7/6
ECL80 12/6	KT86 17/6	UABC90 8/6	6B76 7/6
ECL82 12/6	LZ319 12/6	UAF42 4/-	6B77 8/6
EF37A 9/6	MKT45 10/-	UBC11 9/6	6B86 7/6
EF30 15/-	(or T) 17/6	UBF60 9/6	6B7 7/6
EF41 9/3	ML4 15/-	UBH42 7/6	6D2 6/-
EF42 12/6	MS14 17/6	UCH42 6/6	6F1 15/6
EF50 A) 12/6	MU14 9/-	UCH42 6/6	6F12 5/6
EF80 7/6	MX40 17/6	UCL33 23/6	6F13 17/6
EF85 7/6	N142 9/6	UCL33 23/6	6J5G 4/6
EF86 13/6	N153 11/6	UF41 9/-	6J7GT 9/6
EF89 10/-	PCC34 9/6	U189 9/-	6K7 4/6
ET91 6/6	PCF80 12/6	UL41 9/6	6KTG 4/-
		UL34 9/6	6K7GT 8/-
		UY41 8/-	813 50/-

SEND FOR LISTS.
Quotations given for any types not listed. Obsolete and old types a speciality.

Great Money-Making Opportunity!

NEWNES

Radio and TV Servicing

Complete in 1 Volume

300 MODELS (1958-1959)

In response to the heavy demand more copies of Newnes latest volume have now been printed. It contains the circuits, component and chassis layout diagrams for 300 popular Models—672 pages of invaluable data for TV Servicing . Radio Servicing . Record Reproducers (including Stereo) . Tape Recorders, etc.

TELEVISION SERVICING DATA FOR—

Alba, Argosy, Beethoven, Bush, Cossor, Cyldon, Decca, Defiant, Ekco, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B., McMichael, Marconiphone, Masteradio, Murphy, Pageant, Pam, Peto Scott, Philco, Pilot, Portadyne, Pye, Raymond, Regentone, R.G.D., Sobell, Spencer-West, Stella, Ultra.

**300
MODELS**

**672
PAGES OF
WANTED
DATA**



RADIO RECORD & TAPE SERVICING DATA FOR—

Alba, Berec, Bush, Champion, Collaro, Cossor, Decca, E.A.R., Eddystone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B., McMichael, Marconiphone, Masteradio, Murphy, Pam, Perdio, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Regentone, R.G.D., Roberts' Radio, Sobell, Stella, Vidor, Walter.

RECENT DEVELOPMENTS SECTION

Includes : Picture Tube Repair, Car Radio Interference Suppression, Valve and Picture Tube Data.

HEATER RATINGS, BASE CONNECTIONS, EQUIVALENTS

Full set in 7 Volumes

2,300 MODELS (Pre 1953-1959)

(including the 300 models in the volume on left)

Here you have Newnes Complete Servicing Library—early popular models to 1959—almost every set you will ever be called upon to service. This data is absolutely invaluable. It is worth its weight in gold for years on end.

TELEVISION SERVICING DATA FOR—

Ace, Alba, Ambassador, Argosy, Baird, Banner, Beethoven, Brayhead, Bush, Champion, Cossor, Cyldon, Decca, Defiant, Ekco, E.M.I., English Electric, Ferguson, Ferranti, G.E.C., H.M.V., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Murphy, Pageant, Pam, Peto Scott, Philco, Philips, Pilot Portadyne, Pye, Rainbow, Raymond, Regentone, R.G.D., Sobell, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, White-Ibbotson.

RADIO, RECORD, TAPE AND CAR RADIO SERVICING DATA—

Ace, Alba, Ambassador, Argosy, Armstrong, Banner, Beethoven, Berec, Bush, Champion, Collaro, Cossor, Decca, Defiant, E.A.R., Eddystone, Ekco, Ever Ready, Ferguson, Ferranti, G.E.C., Grundig, H.M.V., Invicta, K-B., McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Pye, Pye Telecommunications, Radio mobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Stella, Strad, Ultra, Vidor, Walter, Webcor.


Also—Large Fold-out Charts on TV Troubles.

**2,300
MODELS**

**1,150
PAGES**

**1,250
CIRCUITS
ETC.**

2 YEARS' Free Postal Advisory Service

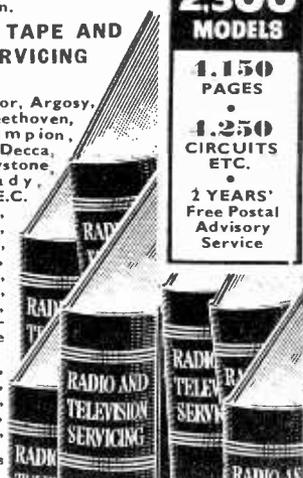

EXAMINE EITHER —

Free for 7 days without obligation!

PLACE TICK AGAINST YOUR CHOICE

Radio and Television Servicing
(Pre-1953 to 1959 Models)
SEVEN VOLUMES

10 - Deposit. 15 monthly payments of 15 - . Paying £11.15s. in all. Cash price in 8 days £11.5s.

Radio and Television Servicing
(1958-1959 Models)
SINGLE VOLUME

12 6 Deposit. 4 monthly payments of 10 - . Paying 52,6 in all. Cash price in 8 days 50 - .

GEORGE NEWNES, LTD., 15-17 Long Acre, London, W.C.99

Send me the book or books I have selected without obligation to purchase. I will either return the book or books in 8 days or send the deposit 8 days after delivery, then the monthly subscriptions as set out on left, until the total subscription price of the book or books I have selected has been paid.

Mr., Mrs., Miss.....

Address


Occupation

Your Signature..... **R30/RV48**
(Or Parent signs if you are under 21)

Tick (✓) where applicable

HouseOWNER	
Householder	
Living with Parents	
Lodging Address	

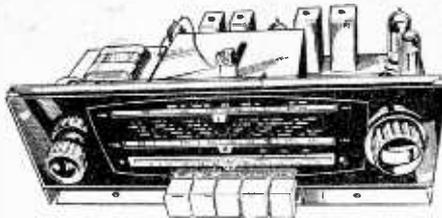BRAND NEW A.M.-F.M. CHASSIS AT £13.6.8 (P. & P. 10/-)




Why buy a F.M. Tuner at the same price?
Tapped input 200-225 v. and 226-250 v. A.C. ONLY.
Chassis size 15" x 6 $\frac{1}{2}$ " x 5 $\frac{1}{2}$ " high. New manufacture.
Dial 14 $\frac{1}{2}$ " x 4" in gold, red and deep brown.
Pick-up. Extension speaker. Ae. E. and Dipole sockets.
Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. With valves. Tone control.
Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s.
Valves E280 rect., ECH81, EF89, EABC80, EL84, ECC85.
Speaker & Cabinet to fit, polished with back, 67/6.
8" x 5" ELLIPTICAL SPEAKER, 20/-.
TERMS:—(Chassis) £4.16.8 dep. + 10/- carr. and 6 Mthly.
£5.9.2 dep. + 10/- carr. and 7 Mthly. Payments of 35/-.

Payments of 30/-, or with Cabinet and Speaker

We are specialists in I.T.A. Converters. Our converters give direct switching I.T.A. to B.B.C., have internal power pack, metal rectifier, co-axial plug, can be fitted in 5-10 mins., and need no alteration to your set. ALL AREAS, ALL SETS, ALL CHANGES. 12 months' guarantee (3 months on valves).

"READY TO USE" I.T.A. CONVERTER

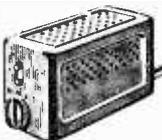
Separate gain controls. Valves PCF80 and PCC84. Switch positions I.T.A. (1) — I.T.A. (2) — B.B.C. Bakelite moulded cabinet 8 $\frac{1}{2}$ " x 4" x 6". £5.5.0 P. & P. 3/-.



For the last 400 I.T.A. Converters of this type (Brand New and Fully Guaranteed) we will accept the "Below Cost" figure of ONLY 60/- (3/- P. & P.) Reduced from £4.7.6. Two valves ECC81—grey hammer finish—Switch positions OFF, I.T.A., B.B.C. Own Power supply. BUY IT NOW.




60/-
(3/- P. & P.)

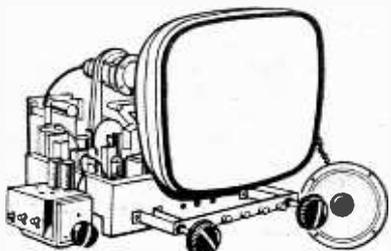

UNUSED 14in. TV CHASSIS WITH 6 $\frac{1}{2}$ in. SPEAKER AND RECTANGULAR TUBE


TV chassis in working order. 16-19 Mc/s Tunes Channels 1-5 B.B.C. and I.T.A. 8-11. When tuned for local reception only switching is necessary for I.T.A. or B.B.C. To convert to I3 Channel set, special price of 60/- for suitable Cydon Turret Tuner to customers purchasing this chassis. Includes 2 sets of coils. Carr. and Ins. 20/- extra. COMPLETE £30 (17in. tube, £36). Cabinet for either size with mask and perspex, 60/-, 6 months' guarantee on tube, 3 months on valves.

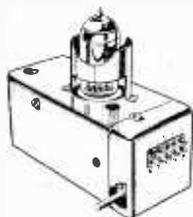BATTERY ELIMINATOR. Converts your Battery Set to Mains. For 4 Low Consumption Valves (DK96 range). 90 v. 15 mA., and 1.4 v. 125 mA., 42/6 (2/6 post). 200-250 v. A.C. Size 5 $\frac{3}{8}$ " x 3 $\frac{1}{8}$ " x 2". Also for 250 mA. 1.4 v. and 90 v. 15 mA. at same price. Please specify which, or state valves.



TELEFUNKEN FM TUNER UNITS FROM DECCA.


With ECC 85 Valve 22/6
LESS VALVE 15/-

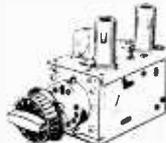

INCREMENTAL TURRET TUNER by famous manufacturer for 35 Mc/s only; with knobs. Valves PCC84 and PCF80. ONLY 77/6, post free, or valves UCC84 and UCF80.

THE BRAYHEAD TURRET TUNER, £7.7.0, post free.

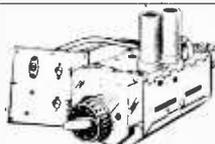Complete with booklet and fitting instructions. State set and model no. when ordering.




NEW SILVERED MICA & CERAMIC CONDENSERS. 50 different values. 10/-, post paid.

RESISTORS. 50 values. 1 w. to 1 w., 5/-, post paid.

I.T.A. AERIALS clipping to existing mast 1-2" dia. 3-element, 27/-; 5-el., 35/-; 9-el., 55/-; Loft mount, 3-el., 20/-; 5-el., 27/6; Combined single B.B.C. and 5-el. I.T.A., 75/- with chimney lashings; Co-axial cable semi-air-spaced, 8d. yd. or 20 yds. 12/6; aerial and cable prices carr. pd.

PERSPEX UNSCRATCHED. (Post 2/- each or 6 post free.) 12 $\frac{1}{2}$ " x 9 $\frac{3}{8}$ " x $\frac{1}{8}$ " clear, 4/6; 14 $\frac{1}{2}$ " x 11" x $\frac{1}{8}$ " clear, 5/-; 15" x 12" x $\frac{1}{8}$ " tinted, 6/-; 17" x 13 $\frac{1}{2}$ " x 3/16" clear, 7/- (Also 15" x 12" slightly scratched 3/-).

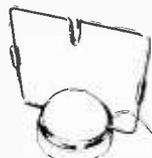I.T.A. TABLE TOP AERIAL
An I.T.A. table top aerial with amazing performance. The Wolsey Hi-Q at 19/6 (2/6 post). Gives good reception up to 20 miles, and has cross-over unit in base with socket for B.B.C. aerial. Same model but very slightly tarnished for ONLY 12/6 (P&P 2/6).




Delivery by return. Terms:—One-third down and balance plus 7/6 in four equal monthly payments. Postage with down payment. (C.O.D. 2/- extra).

These terms are applicable to all items except A.M.-F.M. chassis. All goods are new unless otherwise stated. SEND 6d. FOR NEW CATALOGUE OF 16 PAGES

GLADSTONE RADIO, 58A, HIGH STREET, CAMBERLEY, SURREY. Tel. 2722



Practical Television & TELEVISION TIMES

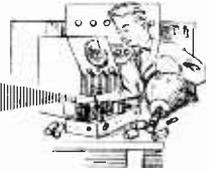

Vol. 10 No. 109

EVERY MONTH

OCTOBER, 1959

TELEVISIONS

Editorial and Advertisement Offices :
PRACTICAL TELEVISION

George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1959.

Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

-including postage for one year

Inland - - 19s. per annum
Abroad - - 17s. 6d. per annum
Canada - - 16s. per annum

CONTENTS :

	Page
Editorial	5
A Closed-Circuit Colour TV System	6
TV at the Radio Show	9
Replacing C.R. Tubes	12
Servicing TV Receivers	13
Telenews	16
Analysing and Servicing TV Receivers	18
From Metal to Glass	23
TV Without Mains	24
A Band V Signal Generator	26
Correspondence	30
TV in the Mountains	33
Amateur Television To-day	37
Underneath the Dipole	41
Your Problems Solved	45

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles, published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

TV RECEIVER DESIGN

AS many readers will have seen for themselves, at this year's National Radio and Television Exhibition, the emphasis in the field of TV receiver design was laid upon the 110 deg. C.R. tube with its associated shorter cabinet. However, it was noticeable that very few manufacturers had made the greatest possible use of this development. True, many of the cabinets were shorter, but in many instances, the cardboard back of the receiver had been extended so that the total depth of the cabinet was very little less than formerly.

Full use of the new tube was made in a receiver which could be suspended in the corner of a room giving a very striking effect. As audio enthusiasts will know, the corner position is held to be the best for a loudspeaker and also means that the sound output is greater. Thus, good sound reproduction is achieved. However, television sound transmissions are of a high quality and often deserve to be heard through a good amplifier and loudspeaker system, and now that so many sets incorporate the V.H.F./F.M. waveband, surely an output for a high quality amplifier should be a standard feature.

THE "P.T." AND "P.W." FILM SHOW

WE are pleased to announce that another film show, sponsored by this journal and our companion journal PRACTICAL WIRELESS, is to be held at Caxton Hall, Westminster, on Friday, January 22nd, 1960, at 7.30 p.m. when the Editor will take the chair. Admission will be by ticket only. The event, which has proved so popular in previous years, is being arranged in conjunction with Mullard Limited.

The films are entitled "Photo Emission", "From Us to View" and "Mirror in the Sky". The latter film deals with events leading up to the experiments by Sir Edward Appleton to confirm the existence of the Heaviside layer, and continues with the discovery of the Appleton layer and the development of the pulse techniques which became the basis of radar. The film concludes with one of the latest scientific achievements—the radio telescope.

Applications for tickets should be made now. Please mark your envelopes "Caxton Hall" in the top left-hand corner. All applications will be dealt with in strict rotation.

THE printing dispute which has prevented normal publication of this journal since the issue dated July, 1959, has been settled and we shall now be able to publish normally.

We greatly regret the inconvenience which this dispute has caused to readers, but we are certain they will appreciate that this break in publication has been due to circumstances beyond our control.

Our next issue, dated November, will be published on October 22nd

A Closed-Circuit Colour TV System

A SEQUENTIAL SYSTEM WITHOUT MOVING PARTS
By R. W. Wells (Continued from p. 606, July issue.)

IN the experiments described in the previous article, coloured light was produced from polarised white light, using Cellophane filters. Change in colour was brought about by manually rotating the plane of polarisation of the light through a few degrees. The Faraday cell described below performs the same function without any moving parts.


The Faraday Cell

Faraday discovered in 1845 that the plane of polarisation of a beam of light was rotated on being passed through lead glass in the presence of a magnetic field. The Faraday cell consists, therefore, of an electro-magnet with a glass core. Figs. 5 and 6 give details of the coil former, which, it will be seen, consists of two winding sections. Each section should be filled up with 30 s.w.g. enamelled copper wire and should have an individual inductance of about 10H after the magnetic shroud has been added. The coils should be connected in parallel, to give a combined inductance of about 5 or 6H.

The core ought to be extra dense flint glass

(Chance 030181 or 927210) and the ends should be flat and polished.

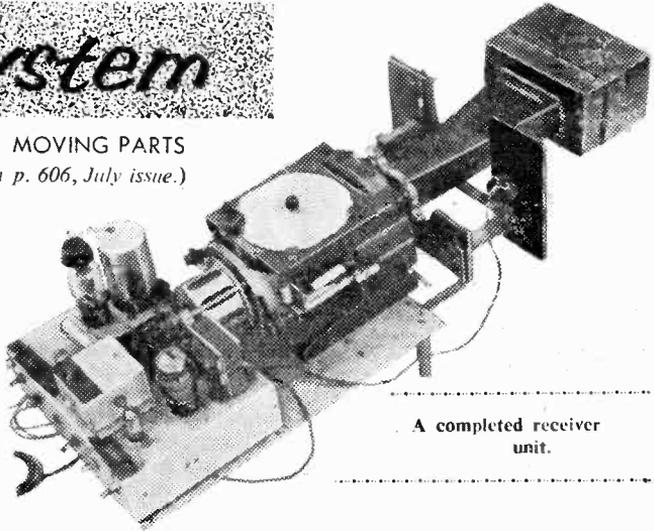The polaroids and Cellophane layers have to be fitted with considerable ingenuity in order to obtain the correct orientation for each layer. To cut down loss of light, the layers may be interspersed with oil and compressed against the glass. It is suggested that the experimenter should try to aim at an orientation angle of about 6 deg., as this value has been found to set a



A completed receiver unit.


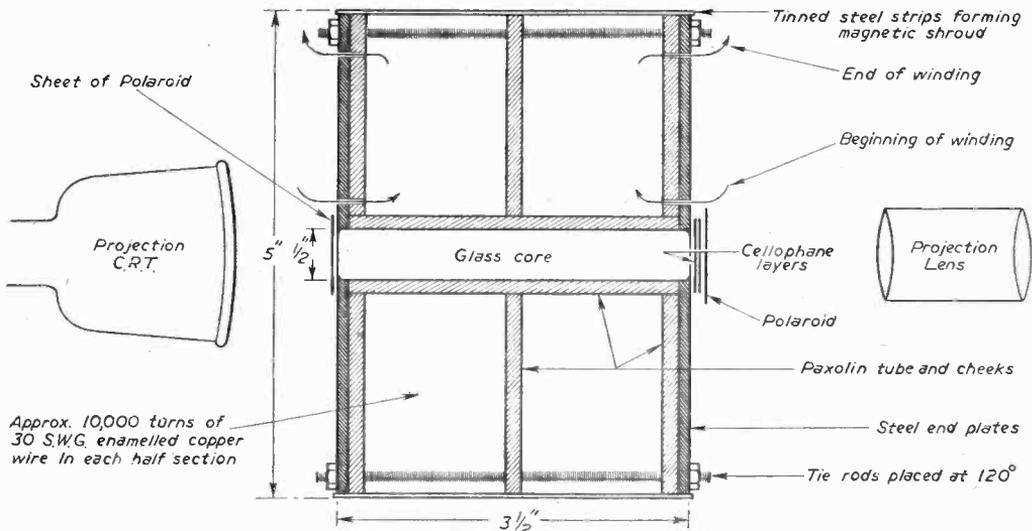


Fig. 5.—The Faraday cell as a colour switching device.

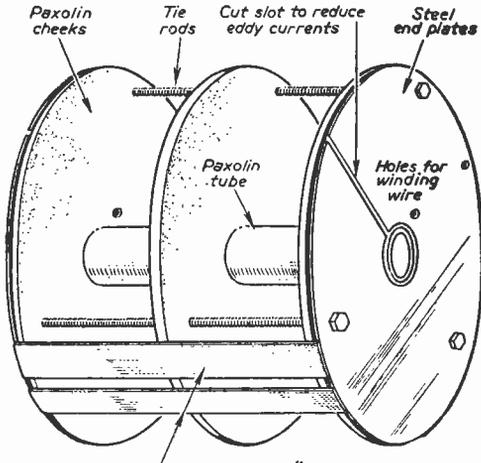

Tinned steel strips 1" wide with $\frac{1}{8}$ " gap between should make good contact with end plates. Bind on with insulating tape

Fig. 6.—Coil former and shroud for Faraday cell.

compromise between loss of light and power to be supplied to the Faraday cell.

Colour Switching at the Receiver

The black and white image measuring about $1\frac{1}{2}$ in. \times 1 in. on the screen of the MW 6/2 tube.

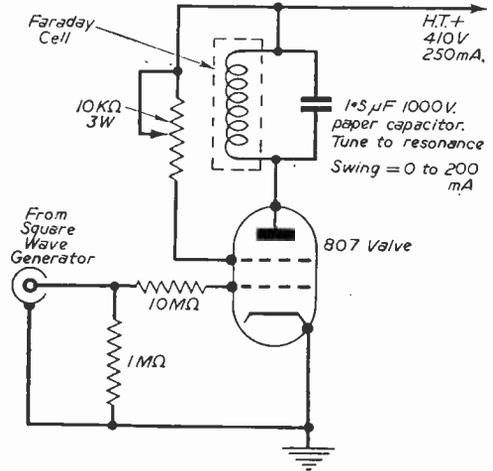


Fig. 7.—Circuit of the Faraday cell driver unit.

after passing through the Faraday cell and filter combination and the lens as shown in Fig. 5, may be projected on to a ground glass or specially prepared Perspex sheet fitted with a hood. The colour frame switching signals are taken from one output of the 25c/s double square wave generator, a circuit diagram of which is shown in Fig. 8. This output is then amplified

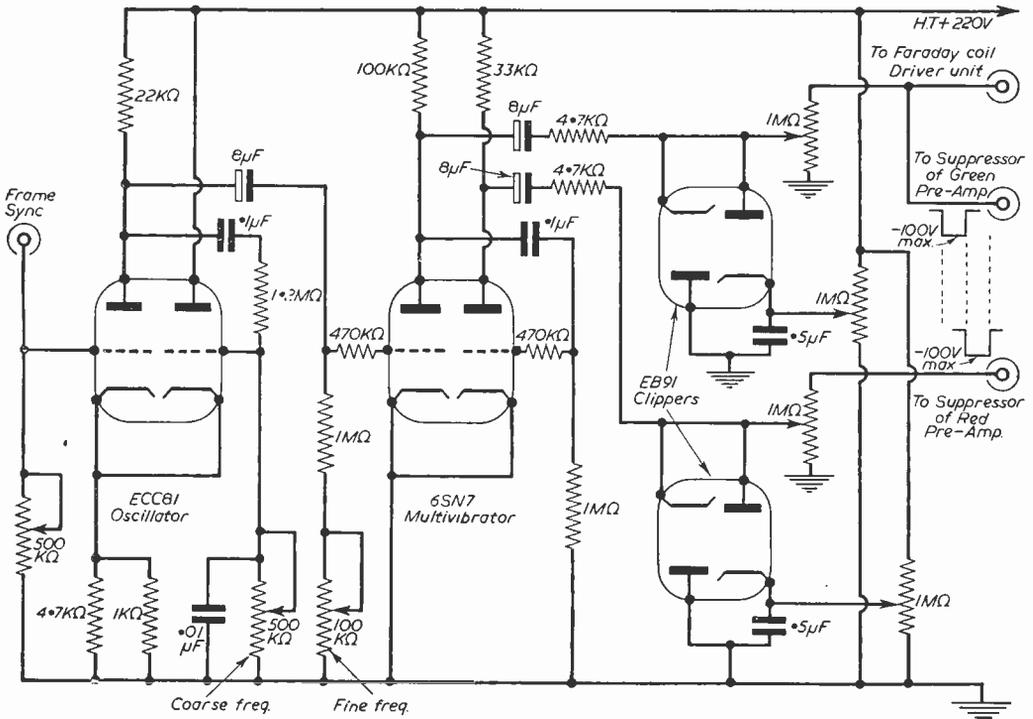


Fig. 8.—Circuit of the 25c/s double square-wave generator.


by the Faraday cell driver unit shown in Fig. 7.

Colour Switching at the Transmitter

For colour switching the transmitter in synchronisation with the receiver, either of the following methods should prove suitable.

(1) The colour transparency is scanned by the projection tube raster (Fig. 1) and the transmitted light allowed to fall in even distribution on the photo-cells, one being covered by a fixed red filter and the other by a green filter. Associated with each photo-cell are the preamplifiers, one of which is shown in Fig. 2. These are capable of being switched alternately by feeding the generator outputs (Fig. 8) to the suppressors of the second amplifier valve.

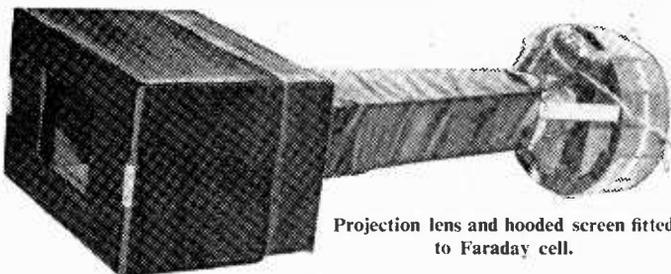(2) The Faraday cell arrangement shown in Fig. 5 may also be used at the transmitter to



Projection lens and hooded screen fitted to Faraday cell.

operate a single photo-cell having a reasonably flat spectral response over the required region.

Adjustments for Correct Colour Mixing

Each photo-cell preamplifier is fitted with a gain control. This has to be adjusted to give white in the case of a magenta/green system and yellowish white in the case of a red/green system. Wrong settings will give incorrect additive colours and will also lead to bad apportionment of brightness between each colour frame.

Forthcoming Conventions

THE IMPACT OF NUCLEAR DEVELOPMENT ON ELECTRICITY SUPPLY AND INSTRUMENT TECHNIQUES

THE Measurement and Control Section and the Supply Section of The Institution of Electrical Engineers announce that with the support of the council they are organising jointly a convention on the Impact of Nuclear Development on Electricity Supply and on Instrument Techniques, to be held in London in September, 1961.

Discussions

Among the subjects to be discussed will be present and future energy requirements in relation to energy resources available; economics; operating characteristics; the siting of nuclear power stations and its effect on system planning; health physics; radiation detectors; pulse circuits; nuclear measuring instruments for research, processing control, and for prospecting and mining applications; instruments for nuclear reactors and associated plants; and data processing for nuclear applications. It is proposed that visits of technical interest will be associated with this convention.

The organising committee will be pleased to receive offers of papers for consideration for inclusion in the convention.

Nuclear Generation

The council understand that the Federation of British Industries are considering holding a conference on the general problems of nuclear generation during 1961, and there will be an appropriate co-ordination of arrangements where possible.

THE THIRD INTERNATIONAL CONFERENCE ON MEDICAL ELECTRONICS

The Electronics and Communications Section of The Institution of Electrical Engineers announces that with the support of the council they are organising the Third International Conference on Medical Electronics in London in the second half of July, 1960, in association with the International Federation for Medical Electronics, which was inaugurated this year.

Scope

The keynote of the conference is the bringing together of members of the medical and electrical engineering professions in discussion to which both sides can contribute, so that each will gain a better understanding of the problems of the other. For this purpose there will be general sessions to enable medical practitioners and electrical engineers who are not experts in medical electronics to increase their background knowledge of the field, and specialist sessions in which those engaged in medical electronic work can present papers on the latest developments and discuss particular problems in greater technical detail.

Present plans include the organisation of an international scientific exhibition on medical electronics in conjunction with the conference.

OUR COMPANION JOURNAL


PRACTICAL WIRELESS

1/6 Every Month


TV at the National Radio Show

A REPORT ON THE TRENDS OF DESIGN OF THE MODERN RECEIVER AS SEEN AT THIS YEAR'S EXHIBITION

IN previous years the keen experimenter has looked forward eagerly to the Radio Show in order to see what modifications have been made to the standard television receivers during the year. New circuits have appeared annually, with various features designed to surpass those given by the previous year's models, and manufacturers have vied with one another to introduce some exclusive feature. Thus we have seen A.V.C., flywheel sync, automatic picture control, and other ideas, and it would appear that at last the circuit has reached finality. Thus there was a very keen interest aroused at the opening of the Radio Show as to what might appear, but when the opening day came the prophecies of many were fulfilled—there was little new circuitry. As most readers are aware, the BBC have been experimenting in Bands IV and V, and in many quarters it was expected that some developments would be seen in tuning ideas in order to cover these bands with existing techniques. The question of higher definition has also arisen recently, and speculation centred round the possibility of new timebases which would readily lend themselves to quick modification should a high-definition system appear later in this country. However, nothing on these lines appeared, and the circuits which were employed were more or less as before.

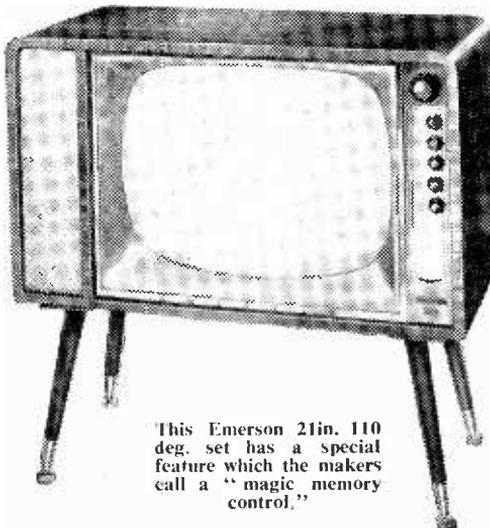

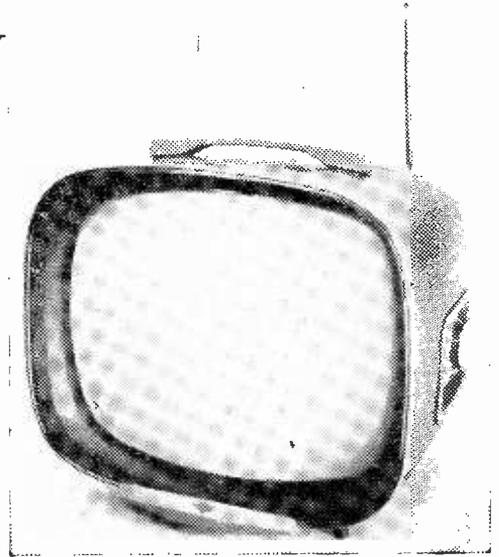This Emerson 21in. 110 deg. set has a special feature which the makers call a "magic memory control."



The K.B. 17in. Royal Star with 110 deg. tube and slender cabinet.

Smaller Cabinets

Most of the developments which were visible to the lay public in past years were concerned with the tube, which has gradually increased in size from 7in. up to the now commonplace 21in. This year, however, whilst size remained constant, the use of wider deflection angles resulted in the production of much shorter tubes with the result that cabinet sizes have been reduced considerably. This, then, was the only outward sign of development at this year's Show. Coupled with the modern designs used by many manufacturers, the result was a pleasing departure from many of the sets seen at previous Shows.

Although transistors were employed in certain stages of some receivers, it was not expected that there would be a marked development in this field, especially in view of the details given in our recent article on this subject. The all-transistor TV set is a long way off, although just before the Show opened, an announcement was made in the U.S.A. that a manufacturer there had developed a successful set using transistors.

The illustration on page 10 shows some of the features of the modern television set, and in this product of the Spencer-West company, the shortness of the tube, the compact turret tuner and the printed circuit layout show how the overall size has been satisfactorily reduced.


Printed Circuits

The printed circuit technique is now more widely used and though still a point of controversy amongst service engineers it is playing a large part in design. It has resulted in some price decreases by reducing manufacturing time but conventional wiring remains popular.

Separate "boards" for the timebases and other sections—which are easily replaced in the event of a breakdown—are a feature of some receivers. We did not see one printed chassis this year which was complete in itself.

Accessibility

Manufacturers appear to have paid particular attention this year to the serviceman, and various ideas have been adopted to facilitate access to the wiring, etc., for servicing. In the Ekco receivers, for instance, there is a quick-release back cover, whilst the swing-out, or other easily removable chassis, was featured by other firms. It appears that many firms still do not make the front of the screen easily accessible so that the layer of dust and dirt which accumulates owing to electrostatic action can be removed. In most cases the set must be removed and the glass cleaned from inside the cabinet, whereas a simple, hinged implosion guard would appear to be fairly simple to fit to most cabinets, and would surely be a good selling point.

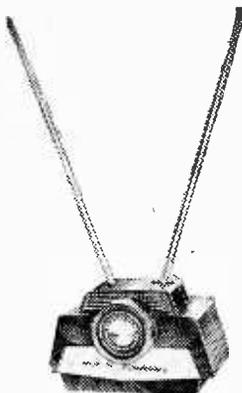


Push-button Control


One development which appears to be interesting a number of manufacturers, and which is regarded by many amateurs as a retrograde step, is the inclusion of push buttons for control purposes.

The Belling-Lee "Metropolitan" all-channel set-top aerial, with gold plated telescopic rods and finger-tipped tuning.

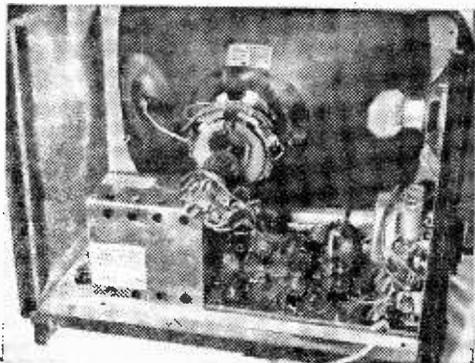At one time these were extremely popular on normal radio receivers, but they appeared to die out, either because the mechanism in use at the time was noisy or unreliable, or because the user preferred to turn a knob and feel that he was locating the correct tuning point. With the appearance of the tape recorder, how-



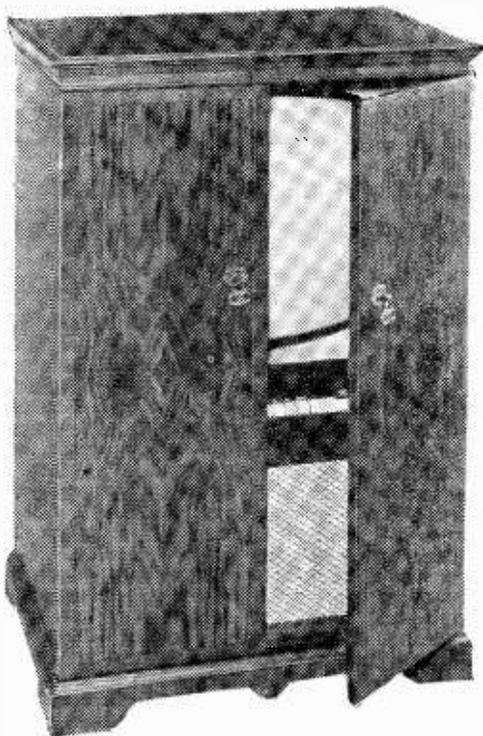The inside of one of the Spencer-West receivers showing how compactness has been achieved.




The Dynatron 21in. push-button receiver for TV and F.M. sound.

ever, there was a return to this type of mechanism, and the majority of recorders now use this method of control for the various functions. The mechanics of the method have now been improved and push-button control should be effective and reliable. In the Dynatron receiver, for instance (see the illustration above), buttons select the programme (including I.T.A.), as well as the normal BBC sound programmes on V.H.F./F.M. In addition there is a remote control device so that stations can be changed without the viewer rising from his chair. In this arrangement a synchronous motor operates the turret-tuner.

V.H.F. Sound Radio

Many receivers now include a section or circuit modification for reception of V.H.F./F.M. radio so that advantage can be taken of the higher quality available.

Whilst on the subject of higher quality, it still appears that the majority of manufacturers do not pay sufficient attention to the sound reproduction aspect of the modern television receiver. In view of the very high quality which can be obtained on the television frequencies (and with the reception of the F.M. programmes) one would certainly have expected more manufacturers to have fitted a speaker capable of doing justice to the wide frequency range which is available and to have provided a cabinet suitable for housing such

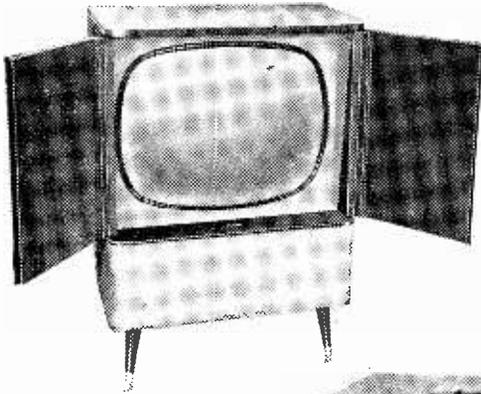


This is the Pam Model 666, with 21in. tube and polaroid filter giving good pictures under all lighting conditions.

a speaker. In many instances there is a small speaker mounted on the side of the cabinet near the front or back with virtually no baffle area, and a very simple audio amplifier section is provided in the receiver. Whilst it may be said that the majority of the programmes on TV are plays or advertisements, there are some occasions upon which good sound reproduction would be worthwhile. Many constructors still use a separate amplifier and speaker assembly but we do not recall having seen one commercial receiver in which facilities are provided for using a separate amplifier. In these days of "hi-fi", one would have expected some facilities to be made available. Perhaps the necessary switching is the main deterrent.

Aerials

Although TV aerials are often thought of as incidental to the set, they are, nevertheless, a vital part of any installation. They ranged this year from elaborate Yagi arrays, down to neat portable units designed to stand on top of the receiver. A typical unit in the latter category is shown on page 10, the Belling-Lee "Metropolitan." This is an all-channel set-top aerial with finger-tip control which enables the aerial to be tuned for maximum performance on all channels. Similar to the previous aerials of this design by the same makers, this aerial is gold-plated on the telescopic elements and covers all channels, horizontal or vertical polarisation, and the F.M. band.

In the field of the larger arrays is the Labgear assembly shown at the bottom of this page. This is a 3-channel model catering for one Band I and one Band III station originating from one direction, and an additional Band III station originating from a completely different direction. With this particular aerial only one feeder connection is needed, no diplexer or triplexer having to be employed. The makers give as an example

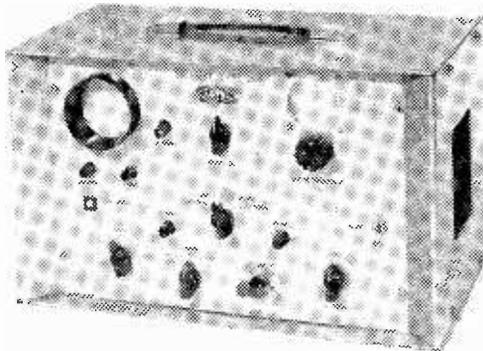


a viewer living in the Oxford area who may orient this aerial to receive Channel 1 and Channel 9 from London, and Channel 8 from the Midlands, thus having the choice of three stations.

In addition to the standard types of diplexer already well known, Labgear introduced a new design for East anglia. With the opening of the East Anglian I.T.A. station many viewers will have available both Channel 9 and Channel 11, and thus there will be a need for a diplexer to avoid changing aerial leads or introducing switching. This new unit is designed to overcome such difficulties.

It is interesting to note that one manufacturer has withdrawn some models which were previously on the market 10 element arrays have been replaced by a super 11 element array.

All horizontal stacked arrays of this company (Antiference) have been withdrawn, but separate stacking bar kits have been introduced so that any pair of single arrays may be stacked as desired.

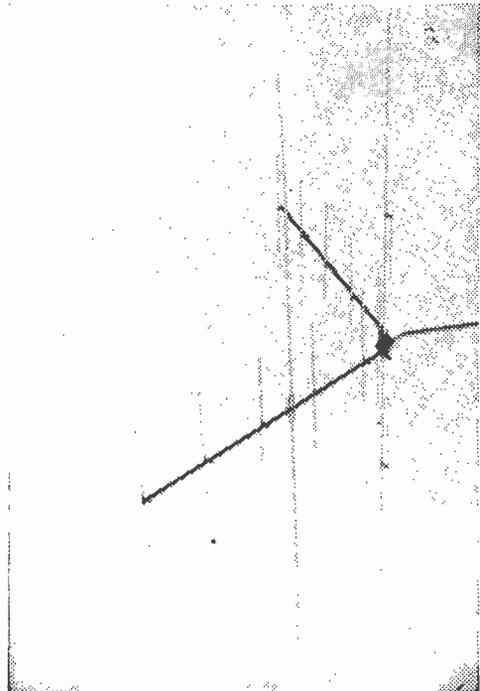The very latest model "Televet" tester, which is, in effect, a combined signal generator and oscilloscope, and will be found invaluable for servicing TV sets.



A Labgear three-channel array, providing reception of two stations from one direction and another from a different direction.

Replacing C.R. Tubes—7

MURPHY RECEIVERS

By H. Peters

(Continued from page 597 of the July issue)

Latest Models V310, V310A, V310C, V310D, V310CA, V310AD, V320, V320C, V320A, V320AD, V330, V330D and V330F

THE previous article of this series concluded with details for replacing the tube in the range of models listed above. The basic model is the V310 which is illustrated in Fig. 17. The methods of setting-up and boosting the tube are as follows:

Setting Up

Picture tilt is altered by the thumbscrew in the slot in the middle of the scancoils and this adjustment should be made after the ion trap and focus

KEY TO LETTER REFERENCES IN FIGS. 13-17

- B: Clamping bolt.
- C: Clamping band.
- F: Focus magnet lateral adjustment (focused with user's control set midway).
- I: Ion trap magnet.
- L: Loudspeaker contact.
- M: Adjustment for centring tube in mask.
- P: Picture positioning adjustment (needs unlocking first).
- R: Rubber seating blocks.
- S: Scancoils.
- SP: Spring clips holding tube cradle to chassis.
- T: Picture tilt.

magnets have been correctly set up. The joystick picture position control functions in the same way as the one on the V270/280 series.

Boosting the Tube (A.C. Only)

A 13 volt low capacity transformer should be used and fit as far away from the tube as practicable to avoid distorting the scanning field. A 40 ohm, 5 watt resistor should be substituted for the tube heater across the existing wiring to pins 1 and 12 of the tube, and the 13 volt winding of the boost transformer connected to the vacated pins. Mains for the transformer can be picked up from between chassis and the set side of the mains fuse.

Model V350—Unboxing

Remove mains and aerial inputs, turn the knobs to BBC and off respectively and lay the set on its face. Remove the knobs by unscrewing their clamps which are inside the cabinet and accessible via the two long slots in the cabinet back. Any attempt to remove the channel selector knob whilst switched to a position other than BBC will break it. Remove the two large bolts at the back on either side of the protective bulge, and lift the cabinet off the set. It will almost certainly be very stiff, and may need holding

about $\frac{1}{2}$ in. off the bench while somebody else forces down upon the contrast and brightness controls. Do not attempt to "pick" the chassis out. Remove the C.R.T. base, ion trap magnet, and anode cap. Stand the chassis face down, remove the four cross headed screws supporting the side plates and also the two diagonal strengthening stays and lift the chassis off the tube. Clean and replace in reverse order. Picture position is fixed by two rotary magnets, which are controllable from the back via a steel rod which is moved in and out to engage either disc.

Model V230

The tube change on this model follows closely the V240, once unboxed.

Unboxing

Lay set on its face and remove the two gilt screws holding the cabinet handle. Also remove their two opposite numbers underneath. Lift out the three gilt mouldings and the brown foot underneath, when the two halves of the cabinet shell may be parted and withdrawn. Be careful not to catch the brown bakelite feet, as the plastic studs which hold them may fracture.

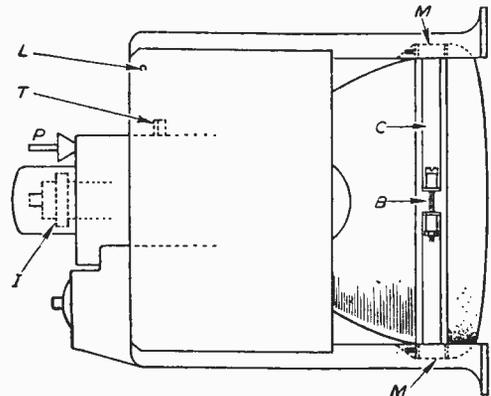


Fig. 17.—Side view of the V310.

To replace the C.R.T., remove focus dome, C.R.T. base, ion trap magnet, and EHT cap. Remove the four 2 B.A. nuts securing the rubber mask and clamp to the chassis and withdraw the tube and clamp forward. Note the position of the EHT connector in relation to the clamp and unclamp the tube. Clean all parts before re-assembling.

Setting Up

As for V310. When reboxing be careful to locate the control knobs in the centre of the bakelite discs, otherwise the disc will spring out

(Continued on page 20)

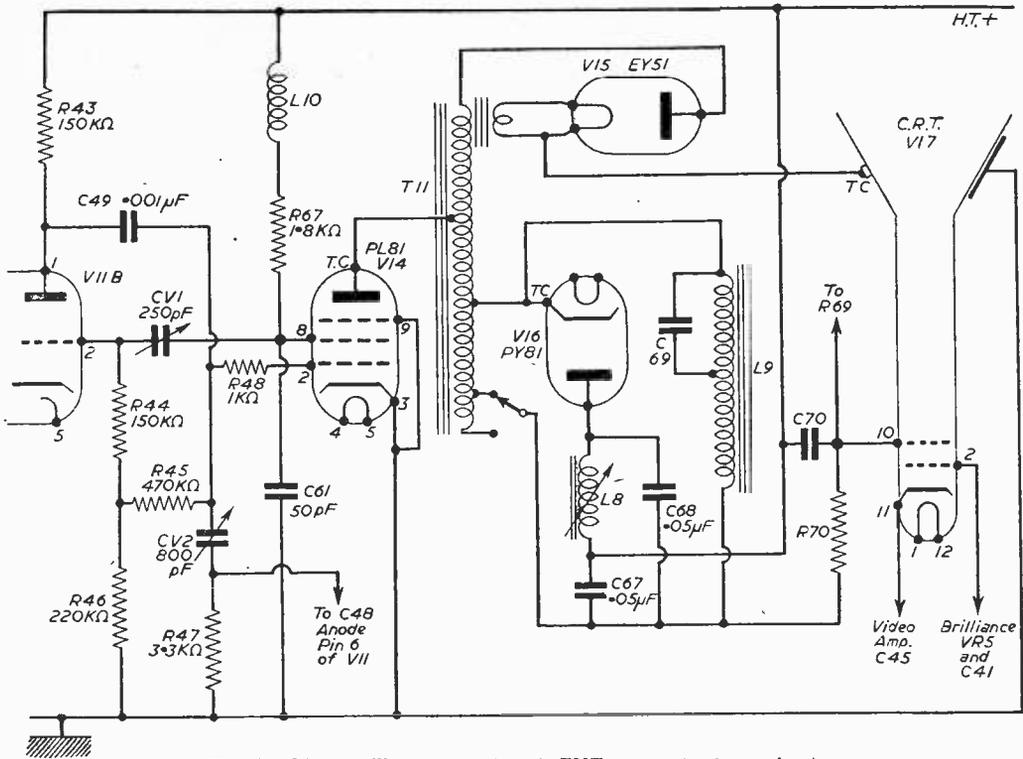


Fig. 2.—Line oscillator, output and EHT stages (early versions).

No Picture

Advance *brilliance*. If there is no raster remove rear cover and screening case of line output section. Listen for the characteristic whistle of the line timebase and note EY51 EHT rectifier heater. If line whistle is absent the EY51 will be out whereupon V14, PL81 and V11, ECL80 should be checked. If line whistle is audible but the EY51 is out check for spark at the single

wire end of the EY51. If a heavy spark is available the EY51 is probably at fault due to an o.c. heater. If the spark is subdued or the EY51 is glowing blue, or both, remove the EHT clip from the tube. If the glow subsides but the spark obtained at either end of the EY51 seems of the same (rather vicious) quality, the valve should be replaced as it is probably shorted internally. If the spark at the heater end (EHT clip) is thin as compared to the anode (single

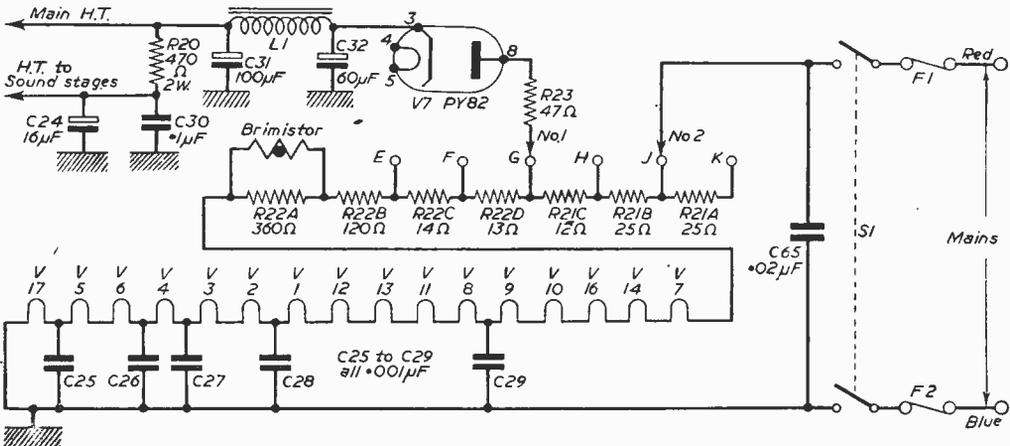


Fig. 3.—Heater wiring and the H.T. supply.

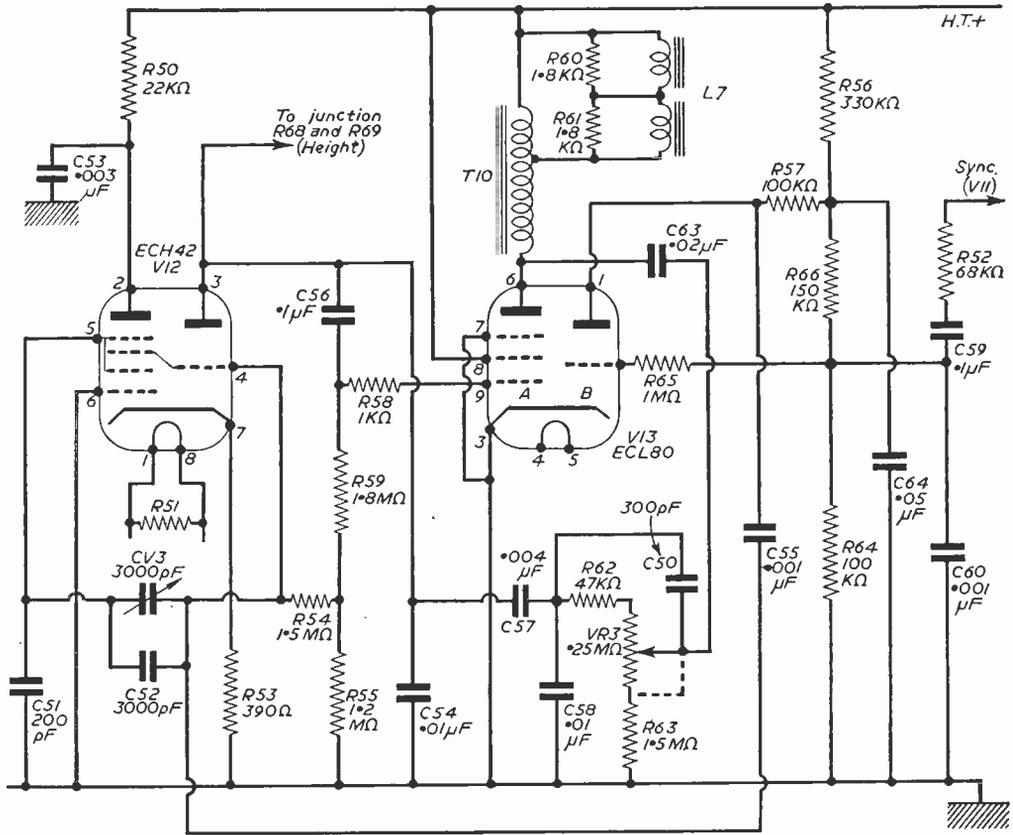


Fig. 4.—Frame oscillator and output stages.

wire), replace the clip on the tube. remove the tube base socket and short pins 1 and 12 (to preserve heater continuity). If the EY51 now behaves normally and the EHT is present, the tube can be assumed at fault.

Lack of Width

Check valves PL81, PY81 and PY82 after having checked the setting of CV1. If there is no improvement, check V11 (ECL80) and R43 (150k Ω). The 1.8k Ω resistor R67 to pin 8 of the PL81 can change value but this is not very common. The line timebase circuit given is the early version and the wiring may be found to differ but only as far as the line output transformer and scanning coils are concerned.

Lack of Height

If the loss is even top and bottom check R68, 8.2M Ω and R69, 20M Ω . If these are in order, check V12, V13 and resistors R54, R55 and R59, capacitors C56 and C54, etc. If the bottom of the picture is compressed, first check V13 (ECL80) then C56, C54, etc. If the top of the picture is compressed, check the linearity circuit components C63, VR3, R63, C57 and C58.

Inability to Lock

If CV3 is at the end of its travel, i.e., screwed

right in, check V12 then R54, 1.5M Ω . If CV3 will not screw in but just clicks, note previous remarks concerning stripped thread.

If the picture rolls up or down but will not lock, check R37, C59 and C60, then V11 and V13, R56 and R57.

Horizontal White Line Only

This denotes a complete absence of frame scanning. Check V12 and V13 and then V10. If these valves are in order, check T10, the frame output transformer, by taking a voltage check at pin, 6 of V13. Absence of H.T. will denote an open-circuited winding. If this is in order ensure that CV3 is not shorted.

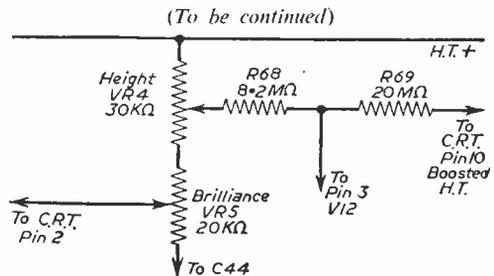


Fig. 5.—Height and brilliance control network.

TELENEWS



Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of July, 1959, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal ...	1,726,212
Home Counties ...	1,241,324
Midland ...	1,475,326
North Eastern ...	1,587,792
North Western ...	1,303,231
South Western ...	778,463
Wales and Border Counties ...	566,033
Total England and Wales ...	8,648,381
Scotland ...	784,843
Northern Ireland ...	116,565
Grand Total ...	9,549,789

Anglo-Dutch Church Service

SOMETHING new in Euro-vision is to be undertaken on Sunday, September 27, when two church services—one in Hull, the other in Rotterdam—are to be televised together. The services will be held simultaneously, the congregations singing the same hymns and listening to their respective ministers speaking in Dutch and English. The churches are Holy Trinity Church, Hull, and the Morning Star Dutch Reform Church, in Rotterdam. The latter church is new and not yet equipped with an organ, so the organ music for both congregations will be provided by Hull.

ITV Area Survey

A PRE-TRANSMISSION survey to determine the number of Band I (BBC only) and Band III (potential BBC and ITV) sets in the area to be covered by the new ITV transmitter at Mendlesham, Suffolk, is now being carried out by Television Audi-

ence Measurement Limited. The survey will also determine the composition of audiences in homes with television sets and, separately, in homes with Band III sets.

I.T.A. Appointments


THE INDEPENDENT TELEVISION AUTHORITY has appointed Commander Guy W. Alcock, O.B.E., R.N., M.I.Mech.E., as its officer in East Anglia. Commander Alcock, aged 50, has recently been attached to the authority's headquarters in London. He will act as the authority's representative in the area to be served by its Mendlesham station.

The authority has also appointed Mr. Llywelyn John Evans, B.L., as its officer for Wales and the West of England.

Mr. Evans is 45 and Welsh speaking. He was educated at Aberacron, Cardiff and Aberystwyth and until recently held the position of Welsh Editor of the "News Chronicle." Before that he was with the Central Office of Information, the "Daily Herald" and the "Western Mail." He has made a special study of industry and Welsh affairs and was called to the bar in 1945.

East Anglian Programmes

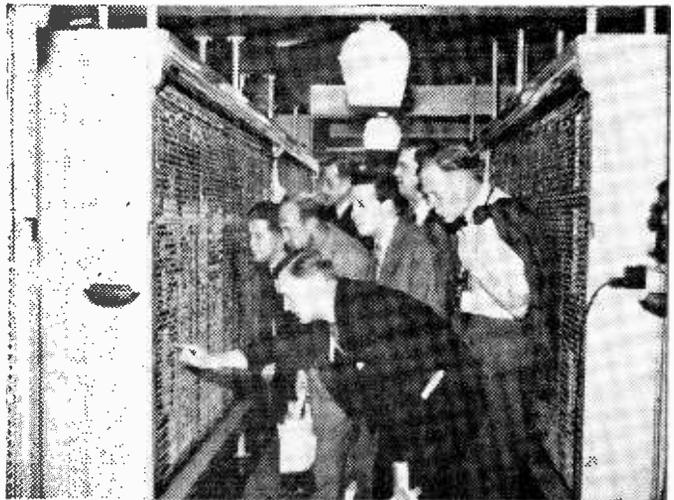THE I.T.A. and Anglian Television announce that Independent Television programmes



Recently a group of Finnish television and advertising executives have been studying methods of TV production, presentation and advertising in Britain. The illustration above shows members of the delegation closely studying the "traffic" room of Granada TV's Sales and Advertising Dept. The indicators in this room record future advertisements, the time and date they will be shown, and their duration.

will begin in the East Anglia area on Tuesday, October 27th. The programmes will be transmitted from the authority's new station at Mendlesham near Stowmarket and more than two million people will be within its service area. This will stretch from The Wash to the Thames Estuary and as far west as Huntingdon.

The Mendlesham station will operate on Channel 11, and it will transmit horizontally polarised signals.

TV in Radio

AN interesting development to speed the presentation of news items in the BBC's Sound Broadcasting Service is the introduction of a closed-circuit television system to provide news-readers and announcers with news flashes whilst they are actually broadcasting.

When any items of special interest come into the news room a script is prepared and placed under the camera lens. An image is immediately reproduced on a high-grade 14in. picture monitor in the sound studio as required, and the news-reader or announcer can then read the item at a convenient point in his broadcast.

Nigerian TV

AFRICA will have its first permanent television service when two stations begin programme transmissions later this year. The West Nigerian Government, having decided to establish a television service, has placed contracts with Marconi's Wireless Telegraph Company for the supply and installation of transmitting and studio equipment for two stations; these are located at Ibadan and Abafon. A further contract awarded provides for the technical operation and maintenance of the stations for a preliminary period of one year during which Nigerians will be trained to help take over the operation of the new service.

Scottish I.T.A. Stations

THE INDEPENDENT TELEVISION AUTHORITY has ordered Marconi vision and sound transmitters for the proposed two new Scottish ITA transmitting stations, for the Aberdeen and Inverness areas. They are the same type as those which are used in ITA stations at Chillerton Down, Isle of


Wight (Southern Television) and Burnhope (North-east).

TV and Radio Despatches

MORE than a million television receivers were despatched by the manufacturers to

TV "Saturation"

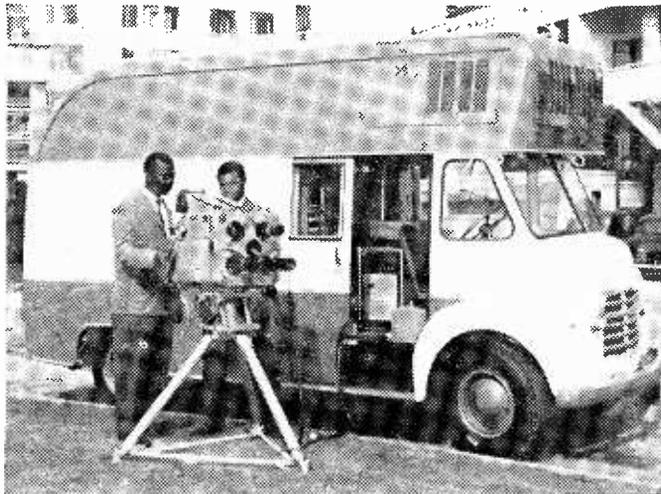THE United Kingdom, with nearly 9½ million TV licences at the end of last June, had TV sets in more than 50 per cent. of households. The highest percentage was in the Mid-



The outside broadcast vehicle which Marconi's have built for operation in Nigeria. Two Nigerian engineers, who are training in England, are examining one of the cameras. (See "Nigerian TV").

the radio trade in the first six months of the year, according to the estimates for June, published by the British Radio Equipment Manufacturers' Association. The figures for January-June, 1,033,000, are 80 per cent. above those for the first six months of last year (573,000). Despatches of radio receivers, 645,000, are 17 per cent. above those for the first six months of last year (550,000) and of radiograms, 67,000, 6 per cent. lower. Despatches are net figures of deliveries by manufacturers to the home trade.

TV in Ghana

AN order has been placed with E.M.I. Electronics Ltd. for what is believed will be the first television system to go into operation in the new West African republic of Ghana.

The system will be used at a large gold mine as an added security measure to guard against pilfering and unauthorised processing of gold ore. Three cameras are being mounted at vantage points to scan the working area and relay pictures to receivers placed in the offices of senior security officers.


land region and the second highest in the North Midlands. The 10 millionth licence is imminent.

Already claiming to have the highest television coverage of any country in the world, the UK networks go on expanding; by the end of the year, 98.7 per cent. of the population will be within the BBC service areas and 94 per cent. within the I.T.A. service areas.

German TV

THE German Radio Exhibition at Frankfurt-on-Main, which opened on August 14th and closed on August 23rd, just before the Radio Show opened, presented a number of new features which have not been seen in this country.

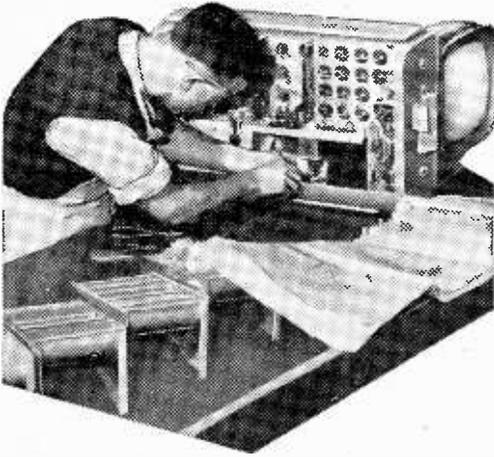Television sets have more automatic control (A.F.C. for automatic tuning, automatic contrast control according to ambient lighting, automatic mains voltage regulation, and automatic width control) all in addition to A.G.C. and flywheel sync that are common over here. Some areas also are already using Bands IV and V (for their second programme).



Analysing and Servicing TV Receivers

No. 9.—THE C.R. TUBE

By "Diadem"

the anode of V1. and therefore the grid of the C.R. tube, assume the potential of the H.T. supply because there will be no potential drop across the load components of V1 (Ohm's law). This will promote excessive beam current in the C.R. tube. However, with cathode modulation, a faulty video

THIS month's article deals with the use of the cathode ray tube in television receivers, and covers grid and cathode modulation, together with faults in C.R. tubes.

Modulation

There are two methods of modulating the C.R. tube with picture information. The first is to couple the output from the anode of the video amplifier valve direct to the cathode of the tube (Fig. 35) and the second is to couple the output direct to the grid (Fig. 36). In the first instance, a negative-going video signal is required and in the second a positive-going signal is required. As can be seen from Fig. 37, in the case of grid modulation it is likely that the C.R. tube will be damaged if for any reason V1 ceases to pass current. In this instance,


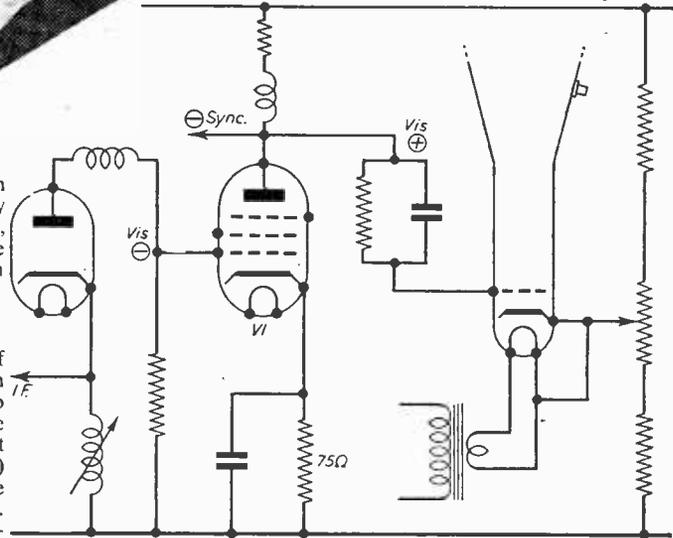


Fig. 36—Grid modulation (and the use of an isolating heater transformer).

Fig. 35.—Cathode modulation of the C.R. tube.

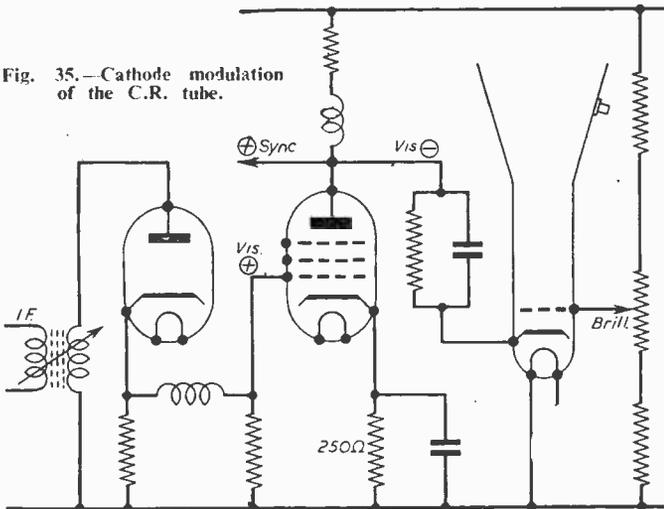

stage can only bias-back the C.R.T. to a point of lower beam current. Fig. 37 shows how grid modulation can still be used without the danger to the tube. Two extra valves and three resistors are needed. If the 6J5 were to fail, the grid of the C.R.T. would assume chassis potential and beam current would be thereby reduced. The 6J5, it will be noted, is functioning as a cathode follower.

In modern receivers using cathode modulation the trend is to feed direct from the video amplifier into the cathode follower (Fig. 38). By dispensing with the coupling capacitor, a D.C. restoring diode is no longer required. (If a negative sync pulse is needed it can be taken from the anode providing a load resistor is inserted in the circuit).

Tube Shorts

One of the most commonly occurring faults is a short between heater and cathode. As the heater

of the tube is generally connected to chassis, either directly, or through valve heaters, the potential of the tube cathode is altered. The remedy for this fault is to feed the heater of the tube from an isolating transformer as shown in Fig. 36. One side of the heater can be directly joined to the cathode. However, if this transformer has an appreciable capacity to chassis, the quality of the picture will be degraded. Even the use of "low loss" transformers may produce a noticeable effect upon the quality of the picture and the procedure indicated in Fig. 39 may be adopted. (See Tube Faults.)

Faulty Tetrode Tubes

The normal circuit for a tetrode tube is shown in outline in Fig. 40a. If a heater-to-cathode short develops, an isolating transformer can be used (Fig. 40b). If a cathode-to-grid short occurs the supply to the first anode is removed and the first anode is then used as the control grid

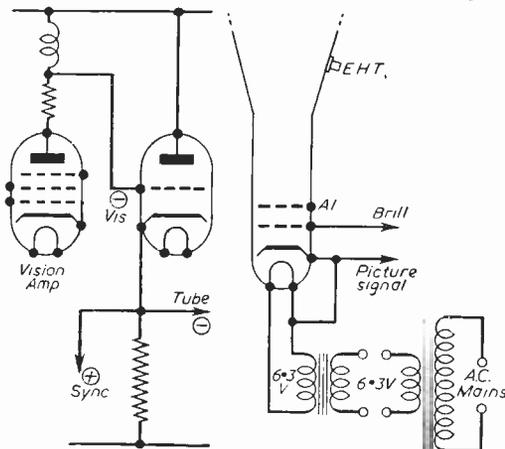


Fig. 38 (Left)—Feeding the cathode follower direct from the anode of the video amplifier.

Fig. 39 (Right)—A method of using an isolating transformer in conjunction with the existing transformer.

(Fig. 40c). The original control grid (g1) is strapped direct to the cathode.

Heater Wiring

When removing the heater wires from a faulty tube in an A.C./D.C. heater chain a resistor should be connected across them, the value and wattage of the resistor depending upon the tube voltage and current (Fig. 41). The resistance is obtained by dividing the heater voltage by the heater current. Next multiply the tube heater voltage by its current to find the required wattage of the resistor. For example: 13.3 divided by

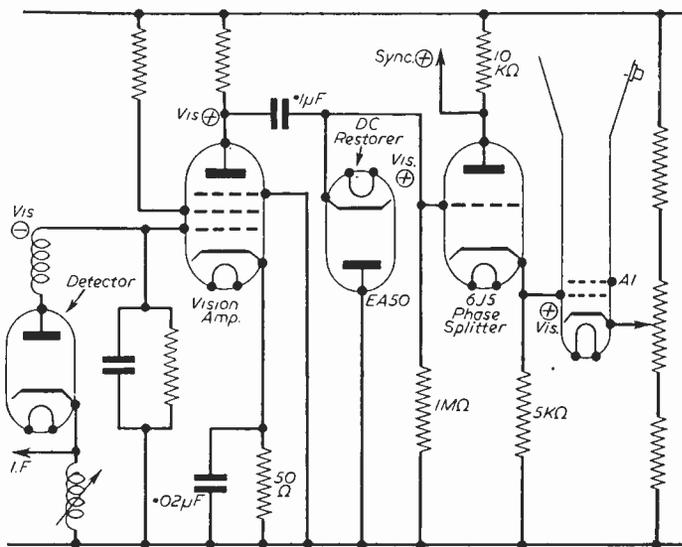


Fig. 37.—The use of two extra valves to remove the danger to the tube when grid modulation is used.

0.3 gives 44 ohms and 13.3 multiplied by 0.3 gives 5 watts. A 40 ohm resistor would be easier to obtain and the use of a 10 watt type would give better heat dissipation. For a 6.3V, 0.3A tube, the resistor would be 21 ohms, 2 watt rating. Here again the wattage could be increased if desired.

If a tube is replaced with one having an external graphite coating it is important that this be connected to the chassis with a flexible metal spring, otherwise very high voltages will develop on the coating.

Tube Faults

Uncontrollable brilliance. When the cathode of the vision noise limiter, usually an EB91, is connected direct to the video amplifier anode, and this in turn is connected to the tube cathode, a heater-to-cathode short in the limiter valve will provoke this symptom. A heater-to-cathode or a grid-to-cathode short in the tube will also cause the brilliance to be uncontrollable. If the tube heater is connected to an isolated winding, the same fault will show itself. If the heater is decoupled by a condenser to chassis and this component develops a short or leak, check cathode potential and, if low, suspect a heater-to-cathode short.

Excessive brilliance can be caused if the resistor at the "earthy" end of the brilliance chain goes high or open circuit.

Erratic, excessive or no brilliance. Check the video amplifier valve.

Inability to obtain raster without signal. Check the brilliance control resistor chain for increases in resistance or reduce present resistors in chain, but see that the grid potential does not exceed the cathode potential when the control is at maximum.

Smearing. Heater-to-cathode leak in tube.

Defocused tube. Low emission, heater-to-cathode leak, or low H.T.

Intermittent dark bands with watery effect, out

of focus double image, and smearing. This is the effect of a cathode-to-heater short when the tube filament is fed by an isolated heater winding from a transformer.

White blurred bands across screen. Picture enlarges or disappears on operating brilliance or contrast controls and sometimes the brilliance control is ineffective. Check for cathode-to-grid short in tube.

Picture enlarges or disappears on highlights. After checking the EHT rectifier for low emission, suspect low emission tube or faulty vacuum. Examine the getter. This should be silver or silvery black, not cloudy white.

Short in tube. The EHT may be overloaded and prevent the line transformer from oscillating with the result that in some circuits the line output valve will get red hot. Remove the tube EHT cap and see if valve and EHT return to normal. It may be necessary to replace the EHT

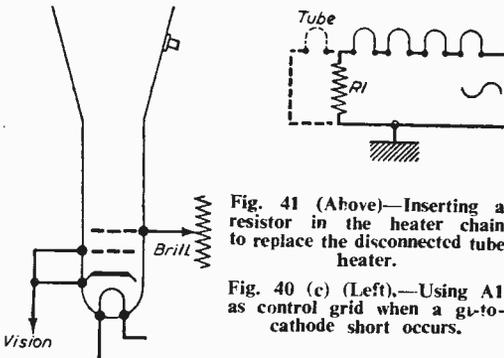


Fig. 41 (Above)—Inserting a resistor in the heater chain to replace the disconnected tube heater.

Fig. 40 (c) (Left).—Using A1 as control grid when a g1-to-cathode short occurs.

rectifier if damaged by short. In tetrode tubes a short from A1 to chassis often provokes this symptom.

Raster faint picture grey. Check the voltage on the tube cathode, the video output valve and its resistors, and resistors and condenser (if any) feeding the tube cathode. See articles 2 and 3 October and December, 1958, issues.

Poor definition. Besides being caused by a low emission or faulty tube, the voltage on A1 in tetrode tubes affect the scanning spot size. This voltage is not always easy to check when it is fed through a high value resistor or "Metrosil." In this case check with a high resistance meter of at least 20 kΩ per volt. Between 300 to 400 is average voltage.

Brilliance control works in reverse. When the control is at minimum a brilliant raster is obtained which disappears when the control is turned up. Suspect heater-to-cathode short in tube.

Picture too dark. With slight movement of brilliance control, picture becomes too bright. Examine brilliance control resistor chain for high or open circuit resistors.

Tube heater open circuit. Examine carefully the solder joints on the valve pins and resolder to be sure.

Ion trap magnet. If this is tight on the tube neck, leave it alone, and search elsewhere for the fault if a raster cannot be obtained. If it is loose

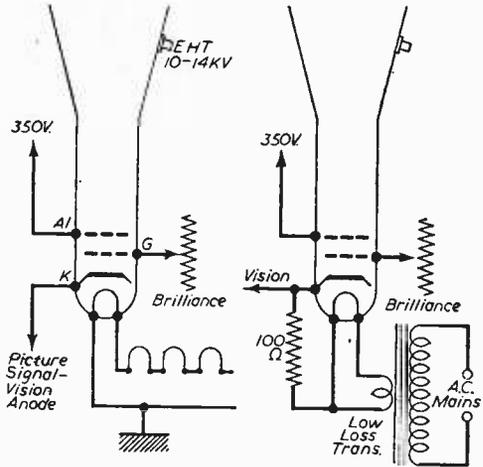


Fig. 40 (a) (Left).—Outline of circuit for a tetrode tube. Fig. 40 (b) (Right).—Using a heater isolating transformer.

or has been knocked, twist it round slightly each way to see if a raster can be obtained. It is unlikely that it has been knocked forward or back.

(To be continued)

REPLACING C.R. TUBES

(Continued from page 12)

of the spring clip. Should this happen, the clip can be refitted to the disc by equal pressure all round.

Screen Cleaning (Models V230 and V350)

This can be done without unboxing the set by picking the safety glass out of the rubber mask, and carefully replacing in the same way, scoring round the edge with a non-metallic tool.

Earlier Models V180, V178, V176, V120, V118, V116 and V114

These are all designed for easy tube changing. The back is removed, the EHT discharged, and the C.R.T. base connector and anode cap removed. The safety glass or front fascia board is then removed and where springs hold the tube mask or the tube is clamped at the back of the neck, these are released, when the tube and mask may be withdrawn through the front of the set.

Picture tilt is corrected by moving the scan-coils after the two locknuts have been slackened in the slots on each side of the focus magnet. Focus and positioning are interdependent, and the user control is set midway throughout all adjustments. Separately moving each of the three thumbscrews projecting from the focus magnet will give picture position, whilst moving all three in or out together will correct focus. Coarse adjustment of focus may be obtained by moving the circular band which supports the tube.

Boosting

Remove the wires from pins 1 and 8 of the tube and tape them back. Fit a 2 volt low capacity boost transformer.

Out in the blue

2 radio men on 4 wheels

Take one wireless truck, one wireless operator, one wireless mechanic. Drive 300 miles on rough tracks, find a spot that's just a map reference. Set up a radio station and link strike aircraft with base. Keep it going . . . stay fit. . .

These R.A.F. men are no mere tradesmen. Nobody's mere anything in the R.A.F. Every man has skilled training, and a job he's counted on to do supremely well.

But the R.A.F. gives a man far more than 'know-how.' It gives him a career that's both secure and exciting. It gives him a standard of living that's hard to better in civilian life. It takes him—with his family—all over the world.



A full life in the R.A.F.

IS THIS YOUR LIFE ? The R.A.F. wants men who make the most of life's chances. There are vacancies now in these key jobs. Full pay while you train, specialist pay when you qualify. Tick your particular interests, and post the coupon for free booklets about R.A.F.

- Wireless Mechanic
- Electrical Mechanic
- Nursing Attendant
- R.A.F. Regiment
- Operations Clerk
- Radar Mechanic
- R.A.F. Police
- Progress Clerk
- Teleprinter Operator
- Typist
- Wireless Operator
- Tape Relay Operator

NAME DATE OF BIRTH

ADDRESS

Post to: Royal Air Force Central Recruiting Office, Dept. PW19, Victory House, Kingway, London, W.C.2.

Completely rebuilt with new electron Gun Units delivered immediately—free in the U.K.

CATHODE RAY TUBES



All covered by a full 12 months guarantee. Midland Tubes for service and quality. A member of the Association of Tube Rebuilders.

For full details and prices please write direct to :

MIDLAND TUBES LIMITED

37 George Street, Manchester, 1.

Tel.: Cen. 4568.

TRANSISTORS

Surplus:	each
RED SPOT (Audio/Experimental Application)	7/6
WHITE SPOT, R.F. up to 2.5 Mc/s...	12/6
Standard:	
MAZDA XA104 R.F. up to 6 Mc/s...	18/-
.. XA103 R.F. up to 4 Mc/s...	15/-
.. XB104 Audio up to 1 Mc/s...	10/-
MULLARD OC16 Power 3 watt ...	54/-
.. OC44	26/-
.. OC45 R.F. up to 6 Mc/s...	22/-
.. OC70	14/-
.. OC71	14/-
.. OC72	17/-

RECTIFIERS FOR BATTERY

CHARGERS
12 v. 1 amp. 4/3. 12 v. 2 amp. 7/-. 12 v. 3 amp. 10/-. 12 v. 4 amp. 12/6. 12 v. 5 amp. 14/6. 12 v. 6 amp. 15/9.

EX-GOVERNMENT HEADPHONES, Etc. High Resistance Headphones type CHR 13/6, pair, available either cream or black. Low Resistance Headphones, impedance 120 ohms, type CLR 7/6 pair, American Throat Microphones, type T30 3/- set.

ACOS MICROPHONES

Acos Mic 39-1. Crystal Stick Microphone for use as a hand, desk or floor stand unit for high quality recording, broadcasting and public address work. LIST PRICE £5.0.0. OUR PRICE 39/6. With Stand. 47/6. Postage 1/6.
Acos Mic Type 38-1. Crystal hand or table microphone. Flat response 30-7,000 c.p.s. Omni-directional. Suitable for tape recording, etc. Dark brown plastic case. Brand new in maker's cartons. List 50/-. OUR PRICE 29/6. Postage 1/6.
Mic 40, as supplied with most modern tape recorders, listed at 35/-. Our Price 25/-. With folding rest and 8ft. lead 40/6.000 c.p.s.

ALPHA RADIO SUPPLY CO.

VALVES GUARANTEED ALL TESTED BEFORE DESPATCH

CV31	16/7	KTW61	6/6	5U4G	7/-
DAF96	8/9	N78	19/11	5Y3GT	8/-
DF96	8/9	OZ4	5/6	5Z4G	9/-
DK96	8/9	PCC94	9/-	6A7	13/-
DL96	8/9	PCF80	9/6	6AL5	8/6
EBC33	6/9	PL81	12/6	6AM6	6/9
EB41	9/6	PL82	8/6	6F9G	7/6
EBF80	9/9	PX25	12/6	6F1	14/-
ECC84	10/-	PY80	7/6	6F13	14/-
ECC85	9/8	PY81	8/6	6F15	14/-
ECH42	9/8	PY82	7/-	6K7G	4/-
EH31	9/-	PEN4VA15-		6K8G	7/6
ECL80	10/-	PEN25	8/-	6L6	8/-
EP39	5/9	PENA4	15/-	6L8	13/6
EP40	14/8	SP41	3/-	6Q7G	8/6
EP41	9/9	SP61	3/-	6SL7GT	8/-
EP42	11/-	TP25	26/6	6SN7GT	7/6
EP50	4/-	U14	8/6	6U4GT	12/-
EP80	8/-	U25	14/-	6V6G	8/6
EP86	13/-	U191	11/6	6V6GT	7/9
EL41	10/6	UCH42	10/6	6X5G	7/6
EL42	10/6	UF41	9/-	12AT7	7/-
EL84	9/-	VU39 (MU12)		12AU7	8/-
EM90	10/-	14)	8/9	12AX7	8/-
EY51	10/-	X78	16/-	12C8	9/-
EY86	10/-	1CSGT	12/6	25A8G	11/6
EZ40	7/6	1HSGT	10/6	25L8GT	10/-
EZ80	7/-	1N5	10/6	2Y5	9/9
GZ32	12/-	1S5	7/6	3Z4GT	8/-
HL23DD	8/6	1T4	6/6		
KT33C	8/6	3S4	7/6		
KT66	17/6	3V4	8/8		

CATALOGUE

Our 1960 catalogue is now available. Please send 1/- stamps for your copy. Trade Catalogue also available, please attach your Business Letter Heading.

AUTOMATIC CHANGER UNITS

B.S.R. UA8. 4-speed Mixer Automatic changer, manual and auto-control complete with latest B.S.R. "ful-fl" pickup. Carriage and packing 3/6. OUR PRICE £6.19.6.

The new B.S.R. Model UA12. 4-speed Mixer Automatic record changer, fitted with latest type turnover cartridge. OUR PRICE £8.17.6. Carriage 3/6.

The latest Collaro Conquest. 4-speed auto-changer, in cream with Studio "0" insert. Brand new, fully guaranteed. £7.19.6. plus packing and post 3/6. Collaro. 4-speed single player unit with automatic stop, cream, turnover crystal cartridge, brand new and guaranteed. £6.19.6.

LOUDSPEAKER UNITS

* All brand new. * Note Special Prices. All Permanent Magnet 3ohms Impedance. each

3in. Units by Plessey, Goodmans, Lectra	17/6
6in. Units by Plessey	18/6
8in. Units by Goodmans	19/6
6in. x 4in. Units by Plessey	25/6
7in. x 4in. Units by Goodmans	19/6
8in. x 5in. Units by Goodmans	19/6
10in. x 6in. Units by Plessey	25/6
8in. Loudspeaker Unit 3 ohms Impedance with a Matching Output Transformer suitable for 6V6. Brand New but soiled, offered at a Special Price of 11/6 each, postage 2/-	
6in. Mains Energised Loudspeaker with Matching Output Transformer, Field Coil, 600 ohms. 17/6 each.	
8in. Mains Energised Loudspeaker with Matching Output Transformer, Field Coil, 600 ohms. 21/- each.	


ALPHA RADIO TERMS.—Cash with order or C.O.D. Postage and Packing charges extra, as follows : Order value 10/- add 1/3 ; 20/- add 1/9 ; 40/- add 2/6 ; 65 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

103. LEEDS TERRACE, WINTOWN STREET, LEEDS, 7.

From Metal to Glass


By C. Smallwood, Grad.I.P.R.E.

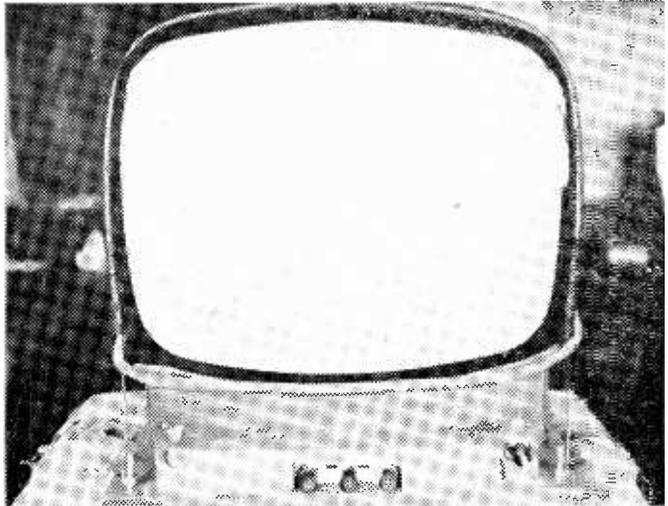USING A MODERN TUBE IN FERGUSON 989 and 990



Front view of the modified receiver showing the new tube support.

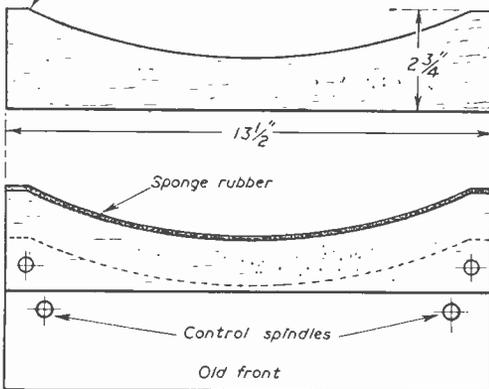Dimensions of new front made from 1/2" or 3/8" plywood



a chassis with a metal tube are eliminated. (The metal cone of the 16in. tube is connected to the final anode and therefore to the EHT supply--some 15 or 16 kV.)

It was decided to use an MW43-69, 17in. rectangular tube which is aluminised and also has a filter glass screen. Electrically, it is interchangeable with the 16in. type, except that its external conductive coating must be earthed and that pin 7 must be connected to pin 11 (cathode). The pentode gun gives better overall focus than the tetrode type--another advantage over the 16in. tube.

Mechanical Details

As will be seen from the illustrations the mechanical considerations are small. A new tube rest

(Continued on page 30)


Fig. 1 (above).— Dimensions of the new support and its position above the original support (shown dotted).

(Below right)—Side view of the modified viewer.

HAVING had considerable difficulty in obtaining a new 16in. metal tube (MW41-1) for one of the above receivers, and bearing in mind the very high cost of these near obsolete tubes, it was decided to try to modify the set to take a 17in. rectangular type.

Advantages

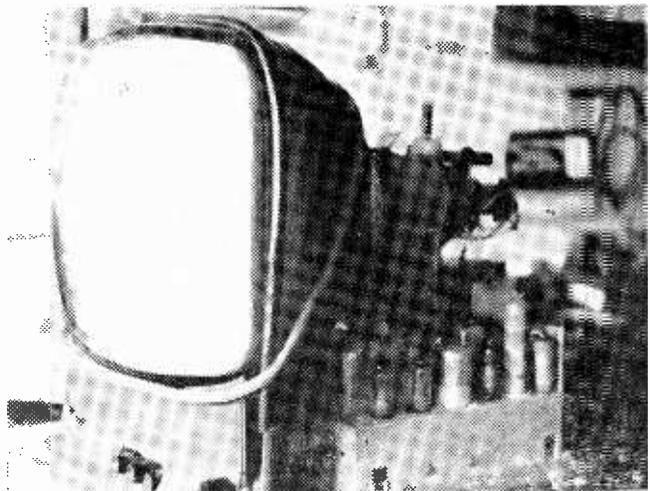The advantages to be gained were numerous; firstly, there are large quantities of rebuilt and re-conditioned 17in. tubes on the market and these cost less than the 16in. metal type. Secondly, an aluminised tube could be chosen to give a far brighter picture, and thirdly, the dangers of servicing



TV WITHOUT MAINS

METHODS OF OPERATING TV RECEIVERS IN REMOTE DISTRICTS

By F. G. Rayer

IN scattered country houses where no mains supply is available, private generating plants may be used for lighting. There is a considerable range, both new and ex-service, and although the usual plant does not have sufficient output for heating and similar appliances, it is usually possible to obtain current for a TV receiver or radio. Running a TV set in

demands are made on current, and are used for lighting only. With such plants, the TV set can be run by adding a converter. The low price of such plants, especially as "surplus," means that they are sometimes obtained mainly to provide current for a TV receiver. Large accumulators are not necessary with them. For example, a 24V bank can consist of four 6V or two 12V car-type batteries. For a 30V plant, five 6V accumulators could be used.

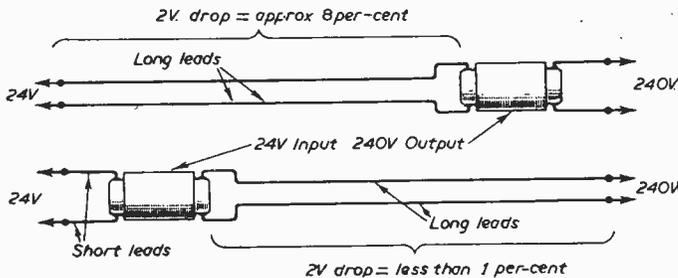


Fig. 1.—With low voltages, voltage drop is particularly serious.

this way will in such circumstances be the only means of obtaining TV reception, and the best method of securing satisfactory results then has to be considered. In practice, a few snags tend to arise, but these can usually be overcome fairly easily.

Type of Plant

Home generating equipment can be of several kinds. With large houses, a generator providing 200/250V and of quite large capacity may be used. With such plants, accumulator storage is not normally included, because of the size and expense this would entail. The plant therefore needs to be running whenever any electrical appliance is in use. An automatic self-starting circuit may be included, so that the plant is started when any switch is closed. With such plants, the TV receiver can be run in the same way as when house mains are available, but the exact voltage should be checked, and an A.C./D.C. type receiver used if the current is D.C. The precautions against interference mentioned later will also usually prove to be necessary.

Other large plants provide about 100V D.C., and are used with a bank of about 50 cells. These have the advantage that the generator does not need to be running when moderate current demands are being made, as for lighting, or the isolated use of lights during the night. But a means of stepping up the voltage will be needed to operate a 200/250V TV set, as with low voltage plants.

Low voltage plants usually provide about 24V to 30V so that the cost of accumulators is much less than with the 100V plant. They are only suitable for small houses, or where moderate

for a converter. 2A would be drawn from a 100V supply. This would also be within the capacity of such equipment. But with a low voltage plant, about 8A would be required at 24V, so it will probably be necessary to have the generator running when the TV is in use, despite the fact that accumulators are present. If this is not done, the voltage is likely to drop so that proper working of the receiver is impos-

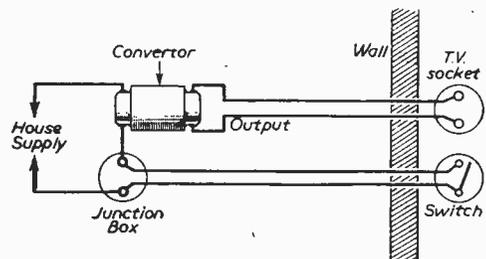


Fig. 2.—Connecting an input switch.

sible. With a bigger TV set, the consumption will be over 100W and the current required will then be even larger.

Planning

Thus, with a low voltage plant, it is wise to plan the installation on the assumption that the generator will need to be run when TV reception is required. This will, of course, also be necessary with plants having no accumulators.

The way in which the current increases as the voltage is reduced also means that regular, long

period running of a TV set from a 12V accumulator is not likely to prove satisfactory, unless some means of charging is available. Moderate use of a small receiver, or 12V portable, is feasible from a 12V accumulator maintained in good condition. In a few cases it may be convenient to charge this accumulator from a higher voltage, D.C. house supply, as explained later.

Voltage Drop

Fig. 1 shows the importance of voltage drop in a high current, low voltage circuit. Resistance

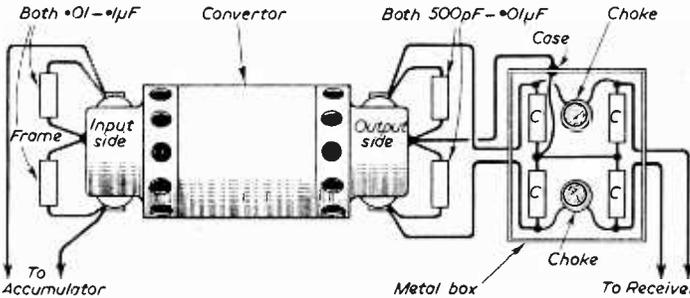


Fig. 3.—Wiring-in suppressor condensers and chokes.

between generator, accumulators and converter, must be kept as low as possible. With a 200V supply, a drop of 1V would be quite insignificant. With a 100V supply, it would constitute only 1 per cent. But with a 24V supply, it would be over 4 per cent. Furthermore, for a given wattage the current flowing increases. The voltage drop in the circuit with low voltage plants can thus become too large a percentage of the available voltage, unless care is taken. In some cases, the converter is designed to compensate to some extent for this, as with converters intended for 11V input from a 12V supply, or the receiver input tapping can be adjusted to suit. For example, if the converter is rated to provide 240V, on load, but the voltage is only perhaps 210V, due to a slightly reduced converter input voltage, then the receiver can be set as for 210V mains.

Unnecessary voltage drop will be avoided by using a reasonably short wiring run between accumulators and converter, and a stout conductor. For example, some 30ft. or so of 15A cable would usually introduce no particular difficulty with a 24V supply. The wiring between converter and receiver is less important, because the current is so much smaller.

Noise

The better type of plant, designed for house lighting, etc., is often well silenced. But the small, ex-service charging plants frequently use a small, air-cooled petrol engine, and can be rather noisy. This is important when it is remembered that the engine will most probably have to be kept running during periods of viewing.

An outside shed, separated from the house, will thus be a good place to house the plant. If the building is solidly constructed, and perhaps at the other side of the house to the room where

the TV will be installed, this will help reduce noise. It may be necessary to replace small, mushroom exhaust fittings by means of a proper silencer. A method sometimes used is to fit a long exhaust pipe discharging into a pit dug in the ground, and covered with stones, or earth supported on stout planks, etc., with small gaps for the escape of exhaust gases. There is, however, a certain amount of noise from the engine and generator themselves, and this can become very annoying unless some care is taken when deciding where the plant shall be situated.

Converter Noise

The converter will also produce some noise when running, so that it should not be near the receiver. It may be possible to place the converter in an adjoining room or passage, where the noise will not be troublesome while viewing. A stout containing case, cover or box, lined with sound-absorbing material, will help to keep the noise down. Direct sound transmission through the floor can be reduced by standing the equipment on sponge rubber blocks, and can be worth while with wooden floors.

In some circumstances the converter may be housed with the generating plant. Sufficient ventilation must always be allowed to avoid overheating.

With a little care, noise from the converter need not be troublesome. But if this is entirely overlooked, and the unit perhaps placed behind the set, or in direct contact with a fragile wooden box, the sound when it is running will become a nuisance.

Converter Wiring

The converter is only switched on when the receiver is needed, so that a switch must be included in the input circuit. An extension lead may be necessary to allow this switch to be situated at a convenient spot as shown in Fig. 2, but wiring should be arranged to avoid long connections, or excessive voltage drop can arise.

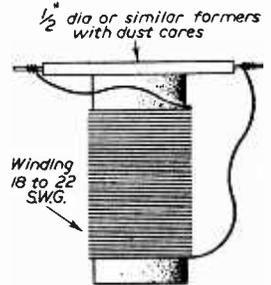



Fig. 4.—Small suppressor chokes.

The converter will generally be an ex-service unit, and these are quite inexpensive. Its input voltage should suit the supply available. The output voltage must suit the receiver, or the receiver must have an input tapping which can be adjusted to match the converter output. The converter must also have a wattage rating at least equal to that of the receiver. The receiver consumption will be indicated in the operating instructions, or elsewhere and should be known when buying the converter.

(To be continued)

A BAND V GEN

THIS INSTRUMENT HAS
CONSTRUCTION AND

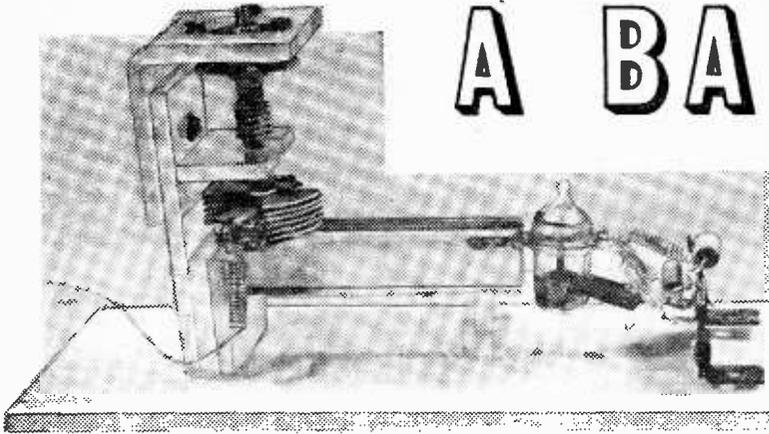

THE signal generator described in this article will enable testing of apparatus for Band V to be carried out in the absence of the BBC experimental television transmissions. The generator is tunable and has provision for amplitude modulation of the output—a great convenience for alignment purposes.

Components

There is at present a good deal of difficulty in obtaining special U.H.F. components at any price—let alone at a reasonable price. This applies with equal force to valves; one very well-known firm informed the writer on enquiry that at present only “experimental” quantities were available, and those only to manufacturing firms.

However, by using the “surplus” market and some artifices, an apparatus has been evolved which is easily made from readily obtainable parts, and which has a good performance. The moderately experienced will find little difficulty in constructing it, and it is thought that every satisfaction will be obtained.

The Circuit (Fig. 1)

The U.H.F. oscillator consists of a single-ended tuned-line circuit, the cathode being the common

LIST OF COMPONENTS

- 1 Acorn valve type 955.
- 1 SP61 (CV1065) or EF91.
- 1 Butterfly 25pF.
- 1 Muirhead slow-motion drive.
- 1 Flexible coupler (insulated).
- 1 Small A.F. transformer.
- 1 Miniature mains Transformer (output 250V H.W., 30mA, 6.3V at 1 amp.).
- 1 Metal rectifier 250V 30mA.
- 1 Valveholder B8A.
- 1 Valveholder MO or B7G as required.
- 1 25k TV type pot (wire-wound).
- 1 1k TV type pot (wire-wound).
- 1 coaxial socket.

Aluminium sheet, brass curtain-rail (channel type), Perspex sheet, quantity of Tufnol rod $\frac{1}{16}$ in. diameter, self-tapping screws, $\frac{1}{16}$ in. diameter by $\frac{1}{2}$ in., 1 oz. chloroform.

Conventional circuit components as given in the circuit diagram.

of a phase-shift audio bridge type, and this is used to effect grid-modulation of the oscillator. Output is obtained by means of a loop, coupled loosely to the tuned lines, the output impedance being 80 ohms—suitable for feeding into a coaxial lead. This should be terminated permanently in an 80 ohm resistor to avoid reflections (which otherwise might prevent the oscillator from working, if fed back along the cable and appearing at the coupling loop in anti-phase).

The circuitry is thus simple in the extreme, and the important details are the constructional ones.

Discussion of Circuit

As is well known, the Q of tuned lines is highest when one quarter-wavelength long. However, experiment showed that not only are the Lecher lines unmanageably short when working with short-circuited quarter-wavelength lines but, because much of the capacitance and inductance is within the valve itself, an actual improvement in Q is obtained by using half-wavelength lines. Any improvement in Q is valuable because it helps in stability of frequency and also allows the valve to operate at a higher frequency. Tuning by variable capacitor is also possible, since by putting this component at the opposite end of the lines from the valve it is at a high R.F. voltage position; the anode and grid are at the other high-voltage position. Besides, the use of a variable short-circuit is tricky to arrange, and although some success was had by using a “slide” incorporating small carbon brushes, the re-setting accuracy was low.

To obtain mechanical rigidity in the Lecher lines, sections of brass curtain-rail have been used, each 7.0 cm. in length. These, silver plated and

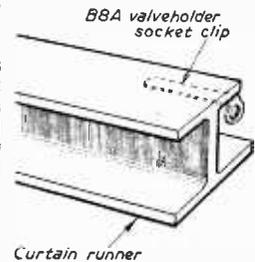


Fig. 2.—Fitting the valveholder sockets to the Lecher lines.

SIGNAL GENERATOR


BEEEN SPECIALLY DESIGNED FOR EASE OF STABILITY IN OPERATION By R. B. Archer

set close together, afford a pair of lines of good Q and manageable dimensions.

For the tuning capacitor a "butterfly" was selected. This component has the advantage (over a normal variable capacitor) of having no sliding contacts and of being symmetrical electrically. The item, as bought, has to be modified to be useful in this circuit, as it is mounted directly on the end of the Lecher lines. This will present no difficulty, given reasonable mechanical skill.

Valve Supplies

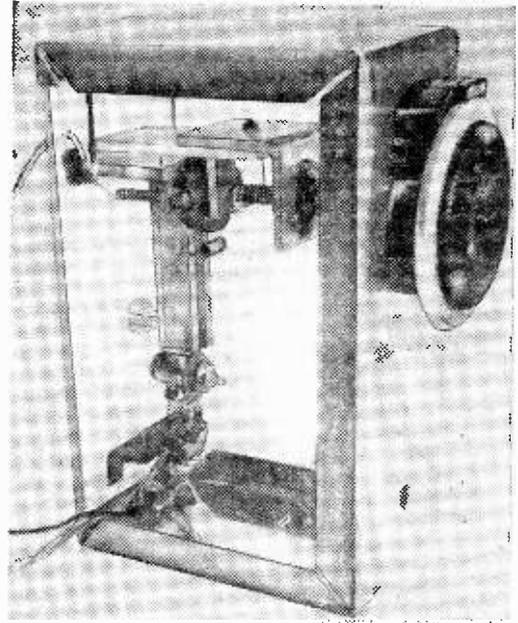The D.C. connections to anode and grid lines are made at about the mid-point of the lines. This ensures that valve supplies are made at points where the R.F. voltage is near zero, and thus capacitance effects are not introduced into the tuned circuit. The fact that the oscillator is tunable means that the point of zero R.F. voltage is not fixed, but varies with the tuning.



The oscillator works with the cathode choked and, because the heater-cathode capacitance represents only a small impedance at the frequencies covered, the heater is also choked so as to remain at the same R.F. potential as the cathode. The inclusion of chokes in these leads also has

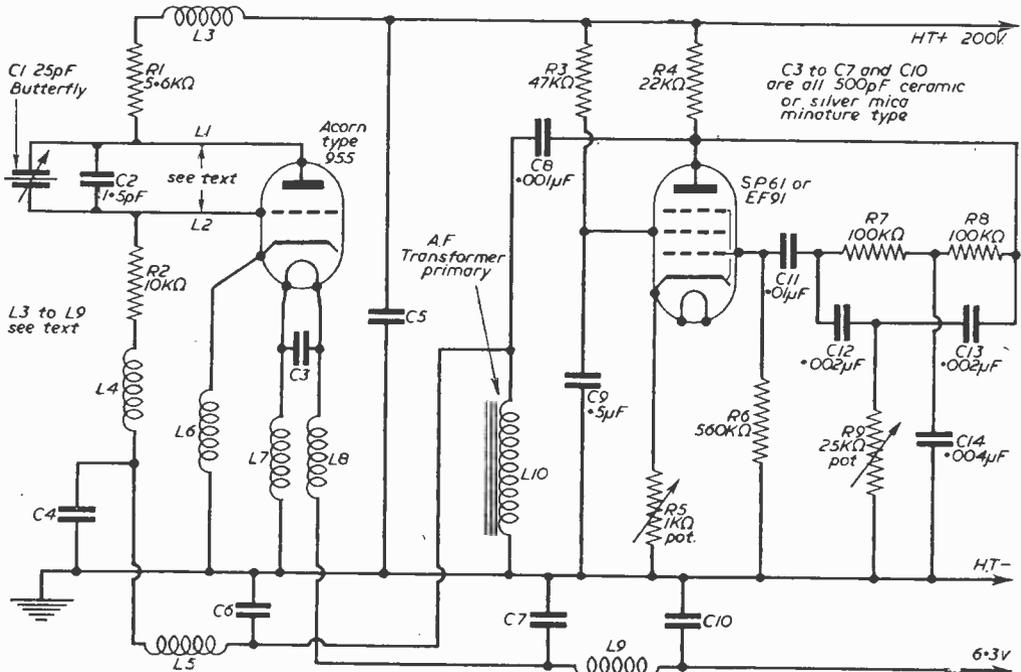


Fig. 1.—The circuit diagram.

the valuable property that the frequency of operation is less affected by capacitances outside the valve and tuned circuit; hence calibration is less upset by valve replacement.

Grid modulation by the generated tone was chosen because it causes noticeably less frequency-modulation in this circuit than does anode modulation. A change of grid voltage from -1 volt to -2 volts causes the frequency to shift by only 4kc/s at 650Mc/s . and this is nearly negligible. Provision is made for altering not only the pitch of the note (by R9) but also (R5) the intensity (voltage). This enables a considerable voltage

The acorn valve was chosen as being easily available and not too difficult to mount. The NR88 has also been used. This is equivalent to the EC52, and it will oscillate up to at least 750Mc/s in this circuit. The Lecher lines have to be cut somewhat shorter however. The acorn is recommended in preference.

The essential constructional details concern the R.F. oscillator, because here the layout is much more critical than is the remainder of the circuit. However, the situation is not unlike that existing when coils and condensers have to be made at home; provided essential dimensions are adhered to approximately there is no difficulty in calibration, and the required waveband is easy to achieve.

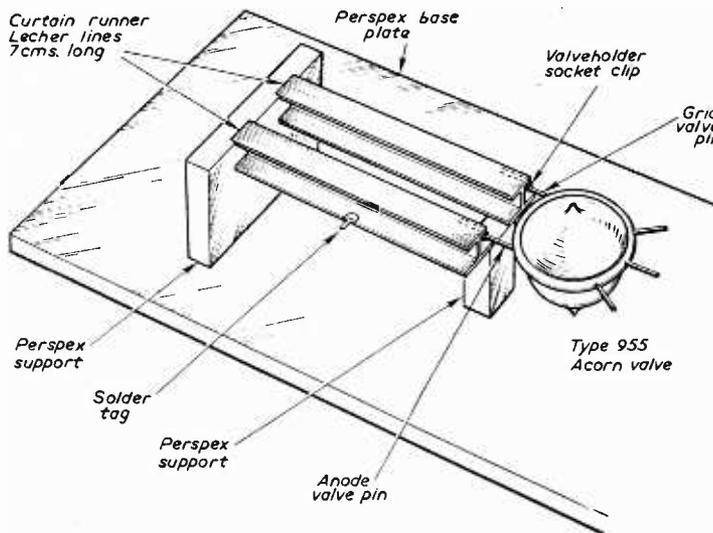


Fig. 3.—Mounting the Lecher lines and valve on the Perspex baseplate.

to be generated at will, and in such a case the frequency deviation of the oscillator is a good deal more; the exact amount is not known and hardly matters since it is only used for alignment purposes and has little entertainment value.

Audio Oscillator

The phase shift oscillator is of conventional design, and requires little comment. The audio tone generated can be varied from about 800c/s to about $1,200\text{c/s}$. Negative feedback applied by means of R5 helps in securing purity of waveform; as the voltage generated is increased by reducing R5, the tone becomes much more distorted by the inclusion of harmonics. This is caused by running the valve outside the linear part of its characteristic curve.

The writer's final version of the signal generator, which is described in this article, is capable of supplying 25mA of R.F. current into a dipole at 650Mc/s . feeding at 80 ohms impedance. The frequency range is a little below 550Mc/s to a little over 750Mc/s , and thus the BBC is covered with plenty of room to spare. An exactly similar design, using longer Lecher lines, can be constructed to cover Band IV, and so the circuit has a wide range of utility.

The R.F. Oscillator

Two pieces of brass curtain-runner are carefully cleaned with metal polish and then in hot detergent solution. After rinsing well in cold water (using tongs or tweezers when handling) they are silver-plated reasonably heavily and are cut down to exactly 7.0 cm. each in length. Burred edges are smoothed with a file.

Silver Plating

The art of plating has an extensive literature, but experimenters need have no qualms about the simple method which can be used for silvering the brass Lecher lines. There is only one solution required and it is made

as follows. The chemicals needed are:

2 grams silver nitrate.

5 grams potassium (or sodium) cyanide.

Dissolve the silver nitrate in a teacupful of warm water, and the cyanide in a glass bottle containing about the same amount of water. Add the cyanide solution drop by drop to the silver nitrate; a whitish precipitate forms which redissolves on adding more cyanide. Go on adding drops of cyanide solution until the solution is just clear again.

Then, because the cyanide is dangerously poisonous, pour the rest of it away where it can do no harm. The silver cyanide plating solution is not quite as dangerous, but it should be labelled clearly and kept out of the reach of children. It should never on any account be used anywhere near foodstuffs or where food is prepared.

Plating the Lecher Lines

To plate the Lecher lines, they should first be polished with metal polish and then scrubbed in hot detergent solution. After rinsing thoroughly in cold water, using tongs or tweezers to handle them (never the fingers), a wire is attached lightly to one end and the Lecher line to be plated is immersed in the plating solution.

To a small piece of scrap silver, a second wire is attached, and this piece of silver is also immersed in the solution, not too close to the Lecher line (about 2in. to 3in. separation will do). The wire from the Lecher line is connected to the negative terminal of a 1.5V battery, and the wire from the scrap of silver to the positive terminal.

Plating begins at once and is clearly visible. The solution is stirred while the process progresses, and if discoloration or darkening appears on the Lecher line the separation of the silver and the line should be increased or the solution diluted with water. About half-an-hour will be needed to give a sufficient coating.


When the plating is finished, a rinse under the tap is needed, after which the Lecher line can be dried and is ready for use.

If desired (and a large enough container is available) the brass curtain-rail can be plated in one operation before cutting to size. In any case it must be emphasised that success depends entirely on absolute cleanliness; the touch of even a well-washed finger will deposit enough grease to spoil the plating at the point of contact.

Photographers who have a bottle of well-used (or better still, exhausted) fixing solution can use it instead of the bath described above. A silver anode is not needed—a carbon rod can be used instead.

Valve Pins

The B8A valveholder is dismantled to obtain the sockets. These are used because they form an edge-grip for valve pins, but other types of socket which can grip a valve pin very close to the valve glass itself can be used. Two of these are required. One is soldered to the underside of the small flange of each curtain-runner, as shown in the diagram (Fig. 2). The soldering has to be done in such a way that eventually the

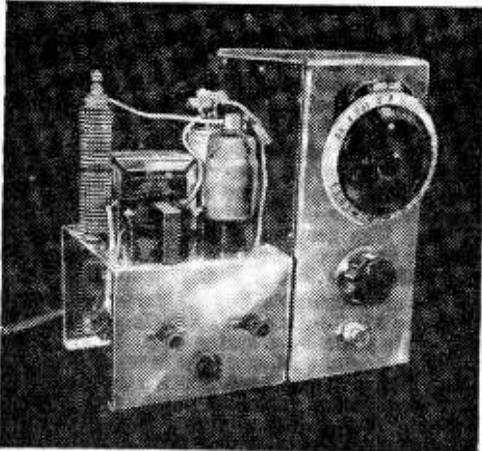

The completed generator with attached power-pack.

valve pins will lie parallel to the Lecher lines—the pieces of curtain-runner—and both clips are soldered on to the same "hand" side. For soldering to the brass rail either a $\frac{1}{2}$ lb. soldering iron or a small blowlamp will be needed since the brass itself has a high thermal capacity

Mounting Plate

Small soldering tags are now attached to some convenient part halfway along each Lecher line. The next operation is to prepare a mounting plate of Perspex sheet, and Perspex supports for the Lecher lines themselves. Fig. 3 shows how this may be done. The supports themselves are cemented to the baseplate by means of a few drops of chloroform. It should be noted that a chloroform-cemented junction takes several hours to dry hard. The smaller flange of each

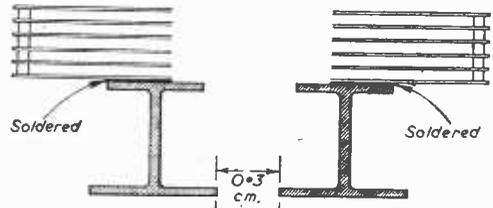


Fig. 4.—The "butterfly" stator plates are soldered to the Lecher lines.

Lecher line is uppermost, and it is arranged so that the larger flanges, at the bottom, are 0.3 cm. apart all along their length. The mounting must be very rigid, and to this end the L-channels are let into the Perspex supports; the latter are afterwards heated gently and squeezed between hot pliers so as to make a tight fit.

Capacitor

The next process is to fit the tuning capacitor. For this purpose the "butterfly" is completely dismantled, and a pair of stator plates are soldered direct to the ends of the Lecher lines (Fig. 4). Care must be taken that the stators are quite flat, and parallel to the baseplate when mounted.

The next procedure is to remove one set of rotors from the shaft of the butterfly: this gives a spindle of ceramic material with a bearing at each end. One bearing is used as the "top" fixing, but since the other bearing cannot be used it is removed and a suitable hole is cut in a Perspex sheet: this is used as an intermediate bearing to locate the spindle positively. A suitable mount is cut from Perspex sheet, the top and intermediate bearings fitted, and the whole is adjusted so that the rotor can mesh with the stator plates without touching either. The arrangement can be seen in the illustrations. Eventually a flexible coupler will be used to connect this spindle with the slow-motion drive. If it is required to have a positive stop to movement of the rotor at maximum or minimum, this can be devised at this stage.

Case

The containing (and screening) box should now be constructed. This is made in two interlocking halves from aluminium sheet. By this means, the mechanical drive, the coupling loop, and the coaxial output can be attached to the oscillator baseplate and all adjustments carried out with the oscillator working, before finally completing the screening.

(To be continued)

CORRESPONDENCE

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

SMALLER TUBES

SIR.—Much has appeared in the daily press lately about the wonderful new development in picture tubes, resulting in much smaller sets. Surely this is not so wonderful. Did we not see many years ago short neck tubes. I believe by Cossor, and these were surely developments of the radar equipment used in the Services. I also remember a French development, I think it was, which gave a remarkably short tube. However, the point of this letter is not so much on whether or not the short tube is a modern development but whether the development is in the right direction. Is the cathode-ray tube, in fact, the correct approach to the television problem? At the moment it is true, there does not appear to be an alternative, but surely the ultimate in the domestic reproduction of a picture will dispense with this bulky and dangerous device and give us a projection unit which will give a really large picture, on the wall or a screen, from a very simple box. Have inventors forsaken this line of approach?—G. BUCKMASTER (N.W.).

TRANSISTOR TV

SIR.—I read with interest the series a short while ago on the use of transistors in a television receiver, and note that there are still no components for this type of set. The articles did not mention the question of heat, and as the transistor seems notorious for its temperature effects, it does not seem that a transistorised TV set will be of much use. It has been reported that the Americans have produced an all-transistor set and it would be interesting if details could be given of where, if at all, their technique differs from that given by your correspondent.—G. R. BRASING (Norwich).

A STRANGE FAULT

SIR.—I have seen from time to time in your pages details of faults and troubles experienced by your readers and in many cases the cures which have proved satisfactory.

Perhaps the following experience will interest other experimenters. I have a home-made TV set, incorporating many commercial products originally intended for other receivers, but have managed satisfactorily to combine them in a set prepared from makers' service sheets and circuits in your pages. It has worked very well for a considerable period, but recently has commenced to become erratic. The picture breaks up exactly in the same manner as when the line hold control is incorrectly set—verticals jump in sections, etc. After trying a few times to obtain a better adjustment I got fed up and left it. It righted itself in half an hour or so, and has worked in this way

now for some time. The picture breaks up, rights itself and breaks without any definite time period, and always ends up by righting itself for the rest of the evening. This does not happen every night, but once or twice a week. Can it be due to mains fluctuations, which I thought were now so controlled that they gave a constant output?—R. Cox (Edgware).

AERIAL ARRAYS

SIR.—We are told that the BBC are probably going to use Bands IV or V for future transmissions to avoid crowding on the bands. In

certain parts of the country the viewer is within range of perhaps two stations in Band I and two in Band III. If extra bands are added what will the aerial array become? Will he have to use an aerial for each band, each station, or what? Is it not time

that some form of pick up device were introduced which would give a good signal on anything from Band I to Band V, or does the receiver technique need revising so that a good signal can be obtained with a modest or inefficient aerial system, to avoid the unsightly arrays which we may at present foresee.—G. F. RIDGWAY (Rugby).

SPECIAL NOTE

Will readers please note that we are unable to supply Service Sheets or Circuits of ex-government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

FROM METAL TO GLASS

(Continued from page 23)

is made as shown in Fig. 1 and lined with sponge rubber. This is bolted to the original rest by means of the two existing bolts. Next, the tube clamp is shortened by about 2in. and a piece of sleeving threaded on.

As the 17in. tube bulb is considerably longer than the 16in. type, two measures have to be taken: the deflection coil securing bolts are loosened and the coils pushed back as far as they will go. The Perspex mask must be removed from the inside of the cabinet and mounted on the outside with four chrome headed screws.

It was mentioned earlier that the external coating of the 17in. tube must be earthed and this is most easily done by a spring clip. Mount it on the H.T. smoothing electrolytic fixing screw. This coating acts with the inner coating to provide an EHT smoothing capacitor, and the original smoothing capacitor(s) can be removed, a lead now going directly from the EY51 EHT rectifier to the top cap of the tube. It will be necessary to change the existing top cap connector.

Finally, a rubber dust-sealing band should be slipped over the tube (as shown in the illustrations) and sprung in position between the tube face and mask when the chassis is bolted in the cabinet.


REGUNNED TV TUBES

NEW REDUCED PRICES!

And now 12 months Guarantee!

12in.....£6	17in.....£8. 10. 0
14in.....£7	21in.....£10. 10. 0
15in.....£7. 10. 0	Carr. and Insur. 10/-

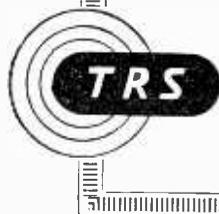All tubes Rebuilt with new Heater, Cathode and Gun Assembly—reconditioned virtually as new! Full 12 months' unconditional Guarantee. As used by our own Service Dept. Comprehensive stocks—quick delivery. 10/- part exchange allowance on your old tube.



TRANSISTOR 'ONE-WATT' AMPL.

6 v. Battery Operated
G.E.C. Push-Pull 4 Transistor circuit giving full 1 watt output using standard 3 ohm speaker. Good sensitivity (approx. 10 mV.) and improved frequency response. Neg. feedback, volume and tone controls. Chassis size 6 1/2 in. x 3 1/2 in. x 1 1/2 in. Current consumption 10 mA. quiescent—250 mA. at 1 watt.
2 matched GEC 6ET15 Transistors ... 42/- pr.
2 GEC 6ET15 Transistors ... 21/- pr.
Driver Trans. 8/6
Output Trans. (for 3 ohms) ... 10/6
Complete kit of parts incl. speaker, etc., less speaker, only **99/6** P. & P. 2/6
Recommended 7 1/2 in. 4 in. speaker 18/6. P. & P. 1/6.

STAAR 45 r.p.m. SINGLE RECORD PLAYER
6 v. Battery operated. Lightweight Xtd Pickup with Twin Sapphire stylus (one spare). Auto stop. Mounting 7 1/2 in. x 6 in. Attractive Continental styling. Ideal companion unit to above Transistor Amplifier.
RECOMMENDED BARGAIN 92/6 P. & P. 3/6
only
Suitable cabinet to house above 2 units 22/6. P. & P. 2/6.

RECORD PLAYER CABINETS

Contemporary styled, revivite covered cabinet in two-tone fawn and brown, or mottled red with white polka dot. Size 14 1/2 x 13 1/2 x 8 1/2 in., fitted with all accessories, including baffle board and anodised metal feet. Space available for all modern amplifiers and autochangers, etc. Uncut record player mounting board 14 x 13 in. supplied.
£33.0. Carr. and Ins. 3/6.



2-valve AMPLIFIER Mk. 2
Latest developed circuit giving a higher fidelity response and greater output (2-3 watts) using twin stage valve EK192 and hex. feedback Tone Control. Complete with knobs wired and tested with 6in. Speaker, etc., ready to fit in above cabinet. Only **£3.19.6.** Carr. 2/6.

RECORD PLAYER BARGAINS ALL NEW 4-SPEED MODELS

SINGLE PLAYERS BSR (TU9), £4.10.0.
COLLARO (4/564), 6 kns. GARRARD (48P), £7.10.0, carr. 3/6. GARRARD (TA Mk. 11), £8.5.0, carr. 3/6.
AUTOCHANGERS BSR (UA8), £6.10.6.
BSR (UA12) with stereo/monaural pln. 10 kns.
COLLARO CONQUEST, £7.10.6. GARRARD RC121/D/Mk. 11. Plug-in GC8 Monaural head, stereo adapted. 10 kns., GARRARD GCS.10 stereo head £2 extra. Carr. 4/6.
FINEST SELECTION AVAILABLE ALL BRAND NEW & GUARANTEED

Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

REDUCED VALVES

1R5, 1T4 7/6	DP96 9/-	EP80 9/6	PC183 12/6
185 7/6	DK96 9/-	EP86 13/6	PC183 12/6
384, 3V4 8/-	DL96 9/-	EP91 8/6	PL81 12/3
6K7 9/6	EAC80 9/6	EL41 10/6	PL82 9/6
6K7 5/6	ER341 9/6	EL84 9/6	PL83 11/6
6K8 8/6	EX3 5/6	EX3 9/6	PS80 7/6
6Q7 8/6	EX34 1/6	EV51 10/-	PS81 9/6
6N7 8/6	EPF80 11/6	EV86 10/-	PS82 7/6
6V6 7/6	EPF82 11/6	EZ80 7/6	PS83 10/6
6X3 7/6	ECF42 10/6	EZ81 7/6	UT25 12/6
7C5 9/-	ECF41 10/6	MC14 8/6	UT42 10/6
7Y4 8/6	ECF40 10/6	PC84 10/6	UT41 10/6
DAP96 9/-	ECF42 11/6	PCF80 10/6	UT41 10/6

SPECIAL PRICE PER SET
1R5, 1T4, 185 or 384, or 3V4 ... 27/6
DK96, DP96, DAP96, DL96 ... 35/-
6K8, 6K7, 6Q7, 6V6, 3Z4 or 6X5 ... 35/-

VOLUME CONTROLS

10,000 ohms—2 Megohms. All long spindles. Morazite Midget type. 1 1/2 in. diameter. Gear 1 gear. Log. or Lin. Ratios. Less Sw. 3/-. D.P. Sw. 4/6. Twin Ganged controls, 1 meg., 1 meg., 1 meg., less Sw. 8/6 ea.

ELECTROLYTICS ALL TYPES NEW STOCK


Tubular Wire Ends Can Types, Clips 3d. ea.
25/25 v., 50/12 v. 1/4 5/600 v. Dub. 3/-
30/50 v., 4/500 v. 2/- 4+8 450 v. T.C.C. 4/6
8/450 v. T.C.C. 2/3 32+32 275 v. Hunts 4/-
8+16/450 v. T.C.C. 5/- 32+32 450 v. T.C.C. 6/6
16/450 v. B.E.C. 3/6 32+32 450 v. T.C.C. 6/6
16+16/450 v. T.C.C. 5/6 30 350 v. T.C.C. 6/6
32/350 v. B.E.C. 4/- 30+100/350 v. B.E.C. 11/6
50+30/350 v. B.E.C. 6/6 30+250/275 v. B.E.C. 12/6
32+32/350 v. B.E.C. 6/6 100+200/275 v. B.E.C. 12/6

SEMI-REGL. RECTIFIERS. E.H.T. Type

Back Voltages. K3/25 2 kV., 5/-; K3/10 32 kV., 6/6; K3/45 3.6 kV., 7/6; K3/50 4 kV., 7/9; K3/100 8 kV., 13/6. **MAINS TYPE.**—RM1, 125 v. 60 mA., 4/8; RM2 125 v. 100 mA., 5/8; RM3 125 v. 120 mA., 7/8; RM4 250 v. 250 mA., 10/-; RM4B type 270 mA., 17/8; RM5, 250 v. 300 mA., 21/6.
TYGAL FRET.—Expanded Bronze anodised metal 8 x 8 in., 2/3; 12 x 12 in., 3/-; 12 x 12 in., 4/6; 12 x 15 in., 6/-; 24 x 12 in., 9/-, etc.
MURPHY PATENT 12 x 12 in., 2/-; 12 x 15 in., 3/-; 12 x 24 in., 4/-, etc.
SPEAKERS P.M. 3 ohm 2 1/2 in. Elec. 16/8. 3 1/2 in. Goodman 15/8. 5 in. R. & A. 17/8. 6 in. Celestion 18/8. 7 1/2 in. Go. G. 19/8. 8 in. Rola 70/-, 8 in. Special Cone G. 19/8. 10 in. R. & A. 27/-

2 Waveband Car Radio Kit

12 v. operation Med. & Long Waves
Development of the famous Brimar Hybrid vibratorless Car Radio Circuit. Latest type low voltage valves and Power Transistor. R.F. stage and permeability pre-aligned Cyclon Tuner Unit provide extremely good sensitivity and signal/noise ratio. Printed circuit and 7 in. x 4 in. speaker self-contained in neat Metal Cabinet 8 in. x 7 in. x 2 1/2 in. with attractive dial. Speaker and Power Transistor stage mounted separately, approx 8 in. x 5 in. x 2 in.
RECOMMENDED BUY
Complete Kit **Bargain Price £12. 19. 6**
P. & P. 3/6.
Instruction Booklet and Parts List now available 3/6 post free.

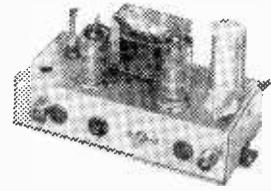

BAND 3 TV CONVERTER

All channels 7-13 (180-205 Mc/s).
Mk. 2 Model. Latest cascade circuit using EC704 and EP80 valves, 15db gain over standard circuit. Built-in Power Supply 200-250 v. A.C. Size 6 1/2 in. x 3 in. x 4 in. Simple to fit—only external plug-in connections. Wired and aligned ready to use. Only 29/6. p. & n. 2/6.
Recommended addition—Band 1/Band III channe-over Sw. and BB7 Aerial Socket fitted and wired. 9/- extra.
Band 3 Aerials. Single Dipole with 4 yds. cable, 13 B, 5 Element Beam, 25/-, 5 Element, 32/6, etc. B1-B3 Cross-over Units, 7/6.

PERDIO POCKET TRANSISTOR "6"

Medium and Long Wave Midget Stretched Personal Radio. Printed circuit, 6 transistors and 1 crystal diode, and stage by stage instruction manual. Internal ferrite aerial. Push pull output.
ONLY
Complete Kit incl. **£9.19.6** P. & P. 2/6
Cabinet and 2 1/2 in. Speaker.

COAX 80 OHM CABLE.

Stand 1 1/2 in. diam. Low Loss Semi-Air Spaced Aerialial.
SPECIAL REDUCED PRICES
20 yds. 12/6. p. & p. 1/6; 60 yds. 32/6. p. & p. 2/-; 40 yds. 22/6. p. & p. 2/6; All other lengths 8d. per yard.
Coax Plugs 1/-, Sockets 1/-, Couplers 1/3, Cable End Sockets 1/6, Outlet Boxes 4/6.

G.R.T. Heater

Isolation Transformers
New Improved types—mains prim. 200/250 v. tapped.
All Isolation Transformers now supplied with alternative no heat plus 25%, and plus 50% heat taps, at no extra charge.
2 v. 2A type 12/6 (P. & P. 1/6)
6.3 v. 3A .. 12/6 ..
11.5 v. 3A .. 12/6 ..
13 v. 3A .. 12/6 ..
Other voltages available at same prices.
Small size and low terminated for easy fitting.

NOW! The TOURIST Portable

3 valve, Med. & L.W., 1 1/2 watt battery. Size only 5 in. x 5 1/2 in. Weight 3 1/2 lb. with battery. Complete receiver component kit 57/6. p. & p. 1/6. Set 4 m. inductance valves (96 series) 25/-, p. & p. 5/4. 5 in. Speaker & Output Trans. 21/-, p. & p. 1/6. Cabinet, Dial and Knobs, etc. ... 22/6. p. & p. 2/-
Complete kit—BARGAIN—only £6.10.0. post free.
Latest superb circuitry, delayed AVC and A.F. Neg. feedback.
Terrific performance—
Remarkable size—
Staggering value
Send for Booklet NOW! 1/6 post free.
As featured by Radio Constructor.

MAINS TRANSFORMER WINDING CAPACITY AVAILABLE PROTOTYPES & SMALL RUNS



Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 1 1/2 7d., 1 1/2, 1 1/2, 1 1/2, 5d., 2/-, 10 1/2, 2/9. Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.
RADIO COMPONENT SPECIALISTS (Est. 1946)
70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)
50 yards Thornton Heath Station.
Buses: 130A, 133, 159, 166 and 190



Now Open! LASKY'S New Showrooms

207 EDGWARE ROAD, W.2.

The largest stocks of leading makes of Electronic, Radio & TV Components, Units, Tape Recorders, Constructor Kits, Cabinets, Cases, etc., in London. Everything for Constructors and high fidelity enthusiasts.

NOW READY | **THE FINEST COMPONENTS CATALOGUE**
 ever produced for the "ham" or service man. **OVER 100 PAGES.** Post size 8½" x 5½", with hundreds of illustrations, and our prices will **2/-** Post save you pounds. Send for your copy now! **6d.**



207 EDGWARE ROAD, W.2. | **42 TOTTENHAM COURT RD., W.1.**
 Few yards from Praed Street. | Nearest Station: Goodge Street.
 LAD 4075 and CUN 1979. | MUSEum 2605.

Both addresses open all day Saturday. Close 1 p.m. Thursday.
 Please address Mail Orders and enquiries to:
 Lasky's (Harrow Rd.) Ltd., 207 Edgware Road, London. W.2.

It pays to go—
to **VIDIO**

For value in Rebuilt Cathode Ray Tubes try Vidio. Each tube fully Guaranteed for twelve months and fitted with a **BRAND NEW** electron Gun Unit.

Free Delivery in the U.K. with an immediate, off-the-shelf service. Trade enquiries invited.

Write direct to the
VIDIO REPLACEMENT COMPANY

(They're Trade Association Approved)

Hales Street,
Deptford High Street,
London, S.E.8.

Tel.: Tideway 4506.



NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING...

ANNOUNCING—after years of successful operating in other countries—the latest system in home training in electronics introduced by a new British training organisation. **AT LAST**—a simple way of learning —by *practical* means—the 'how and why' of electronics with the minimum of theory and *no mathematics!* **YOU LEARN WHILST BUILDING** actual equipment with the components and parts which we send you —and you really have fun whilst learning! **And afterwards**—you have a first rate piece of home equipment plus the knowledge of how it works and how it can be serviced. **THIS NEW SYSTEM** brings an exciting new opportunity and is very moderate in cost. Post the coupon now *without any obligation* for full details.



LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!

No Mathematics!



To: **RADIOSTRUCTOR** (Dept G29)
 46 Market Place, Reading, Berks.
 Please send brochure without obligation to:

Name


Address

(807) 10-59

RADIOSTRUCTOR
 BRITAIN'S LEADING ELECTRONIC TRAINING ORGANISATION

TELEVISION IN THE MOUNTAINS

A DESCRIPTION OF A SWISS RELAY STATION

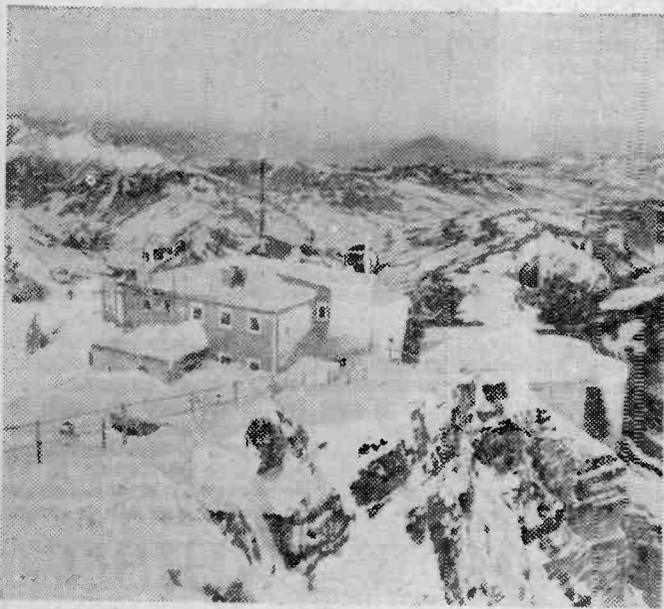

Above—View of the transmitter with the fantastic panorama of mountains.

Below, right—The transmitter station towers on the peak of the Santis mountain in Switzerland, like some space-age fortification.

AS in the British Isles, television has become a vital part of everyday life in most European countries. Oddly shaped aerials, often much more complicated than those seen in this country, can be seen on many rooftops in Switzerland, and viewers today switch on their television sets with the nonchalance of switching on the electric light.

Obstacle


Switzerland has its own particular problems where transmission signals at UHF are required. The range of signals at high frequencies is virtually the "optical" range and the towering peaks of the Swiss mountains are a natural obstacle which make the relaying of television signals extremely difficult. Here, then, the only method open to the engineers was to transmit the signal from moun-

tain top to mountain top. Today, modern aerials and masts now stand in the mountains by the side of that comfort to travellers, the ancient Calvary.

The latest television relay station to be built in Switzerland is at the summit of the mountain Santis which is some 2,500m high. The station covers the north-eastern half of Switzerland as well as Liechtenstein and certain parts of southern Germany. Not only is the station equipped for television, but there is also provision for high frequency radio and telephone signals.

Construction

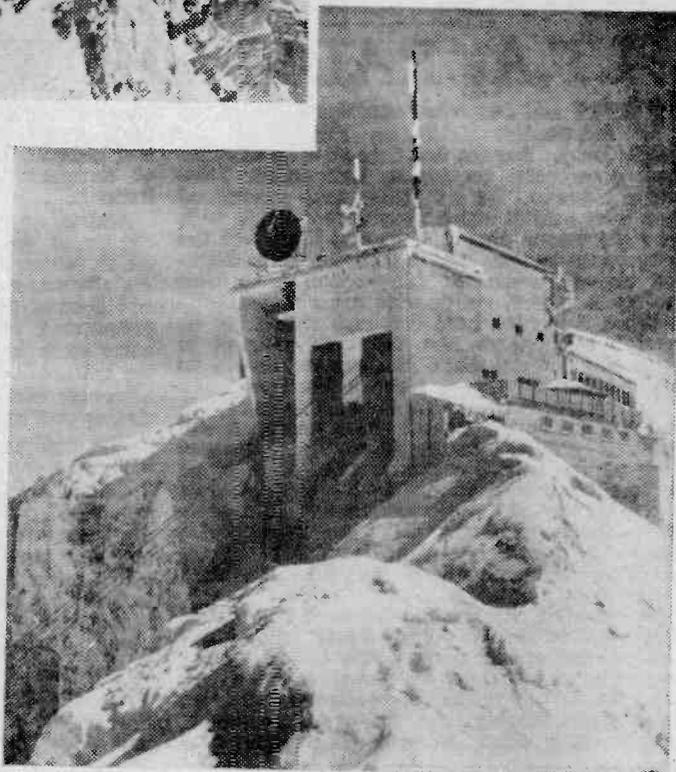The Santis transmitter is built at one of the highest levels in Europe and is a good example of




how the problems confronting transmission in mountainous areas can be tackled. The station is reached by funicular railway. The buildings, five stories high, are painted white and blend with the snow masses surrounding them, thus making the station quite unobtrusive.

Santis is exposed to the elements and the engineers at the station report that snowfalls and storms can reach quite unbelievable degrees of severity. These hazards called for the use of special methods when the buildings were constructed. The walls are built with double thickness; the outer layer is reinforced concrete and the inside walls are brick. The hollow part between the walls is filled with granulated cork for thermal insulation, a special method being used to protect the cork from damp and moisture.

The constructional work began early in 1956, the new transmitter was built on to another building which houses the machinery for the funicular railway. More than 1,500 cu. ft. of solid rock had to be cleared with explosive before the work could begin. As one would expect, the mixing and use of concrete proved to be exceptionally difficult as not one of the twelve months in the year is without frost. Many other problems confronted the builders such as transportation of materials, oil, water and other supplies, but eventually all were overcome. The buildings were completed in 1958 and after the equipment had been installed, the station was soon fully operational.

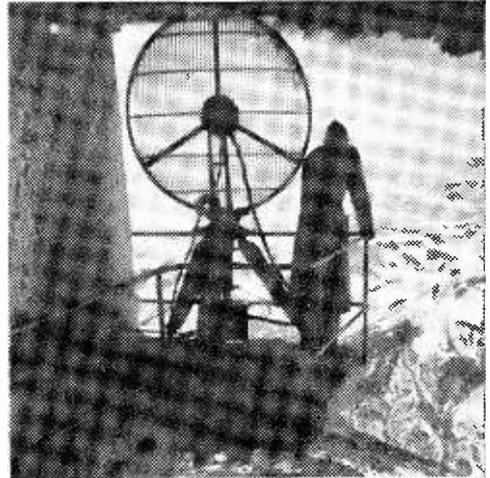Besides the actual transmitter, the buildings house an emergency electricity unit, worked by diesel engines, store rooms, engineering shops and



This view shows a portable "mirror" directed at the valley below, where a mobile television unit is transmitting.

so on. The top storey of the main building provides modern and comfortable accommodation for those employed at this bleak outpost.

Large high gain aerials are used at Santis to receive signals from the nearest transmitter. After amplification, the signals pass to the transmitting system where they are sent into space to be picked up by similar stations on distant mountain tops or by domestic television sets within range.

I.T.A. RADIO SHOW EXHIBIT

"UNITY and Diversity" was the theme of the Independent Television Exhibit at the Radio Show. For the first time all nine independent programme companies, Independent Television News and the T.V. Times were represented in a joint exhibit which showed how I.T.A. with its eight transmitting stations and links, and the programme companies with their studios in different regions, combined to produce unity with variety in a vast, nation-wide organisation.

When it is considered that each region has its special requirements and that each company is essentially individualistic in character, it will be realised that this is no mean achievement. To many people, it came as a surprise to learn that so many different programmes are produced; still more astonishing were the intricate and complex arrangements which enable a programme to be switched from one control centre to another to meet split second timing requirements. The unity of the system was exemplified by the Celebrity Stage—the centre piece and focal point of the exhibit—where artists of all the programme companies were appearing.

The exhibit, attractive in concept and design with effective use of light and colour, had a direct and personal appeal to the public in emphasising how unity and diversity are brought together. The outer "wall" of the exhibit was made up of 43 large panels bearing huge photographs arranged with striking effect, showing the various pro-

grammes seen on ITV. Large maps indicated how the various networks fit together. The exhibit was designed by Jack Foxell and a young team of designers from Sir William Crawford and Partners.

Activity on the Celebrity Stage was televised by equipment provided by Tyne Tees Television which serves viewers in North-east England. Activity was continuous throughout the exhibition and showed the preparations involved in a TV programme, and included also personal appearances by a host of TV stars. The public saw the extraordinary camera acrobatics employed in achieving unusual angle shots, and the elaborate staging and backgrounds required in modern TV.

The equipment provided by T.T. Television included a complete outside broadcasting unit and a mobile video tape recording machine. There are already four mobile video tape recording machines in the ITV network and another 19 are installed permanently in the studios. These machines, costing some £35,000 each, record sound and vision simultaneously on a 2½ in. wide, plastic based tape.

Unlike movie film, the tapes do not require to be processed. They can be played back immediately or stored for an indefinite time, and produce sound and vision virtually indistinguishable from "live" transmissions.

TUBES

FACTORY REVACUUMED. ALL GUARANTEED 6 MONTHS. Carriage and insurance 12/6.

Enquiries welcomed for any types not listed. Due to the high quality of our tubes and low number of returns, we are able to maintain the following unusually low prices.

- 6501, 6504, 6505, CRM91, CRM92, MW22-7, MW22-14, MW22-14C, MW22-17, MW22-18, **£2/15/-**
- C12FM, CRM121, CRM121A, CRM122, MW31-7, MW31-14C, MW31-17 **£3/-**
- MW31-18, T12/54.
- 316, 3/31, 14KP4, 14KP4A, 108K, 121K, 141K, 7201A, 7202A, 7203A, AW36-21, C14FM, CRM141, CRM142, MW31/16, MW31-74, **£3/10/-**
- ME36-24, MW36-44, T12-549.
- 17AP4, 17ASP4, 6706A, C17FM, CRM171, CRM172, MW43-43, **£4/5/-**
- MW43-64, 7401A.
- 36A, 415, 9001A, C14BM, C17BM, CRM151, CRM152A, CRM152B, CRM153, MW41-1, MW43-80, T415, **£5/5/-**
- TR14-2, MW43-69.
- C21HM, C21NM, CRM211, CRM212, **£6/15/-**
- MW53-20, MW53-80.

REGUNNED TUBES

ALL GUARANTEED 12 MONTHS.

- Excellent workmanship, Carr. & Ins. 12/6.
- MW31/16, MW31/74, **£5/10/-**
- 121K, 12KP4.
- MW36-24, AW36-21, 141K, **£5/15/-**
- 14KP4, CRM141, CRM142.
- CRM152A, CRM152B, CRM153, **£6/15/-**
- CRM171, MW43/64, 171K, 17ASP4.
- MW53-20, MW53-80, **£9/10/-**
- CRM211, CRM212.

NEW TV TUBES

Sublet 12 month Guarantee. Carriage and insurance 12/6 extra.

- MW31/14, **£7/19/-** MW43/64 **£8/19/-**
 - MW36/24.
- All other types of new TV Tubes available at standard list prices plus carriage.

SPECIAL OFFERS

4-SPD. RECORD PLAYERS

Latest B.S.R. TU5 Turntable, together with lightweight stator galaxy dual sulphire crystal turnover pick-up head. £37/10/- 3/-.

STEREO 4-speed Single Player. Famous make. Just released. Limited Quantity. £6/19/- Carr.

RADIO Receivers, complete with 6 volt Vibrator Pack. 6K7, 6X5, 6Q7, 6V6, suitable for adaption as car radio. Secure 29/- Carr. 3/-.

AVO Valve tested. Standard Two Unit Type in teak £9/- Carr. 3/-.

G73 Signal Generator and Wavemeter. 100 Ke-s-1 met. crystal calibrator, precision attenuator. £9/10/- Carr. 2/-.

VALVES ALL GUARANTEED 3 MONTHS. P181 SOILED. AMAZING 7/- VALUE AT ONLY 7/-.

EY51 SHORT ENDS 10/ U25 SHORT ENDS 7/-

100 CONDENSERS 10/-

A well balanced range of mainly miniature ceramic and silver mica. From 3pF to 10,000 pF. A must for your spare box. Only 10/-

PM SPEAKER SNIPS

Tested, top makes, performance guaranteed. 5in. 10in. 12in. 14in.

8in. 7/6 12/- 10 x 6 14/-

TRANSISTORS AND DIODES

RED SPOT. Transistors for I.F., L.F. and Output up to 200 Kcs, 6/-.

WHITE SPOT, R.E. and L.F. 2.5 Mc/s, 8/6. XA102, 12/6. XA104, 15/-.

XB104, 9/-.

GET15, 10/-.

GERMANIUM DIODES. General purpose, famous make, 9/6.

8/- doz. DIODES. Equivalent to 6BX4, 3/9.

H.T. RECTIFIERS

2801, 6W79A (240 v 80 mA), 6/-.

RM2, 6/6; RM3, 9/-.

RM4 (PR4), 15/6; RM5 (PR5), 21/-.

14A8, 17-3; 14A9, 23/-.

14A10, 25/-.

14A11, 27/-.

14A12, 29/-.

14A13, 31/-.

14A14, 33/-.

14A15, 35/-.

14A16, 37/-.

14A17, 39/-.

14A18, 41/-.

14A19, 43/-.

14A20, 45/-.

14A21, 47/-.

14A22, 49/-.

14A23, 51/-.

14A24, 53/-.

14A25, 55/-.

14A26, 57/-.

14A27, 59/-.

14A28, 61/-.

14A29, 63/-.

14A30, 65/-.

14A31, 67/-.

14A32, 69/-.

14A33, 71/-.

14A34, 73/-.

14A35, 75/-.

14A36, 77/-.

14A37, 79/-.

14A38, 81/-.

14A39, 83/-.

14A40, 85/-.

14A41, 87/-.

14A42, 89/-.

14A43, 91/-.

14A44, 93/-.

14A45, 95/-.

TV SETS

TRULY AMAZING VALUE MADE POSSIBLE ONLY BY THE LARGE QUANTITIES SOLD. PICTURES NOT GUARANTEED, AS RECEIVED IN PART EXCHANGE. ABSOLUTELY COMPLETE, ALMOST ALL ARE LATEST A.C. D.C. TYPES. CARRIAGE, ETC., 9/- EXTRA ON ALL TYPES.

5-CHANNEL T.V.s

Modern. Table 12in., Untested. All top makes, tunable all B.B.C. stations. **£4/10/-**

12in. T.V.s. Single channel, absolutely complete. As above. Mainly Ch. 1. **£2/19/-**

14in. T.V.s. 5 Channel, untested, modern rectangular or C.R.M.I. 41 Tubes. Selling at twice the price elsewhere. **£7/10/-**

17in. T.V.s. Limited number as above, all ultra tubes. **£12/10/-**

I.T.V. CONVERTERS WITH INTERNAL POWER PACK. Well-known make. Very compact. Can be purchased practically all T.V.s. Gain and trimming **£3/10/-** Carr. 3/-.

Controls. **£3/10/-** (Listed at £7.7.0.)

If purchased with any of above sets. **£3.9.0.**

CO-AXIAL CABLE

Semi-air spaced low-loss. 1-19 yds., 7d. per yd. P. & P. 1/3. 20-29 yds., 6d. per yd. P. & P. 1/9. 50 YARD DRUMS 22/6. P. & P. 2/-.

1 WATT TRANSISTOR PUSH-PULL STAGE KIT.

Can transform your existing Transistor Receiver or Amplifier into a really high volume set. Two Matched GEB12 Power Transistors, correct Push-Pull Input and 3 Ohm output transformers. Instructions. **£2.19.0.** Post 2/-.

CRYSTAL PICK-UPS

STAAER GALAXY. Single hole mounting, lightweight adjustable needle pressure. For any 3- or 4-speed turntable. Amazing value.

1. With latest Steige and Reuter or Sossone tone cartridge. Interchangeable with and similar to the Acos GP65. Excellent reproduction 17 6

Cartridge only 15 -

2. As above, with Acos GP65 cartridge 22 -

Cartridge only 19 6

ACOS HQP37 Cartridge 25 -

CHARGING EQUIPMENT

RECTIFIERS. Iron selenium full wave. 12 v. 2a., 8/6. 12 v. 2i., 12 v. 1a., 5/9.

6V80 RED HVX2 6/6 PV81 7/- UCHX5 8/9

EF50 USA 2-RT32 6/- PY82 7/6 UCF90 16/-

6V80T 6/6 RT32 6/6 UCHX2 6/6 UCHX1 9/3

VALVES

PRICES REDUCED

GUARANTEED 3 MONTHS. 24 HOUR SERVICE

FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex Government or ex equipment origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days. 4d. FOR LIST OF 800 TYPES.

10% DISCOUNT SPECIAL OFFER TO PURCHASERS OF ANY SIX VALVES marked in black type (15% in dozens). Post: 1 valve, 6d.; 2-11, 1/-.

6587 6/6 12K8GT 77 4/6 EAH90 7/9

6V80GT 6/6 12K8GT 77 4/6 EAH90 7/9

6V80 6/6 12Q7GT 6-80 8- EA91 5/3

6V80GT 6/6 12K8GT 6-80 9/6 EAF42 8/6

6X4 6- 12K8GT 6- 90AY 4/6 EB34 1/6

6X4GT 6- 12K8GT 6- 90AY 4/6 EB41 7/-

6X4GT 6- 12K8GT 6

YOUR C.R.T. completely FACTORY REBUILT

New heater and Cathode assembly

9 months'
Guarantee

COMPARE OUR PRICES

- | | |
|--|-----------------|
| ★ 12 in. £3.0.0 | ★ 14 in. £4.0.0 |
| (Money back if not completely satisfied) | |
| ★ 17 in. £5.0.0 | ★ 21 in. £7.0.0 |

Carriage and Insurance add 12'6

All Mullard and Mazda Types Rebuilt—Fast Service
Send your Tube now—Terms C.W.O. or C.O.D.

KING'S TELE SERVICE CO.,
101-111, DAWES ROAD :: FULHAM, S.W.6

TELEVISION SPARES

All Makes

All Models

By return of post

LINE OUTPUT TRANSFORMERS

FRAME OUTPUT TRANSFORMERS

DEFLECTOR COILS

LINE AND FRAME BLOCKING OSCILLATOR TRANSFORMERS

ALL POTENTIOMETER AND SLIDER CONTROLS

MAINS DROPPERS

METAL RECTIFIERS

GERMANIUM DIODES

FOCUS MAGNETS

ION TRAPS

E.H.T. CONDENSERS

Our Range of Spares is probably the most extensive in the country and includes all Spares for Tape Recorders, Radio and Record Player Units.

Technical Advice Free. Service Manuals supplied on loan.

Terms: C.W.O. or C.O.D. All Components are supplied at list prices, plus 2/6 p.p.

Please enclose S.A.E. with all enquiries.

NEWBURY RADIO

272, ROMFORD ROAD, FOREST GATE, LONDON, E.7.

MARyland 3100

Amateur Television To-day

INTEREST IN TELEVISION AS A HOBBY IS GROWING RAPIDLY


By C. Grant-Dixon

THE BRITISH AMATEUR TELEVISION CLUB was founded some 10 years ago as an organisation linking up the activities of those who were interested in the transmission side of television. Initially, membership was confined to this country, but it soon became apparent that there were amateurs in other countries who were interested in television, even in places where there was no public television service. Hence it is not surprising that a fair proportion of the 300 or so members of the club reside overseas.

The activities of the club comprise the publication of a small quarterly magazine—"CQ-TV"—back numbers of which are available on microfilm; the loan of tape recordings on amateur television topics; the organisation of conventions, and the stimulation of interest in amateur television by demonstrations at local exhibitions. The last convention, held on September 6th, 1958, was featured in a subsequent edition of "Panorama" on BBC television. Films taken at the convention were shown and there was a live interview in the studio with G8PY/T's roving eye camera. On this occasion the BBC for the first time transmitted pictures from an amateur-built camera.

In the early days of amateur television in this country there were no camera tubes available except one at a price of £27. 10s. This tube, which is now obsolete, was very insensitive, although

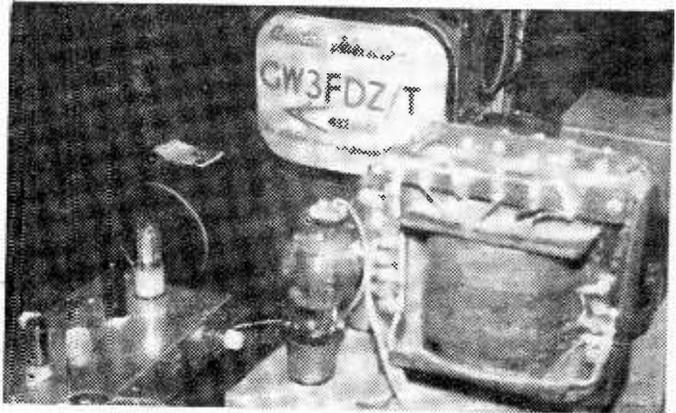of convenient size and easily scanned by electrostatic deflection. One amateur was fortunate enough to find one in one of the London surplus stores, but this is the only record of any having been bought this way over here, although in the USA complete surplus TV cameras are still available. With the disappearance of this tube, the British Amateur Television Club managed to



The 931A (on the left) is set up in front of a scanning tube with a transparency on its face.

persuade certain British manufacturers to part with some of their second grade camera tubes at greatly reduced prices and the Vidicon (Stacicon) is currently available in this way. This tube, which is the basis of most industrial television camera chains, is fairly sensitive but should be

operated with a high level of illumination to reduce the "lag" which is inherent in the conductive photocathode. The tube is magnetically scanned and focused, and has a special (and rather expensive!) socket. It is only just over 1in. in diameter and standard 16mm cine camera lenses can be used; in fact it is eminently suitable for most amateur purposes.

Not every amateur, however, is able to afford the £25 for a camera tube and quite a large number of satisfactory slide scanners have been built up from surplus material. Basically this involves putting a photomultiplier type of photocell (such as the 931A) in front of a short-persistence C.R. tube which displays a blank raster. A transparency or photographic negative is mounted on the face of the tube and the output from the photocell is then proportional to the light and shade of the



The author's colour TV camera on display at a Hobbies Exhibition in Ross-on-Wye.

picture as it is scanned and thus constitutes a video signal. A typical arrangement is shown in Fig. 1. For best results, both this type of picture generator and the camera have to be run from a



The "Roving Eye" camera (on the roof of a former taxi) operated by G3KKD/T.

proper pulse generator which consists of three parts.

(i) A timer unit which divides the output of a master oscillator running at 20,250 cycles by 9.9 and 5 in stages; the resulting 50 cycle pulse is then compared with a 50 cycle reference signal obtained from the mains and the error signal is used to lock the master oscillator precisely. This master frequency of 20,250 is then divided by 2 to give the standard line frequency of 10,125 cycles.

(ii) A pulse generator unit which accepts the 50 cycle and 10,125 cycle trigger pulses from the timer unit and produces synchronising and blanking waveforms.

(iii) A blank-sync-video mixer unit which takes the video signal and blanks it with a gate valve so that no video signal passes during the line and frame blanking period. To this signal the sync pulses are added and the result is a composite video signal which can be sent over a coaxial cable or passed to the modulator of a transmitter.

The precise circuits for these units have been the subject of many experiments by B.A.T.C. members with a view to reducing the number of valves without sacrificing too much in the way of reliability. The basic "building blocks" of these circuits are the rectangular pulse generator and the gate valve. Multivibrators are usually used for the former, and a pentode such as the 6F33 or even two triodes in cascade can be used as a gate. By interconnecting these basic circuits it is possible to build up any desired waveform. Circuit designs can be calculated mathematically, but the more "hit or miss" methods commonly employed by amateurs can often be used with

complete success. Many books give the theory of these and other circuits and are readily available from any good public library; but the reader who looks for complete circuits with all components values given may be disappointed. It was, in fact, the absence of practical information of use to the amateur which led to the formation of The British Amateur Television Club and the publication of "CQ-TV."

In short, the construction of a complete television camera chain is not a task to be undertaken lightly, and it will undoubtedly baffle the constructor who has had no more experience than the construction of a simple straight radio receiver. For the person who has already built a TV receiver, however, it is a logical step and opens up vast new fields of interest and experimentation; apart from the excitement of producing one's own pictures on the screen, there is the possibility of colour and even of recording on tape. Some members are experimenting with a low frequency television with a view to recording pictures on tape so that an illustrated lecture could be recorded on a twin track tape.

Finally, for those who wish to pursue this further, the secretary of the British Amateur Television Club is D. S. Reid, 149, Ongar Road, Brentwood, Essex, who will be pleased to send further details to any enquirers.

New Thermostatic Soldering Iron

A NEW thermostatic soldering iron, with accurate temperature control, has been developed from an N.R.D.C. patent by a small Scottish engineering company. It is particularly useful for fine work.

The firm is the Cardross Engineering Co. Ltd., whose managing director (Mr. G. S. Meek) believed that there was an urgent need for a high-quality instrument of this kind. His idea was to provide a temperature control of plus or minus 15 deg. C. at a normal setting of 230-250 deg. C. Enquiries at the Patents Library, however, showed that the General Post Office already had a patent in existence covering the idea and as this was in the hands of the National Research Development Corporation for exploitation, Mr. Meek applied for a licence to manufacture.

Cutting Costs

The next step was the development of the basic idea, which was to make the differential expansion of an inner non-ferrous metal rod and an outer case operate a micro-switch by an intermediary magnifying lever movement. Trials showed that a number of points required further investigation and experiment. Mr. Meek, who is an engineer, carried out this work personally, as a result of which he succeeded in dispensing with the expensive Invar steel (an iron-nickel alloy with a low co-efficient of expansion) originally specified. In its place, he used ordinary mild steel, cutting costs by about 50 per cent.

R.S.C. (LEEDS) LTD. (LEEDS, MANCHESTER and BRADFORD)

Dept. N, 5/7 COUNTY ARCADE, LEEDS, 1
54 MORLEY STREET, BRADFORD
8/10 BROWN ST. (MARKET ST.), MANCHESTER

Post Terms C.W.O. or C.O.D. NO C.O.D. under £1. Postage 1/9 extra under £2.
2/9 under £5. Open to callers 9 a.m. to 6 p.m. Wednesdays until 1 p.m. S.A.E.
with enquiries, please. Full list 6d. Trade supplied.

R.S.C. TRANSFORMERS

Fully Guaranteed
Interleaved and Impregnated
Primarys 200-230-250 v. 50 c/s screened
TOP SHROUDED DROP THROUGH
 280-0-280 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 16/9
 350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 18/9
 350-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 22/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 29/9
FULLY SHROUDED UPRIGHT
 250-0-250 v 60 ma, 6.3 v 2 a, 5 v 2 a
 Midget type 21-3-9in. ... 17/9
 300-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9
 350-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 25/9
 350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 25/9
 350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 33/9
 425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v
 4 a, C.T. 5 v 3 a ... 49/9

FILED TRANSFORMERS
 All with 200-250 v. 50 c/s Primarys
 15 a, 5/9; 6.3 v 2 a, 7/6; 0-4-6.3 v 2 a, 7/9;
 12 v 1 a, 7/11; 6.3 v 3 a, 3/11; 6.3 v 6 a, 17/9.

CHARGER TRANSFORMERS
 200-250 v 0-9-15 v 11 a, 11/9; 0-9-15 v 3 a, 16/9;
 0-9-15 v 5 a, 19/9; 0-9-15 v 6 a, 23/9.

OUTPUT TRANSFORMERS
 Standard Pentode 5,000 to 3 ohms ... 4/9
 Small Pentode 5,000 to 3 ohms ... 3/9
 Standard Pentode 7,000 to 3 ohms ... 4/9
 Standard Pentode 10,000 to 3 ohms ... 4/9
 Push-Pull EL84 to 3 or 15 ohms ... 16/9
 Push-Pull 10-12 watts 6V6 to 3 or 15
 ohms ... 15/9
 Push-Pull 10-12 watts 6V6 to 3, 5, 8 or
 15 ohms ... 18/9

SMOOTHING CHOKES
 100 ma 10 h 250 ohms ... 8/9
 10 ma 10 h 350 ohms ... 5/6
 10 ma 10 h 400 ohms ... 4/11

SELENIUM METAL RECTIFIERS
 250 v 250 ma, 11/9; 250 v 80 ma, 7/9;
 250 v 50 ma, 4/11; 120 v 40 ma, 3/9;
 24 v 2 a, 1/9; 12 v 2 a, 1/9; 6 v 2 a, 1/9;
 112 v 2 a F.W., 6/11; 612 v 3 a, 9/9; 612 v
 a, 12/3; 612 v 5 a, 14/6; 612 v 6 a F.W.,
 15/5; 612 v 10 a, 25/9; 612 v 15 a, 35/9.
 Heavy duty type 24 v 15 amp F.W. Bridge
 with large square alum. coolers, 27/9
 each.

CO-AXIAL CABLE 1in.
 75 ohms 14/36 ... 8d. yd.
 Twin-screened Feeder ... 11d. yd.
STANDARD JACK PLUGS, with
 4ft. screened lead, 1/11.
STANDARD JACK SOCKETS
 (STANDARD), 2/9.
5-CORED FLEX, Rubber insulated
 14/36, 1/3 yd.; 50-56 yds.; £4 10 yds.

BATTERY SET CONVERTER KIT
 All parts for converting an normal type
 of Battery Receiver to A.C. mains 200-250v
 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma,
 fully smoothed and fully smoothed L.T.
 of 2 v at 0.4 a to 1 a. Price including circuit,
 49/9. Or ready for use, 9/9 extra.

**ALL DRY RECEIVER BATTERY
 ELIMINATOR KIT**—All parts for the
 construction of a unit (metal case
 51-41-2in.) to supply Battery Portable
 receivers requiring 90 v and 1.5 v. Fully
 smoothed. From 200-250 v 50 c/s mains.
 Price, inc. point-to-point wiring diagrams,
 39/9. Or ready for use, 46/9.

D.C. SUPPLY KIT—Suitable for Electric
 Trains. Consists of mains transformer
 200-250 v 50 c/s, A.C. 12 v 1 a Selenium,
 F.W. Bridge Rectifier, 2 Fuseholders, 2
 Fuses, Change Direction Switch, Variable
 Speed Regulator. Partially
 drilled Steel Case, and Circuit. **29/9**

EX-GOVT. CANES, Well ventilated,
 black crackle finished, undrilled cover.
 Size 14 x 10 x 8 1/2 in. high. IDEAL FOR
**BATTERY CHARGER OR INSTRUMENT
 CASE, OR COVER COULD BE USED FOR
 AMPLIFIER.** Only 9/9, plus 2/9 postage.

TELEVISION RECTIFIERS
 250 v 200 ma. Size 2 x 1 1/2 in. Brand
 New, 6/8.

11-11-8-WATT AMPLIFIER, Special
 purchase due to cancelled export orders,
 £4/19/9, Carr. 7/6. For 200-250 v A.C.
 A limited number is available of these
 highly sensitive push-pull units, guaranteed
 brand new and in working order and
 with separately controlled inputs for
 "mike" and gram., etc. etc. Latest
 B.V.A. valves. Excellent performance.

EX-GOVT. MAINS TRANSFORMERS

All 200-250 v 50 c/s input.
 Removed from New ex-Govt. units, **22/9**
 275-0-275 v 100 ma, 6.3 v 7 a, 5 v 3 a
 350-0-350 v 160 ma, 6.3 v 5 a, 5 v 3 a ... 27/9
 400-0-400 v 200 ma, 5 v 2 a, 5 v 2 a ... 18/9
 450-0-450 v 250 ma, 6.3 v 3 a, 6.3 v 1 a,
 5 v 6 a ... 49/9
 12.5 v 3 a, 5 v 3 a ... 12/9
 0-24-26-28 v 15 a, A.C. (marked with D.C.
 rating after rectification), 69/6 carr. 15-
 10-25 v 24 a, 79/6 carr. 15-.

EX-GOVT. SMOOTHING CHOKES—
 60 ma 5-10 h 250 ohms ... 2/11
 80 ma 10 h 150 ohms ... 6/9
 100 ma 5 h 150 ohms Tropicalised ... 3/11
 100 ma 8-10 h 100 ohms Parmeko ... 6/9
 120 ma 12 h 100 ohms ... 3/9
 150 ma 6-10 h 150 ohms Trop. ... 6/9
 150 ma 10 h 150 ohms ... 9/9
 200 ma 2-5 h 100 ohms Parmeko ... 7/9
38683 UNITS, Comprising chassis with
 strong cover 17 x 10 x 8 ins. Over 60 re-
 sistors (many high stability) and con-
 densers, wholders, I.F.T.s, co-ax sockets,
 controls, fuse-holders, tarboards, etc.
 etc. Except. value at only 12.6 carr. paid.

ELECTROLYTICS (NEW)

Tubular		Can type	
8 mfd 450 v	2/6	8-8 mfd 450 v	1/8
16 mfd 450 v	3/6	8-16 mfd 450 v	4/8
E-16 mfd 500 v	4/11	16-16 mfd 450 v	5/8
25 mfd 25 v	1/6	32-32 mfd 350 v	5/6
50 mfd 12 v	1/6	32-32 mfd 450 v	7/6
50 mfd 50 v	2/6	150 mfd 450 v	5/9
100 mfd 25 v	2/9	100-100 mfd 350 v	7/5
3,000 mfd 6 v	5/9	100-200 mfd 275 v	9/9
6,000 mfd 6 v	6/9		

BATTERY CHARGERS

For 200/250 v 50 c/s A.C. mains. 12 months guarantee. Attractive, well ventilated, hammer finished cases, 6 v or 12 v 4 amp, with meter and variable charge rate selector, as illustrated **69/9**
 6 v or 12 v 1 amp type. Also suitable for electric train power supply. Only 27/9, post 2/9.



NEW STOCK 24 HOUR SERVICE VALVES ALL GUARANTEED

Postage:—Up to 3 6d.; 4-6 9d. U_pwards of 6 see our normal terms.

1A96	6/9	6HX6	6/6	6V6G	6/9	20P1	12/9	DD41	8/9	EF50	4/9	KTW63	4/9	PY82	8/9	UCC85	10/6	
1A4J	6/9	6B9	11/9	6X2	6/9	20F2	8/9	DH77	7/9	EF54	5/11	KTZA1	7/8	PY83	8/9	UC182	16/9	
1CIEM	6/9	6D1	1/9	6X4	6/9	21A6	13/9	DH63	6/9	EF80	7/9	L63	4/9	P230	16/9	UC182	14/9	
1CJ	6/9	6D2	6/9	X5	5/11	25L6	9/9	DH109	10/6	EF85	7/3	LN152	9/9	R2	9/9	UF42	8/9	
1L4	5/11	6D3	6/9	7B7	9/9	30L1	8/9	DH12	8/9	EF86	16/9	MH4	6/9	R3	9/9	UF89	8/9	
1AH5	6/9	6F1	11/9	7C5	7/9	30P16	9/9	DH47	6/9	EF89	9/9	MU12	9/9	SD61	1/9	UL41	9/9	
1FD1	6/9	6F12	6/9	7C1	7/9	35Z4	9/9	DH150	8/9	EF91	9/9	MU14	9/9	S76	8/9	UL36	14/9	
1FD9	6/9	6F13	11/9	7AN7	7/9	41MHL	6/9	DH719	8/9	EF93	9/9	N17	3/3	SP3	9/9	UY35	10/6	
1F1	6/9	6F14	11/9	757	9/9	53KU	10/9	DK91	7/9	EK90	9/9	N19	9/9	SP42	11/9	UO3	9/9	
1F2	6/9	6F15	11/9	774	7/9	54KU	11/9	DK96	9/9	EL32	4/9	N37	19/9	SP61	2/9	UU4	9/9	
1F3	5/11	6H5	2/3	8D2	3/3	6DPT	8/9	DL32	2/3	EL33	11/9	N77	4/9	SP64	8/9	UO5	9/9	
1P1	6/9	6J5	4/9	8D3	3/9	62VP	7/9	DL93	9/9	EL38	19/9	N142	9/9	T41	16/9	UY51	7/9	
1P10	6/9	6J5G	4/6	807	7/6	63ME	6/9	DL94	9/9	EL38	19/9	N144	9/9	U22	7/9	VP120A	3/9	
1P11	8/9	6J6	4/9	8D2	3/9	65ME	8/9	DL96	9/9	EL41	10/9	N148	7/9	U24	7/9	VP32	3/9	
1RS	7/9	6J7G	5/9	908	6/9	141TH	8/9	EA50	1/9	EL49	9/9	N152	13/9	U25	15/9	VS110	3/9	
1T4	5/11	6K7M	5/9	10C1	1/9	171DDP	8/9	EAC080	9/9	EL60	9/9	N329	9/9	U31	9/9	W17	5/11	
3A4	6/9	6K8G	8/9	10F1	17/9	315SU	9/9	EAF42	9/9	EL91	4/9	N54	9/9	U35	8/9	W147	3/9	
3C4	6/9	6LD3	3/9	10LD3	3/9	415PT	7/9	EB34	2/3	EM80	9/9	N59	9/9	U46	9/9	W150	9/9	
3C4	6/9	6LD12	8/9	10LD12	15/9	44U	9/9	EB41	7/6	EY86	13/9	N709	9/9	U49	9/9	W179	9/9	
3V4	6/9	6LD20	8/9	10LD14	15/9	AC/PH	5/9	EB41	7/6	EZ35	9/9	N727	9/9	U50	8/9	W272	9/9	
4D1	5/9	6L1	8/9	10P14	9/9	AC/PH	5/9	EBC33	6/9	EZ80	9/9	OA81	4/9	U52	6/3	W727	9/9	
5U4G	6/9	6L12	8/9	10P14	9/9	B65	5/9	EBC39	6/9	EZ81	8/11	OC72	25/-	U54	10/9	W709	9/9	
5Y3G	7/9	6L18	11/9	10P18	9/9	B152	8/9	EBF80	9/9	EZ90	6/9	OM4	6/9	U78	9/9	W142	9/9	
5Z4G	9/9	6L6G	8/11	12A6	5/9	B309	8/9	EBF89	9/6	GZ32	11/-	P61	2/9	U139	9/9	X17	9/9	
6AB8	12/9	6M19	11/9	12AT7	7/9	B319	8/9	ECC35	7/9	GZ30	9/9	PCF80	12/3	U142	9/9	X142	9/9	
6AC6G	11/9	6M1	6/9	12AU6	7/9	B329	8/9	ECC32	7/9	GZ33	10/9	PCL84	8/9	U152	9/9	X719	9/9	
6AJB	8/9	6Q7G	8/9	12A7	7/9	B339	9/9	ECC33	9/9	GZ34	13/9	PCL82	12/6	U153	9/9	X727	9/9	
6AK8	8/9	6P25	11/9	12AX7	8/9	B719	8/9	ECC34	9/9	GZ37	9/9	PCF82	9/9	U154	9/9	Y83	5/9	
6AL5	5/9	6P28	9/9	12BN7GT	8/9	D1	8/9	ECC35	9/9	HLA1DD		PEM46	8/9	Z61	9/9	Z66	8/9	
6AM5	6/9	6S67	8/9	15SPA	8/9	D63	8/9	ECC31	4/9			PER383	8/9	Z62	8/9	Z66	8/9	
6AM6	4/9	6S67	8/9	18VPA	3/9	D77	5/11	ECF80	12/9			PL33	9/9	U319	9/9	Z77	7/9	
6AT6	7/9	6SK7	6/9	18VPA	3/9	D152	9/9	ECF82	12/9			PL38	16/9	U401	8/9	Z142	9/9	
6AQ5	7/9	6SL7GT	7/9	15A6	7/9	D152	9/9	ECF81	8/9			PL41	13/9	X383	9/9	Z145	9/9	
6AQ6	7/9	6SN7GT	7/9	16A5	6/9	DAF91	7/9	ECL80	10/9			PL42	9/9	UABC90	10/6	Z152	5/9	
6B83	3/11	6USG	6/9	16A8	7/9	DAF96	9/9	ECL82	11/9			PL83	10/9	UAF42	10/6	Z159	5/9	
6B86	9/9	6U4GT	12/9	17Z3	9/9	DF96	9/9	EF39	5/11			PY31	7/9	UB41	11/9	Z729	16/9	
6BE6	9/9	6V8	8/9	19Y3	9/9	DF92	9/9	EF41	8/11			PY80	7/9	UBC41	9/9	ZD17	9/9	
6BGGG	16/9	6V8	8/9	19X3	9/9	DD6	11/9	EF42	8/9			PY81	9/9	UBF80	9/6	ZD152	5/9	
6BY5	9/9	6V8	8/9	19X3	9/9													
6B77	7/9	6V6GT	7/9	20D1	14/9													

SUFFOLK'S COUNTRY WIDE OFF-THE-SHELF SERVICE FOR PICTURE TUBES

OBTAINABLE FROM :

- J. T. Richardson, A.M.I.E.E., A.M.Brit.I.R.E., 69, Bedford St., City Rd., Cardiff. *Tel. : Cardiff 29972.*
- Kings (of Sandy Row), Ltd., 68/70, Sandy Row, Belfast. *Tel. : Belfast 31985.*
- Frank H. Hunt & Co., Stepote Hill, Exeter, Devon. *Tel. : Exeter 56687.*
- Scotts Radio, Ltd., 4, Church St., Brighton. *Tel. : Brighton 26891.*
- Messrs. Taylors, 162, Eastney Rd., Milton, Portsmouth. *Tel. : Portsmouth 35000.*
- Lawsons (Bury St. Edmunds), Ltd., 36, Cornhill, Bury St. Edmunds, Suffolk. *Tel. : Bury St. Ed. 3304.*
- Messrs. Youngs, TV Specialists, High St., Ryde, I.O.W. *Tel. : Ryde 2489.*
- Ellison (Radio Distributors), Ltd., 3, Victoria Rd., Northampton. *Tel. : Northampton 3372.*
- R. Watson, Rose Inn, Cotton End Rd., Wilstead, Beds. *Tel. : Wilstead 267.*
- Inraxia Ltd., 65/66, Coleshill St., Birmingham, 4. *Tel. : Aston X 4815.*

12 MONTHS FULL GUARANTEE

SUFFOLK TUBES LTD

London's Largest Independent
Tube Rebuilders



SUFFOLK HALL, 1-3 UPPER RICHMOND ROAD, PUTNEY, S.W.15. TEL. : VAN 5267,4304.

Now . . . in your own home, LEARN

RADIO - TELEVISION - ELECTRONICS

NO PREVIOUS TECHNICAL EXPERIENCE NEEDED!
PRACTICAL EQUIPMENT
(INCLUDING TOOLS)
GIVES YOU A REAL LABORATORY TRAINING

"The trained electronics engineer has a great career ahead of him."

Valuable FREE Book shows how E.M.I. Institutes School of Electronics can train you for today's wonderful opportunities.

Radio, Television and Electronics provide an exciting field for the trained man—high pay, a prosperous future—or if you prefer it—independence in your own business. If you are trained at home by E.M.I. Institutes you will be in the hands of specialists who know the quickest way to prepare you for one of the fine jobs open to trained electronics-men. Whether you are a beginner or an advanced student with an examination in mind, E.M.I. Institutes School of Electronics has a Course exactly suited to your needs—with or without practical equipment—from electricity and magnetism to automation techniques.

Practical Radio
Radio & Television
Servicing
Practical Electronics
Electronics Engineering
Automation
Basic Practical and
Theoretic Courses for
beginners in Radio,
T.V., Electronics, Etc.
A.M.Brit.I.R.E.,
City & Guilds Radio
Amateurs' Exam.
R.T.E.B. Certificate
P.M.G. Certificate
"NO PASS—NO FEE"

We Definitely Guarantee
"NO PASS—NO FEE"
Full details of the Courses, Practical Equipment, convenient monthly payments, our Employment and Advisory Depts., and much other helpful information is given in our Guide to Careers in Electronics. Write for your copy today. There is no obligation and the book will be sent to you quite free of charge.

FREE BOOK - POST NOW!

Please send me a free copy of your Guide to Careers in Electronics.

NAME

ADDRESS


Subject or Exam



E.M.I. INSTITUTES

SCHOOL OF ELECTRONICS

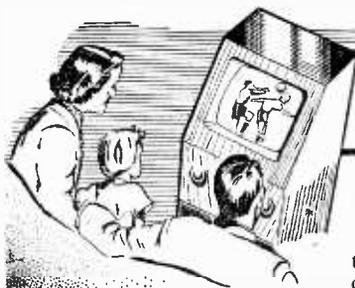The Specialist Electronics Division of the British Institute of Engineering Technology.
(DEPT. SE/21), COLLEGE HOUSE, 29-31, WRIGHT'S LANE, KENSINGTON, LONDON, W.8.



UNDERNEATH THE DIPOLE

A MONTHLY COMMENTARY

By Iconos

DURING recent weeks I have heard several amusing descriptions of the activities and methods of operation at some of the smaller independent television stations in America, which appear to be following the free-and-easy trends of the much older small-town sound radio stations. The happy-go-lucky atmosphere is apparently quite different from the nervous tension of the large network studios in New York, Chicago and Hollywood.

The programmes are based mainly upon sponsored features relayed from the major networks, eked out with hired 16mm. films and a strictly limited amount of local live programmes. In some stations, locally originated live features are limited to interviews and news. Others boast a 16mm. film unit, and, in a very few cases, an O.B. truck. It must be remembered that in some isolated districts in the USA,

there are two or three independent TV stations competing for the attention of viewers in areas which have populations of little more than 100,000 persons. Naturally, the income derived from sales of advertising space is not very great. Consequently, stations have to be run on a most economical basis, with the minimum of staff. Quite a few stations are able to carry on a service with only about forty programme and engineering staff—and there is no sharp line of demarcation between the two sides. Some stations employ a number of part-timers, who spend the day in radio shops or garages, before coming along to the TV station in the evening. My informants told me that the average standard of transmission was not very high in these stations (with a few exceptions). But there was no doubt about the enthusiasm of the staff.


Studio Equipment

As for the equipment, many stations operate with "packaged" basic equipment sold by

four or five leading manufacturers. This comprises a two-camera studio equipment, with a simple master control for dealing with it and with incoming network programmes, a 16mm. tele-cine apparatus, and, of course, a transmitter. It should not be forgotten that, unlike the pattern of British television operation, in America the transmitter side is often very much integrated with the studio equipment, and is in the same building, even in the same room! In some cases, the engineers in charge of the transmitter also carry out other duties, such as watching the camera control units and adjusting the racks. One of the results of such a method of operation is that the engineers acquire a very wide knowledge of all sides of their work—in some cases, even of work on the programme and announcing sides.

Provincial Atmosphere

THE contrast between the large London television centres and the smaller provincial stations in Britain is much less than in America. Nevertheless, the atmosphere in the British provincial stations has some of the informal characteristics of the smaller American stations, at the same time retaining the high pitch of efficiency expected of a metropolitan TV centre. The staffs are much larger, but not as great as the legions of programme and engineering personnel necessary in London or New York. A recent re-visit to TWW's Pontcanna Studios at Cardiff was a pleasant experience. Here, a certain element of informality and a maximum of enthusiasm had not yet been tempered by the frustrations so often noticeable in London. The influence of American master control layout is seen here at its best. Additional camera equipment, presentation studios and camera control rooms had been

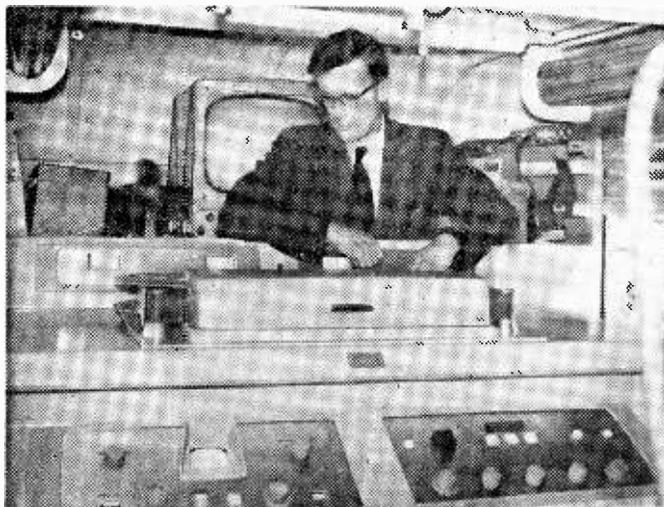

Tyne-Tees Television's Videotape Recording Unit. This machine was exhibited by TTT on the Independent Television stand at the recent National Radio and Television Exhibition at Earls Court.

added since my last visit and the staff were looking forward to the prospects of using an Ampex video-tape equipment. This will be mounted on a vehicle so that it can be used either at Pontcanna Studio or at TWW's new Bristol studio, due to open in a few months. It will also probably be able to be used on exterior locations, in the same way as Granada's mobile Ampex equipment. The decision to construct a large main studio stage 80ft. X 60ft., and only about 23ft. high to the "grid," has been a wise one, although it was surprising at the time when they started operations. I noticed a number of small sets around the stage which, I was told, were more or less permanent and available for regular features. Heights in excess of 23ft. are rarely required and necessitate more expensive and complicated equipment for carrying the lights.

TWW's new Bristol studio will be slightly larger than Pontcanna and will include many of the newest developments in equipment and techniques that have come to light in the last couple of years.

TV's Growing Power

COMPETITION between BBC and I.T.A. grows, and, in spite of all the network tie-ups, so does rivalry between the various commercial programme companies. The major four, A-TV, Associated Rediffusion, Granada, and ABC Television, now wield enormous power, and even the smaller companies are able to buy their way into the newspapers, radio relay companies, foreign and Commonwealth TV and radio fields, and equipment companies. They have undertaken their responsibilities with great discretion, and even dignity. The major mistakes have occurred when unfettered politics have occupied the television screens.

Video-tape

THE standard Ampex video recorder, now used by nearly all the British television organisations, including the BBC, is a streamlined looking piece of equipment. Nevertheless, it is heavy and bulky, intended for

use in a large control room. Granada TV have modified one of their Ampex machines to fit in a much smaller console, with its monitor and racks. This smaller sub-divided version of the Ampex has been fitted into one of the Granada "Travelling Eye" mobile trucks, which carries complete equipment for a single TV camera, sound channels and control apparatus. The camera can be operated on the roof mounting or remote, with lengthy cables, and both vision and sound can be recorded while the event is taking place. Power is supplied from a mobile generator, which can be towed behind the camera truck. Thus, the television camera and microphone can be sent at short notice on news assignments without the necessity of microwave links or post office lines for communication with the studio, and is independent of the mains electricity supply.

The Theatre

THEATRES, one by one, seem to be closing their doors. Television is partly, but not wholly, to blame for this. A few theatres in London and provincial towns continue to attract large audiences, principally through a combination of good and well-known actors, good plays, modern seating comfort and ventilation. A few would like to bring their houses up to date with such modern refinements as multiple channel dimmer switchboards, the latest types of lighting, new decorations, fixtures and fittings.

Alas! They cannot afford it. That is where television comes to their aid, and in various ways both the BBC and I.T.A. programme companies help con-

siderably and several theatres have cause to be grateful for financial help received.

The Organ and TV

THE organ was more or less exclusively used by the Church and the fairground for many, many years—for it is an ancient instrument. Then, in the 1900's, a few large organs were used in big halls for concerts other than religious ones. A little later, huge travelling organs, which could be divided up into small sections for mobility, toured the English music-halls. Max Erard and Zona Vevey were exponents of the most famous of these 20-ton monsters, which required quite a team of skilled removal men to take them down and assemble them. Next, the cinema took up the organ as an interval turn—still huge, but operated partly by electrical controls. The electronic organ was developed over many years before it became a practical and reliable proposition. Its portability compared with any of its predecessors was striking, to say the least.

Cinema organs have lost popularity for the moment, but the organists have found other employment, playing these highly portable, and now quite reliable, electronic devices. Television studios, particularly the I.T.A. programme companies, find that they fulfil programme requirements of all kinds, from parlour games to epilogues, and at the same time are sufficiently light to move around from studio to studio. They vary in size from the small monophonic type, used in conjunction with other instruments, to elaborate multi-keyboard instruments, at prices from about £100 to over £2,000.

PRACTICAL WIRELESS


CHIEF CONTENTS OF SEPT./OCT. ISSUE

- A DIRECT-COUPLED AMPLIFIER
- BEGINNERS' TEST METER
- NOTES ON M.W. AERIALS
- TRANSMITTING TOPICS
- A MICROPHONE PRE-AMPLIFIER
- A T.R.F. COMMUNICATIONS RECEIVER
- A PRE-SET M.W. BOOSTER STAGE
- AN S-METER FOR THE RI155
- SILICON POWER RECTIFIERS
- A HANDY SIGNAL TRACER

FOR YOUR CONVENIENCE! EASY, NO DEPOSIT, INTEREST FREE DEFERRED TERMS ON ALL GOODS

17" T.V. 19 GNS.

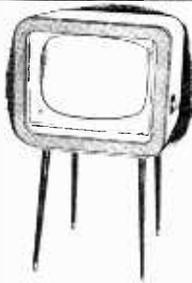
- ★ Beautiful latest finish cabinet in contemporary style covered and washable.
- ★ Polished legs 18in. Optional extra for 25/-.



WHILE STOCKS LAST!

- ★ 17in. **BRITISH** Rectangular Tube. Guaranteed fully for 12 months.
- ★ 13 channels "Turret Tuned"—ITV/BBC. Extra coils at only 7/6 a pair (with order).
- ★ Chassis. 14 B.V.A. Valves. Salvaged but re-conditioned and guaranteed 3 months. Carr. & Ins. 30/-.

RECORD PLAYER R.P.3. CABINET 69/6

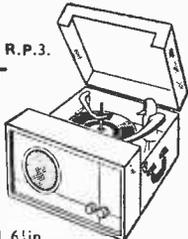

A delightful looking cabinet 14 1/2 in. x 17 1/2 in. x 8 1/2 in. in 2-tone leatherette. Will take a B.S.R. Monarch 4-speed autochanger and 6 1/2 in. round speaker. Carr. & Ins. 4/6.

REPLACEMENT RE-BUILT T/V TUBES

12 months full guarantee

Yours for 8/6 initial payment (plus carr. & Ins.) and 19 weekly payments of 8/6.

All sizes except 10in. Completely rebuilt gun assembly new cathode, heaters, etc., giving the high standard required for long picture life, quality and value. Carr. & Ins. 15/6.



CASH PRICE £8'10'/-

WORLD'S FINEST AUTOCHANGER

U.A.8. B.S.R. MONARCH 4-SPEED AUTO-CHANGER, £6.19.6.

U.A.12. B.S.R. MONARCH Latest 4-SPEED MIXER, £8.9.6.

T.U.9. B.S.R. 4-SPEED SINGLE PLAYER, 89/6.

COLLARO CONQUEST 4-SPEED AUTO-CHANGER, £6.19.6.

COLLARO CONQUEST STEREO AUTO-CHANGER, 11 GNS.

Carr. & Ins. on above 5/6.

★ EXPRESS DESPATCH SERVICE

Please phone to confirm Tube in stock. Send Telegraph Money Order. Tube despatched Passenger Train same day. This service only available with remittance by a Telegraph Money Order and cash sales—not terms.

PORTABLE AMPLIFIER MK. D.I. 59/6

12 months guarantee.

Brand new. Latest design with printed circuit. Dimensions 7 x 2 1/2 x 5 in. A.C. only. Mains isolated. 2-3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P 3/6.

EXTENSION SPEAKERS

Polished oak cabinet of attractive appearance. Fitted with 8in. P.M. Speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Ins., carr., 3/6.



★ IDEAL FOR STEREPHONIC SOUND

- | | |
|-------------------------------|------------------------------------|
| Bin. P.M. Speaker, 8/9. | 7 x 4in. Elliptical speaker, 19/6. |
| 6 1/2 in. P.M. Speaker, 12/6. | 8 x 5in. Elliptical speaker, 15/9. |
| Post 2/6. | Post 2/9. |

★ STEREPHONIC CABINET, 99/6

Continental style cabinet including extra clip on speaker cabinet. 15 1/2 x 10 1/2 x 24 1/2 in. deep. Takes B.S.R. 4-speed stereo autochanger. Printed circuit amplifier. Two Bin. speakers. Carr. & Ins. 12/6.


STEREPHONIC AMPLIFIER, £7.19.6

12 months guarantee.

Beautifully made for portable stereophonic record players. Latest design with printed circuit. Dimensions 3 x 5 1/2 x 9 1/2 in. A.C. only. Mains isolated. Twin amplifiers each side giving 3-4 watts output. Incorporating ECL82 triode pentode valve. Full tone, volume and balance controls. Complete and ready to fit. Knobs 3/6 per set extra. P.P. & Ins 3/6.

SUPER CHASSIS 79/6

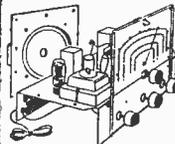5 valve superhet chassis including 8in. P.M. speaker and valves. Four control knobs (tone, volume, tuning w/change switch). Four w/bands with position for gram. p.u. and extension speaker. A.C. Ins., carr. 5/6.



SOLO SOLDERING TOOL 12/6

110 v., 6 v., or 12 v. (special adaptor for 200/240 v., 10/- extra). Automatic solder feed including a 20 ft. reel of Ersin 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 3/6.



14in. T.V. CHASSIS, TUBE & SPEAKER, 11 GUINEAS.

With 14in. Rectangular Tube. 12 months guarantee on Tube, 3 months guarantee on chassis and valves. Chassis with tube and speaker (less valves), 11 guineas. Complete and working with valves and Turret Tuner, 15 guineas. Ins. (incl. Tube) 25/-.

FAMILY RADIO, 99/6

5 valve (octal) superhet. A.C. 3 waveband and gram. position. 4 controls. Modern attractive cabinet size 15 1/2 x 18 x 10 1/2 in. in cream and brown. Carr. & Ins. 8/6.

DUKE & CO.

(Dept. E.10.)

621/3, Romford Road, Manor Park, E.12.

Tel. ILF. 6001/3,

Catalogue FREE upon request.

AUTUMN ATTRACTIONS

- BATTERY PLAYER.** 6 or 9 volt. 4 speed. 99/6. P. & P. 4/6.
- VALVE BATTERY AMPLIFIER.** 39 6. 14 v. L.T. 60 or 90 volt H.T. Suitable for above. P. & P. 3/6.
- 3 TRANSISTOR AMPLIFIER.** 79/6. Ideal for use with player above. 9 volt. P. & P. 3/6.
- SPEAKERS.** 12 6. Round 6 1/2" Std.; matching. 2.5 ohms. P. & P. 2/6.
- ELLIPTICAL SPEAKERS.** 19/6. 2 sizes. 7" x 4" or 8" x 5". P. & P. 2/6.
- 8" P.M. SPEAKERS.** 5 9. Limited quantity. Tested and Guaranteed. Had a slight cone repair. Not affecting the quality. P. & P. 2/9. On 2 3/6.

FOR THE RADIO ENTHUSIAST

- FOCUS MAGNETS.** 9 9. Brand new 38 mm. Incorporating picture shift control. P. & P. 1/3.
- BLAC FOCUS MAGNET.** 12 9. New. 35/38 mm. P. & P. 1/3.
- 17" T.V. MASKS.** 7 9. White plastic. P. & P. 2/3.
- TUNING CONDENSERS.** 2 6. New. 2-gang. Std. size. P. & P. 1/3.
- INSULATING TAPE.** 1 6. Good quality. 75" x 1" wide. In sealed metal tin. Post 9d.
- T.V. AERIALS.** 7 9. Fitted with 9' co-ax. cable. For door, rod or loft. P. & P. 1/3.
- T.V. AERIALS.** 15 6. Indoor type. Folded dipole with 12' co-ax. fitted. P. & P. 1/9.
- CAR AERIAL.** 6 9. Cadmium plated. Whip antenna 50" long. Collapsing to 11". One hole fixing. Post 1/-. (Not telescopic.)

- S/VISION STRIP.** 2 9. S/net. Takes 6-EP91, 6D1 and 6F14. Post 2/6. Less valves. Plessey. S.V. 4/9. P. & P. 2/6.
- TIME BASE.** 2 9. Including line trans. scanning coils and focus unit. P. & P. 3/6.
- T.V. SLIDER CONTROLS.** 5 7. 5 on a panel. Complete with knobs. P. & P. 1/-.


SPECIAL OFFER
EXTENSION SPEAKER. 19 9. Fitted in attractive cabinet with flex and switch. Make an ideal present, or keep the lady of the house happy. Ins., carr., 3/6.

- MAINS POWER TRANSFORMER...** 12/6
 350-0-350 v. at 250 m.a. 6.3 v. at 4 amp., 6.3 v. at 4 amp., 4 v. at 3 amp. 22 v. at 3 amp. 4 v. centre tapped at 1.5 amp. Primary 200-250 v. 50 cycles. P. & P. 3/9. Drop through type. ...
- MAINS POWER TRANSFORMER...** 12/6
 350-0-350 v. at 250 m.a. 6.3 v. at 5 amp., 4 v. at 4 amp., 4 v. at 7 amp., 4 v. centre tapped at 1 amp. Primary 200-250 v. 50 cycles. Drop through type. P. & P. 3/9.
- MAINS TRANSFORMER...** 5 9
 300-0-300 v. 80 m.a. 4 v. at 5 amp., 4 v. at 2 amp. Drop through type. Half shrouded. Prim. 200/250. P. & P. 3/9.
- MAINS TRANSFORMER...** 3 9
 350-0-350 v. 80 m.a. 4 v. at 5 amp., 4 v. at 5 amp. Prim. 200/250 v. Post 3/9.
- HEATER TRANSFORMER...** 1 9
 4 v. to 6 v. at 3 amp. Ideal auto trans. P. & P. 1/3. ...
- O.P. TRANSFORMER...** 1 3
 Std. ; size 2-5 ohms. P. & P. 1/-. 20 for £1. Post 3/6. ...
- VOLUME CONTROLS...** Dozen 2/6
 Mixed parcel of Volume and Tone controls from working chassis. P. & P. 2/-.

CO-AX. CABLE. 6d. yd. Good quality. Cut to any length. Post on 20 yds. 1/6. 45/- per 100 yds. Post 3/6.

COIL PACK SETS. 3 9. Including pair 465 L.F.S. 2-gang cond. 3 w/band. P. & P. 2/3.

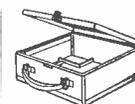PRESS BUTTON COIL PACK. 10/6. 3 w/band. F.M. and gram. Post 1/6.



STURDY CASES (Ideal Record Case) 12/6. Covered in burgundy and grey washable rexine. Size 8 1/2" x 7 1/2" x 3 1/2" deep. Strong clasp, hinges and carry handle. Ideal for Portable Radio Chassis or Transistor Case to hold eighteen 7 1/2" long-playing records. Post and packing 2/6.



219, ILFORD LANE, ILFORD, ESSEX

Stamp for Catalogue, FREE.

NOW!

UNBEATABLE PRICES

12 MONTHS GUARANTEE

ELECTROVAC

BRAND NEW GUN

CATHODE RAY TUBES

<ul style="list-style-type: none"> 12" Mullard Types ... £4 19 0 12" Mazda Types ... 6 5 6 12" Pentrid Types (3174) £4.19.00 ... 6 5 6 12" Brimar Types (C12FM) £4.19.00 ... 6 5 6 12" Emicope Types ... 7 1 0 12" Cossor Types ... 4 19 0 12" G.R.C. Types ... 6 5 6 12" Emitron Types ... 4 19 0 	<ul style="list-style-type: none"> 14" All Current Types. All prices as 12" tubes above. 15" All Current Types ... 8 2 0 16" All Current Types ... 9 3 0 17" Mullard, Mazda and Emitron Types ... 6 0 0 All other types ... 8 2 0 21" Mullard, Mazda, Pentrid, Brimar, Cossor and Emitron Types ... 9 13 0 All other types ... 13 6 0
--	--

Under the ELECTROVAC PROCESS, at our own 6,000 sq. ft. factory, all tubes are opened, the gun replaced with the latest type new English gun, the tube reassembled to the highest specifications AS NEW and a vacuum produced to give a performance and life of the highest standard. The above prices are for the most widely used types. EX STOCK. Prices for every current type available on request.


ELECTROVAC MANUFACTURING CO.
 (Dept. P.T.10) Chapel Works, Sunnyside Road, Chesham, Bucks.

GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

- METERS.** 0-1 mA, 2 1/2 in. diam., 2 1/2 v. each. 500-0-500 microamp. 3 1/2 in. diam. 37/6 each.
 - I.T.A. AERIALS.** New and Boxed. 2 element, 22/6. 5 element, 27/6. CO-AXIAL CABLE. 6d. per yd. AIR SPACED, 9d.
 - NIFE CELLS.** 3 x 2 1/2 x 1 1/2 in. Unused. 5/- 3a., 48/- doz.
 - GERMANIUM CRYSTAL DIODES.** 1-10/- per doz.
 - HEADPHONES.** Moving iron, low impedance. 6/- high. 9/- Balanced armature, low. 10/- high. 15/- Moving coil, low only. 10/- per pair.
 - VOLUME CONTROLS LONG SPINDLE MIDGET.** 10K to 2 Meg. Less switch. 3/- D.P. switch. 4/6.
 - CONDENSERS.** Twin Gang .0005 Standard 5/6. Midget. 6/6.
 - VENER SYNCHRONOUS A.C. MOTORS.** 200/250 v. for clocks, models, etc., 12/6 ea.
 - KEY SWITCHES.** D.P.C.O. each way. 2/6 ea.
 - RELAYS.** High speed. 1,000+1,000 ohms. plat. cont., 7/6.
 - SELENIUM RECTIFIERS.** 12 V. 1 amp. 5/-; 2 amp. 11/6; 4 amp. 15/- each.
 - VALVES.** All valves tested before despatch on MULLARDS latest ELECTRONIC TESTER.
- | | | | | |
|----------|----------|------------|-----------|-----------|
| 1L4 5/- | 6D2 6/- | 6X4 7/- | EASO 1/6 | EY51 5/- |
| 1T4 6/6 | 6F1 7/6 | 6X5 7/- | EABC80 | EY51 8/- |
| 1U4 6/- | 6F6 7/- | 8D2 4/6 | | P61 4/6 |
| 3A4 6/- | 6F9 7/6 | 9D2 5/- | EB41 7/6 | PEN45 7/6 |
| 5Z4 9/- | 6J5 6/- | 10F1 7/6 | EB91 5/6 | PEN46 7/6 |
| 4D1 4/- | 6J6 6/- | 12A6 7/6 | ECH42 8/- | SP41 4/- |
| 6AG5 5/- | 6J7 6/- | 12A7B 8/- | ECL80 9/- | SP61 4/- |
| 6AL5 5/- | 6K7 4/6 | 12A7H 8/- | ECF36 5/- | VR150/30 |
| 6AM5 5/- | 6L6 6/6 | 12AU7 7/- | EF50 3/6 | |
| 6AM6 6/- | 6SA7 6/- | 12AX7 7/- | EF50 5/- | UL84 9/- |
| 6AQ5 6/- | 6SCT 4/6 | 12BH7 10/- | EF97 9/- | VCR97 |
| 6AU6 7/- | 6SJ7 5/- | 12SH7 5/- | EF39 5/6 | |
| 6BA6 8/- | 6SK7 5/- | 12SJ7 6/6 | EF90 8/- | |
| 6BE6 5/6 | 6SL7 6/- | 12SK7 5/- | EF91 9/- | VCR138A |
| 6BH6 5/- | 6SN7 7/- | 15D2 6/- | EP92 7/- | 25/- |
| 6BW6 6/6 | 6SU5 6/6 | 50C5 10/- | EL32 5/- | VCR139A |
| 6C4 5/- | 6V6 6/6 | 807 6/- | EL91 5/6 | 25/- |

OBSOLETE TYPES. LARGE STOCKS. ENQUIRIES INVITED.
SECONDHAND VALVES. YOUR CHOICE. £1.0.0 for EIGHT
 PL81, ECL80, 6C4, 6AM6, 8AG5, 6J6, EF50, 6BE6, 3A4, PCF80, EF90, SP61, P61, 6J5, PY80, PY82, PC64, Z77, 6AL5, 6K7, 6SJ7, EL32, EF42, 6D2.

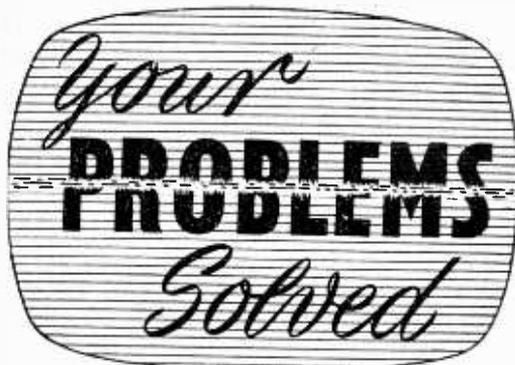HUGGETT'S LIMITED
 2-4 PAWSONS ROAD, WEST CROYDON



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 49 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

PYE V14

There is a 1in. gap all round the picture, although I have improved this by adjusting the width plug to the maximum. When switching the set on, there is no line lock, but by turning contrast to maximum then back to normal, the picture locks. Adjusting the picture vertically only results in cramping on foldover at the top. Could this be low H.T. volts as both line and frame are affected although frame locks perfectly?—B. Canter (Footing, S.W.17).

The metal rectifier, contact cooled type 14-RA-1282 should be replaced. If the poor line lock continues, replace the top centre PCF80.

FERGUSON 3081

The sound is all right but the picture is very dark on both ITV and BBC. I have replaced valves PCF80, PL81, PY81 and EY86, also H.T. rectifier. With the gain control full on and increasing brilliance control picture goes negative, but does not get any brighter.—C. P. Johns (Sheerness).

The tube appears to have lost emission. However, the rear focus cone should be removed and the ion-trap magnet on the tube neck adjusted for maximum brilliance. Check the 220k Ω feed resistor to pin 10 of the C.R.T. base and the .01 μ F decoupling capacitor, also 10k Ω anode resistor (pin 6) of the PCF80 video amplifier.

FERRANTI T1205

There is a bright $\frac{1}{2}$ in. vertical bar at the left of the picture with a gradual darkening of the picture towards the right hand side. Thus, if the right hand side of the picture is visible the left hand side is far too bright. All capacitors and EL38 in the line timebase have been checked by substitution and also resistors (except the two pots). The line lock is O.K. and little non-linearity of the trace is apparent except the bright bar at the left hand side.—F. B. Pemberton (Cheshire).

The 560k Ω resistor which feeds the EL38 suppressor grid does not connect the H.T. as may be thought. It is connected to the brilliance control and if the grid of the tube is not properly decoupled, the grid will be modulated at line frequency. The 0.1 μ F capacitor wired from the feed to pin 5 of the C.R.T. to H.T. should, therefore, be replaced.

Quite apart from this we would direct your attention to the 120k Ω 2W resistor situated at the top of the line output transformer which is a common cause of timebase trouble.

DEFIANT TABLE MODEL TR1756T

For about the last year I have been having trouble with picture size. After about an hour's running figures on the screen become elongated and the raster widens into thick lines, after which, if I don't switch off, the picture seems to move up from the bottom of the screen. It begins to black out until I am left with a line of light about an inch wide across the centre of the screen. The sound is perfect.—F. Hurley (Liverpool).

You should replace the front left side ECL80 valve (as viewed from the rear). This is the frame output valve and the symptoms given describe the effect of loss of emission in this.

VIEWMASTER

My set has been in use now for almost nine years, with the original C.R. tube, a Mullard MW31/17, still in good order. On switching on, sound is normal, but line and frame hold controls must be adjusted to get a picture. After about ten minutes the picture fades slightly (gradually) and starts to slip, needing readjustment of both sync controls. After about an hour picture brightness returns to normal, but during a viewing period occasional adjustments to sync controls are necessary to hold the picture.

This happens each time the set is used, picture quality seems about normal, but frame and line holds are very sensitive and need to be readjusted occasionally to resolve picture. I have checked valves by substitution and also tried realignment, but no improvement. These symptoms have developed gradually during the last 12 months.—H. E. Tonkin (Yatton).

There may be several causes for the poor synchronising you now experience. We suggest replacing R21 and C18; also checking, and if necessary replacing, R70 and C55. Also check that the alignment of the vision receiver is as specified.

COSSOR MODEL 932

This set uses a Mullard MW31/74 tube (round). When the set is first switched on, the picture appears, but the vertical edges do not fill out and have a wavy appearance. This gradually fills out as the set warms up. The tube is certainly on the low side, and is boosted. I tried a new tube at one time and the effect stayed at all times, never filling out, whilst the wavy edge just kept changing shape all the time. With the new tube there was pronounced fold over with a light star-shaped impression from corner to corner across the screen. The EY81 is new and I tried a new PL81 and PY81, but these had no effect.

I should also like to replace the present tube with a 14in. rectangular tube. What components, if any, would have to be changed to make this possible?—J. Running (Aberdeen).

The wavy edge on your screen is due to glass charges on the tube and is present to some extent on all the Mullard 12in. tubes. A remedy which sometimes works is to clean the screen with an anti-static paste, allowing as long as possible between its application and removal.

The substitution of a 14in. tube into your set presents the problem of scanning power, as we doubt if the 932 will be capable of providing enough width for a 14in. tube.

EKCO T216

This set is five years old; I have fitted a transformer for boosting the tube, and have now got a good picture. Now I would like to fit a converter or turret tuner. Could you please suggest a suitable one which would be simple and easy to fit (for channels 5 and 10)?—G. Corbin (Newport, Mon).

You may either use the Cyldon U16H or the Brayhead 16S with 16BA4 converter (if you use the latter ask for it to be supplied with UCC84 and UCF80). They both plug in to the holders of the first two valves in the set, but are both rather large for inclusion in the receiver cabinet. They will go in but you may be better advised to purchase the external mounting type in its own box.

PYE CONTINENTAL

Some time ago, the picture started to close, a broad black line shows at the bottom of the screen, and a narrower line at the top and sides. I have renewed the PCL82 frame output valve, with no improvement. The picture also, whilst being very steady, is losing definition, and appears "hazy" except in close up. I also notice, at times, the picture and sound "dim" together, and there is a noticeable mains hum present.—E. J. Webber (Fulham, S.W.6).

The metal rectifier may easily be the cause of your trouble, as other readers have experienced similar failures. Our own remedy is to use an Automat TV5 metal rectifier. This needs mounting on top of the EHT unit on a strip metal bracket.

COSSOR 937

After the set has been working for some time noise somewhat like a motor cycle develops. It continues on and off for lengthy periods, but I can get rid of it by switching either over to channel 4 or channel 2 and back again. Can you please tell me where the trouble lies?—S. H. Hewings (Norwich).

This is usually caused by a faulty decoupling capacitor (.001 μ F) associated with the sound I.F. stages. These are the two 6BX6 valve stages at the rear of the R.F. unit. The capacitors are wired from pin 8 to chassis in each case. The valves may also be suspected.

FERGUSON T103

I have not been able to obtain EHT. I have renewed the line output transformer, PY81 and

PL81, also EY51 but cannot hear any whistle at all. All the valves light up except EY51. I have tried spark tests. Could the trouble lie in the oscillator can?—I. Bevan (Rhondda).

If there is no whistle at all, not even a faint one, check the two EF80 valves on the left side of the chassis. If both are in order, check the 4.7k Ω 2W resistor connected to pin 8 of the PL81. The line output transformer may then be suspected.

PHILIPS 1115U

I would be very pleased if you could help me with a fault which has appeared on my set. After it has been on for about 30 minutes a series of white lines appear, covering the bottom inch of the screen. After a while these change to a black band blotting out that part of the picture.—W. Hiron (Tipton, Staffs).

The PL82 frame output valve on the front left side chassis is to be suspected, then the ECL80 to its rear. The capacitors associated with the PL82 should be checked if the fault remains.

SOBELL T347

My trouble is lack of brightness with the control fully turned up. On looking at the back of receiver I find the voltage selector flange wrongly set at 230V, the voltage in this district being 240. This was set by the supplier 18 months ago.

I would also welcome instructions regarding removal of the chassis from the cabinet, together with methods of making condensers safe to handle.

Could you tell me whether it is possible to replace the EY51 without removing chassis?—Wm. Hunter (Lydiate).

Lack of brilliance can be due to low EHT, in which case the EY51 could well be responsible. We also suggest you check the voltage on the grid of the C.R.T. It should read 0-110V, dependent upon the setting of the brilliance control. If, however, with control at maximum, the voltage is not about 75 volts, this could then suggest that your C.R.T. is suffering from low emission.

The fact that your mains voltage is 240V and the tapping is for 230V should not be detrimental in any way.

To remove the chassis, remove mains plug—back and front control knobs, side escutcheon, inspection panel and speaker leads. Finally, remove the four chassis bolts and the chassis can then be withdrawn. Normally, on switching off a receiver, the electrolytic condensers discharge through the circuit.

Before touching EHT components, short circuit them to earth.

It is possible to replace the EY51 without removing set from the cabinet. Remove screening can and lay the set on its side: the tags can then be soldered, making good, rounded joints.

REGENTONE "BIG 12"

I cannot obtain sharp focus on this set. There seems to be no medium between white and black and at its best the focus is poor (for example, one

(Continued on page 49)

A television course for you to study at home

*Entirely new! Practical!
Bang up to date!*

THE FAMOUS BENNETT COLLEGE OFFERS YOU THIS

An entirely new course of study based upon up-to-date techniques has now been prepared by The Bennett College.

The course is non-mathematical, and contains numerous clear diagrams, starting from the very beginning (even including the basic principles of sound radio receivers, if desired) and covering all the relevant knowledge that you need to know!

This is what you've been looking for! You can now gain thorough knowledge of this vast subject in your spare time at home. The course includes: production of the signal,

scanning and reproduction of picture from signal. Aerials, types and purpose. The cathode ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret, incremental, etc. Television test gear. Television faults.

For more details, fill in the coupon below. Your studies cost you very little, the book you need is included in the cost.

To THE BENNETT COLLEGE
(DEPARTMENT K55TV) SHEFFIELD

*Please send me details of the new
Television Servicing Course*

NAME _____

ADDRESS _____

AGE _____

VALVES

SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS		1R5, 1S5, 1T3, 3S4, 5V4, DAF91, DF91, DK91, DK92, DL92, DL94, any 4 for 27/6		DAF96, DF96, DK96, DL96 4 for 32/6		8K7G, 6K7G, 6Q7G, 6V6G, 6X5G or 5Y3G 5 for 27/-					
1A7GT	14/6	GL18	12/3	25Z6GT	9/6	EBF89	8/9	EZ60	7/6	TH41	16/6
1I5	9/6	6P25	10/-	30C1	8/-	EBL21	20/6	EZ81	7/6	U25	12/6
1H5GT	10/-	6Q7G	7/6	30L1	8/-	ECC81	8/-	FW4 500	9/6	U26	12/6
1V8GT	10/-	6Q7GT	9/6	35L6GT	10/-	ECC82	6/6	GZ32	9/-	U50	7/6
1H5	7/6	(S1,7GT	7/6	35Z4GT	8/6	FCC83	8/6	KT33C	7/-	U52	6/6
1B4	9/-	6SN7GT	5/6	35Z5GT	8/6	ECC84	9/6	KT41	14/6	U76	6/6
1B5	7/6	6U4GT	11/-	43	12/6	ECC85	9/6	KT61	10/-	U78	6/6
1T4	6/3	6V6G	8/-	50CD8G	26/9	ECF80	11/6	KT63	6/6	UABC80	9/-
1U5	8/6	6V6GT	7/6	50L6GT	9/9	ECF82	11/6	KT71	12/6	UAF42	9/6
3A5	10/6	6X4	8/6	AZ31	9/8	ECH21	17/6	MH4	8/-	UBC41	8/6
3Q4	8/6	6X5GT	6/-	B36	15/6	ECH35	6/9	MU14	9/-	UBF80	9/6
3B4	7/6	7B7	8/-	CL33	11/6	ECH42	9/6	MX40	12/6	UBF89	9/6
3V4	8/-	7C5	8/-	DAC32	10/-	(ECH81	8/6	N18	8/6	UBL21	20/6
5U4G	8/6	7C8	8/-	DAF91	7/6	ECL80	9/6	N152	11/6	UCC84	12/9
5V4G	11/-	7F7	8/-	DAF96	9/6	ECJ82	11/6	PCC84	8/-	UCC85	9/-
5Y3GT	7/6	7S7	9/9	DC900	10/6	EP39	5/6	PCC89	14/-	UCF80	14/-
5Z4G	9/6	7Y4	8/-	DF33	10/-	EF41	9/6	PCF80	8/-	UCH21	20/6
6AL5	5/6	10C1	14/6	DF91	6/3	EF42	11/6	PCF82	10/6	UCH42	9/-
6AM5	5/-	10C2	17/6	DF96	8/6	EP80	6/6	PCL82	10/6	UCH81	9/-
6AM6	4/9	10P1	17/6	DH76	6/6	EP85	7/6	PCL83	12/6	UCL82	11/6
6AQ5	7/-	10F9	10/6	DI77	7/3	EP88	11/6	PCL84	11/6	UCL83	14/3
6AT6	7/3	10P13	15/9	DK32	14/6	EP89	8/-	PENA1	11/-	UF41	9/3
6BA6	7/6	12A8H	10/6	DK40	14/-	EP91	4/9	PEN3C	9/6	UF42	8/6
6BE6	7/-	12A7T	8/6	DK91	7/6	EP92	5/-	PEN45	8/-	UF89	7/6
6BH6	8/-	12A7U	6/6	DK92	8/6	EL33	10/-	PEN46	5/6	UL41	8/-
6BJ6	6/6	12Z3	7/6	DL96	8/6	EL36	21/6	PL36	13/-	UL44	21/6
6BR7	10/6	12BA6	8/-	DL33	9/-	EL41	9/-	PL38	21/6	UL84	8/6
6BW7	6/6	12K7GT	6/6	DL35	12/3	EL42	10/6	PL81	11/6	URIC	9/6
6CD6G	26/9	12K8GT	12/6	DL92	7/6	EL84	8/6	PL82	8/6	UY1N	12/6
6F1	14/6	12Q7GT	8/6	DL94	8/-	EM34	8/6	PL83	9/6	UY21	14/-
6F8G	6/6	12Z3	7/6	DL96	8/6	EM80	9/6	PY32	12/6	UY41	7/-
6F13	12/6	14S7	14/9	EABC80	9/9	EM81	9/6	PY80	7/6	VP4B	9/6
6F14	17/6	19AQ5	7/6	EAFA2	9/6	EM84	10/-	PY81	7/6	VP4B	9/6
6K7G	3/9	20F2	17/6	EB91	5/6	EY51	9/6	PY82	8/-	VP41	6/6
6K7GT	6/-	20L1	17/6	EB93	7/-	EY86	9/-	PY83	8/6	W76	6/6
6K8G	6/9	25A6G	11/-	EB94	8/6	EZ40	7/6	PZ30	17/-	W77	5/-
6L1	16/8	25Z4G	9/-	EBF80	8/9	EZ41	7/6	PE61	3/6	Z77	4/9

SUPER-VISION LIMITED

Every Item Brand New and Guaranteed at Low Prices

- VALVE HOLDERS**
Int. Octal 4d. each. B7G 4d. each. B9A 6d. each. CER. B9A with screen 1/9 each.
- CONDENSERS**
2 to 100 pF., 5d. each. 220-5,000 pF., 7d. each. .01 to .1, 8d. each.
- RESISTANCES**
Variable T.V. type pots. 3K, 5K, 25K and 1M, 2 6 each.
- REGEN SLIDER TYPE**
3K, 5K and 25K, 1/9 each.
- VOLTA ME CONTROLS**
.5M, 2/9 each. .5M with DPS switch, 4/3 each.
- ELECTROLYTICS**
60/160 mfd., 5.6 each. 32+32+16 mfd., 35v., 3/6 each.
- AUTO TRANSFORMERS**
50 w. to 1,000 w., from £1.10.0 to £9.0.0.
- D.C. A.C. CONVERTERS** for operating shavers, radio and tape recorders from 6 and 12 v. car batteries.
6 v. D.C. - 230 v. A.C. 20 w. shaver converter, £2.15.0.
6 v. D.C. - 230 v. A.C. 30 w. converter for radio, etc., £4.5.0.
12 v. D.C. - 230 v. A.C. 20 w. shaver converter, £3.18.0.
12 v. D.C. - 230 v. A.C. 40 w. converter for radio, etc., £6.10.0.
12 v. D.C. - 230 v. A.C. 80 w. converter for tape recorder, £12.15.0.
- Other types available. Send for List. Please include sufficient to cover Postage.*

SUPER-VISION LIMITED
136, High Street, Teddington, Middlesex. KINGSTON 4393.

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

Postage 6d. per valve extra; Any Parcel insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 2/6 extra.

EDDY'S (Nottm.) LTD.

DEPT. P.T.

172 ALFRETON ROAD
NOTTINGHAM

LUXEMBOURG EXPANDING AERIALS.—Compact and Easy to Fit. No technical knowledge required. Greatly improves reception, 3/11. Post 6d.

NIFE ACCUMULATORS.—Midget Single Unit Size 3 x 2 3/4 x 1/2 in., 1/11 ea. Post 1/6.

DIMMER SWITCHES.—Ideal for Train Speed Regulators, 1/11. Post 6d.

PLASTIC CASE.—Suitable for Transistor Portables. Size 6 x 3 1/2 x 1 1/2 in. Attractive Black and White, 3/11. Post 1/-.

THROAT MIKES, 1/- each. Could be used for electrifying musical instruments. Post 6d.

NEON MAINS TESTER/SCREW-DRIVERS, 4/6 each. Post 6d.

GERMANIUM CRYSTAL DIODES, 1/- each. 10/- doz. Post 4d.

MORSE TAPPERS.—Plated contacts Adjustable Gaps Heavy Duty, 3/6. Post 9d.

JACK PLUGS.—Standard Type, 1/11 each. 3 for 5/6. Post 6d.

RECTIFIERS.—Contacts Cooled 250 v. 60 mA., 8/6. RM1. 4/9. RM2. 4/6. RM3. 7/6. RM4. 15/6. RMS. 19/6. Post 1/-.

CONDENSERS.—Tubular Wire End (not Ex. Govt.), 8 mfd. 450 v., 1/9. 8-8 450 v. 2/9. 16 mfd., 2/9. 16-8 450 v., 4/-. 16-16 450 v., 3/9. 32 mfd. 450 v., 3/9. 32-32 350 v. 4/-. Post 9d.

CONDENSERS.—Tubular Wire End Midget 25 x 25. 1/3. 50 x 50. 1/9. Post 6d.

VIBRATORS.—12 v. 4-pin, 4/11. Post 1/-.

DYNAMOTORS.—200 v. D.C. to 12 v. D.C. Ideal for Train Sets. 19/11. Post 2/6.

ACOS CRYSTAL TURNOVER PICK-UPS (2 sapphire styli), 29/11. Post 2/6.

AUDIOTORS.—A. F. (Audio), 5/11. R.F. Yellow/Red Spot, 13/11. Post 4d.

TRANSISTOR SUB MINIATURE CONDENSERS.—1.6 mfd. 5 mfd., 8 mfd., 16 mfd., 15 mfd., 32 mfd., 2/6 each. Post 6d.

ACOS CRYSTAL MIKES.—Type MIC. 35/1. 25/11. Post 2/6.

All above are new and guaranteed.

New and Surplus Guaranteed Valves

1D5	9/6	12AT6	9/-	ECC85	8/6
1R5	7/-	25L6GT	9/6	ECC80	11/-
1S5	6/6	25Z4GT	8/-	ECH42	9/-
1L4	3/9	35L6GT	9/6	EF36	2/6
1T4	5/3	35V4	7/6	EF37	4/6
3Q5	7/6	80	8/-	EF40	13/6
3Q5GT	9/-	11F42	8/6	EF41	8/9
5U4	6/6	90AY	4/6	EF42	9/6
6AG5	5/-	807(B)	3/9	EF85	7/-
6AL5	4/6	807(US)	5/9	EF86	13/6
6AM6	4/-	954	1/6	EF91	4/6
6B8G	2/11	955	3/11	EL41	9/6
6BA6	6/6	956	2/11	EL42	9/6
6Bj6	7/6	9001	4/6	Z77	4/6
6C4	4/-	9003	4/-	EL84	9/6
6C46	10/6	9006	4/-	EL85	9/6
6F6M	7/6	AZ31	9/-	EY86	9/6
6F33	6/3	B36	9/6	GTIC	7/6
6F15	9/-	DAF96	8/3	KTW61	6/6
UCH42	9/-	DH63	8/6	MU14	8/6
6J5G	2/9	DH77	8/-	PCC84	8/6
6J5GT	3/6	DK92	9/6	PCF80	8/6
6K7G	2/6	DK96	8/6	PEN45	5/6
6K8G	6/6	DL96	8/6	PL33	8/6
6P2B	9/6	DF96	8/6	PL81	13/6
6Q7G	8/3	DM70	7/-	PL82	8/-
6SA7M	7/-	Z66	8/-	PL83	9/-
6SG7M	5/6	EB41	7/6	PY80	8/6
6SN7GT	3/9	EB91	4/6	PY81	8/6
6V6G	5/11	ECC81	6/-	PY82	8/6
6V6GT	6/-	ECC82	7/-	PZ30	9/6
6X5GT	6/6	ECC83	8/-	U35	9/6
12AH7	5/6	ECC84	9/-	UBC41	8/6

All parcels insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers risk. C.W.O. or C.O.D. only. Postage 6d. per valve extra. Over £3 Free. S.A.E. with all enquiries.

TELEVISION SERVICING HANDBOOK

A practical guide to television receiver fault-tracing, alignment, adjustment and repair, for the service engineer, amateur and student, with chapters on aerials and Band III conversion.

By Gordon J. King.

30/- Postage 1/3.

OSCILLOSCOPE TECHNIQUES, by A. Haas, 23/- Postage 1/-.

TV FAULT FINDING, a Data Pub., 5/- Postage 6d.

BASIC ELECTRONICS, 6 vols., 63/- complete. Postage 2/-.

A BEGINNER'S GUIDE TO TELEVISION, by F. J. Camm, 7/6. Postage 6d

BRIMAR VALVE AND TELETYPE MANUAL, No. 8, 6/- Postage 9d.

RADIO VALVE DATA, 6th Ed. Compiled by "WW," 5/- Postage 9d.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

THE MODERN BOOK CO.

19-23 PRAED STREET,
LONDON, W.2.

Complete catalogue 6d.

Phone : PADdington 4185.

Open 6 days 9-6 p.m.

FIRST-CLASS TELEVISION and RADIO COURSES . .

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A. M. I. Mech. E., Draughtsmanship (all branches),** etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES—

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne.

54 Gns.—'17'



A full specification 17in. Television Receiver to Spencer-West standards now available at your Dealers. Remarkable performance and priced at **54 Gns. only, complete.**

For Leaflet apply to—

SPENCER-WEST LTD.
Quay Works, Great Yarmouth
Norfolk

Phone : Sales 4908/9

Grams : Spencer-West, Great Yarmouth

B.B.C.—I.T.V.—F.M. AERIALS

B.B.C. (BAND 1). Telescopic loft. 19/6. External. S/D. 26/3.

I.T.V. (BAND 3). 3 Element loft array. 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 49/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element 63/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H", 28/-, 3 Element loft, 52/6. S/D loft, 12/6. External S/D, 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plus, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. T.P.)
3B, Godstone Road, Kenley, Surrey

RES/CAP. BRIDGE 37/-

p. & p. 2/-
Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading **READY CALIBRATED**
Stamp for details of this and other kits.
RADIO MAIL (Dept. VQ)
Raleigh Mews, Raleigh Street, Nottingham

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

Rewinds to all makes.
H.W. FORREST (Transformers) Ltd.
Shirley, Solihull, Warwickshire
Tel. : SHIRley 2483

cannot read small print on the screen). Also, after operating for about 30 minutes, the picture suddenly becomes very bright, although this can be adjusted by the brightness control. I have just renewed the EL38 and the EY51 and also the resistor R68. The metal rectifier, which was 14A100, has been replaced by 14A86. Do you think this will be suitable for any length of time?—S. Berry (Chorley).

The voltage applied to a 14A86 should not exceed 250, and as a higher voltage is applied to the "Big 12" the life of the 14A86 may be curtailed.

We advise you to check the video amplifier stage components, resistors, etc., adjust the focus magnet gantry for optimum focus and then suspect the tube itself.

FERGUSON 992

This set has been converted to I.T.A. with the maker's own converter, type "A." The BBC is perfect but I cannot get sound or vision on I.T.A. When a probe is placed on L2 of the converter heavy "mush" results on sound and vision. There is no response whatever when tuning pedals are pressed. All valves have been checked by substitution. The gain control is in order but valve voltages are not stated on the service sheet. Is it possible that the oscillator is not working? When the switch on the converter is turned, usually loud clicks and flashes on the screen are evident.—F. Johnson (London, S.W.6).

It would appear that the oscillator stage is not working although defective aerial or aerial plug could give rise to similar symptoms. We mention this since the probe at L2 does promote "mush." The suspects are the 8.2k triode anode feed receiver, its 800pF decoupling capacitor and the grid components. Upon inspection it may be found that the 8.2k resistor is overheating owing to the capacitor having developed a short circuit.

DEFIANT TR1252/TA

The tube is soft, and I am going to replace it with a new one, but could you tell me if it will take a larger tube? Will it take a turret tuner, or will it need one that runs off the mains, for converting to I.T.A. channel and BBC channel?—R. E. Perrett (Peterlee).

Although the CRM152a 15in. is strictly speaking a wide-angle tube, the deflection angle is only 67 deg. and the existing scanning circuits should be able to fill it. A duodecal base is required. A turret tuner can be used and the Cyldon U10L or Brayhead 10s (with "U" series valves) is recommended.

PHILIPS PROJECTION TG1800A/15

The picture has collapsed to a thin line across the screen. I cannot get height by adjusting the height or frame hold controls. What valve or component do you advise checking or replacing in the frame section? I have no service sheet for this receiver.—L. Blackburn (Oldham).

The first component we would advise you to

check is the frame blocking oscillator transformer. This is a small black component with four tags, secured by two screws under the rear centre of the chassis. Check the continuity of each pair of tags: normally, one winding will be found open circuited. The thin line should not be observed on the screen unless the protection circuit is inoperative or the frame scanning coils are disconnected or defective. We presume, therefore, you have observed the line on the face of the actual tube.

C.R.T. BOOSTING

I wish to boost my C.R.T. The set is a Corsor 932 and the tube a Mullard MW31/74.—W. Smeson (Donnington, Salop).

We would make one point clear before dealing with your query, it is that the M.W. 31/74 should not have excessive boost applied to its heater as this will almost certainly result in complete loss of emission. To moderately boost the heater, wire a 5k Ω 10W resistor from the live fuse to pin 1 or 12 of the tube base socket, whichever causes the heater to glow more intensely.

KOLSTER-BRANDES FV40

There is no picture, though the sound is in order. Valve EY51 will light up only when the width plug is left out. Then I get only a line from top to bottom of the screen and this line is broken in two places. I can then draw about a 1/2 in. spark from the anode of EY51 with a screwdriver. I have a service sheet for this receiver.—H. Gass (Nottingham).

First check the 0.25 μ F capacitor wired from the boosted H.T. line to the 5V4 anodes. If this is in order, a short could be present in the line scanning coils or the line output transformer could have shorted turns.

BUSH TV24

The picture keeps on rolling downwards. When I do get it to lock the vertical hold control is fully anti-clockwise. I replaced the first ECL80 and the PZ30. It stayed all right for a week and then started rolling again and sometimes it is hours before I can get it to relock.—S. Brett (London, E.17).

There are a number of resistors connected with the frame hold control. Check the 680k (blue-grey-yellow) feed resistor which has probably "gone high." If this restores the optimum position to approximately the centre but the sync is weak (no positive lock) check the WX6 interlace rectifier (small red and black rectifier).

QUERIES COUPON

This coupon is available until OCTOBER 22nd, 1959, and must accompany all Queries sent in accord with the notice on page 45.

PRACTICAL TELEVISION, OCTOBER 1959.

SETS & COMPONENTS

MAKE YOUR OWN AERIALS with our fully machined parts. Example: full kit of ready to assemble parts for 5-element array, plus 3ft. mast and universal clip. 35/-. post paid. Get our full lists and Aerial Data Chart for 1/- postal order. SKYLINE WORKS, Burnhall Rd., Coventry.

T.V. TUBES. rebuilt. 12in.. £6; 14in. and 17in.. £7; 6 months' guarantee. Send for list. Dealers supplied. Aerials and Co-ax. cheap. H. CLAYTON & CO., 1, High St., Chalvey, Stough. (Tel.: 21860.)

H.M.V. 151N. English Electric 15in.. Ultra. etc.. Televisions not working. originally £175 each. £5/10/-. TOMLINS, 127, Brockley Rise, Forest Hill. S.E.23.

SALVAGED VALVES

All at 2/6 each

EF91	U31	10F1
DH77	VP4B	B36
Z77	ECC81	KT33C
EB91	EF90	KT36
	6P28	& Many Others

Minimum Order 5l. S.A.E. for List. All Valves Tested on Mullard High Speed Valve Tester. C.W.O. to—
ARION TELEVISION, 4 Macted Rd., S.E.15.

THOUSANDS OF SPARES : Transformers. Coils. Valves. Tubes. cheap. from dismantled radio, television sets. 1938-1958. We may have what you need. 9-19in. Projection Tubes. 30/-; 13-14in.. £3/10/-; 17in.. £5. All picture tested! EF80. EF91. EB91. 3/6. Obsolete sets our speciality. Write, phone, call. "ST. JOHN'S RADIO," 156, St. John's Hill, S.W.11. (BAttersea 9838.)

WE HAVE large Stocks of pretty well all TV Components, Valves and Tubes, at much lower than standard prices, especially for old type receivers. CUTTRISS LIMITED, Birmingham. 1.

VALVE KITS.—One of each type for your set; reclaimed but guaranteed. Standard Kits from 50/-, including post and packing. Quote make and model No. T.C.S. LTD., 28, Brockley Cross. S.E.4. (TIDeway 5394.)

CALLING 9in. Television owners. Brand new, factory fresh. 9in. Ferranti Tubes, originally £14/10/-, will replace Mazda, Brimar, G.E.C., etc. £4/10/- each. 6 months' guarantee. TOMLINS, 127, Brockley Rise, Forest Hill. S.E.23.

YOUR GUARANTEE TO CHEAPER VIEWING

Renfrew Electronics, Anderson Drive, Renfrew.
Phone Number REN 2642

17" Mazda Tube with new American Gun-mount	£7.15.0
14" Mazda Tube with new American Gun-mount	£6.10.0
17" Mullard Tube with new American Gun-mount	£7.15.0
14" Mullard Tube with new American Gun-mount	£6.10.0
For the First Time available from us:	
17" Mullard Tube with new Mullard Gun-mount	£8. 5.0
14" Mullard Tube with new Mullard Gun-mount	£7. 5.0

One Year's Guarantee.
Cash with Order; 7/6 allowed on old tube returned in carton supplied. Dealers' Inquiries invited.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

SETS & COMPONENTS (continued)

NEW TUBES

2 years' guarantee.

12in. Type M.W. ...	£10.10.0
14in. Type M.W. ...	£10.10.0
17in. Type M.W. ...	£12. 0.0

All Brimar, Mazda, Mullard, etc. equivs. Carriage 5/-.

LINE OUTPUT TRANSFORMERS

Direct replacements for 500 sets. State Make and Model No. S.A.E. with enquiries, please.

WESTWAY RADIO

5, Westward Way, Harrow, Middlesex.

RECLAIMED VALVES. tested and perfect. Huge stocks. Any type, price 5/- plus 6d. postage each; delivery by return. LEWIS, Chalford Walk, Woodford Green, Essex.

GUARANTEED VALVES.—Send s.a.e. for list. EY51. ECL80. PZ30. 10/6; EF80. ECH35. 10P1. EF41. 7/6; many others available. HALSEY ELECTRONICS, 1 and 2, Old Holmsdale Rd., Bromley, Kent.

RENTAL TV.S—Special offer: full 13-channel 14in. TV.S (working or with slight faults) from £15. Other bargains: TV.S working or non-working 5 or 13 channels. from 12in. £4/10/-, 14in. £8. 15in. £10. TELEVIEW, 3, Griffin St., Blackburn, Lancs. (Tel.: Blakewater 42157.)

TELEVISION TUBES

NEW TV TUBES SIX Months' Guarantee

9" T93 T9 5	£ 5. 0. 0
10" 108K 75K	£ 3. 10. 0
12" T 12/44 T 12/51	£ 4. 10. 0

NEW TV TUBES, TWELVE Months' Guarantee

12" MW 31/74 MW 31/16	£ 7. 10. 0
14" MW 36/24 14 KP 4A	£ 8. 0. 0
14" AW 36 21	£ 8. 0. 0
17" MW 43 64 172 K	£ 9. 0. 0
17" MW 49/80	£ 10. 0. 0
21" MW 53 20 MW 53/80	£ 15. 0. 0

FULLY Rebuilt TV Tubes, TWELVE Months' Guarantee

12" MW 31/74 CRM 121	£ 5. 0. 0
14" MW 36 21 CRM 141	£ 5. 10. 0
14" AW 36/21 CRM 142	£ 5. 15. 0
17" MW 43 64 CRM 171	£ 6. 10. 0
17" MW 43 60 CRM 172	£ 6. 15. 0
17" MW 43 80 CRM 173	£ 6. 15. 0
21" MW 53 20 CRM 211	£ 8. 15. 0
21" MW 53 80 CRM 212	£ 8. 15. 0
15" CRM 153 CRM 152	£ 6. 10. 0

Collor Conquest 4-speed changer... £6 10 0
BSR Monarch UA8 4-speed changer £6 10 0
PILOT "Clipper" VHF FM AM listed at £24. Our price £15 0 0
PILOT "Caprice" VHF/FM listed at £21. Our price £12 10 0
Carriage for each item 10/-

CATHODE RAY TUBE SERVICE
35, Broomwood Road, St. Paul's Cray, Orpington 21285

SETS & COMPONENTS (continued)

AERIALS AT TRADE PRICES
For Example: DOUBLE FIVE ARRAY COSTS ONLY 70/-

Band III Self-contained Pre-Amplifiers Only 60/-. Band II Converters, 100/-, Turret Tuners, 94/-. Complete Rebuilt T.V. Tubes from £5. Revacuumed ones, All Sizes, £2, 10.0. All Tubes are Guaranteed. Super Low-Loss Coaxial Cable, 111 yd. Standard, 6d. yd. Diplexes, 5/- each. S.A.E. FOR FULL LISTS.
G. A. STRANGE, Broadfield, North Wrexham, Nr. Chippenhain, Wilts. Tel.: Marshfield 236.

VALVES, second-hand but tested, any type 5/- each or 48/- per doz. assorted, any three of your choice included, cash with order. BURCHILL, MORGAN, 54, Wells Road, Bristol. 4.

BREAKING HUNDREDS OF TV.S for Spares. L.O.P. from £1. Scanning Coils from 15/-. Valves from 2/6, complete Chassis from 25/-. No lists. Send requirements for immediate attention. T.C.S. LTD., 28, Brockley Cross. S.E.4. (TIDeway 5394.)

FIX IT YOURSELF AERIALS! Pre-Assembled Ready for Fitting. No Tech. Gen. required. Loft 3E1 24", Wall 5E1, 8E, Clip On SEL 2E1, 40", Indoor B.B.C./I.T.V. 16E, Dipole + 5E1 + Chimney Kit, 73", Double 5 array, 72/6. Fringe Area Super Low Loss Co-axial, 1/3 yd. Standard Low Loss, 71d. yd. Diplexes, 12/6. (B.A.H.E.A.) TUBES FOR ANY area. Will convert over 600 models. 137E. Plug In Adaptor, 3/- extra. State model + Channel. ALL ITEMS CARRIAGE PAID C.W.O. S.A.E. for Aerial List. Enquiries invited for full range of T.V., Radio, Valves and Spares.

HAVE SUPPLIES, 34, PRINCE ST., BRISTOL (Dept. P.T.).

600 BARGAINS. Send stamped addressed envelope for free list. W. A. BENSON, 136, Rathbone Rd., Liverpool, 15.

VALVES (secondhand): PL81, PY82, PY81, PCF80, PCC84, ECL80 and Tubes. Please send s.a.e. for lists. to D.E.S., 63, Dockar Rd., Northfield, Birmingham, 31.

BUILD YOUR OWN STEREO. With our full kit of parts and simple instructions, 4 valves, 3 1/2 watts. Send stamp for details of this and other quality kits. We operate an efficient mail order service for TV, and Radio Components. R. J. HULBERT, 211, Gander Green Lane, Cheam, Surrey.

REBUILD TUBES.—Every tube fitted new gun. All sizes Mazda and Mullard. 12in. £4/10/-; 14in. £5. 15in. £5/10/-; 17in. £6. 21in. £8; 10/- carriage; free delivery London. Guaranteed 1 year. Revacuumed (R.F. fired) Tubes available at £1 each. C. R. T. REBUILDS, 165, West St., Erith, Kent. (Erith 4095.)

NEW TUBES WITH ONE YEAR'S GUARANTEE

12in.. £7.10.0; 14in.. £8.15.0; 15in.. £9.10.0; 17in.. £10.10.0; 21in.. £13.0.0. All prices include carriage and insurance. All orders despatched by passenger train within 24 hours of receipt of order. Scanning components for nearly all makes supplied.

S.A.E. all enquiries please.

KIRK GATE RADIO,
82 Kirkgate, Huddersfield.

PHILIPS PROJECTION CHASSIS, complete with optical unit as specified for closed-circuit colour T.V. system. £10. HABGOOD, Elm Grove, Cirencester, Glos.

SETS & COMPONENTS (continued)

NEW PINNACLE VALVES, guaranteed 12 months at maker's list price. Most types available; prompt attention given to all enquiries. **TELESERVICE (SALISBURY)**, Quidshin Works, Quidhampton, Salisbury.

CHASSIS

Made drilled and punched to your design, any metal. Single or quantities. Standard sizes 18 s.w.g. aluminium, 21in. deep, undrilled, 6 x 4, 4'-; 7 1/2 x 5 1/2, 5' 0"; 10 1/2 x 7 1/2, 6' 0"; 12 x 8, 8'-; 14 x 9, 12'-. Flanges, 1/- extra. Plus postage 1/-. Latest Collaro 4-spd. Auto-changers, £7/10/- Post 4/6.

BOWERS ENGINEERING

208a, Hertford Road, Edmonton, N.9
HOWARD 2231

FOR SALE

ASTOUNDING VALUE.—9in. Televisions, 45/-; 12in. Televisions, 70/-; 14in., £9/10/-; 15in., £5/10/-; 17in., £14. Complete but not guaranteed working; as received in part exchange. **TOMLINS 127**, Brockley Rise, Forest Hill, London, S.E.23. All famous makes available; carriage 7/6.

VALVES, Condensers, Record Changers and Players, Cabinets, Amplifiers, Speakers, etc., etc. Send for free list to: **H. F. JAMES**, 21, Claremont Rd., Twickenham, Middx.

SATISFACTION ASSURED.—12in. Televisions, £9/10/-; 14in., £18; 17in., £19/10/-. Write for quotation, stating requirements. We guarantee satisfaction. **TOMLINS 127**, Brockley Rise, Forest Hill, S.E.23.

VALVE CARTONS at keen prices. Send 1/- for samples and list. **J. & A. BOXMAKERS**, 75a, Godwin St., Bradford, 1.

1,000 TELEVISIONS, all makes, from £3 working, 10/- not. Callers only. 9 till 6, including Sats. 39, Whitehorse Lane, Stepney, London.

300 ASSORTED TELEVISION CABINETS.—Table Models/Consoles with doors from 3/6 to 12/6 each. Phone: **LIVERPOOL** North 0820 or Anfield 7272, or write to: **MANAGING DIRECTOR**, 290, Kensington, Liverpool, 7.

SPECIAL OFFER.—Famous Pye Invicta 12in., 13 channel, Televisions (without tubes or valves), £2/15/-, otherwise complete. Each one with walnut cabinet and Pye 13-channel turret. **TOMLINS 127**, Brockley Rise, Forest Hill, S.E.23.

BETTER SAFE THAN SORRY!

Our 'Gold Star' Fully Reconditioned 14in and 17in. T.V.'s by All Leading Makers are fitted with Brand New Not Rebuilt Tubes with 12 Month Guarantees.

14 Inch All Channel 29 gns., 17 inch All Channel 39 gns. Terms Available. Part Exchange Welcomed and Money Back Guarantee. Trade Supplied Standard Models BBC from £5. BBC/ITA from £10.

T.C.S. LTD.

28, BROCKLEY CROSS, S.E.4.
TIDeway 5394.

FOR SALE (continued)

TELEVISIONS, 12in., 14in., 17in. and Projections. Require attention. From £3. In working order—12in. B.B.C. from £7; B.B.C./I.T.A. 14in. from £18; 17in. from £25. Send for Lists. Carriage Paid.

CADMAN'S

Service Department, Bryan Street, Hanley, Stoke-on-Trent.

SERVICE SHEETS; also Current and Obsolete Valves for sale. **JOHN GILBERT RADIO**, 20, Extension, Shepherds Bush Market, London, W.12. (Phone: SHE 3052.)

UNIVERSAL AVOMETER, £10; AVO Valve Tester with manual, £10. **WESTBY**, 89, Trellewelln Rd., Rhyl, Flint.

TELEVISION ENGINEERS

in all districts to act as Agents for our rebuilt T.V. tubes. Write for details.

E.M. SERVICES,

131-137, St. Ann's Road, N.15. STA. 3267.

MAKING YOUR OWN TELESCOPES, Enlargers, Projectors, Viewers, Microscopes, Episcopes, etc., then our booklets "How to Use Ex-Gov. Lenses and Prisms," Nos. 1 and 2. 2/6 ea., will show you easily and quickly how to achieve the finest possible results at lowest possible cost. The most comprehensive lists of optical and scientific equipment in the British Isles is free for s.a.e. **H. W. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

MAKING THE STACKED ARRAY in July issue? Kit of 10 Directors. "Slot," 8 Stub, as detailed, 30/-; "Yagi" Kits and all "Bits and Pieces" available. Requirements to: **AERIAL SUPPLY**, 165, Bedley Rd., Redditch, Worcs.

BRAND NEW TELEVISION TUBES

12 Months' Guarantee
12in., £7.10.0; 14in., £8.0.0;
17in., £9.0.0; 21in., £15.0.0.
Carriage & Insurance Paid.

FIDELITY RECORD PLAYER
Four speeds. Takes 7in., 10in. or 12in. records. Amazing reproduction. Colours: Fawn, Tweed Tan, or Grey Cord/Maroon. A.C. only 200-250 volts. ONLY 94 Gns. Carr. 5/-. S.A.E. with all enquiries.

RELIANCE ELECTRICAL SERVICES
124, Salmon Street, London, N.W.9
COL 6842

MISCELLANEOUS

LOUDSPEAKERS, Electric Clocks and Shavers repaired promptly. **MODEL LOUDSPEAKER SERVICE**, Shipton on Cherwell, Oxford.

RADIO

AT LAST VHF FM AM for the family man. Astonishing De Luxe VHF FM Radio offer. Merging of world famous Co., enables us to offer £24 **DE LUXE VHF FM/AM** Radios for £15.10.0. Factory fresh. Maker's guarantee, extra thrilling quality. All features including Ferrite aerials. Our satisfaction guarantee or purchase price refunded. A.C./D.C. 200/250 v. Smaller radio with VHF FM AM, £13.10.0, originally £21. Or Miniature Superhet two-wave model, £8.10.0. Carriage paid. Send for illustration. **TOMLIN ELECTRIC**, 117, Brockley Rise, London, S.E.23.

SERVICE SHEETS

TELEVISION SERVICE SHEETS, over 100 sheets covering 330 popular models, 18/6, post free. Send for full details. All types of Service Sheets for sale and hire. Radio, Television, Electronics Books, Television Servicing, 5/-; Radio Servicing, 4/-, List free. **HAMILTON RADIO, BCM/DATA3**, London, W.C.1.

SERVICE SHEETS—1 working day delivery. T.V., 4/- ea.; Radio, 3/- ea., plus postage. Faultfinder Files, 2/- ea., plus postage. Manuals for hire and sale. List 1/-; s.a.e. Sultan Radio, 6, Mt. Ephraim Rd., Tunbridge Wells, Kent.

SERVICE SHEETS.—Radio and T.V. for sale at 4/- each, and for hire. Why tolerate delay in obtaining service sheets when we will despatch by return. List 1/-; s.a.e. **S.P. DISTRIBUTORS**, 11, Old Bond St., London, W.1.

SERVICE SHEETS, Radio TV for sale from 1/- each. List free. **J. PALMER**, 32, Neasden Lane, N.W.10.

SERVICE SHEETS for sale, 2/6 each, or hire. Radio and Television. List 1/-, s.a.e., with enquiries please. **GLOBE SUPPLIES**, BCM/Electrique, London, W.C.1.

MAKER'S MANUALS. We have a large quantity of maker's manuals for sale, or hire, radio and T.V. List 4d.; s.a.e. with enquiries, please. **S.P. DISTRIBUTORS**, 11, Old Bond Street, London, W.1.

EDUCATIONAL

EASY MATHEMATICS.—Course 21- for Radio/TV. Write: **TUTORIALS**, 200, Buchanan St., Glasgow, C.1.

INCORPORATED Practical Radio Engineers home study courses of radio and T.V. engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text free. "The Practical Radio Engineer," journal, sample copy 2/-, 6,000 Alignment Peaks for Superhets, 5.9. Membership and Entry Conditions booklet 1/-, all post free from the **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

BUILD YOUR OWN HI-FI at home! At last, for reasonable cost—the chance to make your own quality Hi-Fi Audio Equipment and to gain the knowledge to service and maintain it. Free brochure from: **Dept. P.T.20, RADIOSTRUCTOR**, 46, Market Place, Reading, Berks.

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation—**I.C.S.** Courses for the enthusiast and for those seeking examination qualification. **Brit.I.R.E.**, City and Guilds, R.T.E.B., etc. Build your own equipment with Practical Radio Course. Write to-day for free book. **INTERNATIONAL CORRESPONDENCE SCHOOLS**, 71, Kingsway (Dept. 516), London, W.C.2.

"HOW AND WHY" of Radio and Electronics made easy by a new, non-maths, practical way. Postal instruction, based on hosts of experiments and equipment building, carried out at home. New Courses being enjoyment as well as knowledge of this fascinating subject. Free brochure from: **Dept. P.T.12, RADIOSTRUCTOR**, 46, Market Place, Reading, Berks.

(Continued overleaf)

SITUATIONS VACANT

SALES MANAGER (Radios and T.V.) required by a leading British Company in East Africa. Applicants should be capable of creating and running an external dealer organisation, of controlling supply, stocks and credit and of planning the whole sales effort. Some technical knowledge of radios and television is highly desirable. Candidates should be aged between 27 and 40 years. The starting salary will not be less than £1,600 per annum. Tours in East Africa are 2 or 4 years followed by leave in the United Kingdom on full pay. - Furnished housing provided at subsidised rent or allowances in lieu, contributory pension fund, free passages including wife and family, and free medical treatment. Apply, giving full details of qualifications and experience, to: Box No. 19, c/o PRACTICAL TELEVISION.

Your Technical skill PLUS equal skill in Outdoor Selling gives you the DOUBLE QUALIFICATION so much sought by managements and worth £1,000-£3,000 p.a. as Outdoor Technical Representative. HOME training by world experts in Outdoor Selling thus gets you flying start whilst the other fellow is still chasing that elusive indoor job. Literally thousands of successes (CHECKABLE PROOF supplied). Top-grade. GUARANTEED. Appointments Service. Details free. No obligation whatever. Write today:

The National School of Salesmanship Ltd.
Dept. P.T.,
Head Office:
National House, Manchester, 2,
Bl. Aekfriars 8811 2, London: 2, Dances
Inn House, 265 Strand, London, W.C.2.
CH. Ancrey 4211-2.

"The DOUBLE qualification for
the DOUBLE income!"

LINE OUTPUT TRANSFORMERS

Most types available. State
Make and Model Number
of Receiver when ordering.

S.A.E. please with all enquiries.

HOWORTH

51 POLLARD LANE,
BRADFORD, 2, YORKS

Tel. 37030

RADIO AND TELEVISION COMPONENTS

We operate a prompt and efficient MAIL-ORDER Service. 3d. stamp (only) for Catalogue.

JAMES H. MARTIN & CO.
FINSTHWAITE, NEWBY BRIDGE,
ULVERSTON, LANCs.

SPECIAL VALVE OFFER FOR LIMITED PERIOD

EF80	6/-	PY82	6/6	6P28	7/6
10F1	6/6	PL82	6/6	EB34	1/6
6F1	7/-	PL83	6/6	7C5	6/6
EB91	4/6	6P25	7/6	7Y4	7/-
EF91	5/-	KT33C	7/-	3D6	2/-
ECL80	8/6	EY83	7/6	1625	5/-
DH76	6/6	UCH42	8/6	807	4/-
DH77	6/-	SP61	3/-	4D1	2/6
UL46	8/6	SP41	3/-	EB41	7/-
6F13	6/6	Z63	6/-	6L18	9/6
6F14	6/6	Z66	6/-	N37	9/-
6F15	6/6	B36	7/-	20LD20	9/-
6L1	7/6	L63	5/6	UF42	7/-
20F2	7/-	6SN7GT	5/6	6F6G	6/6
PY80	6/6	20P1	7/6		

Postage 6d. per Valve.

Air-Spaced Coaxial Cable 75 ohms, 8d. per yard; Ion Traps, 5/-; F.M. Twin Feeder, 4d. per yard; T.V. Aerials, Band III, 3 E.L., 23/6; 8 E.L., 57/6; F.M. Aerials, Single Dipole Wall Fixing, 29/6.

MAIL ORDER ONLY—NO CALLERS.
Terms: C.W.O. or C.O.D. Minimum C.O.D. charge 3/6. Postage and Packing other than valves: Under £2. 1/6; Under £5, 2/-; Aerials, 2/6 Carriage.

ELECTRO-SERVICES & Co.

221 BATTERSEA PARK ROAD,
LONDON, S.W.11. MAC 6833/4



The Royal Air Force

PILOTS, NAVIGATORS AND AIR ELECTRONICS OFFICERS COMMISSIONS IN THE GENERAL DUTIES BRANCH

Vacancies now exist for fit young men of character and good education and who are capable of taking responsibility, to train as pilots, navigators or air electronics officers in the general duties branch of the Royal Air Force.

Methods of Entry

University Entry—University graduates may enter on permanent or four-year short-service commissions. Permanent commissions carry an ante-date. University students may be accepted subject to graduation. Maximum age limit 25.

Direct Commissions—The direct commission scheme offers the choice of a permanent career leading to a pension, or a twelve-year commission with the option of leaving after eight years. Age limits: 17½ to 25.

Short-Service Commissions—The short-service commission is for

five years and there are opportunities for transfer to either form of direct commission. Age limits: 17½ to 21.

Pay and Gratuities—Pay is high and terminal gratuities are generous. For example, a Flight Lieutenant of 25 can earn, with full allowances, nearly £1,700 a year. The tax-free gratuity paid at the end of a twelve-year commission is £4,000.

Write for further details, stating age and education, and the method of entry in which you are interested, to the Air Ministry M9, Dept. PTN526a, Admiralty House, London, W.C.1.

WANTED

IMPORTANT! New Valves and Metal Rectifiers wanted, state price. Same day payment. ROBERT, 414, Whitefoot Lane, Bromley, Kent.

ALL TYPES OF VALVES WANTED. PL81, ECL80, EY51, U25, PCF80, PZ30, U801, etc., etc. Best cash price by return. STAN WILLETT, 43, Spon Lane, West Bromwich, Staffs. (Tel.: WES 2392.)

NEW T.V. VALVES WANTED. Send valves, cash by return, to: P. J. F. ANDREWS, 61-63, Rosemary Rd., London, S.E.15.


WANTED (continued)

NEW VALVES WANTED. all types, state prices, prompt payment. D.X. 56, Teign Bank, Hincley, Leics.

NEW VALVES WANTED.—EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. DURHAM SUPPLIES, 175, Durham Rd., Bradford, 8, Yorkshire.

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., 155, Swan Arcade, Bradford, 1.

Build your own Aerials...

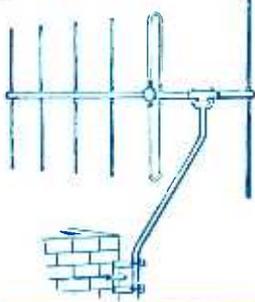

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.
 Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above to :-

*Fringe*vision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

Save £££

12 Months' Guarantee

FACTORY REBUILT... TELEVISION TUBES

Immediate delivery

Double the guaranteed life of a new tube

TYPES

MW31-74	- 12 in.	£5.12.6	MW36-24/44	14 in.	£5.17.6
MW43-64/69	17 in.	£7.0.0	MW53-20/80	21 in.	£9.10.0
CRM141	- 14 in.	£5.17.6	CRM152-153	- 15 in.	£6.5.0
CRM171	- 17 in.	£7.0.0			

TERMS TO
THE TRADE

Plus 10/- carriage and insurance.
Cash with order or C.O.D.

RE-VIEW (LONDON) LTD.
 10 High Street - - Colliers Wood, S.W.19

Telephone: Liberty 3272

C.R.T. ISOLATION TRANSFORMERS
 TAPPED MAINS PRIMARIES
 TYPE A. OPTIONAL 25% AND 50% BOOST.
 2V. OR 4V. OR 6.3 V. OR 10.8 V. OR
 13.3 V. 12/6.
 OUR LATEST SUPERIOR PRODUCT
 TYPE AC. HIGH QUALITY. LOW CAPACITANCE.
 10/13 PF. OPTIONAL BOOST 25%, 50%,
 75%. 1b/3 EACH.
 TYPE B. MAINS INPUT. MULTI OUTPUT 2,
 4, 6, 3, 7.3, 10 AND 13 VOLTS. BOOST 25%
 AND 50%. LOW CAPACITY. 21/-

TRIMMERS, Ceramic, 30, 50, 70 pf., 100 pf.,
 150 pf., 1.3; 250 pf., 1/8; 500 pf., 750 pf.,
RESISTORS, Preferred values, 10 ohms to 10 meg.,
 1 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/-
HIGH STABILITY, 1 w., 1/2; Preferred values,
 100Ω to 10 meg., 1/10, 5/10, 100Ω to 1.5 meg., 1/8, 9d.,
 1/2 watt; **WIRE-WOUND RESISTORS** 1/3
 1/2 watt; 25 ohms—10,000 ohms } 2/-
 5,000 ohms—50,000 ohms, 5 w., 1/9; 10 w., 2/3

GEVARTON GEVASONER

50% extra long play plastic tape, 1,700 ft. Tin.
 Reel, 35" x 850ft., 5in. reel, 21/-.
**SUPERIOR I,200 ft. Plastic Tape on 7" Plastic
 Reels, Quality Guaranteed, 21/-.**
SPARE REELS, ALL SIZES, 3/-.

*Install Bulk Tape Eraser and Head De-
 fluxer, 200/250 v. A.C., 27/8. Leadlet, S.A.E.

O.P. TRANSFORMERS, Heavy Duty 50 mA., 4/6.
 Multiratio, push-pull, 7/8. Miniature, 384, etc. 4/6.
E.F. CHOKES 15/10 H., 50/65 mA., 5/-; 10 H.,
 5 mA., 10/8; 10 H. 150 mA., 14/-

MAINS TRANSFORMERS 200/250 v. A.C.
STANDARD, 250-0-250, 80 mA., 6.3 v., 3.5 a.
 tapped 4 v., 6 v., Rectifier 5.5 v., 1 a., 5 v.,
 2 a. or 4 v., 2 a., ditto, 350-0-350 ... 22/8
MINIATURE, 200 v., 20 mA., 6.3 v., 1 a. ... 10/8
MIDGET, 220 v., 45 mA., 6.3 v., 2 a. ... 15/8
SMALL, 250-0-250, 100 mA., 6.3 v., 3.5 a. ... 19/8
STANDARD, 250-0-250, 65 mA., 6.3 v.,
 3.5 a. ... 17/8
HEATER TRANS., 6.3 v., 11 amp. ... 7/8
 Ditto, tapped sec. 2, 4, 6.3 v., 11 amp. ... 8/8
 Ditto, sec. 6.3 v., 3 amp. ... 10/8

ALADDIN FORMERS and core, 1in., 8d.; 1in., 10d.,
 2in., and 1in. sq. x 1 1/4in., 2/- ea., with cores.
TYANA, Midget Solenoid Iron, 40 v., 18/9.

EMPLOY Instrument Iron, 25 w., 17/6.
MAINS DROPPERS, 3in. x 1 1/4in., Ad. Sliders,
 63 amp., 750 ohms, 4/3, 0.2 amp., 1,000 ohms, 4/3.
LINE CORD, 3 amp., 60 ohms per foot, 2 amp., 100
 ohms per foot, 2-way, 6d., per foot, 3-way, 7d., per ft.
LOUDSPEAKER P.M., 3 OHM, 2 1/2in., & 5in., 17/6.
 5in. Plessey, 12/6, 8in. x 4in., Rola, 18/-, 6in., K.A.,
 18/6, 8 x 5in., 21/-, 10 x 6in., 27/6, 10in. Rola, 15/-,
 5 1/2-Pi Turner, 25/-, 12in. K.A., 30in., 12in., 15/-,
 5 w., Plessey, 45/-

STENTORIAN HF1012 10in. 3 to 15ohm 10 w., 59/8
 12in. Baker 15 watt 3 ohms, or 15 ohms, 105/-
CRYSTAL DIODE G.E.C., 2/-, GEX34, 4/-
HIGH RESISTANCE PHONES, 4,000 ohms, 16/6
PRIME TRANS., 50:1, 3/9 ea.; 100:1, Potted, 10/6
SWITCH CLEANER, Fluid squirt sprout, 4/3 tin.
TWIN GANG TUNING CONDENSERS, 365 pf.,
 miniature 1in., 10/-, 1in., 10/-, 4005 Standard
 with trimmers, 9/-; less trimmers, 8/-; midget, 7/6
SINGLE, 50 pf., 2/8; 80 pf., 100 pf., 160 pf., 7/-
 Solid dielectric 100, 300, 500 pf., 3/8.
SPEAKER FRET GOLD CLOTH, 17in. x 25in., 1/-
 25in. x 35in., 1/-, 35in. x 41in., 6in. wide, 10/-; 1 1/2in.,
 2in. wide, 5/-; 1in. Scintilles, S.A.E.

New and Boxed VALVES 90-day Guarantee.

1J3	8/6	KKG	8/6	EAB30	10/6	HA800	
185	8/1	104	10/8				10/6
2T4	8/6	INTM	7/6	ER91	6/6	HVR2A	7/8
2X2	8/6	Q7G	10/8	EMC43	8/6	MU14	10/6
2X4	8/6	9A47	7/6	ER441	10/6	PH1	6/8
2V4	8/6	9A7M	10/6	EP80	10/6	PC84	12/6
6B4	8/6	9N7	8/6	PC84	12/6	PCF80	11/6
6F3	8/6	6V6G	7/6	ECF50	11/6	PC182	11/6
6Z4	10/6	6X4	7/6	EC42	10/6	PEN25	6/8
6AM6	8/6	6X3	7/8	EC182	12/6	PH1	10/6
6B8	5/6	12A77	8/6	EP39	7/6	PH80	10/6
6BE1	7/6	12A7	9/6	EP41	10/6	PH81	10/6
6BH	10/6	12AX7	9/6	EF50	5/6	PH82	10/6
6BW6	10/6	12BE6	10/6	EP80	10/6	PH1	5/6
6F6	7/6	12K7	8/6	EP91	8/6	PH41	10/6
6F68	7/8	12Q7	8/6	EP92	5/6	UC42	10/6
6R3	3/1	15A	9/6	EL22	5/6	UC41	10/6
6K3	8/6	3Z4	9/6	EL41	10/6	UC41	10/6
6J6	7/6	80	10/6	EM81	12/6	UY41	10/6
6J7G	8/6	807	10/6	EZ40	10/6	UZ2	10/6
6K61	6/6	154	11/6	EP20	9/6	VR105	8/6
6K74	5/6	EA50	11/6	EL149	11/6	VR180	8/6

TELEVISION REPLACEMENT LINE OUTPUT TRANSFORMERS

70/- ea. from stock.

For Makes and Models

Argosy: T2, CTV517, Decca: D17 & C. Defiant: TR1753.
RGD: 6017T, 7017C, C54.
Regentone: 17C, 17T, 17 Comb.

Argosy: T3, Decca: D14.
Defiant: TR1453T, **Regentone**: 14T, **RGD**: 6014T.

Marconi: VT63DA.

Baird: 2014, 2017, 2114, 2117.

Cossor: 930 & T, 931, 933-4-5,
 937, 938 & A & F,
 939 & A & F, 943T, 946.

H.M.V.: 1824 & A, 1825 & A,
 1826 & A, 1827 & A,
 1829 & A.

Marconi: VT68DA, VT69DA.

Sobell: TS17, T.346.

Ferguson: 306T, 308T.

Most other makes and models available (10 days). S.A.E. with all enquiries.

LINE BLOCKING OSCILLATOR TRANSFORMERS, 10/- to 16/6.

FRAME BLOCKING OSCILLATOR TRANSFORMERS, 13/6 to 21/-.

FRAME OUTPUT TRANSFORMERS, 27/6 to 39/-.

Most makes available (10 days). S.A.E. with all enquiries.

ALUMINIUM CHASSIS, 18 s.w.g. un drilled, with 4 sides, riveted corners and latrine fixing holes, 2 1/2in. sides, 7 x 4in., 4/8; 9 x 7in., 5/8; 11 x 7in., 6/8; 13 x 9in., 8/8; 14 x 11in., 10/8; 15 x 14in., 12/6; 18 x 16 x 3in., 16/6.

TRANSISTORS, GENUINE PYE GOLTOP, Audio, 10/-, R.P. (3 Mc/s average), 18/-, Power, 20/-, Complete data sheets supplied.

CRYSTAL MIKE INSERT by Acos, precision engineered, Size only 1in. x 3/16in., 6/8.

HI-GAIN BAND 3 I.T.A. PRE-AMP KIT, Cascade circuit with valve EC84, Price 28/6. With Power Pack, 48/6. Plans only 8d. Band I.B.C. version same prices.

TELETRON "TRANSIDYNE"
MIDGET SUPERET PORTABLE 6" x 4" x 1 1/2"
 8 transistors, printed circuit, Ferrite aerial. All parts and cabinet, 111.19.8.
 We include 6 Goltop or Mullard Transistors for maximum performance. Details 8d.

BEC T.V. TRANSISTOR RADIO, Complete kit 32/8, phones 7/6 extra. Deaf Aid Ear-piece 12/8. Special Lead 2/8.

GARRARD 4SP. SINGLE PLAYER AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records 7in., 10in., 12in. Lightweight Xtal pick-up. GG2 turnover head, two separate sapphire styl. **OUR PRICE £7.10.0** each. **1st Free**
 Model TA Mk. II ES-10-0. Model 4HF ES10-0. (Stereoheads 2/8 extra).

Volume Controls 80 ohm CABLE COAX

Long spindles. Guaranteed 1 year. Midget 5K ohms to 2 Mc. Stamped out 50%. No sw. D.P.S.W. 3/-, 4/9. Linear or Log Tracks. Air Spaced. **1/6 yd.**

COAX PLUGS ... 1/- **LEAD SOCKET** ... 2/-
PANEL SOCKETS 1/- **OUTLET BOXES** ... 4/6
BALANCED TWIN FEEDER pf. 6d. 80 or 300 ohms.
DITTO SCREENED per yd. 1/3. 80 ohms only.
WIRE-WOUND POTS 3 WATT. Pres. 30 Min. T.V. Type. All values 25 ohms to 25 K., 3/- ea. 50 K., 50 K., 4/-, (Carbon 30 K., 2 to meg., 3/-).
WIRE-WOUND 4 WATT, Pots 2 1/2in. Spindle Values: 100 ohms to 50 K., 6/8; 100 K., 7/8.
CONDENSERS, New Stock, 1001 mfd., 7 kv. P.C.C., 5/8; Ditto, 20 kv., 9/8; 100 pf., to 500 pf., Micas, 6d.; Tubular 500 v., .001 to .01 mfd., 9d.; .01 to .1 mfd., 1/8; .1 mfd., 2/000 volts, 3/6.
CERAMIC CONDS., 500 v., 2 pf. to .01 mfd., 9d. **SILVER MICA CONDENSERS**, 10% 5 pf. to 500 pf., 1/-; 600 pf. to 3,000 pf., 1/3. Close tolerance ± 1 p.p. 1.5 pf. to 47 pf., 1/6. Ditto 1% 50 pf. to 815 p.p., 1/8; 1,000 pf. to 5,000 pf., 2/-.

I.F. TRANSFORMERS 7/6 pair, 465 Kcs/Sig Tuning Miniature Can. 2 1/2in. x 1in. x 1in. High Q and good bandwidth. By Pye Radio. Data sheet supplied.

Wearite M800 I.F. 465 Kcs, 12/6 per pair. Wearite 550 I.F. 465 Kcs, 12/6 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES

TUBULAR	TUBULAR	CAN TYPES
1550 v. 2/-	64/500v.	5/8 8/500v. 3/-
2450 v. 2/3	100/25v.	2/- 16/500v. 4/-
4450 v. 2/3	250/25v.	2/6 32/350v. 4/-
8450 v. 2/3	500/12v.	3/- 100/270v. 5/-
8700 v. 2/8	84/4500v.	4/8 2/500/3v.
16450v. 2/6	84/4500v.	5/- 6/000/6v.
16500v. 4/-	84/16450v.	5/- 32+32/350v. 4/8
32450v. 5/6	84/16450v.	5/8 50+50/350v. 7/6
35250v. 1/8	16+16/350v.	5/8 64+120/275v. 7/6
35250v. 2/-	32+32/350v.	4/8 64+120/350v. 11/8
8700 v.	24+32/350v.	7/8 100+200/275v. 12/6

SENTERCEL RECTIFIERS, E.H.T. TYPE **FLX-BACK VOLTAGE**, K3/25 2 kv., 6/-; K3/30 3.2 kv., 7/-; K3/45 3.6 kv., 7/8; K3/50 4 kv., 8/-; K3/100 8 kv., 14/8; 50 c.p.s. voltage, 20% of above.
MAINS TYPE CONDENSER 300 v., 85 mA., 7/8.
CONDENSER COOLED 250 v., 50 mA., 7/8; 60 mA., 8/6; 85 mA., 9/6; 200 mA., 2/-; 500 mA., 27/8.
COILS Wearite "P" type, 3/- each. Osmor Midget "Q" type adj. dust core from 4/-, All ranges.
TELETRON L & Med. T.R.P., with reaction, 3/6.
FERRITE ROD AERIALS, M.W., 8/9; M & L, 12/6.
T.P. COILS 4HF, 7/- pair. H.F. CHOKES, 2/6.
FERRITE ROD, 7in. x 8/8in. dia., 2/8.

JASON F.M. TUNER COIL SET 26" H.F. coil, aerial coil, Oscillator coil, two 1 P.F. trans. 10.7 Mc/s. Ratio Detector and heater choke. Circuit book using four 6AM6, 2/-.
COMPLETE JASON F.M. KIT WITH VALVES, £8.15.0. Fringe area kit, 22/6 extra.
MULLARD 3-8 AMPLIFIER READY BUILT, Spare Power for Tuner, etc., 27.17.8.

FULL WAVE BRIDGE SELENIUM RECTIFIERS, 2, 6 or 12 v., 14 amp., 8/0; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS, Tapped input 200/250 v., for charging at 2, 6 or 12 v., 14 amps., 15/6.
 2 amp., 17/6; 4 amps., 22/6. Circuit included.
VALVE and T.V. TUBE EQUIPMENT BOOKS, 5/-
TOGGLE SWITCHES, S.P. 2/-, D.P. 3/6, D.P.D.T. 4/-
WAVECHANGING SWITCHES
 3 p. 4-way 2 water long spindle ... 2/6
 2 p. 2-way or 3 p. 2-way short spindle ... 8/8
 2 p. 2-way, 4 p. 2-way, 4 p. 3-way long spindle ... 3/6
 3 p. 4-way, or 1 p. 12-way long spindle ... 3/6
VALVE HOLDERS, Pax. Int. Oct. 4d. EF50, EA50, 6d. B12A, CRT, 3/-, Eng. and Amer. 4, 5, 6, and 7 pin. 1/-, **MOLDED MAZDA**, and Int. Oct., 6d. BTG, B8A, B8U, B9A, 9d. BTG with can, 1/6. B9A with can, 1/8. **CERAMIC EF50, BTG, B9A**, Int. Oct., 1/-, BTG with can, 1/9.

RADIO COMPONENT SPECIALISTS

OUR ONLY ADDRESS 337 WHITEHORSE RD., WEST CROYDON

Postal service. 1/- over £2 free. (Export Extra.) C.O.D. 1/6. (Wed. 1 p.m.) Catalogue 1/6. THO 1665. Buses 133 or 68