

THE TV CENTRE

Practical Television '6

AND TELEVISION TIMES



CONTENTS

THE EF50 CONVERTER
GUIDED GRID VALVES
SERVICING TV RECEIVERS
YOUR PROBLEMS SOLVED
ETC. ETC. ETC.

TELEVISION SPARES

All Makes All Models By return of post

- LINE OUTPUT TRANSFORMERS FRAME OUTPUT TRANSFORMERS
- DEFLECTOR COILS
- LINE AND FRAME BLOCKING OSCILLATOR TRANSFORMERS
- ALL POTENTIOMETER AND SLIDER CONTROLS
- MAINS DROPPERS METAL RECTIFIERS
- GERMANIUM DIODES FOCUS MAGNETS
- ION TRAPS E.H.T. CONDENSERS

Our Range of Spares is probably the most extensive in the country and includes all Spares for Tape Recorders, Radio and Record Player Units.

Technical Advice Free. Service Manuals supplied on loan.

Terms: C.W.O. or C.O.D. All Components are supplied at list prices, plus 2/6 p.p.

Please enclose S.A.E. with all enquiries.

NEWBURY RADIO

272, ROMFORD ROAD, FOREST GATE, LONDON, E.7.

MARyland 3100

ERSIN MULTICORE SOLDERS

for a first class joint every time

Ersin Multicore contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON
5/-



HANDYMAN'S CARTON

Suitable for 200 average joints. **6d.**

HOME CONSTRUCTORS 2/6 PACK

In addition to the well-known Home Constructors Pack (containing 19ft. of 18 s.w.g. 60/40 alloys) a similar pack is now available containing 40ft. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits.



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SAVBIT TYPE 1 ALLOY

A specially formulated alloy to reduce the wear of soldering iron bits. Contains 5 cores of non-corrosive Ersin Flux and is ideal for all soldering purposes.

SIZE 1 CARTON 5/-

Available in three specifications.



BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire. cuts wire cleanly. splits extruding flex. **3/6 each**



TELEVISION TUBES REBUILT

BUY DIRECT FROM THE FACTORY!

12 MONTHS' GUARANTEE

12" - - - - £5. 0.0

14" - - - - £5.10.0

17" - - - - £6.10.0

Immediate dispatch on receipt of Remittance

Carriage and insurance 12/6 extra.

MARSHALLS for TELEVISION LTD.

131 St. Ann's Road, Tottenham, London, N.15.

Telephone: STAmford Hill 3267

MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)


A REVOLUTIONARY NEW BRITISH INVENTION!

- ★ Uses standard tapes
- ★ Plays at 7½" per. sec. or 3 other speeds
- ★ Records direct from radio or microphone
- ★ Erase and fast rewind

£13.12s

Special moving-coil microphone and tape extra.

EASY TERMS

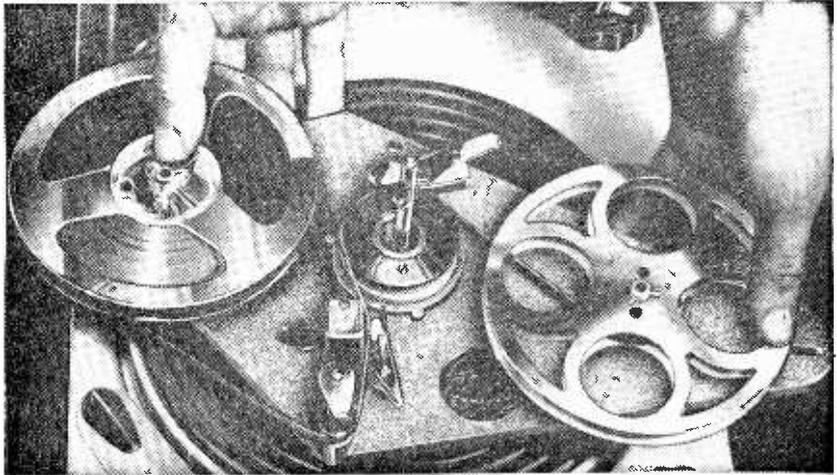

Instantly turns any gramophone into a first-class Tape-Recorder and back into a record-player in a moment!

Gramdeck is completely *new* . . . a revolutionary and ingenious invention that instantly turns your gramophone into a tape-recorder and back into a gramophone at will! Slip the Gramdeck on to your turntable and you have the finest tape-recorder you've ever heard! Lift it off . . . your gramophone is ready to play records again. There are no motors or valves to go wrong—and you get a quality that has to be heard to be believed! Everyone is praising the Gramdeck.

"The quality is at least equal to that obtained from a good microgroove disc," says a leading professional journal.

"Ingenious—simple . . . why on earth did no one think of it before!"—THE TAPE RECORDER.
 "Thoroughly recommended."—GRAMOPHONE RECORD REVIEW.

"Quality of reproduction excellent . . . real hi-fi results . . . potential is tremendous . . . both designer and manufacturer should be congratulated."
 —BRITISH RADIO & T/V RETAILERS REVIEW.

"Better than many so-called hi-fi recorders . . . robust . . . carefully designed . . . excellent value."
 —AMATEUR CINE WORLD.

WORKS FROM ANY RECORD-PLAYER OR RADIOGRAM

Gramdeck records and reproduces with a wonderful depth and breadth of tone. Because it uses equipment that is already in your gramophone it only costs a fraction of the high-quality tape-recorder you would normally require. Full details, specifications, photographs, easy terms, etc., are given in the Gramdeck Book. Send for your FREE copy, today.

MADE BY THE FIRM THAT MAKES RADAR EQUIPMENT FOR VISCOUNTS & BRITANNIAS

FREE BOOK—POST NOW!

I would like to know how to turn my gramophone into a first-class tape-recorder . . . please send me the Gramdeck Book—FREE and without obligation.

(Write if you prefer not to cut page)

NAME

ADDRESS

Gramdeck (Dept. PT/806) 29 Wright's Lane
 Kensington, London, W.8



Gramdeck
 GRAMOPHONE TAPE RECORDER
 HIGH QUALITY TAPE-RECORDING FOR EVERY HOME

GRAMDECK TURNS A TURNTABLE INTO A TAPE-RECORDER

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS. 38 CHALCOT ROAD, LONDON, N.W.1. Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

ANY ORDER INSURED AGAINST DAMAGE IN TRANSIT FOR ONLY 6d. EXTRA.

0A2	17/6	6CB	12/6	6X4	6/6	19BG6G	7475	7/6	EACB90	9/1	EL41	9/1	LN152	10/6	OS150/15	UCH81	9/6			
0B2	17/6	6C9	12/6	6XSGT	6/1	23/3	9002	5/6	EAC91	7/6	EL42	13/11	LN309	11/6	10/6	UCL82	11/6			
0Z4	6/1	6C10	10/6	6/30L2	10/1	19H1	10/1	AC/PEN	EAF42	9/1	EL81	12/6	MH4(C)	7/1	R12	9/6	UCL83	19/3		
1A3	3/1	6CD6G	6/6	7A7	12/6	20D1	15/3	5-pin 23/3	EB34	2/6	EL84	8/6	MHL4	7/6	R18	14/1	UF41	9/1		
1A5	6/1	6CH6	12/6	7B6	21/3	20F2	26/6	7-pin 15/1	EB41	8/6	EL85	13/11	MHLD6	12/6	R19	19/11	UF42	12/6		
1A7	15/1	6D3	19/11	7B7	8/1	20G1	26/6	AC2/PEN	EB91	5/6	EL91	5/1	ML4	12/6	S130	15/1	UF80	10/6		
1C5	12/6	6D6	6/6	7C5	8/1	20P1	26/6	DD 26/6	EBC3	23/3	EL95	10/6	MU14	9/1	SD6	12/1	UF85	10/6		
1D5	9/1	6E5	12/6	7C6	8/1	20P3	23/3	AC5/PEN	EB333	7/1	EM34	10/1	MX40	15/1	SP4(7)	15/1	UF86	17/11		
1D6	10/6	6F1	26/6	7D8	23/3	20P5	23/3		EBC41	8/6	EM71	23/3	N37	19/11	SP41	3/6	UF89	9/1		
IHSGT	11/1	6F6G	7/1	7H7	7/1	25A6G	11/1	AC6PEN 7/6	EBC81	8/1	EM80	9/6	N78	19/11	SP42	12/6	UL41	9/1		
IL4	6/1	6F6GTM	8/1	7R7	12/6	25L6GT	10/1	AC/SG 23/3	EBC80	10/1	EM81	9/6	N108	19/11	SP61	3/6	UL44	26/6		
ILD5	5/1	6F8	12/6	7S7	10/6	25U4	16/7	AC/TP 33/2	EBF83	13/11	EM84	10/6	N308	20/7	SU25	26/6	UL46	14/6		
ILNS	5/1	6F11	17/3	7V7	8/6	25Y5	10/6	AC/VPI 15/3	EBF89	9/6	EN31	37/1	N339	29/10	SU61	9/6	UL84	8/6		
INSGT	11/1	6F12	5/6	7Y4	8/1	25Y5G	10/6	AC/VJP2 23/3	EBL21	23/3	EY51	9/6	P61	3/6	T41	23/3	UM14	17/3		
IR5	7/6	6F13	11/6	7Z4	18/7	25Z4G	9/6	ATP4	5/1	EBL31	23/3	EY83	16/7	PABC80	TDD4	24/6	UN80	15/3		
IS4	9/1	6F14	26/6	8D3	3/6	25Z6	10/6	AZI	10/1	EC52	5/6	EY84	14/1	PCC84	13/11	TH4B	26/6	URIC	9/1	
IS5	7/6	6F15	15/3	8D3	5/6	25Z6G	10/1	AZ41	13/11	EC54	6/1	EY86	10/1	PCC85	9/6	TH233	33/2	UJ7	19/11	
IT4	6/1	6F6	9/6	9B8W6	15/3	25Z6GT	10/1	AZ41	13/11	EC90	12/6	EZ35	6/1	PCC88	23/11	TH2321	20/1	UJ8	26/6	
1U5	10/1	6F17	12/6	9D2	4/1	B36	24/7	B36	24/7	EC92	13/3	EZ40	7/6	PCC89	14/1	TP22	15/1	UJ9	7/6	
2A7	10/6	6F32	10/6	10C1	12/1	27SU	19/11	BL63	7/6	EC33	10/6	EZ41	7/6	PCF80	8/1	TP25	19/6	UYIN	18/7	
2P	26/6	6F33	7/6	10C2	26/6	28D7	7/1	CI	12/6	EC33	8/6	EZ80	7/1	PCF82	11/6	TP2620	33/2	UY21	16/6	
2X2	4/1	6G6	6/6	10D2	12/1	30C1	8/1	CIC	12/6	EC34	24/7	EZ81	7/1	PCF82	11/6	TP2620	33/2	UY21	16/6	
2A4	7/6	6H6GTG	3/1	10F1	17/5	30F5	7/1	CBL1	26/6	EC35	8/6	FC2A	24/7	PCLB2	12/6	TY86F	13/3	UY41	7/6	
3A5	10/6	6H6GTG	3/1	10F9	10/6	30FL1	10/1	CBL31	23/3	ECC40	23/3	FC4	15/1	PCLB3	11/6	UI2/14	12/1	UY85	7/1	
3B7	12/6	6J5G	5/1	10LD3	8/6	30L1	8/1	CCH35	23/3	ECC81	8/1	FC13	26/6	PCLB4	12/6	UI6	12/1	VMS4B	23/3	
3D4	5/1	6J5GTG	5/6	10LD11	30L15	14/1	30L15	CK506	6/6	ECC82	7/6	FC13C	26/6	PENA4	23/3	UI8/20	9/1	VP2(7)	12/6	
3Q6	7/6	6J5GTG	6/1		15/11	30PJ2	8/1	CL33	19/3	ECC83	8/1	FW4/500		PENB4	2/6	U22	8/1	VP4(7)	15/3	
3QSGT	9/6	6J6	5/6	10P13	15/6	30P16	8/1	CV63	10/6	ECC84	9/6			PEN4DD	U24	29/10	VP2B	14/6		
354	7/6	6J7G	6/1	10P14	19/3	30PL1	11/6	CV271	10/6	ECC85	8/6	FW4/800			26/6	U25	17/11	VP4B	23/3	
3V4	7/6	6J7GT	10/6	11D3	24/7	31	7/6	CV42B	30/1	ECC88	23/11			PEN25	19/11	U26	10/1	VP13C	7/1	
5R4GY	17/6	6K6GT	8/1	12A6	6/6	33A/158M		CY1	18/7	ECC91	5/6	GZ30	10/6	PEN36C	U31	9/6	VP23	6/6		
5U4G	8/6	6K7G	5/1	12AC6	15/3			CY31	16/7	ECC80	11/6	GZ32	12/1		U31	9/6	VP23	6/6		
5V4G	11/1	6K7GT	6/1	12AD6	17/3	35/51	30/1	D1	3/1	FCF82	10/6	GZ34	14/1	PEN40DD	U35	26/6	VR105/30	6/6		
5Y3	8/1	6K8GT	8/1	12AE6	13/1	35A5	21/3	D15	10/6	ECC83	26/6	H30	5/1		25/1	U37	26/6		9/1	
5Y3GT	7/6	6K8GTG		12AH7	8/1	35L6GT	9/6	D63	5/1	ECH21	23/3	H63	12/6	PEN44	26/6	U43	9/6	VR150/30		
5Z3	12/6	12/6	12/6	12AH8	12/6	35W4	7/6	D77	5/6	ECH35	9/6	HABC80		PEN45	19/6	U45	9/6		9/1	
5Z4G	10/6	6K25	19/11	12AT6	7/6	35Z3	10/6	DAC32	11/1	ECH42	10/6		13/6	PEN45DD	U50	8/1	VT61A	5/1		
5Z4GT	12/6	6L1	23/3	12AT7	8/1	35Z4	6/6	DAF91	7/6	ECH81	9/1	HL23	10/6		26/6	U52	8/1	VT501	5/1	
6A7	26/6	6L6G	9/6	12AU6	23/3	35Z5SGT	9/1	DAF96	9/1	ECH83	13/11	HL23DD		PEN46	7/6	U54	19/11	W61M	26/6	
6A8	10/1	6L6M	12/6	12AU7	7/6	41MTL	8/1	DD41	13/11	ECL80	10/6		17/3	PEN383	23/3	U76	6/6	W76	6/6	
6A87	8/1	6L7GT	12/6	12AV6	12/7	42	23/3	DF33	11/1	ECL82	10/6	HL41	12/6	PEN453DD	U78	6/6	W81M	6/1		
6A88	10/6	6L18	13/1	12AX7	8/1	43	12/6	DF66	15/1	ECL83	19/3	HL41DD			33/2	U107	16/7	W107	15/3	
6AC7	6/6	6L19	23/3	12BA6	8/1	50C5	12/6	DF70	15/1	EF9	23/3		19/3	PEN/DD	U191	16/7	W729	18/7		
6AG5	6/6	6LD3	8/6	12B86	10/1	50CD6G		DF91	6/1	EF22	14/1	HL42DD			30/20	33/2	U201	16/7	X24M	24/7
6AK5	8/1	6LD20	15/11	12BH7	21/3			DF96	9/1	EF36	6/1		19/3	PL33	19/3	U251	14/1	X31	26/6	
6AL5	5/6	6N7	8/1	12E1	30/1	50L6GT	9/6	DF97	9/1	EF37A	8/1	HN309	24/7	PL36	14/1	U281	19/11	X41	15/1	
6AM6	5/6	6P1	19/3	12J5GT	4/6	53KU	19/11	DH30	15/6	EF39	5/6	HVR2	20/1	PL38	26/6	U282	22/7	X61(C)	12/6	
6AQS	8/6	6P25	12/6	12J7GT	10/6	72	4/6	DH63	8/1	EF40	15/1	HVR2A	6/1	PL81	12/6	301	23/3	X61M	26/6	
6AT6	10/6	6Q2B	26/6	12K5	17/11	75	24/7	DH63(M6)	15/6	EF41	9/6	KF35	8/6	PL82	8/1	U29	14/1	X62	10/6	
6AU6	8/6	6Q7G	8/1	12K7GT	12/6			EF42	11/6	EF42	11/6	KK32	21/11	PL83	9/1	U339	16/7	X65	12/6	
6AV6	12/7	6Q7GT	11/1	12K8GT	14/7	78	8/6	DH76	6/6	EF50(A)	7/1	KL35	8/6	PL84	12/8	U403	16/7	X66	12/6	
6B7	10/6	6R70	10/6	12Q7GT	6/6	80	9/1	DH77	8/6	EF50(E)	5/1	KLL32	24/7	PL820	18/7	U404	8/6	X76M	14/1	
6BBG	4/6	6SA7GT	8/6	12SA7	8/6	83	15/1	DH101	28/6	EF54	5/1	KT2	5/1	PM2B	12/6	U801	29/10	X78	21/3	
6BBGT	5/1	6SCT	10/6	12SCT	8/6	85V	12/6	DH107	13/11	EF73	10/6	KT33C	10/1	PM12	6/6	U4020	16/7	X79	21/3	
6BA6	7/6	6S7GT	8/6	12SCT	8/6	85A2	15/1	DK32	15/1	EF80	7/1	KT36	29/10	PM12M	6/6	UA08C80	9/1	X101	33/2	
6BE6	7/6	6S7HGT	8/6	12SHT	8/6	150B2	15/1	DK40	21/3	EF85	7/1	KT41	26/6	PM24M	21/3	UA4F2	9/6	X109	17/3	
6BG6G	23/3	6S7GT	8/1	12SHT	8/6	185B7	33/2	DK91	7/6	EF86	12/6	KT44	15/1	PX4	10/6	UBA1	12/1	XD(1.5)	6/6	
6BH6	9/1	6S7GT	8/1	12SK7	8/6	185B7A	33/2	DK92	10/6	EF89	9/1	KT61	12/6	PX25	59/8	UBC41	8/6	XFG1	18/1	
6B8	7/6	6SL7GT	8/1	12SQ	12/6	1304	10/6	DK96	9/1	EF91	5/6	KT63	7/1	PY31	16/7	UBC81	11/4	XFY12	9/6	
6BQ7A	15/1	6SN7GT	6/6	12SR7	8/6	305	10/6	DL33	9/6	EF92	5/6	KT66	15/1	PY32	17/11	UBF80	9/1	XFY34	17/6	
6BR7	23/3	6SQ7GT	9/1	12Y4	10/6	402Pen/A		DL66	15/1	EF97	13/3	KT88	22/6	PY80	7/6	UBF89	9/1	XH(1.5)	6/6	
6BW6	10/6	6S57GT	8/1	14B6	19/3		23/3	DL68	15/1	EF98	13/3	KTW61	8/1	PY81	9/1	UBL21	23/3	XSG(1.5)		
6BW7	7/1	6U4GT	12/6	14H7	23/3	807	7/6	DL92	7/6	EK32	8/6	KTV62	8/1	PY82	8/1	UCB84	14/7			
6BX6	7/1	6U5G	7/6	14S7	27/10	956	3/1	DL94	7/6	EL32	5/6	KTV63	8/1	PY83	9/6	UCG85	16/7	Y63	7/6	
6C4	7/1	6V7G	8/1	15D1	26/6	1821	17/6	DL96	9/1	EL33	12/6	KTZ41	8/1	PZ23	19/11	UCF80	16/7	Z63	10/6	
6C5G	6/6	6V6G	7/1	18	23/3	5763	12/6	DM70	7/6	EL34	15/1	KTZ63	10/6	Q21	7/1	UCH21	23/3	Z66	20/6	
6C6	6/6	6V6GTG	8/1	19AQ5	10/6	7193	5/1	EA50	2/1	EL38	26/6	L63	6/1	QP25	15/1	UCH42	9/6	Z77	5/6	

FULL RANGE OF TRANSISTORS AND GERMANIUM DIODES IN STOCK. TECHNICAL DATA AND PRICES FREE ON RECEIPT OF SELF-ADDRESSED ENVELOPE.

NEW METAL RECTIFIERS—FULLY GUARANTEED

DRM-1B	15/4	RM-1	7/1	WX3	3/6	14A100	27/1	14RA 1-2-8-2	17/6	16RE 2-1-8-1	8/6
DRM-2B	16/2	RM-2	9/1	WX4	3/6	14A124	28/1	14RA 1-2-8-3	21/1		

COMPLETELY RE-SCREENED C·R·T'S

Midland Tubes Ltd., offer a new service in the rebuilding of C.R. Tubes.

Each tube is completely re-screened and aluminised, and fitted with a new Gun Unit. All types—Triodes to Electrostatics.

12 months' Guarantee and Free, immediate delivery.

Please write or 'phone.

MIDLAND TUBES LIMITED

37 George Street, Manchester, 1. Tel.: Central 4568.



FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee "NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/20), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT ?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.
A.M.I.C.E.
A.M.I. Prod. E.
A.M.I.M.I.
I.L.O.B.
A.F.R. Ae. S.
B.Sc.
A.M. Brit. I.R.E.
City & Guilds
Gen. Dept. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page 'ENGINEERING OPPORTUNITIES' (Write if you prefer not to cut page)

NAME

ADDRESS


.....

.....

SUBJECT OR EXAM THAT INTERESTS ME

(SE 20.)

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

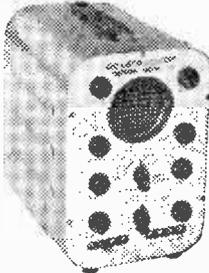D.C. OSCILLOSCOPE

A.C. MAINS 200-250 VOLTS
SIMPLIFIED SERVICING
PROBLEMS WHEN USING

THE
'TESTGEAR' SCOPE

3in. D.C. OSCILLOSCOPE

Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable differential

Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transients under operating conditions where maintenance of D.C. level is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking I.V. Line (0/P Transformers, etc.); Provision for external X 1/4 and CRT. Brightness Modulation. Size 10in. high, 6 1/2in. wide, 9in. deep. Wgt. 1 1/2 lbs. £15.15.0, plus P. & P. 7/6, or 30/- deposit, plus P & P. 7/6 and 12 monthly payments of 29/6.

FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBES

ALIGNMENT ANALYSER TYPE MC12

A.C. mains 200/250V. Provides: "Wobulator" (Sweep Frequency) operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s-80 Mc/s. Capacitance Measurement. Two ranges provided 0-60pF and 0-120pF. Special Facility enables true resonant frequency of any tuned ckt. I.F. transformer, etc., to be rapidly determined. Cash price £6.19.6, plus 5/- P. & P. H.P. terms 25/- deposit plus 5/- P. & P. and six monthly payments of 21/6



WOLSEY 3-ELEMENT FOLDED DIPOLE

I.T.V. Aerial less mounting bracket for External use, complete with 12 yds. of coaxial cable, 15/-; 4 element, 17/6; 5 element, 25/- . P. & P. on above, 3/6.

E.H.T. Smoothing Condenser 500 p.f., 18 KV. D.C. 1/6 working,

LINE E.H.T. TRANSFORMER

By famous manufacturer. 14 Kv. Complete with built-in line and width controls. Winding for EY51 Rectifier. 19/6 Plus P. & P. 2/6

LINE E.H.T. TRANSFORMER

With built-in line and width control and winding for EY51. 14 KV. Scan coil, 90° deflection, on ferrite yokes. Frame O.P. transformer 500 p.f. 18 KV. smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram. 29/6 Plus P. & P.

Focus Magnet suitable for the above (state tube). 10/- Plus 2/6 P. & P.
17in. PERSPEX MASK, 8/6. Plus 2/6 P. & P.

F.M. TUNER UNIT

Permeability tuned, by famous German manufacturer. Coverage 88-100 Mc/s. Complete with ECC85, size 4in. x 2in. x 2in.


25/- P. & P. Circuit Diagram 1/-, 1/6. FREE with Unit.

10.7Mc/s. I.F. and Discriminator Coil, 4/- pair.

MAINS TRANSFORMERS

All with tapped primaries. 200-250 volts, 0-180, 180, 200 v., 60 ma., 6.3 v. 2 amps, 10/6, 320-0-320 v. 75 ma., 6.3 v. 2.5 amp., 5 v. 2 amp., 10/6, 250-0-250, 80 ma. 6.3 v. 2 amp., 6.3 v. 1 amp., 10/6. Postage and packing on the above, 3/-.

AC/DC POCKET MULTI-METER KIT

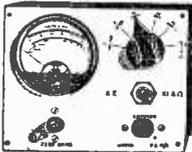

Comprising 2in. moving coil meter scale calibrated in AC/DC volts, ohms and milliamps. Voltage range AC/DC 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel range switch, wire-wound pot (for ohms zero setting), toggle switch, resistor and rectifier. In grey hammer finish case.

19/6 Plus Built and tested P. & P. 1/6 7/8 extra.

Point to point wiring diagram 1/-, free with kit.

SIGNAL GENERATORS




£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6 1/2in. x 5 1/2in. grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal Modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 100 milli-volts.

C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing, 5/-


Coverage 120 Kc/s-84 Mc/s. Metal case 10in. x 6 1/2in. x 4 1/2in. Size of scale, 6 1/2in. x 3 1/2in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30%, modulated or unmodulated R.F. output continuously variable. 100 milli-volts. C.W. and mod. switch variable A.D. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%

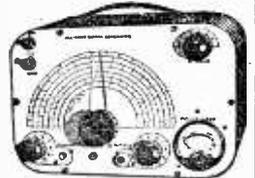

SIGNAL & PATTERN GENERATOR

£6.19.6. P. & P. 5/-.

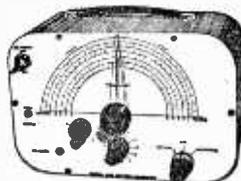Or 25/- deposit, P. & P. 5/- and 6 monthly payments of 21/6. Coverage 7.6 Mc/s-210 Mc/s. In five bands, all on fundamentals, slow motion tuning audio output, 3 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1% A.C. mains 200-250 v.




CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series). I.F. 16-19 or 33-38. Also can be modified as an aerial converter (instructions supplied). Complete with knobs.

22/6 Plus 3/6 P. & P.

HEATER TRANSFORMER

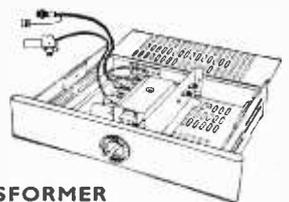To suit the above, 200-250 v., 6/-, Plus 1/6 P. & P.



8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER

A.C. mains 200-250 v. Size 10 1/2in. x 6 1/2in. x 2 1/2in. Incorporating 6 valves. H.F. pen., 2 triodes, 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feed back. Two inputs, mike and gram., and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 Kcs., -2 db; 4 db down to 20 Kcs. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records, musical instruments such as Guitars, etc. £4.19.6 Plus P. & P. 7/6.

Or 20/- deposit Plus P. & P. 7/6, and 4 monthly payments of 23/-.

RADIO & T.V. COMPONENTS (Acton) LTD.

23, HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

Every keen radio man must see it!

NOW COVERS RADIO-ASTRONOMY

FREE for 7 days

AND WITHOUT OBLIGATION

The long-awaited New Edition of this practical engineering and servicing work is now ready for you. If you are a Radio Engineer, Technician, Mechanic, Instructor, Student or Keen Amateur, this great wealth of data will prove invaluable. Newest developments and techniques are included—from latest transistors to low noise microwave devices; from advances in quality reception to radio-astronomy and space probe communication. Be up-to-date by sending to-day for FREE EXAMINATION. This New Edition is of absorbing interest to you—*post coupon to-day!*

PACKED WITH DATA FOR DAY-TO-DAY NEEDS—WRITTEN BY 50 SPECIALISTS

Formulae. Calculations. Communication Theory. Electron Optics. Colour, Projection and Industrial TV. Materials. Studio Equipment. Transmitter Power Plant. V.H.F. Transmitter-Receiver Equipment. Amateur Equipment. Waveguides. Receiver Design. Radio Links. Broad-band Systems. Radio Navigation & Radar. Radio Astronomy & Satellite Communication. Valves. Cathode-Ray Tubes. Transistors. Crystal diodes. Resistors. Capacitors. Inductors. Transformers. Microphones. Gramophone Mechanisms. Loudspeakers. Interference. Recording. Measuring Instruments. Installation & Servicing. Ionospheric Forecasting. Units & Symbols. Developments, etc.

SEE THESE PRACTICAL FEATURES

Latest types of Transistors and their use • Single-Sideband Transmitters • V.H.F. Scatter & Meteor Burst Communication Systems • Travelling Wave Tubes • Radio Astronomy • Modern Car Radio Receivers • Stereophonic Reproduction and Recording Techniques • TV. & Radio—latest Practice in Receiver Installation and Servicing • New Air Navigation Aids.

Broadcasting • Communications • Navigation • Radar, etc.



Over 1,800 Pages

47 Main Sections

2,000 DIAGRAMS,
TABLES, FORMULÆ &
CALCULATIONS

Many Exciting New
Features

JUDGE FOR YOURSELF

Post Now
for 7 day
Free Test!

GEORGE NEWNES, LTD., 15-17, LONG ACRE, LONDON, W.C.99.

Please send me Newnes RADIO AND TELEVISION ENGINEERS' REFERENCE BOOK without obligation to purchase. I will either return the work within eight days or I will send the first payment of 5/- eight days after delivery, then ten monthly subscriptions of 10/-, until the sum of 105/- has been paid. Cash price within eight days is 100/-.

Name

Address

Occupation


Your Signature
(Or your Parent signs if you are under 21)

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

RB34

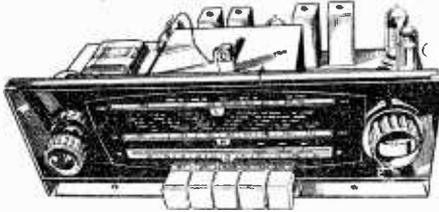BRAND NEW AM/FM (V.H.F.) CHASSIS AT £13.6.8. (P. & P. 10/-)



Why buy a F.M. Tuner at the same price?
Tapped input 220-225 v. and 226-250 v. A.C. ONLY.
Chassis size 15 x 8 1/2 x 5 1/2 in. high. New manufacture.
Dial 1 1/4 x 4 in. in gold and black.
Pick-up. Extension Speaker, Ae. E., and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. With all valves & O.P. Transformer. Tone-control fitted.
Covers 1,000-1,900 M.C. 200-500 M.C.: 88-49 Mc/s.
Valves E290 rect., ECC81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit chassis, 47/6.
10 x 7 1/2 in. ELLIPTICAL SPEAKER, 20/-.

TERMS:—(Chassis) £4.16.8 down—10/- carr.—and 6 Monthly Payments of 30/-, or with Cabinet & Speaker £5.9.2 down and 7 Monthly Payments of 32/-.

We are specialists in ITA Converters. Our converters give direct switching ITA to BBC, metal rectifier, co-axial plug. Can be fitted in 5-10 mins., and need no alteration to your set. ALL AREAS. ALL SETS. ALL CHANNELS. 12 months' guarantee (3 months on valves).


"READY TO USE" ITA CONVERTER

Separate gain controls. Valves PCF80 and PCC84. Switch positions ITA (1)—ITA (2)—BBC. Bakelite moulded cabinet. 8 1/2 x 4 x 6 in. £5.5.0. P. & P. 3/-.




For the last 50 ITA Converters of this type (Brand New and Fully Guaranteed) we will accept the "Below Cost" figure of ONLY 60/- (3/- P. & P.) Reduced from 24/7.6.

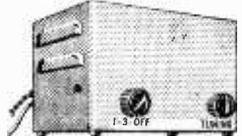18v. valves ECC81—grey hammer finish—Switch positions OFF, ITA, BBC. Own Power supply. BUY IT NOW.



60/- (3/- P & P.)

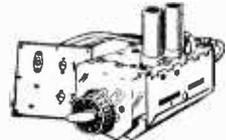THE BRAYHEAD TURRET TUNER, £7.7.0 post free. Complete with booklet and fitting instructions. State set and model No. when ordering. Converts your 5-channel BBC only set to receive ITA as well.



ITA AERIALS clipping to existing mast 1-2 in. dia. 3-element. 27/-; 5-el. 35/-; 9-el. 55/-; Loft mounting. 3-el. 20/-; 5 el. 27/6; Combined single BBC and 5-el. ITA. 75/- with chimney lashings; Co-axial cable semi-air-spaced. 8d. yd. or 20 yds., 12/6. Aerial and cable prices carr. paid.

50 SILVERED MICA AND CERAMIC CONDENSERS, 10/-, 50 RESISTORS, 5/-, ALL NEW.

NEW WAXED TUBULARS, 350 v. or above. 3 of each. .001, .002, .005, .01, .02, .05, .1 mF. Total 21 for 4/6, post paid.



NEW ITA AND BBC TUNER. By well-known manufacturer for superhet TVs with 35-38 Mc/s I.F. For all areas; covers all 13 channels. Switch gives BBC and two ITA selections. Suits G.E.C. sets BT4543, 4544, 5146, 5147, 5543, 5642 and 8641 without alteration. Easily adapted as aerial converter, and instructions can be provided free. Has ITA and BBC co-axial sockets and separate gain controls. WITH VALVES PCF80 and PCC84, 22/6 (P. & P. 3/-). Some without valves at only 12/6 (P. & P. 3/-).




GRAMOPHONE AMPLIFIER with 5 in. SPEAKER. On Fabric-covered Baffle 12 1/2 x 5 1/2. Mains and Output Transformers. Metal Rectifier. ECL82 Valve. Tone and Volume Controls. On/Off switch. Plenty of Volume. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.

ONLY 57/-, post 3/-

BEEC "PIONEER" RADIO IN MAKER'S CARTON. Valves DK96, DP96, DAF96, DL96. Beec Ever-Ready Battery B103. 18/6 extra. Two Short Wavebands 2.5 to 7 Mc/s and 6.5 to 17 Mc/s. Cabinet, 12" x 7 1/2" x 6". **ONLY £4.15.0** (2/6 p. & p.). In kit form with instructions and fully wired coil pack. Two Short Wavebands 24. One M.W. and S.W. £4.5.0. Plus 2/6 p. & p. Separate items supplied.




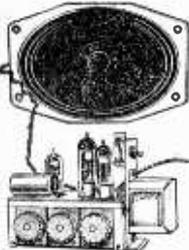Delivery by return. C.O.D. 2/- extra. Terms: Cash with order or one-third down and balance plus 7/6 (up to £7.10.0) in four equal monthly payments. Balance over £7.10.0 add 1/- in £1 and pay in not more than 6 monthly payments. See special terms for A.M.-F.M. chassis. All new goods unless stated. Send 6d. for 16-page catalogue.



3-VALVE AMPLIFIER (INCL. RECT.) Capable of giving 6 watts. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2 x 3 x 2 1/2 in.; with 7 x 4 in. elliptical speaker or 6 1/2 in. round (Goodmans); state which.

Only 67/- (3/- P. & P.)

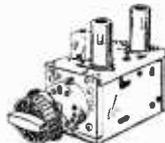

BRAND NEW INCREMENTAL TURRET TUNER by famous manufacturer for 35 to 38 Mc/s with knobs. Valves PCC84 and PCF80, or valves UCC84 and UCF80. LAST FEW DOZ. REDUCED ONLY 40/-.


ITA TABLE TOP AERIAL. An ITA table top aerial with amazing performance. The Wolsey Hi-Q at 19/6 (2/6 post). Gives good reception up to 20 miles, and has cross-over unit in base with socket for BBC aerial. Same model but very slightly tarnished for **ONLY 12/6** (2/6 post).



PERSPEX UNSCRATCHED. (Post 2/- each or 6 post free.) 12 1/2 x 9 1/2 x 1 in. clear, 4/6; 14 1/2 x 11 x 1 in. clear, 5/-; 15 x 12 x 1 in. tinted, 6/-; 17 x 13 1/2 x 3/16 in. clear, 7/- (Also 15 x 12 in. slightly scratched at 3/-).

AUTOMATIC RECORD CHANGERS. COLLARO CONQUEST with manual play also. Turnover crystal pick-up. 4-speed. A.C. mains 200-250 v., see illus.

£7.10.0 (5/- P. & P.)

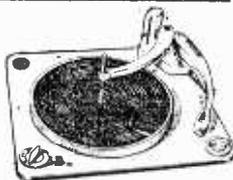

GLADSTONE RADIO

or callers to 3 Church Road, Bristol 5 Tel. 51207


58A HIGH STREET, CAMBERLEY, SURREY.

(Camberley closed Sats.)

Tel. 22791



Practical Television

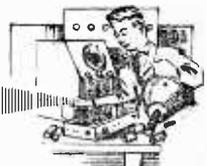

& TELEVISION TIMES

Vol. 10 No. 114

EVERY MONTH

MARCH, 1960

Editorial and Advertisement Offices:
PRACTICAL TELEVISION
George Newnes, Ltd., Tower House,
Southampton Street, Strand, W.C.2.

© George Newnes Ltd., 1960.

Phone: Temple Bar 4363
Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - £12.0 per annum
Abroad - - £10.6 per annum
Canada - - 19s. per annum

CONTENTS:

	Page
Editorial	283
Guided Grid Valves	284
The EF50 Converter	285
Short Cuts with a Multi- meter	289
Resolution	291
Making Slot Aerials	292
Telenevs	294
Western Summit TV	296
Voltage Regulation	297
Servicing TV Receivers	301
The TV Centre	304
Frame Sync Separator	307
Sitting TV Aerials	311
Underneath the Dipole	315
Letters to the Editor	319
Trade News	320
Your Problems Solved	323

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

EUROVISION

THE interchange of live television programmes between European countries has developed rapidly since the early attempts made in 1954, and the communication engineer has been presented with some interesting technical problems. Exchanges first took place in 1952 and 1953 and earlier in August 1950 when the BBC carried out two outside broadcasts from Calais. This was the first occasion on which television had been brought to British viewers from outside the United Kingdom. The first programme to be simultaneously broadcast in two countries, France and Great Britain, took place in July 1952. This was made possible by the development of apparatus for converting from the French 819-line picture to the British 405-line picture and by the extension of the French television network as far as Lille, thus reducing the number of temporary radio links which had to be installed to connect Paris with London.


In 1954 a proposal was put to, and approved by, the Administrative Council of the European Broadcasting Union that the Union should assume responsibility for planning and supervising programme interchanges. With the increasing complexity of Eurovision, a technical co-ordination centre was needed, and this was established in Brussels in January 1956. Initially its function, as its title suggests, was largely passive but its functions became progressively more active as time went by. The Eurovision control centre, as it is more now correctly styled, is now analogous to the national centres which control the various national networks.

In recent years radio-link equipment using decimetric and centimetric waves has made possible a much more reliable system of vision links. Methods of measuring and assessing distortion on long links have now been drawn up and adopted and methods have been devised for reducing and correcting this distortion. Improvements are continually being made although a more sophisticated method of transcription from one line standard to another is still needed.

The development of Eurovision has shown how the engineer, by facilitating the exchange of ideas between countries, can improve co-operation on the international plane. A few sporadic exchanges have taken place with the countries of Eastern Europe and it seems likely that permanent links between Western and Eastern Europe will be set up in the near future. The handicap in the establishment of a similar television link with North America is likely to be its cost but meanwhile a scheme for the slow speed transmission of film over the transatlantic telephone cable has already been operated.

Only a matter of ten years ago, no communication engineer could have predicted the continental coverage of television; it is to be hoped that in ten years from now the coverage will be world wide.

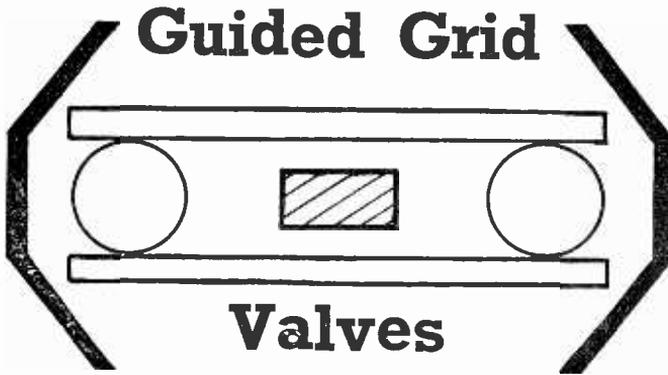Our next issue, dated April, will be published on March 22nd




A NEW TYPE FOR HIGH GAIN

THE trend in modern television design is to reduce the size of components and receivers so that entertainment can be obtained without the apparatus taking up valuable space. The size of picture tubes is gradually being reduced so that the large screen types need only shallow cabinets. Reductions in the sizes of other sections of the receiver, such as I.F. strips and time base units have been made, but it is only recently that the design engineers have begun to make smaller tuner units.

New Turret

Several new British designs have been announced which are now widely used and a new turret tuner is now being marketed in the U.S.A. and is substantially smaller than other current types. The reduction in size is obtained for the most part by using a new type of valve known as a "guided grid" valve. The new miniature turret occupies only a quarter of the volume of earlier tuners but has a

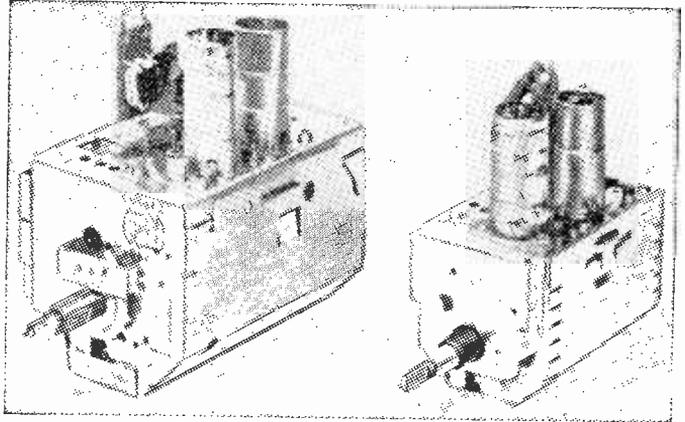current (Fig. 1). Their inclusion in the valve reduces the anode-to-grid capacitance, thereby increasing the anode impedance. Radiation from the local oscillator into the aerial circuit is also



The tuner on the left uses conventional valves while the smaller tuner on the right uses a frame grid valve.

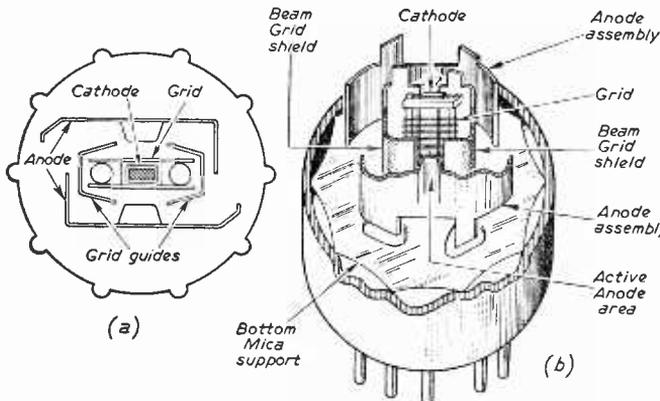


Fig. 1.—Internal construction of guided grid valves.

reduced and with the increased anode impedance the coupling coil in the anode circuit is less heavily damped. As a result, the signal-to-noise ratio of the tuner is improved and its gain is considerably higher.

Although guided grid valves are not available here as yet, no doubt British manufacturers will introduce suitable types in the future. The introduction of frame grid valves in this country has enabled substantial improvements to be made in TV front end design. With these new valves excellent reception can be obtained with simpler, neater, and less bulky tuners and the increase in efficiency enables reception to be obtained even at the limits of the fringe areas.

The EF50 Converter

AN INEXPENSIVE HIGH-GAIN UNIT

IN a large number of published designs there is a feeling by the user that more gain is required, but there is no means of "turning up the wick" apart from adding an I.F. or R.F. amplifier to the converter. With the circuit about to be described, in a low-lying city, 30 miles from the transmitter, the gain can be increased until the picture goes negative, and this is not a swamp area, as a five element array is necessary for a good picture. The grain is not normally noticeable at usual viewing distances, and the picture is very sharp and clear, with full transmitted bandwidth.

Contrast Controls

Readers with contrast controls in the first R.F. stages of their receivers would be wise to fit one in the last I.F. or video output stage, and then the first R.F. stage contrast would become the sensitivity control and in most cases could be left at maximum, and the new control finally operated to obtain correct contrast on BBC programmes and left alone. By this method the sound on the BBC is not affected and, more important, neither is the sound output from the converter affected. With no perceptible oscillator drift, and the contrast controls arranged as above, the writer is in a rather fortunate position of only having to

turn the band switch to change the programmes, no other adjustments being required to brilliance or contrast controls.

The writer, although just in the service area a mile uphill from a city centre, is living in an awkward spot where five element aerials are necessary, and only a mile away on higher ground strong signals of Band III are obtained on an ordinary BBC "H" aerial by using the third harmonic (Channel 4 and 8).

Converters with modern valves specially designed for Band III work quite satisfactorily here, but it is difficult to make a conventional circuit work with EF50 valves. Many circuits were tried such as EF50 R.F. and EF50 osc./mix. two earthed grid triodes EC54s in cascade, and EF50 osc./mix, two EF54 R.F. stages and EF50 osc./mix, but none was really satisfactory until R.F. mixer and separate oscillator were tried, and even then the signal was very poor until the R.F. cathode decoupling condenser was removed and regeneration was controlled by a variable potentiometer. The signal then improved 100 per cent. At first glance, by removing the condenser the characteristics of the EF50 are altered; the transit time, gain, mutual conductance should drop and feedback be introduced. In fact, the whole thing should be a dead loss on Band III, but in this case it is not so. Theoretically it should

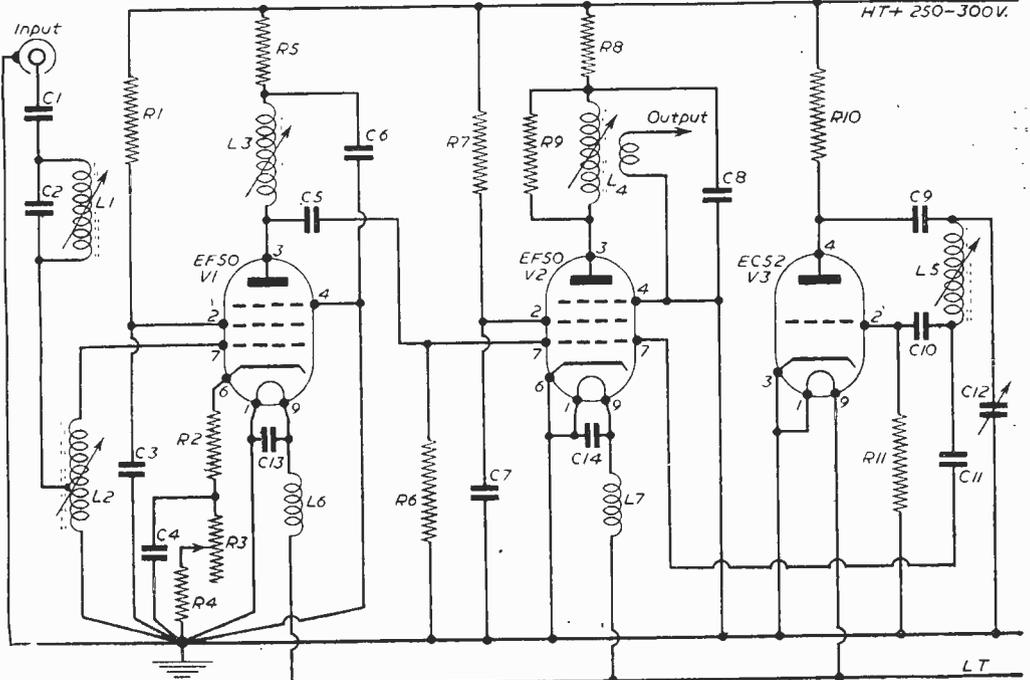


Fig. 1.—The complete circuit diagram.

work more efficiently with a low capacity of about 50pF than without one, and a low resistor, but in practice this was not so.

The design requires to be well thought out in advance to keep the wires from the components to a minimum of $\frac{1}{4}$ in. if possible. This is very

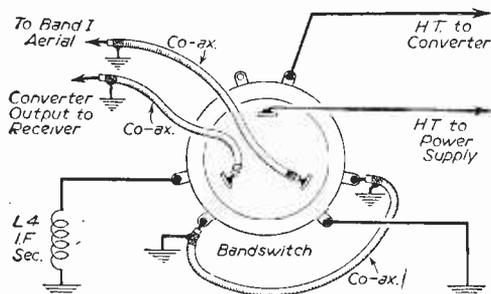


Fig. 2.—The wiring of the bandswitch.

important, and great losses can occur if the wires are $\frac{1}{4}$ in. or more in certain parts of the circuit. With these valves the screened grid decoupling condenser C3 is one example in the first stage. The wire from this condenser to chassis should be as short as possible, and must be to the same tag as the earthy end of the first R.F. coil L2. The same applies to R2 which must be wired close to the cathode pin, as it is part of the tuned circuit. On C4 the earthy end wire must be very short, and taken to the same chassis tag as C3.

The first stage in converters seems to be the most critical and if weak signals are encountered the design of this stage is usually responsible. The mixer and oscillator stages are not critical provided reasonable precautions are taken.

Power Supply

The set will work quite well with lower gain on 200V, but at 250V, or higher, the gain is considerably increased. The converter has worked satisfactorily at 300V up to 45 miles from the transmitter,

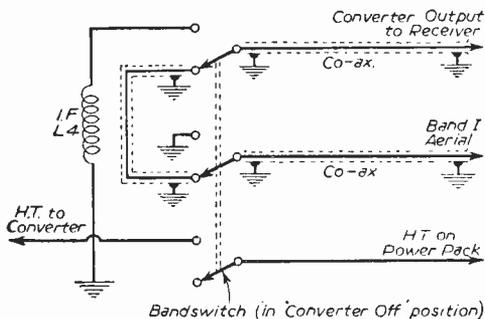


Fig. 3.—Circuit of the bandswitch.

and may be satisfactory beyond this mileage under suitable receiving conditions. Raising the H.T. from 240V to 300V appears to have very little effect on the volume of sound but the vision is very much affected. The L.T. is 6.3V at 1A. The power pack is isolated from mains for safety, and transformer fed.

The Circuit

This is a three valve arrangement using an EF50 as R.F. amplifier, an EF50 as the mixer, and an EC52 (VR137) as the oscillator. The circuit is designed for 80Ω co-axial input. Capacitor C1 in the aerial lead has a marked effect on signal strength and helps to improve matching to the input. A value of 1000pF was found to give best results, but as this is rather higher than usual a variable trimmer can be wired in its place if desired to find the correct value to suit individual cases. This feeds into a filter circuit L1 and C2 and to the grid input coil L2, which is tapped $\frac{1}{2}$ turn from the earthy end.

No improvement was found by winding a separate primary over L2 for the aerial input,

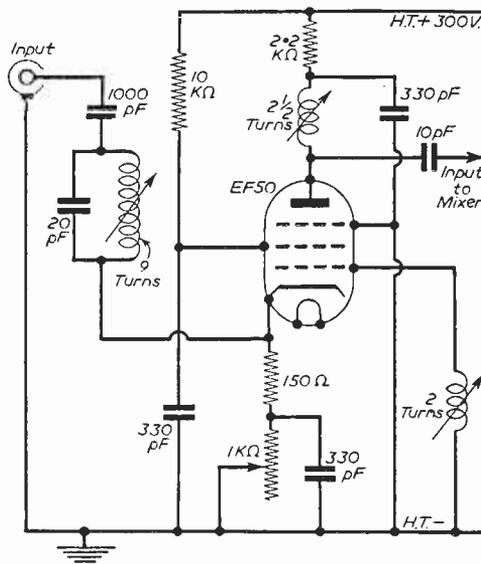


Fig. 4.—An alternative circuit for the input stage.

although a separate primary of 2 turns will be required for correct input matching if the cable is 300Ω.

The cathode is not decoupled in the usual way, but C4 is connected between R2 and R3 and the gain controlled by R3. By omitting the usual condenser direct from the cathode to the chassis, feedback is introduced, and also the input resistance increased, thus reducing the damping on the tuned circuit. As the input resistance of the EF50 is only a few hundred ohms at 200Mc/s, losses would be considerable if 1.000pF was introduced into the cathode circuit. The EF54 has an input impedance of some 700Ω at 200Mc/s, and this valve gives an improvement over the EF50 for V.H.F. work. The EF54 has the suppressor grid connected internally to the cathode, and was not found as suitable for this circuit as the EF50. Leaving the cathode completely unbypassed reduces the mutual conductance slightly but this seems to be well compensated by an increase in input resistance.

The output of V1 goes direct to C5, the coupling condenser, and to the mixer grid.

COMPONENTS LIST for Fig. 1


R110k	C1—0.001 μ F
R2—150 Ω	C2—20pF
R3—300 Ω	C3—330pF
R4—200 Ω	C4—330pF
R5—2.2k	C5—10pF
R6—100k	C6—330pF
R7—100k	C7—330pF
R8—2.2k	C8—330pF
R9—4.7k	C9—50pF (neg. temp. co-efficient)
R10—10k	C10—15pF
R11—27k	C11—2pF
A11—1W	C12—0.20pF
R10—1W	C13—100pF
	C14—100pF
	C1—Var. or Mica.
	All others ceramic.

The oscillator V3 is very stable, and no drift was perceptible from the moment of switching on to switching off, even after several weeks' use, which is most unusual at these frequencies. The oscillator is not the usual Colpitts type as the Hartley type was found to be better. This valve operates with two condensers, C9 and C10, to couple the oscillator coil L5 to V3. C9 has negative temperature coefficient. C12 is the manual oscillator trimmer. The output from the oscillator is taken through C11 and fed into the mixer grid.

Output

The converted output is taken from the I.F. transformer secondary (which is in the anode circuit of V2), and after switching is fed into the receiver.

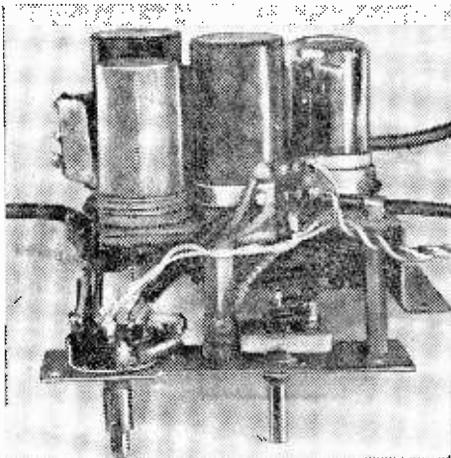The 330pF decoupling condensers were found to be adequate. Larger ones up to 1,000pF were tried and can be used without affecting performance. All the other condenser and resistor valves must remain as stated. "Red" Sylvania EF50s were found to be much better than the "silver" type and more stable, and gave better contact,



The completed converter

especially the spigot which is of different metal and does not oxidise so rapidly.

Ceramic valveholders were used to reduce losses. The sockets are silvered and turn black. Some of this can be removed with carbon tetrachloride, and a flat nail file very lightly passed up and down the sockets a few times removes the rest. Do not forget the centre spigot hole, and pinch the spigot contacts together. Clean all the valve pins the same way and make sure the aluminium ring on the valve base which holds the spigot is making good contact with the valve can, as both these parts film over with age.

Screening

At the start all the stages were screened from one another and screens were also placed across the valveholders. All this screening was removed

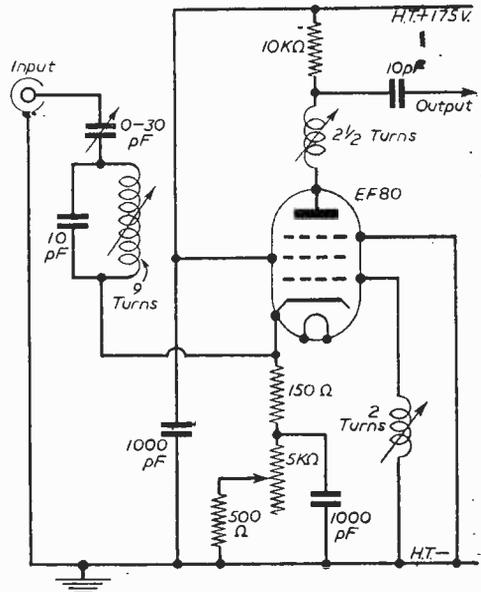


Fig. 5.—Circuit for an EF80 input stage.

piece by piece and now only coils L1 and L4 are "canned," with no ill effect on performance.

The valveholder bolts are longer than usual and pass through the valve retainer ring, the valveholder collar, the chassis, and, underneath, the solder tag, nut, Aladdin coil former, washer and nut. This enables the coils to be as near as possible to the valves. On coils L2, L3, L5, only one bolt was required when the thick wire was soldered in place. No holes were drilled through the chassis for the cores as these were found not to be necessary. Coils L1, L4 were held by two bolts each and screened to prevent BBC pick-up.

The formers are 1/4 in. Aladdin with purple cores. When the converter is working satisfactorily the cores can be removed and a thin piece of elastic inserted down the inside of the former and the cores put back. This is necessary, especially if the cores of L2, L5 are loose.

Wind the coils on 1/4 in. control spindle and press them on to the formers; as the formers are slightly over 1/4 in. the coils make a tight fit.

The heater chokes are wound on a thick knitting needle (plastic) which is also used for trimming purposes after filing to a screwdriver tip.

In weak signal areas increase R9 across L4 to 6k or remove it. It should be left in circuit wherever possible.

Patterning

BBC and ITV co-ax cables running side by side from the aerials have not been found to be the cause of patterning on ITV unless the cables have been cut or joined or extended. If the BBC cable is cut or extended use a proper cable joiner, not tape, as the cable inner must be screened. The Band I co-ax must always be shorted out when receiving ITV, or pronounced patterning will result. Switching the inner co-ax out of circuit or removing the plug is not effective.

Keep the output leads from the converter away from A.C. wiring in the power pack and mains wiring.

The filter coil L1 will overcome patterning from the BBC being fed into the unit. If patterning is experienced on BBC, fit a switch in the H.T. lead

COIL DATA								
Channel	L1	L2	L3	L4		L5	L6	L7
				Pri.	Sec.			
1	11	2	2½	11	3	5	10	10
2	10	2	2½	10	3	5	10	10
3	9	2	2½	9	2	5	10	10
4	8	2	2½	8	2	5	10	10
5	7	2	2½	7	2	5	10	10
	Close wound 28 s.w.g. s.c.	Space diam. wire tapped ½ turn earthy end 22 s.w.g. enamel	Space diam. wire 22 s.w.g. enamel	Close wound 28 s.w.g. s.c.	Close wound 28 s.w.g. s.c. spaced ¼ from primary		Close wound 26 s.w.g. enamel self-supporting	Same as L6

¼ in. Aladdin formers with purple cores.

from the converter power supply or in the mains lead. This is usually switched out automatically when the band switch is operated.

Although an ordinary 3-pole 3-way switch is used without screening, no patterning will be experienced if co-ax is used liberally. Connect the co-ax screening to the nearest possible points of the chassis or solder them to the metal pillars on the switch framework.

Wiring

The lead between the converter and the receiver should be as short as possible to prevent BBC pick-up causing patterning.

(Continued on page 298)

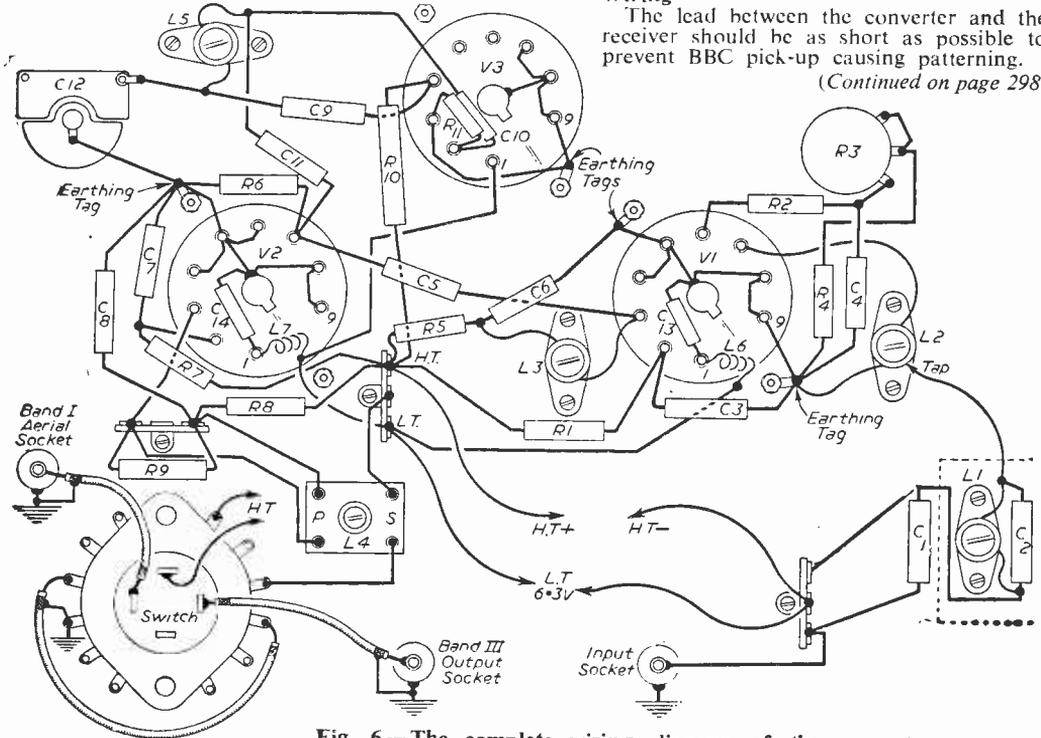


Fig. 6.—The complete wiring diagram of the converter.

Short Cuts with a Multimeter

PRACTICAL SERVICING HINTS

By L. E. Higgs

TELEVISION fault-finding with a multi-range meter calls mainly for voltage tests of valve feeds, occasional mains voltage checks and continuity of circuits, windings, components, etc. Quite properly, these constitute the bulk of diagnostic procedure. There are, however, a number of

and the possibility of a bad heater connection, makes the A.C. voltage test better if the connections to valves and parts are accessible. Here, the negative of the meter (500V A.C. range) is clipped on to the chassis and, with the other prod, the mains is traced along the volts dropper, through the thermistor, valve chain and from heater to heater until the break is detected. This often only takes a minute or so and there is no disturbance of the circuit and even inaccessible valves can be tested if the mains potential is found further down the heater chain. Should two or three valves be left untested by this method, then check them on the ohmmeter.

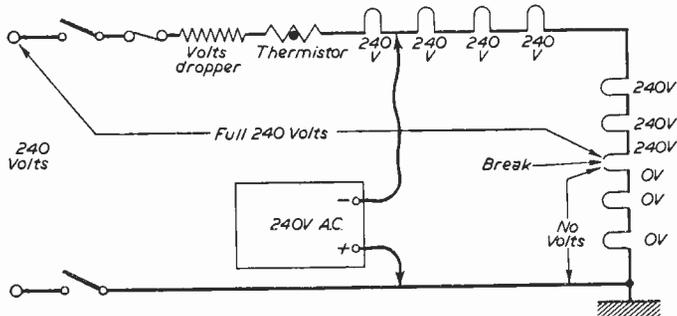


Fig. 1.—Testing heater chains.

checks and uses of the meter that can speed up the tracing of faults and in some cases save the requirement of another instrument or of tests by substitution, particularly when the internal resistance of each volts range is appreciated and allowed for in tests.

Current Ranges (Fig. 2)
The understandable reluctance of the harassed engineer to make current tests with their associated bother of switching off, breaking the circuit, connecting up, testing, and repair afterwards, if the test shows to be uninformative, makes the current ranges in quick servicing the least used.

Heater Chain Test (Fig. 1)

Many newcomers to fault finding when confronted with an open circuited heater chain start to withdraw the valves (not always one at a time) and test the heaters for continuity until the defective valve is found. This is sometimes the best way with certain sets. Generally, however, the possible damage to valve pins, top caps and air pipes and the incompleteness of the test which omits the thermistor, volts dropper, fuses, switch

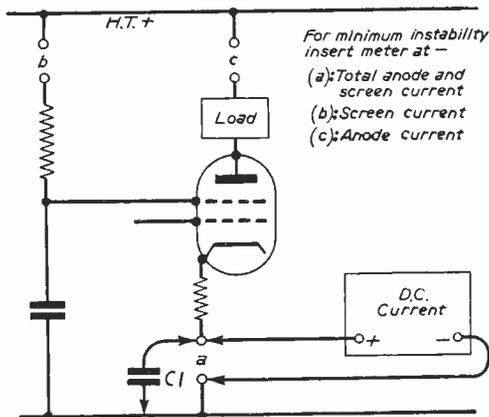


Fig. 2.—Measuring valve currents.

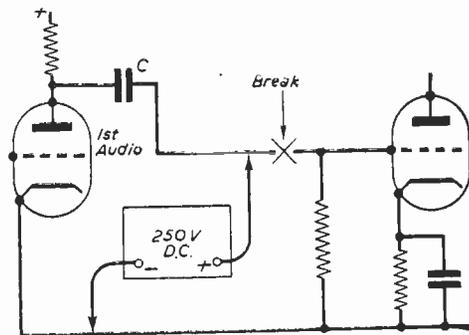


Fig. 3.—Testing coupling capacitors.

However, there are places where vital currents can be measured with no trouble; remove the fuses and substitute the meter. The fuses of some receivers give the line time base current; heater chain current (alternating); total receiver drain. A number of anode currents can be deduced easily by measuring the drop across known resistor loads by Ohm's law.

Always insert the meter at the earthy end of valve circuits and if instability is suspected owing to the disturbance then decouple with a capacitor across the circuit break—not across the meter terminals despite the convenience of this.

D.C. Volt Checks

Do not forget to check the cathode voltage, where applicable, after checking the anode and screen potentials. The voltage across the cathode resistor can be very informative, and from it the total valve current (screen plus anode) can be deduced easily by Ohm's law.

Leakage Meter (Fig. 3)

When a positive potential shows on an output valve grid, a leaking coupling capacitor, valve gas or inter-electrode shorts can be responsible. By making only one disconnection to the coupling capacitor, at the grid side, the grid can be isolated and by placing the meter (250V D.C. range) between the end of the capacitor and chassis, no voltage should show after the initial charging kick. A slight steady positive voltage proves a leaky capacitor almost as well as a megger test. If the condenser proves normal, a blob of solder from the iron makes good the only circuit disturbance.

Detuning Effects

Most of us make allowance for the meter drain when measuring in high impedance circuits, yet I am still surprised when checking an AVC voltage first with a 1000 Ω /V meter and then with a valve voltmeter. One showed approximately 10V, on tune, using the 400V range, yet the valve voltmeter

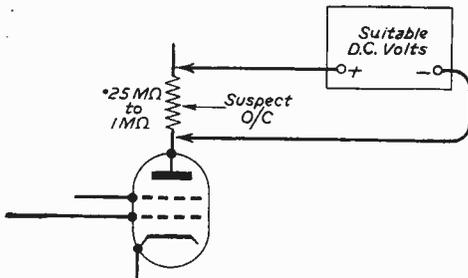


Fig. 4.—Using the meter as a substitute for a high resistance.

read 35V. Some of this difference was due to a detuning effect on the output tuned circuit caused by the meter leads. Always beware of the capacitive effect of the prod lead when probing R.F., I.F. and oscillator circuits or the frequency sensitive sections of the time bases in TV.

Substitute Resistor (Fig. 4)

The D.C. voltmeter can be used to advantage as a substitute grid leak, a high anode, or screen, resistance just by bridging it across the suspect component and switching to the appropriate range. If you need 0.5M, $\frac{1}{2}$ W, then switch to 500V on a 1000 Ω /V meter or 25V on a 20,000 Ω /V meter, but of course, start as usual with the highest volts range first and work down, in case too high a potential is dropped across the meter. Once a quick test like this proves the part faulty or eliminates it, work can continue. There is no need to find a substitute part, fit it in and probably remove it again.

Audio Tracer (Fig. 5)

To save switching on the 'scope or reaching for the phones, just to make sure a line or frame oscillator is functioning, or to monitor the presence of a video waveform on the cathode of a dead picture tube, try linking the top of the volume control to the point of test (preferably at a low H.T. potential), again using the 1000V D.C. range. This high resistance to a high gain point allows sufficient waveform to the volume control to give a clear audio indication in the speaker and any

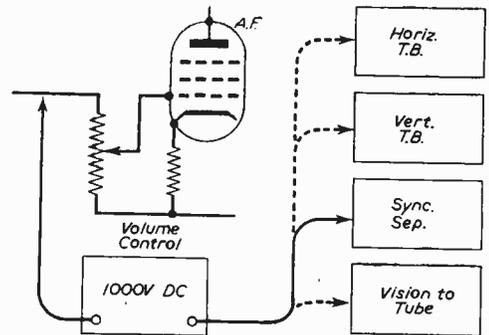


Fig. 5.—Monitoring audible waveforms by using the audio stages of the receiver.

D.C. present is made virtually harmless through this high leak. This is a good quick check to see if a circuit point has an audibly identifiable waveform present or not—and using only this convenient high meter resistance on its own flex leads, missing sync can often be traced.

APC Controls

The ohms range can be used when working on TV for purposes other than continuity and resistance measurements.

When checking the operation of an AGC line, switch on the meter to the ohms range, clip it to the chassis and touch the suspect line terminal with the probe. If the I.F. stages are biased back, the application of this low positive D.C. meter voltage will raise the gain and, if a reduction test is required in a line normally negative, then reversing the meter connections will show whether the control line is effective and the missing or excessive control voltage can be traced back. Manual contrast control lines can also be tested in this way as can missing bias on limiter diodes.

Electrolytics

Electrolytic capacitors can be tested (out of circuit) with the high ohms range, by connecting the meter, with correct polarity to the capacitor and observing the violence of the charging kick. A final high resistance reading shows a low leakage factor. With a little experience of various values and working voltages this method gives a quick check of electrolytics before fitting them into a circuit.

Resolution

3MC/S DEFINITION IS NOT ALWAYS AN ADVANTAGE

By J. K. Lockyer

THE "goodness" or quality of a picture is determined its definition, and by this we mean the faithfulness of the reproduction as compared with the original. We have a homely parallel in the pictures produced in periodicals. If a picture from a newspaper or magazine is closely examined with the aid of a magnifying glass, it will be seen to be constructed from a large number of elemental dots. In the dark areas the dots are very close together while in the lighter areas they are farther apart.

The dots are produced by the photographic process employed in making the plates for printing. In high-speed presses using fairly coarse paper such as newsprint the dots are larger and fewer in number; we cannot have too many dots as the process of printing at high speed on this class of paper would clog the plate and a very blurred reproduction would result.

Detail

When the speed of printing is slower and very finely graded paper is used then the dots can be made smaller and there will be many more of them. The practical result of this is that a picture produced on newsprint is lacking in fine detail.

The important point to note is that where the dots are smaller, a greater number are required to cover a given area, and the smaller the dots (or in other words the greater the number of picture elements) then the greater is the detail produced.

A similar reasoning exists in TV practice. For example, a receiver which has very good definition will show the strings attached to the puppets in a puppet show; a receiver with inferior definition will not show the strings and the viewer just does not see them and the puppets appear to be entirely self-activated.

In order to arrive at some standard of quality it has been stated that if the horizontal resolution is equal to the vertical resolution then satisfactory definition is achieved.

Estimating Bandwidth

In the 405 line system using interlaced scanning we have in each half cycle 202½ lines. Of these lines 14 are taken up for synchronising purposes, leaving a total number of 188½ lines containing picture intelligence. Therefore, in each complete interlaced picture we will have a total of 377 lines containing picture intelligence.

In other words our picture is actually 377 lines high. The ratio of width to height is 4 : 3, or we can say that each line is 4/3 times as long as the height of the picture. If there are 377 lines we can say that the vertical dimension contains 377

elements and one line should therefore contain:

$$\frac{4}{3} \times 377 = 503 \text{ elements.}$$

Our line will therefore be divided into a total of 503 elements, half of which will be black and the other half white. We can represent the white squares as positive pulses and the black squares as negative pulses; the result is an alternation which is something like a sine wave. There will, therefore, be a total of:

$$\frac{1}{2}(503) = 256\frac{1}{2} \text{ cycles for each line.}$$

Now there are 377 lines in the active picture so the total number of cycles in each picture is:

$$256\frac{1}{2} \times 377 = 96,700 \text{ cycles.}$$


The number of complete frames transmitted each second is 25 and there will therefore be a total of:

$$96,700 \times 25 = 2,417,500 \text{ c/s.}$$

$$= 2.4 \text{ Mc/s approx.}$$

From the above it will be seen that we could have adequate definition for a bandwidth of only 2.4Mc/s. Unfortunately there is one flaw in the argument and that is in interpreting the square-wave formation representing the black and white squares directly into a simple sine wave. In actual fact the square-topped waveform contains an infinite number of harmonics and to obtain a good approximation the bandwidth would have to be in the region of 3.0Mc/s wide.

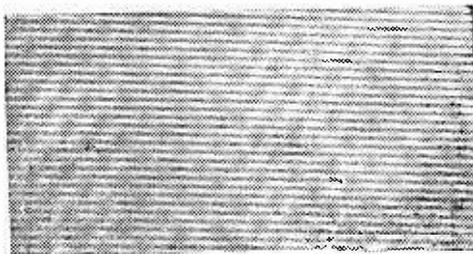This is obviously not practical; the total number of picture elements is taken as if the whole of the lines were active lines which gives a frequency of about 2.75Mc/s.



An example of a well-interlaced scan.

Resolving the 3Mc/s Bars

In order to obtain the best definition from the signal transmitted, it should be possible to align the set to that the 3Mc/s bars are visible.

For the majority of home constructors the only time available is on Saturday mornings and quite a large number of Saturdays are required before it is possible to complete the job. It is a fairly simple matter to resolve the 1Mc/s bars and not at all difficult to resolve the 1.5Mc/s bars. The 2.0Mc/s bars are a little more difficult and the 2.5Mc/s bars require a great deal of patience. The 3.0Mc/s bars are rather difficult, and while many commercial receivers will show those of 2.5Mc/s they do not reveal the 3.0Mc/s bars.

Factors Affecting Bandwidth

It is important to remember that there are factors other than the tuning stages which affect the bandwidth. It is possible for the tuning stages to

(Continued on page 308)

Making Slot Aerials

EASILY INSTALLED IN THE LOFT

By J. B. Lancaster

AS the number of television transmitters increases many more viewers are getting better signals by virtue of the increase in signal strength in their locality. However, the increased signal strength often brings other problems with it, not the least being the production of "ghost" signals which can often completely spoil reception.

The slot aerial is a very effective antidote to ghost troubles besides being one of the best types of aerial to erect in a loft where space is


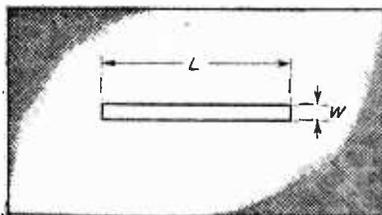


Fig. 1.—Simple slot aerial.
Fig. 2.—Connecting the feeder.

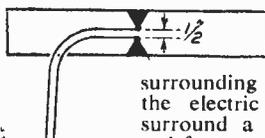

restricted, and more and more amateurs are investigating the possibilities of them.

In Band III they are also received with favour and, because of the smaller dimensions, outdoor slots are a practical possibility.

Polarisation

Whether a wave is vertically or horizontally polarised is determined solely at the transmitter, the deciding factor being the plane in which the aerial is situated.

If the aerial is placed vertically, then the field will be vertically polarised and vice versa.

It is important to note that when receiving a signal the maximum results are obtained when the receiving aerial is placed in the same plane as the sending aerial. For a vertically polarised signal this means that the receiving dipole must be mounted vertically.

A rod aerial uses the electric part of the electro-magnetic wave; we can say it uses the electric field. The cap-transmitted wave consists of two fields, one being electric and the other being magnetic. It is possible to make an aerial which will make use of the magnetic field.

Length

Fig. 1 shows the scheme. Here we have a metal plate in the centre of which is cut a slot. The length of the slot "L" determines the wavelength to which the aerial will tune and is made the same length as a normal dipole. The width of the slot has a bearing on the bandwidth of the signals received but is not over critical and can be in the region of 9in.-12in.

The dimensions of the material surrounding the slot should be sufficient to cover the electric and magnetic fields which would surround a dipole and the minimum figure for satisfactory operation can be taken to be in the region of one-fifth of a wavelength.

The slot can be taken to have similar characteristics to that of the complementary normal dipole which is in the form of a strip.

Another interesting point is that the surrounding material need not be of solid construction; the aerial will work quite effectively if an open mesh material such as chicken wire is used.

It should be noted that the slot aerial uses the magnetic part of the electro-magnetic field and as

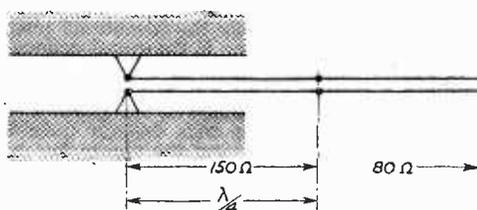


Fig. 3.—A matching section.

Table I: Overall size of wire netting.

Channel	Length	Width
1	15ft 0in.	5ft 0in.
2	14ft 0in.	5ft 0in.
3	12ft 0in.	4ft 6in.
4	10ft 0in.	4ft 0in.
5	9ft 0in.	4ft 0in.
8	3ft 6in.	1ft 6in.
9	3ft 6in.	1ft 6in.
10	3ft 6in.	1ft 6in.
11	3ft 6in.	1ft 6in.

Table II: Length of slot.

Channel	Length
1	10ft 10in.
2	9ft 4in.
3	8ft 6in.
4	7ft 9in.
5	7ft 3in.
8	2ft 5 1/2 in.
9	2ft 5in.
10	2ft 4in.
11	2ft 3 1/2 in.

this at right angles to the electric field the slot must be mounted at right angles to the normal dipole. For *vertical polarisation*, then, the slot should be mounted *horizontally* and vice versa.

The material in which the slot is made can be of very simple form and $\frac{1}{2}$ in. chicken wire will be found quite suitable.

Connecting the Feeder

At the centre of the slot we have an impedance of about 500 ohms, which is approximately the impedance of a triple folded dipole.

For correct matching 600 ohm balanced twin feeder should be used. Connection can be made at the centre as shown in Fig. 2, triangular metal plates (brass or copper or tin) being fitted at the centre of each inner edge. The distance between the ends of these pieces should be $\frac{1}{2}$ in.

Where the receiver uses a different feeder input (usually 80 ohm instead of 600 ohm), then a

stout copper wire is used to connect the rod to the slot edges at intervals of not less than 1ft as shown in the diagram.

The centre conductor of the coaxial cable is connected to the rod at the central position.

This method of connection overcomes the objection of balance-to-unbalance conditions and the matching of 80 ohm coaxial cable to the 500 ohm slot.

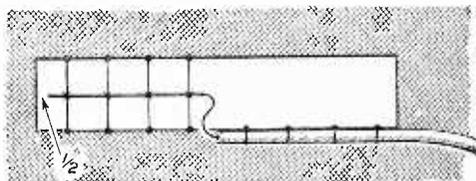


Fig. 4.—Connecting coaxial cable.

Folded Slots

When a normal dipole is folded the impedance is *increased* four times. When a slot is folded the impedance is *reduced* by a quarter. Therefore, where space is available, a simple method of reducing the impedance of the slot is to fold it.

In Fig. 5(a) we have shown the elements of a folded dipole and in Fig. 5(b) the elements of a folded slot. The centre section "A" must be insulated from the outer "B" and this involves difficulties with mechanical construction.

At the U.H.F. range such application becomes more practical and slots can be arranged in curtain arrays as shown in Fig. 6.

Practical Slot Construction

The construction of slot aerials is of the simplest degree. All that is necessary is a quantity of wire netting with some copper wire or rod and some solder.

The overall measurement of the chicken-wire netting is given in Table I and the slot dimensions in Table II for Band I.

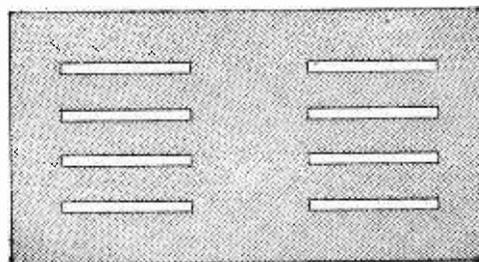


Fig. 6.—Curtain slots.

Use $\frac{1}{2}$ in. chicken wire, though 1 in. can be used if to hand. Cut the overall dimensions as given in the tables, and if the dimensions cannot be accommodated within the width of the wire, then two pieces can be joined together provided copper wire is used, which is tinned and is soldered at **every** possible point.

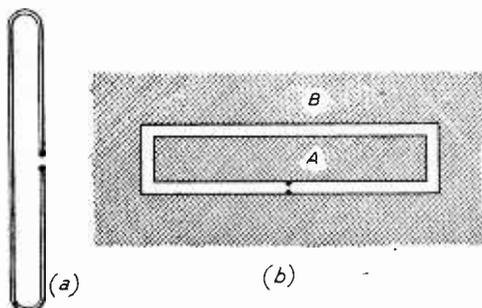


Fig. 5.—(a) A folded dipole; (b) A folded slot.


matching stub or transformer must be used. A simple method is to use a quarter wavelength section of 150 ohm balanced twin cable connected between the 80 ohm feeder and the aerial as shown in Fig. 3.

Fig 4 shows the method of connecting coaxial cable. The cable has its sheath removed to expose the outer conductor. Cut the inner polythene so as to leave about 6in. of the inner conductor available, and then there should be sufficient bare outer conductor so that it can be fitted along one half of the slot. (The length of this portion will vary with the length of the slot and hence the wavelength it is desired to receive.) It is important that the outer braid should not touch the aerial at any other point than along the bottom edge of the slot as shown in the diagram.

Soldering

In order to make good contact, the braided outer cover should be bound and soldered at intervals along the bottom edge of the slot at not more than 12in. between the points. It is a good idea to strengthen the edges of the slot all round by the use of heavy gauge copper conductor, especially if chicken-wire netting is used.

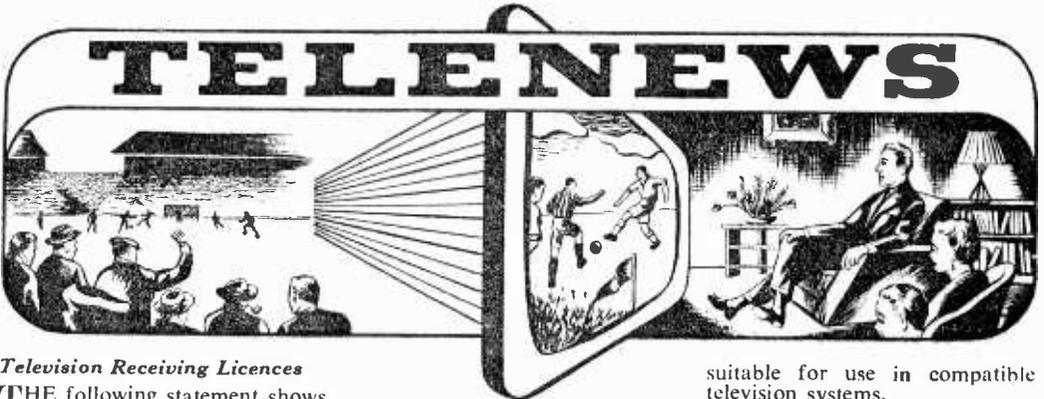The braided outer cover goes along one half of the slot. In the centre of the other half is fitted a length of stout copper wire or rod of brass, copper or duralumin. It is fitted so as to lie halfway between opposite edges of the slot, one end being central in the slot and the other end $\frac{1}{2}$ in. from the vertical edge.



Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of December, 1959, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,773,581
Home Counties	1,347,013
Midland	1,546,367
North Eastern	1,654,684
North Western	1,356,349
South Western	842,682
Wales and Border Counties	602,443
Total England Wales ..	9,123,119
Scotland	859,839
Northern Ireland	131,461
Grand Total	10,114,419

Cardiff TV Centre

BBC TV in Wales is now fully technically equipped for television. At the television studio centre in Broadway, Cardiff, are two studios, a scene dock, wardrobe, make-up room and eight dressing rooms, as well as the associated technical areas. Television from the Welsh studio began in 1955, but recently the facilities have been re-equipped. The first programme from the new centre was broadcast just before Christmas.

Colour for China

ONE of the latest E.M.I. colour television cameras left the Hayes headquarters of E.M.I. Electronics Ltd., recently en route for China. With the camera went control equipment and a Rank-Cintel large screen colour projector, which together form a complete closed circuit installation. It is the first colour television equipment to be exported to China by a British company. Designed specially for a wide range of industrial, medical and

scientific applications, as well as for broadcast studio use, the colour camera incorporates several outstanding features. It is of an entirely new British design, and uses three vidicon tubes, and a novel optical system to give an improved quality even under difficult lighting conditions. It carries a lens turret with four positions, and the optical system has been designed so that the maximum amount of light falls on the photo-conductive surfaces of the vidicons.

Notable for lightness and small size, it also has the advantage of being cheaper and easier to operate than the more elaborate Image Orthicon camera. Capable of producing broadcast quality simultaneous colour television signals on either 405, 525 or 625 line standards, the camera is


suitable for use in compatible television systems.

Amateur TV Convention

THE fifth Amateur Television Convention, arranged by the British Amateur Television Club, will be held in the Conway Hall, London W.C.1, on Saturday, 10th September, 1960.

Educational TV

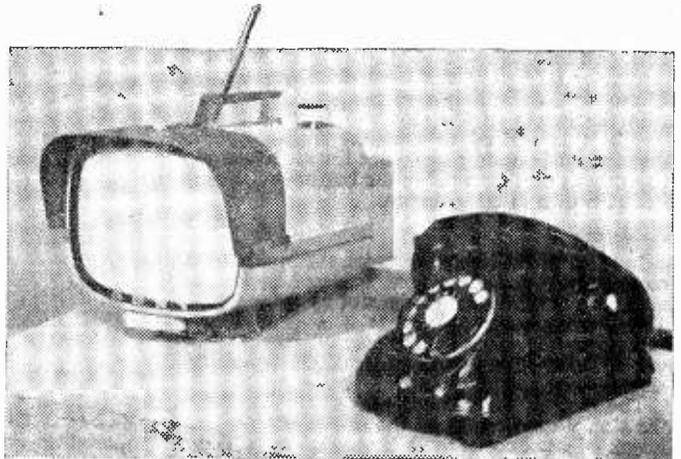THE Radio Corporation of America has recently completed a survey made at the request of the Dominican Republic Government on the possibility of using television in the drive to end illiteracy. For the survey, R.C.A. has had the advice of several education experts. Improvements which could be introduced into the present television system to increase reception, including



The Sony Corporation of Japan announced recently a portable transistorised TV Receiver which is claimed to be ready for mass production. It has an 8in. screen and the tuning covers 14 channels. Its weight is just over 12½lb.

three new relay stations, have been suggested. Programmes will range from the purely technical to the educational and cultural. R.C.A. has studied the life and interests of the people so that programmes of human interest and of educational value can be sent out.

The Dominican Republic Ambassador in Washington, in welcoming the report on behalf of his Government, said that as well as bringing the benefits of a higher level of education to the Republic it was hoped that other countries in the world with similar problems would be able to make use of the full R.C.A. report.

Appointments

MR. H. J. Walters, Senior Public Sales Representative, has been appointed an Assistant Sales Manager for the Public Sales Division of Belling and Lee Limited, with effect from 1st January, 1960.

His duties include the supervision of the field activities of all technical sales representatives in the division, the training of new representatives and the introduction of new products. Mr. Walters will also represent the Sales Director at certain trade functions throughout the country.

Mr. C. R. B. Townend, M.A., A.C.A., Secretary of Belling and Lee Limited, has been appointed to the board of Executive Directors with effect from 1st January, 1960.

TV for "Oriana"


PASSENGERS in the Orient Line's new 40,000-ton luxury liner Oriana will be able to enjoy local television programmes at ports of call throughout the world, and closed-circuit telecine and live television programmes while the ship is on the high seas.

Oriana will be the first passenger vessel in the world to be equipped with a completely coordinated internal and off-air television service. The order for the entire system has been negotiated by the Marconi International Marine Communication Co. Ltd., acting on behalf of Marconi's Wireless Telegraph Co. Ltd., who have designed and engineered a unique marine television installation, enabling standard and unmodified television broadcast receivers to be

used for reception of local transmissions in any part of the world.

The installation provides for the reception of television broadcasts employing the 405-line system used in Britain, the 625-line system used in Australia and the greater part of Europe, and the 525-line system used in the

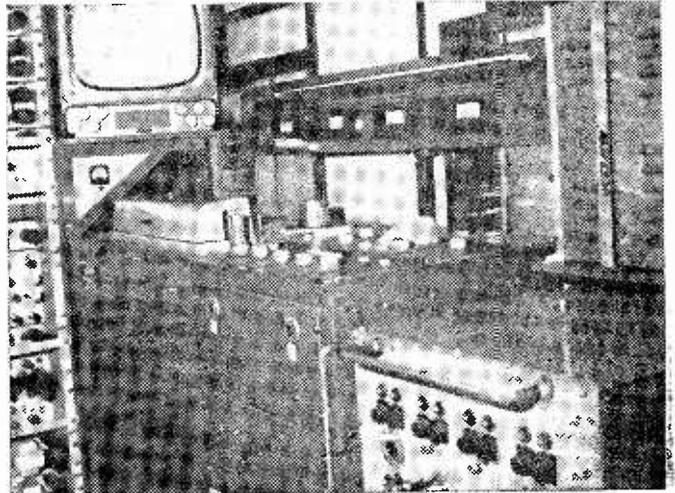television system has been specially designed by E.M.I. Electronics Ltd., to operate under all weather conditions, and will be used to assist the police in traffic control while road widening work is in progress. Without the aid of television three policemen would have been required to regulate traffic. The point



Many of the independent television companies have facilities for the use of videotape recordings. Granada have rehoused an Ampex TV recorder in a small console for mobile use. The interior of the videotape recording vehicle is shown above.

United States, Canada, Japan and some South American countries.

ITA Appointment

THE Rt. Hon. Reginald Bevins, M.P., Postmaster General, has made the following appointment to the Independent Television Authority.

Sir (Frederick) Lucius O'Brien, from 1st January, 1960, to 29th July, 1964.

The appointment of Sir Lucius O'Brien fills the vacancy caused by the expiry of the term of office of Lt. Col. Arthur Chichester.

Sir Lucius will make the interests of Northern Ireland his special care.

TV Traffic Control

CLOSED circuit television, which enables one policeman to control four busy traffic lanes at West Drayton, Middlesex, went into operation recently. The

duty-policeman is able to watch traffic conditions on two roads, which he would not otherwise be able to see, on a monitor screen set up in a special police box.

The television camera has been mounted on a lamp standard twenty feet above ground. To protect it from rain and frost, the camera is enclosed in a special weather-proof housing. Even under difficult lighting conditions, the highly-sensitive camera is able to relay good quality pictures to the police box. The installation is expected to be in use for about a year, during the reconstruction of a railway bridge spanning High Street and Station Road, West Drayton. Closed-circuit television was chosen because there was no other effective way of controlling the intersections during periods of heavy traffic. When traffic is comparatively light, the signals will operate automatically on a "time shared" basis.

Western Summit TV

RELAYING PICTURES TO AMERICA

FOLLOWING the successful relay of pictures of President Eisenhower from Turkey through the BBC to New York using cable film, the BBC is co-operating with the National Broadcasting Company of America on another news enterprise.

During the Western Summit Conference in Paris from December 19th to 21st, 1959, the BBC provided technical facilities to enable the NBC to show recorded news pictures to American viewers in the quickest possible time.

Recordings

The pictures were sent from Paris, using the French television standards of 819 lines, 50 fields per second, over the Eurovision circuit to the British Post Office terminal of the cross-Channel radio link at Tolsford Hill near Folkstone. From this point the signals were transmitted over BBC super high frequency radio links to the Crystal Palace television station and from there to the BBC's Research Department at Kingswood Warren, Surrey. Here the pictures were converted to American television standards of 525 lines 60 fields per second on equipment which has been specially developed by the BBC. The picture signals at the converted standards were then transmitted by radio link via Crystal Palace to London Airport where they were recorded on video magnetic tape equipment together with the associated sound signals which were fed from Paris by line. The recordings were then dispatched by transatlantic plane direct to New York. In addition film material can be transmitted over the transatlantic telephone cable by the BBC's cable-film process.

Thus video tape recordings and short film sequences of the events in Paris were made available to the NBC in New York with the minimum of delay. Pictures recorded in Paris in the morning were on the American screens in the early evening.

These arrangements were in operation during the period, December 17th to 22nd.

As a safeguard against breakdown most of the radio links were duplicated and others had reserves which could be brought into service at short notice. In addition the pictures and sound were recorded on video tape at American standards by the BBC's Research Department at Kingswood Warren as well as at London Airport and these duplicated recordings were despatched to London Airport by fast road transport.

Standards Conversion

The equipment for converting the vision signals from the French 819 lines 50 fields per second standard to the American 525 lines 60 fields per second standard, on which this video recording operation depended, has been developed by BBC engineers along similar lines to that which they pioneered for the conversion of European television standards to the British television standard for Eurovision. In this case, however, there was

the additional problem of the different field frequencies to be solved.

The conversion was carried out by displaying the pictures at the original standards on a picture tube which was scanned by a television camera operating on the required standards. The low frequency flicker, caused by a small difference in the field frequencies of the original and converted pictures, which may have been present when converting from European to British standards was smoothed out by use of a display tube phosphor having a sufficiently long after-glow. In converting from European to American standards the difference in field frequencies gave rise to a flicker at 10 cycles per second, which could not be eliminated in this way without intolerably bad portrayal of moving objects. This problem was overcome in the BBC standards converter by means of a new technique which reduced the flicker to a satisfactory level by adding to the converted picture a correcting signal which was applied so as substantially to remove the flicker.

Cablefilm

For the BBC cablefilm transmissions the pictures were fed from Paris over the Eurovision circuit to the Post Office terminal at Tolsford Hill near Folkstone. Here the vision signals were converted from French to British television standards and then fed to Alexandra Palace where the 16mm optical film telerecordings required for cablefilm process were made.

The new cablefilm system was developed by the BBC for transmitting short film sequences over the Atlantic telephone cable and was first brought into use on June 18th, last year, on the occasion of H.M. the Queen's departure from London and arrival in St. John's, Newfoundland, for her Canadian tour. The system achieves the necessary economy in bandwidth so as to be within the capacity of the Atlantic cable first by restriction of horizontal and vertical definition and by transmitting only alternate frames, and secondly by reduction of the transmission rate so that one complete picture is transmitted over the transatlantic cable every eight seconds, i.e., at one hundredth of the normal rate. Thus a half-minute film sequence is transmitted every 50 minutes. There is some loss of picture quality in the process, but the system makes it possible for short film sequences to be transmitted and reproduced in much shorter time than it takes to fly a film across the Atlantic.

REMEMBER TO BUY
OUR COMPANION JOURNAL
PRACTICAL WIRELESS

1/6 Every Month

Voltage Regulation

DETAILS OF THE METROSIL

By G. K. Crossland

SEVERAL readers have written to us recently to ask for details of the uses and operation of Metrosils. In view of this interest, it is felt that a short article in this connection would be of general interest to constructors and experimenters. The Metrosil is an element possessing a non-linear volt-ampere characteristic, produced by Metropolitan-Vickers Electrical Co. Ltd.

Properties

For general use, the Metrosil takes the form of either a round or square rod, or a disc, and appears very similar to an ordinary carbon resistor. As opposed to an ordinary resistor, however, which follows Ohm's law, the current in the Metrosil can be made to rise approximately 20 times simply by doubling the voltage across it; and further, by trebling the applied voltage the current increases

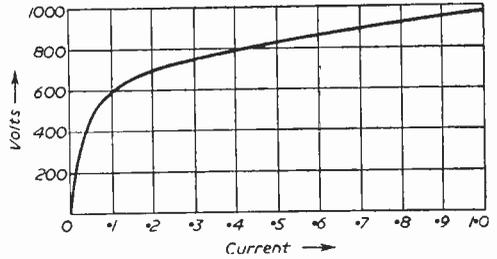


Fig. 1.—The non-linear characteristic of the Metrosil.

certain circuits it may be desirable to allow this characteristic to compensate for the positive temperature-coefficient of a copper coil which might also be included in the network.

Applications

A typical application for Metrosil in a television set is shown in Fig 2. Here the element will be seen to occupy the position of a bleeder resistor in the EHT system. It does, in fact, load the EHT system to a varying degree, but the actual magnitude of loading depends on the voltage. If, for instance the voltage tends to rise as a result of a reduction in beam current—caused by a reduction in the overall brightness level of the picture—the voltage across the Metrosil will also rise, and as a consequence it will pass more current. This rise in EHT current will, therefore, counteract the rise in voltage, and in this way maintain a fairly even EHT loading, irrespective of beam current. A similar effect will, of course, occur should the picture become brighter, and the EHT voltage have a tendency to fall.

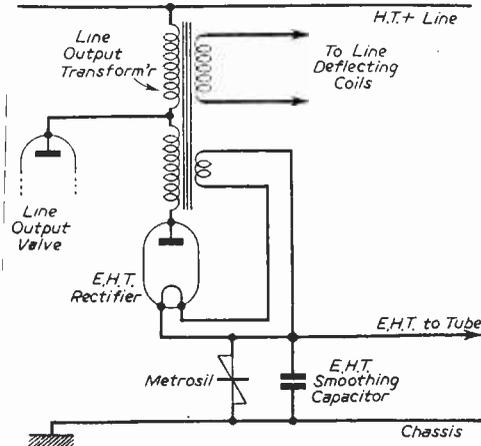


Fig. 2.—Using the Metrosil to improve EHT regulation.

by approximately one hundred times. This property of the Metrosil is shown in graphical form by Fig. 1, and can be expressed mathematically as $I = KEa$, where I is the current, E the applied voltage, and K and a are constants.

The value of K depends mainly on the physical characteristics of the element, while a is mainly dependent on its make-up. A normal Metrosil element has a value a of 4 or 5, which means that the current in the element varies as the fourth or fifth power of the applied voltage. (R. W. Sillars, "Metrosil" "The Metropolitan-Vickers Gazette," July, 1944.)

Before proceeding it should be mentioned that, as opposed to a Thermistor, a Metrosil is primarily a voltage operated device and, for normal application, use is not so frequently made of its inherent negative temperature-coefficient, although in

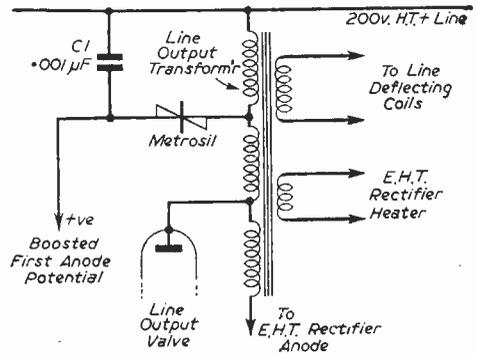


Fig. 3.—Obtaining a boosted first anode potential.

H.T. Boost

Another application of this versatile element is an aid to obtaining a first anode potential for a tetrode picture-tube. A potential here in the region of 300V or more is desirable to provide optimum focus, and in certain sets 200 to 250V represents the maximum D.C. voltage available.

A suitable pulse voltage can often be found on one of the inductive components associated with

the line timebase. This voltage can be rectified by a Metrosil and used quite successfully as a first anode potential. Fig. 3 shows a typical circuit of this arrangement in which the pulse voltage is picked up from a tapping on the line output transformer. This produces about 200V above the H.T. line potential across C1.

It is often possible to obtain a pulse potential of suitable magnitude from the blocking oscillator transformer or from a feedback winding on the line output transformer, while in certain cases the voltage which is developed across the line deflecting coils can be used. In all cases, however, the relevant voltage is in the form of a pulse which is developed in the line output stage during the line flyback.

Pulse-voltage rectification takes place mainly owing to the relatively low A.C. impedance, as opposed to D.C. resistance, of Metrosil. This characteristic can also be used to advantage in the cathode circuit of a video amplifier valve. Fig 4 shows such a circuit in which the Metrosil acts successfully as a bias resistor, but owing to its low A.C. impedance it tends to prevent the feedback of inverse video voltages. It can, therefore, be compared in operation to a bias resistor bypassed by an infinitely large value capacitor to minimise attenuation at the low video frequencies.

In conclusion it should be mentioned that the three briefly described Metrosil applications must

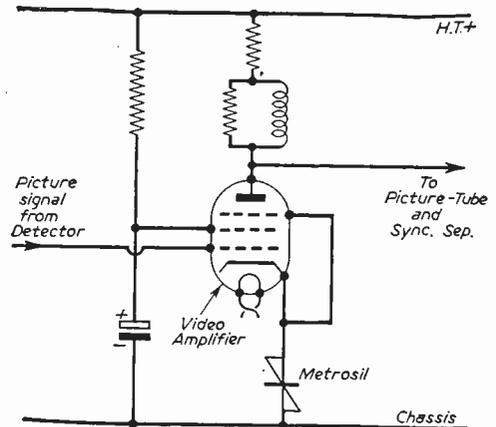


Fig. 4.—A Metrosil in the cathode circuit of a video amplifier assists in maintaining a linear response.

not be considered exhaustive, for in the field of electronics generally it has hosts of applications, some of which it is hoped may now appear obvious to the experimenter.

THE EF50 CONVERTER

(Continued from page 288)

Keep the wiring short and wire components right to the valvholder where possible, especially V1. When "earthing" V1 spigot, solder the wire at the bottom of the spigot tag nearest the valvholder. Position R2 to be at least $\frac{1}{4}$ in. above the chassis.


Alignment

Turn down the gain control at least a quarter of the way. Switch on the converter, place the Band I aerial lead on the grid of V2 and tune L4 for maximum vision. Remove the aerial, plug in the Band III aerial and set C12 and the cores of L1, L2, L3 all midway and L5 on a level with the former top. Tune L5 slowly and rock C12. Vision may be received in two positions of the core of L5 but there is only one where sound and vision are received together; this is the correct one. Tune for maximum sound, then tune L2. This tuning may be a little sharper than might be expected, and if the gain is set too near maximum, the removal of this core or the aerial may cause V1 to oscillate to give a bright plain raster, and no signal will be received. Keep tuning L2 and L5, and when a signal is received tune L3 for maximum vision. This coil tunes rather broadly. Now tune L4 for maximum vision, and turn the core slightly towards the sound if necessary and increase the gain with R3. Now tune L1 if patterning is experienced; this may not seem to have much effect, as it tunes broadly, but it removes BBC patterns. Finally set C12 oscillator trimmer for maximum sound.

The gain control was a 300 Ω wire-wound midget pot, as it was to hand, but it can be 500 Ω

or up to 1k Ω , but then R4 is omitted, the slider being taken direct to chassis.

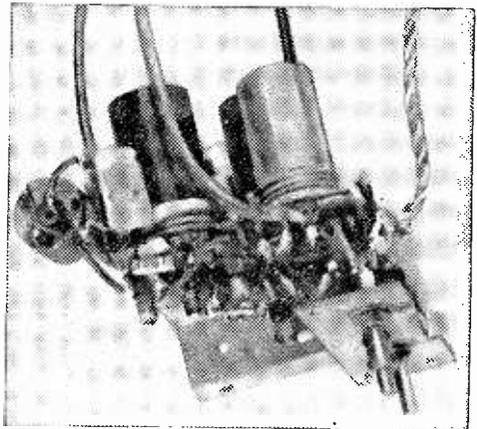For those who like to experiment, the circuit in Fig. 4, with EF50 valves, has slightly less gain. Do not omit the condenser in the aerial lead.



A view of the complete converter.


With the EF80 it works exceptionally well on low voltages (Fig. 5). About 10pF seemed about right for matching in the aerial lead; a postage stamp trimmer was used. This matching was found to be very important for this valve, as the impedance of the valve is altered and mismatching takes place when the aerial is taken to the cathode. The EF50 requires 1,000pF aerial condenser, but this can be varied to suit individual requirements.

7-VALVE AM/FM RADIOGRAM CHASSIS

Surplus Bargain Offer

TRS

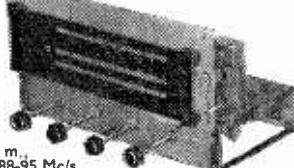Valve Line up:
ECC85, ECH81,
EF89, EAB C80,
EL84, EM81, EZ80.



3 waveband and switched gram positions. Med. 200 m.-500 m. Long 1,000 m.-2,000 m., VHF/FM 88-95 Mc/s.
4 Controls. Vol., On-off, Tone, Tuning. Wavechange. P.U., Ae. and E., and speaker sockets. Magic eye tuning. Philips continental tuning insert with permeability tuning on FM, and combined AM/FM IF transformers, 460 Kc/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry, including AVC and Neg. Feedback. 3 watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 in. x 6 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/2 in. x 3 1/4 in. Vertical pointer. Horizontal station names, gold on brown background. **13.0. A.C. 200/250 v. operation.**

£13.10 Carr. and Ins. 5/-. Complete with 4 knobs walnut or ivory to choice.

We are sorry to cause our customers disappointment, but existing orders have already exhausted present stocks of the above. A new replacement chassis, virtually identical, will be available from early February, price unchanged.

REGUNNED TV TUBES New Reduced Prices! And now 12 months' Guarantee!

12in.	£6	17in.	£9.10.0
14in.	£7	21in.	£10.10.0
16in.	£7.10.0		

All tubes Rebuilt with new Heater Cathode and Gun Assembly—reconditioned virtually as new! Full 6 months' unconditional Guarantee. As used by our own Service Dept. Comprehensive stocks—quick delivery. 10/- part exchange allowance on your old tube.

RECORD PLAYER CABINETS

Contemporary Cabinet styled, rexine covered cabinet in two-tone fawn and brown, or mottled red with white polka dot. Size 18 1/2 x 13 1/2 x 6 1/2 in. Space available for all modern accessories, including baffle board and anodised metal fret. Space available for all modern amplifiers and autochangers, etc. Uncut record player-mounting board 14 x 19 in. supplied.



2-valve AMPLIFIER Mk. 2

Latest developed circuit giving a higher fidelity response and greater output (2-3 watts) using twin stage valve ECL82 and neg. feedback Tone Control. Complete with knobs, etc., wired and tested ready to fit in above cabinet.
ONLY £2.17.6. P. & P. 1/-.
6in. speaker and matching transformer. £2/- P. & P. 1/6.

SENTERCEL RECTIFIERS. E.H.T. Type Fly-back Voltages. K3/25 2 kV., 5/-; K3/40 3.9 kV., 6/9; K3/45, 3.6 kV., 7/8; K3/50 4 kV., 7/9; K3/100 8 kV., 18/6. MAINS TYPES.—RML 125 v. 60 mA., 4/8; RM2, 125 v. 100 mA., 5/8; RM3, 125 v. 120 mA., 7/8; RM4, 250 v. 250 mA., 16/-; RM4B type 270 mA., 17/6; RM5, 250 v. 300 mA., 21/-.

SPEAKER FRET.—Expanded Bronze anodised metal 8 x 8 in., 2/3; 12 x 8 in., 3/-; 12 x 12 in., 4/6; 12 x 15 in., 6/-; 24 x 12 in., 9/-, etc.

Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

FULLY GUARANTEED	NEW REDUCED PRICES
1RS, 1T4 7/8/DAP96 9/-	EF80 9/6
1RS, 7/6 DP96 9/-	PCF82 10/6
1RS, 3V4 8/-	PCCL83 12/6
5Z4 9/6	PL41 12/8
6X7 6/6	PL82 9/6
6K8 8/6	PL83 11/8
6Q7 8/6	PY80 7/6
6BN7 8/6	PY81 9/6
6V6 7/6	PY82 7/8
6X4 7/6	PY83 10/8
6C3 7/6	U25 12/6
7Y4 8/6	U191 12/6
35L6 9/6	UCH42 10/6
	UF141 10/-

Send for List.

SPECIAL PRICE PER SET

1RS, 1T4, 1RS, 3V4 or 3V4 ...	27/6
DK96, DP96, DAP96, DL96 ...	35/-
6K8, 6K7, 6Q7, 6V6, 5Z4 or 6X5 ...	35/-

COAX 80 OHM CABLE. Stand 1/2 in. diam. Low Loss Semi-Alr Spaced Aerials.

SPECIAL REDUCED PRICES

20 yds. 12/6, p. & p. 1/6; 60 yds. 22/6, p. & p. 3/-; 40 yds. 22/6, p. & p. 2/6; All other lengths 8d. per yard.

Coax Plugs 1/-. Sockets 1/-. Couplers 1/3. Cable End Sockets 1/6. Outlet Boxes 4/6.

TRANSISTOR 'ONE-WATT' AMPLIFIER
6 v. Battery operated

Latest Push-Pull, 4 Transistor circuit giving full 1 watt Output into standard 3 ohm speaker. Good sensitivity and improved freq. response. Neg. feedback. Var. Tone and Volume Controls. Chassis Size 6 1/2 in. x 3 1/2 in. x 1 1/2 in. Current consumption 10 mA quiescent—250 mA at 1 watt.


2 matched GEC GET15 Transistors... 42/- pr.
2 GEC GET3 Transistors 21/- pr.
Driver Trans. 8/6
Output Trans. (to 3 ohms) 10/6

Complete Kit of Parts incl. circuit etc. Less speaker. **ONLY 99/6 P. & P. 2/6.**

Circuit and instruction booklet 1/6 post free.

VOLUME CONTROLS

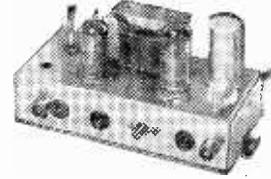10,000 ohms—2 Megohms. All long spindles—Morganite Midget type. 1 1/2 in. diameter. Guar. 1 year. Log or Lin. Ratios. Less Sw. 3/-. 1 D.P. Sw. 4/8. Twin Ganged controls, 1 meg. 1 meg., 1 meg., less Sw. 8/8 ea.



BAND 3 TV CONVERTER

All channels 7-13 (180-205 Mc/s).
Mk. 2 Model. Latest cascade circuit using ECC84 and EF80 valves. 150b gain over standard circuits. Built-in Power Supply 200-350 v. A.C. Size 6 1/2 in. x 3 1/2 in. x 4 in. Simple to fit—only external plug-in connections. Wired and aligned ready to use. Only 79/6, P. & P. 2/6.
B1-B3 changeover Sw. and BBC Aerial Socket fitted and wired, 8/- extra.
Band 3 Aerials. Single Dipole with 4 yds. cable, 18/8, 3 Element Beam, 25/-, 5 Element, 32/6, etc. B1-B3 Crossover Units, 7/6.

RECORD PLAYER BARGAINS

NEW RELEASE by E.M.I.—4-speed Single Player Unit fitted with latest stereo and monaural Xtal cartridge and dual sapphire styli. Auto stop and start. A fidelity unit and bargain buy at only £6.18.6.

BRR—UAS Model.—4-speed autochanger with crystal turnover cartridge, etc., wired for stereo, Bargain £6.18.6.

Garrard—Latest RC121/D/Mk 2—fitted with GCS Xtal cartridge, plug-in monaural head. Auto/manual selector, etc. The connoisseur's choice for audio perfection. Bargain 10 gns.

Plug-in stereo head GCS/10 £2 extra.

All above are brand new, fully guaranteed models. Carr. and Ins. 4/6.

Comprehensive bargain range of Collaro, BSR and Garrard Units in stock. Send for comprehensive bargain lists.

C.R.T. Heater Isolation Transformers

New - improved types—mains prim. 200/250 v. tapped.

All Isolation Transformers now supplied with alternative no boost plus 25%, and plus 50% boost taps, at no extra charge.

2 v.	2A type 12/6	(P. & P. 1/6)-
6.3 v.	.6A ..	12/6 ..
10.5 v.	.3A ..	12/6 ..
13 v.	.3A ..	12/6 ..

Other voltages available at same prices.
Small size and tag terminated for easy fitting.

JASON FM TUNER UNITS (87-105 Mc/s)

Designer-approved kits of parts for these quality and highly popular tuners available as follows.

STANDARD MODEL (PMT)—as previously extensively advertised. COMPLETE KIT, 5 gns., post free. Set of 4 spec. valves, 30/-, plus free.

LATEST MODEL (PMT2)—attractively presented shelf mounting unit to enclose Metal Cabinet with Built-in Power Supply. COMPLETE KIT, 27/-, p. & p. 3/6. Set of 5 spec. valves, 39/6.

NEW JASON COMPREHENSIVE F.M. HAND-BOOK, 2/6 post free. 48 hr. Alignment Service, 7/6, p. & p. 3/6.

TYGAN FRET (Murphy pattern) 12 x 12 in., 2/-; 12 x 18 in., 3/-; 12 x 24 in., 4/-, etc.

SPEAKERS P.M. 3 ohm 2 1/2 in. Elac. 16/6. 3 1/2 in. Goodmans, 18/6. 5 in. R. & A., 17/6. 6 in. Celestion 18/6. 7 x 4 in. Goodmans, 18/6. 8 in. Rola, 20/-, 8 in. Special Cone G'mans, 21/6. 10 in. R. & A., 25/-

Terms: C.W.O. or C.O.D. Kindly make cheques, P.O.s, etc., payable to T.R.S. Post/Packing up to 3lb. 7d. 1lb. 1/3, 3lb. 1/6 5lb. 2/-, 10lb. 2/9. Hours: 9 a.m.-6 p.m. 1 p.m. Wed. Open all day Saturday.

TRS

RADIO COMPONENT SPECIALISTS (Est. 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Buses: 130A, 133, 159, 166 and 190

More

for less...



Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor is now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS.

The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red coloured pointer and effectively damped movement facilitate easy and rapid reading.

For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter!

Use PRODCLIPS with the MULTIMINOR (Pat. No. 748811)

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be.

15/- per pair

...with the MULTIMINOR

Write now for illustrated literature to:—

AVO LTD

AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD
LONDON - S.W.1

VIctoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

19 Ranges

D.C. Voltage	A.C. Voltage
0—100mV.	0—10 V.
0—2.5 V.	0—25 V.
0—10 V.	0—100 V.
0—25 V.	0—250 V.
0—100 V.	0—1000 V.
0—250 V.	
0—1000 V.	
Resistance	D.C. Current
0—20,000Ω	0—100μA
0—2MΩ	0—1mA
	0—10mA
	0—100mA
	0—1 A

List Price: **£9:10s.**
complete with Test Leads
and Crocodile Clips.

Leather Case if required 39/-
Size: 5 $\frac{1}{2}$ x 3 $\frac{1}{2}$ x 1 $\frac{1}{2}$ in.
Weight: 1 lb. approx.

MM12

**TAKE THE PROBLEMS
OUT OF SOLDERING**



HENLEY
SOLON

TRADE MARK

FOR 25 YEARS THE BEST
ELECTRIC SOLDERING IRON

RELIABLE
SPEEDY
LONG-LASTING

Leaflets on request from:

AEI

CABLE DIVISION
**Associated Electrical
Industries Ltd**
Distribution Equipment
Sales Dept
59-62 High Holborn
London W.C.1
Telephone: CHAncery 2441-9
25 watt instrument
model (Illustrated)

Factory Replacement TV TUBES

TELEVISION TUBES COMPLETELY RE-MANUFACTURED AND INCORPORATING THE VERY LATEST ADVANCES IN TUBE DESIGN

SPECIFICATION:

1. Correct plug replacements.
2. Aluminised and rescreened with latest type phosphors.
3. Complete new gun and electrode assembly.
4. Regraphited and new getters fitted.
5. Full 12 months new tube guarantee.

In fact a completely new tube except the glass. Correct replacements for all Mazda, Mullard, Cossor, G.E.C., Cathodion, Emitron, English Electric, Brimar and Emiscope (including Hard Glass) types.

ALL 12" Types **£5.50**

14" Types **£6.10.0**

15" and 17" Types **£6.19.0**

Terms C.W.O. or C.O.D.

Post, packing and insurance 10/6

Following allowances refundable on return of old tube in our containers:


12" and 14" **15/-**

15" and 17" **£1.0.0**

LAWSON TUBES

156 Pickerleigh Road, Malvern, Worcestershire
Phone: Malvern 3798

Servicing Television Receivers

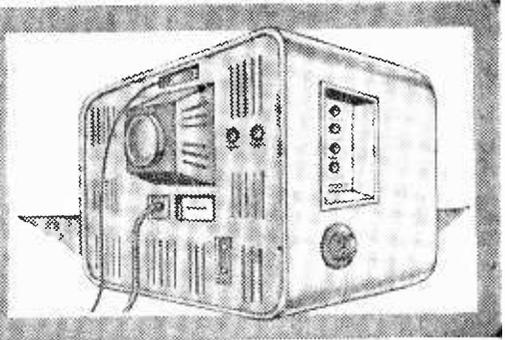

No. 53—THE FERGUSON 992T SERIES

By L. Lawry-Johns

(Continued from page 230 of the February issue)

THE previous article dealt with EHT faults and we now deal with timebase and linearity faults.

Striations

Vertical rulings down the left side of the picture should direct attention to R35 which is a 910Ω resistor across the linearity coil. This should not be confused with B.K. effect in the PL81 which produces one ragged vertical line on the left side. Severe interference producing a more violent white ragged bordered with lines shooting across usually denotes a discharge associated with the EHT winding on the line output transformer and the discharge can often be seen occurring where the lead to the EY51 anode comes up, looking between the PL81 and the PY81.

Raster Present. No Picture. Sound O.K.

Readers often write in to say that although they have traced the fault to a defective V5 video amplifier, and that this had a short and that the damaged resistor (grid leak 3.9K) has been replaced, there is still no picture signal. The answer to this one is that the short has damaged the OA60 (OA70) crystal diode detector which is located inside the I.F. coil can next to the video amplifier. This small component is clearly marked; it is white with one red end. Note the connection of the red end.

Raster Present. No Picture or Sound

Check aerial and cable connections and then replace the ECC81 (V2). Check H.T. to the V1 stage (EF80) plus 7 and 8, H.T. to V2 plus 1 and 6.

Picture O.K. No Sound

Check EBF80 and H.T. to screen and anode.

Distorted Sound

Check 3.3M (orange, orange, green) resistor to EB91 (V6) noise limiter diode, and ECL30 (V11).

Loud Howl

Check 50μF electrolytic capacitor, pin 3 to chassis (C39). If this is open-circuit, feedback occurs between the pentode and triode sections.

Frame Faults

Vertical lock at one end of its travel, frame still revolving. Check ECL80 valves V12 and V13. If still defective check 220kΩ resistor (red, red, yellow) to hold control, 470kΩ (yellow, violet, yellow) to pin 2 of V13.

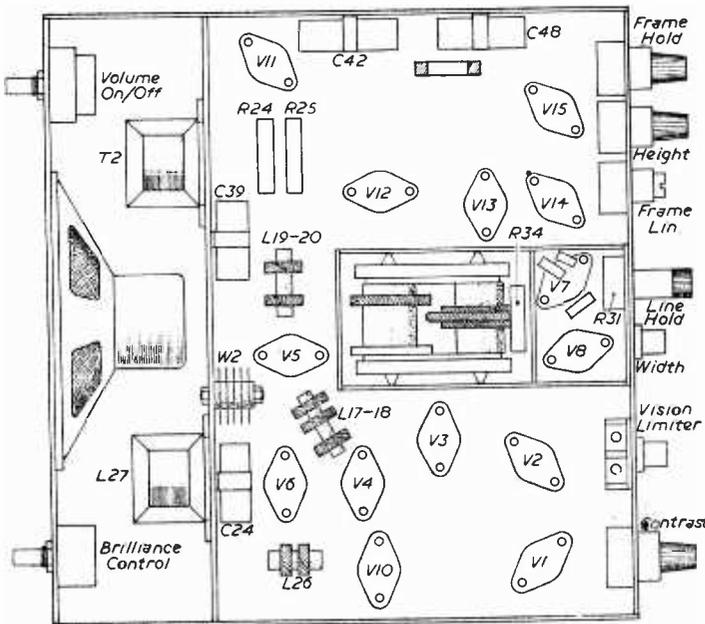


Fig. 5.—Simplified underchassis view (schedule A. and B.).

Persistent jitter unaffected by controls. Check both V12 and V13 and the capacitors of 0.02 μ F, 500pF and 0.1 μ F.

Compression at Bottom, Top Expanded

Check V12 and V13, 0.1 μ F, 0.05 μ F, 0.01 μ F capacitors and associated components.

Loss of Height, Frame Hold, etc.

Check C48, 50 μ F capacitor from pin 3 of V13 to chassis.

No Raster or Signals at all

Valves lighting up. Check R74 and R75, 40 Ω wire wound resistors. What usually happens is that one resistor fails leaving one PY82 and the other resistor to carry the full load. This may result in the other resistor overheating and failing, giving the above symptoms.

No Signals. No Valves Glowing

This normally results as a valve heater becomes open-circuit (or the tube heater), the thermistor (CZ1) being cracked or broken or a section of the

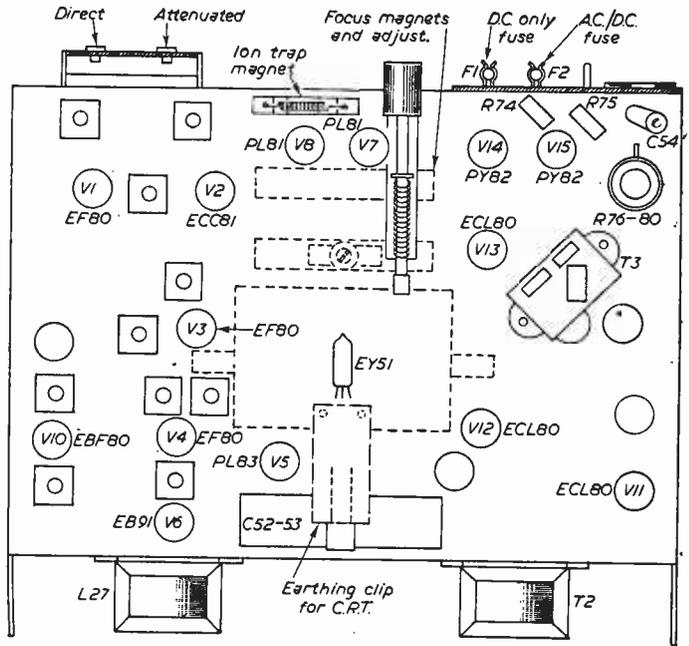


Fig. 6.—Layout (schedule A. and B.).

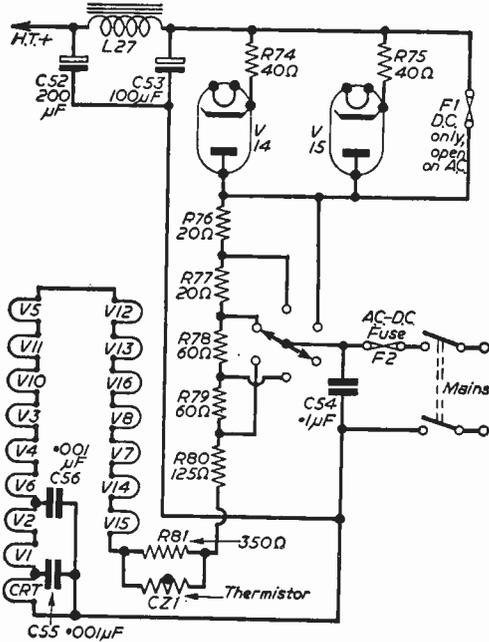


Fig. 7.—H.T. and L.T. circuits.

mains dropper being open circuited (R78-R79-R80). This fault is not always easy to trace unless a voltmeter is available which would enable the mains voltage to be followed from the fuse, through the dropper, thermistor and through the heater chain V15-V14-V7, etc., to the point where the voltage is absent. On most valve bases the heater pins are 4 and 5, 4 and 4 on the EB91, 1 and 12 on the tube. On the ECC81 base, 4 and 5 are joined, pin 9 being the other heater (centre tap) connection. If a voltmeter is not available, use a neon screwdriver to trace the voltage, but first ensure that the chassis is not "live." If it is, reverse the mains leads. The neon will glow at the A.C./D.C. fuse on the dropper and along the heater chain until the break occurs.

Distorted Picture Hum on Sound

Check C52-C53. Note, however, that when C53 is open-circuit the H.T. voltage drops to a low figure and the signals are normally absent.

D.C. Fuse

In areas of low voltage D.C. mains only, a fuse can be inserted into the D.C. fuse holder to short out the rectifiers and surge resistors and thus avoid the voltage drop across them. Note, however, that the polarity of the mains must be very strictly observed and it must be made impossible for the mains plug to be reversed. Failure to observe this warning will result in severe damage as the mains is applied direct to the H.T. line when the D.C. only fuse is occupied.

Conversion

The Ferguson type A tuner was intended for use with the schedule E 992T series and the schedule B 998T. The Ferguson type B1 was intended for use with 992T series schedule A to D and 998T schedule A.

As these tuners are not now available, the Clydon P16H or the Brayhead 16s can be directly fitted, following the instructions provided. The surplus Pye type 47 can also be used with the unit wired in and the I.F. output applied across the ECC81 cathode resistor, suitably modified, the oscillator section being rendered inoperative. The V1 EF80 is removed, the H.T. derived from pin 8, the heater supply from pins 4 and 5. The I.F. is sound 19.5Mc/s. Vision 16Mc/s.

Tube Faults

As mentioned last month, some of these models are fitted with ion trap magnets held by a fibre strap. On all occasions when no picture, or a faint, dim, picture only can be obtained, it is wise to check that the fibre band has not snapped and caused the ion trap magnet to be displaced. The magnet should be positioned for maximum brilliance.

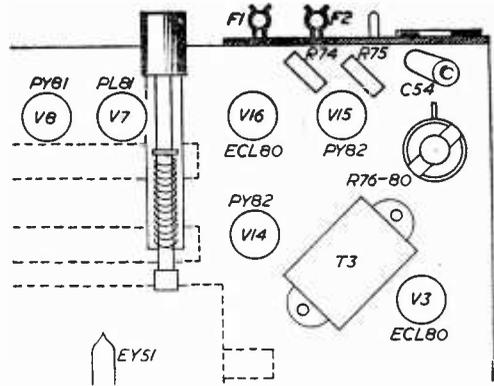


Fig. 8.—Layout of schedules C., D. and E. (see also Fig. 6). On all late models, V5 is an EF80.

TIMEBASE FAULTS

G.E.C. MODELS BT1748, BT2747, BT8246

By G. J. King

THE timebase circuits of these receivers are easily followed and only the circuit of the frame amplifier stage is shown (Fig. 1). The most common faults which develop are set out below together with their remedies.

Frame Bounce

If this symptom is accompanied with the height varying in a somewhat random manner, it would be as well to check the condition, preferably by substitution, of the feedback capacitor in the frame amplifier section. This is the 0.04µF capacitor (C107) in the frame amplifier circuit in Fig. 1.

Excessive Height

This effect may be present with poor frame linearity which cannot be corrected by adjustment to the frame linearity controls. If this is so, a check should be made to the 500µF capacitor (C106) connected across the cathode resistor of the frame amplifier valve (see Fig. 1). A short-circuit in this component is usually responsible.

Weak Line Lock

In some cases of this symptom, especially if the smaller resistors and capacitors associated with the sync separator and line oscillator appear to be normal, poor insulation of the windings of the line oscillator transformer gives the trouble. It is rather difficult to prove such a fault by a series of tests, and it is nearly often necessary to check the transformer by substitution.

After transformer replacement, it may be discovered that the line hold control is at the end of its range. This can be balanced, however, by disconnecting the 100k resistor (R116) which is in parallel with an 18k resistor (R68), the pair being connected from one side of the line hold control to receiver chassis.

Similar trouble is sometimes produced by a fault developing in the 300pF capacitor connected between the control grid of the N339 line amplifier valve and chassis. A substitution test in this case is desirable.

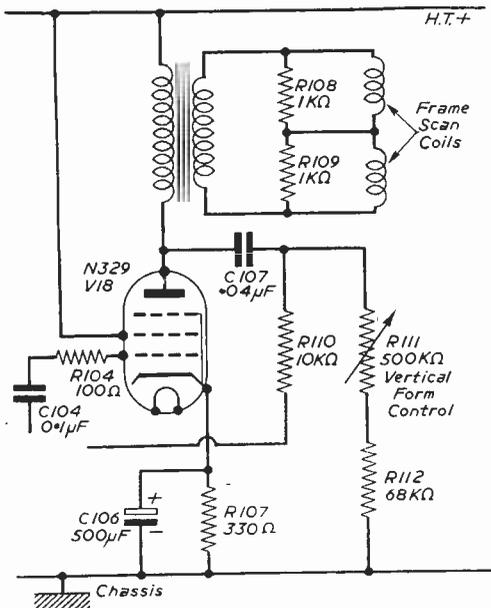


Fig. 1.—The frame amplifier section of the G.E.C. BT1748 series. Intermittency of C107 can result in frame bounce.


THE TV CENTRE

THIS NEW HEADQUARTERS FOR THE BBC IS SITUATED
IN SHEPHERD'S BUSH, LONDON

THE modern building now under construction in Shepherd's Bush, London, to be known as the BBC Television Centre, will give the BBC the first studios especially built for television productions. As many readers may know, since 1936, the BBC Television Service has used converted premises. When the television centre is completed it will be the largest TV headquarters in Europe. The site occupies some 13 acres and the building will consist of a large main block, containing seven studios and several hundred offices; a scenery block; a restaurant block; a works block; and eventually a "spur or tail" running from the main block. The scenery block and certain of the offices in the main block are already in use. More of the offices in the main block will be brought into service in the near future and it is expected that the first studio will be ready for operation by the middle of this year. Following the completion of the main and restaurant blocks, the work block will be constructed, but so far no detailed planning for the spur has yet been made. The cost of building the mains block and works block and completing the restaurant section will be in the order of £10 million including technical plant and wiring.


Main Block

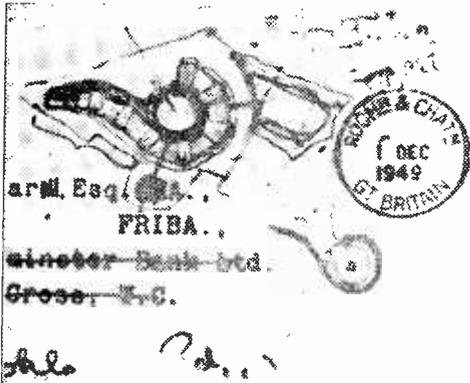This structure is now well advanced. It is a circular building covering $3\frac{1}{2}$ acres, nearly twice the area covered by St. Paul's Cathedral. It has



The design for the BBC television centre began when Mr. Graham Dawbarn, C.B.E., M.A., F.R.I.B.A., sketched on an envelope when discussing the project with Mr. M. T. Tudsbery, the BBC's Civil Engineer.

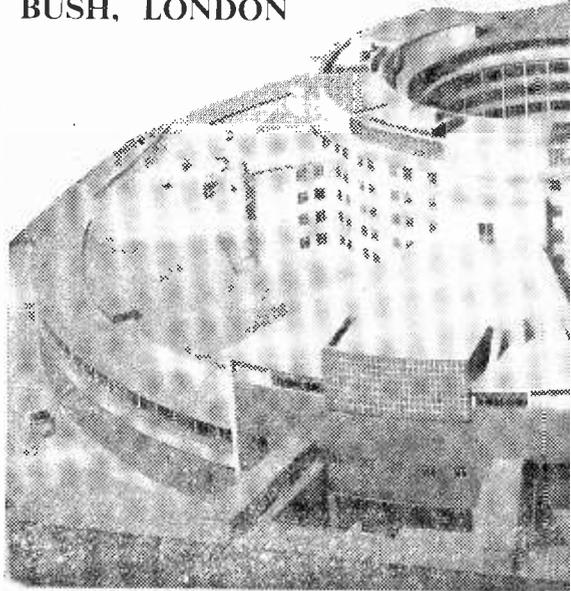an inner ring going up to the seventh floor and outside this ring radiating from it are the studios and the central wedge. The ring encloses a circular garden, some 150ft in diameter, in centre of which will be a fountain and sculpture. The size of this block can be judged from the fact that it will include more than 2,500 doors.



This view (of a model of the TV centre) is from "and future"

The Studios


The layout of the studios has been so designed that the additional requirements in ventilation, lighting, power supply, for colour television can be accommodated when required and is evidence of the planning which has gone into the development of the centre. Four of the studios will be bigger than any television studio now in use in Britain and each studio will have its own air-conditioning plant.

It is planned to complete studios 2, 3, 4 and 5 first. Number 3 is expected to be in service during this year and the remainder will be brought into service about the middle of this year and it is planned to complete all four by the end of 1961. Orders have already been made for the purchasing of the most advanced television camera channels (a camera channel includes a TV camera and its associated electronic equipment).

The two largest studios have a floor area of some 8,000sq. ft each compared with 6,000sq. ft. in the largest studio at Riverside Hammersmith. In these two studios there will be four working channels and one spare.

Studio One

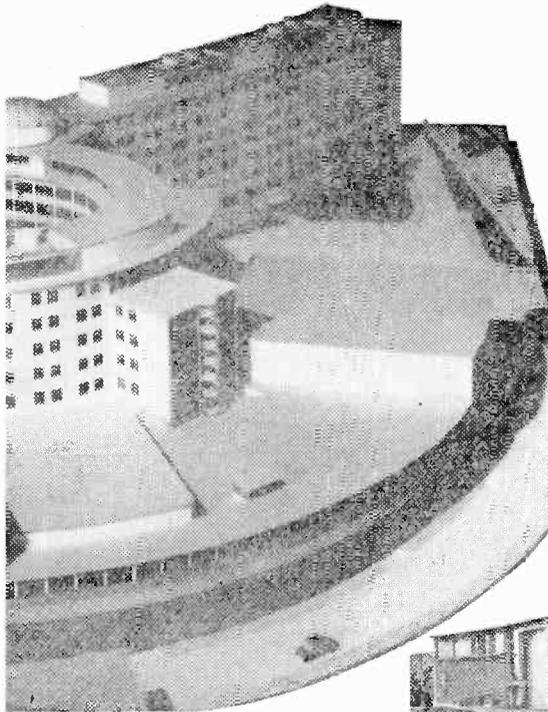This will be the largest—some 180ft x 100ft x 54ft high—and will have a pit, 7ft 6in. deep into which part of the floor, 50ft by 30ft can be lowered. If required it will be possible to fill this pit with water for programmes of an aquatic nature. It is interesting to note that the floor is





south-east and shows the main block of it."

designed to carry quite heavy loads and could be used to accommodate a circus with "a line of elephants each with its forelegs resting on the hindquarters of the one in front." This studio will be used for light entertainment and musical programmes and it will be possible to accommodate an audience of 600. The other studios are intended for general purposes (dramatic productions, talks, etc.) and Studio 6 will be so constructed that if experience shows that two small studios will be more useful, it can be divided.

Control Room

The first and second floors of the building will house the technical areas; the studio and control rooms at first floor level in the ring look down into

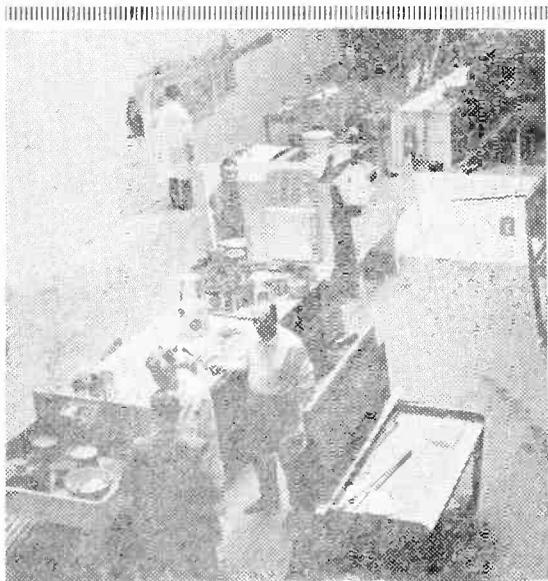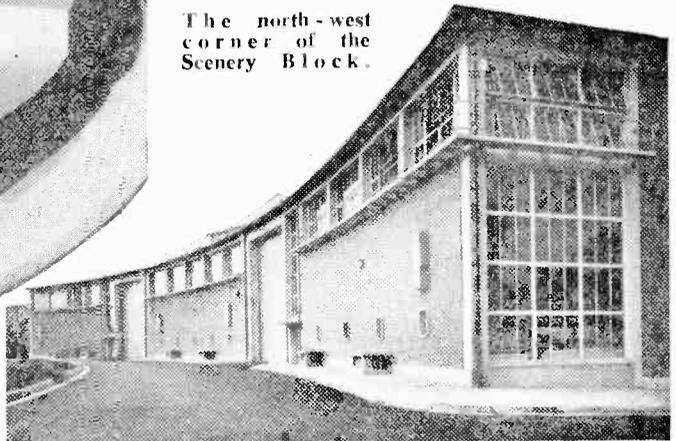The north-west corner of the Scenery Block.



Scenic artists' studio where painted backcloths are used. The studio houses six frames each of which can be raised or lowered to enable the artist to work on floor level.

each of the seven studios radiating from it. The central wedge between Studios 3 and 4 will accommodate other technical areas including Tele-Cine Presentation Suites in the central apparatus rooms. The Continental Control Point for Eurovision Programmes in this country, which is at present in Broadcasting House, will also be housed in this central wedge. The roof of this section will be used when necessary for outdoor filming.

Offices

From the third floor of the ring upwards to seventh floor, much of the space will be used for offices, with wardrobe section including tailoring and laundry; make-up and music departments will be at the third floor. Part of fourth floor will be used as BBC club with roof garden on the top of Studio 6.

The Scenery Block

This was completed in 1953 and it includes the workshops, the lighting and scenery and properties used in stage sets in television productions, a scenery painting studio, extensive storage space for scenery and properties and about 200 offices.

At the outer end, the studios are linked by an internal runway, 25ft wide.


Along this, properties and scenery will be conveyed to the studio. These will come direct from

the Scenery Block. Supplementary lights and backcloths will be operated from a lighting gallery which will surround each studio at a high level. The Scenery Block is already in use and covers one acre. It houses the Television Design Department

central wedge between studios 3 and 4. All programmes, whether they originate from inside the building, from other studios or from outside broadcasting units will pass through this control room.

Seating

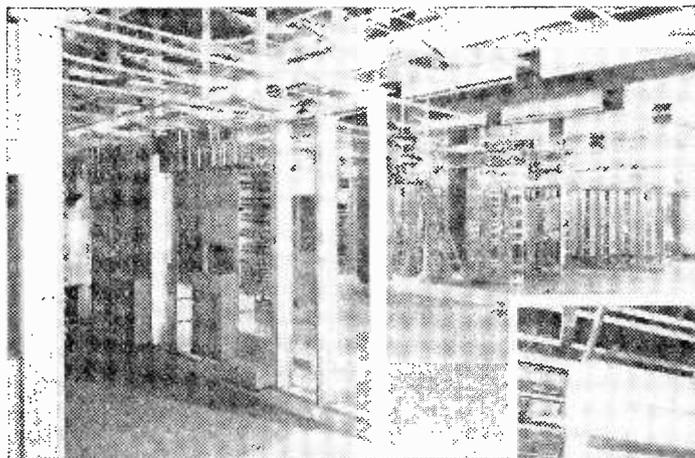Public audiences will be admitted to the studios for certain programmes and tiered demountable seating will be provided in each studio according to need. The public will be conducted around the Central Courtyard to audience entrances and then direct to the studios along wide corridors. These corridors are isolated from the dressing rooms and skirt the Assembly Areas, en




General view of the sound and vision bays in the Central Apparatus Room.

where scenery is devised and made in the adjoining carpentry and plaster shops. The scenic artists' studio (illustrated on the previous page) is used for the painting of backcloths and is 65ft high. The artists work on an intermediate platform which is about 25ft above the floor of the studio and the surface to be painted can be moved up or down electrically from a console

The Performers

On the ground floor and the basement there will be about 120 dressing rooms, with accommodation for about 550 people. These rooms are all arranged around or under the central ring, and entry to the studios is therefore through doors at their inner end. There are three assembly areas, serving different groups of studios, each with its own Green Room, tea bar, and other services. Parts of the first and second floor of the central wedge will be devoted to telecine equipment and the final check on the quality of television pictures from the studios, before they are passed on to the transmitters, will be made in "quality check rooms" which will be on the third floor. All the apparatus which can be conveniently accommodated in one central area will be in a central apparatus room also on the third floor. A major part of the area below the central lawn, which will be some 150ft in diameter, is for tele-recording equipment. On the second floor of the main building will be the base technical maintenance workshops, rest rooms and equipment stores. There, immediate repairs to the television engineering equipment will be carried out. The central control room will be positioned in the

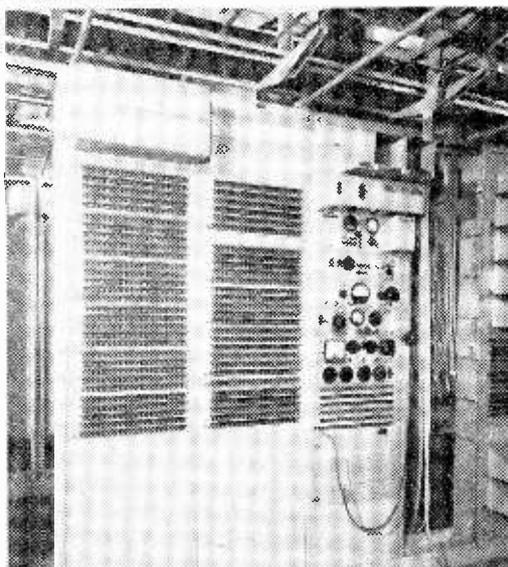

Sound jackfield and A.C. test bays.

route to the studios. Between studios are storage areas for the housing of technical equipment such as cameras and microphone booms; also for furniture and other properties when not needed on the studio floor.

At 13ft 6in. above studio floor level are the studio control rooms. These, covering vision, sound and lighting are provided within the ring ranged along the end of each studio and the control staff look down into the studio through a window running along the full width. Behind each set of studio control rooms are the apparatus rooms, and attendant first-aid repair workshops, with two small electric hoists to the maintenance workshops on the floor above.

The architect for the TV Centre project is Graham Dawbarn (Norman and Dawbarn) in association with M. T. Tudsbury, C.B.E., consulting engineer to the BBC.

Frame Sync Separator

A STABLE, TWO-VALVE CIRCUIT


By J. Woodhead

BECAUSE of the inconstant output waveform of the normal frame pulse integrator, an accurate interlacing of odd and even frames is difficult, if not impossible, to attain.


The following method of separating the frame from the line pulses does not depend on any form

practically unattenuated. C2 is merely a coupling condenser.

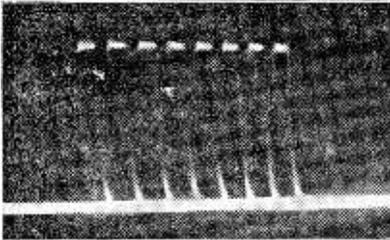V2 is the frame pulse separator. Working as an anode bend detector it is biased beyond cut-off, only the frame sync pulses causing anode current to flow. The bias, and thus the amplitude of the output is adjusted by R7.



Waveform at anode of V2.

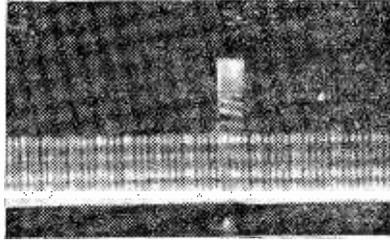

Waveform at grid of V2.

of integrating network. With this kind of separator only the leading frame pulse is required for triggering the time base oscillator, although all eight are produced in the output. This does not mean that perfect interlacing is ensured, as so much depends on the accurate firing of the time base, but a definite improvement should result, even if it tends to fire erratically.

will be of constant amplitude, provided the sync input to the grid is sufficient to cause clipping of the pulses.

Function

The working of the circuit is fairly straightforward. A negative-going sync input is required.

V1 clips the sync pulses and reverses their phase, producing a positive-going signal at the anode. L and C3 form a combination which works as a rejector circuit for the line sync, leaving the frame pulses

Stability

The circuit is very stable in operation, the bias of V2 being set to a satisfactory point at which it can then be left, as all pulses at V1 anode

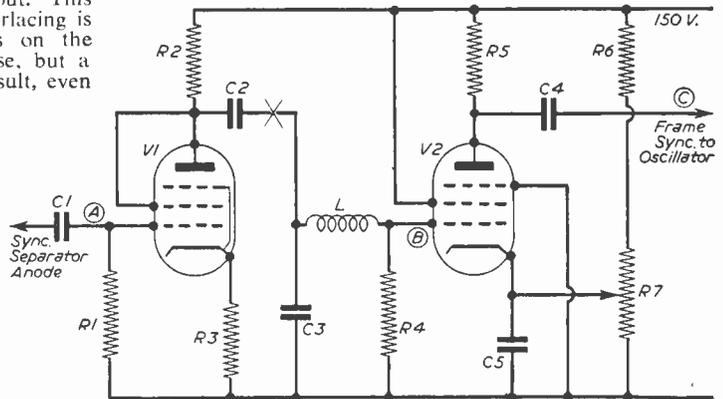


Fig. 1.—Circuit of the separator.

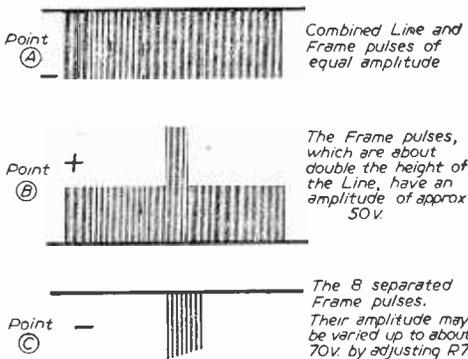


Fig. 2—Waveform at the points indicated.

LIST OF COMPONENTS

- V1—6AK5 or 6AM6 for 0.3A series heater operation.
- V2—6AM6.
- R1—22k ½W.
- R2, R5—47k ½W.
- R3—150 ½W.
- R4—2.2M ½W.
- R6—33k 1W.
- R7—10k wire wound.
- C1, C2, C4, C5—0.1µF paper.
- C3—300pF Mica.
- 2 B7G holders.
- L—Wearite PHF1, longwave coil with the aerial winding removed.

For ease of insertion into an existing receiver the circuit can be built up on two small chassis, or small aluminium sheets which can be bolted to the existing chassis at convenient points. At point X, the lead can be broken and extended by up to a foot, provided it is kept away from points of interference like the line time base.

H.T. Droppers

It is left to the constructor to calculate the value of resistors for dropping the H.T. to about 150 volts from the H.T. rail of his receiver. Large value de-coupling condensers can be used to ensure that 50c/s ripple, or interference, on the H.T. line, does not affect the pulses.

These components are best fitted in the existing receiver so the unit(s) can be made as small as possible.

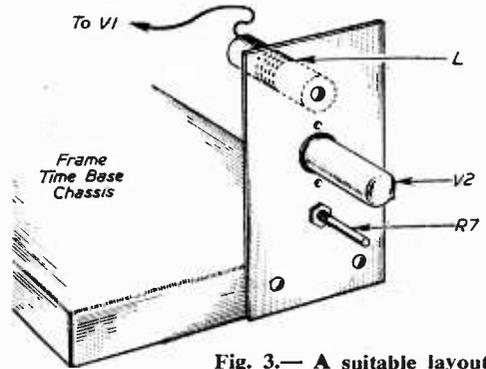


Fig. 3.— A suitable layout.

RESOLUTION *(Continued from page 291)*

embrace the required range of frequencies and yet the picture still does not show the full complement of bars.

Spot size is one factor because if the diameter of the spot is larger than the width of the bar then the bar will not be seen.

Another factor is the video output stage; it is useless for the tuning stages to be broadened if the video output stage will not pass the full bandwidth.

A further factor is the aerial system. Where highly directional arrays are used as in the fringe areas the aerial itself may not provide sufficient gain at the edges of the band it is supposed to encompass.

The range of frequencies injected into the receiver by the aerial system at a fairly even level may not cover the 3Mc/s. Much depends not only on the aerial itself but also on its proximity to local objects, the type of feeder and method of injection.

It has been the author's experience that there are very few commercial sets which will reproduce the 3Mc/s bars in true black and white.

Vertical versus Horizontal Definition

The figures for the bandwidth necessary for reasonable definition have been based on the vertical definition of the picture. We have assumed that the picture is divided into a number of horizontal lines, the total number of active lines being 377, and from this we have derived a figure for the required bandwidth.

One factor which has not been taken into account is that there is a certain distance between adjacent lines which is included in the aspect ratio of 4/3.

To obtain the optimum horizontal definition we must make it equal the vertical definition. The optimum viewing distance is where the horizontal lines comprising the picture just merge together so that line structure is not observed.

This optimum viewing distance will vary with the visual acuity of the observer; a person with good sight should sit farther from the screen than one with poorer sight.

Now here is a simple experiment which you can make yourself, if your set will resolve the 3Mc/s bars, or if you have access to one which will.

First check that the bars are received correctly and are not spurious owing to "ringing." The best method is to count the number of bars seen in

each square on test card "C". The 2.0Mc/s bars should have 8 distinct black lines, those representing 2.5Mc/s should have 10, and the 3.0Mc/s bars should have 12.

Count the lines carefully to see that they are all there and, if necessary, adjust the focus on the bars and not on the horizontal lines. Normally, the 3.0Mc/s bars will be reproduced at reduced contrast, but they should be distinctly observed as individual bars.

Having verified that the bars are correctly reproduced, ignore them for the moment and then move back from the screen until the *horizontal lines* merge together so that they are no longer visible as separate lines; the background of the picture should appear complete and whole.

The position in which you are now is the optimum position for viewing for yourself. At this point observe the screen closely (without falling into the temptation of moving your head forward) and endeavour to see the 3Mc/s bars. If you cannot see them clearly then move forward towards the screen until they can be distinguished. This will be the position of optimum horizontal resolution.


Generally, you will find that to distinguish the vertical bars you will have to move forward and when you can observe them you will note that the line structure of the picture is also quite visible.

From this it follows that the optimum viewing position for horizontal resolution is not the same as for vertical resolution. As it is important that the line structure should not be observed, then if at this point the 3Mc/s bars cannot be distinguished it is *useless making the receiving circuits capable of resolving them!*

Advantages of Reduced Bandwidth

Reducing the bandwidth to a lower figure has several advantages. The most important is that the gain of the receiver is increased—a not inconsiderable factor for the fringe viewer. For fringe reception 2.5Mc/s is adequate.

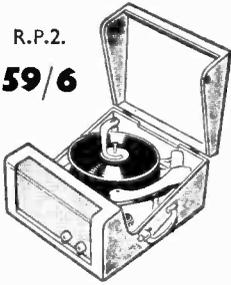The fringe viewer would do well to bear this in mind. A picture with decreased horizontal definition but increased overall clarity with absence of background mush and "snow" is much preferable to one which has a marvellous definition, but in which all action appears to take place in a snow-storm.




R.P.2.
59/6

A beautifully styled cabinet. Made by a famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½ in. deep. Will take a B.S.R. Monarch 4-speed Auto-changer and 7 x 4 in. elliptical speaker and most of the modern portable amplifiers. Carr. & Ins. 4/6.


EXTENSION SPEAKERS 19/9

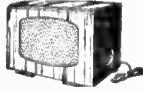Polished oak cabinet of attractive appearance. Fitted with 8 in. P.M. speaker W.B. or Goodmans of the highest quality. Standard matching to any receiver (2.5 ohms). Switch and flex included. Ins. & Carr. 3/9.




R.P.3.
69/6

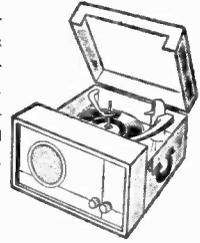A delightful looking cabinet 14½ in. x 17½ in. x 8½ in. in 2-tone leatherette. Will take a B.S.R. Monarch 4-speed auto-changer and 6½ in. round speaker. Carr. & Ins. 4/6



MODERN 17" T/V CHASSIS 24 GNS. COMPLETE AND WORKING

A chassis including 17 in. tube, permanent magnet speaker, 13 channel Turret Tuner (any two selected channels fitted). Other channels supplied on request at 7/6 each. 13 valves. Chassis and valves guaranteed for three months. CRT. 2 months' full guarantee. Sound I.F. 19.5 Mc/s. Vision 16 Mc/s. A.C. only. Ready and working to fit into your own cabinet. Carr. & Ins. 25/- As above, with 14in. tube, complete and working. £19.19.0.

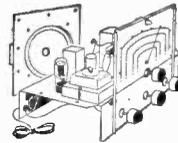

CASH PRICE
79/6

SUPER CHASSIS


5/1 initial payment & 19 weeks at 3/11

5-valve superhet chassis, including 8 in. P.M. speaker and valves. Four control knobs (tone, volume, tuning, w/change switch). Four w/bands with position for gram. p.u. and extension speaker. A.C. Carr. & Ins. 5/6.

NO DEPOSIT—INTEREST FREE—20 or 36 WEEKS TO PAY
send for a **FREE** catalogue—full details on goods and easy payments

AMPLIFIERS

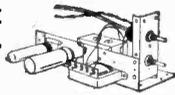12 months' guarantee
ALL PORTABLE AMPLIFIER Mk. D.1. 59/6



Brand new. Latest design with printed circuit. Dimensions 7 x 2½ x 5 in. A.C. only. Mains isolated 2-3 watts output. Incorporating EL84 as high gain output valve. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

AMPLIFIER Mk. D.2 79/6

Printed circuit. Latest design. Dimensions 7 x 2½ x 5 in. A.C. only. Mains isolated. 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve giving higher undistorted output. Volume and tone controls. Knobs 2/6 extra. P. & P. 3/6.

AMPLIFIER Mk. D.3 89/6

De-luxe model. Printed circuit. Latest design. Dimensions 7 x 2½ x 5 in. A.C. only. Mains isolated. 3-4 watts output. Incorporating the latest ECL82 triode pentode output valve, giving higher undistorted output. Volume, treble and bass control. Knobs 3/6 extra. P. & P. 3/6.

AMPLIFIER Mk. D.5 39/6

Simple circuit employing ECL80 triode pentode output valve giving 2-3 watts output. A.C. only. Mains isolated. Single control for volume and on/off switch with knob. P. & P. 3/6.

3 TRANSISTOR AMPLIFIER 79/6

9 volts. 1 control. P. & P. 3/6.


Many other types and sizes of beautifully designed cabinets in stock at prices from 29/6 to 79/6.

U.A.8. B.S.R. MONARCH 4-SPEED AUTO-CHANGER
8/1 initial payment and 19 weekly payments of 6/11. (Cash Price £6.19.6.)

T.U.9. B.S.R. 4-SPEED SINGLE PLAYER, 89/6
Carr. & Ins. 5/6

COLLARO CONQUEST 4-SPEED AUTOCHANGER
8/1 initial payment and 19 weekly payments of 6/11. (Cash price £6.19.6.)

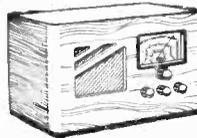COLLARO CONQUEST STEREO AUTOCHANGER
12/6 initial payment and 19 weekly payments of 11/6. (Cash price 11 guineas.) Carr. & Ins. on the above 5/6.




HOME RADIO 5/1 (Initial Payment)

BALANCE PAYABLE AT 3/11 OVER A PERIOD OF 19 WEEKS.
A.C./D.C. Universal mains 5-valve octal superhet 3 waveband receiver can be adapted to gram p.u. In attractive wooden cabinet, 9½ x 18½ x 11½ in. Carr. & Ins. 4/6.
CASH PRICE 79/6

STURDY CASE, 12/6

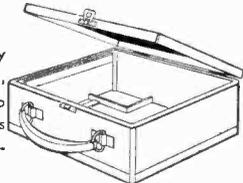8½ x 7½ x 3½ in. deep. Covered in burgundy and grey washable rexine. Strong clasp, hinges and handle. Ideal for portable radio chassis or transistor set. Can be adapted as a record carrying case to hold 18 seven-inch long-playing records. P. & P. 2/6.



DUKE & CO. (Dept E.3.)

621/3 Romford Road, Manor Park, E.12.

ILF 6001/3

A NEW SERVICE BY SUFFOLK

Suffolk Tubes now offer the finest service available in rebuilt picture tubes.

EACH TUBE IS COMPLETELY RE-SCREENED AND ALUMINISED

Normal rebuilds still available at reduced costs.
All fitted with **NEW GUN UNITS**
and fully guaranteed for **12 MONTHS**.
Free, immediate delivery in U.K.

SUFFOLK TUBES LTD

The largest independent Tube Rebuilders in London.




Suffolk Hall, 1-3 Upper Richmond Road, Putney, S.W.15. Tel.: VAN 5267, 4304.

NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING... 1st stage receiver

ANNOUNCING—after many years of highly successful operation in the U.S.A. and in Europe—the latest system in home training in electronics is now introduced by an entirely new British training organisation. **AT LAST**—a comprehensive and simple way of learning—by practical means—the basic principles of radio and electronics, with a minimum of theory. **YOU LEARN BY BUILDING** actual equipment with the components and parts which we send you. You advance by simple steps using high quality equipment and performing a whole series of interesting and instructive experiments. No mathematics! **INSTRUCTION MANUALS** and our teaching staff employ the latest techniques for showing clearly how radio works in a practical and interesting manner. You really have fun whilst learning! And you end by possessing a first rate piece of home equipment with the full knowledge of how it operates and—very important—how to service and maintain it afterwards. A full library of magnificent illustrated textbooks are included with the Courses. **IN FACT** for the 'Do-it-Yourself' enthusiast, the hobbyist, or those wanting help with their radio career training, or to set up their own full or part-time servicing business—then this new and exciting instructional system is exactly what is needed and it can all be provided at very moderate cost. Easy payments available. Post the coupon now, for full details. There is no obligation.

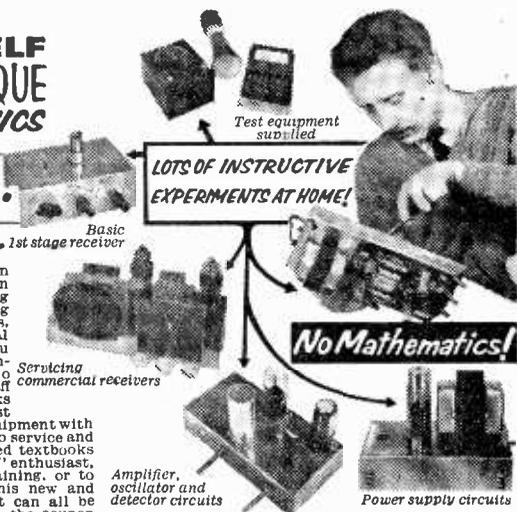

BUILD YOUR OWN • RADIO EQUIPMENT • TEST GEAR
• HI-FI INSTALLATION—AND LEARN AS YOU DO IT

RADIOSTRUCTOR



BRITAIN'S LEADING RADIO TRAINING ORGANISATION

To: **RADIOSTRUCTOR (Dept. G40)**,
40 Russell Street, Reading, Berks.

Please send brochure, without obligation, to:

Name _____
Address _____
BLOCK CAPS. PLEASE

(821) We do not employ representatives **3-80**

Siting TV Aerials

ALIGNING AERIALS FOR OPTIMUM RESULTS

By P. J. Clark

AERIAL siting is a relatively simple procedure on Band I, and in many instances it is only necessary to set the aerial on a pre-determined compass bearing. This procedure is generally adequate in service areas and in near fringe areas where little interference and ghosting is experienced.

In extreme fringe areas or where ghosting and interference is troublesome, however, the task may not be quite as simple. Here it often pays either to site the aerial for maximum pick-up, maximum signal-to-noise ratio, or for minimum ghosting. The trouble is, of course, aggravated to a large degree where a complex multi-element array is necessary, owing to its relatively small angle of pick-up.

In cases such as these, some form of contact between the man on the roof and an operator at the receiver is most desirable, as then the array may be readily rotated for the best picture.

Now that Band III is open, many multi-element Band III aerials are being installed. These aerials, owing to their high gain and large number of elements, possess an extremely narrow angle of pick-up, considerably less than any Band I aerial of the multi-element variety.

Critical Positioning

With certain arrays of this kind it is necessary only to swing it a matter of 5 to 10 degrees to pass right across the acceptance angle and thus go from a point of minimum pick-up to a maximum pick-up and then again to a point of minimum pick-up, even if an accurate compass bearing can be obtained at the site in relation to the transmitter, it is most difficult and in some cases almost impossible to set the aerial within such a fine tolerance.

This is particularly marked in areas of very low signal strength, where it is quite feasible to install the array by compass and then discover later that the picture is well below expectations. In a lot of cases of poor Band III pictures investigated in the fringe area by the writer, the trouble has been caused solely by inaccurate aerial siting. In some extreme cases no picture at all could be obtained until the array was rotated just a matter of degrees!

Clearly, then, something more than purely verbal contact is required between the receiver operator and the aerial rigger. A telephone can be a great help, of course, but some more definite means of setting the aerial is almost essential.

A Solution

Several experiments have been carried out by the writer in an endeavour to find a simple solution to the problem. It was first thought that the obvious solution simply involved running a length of twin cable from across the receiver's low-impedance loudspeaker tags to an A.C. voltmeter or audio output meter conveniently situated in proximity to the aerial.

This method was tried by adjusting the receiver to give a readable indication on the meter during a

test-tone transmission. The aerial could undoubtedly be adjusted to provide a peak reading, but three main drawbacks were observed.

First, it was soon discovered that a steady test-tone transmission is not always available when required, and it is hopeless trying to make a delicate adjustment when the meter needle is flicking to-and-fro in rhythm with any other modulation.

Secondly, it was noticed that even if the aerial was adjusted for maximum sound, this may not represent the optimum position for maximum vision. This effect, however, may have been aggravated since the aerial which was used appeared to have a wider pick-up angle at the sound frequency than at the vision frequency—though this was not proved conclusively.

Thirdly the effect of the sound AVC was most noticeable unless the input signal to the receiver was sufficiently attenuated. It may have been the AVC action, of course, which was tending to emphasise effect number two. Unfortunately, the AVC system on most commercial TV receivers cannot quickly be disconnected and reconnected.

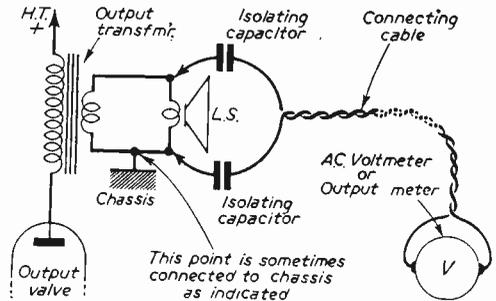


Fig. 1.—Using the sound signal.

Isolation

If any reader wishes to try out this method for himself, care should be taken to ensure that the chassis of the receiver used is adequately isolated from the cable. Remembering that a TV aerial is usually well earthed, and that if the cable connected to the output meter is live and happens to be touched by the rigger at the same time as the aerial, the effect may be dangerous, particularly if the rigger is perched precariously on the apex of a roof.

Two good A.C. isolated capacitors should be used between the loudspeaker terminals and the cable as shown in Fig. 1, and to be on the safe side it is as well to make sure that the receiver is connected to the mains in such a way that the chassis is in contact with the neutral side, where the receiver is of the A.C./D.C. variety, bearing in mind that the loudspeaker is connected direct to chassis on a large number of commercial sets.

Using the Vision Signal

Next, it was decided to experiment by using the vision signal as a general reference. The problem, however, was that of obtaining a meter indication at a point well removed from the receiver without unduly disturbing the function of the video stages. This was eventually solved by building a rectifying circuit into a small box which could readily be connected between the cathode connection at the picture-tube and receiver chassis.

Provided such an arrangement is connected to the set through short leads, it has very little adverse effect on the general function of the receiver, but is capable of supplying a D.C. voltage sufficient to give a usable indication on a standard moving-coil meter.

The circuit which was finally adopted is shown in Fig. 2. From this it will be realised that the voltage developed across the load resistor R3 corresponds to an average voltage representative of the composite picture-signal and synchronising pulses. This, the greater the white content of the picture, the greater will be the voltage across R3.

Modulation

For this reason, therefore, it is necessary to use the indicator for aerial siting purposes only during the transmission of a still picture, such as the test card. Nevertheless, the test card is radiated more frequently than the test-tone on sound, and at more convenient times—it is understood that the same will apply on Band III.

The rectifier unit makes use of a small crystal diode, and two isolating capacitors C1 and C2 are incorporated to eliminate the risk of shock. The variable resistor R1 acts as a form of sensitivity control which can be adjusted to provide the best indication on the voltmeter. A 4.7k resistor may, if desired, be connected in series with R1, so that the video circuits of the receiver will not be subjected to excessive damping by the diode circuit when R1 is set to minimum resistance. Capacitor C4 acts as a reservoir and also provides a certain degree of damping on the voltmeter. This is bypassed by a 50pF non-inductive capacitor C3 to keep R.F. out of the connecting cable.

Even when used with receivers embodying AGC in the vision channel a maximum can usually be obtained on the voltmeter when the aerial is accurately sited. In areas of very high signal strength, however, the vision AGC may tend to flatten the peak, though this effect can nearly always be countered by the use of a suitable attenuator in the aerial lead, or by reducing the sensitivity setting on the receiver. But, as was intimated earlier, a device of this kind is of most use in areas of low signal strength.

Experiments seem to indicate that siting the aerial for maximum vision signal is much better than siting for maximum sound.

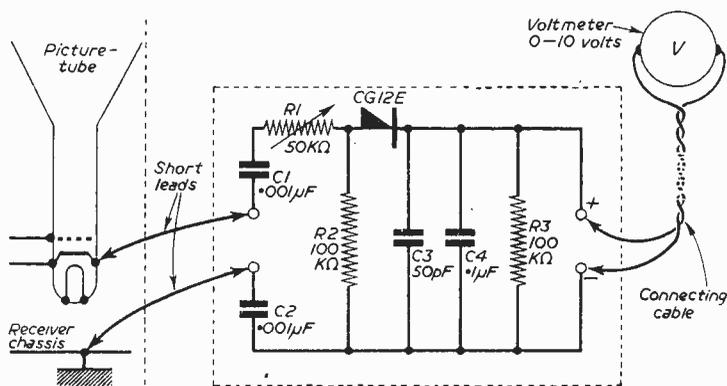


Fig. 2.—Using the vision signal.

AUSTRALIAN TV

by G. W. Oliphant

FOLLOWING the "boom" of 1958, the past twelve months have seen a phenomenal expansion of TV in Australia.

In 1958, when transmitters were operating only in Melbourne and Sydney, over 300,000 receiving licences were issued. Now, transmitters have been established in three other State capitals, Brisbane, Adelaide and Perth (Hobart is to follow suit in May), and the estimate is that new licences will total over 200,000.

Operation

At present the transmitter grouping is that each locality has one ABC station, operating non-commercially, and closely following BBC lines, together with two commercial stations. The standard of 625 lines at 50 frames, together with positive modulation and the use of equalising pulses in the vertical sync block, makes receiver design relatively straightforward, and both definition and interlace are of high quality.

Among the receiver manufacturers there are several British representatives, including H.M.V., the Ferguson Radio Corporation (who use the trade name 'Atlas'), Pye and Ekco, and there is strong competition both from American firms—Healing, Admiral and Stromberg-Carlson amongst others—and from the huge Amalgamated Wireless Australasia. The 21in. set is firmly established as the popular size receiver; the average cost of a table model now is about £120 sterling, compared with £160 a year ago.

Fringe Area Models

Already, with an eye to the future, designers are concentrating on models for use in areas of poor signal strength. Extra I.F. stages are making their appearance, and the phase discriminator, with its better horizontal hold, is tending to replace normal synchroguide in the horizontal sync circuit.

In the country areas, some distance from the capital cities, it is now a common sight to see "toast-rack" aerial arrays on masts forty or fifty feet high.

VITAL OPPORTUNITY for "Practical Television" readers

YOURS-the key to **BIGGER PAY** and **SUCCESS!**

MATHS FOR ALL



ALL AT YOUR FINGER-TIPS!

Arithmetic, Algebra, Geometry, Trigonometry, Calculus, Graphs, Mechanics for the Layman. Maths for the Builder and Handyman. Mathematics of Electricity. Living within your means. Keeping Accounts, Etc.

HELPS IN YOUR CAREER — SOLVES HUNDREDS OF EVERYDAY PROBLEMS!

Hurry to secure your copy of this amazing quick-results aid to the subject that can prove for you—just as it has for thousands—the stepping stone to success! Here is the book with which YOU can master MATHS—actually find it FUN! Will prove invaluable to you in your daily life. Specially written for the general reader, it reveals mathematical "short cuts," the simple way to solve hundreds of business and home problems. Helps you tackle all kinds of jobs with greater success; even helps with your football pools! 448 pages of clear examples, self-testing questions and entertaining brain-teasers.

448 PAGES OVER 400 DIAGRAMS

A GOLD-MINE OF FACTS FOR THE PRACTICAL MAN



Learn how, with a knowledge of maths, you can save money in the home, solve all kinds of problems. Even on home improvements you will cut out guess work, do jobs more economically.



A LIFETIME'S INVESTMENT!

Whatever your reason for wishing to improve your knowledge of MATHS, you will find this great volume an investment that will pay you rich dividends for the rest of your life.

TO HELP YOU BALANCE YOUR BUDGET


With a knowledge of mathematics and some applied common sense you can avoid some of the shocks we all experience with our personal and household accounts. Learn all about hire purchase, mortgages, how to work out your own income tax allowances, etc.



DO THIS NOW!

Simply complete form, and post in 2d. stamped, unsealed envelope to Dept. H.F. 21, People's Home Library, Basted, Sevenoaks, Kent. Offer applies in U.K. and Eire only, closes March 31.

FULL SATISFACTION GUARANTEE

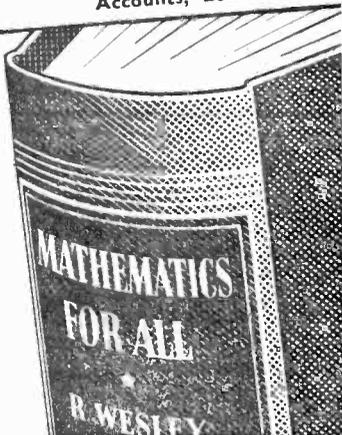

CLAIM YOURS AT ONCE!

Reserve NOW at amazingly low cost! Standard Edition, 16/6. or De Luxe Edition, superb leathercloth, at extra cost of only 2/-. Prices include postage, etc.

WORKING MAN or BUSINESS MAN—YOU NEED MATHS!

From sizing up the best way to tackle a job or estimate quantities, to knowing how to price goods or calculate overheads, you need the knowledge this book gives.

FOR STUDENT OR OFFICE WORKER

Increase your earning power and enhance your chances of promotion by acquiring a sound knowledge of mathematics from the pages of this invaluable volume.



MATHS TO THE AID OF THE HANDYMAN



There is a complete section in the book specially for the handyman—packed with advice that will help you to do all kinds of jobs in the quickest and most economical way.

SEND NO MONEY NOW!

To: Dept. H.F.21, People's Home Library, Basted, Sevenoaks, Kent. WITHOUT OBLIGATION reserve me "Mathematics for All" and send Special Invoice with "100% Satisfaction or No Charge" Guarantee. Cross out Edition NOT required: STANDARD/DE LUXE

NAME BLOCK LETTERS
Full Postal ADDRESS
H.F.21/March 1960
Firmly affix 2d. stamp in margin

RECORD PLAYER UNIT
BSR Monarch, Model UA8. 4-speed. 10 records capacity. Ful-FI turnover crystal cartridge. £6.19.6. Carriage 3/6.

TELEVISION TUBES
Regunned, 12 months' guarantee. Most types available. E.G., M.W. 43/64, £6. CRM 141, £5.10.0. CRM 171, £6. Carriage and Insurance 10/-.

CHASSIS
Aluminium Un drilled with Reinforced Corner. Available in the following sizes:
each each
8" x 4" x 2 1/2" .. 4/6 12" x 8" x 2 1/2" .. 8/6
8" x 6" x 2 1/2" .. 6/3 14" x 3" x 2 1/2" .. 6/-
10" x 7" x 2 1/2" .. 7/3 14" x 9" x 2 1/2" .. 12/-
12" x 3" x 2 1/2" .. 5/9 16" x 6" x 2 1/2" .. 8/6
12" x 5" x 2 1/2" .. 6/9 16" x 10" x 2 1/2" .. 14/-

HEATER TRANSFORMERS—Primary 240 volts
2 v. 1 amp. .. 5/- 6.3 v. 1 1/2 amp. .. 6/9
2 v. 3 amp. .. 8/3 6.3 v. 3 amp. .. 10/-
4 v. 1 1/2 amp. .. 5/8 6.3 v. 1 1/2 amp. .. 5/6
4 v. 3 amp. .. 10/- 12 v. 1 amp. .. 5/9
5 v. 2 amp. .. 10/-

ACOS MICROPHONES
Acos Mic 39-1. Crystal Stick Microphones for use as a hand, desk or floor stand unit, for high quality recording, broadcasting and public address work. List price £5.50. OUR PRICE 39/6. With stand 47/6. With floor stand adaptor 52/6. Postage 1/6.
Acos Mic 40, as supplied with most modern tape recorders, with folding rest and 8' lead response 40-6000 c.p.s. Listed at 35/-, OUR PRICE 25/-.

MULTI-WAY CABLE
5 colour-coded wires (1 screened). Ideal for mobile or inter-chassis connection. Any lengths cut 1/- per yard. P. & F. 1/6 min.

MICRO SWITCHES 3/9 each.

BATTERY BUZZERS 3/9 each.

ALPHA RADIO TERMS.—Cash with order or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 1/3; 20/- add 1/9; 40/- add 2/6; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

ALPHA RADIO SUPPLY CO.

VALVES GUARANTEED ALL TESTED BEFORE DESPATCH

AZ31 10/-	MHL4 (Met) 5Z4G 9/-
D42 7/-	6A7 10/-
DF96 8/9	MKT4 (7-pin) 6AL5 4/6
DH101 10/-	12- 6AM5 12/6
DK96 8/9	PCC84 9/-
DL96 8/9	PCF80 9/6
EBC33 6/9	PL81 12/6
EBC41 9/6	PL82 8/6
ECC84 10/-	PX25 12/6
ECC85 9/6	PY81 8/6
ECC90 12/-	PEN4VA 8/6
ECH82 9/6	12/6 6Q7G 7/6
ECH81 9/-	PEN25 6/-
ECL80 10/-	PEN44 15/-
EP39 5/9	SP41 3/-
EP40 14/6	SP61 3/-
EP41 9/9	U25 14/-
EP42 11/-	UCH42 10/6
EP86 13/-	VU39 12A06 8/-
EL41 10/6	(MU)12/14/8/9 12AX7 8/-
EL42 10/6	W91M 10/6
EL84 9/-	W101M 12/6
EM80 10/-	X76M 10/-
EY51 10/-	Z21 (4-pin) 25Z4 9/6
EY86 10/-	42 8/-
EZ30 7/-	80 8/6
GZ32 12/-	1N5 10/6
KT32 14/-	1R5 7/6
KT33C 8/6	1T4 6/-
KT66 17/6	3S4 7/6
KT101 10/6	5U4G 6/6
KTW81 8/6	5Z3G 8/-
	10P13 15/-

CATALOGUE
Our 1960 catalogue is now available. Please send 1/- in stamps for your copy.

RECTIFIERS FOR BATTERY CHARGERS
12 v. 1 amp. .. 4/3 12 v. 3 amp. .. 10/6
12 v. 2 amp. .. 7/- 12 v. 4 amp. .. 12/-
12 v. 5 amp. .. 14/6

CHARGER TRANSFORMERS
Tapper Primary 200/240 v., Secondary 3.5 v., 5 v. and 17 v., 1 amp. type 13/6. 2 amp. type 15/6. 4 amp. type 21/- 6 amp. type 32/6. Post 2/-

DPDT TOGGLE SWITCHES
(by Cutler Hammer) 2/6 each.

100 RESISTORS
Assorted 1, 1 1/2 and 1 watt. 12/6 packet.

WIRELESS WORLD VALVE DATA BOOK. 5/- each. Post 4d.

DATA TV FAULT FINDING BOOK
(Illustrated), 5/-, Post 4d.

MORSE KEYS 3/- each.

ACOS CRYSTAL PICK-UPS
Turnover Head (2 sapphire styl) 29/11. P. & P. 2/6.

DUBILIER TYPE "C" CONTROLS 500K. 6/6 each.

CO-AXIAL CABLE, semi-airspaced, 75 ohms. 6d. yard.

CRYSTAL CARTRIDGES. Complete with styl. Acos HEP3Y/1, HGP59/5C, BSR, TC8. Collaro Studio. All 15/6 each.

OUTPUT TRANSFORMERS
Elstone OT3 for Mullard 3 watt. Amplifier. 25/-.

Elstone OT8 Low Load, OT8 Normal Load, OP/ML Dist. Load, all 45/- and all for Mullard 5/10 amp.

Single ended 5000/3 ohms 40 m/a. 4/6. 5000/3 ohms 80 m/a. 5/9. 10000/3 ohms 30 m/a. 4/6.

Universal 18 Ratio Type 40 m/a. 5/9 each.

103 LEEDS TERRACE, WINTOUN STREET, LEEDS, 7.



Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Post Free 15/- per pair.

AVO LTD · AVOCET HOUSE, 92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1. VICTORIA 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES.

REGUNNED TV TUBES

Supplied from Stock and despatched by British Railways same day. COMPLETE NEW GUNS fitted in every tube and fully guaranteed for TWELVE MONTHS FROM DATE OF INSTALLATION.

	Mullard	Mazda
12 in.	£5.0.0	£5.0.0
14 in.	£5.0.0	£5.0.0
15 in.	—	£6.0.0
17 in.	£6.0.0	£6.0.0
21 in.	£8.0.0	£8.0.0


Carriage 5/- extra.

Other types available. Please contact:—

CLARKSONS (Tube Distributors)

120 Commercial Road, LEEDS 5

Phone: Leeds 56916

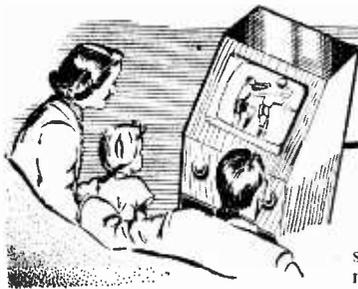

UNDERNEATH THE DIPOLE

A MONTHLY COMMENTARY

By Iconos

THE explosive effect of the American TV "payola" scandals continue to reverberate around the world. In the U.S.A. the elaborate quiz competition programmes have been much reduced and subjected to such close control and scrutiny that some viewers think that the life—and certainly the liveliness—has been squeezed out of them. But even in a form which is said to be "stodgy," they are still regarded with suspicion by some of the viewers. Any kind of deception, legitimate or otherwise, that may be practised is likely to be queried. Even the simple illusion of passing off Ampexed programmes as real live transmissions is regarded with disfavour. An announcement or a sub-title stating that a programme is recorded is often put on before Ampexed transmissions take place; otherwise there might be an accusation of trickery!

Trickery?

American newspapers made such a fuss—and rightly so—about the contrived and rigged quizzes, that they started a chain-reaction which has caused annoyance and consternation all over the world. Even the new Ulster ITA station has felt the icy blast of criticism. This station sponsored an ITN item which featured a story about Belfast prison and its parole system at Christmas for "good behaviour" prisoners. For certain shots warders played the part of prisoners walking down corridors, mainly with their backs to the camera. There arose a local outcry against "faking"! I would have thought that it was to the advantage of prisoners and all concerned that they should not be recognised, and that a simple stratagem of this kind was perfectly legitimate. A few days later the UTV "Roundabout" programme featured a local blues

singer, Otilie Patterson, who mimed her songs to a sound playback. A further howl of indignation arose, condemning the "fake" as being phoney and misleading to the public. Really! How very startling!

Playback

Playback has been used in film studios for many years, and vocal numbers are now rarely recorded direct. The sound is first recorded, with or without orchestra, and this is reproduced from film or tape for the actor to mime to when he is in front of the camera, moving about without the restrictions of a microphone hovering over his head. If the original recording is made without orchestral backing, a "quiet piano" system is used as an accompaniment. This quiet piano is barely audible on the sound track but is necessary for keeping the artiste in time and in tune! A full orchestral treatment is dubbed on the track when the picture is finally edited; otherwise an expensive and large orchestra would have to hang about the studios while complicated shots were made, with the usual lengthy breaks while the cameraman adjusts lighting. The same advantages apply to the use of musical playback for live television. The real point of criticism arises when the playback system is not carried out correctly.


Photographic Trickery

Now the advertisers are coming under the microscope of the witch-hunters of TV trickery. Someone has found out that products that polish floors or paint walls are not always used when the advertisement filmlets are photographed in a studio for television. The fact is, that unless the camera is aided a little, many subtle effects just do not register. The trivial deceptions of putting make-up on actors' faces, introducing perspective distortion in scenery, using fruit salts (mild, I

hope!) for champagne bubbles, have been used for stage and screen for many years. I am quite sure that the actors themselves would prefer drinking real whisky instead of cold tea or ginger ale! But these substitutions are all born of necessity, in the interests of the audience.

BBC News

THE British Kinematograph Society continues to sponsor many lectures of great interest to television technicians and viewers. Mr. S. W. Smithers, Manager of BBC Television News, recently gave a comprehensive and practical lecture on the complex organisation involved in world coverage for television news, not omitting valuable references to technical matters. The preferred medium for film interpolation is 16mm film with magnetic sound. It was a pleasure to listen to a programme executive who had such a sympathetic appreciation of the technical problems involved—including a realisation of the possibilities and limitation of new techniques such as Ampex.

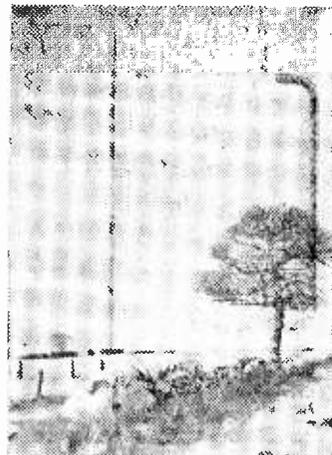

This view of the ITA station at Burnhope, near Durham, was taken after a snowfall and shows the 750ft. mast and buildings.

reversal film stock, the different types of cameras and so forth. Future lectures include "Modern Television Studios" by W. H. Cheevers of Associated Rediffusion, who will presumably deal with the new super studios at Wembley, "Film Editing Techniques for Television," a symposium, and "Planning of Regional Television Studios" by Walter Kemp, who was mainly responsible for TWW's Cardiff and Bristol Studios.

Site Values

THE planning of a new television studio starts with the selection of a site. The BBC and ITA contractors have all been faced at various times with the choice of a site in the centre of a town—which is probably expensive and requires the adaptation of existing premises—or the alternative of a bare piece of ground in a suburb, ripe for building entirely new premises especially designed for television purposes. The first organisation to achieve this was, of course, the BBC, which acquired a large plot of ground at Shepherd's Bush and has been building its huge television centre for the last three years or so. Of the I.T.A. contractors, Granada were the first to build premises from zero, taking a fine piece of bombed-out ground within a stone's throw of Deansgate, Manchester. Scottish Television bought the Theatre Royal, Glasgow, and adapted it. Tyne-Tees converted a warehouse at Newcastle, Southern converted a cinema in a suburb of Southampton and Anglia acquired the old Agricultural Hall in the very centre of Norwich. And now the latest television contractor, Westward Television, has announced that its studios will be built brand new, on a bare piece of ground in the "Theatre precinct" of Plymouth. This site adjoins the Drake Cinema, also the Athenaeum (now being built), and is very close to the Civic Centre. Thus Westward will be able to cover a large number of outside broadcasts without even taking their O.B. truck on the road! This is a really good move in the interests of locally originated programmes at Plymouth, and sounds to me like first-class regional planning. In any case, I would think that a good looking frontage in an important part of a town was most important from the public relations point of view.

Entertainment Standards

CRITICISM of TV programmes is loudly voiced in the morning train, in pubs and in clubs about individual programmes and items seen the previous evening, but the entertainment standards of both BBC and ITV are extremely high—thus throwing into the shadow the odd features which have limited appeal or are just a little below par. When the ordinary man-in-the-street goes on a seaside holiday and sees a local summer show or concert party, his comment, heard loudly in the local hostelry afterwards, probably goes like this: "Ah! It were a good show, and funny, too! But it wasn't as good as Benny Hill last night on the telly. Why can't they get Benny Hill down here in this show?" The fact that Benny Hill is a first-class comic requiring a first-class salary, that the authors and producers worked for days on writing and rehearsing his TV show, that the musicians and all the other contributors probably received in aggregate at least £3,000 for a 30 minute TV feature, is not taken into account. "Why don't they have an orchestra at the Picture Pavilion?" and "What they ought to do is to give quiz puzzles—refrigerators and washing machines" were other fatuous comments that I have heard, spoken by presumably intelligent people. The television companies are rich and prosperous. It is only right that they should divert some of their wealth to support

the remnants of local show business, especially the live theatre, the music hall, the summer shows and the orchestral concerts.

Film Transmission

IN my article last month, I mentioned that 70mm films pose problems for transmission on TV. The equipment cannot handle film 70mm wide. One method of sending excerpts from these films out on telecine is to have a special optical reduction print made on 35mm film of a section of the very wide picture, panning this particular part about on the main action during the optical reduction process, but the television reproduction of just a small section of the film frame will give a comparatively poor impression of "Ben Hur" or any similar epic made on this broad gauge film. The increase in definition, the improved colour values and the "solidness" of the sound, together with the tremendous size of the screen are all factors which the film people hope will draw audiences back into the cinemas. Over 400 cinemas in the USA have been equipped with suitable 70mm film projection equipment and there are already 38 installed in British cinemas. An important innovation of this kind cannot be ignored by the television film commentators. They will probably only be able to illustrate their remarks with still transparencies or reductions to narrow gauge film for the present telecine equipment.

PRACTICAL WIRELESS

Chief Contents of March Issue

Now on Sale, 1/6

TRANSISTORS FOR P.A.

SWITCHED TUNED T.R.F.

A COMPREHENSIVE PRE-AMP

TRANSISTORISED TIMING UNIT

IMPROVING THE No. "19" SET

MEASUREMENTS WITH MULTIMETERS

AN INDUCTANCE MEASURING INSTRUMENT

THE D.C.2 STEREO AMPLIFIER

A TRANSISTORISED VOLTMETER

EXPERIMENTAL S.W. THREE

ETC., ETC., ETC.



'Any fruit, today?' The pedlar calls at the Singapore home of Mrs. C., wife of an R.A.F. Corporal. Mrs. C.'s children seem to be looking for samples! The local girl is a home help.

The private life of Corporal C., R.A.F.

When you see a man in R.A.F. uniform, do you ever think about his life? Not just the essential job he does, but his home and his family? These family album pictures are from the life of Corporal C. He's an R.A.F. cook out in Singapore. He earns over £20 a week with overseas allowances, and pays 30/- for his house. This is his life, and it could be your life, too. Even if you're not yet trained for a trade, because the R.A.F. are ready to train you. Send the coupon below for all the details.



Corporal C. is in the airmen's mess. In the R.A.F. every man has a trade, and every trade has a place. See the list on the coupon for training opportunities.



Going swimming? Or just taking it easy? There's always plenty going on in the R.A.F. Like so many R.A.F. people overseas, they have their own car.



Their children go to this excellent Forces primary school. Like most Service children they love the life—and how many children fly half-way round the world?

POST TODAY. There are vacancies now for training in these R.A.F. trades. Tick your particular interest, and send for full details of R.A.F. careers.

Post to R.A.F. Central Recruiting Office (PTN45), Victory House, Kingsway, London, WC2

Wireless Operator.....	<input type="checkbox"/>	Teleprinter Op.	<input type="checkbox"/>	NAME
Radar Mechanic.....	<input type="checkbox"/>	Typist	<input type="checkbox"/>	
Tape Relay Op.	<input type="checkbox"/>	Nursing Attendant ..	<input type="checkbox"/>	ADDRESS
Progress Clerk.....	<input type="checkbox"/>	Electrical Mechanic ..	<input type="checkbox"/>	
Fireman	<input type="checkbox"/>	Air Defence Op.	<input type="checkbox"/>
Wireless Mechanic ..	<input type="checkbox"/>	Operations Clerk	<input type="checkbox"/>
Instrument Mech.	<input type="checkbox"/>	R.A.F. Police	<input type="checkbox"/>	DATE OF BIRTH.....

You'll get more out of life in the Royal Air Force

LASKY'S RADIO

MAKER'S SURPLUS COMPONENT BARGAINS


- WIDE ANGLE 38 mm.**
- Line E.H.T. Trans. Ferro-cube core, 9-16 kv. 19/6
 - Scanning Coils, Low imp. line and frame..... 19/6
 - Ferro-cube cored Scanning Coils and Line Output Trans., 10-15 kv., EY51 winding Line Trans. with width and linearity controls, circuit dia., pair... 50/-
 - Frame Output Transformer Focus or line block osc. Transformer..... 4/6
 - Focus Magnets Ferro-core P.M. Focus Magnets, iron Cored..... 19/6
 - Duomag Focalscers..... 22/6
 - 300 m/a Smoothing Chokes 10/6
- STANDARD 35 mm.**
- Line Output Transformers 3.9 kv. E.H.T. and 6.3 v. winding, Ferro-cube..... 17/6
 - Scanning Coils, Low imp. line and frame..... 7/6
 - Frame or line blocking oscillator Transformer..... 4/6
 - Frame Output Transformer Focus Magnets : Without Vernier..... 12/6 With Vernier..... 17/6
 - 200 m/a Smoothing Chokes 7/6

RECORD VALUE! 12-channel TURRET TUNER

Complete with PCC84 and PCF80 valves, I.F. 33-38 Mcs. Complete with coils for five Band I channels and channels 8, 9, 10. Band III. New and unused.

TO-DAY'S VALUE OVER £7.

LASKY'S PRICE 39/6
Post 3/6

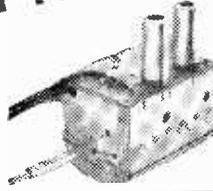

SEND FOR OUR NEW COMPONENTS CATALOGUE

OVER 100 PAGES, SIZE 8 x 5 1/2 in., COPIOUSLY ILLUSTRATED

Never before has such a comprehensive and useful components catalogue been made available to the home constructor, and our prices will save you pounds! Price 2/- post 6d.

Our latest 12 page BARGAIN BULLETIN free with every copy. Also available separately by post, price 6d.

20,000 VALVES in stock including new and manufacturers' surplus, also imported Valves. Send for our new list and save money. Large stocks of TRANSISTORS.

LASKY'S (HARROW ROAD) LTD.

Open All Day Saturday, Early Closing, Thurs. Mail Orders to Dept. P.T., Edgware Road, 42, TOTENHAM COURT ROAD, W.1. 207, EDGWARE ROAD, LONDON, W.2. Telephone: MUSeum 2805. PADDINGTON 3271/2.



C.R. TUBES NEW, UNUSED & GUARANTEED

16in. Metal Cone, famous make. Type T901/B. 6 volt, .3 amp. heater, ion trap, 12-14 kv., E.H.T., wide angle, standard 35 mm. neck. LIST £16.

LASKY'S PRICE £6.9.6.
Carr. & Insur. 21/-.

Masks, Anti-Corona, Bases and Ion Traps available.

FERRANTI 9in., T9/3. 4 v. heater, triode, octal base, standard deflection. LIST £3.

LASKY'S PRICE 50/-

FERRANTI 12in., T12/44 and T12/54. LIST £12.

LASKY'S PRICE 84/-
Carr. & Insur. 12/6.

FERRANTI 17in. type TR17/10. 6.3 v., .3 amp. heater.

LASKY'S PRICE £7.19.6
Carr. & Insur. 12/6.

RE-GUNNED C.R. TUBES

- 14 in. £6.10.0 ... Carr. 12/6
- 17 in. £6.19.6 ... Carr. 21/-
- 21 in. £7.19.6 ... Carr. 25/-

VALVES

SAVE DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, and 4 for 23/6
DAF98, DF98, DK98, DL98 4 for 30/-
8K7G, 6R8G, 6Q7G, 6V6G, 6X5G, or 5Y3G 5 for 27/-

1A7GT 12-	6L1 15-	2524G 9-	EBC41 8/6	EY86 8/3	PZ30 17-
1D5 9/6	6L18 12/3	2526GT 9/6	EBF89 8/9	EZ40 6/9	SP81 3/6
1HG5T 10-	6Q7G 7/8	30C1 8-	ECL21 20/6	EZ41 7/6	T41 15/6
1NG5T 10-	6Q7G 7/8	30L1 8-	EBL21 20/6	EZ80 6/3	U25 12-
1R5 6/9	6Q7GT 9/6	35L6GT 10-	EC92 11/-	EZ81 7-	U26 12-
1S4 9/-	6SL7GT 6/3	3524GT 8-	ECC81 5/9	FW4 500 8-	U50 7/6
1S5 6/3	85N7GT 4/9	3525GT 8/6	ECC82 6/9	GZ32 9-	U78 6/-
1T4 5/3	6U4GT 11-	43 12/6	ECC83 7-	KT33C 9-	U78 6/-
1U5 6/6	6V6G 5-	50CD6G 26/9	ECC84 8/9	KT41 14/6	UABC80 7/9
3A5 10/6	6V6GT 6/6	50L6GT 8-	ECC85 8/3	KT61 10-	UAF42 9/6
3Q4 8/6	6X4 5-	AZ31 9/6	ECP80 10-	KT63 6/6	UBC41 7/9
3V4 6/9	6X5GT 5/6	B36 9/6	ECP82 10-	KT71 8/6	UBF89 9/6
5U4 5/3	7C5 8/-	CL33 13-	ECL81 20/6	M43 6-	UBF89 8/6
5U4G 9/6	7C6 8/-	DAC32 10-	ECH35 6/9	MU14 8/-	UBL21 20/6
5Y3GT 6/9	7HT 8/-	DAF91 6/3	ECH42 8/9	MX40 12/6	UCC84 12/9
5Z4G 9/6	7S7 9/9	DAF96 8/3	ECH81 8/6	N18 8/6	UCC85 8/-
6AL5 3/9	7Y4 10/-	DCC90 10/6	ECL80 8/6	PCC84 9-	UCF80 14/-
6AM5 3/9	10C1 14/6	DF33 10/-	ECL82 10/-	PCO88 14/-	UCH21 20/6
6AM6 3/6	10C2 17/8	DF91 5/3	EP39 4/6	PCF80 8/-	UCH42 9/-
6AQ5 7-	10F1 15/6	DF96 8/3	EF41 8/9	PCF82 9/3	UCH81 8/6
6AT6 7/3	12A8H 10/6	DH76 6/6	EF42 11/6	PCL82 9/3	UCL82 11/6
6BA6 6/6	12AT7 5/9	DH77 7/3	EF80 6/6	PCL83 11/9	UCL83 13/-
6BE6 6-	12AU6 7/6	DK32 12-	EP38 6/9	PCL84 8-	UF41 8/9
6BH6 6/9	12AU7 6/6	DK40 14-	EP86 10/6	PEN44 11/-	UF42 8/6
6BJ6 6-	12AX7 7-	DK91 6/9	EP89 3/6	PEN36C 9/6	UF89 7/6
6BR7 10/6	12BA6 8/-	DK92 8/6	EP91 3/6	PEN45 8-	UL41 8/-
6BW6 10-	12BT6 5/9	DK96 8/6	EP92 4/6	PEN46 8-	UL42 8/-
6C8G 26/9	12K8GT 11/8	DL33 9/-	EP95 6/9	PL36 13-	UR1C 8/-
6F1 14/8	12Q7GT 5/6	DL35 10/6	EL38 21/6	PL38 14/6	UY21 14/-
6F8G 6/6	14S7 16/9	DL92 6/9	EL41 9-	PL81 10/-	UY41 6/6
6F14 12/6	18AQ5 7-	DL94 7/6	EL42 10/6	PL82 7/6	UY85 6/6
6F14 17/6	20F2 17/6	DL96 8/6	EL84 7-	PL83 13/6	Y4B 9/6
6K7G 3/9	20L1 17/6	EABC80 7-	EM34 8/6	PY32 12/-	YP41 6/-
6K7GT 6-	25A6G 11-	EAC91 5/-	EM80 9/-	PY80 7/6	W76 6/6
6K8G 6/9	25L6GT 9/-	EAF42 8/6	EM81 9/-	PY81 6/9	W77 4/6
		EB91 3/9	EM84 10/-	PY82 7/-	X76M 11/6
		EBC33 5/-	EY51 9/-	PY83 8/-	Z77 3/6

READERS RADIO

24, COLBERG PLACE, STAMFORD HILL, LONDON, N.16. STA. 4587

INRAXIA LTD.

The Name for High Grade REBUILT TUBES

ALL TYPES OF 12" to 17" only £7/15/0

CARRIAGE FREE

£1 allowed for old Tube

12 MONTHS' GUARANTEE

INRAXIA LTD., 65/66 Coleshill Street, BIRMINGHAM, 4.

'Phone : ASTON CROSS 4815

A 3d. stamp will bring you a copy of our latest

RADIO & TELEVISION COMPONENT Catalogue
JAMES H. MARTIN & CO.
FINSTHWAITE, NEWBY BRIDGE, ULVERSTON, LANCs

Post 6d. per valve extra.
Any Parcel Insured Against Damage in Transit 6d. extra.
Any C.O.D. Parcel 2/6 extra.

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

SPECIAL NOTE: Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

HUM BARS

SIR.—During some time base experiments I was continually coming across a fault which showed itself in the form of a series of solid horizontal bars travelling upwards slowly. At first I thought this was some fault in the circuit, but after modifying various components I found that the bars were present even when I had the tube and timebases disconnected from the sync separator. Is there any proof that such a defect could be caused by hum from the timebase H.T. line? I have previously experienced 50c/s and also 100c/s hum bars, but they have always remained locked by the 50c/s frame timebase, whereas my picture remained stationary, but the bars travelled quite slowly from top to bottom.—R. E. BADDELY (Worthing).

TUNER ALIGNMENT

SIR.—I recently fitted a turret tuner to my set and whilst I can receive both Channel 1 and Channel 9 satisfactorily, I find that on Channel 9 there is a noisy background when the picture is properly tuned. Thinking this might be due to wrong alignment of the oscillator circuits in the tuner, I retrimmed them slightly, but now find that on the BBC, for instance, when a very light scene is projected there is quite a noisy background. On dark scenes, everything is perfect. The video and sound channels have been aligned with a signal generator. Is there any possibility that some form of modulation is taking place between the set and the timebases, or is it just mis-alignment of the tuner? Perhaps some reader has experienced a similar trouble and would be willing to pass on hints as to the cure.—G. TRIMBLE (Gt. Yarmouth).

A USEFUL HINT

SIR.—I have experimented for a long time with TV circuits and layouts and have found it extremely difficult to remove and replace components on the standard metal chassis. I have therefore made up a 'plug-in' chassis, using for the sides standard sheet aluminium, with a half-inch turnover at the upper edge, to which I bolt ordinary perforated zinc sheet. I find that I can attach leads to certain components, slip over a piece of insulated sleeving and then pass the lead through a hole, and when the lead is bent to go to the next item it automatically holds the component in position. Where a component which has fixing

holes is used, the bolts are passed through the perforated sheet. This makes for speedy assembly and very rapid dismantling and I am sure will save constructors and experimenters many hours of 'wasteful' work. The sheet can be used over and over again.—A. LINSTROM (N.W.5).

TV AND THE EYES

SIR.—In your November issue you published a letter from a reader commenting on the harmful effect of TV on the eyes. I was very interested to see in the daily Press very recently a comment by some doctors on the TV position and it was there stated that there are many other ill effects caused as a result of prolonged viewing. One of these was a reliable report that a fit had been induced in one patient as a result of the flicker present in every receiver. Is it not possible that other effects may be experienced by a viewer, not necessarily at the time but over a long period? I have heard that one doctor has blamed TV for acute indigestion and resultant sleeplessness.—N. MANSELL (Westminster).

COLOUR TV

SIR.—We do not seem to be progressing much in the way of commercial colour TV. Some time ago there were some coloured sheets on the market which one placed in front of the tube to give the effect of sky, sea, etc., but these were not popular. I would think there is a market for a similar type of colour device consisting of numerous coloured miniature bulbs surrounding the picture tube (hidden in a semi-transparent mask for instance) which could be operated by the viewer or mechanically. By a blue flood at the top of the screen, for instance, one could certainly give added effect to an outdoor view, whilst an overall green effect would be wonderful for the under-sea shots produced by Hans and Lotte Haas. Do readers think the idea is worth proceeding with and would there be a market for such a device?—G. HUMBERSTONE (N.W.).

[We feel that such a device would be popular only with experimenters; most viewers have enough controls to adjust already!—Ed]

110 DEG. SCANNING


SIR.—I am very interested in the latest 110 deg. tubes and I wonder whether any readers have successfully modified an existing scanning coil unit so that it may be used with these wide angle tubes. It does not appear that such a modification would be impossible, but I do not want to start modifying my spare coil until I am certain as to just what is needed. Perhaps someone can help me?—F. LUCAS (Birmingham).

Trade News

NEW PRODUCTS AND DEVELOPMENTS


The "Skantest"

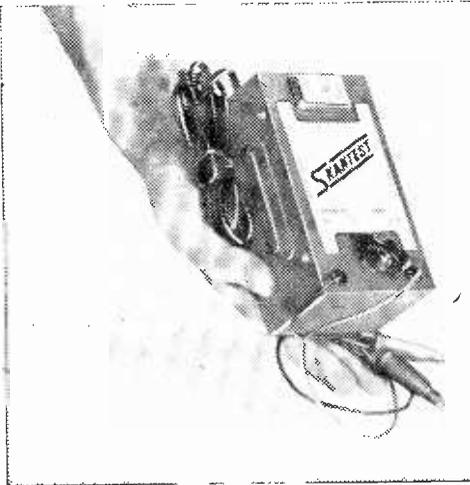IT is well known that, with the exception of intermittent faults, one of the most time wasting and difficult faults to diagnose with certainty is that of a single shorting turn in a time-base winding. "Skantest" is a new device for



The Skantest

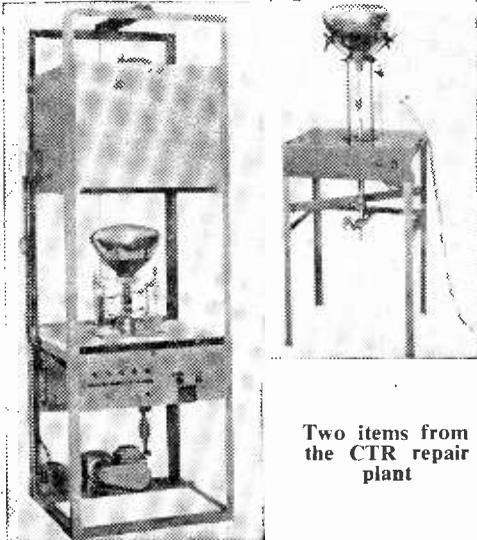
detecting shorted turns and is very similar in principle to most other instruments of this type, in so far as it employs an oscillating circuit, the valve of which is being fed by alternating current,



Two items from the CRT repair plant

so that the oscillations are, in fact, pulsed and a very peaky output is obtained. Across this oscillatory circuit is placed the inductance under test. In the case of the winding under test having one or more short circuited turns, there is a heavy damping effect, and the very low current neon indicating device ceases to glow.

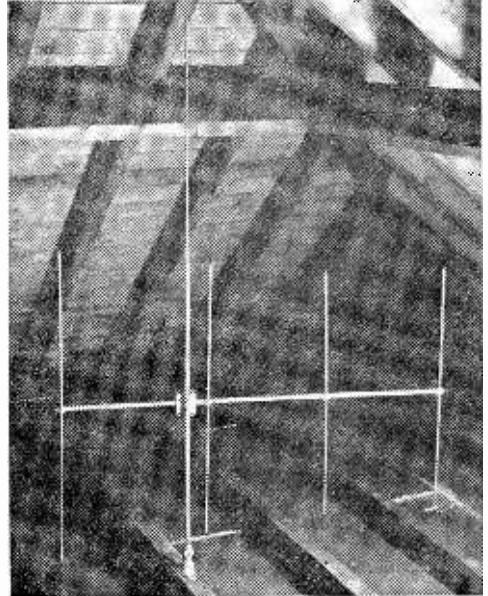The "Skantest" is available from *Direct TV Replacements, 158 Lewisham Way, London, S.E.14.*



The Loft Ranger

CRT Repair Plant

A complete set of equipment required for CRT repairs is now available for less than £600 and should be of interest to the smaller dealer. The N.E.V. 400 Range Plant includes all the necessary equipment for repairing cathode ray tubes. The basic plant will produce 25 tubes per week, but is an economical proposition if only one half of this quantity is required.


The plant is manufactured by *The Notting-Electronic Valve Co. Ltd., Kenrick Street, Netherfield, Nottingham.*

The "Loft Ranger"

THE Loft Ranger is a combined Band I/III high gain loft aerial, with a rigid locking multiplane ball joint of new design. All elements have a turn and lock assembly. High efficiency is claimed on Band III and it only requires a single feeder. It is extremely light in weight and easy to install. The Loft Ranger is priced at 30s. 0d., and is marketed by *Wolsey Electronics Ltd., Cray Avenue, St. Mary Cray, Orpington, Kent.*

Radio Stethoscope

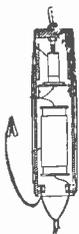This can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator. The stethoscope is a complete fault-finder. All the necessary parts to make this tracer 6/6, post 1/-.



Tester & Reactivator

We can supply all the main components for making this unit which will not only test Cathode Ray Tubes but also will reactivate them, supplied complete with full instructions. Price £3, plus 2/6 post and ins.

TV Service Sheets

200 sheets covering most popular post-war televisions by leading makers—Cossor, Ekco, Ferguson, Pye, etc. £2, Post free. PREVIOUS PURCHASERS OF THESE SHEETS PLEASE NOTE: WE CAN SUPPLY SHEETS Nos. 100-200, £1, or 150-200, 10/-.

TV Masks



Latest type grey crystallate. 14in., 10/-; 17in., 12/- Plus 1/- post.

Morganite Potentiometers

Single and 2-gang types available, standard size with length spindle, all new and boxed. Single types, 1/- each. Valves available: 5K, 10K, 25K, 50K, 100K, 250K, 1 meg., 2 meg. Gang type 3/- each—valves available: 5K+5K, 100K+100K, 1 meg., + 1 meg., 2 meg., +2 meg.

Avo Prodclips

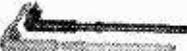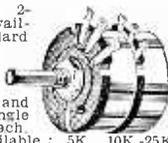The advantage of these testprods is that by pressing the trigger at the side they become crocodile clips and can be left in circuit. This is a great time saver when servicing. Price 15/- pair.



Fluorescents

All complete with polyester filled choke and interference suppressors, starters, and fluorescent tube—all ready, in fact, to switch on.

5ft 80 watt, 54/9 plus 5/6 carriage and insurance.
4ft 40 watt, 39/6 plus 5/6 carriage and insurance.
3ft 40 watt, 39/6 plus 4/6 carriage and insurance.
2ft 20 watt, 39/6 plus 4/6 carriage and insurance.
Circular 40 watt, 37/- plus 5/6 carriage and insurance.
Circular 80 watt, 104 6 plus 5/6 carriage and insurance.
These fittings are suitable for hanging or direct fixing—carriage and insurance applies for distances up to 250 miles, over and above this carriage will be extra.



This Month's Snip

Super Transistor Kit




Makes ideal bedroom radio, uses one transistor and one crystal diode.

Complete with case 19/8 Post 2/6.


Component Storage Drawers

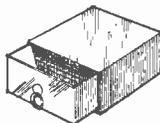Stout board construction these drawers are ideal for small parts. Supplied complete with simple erection instructions—1 6 each or 12 drawers each 6 x 2 1/2 x 6 1/2in., 13/6, post 2/-.




INFRA RED HEATERS

These latest type heaters are ideal for bathroom, kitchen, bedroom, etc. They are simple to make from our easy to follow instructions—uses silica enclosed elements designed for the correct infra-red wavelength (3 microns). Price for 750 watt and instructions, 15/6, plus 2/6 post and insurance. Or made up heater 52 6 plus 3/6 post and insurance—fully tested and guaranteed.

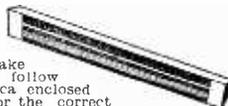

Our 68-page Hi-Fi Catalogue is now being sent out to customers—gives details of the latest and best Hi-Fi equipment with over 400 illustrations. Price 2/6 per copy which is refundable from purchases.

FOUR ITEMS FOR PRICE OF ONE

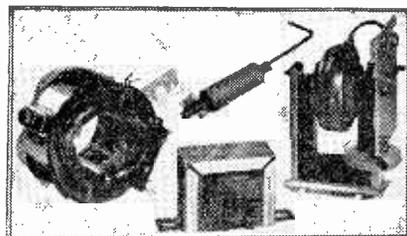

Set of modern T.V. parts, suitable for modernising old television or for a new one. For wide angle 14in. or 17in. tubes comprises: (1) Line output E.H.T. transformer. (2) 700 scanning coils on ferrite yokes. (3) Width control with ferrite core. (4) Frame output transformer. (5) Circuit diagram of a modern television. Offered at the price of the Line output transformer only, namely, 57/6, plus 2/6 post and insurance.

ELECTRONIC PRECISION EQUIPMENT LTD.

66, GROVE ROAD, EASTBOURNE, SUSSEX


Band III Converters

Suitable Wales, London, Midlands North Scotland, etc. All the parts including two EF80



valves, coils, fine tuner, contrast control, condensers and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and insurance. Data free with parts or available separately, 1/6. Please send two more kits, the one you sent last week is performing magnificently. We receive this sort of letter every day of the week, so if you have hesitated because you thought our kits too cheap you need hesitate no longer.

Building A Scope?

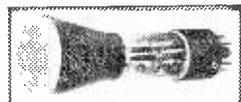

3in. oscilloscope tube. American-made type No. 3FP7, octal base 6.3 v. 5 amp. heater, electrostatic deflection, brand new and guaranteed, with circuit diagram of scope. 15/- each, plus 1/6 post and ins.

A.C./D.C. Multimeter Kit

Ranges: D.C. volts, 0-5, 0-50, 0-100, 0-500, 0-1,000. A.C. volts 0-5, 0-50, 0-100, 0-500, 0-1,000. D.C. millamps 0-5 0-100, 0-500. Ohms 0-50,000, with internal batteries. 0-500,000 with external batteries. Measures A.C./D.C. volts, D.C. current and ohms. All the essential parts including metal case, 2in. moving coil metre, selected resistors, wire for shunts, range selector, switches, calibrated scale and full instructions, price 19/6, plus 2/6 post and insurance.



Yaxley Switches

1 Pole 3 way	...	1/6
1 Pole 5 way	...	2/6
1 Pole 11 way	...	2/6
2 Pole 2 way ceramic	...	2/6
2 Pole 4 way	...	2/-
2 Pole 6 way	...	2/6
2 Pole 8 way	...	3/6
2 Pole 11 way	...	3/6
2 Pole 12 way	...	4/6
3 Pole 3 way	...	1/6
3 Pole 6 way	...	3/6
4 Pole 4 way	...	3/-
6 Position shorting	...	2/-
6 Pole 3 way	...	3/6
6 Pole 3 way ceramic	...	3/6
8 Pole 2 way	...	2/-
9 Pole 3 way	...	2/6
12 Pole 2 way	...	2/-

Miniature Microphone

American made, Dynamic type, real bargain at 2/6, plus 6d. post.



This is the correct address for post orders and for prompt attention please mark your envelope Dept. 5, also enough for postage. Personal shoppers should use one of the companies below.

Electronics (Crowdon) Ltd. 266, London Road, Crowdon. Phone: CRO 6558. Half day Wednesday.	Electronics (Finsbury Park) Ltd. 29, Stroud Green Rd., Finsbury Park, N.4. Phone: ARChway 1049. Half day Thursday.	Electronics (Manor Park) Ltd. 520, High St. North, Manor Park, E.12. Phone: ILFORD 1011. Half day Thursday.	Electronics (Ruislip) Ltd. 42-46, Windmill Hill, Ruislip, Middx. Phone: RUISLIP 5780. Half day Wednesday.
--------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------

R.S.C. (BRADFORD, LEEDS) (Leeds) Ltd. (and MANCHESTER)

Post Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/9 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 6 p.m. Wednesdays until 1 p.m. S.A.E. with enquiries, please. Trade supplied.

R.S.C. TRANSFORMERS

Fully Guaranteed

Interleaved and Impregnated

Primaries 200-230-250 v 50 c/s screened

TOP SHROUDED DROP THROUGH

280-0-280 v 70 ma, 6.3 v 2 a, 5 v 2 a ... 17/9

350-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a ... 18/9

280-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9

350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 23/9

350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 29/9

FULLY SHROUDED UPRIGHT

250-0-250 v 80 ma, 6.3 v 2 a, 5 v 2 a

Midret type 21-3-3 in. ... 17/9

250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 25/9

300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 27/9

350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a ... 27/9

350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a ... 35/9

425-0-425 v 200 ma, 6.3 v 4 a, C.T. 5 v 3 a ... 49/9

FILAMENT TRANSFORMERS

All with 200-250 v 60 c/s Primaries: 6.3 v

1.5 a, 5/9; 6.3 v 2 a, 7/6; 0-4-8.3 v 2 a, 7/9;

12 v 1 a, 7/11; 6.3 v 3 a, 8/11; 6.3 v 6 a, 17/9.

CHARGER TRANSFORMERS

200-250 v 0-9-15 v 1 a, 11/9; 0-9-15 v 3 a, 16/9

0-9-15 v 5 a, 19/9; 0-9-15 v 6 a, 23/9.

OUTPUT TRANSFORMERS

Standard Pentode 5,000 to 3 ohms ... 3/9

Small Pentode 5,000 to 3 ohms ... 5/9

Standard Pentode 7,500 to 3 ohms ... 5/9

Push-Pull EL84 to 3 or 10 ohms ... 18/9

Push-Pull 10-12 watts 6V6 to 3 or 15 ohms ... 18/9

Push-Pull 10-12 watts 6V6 to 3.5, 5, 8 or 15 ohms ... 19/9

SMOOTHING CHOKES

100 ma 10 h 250 ohms ... 8/9

80 ma 10 h 350 ohms ... 5/6

60 ma 10 h 400 ohms ... 4/11

SELENIUM METAL RECTIFIERS

Special quotes for quantities of 50 to 5,000.

H.T. (H.W.) F.W. (Bridge)

250 v 50 ma ... 3/11 612 v 1 a ... 6/11

250 v 100 ma ... 5/11 612 v 2 a ... 9/9

Contact Cooled 612 v 4 a ... 12/3

250 v 90 ma ... 8/11 612 v 6 a ... 14/8

250 v 75 ma 612 v 6 a ... 15/6

F.W. (Bridge) 8/11 612 v 10 a ... 25/9

612 v 15 a ... 27/9

CO-AXIAL CABLE 1in.

75 ohms 14/36 ... 8d. yd.

Twin-screened Feeder ... 11d. yd.

ACCUMULATORS, 2 v 18 A.H. New

ex-Gov., 5/6 ea.; 3 for 15/.

BATTERY SET CONVERTER KIT

All parts for converting any normal type

of Battery Receiver to A.C. mains 200-250v

50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma,

fully smoothed and fully smoothed L.T.

of 2 v at 0.4 to 1 a. Price including cir-

cuit, 49/9. Or ready for use, 9/9 extra.

ALL DRY RECEIVER BATTERY

ELIMINATOR KIT—All parts for the

construction of a unit (metal-case

51-44-2in.) to supply Battery Portable

receivers requiring 90 v and 1.5 v. Fully

smoothed. From 200-250 v 50 c/s mains.

Price, inc. point-to-point wiring dia-

grams, 39/9 Or ready for use, 46/9.

D.C. SUPPLY KIT—Suitable for Electric

Trains. Consists of mains trans.

200-250 v 50 c.p.s. A.C. 13 v 1 a Selenium

T.V. Bridge Rectifier, 2 Fuseholders, 2

Fuses, Change Direction Switch, Variable

Speed Regulator. Partially 33/9

drilled Steel Case, and Circuit.

TELEVISION RECTIFIERS

250 v 200 ma. Size 3 x 1 1/2 in. Brand

New, 6/9.

54-56 MORLEY ST. (Nr. Alhambra) BRADFORD.
5/7 COUNTY ARCADE, BRIGGATE, LEEDS, 1.
8/10 BROWN St. (Market St.), MANCHESTER.
Mail orders to
Dept. N., 29-31 Moorfield Rd., Leeds, 12.

EX-GOVT. MAINS TRANSFORMERS

All 200-250 v 50 c/s input.

Removed from New ex-Govt. units. 22/9

275-0-275 v 100 ma, 6.3 v 7 a, 5 v 3 a ... 11/9

300-0-300 v 80 ma, 6.3 v 2 a ... 11/9

285-0-285 v 150 ma, 6.3 v 11 a, 5 v 8 a, 5 v

3 a ... 29/11

350-0-350 v 100 ma, 6.3 v 2 a, 5 v 2 a ... 18/9

0-24-26-28 v 15 a A.C. (marked with D.C.

rating after rectification). 69/6, carr. 15/-.

AUTO 0-110/120-220/240 v, 50 watts ... 8/11

EX-GOVT. SMOOTHING CHOKES—

80 ma 5-10 h 250 ohms ... 2/11

80 ma 10 h 150 ohms ... 6/9

100 ma 5 h 100 ohms Tropicalised ... 9/11

100 ma 8-10 h 100 ohms Parmeko ... 6/9

120 ma 12 h 100 ohms ... 8/9

150 ma 10 h 150 ohms ... 8/9

200 ma 3-5 h 100 ohms Parmeko ... 7/9

0-10-25 v 24 a, 79/6, carr. 15/-.

EX-GOVT. CASTS. Well ventilated,

black crackle finished, undrilled cover.

Size 14 x 10 x 9 1/2 in. high. IDEAL FOR

BATTERY CHARGER OR INSTRUMENT

CASE, OR COVER COULD BE USED FOR

AMPLIFIER. Only 9/9, plus 2/9 postage.

BATTERY CHARGERS

For 200/250 v 60 c/s A.C.

mains. 12 months guarantee. Attractive, well

ventilated hammer finished cases, 6 v or 12 v

4 amp, with meter and variable charge

rate selector, as illustrated 69/9

carr. 5/-.

Or Deposit 13/3 and 5

monthly payments of 13/3. 6 v or 12 v 1 amp

type. Also suitable for

electric train power supply. Only 29/9

post 2/9.



RST

MAIL ORDER DEPARTMENT
211 Streatham Road, Mitcham, Surrey
ALL VALUES LISTED ARE NEW STOCK
• Terms C.I.V.O. or C.O.D. Postage 3d. per valve.
MITCHAM 390L.

AZ31 10/6	EF92 5/-	PCF82	UY85 7/6	6K80 7/6
B65 8/8	HL42 10/-	11/6	YV43 17/6	6K8GT
DAF91 7/6	HL84 7/-	PCL82	W81M 6/9	6L1 12/6
DAF95 9/8	HL90 8/6	11/6	W142 9/-	6L1 15/6
DF91 5/-	EM80 10/-	PCL83	W719 7/6	6L8G 7/6
DH719 7/6	EM81 10/-	12/-	W727 7/6	6L18 12/6
DK91 9/-	EV91 10/6	PENA4	X78 21/-	6L19 21/-
EABC80	EV94 10/6	X79 17/6	221 12/6	6N7GT
7/6	EY88 9/8	PEN4VA	221 12/6	6N7GT
EAF42 10/6	EY91 9/-	17/8	Z77 5/-	68L7GT
EB61 5/-	EZ35 7/6	PL38 15/-	Z152 7/6	68L7GT
EBC41 9/6	EZ40 7/6	PL61 14/9	Z191 7/6	68N7GT
EBF80 9/6	EZ41 7/6	PL82 8/-	1R3 1/3	6V6G 5/6
EBF89 9/6	EZ60 7/6	PL83 10/6	5U4G 7/6	8X5GT 5/6
EC91 9/8	EZ21 7/8	PY80 8/8	5V4G 9/6	7S7 10/6
ECC33 8/-	FC2 21/-	PY81 7/6	5X5GT 5/6	7Y4 7/6
ECC81 8/-	FC4 17/6	PY84 9/-	5Y3GT 9/6	8D3 5/6
ECC83 9/6	FC13 17/6	PY83 8/6	5Z4G 10/6	10L11
ECC84 9/6	FC13C 21/-	R10 21/-	6A8GT	10L11
ECC85 9/6	QZ32 11/6	R19 19/6	6A15 8/-	12A8H 15/-
ECF80	H39 5/6	TD4 17/8	6AN6 8/6	12A7G 9/-
12/6	H83 9/6	TP22 17/6	6AN5 7/6	12A7 8/-
ECF82	HB90 9/8	U142 8/-	6AN5 7/6	12A7 8/-
12/8	HL92 6/3	U147 7/-	4A05 8/3	12A7 9/-
ECH35 9/-	HL133D	U153 9/-	6BA5 7/6	12A7 9/6
ECH42 10/-	KT33C 10/-	UABC80	6BE6 7/8	12BA6 9/-
ECH81 9/-	KT86 10/-	UAF42 9/8	6BE7 7/6	12BE6 9/6
ECL80	LZ319 12/6	UBC41 9/6	6BR7 15/-	12BH7 15/-
9/-	MK74(5)	UBW3 8/6	6BW3 8/6	12J7G/GT
ECL82	(Gr 7)	UBF80 9/8	6BW7 6/6	12K7GT
13/8	ML4 15/-	UCH42	6BX6 7/8	12K8GT
EP37A 8/8	MSP4 17/6	UCH81 9/-	6C15 5/-	12K8GT
EP40 15/-	MU14 9/-	UCL83	6F12 15/6	12Q7 8/6
EP41 9/3	MX40 17/8	23/8	6F13 17/6	12Q7GT
EP42 10/6	N142 9/8	UF41 9/-	6J5G 4/6	35Z4GT
EP50(A) 4/8	N153 11/6	UF89 8/6	6K7 4/6	50L6GT
EP80 7/-	PCP34 9/6	UL41 9/8	6K7G 4/-	813 50/-
EP85 7/-	PCP90	UY41 7/8	6KGT	
EP86 11/-				
EP89 10/-				
EP91 5/-				

SEND FOR LISTS. Quotations given for any types not listed. Obsolete and old types a speciality.

TV TUBES

BRAND NEW GUN
RESCREENED, REALUMINISED
ALL SIZES, ALL TYPES

Brimar, Emscope etc. 8/6 with
order, bal. 8/6 for 19 weeks;
or £7.10.0. cash

FREE CARRIAGE AND INSURANCE
21", 24" — £1.5.0. Extra

EXPRESS ELECTRONICS
281 Parliamentary Road, GLASGOW

Bel 4569



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 327 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

FERGUSON 988T

My television set has developed the following fault. Superimposed on the left hand side of the picture there appear three dark grey vertical lines each about $\frac{1}{2}$ in. wide and the same distance apart. This does not alter by any adjustment of the contrast control. The tube is a rebuilt one, giving a very good picture in every other respect.—J. Taylor (Leitchworth, Herts).

We suggest that you check the $0.001\mu\text{F}$ capacitor wired from pin 2 of the CRT base socket. This is probably open circuited.

ENGLISH ELECTRIC T30365

The set is giving good sound and picture but when it has been on for a short while, the picture will fade out and sometimes comes back of its own accord. However, if it takes quite some time coming back, I turn the brightness control on the front of the set and the picture is all right for half an hour or more but then fades away again. Also, when the picture is OK, there are wide shadow lines moving up and down at the back of the picture. I have replaced the PL83 but this made no difference. The sound is perfect.—A. Harper (Pontypridd, Glam).

You should check tuner valves PCC84 and PCF80 and the base connections of the EF80 valves. Also check the tuner switch contacts. The tube could be at fault, but this is less likely. The shadow lines are due to the reception of interfering signals which the tuner is incapable of rejecting.

G.E.C. TV1746

The trouble is sound on vision on Band I and Band III. I have tried the oscillator trimmer, etc. Also the sound rejects on L22 but I cannot remove it. I have tried cutting down signal strength but no luck. There is no mid position between vision and sound; vision on sound in one position; sound on vision in the other.—T. Pearson (Salford 6).

You should first check the $16+32\mu\text{F}$ electrolytic capacitor which decouples the H.T. of the sound A.F. and output stages. If this is in order check by

shunting a good condenser (say $16\mu\text{F}$) across each tag to chassis in turn. Check the H.T. decoupling $0.001\mu\text{F}$ capacitor and the decoupling capacitors generally. We assume the beehive type rotary capacitors in the centre of the I.F. chassis have not been disturbed.

MARCONI V.C.152

I cannot stop the picture from rolling up or down and I lose about $\frac{1}{4}$ th of the picture at the bottom.—S. Stanway (Westcliffe-on-Sea).

Your letter indicates that the picture can be made to roll downward or upward with the hold control but cannot be locked. This indicates lack of sync pulses or at least weakened sync pulses. You should, therefore, suspect the interlace diode (small metal rectifiers associated with the LN152 (ECL80) from timebase valve), also the shunt 2.2M resistor. The LN152 should also be replaced as this may be causing the cramping at the bottom.

AMBASSADOR TV5

I have been trying to repair the above set. There was no audible line whistle and no EHT. The owner informed me that before the screen went blank there were multiple horizontal pictures on it. I checked V14, 20P1 by substitution with a known good valve and renewed R79 and C56, checked R76, 77, 78, 74 and R83, C53, C54 and C55, had V15 (U281) tested. I finally renewed the line output transformer without much improvement. I have checked for line sync pulse at V11 anode with signal tracer and can hear it quite clearly. I checked C51 by substitution. The heater in the EY51 does glow faintly. I can draw a small spark from cathode and one about $\frac{1}{2}$ in. long from anode. There is still no line whistle. EY51 heater glows the most with R79 set at minimum resistance. All there is on the screen is a round patch of light on the bottom half, extending just above half-way. The H.T. output from the metal rectifier is 250V.—G. V. Walker (Bilston, Staffs).

We are inclined to think that the installation of the U281 heater winding on the mains transformer has partially broken down. Is it possible for you to check this with a megger? R76 is 270ohms (not 270k or 27k). Try the effect of putting a 270ohm across the existing R76.

BUSH TV62

I am trying to locate a fault in the above set. The symptoms are: No raster—no H.T. boost. Sound normal. The line whistle can be heard. A $\frac{1}{2}$ in. arc can be drawn from EHT but is not very "fat". The tube is an AW36-21 and valves P181, ECC82, PY81, EY86, PY82 (2) have all been tested and found to be in order except that the rectifiers are down a little.—G. Kaye (Edgbaston, B'ham).

You do not say whether the EY86 lights up normally or not or whether the EHT was tested at the EY86 anode or the CRT cap. Also we are not sure what is meant by H.T. boost. In view of this we would advise you first to ensure the ion trap magnet is correctly aligned, that the EY86 does light up (if it does the boosted H.T. line must be in order). If it does not, remove the EHT clip from the CRT and note the effect. If the EY86 does not light up at all, check the 140pF width capacitor, the 3.3k resistor to pin 8 of the PL81 and the $1\mu\text{F}$ boost capacitor. Also check H.T. electrolytics.

ARGOSY 21K40

My set, which is 18 months old, has developed a fault. It is needing constant adjustment of the line hold control. This is very erratic sometimes needing constant adjustment of the line hold a dozen or more times during an evening and then it will hold good for several evenings with no bother. The picture is good otherwise. When it starts to slip, it only affects the top third of the picture at first and then after some seconds the whole picture. I have tried substituting valves, sync sep., interlace diode, removing EHT connection but with no better result. I wonder whether it may be some of smaller components associated with the valve V7B.—W. Barthwick (Liverpool 6).

The 21K40 differs in many respects from the 17K40. The line oscillator for example is an ECC82 and it is this valve which should be replaced. The associated components should be checked.

PHILIPS MODEL 1236U-15

There is no EHT on this set. The sound is good. I have had all the valves tested and they are all right. I have had the EHT transformer out and it appears OK for continuity in the windings. The EY51 does not light up, the filament has been tested and is intact.—S. Pilling (Derby).

You should not suspect the transformer at this stage. If the PY80 and PL81 valves are in order, check H.T. to pin 8 of the PL81 (assuming there is no line whistle at all). If there is no H.T. present check 6.8k resistor from H.T. to line blocking oscillator transformer and continuity of this winding. If there is a line whistle suspect EY51, EHT smoothing capacitor (on the side of transformer—disconnect top end) or tube (remove anode clip from tube).

MURPHY V150/8

I recently acquired the above set on the understanding that sound was working but no picture. When I first switched on there was good sound and a raster, but no picture. After about half an hour smoke came out of the back and the set completely cut out. I tried the set again the following morning—there was no smoke this time but sound and raster are still in order.—A. Anderson (Coventry).

Without some further details we cannot give a specific reply, but suggest you check for charred components around the base of the valves in the sound I.F. stage. Replace any resistors burned out and their decoupling condensers, and also check the valve concerned for inter-electrode shorts.

STELLA ST6417V

The above set, a 17in. model, has run almost trouble free for nearly five years, but as the tube was becoming "low" I decided to renew same. My dealer supplied the New Mullard Tube—MW/4369 instead of MW/43/64 as he said it is a later tube and a direct equivalent. Since fitting the tube the set suffers badly from a fault which it did not have before: defocusing on peak white. When the contrast control is only slightly on, it is a fair but watery picture. The slightest advance of the control makes peak white lettering, etc.,

blurred. As I assumed this was the tube, I notified the dealer and he was good enough to let me try a further new tube, but with identical results. I have an average knowledge of TV and have delved into all the accepted cures for this annoying fault but have had no success. Valves replaced include EY51, PL81, PY81, EF80.—A. H. Violet (Kidderminster, Worcs).

We are inclined to suspect the video amplifier anode circuit decoupling capacitor which may well be open circuited. The focus magnet may be defective but this is less likely.

CLEVELAND CONVERTER (A.C.29)

I am using a Band III converter tuned to Channel 9 London ITV. In December the new Dover transmitter opened up on Channel 10. Will this converter tune to this new channel? Low power transmissions were radiated for tests but I have been unable to pick up anything, not even sound. I know of a few people who picked them up. It appears also that reception is obtained with the aerial still in the direction of the London transmitter. Will I have to alter the coils for reception?—F. W. Angus (Canterbury).

You will have to unscrew the dust-iron cores slightly to receive Channel 10. However, the I.F. output coil which remains tuned to the existing Band I channel. There are therefore three adjustments to make, the aerial, R.F. and oscillator coil cover, the latter of course being the most important and most critical.

DEFIANT TR1453:T

I wish to fit a turret tuner in my set. Could you please advise a suitable tuner, also the I.F. of this set.—F. Hughes (Co. Durham).

The I.F.'s are: sound, 37.5Mc/s and vision, 34Mc/s. You would be well advised to contact your supplier regarding the best type of tuner for this model, as this model varies somewhat in different areas.

PYE B18T

About 20 seconds after switching on, I get a rasping sound from the speaker. This lasts for a couple of seconds and then the sound comes on; about ten seconds after this the picture comes on and is perfect. Sometimes I get a little cramping at the top right-hand corner, but this clears within a minute.—D. F. Jones (Sutton, Surrey).

The initial disturbance may be caused by instability resulting from an impaired valve, which tends to correct itself as it warms up. The cramping at the corner of the screen is caused by the formation of electro-static charges on the tube face, and is often the mark of a failing tube.

SOBELL T121

Recently I could only obtain a picture occupying about three-quarters of the screen, eventually no picture at all, with a white bar about $\frac{1}{4}$ in. wide, extending vertically down the centre of the screen. Would you let me know if the tube is finished, or would it be possible to use a boosting transformer?—R. J. Spencer (Belfast).

The fact that your picture has developed into a vertical line does not indicate that your CRT is at fault, it is more likely to be due to a faulty

(Continued on page 327)

Let I.C.S. train YOU!



COURSES ON:—

- **RADIO and TELEVISION**
- **SERVICING** **ELECTRONICS**

EXAMINATION COURSES FOR:—

- **C. & G. Radio Servicing Certificate** (R.T.E.B.)
- **C. & G. Radio Amateurs' Exam.** (Amateurs' Transmitting Licence)

British Institution of Radio Engrs., etc.


Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.

LEARN - AS - YOU - BUILD

Practical Radio Course

A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester.

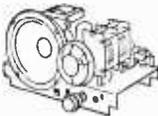
Other Learn-as-you-Build radio courses are available



5-VALVE SUPERHET RECEIVER



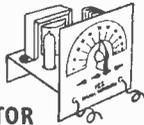MULTI-TESTER
(Sensitivity 1,000 ohms per volt)



RF/AF SIGNAL GENERATOR

Post this Coupon TODAY! for FREE book on careers in Radio, etc., and full details of I.C.S. Courses.

International Correspondence Schools
(Dept. 164B), Intertext House, Parkgate Road,
London, S.W.11.

Please send book on

Name and Address Age

Occupation..... 3.60

INTERNATIONAL CORRESPONDENCE SCHOOLS

GOVERNMENT SURPLUS AND MANUFACTURERS CLEARANCE

METERS. 500-0-500 Microamp. 3 1/2 in. dia. 37/8 ea. Dual Range 0-5 v. 0-100 v. FSD 1 m/a. 20/- ea. 50-0-50 Microamp. 2 1/2 in. 30/-
TV AERIALS. Combined BBC/ITV. 3 element 32/6, 5 element 37/8. ITV 3 element 22/6, 5 element 27/6.
CO-AX CABLE 6d. yd. AIR SPACED 9d. **DIPLEXERS** 12/-
GERMANIUM DIODES 1/-, 10/- doz. **TRANSISTORS** from 6/-
VOLUME CONTROLS. Long Spindle Midget. 10K-2 meg. Less Switch. 3/-, D.P. switch 4/6.
CONDENSERS. Twin Gang .0005 Standard 5/9. Midget 6/6. V.H.F. CHASSIS, contains over 50 components, 5/6 ea.
FERRITE ROD AERIALS M. and L. Wave. Mrs. Surplus 6/6 ea.
METAL BOXES. Well vent. D. backs, etc. 11" x 11" x 7" H. 8/6 ea.
SEL. RECS. 12 v. 1 amp. 5/-, 2 amp. 11/6. 1 amp. 15/-, 500 v. 1 amp. containing 30/35 mm. discs. 10/- ea.
ELECTROLYTICS. Canned. 20+20 mfd. 450 v., 2/6 ea. 25/- doz.
V.A.R. SLIDERS. 10 ohm 30 w. for chargers, trains. 3/- ea.
CONNECTING WIRE. P.V.C. 100 ft. 2/6. various colours.
RELAYS. Large stocks, assorted sizes, from 2/6 ea.
PICK-UP ARM with turn-over cartridge 19/6.
VENNER SILVER-ZINC ACCUMULATORS. H.105. New. 15/-

VALVES TESTED ON MULLARDS ELECTRONIC TESTER

1L4	5/-	6F1	7/6	8D2	4/8	EB41	7/6	PEN45	7/6
1T4	6/8	6F6	7/-	9D2	5/-	EB91	5/6	PEN46	7/-
1U4	6/-	6P13	7/6	10F1	7/8	ECH42	8/-	PL81	12/6
3A4	6/-	6J5	6/-	12A5	7/8	ECL80	9/-	PL83	5/-
5Z4	9/-	6J8	6/-	12AH8	8/-	EF36	5/-	SP41	4/-
4D1	4/-	6J7	6/-	12A17	6/-	EF37	5/6	SP61	4/-
6AG5	5/-	6K7	4/6	12A17	7/-	EF39	5/6	VR150/30	5/-
6AL5	5/-	6L8	6/6	12AX7	7/-	EF50	3/8	UL84	9/-
6AM6	9/-	6S7	4/6	12BH7	10/-	EF90	8/-	VCR97	15/-
6AQ5	7/-	6S7	5/-	12SK7	6/6	EF91	6/-	VCR138A	25/-
6AU6	6/-	6SK7	5/-	12SK7	7/-	EF92	7/-	VCR139A	25/-
6BA6	8/-	6SL7	6/-	15D2	6/-	EL32	5/-		
6BE6	6/6	6SN7	7/-	60C5	10/-	EL94	5/8		
6BH6	5/-	6U5	6/6	807	6/-	EY61	5/-		
6BW6	6/6	6V6	6/6	EA50	1/6	EY81	8/-		
6C4	5/-	6X1	7/-	EABC80		EY86	9/6		
6D2	8/-	6X5	7/-		8/-	F61	4/-		

SECONDHAND VALVES, YOUR CHOICE, £10.0 for EIGHT. ECL80, 6C4, 6AM6, 9A6, 6J6, EF50, 6BE6, 3A4, EF90, SP61, P61, 6J5, PY80, PY82, 277, 6AL5, 6K7, 6SL7, EL32, EF42, 6D2, 20P1, 6F13, SP41, EY61, EB91, EF91, EF39, PCL83, EF36, PEN45, PEN46.

ENQUIRIES—S.A.L. PLEASE

HUGGETT'S LIMITED

2-4 PAWSONS ROAD, WEST CROYDON

Now Vidio offer even better value with a new service.

C.R.T'S RE-SCREENED AND ALUMINISED

All types of tubes available, each fitted with new Gun Units and completely guaranteed for a year, and delivered anywhere in the United Kingdom—now. Standard C.R.T's still available at reduced prices.

For full details write direct to :

VIDIO REPLACEMENTS LIMITED

R.T.R.A. Approved.
Hales Street,
Deptford High Street
London, S.E.8.

or
Tel.: TIDeway 4506.



PL81 valve or the 600pF condenser which comes from the cathode of EY51 to the anode of the PY80.

C.R. TUBE BOOSTING

I wish to boost my C.T.R. The set is a Cossor 932 and the tube a Mullard MW31/74. — W. Smeson (Donnington, Salop).

We would make one point clear before dealing with your query, it is that the MW31/74 should not have excessive boost applied to its heater as this will almost certainly result in complete loss of emission. To moderately boost the heater, wire a 5k 10W resistor from the live fuse to pin 1 or 12 of the tube base socket, whichever causes the heater to glow more intensely.

KOLSTER-BRANDES FV40

There is no picture, though the sound is in order. Valve EY51 will only light up when the width plug is left out. Then I get only a line from top to bottom of the screen and this line is broken in two places. I can then draw about a 3/4 in. spark from the anode of EY51 with a screwdriver. I have a service sheet for this receiver. — H. Gass (Nottingham).

First check the 0.25µF capacitor wired from the boosted H.T. line to the 5V4 anodes. If this is in order, a short could be present in the line scanning coils or the line output transformer could have shorted turns.

BUSH TV24

The picture keeps on rolling downwards. When I do get it to lock the vertical hold control is fully anti-clockwise. I replaced the first ECL80 and the PZ30. It stayed all right for a week and then started rolling again and sometimes it is hours before I can get it to relock.—S. Brett (London E.17).

There are a number of resistors connected with the frame hold control. Check the 680k (blue-grey-yellow) feed resistor which has probably 'gone high'. If this restores the optimum position to approximately the centre but the sync is weak (no positive lock) check the WX6 interlace rectifier (small red and black rectifier).

SOBELL T347

My trouble is lack of brightness with the control fully turned up. On looking at the back of receiver I find voltage selector flange wrongly set at 230V, the voltage in this district being 240. This was set by the supplier 18 months ago. I would welcome instructions regarding removal of the chassis from the cabinet, together with methods of making condensers safe to handle. Could you tell me whether it is possible to replace the EY51 without removing chassis.—W. Hunter (Lydiat).

Lack of brilliance can be due to low EHT, in which case the EY51 could well be responsible. We also suggest you check the voltage on the grid of the CRT. It should read 0-110V, dependent upon the setting of the brilliance control. If, however, with control at maximum, the voltage is not about

75 volts, this could then suggest that your CRT is suffering from low emission. The fact that your mains voltage is 240V and the tapping is for 230V should not be detrimental in any way. To remove the chassis, remove mains plug—back and front control knobs, side escutcheon, inspection panel and speaker leads. Finally, remove the 4 chassis bolts and the chassis can then be withdrawn. Normally on switching off a receiver, the electrolytic condensers discharge through the circuit. Before touching EHT components they short circuit them to earth. It is possible to replace the EY51 without removing set from the cabinet. Remove screening can and lay the set on its side; the tags can then be soldered making good rounded joints.

REGENTONE "Big 12"

I cannot obtain sharp focus on this set. There seems to be no medium between white and black and at its best the focus is poor (for example, one cannot read small print on the screen). Also, after operating for about 30 minutes the picture suddenly becomes very bright although this can be adjusted by the brightness control. I have just renewed the EL38 and the EY51 and also the resistor R68. The metal rectifier which was 14A100 has been replaced by 14A86. Do you think this will be suitable for any length of time?—S. Berry (Chorley).

The voltage applied to a 14A86 should not exceed 250, and as a higher voltage is applied to the "Big 12" the life of the 14A86 may be curtailed. We advise you to check the video amplifier stage components, resistors, etc., adjust the focus magnet gantry for optimum focus and then suspect the tube itself.

FERGUSON 306T

At times, after the set has been switched on, sound goes dead and when the set is turned off for a few minutes and then turned on sound is restored, only to go dead after a period. If the set is not turned off, but volume fully advanced, sometimes sound is heard very faintly and occasionally I am taken unawares when the sound rectifies itself and comes out full volume only to break down again.—A. McLean (Co. Down).

This is, indeed, a difficult fault to solve without the abundant use of instruments. We would not consider valve trouble initially, check for instance, the A.F. coupling capacitor, the loudspeaker connections, the sound detector and circuit, and wires to the volume control. There is every likelihood that the A.F. section is to blame. A few simple checks should prove this for you.

QUERIES COUPON

This coupon is available until MARCH 22nd, 1960, and must accompany all Queries sent in accord with the notice on page 323.

PRACTICAL TELEVISION, MARCH 1960.

SETS & COMPONENTS

H.M.V. 151N., English Electric 151n., Ultra, etc., Televisions not working, originally £175 each, **£510/0**.
TOMLINS, 127, Brockley Rise, Forest Hill, S.E.23.

SALVAGED VALVES

All at 2/6 each

EF91	U31	10F1
DH77	6F1	B36
Z77	6F13	KT33C
EB91	6P25	EF50
	6P28	

Minimum Order £1. S.A.E. for List. All Valves Tested on Mullard High Speed Valve Tester, C.W.O. to—

ARION TELEVISION, 4 Maxted Rd., S.E.15

TURRET TUNERS, brand new, famous make, 12-channel, coils 1 to 5 and 8/9 fitted, 34/38 mc/s. complete with P.C.F. 80 and P.C.C. 84, circuit diagram included, **£117/6**, p. and p. 3/6; discounts for quantities; cash with order. **SOUTH SUPPLIES (ELECTRICAL) LTD.**, 95, Old Kent Rd., London, S.E.1.

INDICATORS, Type 277, with lin. C.R.T., 4/VR91, 2/VR92, 37/6 (p.p. 3/6). Type 101, with VCR530 (6in. blue, magnetic, octal base), and 2/EB91, 2/EF91, 2/R10; new cond. 30/- (post 3/6). Type 1, with VCRX269, 2/EF52, 5/536, 1/6V6, 1/EF51, 2/EB91, 3/EF91 with R.F. E.H.T. generator and 28 kc/s. xtal, 48/- (rail 7/6). Type 97 with VCR517, 10 valves, 30/-. Potentiometers, miniature wirewound, 6 ohms, 100 ohms, 600 ohms, 1k or 2k; each 1/0. Chokes, L.F. 10H 200mA, 8/6; Potted 10F 100mA, 7/6; "C" 5H 400mA, 10/6. Monitor, Type 56 (2 units Oscilloscope and power unit), **£8/10/-** (rail 20/-). List and enquiries: s.a.e. please. Terms, c.w.o. Postage extra. Immediate despatch. **W. A. BENSON (PT)**, 136, Rathbone Rd., Liverpool, 15.

FIX IT YOURSELF AERIALS! Pre-assembled ready for instant fitting. New season models. Loft 5EL, 30/-. Clip on 5EL, 30/-. 8EL, 42/6. Diapole + 5EL + Chimney for 75/-. **FRINGE AREA MODELS** for High gain. Band 1, 3EL array, 80/-. Band 3, Double 5 Array, 72/6. Double 8 Array, 100/-. Fringe area super low loss Coaxial, 1/3 yd. Standard low loss, 7td. yd. All items carriage paid. C.W.O. S.A.E. for aerial list, etc.

HASE SUPPLIES, 34 PRINCE STREET BRISTOL (Dept. P.T.)

TV TUBES, Factory rebuilt. Top quality with brand new gun assembly. 12 months guarantee. 12 inch. **£5/17/6**; 14", 15", 16", 17" inch. **£6/10/0**, carriage 12/6. **R. HAINSWORTH (Dept. C2)**, 31 Alredale College Mount, Undercliffe, Bradford 3, Yorks.

LONDON TELEVISION

OFFER THE FOLLOWING BARGAINS. RIGIDLY TESTED EQUIPMENT TELEVISION VALVES. Individually Boxed, 3/- to 7/6 each.

WIDE ANGLE SCANNING TELEVISION CHASSIS. Complete less valves. 30/- each. Most makes in stock.

TELEVISION COMPONENTS at Bargain prices. Please write for your individual requirements. Carriage extra.

The undermentioned Televisions for Personal Callers Only.

14in. TELEVISIONS. Working. **£4.0.0** to **£8.0.0**. 17in. TELEVISIONS. **£9.0.0** to **£14.0.0**. Trade enquiries invited.

4, HENDERSON RD., EASTNEY, PORTSMOUTH.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., Strand, London, W.C.2.

SETS & COMPONENTS (continued)

NEW TUBES

	2 Years' Guarantee	1 Year Guarantee
14 in. Type M.W. ...	£10.10.0	£8. 0.0
17 in. Type M.W. ...	£12. 0.0	£9. 0.0
17 in. Type C.R.M. ...	£13.10.0	£10.0.0
and Equivs. Carriage 5s.		

12 in. NEW 1 year Guarantee tubes ONLY **£5.19.6**

LINE OUTPUT TRANSFORMERS

Direct Replacements for 500 sets. Compare these prices (add 2s. 6d. post) :

Pye. LV30, 16T, CS17, etc. ...	50/-
18T, V4, etc., LV21, Luxury 17 ...	60/-
Cossor. 930, 931, 933, 934, etc. ...	60/-
Baird. T29, T163 ...	53/-
T164, T167, T172, 2014, 1712 ...	60/-
Ferguson. 990T to 997T; 103T to 145T, 203T to 246T ...	66/6
Ekco. TS46; TS113-114; T161, 164; T222, 231; TSC311, etc., etc. ...	55/-
Invicta. T108 to T110 ...	52/-
T101 to T104; T114 to T126; T133 to T142 ...	60/-
Bush. TV 11A, B; 12A, B; TVF 12A, TUG 12A, B; TRG12A, B ...	45/-
TV12AM; TV22, 24; TRG24, TUG24 ...	60/-

WESTWAY RADIO

5 Westward Way, Harrow, Middlesex.

RECLAIMED VALVES, tested and perfect. Huge stocks. Any type, price 5/-, plus 6d. postage each; delivery by return. **LEWIS**, 57, Chalford Walk, Woodford Green, Essex.

TELEVISION TUBES

NEW TV TUBES. TWELVE Months' Guarantee

12" MW 31-74 ...	£s. d.
14" MW 36-24 ...	7. 0.0
17" MW 43-64 ...	8. 0.0
17" MW 43-69 ...	8. 0.0
Carriage ...	10/-

FULLY Rebuilt TV Tubes TWELVE Months' Guarantee

12" MW 31-74 CRM 123 ...	£s. d.
14" MW 36-24 CRM 141 ...	5. 10.0
14" AW 36-21 CRM 142 ...	5. 10.0
17" MW 43-64 CRM 171 ...	6. 10.0
17" MW 43-69 CRM 172 ...	6. 10.0
17" MW 43-80 CRM 173 ...	6. 15.0
21" MW 53-20 CRM 211 ...	8. 15.0
21" MW 53-80 CRM 212 ...	8. 15.0
15" CRM 152 CRM 153 ...	6. 10.0
Carriage paid	

CATHODE RAY TUBE SERVICE

35 Broomwood Road, St. Paul's Cray, Orpington 21285 Battersea 6859

SETS & COMPONENTS (continued)

TELEVISIONS. 12in., 14in., 17in. and Profections. Require attention, from **£3**. In working order—12in. BBC from **£7**. 14in. BBC/ITA with regunned CRT from **£18**. 17in. from **£25**.

Send for Lists. Carriage Paid.

CADMAN'S

Service Department, Bryan St., Hanley, Stoke-on-Trent.

CALLING 9in. Television owners. Brand new, factory fresh, 9in. Ferranti Tubes, originally **£14/10/-**, will replace Mazda, Brimar, G.E.C., etc. **£4/10/-** each, 6 months' guarantee. **TOMLINS**, 127, Brockley Rise, Forest Hill, S.E.23.

VALVES from 1/8. All guaranteed. Radio T/V Components. Lists 3d. **HAMILTON RADIO (T)**, 237, Sedlescombe Rd. N., Hastings.

T/V SPARES

LARGEST RANGE OF NEW AND USED SPARES

Line Outputs our Speciality. Used from **£1**. New from 45/-. Also breaking hundreds of T/Vs for Spares. All Coils, Transformers, Chassis, Valves, etc. No Lists. Send S.A.E. and State Requirements for Immediate Quote.

VALVE KITS. A complete Kit for YOUNG set (one of each type) from 50/-. Quote Model Number for exact price.

T/V BARGAINS. Reconditioned All-channel Models at New Low Prices. 14inch from 22 gns., 17inch from 29 gns. Fully Guaranteed. Terms available.

T.C.S. LTD., 28, Brockley Cross, S.E.4 TIDeway 5394.

TV TUBES. Genuine re-gunned tubes with 6 months' guarantee; 14in. rectangular and 17in., **£6** each, carriage extra. **TV ELECTRIC & CYCLE CO.**, 1 High St., Chalvey, Slough (Tel.: 21860).

AERIAL "GEN" in the January issue. We have the "pukka" materials. Band III folded dipole, fitted insulator, 8/-; elements 1/8 each, post 1/6. Stacked array element kits, July issue, still available, 30/-. S.A.E. price list. **AERIAL SUPPLY**, 165 Beoley Road, Redditch, Worcs.

BAR PATTERN GENERATOR; Bands I and III; **£5** incl. p. and p. Box 21.

RENFREW ELECTRONICS ANDERSON DR., RENFREW REN 2642

YOUR GUARANTEE TO CHEAPER VIEWING

17" Mazda Tube with new American Gun-mount ...	£7.15.0
14" Mazda Tube with new American Gun-mount ...	£6.10.0
17" Mullard Tube with new American Gun-mount ...	£7.15.0
14" Mullard Tube with new American Gun-mount ...	£6.10.0

One Year's Guarantee. Cash with Order. 7s. 6d. allowed on old tube returned in carton supplied.

Dealers' Inquiries Invited. Less than 1 per cent. returns.


SETS & COMPONENTS (continued)

C. EDWARDS

1070 HARROW ROAD,
LONDON, N.W.10,
LADBROKE 1734

Offers
S/H TV in
First-class
Condition.

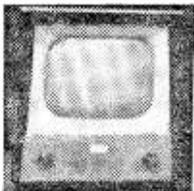12in. £5. 0/0.
14in. £7. 10/0.
17in. £15. 0/0.
(all 5 channel)
+ 15" carriage.
Guaranteed
tubes, all sizes,
12" 30/-, 14" £3.
17" £4.



in stock : **PYE, FERGUSON, EKO**
CASH ONLY. 15/- Carriage.
Trade Enquiries Welcome.

BRAND NEW TESTED VALVES in
Makers' printed cartons. EY85. ECL80.
8/-; N339. PL81. 9/6; PY32. R19. 10/6;
PL36. 20P1. 12/6. STEVENSON, 653
Maryhill Road, Glasgow.

AERIALS AT TRADE PRICES
For Example **DOUBLE FIVE ARRAY**
COSTS ONLY 60/-

Band III Self-contained Pre-Amplifiers
Only £3.15.0. Band III Converters 100/-
Turret Tuners. 94/-. Complete Rebuilt T.V.
Tubes from £5. Revacuumed ones, All Sizes,
£2.10.0. All Tubes are Guaranteed.
Super Low-loss Coaxial Cable. 1/1 yd.
Standard. 6d. v.d. Dilexers, 8/8 each.
S.A.E. FOR FULL LISTS.

G. A. STRANGE, Broadfield, North
Wraxall, Nr. Chippenham, Wilts.
Tel.: Marshfield 236.

SELLING UP. Must clear. 17 inch
TV's. Test Gear and S. Sheets. Chassis,
Cabinets, Components, Valves, Tuners,
etc. Your Price Bargains. A.
PHILLIPS, 8 Fettes House, N.W.8.
PRI 7085. Evenings, Sundays.

REBUILT TV TUBES

FULLY GUARANTEED 12 MONTHS

ALL MAKES — 12" to 21"

BLANE & MARTIN ELECTRONICS
SANDOWN LANE
LIVERPOOL

Details on request. Tel. SEF. 3428

SAVE ON REPAIRS.—100,000 salvaged
Radio and TV Spares. Valves, Tubes
for practically any set made since
1936. Prices from: LOT, 17/6; FOT,
7/8; osc. tr., 6/-; Sound, 2/6; Mains,
10/-; EHT Mains, 50/-; Def. Coils,
12/6; Speakers, 5/-. Tubes, Mullard,
Mazda, etc., 9-10in., 30/-; 12-14in.,
£2/19/6; 17in., £3/19/6. All picture
tested, fitted free or sent subject to
14 days' money-back guarantee;
Mullard 6 months' guarantee. Valves,
1,000 types from 1/6; EP91, EB91,
GJ5, 2/6; EF90, UF42, 10P1, 6F1,
6SN7, 3/6. We can save you pounds!
Send s.a.e. with enquiries or for complete
list. "ST. JOHN'S RADIO,"
156, St. John's Hill, S.W.11. (BAT 9838.)

BRAND NEW TELEVISION TUBES
12 Months' Guarantee
12in., £5.12.6; 14in., £8.0.0; 17in., £9.0.0
CRM type 17in. £10.0.0. Carr. & Ins. 5/-
FIDELITY RECORD PLAYER
Four speeds. Takes 7in., 10in. or 12in.
records. Amazing reproduction. Colours:
Fawn, Tweed/Tan or Grey Cord/Maroon.
A.C. only 200-250 volts. Only 91 gms.
Carr. 5/-. S.A.E. with all enquiries.
RELANCE ELECTRICAL SERVICES
Mail Order Dept., 73, Vista Way,
Kenton, Harrow, Middx. WOR. 4512

SETS & COMPONENTS (continued)

T.V. TUBES, factory rebuilt (re-
gunned), fully guaranteed, 14in. £4,
17in. £5, p. and p. 10/-. 24, Bristol
Rd., Brighton.

FOR SALE

ASTOUNDING VALUE.—9in. Tele-
visions, 45/-; 12in. Televisions, 70/-;
14in., £9/10/-; 15in., £5/10/-; 17in.,
£14. Complete but not guaranteed
working; as received in part ex-
change. TOMLINS, 127, Brockley
Rise, Forest Hill, London, S.E.23. All
famous makes available; carriage 7/6.

SERVICE SHEETS: also Current and
Obsolete Valves for sale. JOHN
GILBERT RADIO, 20, Extension,
Shepherds Bush Market, London,
W.12. (Phone: SHE 3052.)

VALVE CARTONS at keen prices.
Send 1/- for sample and list. J. & A.
BOXMAKERS, 75a, Godwin St.,
Bradford, 1.

SATISFACTION ASSURED.—12in.
Televisions, £9/10/-; 14in., £16;
17in., £19/10/-. Write for quotation,
stating requirements. We guarantee
satisfaction. TOMLINS, 127, Brockley
Rise, Forest Hill, S.E.23.

MAKING YOUR OWN TELESCOPES.
Enlargers, Projectors, Viewers,
Microscopes, Episcopes, etc., then
our booklets "How to Use Ex-Gov.
Lenses and Prisms." Nos. 1 and 2.
2/6 ea., will show you easily and
quickly how to achieve the finest
possible results at lowest possible
cost. The most comprehensive lists
of optical and scientific equipment
in the British Isles is free for s.a.e.
H. W. ENGLISH, Rayleigh Rd.,
Hutton. Brentwood, Essex.

1,000 TELEVISIONS, all makes, from
£3 working, 10/- not. Callers only.
9 till 6, including Sats. 39, White-
horse Lane, Stepney, London.

100 BAYS of brand new adjustable
steel Shelving, 72in. high x 34in. wide
x 12in. deep, stove enamelled dark
green; sent unassembled, 6-shelf bay,
£3/15/-; sample delivery free; quan-
tity discounts. N. C. BROWN LTD.,
Eagle Steelworks, Heywood, Lancs.
(Tel.: 69018.)

WANTED

WANTED. Service Sheets and
Manuals. No quantity too large or
too small; highest prices paid.
SULTAN RADIO, 2 Stanley Road,
Tunbridge Wells, Kent.

NEW TV VALVES WANTED. Send
valves, cash by return to: P. J. F.
ANDREWS, 61-63, Rosemary Rd.,
London, S.E.15.

A PROMPT CASH OFFER for your
surplus Brand New Valves, Speakers,
Components, Test Instruments, etc.
R.H.S. 155, Swan Arcade, Brad-
ford, 1.

NEW VALVES WANTED.—EY51,
ECL80, PCC84, PCF80, PCL83, PL81,
PCL82, PY81, R19, U801, 30P4, etc.
Best cash prices by return. DURHAM
SUPPLIES, 175, Durham Rd.,
Bradford 8, Yorkshire.

WANTED—VALVES. Modern TV
and radio types. Large or small
quantities. Box No. 22.

AERIALS

MAKE YOUR OWN AERIALS

SAVE £££
TV aerial manufacturer offers "do-it
yourself" kits. 60 components include
castings, pressings, mouldings, tubes,
brackets, can be utilized to make 100 different
models, TV, V.H.F., amateur. Brochure
gives full illustrations, element dimensions
and prices. Discounts for quantities.

THE RICHARD MAURICE
EQUIPMENT CO.
Portsmouth Road, Cobham, Surrey.
COBHAM 3239.

MISCELLANEOUS

LOUDSPEAKERS. Electric Clocks
and Shavers repaired promptly.
MODEL LOUDSPEAKER SERVICE,
Shipton on Cherwell, Oxford.

PROTECT YOUR CAR AT NIGHT
"LITON"
PHOTOELECTRIC
PARKING LIGHT
SWITCH

will switch your lights on at dusk—off
at dawn, automatically, while you are
at work, in bed, or away from home.
Controlled by light. Transistorised.
Avoid accidents, fines. Save your
battery.

KIT OF PARTS. 52/6
BUILT AND TESTED. 57/6
Pat. Pending. Send 6d. stamp for pamphlet.
"St. John's Radio," 156, St. John's
Hill, S.W.11. BAT7ersea 9838

SERVICE SHEETS

FAULTFINDER FILES (TV) showing
common faults that each receiver is
prone to and other useful servicing
information. 2/- ea. List 9d. plus
postage. S.P. DISTRIBUTORS, 11,
Old Bond St., London, W.1.

SERVICE SHEETS. Radio, T.V.,
5,000 models. Lists 1/-, S.A.E.
enquiries. TELRAY, 11, Maudland
Bk., Preston.

SERVICE SHEETS, Radio and TV,
4/- ea.; also hire. List 1/-. **GLOBE**
SUPPLIES, 33, Fairfield Close,
Sidcup, Kent.

SERVICE SHEETS for sale, T.V. 4/-;
Radio 3/-; also hire; immediate
delivery; s.a.e. please. **SULTAN**
RADIO, 2 Stanley Road, Tunbridge
Wells, Kent.

SERVICE SHEETS for sale, all types,
from 1/-. Free Fault Finding Guide
with all service sheets. 100 T/V Service
Sheets covering 330 popular
models. 18/6. Radio, T/V, Electronic,
Books. S.A.E. lists / enquiries.
HAMILTON RADIO (T), 237, Sedles-
combe Rd. N., Hastings.

SERVICE SHEETS.—We have the
largest stock of Radio and TV. Service
Sheets in the Country for sale
at 4/- each and for hire. Why
tolerate delay in obtaining Service
Sheets when we will despatch by
return? List 1/-; s.a.e. with en-
quiries. Mail Order Only. S.P.
DISTRIBUTORS, 11 Old Bond Street,
London, W.1.

SITUATIONS VACANT

LABORATORY TECHNICIAN AND WIREMEN for interesting work in the building and testing of Electronic Apparatus, for medical and industrial equipment. Permanent posts for suitable applicants, in pleasant, modern premises in central area, easily accessible by Tube and bus. Box 20.

TELEVISION ENGINEERS

required for

PRODUCTION FAULT-FINDING TESTING AND REPAIR

Work is varied and interesting with opportunities for employment on Experimental work.

All appointments are to the Permanent staff, with Pension Fund and Sports and Social Club.

Exceptional prospects in a large and rapidly expanding organisation.

Apply to:—

BRITISH RELAY WIRELESS LIMITED

(Staff Appointments),

1-7 CROFT STREET, SOUTH BERMONDSEY, S.E.8.

EDUCATIONAL

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text free. "The Practical Radio Engineer," journal, sample copy 2/-. 6,000 Alignment Peaks for Superhets, 5/9. Membership and Entry Conditions booklet 1/-. all post free from the SECRETARY, I.P.R.E., 20, Fairfield Road, London, N.8.

"**HOW AND WHY**" of Radio and Electronics made easy by a new, non-maths, practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New Courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept. 12 P.T., RADIO-STRUCTOR, 40, Russell St., Reading, Berks.

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation—I.C.S. Courses for the enthusiast and for those seeking examination qualification. Brit.I.R.E., City and Guilds, R.T.E.B., etc. Build your own equipment with Practical Radio Course. Write to-day for free book. INTERNATIONAL CORRESPONDENCE SCHOOLS, Intertext House, Parkgate Road (Dept. 516), London, S.W.11.

EDUCATIONAL (continued)

BUILD YOUR OWN HI-FI at home! At last, for reasonable cost—the chance to make your own quality Hi-Fi Audio Equipment and to gain the knowledge to service and maintain it. Free brochure from: Dept. 20 P.T., RADIOSTRUCTOR, 40, Russell St., Reading, Berks.

**★ LEARN ★
RADIO & T/V
SERVICING
for your OWN
BUSINESS/HOBBY**

● by a new exciting no-maths system, using practical equipment, recently introduced to this country.

**FREE Brochure from:—
RADIOSTRUCTOR
DEPT. G78, 46, MARKET PLACE
READING, BERKS. 1/60**

**FIRST-CLASS
TELEVISION and
RADIO COURSES . .**

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of **SUCCESS OR NO FEE** Write now for your copy of this invaluable publication. It may well prove to be the turning-point in your career.

**FOUNDED 1885—OVER
150,000 SUCCESSES**

**NATIONAL INSTITUTE OF
ENGINEERING
(Dept. 462), 148, HOLBORN,
LONDON, E.C.1.**

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne.

TRANSFORMERS

Suppliers to B.B.C., I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

Rewinds to all makes.
H.W. FORREST (Transformers) Ltd.
Shirley, Solihull, Warwickshire
Tel.: SHIRLEY 2483



**Fly with the R.A.F.
as an Air Signaller**

There are immediate vacancies for fit young men to train as Air Signallers. They will carry out a wide range of skilled duties in the latest types of aircraft.

Candidates must be between 17½ and 25 and have reached G.C.E. standard (or equivalent) with 'O' level passes in English and Maths; they must have studied elementary Science. Initial engagement is for 9 years but service may be extended to the age of 55. There are opportunities for Air Signallers to be considered for commissions as Pilots, Navigators or Air Electronics officers.

Pay whilst under training starts at £8 4s, 6d.. On successful completion of training and promotion to sergeant, pay increases to £13 6s. 0d. Food and accommodation are provided free; marriage allowance and ration allowance are issued where appropriate; and other allowances are payable in special circumstances.

Write for full details stating age and educational qualifications to:—

The Under-Secretary of State

AIR MINISTRY (M.9) (PTN 565), ADASTRAL HOUSE
LONDON, WC1

A SUPER SPECIAL TV TUBE OFFER

Why buy rebuilt or reconditioned tubes when we can supply you with a brand new 17in. tube to replace the MW 43-64, 43-69, 171K, 172K, 17 ASP4, 17 AXP4, C17-1, C17-A, CR17-22, C17-FM, MW 43-80. Made by world-famous manufacturers complete with 12 months' maker's guarantee. Our Unbeatable Price £8.10.0. Also available brand new 14in. to replace 36-24, 36-44, TR14-21, TR14-22, 14 KP4A, 14-LP4, 141K, C36-24 or for AW 36-20, 36-21 12in. brand new 31 MW 31-74, all at £7 each. Also Cossor 65K 15in. 4 volt filament, equivalent to TA15 or 85K by fitting 6 volt filament transformer 10 gms. Cossor 108K 10in. equivalent to EMI 316 £6.10.0. Ferranti 9in. T9/5 4 volt filament 50/-, Post. packing & insurance 10/- extra.

NEW MAX ELECTRONICS

for London's Finest Bargains in electronic and radio equipment. Also Largest Selection of Tape Recorders in the U.K. All in stock 500 shop soiled and H.P. reprocessed TV sets in all sizes. All Guaranteed.

220, Edgware Road, London, W.2.

Tel. PAD 5807

RES/CAP. BRIDGE 37/-
p. & p. 2/-
Checks all types of resistors, condensers 6 RANGES
Built in 1 hour. Direct reading
READY CALIBRATED
Stamp for details of this and other kits.
RADIO MAIL (Dept. VW)
Raleigh Mews, Raleigh Street, Nottingham

BRAND NEW GUARANTEED VALVES

CHECK THESE PRICES AND SEE HOW WE CATER FOR THE CITIZEN'S POCKET

DAF96	8/-	EF86	11/-	PY82	6/9
DF96	8/-	EL41	9/-	PY83	7/9
DK92	8/3	EL84	8/-	UAF42	9/-
DK96	8/3	EY51	9/6	UBF89	7/9
DL94	7/3	EY86	8/6	UCC85	7/9
DL96	8/-	PCC84	7/6	UCH42	9/-
EBC41	8/3	PCC85	11/-	UCH81	8/9
ECC81	5/9	PCF80	7/3	UF41	8/6
ECC82	6/3	PCF82	9/-	UF89	7/3
ECC83	6/9	PCL82	9/-	UL41	8/6
ECC84	8/6	PL36	14/-	U25	11/3
ECC85	8/6	PL81	9/9	IR5	6/9
ECF80	10/10	PL82	8/-	IS5	6/-
ECL80	8/3	PL83	7/9	IT4	5/-
EF80	6/3	PY81	6/6	354	6/6

Postage 6d. valve extra.

May we quote for obsolete and transmitting types? (S.A.E. please.)

CITIZENS' VALVE SERVICE (REGD.)

Office Address—No Callers :

103, GANTSHILL CRESCENT, ILFORD, ESSEX.

B.B.C. - I.T.V. - F.M. AERIALS



B.B.C. (BAND 1). Telescopic loft, 19/6. External, S/D, 26/3.

I.T.V. (BAND 3). 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 66/3. 1+5 Element, 83/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "11", 28/-. 3 Element loft, 52/8. S/D loft, 12/6. External S/D, 26/3. State channel when ordering, C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. T.P.)
3b, Godstone Road, Kenley, Surrey

TELEVISION ENGINEERS' POCKET BOOK

The new and enlarged edition of this pocket manual and data book has been extensively revised. Many pages of essential reference data on cathode-ray tubes, valves, also special sections on servicing equipment, dealing with printed-circuit models and projection receivers, aerials and interference problems.

Ed. by J. P. Hawker.

12/6. Postage 6d.

T.V. FAULT FINDING. A Data Pub; 5/-. Postage 6d.

TELEVISION SERVICING HANDBOOK by G. J. King. 30/-. Postage 1/6.

THE OSCILLOSCOPE AT WORK by A. Haas & R. W. Hallows. 18/-. Postage 1/-.

WORLD RADIO HANDBOOK FOR LISTENERS 1960. Ed. 15/6. Postage 1/-.

MODEL RADIO CONTROL by E. L. Safford. 21/-. Postage 1/-.

RADIO VALVE DATA 6th Ed. Compiled by "WWW" 5/-. Postage 9d. NEW 1960 CATALOGUE 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET,

LONDON, W.2.

Phone: PADdington 4185.

Open 6 days 9-6 p.m.

Factory Rebuilt . . . Super TELEVISION TUBES

All types fitted with New Gun Assembly. Fully guaranteed 12 months.

Mullard, Mazda, etc.:

12 inch £5.0.0

14/15 inch £5.10.0

17 inch £6.0.0

Carriage and insurance 12/6.

ALLOWANCE ON OLD TUBE.

C.W.O.

C.O.D. or Credit terms available. S.A.E. for all enquiries. **K.V.A. ELECTRONICS (Dept. P/1)** 3B Godstone Rd, Kenley, Surrey

EDDY'S (Nottm.) LTD.

172 ALFRETON ROAD, NOTTINGHAM

Surplus New and Guaranteed Valves

DAF96	8/3	EF80	6/6	U25	12/-
DF96	8/3	EF85	7/-	U31	7/9
DH63	7/6	EF86	11/-	U35	8/6
DK91	7/-	EF91	4/-	UB41	8/-
DK92	8/6	EL41	9/3	UY41	6/6
DK96	8/6	EL42	9/6	IA7GT	12/6
DL96	8/3	EL84	8/3	ID5	9/6
EABC80	7/9	EL85	10/6	IL4	3/9
EB34	1/6	EL91	4/9	IR5	7/-
EB41	7/-	EY51	9/6	IS5	6/6
EB91	4/-	EY86	9/6	IT4	4/9
EBC41	8/9	EZ80	6/9	5U4G	5/9
EBF80	8/6	GTIC	7/6	6C7G	3/6
ECC81	6/-	MU11	8/-	6K7G	2/3
ECC82	7/-	Pe1	2/6	6K8G	6/6
ECC83	7/6	PCC84	8/6	6S7M	5/-
ECC84	8/9	PCF80	9/-	6SN7GT	6/9
ECC85	8/6	PCF86	9/6	6X5GT	4/6
ECH42	8/9	PEN46	5/-	6V6G	5/9
ECL80	9/6	PL81	11/6	6V6GT	6/6
ECL82	10/6	PL82	7/9	6X4	6/-
EF36	2/6	PY31	8/6	12A6	5/6
EF37	4/-	PY80	6/9	25A6G	8/9
EF41	8/6	PY81	8/6	807 (B)	3/9
EF42	7/6	PY82	7/6	954	1/6

LUXEMBOURG EXPANDING AERIALS. Compact and easy to fit. No technical knowledge required. Greatly improves reception. 3/11. Post 6d.

THROAT MIKES. 1/-, Post 6d. Could be used for electrifying musical instruments.

JACK PLUGS. Standard. 1/11. Post 6d.

DIMMER SWITCHES. Ideal for train speed regulators. 1/11. Post 9d.

HANDMIKES. Carbon. 3/11. Post 1/-.

SPECIAL OFFER—CAR RADIO KITS. 7 transistors, long and medium. 2 watts output, R.F. stage and automatic gain control. 6 or 12 volts. Complete kit with cabinet. 10 1/2 gms. Post and Packing 5/-.

VIBRATORS. 12 v., 4 pin. 4/11. Post 1/-.

NIFE ACCUMULATORS. Size 3 x 2 1/2 x 7 in. 7 amp. hrs. 1.25v. Weight 13 ozs. 1/11 ea. P. and P. 1/6 one only, add 9d. each cell.

HEADPHONE CORDS. High Quality. 6 ft. lengths. 1/11 Pair. Post 6d.

SPEAKER GOLD GRILLE. 6 1/2" x 4". 1/-, Post 6d.

GERMANIUM DIODES. 1/- each; 9/6 dozen. Post 4d.

NEON MAINSTESTER/SCREWDRIVERS. 3/11. Post 9d.


RECTIFIERS. RM1 4/9, RM2 6/6, RM3 7/6, RM4 15/-, RM5 19/6. Contact cooled. 200-60 m.a., 7/6. Post 1/-.

CONDENSERS. Tubular wire end (not ex-govt.). 8 mfd., 450 v., 1/9; 8-8, 450 v., 2/6; 16 mfd., 450 v., 2/9; 16-16 450 v., 3/9; 16-8, 450 v., 4/-; 32 mfd., 450 v., 3/9; 32-32, 350 v., 4/-, Post 1/-.

CRYSTAL SETS. Complete 2-wave bands. High Gain. Good quality. 19/11. Post and packing 2/-.

HEADPHONES. High Resistance to suit above crystal set. Good quality. 12/11 pair. Post and packing 1/6.

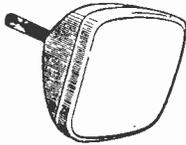Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and packing 6d. per valve extra. Over £3 free C.O.D. or C.W.O. only. C.O.D. charge 3/- extra. S.A.E. with all enquiries.



*** TOP QUALITY AT UNAPPROACHABLE PRICES**

With 12 Months Full Guarantee

NEW GUN TV TUBES

*This means Completely New Gun Assembly with New Button and Base. Rescreened and Realuminised. **VIRTUALLY A NEW TUBE.** All Mullard and Mazda and Hardglass Types.

12" — 14"	-	-	-	-	£6. 0. 0
15" — 17"	-	-	-	-	£6. 10. 0
21"	-	-	-	-	£9. 0. 0

Electro Statics 10/- extra.

All carriage and insurance now paid by us, to your address and on return of old tube all by passenger train, inclusive at £1. All C.W.O. Old tubes must be returned to us, or an extra charge of 10/- will be made on 12"-17" tubes.

SABRINA C.R.T. COMPANY

"Electron Works," North Bar, Banbury, Oxon. Phone 2390

REBUILT TV TUBES

FULLY GUARANTEED 12 months

Complete New Gun fitted in every Tube

12 in.	£5.0.0
14 in., 15 in. ...	£5.10.0
17 in.	£6.10.0
21 in.	£9.0.0.

Carriage & Insurance 10/- extra

NU-GUN TELETUBES Limited

3 The Mews, Duckett Rd., Harringay, London, N.4.

Telephone: MOUntview 2903

The book for every model maker . . .

RADIO-CONTROLLED MODELS

by F. J. CAMM

This practical book is the result of numerous experiments and long research on the subject and includes information already published in his nationally read "Practical Mechanics" plus additional material. Contents include steering control gear; receivers; transmitters; control box; tuned reeds; model actuators; tuning transmitting aerials; details for model battleship and aircraft, etc. Fully illustrated with circuit details, diagrams and photographs, etc.

12s. 6d. FROM ALL BOOKSELLERS

. . . or in case of difficulty 13s. 6d. by post from C. ARTHUR PEARSON LIMITED, Tower House, Southampton Street, London W.C.2.

ALUMINIUM, LIGHT ALLOYS BRASS, COPPER, BRONZE,

IN ROD, BAR, SHEET, TUBE, STRIP WIRE, ANGLE, CHANNEL, TEE

3,000 STANDARD STOCK SIZES

H. ROLLET & CO. LTD.

6 CHESHAM PLACE, LONDON, S.W.1 SLOane 3463


Works :

36 ROSEBERY AVE., LONDON, E.C.1

Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small"

54 Gns. — '17'

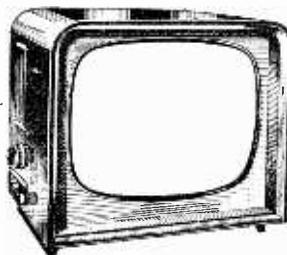

A full specification 17in. Television Receiver to Spencer-West standards now available at your Dealers. Remarkable performance and priced at 54 Gns. only, complete.

For Leaflet apply to :—

SPENCER - WEST LTD.
Quay Works, Great Yarmouth Norfolk

Phone : Great Yarmouth 4908/9
Grams : Spencer-West, Great Yarmouth

NEW VALVES !

Guaranteed Set Tested 24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, SET of 4, 21/6, DAF96, DF96, DK96, DL96, SET of 4, 29/6.

1D5	8/-	DL33	9/-	PCF82	9/-
1R5	6/3	DL35	10/6	PCL82	9/-
1S5	8/-	DL92	8/9	PCL83	11/6
1T4	4/6	DL94	7/3	PCN44	11/-
3S4	6/9	DL96	7/11	PEN36C	8/6
3V4	7/3	DBC41	8/6	PL36	13/-
5U4G	5/3	EBF80	8/-	PL38	14/6
5Y3GT	6/6	ECC81	5/6	PL81	10/-
5Z4G	9/6	ECC82	6/-	PL82	7/6
6K7G	2/-	ECC83	6/6	PL83	7/9
6R8G	5/6	ECC84	8/9	PY32	11/9
6Q7G	7/-	ECC85	8/-	PY80	7 -
6SL7GT	6/-	ECH35	6/9	PY81	6/9
6SN7GT	4/6	ECH42	8/9	PF82	7/-
6V6G	5/-	ECL90	8/3	U25	11/6
6X5GT	6/3	EF41	8/6	U26	11/6
6X5GT	5/-	EF80	5/6	U52	5/3
12K7GT	5/6	EF85	6/6	UABC80	7/6
12K9GT	11/6	EF86	10/3	UF42	9/-
12Q7GT	5/6	EF89	8/-	UBC41	7/9
35L8GT	9/-	EL33	10/-	UBF80	8/8
35Z4GT	5/6	EL41	9/-	UCC84	12/9
AZ31	8/9	EL84	6/9	UCC85	7/9
B36	8/6	EY31	8/9	UCF80	14/-
CL33	12/6	EY85	9/-	UCI42	7/9
DAC32	9/9	EZ40	6/9	UCH81	8/-
DAF91	6/-	EZ41	7/6	UCL82	11/6
DAF96	7/11	EZ80	6/3	UCL83	12/6
DF33	9/9	EZ81	7/-	UF41	8/9
DF91	4/9	CZ32	9/-	UF42	8/-
DF96	7/11	KT61	10/-	UF89	7/6
DH77	7/3	KT63	6/6	UL41	7/6
DK32	12/-	MU14	7/9	UL84	7/6
DK91	6/3	MX40	12/6	UY21	13/6
DK92	8/6	PCB84	8/-	UY35	6/9
DK96	8/3	PCF80	8/-	VP4B	9/6

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 2/6 extra. Office address, no callers.

GERALD BERNARD
90 CARR MANOR AVENUE, LEEDS 17

IS YOUR T.V. TUBE DIMMING? YOU CAN EXTEND THE LIFE OF THAT TUBE AND IMPROVE THE PICTURE



PRICE **30/-**

Post, packing,


& ins. 2/6.

C.W.O. C.O.D.

● NO WIRING ● NO SOLDERING ● JUST PLUG IN ● IT'S AUTOMATIC ● IT'S GUARANTEED ! We can offer these units for any make of set. **IMPORTANT.** State name, address, & make and model no. of set, & tube in block caps.

SINCLAIR ELECTRONICS,
Dept. P.T., 33, BERWICK ST., W.1. Callers Welcome—Trade Enquiries Invited.

Build your own Aerials...

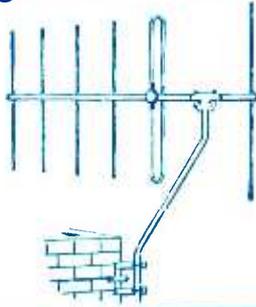

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M. Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:—

Fringevision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

AS ADVERTISED ON TELEVISION

Save £££

12 Months' Guarantee

FACTORY REBUILT ...

TELEVISION TUBES

**ALL TYPES AND SIZES—Immediate Delivery
FITTED WITH COMPLETE NEW GUN**

Price

12" £5.12.6 14" £5.17.6 15" £6.5.0 17" £7.0.0
21" £9.10.0

TERMS TO
THE TRADE

Plus 10/- carriage and insurance.
Cash with order or C.O.D.

RE-VIEW (LONDON) LTD.

10 High Street

Colliers Wood, S.W.19

Telephone : Liberty 3272

G.R.T. ISOLATION TRANSFORMERS
TYPE A. OPTIONAL 25% and 50% BOOST.
 2 V. OR 4 V. OR 8 V. OR 10 V. OR
 13.3 V., 12/6. TAPPED MAINS INPUT.
TYPE A2. HIGH QUALITY, LOW CAPACITANCE,
 10/15 pF. OPTIONAL BOOST 25%, 50%,
 75%, 10/6. TAPPED MAINS INPUT.
TYPE B. MAINS INPUT, MULTI OUTPUT 2,
 4, 6, 3, 7.3, 10 AND 13 VOLTS. BOOST 25%
 AND 50%. LOW CAPACITY, 21/-.

TRIMMERS, Ceramic, 30, 50, 70 pf., 9d.; 100 pf.,
 150 pf., 1/3; 250 pf., 1/6; 500 pf., 750 pf., 1/9.
RESISTORS, Preferred values, 10 ohms to 10 meg.
 1 w., 4d.; 1 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/-
HIGH STABILITY, 1 w., 1%; 2 w., Preferred values
 100 Ω to 10 MΩ. Ditto, 5%, 100 Ω to 5 meg., 9d
 10 watt) **WIRE-WOUND RESISTORS** (1/8
 15 watt) 25 ohms—10,000 ohms (1/8
 15,000 ohms.—50,000 ohms., 5 w., 1/9; 10 w., 2/3.

PLASTIC RECORDING TAPE

Long Play 7in. reel, 1,700ft. ... 35/-
 Long Play 5 1/2in. reel, 1,200 ft. ... 28/-
 Long Play 5in. reel, 850ft. ... 23/-
 Long Play 5in. reel, 250ft. ... 7/8

Standard 7in. reel, 1,200ft. ... 24/-
 Standard 5in. reel, 600ft. ... 15/-
 "Instant" Bulk Tape Eraser and Head De-
 flexer, 200/250 v. A.C., 27/8. Leaflet, S.A.E.

O.P. TRANSFORMERS, Heavy Duty 50 mA., 4/6.
 Multiratio push-pull, 7/6. Miniature, 384, etc., 4/6.
L.F. CHOKES 15/19. H. 60/65 mA., 5/-; 10 E.
 85 mA., 10/6; 10 H., 150 mA., 13/-.

MAINS TRANSFORMERS 200/250 v. A.C.
 STANDARD, 250-0-250, 80 mA., 6.3 v. 3.5 a.
 tapped 4 v. 4a. Rectifier 6.3 v. 1a. 5 v. ... 22/6
 2 v. or 4 v. 2a. ditto, 350-0-350 ... 10/6
MINIATURE 200 v. 20 mA., 6.3 v. 1 a. 10/6
MIDGET, 220 v. 45 mA., 6.3 v. 2 a. ... 15/6
SMALL, 250-0-250, 100 mA., 6.3 v. 3.5 a. 19/8
STD., 250-0-250, 65 mA., 6.3 v. 3.5 a. 17/6
HEATER TRANS. 6.3, 11 amp. ... 7/8
 Ditto, tapped sec. 2, 4, 6.3 v., 11 amp. ... 8/6
 Ditto, sec. 6.3 v. 3 amp. ... 10/6

ALADDIN FORMERS and core, jin., 8d.; jin., 10d.
 0.3in. FORMERS 5937/8 and Cans TV1/2, jin. sq. x
 2 1/2in. and jin. sq. x 1 1/2in., 2/- ea., with cores.
TYANA—Midget Soldering Iron, 230 v. 40 w., 16/9.
REMPLOY Instrument Iron, 230 v. 25 w., 17/6.
MAINS DROPPERS, Sin. x 1 1/2in., 400 ohms, 4/3.
 0.3 amp., 1,000 ohms, 4/8. 0.2 amp., 1,000 ohms, 4/3.
LINE CORD, .3 amp., 60 ohms per foot. .2 amp., 100
 ohms per foot. 2-way, 6d. per foot. 3-way, 7d. per ft.
LOUDSPEAKER P.M. 3 OHM. 5in. Rola, 17/6.
Sp. Plessey, 19/6. 6in. x 4in. Rola, 18/-
 6in. Rola, 18/6. 10 x 6in., 27/6. 10in. Rola, 30/-
 4in. Hi-Fi Tweeter, 25/- 12in. R.A., 30/-
 12in. 15 ohm 10 w. Plessey 45/-

STEMTONE HF1012 10in. 3 to 15ohm 10 w., 95/-
 12in. Baker 15 watt 3 ohm or 15 ohm, 105/-
CRYSTAL DIODE G.E.C. 2/- GEX34, 4/-
HIGH RESISTANCE PHONES, 4,000 ohms, 10/6 per
MIKE TRANS. 50 : 1. 3/9 ea.; 100 : 1. Potted, 10/6.
SWITCH CLEANER, Fluid squirt spout, 4/3 tin.
TWIN GANG TUNING CONDENSERS .365 pf.
 miniature tin. x 1 1/2in. 10in., .0005 Standard
 with trimmers, 9/-; less trimmers, 8/-; midget, 7/6.
SINGLE, 50 pF., 2/-; 75 pF., 100 pF., 160 pF., 7/-
 100 dielectric 100, 300, 500 pF., 8/-
SPEAKER FBET. GOLD CLOTH. 7in. x 2 1/2in. 5/-
 3 1/2in. x 3 1/2in., 10/-; 4 1/2in. 6in. wide, 10/-; 2ft.
 3in. wide, 5/-; Samples S.A.E.

New and Boxed VALVES 90-day Guarantee.

1R5	8/6	6R9G	8/6	EABC80	HABC80
1R5	8/6	6L6G	10/6		
1T4	8/6	6N7M	7/6	EB91	6HVR2A
2K2	8/6	6Z7G	10/6	EBC33	6MU14
6BM6	8/6	6X7	10/6	EB7C41	10G/P41
3V4	8/6	6BJ7M	10/6	EBF60	10G/PC84
5Y4	8/6	6SN7	8/6	ECC84	12G/PCF80
5U3	8/6	6V6G	7/6	ECP80	11G/PCLR2
5Z4	10/6	6X4	7/6	ECH42	10G/PN25
6AM6	8/6	6X5	7/6	ECL82	12G/PI82
6B8	5/6	612A7	9/6	EF39	7/6/PY80
6BE6	7/6	12A7U	9/6	EF41	10G/PY81
6BE6	10/6	12A7X	5/6	EF50	5/6/PY82
6BW6	10/6	12BE6	10/6	EF80	10G/EP91
6C6	7/6	12C7	8/6	EF89	8/6/UC41
6FG6	7/6	12Q7	8/6	EF92	5/6/UC42
6H6	3/6	35L6	9/6	EL32	5/6/UF41
6J5	8/6	35Z4	9/6	EL41	10G/UL11
6J6	7/6	80	10/6	EL84	10G/UY41
6J7G	8/6	87	8/6	EL92	10/6
6K6GT	6/6	954	1/6	EZ80	8/6/VR105
6K7G	5/6	EA50	1/6	E1148	1/6/VR150

TELEVISION REPLACEMENT LINE OUTPUT TRANSFORMERS

70/- ea. from stock.

For Makes and Models

Argosy: T2, CTV517. Decca :
 D17 & C. Defiant : TRI753.
RGD : 6017T, 7017C, C54.
Regentone : 17C, 17T, 17
 Comb.

Argosy: T3. Decca : D14.
 Defiant: TRI453T. Regentone:
 14T. RGD : 6014T.

Marconi : VT63DA.

Baird : 2014, 2017, 2114, 2117.

Cossor : 930 & T, 931, 933-4, 5,
 937, 938 & A. & F.
 939 & A & F, 943T, 946.

H.M.V. 1824 & A, 1825 & A,
 1826 & A, 1827 & A,
 1829 & A, 1865, 1869.

Marconi : VT68DA, VT69DA.

Sobell : TS17, T.346.

Ferguson : 306T, 308T.

Other makes available (7 days).
 S.A.E. with enquiries.

**LINE BLOCKING TRANS-
FORMERS, 10/- to 16/6.**

**FRAME BLOCKING
TRANSFORMERS, 13/6 to 21/-**
**FRAME OUTPUT TRANS-
FORMERS, 27/6 to 39/-.**

Most makes available (7 days).
 S.A.E. with all enquiries.

**TV and RADIO SERVICE
SHEETS 1,500 models. Send
2/6, your Model No. and S.A.E.**

ALUMINIUM CHASSIS, 18 s.w.g. undrilled.
 With 4 sides, riveted corners and lattice fixing
 holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/6;
 11 x 7in., 6/9; 13 x 9in., 8/6; 14 x 11in., 10/6;
 15 x 14in., 12/8; 18 x 16 x 1in., 16/8.

TRANSISTORS, GENUINE EDISWAN.
 Audio 10/-, R.F. 2 Me/154, 4 Me/5, 15/-.
 Complete data supplied. Continental OC71, 7/6

CRYSTAL MIKE INSERT by Acos, precision
 engineered. Size only jin. x 3/16in. 6/6.

HI-GAIN BAND 3 I.T.A. PRE-AMP KIT
 Cascade circuit with valve ECC84. Price 29/6
 With Power Pack, 49/6. Plans only 6d.
 Band 1 B.B.C. version same prices.

TELETON "TRANSIDYNE"
MIDGET SUPERHEAT PORTABLE 6" x 4" x 1"
 6 transistors, printed circuit, Ferrite aerial.
 All parts and cabinet, £11.19.6.
 We include Ediswan Transistors for maximum
 performance. Details 9d.

BBC TRANSISTOR RADIO. Med. and Long
 Wave. Complete kit, 32/6, phones 7/6 extra.
 Deal! Aid Sparekit with Special Lead 15/6.
 Details 6d.

GARRAD TANK 11 SINGLE PLAYER AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records
 7in. 10in., 12in. Lightweight metal pick-up.
 GG8 plug-in head, Auto stop. Stereo-wired.
OUR PRICE £8.10.0 each. Post Free
 (Stereo Heads £2 extra).

Model 4HF TRANSCRIPTION QUALITY.
 With Plug-in Norma Heads, £18.0.0.
 (Stereo Heads £2 extra).

Volume Controls 80 ohm COAX

Long spindles. Guaranteed 1 year. Midget 5K ohms to 2 Meg. 50% D.P. Sw. 3/-
 8/-
 Linear or Log Tracks. 4/9
 Post 1d. per yard extra. Semi-air, spaced. 1in. dia. Losses cut 6d. per yard. Fringe Quality. 1 1/2 in. Air Spaced. 1/- yd.

COAX PLUGS ... 1/- LEAD SOCKET ... 2/6
PANEL SOCKETS 1/- OUTLET BOXES ... 4/6
BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms.
DITTO SCREENED per yd. 1/6. 80 ohms only.
WIRE-WOUND POTS 3 WATT. Pre-set. 300
 Ohm. All value 25 ohms to 25 K., 3/- ea.
 T.V. Tube. All value 25 Ohms to 25 K., 3/- ea.
 10 K. 50 K., 4/- (Carbon 30 Ohms to 2 meg., 3/-)

WIRE-WOUND 4 WATT. Pots. Long Spindle
 Values, 100 ohms to 50 K., 6/8; 100K, 7/8.
CONDENSERS, New Stock. 100V. 5 pf. to 7 kV.
 T.C.C., 5/8; Ditto, 20 kV., 9/8; 1 mfd., 7 kV., 9/8;
 Tubular 500 v., .001 to .05 mfd., 9d.; .1, 1/-;
 .25, 1/6; .6/350 v., 1/9; .1/350 v., 9d.; .01/2,000 v.,
 .1/1,000 v., 1/9; .1 mfd., 2,000 volts, 3/8.

CERAMIC CONDS. 500 v., .3 pf. to .01 mfd., 9d.
SILVER MICA CONDENSERS. 500 v., 1 pf. to 300 pf.
 1/-; 600 pf. to 3,000 pf., 1/3. Close tolerance
 (± 1 pF.) 1.5 pF. to 47 pF., 1/8. Ditto 1/5 50 pF.
 to 815 pF., 1/9; 1,000 pF. to 5,000 pF., 2/-.

I.F. TRANSFORMERS 7/6 pair.
 465 Kc/s Slug Tuning Miniature Can. 2 1/2in. x
 1in. x 1in. High Q and good bandwidth.
 By Pye Radio. Data sheet supplied.

Wearite M800 I.F. 465 Kc/s. 12/6 per pair.
 Wearite 550 I.F. 465 Kc/s. 12/6 per pair.

NEW ELECTROLYTICS. FAMOUS MAKES
TUBULAR TUBULAR CAN TYPES

1/350 v. 2/-	60/350v.	5/6	8/500v.	2/-	
2/450 v. 2/3	100/25v.	2/-	16/500v.	4/-	
4/450 v. 2/3	250/25v.	2/6	32/250v.	4/-	
8/450 v. 2/3	500/12v.	3/-	100/270v.	5/6	
8/500 v. 2/9	8+8/450v.	4/6	2,500/3v.	4/-	
16/450v.	3/8+8+8/500v.	5/-	5,000/6v.	5/-	
16/500v.	4/8+16/450v.	5/-	32+32/350v.	4/8	
32/450v.	5/8+8+16/500v.	5/6	50+50/350v.	7/-	
22/25v.	1/9+16+16/450v.	5/6	64+120/27v.	6/6	
50/25v.	2/-	16+16/500v.	6/-	64+120/350v.	11/8
50/50v.	2/-	32+32/350v.	4/6	100+200/275v.	12/6

**LATEST EMI. 4-SPEED SINGLE RECORD
PLAYER.** Acco 73 hi-fi and normal
 crystal pick-up. Silent motor, heavy turn-
 table. Special Offer, £8.19.6. Post 3/6.

MAINS TYPE SELENIUM 800 v. 55 mA., 7/6
CONTACT COOLED 250 v. 50 mA., 7/6; 60 mA., 8/6;
85 mA., 9/8; 200 mA., 21/-; 300 mA., 27/6.
COILS wearite "P" type, 3/- each. Osmer Midget
 "Q" type adj. tap core, 3/- each. All ranges.
TELETON L & Med. T.R.P. with reaction, 3/6
FERRITE ROD AERIALS. M.W. 8/8; M. L. & L. 2/-
T.R.F. COILS A/H/F. 7/- pair. H.F. CHOKES, 2/6.
FERRITE ROD. Tin x 3/8in., dia., 2/6.

JASON P.M. TUNER COIL SET. 26/-, H.F. coil,
 aerial coil. Oscillator coil, two I.F. trans,
 10.7 Mc/s. Reaction Detector and heater choke.
 Circuit book, using four 6AM6, 2/6.
COMPLETE JASON P.M. KIT WITH VALVES.
 £8.15.0. Fringe area kit, 22/6 extra.

FULL WAVE BRIDGE SELENIUM RECTIFIERS:
 2, 6 or 12 v. 14 amp., 8/4; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped input 200/
 250 v. for charging at 2, 6 or 12 v., 14 amps., 15/6.
 2 amp., 17/6; 4 amps., 22/6. Circuit included.
VALVE and TUBE EQUIVALENT BOOKS, 5/-.
TOGGLE SWITCHES. 3 P. 2/-, D.P. 8/6. D.P.D.T. 4/-
WAVECHANGING SWITCHES

5 p. 4-way 2 water long spindle ... 6/6
 2 p. 2-way, or 3 p. 2-way short spindle ... 2/6
 2 p. 6-way, 4 p. 2-way, 4 p. 3-way long spindle ... 3/6
 3 p. 6-way, or 1 p. 12-way long spindle ... 3/6
VALVEHOLDERS. Par. Int. Oct. 4d. EP50, EA60,
 6d. B12A, CRT. 1/3. Eng. and Amer. 4, 5, 6 and
 7 pin. 1/- MOULDED MAZDA and Int. Oct., 6d.
 BTG, B8A, B80, B9A, 6d. BTG with can., 1/6.
 B7C with can., 1/6. CERAMIC EP50, BTG, B9A.
 Int. Oct. 1/-, S/CANS BTG, B9A, 1/- ea.

RADIO COMPONENT SPECIALISTS

Post and Packing 1/- over £2 free. (Export post extra.) C.O.D. 1/6. (Wed. 1 p.m.)

**OUR ONLY ADDRESS
337 WHITEHORSE RD.,
WEST CROYDON**

THO 1665. Buses 133 or 68