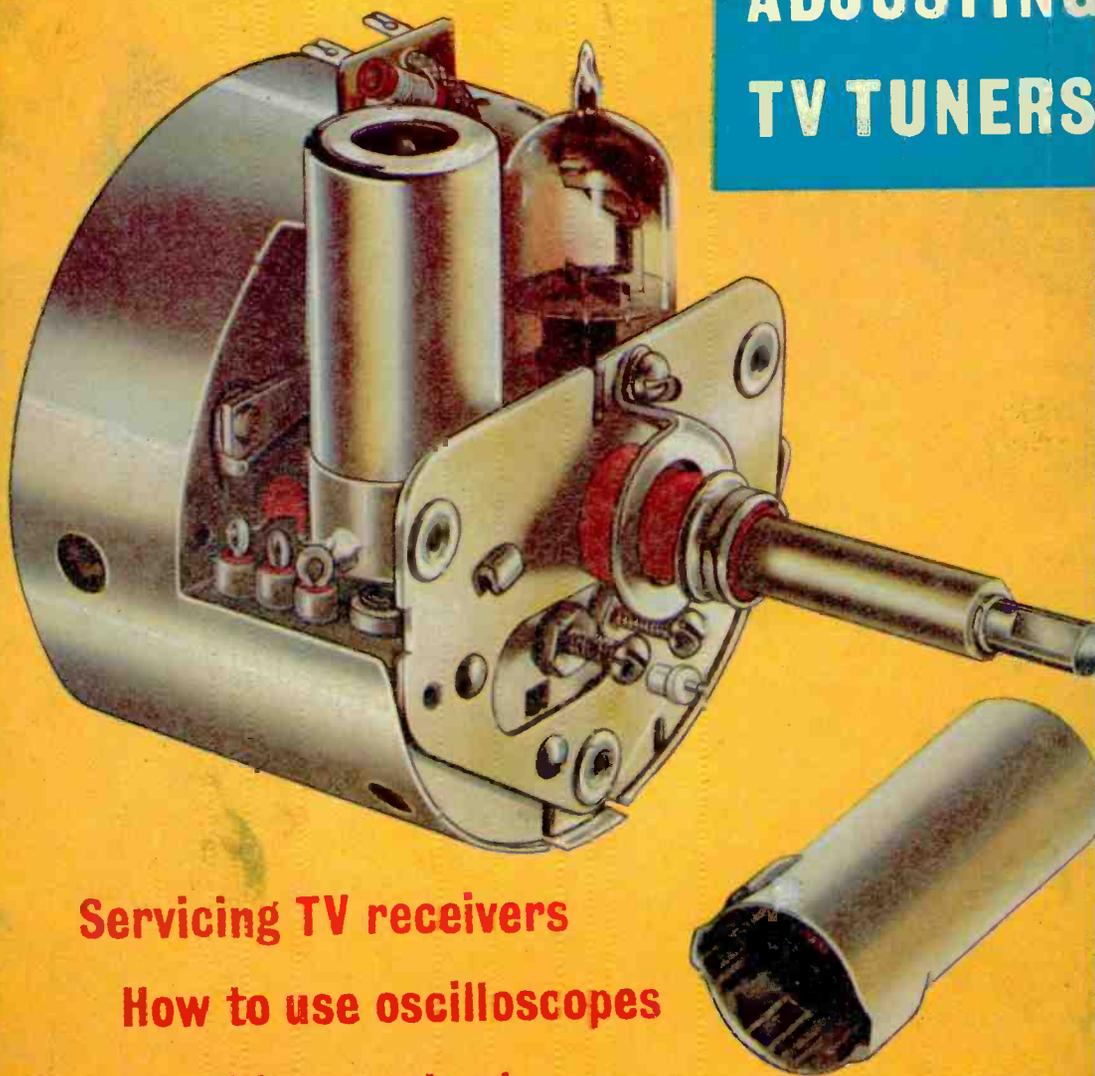


Practical TELEVISION

AUGUST
1961

1'6

ADJUSTING
TV TUNERS




Servicing TV receivers

How to use oscilloscopes

Your problems solved

Build your own Aerials...

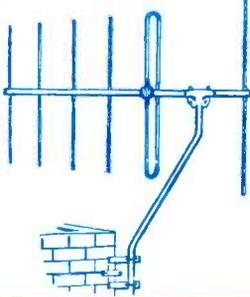

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.
 Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:—

Fringelevision Ltd.


MARLBOROUGH, WILTS. Phone: 657/8

SPECIAL FOR THE "HAMS" RADIO STATION

Illustrated

1/8 inch detachable bit soldering instrument
List No. 70

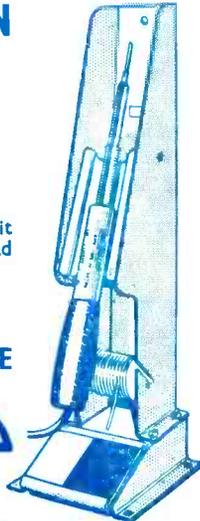Combined Protective Unit with Wiper/Abrasion Pad and Solder Reel
List No. 700



British & Foreign Patents, Registered Designs, etc.

Telegrams: "SOLJOINT, LONDON"

Apply SALES & SERVICE

ADCOLA

(Regd. Trade Mark)

GAUDEN ROAD
CLAPHAM HIGH ST.
LONDON, S.W.4

Telephones:
MACaulay 4272 - 3101

THOUSANDS

OF SATISFIED PEOPLE

VIEW ON **E.M.S.**

REBUILT TELEVISION TUBES

- ★ A NEW GUN IN EVERY TUBE
- ★ BUY DIRECT FROM THE FACTORY
- ★ 18 MONTHS' GUARANTEE

12 inch £5.0.0 14 inch £5.10.0
 17 inch £6.10.0

Immediate dispatch on receipt of Remittance
 Carriage and insurance 12/6 extra
£1 Refunded on receipt of your old Tube

SPECIAL TERMS TO THE TRADE

MARSHALL'S for TELEVISION LTD.
 131 St. Ann's Road, Tottenham, London, N.15
 STAMFORD HILL 3267 & 5555

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE. ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.

OA2	17/6	6F6G	7/-	10F1	26/6	35Z4GT	6/-	DH76	5/-	EF40	15/-	HN309	24/7	PL84	12/8	UABC80	9/-	XFY34	17/6
OB2	17/6	6F11	17/3	10F9	11/6	35Z5GT	9/-	DH77	7/-	EF41	9/-	HVR2	20/-	PL820	18/8	UAF42	9/6	XH(1.5)	6/6
OZ4	5/-	6F12	4/6	10D11	15/11	43	10/-	DK32	12/-	EF42	10/6	HVR2A	6/-	PM84	17/7	UB41	12/-	XSG(1.5)	6/6
IA5	6/-	6F13	11/6	10P13	15/-	50CS	10/-	DK91	6/6	EF50(A)	7/-	KF35	8/6	PX4	10/6	UBC41	8/6	Y63	7/6
IA7GT	12/-	6F15	10/6	10P14	19/3	50CD6G	10/-	DK92	9/-	EF50(E)	5/-	KL35	8/6	PY31	16/7	UBC81	11/4	Z63	7/6
ID5	12/6	6F24	12/6	12A6	5/-		36/6	DK96	8/6	EF54	5/-	KLL32	24/7	PY32	12/6	UBF80	9/-	Z66	17/6
IG6	17/6	6F32	10/6	12AC6	15/3	50L6GT	9/6	DL33	9/6	EF73	10/6	KT2	5/-	PY80	7/6	UBF89	9/6	Z77	4/6
IHS5GT	10/6	6F33	7/6	12AD6	17/3	53KU	19/11	DL66	17/6	EF80	6/-	KT33C	10/-	PY81	8/6	UBL21	23/3	Z719	6/-
IL4	3/6	6G6	6/6	12AE6	13/11	77	8/-	DL68	15/-	EF85	6/-	KT36	10/-	PY82	7/-	UC84	14/7		
ILD5	5/-	6H6	3/6	12AH8	12/6	80	9/-	DL72	15/-	EF86	10/6	KT41	23/3	PY83	8/6	UC85	9/-	Transistors	
ILN5	5/-	6I5	5/-	12AT6	7/6	83	15/-	DL92	7/-	EF89	9/-	KT44	12/6	PY88	13/3	UC80	16/7	and diodes	
INSGT	10/6	6I6	5/6	12AT7	6/-	85A2	16/-	DL96	8/6	EF92	4/6	KT61	12/6	PZ30	19/11	UCH21	23/3	CG1C	7/6
IR5	6/6	6I7G	6/-	12AU6	23/3	90AG	67/6	DM70	7/6	EF97	13/3	KT66	15/-	QP25	14/6	UCH81	9/6	CG6E	7/6
IS4	9/-	6I7GT	10/6	12AU7	6/6	90AV	67/6	EB0F	30/-	EF98	13/3	KT88	24/-	QS150/15		UCL82	11/6	CG7E	7/6
IS5	6/-	6K7G	5/-	12AV6	12/6	90CI	16/-	EB3F	30/-	EF183	18/7	KTW61	6/6		10/6	UCL83	19/3	CG10E	7/6
IT4	3/6	6K7GT	6/-	12AX7	7/6	90CG	37/6	EA50	2/-	EF184	12/6	KTW62	7/6	R12	9/-	UCL41	9/6	GD3, 4, 5,	
IU5	6/-	6K8GT	10/6	12BA5	8/-	101	13/6	EA76	9/6	EK32	8/6	KTW63	6/6	R18	14/-	UF42	12/6	6, 8	4/-
2D21	15/-	6K8G	6/6	12BB6	9/-	150B2	18/-	EABC80	9/-	EL32	5/-	KTZ41	5/-	R19	19/11	UF80	10/6	OA70	3/6
2P	26/6	6K25	19/11	12BH7	21/3	161	10/6	EAC91	4/6	EL33	12/6	KTZ63	7/6	RG1/240A		UF85	9/6	OA73	3/-
2X2	4/6	6L1	23/3	12E1	30/-	185B2	33/2	EAF42	9/-	EL34	5/-	L63	6/-		54/-	UF86	17/11	OA79	3/-
3A4	6/-	6L6G	8/-	12J5GT	4/6	304	10/6	EB34	2/6	EL38	26/6	MHL4	7/6	RK34	7/6	UF89	9/-	OA81	3/-
3A5	10/6	6L6M	9/6	12J7GT	9/6	305	10/6	EB41	8/6	EL41	9/-	MHLD6	12/6	S130	22/6	UL41	9/-	OA86	4/-
3B7	12/6	6L7GT	7/6	12K5	17/11	807	7/6	EB91	4/-	EL42	10/6	ML4	8/6	SP4(7)	14/6	UL44	26/6	OA91	3/6
3D6	5/-	6L18	13/-	12K7GT	5/6	956	3/-	ECB3	23/3	EL81	16/7	MS4B	23/3	SP4	3/6	UL46	14/6	CA95	3/6
3Q4	7/6	6L19	23/3	12K8GT	14/-	1821	16/7	EBC33	5/-	EL83	19/11	MUI12/14	8/-	SP6	3/6	UM4	17/3	OA211	20/-
3Q5GT	9/6	6LD20	15/11	12Q7GT	4/6	4033L	12/6	EB41	8/6	EL84	7/6	N78	23/3	SP1	26/6	UM34	17/3	OC16	48/-
3S4	7/-	6N7	8/-	12SA7	8/6	5763	12/6	EBC81	8/-	EL85	17/11	N108	23/3	T41	9/-	UMB0	15/3	OC19	48/-
3V4	7/6	6P26	19/11	12SC7	8/6	7193	5/-	EBF80	9/-	EL86	9/6	N308	20/7	TD4	12/6	UR1C	18/7	OC23	87/-
5R4G	17/6	6P28	26/6	12SG7	7/-	7475	7/6	EFB83	13/11	EL91	9/6	N339	15/-	TH41	26/6	UJ6	19/11	OC26	25/-
5U4G	6/6	6Q7G	6/6	12SH7	8/6	9002	5/6	EFB89	9/6	EL95	10/6	N339	15/-	TH43	26/6	UJ6	19/11	OC28	25/-
5V4G	10/-	6Q7GT	11/-	12SI7	8/6	AC/9P		EBL1	29/6	ELB20	18/7	P61	3/6	TH33	33/2	UJ7	16/11	OC29	25/-
5Y3	6/6	6R7G	10/6	12SD7	11/6	5-pin 23/3		ECL21	23/3	ELB22	19/-	PABC80		TP22	15/-	UJ8	26/6	OC35	25/6
5Z4	19/11	6SA7GT	8/6	12SD7	11/6	7-pin 15/-		EBL21	23/3	EM34	9/6		13/11	TP25	15/-	UJ9	7/6	OC44	11/6
6A7	10/6	6SG7GT	7/6	12SR7	8/6	AC/2PN		EC52	5/6	EM71	23/3	PCC84	8/-	TP2620	33/2	UY1N	18/7	OC45	10/6
6A8	9/-	6SH7GT	8/-	12Y4	10/6	DD	12/6	EC54	6/-	EM30	9/-	PCC85	9/6	TY86F	13/3	UY21	16/7	OC65	22/6
6AC7	4/-	6SI7GT	8/-	19AQ5	10/6	AC/6PN	7/6	EC70	12/6	EM81	9/6	PCC88	18/-	UI2/14	8/6	UY41	7/6	OC66	25/-
6AG5	5/6	6SK7GT	6/-	19H1	10/-	ATP4	5/-	ECC32	5/6	EM85	17/3	PCC89	11/6	UI6	10/-	UY85	7/6	OC70	6/6
6AG7	7/6	6SL7GT	6/6	20D1	15/3	AZ1	18/7	ECC33	8/6	EM81	5/3	PCF82	10/6	UI9	36/-	VMS4B	15/-	OC72	8/-
6AK5	8/-	6SN7GT	5/6	20F2	26/6	AZ31	10/-	ECC34	24/7	EY51	10/6	PCF84	16/7	U22	8/-	VP2	12/6	OC73	16/-
6AL5	4/-	6SQ7GT	9/6	20L1	26/6	AZ41	13/11	ECC35	8/6	EY83	16/7	PCF86	15/-	U24	29/10	VP4	15/6	OC75	8/6
6AM6	4/-	6SS7GT	8/-	20P1	26/6	B36	15/-	ECC40	23/3	EY84	14/-	PCL82	10/6	U25	17/11	VP2B	14/6	OC77	15/-
6AQ5	7/6	6U4GT	12/6	20P3	23/3	BL63	7/6	ECC81	6/-	EY86	9/6	PCL83	10/6	U26	10/6	VP4B	23/3	OC78	8/6
6AT6	7/-	6U5G	7/6	20P4	26/6	CI	12/6	ECC82	6/6	EZ35	6/-	PCL84	12/6	U31	9/6	VP13C	7/6	OC81	8/6
6AU6	10/6	6U7G	8/6	20P5	23/3	CIC	12/6	ECC83	7/6	EZ40	7/-	PCL85	16/7	U33	26/6	VP23	6/6	OC170	13/6
6AV6	12/8	6V6G	7/-	25A6G	10/6	CBLL	26/6	ECC84	9/-	EZ41	7/-	PCL86	16/7	U35	26/6	VP41	6/-	OC171	14/6
6B8	5/-	6V6GTG	8/-	25L6GT	10/6	CBL31	23/3	ECC85	8/6	EZ80	7/-	PEN4A	23/3	U37	26/6	VR105	8/6	OC200	16/6
6BA6	6/6	6X4	5/-	25Y5G	10/-	CCH35	23/3	ECC88	18/-	EZ81	7/-	PEN4B	26/6	U45	9/-	VT61A	5/-	OC203	24/-
6BE6	6/6	6X5GT	6/-	25Z4G	9/6	CC506	6/6	ECC91	5/6	FC4	15/-	PEN4D		U50	6/6	VT501	5/-	OC271	29/6
6BG6G	23/3	6/30L2	10/-	25Z5	9/6	CL33	19/3	ECF80	10/6	FW4/500	8/6			U52	6/6	W76	5/6	TJ2	45/-
6BH6	8/-	7A7	12/6	25Z6G	10/6	CV63	10/6	ECF82	10/6	FW4/800	8/6	PEN25	4/6	U54	19/11	WH81M	6/-	TJ3	50/-
6BJ6	6/-	7B6	21/3	27S1	19/11	CY1	18/7	ECF86	19/11	GUSO	27/6	PEN40DD		U76	6/-	W107	18/7	TP1	40/-
6BQ7A	15/-	7B7	8/6	28D7	7/-	CY31	11/-	ECH3	26/6	GZ30	9/-			U78	5/-	W729	19/11	TP2	40/-
6BR7	12/6	7C5	8/-	30C1	8/-	D1	3/-	ECH21	23/3	GZ32	10/-	PEN44	26/6	U78	6/-	X24M	24/7	TS1	10/6
6BS7	25/-	7C6	8/-	30F5	6/-	D15	10/6	ECH35	6/6	GZ33	19/11	PEN45	19/6	U107	16/7	X41	15/7	TS2	12/6
6BW6	8/6	7H7	8/-	30FL1	10/-	D77	4/-	ECH42	9/-	GZ34	14/-	PEN46	7/6	U191	16/7	X41	15/7	TS2	12/6
6BW7	6/-	7R7	12/6	30L1	8/-	DAC32	10/6	ECH81	9/6	GZ37	19/11	PEN383	23/3	U201	16/7	X61(C)	12/6	TS3	15/-
6C4	5/-	7S7	9/6	30L15	11/6	DAF91	6/-	ECH83	13/11	H63	12/6	PEN453DD		U251	14/-	X63	9/-	TS4	24/-
6C5	6/6	7Y7	8/6	30P4	12/-	DAF96	8/6	ECL80	9/-	HABC80				U281	19/11	X65	12/6	V30/10P	28/6
6C6	6/6	7Y4	7/6	30P12	7/6	DD41	13/11	ECL82	10/6		13/6	PEN/DD		U282	22/7	X66	12/6	XA101	23/-
6C9	13/6	8D2	3/6	30P19	12/-	DET25	7/6	ECL83	19/3	HL2	7/6	4020	33/2	U301	23/3	X76M	14/-	XA102	26/-
6C10	9/-	8D3	4/6	30PL1	10/6	DF33	10/6	ECL86	16/7	HL23	15/3	PL33	19/3	U329	14/-	X78	23/3	XA103	15/-
6CD6G	36/6	9BW6	15/3	30PL13	16/6	DF66	15/-	EF9	23/3	HL23DD	7/6	PL36	12/6	U339	16/7	X79	23/3	XA104	18/-
6CH6	9/-	9D2	4/-	35A5	21/3	DF91	3/6	EF22	14/-	HL41DD		PL38	26/6	U403	9/-	X109	17/3	XB102	10/6
6D6	6/6	10C1	13/-	35L6GT	9/6	DF96	8/6	EF36	4/-		19/3	PL81	10/6	U404	8/6	XG(1.5)	6/6	XB103	14/-
6E5	12/6	10C2	26/6	35V4	7/6	DF97	9/-	EF37A	8/-	HL42DD		PL82	7/6	U801	29/10	XFD1	18/-	XB104	10/6
6F1	26/6	10D2	12/-	35Z3	10/6	DH63	6/6	EF39	5/6		19/3	PL83	9/-	U4020	16/7	XFY12	9/6	XC101	16/-

ALL GOODS BRAND NEW AND SUBJECT TO FULL MAKERS' GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL SECOND-HAND GOODS OR MANUFACTURERS' REJECTS.

VOLUME CONTROLS

All with Long Spindle and Double-pole Switch, 4/6 each.

10 K 25 K 50 K 100 K

1/2 mg. 1 mg. 2 mg. 2 meg.

METAL RECTIFIERS Full List with ratings free for S.A.E.

DRM1B	13/-	RM-1	5/3	1A486	17/6	14B130	35/-	14RA	1-2-8-3	21/-	18RA	1-1-16-1	6/6
DRM2B	15/6	RM-2	7/6	1A497	25/-	14B261	11/6	(FC31)				(FC16)	
DRM3B	15/6	RM-3	7/9	1A4100	27/-	14RA	1-2-8-2	17/6	16RD	2-2-8-1	12/-	18RA	1-2-8-1</

Transistors for R.F., F-M., T.V. and U.H.F.

Frequencies quoted are approx. cut-off.

SB 078 15-20 Mc/s.....	8/6
SB 305 20-30 Mc/s.....	9/-
SB 231R 40-50 Mc/s.....	15/-
American 2N1727 100-150 Mc/s.....	15/-
American 2N1728 100-150 Mc/s.....	12/6
American T1838 1000-1300 Mc/s.....	25/-
American T1833 1000-1300 Mc/s.....	25/-

SUB-MINIATURE COMPONENTS

Push-pull driver with Sep. Secondaries for transformerless output 8/6.
3 I.F. transformers and oscillator and circuit 83/8.

Smallest possible electrolytics 1/9 each. 1 mfd., 2 mfd., 8 mfd., 10 mfd., 20 mfd., 30 mfd., 50 mfd., 100 mfd., 200 mfd.

Smallest 1/2 watt resistors 5d. each. Miniature 0.1 mfd., 1/4, 0.05, 0.01 8d. values up to 0.05 6d. each.

Miniature slide switch 2/6.

Edgewise Volume controls, 2K., 5K., 10K., 20K., all 2/6 each or 4/6 with Switch.

Set of 8 transistors for superhet in original packets guaranteed. Mullard OC44, OC45, OC81D matched pair OC81. 22.00 the set.

3in. Speakers 3 ohm or 80 ohm 18/6.

2in. Speakers 3 ohm 19/6.

Elliptical Speaker, 7in. x 5in. 35 ohm 19/6.

35 ohm 5in. normal flux 18/6. Hiflux 22/6.

Post & Packing on all speakers 1/6 each.

POCKET LOUDSPEAKER TRANSISTOR RADIO

Available Again at 42/6

READ THESE TESTIMONIALS

Mr. J. Bell, Wolverhampton.
I am writing to express my satisfaction at the standards of your kit for your Pocket 4 Transistor set and also to state that it has come up to my expectations in regard to performance."

Mr. R. Bell, Newcastle-on-Tyne.


"I have built your Pocket 5 Transistor set, I am very pleased with it".

Mr. F. Jackson, Ickenham, Middx.

"I have built the Pocket 4 and am more than pleased with the results."

GOOD RESULTS EVERYWHERE

Nothing can be more disappointing than to find that despite care in making up, your radio just will not work or needs a long high aerial and water pipe earth. We can prove good results in all areas and we guarantee all components for 12 months. Read just a few of the hundreds of testimonials we have received from constructors who have made these sets. Send in confidence. Money refunded if components not up to your expectations. Plans free with parts, or separately 1/6. More details S.A.E.

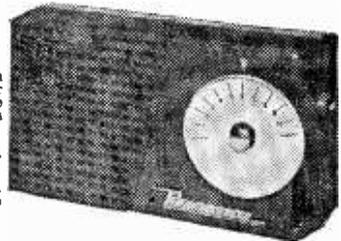

TRANSISTOR AMPLIFIER COMPLETE WITH HI/FLUX SPEAKER

Uses four first grade Mullard Transistors including matched pair of OC81's (with heat sink) on printed board with transformer and connected to Hi/flux 5in. round speaker. Price 23.12.6 complete. Post and packing 2/6. In wooden cabinet with 7 x 4 speaker, 24.17.6. Post and packing 4/6.

Circuit comprises 2 HF transistors reflexed to equal 4 stages. Permanent germanium diode and high gain AF output stage, fitted with miniature speaker proper tuning condenser, volume control and in case with handle as illustrated (less monogram), completely portable. No aerial or earth required. Pocket 4 uses 3 transistors and 1 diode, price 42/6, plus 2/6 post and insurance. Pocket 5 uses 4 transistors and 1 diode and has feedback control. Price 55/-, plus 2/6 post and insurance. Prices are for medium wave models, long or medium versions 8/6 extra.

ELECTRONIC PRECISION EQUIPMENT LTD.

post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road, Eastbourne, marked Department 7. Callers may use any one of the Companies below.

226 London Road, Croydon. Phone: CRO 6558 Half day Wednesday	23 Stroud Green Rd., Finsbury Park, N.4. Phone: AR.Chway 1049 Half day Thursday	520 High Street North, Manor Park, E.12. Phone: IL.Ford 1011 Half day Thursday	42-46 Windmill Hill, Ruship, Middx. Phone: RUSHIP 3780 Half day Wednesday	246 High Street, Harlesden, N.W.10. Phone: EL.Gar 4444 Half day Thursday
---	--	---	--	---

RST

MAIL ORDER DEPARTMENT
811 Streatham Road, Mitcham, Surrey
ALL VALVES LISTED ARE NEW STOCK & Terms C.W.O. or C.O.D. Postage 3d. per valve, MITCHAM 6201

AZ 15/6	EF92 5/-	PCF82	UY85 8/6	6K3G 7/6
B65 8/6	EL42 10/-	VF4B 17/6	VP4B 5/9	6K8GT 12/6
DAF91 7/6	EF94 10/-	PCL82 8/6	W142 9/-	6L1 15/6
DAF96	EL90 8/6	POL83 10/6	W719 7/6	6L6G 7/6
DF91 10/-	EM80 10/6	POL83 12/6	W727 7/6	6L8 12/6
DH19 4/-	EM81 10/6	PEN4A 17/6	X78 21/-	6L19 21/-
DK1 7/6	EY81 10/6	PEN4VA 17/6	X79 21/-	6N7G/GA 7/6
EABC80 7/6	EY86 9/6	PL36 15/-	Z21 12/6	68L1GT 7/6
RAF42 10/-	EY91 9/-	PL36 15/-	Z27 4/6	68N7GT 8/6
EB91 5/-	EZ35 7/-	PL81 14/9	Z152 6/6	68N7GT 8/6
EB91 5/-	EX40 7/6	PL82 8/-	Z152 6/6	68N7GT 8/6
EB91 5/-	EZ41 7/6	PL83 10/6	IR5 9/-	68N7GT 8/6
EBF80 9/6	EZ80 7/6	PL83 10/6	5V4G 4/6	6V8G 5/-
EBF89 7/6	EZ81 7/6	PY80 8/-	5U4G 9/6	6X5GT 5/-
EC21 9/6	FC2 21/-	PY81 7/6	5Y3GT 8/6	757 10/6
ECC33 5/-	FC4 17/6	PY82 8/-	SZ4G 10/-	754 7/6
ECC81 8/-	FC13 17/6	PY83 8/6	6A8GT 6/6	8D3 4/-
ECC83 9/6	FC13C 21/-	R10 21/-	6A8GT 6/6	10LD11 15/-
ECC84 9/6	GZ32 11/6	R19 19/6	SAL5 6/6	12A8H 10/-
ECC85 8/-	H30 5/6	TDD4 17/6	SAM3 4/6	12AT6 9/-
ECP90 12/6	HBC90 9/6	TF22 17/6	GAN5 7/6	12AT7 9/-
ECP82 12/6	HL82 6/6	U142 8/-	6AQ5 8/6	12A07 9/-
ECH42 10/-	HL133D 10/-	U147 7/6	6BA6 7/6	12A07 9/6
ECH81 9/-	KT33C 10/-	U153 9/6	6B6 7/6	12A07 9/6
ECL90 9/-	UABC80 10/-	UABC80 10/-	6B7 7/6	12BA6 9/6
ECL82 12/6	UAF42 9/6	UAF42 9/6	6B7 7/6	12BE8 9/6
EF37A 8/6	UBC41 9/6	UBC41 9/6	6B7 7/6	12BH 15/-
EF40 15/-	UBF80 9/6	UBF80 9/6	6B7 7/6	12J7G/GT 9/6
EF41 9/3	MKT4(5) 4/6	UCH24 8/6	6BX6 6/6	12K7GT 8/6
EF42 10/6	(or 7) 17/6	UCH81 8/6	6C2 5/-	12K8GT 8/6
EF50(A) 4/-	ML4 15/-	UCL83 8/6	6F1 15/6	12Q3GT 8/6
EF80 5/-	MSP4 17/6	UF41 9/-	6F13 4/6	12Q7GT 8/6
EF85 5/6	MU14 9/-	UF41 9/-	6F13 4/6	12Q7GT 8/6
EF88 11/-	MX40 17/6	UF99 8/-	6J5G 4/6	12Q7GT 8/6
EF89 10/-	N142 9/6	UL41 9/-	6J7GT 9/6	50L6GT 9/-
EF91 4/-	N153 11/6	UL94 7/6	6K7 4/6	
	PCC84 9/-	UY41 7/6	6K7G 3/6	
	PCF80 9/6	UY41 7/6	6K7GT 8/6	

SEND FOR LISTS.

Quotations given for any types not listed. Obsolete and old types a speciality.

VACUUM ELECTRONIC LIMITED

KEEPS YOU IN THE PICTURE

WITH THE FINEST REBUILT CATHODE RAY TUBES

12 MONTHS GUARANTEE

12"-14" £4.15.0

15"-17" £5.5.0

21" £7.15.0

15/-

CASH WITH ORDER OR PRO FORMA, ADD 12/6 FOR CARRIAGE AND INSURANCE.

ALLOWED ON RECEIPT OF OLD TUBE

DELIVERY FREE IN LONDON AREA

VACUUM ELECTRONIC LTD.

WRITE PHONE OR CALL

35, SACKVILLE STREET LONDON, W.1
REGENT 6404

NEW 1961 EDITION

**THE GREATEST MONEY-MAKER
EVER OFFERED TO THE RADIO MAN!**

ALL THE CIRCUITS, DIAGRAMS, REPAIR DATA
AND INFORMATION YOU NEED FOR NEARLY

2,700 Models

TELEVISION • RADIO • RADIOGRAMS • CAR RADIOS
TAPE RECORDERS • RECORD REPRODUCERS

Newnes RADIO AND TELEVISION SERVICING provides at instant call, any time, day or night, all the circuits and data you need for almost all the popular TV and Radio sets in use. It is the only complete library of servicing data and worth its weight in gold!

1954-1961. Popular Models—Over 4,400 Pages


Servicing Data for all these makes—Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, Ford Motor Co., Garrard, G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Portogram, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Robert's Radio, Sobell, Sound, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.



TEST IT ON
7 DAYS
FREE TRIAL
ABSOLUTELY
NO OBLIGATION
TO BUY!
Make sure of seeing
this great profit-maker
in the quiet of your
own home!
ACT TO-DAY

**MORE THAN 4,500 CIRCUITS AND
COMPONENT LAYOUT DIAGRAMS
ALSO LATEST DEVELOPMENTS AND
TIME-SAVING HINTS**

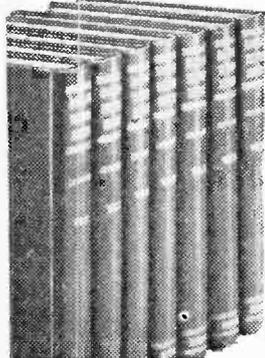**Every purchaser is entitled to 2 YEARS'
FREE POSTAL ADVISORY SERVICE**



Please send me Newnes RADIO AND TELEVISION SERVICING (in 7 volumes) without obligation to purchase. I will return it in 8 days or send 16/- deposit 8 days after delivery, then twenty monthly subscriptions of 16/- paying £16.16s. in all. Cash price in 8 days is £16.

To: George Newnes, Ltd., 15-17 Long Acre, London, W.C.2

Name _____

Address _____

Occupation _____

Your Signature _____
(Or Your Parent's Signature if under 21)

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

RV2U

The A.T.R. Group

Rebuilt and Rescreened

Cathode Ray Tubes

SUFFOLK TUBES LIMITED
1/3 UPPER RICHMOND ROAD
PUTNEY, LONDON, S.W.15.
Tel: Vandyke 4304/5267

MIDLAND TUBES LIMITED
37 GEORGE STREET
MANCHESTER, 1.
Tel: Central 4568/4569

VIDIO REPLACEMENTS LIMITED
HALES STREET
DEPTFORD HIGH STREET
DEPTFORD, S.E.8.
Tel: Tideway 2177/4506

Scotts Radio Ltd.
4 Church Street
Brighton
Tel: Brighton 26891

Weston Hart Ltd.
236/8 Fratton Road
Portsmouth
Tel: Portsmouth 24125

Lawsons Ltd.
36 Cornhill
Bury St. Edmunds, Suffolk
Tel: Bury St. Edmunds 3304

J. H. Sunderland
11 Clements Street
Rochdale, Lancs.
Tel: Rochdale 48484

Wizard Productions
16 Withy Grove
Manchester
Tel: Dea 2772

J. Charlesworth & Son
14 Hightown
Crewe, Cheshire
Tel: Crewe 2535

Taylor's
162 Eastney Road
Milton, Portsmouth
Tel: Portsmouth 35000

Wanda Electrics
9 Manor Road
Gravesend
Tel: Gravesend 3766

Stowmarket Co-operative
Bury Street
Stowmarket, Suffolk
Tel: Stowmarket 51/52

Frank H. Hunt & Co.
Stepcote Hill
Exeter, Devon
Tel: Exeter 56687

H. Knowles
54/56 Chester Road
Manchester
Tel: BLa 9031

Radio Services Ltd.
30 Mona Street
Amlwch, Anglesey
Tel: Amlwch 594

Hi-Lite Ltd.
89 Southbourne Grove
Southbourne, Bournemouth
Tel: Bournemouth 44344

R. Watson
Leathern Bottel
Wavenden, Woburn Sands, Bucks
Tel: Woburn Sands 2027

R.E.S. Ltd.
17/19 Paynes Lane
Coventry
Tel: Coventry 28781

Gwalia Radio & T.V.
Llanstephan
Carmarthen
Tel: Llanstephan 284

J. Wildbore Ltd.
6-12 Peter Street
Oldham
Tel: Mai 4475

Tele-Car Ltd.
66 Osborne Street
Glasgow, C.1
Tel: Bell 1912/3

BEST VALUE

FINEST QUALITY

12 MONTHS GUARANTEE

Practical Television

AND TELEVISION TIMES

VOL. 11, No. 131, AUGUST, 1961

Editorial and Advertisement
Offices:

PRACTICAL TELEVISION

George Newnes, Ltd., Tower House
Southampton Street, W.C.2

© George Newnes Ltd., 1961

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for trans-
mission by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.2.0 per annum
Abroad - - - - £1.0.6 per annum
Canada - - - - 19s. per annum

Contents

Editorial	545
Telenews	546
Some Interesting Features of a Pre-War Receiver	548
How to use Oscilloscopes	550
Transistor Tuners	553
Add-on Colour Tests	555
Servicing Television Receivers	557
Portrait of a Sideband... ..	561
Adjusting TV Tuners	564
Underneath the Dipole	568
A New Mast at the ITA's Lich- field Station in the Midlands	570
Trade News	571
Letters to the Editor	575
Your Problems Solved	579

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television" George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

The Pilkington Committee

FROM time to time notices are received from various organisations concerning recommendations which they are putting before the Pilkington Committee. As our readers know, this Committee is sitting to investigate the position of television broadcasts in all its aspects, but it is becoming evident that its task is not an enviable one. Instead of concerning themselves with matters such as line frequency, colour, and channels, it now appears that they will have to include an investigation of programme material and advertisement copy on the commercial channel, as so many organisations are taking an opportunity of trying to enforce their points of view. Temperance bodies, church and religious organisations, anti-betting, anti-noise and so many others are placing the most comprehensive documents before the Committee, that one wonders whether the latest estimate of the time when their Report is due will not be very seriously lengthened. We were told that it would be received about the beginning of next year, if all these other matters are also to be investigated it appears to us that the more important matters, namely channels available, line definition and colour are being very seriously interfered with, and perhaps it would be as well for the Committee to split its work up into sections, dealing with the most important first, and leaving the remainder for later study. In this way we could arrive at a decision for the future of television as a whole, and this would give both the BBC and ITV the chance to plan their broadcasts for some time ahead, then the contents of the programmes would automatically fall into place,—the probability of an additional channel perhaps simplifying programme planning.

Perhaps arrangements could be made for an interim report to be issued, or some time limit could be placed on the supply of further information and so allow the Committee to proceed with their investigation undisturbed and perhaps shorten the period over which we must wait before their deliberations are finalised.

THE TRADE SLUMP

THE latest figures released by the Radio and Television Traders Association show that there was a fall in sales, which they attribute to the aftermath of the Easter spending spree. Is this in fact, the correct explanation? Could it not be caused by the many conflicting reports which have been published in the National Press concerning line definition and colour, and the resultant doubts which have been raised in the minds of the general public as to the expediency of buying a receiver which might be made obsolete in a very short time? It would appear to us that greater publicity should be given by the two broadcasting companies to the actual position, so as to remove these doubts, and the manufacturers themselves should also commence a publicity campaign at the same time. Our correspondence files show that this is a real factor governing the so-called stagnation or lack of interest in buying, whilst this doubt concerning the life of new receivers still exists.

Our next issue, dated September, 1961, will be published on August 22nd.

Telenews

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of May, 1961, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,932,145
Home Counties	1,578,925
Midland	1,708,999
North Eastern	1,838,275
North Western	1,490,524
South Western	868,522
Wales and Border Counties	687,487
Total England and Wales	10,200,887
Scotland	1,025,300
Northern Ireland	165,875
Grand Total	11,391,863

Outside Broadcast Vehicle for Russia

THE Russian Authorities have purchased the Marconi television outside broadcast vehicle which gave daily working demonstrations during the British Trade Fair in Moscow.

This vehicle embodies latest technical advances, including four Marconi Mark IV television cameras as used by the BBC and other television authorities throughout the world. This is the camera which recently won the engineering award of the American National Academy of Television Arts and Sciences.

Broadcasting Exhibition

THE British Broadcasting Corporation is to present, in conjunction with the National Book League, an exhibition, "Broadcasting: Radio and Television", of books and archives on the history of radio and television. The exhibition will take place from 31st October to 25th November in the Stallybrass Galleries of the National Book League.

Current and out-of-print books, documents and papers from archives, historic BBC equipment, models and BBC publications will be among the exhibits.

Trooping the Colour on Russian TV

ON 10th June the Trooping the Colour ceremony was televised direct to Russia. Mr. Fokin, chief television commentator and head of news for U.S.S.R. Television, expected fourteen million Russians to view the ceremony, for which he gave the commentary.

Beforehand, the cameras overlooking Horse Guards Parade and others at vantage points in Central London, presented a special forty-minute programme

about London for Russian viewers.

Television Transmitting Station for Scotland

A 750ft mast to carry the aerials of the new South-East Scotland television and VHF sound station, which is to be built at Dryden Hill, between Selkirk and Hawick, will be supplied and erected for the BBC by J. L. Eve Construction Co. Ltd.

This is one of several stations which the BBC is building to extend and improve the coverage of its television and VHF sound services.

The South-East Scotland station will serve an area including Galashiels, Lauder, Duns, Selkirk, Hawick, Jedburgh and



Looking at a Marconi Mark IV, 4½in. image orthicon camera, in this picture is Mr. A. H. Victory (centre), Chief Engineer of Television of Iran. Accompanied by his wife, Mr. Victory recently paid a visit to the Marconi works at Chelmsford.

Coldstream. It is expected that the station will be completed by the autumn of 1962.

Advertising by Unit Trusts

ON the recommendation of its Advertising Advisory Committee, and after consultation with the Postmaster-General under Section 4 (5) of the Television Act, the Independent Television Authority has amended its rules about financial advertisements expressly to allow advertisements by authorised Unit Trusts. The advertisements must be strictly limited to the name and description of the Trust, the address of its manager, and an invitation to write to the manager for full particulars of the units available. No person may be shown on the screen during the course of the advertisement.

Additional Officer for Scotland

MR. JOHN LINDSAY has been appointed as additional officer in Scotland of the Independent Television Authority. He took up his appointment on 1st June.

Mr. Lindsay has been associated for many years with a wide variety of BBC radio and television programmes. He is well known as a commentator, interviewer and announcer at the National Radio Show.

Distribution Research in Northern Ireland


A TEAM of experts visited Northern Ireland during June to begin fieldwork on a major research into the distribution of consumer goods in the province.

This survey into the Northern Ireland market has been commissioned by Ulster Television. It is the first comprehensive investigation to be undertaken into distributive channels in Northern Ireland and will provide advertisers with vital information on the Province.

Northern Ireland is not included in the Board of Trade's "Census of Distribution" and the results of the research should make a valuable contribution to the present statistical coverage of the area.

New Director

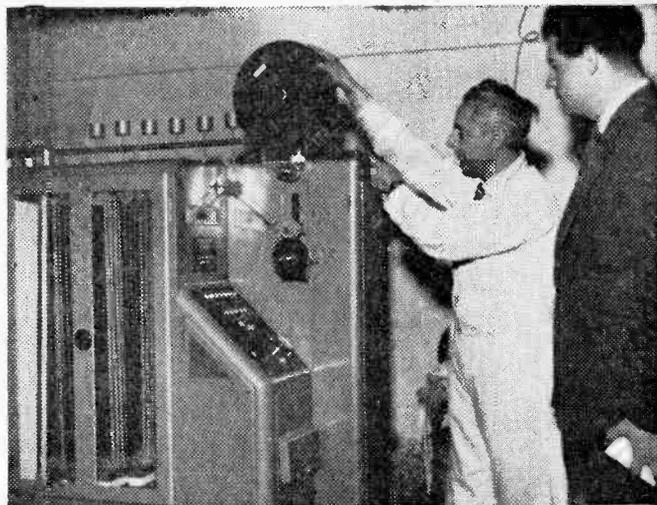MR. C. R. THOMPSON has recently been appointed an executive director of Pye T.V.T. Ltd., Cambridge. Mr. Thompson,



This Lawley film processing machine plays an important part in the production of Westward Television's news programmes.

who is 49, joined Pye in 1930. From 1941 to 1945 he was a civilian Technical Officer in the Royal Air Force, and returned to Pye in 1949, since when he has been Service Manager of Pye T.V.T. Ltd.

Iran TV Engineer in Britain

MR. A. H. VICTORY, Chief Engineer of Television of Iran, recently paid a visit to Marconi's Wireless Telegraph Co. Ltd. He and his wife toured the Marconi works at Chelmsford, Essex. Mr. Victory showed some interest in a Marconi Mark IV 4½in. image orthicon camera, which he saw in the Broadcasting Division.

Weather Service for Airport

AT Idelwild Airport, New York, B.O.A.C. has installed its own closed-circuit television, to provide pilots with weather briefing.

This new weather service consists of daily, and continuous weather briefing on international flying conditions. This improvement in ground operations will undoubtedly result in greater efficiency in weather briefing and in time-saving convenience for pilots.

Television on "Queen Elizabeth" Liner

THE Cunard White Star Company, in conjunction with

Westward Television Ltd. and Wolsey Electronics Ltd., recently carried out a programme experiment during the "Queen Elizabeth's" return voyage from New York to Southampton.

Westward Television Ltd. opened their Axminster transmitters at 7.30 to provide a special programme of welcome to V.I.P. American guests on board the "Queen Elizabeth".

A television set was installed especially for this transmission and a Wolsey Interceptor Broad-side array was erected 150ft high on the uppermost deck.

TV coverage of Archbishop's Enthronement

WHEN Dr. Michael Ramsey was enthroned as the 100th Archbishop of Canterbury, on June 27, eight EMI Electronics image orthicon cameras brought, to the ITV network, complete television coverage of the scene inside Canterbury Cathedral during the two-hour ceremony.

The enthronement posed particularly difficult problems, because of the large area to be covered and the different floor levels.

For the first time in the long history of the Cathedral, modern electronic equipment was housed in the ancient vaults of the Crypt, which was turned into a television control studio for the occasion.

Some Interesting Features of a Pre-War Receiver

IN THE YEARS PRECEDING THE SECOND WORLD WAR, TELEVISION MANUFACTURERS INCORPORATED MANY INGENUOUS DEVICES IN THEIR SETS, SOME OF WHICH ARE EXPLAINED IN THIS ARTICLE.

By M. B. Allan

ALTHOUGH the basic design of television receivers has changed very little over the past 25 years, some early models used circuits which, in detail may appear strange to eyes used to scanning post-war designs.

Misplaced Video-amplifier

For example we are used to finding the vision detector or demodulator followed by a video amplifier. Therefore the circuit shown in Fig. 1 may appear most unorthodox, perhaps to some unworkable. However, it did work and very well since the receiver in which it was used was operating efficiently until quite recently. The circuit shows a full wave detector (following a double side-band TRF amplifier), feeding the CRT grid and sync separator directly.

Since there is no H.T. at the diode cathodes, the need for an isolating sync coupling capacitor did not arise. The brilliance control biased the CRT cathode from zero to 120V. The use of fly-back suppression (C54-R56, Fig. 1), is also an interesting point, bearing in mind that the particular receiver was marketed in 1938. It was also quite common practice to omit the audio stages and loudspeaker! The audio signals from the detector were taken to output terminals or via a screened lead for connection to the pick-up sockets of a radio receiver. This had several disadvantages since if a fault occurred in the radio, there was no TV sound. The radio had to be kept near the TV receiver in order for the sound to issue from approximately the right place and of course both receivers had to be on at the same time.


The Cathode Ray Tube

The tube is a tetrode with quite low first anode voltage, 165V, and an EHT for the final anode of about 3.5kV. The EHT is mains derived from a special winding on the mains transformer and rectified by an HVR2 half-wave rectifier.


Focus control is achieved by a normal coil on the tube neck, shunted by the focus control and a series resistor, wired in the H.T. negative return. Most of the biasing is derived from this circuit which also includes two smoothing chokes.

Smoothing

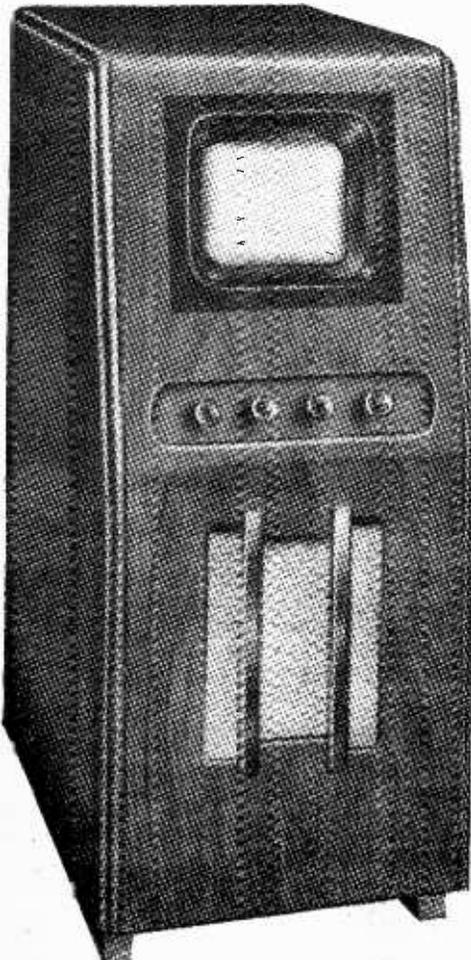These latter items are necessarily quite bulky since the smoothing capacitors are three 16 μ F sections of a single 350V electrolytic block. The H.T. line to the frame timebase and line oscillator are further smoothed by 2 μ F capacitors. Thus the total smoothing capacity is very small compared to modern standards.



A Cosmor television receiver of 1939.

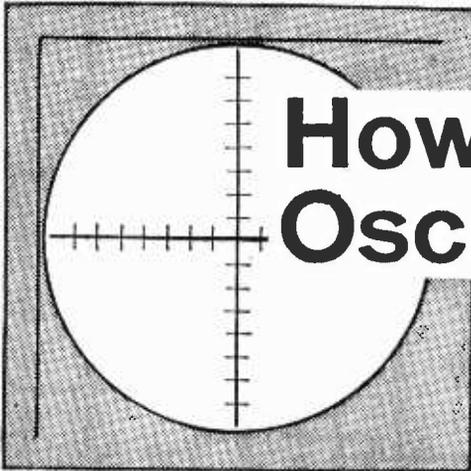

How to use Oscilloscopes

By D. R. Bowman

CONSTRUCTING AN ADVANCED INSTRUMENT

(Owing to lack of space, this article was omitted from the July issue, and so is continued from page 455 of the June issue.)

PREVIOUS articles have outlined the uses of the oscilloscope, and an indication has been given of the requirements of an instrument. The recent article by H. Peters (June and July issues) described the construction of a simple and effective instrument, and its limitations were stated. Here, a somewhat more advanced instrument will be described, which can use some of the components specified in the above article. This means that the cost of development will be relatively small for a constructor who, having made the simpler oscilloscope, wishes to improve on it later.

The timebase generator consists of a Miller valve which is connected as a transition oscillator.

One big advantage of using the Miller effect is the very precise linearity obtained at even the highest frequencies. This circuit is arranged to give only a relatively small voltage output, and the sawtooth is amplified by a two-valve push-pull stage before application to the X-plates of the cathode ray tube. As a result of the application of push-pull deflecting voltages the average potential of the X-plates is kept sensibly constant during scan and flyback, thus eliminating, or at least minimising, deflection defocusing which would otherwise prevent focus being obtained all along the trace at the same time. As direct coupling is used between amplifier and X-plate, a simple potentiometer control enables an X-shift readily to be obtained without the need for readjustment of the focus.


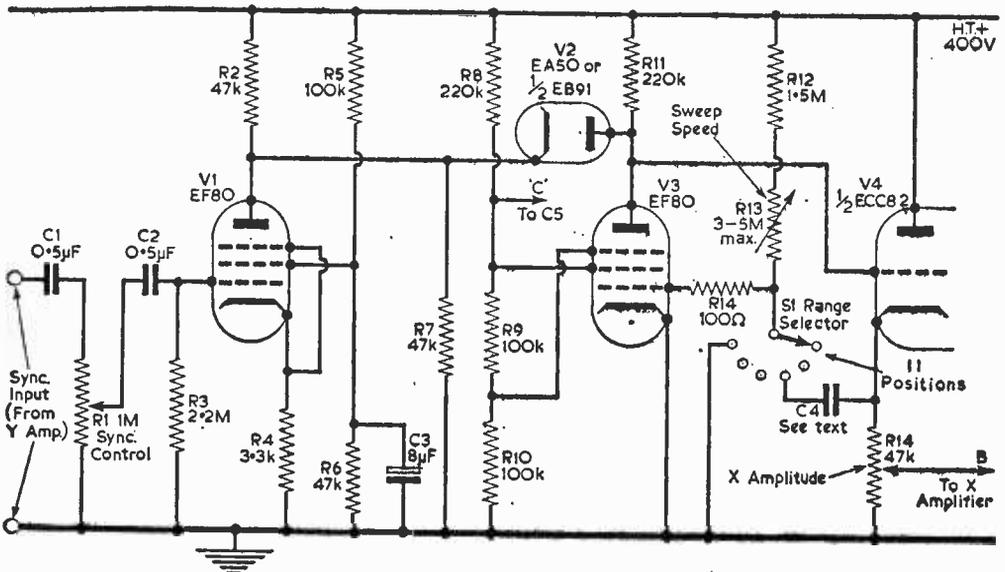


Fig. 9.—The circuit of the Timebase generator.

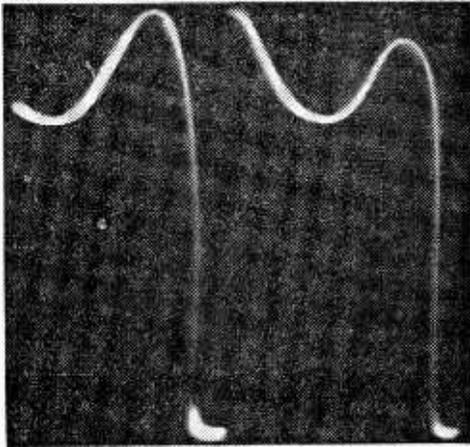

The oscilloscope trace of a screen pulse (for fly-back blanking) : $f=100kc/s$.

One of the chief problems with the Miller sawtooth generator is the maintenance of a rapid flyback at the higher frequencies. Too much should not be made of this drawback; although the whole of the leading edge of a pulse can be lost because it occurs during the flyback period, all that is needed is to display two pulses rather than one and the whole pulse may then be examined. However, a long flyback does mean the flyback trace itself may be visible, or may turn up unexpectedly when a long exposure is made for photographic purposes. Accordingly, a cathode follower circuit is used to reduce flyback time, and by using a pentode as a limiter, provision can be made for 'automatic' synchronisation.

The action of the Miller-transition sweep generator will be familiar to all readers, and the only points in which Fig. 9 differs from the well-known circuits are as follows. First, direct coupling is used between suppressor and screen. This avoids having to change the coupling capacitor as the speed of the timebase generator is altered, and helps in obtaining a quick flyback. It is also possible to omit the coupling resistor R9, relying on stray coupling inside the valve, but results are more predictable with EF80 if it is included.

Secondly, Miller feedback is applied via the grid-cathode conductance of V4, the cathode follower. This can occur because the grid of V4 will be always a little positive relative to the cathode during the sweep—the run-down of V3 anode voltage. When the valve V3 is passing its maximum current, at the end of the sweep Miller feedback ceases—the valve is said to be 'bottomed'. The H.T. now dives V3 grid positive via R12 and R13. The capacitor C4 now changes, but its time-constant is dependent only on the input resistance of V3 under grid-current conditions and the output resistance of the cathode-follower V4; in all the resistance is only of the order of 1k and the changing time is very short. The resistor R14 does not add appreciably to this—R14 is included to avoid parasitic oscillations that may occur under certain circuit conditions—

one prototype built by the writer was found to emit radiation at about 70Mc/s—heavily frequency-modulated by the timebase frequency. Similar grid-stoppers are added in the amplifiers. The flyback is fixed at a definite value by the above circuit, and hence there is a progressive decrease in the ratio of sweep to flyback in each switched range as the frequency is increased by varying R13. This is quite unimportant in the circuit given.

A negative pulse is obtained at the screen, of good square shape, on the flyback. This is how-


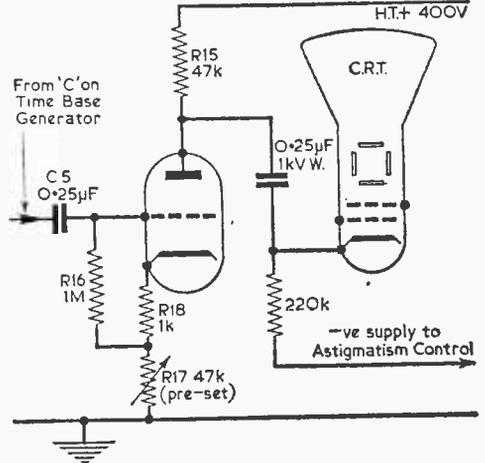


Fig. 10 (above).—The cathode connection to the CRT, with flyback blanking.

Fig. 11 (below).—The circuit of the X-amplifier, including the shift control.

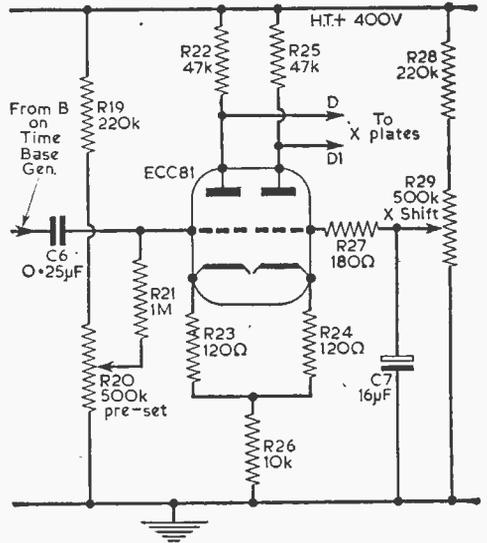

ever of insufficient voltage to give good blanking by application to the grid of the cathode-ray tube. It is hence applied to the grid of one half of an ECC82, and the positive pulse at the anode of

this valve is applied to the cathode of the cathode-ray tube. The lead from connection C in Fig. 9 is the take-off point for this. Fig. 10 shows the circuit—R17 is made adjustable, a pre-set control—so that the D.C. potential of the anode can be altered. It does not need adjustment, once set, so is not brought out to the front panel of the instrument.

Suitable values for C4 are as follows:

10c/s	—	50c/s	—	1 μ F
40c/s	—	250c/s	—	0.25 μ F
200c/s	—	1.5kc/s	—	0.1 μ F
1kc/s	—	5kc/s	—	0.02 μ F
4kc/s	—	20kc/s	—	0.005 μ F
18kc/s	—	35kc/s	—	0.001 μ F
30kc/s	—	100kc/s	—	250pF
80kc/s	—	250kc/s	—	75pF
250kc/s	—	750kc/s	—	25pF

- (a) Set sweep generator to about 2kc/s and by manipulation of the controls obtain a trace on the tube;
- (b) Rotate R20 and R29 (one with each hand) and adjust for maximum width of trace; if necessary, reduce the input by varying R14.

R20 is a pre-set control, and should only need adjustment at infrequent intervals to correct for ageing of the valves. R19, 20, 28 and 29 should not be put anywhere in the case where they will become hot, and should be of ample wattage rating (1W minimum).

Hum may be picked up by the anode circuits, so if any great distance separates D and D1 from the CRT, low-loss co-axial cable, semi-air-spaced, should be used to make the connections, the outer of the cable being earthed to chassis.

The Y-amplifier

The Y-amplifier must be constructed so that all circuit capacitances are kept as small as possible. Since voltages of the order of 250 maximum may

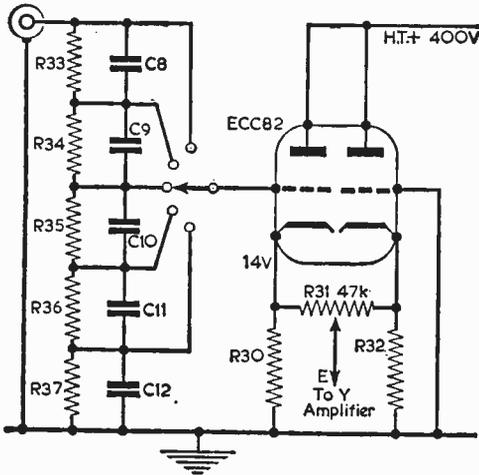


Fig. 12.—The input attenuator and cathode-follower input to the Y-amplifier. R30 and R32 are equal in value (2.2k) and should be matched.

A spare connection is allowed for, since it may be desirable to experiment a little at the higher frequencies to get the correct coverage of frequency, especially if only a 3M variable resistor is available for R13. Calibration of the ranges will be required in any case. The final connection connects the grid of the Miller valve to chassis to put the sweep generator out of operation so that D.C. measurements may be made, or an external timebase generator used.

The X-amplifier

The X-amplifier produces a push-pull voltage for driving the spot. Its bandwidth does not need to exceed about 500kc/s, since sweep at higher frequencies is very seldom required. The required gain can thus be obtained with a single valve. Direct coupling is used between the anodes of the X-amplifier and the X-plates of the cathode-ray tube. D and D1 in Fig. 11 connect direct to the X-plates.

R20 and 29 have to be adjusted together to obtain the correct conditions. The procedure is as follows:

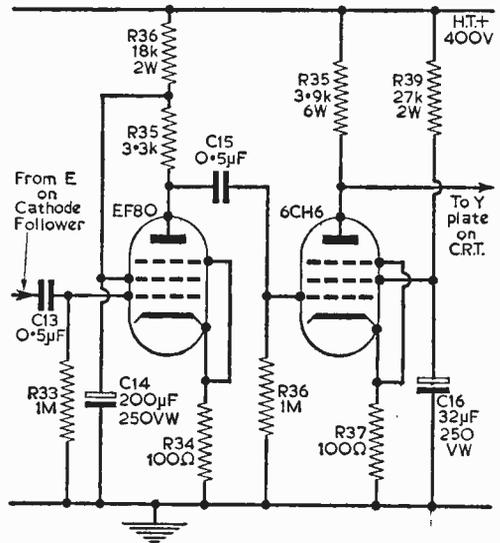


Fig. 13.—The Y-amplifier circuit: A.C. coupled only. The gain is about 800, and the bandwidth is approximately 3.4 Mc/s.

need to be displayed, an input attenuator of flat frequency response is provided. The circuit diagram is shown in Fig. 12. The values of R33 to R37 are 100k each. C8 to C12 are each 5pF, on the assumption that the usual values of stray capacitance emit. Care should be taken to keep these strays to a minimum in constructing the switch. The attenuator should be placed as near the co-axial socket as possible, and so should the ECC82 cathode follower. The connection E should be of plain insulated wire well spaced out from anything connected to chassis, and may be several inches in length.

Fig. 13 shows the first of the two Y-amplifiers which may be built.

(To be continued)

THE uses to which modern transistors may be put are forever increasing. This article describes the development and operation of two television tuners—both evolved in the U.S.A.—which employ transistors.

Transistor Tuners

The swift development of the transistor has allowed designers, in all fields of electronics, to use them in equipment which at one time had to employ valves, as the requirements of the circuits were beyond the scope of the transistor, owing to its limited capabilities. Now, however, the transistor is being used more and more in place of valves, and the transistorised TV turret tuner is accepted, in the USA at least, as standard equipment on some television receivers.

A lead in making transistorised TV tuners was taken by the Philco Corporation of America when, two years ago, their designers began work on

near to that of valve types and the noise figure remained only slightly higher.

Engineers of the Lansdale division of the Philco Corporation made the first transistor tuners by replacing valves and most of the circuitry of a Standard VHF tuner with transistors; keeping the turret and most of the coils.

The single channel circuit of one of these early experimental tuners is shown in Fig. 1. The R.F. signal from the aerial passes, via a 75Ω coaxial cable, through an F.M. trap to earth, and through a 45Mc/s trap in series with the input circuit, to the base of a T1694 transistor. This transistor is

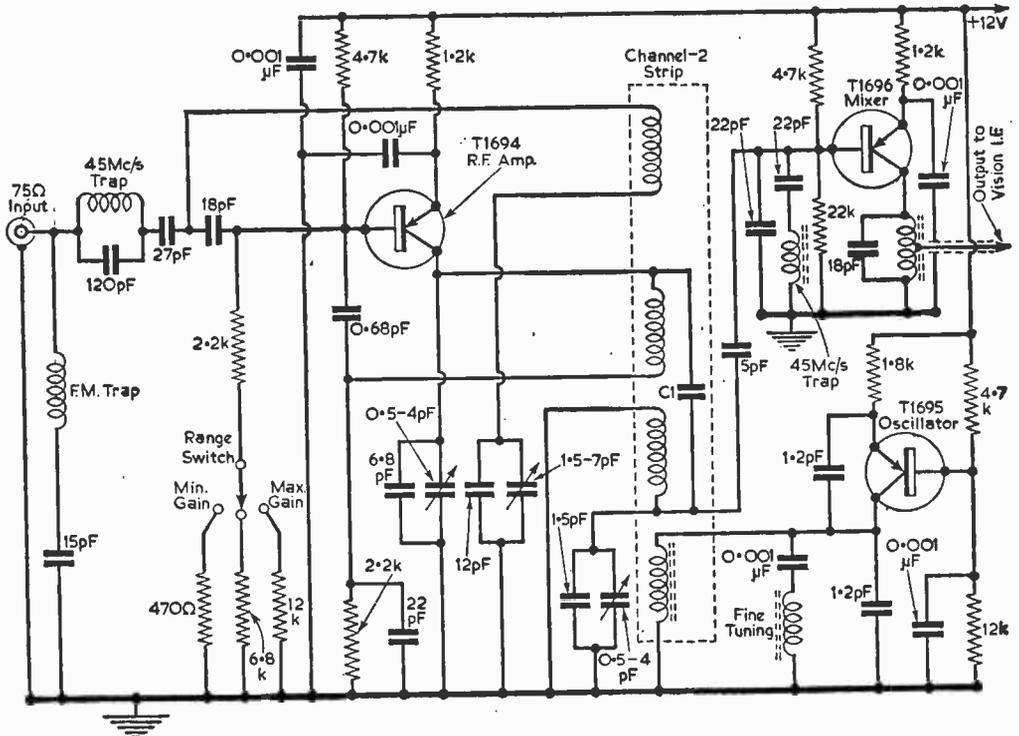


Fig. 1.—An early transistor tuner, designed by Philco.

transistor television receivers, including VHF tuners. They also designed F.M. tuners using transistors.

Although as yet not as suitable as valves, the gain of early transistor tuners came remarkably

the R.F. amplifier which uses a common-emitter circuit with fixed neutralisation. The output signal is coupled inductively and injected into the base of the mixer. The opinion of C. R. Gray of Philco, on this form of coupling, is, that, although straight-

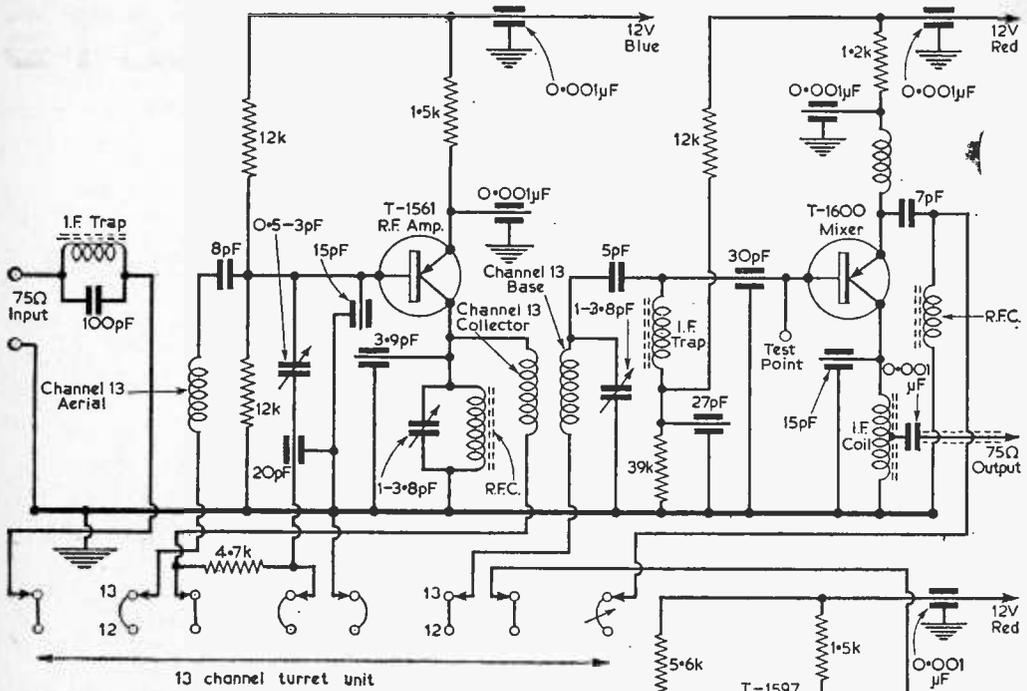


Fig. 3.—The circuit of the Sickles Mark 6T VHF tuner.

forward emitter injection produces slightly higher mixer conversion gains, it is difficult to employ this in a turret tuner, as unwanted coupling is obtained, through the coils. One of the means taken to overcome the lower mixer conversion gains is the 45Mc/s series trap to the base of the transistor, which eliminates 45Mc/s degeneration in the mixer. In this early Philco design, the local

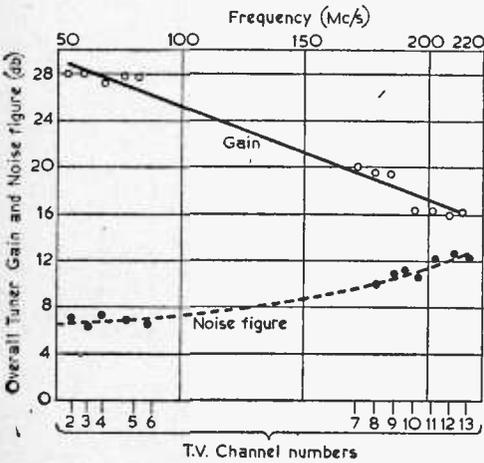


Fig. 2.—The gain and noise figures of the tuner shown in Fig. 1.

oscillator, a T1695 transistor, was specified to deliver a minimum of 1.5mW of power at 257Mc/s (for channel 13). The mixer was planned to give high conversion gain with a minimum of 1.0mW of power injected by the local oscillator. The overall gain and noise figures are shown as a graph in Fig. 2. There are obviously two groups of channels to consider; 2 to 6 and 7 to 13. The low-band VHF channels—2 to 6—have an average gain value of about 28dB, with a noise figure of 7dB. As might be expected, channel 10 to 13 have much lower gain figures, and higher noise figures; approximately 17 and 13dB respectively.

In the tuner shown in Fig. 1, a manual gain switch is employed. The three resistors of this range switch are used for base bias.

(Continued on page 563)

ADD-ON COLOUR TESTS

(2) COMPLEMENTARY COLOURS

By A. O. Hopkins

(Continued from page 509 of the July issue)

Saturation

THE ordinary meaning of saturation—to be too full to accept more—does not apply in colorimetry. Instead it means “absence of white”, which seems difficult in view of rod function and brightness curves. What is this mysterious “white” which can desaturate a colour—without taking anything from it?

Very simply, a single primary or any combination of two are *always saturated*, simply because the *third primary is missing*. The saturated colour does not need to be bright or vivid in hue. For example, green of medium brightness remains a saturated colour when strong red is added to form orange.

Desaturation would occur if blue were added to the orange. If the blue were weak it would form a

three primaries are required, and for best results they should be “gelatin” filters such as Ilford’s Tricolour Red (205), Blue (306) and Green (405), specially made for colour experiment. For these stiff filters a simple slip-in frame as in Figs. 2 and 3 can be easily added in front of each lens. Some Cellophane wrappings are in good primary colours, and are worth trying singly or in pairs over each lens. For example magenta and yellow give a red filter for a quick test, while blue and yellow give green.

If the primary colours are balanced, the central area on the screen will be white. If tinged you will know which colour is too strong, and that filter can be partly covered by a piece of card. When central white is obtained the three overlapping areas about it will each be in the colour complementary to the primary colour opposite it on the screen, as shown in the table:—

Primary	Complementary
Blue	Yellow (G + R)
Green	Magenta (B + R)
Red	Cyan (B + G)

Colour Sectors

If you have only one lens you can still test the colour balance of your filters. Form complementary colours, and test whether the three primaries will reproduce every colour with which you test them. Fig. 8 shows how the three filters share the lens as equal sectors of a circle. Each filter receives $\frac{1}{3}$ of the light from an “opal” lamp mounted horizontally. Cut one corner of each filter to the wide angle of 120° , and mount them to overlap slightly. They are best mounted as a “sandwich” between two cut-out cardboard frames.

A white card about two feet away will receive a circular image of the lamp. To form colour combinations, a postcard partly covering the lens at different angles will admit a different colour for each position. The pure primaries and complementaries may be seen by dividing the card with an angle-cut of 120° to the centre to form two masks. The larger mask will just cover two primaries, admitting the third. The smaller mask covering each primary in turn, will separate the complementaries. Intermediate colour combinations will appear as each mask is turned about the lens centre.

Picture Tests

The coloured magazine covers previously tested can now be “reproduced” in their exact colour by either of the three-colour projectors. If the room illuminant is similar, on switching if off and switching on the projector the colours in the picture should not change when all filters are exposed.

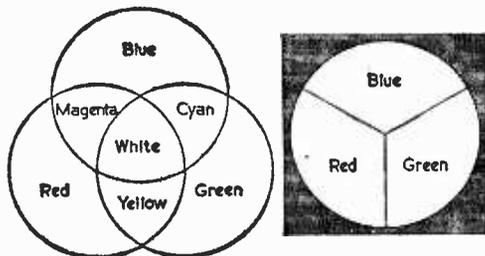


Fig. 7 (left).—Additive colour primaries superposed to show the formation of white and three complementary colours.

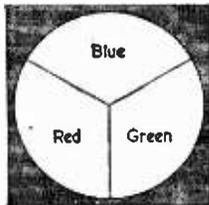


Fig. 8 (right).—A primary colour separation filter for use with a single lens—it consists of three equal sectors mounted in a frame.

white level with part of the green and red, giving a pastel tone to the predominant orange. More blue would make the orange paler. Blue as strong as the red could not raise the white level above the green level, so the blue and red excess would form purple made pale by the medium brightness white.

Complementary Colours

With the “additive colour” effects of the three primaries understood in theory, several experiments can be made with inexpensive home-made apparatus with a view to testing whether the add-on principle could provide a practical colour system for current TV transmission.

If three similar lenses (cheap “reading glasses” will do) are available, an “opal” lamp mounted horizontally behind each, and a simple light-proof box with three openings for them will make a triple-projector. The three circular lamp images can be made to overlap as in Fig. 7 by adjusting the lamp-holder positions. Colour filters in the

As with the two-colour tests, the pictures should be illuminated in each primary in turn. Of the three "colour positives" obtained, the green will be found to give best contrast and most natural rendering of light and shade. It will not be difficult to visualise it as a monochrome picture on a TV screen. Now admit the blue and red light from the projector, virtually "adding on" (by illumination) two colour positives, to complete the picture in full colour.

Colour Wheel

If you have made the three-lens projector, some very simple masks will enable you to project a nine-colour wheel image. First cut three pieces of cardboard to leave wide-angle sectors of 200° as shown in Fig. 9(a). Cut six pieces of tracing paper and fix over each mask to overlap each side of the open sector by 40° . A touch of grease or vaseline will make these small sectors translucent. A clear sector of 120° is left ($360-160-40-40$). With the colour filters in place over the lenses cover each with a sector mask set mutually at 120° to the others. Focus the three primary images to superpose in sharp registration, and the colour wheel will show nine sectors in distinct hues ranging through the spectrum from blue to red and back through magenta and purple as illustrated in Fig. 9(b). Unfocused, this projector will throw white light to your screen.

Newcomers to colour may wonder what has happened to "brown". Well, brown is really a whole group of hues and shades, but always contains green and red. Unless desaturated (made greyish) by blue, brown is merely dark orange or dark yellow ("dark" meaning little light), as experiment with your projector will show.

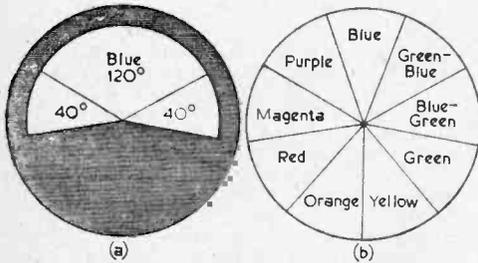


Fig. 9.—A nine-colour wheel. Three primary images are superposed to form the wheel on the screen. One positive mask is shown.

Colour Focus

Serious experimenters who have scanned monochrome film or slides for closed circuit TV may have wondered how to combine the three primary images of a three-colour scan. They will know that the three scans can be made on one CR tube or on three, and that ordinary monochrome tubes can be employed. It is clearly an advantage if the optical system can be tested on a well-lit scene or

colour transparency, but three lenses with filters cannot bring their focused images to coincide on a screen. To bring the three diverging axes together three pairs of reflectors can be used, but this complication is not attractive.

I have simplified the optical arrangement to employ only four reflectors, and combine three of them with lens and filters for easy handling. Fig. 10 shows the arrangement in diagram, including a convex reflector positioned on the "normal" or main axis of the viewing screen and with its back to the focused scene. I group lens, filter and reflector (a hand-bag mirror does nicely) as a "sandwich" to form a compact optical unit for

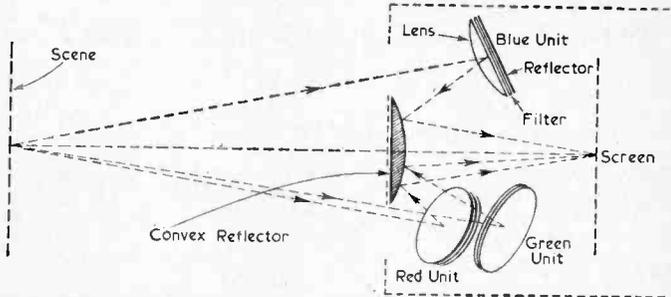



Fig. 10.—Colour focus camera; the focused scene is analysed into three primaries and combined on the screen. The colour units are optical "sandwiches" of lens, filter and reflector. The convex reflector collects and registers the coloured rays.

each colour. Each unit is actually a magnifying reflector, doubling the power of the lens. I mounted the three units at equal spacing round a circular plastic frame (which originally held a mirror), clipping each to a plywood holder with a stiff hinge connecting it to the frame for easy adjustment. The hinges had one-screw fixing to give "universal" movement to the units. The convex reflector, collecting light from the three units, must be firmly fixed to a base, and so must the frame holding them. A piece of half-inch board is a suitable base, and the viewing screen, preferably a piece of "flash opal" glass, can be mounted to slide along this for easy focus. A cardboard box, with open back extending to "hood" the screen, and three openings in front of the lens units, will be adequate for this colour-focusing camera. The paths of the diverging and converging axial rays are indicated in the diagram, and the relative size and shape of the box is shown in outline.

To test the efficiency of this method a well-lit scene or colour transparency may be focused with the three units so that the primary images coincide. If colour scanning is tackled later on, the three flexibly mounted units will easily collect and register the three scans however they may be traced on CR tube or tubes.

Less experienced readers will, I hope, feel that the mystery of colour is now dispelled, and that a profound knowledge of optics and a well equipped laboratory are not essential if new ideas are to be tested. Principles upon which great inventions depend are simple, and television is waiting for a new principle, not complicated apparatus, which will lead to the development of a colour system which everyone can afford. ■

Servicing Television Receivers

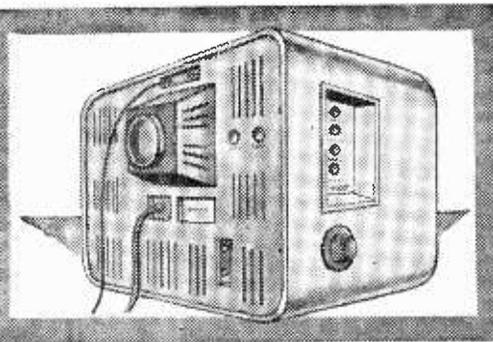

No. 70—THE REGENTONE TR177 AND ASSOCIATED MODELS By L. Lawry-Johns

(Continued from page 522 of the July issue)

THE frame oscillator consists of a multivibrator circuit employing the triode sections of V13 (PCL82) and V7 (PCF80). The frame amplifier is the pentode section of V13.

Bottom Compression

This is normally caused by a low emission PCL82 (V13), but if lack of width is also

compression after the height control has been adjusted to compensate for the initial loss of overall height.



When the height of the picture is reduced equally top and bottom, check R59 (820k).

Distorted Frame Scan

When one section of the picture is vastly distorted or stretched with respect to a remaining narrow strip, check the linearity controls (500k each) which sometimes become o.c. at one end of the track. When this happens, it is sometimes possible to restore normal conditions by rewiring the defective control so that only one end and the centre tag is in use at a time.

Frame Hold

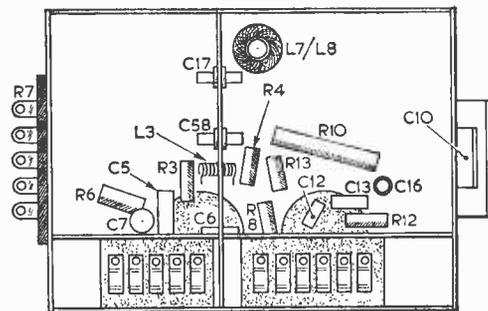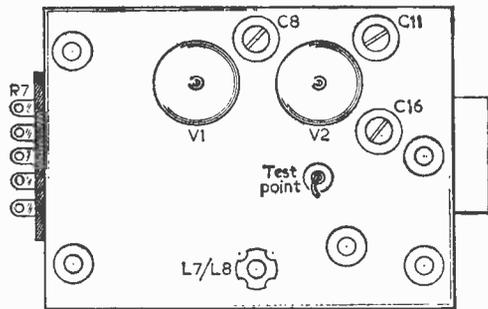If the hold control is at one end of its travel the 680k resistor wired from the hold control to pin 9 of the PCF80 (V7) should be checked. This sometimes "goes high", putting the hold outside the range of the control. Also check V7.



(Left).—These two diagrams of the tuner unit were included in last month's issue, but it has been found desirable to repeat them with this instalment.

experienced, check the H.T. as the PY32 could be responsible.

If the PCL82 is in order, and the H.T. is normal check C89 (100µF 25VW), which sometimes dries up or becomes o.c. This results in current feedback, which appears on the screen as bottom

If the picture rolls up or down but will not lock securely, the OA71 (MR3) interlace diode should be checked and, if this is not at fault, the 0.01µF feed capacitor (C77) is the next suspect.

Erratic Hold

If the setting of the hold control is frequently changing, necessitating constant adjustment, the control itself (R64 1M) should be changed.

Heater Chain

The heater circuit is quite conventional, all the heaters being in series in a single chain. Quite obviously if one heater becomes o.c. the entire heater chain will be broken and no valves will light up. It is then necessary to trace the mains voltage through the chain until the break is located at one valve base. A replacement valve should then restore normal conditions. It is not necessary to use a voltmeter (when the set is on) or ohmmeter (when

the set is off) to trace the break; a simple neon screwdriver serves this purpose, and the following procedure should be adopted when using a neon. With the receiver switched on touch the neon to chassis. It should not light. If it does, reverse the mains plug or wires. Then apply the neon to R91 mains dropper to ensure that the mains is applied to this point (if not, check the 1A fuse and on/off switch, mains cable, etc.). Having ensured that the mains is present at the dropper, check that it is present at all tappings (one section could be o.c.) to the white lead. Then follow to the thermistor, thence to the valve chain, PY32 pin 7, then pin 2, PY81 pin 4, then pin 5, PL81 thence through the heater chain where all heater pins are 4 and 5 except, of course, for the PY31 (2 and 7), the EB91 (3 and 4) and the tube (1 and 12).

The chain terminates at the tube, and if the neon lights at pin 1 and not at pin 12 the tube heater is open circuit. In this case the break can sometimes be welded by applying a high pulse voltage from a fairly low impedance source (such as the top cap of the PL81) to pin 12, with pin 1 connected to chassis (the base socket being removed, of course).

Defects in the heater circuit are not confined to an open circuit, which results in the whole chain being out of action. A heater-cathode short in a valve will result in a heavy current flow through those valves preceding the defective one in the chain, with the remainder being unheated. For example, should V7 develop a heater-cathode short in section A, the heater current flow will be through the dropper, V10, V9 and V8, resulting in these valves lighting up very brightly, possibly sustaining damage, blowing a heater or causing heater-cathode shorts in one or all three, and then causing the 1A fuse to fail. Therefore, when the fuse is found to be blown it is prudent carefully to observe the behaviour of the circuit when a replacement is tried, with one hand on the on/off switch. The correct procedure is, of course, to check the circuit for shorts before fitting a replacement fuse.

Tube Troubles

Quite a number of AW43-80 tubes seem to fail owing to an impaired vacuum, which results in a purple glow in the gun assembly, and perhaps

arcing between the electrodes. Replacement is the only cure for this condition.

Focus

The focus is preset; the focus electrode is brought out to pin 6, and the lead from this may be connected to pin 10, pin 9 or pin 12 on the tube base, whichever gives optimum focus.


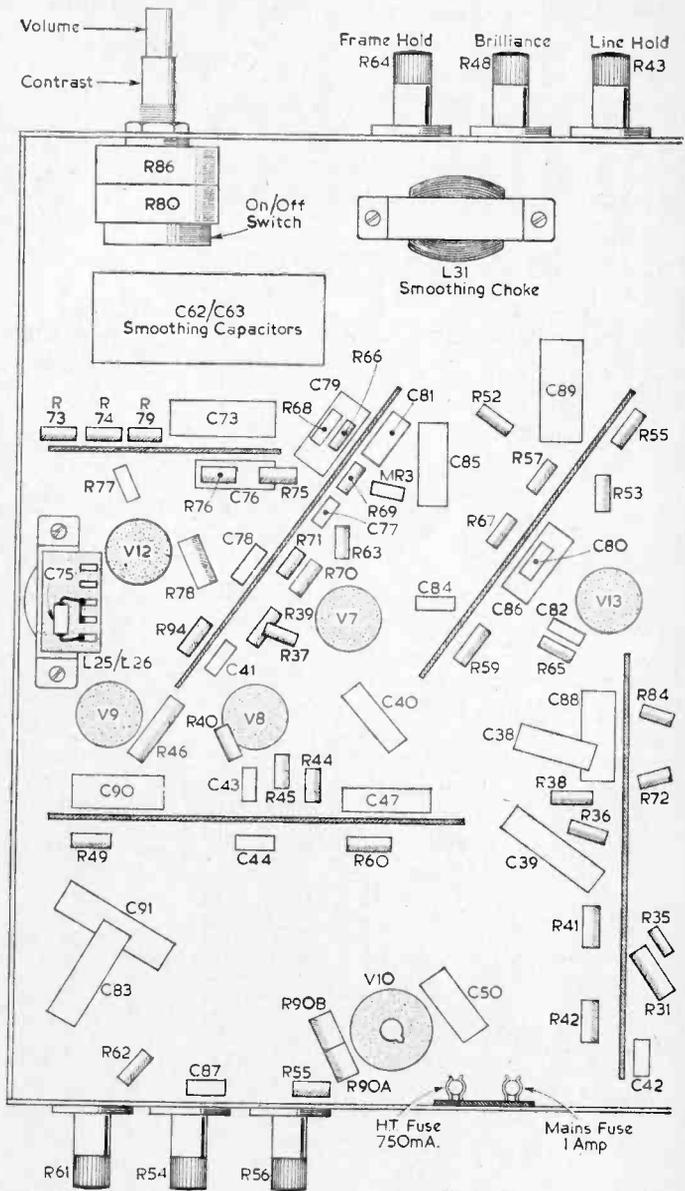


Fig. 6.—The underchassis view of the receiver.

BRAND NEW AM/AF (V.H.F.) CHASSIS AT £14

Tapped input 200-225 v. and 226-250 v. A.C. ONLY. Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture. Dial 1 1/4 x 4 in. in gold and black. Pick-up. Extension Speaker. Ae., E., and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., FM., and Gram. Aligned and tested. With all valves & P.O. Transformer. Tone-control fitted. Covers 1,000-1,900 M.; 200-500 M.; 88-98 Mc/s. Valves E230 rect. ECH81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit chassis, 47/6 (post 3/6). 10 x 6 in. ELLIPT. SPEAKER, 20/- TEHRMS:—(Chassis) £5.0.0 down—and 5 monthly pymts. of £2, or with Cabinet and Speaker £5.0.0 down and 6 monthly pymts. of £2.

(carr. paid)

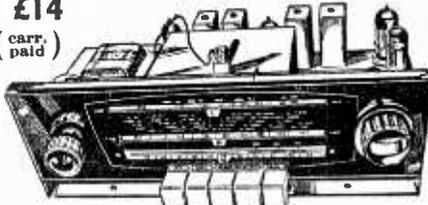


BUYING A NEW COMPLETE V.H.F./A.M. RADIO—VALUE OVER £20 OUR PRICE RADIO? SAVE ££'s



£13.10. (Carr. paid) Brand new set by famous maker, in superb walnut cabinet (size 19 x 8 1/4 x 14 in high) 3 wave-band, Med., Short and V.I.F. (F.M.). Mains input 200-250 v. A.C. Ferrite rod aerial or A.M. Controls: volume on/off, tone, tuning, w/change, Gram and ext. speaker position provided. 5 valves and metal rectifier. Ready to use. Fully guaranteed. Terms available.


STEREO AMPLIFIER £4.15.0.
d. & p. 3/-.

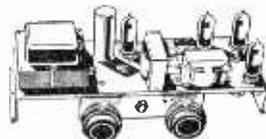

Brand new. 200-250 A.C. Tone and volume controls each channel. E280; ECC83; and 2-EL84; giving 2 x 4W. Size 12 x 3 1/4 x 3 1/2 ins. O.P. Trans. for 2-40 speaker. Separate on-off switch to allow balancing to remain set. Monaural push/pull amplifier giving 8W same price.

SAVE 10/- Swiss made Unic Shaver operating from 1.5 v. battery, usual price 59/8. Our price, 50/-. Including battery. Not a toy, but a shaver (carr. paid). Uses standard U2 cell.

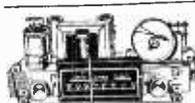MAINS TRANSFORMER. 6.3v 1A and 200 v. 30 ma. 7/- (post 1/6)



SELF-POWERED VHF TUNER CHASSIS

Covering 88-96 Mc/s Mullard permeability Tuner Dims. 10 1/2 x 4 1/2 x 5 1/2 in. high. ECC85, EF91, EF91 and 2 diodes. Metal Rectifier. Mains transformer. Fully wired and tested. Only £7.14.0 (carr. pd.). Room dipole 10/- 300 ohm twin feeder 6d. yd. Tuner without power pack £6.14.0 (carr. paid).

£7.14.0 (carr. pd.)

"READY TO USE" ITA CONVERTER
Direct switching ITA to BBC, metal rectifier, co-axial plug. Can be fitted in 5-10 mins., and needs no alteration to your set. ALL AREAS. ALL SETS. ALL CHANNELS. 12 months' guarantee (3 months on valves). Balancing control on ITA. 3 valves. Switch position off-ITA-BBC. Bakelite moulded cabinet 8 1/2 x 4 x 6 in. 70/- (3/- P. & P.).



PANEL OF 7 POTS

10 x 1 1/2 in.—4 x 1M & 3 x 2M 4/- (post 1/-)



6 DIFFERENT PRE-SET POTS. 5K to 500K 3/- (post 1/3).

Delivery by return. C.O.D. 2/- extra. All new goods unless stated. Send 6d. for NEW 20-page catalogue.

POSTED ORDERS TO CAMBERLEY PLEASE
58A HIGH STREET, CAMBERLEY, SURREY. Tel. 22761
56 Stokes Croft, Bristol, and 247 NEW RD., PORTSMOUTH

GLADSTONE RADIO

(Camberley closed Sats.. Bristol & Portsmouth closed Weds.)



HENLEY SOLON
Trade Mark

Best electric soldering irons in the business—first choice with Industry for over 25 years. Full range available. 25 watt model illustrated. For leaflet write:

AEI CABLE DIVISION

Associated Electrical Industries Limited
Distribution Equipment Sales Department,
145 Charing Cross Road, London, W.C.2.
Tel. GERrard 9797.



"SABRINA"
STILL WELL IN FRONT

LOWER PRICES for 12 Months guaranteed tubes.

COMPLETELY REBUILT

ALL TYPES (including electrostatics)
12" to 17", One Price **£5.10.0** (C.W.O.)
21" also available at **£8.0.0**

Including Free Passenger Transit and Insurance. (Old tubes not required.)

BRAND NEW TUBES

2 Years guaranteed.
(17"—70°, 90° & 110° **£10.** (Elec. focus 10 gns.)
30/- on old tube, trade supplied.

SABRINA C.R. TUBE CO.
Electron Works, North Bar
BANBURY, OXON
Telephone 2390

RADIO BARGAINS

SIGNAL GENERATOR



£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kcs/100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 x 6 1/2 x 5 1/2. Grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 230/250. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 100 milli-volts. C.W. and mod. switch Indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing 5/-. Coverage 120 Kcs/84 Mc/s. Metal case 10 x 6 1/2 x 4 1/2. Size of scale 6 1/2 x 3 1/2. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30% modulated or unmodulated R.F. output continuously variable. 100 milli-volts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.




ALIGNMENT ANALYSER TYPE MC12

A.C. mains 200/250 v. Provides "Wobbulator" (Swept Frequency) Operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 Kcs/80 Mc/s. Capacitance Measurement. Two ranges provided 0-50pF and 0-12pF. Special Facility enables true resonant frequency of any tuned ckt. I.F. transformer, etc., to be rapidly determined. Cash price £6.19.6, plus 5/- P. & P. H.P. terms 25/- deposit, plus 5/- P. & P. and six monthly payments of 21/6.



CHANNEL TUNER

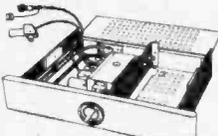Will tune to all Band 1 and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series) I.F. 16.19 or 33-38. Also can be modified as an aerial converter (instructions supplied). Complete with knobs. **32/6** Plus 3/6 P. & P.




HEATER TRANSFORMER

To suit the above, 200-250 v. & 611v. plus 1/6 P. & P

LINE E.H.T. TRANSFORMERS

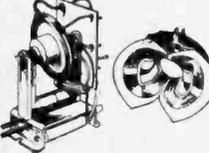With built-in line and width control. 1kV. Scan coil. 90in. deflection on ferrite yokes. Frame O.P. transformer pi 18 kv smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.



29/6 Plus 4/- P. & P.

As above, but for 625 lines. £2.10.0, plus 4/- P. & P.

Foetus Magnet suitable for the above (state tube). 10/- plus 2/6 P. & P.



A.C./D.C. POCKET MULTIMETER KIT

2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wirewound pot. (for ohms zero setting), toggle switch, resistor and rectifier, 10/6. P. & P. 1/6. Wiring diagram 1/-. free with kit.

RADIO & T.V. COMPONENTS (Acton) LTD.

23c HIGH STREET, ACTON, LONDON, W.3

All enquiries S.A.E. Goods Not Despatched Outside U.K.

TUBES

HIGHEST QUALITY—NEW LOW PRICES

Cartr. No.	6 Months seconds	12 Months REGUNNED	12 Months NEW TYPES
MOST MULLARD, MAZDA COSSOR, EMITRON FMI-SCOPE BRIMAR, FERRANTI TYPES, PROCESSED IN OUR OWN FACTORY.	9/10in. £1-10-0	£3- 0-0	£4-0-0
New Mullard, Mazda + U.S.A. runs used.	12in. £1-15-0	£3-10-0	MW 36/44, MW 38/4, CRM 172, MW 43/64, £26-0-0
	14in. £2- 0-0	£4- 0-0	
	15/17in. £2-15-0	£4-15-0	
	21in. £3-15-0	£5-15-0	

★ Record Players Carriage 4/- ★

COLLARO CONQUEST .. £6 10 0
B.S.R. (U414) AUTOCHANGERS .. £7 19 0
B.S.R. (U43) STEREO AUTO .. £6 19 0
GARRARD RCL2-D MK11 .. £9 7 8

4-SPD. RECORD PLAYERS

Latest 3.B.R. TU9 Turrotable to either with turntable or Sile-Glaxial sapphire crystal turnover pick-up head. Truly amazing value at **£3.10.0** Cartr. 3/-

GALAXY PICK-UPS, as above, only 19/6.

13 CHANNEL TVS

Table Models. Complete with Vaeres and Tute. They are untested, not guaranteed to be in working order. 12 in. £2.10.0 (P.P. 12/6). 14 in. £4.10.0 (P.P. 15/-)

Special Offer

A huge Purchase of 21 Speakers, direct from Manufacturers. Only 13/- P.P. 1/- 100 Condensers 10/- 100 Resistors 6/6.

VALVES

BY RETURN OF POST

GUARANTEED 3 MONTHS

NEW LOW PRICES

10% DISCOUNT SPECIAL OFFER

TO PURCHASERS

of any SIX VALVES marked in back type (15% in dozens). Post. 1 valve 8d. 2/- 1/-

FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money Back Refund on goods if returned unused within 14 days.

074	5/-	11/1	12/6	20P1	15/-	ERCR1	7/9	KT38	9/-	U78	5/-
147G7	11/3	61A	9/9	2E4G1	6/9	ERF80	7/9	KT44	7/6	U82	7/-
105G7	9/6	4L60	7/3	25L6G	6/9	FPB93	8/6	KT45	8/6	U107	11/-
1145G1	9/9	1L7G	6/7	25L6GT	9/-	EBL21	12/6	KT61	8/6	U118	6/-
1L4	3/6	6L18	8/6	25Z4G	7/3	EBL21	21/-	KT68	6/3	U119	6/9
1N5GT	9/9	6L19	12/6	27F5	16/-	EC52	5/6	KT69	12/6	U132	8/-
1B3	5/6	4L20	8/6	30F5	6/9	EC31	8/6	KT69	5/6	U143	9/-
184	8/-	4P25	8/6	30P1L1	9/6	EC32	4/-	KT69	5/6	U145	6/-
185	8/6	4P25	12/6	30P1L2	12/6	EC33	4/8	KT69	5/6	U147	5/6
174	3/9	6P12	8/9	30P12	3/-	EC34	9/-	KT69	5/6	U149	7/-
2A3	7/6	6A7GT	8/9	30P1L1	10/6	EC35	5/6	KT69	5/6	U150	6/6
2D1	4/6	8SA7	5/9	35L6GT	9/6	EC35	5/6	KT69	5/6	U151	3/-
3A4	4/9	8S67	4/9	35W4	6/9	EC32	6/-	KT69	5/6	U152	7/-
3A4	7/-	8H7	4/9	36Z4GT	5/3	EC34	6/9	KT69	5/6	U153	6/-
3B4	6/-	8H7	4/-	36C16G1	9/-	EC34	5/9	KT69	5/6	U154	6/3
3V4	6/9	8K7	5/3	30L6GT	9/-	EC38	7/9	KT69	5/6	U191	11/-
3B4G	9/6	68.7GT	6/-	61B1	16/-	ECF80	8/6	UC94	7/-	UC91	9/6
3T4	8/9	68N7GT	4/8	61BPT	11/-	ECF82	12/6	UC95	9/3	UC91	15/-
3D4G	4/9	8K7	6/-	18B5T	8/6	ECB21	8/6	UC98	9/3	UC99	7/-
3V4G	4/9	8K7	4/6	8007A	5/6	ECB25	8/6	UC99	13/6	UC99	11/-
3Y3G	5/9	60A4GT	10/6	807D	3/6	ECB25	8/6	UC99	13/6	UC99	11/-
3Y3GT	6/-	6V6G	5/6	855	3/9	ECB21	8/6	UC99	7/9	UC99	9/6
6Y4G	8/6	8V6GT	6/6	855	2/6	ECB20	7/-	UC94	10/6	UC99	9/6
3Z4GT	11/-	6A7	9/-	9001	4/6	ECL82	7/6	UC92	7/3	UC91	19/-
8A8	4/9	6X3G	5/6	9003	4/-	ECL83	12/-	UC92	10/6	UC95	8/6
6A8G	9/6	6X3GT	5/6	ATP4	2/9	ECF81	12/6	UC94	7/6	UC94	8/6
6A7	4/3	6V6G	7/9	AZ31	9/-	EP54	3/6	UC94	7/6	UC94	7/6
6A65	3/6	7B	9/-	8B6	8/6	EP80	4/9	UC94	7/6	UC94	7/6
6A7	3/6	7B7	7/9	8B6	4/8	EP86	4/9	UC94	7/6	UC94	7/6
6A85	5/6	7B7	7/3	8C3	8/6	EP86	4/9	UC94	7/6	UC94	7/6
6A15	3/6	7C5	7/3	8C3L21	21/-	EP89	6/9	UC94	7/6	UC94	7/6
6AM6	3/-	7H7	7/6	8C35	14/-	EP91	3/6	UC94	7/6	UC94	7/6
6A45	6/-	787	9/-	CL38	11/9	EP92	4/6	UC94	7/6	UC94	7/6
6A7B	6/-	7Y7	7/-	CT31	9/9	EP92	12/6	UC94	7/6	UC94	7/6
6A06	7/6	10C1	11/-	D63	1/6	EP92	4/6	UC94	7/6	UC94	7/6
6B9G	3/6	10C2	13/6	DA90	2/6	EL32	3/-	UC94	7/6	UC94	7/6
6BA8	5/-	10F1	5/6	DAC32	9/9	EL35	7/-	UC94	7/6	UC94	7/6
6BE6	5/9	10L1	14/6	DAF91	4/9	EL37	11/6	UC94	7/6	UC94	7/6
6B06	12/6	10P13	9/-	DAF96	7/3	EL38	12/6	UC94	7/6	UC94	7/6
6B9E	7/6	10P14	9/-	DFK3	9/6	EL41	8/-	UC94	7/6	UC94	7/6
6B97	5/6	12A1H	6/9	DF91	3/9	EL42	7/-	UC94	7/6	UC94	7/6
6C4	3/6	12A1H	6/9	DF92	3/9	EL42	7/-	UC94	7/6	UC94	7/6
6C8	4/9	12A1E	7/6	DF96	7/3	EL91	4/6	UC94	7/6	UC94	7/6
6C9	4/9	12A1T	7/6	DH77	7/-	EM34	8/6	UC94	7/6	UC94	7/6
6CDDG	21/6	2A7	7/6	DR81	3/6	EM34	8/6	UC94	7/6	UC94	7/6
6CH6	8/3	12A1T	6/9	DK32	11/3	EM81	8/9	UC94	7/6	UC94	7/6
4D6	4/9	1236GT	3/8	DK91	5/6	EM84	9/9	UC94	7/6	UC94	7/6
8F1	4/9	12K7GT	5/-	DK92	7/6	EM85	10/6	UC94	7/6	UC94	7/6
6F8G	6/6	12K7GT	5/-	DK96	7/6	EM81	16/1	UC94	7/6	UC94	7/6
6F12	3/6	12K7GT	5/-	EL31	3/6	EM81	16/1	UC94	7/6	UC94	7/6
6F13	6/9	12K7GT	4/9	DL35	9/6	small	8/-	UC94	7/6	UC94	7/6
6F14	9/6	12K7GT	4/9	DL91	8/6	EM84	8/-	UC94	7/6	UC94	7/6
6F15	9/6	12K7GT	4/9	DL92	8/6	EM84	8/-	UC94	7/6	UC94	7/6
6E6	9/-	128N7GT	4/9	DL93	4/9	EM84	8/-	UC94	7/6	UC94	7/6
6G5E	2/9	128N7GT	4/9	DL94	4/9	EM84	8/-	UC94	7/6	UC94	7/6
6J5GT	3/9	13D3	7/-	DL96	7/3	EM81	8/-	UC94	7/6	UC94	7/6
6G7E	5/-	1487	22/6	E430	9/-	GTIC	7/6	UC94	7/6	UC94	7/6
6J7GT	7/6	19B6G15	1/6	E430	7/6	G230	11/6	UC94	7/6	UC94	7/6
6K6GT	6/6	20F1	8/6	E432	8/6	G230	8/6	UC94	7/6	UC94	7/6
6K7E	2/3	20F2	8/6	EB34	1/6	H4C80	9/8	UC94	7/6	UC94	7/6
5K7GT	4/9	20L1	16/-	EB41	7/-	HBC90	7/6	UC94	7/6	UC94	7/6
6K9G	5/6	20P1	9/9	EB91	3/6	LL41DD	9/8	UC94	7/6	UC94	7/6
6K8GT	9/9	20P3	12/6	EC33	4/9	HV R	6/6	UC94	7/6	UC94	7/6
6K9E	7/6	20P4	17/-	EC41	8/-	KT33C	7/6	UC94	7/6	UC94	7/6

AMAZING VALVE AND COMPONENT LIST 6d. TECHNICAL TRADING CO. 350/352 FRATTON ROAD, PORTSMOUTH

PORTRAIT OF A SIDE BAND

By L. E. Higgs

VISUALISING electronic processes in the form of mental images helps us in understanding abstract, invisible radio concepts. Pictures of electrons boiling off red-hot cathodes, electrical currents as water flowing through pipes from a water tank battery, and lately, transistors playing a game of Chinese chequers—electrons flowing up the crystalline board one way, leaving holes flowing the other way, are all means of understanding electrical technicalities.

A common picture painted in schools and text books is of the amplitude modulated carrier wave. This familiar waveform is shown in Fig. 1. Most of us can picture it snaking across the ether from the transmitter to our aerials carrying the audio on its back, ready for amplification, sliced down the middle by the detector, R.F. smoothed, and fed to the volume control.

The Problem

This presents a perfectly clear explanation, until the word "sideband" appears; and when a non-mathematical practical man with little or no knowledge of trigonometry looks at this wave shape, he wonders where the sidebands are. Despite this gently undulating single frequency, the practical man realizes that sidebands exist if only from the broadness of a radio station on a receiver scale. The efforts made by designers to damp down coil Qs, stagger tuned wideband vision amplifiers, and the appearance of test card C definition gratings when the wrong slug is turned in the vision strip, are further manifestations of the width of sidebands.

We can manage quite well with the carrier envelope image of modulation in radio and TV work, provided it is confined to orthodox A.M. practice, but with the coming of colour, certain processes such as chrominance sub-carrier interleaving and carrier suppression are impossible to envisage this way. With reference to Fig. 1 once more, how can one visualise removing the carrier from this gently undulating wave that is so obviously all carrier? It can be shown, however, that Fig. 1, consists of a central carrier and two side frequencies. This is done either graphically, mathematically or experimentally with a communications receiver possessing "razor-edge" selectivity, whence three separate spot frequencies will be received.

Modulation

Another mental image is now required to help us to visualize the width and composition of a radio signal and will enable the extraction of the carrier to be "seen" clearly. Just as a number of musical

AN UNUSUAL
METHOD OF
MAKING CLEAR
SOME OF THE
INTRICACIES
OF WAVEFORM

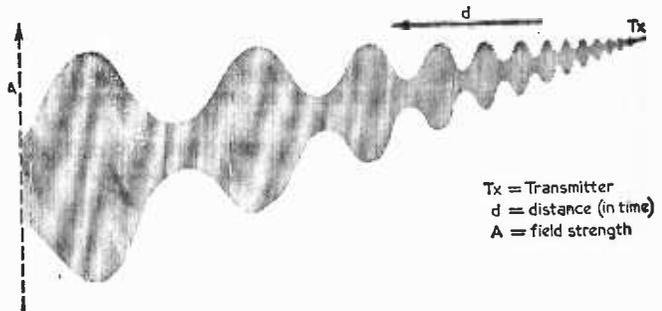


Fig. 1.—The well known representation of an amplitude modulated carrier wave.

instruments playing together different musical notes can be simulated by a complicated wobbly groove on a gramophone record, so the complex A.M. waveform is produced by the separate sound frequencies mixing with the carrier. If this complex wave is considered instead by its constituent components all through the communication system, the production of sidebands becomes clearly understood. Consider the many different audio frequencies from the microphone being amplified, and mixed or frequency-changed at the modulator with the steady carrier R.F. The resultant sum and difference frequencies developed in the transmitter tank coil will be audio band plus carrier, carrier minus audio band and the original steady R.F. (The audio cannot exist in the R.F. tuned transmitter output circuit.) These three separate components can now be easily pictured as two mirror image sidebands grouped on each side of a steady unchanged carrier central frequency. This is modulation explained in the simple frequency changer action that is well understood in receiver

superhets. The sidebands will vary in spectrum width according to the highest audio frequency applied, and the space within the sideband filled with many or few spot frequencies that may be present with the complexity of the sound input from moment-to-moment. The size or amplitude of each of these side frequencies will depend on the strength of the audio at the microphone but will never exceed half the power of the central carrier for unity modulation index. Clearly the carrier can be picked out, if required, from this picture by filters or phase cancelling and the side bands left to radiate unaffected. This spectrum view of a radio signal can be made more real by combining it with a time axis. When mechanical engineers wish to make a workshop plan and elevation of a object immediately recognisable, they give them a three-quarter twist and produce the isometric view. By giving the spectrum/amplitude and time/amplitude graphs a similar twist but in perspective, we get the best of both views with a portrait as in Fig. 2. Points to note in the diagram are the steady high-amplitude central carrier frequency—unaffected by modulation, the mirror image sidebands—always lower in amplitude than the carrier with a maximum of half the modulation index of it—and amplitude variations on a single side frequency being caused by changes in tone volume. During pauses in the modulation, side frequencies all disappear, leaving the steady carrier.

Complex Modulation

Complex modulation — the irregular ragged speech or music envelope—now shows as a variable


series of sinusoidal Fourier component frequencies. Amplitude and the number of side frequencies change from moment-to-moment with the composition of the modulation. Low modulating tones are closest to the carrier and the side frequencies extend out from the carrier with pitch, until the highest note sets the outer limit of the sidebands. It is these outer frequencies that suffer from cramped receiver bandwidth, causing treble loss in sound and fine definition blurr on vision.

Having produced this working picture of sidebands from the action of modulation how does it apply to detection or demodulation?

Demodulation

Demodulation is well understood in terms of envelope modulation waveform (Fig. 1) as a passive process of blocking each half cycle of R.F. With the sidebands and carrier view however, an interesting picture of heterodyning, of all things, appears. When the group of frequencies comprising the radio signal present themselves to the non-linear demodulator at the receiver, the steady central carrier mixes with every side frequency in both sidebands, producing a pair of sidebands at twice the carrier frequency (addition components) and a pair of heterodyne audio frequencies (subtraction components). The energy from the audio pair add together and pass through the R.F. smoothing circuit to the volume control and on to further amplification. The addition components, being R.F., are bypassed to earth by the R.F. filter circuit. This explains why the carrier steady frequency must be present at the demodulator,

Fig. 2.—A spectrum view of an audio modulated wave.

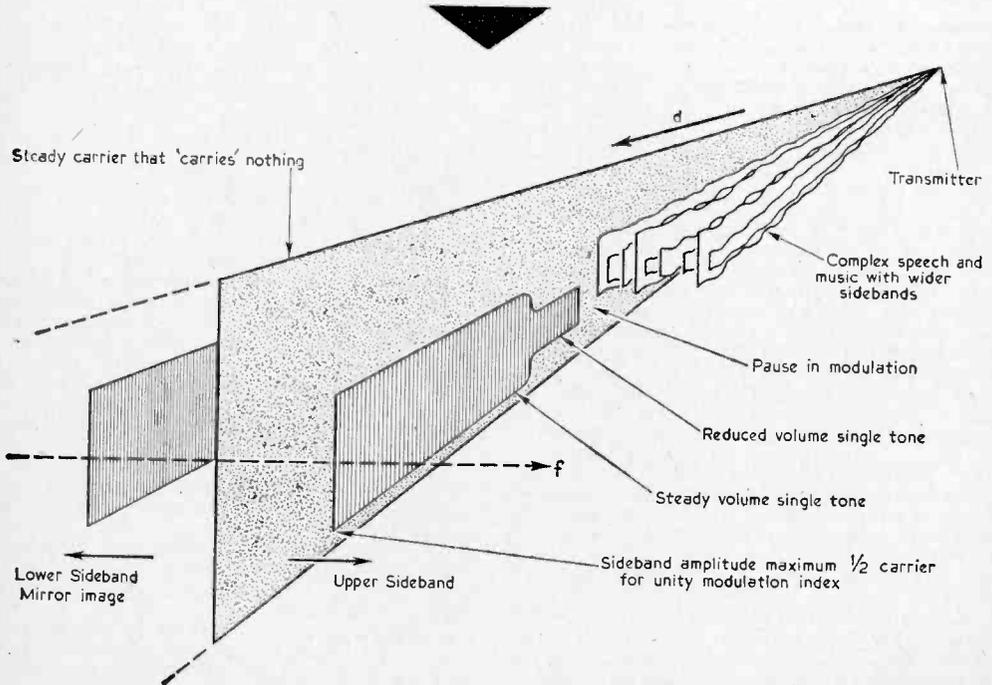

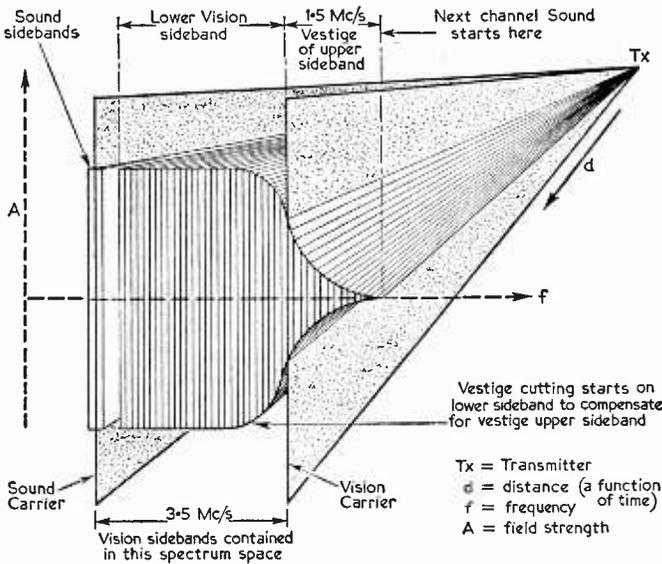


Fig. 3.—A "picture" of a television channel with equal vision/sound power ratio.

naturally with A.M. or artificially inserted with carrier suppressed signals, in order to heterodyne the A.F. from the signal sidebands.

Television

Television channels are particularly interesting when viewed as in Fig. 3. This shows a channel as a solid spectrum space boundary in which sidebands can occur. The vision vestigial upper sideband and the whole lower sideband, depict the cutting

action of the vestige filter commencing slightly inside the lower sidebands. This is deliberately arranged to compensate for the rise in low vision frequency response that results from the presence of the vestige of the upper sideband—the power of which adds to its equivalent components in the lower sideband. The sound channel position of the next adjacent channel is seen to commence only 1.5Mc/s away from the central vision carrier of the lower channel instead of 3.5Mc/s that would be required if double sideband working were used; thus saving spectrum space.

Colour TV

The vision channel spectrum differs from that of the sound in having the sidebands distributed at discreet 10,125Mc/s intervals from the carrier, continuing up to the 3Mc/s outer sideband limit. These clusters of sidebands around each harmonic of the line frequency are caused by the "chopping-up" of the carrier at the line repetition rate, and between the clusters are empty spaces never reached by line harmonic side frequencies. Colour television makes use of these unused gaps by interleaving the chrominance of colour signal between them (similar to the positioning of the teeth of two identical combs into each other). The colour signal is carrier suppressed and a locally generated carrier has to be accurately inserted at the receiver.

With only the carrier envelope notation to guide us the processes of carrier suppression, sub-carrier interleaving, and even sidebands are difficult if not impossible to envisage.

Transistor Tuners

(Continued from page 554)

A more recent Philco design has forward AGC applied. To achieve this, the upper end of the 1.2k resistor (see Fig. 1) in the emitter circuit of the R.F. amplifier, is disconnected from the upper end of the 4.7k resistor in the base circuit. The AGC voltage is then applied through this 4.7k resistor. In this design the 2.2k resistor and the three resistors of the range switch are omitted.

The Sickles Mark 6T Tuner


The circuit diagram of this tuner is shown in Fig. 3. The 75Ω aerial input is unbalanced, as this tuner was designed for use with a portable TV receiver, which used a whip aerial. After the I.F. trap, the signal passes to groups of aerial coils, which are selected by switch. Neutralisation at the R.F. amplifier is obtained by including in the circuit, a variable capacitor. The pairs of coils—for the different channels—on the turret unit, couple the amplified R.F. signal to the base of the mixer,

a T-1600 transistor. (Note the channel 13 collector and base coils in Fig. 3.) As in the Philco tuner in Fig. 1, the mixer base of the Sickles tuner is connected to earth via an I.F. trap. The Sickles tuner, however, uses a common-base local oscillator, with selective and tunable oscillator coils in the collector circuit. The local output is from the emitter and this oscillator signal is injected into the mixer base.

The mixer is a common-emitter type, with its output—the desired I.F. signal—appearing at the collector terminal and then going to the tunable I.F. coil as shown.

The measurements obtained when using a Sickles Mark 6T, warrant some attention, as they show a marked improvement over the experimental Philco tuner. The gain of the lower channels ranges from 34.5 to 29dB, and channels 7 to 13 ranges from 24 to 21.5dB. The corresponding noise figures are 4.8 to 5.3dB, and 9.1 to 10.4dB.

adjusting TV

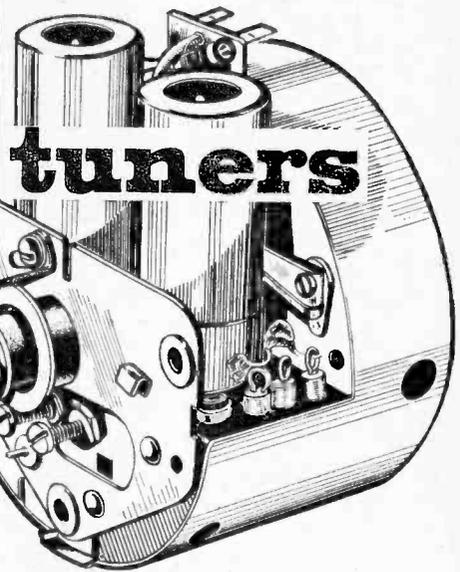

By K. Dawe

The "Fireball" tuner is used with many television receivers, and any adjustments made to it—as with any TV tuner—must be executed with the greatest care. Servicing either the mechanical or electrical parts of the tuner, should be attempted only if some knowledge of the construction of the unit is available. This article provides this information and also the procedure for making some adjustments to the tuner.

This, by now, well known tuner unit is fitted in a large number of receivers of various makes. Although all tuners of this type look alike there are many circuit variations and the diagrams shown are representative only.

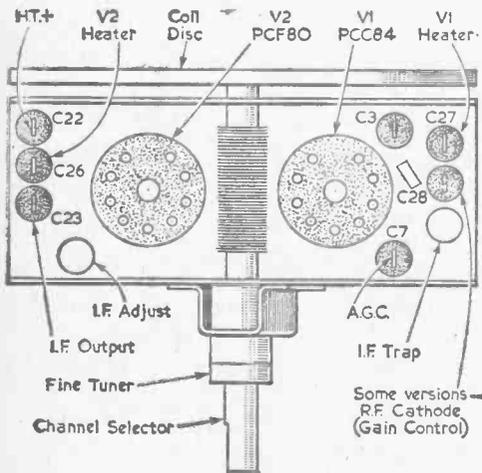


Fig. 1.—The top view of the original Fireball tuner. The shaded components are lead-through decoupling capacitors.

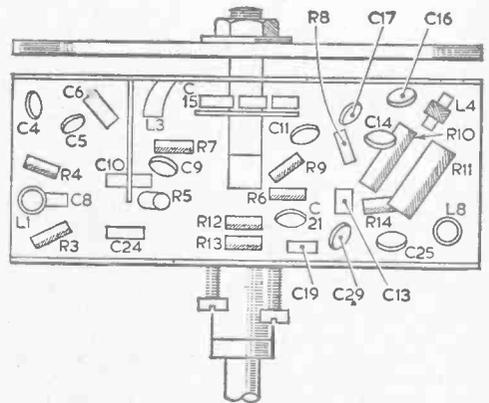


Fig. 2.—The underchassis view of the first Fireball.

The Basic Design

Basically the design consists of a radial arrangement of coils on a disc which is rotated by the channel selector to engage with a horizontal bank of spring contacts. The exact point of contact is, or should be, determined by a spring loaded stoppin, engaging in the grooves of a star wheel or sprocket on the channel selector shaft.

The coil disc has two grooves set at an angle which fit two corresponding rises on the star wheel and is held in this position by a retaining nut. The

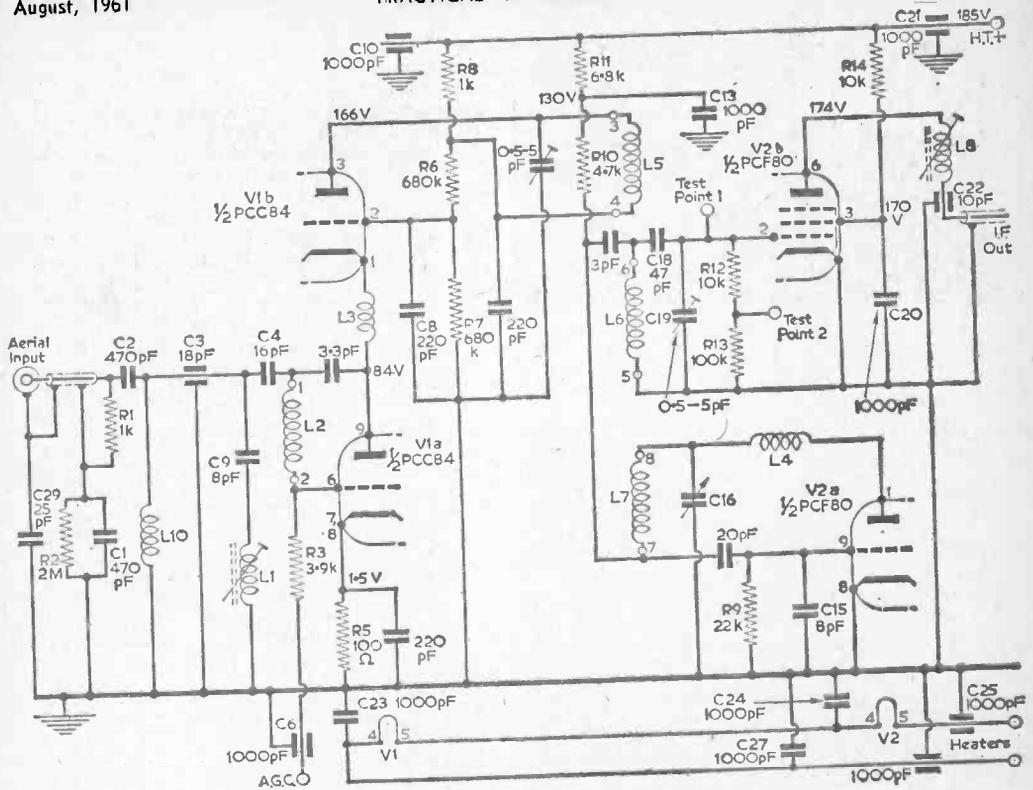


Fig. 3.—The circuit of the tuner.

coil disc and underside of the tuner are covered by a metal shell which has two slots at the top and one at the bottom-centre. This latter fixing, which is a clip fit, may be found soldered. When removing the cover this bottom fixing must be released first to enable the cover to be swung up and off the top fixings. Removal of the cover exposes the coil disc (not the contacts) and circuit components under the valve bases.

Contact Studs and Springs

To gain access to the contact studs and springs, the retaining nut and washer should be removed and the disc lifted off. The coils are connected to silver plated studs on the front face. These studs, of course, tarnish in time and therefore require cleaning in precisely the same way as those on normal turret tuner coil biscuits.

Cleaning the Studs

Different schools of thought exist on this subject of cleaning. It is maintained by some that thorough polishing of the studs is all that is required (and desired); this to be done with a soft cloth using no cleaning fluid or contact lubricants either before or after cleaning. Others support the stud polishing but recommend a light smearing of a proprietary

lubricant, such as MS4 or Electrolube to preserve the surface contact and delay further tarnishing. Normal switch cleaner is not advised.

The leaf contacts should be similarly cleaned, and it should be noted that these leaves locate in slots at their free end. *On no account are these leaves to be distorted or kinked as this can not only*


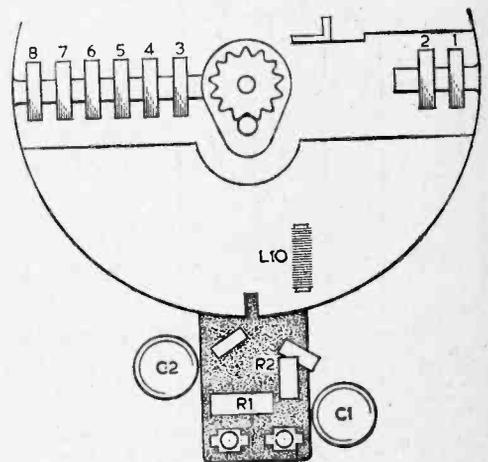


Fig. 4 (right).—The rear of the tuner with the disc removed to show the contacts and the star wheel.

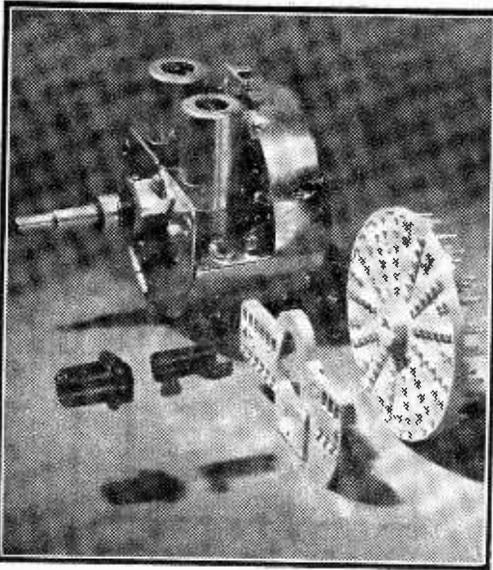

The Fireball tuner with the Bakelite mouldings which form a large part of the tuner.

cause obvious damage, but also failure of the disc to locate properly, as the position is determined by the bow of the leaves rather than the star wheel and stop-pin, which, as previously stated, is spring loaded but not heavily so. When refitting the disc, ensure that the centre grooves engage with the corresponding rises on the star wheel, and tighten the retaining nut to maintain this fitting. When programmes are received in the wrong switch positions and give unreliable reception, it should be ensured that the disc is properly located and the nut tightened.

Circuit Faults

Apart from switch location and poor contact troubles, complaints of poor reception, particularly on Band III are usually the result of a low emission PCC84 or PCC89 valve in the V1 position. Note: these valves cannot be interchanged. If the poor reception is not due to local reception conditions or aerial troubles, i.e. the reception has previously been acceptable and the valves are not at fault, check the resistors under the tuner, particularly the H.T. feed resistor(s) of the PCF80 triode section, R10 and R11 in Fig. 3, noting that the value may be found different in varying types of tuner. (Some versions may use only a single 6.8k resistor in this position.) Also check the values of R6 and R7 which should be equal. If V1 and


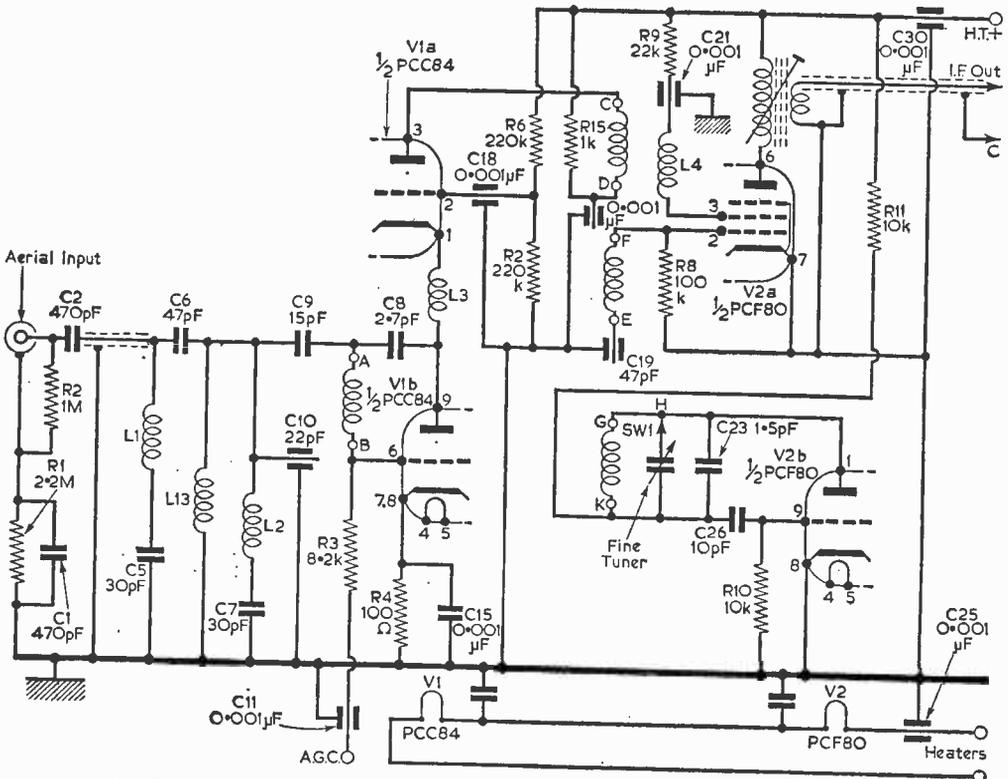


Fig. 5.—The circuit of the unit used in recent Sobell and McMichael television receivers.

Fig. 6.—Another of the many variations of the Fireball tuner.

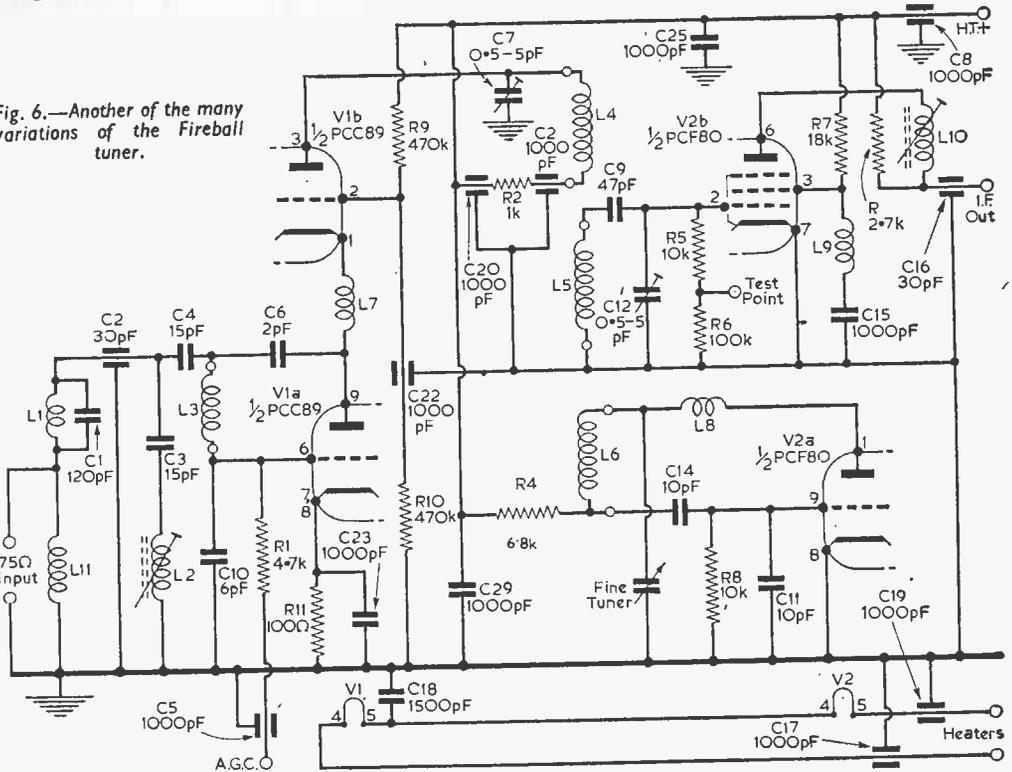

V2 are ever accidentally transposed and subsequent reception is nil or poor after the mistake has been rectified, check R5 (pins 7 and 8 of V1 to chassis) and R8 (H.T. feed to V1).

When the fine tuner fails to bring in the required channel, with the selector correctly set, or the sound can only be received with a vision buzz superimposed on it, (not caused by incorrect setting of contrast or sensitivity or excessive signal input) it is necessary to adjust the oscillator coil core for that particular channel.

(Continued on page 572)

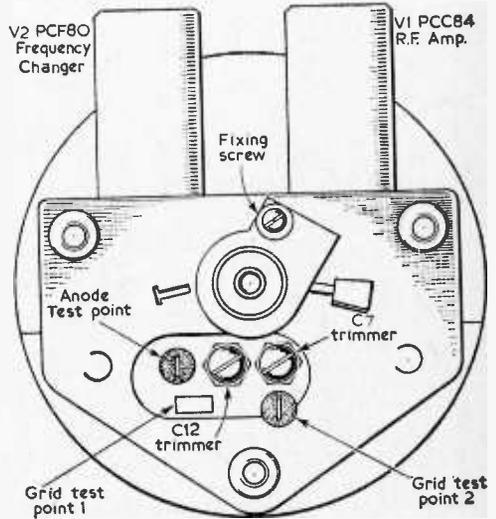
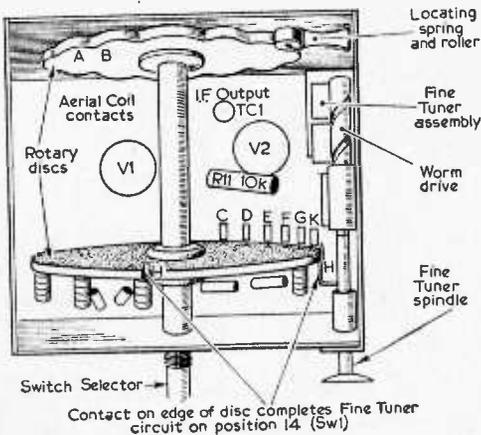


Fig. 7 (left).—The version of the tuner which is used in some Sobell and McMichael receivers.

Fig. 8 (above).—A front view of the tuner, showing tuning and test points.

Underneath the Dipole

A MONTHLY
COMMENTARY

By Iconos

SIMPLICITY! That should be the keynote of all art directors, designers, graphics, caption artists or anybody else who is responsible for the visual backings to light entertainment on television.

The simple approach is especially necessary for musical and dancing features, quiz games and the like, where the personalities in the foreground are the centre of attention. "Something Old and Something New"—Associated Rediffusion's late-night musical is a fast-moving cavalcade of song and dance in which the scenery is practically non-existent, but a sense of design is provided by variations of lighting patterns on the background: cyclorama, use of stairways, rostrums etc. A few simple character costumes and stage properties are introduced as required; but for the rest, the main background is provided by the bright cheerful pre-recorded vocal and orchestral music, which sets a crackling pace and gives the choreographer (Ross Taylor) scope for rapid moves without the usual microphone impedimenta. The miming of chorus songs is first rate. Presentation of this kind would possibly appear stark and contrived if the artistes in the foreground were not of the highest professional standard.

In the case of "Something Old and Something New", the foundation of the show is the skilled orchestration which includes dozens of songs old and new, in a cheerful continuous half-hour of familiar music performed by the Cliff Adam Singers and a star guest artiste. The adroit transitions from one tune to another are accomplished with skill and precision by musicians and dancers.

Quiz Shows

Simplicity should be the guiding factor in dealing with quiz

shows too. The problem is not quite so easy. Many of the quiz shows have elaborate mechanical and electrical stage props, such as Granada's "Crisis Cross Quiz" and Westward's "Ordinary People". Here, the designer has a difficult time in avoiding the patterning and interference caused by visually "busy" backgrounds which are essential parts of the games and competitions.

No quiz game has had quite the impact of "What's My Line", which Maurice Winnick brought over from America to the BBC years ago and which has stood the test of time. This always has the simplest of backgrounds.

Associated-Rediffusion's "Double Your Money" and "Take your Pick" have high ratings because they are not complicated and are very professionally steered by Hughie Green and Michael Miles respectively. It is interesting to note that some

of the most successful quiz games are recorded on film and are afterwards cut to the right length, sometimes with contestants transposed in their order of presentation, so that the game can work up to a climax. Give-away and competitive quizzes can be very chancy. There is always the risk of competitors being such morons and so nervous that they can scarcely speak above a whisper, completely putting a damper on the proceedings, with poor entertainment value as the end-product. It is the Question Master's job to draw these people out and make them interesting to the viewer, without subjecting them to ridicule.

Some American companies running television quizzes habitually pre-select their quiz audiences by personal interviews and questioning, to make sure that contestants will be bright and interesting. This is legitimate and



The Rt. Hon. Peter Thorneycroft, Minister of Aviation, recently visited the Mullard research laboratories. The illustration shows him inspecting an experimental colour television receiver.

necessary for the elimination of bores, exhibitionists and cranks—always a danger when a quiz game is sent out live.

Even more dangerous, however, has been the inclination to give contestants clues about their probable questions; a course of action which was inevitably exposed and which pretty well finished quiz games for a time in the U.S.A. Over here, the Independent Television Authority and the BBC are extremely strict about these things — and woe betide the producer who doesn't toe the line!

The Royal Wedding

Once more, television had a royal outside broadcast day out, when H.R.H. The Duke of Kent and Miss Katherine Worsley were married in York Minster.

Enormous technical and staff resources were allocated to this event both by the BBC and by the ITV—the latter being a joint effort by Tyne Tees, Granada, ABC and others. This joint ITV effort fielded twenty-one cameras, thus being one up on the BBC's total of twenty cameras, although the BBC had six cameras actually in York Minster compared with ITV's five.

It was possible to compare results by viewing the tape recordings later in the day. The presentation by both organisations was first class, though I thought that visually the ITV version had the slight edge on the BBC because of certain unusual following shots of the bride and bridegroom walking down the aisle after the ceremony. One of these was a beautifully operated zoom lens close-up of the bride smiling at her friends as she slowly progressed. On the sound side, however, I thought the BBC put up a better show, the musical balance being superior and the commentary of Richard Dimpleby following his usual quiet and authoritative style for such occasions.

It has been suggested in some quarters that the competitive television coverage of royal occasions is wasteful. I disagree. It is because there is this competition that the job is so well carried out and so well worth looking at, no matter which channel you decide to use. It is doubly interesting to be able to see how the rival networks did the job, thanks to video tape recordings.

The National Anthem

The playing of the National Anthem at the beginning or end of an entertainment has been a custom of many years standing. Its execution has varied from just the first few bars only, hurriedly played by a music hall orchestra, to the elaborate arrangement for symphony orchestra and organ, played at the Albert Hall. Ballet seasons and opera are usually preceded by a full playing, after which it is not played again until the end of the final performance of the season.

The BBC end both sound and television programmes with the National Anthem, as do most of the ITV companies—the elaboration varying according to local tastes and customs. Ulster Television presents a very fine visual and sound anthem at the end of each day's programme—probably the most elaborate and impressive of the lot. Westward commence each day's programme with the anthem including an informal sequence of the Royal Family at home. Granada do not have a National Anthem on television, a regrettable break with tradition.

Opinions differ as to which is the right way to deal with this matter. Personally, I like to hear (and see) the National Anthem at the end of a television programme but would prefer to have its presentation varied a little from

night to night, either by different musical arrangement or by a variation of the film sequence,

Newsreels

What a wonderful job the television newsreels do, both the BBC and ITA. The country is now literally covered with staff and "stringer" cameramen working for the BBC and Independent Television News. In addition, both services run their own local news supplements, which necessitates the installation of special equipment and the organisation of quite a complicated operation, involving the gathering of the latest news by telephone from reporters and correspondents, supplemented by visual news and interview stories sent in by "stringer" cameramen. Stringers, it should be explained, are freelance cameramen with their own equipment who are on the spot, probably miles away from headquarters.

Visual News

Naturally, the visual news is the most popular and the regional trend is to include as many filmed stories as possible, such as royal visits, sporting events, ship launchings, county shows and laying of foundation stones. In some regions, the faces and chains of office of local mayors must be becoming as familiar as film-star pin-ups!

PRACTICAL WIRELESS

Chief Contents of the August Issue

Now on Sale, 1/6

AN ACORN F.M. TUNER

A SENSITIVE MULTIMETER

A STABILISED POWER SUPPLY

AN AMATEUR COMMUNICATIONS RECEIVER

PHASE SPLITTERS AND PHASE REVERSERS

NOISE LIMITER AND SPEECH CLIPPER

ADDING COMMUNICATION FEATURES

SIGNAL GENERATOR OUTPUTS


VOICE-OPERATED SWITCH

AN INEXPENSIVE AMPLIFIER

CLUB NEWS

ETC., ETC., ETC.

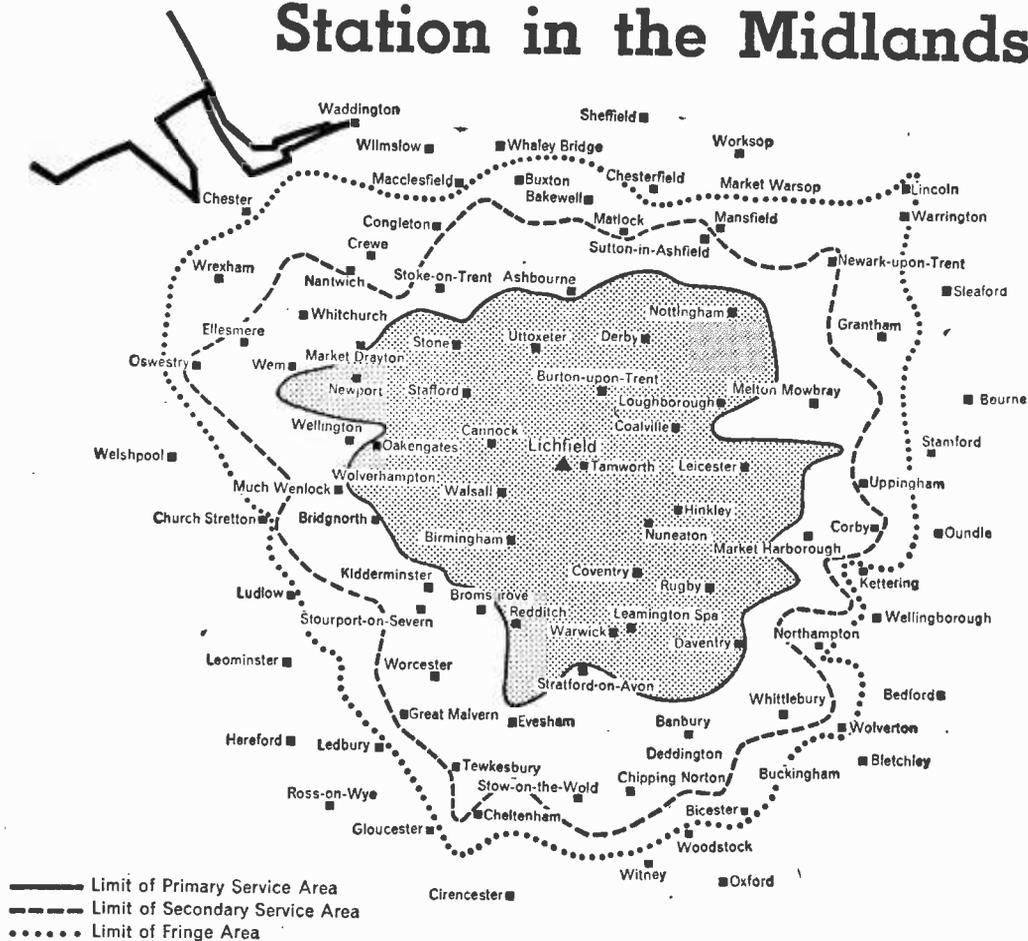A New Mast at the ITA's Lichfield Station in the Midlands



The estimated coverage of the new mast.

JHIS month, transmissions from the Independent Television station at Lichfield will be radiated by a new 1000ft mast, which replaces the original 450ft mast. A directional aerial system also comes into operation, radiating a maximum power of 400kW to the South, 200kW to the North and West, and 100kW to the east. The effect of this will be to increase the total coverage of the station to 7.45 million, and reception will improve throughout the area.

Another improvement which has been recently introduced at Lichfield has been the addition of

high-power amplifiers to the standby transmitter. Previously, if a fault occurred in the main transmitter, programme transmissions had to continue on reduced power. In future, if a fault should occur, programme transmission from the standby transmitter will continue, without reduction of power, while the fault on the main transmitter is being rectified.

The Lichfield station is 500ft above sea level, which gives the aerial a mean height of 1450ft. The vision frequency is 189.75Mc/s, and the sound frequency is 186.25Mc/s. The signal is vertically polarised and is received on channel 8.

T N

rade ews

Aerials at Radio Show

AN extensive range of pre-assembled aerials will be exhibited by Aerialite Ltd., at this year's Radio Show. Aerials suitable for mounting in a room or on top of a television receiver will be on show, along with a range of loft-aerials.

Many television accessories will be on view, including coaxial plugs and sockets, duplexers, triplexers, etc. A copper taped television relay cable, made by Aerialite Ltd., with improved lower attenuation figures, will be featured on their stand. All these items will be shown by *Aerialite Ltd., Aerial and Electronics Division, Hargreaves Works, Congleton, Cheshire.*


Remote Control Colour TV Camera

A NEW colour television camera is now available from EMI Electronics Ltd.

The main advantage of this camera is that it can be sited in positions that would not permit the

use of ordinary cameras. It is also remotely-controlled. It can, for example, televise colour pictures from inside a steel furnace at the moment when a charge of metal reaches "white heat".

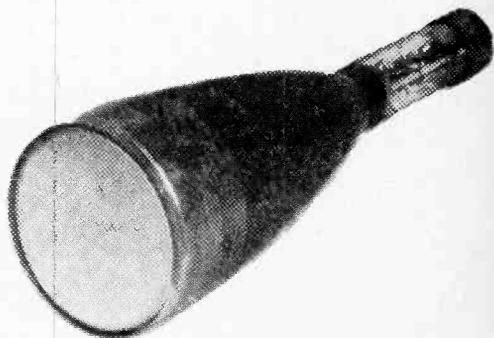The camera uses three vidicon tubes and a novel optical system capable of producing good-quality pictures under difficult lighting conditions. It will operate on 405, 525 or 625 line standard. The camera is made by *EMI Electronics Ltd., Hayes, Middlesex.*



A new cathode ray tube, made by The M-O Valve Co. Ltd.

New TV Receiver

THE "Senator" (model 705T) is the first of a new range of television receivers, made by Ferguson.

The model 705T is a 19in. receiver incorporating a 110° picture tube. Push button control on the motor driven tuner, switches to either BBC or ITA, and the 13 channel tuner is easily pre-adjusted to the appropriate stations in the area where the receiver is to be used. The tuner unit also has provision for VHF coils, if and when new programmes start on Bands IV and V.


All of the main circuitry is on two printed boards, placed in easily accessible positions.

Available with this receiver at two guineas extra, is a remote control unit, which will operate the volume, on/off, and channel selector at some distance from the set. The "Senator" costs 68 guineas and is made by *Thorn Electrical Industries Ltd., Thorn House, Upper St. Martin's Lane, London, W.C.2.*

Spares Units for TV Cameras

A FEATURE of the Beulah range of closed circuit television cameras is the unit construction which they employ. This allows unskilled labour to be used to replace parts of the camera quickly and easily.

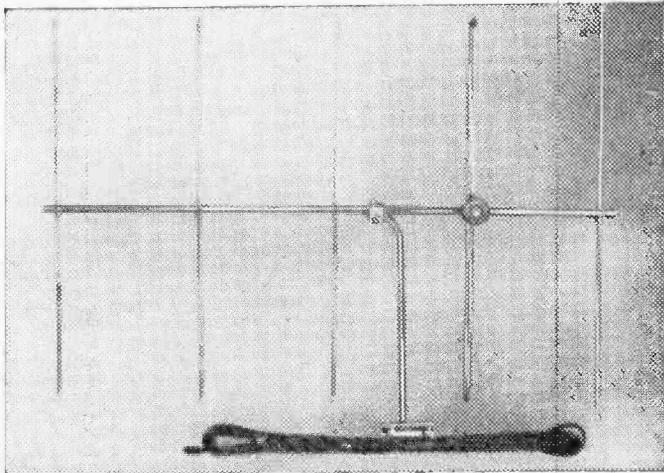The makers of this camera Beulah Electronics, supply spare-part kits, which consist of a pulse unit, a video chassis, a



A complete Band III aerial which can be made from a Ben Nevis kit.

scanning chassis and a power supply. Never more than nine connections are required in fitting any of these units. The Beulah D800 camera and spares kit are manufactured by *Beulah Electronics, 138 Lewisham Way, New Cross, London, S.E.14.*

Aerial Kit for Band III


ON display at the recent Scottish Council Exhibition, held in London, were several of the Ben Nevis range of aerials, including a kit which, when assembled, makes a complete Band III aerial, for either horizontal or vertical polarisation. These aerials are suitable for use anywhere in Britain and can be mounted on a mast, chimney or in a loft.

Complete with each kit comes 45ft of coaxial cable with a plug already fitted. Ben Nevis aerials are manufactured by *Andrew Sloss, Belmont Works, Belmont Site, Lewis Street, Stranraer, Scotland.*

New Cathode Ray Tube

THE LD603, a new 5in. instrument cathode ray tube by the M-O Valve Co. Ltd., is currently being prepared for production. By mounting a mesh about an inch behind the screen, this CRT eliminates the loss of deflection sensitivity and scanned area which occurs in existing post deflection accelerators; and the post deflection acceleration of this tube becomes 100per cent efficient.

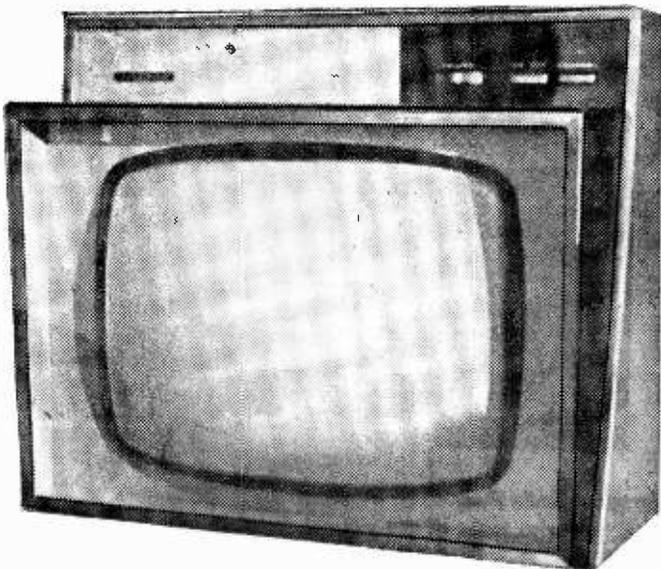In the LD603, this principle has been employed



The "Senator" television receiver, made by Ferguson, features a remote control unit.

to reduce a tube possessing three times the deflection sensitivity of helical p.d.a. tubes, while maintaining a scanned area of 10cm x 6cm. An additional advantage of this method of p.d.a. is its greater freedom from pattern distortion and deflection defocusing. The LD603 has been developed by *The M-O Valve Co. Ltd., Brook Green, London, W.6.*

ADJUSTING TV TUNERS

(Continued from page 567)

This must be done with a thin non-metallic screwdriver inserted into the opening (to the rear of casing, on the V2 side) adjusting L7 for optimum sound. The location as indicated is on the left side, with the tuner in an upright position and viewed from the front. On no account must a larger tool than necessary be used and only very light pressure is required. Failure to observe this will result in damage to the oscillator coil and former.

Semi-Incremental Tuners

In recent years Sobell and McMichael receivers have been fitted with fourteen-position switched tuners of the above type. This tuner is larger than the "Fireball" and uses two rotating discs, one carrying the aerial coils and segments, the other the R.F. and oscillator.

The fine tuner, which is worm driven, is only fully contacted in the fourteenth position which is VHF/F.M. Its effect on Band I is therefore a little restricted and this tends to necessitate realignment of the Band I oscillator coil core occasionally.

Oscillator Tuning

This is carried out from the front of the tuner,

this being exposed by removing the side knobs and panel. The selector is switched to the desired channel and the fine tuner is turned midway. Access to the oscillator cores is by three holes in the front of the tuner. When only one core is visible this should be set for *maximum sound*. When two cores are visible the core nearer to the fine tuner spindle should be adjusted for maximum sound.


Servicing

The unit is held by three 4B.A. screws. With these removed and the connecting leads unsoldered, it can normally be removed through the side of the chassis. Always ensure that the nylon lug engages the hole in the coupler unit on the fine tuner spindle, when refitting.

Resistor Check

The notes referring to the PCF80 triode section anode feed resistor mentioned in connection with the Fireball tuner should also be applied to the Sobell model. A single resistor R11 is used and the value is 10k. Weak Band III reception or no reception on one or all bands should direct attention to this resistor after the valves have been checked. ■

COMPLETE 17ins. TV
£11-10-0

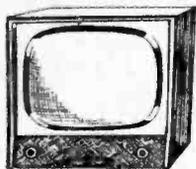

An excellent ex-Rental Table model. Famous manufacturer, Tuned ITA/BBC. Guaranteed 12 months. Terms available. Personal collection advised. Special delivery rate by arrangement up to 50 miles, or despatched in 3 parcels for easy assembly, 25/- extra.

VALVES

1/9d. Each Salvage Guaranteed 17 6d. Doz.

11C6, 6AG6, 6AK8, 6AM6, 6C4, 6F1, 6F12, 6F13, 6F14, 6F15, 6K7, 6LD, 6P25, 6P28, 6U4, 7C5, 7Q7, 7Y4, 813, 128J7, 128K7, 14H7, D77, DH77, EB41, EBC41, EBC80, EF39, EF41, EF91, K761, N142.


2/9d. Each. 6C16, 6L1, 6L18, 6SN7, 6U4GT, 10D1, 10P13, 10P14, 12AT7, 12AU7, 12BE6, 20D1, 20P3, 25A6, 25RE, 25Z4, 35L6, 42, 43, 807, 874, APV4, B36, ECC31, ECC34, L83, ECC81, ECC82, ECC83, ECC85, ECU91, ECH42, U22.

5/9d. Each. 6016, 6L1, 6L18, 6SN7, 6U4GT, 10D1, 10P13, 10P14, 12AT7, 12AU7, 12BE6, 20D1, 20P3, 25A6, 25RE, 25Z4, 35L6, 42, 43, 807, 874, APV4, B36, ECC31, ECC34, L83, ECC81, ECC82, ECC83, ECC85, ECU91, ECH42, U22.

POSTAGE: On 1 valve—7d. On 6—1/6d. On 12—3/6d.

14 INCH TUBES 36/24 35/-
Salvage purchase of guaranteed replacement tubes. Carriage 5/-.

REBUILT REPLACEMENTS

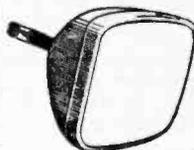

12
Months'
Guarantee

2lin. 99/6 } H.P.
17in. 90/- } T
15, 14, 12in. 70/- } E
R
M
S

Ins. carr., 15/6.

£1 extra without old bowl, refundable if same received within 14 days.

MULLARD TRANSISTORS
47/6 Set

6 and 1 Diode.

1 OC81D 6/9 1 OC44 9/9
Pair OC81 6/9 Pair OC45 8/9
1 Diode 1/9.

G.E.C.

114 6/9, 874 9/9, 873 8/9.

EDISWAN

XC121 and XB113 8/9d. each.

POST FREE

SPEAKER BARGAINS

MINIATURE SPEAKER 16/9. Brand new, 2 1/2 and 3in. Post and Packing 1/-.

ELLIPTICAL SPEAKERS 15/9. Slot type, New. 7 x 4 and 8 x 3in. Postage and Packing 2/9.

SPEAKER SALE, 8/9. All sizes, 5, 6, 8 and 7 x 4in. Manufacturer's salvage. Money back guaranteed. Post and Packing 2/9.

DUKE & CO. (LONDON) LTD.

621/3 Romford Road, Manor Park, E.12.

ILF 6001/3

SEND FOR FREE LIST

RECORD PLAYER CABINET

69/6



Luxury cabinet in two tone coffee colour. Size 15 1/2 x 17 x 9 1/2in. Takes all popular record player units and amplifiers. Position for 6" speaker. Detachable lid for Stereo conversion or extra speaker. P. & P. 4/6.

ALL TUBES

NEW

Guaranteed 12 months
Carriage FREE
Speedy Passenger Train despatch

12"	MW31-74 etc.	£5.5.0
14"	MW36-24 etc.	£6.6.0
17"	(in short supply) CRM171, 172	£7.0.0

COMPLETELY REPROCESSED

TO MAKERS' SPECIFICATIONS!

REBUILT, RESCREENED, REALUMINISED TUBES OF THE HIGHEST QUALITY

14"	£5.5.0
15"-17"	£5.10.0
21"	£8.0.0

THAT "DIFFICULT" TUBE? LET US QUOTE

ASTOUNDING BARGAIN! The "Clarion" Transistor Battery Tape Recorder. Push-button controls, 3 1/2 i.p.s. Portable. Durable plastic case. List price 25 gns. Complete with Mike and Tape. Our Price ONLY **16** GNS. Carr 7/6.

TRADE ENQUIRIES INVITED

LINE OUTPUT TRANSFORMERS

Direct Replacements for 500 sets.

Baird, T29, T183	53/-
T164, T167, T172, 2014, 1712	60/-
Bush, TV 11A, B; 12A, B; TVF 12A,	45/-
TUG12A, B; TRG 12A, B	60/-
TV12AM, TV 22, 24; TRG24, TUG24	58/-
Cossor, 930, 931, 933, 934, 948, etc.	45/-
Ekeo, TS146; TS113-114; T161	50/-
T221, 231; TSC311, etc.	55/-
Ferguson, 841, 2, 3; 941 to 945	68/6
990T-998T; 103-143T; 203-246T	45/-
Ferranti, 1473, 1474, 17K3, 17T3	12325
14T2, T1205, T1215, T1225, T1325,	65/-
T1405, T1415, T1425, T1505, T1825	50/-
G.P.C. and H.M.V. mostly 55/- to	52/-
Invicta, T101-104; T106-110	60/-
T114-126; T133-142	45/-
Murphy, V114C, V116C, V118C	57/6
V120C, V180, V178, V200, V202C	68/-
V240, 250	60/6
Philips, 114, UF7M; 1115 U, 1437 U,	65/-
1446 U, 1736 U, 1746 U, 1747 U	60/-
383A, 483A, 563A, 683A	60/-
Pye, LV30, 16T, CS17, VT17	52/6
CTM4, V4, VT4, VT, VT7	85/-
Ultra, 814, 815, 817, 915, 917	17/60-4,
VYA730, YVW84, VVW720, V710	17/70-1-2, 21/50, 21/60, 21/70-1-2
(complete assembly with U25)	60/-
14/53, 15/60, 17/50, 17/53, 17/60, 17/63-4,	26/6
17/70-1-2, 21/50, 21/60, 21/70-1-2	26/6
All Ultra Frame O.P.T.'s	26/6

100 mixed resistors. 1W-2W — 7/6 post 1s.
ANOTHER BARGAIN. Complete set of 6 NEWMARKET High Gain Transistors and 1 Diode. Individually selected for max. gain and stability. Equip. OC44, OC45(2), OC71, OC74 (matched pair). ONLY £2. Valves, Multimeters, Record Players, Tape Recorder Decks, see previous issues.

S.A.E. with enquiries please.
5 Westward Way
Preston Road, Harrow, Middx.
Tel. WOR 2663

WESTWAY RADIO

"WAVE GUIDE AERIALS"

Manufacturers of TV Radio and Ham Transmitting Antennas wish to offer examples from their range of products. For the amateur Enthusiast and the Do-it-Yourself type.

A SUPER HIGH GAIN ARRAY FOR THOSE DIFFICULT RECEPTION SPOTS

	£ s. d.		£ s. d.
3 Element BBC Folded Dipole, Channel I, with a Double Five Channel 9 ITA, complete with all clamps	7 10 0	5 Element ITA loft Aerial	1 6 0
or Double Eight Element ITA	8 10 0	8 Element ITA Aerial outdoor	2 9 4
Mast Equipment per your specification extra		Double 5 ITA Super Fringe outdoor Aerial	4 0 0
S/D 5 Combined BBC, ITA Loft Aerial	1 10 0	Double 8 ITA Super Fringe outdoor Aerial	5 0 0
S/D 5 Combined BBC, ITA Outdoor Aerial, wall mounting, complete ...	2 13 6	32ft. Garden Masts, complete for erection, two sets guy pickets, etc., with fitting instructions	12 10 0
H & 7 combined BBC, ITA with chimney lashing equipment	4 13 0	Coax Cable semi low loss, 7d. per yard; super low loss 1/2d. per yard.	
BBC Loft Aerial	12 9	Cross over boxes for combining separate BBC and ITA Aerials 9/6d.	
V.H.F. Loft Aerial	11 3	Please send 6d. stamp for full list of aerials and accessories. Terms C.W.O. orders over £4 post and packing free.	
5 Element ITA Aerial for attaching to existing mast	1 10 0		

PLEASE STATE CHANNELS REQUIRED WHEN ORDERING

WAVE GUIDE AERIALS

MIDLAND BANK CHAMBERS, FORE STREET, HERTFORD

TELEVISION TUBES

RE-GUNNED. Super screen TV tubes with a 12 months' guarantee. Tubes all types 12in. to 14in. ... £4.5.0
Tubes all types 15in. to 17in. ... £4.15.0
Carriage and insurance 10/- extra.
Allowance against the return of old tube

RECTIFIERS

RMI 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RM5 19/6, 1A486 19/6, 1A497 19/6, 1A4100 19/6, LW7 17/6, 18RA 1-1-16-1 6/-, FC31 (14RA 1-2-8-3) 22/6, FC101 (14RA 1-2-8-2) 10/6.

REDUCTIONS IN MULLARD TRANSISTORS

OC19 48/-	OC72 8/-	OC78D 8/-
OC35 25/6	OC72pr 16/-	OC81 8/-
OC44 11/-	OC73 16/-	OC84 11/-
OC45 10/-	OC75 8/-	OC170 13/6
OC70 6/6	OC77 10/-	OC171 14/6
OC71 6/6	OC78 8/-	OC202 36/-

A SPECIAL OFFER OF SIX MULLARD TRANSISTORS

1 OC44, 2 OC45, 1 OC81D, 2 OC81.
Only 37/6 set.

EDISWAN TRANSISTORS

XA104 12/-, XA103 10/-, XB102 6/6 ea.

ALPHA RADIO SUPPLY CO.

VALVES BY RETURN POST

AZ1 10/-	EY51 9/6	UCC8410/11
DAF96 8/-	EZ40 7/6	UCH42 9/6
DK96 8/-	EZ80 7/-	UCL82 11/6
EABC80 9/-	FC13 5/-	UCL83 16/-
EB91 4/6	GZ32 11/6	UF85 9/-
EBC33 6/9	HL42DD	UL41 9/-
EBF80 9/9	OZ4 10/-	UU6 19/3
ECC81 8/-	OZ4 4/6	UY41 6/6
ECC83 9/6	PCC83 13/6	VP23 5/-
ECC85 9/6	PCC84 8/6	VR105/30 8/-
ECC87 10/6	PCC85 11/6	VR150/307/6
ECH81 9/-	PCF80 8/9	VU39 (MU
ECL82 10/6	PCF82 11/6	12/14) 8/9
EF36 3/6	PL36 13/6	1A7G 13/6
EF50 5/-	PL81 11/-	1C5G 12/6
EF80 7/-	PL82 8/6	IN5 10/6
EF86 12/6	PX25 12/6	1S5 6/6
EF91 5/9	PY81 8/6	3D6 5/-
EF92 6/-	PEN25 5/-	3Q5GT 9/6
EL32 4/6	U25 13/6	3V4 8/-
EL41 9/-	U50 8/-	5R4GY 9/6
EL91 4/6	UAF42 9/6	5V4 11/6
EM80 9/6	UBC81 11/4	5Y3GT 7/6

LIGHTWEIGHT SOLDERING IRON

Latest design for use on 200/250 volts, with detachable handle, can be carried quite comfortably in pocket, 18/9 each.

RECORDING TAPE

Special Offer of Top quality recording tape, 3 1/2 in. spool 200ft. 5/3, 5 in. spool 600ft. 13/9, 5 1/2 in. spool 850ft. 18/6, 7 in. spool 1200ft. 23/-. Extra-play tape, 3 1/2 in. spool 300ft. 7/-. 5 in. spool 900ft. 21/-. 5 1/2 in. spool 1275ft. 26/6, 7 in. spool 1800ft. 37/6.
Empty spools, 3 1/2 in. 1/6, 5 in. 2/-. 7 in. 3/-.

CATALOGUE

OUR 1962 CATALOGUE IS NOW AVAILABLE. PLEASE SEND 1/- IN STAMPS FOR YOUR COPY. TRADE CATALOGUE ALSO AVAILABLE, FOR WHICH PLEASE ATTACH YOUR BUSINESS LETTER HEADING

TAPE DECKS

Collaro Studio Tape Transcriber 3 motors, 3 speeds, 1 1/2, 3 1/2, 7 1/2 i.p.s., take 7 in. spool. Push-button control. Price £12.12.0. Tape extra. Carr. & Ins. 5/6.

Latest B.S.R. "Monardeck" Single Speed

3 1/2 i.p.s. takes 5 1/2 in. spools. Simple controls. £8.8.0. Tapes extra. Carr. and Ins. 5/6.

ALPHA RADIO TERMS.—Cash with or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 1/3; 20/- add 1/6; 40/- add 2/6; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

ALPHA FOR VALVES AND SPARES FROM STOCK

103 LEEDS TERRACE, WINTOUN STREET, LEEDS 7.

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

SPECIAL NOTE: Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

TELEVISION AERIALS

SIR,—I have noted in the past that readers have asked questions concerning the reception of two or more stations; where they were able to pick these up. What is the position, however, where a viewer is able to receive two stations, one of which is vertically, and the other horizontally polarised? Does one have to rotate the aerial, or does it mean that yet another monstrosity has to be put on the roof. What with F.M., normal radio and the TV our houses will soon have to be specially designed to carry the aerials—or is there some way in which all of these, including right-angled polarisation, may be received on one aerial—perhaps of a type which has not yet been designed.—G. BATES (Northampton).

NOVEL AERIAL

SIR,—After reading the letter by N. A. S. Payn in the June issue, I thought perhaps he and other readers might be interested to know that I have been operating a receiver for a long while on little more than a yard of unscreened multistrand wire, and obtaining a very good picture.

The wire hangs from a picture rail and is connected to the centre pin of the aerial socket. However, a few weeks ago a new television was installed and when both new and old are on together (on BBC), the sound on the older model breaks through on to the vision. When the new receiver is switched off the interference stops. I assume that this is due to the simple aerial of the old television.—D. E. O'CONNOR (Wanstead).

CHANNEL CHANGING

SIR,—Of late the programme material has deteriorated on both channels so that it has become necessary for me to make more constant changes from one channel to another. Previously, I could tolerate one channel an evening, but I find that now I sometimes have to change five or six times in one evening, and I think that the modern tuner is unsuitable for this purpose. I have to go through eight unused channels before I obtain the new station, and I would have thought it would not have been beyond the capability of the manufacturers either to have made a tuner with wafers which could be arranged so that the viewer in any part of the country could re-position them so as to bring his alternatives next to each other, or to

make tuners with just two switched positions (or three perhaps)—again with wafers to suit the locality. In the absence of such units, could not someone tell us how to modify the more popular tuners, i.e. Cyldon, Fireball, etc., so as to obtain this desirable feature?—F. R. OLIVANT (N.W.).

COLOUR TELEVISION

SIR,—It is very obvious that on many transmissions which are now radiated, the colour system is being used. No doubt this is for the benefit of certain sections of the BBC and ITV, but it is very hard on the poor viewer, who is not at the moment interested. If you look closely you can see there is a "walking" pattern over the picture, and the contrast is very much poorer than a standard black and white transmission. We are told that the colour system, when it is adopted, must be compatible, but it appears to be far from that at the moment. Another thing I would like to criticise is the way the producers play about with the lighting, doing clever tricks with light and shade. I suppose they call it arty-crafty, but unless you are prepared to keep adjusting your contrast control, you do not know whether your set is going wrong or they are just being clever. In the Black and White Minstrel shows, for instance, the faces are lost most of the time, and how often do we see singers in deep shadow, without the slightest details to help us to identify them? Could not the lighting be standardised so that we would know our sets were all right?—D. G. BEST (Watford).

SIR,—I noted in a recent press report that the tubes which are now being used in experimental commercial colour receivers are of American origin, and are actually imported under licence as no British manufacturer is allowed to manufacture them. This is surely a bottle-neck which must be broken! Are we to rely upon an imported item, without which the set will not function? It is to be hoped that sooner or later an alternative to this complicated system of colour television will be invented in which standard items will be used—or, at the very least, in which a much simplified form of tube may be employed. It would appear that there is still much to be said for the use of rotating glass filters which could be used with standard tubes. Did I not see, at an exhibition some time or another, a scheme in which three standard tubes, each with a separate coloured filter in front of it, were so placed as to be seen simultaneously through a single opening in the cabinet, and the combined image was in colour and indistinguishable from the orthodox colour picture as seen on a modern tube? Perhaps some reader has technical details of such a scheme or can remember the details and maker.—F. R. WESTBURY (Penge).

SIR.—I was most interested in your articles on colour in the last two issues, but this will not be of much use for receiving modern colour systems. Cannot something be published which will help us to construct units to add to our sets to pick up the experimental transmissions? I know that the tubes cannot be obtained, but is there anything which would show how the test was proceeding? I feel that there is a real need here for one of the service engineers on your staff to produce something for the home constructor as this will afford us a vast new field for experiment.—**D. J. ATKINS** (Gloucester).

AN UNUSUAL FAULT

SIR.—I recently experienced erratic effects on my TV set, and finally found a trouble which might occur to others and the experience might be of assistance to your readers. The frame kept collapsing, and operating the frame hold control would restore it only temporarily. I finally bought a new control, but the effect was still there. A substitute valve was to hand but gave no improvement. It was decided, as it happens, correctly, that the oscillator stage was responsible, and all parts in this stage were removed and tested on an R/C bridge, and apart from two resistors, tests were satisfactory. The resistors were replaced and all parts were put back and that evening the same trouble recurred. To cut a long story short, after much testing, the charging condenser in the oscillator stage was found faulty, in the form of an intermittent open circuit. When tested on the bridge it functioned correctly (no voltage across it?), but under use it broke down periodically. It would appear, therefore, that when testing condensers, the maximum voltage should be put across them, but perhaps peak voltages might be important also.—**F. TRIMBLE** (Lewisham).

MAINS FREQUENCY LOCKING

SIR.—A fault which I often see on friends' sets is false line lock, where a dark line appears across the middle of the screen, with the bottom of the picture at the top and vice versa. I believe this is due to the mains frequency triggering the frame timebase, but I am not sure of this. The frame frequency is 50c/s and this would appear to be due to the fact that the mains are, in fact, employed in the transmitting circuits to triggering, and if so, how can they prove stronger than a signal, or is there some more intricate reason for both the 50c/s frame frequency and the false line lock? I would be glad to see a discussion on this subject.—**R. MEADOWS** (Harrow).

LONG-DISTANCE RECEPTION

SIR.—I would like to know of anyone who has picked up television signals up to a hundred miles or more. I have done this at different times on channels 9, 10, 11, 1, 2 and 5. The signal strength varies. I have achieved this by juggling with the tuning coils at the back of the set, but am always able to put them back in their original places to receive normal channels 8 and 4. Channel 9 Granada television is the strongest of all the ITV channels; channel 2 is usually the strongest of all the BBC channels. Horizontal lines moving down the screen spoil the signals and, at times, the London ITV transmitter inter-

feres with the signals coming in from the north on the same channel and helps to spoil the northern picture, which is always stronger. The aerial is an ordinary BBC dipole with a 5-element ITV combined. I am very interested in TV reception and would be very pleased to hear from anyone else who has picked up television signals from a transmitter that is 100 miles or more away from the receiving point with an aerial of the type I have mentioned.—**R. FRANKLIN** (105 Redditch Road, Studley, Warwickshire).

MANUFACTURERS' SURPLUS

SIR.—From time to time your pages carry advertisements from firms who deal in the supply of surplus items. Many of these look most attractive and seem, on the face of it, to be suitable for a particular purpose. However, one is rather doubtful about using them, and the manufacturers will not, naturally supply information about them. I remember some time ago you did a complete instrument built from such parts, but the difficulty is that stocks are limited. Would it not be a good idea for the firms dealing with such items to issue leaflets giving the most salient details so that those of us who are interested could try and make conversions where necessary or could adapt our equipment so as to make full use of them? I feel that there is a very good need for such information.—**G. BANGAY** (Lowestoft).

INDOOR AERIALS

SIR.—I would like to point out that many cases of unsatisfactory results with indoor aerials are due to pipes and similar items inside walls. I recently called on an acquaintance and he was sadly bemoaning money spent on a popular "V" type of indoor aerial. I told him I thought they were very good and he switched on and showed a very poor picture which no adjustment of the arms of the "V" would improve. I then moved the aerial a few yards to the side and he was astounded at the improvement (he thought the aerial had to stand on the set!) The trouble here was that there was a comprehensive run of hot and cold water pipes in the wall immediately behind the set and these screened most effectively the aerial from his particular local station. It was also found in this particular case that opening and closing the door made most remarkable variations in the brightness of the received signal.—**R. BARRINGTON** (Highbury).

PAY-AS-YOU-SEE TELEVISION

SIR.—In Canada, I believe, "Pay-as-you-see" TV is already past the experimental stage, and in one region, at least, is used by many of the viewing public. When, I wonder, will we see this development in Britain? Its advent will almost certainly draw as much attention as the long-discussed colour and line standard problems, and will probably give rise to even more controversy.

From what I have read about this system, the programmes are carried through wire to the receiver and not as transmitted signals. Is this the only possible means to obtain pay-TV, or can our present system be modified to give the same results? Surely an addition could be made to existing receivers so that the amount of television seen could be controlled in the same way that gas is used from a gas-meter. This would, I am sure, make a satisfactory arrangement.—**K. AUSTIN** (Pershore).

For Safety's Sake
use
AVO Prodclips

Pat. No. 748811

.. with Trigger-Action Spring-Loaded Clips

PRESS TRIGGER TO OPEN

RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Post Free
15/-
per pair.

AVO LTD. • AVOCET HOUSE,
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
Victoria 3404 (12 lines)

M A Member of the Metal Industries Group of Companies

HARVERSON SURPLUS CO. LTD.
83 HIGH ST., MERTON, S.W.19. Cherrywood 3985/6/7

F.M. TUNER KIT

At last a quality F.M. Tuner Kit at a price you can afford. Just look at these fine features which are usually associated with equipment at twice the price!

- ★ F.M. Tuning Head by famous maker. ★ Guaranteed Non-drift. ★ Permanently Tuning. ★ Frequency coverage 88-100 Mc/s. ★ O.A.B. Balanced Diode Output. ★ Two I.F. Stages and Discriminator. ★ E.M.84 Magic Eye. ★ Self-powered, using a good quality mains transformer and valve rectifier. ★ Valves used ECC85, two EF80's. EM84 (Magic Eye) and EZ80 (rectifier). ★ Fully drilled chassis. ★ Everything supplied, down to the last nut and bolt. ★ Size of completed tuner 8 x 6 x 5 1/2 in.

All parts sold separately. **★ £4.19.6** Plus 8/6 P.P. & Ins.

Circuit diagram and illustrations, 1/6 post free.

Note:—To show the chassis clearly the attractive dial supplied is not shown.

TELEVISION TUBE BARGAINS

COSSOR 108K 10-in. New & boxed, 15/-, plus 6/- P. & P. & 75K 10-in. New & boxed, 15/-, plus 6/- P. & P. Ion trap magnets to suit the above, 2/9, 3d. P. & P.

17in. MAZDA CRM 172
Not a Regun. Picture tested—**£3.17.6** P. & P. 12 months' Guarantee. 12/6

"6 plus 1" TRANSISTOR RADIO KIT
— UNBEATABLE VALUE —

Mrs. Current Production Offer—A fortunate date purchase enables us to offer one of the season's most outstanding bargains in Portable Transistor Radio Kits. This kit is a modern, sensitive quality circuit Receiver Unit with all the latest features. Six B.V.A. Transistors and 1 Diode, Printed Circuit, Med. and Long Waves, Ferrite Aerial, Car Radio Input, \pm w Push-Pull output into 3 ohm Speaker, Calibrated Dial and Slow Motion Tuning, etc. Size: Approx. 8 1/2 x 2 1/2 in.

COMPONENT KIT 5 Gns. SET OF 6 TRANSISTORS and 1 DIODE **45/-**
p. & p. 2/6

7 x 3 1/2 in. Speaker **15/6** carr. 1/6. Complete Kit (less speaker) Bargain Price **£6.19.6** carr. 2/6. 3d. stamp, full details Circuit and Instrn. **1/6** Cabinets 2/- extra.

NEW VALVES	ALL GUARANTEED	TRANSISTOR BARGAINS!
1T4	6/- EF86	12/6
1R5, 1R5	7/6 EL84	3/6
3B4, 3V4	7/6 EY51	9/6
DAF96	9/- EY88	10/-
DF96	9/- EZ80/81	7/6
DK96	9/- PC84	9/6
DL96	9/- PCF80	9/6
ECL80	10/6 PCL83	18/6
ECL82	10/6 PL81	12/6
EF80	8/- U25	12/6

BRAND NEW—BVA 1st Grade
OC44 10/8 874
OC45 9/6 873
OC81D 7/6 GET114
9/OC81 18/6 OC79
X A102 10/- OC70
X A101 9/6 OC71
X B103 7/6 GEX34
XC101 3/6 O A70
8B305 9/6 OA81

SPEAKER FRET. Expanded Bronze anodised metal 8 x 8 in., 2/3; 12 x 8 in., 3/-; 12x12 in., 4/6; 12x16 in., 6/- etc.

TYGAN FRET (Contemp. pattern) 12 x 12 in., 2/-; 12 x 18 in., 3/-, etc.

CONDENSERS—Silver Mica. All values, 2 pF to 1,000 pF., 6d. each. Ditto. ceramiles 9d. Tub. 450 v. T.C.C., etc., .001 mid., .01 and 1/500 v., 9d.; .02-1/500 v., 1/-; .25 Hunts 1/8; 5 T.C.C. 1/9, etc., etc.

RESISTORS—FULL RANGE 10 ohms—10 megohms 20% \pm w. and \pm w., 8d.; 1 w., 5d.; (Midget type 4 modern rating), 1 w., 6d.; 2 w., 9d.; 10% Hi-Stab., 1 w., 5d.; 1 w., 7d.; 5% 1w., 9d.; 1% Hi-Stab., 1 w., 1/6. W/W RESISTORS, 26 ohms to 10K, 5 w., 1/8; 10 w., 1/8; 15 w., 2/-.

PRE-SET T/V POT. Full range 26 ohms—2 meg., 3/-.

SPEAKERS P.M. 3 ohms 2 1/2 in. Elac., 17/6. 3 1/2 in. Goodmans, 18/6. 5 in. Rola, 17/6. 6 in. Elac., 18/6. 7 x 4 in. Goodmans, 18/6. 8 in. Rola, 20/- 9 x 6 in. Goodmans, 25/- EMI Tweeter, 28/6.

VOLUME CONTROLS—EK—2 Meg-ohm, 3 in. SPINDLES MORGANITE MIDGET TYPE, 1 1/2 in. diam. Guar. 1 year. LOG or LIN ratios less 5w., 3/-; D.P. Sw., 4/6. Twin Stereo less Sw., 5/6. D.P. Sw., 8/-.

Electrolitics All Types New Stock

TUBULAR	CAN TYPES
25/25v. 50/12v.	8+8/450v. 4/6
50/150v., 100/25v. 1/9	32+32/275v. 6/6
50/150v., 100/25v. 2/-	80+50/350v. 6/6
8/450v. 4/850v. 2/3	80+250/375v. 1/6
16+16/450v. 5/6	100+200/375v. 18/6
32+32/450v. 8/6	Transistor Midget Types—all values 1 mid. to 100 mid. 1/6 ea. 6v/12v.

RECORDING TAPE—Special Offer

American COLUMBIA (C.B.R.) 1st Grade P.V.C. TAPE. Fitted leader and auto stop folia. Brand New, Boxed, and fully guaranteed.

Standard	Long Play
5in., 600ft. 15/-	900ft. 19/6
5 1/2 in., 900ft. 18/6	1,200ft. 23/6
7in., 1,200ft. 22/-	1,800ft. 33/-

DOUBLE PLAY and OTHER SIZES AVAILABLE AT SPECIALLY REDUCED PRICES

Plastic Tape Reels 3in. 2/6. 5in. 3/- . 6 1/2 in. 3/3. 7in. 5/6.

TAPE RECORDER KIT ONLY £16 10s.

Latest 5-valve circuit based on Mullard's design. Magic eye and tone controls. Printed circuit already wired. A sensitive quality recorder, B.S.R. Kit 95/-, B.S.R. Tape Deck £8.10.0. Collars Kit £6.5.0. Collars Tape Deck £12.10.0. Set of 5 valves 45/-. Special Unit Kit Prices—Send stamp for detailed list. Handbook (full details) 2/6.

Jason Tuners—Approved Kits—comprehensive range in stock. Model FMT1 5 gns. etc., 48-hour Alignment Service. Send for complete bargain list.

TRS RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY
Telephone THO 2188
Est. 1944
Terms C.F.O. or O.O.D. Post and Packing up to 1/2 lb., 7d., 1 lb. 1/1, 3 lb., 1/6, 5 lb., 2/-, 10 lb., 2/9. Hours: 9 a.m.—6 p.m.; 1 p.m. Weds.

REBUILT TV TUBES—12 Month Guarantee

Complete NEW GUN fitted in EVERY tube

12in. ... £4.00 • 14-15in. ... £4.10.0 • 17in. ... £5.00 • 21in. ... £7.0.0
 Immediate Delivery Allowance on old tube Carriage and Insurance 10/- extra

NU-GUN TELETUBES LTD. 3 THE MEWS, DUCKETT RD., HARRINGAY, N.4
 Telephone: MOUntview 2903

FIRST-CLASS TELEVISION and RADIO COURSES

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compiling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches)** etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING
 (Dept. 462), 148 HOLBORN LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.
 Australia: P.O. Box 4570, Melbourne.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS IR5, IS5, IP4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ... Set 4 for 19/8
 6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 5Y3G ... 4 for 27/8
 ... 5 for 24/6

1A7GT 11/8	6P1 13/6	35A5 14/-	ECC82 6/3	EZ81 7/-	U22 7/8
1D5 8/-	6P25 9/-	35LGT 9/-	ECC83 7/3	FW4/500 8/-	U24 17/6
1H5GT 10/-	6Q7G 8/-	35Z4GT 6/9	ECC84 8/9	GZ30 8/6	U25 13/-
1N5GT 10/-	6L7GT 9/8	35Z5GT 8/6	ECC85 8/9	GZ32 9/6	U26 10/-
IR5 5/8	6SL7GT 6/3	50L5GT 8/9	ECP80 8/6	KT33C 7/7	U56 6/8
IS4 8/-	6SN7GT 4/9	AC/TH1 18/8	ECP82 8/8	KT41 11/8	U52 4/6
IS5 5/6	6U4GT 11/-	AZ31 9/6	ECH21 13/6	KT44 6/8	U78 4/8
IT4 3/6	6V6G 5/8	B36 8/6	ECH35 6/3	KT61 10/-	UAC80 7/9
IU5 5/9	6V8GT 9/8	CL33 12/3	ECH42 8/9	KT63 6/8	UAF12 9/-
3A5 9/-	6X4 4/9	DAC32 10/-	ECH81 8/-	MU14 7/8	UB41 8/6
3Q4 4/6	6X5GT 5/-	DAF91 5/3	ECL80 7/8	MX40 9/8	UBC41 7/9
3S4 6/-	7B6 7/6	DAF96 7/6	ECL82 9/6	N18 7/-	UBF80 8/9
3V4 7/-	7B7 7/6	DDC90 9/-	EPF39 4/6	N37 10/6	UBF89 8/-
5U4GT 4/6	7C5 7/6	DF33 10/-	EPH40 12/6	PC85 10/-	UC92 12/6
5V4 8/-	7C6 7/6	DF91 9/6	EPH41 8/6	PC84 7/8	UCC84 12/9
5Y3GT 6/-	7H7 7/6	DF96 7/6	EPH42 8/6	PC88 7/6	UC85 7/6
5Z4G 7/9	7S7 9/-	DH76 4/9	EPF80 5/3	PCF80 7/9	UCF80 14/-
6AL5 3/9	7Y4 7/-	DH77 6/9	EPF85 5/6	PCF82 8/-	UCH21 13/6
6AM6 3/9	10C2 17/6	DK32 11/8	EPF86 9/6	PCF86 14/6	UCH42 8/-
6AQ5 6/-	10P13 14/6	DK91 5/6	EPF89 7/-	PCL82 9/6	UCH81 8/-
6AT6 6/9	12A7B 7/-	DK92 7/8	EPH43 3/6	PCL83 11/8	UCL82 10/9
6BA8 6/-	12A7T 5/-	DK96 7/6	EPF92 4/6	PCL84 7/8	UCL83 13/3
6BE6 5/9	12A7U 6/3	DL33 9/-	EPF183 14/6	PCL85 13/6	UF41 8/9
6BH6 5/9	12A7X 7/-	DL36 9/6	EL33 10/-	PEN44 11/-	UF42 5/8
6BJ6 5/9	12K7GT 5/3	DL82 9/-	EL41 9/6	PEN36C 8/-	UF85 8/6
6BW6 8/-	12K8GT 11/6	DL94 7/-	EL42 9/-	PL36 11/8	UF89 7/-
6CD6G 26/9	12Q7GT 4/9	DL96 7/6	EL84 7/6	PL81 8/6	UL13 8/6
6F1 12/8	12Z3 7/6	EABC80 7/9	DM34 6/9	PL82 7/8	UL84 7/6
6FG 6/8	145T 18/6	EAF42 8/6	EM80 8/6	PL83 7/8	URIC 8/-
6F13 11/6	20F2 17/6	EB91 9/9	EM81 8/6	FL84 10/-	UY21 11/3
6F14 18/6	20L1 17/6	EBC33 5/-	EM84 10/-	FX32 11/-	UY41 6/6
6K7G 2/6	25A6G 8/-	EBC41 8/-	EY51 7/6	PY80 7/8	UY85 6/6
6K7GT 5/-	25L6GT 7/9	EBF90 8/-	EY84 3/6	PY81 6/9	VP18 9/6
6K8G 6/3	25Z4G 7/8	EBF89 8/9	EY86 7/9	PY82 6/8	VP41 5/-
6K8GT 9/3	25Z6GT 9/8	EBL21 15/6	EZ40 6/9	PY83 7/9	W76 5/3
6L18 10/3	30L15 11/-	ECC40 15/-	EZ41 7/-	EZ30 17/6	W77 4/6
6LD20 8/-	30P12 7/-	ECC81 5/-	EZ80 6/3	T41 9/8	Z77 3/6

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587

Post 6d. per valve extra.
 Any Parcel insured Against Damage in Transit 6d. extra.
 Any C.O.D. Parcel 3/- extra.

P.P. COMPONENTS LTD.

219 ILFORD LANE, ILFORD, ESSEX
 Stamp for FREE Catalogue
EXTENSION SPEAKERS 19/9
 Polished Cabinet. With 8in. P.M. Speaker, flex & switch. Ideal for Kitchen, Bedroom, Workshop & Carr. 3/9d.



VALVES REVISED LIST

9d. each. 7/8d. Doz.
 4D1, 6AK5, 6AL5, 6AQ5, 6CH6, 6D1, 6D2, 6H6, 6D2, 9D2, 10C1, 10C2, 10F3, 12V4, 15D2, 75, 77, 78, 80, 2050, 2151, 7193, 4CP4, AR6, A1510, C2C, CV68, D1, DL2, EA50, EB34, EB91, EF34, EF36, EF50, HL41(D), HL42(D), KT26S, LP2, P41, P61, SP41, SP61, T41, TT1, VR35, VR37, VR51, VR106, VR107, VR108, VR109, VR137, VR201, W150, Z68, Z69,
 1/9d. Each. 17/6d. Doz.
 1L08, 6AG6, 6AK9, 6AM6, 6AT6, 6C4, 6D6, 6F1, 6F12, 6F13, 6F14, 6F15, 6K7, 6K8, 6LD, 6P25, 6P28, 6SL7, 6U4, 7C5, 7Q7, 8D3, 12XJ7, 12XK7, 14B7, D77, EB41, EBC41, EBC80, EP30, EP91, K761, N142, PEN45, PEN40, W61M, W148, Z77,
 2/9d. Each. 30/-d. Doz.
 1C2, 1C3, 184, 185, 3V4, 6BX6, 6C10, 6L1, 6L18, 6U4GT, 10D1, 10P1, 10P13, 10P14, 12A7T, 12A7U, 12BE6, 18, 20D1, 20F3, 25A6, 25B6, 25Z4, 25Z5, 35L6, 42, 43, 874, 898, CY1, DAF91, DH76, DK96, DL94, EBF80, ECC31,
 Post 1-7d; 8-1/8; 12-2/6d.

CLARKSON'S TUBE CHANGE

6A DENISON ROAD, LEEDS 2 Tel. Leeds 24576

We are now able to offer SUPER SCREEN TV TUBES with 12 months' guarantee at the keenest exchange price ever.

Example:

Tubes all Types	Cash allowance on return of old tube	Actual Cost of Tube
12" — 14" : £5	15/-	£4. 5. 0
15" — 17" : £6	25/-	£4. 15. 0
21" : £8	30/-	£6. 10. 0

Carriage and Insurance 10/- extra

These tubes are COMPLETELY REBUILT by experts, with the most up-to-date electronic equipment, and are fitted with the famous American Golden Grid Electron Gun. Many thousands of these tubes are in service today. Our factory is open to inspection to readers of "Practical TV". Technical advice and queries are answered free of obligation. All tubes are dispatched with adhesive paper and return labels. Cash allowance is sent on receipt of old tube.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 583 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

DECCA 222

This set is for use with 200-250V 50c/s A.C. mains. The set receives BBC only. I should like your advice as to the most suitable converter to use, how much work is involved and the approximate cost of converting this set.—W. Lewis (Port Talbot).

The Decca 222 can be very easily converted by the use of a Cyldon P10L or Brayhead 10s turret tuner. If purchased at the retail price as advertised these have R.F. and mixer plugs which simply replace the V1 and V2 EF80 valves respectively. V1 is the rear right side EF80. V2 is to the right of the triangular tuner unit. You will require the unit, an aerial suitable for the area, and cable. The approximate cost is £10.

STELLA ST2717U

I have used this set in the Midlands for three years, and six months ago I came to North Wales and used the same attic aerials. I have had good results until recently, when I changed from ITV channel 9 to BBC channel 2. The picture narrowed on the screen, dark down the centre with a lighter picture on the sides, causing a double and treble picture. Would you enlighten me as to what is the cause? I followed the instruction booklet for the width control, but this does not have any effect.—T. Treadwell (Llandudno).

First try a replacement PL81 line oscillator/output valve. Then test the PY32 and ensure the ion trap magnet on the rear of the tube neck is correctly adjusted and that the controls are correctly set up; line hold, etc. The PL81 is the valve next to the PY81 on the right side as viewed from the rear (with top caps to each).

BAIRD P2017

The following faults have developed in my set: vertical lines broken; picture breaks up (this is not a complete break up, but takes the form of a horizontal bar varying in width in lower half of the screen).

The vertical lines are straightened if the contrast

control is advanced to a point where there is hardly any difference between black and white, this also clears the bar effect. The bar is also cleared for a short time when the line hold control is turned to the right. (Altering volume control does not have any effect.) When the volume control is advanced operation of contrast control causes a scratching noise in the loudspeaker.—B. Morgan (Caerphilly).

There is a 5pF capacitor between pin 6 of the sync separator (frame oscillator) ECL80 (V9) and the line oscillator (frame output V10) ECL80, pin 1. Change this capacitor and check other sync separator components. Examine picture for ghost images and resite or redirect aerial if necessary to clear these.

VIDOR

I would like to change the valves in this set for new ones but the numbers have worn off and the dealers say they cannot test them without knowing the valve numbers. Also the picture has closed up into a line across the screen. Can you tell me the trouble? The sound is perfect and normally the picture is very good.—R. Franklin (Burton-on-Trent).

We would advise you not to replace the valves unnecessarily. You should replace the 6K25 (grey metallised valve on the left centre); first check the EL41 on the rear right side, and if necessary the 0.5µF capacitors under the chassis near the 6K25 valve base.

MARCONI V.T. 68DA

The fault on this set is short frame scan. This is about ½ in. top and bottom when the set is first switched on and will creep up and down equally to about 1 in. top and bottom. There is also a fault in the tuner and I get white splashes going across the screen from right to left when the set is switched to BBC but the raster is correct when switched to the other channel. As this is an incremental tuner I notice that after a certain point is reached as I go from channel 10 to 3 I get the splashing effect.—J Blackshaw (Glasgow).

To cure the lack of height, replace the LN152 frame oscillator output valve. If there is no improvement, check associated resistors and capacitors. The splashing effect is likely to be due to poor contact on one of the tuner switch banks or the pressure of a component against a contact. Check by probing with an insulated tool. The effect could be caused by instability in the tuner or I.F. circuit: check decoupling capacitors.

DEFIANT TRI453T

Although I have been unable to obtain a service sheet for this set I have a service sheet for a Marconi V.T.63DA which looks the same. Can you tell me if they are the same?

By mistake I put a wrong valve, EF80, instead of ECL80, in V9. Smoke came from the set and PL81 now glows red hot inside, and there is now no line whistle and no EHT. Underneath the T5 transformer is a pile of wax, which seems to have melted from the transformer. I think T5 is a line blocking oscillator transformer, but when I sent it to a firm advertising in your magazine, they informed me that there is no line blocking

oscillator transformer in this model. All the numbers have been taken from the Marconi service sheet.—J. Bendle (Bishop Auckland).

The VT63DA is almost identical to the TR1453T and a line-blocking oscillator transformer is most certainly used. The transformer is probably burned out due to the fact that in an EF80 valve pins 1 and 3 are both cathode connections. This means that H.T. would be applied to pin 1 via the transformer and this direct to chassis through pin 3 of the V9 base.

REGENTONE

This is a second-hand model and although there is no number on it I believe it is a Big 12. I am having trouble with the sound which takes about 15 minutes to become audible, even then with the volume full on it can only just be heard. The valves in the set are 10F1, 30C1, 10C2, 2001, 20F2, ECL80, etc. From this information could you tell me what the trouble could be and the type number of the set?—B. Jones (Pontllanfraith).

Your letter suggests the receiver has a 12in. tube. The valve details given, however, do not substantiate this and the receiver is more likely to be a Big 15/5 or 15T with a 15in. CRM152B tube. In any case you will find the trouble is on the right hand side as viewed from the rear. Check the 10F1 and 10P13 valves and the base voltages, audio coupling capacitors, noise limiter, etc.

COLUMBIA C506

I wish to modify the receiver to receive UTV programmes as well as the BBC. I have unfortunately been unable to obtain a wiring circuit. Perhaps you could advise me regarding the I.F. frequency as I would like to fit either a G.E.C. or Cyldon tuner units advertised, by modifying the oscillator coil.—A. Gent (Co. Antrim).

The Columbia C506 is almost identical to the Sobell T144. The I.F. is 16-19.5Mc/s. A Cyldon P16H turret tuner is suitable. When fitting remember that V2 is an ECL80 (rear left) and that the anode pin of this is 6, not 7 as in the case of an EF80. The rear centre EF80 (V1) can be directly replaced by the R.F. plug.

INVICTA T120

A black line flickers every few seconds across the bottom half of the picture. It also appears to cramp slightly at the bottom. There was a black band at the bottom of the picture, but I have changed PL82 which has cured this, but the flickering and cramping still persist. The brilliance seems to be slightly unstable, especially on outside broadcasts.—A. Nichols (Liverpool).

Check C42 and C43 capacitors and ensure a good contact of the height and linearity controls. We are not sure of what is meant by unstable brilliance. Ensure the EF80 valves are seated properly in their holders. We will advise you further if necessary.

ALBA T321

The trouble is that the picture is stretched on the left. The horizontal form control has little effect on this side of the picture although it increases the width slightly.—K. Stone (Somerset).

You should check the 10k 5W resistor, wired

across the horizontal form coil. If this is of the correct value, check the 3-3k 3W resistor to pin 8 of the PL81.

PHILIPS 1502U

The fault on the above set is as follows: hardly any sound is received: frame instability, receiving three horizontal pictures. The valves and electrolytics have been tested and are all in order. T3, a blocking transformer, was found to be open-circuited and was replaced, but the fault was still present. The H.T. was correct. Both faults appear together. The CRT and three electrolytics, C20, C57 and C75 were renewed 12 months ago.—G. Harris (Canvey Island).

Since you state that the valves and electrolytics are not at fault (we would have suspected electrolytic trouble) we can only suggest that you check the alignment with particular reference to the oscillator trimmer. If the alignment is in order, check the decoupling capacitors by shunting each in turn.

PAM 751

The picture is unobtainable when switching on without first adjusting horizontal hold. The setting required may be at any position of the control when the picture locks—usually a different position each time. Then the picture is perfect. After a time—sometimes an hour, sometimes a minute or two—the picture breaks up into a series of lines. By chance I noticed that by switching off and on the picture is often restored. This has happened before and the set has been in for repair on several occasions, usually with a bill for a PCF80 amongst other things. A new tube was put in in 1959, Mullard 36/44 and new PCF80 early 1960.—N. Allen (Norwich).

Your symptoms are usually caused by a faulty PCF80 as the line oscillator stage is a critical one in which only first-class valves will operate correctly. Later versions of the set use a modified line oscillator circuit, and this modification which virtually entails rebuilding the entire stage, can be fitted to your set and is well worth while. Pam dealers can obtain details and kits of parts from the manufacturers service organisation, where the modification is usually referred to as the "Green Spot" modification.

MURPHY V178C

Whilst servicing this set for a frame fault, I found that a black lead to tube cathode had come adrift. At 6F13 is video amplifier and the lead reaches to tag-board under this valve. I cannot find any clean copper showing on the tags, so could you tell me which tag I should reconnect to?—J. Ralph (Nottingham).

We cannot give you the precise tag to which the black wire is connected, but you will find it is at the end of the 4-7k video amplifier anode load, which is connected to the anode (pin 2) of the 6F13 video amplifier. We feel confident that you will be able to find the tag from this description, but if not, take the wire directly to the anode pin of the 6F13.

BUSH TV24C

Would you let me know the purpose of the magnet clipped round the line output valve (PL81)



**A NEW-PRACTICAL WAY
of UNDERSTANDING**

Radio • Television • Electronics

Including: Transistors; VHF/FM; Hi-Fi equipment; Computers; Servo-mechs; Test Instruments, Photo-electrics; Nucleonics, etc.

FOR ...Your Career ...Your Own Business ...An Absorbing Hobby

Radiostructor—an organisation specialising in electronic training systems offers a new self-instructional method using specially designed equipment on a "do-it-yourself" basis.

You learn by building actual equipment with the big kits of components which we send you. You advance by simple steps, performing a whole series of interesting and instructive experiments—with no complicated mathematics! Instructional manuals employ the latest techniques for showing the full story of electronics in a practical and interesting way—in fact—you really have fun whilst learning! Post the coupon below, now, for full details—

RADIOSTRUCTOR
LEADS THE WORLD
IN ELECTRONICS TRAINING

POST NOW

To RADIOSTRUCTOR (Dept. G102)
READING, BERKS.

Please send brochure, without obligation, to:

★ Name _____



Address _____

8/61

★ **BLOCK CAPITALS PLEASE**
(We do not employ representatives)

LAWSON

DIRECT REPLACEMENT Reprocessed TUBES

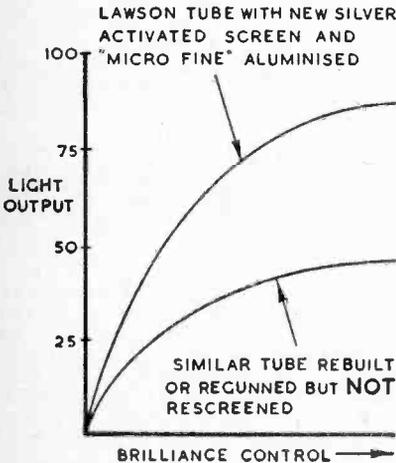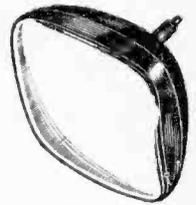

FULLY GUARANTEED 12 MONTHS

ENGINEERS WITH EXPERIENCE

Know that as a tube gets old, not only does it become Low Emission but the light efficiency of the Phosphor Screen also deteriorates (up to 10% per year). This deterioration of the Screen obviously continues if the tube is only rebuilt or regunned. Don't risk a "DEAD SCREEN", enjoy the brilliant crisp high definition of a LAWSON TUBE. Tubes which are absolutely BRAND NEW throughout (excepting the glass), and which incorporate the very latest CRT improvements. New silver activated screens, micro fine aluminising, high efficiency gettering, plus Brand New electron guns by Britain's premier manufacturers, Mullard, Mazda, Emiscope, Brimar, Emossor, Emitron, English Electric, etc.

ALL MAKES AND TYPES FROM STOCK

12" = £4.10.0

C.O.D. or C.W.O.

14" = £5.5.0

10"

15-17" = £5.15.0

Gladly refunded if you wish to return your old tube (excepting 12")

CARR. and INS. 7/6

EXPRESS SERVICE—
Orders received by 3 p.m. are dispatched same day.
Special direct services to Scotland and Ireland.

LAWSON TUBES

156, PICKERSLEIGH RD. MALVERN. Worcs.
TEL. 3798

AERIALS

BAND I BAND II BAND III

Combined Arrays I and III

- 1+3 Element Loft Mounting .. 38/3
- 1+5 Element Loft Mounting .. 46/9
- 1+3 Element Wall Mounting .. 45/3
- 1+5 Element Wall Mounting .. 61/-
- 1+3 Element Chimney M'ting. .. 57/10
- 1+5 Element Chimney M'ting. .. 66/9

Band I

- Single Dipole Wall Mounting .. 24/7
- Single Dipole Chimney M'ting. .. 40/2
- X Aerial Chimney Mounting .. 62/3
- H Aerial Chimney Mounting .. 67/7

Band III

- 3 Element Yagi Wall Mounting 33/-
- 6 Element Yagi Wall Mounting 43/-
- 9 Element Yagi Wall Mounting 56/-
- Chimney Lashing Mounting add 10/-
- Double 6 Array, only with clamp 83/-

Band II

- Single Dipole Wall Mounting .. 20/5
- Single Dipole Chimney M'ting. .. 29/9
- H Array Chimney Mounting .. 52/4

REPAIR KITS

- Band III Folded Dipole With Insulator, Complete .. 9/3
 - Band I Insulator With Two 4 inch Dipoles For 1 or 2 inch Booms, Complete .. 19/5
 - 6 inch Lashing Kit, 12/11. 7 1/2 inch Lashing Kit .. 14/8
 - 6 inch Wall Bracket With U Bolts .. 7/10
 - 1-1/2 inch Clamps, 3/10. 1-2 inch Clamps Universal .. 5/4
 - Bracket Repair Kit, J Bolts; U Bolts; 20ft Lashing .. 2/6
 - Wire; Thimbles; Corner Plates (Enquire)
 - Insulators, All Types (Enquire)
 - Co-Ax. Semi Air Spaced, 7d. yd. Plugs 1/2
 - Send 6d. for Lists. Please state Channel when ordering.
- Cash with Order. Post and Packing 3/- extra.

SATISFACTION OR MONEY BACK GUARANTEE

WALKER & SQUIRES

PINNOX STREET, TUNSTALL, STOKE-ON-TRENT

Phone: Stoke-on-Trent 89767

EXPRESS ELECTRONICS

ROSEDENE LABORATORIES

KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	7/6	6B4A	7/-	7B7	9/6	DF96	8/-	EF80	8/-	PCL84	7/-
1C3	8/-	6BE6	7/-	8D3	4/-	DLH76	7/6	EF86	9/-	PL81	12/6
1F1	8/-	6BH6	5/9	12AH8	10/-	DR77	8/-	EF91	4/-	PL82	7/-
1F3	7/6	6BJ6	5/9	12AT7	8/-	DH142	8/6	EF92	5/6	PY81	6/9
1FD1	8/-	6BR7	8/9	12AU7	5/-	DH156	10/-	EL41	9/6	PY82	7/6
1F09	7/6	6BS7	10/6	12AX7	7/6	DK91	7/6	EL84	7/-	PY83	7/6
1L4	8/9	6BW5	7/6	12BE6	8/6	DK92	7/6	EM84	10/-	R19	11/6
1P1	8/-	6BW7	7/-	12BH7	10/6	DK96	8/-	EM85	10/-	U26	9/6
1P10	7/6	6C10	9/-	12K8GT11	7/6	DL92	7/6	EY51	7/6	U52	7/6
1P11	7/6	6D2	4/-	12K9GT	7/6	DL94	7/6	EY81	10/-	U78	7/6
1R5	6/-	6E12	4/-	18A5	9/-	DL96	8/-	EZ40	7/6	U78	5/-
1R7	6/-	6E12	4/-	25A6G	8/6	EB91	4/-	EZ80	5/6	UCH41	8/6
1T4	7/6	6J7GT	7/6	25L6GT	7/6	EBC41	10/-	EZ81	6/9	UCH42	9/6
1U5	6/-	6K7G	5/6	25Z4G	9/-	EBF80	8/6	KTS30	9/6	UF41	8/6
3Q4	8/-	6K9G	6/-	30C1	6/6	ECC81	6/-	KT66	11/6	UL41	8/6
384	7/6	6J7GT	8/6	35W4	8/6	ECC84	7/6	N17	7/6	UY41	7/6
3V4	7/6	6SL7GT	6/-	35W4	8/6	ECC84	7/6	N18	8/-	W76	6/6
5V4G	7/6	6SN7GT	6/-	35Z4GT	8/-	EF90	8/6	N19	7/6	W143	8/6
6V4GT	4/6	6V8G	7/6	35Z4U	10/6	EF92	6/9	N37	10/6	X17	7/6
6Z4G	9/6	6X4	5/-	5F8	7/6	ECH43	8/6	PC84	6/9	X142	8/-
6AKG	6/6	6X6G	5/-	80	6/-	ECH81	10/-	PCF80	6/9	X150	9/-
6AL5	4/-	6X5GT	6/-	DAF91	7/6	ECL30	8/6	PCF92	7/-	Z77	4/6
6AM6	4/-	7B4	7/6	DAF96	8/-	ECL32	9/6	PCF92	7/-	ZD17	7/6
6AT6	6/-	7C5	7/6	DF91	7/6	EP41	8/-	IPCL52	7/-	ZD17	4/6

COAX. SUPER QUALITY 4in. 6d. yd. PLUGS 9d. SOCKETS 9d.

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES. D.P. switch 4/- Less switch, 2/6. Values 10K to 2M, B9A, B7C y. Holders 8d., Screens 8d., Contact Coated Reconnectors 250v. 50 ma. 6/6, 35ma. 8/6.

MATCHED PAIRS

EL84 17/-, 6V6G 17/-, 6BW5 18/- per pair, Push Pull O.P. Transformers for above 3-15 1/2 14/8, P. & P. 150, 12in. P.M. Speakers 3d 24/6, Baker's "Selhurst" 12in. 10d 15W, 90/-, P. & P. 2/6, 12in. Stereo Model 27.7.0.

SETS OF VALVES

DK91, DP91, DAF91, DL96 or DL941 .. 19/6
 ECH42, EF41, EBC41 .. 37/6
 DK96, DP96, DAF96, DL96 .. 27/6
 EL41, EZ40 .. 37/6
 1C3, 1F1, 1FD1, 1P1 .. 27/6
 UCH42, UF41, UBC41 .. 37/6
 1R5, 1T4, 1R5, 384, or 3V4 .. 19/6
 UL41, UY41 .. 35/-
 Postage and packing 6d. Over 1 post free. C.O.D. 2/6.

of this set? Is the magnet position critical?—G. Byrne (Ilford).

Some line output valves have a tendency to self oscillation which gives rise to interference on the left side of the screen. The purpose of the magnet is to damp out any tendency of this in the PL81. It is more effective in doing this in one position than any other. If there is no sign of a ragged line down the left side there is no need to alter the magnet in any way.

K.B. MV50

This set has two distinct faults. On ITV there is severe line pulling (whites cause the picture to shift to the left) and sometimes a line appears about $\frac{1}{2}$ in. from the top, and the whole picture above this line is displaced to the left by about 1 in. The picture does not bend, but shifts solidly and squarely, especially if the picture content is white. The width is just sufficient on the tube, but still fills the mask. A reasonable picture, without pulling, can be obtained by turning the fine tuner to its limit, but then there is no sound, only a loud hum.

The other fault is an intermittent BBC picture. On investigation it was found that the contact on the BBC coil set, in the tuner, was very worn. The contact in question is the fourth from the front on the channel set. Since I cannot find any marks identifying the tuner, I am unable to order the coil strip.—P. Bardos (London).

The effect you describe is most likely to be caused by "ghost" reflections (reflected signals) on the aerial. First try rotating the aerial a few degrees and if this does not help, resite the aerial or use a more directional type.

The correct BBC coil biscuit should be ordered from your K.B. dealer, specifying the channel required, and the model number of the receiver.

G.E.C. BT1746

There is sound-on-vision on ITV only, and this cannot be corrected by the tuner trimmers. Also the contrast control does not affect the picture as much as it should. Is there any way to omit the Barretter valve as this only short lived; can it be replaced by a resistor?—G. Wilson (Cheshire).

If the sound-on-vision is on ITV only and it cannot be corrected by the oscillator trimmer on the tuner unit, we suggest that too much signal input is being received on ITV. Attenuation or a different position for the aerial is the answer. The Barretter valve can be omitted and a 35Ω resistor put in its place; at least 10W.

PYE VT4

The picture recently broke up and could not be held by adjustment to the vertical and horizontal hold controls. Replacing the two ECL80s with two new ones and also two from a set working normally, would not cure the fault. The sound has also developed a hum. Whilst trying to adjust it I found positions when the picture remained still, momentarily, and it appeared normal at the bottom, but large and off the screen at the top

and increased considerably in brilliance.—W. Cummins (Virginia Water).

Faulty main smoothing may well be the cause of your trouble. Check the $100\mu\text{F}$ and $200\mu\text{F}$ electrolytic condensers and also check for heater-cathode leakage on the frequency changer and R.F. amplifier valves.

EKOC TRC1124

This set develops a $\frac{1}{2}$ in. foldover at the bottom of the screen. I have changed several valves with little effect and would be grateful for any help you could give.—W. Young (Worcester).

Your trouble is centred around the SP61 which is in the centre of the row of three valves below the scan coils. Check for poor valveholder pin connections and a leaky $0.01\mu\text{F}$ condenser from the frame linearity control to height control.

FERGUSON 996T

I obtained this receiver quite recently. The sound is good though contrast is a little harsh and there is a series of bright perpendicular lines of varying intensity from the left hand side of the picture (maximum) to centre (minimum). I have tried a change of valves including PY81, PL81, PCF80s and EF80s in video and timebase circuits, but with little improvement.—L. Colledge (Aber-tillery).

Check the resistor and capacitor which are connected in parallel with the line linearity induction. Suspect a fracture in the core of the line output transformer.

FERRANTI 207A

This projection set has the following fault. The raster is cut by a number of horizontal blanked out lines. These are spaced equally, about every tenth line, and they roll upwards. Otherwise the picture is satisfactory, apart from a general lack of brightness. The line hold control is working satisfactorily.—B. Harvey (Cardiff).

You should check the frame output valve and check the electrolytic capacitor ($32\mu\text{F}$) wired to pin 8 of V13 (ECL80), situated on the front left side. The $32\mu\text{F}$ is one of the sections of a $32 + 32 + 8\mu\text{F}$ can in the centre of the chassis.

STELLA ST1522U

The picture on my set rolls upwards and downwards and will not lock. Can you suggest a remedy?—T. Cox (Hull).

Check the electrolytic capacitors associated with the video amplifier ($50\mu\text{F}$ and $5\mu\text{F}$) which are of the white cardboard covered type. Then check the components associated with the UCH42 frame sync clipper.

QUERIES COUPON

This coupon is available until AUGUST 22nd, 1961, and must accompany all Queries sent in accordance with the notice on page 579.

PRACTICAL TELEVISION, AUGUST, 1961.

SETS & COMPONENTS

SPARES—VALVES—TUBES

NEW, EX-EQUIPMENT or SURPLUS

6K25	4/6	EB91	2/-	PL33	4/6
12A17	3/-	ECL80	4/6	PL38	10/-
10P1	4/6	EF80	2/-	PL81	4/6
10P13	4/6	EF91	2/-	PL82	4/6
10P14	4/6	EL33	4/6	PY31	4/6
20D1	3/-	EL38	4/6	PY80	4/6
20P1	4/6	EY51	4/6	PY81	4/6
27S1	10/-	KT38	4/6	PZ30	4/6
188BT	12/6	PC84	4/6	U24	7/6
538	4/6	PCF80	4/6	U801	12/6

Pre-war 4, 5, 7 pin types, 5/-, postage 6d. each
NEW TRANSISTORS. Red Spot, 2/6; OC45, OC72, 7/6; OC44, 8/6; OC35, 20/-.
SPEAKERS: 8, 8in., 5/-, 10in., 10/-, elipt. 7/6. Send S.A.E. with enquiries or for full list.
"ST. JOHN'S RADIO", 156 St. John's Hill, London S.W.11. Phone BAT 9838

RECLAIMED VALVES. Tested and perfect; all one price, 5/- plus 6d. postage each. Also surplus new valves, guaranteed. S.A.E. for list. New Valves bought. LEWIS, 46 Woodford Avenue, Ilford, Essex.

SALVAGED VALVES

Now from 1/3 each
 New and Boxed Valves
 all at 10/- each

Send 9d. for full list of valves and components.

ARION TELEVISION, 4 Macted Road S.E.15
NEWX 7152

ELECTRICAL FACTORS

OFFER THE FOLLOWING UNREPEATABLE BARGAINS

Brand New Television 12in. Tubes, Type M.W. 31-74. £2.19.6 (Carr. & ins. 12/6)

8-watt Push-pull Amplifiers, EL84 x EL84, ECC83, EZ80. Complete production line purchased, enables us to sell at £2.15.0 less valves (carriage 2/6).

Short List New Valves

EF183	7/6	6F19	8/6	30P4	12/-
EF184	7/6	6F23	10/-	30F5	6/-
U26	9/6	10LD12	8/6	30PL1	10/6
U193	8/6	10F18	9/6	30PL13	12/6
PC839	11/6	30C1	8/-	30FL1	9/6
6D2	5/-	30L1	8/-	30L15	10/6

Fantastic clearance of Stereo Amplifiers, including two Mullard ECL82 and EZ90, pilot lights, knobs, one speaker circuit diagram, etc. £2.19.6 (carriage 3/6).

Rigidly tested Television Valves, individually boxed, 3/- to 7/6 each.
 Television Chassis, complete less valves, 30/- (carriage 5/-).

TELEVISION COMPONENTS AT BARGAIN PRICES

Please write for your individual requirements. S.A.E. for Free Lists

4 HENDERSON ROAD EASTNEY : PORTSMOUTH

RATES: 4/- per line or part thereof, average live words to line, minimum 2 lines, Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television" Tower House, Southampton St., London, W.C.2.

SETS & COMPONENTS

(continued)

14in. TELEVISIONS. BBC/ITA, newly fitted rebuilt tubes. To clear £8. Tube guaranteed 12 months, Callers only. NU-GUN TELETUBES LTD., 3 The News, Duckett Road, N.4. MOU 2903.

ST. HELENS 4246 for Television tubes. S.A.E. list. DARWINS, 45 Show St., St. Helens Station, Lancs.

TV SPARES

Britain's Largest Range—New or Used

LINE OUTPUT TRANSFORMERS and SCAN COILS

for nearly every make and model.

New from 45/- Used from 20/-

Just a few examples from our extensive range **IN STOCK.** Add 2/6 for P. & TELEPHONE ORDERS SENT SAME DAY C.O.D.

NEW LINE OUTPUTS

Pye V4/7, VT4/7, LV30, FV1, V14, 55/-
 Ferranti 14T3/4/5, 47/6; 14T2/1T225, 62/6
 Ferguson 992/6/8, 66/9; 941-55, 57/6
 Ekco T221/231, 311, 284, 330, 55/-, Scan 50/-
 H.M.V. 1824/9, 58/6; 1840-8, 59/6
 Cossor 930-9, 58/6 (new), 30/- (used)
 Murphy V240/250/280, 62/6; C200, 49/6
 Ultra VT9-17, etc., 108/6 with U25
 Bush TV53, 69/6; TV24C, 89/6; TUG34, 5gns.
 Philips 1114U, 91/8; 1768U, 102/6
 Masteradio T917, TE7T, etc., 58/6
 Decca D14/17, 58/6; DM14/17, 55/-
 Sobel TS17, T346, 58/6; T171, 80/-
 Baird P2014/7, 2114/7, 58/6.
 New Scan Coils for Pye V4/7, VT4/7, 65/-

ITA TURRETS for Pye Ferguson type A, B, 30/- (used); Murphy, Pye 47/124, all tested (used) 30/-. Chassis for VT4 less LOPT and Scan, 30/-.

COMPLETE TVs, not tested but complete, callers only. Cossor 928, 30/-.

We stock or can obtain most L.O.T.s, Scan Coils, Frame O.P.s and spares.

PLEASE SEND S.A.E. FOR IMMEDIATE QUOTE.

SENSATIONAL TV OFFER

We have a limited number of 1961, Push Button, Slimline Television Receivers by Famous Makers at reduced prices. List 59 gns. Our Price 43 gns. plus 25/- Carr. & Ins., 110 Tube, Printed Circuit, High Gloss Cabinet, all channels. Full guarantee. All in sealed boxes. Immediate despatch on your order.

TELEVISION CONSUMER SERVICES LTD.

28 BROCKLEY CROSS, S.E.4. Tideway 5394
 112 CAMBERWELL RD., S.E.5. RODney 7917

SETS & COMPONENTS

(continued)

H.P. on Regunned C.R.T.s

At No Extra Charge
 12 Months' guarantee

12" & 14"	..	£3.10.0
17"	..	£4.10.0
21"	..	£5.10.0

Phone or Call only:
 Rod 7778

P. J. F. Andrews
 61-63 ROSEMARY RD.
 LONDON, S.E.15

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. DIRECT TV REPLACEMENTS LTD., Dept. PT/22/7, 138 Lewisham Way, S.E.14. Tideway 6666.

GUARANTEED VALVES

1L4	2/6	12AT7	8/6	EF91	3/-
6F1	6/6	20D1	6/6	EL32	3/-
6F18	5/6	20P2	7/6	PC84	6/6
6F14	7/6	20L1	8/6	PY80	6/6
6F15	7/6	D77	3/6	PY82	6/6
10C1	7/6	EABC80	7/6	UF41	7/6
10P1	6/6	EF90	6/-	UL46	7/6

Postage 6d. each. List 3d.

SERVICE SHEETS

List 6000 Models. 1/- S.A.E. Enquiries. Hamilton Radio (D), 13 Western Rd., St. Leonards, Sx.

In Scotland RENVUE for Better Value

COMPLETELY REPROCESSED TUBE (NEW GUN, RESCREENED, ALUMINISED)

12.6v. and 6.5v. 0.3 amp., 17 and 15in. Types	£6.10.0
12.6v. and 6.5v. 0.3 amp., 14in. Types	£6. 0.0
12v., 15in. Types	£7. 0.0
2v., 12 and 15in. Types	£6. 0.0

Electrostatic 90 degree and 110 degree tubes 10/- extra. Carr. paid.

10/- ALLOWED ON OLD TUBE
 Terms arranged.

FERGUSON

14in. BBC and STV Consoler	£12.10.0
14in. BBC and STV Receivers	£10.10.0
17in. BBC and STV Receivers	£19. 0.0

COMPLETELY OVERHAULED AND FITTED WITH COMPLETELY REBUILT TUBE

with One Year's Guarantee

£5 Deposit. Terms on Balance

Renfrew Electronics Ltd.
 Anderson Drive
 Renfrew : Scotland

Tel.: Renfrew 2642

SETS & COMPONENTS
(continued)

C. EDWARDS

1070 Harrow Rd., London N.W.10.
Ladbroke 1734.

500 S/H TV Sets must be cleared
as taken part exchange. Condition
unknown.

ALL SETS COMPLETE

- 12in. BBC 25/- 13 Channel 50/-
 - 14in. " 50/- " " 75/-
 - 17in. " 85/- " " 125/-
- Plus 15/- carriage.

Guaranteed Valves

- 10C2 10/-, 20D1 6/-, 6K25 8/-,
- PL38 10/-, PL81 8/-, PY81 8/6,
- PY80 7/6, PZ30 10/-.

TUBES-AERIALS-VALVES

Rebinned tubes, guaranteed one year
full range of aerials and fittings, I.T.V.
boosters, valves, brayhead tuners, TV sets,
transistor radios and all electrical applian-
ces. Co-axial cables and house wiring
cables, fluorescent fittings.
All quotations without obligation. Special
terms to the trade, and Home Engineers.
S.A.E. for Catalogue.

G. A. STRANGE

BROADFIELD, NORTH WRAXHALL,
Nr. Chippenham, Wiltshire, Tel. Marshfield 238

Television Tube Shop

now stock

Tubes for every make of set

OVER 600 TUBES ALWAYS IN STOCK

- 12 inch Mullard type £4. 5.0
- 12 inch Mazda type £4.15.0
- 14 inch Mullard type £5. 5.0
- 14 inch Mazda type £5.10.0
- 15 inch Mazda type £5.15.0
- 16 inch G.E.C. & Mullard type £6.12.6
- 17 inch Mazda & Mullard type £6.10.0
- 17 inch G.E.C. & Brimar type £6.15.0
- 21 inch Mullard type £8. 0.0

Add 10/- for insured carriage to your door
within 48 hours, or 5/- via B.R.S.

All tubes tested before despatch and guar-
anteed for 12 months. Guarantee cards
enclosed with each tube.

Special Purchase of 110*, 17 inch tubes—
Slight mark, Guaranteed for 12 months.
MazdaCME1703 } replace AW43-88, £6.
GEC 7405A }

Shop Soiled Tubes.
(Slight scratches or marks) Guaranteed 12
months. Ideal for second set. 12in. 3/18, 3/31
37/6. MW31-74 50/-, 14in. MW 36-44 52/6.
CRM141 55/-. 17in. CRM171, MW43-64 60/-.
Others available from time to time. Please
enquire.

Service Engineers
Our Rebate Scheme shows real savings—
send for details.

TELEVISION TUBE SHOP

48 Battersea Bridge Road, S.W.11
BAT 6859

Just South of the Bridge. Open Saturdays.

SETS & COMPONENTS
(continued)

TELEVISION TUBES! 1st quality,
new guns. Year's guarantee, most
75/- exchange. Rescreened from 85/-.
3 Pank Ave., New Barnet. BAR 1934.

B.V.A. NEW and rebuilt TV tubes.
S.A.E.: REDWATT TUBE DIST-
RIBUTORS, 41 Denmark Street,
Wakefield, Yorks.

FOR SALE

VALVE CARTONS at keen prices.
Send 1/- for sample and list. J. & A.
BOXMAKERS, 75a Godwin Street,
Bradford 1.

METAL RECTIFIERS

RECTIFIERS—CONTACT COOLED.
14RA1282 (FC101) type 250 v., 250 mA, 18/6;
14HA1283 (FC31) type, 250 v., 300 mA, 17/6;
350 mA, 19/8.
RECTIFIERS—FIN TYPES
Equiva. for RM4 250 v., 250 mA, 14/-; RM5
250 v., 300 mA, 17/8; 14A889 400 mA, 18/6;
14A90 18/8; 14A97 30/-; 14A100 22/6 14A124
22/6; LW7 20/6.

CABY MULTIMETERS

A10 - 10 ranges, £4.12.8; B20 - 20 ranges,
£6.10.0. S.A.E. for full details.
ARMCHAIR EXTENSION VOLUME CONTROL
unit for TV Radio Amplifiers, etc. Easily
used, perfectly safe, 18/6.

TRANSISTORS

OC16 18/-; OC71 5/-; OC81 8/-; OC45 7/-.
Cash with order, Post Free. C.O.D. 2/6.

DURHAM SUPPLIES

175 Durham Road, Bradford 8, Yorkshire.

1,000 TELEVISIONS, all makes, from
£3 working, 10/- not. Callers only.
9 till 6 including Sats. 39 White-
horse Lane, Stepney, London.

TV's FOR SALE

Examples BRCITA	C.R.T.
in good working order	Good Rebuilt
14in. Ultra VTS15: KB LVT 30	£17 £21
14in. Ekco T221 or T283.. ..	£19 £23
14in. Ferguson 992	£14 £18
17in. Plessey: RGD etc.	£19 £24
Send for Lists.	Carr. Paid.

CADMAN'S

Bryan Street, Hanley.
Phone: Stoke-on-Trent 23567.

SERVICE SHEETS: also Current and
Obsolete Valves for sale. JOHN
GILBERT RADIO, 20 Extension,
Shepherd's Bush Market, London
W.12 (Phone: SHE 3052).

Star TV Tubes

70/-

all sizes up to and including 17in. includes
old glass or plus 7/6 without
C.W.O. Carriage 7/6.

WHY PAY MORE?
new guns, 12 months' guarantee.

also 20/- each

12in., 14in., Part Exchange Televisions

ARTHUR SLARK

43-45 Thicketford Road, Tonge Moor,
Bolton.

Phone: 6684.

FOR SALE
(continued)

100 BAYS of brand new adjustable
Steel shelving, 72in. high by 34in.
wide by 12in. deep, stove enamelled
dark green. Sent un assembled. Six
shelf bay—£3/15/0. Sample delivered
free. Quantity discounts. N. O.
BROWN LTD., Eagle Steelworks,
Heywood, Lancs. Tel.: 69018.

WHY PAY ridiculous prices? Try
our special tuner cleaner, suitable
for cleaning and lubricating all tuner
and switch contacts, ideal for volume
controls, etc. Sample dispenser
approximately 4 gill 9/6 C.W.O.
REDLEA, West Main Street, Darvel,
Ayrshire.

WANTED

WANTED Service Sheets. No
quantity too large, highest prices
paid. SULTAN RADIO, 29 Church
Road, Tunbridge Wells, Kent.

A PROMPT CASH OFFER for your
surplus Brand New Valves, Speakers,
Components, Test Instruments, etc.
R.H.S., 155 Swan Arcade, Bradford 1.

NEW VALVES WANTED — EY51,
ECL80, PCC84, PCF90, PCL83, PL81,
PCL 82, F781, F19, U801, 30P4, etc.
Best cash prices by return. DURHAM
SUPPLIES, 175 Durham Road,
Bradford 8, Yorkshire.

NEW TV VALVES WANTED. Send
valves, cash by return, to: P. J. F.
ANDREWS, 61-63 Rosemary Road,
London S.E.15.

SERVICE SHEETS

SERVICE SHEETS. Radio, TV, 5,000
models. Lists 1/-. S.A.E. enquiries:
TELRAY, 11 Maudland Bk., Preston.

FAULTFINDER FILES (TV) showing
common faults that each receiver is
prone to and other useful servicing
information. 2/- each. List 9d., plus
postage. S.P. DISTRIBUTORS, 44
Old Bond Street, London W.1.

SERVICE SHEETS (1930-1961) from
1/- with Free Fault-Finding Guide,
Catalogue, 5,000 models 1/-. 125
Radio/TV Sheets covering 370 popu-
lar models 20/-. S.A.E. enquiries:
HAMILTON RADIO, Western Road,
St. Leonards, Sussex.

SERVICE SHEETS — We have the
largest stock of Radio and TV Service
Sheets in the country for sale at 4/-
each. Why tolerate delay in obtaining
your supplies when we will dispatch
by return? Service Sheet List 1/-. Also
Manufacturers' Manuals for sale and
hire. 1961 List now available 1/-.
S.A.E. please. Mail orders only to:
S.P. DISTRIBUTORS, 44 Old Bond
Street, London W.1.

SERVICE SHEETS. Radio and TV
4/- each. List 1/-. All orders des-
patched on day received. Also
manuals for sale and hire. S.A.E.
please. SULTAN RADIO, 29 Church
Road, Tunbridge Wells, Kent.

BOOKS

**FIND TV SET TROUBLES IN
MINUTES** from that great book "The
Principles of TV Receiver Servicing."
10/6 all book houses and radio
wholesalers. If not in stock from:
Secretary, I.P.R.E., 20 Fairfield Road,
London N.8.

(continued on next page)

LINE OUTPUT TRANSFORMERS

SCAN COILS SPECIALISTS

Makes	Models	Prices
ACE:	Spares available.	
ALBA:	T301, T304, T394, T484, TV11A, 11B, 12A, 12B, TVG12A, 12B, TRG12A, 12B	39/6
AMBASSADOR:	Spares supplied.	
ARGOSY:	Most models available.	
ARMSTRONG:	Spares supplied.	
BAIRD, BANNER, BEEHIVEN:	Spares supplied.	
BUSH:	TV368, TV56, T57, TV57, Rev'd TVG38, TVG2, TVG, TV60, only TV67, etc.	69/6
COSSOR:	930 & T, 931, 933-4-5, 937, 938A & F, 939 & A & F, 943PT, 940-945, 945, 945B, 949	69/6
CHAMPION, COLUMBIA:	Spares supplied.	
DECCA:	D17 & C	69/6
	DM1, DM2C, DM3, DM4/C	65/-
	DM5, DM14, DM17, 44, 565	65/-
DEFIANT:	DT145, TR1733	59/6
DYNATRON:	Spares supplied.	
EKCO:	TS93, TC8102, TS105, TS114 TRC124, TC138, TS188, TS192, TRC138, TC140, T14, TV142	55/-
	T161, TC182, T164, T165, etc.	47/6
	TC208, TV209, T231, T291, T231F, T248, T283, T284, T293, etc.	55/-
ENGLISH ELECTRIC/ELECTRONIC:	Spares supplied.	
FERGUSON:	103T, 103T, 118T, 132T, 145T	66/6
	941T-953T inclusive	59/6
	991T-997T inclusive	66/6
	33PT-24CT inclusive	69/6
	30AT, 30RT	65/-
FERRANTI:	14T3, 14T3F, 14T4	45/-
	17K3 & F, 17T3 & F	45/-
	17K4 & F, 17SK4 & F	45/-
	17T4 & F	45/-
	14T3, 17SK5, 17K5	45/-
G.E.C.:	BT1251, BT1252, BT1746, BT1748, BT1743	49/6
	BT4643, BT3147, BT6246-48	89/6
	BT5348-BT6448 inclusive	49/6 and 89/6
H.M.V.:	1834 & A to 1831 inclusive	67/6
	1840, 1841, 1842-1848	67/6
INVICTA:	T118, T119, T120	65/-
	All other models available	
K.B.:	LF750, LVT50, LFT60, MV60	107/6
	All models available, etc.	
MARCONI:	All models available.	
MASTERADIO:	All models available.	
McMICHAEL:	All models available.	
MURPHY:	V200, V202C	57/6
	V240, V260	95/-
PAM, PETO SCOTT, PHILCO:	All models available.	
PHILIPS:	1785L, 2180L	105/-
	All models available.	
PILOT:	All models available.	
PORTADYNE:	All models available.	
PYE:	CTM4, PV4C, PV4COL	55/-
	V4, V7, V7, V7	55/-
	LV30, FV1, FVIC	69/6
	CM17, CTM17F, CW17	69/6
	CW17C, CW17CF, CW17F, etc.	69/6
	All models available.	
RAYMOND:	All models available.	
REGENTONE:	All models available.	
R.G.D.:	6017T, 7017, C54, etc.	59/6
	All models available.	
SOBELL:	All models available.	85/-
STELLA:	ST5721U	105/-
	ST5817U, ST5821U	105/-
	ST5817U	105/-
STRAD, TELEVOICE, TRIVIEW:	Available.	
ULTRA:	86 series, 815 series, with U25 etc., complete	79/6
	All models available.	
VALRADIO:	Spares available.	
VIDOR:	CN4217-CN4231 inclusive	85/-
WESTMINSTER:	Spares available.	
WHITE-IBBOTSON:	Spares available.	
	Sensocins, Osc. and Output Txs. for all above makes available.	
	Post and Packing 2/6. C.O.D. 3/- extra.	
	All Enquiries S.A.E.	

WYNDSOR TELEVISION
Dept. P.T.
ST. ALBANS RD., BARNET, HERTS.
BAR 1789

SITUATIONS VACANT

UNITED KINGDOM
ATOMIC ENERGY AUTHORITY
ATOMIC ENERGY
ESTABLISHMENT, WINFRITH

Vacancies exist at A.E.E. Winfrith, Dorchester, Dorset, for

INSTRUMENT MECHANICS

(Electronic and Electro-Mechanical)

Applicants should be familiar with the construction of Electro-Mechanical experimental equipment and components; ability to read circuit diagrams and drawings, and to construct, wire and test electrically complex equipment is desirable. Duties will include the major overhaul and repair of a wide variety of electronic and electro-mechanical equipment including potentiometric recorders, moving coil instruments, pressure, vacuum and flow transducers, oscilloscopes, signal and pulse generators, all types of amplifiers and high vacuum ionisation gauges.

Housing may be available to the successful applicants, but this would be determined at the time of interview. Excellent working conditions including sick-pay and pensions schemes.

Further details of conditions of employment, rates of pay and application forms, may be obtained from—

THE LABOUR DEPARTMENT
A.E.E. Winfrith, Dorchester, Dorset
quoting Reference Number IM/PW/PT.

EDUCATIONAL

"HOW AND WHY" of Radio and Electronics made easy by a new, no-maths practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from Dept. 12, P.T. RADIOSTRUCTOR, Reading.

Radio Television & Electronics

Learn at home with the world's largest home study organisation. Brit. I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for FREE prospectus stating subjects to

I.C.S.
Dept. 516
Intertext House, Parkgate Road,
London, S.W.11.

EDUCATIONAL

(continued)

FREE FROM THE I.P.R.E. Syllabus of famous radio and TV courses. Membership Condition booklets. 1/- Sample copy the Practical Radio Engineer 2/- post free. Secretary, 22 Fairfield Road, London N.8.

★ **LEARN** ★
RADIO & TV SERVICING
for your OWN
BUSINESS/HOBBY

● By 2 new exciting no-maths system, using practical equipment recently introduced to this country

FREE Brochure from:—
RADIOSTRUCTOR
DEPT. G78
READING, BERKS. 8/61

RES/CAP. BRIDGE 38/-
p. & p. 2/-

Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading
READY CALIBRATED

Stamp for details of this and other kits.
RADIO MAIL (Dept. OV)
Raleigh Mews, Raleigh Street, Nottingham

NEW VALVES!

Guaranteed Set Tested

24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, 6AF91, DF91, DK91, DL92, DL94, SET of 4, 18/6.			
6AF96, DF96, DK96, DL96, SET of 4 26/-			
1D5	7/-	DL62	5/11
1R5	5/-	DL84	6/9
1S5	4/6	DL96	6/9
1T4	3/3	EB91	3/-
3S4	5/11	EBC41	7/6
3V4	6/9	EFB90	7/9
5Y4G	4/3	EL21	12/9
5Y3GT	5/6	ECC40	14/6
5Z4G	7/3	ECC81	4/9
6AM6	2/9	ECC82	5/9
6K7G	1/9	ECC83	6/3
6K8C	4/9	ECC84	3/-
6Q7G	5/6	ECC85	7/9
6V6G	4/9	ECF80	8/3
6V6GT	6/6	ECF82	8/3
6X3GT	4/9	ECH21	12/6
12K8GT	4/9	ECW42	7/9
12Q7GT	4/6	ECL80	6/9
35L6GT	8/6	EP40	12/3
35Z4GT	5/9	EP41	7/6
4Z31	8/9	EP80	4/9
CL33	11/9	EP82	12/9
DAC32	9/6	EP86	8/9
DAF91	4/6	EP89	6/9
DAF96	6/9	EP91	2/9
DK91	3/9	EL41	7/-
DF91	6/9	EL84	6/3
DF96	6/9	EY51	7/3
DH77	6/-	EY86	7/6
DK32	11/-	EZ40	6/-
DK91	5/-	EZ41	6/9
DK92	7/3	EZ81	6/6
DK96	6/9	MU14	7/-
DL33	8/6	PC84	6/9
DL35	9/6	PC89	10/-
		UF41	8/6
		UF81	8/6
		UF85	6/3
		UP4B	8/6
		Z77	2/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 3/- extra. Office address, no callers.

GERALD BERNARD
(Note new address—formerly of Leeds)
25 NEWBURY ROAD
HIGHS PARK, LONDON, E.4

FOR THE FINEST, FASTEST SERVICE IN THE COUNTRY, CONTACT—

D. & B. TELEVISION

Phone: Cherrywood 3856

131a KINGSTON ROAD, SOUTH WIMBLEDON, S.W.19

OUR COMPREHENSIVE SERVICE INCLUDES:

12 CHANNEL TURRET TUNERS, 10, 16, 36 Mo/s, 40/-; VALVES, PCF80 and PCC84, 7/- each; Cabinets, Glasses, Masks, Condensers, Resistors, Ion Traps, Speakers, RECLAIMED C.R. TUBES (Not boosted or reactivated), 9in. and 12in., 35/-; 14in., 50/-; 17in., 60/-. All picture tested, taken from stripped TVs. REGUNNED C.R. TUBES (12 months' guarantee): 12in., 80/-; 14in., 90/-; 17in., 100/-.

EXAMPLE OF TRANSFORMER LIST

L.O.T. SCAN COILS		L.O.T. SCAN COILS	
(New)	(Used)	(New)	(Used)
FERGUSON: 103T, 105T	89/9 35/- 80/- 35/-	PYE: V7, V74, V7	52/6 35/- 55/ 35/-
89/9 35/- 80/- 35/-		V7, CTM4.	52/8 35/- 55/- 35/-

These are only examples of stocks, we have many thousands more, and would be pleased to quote for any component you may require.

We pride ourselves that we can obtain and supply any TV spare. OUR GIGANTIC STOCKS INCLUDE: LINE OUTPUT, FRAME OUTPUT, SOUND OUTPUT, LINE AND FRAME BLOCKING, OSC. TRANS. AND SCAN COILS, FOR ANY MAKE OR MODEL TELEVISION. SOME OF OUR VALVES:

AZ31 8/6	ECF80 8/-	KT33C 6/6	PY31 7/-	U801 22/6	5V4 9/-	10P13 9/-
B36 5/8	ECH35 9/-	KT36 8/-	PY32 10/-	UAF82 3/-	5Y3 10/8	10P14 9/-
D77 3/-	ECH81 6/-	KT66 15/-	PY80 6/8	UBC41 7/9	5Z4 10/-	12A7 5/6
DH77 4/6	ECL80 6/9	PC84 7/-	PY81 6/-	UCH42 7/-	6AL5 3/-	12AU7 5/9
DK91 5/9	EP39 5/-	PC89 8/6	PY82 6/8	UF1 8/6	6AM6 3/-	20P2 8/8
DK92 3/8	EP80 3/9	PCF80 7/-	PZ30 10/-	UF42 3/9	6CD6 27/6	20P2 9/-
DK96 7/8	EP91 3/-		U22 9/8	UL41 7/3	6D2 3/-	20L1 12/6
DL82 5/9	EP82 5/-	PCL83 11/3	U24 10/-	UL46 7/3	6F1 5/-	20P1 10/6
DL94 6/8	EL33 8/6		U25 12/-	UL44 11/6	6F2 3/-	20P3 12/-
DL98 7/8	EL38 14/6	PCL84 9/6	U31 9/8	UU8 14/6	6F14 9/8	20P4 16/6
EB91 3/-	EL84 7/-	PL33 8/6	U50 8/8	UU9 6/6	6F15 9/8	27SU 14/-
BBC33 5/6	EY618E 6/-	PL36 10/9	U52 7/-	SP41 2/3	6L1 12/6	30C1 7/-
EBF80 9/6		PL38 14/6	U81 9/-	SP61 2/3	6V3 5/-	30L1 7/-
ECC81 5/3	EY61 7/8	PL42 8/6	U281 9/-	WT 5/-	10P1 4/6	30P4 10/9
ECC82 5/9	EY86 7/8	PL82 9/6	U282 20/-	Z77 3/-	10C1 10/-	185BT 14/-
ECC84 8/-	EZ40 6/6	PL83 7/8	U301 20/-	5U4 5/-	10C2 13/-	

These are only examples of our valves: if you do not see what you require send stamped addressed envelope for special quotation. And that's not all—WE ARE OPEN FROM 10 a.m. UNTIL MIDNIGHT.

For any information or problems you have call or phone, we are always pleased to help.

TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra.

Postage on Valve 6d. each. C.R.T.s 12/6 inc. Insurance.

SATISFACTION ASSURED. RETURN POST SERVICE.

EDDY'S (NOTTM.) LTD.

172 ALFRETON RD., NOTTINGHAM
GUITAR PICK-UPS. Super Hi-Fi non acoustical universal fitting. High Output complete with lead and plug. Full and easy instructions. 49/11. P. & P. 2/6.

Build your own CAR RADIO!

★ 7 Transistors ★ Long and Medium Waves ★ Two Watts Output ★ R.F. Stage and Automatic Gain Control



10 1/2 Gns.

P & P 5/- extra

6 or 12 volts (state which)
Supplied with full instructions
Size 7 3/4 x 7 1/4 x 2 1/2 in.
SPEAKER, extra 17/11

NIFE ACCUMULATORS. 1.25v. size 3 x 2 1/2 x 1/2 in. 7 amp hrs. weight 13 ozs. 1/11 each. P. & P. 1/6. one only add 9d. per cell. THROAT MIKES. 1/- each. Post 6d. could be used for electrifying musical inst., etc.

VIBRATORS. 12 volt 4 pin 4/11. Post 1/6. POCKET RADIO. 2 Transistor with miniature speaker complete with all parts wiring diagram and full instructions, 27/6. Batteries 1/- . P. & P. 1/6.

V.H.F. AERIALS Complete and easy to fit. No technical knowledge required. 6/11. Post 10d.

ALL ABOVE ARE NEW & GUARANTEED

AC2/ PENDD	EY86 7/9	6F15 9/6
	EZ40 6/3	6F33 6/6
	EZ41 7/-	6J5G 2/9
CY31 9/6	EZ80 6/11	6J5GT 3/9
DAF91 4/9	EZ81 6/9	6J5M 4/3
DAF96 6/11	GTIC 7/6	6J7GT 5/-
DF91 3/11	HL23DD	6K7G 1/11
DP96 6/11		6K7GT 3/11
DL96 6/11	MU14 7/-	6K8G 5/3
DL93 4/11	PCC84 7/6	6Q7G 5/9
EAF42 8/6	PCC85 9/3	6SA7M 5/9
EB41 6/11	PCF80 7/6	6SG7M 4/9
EB91 3/6	PEN36C 8/-	6SJ7M 5/9
EB41 7/6	PEN46 6/11	6SL7G 6/6
EBF80 8/-	PEN4A 12/6	6SN7GT 4/3
ECC81 5/3	PL33 8/3	6U4GT 10/6
ECC82 5/11	PL36 10/9	6V6G 4/9
ECC83 6/6	PL81 9/-	6V6GT 6/-
ECC85 6/11	PL82 7/-	6X5G 4/11
ECH42 7/9	PL83 7/-	6X5GT 6/11
ECH81 9/-	PY80 7/-	10F1 6/6
ECL80 7/-	PZ30 9/6	12A6 5/3
ECL82 9/11	SP61 2/6	12A7 5/6
ECF82 9/-	TDD4 7/6	12A7 F 5/3
EF36 3/-	VP23 6/6	12AU7 5/11
EF37 6/11	ID5 7/6	12K7 5/3
EF40 12/3	IL4 3/6	12Q7 5/3
EF41 7/6	IS5 4/9	20D1 8/6
EF42 7/6	IT4 3/11	20P3 12/6
EF50 1/9	3S4 5/11	25A6G 8/6
EF80 5/-	3A4 4/11	25L6GT 7/6
EF86 9/6	5Y3GT 6/9	25Z4G 7/6
EF91 3/6	5Z4G 7/6	30F5 7/6
EF92 4/6	5U4G 4/9	35W4 6/9
EL41 7/3	6AG5 4/-	35A5 15/-
EL84 6/6	6B8G 2/11	95A 1/6
EL85 10/3	6C4 3/6	95S 3/6
EL91 4/6	6C6 4/9	956 2/11
EY51 7/11	6F13 11/6	

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers risk. Post and Packing 6d. per valve extra. C.W.O. or C.O.D. only. C.O.D. charge 3/- ex. S.A.E. with enquiries.

1961 EDITION

RADIO AMATEUR'S HANDBOOK

32/6 by The A.R.R.L. Post 2/-

WORLD RADIO TV HANDBOOK 1961 Ed. 16/6. Postage 1/-.

TELEVISION ENGINEERS' POKET BOOK by J. P. Hawker 12/6. Postage 6d.

CORRECTING TELEVISION PICTURE FAULTS by J. Cura and L. Stanley, 4/-. Postage 4d.

A BEGINNER'S GUIDE TO TELEVISION by F. J. Camm, 7/6. Postage 6d.

IMPROVE YOUR RECEPTION by J. Cura and L. Stanley, 5/-. Postage 4d.

OSCILLOSCOPE TECHNIQUES by A. Haas, 23/-. Postage 1/-.

PRACTICAL TV TROUBLE-SHOOTING a Gernsback Lib. Pub. 18/6. Postage 9d.

TRANSISTOR PROJECTS a Gernsback Lib. Pub., 23/-. Postage 1/-.

Complete Catalogue 1/-

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET LONDON, W.2
Phone: PADdington 4185
Open 6 days 9-6 p.m.

"TELFAC"

Regunned TV Tubes

Supplied from stock and despatched per British Railways SAME DAY. COMPLETE NEW GUNS fitted in every tube and fully guaranteed for TWELVE MONTHS.

	Mullard	Mazda
12 in. ...	£4. 0.0	£4. 10.0
14 in. MW ...	£4. 10.0	£5. 0.0
14 in. AW ...	£5. 0.0	£5. 0.0
15 in. 2 Volt ...	£5. 10.0	£5. 0.0
15 in. 12 Volt ...	£5. 0.0	
16 in. ...	£5. 10.0	
17 in. MW ...	£5. 0.0	£5. 0.0
17 in. AV ...	£5. 10.0	£5. 10.0
21 in. MW ...	£6. 10.0	£6. 10.0
21 in. AV ...	£7. 0.0	£7. 0.0

MW=Magnetic Focus
AV=Electrostatic Focus
Plus 10/- for Carr. & Ins.

Other types not listed available. Please contact:—

J. P. WRIGHT

Television Factors
103 Carr House Road, Doncaster
Sole Distribution Agent
Phone: DON 2636

COYNE'S

NEW JOB TRAINING BOOKS

Put Money-Making Time Saving Know-how at your fingertips!

Shows you the way to easier TV—Radio repair—time saving, practical working knowledge that helps you to repair sets faster! How to install, service and align ALL radio and TV sets, even colour-TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated maths or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home.

TRY ANY THREE BOOKS ON NO RISK FREE TRIAL

Look over the list of books and select the first three books you would like to examine. Circle the book numbers on the coupon. Additional books you would like to see may be entered on a separate piece of paper, and these will be sent to you after completion of the first transaction.

SPECIAL OFFER COYNE'S ELEMENTARY PRACTICAL RADIO-TELEVISION SET OF THREE VOLUMES, total 1,038 pages, sturdy Vinyl washable covers. £3.12.6d. the set!

These three volumes present the principles of construction, operation and testing of radio and television equipment in a SIMPLE, EASY TO FOLLOW manner.

By using NEW & DIFFERENT methods of explanation these books clearly explain the direct relation between the various parts of sets. This information is especially helpful in repair work where many times a burned out valve, resistor or transformer is actually caused by some other defective part of a circuit. Until the cause of the trouble is removed the parts would continue to burn out. For this reason, each part of the radio or television unit is explained, thus, making the material especially helpful to the experienced radioman, as well as the amateur.

One very important way in which these books differ from many other radio and television books is that the publishers did not try to assume the "extent of technical knowledge" of the reader. Every subject is explained COMPLETELY—while at the same time keeping it brief and to the point. You will find hundreds of photos, charts, diagrams, etc., in these books. These have been provided to make it easier to understand the explanations. To get this special offer, send no money now, then 12/6d. after free examination, and 20/- per month.

No. 9

Pin-Point

Tranistor troubles in 12 minutes



In this extremely practical handbook, the famous Coyne Check-Chart Trouble Shooting Method is applied to Transistorized Equipment and includes such subjects as Pre-amplifiers and Hearing Aids; Audio Amplifiers, Portable Sets, and Special Types of equipment. Hundreds of photos, illustrations, diagrams and Check-Charts; Valuable reference sections. 525 pages. Spiral Binding. Price 47/6. (Please send coupon with order).

No. 4. LATEST INSTRUMENT FOR SERVICING RADIO AND TELEVISION. Coyne.

This up-to-the-minute book tells all about modern radio, TV and electrical testing equipment and how to use it. Money-making short cuts on trouble-shooting, servicing, construction, and other jobs. Over 350 pages, 220 photos and diagrams. Covers Multimeters, Resistors, Ohmmeters, Oscilloscopes and many others. All data has been pretested in the Coyne radio shops. Vinyl cloth covers. 28/-.

No. 5. PRACTICAL TELEVISION SERVICING AND TROUBLE SHOOTING MANUAL. Coyne.

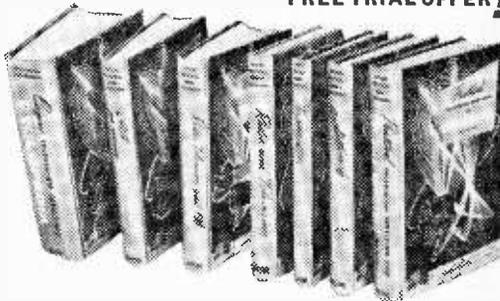
A book of fast time saving methods for servicing TV receivers. Includes dozens of new testing ideas all of which have been proven on the job. This book shows how radio knowledge can be applied to help solve television problems. Contents include TV Servicing methods, TV Servicing Instruments, Tuners, Video I.F., Amplifiers, alignment, etc., with 200 crystal clear photos and diagrams. 457 pages. Washable vinyl cloth covers. Price 34/-.

No. 6. COYNE TELEVISION SERVICING CYCLOPEDIA. Harold P. Manly, Coyne.

Quick and concise answers to TV problems in alphabetical order, cross indexed, fully illustrated, covers hundreds of questions involving radio, TV, electronics operation and repair. 450 illustrations; photos, diagrams, charts, test patterns, etc., 850 pages. Vinyl cloth covers. Price 47/6.

No. 10. TELEVISION EXPLAINED. Miller and Spreadbury. (LIFPE)

In simple terms and non-mathematical language gives step-by-step survey of modern television receivers and aerial systems, including AGC and Flywheel Synchronising. 134 pages. 12/6.

FREE TRIAL OFFER!


No. 8

COYNE'S NEW PIN-POINT TV TROUBLES

TAKES HEADACHES OUT OF ALL SERVICING PROBLEMS

Your most useful on-the-job "too"! Quickly and easily pin-points the exact trouble in any TV set. Covers 70 symptoms, 700 trouble spots. Over 340 cross-indexed pages; 50 time-saving Check-Charts; 290 diagrams and photos; explanation of circuits and designs.

SIMPLE CHECK-CHART SYSTEM SAVES TIME!

This amazingly practical handbook shows you how to find the trouble in any TV circuit FAST! Simple cross-index tells you in what section you'll find cause of trouble. Handy Check-Charts then help you accurately locate the EXACT trouble spot. Cut waste time, eliminate hours of aggravation, get right to the heart of the trouble in minutes.

USE THIS BOOK RIGHT ON THE JOB—NO NEED TO MEMORIZE! This Pin-Point Book was designed especially for on-the-job trouble-shooting. You simply turn to the indexed section, locate the circuit description and Check-Chart, and in minutes you have the trouble spot located and ready for repair. No complicated theory or mathematics. Down-to-earth, practical circuit description, service methods and trouble-shooting techniques. Published by the famous Coyne Electrical School and approved by leading authorities in the field.

No. 7. TRANSISTOR CIRCUIT HANDBOOK. Louis E. Garner, Jr. Coyne. A practical Transistor Circuit Reference Handbook by the eminently qualified Louis E. Garner, Jr., one of the greatest writers on transistor applications. Covers Transistor Circuitry, Basic Circuits, Circuit Applications and General Reference Material. Dozens of how-to-do-it illustrations with more than 300 circuit diagrams. Over 400 pages. Vinyl cloth covers. 38/6. (When ordering this book please be sure to clip the coupon).

No. 10. TELEVISION RECEIVER SERVICING. Vol. 1, by E. A. W. Spreadbury. 1961 Edition. (LIFPE) Timebase Circuits, including the Cathode Ray Tube. How to check the Waveform at the Input and Output of each section—Faults—Blank Screen—Obtaining a Baster, Applying a Signal, Synchronisation, Interlace Quality, etc. 362 pages. 25/-.

NOTE

* Any liffe or Coyne book is available on time payment plan! * Send name of title required.

Just mail coupon for free trial. After 7 days send only low price or return books and pay nothing. If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum three books). To buy one book send one-half in 7 days, and one-half in 30 days.

LIMITED OFFER! ACT NOW!

To SIM-TECH BOOK COMPANY

Mail Order Division, DEPT. PTV12, Gaters Mill, West-End, Southampton, Hants.

Please send me the special Elementary Radio TV Set as per special offer.

Rush the books circled below for 7-day FREE TRIAL as per offer.

9 4 5 6 13 8 7 10

Tick here if enclosed full price. Same 7-day money back guarantee

Name

Address

City.....County.....

Postage 1/3, orders under £3. 2/- orders over £3.

TELEVISION TUBES RE-BUILT BY "RE-VIEW"

	PRICE:		
12in.	£4.10.0
14in.	£4.15.0
15in.	£5. 0.0
17in.	£5. 0.0
21in.	£7. 0.0

SAVE £££s

Correct voltage heaters
All types



TWELVE MONTHS' GUARANTEE

Free carriage and insurance
Cash with order or C.O.D.

Be one of our satisfied customers. Call and see our TUBES REBUILT and TESTED
RE-VIEW (London) LTD., 10 High St., Colliers Wood, London S.W.19

Terms to the Trade

Tel.: LIBERTY 3272

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee
"NO PASS — NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

**WHICH IS YOUR
PET SUBJECT?**

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtmanship,
Television, etc.

**GET SOME
LETTERS AFTER
YOUR NAME!**

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
A.I.O.B.
A.F.R.Ac.S.
B.Sc.
A.M.Brit.I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

**PRACTICAL
EQUIPMENT**

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.H.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

**INCLUDING
TOOLS!**

The specialist Electronics Division of B.I.E.T. incorporating E.M.I. Institutes NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.
SCHOOL OF
ELECTRONICS**



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
 (Write if you prefer not to cut page)
NAME.....
ADDRESS.....
.....
SUBJECT OR EXAM THAT INTERESTS ME..... (SE/20.)

**BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY (Incorporating E.M.I. Institutes)**
(Dept. SE/20), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

C.R.T. BOOSTER TRANSFORMERS
TYPE A. OPTIONAL 25% and 50% BOOST.
 2 V. OR 3 V. OR 6.3 V. OR 10.8 V. 2/2
 18.2 V. MAINS INPUT. 1/6

TYPE A2. HIGH QUALITY, LOW CAPACITY.
 10/15 pF. OPTIONAL BOOST 25%, 50%,
 75%. MAINS INPUT. 1/6

TYPE B. MAINS INPUT. MULTI OUTPUT 2,
 4, 6.3, 7.8, 10 and 13 VOLTS. BOOST 25%
 AND 50%. LOW CAPACITY. 2/1-
 Full instructions supplied.

TRIMMERS. Ceramic, 30, 50, 70 pF. 8d.; 100 pF.
 150 pF. 1/3; 250 pF. 1/6; 500 pF. 750 pF. 1/8.

RESISTORS. Preferred values, 10 ohms to 10 meg.
 1/2, w. 4d.; 1/4, w. 4d.; 1 w. 8d.; 2 w. 1/1-
 HIGH STABILITY. 1/4 w. 1%, 2/1- Preferred values,
 10 Ω to 10 meg. Ditto, 5 Ω, 100 Ω to 5 meg. Ω. 8d.
 5 watt }
 10 watt } **WIRE-WOUND RESISTORS** } 1/6
 15 watt } 25 ohms—10,000 ohms } 1/6
 12.5K to 50K 10 w. } 3/1-

AMERICAN "BRAND FIVE"
PLASTIC RECORDING TAPE

Double Play 7in. reel, 2,400ft. 80	Spac. 6
5in. reel, 1,200ft. 37/8	Plastic
Long Play 7in. reel, 1,800ft. 35/	Reels
5in. reel, 1,200ft. 23/8	3 in. 1/6
5in. reel, 900ft. 18/6	4 in. 2/1-
	5 in. 2/1-
Standard 7in. reel, 1,200ft. 25/1-	5 1/2 in. 2/1-
5in. reel, 600ft. 16/1	7 1/2 in. 2/6

"Instant" Bulk Tape Eraser and Head De-
 fluxer. 200/250 v. A.C., 27/6. Leadat, S.A.E.

O.P. TRANSFORMERS. Heavy Duty 50 mA, 4/6.
 Multiratio, post-pull. 7/6. Ditto, 10 w. 15/6. Mini-
 nature, 354, etc. 4/6. L.F. COILS. 12 to 14 ohms.
 5 mA, 5/1-; 10 H. 85 mA, 10/6; 10 H. 150 mA, 14/1-

MAINS TRANSFORMERS 200/250 v. A.C.
STANDARD. 250-0-250, 80 mA, 6.3 v. 3.5 a.
 tapped 4 v. 4. Rectifier 6.3 v. 1 a. 5 v.
 2 a. or 4 v. 2 a. ditto, 350-0-350 2/6

MINIATURE 200-0-200 mA, 6.3 v. 1 a. 10/6

MIDGET 220 v. 45 mA, 6.3 v. 2 a. 15/6

SMALL 220-0-220, 50 mA, 6.3 v. 2 a. 17/6

STD. 250-0-250, 65 mA, 6.3 v. 3.5 a. 17/6

HEATER TRANS. 6.3 v. 1 1/2 amp. 7/6

Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp. 8/6

Ditto, sec. 6.3 v. 3 amp. 9/6

GENERAL PURPOSE LOW VOLTAGE 2a.
 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/6

AUTO TRANSFORMERS. 150 w. 22/6
 0, 10, 120, 200, 330, 250 v. 22/6

ALADDIN FORMERS and core, 4in., 8d.; 1in., 10d.
 0.3in. FORMERS 5937/8 and Cans 71/2. 4in. sq. x
 2 1/2 in. and 4in. sq. x 1 1/2 in., 2/1- each.

SOLIN Soldering Iron, 200 or 240 v. 25 w. 24/1-

MAINS DROPPERS. 200 v. 1 1/2 in. A.C. sliders,
 0.3 amp., 1,000 ohms. 4/3. 0.2 amp., 1,000 ohms, 4/3.
LINE CORD. 0.3 amp., 60 ohms per ft., 0.2 amp., 100
 ohms per ft., 2-way, 1/1- per ft., 1-way, 1/1- per ft.

LOUDSPEAKER P.M. 3 OHM. 2 1/2 in., 18 Ω, 3in., 17/6.
 8in. Plessey, 18 Ω, 6in. x 3in. Rola, 18 Ω, 6in.
 Rola, 18 Ω, 10 in. x 3in., 27/6. 10 in., 30/1-

Hi-Fi Tweeter, 25in., 12 Ω, 1R., 30/1-

STENTORIAN HF 1012. 10 Ω, 3 to 15 ohms, 10w., 95/1-

BAKER 15 watt 3 ohms, or 15 ohms, 90/1-

CRYSTAL DROPS. 0.2, 0.25, 0.3, 0.4, 0.5, 0.6, 0.7, 0.8, 0.9, 1.0, 1.1, 1.2, 1.5, 2.0, 3.0, 4.0, 5.0, 6.0, 7.0, 8.0, 9.0, 10.0, 15.0, 20.0, 30.0, 40.0, 50.0, 60.0, 70.0, 80.0, 90.0, 100.0, 150.0, 200.0, 300.0, 400.0, 500.0, 600.0, 700.0, 800.0, 900.0, 1000.0, 1500.0, 2000.0, 3000.0, 4000.0, 5000.0, 6000.0, 7000.0, 8000.0, 9000.0, 10000.0, 15000.0, 20000.0, 30000.0, 40000.0, 50000.0, 60000.0, 70000.0, 80000.0, 90000.0, 100000.0, 150000.0, 200000.0, 300000.0, 400000.0, 500000.0, 600000.0, 700000.0, 800000.0, 900000.0, 1000000.0, 1500000.0, 2000000.0, 3000000.0, 4000000.0, 5000000.0, 6000000.0, 7000000.0, 8000000.0, 9000000.0, 10000000.0, 15000000.0, 20000000.0, 30000000.0, 40000000.0, 50000000.0, 60000000.0, 70000000.0, 80000000.0, 90000000.0, 100000000.0, 150000000.0, 200000000.0, 300000000.0, 400000000.0, 500000000.0, 600000000.0, 700000000.0, 800000000.0, 900000000.0, 1000000000.0, 1500000000.0, 2000000000.0, 3000000000.0, 4000000000.0, 5000000000.0, 6000000000.0, 7000000000.0, 8000000000.0, 9000000000.0, 10000000000.0, 15000000000.0, 20000000000.0, 30000000000.0, 40000000000.0, 50000000000.0, 60000000000.0, 70000000000.0, 80000000000.0, 90000000000.0, 100000000000.0, 150000000000.0, 200000000000.0, 300000000000.0, 400000000000.0, 500000000000.0, 600000000000.0, 700000000000.0, 800000000000.0, 900000000000.0, 1000000000000.0, 1500000000000.0, 2000000000000.0, 3000000000000.0, 4000000000000.0, 5000000000000.0, 6000000000000.0, 7000000000000.0, 8000000000000.0, 9000000000000.0, 10000000000000.0, 15000000000000.0, 20000000000000.0, 30000000000000.0, 40000000000000.0, 50000000000000.0, 60000000000000.0, 70000000000000.0, 80000000000000.0, 90000000000000.0, 100000000000000.0, 150000000000000.0, 200000000000000.0, 300000000000000.0, 400000000000000.0, 500000000000000.0, 600000000000000.0, 700000000000000.0, 800000000000000.0, 900000000000000.0, 1000000000000000.0, 1500000000000000.0, 2000000000000000.0, 3000000000000000.0, 4000000000000000.0, 5000000000000000.0, 6000000000000000.0, 7000000000000000.0, 8000000000000000.0, 9000000000000000.0, 10000000000000000.0, 15000000000000000.0, 20000000000000000.0, 30000000000000000.0, 40000000000000000.0, 50000000000000000.0, 60000000000000000.0, 70000000000000000.0, 80000000000000000.0, 90000000000000000.0, 100000000000000000.0, 150000000000000000.0, 200000000000000000.0, 300000000000000000.0, 400000000000000000.0, 500000000000000000.0, 600000000000000000.0, 700000000000000000.0, 800000000000000000.0, 900000000000000000.0, 1000000000000000000.0, 1500000000000000000.0, 2000000000000000000.0, 3000000000000000000.0, 4000000000000000000.0, 5000000000000000000.0, 6000000000000000000.0, 7000000000000000000.0, 8000000000000000000.0, 9000000000000000000.0, 10000000000000000000.0, 15000000000000000000.0, 20000000000000000000.0, 30000000000000000000.0, 40000000000000000000.0, 50000000000000000000.0, 60000000000000000000.0, 70000000000000000000.0, 80000000000000000000.0, 90000000000000000000.0, 100000000000000000000.0, 150000000000000000000.0, 200000000000000000000.0, 300000000000000000000.0, 400000000000000000000.0, 500000000000000000000.0, 600000000000000000000.0, 700000000000000000000.0, 800000000000000000000.0, 900000000000000000000.0, 1000000000000000000000.0, 1500000000000000000000.0, 2000000000000000000000.0, 3000000000000000000000.0, 4000000000000000000000.0, 5000000000000000000000.0, 6000000000000000000000.0, 7000000000000000000000.0, 8000000000000000000000.0, 9000000000000000000000.0, 10000000000000000000000.0, 15000000000000000000000.0, 20000000000000000000000.0, 30000000000000000000000.0, 40000000000000000000000.0, 50000000000000000000000.0, 60000000000000000000000.0, 70000000000000000000000.0, 80000000000000000000000.0, 90000000000000000000000.0, 100000000000000000000000.0, 150000000000000000000000.0, 200000000000000000000000.0, 300000000000000000000000.0, 400000000000000000000000.0, 500000000000000000000000.0, 600000000000000000000000.0, 700000000000000000000000.0, 800000000000000000000000.0, 900000000000000000000000.0, 1000000000000000000000000.0, 1500000000000000000000000.0, 2000000000000000000000000.0, 3000000000000000000000000.0, 4000000000000000000000000.0, 5000000000000000000000000.0, 6000000000000000000000000.0, 7000000000000000000000000.0, 8000000000000000000000000.0, 9000000000000000000000000.0, 10000000000000000000000000.0, 15000000000000000000000000.0, 20000000000000000000000000.0, 30000000000000000000000000.0, 40000000000000000000000000.0, 50000000000000000000000000.0, 60000000000000000000000000.0, 70000000000000000000000000.0, 80000000000000000000000000.0, 90000000000000000000000000.0, 100000000000000000000000000.0, 150000000000000000000000000.0, 200000000000000000000000000.0, 300000000000000000000000000.0, 400000000000000000000000000.0, 500000000000000000000000000.0, 600000000000000000000000000.0, 700000000000000000000000000.0, 800000000000000000000000000.0, 900000000000000000000000000.0, 1000000000000000000000000000.0, 1500000000000000000000000000.0, 2000000000000000000000000000.0, 3000000000000000000000000000.0, 4000000000000000000000000000.0, 5000000000000000000000000000.0, 6000000000000000000000000000.0, 7000000000000000000000000000.0, 8000000000000000000000000000.0, 9000000000000000000000000000.0, 10000000000000000000000000000.0, 15000000000000000000000000000.0, 20000000000000000000000000000.0, 30000000000000000000000000000.0, 40000000000000000000000000000.0, 50000000000000000000000000000.0, 60000000000000000000000000000.0, 70000000000000000000000000000.0, 80000000000000000000000000000.0, 90000000000000000000000000000.0, 100000000000000000000000000000.0, 150000000000000000000000000000.0, 200000000000000000000000000000.0, 300000000000000000000000000000.0, 400000000000000000000000000000.0, 500000000000000000000000000000.0, 600000000000000000000000000000.0, 700000000000000000000000000000.0, 800000000000000000000000000000.0, 900000000000000000000000000000.0, 1000000000000000000000000000000.0, 1500000000000000000000000000000.0, 2000000000000000000000000000000.0, 3000000000000000000000000000000.0, 4000000000000000000000000000000.0, 5000000000000000000000000000000.0, 6000000000000000000000000000000.0, 7000000000000000000000000000000.0, 8000000000000000000000000000000.0, 9000000000000000000000000000000.0, 10000000000000000000000000000000.0, 15000000000000000000000000000000.0, 20000000000000000000000000000000.0, 30000000000000000000000000000000.0, 40000000000000000000000000000000.0, 50000000000000000000000000000000.0, 60000000000000000000000000000000.0, 70000000000000000000000000000000.0, 80000000000000000000000000000000.0, 90000000000000000000000000000000.0, 100000000000000000000000000000000.0, 150000000000000000000000000000000.0, 200000000000000000000000000000000.0, 300000000000000000000000000000000.0, 400000000000000000000000000000000.0, 500000000000000000000000000000000.0, 600000000000000000000000000000000.0, 700000000000000000000000000000000.0, 800000000000000000000000000000000.0, 900000000000000000000000000000000.0, 1000000000000000000000000000000000.0, 1500000000000000000000000000000000.0, 2000000000000000000000000000000000.0, 3000000000000000000000000000000000.0, 4000000000000000000000000000000000.0, 5000000000000000000000000000000000.0, 6000000000000000000000000000000000.0, 7000000000000000000000000000000000.0, 8000000000000000000000000000000000.0, 9000000000000000000000000000000000.0, 10000000000000000000000000000000000.0, 15000000000000000000000000000000000.0, 20000000000000000000000000000000000.0, 30000000000000000000000000000000000.0, 40000000000000000000000000000000000.0, 50000000000000000000000000000000000.0, 60000000000000000000000000000000000.0, 70000000000000000000000000000000000.0, 80000000000000000000000000000000000.0, 90000000000000000000000000000000000.0, 100000000000000000000000000000000000.0, 150000000000000000000000000000000000.0, 200000000000000000000000000000000000.0, 300000000000000000000000000000000000.0, 400000000000000000000000000000000000.0, 500000000000000000000000000000000000.0, 600000000000000000000000000000000000.0, 700000000000000000000000000000000000.0, 800000000000000000000000000000000000.0, 900000000000000000000000000000000000.0, 1000000000000000000000000000000000000.0, 1500000000000000000000000000000000000.0, 2000000000000000000000000000000000000.0, 3000000000000000000000000000000000000.0, 4000000000000000000000000000000000000.0, 5000000000000000000000000000000000000.0, 6000000000000000000000000000000000000.0, 7000000000000000000000000000000000000.0, 8000000000000000000000000000000000000.0, 9000000000000000000000000000000000000.0, 10000000000000000000000000000000000000.0, 15000000000000000000000000000000000000.0, 20000000000000000000000000000000000000.0, 30000000000000000000000000000000000000.0, 40000000000000000000000000000000000000.0, 50000000000000000000000000000000000000.0, 60000000000000000000000000000000000000.0, 70000000000000000000000000000000000000.0, 80000000000000000000000000000000000000.0, 90000000000000000000000000000000000000.0, 100000000000000000000000000000000000000.0, 150000000000000000000000000000000000000.0, 200000000000000000000000000000000000000.0, 300000000000000000000000000000000000000.0, 400000000000000000000000000000000000000.0, 500000000000000000000000000000000000000.0, 600000000000000000000000000000000000000.0, 700000000000000000000000000000000000000.0, 800000000000000000000000000000000000000.0, 900000000000000000000000000000000000000.0, 1000000000000000000000000000000000000000.0, 1500000000000000000000000000000000000000.0, 2000000000000000000000000000000000000000.0, 3000000000000000000000000000000000000000.0, 4000000000000000000000000000000000000000.0, 5000000000000000000000000000000000000000.0, 6000000000000000000000000000000000000000.0, 7000000000000000000000000000000000000000.0, 8000000000000000000000000000000000000000.0, 9000000000000000000000000000000000000000.0, 100.0, 15000000000000