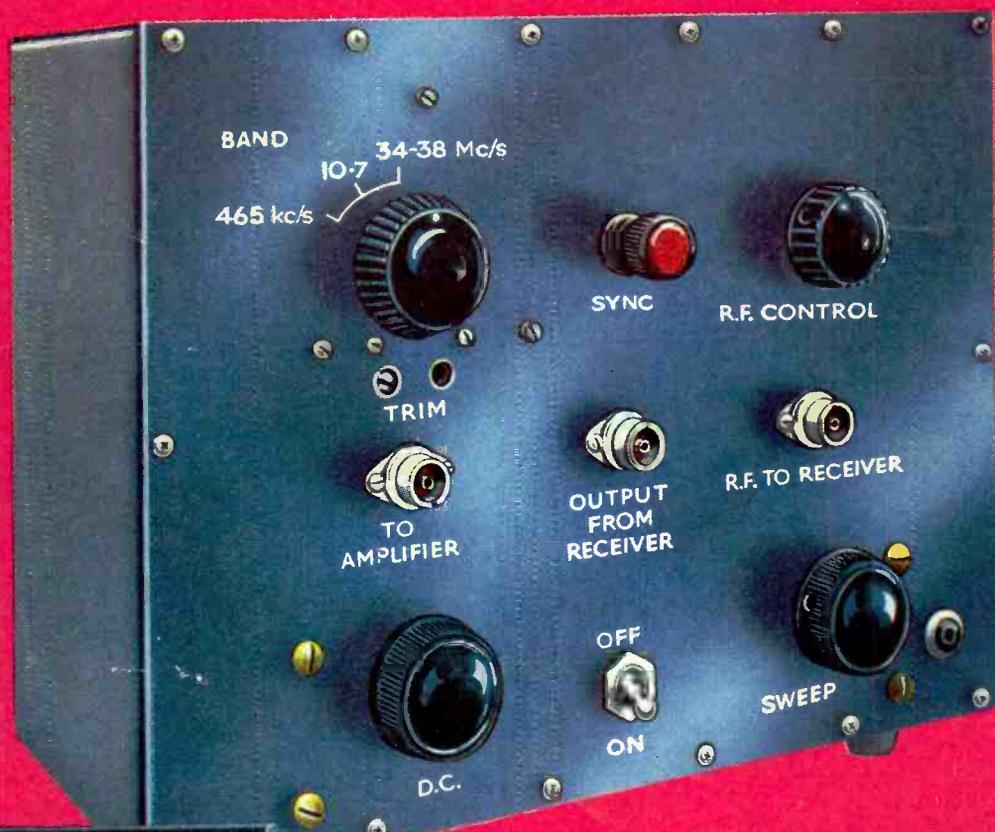


# Practical SEPTEMBER 1961 1'6 TELEVISION

*A Precision Wobbulator*



## **A TV VALVE TESTER**

**Recognising transmitter defects  
Servicing the Invicta 338**

# Build your own Aerials...



## AT HOME

**AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.**  
Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to—

# Fringevision Ltd.

**MARLBOROUGH, WILTS. Phone: 657/8**

### RST

**MAIL ORDER DEPARTMENT**  
211 Streatham Road, Mitcham, Surrey  
**ALL VALVES LISTED ARE NEW STOCK**  
& Terms C.A.O. or C.O.D. Postage 3d. per valve.  
**MITCHAM 6201**

AZ 15/6	EF92 5/-	PCF82 8/6	UY35 6/6	6K8G 7/6
R65 8/6	EL42 10/-	PL82 8/6	VP4B 17/6	6R8GT 12/6
DAF91 7/6	EF84 7/-	PCL82 10/6	W81M 5/9	6L1 15/6
DAF96 10/-	EL90 8/6	PCL83 12/6	W142 9/-	6L18 12/6
DF91 4/-	EM80 10/-	PEN4A 17/6	W727 7/6	6L19 21/-
DH719 7/6	EM81 10/-	PEN4A 17/6	X78 21/-	6N7G/GT 7/6
DK91 9/-	EY81 10/6	PEN4VA 17/6	X79 21/-	Z21 12/6
EABC80 7/6	EY86 6/6	PL36 15/-	Z27 4/9	Z152 6/6
EAF4210/-	EY91 9/-	PL81 14/9	Z152 6/6	Z719 7/9
EB91 5/-	EZ33 7/-	PL82 8/-	IR3 9/-	6V6G 5/6
EBC41 9/6	EZ41 7/6	PL83 10/6	PY80 8/-	6X5GT 5/-
EBF30 9/6	EZ80 7/6	PY81 7/6	PY82 8/-	7S7 10/6
EBF89 7/6	EZ81 7/6	PY83 8/6	PY83 8/6	7Y4 7/6
EC91 9/6	FC2 21/6	R10 21/-	R10 21/-	8D3 4/-
ECC33 5/-	FC4 17/6	R19 19/6	R19 19/6	10LD11 15/-
ECC81 8/-	FC13 17/6	TDD4 17/6	TDD4 17/6	12AH8 10/-
ECC83 9/6	FC13C 21/-	TP22 17/6	TP22 17/6	12AT6 9/-
ECC84 9/6	GZ32 11/6	U142 8/-	U142 8/-	12AT7 6/-
ECC85 8/-	H30 5/6	U147 7/-	U147 7/-	12AU7 9/-
ECF80 12/6	H63 9/6	U153 9/6	U153 9/6	12AX7 9/6
ECF82 12/6	HBC90 9/6	UBC80 7/-	UBC80 7/-	12BA6 9/-
ECH4210/-	HL92 6/6	UBF90 9/6	UBF90 9/6	12BE6 9/6
ECH81 9/-	HL33D 10/-	UCH2 8/6	UCH2 8/6	12B7 15/-
ECL80 9/-	KT33C 10/-	UCL81 8/6	UCL81 8/6	12J7G/GT 9/6
ECL82 12/6	KT66 17/6	UCL83 8/6	UCL83 8/6	12K7GT 8/6
EF37A 8/6	L7319 12/6	UF41 13/8	UF41 13/8	12K8GT 12/6
EF40 15/-	MKT315 9/-	UF89 8/-	UF89 8/-	12Q7 8/6
EF41 9/3	ML4 15/-	UL41 9/-	UL41 9/-	12Q7GT 8/6
EF42 10/8	MS14 17/6	UL31 7/6	UL31 7/6	35Z4GT 7/6
EF50(A) 4/-	MU14 9/-	UY41 7/6	UY41 7/6	50L6GT 9/-
EF80 4/-	MX40 17/6			
EF85 5/6	N142 9/6			
EF86 11/-	N153 11/8			
EF89 10/-	PCC84 9/-			
EF91 4/-	PCF80 9/-			

**SEND FOR LISTS.**

Quotations given for any types not listed. Obsolete and old types a speciality.

## THOUSANDS

OF SATISFIED PEOPLE

VIEW ON **E.M.S.**

### REBUILT TELEVISION TUBES

- ★ A NEW GUN IN EVERY TUBE
- ★ BUY DIRECT FROM THE FACTORY
- ★ 18 MONTHS' GUARANTEE

**12 inch £5.0.0 14 inch £5.10.0**  
**17 inch £6.10.0**

Immediate dispatch on receipt of Remittance

Carriage and insurance 12/6 extra  
**£1 Refunded on receipt of your old Tube**

**SPECIAL TERMS TO THE TRADE**

**MARSHALL'S for TELEVISION LTD.**

131 St. Ann's Road, Tottenham, London, N.15  
STAMFORD HILL 3267 & 5555

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the RIGHT course:

RADIO & TELEVISION ENGINEERING  
INDUSTRIAL TELEVISION

RADIO & TELEVISION SERVICING  
RADIO SERVICE AND SALES

VHF/FM ENGINEERING : ELECTRONIC  
COMPUTORS & PROGRAMMING

ICS provides thorough coaching for professional examinations:


Brit. I.R.E., City and Guilds Telecommunication Technicians, C. & G. Radio & TV Servicing (R.T.E.B.); C. & G. Radio Amateurs.

### LEARN AS YOU BUILD

*Practical Radio Courses*

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build YOUR OWN 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-meter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.
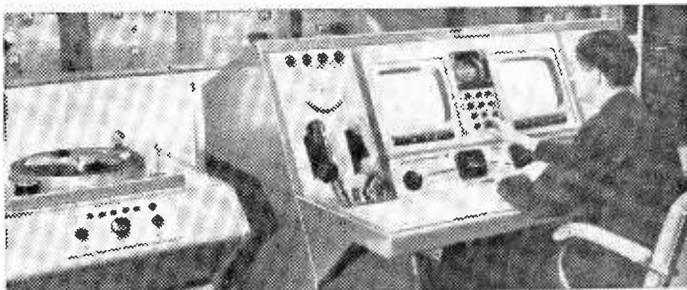
# Technical Training in Radio, Television and Electronics Engineering with



**THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.**

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include: MECHANICAL, MOTOR, FIRE, ELECTRICAL & CHEMICAL ENGINEERING. FARMING, GARDENING. ARCHITECTURE & WOODWORKING. SELLING & MANAGEMENT. ART. PHOTOGRAPHY, etc., etc.

**PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . . .**

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
 (DEPT. 172). INTERTEXT HOUSE, PARKGATE RD., LONDON, S.W.11

PLEASE SEND FREE BOOK ON.....

NAME .....

ADDRESS .....

.....

OCCUPATION..... AGE.....

9.61

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE. ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.


OA2	17/6	6F6G	7/1	10F1	26/6	35Z4GT	6/1-	DH76	5/1-	EF40	15/1-	HJN309	24/7	PL84	12/8	UJABC80	9/1-	XFY34	17/6	
OB2	17/6	6F11	17/3	10F9	11/6	35Z5GT	9/1-	DH77	7/1-	EF41	9/1-	HVR2	20/-	PL820	18/8	UJAF42	9/1-	XH(1.5)	6/6	
OZ4	5/1-	6F12	4/6	10LD11	15/11	43	10/1-	DK32	12/1-	EF42	10/6	HVR2A	6/1-	PM84	17/7	UB41	12/1-	XSG(1.5)	6/6	
IA5	6/1-	6F13	11/6	10P13	15/1-	50C5	10/1-	DK91	6/6	EF50(A)	7/1-	KF35	8/6	PK4	10/6	UBC41	8/6	Y63	7/6	
IA7GT	12/1-	6F15	15/3	10P14	19/3	50C6DG		DK92	9/1-	EF50(E)	5/1-	KL35	8/6	PY31	16/7	UBC81	11/4	Z63	7/6	
ICS	12/6	6F23	10/6	12A6	5/1-		36/6	DK96	8/6	EF54	5/1-	KLL32	24/7	PY32	12/6	UBF80	9/1-	Z66	17/6	
ID6	10/6	6F24	12/6	12AC6	15/3	50L6GT	9/6	DL33	9/6	EF73	10/6	KT2	5/1-	PY80	7/6	UBF89	9/6	Z77	4/6	
IG6	17/6	6F32	10/6	12AD6	17/3	53KU	19/11	DL66	17/6	EF80	6/1-	KT33C	10/1-	PY81	8/6	UBL21	23/3	Z719	6/1-	
IHSGT	10/6	6F33	7/6	12AE6	13/11		7/7	DL68	15/1-	EF85	6/1-	KT36	15/1-	PY82	7/6	UC84	14/7			
IL4	3/6	6G6	6/6	12AH7	8/1-	78	6/6	DL72	15/1-	EF86	10/6	KT41	23/3	PY83	8/6	UC85	9/1-	Transistors		
ILD5	5/1-	6H6	3/1-	12AH8	12/6	80	6/6	DL92	7/1-	EF89	9/1-	KT44	12/6	PY88	13/3	UC88	16/7	and diodes		
ILN5	5/1-	6J5	5/1-	12AT6	7/6	83	15/1-	DL94	7/6	EF91	4/6	KT61	12/6	PZ30	19/11	UCH21	23/3	CGIC	7/6	
INSGT	10/6	6J6	5/6	12AT7	6/1-	85A2	16/1-	DL96	8/6	EF92	4/6	KT63	7/1-	QP21	7/1-	UCH42	9/6	CGE	7/6	
IR5	6/6	6J7G	6/1-	12AU6	23/3	90AG	6/76	DM70	7/6	EF97	13/3	KT66	15/1-	QP25	14/6	UCH81	9/6	CGE6	7/6	
IS4	9/1-	6J7GT	10/6	12A07	6/6	90AV	6/76	EB0F	30/1-	EF98	13/3	KT88	24/1-	QS150/15		UCH82	11/6	CGE7	7/6	
IS5	6/1-	6K7G	5/1-	12AV6	12/8	90C1	16/1-	EB3F	30/1-	EF183	18/7	KTW61	6/6		10/6	UCH83	19/3	CG10E	7/6	
IT4	3/6	6K7GT	6/1-	12AX7	7/6	90CG	37/6	EA50	2/1-	EF184	12/6	KTW62	7/6	R12	9/1-	UF41	9/1-	GD3, 4, 5		
IUS	6/1-	6K8GT	10/6	12BA6	8/1-	101	13/6	EA76	9/6	EK32	8/6	KTW63	6/6	R18	14/1-	UF42	12/6	6, 8	4/1-	
2D21	2P	15/1-	6K8G	6/6	12BE6	9/1-	150B2	18/1	EABC80	9/1-	EL32	5/1-	KTZ41	8/6	R19	19/11	UF80	10/6	OA70	3/1-
2P	26/6	6K25	19/11	12BH7	21/3	161	10/6	EAC91	4/6	EL33	12/6	KTZ63	7/6	RG1/240A		UF85	9/1-	OA73	3/1-	
X2	4/6	6L1	23/3	12E1	30/1-	185B1	33/2	EAF42	9/1-	EL34	15/1-	L63	6/1-		54/1-	UF86	17/11	OA79	3/1-	
3A4	6/1-	6L6G	8/1-	12J5GT	4/6	304	10/6	EB34	2/6	EL38	26/6	MHL4	7/6	RK34	7/6	UF49	9/1-	OA81	3/1-	
3A5	10/6	6L6M	9/6	12J7GT	9/6	305	10/6	EB41	8/6	EL41	9/1-	MHL D6	12/6	S130	22/6	UL41	9/1-	OA86	4/1-	
3B7	12/6	6L7GT	7/6	12K5	17/11	307	7/6	EB91	4/1-	EL42	10/6	ML4	8/6	SP4(7)	14/6	UL44	26/6	OA91	3/6	
3D6	5/1-	6L18	13/1-	12K7GT	5/6	956	3/1-	EB3C	23/3	EL81	16/7	MS4B	2/3	SP41	3/6	UL46	14/6	OA95	3/6	
3Q4	7/6	6L19	23/3	12K8GT	14/1-	1821	16/7	EB33	5/1-	EL83	19/11	MU12/14	8/1-	SP42	12/6	UL84	8/6	OA210	11/1-	
3Q5GT	9/6	6LD20	15/11	12Q7GT	5/1-	4033L	12/6	EB44	8/6	EL84	7/6	N37	23/3	SP61	3/6	UM14	17/3	OA211	20/1-	
354	7/1-	6N7	8/1-	12QA7	8/6	5763	12/6	EB41	8/6	EL85	13/11	N78	19/11	SU25	26/6	UM34	17/3	OC16	48/1-	
3V4	7/6	6P26	19/11	12SC7	8/6	7193	5/1-	EBF80	9/1-	EL86	17/3	N108	23/3	T41	9/1-	UM80	15/3	OC19	48/1-	
5R4GY	17/6	6P28	26/6	12SG7	7/1-	7475	7/6	EBF83	13/11	EL91	5/1-	N308	20/7	TD04	12/6	UR1C	18/7	OC23	87/1-	
5U4G	6/6	6Q7G	6/6	12SH7	8/6	90C2	5/6	EBF89	9/6	EL95	10/6	N339	15/1-	TH41	26/6	UU6	19/11	OC26	25/1-	
5Y4G	10/6	6Q7GT	11/1-	12S17	8/6	AC/PEN		EBL1	29/6	EL820	18/7	P61	3/6	TH233	33/2	UU7	16/7	OC28	25/1-	
5Y3	6/6	6R7G	10/1-	12SK7	6/1-	5-pin 23/3		EBL21	23/3	EL822	19/1-	PAB80		TP22	15/1-	UU8	26/6	OC35	25/6	
5Z3	19/11	6SA7GT	8/6	12SQ7	11/6	7-pin 15/3		EBL31	23/3	EM34	9/6		13/11	TP25	15/1-	UU9	7/6	OC44	11/1-	
5Z4G	9/1-	6SCT	7/6	12SR7	8/6	AC/2PEN		EC52	5/6	EM71	23/3	PCC8A	8/1-	TP2620	33/2	UY1N	18/7	OC45	10/1-	
6A7	10/6	6S7GT	7/6	12Y4	10/6	DD	12/6	EC54	6/1-	EM80	9/1-	PCC85	9/6	TY86F	13/7	UY21	16/7	OC56	22/6	
6A8	9/1-	6S7GT	8/1-	14S7	27/10	AC6PEN	7/6	EC70	12/6	EM81	9/1-	PCC88	18/1-	U12/14	8/6	UY41	7/6	OC66	25/1-	
6AC7	4/1-	6S17GT	8/1-	19AQ5	10/6	AC/TP	33/2	EC92	13/3	EM84	10/6	PCC89	11/6	U16	10/6	UY85	7/1-	OC70	6/6	
6AG5	5/6	6SK7GT	6/6	19H1	10/1-	ATP4	5/1-	EC33	5/6	EM85	17/3	PCF80	8/1-	U18/20	8/6	VMP4G	15/1-	OC71	6/6	
6AG7	6/6	6L7GT	6/6	20D1	15/3	AZ1	18/7	EC33	8/6	EN81	5/3-	PCF82	10/6	U19	36/1-	VMS48	15/1-	OC72	8/1-	
6AK5	8/1-	6SN7GT	5/6	20F2	26/6	AZ31	10/1-	EC34	24/7	EY51	9/1-	PCF84	16/7	U22	8/1-	VP2	12/6	OC73	16/1-	
6AL5	4/1-	6SQ7GT	9/1-	20L1	26/6	AZ41	13/11	EC35	8/6	EY83	16/7	PCF86	15/1-	U24	29/10	VP4	15/1-	OC75	8/1-	
6AM6	4/6	6S5GT	8/1-	20P1	26/6	B36	15/1-	EC40	23/3	EY84	14/1-	PCL82	10/6	U25	17/11	VP28	14/6	OC77	15/1-	
6AQ5	7/6	6U4GT	12/6	20P3	23/3	BL63	7/6	EC81	6/1-	EY86	9/1-	PCL83	10/6	U26	10/1-	VP48	23/3	OC78	8/1-	
6AT6	7/1-	6U5G	7/6	20P4	26/6	C1C	12/6	EC82	6/6	EZ35	6/1-	PCL84	12/6	U31	9/6	VP13C	7/1-	OC81	8/1-	
6AU6	10/1-	6U7G	8/6	20P5	23/3	CIC	12/6	EC83	7/6	EZ40	7/1-	PCL85	16/7	U33	26/6	VP23	6/6	OC170	13/6	
6AV6	12/6	6V6G	7/1-	25A6G	10/6	CB1L	26/6	EC84	9/1-	EZ41	7/1-	PCL86	16/7	U35	26/6	VP41	6/1-	OC171	14/6	
6BB	5/1-	6V6GT	7/1-	25L6GT	10/6	CB31	23/3	EC85	8/6	EZ80	7/1-	PEN4A	23/3	U37	26/6	VR105	8/1-	OC200	16/6	
6BA6	7/6	6V6G	5/1-	25Y5G	10/6	CC35	23/3	EC88	18/1-	EZ81	7/1-	PEN8A	26/6	U43	9/1-	VR150	7/6	OC203	24/1-	
6BE6	6/1-	6X5GT	6/1-	25Z4G	9/6	CC506	6/6	EC91	5/6	EC4	15/1-	PEN4DD		U50	6/1-	VT51A	3/1-	OC271	29/6	
6BG6G	23/3	6J30L2	10/1-	25Z5	9/6	CL33	19/3	ECF80	10/6	FW4/500	8/6			U50	6/1-	VT51	4/1-	T12	45/1-	
6BH6	8/1-	7A7	12/6	25Z6G	10/1-	CV63	10/6	ECF82	10/6	FW4/800	8/6	PEN25	4/6	U52	6/6	W76	5/6	T13	40/1-	
6BJ6	6/1-	7B6	21/3	27SU	19/11	CY1	18/7	ECF86	19/11	GU50	27/6	PEN40DD		U54	19/11	W81M	6/1-	T13	50/1-	
6BQ7A	15/1-	7B7	8/1-	28D7	7/1-	CY31	11/1-	ECH3	26/6	GZ30	9/1-		25/1-	U76	6/1-	W107	18/7	TP1	40/1-	
6BR7	12/6	7C5	8/1-	30C1	8/1-	D1	3/1-	ECH21	23/3	GZ32	10/1-	PEN44	26/6	U78	5/1-	W279	19/11	TP2	40/1-	
6BS7	25/1-	7C6	8/1-	30F5	6/1-	D15	10/6	ECH35	6/6	GZ33	19/11	PEN45	19/6	U107	16/7	X24M	24/7	TP5	10/1-	
6BW6	8/6	7H7	8/1-	30FL1	10/1-	D77	4/1-	ECH42	9/1-	GZ34	14/1-	PEN46	7/6	U191	16/7	X41	15/1-	TS2	12/6	
6BW7	6/1-	7R7	12/6	30L1	8/1-	DAC32	10/6	ECH81	9/1-	GZ37	19/11	PEN383	23/3	U201	16/7	X61(C)	12/6	TS3	15/1-	
6C4	5/1-	7S7	9/6	30L15	11/6	DAF91	6/1-	ECH83	13/11	H63	12/6	PEN453DD		U251	14/1-	X63	9/1-	TS4	24/1-	
6C5	6/6	7Y7	8/6	30P4	12/1-	DAF96	8/6	ECL80	9/1-	HABC80			33/2	U281	19/11	X65	12/6	V30/10P	28/6	
6C6	6/6	7Y4	7/6	30P12	7/6	DD41	13/11	ECL82	10/6			PEN/DD		U282	22/7	X66	12/6	XA101	23/1-	
6C9	13/6	8D2	3/6	30P19	12/1-	DET	7/6	ECL83	19/3	HL2	7/6		4020	33/2	U301	23/3	X76M	14/1-	XA102	26/1-
6C10	9/1-	8D3	4/6	30PL1	10/6	DF33	10/6	ECL86	17/7	HL23	15/3	PL33	19/3	U329	14/1-	X78	23/3	XA103	15/1-	
6CD6G	36/6	9W6W	15/3	30PL13	16/6	DF66	15/1-	EP9	23/3	HL23DD	7/6	PL36	12/1-	U339	16/7	X79	23/3	XA104	18/1-	
6CH6	9/1-	9D2	4/1-	35A5	21/3	DF91	3/6	EP22	14/1-	HL41DD		PL38	26/6	U403	16/7	X109	17/3	XB102	10/1-	
6D6	6/6	10C1	13/1-	35L6GT	9/6	DF96	8/6	EP36	4/1-			PL81	10/6	U404	8/6	XD(1.5)	6/6	XB103	14/1-	
6E5	12/6	10C2	26/6	35W4	7/6	DF97	9/1-	EP37A	8/1-	HL42DD		PL82	7/6	U801	29/10	XF81	18/1-	XB104	10/1-	
6F1	26/6	10D2	12/1-	35Z3	10/6	DH63	6/6	EP39	5/6			PL83	9/1-	U4020	16/7	XFY12	9/6	XC101	16/1-	

ALL GOODS BRAND NEW AND SUBJECT TO FULL MAKERS' GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL SECONDHAND GOODS OR MANUFACTURERS' REJECTS.

### VOLUME CONTROLS

</

**More** for less...

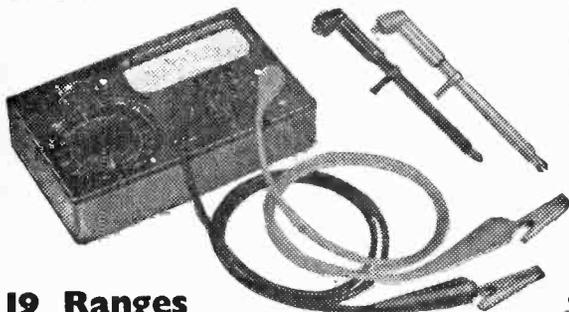

**19 Ranges**

<b>D.C. Voltage</b>	<b>A.C. Voltage</b>
0—100 mV.	0—10 V.
0—2.5 V.	0—25 V.
0—10 V.	0—100 V.
0—25 V.	0—250 V.
0—100 V.	0—1000 V.
0—250 V.	
0—1000 V.	
<b>D.C. Current</b>	
0—100µA	
0—1mA	
0—10mA	
0—100mA	
0—1A	
<b>Resistance</b>	
0—20,000 Ω	
0—2M Ω	

List Price: **£9:10s.**  
complete with Test Leads  
and Crocodile Clips.  
Leather case if required 39/-  
Size: 5½ x 3½ x 1¼ in.  
Weight: 1 lb. approx.

MM12

Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor is now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS. The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red coloured pointer and effectively damped movement facilitate easy and rapid reading. For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter.

Use **PRODCLIPS** with the **MULTIMINOR** (Pat. No. 748811)

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be. 15/- per pair.

...with the  
**MULTIMINOR**

Write now for illustrated literature to:—

**AVO LTD**


**AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD  
LONDON - S.W.1** Victoria 3404 (12 lines)

**M** A Member of the Metal Industries Group of Companies

**HARVERSON SURPLUS CO. LTD.**  
83 HIGH ST., MERTON, S.W.19. Cherrywood 3985/6/7

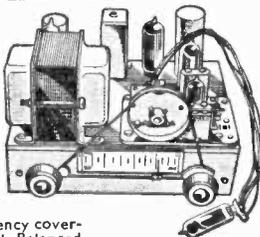**F.M. TUNER KIT**

At last a quality F.M. Tuner Kit at a price you can afford. Just look at these fine features which are usually associated with equipment at twice the price!



★ F.M. Tuning Head by famous maker. ★ Guaranteed Non-drift. ★ Permeability Tuning ★ Frequency coverage 88-100 Mc/s. ★ OA81 Balanced Diode Output. ★ Two I.F. Stages and Discriminator. ★ E.M.84 Magic Eye. ★ Self powered, using a good quality mains transformer and valve rectifier. ★ Valves used ECC85, two EF80's, EM84 (Magic Eye) and EZ80 (rectifier). ★ Fully drilled chassis. ★ Everything supplied, down to the last nut and bolt. ★ Size of completed tuner 8 x 6 x 5¼ in.

All parts sold **£4.19.6** Plus 8/6 P.P. & Ins. separately.

Circuit diagram and illustrations, 1/6 post free.  
**Note:**—To show the chassis clearly the attractive dial supplied is not shown.

**TELEVISION TUBE BARGAINS**

**COSSOR** 108K 10-in. New & boxed, 15/-, plus 6/- P. & P.  
75K 10-in. New & boxed, 15/-, plus 6/- P. & P.  
Ion trap magnets to suit the above, 2/9, 3d. P. & P.

SEND FOR OUR  
**NEW VALVE LIST**  
ENCLOSING S.A.E.

VACUUM  
ELECTRONIC  
LIMITED

**KEEPS YOU IN  
THE PICTURE**

WITH THE  
**FINEST REBUILT CATHODE RAY TUBES**  
12 MONTHS  
GUARANTEE

12"-14" £4.15.0	<b>15/-</b>
15"-17" £5.5.0	
21" £7.15.0	

**ALLOWED ON RECEIPT OF OLD TUBE**

CASH WITH ORDER OR PRO FORMA, ADD 12/6 FOR CARRIAGE AND INSURANCE.

**DELIVERY FREE IN LONDON AREA**

WRITE PHONE OR CALL  
**VACUUM ELECTRONIC LTD.**  
35, SACKVILLE STREET  
LONDON, W.1  
REGENT 6404

# REPLACEMENT TUBES

**REBUILT CATHODE RAY TUBES ARE NOW USED BY  
OVER 80% OF RETAIL SERVICE DEPARTMENTS  
AND RENTAL ORGANISATIONS.**

**FOR QUALITY, RELIABILITY AND SERVICE BUY FROM BRITAIN'S  
LEADING GROUP OF INDEPENDENT MANUFACTURERS OF REBUILT  
CATHODE RAY TUBES**

**SUFFOLK TUBES LIMITED**  
1/3 UPPER RICHMOND ROAD  
PUTNEY, S.W.15.  
Tel: Vandyke 4304/5267

**MIDLAND TUBES LIMITED**  
37 GEORGE STREET  
MANCHESTER, 1.  
Tel: Central 4568/9

**VIDIO REPLACEMENTS LIMITED**  
HALES STREET  
DEPTFORD HIGH STREET, S.E.8.  
Tel: Tideway 4506/2177

**ALL TYPES - KEEN PRICES - PROMPT DELIVERY  
WRITE FOR BROCHURE**

**Scotts Radio Ltd.**  
4 Church Street  
Brighton  
Tel: Brighton 26891

**Weston Hart Ltd.**  
236/8 Fratton Road  
Portsmouth  
Tel: Portsmouth 24125

**Lawsons Ltd.**  
36 Cornhill  
Bury St. Edmunds, Suffolk  
Tel: Bury St. Edmunds 3304

**J. H. Sunderland**  
11 Clements Street  
Rochdale, Lancs.  
Tel: Rochdale 48484

**Wizard Productions**  
16 Withy Grove  
Manchester  
Tel: Dea 2772

**J. Charlesworth & Son**  
14 Hightown  
Crewe, Cheshire  
Tel: Crewe 2535

**Taylors**  
162 Eastney Road  
Milton, Portsmouth  
Tel: Portsmouth 35000

**Wanda Electrics**  
9 Manor Road  
Gravesend  
Tel: Gravesend 3766

**Stowmarket Co-operative**  
Bury Street  
Stowmarket, Suffolk  
Tel: Stowmarket 51/52

**Frank H. Hunt & Co.**  
Stepcote Hill  
Exeter, Devon  
Tel: Exeter 56687

**H. Knowles**  
54/56 Chester Road  
Manchester  
Tel: BLa 9031

**Radio Services Ltd.**  
30 Mona Street  
Amlwch, Anglesey  
Tel: Amlwch 594

**Hi-Lite Ltd.**  
89 Southbourne Grove  
Southbourne, Bournemouth  
Tel: Bournemouth 44344

**R. Watson**  
Leathern Bottel  
Wavenden, Woburn Sands, Bucks  
Tel: Woburn Sands 2027

**R.E.S. Ltd.**  
17/19 Paynes Lane  
Coventry  
Tel: Coventry 28781

**Gwalia Radio & T.V.**  
Llanstephan  
Carmarthen  
Tel: Llanstephan 284

**J. Wildbore Ltd.**  
6-12 Peter Street  
Oldham  
Tel: Mai 4475

**Tele-Car Ltd.**  
66 Osborne Street  
Glasgow, C.1  
Tel: Bell 1912/3

# Practical Television

AND TELEVISION TIMES

VOL. 11, No. 132, SEPTEMBER, 1961

Editorial and Advertisement  
Offices:

**PRACTICAL TELEVISION**

George Newnes, Ltd., Tower House  
Southampton Street, W.C.2.

© George Newnes Ltd., 1961

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for trans-  
mission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.2.0 per annum  
Abroad - - - - £1.0.6 per annum  
Canada - - - - 19s. per annum

## Contents

	Page
Editorial ... ..	593
Variable Voltage Stabilised Power Supply ... ..	594
Using a Signal Generator ... ..	597
Telenews ... ..	600
Servicing TV Receivers Recognising Transmitter Defects ... ..	602
A TV Valve Tester ... ..	605
How to Use Oscilloscopes ... ..	609
A Precision Wobblulator ... ..	610
Tracing TV Faults ... ..	612
Underneath the Dipole ... ..	616
ITA Border Stations in Scotland ... ..	619
Letters to the Editor ... ..	623
Your Problems Solved ... ..	624

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender.

Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television", George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

## "Convertible" Receivers

BEFORE the Radio Show, advance information was received from various manufacturers of their new season's models. Amongst this information, we repeatedly found references to receivers which were said to be "convertible". Up to the time of going to press, however, no actual details as to what is meant by the term "convertible" had been received. The inference was that the receivers concerned could be adjusted to receive any transmissions which might be made using new standards decided upon either by the Pilkington Committee or by the authorities. It is, however, very necessary that full details of any conversion facilities be made public, as there are so many possible differences which may be introduced by a change of standards. If a change were made to a completely different system, the video detector polarity might have to be reversed (a simple matter in many instances), AGC modifications might be necessary and the sound receiver might have to receive F.M. signals or inter-carrier sound. As it is not yet decided which system will be used in the future, and experiments and tests are still being carried out, we do not see how any manufacturer can have produced a receiver which may be "converted" when any changes are made in the standards of transmission; certainly "conversion" will not be made possible solely by altering the frequency of the line timebase.

## ANOTHER FREE BLUEPRINT

NEXT month we shall be giving away with each issue another large blueprint (size 22in. x 16in.), but unlike previous blueprints in this magazine, it will not consist of a design for a television receiver. In the past we have published details of several complete television receivers but, unfortunately, in nearly every case, the suppliers of essential components have been unable, after a short period of time, to continue the supply. There are, however, a number of pieces of apparatus (apart from receivers) which are of great value to the television enthusiast and it is felt that by issuing a blueprint for a comprehensive multimeter of high sensitivity, we shall be filling a long-felt want in the ranks of the home-constructor whose main hobby is television. The serviceman also, if he is enthusiastic about his trade and likes to make his own equipment, may find that home-built apparatus possesses advantages over the commercial article and will prefer to make such items for himself.

The design is such that much internal wiring is eliminated by the use of a printed circuit. Two rotary switches are connected directly to this circuit board to give about double the number of ranges usually found on a home-constructed meter. The movement used is robust and extremely sensitive—the basic f.s.d. is 50 $\mu$ A. The scale employed is well spaced, clear, and, to facilitate accurate readings, extends over an effective length of 4 $\frac{1}{2}$ in.

All readers will find this precision instrument of value and the keen experimenter and constructor especially will be able to build this comprehensive multimeter at a considerable saving.

Our next issue, dated October, 1961, will be published on September 22nd.

# Variable Voltage Stabilised Power Supply

By R. Brown

MAKING A SIMPLE UNIT FOR WORKSHOP EXPERIMENTAL PURPOSES

HIGH tension and filament supplies are two of the basic requirements for any experimenter or serviceman, yet the provision of these supplies is often given scant attention when setting up a laboratory or workshop, and for ever after, one is forced to delve into the spares box for the odd mains transformer, chokes and capacitors when these supplies are required. Inevitably the output of such a temporary arrangement turns out to be other than the one required. The H.T. voltage has to be obtained with dropping resistors, to bring it to the correct value for the circuit being tried out. The regulation of such a supply, even without the

dropping resistors, is very poor, so that quite frequently one can change a component in the circuit, with the object of improving its performance, only to find that the change has, as a side effect, altered the H.T. current and this in turn has caused the H.T. voltage to change: an effect which frequently masks the desired result or gives a completely erroneous impression of the results of the component change.

It was after a series of such time-wasting, and incorrect interpretation of results, and one final fiasco when a whole series of laboriously plotted results had to be thrown away, that the author decided that something had to be done.

What is required is an H.T. supply which can be varied over a certain range and set to give an accurately known voltage. Once set the voltage must remain constant, irrespective of mains variation, and, perhaps most important of all, it must

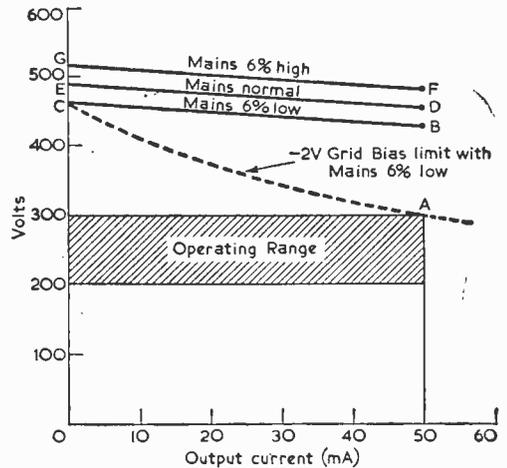


Fig. 2.—The operating range of the valve stabilised power supply.

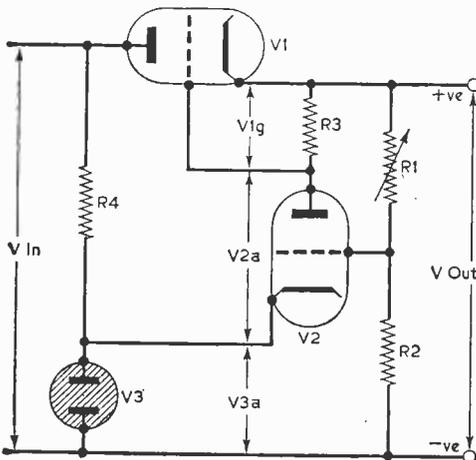


Fig. 1.—The basic circuit of a variable voltage stabilised power supply.

remain constant when the load current is varied. In other words, what is required, is a supply which can be set once, and then forgotten.

### Choice of Circuit and Performance

Voltage stabiliser circuits seem to have been analysed in great detail and a very great many different circuits have been produced. This causes considerable difficulty to anyone looking for a circuit to use—a difficulty which was further increased in this case, for the unit had to be a general-purpose one, and there was no fixed specification to work to. It was decided that the unit should be relatively cheap to make; should meet the needs of most experiments; should use components which are either in a spares box or are easily obtainable on the surplus market, and it should be possible to increase the output at some later date should this be found desirable.

### The Series Valve Stabiliser

The useful range of output voltage and current was felt to be, 200V—300V, 5mA—50mA. A circuit suitable for stabilising and setting the voltage

of such an output is the series valve stabiliser. This is shown in Fig. 1 in basic form. Two valves are used, one connected in series with the H.T. + line, and one connected across the H.T. line. A neon stabiliser, V3, is also included. The action of this circuit can perhaps be best understood by seeing first of all how it maintains a constant output voltage when the input voltage is varied. Suppose, for instance, the input voltage  $V_{in}$  increases. This will initially cause the voltage  $V_{out}$  to increase; the voltage drop across R2 will also increase, so that the grid voltage of V2 moves in a positive direction. The cathode of V2 is, however, connected to the anode of the neon stabiliser and this will tend to keep the cathode voltage of V2 constant whatever the variation in  $V_{in}$ . The result of the increase of  $V_{in}$  will, therefore, be to cause the grid voltage of V2 to go positive. This will cause the anode current of V2 to increase, and the voltage drop across the anode load resistor R3 will increase; the voltage across R3 provides the grid bias for V1, and the V1 grid will thus go negative. This increased negative voltage, on the grid of V1, will cause the voltage drop across V1 (anode to cathode) to increase, and this will reduce the value of  $V_{out}$ . Thus the initial increase in  $V_{in}$  has resulted in a larger voltage drop across V1 which will almost completely cancel it out, leaving  $V_{out}$  almost the same as before.

A similar state of affairs occurs when  $V_{in}$  falls. This time the bias on V2 goes negative, decreasing its anode current, and reducing the bias on V1. This will cause the voltage drop across V1 to decrease and the value of  $V_{out}$  will remain constant.

When the load current taken from the unit varies, it will also cause  $V_{in}$  to vary, and these variations will be compensated for as described, and  $V_{out}$  will remain constant.

**Pre-setting the Output Voltage**

When it is desired to vary the value of the output voltage, and set it to a desired level, the potentiometer R1 is used.

If it is desired to reduce the output voltage, the value of R1 is decreased. This will cause the grid of V2 to go positive, increasing the anode current and, therefore, increasing the negative bias on V1. Thus the voltage drop across V1 will increase, and the output voltage will be reduced to the required value. In this way the output voltage can be varied over quite wide limits.

**V1 Operating Range**

The action of the stabiliser can be examined in greater detail with the aid of the load diagram (Fig. 2).

This is drawn in the following manner: the maximum-current/maximum-voltage point (A; 50mA/300V) is first plotted. At this point the current through V1 is a maximum and the voltage drop across it must be a minimum. This means that the grid bias on V1 must have its minimum value. The actual value of this minimum grid bias must be such as to ensure that under no circumstances does grid current flow. A value of -2V gives a wide safety margin and this value was chosen.

The next step is to look at the  $I_a/V_a$  characteristics of the valve chosen for the V1 position. This


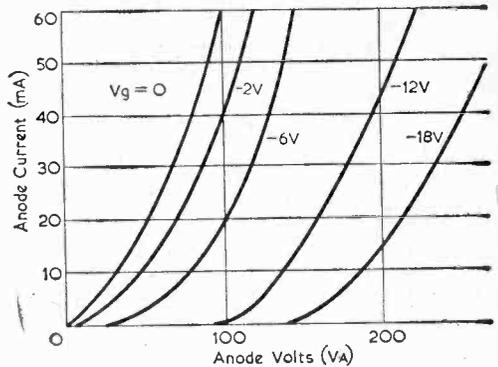


Fig. 3 (above).—The  $I_a/V_a$  characteristics of the EL37 triode-connected.

Fig. 4 (below).—This circuit gives a higher and more uniform gain from V2.

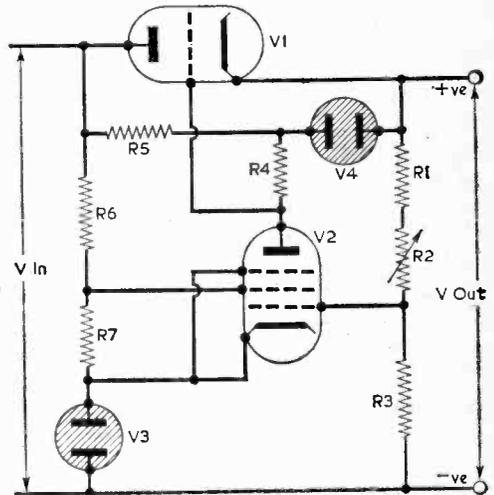

is an EL37 tetrode with its anode and screen connected together as a triode. Fig. 3 shows the characteristics of this valve, and from these characteristics it can be seen that with the grid voltage at -2V and the anode current at 50mA, the anode voltage is about 115V. The transformer/rectifier unit must therefore provide a voltage equal to the voltage drop across V1 of 115V, plus the output voltage of 300V, when 50mA is being delivered to the load, and when the mains voltage is at its minimum. This fixes point (B) at 415V (Fig. 2).

The line BC can now be drawn and this shows the output voltage from the transformer/rectifier unit at different load currents. This is for the condition where the mains are 6per cent low, and the line DE can now be drawn in the position corresponding to the normal mains voltage. A further line parallel to this and 6per cent higher can now be drawn to show the conditions when the mains are 6per cent high.



# USING A SIGNAL GENERATOR

By F. Burton

## INJECTING SIGNALS INTO TV RECEIVERS

**T**HE work of servicing and adjusting television receivers can be considerably simplified if an accurately controlled signal is available—a signal which can be set to the required frequency and its strength adjusted to a convenient level. For simple work, such as correcting straightforward faults or for roughly aligning I.F. strips, the transmitted television or sound carrier can be used. The limitations imposed by such a signal are, however, very great. A much more versatile test signal is really necessary. Such a signal can be produced with a signal generator. These instruments do, however, come in all shapes and sizes and before venturing to build or to purchase a signal generator, it is best to have a very clear idea of just what the requirements are.

purposes and so here is the first requirement—an audio frequency output. The actual output voltage will depend upon the test point and an output of only a few millivolts will probably be all that is necessary at the input of the first audio amplifier, but anything up to 20V may be necessary when testing the loudspeaker transformer.

### I.F. Amplifier

The next stage in the receiver is the intermediate frequency amplifier. Here a radio frequency signal at the I.F. is required. An output voltage from the signal generator varying from say  $50\mu\text{V}$  to  $10\text{mV}$  will probably be sufficient. As we are using a loudspeaker to show the presence of a signal, the signal generator output must be modulated at an audio frequency. The  $1000\text{c/s}$  tone, already mentioned, is usually used for this

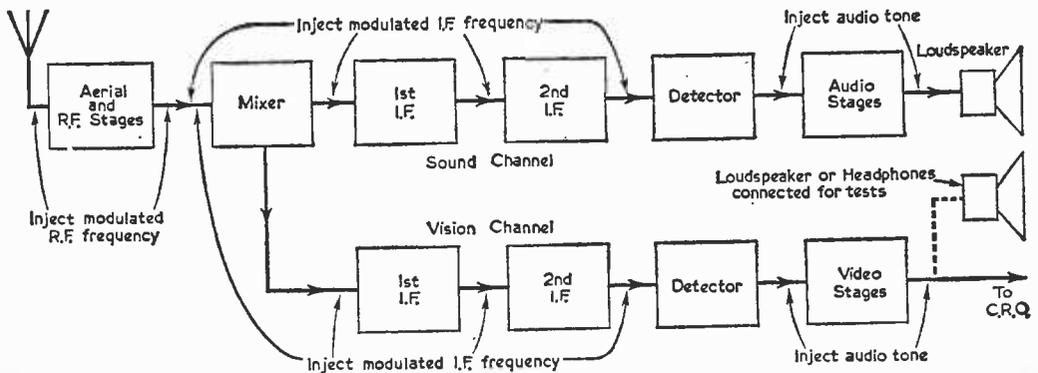


Fig. 1.—Using a signal generator to test for breaks in the sound and vision channels.

### Basic Requirements

As a fault finding instrument, the signal generator can be used to find the position of a break in the signal path. To do this some form of output monitoring is connected to the output of the receiver and the signal generator is set to give a suitable signal which can be injected into the receiver, at different points back towards the aerial. The position of the break is found between the point at which the signal last gets through and the first point at which it fails to get through.

Obviously the signal generator should be capable of producing any signal necessary for fault finding. The block diagram of a television receiver (Fig. 1) begins with the sound channel. Testing this can be done with the loudspeaker as the monitor. The loudspeaker and the audio stages require an audio frequency signal, say  $1000\text{c/s}$  tone, for testing

purpose. To check for a break between the aerial and the first I.F. stage a radio frequency signal, at the frequency of the sound carrier must be used. This should have a level of around  $10\mu\text{V}$  to  $10\text{mV}$ .

### Video Stages

When investigating the vision section of a receiver a video frequency signal is required to test continuity in the video stages. A  $1000\text{c/s}$  tone is good enough

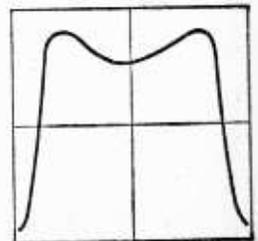


Fig. 2 (right).—A typical response curve of the sound I.F. stages.

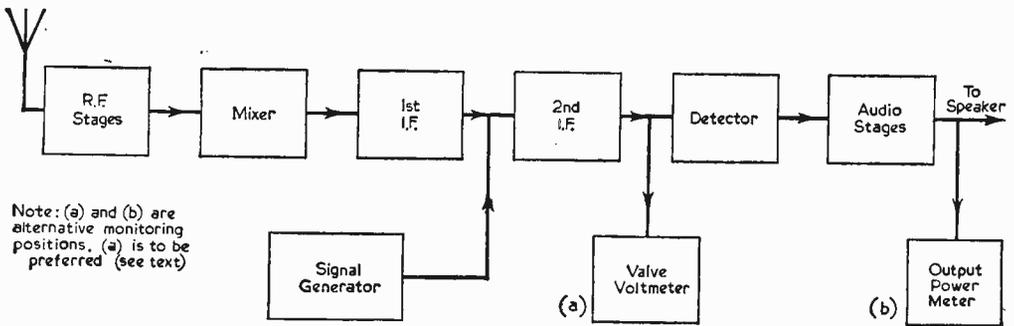


Fig. 3.—How the signal generator is used to align the I.F. amplifier.

for checking for actual breaks. A modulated radio frequency signal at the intermediate frequency is needed for testing the I.F. stages and the detector, and a radio frequency signal at the vision carrier frequency for testing the stages between the aerial and the first I.F. stage.

So for fault finding, a fairly simple instrument giving a radio signal covering the intermediate frequency and Band I and Band III television frequencies, which can be modulated with an audio frequency tone; the output of which can be varied (very roughly) in steps from approximately  $10\mu\text{V}$  to  $10\text{mV}$ , and which can give an audio frequency output of from a few millivolts to several volts, preferably as much as  $20\text{V}$ , is required.

#### Bandwidth Measurements

The next most important application of the signal generator is the alignment of the intermediate frequency sound and vision strips. These strips must be adjusted to have a response curve which will pass signals at the required frequency

set to the middle of the pass band, and then at various frequencies above and below the middle of the pass band. Results are then plotted and if the curve which results differs from the desired one, the I.F. can trimmers must be adjusted and the readings repeated until a correct response curve is obtained. The signal generator output is then transferred to the next but last valve in the I.F. strip and the whole process repeated, and so on until all the I.F. cans are correctly adjusted.

There is one disadvantage with this arrangement, and is one which is frequently overlooked. This arises from the fact that it is impossible to produce amplitude modulation without also producing a certain amount of frequency modulation. This causes trouble when the signal generator frequency is on or near the skirts of the response curve. Because of this frequency modulation, the signal generator frequency will vary throughout the audio frequency modulating cycle and for part of the time will be way down on the skirt, or possibly right outside the response of the amplifier. The result is that the output meter will indicate a lower level than the true one and the response will appear to have fallen off much quicker than it actually has.

Signal generators can be designed so that this effect is negligible, but it is a very expensive process and an instrument on the market which has been designed in this way costs over £300! The way to avoid this disadvantage is to use a technique which does not require the signal generator to be modulated. One method is to connect a valve voltmeter across the input to the detector where it will indicate the level of the un-

modulated carrier (Fig. 3).

The second disadvantage, which is never overlooked, is the great amount of time required to complete an operation. If the signal generator is provided with an external frequency modulation facility, a sweep technique can be used. The response curve can then be displayed on an oscilloscope and the whole process is completed very quickly. A suitable arrangement is shown in Fig. 4. The timebase of the oscilloscope is used to sweep the frequency of the signal generator

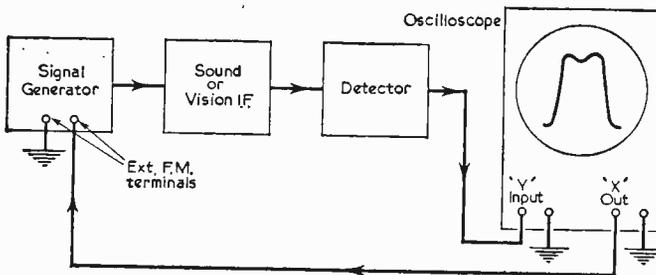


Fig. 4.—Using an oscilloscope with a signal generator to display the I.F. response curve.

at the minimum of distortion, while preventing the passage of unwanted signals. The typical response curve of the sound channel is shown in Fig. 2.

One way of adjusting this, is to connect an output meter across the loudspeaker and connect the signal generator to the grid of the last I.F. valve. The trimmers in the I.F. can, in the anode circuit of this valve, are then adjusted to their middle position. The signal generator is modulated and the output voltage is recorded with its frequency first

across the pass band of the I.F. strip and the output from the detector is connected to the "Y" plates of the oscilloscope.

For bandwidth measurements then, the signal generator should, in addition to the facilities already mentioned, have facilities for external frequency modulation and if possible, although this may be expensive, produce negligible frequency modulation when amplitude modulated.

### Sensitivity Measurements

The sensitivity of the whole receiver or of individual parts of it, such as the video amplifier, I.F. amplifier or radio frequency stages, are usually quoted in terms of the minimum signal generator output, modulated 30 per cent, required to produce an audio frequency output of 50mW. An audio frequency power meter is required for this test and it should be connected in place of the loudspeaker. The signal generator is then connected to the aerial socket of the receiver, the amplitude modulation switched on and the modulation depth, if this is variable, set to 30 per cent. The attenuator of the signal generator should then be used to reduce the level of the generator output until the power output meter reads 50mW (some manufacturers quote different figures than this, but the basic method of measurement is the same).

To carry out measurements on the sensitivity of the other stages, the signal generator output should be injected into the input of the stage and its frequency set to the appropriate value. These results are then compared with the manufacturers' figures.

Many of these figures are not given by the manufacturers, but it is worth while making a note of the figures for a good receiver so that when one is in doubt as to whether another receiver is really performing well or not, some definite yardstick to judge its performance is available. It would certainly help to save those arguments on whether or not a receiver or a stage in the receiver is functioning correctly.

### Connecting the Signal Generator

When making fault finding checks and when aligning the I.F. strip, it is not usually important how the signal generator is connected; only ensure that there is sufficient signal reaching the point

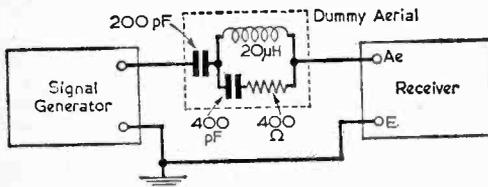


Fig. 5.—Connecting the signal generator to a broadcast band receiver via a dummy aerial.

where it is needed. Screened leads should always be used, however, so that the signal is not picked up by later stages in the receiver, where it might well give false results.

When making sensitivity measurements however, the signal generator should appear to the receiver as if it were the same as the normal aerial. For television receivers, of course, the aerial looks like a  $80\Omega$  impedance and most signal generators

designed for these frequencies have output impedances of this value. All that is necessary when setting up the signal generator is that it is connected via a length of  $80\Omega$  coaxial cable. This does not, however, apply to short waves and broadcast band receivers and some form of dummy aerial may be necessary between the signal generator and the receiver. Generally speaking one should, with a signal generator having a source impedance of around  $70\Omega$ , connect it directly to a receiver designed to operate above about 30Mc/s and via a  $300\Omega$  series resistance to receivers designed to work between 2Mc/s and 30Mc/s. In the medium and long wave broadcast bands, a dummy aerial consisting of resistances, capacitors and inductors should be constructed. This should have an impedance roughly equal to the impedance of a typical aerial used at these frequencies. A suitable dummy aerial is shown in Fig. 5.

### The Complete Signal Generator

Having decided what can be done with a signal generator, the specification of the instrument may be examined a little more closely. Fig. 6 shows a block diagram of a typical instrument. First there is the oscillator. This must be a variable frequency type and must cover all the radio frequencies to be used. Although its tuning dial will be calibrated in frequency, it is quite impossible accurately to calibrate a wide range variable frequency oscillator, but the frequency accuracy, which may be anything between 1 and 5 per cent should be more than sufficient for servicing television receivers.

The H.T. supplies to the oscillator should be regulated, otherwise it will have a small amount of amplitude and frequency modulation which will result in noise and possibly false measurements.

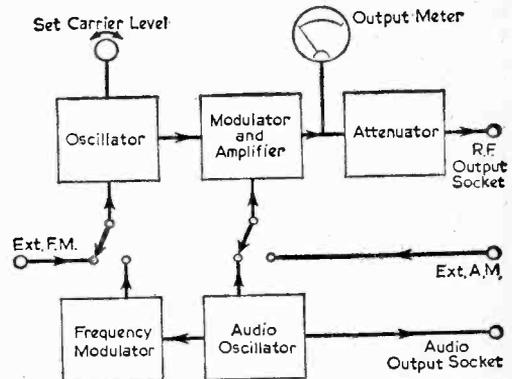


Fig. 6.—The main sections of a complete signal generator.

### A.F. Generator

The audio frequency generator can be of many forms. The simplest is a single frequency, say 1,000c/s, oscillator with a fixed output. This is useful but a variable frequency output can be used to check the audio frequency response of video and audio stages, and a variable output is almost essential, for without it severe overloading may occur when checking the first audio stages.

(Continued on page 618)

# Telenews

## Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of June, 1961, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal .. .. .	1,940,774
Home Counties .. .. .	1,597,496
Midland .. .. .	1,716,331
North Eastern .. .. .	1,840,171
North Western .. .. .	1,494,850
South Western .. .. .	971,965
Wales and Border Counties .. .. .	690,158
<b>Total England and Wales .. .. .</b>	<b>10,241,715</b>
Scotland .. .. .	1,031,534
Northern Ireland .. .. .	187,635
<b>Grand Total .. .. .</b>	<b>11,440,884</b>

## British TV Equipment for Brazil

RADIO GAUCHA of Brazil have recently concluded a contract with Pye T.V.T. Ltd. for the supply of the equipment of a complete television station. The completion of the station is planned for the beginning of next year at Porto Alegre.

The station is to include the necessary equipment for a three-studio television centre, with cameras, mixing systems and all ancillary apparatus. A 5kW Band III transmitter will also be supplied and additional equipment has been purchased to fit out an outside broadcast unit.

## Underwater TV Inspection in the Suez Canal

THE canal dredgers which operate in the Suez Canal and in the entrances to Port Said and Suez Harbours suffer much damage to their cutting teeth, by submerged debris, which causes time-wasting and costly delays while they are being repaired. The canal authority therefore are to use a Marconi-Siebe, Gorman underwater TV camera to examine the condition of the canal beneath the water, in an

attempt to eliminate much of the damage and to provide more accurate control of the dredging operation.

When any submerged parts of a vessel need to be inspected, the underwater TV equipment can be used to examine the damaged area and an engineer viewing on a monitor screen can supervise the repair work.

## Television for Lighthouse Keepers

TRINITY HOUSE has decided to equip isolated lighthouses and lightships with Ekcovision television receivers. In the past a number of Trinity House establishments have been provided with television — principally through the efforts of local charitable organisations.


Now, however, all crews within range of a transmitter will, eventually, be able to watch television programmes.

## Trade Tests in the Border Area

TRADE test transmissions from the Independent Television Authority's Caldbeck station, near Carlisle, began on Monday, 3rd July. The transmissions are broadcast from 10 a.m. to 5.30 p.m. daily except on Sundays. (See page 623.)
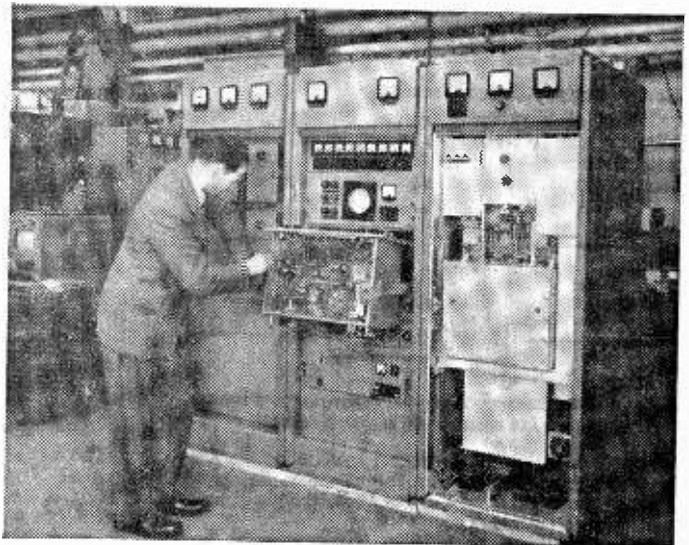
## New TV Stations for Morecambe Bay

A NEW television station is to be built at Stewnor Park, six miles to the north of Barrow, to provide the Morecambe Bay area with BBC television programmes.



This is one of the vision transmitters which will be supplied by Marconi Wireless Telegraph Co. Ltd., to the Compagnie de Television du Liban et du Proche-Orient, a Lebanese commercial television organisation.

This will give improved reception of the BBC over the whole of the area, which includes Barrow-in-Furness, Lancaster, Morecambe, Carnforth, Grange, Dalton-in-Furness and Ulverston.

The Morecambe Bay Station will transmit programmes received by radio link from a receiving station which will be built at Walthwaite, about one mile to the South-East, where the programmes will be picked up from the BBC's television station at Holme Moss.

It is expected that the new station will be ready for service during the summer of next year. The transmissions will be on Channel 3 (vision 56.75Mc/s, sound 53.25Mc/s) with horizontal polarisation, which means that receiving aerials will need to be mounted horizontally.

#### TV at Southend Airport

**I**N order to survey a busy intersection at Southend Airport which is not visible from the control tower, the airport authorities have installed a Marconi closed circuit television camera channel.

Mounted on a hangar gantry, the camera overlooks a main aircraft holding area and an important road and runway intersection.

Vehicles using the road between a nearby industrial site and the airport, as well as airport vehicles and aircraft taxiing on the runway, can now be supervised from the control tower, where a 14in. monitor has been installed.

#### Closed-Circuit TV at "Northern Star" Launching

**O**N June 27th, at a Newcastle-on-Tyne shipyard, H.M. Queen Elizabeth the Queen Mother launched the new liner, "Northern Star."

At the subsequent lunch, the Queen Mother and other speakers were seen by overflow audiences, in adjoining rooms, over an EMI closed-circuit television system which televised the speeches.

#### New Design of TV Station

**A** COMPLETE television broadcasting system of an entirely new design was demonstrated recently by Pye T.V.T. Ltd. With studio, control room,



Australian harbour officials and shipping representatives recently saw a demonstration of Marconi-Siebe, Gorman underwater TV equipment. The authorities think the cameras might be used for the Australian cray-fishing industry.

telecine, transmitters, mast, aerial and all other equipment, the new system costs only £17,000.

The "Cambridge Station," as it is called, is a simple, economic TV station which, although low in price, has all the technical facilities necessary.

The studio contains two cameras, four microphones and lighting system. In the control room is a console with all monitoring and mixing facilities, two 16mm telecine units with slide projectors, two transcription/gramophone units, a monitor loudspeaker, two equipment cubicles and the vision and sound transmitters. An appropriate aerial system is mounted on a 100ft high mast erected immediately beside, or on top of, the station building.

#### TV Camera for Italy

**T**HIRTEEN complete television camera channels have been ordered from EMI Electronics Ltd., by Radiotelevisione Italiana for use in their studios in Milan and Turin.

This order is for complete 4½in. Image Orthicon camera channels type 203 and follows the earlier sale to the Radiotelevisione Italiana of four similar channels which were used in the coverage of the Rome Olympic Games last year.


#### Television Station on Norwegian Island

**T**HE Norwegian Telegraph Administration is building a television station on the island of Bokn in Stavanger Fjord and is to operate it by remote control from the mainland by means of a VHF radio link.

The transmitters selected for this purpose—two 4kW vision and two 1kW sound—are of Marconi manufacture and are suitable for unattended operation. In addition to the transmitters, Marconi's are to supply and install programme input and ancillary equipment.

The equipment will operate in Band III to 625 line CCIR standards. The two vision transmitters are to be connected for parallel working, as will the F.M. television sound equipments. Remote control facilities over the VHF link will include the independent on/off switching of all four transmitters; the control of blanking level, and the control of video and audio gain. An indication of power output at normal, high and low levels will also be provided over the link. It is intended that adjustments to the controls will be made in conjunction with a waveform display derived from a high-grade receiver and oscilloscope sited at the remote control position on the mainland.

# Servicing Television Receivers

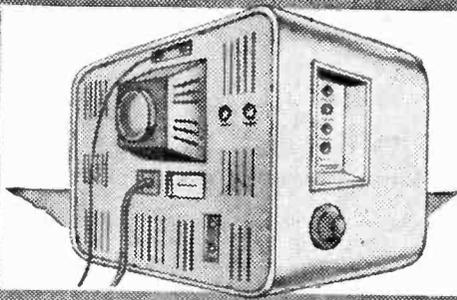

## No. 71—THE INVICTA 338

By L. Lawry-Johns

**T**HIS is a 17in. table model with a 110° tube and a single printed circuit panel. It is identical to a little known Pye model called the CIOV and has circuit features in common with several Pye and Pam models.

The cabinet and chassis layout has much to commend it since all but three of the valves are immediately accessible with no difficulty once the rear cover is removed. The three exceptions are the tuner unit valves, PCC84 and PCF80, and the EHT

rectifier EY86. The tuner unit does present a little difficulty since the valves are sunk down and only the tops of them protrude. Loops of tape may be found however which, passing under each valve, render removal easier. Since the chassis is secured in the generous cabinet by four easily removed screws, dismantling may be carried out in a matter of moments. The front knobs require their centre grub screws slackened (volume and channel selector), the brilliance and fine tuner knobs pull

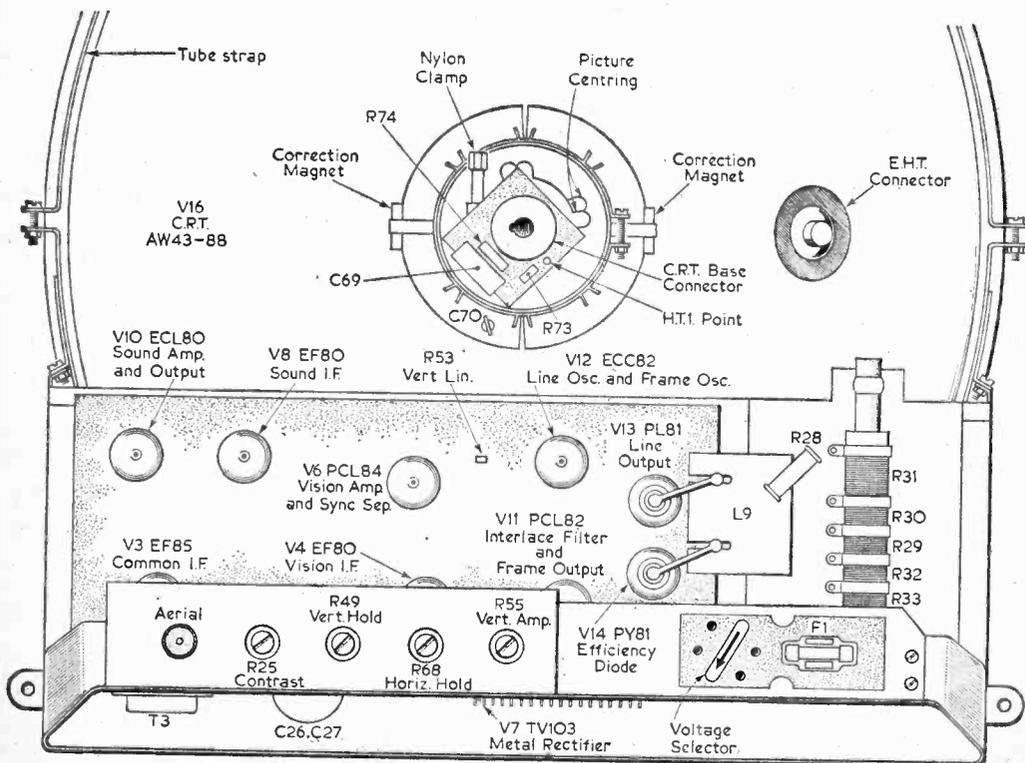


Fig. 1.—A rear view of the receiver showing the positions of some of the larger components.


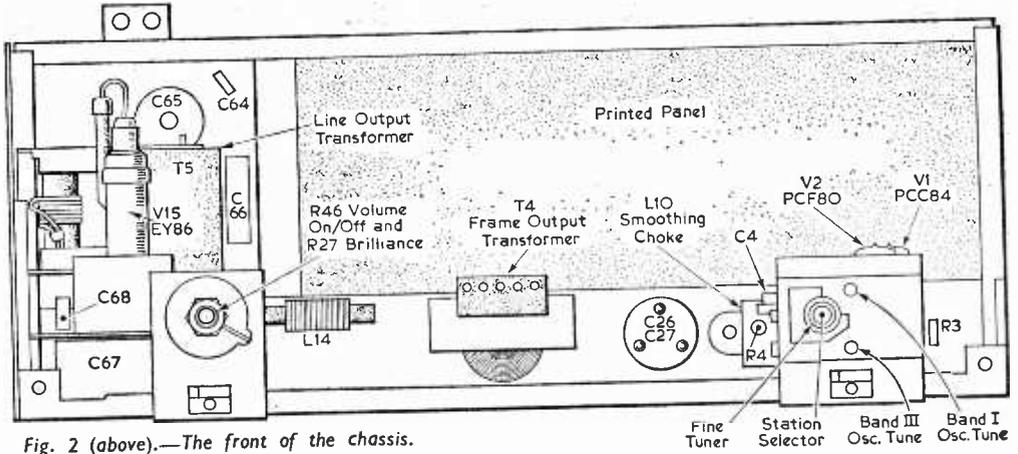


Fig. 2 (above).—The front of the chassis.

Fig. 3 (below).—The frame timebase circuit—note the bias arrangements for the pentode section of V11; R56 and R57.

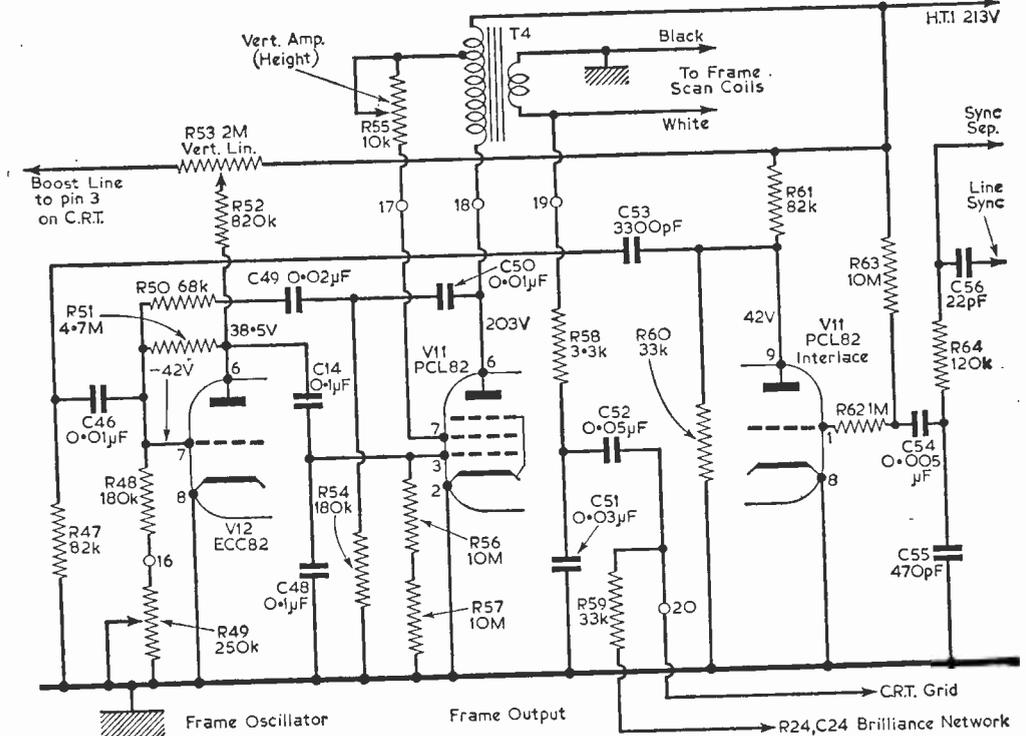

off in the usual way. The loudspeaker leads clip on to the rear left side output transformer (T3).

**A Tuner Fault**

With the chassis removed, the tuner is more easily handled and although it may appear compact and intricate it may be stripped and reassembled in

a very short time. This is rarely necessary, but the writer had occasion to remove the rotor for examination in connection with a rather interesting fault which at first sight appeared a trifle puzzling. The owner of the set complained that although BBC remained constant and good on channel 1, the ITV reception on channel 9 would fail after about ten

minutes or so. This in itself is not so unusual but he also reported that at all times he could still receive channel 9 on the channel 10 position with the fine tuner hard over and with poor sound as is usual with continuously tuned units, the point being that this reception did not vary at all, although the reception on switch position 9 failed completely. This information, which was confirmed by trial, indicated that the valves must be in order and the tuning could not be drifting. It meant that there

was apparently a poor contact between the coil studs and the contact springs in the channel 9 position only. Examination with the cover removed proved the contacts to be faultless. Until one is familiar with the type of tuner and realises that there is only a small loop of thick wire making the difference between channels 8 and 10 it cannot be appreciated just how awkward the symptoms were. However the rotor assembly was removed and upon very

close examination, traces of white powder were observed in the soldered connection of the channel 9 stud. It was a matter of moments to clean and re-solder the connection, reassemble the tuner and have the set working on test to prove that channel 9 stayed put for longer than the specified ten minutes. A simple fault, only a "dry joint", but instructive all the same.

**Unusual Features**

The circuit of the main deck is fairly conventional but the method of biasing the frame output valve V11A should be noted. There are no cathode components and the control grid is biased by the high value of R56 and R57 (total 20M). The mean bias is about (-11.5)V.

*(To be continued)*

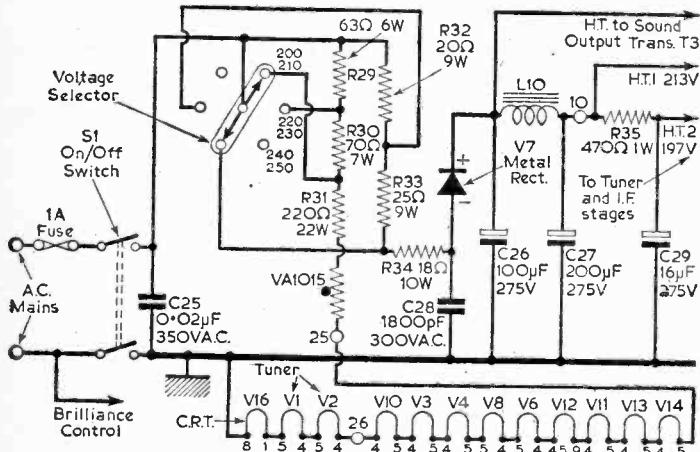


Fig. 4 (above).—The mains supply and H.T. circuit.


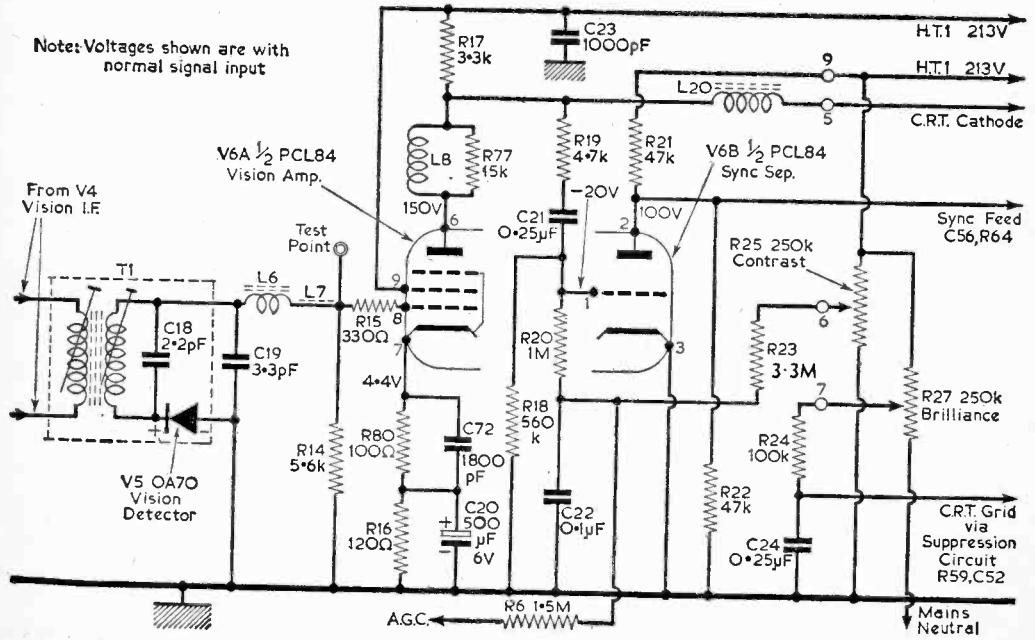


Fig. 5.—The video strip.

## SOME APPARENT FAULTS ORIGINATE OUTSIDE THE RECEIVER

By L. E. Higgs

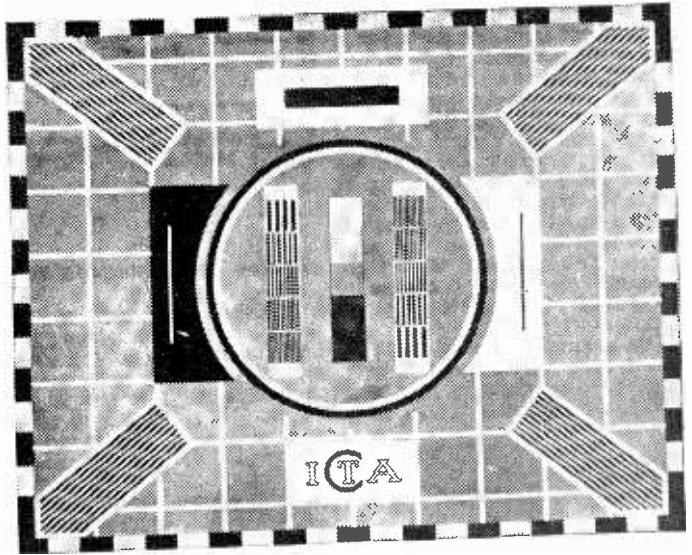

# Recognising Transmitter Defects

**A**FTER spending a whole evening trying to clear a mysterious flickering picture on my television receiver similar to that produced by intermittent valve base contacts, I was dumbfounded by an apology by the announcer for the interference which was due to damage to the transmitter aerial by gale force winds. It was then that the importance of recognising defects originating from the transmitter, was finally brought home to me. Because most transmitter troubles can simulate receiver defects, and because of the high standard of reliability of our TV transmitters, it is easy to jump to the conclusion that the fault must be in the receiver, and a lot of mis-adjustment can take place before the truth emerges.

The first and easiest test, where transmission is suspect, is to switch over to another channel and

see if the trouble exists there also. If reception is normal then the transmitter may be broadcasting the faulty condition or it may be caused by interference pick-up on that particular frequency. Even after this check it is always best to sit back and wait for a possible announcement rather than disturb a receiver that may be functioning perfectly. Even a simple action such as centering the picture on the Test Card could well be left until it is certain that the picture is not constantly off-set (as it is not unknown for the test cards on each channel to each be displaced with respect to each other).

### Studio Defects

These may be conveniently described as effects originating at the camera, possibly due to errors in handling or to adverse conditions—the transmitter being in normal working order.

Studio plays often display a picture with a flare of white at the bottom of the raster. This can be seen to come and go as the cameras are changed or as they shift about the studio. A badly placed studio light is often the culprit.

Out of focus subjects are quite frequently seen but the viewer must not expect to see all of the scene—near, centre, and distant in focus at the same time, as some customers complaints have suggested they should.

The aspect ratio of TV is 4:3 and cinemascope and other widescreen film types have the wrong shape to fit this mask. Consequently the broadcasters are compelled to reduce the transmitted height to accommodate all the film frame. The black gaps that result at top and bottom of the raster still

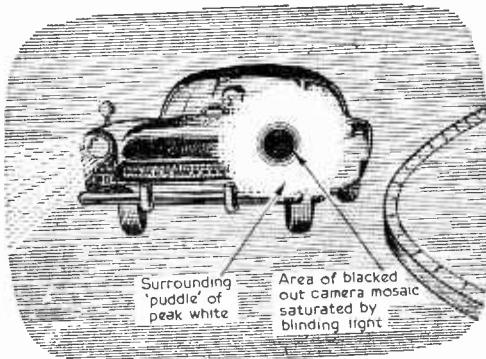


Fig. 1.—The effect of bright, direct light on the TV camera.

cause concern, and service calls are frequent from persons unaware that it is intentional.

Microphone shadows on a singer's face can be puzzling, as can the occasional light which shines directly into the camera (Fig. 1). This saturates the sensitive mosaic retina in the camera, up to and past peak white, leaving a charged-up black blot on the raster surrounded by a "pool" of peak white. This saturated area takes a second or two to discharge if the control room staff do not switch in the next camera quickly.

Low contrast and wandering black level from one camera only, can be compared with the results from another and the changing grey background tolerated, leaving the brilliance control strictly alone.


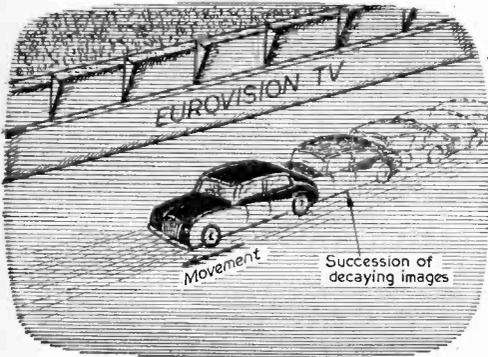


Fig. 3.—The effect of long-persistence phosphors in the standards translation.

Fig. 4.—When the vertical (frame) sync is not locked to the local mains, hum in the timebases of the receiver causes curves in vertical lines.

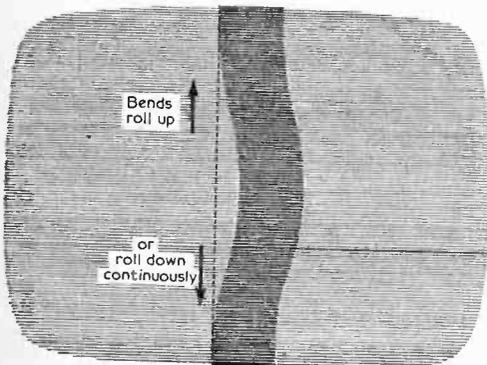

#### Outside Broadcasts

Horse racing and outside broadcasts in bad weather transmit some pictures of indifferent quality. Every

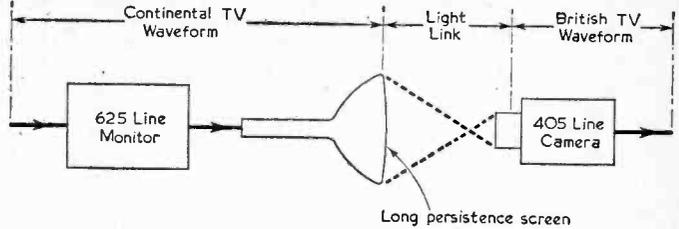


Fig. 2.—The basic method of translating Continental TV to British standards.

bit of gain is used to obtain maximum sensitivity for those long-distance telephoto shots through the rain, and the white noise of electron movement and thermal agitation shows on the screen as a background of crawling drizzle. When the camera is changed the picture background usually clears. Unfortunately this "grain" looks exactly the same as that produced by frequency changer noise in the front end of the receiving TV—the effect of fringe reception on a TV with automatic gain control working on a poor aerial. To avoid jumping to conclusions wait until the announcer appears in the studio for the advertisements and use them for comparison.

#### Transmission Faults

Through a desire to maintain service as continuously as possible, it sometimes happens that a channel is compelled to radiate at reduced power. Local viewers notice no difference in such a case, intermediate distance viewers notice an increase in grain or decrease in contrast; but the fringe viewer loses sync with a rolling maze of lines.

The importance of taking note of breakdowns and transmission defects by persons who are called on to service TV is obvious here to save wasted time and money.

#### Trans-Atlantic Telerecordings

Probably the worst set of images which appear on television from time to time, are trans-Atlantic telerecordings. Smudgy, low definition pictures, sometimes accompanied by flickering ribbons of horizontal light from variations in tape speed across the head, are frequent. Far from doubting the efficiency of the receiver, most people start rubbing their eyes, but it is to be hoped that these transmissions will improve with time.

#### Standards Translation

Eurovision reception is remarkably good considering, not only the distance but the standards translation link from 625 to 405 lines (Fig. 2). This requires a display of the picture on a cathode ray screen with a long-persistence phosphor, from which it is re-televised on another standard.

The long persistence of screen light decay also fails to reproduce quick changes of movement of subjects being televised. Thus a man quickly raising his arm for a brief moment appears to have a succession of jerky arm movements; or a car travelling is followed by a series of fading smudges due to the slow die-away of light (Fig. 3). These pictures can be identified as "translated" from this effect.

**REBUILT REPLACEMENTS**



**12**

Months' Guarantee

21in. ...	99/6	} H.P. TERMS
17in. ...	90/-	
15, 14, 12in. ...	70/-	

Ins. carr., 15/6.  
£1 extra without old bowl, refundable if same received within 14 days.

**14in. Tubes 35/-**  
**36/24** Due to purchase of rental replacement stock. **14KP4**

**EXTENSION SPEAKERS 19/9d.**

8in. P.M. Speakers Fitted into polished cabinets. Complete. P. & P. 3/6.



**DUKE & CO. (LONDON) LTD.**

621/3 Romford Road, Manor Park, E.12.  
ILF 6001/3 SEND FOR FREE CATALOGUE

**COMPLETE 17in. TV £11.10.0**



An excellent ex-Rental Table model. Famous manufacture. Tuned 1TA/EBC. Guaranteed 12 months. Terms available. Personal collection advised. Special delivery rate by arrangement up to 50 miles or (despatched in 3 parcels for easy assembly. 25/-

**TAPE RECORDER AMPLIFIER £7.19.6**



Compact, well designed 5 valve amplifier. Output 2.5 watts. Input for Microphone, Radio and Gram. Size 8 1/2 x 3 x 4 1/2 in.

Ins. Carr 4/6. 12 months' guarantee. Terms available.

EXTRAS—Dial plate incl. sockets and super-impose switch. 3/6. Knobs 2/6.

**VALVES**

**SALVAGE GUARANTEED**

9d. Each. 4B1, 6AL5, 6D1, 6D2, 6SH7, 9D2, 10F3, 12Y4, 15D2, 78, 210VPT, 2050, 2151, 7193, C2C, CV66, D1, D132, EA50, EB91, EF50, HL41DD, HL42DD, LP210, P61, PM202, SP41, SP61, TDD13C, V135, VR31, VR106, VR107, VR109, VR137, VR201, VR301, Z86.  
1/9d. Each. 17/6 Doz. 6AM6, 6AT6 6F1, 6F12, 6F13, 6F14, 6F15, 6K7, 6P25, 6P28, 7C5, 7Y4, 8D3, 12837, 128K7, D77, DH77, EB41, EF91, N142, PEN45, PEN46, W148, Z77.  
2/9d. Each. 30/- Doz. 6C10, 6U4GT, 10D1, 10F1, 10P13, 10P14, 12AT7, 12AU7, 20D1, 20F3, 6L19, 6SN7, 25A6, B36, ECC31, ECC34, ECC35, ECC31, ECH42, EP80, EP92, EL32, EY51, KT36, KTW61, L63, N87, N18, EL38, TH41, TH233, U22, U31, U85, U151, U281, U282, UAF42, UB41, ECH42, EF41, UF42, UY41.  
5/9d. Each. 80/- Doz. 9AB5, 6F6, 6K4, 6Q7, 6V6, 12K7, 12K8, 12Q7, 7AN7, 1625, 6BW8, 15A6, 12AX7, 30P5, 21A6, 20P2, 20L1, 20P1, 30C1, 20F5, 30L1, 30L2, 30P11, 30P13, ECL40, ECC33, EPF90, FCC84, PCF80, PL38, PL81, PL82, PL83, PY80, N309, U142, U801.

Postage: 1—7d. 6—1/6d. 12—2/6d.

**Transistors**

6 and 1 Diode 47/6 per set.

Mullard 1-OC81D 6/9, 1-OC44 9/8, 2-OC81 6/9, 2-OC45 8/9, Diode 1/9. G.E.C. 114 6/9, 2-874 9/9, 873 8/9.

Ediswan XCL12 and XB113 at 8/9. Post free.

**Speakers**

Miniatures 16/9. New, 2 1/2 and 3 inch. P. & P. 1/-.

Ellipticals 15/9. New, slot type. 5 x 3 and 7 x 4 inch. P. & P. 2/9.

Sale 8/9. 5, 6, 8 and 7 x 4 inch. Ex-manufacturers salvage. Money back guaranteed.

P. & P. 2/9.

# Become a Television expert this easy way

*The Bennett College offers you a complete course*

You have to be really in the know to keep up with television these days. And the value of this special new course prepared by The Bennett College is that you are taught *all* the latest methods and techniques. You have the advantage of studying this profitable and fascinating medium in the quiet of your own home. And personal tuition by The Bennett College makes all the difference.

The Bennett College offers you a course that's non-mathematical and particularly easy to follow. It contains clear diagrams which cover everything you want to know from beginning to end (and

even includes the basic principles of sound radio if you wish).

The complete home-study course covers *everything*: Production of the signal, scanning and reproduction of picture from signals. Aerials, types and purpose. The cathode-ray tube. Time-base oscillators, and output circuits. Synchronisation. Video frequency amplifiers. The TV tuner, turret incremental, etc. Television test gear. Television faults.

For more details, please fill in the coupon below. Your studies cost very little and the book you need is included in the cost.

**To THE BENNETT COLLEGE**  
(Dept. I 55NTV,) Sheffield

*Please send me details of the new TELEVISION SERVICING COURSE*

NAME.....

ADDRESS.....

..... AGE.....

# RADIO BARGAINS


## SIGNAL GENERATOR

£8.19/6 or 25/- deposit and 6 monthly payments of 2/16. P. & P. 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 x 6 1/2 x 5 1/2 in. Grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F., output continuously variable. 800 milli-volts. O.W. and mod. switch indicator. Accuracy plus or minus 2%.



variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 2/16. Plus Postage and Packing 5/-. Coverage 120 Kc/s-84 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30% modulated or unmodulated R.F., output continuously variable. 100 milli-volts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

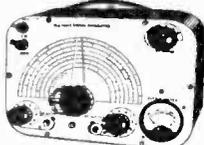

## ALIGNMENT ANALYSER


TYPE MC12

A.C. mains 200/250 v. Provides: 1. V.O. dial for "Swept Frequency" Operation. For FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s-80 Mc/s. Capacitance Measurement. Two ranges provided 0-60pF and 0-12pF. Special Facility enables true resonant frequency of any tuned out. I.F. transformer, etc., to be rapidly determined. Cash price £19.16. plus 5/- P. & P. H.P. terms 25/- deposit, plus 5/- P. & P. and six monthly payments of 2/16.


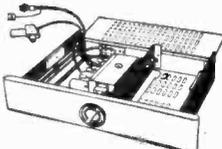
## CHANNEL TUNER

Will tune to all Band 1 and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series). I.F. 16-18 or 33-38. Also can be modified as an aerial converter (instructions supplied). Complete with knobs.



32/6 Plus 3/6 P. & P.

## HEATER TRANSFORMER


To suit the above, 200-250 v., 6/-, plus 1/8 f. & p.

## LINE E.H.T. TRANSFORMERS

With built-in line and width control, 14kV. Scan coil, 90° deflection on ferrite yokes. Frame O.P. transformer pin. 16 kv smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.

29/6 Plus 4/- P. & P.

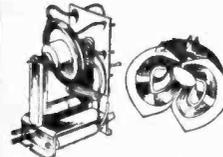As above, but for 825 lines, £2.10.0, plus 4/- P. & P.



Focus Magnet suitable for the above (state tube). 10/- plus 2/6 P. & P.

## A.C./D.C. POCKET MULTIMETER KIT

2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamperes 0-100. Ohms range 0-1000. Front panel, range switch, wirewound pot. (for ohms zero setting), toggle switch, resistor and rectifier, 19/6. P. & P. 1/6. Wiring diagram 1/1, free with kit.



## RADIO & T.V. COMPONENTS (Acton) LTD.

23c HIGH STREET, ACTON, LONDON, W.3  
All enquiries S.A.E. Goods Not Despatched Outside U.K.

# TUBES

HIGHEST QUALITY—NEW LOW PRICES  
Carr. & Ins. 12/6 **GUARANTEED**

	6 Months	12 Months	18 Months	NEW TYPES
9/10in.	£1-10-0	£3- 0-0	£4-0-0	MW 31/74
12in.	£1-15-0	£3-10-0	£4-4-0	MW 36/44
14in.	£2- 0-0	£4- 0-0	£5-0-0	MW 36/24
15/17in.	£2-15-0	£4-15-0	£5-0-0	CRM 172
21in.	£3-15-0	£5-15-0	£6-0-0	MW 43/64

New Mullard, Mazda + U.S.A. tubes used.

## 13 CHANNEL TVS

Table Models. Complete with Valves and Tube. They are untested, not guaranteed to be in working order. 12in. £2.19.0, (P.P. 12/6). 14in. £4.19.0, (P.P. 15/-).

## 5 CHANNEL TVS

12in. 39/-, 14in. 59/-, (P.P. 12/6).

## 5 CHANNEL CHASSIS

12in. 15/-, 14in. 35/-, (P.P. 4/-). Speaker, L.O.T. Cabinet.

**LOUDSPEAKERS.** Manufacturer (resb, 2 1/2in. 18/8; 3in. 19/-; 10in. 23/6; 6 x 4in. 18/6; 8 x 5in. 19/6; 8 x 6in. 21/-; 7 x 4in. 18/-; 5in. 16/-; 8 x 13in. 35/-, (P. & P. 1/6).

100 RESISTORS. 1-2 watt., 6/6. 100 CONDENSERS. 3-5,600 pF., 10/- SILICON DIODES, 125 v. 300 M.A. 2 in case like superior replacement for RM4, RM5, etc., 8/- each. We are always pleased to answer your enquiries, S.A.E.

# VALVES

BY RETURN OF POST


GUARANTEED 3 MONTHS

NEW LOW PRICES

10% DISCOUNT SPECIAL OFFER OF ANY SIX VALVES marked in black type (15% in dozens). Post: 1 valve 6d.; 2-11, 1/- FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-military origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

02A	5/-	6K25	7/6	30P1	9/6	EB33	4/6	11R2	7/6	U78	5/6	
1A7GT	1/3	6L1	12/6	20P3	12/6	EB41	8/6	KT33C	6/6	U78	5/6	
1C5GT	9/6	6L6	9/6	30P4	17/6	EB41	7/6	KT36	9/6	U82	7/6	
1J8GT	9/6	6L6G	7/3	30P5	15/6	EB41	8/6	KT44	7/6	U107	11/-	
1L4	3/6	6L7G	6/-	25A6G	8/6	EB41	3/6	KT44	7/6	U111	8/6	
1N5GT	9/6	6L8	8/6	25L6G	6/6	EB12L	12/6	KT1	8/6	U119	6/6	
1S5	5/6	6L12	12/6	26L6GT	9/6	EB31	19/-	KT63	6/3	U142	6/6	
1S4	4/6	6L12D	8/6	30P6	9/6	EB31	8/6	KT66	12/6	U148	9/6	
185	4/6	6P25	8/6	30P5	9/6	EB31	8/6	KT66	12/6	U148	9/6	
174	3/6	6P28	12/6	30FL1	9/6	EB32	4/6	KT66	12/6	U148	9/6	
2A3	7/6	6P7G	8/3	30P4	9/6	EB32	4/6	KT66	12/6	U148	9/6	
2D21	4/6	6P7GT	8/3	30P12	8/6	EB34	8/6	KT66	12/6	U148	9/6	
3A4	4/6	6P6A7	5/6	30FL1	10/6	EB35	8/6	MU14	8/6	U151	8/6	
304	7/6	6S67	4/6	38L6GT	9/6	EB38	5/6	N78	7/3	U152	7/6	
384	6/6	6H7	4/6	35V4	5/6	EB38	5/6	N78	7/3	U152	7/6	
3V4	6/6	6S37	4/6	3524GT	6/3	EB38	5/6	N78	7/3	U152	7/6	
3Z4G	9/6	6S67	5/3	30CD6G	9/6	EB34	8/6	N108	18/-	U191	11/-	
5D4	4/6	6S17GT	6/6	30L6GT	8/6	EB38	5/6	P41	4/6	U281	6/6	
5V4G	8/6	6S47	6/-	61B1	18/-	EB38	5/6	PCC84	7/6	U282	15/-	
5X3G	6/6	6S87	4/6	61B1PT	11/-	EB38	5/6	PCC88	8/3	U309	6/6	
5Y3GT	9/6	6U4GT	10/6	185B1	18/-	EB38	5/6	PCC88	13/6	U329	7/6	
6Z4	6/6	6V6G	8/6	807(A)	5/6	EB38	5/6	PCC88	13/6	U329	7/6	
6Z4G	6/6	6V6GT	8/6	807(E)	5/6	EB38	5/6	PCC88	13/6	U329	7/6	
7Z4GT	11/-	4V6G	5/6	955	3/6	EB38	5/6	PCC88	13/6	U329	7/6	
8A6	8/-	4X4	5/-	956	2/6	EB38	5/6	PCC88	13/6	U329	7/6	
8A6G	6/6	6X5G	5/-	9001	4/-	EB38	5/6	PCC88	13/6	U329	7/6	
8A6GT	4/3	6X5GT	5/6	9003	4/-	EB38	5/6	PCC88	13/6	U329	7/6	
8A6S	3/6	7B6	7/6	ATP4	2/6	EB38	5/6	PCC88	13/6	U329	7/6	
8AG7	7/6	7B7	7/6	AZ31	3/6	EB38	5/6	PCC88	13/6	U329	7/6	
8AK5	6/6	7C5	7/3	B38	8/6	EB38	5/6	PCC88	13/6	U329	7/6	
8AL5	3/6	7C6	7/3	B65	4/6	EB38	5/6	PCC88	13/6	U329	7/6	
8AM5	3/-	7A7	7/6	CB31	21/-	EB31	3/6	PCC88	13/6	U329	7/6	
8AQ5	6/6	7A7	7/6	CB31	21/-	EB31	3/6	PCC88	13/6	U329	7/6	
8AT6	6/-	7X4	7/6	CB35	14/-	EB32	4/6	PCC88	13/6	U329	7/6	
8AU6	7/6	10C1	11/-	CL33	11/6	EB32	4/6	PCC88	13/6	U329	7/6	
8BG	8/6	10C2	13/6	CV31	9/6	EB32	4/6	PCC88	13/6	U329	7/6	
8BR6	6/-	10F1	14/6	DA90	2/6	EB32	4/6	PCC88	13/6	U329	7/6	
8BE6	5/6	10LD11	14/6	DA90	2/6	EB32	4/6	PCC88	13/6	U329	7/6	
8BG6G	12/6	10LP13	9/-	DAU32	9/6	EB32	4/6	PCC88	13/6	U329	7/6	
8BW6	7/6	10P14	9/-	DAU31	9/6	EB32	4/6	PCC88	13/6	U329	7/6	
8BW7	5/6	12A4H7	6/6	DAF96	7/3	EB31	6/6	PY81	6/6	U86	14/6	
8C4	3/6	12A4H8	6/6	DF33	9/6	EB32	4/6	PY82	6/6	U89	7/6	
8C6	4/6	12A4H9	7/6	DF91	3/6	EB34	7/6	PY83	7/6	U91	8/6	
8C9	8/6	12A7	5/6	DF96	7/6	EB34	7/6	PY83	7/6	U91	8/6	
8CD6G	21/-	12A7	5/6	DH77	6/6	EM54	8/6	R19	11/6	U84	9/6	
8CH6	8/6	12A7	5/6	DH81	9/6	EM80	8/6	R19	11/6	U84	9/6	
8D6	4/6	12A5GT	6/6	DK32	11/3	EM81	8/6	T41	7/6	U80	6/6	
8P1	4/6	12K8GT	5/6	DK32	11/3	EM81	8/6	T41	7/6	U80	6/6	
8F6G	6/3	12K8GT	5/6	DK92	3/6	EM84	9/6	TDD4	7/6	U8	12/6	
8F12	3/-	11/-	DK96	7/6	EN31	18/-	U22	2/6	UY11	11/6		
8F13	8/6	12Q7GT	5/-	DL33	3/6	EY81	18/-	U22	2/6	UY11	11/6	
8F15	9/6	12SK7	4/6	DL36	9/6	Small	8/6	U24	15/6	UY85	6/6	
8H6	2/-	9/6	12SK7GT	4/6	DL31	8/6	EY81	18/-	U22	2/6	UY11	11/6
8J5G	2/6	12B87GT	DL93	4/6	EY26	7/6	U31	11/6	UY11	11/6		
8J5GT	3/6	8/6	DL94	6/6	EY80	6/6	U33	14/6	X63	9/6		
8T7	5/-	13D3	7/6	DL36	7/3	EY81	18/-	U33	14/6	X63	9/6	
8T7GT	7/6	14S7	22/6	EA30	9/6	GZ30	11/6	U37	28/6	X68	11/6	
8K6GT	6/6	19B6G	6/6	EA30	9/6	GZ30	11/6	U37	28/6	X68	11/6	
8K7G	2/3	15/-	EA42	8/6	HAC80	9/6	U37	28/6	X68	11/6		
8K7GT	4/6	20D1	8/6	EB34	1/6	HAC90	7/6	U70	5/6	X79	16/6	
8K8G	5/6	20P2	8/6	EB41	7/6	HLA1DD	U71	8/6	Y63	6/3		
8K8GT	8/6	20L1	18/-	EB91	3/6	8/6	U74	8/6	Z68	9/6		

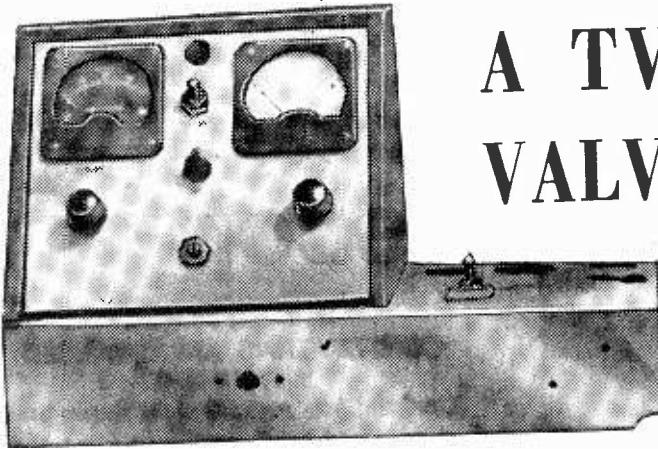The most Competitive Comprehensive Valve List in the Country  
**TECHNICAL TRADING CO.**  
350/352 FRATTON ROAD, PORTSMOUTH



# A TV VALVE TESTER

A USEFUL CIRCUIT WITHOUT COMPLICATED SWITCHING

By D. V. Curtis

**T**HIS TV valve tester was built up mainly of surplus components and enables a large range of common valves to be tested for mutual conductance and behaviour under various working conditions. Nothing new is claimed for the circuit, indeed it is extremely simple (Fig. 1) with no multiplicity of switching, but almost any normal voltage or bias can be fed to the valve and voltage and anode current readings observed simultaneously.

### Voltage Supplies

The H.T. is supplied from a 350-0-350V transformer connected to a full-wave rectifier with conventional smoothing. The screen grid supply is

taken via a 50k wire-wound potentiometer. The anode supply is taken from a 20k wire-wound variable resistance and the variable bias resistance is 500Ω; also wire-wound.

These voltages are connected via a 2-pole 3-way switch to the 0-400, 0-40 voltmeter. The second half of this switch is used to switch in the necessary series resistor to cover the two ranges.

The two meters are both of the small ex-government type, the best of these two was utilised as the voltmeter, and this one had a sensitivity of 500Ω/V; not ideal for the purpose, but sensitive enough to give satisfactory results. The anode supply is metered by a milliammeter with a switch giving either 0-80mA or 0-20mA. The anode, screen and

*(Continued on page 631)*


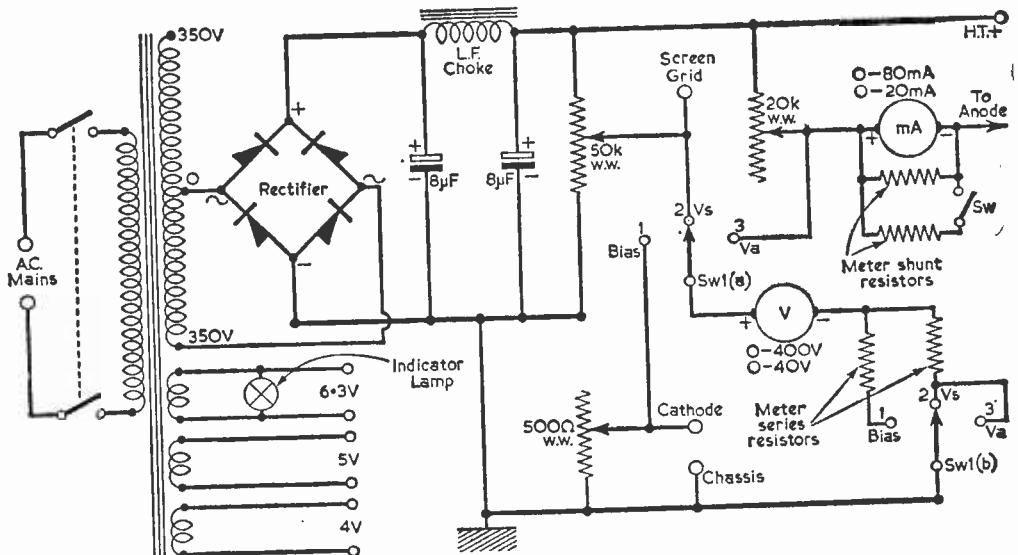


Fig. 1.—The basic circuit of the tester.

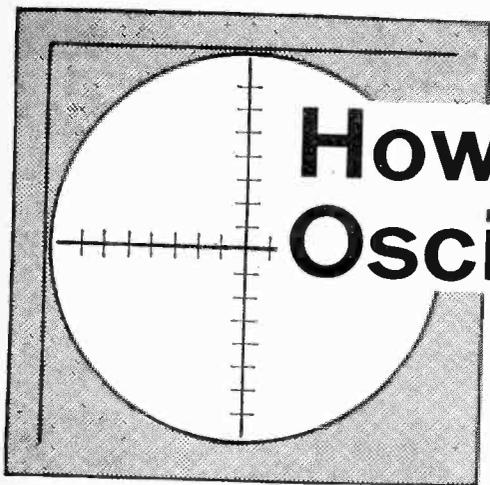

# How to use Oscilloscopes

By D. R. Bowman

## CONSTRUCTING AN ADVANCED INSTRUMENT

(Continued from page 552 of the August issue)

**T**HE construction of two Y-amplifiers is described in this article; the circuit of the first was given in Fig. 13 on page 552 last month. The gain is very great and the bandwidth reasonable, and these combined with sufficient voltage output to give full deflection in the Y-direction may make it attractive for some purposes. Note that C14/R35 (3.3k) forms a corrective network which enables square waves to be amplified with

negligible 'sag' down of frequencies of less than 10c/s.

The circuit of a Y-amplifier which may be preferable to Fig. 13 last month is given in Fig. 14. The correcting choke consists of 85 turns of 36s.w.g. enamelled copper wire on 0.3in. diameter former, with a dust core. The method of adjustment of the core is as follows.

Apply a signal at 1.1Mc/s at the grid of the 30F27. Temporarily short-circuit the 6.8k resistor in the anode circuit, and place a capacitor of 200pF across the choke. Then adjust the core for resonance as shown by an indicator attached to the output from the cathode-follower. Remove the capacitor from across the choke, and remove the short across the anode resistor.


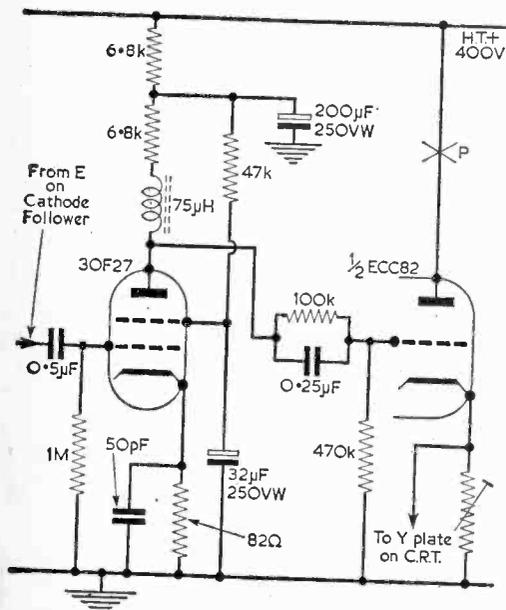


Fig. 14.—The circuit of a Y-amplifier using a frame-grid tetrode and cathode follower. The gain is at least 80 and the output voltage is over 80 with a bandwidth of 6Mc/s.

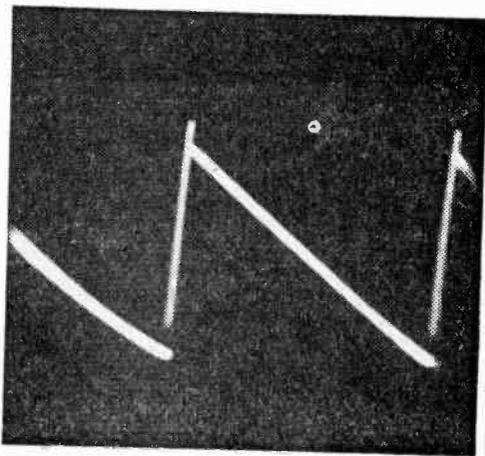

A sweep and flyback wave-form:  $f = 100kc/s$


The adjustment of the cathode follower resistor, which is a pre-set component, is carried out by breaking the anode lead at point P (see Fig. 14) and inserting a milliammeter (on its 0-20mA range). Adjust until the reading is 10mA. Re-connect the anode circuit.

This amplifier is quite suitable for most purposes, and has a good bandwidth. The video signal of a TV receiver, picked up at the detector,

gives a trace about 1/2 in. in height, which is often enough. There may be a little 'overshoot' on fast pulses, and, if this is more than about 2 per cent, the inductance of the correcting choke can be reduced a little by slightly withdrawing the core. A small grid-stopper of 50 to 100Ω may be needed to avoid parasitic oscillations. It should be noted that the heater voltage of 30F27 valve is only 3.7V, so that a 9Ω resistor must be placed in series with the 6.3V supply. This may be fashioned from a few inches of resistance-wire, or a 1W 10Ω carbon resistor may be used.

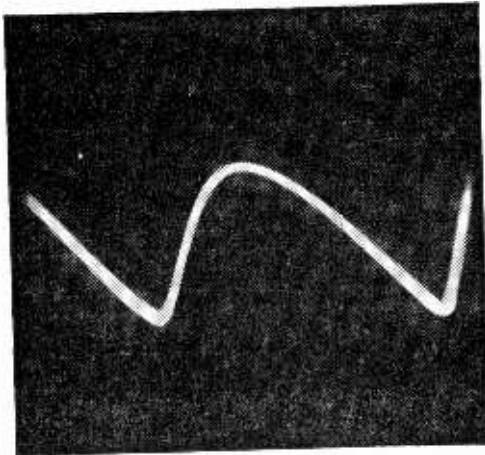**Y-shift**


The other Y-plate is connected to a potentiometer slider across the H.T. supply. Fig. 15 gives suggested values of components. With this arrangement of Y-shift and Y-amplifier, the extremes of the trace in the Y direction will be not as well focused as the middle part of the trace. This effect is only serious with traces of large



With  $f=420\text{kc/s}$ , there is still a linear part to the sweep stroke.

amplitude, and the arrangement shown proves satisfactory in practice. If required, a balanced amplifier (push-pull) can incorporate Y-shift; the circuit would be similar to that of the X-amplifier, but using pentodes instead of triodes.

**Power Supplies**

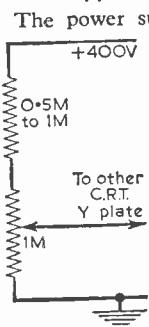

The power supplies described in the article by H. Peters on the simple oscilloscope (June issue) will be found satisfactory if the H.T. is capable of delivering about 70mA. However, it may be found desirable to use two old 350V mains transformers instead of one; then the main H.T. supply can be of full-wave rectification, and the use of a

Fig. 15 (left).—The Y-shift control circuit.

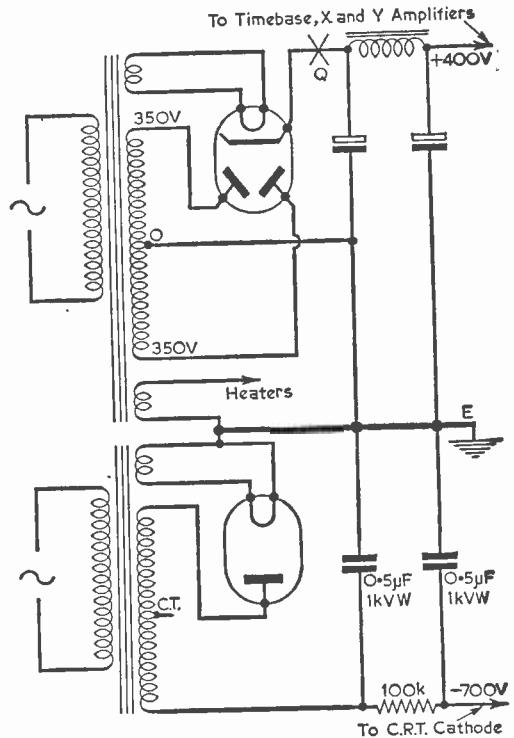


Fig. 16.—The circuit of the power supplies for the oscilloscope.

valve rectifier such as the EY51 can be an advantage. The second mains transformer will have a spare L.T. winding which can be used as in Fig. 16.

*Separate H.T. and L.T. switches should be provided, which can conveniently be a Yaxley wafer.* The first contact is 'off', the second switches on the mains; but the H.T. supply is broken at the point Q (Fig. 16) until the third contact is made. This arrangement allows the valves to warm up before H.T. is supplied, and this then gives a negligible 'surge' and the smoothing and decoupling capacitors are protected. This is necessary because, for economy, 250VW capacitors are specified in general as being much cheaper than 500VW components.

If care is taken in layout, the stray magnetic fields of two mains transformers can be made partially to cancel each other out. However, in the writer's instrument, these transformers are housed in a separate box, and connections are made by a cable form to the oscilloscope. In this way no difficulty exists with stray fields.

**PRACTICAL WIRELESS CIRCUITS**

17th Edition

By F. J. CMM


17/6 by post 18/7

from  
**GEORGE NEWNES, LTD.**  
Tower House, Southampton Street, London W.C.2
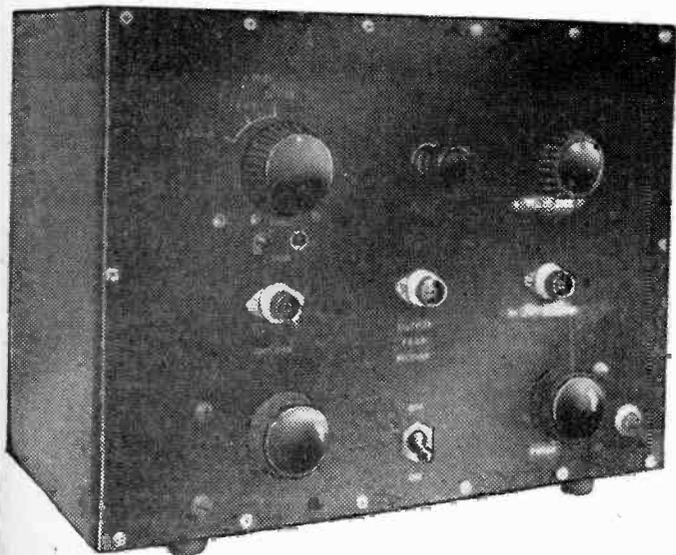
# A Precision Wobbulator

By N. Mears

THIS VERSATILE  
WIDE-RANGE  
INSTRUMENT  
WAS DEVELOPED  
AROUND  
A MODERN  
SEMICONDUCTOR  
JUNCTION DIODE



**T**HE comparatively recent introduction of semi-conductor diodes which vary considerably in capacitance with applied voltage enables some interesting and useful circuitry to be developed. Applications such as remote tuning by D.C. control, automatic frequency control and parametric amplification at VHF are practicable. The writer recently acquired such a diode, and used it to develop a wide-range wobbulator for use with television receivers. The device proved so simple to use that it was thought worthwhile to extend the range of the wobbulator to cover F.M. response curves, and it also proved possible to add the usual broadcast I.F. range of 465kc/s. Thus, a general purpose instrument was designed, and is described here.

## Capacitance Law

A preliminary investigation of the properties of the diode showed that if a linear relationship between oscilloscope trace and displayed frequency was to be achieved, the oscilloscope timebase generator could not be used to provide the voltage sweep needed, especially with TV and broadcast band ranges. It was therefore necessary to provide a separate source of variable voltage, with the correct waveform. This necessitated a waveform generator with special characteristics; and, as some complication was going to be incurred in any case, it was decided to make no effort to simplify the instrument, but to develop it into a more useful device by the provision of markers, sync output to lock the oscilloscope firmly, variable R.F. output, and a pre-amplifier and waveform mixer combined. It now became possible to arrange a logical layout of leads to and from oscilloscope and receiver—in fact, the wobbulator is also used as a distribution centre. This obviates the tangle of leads so frequently found when wobbulators are in use.

## Sections

The instrument thus consists of the following elements—waveform generator, marker generator, R.F. oscillator, with variable reactance circuit, and waveform mixer. Outputs are provided at low impedance by using cathode followers. Fig. 1 shows in a block diagram how these various units are combined into one instrument.

## R.F. Oscillator

It will be convenient first to describe the R.F. oscillator and its associated variable reactance circuit—which includes the variable capacitance diode type SVC1—since the requirements of this stage determine the design of the rest of the apparatus to a large extent. The variable capacitance diode is a semiconductor device in which, when biased in the reverse or non-conducting direction, the capacitance of the "deflection layer", at the interface of p-type and n-type materials, varies with the applied

bias voltage. If this diode is made part of the tuned circuit of an R.F. oscillator, the frequency of oscillation will vary if the applied bias potential across the diode is made to vary. It might be thought at first sight that if part of the X-deflecting voltage of an oscilloscope were applied across the diode a suitable frequency sweep would result. Roughly this is true, but if no precautions are taken certain undesirable features appear. These are enumerated below.

- The frequency sweep is non-linear, being cramped at one end and extended at the other. Thus the oscilloscope trace is misleading, although, if corrections are applied, it can be useful. This effect will be discussed shortly.
- Sufficient sweep may not be obtained to cover the required range.
- The shape of the response curve may be affected by the speed of sweep, especially where selective circuits occur in the receiver under experiment.

The effect first mentioned above depends on the fact that in an LC tuned circuit, frequency of oscillation depends on the square root of the capacitance, the other parameters being constant.

$$f = \frac{1}{2\pi\sqrt{LC}} \text{ or } f = \frac{k}{NC}$$

The linearity or otherwise of the relationship between applied voltage and oscillator frequency depends on the relationship between applied voltage  $V$  and diode capacitance  $C$ . If  $C$  were inversely proportional to  $V^2$  the above equation could be rewritten

$$f = \frac{k}{VC} = \frac{k'}{\sqrt{1/V^2}} = k'V$$

and linearity of frequency sweep would be obtained by applying a linear sawtooth voltage across the diode. The relationship  $C \propto 1/V^2$  is approximately true for point-contact diodes, but is not precise enough for junction diodes. Fig. 2(a) shows the variation of capacitance of the writer's specimen of the SVC1, and it will be seen that there is a major departure from the law  $f=kV$  when, as in Fig. 2(b), frequency is plotted against diode voltage.

Consideration of Fig. 2(b) shows that as the diode voltage drops from a certain value, the frequency drops more rapidly than it should. This effect could be reduced by adding capacitance to the circuit and so swamping the irregularity, but this would minimise the sweep available, by reducing the percentage capacitance change.

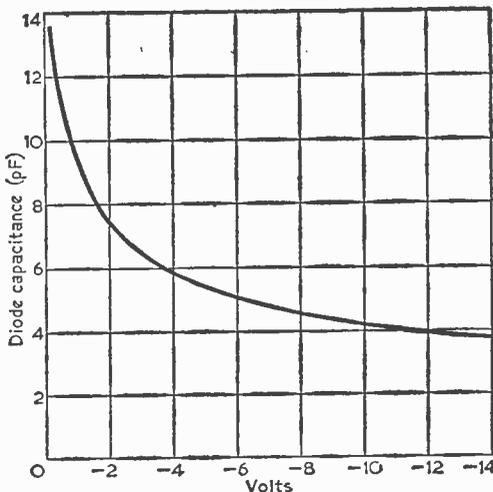


Fig. 2a (above).—The variation of capacitance with applied voltage of the SVC1.

Below! Alignment of wave-form generators.

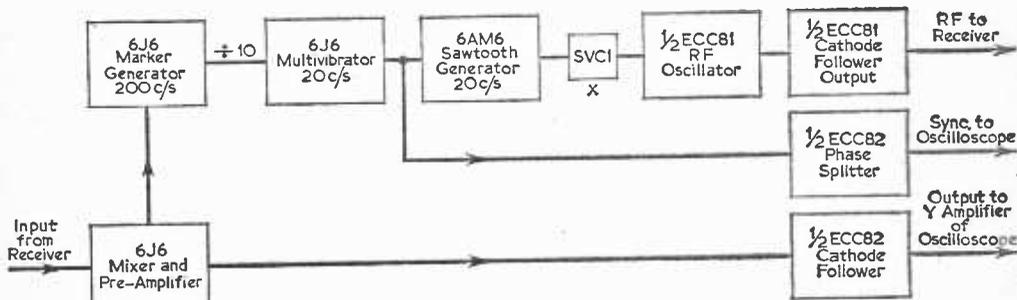
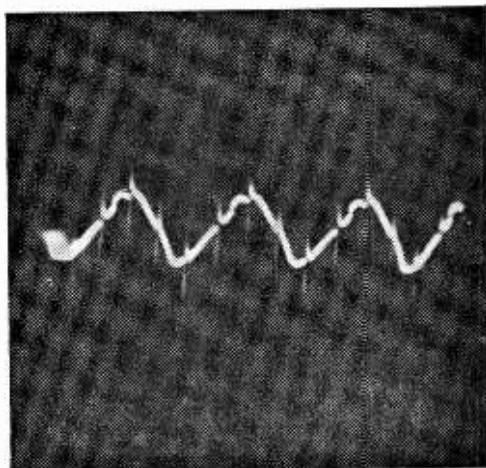


Fig. 1.—The block diagram of the wobulator.

### Exponential Sweep

It will be seen also that if it could be arranged for the voltage to drop less rapidly as it approaches zero, a much more linear frequency sweep could be obtained. A little calculation shows that an exponential drop in voltage gives a great improvement, and the resulting sweep—shown in Fig. 3 by plotting frequency against voltage on logarithmic graph-paper—is practically good enough. A little extra capacitance in the circuit can be afforded, since the sweep is ample, and occurs in any case


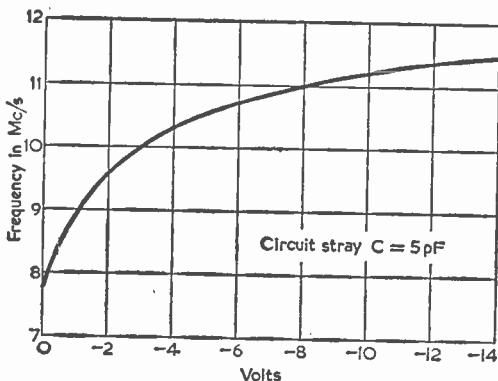


Fig. 2b (above).—Variation of the frequency with applied voltage of the SVC1.

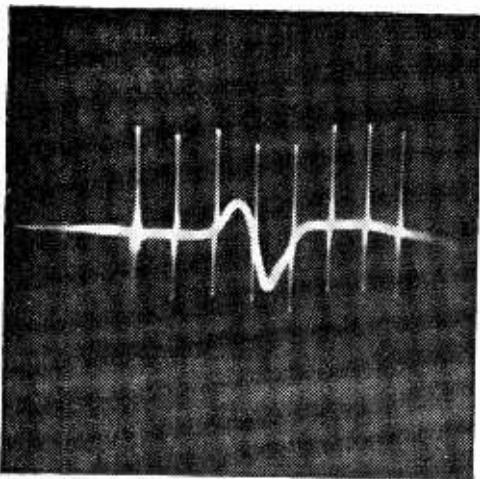Below! Curve from a VHF transistor portable.



because of "strays". This also improves results, and by the correct choice of voltage waveform an essentially linear sweep is achieved. However, only one or two pF can be allowed, and thus the aim must be to cut circuit strays to the minimum.

The choice of sweep generator is thus limited to one having ready exponential waveform output. In addition it should be negative-going; in this way, by combining it with a D.C. potential across the diode, the best sweep of frequency can be obtained. The choice is thus for a screen-coupled phantatron, whose source is a low D.C. potential. The

usual Miller run-down is very linear when the H.T. line, the source of voltage, is at a fairly high potential. At low potentials, however, the run-down is "slightly" exponential in form, and by adjusting the charging potential to the correct value an excellent correcting waveform can be obtained.

### Stray Capacitance

Obtaining sufficient sweep is essentially a problem reducing to that of minimising circuit capacitances. If this is carried out, very little voltage sweep is needed. With the SVC1 the maximum voltage is (-20)V, which allows for a maximum D.C. potential of (-10)V with a peak-to-peak sweep of 20V. It proves sufficient in this design to use a D.C. potential of (-8)V; a sweep of 16V to cover the required wavebands. It is probable, however, that in the 34-38Mc/s band, the usual I.F. for television receivers, the sound channel cannot be covered at the same time as the whole of the vision band. This is normally quite unimportant.

### Sweep Speed

Highly selective circuits cannot deal with fast sweeps, and if the effort is made to use fast sweeps, it is found that the shape of the response curve varies with sweep speed. Ideally, something under 10c/s is preferable, especially where steep-skirted response curves are involved. This however requires A.F. couplings, in the various amplifiers, having time-constants of the order of seconds if distortion is to be avoided. In this design a sweep

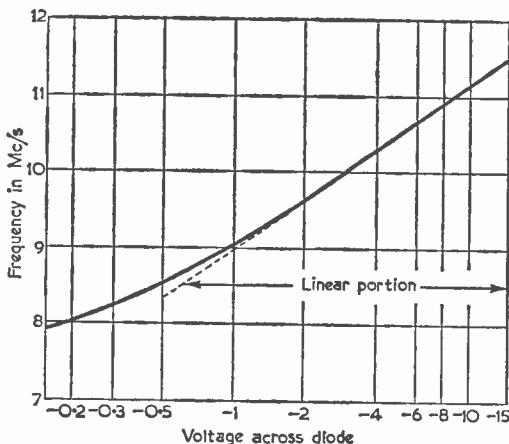


Fig. 3.—The SVC1 in variable circuit—strays = 5pF.

of about 20c/s is arranged; this is a compromise, certainly, but on the whole not a bad one.

Circuit capacitances are normally reduced to the minimum by using as the R.F. oscillator, a Colpitts circuit. The Colpitts circuit is inconvenient however when combined with the reactance diode, and an alternative circuit, the "Cathode Hartley" is here employed. By tapping the cathode into the tuned circuit as near "earth" as possible, the heater-cathode capacitance is reduced in effect. In addition, a relatively small coupling capacitor, connecting the tuned circuit to the valve grid, helps

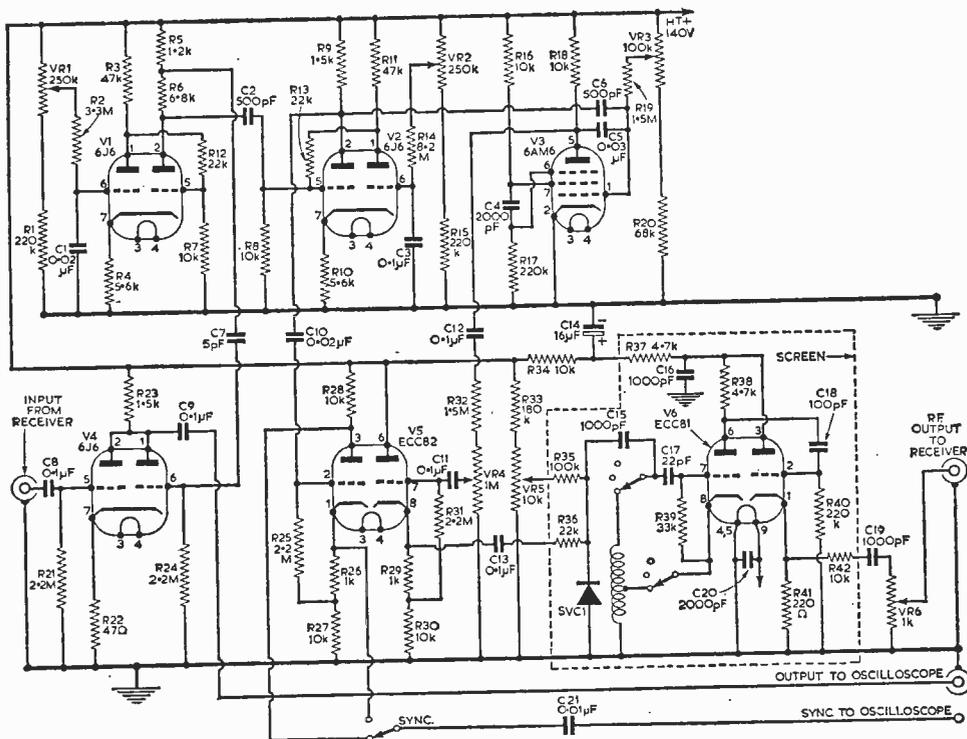


Fig. 4.—The circuit of the wobbulator.

to “stand-off” the tuned circuit from Cag and Cgk.

**Marker Circuit**

Markers for the oscilloscope trace are generated by a Schmitt trigger circuit—arranged to be free-running. With this circuit, sharp and narrow pulses are obtained which, on differentiation, afford positive and negative-going spikes of negligible width. This multivibrator runs at 200c/s, and is used to count-down to another similar multivibrator running at 20c/s. The output from the latter triggers a screen-coupled phantastron which also runs at 20c/s and provides the sweep voltage across the reactance diode. The 20c/s Schmitt valve also provides a sync pulse, brought out to a terminal on the instrument, to enable the oscilloscope to be locked to the same frequency. By interposing a cathode follower in this lead, the effect of external connections is reduced to negligible proportions, and by providing the cathode follower with an anode load resistor, a choice of either positive or negative sync pulses—to suit the oscilloscope—is available by way of a single-pole, two-way switch.

**Mixers**

The waveform from the receiver being tested is mixed with the marker pulses by using two valves (each half of a 6J6) with a common anode load resistor. A small amount of pre-amplification is provided by this stage, as this has been found to be convenient when a wide-band Y-amplifier is

used in the oscilloscope. The displayed trace is thus divided by ten marker pulses, and it must be stressed that these are *equally spaced irrespective of the linearity of frequency sweep*. In use, the space between the markers is calibrated by using an external signal generator. The method will be described later.

The D.C. voltage across the reactance diode is applied by means of a potentiometer across the H.T. supply—an external control is provided. This is not used to set a critical control point—this is unnecessary since the trace is substantially linear with regard to frequency. It is used in practice to shift the trace to the desired point relative to the markers, which are fixed in position. Thus, accurate alignment with a desired marker can be carried out, and this is convenient where actual measurements are to be taken. Neither is the D.C. control used to tune the oscillator; it could be, but it is best to do any trimming on the actual oscillator coils themselves, leaving the D.C. control in a central position.

The extent of sweep is controlled by varying the amplitude of the sawtooth voltage across the SVC1 diode. For checking work only, any convenient sawtooth voltage can be used, but for measurement the maximum setting should always be used.

Fig. 4 shows the complete circuit diagram. This is by no means as complicated as it may seem, and the layout is far from critical. Some explanation of the practical arrangements used will be given next month.

(To be continued)

# TRACING TV FAULTS

By G. J. King

**T**ELEVISION servicing comprises two essential operations: finding out where the trouble lies; and repairing the fault. It is quite a simple matter to replace the faulty part once it has been found, but the biggest problem is in finding out exactly where it is located in the jumble of wires, components and valves making up a television chassis. The wrong thing to do is to remove the back cover and base and start making half-hearted tests on valves, components and circuits before giving considerable thought to the fault symptom and becoming acquainted with the general make-up of the circuit and the location of the key components.

## Logical Procedure

Trouble tracing is really an exercise in logic, but before a logical sequence of testing can be carried out several factors have to be known. One of these factors is a full appraisal of the fault symptom. Even before the back cover is removed, the experimenter or service technician can often obtain a profile of a defect that will pinpoint the trouble to a particular stage and sometimes even to a particular component. This is possible by carefully observing the sound and picture (if present) while the various main and pre-set controls are adjusted.

Some knob twisting, coupled with clear thinking, will invariably provide a clue as to the

approximate whereabouts of the trouble—but if what is wrong is not indicated, there should at least be some indication as to what is *not* wrong, and such information can be extremely useful at this stage of the exercise, bearing in mind that fault diagnosis sometimes develops into a process of elimination.

Let us take a typical case. Suppose that the picture is all right on all receivable channels, but there is no sound. The symptom has obviously told us that the vision stages are in order, including the timebase, the EHT section and the H.T. section. We know immediately, then, that the sound trouble is not in the H.T. rectifier, nor the tuner, nor the aerial system or diplexer, nor in the common I.F. amplifier stage (if fitted).

## A.F. Stage

By turning up the volume control and listening closely near to the speaker we should hear residual mains hum. If we do, then the speaker is working and H.T. voltage is present on the output valve. When the volume control is turned we may hear a slight crackle from the speaker, indicating that the A.F. amplifier as well as the output valve is working. By that simple process and *without removing the back cover*, we have narrowed the trouble down to two stages. This is not bad, bearing in mind that there are twenty or so stages in a set.

Given in Fig. 1 is a block diagram of the sound, vision and sync stages of a typical receiver. By

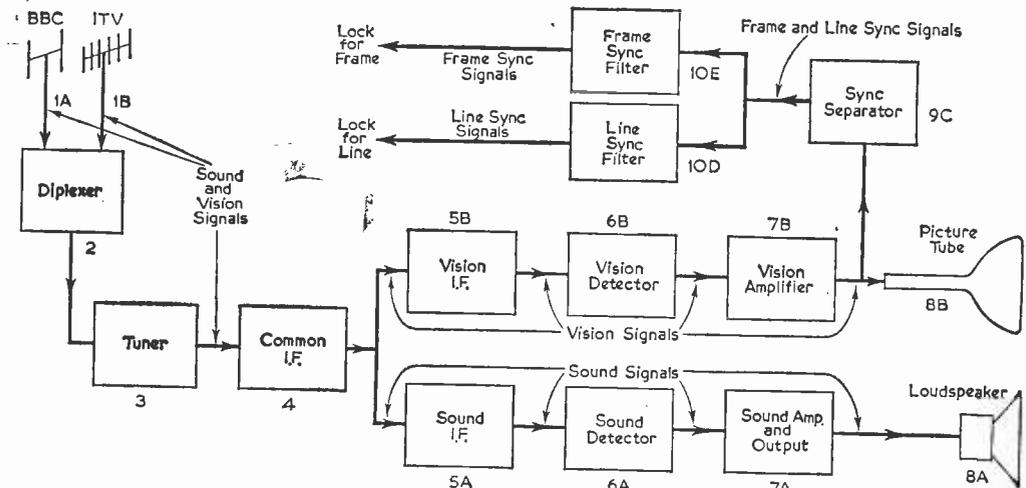


Fig. 1.—A block diagram of the signal stages of a television receiver showing the signal paths.

the process given above we know that sections all but stages 5A and 6A are working.

Had there been no residual hum from the speaker, then we could have been pretty well certain that the trouble would have been either in the speaker itself or in the output stage. The speaker leads could have become disconnected, which sometimes happens with plug and socket arrangements, the H.T. feed to the sound channel could have failed, or, most likely, the primary of the speaker output transformer could have gone open-circuit.

**Stage Identification**

The next move, then, would be to remove the back cover, but, before doing anything more, the primary stages of the receiver in terms of valves and major components should be identified. This is a simple matter if the service manual or service sheet for the particular receiver is available.

Most often, however, a service sheet is not

available, and other methods for identifying the components have to be adopted. Our Query Service is always prepared to undertake this, for the experimenter, provided that a rough sketch of the chassis, showing the positions of the valves and major components requiring identification is included with the query together with a stamped addressed envelope and the current Query Coupon.

The general layout of most receivers follows a fairly consistent pattern and, with some straight thinking, quite a lot can be learned from observation alone. Again, the process is one of elimination; for example, one can quickly identify the H.T. rectifier, whether it be of the valve or metal type. This is invariably mounted near the power input end of the chassis, close to the mains transformer or mains dropper (the fairly large resistor carrying taps and which becomes hot). Moreover, the type number of the valve usually indicates conclusively that it is a power rectifier, and its

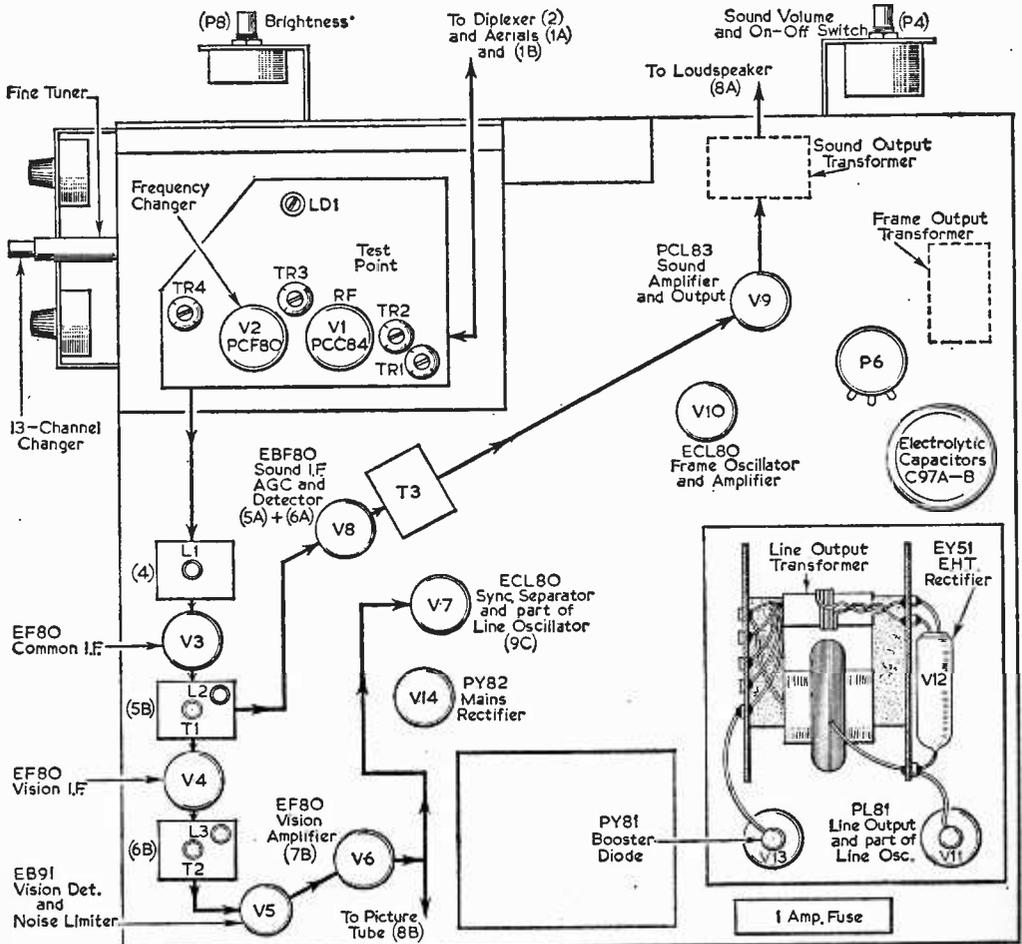


Fig. 2.—The above-chassis view of a typical receiver showing the various stages and signal paths in accordance with the block diagram in Fig. 1.

internal structure clinches the matter. If in doubt about any particular valve, its type can be looked up in a valve data booklet.

Similarly, the line output valve and booster or efficiency diode can quickly be located. These are close to the line output transformer, which itself cannot be missed as it carries the EHT rectifier valve and is highly insulated with a plastic material. It will usually be quite dusty, since the high electrostatic charges forming on its winding act on dust as a magnet acts on iron filings. Insulated leads from tappings on the line output transformer go direct to the top caps of the line output valve and booster diode. In a large number of sets, the EHT rectifier is of the wire-ended variety and is wired direct to tags on the line output transformer. More recent sets, however (or very old ones) may feature a plug-in type of EHT rectifier, but, again, it will be very close to the line output transformer and will be plugged into a highly insulated valveholder, possibly moulded in plastic on to the insulation of the line output transformer.

### Tuner

The channel tuner is obvious, and its two valves indicate which ends are concerned with R.F. amplification and frequency changing. The triode-pentode (such as the Mullard PCF80) is the frequency changer (the pentode acts as the mixer and the triode acts as the local oscillator), and the double-triode (such as the Mullard PCC84) is the R.F. amplifier, the two triodes being wired in a "cascode" circuit. Very recent tuners use a single-triode R.F. amplifier in an "earthed grid" stage.

In Fig. 2 is given the above-chassis view of a typical receiver, on which is marked the functions of the various valves and also the stages and signal paths to tie up with the block diagram in Fig. 1. The features already described, such as the H.T. rectifier, line output valve, booster diode, tuner, etc., can be seen clearly.

### Common I.F. Amplifier

The signal from the tuner goes to the common I.F. amplifier (V3), at the output of which the signal splits to sound-only and vision-only paths. The vision signal goes to the vision I.F. stage

(V4), to the vision detector and noise limiter (V5), to the vision amplifier (V6) and then on to the picture tube (stage 8B—see Fig. 1). The sound signal, from the common I.F. stage, goes first to the sound I.F. amplifier (V8), to the sound detector (also in V8 in this set), to the sound amplifier and output stage (V9) and then to the speaker via the sound output transformer (stage 8A—see Fig. 1).

It should be noted that designers often employ various devices to reduce the number of valves and components, and they often make one valve do more than one job. Stage V8 in Fig. 2, for example, is concerned not only with sound I.F. amplification, but also with sound detection and sound automatic-gain-control (AGC). The EBF80 valve employed is a double-diode pentode. The pentode section serves as the sound I.F. amplifier in the normal way, while one of the diodes gives sound detection and AGC. In this particular set, the other diode section gives vision AGC of the mean-level type, the signal being picked up from the sync separator.

### Other Circuits

In other sets, the sound I.F. amplifier may be a straight pentode valve, with detection and AGC being accomplished either by a separate double-diode valve or by semiconductor diodes (germanium diodes) possibly housed in the can of the final sound I.F. transformer.

Similarly, a triode-pentode valve is almost invariably used as sound A.F. amplifier and output, and this is often of the PCL83 or ECL80 class. Other double-valves are found in the frame timebase and line timebase circuits. In the frame timebase, a triode is often used as blocking oscillator and the associated pentode as frame output, feeding the frame scanning coils. In the line timebase, a double-triode may be used in a multivibrator arrangement, or the pentode of a triode-pentode valve may be used as sync separator, and the triode as part of the line oscillator, the other part being the line output valve, as in stages V7 and V11 in Fig. 2. Vision detection is nearly always accomplished by a double-diode valve, one diode acting as the detector and the other diode as an interference limiter.

*(To be continued)*

## USING A SIGNAL GENERATOR *(Continued from page 599)*

The modulator, for amplitude modulation, should preferably allow the radio frequency carrier to be modulated either from the internal or an external audio generator. A fixed depth, usually 30 per cent, is standard on the cheaper instruments, but it can be very helpful if the modulation depth can be varied.

### Deviation

The frequency modulator, which works on the oscillator directly, should allow of deviation of up to  $\pm 200$ kc/s from the internal audio generator, for testing F.M. receivers, and deviations up to 5Mc/s from an oscilloscope timebase for displaying the response curve of I.F. stages.

An output level meter is a very useful device for the output can vary quite considerably over the

frequency range and with variations in the mains. Usually this meter has only one calibration mark, known as the set carrier level, and the oscillator power output can be adjusted by a knob usually marked "set carrier level" to give a power output corresponding to this level. There is thus always a definite known value of voltage going into the attenuator.

### The Attenuator

The attenuator is usually of the resistive type. It is stepped usually in dB steps, which are also calibrated in terms of the output voltage developed across the end of the output cable when it is terminated in impedance equal to its characteristic impedance.

# Underneath the Dipole

A MONTHLY  
COMMENTARY

By Iconos

**S**TATEMENTS by both BBC and ITV spokesmen that television coverage has now been achieved to a very high proportion of the population of the country—not far off 100per cent—will be received with scepticism in a good many localities. At a guess, I would estimate that really good reception is only achieved by little more than 60per cent, the remaining viewers' pictures being subject to interference troubles and ghosting, often aggravated by very weak signals. There must be hundreds of towns and villages in valleys and particularly along our coastlines, behind cliffs and downs, which are effectively screened from their nearest BBC or ITV transmitters. Geographically cut off from their programme sources, only drastic and quite impossible measures, such as bulldozing a hill away, could give satisfactory improvements to reception in these places, particularly on the ITV channels. The surprising thing is the contented way in which these unfortunate viewers sit before their sets and watch a picture full of "noise" and grain, interference patterns and static. They become so "drugged" with these imperfect pictures that they come to accept them as the inevitable. Nevertheless, they are included in the set-counts of both services.

## Alternative Signal Sources


Country-wide reception, good, bad and indifferent, having been more or less achieved, BBC and ITV are now trying to do something about these patchy areas, the Cinderellas of TV. An increasing number of low-power booster relay stations will be erected and linked with main parent transmitters by microwave transmitters or other means. Much progress has been made with the design of unattended and entirely automatic relay transmitters for picking up good

signals from the top of a hill near the screened district and re-radiating them on a different frequency and with different aerial polarisation. The number of such relay stations has been limited up to now and the BBC paved the way with such relay stations near Brighton, Dover, Peterborough, Douglas (Isle of Man) and in the remote parts of Scotland, where relatively large populations received little or no signal at all. This train of events has followed the pattern of early BBC radio stations, when sound relay transmitters were erected at Sheffield, Plymouth, Leeds, Edinburgh, Liverpool and six other main centres of population that were out of crystal-set range. Now the BBC are continuing this policy in areas where a TV signal can be received, though not well. Hence the erection of a booster relay of North Hessary Tor's transmissions at a point near Redruth and new proposal for a relay transmitter at Walthwaite, near Barrow-in-Furness, which

will pick up and relay the transmissions from Holme Moss. In the latter area, a surprisingly large population—2,250,000—will receive a much improved picture. Similarly, ITV are opening a relay transmitter at Strabane in Ulster, one near Bedford, one near Selkirk (which is a satellite of the new Border Television transmitter at Caldbeck, Cumberland), and have several others under consideration.
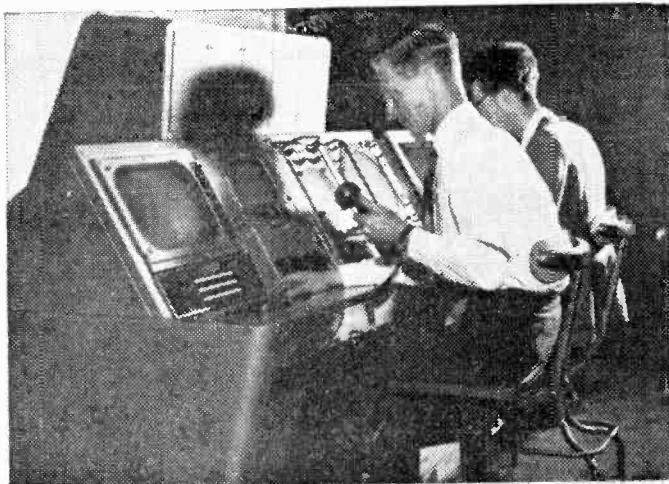
## Wired Television

The ultimate number of television relay transmitters is necessarily limited, and though ITV and BBC will compete for the untapped pockets of population in many places, there will be many more places which still require help. The best alternatives to a booster station are the wired television systems, L.F. or R.F. The L.F. system, such as that installed by Rediffusion, Relay Vision and others in large towns and cities, requires networks of special cable, usually laid under-



This Tabular Display unit and combined Radar/Synthetic Display unit, made by Marconi, will be shown at the S.B.A.C. exhibition in the near future. Of special interest is the closed circuit television screen, which is used to give an updated display of meteorological information.

ground, which distributes television and sound signals picked up at a good receiving site on a hill nearby. The signals are converted into comparatively low frequencies for easier sending over underground cables, aided by distribution amplifiers at strategic points. A special type of television receiver is hired as a part of the service, obtainable only from the relay company.

On the other hand, the R.F. system converts the incoming signals to channels 1, 2 and 4, which are sent on coaxial lines, frequently overhead, which run behind houses attached to electrical or telegraph poles, for easy connection to viewers's own sets. These sets can be of standard type, purchased from any TV shop. Naturally, the radio dealers prefer the R.F. system, and in some districts where reception is patchy, dealers have formed syndicates to construct and operate wired television services, thereby saving themselves headaches with aerials (and the customers complaints about poor pictures). By providing good, strong signals in these places, moreover, they have promoted the sales of their TV sets. There are dozens of such systems in the valleys of South Wales, Devon and Cornwall, where so many towns and villages are situated at the estuaries of rivers, screened by hills from BBC and ITV transmitters. Even East Anglia has its quota of awkward reception spots which are now admirably served with a comprehensive choice of programmes which include BBC and two ITV transmissions, VHF radio on the Home, Light and Third programmes.

In Devon, Sidmouth, Seaton, Beer and Lyme Regis are served by the Viewline R.F. system, whose wired television service was first established at Branscombe when the BBC's London transmitter was the only television signal available. One of Viewline's hill-top receiving stations has a high mast with a sixty-four element aerial array directed at Southern's Chillerton Down transmitter in the Isle of Wight. It produces a very fine picture, seen by a thousand subscribers who live in houses strongly devoid of the usual aerial ironmongery. The unencumbered chimney stack and roofs are a strange sight.

### **The Burden of Proof**

I do not go to the cinema so often these days, like many others. I "shop" for my films instead of making regular visits week after week, whatever is on. Sometimes, during the fifteen to twenty minutes of advertising filmlets and exhortations to buy ice-cream, trailers of forthcoming films entice me to make a return visit the following week—that is, if the trailer is well-presented and not cluttered up with too many superlative adjectives. The same applies to the trailers or "promotion material" put out by the BBC and ITV companies. If the announcements and preview pictures are not very attractive, they serve as a warning *not* to view the subject advertised. I very nearly formed a wrong opinion in advance of Anglia's superb play, "The Burden of Proof", owing to the rather drab series of still photographs and spoken patter which were the "promotion material". I formed the opinion that it was to be just another kitchen-sink drama of unrelieved gloom—until I noticed that George More O'Ferrall was to be the director. So, in spite of the "promotion", I switched on for "The Burden of Proof" and was rewarded with about ninety minutes' realistic and gripping "who dunnit" entertainment which kept the tension up from the starting sequence of an identification parade to the highly

satisfactory dénouement at the end. Richard Pearson had another very meaty role as the man who volunteered for an identification parade at the police station, only to be picked out as the wanted man—and around whom circumstantial evidence seemed to build a strong case that he was, in fact, the guilty party. So well was the play constructed and developed by George More O'Ferrall that the majority of viewers probably supported the growing suspicions of the police.

With superb technical work and realistic settings, the actors had good backgrounds to help the atmosphere. All the players were first-class, the unfortunate victim, Lionel Bellows, being played by Richard Pearson, the detectives by Basil Dignam and Richard Walton, Mrs Bellows by Annette Carrell and Milly, the barmaid—the only person who believed in his innocence—by Pauline Jameson. Many other players in large and small parts made contributions to the success of this TV play by Gerald Savory. Lastly, the background music was sparingly used and unobtrusive, which is as it should be. James Clarke was the composer.

Anglia have made a lot of excellent contributions to the ITV network, more than any other regional station, and "The Burden of Proof" was proof indeed that they intend to sustain their high reputation in the drama field.

## **PRACTICAL WIRELESS**

### **Chief Contents of the September Issue**

**Now on Sale 1/6**

**AN INTERCOM AMPLIFIER  
PRE-WIRED VALVEHOLDERS  
A CRYSTAL FREQUENCY MARKER  
A WIDE-RANGE AUDIO OSCILLATOR  
A WOBBLATOR FOR F.M., I.F. ALIGNMENT  
CONVERTING THE TRF TRANSISTOR FOUR TO L.W.  
RECORD-PLAYER AND RADIOGRAM FAULTS  
FERRITE ROD AERIAL CONVERSION  
A TRANSISTORISED VHF SUPERHET  
RECORDING FROM THE RADIO  
CLUB NEWS  
ETC., ETC., ETC.**

**Transistors for R.F., F-M. T.V. and U.H.F.**  
 Frequencies quoted are approx. cut-off.  
 SB 078 15-20Mc/s ..... 8/6  
 SB 305 20-30Mc/s ..... 9/-  
 SB231R 40-50 Mc/s..... 15/-  
 American 2N1727 100-150 Mc/s..... 15/-  
 American 2N1728 100-150 Mc/s..... 12/6  
 American 11832 1000-1300 Mc/s..... 25/-  
 American 11833 1000-1300 Mc/s..... 25/-

**SUB-MINIATURE COMPONENTS**

Push-pull driver with Sep. Secondaries for transformerless output 6/6.  
 3 I.F. transformers and oscillator and circuit 23/6.

Smallest possible electrolytics 1/9 each. 1 mfd., 2 mfd., 8 mfd., 10 mfd., 20 mfd., 30 mfd., 50 mfd., 100 mfd., 200 mfd.

Smallest 1 watt resistors 5d. each. Miniature 0.1 mfd. 1/-, 0.05, 0.01 8d. values up to 0.005 6d. each.

Miniature slide switch 2/6.  
 Edgewise Volume controls. 2K, 5K., 10K., 20K., all 2/6 each or 4/6 with Switch.

Set of 6 transistors for superhet in original packets guaranteed. Mullard OC44, OC45, OC81D matched pair OC81, £2.00 the set.

3in. Speakers 3 ohm or 80 ohm 18/6.

2 1/2in. Speakers 3 ohm 19/6.

Elliptical Speaker, 7in. x 5in. 35 ohm 19/6.  
 35 ohm 5in. normal flux 18/6. Hiflux 22/6.  
 Post & Packing on all speakers 1/6 each.

**NOW THE MARK IV Pocket '4' Transistor Radio Read these Testimonials**


**D. A. Hilton, Leigh, Lancs.**  
 "I received 'Pocket' 4 on Christmas Day. I made it up on Boxing Day and I am very pleased with the results. It brings in local stations and many foreign stations including Luxembourg at good strength. I am 13 years old!"

**Mr. J. Bell, Wolverhampton.**  
 "I am writing to express my satisfaction at the standard of your kit for your Pocket 4 Transistor set and also to state that it has come up to my expectations in regard to performance."

**Mr. R. Bell, Newcastle-on-Tyne.**  
 "I have built your Pocket 5 Transistor set, I am very pleased with it!"

**Mr. F. Jackson, Icknham, Hiddx.**  
 "I have built the Pocket 4 and am more than pleased with the results".  
**Seven days' approval**  
 Order in confidence. We allow you seven days to decide whether or not to make the set, you may return the parcel as received within this time and your money will be refunded in full.

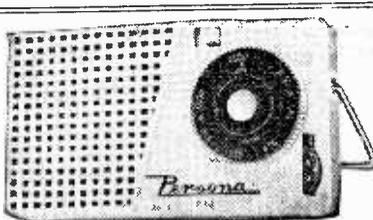Read some of the testimonials, over 1,000 of which have been received about our Pocket Receivers.



Our famous Pocket "4" which is doing yeoman service all over the country has been modified and improved to make it an even better receiver. The new features include:-

- New elegant dial graduated for Long and Medium Waves.
- Switched Long and Medium Waves.
- Slide switch on/off control.
- Printed circuit.
- Ferrite Rod Aerial.
- Improved reaction circuit.
- Positive spindle coupling to tuner.
- Battery containers.

The Pocket "4" of course retains its original r.f. circuit which means still no aerial or earth needed.

The Pocket "4" Mark IV uses 3 transistors, crystal diode, miniature loud speaker and has all the above refinements, complete in case as illustrated (less mot(f) 52/6, battery 10d., post and insurance 2/6. Mot(f) 2/-.

Pocket "6" as Pocket "4", but with Moving Coil Speaker and Q.P.P. output stage, 95/-.

**ELECTRONIC PRECISION EQUIPMENT LTD.**

post orders are dealt with from Eastbourne, so for prompt attention please post your orders to 66 Grove Road, Eastbourne, marked Department 7. Callers may use any one of the Companies below.

286 London Road, Croydon.  
 Phone: CRO 6558  
 Half day Wednesday

29 Stroud Green Rd., Finsbury Park, N.4.  
 Phone: ARCHWAY 1049  
 Half day Thursday

520 High Street North, Manor Park, E.12.  
 Phone: LIFORD 1011  
 Half day Thursday

42-46 Windmill Hill, Rushlip, Middx.  
 Phone: RUSHIP 5780  
 Half day Wednesday

246 High Street, Harlesden, N.W.10.  
 Phone: ELGAR 4444  
 Half day Thursday

**EXPRESS ELECTRONICS**

ROSEDALE LABORATORIES

KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

IC1	7/8 6BA6	7/- 787	9/8 DF96	8/- EF80	8/- PCL82	7/-
IC3	8/- 6BE5	7/- 873	4/- DF76	7/8 EF86	9/- PCL84	7/-
IF1	8/- 6BH6	8/9 12AH8	10/- DB77	6/- EP91	4/- PL81	12/6
IF3	7/8 6BJ6	5/9 12AT7	6/- DB142	8/8 EF92	5/8 PL82	7/-
IFD1	8/- 6BR7	8/9 12AU7	5/- DH150	10/- EL41	9/8 PY81	6/9
IFD9	7/8 6Bs7	10/8 12AX7	7/8 DK91	7/8 EL84	7/- PY83	7/6
1L4	6/9 6BW6	5/8 12BH7	10/8 DK96	8/- EM84	10/- R19	11/6
1P1	8/- 6BW7	7/- 12K8GT11/	DL92	7/8 EM85	10/- U26	9/8
1P10	7/8 6C10	9/- 12Q7GT	7/8 DL94	7/8 EY81	7/8 U52	7/8
1P11	7/8 6D2	4/- 16A5	9/- DL96	8/- EY81	10/- U76	7/8
1B5	8/- 6P12	4/- 25A83	8/8 EP91	4/- EZ40	7/6 U78	5/-
1B5	8/- 6H4GT	2/- 25L6GT	7/8 EBC41	10/- EZ80	8/6 UBC41	8/6
1T4	7/8 6J7GT	7/8 25Z4G	9/- EBF80	8/8 EZ81	8/6 UCH42	9/8
1U5	8/- 6K7G	5/8 30C1	6/9 EOC81	6/- KZ13C	9/8 UF41	8/8
3Q4	8/- 6K9G	6/- 30L1	7/- EOC82	6/- KT68	11/6 UY41	7/8
3S4	7/8 6J7GT	8/8 35L6GT	8/8 EOC83	7/8 KT68	11/6 UY41	7/8
3V4	7/8 6L7GT	6/- 35W4	8/8 EOC84	7/8 N17	7/8 W76	6/8
5U4G	7/8 6N7GT	6/- 35Z4GT	8/8 ECF90	8/8 N18	8/- W142	8/8
5Y3G	4/8 6V6G	7/8 53U6	10/8 ECF92	6/9 N19	7/8 X17	7/8
5Z4G	8/8 6X4	4/- 5763	7/8 ECH42	8/- N37	10/8 X142	9/-
6AK6	6/8 6X6G	5/- 80	6/- ECH81	10/8 PCC84	6/9 X150	9/-
6AL5	4/- 6X6GT	6/- DAF91	7/8 ECL80	8/8 PCF80	8/9 Z77	4/-
6AM6	4/- 7B7	7/8 DAF96	8/- ECL82	9/8 PCF82	7/- ZD17	7/8
6AT6	6/- 7C5	7/8 DF91	7/8 EEP41	9/-		

Coax. Super quality in. 8d. yd. Plugs, 9d. Sockets, 9d.

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES. D.P. switch 4/- Less switch, 2/8. Values 10K to 2M, B9A, BTG v. Holders 9d., Screws 9d., Contact Cooled Rectifiers 250 v.50 mA, 8/6, 85mA, 8/6.

**MATCHED PAIRS**

EL84 17/-, 6V6G 17/-, 6BW6 18/- per pair. Push Pull O.P. Transformers for above 3-15 £ 14/6. P. & P. 1/6. 12in. P.M. Speakers 3 Q 24/6. Baker's "Selhurst" 12in. 15 Q 15W. 90/-, & P. 3/6. 12in. Stereo Model £7.70.

**SETS OF VALVES**

DK91, DF91, DAF91, DL92 or DL941. 19/6  
 DK96, DF96, DAF96, DL96. 27/6  
 IC3, IF1, IFD1, IP1 ..... 27/6  
 1B5, 1T4, 1S5, 3S4, or 3V4 ..... 19/6  
 Postage and packing 6d. Over £1 post free.

ECH42, RF41, EBC41  
 EL41, EZ40 ..... 37/6  
 UCH42, UF41, UBC41,  
 UL41, UY41 ..... 35/-  
 C.O.D. 2/6.



**"SABRINA"**

STILL WELL IN FRONT

LOWER PRICES for 12 Months guaranteed tubes.

COMPLETELY REBUILT

ALL TYPES (including electrostatics)

12" to 17", One Price £5.10.0 (C.W.O.)  
 21" also available at £8.00

Including Free Passenger Transit and Insurance. (Old tubes not required.)

BRAND NEW TUBES  
 2 Years guaranteed.

17"-70°, 90° & 110° £10. (Elec. focus 10 gns.)  
 30/- on old tube, trade supplied.

**SABRINA C.R. TUBE CO.**

Electron Works, North Bar

BANBURY, OXON

Telephone 2390

**ALL TUBES**  
**Guaranteed 12 Months**  
**Carriage Free**  
*Speedy Passenger Train despatch.*



**NEW**  
 12" MW31-74 etc. **£5.50**  
 17" CRM 171, 172 **£7.00**

**COMPLETELY REPROCESSED**

TO MAKERS' SPECIFICATIONS!

**REBUILT, RESCREENED, REALUMINISED TUBES OF THE HIGHEST QUALITY**

14" ..... **£5.50**  
 15"-17" ..... **£5.10.0**  
 21" ..... **£8.0.0**

THAT "DIFFICULT" TUBE? LET US QUOTE

**ASTOUNDING BARGAIN!** The "Clarion" Transistor Battery Tape Recorder. Push-button controls, 3½ i.p.s. Portable. Durable plastic case. List price 25 gns. Complete with Mike and Tape. Our Price ONLY **16 GNS. Carr 7/6.**

**TRADE ENQUIRIES INVITED**

**LINE OUTPUT TRANSFORMERS**

Direct Replacements for 500 sets.  
 Baird. T29, T183 .. .. 52/-  
 T164, T167, T172, 2014, 1712 .. .. 80/-  
 Bush. TV 11A, B; 12A, B; TVF 12A, TUG12A, B; TRG 12A, B. .. 45/-  
 TV12AM; TV22, 24; TRG24, TUG24 .. 80/-  
 Cossor. 830, 931, 933, 934, 948, etc. .. 45/-  
 Ekeco. TS146; TS113-114; T181 .. 50/-  
 T221, 231; TSC311, etc. .. .. 50/-  
 Ferguson. 841, 2, 3; 941 to 945 .. .. 55/-  
 950T-948T; 103-145T; 203-248T .. 66/8  
 Ferranti. 1473, 1474, 1733, 1773 .. 45/-  
 1472, T1205, T1215, T1225, T1325, T1405, T1415, T1425, T1505, T1825 .. 65/-  
 G.E.C. and H.M.V. mostly 55/- to .. 80/-  
 Iniveta. T101-104; T108-110 .. .. 52/-  
 T114-126; T133-142 .. .. 45/-  
 Murphy. V114C, V116C, V118C .. 90/-  
 V120C, V180, V178, V200, V202C .. 57/8  
 V240, 250 .. .. 62/8; V214, 216 .. 89/-  
 Philips. 114 U/FUM, 1115 U, 1437 U, 1496 U, 1726 U, 1746 U, 1747 U .. 85/-  
 383A, 483A, 583A, 683A .. .. 80/-  
 Pye. LV30, 18T, CS17, VT17 .. .. 60/-  
 CTM4, V4, V74; V7, VT7 .. .. 52/8  
 Ultra. 814, 815, 817, 915, 917; VW80, 972A730, YVW84, WYV720, V710 .. 85/-  
 (complete assembly with U25) .. 85/-  
 14/53, 15/60, 17/50, 17/53, 17/60, 17/63-4, 17/70-1-2, 21/50, 21/60, 21/70-1-2 .. 80/-  
 All Ultra Frame O.P.T.'s .. .. 28/8

Add post 2/6.  
 100 mixed resistors. 1W-2W-7/8 post 1s.  
**ANOTHER BARGAIN.** Complete set of 6 NEW MARKET High Gain Transistors and 1 Diode. Individually selected for max gain and stability. Equiv. OC44, OC45(2), OC71, OC74 (matched pair) .. ONLY £2.  
 Valves, Multimeters, Record Players, Tape Recorder Decks, see previous issues.

**WESTWAY RADIO**

S.A.E. with enquiries please.  
**5 Westward Way**  
**Preston Road, Harrow, Middx.**  
 Tel. WOR 2663

**TELEVISION TUBES**

**RE-GUNNED.** Super screen TV tubes with a 12 months' guarantee. Tubes all types 12in. to 14in. ... £4.5.0  
 Tubes all types 15in. to 17in. ... £4.15.0  
 Carriage and insurance 10/- extra.  
 Allowance against the return of old tube

**RECTIFIERS**

RM1 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RM5 19/6, 14A86 19/6, 14A97 19/6, 14A100 19/6, LW7 17/6, 18RA 1-1-16-1 6/-, FC31 (14RA 1-2-8-3) 22/6, FC101 (14RA 1-2-8-2) 10/6.

**REDUCTIONS IN MULLARD TRANSISTORS**

OC19 48/- OC72 18/- OC78D 8/-  
 OC35 25/6 OC72pr 16/- OC81 8/-  
 OC44 11/- OC73 16/- OC84 11/-  
 OC45 10/- OC75 8/- OC170 13/6  
 OC70 6/6 OC77 10/- OC171 14/6  
 OC71 6/6 OC78 8/- OC202 36/-

**A SPECIAL OFFER OF SIX MULLARD TRANSISTORS**

1 OC44, 2 OC45, 1 OC81D, 2 OC81.  
 Only 37/6 set.

**EDISWAN TRANSISTORS**

XAI04 12/-, XAI03 10/-, XBI02 6/6 ea.

**ALPHA RADIO SUPPLY CO.**  
**VALVES BY RETURN POST**

AZ1 10/-	EF91 5/9	PCL84 13/6
DF96 8/-	EF92 6/-	PL36 13/6
DAF96 8/-	EL41 9/-	PL81 11/-
DK96 8/-	EL84 9/-	PL82 8/6
DL96 8/-	EL91 4/6	PL84 12/7
EABC80 9/-	EM80 9/6	PX25 12/6
EAF42 9/6	EM81 10/6	PY32 15/6
EBF41 8/9	EY51 9/6	PY80 8/6
EBF80 9/9	EY86 10/6	PY81 8/6
EBF89 9/6	EZ40 7/6	PY82 7/-
ECC81 8/-	EZ80 7/-	U25 13/6
ECC82 7/6	EZ81 7/-	UAF42 9/6
ECC83 9/-	FC13 5/-	UBC81 11/4
ECC84 10/-	GZ32 11/6	UCC8410/11
ECC85 9/6	HL42DD	UCH42 9/6
ECF80 12/-	HZ44 10/-	UCL82 11/6
ECF82 10/6	OZ4 4/6	UCL83 16/-
ECH42 9/6	PCC83 13/6	UF85 9/-
ECH81 9/-	PCC84 8/6	UL41 9/-
ECL80 9/6	PCC85 11/6	UY41 6/6
ECL82 10/6	PCF80 8/9	3D6 5/-
EF50 5/-	PCF82 11/6	
EF86 12/6	PCL82 11/6	

**LIGHTWEIGHT SOLDERING IRON**

Latest design for use on 200/250 volts, with detachable handle, can be carried quite comfortably in pocket, 18/9 each.

**RECORDING TAPE**

Special Offer of Top quality recording tape, 3½in. spool 200ft. 5/3, 5in. spool 600ft. 13/9, 5½in. spool 850ft. 18/6, 7in. spool 1200ft. 23/-. Extra-play tape, 3½in. spool 300ft. 7/-. 5in. spool 900ft. 21/-. 5½in. spool 1275ft. 26/6, 7in. spool 1800ft. 37/6.  
 Empty spools, 3½in. 1/6, 5in. 2/-, 7in. 3/-.

**CATALOGUE**

**OUR 1962 CATALOGUE IS NOW AVAILABLE. PLEASE SEND 1/- IN STAMPS FOR YOUR COPY. TRADE CATALOGUE ALSO AVAILABLE, FOR WHICH PLEASE ATTACH YOUR BUSINESS LETTER HEADING**

**TAPE DECKS**


Collaro Studio Tape Transcriber 3 motors, 3 speeds, 1½, 3½, 7½ i.p.s., take 7in. spool, Push-button control. Price £12.12.0. Tape extra. Carr. & ins. 5/6.  
 Latest B.S.R. "Monardeck" Single Speed  
 3½ i.p.s. takes 5½in. spools. Simple controls. £8.8.0. Tapes extra. Carr. and ins. 5/6.

**ALPHA RADIO TERMS.**—Cash with or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 1/3; 20/- add 1/9; 40/- add 2/6; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

**ALPHA FOR VALVES AND SPARES FROM STOCK**

**103 LEEDS TERRACE, WINTOUN STREET, LEEDS 7.**

# ITA Border Stations in Scotland

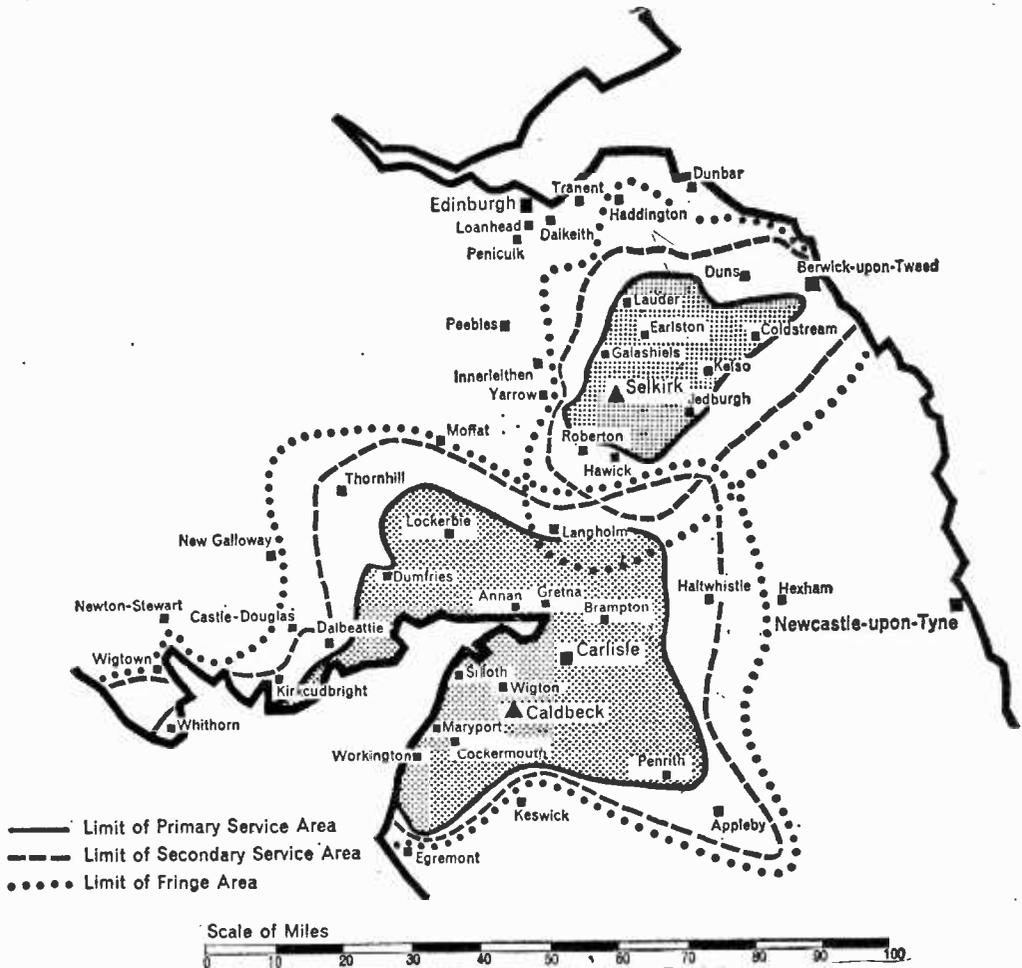

The estimated coverage of the new mast.

**G**RADE test transmissions from the Independent Television Authority's Caldbeck station in Cumberland began in July, and programme transmissions will commence on 1st September. Signals will be sent out on Channel 11, horizontally polarized.

The Selkirk station will be a fully automatic unattended satellite and will rebroadcast the signals radiated from the Caldbeck station. Transmissions from this station will start around the end of 1961 and the signals will be on Channel 13, vertically polarized.

The aerial height above sea level of the Caldbeck

station will be 1,900ft and that of the Selkirk station 1,644ft.

The effective radiated power from the Caldbeck site will be: 100kW to the North-East and South-West, 70kW to the North-West and 20kW to the South-East. The vision frequency will be 204.74Mc/s and the sound 201.25Mc/s.

The Selkirk station will have an effective radiated power of 25kW over a semicircular arc to the East. Its vision frequency will be 214.723Mc/s, and its sound frequency will be 211.223Mc/s.

The estimated number of people who will be able to receive transmissions from the Caldbeck station is 392,000, and from the Selkirk station 121,800.

# Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

**SPECIAL NOTE:** Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

## AERIAL SCREENING

**SIR,**—I believe, some time ago, I saw in your pages a note about the effects of screening an aerial (unwanted) and I would like to point out that I experienced a spot of trouble which might be of interest to others who become similarly placed. When my aerial was installed by the local radio shop it gave what appeared to be perfect results and has done so for two years. Recently I felt that the performance of the receiver was not up to standard but did not do anything about it. A friend who is radio-minded came to see me one day and told me that the picture was inferior, naming a lot of faults which I could only see when they were pointed out. He adjusted one or two controls on the rear and then asked to see the aerial and feeder. When we went into the attic he said "There's your trouble," and pointed to the large water cistern, and after rerouting the down-lead he suggested that the aerial would be much better in another position. I eventually made this move and the set has, as a result, been rejuvenated. The cistern was below the aerial level, but definitely had a marked absorption effect. I imagine the aerial was just put in the most easily accessible position and no real tests were made to see whether it could be improved. The progressive deterioration of the receiver has now shown that the position chosen was not the best.—F. J. KING (Gloucester).

## PICTURE DETERIORATION

**SIR,**—In your issue of May you replied to a query by a Mr. Glover of Leicester who had the same trouble which I experienced some time ago. I had tried several things unsuccessfully, and eventually replaced the tube, which promptly cured the trouble. I firmly recommend Mr. Glover to do the same, when I am certain that he will find his worries at an end. Incidentally, I note that your expert recommended that he should do this, and it is not worth while experimenting with boost volts and transformers.—F. R. YOUNG (Blackheath).

## SYNC SEPARATOR

**SIR,**—Mr. Slingen in the April issue asks about the differences in the method of taking out the frame and line pulses, and enumerates different systems as found in commercial receivers. I have carried out many experiments in this direction, and find that there is very little actual difference in the split anode or separate cathode and anode feeds. What I have found, however, is that better results are obtained when the frame is fed from the cathode circuit, and diodes are employed in the limiting

circuits. This does seem to be a more stable method of obtaining frame working, but is more complicated.—F. R. BENBOW (York).

## LINE SLIP

**SIR,**—From time to time you publish details of faults and I have just cured a most annoying defect which did not answer to any of the accepted tests, etc. The trouble was line slip in the form of gradually increasing tearing at the top of the picture. This occurred after about one hour's viewing, and from a start of a strip about half an inch deep it gradually increased to three or four inches, and no amount of valve replacement or component changes would get rid of it. I decided one day to clean the set out as it had become very dusty, and accordingly carefully removed the complete chassis with tube (which was bolted to the chassis), and started dusting. I was surprised to find two fair sized washers firmly adhering to the scanning coils, apparently due to the strength of the focusing magnet. I removed these, not thinking they would have any effect on the line trouble, but when the set was replaced, the trouble did not occur again and reception has been perfect for three months. How could these washers on the coil assembly cause a fault of a variable nature? Perhaps one of your expert readers may be able to offer a solution.—F. N. HUMBERSTONE (N.W.).

## HOME CONSTRUCTION SETS

**SIR,**—I started taking an interest in home-made apparatus when looking through some back numbers of P.T. I came across a very interesting aspect as a result of this research and wonder if there is any explanation of the following points. All I.F. transformers which I have seen so far, have their trimming cores at top and bottom, with the result that the chassis has to be turned over when lining up. Why cannot the adjustment be made from the side? Surely the two coils could be wound on two formers situated side by side, to avoid the above disadvantage. When testing a set, access must be had to the valveholder terminals, and this necessitates access to the underside of a chassis. The tube connections are accessible only from the rear, and thus one would apparently have to be continually turning a heavy set end to end and over and over. What happened to the old idea of using a standard type of chassis standing vertically? It would appear to be ideal, if only the valves could be placed on the undersurface, but I do not think this would be a bad point and it would certainly give access to every part which one needs to test in a modern television receiver, and the coils would be out in the cool and ventilation would surely be at its best. Perhaps you would bear this idea in mind in your next design for the home constructor—if only some manufacturer would make available I.F.'s of the type above suggested.—B. NEVILLE (Northolt).


# NOW! YOU can MASTER ELECTRONICS!

**BRITAIN'S MOST COMPREHENSIVE  
PRACTICAL COURSE  
IN RADIO • ELECTRONICS  
TELEVISION!**


**THESE SPECIAL TRAINING  
KITS — YOURS TO KEEP**



**Multi - Range  
TEST METER**

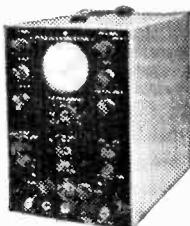

**CATHODE RAY  
OSCILLOSCOPE**

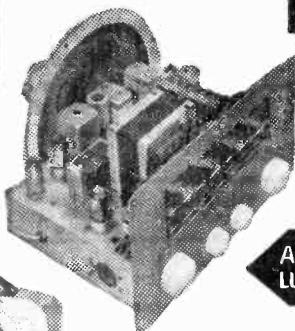

**AM and VHF/FM  
LUXURY RECEIVER**



**SIGNAL GENERATOR**




**Complete set of  
Picture Way books and  
Experimental Manuals**

**LEARN BY BUILDING  
NOW for your  
CAREER • HOBBY  
OWN BUSINESS**

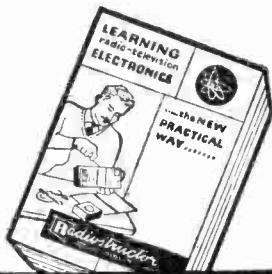**YOU RECEIVE**

- Complete kits of equipment as illustrated.
- Complete set of experimental manuals.
- Complete set of "picture-way" theory books.
- Modern test-yourself examination sheets.
- Study programme.
- Unlimited consultation with Tutors.



**FREE  
BROCHURE**

**POST NOW**

**RADIOSTRUCTOR**

TO RADIOSTRUCTOR (DEPT. M102)  
READING, BERKS.

Name \_\_\_\_\_ **BLOCK**

Address \_\_\_\_\_ **CAPS**

\_\_\_\_\_ **PLEASE**

(We do not employ representatives)

9/61

### "6 plus 1" TRANSISTOR RADIO KIT

— UNBEATABLE VALUE —

Mrs. Current Production Offer—A fortunate bulk purchase enables us to offer one of the season's most outstanding bargains in Portable Transistor Radio Kits. This kit is a modern, sensitive quality circuit Receiver Unit with all the latest features. Six B.V.T. Transistors and 1 Diode, Printed Circuit, Mod. and Long Wave Ferrite Aerial, Car Radio Input, 4w Push-Pull output into 3 ohm speaker, Calibrated Dial and Slow Motion Tuning, etc. Size: approx. 8 1/2 x 2 1/2 in.



**COMPONENT KIT** 5 Gns. SET OF 6 TRANSISTORS and 1 DIODE 45/-

7 x 3 1/2 in. speaker Complete Kit (less speaker) Bargain Price 3d. stamp, full details. Circuit and Instrs. 1/6

15/6 carr. 1/8. £6.19.6 carr. 2/6.

NEW VALVES GUARANTEED		ALL TRANSISTOR BARGAINS!	
1T4	8/-	RP66	12/8
1E5, 1A5	7/8	EL64	8/8
3A4, 3A7	7/8	EY51	9/8
DAF96	9/-	EY86	7/8
DF96	9/-	EZ50/81	10/-
DE96	9/-	PC84	9/8
DL96	9/-	PCF80	9/8
ECL80	10/8	PCL35	12/8
ECL82	10/8	FL81	12/8
EF80	8/-	U35	12/8

BRAND NEW—BVA 1st Grade	
OC44	10/8
OC45	9/8
OC81D	7/8
2/OC81	15/8
XA109	10/-
XA101	9/8
XB105	7/8
XC101	8/8
SB305	9/8

**SPEAKER FRET.** Expanded Bronze anodized metal 8 x 8in., 2/3; 12 x 8in. 2/-; 12x12in., 4/6; 12x16in., 6/-, etc.

**TYGAM FRET** (Contemp. pattern) 12 x 12in., 2/-; 12 x 18in., 3/-, etc.

**SPEAKERS P.M.** 3 ohms 2 1/2" Elec., 17/8. 3 1/2in. Goodmans 15/8. 5in. Bala, 17/8. 6in. Elac. 18/8. 7 x 4in. Goodmans, 18/8. 8in. Rola, 20/- 9 x 6in. Goodmans, 25/- EMI Tweeter, 22/8.

**CONDENSERS—Silver Mica.** All values, 2 pF to 1,000 pF, 6d. each. Ditto, ceramics 8d. Tub. 450 v. T.C.C., etc., .001 mfd., .01 and .1/350 v. 9d.; .02-.1/500 v. 1/-; .25 Hunts 1/8; .5 T.C.C. 1/8, etc., etc.

**RESISTORS—FULL RANGE** 10 ohms—10 megohms 20% ± w. and 5% ± w., 8d.; 1 w., 6d.; (Midget type modern ratings), 1 w., 6d.; 2 w., 8d.; 10% HI-Stab. 1 w., 5d.; 1 w., 7d.; 5% ± w., 9d.; 1% HI-Stab. 1 w., 1/6.

**W/W RESISTORS.** 25 ohms to 10K, 5 w., 1/8; 10 w., 1/8; 15 w., 2/-.

**PRE-SET 1/4 W POTs.** Full range 25 ohms—2 meg., 3/-.

**VOLUME CONTROLS—5K—2 Meg.** ohms. 3in. SPINDLES MORGANITE MIDGET TYPE, 1 1/2in. diam. Guar. 1 year. LOG or LIN ratios less 8w., 3/-, D.P. Sw., 4/6. Twin Stereo less Sw., 6/6. D.P. Sw., 8/-.

**Electrolytics All Types New Stock**

TUBULAR	CAN TYPES
85/25v. 50/12v.	8+8/45v. 4/6
50/50v., 100/25v.	32+32/275v. 4/6
8/450v. 4/350v.	50+50/350v. 6/6
	60+250/275v. 12/8
	18+18/450v. 2/8
	32+32/450v. 6/6

12/8 type Transistor Midget Types—all values 1 mfd. to 100 mfd. 1/9 ea. 6v/12v.

### RECORDING TAPE—Special Offer

American COLUMBIA (C.B.S.) 1st Grade P.V.C. TAPE. Fitted leader and auto stop foil. Brand New, Boxed, and fully guaranteed.

Standard	Long Play
5in., 600ft. .. .. 15/-	900ft. .. .. 19/8
5 1/2in., 900ft. .. .. 18/8	1,200ft. .. .. 22/8
7in., 1,200ft. .. .. 21/-	1,800ft. .. .. 32/-

P. & P. per reel 1/8, 6d. on ea. additional reel.

**SPECIAL BARGAIN** 3in. mtr. Tape 225ft. 5/8. P. & P. 6d. Plastic Tape Reels .. .. 3in. 2/6, 5in. 3/8, 7in. 3/6.

### TAPE RECORDER KIT ONLY £16 10s.



Latest 5-valve circuit based on Mallard's design. Magic eye and tone controls. Printed circuit already wired. A sensitive quality recorder. B.B.R. Amp Kit 95/-. B.S.R. Tape Deck 28.10.0. Collaro Amp Kit 26.5.0. Collaro Tape Deck 212.10.0. Set of 5 valves 45/-. Special Unit Kit Prices—Send stamp for detailed list. Handbook (full details) 2/6.

Jason Tuners—Approved Kits—comprehensive range in stock. Model FMT1 5 gns. etc., 48-hour Alignment Service. Send for complete bargain list.

## TRS RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY  
 Est. 1946. Telephone THO 2188

Forms O. W. O. or C. O. D. Post and Packing up to 1 lb., 7d., 1 lb. 1/1, 3 lb., 1/8, 5 lb., 2/-, 10 lb., 2/8. Hours: 9 a.m.—6 p.m.; 1 p.m. Weds.

## AERIALS

BAND I BAND II BAND III

**Combined Arrays I and III**

- 1+5 Element Loft Mounting .. 38/3
- 1+5 Element Loft Mounting .. 46/9
- 1+5 Element Wall Mounting .. 45/3
- 1+5 Element Wall Mounting .. 51/-
- 1+5 Element Chimney M'ting. .. 57/10
- 1+5 Element Chimney M'ting. .. 68/9

**Band I**

- Single Dipole Wall Mounting .. 24/7
- Single Dipole Chimney M'ting. .. 40/2
- X Array Chimney Mounting .. 62/3
- H Array Chimney Mounting .. 67/7

**Band III**

- 3 Element Yagi Wall Mounting 33/-
- 6 Element Yagi Wall Mounting 43/-
- 9 Element Yagi Wall Mounting 58/-
- Chimney Lashing Mounting add 10/-
- Double 6 Array. only with clamp 83/-

**Band II**

- Single Dipole Wall Mounting .. 20/5
- Single Dipole Chimney M'ting. .. 29/9
- H Array Chimney Mounting .. 52/4



### REPAIR KITS

Band III Folded Dipole with Insulator. Complete .. 9/3

Band I Insulator with Two 1/2 inch Dipoles For 1 or 1/2 inch Booms. Complete .. 19/5

6 inch Lashing Kit. 12/11. 7 1/2 inch Lashing Kit. .. 14/8

6 inch Wall Bracket with U Bolts .. 7/10

1-1/2 inch Clamps, 3/10. 1-2 inch Clamps Universal. .. 5/4

Bracket Repair Kit. J Bolts; U Bolts; 20ft Lashing Wire; Thimbles; Corner Plates .. 6/-

Insulators. All Types .. .. (Enquire)

Co-Ax. Semi Air Spaced. 7d. yd. .. .. Plugs 1/2

Send 6p. for Lists. Please state Channel when ordering. Cash with Order. Post and Packing 3/- extra.

## SATISFACTION OR MONEY BACK GUARANTEE

# WALKER & SQUIRES

PINNOX STREET, TUNSTALL, STOKE-ON-TRENT  
 Phone: Stoke-on-Trent 88767

## KARLSON'S TUBE CHANGE

6A DENISON ROAD, LEEDS 2  
 Tel. Leeds 24576.

We are now able to offer SUPER SCREEN TV TUBES with 12 months' guarantee at the keenest exchange price ever.

*Example:*

Tubes all types	Cash allowance on return of old tube	Actual Cost of Tube
12"—14" £5	15/-	£4. 5. 0
15"—17" £6	25/-	£4. 15. 0
21" £8	30/-	£6. 10. 0

Carriage and Insurance 10/- extra

These tubes are COMPLETELY REBUILT by experts, with the most up-to-date electronic equipment, and are fitted with the famous American Golden Grid Electron Gun. Many thousands of these tubes are in service today. Our factory is open to inspection to readers of "Practical TV". Technical advice and queries are answered free of obligation. All tubes are dispatched with adhesive paper and return labels. Cash allowance is sent on receipt of old tube.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDER-TAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 631 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

#### EKCO T161

I can obtain sound and vision separately on this set but not together. I have realigned with two Avo 8s and signal generator following the makers' instructions. What is the purpose of the capacitor across the pins of the tube? It seems to be going back to the sync separator.—A. Phillips (Swansea).

Your symptoms are those of a weak signal and may be due to faulty decoupling in the I.F. stages. The condenser on the tube base is a 0.25 $\mu$ F and is part of an anti-flutter circuit connected to the anode of the video amplifier.

#### PYE 17 21/5

This set has a dull picture. The sound is fine and all valves and the tube are in order. The brightness and contrast controls are in order and also the sensitivity control. Can you help please?—J. Whiteside (Co. Armagh).

The usual causes of a dull picture are a faulty tube or a low PCC84 in the tuner. Assuming that you have checked both of these items by substitution, try replacing the vision detector diode, a CG12E crystal in the compartment at the underside end of the vision I.F. strip.

#### PHILIPS 115UF-45

The tube suffered from uncontrolled brilliance and the wiring was altered and the fault corrected. The picture is now going up or down, and is very difficult to lock. It does lock in the middle of the frame hold travel but is very critical and after a few minutes the picture starts to slip again. I suspect the ECL80 V16 or one of the resistors.—J. Coltham (Long Ashton).

The suspect resistor is R81 (2.2M) in the makers' sheet but as you seem to have a trade service sheet this is given as R83. Also check sync separator and video components if necessary.

#### K.B. RV60

There is trouble on sound on this receiver. This is in the form of distortion, mainly on BBC. Some days the sound is completely free of this distur-

tion. Can you give me an indication of the trouble?—R. Cash (Weymouth).

The trouble appears to be due to a defective resistor associated with the sound noise limiter circuit. As the receiver is fairly new, we would advise you to allow your dealer to rectify the fault.

#### MURPHY V240

Can you assist me in replacing the volume control on this set? What replacements do I need? Also, can you tell me the cause of the following faults. The raster is cut off at the right, top, left and bottom. The scanning lines are very weak and the line hold is critical in its setting. The setting is in the centre of the control. There is very bad arcing from the outer coating of the tube to chassis members and coil assembly. This only starts on heating up from cold. What adjustments do I need to make to the line drive if the line output valve is replaced?—E. Connor (Camberwell, S.E.5).

The volume control is a 250k with double-pole switch and an extra large "flat" on it to accommodate the knob. Your other symptoms indicate low gain and suggest a low 30L1 in the tuner, a low emission tube, or a faulty 20P3 frame output valve. The "current" control should be set to read 95mA cathode current with a new 20P4 fitted.

#### ULTRA W84L

I wish to fit a 13-channel tuner to the above set. Can you advise me as to the type best suited and how to fit it into the television set?—G. Hammond (Edgware).

There is only one type of turret tuner which is immediately adaptable to your receiver. This is the Cyldon E162 which may be ordered through our advertisers. It is supplied with R.F. and mixer plugs which replace the R.F. amplifier and frequency changer 6F1 valves.

#### COSSOR 933

This set was repaired some time ago when a new line transformer and valve SU61 and 21A6 were fitted. When the set was switched on, it did not give a very clear picture as I had the aerial on a short pole but recently I had it placed on the chimney and the picture is still poor and can only be seen with the room light off. When I tried to adjust the receiver it developed a flash in the top right hand corner of the screen. This only happens when it has been switched on for about half an hour and continues to flash at intervals of about five minutes. When this happens there are sparks underneath the earthing clip on top of the tube.—V. Dowling (Hanley).

The main fault is similar to a faulty C.R. tube and we suggest that you check that you have not disturbed the ion trap magnet when repairing the set. The flashes can be due to a poor contact of the metal strip on the graphite coating or to flash-over inside the EHT box due to a faulty SU61 or ragged soldering of its wiring.

#### FERGUSON 968T/978T

This receiver has been giving interference in the form of corona discharge, but I cannot find any fault with it: the picture is good and the sound

perfect. When trying to trace the interference I placed alongside it a Murphy 240 and when the Ferguson was switched on there was corona discharge on the other set but this only lasted while my own set was warming up, but the Ferguson screen stays clear of corona discharge.—R. Godfrey (Chatham).

This is probably caused by poor insulation in the line output transformer causing internal corona (within the windings) during the line flyback. In this event, transformer replacement represents the only cure. However, also check the PL38 and PY31 valves.

#### H.M.V. 1826

After receiving normal sound and picture for five minutes the sound disappears completely. By switching off and on quickly it returns. For the next few minutes the process is repeated and the set will then settle down for the rest of the evening without further trouble.—C. Riches (S.E.20).

You should check the 0.1 $\mu$ F audio coupling capacitor under the R.F. unit (connecting to the screened cable which goes to the volume control) and the 0.022 $\mu$ F which connects to the noise limiter diode. In the June and July 1960 issues these were shown as C44 and C42 in "Servicing TV Receivers". Check the Z152 valves (including V9 on front left) and the 0.001 $\mu$ F capacitor between L15 and L16 if necessary.

#### PORTADYNE T237

When I switch on there is a curved black line about 3in. wide on the left side and a 2in. black line on the right. I have changed valves ECC82 and EF80 but the fault still persists. I would be pleased to have your comments.—A. Dyan (Romford).

You should check valves PY32 and PL81. If these are in order check the PY81 and the 120pF 6kV capacitor from the PY81 top cap connection to the width control.

#### VIDOR CN4225

The PY81 booster diode anode glows very red and at the same time the H.T. line voltage falls off to about 80. I have replaced the PL81 line output valve but the fault remains. I suspect that there is an H.T. short in the line output stage as the glowing in the PY81 ceases when I remove the PY81 top cap.—F. Erridge (York).

You will probably find that one of the leads passing through a hole in the chassis near the transformer and PY81, PL81 valve bases is touching due to its insulation having been impaired. This is not unusual on this model.

#### DECCA D17

The trouble is lack of width with correct height. I have changed the PL81, PY81, EY51 valves but with no improvement. Sometimes the picture creeps in or goes wider and adjusting the two metal rods that are under the line transformer helps. The set was not used for a week and on switching on the width was correct. I wonder if the line transformer needs replacing?—J. Pringle (Edinburgh 9).

We would advise you to replace the 14A97 metal rectifier which is on the front right side near the fuses.

#### BUSH TV33

Is it possible to replace a 14in. tube with a 17in?

The present tube in the set is a MW36-24 and as I have a MW43-69 to hand this is the tube I wish to use.—J. Wetherall (Newbury).

The electrical modifications are very minor; merely ensure that pin 7 is connected to pin 10 or to pin 11.

The snags are in the mechanical alterations necessary to accommodate the larger tube.

#### DYNATRON TV38

This set has developed a fault in vision and sound. There is no vision on ITV and the sound is weak. Vision on BBC is weak, moderate sound. Contrast control works from no picture to weak picture but any further advance of the control gives no further strengthening of the picture. This is a television receiver with F.M. sound. No sound is obtained on the Third Programme and it is just audible on the Home Service and weak on the Light Programme. I have checked the contrast variable resistor and the two 33k resistors soldered to it, they all seem satisfactory with an ohmmeter.—R. Beagle (London N.W.4.).

You should first check the tuner unit valves, 30L1 (PCC84) and 30C1 (PCF80). If both are in order, check the 27k resistor in the tuner unit connecting from H.T. via a choke and series 1k resistor to the front leaf connection or tag.

#### INVICTA 136

Frame linearity is causing me trouble with this set. The top is expanded and the bottom cramped and this cannot be rectified by the frame controls, only the top half of the raster responds sufficiently; the bottom half fails to open out enough.—H. Malton (Plymouth).

You should change the PCL82 frame output valve. This is on the rear of the chassis just behind the fuses, mains droppers etc.—to the left of the PY32 H.T. rectifier. If necessary check its 390 $\Omega$  cathode bias resistor (pin 2 to chassis).

#### McMURDO CR52

Sound and vision are good on this receiver but the brilliance or contrast is unstable. I have recently fitted a new 12in. tube to the set. The brilliance slowly increases with black horizontal lines following whites. Cutting back the brilliance corrects the picture, but I have to balance contrast frequently. I have changed 12AU7, 12AT7 and several EF91's and also the brilliance control.—W. Chester (Barnsley).

We are of the opinion that the new tube is defective and that the effect will gradually worsen until the brilliance will be excessive in the minimum position. The tube should therefore be returned to the suppliers before the expiry of the guarantee.


#### PETO SCOTT 17-22

Recently I replaced the PY81 valve because of severe arcing, then I replaced the PL81 because of a narrow picture. Another fault has now developed. When the set is switched on and allowed to warm up, the picture appears smaller than the screen with a 1 $\frac{1}{2}$ in. black margin around it, after a few minutes it fills up the screen but appears rather grainy and never in completely sharp focus.—C. Evans (Wolverhampton).

You should replace the PY32 H.T. rectifier and reset the ion trap magnet on the rear of the tube. If the picture is still unsatisfactory, check the PCF80 video amplifier and associated components.

# LAWSON

## DIRECT REPLACEMENT Reprocessed TUBES

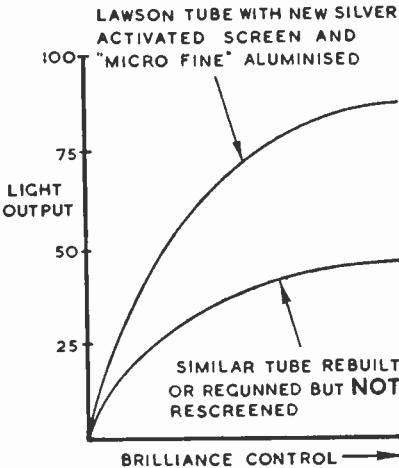

### FULLY GUARANTEED 12 MONTHS ENGINEERS WITH EXPERIENCE

Know that as a tube gets old, not only does it become Low Emission but the light efficiency of the Phosphor Screen also deteriorates (up to 10% per year). This deterioration of the Screen obviously continues if the tube is only rebuilt or regunned. Don't risk a "DEAD SCREEN", enjoy the brilliant crisp high definition of a LAWSON TUBE. Tubes which are absolutely BRAND NEW throughout (excepting the glass), and which incorporate the very latest CRT improvements. New silver activated screens, "micro fine" aluminising, high efficiency gettering, plus Brand New electron guns by Britain's premier manufacturers, Mullard, Mazda, Emiscope, Cossor, Brimar, Emitron, English Electric, etc.

ALL MAKES AND TYPES FROM STOCK

EXPRESS SERVICE—  
Orders received by 3 p.m. are dispatched same day.  
Special direct services to Scotland and Ireland.

**LAWSON TUBES LTD.**  
156. PICKERSLEIGH RD. MALVERN. Worcs.  
TEL. 3798

**12" - £4.10.0**  
**14" - £5.5.0**  
**15-17" - £5.15.0**

CARR. and INS. 7/6

C.O.D. or C.W.O.

10/-

Gladly refunded  
if you wish to return  
your old tube  
(excepting 12")

FOR THE FINEST, FASTEST SERVICE IN THE COUNTRY, CONTACT—

**D. & B. TELEVISION** Phone: Cherrywood 3865  
131a KINGSTON ROAD, SOUTH WIMBLEDON, S.W.19

OUR COMPREHENSIVE SERVICE INCLUDES:

12 CHANNEL TURRET TUNERS, 10, 16, 38 Mc/s, 40/-; VALVES, PCF80 and PCC84, 7/- each. Cabinets, Glasses, Masks, Condensers, Resistors, Ion Traps, Speakers.  
RECLAIMED C.R. TUBES (Not boosted or reactivated)  
9in. and 12in., 35/-; 14in., 50/-; 17in., 60/-. All picture tested taken from stripped TVs.  
REGUNNED C.R. TUBES (12 months' guarantee); 12in., 80/-; 14in., 90/-; 17in., 100/-.

EXAMPLE OF TRANSFORMER LIST

L.O.T. (New) (Used)		SCAN COILS (New) (Used)		P.YE. (New) (Used)		L.O.T. (New) (Used)		SCAN COILS (New) (Used)	
FERGUSON: 10T, 105T	89/9 35/-	KT36	8/6	PY32	10/-	V4, VT4, V7	52/8	35/-	55/- 35/-
92/2/4/8	89/9 35/-	KT98	15/-	PY80	8/6	VT7, CTM4	52/8	35/-	55/- 35/-

These are only examples of stocks, we have many thousands more, and would be pleased to quote for any component you may require.

We pride ourselves that we can obtain and supply any TV spare.

OUR GIGANTIC STOCKS INCLUDE: LINE OUTPUT, FRAME OUTPUT, SOUND OUTPUT, LINE AND FRAME BLOCKING, OSC. TRANS. AND SCAN COILS, FOR ANY MAKE OR MODEL TELEVISION. SOME OF OUR VALVES:

AZ31 8/8	ECP90 8/-	KT30C 8/-	PY31 7/-	U801 22/6	5V4 9/-	10P13 9/-
B36 5/8	ECH35 9/-	KT36 8/6	PY32 10/-	UAF82 8/-	5Y3 10/8	10P14 9/8
D7 3/-	ECH81 8/-	KT98 15/-	PY80 8/6	UBC41 7/9	5Z4 10/-	12AT7 5/6
DH77 4/6	ECL80 6/9	PCC84 7/-	PY81 6/-	UCH42 7/-	8AL5 3/-	12AU7 5/9
DK91 5/8	EF39 5/-	PCC89 8/6	PY82 8/6	UF41 8/8	8AM6 3/-	20D1 8/6
DK92 8/8	EF50 3/9	PCF80 7/-	PZ53 10/-	UF42 3/9	8CD8 27/8	20F2 8/6
DK96 7/-	EP90 4/8	PCL82 7/-	U22 8/6	UL41 7/3	6D2 3/-	20L1 12/6
DL92 5/9	EP91 3/-	U24 10/-	U24 10/-	UL46 7/3	8F1 5/-	20L2 9/8
DL94 6/9	EP92 5/-	PCL83 10/9	U25 12/-	UL44 11/8	8F12 3/-	20P1 10/8
DL96 7/8	EL33 8/6	U26 12/-	U26 12/-	UY41 8/8	8F13 7/-	20P3 12/-
EB91 3/-	EL38 14/8	PCL84 9/8	U31 9/6	UJ6 14/8	8F14 9/8	20P4 18/6
EBF80 9/6	EL84 7/-	PL33 2/6	U50 8/6	UJ8 8/8	8F15 9/8	27SU 14/-
ECC31 5/3	EY31SE 6/-	PL36 10/9	U52 7/-	SP41 2/3	6L1 12/6	30C1 7/8
ECC32 5/9	EY31SE 6/-	PL38 11/6	U191 9/-	SP61 2/3	6V6 5/-	30L1 7/8
ECC34 8/-	EY81 7/8	PL81 8/6	U281 9/-	W7 5/-	10F1 4/8	30P4 10/9
	EY88 7/8	PL82 8/9	U282 20/-	Z77 3/-	10C1 10/-	185BT 14/-
	EZ40 6/6	PL83 7/-	U301 20/-	304 5/-	10C2 13/-	

These are only examples of our valves: if you do not see what you require send stamped addressed envelope for special quotation.  
And that's not all—we ARE OPEN FROM 10 a.m. UNTIL MIDNIGHT.  
For any information or problems you have Call or Phone, we are always pleased to help.  
TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra.  
Postage on Valve 6d. each. C.R.T.'s 12/6 inc. Insurance.  
SATISFACTION ASSURED. RETURN POST SERVICE.

### FIRST-CLASS TELEVISION and RADIO COURSES GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

#### FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ. London, B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of

#### SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER  
150,000 SUCCESSES

NATIONAL INSTITUTE OF  
ENGINEERING  
(Dept. 462), 148 HOLBORN  
LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.  
Australia: P.O. Box 4570, Melbourne.

# "WAVE GUIDE AERIALS"

Manufacturers of TV Radio and Ham Transmitting Antennas wish to offer examples from their range of products. For the amateur Enthusiast and the Do-it-Yourself type.

## A SUPER HIGH GAIN ARRAY FOR THOSE DIFFICULT RECEPTION SPOTS

	£	s.	d.		£	s.	d.
3 Element BBC Folded Dipole, Channel 1, with a Double Five Channel 9 ITA, complete with all clamps ...	7	10	0	5 Element ITA Loft Aerial ...	1	6	0
or Double Eight Element ITA ...	8	10	0	8 Element ITA Aerial outdoor ...	2	9	4
Mast Equipment per your specification extra ...				Double 5 ITA Super Fringe outdoor Aerial ...	4	0	0
S/D 5 Combined BBC, ITA Loft Aerial ...	1	10	0	Double 8 ITA Super Fringe outdoor Aerial ...	5	0	0
S/D 5 Combined BBC, ITA Outdoor Aerial, wall mounting, complete ...	2	13	6	32ft. Garden Masts, complete for erection, two sets guy pickets, etc., with fitting instructions ...	12	10	0
H & 7 combined BBC, ITA with chimney lashing equipment ...	4	13	0	Coax Cable semi low loss, 7d. per yard; super low loss 1/2d. per yard.			
BBC Loft Aerial ...				Cross over boxes for combining separate BBC and ITA Aerials 9/6d.			
V.H.F. Loft Aerial ...				Please send 6d. stamp for full list of aerials and accessories. Terms C.W.O. orders over £4 post and packing free.			
5 Element ITA Aerial for attaching to existing mast ...	1	10	0				

PLEASE STATE CHANNELS REQUIRED WHEN ORDERING

### WAVE GUIDE AERIALS

MIDLAND BANK CHAMBERS, FORE STREET, HERTFORD

# "TELFAC"

## Regunned TV Tubes

Supplied from stock and despatched per British Railways SAME DAY. COMPLETE NEW GUNS fitted in every tube and fully guaranteed for TWELVE MONTHS.

	Mullard	Mazda
12 in. ...	£4. 0. 0	£4. 10. 0
14 in. MW ...	£4. 10. 0	£5. 0. 0
14 in. AW ...	£5. 0. 0	£5. 0. 0
15 in. 2 Volt ...	£5. 10. 0	£5. 0. 0
15 in. 12 Volt ...	£5. 0. 0	£5. 0. 0
16 in. ...	£5. 10. 0	£5. 0. 0
17 in. MW ...	£5. 0. 0	£5. 0. 0
17 in. AW ...	£5. 10. 0	£5. 10. 0
21 in. MW ...	£6. 10. 0	£6. 10. 0
21 in. AW ...	£7. 0. 0	£7. 0. 0

MW=Magnetic Focus  
AW=Electrostatic Focus

Plus 10/- for Carr. & Ins.

Other types not listed available. Please contact:—

## J. P. WRIGHT

Television Factors

103 Carr House Road, Doncaster

Sole Distribution Agent

Phone: DON 2636

# VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS IR5, IS5, IT4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 .. Set 4 for 19/6  
DAF96, DF96, DK96, DL96 .. .. .. .. 4 for 27/6  
6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 5Y3G .. .. .. 5 for 24/6

1A7GT 11/6	6F1 13/6	35A5 14/-	ECC82 6/3	EZ91 7/-	U24 17/6
1D5 8/-	6P25 9/-	35L6GT 9/-	ECC83 7/-	FW4/500 8/-	U25 13/-
1N5GT 10/-	6Q7G 0/-	3Z4GT 6/9	ECC84 8/9	GZ30 8/6	U26 10/-
1N5GT 10/-	6Q7GT 0/6	3Z5GT 8/6	ECC85 8/3	GZ32 9/6	U50 6/-
1R5 5/6	6SL7GT 6/3	50L6GT 8/9	ECC80 8/6	KT33C 7/-	U52 4/6
1S4 8/-	6SN7GT 4/9	ACTH1 16/9	ECC82 8/6	KT41 11/6	U78 4/9
1S5 5/3	6U4GT 11/-	AZ31 9/6	ECH21 13/6	KT44 8/6	UABC80 7/9
1T1 3/6	6V6G 5/-	B36 8/6	ECH35 6/3	KT61 10/-	UF42 9/-
1U5 5/9	6V6GT 6/8	CL33 12/3	ECH42 8/9	KT63 6/6	UB41 8/6
3A5 9/-	6X4 4/9	DAC32 10/-	ECH81 8/-	MU14 7/6	UBC41 7/6
3Q4 7/-	6X5GT 5/-	DAF91 5/3	ECL60 7/6	MX40 9/8	UBF80 8/9
3S4 6/-	7B8 4/9	DAF96 7/6	ECL82 9/6	N18 7/-	UBF89 9/-
3V4 7/-	7B7 7/6	DCC90 9/-	EF39 4/6	PC95 10/-	UC92 12/6
504G 4/8	7C5 7/6	DF33 10/-	EF40 12/6	PCC84 7/6	UCC84 12/9
5V4G 8/-	7C8 7/6	DF91 3/6	EF41 8/3	PCC89 11/-	UCC85 7/6
5Y3GT 6/-	7H7 7/6	DF96 7/6	EF42 9/6	PCF90 7/9	UCF80 14/-
5Z4G 7/9	7S7 7/6	DH6 4/9	EF80 9/6	PCF92 7/9	UCH21 13/6
6A1S 3/6	7Y4 7/-	DH7 6/9	EF85 5/6	PCF96 14/-	UCH42 8/6
6AM6 3/6	10C2 17/6	DK32 11/6	EF88 9/9	PCL92 9/-	UCH81 8/-
6AQ5 9/-	10P13 14/6	DK91 5/6	EF89 7/9	PCL83 11/6	UCH82 10/9
6AT6 6/9	12A76 7/-	DK62 7/6	EF91 3/6	PCL84 7/6	UCL83 13/3
6BA6 6/-	12A77 5/-	DK92 4/3	EF92 4/3	PCL85 13/6	UF41 8/9
6BB6 5/9	12A7GT 6/3	DL33 9/-	EF183 14/3	PEN44 11/-	UF42 5/6
6BB6 5/9	12A7 7/-	DL35 9/6	EL33 10/-	PEN36C 8/-	UF85 8/6
6B36 6/9	12K7GT 5/3	DL32 8/-	EL41 8/6	PL36 11/6	UF89 7/9
6B93 8/-	12K8GT 11/6	DL34 7/-	EL42 9/9	PL81 9/8	UL41 8/-
6CD6G 26/9	12K7GT 7/6	DL84 7/6	EL84 7/6	PL82 7/9	UL84 7/6
6F1 12/6	12Z3 7/6	EABC80 7/-	EM34 6/9	PL83 7/8	UL84 7/6
6F6G 6/6	14S7 18/6	EAF42 8/6	EM80 8/6	PL84 10/-	UU6 13/6
6F13 11/-	20F2 17/6	EB91 3/9	EM81 8/6	PY32 11/-	UY21 13/6
6F14 16/6	20L1 17/6	EB92 5/-	EM84 10/-	PY80 7/6	UY41 6/6
6K7G 2/6	25A6G 8/-	EB94 8/-	EY51 7/3	PY81 6/9	UY85 6/6
6K7GT 5/-	25L6GT 7/9	EBF41 8/-	EY84 10/-	PY82 6/6	VP4B 9/6
6K8G 9/3	25Z4G 7/6	EBF89 8/9	EY86 7/9	PY83 7/9	VP41 5/-
6K8GT 6/6	25Z6GT 9/8	EBL21 13/6	EZ40 6/9	PZ30 17/-	WF6 5/3
6L13 10/3	30L15 11/-	ECC40 15/-	EZ41 7/-	T41 9/6	W77 4/6
6LD20 8/-	30P12 7/-	ECC81 5/-	EZ80 6/3	U22 7/3	Z77 3/6

# READERS RADIO

24 COLBERG PLACE, STAMFORD HILL, LONDON, N.16 STA. 4587

Post 6d. per valve extra.

Any Parcel Insured Against Damage in Transit 8d. extra.

Any C.O.D. Parcel 3/- extra.

**ENGLISH ELECTRIC T.41**

I had an open-circuit in the H.T. (not EHT) winding of the line output transformer of my set. This proved to be easily located and I effected the repair myself but on re-assembly find extreme cramping on the right-hand side of the picture. I feel this is due to not knowing the correct gap to introduce when fitting the ferrite core back into place. If you consider this to be so I would be grateful for your advice and suggestions to any other possible causes of their non-linearity. PY81 and PL81 valve changes appear to have no beneficial effect.—C. Carter (London W.3.)

If the cramping was not there previously it would appear that the transformer has been incorrectly reassembled. The gap should be closed as much

as possible but this is not unduly critical. Shorted turns are a distinct possibility and it may be necessary to replace the transformer.

**MURPHY V200**

This is a second-hand receiver to which I fitted a new tube, 12/B. The raster is good and all controls work but there is no picture and flyback lines are visible. The sound is working perfectly.—W. Glover (Darfield).

Your trouble could be anywhere in the vision I.F. stages which are on the bottom left chassis as viewed from the back and which run from front to back along the edge closest to the tube. The regular faults to cause no vision are the burning out of the 10k video amplifier anode load, and a break in the contrast control.

**A TV VALVE TESTER**

(Continued from page 609)

cathode bias feeds are taken to three terminals on a panel at the rear of the instrument. A fourth terminal is connected direct to chassis.

Heater supplies consist of 4V, 5V, and 6.3V windings, taken to three pairs of terminals on the rear panel. Approximately 12V can be obtained by linking the 5V and 6.3V winding in correct phase. This is marked on the panel. An additional winding for higher heater voltages was considered but this was found unnecessary when the tester was put to use.

Seven common valve bases are wired in parallel—the nine wires from the bases are fitted with spade terminals which are then connected to the appropriate supply voltages.

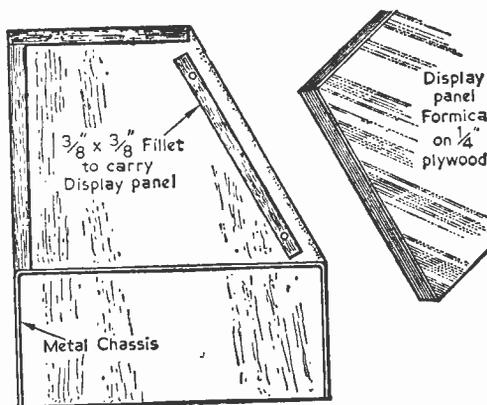


Fig. 2.—Construction of the case and front panel.

**Using the Tester**

The necessary base connections and data are obtained from a valve data book. The heater leads are connected to the corresponding voltage terminals and the lead from the correct pins to the anode, screen and bias terminals. All other leads

are clipped on to the chassis terminal. Switch on, and set up voltages as given in the valve data. The bias can be varied to test Gm of the valve and the readings checked from the data.

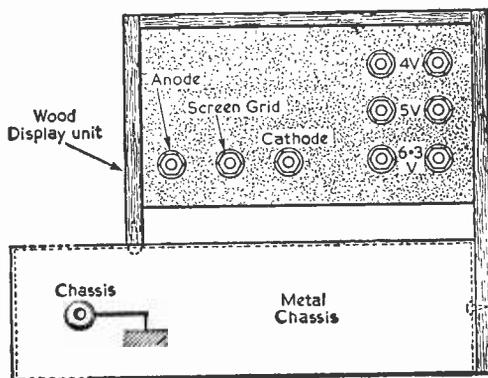


Fig. 3.—Rear view of the terminal panel.

**Constructional Details**

The chassis is an old radio chassis which was very conveniently drilled with several holes for bases in a small area. The chassis size was 12in. x 5½in. The display unit (Fig. 2) consists of a small hardwood box, one side of which sits on top of the chassis and is screwed from underneath, and the other longer side is screwed on the end of the chassis. The display panel with meters and controls is removable, and is made of ¼in. ply covered with a suitable material, and measures 6¼in. x 5½in. It rests on two small bearers glued to the sides of the box (Fig. 2). A signal lamp of the midget variety is set in the panel between the meters. The mains on/off switch is affixed to the horizontal chassis.

**QUERIES COUPON**

This coupon is available until SEPTEMBER 22nd, 1961, and must accompany all Queries sent in accordance with the notice on page 627.

PRACTICAL TELEVISION, SEPTEMBER, 1961.

**SETS & COMPONENTS**

**TELEVISION TUBES!** 1st quality, new guns. Year's guarantee, most 75/- exchange. Rescreened from 85/- 3 Park Ave., New Barnet. BAR 1934.

**REBUILT TELEVISION TUBES—12in.** £5; 14in. £5/10/-; 17in. £8/10/-.  
Twelve months' guarantee. 10/- carr.  
**TRANSISTORS, WHITE SPOT 5/-; RED SPOT 5/-; YELLOW/GREEN 5/6; RED/YELLOW 7/6; CRYSTAL DIODES 1/-, 2/-, 4/6. ELECTROLYTICS,** all values; **CONDENSERS,** silver and paper. **RESISTORS,** all types; **RECLAIMED VALVES,** most types. 5/- each. **AIRSPACED CO-AXIAL CABLE** from 6d. per yard. **BRAYHEAD TURRET TUNERS** £6/19/6; **REPLACEMENT VOLUME CONTROLS, TRANSFORMERS, TELEVISION AND MAINS; SMALL PARTS REPLACEMENTS** and numerous **SECOND HAND COMPONENTS.** Stamped, addressed envelope please with all enquiries.

**DEVICES TELEVISION SERVICE**  
29-30 The Nursery, Bath Road,  
Devises, Wilts. Tel.: Devises 1100.

**B.V.A. NEW** and rebuilt TV tubes. S.A.E.: **REDWATT TUBE DISTRIBUTORS,** 41 Denmark Street, Wakefield, Yorks.

"**HEATHKITS**" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.,** Dept., PT/22/8, 138 Lewisham Way, S.E.14. Tideway 6666.

**In Scotland . . . . .**  
**RENVUE**  
**for Better Value**

**COMPLETELY REPROCESSED TUBE**  
(**NEW GUN, RESCREENED, ALUMINISED**)

- 12.6v. and 6.5v. 0.3 amp., 17 and 15in. Types ... .. £6.10.0
- 12.6v. and 6.5v., 0.3 amp., 14in. Types ... .. £6. 0.0
- 12v., 15in. Types ... .. £7. 0.0
- 2v., 12 and 15in. Types ... .. £6. 0.0

Electrostatic 90 degree and 110 degree tubes 10/- extra. Carr. paid.

**10/- ALLOWED ON OLD TUBE**  
Terms arranged.

**FERGUSON**

- 14in. BBC and STV Consoles ... £12.10.0
- 14in. BBC and STV Receivers ... £10.10.0
- 17in. BBC and STV Receivers ... £19.0.0

**COMPLETELY OVERHAULED AND FITTED WITH COMPLETELY REBUILT TUBE**  
with One Year's Guarantee

£5 Deposit. Terms on Balance

**Renfrew Electronics Ltd.**  
**Anderson Drive**  
**Renfrew : Scotland**

Tel.: Renfrew 2642

**RATES:** 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television" Tower House, Southampton St., London, W.C.2.

**SETS & COMPONENTS**  
(continued)

**TV SPARES**

**LINE OUTPUT TRANSFORMERS**

A few examples from our extensive range.

TELEPHONE ORDERS SENT SAME DAY C.O.D.

- Alba T301, 304, 394, 484, 494, 42/6.
  - Alba T321, 324, 424, 524, 39/6.
  - Baird 164/5/7, 172/5, 181/2/5, 62/6.
  - Baird P201/4/7, P211/4/7, 58/6.
  - Baird B112/4/7, 124, 412, 436, 65/-.
  - Bethoven B77, 80, 94-9, 106-9, 65/-.
  - Bush TV53, 69/6; TV24C, 89/6; TUG34, 5 gns.
  - Cosor 930-9, 58/6; (new) 30/- (used).
  - Decca D14/17, 58/6; DM14/17, 55/-.
  - Ekco T221, 231, 311, 284, 330, 55/-.
  - Ekco T161, TC162, TC166, TU169, 30/- (used).
  - Ferguson 992/6/8 66/9; (new) 30/- (used).
  - Ferguson 205-246; 66/9; 306/8, 58/6.
  - Ferranti 14T3/4/5, 47/6; 14T2/T1225, 62/6.
  - Ferranti T1002/5, 55/-; T129-138, 47/6.
  - G.E.C. BT, 1251/2, 1746/8, 2250, 50/-.
  - H.M.V. 1824/9, 1840-8, 2805-5902, 69/6.
  - K.B. NF 70/FM, MV/OF 100, PVP20, 75/-.
  - Masteradio T917, TE7T, T409/12, etc, 58/6.
  - McMichael TM/C/CR 51-2, 55/-; C/R 53 75/-.
  - Murphy V 240/250/280, 65/-; V200, 49/6.
  - Pye/Pam/Invicta V4/7, VT4/7, LV30, FV1 908-958, T118-120, 55/- CS17 etc, 75/-.
  - New Scan Coils on all above 65/-.
  - Peto-Scott TV122/4/6, 67/6; TV1411, 72/6.
  - Philco 1457-67, 1717-47, 1753-77, 87/6.
  - Philips 1114U, 1115, 1437, 1446, 89/6.
  - Philco CV76, 77, 84, 87, etc, 65/-.
  - TV 94, 89/6.
  - Portadyne TA 17, T237, T417, used 39/6.
  - R.G.D. C55, 1455/6, 1755/6/7, etc, 89/6.
  - Ultra VT9-17 etc. with U25 5 gns.
  - Vidor CN4206-12, 59/6; CN4217-31, 65/-.
- We stock or can obtain most L.O.T.'s, Scan Coils, Frame O.P.'s, and spares.  
PLEASE SEND S.A.E. FOR IMMEDIATE QUOTE.

Callers welcome. Open all day Saturday. Terms C.V.O. or C.O.D. Add 2/6 P. & P.

**NEW TV BARGAINS**

We have a limited number of 1962, Slim line Television Receivers by famous Makers at special prices. For example 17 inch, List 57 gns. Our Price 44 gns., plus 25/- Carr. & Ins., 110 Tube, Printed Circuit. Contemporary Styling, AllChannels. Full guaranteed. All in sealed boxes. Immediate despatch on your order.

**TELEVISION CONSUMER SERVICES LTD.**

**112 CAMBERWELL RD., S.E.5.**  
RODney 7917

**SURPLUS, AND NEW VALVES** guaranteed. S.A.E. for list. Also Reclaimed Valves, tested perfect; 5/- maximum plus 6d. postage each. Genuine Valve bargains. Valves bought: Lewis, 46, Woodford Avenue, Ilford, Essex.

**SETS & COMPONENTS**  
(continued)

**C. EDWARDS**

**1070 Harrow Rd., London N.W.10.**  
Ladbroke 1734.

500 S/H TV Sets must be cleared as taken part exchange. Condition unknown.

**ALL SETS COMPLETE**

- 12in. BBC 25/- 13 Channel 50/-
  - 14in. " 50/- " " 75/-
  - 17in. " 85/- " " 125/-
- Plus 15/- carriage.

**Guaranteed Values**

- 10C2 10/-, 20D1 6/-, 6K25 8/-,
- PL38 10/-, PL81 8/-, PY81 8/6,
- PY80 7/6, PZ30 10/-.

**TUBES-AERIALS-VALVES**

Regunned tubes, guaranteed one year, full range of aerials and fittings. I.T.V. boosters, valves, brayhead tuners. TV sets, transistor radios and all electrical appliances. Co-axial cables and house wiring cables, fluorescent fittings. All quotations without obligation. Special terms to the trade, and Home Engineers. S.A.E. for Catalogue.

**G. A. STRANGE**

**BROADFIELD, NORTH WRAXHALL,**  
Nr. Chippenham, Wilts. Tel. Marshfield 238

**Television Tube Shop**

now stock

**Tubes for every make of set**

**OVER 600 TUBES ALWAYS IN STOCK**

- 12 inch Mullard type ... .. £4. 5.0
- 12 inch Mazda type ... .. £4.15.0
- 14 inch Mullard type ... .. £5. 5.0
- 14 inch Mazda type ... .. £5.10.0
- 15 inch Mazda type ... .. £5.15.0
- 16 inch G.E.C. & Mullard type ... £4.12.6
- 17 inch Mazda & Mullard type ... £6.10.0
- 17 inch G.E.C. & Brimar type ... £6.15.0
- 21 inch Mullard type ... .. £8. 0.0

Add 10/- for insured carriage to your door within 48 hours, or 5/- via B.R.S.

All tubes tested before despatch and guaranteed for 12 months. Guarantee cards enclosed with each tube.

**Special Purchase of 110", 17 inch tubes—**  
Slight mark, Guaranteed for 12 months.  
Mazda CME 1703 } replace AW43-88, £6.  
GEC 7405A }

**Shop Soiled Tubes.**  
(Slight scratches or marks) Guaranteed 12 months. Ideal for second set. 12in. 3/18, 3/31 37/6, MW31-74 50/-, 14in. MW 36-44 52/6, CRM141 55/-, 17in. CRM171, MW 43-64 60/-. Others available from time to time. Please enquire.

**Service Engineers**  
Our Rebate Scheme shows real savings—send for details.

**TELEVISION TUBE SHOP**

**48 Battersea Bridge Road, S.W.11**  
BAT 6859  
Just South of the Bridge. Open Saturdays.

**SALVAGED VALVES TESTED ON A MULLARD HIGH SPEED VALVE TESTER TO 100% STANDARD**

AS0N 2/6	POTENTIOMETERS
AC0P 2/6	Carbon Res. 25k .. 1/- ea.
AC044 2/6	VIC and SP. SW. 500k .. 2/6 ea.
AC0PT 2/6	RESISTORS
DU 2/6	Card of 1/2W Resistors, 72 Per
APV4 2/6	values covers complete card
AZ31 2/6	10% range .. .. 24/-
B36 2/6	Full range of Separate Resistors
B55 2/6	available.
D1 2/6	CONDENSERS
D68 2/6	100µf + 200µf 275 v. D.C. 9/-
D77 2/6	100µf 350 v. D.C. .. 7/6
DD1 2/6	3µf 450 v. D.C. .. 2/3
DD4 2/6	15µf 350 v. D.C. .. 3/-
DDL4 2/6	100µf 15 v. D.C. .. 2/-
DF91 2/6	0.1µf 500 v. D.C. Paper .. 1/-
DH77 2/6	0.01µf 500 v. D.C. Paper .. 10d.
DK96 2/6	0.001µf 500 v. D.C. Paper 10d.
DW4/3502/6	VARIABLE CONDENSERS
EASA 1/3	0.0005 Double-ganged tuning 3/6
EB34 1/3	3-50µf concentric trimmers 3/- doz.
EB41 1/3	Banks of six compression
EB91 2/6	trimmers 3-30µf .. 6d.
EB033 2/6	VALVE HOLDERS
EB21 2/6	American Octal .. 5/- doz.
ECC32 2/6	Noval .. .. 9d. ea.
ECC34 2/6	METAL RECTIFIERS
ECC81 4/-	RM4 New and Boxed 15/- ea.
ECC82 4/-	RM4 Strapped .. 5/- ea.
ECC83 2/6	Silicon Type—
EF50 1/3	250v. 300mA, dia. 8", L17/32 20/-
EF90 2/6	125v. 300mA, dia. 13/32 .. 10/- ea.
EL91 1/3	H/32 .. .. 9d. ea.
EL93 2/6	CRT Converter Cap. .. 9d. ea.
EL1DD2/6	Standard Crocodile Clips .. 6d. ea.
KT330 1/3	Miniature Crocodile Clips .. 6d. ea.
KT42 2/6	1 1/2in. Brown Knobs .. 6d. ea.
KT61 2/6	Igranite Jack Plugs .. 4/6 ea.
KT741 2/6	CATHODE RAY TUBES
L65 2/6	SPECIAL OFFER
M24 2/6	16in. G.C. 6901 .. 80/-
MSP4 2/6	12in. G.E.C. 7192 .. 10/-
N30 2/6	Salvaged out good tubes.
P41 2/6	Personal Callers Only.
P81 2/6	55W/50s and 10M/50s TURRET
PC084 4/-	TUNERS, less valves taken from
PCF84 4/-	sets .. 12/6 ea.
PCL82 4/-	TRANSFORMERS
PEN45 1/3	CRT Boost Transformers 12/6 ea.
PEN48 1/3	Heavy Duty Output Trans-
PENDD 2/6	formers, 6 ratios from 13 : 1
4020 2/6	to 43 : 1 .. 25/- ea.
PL33 2/6	Miniature Output Trans-
PL31 4/-	formers, Multi-match 10/- ea.
PL32 4/-	formers, Multi-match 10/- ea.
PL33 4/-	Transistor Drivers: 1-1 CT 10/- ea.
PY31 2/6	3.0-1 CT 12/6 ea.
PZ30 4/-	Transistor Output: 3.0-1 CT 10/- ea.
SP41 1/3	0.2-1 CT 10/- ea.
SP42 2/6	Microphone Transformers,
SP91 1/3	ratio 65 : 1 .. 35/- ea.
TD130 2/6	I.F. TRANSFORMERS
TN2320 2/6	Standard 405kc/s .. 12/6 per pair
TP2920 2/6	Midge 405kc/s .. 18/- per pair
U1 2/6	AUTO TRANSFORMERS
U21 2/6	250W .. 67/6 ea.
U42 2/6	100W .. 27/6 ea.
U47 2/6	50W .. 20/- ea.
U7 2/6	TRANSISTOR FAULT FINDER
V57 2/6	Enables faults to be located
VP18 2/6	quickly. Consists of a two-
VP47 2/6	transistor, multi-vibrator in a box.
W77 2/6	Complete with battery. 32/6
X91 2/6	VALVES, New and Boxed 10/- ea.
X92 2/6	CRYSTALS
Z66 2/6	GENUINE MULLARD, Boxed
Z70 1/3	0A5 2/-, 0A1 3/-
Z71 2/6	0A70 0A45 3/-
Z84 2/6	0A79 3/-, 0A91 3/6
ZTP 2/6	TRANSISTORS
6AL5 2/6	GENUINE MULLARD, Boxed
6AM6 1/3	OC16W 48/-, OC75 8/-
6BW7 2/6	OC19 48/-, OC72 8/-
6BX3 2/6	OC26 25/-, OC75 8/-
6C8 2/6	OC43 11/-, OC78 8/-
6D2 2/6	OC45 10/-, OC81 8/-
6D3 2/6	OC70 8/6, OC82 12/6
6D4 2/6	OC71 8/6, OC170 17/6
6F13 1/3	10 WATT HI-PI AMPLIFIER KIT
6J5 2/6	instor valves from our salvage
6J7 2/6	range. Complete with treble and
6P25 2/6	base unit. Inc. valves. 27.9s
6P26 2/6	TERMS: C.W.O. ONLY.
8D3 1/3	Orders under £1, P. & P. 1/-.
9D4 2/6	Open till 11 pm. most days.
10F1 2/6	S.A.E. for list or 9d. for full catalogue.

**SETS & COMPONENTS**  
(continued)

**GUARANTEED VALVES**

11A 2/6	12AT7 6/6	EF91 3/-
6F1 6/6	20D1 6/6	EL32 3/-
6F13 5/6	26Z2 7/6	PCU34 6/6
6F14 7/6	20L1 8/6	PY80 6/6
6F15 7/6	177 3/6	PY82 6/6
10C1 7/6	FB08 7/6	UF41 7/6
10F1 6/6	FA80 5/-	UL46 7/6

Postage 6d. each. List 3d.

**SERVICE SHEETS**  
List 6000 Models. 1/-, S.A.E. Enquiries.  
Hamilton Radio (7), 13 Western Rd.,  
St. Leonards, Sx.

St. HELENS 4246 for Television tubes.  
S.A.E. list. DARWINS. 45 Shaw St.,  
St Helens Station, Lancs.

**H.P. on Regunned C.R.T.s**  
At No Extra Charge  
12 Months' guarantee

12" & 14" .. £3.10.0  
17" .. £4.10.0  
21" .. £5.10.0

Phone or Call only:  
Rod 7778  
**P. J. F. Andrews**  
61-63 ROSEMARY RD.  
LONDON, S.E.15

**FOR SALE**

**VALVE CARTONS** at keen prices.  
Send 1/- for sample and list. J. & A.  
BOXMAKERS, 75a Godwin Street,  
Bradford 1.

**TV's FOR SALE**

Examples BBC/ITA	C.R.T.
In good working order	Good Rebuilt
14in. Ultra VHS15: KB LVT 30	£17 £21
14in. Ekco T201 or T283 ..	£19 £22
14in. Ferguson 392 ..	£14 £18
17in. Plessey: RGD etc. ..	£19 £24

Send for Lists. (Carr. Paid.)

**CADMANS**

Bryan Street, Hanley.  
Phone: Stoke-on-Trent 23567.

**1,000 TELEVISIONS**, all makes, from  
£3 working, 10/- not. Callers only,  
9 till 6 including Sats. 39 White-  
house Lane, Steppney, London.

**Star TV Tubes**  
70/-

all sizes up to and including 17in. includes  
old glass or plus 7/6 without  
C.W.O. Carriage 7/6.

**WHY PAY MORE?**  
new guns, 12 months' guarantee.  
also 20/- each  
12in., 14in., Part Exchange Televisions.  
Callers only.

**ARTHUR SLARK**

43-45 Thicketford Road, Tonge Moor,  
Bolton.  
Phone: 26684.

**LINE OUTPUT TRANSFORMERS**  
**SCAN COILS SPECIALISTS**

Makes	Models	Prices
ACE:	Spares available.	
ALBA:	T301, T304, T394, T464, T494, etc. ..	80/8
AMBASSADOR:	Spares supplied.	
ARGOSY:	Most models available.	
ARMSTRONG:	Spares supplied.	
BAIRD BANNER:	BETHOVEN: Spares supplied.	
BUSH:	TV11A, 11B, 12A, 12B, TVG12A, 12B, TRG12A, 12B TVG26, TV32, TV38, TVG34, TVG34A, T36, TV36, TVG36 TV39C, VTG36C, TV43 ..	45/-
	TV53, TV56, T57, TV57, Rew'd TVG58, TV62, TV63, TV66, only TV67, etc. ..	80/8

**COSSOR:** 930 & T, 981, 933-4-5, 987,  
928, P, 935 & A & .. 59/6  
943T, 940-46, 945, 945B, 949 69/8

**CHAMPION, COLUMBIA:** Spares supplied.  
**DIT & C** .. 69/6  
DM1, DM2C, DM3, DM4/C .. 65/-  
DM5, DM14, DM17, 444, 555 .. 65/-  
TR144, TR173 .. 59/8

**DEFIANT:** Spares supplied.  
**DYNATRON:** Spares supplied.  
**EYKON:** T593, TC8102, TS105, TR114  
TRC124, TC138, TR188,  
TR189 .. 55/-

**ENGLISH ELECTRIC/ETRONIC:** Spares supplied.  
**FERGUSON:** 103T, 105T, 113T, 135T,  
145T .. 60/6  
941T-953T inclusive .. 59/6  
991T-997T inclusive .. 58/8  
203T-240T inclusive .. 60/6  
300T, 307T .. 56/-  
FERRANTI: T173, 14T3P, 14T4 .. 45/-  
17K3 & F. 17T3 & F. .. 45/-  
17K4 & F. 17K4 & F. .. 45/-  
17T4 & F .. 45/-  
14T6, 17SK5, 17K5 .. 45/-

**G.E.C.:** BT1251, BT1252, BT1746,  
BT1748, BT4743 .. 49/6  
BT4643, BT5147, BT5246-48 .. 89/8  
BT5348-BT5643B inclusive .. 89/8  
and 89/6

**H.M.V.:** 1824 & A to 1831 inclusive .. 87/6  
1840, 1841, 1842-1848 .. 87/6  
T118, T119, T120 .. 65/-

**INVICTA:** All other models available.  
LFT50, LVT50, LFT60,  
MV60 .. 107/8

**K.B.:** All models available, etc.

**MARCONI:** All models available.  
**MASTERADIO:** All models available.  
**MICHAEL:** All models available.

**MURPHY:** V200, V202C .. 57/6  
V240, V250 .. 95/-

**PAM, PETO SCOTT, PHILCO:** All models available.  
**PHILIPS:** 1705U, 2168U .. 105/-

**PILOT:** All models available.  
**PORADYNE:** All models available.

**PYE:** CFM4, PV4C, PV40UL .. 55/-  
V4, VT4, VT, VT7 .. 55/-  
LV30, PV1, PV10C .. 69/6  
CW17F, CFM17F, CW17 .. 69/6  
CW17C, CW17CF, CW17F,  
etc. .. 69/6

**RAYMOND:** All models available.  
**REYBONTE:** All models available.  
6017T, 7017, C34, etc. .. 59/6

**SOBEL:** All models available.  
TS17, T346 .. 85/-

**STELLA:** All models available.  
ST6721U .. 105/-  
ST8617U, ST8621U .. 105/-  
ST8917U .. 105/-

**STRAD, TELEVOICE, TRUVIEW:** Available.  
**ULTRA:** All series, S1 series, with  
U25 etc., complete .. 79/6

**VALRADIO:** Spares available.  
**VIDOR:** CN4217-CN4231 inclusive .. 65/-  
**WESTMINSTER:** Spares available.  
**WHITE-IBBOTSON:** Spares available.  
Scanocils. Osc. and Output Tra. for all above makes  
available.

Post and Packing 2/6. C.O.D. 8/- extra.  
All Enquiries S.A.E.

**WYNSOR TELEVISION**

Dept. P.T.  
ST. ALBANS RD., BARNET, HERTS.  
BA8 1769

**Arion Television**  
4 Maxted Road, S.E.15 NEWX 7152  
23 Northcross Road, S.E.22.

**FOR SALE**  
(continued)

**100 BAYS** of brand new adjustable Steel shelving, 72in. high by 34in. wide by 12in. deep. stove enamelled dark green. Sent unassembled. Six shelf bay—£3/15/0. Sample delivered free. Quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

**ALUMINIUM LADDERS/STEPS.** Gigantic offer, 400 models. SANCO LTD., 17 (P.T.) Boundary Rd, Hove.

**TURRET TUNERS**

BRAYHEAD £3.19.8

Brand New, any area, complete with fitting instructions. State set and 2 channels, 10 M/c only. EXTRA COILS 10/6 per channel.

**METAL RECTIFIERS**

RECTIFIERS—CONTACT COOLED.

14RA1283 (PC10), type 250 v., 250 mA, 15/6;  
14RA1283 (PC31) type, 250 v., 300 mA, 17/6;  
350 mA, 19/6.

RECTIFIERS—FIN TYPES

Equivs. for RM4 250 v., 250 mA, 14/-; RM5 250 v., 300 mA, 17/6; 14A989 400 mA, 18/6;  
14A86 18/6; 14A87 20/-; 14A100 22/6 14A124 22/6; LW7 20/6.

**CABY MULTIMETERS**

All 16 ranges, £4.17.8; B20 - 20 ranges, £6.10.0. S.A.E. for full details.  
Cash with order, Post Free. C.O.D. 2/6.

**DURHAM SUPPLIES**

175 Durham Road, Bradford 8, Yorkshire.

**WHY PAY ridiculous prices?** Try our special tuner cleaner, suitable for cleaning and lubricating all tuner and switch contacts, ideal for volume controls, etc. Sample dispenser approximately 1/2 gill 9/6 C.W.O. REDLEA, West Main Street, Darvel, Ayrshire.

**SERVICE SHEETS**

**SERVICE SHEETS**, Radio, TV, 5,000 models. Lists 1/- S.A.E. enquiries: TELRAY, 11 Maudland Bk., Preston.

**FAULTFINDER FILES (TV)** showing common faults that each receiver is prone to and other useful servicing information. 2/- each. List 9d., plus postage. S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

**SERVICE SHEETS (1930-1961)** from 1/- with Free Fault-Finding Guide. Catalogue 6,000 models 4/-. 125 Radio/TV Sheets covering 370 popular models 20/-. S.A.E. enquiries: HAMILTON RADIO, Western Road, St. Leonards, Sussex.

**SERVICE SHEETS** — We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- each. Why tolerate delay in obtaining your supplies when we will dispatch by return? Service Sheet List 1/-. Also Manufacturers' Manuals for sale and hire. 1961 List now available 1/- S.A.E. please. Mail orders only to: S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

**SERVICE SHEETS**, Radio and TV 4/- each. List 1/-. All orders despatched on day received. Also manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

**SERVICE SHEETS:** also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20 Extension, Shepherd's Bush Market, London W.12 (Phone: SHE 3052).

**WANTED**

**WANTED** Service Sheets. No quantity too large, highest prices paid. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

**NEW VALVES WANTED** — EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. DURHAM SUPPLIES, 175 Durham Road, Bradford 8, Yorkshire.

**TELETV and RADIVET** wanted, must be in good condition and p.w.o. address N. Ireland. Box 28.

**A PROMPT CASH OFFER** for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., Beverley House, Manville, Terrace, Bradford 7.

**EDUCATIONAL**

**"HOW AND WHY"** of Radio and Electronics made easy by a new, non-maths practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from Dept. 12, P.T. RADIOSTRUCTOR, Reading.

**Radio  
Television  
& Electronics**

Learn at home with the world's largest home study organisation. Brit. I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for **FREE** prospectus stating subject to

**I.C.S.**

Dept. 516  
Intertext House, Parkgate Road,  
London, S.W.11.

**FREE FROM THE I.P.R.E.** Syllabus of famous radio and TV courses. Membership Condition booklets, 1/-. Sample copy the Practical Radio Engineer 2/- post free. Secretary, 22 Fairfield Road, London N.8.

★ **LEARN** ★  
**RADIO & TV  
SERVICING**  
for your **OWN  
BUSINESS/HOBBY**

● by a new exciting no-maths system, using practical equipment recently introduced to this country

**FREE Brochure from:—  
RADIOSTRUCTOR  
DEPT. G78  
READING, BERKS. 9/61**

**PUBLIC APPOINTMENTS**

**MEN WITH KNOWLEDGE** of basic principles of RADIO AND RADAR required in the METEOROLOGICAL OFFICE. After short initial training, those appointed will maintain and operate radio and radar equipment, including facsimile apparatus. There are vacancies in various localities in the United Kingdom and opportunities to serve overseas. Starting salary for Radio (Meteorological) Technicians is £810 (national) at 25 or over, rising annually to £930 subject to deduction for each year below the age of 25. These rates are subject to a small deduction at certain provincial stations and to a small increase in London. Good promotion prospects and allowances for overtime, night duty, etc. Applicants must be British subjects.

Applications to Meteorological Office, (M.O.10 R/M/T), London Road, Bracknell, Berks, or to any Employment Exchange quoting order no. Bracknell 379.

**SITUATIONS VACANT**

UNITED KINGDOM

ATOMIC ENERGY AUTHORITY

ATOMIC ENERGY  
ESTABLISHMENT, WINFRITH

Vacancies exist at A.E.E. Winfrith, Dorchester, Dorset, for

**INSTRUMENT  
MECHANICS**

(Electronic and Electro-Mechanical)

Applicants should be familiar with the construction of Electro-Mechanical experimental equipment and components; ability to read circuit diagrams and drawings, and to construct, wire and test electrically complex equipment is desirable. Duties will include the major overhaul and repair of a wide variety of electronic and electro-mechanical equipment, including potentiometric recorders, moving coil instruments, pressure, vacuum and flow transducers, oscilloscopes, signal and pulse generators, all types of amplifiers and high vacuum ionisation gauges.

Houseing may be available to the successful applicants, but this would be determined at the time of interview. Excellent working conditions including sick-pay and pensions schemes.

Further details of conditions of employment, rates of pay and application forms, may be obtained from—

THE LABOUR DEPARTMENT  
A.E.E. Winfrith, Dorchester, Dorset  
quoting Reference Number IM/PW/PT.

**BOOKS**

**FIND TV SET TROUBLES IN MINUTES** from that great book "The Principles of TV Receiver Servicing," 10/6 all book houses and radio wholesalers. If not in stock from: Secretary, I.P.R.E., 20 Fairfield Road, London N.8.

# NEW VALVES!

Guaranteed Set Tested  
24 HOUR SERVICE

1R5	1R5	1T4	3B4	3V4	DAF91	DF91	DK91	DL22	DL94	SET of 4	1R/6
DAF96	DF96	DK96	DL96	SET of 4	2R/6						
1D5	7/-	DJ22	5/11	PCF80	8/9						
1R5	7/-	DL94	6/9	PCF82	7/8						
1R5	4/6	DL96	6/9	PCL82	8/3						
1T4	3/3	EB91	3/-	PCL83	11/6						
3B4	5/11	EBC41	7/6	PCL84	7/6						
3V4	6/9	EBF80	7/9	PL36	10/9						
5U4G	4/3	EBL21	12/6	PL81	8/6						
5Y3GT	5/8	ECC40	14/6	PL82	6/6						
5Z4G	7/3	ECC81	4/9	PL83	6/6						
6AM6	2/9	ECC82	5/9	PL84	9/6						
8K7G	1/9	ECC83	6/3	PY32	10/3						
8K9G	4/9	ECC84	8/-	PY80	7/-						
8Q7G	5/8	ECC85	7/9	PY81	6/-						
6V6G	4/9	ECCF80	8/3	PY82	6/-						
6V6GT	6/6	ECCF82	8/3	PY83	7/3						
6X5GT	4/9	ECH21	12/6	UC25	12/-						
12Q7GT	4/6	ECH42	7/9	UAF42	7/6						
12K8GT	11/9	ECL80	6/9	UAF46	7/6						
12Q7GT	4/6	EF40	12/3	UBC41	7/-						
12L8GT	8/6	EF41	7/6	UBF80	8/6						
35Z4GT	5/9	EF80	4/9	UCB35	7/-						
AZ31	9/9	EP85	5/-	UCH21	12/6						
CL33	11/9	EP86	8/9	UCH42	7/6						
DAC32	9/6	EP89	6/9	UCH81	8/-						
DAF91	4/6	EP91	2/9	UCL82	10/-						
DAF96	6/9	EL41	7/-	UCL83	13/-						
DF33	9/6	EL64	6/3	UF41	7/9						
DF91	3/9	EY5	7/3	UF85	8/-						
DF96	6/9	EY86	7/6	UF89	6/6						
DH77	6/-	EZ40	6/-	UL41	7/-						
DK32	11/-	EZ41	6/9	UL84	7/-						
DK91	5/-	EZ20	5/9	UY21	13/-						
DQ22	7/3	EZ81	6/6	UY41	5/6						
DK96	8/9	MU14	7/-	UY85	6/3						
DL33	6/6	PCC84	6/9	VP4B	8/6						
DL36	9/6	PCC89	10/-	Z77	2/9						

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 3/- extra.

Office address, no callers.  
**GERALD BERNARD**  
(Note new address—formerly of Leeds)  
35 NEWBURY ROAD  
HIGHAMS PARK, LONDON, E.4

## Television Engineers' Pocket Book

Experienced engineer and the newcomer to the service work will find this handy book invaluable for the on-the-spot repairs.

Edited by J. P. Hawker.

12/6 Postage 6d.

**PRINCIPLES OF TELEVISION RECEIVER SERVICING** by T. A. B. Carmait, 10/-. Postage 6d.

**TELECOMMUNICATIONS**, Principles & Practice, by W. T. Perkins, 21/-. Postage 1/-.

**USING AN OSCILLOSCOPE** by D. W. Easterling, 6/6. Postage 6d.

**THE RADIO AMATEUR'S HANDBOOK 1961** Ed. by A.R.R.L. 32/6d. Postage 2/-.

**RADIO VALVE DATA** 7th Ed. Compiled by "WW" 6/-. Postage 10d.

**G.P.O. HANDBOOK FOR RADIO OPERATORS**. H.M.S.O. 6/-. Postage 1/-.

**TV TROUBLE ANALYSIS**, by H. Milne. 26/-. Postage 1/-.

Complete Catalogue 1/-.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET  
LONDON, W.2

Phone: PADdington 4185  
Open 6 days 9-6 p.m.

## NYLON · P.T.F.E.

ROD, BAR, SHEET, TUBE, STRIP, WIRE

No Quantity too small  
List on application

**ALUMINIUM, LIGHT ALLOYS,  
BRASS, COPPER, BRONZE  
H. ROLLET & CO., LTD.**

6 CHESHAM PLACE, LONDON, S.W.1.  
BELgravia 4300

Works:

36 ROSEBERY AVE., LONDON, E.C.1

Branches at Liverpool, Manchester,  
Birmingham, Leeds.

## RESTORE TV TUBE PICTURE QUALITY & BRIGHTNESS



Pat. No. 836161  
Reg. design.  
**JUST PLUG ON TO  
TUBE**

No technical knowledge required.

Important: State  
Make, Model No.  
Name and Address in Block  
Letters Please.

STANDARD MODEL .. 25/-  
DE LUXE MODEL .. 35/-  
Postage 2/6 either model.

**SINCLAIR ELECTRONICS** Dept. P.W.1  
18 Newport Court, Charing Cross Rd.  
W.C.2.

Terms: C.W.O., C.O.D. REGent 5520.

## REBUILT TV TUBES

FULLY GUARANTEED  
12 MONTHS

Complete New Gun fitted in every Tube

12in. ...	... ..	£4.0.0
14-15in. ...	... ..	£4.10.0
17in. ...	... ..	£5.0.0
21in. ...	... ..	£7.0.0

Immediate Delivery

Carriage and Insurance 10/- extra  
Allowance on old tube

## NU-GUN TELETUBES LTD.

3 The Mews, Duckett Rd.  
Harringay, London, N.4

Telephone: MOUnview 2903

## RES/CAP. BRIDGE 38/-

p. & p. 2/-  
Checks all types of resistors, condensers  
6 RANGES

Built in 1 hour. Direct reading  
**READY CALIBRATED**  
Stamp for details of this and other kits.

**RADIO MAIL** (Dept. PV)  
Raleigh Mews, Raleigh Street, Nottingham

## 'CAPRI' ALL TRANSISTOR RADIO



All Transistor Radio with carrying case. Miniature loud-speaker design. Covers all medium waves. Very reliable. Works for months off 8d. battery. Can be assembled in an hour or two using our simple as ABC pictorial open-out step-by-step plans. Complete set of parts including miniature speaker - everything - only 27/6 plus 2/- P/P (C.O.D. extra). Parts can be bought separately. Demonstrations Daily - Money back guarantee. Send now.

**CONCORD ELECTRONICS**  
(Dept. PT.4), 210 Church Rd., Hove, Sussex

## EDDY'S (NOTTM.) LTD.

172 ALFRETON RD., NOTTINGHAM  
NEW OR SURPLUS VALVES

Guaranteed and Tested by Return Post

ID5	7/6	6V6G	4/9	ECC85	6/11
1L4	3/6	6V6GT	6/-	ECH42	7/9
1R5	5/6	6X4	5/-	ECL80	7/6
1S5	4/6	6X5G	5/6	ECL82	9/-
1T4	3/11	6X5GT	6/6	EF36	3/6
3A4	6/-	10F1	6/6	EF42	7/6
3S4	5/11	12A6	5/3	EF50	1/9
3Y4	6/9	12AT6	7/6	EF80	5/-
5U4G	4/9	20D1	8/6	EF86	9/6
5Y3GT	6/6	20P1	9/6	EF91	3/6
5Z4G	7/6	30F5	6/11	EF92	4/6
6B8G	2/11	35L6GT	8/11	EZ40	6/3
6C4	3/6	35W4	6/9	EZ41	7/-
6C6	4/9	35Z4	5/3	EZ80	6/3
6C6H	8/-	954	1/6	KT33C	6/6
6F1	6/11	955	3/6	MU14	7/-
6F13	8/11	956	2/6	OZ4	5/11
6F15	9/6	AC2/PEN		PCC84	7/6
6F33	6/6	DD	7/6	PCF80	7/6
6J5G	2/9	CY31	9/6	PCL82	7/6
6J5GT	3/9	DAF96	6/11	PCL83	12/6
6J5M	4/3	DF96	6/11	PENA4	12/6
6J7G	5/-	DL96	6/11	PEN36C	8/-
6K7G	1/11	DM70	6/11	PL81	9/-
6K8G	5/3	ECC81	5/3	PZ30	9/6
6Q7G	5/9	ECC82	5/11	TDD4	7/6
6SG7M	4/9	ECC83	6/6	VP23	4/6
6SN7GT	4/3				

**GUITAR PICK-UPS**. Super Hi-Fi non-acoustical universal fitting. High output. Complete with lead and plug. Full and easy instructions. 49/11. P. & P. 2/6.

**NIFE ACCUMULATORS**. 1.25v. size 3 x 2 1/2 x 1/4 in. 7 amp hrs. Weight 13 ozs. 1/11 each. P. & P. 1/6. One only add 9d. per cell.

**POCKET RADIO**. 2 transistor with Miniature Speaker. Complete with all parts, wiring diagram and full instructions. 27/6. Batteries 1/-, P. & P. 1/6.

**THROAT MIKES**. 2/- each, Post 8d. Could be used for electrifying musical instruments, etc.

**VIBRATORS**. 12 volt, 4-pin, 4/11. Post 1/-  
**CRYSTAL SETS**. Complete. 2 wave bands. High gain. Good quality. 19/11. Also with Transistor Amplifier extra, 9/11. P. & P. 2/6.

**HEADPHONES**. High res. to suit above Crystal Sets. 13/11 pr. P. & P. 1/6.

**V.H.F. AERIALS**. Complete and easy to fit. No technical knowledge required. 6/11. Post 10d.

**LUXEMBOURG AERIALS**. Expanding, complete and easy to fit. No technical knowledge required. 3/11. Post 6d.

All Above are New and Guaranteed. Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Post and Packing 6d. per valve extra. C.W.O. or C.O.D. only C.O.D. charge 3/- ex. S.A.E. with enquiries.

# COYNE'S NEW JOB TRAINING BOOKS


Put Money-Making Time  
Saving Know-how at your  
fingertips!

Shows you the way to easier TV—Radio repair—time saving, practical working knowledge that helps you to repair sets faster! How to install, service and align ALL radio and TV sets, even colour, TV, UHF, FM and transistorized equipment. New photo-instruction shows you what makes equipment "tick." No complicated maths or theory—just practical facts you can put to use immediately right in the shop, or for ready reference at home.

## TRY ANY THREE BOOKS ON NO RISK FREE TRIAL

Look over the list of books and select the first three books you would like to examine. Circle the book numbers on the coupon. Additional books you would like to see may be entered on a separate piece of paper, and these will be sent to you after completion of the first transaction.

FREE TRIAL OFFER!

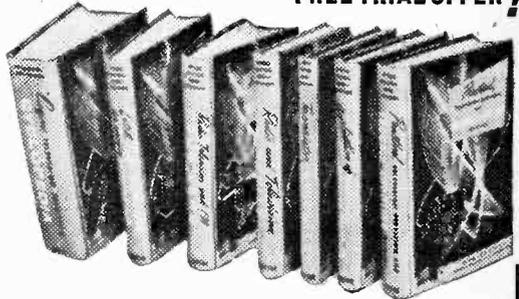

### SPECIAL OFFER COYNE ELEMENTARY PRACTICAL RADIO-TELEVISION SET OF THREE VOLUMES, total 1,038 pages, sturdy Vinyl washable covers. £3.12.6d. the set!

These three volumes present the principles of construction, operation and testing of radio and television equipment in a SIMPLE, EASY TO FOLLOW manner.

By using NEW & DIFFERENT methods of explanation these books clearly explain the direct relation between the various parts of sets. This information is especially helpful in repair work where many times a burned out valve, resistor or transformer is actually caused by some other defective part of a circuit. Until the cause of the trouble is removed the parts would continue to burn out. For this reason, each part of the radio or television unit is explained, thus, making the material especially helpful to the experienced radiomaniac, as well as the amateur.

One very important way in which these books differ from many other radio and television books is that the publishers did not try to assume the "extent of technical knowledge" of the reader. Every subject is explained COMPLETELY—while at the same time keeping it brief and to the point.

You will find hundreds of photos, charts, diagrams, etc., in these books. These have been provided to make it easier to understand the explanations. To get this special offer, send no money now, then 12/6d. after free examination, and 20/- per month.



### No. 9 Pin-Point Transistor troubles in 12 minutes

In this extremely practical handbook, the famous Coyne Check-Chart Trouble Shooting Method is applied to Transistorized Equipment and includes such subjects as Pre-amplifiers and Hearing Aids; Audio Amplifiers, Portable Sets, and Special Types of equipment. Hundreds of photos, illustrations, diagrams and Check-Charts; Valuable reference sections. 225 pages. Spiral Binding. Price 47/6. (Please send coupon with order.)

### No. 4. LATEST INSTRUMENTS FOR SERVICING RADIO AND TELEVISION. Coyne.

This up-to-the-minute book tells all about modern radio, TV and electrical testing equipment and how to use it. Money-making short cuts on trouble-shooting, servicing, construction, and other jobs. Over 350 pages, 220 photos and diagrams. Covers Multimeters, Resistors, Ohmmeters, Oscilloscopes and many others. All data has been pre-tested in the Coyne radio shops. Vinyl cloth covers. 26/-.

### No. 5. PRACTICAL TELEVISION SERVICING AND TROUBLE SHOOTING MANUAL. Coyne.

A book of fast time saving methods for servicing TV receivers. Includes dozens of new testing ideas all of which have been proven on the job. This book shows how radio knowledge can be applied to help solve television problems. Contents include TV servicing methods, TV Servicing Instruments, Tuners, Video I.F., Amplifiers, alignment, etc., with 200 crystal clear photos and diagrams. 437 pages. Washable vinyl cloth covers. Price 34/-.

### No. 6. COYNE TELEVISION SERVICING CYCLOPEDIA. Harold P. Manly. Coyne.

Quick and concise answers to TV problems in alphabetical order, cross indexed, fully illustrated, covers hundreds of questions involving radio, TV, electronics operation and repair. 450 illustrations; photos, diagrams, charts, test patterns, etc., 860 pages. Vinyl cloth covers. Price 47/6.

### No. 13. TELEVISION EXPLAINED. Miller and Spreadbury. (LILFFE)

A simple terms and non-mathematical language gives step-by-step survey of modern television receivers and aerial systems, including AGC and Flywheel Synchronising. 184 pages. 12/6.

No. 8

### COYNE'S NEW PIN-POINT TV TROUBLES

TAKES HEADACHES OUT OF ALL SERVICING PROBLEMS

Your most useful on-the-job "go-to"! Quickly and easily pin-points the exact trouble in any TV set. Covers 70 symptoms, 700 trouble spots. Over 340 cross-indexed pages; 50 time-saving Check-Charts; 290 diagrams and photos; explanation of circuits and designs.

#### SIMPLE CHECK-CHART SYSTEM SAVES TIME!

This amazingly practical handbook shows you how to find the trouble in any TV circuit FAST! Simple cross-index tells you in what section you'll find cause of trouble. Handy Check-Charts then help you accurately locate the EXACT trouble spot. Cut waste time, eliminate hours of aggravation, get right of the heart of the trouble in minutes. Price 31/8.



### No. 22. PIN POINT COLOUR TV TROUBLES IN 15 MINUTES. Edited by Robert G. Middleton.

This book deals with 150 types of faulty pictures and sound with over 1000 troubles which may be the cause. Some of the subjects covered are: Antenna, Tuner, Video and Luminance Amplifiers, Matrices, Picture Tubes (Black and White, and Colour), One-Gun Tubes, Set up of Colour Tube, Colour Killer and Automatic Chroma Control, Low Voltage, Power Supply, TV Sound, etc. Picture Pattern Section — 362 Check Charts, Diagrams and Photos. 548 pages. Price 47/6.

### No. 7. TRANSISTOR CIRCUIT HANDBOOK. Louis E. Garner, Jr. Coyne.

A practical Transistor Circuit Reference Handbook by the eminently qualified Louis E. Garner, Jr., one of the greatest writers on transistor applications. Covers Transistor Circuitry, Basic Circuits, Circuit Applications and General Reference material. Dozens of how-to-do-it illustrations with more than 200 circuit diagrams. Over 400 pages. Vinyl cloth covers. 39/6. (When ordering this book please be sure to clip the coupon.)

### No. 10. TELEVISION RECEIVER SERVICING. Vol. 1, by E. A. W. Spreadbury. 1961 Edition. (LILFFE)

Timebase Circuits, including the Cathode Ray Tube. How to check the Waveform at the Input and Output of each Section—Faults—Blank Screen—Obtaining a Better, Applying a Signal, Synchronisation, Interlace Quality, etc. 382 pages. 25/-.

NOTE

\* Any Lilffe or Coyne book is available on time payment plan! \* Send name of title required. Just mail coupon for free trial. After 7 days send only low price or return books and pay nothing. If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum three books). To buy one book send one-half in 7 days, and one-half in 30 days.

## LIMITED OFFER! ACT NOW!

To SIM-TECH BOOK COMPANY  
Mail Order Division, DEPT. FTV13, Gaters Mill, West-End, Southampton, Hants.

Please send me the special Elementary Radio TV Set as per special offer.

Rush the books circled below for 7-day FREE TRIAL as per offer.

9 4 5 6 13 8 22 7 10

Tick here if enclosed full price. Same 7-day money back guarantee.

Name .....

Address .....

City .....

Postage 1/8, orders under £3. 2/- orders over £3.

# TELEVISION TUBES RE-BUILT BY "RE-VIEW"

	PRICE:		
12in.	...	...	£4.10.0
14in.	...	...	£4.15.0
15in.	...	...	£5. 0.0
17in.	...	...	£5. 0.0
21in.	...	...	£7. 0.0

**SAVE £££s**

Correct voltage heaters  
All types



**TWELVE MONTHS' GUARANTEE**

Free carriage and insurance  
Cash with order or C.O.D.

Be one of our satisfied customers. Call and see our TUBES REBUILT and TESTED

**RE-VIEW (London) LTD., 10 High St., Colliers Wood, London S.W.19**

Terms to the Trade

Tel.: LIBERTY 3272

## FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

**Have you sent for your copy?**

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee  
"NO PASS — NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

**BRITISH INSTITUTE OF ENGINEERING  
TECHNOLOGY (Incorporating E.M.I. Institutes)**  
(Dept. SE/20), 29 Wright's Lane, London, W.8

**WHICH IS YOUR  
PET SUBJECT?**

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

**GET SOME  
LETTERS AFTER  
YOUR NAME!**

A.M.I. Mech. E.  
A.M.I.C.E.  
A.M.I. Prod. E.  
A.M.I.M.I.  
A.I.O.B.  
A.F.R. Ae.S.  
B.Sc.  
A.M. Brit. I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

**PRACTICAL  
EQUIPMENT**

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

**INCLUDING  
TOOLS!**

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.  
SCHOOL OF  
ELECTRONICS**



**POST COUPON NOW!**

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME .....

ADDRESS .....

SUBJECT OR EXAM THAT INTERESTS ME ..... (SE/20).

**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**

**CRT BOOSTER TRANSFORMERS**  
**TYPE A. OPTIONAL 25% and 50% BOOST.**  
 2 V. 0.4 V. 0.16 8.3 V. 0.8 10.8 V. 0.6  
 13.3 V. MAINS INPUT. 12/6

**TYPE A.2. HIGH QUALITY, LOW CAPACITANCE, 10/15 pF. OPTIONAL BOOST 25%, 50%, 75%. MAINS INPUT. 16/6**

**TYPE B. MAINS INPUT. MULTI OUTPUT 2, 4, 6.3, 7.3, 10 and 13 VOLTS. BOOST 25% AND 50%. LOW CAPACITY. 21/-**  
 Full instructions supplied.

**TRIMMERS.** Ceramic, 30, 50, 70 pF, 9d.; 100 pF, 150 pF, 1/3; 250 pF, 1/6; 500 pF, 750 pF, 1/8.

**RESISTORS.** Preferred values, 10 ohms to 10 meg., 1 w., 4d.; 1 w., 4d.; 1 w., 8d.; 2 w., 1/1-1/2.

**HIGH STABILITY.** 1 w., 1/2; 2/- Preferred values, 10Ω to 10 meg. Ditto, 5Ω, 100Ω to 5 meg. Ω, 9d. 5 watt 1/3  
 10 watt 1/8  
 15 watt 1/5

**WIRE-WOUND RESISTORS** 1/3  
 25 ohms—10,000 ohms 2/-  
 12.5K to 50K 10 w. 3/1-

**AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE**

Double Play	7in. reel, 2,400ft.	60/-	Spare
	5in. reel, 1,800ft.	37/6	Plastic
Long Play	7in. reel, 1,500ft.	35/-	Reels
	5in. reel, 1,200ft.	23/6	3 in. 1/6
	5in. reel, 900ft.	18/6	4 in. 2/-
			5 in. 2/-
Standard	7in. reel, 1,300ft.	25/-	5 in. 2/-
	5in. reel, 900ft.	16/-	7 in. 2/6

"Instant!" Bulk Tape Eraser and Head Defuser, 200/250 v. A.C., 27/6. Leadcut, S.A.E.

**O.P. TRANSFORMERS.** Heavy Duty 50 ma, 4/6. Multitap, push-pull, 7/6. Ditto, 10w, 15/6. Miniature, 384, etc., 4/6. L.F. CHOKES 15/10 1/1, 60/25 ma, 5/-; 10 H. 8/5 ma, 10/6; 10 H., 150 ma, 14/-

**MAINS TRANSFORMERS 200/250 v. A.C. STANDARD.** 250-0-250, 80 ma, 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350. 22/6

**MINIATURE** 200 v. 20 ma, 6.3 v. 1 a. 10/6

**MIDGET.** 220 v. 15 ma, 6.3 v. 2 a. 17/6

**SMALL.** 220-0-220, 60 ma, 6.3 v. 2 a. 17/6

**STD.** 200-0-250, 65 ma, 6.3 v. 3.5 a. 17/6

**HEATER-TRANS.** 6.3 v. 1 1/2 amp. 7/6

Ditto, tapped sec. 2, 4, 6.3 v., 1 1/2 amp. 8/6

Ditto, sec. 6.3 v. 3 amp. 10/6

**GENERAL PURPOSE LOW VOLTAGE.** 2a, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/6

**AUTO TRANSFORMERS.** 150 w. 22/6

0, 120, 200, 230, 250 v., 500 w. 22/6

**ALADDIN FORMERS and core, 4in., 8d.; 1in., 10d.**  
 0.5in. FORMERS 6937/8 and Cans TV1/2. 7in. sq. x 2 1/2in. and 2in. sq. x 1 1/2in. 2/- ea., with cores.

**SOLNS** Soldering iron, 200 or 240 v., 25 w. 24/-

**MAINS DROPPERS.** 3in. x 1 1/2in. Adj. Sliders, 0.5 amp., 1,000 ohms, 4/3. 0.2 amp., 1,000 ohms, 4/3.

**LINE COIL** 0.3 amp., 60 ohms per ft., 0 amp., 100 ohms per ft., 2-way, 1/1 per ft., 3-way, 1/1 per ft.

**LOUDSPEAKER P.M. 3 OHM.** 2in., 10/8. 3in., 17/6. 4in., Plessey, 19/8. 6in. x 4in., 19/8. 8in., 27/6. 10in., 30/6. 12in., Hi-Fi Tweeter, 25/-, 12 in. R.A., 30/-

**STENTORIAN HF1012.** 10in., 3 to 15 ohms, 10W, 85/6

**12in.** Baker 15 watt 3 ohms, or 15 ohms, 80/-

**CRYSTAL DIODE G.E.C. 2/- GEX34, 40/-**

**HIGH RESISTANCE PHONES.** 4,000 ohms, 15/- per pair.

**MIKE TRANSF.** 50 x 1 1/2 ea., 100 x 1, Potted, 10/6

**SWITCH CLEANER.** Hand squirt sprayer, 4/3

**TWIN GANG TUNING CONDENSERS.** 4/3 tin. miniature tin. x 1 1/2in., 10/-, 500pF standard with trimmers, 9/-; midget, 7/6 with trimmers, 9/-

**SINGLE.** 50 pF, 2/6; 75 pF, 100 pF, 160 pF, 5/6. Solid dielectric 100, 300, 500 pF, 8/6.

**New and Boxed VALVES 90-day Guarantee.**

1R5	7/6	6K8CG	7/6	EAC80	8/6	HABC80	
1S5	7/6	6L6G	10/6	EB91	6/6	12/6	
2X2	3/6	6N7M	6/6	EB33	8/6	HV2A	6/6
384	7/6	6BA7	6/6	EBF80	10/6	PT 14	9/-
3V4	7/6	6B8J7M	6/6	ECC84	9/6	PC94	9/6
5U4	7/6	6B8N7	6/6	ECP80	9/6	PCF80	9/6
5Y3	7/6	6V6G	6/6	ECH42	10/6	PCU82	11/6
6B6	9/6	6X4	7/6	EL82	10/6	PEN35	8/6
6AM6	5/-	6X5	6/6	EP30	5/6	PT15	10/6
6B8	5/-	12A7	8/6	EP41	5/6	PY80	7/6
6B8	7/6	12AU7	8/6	EP50	5/6	PY81	9/6
6B16	9/6	12AX7	8/6	EP80	8/6	PY82	7/6
6B9	9/6	12BE6	8/6	EP86	12/6	SP61	3/6
6B9	6/-	12CT7	8/6	EP91	5/6	UC84	9/6
6P6G	7/6	12Q7	6/6	EP92	5/6	EGH42	9/6
6H6	3/6	35L6	9/6	EL32	5/6	UF41	9/6
6J5	5/6	35Z4	7/6	EL84	8/6	UY41	9/6
6J6	5/6	500	9/6	EM81	9/6	UY41	8/6
6J7G	6/6	800	9/6	EL240	7/6	V22	8/6
6K6GT	6/6	854	1/6	EZ80	7/6	VR105	9/6
6K7G	6/6	EA50	1/6	EL148	1/6	VR150	9/6

**"REGENT" 4 VALVE "96" RANGE VALVES KIT PRICE £6. 6. Carr. 4/-**

**PRINTED CIRCUIT BATTERY PORTABLE KIT**

Medium and long wave. Powerful 7 x 4in. high Flux Speaker. T.C.C. Printed Circuit and condensers. Components of finest quality clearly identified with assembly instructions. Osmer Ferrite Aerial coils. Resin covered attache case cabinet. Size 12in. x 8in. x 4in. Batteries used B126 (L5512) and AD35 (L5040), 10/- extra. Instructions 9d. (free with kit). Mains Unit ready made for above, 39/6. Sold separately.

**TV REPLACEMENT LINE OUTPUT TRANSFORMERS**

FROM 45/- ea. Most makes available. S.A.E. with all enquiries.

LINE BLOCKING TRANSFORMERS, from 10/-  
 FRAME BLOCKING TRANSFORMERS, from 13/6  
 FRAME OUTPUT TRANSFORMERS, from 27/6.

**NEW MULLARD TRANSISTORS**  
 Audio OC71 8/- RF OC44 10/6  
 OC72 8/6 OC45 9/6

Sub Miniature Electrolytics, 15 volt.  
 1, 2, 4, 5, 8, 25, 50, 100 mfd., 2/6 each.  
 Weyrad Printed Circuit Components in Stock.  
 7 x 4 in. Speaker 35/6 25/-

**HIGH GAIN TV PRE-AMP KITS**

**BRAND I BBC**  
 Tunable channels 1 to 5. Gain 18dB.  
 EOC84 valve. Kit price 29/8 or 49/8 with power pack. Details 6d. (PCC84 valves if preferred.)

**BRAND III ITA**—Same prices.  
 Tunable channels 8 to 13. Gain 17dB.  
 EOC84 valve. (PCC84 valves if preferred.)

**CRYSTAL MIKE INSERT** by Acos precision engineers. Size only 2in. by 3/16in., 6/8.

**ALUMINIUM CHASSIS.** 18 s.w.g. undrilled. With 4 sides, riveted corners and lattice fixing holes, 2 1/2in. sides, 7 x 4in., 4/6; 9 x 7in., 5/8; 11 x 7in., 6/8; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/8; 18 x 15 x 3in., 18/6.

**ALUMINIUM PANELS.** 18 s.w.g. 12in. x 12in., 4/6; 14 x 9in., 4/-; 12 x 8in., 3/-; 10 x 7in., 2/6.

**JASON F.M. TUNER COIL SET, 29/-, H.F. coil, aerial coil, Oscillator coil. Two I.F. trans. 10 1/2 Mc/s Ratio Detector and heater choke. Circuit book using four 5AM6, 8/6.**

**COMPLETE JASON F.M. KIT, PMTL**, with set of 4 valves, etc., 65.5/0.

**BBC TRANSISTOR RADIO.** Med. and Long Wave. Two transistors and diode. Complete kit, 32/6, phones 7/6 extra. Dead Aid Earpiece with Special Lead, 12/6. Details 6d.

**465 Kc/s. SIGNAL GENERATOR.** Total cost 15/-. Uses B.F.O. Unit ZA 30038 ready made. POCKET SIZE 2 1/4 x 4 1/4 in.  
 Slight modifications required, full instructions supplied. Battery 7hr extra 69 v. + 1 1/4 v.

**I.F. TRANSFORMERS 7/6 pair**  
 465 Kc/s Star Tuning Miniature Can. 1 1/2 x 1 1/4 in. High Q and good bandwidth. Data sheet supplied.

**RECORD PLAYER BARGAINS**

4 Speed Autochangers, B.S.R., U.A.R. 66.15.0  
 4 Speed Autochangers, B.S.R., U.A.14 27.10.0  
 Collar Autochanger 27.19.6  
 Garrard Model 210, GC8 Head 210.10.0  
 4 speed Single Players, EMI 26.5.0  
 Garrard T.A. Mk. II, GC8 Head 23.0.0  
 Garrard Model 44P GC8 28.17.8  
 Garrard Stereo Head, 22 extra.  
 Suitable player cabinets (except 4 H.F.) 49/6  
 Amplifier player cabinets (except 4 H.F.) 63/-  
 3-valve amplifier and 6 1/2in. speaker 79/8  
 3-valve amplifier and 8 1/2in. speaker 95/-  
 Wired and tested ready to use with above.  
 All sapphire styli available from 8/-.

**Volume Controls 80 ohm CABLE COAX**

Long spindles. Guaranteed 1 year. Midget 40 ohms to 2 Meg. 5K ohms to 2 Meg. No Sw. D.P.S.w. 3/-  
 Linear or Log Traps 4/6  
 Semi-air spaced. 2in lead 50/-  
 40 yds 17/8 6d. yd.  
 60 yds 25/-  
 Fringe Quality 1/- yd  
 Air Spaced.

**COAX PLUGS 1/- LEAD SOCKET 2/6**  
**PANEL SOCKETS 1/- OUTLET BOXES 4/6**  
**BALANCED TWIN FEEDER 7d.** 6d. 80 or 300 ohms.  
**DITTO SCREENED** per yd. 1/6. 80 ohms only.  
**WIRE-WOUND POTS, 3 WATT.** Pre-set Min. TYP. All valve 25 ohms to 26 K., 3/- ea. 30 K., 50 K., 4/-, (Carbon 30 K., to 2 meg., 3/-).  
**WIRE-WOUND 4 WATT.** Pots Long Spindle Values: 50 ohms to 50 K., 6/8; 100 K., 7/6.  
**CONDENSERS.** New Stock 0.001 mfd. 7 kV. T.C.C. 5/6; Ditto, 20 kV. 9/6; 0.1 mfd., 7 kV. 9/6; Tubular 500 v. 0.001 to 0.05 mfd., 9d., 0.1 1/1-; 0.25, 1/8; 0.5/350 v., 1/8; 0.1/350 v., 9d.; 0.01/2 mfd., 0.1/11,000 v., 1/8; 0.1 mfd., 2,900 volts, 3/6.

**CERAMIC COND.** 600 0.3 pF to 0.01 mfd., 9d.  
**SILVER MICA CONDENSERS.** 10% 5 pF to 500 pF, 1/-; 600 pF to 3,000 pF, 1/3. Close tolerance (±1 pF) 1.5 pF to 47 pF, 1/6. Ditto 1% 50 pF to 815 pF, 1/8; 1,000 pF to 5,000 pF, 2/6.

**NEW ELECTROLYTICS. FAMOUS MAKES**

TUBULAR	TUBULAR	CAN TYPES	
1/350v. 2/-	50/350v. 5/6	16/450v.	5/-
2/450v. 2/3	100/25v. 2/3	32/350v.	5/6
4/450v. 2/3	250/25v. 2/3	100/270v.	5/6
8/450v. 2/3	500/12v. 3/4	2,500/3v. 4/6	
8/500v. 2/3	8+8/450v. 3/6	5,000/6v. 5/6	
16/450v. 3/4	8+16/450v. 5/6	32+34/450v. 6/6	
16/500v. 4/6	8+16/500v. 5/6	32+32+32/350v. 7/6	
32/450v. 3/8	16+16/450v. 4/3	50+30/350v. 7/6	
25/25v. 1/9	16+16/500v. 5/6	120/250v. 11/6	
50/500v. 2/1	32+32/350v. 4/6	100+200/275v. 12/6	

**RECTIFIERS SELENIUM 300 v. 85 ma. 7/6.**  
**CONTACT COOLED 250 v. 50 ma. 7/-; 60 ma. 8/6;**  
 85 ma, 9/6; 200 ma, 21/-; 300 ma, 27/6.

**COILS** Wearite "P" type, 3/- each. Osmer Midget "Q" type adl. dust core 1/2 in. dia. 2/6.

**TELETYPE L. & Med. T.R.F. 4/6. All ranges.**  
**FERRITE ROD AERIALS. M.W. 5/8; M. 1 1/2; T.R.F. COILS A.H.F. 7/- pair. H.F. CHOKES 2/6.**  
**FERRITE ROD, 8in. x 7in. dia. 2/6.**

**FULL WAVE BRIDGE SELENIUM RECTIFIER.** 2 or 3 p. 1 1/2 amp. 2/6. 2 1/2 amp. 3/6.

**CHARGER TRANSFORMERS.** Tapped input 200/250 v. for charging at 2, 6 or 12 v., 11 amps., 15/6. 2 amps., 17/6; 4 amps., 22/8. Circuit included.

**VALVE and TV TUBE EQUIPMENT boxes, 9/6.**

**TOGGLE SWITCHES.** 2 1/2 in. D.P. 3/8. D.P.D.T. 4/6

**WAVECHANGE SWITCHES**  
 6 p. 4-way 2 wafar long spindle 6/6  
 2 p. 2-way, or 3 p. 2-way short spindle 2/8  
 2 p. 6-way, or 2 p. 2-way, 4 p. 3-way long spindle 3/8  
 3 4-way, or 1 1/2 12-way long spindle 3/8  
**VALVEHOLDERS.** Fax Int. Oct. 4d. EF50, EA30, 6d. B12A, CRT. 1/3. Eng. and Amer. 4, 5, 6, 6 and 7 pin, 1/-

**MOULDED MAZDA and Int. Oct. 6d.**  
 BTG, B8A, B8G, B9A, 9d. B70 with can., 1/6.  
 B9A with can., 1/8. 9AEMC EF50, B7G, B9A. Int. Oct. 1/-, 9AEMC B7G, B9A, 1/1- ea.  
**SPEAKER FRET. GOLD CLOTH.** 17in. 25in., 5/-, 25in. x 35in., 10/-, Tygan 29in. wide, 10/- ft.; 26in. wide, 5/-, Green or red. Samples S.A.E.

**RADIO COMPONENT SPECIALISTS**

OUR ONLY ADDRESS  
 337 WHITEHORSE RD.,  
 WEST CROYDON

Post and Packing 1/-, over £2 free. (Export post Extra.) C.O.D. 1/6. (Wed. 1 p.m.) THO 1665. Buses 133 or 68