

# Practical

NOVEMBER 1961 1'9

# TELEVISION

## THE 'LINES' BATTLE

The truth behind the present controversy.

## HOW TV SETS WORK


The tuner circuitry is explained in this first article of a new series.

## THE P.T. MULTIMETER

Making a cabinet and calibrating this latest Practical Television design.

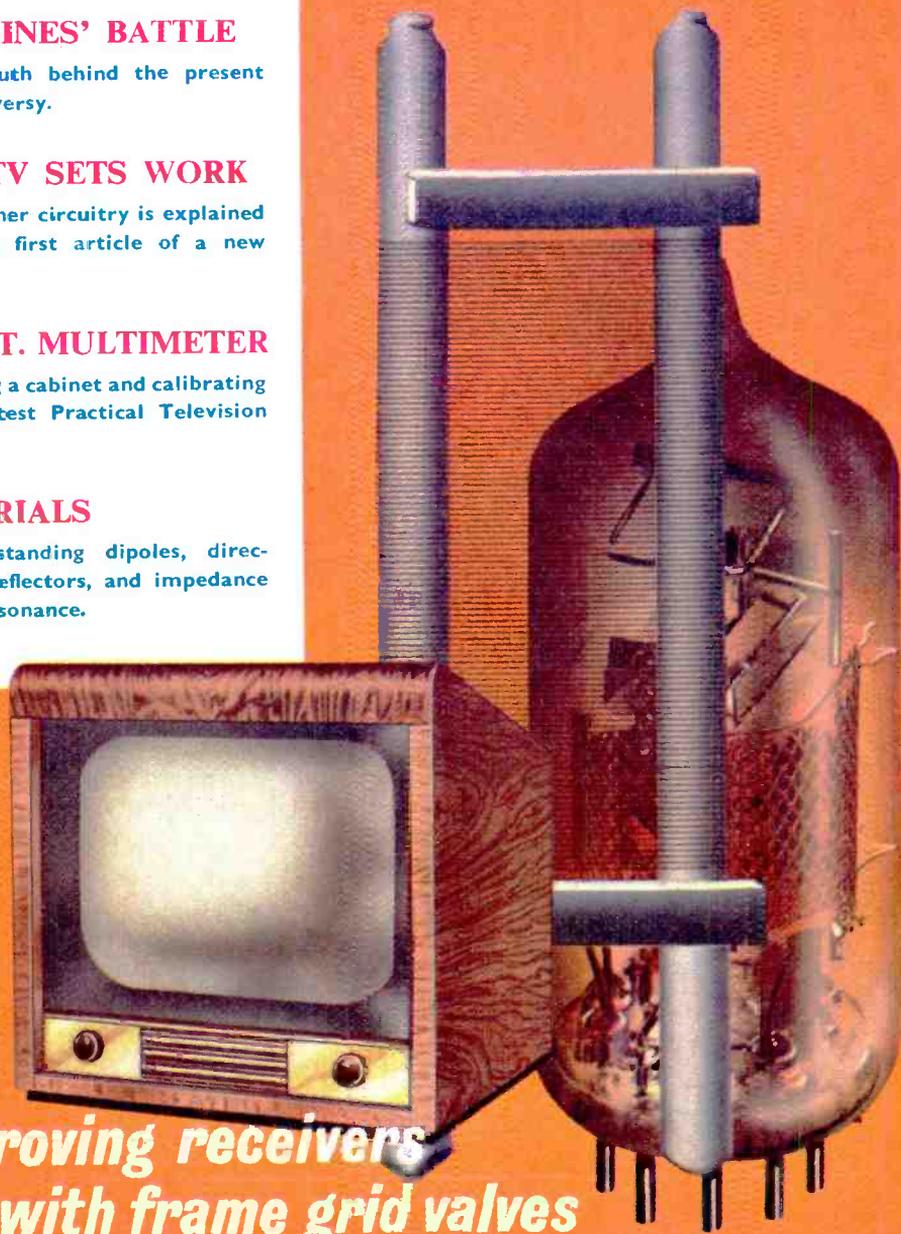
## TV AERIALS

Understanding dipoles, directors, reflectors, and impedance and resonance.



*Improving receivers  
with frame grid valves*

# Build your own Aerials...

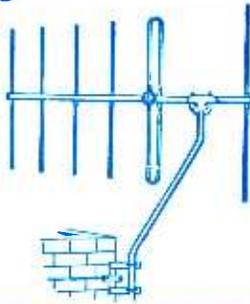

## AT HOME

**AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M.**  
Useful formulæ and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:—

# Fringelevision Ltd.

MARLBOROUGH, WILTS. Phone: 657/8

### EXPRESS ELECTRONICS ROSEDENE LABORATORIES KINGSWOOD WAY, SELSDON, SURREY

#### VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	7/8 6BA6	8/-	8D3	4/-	DF96	8/-	EF41	9/-	PCL84	7/-
1C3	8/- 6BE6	7/-	12AH8	10/-	DH76	7/6	EP80	8/-	PL81	12/6
1F1	8/- 6BH6	5/8	12AT7	6/-	DH77	8/-	EP86	9/-	PL82	7/-
1F3	7/6 6BJ6	5/8	12AU7	5/8	DH142	8/6	EP91	4/-	PL83	7/6
1FD1	8/- 6BR7	8/8	12AX7	6/-	DH150	10/-	EP92	5/8	PY81	6/8
1FD9	7/6 6BR7	10/6	12BE6	8/6	DK91	7/8	EL41	9/6	PY82	7/8
1L4	6/9 6BW8	7/8	12BH7	10/8	DK92	7/8	EL84	7/-	PY83	7/8
1P1	8/- 6HW7	7/-	12K6GT11	10/8	DK96	8/-	EM84	10/-	R19	11/6
1P10	7/6 6C10	9/-	12Q7GT	7/8	DL92	7/8	EM85	10/-	U26	9/8
1P11	7/6 6D2	4/-	16A5	8/-	DL94	8/8	EY51	7/8	U32	7/8
1R5	6/- 6F12	4/-	25A6G	8/6	DL96	8/-	EY81	10/-	U78	7/8
1R5	6/- 6H6GT	2/-	25L6GT	7/8	EB91	4/-	EZ40	7/8	U78	6/-
1T4	7/6 6J7GT	7/8	25Z4G	8/-	EBC41	10/-	EZ40	8/-	UBC41	8/8
1U5	5/6 6K7G	6/8	30C1	9/8	EBP80	8/8	EZ81	6/9	UCH42	8/6
3Q4	8/- 6K8G	6/-	30L1	7/-	ECC81	6/-	K733C	8/-	UF41	8/6
384	7/6 6Q7G	5/8	35L6GT	9/-	ECC82	6/8	K768	11/8	UL41	8/6
3V4	6/8 6RL7GT	6/-	35W4	8/8	ECC83	6/-	N17	7/8	UY41	7/8
5U4G	7/6 6SN7GT	6/-	35Z4GT	8/-	ECC84	7/8	N18	8/-	W76	6/8
5Y3GT	5/- 6V6G	7/8	83KU	10/8	ROP80	8/8	N19	7/8	W142	8/6
5ZAG	9/8 6X4	5/-	5783	7/8	ECP82	9/-	N709	7/-	X17	7/8
6AK6	6/8 6X5GG	5/-	80	8/8	ECH42	9/-	PCF84	6/9	X142	9/-
6AL5	4/- 6X5GT	6/-	DAP91	7/8	ECH81	10/-	PCF80	6/9	X150	9/-
6AM6	4/- 7B7	7/8	DAP96	8/-	ECL80	8/8	PCF82	7/-	Z77	4/-
6AT6	6/- 787	9/8	DF91	7/8	ECL82	9/-	PCL82	8/-	ZD17	7/8

High Stability Resistors 1W 5% 60 Ω to 1M. 9d. Midret Ceramics 500 v. 9d. Coax. Super quality 1in. 6d. 7d. Plus 9d. Booklets 9d. Silicon H.T. Rects. 250v. 300 MA 1" x 1" 17/6. Contact Cooled 250v. 50 MA 8/6. 85 MA 8/6.

**VOLUME CONTROLS MIDGET SIZE LONG SPINDLES.** D. P. switch 4/- Less switch, 2/6. Values 10K to 2M, B9A, BTG v. Holders 9d., Screens 8d.

#### VALVES MATCHED IN PAIRS

EL84 17/-, N709 17/-, 6V6G 17/-, 6BW6 18/- per pair. Push Pull O.P. Transformers for above 3-15 Ω 14/6. P. & P. 1/6. 12in. P.M. Speakers 3 Ω 24/6. Baker's "Schlurp" 12in. 15 Ω 15W, 80/-, 12in. Stereo Model 27.7.0.

#### SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL941 19/6  
 DK96, DF96, DAF96, DL96 27/6  
 1C3, 1F1, 1FD1, 1P1 27/6  
 1R5, 1T4, 1R5, 384, or 3V4 19/6  
 Postage and packing 6d. Over £1 post free. C.O.D. 2/6.

## THOUSANDS

OF SATISFIED PEOPLE

VIEW ON **E.M.S.**

### REBUILT TELEVISION TUBES

- ★ A NEW GUN IN EVERY TUBE
- ★ BUY DIRECT FROM THE FACTORY
- ★ 18 MONTHS' GUARANTEE

**12 inch £5.0.0 14 inch £5.10.0  
17 inch £6.10.0**

Immediate dispatch on receipt of Remittance  
 Carriage and insurance 12/6 extra  
**£1 Refunded on receipt of your old Tube**

For the benefit of South Coast customers we have an agent in BRIGHTON. See our classified advertisement for further details.

#### SPECIAL TERMS TO THE TRADE

### MARSHALL'S for TELEVISION LTD.

131 St. Ann's Road, Tottenham, London, N.15  
 STAMFORD HILL 3267 & 5555

# 20,000

o.p.v.

MODEL

# 127A

## Pocket Size Taylormeter 127a

**PERFORMANCE  
EQUAL TO A HIGH-PRICED INSTRUMENT**

**ADOPTED by the G.P.O.**

**OUTSTANDING FEATURES:**

- ★ Sensitivity 20,000 o.p.v. D.C. 1,000 o.p.v. A.C.
- ★ D.C. Current 50 $\mu$ A, to 1 Amp.      ★ 20 Ranges.
- ★ D.C. Volts 0.3 v. to 1,000 v. (25 kV by probe).
- ★ A.C. Volts 10 v. to 1,000 v.
- ★ 3 Resistance Ranges from 0-20 megohms (self-contained).
- ★ Meter 40 $\mu$ A 3 $\frac{1}{2}$ in. arc.
- ★ Accuracy D.C. 3%, A.C. 4%.
- ★ Dimensions 5 $\frac{1}{4}$  x 3 $\frac{1}{2}$  x 1 $\frac{1}{2}$ in.

**RETAIL PRICE:**

# £10.0.0

*Credit Sale Terms available*

9 monthly instalments of  
£1.4.4


Complete with instruction Manual  
and interchangeable test prods and  
clips. High quality leather case, if  
required, £2.5.0.  
H.V. Probe for 25 kV ... £5.5.0

Write for fully illustrated literature to:

**TAYLOR ELECTRICAL INSTRUMENTS LIMITED**

Montrose Avenue, Slough, Bucks. Tel: Slough 21381 Cables: Taylins Slough

METAL INDUSTRIES GROUP

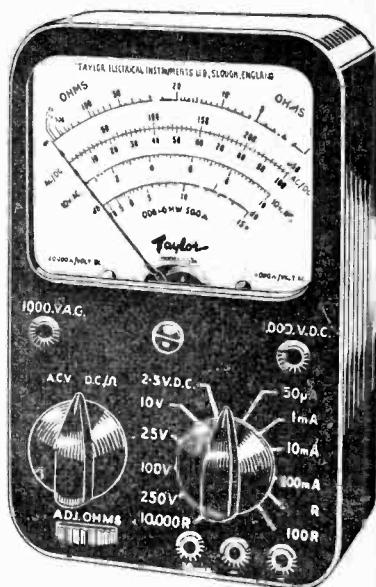

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE. ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.

0A2	17/6	6F1	27/2	2A2C6	15/8	77	81-	DL68	15/-	EF50(A)	7/-	HVR2	20/-	PX4	10/6	UBF89	9/6	Z66	17/6		
OB2	17/6	6F6G	7/-	12AD6	17/8	78	6/6	DL72	15/-	EF50(E)	5/-	HVR2A	6/-	PY31	17/-	UBF89	9/6	Z77	4/6		
OZ4	5/-	6F12	4/6	12AE6	14/3	80	9/-	DL92	7/-	EF54	5/-	KF35	8/6	PY32	12/6	UBL21	23/10	Transistors			
IA5	6/-	6F13	1/16	12AH8	12/6	83	15/-	DL94	7/6	EF73	10/6	KLL35	8/6	PY80	7/6	UCC84	14/11	and diodes			
IA7GT	12/-	6F23	10/6	12AT6	7/6	95A2	15/-	DL96	8/6	EF80	6/-	KL32	25/2	PY81	8/6	UC85	9/6	CG1C	3/-		
IC5	12/6	6F24	12/6	12AT7	6/6	90A2	67/6	DL97	7/6	EF85	6/-	KT2	5/-	PY82	7/6	UCF80	17/6	CG4E	3/-		
ID6	10/6	6F33	7/6	12A7	6/6	90A7	67/6	E80F	30/-	EF86	10/6	KT33C	10/-	PY83	8/6	UCH21	23/10	CG6E	3/-		
IG6	17/6	6H6	3/6	12A7	6/6	90C1	16/-	E83F	30/-	EF89	9/6	KT36	30/7	PY88	13/7	UCH42	9/6	CG7E	7/6		
IH5GT	10/6	6J5	5/-	12AX7	7/6	90CG	37/6	E180F	34/6	EF91	4/6	KT41	23/10	P230	20/5	UCH81	9/6	CG10E	3/-		
IL4	3/6	6J6	5/6	12BA6	8/-	101	13/6	EASO	2/-	EF92	4/6	KT44	12/6	QP21	7/-	UCL81	17/6	CG12E	3/-		
ILD5	5/-	6J7G	6/6	12BE6	9/-	150B2	18/-	EAT6	9/6	EF97	13/7	KT61	12/6	QP25	4/6	UCL83	19/9	CG3	4, 5		
ILN5	5/-	6J7GT	10/6	12BH7	21/9	185BT	34/-	EAC80	9/6	EF98	13/7	KT63	7/-	QS150/15		UF41	12/6	6, 8	4/-		
IN5GT	10/6	6K7G	5/-	12J5GT	4/6	304	10/6	EAC91	4/6	EF183	19/1	KT66	15/-		10/6	UF42	12/6	OA70	3/-		
IR5	6/6	6K8GT	6/6	12J7GT	9/6	305	10/6	EAF42	9/6	EF184	12/6	KT88	24/-	R12	9/6	UF80	10/6	OA73	3/-		
IS4	9/-	6K8GT	10/6	12K5	18/4	807	7/6	EB34	2/6	EK32	8/6	KTW61	6/6	R18	14/-	UF85	9/6	OA79	3/-		
IS5	6/-	6K8G	6/6	12K7GT	5/6	956	3/-	EB41	8/6	EK32	5/6	KTW62	7/6	R19	20/5	UF86	18/4	OA81	3/-		
IT4	3/6	6K25	20/5	12K8GT	14/-	1821	17/6	EB91	4/-	EK33	12/6	KTW63	6/6	RG1/240A		UF89	9/6	OA86	4/6		
IU5	6/-	6L1	23/10	12Q7GT	5/-	4033L	12/6	EBC3	23/10	EK34	15/-	KTZ41	8/-		54/-	UL41	9/6	OA91	3/6		
2P	27/2	6L6G	8/-	12SA7	8/6	5763	12/6	EBC33	5/-	EK38	27/2	KTZ63	7/6	RK34	7/6	UL44	27/2	OA95	3/6		
3A4	6/-	6L6M	9/6	12SCT	8/6	7193	5/-	EBC41	8/6	EK41	9/-	L63	6/-	SP4(7)	14/6	UL46	14/6	OA210	11/-		
3A5	10/6	6L7GT	7/6	12SG7	7/-	7475	7/6	EBC81	8/-	EK42	10/6	MHL4	7/6	SP41	3/6	UL84	8/6	OA211	20/-		
3B7	12/6	6L18	13/-	12SH7	8/6	9002	5/6	EBF80	9/-	EK81	17/6	MHLD6	12/6	SP42	12/6	UM14	17/8	OC16	48/-		
3D6	5/-	6LD20	16/4	12S17	8/6	AC/PEN		EBF83	14/3	EK83	20/5	ML4	8/6	SP61	3/6	UM34	17/8	OC19	48/-		
3Q4	7/6	6M7	8/-	12SK7	6/-	5-pin	23/10	EBF89	9/6	EK84	7/6	MS48	23/10	SU25	27/2	UM80	15/8	OC22	28/-		
3Q5GT	9/6	6P28	27/2	12SQ7	11/6	7-pin	15/-	EBL1	30/6	EK85	14/3	MU12/14	8/-	T41	9/-	URIC	19/1	OC23	87/-		
3S4	7/6	6Q7G	11/-	12SR7	10/6	AC/PEN		EBL21	23/10	EK86	17/8	N37	23/10	TDD4	12/6	U6C	20/5	OC26	25/-		
3V4	7/6	6Q8GT	11/-	12TA	10/6	AC/PEN		EBL31	23/10	EK91	5/6	N78	20/5	TH41	27/2	U88	27/2	OC28	25/-		
5R4GY	17/6	6R7G	10/6	19A5	10/6	AC/PEN		ECS5	5/6	EK95	10/6	N108	23/10	TP22	15/-	UY1N	19/1	OC35	25/6		
5U4G	6/6	6SA7GT	8/6	19A1	10/-	AC/PEN		ECS4	5/6	EK95	10/6	N308	21/11	TP25	15/-	UY21	17/6	OC45	11/-		
5V4G	10/-	6SC7	7/6	20D1	15/8	ATP4	5/-	ECS7	12/6	EK96	19/1	N339	15/-	TP2620	34/-	UY47	7/6	OC65	22/6		
5Y3	6/6	6SG7GT	8/-	20F2	27/2	AZ1	19/1	ECS8	12/6	EK97	12/6	P61	3/6	TY86F	13/7	YMP4G	15/-	OC66	25/6		
5Z3	20/5	6SH7GT	8/-	20L1	27/2	AZ31	10/-	EC92	13/7	EK94	9/6	PCC80	14/3	U12/14	10/6	YMS4B	15/-	OC70	6/6		
5Z4G	9/-	6SI7GT	8/-	20P1	27/2	AZ41	14/3	ECC32	5/6	EM71	23/10	PCC84	8/-	U16	10/6	YP2	12/6	OC72	8/6		
6A7	10/6	6SK7GT	6/-	20P3	23/10	B36	15/-	ECC33	8/6	EM80	9/6	PCC85	9/6	U19	48/6	YP3	12/6	OC74	6/6		
6A8	9/-	6SL7GT	6/6	20P4	27/2	BL63	7/6	ECC34	25/2	EM81	9/6	PCC88	18/-	U22	8/-	YP4	15/6	OC78	8/6		
6AC7	4/-	6SN7GT	5/6	20P5	23/10	CI	12/6	ECC35	8/6	EM84	10/6	PCC89	11/6	U24	30/7	YP2B	14/6	OC79	16/-		
6AG5	5/6	6SQ7GT	9/-	25A6G	10/6	CIC	12/6	ECC40	23/10	EM85	17/8	PCF80	8/-	U25	18/5	YP4B	23/10	OC75	8/6		
6AG7	7/6	6SG7GT	8/-	25L6GT	10/-	CBL1	27/2	ECC81	6/-	EN31	53/-	PCF82	10/6	U26	10/-	YP13C	7/6	OC77	15/-		
6AK5	8/-	6U4GT	12/6	25Y5G	10/-	CBL31	23/10	ECC82	6/6	EY51	9/-	PCF84	17/6	U31	9/6	YP23	6/6	OC78	8/6		
6AL5	4/-	6US7G	7/6	25Z4G	9/6	CCH35	23/10	ECC83	7/6	EY83	17/-	PCF86	15/-	U33	27/2	YP41	6/-	OC81	8/6		
6AM6	4/6	6U7G	8/6	25Z5	9/6	ECC84	9/6	ECC84	9/6	EY84	14/-	PCL82	10/-	U35	27/2	VR105	8/6	OC139	24/-		
6AQ5	7/6	6V6G	7/6	25Z6G	10/-	CL33	19/9	ECC85	8/6	EY86	9/6	PCL83	10/6	U37	27/2	VR150	7/6	OC170	13/6		
6AT6	7/6	6V6GTG	8/-	27U5	20/5	CV63	10/6	ECC88	18/-	EZ35	6/-	PCL84	12/6	U45	13/6	VT61A	5/6	OC171	14/6		
6AU6	10/-	6X4	5/-	28D7	7/-	CY1	19/1	ECF80	10/6	EZ40	7/6	PCL85	17/-	U50	6/6	VT501	5/-	OC200	16/6		
6B8	5/-	6XS7G	6/6	30C1	8/-	CY31	11/-	ECF82	10/6	EZ41	7/6	PCL86	17/-	U52	6/6	W76	5/6	OC203	24/-		
6BA6	7/6	630L2	10/6	30F5	6/-	D15	10/6	ECF86	20/5	EZ80	7/6	PEN4A	23/10	U54	20/5	W81M	6/-	OCP71	29/6		
6BE6	6/-	7B7	8/6	30FL1	10/6	DAC32	10/6	ECH3	27/2	EZ81	7/6	PEN4DD		U76	6/-	W107	19/1	TJ1	40/-		
6BG6G23/10	7C5	8/-	30L1	8/-	ECH21	23/10	FC4	15/-						27/2	U191	17/6	W729	20/5	TJ2	45/-	
6BH6	8/-	7C6	8/-	30L5	11/6	ECH35	6/6	FW4/500	8/6							U201	17/6	W729	20/5	TJ3	50/-
6BL6	6/-	7H7	8/-	30P4	12/-	ECH42	9/6	FW4/800	8/6							U281	20/5	X61(C)	12/6	TP1	40/-
6BQ7A	15/-	7R7	12/6	30P12	7/6	EDT25	7/6	GU50	41/6							U282	23/10	X65	12/6	TS1	10/-
6BR7	12/6	7S7	9/6	30PL1	10/6	DF33	10/6	ECH83	14/3							U301	23/10	X66	12/6	TS2	12/6
6BR8	19/1	7V7	8/6	30PL3	13/6	DF66	15/-	ECL80	9/6							U329	14/-	X76M	14/-	TS3	15/-
6BW6	8/6	7Y4	7/6	35A5	21/9	DF91	3/6	ECL82	10/6							U339	17/-	X79	23/10	TS4	24/-
6BW7	6/-	8D2	3/6	35L6GT	9/6	DF96	8/6	ECL83	19/9							U402	34/-	U339	17/-	TS4	24/-
6C4	5/-	9B9V6	15/8	35W4	7/6	DF97	9/-	ECL86	17/-							PL33	19/9	U403	17/-	U30/10P	28/6
6C5	6/6	9D2	4/-	35Z3	19/1	DH63	6/6	EF9	23/10	HABC80						PL36	12/-	U404	8/6	X109	17/8
6C6	6/6	10C1	13/-	35Z4GT	6/6	DH76	5/-	EF22	14/-							PL38	27/2	U401	30/7	XD(1.5)	6/6
6C9	13/6	10C2	27/2	35Z5GT	9/-	DK32	12/-	EF36	4/-	HL2	7/6	PL81	10/6	U4020	19/1	XFG1	18/5	XAI02	10/-		
6C10	9/-	10F1	27/2	43	10/-	EF37A	6/6	EF37A	8/-	HL2	7/6	PL82	7/6	U4030	9/6	XFY12	9/6	XAI03	15/-		
6CD6G	37/5	10LD11	16/4	50C5	10/-	DK92	9/-	EF39	5/6	HL23DD	7/6	PL83	9/-	UAF42	9/6	XFY34	18/-	XB102	6/6		
6DE	9/6	10P13	15/-	50C6DG		DK96	8/6	EF40	15/-	HL42DD		PL84	13/-	UAF41	12/-	XH(1.5)	6/6	XB103	6/6		
6D6	6/6	10P14	19/9			DL33	3/6	EF41	9/-					19/9	PL820	19/1	UBC41	8/6	XSG(1.5)	6/6	
6E5	12/6	12A6	5/-	50L6GT	9/6	DL66	17/6	EF42	10/6	HN309	25/2	PM84	17/8	UBC81	11/6	Y63	7/6	XC104	7/6		

ALL GOODS BRAND NEW AND SUBJECT TO FULL MAKERS' GUARANTEE. PLEASE NOTE THAT WE DO NOT SELL SECONDHAND GOODS OR MANUFACTURERS' REJECTS.

Standard tubular condensers	MIDGET TUBULAR CERAMIC CONDENSERS	LOW VOLTAGE BIAS CONDENSERS	RESISTORS
-001/1000 v.....9d.    -1/500 v.....9d.	ANY SIZE 9d.	ANY SIZE 1/6	Carbon type, 10% tolerance. 1 watt 6d. 1 watt 9d. Post 6d. doz.
-005 1000 v.....1/3    -1/1000 v..... 2/-			Wire wound types, 5 watt 1/3. 10 watt 1/6. Post 6d. each.
-01/500 v.....9d.    -25/500 v.....1/3			
-02/500 v.....9d.    -5/350 v.....1/3			
-05/500 v.....9d.	METAL RECTIFIERS	Full List with ratings free for S.A.E.	
<b>VOLUME CONTROLS</b>	DRM1B 13/-    RM-1 5/3    1A486 17/6    14B130 35/-    14RA 1-2-8-3 21/-		18RA 1-1-16-1 6/6
Less switch 3/- each.	DRM2B 15/6    RM-2 7/6    1A497 25/-    14B261 11/6    (FC31)		(FC116)
With D.P. switch 4/6 each.	DRM3B 15/6    RM-3 7/9    1A100 27/-    14RA 1-2-8-2 17/6    16R2 2-2-8-1 12/-		18RA 1-2-8-1 11/-
10 K 25 K 50 K 100 K	LW7 21/-    RM-4 14/-    1A124 28/-    (FC101)		18R2 2-2-8-1 15/-
± mg. ± mg. 1 meg. 2 meg.	RM-0 7/11    RM-5 19/6    1A163 38/-    16RC 1-1-16-1 8/6    18RA 1-1-8-1 4/6		(FC124)
<b>JUST OUT. MIDGET SILICON RECTIFIERS. OUTPUT 120 VOLTS AT 1/2 AMP. TWO IN SERIES GIVE</b>			

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the **RIGHT** course:

RADIO & TELEVISION ENGINEERING  
INDUSTRIAL TELEVISION


RADIO & TELEVISION SERVICING  
RADIO SERVICE AND SALES

VHF/FM ENGINEERING : ELECTRONIC  
COMPUTERS & PROGRAMMING

ICS provides thorough coaching for practical examinations:

Brit. I.R.E., City and Guilds Telecommunication Technicians, C. & G. Radio & TV Servicing (R.T.E.B.); C. & G. Radio Amateurs.

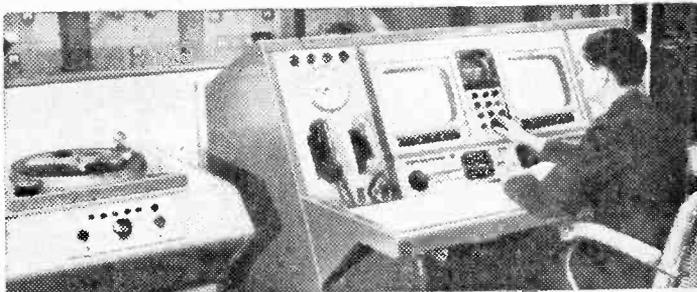*Technical  
Training  
in Radio,  
Television  
and  
Electronics  
Engineering  
with*



**THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.**

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

**LEARN AS YOU BUILD**

*Practical Radio Courses*

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-meter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.

Other ICS courses include:  
MECHANICAL, MOTOR,  
FIRE, ELECTRICAL &  
CHEMICAL ENGINEERING.  
FARMING, GARDENING.  
ARCHITECTURE &  
WOODWORKING.  
SELLING & MANAGEMENT.  
ART. PHOTOGRAPHY,  
etc., etc.

**PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . . .**

**INTERNATIONAL CORRESPONDENCE SCHOOLS**  
(DEPT. 165), INTERTEXT HOUSE, PARKGATE RD., LONDON, S.W. 11

PLEASE SEND FREE BOOK ON.....

NAME .....

ADDRESS .....

.....

OCCUPATION..... AGE.....

11.51

## TUBES DIRECT FROM OUR FACTORY

Due to the increasing demand for our wide range of CRT's and our efficient handling methods we offer unbeatable value.

	6 MONTHS GUARANTEE	12 MONTHS GUARANTEE	12 MONTHS NEW TYPES
Carriette and Insurance 12/6 CRM92, MW22-7, MW22-14, MW22-14C, MW22-17, MW22-18	£1-15	£2-15	MW31/74 £3-10
12PKA, 121K, C12B, CRM121, CRM121A, CRM121B, CRM122, CRM123, MW31-14C, MW31/16, MW31/18, MW31/74	£2	£3-5	
141K, 7201A, C14FM, CRM141, CRM142, CRM143, MW39/24, MW39-44	£2-10	£3-15	MW38/44 MW39/24 £4-10
171K, C17FM, CRM171, CRM172, MW43-64, MW43-69, 7401A, AW43-30, C149M, C17BM, CRM151, CRM152A, CRM152B, CRM163, CRM173, MW43-30, MW41-1, 17A5P4	£3-5	£4-10	CRM172 MW43/64
AW53-30, CRM212, MW53-20, MW53-30	£3-15	£5-15	£6

PLEASE NOTE: Many other types not listed available. S.A.E. enquiries.

**UNIVERSAL VOLT OHM MULTIMETER**  
Reads A.C. and D.C. volts to 1000. 5 ranges at 1000 ohms per volt resistance reading to 200K in 2 ranges. Complete with prods. 59/6 P. & P. 1/6.

**TEST SETS TYPE 74A**  
A service scope easily convertible for standard use. 200/250 v.a.c., all valves, E.C.R.30. tube, excellent case worth £10. Our Price £4.10.

**100 RESISTORS 6/6**  
**100 CONDENSERS 10/-**  
Miniature Ceramic and Silver Mica Condensers, 5pF to 3,500 pF. LIST VALUE OVER £5.

**LINE TRANSFORMERS**  
100's in stock particularly early types, 19/- to 29/-. S.A.E. enquiries.

**CONNECTING WIRE**  
Sold or dex, 25 ft. 15 coils different colours, 50L 1/-, 4/-.

**4-SPD. RECORD PLAYERS**  
Latest B.S.R. TU9 Turntable, together with lightweight Star Galaxy dual sapphire crystal turnover pick-up head. Truly amazing value at £3.10.0 Carr. 3/-.

**COMPLETE RECORD PLAYERS**  
B.S.R. UA8, 4 Speed Autochanger .. 26 15 0  
B.S.R. UA8, 4 Speed Autochanger Stereo .. 26 19 0  
B.S.R. UA8, Autochanger .. 27 19 0  
Garrard 209/210 .. 29 19 0  
EMI 4 Speed Single Player .. 24 12 6  
P. & P. on above 4/-.

**SCREENED COILS**  
Slugged, tagged, standard in. Aladdin Type, 5/- dozen.

**B.B.C./I.T.A. AERIALS**  
Famous make, indoor, local reception, plug straight into standard T.V. socket, listed—amazing value, 7/6. B.B.C./I.T.A. combined 8 element wall mounting, value, 32/6.

## 13 CHANNEL TV'S

TABLE MODELS, FAMOUS MAKERS. Complete with all valves and tubes. Unequaled in value. They are untested and not guaranteed to be in working order.

**AMAZINGLY POPULAR-IDEAL SECOND SET**

**12" - £2.19.** (P. & P. 12/6)

**14" - £4.19.** (P. & P. 15/-)

**12" 5 CHANNEL TV'S 39/-** (P. & P. 12/6)

**14" 5 CHANNEL TV'S 59/-** (P. & P. 12/6)

TUBES ONLY SENT IN U.K.

**CO-AX** standard and low loss, 25 yds., 12/6  
50 yds., 22/6. 100 yds., 42/6.  
Co-ax. Plugs 1/8. Wall outlet boxes 3/6.

**EY51 SHORT ENDS 4/6 U25 SHORT ENDS 8/-**

**MAINS AMPLIFIERS**  
3 valves (10F3, 10P14, UO9), 3 watt, 8in. loud speaker, in two tone cases with controls, ideal for record players. 19/6 P.P. 6/-

**RECTIFIERS** 12 volt 3 1/2 amps., 9/6.  
RM4, 15/6; RM5, 21/-; 14A86, 17/-; 14A97, 23/-; 3A4100, 25/-;  
16CX1-1-16-1, 7/6; 18A1-1-16-1, 7/6; 18R D2-2-5-1, 14/-; 14RA1-2-8-2, 12/-; 8A1-1-2-8-2, 20/-; 5B3-3, 10/6.

**TURRET TUNERS**  
38 Mc. Standard Famous Make, listed £7. Complete PCF80 and PC084 valves. Ex-equipment. 15/- (Carr. 3/-).

# ★ VALVES BY RETURN OF POST ★

THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY

10% DISCOUNT TO PURCHASERS of any SIX VALVES marked in black type (15% in dozen). Post: 1 valve, 6d., 2-11, 1/-.		SPECIAL OFFER		NEW LOW PRICES GUARANTEED 3 MONTHS		FREE TRANSIT INSURANCE. All valves are new or fully guaranteed ex-Government or ex-equipment origin. Satisfaction or Money back Guarantee on goods if returned unused within 14 days.										
024	5/- 1A07	4/3 6B6	2/- 6V6G1	5/6 120C	6/6 35Z5GT	7/8 DA9F1	3/6 ECC34	9/- EL41	8/- N78	15/- 5U2150A	UCLK3	13/6				
1A5GT	11/3 1A07	8/3 6J5	4/3 6V6GT	6/1 12E1	10/8 42	7/8 DA9F6	7/3 ECC35	9/- EL42	9/- N103	16/-	UF11	8/6				
1A7GT	11/3 1A07	7/3 6J5	4/3 6V6GT	6/6 12J3GT	7/6 43	7/8 DF33	9/3 ECC41	5/8 EL134	7/6 N152	8/9 T41	4/6	UF42	5/6			
1C3GT	8/6 6AK5	5/- 6J5GT	5/8 6X4	6/1 12K7GT	4/9 50K3	7/8 DF91	3/6 ECC82	6/8 EL191	4/6 P41	4/6 TDD4	7/6	UF80	7/6			
1D5	8/6 6AL5	6/3 6J6	4/- 6X5C3	5/6 12K9T	11/- 30L8GT	6/6 DF96	7/6 ECC83	6/8 EM34	8/6 P61	2/3	U4	8/6	UF86	8/6		
1D6	9/9 6AM9	8/- 6J7	7/8 6X5GT	5/6 12K5	12/- 32K10	10/6 DH63	6/3 ECC84	7/8 EM90	7/6 P63	3/6	PABC0117	U82	8/6	UF86	14/6	
1H5GT	8/6 6A05	6/- 6J7G	5/- 6Y9G	7/8 12Q7GT	5/- 33K10	10/6 DH76	5/- ECC85	7/8 EM81	8/9 PCC4	7/6	U22	6/9	UF89	7/6		
1H4	8/6 6A70	5/- 6J7GT	7/6 7B5	12/6 12Q7GT	6/- 34K10	8/9 DH77	5/- ECF80	8/6 EM84	8/9 PCC5	7/3	124	15/-	UL41	7/6		
1H3	3/6 6A09	7/6 6J8	8/6 7B6	9/- 12S17	5/6 618PT	11/- DK32	11/8 ECF82	8/6 EM84	9/9 PCC8	10/-	U26	9/6	UL46	11/-		
1N5	4/6 6B7	8/6 6K6GT	8/6 7B7	7/3 12S8K	4/- 75	8/- DK91	5/6 ECH21	12/6 EM85	10/6 PCC9	13/6	U26	9/6	UL54	7/6		
1N5GT	9/9 6B9G	8/6 6K7	5/6 705	7/1 12S7GT	8/6 77	6/6 DK92	7/8 ECH86	8/6 EN31	16/- PPF82	7/3	U35	11/-	UM90	9/6		
1R5	6/- 6BA6	6/- 6K7G	2/3 706	7/3 12Z5	9/- 74	6/6 DK96	7/3 ECH42	7/9 EY51	8/6 PCL82	7/3	U37	28/-	U06	10/-		
1R4	8/- 6B9B	5/9 6K7GT	4/9 7H7	7/3 1487	22/6 90	5/9 DL33	8/6 ECH11	7/9 Small	8/6 PCL83	10/6	U43	8/6	U07	9/6		
1S5	4/6 6B0G	12/6 6K5GT	5/8 7K7	9/6 15A35	7/6 83	6/6 DL35	9/6 ECL82	8/9 EY35	6/6 PCL84	7/6	U50	6/9	U08	17/-		
174	3/9 6BH0	6/- 6L1	12/6 7Q7	7/8 18B0G16	1-45BT	15/- DL37	8/6 ECL38	12/6 EY40	6/6 PEN25	4/6	U52	4/9	UY1N	11/-		
2A3	7/9 6B9	6/- 6L8	9/9 787	9/- 20D1	8/6 807(A)	5/6 DL91	8/6 EFL37	12/6 EY41	7/6 PEN45	7/3	U78	5/6	UY21	11/-		
2121	4/6 6B7	9/3 6L0G	6/9 7V7	6/- 20F2	6/6 807(B)	8/3 DL92	6/- EF22	7/- EY41	7/6 PEN46	5/3	U78	5/6	UY41	8/-		
3A4	9/9 6B9G	7/9 6L18	8/6 7Y4	6/3 30L1	16/- 809	15/- DL94	6/- EF26	3/3 EY20	6/6 PL33	8/3	U81	11/-	UY85	6/6		
8Z3	9/- 6B7	5/9 6L19	12/6 7Z4	6/3 30P1	9/6 854	2/- DL98	7/8 EF39	4/3 EY21	6/6 PL36	10/6	U281	9/6	VR105/30	8/6		
809	4/6 6B6K	4/6 6L12	8/- 8D3	3/- 30P2	12/6 855	9/6 EA30	8/6 EF40	13/6 EY32	8/9 EF41	3/6	HL41DD	PL38	15/6	VR105/30	8/6	
824	7/- 604	3/6 6L13	7/6 10C1	11/- 20P1	17/- 958	2/6 EA00	7/6 EF42	7/6 HL41DD	7/6 HL41DD	7/6	PL81	8/6	U309	7/6	VR150/30	8/6
305GT	3/8 6C3	5/6 6L12D	8/6 10C1A	6/6 20P0	15/- 5763	10/- EA91	4/6 EF42	7/6 HL41DD	7/6 HL41DD	7/6	PL85	7/6	U329	7/6	VR150/30	8/6
381	3/6 6C5	4/9 8N7	8/6 10F1	5/9 35A9G	8/- 9001	4/- EA42	3/6 EF50-BR	8/6 K185	7/6 PL82	6/9	U330	6/9	U309	7/6	VR150/30	8/6
371	6/9 6C9	9/9 6P1	14/- 10L14	7/9 35L6G	9/9 9002	4/9 EB34	1/6 EF50-USA	8/6 K78C	4/9 PL84	9/6	U309	6/9	U404	6/6	VR150/30	8/6
6H4G	9/6 6C0BG	21/- 6P25	8/6 10L13	7/9 35L6G	9/9 9003	4/- EB41	7/6 EF50-USA	8/6 K78C	4/9 PL84	9/6	U309	6/9	U404	6/6	VR150/30	8/6
674	9/9 6C0G	8/3 6P28	12/6 10L11	13/9 35Y3G	8/- AT4	2/9 EB91	3/6 EF50-USA	8/6 K78C	4/9 PL84	9/6	U309	6/9	U404	6/6	VR150/30	8/6
6D4G	4/9 6D1	9d. 6Q7G	6/- 10L12	8/6 35Z4G	7/8 AT4	8/6 EB93	9/- EF54	3/3 K744	6/3 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
5V4G	8/9 6D2	3/6 6Q7GT	8/9 10P18	9/- 35Z5	8/- 838	8/6 EB93C	4/9 EF80	4/9 K745	8/6 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
6Y3GT	6/- 6D8	12/6 6B7G	6/- 10P14	9/- 35Z6	12/- 865	4/9 EB94	4/9 EF80	4/9 K745	8/6 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
6Y4G	11/- 6P1	4/9 6S47	4/9 12A6	5/- 30C1	7/8 CB131	21/- EB99	7/8 EF99	8/6 K763	3/3 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
6Z3	8/3 6P6G	5/9 6S47	4/9 12A7H	8/9 30P5	6/9 CCH35	14/- EB99	8/6 EF92	4/9 K763	3/3 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
6Z4	11/- 6P6M	7/- 6S7	4/9 12A8H	9/9 30P1	9/6 CL33	11/9 EB121	12/6 EF92	4/9 K763	3/3 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
6Z5	8/6 6P6J	8/6 6S7K	6/3 12A7H	7/8 30L1	7/- CY31	7/6 EB131	21/- EF95	6/8 K763	3/3 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
6Z6GT	11/- 6P12	6/6 6S7GT	6/- 12A7T	5/6 30P2	12/6 958	9/6 EA30	8/6 EF40	13/6 EY32	8/9 EF41	3/6	HL41DD	PL38	15/6	VR105/30	8/6	
6A5	7/6 6P13	6/9 6S7GT	6/- 12A7G	6/- 30P12	3/- D77	8/6 EB32	3/6 EF99	8/6 K763	3/3 PX25	11/6	UACB80	8/6	U43	8/6	VR150/30	8/6
6A7	10/- 6P14	9/6 6S7G	6/- 12A7T	6/9 30P16	6/9 D152	5/6 EC91	4/6 EL33	7/- LZ319	7/6 SP1	2/6	U43	8/6	U43	8/6	VR150/30	8/6
6A8G	9/6 6P15	9/6 6S7T	4/9 12A6	8/- 35L6GT	9/- DA90	2/6 EC91	4/6 EL33	7/- LZ319	7/6 SP1	2/6	U43	8/6	U43	8/6	VR150/30	8/6
6A9GT	12/- 6P18	8/6 6H4GT	10/9 12B8E	8/6 35W4	5/9 DA90	2/6 EC92	4/6 EL33	7/- LZ319	7/6 SP1	2/6	U43	8/6	U43	8/6	VR150/30	8/6
6AB8	7/- 6P33	6/6 6H33	6/3 12B7H	10/6 35W4T	5/9 DAC92	9/9 ECC33	4/6 EL38	12/6 N87	11/- SP1	2/6	U43	8/6	U43	8/6	VR150/30	8/6

Post: 2 lbs. 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6, etc. No. C.O.D. ALL ITEMS 5% & POST FREE IN DOZENS (Callers always welcome). LIST OF 1000 SNIPS 6d. P.O. BOX 21 (W) 350-352 FRATTON ROAD, PORTSMOUTH.

# TECHNICAL RADIATING CO.

# THE GREATEST MONEY-MAKER EVER OFFERED TO THE RADIO MAN!

ALL THE CIRCUITS, DIAGRAMS, REPAIR DATA  
AND INFORMATION YOU NEED FOR NEARLY

## 2,700 Models

COMPLETE IN 7 VOLUMES

TELEVISION · RADIO · RADIOGRAMS · CAR RADIOS  
TAPE RECORDERS · RECORD REPRODUCERS

Newnes RADIO AND TELEVISION SERVICING provides at instant call, any time, day or night, all the circuits and data you need for almost all the popular TV and Radio sets in use. It is the only complete library of servicing data and worth its weight in gold!

1954-1961 Popular Models—Over 4,400 Pages

Servicing Data for all these makes—Ace, Alba, Ambassador, Argosy, Armstrong, Baird, Banner, Beethoven, Berec, Brayhead, B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, E.M.I., Emerson, English Electric, Ever Ready, Ferguson, Ferranti, Ford Motor Co., Garrard, G.E.C., Gramdeck, Grundig, H.M.V., In-victa, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola, Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Phillips, Pilot, Portadyne, Portogram, Pye, Pye Telecommunications, Radiomobile, Rainbow, Raymond, Regentone, R.G.D., Robert's Radio, Sobell, Sound, Spencer-West, Stella, Strad, Ultra, Valradio, Vidor, Walter, Webcor.

Every purchaser is entitled to 2 years free postal advisory service




TEST IT ON  
7 DAYS

# FREE TRIAL

ABSOLUTELY NO  
OBLIGATION TO BUY

Make sure of seeing this great profit-maker in the quiet of your own home.

ACT TO-DAY

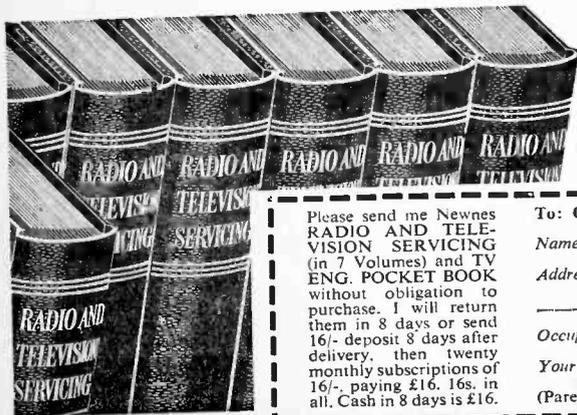

**FREE!** TELEVISION ENGINEERS' POCKET BOOK (Value 12/6)

This 272-page book is the perfect companion to your servicing set. Covers basic circuitry fault-finding, interference, alignment, valves, etc. Presented to you with Newnes RADIO & TV SERVICING.

Please send me Newnes RADIO AND TELEVISION SERVICING (in 7 Volumes) and TV ENG. POCKET BOOK without obligation to purchase. I will return them in 8 days or send 16/- deposit 8 days after delivery. then twenty monthly subscriptions of 16/- paying £16. 16s. in all. Cash in 8 days is £16.

To: George Newnes, Ltd., 15-17 Long Acre, London, W.C.2.

Name \_\_\_\_\_

Address \_\_\_\_\_

Occupation \_\_\_\_\_

Your Signature \_\_\_\_\_

(Parent signs if you are under 21) **RV5X**

Tick (✓) where applicable

HouseOWNER	<input type="checkbox"/>
Householder	<input type="checkbox"/>
Living with Parents	<input type="checkbox"/>
Lodging Address	<input type="checkbox"/>

# REPLACEMENT TUBES

REBUILT CATHODE RAY TUBES ARE NOW USED BY  
OVER 80% OF RETAIL SERVICE DEPARTMENTS  
AND RENTAL ORGANISATIONS

FOR QUALITY, RELIABILITY AND SERVICE BUY FROM BRITAIN'S  
LEADING GROUP OF INDEPENDENT MANUFACTURERS OF REBUILT  
CATHODE RAY TUBES

**SUFFOLK TUBES LIMITED**  
1/3 UPPER RICHMOND ROAD  
PUTNEY, S.W.15.  
Tel: Vandyke 4304/5267

**MIDLAND TUBES LIMITED**  
37 GEORGE STREET  
MANCHESTER, 1.  
Tel: Central 4568/9

**VIDIO REPLACEMENTS LIMITED**  
25 ADDINGTON SQUARE  
CAMBERWELL, S.E.5.  
Tel: Rodney 7550/7559

ALL TYPES - KEEN PRICES - PROMPT DELIVERY  
WRITE FOR BROCHURE

**Scotts Radio Ltd.**  
4 Church Street  
Brighton  
Tel: Brighton 26891

**Weston Hart Ltd.**  
236/8 Fratton Road  
Portsmouth  
Tel: Portsmouth 24125

**Lawsons Ltd.**  
36 Cornhill  
Bury St. Edmunds, Suffolk  
Tel: Bury St. Edmunds 3304

**J. H. Sunderland**  
11 Clements Street  
Rochdale, Lancs.  
Tel: Rochdale 48484

**Wizard Productions**  
16 Withy Grove  
Manchester  
Tel: Dea 2772

**J. Charlesworth & Son**  
14 Hightown  
Crewe, Cheshire  
Tel: Crewe 2535

**Taylor's**  
162 Eastney Road  
Milton, Portsmouth  
Tel: Portsmouth 35000

**Wanda Electrics**  
9 Manor Road  
Gravesend  
Tel: Gravesend 3766

**Stowmarket Co-operative**  
Bury Street  
Stowmarket, Suffolk  
Tel: Stowmarket 51/52

**Frank H. Hunt & Co.**  
Stepcote Hill  
Exeter, Devon  
Tel: Exeter 56687

**H. Knowles**  
54/56 Chester Road  
Manchester  
Tel: BLA 9031

**Radio Services Ltd.**  
30 Mona Street  
Amlwch Anglesey  
Tel: Amlwch 594

**Hi-Lite Ltd.**  
89 Southbourne Grove  
Southbourne, Bournemouth  
Tel: Bournemouth 44344

**R. Watson**  
Leathern Bittel  
Wavenden, Woburn Sands, Bucks  
Tel: Woburn Sands 2027

**R.E.S. Ltd.**  
17/19 Paynes Lane  
Coventry  
Tel: Coventry 28781

**Gwalia Radio & T.V.**  
Llanstephan  
Carmarthen  
Tel: Llanstephan 284

**J. Wildbore Ltd.**  
6-12 Peter Street  
Oldham  
Tel: Mai 4475

**Tele-Car Ltd.**  
66 Osborne Street  
Glasgow, C.1  
Tel: Bell 1912/3

# Practical Television

AND TELEVISION TIMES

VOL. 12, No. 134, NOVEMBER, 1961

Editorial and Advertisement  
Offices:

**PRACTICAL TELEVISION**

George Newnes Ltd., Tower House  
Southampton Street, W.C.2.

© George Newnes Ltd., 1961

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

## SUBSCRIPTION RATES

including postage for one year

Inland - - - - £1.50 per annum  
Abroad - - - - £1.3.6 per annum  
Canada - - - - £1.2.0 per annum

## Contents

	Page
Editorial ... ..	63
Telenews ... ..	64
Servicing TV Receivers ... ..	66
The "Lines" Battle ... ..	68
TV Aerials ... ..	70
The Practical Television Multimeter ... ..	73
How TV Sets Work ... ..	76
A Precision Wobbulator ... ..	81
Improving Receivers with Frame Grid Valves ... ..	84
Tracing TV Faults ... ..	87
Trade News ... ..	92
Underneath the Dipole ... ..	95
Letters to the Editor ... ..	99
Metal Rectifiers and Crystal Diodes ... ..	100
Your Problems Solved... ..	103

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscript, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television", George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

## New Standards

THE repercussions of the many claims made at this year's Radio Show regarding sets which were supposed to be convertible, have now made themselves felt. As we expected, many of the public were confused by the various claims, and so much doubt seems to have arisen that we include in this issue a detailed account of the many problems involved, and their possible solution. There did not seem to be a single manufacturer at the Show who mentioned the fact that any convertible receiver will have to be fed from a new aerial system. The higher definition cannot be obtained using the present frequencies, and, as stated in our article "The 'Lines' Battle", any improvement will have to be in Bands IV or V, and this will entail a new aerial system, in addition to the tuner and modified circuitry. We feel sure that many prospective purchasers of these convertible receivers, whilst not unwilling to purchase at a later date a tuner for the receiver, would be unwilling to put up another aerial. This latter fact should, we feel, have received more emphasis in the various manufacturers' advertisements and receiver details as we are sure that it is a very important point so far as the house-owner is concerned. An enthusiastic listener and viewer will already have Band I, Band II and Band III aerials, and the addition of yet another may present difficulties, not so much from its size, as it will in its simplest form be quite a small assembly, but in its actual location to avoid interaction between other aerials. In fringe areas, the difficulty will become most pronounced unless some new type of aerial, equally efficient on all bands, can be developed. Some of the novel aerials from America may make their appearance here, as some (not all) appear to offer some relief from the mass of aluminium tubing which is seen on some houses in certain parts of this country.

However, as no definite progress can be made in the direction of a new line standard, or with colour, until the report of the Pilkington Committee is issued, we feel that it is once more necessary to recommend that some sort of interim report should be issued as soon as possible, not only in the interests of the manufacturer, but also in the interests of the viewer.

## A FILM SHOW

ANOTHER film show has been arranged in collaboration with Mullard Ltd. It will be held at Caxton Hall, Westminster, and readers are invited to send for their free tickets which are now available from these offices. The films will be shown on Friday, February 2nd, 1962, and the programme will begin at 7.30 p.m. When applying for tickets, enclose a stamped addressed envelope (at least 3½ in. x 6 in.). Mark your envelope "Caxton Hall" in the top left-hand corner.

Our next issue, dated December, 1961, will be published on November 22nd

# Telenews

## Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of August, 1961, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London .. .. .	1,950,384
Home Counties .. .. .	1,601,539
Midland .. .. .	1,729,134
North Eastern .. .. .	1,845,992
North Western .. .. .	1,507,521
South Western .. .. .	982,867
Wales and Border Counties .. .. .	694,776
Total England and Wales .. .. .	10,312,113
Scotland .. .. .	1,040,916
Northern Ireland .. .. .	169,025
Grand Total .. .. .	11,522,054

## Czechoslovakian Trade Fair

AS part of their stand at the Brno International Trade Fair, Czechoslovakia, from September 10th to 24th, EMI demonstrated their Image Orthicon television camera channel type 203/6. This camera was mounted on a remotely controlled pan and tilt head and fitted with a remotely controlled zoom lens. The equipment also included a shot selection box which enables a series of pre-selected shots to be put into sequence merely by pressing buttons.

EMI also exhibited tape recorders, electronic computers, instruments, etc.

## TV at Bingo Sessions

WEEKLY Bingo sessions are televised for thousands of players as they sit checking their numbers in bars and restaurants all over the stadium at Clapton dog track.

As winning numbers are called they are shown on a board in the middle of the track. But because this board is out of sight for many of the players, a Marconi closed circuit camera is being used to show it simultaneously on over a

dozen TV receivers in different parts of the stadium.

## International Control Room at the Television Centre

THE BBC has recently brought into operation a new Television International Control Room at its Television Centre in London. The Control Room replaces the Continental Control Point at Broadcasting House and marks a further stage in the concentration of the BBC's main television activities in London at a single centre.


The BBC's technical and programme control in vision and sound is carried out in the new Control Room in which are now centred the operations involved in contributing programmes, often with commentaries in many foreign

languages, to the Eurovision network, and in receiving programmes from it.

Positions are provided at a control desk for the senior television engineer, vision engineer, presentation assistant, and sound engineer. Facing the inner side of the desk, and remotely controlled from it, are six 21in. multi-standard picture monitors, below each of which is a visual indication of the source of programme. The room also contains apparatus bays and the area is fully equipped with test apparatus.
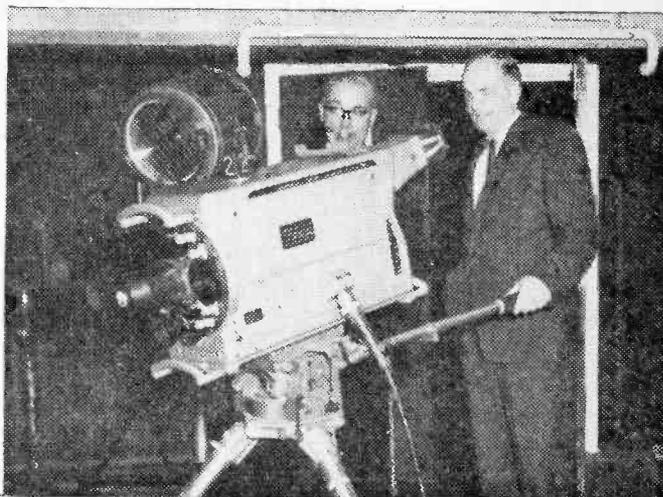
## Television for New Liner

THE new passenger liner "Northern Star", of the Shaw Savill Line, will be fitted with a television system providing



Among recent visitors from overseas to Marconi's was Mr. G. Stringer, assistant director to broadcasting, New Zealand Broadcasting Services. He is pictured here (right) examining a Marconi Mark IV Image Orthicon television camera at the company's television laboratories near Chelmsford. Marconi's have supplied a number of transmitters and a quantity of studio equipment, including Mark IV cameras, for New Zealand's new television service.

a completely co-ordinated internal and off-air service all over the world. This is to be supplied and installed by Marconi's Wireless Telegraph Co. Ltd.

Passengers on the "Northern Star" will be able to receive local television programmes at ports of call, and will also have the added facility of closed-circuit telecine and live television programmes while the liner is at sea.

#### Surgeons See Operation on Colour TV

TWO thousand surgeons from all over the world were able to see colour television pictures of delicate surgical operations on an 8ft by 6ft screen, whilst attending meetings of the International Society of Surgery and the International Cardio-Vascular Society, in Dublin, from September 6th to 9th.


EMI Electronics Ltd.'s colour television cameras, controlled from the EMI colour TV mobile unit, televised the operations at St. Vincent Hospital, and the colour pictures were transmitted by microwave link to the Coffey Memorial Hall of Dublin's University College.

#### TV Cameras for ITN

THREE of the four Marconi Mark IV television cameras ordered by Independent Television News are now in use at the ITN headquarters in Television House, Kingsway, London. By November all four cameras will be fully operational in a new studio which is being built on the eighth floor of Television House. This is part of a general re-equipment of ITN's facilities to enable them to carry out more ambitious programmes. When the new installation is completed the main studio will have three Mark IV cameras with provision for a fourth, if required, in a small interview studio on the seventh floor.
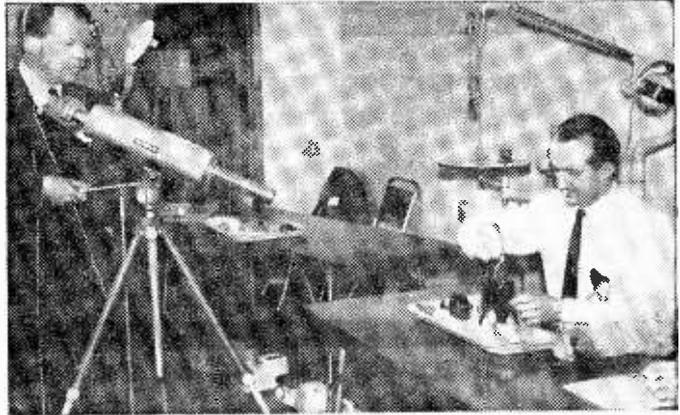
#### ITV for Wales

SOME 738,000 people in the South-Western and North-Western areas of Wales will be able to watch Independent Television programmes for the first time by the end of 1962. The Independent Television Authority has placed contracts with EMI Electronics Ltd. to supply and erect aerials and masts in Carmarthen and Caernarvon, which



Closed circuit television by Marconi played an important part in the 16th Australian Dental Congress, held recently in Sydney. Delegates to the Congress were able to see the newest techniques and equipment developments demonstrated by leading Australian and overseas experts. This picture shows one of the practical clinics in progress. In an adjoining hall a large audience is watching the demonstration on the screens of the viewing monitor.

are scheduled to be completed by next July.

On the Prescelly Mountains in Carmarthen, a 40ft aerial array on a 750ft mast will transmit Channel 8 programmes at good strength to South-West Wales.

A 1,000ft mast in Caernarvonshire will carry a 60ft aerial array which will supply Channel 10 programmes to North-West Wales. The programme contractor for both stations will be the Wales Television Association.

Both aerials will be horizontally polarized.

#### TV Aerials for Liners

TWO broadband aerial arrays designed by Belling-Lee are used on board the 45,270 ton "Canberra" owned by P. & O. Orient Lines. These aerials enable the ship to pick up programmes on all possible channels of the world's television. The 42,000 ton "Oriana", is equipped with similar aerials and television systems.

The television installation provides for the reception of television broadcasts employing the 405-line system used in Britain, the 625-line system used in Australia and the greater part of Europe, and the 525-line system used in the United States, Canada, Japan and some South American countries.

Where alternative programmes are available, viewers can change from one channel to another by

using the normal channel selector on the receiver.

The "Canberra" carries more than 3,200 passengers and crew, and has fifty television receivers installed with provision for a further three hundred.

#### Sound Equipment for TV Centre

A NEW 24-channel sound mixing system is to be supplied under an order placed by Tyne Tees Television with Pye T.V.T. Ltd., of Cambridge. This system will be used for Studio One in the Television Centre, Newcastle Upon Tyne.


The use of transistors throughout has meant a considerable reduction in the size of the amplifiers over conventional valve types; and there is easy access to all components for servicing.

The equipment, which will replace the existing 14-channel sound installation in TTT's Studio One, will give the sound department many more facilities than they have had in the past. The equipment will be delivered and installed in the summer of 1962.

#### TV Aerial System on Bognor Estate

FOR the 800 bungalows and flats of Bognor Regis' Westmeads Estate, a wired television system has been installed with the gas, water and electricity. This is to preserve the amenities of the estate against disfigurement of unsightly aerial arrays.

# Servicing Television Receivers

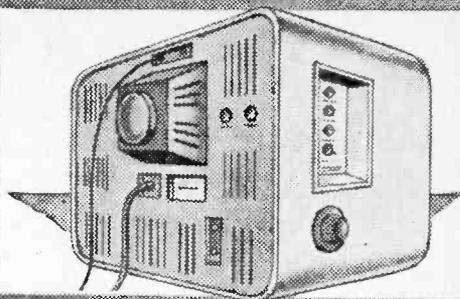

No. 73—THE ENGLISH ELECTRIC 16T11D AND SERIES

By L. Lawry-Johns

THE other receivers in this series are the 16T18 and the 16C19D, the former a table model as is the 16T11D, the latter a console. The fringe versions 16T11F, 16T18F and 16C19F use a much modified circuit with an extra I.F. stage and flywheel line sync. Also, the EF80 line oscillator is removed, its place being taken by two ECC81 valves, an extra stage of vision and sound I.F. employs the EF80.

## Tube

These receivers use a 16in. circular metal cone tube, English Electric type T901A or T901B, the direct Mullard equivalent being the MW41-1. Details have been given in past issues of *Practical Television* for fitting 17in. rectangular tubes, modifying the front cradle and EHT connection.

Points of interest are the two R.F. stages before the frequency changer and the use of a voltage doubler system for EHT. The stage gain is not as great as might be expected from the number of valves employed and this is almost certainly due to the type of I.F. coupling. High-Q band-pass coils would no doubt have provided a much enhanced performance. For this reason it is best to modify V3 to an extra I.F. amplifier when fitting one of the conventional turret tuners. Whilst plugging the

mixer plug or adaptor into the V3 socket is a much simpler method this is unlikely to give the performance required except in strong signal areas. The writer would suggest the V3 stage be modified as follows. Wire a  $0.005\mu\text{F}$  capacitor from pin 8 to chassis. Remove L3 from V2 anode circuit and connect this from pin 2 (V3) to chassis, removing C11 and R14. Disconnect pins 1 and 3 (V3) from chassis and connect to pins 1 and 3 of the V2 base. Connect a  $0.005\mu\text{F}$  condenser from pins 1 and 3 (V3) to chassis. Valves V1 and V2 are removed, pins 4 and 5 used as heater supply for the tuner on one base and shorted on the other. The H.T. for the tuner is taken from pin 7 of the V1 base. The I.F. output of the tuner connect to pin 2 of V3 with L3, screening to chassis of course. L3 is tuned down to about 37Mc/s by screwing in the iron-dust core. The gain of V3 is then pre-set with sensitivity control to the required level; note that the tuning of L3 is slightly upset by the sensitivity setting.

## EHT System

The EHT system is worthy of close study since trouble is almost bound to be experienced in this section, usually due to one or more of the  $0.001\mu\text{F}$  6kV capacitors becoming leaky. This results in a


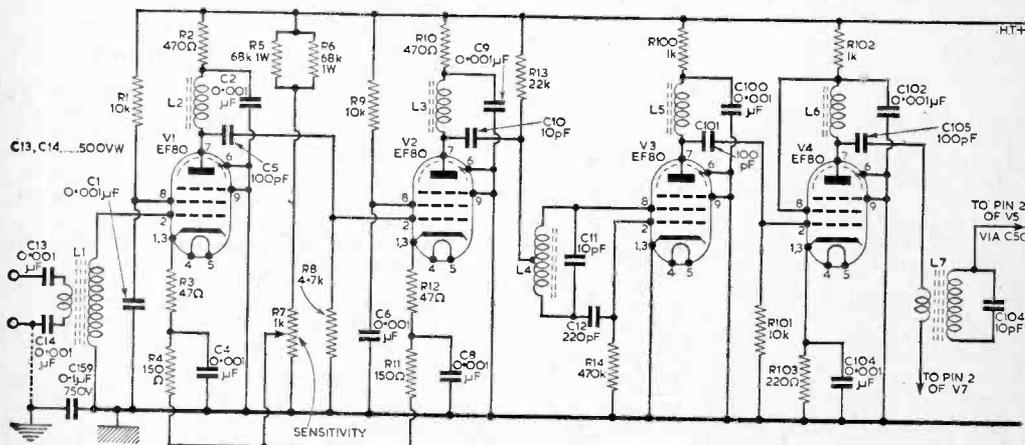


Fig. 1.—The circuit of the R.F. frequency-changer and vision I.F. stages.

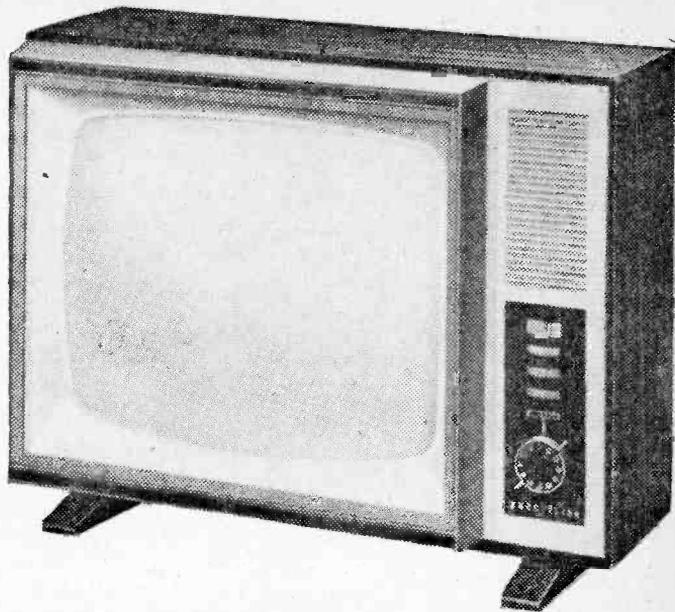

405  
or  
625?



(Above).—This receiver may be used on the present 405-line standard, but may be adapted for 625-line transmissions should this become necessary.

# The "Lines" Battle

THE TRUTH BEHIND THE PRESENT  
CONTROVERSY

By J. Harwood

**E**VEN though there will not be a final decision on the future of television broadcasting for some time, most manufacturers have recently launched so-called "convertible" receivers. In essence, these operate normally on the existing 405-line standards and are designed towards the possibility of conversion to 625 lines.

## Switched Design Not Possible

At the outset, one must fully appreciate that it is impossible for any manufacturer to launch a set on the British market which may be switched from 405 to 625 lines, and vice versa, for the simple reason that no decision has yet been given on the type of transmission standards that would be used should, in fact, the Pilkington Committee eventually recommend a change to 625 lines.

Basically, a change from 405 lines to 625 lines is not difficult in itself. Basically, it means that the line timebase would have to be switched from 10kc/s to 15kc/s. With a frame timebase frequency

of 50c/s, as it is at present, and the correct signal applied to the set, then a picture of either 405 lines or 625 lines could be produced by the turn of a switch.

However, to give a 625-line picture on an existing receiver so adapted, the characteristics of the picture signal, apart from the sync pulses, of course, would need to be identical to those of the 405-line signals. That is to say, the signals would have to operate in the existing Band I and Band III channels; the spacing between the sound and vision carriers would have to be 3.5Mc/s; the vision bandwidth would have to be the same as at present; the vision modulation would have to be positive; the existing sound/vision frequency relationship (i.e., vision 3.5Mc/s above sound) would have to be maintained, and also the existing A.M. sound system would have to be retained. With all these factors constant on both services, then 405/625 switching could be accomplished in the line timebase alone.

*405-line system to be retained for some years to come*

The Government has promised that even in the event of a change of television standards, 405-line transmissions would continue in parallel with the new system for a number of years. One can be sure, therefore, that 405-line sets purchased today

will still be suitable for reception in this country for, at least, five years, and most likely for double this time, even though they are not "switchable" or "convertible".

Now, since the existing standards are to be maintained it is impossible to launch a second 625-line service in Bands I and III because almost all the channels in those bands are already occupied by the existing services. This means, then, that any new service will have to operate in new bands, and the two which are available are Bands IV and V. These bands, in fact, have already been set aside for the development of the television service and embrace frequencies from 470-585Mc/s and 610-960Mc/s respectively.

The upper part of Band V is at present being used for work on tropospheric scatter, but when the whole of this band is available for television, no less than 92 separate television channels could be accommodated in the two bands with the existing channel bandwidth (i.e., 5Mc/s).

#### Conversion Also Requires UHF Tuners

Clearly, it is not enough simply to switch the line timebase, even assuming that the fundamental transmission standards are maintained, for it will be necessary also to have some sort of VHF/UHF switching. Some of the new convertible sets provide both for timebase switching and UHF switching, but the UHF tuner is not usually installed, as it is envisaged that this will be an entirely separate unit, possibly reminiscent of the Band III Converter days.

#### The CCIR System

There would be many more complications if it were eventually decided to adopt the CCIR 625-line system, for the standards of this system differ considerably from those at present used in Great Britain. Apart from the number of lines, the essential differences between the two systems are a channel width of 7Mc/s (British 5Mc/s), resulting in 5.5Mc/s spacing between the sound and vision carriers compared with the British 3.5Mc/s; a reversal of the positions of the sound and vision carriers (the sound is "high" on the CCIR system); F.M. sound instead of A.M. and negative vision modulation against the positive modulation of the British system. In the CCIR system this means that peak white is represented by zero modulation and that the sync pulses are 100% modulation—exactly the opposite of the British standard.

The CCIR system is used in most of Western Europe, excluding France. The French system uses 819 lines and has other differences in channel width, spacing, etc., but uses A.M. for sound. There are other standards, including a 625-line system used in Russia, East Germany, Hungary, Czechoslovakia and Poland, and the 525-line FCC system is used in the U.S.A., Canada, Iran, Japan, Thailand and certain Latin American countries. The Russian system is almost the same as the CCIR system, but the channel width is 8Mc/s and the channel spacing 6.5Mc/s.

#### UHF Standards

It was agreed at a CCIR Conference on frequency allocation that a standard of 8Mc/s channel spacing

with 6Mc/s vision bandwidth be adopted in Bands IV and V in the event of a British 625-line system being launched in these bands. Even with such a wide spacing, 57 channels could still be accommodated in the two UHF bands.

It will now be understood that if the slightly modified CCIR system is finally adopted in Great Britain, set conversion will represent considerably more than a mere change of line frequency coupled with facilities for UHF reception. Indeed, in some cases, the term "convertibility" could well mean a complete change of chassis or, at least, the inclusion of a entirely new vision strip and UHF tuner.

#### Flywheel Sync

Since the sync pulses in the CCIR system are positive-going, they are more susceptible to interference and noise than are the negative-going pulses of the British system, and for this reason it has been found almost essential to include flywheel line sync in sets operating on a negative-going picture signal to avoid "line tearing".

It will be recalled that flywheel sync was very popular in Great Britain some years ago, but with improved signal coverage its popularity has waned somewhat. Although impulsive interference may

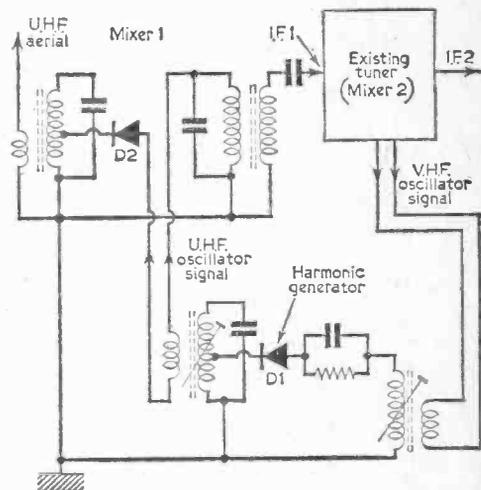


Fig. 1.—The components of this UHF segment are mounted on a biscuit moulding. The oscillator signal is increased in frequency by D1, and this is mixed with the UHF signal in D2 to give I.F.1.

not be very troublesome at UHF, first stage noise may well be sufficient to cause "ragged verticals", particularly since there is likely to be a large number of fringe areas when the service is first launched.

#### Intercarrier Sound

There is also the possibility that intercarrier sound will be used on the new system. This arrangement is used in America and the sound I.F. is taken right through the video amplifier, where it is extracted by beating it against the vision I.F. and then detecting it in the usual F.M. manner.

(To be continued)

# TV AERIALS

FROM the theoretical aspect, one usually looks upon an aerial as a radiator of signal energy rather than a receptor. This is of no consequence, however, since basically an aerial is the same whether it is transmitting or receiving.

The simplest aerial is the so-called "long wire" type, and this is sometimes looked upon as being of infinite length and connected to a signal source through a coupling transformer with one end of the coupling winding connected to the long wire and the other end to earth, as shown in Fig. 1.

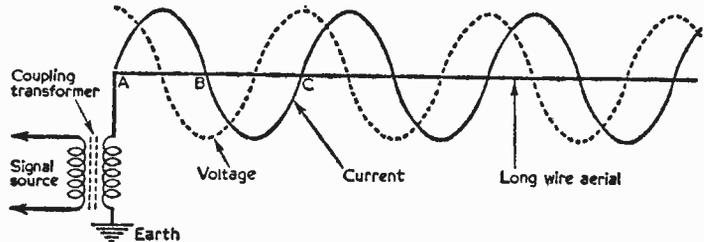


Fig. 1.—The current and voltage distribution in a long-wire aerial.

### Delay

A signal applied at the start of the wire will not simultaneously appear at the end (indeed, it will never reach the end of an infinitely long wire), but will take time and will travel along the wire in the form of a sine wave.

Actually, the signal is composed of two sine waves, a current sine wave and a voltage sine wave the peaks of which occur at the points of the greatest rate of change of the current wave. Conversely, the points of zero voltage occur at the points of zero current change, at the peaks of the current wave. This is made clear in Fig. 1.

It will be seen, therefore, that the voltage is out of phase with the current by  $90^\circ$ . That is to say the current leads the voltage by  $90^\circ$ . This goes on all the way along the wire, relative to earth, and the current waves produce magnetic fields, while the voltage waves produce electrostatic fields.

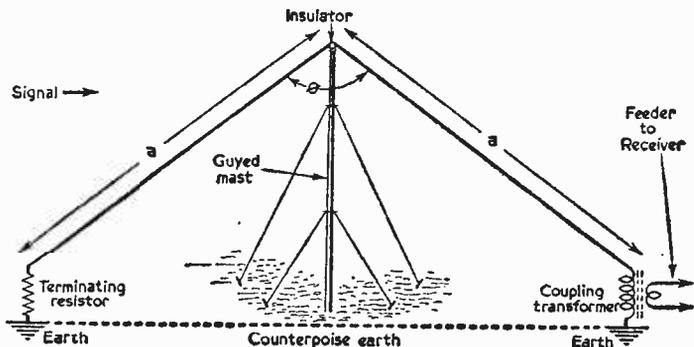


Fig. 2.—A practical vertical half-rhombic aerial for television reception.

### Radiation

These two fields combine to form self-supporting waves of energy which are radiated into space. In the case of a receiving aerial, the waves of energy are picked up by the wire where they produce current and voltage waves, exactly the same as in Fig. 1, and reform as signal across the coupling transformer.

By J. Jenkins

In a practical long wire aerial of finite length, some signal is present at the end of the wire and, unless this is fully absorbed in a suitable terminating resistor, it will start travelling back again along the wire and produce fields in opposition to those required for normal radiation. If the aerial is not properly loaded there will be a reduction in efficiency which will be greater with relatively short aerials than long ones.

### Half-rhombic Aerial

Forms of long wire aerials have been used for television reception, which are sometimes termed "tilted wire", "half-rhombic" etc. The general idea of a vertical half-rhombic aerial is shown in Fig. 2. This requires rather a lot of space to erect, since it does not give a great deal of improvement over a dipole unless the sides 'a' are several wavelengths long.

The terminating resistor should be around 300 $\Omega$  or 400 $\Omega$  and the coupling transformer should be designed to match this value to the type of feeder used, usually 75 $\Omega$  coaxial cable. A coaxial transformer consisting of a quarter-wave matching section of 170 $\Omega$  impedance could be used for coupling to 75 $\Omega$  coaxial, in which case the terminating resistor should be 400 $\Omega$ . A typical arrangement would be sides of 51ft and a mast of 32ft. This would give the aerial a total length along the ground of approximately 80ft.

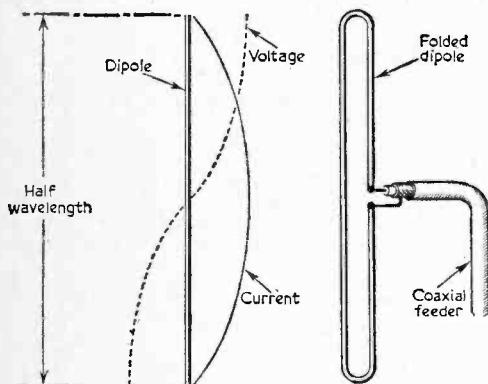


Fig. 3 (left).—The current and voltage distribution in a tuned half-wave aerial.

Fig. 5 (right).—A dipole is folded in the manner shown to bring the centre impedance to a reasonably high value. (When parasitic elements are added to a dipole, the centre impedance is considerably reduced; folding the dipole quadruples this value of impedance and the final value is generally suitable for matching to standard cable.)

### High Gain

The actual characteristics depend essentially on the length of the sides, and on the angle  $\theta$  which, of course, is governed by the height of the mast. A well designed array of this kind is capable of giving a gain approaching 20dB over quite a wide band and with very useful directivity, but, since the other half of the rhombic is provided by the earth, the ground conductivity at the site is of some importance. This can be enhanced at poor sites, how-

ever, by the use of a counterpoise earth consisting of several copper conductors stretched along the whole length of the base of the aerial, as shown in Fig. 2.

### Resonant Aerials

Any aerial will act as a resonant aerial provided that it satisfies two conditions at the working frequency. These are that the length is an exact multiple of quarter wavelengths and that the length is greater than one quarter wavelength. This means, then, that the shortest possible resonant aerial is one half wavelength. The physical length, of course, depends upon the frequency at which it is to operate.

A complete cycle of the current or voltage wave in Fig. 1 (from A to C of the current wave, for example) occupies a distance along the wire approximately equal to one wavelength of the signal frequency. If the wave were propagated in free space instead of along a wire, then the distance would be exactly equal to one wavelength of the signal frequency, and if the frequency were, say, 200Mc/s the distance would be 1.5m, or 59in. The half wavelength in free space would thus be 29.5in. A half-wave dipole tuned to 200Mc/s is slightly shorter than this because the signal does not travel at quite the same speed down a conductor as it does in free space. The length of a half-wave dipole for Channel 11, which is very close to 200Mc/s, is about 27½in.

### Frequency (f) / Wavelength ( $\lambda$ ) Relationship

The product of the frequency and the wavelength is equal to the velocity of propagation of wireless waves in free space (which is the same as the velocity of light). For example ( $\lambda$  in metres)  $\times$  ( $f$  in kc/s) = 300,000. Thus, knowing either the wavelength or the frequency, the unknown can be found from ( $\lambda$  in metres) = 300/( $f$  in Mc/s) or, ( $f$  in Mc/s) = 300/( $\lambda$  in metres).

The retarding effect on the signal owing to the conductor is called the "velocity factor", and this is fairly high in R.F. cables, such as coaxial, and long wire aerials. As an example, the natural wavelength of an aerial is approximately 4.5 times its electrical length, bearing in mind that the aerial resonates at its half wavelength. With coaxial cable with a velocity factor of 0.66, which is a common value, the physical length of a resonant cable is 33% shorter than the electrical wavelength.

Dipole aerials for television are mostly cut to one half wavelength corresponding to the mean of the channel on which it is to operate. Some designers favour cutting more towards the vision carrier frequency while others may, in fact, tune slightly in favour of the sound carrier, and it is for this reason that small discrepancies occur between aerials of different design and manufacture.

### Half-wave Dipole

In Fig. 3 is shown the voltage and current distribution in a tuned half-wave dipole, which is exactly the same as the distribution over the first half wavelength of the long wire aerial. The most important facts about this are that the voltage is at a minimum at the centre and maximum at the ends, and the current is at a maximum at the centre and minimum at the ends. This state of affairs continues as long as the aerial is receiving or radiating signal energy.

The impedance of the dipole is, therefore, at a minimum at the centre and at a maximum at the ends, and intermediate positions down the aerial correspond to intermediate impedances. It is usual to feed the dipole at a low impedance point, and to facilitate this, the dipole is generally cut into two quarter-wave limbs at the centre point. The two points are held about an eighth of an inch apart by an insulator, which also serves to hold the dipole rigid.

When the dipole is cut in this way, the impedance between the two adjacent ends is around  $70\Omega$ , which represents a very close match to  $70\Omega$  coaxial feeder. Indeed, this is one of the reasons why feeders are manufactured with impedances around that value.

### Effects of Mismatch

The impedance of a coaxial cable results from the distributed inductance throughout the length of the conductors and the distributed capacitance between them. These combine to give a specific impedance value, usually called the "characteristic impedance". Maximum transfer of energy will take place only when the two ends of the coaxial cable are loaded to impedances which equal the characteristic impedance. If, for example,  $70\Omega$  feeder were connected to a point on the aerial where the impedance were, say,  $200\Omega$ , some of the signal in the aerial would make its way down the cable, but a proportion of it would be reflected back into the aerial. Similarly, if there is a mismatch at the set end, all the signal in the cable will not be absorbed by the set, but some of it will be reflected back up the cable and will be lost. It may undergo a second reflection at the aerial connection, in which case a reflected signal will be received by the set a little later than the direct signal, and if the feeder is long this could result in a ghost image or impair the picture definition.

Mismatching of this nature produces "standing waves" on the cable the amplitude of which is proportional to the degree of mismatch. Standing waves represent a total loss of energy and should not be confused with the useful signal which travels along the feeder. Mismatching also makes the cable itself susceptible to signal pick-up and radiation. From a receiving point of view, this means that excessive interference from cars may be caused by pick-up on the downlead which is closer to the source than the aerial itself.

### The Addition of a Reflector

An ordinary vertical dipole has what is called an omnidirectional polar diagram, and gives all-round reception and transmission, as shown in Fig. 4(a). This pattern is highly desirable for mobile radio services where the aim is to cover the widest possible area, but for point-to-point television reception a directional arrangement is favoured, since then there is less possibility of interference from signals arriving from different directions.

Moreover, the gain or pick-up sensitivity of a directional aerial is automatically increased over a dipole in the forward direction. Single dipoles are employed mainly in areas of very high signal strength, where the strength of the wanted signal far outweighs that of unwanted signals.

An aerial is made directive by adding a reflector. This simply consists of a single conductor about 5% longer than the dipole and spaced from the dipole by a quarter wave-length. Since it is

inductively coupled to the dipole it has induced into it a signal from the dipole, and thus itself radiates. However, there is a phase alteration of  $90^\circ$  due to

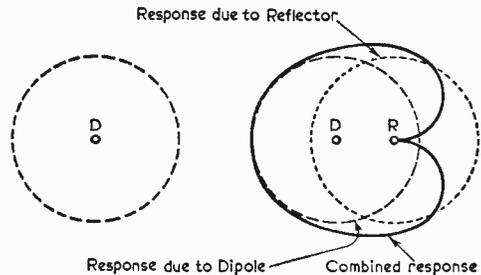


Fig. 4(a).—The polar response of a simple dipole, and (b), the directional response produced by adding a reflector. Further directivity and gain is produced by adding directors.

the coupling, and there is a further alteration of  $90^\circ$  due to the signal passing back again from the reflector to the dipole. This means that the dipole now receives two signals, the direct signal and that reflected back at anti-phase from the reflector. The reflected signal tends to cancel the response pattern at the rear and enhance it at the front, and the combined effect is the production of a polar diagram as shown in Fig. 4(b).

### The Addition of Directors

Even greater directivity is secured by mounting parasitic elements in front of the dipole. These are called directors and are cut slightly shorter than the dipole so that they resonant at a slightly higher frequency. They have the effect of reinforcing the signal in the forward direction by several artifices closely related to phase and spacing.

Up to a limit, as more directors are added so the polar response is continually narrowed, but there comes a point, after about seven or eight directors, where there is hardly any improvement in gain or directivity. As a general guide, directors diminish progressively in length in relation to the dipole at a rate of approximately 5% per director and eighth-wave spacing is often used, though these factors depend to a large degree on the exact design of the array.

### Folded Dipole

Although a reflector does not have a large effect on the centre impedance of a dipole, there is a marked reduction in impedance when directors are added. This makes it almost impossible to match direct to  $70\Omega$  coaxial cable. There are various ways of correcting this, and the most popular is to "fold" the dipole (Fig. 5 page 71). The signal pick-up of a folded dipole is approximately equal to that of a simple dipole, but owing to the effect of the signal current being divided between the two sections, the impedance is increased by a factor equal to the square of the impedance of a simple dipole.

Thus, if the centre impedance of a simple dipole falls, say, to  $8\Omega$  due to the addition of a reflector and a number of directors, and this is a common value, the impedance is raised to about  $64\Omega$  by folding the dipole, and it then represents a reasonable match to  $70\Omega$  coaxial cable.

# Practical Television MULTIMETER

(Continued from page 51 of the October issue)

**T**HERE is no absolute necessity for the reader to follow the details of the cabinet illustrated in Figs. 2 and 3, but this design is simple, and therefore suitable for those who are not skilled carpenters. It is made from inexpensive materials, but is nevertheless attractive in appearance.

Soft wood constitutes the largest part of the materials needed. A few shillings will procure all the timber necessary; about two and a half feet of  $\frac{3}{4}$  in. wood of the nearest stock size to  $4\frac{1}{2}$  in. wide will be required, or some off-cuts from the local wood shop merchant will prove even cheaper.

## Sides

The first pieces to be sawn to size are the two side pieces. It would perhaps be best to make a cardboard template for these parts, taking the measurements given in Figs. 2 and 3; i.e.,  $9\frac{1}{2}$  in. long at the base and slightly less than  $4\frac{1}{2}$  in. wide at one end and slightly more than  $1\frac{3}{4}$  in. wide at the other (this takes into account the fact that the two Perspex panels slope from one end to the other, thus giving rise to slight differences from the measurements given for the extreme ends (see Fig. 3).


The back of the cabinet is a piece of soft wood  $6\frac{7}{8}$  in. x  $4\frac{1}{2}$  in., the top edge of which must be planed or otherwise shaped to conform to the slope of the meter panel. The front portion of the cabinet is a piece  $6\frac{7}{8}$  in. x  $1\frac{3}{4}$  in. similarly planed to suit. There is one other piece to be cut, and that is the centre panel (see Fig. 3), which is  $6\frac{7}{8}$  in. x  $1\frac{1}{2}$  in. This last piece has to be planed along both edges to meet the meter and control panels.

The base of the cabinet is simply a piece of  $\frac{1}{8}$  in. hardboard, which may easily be obtained from a wood merchant already sawn to the correct size;  $10\frac{1}{4}$  in. x  $6\frac{7}{8}$  in.

The two black Perspex panels, one supporting the meter and one the controls



Fig. 2 (below).—Side view of the case of the complete multimeter.

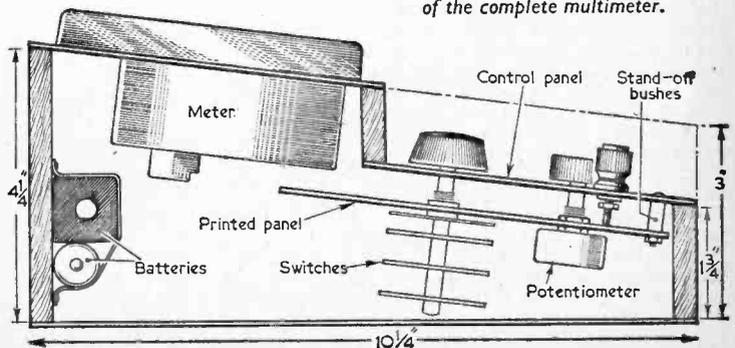

and printed circuit board, can best be obtained new, or as off-cuts, from a "do-it-yourself" shop. They are both  $\frac{1}{8}$  in. thick and  $6\frac{7}{8}$  in. wide, but the control panel is  $5\frac{1}{4}$  in. in length and the meter panel  $5\frac{1}{2}$  in. in length.

Perspex is almost as easy to handle and tool as wood, and with care will not crack, break or splinter. All the edges should be lightly filed to give a better finish than the raw saw cut, and the holes which are drilled should also be finished with a half round file. All the holes in the control panel are drilled to the measurements given in Fig. 3.

### Meter Mounting

The hole for the meter can be cut with a fret saw starting from a small hole drilled somewhere towards the centre of the final circle. The three slots placed at  $120^\circ$  intervals round


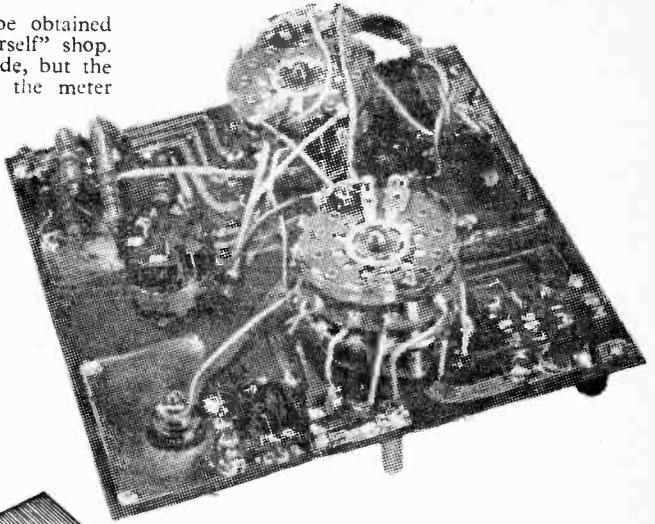


Fig. 3 (below).—The dimensions of the case for the multimeter.

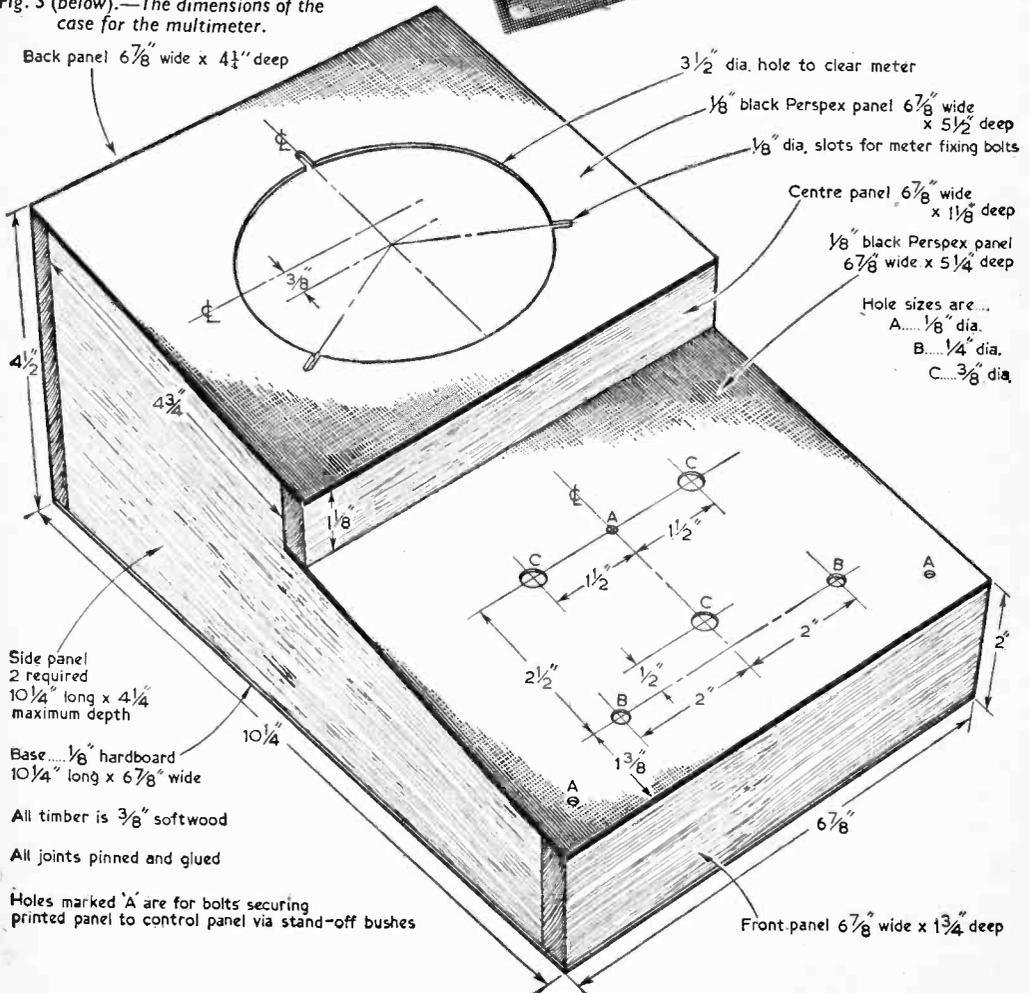

circumference of the circle are best made from a saw-cut, widened with a small file.

The printed circuit board is fixed to the Perspex panel by three bolts through the holes marked "A" in Fig. 3. The two situated at the corners of the cabinet are drilled to correspond to those shown on the printed circuit on the Blueprint. The third hole is positioned as shown in the diagram and to receive the bolt a corresponding hole must be drilled in the printed circuit board, and it will be found that this will conveniently be on a piece of the board free from copper; on no account must this fixing bolt come into contact with the copper on the printed circuit board.

Stand-off bushes are used on all three fixing bolts to keep the board at a suitable distance from the Perspex panel. The shanks of the two switches and the potentiometer must be sawn off to the correct length and knobs fitted on them. The two terminals are mounted on the front panel and *not* on the printed board, so that the shanks pass through the two holes left for them on the board. The sides, back and front of the cabinet should now be placed together to ensure that all the sides

connected to R18 and the 1.5V cell (positive end) is connected to tag 10 on S2C.

The base may now be screwed into position—and lettering can be put round the switches, terminals and potentiometer, either by hand-painting or by the use of transfers, to correspond to the ranges given.

#### Calibration

The procedure necessary for the calibration of the meter was given in detail last month and it should be found relatively easy to achieve the required degree of accuracy. The main difficulty will consist of transferring the results of the various calibration exercises to the meter so that direct readings are possible. If desired, the calibration could be carried out in the form of various graphs, one for each scale or set of scales, but this method, while accurate, makes the taking of readings tedious and unnecessarily complicated. What is needed is the ability to take readings directly on all ranges. In order to help the constructor, a sample set of scales is printed in Fig. 4 below and shows the type of professional layout which it is possible to achieve. The amateur could well draw out similar scales

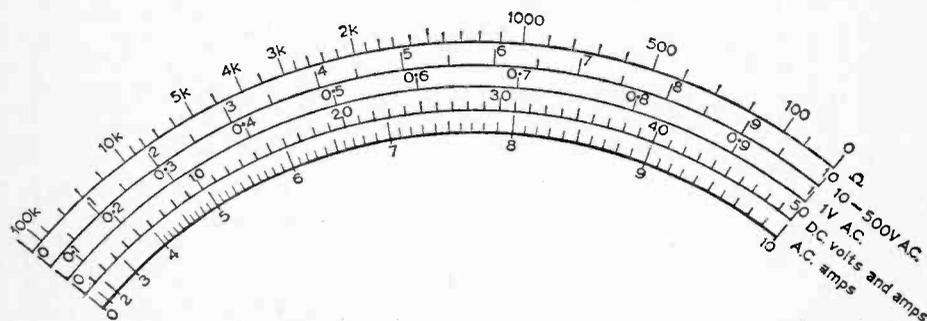


Fig. 4.—An example of the type of scale produced in calibrating the multimeter—in fact, this scale may be used on the completed instrument.

line up and then, by using one of the modern contact adhesives and panel-pins, the four pieces may be permanently joined. The meter and control panels may now be placed in position and glued with a suitable adhesive.


#### Switch Wiring

At this point in the construction, the two terminals, the shanks of which pass through the printed circuit board as explained earlier, are connected with 16s.w.g. tinned copper wire to the two switches. Refer to the blueprint—Terminal Y is connected to tag Y on S2A. Terminal Z is connected to tag Z on S1A. The meter movement may now be connected as shown on the Blueprint.

The 9V battery and 1.5V cell are now strapped to the back of the cabinet as shown in Fig. 2. Strips of plastic or leather held by drawing pins are all that is needed. The two batteries are, in effect, wired in series, the junction of the two forming the "0V" connection (the positive tag of the 9V battery is connected to the negative tag of the 1.5V cell). The 9V battery (negative end) is con-

when calibrating his meter and, if the scales are drawn on thick card, then the card can finally be cut to fit above the glass of the meter so that readings can be taken easily. Of course, although this method avoids the necessity of tampering with the meter and attempting to mount the scale on top of the existing scale, great care must be taken to avoid parallax error—the eye must be kept directly above the meter needle or the reading taken will be too high or too low. The scales shown above are suitable for direct use on the home constructed meter and can be mounted on card and used as described above; the accuracy obtained should be at least 5% on A.C. ranges, provided full scale reading is adjusted to be correct. Voltage readings, using the proper value of series multiplier, will be equally accurate without such adjustment. With current ranges, however, accuracy depends only on the resistance of switch contacts so that for the higher current ranges (50mA and over) this needs to be taken into account. Consequently, for the higher current ranges (on both A.C. and D.C.) scales are only correct if the full-scale reading is adjusted to be correct. ■

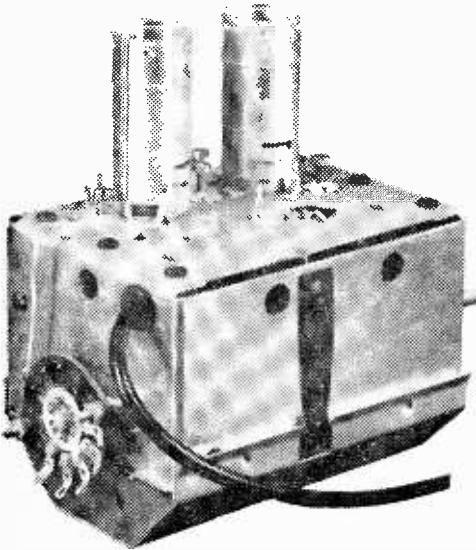*I*t is the purpose of this series of articles to describe in a practical manner the function of each particular component making up a television receiver. Details will also be given where appropriate of the likely effect on receiver performance should the component under discussion be in any particular way defective.



# HOW TV SETS

## WORK - 1: The tuner

By K. James

To start the series, a typical turret tuner will be considered, the circuit of which is shown in Fig. 1. Although tuner circuits differ slightly between models, the basic make-up is fairly standard, even with switch tuners and modern turrets. There are usually two valves, a double-triode (V1) arranged in a cascode R.F. amplifier circuit and a triode-pentode arranged in a frequency changer circuit (V2), with the triode acting as local oscillator and the pentode as mixer.

### Aerial Isolation

The aerial downlead is connected to a coaxial input socket and fed to the aerial coupling transformer L1/L2 through capacitors C1 and C2. These isolate the mains-connected chassis of the receiver from the aerial, and may have a value between 470pF and 1,000pF. It is unwise to replace these with components of greater value, as then the capacitive reactance at 50c/s may be increased sufficiently to cause a person touching the aerial system to suffer serious electric shock if the chassis of the set happens to be connected to the "live" side of the mains supply. Replacement components should also have a rating around 1,750V (1.75kV).

Resistors R1 and R2 connected in parallel with the isolating capacitors provide a discharge path between the aerial system and receiver chassis, and thus avoid the build up of a large static potential which would cause interference to the reception and, under certain conditions, also cause the aerial to charge up to a dangerous voltage.

Section A of the double-triode V1 is connected as a neutralised triode, the signal from the coupling transformer being applied to the grid. The pre-set capacitor C3 and the capacitor C4 are the neutralising elements which cancel out the effects of the anode-to-grid capacitances of V1A. In conjunction with the valve capacitances, C3 and C4 form a bridge circuit, and, by careful adjustment to C3, the stage is effectively neutralised.

### Critical Adjustment

Neutralisation is necessary to prevent the triode from oscillating and to maintain the lowest possible noise factor for the first stage. C3 is adjusted at the factory, and, as very small values of capacitance are involved, the adjustment is critical.

The cathode resistor R4 provides a part of the grid bias for V1A, depending on the setting of the gain control R103. When R103 is at maximum gain, the voltage drop across R4 gives all the fixed bias, but, when R103 is turned towards minimum gain, V1A receives an increased bias which effectively decreases the mutual conductance of the valve and hence the gain of the stage.

Resistor R4 is decoupled by C7 to prevent negative feedback from unnecessarily reducing the gain. Similar decoupling is provided by C6 in relation to the gain control circuit. R103 is connected between chassis and H.T. positive in a potential divider arrangement. Thus, as the gain

control is turned down, so the cathode of V1A becomes progressively more positive with respect to the grid. As this is the same as the grid becoming progressively more negative with respect to cathode, a wide control of stage gain is provided.

### Automatic Gain Control

In addition to the fixed bias and that provided by the gain control, bias is also applied to V1A from the AGC line, via R3. This negative bias increases with increase in signal strength and thereby automatically adjusts the gain of the stage to accommodate a range of input signals.

In poor signal areas, the gain control should always be set at maximum, and the general gain of the receiver adjusted by the contrast control. This ensures that the first stage is providing the best noise performance. This can be demonstrated by

in very strong signal areas, where sound-on-vision and vision-on-sound might occur. Open-circuit of R3 would result in modulated hum bars on the picture and hum on sound.

### The Other Half of the R.F. Stage

Section B of V1 is an earthed-grid R.F. stage which receives the amplified signals at V1A anode in its cathode circuit. These signals are applied through inductor L3, which is sometimes called a coupling or peaking coil. This coil is made to resonate just below Channel 13 and, since the Q is low owing to the input impedance of V1B, it preserves the stage gain at high frequencies in a similar manner as the "peaking coil" in video amplifier stages.

The grid of V1B is maintained at chassis potential (so far as the signals are concerned) by C8. Bias

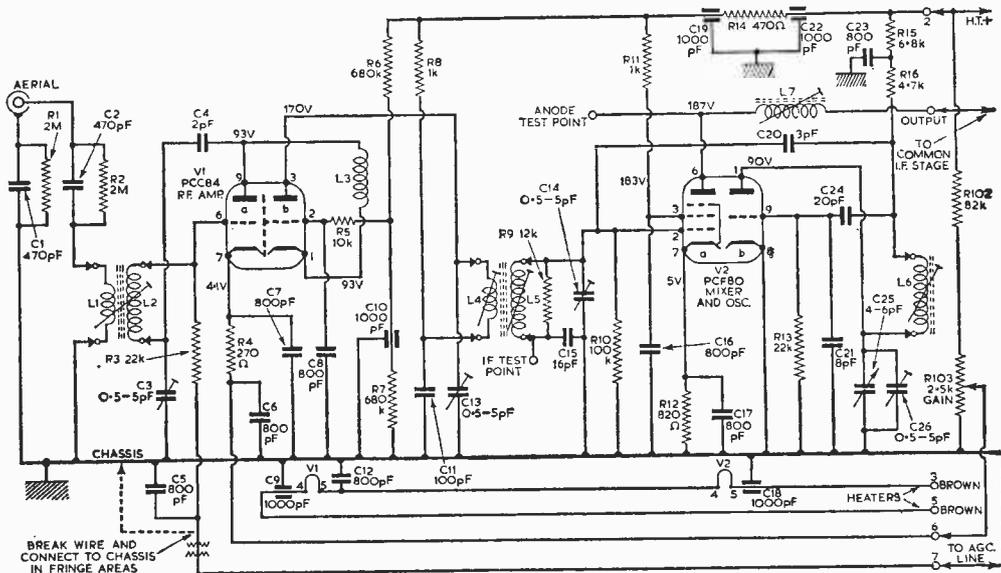


Fig. 1.—The circuit diagram of a typical turret tuner. The components making up this tuner are described in detail in the text.

turning down the gain control and turning up the contrast control to compensate. In areas where the signal is not too strong, this practice will result in a picture which is very noisy (i.e. covered with grain). The reason for this is that the noise from the R.F. stage increases as its gain is decreased.

For optimum results in fringe areas it sometimes pays to disconnect the AGC to the tuner, by breaking the AGC wire (the C5 end) and connect it direct to chassis, as shown in Fig. 1. This ensures that the stage performance is not impaired by unnecessary bias when the aerial signal is very weak.

### Biasing Faults

Open-circuiting of R4 would cause complete failure of V1A and lack of sound and vision signals. A short in C6 or C7 would be revealed by R103 not operating. Open-circuiting of R102 would seriously limit the range of gain control, while a short across C5 would hardly be noticed other than

for V1B is fixed by means of the potential divider, R6 and R7, and from the D.C. point of view, V1B appears as a cathode-follower. Further decoupling of the grid circuit is provided by R5 and C10.

It sometimes happens that the "lead-through" condenser C10 develops a short-circuit. This destroys the bias of V1B and, in certain tuners, causes R6 to overheat and burn out. In some cases, the tuner may continue working with very low efficiency.

The two sections, V1A and V1B, form the well-known cascode circuit, in which the amplified signals are developed across the anode coil L4 and the coupled coil L5, which together form a band-pass coupling to the mixer. The anode circuit is decoupled by R8 and C11 and the anode coil is tuned by its slug and the trimmer C13. C13 is adjusted at the factory to provide the best compromise over all the channels, and improvement can never be obtained by altering this setting.

### Mixer Section

The pentode section of V2, V2A, receives at its control grid the amplified R.F. signals across L5. This inductor is tuned by the slug in its former and by the pre-set C14, which should not normally be adjusted. Resistor R9 is included to set the Q of L5 for the required passband characteristics, while C15 gives a coupling for the "I.F. test point". Such a test point is made available on most tuners to allow easy connection of an I.F. signal for alignment purposes.

A grid return for the pentode is provided by R10, and the stage is biased by the cathode resistor R12 and grid current in R10 as the result of the applied heterodyne signal from the local oscillator. R11 is the screen feed resistor and C16 and C17 are decoupling capacitors.

### Local Oscillator

The triode V2B is arranged in a simple oscillator circuit of modified Colpitts form. The H.T. feed to the anode is via R16, and the oscillator coil is L6. The oscillator is tuned by the slug in the coil, by the fixed capacitor C21, by the fine tuner C25 and by the trimmer C26. The latter, again, is a pre-set which is adjusted for optimum results on all channels at the factory. As these components are chosen in terms of temperature co-efficient to compensate for capacitance changes with temperature, it is essential, if oscillator drift is to be avoided, to make any necessary replacements with components of the original characteristics. This also applies to the oscillator coupling capacitor C24 and the heterodyne feed capacitor C20.

As a fairly high R.F. voltage exists across the oscillator feed resistor R16, this is returned not direct to H.T. line, but to an H.T. decoupling network comprising R15 and C23. Further decoupling for the remainder of the tuner is provided by R14 and C19.

Excessive frequency drift should lead to a check of the fine tuner and associated capacitors, after first proving that the frequency changer valve is not responsible, preferably by substitution.

Excessive oscillator radiation, as may be picked up on a nearby set as pattern interference, could be caused by a fault in R15 or C23.

### WIRED TV SYSTEM

A CONTRACT has been placed by the Independent Television Authority with EMI Electronics Ltd. for the installation of a wired TV and sound system at their new headquarters in Brompton Road, London.

Work is already being carried out on this installation which, when complete, will provide ITV Channel 9 and BBC Channel 1 television programmes and BBC VHF sound programmes in most of the offices in the new headquarters.

A modulator will permit pictures from other TV programmes—supplied by cable from the Museum telephone exchange—to be displayed.

Aerials will be fitted to a 30ft tower on the roof.

### COLOUR TV FOR SOUTH AFRICA

A LARGE screen colour television projector developed by Marconi's was recently demonstrated in South Africa, when the Smith Kline and French medical colour TV unit visited hospitals and medical centres in the Republic.

The mobile unit, manned by Marconi engineers,

### Intermediate Frequency

Grid bias for V2B is provided by the grid current in R13 which is produced by the oscillatory condition of the valve. The oscillator voltage is fed to the control grid of the mixer section through C20. In most tuners, the oscillator frequency is the signal-frequency plus the intermediate-frequency, which gives sound and vision I.F.'s in the I.F. coil L7 such that the sound I.F. is *above* the vision I.F. in frequency. In tuners with the oscillator at the I.F. below the signal-frequency, the sound I.F. falls *below* the vision I.F.—a point worth remembering.

The "lead-through" capacitors in tuners appear vulnerable to short-circuiting or intermittent breakdown—these are indicated on the circuit by two lines, one either side of the circuit wire, such as C19, C22, C10, etc. Should the faulty capacitor happen to be decoupling an H.T. circuit, then the associated resistor will nearly always burn out, but the capacitor, when later checked with an ohmmeter, may not show a short. To be on the safe side it pays to replace the capacitor if there is any doubt at all. For example, should C19 short, a very high H.T. line current will flow in R14 and cause it to burn out.

The I.F. coil L7, should be adjusted for the best overall response of both sound and vision. In the event of instruments not being available, the coil slug should be adjusted to give the best reproduction of Test Card C, consistent with good sound.

### Heater Circuit

Most modern tuners feature a series-connected heater chain, as shown in Fig. 1. The heater line is decoupled to R.F. by C9, C12 and C18. It is rare for these capacitors to fail, but if they do, pattern interference effects may be present on the picture at certain critical points of the fine tuning control owing to the injection of spurious R.F. and oscillator signals into the heater circuits of other valves in the set. The tuner heater chain is usually introduced into the main heater chain between the picture tube heater and the other valves, the other side of the picture tube heater, of course, being connected to chassis.

(To be continued)

gave demonstrations at the 43rd South African Medical Congress in Cape Town in September. Also in use was a new colour television projector.

The Smith Kline and French medical colour TV unit has given demonstrations to doctors, hospital staff and medical students all over the world and last year carried out a successful tour of Australia.


In South Africa, after leaving Cape Town, it will give demonstrations in Johannesburg and Durban before returning to England late in October.

### TV CONFERENCE IN BUDAPEST

MORE than 100 foreign guests besides official delegates are expected in Budapest next summer for the conference of the International Radio and Television Organisation.

Observers will be attending from Iraq, the United Arab Republic and a number of Asian and African countries.

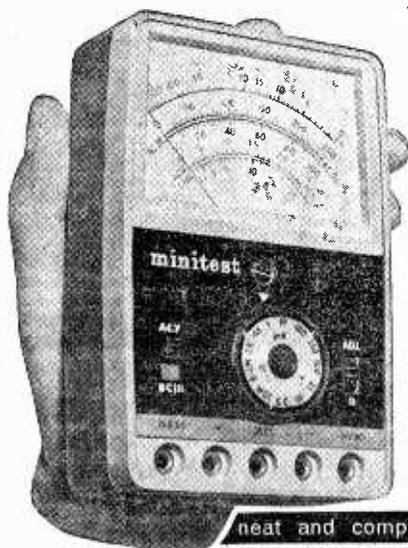The meeting will discuss, among other things, exchanges of documentary and feature films for television, and exchange of radio programmes.



another NEW instrument  
from Salford, the  
**minitest**  
POCKET-SIZED MULTIRANGE TEST SET

A new compact instrument suitable for the measurement of D.C. voltages and currents, A.C. voltages and ohms. Its high sensitivity renders it suitable for testing and fault location in all types of electrical and electronic circuits. It is well built to ensure long and satisfactory service. The instrument is economically priced and supplied with test leads with plug connections at one end. (Leather carrying case available as an extra).

**RANGES:** A.C. Volts. 2.5, 10, 25, 100, 250, 1000.  
D.C. Volts. 2.5, 10, 25, 100, 250, 1000.  
D.C. Amps. 50  $\mu$ A, 1mA, 10mA, 100mA, 1A.  
Ohms. 2000 200,000 20 M $\Omega$

**ACCURACY:** D.C. Volts & Amps.  $\pm 2\%$  of full scale deflection  
A.C. Volts  $\pm 3\%$  of full scale deflection  
 $\pm 5\%$  at centre scale.

Send for leaflet MIN/6009/PT

neat and compact... with large instrument performance

**SALFORD ELECTRICAL INSTRUMENTS LIMITED**  
Peel Works · Silk Street · Salford 3 · Lancs · Tel: Blackfriars 6688  
London Sales Office: Magnet House, Kingsway, W.C.2. Tel: Temple Bar 4668  
A Subsidiary of THE GENERAL ELECTRIC CO. LTD. OF ENGLAND



**"SABRINA"**  
STILL WELL IN  
FRONT

Make your TV set 100% again before Prices rise. (You have been warned!)

**COMPLETELY REBUILT C.R. TUBES  
ALL TYPES (including electrostatics)**

12" now	...	...	...	...	£5. 0.0
14" to 17" now	...	...	...	...	£5.10.0
21" now	...	...	...	...	£8. 0.0

ALL C.W.O.

**Special Bonus Scheme for Service Engineers**

**FREE** Pass. transit & Ins. anywhere in British Isles or N. Ireland (12 months guarantee).

**SABRINA C.R. TUBE CO.**

Electron Works, North Bar  
**BANBURY, OXON**  
Telephone 2390

**HARVERSON SURPLUS CO. LTD.**

83 HIGH ST., MERTON, S.W.19. Cherrywood 3985/6/7

**SUPER  
STEREO KIT  
MK. II**

A kit of ready-built units only requiring interconnection. Comprising two midget 3W amplifiers, push button switch, transformer, control unit (bass, treble and vol.), power pack, two speakers, indicator light, valves (ECL 82, EZ80 range), and comprehensive instructions.

**£3.19.6**

Plus 6/6 P. & P.

**HARVERSON'S  
6 TRANSISTOR  
& DIODE  
SUPERHET KIT**

A first class 2 wave band transistor superhet in kit form.  
★ Printed circuit panel (size 8 $\frac{1}{2}$  x 2 $\frac{1}{2}$  ins.)  
★ 3 Pre-aligned I.F. Transformers.  
★ Output Transformer.  
★ 5 inch 5 $\Omega$  Speaker.  
★ High gain Ferrite rod aerial.  
★ First grade G.E.C. transistors.  
★ Push/Pull output.

All parts down to the minutest item with instructions. ONLY  
**£6.19.6** Plus 2/6 P. & P.  
Cabinet if available 15/- extra.



**TELEVISION TUBE BARGAINS**

**COSSOR** 108K 10-in. New & boxed, 15/-, plus 6/- P. & P.  
75K 10-in. New & boxed, 15/-, plus 6/- P. & P.  
Ion trap magnets to suit the above, 2/9, 3d. P. & P.

**REBUILT TV TUBES.** We can supply all types and all sizes of quality rebuilt tubes at very competitive prices. Write, call or phone for your requirements.

## "6 plus 1" TRANSISTOR RADIO KIT — BEST EVER VALUE —

Mrs. Surplus Bargain Offer—Further kit supplies now available. Original purchases of this popular kit were rapidly sold out. This kit is a modern, sensitive quality circuit Receiver Unit with all the latest features. Six B.V.A. Transistors and 1 Diode, Printed Circuit, Med. and Long Waves, Ferrite Aerial, Car Radio Coupling Coil, 1w Push-Pull output into 3 ohm Speaker, attractive Gilt Dial and Slow Motion Tuning, etc. Size: approx. 8 1/2 x 3 1/2 in. Cabt. size 9 x 5 1/2 x 3 1/2 in.



**COMPONENT KIT 5 Gns. SET OF 6 TRANSISTORS and 1 DIODE 45/-**

7 x 3 1/2 in. speaker 15/6 carr. 1/6. Complete Kit (less speaker) Bargain Price **£6.19.6** carr. 2/6. 3d. stamp, full details. Circuit and Instrat. **1/6**

NEW VALVES		ALL GUARANTEED	TRANSISTOR BARGAINS!	
1T4	6/-	EF86	12/6	BRAND NEW—BVA 1st Grade
1R5, 1R5	7/6	EL84	8/6	OC44
3R4, 3V4	7/6	EV41	9/6	10/8 874
DAF96	9/-	EY86	10/-	OC45
DF96	9/-	EZ80/81	7/6	12/8 873
DK96	9/-	PCC84	9/6	OC81D
DL96	9/-	PCF80	9/6	7/6 GET114
ECL80	10/8	PCL83	12/6	2/OC81
ECL82	10/8	PL81	12/6	15/6 OC72
EF80	8/-	U25	12/6	X A102
				10/- OC70
				X A101
				9/6 OC71
				X B103
				7/6 OEX34
				8/6 OA70
				8/6 OA81
				2/8

**SPEAKER FRET.** Expanded Bronze anodised metal 3 x 8 in., 2/3; 12 x 8 in., 3/-; 12x12 in., 4/6; 12x16 in., 6/-, etc

**TYCAN FRET** (Contemp. pattern) 12 x 12 in., 2/-; 12 x 18 in., 3/-, etc.

**SPEAKERS P.M.** 3 ohms 2 1/2 in. Elasc., 17/8. 3 1/2 in. Goodmans, 18/6. 5 in. Rola, 17/8. 6 in. Elasc., 18/6. 7 x 4 in. Goodmans, 18/8. 8 in. Rola, 20/-.

**CONDENSERS—Silver Mica.** All values, 2 pF to 1,000 pF., 6d. each. Ditto, ceramics. 9d. Tub. 450 v. T.O.C., etc., .001 mfd., .01 and 1/350 v., 9d.; .02-1/500 v., 1/-; 25 Hunte 1/8; 3 T.O.C. 1/8, etc., etc.

**RESISTORS—FULL RANGE** 10 ohms—10 megohms 30% 1/2 w. and 3/4 w., 3d.; 1/2 w., 5d.; (Midget type modern rating), 1 w., 6d.; 3 w., 9d.; 10% Hi-Stab. 1 w., 5d.; 1/2 w., 7d.; 5% 3/4 w., 9d.; 1% Hi-Stab. w., 1/6.

**W/W RESISTORS.** 25 ohms to 10K, 5 w., 1/3; 10 w., 1/8; 15 w., 2/-.

**PRE-SET T/V POTS.** Full range 25 ohms—2 meg., 3/-.

**VOLUME CONTROLS—5K—2 Meg.** ohms, 3in. SPINDLES MORGANITE MIDGET TYPE, 1 1/2 in. diam. Guar. 1 year. LOG or LIN ratios less Sw., 3/-; D.P. Sw., 4/6. Twin Stereo less Sw., 6/8. D.P. Sw., 8/-.

**TURRET TUNER — BAND 1/BAND 3.** Ex. mfrs. current production offer—std. type 13-channel unit, 35-38 Mc/s I.F. Complete with PCC84 and PCF80 Valves and coils for channels 1-3-9. No knobs or circuit diagram, but connection data supplied. Clearance Bargain Only 32/6. Carr. 2/6. Worth 5 gns.

Transistor Midget Electrolytics—all values 1 mfd. to 100 mfd., 1/9 ea. Transistor Condensers—.01 mfd., .03 mfd., 9d.; .05 mfd., 1 mfd., 1/-; .25 mfd., 1/8; .5 mfd., 1/8.

## RECORDING TAPE—Special Offer

American COLUMBIA (C.B.S.) 1st Grade P.V.C. TAPE. Fitted leader and auto stop foils. Brand New, Boxed, and fully guaranteed.

Standard	Long Play
5in., 600ft. ... .. 15/-	900ft. ... .. 19/6
5 1/2 in., 900ft. ... .. 18/6	1,200ft. ... .. 22/6
7 in., 1,200ft. ... .. 21/-	1,800ft. ... .. 32/-

**SPECIAL BARGAIN** 3in. mfrs. tape on ea. additional reel. P. & P. per reel 1 1/2. 6d. on ea. additional reel. Plastic Tape Reels ... 3in. 2/6, 5in. 3/-, 5 1/2 in. 3/8, 7in. 3/8.

## TAPE RECORDER KIT ONLY £16 10s.

Latest 5-valve circuit based on Mullard's design. Magic eye and tone controls. Printed circuit already wired. A sensitive quality recorder. B.S.R. Amp Kit 95/-. B.S.R. Tape Deck £8.10.0. Collaro Amp Kit £8.5.0. Collaro Tape Deck £12.10.0. Set of 5 valves 45/-. Special Unit Kit Prices—Send stamp for detailed list. Handbook (full details) 2/6.



Jason Tuners—Approved Kits—comprehensive range in stock. Model FMT1 5 gns. etc., 48-hour Alignment Service. Send for complete bargain list.

## TRS RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY EN11 1AB.  
Telephone THO 2188  
Terms C.W.O. or G.O.D. Post and Packing up to 1 lb., 7d., 1 lb. 1 1/4, 3 lb., 1/6, 5 lb., 2/-, 10 lb., 2/6. Hours: 9 a.m.—6 p.m.; 1 p.m. Weds.

## AERIALS

BAND I BAND II BAND III

**Combined Arrays I and III**  
1+3 Element Loft Mounting .. 38/3  
1+5 Element Loft Mounting .. 46/9  
1+3 Element Wall Mounting .. 45/3  
1+3 Element Wall Mounting .. 57/1-  
1+3 Element Chimney M'ting. .. 57/10  
1+5 Element Chimney M'ting. .. 66/9

**Band I**  
Single Dipole Wall Mounting .. 24/7  
Single Dipole Chimney M'ting. .. 40/2  
X Aerial Chimney Mounting .. 82/3  
H Aerial Chimney Mounting .. 67/7

**Band III**  
3 Element Yagi Wall Mounting 33/-  
6 Element Yagi Wall Mounting 43/-  
9 Element Yagi Wall Mounting 56/-  
Chimney Lashing Mounting add 10/-  
Double 6 Array, only with clamp 83/-

**Band II**  
Single Dipole Wall Mounting .. 20/5  
Single Dipole Chimney M'ting. .. 29/9  
H Array Chimney Mounting .. 52/4



## REPAIR KITS

Band III Folded Dipole With Insulator. Complete ... 9/3  
Band I Insulator With Two 1/2 inch Dipoles For 1 or 1/2 inch Booms. Complete ... .. 19/5  
6 inch Lashing Kit, 12/11. 7 1/2 inch Lashing Kit. ... 14/8  
6 inch Wall Bracket With U Bolts ... .. 7/10  
1 1/2, 1-1/2 inch Clamps, 3/10. 1-2 inch Clamps Universal. 5/4  
Bracket Repair Kit, J Bolts; U Bolts; 20ft Lashing Wire; Thimbles; Corner Plates ... .. 6/-  
Insulators, All Types ... .. (Enquire)  
Co-Ax. Semi Air Spaced, 7d. yd. ... .. Plus 1/2  
Send 6d. for Lists. Please state Channel when ordering.  
Cash with Order. Post and Packing 3/- extra.

**SATISFACTION OR MONEY BACK GUARANTEE**

## WALKER & SQUIRES

PINXON STREET, TUNSTALL, STOKE-ON-TRENT

Phone: Stoke-on-Trent 88767

## Better, Brighter Picture Tubes

**BRAND NEW THROUGHOUT** excepting glass.

12in. ...	£4.10.0	14in. ...	£5. 5.0
15-17in. ...	£5.15.0	21in. ...	£7.15.0

New Silver Screen and Aluminising. All makes Mullard, Mazda, Emiscope, Cossor, Brimar, Emitron Etc.

## REBUILT MULLARD AND MAZDA TUBES

12in. ...	£3. 0.0	14in. ...	£4. 0.0
15-17in. ...	£4.10.0	21in. ...	£6.10.0

All Tubes Fully GUARANTEED 12 MONTHS. Dispatch same day. C.W.O. or C.O.D. Carriage and Insurance 10/-.

## S.T.S. Ltd.

35 POUND STREET, CARSHALTON, SURREY.

Telephone: WALLINGTON 9665


# A Precision Wobbulator

By N. Mears

(Continued from page 27 of the October issue)

THIS VERSATILE  
WIDE RANGE  
INSTRUMENT  
WAS DEVELOPED  
AROUND  
A MODERN  
SEMICONDUCTOR  
JUNCTION DIODE

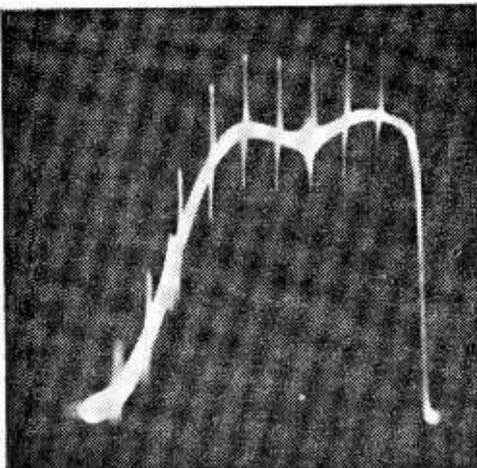**S**CREENING for the wobbulator was described in last month's issue, and a means of decoupling the mains leads was also explained. Thus the only leakage of R.F. field is from the centre spigot of the coaxial connector and the  $\frac{1}{4}$  in. holes in the front panel.



TV receiver response: note the marker pip.

The former is by far the larger leakage except when a metal screwdriver is used to trim the coil cores—the use of an insulated tool is therefore recommended. The 465kc/s coil is aligned before the can is screwed over the oscillator assembly, and no external trimming hole is needed.

## Control of Output

It is important for the R.F. output control—or 1000 $\Omega$  variable resistor—to have zero resistance at its minimum. If it does not, R.F. output will not

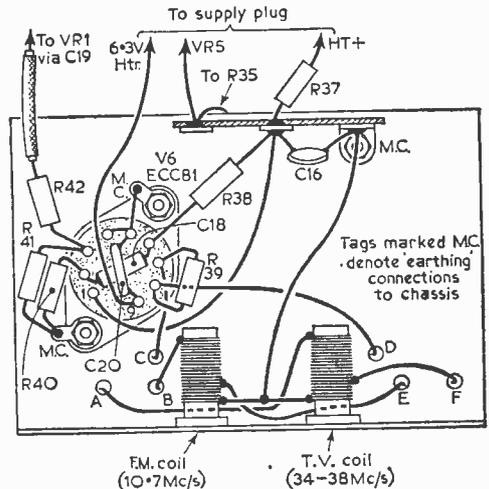


Fig. 10.—The wiring details of the oscillator circuit.

reduce to a sufficiently low value at the minimum setting of the control. The earth connection must also be of very low impedance. Several wires in parallel, or thick copper braid, must be used and the length of this connection must be kept to the minimum. A wire-wound potentiometer is quite unsuitable, as its inductance is very appreciable. A similar low value of minimum resistance must be obtained in the sweep control, or it will be impossible to achieve an unmodulated R.F. output. It is difficult to find a commercial component with a low enough resistance and the writer found that an ex-Government wire-wound component proved most successful, giving at its lowest setting only 5kc/s sweep. It should be noted that the SVC1 diode, at moderate D.C. potentials, is relatively very sensitive to a small A.C. input.

## Components

Apart from the foregoing simple precaution, there are no special difficulties about the circuit. All resistors are  $\frac{1}{4}$ W; the oscillator capacitors of 100pF or less are silver-mica; all the 1000pF capacitors are disc-ceramic types, while the remainder may be of tubular or ceramic type. Layout is not critical in any respect, although of course in the oscillator circuit, stray capacitances must be kept to the minimum by careful wiring.

## Alignment

1. *Aligning the 200c/s multivibrator*  
(a) Attach phones via 0.01 $\mu$ F capacitor between R7 and chassis.

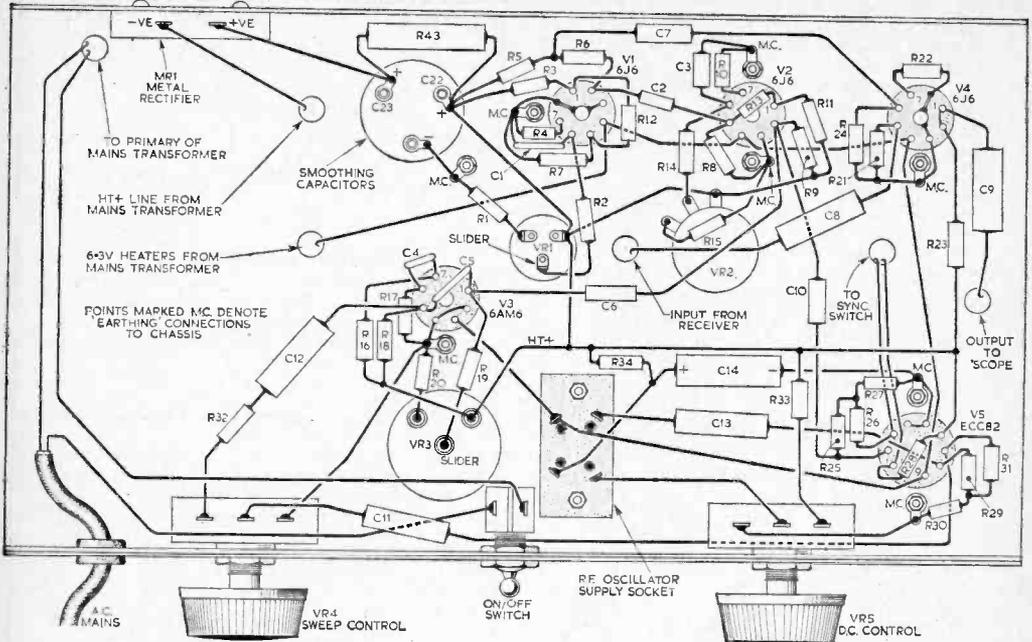


Fig. 11.—The underchassis wiring diagram.

(b) Rotate VR1, until the note is flat on A below middle C and a little sharp on F below middle C. If an audio generator is available, adjust to 200c/s. The above gives "near enough" alignment.

- (a) Attach phones between R10 and chassis.
- (b) Rotate VR2 until a rapid flutter is heard—not really recognisable as a note.
- (c) Insert 4-6in. of bare wire in the "input from receiver socket, to pick up hum.
- (d) Connect Y-amplifier output to oscilloscope, and adjust trace to about 10 sweeps/sec.

2. Aligning the 20/c/s multivibrator and sawtooth generator

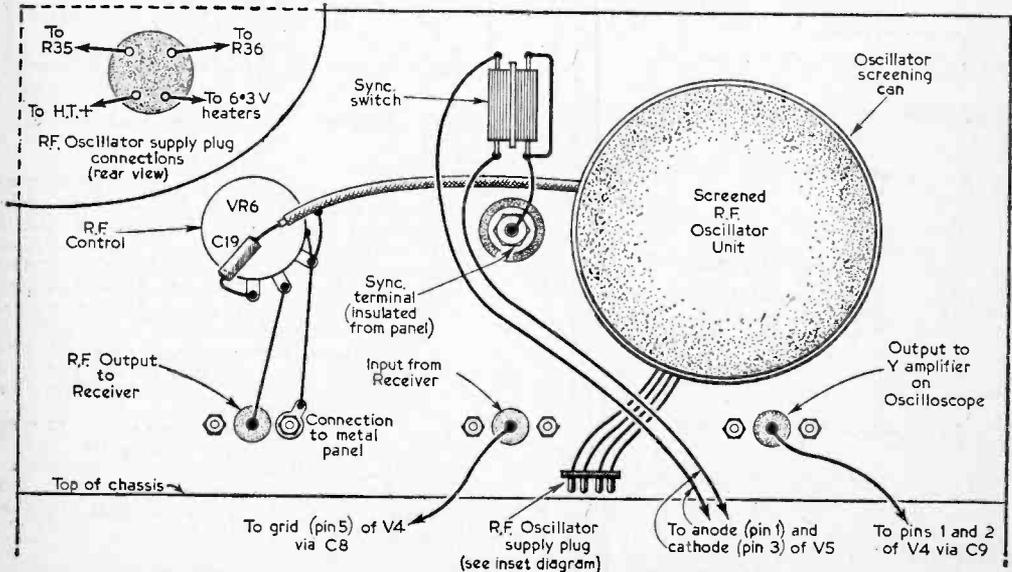


Fig. 12.—The connections to the rear of the front panel (inset: the plug connections for the R.F. oscillator).

(d) An A.C. waveform should now be visible on the scope. Keep it as steady as possible without sync, and adjust to show 4 or 5 traces.

(e) Correct the adjustment of the 200c/s multivibrator by rotating VR1 until each A.C. wave shows 4 markers exactly (see illustration on page 613 of the September issue).

(f) Remove the plug from the "Y-amplifier" socket on the wobulator and connect the lead instead to the "sync" terminal on wobulator. Rotate VR2 until over 5 A.C. waves are displayed, 2 pulses are visible and steady.

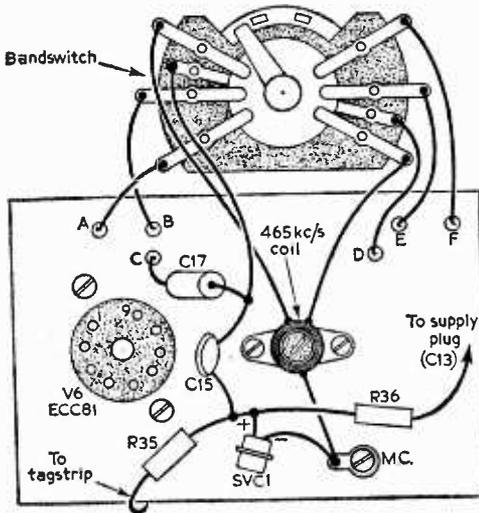


Fig. 13 (above)—R.F. oscillator coil switching.

Fig. 14 (below)—The dimensions of the side panels.

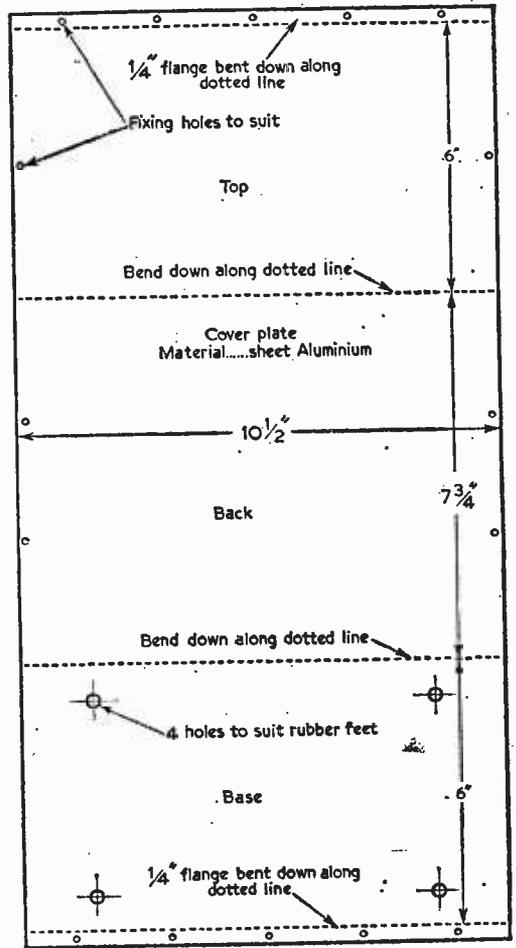
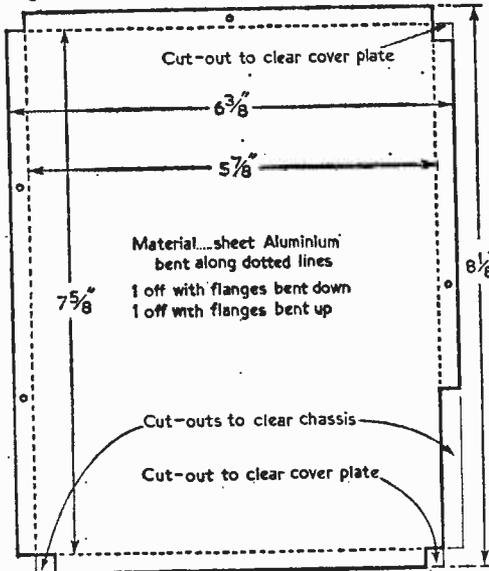


Fig. 15.—Construction details of the wrap-round case.

(g) Disconnect the lead to the oscilloscope from the sync terminal and attach it to the anode of the 6AM6. Disconnect the length of pick-up wire from the "output from receiver" socket; rotate VR3 until 2 perfect sawtooths appear. These should be somewhat "exponential" in shape, negative-going, as shown in Fig. 6 (last month). If they are too linear, try connecting a 1M or 500k resistor between the grid of the 6AM6 and its anode, but this need not be tried just yet.

(h) Connect the oscilloscope "external sync" terminal to the wobulator "sync" terminal, and adjust the oscilloscope trace to 20c/s; use as little sync as possible. The trace should now lock, displaying one sawtooth only.

(To be continued)

**J**HERE are times when a little extra sound and vision gain would make the difference between tolerable reception and good reception. In past pages of this magazine various methods have been discussed for improving the overall gain, especially of the older type "service area" television receiver, by the use of a pre-amplifier, an extra I.F. amplifier stage, decreasing bandwidth and similar dodges. Most of these have their own particular appeal to the experimenter.

#### Low-noise Input Stage

A pre-amplifier, for example, is simple to fit and rarely calls for modifications to the receiver. By using a preamplifier with an ultra-low-noise input stage (see, for example, "A Nuvistor Band III Preamplifier" by R. E. F. Street, PRACTICAL TELEVISION July, 1961) an improvement in noise performance over that of the receiver's first stage is often accomplished. This is highly desirable in those areas where the aerial signal is notoriously weak, for it lifts the overall sound and vision gain without introducing extra noise in the form of "snow" on the picture and "hiss" on the sound.

However, quite a few of the more recent receivers using multi-channel tuners with a double-triode cascode R.F. amplifier already possess a reasonably good noise performance, and it is often difficult to improve on this by adding a similar type of preamplifier. Indeed, if the pre-amplifier is of poor design or construction the receiver's noise performance may be impaired instead of improved and, although a "brighter" picture may be obtained, the snow effect may be so bad as to make viewing virtually impossible on all but strong signals.

The sensitivity of a receiver is given in terms of so much signal voltage required to produce a given peak white picture signal at the cathode of the

picture tube. Vintage receivers require approaching  $100\mu\text{V}$  to give about 2V at the cathode of the tube. Modern receivers give about the same cathode voltage for around  $10\text{-}20\mu\text{V}$  of aerial signal.

This is only one factor, however, for it is the maximum *usable* sensitivity that is most important, and this is governed by the noise factor of the R.F. amplifier or pre-amplifier. It would be pointless to say:—"my set is highly sensitive, it only requires  $10\mu\text{V}$  aerial signal to give a peak white picture"—if, in fact, the set requires about  $100\mu\text{V}$  to outweigh the noise of the first stage or pre-amplifier!

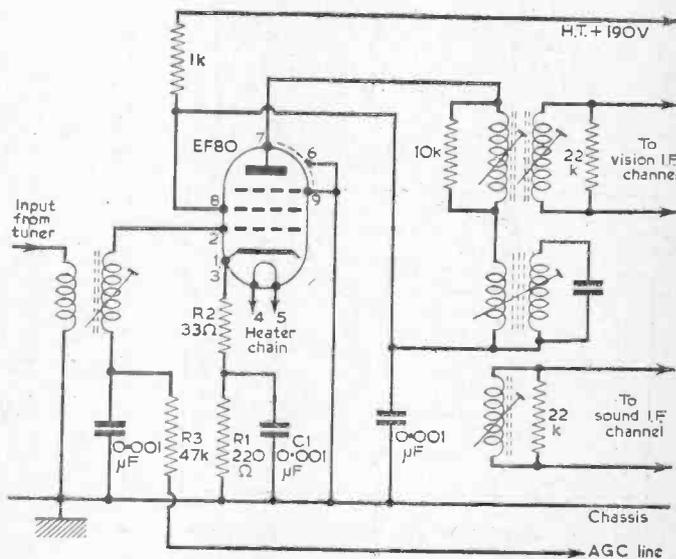


Fig. 1.—A conventional common I.F. amplifier stage, using an EF80, working at a maximum gm of about  $6\text{mA/V}$ .

An extra I.F. amplifier stage, if common to both sound and vision, would give considerably improved sensitivity and would have no effect on the noise performance. The noise performance would, in fact, remain almost exactly the same as the original conditions. An extra stage of this kind requires to be built on the receiver chassis, and requires extra components, including coils.

Reducing the vision bandwidth to achieve a greater overall vision gain was the vogue among experimenters in days gone past. Test Card C was usually used as the signal source and the various vision channel cores were judiciously adjusted one at a time to produce a brighter picture whilst retaining as much bandwidth as possible, as revealed by the frequency gratings on the Test

**IMPROVING  
RECEIVERS  
WITH**

**FRAME GRID VA**

Card. Invariably the whole process used to go out of control and the experimenter was left with a grossly misaligned receiver and with poorer pictures (and sound) than when he started the exercise.

#### Frame Grid Valves

With the advent of frame grid valves the problem has been considerably simplified. In essence, the frame grid valve has a far higher slope or mutual-conductance (gm) than its conventional counterpart, and since the gain of an amplifier stage is equal to  $gm \times Z_p$ , where  $Z_p$  is the impedance of the anode circuit of the valve, it follows that the higher the gm the higher the stage gain.

Slope or gm is dependent on the distance between the cathode and grid of the valve—the smaller the spacing the higher the slope. The higher slope of frame grid valves results, therefore, from the use of finer, closely spaced grid wires. The diameter of the grid wire is no more than 10 microns, and the grid-cathode spacing is 50 microns. These are small distances when it is realised that an average human hair is about 75 microns in diameter and that it would not be possible to insert a piece of it between the cathode and grid, and the diameter of the grid wire itself is about seven times smaller than a hair! (A micron is one ten-thousandth of a centimetre, and there are approximately two and a half centimetres to the inch.)

In order to produce such an exacting grid assembly, the grid wires are wound on backbones of rigid molybdenum rods, which are held a determined distance apart by cross pieces, giving the frame grid construction. The backbones are drawn to size within a close tolerance of  $\pm 5$  microns, while the tolerance of the grid wire is as small as  $\pm 0.2$  microns.

#### Available Valves


There are four main types of frame grid valves for use in signal circuits, and these are a double-triode for cascode R.F. amplifiers; a triode-pentode frequency changer; a variable- $\mu$  R.F. pentode for AGC I.F. amplifiers; and a straight R.F. pentode for I.F. amplifiers using little or no automatic or manual gain control. There are also other types

being launched and coming into full scale production.

It should be understood that increased gain cannot usually be achieved simply by replacing the conventional valves in a receiver with frame grid specimens. When a designer decides to use frame grid valves, then he develops the circuit to take full advantage of the attributes of the new valves. From the point of view of set design, frame grid valves mean that a given gain can be accomplished by the use of fewer stages or that improved sensitivity can be achieved by using the same number of valves as in a conventional receiver but using combination of frame grid and conventional valves.

Sets are now being made with frame grid valves in the tuner (e.g., Mullard PCC89 and PCF86) and a frame grid common I.F. amplifier (EF183). If the sound and vision I.F. amplifiers each use a conventional EF80, the sensitivity on Band III for a 2V vision signal at the tube cathode is about  $10\mu V$  (less on Band I). Similar sensitivity figures are achieved by the use of a PCC89 R.F. amplifier, PCF80 (conventional valve) and frame grid I.F.

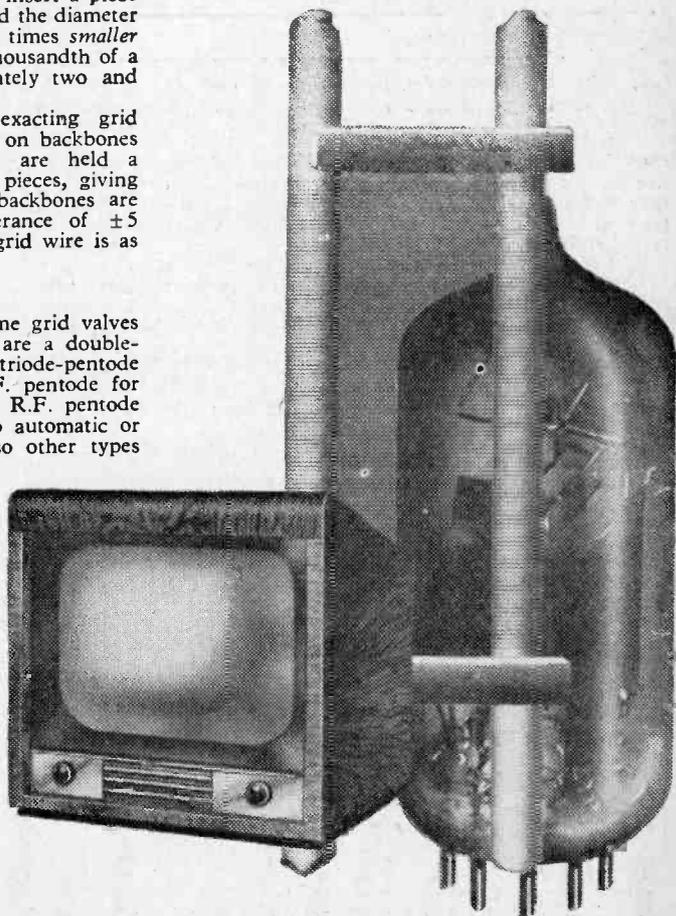BY MODIFYING CERTAIN STAGES IN A TELEVISION RECEIVER, VISION AND SOUND GAIN CAN BE INCREASED.



By D. B. Chappell

VALVES

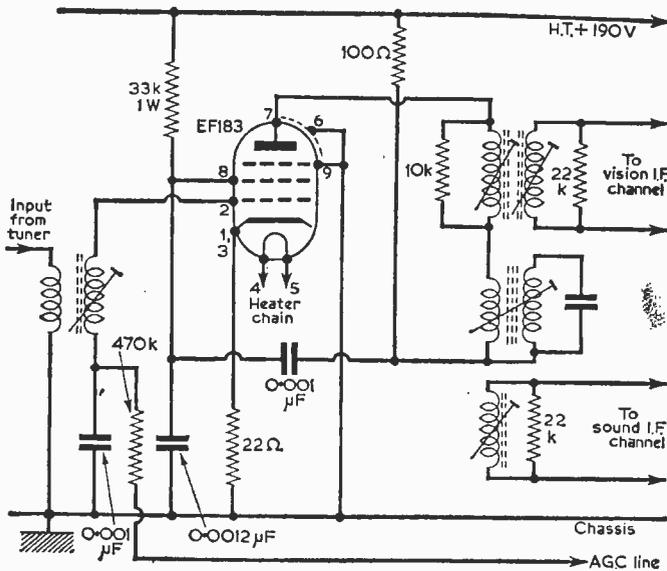


Fig. 2.—The circuit of Fig. 1 rearranged for use with an EF183 frame grid variable- $\mu$  pentode. This circuit gives an effective gm of about 12mA/V.

amplifiers—e.g., EF183 common, EF183 sound I.F. and EF184 vision I.F. The EF183 is a variable- $\mu$  type and the EF184 a straight pentode, and compare with the lower slope EF85 and EF80 valves respectively.

The gain advantage of the frame grid type valves in comparison with conventional types is of interest and is detailed below:—

- PCC84 to PCC89—5—7dB
- PCF80 to PCF86—6dB
- EF85 to EF183—6—8dB
- EF80 to EF184—6—8dB

These figures show that a receiver can be made

approximately twice as sensitive by replacing a conventional valve with a frame grid counterpart—6dB being a 2:1 step up in voltage gain, which is brought about by a gm of a frame grid valve being approximately twice that of the conventional counterpart.

It should be understood, of course, that twice the gain in a single stage would mean four times the gain in two stages, eight times the gain in three stages, sixteen times the gain in four stages and so on, but in practice a receiver is rarely designed to exploit a valve to its very maximum.

**Lower Noise**

The total gain that can be obtained in a tuner by the use of two frame grid valves (e.g., PC89 and PCF86) is in the region of 60dB (1,000 times), and this can be accomplished without any impairment in noise performance. Indeed, by sacrificing just a little of this gain, and paying extra special attention to the design of the tuner, the noise performance can be enhanced.

It must be stressed, however, that this is not possible simply by replacing the tuner valves; the circuit has to be carefully engineered to suit the valves. Experimental work is in hand to adapt old-style tuners to work with the new valves, and details of this work will be given in a later issue of PRACTICAL TELEVISION.

The PCC89 can also handle about five times more signal than its conventional counterpart before intermodulation becomes troublesome. This means that sound-on-vision and vision-on-sound interference does not occur so quickly when the aerial signal is increased. In older sets, it will be recalled, it was often necessary to introduce external attenuators in areas of high signal strength to eliminate intermodulation effects. Sets using the new valves can handle a far greater signal range for a given intermodulation factor.

**The EF183 as Common I.F. Amplifier**

In Fig. 1 is shown a fairly conventional common I.F. amplifier stage using an EF80 R.F. amplifier. This employs cathode biasing (R1) and is decoupled to R.F. by C1. The unbypassed 33Ω resistor is to prevent detuning of the amplifier by the AGC voltage which is applied to the control grid through R3. Without R2, the input capacitance of the valve would alter sufficiently with changes in bias to cause detuning of the grid circuit. This is avoided by the negative feedback resulting from the un-

(Continued on page 99)

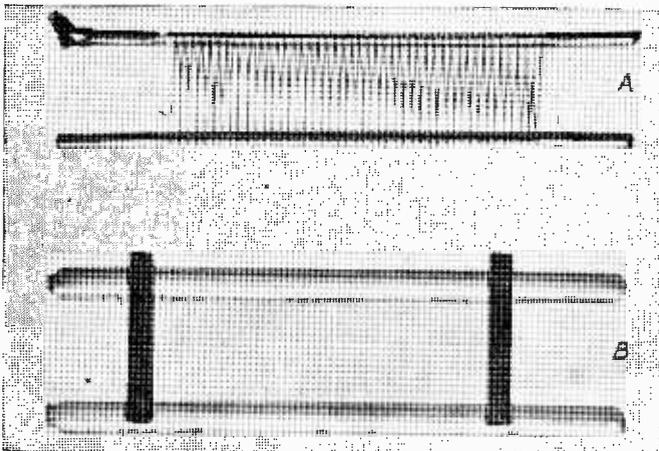


Fig. 3.—“A” illustrates a conventional grid, and “B” is a frame grid. Both are shown magnified.

# TRACING TV FAULTS

(Continued from page 22 of the October issue)

By G. J. King

**T**HIS month the tuner will be dealt with fully (stage 3 in Fig. 1 in the September issue) as will the Common I.F. stage (stage 4).

## Blank Raster (No Sound or Vision)

Because a raster (illumination on the whole of the screen) is present, one can conclude immediately that the H.T. circuits are working, that both timebases are working, that EHT voltage is present on the picture tube and, if the brightness control turns the raster brightness up and down correctly, that the video amplifier and tube biasing circuits are in order.

It would now be a good idea to turn to Fig. 1 again. Since there is neither sound nor vision, the trouble is almost certain to lie somewhere in those stages common to both the sound and vision signals. If the symptom occurs only on one channel, say, the BBC channel, then the most likely cause would be a break in the connections between the BBC aerial (1A—Fig. 1) and the diplexer—2.

The aerial could be all right, of course, in which case the fault would lie in the tuner. In turret tuners, in particular, it sometimes happens that a connection on one of the coil biscuits breaks or that the biscuit falls out of position preventing its contact studs from making good connection with the spring contacts connected to the tuner circuits.

When this kind of trouble is responsible, the raster is perfectly clear when the tuner is switched to the offending channel. There is no grain, not even with the contrast control turned right up, and there is only a very slight trace of a hiss on sound. However, if a broken aerial connection is responsible, the raster will be full of grain (snow effect) and there will be an appreciable hiss from loudspeaker, and possibly very slight sound in the background.

## Failure in a Common Stage

We must now assume that the raster is clear of grain on both channels and that there is virtually no hiss from the loudspeaker. In this event, a fault in a stage common to both the vision and sound signals is most likely. The symptoms could be caused by separate failures in individual sound and vision stages, but this is extremely unlikely.

We have cleared stages 1A, 1B and 2 (Fig. 1), and all the other stages, of course, except the common ones, 3 and 4. Thus, the exercise starts with the examination of these.

The best thing to do first of all is to eliminate the tuner. This is a simple matter if one is in possession of a signal generator tunable over the I.F. bands, for then a signal may be injected at the control grid of the common I.F. stage, and the

modulated signal tuned first to the sound I.F. and then to the vision I.F. If the common stage is working, the modulation will be heard from the loudspeaker and horizontal bar patterns, due to the modulation, will appear on the raster. If the stage is "dead" neither of these things will happen, and it would be concluded that the trouble is in the common stage, thereby clearing the tuner itself.

## Long-wire Aerial (see Fig. 4)

Without a signal generator, things may not be quite so conclusive. Nevertheless, it is usually possible to glean some idea of the condition of the stage by connecting a long-wire aerial to the control grid of the common I.F. valve. The receiver's contrast, volume and sensitivity (if fitted) controls should be turned full on and the brightness control adjusted to give a raster of normal brightness.

When the long-wire aerial is connected a distinct crackle should be heard from the speaker and, under certain conditions, sound programmes of Continental origin will also be heard. On the raster, moving, dark, horizontal bands will appear due to the modulation of the sound signals (falling within the vision I.F. spectrum) which are amplified by the common I.F. stage and the vision I.F. stage.

Another way of injecting a signal, if stations do not happen to be radiating within the I.F. bands, is to direct the long-wire aerial close to a domestic electrical appliance, such as a vacuum cleaner or hair dryer. The interference from the appliance as picked up by the aerial will cause severe interference effects on the raster and typical interference disturbance on sound or from the speaker.

## Circuit

In Fig. 4 is given the circuit of a turret tuner and common I.F. stage, and the point at which the long-wire aerial should be connected is also shown.

If signals cannot be directed through the common stage then this should be examined in some detail. There is really not a lot in the circuit, and observation will show whether the valve heater is intact. A finger test of temperature will indicate whether H.T. current is passing through the valve, and the envelope temperature should be comparable to that of a correctly working I.F. stage, as already dealt with. If the valve is only just warm, an emission test at a dealer's shop would pay. If the valve is in good order, attention should be given to the anode and screen grid feed resistors and their associated decoupling capacitors, such

as R27 and C33 in Fig. 4. An open-circuited cathode resistor (R24 or R25) would destroy normal operation, and a voltmeter test at the cathode (pins 3 and 1) would show almost full H.T. voltage between that point and chassis in that event. If a meter is not available, a quick test could be made by connecting a 180Ω resistor between cathode and chassis. Shorting decoupling capacitors would be revealed by the associated decoupling or feed resistor being burnt and possibly cracked.

### Checking the Tuner

Assuming now that the common I.F. stage is without fault, then the trouble must lie somewhere in the tuner. Unfortunately, the tuner is rather a tricky item to test without instruments; indeed, even with instruments, it can present a problem, since the components are soldered in circuit with very short leads close to the base of the valveholders, which are usually deep down in the tuner chassis, beneath the switch or turret mechanism.

It is recommended that if the fault is proved to be in the tuner, and the valves check normal, the repair should be handed to a person fully experienced in the art of television servicing. Even dealers' service engineers sometimes return defective tuners to the manufacturer for service—and some manufacturers, in fact, recommended this procedure.

### Critical Circuits

Apart from the mechanical difficulties involved, tuner circuits are highly critical as they have to handle very-high-frequency (VHF) signals. They also have to be in perfect balance so that the overall response remains identical on all channels. Unskilled servicing can quickly destroy the balance

and, although the tuner may eventually be made to work again, it is always debatable whether it is working efficiently or not. The tuner is really the most important part of the set, for it is here that the aerial signals are developed into noise-free I.F. signals for subsequent amplification. Poor servicing may well increase the "noise factor" of the tuner and make it almost unsuitable for use in poor reception areas, especially on Band III—the ITV band.

There are one or two consistent faults which occur in tuners and result in failure of sound and vision. These are: a short developing in C18 or C21 causing burn-out of R12 or R14 (see Fig. 4) and sometimes the main H.T. decoupling capacitor (C24), which is often a feed-through type, becomes short-circuited and the tuner H.T. feed resistor (R18) then burns out. Burn-outs of this nature can usually be seen by carefully examining the likely components.

Before finally deciding to remove the tuner for repair or to have the local dealer service the set, attention should be given to the various leads and cables coupling the tuner to the main chassis, for the symptom under discussion has been known to be caused by a fracture of the inner conductor of the coaxial cable linking the tuner to the main chassis. This cable may also become hot owing to incorrect routing near a valve or hot resistor, and when this happens there is a likelihood of the polythene melting and the inner conductor making connection with the outer braid. Similar trouble may occur owing to the soldering iron being left in contact with the conductors too long when soldering the ends. The short may not occur immediately, but may only develop after the set has been in service for some time.

(Continued on page 91)

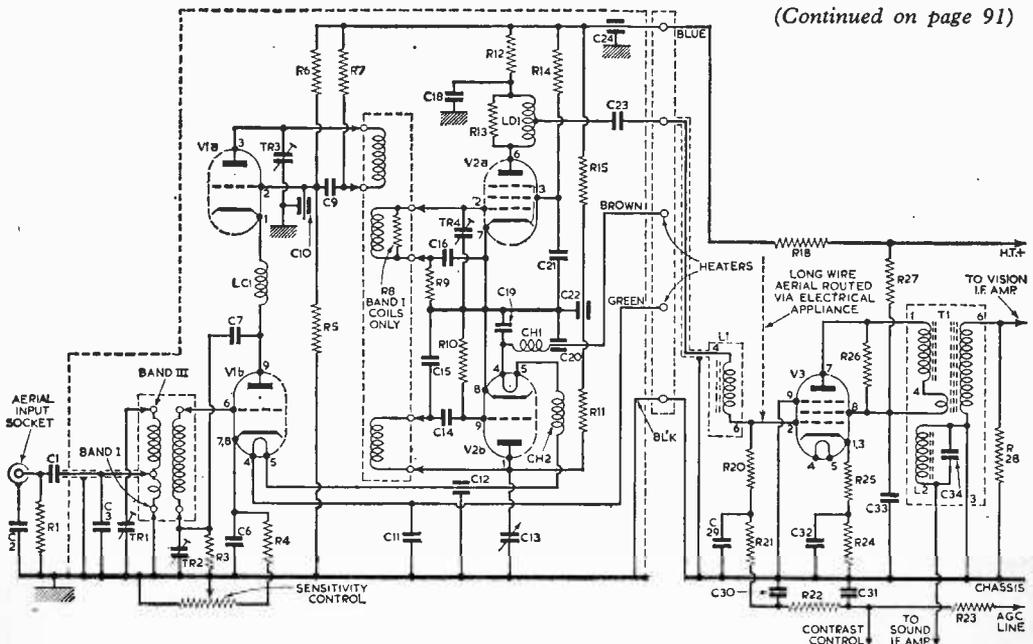


Fig. 4.—The tuner and common I.F. stages (stages 3 and 4 in Fig. 1 on page 616 of the September issue).

# THIS YEAR'S BARGAIN IN CATHODE-RAY TUBES

**12" ENGLISH ELECTRIC**      **39'6**      **12" ENGLISH ELECTRIC**

(plus 5/- carriage home)

**Brand new tubes directly equivalent to:**

**Mullard MW31/74 (or 31/16)**

**Brimar C12FM**

**Cossor I21K**

**Emitron I2AXP4 (or I2XP4A)**

**Ferranti T12**

These are not sub-standard or regunned but brand-new tubes in original cartons made for a well-known manufacturer, and now surplus to requirements.

*Every one guaranteed tested and perfect on dispatch.*

**Also 14 and 17 inch.**

14in. electrostatically-focused tube directly equivalent to **AW36/21** at 80/- plus 5/- carr.

17in. directly equivalent to **Mazda CRM172** at 100/- plus 5/- carr.

17in. exactly as **Mazda CRM171**, but with 6.3 volt heater at 90/- plus 5/- carr.

**ALL BRAND-NEW AND GUARANTEED TESTED ON DISPATCH**


CASH WITH ORDER, please, to:

**MERCHANT FINANCE (LONDON) LTD.**

**Berkeley Square House, Berkeley Square  
London, W.1.**

Mail Order only. We regret that we cannot cater to callers.

## EX-RENTAL SETS

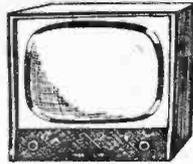

**17 INCH £11.10.0**

Excellent Table models. ITA/BBC. Famous manufacturer. 12 months' guarantee. Terms available. Collection advised. Delivery rate by arrangement up to 50 miles, or despatched in 3 parcels for easy assembly, 25/-.

**14 INCH £7.10.0**

ITA/BBC. Identical to 17in. TV. Ideal for Caravans, Weekend Bungalows, Chalets, etc. 12 months' guarantee. Terms available. Carriage 20/-.

## REBUILT REPLACEMENTS TV TUBES

21in. . . . . **99/6**


17in. . . . . **90/-**

15, 14, 12in. . . . . **70/-**

Ins. and Carr. 15/6  
12 Months' Guarantee.



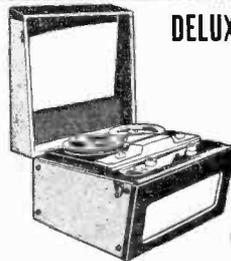£1 extra without old bowl, refundable if same received within 14 days.



## DELUX RECORDER CABINET

**79/6**

Beautifully styled rexine covered cabinet, in Red or Beige. Size 14½ x 13 x 9½in. Storage comp. in lid for tapes and mike. Easily adapted to Record Player Cabinet. Ins., Carr. 5/-.

## TAPE RECORDER AMPLIFIERS

**£9.15.6**

**£7.19.6**




By famous manufacturer. Superb 4-valve amplifier. Two controls and superimpose switch. Sockets for Mike and Gram. Size 11 x 4 x 6in. Ins., Carr. 5/-. Drawings FREE with order.

Compact, well designed 5-valve amplifier. Output 3.5W. Input for Microphone, Radio and Gram. Size 8½ x 3 x 4½in. Ins., Carr. 5/-. 12 months' guarantee. Terms available. Extras: Dial plate, including sockets and superimpose switch, 3/6. Knobs 2/6.

## SCOTCH BOY TAPE 19/9

5½in. Limited Quantity. Post Free.

## EXTENSION SPEAKERS 19/9

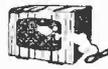

Bin. P.M. Speaker fitted into polished cabinet. Complete. Switch and flex included. P. & P. 4/-.

## ELLIPTICAL SPEAKERS

**15/9**

Brand new slot type. 8 x 3in. and 7 x 4in. P. & P. 2/9.

## TRANSISTORS

Per Set **47/6** Post Free

MULLARD

1—OC81D 6/9, 2—OC81 6/9, 1—OC44 9/9, 2—OC45 8/9, Diode 1/9.

GEC — EDISWAN

114 6/9 1 XC121 8/9  
873 8/9 1 XB113 8/9  
2—874 9/9

## VALVES

Salvage Guaranteed

**5/9 each 60/- Doz.**

6AB6, 6F6, 6Q7, 6V6, 12K7, 12Q7, 7AN7, 9BW6, 15A6, ECL80, ECC83, PCC84, PCF80, PL38, PL81, PL82, PY80, PY81, PY82.

Postage

1—7d. 6—1/6 12—2/6

**DUKE & CO. (London) LTD.**

621/3 ROMFORD RD.  
MANOR PARK E12  
ILford 6001/3  
Send for Free List

# ALPHA RADIO SUPPLY CO

## MULLARD TRANSISTORS

OC19 48/-	OC72 8/-	OC78D 8/-
OC35 25/6	OC72pr 16/-	OC81 8/-
OC44 11/-	OC73 16/-	OC84 11/-
OC45 10/-	OC75 8/-	OC170 13/6
OC70 6/6	OC77 10/-	OC171 14/6
OC71 6/6	OC78 8/-	OC202 36/6

## A SPECIAL OFFER OF SIX MULLARD TRANSISTORS

1 OC44, 2 OC45, 1 OC81D, 2 OC81.  
Only 37/6 set.

## EDISWAN TRANSISTORS

XAI04 12/-, XAI03 10/-, XBI02 6/6 ea.

## LOUDSPEAKER UNITS

All Brand New

2 1/2 in. square Rola C25	26/10
2 1/2 in. square EMI	18/6
4 in. square Elac Tweeter	12/6
5 in. round Plessey with O.P.T.	16/6
6 1/2 in. round Celestion	17/6
8 in. round Richard Allen	18/6
10 in. round Elac	25/-
12 in. round Plessey	29/6
6 in. x 4 in. Plessey	19/6
7 in. x 4 in. Plessey	19/6
8 in. x 5 in. Celestion and Richard Allen	19/11
10 in. x 6 in. Celestion and Plessey	22/6

## VALVES BY RETURN POST

AZ1 10/-	EF91 5/9	PCL82 11/6
DF96 8/-	EF92 6/-	PCL84 13/6
DAF96 8/-	EL41 9/-	PL36 13/6
DK96 8/-	EL84 9/-	PL81 11/-
DL96 8/-	EL91 4/6	PL82 8/6
EABC80 9/-	EM80 9/6	PL84 12/7
EAF42 9/6	EM81 10/6	PX25 12/6
EBC41 8/9	EY51 9/6	PY32 15/6
EBF80 9/9	EY86 9/6	PY80 8/6
EBF89 9/6	EZ40 7/6	PY81 8/6
ECC81 8/-	EZ80 7/-	PY82 7/-
ECC82 7/6	EZ81 7/-	U25 13/6
ECC83 9/-	FC13 5/-	UAF42 9/6
ECC84 10/-	GZ32 11/6	UBC81 11/4
ECC85 9/6	HL42DD	UCC8410/11
ECF80 12/-		UCH42 9/6
ECF82 10/6	OZ4 4/6	UCL82 11/6
ECH42 9/6	PCC83 13/6	UCL83 16/-
ECH81 9/-	PCC84 8/6	UF85 9/-
ECL80 9/6	PCC85 11/6	UL41 9/-
ECL82 10/6	PCF80 8/9	UY41 6/6
EF50 5/-	PCF82 11/6	3D6 5/-
EF86 12/6		

Hi-Fi Transistor FM Tuner for the Home Constructor, complete kit £18/18/-. Fully illustrated booklet with diagrams, full shopping list etc. 3/6.

## LOUDSPEAKER CABINETS

Type suitable for an 8 in. unit.....21/-  
Type suitable for a 10 in. unit.....25/6  
Type suitable for a 7 x 4 in. unit.....17/6

## CATALOGUE

OUR 1962 CATALOGUE IS NOW AVAILABLE. PLEASE SEND 1/- IN STAMPS FOR YOUR COPY. TRADE CATALOGUE ALSO AVAILABLE, FOR WHICH PLEASE ATTACH YOUR BUSINESS LETTER HEADING.

## CRYSTAL CALIBRATOR No. 10

Crystal controlled. Directly calibrated. Functions: Crystal controlled oscillator providing fixed frequency signals of 500 kcs and all harmonics of 500 kcs up to 30 mcs variable oscillator from 250 kcs—500 kcs, enabling all intermediate frequency between 250 kcs to 500 kcs to be produced and modulated. Complete in carrying case/bag with all valves, leads and instruction book. £4/10/- each.

## RECTIFIERS


RM1 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RMS 19/6, 14A86 19/6, 14A97 19/6, 14A100 19/6, LW7 17/6, 18RA 1-1-16-1 6/-, FC31 (14RA 1-2-8-3) 22/6, FC101 (14RA 1-2-8-2) 10/6.

ALPHA RADIO TERMS.—Cash with or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 1/3; 20/- add 1/9; 40/- add 2/6; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday. Saturday 10 a.m. to 1 p.m.

**ALPHA FOR VALVES AND SPARES FROM STOCK**

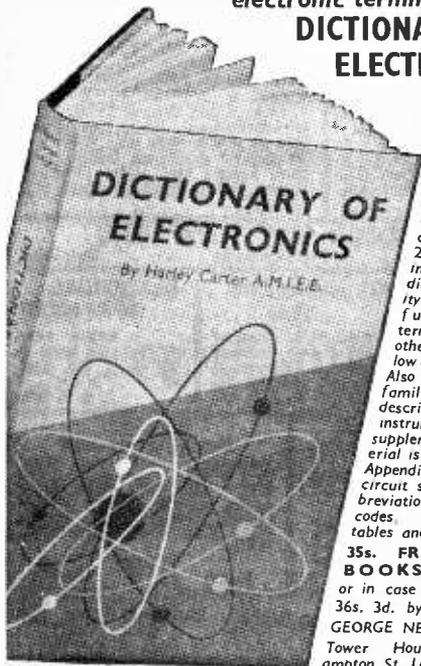**103 LEEDS TERRACE, WINTOUN STREET, LEEDS 7.**

For all who want to understand modern electronic terminology—  
**DICTIONARY OF ELECTRONICS**



by HARLEY CARTER A.M.I.E.E.

384 pages with extensive cross-indexing 232 line drawings and circuit diagrams. Priority is given to fundamental terms and the other entries follow on from these. Also listed are familiar terms and descriptions of instruments. Much supplementary material is given as an Appendix, including circuit symbols, abbreviations, colour codes, conversion tables and valve bases.  
**35s. FROM ALL BOOKSELLERS** or in case of difficulty 36s. 3d. by post from GEORGE NEWNES Ltd Tower House, Southampton St. London, WC2

# CLARKSON'S TUBE CHANGE

6A DENISON ROAD, LEEDS 2  
Tel. Leeds 24576.

We are now able to offer SUPER SCREEN TV TUBES with 12 months' guarantee at the keenest exchange price ever.

Example:

Tubes all types	Cash allowance on return of old tube	Actual cost of Tube
12"–14" £5	15/-	£4. 5. 0
15"–17" £6	25/-	£4. 15. 0
21" £8	30/-	£6. 10. 0

Carriage and Insurance 10/- extra

These tubes are COMPLETELY REBUILT by experts, with the most up-to-date electronic equipment, and are fitted with the famous American Golden Grid Electron Gun. Many thousands of these tubes are in service today. Our factory is open to inspection to readers of "Practical TV". Technical advice and queries are answered free of obligation. All tubes are dispatched with adhesive paper and return labels. Cash allowance is sent on receipt of old tube.

(Continued from page 88)

**Blank Raster (Sound Normal)**

The fact that the sound is normal would indicate that the fault resulting in this symptom lies somewhere in the vision I.F. amplifier, vision detector or video amplifier stage (stages 5B, 6B or 7B Fig. 1). There is also a possibility that the tube is responsible, but this will show up by making a few control knob adjustments.

The first clue lies in the behaviour of the brightness control; if this has no effect on the brightness of the raster, then we can conclude that the tube biasing is faulty and that it is not being varied,

**Faulty Valve**

Now, if it is necessary to turn the brightness control fully down to black out the screen, it would follow that the cathode has gone less positive than it should, and this would be caused by a short-circuit within the video amplifier valve itself.

If the emission of the video amplifier valve fails, the anode voltage (and hence the tube cathode voltage) will rise and produce the opposite effect on the brightness control—the control would need to be turned up fully to obtain any illumination. Thus, the operation of the brightness control has provided a key clue.

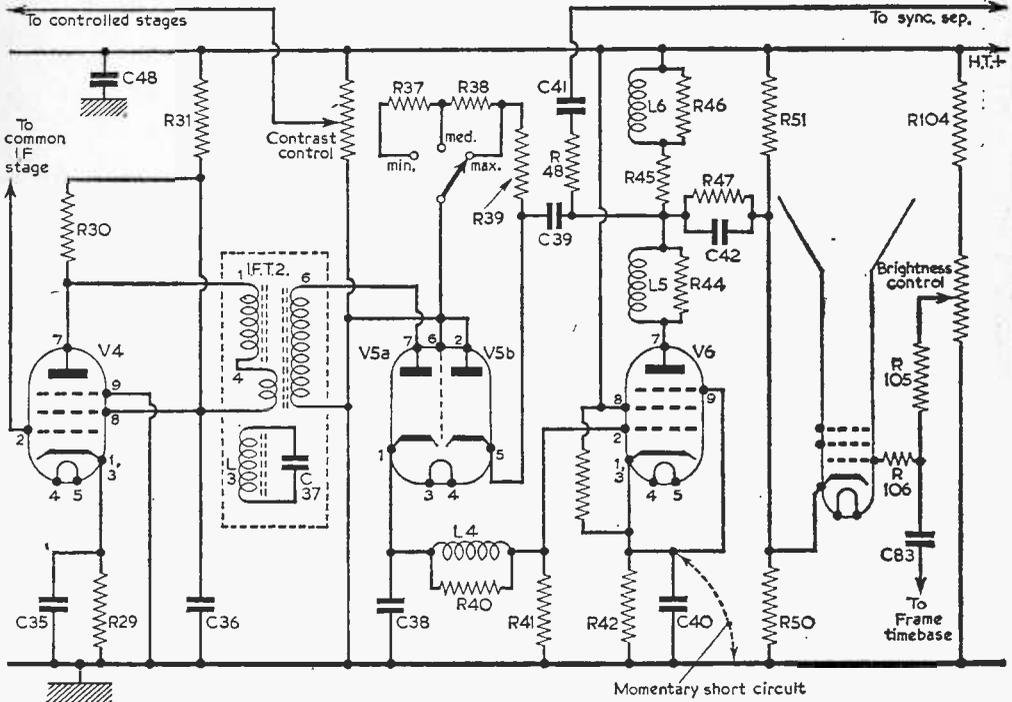


Fig. 5.—The vision I.F., detector, vision amplifier, and picture tube biasing circuit.

as it should be, by the brightness control. In nine cases out of ten, this is caused by a heater-to-cathode short in the picture tube.

**Bias Arrangements**

If the brightness control does work in a limited manner, in that it is necessary to turn the control fully anti-clockwise to black out the raster, then, if this is not normal when the set is working properly, the loss of picture has also resulted in a disturbance to the tube biasing conditions. Generally, the tube cathode is in direct connection with the video amplifier anode (see Fig. 5). The cathode is thus at a positive potential, and the correct bias is produced by the grid also being positive, but to a smaller degree, as set by the brightness control. In effect, the grid is negative with respect to the cathode, even in the position of maximum brightness, and the negative voltage at the grid rises as the brightness control is turned down.

Let us now assume that the brightness control operates normally on the raster. We can be fairly certain that the video amplifier stage is *not* responsible; however, to be absolutely sure, all we need to do is put a momentary short-circuit across the cathode resistor (R42 in Fig. 5). If the video amplifier is working correctly, this will produce a change in the brightness of the raster. At that point the video amplifier stage can be eliminated.

If the cathode resistor short has no effect on the brightness (without altering the brightness control), then the trouble is undoubtedly in the video amplifier stage. In the latter event, close examination of the components associated with stage V6 should be undertaken. In Fig. 5 is shown a circuit of the vision I.F. stage, the vision detector and noise limiter, the video amplifier and the picture tube biasing arrangements.

(To be continued)

# T rade N ews

## Closed Circuit TV Trade Service

A LARGE stock of closed circuit equipment is now available to dealers, public address operators, and other similar organisations for use at conferences and exhibitions either with or without technical and production teams, from Audio and Video Rentals Ltd. The equipment, which includes cameras, tripods, lighting, sound system, cables, etc., is available by the day, or week.

The Trade Hire Service for Closed Circuit Television Equipment, as this new promotion is called, is operated by *Audio and Video Rentals Ltd., Video House, 27-29 Whitfield Street, London W.1.*

## Two New Receivers

TWO new TV receivers have been released by Stella under the name Stellascope.

Both the 19in. model (ST.1029U) and the 23in. model (ST.1023U) have pre-set stops on the channel selector combined with pre-set automatic fine tuning. Both receivers have cabinets with African walnut veneer finish and polyester protective gloss.

The 23in. model costs 74 guineas and the 19in. model costs 64 guineas.

*Stella Radio and Television Co. Ltd., Astra House, 121-123 Shaftesbury Avenue, London W.C.2.*

## Closed Circuit TV Camera

A CLOSED circuit television camera is available which can be connected to the aerial socket of a normal domestic receiver and produce a good picture in normal room lighting. This camera is the Beulah D.800 and costs 225 guineas.

*Beulah Electronics, 138 Lewisham Way, New Cross, London S.E.14.*

## TV Aerials at the Radio Show

THE "Monitor" aerial is the latest addition to the Belling-Lee range of set-top aerials. In addition to the adjustable telescopic elements, a fine tuner is incorporated, enabling the user to obtain the optimum adjustment. The change from one band to another is effected simply by means of a push-button switch. Provision has been included for future use on Bands IV and V, in anticipation of the requirements of a colour television service.


Another new aerial for use in the same room as the receiver is the Envoy. It functions as a compressed dipole in Band I, the length of the elements being compensated electrically by means of an internal loading coil according to the channel required, at the same time being correctly matched in Band III.

For the outer regions of the primary service areas a new collapsible attic aerial has been introduced, employing tubular elements which snap positively into position on erection. All these aerials are made by *Belling and Lee Ltd., Great Cambridge Road, Enfield, Middlesex.*
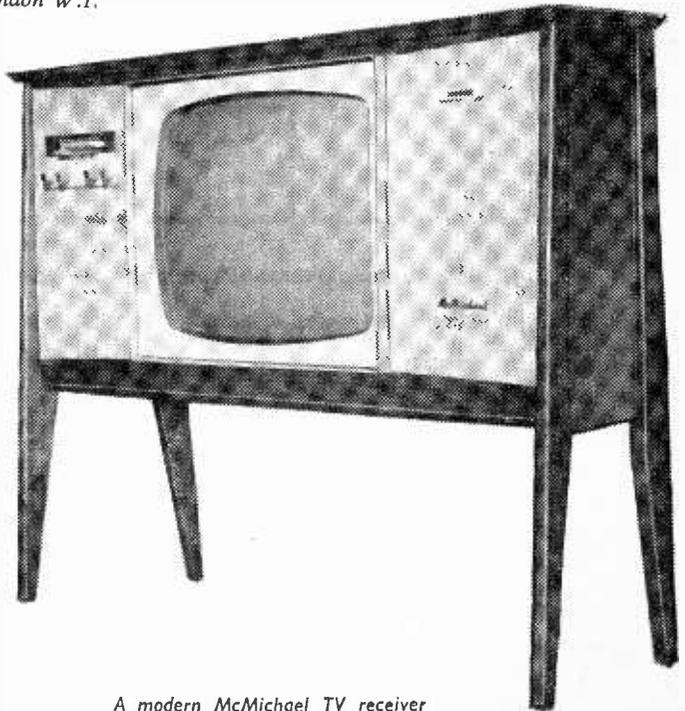
## 405/625 Line TV Receivers

THE Model T398 Ekco receiver, has a 19in. screen and provides for reception of existing 405-line transmissions and also 625-line programmes should they be introduced. All that will be required is a UHF tuner, which will be fitted by Ekco dealers at minimum cost when details of any new transmissions are available.

The price of this set is 73 guineas. It is made by *Ekco Radio and Television Ltd., Southend-on-Sea, Essex.*




A modern McMichael TV receiver

**NOW**

# YOU can MASTER ELECTRONICS!

## BRITAIN'S MOST COMPREHENSIVE PRACTICAL COURSE IN RADIO • ELECTRONICS TELEVISION!

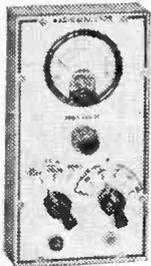
**THESE SPECIAL TRAINING KITS — YOURS TO KEEP**



Multi-Range TEST METER



CATHODE RAY OSCILLOSCOPE

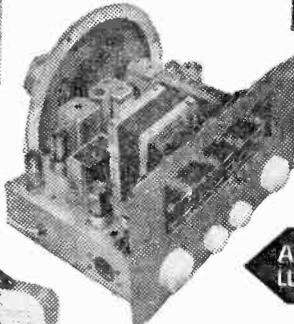

AM and VHF/FM LUXURY RECEIVER



SIGNAL GENERATOR




Complete set of Pictu-Waybooks and Experimental Manuals

LEARN BY BUILDING NOW for your CAREER • HOBBY OWN BUSINESS
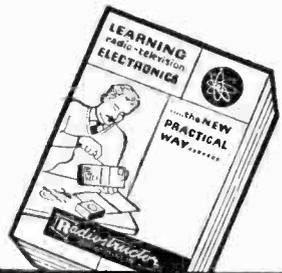
### YOU RECEIVE

- Complete kits of equipment as illustrated.
- Complete set of experimental manuals.
- Complete set of "picture-way" theory books.
- Modern test-yourself examination sheets.
- Study programme.
- Unlimited consultation with Tutors.



**FREE BROCHURE NOW**

## RADIOSTRUCTOR

TO RADIOSTRUCTOR (DEPT. M102) READING, BERKS.

Name \_\_\_\_\_ BLOCK  
 Address \_\_\_\_\_ CAPS  
 \_\_\_\_\_ PLEASE

(We do not employ representatives) 11/61

**SUB-MINIATURE COMPONENTS**

1. Ferrite aerial with Long and Medium Wave Coils 4 1/2 in. long for pocket superhet, complete with circuit showing component values etc. 7/6d.
2. Ferrite aerial as above, but 1/2 in. diameter, 5 in. long for table model receiver or portable. 10/6d.
3. Three I.F. Transformers with oscillator coil and circuit details to work with item 1. 19/6d.
4. Three I.F. Coils and oscillator to work with item 2. 23/6d.
5. Smallest possible electrolytics. 1MF, 2MF, 4MF, 5MF, 6MF, 8MF, 10MF, 20MF, 30MF, 50MF, 100MF, 200MF, all 1/9 d. each.
6. Smallest 1/2 watt resistors all 10% values 5d. each.
7. Miniature condenser .1 1/0d., .5, .04, .02, .01 all 8d. Values below this 7d.
8. Miniature slide switch double pole change over 2/6d.
9. Edgewise volume controls 2K, 5K, 10K and 20K 2/6d. each.
10. Small edgewise controls with switch 2K, 5K, 10K and 20K 4/9d. each.
11. Red Spot Transistors tested and suitable all A.F. applications 2/6d.
12. White Spot Transistors tested and suitable as I.F. or mixer 3/6d.
13. Set of six transistors for superhet Mullards in original packets, fully guaranteed, comprising OC44, OC45, OC45, OC81D and matched pair OC81. 22 the set.

**SPECIAL SNIP—this month**  
The Pocket "6" as described alongside, but fully made up and ready to work. £5.15.0, plus 2/6 post and insurance.

**NOW THE MARK IV**

Read These Testimonials

**D. A. Hillou, Leigh, Lancs.**  
"I received 'Pocket 4' on Christmas Day. I made it up on Boxing Day and am very pleased with the result. It brings in local stations and many foreign stations including Luxembourg at good strength. I am 13 years old."


**Mr. J. Bell, Wolverhampton.**  
"I am writing to express my satisfaction at the standard of your kit for your Pocket 4 Transistor set and also to state that it has come up to my expectations in regard to performance."

**Mr. R. Belt, Newcastle-on-Tyne.**  
"I have built your Pocket 4 Transistor set. I am very pleased with it."

**Mr. F. Jackson, Ickenham, Middx.**  
"I have built the Pocket 4 and am more than pleased with the results."

**Mr. G. Bamford, Ramsate.**  
"I find this set even better than you claim it to be and most certainly up to your usual standard of quality. I feel they probably could fail to build it and get results. Even the first-time-er novices, as your circuit diagrams and instructions are so clear and precise."

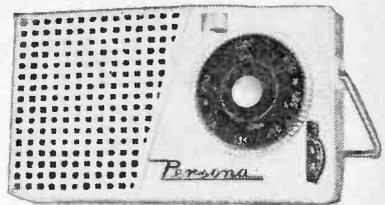**Mr. A. J. Simmonds, Welling, Kent.**  
"I purchased from you a week ago the Pocket 4 Transistor Kit, I put it together last night in 1 1/2 hours, on switching on the set I was right on Radio Luxembourg. I must say thank you because not only has the set a very attractive appearance, it also behaves fantastically."



Our famous Pocket "5" which is doing yeoman service all over the country has been modified and improved to make it an even better receiver. The new features include:—

- New elegant dial graduated for Long and Medium Waves.
- Switched Long and Medium Waves.
- Slide switch on/off control.
- Printed circuit.
- Ferrite Rod Aerial.
- Improved reaction circuit.
- Positive spindle coupling to tuner.
- Battery containers.

The Pocket "5" of course retains its original r.f. circuit which means still no aerial or earth needed.

The Pocket "5" Mark IV uses 4 transistors, crystal diode, miniature loudspeaker and has all the above refinements, complete in case as illustrated (less motif) 52/6. battery 10d., post and insurance 2/6. Motif 2/-.  
Pocket "5" as Pocket "5" but with Moving Coil Speaker and Q.P.F. output stage, 85/-.

Seven days' approval.  
Order in confidence. We allow you seven days to decide whether or not to make the set, you may return the parcel as received within this time and your money will be refunded in full.

Read some of the testimonials, over 1,000 of which have been received about our Pocket Receivers.

**ELECTRONIC PRECISION EQUIPMENT LTD**

★ Orders received by post are despatched from our warehouse, Dept. 34, 66 Grove Road, Eastbourne, and to save time, please post your order to this address. Please include enough for postage. Callers, however, should use one of the following addresses:

520 High Street North 42-46 Windmill Hill 266 London Road 29 Stroud Green Road 246 High Street  
Manor Park, E.12 Ruislip, Mdx. Croydon Finsbury Park, N.4 Harlesden, N.W.10

**VALVES SAME DAY SERVICE**  
NEW! TESTED! GUARANTEED!

<b>SETS</b>	1R5, 1S5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94 ..	Set 4 for 19/6
	DAF96, DF96, DK96, DL96	.. .. . 4 for 27/6
	6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 6Y3G .. .. .	.. .. . 5 for 24/6

1A7GT 11/8	6L19 12/-	30FL1 10/-	EBL21 13/6	EZ60 6/3	U50 6/-
1D5 8/-	6LD20 8/-	30L15 11/-	ECC40 15/-	EZ81 7/-	U52 4/6
1H5GT 10/-	6P1 13/6	30PL1 10/6	ECC81 5/-	KT33C 7/-	U78 4/9
1N5GT 10/-	6P25 9/-	35A5 14/-	ECC82 6/3	K741 11/6	U191 15/-
1R5 6/-	6V7G 8/-	35L3GT 9/-	ECC83 7/1	K745 5/9	U291 16/6
1S4 8/-	6Q7GT 9/6	35Z4GT 6/9	ECC84 8/9	K761 10/-	UABC80 7/6
1S5 5/3	6SL7GT 6/3	35Z5GT 8/6	ECC85 8/3	K763 6/6	UAF42 9/-
1T4 3/6	6SN7GT 4/9	50L3GT 8/9	ECP80 8/6	MU14 6/8	UB41 8/6
1U5 5/6	6U4GT 11/-	AC/TH1 16/9	ECP82 8/6	MX40 9/8	UBC41 7/9
3A5 9/-	6V6G 5/-	A231 9/6	ECH21 13/6	N16 7/-	UBF80 8/9
3Q4 7/-	6V8GT 6/6	B36 8/6	ECH55 6/3	PC95 10/-	UBF89 9/-
3S4 6/-	6X4 5/-	CL33 12/3	ECH42 8/9	PCC84 7/6	UCC84 13/3
3V4 7/-	6X5GT 5/-	DAC32 10/6	ECH81 8/-	PCC89 11/-	UCC85 7/6
5U4G 4/6	7B6 9/-	DAF91 5/3	ECL80 7/6	PCF80 7/9	UCF80 14/6
5V4G 8/-	7B7 7/6	DAF93 7/6	ECL82 9/6	PCF82 8/-	UCH21 13/6
5Y3GT 6/-	7C5 7/6	DCC90 9/-	EF39 7/6	PCF86 14/-	UCH42 8/-
5Z4G 7/9	7C8 7/6	DF33 10/-	EF40 12/6	PCL82 9/-	UCH81 8/-
6AL5 3/9	7H7 7/6	DF91 3/6	EF41 8/3	PCL83 11/6	UCL82 10/9
6AM6 3/6	7S7 9/-	DF96 7/6	EF42 10/6	PCL84 7/6	UCL83 13/3
6AQ5 6/-	7Y4 4/-	DF98 4/9	EF50 5/6	PL45 13/6	UF41 8/9
6AT6 6/9	10C2 17/6	DH77 6/9	EF85 9/9	PEN34 11/-	UF42 8/6
6BA6 6/-	10P13 14/6	DK32 11/6	EF86 9/9	PEN36C 8/-	UF85 6/6
6BE6 5/9	12AT6 7/-	DK91 6/-	EF89 7/6	PL36 11/6	UF89 8/-
6BH6 5/9	12AT7 5/-	DK92 7/6	EF91 3/6	PL81 9/6	UL41 3/-
6BJ6 5/9	12AU7 6/3	DK96 7/6	EF92 4/3	PL82 7/6	UL84 7/6
6BR7 12/6	12AX7 7/-	DL33 9/-	EL33 10/-	PL83 7/6	UR15 15/9
6BW6 8/-	12K7GT 5/3	DL35 9/6	EL41 9/6	PL84 10/-	URIC 7/-
6CD93 27/3	12K8GT 11/6	DL92 6/-	EL42 9/-	PY32 11/-	U06 13/6
6F1 12/6	12Q7GT 4/9	DL94 7/-	EL84 7/-	PY80 7/6	UY21 13/6
6F8G 8/6	12X7 7/6	EL96 7/6	EM34 8/6	PY81 8/6	UY41 6/6
6P13 11/-	14S7 19/6	EABC80 7/6	EM80 8/6	PY82 6/6	UY85 6/6
6P14 16/6	20F2 17/6	EAF42 8/6	EM81 8/6	PY83 7/9	VP4B 9/6
6K7G 2/6	20L1 17/6	EB91 3/9	EM94 10/-	T41 9/6	VP41 5/-
6K7GT 5/-	20P4 25/-	EBC30 5/-	Y51 7/6	U22 7/3	VP1921 16/6
6K8G 6/3	25AGG 9/-	EBC41 8/-	Y54 7/6	U24 17/6	W76 5/3
6K8GT 9/3	25L6GT 7/9	EBF80 6/3	EZ40 8/3	U26 13/-	W77 4/6
6L18 10/3	25Z4G 7/6	EBF89 8/9	EZ41 7/-	U28 10/-	Z77 3/6

**REBUILT TV TUBES**

FULLY GUARANTEED  
12 MONTHS  
Complete New Gun Fitted  
In Every Tube

12in. ....	£4.00
14-15in. ....	£4.10
17in. ....	£5.00
21in. ....	£7.00

Immediate Delivery. Carriage and Insurance 10/- extra.

ALLOWANCE ON OLD TUBE

**NU-GUN TELETUBES LTD.**

3 THE MEWS  
Duckett Road, Harringay,  
London, N.4  
Telephone: MOUnview 2903

**RES/CAP. BRIDGE 38/-**  
p. & p. 2/6

Checks all types of resistors, condensers  
6 RANGES

Built in 1 hour. Direct reading.  
READY CALIBRATED  
Stamp for details of this and other kits.

**RADIO MAIL (DEPT. RV)**  
Raleigh Mews, Raleigh Street, Nottingham

**READERS RADIO**

24, COLBERG PLACE, STAMFORD HILL,  
LONDON, N.16 STA. 4587

Post 6d. per valve extra.  
Any Parcel insured Against Damage in Transit 6d. extra  
Any C.O.D. Parcel 3/- extra.

# Underneath the Dipole

A MONTHLY  
COMMENTARY

By Iconos

**J**HERE are many different shades and varieties of comedy, from the robust traditional slapstick romps of the circus clowns to the delicate nuances of the high comedies of words and wit. And yet the widely contrasted comedy offerings of Groc, Charlie Cairoli, Dan Leno, Chaplin, Wilde, Marx Brothers and Noel Coward have a common denominator: a storyline of some kind, culminating in a tag which might be a smart or witty speech on the one hand or the squish of a custard pie on the other.

## Spike Milligan


When the BBC announced the reappearance of Spike Milligan on television they took the precaution of warning viewers by the title, "A Series of Unrelated Incidents at Current Market Value," that the traditional story background or continuity links would be missing. Even the comic incidents in this feature had no particular shape excepting when they were terminated by a well-aimed custard pie. Many excellent ideas, utilising the special effects facilities of the modern TV studio, were harnessed by the producer, G. B. Lupino, in this nightmarish Milligan production. The singing of a ballad by Spike Milligan in front of a most inappropriate film background (Hitler's troops goosestepping, etc.), the use of background slides and other technical tricks were brilliantly carried out. Goon shows are an acquired taste and I like to see them. But "A Series of Unrelated Incidents"—etc., was a little too unrelated for the tastes of most viewers and smacked rather of an end-of-term rag than of a professional presentation of unconventional twists of modern comedy or topical revue. Spike Milligan is a comic anarchist, unable to conform to the estab-

lished forms of the comic art, whose extraordinary sense of humour and gifted clowning are often ruined by his queer mumblings. A little more audibility and clarity of speech would be less wearing upon the ears of Milligan enthusiasts, especially those whose receiving sets are not very good for sound! It was significant that the biggest laughs in this show were scored by the impassive "straight man", Valentine Dyall, when receiving a custard pie squarely on the face!
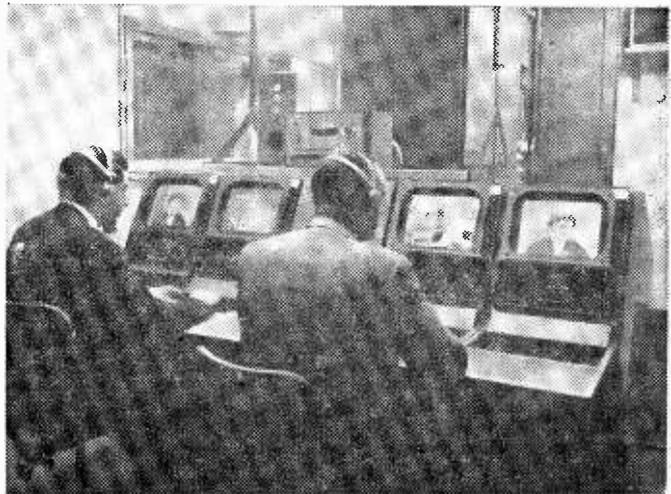
## Lighting

Just how important is the art or technique of lighting in television production? The final result depends upon how well the average receiver is adjusted, otherwise subtleties will be lost. Film studio lighting started from the all-glass daylight studios, progressed to mercury vapour tubes and enclosed violet-coloured carbon arcs, and later to

the tungsten bulb. Carbon arcs are still used, particularly for colour cinematography. Television studios started by making use of film studio types of tungsten lamps and housings. Several makers have competed in developing a wide range of lightweight spotlights, floods, skypans and so forth, apart from special effect lanterns capable of producing the hard shadow effects hitherto obtainable only with arc lamps. Carbon arcs are not normally used in TV studios, though fluorescent tubes, high-pressure mercury lamps and xenon arcs have received attention from time to time, with varying success. Mole Richardson, G.E.C. and Strand Electric are three British firms which are now making lamp-housings for the individual telescopic support (as used by Granada, TWW and Westward) or the tubular barrel support (as used at BBC's TV Centre, Riverside Studios and AR's Studio 5 at



The first of four Marconi Mark IV television cameras ordered by Independent Television News is now in use at the I.T.N. headquarters in London. By November all four cameras will be fully operational in a new studio which is being built on the seventh floor. This picture shows the I.T.N. control room, with the control desk for the cameras.

Wembley). The BBC had rather special lighting problems at Lime Grove Studios when several different types of camera were in use, each requiring its own particular key-light and filler-light intensities.

### Photogenic Faces

Lighting for television is not easy. The lighting man, who should preferably have had some experience of camera control units or racks together with some knowledge of portraiture, has a constant battle with directors, set designers, wardrobe, make up and even the casting department. Possibly the last mentioned—casting—is one of the most important factors. The faces have to be photogenic. The TV lighting man hasn't the time or facilities to give individual attention to each camera set-up, like the film studio cameraman. Once set for a show, his lamps are fixed for all scenes and shots, excepting for the measure of control afforded him by a dimmer-switchboard to vary the intensity of individual lamps. Actors with deep set eyes and overhanging eyebrows, large noses, wobbling Adam's apples and shady hats all present him with problems, mainly by creating ugly shadows. His lighting units are all overhead, for it must be remembered that the studio floor must be kept clear of all cables excepting those to the television cameras. Nevertheless, I feel that many of these unpleasant shadows could be softened, reduced or eliminated by the use of a small lamp fitted on top of the camera. One or two TV companies are already adopting this system, notably Southern Television. It certainly enables viewers to see the most important part of an actor (or actress)—the eyes.

### Horse Racing O.B.s

Ever since the first hazy long-shots of races at an Alexandra Park meeting were put out many years ago by the BBC, race meeting outside broadcasts have been one of the most popular items in the afternoon programmes. Competition between the BBC and ITV companies is pretty strong for covering the wide choice of courses and horses all over the country. The degree of expert handling of the number one camera (and especially of its zoom

lens) can make or mar these racing O.B.s, and the most skilled and experienced men are always allocated to these jobs. Some courses are technically well suited for television, with ready-made camera positions on the top of grandstands, commanding a view of the whole course. This gives great opportunities for the dramatic use of the new long focus zoom lens made by the two British firms of Watson and Taylor, Taylor, Hobson. Sandown Park, for instance, is an ideal course for television, with the sun in the right position, a ready-made camera platform and a handy parking place for the O.B. truck and the microwave link for sending the picture back to the network. At Epsom, complete coverage of the Derby requires the erection of a high tubular steel tower, sometimes shared with cinema newsreel cameramen. This naturally requires the hauling up of cameras and equipment on tackle, a hazardous operation on a windy day. Screen time actually devoted to racing is short, however, and producers, commentators and cameramen are busily occupied in capturing the atmosphere of the racecourse, from the Royal Enclosure to the silver ring, the paddock, the bookies and the tipsters—and in long discourses

by the commentator on the antecedents and the present form of the contestants for the next race. It is all good exciting television material, though not so continuous in entertainment value as spectacular equestrian jumping shows, such as the Horse of the Year and similar amateur events. A tremendous lot of preparatory work goes into O.B.s at race meetings, including the setting up and testing of several microwave "hops" for those race courses far removed from television centres. This can involve technical and production crews numbering anything from fifteen to forty people.

### Border Television

The opening of yet another ITV programme company, Border Television, at Carlisle, brings the commercial programmes to another 500,000 viewers and adds two more television studios to the long list. A recent survey made by a television equipment company revealed that there are now no less than ninety-three TV studio stages in Great Britain which are more than 500 square feet each in area. This figure, therefore, does not take into account the dozens of small announcers, presentation or continuity studios with fixed cameras.


## PRACTICAL WIRELESS

### Chief Contents of the November Issue (Including FREE 'Mini-Amp' blueprint)

Now on Sale 2/-

SHORT WAVE SECTION  
HIGH GAIN AMPLIFIER  
ELECTROLYTIC CAPACITORS  
A SIMPLE CONDENSER BRIDGE  
FAULTS IN VHF/F.M. RECEIVERS  
PRACTICAL WIRELESS 'MINI-AMP'  
A TRANSISTORISED VHF SUPERHET  
THE P.W. BEGINNERS S.W. TWO  
TRF UNITS AND INSTABILITY  
TRANSMITTING TOPICS  
CLUB NEWS  
ETC., ETC., ETC.

# More for less...

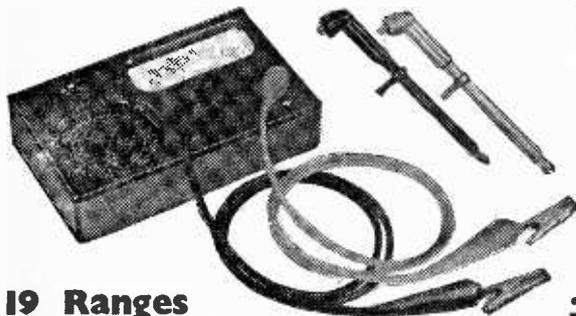

## 19 Ranges

<b>D.C. Voltage</b>	<b>A.C. Voltage</b>
0—100 mV.	0—10 V.
0—2.5 V.	0—25 V.
0—10 V.	0—100 V.
0—25 V.	0—250 V.
0—100 V.	0—1000 V.
0—250 V.	
0—1000 V.	
<b>D.C. Current</b>	
0—100µA	
0—1mA	
0—10mA	
0—100mA	
0—2mA	0—1A
<b>Resistance</b>	
0—20,000Ω	
0—2MΩ	

List Price: **£9:10s.**  
complete with Test Leads and Crocodile Clips.  
Leather case if required 39/-  
Size: 5½ x 3½ x 1½ in.  
Weight: 1 lb. approx.

MM12

Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multimeter is now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS. The Multimeter takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red coloured pointer and effectively damped movement facilitate easy and rapid reading. For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multimeter a great little meter.

**Use PRODCLIPS with the MULTIMINOR (Pat. No. 748811)**  
These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be. 15/- per pair.

# ...with the MULTIMINOR

Write now for illustrated literature to:—



**AVOCET HOUSE - 92-96 YAUXHALL BRIDGE ROAD**  
**LONDON - S.W.1** Victoria 3404 (12 lines)

**M** A Member of the Metal Industries Group of Companies

**ALL TUBES**  
Guaranteed 12 Months  
Carriage Free  
Speedy Passenger Train despatch.

**NEW**

12"	MW31-74 etc.	£5.5.0
17"	CRM 171, 172	£7.0.0



**COMPLETELY REPROCESSED**  
TO MAKERS' SPECIFICATIONS!  
REBUILT, RESCREENED, REALUMINISED TUBES OF  
THE HIGHEST QUALITY

14"	..	..	..	..	£5.5.0
15"—17"	..	..	..	..	£5.10.0
21"	..	..	..	..	£8.0.0

**ASTOUNDING BARGAIN!**

The "Clarion" Transistor Battery Tape Recorder. Push-button controls, 3¼ i.p.s. Portable. Durable plastic case. List price 25 gns. Complete with Mike and Tape.

**16** GNS. Carr. 7/6.



**TRADE ENQUIRIES INVITED**

## LINE OUTPUT TRANSFORMERS

Direct Réplacements for 500 sets.

Baird. T29, T163	..	..	53/-
T164, T167, T172, 2014, 1712	..	..	60/-
Bush. TV 11A, B, 12A, B; TVF 12A.	..	..	45/-
TUG12A, B; TRG 12A, B	..	..	80/-
TV12AM; TV22, 24; TRG24, TUG24	..	..	58/-
Cossor. 930, 931, 933, 934, 948, etc.	..	..	45/-
Elec. TS146; TS113-114; T161	..	..	60/-
T221, 231; TSC311, etc.	..	..	55/-
Ferguson. 841, 2, 3; 941 to 945	..	..	66/6
990T-998T; 103-145T; 203-246T	..	..	45/-
Ferranti. 14T3, 14T4, 17K3, 17T3-4, 1472, T1205, T1215, T1225, T1325, T1405, T1415, T1425, T1505, T1925	..	..	60/-
G.E.C. and H.M.V. mostly 55/- to	..	..	60/-
Invicta. T101-104; T108-110	..	..	40/-
T114-126; T133-142	..	..	60/-
Murphy. V114C, V116C, V118C	..	..	57/6
V120C, V180, V178, V200, V202C, V280, 250, 82/6; V214, 216	..	..	69/-
Philips. 114 UF/UM, 1115 U, 1437 U, 1446 U, 1726 U, 1746 U, 1747 U	..	..	80/-
383A, 463A, 563A, 663A	..	..	60/-
Pye. LV30, 16T, CS17, VT17	..	..	60/-
CTM4, V4, V14, V7, VT7	..	..	52/6
Ultra. 814, 815, 817, 915, 917, VW80, Y/YA730, YVW84, VVW720, V710	..	..	85/-
(complete assembly with C25)	..	..	14/53, 15/60, 17/50, 17/53, 17/60, 17/63-4, 17/70-1-2, 21/50, 21/60, 21/70-1-2
All Ultra Frame O.F.T.'s	..	..	60/-
.. Add post 2/6.	..	..	26/6

100 mixed resistors, 4W-2W—7/6 post 1s.  
**ANOTHER BARGAIN.** Complete set of 6 NEWMARKET High Gain Transistors and 1 Diode. Individually selected for max. gain and stability. Equiv. OC44, OC45(2), OC71, OC74 (matched pair) ONLY £2. Valves, Multimeters, Record Players, Tape Recorder Decks, see previous issues.

S.A.E. with enquiries please.  
**5 Westward Way**  
**Preston Road, Harrow, Middx.**

# WESTWAY RADIO

If you have ever wanted to  
write for radio or television  
here is the book to show you how . . .

# PROFITABLE SCRIPTWRITING for TV and RADIO



by  
Gale Pedrick

Gale Pedrick, the BBC's first Script Editor, has put all his vast knowledge and experience at the service of the would be television and radio script writer in this encouraging book. Much of the "know-how" he gives had to be learned the hard way but those who follow his advice and guidance on the techniques involved will soon acquire a solid background to this fascinating and important subject. The market for good scriptwriters is growing daily, particularly with the expansion of television—Gale Pedrick, a real professional, shows you how to meet this demand and make a profit.

208 pages

#### YES, IT CAN BE DONE

Sound Must Survive — The Elusive Idea

#### FIRST CATCH YOUR IDEA

Jack of All Trades — "Tunes of All Trades" — Meet the Rev. — These Radio Times — Overdraft — "Ballerina Story" — "Mad about the Boy" — "The Key of the Door" — "Ghost at my Elbow" — "Never Short of a Pound" — "By Royal Command", etc.

#### THE PLAY

B.B.C. — Associated Television — Associated Rediffusion — A.B.C. TV — Granada TV — Southern Television — T.W.W. — Anglia Television — The "Regions"

#### FASHIONS IN BROADCASTING

Length of a TV Play — Over-Writing — Type of Material — Characters and Sets — Use of Film — "Sound" Ideas — Those Breaks

#### THE AMERICAN INFLUENCE

A "Heavy" Industry — Jive v. Grand Hotel — Accent on America — Laughter or Clap Hands

#### THE WRITING OF COMEDY

Supply and Demand — The Jesters' Art — "That Man" — "Bootsie and Snudge" — The Geography of Wit — Pickles v. Wightman — The Humour of the Home — "The Larkins", etc.

#### COLLABORATION

Division of Labour — Philosophy of a Comic — Words by Frank and Denis — Writing to the Clock — Writing for Tony — Lyons in their Den — Monkhouse and Goodwin — Sykes at Large

#### ADAPTATION

Fiction by Instalments — Adapting for Sound — Fiction — and Fact

#### THE BROADCAST SHORT STORY

#### THE BROADCAST TALK

#### IT'S WORTH TEN PER CENT


#### SUMMING UP

Practical guidance by Gale Pedrick, the B.B.C.'s first  
Script Editor.

21s. FROM ALL BOOKSELLERS

... or, in case of difficulty, 22s. 3d. by post, from C. ARTHUR PEARSON LTD.,  
Tower House Southampton Street, London, W.C.2.

PEARSON

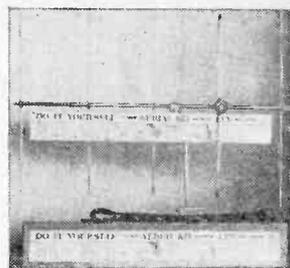

## DO IT YOURSELF AERIAL KIT

For all Band 3 Stations. Horizontal or Vertical Polarisation, fits either in Loft, on Window Frame, Chimney, Wall or Mast, up to 2in. dia. Complete with all fittings and 45 feet Co-Axial Cable with Plug, full illustrated instructions.

Price 59/6. Carr. paid.

ANDREW SLOSS

Ben Nevis Works, Stranraer.

## "TELFAC" Regunned TV Tubes

Supplied from stock and despatched per British Railways SAME DAY. COMPLETE NEW GUNS fitted in every tube and fully guaranteed for TWELVE MONTHS.

	Mullard	Mazda
12 in. ...	£4. 0. 0	£4. 10. 0
14 in. MW ...	£4. 10. 0	£5. 0. 0
14 in. AW ...	£5. 0. 0	£5. 0. 0
15 in. 2 Volt ...		£5. 10. 0
15 in. 12 Volt ...		£5. 0. 0
16 in. ...	£5. 10. 0	
17 in. MW ...	£5. 0. 0	£5. 0. 0
17 in. AW ...	£5. 10. 0	£5. 10. 0
21 in. MW ...	£6. 10. 0	£6. 10. 0
21 in. AW ...	£7. 0. 0	£7. 0. 0

MW = Magnetic Focus  
AW = Electrostatic Focus  
Plus 10/- for Carr. & Ins.

Other types not listed available. Please contact:—

**J. P. WRIGHT**

Television Factors

103 Carr House Road, Doncaster  
Sole Distribution Agent  
Phone: DON 2636

# Letters to the Editor

*The Editor does not necessarily agree with the opinions expressed by his correspondents.*

**SPECIAL NOTE:** Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

## RECEIVER ALIGNMENT

**SIR,**—I recently had to align a television set and would like to pass on a tip to any other reader who is not too familiar with this aspect but who may have to do such a job. The majority of modern sets are A.C./D.C. and the signal generator will probably be A.C. only. The connection of one of the generator padder leads to the chassis of the receiver will render this "live" so a really good condenser should be used in each of the leads from the terminating padder or outlet from the generator. To preserve a balance both condensers should be of the same value. Various false readings can be obtained by the omission of these condensers. I also found, incidentally, that the C.R. tube made a very much better alignment aid than the customary meter in the particular set under test, keeping a modulated signal on for vision alignment and adjusting brilliance to keep the lines on the tube just visible. In this way more accurate changes were observed than the movement of a meter needle in the video valve anode circuit. —G. H. BRANDON (Norfolk).

## CONTINENTAL BROADCASTS

**SIR,**—I wonder if any of your readers living on the coast could pass on any hints for the adjustment of a commercial set so as to enable me to pick up one or more of the Continental broadcasts. As the systems are different, and as I understand that many people pick up these transmissions (especially in the Folkestone area), I should like to try my hand with the unused channels on my set. I do not want to go to a

lot of trouble and alteration, and the stations may be out of range, but I should like to try and pick up one or more. I have managed to see a very weak picture on Channels 3 and 2 at various times, but not consistently. Probably the aerial is an important factor in the reception of signals on other channels than that for which the aerial and set are normally used, but there must be some way in which this could be adjusted.—F. T. WAITE (Hatfield).

[We hope to publish an article on this subject in the near future.—ED.]

## SERVICING TV RECEIVERS

**SIR,**—I follow very closely the series you run on the above, and would like to add a note which is not too often given in these articles. When a fault develops, it is nice to have such an article to refer to, but I would like to emphasise that the first thing to do is to check normal H.T. at all available points. (Not the EHT). One must, of course, have a service manual, but a check of H.T. will find the majority of faults, as these are nearly always caused by a faulty resistance or condenser, and the resultant change of current in the circuit will nearly always reveal itself by a change in an H.T. voltage.—P. SELWAY (N.W.5).

## AN INDUCTANCE TESTER

**SIR,**—Your recent article on a Capacity-Resistance bridge interested me greatly, but I have seen similar articles before in your pages. There is, however, one form of tester which is not often described and which I think would be found very acceptable by most amateurs. I refer to an inductance tester, which would measure inductance values. Correction chokes, etc., are often needed in TV, and a simple instrument which would enable one to check a home-made coil would be most valuable. I have been unable to find such an instrument in any of your back numbers, either wireless or television.—G. BLAKE (Perth).

## IMPROVING RECEIVERS WITH FRAME GRID VALVES

*(Continued from page 86)*

bypassed resistor. However, an attendant effect is a small loss in gm, and the stage as shown is operating with an effective or dynamic gm of about 6mA/V, although the gm of the valve is 7.4mA/V.

In Fig. 2 is shown that same stage altered for the best performance of an EF183. The cathode bias has been eliminated, and grid current bias has been adopted by increasing the grid resistor (R3 in Fig. 1) from 47k to 470k. The unbypassed cathode resistor has been reduced from 33Ω to 22Ω and slight alterations have been made to the screen and anode H.T. feed and decoupling arrangements.

### Screen Feed

The screen grid is now fed from a 33k resistor from the 190V H.T. line, while the anode is fed through a 100Ω resistor. The 0.0012μF screen

decoupling capacitor in conjunction with the 0.001μF anode decoupling capacitor and 100Ω anode feed resistor provides a degree of neutralisation.

In this arrangement, a small percentage of the I.F. signal is introduced into the grid circuit in the opposite phase from that introduced via the capacitance between the anode and grid one of the valve. The out of phase component is introduced via the capacitance between the screen grid and the control grid (grid one) of the valve by virtue of the decoupling components.

The stage as set up provides an effective gm better than 12mA/V, and thus in comparison with the circuit in Fig. 1 gives a two-to-one stage gain, which can be extremely useful if a service area type receiver is operating under fringe area conditions. ■

# metal rectifiers

(Continued from page 14 of the October issue)

One of the most popular applications of the point-contact diode is for sound or vision detector. Fig. 7 shows a typical vision detector circuit suitable for an I.F. around 30Mc/s. The diode should have a low forward resistance and a relatively high reverse resistance, which is typified in the Mullard OA70 or equivalent.

A sound detector circuit is very similar, but would normally use a load resistor in the region of 47,000Ω and a 30pF reservoir capacitor. The OA70 has an inverse resistance of 100k, while the OA71 has a value of 1M which, depending on the peak inverse voltage in the circuit, may be considered more suitable as sound detector with a higher load resistance.

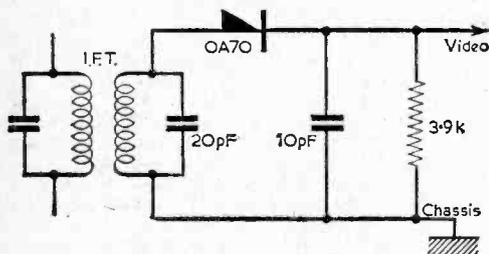


Fig. 7—A vision detector circuit, using a medium impedance diode.

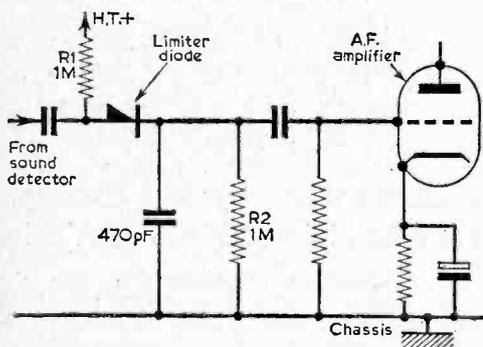


Fig. 8.—A germanium diode used in a sound noise limiter circuit.

## DETECTOR CIRCUITS

### Sound Noise Limiter

Germanium diodes are also extensively used in limiter circuits, a typical application being sound noise limiter in a circuit such as Fig. 8. The limiter diode should have a high reverse resistance, and the diode is held in its conducting region by resistors R1 and R2 across the H.T. supply. Under normal conditions, therefore, the diode, being in series with the A.F. signal, provides a path for the signals from the detector to the A.F. amplifier. The occurrence of impulse interference, such as produced by car ignition systems and domestic electrical appliances, drives the diode into its reverse current region where the high reverse resistance virtually open-circuits the signal path.

### AGC Applications

In television receivers especially, crystal diodes are often used not only to produce a negative bias for AGC but also to ensure that the AGC line does not go positive in the absence of a signal. This could happen in some circuits and the resulting positive bias could cause the controlled valves to exceed their anode current rating and thus reduce their life.

In Fig. 9 is shown a circuit of an AGC clamping diode; under normal conditions, forward current will flow through the rectifier and a negative voltage will appear at the junction of R1 and R2 of an amount governed by their values. The negative voltage from the AGC source will, of course, be added to the standing bias produced by the voltage drop across the diode.

(Continued on page 107)

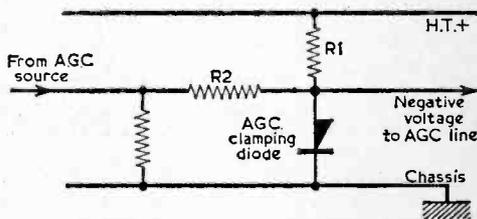


Fig. 9.—A diode clamping circuit which may also be used to provide AGC delay to one or more controlled stages.

# and crystal diodes

THE FUNCTIONS AND METHODS OF OPERATION  
OF THESE TWO COMPONENTS

By W. Faine

# LASKY'S RADIO

## GREAT TV OFFER

Don't neglect this final offer of well-known television products, all brand new, at clearance prices. Full data and instructions supplied. Call or post your order without delay.

### 90° 17 in. TV CHASSIS

Complete with 13 valves and latest Fireball turret covering all Bands I and III channels. Valves: 3 PCF80, PCC34, 3 6BW7, PCL84, PCL82, PY82, PL81, PY83, EY51. Overall dim: 8 x 15½ x 6in.

**LASKY'S PRICE £18.19.6**  
less C.R. Tube  
Carr. & Ins. 7/6.

Complete with new Brimar C175M 17in. tube, £23.19.6. Carr. & Ins. 19/6.

Above Chassis less valves, C.R. tube and Line Output Transformer, 77/6. Post 7/6.

### LASKY'S FOR NEW C.R. TUBES

All sizes in stock at lowest prices. 17in. from 79/6. Send for list.

**FERRANTI** 17in. type TR17/10. 6.3 v., 0.3 amp. heater. New and unused £6.16.6. Carr. & Ins., 12/6.

### REGUNNED C.R. TUBES

GUARANTEED FOR 12 MONTHS

Type	Carr. & Ins.
12in. round ...	£5 10 0
14in. rect. ....	£5 10 0
15in. & 16 round	£5 19 6
17in. rect. ....	£5 19 6
21in. rect. ....	£7 19 6

### MAKER'S SURPLUS COMPONENT BARGAINS

Wide Angle 38 m.m. Line E.H.T. Trans. Ferro-cube core, 9.16 kv.....	19/6
Scanning Coils, Low imp. line and frame .....	19/6
Ferro-cube cored Scanning Coils and Line Output Trans., 10-15 kv EY51 winding Line Trans. with width and linearity controls, circuit dia. pair .....	50/-
Frame Output Transformer..	6/6
Frame or line block osc. Transformer .....	4/6
Focus Magnets Ferro-core..	19/6
P.M. Focus Magnets, Iron-cored .....	12/6
Duomag Focallisers .....	15/-
300 m/a Smoothing Chokes..	10/6

### STANDARD 35 m.m.

Line Output Transformers 6.9 kv E.H.T. and 6.3 v. winding, Ferro-cube .....	17/6
Scanning Coils, Low imp. line and frame .....	7/6
Frame or line block osc. oscillator Transformer .....	4/6
Frame Output Transformer..	7/6
Focus Magnets: Without Vernier .....	9/6
With Vernier .....	12/6
200 m/a Smoothing Chokes..	7/6

### 110° SLIMLINE 17" TV CHASSIS

Complete with 14 valves and 12-channel turret covering all Bands I and III. Valves: 2 PY82, 2 PL81, EY52, 2 PCL82, 2 PCF80, PCL84, 3 6BW7, PCL89. Uses 17in. C.R. tube type C17A7. Overall dim.: 19 x 12 x 6in.

**LASKY'S PRICE 19 Gns.** Carr. & Ins. 7/6 less C.R. Tube

Complete with C.R. tube, £24.19.6. Carr. & Ins. 19/6.

Above Chassis less valves, C.R. tube and Line Output Transformer, 99/6. Carr. 7/6.

**C.R. TUBE** type C17A7, separately, £6.19.6. Carr. & Ins. 19/6.

Line Output Transformer with EY51, 29/6. Post 2/6.

**Sound & Vision Chassis.** Printed circuit, all components wired, complete with valves: 3 6BW7, PCL84, 2 PCL82, PCF80. Overall size 4 x 16 x 5in. (including valves), £5.19.6. Carr. 7/6. Less valves, 59/6. Carr. 5/-.

### PRESS BUTTON TURRET TUNER

Covers all channels Bands I and III also VHF/FM. I.F. 35-38 Mc/s. Operated by 5 press buttons. Complete with valves 30L15 and 30C15. Overall measures: 5 x 4½ x 2½in.

**LASKY'S PRICE 49/6** Post 2/6.

207 EDGWARE ROAD, LONDON, W.2.

PAAddinaton 3271/2.

33 TOTTENHAM COURT ROAD, W.1.

MUSEum 2605.

BOTH OPEN ALL DAY SAT. Early Closing, Thurs. Mail Orders to Dept. P.T., Edgware Road.

## RST

### MAIL ORDER DEPARTMENT

211 Streatham Road, Mitcham, Surrey

ALL VALVES LISTED ARE NEW STOCK & Terms C.W.O. or C.O.D. Postage 3d. per valve. MITCHAM 6201

AZ1 15/-	EF92 4/-	PCF82 7/-	UY35 7/-	6K8G 7/6
B65 8/6	EL42 10/-	PCL82 9/6	W1B 17/6	6K8GT 9/6
DAF91 7/6	EL90 8/6	PCL83 12/6	W81M 6/6	6L1 13/-
DAF96 8/9	EM80 8/6	PEN4A 17/6	W19 7/6	6L8G 7/6
DF91 4/-	EM81 8/6	PEN4VA 17/6	W27 7/6	6L18 10/-
DH719 6/-	EY81 10/-	PL36 15/-	X78 21/-	6L19 17/6
DK91 8/-	EY86 8/6	PL81 12/-	X79 21/-	6N7G/GT 6/6
EABC80 6/-	EY91 4/-	PL82 10/6	Z21 12/6	6SL7GT 6/6
EAF42 9/6	EZ35 6/-	PY80 7/6	Z21 12/6	6SN7GT 6/-
EB91 4/-	EZ40 7/-	PY81 7/6	Z77 4/-	6SNTGT 5/6
EC41 9/-	EZ41 7/-	PY82 7/6	Z77 4/-	6V6G 5/-
EBF90 8/6	EZ80 7/-	PY83 8/6	Z77 4/-	6X5GT 5/-
EBF99 8/6	EZ81 7/-	R10 10/-	Z77 4/-	7S7 10/-
ECC91 9/6	FC2 21/-	R19 19/-	Z77 4/-	7Y4 7/6
ECC33 5/-	FC4 15/-	TD4 12/6	Z77 4/-	8D3 4/-
ECC81 5/9	FC13 21/-	TP22 15/-	Z77 4/-	10LD11 15/-
ECC83 5/6	FC3C 21/-	U147 7/-	Z77 4/-	12AH8 9/-
ECC84 8/6	G232 10/6	U153 8/6	Z77 4/-	12AT6 7/6
ECC85 8/-	H30 5/-	U153 8/6	Z77 4/-	12AT7 5/-
ECF90 8/6	H63 9/-	UABC80 7/-	Z77 4/-	12A7 8/6
ECF82 8/6	HBC90 9/6	UF42 8/6	Z77 4/-	12AX7 7/6
ECH42 9/6	HL92 8/6	UBC41 8/6	Z77 4/-	12BA6 7/6
ECH81 8/6	HL133D 10/-	UBF80 8/6	Z77 4/-	12BE6 7/6
ECL30 9/-	KT33C 9/-	UCH42 9/6	Z77 4/-	12BH7 10/-
ECL82 9/6	KT86 15/-	UCH42 9/6	Z77 4/-	12J7G/GT 8/6
EF37A 8/-	LZ319 12/6	UCH81 8/-	Z77 4/-	12K7GT 5/-
EF40 15/-	MKT45 (or 7) 17/6	UCH83 8/-	Z77 4/-	12K3GT 10/-
EF41 8/-	ML4 8/6	UF41 7/6	Z77 4/-	12Q7 8/6
EF42 10/-	MSP4 17/6	UF89 6/6	Z77 4/-	12Q7GT 8/6
EF50(A) 4/-	MU14 9/-	UL41 8/6	Z77 4/-	35Z4GT 8/6
EF80 4/-	N142 9/6	UL84 7/-	Z77 4/-	50L6GT 9/-
EF85 5/-	N153 10/-	UY41 7/6	Z77 4/-	
EF86 10/6	PCC84 9/-		Z77 4/-	
EF89 9/-	PCF80 9/6		Z77 4/-	
EF91 4/-			Z77 4/-	

### SEND FOR LISTS.

Quotations given for any types not listed. Obsolete and old types a speciality.

### VACUUM ELECTRONIC LIMITED

## KEEPS YOU IN THE PICTURE

WITH THE FINEST REBUILT CATHODE RAY TUBES

12 MONTHS GUARANTEE

12"-14" £4-15-0  
15"-17" £5-5-0  
21" £7-15-0

**15/-**

CASH WITH ORDER OR PRO FORMA, ADD 12/6 FOR CARRIAGE AND INSURANCE.  
DELIVERY FREE IN LONDON AREA

ALLOWED ON RECEIPT OF OLD TUBE

WRITE PHONE OR CALL

### VACUUM ELECTRONIC LTD.

35, SACKVILLE STREET LONDON, W.1  
REGENT 6404

# » TUBES 15' - «

MULLARD, Etc.

**15"** EX-RENTAL SERVICE STOCK **12"**  
IDEAL FOR SPARES. Carriage 5/-

**14"** EX-RENTAL REPLACEMENT STOCK **35' -**  
Carriage 5/-



## TV CHASSIS 5/6

Plessey, less valve and tube. Circuit Inc. Ins. and Carr. 7/6. Salvage. Badly Stored.

## 12/6 SOLO SOLDERING TOOL

110 v., 6 v. or 12 v. (special adaptor for 200/250 v., 10/- extra). Automatic solder feed including reel solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Cannot burn. Full instructions for use. Post 4/-.



In light metal case with



## SPEAKERS

5 inch—6 inch—8 inch—7 x 4 inch. Ex. manufacturers salvage. P. & P. 2/9.

# 8/9

## Valves, 9d. VALVES Salvage Guaranteed.

C2C	EB91	VR35	VR137	6D2
CV66	EF50	VR51	VR201	9D2
D1	HL42DD	VR106	6AL5	12Y4
D152	PM202	VR107	4D1	15D2
EA50	SP61	VR109	6D1	78

1/9d.	2/9d.	5/9d.
D77	B36	EBC33
DH77	ECC31	EBF80
EB41	ECC34	ECL80
EF91	ECC81	EL33
NI42	ECC82	EL38
PEN46	EF80	EL41
W148	EF92	6Y80
Z77	EL32	6Y81
6F1	EY51	6Y82
6F12	KT36	PZ30
6F13	KTW61	6XN7
6F14	L63	LN309
6F15	N37	LZ319
6K7	PL33	N152
6P25	TH233	N309
		N339
		PCC84
		PCF80
		PCF82
		PL38
		PL81
		PL82
		PL83
		PL84
		PL85
		PL86
		PL87
		PL88
		PL89
		PL90
		PL91
		PL92
		PL93
		PL94
		PL95
		PL96
		PL97
		PL98
		PL99
		PL00

Post 1—7d. 6—1/6. 12—2/6.

★—★—★—★—★—★—★—★—★—★

**PP** MAIL ORDER ONLY  
**COMPONENTS LTD.**  
819 ILFORD LANE, ILFORD, ESSEX  
Stamp for FREE Catalogue



## OUTSTANDING OFFER!

While stocks last

## GUARANTEED REBUILT CATHODE RAY TUBES

12" & 14". Types MW 31—74 : MW 36—24 : SE 14—70 : 4/14 : C 14 FM

# 59/6

each Carriage Paid CASH WITH ORDER

Your old tube not required.

## TATES ELECTRONIC SERVICES LTD

3 Waterloo Road, Stockport, Cheshire. Tel. : Sto. 7301.

*If you are a 'practical' television engineer you'll appreciate this book—*

# TELEVISION PRINCIPLES and PRACTICE

by **F. J. Camm**

A fully-illustrated, authoritative and up-to-the-minute work on the underlying principles of television


transmission and reception, covering *The BBC Television System—The Television Camera—From Transmitter to Receiver—Projection Receivers—Stereoscopic and Colour Television—Time Bases—D.C. Receivers—Aerials—A London-Birmingham Converter—Servicing—Interference—A Pattern Generator—Choosing a Receiver—The Beverage Report—Dictionary of Television Terms.*

2nd edition. 216 pages. 144 illustrations.

25s. FROM ALL BOOKSELLERS

(26s by post)

NEWNES

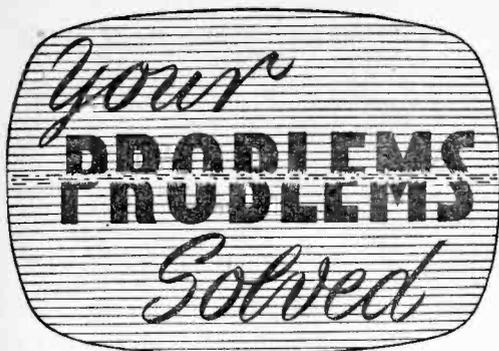

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from page 107 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

#### MURPHY VU210C

When first switched on, the picture is enlarged and out of focus. After it has been working for ten minutes or so, the picture is normal, and stays normal, except that black parts of the picture are not as black as before. The EHT rectifier is an EY51, but I am told that it should be a U25.—F. C. Bennett (Edgware).

The basic symptoms indicate a faulty C.R. tube, but may be due to other causes. The EHT rectifier is given as a U25, but some replacement line output transformers are fitted with an EY51. The correct valve type is usually stamped on the black bakelite, near to or below the valve.

#### SOBELL T274T

The height decreased and I remedied this by wiring another resistor of the same value across the one in series with the height control; but, a few days later, the picture started to roll, sometimes up, sometimes down, and now I have to adjust the frame hold every few minutes. I have checked the ECL80's by substitution with no improvement.—J. Wilson (Newport).

If the ECL80 valves are in order, check the 0.01 $\mu$ F capacitors wired around the frame sync separator/sync gate ECL80; particularly the one from pin 1 to pin 2 of the oscillator ECL80. Check resistors if necessary, but usually if the valves are in order, one of the capacitors is o.c.

#### ULTRA 84L

I wish to change the old tube for a new one. How do I proceed?—A. S. Deadman (Eastbourne).

If the chassis is removed from the cabinet it is only necessary to remove the EHT cap from the side of the tube, release the front clamping band and slacken the rubber-lined clamp on the neck of the tube. Remove the base socket and ease the tube forward taking all the weight at the front, carefully withdrawing the neck through the focus magnet clamp at the same time supporting the scanning coils so as to impose no strain. Reverse this procedure when fitting the new tube.

#### GEC BT6145

The picture is poor and there is no horizontal hold. The voltage setting has to be at 210V instead of 230V to obtain a picture. I have changed the metal rectifier (RM4) with no effect.—D. J. Williams (Port Talbot).

Probably V14—L63—is intermittent, but also suspect the KT36, U25 and U239. The heater transformer may have developed a fault, giving low output.

#### PORTADYNE 517

The lines on the screen are much wider at the top of the picture than at the bottom, and this is distorting the picture for about 2in. from the top.—A. Stokes (Edmonton).

You should change the 100 $\mu$ F (25VW) condenser wired from pin 3 of the frame output ECL80 to chassis.

#### DECCA DM3/C

There is a 3in. black margin down each side of the screen. The width control does not remedy the defect but just brightens and dims the picture. The brightness control enlarges the picture. I have changed valves and condensers but have not found any fault. I do not have a meter—only a service sheet. The picture is also out of focus.—R. Andrews (Creggan).

You do not say which valves you have changed. Two versions of the DM3/C are in current use. That version which uses serial numbers up to 50,000 employs a chassis similar to the DM2/C and DM4/C, but if the serial number is over 50,000, a revised chassis is fitted using PCL82 and ECC82 valves in the timebase and sound sections. You should check the PL81 valve and the resistor to pin 8 of this valve. Early versions used a 4.4k 2W, later versions a 2.7k 2W resistor in this position.

#### AMBASSADOR TV2

This is a 12in. table set, BBC only. The set has gone completely dead. On switching on, one fuse blows and there is a blue flash in the V801 valve.—T. Allen (West Bromwich).

You should replace the V801 valve and check each of the four 47 $\Omega$  resistors to the valve base.

#### VIDOR CN4225

The picture is of very poor quality and, on advancing the brightness, the picture goes grey in colour and expanded vertically. I replaced valves SU61 and PY81. My picture is now very good as to detail etc. but I cannot obtain full width on advancing the control to maximum. It is approximately 1in. short on either side. The focus lever is over to maximum on one side also. I do not have a service sheet or any instruments to make tests. This set is BBC only and is fitted with a convertor.—J. Collins (Heckmondwike).

You should check the PL81 valve and the resistors etc.; associated with it. These are 1.5k to pin 8, 100 $\Omega$  to pin 3 and 50 $\mu$ F capacitor across it. Check 1.2M resistor to pin 1 of the ECL80 valve base if necessary.

**McMICHAEL TM54F**

On switching on the set there is very low sound and no picture, although the raster is there. After waiting a few minutes and then switching the set on and off several times the sound comes up to its normal level and the picture comes on with a lot of noise through the speaker and interference on the screen. I have changed the PCF80's the PCC84, and also the PY81. Once the picture is on, it will stay until being switched off again. The picture quality is good.—G. Cooper (Rotherham).

The trouble appears to be in the tuner unit and the connections should be checked. The suspect resistor is the 6.8k 1W to pin 1 of the PCF80 valve base (first spring contact).

**PHILCO 1019**

I would like to receive Midlands ITV from Birmingham on this set. I do not think I could receive a picture, but surely I may receive the sound if I alter the coils on channel 8 of my turret tuner. Could you please advise me on the coil to put in and any minor alteration. I can receive Granada ITV but should also like to receive Birmingham. Is this possible?—A. Burns (Liverpool 17).

To receive the Midlands ITV transmission you should have an aerial directed suitably and if necessary retrim the channel 8 oscillator coil core. No alterations are necessary.

**INVICTA 138**

When the set is switched on, the sound is fine and the picture eventually appears but only fills the screen from the top to half way down. The picture gradually fills up but leaves a 2½in. black band along the bottom. Altering the controls, or adjusting the ion trap or picture shift, will not fill the screen.—M. Kemp (Birmingham).

You should replace the rear right side PCL82 frame output valve. If necessary check the 330Ω bias resistor which is to the left of the valve and further to the front (as viewed from the rear).

**G.E.C. BT.5144**

I have recently moved from London to Bristol and wish to know the procedure for altering this set to receive the local BBC programmes. I do not have a service sheet to follow.—L. Godding (Bristol).

This set is a single sideband TRF made only for receiving London or Midlands stations. To receive any other channel a complete change of coils would be necessary and then re-alignment.

**COSSOR 938**

A few weeks ago the picture began to fade and at present it is a dull grey. No amount of adjustment of the brightness and contrast has any effect. It takes about 15 minutes for even a very faint picture to show.—H. Dunn (Leeds 7).

If the faint picture is full size and in focus, the cathode ray tube is at fault. It may possibly have an open-circuit cathode, but the ion trap magnet around the tube neck should be checked first of all as it may have slipped. If the picture is defocused and lacks width, suspect the 21A6 line output valve and its associated circuits.

**MARCONIPHONE VT150**

The trouble with the above set is that the picture continues to slip with a jump unless the height control is reduced until the picture is at least 1½in. from the bottom of the screen. Adjusting the other controls does not stop this.—W. Coleman (Co. Durham).

There is a 1.5M resistor (brown, green, green) wired from the hold control to the black lead connection of the oscillator transformer. It is one of a group of three resistors between the 0.022μF capacitors under the chassis near one of the U154 (PY82) valve bases. Check by substitution.

**FERGUSON 991T**

Can a K.B. adaptor, serial number 27485, be fitted to the above set or a Pye V4—W. Smith (Umberleigh).

Only the type D K.B. adaptor is suitable for use with the V4 or 991T. This adaptor uses series heated PCC84 (6AN7) and PCF80 (PLF82-8A8 or 9U8) valves.

**H.M.V. 2806**

I am unable to purchase a circuit diagram for this set and it has developed the following fault. A new tube has been fitted as the old one had an o.c. heater. Now, all I can obtain is a very fine vertical line and other lines across the screen but nothing else at all. I have changed the line output valve with no success.—C. Fisk (Eye).

The 1806 uses a similar chassis to the H.M.V. 1805 and 1851. Marconi models VT52A, VC52A, VRC52 etc. You should check the line oscillator valve next to the KT44 (or KT45) which is a Z66 and the line blanking oscillator transformer which is associated with the Z66. If the transformer is at fault, no H.T. will be applied to pin 4 of the Z66 valve base. If the line output transformer is at fault no H.T. will be applied to the top cap of the KT44 (KT45).

**REGENTONE BIG 12**

The screen will not light up although the tube heater does. The sound is perfect. I have replaced the EL80 valve, also the condenser between line output transformer and final anode on the tube. Also, I replaced the EY51 with a new one and this does not light up.—J. Howard (Manchester 11).

We presume the valve referred to as EL80 is actually the EL38 and that this has been changed. You should check the resistor to pin 4 of this valve base (6.8k wire-wound) and the continuity of the controls (line hold and linearity). It would then appear to be necessary to change the line output transformer.

**SOBELL PORTABLE TPS180**

The above set has been in use for approximately 12 months. During the last few weeks, the tuning position for both BBC and ITV have slowly crept upwards on the tuning scale until it is now only just possible to tune in the BBC when the pointer is at the very top of the scale. I have checked that this trouble is not caused by the pointer changing

(Continued on page 107)

# D. & B. TELEVISION

Phone: Cherrywood 3855

131 & 131a KINGSTON ROAD,  
SOUTH WIMBLEDON, LONDON S.W.19

FOR THE FINEST, FASTEST SERVICE IN THE COUNTRY. We are Open from 10 a.m. Until Midnight. For any information or problems you have Call or Phone, we are always pleased to help.

**NEW!** SEND FOR OUR COMPREHENSIVE L.O.P.T. SCAN COIL L.B.O., F.O.P.T. LIST Prices of nearly all makes and models, 2/6, post 7d. Invaluable as a service list. The finest list ever compiled. Special quotations for the trade.

### TRANSISTORS

Genuine Mullard Transistors in sets of Six: 1. OC44; 2. OC45; 1. OC81D; 2. OC81's in matched pair. Including OA81. Diode, for ONLY £2.2.6.  
Genuine G.E.C. Transistors in Sets of Six: 1. GET874; 2. GET875; 1. GET114; 2. GET114's in matched pair; plus 1. GEX34 for ONLY £1.18.6.

### SINGLE TRANSISTORS PRICE LIST

Mullard: OC44. 10/-; OC45. 9/-; OC70. 6/-; OC71. 6/-; \*OC72. 7/-; OC76. 7/-; OC78. 7/-; \*OC81. 7/-; OC81D. 6/-.  
G.E.C.: GET874. 9/-; \*GET875. 8/6; \*GET114. 5/9.

Available in matched pairs at 1/- extra.

Mullard Diodes: OA70. 2/9; OA79. 2/9; OA81. 2/9; OA91. 3/6. G.E.C.: GEX34. 3/3.

All above are genuine manufacturers new 1st grade.

### SURPLUS TRANSISTORS

Red Spot. A.F. OC71 and 72. Equivalent .. .. 4/3 each  
White Spot. R.F. OC44 and 45. Equivalent .. .. 5/- each  
Diodes, general purpose .. .. 1/- each  
Various other types in stock. Please ask for prices of types not listed.

TURRET TUNERS. Various Makes: 10, 16, 38 Mc/s. 40/-.

### EXAMPLE OF TRANSFORMER LIST

FERGUSON:		L.O.T.		SCAN COILS	
10T. 10T	.. .. .	(New)	(Used)	(New)	(Used)
992/4/6/8	.. .. .	69/9	35/-	60/-	35/-
PYE:	.. .. .	(New)	(Used)	(New)	(Used)
V4. V74. V7	.. .. .	52/6	35/-	55/-	35/-
V77. CTM4	.. .. .	52/6	35/-	55/-	35/-
MURPHY:	.. .. .	(New)	(Used)	(Used only)	
V214. V240. V250	.. .. .	60/6	35/-	45/-	
EKCO:	.. .. .	(New)	(Used)	(New)	(Used)
221. 283	.. .. .	47/3	30/-	40/6	27/6
231. 284. 293	.. .. .	54/6	35/-	40/6	27/6

### REGUNNED CATHODE RAY TUBES

all with 12-month Guarantee

ALL MAKES: 12in. £3.15.0; 14in. £4.5.0; 17in. £4.15.0.  
ADD: 10s. for 90° tubes; 15/- for 110° tubes; 5/- for Electrostatic types.  
SECONDS, with 12-month Guarantee—ALL MAKES: 12in., £2.15.0; 14in. £3.5.0 (when available); 17in., £3.15.0.  
SECONDS, No Guarantee—ALL MAKES: 12in., £1.5.0; 14in., £1.15.0 (when available); 17in., £2.15.0.  
NOT APPLICABLE TO NO GUARANTEE SECONDS: 10/- allowance on old tube if in good condition.

### THE FABULOUS R.T.D. TRANSISTOR SIX

LATEST ON THE KIT MARKET

Spec.: Six transistor plus diode, printed circuit, superhet, ferrite rod aerial. Automatic gain control to stop overloading. Output 450mW in push pull. All components brand new and guaranteed. Neat, small, two-tone grey cabinet. Two radios in one portable and car radio. Incorporates car aerial input socket. Everything to build this superb transistor radio. Only £8.9.6.

## VALVES—GUARANTEED 90 DAYS

AZ31	8/6	ECL80	6/9	PC1.82	10/9	U31	9/6	8P41	2/3	10F1	4/6
B36	5/6	EF39	5/-	PC1.83	11/3	U90	8/6	8P61	2/3	10C1	10/-
D77	3/-	EF50	3/9	PC1.84	9/6	U93	7/-	W77	5/-	10C2	13/-
DH77	4/6	EF80	4/6	PL33	8/9	U91	9/-	Z77	3/-	10P13	9/-
DK91	6/9	EF91	3/-	PL36	10/9	U281	9/-	5U4	6/-	10P14	9/-
DK92	6/-	EF92	5/-	PL38	14/6	U389	20/-	5Y4	9/-	12A7	5/6
DK96	7/6	EL33	8/6	PL81	8/9	U301	20/-	5Y3	10/6	12AU7	5/6
DL92	5/9	EL38	14/6	PL82	8/9	U801	22/6	5Z4	10/-	20D1	8/9
DL94	6/9	EL84	7/-	PL83	7/-	UAF42	8/-	6AL5	3/-	20P2	9/-
DL96	7/6	EY518E	6/-	PY31	7/-	UFC41	7/9	6AM6	3/-	20L1	12/6
EB91	3/-	EY91	7/9	PY32	10/-	UCH42	7/-	6CD6	27/6	20P1	10/6
ERC33	5/-	EY86	7/9	PY80	6/6	UF41	8/6	6D2	3/-	20P3	12/-
EFB90	9/6	EZ40	6/-	PY81	6/-	UF42	3/9	6F1	5/-	20P4	16/6
ECC81	5/3	KT3C	6/-	PY82	6/6	UL41	7/3	6P12	3/-	278U	14/-
ECC82	5/9	KT36	8/6	PZ30	30/-	UL46	7/9	6P13	7/-	30C1	17/-
ECC94	8/-	KT66	15/-	U22	9/6	UL44	11/8	6P14	9/6	30C1	17/-
ECF80	8/-	PCC84	7/-	U24	10/-	UY41	6/6	6P15	9/6	30L1	7/-
ECH35	9/-	PCC89	8/6	U25	12/-	U98	14/6	6L1	12/6	30P4	10/9
ECH81	6/-	PCF80	7/-	U36	12/-	U99	6/6	6V6	5/-	188BT	14/-

These are only examples of our valves: if you do not see what you require send stamped addressed envelope for special quotation.

We pride ourselves that we can obtain and supply any TV spare OUR GIGANTIC STOCKS INCLUDE: Line Output, Frame Output, Sound Output, Line and Frame Blocking, Osc. Trans. and Scan Coils for any make or model Television. Please ask us for ANY components you require we are almost certain to have them.

TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra. Postage on Valves, 6d. each. C.R.T.s 12/6 inc. Insurance. SATISFACTION ASSURED. RETURN POST SERVICE.


# RADIO BARGAINS
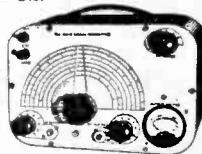
## SIGNAL GENERATOR



£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 x 6 x 5 1/2 in. grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 800 milli-volts. O.W. and mod. switch indicator. Accuracy plus or minus 2%.


variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.  
Cash £4.18.6 or 25/- deposit and 4 monthly payments of 21/6. P. & P. 5/- extra and Packing 5/-. Coverage 120 Kc/s-84 Mc/s. Metal case 10 x 6 1/2 x 4 1/2 in. Size of scale 6 1/2 x 3 1/2 in. 2 valves and rectifier. A.C. mains 230-250 v. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 100 milli-volts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.


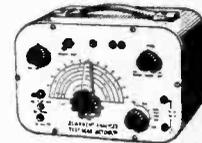
## ALIGNMENT ANALYSER


TYPE MC12

A.C. mains 200/250 v. Provides: Wobbulator. (Sweep Frequency Operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s-80 Mc/s. Capacitance Measurement. Two ranges provided 0-50pF and 0-12pF. Special Facility enables true resonant frequency of any tuned oct. I.F. transformer, etc. to be rapidly determined. Cash price £6.19.6 plus 5/- P. & P. terms 25/- deposit, plus 5/- P. & P. and six monthly payments of 21/6.


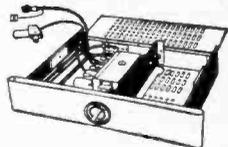
## CHANNEL TUNER

Will tune to all Band 1 and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.P. 80 valves (in series). I.F. 16.19 or 33.38. Also can be modified as an aerial converter (instructions supplied). Complete with knobs. 32/6 plus 3/6 P. & P.



HEATER TRANSFORMER To suit the above. 200-250 v. 6/-, plus 1/6 P. & P.

## LINE E.H.T. TRANSFORMERS

With built-in line and width control, 14kV. Scan coil, 50in. deflection on ferrite yokes. Frame O.P. transformer pl. 18 kV smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.

29/6 Plus 4/- P. & P.  
As above, but for 625 lines. £2.10.0, plus 4/- P. & P.

Focus Magnet suitable for the above (state tube). 10/- plus 2/6 P. & P.

## A.C./D.C. POCKET MULTIMETER KIT

2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamperes. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Millamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wirewound pot (for ohms zero setting), toggle switch resistor and rectifier, 19/6. P. & P. 1/6. Wiring diagram 1/-. free with kit.


## RADIO & T.V. COMPONENTS (Acton) LTD.

23c HIGH STREET, ACTON, LONDON, W.3

All enquiries S.A.E. Goods Not Despatched Outside U.K.

# LAWSON

## DIRECT REPLACEMENT Reprocessed TUBES

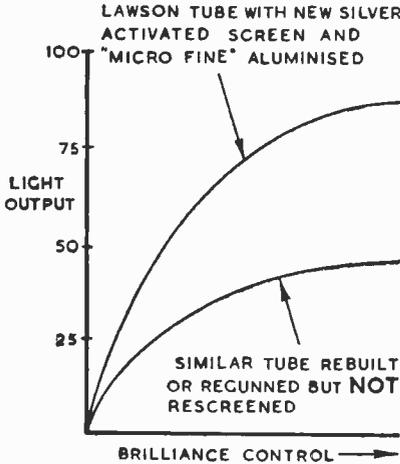

12 MONTHS **FULL REPLACE-  
MENT GUARANTEE**

**ENGINEERS WITH  
EXPERIENCE**

Know that as a tube gets old, not only does it become Low emission but the light efficiency of the Phosphor Screen also deteriorates (up to 10% per year). This deterioration of the Screen obviously continues if the tube is only rebuilt or regunned.

Don't risk a "DEAD SCREEN", enjoy the brilliant crisp high definition of a LAWSON TUBE. Tubes which are absolutely BRAND NEW throughout (excepting the glass), and which incorporate the very latest CRT developments. New silver activated screens, "micro fine" aluminising, high efficiency gettering, plus Brand New electron guns by Britain's premier manufacturers, Mullard, Mazda, Emscope, Cossor, Brimar, Emitron, English Electric, etc.

**ALL MAKES AND TYPES FROM STOCK**

LAWSON. The ONLY replacement tubes, for which all types are guaranteed, correct and direct plug-in replacements.

**12" - £4.10.0**

**14" - £5.5.0**

**15-17" - £5.15.0**

CARR. and INS. 7/6

C.O.D. or C.W.O.

**10'**

Gladly refunded if you wish to return your old tube (excepting 12")

**EXPRESS PASSENGER SERVICE—**  
Orders received by 3 p.m. are dispatched same day.  
Special direct services to Scotland and Ireland.  
**TRADE AND QUANTITY DISCOUNTS**

**LAWSON TUBES LTD.**

156. PICKERSLEIGH RD. MALVERN. Worcs.  
TEL. 3798

### Just Published

## RADIO CONTROL MANUAL

by E. L. Safford Jr.

25/- Postage 1/-

TRANSISTORS, Gernsback Lib. 16/- Postage 9d.

NEW SHORTCUTS TO TV SERVICING, 2 vols. 25/- each. By L. C. Lane. Postage 1/-.

TELEVISION EXPLAINED, by W. E. Miller. 12/6. Postage 1/-.

BASIC ELECTRONICS, by Van Y. Nooger and Neville. Set of 6 vols. £3.6.0 com. Postage 1/-.

ELEMENTARY TELECOMMUNICATIONS EXAMINATION GUIDE, by W. T. Perkins. 17/6. Postage 9d.

PRACTICAL AUTO RADIO. Servicing and Installation, by J. Greenfield. 23/- Postage 9d.

VALVE & TELETYPE MANUAL No. 9, by Brimar. 6/- Postage 9d.

RADIO VALVE DATA. Compiled by "WV". 6/-, 7th Ed. Postage 9d.

COMPLETE CATALOGUE, 1/-.


## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET LONDON, W.2

Phone: PADdington 4185  
Open 6 days 9-6 p.m.

## 'CAPRI' ALL TRANSISTOR RADIO

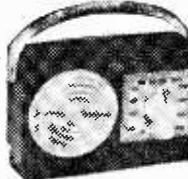

All Transistor Radio with carrying case.  
Miniature loud-speaker design. Covers all medium waves. Very reliable. Works for months off 8d. battery. Can be assembled in an hour or two using our simple as ABC pictorial open out-step-by-step plans. Complete set of parts including miniature speaker - everything - only 27/6 plus 2/- P/P (C.O.D. extra). Parts can be bought separately. Demonstrations Daily - Money back guarantee. Send now.

## CONCORD ELECTRONICS (Dept. PT6), 210 Church Rd., Hove, Sussex

## ALUMINIUM, LIGHT ALLOYS BRASS, COPPER, BRONZE

IN ROD, BAR, SHEET, TUBE, STRIP  
WIRE, ANGLE, CHANNEL, TEE

3,000 STANDARD STOCK SIZES

**H. ROLLET & CO. LTD.**  
6 CHESHAM PLACE, LONDON, S.W.1  
BELGRAVIA 4300

Works:  
36 ROSEBERY AVE., LONDON, E.C.1

Branches at Liverpool, Manchester, Birmingham, Leeds.

No Quantity too small

## NEW VALVES!

Guaranteed Set Tested

### 24-HOUR SERVICE

1R5, 1S5, 1T4, 3E4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6.  
DAF96, DF96, DK96, DL96, SET of 4 26/-.

1D5	7/-	DL92	5/11	PCF80	7/9
1R5	6/-	DL94	6/9	PCF82	7/6
1S5	4/6	DL96	6/9	PCF82	8/3
1T4	3/6	EB81	3/-	PCL83	13/6
3E4	5/11	EBCA1	7/6	PCL84	7/6
3V4	6/9	EBF90	7/9	PL36	10/9
5U4G	4/3	EBL21	12/6	PL81	8/6
5Y3GT	5/6	ECC40	14/6	PL82	6/6
6Z4G	7/3	ECC81	4/9	PL83	6/6
6AM6	2/9	ECC82	5/9	PL84	8/6
6K7G	1/9	ECC83	6/3	PY32	11/-
6K9G	4/9	ECC84	8/-	PY80	7/-
6Q7G	5/6	ECC85	7/9	PY81	7/-
6V6G	4/9	ECP90	3/3	PY82	6/-
6V8GT	6/6	ECP82	8/3	PY83	7/3
6X5GT	4/9	ECH21	12/6	U25	12/-
12K7GT	4/9	ECH42	7/9	UA8C80	7/6
12K8GT	11/-	ECL90	8/9	UAF42	8/6
12Q7GT	4/9	EF40	12/3	UBC41	7/-
35L8GT	8/6	EF41	8/9	UBF38	8/6
35Z4GT	5/9	EF80	4/9	UC85	7/-
AZ31	8/9	EF85	5/-	UCH21	12/6
CL33	11/9	EF86	8/9	UCH42	7/6
DAC82	9/6	EF89	6/9	UCH61	8/-
DAF91	4/6	EF91	8/9	UC82	10/-
DAF96	6/9	EL41	9/-	UCF83	13/-
DF33	9/6	EL84	6/3	UF41	7/9
DF91	3/3	EY31	7/3	UF85	8/-
DF96	6/9	EY83	7/6	UF89	7/9
DH77	6/-	EZ40	6/9	UL41	7/-
DK32	11/-	EZ41	6/9	UL84	7/-
DK81	8/-	EZ80	5/9	UY21	13/-
DK92	7/3	EZ81	6/6	UY41	5/6
DK96	6/9	MU14	8/-	UY85	6/3
DL83	8/6	PCC84	6/9	VP4B	8/6
DL35	9/6	PCC89	10/-	Z77	2/9

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra Any C.O.D. Parcel 3/- extra. Office address, no callers.

### GERALD BERNARD

(Note new address—formerly of Leeds)  
83 OSBALDESTON ROAD,  
STOKE NEWINGTON, LONDON, N.16

(Continued from page 104)

its position on the cord connecting it with the tuning condenser pulley, but the original position on the scale can almost be regained if the screening-can of the PCF80 valve is pressed downwards so that it is not centrally situated on the valve. just below and to the right of the same valve is a long brass screw with a square head and I have tried adjusting this on the assumption that it might be a trimmer for that particular valve. However, such adjustment has no effect that I can detect and I have therefore left it in its original position. How can the trouble be rectified please?—G. Mott (Nottingham).

You should change the PCF80 valve. If the tuning is still out remove the side panel (over the controls—remove the switch knob etc., and unclip the panel inside) to expose the oscillator coil cores near the fine tuner spindle. Switch to channel required and tune core with the fine tuner spindle mid-way.

#### BUSH TV83

This set is 14 months old and works satisfactorily except when it is switched off. After a few seconds have elapsed a spot appears on the centre of the screen starting as a pinpoint and enlarging to  $\frac{1}{2}$  in. diameter and closing to a pinpoint. This takes about 12 seconds and the spot is very brilliant.—R. Christian (Wembley).

The appearance of the spot does not indicate a fault. There is no circuit incorporated in the TV83 to discharge the EHT at switch off and therefore the spot must be regarded as normal. It will not burn the screen.

#### ULTRA V8-15

This is no EHT. The line output transformer has been completely renewed including the U25 rectifying valve. Valves 20P4 and U329 have also been renewed. The U25 heater does not light up.—W. Shawcross (Leeds).

We presume the complete line output transformer included the EHT smoothing capacitor. It now remains to check the supplies to the 20P4 and the 0.5 $\mu$ F boost line capacitor, the screen feed to pin 4 of the 20P4 (3k 4W) and the 20L1 (also components to pins 5 and 6).

#### PYE V14

There is a raster on all channels but no picture or sound. There is a hissing noise which appears to be coming from underneath the EHT box.—R. Hardy (Sunderland).

The hiss that you can hear is EHT "brushing" and will probably disappear when the picture is restored. Check the tuner, especially the PCF80 local oscillator and its associated circuits including the sensitivity control and make sure that none of the lead-out wires from the tuner has come adrift.

#### PHILIPS 1446U

Would you please tell me what make of turret tuner I require for this set. The number is M.61799.—S. Edwards (Birkenhead).

We would suggest you fit a Cyldon P101 for Brayhead 10s. tuner unit. These have R.F. and mixer (or adaptor) plugs which replace V1 and V2 EF80 valves respectively. State the channels required when ordering.

## METAL RECTIFIERS AND CRYSTAL DIODES

(Continued from page 100)

Such an arrangement is sometimes used to provide a delay on one of the controlled valves, usually the R.F. valve, for, in the interest of noise performance, the R.F. amplifier should not be biased on weak aerial signals. Thus, if a delay of the kind shown in Fig. 9 were applied, extra control bias would only influence the stage when the AGC bias is greater than the standing bias of the diode, and the I.F. stages will, therefore, first come under control.

#### Voltage Stabilising

Voltage stabilising is also being accomplished by rectifiers of various types, and typical in this application is the zener diode; this is a silicon diode but one with a reverse characteristic in which the current rises very quickly at the reverse turnover voltage point.

The diode, in fact, functions in this part of its negative curve and the design is such that it can withstand relatively large reverse currents without ill effect. One application is in the cathode circuit of a valve amplifier, such as a video amplifier of a

television receiver, where it serves to stabilise the cathode voltage whilst having virtually no effect on the signal component.

Used in this condition, the reverse resistance of the diode biases the valve in the usual manner and holds the cathode voltage constant. As the A.C. resistance of the diode is very small, there is no undue loss of signal owing to negative feedback and cathode decoupling is unnecessary.

Selenium rectifiers may also be found connected in this manner, but with the opposite polarity to a zener diode. That is to say, the negative terminal of a selenium rectifier would be connected to the cathode of the valve concerned.

### QUERIES COUPON

This coupon is available until NOVEMBER 22nd, 1961, and must accompany all Queries sent in accordance with the notice on page 103.

PRACTICAL TELEVISION, NOVEMBER, 1961.

**SETS & COMPONENTS**

**SURPLUS, AND NEW VALVES.** guaranteed. S.A.E. for list. Also reclaimed Valves, tested perfect; 5/- maximum plus 6d. postage each. Genulin Valve bargains. Valves bought. Lewis, 46 Woodford Avenue, Ilford, Essex.

**TV TUBES**

**12 MONTHS' GUARANTEE**

- 12in. and 14in. £5.00
- 15in. and 17in. £5.10.0
- 21in. £7.10.0
- 7/6 allowance on old glass

All fitted new American Guns. Phone or Call only NUN 3946

**FELMARC LTD.**

**15 Kingsway, Nuneaton, Warks.**

Callers to Works:

R/O 15 Marlborough Road

**B.Y.A. NEW** and rebuilt TV tubes. S.A.E.: REDWATT TUBE DISTRIBUTORS, 41 Denmark St., Wakefield, Yorks.

**Television Tube Shop**

now stock

**Tubes for every make of set  
OVER 600 TUBES IN STOCK**

- 12 inch Mullard type ... £4. 5.0
- 12 inch Mazda type ... £4.15.0
- 14 inch Mullard type ... £5. 5.0
- 14 inch Mazda type ... £5.10.0
- 15 inch Mazda type ... £5.15.0
- 16 inch G.E.C. & Mullard type £6.12.6
- 17 inch Mazda & Mullard type £6.10.0
- 17 inch G.E.C. & Brimar type £6.15.0
- 21 inch Mullard type ... £8. 0.0

Add 10/- for insured carriage to your door within 48 hours, or 5/- via B.R.S. Terms £2 down (plus carriage).

All tubes tested before despatch and guaranteed for 12 months. Guarantee cards enclosed with each tube.

**Special Purchase of 110", 17 inch tubes—**  
Slight mark, Guaranteed for 12 months.  
Mazda CHE 1703 } replace AW43-88,  
GEC 7405A } £6.

**Shop Soiled Tubes.**  
(Slight scratches or marks) Guaranteed 12 months. Ideal for second set. 12in. 3/18, 3/31 37/6. MW31-74 50/-. 14in. MW 36-44 52/6. CRM141 55/-. 17in. CRM171, MW 43-64 60/-.  
Others available from time to time. Please enquire.

**Service Engineers**  
Our Rebate Scheme shows real savings—send for details.

**Television Tube Shop**

**48 Battersea Bridge Road, S.W.11**  
BAT 6859  
Just South of the Bridge. Open Saturdays.

**RATES:** 4/- per line or part line (not average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television" Tower House, Southampton St., London, W.C.2.

**SETS & COMPONENTS**  
(continued)

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure, DIRECT TV REPLACEMENTS LTD., Dept. PT/22/10, 138 Lewisham Way, S.E.14. Tideway 6666.

**TV SPARES**

**LINE OUTPUT TRANSFORMERS**

A few examples from our extensive range.

TELEPHONE ORDERS SENT SAME DAY C.O.D.

- Alba T301, 304, 394, 484, 494, 421/6.
- Alba T321, 324, 424, 524, 391/6.
- Baird 164/5/7, 172/5, 1812/15, 621/6.
- Baird P2014/7, P2114/7, 581/6.
- Banner B112/4/7, 124, 412, 436, 651/-.  
Beethoven B77, 80, 94-9, 106-9, 651/-.  
Bush TV53, 691/6; TV24C, 891/6; TUG34, 5 gns.
- Cosmor 930-9, 581/6; (new), 301/ (used).
- Decca D14/17, 581/6; DM14/17, 551/-.  
Ekco T221, 231, 311, 284, 330, 551/-.  
Ekco T161, TC162, TC166, TU169, 301/ (used).
- Ferguson 992/6/8 661/9; (new) 301/ (used).
- Ferguson 205-246; 661/9; 306/8, 581/6.
- Ferranti 14T3/4/5, 471/6; 14T2/T1225, 621/6.
- Ferranti T1002/5, 551/-.; T129-138, 471/6.
- G.E.C. BT, 1251/2 1746/8, 2250, 501/-.  
H.M.V. 1824/9, 1840-8, 2805-5902, 691/6.
- K.B. NF 70/FM, MV/OF 100, PVP20, 751/-.  
Masteradio T917, TE7T, T409/12, etc, 581/6.
- McMichael TM/C/CR 51-2, 551/-.; C/R 53 751/-.  
Murphy V 240/250/280, 651/-.; V200, 491/6.
- Pye/Pam/Invicta V417, VT417, LV30, FV1 908-958, T118-120, 551/-.; CS17, etc., 751/-.  
New Scan Coils on all above 651/-.  
Peto-Scott TV122/4/6, 671/6; TV1411, 721/6.
- Philco 1457-67, 1717-47, 1753-77, 871/6.
- Philips 1114U, 1115, 1437, 1446, 891/6.
- Pilot CV76, 77, 84, 87, etc. 651/-.; TV94, 891/6.
- Portadyne TA 17, T237, T417, used, 391/6.
- R.G.D. C55, 1455/6, 1755/6/7, etc. 891/6.
- Ultra VT917, etc. with U25 5 gns.
- Vidor CN4206-12, 591/6; CN4217-31, 651/-.  
We stock or can obtain most L.O.T.'s Scan Coils, Frame O.P.'s and spares.

PLEASE SEND S.A.E. FOR IMMEDIATE QUOTE.  
Callers welcome. Open all day Saturday. Terms C.W.O. or C.O.D. Add 2/6 P. & P.

**NEW TV BARGAINS**

We have a limited number of 1962, Slim line Television Receivers by Famous Makers at special prices. For example 17 inch. List 57 gns. Our Price 44 gns., plus 25/- Carr. & Ins., 110 Tube, Printed Circuit. Contemporary Styling. All Channels. Full guarantee. All in sealed boxes. Immediate despatch on your order.

**TELEVISION CONSUMER SERVICES LTD.**  
**112 CAMBERWELL RD., S.E.5.**  
RODney 7917

**SETS & COMPONENTS**  
(continued)

**Television Picture Tubes**

**Twelve Months**

Manufacturers' Guarantee

- 12 inch .. .. £5. 0. 0
- 14 inch .. .. £5. 10. 0
- 15 inch .. .. £7. 0. 0
- 16 inch .. .. £7. 0. 0
- 17 inch .. .. £7. 0. 0
- 21 inch .. .. £8. 15. 0

Deposit 20/- plus 12/6 carriage.

Tubes for ALL H.M.V. and Marconi sets at reduced prices.

**Cathode Ray Tube Service**

35 Broomwood Road  
St. Paul's Cray, Kent  
Orpington 21285

**In Scotland . . . . .**

**RENVUE**

**for Better Value**

**COMPLETELY REPROCESSED TUBE  
(NEW GUN, RESCREENED,  
ALUMINISED)**

- 12.6v. and 6.3v., 0.3 amp.,  
17 and 15in. Types ... .. £6.10.0
- 12.6v. and 6.3v., 0.3 amp.,  
14in. Types ... .. £6. 0.0
- 12v., 15in. Types ... .. £7. 0.0
- 2v., 12 and 15in. Types ... .. £6. 0.0
- Electrostatic 90 degree and 110 degree tubes  
10/- extra. Carr. paid.

17in. BBC and STV Receivers ... £19.0.0  
COMPLETELY OVERHAULED AND  
FITTED WITH PROCESSED TUBE  
STV and BBC 14in. Receivers ... £2.10.0  
COMPLETE WITH VALVES AND TUBE.  
CALLERS ONLY. CARRIAGE EXTRA.  
OPEN SATURDAY AFTERNOON

**Renfrew Electronics Ltd.**

**Anderson Drive**

**Renfrew : Scotland**

Tel.: Renfrew 2642

**SALVAGED VALVES TESTED ON A MULLARD HIGH SPEED VALVE TESTER TO 100% STANDARD**

AS0N 2/6	POTENTIOMETERS
AC/P 2/6	Carbon Pots, 25k .. .. 1/- ca.
AC3PEN	V/C and SP/SH, 500k .. .. 2/6 ca.
DI 2/6	RESTORERS
AC/TP 2/6	Card of 1W Resistors, 72 Per
APV4 2/6	values covering complete card
AZ31 2/6	10% range .. .. 2/-
B36 2/6	Full range of Separate Resistors
B95 2/6	
D1 2/6	CONDENSERS
D03 2/6	100µf + 200µf 275 v. D.C. 9/-
D77 2/6	100µf 350 v. D.C. .. .. 7/6
DD4 2/6	8µf 450 v. D.C. .. .. 2/3
DD41 2/6	15µf 350 v. D.C. .. .. 3/-
ED13 2/6	100µf 150 v. D.C. .. .. 2/6
DF91 2/6	0.1µf 500 v. D.C. Paper .. 1/-
DH77 2/6	0.01µf 500 v. D.C. Paper .. 10d.
DK96 2/6	0.001µf 500 v. D.C. Paper 10d.
DW4/300/6	VALVE HOLDERS
E20 1/3	Standard Double-ended tuning 2/6
EB34 1/3	3-50pF concentric trimmers 8/- dos.
EB41 1/3	Banks of six compression
EB91 2/6	trimmers, 3-50pF. .. .. 6d.
EB93 2/6	VALVE HOLDERS
EB41 2/6	American Octal .. .. 5/- dos.
EC32 2/6	Novel .. .. 9d. ca.
EC34 2/6	METAL RECTIFIERS
EC91 4/-	RM4. New and Boxed 15/- ca.
EC92 4/-	RM4 Salvaged .. .. 5/- ca.
ED13 2/6	Silicon Type
EP30 1/3	250v. 300mA, dia. 1", L 17 1/2", 20/-
EP30 1/3	125v. 300mA, dia. 1 1/2", H 3 1/2",
EP91 1/3	10/- ca.
EL3 2/6	CRT Converter Caps .. .. 9d. ca.
HL41DD/6	Standard Crocodile Clips .. 6d. ca.
K730 1/3	Miniature Crocodile Clips .. 6d. ca.
K742 2/6	1 1/2" Brown Knobs .. .. 6d. ca.
K761 2/6	Igramic Jack Plugs .. 4/6 ca.
K761 2/6	GATIWAY RAY TUBES
L03 2/6	SPECIAL OFFER
M14 2/6	150n. G.E.C. 8901 .. .. 30/-
MSP4 2/6	120n. G.E.C. 7102 .. .. 10/-
N30 2/6	Salvaged but good tubes.
P41 2/6	Personal Callers Only.
P61 2/6	35M/CS and 10M/CS TURRET
PC334 4/-	TUNERS, less valves taken from
PCF50 4/-	sets .. .. 18/6 ca.
PCF84 4/-	TRANSFORMERS
PCL92 4/-	CRT Boost Transformers 12/6 ca.
PEN45 1/3	Heavy Duty Output Trans-
PEN49 2/6	formers, 6 ratios from 13 : 1
PENDD	to 43 : 1 .. .. 25/- ca.
4020 2/6	Miniature Output Trans. 3/6 ca.
PL33 2/6	Standard Output Trans.
PL31 4/-	formers, Multi-match 10/- ca.
PL29 4/-	Transistor Drivers: 1-1 CT 10/- ca.
PL83 4/-	3.6-1 CT 12/6 ca.
PY31 2/6	Transistor Output: 3.6-1 CT 10/- ca.
PZ30 4/-	9.2-1 CT 10/- ca.
SP41 1/3	Microphone Transformers,
SP42 2/6	ratio 65 : 1 .. .. 35/- ca.
SP61 1/3	L.F. TRANSFORMERS
TDD13C 2/6	Standard 45k/s .. .. 12/6 per pair
TN2320 2/6	Midrange 45k/s .. .. 16/- per pair
TP29 2/6	AUTO TRANSFORMERS
U3 2/6	250W .. .. 67/6 ca.
U31 2/6	100W .. .. 27/6 ca.
U251 2/6	50W .. .. 20/- ca.
UF42 2/6	TRANSISTOR FAULT FINDER
UL7 2/6	Enables faults to be located
V37 2/6	quickly. Consists of a two-
VP4 2/6	transistor, multi-selector in a box.
VP1B 2/6	Complete with battery. 32/6
W77 2/6	X-RAY
X41 2/6	250v. .. .. 2/6 ca.
Y26 2/6	250v. .. .. 2/6 ca.
Z66 2/6	CRYSTALS
Z77 1/3	GENUINE MULLARD. Boxed
Z90 1/3	OA5 6/- OA81 3/-
Z719 2/6	OA70 3/- OA85 3/-
PL29 2/6	OA79 3/- OA91 3/6
4TPB 2/6	TRANSISTORS
6AL5 2/6	GENUINE MULLARD. Boxed
6AM6 1/3	OC16W 48/- OC75 8/-
6BW7 2/6	OC19 48/- OC79 8/-
6C8 2/6	OC36 25/- OC76 8/-
6D2 2/6	OC44 11/- OC78 8/-
6D3 2/6	OC45 10/- OC81 8/-
6D5 2/6	OC70 8/- OC82 18/-
6D6 1/3	OC71 6/- OC170 17/6
6F13 1/3	10 WATT HI-FI AMPLIFIER KIT
6J5 2/6	using valves from our salvage
6J7 2/6	range. Complete with trouble and
6P25 2/6	base unit. Inc. valves. 87.9.6
6P28 2/6	TERMS: C.W.O. ONLY.
8D3 1/3	Orders under £1. P. & P. 1/-.
9D6 2/6	Open till 11 p.m. most days.
10P1 2/6	

S.A.E. for list or 9d. for full catalogue.

**Arion Television**  
4 Macted Road, S.E.15 NEWX 7152  
23 Northcross Road, S.E.22.

**SETS & COMPONENTS**  
(continued)

**C. EDWARDS**

1070 Harrow Rd., London N.W.10  
Ladbroke 1734

500 S/H TV Sets must be cleared  
as taken part exchange. Condition  
unknown.

**ALL SETS COMPLETE**

12in. BBC 25/- 13 Channel 50/-  
14in. " 50/- " " 75/-  
17in. " 85/- " " 125/-  
Plus 15/- carriage

**Guaranteed Valves**

10C2 10/-, 20D1 6/-, 6K25 8/-,  
PL38 10/-, PL81 8/-, PY81 8/6,  
PY80 7/6, PZ30 10/-.

**BRAND NEW 17in. Television Cabinets**  
by famous maker Continental design.  
Complete with screen, mask, back,  
knobs and tube mountings. Ideal for  
converting your old 14in. to 17in. set.  
£4.12.6, tubes supplied £4.10.0; carr.  
7/6. 12 months guarantee. GLICK-  
SONS, 32 Cradock St., Swansea.

**IMPORTANT NOTICE !!**

"LUMENAR" The Finest Replacement  
Tube now available with new low prices.

12in. .. .. £5.10.0  
14in. .. .. £7. 2.6  
17in. .. .. £8.10.0  
21in. .. .. £11. 0.0  
Carr./Ins. 10/-

"LUMENAR" Tubes are made by  
MULLARD, The Original Manufacturers,  
and are Fully Guaranteed.

C.W.O. to:

**REDWATT TUBE DISTRIBUTORS**  
(BVA Specialists)

41 Denmark Street, Wakefield, Yorks.

**TUBES! BRAND NEW, 12in., 14in.,**  
£3/£4. 1 year guarantee. Also most  
rebuilds. Finest value!—3 Pank Ave.,  
New Barnet. BAR 1934.

**COMPLETELY REBUILT**  
**C.R.T.s**

**Fully Guaranteed**

14in. ... .. £6. 0.0  
17in. ... .. £6. 10.0  
21in. ... .. £8. 10.0  
10/- Old Tube Allowance. C.W.O.

Free Carr. and Ins. Passenger.  
All types and sizes. S.A.E.  
Enquiries.

**TRADE SUPPLIED**

**BROADBENT, Canal Bridge,**  
**Birmingham Road, Stratford-**  
**on-Avon.**

**LINE OUTPUT**  
**TRANSFORMERS**  
**SCAN COILS**  
**SPECIALISTS**

Makes	Models	Prices
ACE:	Spares available.	
ALBA:	T301, T304, T394, T484, T494, etc.	39/6
AMBASSADOR:	Spares supplied.	
ARGOSY:	Most models available.	
ARMSTRONG:	Spares supplied.	
BAIRD, BANNER, BETHOVEN:	Spares supplied.	
BUSH:	TV11A, 11B, 12A, 12B, TVG12A, 12B, TRG12A, 12B 45/- TVG26, TV32, TV38, TVG34 TVG34A, T86, TV38, TVG36 TVG38, TVG40, T87, TV57, Best 1 TVG58, TV62, TV63, TV66, only TV87, etc.	69/6
COBSOR:	930 & T. 931, 933-4-5, 987, 988A & F, 989 & A & F .. 59/6 930T, 940-945, 946, 945B, 949	69/6
CHAMPION, COLUMBIA:	Spares supplied.	
DECCA:	D17 & C .. 69/6 DM1, DM2C, DM3, DM4/C .. 65/- DM5, DM14, DM17, 444, 555	65/-
DEFIANT:	Spares supplied.	
DYNATRON:	Spares supplied.	
EKCO:	TS93, TC8102, TS105, TS114 TRC124, TC138, TS188, TR393 TRC139, TC140, T141, TV142 T164, TC162, T164, T165, etc. 47/6 TC208, TV209, T231, T231, T231F, T248, T283, T284, .. T293, etc.	55/-

**ENGLISH ELECTRIC/ELECTRONIC.** Spares supplied.

**FERGUSON:** 140T, 160T, 113T, 130T,  
145T .. .. 68/6  
941T-958T inclusive .. .. 59/6  
991T-997T inclusive .. .. 68/6  
203T-240T inclusive .. .. 69/6  
309T, 309T .. .. 69/-

**FERRANTI:** 14T3, 14T3F, 14T4 .. 45/-  
17K3 & F, 17T3 & F. .. 45/-  
17K4 & F, 178K4 & F. .. 45/-  
17T4 & F, 178T4 & F. .. 45/-  
14T5, 178K5, 17K5 .. 45/-  
BT1251, BT1252, BT1746, .. 49/6  
BT1748, BT4743 .. 49/6  
BT3443, BT5147, BT5246-48 39/6  
BT5348-BT5643R inclusive 49/6

**G.E.C.:** 14T5, 178K5, 17K5 .. 45/-  
BT1251, BT1252, BT1746, .. 49/6  
BT1748, BT4743 .. 49/6  
BT3443, BT5147, BT5246-48 39/6  
BT5348-BT5643R inclusive 49/6

**H.M.V.:** 1824 & A to 1831 inclusive .. 67/6  
1840, 1841, 1842-1848 .. 67/6  
1849, 1850, 1851 .. 55/-  
T118, T119, T120 .. 55/-

**INVICTA:** All other models available.

**K.E.B.:** LFT50, LVT50, LET50, Mv80  
Mv80 All models available, etc.

**MARCONI:** All models available.

**MASTERADIO:** All models available.

**MICHAEL:** All models available.

**MURPHY** V200, V202C .. .. 67/6  
V200, V250 .. .. 95/-

**PAM, POTO SCOTT, PHILCO:** All models available.

**PHILIPS:** 1785U, 2185U .. .. 105/-  
All models available.

**PILOT:** All models available.

**PORTADYNE:** All models available.

**PYE:** CFM4, FV4C, FV4COL .. 65/-  
V4, V74, V7, V77 .. 65/-  
LV30, FV1, FV1C .. 69/6  
CS17F, CFM17F, CW17 .. 69/6  
CW17C, CW17CF, CW17F, etc. .. 69/6

**RAYMOND:** All models available.

**REGENTONE:** All models available.

**R.G.D.:** 6017T, 7017, C54, etc. .. 59/6

**SOBELL:** All models available.

**STELLA:** ST5721U .. .. 105/-  
ST8621U, ST8621U .. .. 105/-  
ST8921U .. .. 105/-

**STRAD, TELEVOICE, TRUVIEW:** Available.

**ULTRA:** 8L series, 8L series, with U25 etc., complete .. 79/6

All models available.

**VALRADIO:** Spares available.

**VIDEOR:** CN4217-CN4231 inclusive .. 66/-

**WESTMINSTER:** Spares available.

**WHITE-IBBOTSON:** Spares available.

Scancoils, Osc. and Output Tx. for all above makes available.

Post and Packing 2/6. C.O.D. 3/- extra.

All Enquiries S.A.E.

**WYNDSON TELEVISION**  
Dept. P.T.  
ST. ALBANS RD., BARNET, HERTS.  
BAR 1769

## SETS & COMPONENTS

(continued)

### TUBES-AERIALS-VALVES

Regunned tubes, guaranteed one year, full range of aerials and fittings. I.T.V. boosters, valves, brayhead tuners, T.V. sets, transistor radios and all electrical appliances. Co-axial cables and house wiring cables, fluorescent fittings. All quotations without obligation. Special terms to the trade, and Home Engineers. S.A.E. for Catalogue.

#### G. A. STRANGE

BROADFIELD, NORTH WRAXHALL, Nr. Chippenham, Wilts. Tel. Marshfield 236

REBUILT TUBES, 18 months' guarantee; free advice. S.A.E. to G. HURST, 3 Coniston Rd, Sheffield 8.

### H.P. on Regunned C.R.T.s

At No Extra Charge  
12 Months' guarantee

12" & 14" .. £3.10.0  
17" .. £4.10.0  
21" .. £5.10.0

Phone or Call only:

Rod 7778

**P. J. F. Andrews**  
61-63 ROSEMARY RD.  
LONDON, S.E.15

#### FOR SALE

VALVE CARTONS at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a Godwin Street, Bradford 1.

Television Tubes Rebuilt. Please note we have appointed M/S R. S. Strudwick, 17 Hollingdean Road, Brighton 7, as Sole Agent for our Genuine Rebuilt Television Tubes for the South Coast. For details of prices, etc., please refer to our advertisement in the inside front cover.

### MARSHALL'S

for TELEVISION LTD.

131 St. Ann's Road, Tottenham, London, N.15.  
Stamford Hill 2267 & 5555

ALUMINIUM LADDERS/STEPS. Gigantic offer, 400 models. SANCO LTD., 17 (P.T.) Boundary Rd., Hove.

**TV AERIALS POST FREE**  
**UNBEATABLE QUALITY**  
**AND PRICES.**  
**LOW LOSS CO-AX CABLE**  
6d. YD.

CATALOGUE AND CABLE SAMPLE FROM  
A.E.S.  
13 ST. THOMAS STREET, WEYMOUTH

## FOR SALE

(continued)

100 BAYS of brand new adjustable Steel Shelving, 72in. high by 34in. wide by 12in. deep, stove enamelled dark green. Sent unassembled. Six free by—£3/15/0. Sample delivered free. Quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel: 69018.

### TV's FOR SALE

#### PRICES REDUCED

BEC/ITA in good working order:	C.R.T. Good Rebuilt
14in. Ultra VT315: KB LVT30	£13 £17
14in. Ekco T221 or T283	.. £18 £21
14in. Ferguson 992	.. £9 £13
17in. Plessey: RGD ..	.. £17 £21

Send for Lists Carr. Paid

### CADMAN'S

Bryan Street, Hanley  
Phone: Stoke-on-Trent 23557

GARRARD 210 £9/8/6; B.S.R. UA14 £7/15/0; T.U.9 £4/2/6; B.S.R. Tape Deck £7/10/0. Set of 7 Transistors, standard quality 32/6. Full list from—H. F. JAMES, 21 Claremont Road, Twickenham, Mdx.

### METAL RECTIFIERS

RECTIFIERS—CONTACT COOLED.  
14RA1283 (FC10) type 250 v., 250 mA, 13/6;  
14RA1283 (FC31) type 250 v., 300 mA, 17/6;  
350 mA, 19/6.  
RECTIFIERS—FIN TYPES  
Equiva. for RM4 250 v., 250 mA, 14/-; RM5 250 v., 300 mA, 17/6; 14A989 400 mA, 18/6;  
14A86 16/6; 14A97 20/-; 14A100 22/6; 14A124 22/6; LW7 20/6.

### CABY MULTIMETERS

A10 - 16 ranges, £4.17.8; B20 - 20 ranges, £6.10.0. S.A.E. for full details.  
ARMCHAIR EXTENSION VOLUME CONTROL unit for TV Radio Amplifiers, etc. Easily fitted, perfectly safe, 19/6.

### TRANSISTORS

OC18 16/-; OC71 5/-; OC31 6/-; OC170 9/6;  
OC28 10/-.  
Cash with order. Post Free. C.O.D. 2/6.

### DURHAM SUPPLIES

175 Durham Road, Bradford 8, Yorkshire.

#### WANTED

NEW VALVES WANTED — EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. DURHAM SUPPLIES, 175 Durham Rd., Bradford 8, Yorkshire.

A PROMPT CASH OFFER for your surplus brand new Valves, Speakers, Components, Test Instruments, etc. R.H.S., Beverley House, Manville Terrace, Bradford 7.

### SERVICE SHEETS

SERVICE SHEETS, Radio, TV, 5,000 models. List 1/-. S.A.E. enquiries: TELRAY, 11 Maudland Bk., Preston.

FAULTFINDER FILES (TV) showing common faults that each receiver is prone to and other useful servicing information, 2/- each. List 9d., plus postage. S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

SERVICE SHEETS, Radio and TV 4/- each. List 1/-. All orders dispatched on day received. Also manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

## SERVICE SHEETS

(continued)

SERVICE SHEETS. We have the largest stock of Radio and TV Service Sheets in the country for sale at 4/- each, old type receivers a speciality. Guaranteed return of post service. Service Sheet list: 1/-, manufacturers' Manuals for sale and hire, list 1/-. S.A.E. please. Mail orders only to: S.P. DISTRIBUTORS, 44 Old Bond Street, London W.1.

SERVICE SHEETS; also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20 Extension, Shepherd's Bush Market, London W.12. (Phone: SHE 3052).

### SERVICE SHEETS

For all makes of Radio and Television—1930-1962. Prices from 1/-. Free fault-finding guide with all Service Sheets. Please send S.A.E. with enquiries.

Catalogue of 6000 models, 1/6.

Special offer of 125 Radio/TV Sheets covering 370 popular models, 20/-.

Hamilton Radio, Western Road, St. Leonards, Sx.

## EDUCATIONAL

### Radio Television & Electronics

Learn at home with the world's largest home study organisation. Brit. I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for FREE prospectus stating subject to

I.C.S.

Dept. 516  
Intertext House, Parkgate Road,  
London, S.W.11.

THE INCORPORATED Practitioners in Radio & Electronics (I.P.R.E.) Ltd. Membership Conditions booklet 1/-. Sample copy of I.P.R.E. official journal 2/- post free.—Secretary, 20 Fairfield Road, London, N.8.

## ELECTRONICS

Key to YOUR Future?

An exciting career—  
A new Hobby—Your  
own spare- or full-  
time BUSINESS?



New experimental course includes big kits for building test gear and a complete AM/VHF receiver.

FREE  
brochure from

**RADIOSTRUCTOR**

DEPT. E78, READING, BERKS.



**EDUCATIONAL**  
(continued)

"HOW AND WHY" of Radio and Electronics made easy by a new, non-maths practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from Dept. 12, P.T. RADIOSTRUCTOR, Reading.

**BOOKS & PUBLICATIONS**

**FIND TV SET TROUBLES** in minutes from that great book, "The Principles of TV Receiver Servicing," 10/6 all book houses and radio wholesalers. If not in stock, from Secretary I.P.R.E., 20 Fairfield Rd., London, N8.

**EDDY'S (NOTTM.) LTD.**  
172 ALFRETON RD., NOTTINGHAM  
NEW AND SURPLUS VALVES

Guaranteed and Tested by Return Post

IDS	7/6	6V6G	4/9	EF41	7/6
IL4	3/6	6V6GT	6/-	EF42	7/6
IR5	5/6	6X4	5/-	EF50	1/9
IT4	3/6	6X5G	5/6	EF80	5/0
3A4	6/-	6X5GT	6/6	EF86	9/6
354	5/11	7C5	7/6	EF91	3/6
5U4G	4/9	10F1	6/6	EF92	4/6
5Y3GT	6/6	12A6	5/3	EL41	7/6
5Z4G	7/6	20P1	9/6	EL91	4/6
6AG5	3/6	20P3	12/6	EY51	7/11
6AC7	4/-	25L6GT	7/6	EY86	7/9
6B8G	2/11	30F5	6/11	KT33C	6/6
6C4	3/6	35W4	6/9	MU14	7/-
6C6	4/9	35L6GT	8/6	OZ4	5/11
6F1	6/11	35Z4	5/3	PEN36C	8/-
6F13	8/6	80	7/-	PEN45	5/-
6F15	9/6	954	1/6	PL81	9/-
6F33	6/6	955	3/6	PL82	7/6
6J5G	2/9	956	2/6	PL83	7/6
6J5GT	3/9	AC2/		PY80	7/-
6J5M	4/3	PENDD	7/6	PY81	6/11
6J7G	5/-	CY31	9/6	PY82	6/6
6K7G	1/11	DM70	6/11	PZ30	9/6
6K8G	5/3	ECC82	5/3	TD44	7/6
6P25	9/6	ECC82	5/11	SP61	2/6
6Q7G	5/9	ECC83	6/6	UCH42	7/6
6S7M	4/9	ECC85	6/11	U25	12/6
6SA7M	5/9	ECH42	7/9	UY41	6/3
6S7M	5/9	ECL80	7/6	VP23	6/6
6SN7GT	4/3	EF36	3/-		

**CRYSTAL SETS.** Complete 2 wave bands high gain 19/11. Also with transistor amplifier extra 9/11. P. & P. 2/6.

**HEADPHONES.** High res. to suit above crystal set. Good quality 13/11. P. & P. 2/-.

**NIFE ACCUMULATORS.** 1.25v. size 3 x 2 1/2 x 3/4 in. 7 amp hrs. weight 13 ozs. 2/6 ea. P. & P. 2/-.

**VIBRATORS.** 12 volt 4 pin 4/11. 2/6 volt 4 pin 8/11. Post 1/6.

**THROAT MIKES 2/- ea.** Post 8d. Could be used for electrifying musical inst. etc.

**DIMMER SWITCHES.** Ideal for train speed regulations. 1/11. Post 1/3.

**GERMANIUM DIODES 9d. each.** 7/- dozen. Post 6d.

**HEADPHONE CORDS.** 6ft. 1/11 P. 6d.

**MORSE TAPPERS.** Plated contacts adjustable gaps. Heavy duty 3/6. Post 1/3.

**POCKET RADIO.** 2 Transistor with miniature speaker. Complete with all parts. Wiring diagram and full instructions. 27/6. Batteries 1/-, P. & P. 2/-.

**SPEAKER GRILL.** Gold 6 1/2 x 4 in. 1/- Post 1/-.

**JACK PLUGS.** Standard 1/11. Post 9d.

**V.H.F. AERIALS 6/11.** Post 1/-.

**ALL ABOVE ARE NEW AND GUARANTEED**

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk. Post and Packing 6d. per valve extra. C.W.O. or C.O.D. Only C.O.D. charge 3/- extra. S.A.E. with enquiries.

**BBC - ITV - F.M. AERIALS**



**B.B.C. (BAND 1).** Telescope loft, 19/6. External. S/D. 26/3.

**I.T.V. (BAND 3).** 3 Element loft array, 24/- 5 Element. 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

**COMBINED B.B.C. + I.T.V.** Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 54/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.

**F.M. (BAND 2).** Loft "H", 28/- 3 Element loft, 52/6. S/D loft, 12/6. External S/D, 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable. 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

**K.V.A. ELECTRONICS (Dept. P.T.)**  
3B Godstone Road, Kenley, Surrey

**FIRST-CLASS TELEVISION and RADIO COURSES**

**GET A CERTIFICATE!**

After brief, intensely interesting study —undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

**FREE GUIDE**

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

**FOUNDED 1885—OVER 150,000 SUCCESSES**  
**NATIONAL INSTITUTE OF ENGINEERING**  
(Dept. 462), 148 HOLBORN LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.  
Australia: P.O. Box 4570, Melbourne.

**TV TUBE RESTORER**

EXTRA LIFE, EXTRA BRILLIANCE

PLUGS ON TO YOUR TV TUBE

ANY SIZE

PATENTED

Important! State Make, Model No. Name and Address in Block Letters Please.



STANDARD MODEL .. 22/6  
DE LUXE MODEL .. 30/-  
Postage 2/6 either model

**SINCLAIR ELECTRONICS** Dept. P.T.3  
18 Newport Court Charing X Rd. WC2  
Terms: C.W.O., C.O.D.

**COYNE'S NEW PIN-POINT TV TROUBLES**

**TAKES HEADACHES OUT OF ALL SERVICING PROBLEMS**



Your most useful on-the-job "tool"! Quickly and easily pin-points the exact trouble in any TV set. Covers 70 symptoms, 700 trouble spots. Over 340 cross-indexed pages; 50 time-saving Check-Charts; 290 diagrams and photos; explanation of circuits and designs.

**SIMPLE CHECK-CHART SYSTEM SAVES TIME!**

This amazingly practical handbook shows you how to find the trouble in any TV circuit FAST! Simple cross-index tells you in what section you'll find cause of trouble. Handy Check-Charts then help you accurately locate the EXACT trouble spot. Cut waste time, eliminate hours of aggravation, get right to the heart of the trouble in minutes.

**USE THIS BOOK RIGHT ON THE JOB—NO NEED TO MEMORIZE!**

This Pin-Point Book was designed especially for on-the-job trouble-shooting. You simply turn to the indexed section, locate the circuit description and Check-Chart, and in minutes you have the trouble spot located and ready for repair. No complicated theory or mathematics. Down-to-earth practical circuit description, service methods and trouble-shooting techniques. Published by the famous Coyne Electrical School and approved by leading authorities in the field.

J. E. C. Grover of Streatham says: "Immediately I glanced through this book I was convinced that your claims concerning the merits of this work were justified, for it is, without a doubt, the finest book of its kind that I have ever come across. It is not only unique in its presentation but it is also superbly produced."

G. Axam of London S.E.9, says: "I have spent nearly £50 on technical books over the past 5 years all of which I feel has now been wasted as your book is the best I have yet had the pleasure of examining. It is practical, to the point, with just the right amount of technical information needed, covering almost every aspect of TV servicing."

**SEND NO MONEY!**

Just mail coupon to free trial. After 7 days send only low price or return book and pay nothing!

**FREE TRIAL OFFER!**

Mail Coupon NOW!

Mail Order Division, SIM-TECH BOOK COMPANY, Dept. P.3, Gater's Mill, West End, Southampton, Hants.

RUSH. TV Troubles 31/6d. plus 1/9d. postage for 7 day FREE TRIAL as per offer.

Tick here if enclosing full price, we pay postage: Same 7 day money back guarantee

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ County \_\_\_\_\_

# COYNE'S

## NEW JOB TRAINING BOOKS

Put Money-Making Time  
Saving Know-how at your  
fingertips!

TRY ANY THREE BOOKS ON NO RISK FREE TRIAL

Look over the list of books and select the first three books you would like to examine. Note the book numbers on the coupon. Additional books you would like to see may be entered on a separate piece of paper, and these will be sent to you after completion of the first transaction.

### SPECIAL OFFER COYNE ELEMENTARY PRACTICAL RADIO-TELEVISION SET OF THREE VOLUMES, total 1,038 pages, sturdy Vinyl washable covers. £3.12.6. the set!

These three volumes present the principles of construction, operation and testing of radio and television equipment in a SIMPLE, EASY TO FOLLOW manner.

By using NEW & DIFFERENT methods of explanation these books clearly explain the direct relation between the various parts of sets. This information is especially helpful in repair work where many times a burned out valve, resistor or transformer is actually caused by some other defective part of a circuit. Until the cause of the trouble is removed the parts would continue to burn out. For this reason each part of the radio or television unit is explained, thus, making the material especially helpful to the experienced radioman, as well as the amateur.

One very important way in which these books differ from many other radio and television books is that the publishers did not try to assume the "extent of technical knowledge" of the reader. Every subject is explained COMPLETELY—while at the same time keeping it brief and to the point.

You will find hundreds of photos, charts, diagrams, etc., in these books. These have been provided to make it easier to understand the explanations. To get this special offer, send no money now, then 12/6 after free examination, and 20/- per month.



#### No. 9 *Pin-Point* Transistor troubles in 12 minutes (Coyne)

In this extremely practical handbook, the famous Coyne Check-Chart Trouble Shooting Method is applied to Transistorized Equipment and includes such subjects as Pre-amplifiers and Hearing Aids, Audio Amplifiers, Portable Sets, and Special Types of equipment. Hundreds of photos, illustrations, diagrams and Check-Charts; Valuable reference sections. 525 pages. Spiral Binding. Price 47/6. (Please send coupon with order.)

#### No. 4. LATEST INSTRUMENTS FOR SERVICING RADIO AND TELEVISION. (Coyne.)

This up-to-the-minute book tells all about modern radio, TV and electrical testing equipment and how to use it. Money-making short cuts on trouble-shooting, servicing, construction, and other jobs. Over 350 pages, 220 photos and diagrams. Covers Multimeters, Resistors, Ohmmeters, Oscilloscopes and many others. All data has been pretested in the Coyne radio shops. Vinyl cloth covers. 26/-.

#### No. 5. PRACTICAL TELEVISION SERVICING AND TROUBLE SHOOTING MANUAL. (Coyne.)

A book of fast time saving methods for servicing TV receivers. Includes dozens of new testing ideas all of which have been proven on the job. This book shows how radio knowledge can be applied to help solve television problems. Contents include TV Servicing methods, TV Servicing Instruments, Tuners, Video I.F., Amplifiers, alignment, etc., with 200 crystal clear photos and diagrams. 437 pages. Washable vinyl cloth covers. Price 34/-.

#### No. 22. PIN POINT COLOUR TV TROUBLES IN 15 MINUTES. Edited by Robert G. Middleton. (Coyne.)

This book deals with 150 types of faulty pictures and sound with over 1000 troubles which may be the cause. Some of the subjects covered are, Antenna, Tuner, Video and Luminance Amplifiers, Matrices, Picture Tubes (Black and White, and Colour), One-Gun Tubes, Set up of Colour Tune, Colour Filter and Automatic Chroma Control, Low Voltage, Power Supply, TV Sound, etc. Picture Pattern Section — 362 Check Charts, Diagrams and Photos. 548 pages. Price 47/6.

#### No. 18. REFERENCE MANUAL OF TRANSISTOR CIRCUITS. Mullard.

Features 60 circuits you can build, 241 diagrams. 308 pages. 12/6.



FREE TRIAL OFFER!

#### No. 6. COYNE TELEVISION SERVICING CYCLOPEDIA. Harold P. Masny. (Coyne.)

Quick and concise answers to TV problems in alphabetical order, cross indexed, fully illustrated, covers hundreds of questions involving radio, TV, electronics operation and repair. 450 illustrations; photos, diagrams, charts, test patterns, etc., 860 pages. Vinyl cloth covers. Price 47/6.

#### No. 19. REFRIGERATION SERVICE MANUAL. H. P. Masny.

An instruction book on accepted methods of servicing and repairing electric refrigerators and refrigeration systems. It covers every operation in field service, performed where the equipment is installed, and also the shop operations which may be performed with the simpler kinds of equipment. 157 illustrations, 343 pages, cloth. Price 24/-.

#### No. 7. TRANSISTOR CIRCUIT HANDBOOK. Louis E. Garner. (Coyne.)

39/6.

#### No. 8. PIN POINT TV TROUBLES IN 10 MINUTES. 31/6. See other advertisement on page 111.

#### No. 12. RADIO DESIGNER'S HANDBOOK. F. Langford-Smith. 11/6.

55/-.

#### No. 16. PRINCIPLES OF FREQUENCY MODULATION. B. S. Camier. 11/6.

21/-.

#### No. 11. PRINCIPLES OF TRANSISTOR CIRCUITS. S. W. Amos. 11/6.

21/-.

#### No. 20. PRINCIPLES OF SEMICONDUCTORS. M. G. Scroggie. 11/6.

21/-.

#### No. 10. TELEVISION RECEIVER SERVICING. Vol. 1. Spreadbury. 11/6.

25/-.

#### No. 17. ELECTRONIC COMPUTERS. Principles and Applications. T. E. Ivall. 2nd Edition. 25/-.

#### No. 15. WIRELESS SERVICING MANUAL. W. T. Cocking. 11/6.

17/6.

#### No. 38. COLOUR TELEVISION. NTSC System, Principles and Practice. P. S. Carrut, G. B. Townsend. 11/6. 85/-.

#### No. 21. BASIC MATHEMATICS FOR RADIO AND ELECTRONICS. 11/6.

17/6.

#### No. 23. INTRODUCTION TO LAPLACE TRANSFORMS. For radio and electronic engineers. W. D. Day. 11/6. 32/6.

#### No. 24. RADIO VALVE DATA. Compiled by "Wireless World". 11/6. 6/-.

18/-.

#### No. 25. THE OSCILLOSCOPE AT WORK. A. Haas and R. W. Hollows. 11/6. 42/-.

42/-.

#### No. 27. SECOND THOUGHTS ON RADIO THEORY. "Cathode Ray" of "Wireless World". 11/6. 25/-.

15/-.

#### No. 28. FOUNDATIONS OF WIRELESS. M. G. Scroggie. 11/6. 15/-.

## LIMITED OFFER! ACT NOW!

Just mail coupon for free trial. After 7 days send only low price or return books and pay nothing. If you keep more than one book, send £1 after 7 days and £1 each month until completed (maximum three books value not exceeding £5.0.0). To buy one book send one-half in 7 days, and one-half in 30 days.

#### To SIM-TECH BOOK COMPANY (U.K.)

Mail Order Division, DEPT. PTV15, Gaters Mill, West-End, Southampton, Hants.

Please send me the Elementary Radio TV Set as per special offer.

RUSH (insert Book number here) ( ) ( ) ( )

Tick here if enclosing full price, we pay postage (Coyne Books only). Same 7 day money-back guarantee.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

City \_\_\_\_\_ County \_\_\_\_\_

Postage charges: Orders under £3 allow 1/6. Over £3 allow 2/- extra. OVERSEAS ORDERS PROMPTLY SHIPPED on receipt of full amount. Same guaranteed satisfaction.

# TELEVISION TUBES RE-BUILT BY "RE-VIEW"

	PRICE:		
12in.	...	...	£4.10.0
14in.	...	...	£4.15.0
15in.	...	...	£5. 0.0
17in.	...	...	£5. 0.0
21in.	...	...	£7. 0.0

**SAVE £££**

Correct voltage heaters  
All types



## TWELVE MONTHS' GUARANTEE

*Free carriage and insurance*

*Cash with order or C.O.D.*

*Be one of our satisfied customers. Call and see our TUBES REBUILT and TESTED*

**RE-VIEW (London) LTD., 385 London Road, West Croydon, Surrey**

*Terms to the Trade*

*Tel.: THORNTON HEATH 1826*

# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

### Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee  
"NO PASS — NO FEE"**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

**BRITISH INSTITUTE OF ENGINEERING  
TECHNOLOGY (Incorporating E.M.I. Institutes)**  
(Dept. SE/20), 29 Wright's Lane, London, W.8

### WHAT IS YOUR PET SUBJECT?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

**GET SOME  
LETTERS AFTER  
YOUR NAME!**

A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.Prod.E.  
A.M.I.M.I.  
A.I.D.B.  
A.F.R.Ae.S.  
B.Sc.  
A.M.Brit.I.R.E.  
City & Guilds  
Gen. Cert. of Education  
Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio

Radio & Television Servicing  
Practical Electronics  
Electronics Engineering  
Automation

### INCLUDING TOOLS!

The specialist Electronic Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

**B.I.E.T.  
SCHOOL OF  
ELECTRONICS**



### POST COUPON NOW!

Please send me your FREE 156-page  
"ENGINEERING OPPORTUNITIES"  
 (Write if you prefer not to cut page)

NAME .....

ADDRESS .....

.....

.....

SUBJECT OR EXAM  
THAT INTERESTS ME

(SE/20)

**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**

