

Practical


MARCH 1962 1'9

TELEVISION

WESTWARD TELEVISION
--its development and progress



Build your own Aerials...

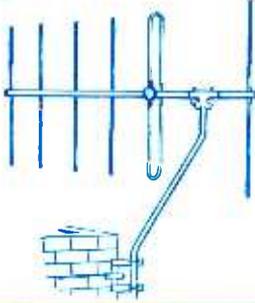

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M. Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:—

Fringevision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

All orders over £1 from January to August will be allowed a cash discount of 10%

EXPRESS ELECTRONICS

ROSEDENE LABORATORIES
KINGSWOOD WAY, SELSDON, SURREY

VALVES NEW TESTED AND GUARANTEED FOR THREE MONTHS

1C1	7/6	6BA6	6/-	8D3	4/-	1F96	8/-	EF41	8/-	PCL84	7/6
1C3	8/-	6BR26	7/-	12AH5	10/-	DH76	7/6	EF60	8/-	PL81	12/6
1F1	8/-	6BR16	5/9	12AT7	6/-	DH77	6/-	EF66	9/-	PL82	7/-
1F3	7/6	6BR6	5/9	12AU7	6/9	DH142	8/6	EF91	4/-	PL83	7/6
1FD1	8/-	6BR7	8/9	12AX7	6/9	DH150	10/-	EF92	5/8	PY-1	6/9
1FD9	7/6	6B47	10/6	12BE6	8/6	DK91	7/6	EL41	9/6	PY-2	7/6
1L4	6/9	6BV6	7/6	12BH7	10/6	DK92	7/6	EL84	7/-	PY-3	7/6
1P1	8/-	6BW7	7/-	12CK6GT	11/-	DK96	8/-	EM84	10/-	R19	11/6
1P10	7/6	6C10	9/-	12QZ7	7/6	DL92	7/6	EM85	10/-	U26	9/6
1P11	7/6	6D2	4/-	16A5	9/-	DL94	6/6	EY51	7/6	U32	7/6
1R5	6/-	6F12	4/-	25A6G	8/8	DL96	8/-	EY81	10/-	U56	7/6
1R5	8/-	6HR6T	2/-	25L6GT	7/6	EB91	4/-	EZ40	7/6	U75	5/-
1T4	7/6	6J7GT	7/6	25Z4G	8/-	EB41	10/-	EZ80	6/-	UB41	8/6
1U5	5/6	6K7G	5/6	30L1	7/6	EBF80	8/6	EZ81	6/9	UH42	9/6
3Q4	8/-	6K8G	6/-	30L1	7/6	EC081	6/-	KT33C	6/-	UP41	8/6
3R4	7/6	6Q7G	5/6	35L6GT	9/-	ECC82	6/9	KT66	11/6	UL41	8/6
3V4	6/6	6R17GT	6/-	35W4	8/6	ECC83	6/9	N17	7/6	UY41	7/6
3Y4	7/6	6SNTGT	6/-	35Z4GT	8/6	ECC84	7/6	N18	8/-	W76	8/6
5Y3HT	5/-	6Y3G	7/6	33K15	10/6	ECC80	8/6	N19	7/6	W142	8/6
5Z4G	8/6	6X4	5/-	5763	7/6	ECP82	8/-	N709	7/-	X17	7/6
6AK6	6/6	6X5G	5/-	80	6/-	ECH42	9/-	PCN84	7/6	X142	9/-
6AL5	4/-	6X5GT	6/-	DAF91	7/6	ECM81	10/-	PCF80	7/6	X150	9/-
6AM6	4/-	7B7	7/6	DAF96	8/-	ECL80	8/6	PCF82	7/6	Z77	4/-
6AT6	6/-	757	9/6	DF91	7/6	ECL82	9/-	PCL82	8/-	ZD17	7/6

High Stability Resistors 1W 5%, 50 Ω to 1M, 94. Midset Ceramics 500 v. 9d. Coax. Super quality 1in., 6d. yd., Floor P., & P. 1/6., 12in. P.M. Speakers 3 Ω 24/6. Baker's "Selhurst" 12in. 15 Ω 15W. 90/-, 12in. Stereo Model. 27.7.0.

VOLUME CONTROLS MIDGET SIZE LONG SPINDLES. D. P. switch 4/- Less switch 2/6. Values 10K to 2M, B9A B7G v. holders 8/-, screens 9d.

VALVES MATCHED IN PAIRS

EL84 17/-, N709 17/-, 6V6G 17/-, 6BW6 18/- per pair. Push Pull O.P. Transformers for above 3-15 Ω 14/6. P. & P. 1/6., 12in. P.M. Speakers 3 Ω 24/6. Baker's "Selhurst" 12in. 15 Ω 15W. 90/-, 12in. Stereo Model. 27.7.0.

SETS OF VALVES

DK91, DF91, DAF91, DL92 or DL94L	19/6	EH42, EF41, EBC41	
DK96, DF96, DAF96, DL96	27/6	EL41, EZ40	37/6
1C3, 1F1, 1FD1, 1P1	27/6	UCH42, UP41, UBC41	
1R5, 1T4, 1U5, 384 or 3V4	19/6	UL41, UY41	35/-

Postage and packing 9d. Over £1 post free. C.O.D. 2/-.

THOUSANDS

OF SATISFIED PEOPLE

VIEW ON **E.M.S.**

REBUILT TELEVISION TUBES

- ★ A NEW GUN IN EVERY TUBE
- ★ BUY DIRECT FROM THE FACTORY
- ★ 18 MONTHS' GUARANTEE

12 inch £5.0.0 14 inch £5.10.0
17 inch £6.10.0

Immediate dispatch on receipt of Remittance
 Carriage and insurance 12/6 extra
£1 Refunded on receipt of your old Tube

For the benefit of South Coast customers we have an agent in BRIGHTON. See our classified advertisement for further details.

SPECIAL TERMS TO THE TRADE

MARSHALL'S for TELEVISION LTD.

131 St. Ann's Road, Tottenham, London, N.15
STAMFORD HILL 3267 & 5555

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the *RIGHT* course:

- RADIO & TELEVISION ENGINEERING
- INDUSTRIAL TELEVISION
- RADIO & TELEVISION SERVICING
- RADIO SERVICE AND SALES
- VHF/FM ENGINEERING : ELECTRONIC COMPUTERS & PROGRAMMING

ICS provides through coaching for professional examinations:


- Brit. I.R.E., City and Guilds Telecommunication Technicians, C. & G. Radio & TV Servicing (R.T.E.B.); C. & G. Radio Amateurs.

LEARN AS YOU BUILD

Practical Radio Courses

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-meter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.

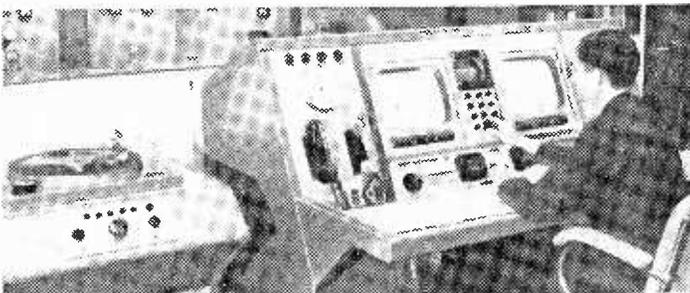Technical Training in Radio, Television and Electronics Engineering with



THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include: MECHANICAL, MOTOR, FIRE, ELECTRICAL & CHEMICAL ENGINEERING. FARMING, GARDENING. ARCHITECTURE & WOODWORKING. SELLING & MANAGEMENT. ART. PHOTOGRAPHY, etc., etc.

PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . .

INTERNATIONAL CORRESPONDENCE SCHOOLS

(DEPT. 165), INTERTEXT HOUSE, PARKGATE RD., LONDON, S.W.11

PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

.....

OCCUPATION..... AGE.....

3.62

REPLACEMENT TUBES

**REBUILT CATHODE RAY TUBES ARE NOW USED BY
OVER 80% OF RETAIL SERVICE DEPARTMENTS
AND RENTAL ORGANISATIONS**

**FOR QUALITY, RELIABILITY AND SERVICE BUY FROM BRITAIN'S
LEADING GROUP OF INDEPENDENT MANUFACTURERS OF REBUILT
CATHODE RAY TUBES**

SUFFOLK TUBES LIMITED
1/3 UPPER RICHMOND ROAD
PUTNEY, S.W.15.
Tel: Vandyke 4304/5267

MIDLAND TUBES LIMITED
37 GEORGE STREET
MANCHESTER, 1.
Tel: Central 4568/9

VIDEO REPLACEMENTS LIMITED
25 ADDINGTON SQUARE
CAMBERWELL, S.E.5.
Tel: Rodney 7550/7559

ALL TYPES - KEEN PRICES - PROMPT DELIVERY
WRITE FOR BROCHURE

Scotts Radio Ltd.
4 Church Street
Brighton
Tel: Brighton 26891

Weston Hart Ltd.
236/8 Fratton Road
Portsmouth
Tel: Portsmouth 24125

Lawsons Ltd.
36 Cornhill
Bury St. Edmunds, Suffolk
Tel: Bury St. Edmunds 3304

J. H. Sunderland
11 Clements Street
Rochdale, Lancs.
Tel: Rochdale 48484

Wizard Productions
16 Withy Grove
Manchester
Tel: Dea 2772

J. Charlesworth & Son
14 Hightown
Crewe, Cheshire
Tel: Crewe 2535

Taylor's
162 Eastney Road
Milton, Portsmouth
Tel: Portsmouth 35000

Millards Southern Rentals
3 High Street
Aldershot, Hants.
Tel: Aldershot 20408

Lucketts of Banbury
57a/58a High Street
Banbury, Oxon
Tel: Banbury 2813

Snell & Sons Ltd.
204 High St.
Swansea
Tel: Swansea 50518/9

H. Knowles
54/56 Chester Road
Manchester
Tel: BLa 9031

Radio Services Ltd.
30 Mona Street
Amlwch, Anglesey
Tel: Amlwch 594

Hi-Lite Ltd.
89 Southbourne Grove
Southbourne, Bournemouth
Tel: Bournemouth 44344

R. Watson
Leathern Bottel
Wavenden, Woburn Sands, Bucks
Tel: Woburn Sands 2027

R.E.S. Ltd.
17/19 Paynes Lane
Coventry
Tel: Coventry 28781

Radiovision of Glamorgan Ltd.
Nolton St., Bridgend
Glam.
Tel: Bridgend 2727

J. Wildbore Ltd.
6-12 Peter Street
Oldham
Tel: Mai 4475

R. L. Television Services Ltd.
33 Charles Street
Cardiff
Tel: Cardiff 26337/8

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE. ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. TELEPHONE AND TELEGRAM ORDERS FOR CASH ON DELIVERY SERVICE ACCEPTED UP TO 3.30 P.M.

Table listing electronic components such as diodes, transistors, and resistors with their respective part numbers and specifications.

PLEASE NOTE THAT WE DO NOT SELL SECONDHAND GOODS OR MANUFACTURERS' REJECTS

MICROPHONES (All with Screened Cable.) Post 1/6 each.


Viceroy, Xtal Studio, 45/-; Stand 15/-; GBC Mic24, Stick type, metal case with switch, 36/-; Romagna Xtal, for hand or desk, 19/6. Acos type 40, hand or desk, 15/-; Acos type 45, metal case, black crackle finish, 25/-. Acos type 39/1, Stick type, 32/6. Eagle type M178, chrome lapel mike, Xtal, 18/-; Eagle, type DM175, Miniature dynamic M.C., 49/6. Tie-pin mike, 32/6. Sub-miniature earpieces (suitable for transistor sets, etc.), high impedance with jack and cord, 9/6. Low impedance with ear clip, less jack, 7/6.

ALL GOODS BRAND NEW, SUBJECT TO FULL MAKERS' GUARANTEE, AND ACTUALLY IN STOCK.

Table listing various electronic components including volume controls, metal rectifiers, silicon rectifiers, electrolytic condensers, and wire-ended tubular components.

Examine it
FREE
on 7 DAYS'
APPROVAL

RADIO, TELEVISION & ELECTRICAL REPAIRS

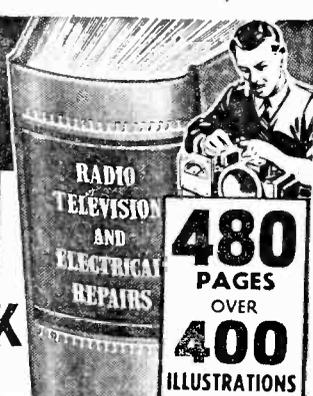

AMAZING 'KNOW HOW' BOOK *Saves You Pounds*

Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install lighting points, or repair any domestic appliance, from a bell or an iron to a vacuum cleaner or washing machine. Explains basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults, carry out maintenance and repairs by the most modern methods. Special section on frequency modulated receivers. See this great volume NOW on 7 days' FREE TRIAL. Yours (if kept) for 21/- (Standard Edition) or 23/- (De Luxe, leathercloth). Or on Easy Terms: 5/- down, and 3 monthly payments (total credit prices: Std. 22/-; De Luxe 24/-).

ESSENTIAL TO EVERY SERVICE ENGINEER, ENTHUSIAST AND HANDYMAN !

Getting the best from RADIO AND TV SETS

Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set.

All you need to know about DOMESTIC WIRING




Learn from these helpful pages how to carry out all kinds of installations and extensions—with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.

BASIC RADIO CIRCUITS

All you want to know about circuits, so that you can find your way around modern sets without hesitation. How components form various types of set: gives circuits for 1-valve receiver, 3-valve receiver, battery TRF receiver 4-valve superhet, Universal sets, etc.

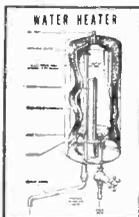See how to maintain
**Vacuum Cleaners
and Floor Polishers,
Refrigerators, Cookers
and Boiling Plates,
Washing Machines, etc.**
Do your own
BATTERY CHARGING
Here are clear, complete instructions.



FIRES & SPACE HEATERS


Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!

TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from how to carry out Preliminary Tests to how to align R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the causes of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loudspeakers and how to deal with any faults that may develop.

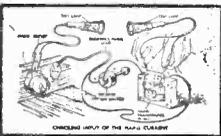

ALL THIS—AND MORE IN ONE GREAT VOLUME!

Comprehensive Contents Include

Current, Voltage and Resistance. Coils, Capacitors and Valves. Basic Radio-Receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers. Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-Amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging. Testing and Repairs, etc.

DO THIS NOW!

Fill in form and post in 2d. stamped, unsealed envelope. Book comes to you on FREE APPROVAL; if satisfied you send remittance, otherwise return book in 8 days. Approval offer applies in U.K. only, closes Mar. 31. Eire customers please remit full cash with order—refunded in full if not completely satisfied.

POST FORM TODAY!

To: Dept. H.F.35 Odhams Press Ltd., Basted, Sevenoaks, Kent.

Without obligation to purchase, please send me "Radio, Television and Electrical Repairs" in Edition indicated. Within 8 days I will either return book in good condition, postage paid OR remit full cash price. Alternatively, I will send correct down payment as detailed in advertisement. Cross out Edition NOT wanted: STANDARD/DE LUXE, Delete Words NOT applicable. I wish to pay CASH/BY TERMS. I am (a) houseowner (b) tenant in house or flat (c) temporary resident (d) single (e) married (f) over 21.

Signature _____
(If under 21, signature of parent or guardian)

BLOCK LETTERS BELOW

NAME _____
Full Postal
ADDRESS _____

H.F.35/March, 1962

Practical Television

AND TELEVISION TIMES

VOL. 12, No. 138, MARCH, 1962

Editorial and Advertisement
Offices:

PRACTICAL TELEVISION

George Newnes Ltd., Tower House
Southampton Street, W.C.2.

© George Newnes Ltd., 1962

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission
by Canadian Magazine Post.

SUBSCRIPTION RATES

including postage for one year

Ireland - - - - £1.50 per annum
Abroad - - - - £1.36 per annum
Canada - - - - £1.20 per annum

Contents

	Page
Editorial	269
Self-powered Band I Sound Receiver	270
Telenews	274
How TV Sets Work	276
A Band V Receiver	279
Intercarrier Sound	281
Servicing Data and Modifica- tions	285
Westward Television	288
Transistorised Sync Separators	291
Underneath the Dipole	293
Television Filters	295
Letters to the Editor	299
Your Problems Solved... ..	300

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Television Developments

WHILST it would be wrong to try and anticipate the findings of the Pilkington Committee it is felt that the time is approaching when the transmitting authorities should be able to give us some indications as to possible definite developments which might be expected to take place in the television fields. Apart from the news that Bands IV and V are to be brought into use at a later date, no really definite construction data has, so far as we are aware, been made available for the man in the street. Details have, of course, been circulated to the trade in order that they may experiment with the design of receivers, but it is conceivable that when the findings of the Committee are made known, the present trends in receiver design may have to be modified. If the lines of experiment are unlikely to be changed, then some definite information should be made more generally available. Most of the bigger firms, in the course of their experimental and development work, make various discoveries which are of general interest, and they make these available to everyone by issuing what are known as Application Reports, and we do, in fact, publish extracts from these from time to time. It would be a good idea if the BBC and the ITA would produce some similar type of information so that experimenters other than those directly employed in the trade, could make experiments, or at least read and study the lines upon which development is proceeding.

Other than knowing that the N.T.S.C. system is being used as the basis for a British colour system, we feel that some further data should now be forthcoming. We also feel that a situation similar to that which arose originally when the Baird 30-line system was gradually supplanted by the present system of television should not again be tolerated, and we should not have to run two or more systems for various periods whilst the public judge which is the better system. A final decision should be made at a really high level and the system chosen should be introduced as a working arrangement which will not carry the risk of having to be modified at some future date because of improvements in circuitry or changes of technique, in the same manner as the line definition standards in use in this country.

NEW P.W. BLUEPRINTS

NEXT month sees the issue of the first of a new series of blueprints by our companion journal *Practical Wireless*. These new designs have been produced to cover the requirements of the absolute novice as well as the advanced constructor, and to this end they are produced in a double-sided form. On one side is a receiver for the beginner, whilst the design on the other side is for the more advanced constructor.

The first double-sided blueprint is presented with the April issue of *Practical Wireless*. The design for the beginner is a battery-operated S.W. receiver, and for the advanced enthusiast, a four-transistor portable. More free double-sided blueprints will be presented with the May and June issues of *Practical Wireless*.

Our next issue, dated April, will be published on March 22nd.

self-powered BAND I sound receiver

By J. B. Willmott

(Continued from page 238 of the February issue)

WHEN the signal has been amplified by V1 and V2 it is then passed via the R.F. transformer L5/L6 to the signal diode in V3 (see Fig. 1 last month), which is an EBC33 valve (a 6Q7 would probably work equally well in this position without change of circuit values). Demodulation takes place, and the A.F. voltage is developed across R6, which is returned to the cathode of V3. Filtering of the R.F. component is carried out by R5, C7 and R7, whilst C6 acts as D.C. blocking capacitor. The filtered A.F. signal is applied to the "top" of VR1, the volume control, the slider of which taps off the desired level of A.F. signal for application to the grid of the triode portion of V3. Considerable A.F. amplification takes place, and the signal is then

conveyed by resistance-capacity coupling (R9 and C9) to the grid of the output valve, V4, which is a beam tetrode (6V6).

It will be noted that as no AVC is considered necessary in a simple unit of this type, the second diode of V3 is not used, and is connected to "earth". The output from V4 is fed by the conventional output transformer T1 to the loudspeaker. Top-cut tone control is provided for by C10 and VR2 in the anode circuit of V4.

The correct amount of fixed bias is provided for V1 and V2 by R1/C2 and R3/C4 respectively, and with only two stages of R.F. amplification, there is no danger of overloading, even when used very near to a Band I transmitter. Biasing for V3 and V4 is provided by R8/C8 and R11/C11, the capacitors being of the electrolytic type. In areas of high signal strength, the effect of omitting C11 can be tried, as this will provide a degree of negative feedback, with a consequent improvement in quality of reproduction, but of course with some loss of output.

Owing to the use of screened coils for the R.F. circuits, the prototype receiver was found to be completely stable in operation, without recourse to elaborate decoupling of H.T. supplies, or the use of heater chokes and decoupling capacitors, as was required in so many early TRF TV receivers. Resistors R2/C13 and R4/C14 provide the necessary amount of decoupling for the R.F. stages, and thus it can be seen that only a minimum of components is required, and wiring is quite simple.


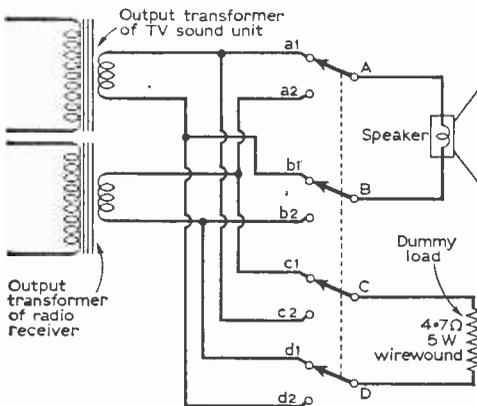


Fig. 3 (above)—The circuit switching to provide change-over of loudspeaker from the TV unit to radio output and dummy loading of the channel not in use.

Fig. 4 (right)—The wiring of a 4-pole 2-way switch for the circuit of Fig. 3.

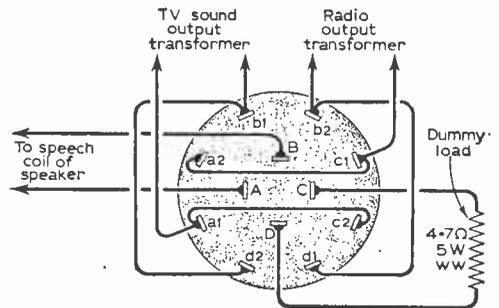

Short and direct wiring is of course essential, and the principle of "single point earthing" of screen and cathode decoupling and biasing components, as shown in the circuit diagram, is very important. Soldering tags are mounted on the valvoholder fixing bolts as shown in Fig. 5, to facilitate this, and the wiring of the H.T. supply is made easy by the use of a tagstrip.


The Power Supply

The power supply should present no problems, and whilst the components used in the prototype are specified in the parts list, there is no reason why any similar suitable components should not be used, provided their physical shape and size allows for their being accommodated in the space available. The mains supply is fed to the correct tapings on the primary of T2 (via the on/off switch). Secondary windings provide the requisite 5V to feed the heater of the rectifier V5 (a 5Z4), and 6.3V to feed the heaters of the other valves, the total heater consumption of which (1.25A) is well within the transformer rating.

It will be noted that one side of each valve heater is earthed, and thus only one lead, carrying the 6.3V supply has to pass from stage to stage. The H.T. secondary of T2 is rated at 250-0-250V, 80mA, and this again is adequate for the requirements of the circuit. Full-wave rectification, followed by smoothing by means of the L.F. choke L7 and double section electrolytic capacitors C12 A/B, ensures a satisfactory low hum level. It may possibly be found in certain districts that "modulation hum" is troublesome, i.e., "hum" is audible

Preparation of the Chassis and Mounting the Components

Work should be begun by drilling all holes in the chassis, using the dimensions shown in Fig. 2 (page 238 last month). The chassis is a standard size component, and can be obtained ready folded from advertisers in this magazine. The drilling layout is shown as it would appear when looking at the chassis from above, with the end and side runners opened out for clarity. It is a good plan to use the actual components as "templates" for marking out the fixing holes. These must be fixed so that their locating spigots are in the direction indicated.

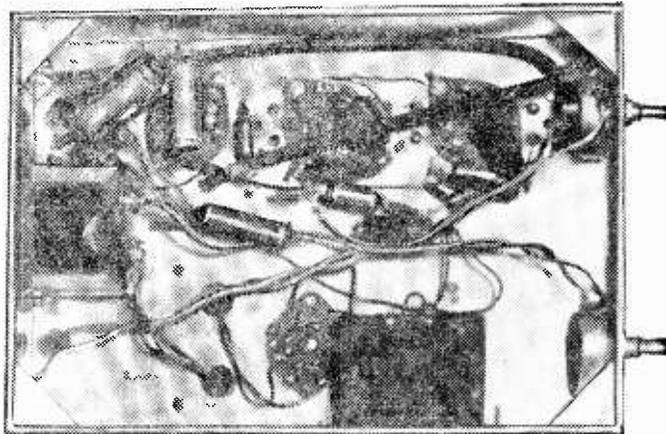

An underchassis view.

The most tedious part of the drilling is without a doubt the provision of the "groups" of holes to accommodate the R.F. coils, and it is essential that this be carefully and accurately carried out, or trouble will almost certainly ensue from lead-out wires contacting the chassis, and as some of these wires carry H.T. voltages, serious breakdown could result.

In the writer's opinion, it is well worthwhile preparing a template from which to drill these "groups" of holes. A friend whose hobby lies in the realm of model engineering, was persuaded to produce an accurately drilled template in mild steel, about 1/4 in. thick. The central hole of each coil group was then drilled in the chassis, and the template rigidly bolted into position with a 2B.A. bolt and nut. The remaining holes in the "group" were then drilled, through the appropriate holes in the template, and the process repeated at each "group" position. The work thus proceeds rapidly and without risk of error, and if any further amount of TV construction is envisaged, the time in providing this template will be repaid over and over again.

The clearance size of all holes is clearly given in Fig. 2. Having completed all drilling, the first action can be to place rubber grommets in the three holes on the chassis top which convey leads to and from the mains transformer. A further grommet is required in the hole on the rear chassis runner which provides for the mains supply lead.

Coil Winding Data			
Channel	L1 turns	L2 turns	L3 turns
1	2	7	3
2	2	6	3
3	2	6	3
4	2	5	3
5	2	4	3
Channel	L4 turns	L5 turns	L6 turns
1	8	3	8
2	6	3	6
3	6	3	6
4	5	3	5
5	4	3	4

as soon as the receiver is brought into tune with the local BBC transmitter. This is easily cured by wiring a good quality mica capacitor of 0.002µF or 0.005µF (at least 750VWV) between the end of the mains transformer primary which is connected to the on/off switch (the "bottom" of the winding as shown in Fig. 1) and chassis (earth).

Mounting of the components can now proceed, and the following order is recommended. First mount the mains transformer, T2, on top of the chassis in the rear right-hand corner. This may have the various windings terminated by connecting tags or wires, and it should be mounted so that the connections to the primary winding are nearest the chassis rear. A soldering tag should be included on the right-hand fixing bolt at the front (nearest the end of the chassis containing the control spindle mounting holes), this will form a convenient anchoring point for certain secondary winding terminations which are ultimately connected to chassis (earth). Now mount the smoothing choke, below chassis, on the side runner, followed by the output transformer, on the rear runner, as shown in Fig. 5. Follow this by mounting the double section electrolytic C12A/B on top of the chassis, with its terminating tags projecting below chassis, using the standard type of fixing clip to secure it in place.

The international octal type valveholders for V3, V4 and V5 can now be fixed, taking care to orientate the locating spigots in the directions shown in Fig. 5. A 6B.A. soldering tag should be mounted (beneath the chassis, of course) on the fixing bolt nearest the locating spigot of the valveholders for V3 and V4. The valveholders for V1 and V2 can next be bolted in position (there are of the larger "B9G" pattern), and in this case, the valve retaining clips are mounted on the fixing bolts above chassis level, and a 6B.A.

soldering tag below chassis on the bolt nearest the locating spigot.

The coaxial aerial socket is now mounted on the rear chassis runner, a 6B.A. solder tag being included on one of the fixing bolts; and the volume and tone controls are fixed on the front chassis runner (the volume control on the "V1" side of the chassis, and the tone control on the "V5" side. Tagstrips can now be bolted into the indicated positions, and this leaves only the R.F. tuning coils to be mounted; these have been purposely left until last, as they require fairly careful handling.

Winding the R.F. Coils

Attention should now be turned to the manufacture of the three R.F. coils. These are wound on standard "Haynes" type formers. On examination, it will be found that each of the four corner holes in the base of the former contains a brass eyelet, and it is through these that the coil terminations pass. A 3in. length of 22s.w.g. tinned copper wire is passed through each hole, so that about half its length projects either side of the base, and is held in position with a small blob of solder on the upper surface of the eyelet (i.e., the side which will be inside the screening can when the coil is completed). Examination of the underside of the coil former will show the existence of reference numbers for each terminating lead, the corner leads being numbered 1, 3, 4 and 6;


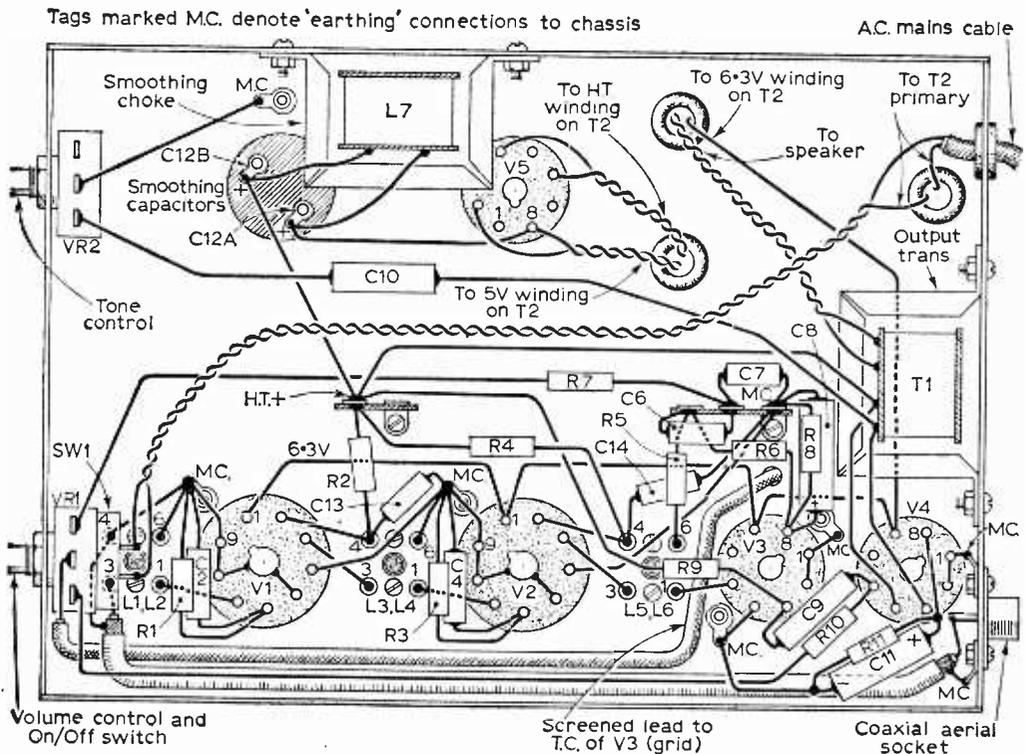


Fig. 5—The underchassis wiring.

numbers 2 and 5 are not used in the design under consideration. These numbers are referred to in the winding instructions, and this nomenclature must be followed.

Start with the aerial input coils L1/L2, which are wound in the following manner. Using 32s.w.g. double silk covered wire, and leaving some 2in. spare for connecting purposes, begin opposite pin 6, about 1in. up from the base of the former, and wind on the requisite number of turns for L2 as shown in the coil winding data table, spacing the turns by a gap equal to the wire diameter. Hold the wire firmly in position, and brush on a layer of coil dope. This will quickly dry and hold the winding firmly. Leave about 2in. of wire for connecting purposes.

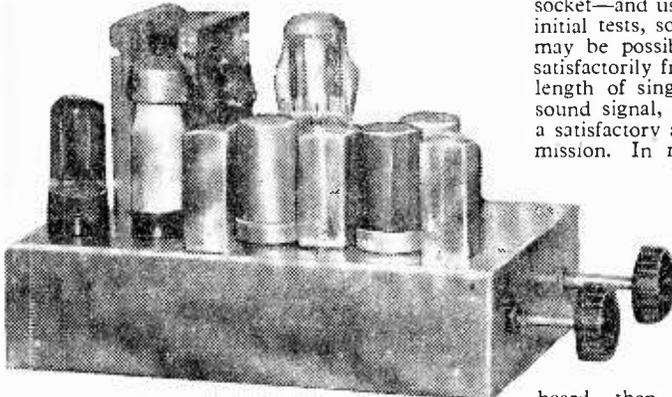Now proceed to wind the primary, L1, starting at pin 4, and placing the turns in between the bottom turns of L2, wind on the number of turns indicated. Fix with coil dope. When satisfied that correct number of turns have been wound, and that the windings are securely held by the coil dope, cut and clean the insulation from the ends of each winding and solder them to their respective "pins", viz.



A view of the finished unit.

bottom of L2 winding to pin 6, top to pin 1; bottom of L1 to pin 4, top to pin 3. Solder the small fixed capacitor C1 between pins 1 and 6 in such a way that it will not touch the inside of the screening can when this is fitted. Make absolutely certain that windings have been correctly terminated, then wrap one turn of oiled silk or cartridge paper around the completed assembly (to provide insulation between the windings, etc., and the screening can), and place in the screening can.

It is a good idea to mark the can "L1/L2" clearly for future identification, it is very easy to mix the three coils up if they are laid side by side on the bench in their unmarked state, prior to fixing on the chassis.

The construction of L3/L4 and L5/L6 can now proceed, in a similar manner, referring to the winding table for details of the number of turns required for each coil. Note that in the case of these coils, the tuned secondary winding is started at pin 6 and terminated at pin 1, and the primary (coupling) winding starts at pin 3 and terminates at pin 4, this latter winding lying between the bottom (earthy) turns of the tuned winding. Do not omit C3 and C5 across the secondary windings.

The prototype receiver was constructed to operate on the Peterborough transmitter, Channel 5, and

the numbers of turns specified in the winding table were those actually used. The data for other channels has been arrived at by calculation, and with the variation of tuning available by adjustment of the coil cores, it should in every case be possible to tune the desired channel, provided the data is used and the windings neatly made and firmly secured. Having wound the coils, insert the iron dust core into each former, using a non-metallic tool (the sharpened end of a plastic knitting needle is ideal) until the core is just about to "engage" the top of the tuner winding in each case. Taking care that the orientation of each coil is correct, as shown in the under-chassis diagram (Fig. 5), they may now be secured by bolting them to the chassis.

Before proceeding with the wiring, it is a good plan once again to check the layout and position of all components so far fitted.

After the wiring has been completed and checked, the constructor may proceed with the alignment.

Alignment Instructions

Insert the TV aerial plug into the coaxial aerial socket—and use a good, efficient TV aerial for these initial tests, so that a strong signal is available. It may be possible later to make the receiver work satisfactorily from a simple indoor aerial, or even a length of single wire, but when searching for the sound signal, success obviously depends on having a satisfactory aerial on which to pick up the transmission. In many cases, the TV sound will be

audible as soon as the aerial is connected, and in that case it is only necessary to screw in the cores of L6, L4 and L2 (in that order) to the position of maximum signal.

If, however, nothing can be heard at first, screw in each core by one turn, and listen carefully; if there is still no sound, screw in each core a further turn, repeating the process until the signal can be heard, then peak it up as required by adjustment of the cores. In the prototype receiver, operating at a distance of eight miles from the low power transmitter at Peterborough on Channel 5, using a single dipole aerial at roof level, more than ample volume was obtainable. If it is found that any of the coils fails to "peak" correctly, adjustment to the number of turns in the tuned winding is necessary. If the core is fully screwed in before a "peak" is reached, there is insufficient inductance in circuit, and the effect of adding one turn to the coil in question should be tried. Conversely, if the coil core has to be fully unscrewed in an attempt to find the "peak", a turn (or turns) will have to be removed from the winding in question. When correctly aligned, the receiver should give really good quality reception, and the tuning should be sufficiently sharp to prevent any trace of break-through of the vision channel (which sounds somewhat like a rough mains hum).

Mention was made at the commencement of this article of the use of a switch whereby the loud-speaker can be switched to the output from either this receiver, or one of the existing output channels of an already existing stereogram, and in Figs. 3 and 4 this is shown both in theoretical form and as a practical wiring diagram, using a 4-pole 2-way wafer switch. This can be easily fitted as an optional extra if so desired.

Telenews

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of December, 1961, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London	1,952,323
Home Counties	1,835,147
Midland	1,746,932
North Eastern	1,861,786
North Western	1,522,623
South Western	989,136
Wales and Border Counties	793,800
Total England and Wales	10,421,777
Scotland	1,063,468
Northern Ireland	172,259
Grand Total	11,657,504

Outside Broadcast/Videotape Recording Vehicle

BUILT for use on the Continent of Europe is a Marconi mobile four-camera television outside broadcast and Videotape recording unit.

The unit has been manufactured for InterTel, N.V., a new television programme recording organisation operating throughout Europe.

The complete unit consists of two semi-trailer vehicles, one housing the camera channels and associated equipment and the other the Ampex Videotape recorders. Each is towed by a 7-ton Bedford long wheel-base tug.

Although in the form of two separate vehicles, each with its own prime mover, the television and Videotape recording units are designed to operate in conjunction whilst on the move.

InterTel, N.V., of Amsterdam, Holland, is the holding company of an international group of InterTel companies engaged in the production of television programmes on an international basis. These companies are at present located in Paris, Brussels,

Munich, London and New York, and further ones will be incorporated in the immediate future in Rome, Madrid and Stockholm.

Wired Television for Newcastle


NEARLY 100,000 people will soon be able to receive good quality television pictures for the first time, when a wired television system now under construction just north of Newcastle-upon-Tyne comes into operation. Reception by normal outdoor aerials in this area is far from perfect, and in many places it is almost obliterated by massive steel pylons carrying National Grid overhead power transmission lines.

At first the systems, supplied by EMI Electronics Ltd. and operated by the Seaton Valley Relay Company, will be available to some 33,000 inhabitants of


Seaton Valley and to some 11,000 in Newbiggin-by-the-Sea. At Seaton Valley future plans include extending the system to the new town now being built at Cramlington, where eventually a further 50,000 population, mostly overspill from crowded parts of Tyneside, are to be housed.

EMTS wide band television system will be supplemented throughout by the Relay Company's existing four programme sound relay service which is being modernised and extended as the wired television system is developed.

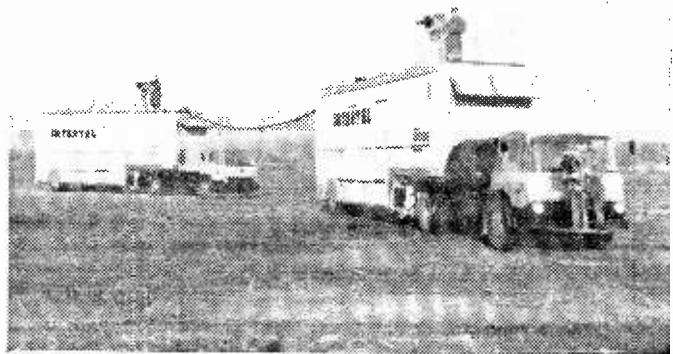When the new wired system is installed, all the existing aerials can be dispensed with, and viewers will be able to obtain high grade reception on their existing receivers of the BBC Northern TV programmes in Band I; ITV Border and Tyne Tees pro-



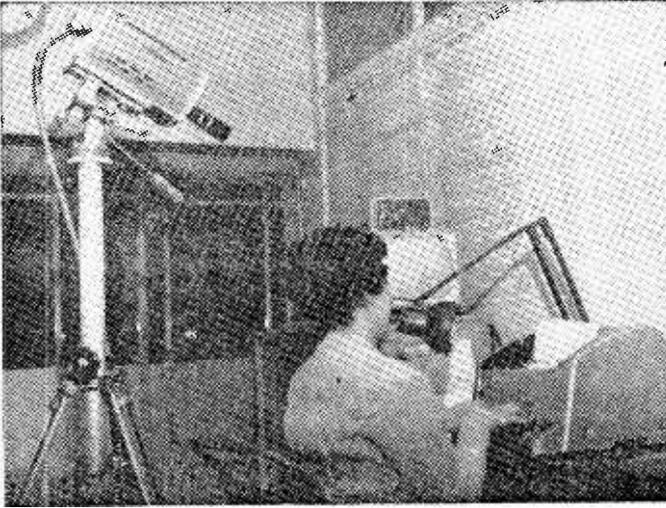This Marconi mobile 4-camera television outside broadcast and Videotape recording unit is designed to operate whilst on the move, and a 20ft cable harness with special spring tension arrangements is used to connect the two vehicles.



A 27in. television screen which is linked to teleprinter equipment, came into experimental operation in January, at Paddington Station, London. The screen relays to travellers the latest information and arrangements.

grammes in Band III; BBC Home, Light, and Third sound programmes and Radio Luxembourg picked up direct and re-distributed at VHF in Band II. Signals will be transmitted from equipment at the base of a centrally situated aerial tower, along coaxial cable to the receiving sets in peoples' homes. EMI Electronics Ltd. will supply all equipment required for distribution.

Wired Television for Abingdon

RESIDENTS of Abingdon in Berkshire, a fringe area for television reception, have always been troubled by bad interference and fading pictures. Now Master Vision Ltd. — a group of local business and professional people — will use EMI Electronic's wide-band equipment to install a wired television system to overcome these difficulties.

EMI aerial arrays, mounted on a 164ft mast, will cover Bands I, II and III. Although Abingdon is over 50 miles from the nearest television transmitter, some 4,000 homes will be able to receive strong, clear pictures on BBC London and Midland TV programmes; London, Midland and Southern ITV; BBC VHF Home, Light and Third sound programmes, and Radio Luxembourg, which will be received direct and

redistributed in the VHF band.

Signals picked up by the aerials will be approximately ten times stronger than those received on private aerials at roof height. When received by subscribers, along a protected cable route, they will produce very high quality vision and sound.

Viewers will also be relieved of the cost, erection and structural problems of individual aerials, both for present programmes and future developments. Extra Channels, colour television, pay TV and the much-discussed 625-line standard can all be received by the system.

Alteration to Trade Test Schedules

THE Independent Television Authority announces that trade test transmissions from its Croydon, Mendlesham, Caradon Hill and Stockland Hill stations are now radiated on half power on Friday mornings. These stations return to full power at 1 p.m. or the start of programme transmissions, whichever is the earlier. At the Black Hill and Durris stations trade tests are radiated on half power on Monday mornings, again returning to full power at 1 p.m. or the commencement of programmes. At these stations transmitters are operated in parallel and these

arrangements are necessary to enable half the station to shut down each week for maintenance purposes.

During January there were no trade tests from the Croydon transmitter on Tuesday and Thursday mornings. On these days test transmissions commenced at 12 noon. This was necessary to enable aerial tests to be carried out in preparation for the construction of the Authority's new station at Fremont Point in Jersey.

Studio Equipment for Channel Islands

INDEPENDENT television will come to the Channel Islands — which have a population of 111,000 — in the Autumn of 1962. Channel Television, contractor for the new station, which will serve the six main islands from St. Helier, Jersey, has placed the major contract for the supply of all the principal items of studio equipment with EMI Electronics Ltd.

These comprise two studio vidicon cameras, vision and sound mixing equipment, two telecine machines and most of the master control room equipment.

The telecine equipment will employ the same type of cameras as those used in the studios, which makes for flexibility and economy of spares.

This station will be the smallest in the British Isles and many items of equipment will be designed for operation by a minimum staff. For example, joystick control of the camera channels enables them to be operated from the master control room, instead of from the studio control room.

TV at Paddington Station

THE travelling public at Paddington railway station, London, can now read of any alterations made to the times of trains on a 27in. television receiver. The receiver is linked, by closed circuit television, to teleprinter equipment, upon which the alterations are typed, and therefore the public receives the information at the earliest possible time.

During the severe weather in January, when train services were disrupted, hundreds of passengers first learned of the delays from the receiver.

HOW TV SETS WORK - 4 : The line circuits

(Continued from page 222 of the February issue)

WE now come to the line oscillator, line output, boost diode and EHT sections of a typical receiver, and in Fig. 4 is given the circuit of these stages. Here V5B is the line blocking oscillator valve (part of a triode-pentode), V7 the line output valve, V8 the boost diode and V9 the EHT rectifier valve.

Line Blocking Oscillator

Starting with the line blocking oscillator, we find that transformer T101 is the major component. This is called the "blocking oscillator transformer". It is this stage (V5B) which provides a suitable drive signal for the line output valve, so that the latter stage can cause the scanning spot of the picture tube to be deflected horizontally across the screen (to produce the scanning lines).

It will be seen that the primary of T101 is connected to the grid circuit of V5B while the secondary is connected to the anode circuit. The phasing of the transformer wiring is such that the valve is caused to oscillate. The coupling provided by the transformer is sufficient to cause vigorous oscillation.

When the set warms up after switching on, the current in the anode winding of the transformer rises, and a large voltage pulse is induced across the grid winding, which swings the grid positive. This results in a further increase of anode current and a rapidly increasing positive pulse at the grid. The resulting grid current in R131 charges up the grid blocking capacitor C120 and swings the grid negative. When there is sufficient charge in C120 the anode current is cut off. During the time that C120 is charging, the rate of change of current in the anode winding decreases and the grid drive collapses.

Repetition

The valve is now cut off and there is no current in the anode winding and no pulse voltage across the grid winding. This state of quiescence continues until the charge in C120 has leaked away through R131. As the charge in C120 decays, a progressive increase of anode current occurs again in the anode winding of T101, and the cycle of events is repeated.

During the time that V5B is in the condition of anode current cut-off, capacitor C121 charges through R135, and an exponential build-up of voltage begins across C121. However, before C121 has time fully to charge, V5B is caused vigorously to conduct, which immediately discharges C121. Thus, C121 charges through R135 during the quiescent periods of the "blocking oscillator" cycle, and the rate of discharge of C121 is controlled by the repetition frequency of the blocking oscillator.

How much charge C121 acquires when the blocking oscillator is cut off depends on the time-constant R135 and C121, and the time-constant is usually arranged so that only a small portion of the initial linear part of the charging cycle is used (see Fig. 5).

Two Time-Constants

We thus have two time-constants, that of the blocking oscillator proper and that of the anode circuit of the blocking oscillator valve. Let us deal with the former first.

So far, we have cited C120 and R131 as the blocking oscillator time-constant components. These govern the repetition frequency of the blocking oscillator. However, the speed at which the charge in C120 is exhausted is governed also by R132 and R133. It will be recalled that the charge at the grid side of C120 is negative. Thus, by applying a positive potential, the negative charge is more speedily overcome and the effective time-constant is increased.

This happens by virtue of R132 and the line hold control R133, and the amount of positive voltage applied to the grid can be controlled by the line hold control. The line hold control, in fact, serves in this respect as a "variable time-constant" control. Clearly, then, the repetition frequency of the oscillator can be adjusted by means of the line hold control.

Range of Control

So that sync may be achieved by the line sync pulses, the repetition frequency must be very close to 10,125c/s, and it should be possible to establish that frequency with the line hold control near to the centre of its range. If this does not happen,

then the picture will not lock horizontally on the screen. We can realise now, then, that this could be caused by alteration in value of R131, C120, R132 and R133 (not so much the latter because it is variable).

Anode Circuit Time-Constant

The suppressed sawtooth waveform across C121 due to its small charge and subsequent discharge represents the drive signal for the line output valve. What happens if that time-constant alters?

Let us suppose that it increases, which is what usually happens owing to R135 or C121 increasing in value. C121 would start to charge through the increased value of R135, but before C121 arrived at the correct charge, the blocking oscillator would conduct and result in its discharge. Thus, the line drive signal would have insufficient amplitude to drive the line output valve fully, and a reduced horizontal scan would result.

Horizontal non-linearity may also set in because the user may endeavour to secure a full scan by advancing the width control in the line output stage as a counter measure.

Over-driving

Should the time-constant shorten due to R135 of C121 decreasing in value, a greater than normal charge would be present in C121 before the blocking oscillator resulted in its discharge. This would

give a greater than normal line drive which, again may be incorrectly counteracted by retarding the width control. Non-linearity would be almost certain to occur in this case since C121 might charge towards the region of non-linearity.

The blocking oscillator is locked by the line sync pulses being fed to the anode from the sync separator stage, through C119. This is a line sync coupling capacitor, but if its value increases, impaired line lock is probable.

R134 and C175, across the windings of the line blocking oscillator transformer are linearity aids and are included to swamp production tolerances in the transformer itself. If the transformer is replaced and poor linearity is introduced, an improvement may be possible by altering slightly the values of R134 and C175 (mainly the former).

Line Output Stage

The line drive signal is coupled to the control grid of V7 through the coupling capacitor C123. If this is leaky, V7 will overheat badly and the horizontal scan will be affected. If it is low in value or open-circuited, the line drive signal will be reduced at the grid and insufficient horizontal scan will be the symptom.

R137 is the grid leak of V7, and if this goes very high in value or becomes open-circuited, a most peculiar modulation effect will appear on the line scan.

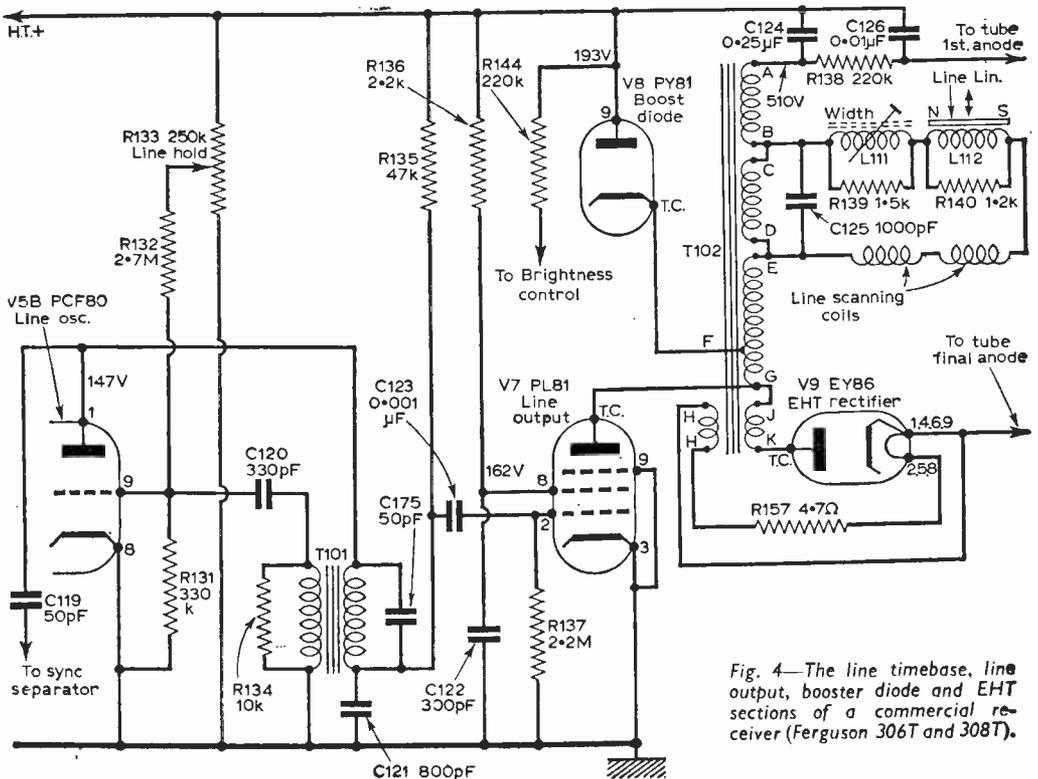


Fig. 4—The line timebase, line output, booster diode and EHT sections of a commercial receiver (Ferguson 306T and 308T).

The screen grid of the valve is fed with H.T. through R136, and by-passing at line frequency is accomplished by C122. R136 is a vulnerable fault point, since the resistor passes a fairly high pulse current. If there is an increase in λ value, the horizontal scan reduces as also does EHT voltage, and poor EHT regulation may be an accompanying symptom. Sometimes C122 develops a leak and results in similar troubles.

Bias Check

Grid bias for V7 is produced by grid current in R137 charging C123 (negative to grid). A good check for line drive is to measure the negative voltage at the control grid, relative to chassis, with a high resistance voltmeter. The actual reading obtained will very much depend on the resistance or sensitivity of the voltmeter, but quite a large deflection on the 100V scale should be obtained on a suitable meter when the drive is correct.

The major item in the line output stage is the "line output transformer", T102 in Fig. 4. The sawtooth drive at the control grid of V7 causes an increase in current through section G-F of the line output transformer (the booster diode is conducting D.C. to point F). This induces a sawtooth current in section C-D of the transformer and also in the line scanning coils. The scanning spot is thus deflected from left to right across the screen.

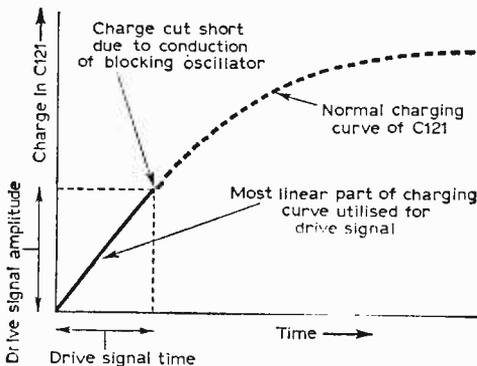


Fig. 5—The charge in C121 (Fig. 4) is cut short within the linear part of the charging curve by conduction of the line blocking oscillator.

Obtaining EHT

When the sawtooth is cut off several things happen. A large pulse occurs across section G-F which is stepped up by the EHT overwind, section J-K. The pulse is applied to the anode of the EHT rectifier valve, V9, and is changed to a steady D.C. voltage at the cathode. A smaller current pulse flows in winding H-H, and this is used to energise the heater of V9. A further voltage pulse occurs between point F of the transformer and the H.T. line. This pulse is rectified by the boost diode V8 and charges the boost reservoir capacitor C124.

The charge is such that the side of C124 connected to the H.T. line goes negative with respect to the side connected to point A on the transformer. If all is well with the line amplifier, C124 charges to about 300V, and this, in view of the polarity

mentioned above, is added to the H.T. line voltage, thus giving a little over 500V between point A on the transformer and the chassis.

This voltage is virtually a spare voltage derived from unwanted disturbances in the line output transformer. It can, in fact, be considered as a by-product which is obtained by employing a rectifier (boost diode) to damp oscillatory effects in the line output stage. The so-called "boost voltage" (the H.T. line voltage plus the voltage across the boost reservoir capacitor) is used in some sets to feed the frame timebase as well as for supplying the tube second anode potential. In the circuit of Fig. 4, it is used solely for feeding the tube second anode, and it does this through R138, which is a filter resistor, and across C126, which is a smoothing capacitor. The final anode of the tube is, of course, supplied by the high-voltage D.C. at the cathode of the EHT rectifier valve.

Also, when the sawtooth is cut off, the scanning spot flies back to the left of the tube ready to trace a subsequent horizontal line upon which one line of the picture is built.

A short in the boost reservoir capacitor would heavily damp the line output transformer and cause a very much reduced horizontal scan, and severe overheating of V8. Ultimately, either the transformer or V8 would fail. Open-circuiting would also produce a reduced horizontal scan accompanied by distortion, but V8 would run at normal temperature (which is quite high).

A short in C126 or an open-circuit in R138 would cut off the H.T. supply to the tube second anode and there would be no picture or raster (or a very dim, defocused picture).

The resistor in the heater circuit of V9 is simply to limit the heater current to prevent premature failure of the heater of that valve. Should the line oscillator and output stages appear to be working correctly and yet the EHT rectifier heater fails to light, even though the heater is intact, R157 should be examined.

R144 is effectively connected to the normal H.T. line and forms a part of the brightness control potentiometer—it is not really associated with the line timebase.

A certain degree of damping is provided by C125, and if this alters in value the EHT and pulse conditions will be disturbed. Low or excessive EHT or line scan would be the symptom.

Width Control

The width control provides a variable reactance or impedance to the sawtooth waveform current in the scanning circuit and thus controls the scan amplitude by controlling the scanning current. The shunt R139 damps resonance effects which might otherwise show up on the picture as alternate dark, and light vertical lines (or shading effects) at the left of the picture. R140 performs a similar function.

The linearity control provides selective reactance control due to a permanent magnet which can be rotated to provide varying degrees of core saturation. Thus, where the rate of change of the scanning current is in excess of that required for a linear scan, the reactance increases and slows down the rate of change, thereby effectively improving the line linearity.

(To be continued)

THE PRACTICAL DETAILS OF THE CONSTRUCTION

By R. B. Archer

(Continued from page 235
of the February issue)

A Band V Receiver

LAST month details of the construction of the coaxial lines oscillator were given.

Acorn Clips

In the prototype the acorn valve is secured in position by a choke of 18s.w.g. wire attached to the cathode pin and the chassis. Chokes of smaller gauge wire carry the heater current. However, it may well be desirable to use a tagstrip to mount the acorn; if care is exercised, it may be possible to solder the valve pins direct to the tag strip, but edge-gripping clips are recommended. Such clips may be obtained by dismantling a popular type of B8A valve-holder; although somewhat difficult to solder, the phosphor-bronze clips make an excellent contact.

All the chokes in this receiver—L5, L6, L7, L8, L9 and L11—consist of 12cm. of 24s.w.g. bare tinned copper wire wound on an $\frac{1}{4}$ in. drill as temporary former. The winding is pulled out a little


and then compressed again; this gives an even spacing between turns of about half the wire's diameter—enough to avoid much self-capacitance. If the acorn is mounted by means of a heavy-gauge cathode choke, the length of wire needed is the same. Stand-off ceramic insulators may be used to carry the H.T. lead.

It will be noted that the oscillator operates with a choked cathode. This renders the circuit operation less dependent on circuit 'strays'. Because of heater-cathode capacitance, the heater leads have to be 'choked' also. They are made to have the same R.F. potential by virtue of the capacitor C6 (Fig. 1, page 184 of the January issue).

I.F. Alignment

Alignment of the I.F. amplifier follows normal practice, using an injected frequency of 40.15Mc/s. The next step is to align the oscillator. For this a signal generator will be needed unless the reader is very close to the transmitter. (The signal generator used by the writer was described by him in *Practical Television*, October and November 1959. This has had much use since it was built, and has proved to be very reliable; such an instrument is almost compulsory for any serious experimenter with Band V frequencies. Its only serious fault is slight detuning as maximum output is reached—but this is very seldom needed in actual practice.)

First, the coupling loop, L10, is arranged to be about 1in. away from the grid of the acorn valve. Its position will be adjusted accurately later. H.T. and L.T. supplies are switched on, and a five to ten minute warming-up period is allowed. The prototype requires seven minutes to reach a stable operating condition. The signal generator is set to 660Mc/s, and the coaxial lead is brought near L1—a separation of about 2in. will be found satisfactory in the inner

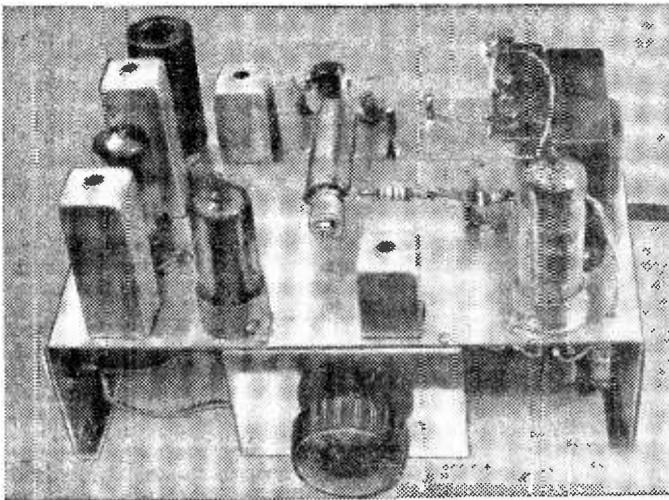

A top view of the completed receiver.

Intercarrier SOUND

By E. Murdock

If a recommendation were made by the Pilkington Committee for a change of television standards this would almost certainly contain provision for frequency-modulated intercarrier sound. Indeed, there would be every possibility that the recommendation would be for the CCIR system.

This system uses 625 lines, has negative-going picture modulation, a wider channel width and vision pass-band than our existing 405-line system and so on. This article is not concerned so much about the vision side of the CCIR system, but it deals essentially with the sound side, which in itself is most interesting.

Existing Arrangements

In the existing British system the sound and vision carriers are separated by 3.5Mc/s — the vision carrier being the higher of the two. Both carriers are applied to the tuner and the local oscillator in the tuner is arranged to work at a frequency above the frequencies of the incoming signals so that the sound and vision I.F. carriers are interchanged—that is, the sound I.F. appears 3.5Mc/s above the vision I.F.

The frequency of the local oscillator in the tuner is adjusted in all recent receivers so that the so-called "standard I.F.'s" are produced. The sound I.F. is 38.15Mc/s and the vision I.F. is 34.65Mc/s, or frequencies very close to these.

These signals, of course, appear at the output of the tuner and are then conveyed to the sound and vision I.F. channels for individual treatment and amplification. The idea is shown in block form in Fig. 1. Here care is taken to keep the vision signals out of the sound channel by accurate alignment of the sound I.F. stage and to keep the sound signals out of the vision channel by sound rejector circuits.

If the sound signal passes into the vision channel, it causes the picture to move in sympathy with the sound modulation because, for one reason, amplitude modulation is used. If the vision signal passes into the sound channel, it causes a disturbing buzz which tends to alter in intensity and tone with changes in picture content.

The CCIR System

In the CCIR system a greater separation is used between the sound and vision carriers, and the radiated sound carrier is above the vision carrier. The separation differs between the various systems used throughout the world. For example, in the American 525-line system the separation is 4.5Mc/s, in the Continental 625-line systems it is either 5.5Mc/s or 6.5Mc/s, in the French 819-line system it is 11.5Mc/s and the sound and vision carriers of some of the French stations are reversed, while in the Belgian 819-line system it is 5.5Mc/s.

The recommendation at the present time is for 6Mc/s, and it is on that basis that British manufacturers are producing dual-standard receivers.

F.M. Sound

In addition to the greater separation between the sound and vision carriers, the sound of the CCIR system is frequency modulated, and certain manufacturers feel that this will apply also in a new system launched in this country and as a consequence are producing receivers with F.M. sound facilities.

F.M. sound has many desirable features, including the possibility of better quality, less interference and less trouble from sound-on-vision effects.

Assuming that the change will be to full CCIR standards with the recommendations given above, then a block diagram of a suitable receiver may well look like that shown in Fig. 2. Here the local oscillator in the tuner is still operating at a frequency above the frequencies of the incoming signals which, again, reverses the I.F. carrier

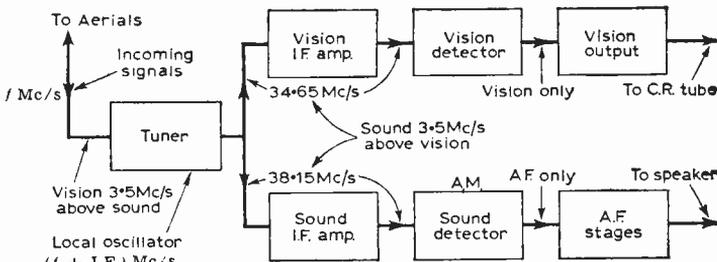


Fig. 1—A block diagram showing the standards adopted in the existing 405-line television system.

positions so that this time the vision is 6Mc/s above the sound.

The sound I.F. amplifier will remain almost the same as it is at present, while the vision I.F. amplifier will have a wider passband to accommodate the greater range of video signals which would be transmitted on the new system. The vision detector and video output stage would also be suitably modified to do full justice to the improved range of video signals.

The ordinary A.M. sound detector would be eliminated and its place would be taken by an F.M. detector of the ratio detector variety.

Intercarrier Sound

While the set-up in Fig. 2 would work adequately it would rarely be adopted except, perhaps, by experimenters. The trend is to use intercarrier sound, and all dual standards receivers are designed for this method of working.

A block diagram of the intercarrier sound system is given in Fig. 3. Here the vision I.F. stages are designed to pass not only the vision signals but also the frequency-modulated sound signals. The vision I.F. amplifier thus has two carriers to contend with, and these are passed to the vision detector.

The vision detector demodulates the vision signals in the ordinary way and passes the picture signal on to the tube in accordance with normal practice. However, the two carriers which are present at the detector become modulated, one with the other, because the detector is a non-linear device.

This means that in addition to the video signal at the output of the detector, there also exists a signal, the frequency of which is equal to the difference in frequency of the sound and vision carriers. This, we have seen, is 6Mc/s.

The 6Mc/s signal is now called the sound I.F.

in the diagram. If it is taken through the video amplifier, then that stage must have a sufficiently wide pass-band to allow its unrestricted passage, but this has the advantage that the signal is given a degree of amplification before it is applied to the sound I.F. stage.

If the signal is taken from the output of the detector, the video amplifier or output stage need not be quite so critical, but greater gain is then necessary in the sound I.F. amplifier section. Both methods are used in commercial dual-standard receivers.

It will also be appreciated, of course, that greater sound I.F. amplification is possible at 6Mc/s than at 32.9Mc/s with a given complexity of circuit. It is thus a fairly straightforward matter to amplify the signal through a single valve so that it is of sufficient strength to operate a ratio detector and to provide good amplitude limiting.

The fact that both sound and vision signals are passing through the vision I.F. stages is of little consequence because the sound signal is frequency-modulated, and will not cause sound-on-vision as with an amplitude-modulated sound signal. Moreover, the response of the vision I.F. stages is arranged so that only a limited amount of amplification is given to the sound signal with respect to the vision signal.

The strength of the sound I.F. (6Mc/s) at the output of the vision detector is some twenty to thirty times less than that of the vision signal at the same point.

The intercarrier signal (6Mc/s) is suppressed either at the output of the video amplifier or in the tube feed circuit.

Advantage and Characteristics

The major advantage of the intercarrier sound system is the high stability of the sound channel. In ordinary systems the sound channel I.F. is governed by the tuner's local oscillator, and if this drifts then also does the sound I.F., necessitating re-adjustment of the fine tuning control.

This cannot happen with the intercarrier system because the sound I.F. represents the difference frequency between the sound and vision carriers, and these never drift since they are held correct at the transmitter.

To give some idea of the stability of the sound channel, the fine tuning control on an intercarrier receiver can be swung from one extreme to the other without any change in sound output. In the existing system it is customary to adjust the fine tuning control for maximum sound, consistent with minimum sound-on-vision at which point, if the alignment is correct, the best picture quality will also occur. With an intercarrier receiver the fine tuning is simply adjusted for the best picture quality.


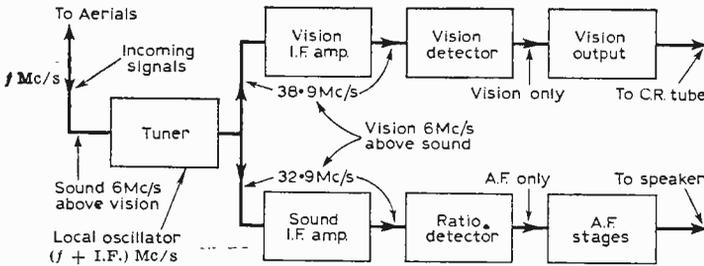


Fig. 2 (above)—The system of Fig. 1 altered to suit the CCIR standards.

Fig. 3 (below)—A block diagram of an intercarrier sound receiver.

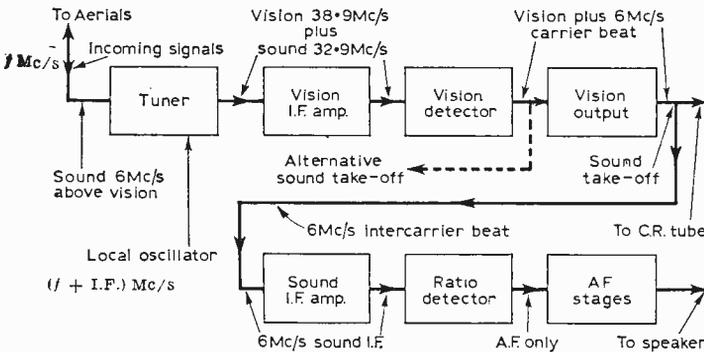

since upon it is superimposed the original frequency-modulation of the sound signal. In some sets it is passed along with the video signal through the video output stage and is extracted at the output and then applied to a separate 6Mc/s sound I.F. amplifier, as shown in the diagram.

In other sets, it may be extracted at the output of the vision detector, as shown by the dotted line

★ VALVES ★ BY RETURN OF POST

THE MOST COMPREHENSIVE COMPETITIVE VALVE LIST IN THE COUNTRY

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozen). Post: 1 valve, 6d., 2-11, 1/-.	NEW LOW PRICES GUARANTEED 3 MONTHS	FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government origin. Satisfaction or Money back Guarantee on goods if returned unused within 14 days.
--	---	---

OZ4	5/-	6J5GT	4/-	12E1	17/6	DF96	7/3	EM80	7/9	8U25	16/-	
LA5GT	5/-	6J6	4/-	12J7GT	9/9	DH163	6/-	EM81	8/6	8U250	9/6	
1A74T	11/-	6J7	8/6	12K7GT	4/9	DH176	6/-	EM84	9/-	UDD4	7/6	
1D5	9/-	6J7B	4/6	12K8	11/6	DK32	11/6	EM85	10/-	UDD4	7/6	
1D5GT	9/-	6J7GT	7/6	12K8GT	9/6	DK91	5/6	EN31	16/-	U14	8/-	
1D6	9/6	6J8	8/6	12Q7GT	5/-	DK92	7/-	EY61	1/-	U18	8/-	
1L54T	9/6	6K6GT	6/6	12M8	9/6	DK96	7/6	Small	7/9	U22	6/9	
1L54	3/8	6K7	6/9	12M8H	3/8	DL33	8/6	EY86	7/6	U24	10/-	
1L1D5	3/6	6K7B	2/9	12M8T	1/6	DL33	9/-	EZ35	5/6	U26	11/6	
1L1S	4/6	6K8	4/6	12N7GT	4/9	DL63	5/6	EZ40	6/6	U26	9/6	
1N54T	9/6	6K4GT	8/9	12K8T	7/9	DL73	7/6	EZ41	7/-	U31	7/-	
1R5	5/6	6K25	7/6	14A87	14/9	DL82	9/6	EZ40	6/-	U33	14/6	
1R4	8/-	6L1	12/6	19A93	7/6	DL91	8/-	EZ81	8/6	U35	12/6	
1R5	4/6	6L2G	6/6	19B3GG	9/-	DL92	6/-	FW4600	8/6	U37	24/6	
1R4	3/6	6L1	9/-			DL94	6/9	FW4600	8/6	U37	24/6	
2A3	6/6	6L19	11/-	2011	9/6	DL96	7/6	GTIC	7/-	U52	4/9	
2A7	9/6	6L1D3	8/-	20F2	9/6	DW4350	6/6	GZ32	8/9	U76	5/6	
3A4	4/9	6L1D12	6/9	2011	18/6			GZ34	12/6	U78	5/6	
3A5	9/-	6L19D20	7/9	20P1	8/9	DW4500	6/6	HABCS9	6/6	U91	9/6	
3D6	4/6	6L1	9/-	20P3	18/6	DL92	6/-	HL14D	10/6	U281	9/6	
8Q4	7/-	6P1	7/6	20P4	18/6	EA09	4/6	HN309	19/-	U301	15/-	
3Q5GT	8/-	6P25	8/6	20P5	15/-	EAF2	4/6	HVR2	10/6	U309	6/9	
384	6/-	6P28	12/6	25A6G	6/6	EAF3	6/6	HW33	10/6	U329	6/9	
3V4	9/6	6Q76	8/-	25L80	6/6	EB41	7/-	1W4350	7/6	U339	6/9	
5RA4Y	12/6	6Q2T	8/6	301GT	7/9	EB91	3/-	1W4350	7/6	U339	11/6	
3T4	9/-	6R7G	8/6	35V3G	8/6	EB93	4/9	KLL32	8/6	U801	19/6	
5U4G	4/9	6SA7	5/6	26Z44	7/-	EB41	4/9	KT32	6/9	UABC80	8/6	
5V4G	7/6	6G97	4/9	25Z5	8/6	EBC81	7/9	KT33C	4/6	UAF42	7/9	
5V3G	5/6	6RH7	3/-	25Z66	8/6	EBC90	7/9	KT36	12/6	UB41	7/9	
5V3GT	5/6	6R47	5/-	3061	7/-	EBC93	9/6	KT44	7/6	UB41	7/9	
3V3	11/-	6R7GT	5/9	30P5	6/6	EBF80	8/6	KT45	8/6	UBC81	9/6	
5Z4	11/-	6N7GT	4/6	30FL1	6/6	EHL21	12/6	KT61	8/6	UBF80	7/6	
5Z44	7/6	6N47	5/9	30L11	6/9	EHL31	17/6	KT63	5/9	UB121	14/6	
5Z4T	11/-	6H57	3/6	30P1	9/6	EY91	4/6	KT78	8/6	UCC84	14/6	
6P30L2	9/-	6U4GT	10/6	30P12	7/6	ECC40	14/6	LM152	7/-	UCL82	9/9	
6A4	4/6	6V84	7/6	30P18	6/6	ECC82	4/6	MT61	5/9	UCF80	15/-	
6A7	10/-	6V8GT	7/6	30P11	9/6	ECC33	4/6	KTW63	5/9	UCR21	12/6	
6A84	8/6	6X2	7/6	351.6GT	8/6	ECC34	8/6	KZ263	5/6	UCH42	7/9	
6A8GT	18/6	8X4	9/-	33T	25/-	ECC35	9/-	L63	2/9	UCR81	8/-	
6A8S	7/6	6X3G	5/-	33V4	6/9	ECC40	14/6	LM152	7/-	UCL82	9/9	
6A8V	3/6	6X3GT	5/6	35Z44T	5/6	ECC81	5/9	MU14	7/6	UCS3	13/6	
6A4S	3/-	6Y6G	7/6	35Z52T	8/6	ECC82	6/-	N37	11/-	UCF41	7/6	
6A4G	7/6	7A7	8/6	41	7/6	ECC83	6/9	N78	13/-	UCF42	5/6	
6A4K	5/-	7B6	9/-	42	7/6	ECC84	8/-	N108	16/-	UF80	7/-	
6A4S	3/-	7B7	17/9	50C3	9/-	ECC86	7/9	N132	8/6	UF85	7/-	
6A4S	6/-	7C8	7/6	50C6DG	6/6	ECC88	16/4	P1	2/9	UF86	14/6	
6A4S	6/-	7C8	7/6			ECC91	4/6	P51	2/9	UF89	8/6	
6A7E	5/9	7H7	7/6	50L6GT	8/6	ECC90	8/6	PABC80		UJ41	11/-	
6A4U	7/6	7K7	8/6	82KU	10/6	ECC92	8/6			UL44	11/6	
6B7	9/6	7Q7	10/6	53KU	10/6	ECC93	8/6	PCC84	6/9	W61M	9/9	
6B8G	3/-	7R7	10/6	181PT	11/6	ECC95	7/6	PCC85	8/3	U46	9/9	
6BA6	5/9	787	9/-	62BT	13/6	ECC42	8/6	PCC88	14/-	UL84	8/6	
6BE8	5/9	7V7	7/9	75	6/6	ECC81	7/9	PCC89	9/-	UC6	12/6	
6BG60	15/-	7Y4	8/9	78	6/9	ECC83	8/6	PCF80	7/-	U17	9/6	
6BH	6/-	7Z4	17/-	80	6/9	ECC80	7/6	PCF82	7/9	U18	17/6	
6B6	6/-	8D3	3/-	83	9/6	ECC82	9/6	PCF84	16/-	U18	11/6	
6BR7	9/6	10C1	11/6	185BT	19/6	ECC83	11/6	PCL82	7/3	UY21	11/-	
6BW4	7/6	10C2	14/6	803	19/6	EP22	7/-	PCL83	10/6	UY21	11/-	
6BW7	5/6	10L1	8/-	807(A)	5/6	EP36	3/6	PCL84	7/6	UY83	6/9	
6BX8	4/8	10P1	5/9	808	5/6	EP39	4/6	PEM45	8/6	VP41	5/6	
6C4	3/6	10P9	5/9	818	5/6	EP46	12/-	PEB46	5/6	VP41	5/6	
6C5	5/6	10L14	7/-	832A	14/6	EF41	8/6	PL33	8/3	VR10530	6/9	
6C6	3/9	10L1D3	7/9	865A	11/6	EF42	7/6	PL36	9/6	VR10530	6/9	
6C9	11/-	10L1D11	14/6	9004	2/9	EF50-BR2	12/6	PL28	16/6		6/9	
6C9DG	19/6	10L1D12	3/6	ATP4	2/9	USA	3/-	PL31	8/6		6/9	
6D3	9/6	10P13	11/6	AZ3A	12/6	EP34	8/6	PL32	8/6		6/9	
6D2	9/-	10P14	9/-	B36	7/6	EP80	4/9	PL38	6/6		7/6	
6D3	9/6	10P18	7/-	C1C	9/6	EP85	6/9	PL84	8/-		W61	4/9
6D6	4/3	12A5	4/9	CB11	26/6	EP86	9/-	PL820	8/6			6/9
6P1	4/9	12AC6	15/-	CB131	21/-	EP89	6/9	PN4	12/6		X63	9/6
6P6G	5/9	12AD6	15/-	CBH33	14/6	EP91	6/9	PC25	9/6		X63	11/6
6F12	3/-	12AE6	18/9	CL33A	9/6	EP92	4/6	PY81	9/-		X66	11/6
6F13	6/9	12AT6	9/-	CV31	9/-	EP96	3/-	PY82	10/-		X76M	11/6
6F14	9/6	12AT6	7/6	D77	3/8	EL32	4/6	PY80	6/9		X78	21/6
6F15	9/6	12AT7	5/6	D152	5/9	EL33	7/6	Y81	6/9		X79	16/6
6F16	8/-	12A16	6/6	D30	12/6	EL35	7/6	Y82	6/9		X81M	9/6
6F19	8/6	12A17	6/-	DAC32	9/6	EL41	8/-	Y83	7/-		Y63	6/3
6F23	6/6	12AX6	6/6	DAP91	4/6	EL42	8/6	PZ30	9/6		Z63	6/9
6F32	6/6	12BA6	7/6	DAP96	7/3	EL43	11/-	R18	11/-		Z68	9/6
6F33	6/6	12BE6	7/6	DET19	2/9	FL44	7/-	R19	11/-		Z152	4/6
6J5	4/3	12BH7	6/9	E33	9/6	EL41	4/6	SP2	2/6		Z19	6/9
6J6G	3/-	12C4	6/6	DF91	3/6	EM34	7/6	SP81	2/6		Z152	7/6

★ Tubes ★

Carr. & Ins. 12/6.

	Guaranteed 6 Months	Guaranteed 12 Months	NEW TYPES
MOST MULLARD, MAZDA, COSSOR, EMITRON, EMISCOPE, BRIMAR, FERRANTI TYPES.	12in. £2. 0.0	£3. 5.0	MW 31/74 £4-0-0
PROCESSED IN OUR OWN FACTORY.	14in. £2.10.0	£3.15.0	MW 30/24 £5-0-0
	15/17in. £3. 5.0	£4.10.0	CRM 178 MW 43/64
	21in. £3.15.0	£5.15.0	£6-0-0

RECTIFIERS

SILICON DIODES 12v. 500 M.A., 2 in series make superior replacement for R.M.4 and R.M.5, etc. 8/- each. 12 volt 31 amp. 9/6; 250 v. 80 m.a. 5/6; R.M. 6/6; R.M.2; 8/-; R.M.3; 9/-; R.M.4; 15/6; R.M.5; 21/-; 14A86; 17/-; 14A97; 23/-; 14A100; 25/-; 16RC1-1-16-1; 7/9; 16RA1-1-16-1; 7/9; 18RD2-2-8-1; 24/-; 14RA1-2-8-2; 17/-; 14RA1-2-8-3; 20/-.

GERMANIUM DIODES, general purpose, 8d. each 8/- doz.

B.B.C./I.T.A. TUNERS

Famous makes complete with PCF80, PCF84 valves. 38 M/c I.F. Fantastic value 19/-

13 CHANNEL TV'S

TABLE MODELS—FAMOUS MAKES Absolutely complete

These sets are unequalled in value due to huge purchase direct from source. They are untested and are not guaranteed to be in working order. CARR. ETC., 15/-.

12" — £2.19.0
14" — £4.19.0

ALSO 12in. 5 CHANNEL TV'S 39/-
14in. 5 CHANNEL TV'S 69/-

CO-AX

standard and low loss, 25 yds., 12/6; 50 yds., 22/6; 100 yds., 42/6. Co-ax Plugs 1/3. Walloutlet boxes 3/6.

100 RESISTORS 6/6

100 CONDENSERS 10/6

Miniature Ceramic and Silver Mica Condensers 3 pF to 10,000 pF. List VAL E OVER 2s.

4 SPEED RECORD PLAYERS

Latest E.M.I. Turntable, together with lightweight Star Galaxy dual sapphire crystal turnover pick-up head. Truly amazing value. Carr. 3/-. £3.10.0

PM SPEAKERS

2 ohms, top makes performance guaranteed.

8" 8/- 3in. 11/- 10in. 13/- 6in. 8/- 5in. 11/- 10x5 13/-

MAINS AMPLIFIERS

3 valve (10F3, 10P14, U19), 3 watt, 8n. loudspeaker in two tone case with controls. Ideal for record players. P. & F. 6/6. 19/-

T.V. PROJECTION UNITS

Complete Standard Philips optical units with Mullard MW-2 projection tube (tested) at a fraction £3.10.0 of cost.

Test Sets Type 74A

A service scope easily convertible for standard use, 200/250 v.a.c., all valves, E.C.R. 30 watt, excellent £4.10.0 case worth £10. Our price.

LINE OUTPUT TRANSFORMERS.

Most types ex-shipment. From 19/-

ISOLATING TRANS.

With 25% boost. Get extra life out of that old C.R.T. 2v. 9/6 6.3v. 12v. 9/6

CONNECTING WIRE, either flexible or solid core. 25ft. P.V.C. Insul. 1/6. 5 coils diff. colours, 4/6.

LINE TRANSFORMERS

Most types available from stock from 19/- Also frame and blocking oscillator. Transforms. S.A.E. enquiry.

DEFLECTION COILS

35mm. standard, most makes. 9/6
38mm. wide angle. 15/-

FOCUS MAGNETS

Standard and wide angle, single and double magnets, 9/6. 10N TRAPS, 2/6.

GERMIC CONDS.

1—10,000 pF, factory fresh 5/- doz. your selection.

POTENTIOMETERS

Standard spindle and preset 1/9 each 100 ohm to 3 meg.

VALVES

Guaranteed 3 months. Short leads.

U25 7/6 EY51 4/6

CONDENSERS

25 mixed. Electrolytic. Many popular sizes. List value 2s. Our price. 10/-

UA20 AUTOCHANGERS

4-speed latest B.S.R. 10 mixed records. Unrepeatable. A real "buy". P. & F. 4/-

AMERICAN RADIO

Post: 2 lbs. 2/-, 4 lbs. 2/6, 7 lbs. 3/6, 15 lbs. 4/- etc. No C.O.D. ALL ITEMS LESS 5% AND POST FREE IN DOZENS (Callers always welcome). LIST OF 1000 SIFPS, 6d.

350-352 FRATTON ROAD, PORTSMOUTH

TREMENDOUS DEMAND! for the new NOMBREX

Our order book shows that this highly efficient and compact signal generator is the finest value in instruments anywhere in the world.

Designed after months of research in our own laboratory, and custom-built to the highest standards in our own factory, it is the ideal instrument for radio service engineers, radio enthusiasts, and for technical training colleges.

NOTE THESE STAR FEATURES


- ★ Compact and portable—only 6½" x 4½"
- ★ Truly lightweight—under 2lb weight
- ★ Operates from standard 9V transistor battery
- ★ Fully transistorised—negligible consumption
- ★ 8 ranges fully covering S/B220 kc/s-220 Mc/s
- ★ Printed circuit for absolute reliability
- ★ Accuracy better than 2% (average 1%)
- ★ Modulated or unmodulated R.F. output, 100mW
- ★ Audio output, sine wave, approx. 1,000 c/s

COMPLETE WITH OUTPUT PLUG ONLY

Send your order in now for earliest possible delivery.

S.A.E. for full technical leaflet.

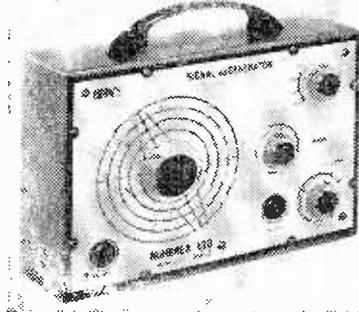TRANSISTORISED WIDE-RANGE
SIGNAL GENERATOR 27
220 Kc/s to 220 Mc/s.



RETAIL £7.10.0 Post and Ins. 3/6
Battery 2/-

CASH WITH ORDER. REGRET NO C.O.D.

NOW IN QUANTITY PRODUCTION
ALL ORDERS IN STRICT ROTATION

Trade and Export Enquiries Invited

NOMBREX LTD.

Instruments
Division 24

ESTUARY HOUSE, CAMPERDOWN TERRACE,
EXMOUTH, DEVON. Phone: 3515.



"SABRINA"

STILL WELL IN
FRONT

Make your TV set 100% again before Prices rise. (You have been warned!)

**COMPLETELY REBUILT C.R. TUBES
ALL TYPES** (including electrostatics)

12" now	£5. 0.0	} For	
14" to 17" now	£5.10.0		} Single
21" now	£8. 0.0		

ALL C.W.O.—TRADE SUPPLIED

Special Bonus Scheme for Service Engineers—Reducing to:

12"—87/6; 14"/17"—97/6; 21"—147/6

FREE Pass. transit & Ins. anywhere in British Isles or N. Ireland (12 months' guarantee).

SABRINA C.R. TUBE CO.

Electron Works, North Bar

BANBURY, OXON

Telephone 2390

14" 36/24, 14KP4, TUBES 35/-

Ex-rental replacement stock. Working. Carr. 10/-.

18/9 SOLDERING IRON
30w. 230v. 64in. long. A.C. For lightweight applications. Can be carried safely while hot. In vinyl bag, with lead and flux. Carr. FREE.

VALVES 9D. 6D1, 6D2, 6F12, 6F13, 6F14, 6F15, 8D3, 9D2, 13D2, 74, EA50, EB91, ECC81, ECC84, EF50, EF91, F61, PM202, 8P61, UB41, UF42, VR35, V351, VR107, VR137, VR201, Z77.

1/9 6F1, 6P25, 6P28, 10D1, 1625, B36, EB41, EL32, N142, U22, U31, U35, W76, W77.

2/9 6AB5, 6L18, 10F1, 10P13, 20D1, 20P3, EBC80, ECL80, EF92, EY91, KT36, N145, LN152, PL33, U151.

5/9 6P6, 12AX7, 12Q7, PL820, 1548, 16A5, 17Z3, 19Y3, PY80, 20P1, 21A6, B330, EB333, EBF80, PV81, EC033, EL33, EL42, EY85, PY82, N152, N153, N154, N309, N329, N339, PZ30, PCC82, PL81, PL82, PL83, U153, U154, U251, U319, U329. Post (—d), 6—1/6.

P.P. COMPONENTS LTD. 623 Romford Road, Manor Park, E12
Mail order only. Stamp for FREE List.

REBUILT TV TUBES

FULLY GUARANTEED 12 MONTHS

Complete New Gun Fitted in Every Tube

12in.	£4.0.0
14-15in.	£4.10.0
17in.	£5.0.0
21in.	£7.0.0

Immediate Delivery. Carriage and Insurance 10/- extra.

ALLOWANCE ON OLD TUBE

NU-GUN TELETUBES LTD.

3 THE MEWS

Duckett Road, Harringay, London, N.4

Telephone: MOUntview 2903

Servicing Data and Modifications

SOME "TEETHING" TROUBLES OF NEW RECEIVERS AND HOW TO CURE THEM

By D. Elliot

(Continued from page 244 of the February issue)

WE continue this series with some information on early Ferguson models, notably the 991T series and others which incorporate so-called long time-constant flywheel synchronisation.

S-Shaped Verticals

Flywheel sync is incorporated essentially to reduce the symptoms of "line tearing" and "ragged verticals" which occur due to irregular "firing" of the line oscillator. Such trouble is caused by random noise and interference signals being superimposed on the tips of the line sync pulses. This happens primarily in areas of high interference and relatively low signal strength.

With flywheel sync, however, the line oscillator is frequency stabilised at the correct repetition frequency by a control voltage produced by the difference in phase between the line sync pulses and the line oscillator, so that as soon as

slightly different problems. For example, any spasmodic change in the frequency of the power supply causes the line starting position to alter laterally. Moreover, any residual phase modulation of the line frequency, sometimes present on certain transmissions, produces an S-curve on the vertical parts of a picture.

Similar trouble can be caused by a fault in the receiver itself. A heater-cathode leak in a valve associated with the line sync and oscillator circuit can produce the trouble, as also can impaired smoothing of the H.T. line. Set faults, however, can be proved by reversing the mains plug. If the S-curve is "mirror-imaged" by such action, then the set is at fault, but if the curve remains the same which ever way round the mains is connected, the trouble lies in the transmission and there is little that can be done without altering the desirably long time-constant of the flywheel circuit.

It should be noted that certain old-style test equipment produces residual phase modulation of the type mentioned, but the trouble occurs only rarely on transmissions nowadays.

Several years ago, flywheel sync was very usual, but then its popularity waned. It is likely to come into mode again, however, should there be a change to CCIR transmission standards on UHF.

Alternative Picture Tubes—Ferguson 996T

Since we receive a number of queries concerning alternative tubes on the above receiver, the following notes should be of interest. The Ferguson 996T is equipped either with a Mullard MW43-64 or Emitron T/ASP4 picture tube. These tubes are not directly interchangeable, and where possible the replacement for which the set is designed should be used.

The neck of the Mullard tube is slightly shorter than that of the Emitron, and sets incorporating the latter tube have the dome on the cabinet back spaced off approximately half an inch by a ring of insulating material and set about one eighth of an inch lower than on receivers using the Mullard tube.

The Mullard tube is a pentode, while the Emitron is a tetrode, which means that the sup-

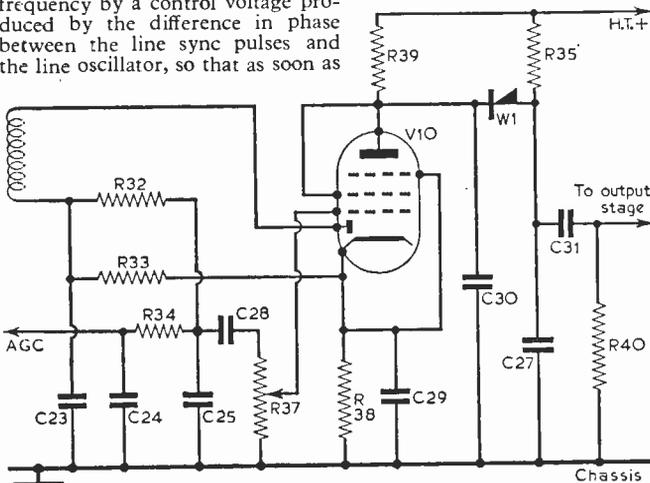


Fig. 5—A circuit for improving the sound interference suppression in Ferguson Models 941T and 951T.

the latter starts falling out of phase, a correction voltage is produced to bring the line oscillator back into step with the sync pulses. The line oscillator, then, does not rely on receiving every line sync pulse clearly defined and free from interference, which means that "line tearing" and "ragged verticals" cannot occur on such a receiver.

Unfortunately, flywheel sync brings in its wake

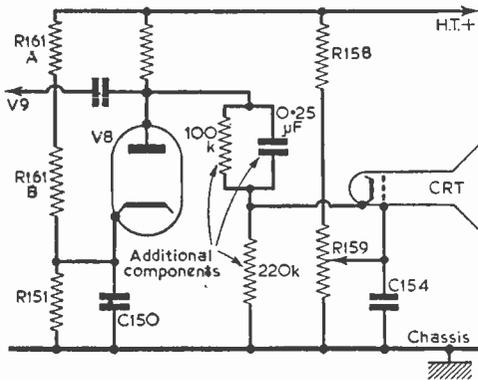


Fig. 7—Reducing the D.C. component of the vision signal in English Electric T40 series. This modification reduces random changes in brightness.

Corona in English Electric C45 and C46 21in Sets.

EHT flashover or corona sometimes occurs around the picture tube mounting in early versions of the above models. This symptom appears to be more troublesome in locations where the receiver is subject to a certain amount of dampness or humidity.

The picture tube is already encased around the flare by a polythene sheet, but by the introduction of an additional double-thickness polythene sheet, turned up 2in. at the bottom, as shown in Fig. 8, the trouble can nearly always be eliminated.

It is sometimes possible to obtain a kit of parts from an English Electric agent, including a specially treated plywood cradle, securing strap and polythene sheets.

effect at the expense of a very small loss of finer "shadow" details.

The additional network, as shown, is connected in series with the tube cathode lead and can be fitted without removing the chassis from the cabinet. The white lead from the tube cathode should be cut about 2in. from the point where it leaves the main chassis, and the two resistors and capacitor should be assembled on a tag strip and secured at the rear of the I.F. chassis. To avoid hum pick-up and instability, the 220k resistor should be "earthed" at the tag strip and not at the picture tube.

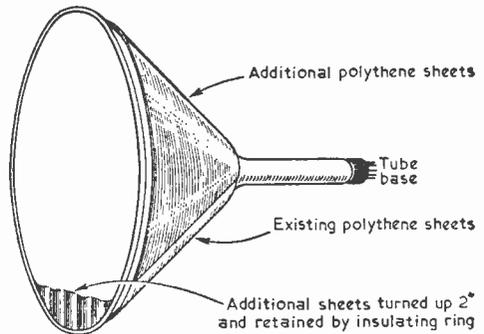


Fig. 8—Eliminating corona on 21in. English Electric models C45 and C46.

(To be continued)

FREE! DOUBLE SIDED BLUEPRINT

INSIDE EVERY COPY OF THE APRIL
Practical WIRELESS

[on sale March 7th]

With detailed instructions for building 2 grand sets

FOR BEGINNERS


2-valve battery-operated short-wave receiver. Easy-to-build for the novice constructor.

FOR EXPERIENCED CONSTRUCTORS

4-transistor medium- and long-wave portable receiver with internal ferrite rod aerial.

★ Coming!
More invaluable FREE Double-Sided BLUEPRINTS in the May and June issues of *Practical Wireless*.

ORDER FROM YOUR NEWSAGENT NOW!

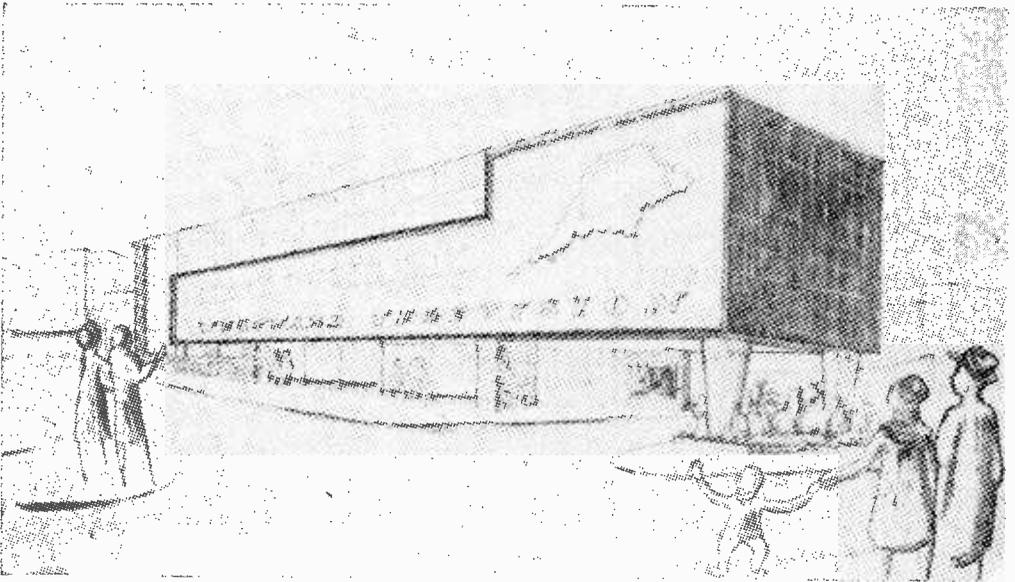

An artist's impression of the Westward Television Centre in Plymouth.



*its
development
and
progress*

WESTWARD TELEVISION

WHEN the war ended, the City of Plymouth was in a distressing state. Few of the impressive buildings in the shopping centre survived the blitz. The huge department stores were razed to the ground; the municipal buildings and the churches were badly damaged, but Derry's Clock, a famous landmark for 99 years, survived.

It was around this clock and the restored civic buildings that the new Plymouth was planned, and in Derry's Cross, the "Piccadilly Circus" of Plymouth, Westward have built their television centre and studios. Little more than eighteen months ago, Derry's Cross overlooked a piece of derelict ground, bisected by a road which, it was proposed, should be removed in the reconstruction plan.

The Time Factor

Almost everywhere in any television station, you are faced by clocks, large, small, illuminated, silenced, synchronous and slaved. But the most menacing of all are the large slave clocks with pulsed minute and second hands. The second hands of these clocks are the controlling influence of any station. Working on a time schedule to the nearest second is a fundamental requirement of any television network, but particularly the commercial stations, where interchange of programmes and insertion of commercials involves sim-

ultaneous switching operations in many Post Office and programme company's centres.

The clocks start ticking long before a station opens, however. From the moment the ITA awards a regional concession to the selected syndicate, the fight with time begins. Probably in no regional area to date has the fight against time been so fierce as in the South West, where Westward have now completed a new, purpose-built television centre in the heart of Plymouth. It takes much longer to build new premises than to convert existing premises, and there lies the danger if the completion date is definitely fixed and immovable.

The First Stage

Even before the Westward group—headed by Peter Cadbury — had secured the concession, the syndicate decided to build new studios rather than convert an old building, and the architects had prepared preliminary plans and perspective drawings of the proposed buildings. These drawings were exhibited to the ITA and were part of the evidence produced to show the ambitious intentions of the winning syndicate (of the fourteen applicants). A splendid site had been reserved near the Continental Hotel, not far from the Post Office Telephone Exchange, through which all vision and sound signals would come from the ITV network (via Bristol). In the reverse direction, these signals integrated with the local production and commercials, would return on separate lines, to the Plymouth Telephone Exchange, to be fed to the transmitters at Stockland Hill (near Axminster) and Caradon Hill (near Liskeard).

The Second Site

The site seemed a good one, but before any building was started the Estates Official of the Plymouth Corporation came forward with the offer of an alternative site, fifty yards from the one originally selected, but of a very different character. This new site, vaguely earmarked for a civic theatre to be built some time in the future, had a frontage on Derry's Cross. But there was one disadvantage to this site: the end of Millbay Road, A38, together with telephone, electric

power and other services underneath it, cut right across the frontage of the site and this road could not be closed to the public until September 1960. It was unthinkable to lose this wonderful frontage, but impractical to delay commencement of building construction until this date.


The outcome of a very lengthy debate one night at Plymouth between the architects and executives of Westward was a somewhat unconventional layout—shown in Fig. 1—which would allow the studios and technical area and production offices, etc., to be built at the rear of the new site, clear of the public road, and for work on these to commence as soon as the plans were passed by the City Council. The "front office block" could follow, work to commence as soon as the Millbay Road section was closed and the public services under the road removed. The front office block and the technical area would be joined by a wing containing canteen, dressing-rooms and a few administrative offices.


Unexpected Advantages

In the meantime, a number of additional advantages for this site had become apparent. It was in the heart of the "theatre precinct" of Plymouth, very close to the Civic Centre, the A.B.C. Cinema, the Drake Cinema and the department stores. These were all within 1,000ft and could be covered for outside broadcasts without the use of an O.B. truck. On the adjoining site was the Plymouth

Fig. 1—A plan of the television centre:

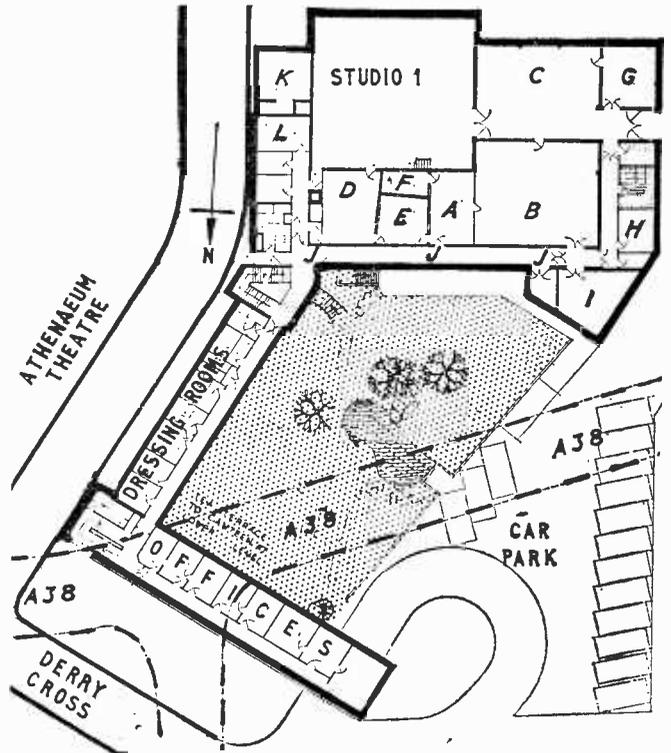- A—Master control room,
- B—Technical area,
- C—Scene dock,
- D—Studio 2,
- E—Studio 2 control room,
- F—Announcers,
- G—Carpenter's shop,
- H—Drawing office,
- I—Technical maintenance,
- J—Public viewing corridor,
- K—Oil storage,
- L—Green room.



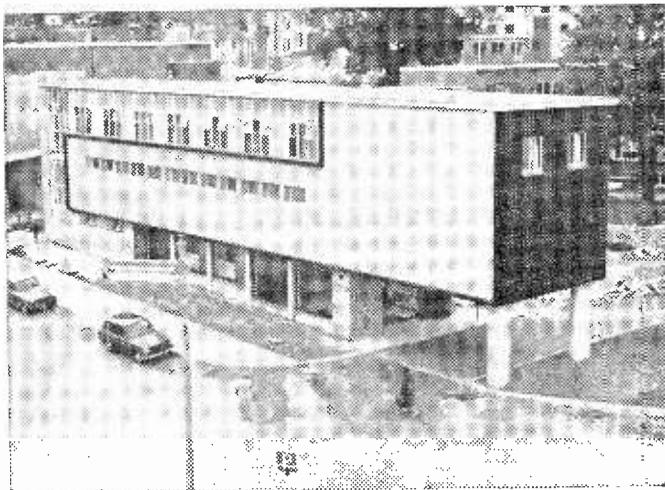

A view of the front of the television studios when nearing completion.

Institution and Devon and Cornwall Natural History Society, who were putting up an impressive building to house lecture rooms, library, photographic dark rooms—and a small theatre seating 356 persons.

The construction of this theatre—the Athenaeum—had only just commenced and the Plymouth Institution Management Committee were willing to make structural modifications in the interest of its regular use for television.

Westward suggested the provision of a modern revolving stage and a compound orchestra lift which virtually added an 8ft apron to the front of the stage; also the provision of additional power supplies for lights, permanent camera, sound and control circuits and even a clock slaved to the master clock system in the Westward building!


This was agreed to and finally, it was decided, that if the Athenaeum was to be regularly used by Westward, an underground connecting passage should be built to enable artists to walk straight from their dressing rooms in the Westward building to the stage of the theatre.

All of this was a most valuable excursion into supplementary facilities.

The Challenge

The fact that the plot of ground chosen for the Westward building faced the busiest thoroughfare in Plymouth was a challenge for the architects to design a frontage which would fit in with the enlightened architecture of the reconstruction area of Plymouth, to harmonise with the dignity of the Civic Centre, without clashing with the gay façade of the Drake Cinema, nor the contemporary loftiness of the big stores in Royal Parade. And—at the same time, to preserve a functional up-to-date building.

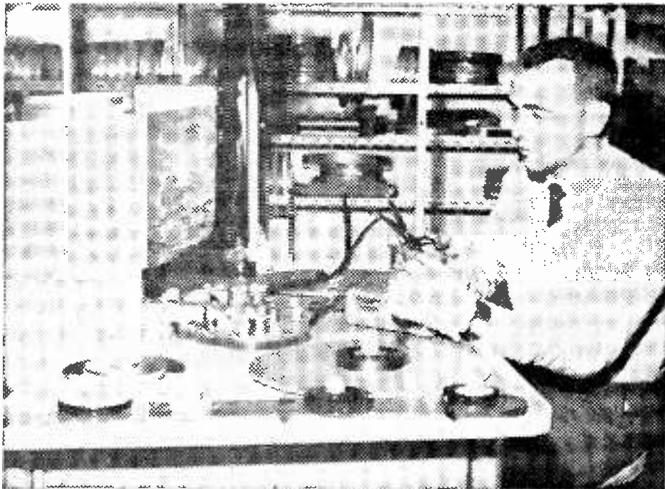future expansion. The film department was to be directly below “telecine”, with a hoist between. Production and technical offices were to be grouped around the technical area. This rear part of the premises was completed in time for the opening of the station but the remainder of the premises have only recently been finished.



A Westward Television film editor at work in one of the film cutting rooms.

Technical Facilities

A wing joining the studio block with a front office block, houses the restaurant on the lower ground floor, dressing rooms on the ground floor and a number of offices on the first floor. The front block contains reception and the sales department on the lower ground floor with the administrative offices above.

The main television equipment contract was arranged with Marconi's Wireless Telegraph Ltd.,

(Continued on page 292)

transistorised SYNC Separators

By G. J. King

NEWLY DEVELOPED CIRCUITRY IN MODERN RECEIVERS

BASICALLY, the requirements of a transistorised sync separator are exactly the same as those of a valve equivalent. The stage is required to eliminate the picture content of the video signal and provide at its output sync pulses of suitable amplitude and polarity for locking the frame and line timebases.

To do these things successfully, the transistor employed should possess a reasonable switching performance and a high current gain factor. Care should also be taken to avoid overloading the base circuit with excessive video input signal, as large signals are likely to cause "bottoming" of the transistor, resulting in undesirable hole storage effects and a lengthening of the output pulses, thereby making frame pulse separation difficult. Very large input

signals may also cause direct feed-through of the picture signal via the collector-to-base capacitance. In the majority of cases, however, these troubles are automatically prevented by the receiver's vision AGC system.

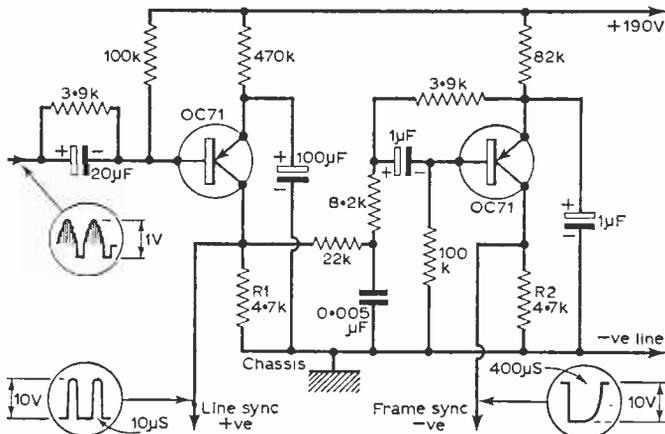


Fig. 2 (above)—The Mullard circuit using two transistors.

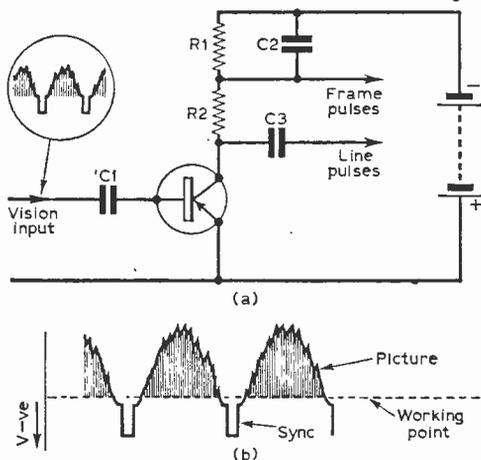


Fig. 1—The basic transistor sync separator circuit.

Basic Circuit

The basic circuit of a transistorised sync separator stage is given in Fig. 1(a). On negative-going sync pulses, capacitor C1 charges via the base-emitter junction of the transistor, and the resulting charge biases the transistor to the working point as shown in Fig. 1(b).


This means that collector current flows only during the negative-going sync pulses, the transistor being effectively switched off during the picture signal. Sync pulses thus occur only across the collector load resistors R1 and R2. The differentiating circuit comprising R2 and C3 passes only the line sync signals, while the integrating circuit of R1 and C2 produces frame pulses only, which, of course, is the usual method of sync pulse separation employed in most valve circuits.

It will be observed that the transistor requires a positive-going picture signal, which is the opposite to valve arrangements. However, a suitable signal of correct polarity can be obtained from the cathode circuit of the video amplifier valve.

The Mullard Circuit

The Mullard circuit (Fig. 2) uses two transistors. This is highly stable and will provide line and frame sync pulses suitable for most types of timebase generator. A composite video signal of one volt peak-to-peak is required for the best operation, but the circuit will lock a raster with an input signal as low as 30mV. Sync pulses of 10V amplitude are produced under ideal

Fig. 3 (left)—One method of obtaining a positive-going picture signal.

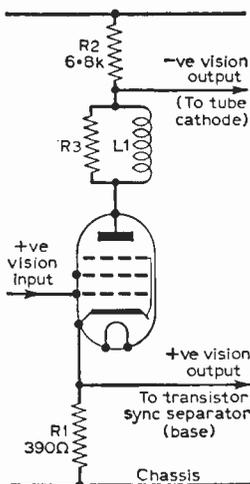

signal input conditions, the line pulses being positive-going and the frame pulses negative-going. Coupling to the appropriate generators should be by way of a capacitor—about 47pF for line and 680pF for frame are suitable. With multivibrator types of generator, the sync pulses are best injected into the cathode circuit rather than the grid.

The value of R1 will also have an effect on the circuit operation, and this should be as near as possible to the value shown.

Commercial Circuit

The arrangement used by Invicta is shown in Fig. 4. Here just one transistor is employed as the first sync separator. This is followed by a valve sync separator for obtaining line pulses of the correct phase for operating the sync phase-splitter stage for the "auto-sync" circuit. A further valve is used for separating the frame sync pulses and for phase correction.

Nevertheless, the circuit of Fig. 4 reveals how the video is coupled from the video amplifier to the transistorised sync separator. Although there is no by-pass condenser across the video amplifier valve cathode resistor, a certain degree of compensation is provided by C1 and R1 in the base circuit of the separator proper. This is a very interesting circuit and performs remarkably well in practice.

Both this and the Mullard circuit operate from the normal H.T. line of the set. This is why the transistors may appear to be inverted; the collector loads in Fig. 2 are R1 and R2, while in Fig. 4 the load is R2—connected, of course, to the negative chassis. The transistors are effectively operating in the "earthed emitter" mode, with C5 in Fig. 4, for example, taking the emitter to chassis.

WESTWARD TELEVISION

(Continued from page 290)

who supplied five 4½ in. image orthicon cameras, a vidicon camera, special effects equipment, etc.

Local Programmes

The anxiety of the early days of Westward, with temporary offices for staff, improvised hook-ups for wiring, the continuous tattoo of hammering, the perils of cement dust on the equipment should be over now, but Westward have already commenced the construction of additional premises on the Notte Street side of their building, mainly to cope with the constantly expanding staff required to produce more local programmes. Under the guidance of Stephen Mitchell and W. H. Cheevers, several local programmes have achieved high ratings for non-peak periods of the evening, notably "Spin Along", "Ordinary People", "Westward Diary" and a very well-edited local news service, with film inserts.

A few weeks ago, film scenes of a big warehouse fire in Plymouth were on the Westward News within forty minutes of being photographed. Not much time for processing, editing and adding a commentary, with all technicians clock-watching to complete a red-hot news assignment by 18.06 hours precisely!

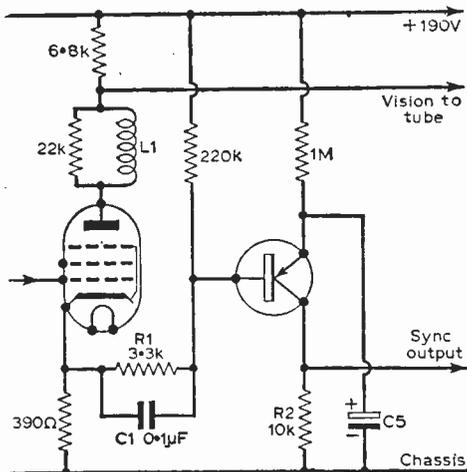


Fig. 4—The transistor sync separator as used in recent commercial receivers.

Again, a positive-going picture signal is required at the input (negative sync), and this can be obtained from the cathode circuit of the video amplifier valve as shown in Fig. 3.

Here R1 is the cathode biasing resistor which is normally by-passed by a small capacitor for compensation. The capacitor should be removed, and if this results in excessive overshoot or poor video response (impaired picture definition) the load R2 should be altered in value as a compensating measure. If the response is still poor, anode compensation, such as L1 and R3, should be tried.

JOIN THE PRACTICAL GROUP

PRACTICAL WIRELESS	2/-
Every Month	
PRACTICAL MECHANICS	1/6
Every Month	
Devoted to Mechanics, Science and Invention	
PRACTICAL MOTORIST	1/6
Every Month	
PRACTICAL HOUSEHOLDER	1/3
Every Month	

Underneath the Dipole

A MONTHLY
COMMENTARY

By Iconos

AT last I have caught up with the BBC's television jubilee film, "Television and the World". I missed a couple of showings of it on my home receiver, but saw it at last in a private cinema in Wardour Street. The occasion was a special viewing to the members of the Society of Film and Television Arts, when the director, Richard Cawston, also addressed the audience and answered questions. On the comparatively large cinema screen, this fine television film held my attention throughout its 85 minute run—and brought home more than anything I have yet seen or read, the almost terrifying impact of television throughout the world.

It is never too late

From the quiet Italian village, where we were shown the old folk, sat in front of a communal television set, learning to read and write, instructed by a patient and understanding teacher, in a programme called "It is never too late", Richard Cawston's film toured us around the army-operated TV station in Thailand, the brash commercials of Brazil, the 24-hour multi-channel service of Westerns in the USA, to the highly commercial mass production of portable transistor TV sets in Japan; and then back to England to the opulence of—yes—the ITV as well as the BBC Television centres. It was a most absorbing film essay, a real classic which demonstrated the hypnotic power of a medium that could become the greatest monster in the history of communications—if wrongly used. And the recurring fusillades of revolver shots from Western film sound tracks, heard in every part of the world, reminded one that action pictures have a greater mass appeal than words. The varieties of studio installations and equipments shown were of great interest. In the discussion afterwards, Richard Cawston, who wrote and directed the


film, referred to the superiority of British equipment, acknowledged even in the USA to be the best. British 4½ in. image orthicon cameras with British lenses are used in many of the leading studios there.

TV Architecture

One of the eye-openers in "Television and the World" is the different treatment applied by architects in the design and construction of new buildings for television.

All of these new purpose-made buildings are functional, utilising steel and concrete, and, no doubt, plastics and similar modern materials for fittings and decor. But some architects have appreciated the fact that because a structure is functional, it will not inevitably be beautiful. The brief views we had of the exterior of the Rome studios were superb examples of pleasing building lines applied to an obviously well-engineered interior layout. Some stations in which the transmitting

mas. arose from out of the studio building were impressive. Equipment layouts, too, varied a great deal, and the best looking seemed comfortable and pleasant to work in. The few shots of new British television studio exteriors were not at all impressive, with the exception of the BBC's Television Centre at White City. Let's face it—Britain was the first in television and most of the buildings are improvisations, conversions from warehouses, cinemas or theatres. Nobody appreciated just how big television would become in those early days, and in any case, building new from the ground took too long. The fine Granada studio premises at Manchester — probably the finest modern building in that city—and the much smaller Westward building at Plymouth—show that it can be done, and in their own way, take their places besides the wonderful BBC building. For the best improvisation of an existing building for television, I would give the "Oscar" to Anglia Tele-

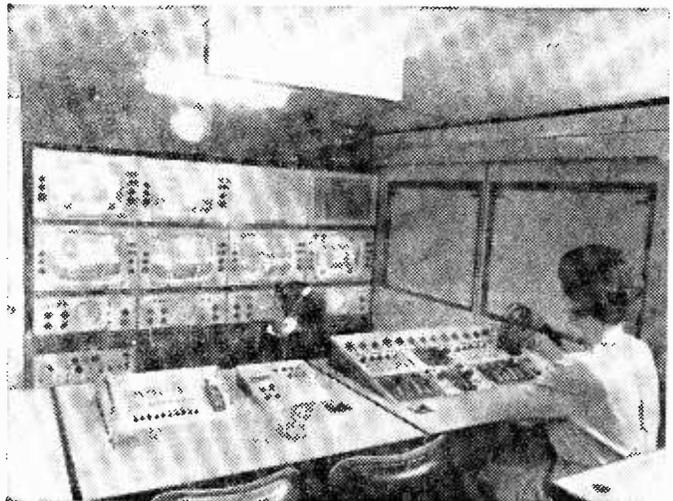

An interior view of the mobile outside broadcast vehicle which has been equipped for Telefís Éireann, the Éireann television service, by EMI Electronics Ltd.

vision, who virtually removed the inside of the Old Agricultural Hall, situated in the very centre of Norwich, without making much alteration to its external appearance. But the inside of the building is now a model layout, with three good stages and a superb engineering layout.

BBC Progress

I wonder if the BBC's "Television and the World" and many other good things television-wise that this colossus of an organisation has produced in the last year or so would ever have emerged if it had not been for the stimulus of competition with the ITV programme companies! In fact, the BBC TV owes a lot of its liveliness and vigour to this competition. The BBC seem to have captured a large proportion of week-end viewers, with the exception of the period when "Sunday Night at the London Palladium" is on, according to the T.A.M. ratings. The Equity strike has had its influence, of course, with the gradual disappearance of live plays and series, that is to say, videotaped television plays, which are virtually the same in production and style as if transmitted live.

They do have a presence and dash somewhat different from the television film dramas and comedies. America is the home of films produced in film studios for television as distinct from live television, made with television cameras and recorded on videotape. Hollywood is experiencing a boom in this type of film production at the moment. Large studios like Warner Brothers and M.G.M. have about eight film units working on television films and television series, compared with about two units on feature cinema films. These films have a large showing in the hundreds of television stations in the USA and many of them entirely recoup their production costs before being offered to Britain or any other countries. Public taste in England may be influenced in this direction, owing to the temporary shortage of "live" TV plays and their substitution by both old and new films.

"Tempo"

"Tempo", ABC-TV's programme about art, films and the theatre, produced by Kenneth Tynan, has been sniping at the film industry. Quite a salvo of

sneers was discharged in the programme which featured John Osborne, who remarked that film booking for the main circuits was largely in the hands of two illiterates! Another statement was that "There is also the special stimulus of the unique awfulness of most British films and the unfunny comedies about leaking houseboats and medical students". Almost at the same time, a weekly critical summary of all the London theatrical shows, published in one of the Sunday newspapers of which Mr. Tynan is the principal theatre critic, aroused the wrath of the West End theatrical managers' association to such a degree that they withdrew all advertising from this particular publication! "Tempo" is an angry-boy viewpoint of the offerings of show business, a strange product to come from ABC, whose basic assets are in the hundreds of large cinemas in all parts of the country and also in the huge and well-run ABPC film studios at Elstree. In any case, it is quite absurd for anyone to "knock" British film producers at a time when their reputation throughout the world has never been so high.

Sidney James

BBC's "Citizen James" series could not be said to have achieved a resounding success, when it first started. But there has been a steady improvement in the story, script and direction, and the combination of Sidney James and Sidney Tafler has now settled down in splendid form. The

richly corrugated face of Sidney James, re-cast into a character slightly reminiscent (but only slightly) of the part that Tony Hancock used to play, fills the home screen in a most welcome fashion. We are now all very much on his side. One of the best "Citizen James" episodes was that broadcast on Christmas Day, with James the victim of his uninvited partyguests. Credit must be given to the producer, John Street, and scriptwriters, Dick Hills and Sidney Green.

Censorship

The British Board of Film Censors is pretty liberal in outlook these days. The "U" "A" and "X" certificates are handed out to film makers according to a new code which is far removed from that of only a few years ago. George Redford or T. P. O'Connor, the Chief Film Censors of years ago, would have blushed at some of the films which are now released generally to the cinemas. The BBC is fairly broadminded in these matters, too, and occasionally an item comes through which seems hardly the type of entertainment for the family circle. On the other hand, the ITA is comparatively strict. When a programme company puts out a "Movie Magazine", "Close Up", or "Stars in the West" type of programme which includes clips of films on general release, these clips which are taken from "X" certificate films are scrutinised very carefully by ITA officials.

PRACTICAL WIRELESS

Chief Contents of the March Issue

Now on Sale 2/-

A DIGITAL COUNTER
 TRANSISTOR S.W. TUNER
 SERVICING TAPE RECORDERS
 EXPERIMENTER'S POWER PACK
 TRANSISTORISED GRID-DIP OSCILLATOR
 DIRECT-READING FREQUENCY-METER
 LOUDSPEAKER CROSS-OVER NETWORKS
 FAULTS IN VHF/F.M. RECEIVERS
 TRANSISTORISED FEEDER UNIT
 TRANSMITTING TOPICS
 CLUB NEWS
 ETC., ETC., ETC.

Television Filters

By T. Kemp

(Continued from page 228 of the February issue)

TELEVISION filters can often assist to suppress R.F. interference at the receiver itself, notably when the unwanted R.F. signal falls outside the major response of the receiver and yet is of a frequency which coincides with a spurious response of the receiver.

Pattern interference often results from an unwanted signal gaining admittance to the receiver along with the vision signal. An unwanted R.F. signal may also cause whistles on sound, but owing to the wider pass-band and response of the vision channel, patterns on vision are usually more troublesome than whistles on sound and more difficult to eliminate.

Interference Within the Pass-Band

When pattern interference is experienced by a group of viewers in close proximity using different sets, one can be almost certain that the frequency of the unwanted signal falls within the vision channel to which the sets are tuned. In such cases there is little that can be done at the set itself by way as a palliative, since the interference has a frequency similar to that of the wanted signal.

About the only thing that can be done is to contact the interference-investigation department of the Post Office so that the source of interference can be traced and eliminated. Full details of the type of interference and the number of viewers affected should be given.

Interference Outside the Pass-Band

When only one receiver is affected and other nearby receivers are completely free from the disturbance, the interfering R.F. signal is probably removed in frequency from the vision pass-band, but is entering the affected set by way of a secondary channel or spurious response. Not all sets have the same intermediate-frequency and oscillator-frequency, which means that secondary channels of one set may differ considerably in frequency from those of a different set.

A common secondary channel corresponds to the intermediate-frequency, but although the response to signals on that frequency is very low, a very strong interfering signal at the I.F. may well gain entry into the vision I.F. channel and cause pattern interference. As illustrated earlier on in this series, most receivers feature an I.F. rejector in the aerial input circuit, but unless this is tuned accurately to the interfering signal it will have little or no effect in attenuating the unwanted signal.

Image Frequency

Another secondary channel corresponds to the "second channel" or "image frequency." As an

example, an old set with sound and vision I.F.'s of 9.5Mc/s and 13Mc/s respectively would have its local oscillator working at approximately 32Mc/s when tuned to Channel 1 (the fact that the sound I.F. is below the vision I.F. means that the local oscillator is working below the signal frequency). This means that an unwanted signal falling in the region of 19Mc/s will beat with the oscillator signal and still produce the intermediate-frequency. This spurious 19Mc/s response is called the "second channel" or "image frequency."

The vision second channel of a more modern set with sound and vision I.F.'s of 19.5Mc/s and 16Mc/s respectively would fall around 77Mc/s when tuned to Channel 1, for here the oscillator frequency is above the signal frequency since the sound I.F. is above the vision I.F.

With really up-to-date sets using the standard I.F. (vision 34.5Mc/s and sound 37.5Mc/s) the vision second channel falls around 114Mc/s for Channel 1, for here again the oscillator frequency is above the signal frequency, being in the region of 79.5Mc/s when the set is tuned to Channel 1.

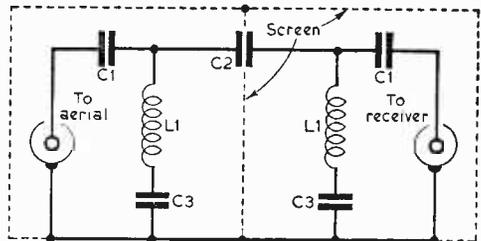


Fig. 15—The circuit of a practical high-pass two-stage filter. This is designed for 75Ω coaxial cable and to provide the characteristics of Fig. 16, the components should have the following values: C1, 68pF; C2, 33pF; C3, 500pF; L1, 0.24μH (produced by 7 turns of 16s.w.g. tinned copper wire on 2in. former).

Finding the Second Channel

The second channel frequency can easily be discovered for any set by subtracting twice the I.F. (sound or vision as the case may be) from the receiver's primary response (e.g. the sound or vision frequency to which the set is tuned) where the local oscillator frequency is below the signal frequency, and by adding twice the I.F. to the receiver's primary response frequency where the local oscillator frequency is above the signal frequency. The local oscillator frequency is always below the signal frequency when the vision I.F. is above the sound I.F. and above the signal frequency when the vision I.F. is below the sound I.F.

There are other spurious responses due to harmonics of the local oscillator and so on, and the spurious responses possessed by any set can be exhibited by injecting a strong signal from a signal generator into the aerial socket and then tuning the generator over the various ranges. Excluding signal generator harmonics and the set's primary acceptance, the second channel response should quickly be established, as also should the I.F. response. Apart from these, other relatively

weaker responses may also be observed due to the I.F. being produced by the generator signal and harmonics of the receiver's local oscillator.

The chief offenders, like the second channel and I.F. responses should to some extent be taken care of by the relevant rejectors in the set, but if such responses appear to be unduly strong the rejectors may require to be tuned more accurately.

How Patterns are Caused

Pattern interference is caused by an interfering R.F. signal heterodyning with the vision carrier. This produces a difference or beat frequency, which, while being within the response of the vision I.F. channel, arrives together with the normal modulation at the picture tube. In effect, the difference frequency is like modulation to the tube—a modulation that produces patterns instead of pictures.

The formation of the pattern superimposed on a picture is dependent on the difference frequency. For example, if the difference frequency is in the region of 2.5Mc/s the effect is to break up the line structure into a series of dashes with a consequent reduction in picture definition.

A slightly lower difference frequency produces a set of vertical bars, while a set of horizontal bars indicates that the difference frequency is below the frequency of the line timebase. The gentle drifting and twisting nature of some patterns means that the frequency of the interfering signal is itself somewhat unstable and is likely to emanate from a radiating television set or some other unstable R.F. source rather than from another transmitter.

Should the interfering signal itself be modulated by hum, within the main pattern are produced smaller subsidiary patterns within dark bands. Diathermy interference often provides an example of this kind, for in such equipment the activating R.F. is usually obtained by applying unsmoothed or "raw A.C." to a large power oscillator. The radiation is then heavily modulated at 50c/s and on a picture appears as a single horizontal band of herring-bone pattern occupying approximately one-tenth of the picture height. Moreover, the pattern formation may drift from time to time due to the dielectric effect of the patient altering the oscillator frequency.

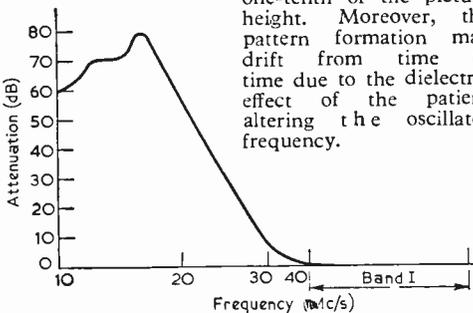


Fig. 16—The frequency/attenuation characteristics of the high-pass filter of Fig. 15.

Transmitters

Although it is beyond the scope of this article to deal with all the possible causes of pattern interference, one or two further examples may be of interest. R.F. interference from mobile and fixed commercial transmitters often causes trouble in

metropolitan areas of fairly low television signal strength. Interference of this kind is rarely consistent, but in some cases, where the set is very close to the station, the actual message may be heard on the receiver's speaker.

Process and heating appliances employing powerful R.F. generators are other offenders. These appliances are finding increasing favour in factories and small works, and they may not be efficiently screened. Although the Post Office and others are endeavouring to ensure that such signals are not radiated in the television bands, harmonics of the R.F. signals often find their way into spurious acceptance channels of nearby television receivers.

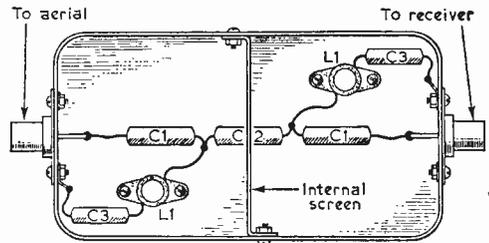


Fig. 17—A suggested construction for the filter of Fig. 15.

Furthermore, it sometimes happens that pattern interference is caused by a relatively "pure" R.F. signal which is far removed in frequency from the primary acceptance of the receiver. Interference in this case arises from the fact that nearby receivers are unable to reject the unwanted signal sufficiently. It thus breaks through the first tuned circuits and overloads the R.F. amplifier valve, which gives rise to the production of harmonic frequencies. Once these are produced they cannot be rejected by the following stages and so are amplified along with the required signals.

The Uses of Filters

In all cases where the interfering R.F. signal falls outside the normal receiver pass-band the resulting patterns can be cleared by the insertion of a suitable filter in the aerial download.

If the frequency of the unwanted signal is below the signal frequency, then a high-pass filter would solve the problem, for, as we have already discovered, such a device offers a high attenuation to signals below a specific cut-off frequency and low attenuation to signals above the cut-off frequency. Conversely, if the frequency of the unwanted signal is above the signal frequency the call would be for a low-pass filter, as this offers a high attenuation to all signals above and a low attenuation to all signals below a specific cut-off frequency.

The terms low-pass and high-pass mean just what they imply. A low-pass filter passes only the lower frequencies while a high-pass filter passes only the higher frequencies in relation to a designed cut-off frequency.

(Continued on page 299)



THE ONLY BOOKSHOP where you can buy Top

Quality Technical Books on NO INTEREST, TIME PAYMENT PLAN!

Look over the list. Select up to three books you wish to see. Send only ONE THIRD of the total purchase price (including postage) with order, then 20/- per month or 10/- each two weeks until books are paid for. (Offer open to all HOUSEHOLDERS, money refunded if not satisfied and books returned in clean condition within 7 days.)

TELEVISION

- No 13. TELEVISION EXPLAINED. Miller & Spreadbury. Hiffe. 12/6.
- No 10. TELEVISION RECEIVER SERVICING. Vol. 1. Spreadbury, 1961 edition. 382 pages. 25/-.
- No. J. PRACTICAL TELEVISION SERVICING AND TROUBLE SHOOTING MANUAL by Coyne. Vinyl covers. 425 pages. 34/-.
- No 6. TELEVISION SERVICING CYCLOPAEDIA. Coyne. Hard Vinyl covers. Hundreds of facts on servicing. Over 800 pages. 47/6.
- No 22. TELEVISION SERVICING HANDBOOK. Gordon J. Ling. Odhams. 30/-.
- No 40. TELEVISION RECEIVING EQUIPMENT. W. T. Cocking. Hiffe. 30/-.
- No 8. PIN-POINT T.V. TROUBLES IN 10 MINUTES. Coyne. Thousands already sold. This is a *must* for every T.V. enthusiast. 31/6.
- No 41. IMPROVE YOUR TELEVISION RECEPTION. John Cura. Hiffe. 5/- (C.W.O.).
- No 22. PIN-POINT COLOUR T.V. TROUBLES. Coyne. 550 pages. 47/6.
- No 38. COLOUR TELEVISION. NTSC SYSTEM, PRINCIPLES AND PRACTICE by Coyne & Townsend. Published 1961 by Hiffe. 85/-.
- No 42. BIGGER PROFITS IN T.V. (U.S.A. book. 12/- C.W.O.).
- No 43. TELEVISION SERVICING COURSE. (Theory of T.V. using U.S.A. T.V. sets as an example but very suitable for beginners. Hundreds of illustrations, quarto size, 192 pages. 27/6.
- No 60. RAPID T.V. REPAIR. G. Warren Heath, Gernsback. 23/-.
- No 62. T.V. IT'S A GINCH. E. Alsherr. Gernsback. 23/- C.W.O. only.
- No 65. SERVICING COLOUR T.V. Middleton. Gernsback. 23/-.
- No 95. NEW SHORTCUTS TO T.V. SERVICING. Lane, Gernsback. Vol. 1. 25/6.

TRANSISTORS

- No 9. PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES. Coyne. How to trouble shoot all kinds of transistor circuits. 525 pages. 47/6.
- No 18. REFERENCE MANUAL OF TRANSISTOR CIRCUITS. Mullard. 408 pages. 12/6.
- No 11. PRINCIPLES OF TRANSISTOR CIRCUITS. Amos. Hiffe. 21/-.
- No 20. PRINCIPLES OF SEMICONDUCTORS. Scroggie. Hiffe. 21/-.
- No 7. TRANSISTOR CIRCUITS HANDBOOK. Garner, Coyne. 410 pages, fully illustrated, more than 200 circuit diagrams. Vinyl bound covers. 39/6.
- No 44. TRANSISTORS AND THEIR APPLICATION IN TELEVISION—RADIO—ELECTRONICS. Garner, Coyne. Paper cover. 100 pages. 12/- C.W.O. only.
- No 98. HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS. Lane, Gernsback, latest book. Vol. 1. 160 pages. 25/6.
- No 94. TRANSISTORS—HOW TO TEST THEM. Gernsback. 15/6. U.W.O. only.
- No 63. TRANSISTOR CIRCUITS. Rufus P. Turner, Gernsback. 22/-.
- No 61. TRANSISTOR TECHNIQUES. How to work with and test transistors. 96 pages. 12/- C.W.O. only.
- No 75. TRANSISTORS—THEORY AND PRACTICE. Rufus P. Turner, Gernsback. 160 pages. 22/-.
- No 76. SERVICING TRANSISTOR RADIOS. D'Airo, Gernsback. 224 pages. 23/-.

MISCELLANEOUS

- No 4. LATEST INSTRUMENTS FOR SERVICING RADIO-TELEVISION. Coyne. 350 pages, vinyl covers. 26/-.
- No 45. PIN-POINT RECORD CHANGER TROUBLES IN 5 MINUTES. Coyne. 31/6.
- No 23. THE OSCILLOSCOPE AT WORK. Haas & Holloway. Hiffe. 18/-.
- No 43. RADIO & ELECTRONIC LABORATORY HANDBOOK. Scroggie. "Wireless World." Just published. 637 pages. 65/-.
- No 24. RADIO VALVE DATA. "Wireless World." 6/-. C.W.O. only.
- No 12. RADIO DESIGNER'S HANDBOOK. Langford-Smith. Hiffe. This is a mine of information. 1498 pages. 55/-.
- No 17. ELECTRONIC COMPUTERS. PRINCIPLES & APPLICATIONS. Ivaldi. Hiffe. 2nd edition. 25/-.
- No 21. BASIC MATHEMATICS FOR RADIO & ELECTRONICS. Hiffe. 17/6.
- No 19. WIRELESS SERVICING MANUAL. Cocking. 263 pages. 17/6.
- No 30. The Practical Hi-Fi Handbook. King, Odhams. 25/-.
- No 31. F.M. RADIO SERVICING HANDBOOK. King, Odhams. 25/-.
- No 23. FOUNDATIONS OF WIRELESS. Scroggie. Hiffe. 18/-.
- No 47. INDUSTRIAL ELECTRONICS. Coyne. 400 pages. 30/-.
- No 80. STEREO—HOW IT WORKS. Nurstein, Gernsback. 224 pages. 23/-.
- No 31. SERVICING PRINTED CIRCUITS. Moses, Gernsback. 224 pages. 23/-.
- No 32. MULLARD MAINTENANCE MANUAL. Latest Edition. 16/-.

No. 39. NOW YOU CAN TAKE A COURSE IN RADIO & ELECTRONICS FOR ONE TENTH THE USUAL COST!

As the result of a special exclusive arrangement, we are able to offer for the first time a complete home study course of 35 lessons designed to train any beginner to be an expert in radio and electronics. Lessons include test equipment, VHF/FM, TV, Radio, etc. All lessons are bound into one giant 8 1/2 x 11 in., 216 page volume, together with instructor's notes and test questions. Price for the complete course. Only 38/-. (Paper covers).

No. 1. SPECIAL OFFER COYNE ELEMENTARY PRACTICAL RADIO-TELEVISION SET OF THREE VOLUMES total 1,038 pages, sturdy Vinyl washable covers. £3 12s. 6d. the set!

These three volumes present the principles of construction, operation and testing of radio and television equipment in a SIMPLE, EASY TO FOLLOW manner.

By using NEW and DIFFERENT methods of explanation these books clearly explain the direct relation between the various parts of sets. This information is especially helpful in repair work where many times a burned out valve, resistor or transformer is actually caused by some other defective part of a circuit. Until the cause or the trouble is removed the parts would continue to burn out. For this reason, each part of the radio or television unit is explained, thus making the material especially helpful to the experienced radio man, as well as the amateur.

One very important way in which these books differ from many other radio and television books is that the publishers did not try to assume the "extent of technical knowledge" of the reader. Every subject is explained COMPLETELY—while at the same time keeping it brief and to the point.

You will find hundreds of photos, charts, diagrams, etc., in these books. These have been provided to make it easier to understand the explanations.

No. 19. REFRIGERATION SERVICE MANUAL. H. P. Manly.

Learn Refrigeration! This manual is a course in itself. Packed solid with information to enable you to do that repair job yourself. Used by many leading refrigeration firms as a standard reference. Features 364 pages together with 157 illustrations bound in cloth. An excellent buy at only 24/- plus postage.

NOTE. YOU CAN ORDER ANY TECHNICAL BOOK IN PRINT ON ANY SUBJECT THROUGH SIM-TECH.

Send name of book and publisher, if known, together with one-half deposit with order, balance payable 20/- per month until paid. Open to all householders or firms. Minimum order accepted, 10/-.

LIMITED OFFER! ACT NOW!

To SIM-TECH BOOK COMPANY (U.K.)

Mail Order Division, DEPT. PTV19, Gaters Mill, West-End, Southampton, Hants.

SEND (Insert Book number here) () () ()

Tick here if enclosing full price, we pay postage (Coyne Books only). Same 7 day money-back guarantee.

ENCLOSED please find ONE-THIRD purchase price amounting to £ s. d. with order. I agree to remit the balance as per offer.


NAME _____

ADDRESS _____

City _____ County _____

Postage charges: Order under £3 allow 1/6. Over £3 allow 2/- extra. Overseas Orders Promptly Shipped on receipt of full amount. Same guaranteed satisfaction.

More for less...

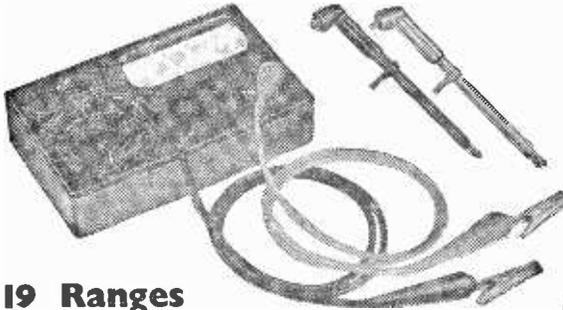

19 Ranges

- | | |
|--------------|--------------|
| D.C. Voltage | A.C. Voltage |
| 0—100 mV. | 0—10 V. |
| 0—2.5 V. | 0—25 V. |
| 0—10 V. | 0—100 V. |
| 0—25 V. | 0—250 V. |
| 0—100 V. | 0—1000 V. |
| 0—250 V. | |
| 0—1000 V. | |
| D.C. Current | |
| 0—100µA | |
| 0—1mA | |
| 0—10mA | |
| 0—100mA | |
| 0—1A | |
| Resistance | |
| 0—20,000Ω | |
| 0—2MΩ | |

List Price: **£9:10s.**
 complete with Test Leads
 and Crocodile Clips.
 Leather case if required 39/-
 Size: 5½ x 3½ x 1½ in.
 Weight: 1 lb. approx.

MM12

Designed to offer the widest possible range of accurate and reliable measurements at the lowest possible price, the versatility and usefulness of the Multiminor is now further extended by specially designed leads. These new leads, available at no extra cost, will accept crocodile clips or PRODCLIPS. The Multiminor takes full advantage of the possibilities of printed circuit techniques to achieve outstanding compactness and economy of weight. The scale is clear and open. The fine red coloured pointer and effectively damped movement facilitate easy and rapid reading. For use in Radio, TV, Electronics, Motor Vehicles, domestic appliances, workshop equipment, you'll find the Multiminor a great little meter.

Use PRODCLIPS with the MULTIMINOR (Pat. No. 748811)

These cleverly designed spring-loaded insulated prods are the complete answer to a long-standing problem. Press the trigger to open, release to grip. Keep your hands free no matter how difficult of access your test points may be. 15/- per pair

...with the

MULTIMINOR

Write now for illustrated literature to:—

AVO LTD

AVOCET HOUSE - 92-96 VAUXHALL BRIDGE ROAD
 LONDON - S.W.1
 Victoria 3404 (12 lines)



**Better, Brighter
 Picture Tubes**

**BRAND NEW THROUGHOUT
 excepting glass.**

- | | | | |
|--------------|---------|-----------|---------|
| 12in. ... | £4.10.0 | 14in. ... | £5. 5.0 |
| 15-17in. ... | £5.15.0 | 21in. ... | £7.15.0 |

New Silver Screen and Aluminising. All makes Mullard, Mazda, Emiscope, Cossor, Brimar, Emitron, etc.

**REBUILT MULLARD AND MAZDA
 TUBES**

- | | | | |
|--------------|---------|-----------|---------|
| 12in. ... | £3. 0.0 | 14in. ... | £4. 0.0 |
| 15-17in. ... | £4.10.0 | 21in. ... | £6.10.0 |

All Tubes Fully **GUARANTEED 12 MONTHS.** Dispatch same day. Cash with Order. Carriage and Insurance 10/-.

S.T.S. Ltd.

**35 POUND STREET, CARSHALTON,
 SURREY**

Telephone: WALLINGTON 9665

VACUUM
 ELECTRONIC
 LIMITED

**KEEPS YOU IN
 THE PICTURE**

**WITH THE
 FINEST REBUILT CATHODE RAY TUBES**

**12 MONTHS
 GUARANTEE**

<p>12" - 14" £4-15-0 15" - 17" £5- 5-0 21" £7-15-0</p>	<p>15/-</p> <p>ALLOWED ON RECEIPT OF OLD TUBE</p>
--	---

DELIVERY FREE IN LONDON AREA

WRITE PHONE OR CALL

VACUUM ELECTRONIC LTD.
 35, SACKVILLE STREET
 LONDON, W.1
 REGENT 6404

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

SPECIAL NOTE: Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

COMPATIBILITY

SIR,—Being confined to my house recently owing to illness, I had an opportunity of day-time viewing. During the course of this, I saw the afternoon experimental colour transmissions carried out by the BBC. I always understood that any colour system must be compatible, and must confess that the picture received on my black-and-white receiver was perfect. In fact, I would go so far as to say that it was infinitely better than the normal black and white transmissions which I receive. Apart from the various "stills" which were transmitted on various days, the documentaries, and travel films seemed to have a remarkable range of tones. The details seemed to stand out more, probably due to the very much better gradation of tones which were reproduced, and at times it even seemed that the picture possessed stereoscopic effects. It would be interesting to know whether other viewers feel the same way about this, or whether knowing it was a colour transmission, I was affected psychologically by the transmission. — G. ROGERS (Kingsbury).

AIRCRAFT FLUTTER

SIR,—In your December issue you included a letter from a reader seeking for a cure for aircraft flutter. Since the aerial picks up this nuisance, everything should be done to stop it receiving it in the first place, otherwise the AGC will not be able to remove the fluctuation in brightness. The aerial should be as directional as possible, and as the unwanted signal arrives from above, aerials with sloping elements should be avoided. If these precautions are taken on installation, coupled with fairly efficient AGC circuits, flutter will be completely eliminated in the majority of cases.—G. POWELL (Marden).

TV FILTERS

SIR,—I know how difficult it is to prevent slight printer's errors slipping in, and in the majority of cases, the fault is usually very slight and obvious. In case readers may not have noticed it, there is a small one in the December issue in the article under the above title where on page 122, Fig. 4. The correct formula should be

$$f = \frac{1}{2\pi \sqrt{(L.C)}} \quad \text{—J. SINCLAIR (South Nutfield).}$$

VALVEHOLDER TROUBLE

SIR, I recently had to service a set which made use of a printed circuit board, and the fault was a weak picture which the usual tests seemed not to cure. When going over the set I found that one of the valves was making poor contact on one pin only. This was in a ceramic type of valveholder into which the valve only sank a fraction of an inch, with the result that there was insufficient room for the springs to grip the valve pins properly. Unfortunately the only solution failing the removal of the valveholder and its replacement, was to bend all the legs slightly in different directions, until the side pressure made good contact on all pins. It appears to me that this is a failing with this type of construction, and I feel that there should be a different type of valveholder, preferably one with the normal type of straight-through socket.—D. PEARCE (Osford).

Television Filters

(Continued from page 296)

Improved Signal-to-Noise Ratio

It is also interesting to note that by the use of filters of this kind the signal-to-noise ratio of the receiver is enhanced. This is because the filters effectively improve the receiver selectivity without detracting from the required pass-band which, of course, is necessary for maintaining a high definition picture.

Design statistics for low-pass, high-pass and band-pass sections have already been given in this series, but at this stage it would be desirable to give a practical example. In Fig. 15 is given the circuit of a high-pass two-stage filter which offers progressively increasing attenuation to all signals falling on the low-frequency side of Band I, as shown in Fig. 16. The cut-off frequency is around 35Mc/s which prevents attenuation of the required television signals and gives almost zero insertion loss over Band I. The attenuation is greatest at 20Mc/s, but useful suppression is given at all frequencies below Band I.

A small tobacco tin is useful for housing a small filter of this nature, and in Fig. 17 is shown a suggested method of constructing the filter of Fig. 15. To avoid interaction between the two sections and to achieve high rejection ratios, the two sections should be separated by a screen as shown.

(To be continued)



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 304 must be attached to all queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

G.E.C. BT302

Could you please assist me in clearing this annoying fault on my receiver? There is a very fine black line permanently across the middle of the picture.—J. W. Davison (Newcastle-on-Tyne).

We suggest that the trouble may be due to V16—B729 or V15—an N379. C113 (0.1 μ F) should also be checked.

FERGUSON T105

A vertical white line about $\frac{1}{8}$ in. wide has appeared, slightly to the left of the centre of the screen. Adjusting the line hold away from the lock position, widens the line into what appears to be a fold in the scan. I have changed the sync separator, sync amplifier valves, line drive and line oscillator valves. I have also replaced the line output transformer. It would appear that with this model the EF80s used in the line drive and oscillator positions are critical, as it was necessary to try about a dozen before a satisfactory lock was obtained, but it was observed that with some EF80s, although the picture would not lock the vertical white line had disappeared. I am not sure of the function of the transformer situated between the line oscillator and EB91, although slight adjustment removed some ghosting from the picture. I have a circuit diagram of the set.—L. Long (Birmingham).

The transformer mentioned is concerned with the line oscillator and discriminator. Adjustment of the cores affects line phasing and frequency. The trouble described, however, appears to be in the line output stage. Check the boost reservoir capacitor and the components connected to the control grid of the PL81 valve.

BUSH TV53

This receiver has a Mullard type A.W.36-21 picture tube, and as it is beginning to show signs of low emission, I would like to fit a new one. I should be pleased if you could instruct me how to do this. I haven't a service sheet for this set. I would particularly like information on how to

remove the neck of CRT from focus assembly, etc. I have never had the chassis out of the cabinet of the receiver and would therefore like to know if this presents any difficulties.—J. Williams (Yorkshire).

Tube removal is not difficult if carried out in the proper manner, taking note of the positions of all removed plugs and sockets. Slacken the front control knob grub screws and pull off knobs. Take off the rear cover and speaker leads from right side of the cabinet, and remove the screws from the rear edge of each chassis. Disconnect the tube base socket and inter-chassis leads and plugs. Disconnect leads from scanning coils to the frame output transformer (a pair), and the two line coils leads, one above the preset form control, one to the top of the line output transformer. Remove the EHT cap to the side of the tube. Slide out both chassis. Lay cabinet face down, remove ion trap magnet (note position) and centring clamp magnet and scanning coils. Remove the tube mask screws and lift out the tube.

K.B. L.V.T.50

Could you please help me with the following fault which has developed on my set? The bottom of the picture is compressed and is now showing a black band to a height of three inches. I have had all valves tested and they seem to be working correctly.—G. Thames (Swansea).

You should check the front left side 6BW6 frame output valve, its 820 Ω bias resistor, 8 μ F bias decoupler and other associated components.

PHILIPS 2168U

Could you please supply me with any information you can, regarding this fault which has developed in my receiver? The screen has divided into two, horizontally, and gives two complete pictures one above the other. What is the cause of the trouble and could you give me the value of the condensers, etc., in the affected section.—G. Charles (Port Talbot).

You will have to check the two valves in the centre of the chassis (PCL82 and ECL80) and also the 3.3M resistor (orange, orange, green) in series with the hold control, if this latter component is at the end of its travel. Check other components associated with pin 6 and pin 2 of the ECL80 valve, if necessary.

AMBASSADOR TV4

I wonder if you can supply me with the following information regarding my receiver? I have the chassis of this set but it has no tube, and as I do not possess a service sheet I would like to know the make and type of tube generally used.—F. C. Hayes (Welling, Kent).

The Ambassador TV4 uses a Mazda CRM123 tube and is a 12in. table model.

MARCONIPHONE V.T.68DA

When this set is first switched on the sound is all right and there is a raster but no picture. After about ten minutes the picture appears and the set

(Continued on page 303)

LASKY'S RADIO

GREAT TV SCOOP

Prices Slashed!

110° SLIMLINE 17in. T.V. CHASSIS

As advertised last month. Few only still available. Chassis complete with 14 valves, tuner, etc. Less C.R.T. and line transformer.

LASKY'S PRICE 16 gns. Carr. & Ins. 7/6

As above with C.R.T. £21.10. Carr. & Ins. 19/6.

Chassis less valves, C.R.T. and Line Output Transformers. 99/6. Carr. 7/6.

C.R.T. type C17AF. £6.10.6. Carr. & Ins. 19/6.

Line Output Transformers. not original type. 29/6. Post 2/6.

S/vision chassis 38 Mcfs. Printed circuit with all valves. £5.19.6. less valves 59/6. post 5/-.

NEW C.R. TUBES

All sizes in stock at lowest prices. 17in. from 79/6. Send for list.

FERRANTI 17in. type TR17/10. 6.3 v., 0.3 amp. heater. New and unused £5.19.6. Carr. & Ins. 12/6.

REGUNDED C.R. TUBES

GUARANTEED for 12 MONTHS

Type	Carr. & Ins.
12in. round	£5 10 0 12/6
14in. rect.	£5 10 0 12/6
15in. & 16 round	£5 19 6 12/6
17in. rect.	£5 19 6 12/6
21in. rect.	£7 19 6 21/-

FRUSTRATED EXPORT ORDER

110° SLIMLINE CHASSIS

For 17, 19, 21 or 23 inch C.R.T.

NEW AND UNUSED BY FAMOUS MAKER 625 LINE TV CHASSIS

Complete with all valves, scanning coils and all controls. 13 position tuner unit, focus and deflector unit.

Valves included are:

- 1-PC89 1-EX786
- 3-PCP80 2-EP89
- 1-EB91 1-PC1A4
- 1-EH90 2-PLC82
- 1-PL36 1-ECC82
- 1-PY81 plus OA79 and OA81 diodes, Selenium rectifiers for HT supplies, line flywheel discrimination and RF delay.

Mains voltage. 230 volts, 50 cycles A.C. Aerial. 240-300 ohms balanced input. Picture stabilisers. Manual control eliminated. Picture height, width and focusing automatically adjusted by a series of new stabilising circuits. In addition the keyed automatic gain control provides a uniform picture irrespective of signal strength—even when channels are changed. Full circuit included. Chassis size, 15 x 54 x 13ins.

LASKY'S PRICE £13.19.6

Complete with all valves, etc., as described above, less C.R.T. Carr. and packing 17/6 extra.

LIMITED QUANTITY ONLY

Offered subject to being unsold

PRESS BUTTON TURRET TUNER

Covers all channels Band I and III also VIII/PM. I.P. 33-38 Mcfs. Operated by 5 press buttons. Complete with valves 30L15 and 30C15. Overall measures: 5 x 41 x 21in.

LASKY'S PRICE 49/6 Post 2/6

MAKER'S SURPLUS COMPONENT BARGAINS

WIDE ANGLE 38 m.m.

- Line E.H.T. Trans. Ferroxcube core, 9-16 kV 12/6
- Scanning Coils, Low imp. line and frame 12/6
- Ferroxcube cored Scanning Coils and Line Output Trans., 19-15 kV EY51 winding Line Trans. 25/-
- Frame Output Transformer. 5/-
- Frame or line block osc. Transformer 3/6
- Focus Magnets Ferroxcube. 7/6
- P.M. Focus Magnets, iron cored 6/8
- Duomag Focallisers 8/8
- 300 m/a Smoothing Chokes.. 7/6

STANDARD 35 m.m.

- Line Output Transformers 6.9 kV E.H.T. and 6.3 v. winding, Ferroxcube 12/6
- Scanning Coils, Low imp. line and frame 5/6
- Frame or line blocking Oscillator Transformer ... 3/6
- Frame Output Transformer.. 5/-
- Focus Magnets:
 - Without Vernier 5/8
 - With Vernier 7/8
- 200 m/a Smoothing Chokes.. 6/8

207 EDGWARE ROAD, LONDON, W.2.

ADDINGTON 3271J2.

BOTH OPEN ALL DAY SAT. Early Closing Thurs.

33 TOTTENHAM COURT ROAD, W.1.

MUSEUM 2605.

Mail Orders to Dept.P.T., Edgware Road.

ALL TUBES GUARANTEED 12 MONTHS Carriage Free Speedy Passenger Train despatch.

NEW

12"	MW 31-74 etc.	£5.5.0
14"	MW 36-24/44	£6.6.0
17"	MW 43-69 (limited)	£7.7.0
	CRM 171, 172	



COMPLETELY REPROCESSED

REBUILT, RESCREENED, REALUMINISED TUBES OF THE HIGHEST QUALITY

14"	£5.5.0
15"—17"	£5.10.0
21"	£8.0.0

TIME BASE COMPONENTS

Suitable for P.T. "Olympic" etc. For 17in. or 21in. 90° tube.	
L.O.P.T. (EY86 base etc.)	30/-
F.O.P.T.	15/6
Scan coils	19/6

ALL NEW. Connection data supplied.

Focus Magnets (Elac.)	15/6
Post etc. on each item	2/9

CONVERTERS, NEW. Mainly Ch. I and 9.

Ultra Y814, 815, 817 (with valves)	42/-
Cossor 930, 931, 933, 934 (with valves)	42/-
Pye V4, V7 series (less valves)	30/-
Salvage Turret Tuners—Contain useful movements, valve bases, coil biscuits, condensers, resistors	5/-
Post etc. on each...	3/6

LINE OUTPUT TRANSFORMERS

Direct Replacements for 500 sets.

Baird, T29, T163	53/-
T184, T187, T172, 2014, 1712	60/-
Bush, TV 11A, B; 12A, B; TVF 12A	
TUG12A, B; TRG 12A, B	45/-
TV12AM; TV22, 24; TRG24, TUG24	60/-
Cossor, 930, 931, 933, 934, 948, etc.	58/-
Ekeo, FS146; TSC13-14; T161	47/6
T221, 231; TSC311 etc.	55/-
Ferguson, 841, 2, 3; 941 to 945	55/-
990T-998T; 103-145T; 203-246T	66/6
Ferranti, 14T3, 14T4, 17K3, 17T3-4	45/-
14T2, T1205, T1215, T1225, T1325, T1405, T1415, T1425, T1505, T1825	65/-
G.E.C. and H.M.V. mostly 85/- to	60/-
Invidia, T101-104; T108-110	52/-
T114-126; T133-142	60/-
Murphy, V114C, V116C, V118C	45/-
V120C, V180, V178, V200, V202C	57/6
V240, 250	62/6; V214, 216
Philips, 114 UF/UM, 1115 U, 1437 U, 1446 U, 1726 U, 1746 U, 1747 U	65/-
383A, 463A, 563A, 663A	60/-
Pye, LV30, 16T, CS1, VT17	60/-
CTMA, V4, VT4, V7, VT7	52/6
Ultra, 814, 815, 817, 915, 917, VV80, Y/YA730, YVW84, VVY720, V710	85/-
(Complete assembly with U25)	
1453, 15/69, 17/50, 17/53, 17/59, 17/63-5, 17/70-1-2, 21/50, 21/60, 21/70-1-2	60/-
All Ultra Frame O.P.T.'s	26/6
Add post 2/6.	
100 mixed resistors, 1W-2W—6/6 post 1s.	

SKANTEST

Tests Line Output Transformers—Deflector Coils—Blocking Oscillator Transformers, etc. for shorting turns and open circuit. SKANTEST is a fraction of the cost of any similar tester available in this country. SKANTEST • Saves hours of work. • Is portable. • Easy to use. • Increases good will. No TV Serviceman should be without SKANTEST. SAVE TIME! SAVE MONEY! Free Leaflet available. £7.10.0. post etc. 5/-.

S.A.E. with enquiries please.

5 Westward Way
Preston Road, Harrow, Middx.
Tel: WOR 2663

WESTWAY RADIO

RADIO BARGAINS

SIGNAL GENERATOR



£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/6 extra. Coverage 100 K/c/s. 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 x 6 1/2 x 4 1/2 in. grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F., output continuously variable. 800 milli-volts. O.W. and mod. switch

variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

OSCILLOSCOPE FOR D.C. and A.C. APPLICATIONS


A high gain, extremely stable differential Y-amplifier (30 mV/C.M.). Provide ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurements of transistor operating conditions where maintenance of D.C. level is of paramount importance. Push-pull X amplifier; Flyback suppression; Internally Time-base Scan Waveform available for external use; pulse output available for checking TV line O/P Transformers, etc. Provision for external -1/P and C.R.T. Brightness Modulation. A.C. mains 200/250v. £15.15.0. P. & P. 3/- or 30/- deposit, plus P. & P. 8/- and 12 monthly payments of 26/6. Full 12 Months' Guarantee including Valves and Tube.



ALIGNMENT ANALYSER


A.C. mains 200/250 v. Provides: "Wobulator" (Swept Frequency) Operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s -80 Mc/s. Capacitance Measurement. Two ranges provided 0-80pF and 0-12pF. Special Facility enables true resonant frequency of any tuned oct. I.P. transformer, etc., to be rapidly determined. Cash price £6.19.6. plus 5/6 P. & P. H.P. terms 25/- deposit, plus 5/6 P. & P. and six monthly payments of 21/6.

TYPE MCI2

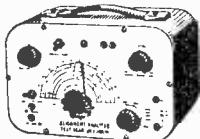

CHANNEL TUNER

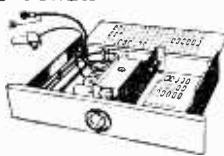Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series). I.F. 16-19 or 33-38. Also can be modified as an aerial converter (instructions supplied). I.P. plus 4/6 with knobs. 32/6 P. & P.



HEATER TRANSFORMER

To suit the above, 200-250 v., 6/-, plus 2/- P. & P.

LINE E.H.T. TRANSFORMERS

With built-in line and width control. 1kV. Scan coil, 90in. deflection on ferrite yokes. Frame O.P. transformer pl. 18 kV smoothing condenser. Can be used for 14in., 17in. or 21in. Tubes. Complete with circuit diagram.


29/6 Plus 4/6 P. & P.

As above, but for 625 lines. £2.10.0. plus 4/6 P. & P.

Focus Magnet suitable for the above (state tube). 10/- plus 3/- P. & P.

A.C./D.C. POCKET MULTIMETER KIT

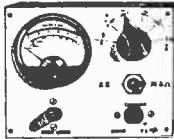2in. moving coil meter, scale calibrated in A.C./D.C. volts, ohms and milliamps. Voltage range A.C./D.C. 0-50, 0-100, 0-250, 0-500. Milliamps 0-10, 0-100. Ohms range 0-10,000. Front panel, range switch, wirewound pot (for zero setting), toggle switch resistor and rectifier, 19/6. P. & P. 2/-. Wiring diagram 1/-, free with kit.



RADIO & T.V. COMPONENTS (Acton) LTD.

23c HIGH STREET, ACTON, LONDON, W.3
All enquiries S.A.E. Goods Not Despatched Outside U.K.

D. & B. TELEVISION

Phone: Cherrywood 3955
Dept. B3 131 & 131a KINGSTON ROAD
SOUTH WIMBLEDON, LONDON, S.W.19

"Compare our prices with any others"

For the FINEST, FASTEST SERVICE in the COUNTRY We are open from 10 a.m. Until Midnight. (1 p.m. Wednesday.) For any information or problems you have, Call or Phone, we are always pleased to help.

NEW!
SEND FOR OUR COMPREHENSIVE L.O.P.T. Scan Coil L.B.O., F.B.O., F.O.P.T. LIST. Prices of nearly all makes and models, 2/6, post 6d. Invaluable as a service aid. The finest list ever compiled.

HUGE PURCHASE ENABLES US TO SELL TRANSISTORS AT THESE ASTONISHING PRICES

Mullard: OC44, 9/-; OC45, 8/-; OC70, 61/-; OC71, 5/-; *OC72, 61/-; OC76, 7/-; OC78, 7/-; *OC81, 7/-; *OC8D, 61/-; G.E.C.: GET874, 8/-; GET873, 7/6; *GET114, 5/-.

* Available in matched pairs at 1/- extra.
Mullard Diodes: OA70, 2/9; OA79, 2/9; OA81, 2/9; OA91, 3/6. G.E.C.: GEX34, 3/3.

TURRET TUNERS, Various Makes: 10, 16, 38 Mc/s, 40/-
ECKO 221/283. TUNERS. Special Price: £2.10.0, including valves.

EXAMPLE OF TRANSFORMER LIST

		L.O.P.T.		SCAN COILS	
ECKO:		(New)	(Used)	(New)	(Used)
221, 283	...	57/9	30/-	—	—
284, 231	...	57/9	—	—	—
311, 327, 310, 326	...	57/9	—	—	—
FERGUSON:		(New)	(Used)	(New)	(Used)
103T, 105T	...	69/9	35/-	60/-	35/-
992/4/6/8	...	69/9	35/-	60/-	35/-
PYE:		(New)	(Used)	(New)	(Used)
V4, VT4, V7	...	55/-	35/-	55/-	35/-
VT7, CTM4	...	55/-	35/-	55/-	35/-
MURPHY:		(New)	(Used)	(Used only)	
V214, V240, V250	...	68/6	35/-	45/-	

REGUNNED CATHODE RAY TUBES

all with 12 months' Guarantee
ALL MAKES: 12in., £3.15.0; 14in., £4.5.0; 17in., £4.15.0.
ADD: 10/- for 90°, 15/- for 110°, 5/- for Electrostatic Types.
10/- allowance on old tube if in good condition.

ALL VALVES ARE SOLD SUBJECT TO FULL GUARANTEE

CURRENT VALVE LIST

AZ31	8/8	ECC84	7/8	KT38C	8/-	R18	10/-	UL44	10/9	6U4	10/-
B36	5/8	ECC85	7/8	KT39	8/8	8P41	2/3	UL84	7/3	7C5	8/9
CBL31	19/-	ECC80	5/-	KT61	8/3	8P61	2/3	U85	14/8	7C9	7/-
CCH35	12/6	ECH21	12/3	KT63	8/3	U22	6/8	U9	6/3	787	8/9
CL23	10/-	ECH35	9/-	KTW61	9/9	U34	10/-	U941	6/1	7Y4	6/9
D77	3/-	ECH42	7/8	KTW63	5/8	U35	12/-	U985	6/8	10P4	4/6
DAF91	6/8	ECH81	7/8	L3	5/3	U28	9/8	W77	4/1	10C1	10/-
DAF96	8/8	ECL80	6/8	PCC84	8/1	U31	7/-	Z77	3/-	10C2	13/-
DF91	3/3	ECL82	9/3	PCC89	8/0	U37	18/9	5U4	4/8	10P13	8/-
DF96	6/8	ECL83	11/3	PCF80	7/1	U50	5/8	5Y4	8/8	10P14	8/-
DH63	8/-	EF39	4/3	PCF82	7/9	U52	5/8	5Y3	5/8	12A7	6/8
DH77	4/8	EF50	1/8	PCF86	14/6	U191	9/-	5Z4	10/-	12A7	5/8
DK91	5/8	EF85	6/3	PCF88	9/0	U282	14/6	6AL5	3/-	12AX7	6/8
DK96	6/8	EF86	8/8	PCF89	14/6	U301	17/8	6AT6	5/8	19HG6	14/8
DL91	5/8	EF89	6/8	PCF85	15/-	U809	12/-	6Y8G	5/8	201P	8/8
DL92	5/8	EF92	4/-	PL33	8/-	UAF42	8/-	6BW6	7/8	201L	12/6
DL94	6/8	EL33	7/8	PL36	9/8	UB41	7/9	6CD6	25/8	20P1	12/6
DL96	6/8	EL38	12/-	PL35	14/8	UBC41	7/9	6F1	4/6	20P3	12/6
EA80	7/8	EL81	7/8	PL37	8/8	UBF89	7/8	6F2	3/6	20P4	12/6
EAF42	7/9	EL84	6/8	PL32	6/8	UC34	12/6	6F12	3/6	20P5	14/8
EB41	6/8	EM80	8/8	PL83	9/8	UC85	7/9	6P13	6/8	278U	14/-
EB91	3/3	EM81	8/8	PL84	8/8	UCF80	14/8	6P14	9/-	30C1	7/8
EMC33	4/6	EM84	9/8	PY41	7/-	UCI21	12/3	6P15	9/-	30P11	9/3
EMC41	7/8	EY51	7/8	PY32	10/-	UCH42	7/-	6P33	6/8	3011	7/-
EF80	7/8	EY86	7/8	PY80	6/-	UCI51	8/8	6L1	12/6	30P4	10/9
EF89	8/3	EZ40	6/3	PY81	6/-	UCI83	12/6	6L6	9/8	30P12	7/8
EHL31	20/-	EZ41	6/8	PY82	6/-	UF42	3/9	6V6	5/-	52K U	10/-
ECC81	4/8	EZ80	6/-	PY83	8/-	UL41	7/-	6118	8/-	53K U	10/-
ECC82	5/8	IC232	8/8	PY88	12/-	UL44	10/9	6119	12/-	54K U	8/8
ECC83	6/3	IC234	12/8	PZ30	8/-	UL48	7/-	68N7	4/6	15B2T	14/-

These are only examples of our values; if you do not see what you require send stamped addressed envelope for special quotation.

We pride ourselves that we can obtain and supply any TV spare, OUR GIGANTIC STOCKS INCLUDE: Line, Frame and Sound Output, Line and Frame Blocking, Osc., Trans., and Scan Coils for any make or model Television. Please ask us for ANY components you may require we are almost certain to have them.

TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra. Postage on Valves, 6d. each. C.R.T.s 12/6 inc. insurance. SATISFACTION ASSURED. RETURN POST SERVICE.

(Continued from page 300)

continues to work normally. I have changed the tuner valves.—R. T. Martin (Leicester).

Your letter does not state whether the brilliance of the raster is controllable or not. If the raster is bright even with the brilliance turned down, suspect the tube of having a heater/cathode short and install a heater isolating transformer (check tube heater voltage which may be 8.5V, 10.5V or 13V). If the raster is quite normal, however, check the vision detector crystal diode XL1 (0A70 or equivalent), the Z152 vision I.F. amplifiers and the video amplifier N153 and associated components.

COSSOR 947

According to service chart this set is fitted with coils for channels 1 to 5 and 9 and 10. It is a 12 channel turret tuner. I understand that the new "Grampian" transmitter has opened at Aberdeen on channel 9. Could you advise me what steps I must take to be able to receive this station. At present I get only faint sound and raster but no picture.—D. Allan (Fife, Scotland).

We would advise you to ensure that an efficient channel 9 aerial is in use and that the tuner unit valves 7AN7 (PCC84) and 8A8 (PCF80) are in good order, particularly the former.

SOBELL 171 TV

Recently I took out the coil biscuits and cleaned the contacts of the tuner but after replacing them I found that the volume on BBC (channel 4) had decreased considerably. Could you please tell me which trimmer on the tuner I might adjust to get the volume back to normal? The lines on the picture are spread out towards the top of the screen. I believe this is the fault of a valve. Could you tell me which ones to check?—B. L. Brown (Northampton).

With regard to the turret tuner, first switch to channel 4 and set the fine tuner midway. Remove both knobs and insert a non-metallic trimming tool into the hole next to the spindles (use a knitting needle with a shaped end) and tune for maximum sound. To remedy the bottom compression, check the rear centre PCL83 valve and the 100 μ F (25VW) electrolytic capacitor to the left of the valve.

McMICHAEL M22T

I am experiencing trouble with the picture of my set. At first, the top few inches of the picture appeared to be stretched upwards, and the left-hand quarter of the picture stretched to the left. I managed to cure the top of the picture by adjusting the frame linearity control, but the left side remains the same. I wonder if you could tell me also where the width control is on this set. At the moment the picture is much too wide. When the new BBC relay station opens at Oxford early in 1962 (channel 2), will a channel 2 coil be all that is needed to convert the set?—A. Inness (Oxford).

The width adjustment is a plug and socket (three position) on the rear right side of the receiver. Near by is the line linearity slider which expands

and contracts the left side of the picture in relation to the right. Channel 2 coils may be obtained and clipped into the required position on the turret when desired. Inspection of the existing coil biscuits will show the method of fitting. The bottom cover of the tuner springs off to expose the turret.

REGENTONE BIG 12/5 AND ULTRA V815

The picture does not completely fill the screen, but after the set has been working a while, it improves slightly. The focus too is slightly out of adjustment. A new EHT rectifier has been fitted which made the picture considerably better. This did not last long, however, and now there is no EHT at all. The heater of the EHT rectifier shows continuity, as does the heater winding on the line output transformer. At the moment I am using an Ultra V815, and though this has quite a reasonable picture, it lacks height at top and bottom. The bottom of the picture also has a thin line of increased brightness. Would it be possible to advise me on both these queries?—N. May (Leamington Spa).

Regarding the Regentone receiver, you should disconnect the EHT lead from the top of the EHT smoothing capacitor (trace lead from U25) which could well be leaky. Have the 20P1 tested. If the resulting picture still lacks width, change the 14A97 metal rectifier on the front right side. With regards to the Ultra, you should check the 20P3 valve (front right) and the 470k (yellow mauve yellow) resistor which is the anode load of the 6K25.

BUSH TV80

When switching on, the sound comes up quite quickly, but there is no picture or raster for about four to five minutes. When the picture first appears it is very dark and just a little lighter at the top. It is also a little small in size but after about 20 seconds it is perfect, but then comes about 10 seconds of a howling noise. From then on the set seems to be working perfectly with all the controls reacting quite normally. I have checked all the heaters and noted that the CRT lights up almost as the set is switched on. I have replaced V9, the PY81 booster diode and also V7, a PL81. I am about to replace the EY51 EHT rectifier (V8). Could the fault lie here or could there be something else which may need replacing?—R. Perriton (Plymouth).

We should advise you to check the PCF80 video amplifier, ensure the ion trap magnet on the rear of the tube neck is correctly adjusted for maximum brilliance and check the video amplifier components if necessary.

PHILIPS 1758U

I should be most grateful for your advice as to the most likely cause of a fault in the above set. There is intermittent bending of the verticals, the setting of the line hold is very critical and a picture can only be held with both the contrast and brightness retarded. Any attempt to advance either of these controls results in either a broad black line down the centre of the screen or a complete breaking up of the picture into black and

white diagonal tears.—D. Mowatt (London, S.W.19).

You should replace the PL81 line oscillator valve and the 47pF capacitor to pin 2 of this valve base.

BUSH TV66

The trouble is a persistent form of flashing on the screen, which appears to be connected with the line timebase circuit. The flashing is generally most noticeable just below the centre half of the screen. I have put in new valves in the positions associated with the line timebase, namely, the ECC82, PL81, PY81, and the EY86. Also, on the advice of a friend, I have replaced the two small metal rectifiers used in the discriminator — line sync circuit — but with no improvement.—H. Richardson (Norwich).

We are not quite clear as to what is meant by "flashing on the lower centre of the screen." If the effect originates from one side and virtually streaks to the other, a discharge in the line output transformer or scanning coils is most likely. If however that effect is of black lines bunching together, the PCL83 frame timebase valve should be suspected. Another cause of flashing, but one which is usually accompanied by varying width, is a partial breakdown in the 140pF 6kVW capacitor (disc type) from the PY81 to the coarse winding tapping on the rear of the line output transformer.

FERGUSON 105T

When the set is switched on it takes about two minutes for the picture to appear, although the sound comes on quickly. Sometimes the picture is distorted, when first switched on, with the images moving quickly across the tube to the left, and also slanting to the left from top to bottom. The line hold does not correct this. Also when the brightness is advanced, the picture blows up slightly and goes out of focus. If you could offer advice on these faults, I should be very grateful.—N. Brown (Frome, Somerset).

This fault is caused by some of the valves becoming slightly weak and requiring a greater time to stabilise. The valves concerned are those in the line oscillator and discriminator section. Also ensure that the line hold control is adjusted (after the set has been on for several minutes) so that the picture jumps into line lock when the aerial is removed and replaced.

MURPHY V240

Could you please help me to find the trouble with my 14in. Murphy V240 set? While watching a programme recently, the screen suddenly went blank. The sound was not affected.

Previous to this occurrence the brilliance and contrast controls were set mid-way for a good picture. Now, with the brilliance full on and the contrast half on, the screen is still blank but there is a faint white outline of the faces or subjects on the screen. With the contrast also full on, the

screen lights up but the picture goes negative. The picture does not blow up and the focus seems correct.

The line whistle is still there and I have checked the ion trap magnet for maximum brilliance.—H. Marshall (London, N.W.2).

The symptoms indicate a faulty C.R. tube, but we suggest that you check that the ion trap magnet has not slipped from its setting of maximum brightness before discarding the tube.

PYE VT17

Immediately the picture fills the screen it collapses into a vertical white line. If the set is left on, it keeps repeating this procedure. The EY86 goes out as the picture collapses. I have replaced this valve with no result. The sound is not affected.—D. Davies (Ronkswood, Worcestershire).

This fault could be due to an inter-electrode short on either the PL81 line output valve or else the PCF80 line oscillator, just outside the screened compartment. You may be able to check these valves by tapping them when the set is operating, when flashes and disappearance of the line scan will indicate the fault.

PHILIPS

After the set has been working for a while the picture starts to "blink," with a definite "blip" on the sound, on ITV. Moving the fine tuner cures this for a few minutes, but then it returns. None of the other controls will stop this fault. On BBC the picture tears to the left in about $\frac{1}{2}$ in. wide strip, anywhere on the screen, depending on the scene and camera (sometimes on close-ups the picture is perfect). The sound is perfect all the time.—N. Mylis (Bristol).

The line pulling experienced on BBC is purely due to reflected signals on the aerial and some adjustment will have to be made to the aerial to clear this effect. There is no adjustment which can be made to the set which can clear it except to reduce contrast (to weaken the interfering signal).

The blinking effect on the ITV channel could be a little awkward to eliminate as it is probably due to inadequate decoupling or a poor chassis return path. Try extra decoupling with a 0.001 μ F capacitor on all tuner unit leads and check chassis connections, etc.


QUERIES COUPON

This coupon is available until MARCH 22nd, 1962, and must accompany all Queries sent in accordance with the notice on page 300.

PRACTICAL TELEVISION, MARCH, 1962.

LAWSON

DIRECT REPLACEMENT Reprocessed TUBES

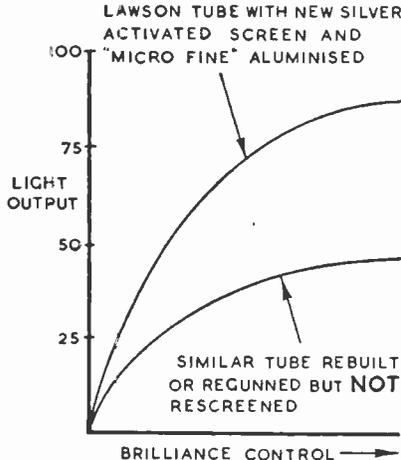

12 MONTHS FULL REPLACEMENT
GUARANTEE

ENGINEERS WITH EXPERIENCE

Know that as a tube gets old, not only does it become Low emission but the light efficiency of the Phosphor Screen also deteriorates (up to 10% per year). This deterioration of the Screen obviously continues if the tube is only rebuilt or regunned.

Don't risk a "DEAD SCREEN", enjoy the brilliant crisp high definition of a LAWSON TUBE. Tubes which are absolutely BRAND NEW throughout (excepting the glass), and which incorporate the very latest CRT developments. New silver activated screens, "micro fine" aluminising, high efficiency gettering, plus Brand New electron guns by Britain's premier manufacturers, Mullard, Mazda, Emiscope, Cossor, Brimar, Emitron, English Electric, etc.

ALL MAKES AND TYPES FROM STOCK

LAWSON. The ONLY replacement tubes, for which all types are guaranteed, correct and direct plug-in replacements.

12" — £1.10.0
14" — £5.5.0
15-17" — £5.15.0
19", 21", 23" also available

C.O.D. or C.W.O.

10/-

Gladly refunded if you wish to return your old tube (excepting 12")

CARR. and INS. 7/6

EXPRESS PASSENGER SERVICE—
Orders received by 3 p.m. are dispatched same day.
Special direct services to Scotland and Ireland.
"YOU HAVE A CRT PROBLEM? Our engineers are Specialists, may we help."

LAWSON TUBES LTD. TEL. 379g
156. PICKERSLEIGH RD. MALVERN. Worcs.

B. E. HAMPSHEIR

(RADIO - TELEVISION)

23 NORTHCROSS RD., LONDON, S.E.22

NEW BOXED VALVES

C.W.O. 1/- POSTAGE ON ALL ORDERS UNDER £1

B35	8/6	EL83	9/-	U403	10/-	1S5	7/6
B65	8/6	EY51	12/-	U404	10/-	6AL5	7/6
DAC32	10/-	EY86	12/-	UAF42	10/-	6AT6	7/6
DAF91	7/6	HD14	5/-	UBC41	10/-	6BA6	10/-
DF91	7/6	KT33C	8/-	UBF80	10/-	6BR7	12/-
DK91	8/6	KT36	8/-	UCH42	10/-	6D2	10/-
DK92	8/6	N17	7/6	UCH81	10/-	6F1	14/6
DK96	10/-	PCF80	11/-	UCL82	10/-	6P28	15/-
DL35	9/6	PCF82	9/-	UCL83	12/6	7K7	10/-
DL94	7/6	PCL82	9/-	UF41	8/6	7Y7	10/-
DL96	7/6	PCL83	12/-	UF42	7/6	9BW6	8/-
EB91	7/6	PENA4	18/-	UF85	10/-	10P13	14/-
ECC81	9/-	PL36	17/6	UF89	7/-	12AT6	9/6
ECC82	9/-	PL81	16/6	UL41	10/-	12AT7	10/-
ECC84	9/-	PL82	12/-	UL81	7/6	19BG6G	13/-
ECH21	11/6	PL83	12/-	UY41	10/-	20D1	8/6
ECH35	11/6	PY80	10/-	UY85	10/-	20F2	14/6
ECH81	11/6	PY81	10/-	W77	6/6	20L1	14/6
ECL80	12/-	PY82	10/-	Z77	6/6	20P1	14/6
EF50	7/6	PY83	12/-	ID5	9/-	20P5	13/-
EF80	7/6	R19	15/6	IFD9	8/6	30C1	10/-
EF91	7/6	RM4	15/-	IP11	8/6	35W4	6/6
EL33	11/6	U25	18/6				



Outstanding offer of

guaranteed
rebuilt cathode
ray tubes 59/6

each

12" & 14" Types MW31-74:
MW 36-24: SE 14-70: 4/14
C 14 FM

Carriage paid
CASH WITH ORDER

Tates
ELECTRONIC SERVICES LTD

3 Waterloo Road,
Stockport, Cheshire

Telephone: Stockport 7301

SERVICE SHEETS

SERVICE SHEETS. Television 4/3; Radio 2/9. DARWINS, 19 George St., St. Helens, Lancs.

SERVICE SHEETS. Radio, TV, 5,000 models. List 1/-. S.A.E. enquiries: TELRAY, 11 Maudland Bk., Preston.

SERVICE SHEETS. Radio and TV 4/- each. List 1/-. All orders dispatched on day received. Also Manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 church Road, Tunbridge Wells, Kent.

SERVICE SHEETS; also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20 Extension, Shepherd's Bush Market, London W12 (Phone: SHE 3052).

SERVICE SHEETS

For all makes of Radio and Television—1930-1962. Prices from 1/-. Free fault-finding guide with all Service Sheets. Please send S.A.E. with enquiries. Catalogue of 6000 models, 1/6.

Special offer of 125 Radio/TV Sheet covering 370 popular models, 20/-.

HAMILTON RADIO

Western Road, St. Leonards, Sussex

GENUINE SERVICE SHEETS: Radio/TV, 5/- each, post paid. REDWATT TUBE DISTRIBUTORS, 41 Denmark Street, Wakefield, Yorks.

SERVICE SHEETS: Radio/Television, 4/- each, list 1/-. All old and modern receiver sheets available. Faultfinder files 2/- each. List now available 1/-. KAYBRO PUBLICATIONS, 44 Old Bond Street, London, W1.

SETS & COMPONENTS

REBUILT TUBES with 13 months' written guarantee. New Gun Mounts. 12in. £4/17/6; 14in. £5/7/6; 17in. £5/17/6; 21in. £7/10/-. 110" Tubes 5/- extra. Carriage free. Terms C.W.O. ALLAN TUBES, 49 Barnehurst Avenue, Barnehurst, Kent.

1/6 each for TESTED VALVES?

YES! EF80, 6BW7, 6BX7, Z152, EF91—1/6. Others at similar top-value rates—all fully tested.

Send S.A.E. for list.

Clive Middleton, 11 Hazelwood Road, Hale, Altrincham, Cheshire. Altrincham 5025.

BAND V Receiver. Ready wound coils and components in stock. S.A.E. list. AJAX ELECTRONICS, 572 Fulham Road, London S.W.6.

BRAND NEW VALVES AND TUBES! 12/14 in. £4. Also others, Mullard EMI, etc. U25 and PY32, 9/11, PL81 7/11, U801 17/6, ECC81/2/3 5/-. PCC84/PCF80 8/6.

Numerous other bargains

P. BEARMAN

PANK AVENUE, NEW BARNET
Tel: Bar 1934
(& Ansaphone Service)

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager "Practical Television", Tower House, Southampton St., London, W.C.2.

NEW and Surplus Valves. fully guaranteed, from 5/6 each. Also reclaimed valves, perfect, from 1/6 each. Many genuine valve bargains. S.A.E. for complete list. LEWIS, 46 Woodford Avenue, Ilford, Essex.

Television Picture Tubes

Twelve Months

Manufacturers' Guarantee

12 inch ALL Types £5. 0. 0
14 inch " " £5. 10. 0
15 inch " " £7. 0. 0
16 inch " " £7. 0. 0
17 inch " " £7. 0. 0
21 inch " " £8. 15. 0

Deposit 20/- plus 12/6 carriage
Four Speed auto-change Record
Players £15.15.0.

Cathode Ray Tube Service

35 Brookwood Road
St. Paul's Cray, Kent
Orpington 21285

13 CHANNEL Turret Tuners less valves 17/6. P. and P. 2/6. CAPITAL TELEVISION, 382 Brockley Road, Crofton Park, SE4.

TV SPARES

LINE OUTPUT

TRANSFORMERS

A few examples from our extensive range.

TELEPHONE ORDERS SENT SAME DAY C.O.D.

Alba T301, 304, 394, 484, 494, 42/6.
Bush TV53, 69/6; TV24C, 89/6.
Ekco T221, 231, 311, 284, 330, 65/-.
Ferguson 993/6/8, 66/9.
Ferranti 14T3/4/5, 47/6; 14T2/T1225, 62/6.
H.M.V. 1824/9, 1840-8, 2805-5902, 69/6.
Masteradio T917, TE77, T409/12, etc., 58/6.
Murphy V240/250/280, 65/-; V200, 49/6.
Pye/Pam/Invicta V4/7, VT4/7, LV30, FV1
908-958, T118-120, 55/-; CS17, etc., 75/-.
Philips 1114U, 1115, 1437, 1446, 89/6.
Ultra VT9/17, etc. with U25, 105/-.

BARGAINS IN USED SPARES:

38 mg turrets, 10/- each.
Pye VT4 sets for spares, 10/- each.
A few other makes available. Callers only. We stock or can obtain most L.O.T.'s Scan Coils, Frame O.P.'s and spares.

PLEASE SEND S.A.E. FOR IMMEDIATE QUOTE

Callers welcome. Open all day Saturday. Terms C.W.O. or C.O.D. Add 3/6 P. & P.

TELEVISION CONSUMER SERVICES LTD.

112 CAMBERWELL RD., S.E.5.

RODNEY 7917

DON'T READ THIS

unless you repair Radio and TV sets. Halve the cost of repairs by using our surplus or reclaimed Valves and Tubes. Most comprehensive selection at keenest prices. All valves re-tested before despatch and guaranteed to be in good working order.

2X2	4/6	D77	2/-	PCL83	6/-
6AB3	4/6	DH77	4/6	PL33	4/6
6AC7	4/6	EB91	2/-	PL38	10/-
6AL5	2/-	EBC90	4/6	PL81	4/6
6AM3	4/6	EF80	2/-	PL82	4/6
6BG6	12/6	ECC81	3/-	PL83	4/6
6BL3	6/-	ECC82	4/6	PL820	7/6
6BX6	3/-	ECC83	4/6	PY31	4/6
6CS	6/-	ECC83	6/-	PY32	7/6
6CD3	17/6	ECC88	6/-	PY90	4/6
6CH6	6/-	ECF80	6/-	PY81	4/6
6CJ6	4/6	ECF82	6/-	PY82	4/6
6F1	2/-	ECL80	4/6	PY83	4/6
6F12	2/-	EP50	2/-	PZ30	6/-
6F13	6/6	EP64	4/6	SP41	2/-
6F14	4/6	EP80	3/-	SP61	2/-
6F15	4/6	EP91	2/-	SU61	4/6
6F33	4/6	EL38	6/-	R19	10/-
6K25	7/6	EL42	7/6	T41	10/-
6L1	6/-	EL81	4/6	T41	4/6
6L18	7/6	EL821	6/-	U21	10/-
6L19	7/6	EN31	4/6	U24	10/-
6LD20	6/-	EY31	4/6	U25	12/6
6P28	6/-	EY31	4/6	U31	4/6
6P38	6/-	EY36	7/6	U35	7/6
6U4	7/6	HV81	6/-	U35	4/6
10C2	6/-	HVR2	5/-	U37	12/6
10F1	4/6	KT38C	6/-	U152	4/6
10LD11	6/-	KT38	6/-	U153	4/6
10P13	6/-	KF4	6/-	U191	10/-
10P14	6/-	KT45	6/-	U281	6/-
12BH7	7/6	LN152	4/6	U382	10/-
12BY7	7/6	LN309	6/-	U391	6/-
20D1	4/6	LZ319	6/-	U319	4/6
20E2	6/-	N37	6/-	U403	6/-
20L1	6/-	N142	4/6	U404	4/6
20P1	6/-	N152	4/6	U801	15/-
20P3	7/6	N153	4/6	U841	4/6
20P4	12/6	N154	4/6	UF42	3/-
20S5	7/6	N309	4/6	UL41	4/6
27S1	12/6	N329	4/6	UL44	4/6
30C1	6/-	N359	4/6	UL46	4/6
30P5	4/6	P41	4/6	U8	10/-
30PL1	6/-	P61	4/6	U241	4/6
30PL2	6/-	PCC84	6/-	Z66	6/-
30PL1	7/6	PCF80	6/-	Z77	2/-
61BT	10/-	PCF82	6/-	Z142	3/-
61SPT	7/6	PCL82	7/6	Z152	3/-

Most pre-war 4, 5, 7, 8 and 9 pin valves, British, American, Continental, 5/- each. Postage and packing (all valves) 6d. each. Orders over £1.0.0 post free.
NEW TRANSISTORS. Red spot 2/6. OC45, OC72, OC78 7/6, OC201 (silicon) 17/6. SPKRS Sin. 5/-, 7 x 4in. 7/6. P. & P. 2/-. LINE O. Tr. Iron 20/-. Many types.
CONSTRUCTOR'S PARCEL. 2 lbs. assorted parts from TV sets. Resistors, condensers, potentiometers, electrolytics, valve holders, 7/6. P. & P. 2/6.
V.A.R.V.E. P.A.M. 12 valves all different as taken out of TVs. Ideal for spares, testinr. etc. 8/6. Postage 1/6.
Before you decide to purchase anything send a S.A.E. for our complete FREE list of 1,000 valves, tubes and transistors. You will be amazed at our prices. For quotation by telephone ring WAN 8822, "St. John's Radio", 3 Jaws Row, London S.W.18.

"LITON" PHOTOELECTRIC CONSTRUCTION MANUAL

10 CENTS interesting PHOTOELECTRIC PROJECTS, fully described with building plans and circuit diagrams which can be easily made by amateurs from standard components. Hints on the use of photo cells and phototransistors. A mine of practical information for the experimenter. All units available ready built or in kit form.
1. Battery burglar alarm. Kit 65/-.
2. Mains burglar alarm.
3. LIGHT saver.
4. Customer announcer.
5. Simple garage door opener.
6. Photoelectric counter.
Price (2) Kit £4.12.6. Built £5.10.0.
7. Long range infra-red mains alarm.
8. "MIRA" Miniature infra-red battery alarm. Total consumption 0.2 watt.
9. Motorised garage door opener.
10. Door opener with electronic lock.

If you are interested in electronics or electro-mechanical gadgets send 1/- stamp for this 24-page, profusely illustrated publication to:
"ST. JOHN'S RADIO," 3 Jaws Row, London SW18. Phone: VAN 8822

LINE OUTPUT TRANSFORMERS

See End Column	SCAN COILS SPECIALISTS	L.O.Tx. Prices
ALBA:	T301, T304, T394, T484, T494, etc. ...	47/6
BUSH:	TV11A, 11B, 12A, 12B, TVG12A, 12B, TRG12A, 12B, TVG26, TV32, TV33, TVG34, TVG34A, T36, TV36, TVG36, TV36C, TVG36C, TV43, TV53, TV56, T57, TV57, TVG58, TV62, TV63, TV66, TV67, etc. ...	45/- 89/6 95/- 110/-
COSSOR:	930 & T, 931, 933-4-5, 937, 938A & F, 939 & A & F, 943T, 940-946, 945, 945B, 945F, 947, 949 ...	62/6 59/6 69/6
DECCA:	D17 & C, DM1, DM2C, DM3, DM4/C, DM5, DM14, DM17, 444, 555 ...	69/6 75/- 75/-
DEFIANT:	TR1453, TR1753 ...	59/6
DYNATRON:		
EKCO:	TS93, TC8102, TS105, TS114, TRC124, TC138, TS188, TS193, TRC139, TC140, T141, TV142, T161, TC162, Y164, T165, etc., TC208, TV209, T231, T221, T231F, T248, T283, T284, T293, etc. ...	55/- 79/6 79/6 59/6
FERGUSON:	103T, 105T, 113T, 135T, 145T, 941T-953T inclusive, 991T-997T inclusive, 203T-246T inclusive, 306T, 308T ...	66/6 59/6 69/6 69/6 65/-
FERRANT:	14T3, 14T3F, 14T4, 17K3 & F, 17T3 & F, 17K4 & F, 178K4 & F, 17T4 & F, 17S4 & F, 14T5, 17SK5, 17K5 ...	48/6 48/6 48/6 48/6 48/6
G.E.C.:	BT1251, BT1252, BT1746, BT1748, BT4743, BT4643, & TS147, BT5246-48, BT5348-BT5643R inclusive ...	49/6 89/6 49/6 and 89/6

Scancoils, Osc. and Output Txs. for all above makes available.
Post and Packing 3/6. All Enquiries S.A.E. See End Column

WYNSOR TELEVISION

Dept. P.T.
ST. ALBANS RD., BARNET, HERTS.
BAR 1769

SETS & COMPONENTS

(continued)

C. EDWARDS

1070 Harrow Rd., London N.W.10

Ladbroke 1734

500 S/H TV Sets must be cleared as taken part exchange. Condition unknown.

ALL SETS COMPLETE

12in. BBC 25/- 13 Channel 50/-
14in. " 50/- " " 75/-
17in. " 85/- " " 125/-
Plus 15/- carriage

Guaranteed Valves

10C2 10/-, 20D1 6/-, 6K25 8/-,
PL38 10/-, PL81 8/-, PY81 8/6,
PY80 7/6, PZ30 10/-.

TUBES-AERIALS-VALVES

Regunned tubes, guaranteed one year, full range of aerials and fittings. I.T.V. boosters, valves, brazehead tuners, T.V. sets, transistor radios and all electrical appliances. Co-axial cables and house wiring cables, fluorescent fittings. All quotations without obligation. Special terms to the trade and Home Engineers. S.A.E. for Catalogue.

G. A. STRANGE

BROADFIELD, NORTH WRAXHALL,
Nr. Chippenham, Wilt. Tel. Marshfield 236

Television Tube Shop

now stock

Tubes for every make of set OVER 600 TUBES IN STOCK

12 inch Mullard type	... £4. 5.0
12 inch Mazda type	... £4. 15.0
14 inch Mullard type	... £5. 5.0
14 inch Mazda type	... £5. 10.0
15 inch G.E.C. & Mullard type	... £5. 15.0
16 inch G.E.C. & Mullard type	... £6. 12.6
17 inch G.E.C. & Brimar type	... £6. 10.0
17 inch Mullard type	... £8. 0.0
Add 10/- for insured carriage to your door within 48 hours, or 5/- via B.R.S. Terms £2 down (plus carriage).	
All tubes tested before despatch and guaranteed for 12 months. Guarantee cards enclosed with each tube.	
New Purchase of 110°, 17 inch tubes—	
Slight mark, Guaranteed for 12 months.	
Mazda CME 1703 } replace AW43-88	
GEC7405A } £5.	
Shop Soiled Tubes.	
(Slight scratches or marks). Guaranteed 12 months. Ideal for second set. 12in. 3/18, 3/31 37/6. MW31-74 50/-. 14in. MW 36-44 52/6. CRM141 55/-. 17in. CRM171, MW 43-64 60/-.	
Others available from time to time. Please enquire. Old bulb required. Service Engineers	
Our Rebate Scheme shows real savings—send for details.	

Television Tube Shop

48 Battersea Bridge Road, S.W.11

BAT 6859
Just South of the Bridge. Open Saturdays until 4 p.m.

LINE OUTPUT TRANSFORMERS

SCAN COILS SPECIALISTS

Make	Models	See First Column L.O.Tx. Prices
H.M.V.:	1824 & A to 1831 inclusive, 1840, 1841, 1842-1848	67/6 All models available. ... 67/6
INVICTA:	T118, T119, T120	55/- All other models available.
K.B.:	LFT50, LVT50, LFT60, MV60	107/6 All models available.

MARCONI:
All models available.

MASTERADIO:
Most models in stock.

McMICHAEL:
Most models in stock.

MURPHY:
V200, V202C ... 57/6
V240, V250 ... 95/-

PETO SCOTT, PHILCO:
Most models in stock.

PAM: 908, 909, 952, 953, 958 ... 55/-

PHILIPS:
1768U, 2168U ... 105/-
1100V, 1200V ... 75/-
122GU, 1236V, 1238V ... 75/-
114UF, 114UM, 115U ... 75/-
1437U, 1446U ... 75/-
Most models in stock.

PILOT: Most models in stock.

PYE: CTM4, FV4C, FV4COL ... 55/-
V4, VT4, V7, VT7 ... 55/-
LV30, FV1, FVIC ... 69/6
C817F, CTM17F, CW17 ... 69/6
CW17C, CW17CF, CW17F, etc. ... 69/6
Most models in stock.

RAYMOND:
Most models in stock.

REGENTONE:
All models available.

R.G.D.: 6017T, 7017, C54, etc. ... 59/6
Most models in stock.

SOBELL:
TS17, T346 ... 65/-
Most models in stock.

STELLA: ST5721U ... 105/-
ST8617U, ST8621U ... 105/-
ST8917U ... 105/-
ST6414U, ST6417U ... 75/-
ST8314U ... 75/-

ULTRA, 917:
U25, etc., complete ... 79/6
Most models in stock.

VIDOR: CN4217-CN4231 inclusive 65/-
Scancoils, Osc. and Output Txs. for all above makes available.

Post and Packing 3/6. All Enquiries S.A.E.

SEE FIRST COLUMN

WYNSOR TELEVISION

Dept. P.T.
ST. ALBANS RD., BARNET, HERTS.
BAR 1769

SETS & COMPONENTS
(continued)

"HEATHKITS" can now be seen in London and purchased on H.P. Free brochure. DIRECT TV REPLACEMENTS LTD., 138 Lewisham Way, SE14. TID 6666.

NOW AVAILABLE !!
REDWATT

Replacement Picture Tubes
Fully Guaranteed and Incorporating all the Latest Developments
Introductory offer:
12in. Types £4.17.6
14in. Types £5.2.6
15-17in. Types £5.7.6
21in. Types £7.15.0

AW43/88, 89, 110 deg. Types £6.10.0

Carr./Ins. 10/-

C.W.O. to:
REDWATT TUBE DISTRIBUTORS
41 Denmark Street, Wakefield, Yorks.

VALVES EX-TV sets 10/- doz. Lists free. 14 Cricklade Road, Swindon.

FOR SALE

100 BAYS of Brand New adjustable Steel Shelving, 73in. high by 34in. wide by 12in. deep, stove enamelled dark green. Sent un-assembled. Six shelf bay - £3/15/-. Sample delivered free. Quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

TELEVISION TUBES REBUILT

Please note we have appointed M/S R. S. Strudwick, 17 Hollingdean Rd., Brighton 7, as Sole Agent for our Genuine Rebuilt Television Tubes for the South Coast. For details of prices, etc., please refer to our advertisements in the inside front cover.

MARSHALL'S for TELEVISION LIMITED
131 St. Ann's Rd., Tottenham, London, N.15
Stamford Hill 3267 & 5555

1,000 TELEVISIONS. all makes, from £3 working, 10/- not. Callers only. 9 till 6 including Sats. 39 Whitehorse Lane, Stepney, London.

Star TV Tubes

70/-

all sizes up to and including 17in. includes old glass, or plus 7/6 without

C.W.O. Carriage 7/6

WHY PAY MORE
new guns, 12 months' guarantee

also 20/- each

12in. 14in., Part Exchange Televisions.
Callers only.

ARTHUR SLARK

43-45 Thicketford Road, Tonge Moor, Bolton

Phone: 26684

VALVE CARTONS at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a Godwin Street, Bradford 1.

SALVAGED VALVES TESTED ON A MULLARD HIGH SPEED VALVE TESTER

AC/P	2/8
B36	2/6
B65	4/-
D1	2/6
DH3	2/6
D77	2/6
DAF91	4/-
DD4	2/6
DI41	2/6
DUL4	2/6
DF91	4/-
DH77	4/-
DK91	4/-
EA50	1/3
EB34	1/2
EB41	1/3
EBG33	2/6
EBG41	4/-
ECC32	2/6
ECC34	2/6
ECC41	4/-
ECC52	4/-
ECL*0	4/-
EF50	1/3
EF50	2/6
EF91	1/3
KT33C	1/3
KT42	2/6
KT61	2/6
KV41	2/6
L63	2/6
MPT4	2/6
P41	2/6
P61	2/6
PCG34	4/-
PCF80	4/-
PCL82	4/-
PCL83	4/-
PCL84	4/-
PEN45	2/6
PN46	2/6
PL33	4/-
PL51	4/-
PL82	4/-
PL83	4/-
PL84	4/-
VP31	4/-
VP32	4/-
VP33	4/-
VP34	4/-
VP4B	4/-
VP4B	2/6
W77	2/6
X41	4/-
Z63	2/6
Z66	2/6
Z90	1/3
Z719	2/6
47PB	2/6
6AL5	2/6
6AM6	1/3
6BW7	4/-
6BX6	2/6
6C6	4/-
6D6	4/-
6F12	1/3
6F13	1/3
6J5	2/6
6J7	2/6
6P25	2/6
6P28	2/6
9D6	2/6
9D7	4/-
10C1	4/-
10C2	4/-
10F1	4/-
10LD11	4/-
20P2	4/-
20L1	4/-
20P1	2/6
20P3	4/-
20P4	4/-
20P5	4/-
25L5	2/6
30C1	4/-
30L1	4/-
30PL13	4/-
32	2/6
42	2/6
43	2/6
307	4/-

EXAMPLES
FULL CATALOGUE 9d.

VALVE HOLDERS
American Octal5/- doz.
Noval9d. ea.

RESISTORS
Card of 1W Resistors, 72 valves covering complete 10% range.
Banks of six compression.
Full range of separate Resistors, Condensers, etc.

VARIABLE CONDENSERS
3-50pf concentric trimmers 3/- doz.
Banks of six compression
trimmers, 3-30pf. . . .6d. ea.

GEC CRT'S (SALVAGED)
SPECIAL OFFER
16in. G.E.C. 990130/- ea.
12in. G.E.C. 710210/- ea.
Personal Callers Only

35M/cs and 16M/cs TURRET TUNERS. less valves (Ex receivers)12/6
We can often supply for the actual set you want to fit the tuner 1/2.

TRANSFORMERS
CRT Boost Transformers.
2V, 4V, 8V, 10V, 13V
Units which required ..12/6 ea.
Heavy Duty Output Trans- formers, 6 ratios from 13 : 1 to 43 : 125/- ea.
Miniature Output Trans. .. 3/9 ea.
Standard Output Trans- formers, Multi-match .. 10/- ea.
Transistor Drives: 1-1 CT .. 10/- ea.
3.5-1 CT 12/6 ea.
Transistor Output 3.5-1 CT 10/- ea.
4.2-1 CT 10/- ea.
Microphone Transformers.
ratio 65 : 135/- ea.

I.F. TRANSFORMERS
Standard 465kc/s .. 12/6 per pair
Midget 465 kc/s .. 16/- per pair

AUTO TRANSFORMERS
250W67/6 ea.
100W27/6 ea.
50W20/- ea.

TRANSISTORISED FAULT FINDER
Enables faults to be located quickly. Consists of a two-transistor, multi-vibrator in a box. Complete with battery. 32/6

CRYSTALS
GUNNIE MULLARD. Boxed
OA5 6/- OA81 3/-
OA70 3/- OA85 3/-
OA79 3/- OA91 8/6

TRANSISTORS
OC16W 48/- OC75 8/-
OC19 48/- OC72 8/-
OC26 25/- OC78 8/-
OC44 12/- OC73 8/-
OC45 10/- OC81 8/-
OC70 6/8 OC82 18/-
OC71 8/8 OC170 17/8

TERMS: C.W.O. or C.O.D.
Orders under £1, P. & P. 1/3.
Open till 11 P.m. most days.

3d. stamp for list or 9d. for full catalogue

Arion Television

4 Macted Road S.E.15 NEWX 7152

FOR SALE
(continued)

GARRARD 210 £9/8/6: B.R.S. UA14 £7/15/-; T.U.9 £4/2/6. Set of 7 Transistors, standard quality. 32/6. Full list from:- H. F. JAMES, 21 Claremont Road, Twickenham, Mdx.

METAL RECTIFIERS

RECTIFIERS—CONTACT COOLED.
14RA1282 (FC101) type 250 v., 250 mA. 18/6;
14RA1283 (FC31) type 250 v., 300 mA. 17/6;
350 mA. 19/6.
RECTIFIERS—FIN TYPES
Equiva. for RM4 250 v., 250 mA. 18/6; RM5 250 v., 300 mA. 17/6; 14A989 400 mA. 18/6;
14A86 16/8; 14A97 19/-; 14A100 22/6; 14A124 19/6; LW7 17/6.

CABY MULTIMETERS
A10 - 16 ranges, £4.17.6; B20 - 20 ranges, £6.10.0. S.A.E. for full details.
ARMCHAIR EXTENSION VOLUME CONTROL unit for TV Radio Amplifiers, etc. Easily fitted, perfectly safe. 1/6.

TRANSISTORS All 1st GRADE
OC81D 5/8, OC81 M. Pr. 13/-, OC44 8/8, OC45 7/6. Set of 6 + OA91 40/-, OC170 12/6, OC23 16/-.
Under £1 P. & P. 6d., over £1 Post Free. C.O.D. 2/6.

DURHAM SUPPLIES

175 Durham Road, Bradford 8, Yorkshire.

WANTED

WANTED NEW VALVES and Transistors, any quantity. S. N. WILLETTTS, 43 Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

A PROMPT CASH OFFER for your surplus brand new Valves, Speakers, Components, Test Instruments, etc. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

NEW VALVES WANTED — EY51, ECL80, PCC84, PCF80, PCL93, PL13, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. **DURHAM SUPPLIES**, 175 Durham Road, Bradford 8, Yorks.

AERIALS

AERIALS TV Aerials save £££'s. Manufacturer offers many models at a fraction of retail price. ITV aerials from 7/6 each. Also components and kits. **RICHARD MAURICE EQUIPMENT CO.** Portsmouth Road, Cobham, Surrey. COBHAM 4283.

EDUCATIONAL

ELECTRONICS

Key to YOUR Future?



An exciting career—
A new Hobby—Your
own spare- or full-
time BUSINESS?

New experimen-
tal course in-
cludes big kits
for building test
gear and a com-
plete AM/VHF
receiver.
FREE
brochure from



RADIOSTRUCTOR
DEPT. E78, READING, BERKS.

EDUCATIONAL

(continued)

THE INCORPORATED Practitioners in Radio and Electronics (I.P.R.E.) Ltd. Membership Conditions booklet 1/-. Sample copy of I.P.R.E. official journal 2/- post free. Secretary 20 Fairfield Road, London N8.

**Radio
Television
& Electronics**

Learn at home with the world's largest home study organisation, Brit. I.R.E.; City & Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy.

Write for **FREE prospectus** stating subject to

I.C.S.
Dept. 516
Intertext House, Parkgate Road, London, S.W.11.

"HOW AND WHY" of Radio and Electronics made easy by a new non-maths practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from Dept. 12, P.T. RADIOSTRUCTOR, Reading.

$$X = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

DON'T FUMBLE with Formulae. Master Mathematics quickly and easily the Understandable Way.



The Dryden School of **UNDERSTANDABLE MATHEMATICS**
11V Dryden Chambers, Oxford St. London, W.1.

Name: _____
Address: _____

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES in minutes from the great book. "The Principles of TV Receiver Servicing". 10/6 all book houses and radio wholesalers. If not in stock, from Secretary I.P.R.E., 20 Fairfield Rd., London N8.

SITUATIONS VACANT

OPPORTUNITY EXISTS for energetic man with technical knowledge to acquire partnership in TV store. London area. Capital immaterial. Box No. 30.

SITUATIONS VACANT

**UNITED KINGDOM
ATOMIC ENERGY AUTHORITY
ATOMIC ENERGY
ESTABLISHMENT, WINFRITH**
Vacancies exist at the A.E.E., Winfrith, for

**ELECTRONIC
INSTRUMENT MECHANICS**

Applicants should have experience of electronic equipment and industrial process control instruments, and of work involving fault diagnosis, repair and calibration for a wide range of instruments used in nuclear reactors and associated experiments. The work requires a good knowledge of instruments for measuring and automatically controlling flow pressures and temperatures of liquids and gases, as well as pulse techniques, wide band and D.C. amplifiers, counting circuits and associated test equipment.

Excellent working conditions including sick pay and pension scheme.

Further details and an application form may be obtained on request from

**THE LABOUR DEPARTMENT,
A.E.E., WINFRITH, Dorchester, Dorset,**
quoting ref. IM/NAT/JN.

RES/CAP. BRIDGE 38/-

Checks all types of resistors, condensers 6 RANGES p. & p. 2/6

Built in 1 hour. Direct reading.

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. VV)

Raleigh Mews, Raleigh Street, Nottingham

NEW VALVES!

Guaranteed Set Tested
24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4 18/6.			
DAF96, DF96, DK96, DL96, SET of 4 26/-			
1D5 7/-	DL35 9/6	PCC89 9/-	
1R5 6/-	DL92 5/11	PCF80 7/6	
1S5 4/6	DL94 6/9	PCF82 7/6	
1T4 3/3	DL96 6/9	PCL82 8/3	
3S4 5/1	EB31 3/-	PCL83 11/6	
3V4 6/9	EB41 7/6	PCL34 6/9	
5U4G 4/6	EBF80 7/9	PL26 10/9	
5Y3GT 5/9	EBL21 12/6	PL81 8/6	
5Z4G 8/6	ECC40 14/6	PL82 6/6	
6AM6 2/9	ECC81 4/9	PL83 6/6	
6K7G 1/9	ECC82 5/9	PL84 8/-	
6K8G 4/9	ECC83 6/9	PY32 11/-	
6K7G 5/6	ECC84 8/-	PY80 7/6	
6V8G 4/-	ECC85 7/6	PY81 7/-	
6V8GT 6/6	ECP90 7/3	PY82 6/6	
6X5GT 4/6	ECP82 8/8	PY83 7/3	
12K7GT 4/3	ECH21 12/6	U25 11/6	
12K8GT 9/-	ECH42 7/9	UABC80 6/6	
12K7GT 4/6	ECL80 6/9	UAF42 8/-	
DAAC32 8/9	EF40 12/3	UBC41 7/-	
35L6GT 8/-	EF41 7/6	UBF80 8/-	
35Z4GT 5/-	EF80 4/3	UCC85 7/-	
AZ31 8/9	EF85 4/6	UCH21 12/6	
CL83 11/9	EF86 8/9	UCH42 7/6	
DAC32 8/6	EF89 6/8	UCH81 8/-	
DAF91 4/6	EF91 6/9	UCL82 6/3	
DAF96 6/9	EL41 9/-	UCL83 13/-	
DF33 8/6	EL84 6/3	UF41 6/6	
DF91 3/3	EY51 7/3	UF89 6/9	
DE77 6/-	EY86 7/8	UL41 7/6	
DK32 10/6	EZ40 6/-	UL84 6/6	
DK91 6/-	EZ80 5/9	UY21 13/-	
DK92 7/3	EZ81 6/-	UY41 5/6	
DK96 7/3	MU14 6/-	UY85 8/6	
DL33 7/6	PCC84 7/-	VP4B 8/3	
		Z77 2/9	

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 3/- extra. Office address, no callers.

GERALD BERNARD
(Note new address—formerly of Leeds)
83 OSBALDESTON ROAD,
STOKE NEWINGTON, LONDON, N.16

**COYNE'S NEW
PIN-POINT TV
TROUBLES**

**TAKES HEADACHES OUT OF
ALL SERVICING PROBLEMS**



Your most useful on-the-job "tool"! Quickly and easily pin-points the exact trouble in any TV set. Covers 70 symptoms, 700 trouble spots. Over 340 cross-indexed pages, 50 time-saving Check-Charts; 280 diagrams and photos; explanation of circuits and designs.

SIMPLE CHECK-CHART SYSTEM SAVES TIME!

This amazingly practical handbook shows you how to find the trouble in any TV circuit FAST! Simple cross-index tells you in what section you'll find cause of trouble. Handy Check-Charts then help you accurately locate the EXACT trouble spot. Cut waste time, eliminate hours of aggravation, get right to the heart of the trouble in minutes.

USE THIS BOOK RIGHT ON THE JOB—NO NEED TO MEMORIZE!

This Pin-Point Book was designed especially for on-the-job trouble-shooting. You simply turn to the indexed section, locate the circuit description and Check-Chart, and in minutes you have the trouble spot located and ready for repair. No complicated theory or mathematics. Down-to-earth practical circuit description, service methods and trouble-shooting techniques. Published by the famous Coyne Electrical school and approved by leading authorities in the field.

J. E. C. Grover of Streatham says:
"Immediately I glanced through this book I was convinced that your claims concerning the merits of this work were justified, for it is, without a doubt, the finest book of its kind that I have ever come across. It is not only unique in its presentation but it is also superbly produced."

G. Axam of London S.E.9, says:
"I have spent nearly £50 on technical books over the past 5 years all of which I feel has now been wasted as your book is the best I have yet had the pleasure of examining, it is practical, to the point, with just the right amount of technical information needed, covering almost every aspect of TV servicing."

FREE TRIAL OFFER!

Mail Coupon now for fast return service! To **SIM-TECH TECHNICAL BOOKS**, Dept. P.7, Gater's Mill, West End, Southampton, Hants.

RUSH TV Troubles for free seven day trial. If not satisfied I may return book and owe nothing. If I keep the book I will send full amount of 33/- including postage within 7 days OK two payments of 17/- within 7 days.

SAVE! Send only 31/6 if paying cash with order. (We pay postage.) Same 7-day-money-back guarantee.

Name _____
Address _____
City _____ County _____

CLARKSON'S TUBE CHANGE

6A DENISON ROAD, LEEDS 2
Tel. Leeds 24576.

We are now able to offer SUPER SCREEN TV TUBES with 12 months' guarantee at the keenest exchange price ever.

Example:

Tubes all types	Cash allowance on return of old tube	Actual cost of Tube
12"—14" £5	15/-	£4. 5.0
15"—17" £6	25/-	£4.15.0
21" £8	30/-	£6.10.0

Carriage and Insurance 10/- extra

These tubes are COMPLETELY REBUILT by experts, with the most up-to-date electronic equipment, and are fitted with the famous American Golden Grid Electron Gun. Many thousands of these tubes are in service today. Our factory is open to inspection to readers of "Practical TV". Technical advice and queries are answered free of obligation. All tubes are dispatched with adhesive paper and return labels. Cash allowance is sent on receipt of old tube.

AERIALS

BAND I BAND II BAND III



Combined Arrays I and III
 1+3 Element Loft Mounting .. 38/3
 1+5 Element Loft Mounting .. 46/6
 1+3 Element Wall Mounting .. 45/3
 1+5 Element Wall Mounting .. 61/-
 1+3 Element Chimney M'ting .. 57/10
 1+5 Element Chimney M'ting .. 66/9

Band I
 Single Dipole Wall Mounting .. 24/7
 Single Dipole Chimney M'ting .. 40/2
 X Aerial Chimney Mounting .. 62/3
 H Aerial Chimney Mounting .. 67/7

Band III
 3 Element Yagi Wall Mounting 33/-
 6 Element Yagi Wall Mounting 43/-
 9 Element Yagi Wall Mounting 56/-
 Chimney Lashing Mounting add 10/-
 Double 6 Array, only with clamp 83/-

Band II
 Single Dipole Wall Mounting .. 20/5
 Single Dipole Chimney M'ting .. 29/9
 H Array Chimney Mounting .. 52/4

REPAIR KITS

Band III Folded Dipole With Insulator, Complete .. 9/3
 Band I Insulator With Two 1 inch Dipoles For 1 or
 1 inch Booms, Complete .. 19/5
 6 inch Lashing Kit, 12/11 .. 7/1
 6 inch Wall Bracket With U Bolts .. 7/10
 1-1; 1-1 inch Clamps, 3/10, 1-2 inch Clamps Universal 5/4
 Bracket Repair Kit, J Bolts; U Bolts; 20ft Lashing
 Wire; Thimbles; Corner Plates 6/-
 Insulators, All Types (Enquire)
 Co-Ax. Semi Air Spaced, 7d. yd. Plugs 1/2
 Send 6d. for Lists. Please state Channel when ordering.
 Cash with Order. Post and Packing 3/- extra.

SATISFACTION OR MONEY BACK GUARANTEE

WALKER & SQUIRES

PINNOX STREET, TUNSTALL, STOKE-ON-TRENT
 Phone: Stoke-on-Trent 88767

FIRST-CLASS TELEVISION and RADIO COURSES

GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how.

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ. London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches) etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING

(Dept. 462), 148 HOLBORN LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.
 Australia: P.O. Box 4570, Melbourne.

TRANSISTOR POCKET RADIOS



ONLY 32/8
 No more to pay

a lifetime. Anyone can assemble it in an hour or two with our easy plan. Complete set of parts including miniature speaker, carrying case—everything only 32/8 plus 2/6 P. & P. (C.O.D. 2/6 extra. (Parts can be bought separately.)

Order Now! Limited offer only.

DEMONSTRATIONS DAILY

CONCORD ELECTRONICS (Dept. B13/2)
 210 CHURCH ROAD : HOVE : SUSSEX

ALUMINIUM, LIGHT ALLOYS BRASS, COPPER, BRONZE

IN ROD, BAR, SHEET, TUBE, STRIP WIRE, ANGLE, CHANNEL, TEE

3,000 STANDARD STOCK SIZES

H. ROLLET & CO. LTD.

6 CHESHAM PLACE, LONDON, S.W.1
 BELgravia 4300

Works:

36 ROSEBERY AVE., LONDON E.C.1

Branches at Liverpool, Manchester, Birmingham, Leeds.

No Quantity too small

New 1962 Edition

WORLD RADIO TV HANDBOOK

18/9. Postage 1/-.

FIRST COURSE IN TELEVISION, by Decibel. 15/-. Postage 9d.

TELEVISION SERVICING, by G. N. Patchett. 25/-. Postage 1/-.

COMMUNICATION RECEIVERS, by G. R. B. Thornley. 2/6. Postage 6d.

TV FAULT FINDING, a Data Pub. 5/-.. Postage 6d.

AN INTRODUCTION TO THE CATHODE RAY OSCILLOSCOPE, by H. Carter. 15/-. Postage 9d.

TELEVISION EXPLAINED, by W. E. Miller, Rev. E. A. W. Spreadbury. 12/6. Postage 1/-.

A BEGINNER'S GUIDE TO TELEVISION, by F. J. Camm. 7/6. Postage 6d.

RADIO VALVE DATA, 7th Ed. Compiled by "WW". 6/-. Postage 10d.

COMPLETE CATALOGUE, 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-21 PRAED STREET LONDON, W.2

Phone: PADDington 4185
 Open 6 days 9-6 p.m.

"THREE STAR"

RE-BUILT TELEVISION TUBES

- ★ Manufacturer's Own Make of Gun
- ★ Re-screened for Greater Contrast
- ★ Aluminised for Better Brightness

TWO WAY TESTED

Free carriage and insurance.

ALL TYPES AND SIZES

- 12" - £4.10 14" - £4.15
 15" - £5. 0 17" - £5.10
 21" - £7. 0

C.O.D. or Cash with order.

DARLING ELECTRONICS

Dept. TV, 62 High Street, Croydon, Surrey

MAIL ORDER ONLY—NO CALLERS

DUKE & CO. (London) Ltd.

621/3 ROMFORD RD.
MANOR PARK, E.12.
ILFord 6001/3.

Stamp for FREE List.

9 a.m.—6 p.m. Half day Thursday.



12 MONTHS' GUARANTEE TV TUBES

- 21 in. 17 in. 15, 14, 12 in.
 99/6 90/- 70/-


Insurance and Carriage 15/6

£1 extra without old bowl, refundable if same received within 14 days.

14 in. 36-24 and 14KP4 Salvage purchase of Rental replacement stocks. Carriage 5/- **35/-**

COMPLETE TELEVISIONS

EX-RENTAL SETS 17 in. £11.10.0

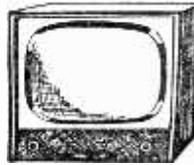

Excellent table models. ITA/BBC. Famous manufacturer. Personal collection advised. Ins., carr., 25/-. (Regret some delay).

12 months' guarantee on tubes. 3 months' guarantee on chassis and valves.

14 in. £7.10.0

ITA/BBC. As 17in. Ideal for caravans, chalets, weekend bungalows, etc. Personal collection advised. Ins., carr. 20/-

TAPE RECORDER AMPLIFIER £9.15.6

By famous manufacturer. Superb 4-valve amplifier. Two controls and superimpose switch. Sockets for Mike and Gram. Size 11 x 4 x 6in. Ins., Carr. 4/6. Drawings FREE with Order.

VALVES

Salvage Guaranteed 9d. Each
 6AL5, 6AM6, 6D1, 6D2, 6F12, 6F13, 6F14, 6F15, 6D3, 6D7, 6D12, 6D3, 6E50, 6E91, 6X33, 6X34, 6F50, 6E91, 6B41, 6F42, 2Z7.
 1/9 Each
 6F1, 6L1, 6K7, 6P25, 6P28, 6D1, 6B25, 6B6, 6B41, 6L32, 6T33C, 6T30, 6N142, 6U2, 6U1, 6U3, 6U4F2, 6U680, 6W6, 6W7.

SPEAKERS

8/9 each



6in.—8in.—7in. x 4in. Money back guaranteed. Enquire for other sizes. Ex. mfd. salvage. P. & P. 3/-.

ELLIPTICAL SPEAKERS

Brand new. Slot type. 8 x 3in. and 7 x 4in. P. & P. 3/-.

MINIATURE SPEAKERS

THREE INCH. Brand new. Post & Packing 1/-. **16/9**

TRANSISTORS

Complete set, **47/6.** Post Free

EDISWAN

XC121, 8/9. XB113, 8/9. G.E.C.

114, 6/9. *74, 9/9. 2—873, 8/9.

MULLARD

OC81D, 6/9. OC44, 9/9. 2—OC81, 6/9. 2—OC45, 8/9. Diode, 1/9.

SOLO SOLDERING TOOL 12/6

110 v., 6 v. or 12 v. (special adaptor for 200/250 v., 10/- extra). Automatic solder feed including reel solder and spare parts. It is a tool for electronic soldering or car wiring. Revolutionary in design. Cannot burn. In light metal case with full instructions for use. Post 4/-.



RST

MAIL ORDER DEPARTMENT
211 Streatham Road, Mitcham, Surrey
ALL VALVES LISTED ARE NEW STOCK & Terms C.W.O. or C.O.D. Postage 3d. per valve. MITCHAM 6201

AZ1 15/-	EF92 4/-	PCF82 7/-	UY95 7/-	6K8C 7/6
B65 8/6	EL42 10/-	PCL82 12/6	VF4B 17/6	6K8GT 9/6
DAF91 7/6	EL84 8/6	W142 8/6	W81M 6/-	6L1 13/-
DAF96 8/9	EL90 8/6	PCL83 12/6	W19 7/6	6L8C 7/6
DF91 4/-	EM80 8/6	PENA4 17/6	W27 7/6	6L18 10/-
DH719 6/-	EM81 8/6	17/6	X78 21/-	6L19 17/6
DK91 8/-	EX81 10/-	PEN4VA 17/6	X79 21/-	6N7G/GT 6/6
EABC80 6/-	EX86 8/6	PL36 15/6	Z21 12/6	6S17GT 6/6
EAF42 9/6	EY91 4/-	PL81 12/-	Z77 4/-	6SN7GT 6/-
EB91 4/-	EZ35 6/-	PL82 8/-	Z152 5/-	6V6G 5/6
EBC41 9/-	EZ40 7/-	PL83 10/6	Z19 5/-	6X5GT 5/-
EBF90 8/6	EZ41 7/-	PL84 10/6	1R5 7/6	7S7 10/-
EBF99 8/6	EZ80 7/-	PL85 10/6	5U4G 4/6	7Y4 7/6
EC91 9/6	EZ81 7/-	PL86 10/6	5V4G 9/6	8D3 4/-
ECC33 9/6	FC2 21/-	PL87 10/6	5Y3GT 8/6	10LD11 15/-
ECC31 5/9	FC4 15/-	PL88 10/6	5Z4G 10/-	12AH8 9/-
ECC83 9/6	FC13 21/-	PL89 10/6	6A8GT 7/6	12A10 8/6
ECC84 8/6	FC19C 21/-	R19 19/-	6A15 13/6	12A17 5/-
ECC85 8/-	GZ32 10/6	TD34 12/6	6A15 6/-	12A17 8/6
ECF90 8/6	H80 9/-	TE22 15/-	6AM6 4/-	12A17 7/6
ECF92 8/6	H83 9/-	UH22 7/6	6AN5 7/6	12B8G 7/6
ECH42 9/6	HBC90 8/6	U147 7/-	6AQ5 6/6	12B8H 10/-
ECH81 8/6	HL133D 9/6	U153 8/6	6BA6 6/-	12B7G/GT 8/6
ECL80 9/-	KT33C 10/-	UABC80 6/6	6BE6 6/-	12K7GT 5/-
ECL82 9/-	KT66 8/-	UAF42 8/6	6BR7 12/6	12K8GT 10/-
EF90 15/-	LT319 12/6	UBC41 8/6	6BWS 7/6	12Q7 8/6
EF41 8/-	(OT 1) 17/6	UBF80 8/6	6C97 7/6	12R8GT 8/6
EF42 10/-	ML4 8/6	UCH42 8/6	6BX6 5/-	12S4GT 8/6
EF50(A) 4/-	MSF4 17/6	UCH81 9/6	6C13 10/-	35 Z4GT 8/6
EF80 5/-	MU14 9/-	UCL83 8/-	6F1 10/6	50L6GT 9/-
EF85 5/-	MX40 15/-	UF41 7/6	6F12 4/-	
EF96 10/6	N142 9/6	UF89 6/6	6G5 4/6	
EF89 9/-	N153 10/-	UL41 8/6	6K7 2/-	
EF91 4/-	PC84 9/-	UL84 7/-	6K7G 3/-	
	PCF80 9/6	UY41 7/6	6K7GT 8/6	

SEND FOR LISTS. Quotations given for any types not listed. Obsolete and old types a speciality.

TRANSISTORISED STETHOSCOPE


Trace signal right through: Radio, TV, Tape amplifier, Hi-Fi, etc.—simplest way to fault find—carry it like a fountain pen—all parts including transistor barrel crystal, everything except battery, 12/6 plus 1/6, data included or separately 1/6. (Or complete with dead air type earphone, 20/-.



Transistors for R.F., F.M., TV and U.H.F.

Frequencies quoted are approx. cut-off.
 SB 075 15-20 Mc/s. 8/6
 SB 305, 20-30 Mc/s. 9/-
 SB231R, 40-50 Mc/s. 15/-
 American 2N1727, 100-150 Mc/s. 15/-
 American 2N1728, 100-150 Mc/s. 12/6
 American 1N1300, 1.000-1.300 Mc/s. 25/-
 SEND T1833, 1.000-1.300 Mc/s. 25/-
 SEND S.A.E. for transistor list and circuits.

TV Service Sheets

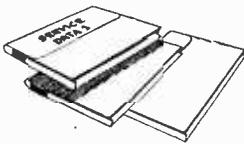


200 sheets covering the most popular post-war Televisions by leading makers—Coscor, Ekco, Ferguson, Pye, etc. Giving circuit diagram, component values, I.F. frequencies, etc. £2, post free.

TV CABINET

FOR 17" MODEL

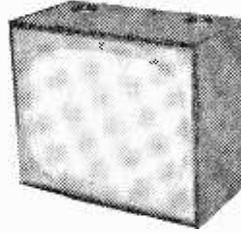
Really well made and finished with polyester lacquer. Originally intended for Philco sets. Price



35/-

plus 10/- carriage and insurance.

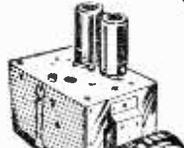THIS MONTH'S SPECIAL BRAYHEAD TURRET TUNER



complete with Band 1 and Band 3 coils. New but removed from unused equipment. Less valves 15/- each or with valves 25/- each, post 2/6.

DEPOT BEING CLEARED !

Unused parts offered at very low prices.

Set of 3 Plessey Parts, comprising line output E.H.T. transformer, wide single scanning coils and width control. 37/6, the 3, with diagram.

Crystalline TV Mask. 14". 5/-; 17". 10/-, post 2/6.

Metal Rectifier. 250 m.a.—250 v—equivalent to the R.M.5.. 10/-.

B7G Valve Holders with skirt for scanning can 5/- per dozen, less skirt 2/6 per dozen.

80 ohm C.O.-X. low loss expanded polythene, 6d. per yard.

Connecting Wire, 25 s.w.g., P.V.C. covered, 100ft. coils 2/- each, 10,000 yards. £7.10.0.

E.H.T. Transformer standard mains input, 1250 volt output, two other secondaries, potted in heavy cast case 25/- plus 6/6, carriage and insurance.

TV from Car Battery. D.C.—A.C. converter with automatic voltage control for running TV set from 24 volts supply, really beautiful job in grey case with handles £45. Carriage extra on cost depending on distance.

V.C.R. 57C Cathode Ray Tube direct replacement for V.C.R.97, 8/6, carriage and insurance. 6/6.

ELECTRONIC PRECISION EQUIPMENT LTD.

• Orders received by post are despatched from our warehouse, Dept. 5, 66 Grove Road, Eastbourne, and to save time, please post your order to this address. Please include enough for postage. Callers, however, should use one of the following addresses:

520 High Street North 42-46 Windmill Hill 266 London Road 29 Stroud Green Road 246 High Street Manor Park, E.12 Ruislip, Mddx. Croydon Finsbury Park, N.4 Harlesden, N.W.10

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS	1R5, 1S5, 174, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ..	Set 4 for 19/6
1A7GT 11/-	6L19 12/-	30C15 13/6
1D5 8/-	6LD20 8/-	30F1L 10/-
1E5GT 9/-	6P5 8/6	30L15 11/-
1N5GT 8/-	6P25 8/6	30P1L 10/-
1R5 6/-	6P28 12/-	30P12 7/6
1S4 8/-	6Q7G 6/-	30P1L13 11/9
1S5 5/3	6Q7GT 8/6	35A5 14/-
174 3/6	6S17GT 5/9	35L6GT 8/3
1U5 5/9	6S27GT 4/9	35ZAGT 5/6
3A5 9/-	6U4GT 9/9	35Z5GT 8/3
3Q4 7/-	6V6G 4/6	50C06G 27/3
3S4 6/-	6V6GT 6/6	50L6GT 8/3
3V4 7/-	6X4 4/6	AC/TH1 16/6
5U4G 4/6	6X5GT 4/9	AZ31 9/6
5V4G 7/6	6Y30L2 9/9	B36 8/6
5Y3GT 6/-	7B6 9/-	CL33 12/3
5Z4G 9/-	7B7 7/6	DA C32 9/-
6AL 3/6	7C5 7/6	DAF91 5/3
6AN6 3/6	7C8 7/6	DAF96 7/6
6A4G5 6/-	7H7 7/6	DCC90 9/-
6A76 6/9	7S7 9/-	DF33 9/-
6BA6 5/9	7Y4 7/-	DF91 3/6
6BE6 5/9	10C2 17/-	DF96 7/6
6BH6 5/9	10F13 14/6	DH76 4/9
6BJ6 5/9	12AT6 7/-	DH77 6/9
6BR7 12/6	12AT7 5/-	DK32 11/9
6BW6 8/-	12AX7 6/3	DK91 6/-
6CD6G 27/3	12AX7 7/-	DK92 7/6
6K7C 11/1	12Q7GT 4/9	DK96 7/6
6P6G 6/6	12K8GT 9/6	DL33 9/-
6P13 10/-	12Q7GT 4/9	DL35 9/6
6P14 10/-	12Z3 10/6	DL92 6/-
6F23 10/-	1A57 19/6	DL94 7/-
6K7C 11/1	20P2 17/-	DL96 7/6
6K7GT 5/-	20L1 17/-	EM84 5/6
6K8G 5/-	25A8G 8/-	EAF42 8/6
6K8GT 9/-	25L6GT 7/9	EB91 3/9
6L18 10/-	25Z4G 8/6	EBC33 5/9
		EBC41 8/-
		EBF30 8/-
		EBF89 8/9
		EBL21 13/6
		ECC40 15/-
		ECC81 5/-
		ECC82 6/3
		ECC83 7/-
		ECC84 8/3
		ECC85 7/9
		ECF80 7/6
		ECF82 8/6
		ECH21 13/6
		ECH35 6/3
		ECH42 8/9
		ECH81 7/9
		ECL80 7/6
		ECL82 9/-
		ECL83 4/6
		EF40 12/6
		EF41 7/9
		EF80 4/9
		EF85 4/9
		EF88 6/9
		EF89 7/6
		EF91 3/6
		EF92 3/6
		EL33 9/6
		EL41 9/6
		EL42 9/6
		EL94 6/6
		EM34 6/9
		EM80 8/9
		EM81 8/-
		EM84 9/6
		EY51 7/6
		EY86 7/9
		EZ40 6/9
		EZ41 7/-
		EZ80 6/3
		EZ81 6/6
		KT3C 7/-
		KT41 11/6
		KT44 5/9
		KT61 9/6
		KT63 6/6
		ML14 6/6
		MX40 14/-
		N18 7/-
		PC85 10/-
		PC88 7/6
		PC89 9/3
		PCF80 7/9
		PCF82 8/-
		PCF86 14/-
		PCL82 9/-
		PCL83 11/6
		PCL84 10/-
		PCL85 13/6
		PEN44 11/-
		PEN36C 8/5
		PL36 11/6
		PL81 9/6
		PL82 7/-
		PL83 7/6
		PL84 8/6
		PL85 11/6
		PY80 7/6
		PY81 7/-
		PY82 6/6
		PY83 7/9
		T11 9/6
		U22 7/9
		U24 17/6
		U25 12/-
		U26 10/-
		U50 6/-
		U52 4/6
		U78 4/6
		U191 14/6
		U251 12/-
		U281 17/-
		U291 16/6
		U301 18/9
		UAB80 6/6
		UAF42 8/3
		UB41 8/6
		UBC41 7/9
		UBF80 8/3
		UBF89 7/-
		UCC84 13/3
		UCC85 7/6
		UCF80 14/6
		UCH21 13/6
		UCH81 8/-
		UCH82 9/9
		UCL83 13/3
		UF41 7/-
		UF42 5/6
		UF89 7/-
		UL41 8/-
		UL84 6/6
		UM4 14/-
		UB1C 5/-
		UY21 13/6
		UY41 6/6
		UY85 6/6
		VP4B 9/6
		VP41 5/-
		VP1321 16/6
		W76 4/9
		W77 3/9
		Z77 3/6

T.V. SPARES

SEND NOW FOR OUR **1962** CATALOGUE
 SEND 1/- IN STAMPS TO ALPHA RADIO SUPPLY CO. LTD.
 103 LEEDS TERRACE, WINTOWN ST. LEEDS, 7 TEL. 25187

TUBES
 All types
12"-17" ONLY 30/-
 Also a few 21in. at only 50/-
WHY PAY MORE?
 These tubes are ex rental stocks, each one fully tested before despatch. Guaranteed to give excellent results, and complete satisfaction, or money refunded. Please state type required, or Model No. of set, and name of nearest railway station.
 (Carry. up to 17in. 10/-; 21in. 12/6.)
SEND NOW WHILE STOCKS LAST TO
REGENT SUPPLIES Dept. P.T.
 124 Athelstan Rd., Southampton

READERS RADIO
 24, COLBERG PLACE, STAMFORD HILL
 LONDON, N.16 STA. 4587

Post 6d. per valve extra.
 Any Parcel insured Against Damage in Transit 6d. extra
 Any C.O.D. Parcel 3/- extra.

TELEVISION TUBES RE-BUILT BY "RE-VIEW"

	PRICE:		
12in.	£4.10.0
14in.	£4.15.0
15in.	£5. 0.0
17in.	£5. 0.0
21in.	£7. 0.0

SAVE £££s

Correct voltage heaters
All types



TWELVE MONTHS' GUARANTEE

Free carriage and insurance

Cash with order or C.O.D.

Be one of our satisfied customers. Call and see our TUBES REBUILT and TESTED

RE-VIEW (London) LTD., 385 London Road, West Croydon, Surrey

Terms to the Trade

Tel.: THORNTON HEATH 7735

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee

"NO PASS — NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/20), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech.E.
A.M.I.C.E.
A.M.I. Prod.E.
A.M.I.M.I.
A.I.O.B.
A.F.R. Ae.S.
B.Sc.
A.M. Brit. I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES" (Write if you prefer not to cut page)

NAME

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME (SF 20)

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

CR1 BOOSTER TRANSFORMERS
 TYPE A. OPTIONAL 25% and 50% BOOST.
 2 V. OR 4 V. OR 6.3 V. OR 10 V. OR
 13.3 V. MAINS INPUT. 12/6

TYPE A.2. HIGH QUALITY. LOW CAPACITANCE.
 10.15 pF. OPTIONAL BOOST 25%, 50%,
 75%. MAINS INPUT. 16/8

TYPE B. MAINS INPUT. MULTI OUTPUT 2-4.
 6.3, 7.5, 10 and 13 VOLTS. BOOST 25%
 AND 50%. LOW CAPACITANCE. 21/-
 Full instructions supplied.

TRIMMERS. Ceramic. 30, 50, 70 pF. 5d., 100 pF.
 150 pF. 1/3; 250 pF. 1/6; 500 pF. 750 pF. 1/9.

RESISTORS. Preferred values. 10 ohms to 10 meg.
 1 w., 4d.; 1/2 w., 4d.; 1 w., 8d.; 1 1/2 w., 11/-;
 2 w., 14/-; 3 w., 18/-; 5 w., 24/-; 10 w., 36/-.

HIGH STABILITY. 4 w., 1/2; 2/- Preferred values.
 100 to 10 meg. Ditto. 5 w., 100Ω to 5 meg. Ω. 9d.

WIRE-WOUND RESISTORS
 25 ohms—10,000 ohms
 12.5K to 50K 10 w. 3/-

**AMERICAN "BRAND FIVE"
 PLASTIC RECORDING TAPE**

Double Play	7in. reel, 2,400ft 87/8	Spare
	5in. reel, 1,200ft 3/7	Plastic
Long Play	7in. reel, 1,800ft 35/-	Reels
	5in. reel, 1,200ft 23/8	3 in. 1/6
	5in. reel, 900ft 18/8	4 in. 2/-
		5 in. 2/-
Standard	7in. reel, 1,200ft 25/-	5 1/2 in. 2/-
	5in. reel, 600ft 18/-	7 in. 2/6

"Instant" Bulk Tape Eraser and Head De-
 fluxer, 200/250 v. A.C., 27/6. Leantel, S.A.F.

O.P. TRANSFORMERS. Heavy Duty 50 mA, 4/6.
 Multitrate, push-pull, 7/8. Ditto, 10w, 15/6. Minia-
 ture, 384, etc. 4/8. L.F. CHOKES 15/10 H, 60/65
 mA, 5/-; 10 H, 85 mA, 10/8; 10 H, 150 mA, 14/-.

MAINS TRANSFORMERS 200/250 v. A.C.
 Postage 2/- each transformer.

STANDARD, 250-0-250, 80 mA, 6.3 v. 3.5 a.	2/6
tapped 4 v. 2 a. Rectifier 6.3 v. 1 a. 5 v.	2/6
2 a. or 4 v. 2 a. 22/6 ditto, 350-0-350	2/6
MINIATURE 200 v. 20 mA, 6.3 v. 1 a.	10/6
MIDGET, 230 v. 45 mA, 6.3 v. 2 a.	15/6
SMALL, 230-0-230, 50 mA, 6.3 v. 2 a.	17/6
STD., 250-0-250, 60 mA, 6.3 v. 3.5 a.	17/6
HEATER TRANS. 6.3 v. 1 1/2 amp.	7/6
Ditto, tapped sec. 2, 4, 6.3 v. 1 amp.	8/6
Ditto, sec. 6.3 v. 3 amp.	10/6
GENERAL PURPOSE LOW VOLTAGE, 250 v.	2/6
3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v.	22/6
AUTO TRANSFORMERS. 150 w.	22/6
0, 120, 200, 230, 250 v., 500 w.	82/6

ALADDIN FORMERS and cores. 1 1/2 in. 8d.; 3 in. 10d.
 0.3in. FORMERS 587/8 and Cans TV1/2, 21/-; 3/4 in. sq x
 2 1/2 in. and 1/2 in. sq x 1 1/2 in., 2/- ea., with cores.

SOLOID Soldering Iron, 200 or 240 v. 25 w. 24/-.

MAINS DROPPERS. 3in. x 1 1/2 in. Adj. Sliders.
 0.3 amp., 1,000 ohms, 4/3. 0.2 amp., 1,000 ohms, 4/3.
 LINE COIL, 0.3 amp., 60 ohms per ft., 0.2 amp., 100
 ohms per ft., 2-way, 1/2 per ft. 3-way, 1/2 per ft.

LOUDSPEAKER 3" P. 3 OHM. 24in. 3in. 4in. 11in. 19/8.
 5in. 17/8. 8in. Plesemy, 19/6. 7in. x 4in. Rola, 18/8.
 6in. Rola, 18/8. 10 x 6in., 27/8. 10in. 30/-.
 4in. HI-FI Tweeter, 25/-; 3 1/2 in. R.A., 30/-.

STENTORIAN HP. 10in. 3 to 15 ohms, 10w, 8/6.
 12in. Baker 15 watt 3 ohms, or 15 ohms, 90/-.

CRYSTAL DIODE G.E.C., 2/-; GEX34, 4/-; OA81, 3/-.
HIGH RESISTANCE PHONES. 4,000 ohms, 15/-.
SWITCH CLEANER. Fluid squirt sprayer, 4/3 tin.

TWIN GANG TUNING CONDENSERS. 365 pF
 miniature 1 1/2 x 1 1/2 in. x 1 1/2 in., 10/-; 500pF Standard
 with trimmers, 9/-; midget, 7/8 with trimmers, 9/-.
 SINGLE, 50 pF, 75 pF, 100 pF, 150 pF, 200 pF, 5/8.
 Solid dielectric 100, 300, 500 pF, 3/6.

New and Boxed. VALVES 90-day Guarantee.

1R5	7/8	6K90	7/8	EABC30	8/8	HABC30
185	7/8	6L6G	10/8	EB91	8/-	12/8
174	8/-	6NT7M	8/8	EBC33	8/8	HVR2A 8/8
2X3	3/6	6QT7G	6/8	EBCA1	8/8	MU14 9/-
384	7/8	68A7	8/-	EBF90	10/-	P61 3/8
3V4	7/8	68J7M	8/-	EBC28	8/8	PC284 8/8
614	7/8	68A7	8/8	ECPF80	9/8	PCF80 8/8
5Y3	7/8	6Y6G	6/8	ECH42	10/8	PCL82 11/8
5Z4	9/8	6X4	7/8	ECL82	10/8	PEN25 8/8
6A6G	5/-	6X5	6/8	EP39	5/8	PLS2 10/8
6B8	5/-	12AX7	8/-	EP41	9/8	PV80 7/8
6BE6	7/8	12AU7	8/-	EP50	6/8	PV41 9/8
6BH6	9/8	12AX7	8/-	EPF80	8/-	PV82 7/8
6BW6	9/8	12BE6	8/8	EPF86	12/8	SV61 3/8
6D6	8/-	12K7	6/8	EP91	5/-	UBCH1 9/8
6E6G	7/8	12Q7	6/8	EP92	5/8	EBC42 9/8
6H6	9/8	35L0	7/8	EL32	5/8	UT41 8/8
6J5	6/8	58Z4	7/8	EL84	8/8	UL41 9/8
6J8	5/8	58	8/8	EM81	8/8	UY41 5/8
6K7G	6/8	807	5/8	EZ40	7/8	UZ22 8/8
6DG6	6/8	95A	1/8	EZ80	9/8	VR105 9/8
6K7G	5/8	EA50	1/8	EL148	1/8	VR150 9/8

**TV REPLACEMENT
 LINE OUTPUT
 TRANSFORMERS**

FROM 45/-ea. Most makes avail-
 able. S.A.E. with all enquiries.

LINE BLOCKING TRANSFORMERS, from 10/-.
 FRAME BLOCKING TRANSFORMERS, from 13/8.
FRAME OUTPUT TRANSFORMERS, from 27/6

HIGH GAIN TV PRE-AMP KITS
 BAND I BBC
 Tunable channels 1 to 5. Gain 18dB.
 ECC84 valve. Kit price 29/6 or 49/6 with power
 pack. Details 6d. (PCC84 valves if preferred.)
 BAND III ITA—Same prices.
 Tunable channels 8 to 13. Gain 17dB.
 ECC84 valve. (PCC84 valves if preferred.)

NEW MULLARD TRANSISTORS
 Audio OC1 1/2 6/- RF OC45 10/6
 OC2 7/8 OC45 9/6
 Sub Miniature Condensers. 0.1mFd. 30v. 1/3.
 1, 2, 4, 5, 8, 25, 60, 100 mfd. 15 volt, 2/6 each
 Weyrad Printed Circuit Components in Stock.
 Book 2/-, 7 x 4in. Speaker 35Ω 25/-.

**BAKER SELHURST
 LOUSPEAKERS**

12in. Baker 15w. Stalwart
 3 or 15 ohms.
 45-13,000 c.p.s. 90/-
 12in. Baker Stalwart four
 suspension, 15 ohms. 58
 40-13,500 c.p.s. 26
 12in. Stereo, 12 w. 58
 35-18,000 c.p.s. 58
 12in. Baker Ultra Twelve
 20 c.p.s. to 25 kc/s. £17.10
 1in. Bass Auditorium
 Mk II, 35 w. 415



CRYSTAL MIKE INSERT by Acos precision
 engineered. Size only 1 1/2 in. by 3/8 in.

ALUMINIUM CHASSIS 15 s.w.g. undrilled.
 With 4 sides, riveted corners and lattice fixing
 holes, 2 1/2 in. sides, 7 x 4 in., 4/8; 9 x 7 in., 5/8;
 11 x 7 in., 6/8; 13 x 9 in., 8/8; 14 x 11 in., 10/8;
 15 x 14 in., 12/8; 18 x 16 x 3 in., 16/8.

ALUMINIUM PANELS. 18 s.w.g. 12in. x 12in.,
 4/8; 14 x 9 in., 4/-; 12 x 8 in., 3/-; 10 x 7 in., 2/3.

JASON F.M. TUNER COIL SET, 29/6. H.F.
 coil, aerial coil, Oscillator coil. Two I.F. trans.
 10.7 Mc/s Ratio Detector and heater choke.
 Circuit book using four 6AM6. 2/6.

COMPLETE JASON F.M. KIT, FM7L, with
 set of 4 valves, etc., £6.50.

BBC TRANSISTOR RADIO. Med. and Long
 Wave. Two transistors and diode. Complete
 kit, 32/6. Details 7/8 extra or Deaf Aid Earpiece
 7/8. Postage 6d.

485 Kc/s. SIGNAL GENERATOR. Total cost
 15/-; Uses B.F.O. Unit ZA 30038 ready made.
POCKET SIZE 2 1/2 x 4 1/2 in.
 Slight modifications required. Full instructions
 supplied. Battery 7/8 extra. 69 v. + 1 1/2 v.

**COMPLETE RADIO
 £4.19.6 post free**



4 Mullard valves, 5in. speaker, frame aerial,
 4 pre-set stations. 1 long, 3 med. wave.
Superhet Circuit.
 Size 9 x 6 x 5 1/2 in. high. Tested ready for
 use. 200/250 v. A.C.—D.C. Mains.

RECORD PLAYER BARGAINS
 Postage 2/- each.



4 Speed Autochangers, B.S.R., U.A.8 £18.10
 4 Speed Autochangers, B.S.R., U.A.14 £27.00
 B.S.R., U.A.12 Stereo/Mono . . . £8.50
 Garrard Model Autolism . . . £8.75
 4 Speed Single Players, EMI . . . £6.50
 Garrard TA Mk.11, GCB Head . . . £8.00
 Garrard Model 45P GCB . . . £13.75
 Garrard Stereo Heads, £2 extra.
 Amplifier player cabinets (except 4 H.F.) 68/-
 2-valve amplifier and 6in. speaker . . . 95/-
 3-valve amplifier and 6in. speaker . . . 106/-

Wired and tested ready for use with above.
 All sapphire styli available from 6/-.

Volume Controls 80 ohm CABLE COAX

Long spindles. Guaranteed 1 year. Midget
 5K Ohms to 2 Meg. 40 yds. 17/8
 N.O. Sw. D.P.5W. 60 yds. 25/-
 Linear or Log Tracks. 3/- 4/8
 Semi-air spaced. 1in.
 Losses cut 50%.
 40 yds. 17/8
 60 yds. 25/-
 Fringe Quality
 Air Spaced. 17/- yd.

TRIPLEXERS Bands I, II, III . . . 12/6
COAX PLUGS 1/- LEAD SOCKETS . . . 2/-
PANEL SOCKETS 1/- OUTLET BOXES . . . 4/8

BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms.
DITTO SCREENED per yd. 1/6. 80 ohms only.
WIRE-WOUND POSTS. 3 WATT. Present Min.
TV Type. All value 25 ohms to 25 K. 3/- ea.
80 K, 30 K, 4/- (Carbon 30 K, 2 to meg. 3/-)
KIRE-WOUND 4 WATT. Pots Long Spindle
 Values. 50 ohms to 50 K. 6/8; 100 K, 7/8.
CONDENSERS. New Stock. 10,000 pF to 8 v. 8 v.
 T.C.C. 5/8; Ditto, 20 K v., 8/8; 0.1 mfd., 7 k v.;
 Tubular 500 v. 0.001 to 0.05 mfd., 9d., 0.1 1/-;
 0.25, 1/6; 0.5/500 v., 1/9; 0.1/350 v., 9d.; 0.01/2,000 v.
 0.1/1,000 v., 1/8; 0.1 mfd., 2,000 volts, 8/8.
CERAMIC CONDS. 500 v., 0.3 pF. to 0.1 mfd. 9d.
SILVER MIC CONDENSERS. 10 pF. to 500 pF. 8 v.
 1/-; 500 pF. to 3,000 pF. 1/3. Close tolerance
 (±1 pF) 1.5 pF to 47 pF, 1/6. Ditto 1% 60 pF to
 815 pF, 1/9; 1,000 pF to 5,000 pF, 2/8.

New Electrolytics. Famous Makes

TUBULAR	TUBULAR	CAN TYPES
1/350v. 2/-	50/350v. 5/8	16/450v. 5/-
2/450v. 2/3	100/25v. 2/8	32/350v. 4/-
4/450v. 2/3	250/25v. 2/8	100/270v. 5/8
8/450v. 2/3	500/12v. 3/8	2,000/3v. 4/-
8/500v. 2/3	8-3/450v. 3/8	5,000/6v. 5/-
16/450v. 3/8	8-16/450v. 3/8	32-34/450v. 6/-
16/500v. 4/8	8-16/500v. 4/8	32-32+32/350v. 7/-
32/450v. 4/8	16+16/450v. 4/8	50+50/350v. 7/-
25/25v. 1/9	16+16/500v. 4/8	64-120/350v. 11/8
56/50v. 2/-	32-32+32/350v. 4/8	100+200/275v. 12/8

RECTIFIERS SELENIUM 300 v. 85 mA, 7/6.
CONTACT COOLED 250 v. 60 mA, 7/-; 50 mA, 8/6;
 58 A, 9/6; 200 mA, 21/-; 300 mA, 27/6.

COILS Wadjet "P" type, 3/- each. Osamor Midget
 "Q" type ad. dust core from 4/-.. All ranges.

TELETRON L & Med. T.R.P. with reaction, 8/6.
FERRITE ROD AERIALS, M.W. 9/8; M & L 18/6.
1 1/2" P.F. COLLS 4HP 7/- each. H.F. CHOKES, 2/6.
FERRITE ROD 3in. x 1/2 in. dia, 2/6.

FULL WAVE BRIDGE SELENIUM RECTIFIER;
 2, 6 or 12 v. 1 1/2 amp., 8/9; 2 a., 11/8; 4 a., 17/8.
CHARGER TRANSFORMERS. Tapped input 200/
 250 v. for charging at 2, 6 or 12 v. 1 1/2 amps. 15/6.
 2 amps. 17/6; 4 amps. 22/8. Circuits included.

VALVE and TV TUBE equivalent books, 9/8.
TOGGLE SWITCHES, S.P. 2/-, D.P. 3/8, D.P.D.T. 4/-.
WAVECHANCE SWITCHES
 8 p. 4-way 2 water long spindle . . . 6/8
 2 p. 2-way, or 3 p. 2-way short spindle . . . 2/6
 2 p. 6-way 4 p. 2-way, 4 p. 3-way long spindle 3/6
 3 p. 4-way, or 1 p. 12-way long spindle . . . 8/6
VALVEHOLDERS. Pax Int. Oct., 4d. EP50. EA50.
 6d. B12A, CRT, 1/3. Eng. and Amer. 4, 5, 6 and
 7 pin. 1/-; MOULDED MAZDA and Int. Oct., 6d.
 6d. B3A, B3B, B3A, 8d. BYG with can., 1/8.
 B5A with can., 1/8; CERAMIC EP50, BTG, B9A.
 Int. Oct., 1/-; OAS B7G, B9A, 1/-.
SPEAKER FRET. GOLD CLOTH. 17in., 26in., 5/-.
 26in. x 26in., 10/-; Tyan 2in. wide, 10/-; 11". 26in.
 wide, 5/-; Green or red, etc. Samples S.A.E.

**OUR ONLY ADDRESS
 337 WHITEHORSE RD.,
 WEST CROYDON**

RADIO COMPONENT SPECIALISTS

Post 1/-, unless otherwise stated. C.O.D. 2/- extra. (Export post Extra.) (Wed. 1 p.m.) THO 1665. Buses 133 or 68