


Practical

NOVEMBER 1962 2⁴-

TELEVISION

***OPERATING
CLOSED
CIRCUIT
TELEVISION
EQUIPMENT***

Camera Techniques Explained

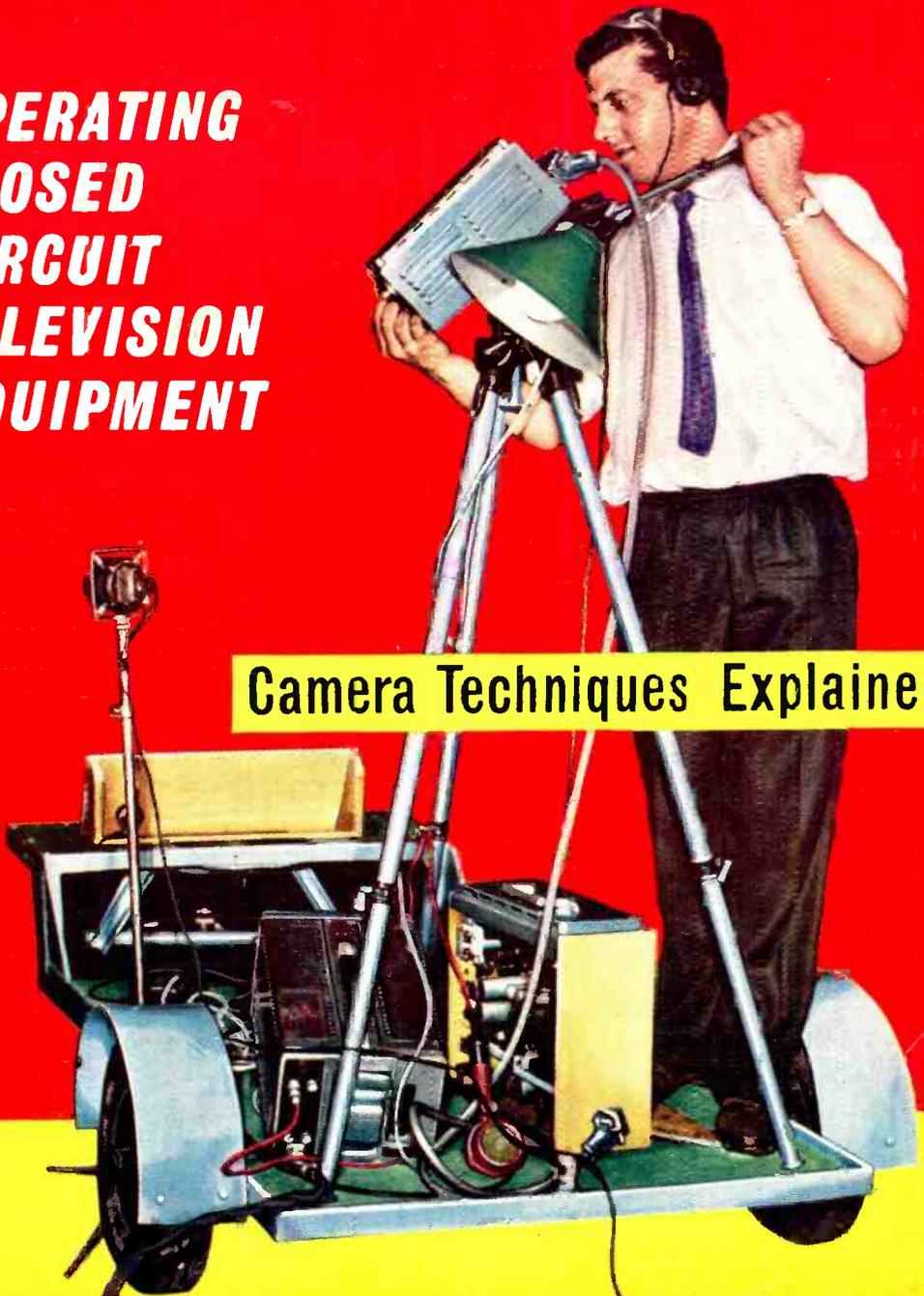

RADIO BARGAINS

SIGNAL GENERATOR



£7.50 or 30/- deposit and 6 monthly payments of 21/6. P. & P. 5/6 extra. Coverage 100 K/c/s, 100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10 x 6 1/2 x 5 1/2 in grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 230/250. Internal modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 800 millivolts. O.W. and mod. switch

variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.


OSCILLOSCOPE FOR D.C. and A.C. APPLICATIONS
A high gain, extremely stable differential V-amplifier (30 mV/C.M.). Provide ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurements of transistor operating conditions where maintenance of D.C. level is of paramount importance. Push-pull X amplifier; Fly-back suppression. Internal Time-base Scan Waveform available for external use; pulse output available for checking TV line O/P Transformers, etc. Provision for external "HP" and "C.R.T.". Brightness Modulation. A.C. mains 20/250. £18.18.0. P. & P. 8/- or £4.13.0 deposit, plus P. & P. 8/- and 12 monthly payments of 26/6. Full 12 Months' Guarantee including Valves and Tube.



ALIGNMENT ANALYSER

TYPE MCL2

A.C. mains 20/250 v. P.p. width: "A" Knob for "Sweep" Frequency Operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 K/s - 80 Mc/s. Capacitance Measurement. Two ranges provided, 0-80pF and 0-120pF. Special Facility enables true resonant frequency of any tuned out. I.F. transformer, etc., to be rapidly determined. Cash price £6.19.6. plus 5/6 P. & P. H.P. terms 25/- deposit, plus 5/6 P. & P. and six monthly payments of 21/6.

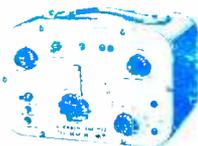

CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series). I.F. 16-19 or 23-38. Also can be modified as an aerial converter (instructions supplied). Complete with knobs. 32/6 plus 4/6 P. & P.



HEATER TRANSFORMER

To suit the above. 200-250 v., 6/-, plus 2/- P. & P.

LINE E.H.T. TRANSFORMERS



With built-in line and width control. 14kV. Scan coil, 90in. deflection on ferrite yokes. Frame O.P. transformer plus 18 kV smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.

29/6 plus 7/6 P. & P.


Focus Magnet suitable for the above (state tube). 10/- plus 3/- P. & P.

CHANNEL TUNER

I.F. 16-19 Mc/s continuously tunable from 174-216 Mc/s. Valves required: PCC 80 and PCC 81 (in series), C. converter B.B.C. and I.T.A. ranges, also Police, Fire and Taxis, etc.

Brand new by famous manufacturer

10/- plus 3/- P. & P.

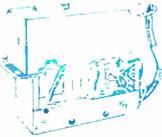

RADIO & T.V. COMPONENTS (Acton) LTD.
21c HIGH STREET, ACTON, LONDON, W.3.
All enquiries S.A.E. Goods Not Despatched Outside U.K.



BRAND NEW AM/FM (V.H.F.) RADIOGRAM CHASSIS AT £14.0.0 (Carriage Paid)

A.C. ONLY. Chassis size 15 x 6 1/2 x 5 1/2 in. High. New manufacture. Dial 14 1/2 x 4in. in 2 colours predominantly gold. Pick-up. Ext. speaker. Av. E. and Dipole Sockets. Five push buttons - OFF L.W., M.W., F.M. and Gram. Aligned and tested. O.P. Transformer. Tone Control. 1,000-1,300 Mc.; 200-500 Mc.; 88-98 Mc.s. Valves £2-50 incl. E.H.T.1, E.F.S.9, E.A.R.50, E.L.S.4, E.W.55. Speaker and Cabinet to fit chassis (table model). 47/6 post 5/6. 9 x 6in. SPEAKER. 20/- TERMS: (1 basket) £5 down and 5 monthly payments of £2 or with Cabinet and Speaker £5.10.0 down and 6 monthly payments of £2. Cheap Room Dipole for V.H.F., 12/6. Feeder 6d. v.d. Circuit diagram 2/6.



6 TRANSISTOR PORTABLE—Fully Built

The "SCALA" for only £9.17.6. carriage paid. 8 1/2 x 2 x 5 1/2 in. High. Choice of colours. Revers. M.W. and F.M. Portable aerial. Battery 2 1/2 extra. Pre-1 circuit. Nicly styled. A professional job. 3 1/2 in. speaker.

THIS SUPERB SET FOR £10

6 transistor radio covered in sponge clean Duracour 10 in. in latest two tone shades. M.W. and F.M. for better reception for an aerial 2 colour scale. With P.P.9 battery giving 300 hours use. Weighs under 4 lbs. with carrying handle. 12 x 7 in. high x 4 in. at base (aperture 6 1/2 in. at top). Brand new, fully guaranteed. £10.0.0 (incl. Worth 4/6).



A FEW NEW BRAVACAD TURRET TUNERS. ALL TYPES, 30/- each while stocks last (one post). Adapt 5/- extra state Model No. Terms Available on Items over £5. Send 5d. stamps will do for 20 page illustrated catalogue. All New Goods. Delivered by return. C.O.D. 2/- only. See our advertisement in "Practical Wireless" for more bargains. **ALL ITEMS GUARANTEED 12 MONTHS. VALVES 3 MONTHS**

GLADSTONE RADIO
"SCALA," CAMP ROAD, FARNBOROUGH, HANTS.
(Farnborough 3371 and at 247 New Road, Copnor, Portsmouth.
FARNBOROUGH CLOSED SATS. PORTSMOUTH WEDS.

E.M.S. TELEVISION TUBES

PROVED with a reliability:-

PACK A GREATER PUNCH THAN EVER
TRY ONE NOW AND SEE THE DIFFERENCE!

18 month guarantee with all our tubes

SIZE	PRICE	COST TO YOU WITH ALLOWANCE ON RECEIPT OF OLD TUBE
12in.	£4. 7.6	£3. 17.6
14in.	£4. 15.0	£4. 5.0
15, 16, 17in.	£5. 15.0	£4. 15.0

Carriage and Insurance 10 6 extra on all tubes

★ BUY FROM ACTUAL MANUFACTURERS WHO KNOW HOW TO REBUILD A TUBE

MARSHALL'S for TELEVISION LTD.
131 St. Ann's Road, Tottenham, London, N.15
STAMFORD HILL 3267 & 5555

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the *RIGHT* course:

RADIO & TELEVISION ENGINEERING
INDUSTRIAL TELEVISION

RADIO & TELEVISION SERVICING
RADIO SERVICE AND SALES

VHF/FM ENGINEERING : ELECTRONIC
COMPUTERS & PROGRAMMING

ICS provides thorough coaching for professional examinations:


Brit. I.R.E., City and Guilds Telecommunication Technicians, C. & G. Radio & TV Servicing (R.T.E.B.); C. & G. Radio Amateurs.

LEARN AS YOU BUILD

Practical Radio Courses

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build **YOUR OWN** 4-valve T.R.F. and 5-valve superhet radio receiver, Signal Generator and High-quality Multi-meter. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill. ICS Practical Radio courses open a new world to the keen Radio amateur.

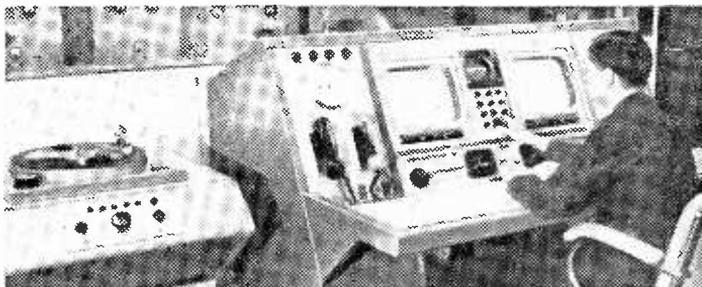*Technical
Training
in Radio,
Television
and
Electronics
Engineering
with*



THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER. FILL IN AND POST THIS COUPON TODAY.

You will receive the FREE 60 page ICS Prospectus listing examinations and ICS technical courses in radio, television and electronics PLUS details of over 150 specialised subjects.

Other ICS courses include: MECHANICAL, MOTOR, FIRE, ELECTRICAL & CHEMICAL ENGINEERING, FARMING, GARDENING, ARCHITECTURE & WOODWORKING, SELLING & MANAGEMENT, ART, PHOTOGRAPHY, etc., etc.

PLEASE STATE ON COUPON SUBJECT YOU ARE INTERESTED IN . . .



INTERNATIONAL CORRESPONDENCE SCHOOLS
(DEPT. 165), INTERTEXT HOUSE, PARKGATE RD., LONDON, S.W.11

PLEASE SEND FREE BOOK ON.....

NAME

ADDRESS

.....

OCCUPATION..... AGE.....

11.62

BENTLEY ACOUSTIC CORPORATION LTD.

THE VALVE SPECIALISTS

38 CHALCOT RD., LONDON, N.W.1

Nearst tube
Chaik Farm.

PRImrose
9090

FOR ONLY 6d. EXTRA PER ORDER WE WILL
INSURE YOUR VALVES AGAINST DAMAGE IN
TRANSIT. ALL UNINSURED PARCELS AT
CUSTOMERS' RISK.

MULLARD MIDGET SILICON RECTIFIERS
OUTPUT 250 VOLTS ½ AMP. NO BIGGER THAN A
SHIRT BUTTON: 8/- EACH. TYPE BY100.


0A3 17/8 6AG7 7/8	6K25 19/5	12AT7* 6/-	90C1 16/-	EAB080 9/-	EF36 4/-	EM81 9/6	PC088 18/-	U12/14 8/8	UCH81 9/6	OA79 3/-	
0B2 17/8 6AK5 8/-	6L1 22/8	12AU7* 6/8	90C3 37/6	EAF42 9/-	EF37A 8/-	EM84 10/6	PC089* 9/-	U16 10/-	UCL82 11/6	OA81 3/-	
0Z4 5/-	6AL5 8/-	6L6G 8/-	12AX7* 7/8	90CV 37/6	EB34 2/8	EF39 6/6	EM85 10/10	PCF80* 8/-	U19 48/8	UCL83 18/9	OA86 4/-
1A5 8/-	6AM6 4/8	6L7GT 7/8	12BA6 3/-	150B2 18/-	EB41 9/6	EP40 15/-	EN31 55/-	PCF82 10/8	U22 9/1	UF41 9/-	OA91 3/6
1A7GT 12/-	6AQ3 7/8	6L8 13/-	12BE6 9/-	807 7/8	EB91 4/-	EF41 9/-	EP41 9/-	PCF84 16/8	U24 29/1	UF42 15/8	OA95 8/6
1C5 12/6	6AT6 7/-	6LD20 15/8	12BE6 9/-	807 7/8	EB03 23/10	EF42 10/8	EY3 13/6	PCF90 9/6	U25* 17/6	UF80* 10/6	OA210 9/6
1D8 10/8	6AU6 10/-	6P28 25/11	19AQ5 10/8	7475 7/8	EB03 23/10	EF42 10/8	EY3 13/6	PCL2* 10/-	U26* 10/-	UF85* 7/-	OA211 13/6
1G8 17/6	6BA6 7/8	6P7G 9/6	19H1 10/-	A231 10/-	EB03 23/10	EF42 10/8	EY3 13/6	PCL3* 10/8	U31 11/6	UF89* 13/6	OC16W 35/-
1H3GT 10/8	6BE9 6/-	6P7GT 11/-	20D1 14/11	AZ41 13/7	EB03 23/10	EF42 10/8	EY3 13/6	PCL5* 12/6	U33 29/1	UF91 9/-	OC22 23/-
1L4 3/6	6BH6 8/-	6R7G 10/-	20P2* 25/11	B36 15/-	EBF80 9/-	EF73 16/8	EY4 13/6	PCL6 16/2	U37 25/11	U144 25/11	OC26 25/-
1L5 5/-	6BL6 6/-	6SUG 7/8	20L1* 25/11	CL33 18/9	EBF83 13/7	EF80* 6/-	EZ80 7/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
1LN5 5/-	6BQ7A 15/-	6V8G 7/8	20P1* 25/11	CY1 18/2	EBF89 9/6	EF86* 6/-	EZ81 7/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
1NSGT 10/8	6BR7* 12/6	6V8GTG 9/6	20P3* 22/8	CY31 11/-	EC54 9/-	EF86* 10/6	EZ80 7/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
1R5 6/6	6BR8 18/2	6X4 6/-	20P4* 25/11	EC32 10/6	EC70 12/6	EF89 9/-	EZ82 10/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
1R4 9/6	6BW6* 10/6	6X5GT 6/-	20P5* 22/8	DAF91 6/-	EC81 27/6	EF91 4/6	EZ84 14/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
1R5 6/6	6BW7* 6/-	6X80L2 10/-	2524G 11/8	DAF96 8/6	EC92 13/-	EP92 4/6	JLN3028/11	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
1T4 8/6	6C4 9/-	7B7 9/6	30T1* 8/-	DD41 13/7	EC93 23/11	EP92 13/6	IVR2 20/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
1U5 6/-	6C5 6/6	7C5 8/-	38L7 7/-	DF33 10/6	EC95 8/6	EP99* 13/-	KT3C 10/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3A4 6/-	6C6 6/6	7C6 8/-	30C1* 8/-	DF66 18/-	EC99 17/8	EP99* 13/-	KT3C 10/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3A3 10/6	6C9 13/6	7H7 8/-	30P5* 6/-	DF91 3/6	EC98* 6/-	EP18* 12/6	KT41 25/11	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3B7 12/6	6CH6 9/-	787 9/6	30FL* 10/-	DF99 9/6	EC98* 6/6	EK32 8/6	KT44 12/6	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3D6 5/-	6CW4 24/-	7T7 9/6	30L1* 8/-	DF97 9/-	EC98* 7/8	EL32 5/-	KT61 12/6	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3E4 7/6	6F1 25/11	7Y4 7/8	30L15* 9/-	DH53 6/6	EC98* 9/-	EL33 12/6	KT68 7/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3Q5GT 9/6	6F6G 7/-	9BW6 14/11	30P4* 115/-	DK32 12/-	EC98* 8/6	EL33 12/6	KT68 7/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3S4 7/-	6F13 11/8	10C1 13/6	30T2 7/6	DK91 6/6	EC98 18/-	EL38 25/11	KT88 43/6	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
3V4 7/6	6F23 10/8	10C2 25/11	30P1 10/6	DK92 10/6	ECF80* 10/8	EL41 9/-	KTW61 6/6	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
5R4GY 17/8	6F24 12/6	10F1 25/11	30P13 12/6	DK96 8/6	ECF82 10/8	EL42 10/6	KTW62 7/8	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
6L4G 6/6	6F33 7/8	10LD11 13/7	33LGT 9/6	DLS3 9/6	ECF86 10/5	EL41 10/2	KTW63 8/8	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
6V4G 10/-	6J5G 5/-	10P13 15/-	33W4 7/6	DL66 17/8	ECF84 20/8	EL43 19/6	KTW63 7/8	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
5Y3 6/6	6J6 5/8	10P14 15/8	35Z4GT 6/-	DL68 15/8	ECF81 9/6	EL9 6/-	R12 3/6	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
5Z3 18/6	6J7G 6/-	12A06 14/11	33Z5GT 9/-	DL72 15/-	ECF85 6/6	EL55 13/7	MHLD612/6	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
6Z4G 9/-	6J7GT 10/8	12AD8 16/10	50C3 10/-	DL92 7/-	ECF82 9/6	EL56 16/10	R18 18/-	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
6A7 10/8	6K7G 9/-	12A28 13/7	50L8GT 10/-	DL94 7/8	ECF81 9/6	EL9 6/-	R12 3/6	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
6A8 9/-	6K7GT 6/-	12A27 8/-	85A2 16/-	DL96 8/8	ECF83 13/7	EL95 10/8	N108 23/10	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
6AC7 4/-	6K8GT 10/8	12A85 12/8	90A0 6/8	DM70 7/8	ECL80 9/-	EL920 18/2	T41 10/8	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6
6AG5 5/6	6K8G 6/8	12A76 7/8	90AV 6/8	E0F 30/-	ECL82 10/6	EL822 19/8	N308 20/1	PEN46 16/2	U43 13/8	U146 14/8	OC28 24/6

Terms of business—Cash with order or C.O.D. only. Orders value £3 or more sent post/packing free. Orders below £3 please add 6d. per valve. C.O.D. 2/8 extra. We are open for personal shoppers. Mon.-Fri. 8.30-5.30. Sat. 8.30-1 p.m. Please enquire for any item not listed.

* indicates valves with new type chemical coating for extra life and reliability.

All valves new, boxed, and subject to makers' full guarantee. We handle first grade goods only, and do not sell seconds, rejects, nor items stripped from new or used equipment. All orders despatched same day. Complete catalogue of valves and components with terms of business 6d.

WORTH LOOKING INTO!

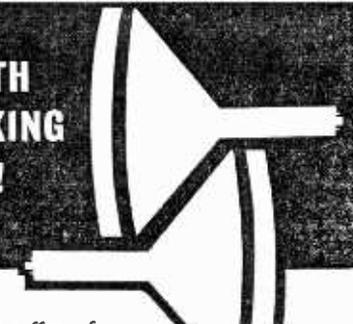

7

Outstanding offer of

guaranteed
rebuild cathode
ray tubes 59/6 each

12" & 14" Types MW 31-74,
M W 36-24, SE 14-70; 4/14
C 14 FM

Carriage paid
CASH WITH ORDER

SIMILAR BUT PARTLY USED, GUARANTEED 30/- EACH

Tates

ELECTRONIC SERVICES LTD

3 Waterloo Road,
Stockport, Cheshire
Telephone: Stockport 7301

COMPLETE TELEVISIONS

14 INCH	17 INCH
£7.10.0	£11.10.0

- ★ Guaranteed 12 months. Tubes, Valves, Components.
- ★ Ex. Rental and repossessed television sets.
- ★ Two channels more, 7/6 extra.
- ★ H.P. Terms—London area.
- ★ Demonstrations daily.
- ★ Legs—39/6 per set.
- ★ Part exchange allowance on Radios, TV's, etc.

Personal collection advised, or Insured Carr., 14", 20/-; 17", 30/-.





SPEAKERS

8/9 EACH

6in. 8in. 7in. x
4in. Money back
guaranteed. Enquire for other
sizes. Ex. mfd. salvage. P.P. 1/3

TRANSISTORS

2/- Each

Send for Free List.

VALVES 9d. Each

Thousands of ex-service stock, and ex-government. All good. MOST TYPES AVAILABLE. 3d. STAMP FOR LIST.

DUKE & Co (London) Ltd

1L Ford 6001/3

621/3 ROMFORD RD.
MANOR PARK E12
Stamp for latest Free List.

REGUNNED TUBES

21 in. 99/6	17 in. 90/-
15, 14, 12 in. 70/-	

Terms Guaranteed Ins. & Carr. available. 1 year. 12/6. Add £1, refundable on receipt of your OLD tube.

35/- 36/24, 14KP4, 14L. Ex. Rental stock 5/- carr.



110° Tubes in Stock.

REBUILT AND RESCREENED CATHODE RAY TUBES

Complete with all new components excepting glass

FOR QUALITY, RELIABILITY AND SERVICE BUY FROM BRITAIN'S
LARGEST GROUP OF INDEPENDENT MANUFACTURERS OF REBUILT
CATHODE RAY TUBES

SUFFOLK TUBES LIMITED
1/3 UPPER RICHMOND ROAD
PUTNEY, S.W.15.
Tel: Vandyke 4304/5267

MIDLAND TUBES LIMITED
37 GEORGE STREET
MANCHESTER, 1.
Tel: Central 4568/9

VIDIO REPLACEMENTS LTD
25 ADDINGTON SQUARE
CAMBERWELL, S.E.5
Tel. Rodney 7550/7559

ALL TYPES - KEEN PRICES - PROMPT DELIVERY
12 MONTHS' GUARANTEE WRITE FOR BROCHURE

Winter Trading Co. Ltd.
95 Ladbrooke Grove
London, W.11
and Branches

Weston Hart Ltd.
236/8 Fratton Road
Portsmouth
Tel: Portsmouth 24125

Lawsons Ltd.
36 Cornhill
Bury St. Edmunds, Suffolk
Tel: Bury St. Edmunds 3304

J. H. Sunderland
11 Clements Street
Rochdale, Lancs.
Tel: Rochdale 48484

Wizard Productions
16 Wither Grove
Manchester
Tel: Dea 2772

Chester Radio
11 City Road
Chester
Tel: Chester 24727

Taylor's
162 Eastney Road
Milton, Portsmouth
Tel: Portsmouth 35000

Millards Southern Rentals
3 High Street
Aldershot, Hants.
Tel: Aldershot 20408

Lucketts of Banbury
57a/58a High Street
Banbury, Oxon
Tel: Banbury 2813

Electrical Marketing Co. Ltd.
12A College Square North
Belfast 1
Tel: Belfast 33340

R.E.D. Ltd.
Waltham Street
Crewe
Tel: Crewe 4364

Fylde Television Services
460 Talbot Road
Blackpool
Tel: Blackpool 31159

Hi-Lite Ltd.
89 Southbourne Grove
Southbourne, Bournemouth
Tel: Bournemouth 44344

R. Watson
Leathern Bottel
Wavenden, Woburn Sands, Bucks
Tel: Woburn Sands 2027

R.E.S. Ltd.
17/19 Paynes Lane
Coventry
Tel: Coventry 28781

J. Wildbore Ltd.
6-12 Peter Street
Oldham
Tel: Mai 4475

FOR
READERS OF
"PRACTICAL
TELEVISION"
AT REMARKABLY
LOW COST!

RADIO, TELEVISION & ELECTRICAL REPAIRS



AMAZING 'KNOW HOW' BOOK Saves You Pounds

Here is just the practical, at-a-glance guidance YOU need, whether you wish to know how to service radio and TV sets, install lighting points or repair any domestic appliance, from a bell or an iron to a vacuum cleaner or washing machine. Explains basic principles and working of modern radio and TV sets and electrical appliances. Shows how to test for faults, carry out maintenance and repairs by the most modern methods. Special section on the operation and servicing of frequency modulated receivers. 480 pages. Over 400 illustrations. Amazing VALUE—Standard Edition, 21/-; De Luxe, leathercloth, 23/- Or on easy terms, 5/- down and 3 monthly instalments. (Total credit prices: Standard, 22/-; De Luxe, 24/-)

ESSENTIAL TO EVERY SERVICE ENGINEER, ENTHUSIAST AND HANDYMAN!

Getting the best from RADIO AND TV SETS

Here is expert advice that will enable you to make the necessary adjustments or repairs in order to get the best possible performance from any radio or TV set.

All you need to know about DOMESTIC WIRING




Learn from these helpful pages how to carry out all kinds of installations and extensions—with efficiency and safety! Complete guidance on conductors, insulation, safety regulations, conduits, cables, earthing, practical work, fuses, flexible cords, etc.

BASIC RADIO CIRCUITS

All you want to know about circuits, so that you can find your way around modern sets without hesitation. How components form various types of set; gives circuits for 1-valve receiver, 3-valve receiver, battery TRF receiver, 4-valve superhet, Universal sets, etc.

See how to maintain
**Vacuum Cleaners
and Floor Polishers,
Refrigerators, Cookers
and Boiling Plates,
Washing Machines, etc.**

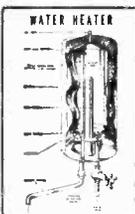Do your own
BATTERY CHARGING
Here are clear, complete instructions.



FIRES & SPACE HEATERS

Full, easy-to-follow instructions for servicing small domestic fires—whether of the radiant, reflector or convector type.

WATER HEATING

All you should know about the various types of electric water-heaters and how to install them and keep them in perfect working order. Advice that will save you POUNDS!

TRACKING DOWN TROUBLE

This grand book is invaluable for tracing faults in radio and TV sets. Tells you all you want to know—from carrying out Preliminary Tests to aligning R.F. and I.F. circuits. Shows how to carry out Dynamic Testing. Also shows how to trace the causes of Noises, Distortion and Instability and deal with the trouble. Gives detailed information on Components and Loudspeakers and how to deal with any faults that may develop.



ALL THIS—AND MORE IN ONE GREAT VOLUME!

Comprehensive Contents Include:
Current, Voltage and Resistance. Coils, Capacitors and Valves. Basic Radio-receiver Circuits. Preliminary Tests. Instruments for Set Testing. Locating Faults. Dynamic Testing. Tuned Circuit Alignment. Noises, Interference, Distortion and Instability. Components. Loudspeakers. Pick-ups. Gramophone Motors. Frequency Modulation. Television Circuits and Test Gear. Television Faults, Symptoms and Cures. Aerials and Pre-Amplifiers. Maintenance of Domestic Electric Wiring. Small Appliances. Fires and Space Heaters. Vacuum Cleaners and Polishers. Rewinding Small Motors. Cookers and Boiling Plates. Washing Machines. Refrigerators. Electric Water Heaters. Battery Charging. Testing and Repairs, etc.

DO THIS NOW!

Simply complete form, indicating Edition preferred, and post in a 2½d. stamped, unsealed envelope to Dept. H.F.35, Odhams Press Ltd., Basted, Sevenoaks, Kent. Offer applies in the U.K. and Eire only, closes November 30.

FULL SATISFACTION GUARANTEE

SEND NO MONEY NOW!

To: Dept. H.F.35, Odhams Press Ltd., Basted, Sevenoaks, Kent.

WITHOUT OBLIGATION reserve me "Radio, Television and Electrical Repairs" and send Special Invoice with "100% Satisfaction or No Charge" Guarantee.

Cross out edition NOT required: STANDARD/DE LUXE

Tick method of payment preferred: CASH TERMS

BLOCK LETTERS BELOW

NAME _____

Full Postal
ADDRESS _____

H.F.35/Nov.'62 _____

Practical Television

AND TELEVISION TIMES

VOL. 13, No. 146, NOVEMBER, 1962

Editorial and Advertisement
Offices:

PRACTICAL TELEVISION

George Newnes Ltd., Tower House
Southampton Street, W.C.2.

© George Newnes Ltd., 1962

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for trans-
mission by Canadian Magazine Post

SUBSCRIPTION RATES

including post for one year

Inland - - - - £1.8.0 per annum
Abroad - - - - £1.6.6 per annum
Canada - - - - £1.5.0 per annum

Contents

	Page
Editorial	53
Telenews	54
Principles and Practice	56
ABC of Television Circuits	59
Servicing TV Receivers	62
Impedance Bridge	64
Servicing Data	69
Closed Circuit TV	72
Underneath the Dipole... ..	77
Your Problems Solved	79
Trade News	87
Letters to the Editor	91

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television" such articles should be written on one side of the paper only and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to The Editor, "Practical Television" George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Pilkington Postscript

At the time of writing, it seems likely that the Government will give the go-ahead for the licensing of "Pay-TV" experiments in order to assess the public demand for such a service and to determine the most suitable types of programmes and which form of pay-as-you-view TV is best technically.

It is not our intention to comment on the rights or wrongs of the case for Pay-TV but it is interesting to observe that if it is authorised then one more Pilkington Report recommendation goes by the board.

In fact, so many bricks have been knocked off the Pilkington edifice that nothing much remains except the foundations and these—the technical aspects—were laid in the earlier work of the Television Advisory Committee (May, 1960). The recommendations of a technical nature, in fact, appear to be the only ones more or less accepted *in toto*. Yet these were a very small part of the Committee's work, covering a mere 25 of the 342 pages in the published Report.

A study of this now celebrated document gives the impression that the Committee found little point in proceeding too far in the deep waters of technicalities which had already been thoroughly investigated by TAC. In fact it is stated that "Provided that since the Report (TAC) was presented . . . no new technical considerations have arisen to question its findings, our concern is essentially to weigh the social and economic aspects of a change in line standards." And, later: "... there is no reason to qualify TAC's findings."

It seems, therefore, that the Committee was prepared to a large extent to accept the TAC findings. We are not arguing this point one way or another, and it must be remembered that there was only one technical member on the Committee. Nor are we going to be drawn, particularly at this late stage, into the highly explosive moral and social issues arising from the recommendations.

But in view of the drastically decimated state of the original suggestions and advice contained in the Report, and bearing in mind the previous work on the technical aspects provided by the TAC, we are sorely tempted to paraphrase the well-known wartime slogan and ask:

"Was the Pilkington Committee really necessary?"

A FILM SHOW

ON February 1st, 1963, beginning at 7.30 p.m., a film show is to be held at Caxton Hall, Westminster, London. As in previous years this show has been arranged in collaboration with Mullard Ltd. and will include the showing of the two films "Fuel for the Future" and "The Electroncers".

Readers are invited to apply to these offices for free tickets which are now available. When applying for tickets, please enclose a S.A.E. (which must measure at least 3½ × 6in.).

Our next issue dated December, will be published on November 22nd

Telenews

Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of August, 1962, in respect of, television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London	2,014,520
Home Counties	1,706,085
Midland	1,792,852
North Eastern	1,919,244
North Western	1,588,143
South Western	1,039,796
Wales and Border Counties	728,202
Total England and Wales	10,788,842
Scotland	1,100,152
Northern Ireland	187,776
Grand Total	12,074,770

Doctors Linked by Telstar

COLOUR Television Monitors, working on the American 525-line standards and supplied by Bush Radio Limited, played a key role in a recent Transatlantic Colour Transmission via the communications satellite Telstar.

Three thousand doctors from 50 countries attending the 12th Annual International Conference in Dermatology, in Washington D.C., saw a live "performance" by British doctors and their patients, broadcast from a special studio in the Royal Naval Air Station at Culdrose, Cornwall. They halted a two-way discussion by Landline with British doctors to watch TV transmission. From Culdrose the programme went by microwave link to Goonhilly and was then relayed by Telstar across the Atlantic.

A party of British doctors in a hangar at Culdrose saw the programme on a colour monitor at the same time as their colleagues were watching the transmission some 4,000 miles away!

Mobile TV Equipment

OUTSIDE broadcast equipment manufactured by EMI Electronics Ltd. is to be operated by

Trans Europe Television, which has bases in Switzerland and France, to provide a compact and versatile mobile multi-standard television and video tape recording facility.

Trans Europe Television will specialise in the provision to television and industrial organisations throughout Europe and America of full facilities in production and networking of television shows, and of international closed-circuit relays.

The equipment provided comprises two mobile units, each equipped with its own diesel electric generator unit. The first vehicle contains four EMI 4½ in. image orthicon camera channels with associated vision mixing equipment and full audio facilities. The second vehicle contains an Ampex 1,000C video-tape recorder. This vehicle is also equipped with 16m telecine and slide scanning equipment. There is a complete range of ancillary equipment including zoom lenses and special effects equipment.

A New 10 : 1 Zoom Lens for Image Orthicon Cameras

NEW types of optical glass, new principles of mechanical construction, developments in non-


spherical lens surfaces and improved techniques in anti-reflection lens coating are features of the latest television zoom lens, the Varotal V, announced by Rank Taylor-Hobson.

This new 10:1 zoom lens for orthicon TV cameras has been specially developed over the last two years to meet the ever growing demands of the TV industry.

This research has resulted in a new type of construction in which the components which move for zooming and for focusing are internal and smaller than before. Although the optical system is more complex the mechanical part is much more simple.

The resultant reduction of drive torque gives better sensitivity of control and the absence of rotating external parts provides adequate sealing against dust and moisture, better resistance to shock and facilitates the attachment of controls and accessories such as ray shades.

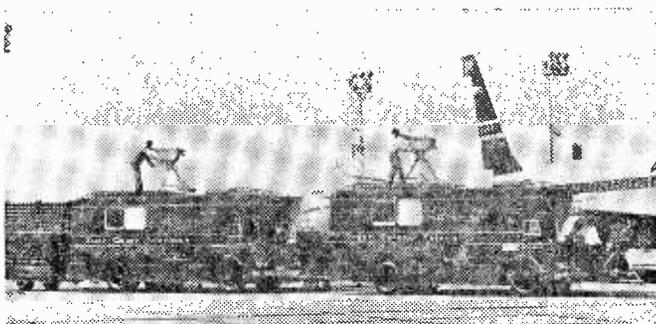The extended focal ratio of 10:1 has been achieved without sacrifice of optical performance, relative aperture or range of object distance. Its relative aperture of f4.0 and its focal range make it equally suitable for outside broadcasting or for studio use.



Mobile units of Trans Europe Television, with EMI cameras mounted on top.

High light transmission characteristics are ensured by the use of new types of optical glass not previously available and by the latest techniques in anti-reflection lens coating.

New Techniques at Cardiff TV Centre

WALES (West and North) Television, the last programme contractor to be appointed by the Independent Television Authority under the Television Act, started transmissions from the new Wales Television Centre in Cardiff, on 14th September.


EMI Electronics Ltd. was appointed the major supplier of studio equipment. The order included the supply of three 4½ in. image orthicon camera channels, complete with ancillary rack mounted units; a vidicon camera channel for the presentation suite; three complete sets of telecine equipment, comprising 16 and 35mm projectors and associated video equipment; and a fully transistorised sound mixing system for the main production studio.

Telecine equipment can be controlled either in the telecine area or in the master control area.

Comparable refinements on the main studio control panel allow programme producers to match up and control the light intensity of pictures coming from all three broadcast cameras, no matter where they are situated in the studio. In the past, the individual camera operators were responsible for these controls. This centralisation of control greatly decreases the margin for human error, an important consideration in any broadcasting work.

Closed-circuit TV in Air Traffic Control System

THE Southern Air Traffic Control Centre, located at the northern side of London (Heathrow) Airport, is responsible for aircraft movements over the southern half of the British Isles, taking over control of inbound airways traffic as it enters the London Flight Information Region from neighbouring regions and shepherding it along the complicated system of airways, spanning the country, until it can be handed over to airfield approach controllers at the final holding point. Outbound traffic is also the responsibility of this

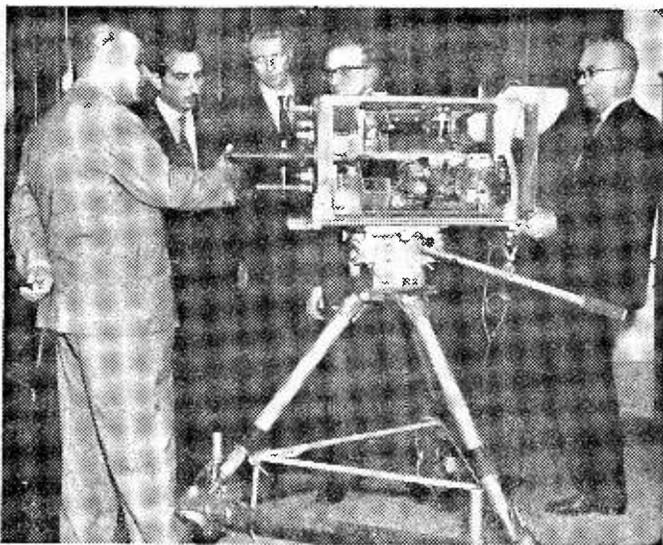

Two Iraqi visitors inspecting a Mark IV image orthicon camera during their recent tour of the Marconi Company at Chelmsford.

centre, from take-off until it leaves the area.

Methods of control have undergone many changes and have incorporated many improvements during the past 12 years. Among the more important has been the extended use of surveillance radar which, subject to certain precautionary measures, allows the procedural separation distances to be appreciably reduced. In this way controllers can accommodate an increased number of aircraft within the system without any reduction in safety. The minimum horizontal separation between two aircraft under radar control is five nautical miles.

The procedural and radar controllers, who look after aircraft within allotted air space, work as a closely knit team, details of every flight being presented to each in the most appropriate and lucid form. Hitherto, the information for the radar controller has been prepared and kept updated by an assistant seated alongside, and displayed on an edge-lit perspex screen. By the use of the Marconi closed circuit television system the requisite flight information appears on a television monitor close to the radar controller's console. This televised information is initiated remotely by an assistant who writes the information on a translucent screen for each of the radar controllers. Television cameras

installed behind each screen will produce a high definition picture for each of the radar controllers.

In order to ensure that this handwritten information appears sufficiently clearly on the television screen to eliminate the possibility of error in reading, even with characters at the very edge of the screen. Marconi's selected a vidicon camera designed for high quality telecine broadcasting work, and incorporated a number of modifications to meet the very high specification demanded by the Ministry of Aviation. The 8½ in. monitors also had to be modified from existing high quality designs, and the standard of definition produced makes it possible for a controller to read easily hastily written symbols.

Iraqi Visitors for British Firm

MAJOR General Mohammed Oli Baghdadi, Director General of the Ministry of Guidance of Iraq, and Mr. Osama Mohammed Ali, Chief Television Engineer, recently visited the Marconi Company at Chelmsford.

The purpose of their visit was to discuss the latest developments in general communication and television equipment. During their visit they stopped to inspect a Marconi Mark IV image orthicon television camera.

The PRINCIPLES and PRACTICE of TELEVISION

By G. J. King

REFER TO THE FREE DATA CHART, GIVEN AWAY WITH THE OCTOBER ISSUE, WHEN READING THIS ARTICLE

(Continued from page 11 of the October issue)

VERY high-frequency sound and vision signals tend to behave vaguely like light, and the effect becomes more pronounced as the frequency is raised. The signals thus travel in almost a straight line and instead of penetrating large, solid objects they tend to bounce off, rather like light being reflected by a mirror.

At ordinary medium sound-broadcast frequencies this does not happen. These signals find it relatively easy to travel through large masses and are not reflected.

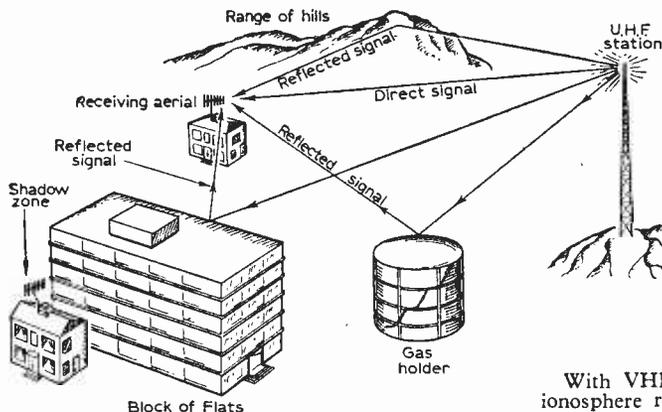


Fig. 7—As UHF signals behave very much like light and because of the very short wavelengths involved, multipath reception will be troublesome in built-up areas. Shadow zones will also be more in prominence than at VHF.

Surrounding our earth are two layers which influence radio and television signals to some extent, depending upon their frequency. The layer nearest the surface of the earth is called the "troposphere" which occurs towards the edge of our atmosphere. The other layer is well above this and, as a general term, is called the "ionosphere". In effect, it consists of several layers of ionisation named after the discoverers.

At broadcast frequencies (e.g., medium and long waves) signals are not affected by the troposphere and they pass straight through without trouble

until they arrive at the ionosphere. Here the effect is entirely different, since this layer is highly reflective to such signals, particularly to those in the lower-medium and shortwave bands.

These signals are thus reflected from the ionosphere back to earth again. Owing to the height of the ionosphere above earth, the signals are propagated over very great distances, and this is emphasised by the signals being reflected from earth back to the ionosphere again, giving multi-hop propagation.

Indeed, it is this phenomena which makes worldwide radio communication possible. Unfortunately, however, the ionosphere is often somewhat unstable, drifting like a large cloud, and this changes the reflecting properties and causes fading of the signals.

Moreover, the ionosphere is not always fully effective as a reflector, the properties changing by day and night, for which reason long-distance radio reception is very much tied to the clock.

With VHF signals in Bands I, II and III, the ionosphere rarely plays any part at all, since these go straight through both the troposphere and ionosphere and are thus lost in space. This is not always strictly true, though, for under certain weather conditions the lower frequency signals in Band I are sometimes reflected by a very dense ionosphere, and bounce off to traverse remarkably great distances as already described. As an example, the BBC television signals have often been received at the other side of the Atlantic! And in some extreme cases strong enough to produce a good picture.

This is abnormal propagation which cannot ever be relied upon for a television link. Normally, VHF

signals curve very slightly, as influenced by the lower troposphere, to follow the surface of the earth over a distance of about 50 to 60 miles but, again, depending upon frequency. The higher frequency signals in Band III, for instance, have less of a curvature than those in Band I, and for that reason reliable reception is reduced to about 40 to 50 miles.

During weather conditions usually associated with a fine spell, the troposphere itself alters slightly in character and may then appear to a VHF signal as the ionosphere appears to a medium-frequency signal. When this happens, television signals can be received well in excess of the normal average of 50 to 60 miles. Very great distances, however, are not covered because the troposphere is nowhere near as high as the ionosphere.

Nevertheless, such conditions often prove an embarrassment to shared-channel working, and

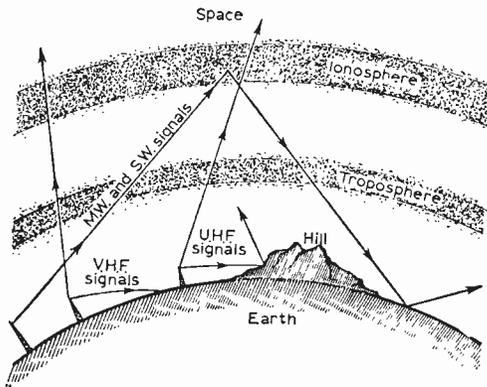


Fig. 8—How the various radio and television signals are affected by the troposphere and ionosphere.

produce the well-known co-channel interference troubles. European stations are then readily receivable in this country, and vice versa, but, unfortunately, often on top of our local programme!

UHF Propagation

Ultra high-frequency signals in Bands IV and V behave more nearly like light than any of the other signals so far considered. They are not affected by the ionosphere and only very slightly affected by the troposphere. There is virtually no bending and far less signal penetration through intervening objects than is the case at VHF.

These things set up various problems which very shortly some of us will be experiencing first hand. Since there is no bending, the range of a UHF station will not be any more than about 20 miles on the same scale as already considered at VHF.

Signals will be very easily cut off due to solid objects such as buildings, trees, roofs, hills and the like, and a signal shadow zone will exist behind them. Because the signals will not penetrate they will be reflected much more easily than we know at present; and because of the small wavelengths involved (30 to 65cm—about 12 to 25in.), even relatively small objects will cause reflections.

One can expect, therefore, that multipath interference (e.g., "ghosting") will be considerably

more troublesome than hitherto, especially in heavily built-up areas (Fig. 7). Thus, in addition to the direct signal, the receiving aerial will pick up random reflected signals all arriving at slightly different times after the direct signal.

Happenings of this kind cause several (the number depending on the number of reflected signals received) less intense pictures to appear to the right of the main picture. If the phase between the signals differs, then the reflected or "ghost" picture will be negative and the line and frame holds of the set may be impaired.

The drawing in Fig. 8 shows how the various signals considered in the foregoing behave in relation to the earth, the troposphere and the ionosphere.

It has been calculated that approximately three times as many UHF stations will be required to provide the same extent of coverage as given at present by the VHF stations. But in spite of that large number, there will still be many local shadow zones virtually without signal, and even in certain areas of high signal field multipath interference may complicate the matter of reception and demand the use of elaborate and carefully orientated aerial systems.

Local coaxial relay systems will almost certainly help to overcome some of these problems, and this kind of reception will be considered next month.

Pye Limited of Cambridge has already published a map showing probable sites and approximate service areas for UHF stations of given power, but so far there has been no definite Government sanction for UHF stations in these areas.

Line Standards

As is well known, the existing television system operates on 405 lines. This means that the picture is composed of 405 horizontal scanning lines. In practice, however, there are slightly fewer lines than this on the picture proper, as a few of the 405 are blacked out during the frame sync pulses.

A system of "interlaced scanning" is adopted. That is, one complete picture is made up of two frames or fields, and each frame contains a picture composed of only half the number of active lines. There are 50 frames and 25 complete pictures each second. The lines of the second frame are so arranged that they interlace with the lines of the first frame and in that way give a picture of the full number of lines.

Or, at least, it appears that way due to the persistence of vision. If something is not quite right in the set, then it sometimes happens that the lines of the second frame fall almost on top of the lines of the first frame. This is called "pairing" and detracts considerably from the overall definition of the picture. Indeed, if the lines of the two frames fall right on top of each other, half the picture is lost, but not only that, since a certain degree of distortion also occurs.

There are many old sets still in operation which give extremely poor interlace performance. The pictures appear very "liny" and such viewers are making do with a picture of 200 lines. On some models careful adjustment of the frame hold control is necessary to secure the best interlace.

More modern sets, however, are not so prone to this trouble under normal conditions, but can, nevertheless, give the effect if a fault occurs in the

frame oscillator or if the screening is removed from the line output stage.

Vertical Definition

The vertical definition of a picture is related directly to the number of lines, the greater the number, the better the definition. This is one of the reasons why there is going to be a change to 625 lines. The lines will still be visible, of course, but provided the receiver is interlacing adequately they will be less noticeable than 405 lines, particularly on the larger type of tube.

There will still be 50 frames per second and 25 complete pictures during the same period, as interlacing, as already described, will continue to be used. The 50 frames per second are tied up with the 50c/s mains frequency used in this country. In America, where the power frequency is 60c/s, there are 60 frames per second and 30 complete pictures, as interlace scanning is also in use over there.

The frames are produced in the receiver by the "frame timebase". This causes the "scanning spot" produced by the picture tube to traverse the screen vertically 50 times per second. On each downward "sweep", the spot moves on the screen at a very constant speed, but when it reaches the bottom of the screen it flies back to the top again at a terrific speed. This is called the "frame flyback", and is not normally visible on the picture because at that time the scanning spot is cut off due to the action of the frame sync signal.

On a receiver with only the frame timebase working, the high scanning speed of the spot gives the impression of a vertical, bright line on the screen. But under normal conditions, of course, the spot is at the same time being deflected horizontally, but very much faster.

In fact, it has to be deflected at a speed that will produce 405 lines on the existing system. Since the picture is fixed at 405 lines and that 25 pictures each made up of that number of lines occur each second, the spot has to be deflected horizontally at a speed equal to 405 times 25. This works out to 10,125, meaning that the "line timebase" has to operate at 10,125c/s for a 405-line picture.

The basic functions of the frame and line timebases are shown in Fig. 9. The vertical line which is produced with only the frame timebase running is shown at (a), while with only the line timebase running a horizontal line would be produced as at (b). At (c) is shown the effect when both timebases are running. As the scanning spot is being deflected much faster horizontally than vertically a series of lines are traced on the screen, slightly diagonal, underneath each other.

In effect, the spot takes off at the top left-hand corner of the screen, traces the first line and then flies back very quickly to the left of the screen again, where it commences to trace out the second line, but by now the frame timebase has deflected the spot down the screen a little, so that line and subsequent lines are traced at equal distance beneath each other.

There are one or two technical points here which modify this simple explanation a bit. It will be

recalled that a picture of only half the number of lines is produced each frame. This means, then, that the frame considered in Fig. 10 is made up of 202½ lines. For this to happen, and to allow the 202½ lines of the second frame (or field) to interlace accurately with the 202½ lines of the first frame, the first frame scan must finish on a half line, while the second frame scan must start on a half line—the idea being revealed in Fig. 10.

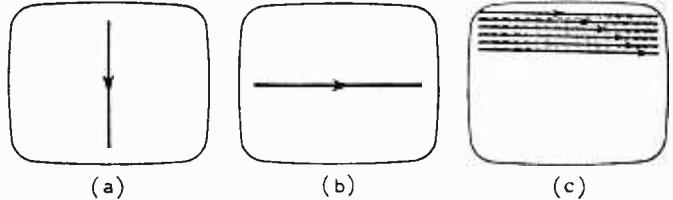


Fig. 9—The action of the timebases: (a) with the frame timebase only; (b) with the line timebase only; and (c) with both timebases.

This demands extremely accurate timing of the timebase, which is accomplished by the synchronising signals radiated along with the picture signals at the transmitter and by the sync circuits in the receiver.

Thus, we have seen that to produce the lines upon which a picture is built (which is called the "raster"), two timebases are required. The frame timebase which works at 50c/s, because this

matches the mains power frequency, and the line timebase which, to give a 405-line picture, works at 10,125c/s. The timebases can sometimes be heard operating due to electro-mechanical stress in the associated transformers. The frame causes a buzz, while the line causes a very highly pitched whistle, which cannot be heard by all.

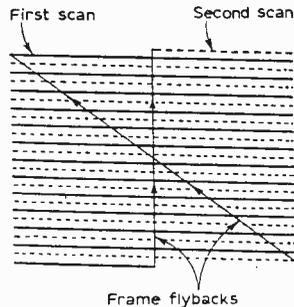


Fig. 10—Showing how an interlaced raster is produced.

How about 625 Lines?

Exactly the same ideas are employed at 625 lines. The frame timebase still works a 50c/s, but the line timebase has got to go faster to give the greater number of lines. We still get 25 complete pictures per second, so if we multiply this number by 625, we get the line frequency—which works out to 15,625c/s. This has the advantage that it is well above audibility and will thus not be heard as the shrill whistle of 405-line sets.

Clearly, then, among other things, the new dual-standard receivers must have some means of changing the line frequency from 10,125c/s on 405 lines to 15,625c/s on 625 lines.

(To be continued)

The ABC of TV Circuits

AN ANALYSIS OF THE DEVELOPMENT OF
TELEVISION CIRCUITS

By T. L. May

(Continued from page 35 of the October issue)

LARGER picture tubes and shorter necks produce greater angles of beam deflection. These in turn demand a greater scanning power than was hitherto required with the earlier types of narrow-angle tubes to deflect the electron beam through the large angle so that it scans the whole face of the tube in a linear manner.

The line timebase is the most important circuit in this respect, for in addition to having to supply scanning power it has to provide EHT for the final anode of the tube, and new tubes and brighter pictures require an EHT voltage which is almost twice that used in sets at the start of the present decade.

With the valve, component and circuit designers working closely together, various new line timebase circuits have been evolved. The aim has been in producing a circuit with the utmost of efficiency, so that the extra power is provided with the minimum of power drain from the H.T. supply, while maintaining the minimum of scan distortion.

New valves and designs for the line output transformer have facilitated these requirements, and the latest type of "wide-angle" receiver is of highly integrated design. The efficiency of the line output stage has been increasing progressively throughout the years and although early receivers had relatively efficient line stages, they are suitable for operating only either narrow-angle tubes and tubes with scanning angles up to about 90 degrees.

This is the reason why it is not usually possible to replace a tube in an early receiver with a wide-angle tube of current vintage without severely modifying the line timebase (and frame timebase in some cases). The new tubes require both a greater scanning power and EHT voltage than the early chassis is capable of providing. The results are usually singularly disappointing if a direct substitution of a new tube in an old set is attempted.

Booster Diode

The booster diode has been a part of the line output stage for almost a decade, and much has been written about its function. Briefly, this diode, apart from boosting the H.T. voltage, provides the first part of the line scanning current. The booster diode then switches out and the line amplifier valve proper switches in to provide the remainder of the line scan.

The extra energy reclaimed by the booster circuit is liberated in the inductive circuits of the line amplifier during the flyback period. In very early sets, this energy was rather an embarrassment, for it used to be responsible for so-called "ringing" in the line output stage, and cause alternate dark and light vertical bars at the left of the picture. This was because the pulse of voltage generated in the inductive elements of the circuit had the form of a damping oscillation (e.g., a decaying sine wave), and this used to modulate the line scanning current in a like manner.

This was partly avoided by causing the inductive elements to be heavily damped during the flyback period, and the power contained in the "ring" or damped oscillation was directed into a high-wattage resistor. The resistor used to get rather hot, and sometimes it was made variable as a rough and ready way of achieving a control of line linearity.

It was later discovered that a diode valve could be used both to suppress the vertical lines at the left of the picture and to capture the energy of the "ring", rectify it and add it to the H.T. line voltage. This was useful, for then it was possible to run the line output stage at greater efficiency.

The next step up the ladder was to get some of the energy of the "ring" to produce a portion of the line scan, and that was also done by rearranging the diode circuit. This kind of system is in use now in all recent models, but the overall efficiency has been enhanced even further during the last two or three years.

This has happened in several ways. A major contribution has been in the line output transformer itself, the efficiency of which has been stepped up remarkably by the use of low-loss ferrite cores. In such components, the "ring" during the flyback is encouraged, for it is this which supplies the extra energy, and thus increases efficiency.

The ratio of turns between the primary and the booster diode

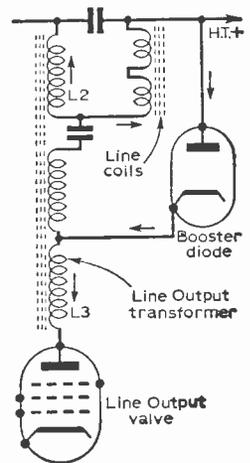


Fig. 16—A basic line output circuit, showing how the flux cancellation occurs in the core of the line output transformer. Since the current flowing in L2 is in the opposite direction to that in L3, the resulting fluxes are in opposition, and the overall flux is zero—or nearly so.

windings determines the relative conduction periods between the line output valve and the booster diode. For maximum efficiency there is a critical ratio, and this is one of the things which has been under examination. Of recent times the ratio has been modified so as to provide a conduction overlap between the line output valve and booster diode.

This arrangement has been found to give a step-up of both scanning current and EHT voltage for a nominal H.T. current. By reducing the tap for the line scanning coils on the transformer, the scanning current and EHT for normal requirements is restored, and the resulting effect is that the H.T. current is reduced—meaning a further increase in efficiency.

High EHT voltage brings in its wake high peak voltages at the line output valve and booster diode, since these are connected direct to the high reflected inductance of the line output transformer. These presented some problems in terms of valve insulations, and special valves were evolved for the new circuits—typically, the Mullard PL36 line output valve and PY800 booster diode.

Although these valves have higher peak voltage and current ratings than their earlier counterparts, it was still necessary to reduce the peaks in a practical circuit on the flyback, and here the circuit designers solved the problem by arranging the line timebase to have a slightly longer flyback time without impairing the newly found efficiency.

While the older type of line output transformer has several separate windings, the new transformers are mainly of the auto-transformer principle, where one highly efficient winding is tapped to the various circuits.

Flux Cancellation

Direct current in the windings of early line output transformer results in a unidirectional component of magnetism in the core, this being superimposed on the normal "swinging flux" caused by the line timebase signal. The flux due to the direct-current (e.g., the anode current of the line output valve) introduces two undesirable features. Firstly, it causes the core of the transformer to saturate on the peaks of the signal. And secondly, it encourages line whistle.

Core saturation is bad since it means that the core has to be of greater volume than strictly necessary for the line signal proper. The line whistle is produced in the core of the line output transformer by a process called "magnetostriction". This is related to the mechanical movement of the core when under the influence of a magnetic field, the movement being proportional to the intensity of the magnetic field produced by the windings.

Now, when the windings are carrying direct-current, the intensity of the magnetic field is greater on one swing of the line signal than the other. On one swing, for instance, the flux due to the direct current will add to the flux of the signal, while on the opposite swing there will be subtraction of the fluxes.

This causes unbalance in the swing of flux in the core, and aggravates line whistle—in rather the same way as an engine becomes noisier when it is out of balance. By cancelling the flux due to the direct current, the swing of flux is made similar on each half cycle, and the whistle is considerably reduced.

This is accomplished basically as shown in Fig. 16. Direct current from the H.T. line flows through L2 of the line output transformer in the direction shown by the arrow, while the current via the booster diode flows through L3 in the opposite direction. This produces two components of flux in the same core, and since these are more or less equal in intensity and opposite in polarity, the over-all flux in the core is almost completely neutralised.

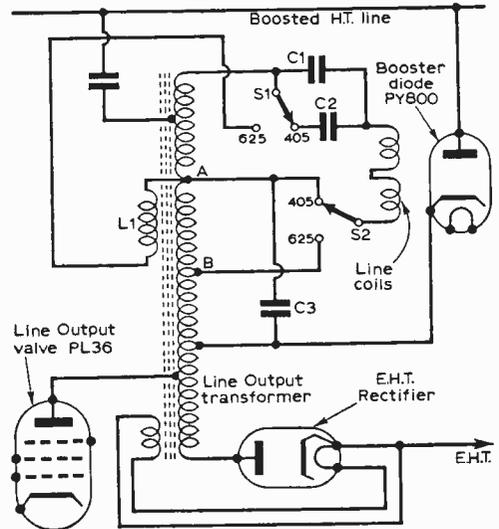


Fig. 17—In order to maintain maximum efficiency in the line output stage on 405 and 625 lines, the line output transformer has to be switched as shown.

This, then, permits the use of smaller cores than in previous transformers and, in spite of the greater power now present in line output stage, the line whistle is now considerably less troublesome than in the earlier receivers.

Tuning on the Flyback

The modern line output transformer is also engineered in relation to its associated components so that its tuned frequency is equal to the third harmonic of the current pulse produced during the flyback period. This is accomplished by a small tuning capacitor being connected to the windings of the transformer.

The transformer, of course, must be specially designed to provide this condition, and it is not usually possible to introduce this feature in a stage employing the old style transformer. Third harmonic tuning ensures that the current generated in the loss inductance of the transformer is completely exhausted at the finish of the flyback.

As a result, the pulse voltage at the anode of the EHT rectifier is increased (thereby providing a greater EHT voltage), while the pulse voltage at the anode of the line output valve is decreased (relieving the strain on the valve). Owing to the

greater EHT pulse, the EHT overwind now requires fewer turns to provide the required voltage. Some transformers use an entirely separate winding for the EHT overwind, and as less turns mean less resistance, the regulation is also improved.

From the foregoing, it will be appreciated that the line output transformer is now very much a part of the actual design of the line output stage, and for that reason the correct replacement transformer should always be used. The former practice of making a replacement with so-called "standard" transformers is now impossible if optimum efficiency of the line output stage is to be maintained. It will also be understood that the line output stage is somewhat delicately balanced in terms of efficiency, so that any shortcoming in a valve, transformer or other component will show up more quickly in the line output stage than in other circuit sections.

405/625 Line Transformer Switching

Since a transformer is geared up to one specific frequency in terms of third harmonic tuning and so on, it follows that its efficiency would be greatly impaired simply by changing the line frequency and without altering any of the other parameters. To provide a 405-line picture the line timebase has to operate at 10,125c/s, while for a 625-line picture the line frequency has to increase to 15,625c/s. This frequency change occurs in the line oscillator stage when a dual standard receiver is switched from one system to the other.

Clearly, then, there must also be some sort of switching in the line output stage to that the efficiency remains high at both frequencies. The

basic method of solving this problem is depicted in Fig. 17.

In the 405-line position, S1 connects C1 in parallel with C2 to give the optimum line linearity correction for 10,125c/s. S2 connects the line scanning coils to tap A on the transformer to provide the correct level of scanning current in the coils. The transformer is tuned to the third harmonic of the flyback frequency by C3 in conjunction with the distributed capacitances of the transformer windings. Thus, the stage operates in the manner already described.

In the 625-line position, however, both S1 and S2 change over. C2 is disconnected so that C1 alone is used for optimum line linearity at 15,625c/s. S2 switches the line scanning coils from tap A to tap B, while S1 also switches in winding L1. As this winding is effectively coupled mainly to the EHT overwind, the leakage inductance is reduced and the transformer is re-tuned to third harmonic of the 14,625c/s flyback.

The circuit is designed so that the ratio of flyback to line scan time remains constant at both frequencies, thereby ensuring that both the EHT voltage and the pulses in the various parts of the circuit also remain constant on both systems.

Without such precautions, the line linearity, line scan amplitude and EHT voltage would change radically from one system to the other. Indeed, this is already being discovered by experimenters changing the line timebase frequency of 405-line-only receivers so that they will be ready for the new 625-line test signals and so that the receiver can be used for the reception of Continental transmissions.

(To be continued)

Testing Decoupling Capacitors

By I. F. Skelton

HERE is a rapid means of testing decoupling capacitors in a television set. Apply a signal from a variable oscillator across the capacitor to be tested and measure the signal with the aid of a crystal diode detector and a moving coil microammeter.

If the capacitor is good it will virtually short-circuit the signal and no reading will be measured. However, if the capacitor is open-circuit or low in value an appreciable reading will be observed.

The signal generator can be adjusted to any I.F. or R.F., thus enabling any set to be tested in this way.

The theoretical circuit is given in Fig. 1. D1 is an ordinary crystal diode of the type used in the video detector stage of a television receiver. C1 is a 50pF silver mica or ceramic capacitor.

The probe was constructed inside a valve screening can, but an I.F. screen would be quite suitable. Layout is not critical provided leads are kept short and normal H.F. constructional practice is observed.

This method really does work and saves many hours of valuable time which might be wasted disconnecting capacitors for testing. A further advantage is the fact that the set is not switched on during the test. ■

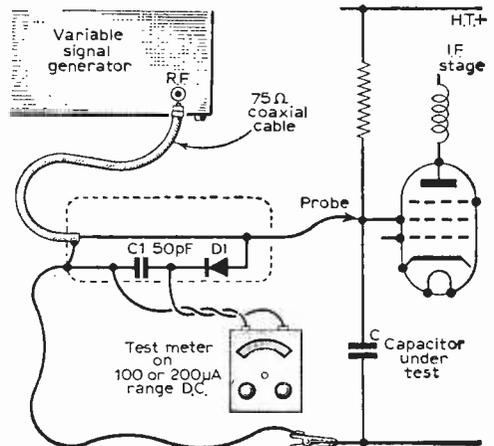


Fig. 1—The arrangement used in the tests.

SERVICING TELEVISION RECEIVERS

No. 83—ALBA T394 and T484

By L. Lawry-Johns

(Continued from page 14 of the October issue)

If the bottom of the picture is compressed in relation to the top which may be extended, check the PL82 and C48 (100 μ F). If stubborn, check C46-C47. If the bottom is folded up check the PL82 and then C49 0.1 μ F for leakage.

Vertical Hold

If the hold control is at the end of its travel check R50 and R53. In later models R50 was changed to 1.5M but R53 remained at 470k. If the control is not at one end but the frame rolls up or down the lock being critical, if available at all, check V8 and all components associated with V8A pins 6, 7, 8 and 9. Also check R25 (1.5M) if the line lock is also critical. Weak sync and loss of contrast also results if C20 (100 μ F) video cathode electrolytic becomes open circuited.

Distorted Sound

This is usually due to R44 (1M) going high. This is the load resistor of the EB91 sound noise limiter. A faulty PL82 (V12) can

also cause distortion as can leakage through C42 (0.01 μ F).

Loud Hum and Distorted Picture

This is usually due to C58 (200 μ F) becoming open circuit and this of course necessitates replacement of the whole C58-C59 main can electrolytic.

Faults in the Power Supplies

The H.T. is supplied through two PY82 valves, the A.C. being applied to pin 9 of each via a 30 Ω wire-wound surge limiter resistor. Always ensure that both resistors are intact. If a meter is not available to check the A.C. at each anode, a neon

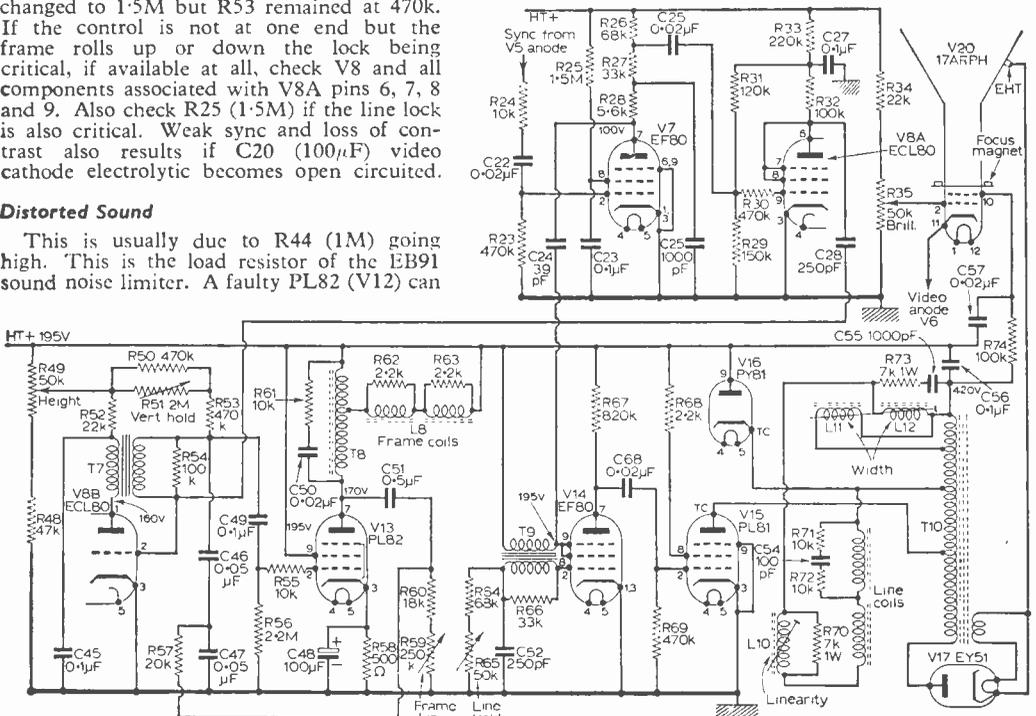


Fig. 4—Timebase circuits.

screwdriver applied to pin 9 of each valve-base will show whether the resistors are intact or not. A visual examination is not sufficient. If the symptoms are of no H.T. at all and neither anode shows the presence of mains voltage, check back to the mains dropper as one section may be open circuited. Although this would normally also put the valve heaters out, if the selector plugs 2 and 3 have been set incorrectly, for example 2 to E, 3 to K, the 9Ω section could fail without affecting the heater chain.

The Heater Chain

This is worth study since a heater to cathode short often develops leaving some valves passing excess current and thus glowing brightly and others without current and therefore unlit. For example, assume that V2 (EF80) develops a heater to cathode short. The circuit as far as heater current is concerned then becomes shorted to chassis before V3, 4, 5, 6, 20 (the tube) and 11. These heaters remain unlit and the others glow more brightly than normal as the circuit contains less resistance and the current is correspondingly higher. The increased current in this case is not generally sufficient to cause other damage but if the failure is further up the heater chain some damage is likely to result. As another example, suppose V7 is defective, all the heater current flows through valves V19, 18, 15, 12, 13, 14, 8 and possibly 7. This could well cause another valve say V13 (PL82) to also become shorted resulting in the whole current passing through valves V19, 18, 15 and 12. At this point several things could happen, one of the PY82 would probably fail and

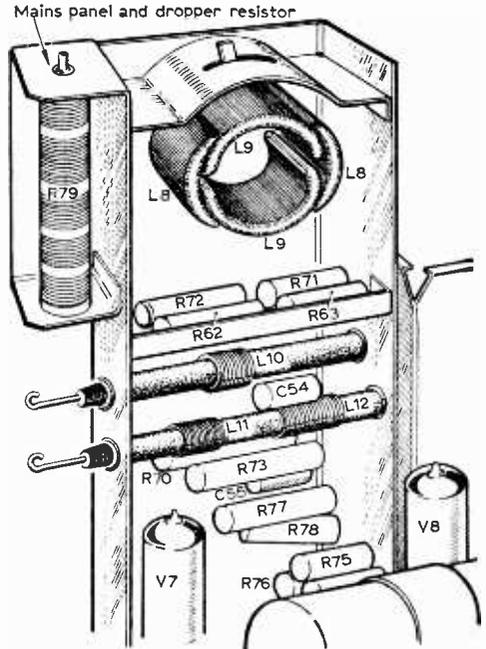


Fig. 5 (above)—A front view of the CRT support, showing the positions of the components beneath the scan coils.

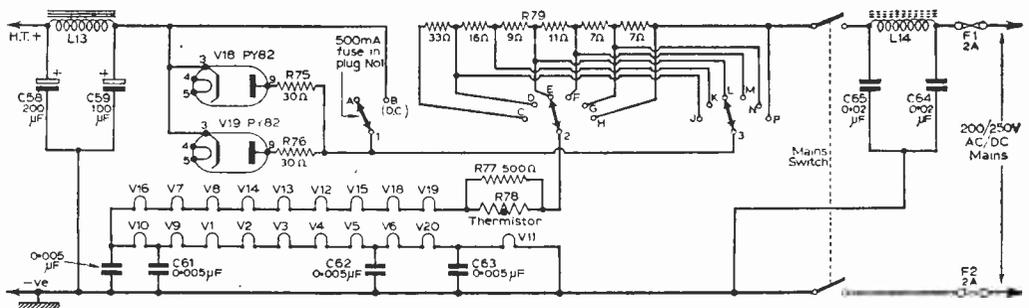


Fig. 6—The mains input and power supplies circuits.

thus blow a fuse leaving the repairer rather a headache in tracing the original cause. Alternatively one of the remaining heaters could become open circuit before the fuse breaks the circuit leaving the repairer with an open heater to trace and two valves with heater to cathode shorts. In some parts of the circuit a heater to cathode failure may not give anything like these symptoms. For example, suppose the detector section of V5 (EB91) develops such a fault, the symptoms are then of bright hum bars (horizontal) on the picture. The centre band may be black with white top and bottom or the bright band may be across the centre leaving part of the top and bottom black. These conditions are reversed when the mains leads are reversed which provides a ready means of identifying this fault from oscillation in the

vision I.F. stages which will normally give rise to an overall bright raster but can result in the hum bars described.

I.F. Oscillation

This often results when a 0.005μF decoupling capacitor becomes open circuited. A test capacitor of similar value shunted across each suspect in turn will usually enable the faulty stage to be located. The test capacitor must have fairly short leads however to avoid setting up oscillation (positive feedback) on this account alone.

Shorted Capacitors

It often happens that one of these 0.005μF decoupling capacitors becomes shorted. In this
(Continued on page 88)

IMPEDANCE BRIDGE for Transistor Measurements

(Continued from page 27 of the October issue)

By N. Mears

THE main wiring is carried out on a small chassis mounted at right angles to the front panel, and arranged so that the R.F. input leads are kept very short. This arrangement also ensures that the leads to the transistor under test are as short as feasible. Below the main chassis is a screen which serves to shield the input and balancing components from the anode coils; leads are taken through this screen as necessary by the most direct route. Thus the screens divide the assembly into three; the top compartment contains the valve envelopes and the balancing circuits, the small middle compartment contains the valve wiring and the input circuits, while the third contains the anode coils and frequency selector switch together with the valve screen balancing potentiometer and the terminals carrying the power supplies.


It is essential that the potentiometers which together make up R1 are of the carbon track type. During the period of development of this instrument it was desired to use a 500 Ω potentiometer for one of these, and the most extraordinary results were obtained. Eventually the case was taken off the potentiometer to see what the arrangement was inside; it was a wire-wound type, possessing very considerable inductance. Replacement of this component by a 1,000 Ω carbon track type removed the cause of the trouble and a very puzzling fault was cleared.

These potentiometers should also be of the smallest physical size that can conveniently be obtained; they have to carry only a minute current and power dissipation is not a problem. Inductance and self-capacitance are serious problems however. Only one at most may have an earthed spindle or slider, and if one has either of these peculiarities it should be placed on the "earth" side—electrically it does not matter which is connected to the chassis, but one must be insulated at least. Neither must be connected to the front panel; earthing is accomplished by means of the "outer" of a piece of coaxial cable equal in length to the coaxial lead to the transistor under test, while the "hot" end of both potentiometers and capacitor C1 is connected to the grid of the corresponding valve by means of the "inner" of the same piece of coaxial lead. In this way compensation for the length of leads to the transistor is effected. Similarly, the capacitor C1 is not earthed to the front panel but by means of the coaxial outer which also earths the potentiometer R1.

Good insulation from the front panel and small stray capacitance to earth are achieved by substantial discs of Perspex or Paxolin.

Frequency Selector Switch

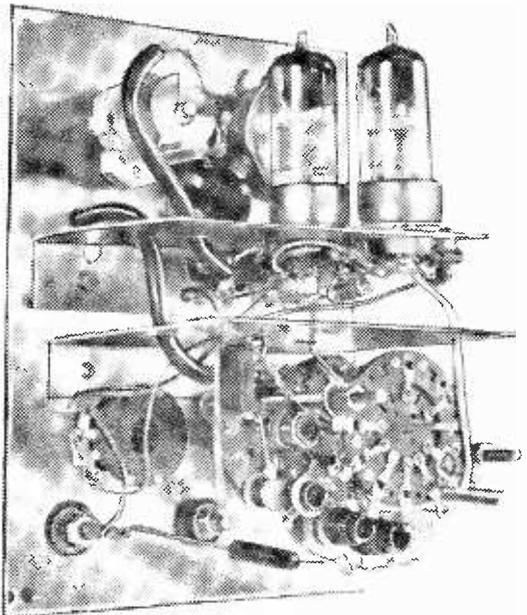For the frequency selector switch two Yaxley type wafers are employed, each of configuration two-pole six-way; one of the sets will remain unused. These are arranged on the selector spindle



A view of the interior of the instrument.

by means of appropriate spacers to be about 1 in. to 1½ in. apart. When wound the anode coils are wired direct between corresponding contacts on the two wafers. The third set of contacts is used to switch the R.F. output cable to the corresponding pick-up coil.

Power Supplies

The instrument has not been provided with its own power supplies, because a suitable bench pack

is available for use with such ancillary equipment as is not in continual use. However, there is no reason why the constructor should not incorporate a self-contained power pack if desired; it need only supply 0.6A at 6.3V and about 20mA at 180V H.T.

Auxiliary Equipment needed

An external signal generator is needed to supply the R.F. input, and if about 10mV is available the indicator can easily be a valve voltmeter or a crystal diode and microammeter. This combination has the big advantage of not needing an external R.F. receiver tunable to the frequencies used. If it were desired to use the design to measure ohms and fractions of a pF the added complication would be difficult to avoid, but for the purpose intended the bridge is sensitive enough to give good accuracy with the simpler equipment.

Alignment and Calibration

Before inserting into the circuit, both the variable capacitor and the potentiometers should preferably be calibrated against known standards. If this is not practicable the makers' stated figures may be accepted to a first approximation and assuming that a "straight line law" applies—the scales can be divided accordingly.

To set up for use the following simple procedure should be adopted. First, it is required to ensure that both halves of the anode circuit are tuned to the same frequency. To do this, the balancing potentiometers are returned to the position of least resistance and the test leads are left open-circuited. The selector switch is put in the desired position and the R.F. input leads are connected to the signal generator. The output leads are connected to the indicator and power is switched on. After an appropriate warming up period of about ten minutes the signal generator is swung slightly about the nominal frequency until an indication is recorded on the output meter. The signal generator is then tuned as nearly as possible to the peak. A dust core or brass slug is next inserted into one end of the anode coil and screwed in a little, while the signal generator setting is varied a little one side or the other. If the output reading increases the slug is screwed in a little more and the signal generator setting varied, until a position of the slug and the generator can be found which gives the maximum output. If on insertion of the core the reading first decreases the core has to be screwed right through the coil until it engages with the opposite winding; again a position is found which

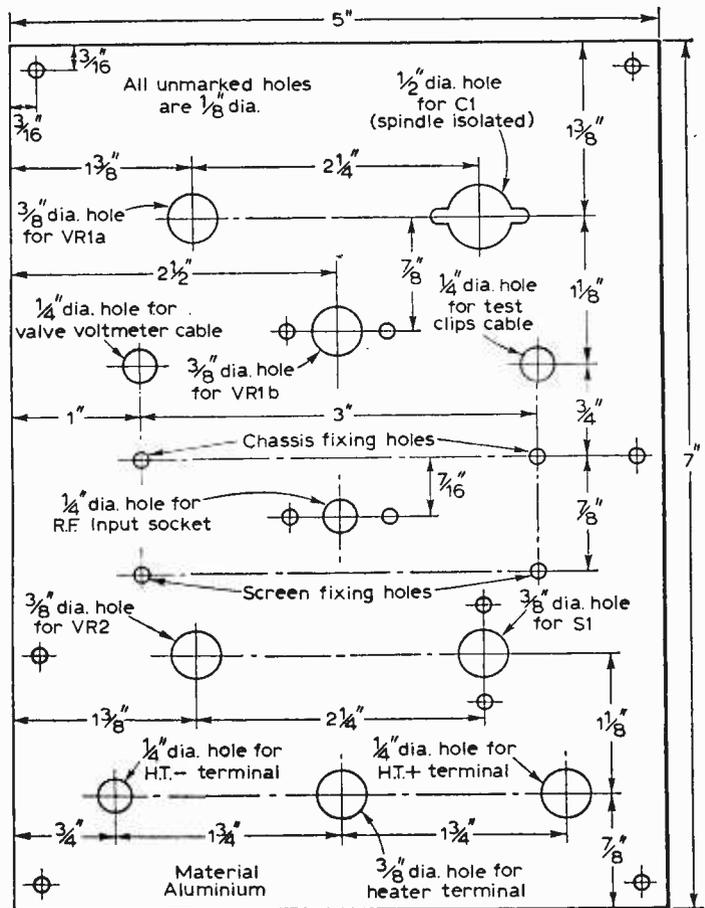


Fig. 5—The front panel drilling diagram.

gives the maximum output reading. This process is now repeated for each selector switch setting in turn. It may well happen that the tuning point is awkwardly sharp, and if this is found the Q of the tuned circuits should be reduced by connecting a resistor of between 5 and 10k direct between the anode contacts on the wafers. This is unlikely to be found necessary if dust cores are used, but if silver-plated brass slugs are employed it may be useful.

Next, the amplification of the pentodes must be equalised. For this purpose the input terminals are left open-circuited and the coaxial leads to the balancing network RIC1 are temporarily unsoldered. Setting the selector to any desired range a R.F. signal is injected and the potentiometer in the screen lead to V1 is rotated until the output reading is zero or very nearly so. It may happen that to obtain a reasonable zero the pentodes have to be changed over, as mentioned earlier.

The balancing network is now soldered into circuiting the test leads, zeroing the balance potentiometers and the capacitor C1, and then

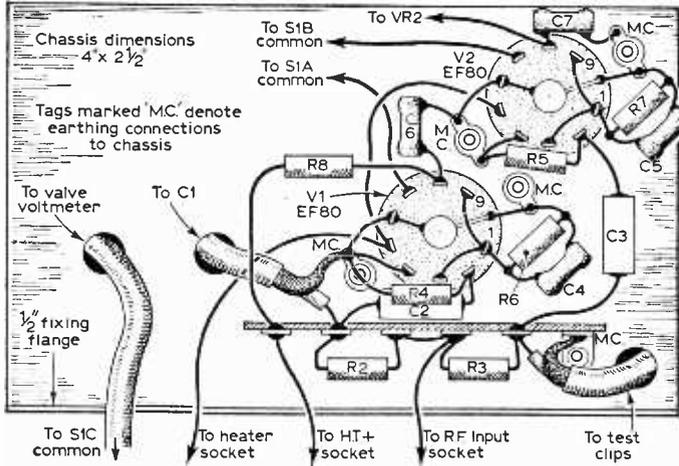


Fig. 6—The valve base wiring diagram.

Taking Readings and Recording Results

To take readings the method is to zero R1 and C1, leaving the test leads open-circuited. Tune the signal generator to obtain maximum output. Connect the test leads to the device whose impedance is to be measured, and rotate R1 and C1 together until zero or as nearly zero as possible is recorded on the output meter. The resistance and capacitance are then read direct from the calibrated scales.

The result may be recorded immediately as so many ohms in parallel with so many pF, and in this form it is suitable for many purpose. If, however, it is desired to introduce the figures obtained into certain calculations, it may be preferable to convert the readings into admittance, when the relationship

$$Y = G + jB$$

holds where $G = Y \cos \theta = R / (R^2 + X^2)$ and is the conductance while $B = Y \sin \theta = X / (R^2 + X^2)$ and is the susceptance; both are given in ohms. θ is of course the phase angle and X is the reactance of the capacitive component.

(Continued on page 84)

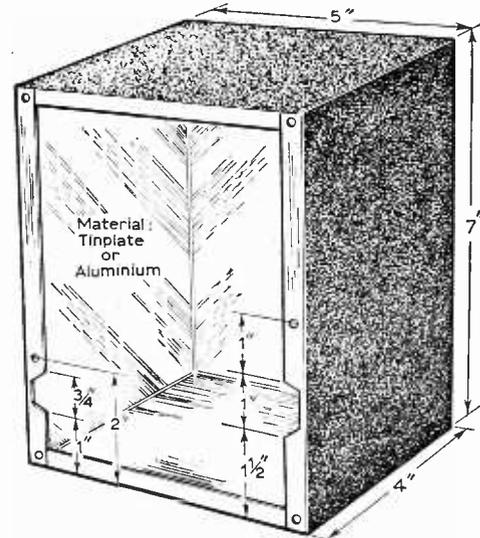


Fig. 7—The construction of the cabinet.

attention must be directed to locating the cause of the trouble. If the former, the balance potentiometers should be removed, the cases opened and a small strip of copper foil soldered to one of the end lugs so that the slider makes good contact with it at the end of its travel. Carbon track potentiometers are especially prone to this absence of a true zero, but the modification needed to correct it is simple to apply.

COMPONENTS LIST

Resistors:

- | | |
|---------------------------------|-----------------------|
| R1 (See VR1a/b) | R7 150Ω |
| R2 1.2kΩ | R8 2.2kΩ |
| R3 1.2kΩ | R9 2.2kΩ |
| R4 1.5MΩ | VR1a 1kΩ carbon pot. |
| R5 1.5MΩ | VR1b 25kΩ carbon pot. |
| R6 150Ω | VR2 10kΩ carbon pot. |
| (all resistors 1/4 watt carbon) | |

Capacitors:

- | | |
|--|-------------------|
| C1 100pF miniature air-spaced variable | |
| C2 500pF suflex | C3 500pF suflex |
| C4 1500pF ceramic | C5 1500pF ceramic |
| C6 1500pF ceramic | C7 1500pF ceramic |
| C8 1500pF ceramic | |

Switches:

- S1 two-wafer type, each wafer 2-pole, 6-way

Valves:

- V1, V2 EF80

Miscellaneous:

- R.F. socket. Terminals. Crocodile clips. Two B9A skirted valveholders. Knobs. Materials for panel and box.

New 10th Edition
Newnes Great
Profit Maker!

COMPLETE IN
 6 VOLUMES



Radio & TV Servicing

MODELS FROM 1962 BACK TO 1956

This NEW EDITION provides all the technical information you need for quicker repair work now and for years ahead! It gives you full servicing data and specialist repair hints for the popular models marketed by 70 principal makers during the past seven years. It is essential to the shrewd repair man because people are keeping their sets longer. If you have never before examined this famous reference work now is your opportunity. See the new edition for a week on free examination without obligation to buy.


TELEVISION · RADIO · RADIOGRAMS · CAR RADIOS
 TAPE RECORDERS · RECORD REPRODUCERS

DATA FOR ALL THESE MAKES—Alba, Ambassador, Argosy, Armstrong, Baird, Beethoven, Berec, Brayhead, B.R.C., B.S.R., Bush, Capitol, Champion, Channel, Collaro, Cossor, Cyldon, Dansette, Decca, Defiant, Dynatron, E.A.R., Eddystone, Ekco, Elizabethan, Emerson, E.M.I., Emisonic, English Electric, Ever Ready, Ferguson, Ferranti, Fidelity, Ford Motor Co., Garrard, G.E.C., Gramdeck, Grundig, H.M.V., Invicta, K-B, McCarthy, McMichael, Marconiphone, Masteradio, Motorola Murphy, Pageant, Pam, Perdio, Peto Scott, Philco, Philips, Pilot, Portadyne, Portogram, Pye, Radiomobile, Raymond, Regentone, R.G.D., Roberts' Radio, Sobell, Sony, Sound, Spencer-West, Stella, Stereosound, Strad, Ultra, Vidor, Walter, Webcor. Includes special 50-page supplementary section of older models.

PLUS 2 YEARS' FREE POSTAL ADVISORY SERVICE

More than 4,000 Circuits and Component
Layout Diagrams · 2,250 Popular Models

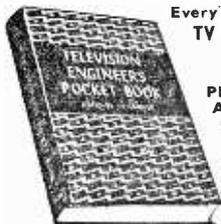Use it **FREE** for 7 days
 to prove its value



Every purchaser receives a Free copy of
TV ENGINEERS POCKET BOOK
 (Value 12/6)

272 PAGES : OVER 200
PRACTICAL ILLUSTRATIONS
 An invaluable companion to
 your set for on-the-spot repairs
 Concise information on installing,
 fault-tracing and repairing, serv-
 icing equipment and align-
 ment, etc.

Hurry - Post Coupon To-day

George Newnes Ltd., 15-17 Long Acre, London, W.C.2.
 Send me Newnes RADIO AND TELEVISION SERVICING (in 6 Volumes) and TV ENGINEERS POCKET BOOK without obligation to purchase. I will return them in 8 days or send 15/- deposit 8 days after delivery, then twenty monthly subscriptions of 15/-, paying £15. 15s. in all. Cash price in 8 days is £15.

Name and Address in block letters please

Mr., Mrs., Miss _____

Address _____

Occupation _____

Signature _____

(Parent signs if you are under 21).

Coupon is invalid if not signed and questions answered.

Tick ✓ where applicable

The address on left is—

My Property	<input type="checkbox"/>
Rented unfurnished	<input type="checkbox"/>
Parents' Home	<input type="checkbox"/>
Furnished Accom.	<input type="checkbox"/>
Temporary Address	<input type="checkbox"/>

(RV)533/31

D. & B. TELEVISION (Wimbledon) LIMITED

131 & 131A Kingston Rd, South Wimbledon, London, S.W.19
"Compare our prices with any others"

Phone:
CHE 3955

Dept. B.7

For more Transistors and Components see our advertisement in "Practical Wireless"
For the FINEST, FASTEST SERVICE in the COUNTRY. We are open from 10 a.m. Until 7 p.m. — 1 p.m. Wednesday For any information or problems you have. Call or Phone, we are always pleased to help.

We pride ourselves that we can obtain and supply any TV spare, OUR GIGANTIC STOCKS INCLUDE: Line, Frame and Sound Output, Line and Frame Blocking Cts., Trans., and Scan Coils for any make or model Television.

LINE OUTPUT TRANSFORMERS (P. & P. 316)

ACE, ASTRA 57/3. ALBA, T301, T304, T394, T494, T494, TR1974, 42/6.
AMBASSADOR, Most Models Available 57/9 ARGOSY, CTV3, 66/9.
ARMSTRONG, T.V. 8/14, T.V. 5/17, 57/9. BAIRD, 2014 to 2217, 57/9.
BANNER, Most Models Available. BETHOVEN, B94 to B99, 57/9.
BUSH, TU226, TV32, TV33, TV33 to TV43, 87/-. CHAMPION REWIND ONLY.
COLUMBIA, C5011 to C592, 69/-. COSBOR, R173, 930, 931, 933, to 944, 946, 50/6.
DECCA, DM1, DM2C, DM3, DM4C, DM5, 72/6. Also Used.
DEFIANT, Some Available. Some Rewind Only.
DYNATRON, Available, but Sample L.O.P.T. Required.
EKCO, TC208, TU209, T291, T248, T267, T294, T293, 57/6. Most Models Available.
ENGLISH ELECTRIC, Rewind Only. EMERSON, 701, 700, 704, 57/9.
FERGUSON, 103T, 105T, 113T, 145T, 64/6. 203T, 246T, Inclusive, 64/6, 99/2 to 99/6, Inclusive 64/6, 308T, 308T, 62/-.
FERRANTI, 14T3, 17K3, 17T3, 45/-. Most Models Available.
FULLOTONF, 12in., 14in., 57/9.
G.E.C., RT1251, BT1252, BT1746, BT1748, 40/-. Most Models Available.
H.M.V. 1824 to 1831, Inclusive, 64/-. 3831 to 5902P, Inclusive, 94/3.
HISPA, T1197A, T1197B, 44/-. T118, T119, T120, 26/6.
K.B., LPT50, LVT50, LFT60, MVT60, 105/-. Most Models Available.
MARCONI, VTS8DA, VTS9DA, VC60, VT61DA, 57/9.
MASTERADIO, TE7C, TE7T, TF7, TG7C, TG7T, TE21C, 57/9.
MICHAEL, TM64F, C417PMF, TM417F, 57/9.
MURPHY, V214, V240, V260, V270, V280, 68/6. All Murphy Spares Available.
PAM, 908, 909, 952, 953, 958, 52/6.
PETO SCOTT, TV91, TV92, TV121, TV122, 48/3. PHILCO, 1707, 1708, 48/2.
PHILIPS, 1114UF, 1115U, 1446U, 72/6. Most Models Available, Also Used.
PILOT, All Models can be Rewound.
PORTADAYE, TC12, 69/-. All other Models Rewind Only.
PYE, V4, V4, V7, VT7, 52/6. Most Models Available, Also Used, at 32/6.
REGENTONE, 12B1G, 12T13, 69/-.
R.G.D., C53, 1453, 1456, 1753, 1757, 80/-.
SOBELL, T21, T21C, T22, 74/-. Most Models Available.
STELLA, SBT21U, ST5617C, 96/-. Most Models Available.
ULTRA, Most Models Available. VIDOR, Most Models Available.
WESTMINSTER, T1455, 69/-. WHITE IBBOTSON, Most Models Available.

TV TUBES

ALL TUBES ARE REGUNNED WITH FULL 12 MONTHS GUARANTEE
12in. MULLARD TYPE.....£3.15.0 13in. MAZDA TYPE.....£3.15.0
14in. MULLARD TYPE.....£4. 5.0 14in. MAZDA TYPE.....£4. 5.0
16in. MAZDA TYPE.....£4. 5.0 16in. G.E.C. TYPE.....£4.15.0
16in. MULLARD TYPE.....£4.3.0 17in. MULLARD TYPE.....£4.15.0
17in. MAZDA TYPE.....£4.15.0 17in. G.E.C. TYPE.....£4.15.0
17in. BRIMAR TYPE.....£4.15.0.

90° AND 110° TUBES ON EXCHANGE BASIS ONLY
ADD 5/- FOR ELECTROSTATIC TUBES. ADD 10/- FOR 80° AND 110° TUBES.
CARR. AND INS. 12/6. C.W.O. OR C.O.D.

ALL VALVES ARE SOLD SUBJECT TO FULL GUARANTEE—CURRENT

VALVE LIST

AZ31	8/8	ECPF80	8/8	IKT61	8/8	U24	10/-	U08	14/6	10C1	10/-
B36	6/6	ECH21	15/-	KT63	8/3	U25	12/-	U09	6/3	10C2	13/-
D77	3/-	ECH35	9/-	KTW61	5/9	U26	9/6	U41	6/-	10P13	8/9
1FAF91	5/-	ECH42	7/6	KTW63	5/9	U31	7/-	Y85	6/6	10P14	8/9
DAF96	7/-	ECH81	7/6	PC84	7/6	U37	5/6	W77	4/-	12AT6	7/3
DF91	3/9	ECL80	7/3	PC89	8/9	U50	5/6	Z77	3/-	12AT7	4/6
DF96	7/3	ECL82	9/9	PCF90	7/6	U52	5/-	SU4	4/9	12AU7	5/6
DH63	6/-	ECL83	11/9	PCF82	7/9	U91	9/6	SV4	8/9	12AX7	6/3
DH77	4/6	EP80	4/6	PCP65	9/9	U281	9/-	SY3	6/3	20D1	8/6
DK91	6/-	EP85	6/3	PCL82	7/9	U282	14/6	SZ4	10/-	20F2	8/3
DK92	7/6	EP86	8/9	PCL83	8/9	U301	17/6	SA15	3/-	20L1	12/6
DK96	7/3	EP89	6/6	PCL84	7/6	U801	32/-	RAM6	3/-	20P1	9/6
DL91	8/3	EP91	3/-	PCL85	15/-	UABC80	8/6	6AT6	5/6	20P3	12/-
DL92	6/3	EP92	4/-	PL33	3/-	UAF42	8/-	6BW6	7/6	20P4	18/6
DL94	7/-	EL33	7/6	PL36	9/9	UB41	7/9	8D2	3/-	20F5	14/6
DL95	7/-	EL38	12/-	PL39	14/6	UB41	7/9	6P1	4/6	278U	14/6
EABC80	7/3	EL41	7/9	PL81	9/9	UBF89	7/9	6E12	3/-	30C1	7/6
EAF42	7/9	EL44	6/9	PL82	6/6	UCC84	12/6	6F13	6/6	30FL1	9/3
EB41	6/6	EM80	8/6	PL83	6/6	UCC85	7/9	6F14	9/-	30L1	7/6
EB51	3/-	EM84	9/6	PL84	8/9	UCF80	14/6	6F15	9/-	30P4	11/3
EB33	4/6	EY31	7/9	PY31	7/9	UC12	12/6	6F33	6/3	30P12	9/6
EB41	7/6	EY85	7/6	PY32	12/-	UL41	7/-	6L1	12/-	52KU	10/-
EBF80	7/6	EZ40	6/3	PY80	6/-	UCH81	8/3	6L6	9/9	53KU	10/-
EBF89	8/3	EZ41	6/9	PY81	6/-	UCL83	12/6	6L18	8/-	54KU	8/6
ECV81	4/6	EZ80	6/9	PY82	6/-	UF42	2/6	6L19	12/-	185BT	14/6
EC82	5/6	EZ82	8/9	PY83	8/-	UL41	7/-	6S8T	4/6		
EC83	6/3	GZ34	12/6	PY88	12/-	UL44	10/9	6V6	5/-		
EC84	7/9	KT33C	6/-	PZ30	8/-	UL46	7/-	6U4	10/-		
EC85	7/6	KT35	8/6	L22	6/9	UL84	7/3	6E1	4/6		

These are only examples of our valves: if you do not see what you require send stamped addressed envelope for special quotation.

Please ask us for ANY components you may require we are almost certain to have them. TERMS: S.A.E. all enquiries. C.W.O. or C.O.D. 3/- extra. Postage on Valves, 6d. each. C.R.T.'s 12/6 inc. insurance. SATISFACTION ASSURED.

RETURN POST SERVICE.



"SABRINA" STILL WELL IN FRONT

Bring your TV set up 100% again by fitting our:

COMPLETELY REBUILT C.R. TUBES
ALL TYPES (including electrostatics)

12" now £5. 0.0 } For
14" to 17" now £5.10.0 } Single
21" now £8. 0.0 } Tubes

ALL C.W.O.—TRADE SUPPLIED

Special Bonus Scheme for Service
Engineers—Reducing to:

12"—87/6; 14"/17"—97/6; 21"—147/6

FREE Pass, transit & Ins. anywhere in British
Isles or N. Ireland (12 months' guarantee).

SABRINA C.R. TUBE CO.
Electron Works, North Bar
BANBURY, OXON
Telephone 2390

"THREE STAR"

RE-BUILT TELEVISION TUBES

- ★ Manufacturer's Own Make of Gun
- ★ Re-screened for Greater Contrast
- ★ Aluminised for Better Brightness

TWO WAY TESTED

Free carriage and insurance.

ALL TYPES AND SIZES

12" - £4.10 14" - £4.15

15" - £5. 0 17" - £5.10

21" - £7. 0

C.O.D. or Cash with order.

DARLING ELECTRONICS

Dept. TV, 62 High Street, Croydon, Surrey

MAIL ORDERS ONLY—NO CALLERS

SERVICING DATA AND MODIFICATIONS

By D. Elliot

(Continued from page 43 of the October issue)

THESSE models are sometimes prone to spurious oscillation in the PL36 line output valve. The effect on the picture is a broken vertical line between one-third and half way in from the left-hand side of the picture, and sometimes more apparent when the set is operating on the Band III channels.

Certain PL36 valves appear to cause the trouble more than others, and in the majority of cases the fault can be eliminated by replacing the valve. However, this is not always a permanent cure, for after the replacement has been in service for a while the symptom is likely to occur again. This can prove expensive if the valve is replaced each time, for usually it is otherwise electrically sound.

Other methods have been adopted to clear the effect, and one which is often successful if the valve was free from the trouble to start with is the fitting of two ferrite beads on the PL36 anode lead, immediately adjacent to the top cap connector. These increase the inductance of the lead and shift the resonant frequency away from the passband of the receiver. Such beads are known as Ferroxcube FX1115. A range of beads suitable for this purpose is also marketed by Radiospares Limited (and are obtainable through a dealer), and cost about 3s. for a packet of one dozen.

If the inductance increase by the use of ferrite beads is insufficient and the trouble remains, a small wire-ended television suppression choke (1A type) can be connected in series with the anode lead. These are also marketed by Radiospares and retail about 1s. each.

In obstinate cases of the fault, it may also be necessary to include beads on the cathode lead of the efficiency diode valve or, if necessary, a second television-type choke.

Dust on Picture Tube Screens

Although this has been a big problem in the past, it will give considerably less trouble in the future since a new range of picture tubes is being produced on which the implosion guard is intimately bonded to the face of the screen. Sets featuring this type of tube, therefore, do not incorporate a separate glass screen or guard in front of the tube face.

The cabinet is so designed that the front of the bonded tube lies flush with the front of the cabinet, it thus being necessary simply to wipe the face of the tube with a damp cloth to clear dust and dirt.

The loss of light through this type of tube is also far less than with the old method, and reflections are less troublesome since there are less reflecting surfaces.

However, there are still millions of sets in use with the original set-up, and the precipitation of dust on the screen and on the inside of the protective glass window results in loss of light and contrast, and the need for periodic cleaning.

Several methods have been devised to minimise the need for cleaning by reducing the intrusion of dust. Some models incorporate a soft rubber loop which fits snugly between the crack round the edge of the tube face and the mask. Others use a rubber mask which has a wide flange firmly clamped over the bulb of the tube with the implosion guard let into the rubber moulding.

Many models, though, have no dust-excluding arrangements at all, and it is often an extremely difficult exercise to remove the tube for cleaning. With that in mind some manufacturers designed their cabinets so that the screen and implosion guard could easily be removed from the front of

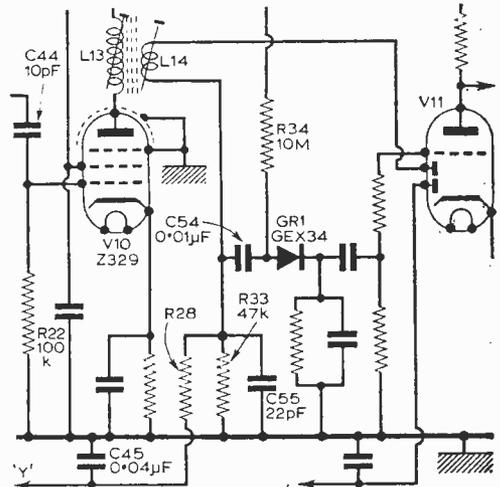


Fig. 38—The G.E.C. circuit without AGC applied to the sound I.F. valve.

the cabinet without having to interfere with the chassis or tube; but, unfortunately, this idea was by no means universally adopted.

Readers often request details for cleaning the tube face and screen so as to reduce dust precipitation in the future, and thereby avoiding frequent cleaning. This can be done by eliminating the electrostatic charge on the tube face, for it is that charge which attracts the dust particles to the screen. Repulsion of the charged particles from the screen causes the characteristic "bloom" on the inside surface of the window.

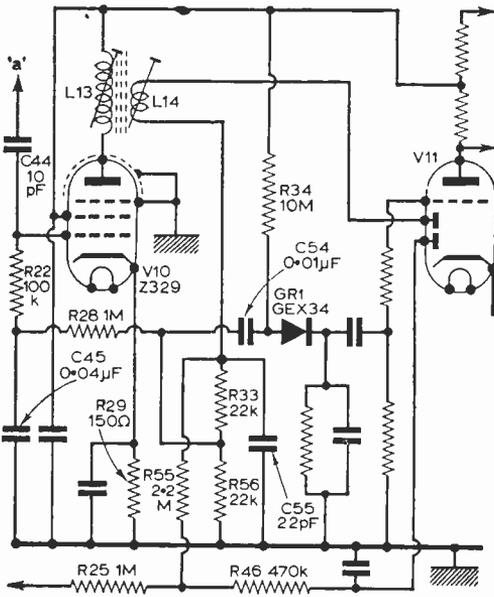


Fig. 39—How the arrangement shown in Fig. 38 can be altered for sound I.F. AGC.

The charge can be effectively decreased by maintaining the tube face at chassis potential by the use of a semi-conducting coating applied to the face. Such a coating has been evolved by the Imperial Chemical Industries Limited, Plastics Division, Welwyn, and is known as "Perspex Polish No. 3". It can also be obtained from an I.C.I. agent or from certain dealers.

A little of the paste should be spread evenly over the whole face of the picture tube, and then lightly polished off with a soft, lint-free cloth. The paste should also be applied round the edges of the screen to touch the parts already treated and to form a band about 2in. wide. This coating should not be polished.

To achieve electrical connection from the paste to the chassis of the set, a thin piece of metal foil should be clamped between the tube support so that it makes contact with the coating on the edge of the tube. The other end of the foil should be clamped to chassis. On some models the metal tube cradle will automatically "earth" the paste coating.

GEC Models BT1746 and BT1252 Series

These models feature a tuner in which the fine tuning cam often breaks away from the plastic shaft. The tuners concerned switch over three programmes (channels) and are sometimes used as converters, going under Models BT201 and

BT206. As it is now often difficult to obtain replacement cams, a few notes on how a broken cam can be repaired may be useful.

The best adhesive to use is the Araldite epoxy resin, which is generally available from retail sources in a small pack containing adhesive hardener. Other adhesives may not give sufficient strength over long periods of time.

The two surfaces should be thoroughly cleaned and a thin, even coating of the previously mixed adhesive and hardener applied. The two parts should then be pressed firmly together. If the hardening action is accelerated by heat, as described in the instructions, the repaired cam is ready for fitting after about thirty minutes.

Care should be taken when refitting to ensure that the metal pressure plate does not bear too heavily on the cam. If necessary, the pressure should be reduced by bending the plate a little.

GEC BT1155, BT2253 and BT3252 Series

On some early versions of the above series excessive sound signal may cause overloading and resulting distortion in the first A.F. amplifier V11 (Figs. 1 and 2). This is essentially because AGC is not applied to the sound I.F. amplifier valve, only to the R.F. amplifier and common I.F. stages.

AGC can be applied to the sound I.F. valve quite easily, however, on Models BT2253 and BT3252 by changing the existing circuit (Fig. 1) to that shown at Fig. 2. This simply involves disconnecting C45 from the 2.2M AGC resistor and reconnecting between R22 and chassis. Replacing the diode load resistor R33 by two series-connected 22k resistors (1/4W type).

Transferring C54 to the junction of the two 22k resistors, and adding a 1M 1/4W resistor from the junction of the two 22k resistors to the junction of R22 and C45. Note that later models already incorporate this modification.

On Model BT1155, remove the connection between R28 and the junction of R24 and R25.

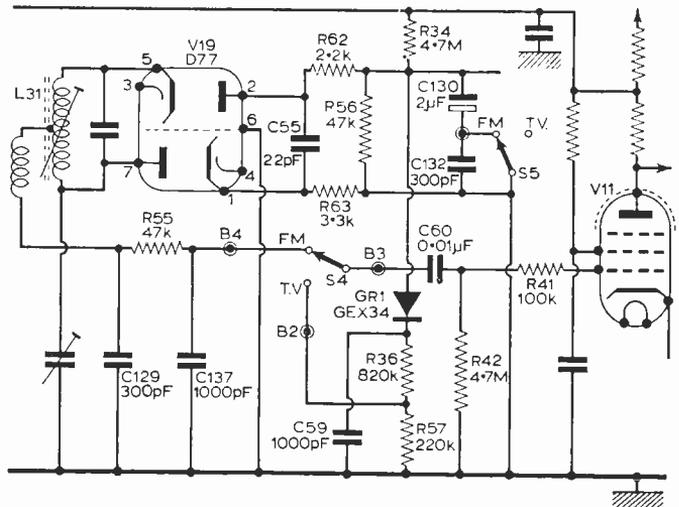


Fig. 40—The modification used in the G.E.C. range of receivers (see text) to improve sound interference suppression.

Add an $0.04\mu\text{F}$ 150V working capacitor between R22 and chassis, and connect R28 to the junction of this capacitor and R22, as shown in Fig. 1.

Improved Noise Suppression on Models BT2748 and BT8742 (GEC)

These sets have facilities for the reception of the F.M. signals on Band II, and a circuit change to provide more efficient sound noise suppression is given in Fig. 3. Later models incorporate this modification and can be identified by the suffix letter "A" after the model number.

The modification involves the following: Transfer C54 from switch B8 to the junction of R62

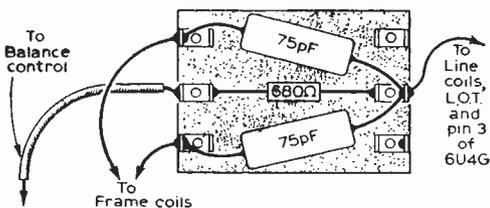


Fig. 41—A 680Ω resistor connected to the "balance control" circuits of Pilot 84 and 87 series receivers helps to eliminate corona effect on the picture.

and C130 in the discriminator circuit. Transfer C60 from the junction of R36 and the GEX34 diode to switch B8. Remove the connection between switch B2 and the junction of R56 and R57 (note that these two resistors may be replaced by a single $47k \frac{1}{2}\text{W}$ component.) Replace R36 by two series-connected $\frac{1}{2}\text{W}$ resistors— $820k$ to the GEX34 and a $220k$ to chassis.

Connect the junction of these two resistors to switch B2. Add $1,000\text{pF}$ capacitor between switch B4 and chassis. Reduce the value of R34 from $10M$ to $4.7M$ ($\frac{1}{2}\text{W}$).

GEC BT1155, BT2253, BT3252, BT2748 and BT8742 Series

It sometimes happens that when the N308 line output valve is changed in these models there is a change in line amplitude and/or in EHT voltage. If this is outside the range of normal correction, then a slight modification should be made to the line oscillator stage. This simply involves changing the value of the anode load resistor of the line oscillator valve. This valve is a Z329 and the anode load resistor is $470k$.

This resistor should be removed and two series-connected $270k$ resistors should be fitted in place. If the line amplitude and EHT voltage are low, the two resistors should be linked in parallel, but if high, then the two resistors should be retained in series.

On some early models the frame hold control was affected by bursts of impulsive interference, resulting in a loss of synchronism. On Models BT1155, BT2253 and BT3252 this can be avoided as follows: Remove the green wire linking pin 2 (anode) of the D77 frame interlace filter valve (V7B) and pin 2 (triode grid) of the LN319 (V17), and insert a $47k \frac{1}{2}\text{W}$ resistor between the two points.

On Models BT2253 and BT3252, remove the $390k$ resistor from its position adjacent to the

vertical hold control and connect the vacated tag to chassis. Transfer the yellow lead on the hold control from pin 9 (pentode grid) of the LN319 (V17) to a spare tag on the adjacent tag panel, and reconnect the $390k$ resistor from that point to pin 9 of V17.

Pilot Models of the 84 and 87 Series

Instability on models featuring a 13-channel turret tuner is sometimes caused by misplacement of the lead from the centre of the coaxial socket into which the I.F. lead from the tuner is plugged. The centre pin of this socket is connected by a short lead to one of the pins of a plug-in type I.F. transformer (underneath the chassis). This lead should be carefully positioned as close as possible to the chassis until the instability is cured.

No other adjustments are usually required, other than replacing the position of the lead, providing that the receiver itself is in satisfactory condition.

Corona discharge effect

The formation of a corona discharge effect, taking the form of a vertical line of white spots about 2in. from the right-hand edge of the picture, may be caused by a high peak voltage appearing across the "balance control".

This can be remedied by connecting a 680Ω resistor ($\frac{1}{2}\text{W}$). The resistor should be fitted on the scanning coil panel, and should be wired in series with the lead to the balance control, using the spare tag for the junction of the resistor and the lead, as shown in Fig. 4.

(To be continued)

INTERESTED IN SCIENCE? LIKE PRACTICAL HOBBIES?


Then PRACTICAL MECHANICS AND SCIENCE is the magazine for you.

November issue, on sale November 1st, price 2/-, contains practical articles on making:—

A WATER-POWERED MICROSCOPE;
TRANSISTORISED STETHOSCOPE; HIGH-EFFICIENCY CONVECTOR HEATER;
PHOTOGRAPHIC DRY-MOUNTING PRESS;
ELECTRICAL CHILDREN'S TEACHING AID—
and other articles and regular features.

Together with scientific articles about:—
N.S. SAVANNAH, FIRST ATOMIC MERCHANT SHIP; SPACE-AGE METALS; THE MAGNUS EFFECT AND V.T.O. PLANES; INFLATABLE SPACE STATIONS; PICTURE NEWS FROM THE WORLD OF SCIENCE.

ORDER YOUR COPY NOW!

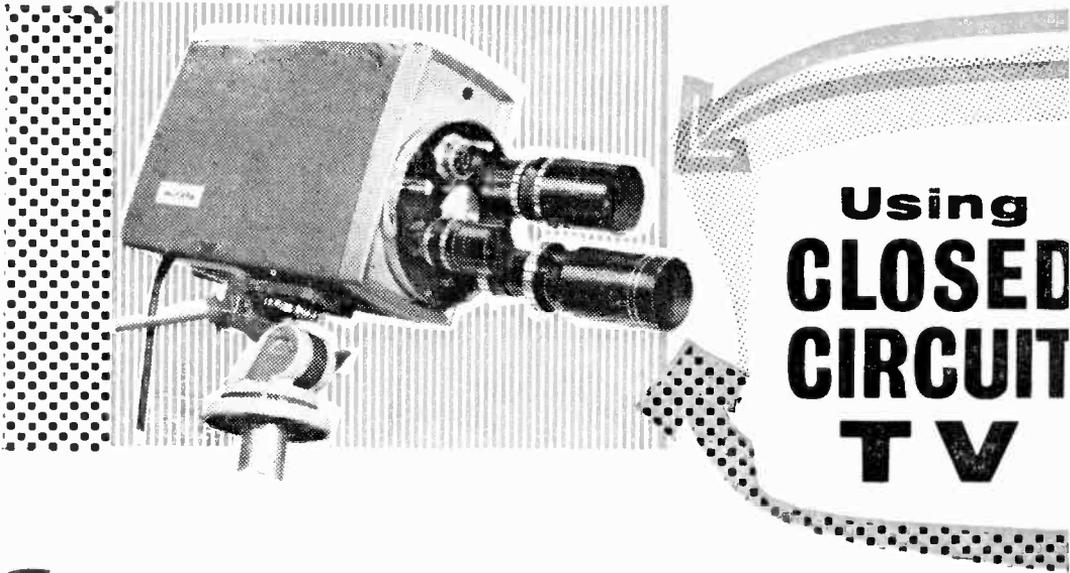

Using CLOSED CIRCUIT TV

THE recent introduction of low priced closed circuit television units makes it almost certain that such equipment will soon be available at reasonable fees to organisers of exhibitions, public meetings, entertainments, and so forth.

Some readers may, by virtue of their interest in television, be prevailed upon to operate the camera—usually at short notice. This has already happened to the writer, and the first part of this article deals mainly with the experiences of attempting to produce pictures and sound of entertainment quality from one of these units at a local exhibition.

A quick glance at Fig. 1 will show how little of the necessary equipment is usually provided as a CCTV unit, and details of the extra gear needed are given for the benefit of those who find themselves in a similar position, handling this fascinating new medium.

The Camera Unit

The camera that was hired was a Pyc Industrial Unit with a 1in. Vidicon tube. This has a single 1in. lens with variable aperture and focus, and gives a field of view comparable to that seen in the viewfinder of the average 8mm or 16mm cine camera.

It can be regarded from an operational viewpoint as typical of the majority of CCTV units. There are no controls on the camera head apart from optical focus and aperture (iris) on the lens. Ten feet of multiple cable separates the head from the suitcase-sized control unit, which houses the controls for "beam current", "target bias", and "electrical focus".

Unlike the newer low priced units, it includes a step counter chain which relates the line and frame scanning speeds to the supply mains and also gives correct sync waveforms permitting accurate interlace and a true BBC type signal. This facility will be discussed later, but is not essential for the production of acceptable pictures.

The outputs from the control unit are a video feed of 1V positive-going picture and 80Ω im-

pedance from which the grey metal-clad monitor receiver is supplied, and a modulated R.F. signal tunable to any Band I channel giving better than 10mV in 80Ω.

It is of course double sideband, and with the average 17in. receiver needs detuning from the nominal carrier frequency by a few hundred kilocycles towards the upper adjacent sound channel in order to approximate the overall response characteristics of a broadcast signal.

The unit just described is ideal for all industrial uses but is rather limited when televising entertainment in the manner now familiar to us. There is of course, no sound channel provided, and portability is limited by the proximity of the camera head to the control unit and the monitor receiver.

A Vidicon tube is a medium sensitivity tube, and to get good pictures indoors a fair amount of stage type lighting is desirable. The operator has no viewfinder and needs to be able to control the lens aperture and focus, point the camera, and use the beam current and target bias controls on the control unit from time to time. He must be able to see the monitor throughout. With only one camera and one lens there is no choice of angles of view.

To overcome most of these limitations the camera, its tripod, control unit and monitor were mounted on a rubber tyred dolly which was loaned by a local builder. A central control point, which mixed the sound, and gave talkback instructions to the camera crew was connected to the dolly by a 50yd home constructed multiple cable.


From the control point sound and vision were

ACKNOWLEDGEMENTS

Cover photograph by courtesy of the Bury Free Press.

Heading photographs show Murphy CCTV camera and Beulah D800 camera in use in a film studio.

CAMERA TECHNIQUES EXPLAINED

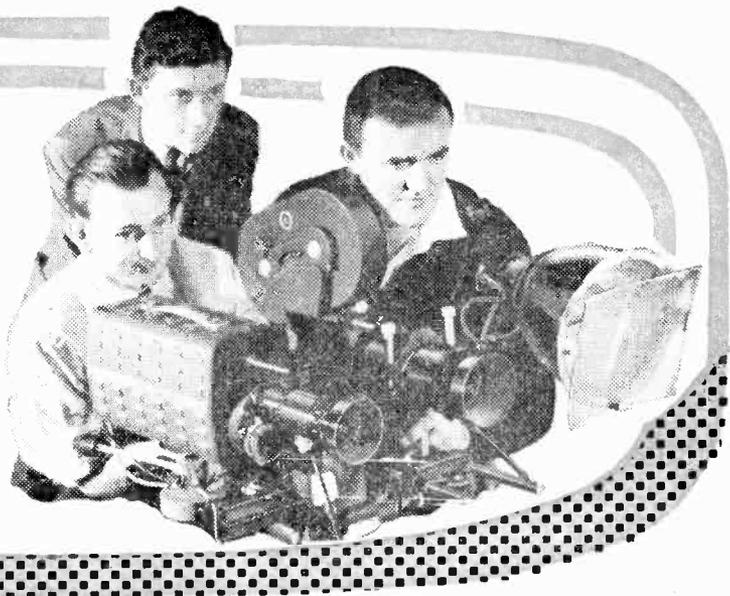

distributed to nine domestic television receivers in various parts of the exhibition hall, with a conventional P.A. amplification system used for the sound in preference to a modulated R.F. supply.

The block diagram of the entire system is given in Fig. 1 and a cross section of the 50yd of multiple cable between the dolly and control unit is given in Fig. 2.

The Camera Crew

A crew of three is needed. The engineer in charge sits at the control console (which in our case housed the sound equipment and a 14in. monitor TV) and directs the camera crew through headphones on a talkback system.

He listens to a combined microphone pick-up from the dolly and from other microphones mixed into the P.A. amplifier in one ear and to the output from the tape recorder in the other ear by splitting the headphone leads, and can thus pre-select music or speech independent of the outgoing sound.

He can, in fact, carry out a two-way conversation with the camera crew whilst music or recorded announcements are being fed into the network of nine receivers. In our case this facility was to be of utmost value as the exhibition organisers sealed off one of the two doors leading into a large side hall from which several programmes were scheduled.

The door that was closed was the large one capable of admitting the dolly, which therefore had to be dismantled of gear, squeezed through the small door and built up again inside. It is to the credit of the camera unit designers that the time taken from switching off prior to dismantling until the camera was back "on the air" again was less than 10 minutes.

During this time a still pattern, usually black level with sync pulses, was fed to the receivers from a pattern generator to stop the line timebase from "running wild".

by **H. PETERS**

The other two members of the crew stay with the dolly. One is the cameraman, whose duties have just been outlined, and the other is the dolly pusher, who also pays out cable, keeps the inquisitive at bay, acts as studio manager, caption peeler, tea boy, and microphone rest.

The Distribution Systems

Vision signals were distributed on channel 1 as the local Band I signal was on channel 3. Although up to a dozen standard receivers can be operated from the camera unit's R.F. outlet without additional amplification, nine is the ideal number as it simplifies the distribution networks as shown in Fig. 3.

The vision signal can be split by four networks each comprising four 39Ω $\frac{1}{4}W$ resistors connected in star and fitted into ordinary electrical junction boxes. This arrangement gives a 78Ω match throughout the system and about 2.5mV to each set (well above the "snow level").

The loudspeakers, each 5Ω approximately, are isolated from the live chassis of the associated receiver and connected in threes in series, resulting in three 15Ω legs, which in parallel matched the

**continued
over
page**

5Ω outlets of the P.A. amplifier and the tape recorder.

Provided a good recorder is used there is adequate output to give the required amount of sound. The one in use had an EL84 single ended output. If difficulty is experienced in isolating the loudspeaker safely from the chassis, as is possible in the more compact sets, a separate extension loud-speaker can be concealed within 3ft of the receiver without anybody spotting the deception.

A dummy load should be connected in place of the receiver speaker to avoid the possibility of extraneous noises being radiated. The cables used are standard coaxial for vision, and cheap plastic lighting flex for sound, and losses over 150yd are negligible.

Receivers

With the type of unit which gives a fully interlaced picture, it is possible to use a mixture of all types of receivers, provided that waveform generators in the camera control unit are correctly set up.

The size of the front and back porches (governed by the line sync blanking pulse) is critical, and so is the ratio of sync to vision. Should these be upset there is a tendency to experience AGC lockout on receivers with gated AGC systems, and an inability to obtain good contrast on receivers with mean level AGC.

In fact the only safe set for a maladjusted camera is one without AGC, and these are becoming very rare, but fortunately, anybody with television servicing experience, can usually set the unit up correctly by comparing the sync waveform at the video amplifier of a receiver with the same waveform on a BBC test card.

When using the lower priced cameras with free running line timebases, it is better to try and avoid using receivers with gated AGC and with flywheel sync. Fortunately most domestic receivers of the last year or two are of the non-flywheel mean-level AGC type.

Lighting

As has already been stated, the average room light is inadequate to produce good pictures with a reasonable depth of focus. Pictures of sorts can be obtained of very dark scenes, but they tend to be noisy and have harsh shadows.

Frontal lighting of the kind recommended for colour photography seems to give the best pictures and to this end our own dolly had two 150W lamps in reflectors mounted on the pan and tilt head of the camera so that they moved around with it.

Whenever possible stray lights (e.g., table lamps) should not be allowed to enter the field of view of the camera as these can cause flaring and flattening of whites, due to the inability of the camera tube beam to fully discharge the target plate around the overloaded area.

For a stage such as the one that most of our programmes came from, three or four 1,000W floodlights gave sufficient overall lighting to enable good pictures to be obtained from all angles at any distance. Spotlights give harsh shadows and should be avoided, or diffused.

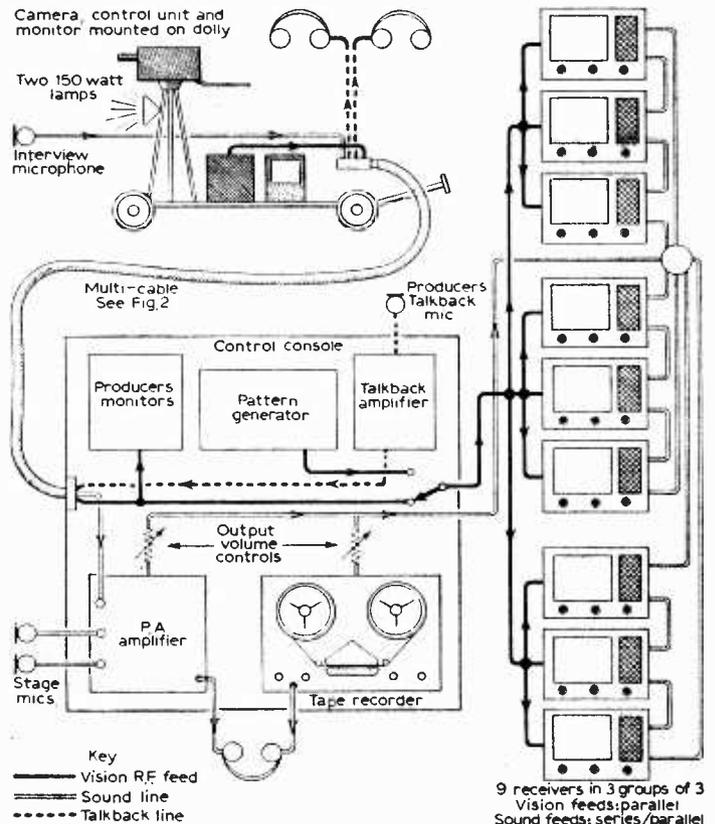


Fig. 1—A block diagram showing the inter-connections of all the equipment.

Programmes

As far as spectators are concerned the operation of a CCTV unit is just as interesting as the pictures it produces. This is fortunate as it permits fairly long intervals of blank screen and music whilst the dolly is moved from one place to another. It is however advisable to fill up as much waiting time as possible with "See yourself on TV" of which the public never seem to tire.

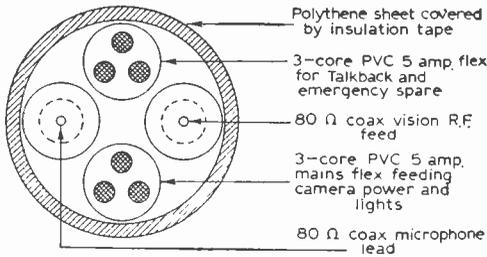


Fig. 2—A section through the 50yd multi-cable connecting the dolly to the control console.

Programme schedules should be laid well in advance, and any very ambitious schemes that the non-technical suggest can be immediately vetoed by a "Can't be done, old boy"!

Simple variety shows, fashion parades, and interviews with exhibition stall holders are practical propositions, and if (as at most exhibitions) the people appearing before the camera have an axe to grind, presentation can follow ITA lines, with "commercials" added between programmes.

These can be printed on cards the same size as the captions and test card. An ideal size is approximately 10in. x 12in. and the cards used should be tinted to give a mean grey shade on the screen. Lettering can be done in white poster paint, with Indian ink backgrounds.

The most effective method of presenting the "commercials" is to arrange them on a music stand in a stack so that they are allowed to fall forward one at a time into a tray. The camera is lined up on the front caption so that it is under-scanned, that is to say the edges stick out beyond the field of view.

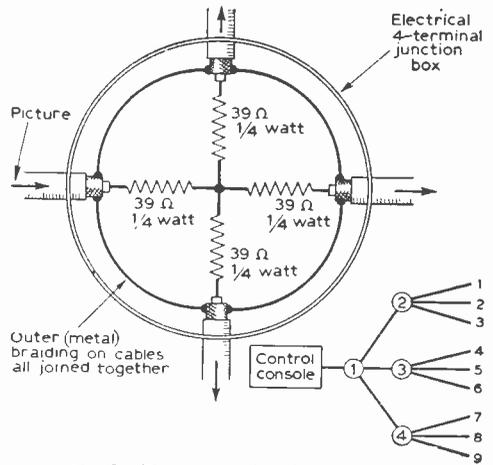


Fig. 3—The picture distribution boxes.

If the fall-down time is fairly rapid and the operators fingers do not appear on the screen, it is difficult to see how the caption change is performed. The accompanying sound can be pre-recorded with speech and "jingles" overlaid on timed music to guide the caption dropper, who may also work from a script.

The Main Problem


The main problem with other types of entertainment is to hold the interest of the viewers eye, limited as one is by "one camera, one lens". The golden rule of amateur cinematography is "Keep the camera still, and let the subject move", and this should be ruthlessly applied whenever possible.

In practice this was found to be simple for the fashion parade, but difficult for the instrumental trio, which didn't move about. Two separate techniques were evolved and are described below.

For *fashion parades* the set up in Fig. 4 is used, the camera being stationary. Models walk slightly diagonally towards the camera. Around about point A the whole of the model is in the field of view.

As she approaches point B, her head and feet go out of shot and it is advisable to tilt down to feature accessories, i.e. handbag, gloves and shoes. At the nearest point to the camera (C) the model slowly turns as is apparently her custom, and the cloth of the garment fills the screen completely.

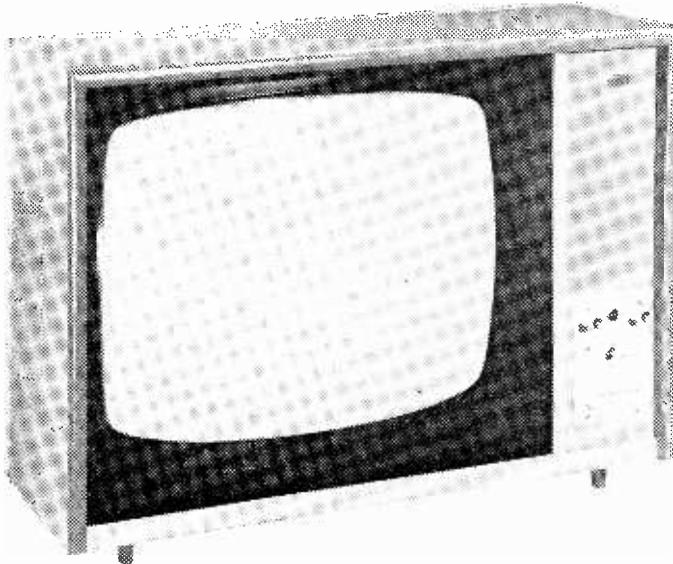By rapidly refocusing, excellent pictures of the texture of the cloth are obtained, usually taken at about waist level where the speed of rotation is slowest. As the model walks back the millinery is



A 23in. video monitor made by Murphy and incorporating a 3-channel press-button selector.

featured at B2, and the final tilt down to the original shot is made as she passes A. At A and B still objects such as a fern or floral display are carefully introduced for focusing purposes.


It is difficult to operate the focus control continuously on a camera not intended for broadcasting, but three separate refocusing at points A, B and C are well within the capabilities of the cameraman.

This process can be repeated from time to time, closing up on the different members of the group as they take their solo, or for light relief, upon the tapping feet of the audience.

Lens Turrets

If the user is more fortunate than we were, and has a choice of two or three lenses, scope is con-

Fig. 4—A simple set-up for a fashion parade.

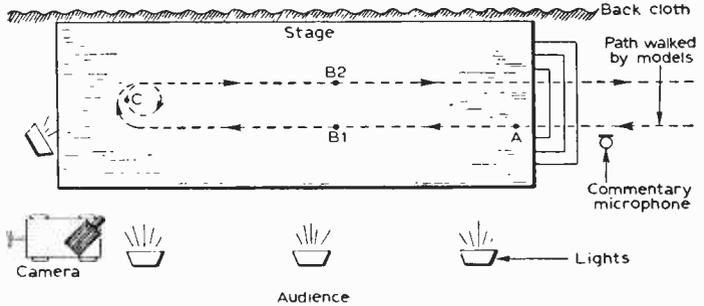

The routine should be worked out in advance with the fashion commentator, so that the sound relates to the picture being screened. It is inadvisable to provide amateur commentators with a monitor screen as there is a tendency for them to get interested in the pictures, whereupon they stop talking.

For *instrumental groups, etc.* the example shown

considerably wider. If some means of blacking out the picture during lens change is not provided on the camera, it should be done optically, by stopping down the aperture, to avoid distressing effects on the screen.

When using a telephoto lens, the dolly and tripod must be kept rock steady as the slightest movement will show as picture shake.

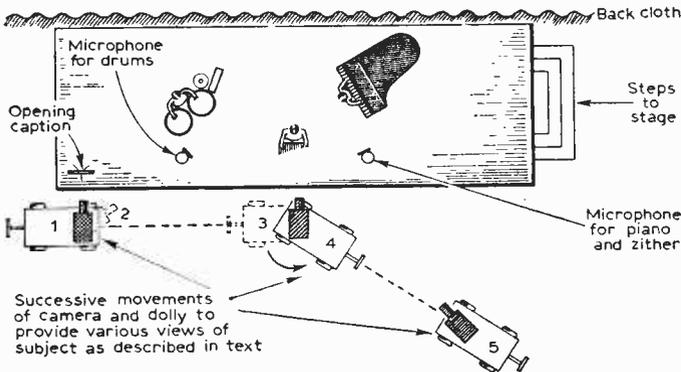


Fig. 5—The same stage as in Fig. 4, used for a musical trio.

in Fig. 5 of a rhythm trio can be regarded as representative. The camera is shown initially lined up on the opening caption, and as the show starts it pans right to give an over-all view of the trio. Panning should be done slowly, as a fast pan makes viewers feel dizzy, and they can occasionally be seen grasping tightly to upright objects.


After dwelling on the opening scene for a while the dolly tracks into the central figure (in our case a man seated playing a zither) the camera closes in so that the fingers plucking the strings fill the whole screen. Whilst the camera dwells on this close-up, the dolly can be carefully swung round to a different angle, and, as interest in the close-up wanes, tracks slowly out to give a different long-shot of the stage.

Faults

There is a limit to how much repair work can be done during the show. Faults in the multi-cable can be overcome by using the 3-core flex originally intended as the talkback circuit. This can carry the mains, or the microphone feed of R.F. picture signal (or both of the latter) in an emergency. The talkback can be restored by using the two coax outers, which seldom go down.

A pre-recorded breakdown apology followed by music should be standing by at all times at the control panel, and a breakdown caption can be put in front of the camera to cover up a hitch in the production side. Ours read: "No apologies for the breakdown—it was bound to happen".

(To be continued)

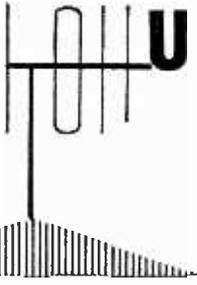

UNDERNEATH THE DIPOLE

A MONTHLY
COMMENTARY



BY ICONOS

IT takes a little time to digest all that one sees at the annual Radio and Television Show at Earls Court. My considered opinion is that the standard of black-and-white commercial television receivers is once again improving—a comment I haven't made for two or three years.

The loudspeakers are now forward-facing, instead of being around the side or the back of the sets, and there are even two or three makes which incorporate some form of D.C. restoration for ensuring a correct reproduction of the grey scale, from black to white. The 625-line closed-circuit pictures were impressive, but the colour sets showed little improvement on previous years and demonstrations.

Colour Television

I have yet to see more than one colour TV camera in operation together that match one another in colour balance, and the wide variation of colour bias on the receivers was very noticeable. It has been said that colour TV receivers will cost about £750 each for the first year or so of regular transmissions.

Colour television cameras cost about £14,000 each, and the increased costs of colour switchers, monitors, lighting and other equipment adds about £100,000 to the cost of each television studio which is turned over from black-and-white to colour.

Actually, the cheapest and most reliable method of making colour television productions is to film them in colour with motion picture cameras and to broadcast them from colour telecine machines. It will be far too expensive to mount a colour television play for a single live transmission; and colour tele-recording is in its very early stages of development.

Retrospect

Thinking again of the stands at Earls Court that most impressed me, neither the BBC nor the ITA take their place in my "top ten". The most interesting exhibits were those of the Post Office and the Armed Forces, where ingenious working models of all kinds attracted crowds. The Independent Television News presented a film about the evolution of the ITA, with emphasis upon the erection of the latest transmitter in Wales.

Too many dawn and sunset scenes cast shadows across a brave effort, which seemed austere when compared with the brashness of the BBC's disc jockey stand. There are rumours that it will be two years before the next Radio and Television show. I may grumble about the show in these columns, but I hope this isn't true. After walking around the stands for a few hours it's not me that protests—it's my feet!

The Granville Studio

There may be no business like show business, and I suppose this is because of its ups and downs. Music halls, theatres, circuses and film studios have all had their good and bad times, though they have been mainly bad of late—for which television is blamed. It is, therefore, sad to have to record that the Granville TV Studio, Walham Green, is closing.

This studio was ingeniously converted from a music hall by Associated Rediffusion, and, quite recently, brought thoroughly up-to-date with a new lighting grid and 4½ in. Pye image orthicon cameras for live TV or for video tape recording via a line to the Museum TV Exchange. Yet it is now off the air—mainly because one of the industry's trade unions will not allow taped advertising commercials to be broadcast more than once!

It is stated that the film tech-

nicians fear they will be out of work if the use of video tape spreads into the "commercials" field! Which only goes to show how stupid some people can be! The video-taped commercial is very limited in use and cannot approach the film for flexibility of handling, editing, captioning and cheapness. Taped commercials have their uses for coupling advertising to hot news, such as the result of a motor race or a beauty competition.

Continental Programmes

Two items of Continental origin which impressed me very much were respectively from Brussels and Munich. From Brussels came the beautifully video-taped ballet "The Four Brothers", which included the famous game of chess with live chessmen. This production was by Granada, who sent a large unit of technicians and director Gordon Flemyng, together with a mobile control room, TV cameras and video tape machine to record it in an improvised TV studio in a circus in Brussels. The result was superb and the recorded tape was broadcast most appropriately at the time of the Edinburgh Festival, where the same talented company also presented it.

The second notable Continental programme was "Too Young to be Blonde", the Bavaria Film Studios prize winning entry from the Montreux Festival. This was a fast-moving revue about a German concert party travelling from town to town by bus to play one-night-stands. The music was lively and gay, the girls were strikingly beautiful, and one didn't have to know the language to appreciate a first-class production. This film was made with the aid of the Arriflex Electronic-Cam System which has been previously mentioned in these columns.

This employs a number of motion picture cameras controlled with the electronic aids and vision

mixer just in the same way as live television or telerecording. This is a new technical philosophy. It isn't really television and it is certainly not filming in the traditional way. The final result is achieved in much the same way as for video-taping—but the end product is high-quality film negative, which yields 35 or 16mm film prints which can be shown on television anywhere in the world.

BBC's Edinburgh Regional Studio

Distinguished artists who appeared in the Edinburgh Festival took part in an "informal" television programme recorded in the BBC Edinburgh Studio. Elizabeth Söderström, the charming and talented Swedish soprano introduced the guests who played or sang music of their own choice. The setting was an elegant drawing room and the guests were in evening dress, moving and talking with poise appropriate for a dazzling salon of the Edwardian era.

If this programme turned out to be far from informal, in the modern sense of Edwardian informality, it was all the more welcome. The fine technical work of the director, Alan Rees, and the designer, Douglas Duncan, was worthy of the fine performances offered by the artists from many nations.

The handling of the cameras and cutting during John Ogdon's short but excellent piano recital, was unusual and effective, especially a new type of overhead shot. The programme concluded with a beautifully modulated song by Elizabeth Söderström herself. Credit must be given in this programme to the excellence of the sound balancing.

"What's In it For Walter"

I wish I could say the same things about the sound balancing in the TV play "What's In It For Walter", Barry Thomas's television play of the Tilsey novel, the dialogue was often drowned by the musical background. This is possibly not surprising, because Walter is the pianist of a dance band at a holiday camp, and he has been persuaded by the crooked manager to play for a hundred hours without stopping—a piano marathon.

Naturally, there was a solo piano background throughout the rest of the play. John Stratton

gave a brilliant performance of the tiring musician, playing the piano with great precision (to playback) and getting the utmost out of rather poor dialogue writing.

The faulty sound balancing occurred mainly in the opening sequences of this play, when the off-stage complete dance band, with saxophones, etc., obscured the dialogue in the nearby manager's office. The main fault of this television play was, however, the contrived story which made one wonder why anybody took the trouble to write a complicated TV play script of it.

Portraiture and Make-up

Television is largely a close-up medium. The immense crowds and spectacular long shots of super-colossal Cinemascope and wide screen films mean little on the small television screen.

It is, therefore, all the more important that lighting supervisors of television plays observe the rules of portraiture. Modelling of the face, avoidance of ugly shadows and ability to see the eyes of the players should be the principal objectives in lighting set-ups. The key lights, filler lights, back lights and kicker lights all play their parts in building up a pleasing picture.

Lighting for two or three TV cameras naturally leads to flatter lighting than is possible in the film studio, where usually only

one camera is used and much time is spent over every individual close-up. That first-class lighting can be obtained with multi-camera technique is demonstrated by the superb results obtained by the BBC in "Steptoe and Son", results which survive the degradation that must result from transfer to magnetic tape or by telerecording to film.


On the other hand, the same remarks do no apply to "Hugh and I", a delightful series in which Terry Scott and Hugh Lloyd take over a situation comedy series of the Tony Hancock—Sidney James type. Terry Scott has improved enormously as a television actor, but he is not helped by the shadows that obscure his and other actors' eyes in this series. The use of small lamps called "bashers" fitted to the cameras, which only become effective at short range, should remove the screening effect of shaggy eyebrows.

As regards the ladies, the lips are particularly important. Pale lipsticks look even paler when the studio lighting is dimmed a little, and it is not difficult to make a healthy looking young female look like an anaemic invalid. By far the best close-ups on television were obtained with CPS Emitron cameras and little or no make-up for the actors. But these cameras need about twice as much light as the modern image orthicon cameras.

PRACTICAL WIRELESS

Chief Contents of the November Issue

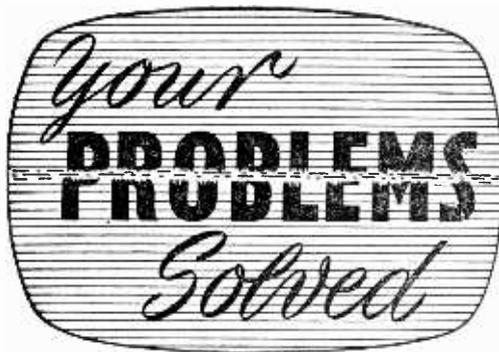THE AUDITRON
THE SAVOY VHF TUNER
THE MAYFAIR PRE-AMPLIFIER
UNIVERSAL TEST OSCILLATOR
TRANSPORTABLE A.C. SUPERHET
WIDEBAND MASTHEAD AMPLIFIER
DIO COMPONENTS AND THEIR FUNCTIONS
VINTAGE-MODEL OR F.M. TUNER?
REFLEXING THE P.W. MINUETTE
CENTRAL CONTROL AMPLIFIER
SHORT WAVE LISTENERS' LOG
ANODISING ALUMINIUM
TRADE NEWS
ETC., ETC., ETC.



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDER-TAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 84 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

PAM 555 F.M.

Until recently this set was working well, but on switching on, the other day, it was completely dead.

On inspection I found that all the valves were alright, except the EY86. This I replaced with no results. The PY32 has also been replaced recently. I would be grateful for any information you could give me regarding this fault.—J. Ward (Londonderry).

The symptoms you describe suggest a lack of H.T. and we advise you to check the 23Ω surge limiter in the PY32 anode circuit and also the mains dropper sections.

COSSOR 950

The sound is as normal, but there is only a bright horizontal white line, about an inch wide, across the screen. All the valves light up.—T. Gormley (Rowlands Gill, Co. Durham).

Check the valves, V14 (ECC82) and V5 (PL84), which are on the frame timebase printed panel.

MURPHY T.V. 270A

The fault with this set is vertical distortion. I have no service data for this receiver, but I have found that by rocking a small potted transformer at the rear of the chassis, the verticals will straighten. Could you confirm that this is the line oscillator transformer?—W. E. Waters (Wade-bridge, Cornwall).

The potted transformer you refer to is the line oscillator transformer. A frequent cause of the trouble you are experiencing is a poor chassis connection, either of the metal case, or on the adjacent tagstrip beneath the chassis in the region of the transformer. Check also for dry joints.

MURPHY V214

This receiver was working normally with an excellent picture until recently, when suddenly the picture vanished completely with no fading at all. The sound is still present.

I noticed at the time, that the U25 rectifying valve was glowing blue, but this was replaced with no results. The line timebase whistle is present.—P. Bottomley (Sutton, Surrey).

Check the EHT rectifier which may have shorted out. (The way to check this component is to disconnect it.) If oil leaks from the line transformer, this may be faulty.

K.B. KV50

Is there any turret tuner which can be easily fitted to this set—which at the moment covers three channels only—to give all channels?—A. R. Ferguson (Dovercourt, Essex).

The Brayhead multi-channel turret tuner type 16P, is suitable for your set. This should be ordered with a B7G R.F. plug and a 16BA6 adaptor. It is then simply a matter of removing two valves from the set and plugging in the tuner in accordance with the instructions supplied.

BEETHOVEN

This 14in. receiver is about eight years old and marked "Beethoven Electrical Equipment Ltd.", but I can find no model number. As I wish to send for the service sheet for this set, I would be grateful if you could possibly identify the model from this information.—S. Swan (Paisley, Renfrewshire).

This is probably of the Beethoven B77 series. It uses EF80 valves and a Mullard MW36-24 CRT.

FERGUSON 992T

The trouble with this set is that the picture has vertical lines on it about $\frac{1}{4}$ in. wide, where the picture content is very bright. Adjusting the line linearity magnet moves these lines but does not remove them.

Another fault is a regular noise, not unlike interference, which is present on sound and sometimes appears as black bars across the screen. This only happens when the set has been on for about five or ten minutes and is tuned to ITV.—L. Pearson (Liverpool).

A low emission PY81 or PL81 aggravates the "ringing" effect described. Other causes are low H.T. and a defective line output transformer.

The noise on Band III should lead to a check of the tuner valves. If the valves themselves are in order, check that they are making good electrical connection with their bases. Also check all other external connections and "earths".

H.M.V. 1843

I would appreciate any instructions you could give me regarding the correct method of resetting the ion-trap magnet on the neck of the tube, as I have recently had to repair the fibre band on this component.

At the moment I receive a picture, but I would like to make sure of the setting.—J. W. Gilton (St Helens, Lancashire).

Once a picture has been obtained by adjustment to the ion-trap magnet it is necessary simply to adjust the magnet along the neck of the tube and axially for the brightest possible picture, with the brightness control turned to about half-way. If necessary, re-centre the picture by the shift controls on the focus assembly.

ULTRA V71

The fault with this set is that although the sound is present, the only picture obtainable is a bright horizontal line across the centre of the screen.

I would be grateful for any advice you could give me regarding this fault and for any information you could let me have as to how to change this set from a channel 5 receiver to channel 4.—G. A. Wood (Peterborough).

The horizontal line is caused by failure of the frame timebase. The usual cause of this trouble is an open-circuit 24 μ F electrolytic capacitor connected between the frame scanning coils and chassis. If the trouble persists, check the UL46 frame amplifier and 6K25 frame oscillator.

There is no specific procedure for changing channel on this fixed channel model, but it is usually possible to change from channel 4 to channel 5 by unscrewing the oscillator trimmer two or three turns and readjusting the grid and anode tuned circuits of the R.F. stage for optimum sound and picture quality. The idea is first to adjust the oscillator to get sound and vision on the new channel (with a strong aerial signal) and then to follow up with the R.F. adjustments while reducing the setting of the contrast control. Alternatively, a signal generator is required to establish the new frequencies as the tuned circuits are adjusted.

H.M.V. 1826

I recently bought a re-gunned Mullard 43MW-64 tube to replace the one in this set. However, I cannot get the picture into proper focus unless the brightness is turned down to such an extent that the picture is not worth looking at. When the tube is lit up, the whites are defocused rather badly. I read in one of your back numbers that pin 7 should be tied to the cathode pin 11 on this tube. Is this correct? At the moment the second anode is left free.—L. Rees (Bristol).

The MW43-64 differs considerably from the Emiscope 4/14, the former being a pentode and the latter a tetrode. The second anode of the former must be connected to the cathode, but the main requirement to worry about is a smaller focusing field with the pentode, and this may necessitate a different focus assembly or considerable readjustment to the original.

DECCA DM 14

The frame linearity on this set takes nearly an hour to reach normal. At first it is stretched at the bottom and although it eventually rights itself, it takes a long while. As the linearity changes, it affects the interlace so that this cannot be controlled for some time. The frame will lock over a wide range of the frame hold setting but the control for the interlace is critical and alters with linearity.

Recently the bars on Test Card C have become indistinct—on BBC the 2.5Mc/s bars are faint and the 3Mc/s bars are missing. On ITA this condition is worse. Would a failing R.F. amplifier valve be the cause of this?—F. Johnson (Fareham, Hampshire).

The frame linearity trouble should first lead to a check of the frame amplifier valve, the H.T. voltage and the setting of the mains adjustment. Also, if necessary, the components associated with

the frame linearity control should be tested, as one or more may alter in value with increase in temperature.

Impaired definition could be caused by the failing tube or misalignment of the vision I.F. channel. A defective R.F. amplifier valve would not usually cause the trouble.

FERGUSON 992 SCH.E.

The screen suddenly went blank except for the raster. Adjusting the brightness and contrast controls fully clockwise brought back the picture but with flyback lines present. However, in this condition the picture was too bright and retarding the brightness control caused the screen to gradually become dark, with the darkness moving across the screen from the right, until all the screen was black.

The voltages on the tube base have been tested and found to be correct. The sound remains good at all times and tapping the tube base has no effect.—J. Hood (Seaham, Co. Durham).

This could be a tube defect, but from your remarks the trouble would appear to lie either in the video amplifier stage or in the vision I.F. amplifier as instability. If the trouble clears when the control grid of the video amplifier is shorted to chassis (there will be no picture, of course) then I.F. instability is the cause. If the uneven illumination remains, however, suspect the tube and video amplifier circuit.

FERGUSON 988T

This set went dead one evening as though it had been switched off. On examination neither the valves nor the CRT showed signs of life, with the exception of the three valves in the converter, which is wired as an integral part of the receiver.

I have completely replaced all the valves and the CRT; I have tested the fuse and checked as much wiring as I can. Everything appears to be in order, but still the set remains dead.—R. Whittington (Thornton Heath, Surrey).

Check the thermistor, the mains dropper and the on/off switch, as one of these items—assuming that the valve and tube heaters are intact—in the series-connected heater chain must be defective.

K.B. PVP.20

I have recently serviced three of these receivers with the same complaint, which is that the horizontal and line hold controls need frequent adjustment. After changing the valves in one receiver in the frame timebase and sync separator stages, I still had occasion to adjust the horizontal hold control several times.

I would be very grateful if you could give some idea of what could cause this condition.—R. Dawson (Gateshead, Co Durham).

The usual causes of this trouble are: drift in the PCF80 triode section used as line oscillator; drift in the 470k resistor connected to the line hold control; a fault in the line blocking oscillator transformer, and alteration in the value, when hot, of the 300pF capacitor connected to the control grid of the line oscillator triode.

DECCA DM.55

This receiver was working quite normally, when the picture suddenly jumped upwards three inches.

(Continued on page 83)

NOW!


YOU can MASTER ELECTRONICS!

BRITAIN'S MOST COMPREHENSIVE PRACTICAL COURSE IN RADIO • ELECTRONICS TELEVISION!


THESE SPECIAL TRAINING KITS—YOURS TO KEEP



Multi-Range TEST METER

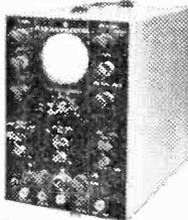

CATHODE RAY OSCILLOSCOPE

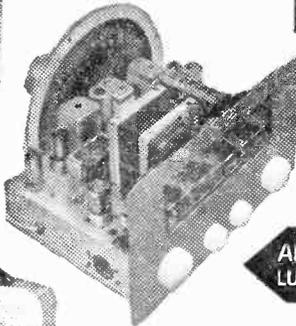

AM and VHF/FM LUXURY RECEIVER



SIGNAL GENERATOR




Complete set of Picture Way books and Experimental Manuals

LEARN BY BUILDING NOW for your CAREER • HOBBY OWN BUSINESS

YOU RECEIVE

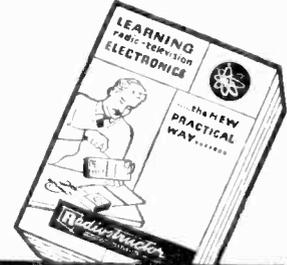- Complete kits of equipment as illustrated.
- Complete set of experimental manuals.
- Complete set of "picture-way" theory books.
- Modern test-yourself examination sheets.
- Study programme.
- Unlimited consultation with Tutors.



FREE POST BROCHURE NOW

RADIOSTRUCTOR

TO RADIOSTRUCTOR (DEPT. MI02) READING, BERKS.

Name BLOCK

Address CAPS

..... PLEASE

(We do not employ representatives) 11/62

BUILD YOUR OWN COMPLETELY TRANSISTORISED TELEVISION CAMERA!

Our basic kit contains Scan and focus coil assembly. All special inductances needed. Full circuit diagrams and drawings showing layouts. Output from the camera is designed to work into domestic TV receiver on bands 1—5. 405 to 625 lines. Simple instructions also contain educational data on the working of vidicon type cameras.

(Educational authorities, please note that this kit will give a very clear understanding of television camera practice).

All transistors, diodes and all other parts are readily available being completely standard!!

DEALER INQUIRIES INVITED

GOLDEN RULE ELECTRONICS LIMITED
SOUTH VIEW LABORATORIES, LITLINGTON,
NR. ROYSTON, HERTS. Phone: Steeple Morden 366.
(3 lines.)

£12.0.0
Basic Kit Complete.

Golden Rule also manufacture Vidicon Scan Coil Assemblies for colour work. These are very accurately wound and matched for linearity. Supplied in sets of three. Complete with Focus and Shift coils. Details on request. All types of Vidicon tubes in stock, from £8.0.0 up.

VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

SETS	IR5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ..	Set of 4 for 19/6 4 for 27/6
OA2	11/6	6P1 7/-
1A7GT	11/-	8P25 8/-
ID5	7/6	8P28 12/-
1HSGT	9/-	8Q7C 6/-
1NSGT	9/-	6Q7GT 8/-
IR5	6/-	6SL7GT 5/9
1S4	8/-	6SN7GT 4/9
1S5	5/3	8U4GT 9/9
1T4	3/8	6V6G 4/6
1U5	5/9	6V6GT 7/3
3A5	9/-	6X4 4/6
3Q4	7/-	6X5GT 6/9
3S4	6/-	7B6 9/-
3V4	7/-	7B7 8/-
5U4G	4/6	7C5 7/9
5V4G	8/-	7C6 7/6
5Y3GT	6/-	7H7 7/6
6Z4G	9/-	7S7 9/-
6AL5	3/9	7Y4 9/-
6AM6	3/6	10C2 16/6
6AQ5	6/-	12A8 110/6
6AT8	6/-	12AT6 7/-
6BA6	5/9	12AT7 5/-
6BE6	5/9	12AU7 6/3
6BH6	6/3	12AX7 7/-
6BJ6	5/9	12KGT 4/9
6BR7	11/-	12K8GT 9/6
6BW6	8/-	12QGT 4/9
6CD8G	27/3	12S7GT 7/6
6C1	10/-	12Z3 10/6
6F6G	6/6	20F2 17/-
6F13	10/-	20L1 16/-
6F14	10/-	20P3 18/9
6K7G	1/11	20P4 20/-
6K8GT	5/-	20P5 15/9
6L16	10/-	25A8G 8/-
6LD20	8/-	25L6GT 7/-
		25Z4G 8/6
		30L15 11/-
		30P19 14/6
		30P113 12/3
		35A5 15/9
		35L6GT 8/3
		35Z4GT 5/6
		50L6GT 9/-
		85A2 8/6
		AZ31 9/6
		B36 7/6
		CL33 12/3
		CY31 10/-
		DAC32 9/-
		DAF91 5/3
		DAF96 7/6
		DCC90 9/-
		DF33 9/6
		DF91 3/8
		DF96 7/6
		DH76 4/9
		DH77 6/6
		DH81 8/-
		DK32 11/-
		DK91 6/-
		DK92 7/6
		DK96 7/6
		EL33 8/-
		EL35 9/6
		EL92 6/-
		EL94 7/-
		EL96 7/6
		EACB9 5/6
		EAF42 5/6
		EB91 3/9
		ERC33 5/9
		ERC41 8/-
		EF90 9/6
		EF98 9/6
		FX51 7/6
		FX96 7/9
		ECC81 5/-
		ECC82 6/3
		ECC83 7/-
		ECC84 8/3
		ECC85 7/9
		ECP80 7/9
		ECP82 8/6
		KT63 6/6
		MU14 8/6
		N18 7/-
		PC95 10/-
		PC97 10/-
		PCC84 7/6
		PCC89 9/3
		PCF80 7/9
		PCF82 8/-
		PCF86 14/-
		PCL82 9/-
		PCL83 10/6
		PCL84 10/-
		PCL85 10/6
		PENA4 11/-
		PEN36C 8/-
		PL36 11/6
		PL61 9/6
		PL82 7/-
		PL83 7/6
		PL84 8/6
		PY41 10/-
		PY35 9/-
		PY32 11/6
		PY80 7/6
		PY81 7/-
		PY82 6/6
		PY83 7/9
		U22 7/3
		U25 12/-
		U26 9/3
		U47 12/-
		U50 6/6
		U52 4/6
		U78 4/6
		U91 14/6
		U281 17/-
		U291 16/6
		U301 17/-
		U801 21/-
		UAF42 8/3
		UB41 7/-
		UBC41 7/9
		UBF80 8/3
		UBF89 8/3
		UC92 9/3
		UCC84 13/3
		UCC85 7/6
		UCF80 14/6
		UCH21 13/6
		UCH42 8/9
		UCH81 8/-
		UCL82 9/9
		UCL83 13/3
		UP41 7/6
		UF89 7/-
		UL41 8/-
		UL84 6/6
		URIC 8/-
		UT21 11/-
		UY41 6/6
		UY85 6/6
		VP4B 9/6
		VP41 5/-
		VF1321 16/6
		W76 4/9
		W77 3/9
		Z77 3/6

TRANSISTOR RADIOS CIRCUITRY & SERVICING

- 5/- by Mullard Postage 6d.
- BASIC TV COURSE by G. Kravitz, 32/-, Postage 1/-.
- RADIO CONTROL MANUAL by E. Safford, 25/-, Postage 1/-.
- TV SERVICING HANDBOOK by G. King, 30/-, Postage 1/6.
- COMMUNAL AERIALS by G. King, 8/6, Postage 6d.
- RADIO AMATEUR'S HANDBOOK by A.R.R.L., 36/-, Postage 2/-.
- ELECTRONIC ORGAN HANDBOOK by H. Anderson, 40/-, Postage 1/-.
- SERVICE VALVE EQUIVALENTS by R.S.G.B., 3/-, Postage 6d.
- RADIO VALVE DATA by W.W., 6/-, Postage 10d.
- COMPLETE CATALOGUE 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books
19-21 PRAED STREET LONDON, W.2
Phone: FADDington 4185
Open 6 days 9-6 p.m.

READERS RADIO
24 COLBERG PLACE, STAMFORD HILL
LONDON, N.16 STA. 4587

Post 6d. per valve extra.
Any Parcel Inured Against Damage in Transit 6d. extra.
Any C.O.D. Parcel 3/- extra.

I have replaced V16, V8, V7, V6 and the 500 μ F capacitor, C76. I have tested by substitution the rectifier PY82, but the fault still remains.—B. Tandy (West Bromwich, Staffordshire).

The trouble lies in the frame timebase. If the valves and smaller components are in order, particularly those associated with the frame linearity control circuit, suspect shorting turns in an associated transformer.

DECCA DM.4

The sound on this receiver is perfect, but there is no picture or raster whatsoever. The EY86 has been replaced but without success. Most of the valves have been checked and found in order, with the exception of an ECL80 which was replaced but with no improvement in the condition of the set. The CRT heater lights up.—C. Saphery (London).

If the EY86 is not lighting up, the trouble is in the line timebase section. If the line whistle can be heard when the line hold control is rotated, the trouble lies in the line output stage. In this event, check the PL81 and PY81 valves. If these are in order, check the smaller associated components. If there appears to be no obvious fault, shorting turns in the line output transformer may well be responsible.

FERGUSON 991T

This set was working well until recently, with both the sound and vision perfect. However the picture suddenly collapsed completely leaving the sound only.

I have replaced the EY51 twice, but each time the set functions for a very short time only, and then the picture goes leaving the sound.

I suspect a short in the windings of the line output transformer, as on close inspection it seems to be overheating.—K. G. Fenner (Sutton, Surrey).

Shorting turns in a winding of the line output transformer is a frequent cause of the trouble described, but this can only be proved conclusively by trying a replacement transformer.

PILOT TV94

This set uses a 14in. C14FM CRT. I have replaced quite a few of the valves which were weak and now I would like to replace the tube which has been boosted for some time and is now nearly useless. Could you please tell me if it would be possible to use a 17in. tube, type C17FM, and what snags I might run into during the process of changing them over.—W. E. Dodd (Doncaster, Yorkshire).

Electrically, the tubes mentioned are very similar and a direct substitution is possible. However, the 17in. tube usually requires slightly more EHT voltage than the 14in. tube to give a picture of equivalent brightness, and this may not be obtainable from the chassis in question. The effect, therefore, should be a slightly less bright picture.

SOBELL TS17

There is a continuous buzzing from the loud-speaker which alters as the volume control is rotated. I have substituted the valves in the sound section. Also I have adjusted, very slightly, the studs on the turret to see if this made any

difference.—J. Henderson (South Shields, Co. Durham).

This could be caused either by faulty H.T. smoothing or vision breakthrough in the sound channel. In the former case, replacement of the defective electrolytic would represent a cure, while in the latter case, complete realignment may be required.

PYE C14

When this is switched on, the screen is covered with "wicket-work" and cannot be corrected with the horizontal hold control. A picture can be obtained, however, by clicking the tuner from one channel to another and back.

The horizontal hold is very critical and usually breaks up when the programme changes. The picture quality seems to have gained in contrast lately. I have tested by substitution V1, 2, 7, 21 and 23.—A. D. Phillips (Sunderland, Co. Durham).

Check the discriminator circuits behind the PCF80 line oscillator valve, particularly the D321Y discriminator diode and the two capacitors connecting it to the sync transformer.

EKCO 169

The trouble with this set appears to be connected with the volume control, which is in the cathode circuit of the first sound I.F. valve (V11). I can receive both sound and vision as normal, but when the volume control is turned fully up, both sound and vision disappear, leaving only a bright raster on the screen. I am unable to understand why the vision should be affected in this way.

The wire-wound volume control is in working order.—H. J. Sagar (Ashton-under-Lyne, Lancashire).

The symptoms you describe suggest instability in the sound I.F. stages. Check the 0.003 μ F and 0.001 μ F capacitors by bridging each with a known good component.

RGD 600

On the BBC channel (Sutton Coldfield) there is sound-on-vision causing a breaking up of parts of the picture, in the form of horizontal lines. This fault occurs particularly during passages of music and loud noises. This fault is not present on the IV channel.

On any other BBC channel, the picture is free from this fault but I receive no sound.—J. Taylor (Nottingham).

We suggest that you check the BBC aerial arrangements for your receiver, as these could be faulty. We do not advise you to adjust the tuner unless you have experience of this operation.

EKCO T327

This receiver functions quite well when first switched on and continues so for a good five minutes. After this, however, the picture gradually fades. The sound is unaffected, and the picture remains complete throughout. After about ten minutes, the set settles down to a position where vague shadows can be seen on the blank screen. These can be faintly brought up when setting the contrast and brilliance controls to approximately the mid-way position in each case, but the picture is completely lost if either control is moved away

from this setting.—F. D. Cosgrove (Marlow, Buckinghamshire).

This fault could either be a faulty U25 or a defective CRT. If the U25 is faulty the picture will swell up if the brightness is advanced, but if the tube is faulty the size of the picture will remain the same.

MURPHY V250C

There is a line timebase fault on this set and I suspect the scan coils as the horizontal scan is reduced to approximately 4in.—D. D. Powell (Horsham, Sussex).

The normal cause of this fault is the failure of the 0.25 μ F efficiency diode smoothing capacitor. This is beneath the U251 and 20P4 valveholders.

Impedance Bridge

(Continued from page 66)

Accuracy

With care in construction and use an accuracy of better than 5% may be obtained on the lower frequency ranges while at 100Mc/s the best obtained has been 7%. The accuracy of 200Mc/s is hard to assess, because the self capacitance of the resistors R2 and R3 affects matters, while the inductance of test resistors and crocodile clips is not negligible. A conservative estimate might be that with care 15% accuracy may be achieved, and this is probably enough for most purposes. ■

The British Amateur TV Club

SIXTH AMATEUR TELEVISION CONVENTION

MEMBERS of the public had an opportunity to see amateur-built television transmitting equipment in operation during the sixth Amateur Television Convention held at The Conway Hall, London, on Saturday, 8th September, 1962. This Convention is a bi-annual event organised by the British Amateur Television Club.

The equipment arrayed around the hall provided examples of the different branches of vision pick-up and transmission technique practised by members. Due to the complexity of the apparatus needed for a complete TV transmitting station, not to mention its cost, it is not surprising to find that for the majority of members specialisation is the order of the day. The individual usually concentrates upon experimenting with either camera equipment, television or TV transmitters.

One of the most important functions of the Club is to co-ordinate these individual activities and thus enable enthusiasts, who so desire, to work in association and to integrate their equipment into complete systems for transmitting and receiving pictures over the permitted frequency channels. Whichever subject the television amateur decides to pursue he is certain to find ample scope for absorbing experimental work.

Camera construction, rather naturally, is highly popular and several closed circuit systems were in operation throughout the day. An interesting exhibit was a "slow scan" equipment. A line rate of 25 per second with one complete frame in five seconds, is used in this system; this allows picture information to be transmitted within bandwidths not exceeding 4kc/s and is also suitable for video recording on to magnetic tape.

Among the transmitting exhibits were complete set-ups for 70cm operation.

During the afternoon three short lectures were given by members of the Club, the subjects being: "Colour Television", "Transmitting Problems" and "Semiconductors in TV circuits". The second lecture included a report of amateur endeavours in establishing two-way contacts, and particularly of the organisation of a network covering a wide area of East Anglia.

Topographical features are limiting factors in cross-country link ups, and opportunities abound today for amateur incentive to "blaze a trail" for VHF TV as in the earlier days of radio communication.

The last lecture was especially notable for the technique of presentation employed for here was an excellent example of amateur constructed closed-circuit equipment performing a serious task. As an accompaniment to the lecture, diagrams and oscilloscope traces were reproduced on a large screen monitor facing the audience, the use of two cameras allowing the lecturer to present a diagram or a trace alone, or one image superimposed on another, at will. ■

QUERIES COUPON

This coupon is available until NOVEMBER 22nd, 1962, and must accompany all Queries sent in accordance with the notice on page 79.

PRACTICAL TELEVISION, NOVEMBER, 1962

“WAVE GUIDE AERIALS”

Manufacturers of TV Radio and Ham Transmitting Antennas wish to offer examples from their range of products. For the amateur Enthusiast and the Do-It-Yourself type.

A SUPER HIGH GAIN ARRAY FOR THOSE DIFFICULT RECEPTION SPOTS

	£ s. d.		£ s. d.
3 Element BBC Folded Dipole, Channel 1, with a Double Five Channel 9 ITA, complete with all clamps	7 10 0	5 Element ITA Loft Aerial	1 6 0
or Double Eight Element ITA	8 10 0	8 Element ITA Aerial outdoor	2 9 4
Mast Equipment per your specification extra		Double 5 ITA Super Fringe outdoor Aerial	4 0 0
S/D5 Combined BBC, ITA Loft Aerial ...	1 10 0	Double 8 ITA Super Fringe outdoor Aerial	5 0 0
S/D 5 Combined BBC, ITA Outdoor Aerial, wall mounting, complete ...	2 13 6	32ft. Garden Masts, complete for erection, two sets guy pickets, etc., with fitting instructions	12 10 0
H & 7 combined BBC, ITA with chimney lashing equipment	4 13 0	Coax Cable semi low loss, 7d. per yard; super low loss 1/2d. per yard.	
BBC Loft Aerial	12 9	Cross over boxes for combining separate BBC and ITA Aerials 9/6d.	
V.H.F. Loft Aerial	11 3	Please send 6d. stamp for full list of aerials and accessories. Terms C.W.O. orders over £4 post and packing free.	
5 Element ITA Aerial for attaching to existing mast	1 10 0		

PLEASE STATE CHANNELS REQUIRED WHEN ORDERING

**WAVE GUIDE AERIALS
DICKER MILL, HERTFORD**

ALL TELEVISION / RADIO COMPONENTS SUPPLIED CHEAPLY AND QUICKLY

CRT's—1 YEAR GUARANTEE

MULLARD & MAZDA, 14in. and 17in. ... £5. 0.0
MAZDA 15in. £5.18.0
MULLARD & MAZDA 21in. £7.10.0
Plus 7/6 via BRS or 12/6 passenger train.

L.O.T.'s

EKCO 221-383 series, **FERRANTI** T1001 to T1012 series, 57/-. **PYE** V4, V7, VT17 series, **PAM** 90-953 series and **INVICTA** 118 to 120 series, 53/-. **HMV** 1840 series, 60/-. **PHILIPS** 1768-2168 series, 98/-. **STELLA** 8917, 98/-. **FERGUSON** 992 series, 65/-. **MURPHY** 200, 214, 240/250 series, 80/-.
Postage and packing 3/6. Cash with order or C.O.D. 1/6 extra.

VALVES

All types at bargain prices.
 Scan coils, width/linearity coils/knobs, controls, ect.
All prices quoted on request.

MANOR SUPPLIES
 64 Golders Manor Drive,
 London N.W. 11

VACUUM ELECTRONIC LIMITED

KEEPS YOU IN THE PICTURE

WITH THE FINEST REBUILT CATHODE RAY TUBES

12 MONTHS GUARANTEE



WRITE PHONE OR CALL
VACUUM ELECTRONIC LTD.
 35, SACKVILLE STREET
 LONDON, W.1
 REGENT 6404 (5 lines.)

LAWSON

DIRECT REPLACEMENT TELEVISION TUBES




12 MONTHS' FULL REPLACEMENT GUARANTEE

DESIGNED FOR PERFORMANCE

The modern Lawson television tubes are specially designed to give all types of television set very much improved performance. Their new silver activated screens are much brighter with better contrast, exclusive "microfine" controlled thickness aluminising gives 50% more light output (superb daylight viewing). New small anode aperture electron guns by Mullard, Mazda, G.E.C., Brimar, E.E., Cossor, etc., ensure needle sharp definition and focus, and silicon vacuum pumping plus depth formed cathodes give very long life. Each tube is 100% **BRAND NEW** (glass excepted), and Lawson are the only tubes guaranteed to be exact replacements for the original tube, ensuring complete accuracy and efficiency.

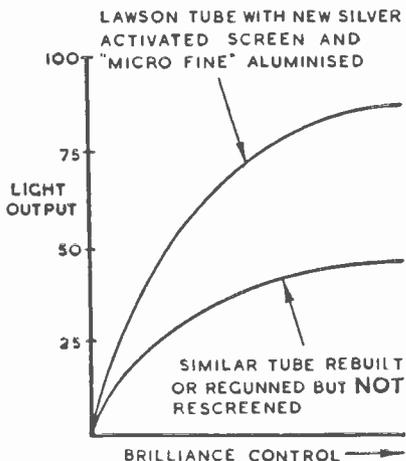FROM STOCKS OF OVER 5,000 TUBES OF 200 TYPES WE CAN SUPPLY THE EXACT TUBE YOU REQUIRE BY RETURN



EXPRESS PASSENGER SERVICE—
Orders received by 3 p.m. are despatched same day.
Special direct services to Scotland and Ireland.

Full fitting instructions with every tube.

LAWSON TUBES LTD. Tel. 2100
2 PEACHFIELD CLOSE, MALVERN, WORCESTERSHIRE.

12" —	£4. 10. 0
14" —	£5. 5. 0
15-17" —	£5. 15. 0
19", 21", 23", also available	

C.O.D. or C.W.O.

10/-

Glady refunded if you wish to return your old tube (excepting 12")

CARR. and INS. 7/6

TAPE RECORDERS



One of the easiest ways to learn anything, is to "tape" it and then keep playing it back. The Industrious Japanese have really gone to town on tape recorders.

this year and many bargains are on offer, it is the writer's opinion that there is bound to be a big demand for them as Christmas presents so there is a good reason why you should buy your tape recorder immediately. Prices range as follows:


- Child's Model..... £4.19.6
- Assemble yourself Model £6.19.6
- Model No. III-3..... £8.19.6
- The "Treasurer"..... £8.19.6
- The "Pocket Secretary"..... £14.14.0

The first two are not really good enough for music but they are quite good for speech. The last three are reasonable also for music. All have a value out of all proportion to their cost. Try this new learning technique—you will be amazed.

Bargain For Service Engineers

You often come up against the old set that won't be parted with. For these we can offer bargain parcel of rectifiers MU12 replacement and 1D5 replacement. Ex-government, of course, six of each for £1. post paid.

"DIPYT" Automatic Headlamp Dimmer

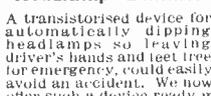

A transistorised device for automatically dipping headlamps so leaving driver's hands and feet free for emergency, could easily avoid an accident. We now offer such a device ready made and tested.

The unit measures 5 x 2 x 5/8 in. and fits under the dash. It is very easy to wire into the circuit and can also be used to control side lamps for parking. Price of unit is £10.19.6, carr. paid, diagram and instructions free with unit or separate 2/6. (Agents Wanted).



MULTI-METER BARGAINS!

MODEL TP58. (illus. on left). 20,000 ohms per volt, D.C. volts, 5 ranges up to 1,000 A.C. volts, 5 ranges up to 1,000 resistance, 2 ranges up to 10 meg., capacity 2 ranges up to 0.1 decibels —20 to +26. One switch control really beautifully made precision instrument, size only 3 1/2 x 5 1/2 x 1 1/2 in., price only £5.19.6. Post free.

MODEL TP10. Similar in size and appearance to TP58, but sensitivity 2,000 ohms per volt, price £3.19.6. Post free.



Triple Purpose Auto Transformer

Ministry Reference 10K/143. This will convert 230 v. to 110 v. or 230 v. to 460 v. Use it also as a filament transformer 230 v. to 6.3 v. 5 amps, or 230 v. to 12.6 v. 3 amps. Price 12/6. Post and packing 2/6.

The J.B. Tangential Air Conditioner



The displacement caused by the new Tangential fan is quite amazing, but what is more amazing is the almost complete absence of noise. Stand the J.B. Air-Conditioner on a window ledge near an open window, and you can have either extraction of bad air, or input of clean, new air, depending upon which way you turn it. In addition to a fan for moving the air, the unit also contains a heater and control switch, wired such that 500, 1000 or 2000 watts of heating may be used. The total building cost is £7.10.0, plus 5/- carriage and insurance. The case is very nicely finished in hammered enamel, and when assembled, the unit is indistinguishable from those selling at £12 and more.

Ice-Stat

This is a small thermostat which cuts on and off at around freezing point. Has many uses, one of which could be an ice warning device to be fitted under your car. Price 7/6, Post 1/-.

ELECTRONIC PRECISION EQUIPMENT LTD.

• Orders received by post are despatched from our warehouse, Dent, 5, 46 Grove Road, Eastbourne, and to save time, please post your order to this address. Please include enough for postage. Callers, however, should use one of the following addresses:
520 High Street North 42-46 Windmill Hill 266 London Road 29 Stroud Green Road 246 High Street
Manor Park, E.12 Ruislip, Mddx. Croydon Finsbury Park, N.4 Harlesden, N.W.10




Trade News

New Receiver

THE model T.115c is a new receiver from Bush Radio Ltd. It has a 19in. picture tube with aluminised screen and electrostatic focus. It incorporates a switchable dual standard timebase as well as flywheel synchronisation. It is sufficiently sensitive to operate under fringe conditions and readily convertible by internal plug-in receiver and tuner units for UHF 625-line reception.

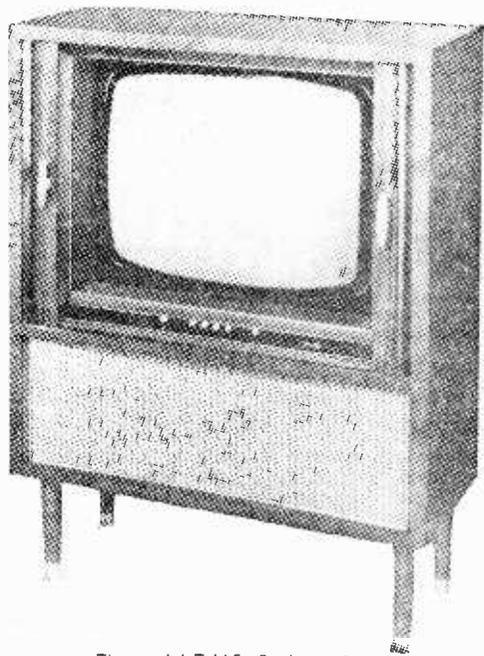
The T.115c is housed in a Walnut veneered cabinet with tambour doors and the price of this receiver is 81 guineas. The manufacturers are *Bush Radio Limited, Power Road, Chiswick, London W.4.*



The model T.115c Bush receiver.

New TV Aerial

A BATCH of aerials, suitable for use at UHF, has been manufactured by Belling and Lee Ltd. for reception of the test transmissions by the BBC from their Crystal Palace station. Although different aerials will be required to receive the London area service transmissions when they commence, these aerials will enable the potentialities of the coming service to be demonstrated. *Belling and Lee Ltd., Great Cambridge Road, Enfield, Middlesex.*

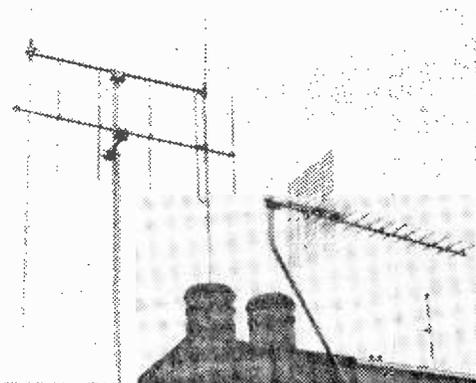


A Belling-Lee Band V aerial mounted beside standard Band I and III arrays.


New Range of Receivers

RECENTLY a new range of television receivers has been brought out by Murphy Radio Limited. The range consists of four Astra Mark 2 receivers each capable of conversion to 625-line/UHF standards. The Murphy conversion unit—incorporating a UHF tuner and 625-line I.F. strip—can be added to the bottom of all their sets now in production.

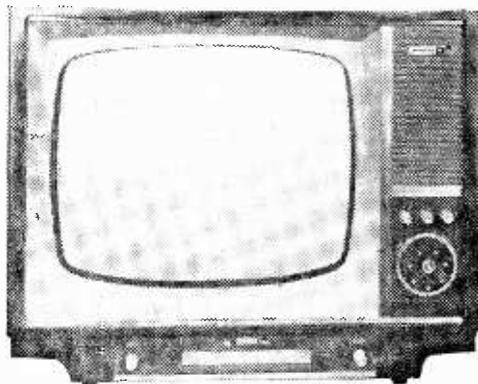The price of these new receivers ranges from £69 6s. to £88 4s. *Murphy Radio Limited, Welwyn Garden City, Hertfordshire.*



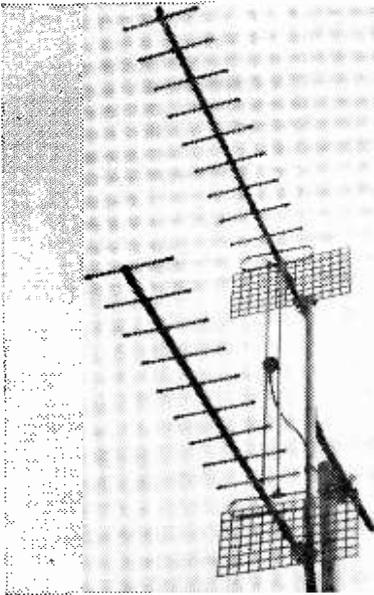
A Murphy receiver fitted with a 405/625 conversion unit at the base of the cabinet.



A new Aerialite aerial for UHF.

UHF Aerial

AMONGST the new range of aerials designed by Aerialite Ltd., for UHF test transmissions, is the model No. 45/D11, which is illustrated on this page. This is a high gain, wide spaced, wide stacked, medium band width type of aerial and is suitable for fringe area reception. It incorporates a broadband mesh reflector and is priced at £11 10s. The makers of this aerial are Aerialite Ltd., Hargreaves Works, Congleton, Cheshire.

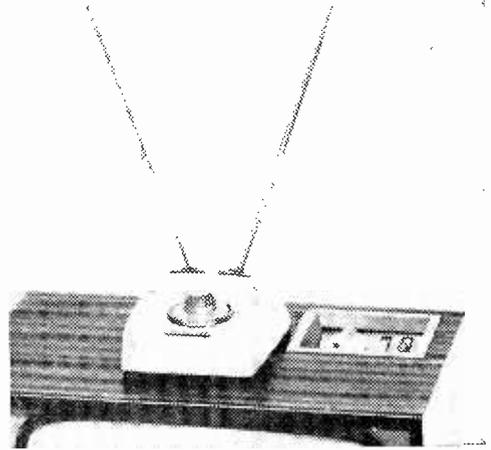

The new "Veemaster" set-top aerial made by Antiference Ltd.

Set-top Aerial

A NEW aerial for use on Bands I to V has been introduced by Antiference Ltd. The name of this aerial is the "Veemaster" and is made to be mounted on top of a television receiver.

The Veemaster incorporates a variable loading circuit which, in conjunction with the natural harmonic content of the elements, enables the aerial to be tuned to any channel in Bands I to V. Its telescopic elements, which have a wide range of adjustment, are chrome plated and isolated from the receiver.

The price of the Veemaster, complete with the lead and plug, is £3 10s. The manufacturers are Antiference Ltd., Aylesbury, Buckinghamshire.

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

SEND A "PRACTICAL" CHRISTMAS GIFT

★ Send your technical friends the ideal Christmas gift... a year's subscription for PRACTICAL TELEVISION. It's a present you know they'll appreciate. And each new issue will be a renewal of your best wishes... month in, month out, right up until Christmas 1963.

★ Simply send your friends' names and addresses, together with your own and remittance* to cover each subscription, to The Subscription Manager (G.1), Practical Television, Tower House, Southampton Street, London, W.C.2. We will despatch first copies to arrive before Christmas, and send an attractive Christmas Greetings Card in your name to announce each gift.

★ * RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES):—U.K. £1.8.0, OVERSEAS £1.6.6, CANADA £1.5.0.

★ ★ ★ ★ ★ ★ ★ ★ ★ ★

SERVICING TELEVISION RECEIVERS

(Continued from page 63)

event the feed resistor is often burned out and becomes open circuited, thus preventing that particular stage from working (resulting in no picture, no sound or both) or the resistor may drop in value to become a virtual short itself thus overloading the H.T. supply and causing a fuse to blow. In this case visual inspection will often reveal the charred resistor and the associated decoupling capacitor is then immediately suspect.

Picture Shift

A means of centring the picture on the screen is provided. Models T394 and T484 may be fitted with three screws on the focus magnet and the adjustment of these also affects the focus as well as moving the picture. Later models in the T301 series used two concentric knobs or a single shuffle plate lever. These adjustments have a considerable effect upon the setting of the ion trap magnet and the adjustment of one will affect the other. The only correct position for the ion trap magnet is that which gives maximum picture brilliance and the picture is lost completely if the trap magnet is moved more than a slight amount from its required position.



**BUILD THE
"REALISTIC" Seven**



The finest receiver at present available for home construction. Fully tunable long and medium wavebands.

Uses 7 Mullard Transistors, OC41, 2 OC45's, OC71, OC81D and 2 Oc81's, plus Crystal Diode OA70.

STAR FEATURES ★★

- ★ 7 Transistor Superhet. ★ 350 Milliwatt output into 4-inch flux speaker. ★ All components mounted on a single printed circuit board, size 5 1/2 ins. in one complete assembly. ★ Plastic cabinet, size 7 x 10 x 3 1/2 in. ★ Socket for car aerial. ★ I.F. 470 kc/s. ★ Ferrite Rod aerial. ★ Operates from PP9 battery. ★ Full data supplied with each Receiver. ★ All coils and I.F.'s, etc., ready wound.

Price of all parts and battery £6.19.6. P. & P. 4/6 (all parts sold separately). Instructions 2/6 (refunded if you purchase parcel).

LAST WEEKS! Rebuilding Clearance Sale

at 42 Tottenham Court Rd., W.1

OUTSTANDING BARGAINS IN RADIO AND T.V. RECEIVERS, COMPONENTS, ACCESSORIES, TAPE RECORDERS, MICROPHONES, VALVES, C.R.T.'s and INNUMERABLE ODDMENTS. FOR THE EXPERIMENTER, HOME CONSTRUCTOR, etc.

CALL EARLY. Your last chance to find the bargain you have been looking for.

LAST WEEKS!

NEW C.R. TUBES

All sizes in stock at lowest prices. 17in. from 79/6. Send for list.

FERRANTI 17in. type TR17/10. 6.3 v., 0.3 amp. heater. New and unused £5.19.6. Carr. & Ins., 12/6.

207 EDGWARE ROAD, LONDON, W.2.

PADdington 3271/2.

BOTH OPEN ALL DAY SAT.

Early Closing Thurs.

33 TOTTENHAM COURT ROAD, W.1.

MUSEum 2605

Mail Orders to Dept., P.T. Edgware Road.

Prices Slashed!

MAKER'S SURPLUS COMPONENT BARGAINS

- WIDE ANGLE 38 m.m. Line E.H.T. Trans. Ferroxx-9-16kV 12/6
- Scanning Coils 12/6
- Frame Output Transformer .. 5/-
- Frame or line block osc. Transformer 3/6
- Focus Magnets Ferroxx-core .. 7/6
- P.M. Focus Magnets, iron-core 6/6
- Duomag Focallisers 8/6
- 300 m/a Smoothing Chokes.. 7/6

REMOTE CONTROL UNITS

Comprising On/Off switch, Brightness and Volume controls. Controls are recessed into smart grey plastic case.



LASKY'S PRICE 14/11. LESS THAN HALF PRICE.

Six Section Telescopic Aerial 27in. open, 1in. projection when closed, chrome plated, strongly made. Ideal for transistor portables remote control models. Today's value 17/6. **Lasky's Price 7/11.**

Diamond

all-NEW T.V. replacement Tubes



BRITAIN'S FINEST—ONLY THE GLASS IS NOT NEW

- ★ RE-SCREENED
- ★ RE-ALUMINISED
- ★ FITTED WITH THE LATEST BRITISH GUN ASSEMBLY
- ★ GUARANTEED 12 MONTHS
- ★ ALL TYPES IN STOCK

Diamond TV Tubes revitalise your TV. Wonderfully improve definition and brilliance.

SPECIAL OFFER — LAB CRAFT

TRANSISTOR SIGNAL INJECTION PROBE

Quickly checks: Radio, TV Sound. All forms of Audio Ccts. Printed Wiring. Complete with long-life Mercury Battery. Price: £4.19.6. Cash with order, carriage paid.

DIAMOND ELECTRONICS CO.

and what Prices!

- 12" — £4. 10. 0
- 14" — £5. 5. 0
- 17" & 15" £5. 15. 0

ALSO 19", 21" and 23"
Carriage and insurance 7/6
C.O.D., C.W.O. or Proforma Invoice
10/- refund on your old tube.

Self contained. Completely safe. Light in weight. Wide frequency range. Use for rapid signal injection. Functions as a Wide-Band Modulated Signal Generator emitting a signal rich in AF, IF and RF components. Useful range: 2 Kc/s to 25 Mc/s.

Siron Works, 96a Wellington Street
MANCHESTER 18. Tel.: EAST 3669

TUBES

Guaranteed 12 mths.—Carr. Free by Passgr. train COMPLETELY REBUILT & RESCREENED

14" - - - £5. 5.0

15" - 17" - - £5.10.0

21" - - - £8. 0.0

BRAND NEW 12in MW31-74 £4.40

"Clarion" Transistor Battery Tape Recorder.

Capstan drive. Constant speed 3 3/4 i.p.s. Durable plastic case. Complete with mike and tape. Free illus. leaflet. List price 25 gns

Our 15 GNS. Price £5 Carr. 7/6

100 mixed resistors. 1W-2W, 6/8 P.P. 1/-.

Scan Culls, 90°, new. 10/8, P.P. 2/9

LINE OUTPUT TRANSFORMERS

Bush, TV 11A, B; 12A, B	.. 45/-
Cosor, 930, 931, 933, 4	.. 62/8
Ecko, TS146; TS113-114; T161	47/8
T221, 231, TS6311, etc.	.. 59/8
Ferguson, 841/2/3; 941-945	.. 59/8
990-8T; 103-146, 203 etc.	86/8
Ferranti, 14T3, 4; 17K3, 17T3, 4	45/-
14T2, T1205, 1215, 1225, 1325	85/-
G.E.C.-H.M.V. mostly	.. 55/- to 60/-
Murphy, V114, 116, 118C	.. 45/-
V129, 180, 200, 202C	.. 57/8
V240/250 94/-	V214/216 88/8
Phillips, 1114, 1115, 1437, 1446, 1726, 1746, 1747	.. 73/-
Pye, LV30, 16T, OS17, VT17	.. 69/8
CTM4 V4, VT4, VT, VT7	.. 55/-

Add post 3/6.

WESTWAY RADIO

S.A.E. with enquiries please.

5 Westward Way, Preston Road, Harrow, Middx.
Tel: WOR 2663

REBUILT TV TUBES

Complete New Guns—12 months' Guarantee

12in.	£3.10.0
14in.	£3.15.0
15-17in.	£4.0.0
21in.	£5.10.0

Old Tube required in exchange. Electrostatic Types 5/- extra. Carriage & Insurance extra.

NU-GUN TELETUBES 3 THE MEWS

Duckett Road, Harringay, London, N.4
Telephone: MOUNTVIEW 2903
Also various Ex Rental TV Sets available.

VALVES BY RETURN GUARANTEED 3 MONTHS

6CD8G	19/8	10C1	11/8	186BT	19/8	EY51	7/9	PL81	8/8	U24	16/-
6F1	4/8	10C2	14/8	EAF42	8/-	EY56	7/8	PL82	6/8	U25	11/8
6F12	3/-	10F1	5/8	EB41	7/-	EZ32	8/8	PL83	6/8	U26	9/9
6F13	6/9	10F9	10/8	EB51	3/-	K732	4/8	PL84	9/-	U31	7/-
6F14	9/8	10L11	14/8	ECV51	5/8	K738	12/8	PY31	9/-	U191	12/6
6F16	9/8	10P13	11/-	ECV52	6/-	PV54	6/9	PY32	10/-	U281	9/6
6L1	12/6	10P14	9/-	ECV53	6/8	PV55	8/9	PY30	6/9	U282	15/-
6L13	9/-	12SN7GT	7/8	EPF80	8/8	PCF50	7/-	PY31	6/8	U301	15/-
6L19	11/-	20F2	9/8	EPF82	8/8	PCF52	7/8	PY32	6/-	U301	19/-
6LD20	7/8	20L1	16/-	EPV80	6/-	PCV52	7/8	PY33	7/-	UCH42	7/3
6P25	8/6	20F3	12/8	EPF42	7/8	PL83	10/8	PZ50	9/8	UF42	5/8
6P28	12/6	20P4	18/-	EPF50-BR2/-	7/8	PL84	7/8	R19	11/-	UL41	7/-
6SN7GT	4/8	30F1	9/8	EPF80	4/9	PL33	8/3	SP61	2/8	UL44	11/-
6U4GT	10/8	30L15	9/8	EPF81	3/-	PL36	9/8	T41	7/8	U18	17/-
6V63	5/-	30P4	9/8	EL33	7/9	PL53	16/8	U22	6/9	Z68	9/8

Post: 1 Valve 6d.; 2-11 1/-; For full list see September issue.
TUBES—Guaranteed 3 Months: MW31 74 29/-; MW36/24 39/-; All Types: 12in. 2/-; 14in. 2.10/-; 17in. 2.35/-; Guaranteed 12 months: 12in. 2.35/-; 14in. 2.35/-; 17in. 2.40/-; 21in. 2.55/- (Carriage 12/6). 6 Page List 6d.

TECHNICAL TRADING CO.

DEVONIAN COURT, PARK CRESCENT PLACE, BRIGHTON

JUST PUBLISHED

A comprehensive guide for engineers, technicians and home constructors

HIGH FIDELITY POCKET BOOK

by **W. E. PANNETT**
A.M.I.E.E.

This addition to the Newnes' series of Pocket Books brings together comprehensive information on all aspects of high fidelity sound reproduction in the home. The clear explanations of the various factors affecting the quality of sound reproduction will appeal to engineers, technicians and dealers who have not previously specialised in this field. The home constructor and music lover will also find much practical information on obtaining the best results from audio equipment. A glossary is included so that the book can be readily understood by those readers with only a little technical knowledge. The book ends with a selection of useful data including valve data, information on Colour codes, the use of the decibel, etc.

CONTENTS

Production and Propagation of Sound—Sound Reproduction—Power Amplifiers—Control and Pre-amplifier Units—A.M. Radio Tuners—F.M. Radio Tuners—Loudspeakers—Loudspeaker Enclosures—Disc Recording and Reproduction—Stereophonic Disc Recording and Reproduction—Magnetic Tape Recording—Power Supply Units—Useful Data—Glossary—Index.

320 pages

extensively illustrated

A mass of detailed data and diagrams for only 40s.

FROM ALL BOOKSELLERS

... or, in case of difficulty, at 42s. by post from **GEORGE NEWNES LTD.**, Tower House, Southampton Street, London, W.C.2.

NEWNES

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents

SPECIAL NOTE: Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

TV SET TO 'SCOPE

SIR,—With reference to the problem of G. J. Powell in the September issue concerning the conversion of a TV receiver to an oscilloscope, I should like to say that a friend and I completed exactly such a task some time ago.

The receiver we used was a 9in. Bush model. We started by stripping the complete chassis with the exception of the EHT unit (line oscillator and line output valve, etc).

We next had to build an oscillator suitable for scanning the oscilloscope. Our lack of knowledge forced us to copy the frame oscillator of a television receiver. The output valve of this system was fed to the line coils. Several transformers were tried and the most suitable selected for matching the output valve anode circuit.

Next we constructed an audio amplifier with gain and feedback controls for stability. This took the form of a single output stage and this was then coupled to the frame coils.

The chassis required no new drilling. The controls were kept as simple as possible. The finished product of this work was a basic 'scope, suitable only for audio frequencies, but which was capable of having further modification.

We have, in fact, replaced the cumbersome EHT unit by a mains EHT transformer, etc.

One point to note is that the line coils, until they are disconnected, act as a load, and a load for the line output transformer may be required if the original EHT unit is to be retained.—G. RAINEY (Cheltenham).

TV SOUND

SIR,—I see on the Data Chart, given away in your October issue, that both the American and European systems for transmitting television employ F.M. sound, while in this country we have to make do with A.M. Although, when one's concentration is mainly centred on the television screen and the audio side of things is taken for granted, how often a good TV show would be made better if the sound were of a higher standard.

Of course, the poor quality of the sound cannot be blamed entirely on the transmitting authorities. The miniature loudspeakers employed in most receivers nowadays must account largely for the poor reproduction of TV sound. I consider this a pitiful economy on the part of the manufacturers and one which could well be dispensed with to the advantage of their sales.

Although I have heard nothing to indicate it, I only hope that the forthcoming changes to our television system will include provision for improvements in the transmission of sound.—D. B. WILLIAMS (Cardiff).

POST-PILKINGTON

SIR,—Now the Press has had a go at the Pilkington report, please let me have my say. As far as I can see the report, as far as colour is concerned, is more or less OK, but the rest of it on extra channels and so forth is so much eyewash. It is too obvious, isn't it? Let's divorce colour entirely from the arguments raging and get on with it, for having colour reception on UHF and 625 lines won't make any moral difference at all. This old diaphragm story of colour not being cheaply available for the public is not or need not be true; that is if certain electronic industrialists stop pouring out their negative propaganda. I for one am working very seriously on an experimental colour chassis. I will build my own motorised UHF "bow-tie" loft aerial and match it up through a UHF booster via a 300Ω twin low-loss feeder.

A good many suitable components are already available if one only takes a little trouble to look. The tricolour kinescopes will become available and a good ham should be able to produce his set at a fraction of the cost of those new ones which will sell far above the price which they are worth. The 300Ω ribbon antenna lead is available at a very reasonable cost and is quite suitable for experimental work and those people who are near the first UHF transmitter need not worry about booster stages.—K. R. CRASKE (Lincoln).

SOUND-ON-VISION

SIR,—Referring to "Your Problems Solved", July *Practical Television*, and the letter from Mr. K. Taylor on the K.B. QV20, if, after adjusting L36, sound-on-vision is not cured or adjusting L36 has no effect, I would suggest the replacement of C42 and C43, both 120pF 5% capacitors, as in several of these sets and other K.B. models these capacitors develop a leak, causing this effect. These capacitors are in the can containing the sound rejector coil. Also check the continuity of the coil.

In one particular set (a QV40) these capacitors, and the coil were OK. Also the alignment of the set was in order. A cure was not effected until the main electrolytic capacitor 100+400μF was replaced.

The 400μF section had reduced in value to 105μF. It is wise to check this component with a parallel capacitor of about 200μF if no fault can be found with the rejector coil circuit.—S. WHITTON (Buckingham).

TELEVISION TECHNICIANS LINE OUTPUT TRANSFORMERS SCAN COILS ETC.

LABORATORY TESTED

ALBA: T301, T304, T394, T434, T494, etc.	46/6
BUSH: TV11A, 11B, 12A, 12B, TVG12A, 12B, TRG12A, 12B	44/-
TVG26, TV32, TV33, TVG34, TVG34A, T36, TV36, TVG36, TV36C, TVG36C, TV43	88/8
TV58, TV56, TV57, TV58, TV62, TV63, TV66, TV67, etc.	94/-
TV80 with EY31	109/-
COSSOR: 930 and T931, 933-45, 937, 938A, and F, 939 and A and F	81/6
943T, 940-946, 945, 945B	58/6
954F, 947, 948	68/6
DECCA: D17 and C	68/6
DM1, DM3C, DM3, DM4C	74/-
DMS, DM14, DM17, 44, 555	74/-
DEPIANT: TR1463, TR1753	58/8
DYNATRON:	
EKCO: T893, TC8102, TS105, TS114, TRC124, TV138, TS188, TS193	54/-
TR139, TC140, T141, TV142	78/6
T161, TC162, T164, T165, etc.	78/6
TC208, TV209, T231, T221, T231F, T248, T253, T254, T293, etc.	58/8
FERGUSON: 1037, 1057, 1137, 1307, 1457, 9411-9533 inclusive	58/8
9917-997T inclusive	68/6
203T-246T inclusive	68/6
306T, 305T	94/-
FERRANTI: 147S, 1473F, 137A, 17K3 and F, 1773 and F	47/6
17K4 and F, 178K4 and F	47/6
17T4 and F	47/6
147S, 178K5, 17K5	47/6
G.E.C.: BT1251, BT1252, BT1746, BT1745, BT1743	48/6
BT4643, BT5147, BT5240-48	88/6
BT5348-BT5643R inclusive	48/6
H.M.V.: 1824 and A to 1891 inclusive 1340, 1341, 1342-1343	88/6
All models available	88/6
INVICTA: A118, T119, T120	54/-
All other models available	
K.B.: LP750, LP750, LP760, MV60	108/6
All models available	
MARCONI: All models available. MASTERRADIO: Most models in stock. MICHAEL: Most models in stock. MURPHY: V200, V295	58/6
V240, V250	94/6
PETO SCOTT, PHILCO: Most models in stock. PAM: 908, 909, 952, 953, 955	54/-
PHILIPS: 1788U, 2168U	104/-
1100F, 1207F, 1217F	74/-
122GU, 1236V, 1238V	74/-
114UF, 114UM, 115U	74/-
1437U, 1446U	74/-
Most models in stock	
PILOT: Most models in stock. PYE: CTM4, FV4C, FV4COL	54/-
V4, VT4, V7, VT7	54/-
LV30, FV1, FV10	88/6
CS17E, CTM17C, CW17	88/6
CW17C, CW17CP, CW17K, etc.	68/6
Most models in stock	
RAYMOND: Most models in stock. REGENTONE: All models available. R.G.D.: 6017T, 654, etc.	58/6
Most models in stock	
SOBELL: TS17, T346	64/-
Most models in stock	
STELLA: ST5721U	104/-
ST8017U, ST8021U	104/-
ST8017U	104/-
ST6414U, ST6417U	74/-
ST8314U	74/-
ULTRA: 86 series, 185 series, with U25, etc., complete	78/6
Most models in stock	
VIDOR: CN4217-CN4231 inclusive	84/-
Post and Packing 3/6	
Also Used U.P. Trans., Scan Coils, etc. ALL GUARANTEED 90 DAYS (All enquiries S.A.E.)	

WYNDSOR TELEVISION TECHNICAL DIVISION

ST. ALBANS RD., BARNET, HERTS.
BAR 1769

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager "Practical Television", Tower House, Southampton St., London, W.C.2.

SETS & COMPONENTS

BARGAIN OFFER

T.V. Tuners. 10, 16 and 38 M/c.s. Brand new, less valves, 19/6, carriage paid. Valves if required, PCF80 and PCC84, 16/- pair.

OSBORN (ELECTRONICS) LTD.
382 Brockley Road, Crofton Park, S.E.4.

A.1 POST FREE BARGAINS. EB91, EF50, EF80, EF91, 10F1, 6F1 9d, each five for 2/6 (mixed). PY82, PL38 4/6, P230 4/-. Speakers 6in. 7/6, 8in. 6/6, 10in. x 6in. 15/-. "Primax" 60W twin light solder guns 92/6. Morse Keys 3/-. All Mullard B.V.A. Transistors and valves stocked. All previous bargains available. A.1 RADIO COMPONENTS, 14 The Borough, Canterbury, Kent.

The K.E. rebuilt tube—your Scottish Re-gunner

12-14in. £4.17/6 } 12 months' guarantee
17in. £5.10/6 } allowance on old tube
21in. £7.10/6 } Free transit and insurance
Cash or cheque with order or C.O.D.
Top quality coaxial cable 9d. per yd. or £2.10s. per 100 yards. Aerial clamps 1in. x 1in. 3/6 each. plus post and packing 1/-, 2in. x 2in. 5/6 each. plus post and packing 1/- (1 doz. or more postage free)
TRADE ENQUIRIES INVITED
FOUntainbridge 3836

H. KINNEAR ENTERPRISES LTD.

25 St. Peter's Place, Edinburgh 3

NEW VALVES, 6 months' guarantee!
ECC81/23, EF80, PY82, EB91 4/11; EY61, EY86, ECL80, PCF80, E281, 7/9; U25/U26, 0/30L2, PCL82, PL81, 9/11; 30L5, R19, PCC83, PL36, 30P4, 12/6; U801, 6CD6G, 50CD6G, 20L1, 20P4, U37 18/-.

P. BEARMAN (TUBES)

3 PARK AVENUE, NEW BARNET, HERTS.
Tel: Bar 1934

TELEVISION TUBES

TWELVE MONTHS' GUARANTEE		
12in. MW 31-74 etc.	£3.0.0
12in. CRM 121 etc.	£4.0.0
14in. MW 36-24 etc.	£5.0.0
14in. CRM 141 etc.	£5.5.0
15in. CRM 152 etc.	£5.10.0
16in. MW 41-1 etc.	£6.0.0
17in. MW 43-69 etc.	£6.0.0
18in. C 19A etc.	£7.0.0
19in. AW 53-85 etc.	£7.10.0
21in. 23 SP4 etc.	£9.0.0

and ALL other types available.
Deposit £2 and £1 monthly carriage 12/6.
ALL orders despatched British Railways Passenger

NEW 17in. 625 line 110 Chassis, Ferguson export model 6400. Complete with valves, data sheet, circuit, diagram. £15.0.0
17in. AW 43-88 to suit 6400 £8.0.0

CATHODE RAY TUBE SERVICE
35 Broomwood Rd. ST PAUL'S CRAY, Kent.
Orpington 212

TELEVISION TUBE SHOP

We have the following
Unused, Guaranteed Tubes
in stock now

Carriage up, but prices down.

AW36-20, 21	£5. 2.6
AW36-80	£5. 7.6
AW43-80, 88	£6. 7.6
AW53-80	£7.12.6
C12A, C12B	£4.12.6
C14BM, FM	£5. 5.0
C17BM, FM, FM	£6. 7.6
C17LM, PM, SM	£6.12.6
C21 HM, SM, TM	£7.17.6
CME1402	£5. 7.6
CME1702, 1703	£6.12.6
CRM91, 92	£4.12.6
CRM93	£4. 2.6
CRM121, 2, 3, 4	£4.12.6
CRM141, 2, 3, 4	£5. 7.6
CRM152, 153	£5.12.6
CRM171, 2, 3	£6. 7.6
CRM211, 212	£7.17.6
MW6-2	£5.12.6
MW22-16	£4. 2.6
MW31-16, 74	£4. 2.6
MW36-24, 44	£5. 2.6
MW41-1	£6.12.6
MW43-64, 69	£6. 7.6
MW43-80	£6. 7.6
MW53-20	£7.12.6
MW53-80	£7.12.6
T901A	£6.12.6
14KP4A, 141K	£5. 2.6
171K, 172K, 173K	£6. 7.6
6901A	£6.12.6
7201A, 7203A	£5. 2.6
7204A	£5. 5.0
7401A	£6. 7.6
7405A	£6.12.6

All tubes tested before despatch and guaranteed for 12 months.

CARRIAGE 7/6, via B.R.S. or 12/6 via passenger train.

TERMS £2 down balance £1 per month.

Just arrived! Brand new 19 & 23in. tubes, will replace existing 17in. and 21in., 110° types. Prices: £9 and £12 respectively.

Shop Soiled Tubes (unused)

(Subject to Availability)
12in. 3/18, 3/31 45/-. Others 57/6
14in. CRM141, 2 67/6. Others 57/6
17in. CRM171, MW43-69, 43-64, 75/- Plus Carriage. Guaranteed for 12 months.

TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD
S.W.11
BAT 6859
South of the Bridge. Open Sats.
until 4 p.m.

SETS & COMPONENTS,
(continued)

"HEATHKITS" can now be seen in London and purchased on H.P. Free Brochure. **DIRECT TV REPLACEMENTS LTD.**, 138 Lewisham Way, SE14. TID 6666.

TV SPARES

LINE OUTPUT TRANSFORMERS

TELEPHONE ORDERS SENT SAME DAY C.O.D.

Ekco T221, 231, 311, 284, 330, 283, TC208, TU209, T248, TC267, all 55/-.
Ferranti T1001, T1002-5, etc., 55/-.
Murphy V240/250, 62/6; V270/280, 77/6.
Pye VT4, VT7, V14, & Pam 906-53, 50/-.
H.M.V. 1840-9, 2805-5902, only 60/-.
Ferranti 14T3/4/5/6, 45/- 14T2, 62/6.
Bush TV53, 79/6; TV24C, TV80, etc., 89/6.
Phillips 1768U, 92/6; 1114-5, 1437-46, 89/6.
Decca DM14, DM3C, 65/-; D17, D14, 65/-.
Masteradio T917, TE7T, T409-12, etc., 75/-.
Alba T301, 304, 394, 484, 494, 42/6.
Cosor 930-8, 58/6; Ferg. 992-8, 62/6.
Baird P2014/7, P2114/7, 59/6, etc.
L.O.P.T.'s For ANY MAKE and MODEL supplied. USED trans., often available ask for quote. SCAN COILS.

Ekco T221, T231, etc. 55/-, Pye VT4-7, 50/-, 110 doz. Conversion Kits only 125/-, including L.O.P.T., F.O.P.T., Scan Coils.

TV & RADIO PARTS

Ceramics all values, 9d. to 11d. each.
High Voltage Pulse Ceramics, 1/6 ea.
Silver Mica Capacitors all values, 1/-.
Carbon Resistors, 1/4W., 5d. ea. 1W 2/ ea.
Wire Wounds, 15 ohm to 8.2K, 2/- ea.
Mains Dropper Resistors, all makes, 7/6.
Volume Controls Midget, 4/6, with SW, 6/9.

Pre Set Controls, all values, 4/- ea.
Mains Trans. 250-0-250, 6.3V., 5V., 39/6.
C.R.T. Isolation and Boost Trans., 15/-.
7/4 Elliptical Speakers, only 7/6 ea.
Auto Trans. 50W, 30/-, 100W, 50/-, 150W, 4/4.

EL84. Sound O.P. Trans. 50/- (scr Taps).
Any Match Sound O.P. Trans., 15/- ea.
Miniature Sound O.P. Trans. (DL94) 7/6.
Transistor Trans., ask List, 9/6 to 17/6.
Microphone Trans. 65 to 1. Screened 49/6.
465 Kcs. I.F. Trans. 2.5in. X 1, 25in. 25/- pr. Midget version above, 465kcs, 25/- pair.

Midget 10.7 Mcs. I.F. Trans., 11/- ea.
Smoothing Chokes, 10, 20, 40, H., 21/-.
Ion Traps to suit any Tube, 5/- each.
Silicon Rectifiers. 250V., 350ma., 25/-.
Vibrators, 6 volt, 12 volt, 39/6, 4 Pinux.
Vibrator Trans. 275-0-275, 6/12, 37/6.

Motor Supp. Capacitors, 5/1.0 5/3.
Cut-Lead Supp. Fit. any car, 2/9 ea.
Wavechange Switches, 4P. 3W, etc., 6/3.
Dolly Switches, D.P.D.T., etc., 5/6 ea.
Glass Fuses, 1, 2, 3, 1in., 1 1/2, 4/9 dozen.

Valveholders, any type (low L), 1/6.
Above Screened, 87C, 89A, 15/- per doz.
Crocodile Clips, Min./Stan. 7/6 doz.
Silicone Grease, 13/6 per Tube, 2 oz.
Electrolube, 39/6 Bottle, 16/6 Tube.
Component Storage Drawers, 13/6 doz.

Control/Instrument Knobs, 1/- to 5/-.
We can supply any small part please let us know your requirements.
Callers welcome. Open all day Saturday.
Terms: C.W.O. or C.O.D. Post and Pack., 3/6.

TELEPHONE ORDERS SENT SAME DAY C.O.D.

TELEVISION CONSUMER SERVICES LTD.

112 Camberwell Road, S.E.5
RODney 7917

SETS & COMPONENTS,
(continued)

NEW AND SURPLUS VALVES, fully guaranteed from 3/6 each. Also transistor Portable Radio Kits. We are specialists. S.A.E. for lists. Many bargains. LEWIS. 46 Woodford Avenue, Gants Hill, Ilford, Essex.

TUBES-AERIALS-VALVES

Regunned tubes, guaranteed one year, full range of aerials and fittings, I.T.V. boosters, valves, brythead tuners, TV sets, transistor radios and all electrical appliances. Co-axial cables and house wiring cables. Fluorescent fittings. All quotations without obligation. Special terms to the trade and Home Engineers. S.A.E. for Catalogue.

G. A. STRANGE

BROADFIELD, NORTH WRANHALL, NR. Chippingham, Wilts. Tel. Marshfield 236

TV VALVES, boxed, used, but guaranteed: PCC84, PCF80, PY32, 20P3, 6/30L2, PL81, PL82, PL83, PL84, PCL82, PCL83, 30L15, PCC89, PY81, PY33, ECL90, ECC82, 20F2, 20L1, 30P12, 3/6 each. 6 for 41, postage 1/-. K. BARTON, 100 Evelyn Road, Dunstable, Beds.

AERIALS

Do-it-Yourself

TV AERIALS

guaranteed complete with instructions.
B.B.C. Normal 44/- Fringe 59/-
I.T.V. 36/- " 54/-
V.H.F. radio aerials 34/-

State Channel Required—Post free c.w.o. Price list, masts, brackets etc. s.a.e.

T.M.S., 8 Seymour Street, Cambridge

MISCELLANEOUS

MUSIC and Musical Accessories. Catalogue 1/-. Agents wanted. DARWINS, 19 George Street, St. Helens, Lancs.

WANTED

WANTED: NEW VALVES and Transistors. any quantity. S. N. WILLETS, 43 Spon Lane, West Bromwich, Staffs. Tel.: WES 2392.

A PROMPT CASH OFFER for your surplus brand new Valves and Transistors. R.H.S., Beverley House, Mannville Terrace, Bradford 7.

NEW VALVES WANTED EY51, ECL80, PCC84, PCF80, PCL93, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. DURHAM SUPPLIES, 175 Durham Road, Bradford 8, Yorks.

VALVES WANTED IMMEDIATE CASH SETTLEMENT

must be new

Phone, write or call—
RADIO FACILITIES, LTD.
38 Chalcot Road, London, NW1
PRImrose 9090
THE VALVE SPECIALISTS

FOR SALE

METAL RECTIFIERS

RECTIFIERS—CONTACT COOLED
14RA1282 (FC101) type 250 v., 250 mA, 18/6;
14RA1283 (FC21) type 250 v., 300 mA, 17/6;
350 mA, 19/6; ECI 15/-.

RECTIFIERS—FIN TYPES
Equival. for RM4 250 v., 250 mA, 18/6; RM5 250 v., 300 mA, 17/6; 14A89 400 mA, 18/6; 14A86 16/6; 14A97 19/-; 14A100 22/6; 14A949 20/-; LW7 17/6; LW15 20/-; EKC 26/-.

MULTIMETERS 39/6
FROM

H1, 39/6; M1, 22.14.0; A10, B20, TE-10, ITI-2-20,000 O.P.V., 25.5.0, M7955, etc.

Stamped envelope for full latest selection and bargain offers.

Under £1 P. & P. 6d., over £1 Post Free. C.O.D. 2/6.

DURHAM SUPPLIES

175 Durham Road, Bradford 3, Yorkshire

TV TUNERS. Ex-equipment, all I.P.S. less valves 12/6 including postage.

Speakers Ex-TV and radios, 7/6 including postage.

Valves. EF80 1/6 each. ECL80 2/- each. PY82 2/- each. ECC82 2/- each. 10F1 2/- each. Thousands of other valves in stock. All tested before dispatch. Postage 6d. per valve orders over 10/- post-free. Send for our bargain list 9d. CAPITAL TELEVISION, 55 Honor Oak Park, London, SE23.

Star TV Tubes
70/-

all sizes up to and including 17in. incl. old glass, or plus 7/6 without

C.W.O. Carriage 7/6

WHY PAY MORE

new guns, 12 months' guarantee

also 20/- each

12in. 14in., Part Exchange Televisions

Callers only

ARTHUR SLARK

43-45 Thicketford Road, Tonge Moor Bolton

Phone: 26684

VALVE CARTONS at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a Godwin Street, Bradford 1.

12 VOLTS CONVERTOR TO 250 VOLTS Run 1/4 for sample and list. J. & A. BOXMAKERS, 75a Godwin Street, Bradford 1.



BRAND NEW tested, Inwater-proofed cartons. ONLY 32/6, cart. 7/6 (feen only). (DEPT. 10, J. T. SUPPLY, 309 Meanwood Road, Leeds, 7.

(Continued on next page)

SALVAGED VALVES TESTED ON A MULLARD HIGH SPEED VALVE TESTER

- AC/P 2/6
- B36 2/6
- B329 4/-
- D1 2/6
- D53 2/6
- D77 2/6
- DAF91 4/-
- D104 2/6
- D14 2/6
- DF91 4/-
- DH77 4/-
- DR91 4/-
- EAS9 1/3
- EB34 1/3
- EB41 1/3
- EB333 2/6
- EB44 4/-
- EB33 2/6
- EB34 2/6
- EB38 4/-
- EB32 4/-
- EB30 1/3
- EB30 2/6
- EP91 1/3
- KT33C 1/3
- KT61 2/6
- KT241 2/6
- KT61 2/6
- N308 4/-
- N329 4/-
- N339 4/-
- N369 4/-
- N379 4/-
- P41 2/6
- P61 2/6
- PC984 5/-
- PCF80 5/-
- PCF82 4/-
- PL83 5/-
- PEN46 2/6
- PEN46 2/6
- PL33 4/-
- PL31 5/-
- PL32 4/-
- PL83 4/-
- PL84 4/-
- PY31 4/-
- PY81 4/-
- PZ30 2/6
- SP41 1/3
- SP42 2/6
- SP61 1/3
- U31 4/-
- U51 4/-
- U329 4/-
- UF42 2/6
- VP4 4/-
- W7 2/6
- Z63 2/6
- Z66 2/6
- Z77 1/3
- Z90 1/3
- Z719 2/6
- 4TFB 2/6
- 8AL5 2/6
- 6AM6 1/3
- 6BW7 4/-
- 6BS6 2/6
- 6C5 4/-
- 6D6 4/-
- 6F12 1/3
- 6F13 1/3
- 8J5 2/6
- 6J7 2/6
- 6P25 2/6
- 6P25 2/6
- 8D3 1/3
- 9J6 2/6
- 10F1 4/-
- 10P13 4/-
- 10P14 2/6
- 12BH7 4/-
- 20P2 4/-
- 20P1 2/6
- 20P3 4/-
- 20P5 4/-
- 25L8 2/6
- 30L1 5/-
- 30L15 5/-
- 30L1 5/-
- 30PL1 4/-
- 30PL13 4/-
- 32 2/6
- 42 2/6
- 43 2/6
- 807 4/-

EXAMPLES
FULL CATALOGUE 9d.

VALVE HOLDERS
 American Octal ... 5/- doz.
 Noval ... 9d. each.

RESISTORS
 Card of 1W Resistors, 72 valves covering complete 10% range.
 Full range of separate Resistors, Condensers, etc.

VARIABLE CONDENSERS
 3-50pf concentric trimmers 3/- doz.

GEC CRTS (SALVAGED)
SPECIAL OFFER
 12in. G.E.C. 7102 10/- ea.
 Personal Callers Only

35 M/cs, 16 M/cs, 10 M/cs INCREMENTAL OR TURRET TUNERS LESS VALVES, EN-RECEIVERS 12/6.

We can often supply for the actual test you want the tuner to fit. But cannot guarantee what channels are fitted.

TRANSFORMERS
CRT Boost Transformers.
 2V, 4V, 6V, 10V, 13V
 State which required. 12/6 ea.
 Heavy Duty Output Transformers, 6 ratios from 13:1 to 43:1 ... 25/- ea.
 Miniature Output Trans... 3/9ea.
 Standard Output Trans... 10/-ea.
 Transistor Driver: 1-1 CT 10/-ea.
 2.5-1 CT 12/6ea.
 Transistor Output: 0-1 CT 10/-ea.
 9-2-1 CT 10/-ea.

Microphone Transformers,
 ratio 65:1 ... 35/-ea.

L.F. TRANSFORMERS
 Standard 465 kc/s ... 12/6 per pair
 Midget 465 kc/s ... 16/- per pair

AUTO TRANSFORMERS
 250W ... 67/6 ea.
 100W ... 27/6 ea.
 50W ... 20/- ea.

TRANSISTORISED FAULT FINDER
 Enables faults to be located quickly. Consists of a 12w Transistor, multi-vibrator in a box. Complete with battery. 32/6.

CRYSTALS
GENUINE MULLARD. Boxed.
 OA5 8/- OA81 3/-
 OA70 3/- OA85 3/-
 OA79 3/- OA91 3/6

TRANSISTORS
 OC16W 48/- OC75 8/-
 OC19 48/- OC72 8/-
 OC26 25/- OC76 8/-
 OC44 11/- OC78 8/-
 OC45 10/- OC81 8/-
 OC50 8/8 OC82 18/-
 OC71 6/8 OC170 17/6

TERMS: C.W.O. or C.O.D.
 Orders under £1, P. & P. 1/3.
 Open till 11 p.m. most days.

3d. stamp for list or 9d. for full catalogue
 Dept. PTA
Arion Television
 Maxted Road, S.E.15 NEWX 7152

FOR SALE
 (continued)

1,000 TELEVISIONS. all makes. from 23 working. 10/- not. Callers only. 9 till 6, including Sats. 39 Whitehorse Lane, Stepney, London.

BAND NEW adjustable Steel Shelving 73in. high by 34in. wide by 12in. deep. stove enamelled dark green. Sent unassembled. Six-shelf bay £3/15/-. Sample delivered free. Quantity discounts. N. C. BROWN LTD., Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

BOOKS & PUBLICATIONS

FIND TV SET TROUBLES in minutes from that great book "The Principles of TV Receiver Servicing". 10/6 all book houses and radio wholesalers. If not in stock from: Secretary, I.P.R.E., 20 Fairfield Rd., London N8.

A BRAND NEW Down-to-earth PRACTICAL BOOK for the EXPERIMENTER AND SERVICE MAN.

RADIO AND TELEVISION 25/-
 TEST INSTRUMENTS

Learn how test instruments work! how they are made! how to connect them and —MOST IMPORTANT—the results to expect on normal and faulty circuits. By post (please add 1/3d. for P. & P.) from **GORDON J. KING,** "Kingsford", South Furzeham Road, Brixham, Devon.

SERVICE SHEETS

WHY TOLERATE DELAY when we can supply your Radio or TV Service Sheet by return of post at 4/- each, plus postage. List 1/-. Also Manuals for sale and hire. List 1/-. S.A.E. with inquiries please. Mail orders only to S.P. DISTRIBUTORS, 44 Old Bond Street, London, W1.

SERVICE SHEETS (30,000). 3/- each with S.A.E. DARWIN. 19 George Street, St. Helens, Lancs.

SERVICE SHEETS

For all makes of Radio and Television—1930-1962. Prices from 1/-. Free fault-finding guide with all Service Sheets. Please send S.A.E. with enquiries. Catalogue of 6000 models. 1/6.

Special offer of 125 Radio/TV Sheets covering many popular models, 20/-.

HAMILTON RADIO
 Western Road, St. Leonards, Sussex.

SERVICE SHEETS. Radio and TV 4/- each. List 1/-. All orders dispatched on day received. Also Manuals for sale and hire. List 1/-. S.A.E. please. **SULTAN RADIO,** Panfles Chambers, Tunbridge Wells, Kent.

FAULTFINDER FILES, showing common faults that each receiver is prone to and other useful servicing information 2/- each. List 9d., plus postage. Mail orders only. S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

SERVICE SHEETS
 (continued)

SERVICE SHEETS; also Current and Obsolete Valves for sale. **JOHN GILBERT TELEVISION,** 1b Shepherd's Bush Road, London W6. Tel.: SHE 8441. Nr. Goldhawk Road Station.

GENUINE SERVICE SHEETS. Radio/TV/T Recorders. S.A.E. please to: **REDWATT TUBE DISTRIBUTORS,** 41 Denmark Street, Wakefield, Yorks.

SERVICE SHEETS. Radio. TV. 5000 models. List 1/-. S.A.E. enquiries: **TELRAY,** 11 Maudland Bk., Preston.

SITUATIONS VACANT

UNITED KINGDOM
ATOMIC ENERGY AUTHORITY
ATOMIC ENERGY
ESTABLISHMENT, WINFRITH

Electronic Instrument Mechanics

A.E.E. Winfrith require experienced men with knowledge of electronic equipment and/or industrial instrumentation for fault diagnosis, repair and calibration of a wide range of instruments used in nuclear reactors and associated experiments.

Men with Services, Industrial or Commercial backgrounds of radar, radio, television, industrial or aircraft instruments are invited to write for further information. Training in Specialised Techniques is provided for successful applicants having suitable background.

Married men living beyond daily travelling distances may be eligible for housing and this will be determined at time of interview. A lodging allowance is payable whilst waiting for housing. Working conditions are good and include sick pay and pension schemes.

Application forms may be obtained by sending a post card quoting your name, address and the reference EL/INST/NAT to **THE LABOUR DEPARTMENT,** A.E.E., Winfrith, DORCHESTER, Dorset.

EDUCATIONAL

TV AND RADIO problems solved by experts. Faults on manufacturers or constructors sets given personal attention with advice on fault finding methods and spares. Box 34.

f's MADE

By repairing Radio and TV Sets as a job or as a spare time business. Our practical course will show you the way. No previous experience is required.

SEND FOR FREE BOOK TODAY!

RADIOSTRUCTOR
 Dept. G73 READING, BERKS.

(Continued on next page)

EDUCATIONAL

(continued)

"HOW AND WHY" of Radio and Electronics made easy by a new non-maths practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from: Dept 12, P.T. RADIO-STRUCTOR, Reading.

THE INCORPORATED Practitioners in Radio and Electronics (I.P.R.E.) Ltd. Membership Conditions booklet 1/-. Sample copy of I.P.R.E. Official Journal 2/- post free. Secretary, 20 Fairfield Road, London N8.

Just published in a new revised 2nd edition

The fully-revised second edition of this popular pocket manual and data book contains much new information. Of particular interest will be the practical guidance on the servicing of transistor receivers and the repair of printed wiring panels.

The sections on servicing and aligning V.H.F./F.M. receivers have been expanded; car radio receivers, the suppression of car electrical interference, and record reproducers (including stereo reproduction) are all dealt with in greater detail.

RADIO SERVICING POCKET BOOK

Apart from the basic sections on modern radio circuits, much useful information is given on servicing instruments, fault-finding and alignment, aerials and electrical interference suppression, gramophone electrical mechanisms and pick-ups. In addition, some 35 pages of tabulated reference data includes valve base connections and equivalents, transistors and crystal diodes, B.B.C. and European broadcasting stations, battery equivalents, wavelength-frequency conversion, etc.

edited by **J. P. HAWKER**

In short, this book provides the essential information and data needed in the day-to-day work of servicing the whole range of modern A.M. and V.H.F./F.M., valve and transistor radios.

Experienced engineers, trainees and newcomers to servicing work will all find that this book shows an understanding of their real needs, and will repay its cost time and time again.

Only 12s. 6d. from all booksellers

... or, in case of difficulty, 13s. 6d. by post from **GEORGE NEWNES LTD.**, Tower House, Southampton Street, London, W.C.2.

NEWNES

Better, Brighter Picture Tubes

BRAND NEW THROUGHOUT—excepting glass

12in. £4.10.0 14in. £5. 5.0
15-17in. £5.15.0 21in. £7.15.0

New Silver Screen and Aluminiuming. All makes Mullard, Mazda, Emiscope, Cossor, Brimar, Emitron, etc.

REBUILT MULLARD AND MAZDA TUBES

12in. £3. 0.0 14in. £4. 0.0
15-17in. £4.10.0 21in. £6.10.0

All Tubes Fully GUARANTEED 12 MONTHS. Dispatch same day. Cash with Order. Carriage and Insurance 10/-.

S.T.S. Ltd.

35 POUND STREET, CARSHALTON, SURREY
Telephone: WALLINGTON 9665

RES/CAP. BRIDGE 38/- p. & p. 2/6

Checks all types of resistors, condensers 6 RANGES

Built in 1 hour. Direct reading

READY CALIBRATED

Stamp for details of this and other kits.

RADIO MAIL (Dept. VE)
Raleigh Mews, Raleigh Street, Nottingham

FIRST-CLASS RADIO AND T.V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. N.I.E. provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio/T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148 HOLBORN LONDON, E.C.1

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne.

PADGETTS RADIO STORE
OLD TOWN HALL, KNOWLER HILL, LIVERSEDGE, YORKS.

Telephone: Cleckheaton 2866

Complete T.V. Sets Untested. 9in. Bush BBC only 20/-, 12in. Bush TV24A 25/-, 12in. Bush TV 24C BBC-TV, all channels 35/-, Pye 14in. VT4 13 channel 50/-, Pye 14in. Console 13 channels VFLSC 50/-. Carr. on each 10/- B.R.S. Well packed, but sent at owner's risk.

TV Converters. Less valves and knobs, coils fitted 2 and 10. Ekco, Ultra, Pye, Murphy, Marconi and Philips, etc. 2/6. Post 2/3. Cylidon converters complete 18/-, Post 2/3. All types coils fitted 2 and 10.

Coax. TV Cable. 75 ohms. Best make stranded 5d. per yd. Post free up to 50 yds.

Complete TV Chassis for Spares. Less valves, 12in., four for 10/-, carr. B.R.S. 7/6. 14in. Chassis, four for 15/-, carr. B.R.S. 8/6.

P.M. Speakers, all 3 ohms. Removed from TV sets perfect condition. Rola 6 x 4in., 5/-; Goodmans 7 x 4in., 6/-; Philips 5in. round, 5/-; Rola, R and A, round 8in., 3/6; 6in. Dish, 5/-; 8in. round, 6/-; Post on any speaker 2/-, up to six can be sent for 3/6.

Valves Removed from TV Sets. All post free. All tested on a Mullard valve tester and are 100% as new. They carry a three months' guarantee. We also have a large stock of old type radio valves and other TV valves not listed.

ECL30	4/-	8G6	2/8	PL22	5/-
ELC32	5/-	8SS7	2/-	PL83	5/-
ELC38	4/-	6U4	5/-	PY80	5/-
EY51	2/6	6X4	4/-	PY81	5/-
EBF80	4/6	10C2	2/-	PY82	5/-
EB91	9d.	10P1	1/-	PL82	5/-
EF50	1/8	10P13	5/-	PZ30	4/-
EF91	9d.	10P14	5/-	PCF80	4/6
6F1	1/-	12A17	4/-	PC84	4/6
6P13	2/-	20D1	3/-	PL33	4/-
6P14	5/-	20P1	5/-	B36	4/-
6P15	5/-	20L1	5/-	N37	5/-
6LD20	5/-	20F2	6/-	L63	3/-
6L18	5/-	20P3	5/-	6J5	3/-
6SN7	2/9	U281	5/-	27SU	5/-
68L7	2/9	U282	5/-	U12	4/-
6P28	5/-	U801	8/6	EF80	1/6
6K25	5/-	U329	5/-	10/- per doz.	
6P25	5/-	EX38	5/-	Grades 2 6d.	
6Y6	2/6	PL81	6/-	4/- per doz.	

Perfect Reclaimed Tubes. 6 months' guarantee, 12in. 17/-, 14in. 30/-. Carr. and Ins. 7/6.

TV Tubes Completely Rebuilt and Refaced. 12 months' guarantee. Old glass not required. 12, 14, 15, 16 and 17in., any make, special trade price of £3.15.0. Carr. and Ins. 7/6.

T.M.K. TEST METERS

A fine selection of testmeters to suit every constructor, A MUST for every T.V. Engineer and Serviceman



2,000 O.P.V. MODEL 7
M.P.D.E.
1000 Reads A.C. & D.C.
Voits up to 1,000; D.C. Current to 500mA; Resistance to 1 Meg.; Capacitance to 1uF; Decibels from -20 to +36; Output jack for Audio Measurements. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in. £8.19.6.



20,000 O.P.V. MODEL TP-5S
Heads voltage up to 1,000; D.C. at 20,000 ohms per volt and A.C. at 10,000 O.P.V.; D.C. Current to 500mA; Resistance to 10 Megs.; Capacitance to 0.1uF; Decibels from -20 to +36. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in. £8.19.6.



30,000 O.P.V. MODEL 7
500. Voits to 1,000; D.C. at 30,000 O.P.V.; A.C. at 20,000; 12 Amps D.C. Current; 60 Megs. Resistance; -20 to +56 Dbs; Internal buzzer short circuit warning. Size 3 1/2 in. x 5 1/2 in. x 1 1/2 in. £8.19.6.

Please add 2/6 postage to each of the above. All new stock with leads, prods and internal batteries. 6 months' guarantee, backed by full service facilities. Further details sent on request.

SPECIAL OFFER AVO MODEL 7
Limited number of reconditioned AVO METERS MODEL 7. Complete with leads and internal batteries £11 each. P. & P. 5/-. Or with solid leather carrying case. £12. P. & P. 5/-.
HARRIS ELECTRONICS (LONDON) LTD.
TEST METER DIVISION
138 Gray's Inn Road, London, W.C.1.
Phone Terminus 7937

NEW VALVES!

Guaranteed Set Tested 24-HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 18/6.	DAF96, DF96, DK96, DL96, SET of 4, 26/-
1D5 7/-	DL33 7/6
1R5 5/6	DL35 9/6
1S5 4/6	DL42 5/11
1T4 3/3	DL91 6/9
3S4 5/11	DI36 6/9
3V4 6/9	E891 3/7
5U4G 4/6	EBC41 7/6
5Y3GT 5/9	EBF90 7/9
5Z1G 8/6	EEL21 12/-
6AM6 2/9	ECC40 13/9
6K7G 4/9	ECC81 4/9
6K9G 4/9	ECC82 5/9
6Q7G 5/6	ECC83 6/3
6V6G 4/-	ECC84 7/3
6V8GT 7/9	ECC85 7/6
6X3GT 6/6	ECP90 7/9
12K7GT 4/3	ECP82 8/3
12K8GT 9/-	ECH42 7/9
12Q7GT 4/6	ECL80 5/9
12SN7GT 7/3	EF40 11/-
35L5GT 9/-	EF41 7/6
35Z4GT 5/-	EF80 4/3
AZ31 8/9	EF85 6/6
CL33 9/6	EF86 8/6
DAC32 8/9	EF89 6/9
DAF91 2/9	EF91 2/9
DAF96 6/9	EL41 9/-
DCC90 8/6	EL84 6/3
DF34 8/9	EY51 7/3
DF91 3/3	EY86 7/6
DF96 6/9	EZ40 6/-
DH77 6/-	EZ80 5/9
DK32 10/6	EZ81 6/-
DK91 5/6	MU14 5/6
DK92 6/9	PC84 6/9
DK96 7/3	PC89 9/-
	Z77 2/3
	UABCO 6/-
	UA42 8/-
	UB41 7/-
	UBP80 8/9
	UC85 7/-
	UCH21 11/6
	UCH42 7/6
	UCI81 5/9
	UCL82 9/3
	UCL83 13/-
	UF41 6/9
	UF89 6/9
	UL41 8/-
	UL84 6/3
	UY21 10/6
	UY41 5/6
	UY85 6/9
	VP4B 8/8
	Z77 2/3

Postage 6d. per valve extra. Any Parcel insured Against Damage in Transit 6d. extra Any C.O.D. Parcel 3/- extra. Office address, no callers.

GERALD BERNARD
(Note new address—formerly of Leeds)
83 OSBALDESTON ROAD,
STOKE NEWINGTON, LONDON, N.16

ALUMINIUM, LIGHT ALLOYS BRASS, COPPER, BRONZE


IN ROD, BAR, SHEET, TUBE STRIP WIRE, ANGLE, CHANNEL, TEE
3,000 STANDARD STOCK SIZES

H. ROLLET & CO. LTD.
6 CHESHAM PLACE, LONDON, S.W.1
BELGRAVIA 4300

Works:
36 ROSEBERY AVE., LONDON E.C.1

Branches at Liverpool, Manchester, Birmingham, Leeds
No Quantity too small

BBC - ITV - F.M. AERIALS

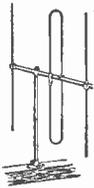

B.B.C. (BAND D). Telescopic lot, 19/6. External. S/D. 26/3.
I.T.V. (BAND 3). 3 Element lot array, 14/-, 5 Element. 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.
COMBINED B.B.C. & I.T.V. Lot 1+3 Element, 41/3. 1+5 Element, 49/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element, 63/9. Chimney and mast mounting units also available.
F.M. (BAND 3). Lot 4+1 28/-, 3 Element lot, 52/6. S/D lot, 12/6. External S/D. 26/3. State channel when ordering. C.W.O. or C.O.D. P.P. 2/6. Coaxial cable, 8d. vd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept. P.T.)
3B, Godstone Road, Kenley, Surrey.

TELEVISION BOOKS ON FREE TRIAL!

THEN ONLY 5/- PER WEEK FOR THOSE YOU KEEP!

No. 200. TELEVISION SERVICING COURSE.
Let this new course help you in T.V. servicing. Amazing bargain, complete, only 32/6 full price for all lessons. Giant in size, numerous in scope. Topics just like a £25 correspondence course. Lessons on picture faults, circuits, adjustments, short-cuts, U.H.F., alignment facts, hints, antenna problems, trouble-shooting, test equipment, picture analysis, etc. **200. 38. RADIO & ELECTRONICS COURSE, 38/-**
A complete home study course of 35 lessons designed to train any beginner to be an expert in radio and electronics. See our previous advertisements for complete details. Price only 38/-.
Graduates of courses No. 39 and No. 200 can qualify for a certificate, additional fee now only 21/-, details sent with each course ordered.

No. 8. PIN-POINT T.V. TROUBLES IN 10 MINUTES, 32/6.
Without a doubt one of the most useful books ever published about television. If you do not yet possess a copy you are really missing something. Thousands of *Practical Television* readers already own and use this book every day. Why not send for a trial copy? Then if you decide to keep it, pay only 5/- per week until completed. This book must be able to earn you more than it's cost within two weeks or your money will be refunded.

Here are the best two books published so far. **No. 38. COLOUR TELEVISION NTSC, System, Principles and Practice, 85/-.**
No. 22. PIN-POINT COLOUR T.V. TROUBLES IN 5 MINUTES, 32/6.
Deals with 150 types of faulty pictures and sound with over 1,000 pictures which may be the cause. Picture Pattern Section. 362 check charts. 478.
If you really want to advance in television you should have the two *Spreiburger Television* Vol. 1, price 25/-, covers Time-Base (Circuits);

YOU TAKE NO CHANCES WHEN YOU BUY FROM SIM-TECH.

If not satisfied you can return the books within 7 days. Pay only 5/- per week on any 1 book. **TELEVISION TEST EQUIPMENT, No. 201.** P. N. Bradley, 80 pages, 5/-.
No. 202S. TELEVISION SERVICING, G. N. Patchett.

Set of 4 books, total 344 pages, complete set only 23/6. (Also available separately). Send for free catalogue of books.
No. 29. TELEVISION SERVICING HANDBOOK, Gordon J. King, 30/-.
How to deduce from a given fault the symptom the most likely cause of the trouble; how then to locate the part concerned; how to do an effective repair. This book together with *Pin-Point T.V. Troubles* will give you real money-making T.V. repair know-how! **ORDER NOW**, to get this special!

No. 1. SPECIAL OFFER, Coyne's Elementary Practical Radio-Television. Set of three volumes. Total 1,928 pages, vinyl covers, £3.12.6 the set. A set of books you will treasure and use for years to come. Written in a simple, easy to follow manner, yet explaining everything completely. Teaches T.V. and radio together, saving time. An ideal set for the amateur or beginner. Pay only 9/- weekly if you wish!

BIG BOOK CATALOGUE SENT FREE! FREE TRIAL COUPON

To Sim-Tech Book Co., Dept. P.14, 25, Gater's Mill, West End, Southampton.

Please send me the books number () () () for seven days' free trial. One at a time. If I am not satisfied with any book I may return it post paid without further obligation on my part. Otherwise I will pay cash or 5/- weekly after seven days until paid.
 Tick here if enclosing full price (we guarantee). Name 7-day money-back guarantee. Postage charges: Orders up to £3 allow 1/6; £3 or over allow 2/-. Overseas customers please send full amount.

Name _____
Address _____

REBUILT TUBES!

You're safe when you buy from
RE-VIEW LTD!

- ★ Each tube is rebuilt with a completely new gun assembly **and** the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for a year against all but breakage.
- ★ Each tube is delivered **free** anywhere in the U.K. and insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

RE-VIEW (LONDON) LTD.

385 LONDON ROAD, WEST CROYDON,
SURREY. TEL. THORNTON HEATH 7735.



HERE IS WHAT YOU PAY:

12in.	£7.10.0
14in.	£4.15.0
15in.	£5. 0.0
17in.	£5. 0.0
21in.	£7. 0.0

Cash or cheque with order, or cash on delivery

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee "NO PASS—NO FEE"

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of "ENGINEERING OPPORTUNITIES" today—FREE.

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
Electrical Eng.,
Civil Engineering,
Radio Engineering,
Automobile Eng.,
Aeronautical Eng.,
Production Eng.,
Building, Plastics,
Draughtsmanship,
Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.Prod.E.
A.M.I.M.I.
A.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
City & Guilds
Gen. Cert. of Education
Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"
 (Write if you prefer not to cut page)
 NAME.....
 ADDRESS.....

 SUBJECT OR EXAM THAT INTERESTS ME..... (SE 20).

BRITISH INSTITUTE OF ENGINEERING
TECHNOLOGY (Incorporating E.M.I. Institutes)
(Dept. SE/20), 29 Wright's Lane, London, W.8

THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD

C.R.T. BOOSTER TRANSFORMERS

for cathode ray tubes having heater cathode short circuit and for C.R. tubes with falling emission. Full instructions. State voltage required. Type A optional 25%, and 50% boost. 2 or 4v. or 6.3v. or 10.8v. or 12.6v. Mains input. PRICE 10/6.

TIMMERS. Ceramic. 30, 50, 70 pF. 9d.; 100 pF, 150pF, 1/2-250 pF, 3/16-500 pF, 750 pF, 1/19. PHILIPS CONCENTRIC. 10pF or 30pF 1/1. RESISTORS. Preferred values, 10 ohms to 10 meg. 4 w. 3d.; 1 w. 4d.; 1/2 w. 6d.; 1/4 w. 8d.; 2 w. 1/1. HIGH STABILITY. 4 w. 1/2. 2/-. Preferred values, 10 to 10 meg. Ditto. 5/10. 10 to 22 meg. 9d. 5 watt. 1/3. WIRE-WOUND RESISTORS 1/8. 15 watt. 25 ohms-10,000 ohms 2/-. 12.5K to 50K 10w. 3/1.

AMERICAN "BRAND FIVE" PLASTIC RECORDING TAPE

Double Play 5in. reel, 2,000ft 60/ Spare Plastic Reels Long Play 7in. reel, 1,800ft 35/ 3 in. 1/6. 9in. reel, 1,200ft 23/6 4 in. 2/1. 9in. reel, 900ft 18/6 5 in. 2/1. Standard 7in. reel, 1,200ft 25/ 5 in. 2/1. 9in. reel, 600ft 16/ 7 in. 2/6 "Instant" Bulk Tape Eraser and Head Duxer, 200/250 v. A.C. 27/6. Leadet, S.A.E.

O.P. TRANSFORMERS. Heavy Duty 50 ma. 4/6. 100 ma. 7/6. 200 ma. 10/6. 500 ma. 15/6. Miniature. 354. etc. 5/9. L.F. CHOKES 15 to 10. 60/65 ma. 5/-; 10 H. 85 ma. 10/8; 10 H. 150 ma. 14/-.


MAINS TRANSFORMERS 200/250 v. A.C.

Standard, 250-0-250, 80 ma. 6.3 v. 3.5 a. tapped 4 v. 4 a. Rectifier 6.3 v. 1 a. 5 v. 2 a. or 4 v. 2 a. 22/6 ditto, 350-0-350 29/6. MINIATURE 200 v. 20 ma. 6.3 v. 1 a. 10/6. BLOW-OUT 220 v. 45 ma. 6.3 v. 2 a. 15/6. SMALL 220-0-220, 50 ma. 6.3 v. 2 a. 17/6. STD. 250-0-250, 63 ma. 6.3 v. 3.5 a. 17/6. HEATER TRANS. 6.3 v. 1 1/2 amp. 7/6. Ditto, tapped sec. 2, 4, 6.3 v. 1 1/2 amp. 8/6. Ditto, sec. 6.3 v. 3 amp. 10/6. GENERAL PURPOSE LOW VOLTAGE. 2a. 3-4, 5, 6, 8, 9, 10, 12, 15, 18, 24, 30 v. 22/6. AUTO TRANSFORMER. 150 v. 22/6. 0, 120, 240, 270, 250 v. 500 v. 32/6.

ALADDIN FORMERS and core, lin. 8d.; lin. 10d. 0.3in. FORMERS 5937/8 and Cans TV1/2, 7in. sq. x 2 1/2in. and lin. sq. x 1 1/2in., 2/- ea., with cores. SOLON Soldering Iron. 200 or 240 v. 25 w. 24/- MAINS DROPPERS. Midget. Adj. Sliders, 8.3 amp., 1,000 ohms 5/-; 0.2 amp., 1,200 ohms 5/-; 15 amp., 1,000 ohms 5/-. 1 amp., 2000 ohms 5/-. LINE CORD. 6.3 amp., 60 ohms per ft., 0.2 amp., 100 ohms per ft., 2-way, 1/1; 3-way, 1/1; per ft. LOUDSPEAKER P.M. 3 OHM. 2 1/2in., 3in., 4in., 19/6. 6in., 17/6. 8in. Pleseye, 19/6. 7in. x 7in. 18in., 10/6. 6in. 18/6. 10 x 6in. 27/6. 10in. 30/6. 4in. H-Pi Tweeter, 25/-, 12in. R.A., 30/-, 13 x 8in., double cone E.M.I., 45/-. STENTORIAN HF 1012, 10in. 3 1/2 x 15 ohms, 10w., 95/- CRYSTAL DIODE G.E.C. 2/-, GEX34, 4/-, OA81, 3/- HIGH RESISTANCE PHONO, 4,000 ohms, 15/- per. MIKE TRANS. 50:1, 3/9 each. SWITCH CLEANER. Fluid squirt spout, 4/3 tin. TWIN GANG TUNING CONDENSERS. 365 pF miniature lin. x 1 1/2in. x 1 1/2in., 10/-, 500pF Standard with trimmers, 9/1; midget, 7/6 with trimmers, 9/1. SINGLE, 10 pF, 25 pF, 50 pF, 75 pF, 100 pF, 150 pF, 5/8. solid dielectric, 100, 300, 500 pF, 3/6.

COMPLETE RADIO £5.19.6

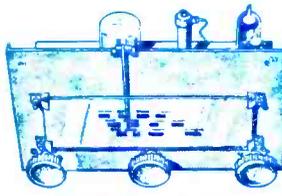4 Mullard valves, 5in. speaker. Superhet Circuit. BRAND NEW. Size 9 x 5 x 5 1/2in. high. Tested by us ready for use. 200/250 v. A.C.-D.C. Mains.



DE LUXE MODEL as illustrated with illuminated dial. Tunable over Medium and Long Wave. 12-month Guarantee.

BARGAIN SALE PRICES

New and Boxed VALVES 90-day Guarantee

Table listing various vacuum tube valves with their part numbers and prices. Columns include valve type (e.g., 6X4, 6BE6), manufacturer codes (e.g., 5/-, 6/-), and prices (e.g., 10/6, 8/6).

BAKER SELHURST LOUDSPEAKERS

12in. Baker 15w. Stalwart 4 or 15 ohms, 45-13,000 c.p.s. 90/-. 12in. Stereo, 12 w., 35-16,000 c.p.s. 26.17.6. 12in. Baker Ultra Twelve, 20 c.p.s. to 25 kc/s. 17.10. 15in. Bass Auditorium Mk11, 35 w. 21S.



S.A.E. for full list and enclosure details.

NEW MULLARD TRANSISTORS

OC71 8/- OC81D 7/6 OC84 8/6 AF117 6/6 OC72 7/6 OC81 7/6 OC84 8/6 OC71 19/8. 3rd Miniature Transistors. 0.1mF 30 p. 1/3. 1, 2, 4, 5, 8, 25, 50, 100, 100 mfd. 15 volt. 2/6 each. Complete Printed Circuit Components in Stock. Book 2/-, 7 x 4in. Speaker 35 0/25/-.

CRYSTAL MIKE INSERT precision engineering.

MINIATURE SIZE, 6/6. ALUMINIUM CHASSIS. 18 s.w.g. un drilled. With 4 sided, riveted corners and lattice fixing holes, 2 1/2in. ideas, 7 x 4in., 4/6; 9 x 7in., 5/9; 11 x 7in., 6/8; 13 x 9in., 8/6; 14 x 11in., 10/6; 15 x 14in., 12/6; 18 x 15 x 3in., 16/6. ALUMINIUM PANELS. 18 s.w.g. 12in. x 12in., 4/6; 14 x 9in., 4/-; 13 x 9in., 3/-; 10 x 7in., 2/3. JASON F.M. TUNER COIL SET, 29/-, H.F. coil, aerial coil, oscillator coil, Two L.F. trans. 10.7 Mc/s Ratio Detector and heater choke. Circuit book using four 6AM6, 2/6. COMPLETE JASON F.M. KIT, FMT1. with 4 valves, components and chassis, 56.5.0.

BBC TRANSISTOR RADIO. Med. and Long Wave Two transistors and diode. Complete kit, 22/6. Earphone 7/6, battery 2/3.

465 Kc/s. SIGNAL GENERATOR. Price 15/-. Uses B.F.O. Unit ZA 400384 ready made with valve. POCKET SIZE 2 1/4 x 4 1/2 in. One resistor to change. Full instructions supplied. Battery 8/6 extra. 69 v. + 14 v.

I.F. TRANSFORMERS 7/6 pair

465 K/s Slus Tuning Miniature Size, High Q and good bandwidth. Data sheets supplied.

TU REPLACEMENT LINE OUTPUT TRANSFORMERS

FROM 45/- ea. s.a.e. with all enquiries

LINE BLOCKING TRANSFORMERS, from 10/-. FRAME BLOCKING TRANSFORMERS, from 13/6. FRAME OUTPUT TRANSFORMERS, from 27/6.

HIGH GAIN TV PRE-AMP KITS BAND I BBC

Tunable channels 1 to 3. (gain 18dB). EC084 valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PC84 valves if preferred). BAND II TV. Same price. Tunable channels 8 to 13. Gain 17dB. EC084 valve. (PC84 valves if preferred).

AUTOCHANGER PLAYER KIT

Complete with ready built amplifier, speaker & cabinet. £12.10.0 carr. & ins. 5/-



All with LP/Std. 4 track leads and stylus. 4 Speed Autochanger B.S.R. U.A.14 £7.10.0. B.S.R. U.A.12 Stereo Mono £8.5.0. Garrard Model Autodisc £7.19.6. 4 Speed Single Players, KM1 £6.5.0. Garrard T.A. Mk II, G.8 Head £8.0.0. Garrard Model 4SP (42) £17.17.6. Garrard 4HF Transcription £17.19.6. Amplifier player cabinets (except 4 H.F.) 70/-. 2-valve amplifier and 6in. speaker 95/-. 3-valve amplifier and 6in. speaker 105/-. All sapphire styli available from 6/-.

Volume Controls 80 ohm CABLE COAX

Linear or Log Tracks. Semiar spaced. 1in. Long spindles. Guaranteed 1 year. Midget 40 yds 17/6. 6d. yd. 5K ohms to 2 Meg. 30 yds 25/-. 40 ohms only. 1.5K 3/-, 1M 4/6. Fringe quality stereo 10/8. D.P. 14/-, Air Spaced. 1/- yd.

TRIPLEXERS Bands I, II, III

COAX PLUGS 1/- LEAD SOCKETS 2/- PANEL SOCKETS 1/- OUTLET BOXES 4/6. BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms. DITTO GREENED per yd. 1/6. 40 ohms only. WIRE-WOUND POTS 3 WATT. Pre-set. Min. TV Type. All value 25 ohms to 25 K. 3/- ea. 30 K, 50 K, 4/-, (Carbon 30 K, 1 on 2, 8/-). WIRE-WOUND 4 WATT. Pots Long Spindle. Values, 50 ohms to 50 K. 8/6; 100 K, 7/6. CONDENSERS. New Stock, 6.000 mfd. 7 v. 9/6; Tubular 500 v. 0.001 to 0.05 mfd., 9d., 0.1 L/-; 0.25, 1/8; 0.5/500 v. 1/9; 0.1/350 v. 9d.; 0.01/2,000 v. 0.1/1,000 v. 1/9; 0.1 mfd., 2,000 cons. 3/6. SILVER MICA CONDENSERS. 10%, 5 pF to 500 pF, 4/6; 600 pF to 3,000 pF, 1/-. Close tolerance (+/- 1 pF), 1.5 pF to 47 pF, 1/-. Ditto 1/6 50 pF to 815 pF, 1/-; 1,000 pF to 5,000 pF, 1/9.

New Electrolytics. Famous Makes

TUBULAR TUBULAR CAN TYPES 1/850V. 2/- 50/350v. 5/6 32/350v. 5/- 2/450v. 2/3 100/25v. 2/- 100/270v. 5/6 4/450v. 2/3 250/25v. 2/6 2,500/3v. 4/- 8/450v. 2/3 500/12v. 3/- 5,000/5v. 5/- 16/450v. 3/- 8+8/450v. 3/6 32-32-32/350/7-32/450v. 4/9 16+16/450v. 4/9 50+50/450v. 7/6 25/25v. 4/9 16+16/450v. 4/8 104+120/350v. 11/6 50/50v. 2/- 32+32/350v. 4/6 100+200/275v. 12/6. RECTIFIERS SELENIUM 300 v. 85 ma 5/-. CONTACT COOLED 250 v. 50 ma, 7/6; 60 ma, 8/6; 85 ma, 9/6; 200 ma, 21/-; 300 ma 27/6. COILS Wearite 'P' type, 3/- each. Osmer Midget 'Q' type adj. dust core from 4/-. All ranges. TELETRON, 100 v. T.R.F. with reaction, 4/-. FERRITE ROD AERIALS, M.W. 8/9; M. & L., 12/6. T.R.F. COILS A.H.F. 7/- pair. H.P. CHOKES 2/6. FERRITE ROD, 8in. x 1/8 in. dia. 3/-, 6 x 1 1/2 in. 3/-, 8 x 1 1/2 in. 3/6.

FULL WAVE BRIDGE SELENIUM RECTIFIER;

2, 6 or 12 v. 14 amp. 8/8; 2 a., 11/3; 4 a., 17/6. CHARGER TRANSFORMERS. Tapped input 200/250 v. for charging at 2, 6 or 12 v., 1 1/2 amps., 15/6. 2 amps., 17/6; 4 amps., 22/6. Circuit included. VALVE and TV TUBE sockets, 100-200/275v. 9/6. TOGGLE SWITCHES 5P 2/-, D.P. 3/6. D.P.D.T. 4/- WAVECHANGE SWITCHES 8 p. 4-way 2 wafer long spindle 6/8 2 p. 2-way, or 2 p. 6-way long spindle 3/6 3 p. 2-way or 4 p. 3-way long spindle 3/6 4-way or 1 p. 12-way long spindle 3/6 VALVEHOLDERS. Pax Int. Oct., 4d. EF50, EA60, 6d. B12A, CRT, 1/3. Eng. and Amer. 4, 5, 6 and 7 pin, 1/1. MOULDED MAZDA and Int. Oct., 6d. B7G, B8A, B8G, B9A, 8d. B7Z with can, 1/6. B9A with can, 1/8. CERAMIC EF50, B7G, B9A, Int. Oct. 1/1. S/Cans B7G, B9A, 1/1-ea. SPEAKER FRET. GOLD COATED. 17in., 25in., 5/-, 25in. x 3 1/2in., 10/-. Tyran 62in. wide, from 10/1. 11. 26in. wide from 5/-. Various colours. Samples S.A.E. Expanded Metal, Gold, 12 x 12 in. 6/-.

RADIO COMPONENT SPECIALISTS NEW LIST 1/-

Post 1/-, unless otherwise stated. C.O.D. 2/- extra. (Export post Extra.) (Wed. 1 p.m.) THO 1665, Buses 133 or 68.