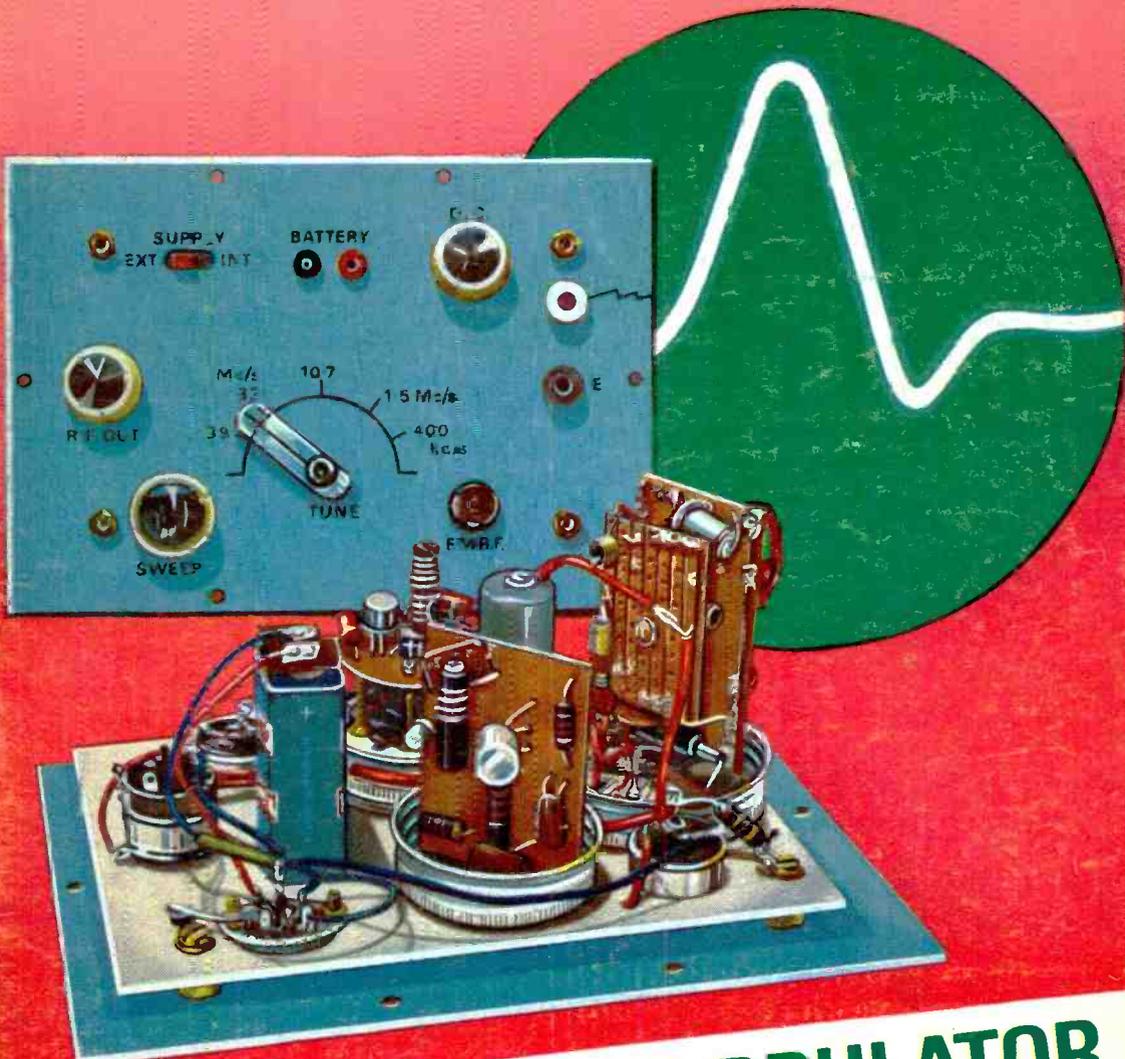


51-Neo

# Practical TELEVISION


MARCH 1967

2'-



## Wide-Range WOBBLULATOR



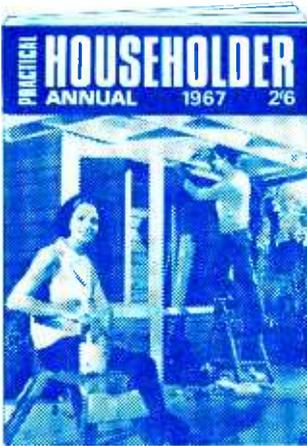

**Get  
it  
Now!**

**YOUR GUIDE TO MAKING  
YOUR HOME BETTER,  
BRIGHTER, MORE EFFICIENT**

Don't miss the 1967 PRACTICAL HOUSEHOLDER ANNUAL! It brings you masses of new ideas for making your home more attractive and efficient to live in.

**SPECIAL SECTIONS ON:**

**HOME HEATING**

All the latest developments in hot water central heating.

**GUIDE TO HOME ELECTRICITY**

A complete run-down for the handyman, with diagrams of domestic wiring circuits and how they work.

**HANDYMAN TOOLS**

Invaluable information on hand and power tools for the enthusiast.

**OUTDOOR IMPROVEMENTS**

How to build garden furniture—a summer house—stone, concrete and brick-work around the house.

**EASY HOME PLUMBING**

How your hot water system works. Information on fittings for modern bathrooms. Install your own shower.

**PLAYTIME**

Complete outdoor play unit of slide, shelter, sandbox and simple toys.

**DECORATING**

Advice on long-lasting and attractive decorations for the inside and outside of your home.




**PRACTICAL  
HOUSEHOLDER  
ANNUAL 2'6**

**BIG DEMAND ! MAKE SURE OF YOURS !**

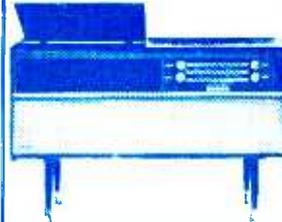**LATEST RADIOGRAM CABINETS £9.10.0**

Superbly made and styled in Veneered English Walnut



LIFT UP LID TO CHANGER & RECORD STORAGE COMPARTMENT

Position 8" x 5" Twin Speakers  
Dimensions: 40 x 16 1/2 x 15 1/2  
Legs 1 gn. Carr. 30/-

Other Models — Send for List



Record Player Cabinets 49.6. Latest designed covered cabinets. Take any modern Autochanger.  
Single Player Cabinets 19.6. P. & P. 7.6.  
T.V. Turret Tuners 2/6 less valves. Slim Models 5/- Press Button Models 19/6 P. & P. 2/6


**17in. — £11.10.0 TWO YEAR GUARANTEE**

3 star Guarantee  
★ Tube ★ Valves ★ Components  
Carr. 30/-

**EX-RENTAL  
TELEVISIONS**

Free illustrated list.  
Wide range of models sizes and prices

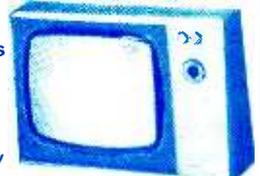**SLIM LINE**  
17" 19" 21" 23"  
demonstrations daily



**DUKE & CO. (LONDON) LTD.**

621/3 Romford Road, Manor Park, E.12  
Phone: ILFord 600-1-2-3 Stamp for free list

**REGUNDED TUBES**  
2 Year Guarantee  
14" 89/6; 17" 89/6  
21" and Slimlines 109.6  
Carr. 10/6



**"SABRINA"  
STILL WELL IN  
FRONT**

**COMPLETELY REBUILT C.R. TUBES  
ALL TYPES**

12" now	..	..	£5. 0.0	} For Single Tubes
14" to 17" now	..	..	£5.10.0	
19" now	..	..	£6.15.0	
21" now	..	..	£8. 0.0	

ALL C.W.O.—TRADE SUPPLIED

**Special Bonus Scheme for Service  
Engineers—Reducing to:**

12"—87/6; 14"/17"—97/6; 21"—147/6  
FREE Pass. transit & Ins. anywhere in  
British Isles or N. Ireland (12 months'  
guarantee).

ALSO FULL RANGE OF VALVES  
(Guaranteed 12 months)

**SABRINA C.R. TUBE CO.**

Electron Works, 50 North Bar  
BANBURY, OXON  
Telephone 2390

# VALUABLE NEW HANDBOOK **FREE** TO AMBITIOUS **ENGINEERS**

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

## On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

## WHICH OF THESE IS YOUR PET SUBJECT?

**TELEVISION ENG.**  
*Advanced Television Eng.—Gen. Television Eng.—Television Servicing and Maintenance.*

**ELECTRONIC ENG.**  
*Advanced Electronic Eng.—Gen. Electronic Eng.—Applied Electronics—Practical Electronics—Radar Tech—Frequency Modulation—Transistors.*

**MECHANICAL ENG.**  
*Advanced Mechanical Eng.—Gen. Mechanical Eng.—Maintenance Eng.—Diesel Eng.—Press Tool Design—Sheet Metal Work—Welding—Eng. Pattern Making—Inspection—Draughtsmanship—Metallurgy—Production Eng.*

**RADIO ENG.**  
*Advanced Radio—Gen. Radio—Radio Servicing—Telecommunications—Sound Recording—Automation—Practical Radio—Radio Amateurs' Exam.*

**ELECTRICAL ENG.**  
*Advanced Electrical Eng.—Gen. Electrical Eng.—Installations—Draughtsmanship—Illuminating Eng.—Refrigeration—Elem. Electrical Science—Electrical Supply—Mining Electrical Eng.*

**CIVIL ENG.**  
*Advanced Civil Eng.—Municipal Eng.—Structural Eng.—Sanitary Eng.—Road Eng.—Hydraulics—Mining—Water Supply—Petrol Tech.*

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

WHICH QUALIFICATION WOULD INCREASE YOUR EARNING POWER?

A.M.I.E.R.E., A.M.I.Mech.E., A.M.S.E., A.M.I.C.E., B.Sc., A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Chem.E., A.R.I.C.S., M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS, GEN. CERT. OF EDUCATION, ETC.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**  
414A ALDERMASTON COURT, ALDERMASTON, Berks

## THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Dept.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.



132 PAGES OF EXPERT CAREER - GUIDANCE

## PRACTICAL INCLUDING EQUIPMENT TOOLS

Basic Practical and Theoretic Courses for beginners in TV, Radio, Electronics, etc., A.M.I.E.R.E. City & Guilds, Radio Amateurs' Exam, R.T.E.B. Certificate P.M.G. Certificate Practical Radio Television & Radio Servicing Practical Electronics Engineering Automation

*The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.*

## B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES", send for your copy now—FREE and without obligation.

## POST COUPON NOW!

To B.I.E.T., 414A Aldermaston Court Aldermaston, Berkshire

3d. stamp if posted in an unsealed envelope

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES". I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE

**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**


# CRT'S

## Rebuilt

- RESCREENED
- RE-ALUMINISED

Regular buyers of Suffolk and Midland Tubes have learnt to rely on their outstanding quality. Every Tube fully guaranteed with proved performance reliability.

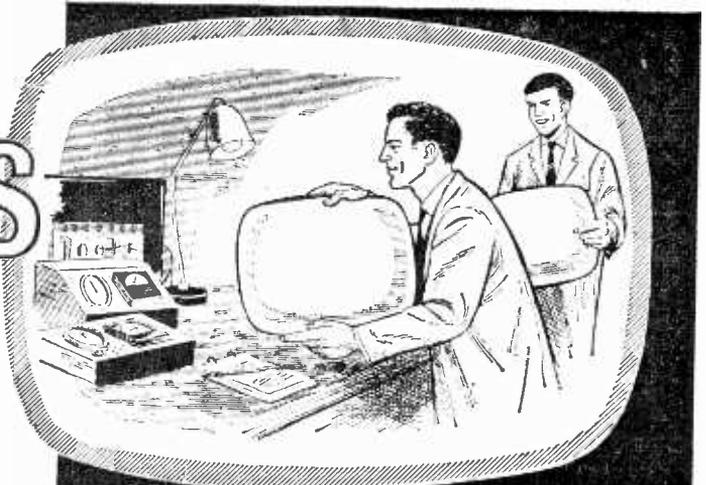PRICES FROM £4.0.0 EACH  
The largest independent rebuilders in the U.K.



### SUFFOLK TUBES LTD

1/3 UPPER RICHMOND ROAD  
PUTNEY LONDON S.W.15  
Tel: Vandyke 4304/5267

### MIDLAND TUBES LTD

477/483 OLDHAM ROAD  
MANCHESTER 10  
Tel: Collyhurst 4412

## ELECTRONICS GALORE!

in the NEW

### dca CATALOGUE

The convenient way to shop for all your electronic needs. Everything from single components to complete equipment all at today's best value prices.

Send 1/6 now for your copy to:  
DEPT. PT/3


dca ELECTRONICS LIMITED  
28 Uxbridge Road, Ealing, W.5

## VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL84, Set of 4 for 18/9, DAF96, DF96, DK96, DL96, 4 for 24/8.

1A7GT	6AC5	5/6	30FL1	10/6	6EF80	6/-	6GZ32	9/-	6Y500	8/6	
6AT6	6/7	30FL15	11/6	6EBP88	5/8	6K181	9/6	6Y501	6/-		
1M5GT	6BA6	4/6	30FL17	12/-	6FC81	3/8	N18	5/8	R19	7/6	
6B86	4/3	30FL14	11/6	6FC82	4/9	N78	14/9	R20	12/9		
1A5GT	6B16	6/8	30P12	9/6	6FC83	7/-	6C86	9/-	D25	9/-	
6B16	6/8	30P12	9/6	6FC83	7/-	6C86	9/-	D25	9/-		
1R5	5/6	6B17	8/8	30P19	11/6	6FC84	6/3	6C88	9/-	U26	8/6
1R4	4/6	6B18	4/8	30P14	12/6	6FC85	5/8	6C87	5/8	U47	8/6
1R5	5/6	6B13	3/8	30PL13	11/9	6CF80	7/6	6C800	8/8	U49	8/6
1T4	2/8	6P23	9/8	35W4	4/6	6CF86	6/9	6C84	5/6	U52	4/6
3A5	7/-	6K70	1/6	35Z4GT	5/6	6CH35	6/-	6C89	9/8	U78	3/8
3Q4	5/6	6K80	4/3	85A2	5/6	6CH42	9/-	6C89	9/8	U78	3/8
3S4	4/6	6K8GT	7/8	185BT.20	2/-	6CH81	5/-	6CF82	6/-	U801	18/3
3V4	5/6	6L18	7/6	6063	12/6	6CH84	8/6	6CF86	8/8	UABC80	5/9
5U4G	4/6	6Q75	5/8	AZ31	3/-	6CL80	6/-	6CF8001016	UAF42	7/9	
5V4G	7/9	6V6G	3/8	B36	3/6	6CL82	7/6	6CF801	8/8	UB41	6/9
5Y3GT5	6V6GT	6/8	6B29	18/-	6CL86	7/6	6CF802	9/6	UBF80	6/-	
5Z4G	7/-	6X4	3/8	DAU22	7/8	6F89	3/8	6CF805	9/8	UBF88	5/6
6 30L25/6	6X5GT	5/9	DAF91	3/9	6F41	4/9	6CL82	8/2	6F121	9/-	
6AL5	2/3	7B7	10/8	DAF96	8/-	6F89	4/3	6CL83	8/6	UC92	5/6
6AM0	3/8	7C7	7/-	DK90	7/-	6F85	5/4	6L84	7/6	UC84	7/8
7C5	9/8	6F33	7/8	6F86	6/3	6F83	6/3	6CL85	8/8	UC25	6/8
7C6	6/9	6F91	2/8	6F89	7/-	6PL86	8/6	6CF86	8/8	UCF80	8/3
7H7	5/8	6F96	6/4	6F91	3/8	6FEN A4	6/8	6UCH21	9/3		
7Y4	8/8	6H77	4/-	6F92	2/8	6FEN 360151/	UCH42	8/9			
802	11/6	6H81	12/6	6F97	7/6	6FEN383	9/8	6UCH31	6/-		
803	9/8	DK32	7/8	6F183	6/9	6F200141/	6U182	7/-			
803	8/6	DK91	5/6	6F184	6/-	6PL86	9/3	6UCL83	8/8		
8A7	3/9	DK92	8/-	6FL23	8/6	6PL81	6/8	6UF41	5/-		
12A06	4/9	DK96	6/8	6FL41	8/6	6PL82	6/8	6UF80	7/8		
12AU7	4/9	DL33	6/8	6FL42	8/6	6PL83	6/8	6UF89	5/8		
12AX7	4/9	DL33	5/4	6FL41	4/9	6PL84	8/8	U141	8/8		
12K8GT	8/6	DL92	4/8	6FL95	5/-	6PL80	13/6	U144	20/-		
12K8GT	7/9	DL94	5/8	6EM80	5/9	6PL801	7/8	U184	5/8		
20E2	10/8	DL96	8/-	6EM81	7/3	6P25	7/9	U221	8/9		
20L1	14/-	DX90	6/8	6EM84	6/8	6FV31	6/8	U341	4/8		
20P1	9/-	DX87	6/8	6EM87	8/8	6FV32	8/6	U385	4/9		
20P3	9/-	EABC80	6/-	6FV31	6/3	6FV33	8/6	U418	11/-		
20P4	13/6	EAF42	7/8	6FV6	6/-	6PY80	5/3	VP121	21/-		
25Z4GT11/8	EB41	4/-	6Z40	8/3	6Y81	5/3					
30C15	19/6	EB91	2/3	6Z41	6/8	6Y82	8/6	W76	3/8		
30C17	11/6	EB33	7/-	6Z60	3/8	6Y83	5/9	W77	2/8		
30F5	9/9	EB41	7/8	6Z81	4/8	6Y88	7/3	Z77	3/8		

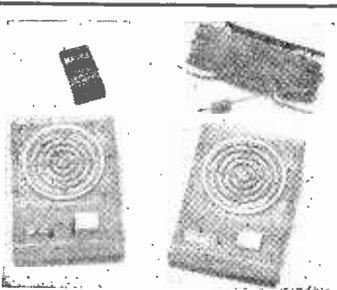

Relax and save your legs, our special price 54/8. Battery included—usually 7 gns. Fitted in seconds! Dispatch by return.

2 Station System—deal for Home, Office, Sick room—endless uses. Operates on one 9 volt battery with a life of 4 to 6 months. Two fully transistorised sets—either one can speak or listen to the other even if switch is at "off" position. Size of both master and sub station 3 x 2 x 4in. Two tone strong plastic cases finished with silver trim. Complete with 50ft. connecting cable and fitted jack-plugs, staples and fixing tape battery and instructions. Postage, packing and transit insurance 3/-.

LOW COST  
BABY ALARM/INTERCOM

**READERS RADIO** 85 Torquay Gardens, Redbridge, Ilford, Essex  
CRE 7441

Postage on 1 valve 9d. ex. 2 or more 6d. per valve ex. Any Parcel insured against damage in transit 6d. ex.

# Practical Television

TV AND THE YOUNG

MARCH  
VOL. 17

1967  
No. 6  
issue 198

TELEVISION already influences the attitudes, thinking and behaviour patterns of many viewers and it is now gaining a foothold, by way of CCTV, in the school rooms. The advantages are not disputed—a central control room can do the work of several teachers and a carefully prepared and well illustrated lesson by CCTV seems a great advance on the blackboard-and-chalk days.

However, there is an inherent danger. The solo teacher cannot compete in the more spectacular aspects of presentation but a CCTV system cannot establish the same personal rapport and project the same individual personality as a flesh and blood teacher directly involved with the pupils.

Teaching by CCTV is obviously attractive but as the techniques advance and applications grow, as they surely will, then we must be prepared for the ultimate situation—arrived at in evolutionary stages—of a standard curriculum on video tape pumped out to a chain of state comprehensive schools. This would be around 1984!

In all directions we are perceptibly drifting towards conformity. The choice of schooling is being progressively eroded and the ad-mass attitudes of state and industry is gradually reducing us to a race of battery hens. *Touché!*

A recent ITA survey shows that series and serials are “for most people the staple diet of TV viewing”. Plays must be “easy to understand”, the plot must become clear in the first few minutes and the viewer must be able to foresee a consistent denouement. Otherwise he will switch off, presumably to another channel in search of something easier to comprehend. The mass TV audience looks for undemanding material—and usually gets it.

The receptive minds of young people are consequently exposed to mass-appeal programmes more than others, as they are to offerings which cause viewers to wax indignant about being “offensive and corrupting to children who may be viewing”—and who are seemingly so befuddled by compulsive viewing or so lacking in parental control that they have forgotten where the on-off switch is located.

Perhaps most people are resigned to the grand theory of “levelling” to the lowest common denominator. And maybe this is the inevitable outcome of science and technology. But it is a pity that television could be, maybe inadvertently, not only lending itself to, but playing a major role in, the march towards the anthill society. W. N. STEVENS—*Editor*.


## THIS MONTH

Teletopics	244
Wide-Range Wobblator <i>by D. R. Bowman, B.Sc., A.M.I.E.R.E.</i>	246
“Locked Oscillator” F.M. Discriminator <i>by S. George</i>	250
Stock Faults—Part IX <i>by H. W. Hellyer</i>	252
Hum in Television Receivers <i>by V. D. Capel</i>	256
Book Reviews	259
Television Pre-amp Baby Alarm <i>by A. Thomas</i>	260
The World of Service—Part III <i>by G. R. Wilding</i>	262
Points about U.H.F. Aerials <i>by K. Royal</i>	264
Letters to the Editor	266
Servicing Television Receivers— Regentone 195 and Associated Models <i>by L. Lawry-Johns</i>	267
DX-TV <i>by Charles Rafarel</i>	270
Underneath the Dipole <i>by Iconos</i>	272
Ideas for Amateur TV—Part IX <i>by M. D. Benedict</i>	274
Gas in Valves and Tubes <i>by K. T. Wilson</i>	278
Your Problems Solved	281
Test Case—52	284

OUR NEXT ISSUE DATED APRIL  
WILL BE PUBLISHED ON MARCH 23

# TELETOPICS

## CCTV aids manufacture of cables

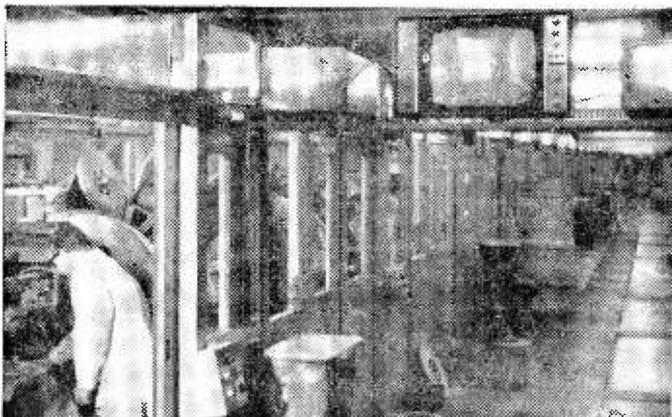

**C**LOSED circuit television is utilised in order to overcome the long distances between machine operators and assistants during the paper lapping process in the manufacture of super-tension cables at the BICC factory at Belvedere, Kent. By the strategic placing of Rank Organisation equipment, consisting of TV cameras and a 19in. central monitor the machine operator can observe, from the control position at the input end of the machine, the coiling-on process which is situated some 70 yards away at the output end. In addition, on two 14in. Pye monitors, he can observe the passage on the far side of the machine.

## East Berlin giant Television mast still growing

**T**HE 1,180 ft. television tower, which is to dominate one of East Berlin's main squares, the Alexanderplatz, has now reached a height of 400 ft. and construction on the second third of the project is well under way. The giant mast due for completion in 1968, will be the tallest building in Europe.

The seven-storey tower, in addition to transmitting and other technical installations, will house a cafe with accommodation for 200 persons and be equipped with an observation platform at a height of 600 ft.

The top of the tower is designed as a steel sphere with a radius of 52.5ft. This upper structure consists of 140 segments, each of them weighing eight tons. The project provides for the installation of an air conditioning system since all windows and portholes of the tower will be hermetically sealed.

The proposed height of the East Berlin TV tower compares with a total height of 620ft. for the GPO tower of London (including 40ft. for television aeriels) and with a total height of 1,033ft. (including 15ft. for transmitter installations) of the Eiffel Tower of Paris.

## TELECINE FOR HONG KONG

**E**MI Electronics have recently been awarded a contract for the supply of four telecine chains to Rediffusion Hong Kong, the contractors who supply the wired television service for the Colony.

These are based on EMI Vidicon Camera type 201 and include the latest Philips 16mm projector. Facilities for separate magnetic replay on 35mm and 16mm are provided, and common magnetic on 16mm.

## EMI TELEVISION GEAR FOR NEW ZEALAND

**E**MI Electronics will be supplying video equipment for the New Zealand Broadcasting Corporation's latest News Studio in Hamilton, North Island.

The installation includes two Vidicon Cameras type 201 fitted with Angenieux zoom lenses, a complete production vision mixer and solid-state monitors. Installation will be carried out by NZBC's own engineers and the Studio will be operational late this year.

## ABC Television broadcast from cathedral crypt

**O**N Sunday, December 11th at 11.00 a.m., ABC Television's Outside Broadcast cameras were positioned in the Crypt of Liverpool's new Metropolitan Cathedral to broadcast Pontifical High Mass. The Service, screened on the ITV network, was the first ever to be televised from this famous new Cathedral which is now nearing completion.

## ENGINEERING CAREERS EXHIBITION A SUCCESS

**A**TTEENDANCE at "The Engineers' Day" Exhibition at the Science Museum, London, well passed the 175,000 mark.


This government-sponsored exhibition, designed to encourage young people to consider professional engineering as a career, was a graphic answer to the question "what does an engineer actually do?"

Over 500 school parties from London and the southern half of England visited the exhibition since it opened in November last year.

A spokesman for the government departments and public bodies taking part in the exhibition said recently: "the response to the exhibition was most encouraging; obviously there is no shortage of interest among young people in this valuable and rewarding type of career".
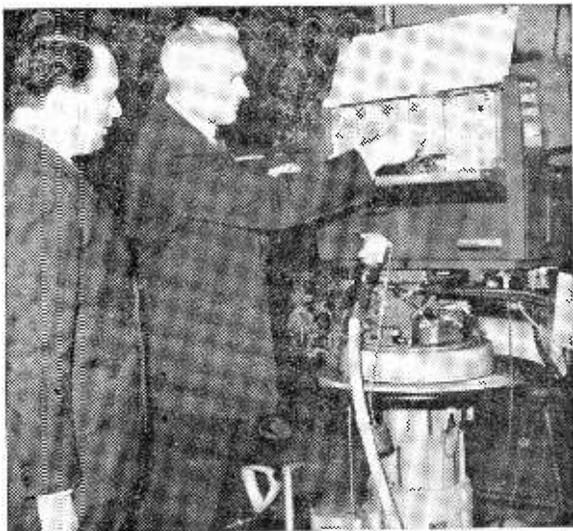
## Russian TV Experts Visit Britain

**D**R. S. Novakovsky, Director of the Scientific Research Institute on Television in Moscow, and three colleagues visited Britain recently, and at the invitation of The Marconi Company, made extensive tours of the Company's laboratories. One of the main reasons for their visit was to see the new Marconi Mark VII colour camera and in the photograph, Dr. Novakovsky (right) is shown examining the camera with Mr. Tom Mayer, Manager of Marconi's Broadcasting Division.



## Colour TV Servicing Exam

The City and Guilds of London Institute, in conjunction with the Radio Trades Examination Board, has introduced an examination in colour television servicing principles as a part of subject 48. There will be a three-hour paper and the first exam will be held in June.

The syllabus is a slightly modified version of the 1963 one and candidates will normally be expected to have passed the final in radio and television servicing.

## Colour from Belmont

**B**ELMONT (Channel 28) now carries experimental colour transmissions as follows:

Monday and Tuesday 14.00-14.15 Black and white test card; 14.15-14.25 Colour bars; 14.25-15.00 Colour slide; 15.00-18.00 As for 14.00-15.00, repeated; 18.00-18.30 Black level and syncs; 18.30-18.35 Colour bars; 18.35-19.15 Colour slides; Wednesday, Thursday and Friday 14.00-18.35 As Monday and Tuesday; 18.35-19.15 Colour slide followed by colour film.

On Wednesday, Thursday and Friday a colour film may be transmitted during the period 16.00-17.00.

## NEW RECEIVING AERIAL FOR BELMONT AREA

**B**ELLING-LEE Aerials have produced a new aerial-type 5U10/4A for use in the area of the new Belmont transmitter.

The new aerial is a combined v.h.f./u.h.f. model with 5 elements covering the whole of Band III, Channels 6 to 13, and 10 elements on Band IV, Channels 21 to 34. Two fully coupled folded dipoles provide band width and high gain and correct impedance matching to standard cables on Band III.

More information is available from Belling-Lee Aerials Ltd., Heysham Road, Netherton, Bootle 10, Lancashire.

## Practical Television Filmshow


**T**HE annual filmshow, organised jointly with Mullard Ltd., and Practical Wireless and Practical Television magazines is to be held as usual at the Caxton Hall, Westminster.

The date is Friday, April 14th and the show will start at 7.30 p.m. prompt.

The programme will include a film "Electrons in Harness" and a topical talk on "Transistors and Television".


Refreshments will be served in the interval. For further details of the filmshow, please see the next issue.

## as seen by others

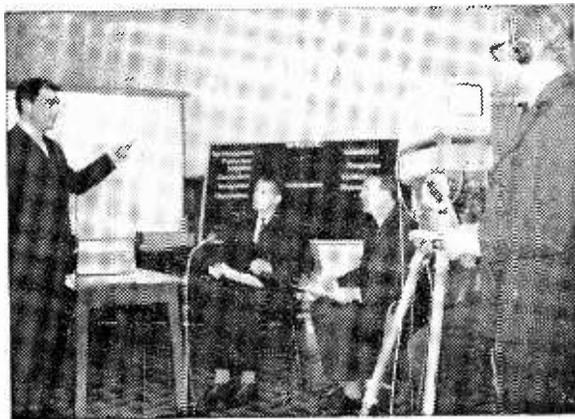

**L**INK 51 Limited, the international storage and materials handling consortium, have introduced closed-circuit television as a visual training aid for their technical storage representatives in Britain.

"Few people", said Mr. J. F. Suriano, Group Training Officer, "really appreciate the visual impact they make on others, and this medium of closed-circuit television can reveal both strengths and weaknesses in communication. It is not enough for our technical representatives to possess the necessary knowledge to solve industrial storage problems, they must be seen to possess it by those with whom they are negotiating. A televised feedback of a discussion between a manager and a colleague acting the role of an industrialist enables the former to analyse his presentation and also provides an opportunity for group discussion". The first of these televised training courses was produced by Zoom TV. Slough, for the Erecto slotted angle company, a member company of Link 51 Limited, at their Hayes, Middlesex, headquarters.

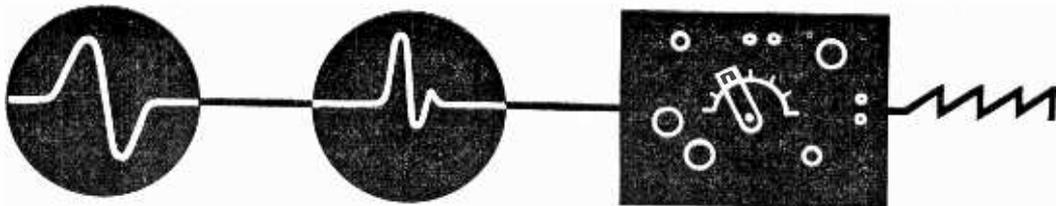

# WIDE-RANGE

# WOBBULATOR

D. R. BOWMAN B. Sc. A.M.I.E.R.E.

**M**ANY readers of PRACTICAL TELEVISION will have experience in the construction and operation of wide-band intermediate-frequency amplifiers necessary for the proper reception of vision signals. These experimenters may have also found that the correct alignment of the vision i.f. amplifier has presented problems. The development of a new circuit always involves the consideration of stage gain, unwanted feedback, overall bandwidth, layout and so on. Some will do it the easy way by beginning with the mathematics, some from inclination or necessity will rely upon experience and experiment alone. Eventually however, the i.f. amplifier is built and switched on, and the moment of truth has arrived: does it give the expected results?

A few years ago it was possible to get by, because vacuum tubes were simpler devices to use than transistors. The experimenter who uses valves still is better off in this respect than those who are more "with it" and are "going solid-state"; they are not handicapped by huge input capacitances, low input resistances and feedback capacitances that by pentode standards are of astronomical size.

Semi-conductor tuners and i.f. strips are appearing publicly, and the v.h.f. transistor receiver is now well established. Design and development for the amateur are going to be more difficult in the future, if more rewarding in their results.

## Frequency Sweep Methods

The device to be described is an all-transistor swept-frequency generator—or "wobbulator" which, correctly used with an oscilloscope, is capable of displaying the receiver response curve visually at a glance. Adjustments to the receiver r.f. and i.f. stages cause changes in this response curve, and these show up at once. If a wobbulator is not available the whole response curve has to be traced out laboriously with a signal generator each time a tuning core is rotated, and this can multiply the development time by a hundred without difficulty!

There are several methods of generating a swept-frequency signal, the easiest being to tune a signal generator rapidly through the pass-band of the amplifier under test, while displaying the amplifier output on the face of a cathode-ray

tube. If the time base generator is set to a slow speed, say one sweep per second, a rough idea of the response can be obtained from the signal trace displayed—if it happens to fall somewhere near the centre of the screen. In default of all else this helps. The next development along this line is to drive the tuning knob of the signal generator by means of a motor running in synchronism with the time base trace. Some very successful wobbulators have been designed for mechanical drive in this way. However, the system is not elegant, some would maintain that it is barbaric, and even if this is discounted there are some big disadvantages in the method, among them the fact that continuous tuning is hard to achieve, while intended variations in frequency sweep are not easy to arrange except by using detachable variable-capacitor vanes or similar artifices.

## Variable Reactance Devices

The reactance-valve, or its equivalent the reactance-transistor, represents a useful and popular way of going about it. This method has the advantage of being voltage-controlled or current-controlled and with no inertia or wear to worry about. While only relatively small frequency sweeps were required—from 5kc/s to 2Mc/s for example—it was, and probably is, the best method to use, especially in vacuum-tube circuits. There are ways of obtaining large frequency sweeps using variable-reactance devices, in any case, and no doubt a number of amateurs possess and use such instruments with every satisfaction.

The present design utilises a variable-reactance device as the frequency-sweeping element, but in this case the simple variable-capacitance diode is used. Readers will be aware that a semi-conductor diode is non-conducting when reverse voltage is applied because current carriers are attracted away from the p-n junction by the applied e.m.f.; the larger the reverse voltage the greater the attraction and the thicker the depletion layer becomes. Hence the junction capacitance falls with increased reverse voltage. Typical diodes of this type, useful at relatively high frequencies, may have depletion layer capacitances varying from about 3pF at about 20 volts reverse e.m.f. to about 10pF at about 1 volt reverse e.m.f.

Consideration of the conditions existing where such a diode is used to tune a circuit of oscillator frequency, say 34-37Mc/s is rewarding. Clearly, the best frequency sweep is obtained when stray circuit capacitances are small, so it will be assumed that a suitable coil has been wound which when tuned only with "strays" resonates at 37Mc/s. In a typical transistor circuit the OC171 might be used. The collector capacitance would be about 6pF, coil and wiring capacitance 1.5pF, and the minimum diode capacitance 3pF, making 10.5pF in all. At minimum reverse e.m.f. the variable reactance diode would add another 7pF, making 17.5pF in all.

Now frequency is inversely proportional to the square root of capacitance, so if these conditions prevailed the lowest frequency the oscillator could operate at would be  $37 \times \sqrt{\frac{10.5}{17.5}}$  Mc/s or 29Mc/s, giving a frequency sweep of 8Mc/s. This would suffice for testing the i.f. strip response of any TV receiver on the 405 or 625 lines standards. The chances are of course that rather less would be achieved—probably about 6Mc/s in all, which although satisfactory from a frequency point of view would be rather pushing one's luck.

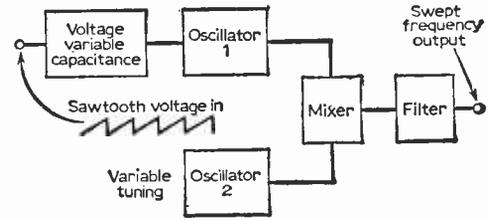


Fig. 1: Schematic diagram of the unit.

frequency. When the generated signal is applied to an amplifier, there is therefore a built-in non-linearity, which will tend to "skew" a response curve as far as the display is concerned; the amplifier will appear to give more amplification at the higher frequencies. Alternatively, an amplifier badly affected by Miller feedback, having a response curve with a large hump at the lower end of the pass-band, may appear to be relatively flat. Nobody will worry until the displayed picture in the completed receiver is horribly affected by "ringing", or turns out to be verging on instability.

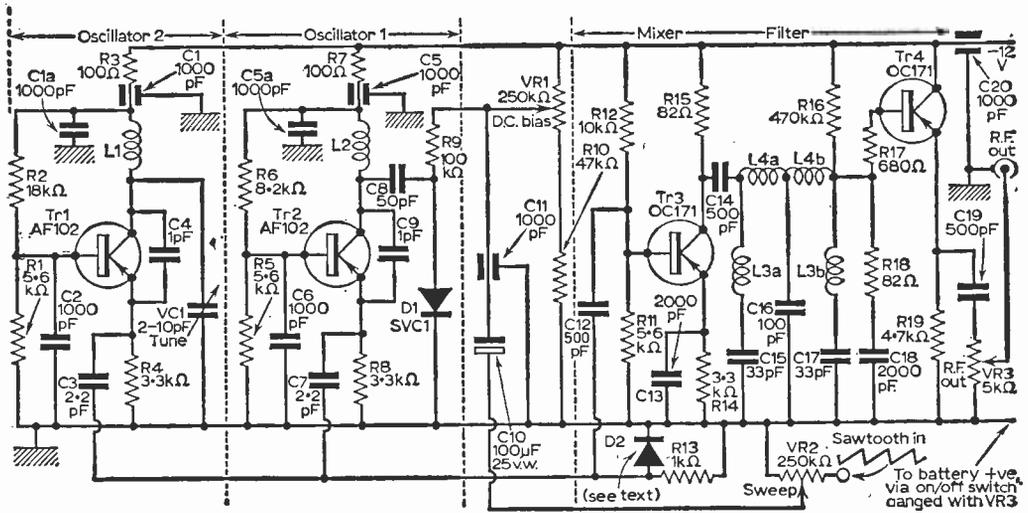


Fig. 2: Complete circuit diagram of the wide range wobblator.

At the same time the variations in load on the tuned circuit have to be considered, and when this is done the picture is not so gaily coloured. At considerable reverse e.m.f. the capacitance across the tuned circuit is small. The semiconductor material of the diode depletion layer carries a small r.f. current and losses in the equivalent series resistance of the diode are small; the oscillator output tends to be high. When the reverse e.m.f. is small the depletion layer capacitance is large, three or four times the r.f. current flows in the equivalent series resistance and losses are high; the output from the oscillator diminishes accordingly. Hence the output varies markedly with

Add to the above the fact that in transistor circuits, 12V is all there is available as a rule, and that the total capacitance range of the diode cannot be achieved, and it will be apparent that some further thought needs to be devoted to the design.

One approach to the problem arises from the observation that if small capacitance variations only are permitted, and these about some low value appertaining to a considerable reverse e.m.f., oscillator output is sensibly constant. Consider the situation existing if the frequency of oscillation is raised to 250Mc/s. Suppose a capacitance variation of 3pF can be tolerated, over this range the

oscillator output being sensibly constant. Then the frequency sweep will be  $250 \times \sqrt{10-15/13.5} \text{Mc/s}$  to  $250 \text{Mc/s}$ , or about  $30 \text{Mc/s}$ . This is highly satisfactory; in fact, it would be possible for most applications to use only a capacitance variation of  $1 \text{pF}$ , equalising oscillator output more effectively still; this would give a frequency swing of  $16 \text{Mc/s}$ .

The OC171 would hardly be usable practically in such a circuit, since its cut-off frequency is of the order of  $75 \text{Mc/s}$  and its transition frequency (at which gain = 1) is about  $120 \text{Mc/s}$ . This is also above its maximum frequency of oscillation. The AF102 is highly satisfactory for this application, and its output capacitance is of the order of  $2 \text{pF}$  thus reducing "strays" still further. Using this transistor, the oscillation frequency can be reduced to  $150-160 \text{Mc/s}$ , in between Band II and Band III, with ample frequency swing for constant output. The reason for this will be apparent later.

The only remaining problem is to convert the  $150 \text{Mc/s}$  frequency to the desired intermediate frequency and this is a relatively simple matter if normal frequency changing methods are employed.

## Difference Frequency

Fig. 1 shows the block diagram relating to the instrument. Oscillator 1 is the variable-frequency oscillator already discussed; its basic frequency is fixed, but because of the reactance-diode across the tuned circuit a sawtooth voltage input will sweep the frequency between limits dependent on the sawtooth voltage input and the residual capacitance in the circuit.

Oscillator 2 is so arranged that the tuned circuit associated with it can be tuned by a variable capacitor. When the vanes of this capacitor are fully meshed it tunes to nearly the same frequency as oscillator 1, and when the variable capacitance is reduced the frequency rises to some  $50 \text{Mc/s}$  above that of oscillator 1. Thus the difference frequency, which is detected in the mixer, varies between about  $0.1$  to  $1 \text{Mc/s}$  and  $50 \text{Mc/s}$ . This difference frequency is fed to the output terminal through a filter designed to attenuate frequencies above about  $45 \text{Mc/s}$ , thus minimising the escape of the waves generated directly in the oscillators.

The design of the mixer and filter will be discussed in due course.

Fig. 2 shows the complete circuit diagram for the instrument, and a number of circuit points may be mentioned at once. In the first place each oscillator is contained within a small aluminium can, the negative battery lead being taken through a lead-through capacitor for decoupling purposes. The sweep oscillator is supplied with its sawtooth input through a similar capacitor; this has negligible effect on the sawtooth at sweep frequencies of interest, but prevents the escape of radiation. The filter unit is similarly enclosed inside a can, which necessarily has to be of somewhat ampler proportions.

Secondly, the filter—whose inductors are L3 and L4 (two of each)—is associated with two transistors. The first provides a little gain, with the average transistor, but this is not its function; the real purpose of this transistor is to effect an impedance-match with the filter. It will be realised that a filter of this type is working near the practicable limits for "lumped" circuits when dealing with frequencies near those of television receivers, and to obtain reproducible results it is necessary to use reasonable values of circuit component. It would be pointless to aim at a circuit using for example  $1$  or  $2 \text{pF}$  capacitors of low tolerance, so a compromise has to be reached between the tolerances of capacitors and the accuracy with which small coils can be wound. The output is also obtained from an emitter-follower transistor, and a glance at the circuit will reveal that the termination of the filter is such that a very nearly constant resistance is presented to the filter whatever the setting of the output control.

## Diode Mixer

Output from the oscillators is taken at the emitter through a small capacitor ( $2.2 \text{pF}$ ) which feeds the signal into the diode mixer. This arrangement imposes less capacitive load on the tuned circuits, and represents a relatively low source impedance for the mixer. Less "pulling" between the oscillator results from this arrangement; it has been found quite practicable for the oscillators to operate at frequencies no more than  $100 \text{kc/s}$  apart, and  $465 \text{kc/s}$  can readily be generated if desired. However, a certain amount of jitter is bound to occur in even these stable oscillators, and if only  $0.01\%$ —negligible at  $150 \text{Mc/s}$ —this represents a random frequency inaccuracy of  $20 \text{kc/s}$  which is hardly tolerable at  $10.7 \text{Mc/s}$  as it is some  $4\%$ . At  $10.7 \text{Mc/s}$  the same jitter is  $0.2\%$ , and this can barely be seen on a  $6 \text{in.}$  oscilloscope, so the instrument can be used very effectively to generate  $10.7 \text{Mc/s}$  for the alignment of v.h.f. receivers.

R.F. current from the fixed-frequency oscillator (oscillator 1) is arranged to be much larger than

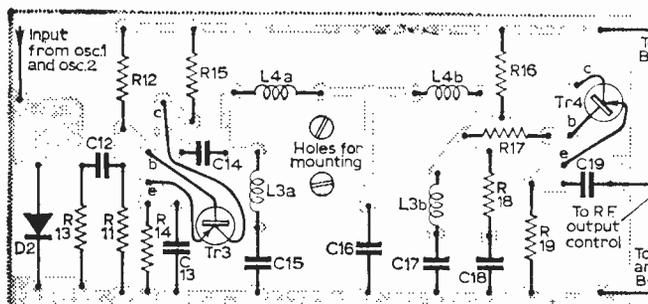


Fig. 3: Etched circuit board for the filter unit. Note: Layout of this unit is fairly critical, the filter operating at new Television frequencies

## COMPONENTS LIST

## Resistors:

R1	5.6k $\Omega$	R11	5.6k $\Omega$
R2	18k $\Omega$	R12	10k $\Omega$
R3	100 $\Omega$	R13	1k $\Omega$
R4	3.3k $\Omega$	R14	3.3k $\Omega$
R5	5.6k $\Omega$	R15	82 $\Omega$
R6	8.2k $\Omega$	R16	470k $\Omega$
R7	100 $\Omega$	R17	680 $\Omega$
R8	3.3k $\Omega$	R18	82 $\Omega$
R9	100k $\Omega$	R19	4.7k $\Omega$
R10	47k $\Omega$		

All 10%  $\frac{1}{4}$ W miniature

VR1 250k $\Omega$     VR2 250k $\Omega$  } carbon  
 VR3 5k $\Omega$  with switch

## Capacitors:

C1	1000pF lead through
C1a	1000pF
C2	1000pF
C3	2.2pF
C4	1pF
C5	1000pF lead through
C5a	1000pF
C6	1000pF
C7	2.2pF
C8	50pF
C9	1pF
C10	100 $\mu$ F 25V electrolytic
C11	1000pF lead through
C12	500pF
C13	2000pF
C14	500pF
C15	33pF 2% silver mica
C16	100pF 2% silver mica
C17	33pF 2% silver mica
C18	2000pF
C19	500pF
C20	1000pF lead through

All 20% ceramics unless otherwise stated

VC1 2-10pF air spaced variable

## Semiconductors:

Tr1 AF102, Tr2 AF102, Tr3 OC171, Tr4 OC171.  
 D1 SVC1, D2 microwave silicon diode (see text)

## Inductors:

L1 2 $\frac{1}{2}$  turns 18 s.w.g. enam. wire  
 L2 3 turns 18 s.w.g. enam. wire  
 L3/L3a 11 turns 26 s.w.g. enam. wire  
 L4/L4a 15 turns 26 s.w.g. enam. wire  
 See text for further details

## Miscellaneous:

Aluminium sheet, Veroboard, copper laminate, knobs, screening cans, two-pole two-way slide switch, coaxial socket, nuts, bolts etc.

that from the variable-tuning oscillator (2) and this is reflected in the differing values of base bias provided. Even so, the mixer diode is not being used as a highly efficient mixer, as the r.f. voltage does not swing the working-point far into the linear part of the characteristic curve. However, there is sufficient non-linearity to produce a respectable i.f. and a few microvolts output is in general all that is required for alignment purposes. If desired, the 680 $\Omega$  resistor in the base lead of the final transistor may be omitted; or, better still, a "high-output" lead taken from the filter termination direct for preliminary alignment purposes or for testing individual stages of an i.f. amplifier. The termination will be approximately correct for a 75 $\Omega$  coaxial cable.

## Low Pass Filter

The mixer diode used in the prototype is a microwave silicon diode, which has to operate at 150-200Mc/s, so the usual OA70 will not be very suitable. The microwave diodes available are frequently of the "coaxial" type, and small clips will have to be fabricated from strip brass (such as can be got from a spent cycle battery) to obtain good electrical contacts with mechanical rigidity.

The filter is designed as a low-pass filter cutting off sharply at 45Mc/s, with a characteristic impedance of 80 $\Omega$ . It consists of a centre section of "constant-k" type, with two half-sections of the same impedance as input and output terminations, each of "m-derived" type. This classical type of filter suffices to keep most of the v.h.f. away from the output terminal, and in fact works better than was expected! Much depends on the care taken in constructing the filter, and some constructional points will next be mentioned.

The filter, with the mixer diode and the two associated transistors, is in the prototype, built on a small piece of copper-clad laminate, appropriately etched, which fits into an aluminium can 2in. diameter and 3 $\frac{1}{2}$ in. long. Such cans can often be obtained—empty, of course, from one's local chemist. The paint is best removed with a paint stripping solvent such as Polystrip or Nitromors. The laminate is cut to size 2 $\frac{1}{4}$ in. by 1 $\frac{1}{2}$ in. and the circuit etched as shown in Fig. 3.

The inductors are wound on a 11/64in. drill shank with No. 26 s.w.g. enamelled copper wire, close-wound. The wire is put on by hand, taking great care that the turns are lying closely side by side, with no gaps. For L3 inductors about 11 turns will be put on first, and for L4 inductors about 15 turns. The wire is then allowed to spring back, and the loose coil will then be 3/16in. inside diameter and will fit with a very slight push on to the shank of a 3/16in. drill. The end turn is removed leaving 9 $\frac{1}{2}$  turns for L3 inductors and 13 turns for L4 inductors.

The ends are carefully trimmed to lie at right angles to the coil, and are cut to length of  $\frac{1}{4}$ in. The end  $\frac{1}{4}$ in. is cleaned and tinned, unless the wire is of the self-fluxing variety.

*To be continued*

# "LOCKED OSCILLATOR" F. M. DISCRIMINATOR

by S. George

WHILE the conventional radio detector is used in many dual-standard TV receivers, there is now a growing tendency to use the EH90 "Locked Oscillator Discriminator" as the f.m. detector, on four main points. (1) It is more economical in design than the conventional ratio detector, since the expensive r.f. transformer is replaced by one simple tuned circuit, while the matched duo-diodes and triodes are eliminated. (2) The circuit has very good amplitude-limiting characteristics. (3) It gives an extremely high a.c. output so that in most commercial designs, the EH90 output directly feeds the sound output pentode, while on 405 it can act as an a.f. amplifier to boost the output from the 405 a.m. detector. (4) The output for a given f.m. deviation is constant irrespective of signal strength.

## Simplified discriminators

Pentodes were used in a simplified form of such discriminators in American receivers, but the present day heptode circuit is the outcome of considerable development by the Mullard Research Laboratories to improve the function of this type of discriminator, and we are indebted to them for much information contained in this article.

All such f.m. discriminators function by virtue of the fact that the anode current of the detector is a function of the phase relationship between two similar frequency sine waves applied to two different grids. Also when an a.c. voltage is applied to the control grid, the electron stream passing through the suppressor grid to the anode, induces a facsimile voltage on the suppressor but lagging by 90°. Such coupling is known as "space charge" coupling and if G3 is returned to cathode via a parallel tuned circuit, the valve becomes analogous to a tuned-grid-tuned-anode oscillator. Over a fairly restricted frequency range, the oscillation produced at the suppressor grid "locks" to the applied input signal the "lock-in" range increasing with increased signal input. Outside this range however, the oscillator fails to synchronise with the input

and beats occur. Inside the "lock-in" range, when the f.m. signal deviates slightly from the tuned circuits resonant frequency in accordance with the modulation, the phase difference between the two r.f. signals is no longer 90° but increases or decreases according to the direction of the frequency shift. Anode current being a function of the two signals phase relationship an a.f. output representing the difference between them is developed across the anode load resistor.

## Space charge coupling

For most effective operation, the valve used should have high "space charge coupling". This implies that the electron stream should have a large effect on Suppressor grid potential or in other words that the gm (G3-A) will be high. The EH90 heptode is particularly suitable in this respect, and superior to a conventional pentode.

## Discriminator circuit

Figure 1 shows the basic EH90 discriminator circuit with L2 being the "quadrature" coil damped by the 39kΩ resistor for optimum gain and "lock-in" range. The G2/4 screen is fed via a low resistance fixed potentiometer network to prevent variation of f.m. output with signal level, while omission of the cathode bypass capacitor compensates for valve input capacitance change with voltage and assists limiting action by negative feedback.

Figure 2 shows an EH90 dual-standard sound circuit (GEC/SOBELE) in which the valve functions as an a.f. amplifier on 405 (sound output stage is not shown). Such discriminator circuits give little trouble, are relatively insensitive to component tolerances, and only the resistors in the screen grid fixed potentiometer network and the cathode lead need be of 10% tolerance. Valves in this mode are very free from microphony and valve replacement has

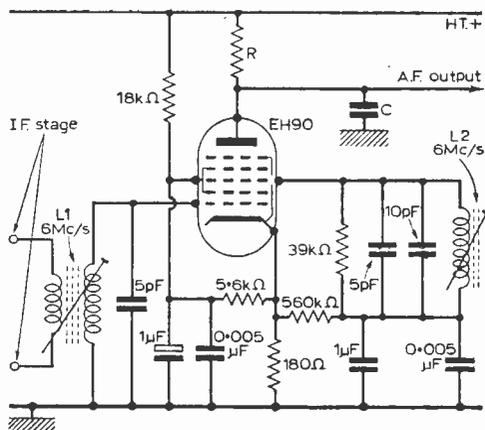


Fig. 1: Basic EH90 'Locked Oscillator' f.m. discriminator. Space charge coupling between G1 and G3 induces a replica of the input frequency on the latter but lagging by 90°. F.M. variations of the input signal then produce slight variations of this phase disparity to produce an a.f. signal across the anode load resistor.



# STOCK FAULTS

## PREVALENT TROUBLES IN COMMERCIAL RECEIVERS

### NEW SERIES

### PART 9: Tuner Units

**I**N and around the tuner unit, more care is needed, because of the higher frequencies involved, where the length of component lead-out wires is a significant inductive and self-capacitative factor, and where component placing and the siting of connecting wires can drastically affect the tuning. Often it is worth spending a little more time diagnosing the fault, making proving tests and eliminating possibilities, before probing about vainly in the electronic undergrowth.

Far and away the most prevalent is the breakdown of a current-carrying resistor: usually the common h.t. feed, or the resistor in series with the oscillator anode, where valved tuner units are employed. We are so used to this fault now, on many different units, that the preliminary proving tests are almost habitual among the servicing fraternity. First, are there faint clicks through from the aerial, and perhaps small flashes on the raster? Do we get clicks and crashes as we rotate the turret or press the buttons and keys? If so, it is a fair bet that h.t. is reaching the tuner and, if absent, is being lost where it divides to feed different parts of the circuit.

If the tuner is 'lively' yet the correct signals cannot be tuned in, the next point to suspect is the oscillator, and again, the most likely trouble (apart from some tuning problems we shall come to later) is lack of h.t. voltages. Often, quite small resistors are used in these h.t. feed circuits, and it needs only a small flashover to burn them out. More likely than this is deterioration through constant use—hot and cold cycles of daily wear causing 'ageing'. When this occurs, though there may still be h.t. present, it may not be enough to sustain oscillation.

### TUNER H.T.

Testing for h.t. with a meter is straightforward enough, the drawback being the near impossibility of getting the average probe to the exact position one needs for the test. Without a meter, it may be necessary to make a 'spark test'. Highly unofficial, this! A screwdriver blade touched quickly between a high tension carrying point and chassis should provide a small spark. For the brief moment of the test, the short-circuit will not damage resistors or blow fuses, but there can be a real danger of burning out the fine wire of some coils.

A glance at Fig. 43 reveals that the popular method of supplying h.t. to the tuner unit is by divided and separately decoupled paths from the main h.t. line of the receiver. This source point

may itself be filtered, and if there is no h.t. at all reaching the tuner, the filter circuit and its decoupling capacitor should be checked. Note that the h.t. feed to the triode oscillator section of the PCF806 is via a 12k $\Omega$  resistor, but that the pentode mixer section has a series feed circuit with decoupling from the junction. This is partly because of the value of resistor needed and the power dissipation, partly to provide the correct frequency-conscious circuit dependent on the physical placing of the components.

H.T. to the r.f. triode is via a parallel pair, in practice a single tapped component, whose position is as shown in Fig 44, adjacent to the valve base. In this model, the components are fairly easy to reach and replace; other units seem designed to defeat such an exercise. This type of permeability-tuned unit is found in the Bush TV135 and 138 range, and the Murphy V923 and 929. Known as the A490, it has four push-buttons which can be arranged to select any combination of Band I and Band III stations by altering the switch actuating tab which is secured to the rocker bar by a rub screw.

To remove the unit, take out one hexagon-headed bolt and withdraw from the rear. It is easier to disconnect the plugs (power and i.f.) from the main panel. The cover can be removed by a slight pressure on the blunt end, raising a bit, then disengaging the other end.

Having chosen whether the appropriate button has to tune BBC or ITV, slacken the grub screw, reposition the tab (downwards for Band III, upwards for Band I) and refit the base. Then, all that is necessary is to press in the button, which operates the bandswitch shown in Fig. 43, pull it gently out until its flange is felt to engage the tuning spindle, and turn till sound and picture tune in, and slide the button clear of the spindle. Selection of another button neutralises the engaged one. This is a streamlining of a common Bush principle, and is very similar to other types of tuner.

An earlier type of Bush tuner, such as used in the TV125 series, also had four push buttons, but was intended to be set for two stations on each band, and altering to receive one Band III and three Band I channels, quite a common requirement, is a bit more difficult. The button to 'doctor' is the inside Band III button, whose switch actuating block should be set upward normally, and can be altered to a downward position for BBC reception. An adjustable core stop which is usually employed to set the neutral return positions of the Band I buttons can be set to tune to the position

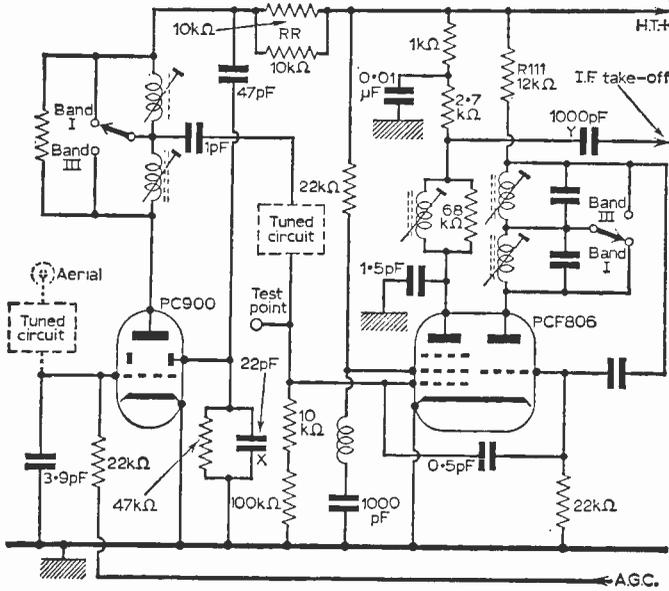


Fig. 43: Permeability tuner for Bands I and III.

taken up by the outside BBC button and then selected by the second button, by first tuning the signal, then slackening the Philips screw on the stop (available through the bottom of the cabinet).

Although we cannot spend too much time on the obvious stock fault of poor h.t., it may be as well to mention that several manufacturers recognise the vulnerability of these resistors and helpfully mount them outside the body of the tuner. (Of course, they have an ulterior motive; heat dissipation). Others, such as the Plessey push-button tuner and the Bird tuner used in Defiant receivers, had their h.t. resistors hidden away in the intestines of the unit, while some of the Philips designs are of particular awkwardness.

**CAPACITOR BREAKDOWN**

A fault with similar effect but more confusing to trace is breakdown of one of the feed-through

capacitors carrying the h.t. line into the tuner unit. One of the common symptoms is an apparent high h.t. current drain, which makes one suspect a valve fault. The valves are replaced and the trouble persists. But switching between channels momentarily regains h.t. voltage at the external feed point. In these cases, suspect a leak across the silvering of one of the feed-through capacitors, or perhaps cracked ceramic of its tube. There is no real solution, but an effective cure is to remove the capacitor altogether, rewire the h.t. line through the hole, make a joint as near the hole as possible, but insulated safely, and connect a 1,000pF bypass, soldered to the body of the tuner as near the original point as possible (see Fig. 45).

Where BBC-2 signals are in order and v.h.f. does not come through, there are two possibilities. First is the r.f. valve, which is not used on u.h.f., second the oscillator of the v.h.f. mixer-osc. If the trouble is not h.t., and valves

are in order, check the system switching, especially the a.g.c. line, which is altered externally, usually on the main slider switch section on the i.f. panel.

Patterning on odd channels is not an unfamiliar fault, and may often be caused by a breakdown in decoupling, generally between the r.f. and mixer stages. In Fig. 43, where a triode r.f. valve in earthed cathode mode is used, the 22pF capacitor marked "X" is part of the neutralising circuit and open-circuiting will cause a severe herring-bone pattern in certain parts of the country.

Leaky coupling from the tuner unit is another problem that can cause peculiar symptoms. Where the leak puts h.t. on the grid of the succeeding common i.f. valve, or upsets the a.g.c. line (the voltage limited by intervening components) symptoms of overloading may be found. This can often be checked by operating the system switch, when the fault may temporarily clear. Check the feed-out capacitors in such cases: Y in Fig. 43 is an example.


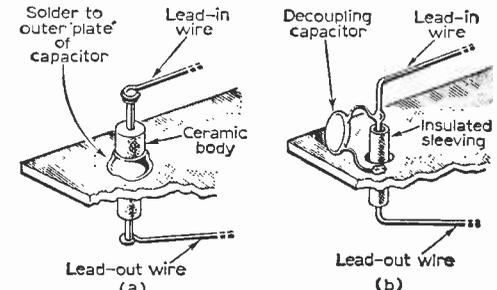


Fig. 44 (left): Permeability type tuner used in the Bush TV135 and 138 series.

Fig. 45 (above): Two methods of replacing faulty lead-through capacitors.

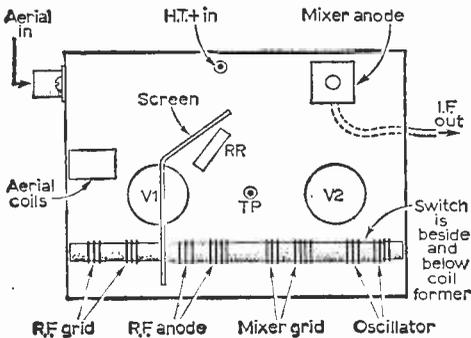

nylon cap on the end of a metal pin (shoulder end goes to the tube side of the capacitor, when replacing, losing the pin is the usual dismantling penalty!) and the plastic tube has the nylon end inwards.

The cam setting is regulated on Band I, adjusting screw A to the mid-position for the channel to be received, having turned the fine tuner knob (depressed to locate the screw) to mid-position. After this, turn to the local Band III channel and tune the grub screw B for best picture and sound. When tuning these modern units, often it is better to set the receiver up slightly toward the sound carrier, i.e. for best sound. Any variation to obtain best picture can be made with the fine tuner knob. A word of warning, too. There are, as we have implied, two main types of tuner. The type discussed has coils with a prefix GB, has an internally mounted i.f. coil and screening skirts to the valveholders. The valves are PCC189 and PCF86. In other sets, coils with GP prefix are used and though these appear similar, they are not interchangeable. In these tuners, the rotor lug comes between channels 2 and 3, and PCC89 and PCF80 valves are employed.

The tuner slug operated by a cam is used on tuners by K-B and GEC as well as Philips, though in a slightly different circuit formation. In these, breaking of the slug can cause queer symptoms, the usual being that one channel appears to drift and another to tune up perfectly until the rotor is turned, when a lot of jiggling is necessary to get the signal back.

Although it may be a poor solution to turn the set on its side each time we change channels, this is the only alternative to repairing the broken slug! However, do not despair, the slug can generally be pushed right through the tube with an orange stick, and can sometimes be repaired with that indispensable aid, Araldite.

On earlier Philips types, if the core is tight in the former, application of a small amount of heat from a soldering iron held near the former can assist removal. Tightening a slider type slug in a former may need the addition of a sliver of elastic. A justifiable remedy, even if the makers do frown on it!

### AERIAL CONNECTION

On some Pye tuners, a prevalent fault was the breaking of connections of the aerial coil at the rear of the rotor. This usually led to poor Band I reception, and the cure was to resolder the tail end and gently reposition the coil. Where incremental tuners are used, as popularised by Pye in earlier days, care must be taken not to alter positioning of coils. The same stricture applies to many of the later units, very different physically, but electrically similar in technique.

### NEXT MONTH

It was intended to end this series with the present article. But tuners offer us much scope for discussion and we need to take a look at transistorised tuners, methods of u.h.f. coupling and mechanical tuning drives and, space permitting, some aerial troubles and their cures. These subjects will be dealt with in our concluding article, next month.

**NEXT MONTH IN**

# Practical TELEVISION

## TV EHT METER

Constructional details of a reliable test unit for the higher voltages. Five ranges (100V, 300V, 1.5kV, 10kV and 30kV), stabilised meter zero, micro-corona damage protection, full overload protection for meter and circuit, switch for positive or negative polarity. Absolutely safe to use, this instrument uses transistor printed circuit construction and can be either mains or battery powered.

## DECODING PAL

As the months go by, colour TV comes nearer. Of the various circuit elements in a colour receiver perhaps the decoder is the least well understood. Here is an authoritative article describing the principles involved. Brush up on your colour theory while there is time!

## 625-LINE UHF PROBLEMS

A valuable article analysing the problems most encountered by readers in 625-line u.h.f. TV, concentrating on the symptoms of grainy picture, instability and sound troubles.

ORDER YOUR COPY ON THE FORM BELOW

TO \_\_\_\_\_ (Name of Newsagent)

Please reserve/deliver the APRIL issue of PRACTICAL TELEVISION (2/-), on sale March 23rd and continue every month until further notice

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

# HUM IN TELEVISION RECEIVERS

V. D. Capel

**W**HEN hum manifests itself in a television receiver, first suspicions are usually directed to the smoothing circuits, especially the smoothing capacitor. There can, however, be many causes of hum in a TV receiver and its effect can be detected in many different ways. Let us consider the smoothing circuits first.

The first leg of the smoothing circuit is provided by the smoothing choke, which is an iron-cored inductor designed to possess the maximum inductance possible for its size. The impedance offered by any inductor to a current flowing through it depends mainly upon the frequency of that current. The impedance is less as the frequency decreases and is almost zero for d.c., the only opposition then offered being that due to its ohmic resistance. Hence while the d.c. h.t. current flows through the smoothing choke with little opposition, a fair impedance is offered to the 50-cycle a.c. ripple current. With most television receivers half-wave rectification is employed, hence the ripple will be 50c/s. Where the rectification is full wave the ripple will be 100c/s and so twice the impedance will be presented by the smoothing choke, hence the smoothing circuit will be more efficient.

## SMOOTHING HUM

The smoothing capacitor has exactly the opposite effect to the choke, this offers a very high opposition to d.c. current but presents a low impedance to alternating currents. Hence whereas the smoothing choke is connected in series with the h.t. supply line, the smoothing capacitor is shunted across it. Less impedance will be offered to a frequency of 100c/s than to one of 50c/s, so, as with the smoothing choke, the capacitor will be more effective with full-wave systems.

Theoretically, ineffective smoothing could be due to either of these components being defective but in practice it is nearly always the capacitor which gives rise to trouble. If the smoothing choke goes open circuit, the result will be no reception at all as the h.t. supply will be interrupted. Failure of the smoothing capacitor, on the other hand, will result in an a.c. ripple being passed along the h.t. line to all circuits of the receiver. The result will be that the sound circuits will be modulated with the familiar hum, also vision, sync and time base circuits will be affected to some degree, varying with different receivers. For example, it is sometimes found that the vision exhibits a black hum bar across the screen whereas the hum on sound is only slight. In other cases it may be that the hum bar is only slight and the main effect on the vision is poor line sync. If the hum is manifested in several circuits, then it is fairly safe to say that the smoothing capacitor is the cause of the trouble.

Receivers are sometimes found with their smoothing capacitors bridged by another one. Presumably the original became defective and a repair was effected by connecting the replacement across it. It is bad practice to leave a defective capacitor in circuit since the original may be passing a high leakage current which could result in an unnecessary load being placed on the h.t. line, and the capacitor may become heated or even explode. The writer has seen cases where this has happened.

The smoothing capacitor is commonly combined in the same can with the reservoir capacitor. If the smoothing capacitor has become defective then it is likely that the reservoir also will soon show a defect even if this is not the case already. While it may be more expensive, it is prudent to replace the complete unit if any section should be faulty. Even if this is not done the defective capacitor should be completely disconnected and a replacement fitted to a separate tag connection.

Another possibility which can prove quite baffling to the uninitiated is a leakage between the smoothing and reservoir capacitors within a common can. Such a leakage in effect shorts out the smoothing choke and hum in all circuits will result just as if the smoothing capacitor had gone open-circuit. The normal practice of bridging the

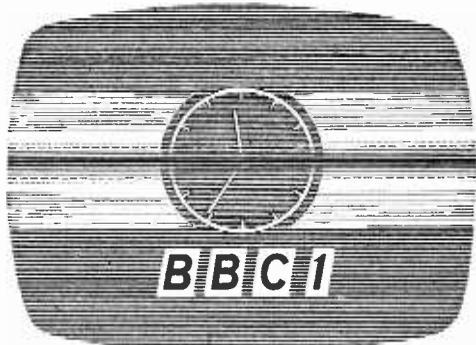


Fig. 1: Hum on vision.

suspected capacitor with a test one will hence not produce any results. The leakage between the sections will not normally be measurable with an ohm-meter due to the low d.c. resistance of the smoothing choke connected between them. If smoothing is suspected because several circuits of the receiver are affected with hum, and if temporarily bridging the smoothing capacitor gives no improvement, then this possibility of leakage between sections must be investigated. The way to do this is to disconnect one section and to temporarily wire in a substitute. The most

convenient one to disconnect will generally be the reservoir capacitor as usually there are only two wires connected to it, one to the rectifier and the other to the smoothing choke, whereas the smoothing capacitor may have a number of feeds to various h.t. circuits.

## WIREWOUND RESISTORS

Many receivers use wire wound resistors in place of smoothing chokes. Circuit operation is different in principle from the smoothing choke as now it becomes a simple decoupling arrangement such as commonly used in other parts of the receiver. It is not so effective as the choke, as a high value of resistance should be used to achieve sufficient decoupling at 50c/s and this value will, of course, cause a loss of h.t. potential across it and so restrict the h.t. voltage to the receiver. Furthermore, heat will be generated in the resistor to add to that present from the various other sources. Cheapness, size and weight makes this a popular alternative with many set manufacturers. Although the principle of operation will, as we have said, be different, our remarks on fault finding with smoothing choke circuits still apply to those using smoothing resistors.

## HEATER/CATHODE LEAKAGE

A further major source of hum is that of leakages between valve cathodes and heaters. Most valve heaters are fed from raw a.c. by being connected in series across the supply mains through a suitable value dropping resistor. Some receivers use a rectifier in place of the dropping resistor and omit a reservoir capacitor so that a suitable reduction in voltage can be obtained. This arrangement has the advantage of cooler running for the receiver due to the absence of heat from the main dropper. Because there is no reservoir and smoothing circuit for this d.c. supplied heater chain, there will be a.c. ripple on it. Hence any heater/cathode leakage within a valve will put a.c. potential on the cathode. While some cathodes, such as those used in output circuits, are generally bypassed by high value capacitors, this is not always the case and any a.c. on the cathode will, as a result, modulate the valve anode current and produce hum in the circuit.

Hum from this source will usually affect only one circuit and so can be easily identified by this manner. If there is hum on sound and yet the picture betrays no trace of hum whatsoever, it can be assumed that the hum is originating in the sound circuits and most likely will be due to a heater/cathode leakage in one of the sound valves. Any of the valves could be responsible, from the first sound i.f. valve to the sound output. Generally though, hum originating from before the detector possesses a different character sound to that coming in at a later point. This is due to the fact that the fundamental 50c/s rarely gets past the detector circuit without undergoing considerable modification to its wave-form. This means that harmonics will be generated and will predominate in the resulting signal. If the hum is harsh with more the characteristics of a buzz, then it is probable that its origin is before the

detector stage; on the other hand, should the hum be pure and deep in tone then most likely the fault is in the audio circuits.

## HUM ON VISION

Another common manifestation of hum is in the vision circuits. Usually this takes the form of a black band near the centre of the screen. If the hum frequency is the same as the field frequency then there will be one band, but if a full wave system were used then the frequency of the hum would be 100c/s and two horizontal bands would be in evidence. The fault will most likely be a leakage in the video valve or in one of the i.f. valves. First, carefully examine the picture to see that the band really is due to modulation of the video signal and not to a wider spacing of the scanning lines. The two effects are very similar when viewed casually, as the areas where the lines are spaced wide apart will have a lower overall illumination than where they are normal. Any such variation in line spacing can also be attributable to hum but in this case the hum will be in the field circuit. When checking these valves by substitution, remember that in many receivers there are three valves or parts of valves which are involved. Some models use a multi-vibrator consisting of two triodes. These may be the triode parts of triode-pentode valves, the pentode section of which are used for other purposes such as sync or video output. Either of these plus the output section are, of course, suspect. As multiple valves normally use separate cathodes then only one section will

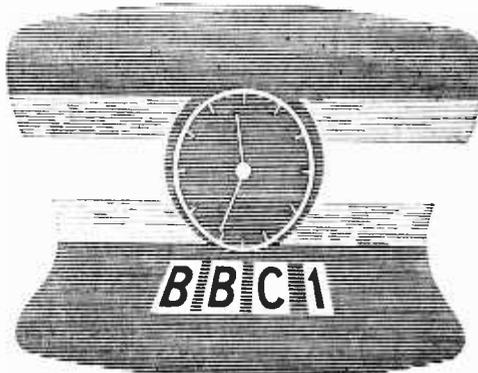


Fig. 2: Hum on line.

be affected by any heater/cathode leak. An exception to this rule is the ECL80 valve which has a common cathode for both sections, hence any leak between the heater and the cathode will affect both circuits alike.

When hum appears in the line circuits, the effect is unmistakable. The vertical edges of the raster become shaped like the letter S. The precise effect will depend a lot upon the circuit. For example, output stages that have their cathodes taken directly to chassis, the bias being provided by the negative drive on the grid, will not exhibit any hum effects at all. In such cases any cathode leakage will effectively bypass the

heater current from the rest of the heater chain, and as the line output valve is normally connected in the top half of the chain, it will mean that it and the valve above it, normally the boost diode, will glow very brightly and the rest of the valves only dimly. If the leak is severe then excess current will flow and the fuse will blow. When hum modulation effects of the line are evident, most professional engineers will change each of the valves in the line circuit in turn until the defective one is located. The amateur repairer may not have a wide selection of valves at his disposal and may have to obtain valves specially, in which case he will not want to get the wrong ones. In such a case it would be wise to check if the cathode of the line output valve is taken directly to chassis. If this is so then the hum cannot be due to this stage and will most likely be found in the line generator. If, on the other hand, there is a low value cathode resistor as fitted by many makers (this being done in order to limit the anode current in the event of a failure of the line oscillator to provide sufficient negative drive on the grid), then the line output valve could be the cause of the hum modulation. If the trouble is, in fact, due to the line output valve, and the resistor is momentarily shorted out, the hum modulation should disappear. If it does not then one of the other line valves should be checked. Should the hum modulation of the line be very pronounced it would be unwise to short the line output cathode resistor in this way as this would indicate that the leakage was heavy and shorting the resistor would immediately draw a heavy heater current through the valve with the possibility of further damage.

## SYNC HUM

An effect of hum perhaps not so obvious is when it affects the synchronising circuits. A heater/cathode leak in the sync separator valve will cause lack of synchronising in both line and field circuits. Again the precise effect will vary from model to model, in some cases one timebase will be affected more than in another, and in a few cases one timebase may seem to be hardly affected at all. Synchronising can also be affected by heater/cathode leaks in the video circuits. Here it will also be accompanied with the bar on the picture. There have been cases where such leaks in the video circuit have produced very little shading of the picture and yet have seriously affected the synchronising. Where sync faults are experienced then, it would be as well to change video valves as well as the sync separator.

## LEAKAGE—TUNER AND I.F.

Another effect that can be obtained by a heater/cathode leakage is the one produced by a leakage in either of the tuner valves or in the common i.f. As these circuits are common to both sound and vision any leakage in one of these valves will produce hum on sound and vision. For this reason it is easy to confuse this effect with that produced by a defective smoothing capacitor. There is one difference which should be looked for before a definite diagnosis is made.

When the smoothing capacitor is at fault not only are sound and vision circuits affected but also some trace of hum will most likely be found in the timebases. These, however, will not be present if the fault is in the tuner or common i.f. The rule is then, when investigating a set that has hum on sound and vision, to make a close examination of the edge of the raster. This may be done by reducing the width control or by moving the picture over by means of the picture shift until the edge becomes visible. Any sign of curvature will indicate smoothing troubles, whereas if the edge is perfectly straight then the fault will probably be as described in the tuner. As a further check an examination of the lines themselves can be made to see if they are all equidistant or whether there is any compression and expansion over the raster. When doing this be careful not to mistake poor field linearity for hum.

## VISION ON SOUND

Another easily recognised source of hum is vision on sound. This is not really hum at all but takes the form of a harsh buzz. Its source is not due to any a.c. component reaching the sound circuits from the mains, but as its name implies, is due to the vision signal finding its way into the sound circuits. Misalignment of the i.f.'s will produce this trouble, but before attempting to alter the alignment of the i.f. coils it is prudent to check one or two other details.

A common cause of this trouble is overloading due to too strong a signal. If the set has a sensitivity control then try turning it down. If there is no such control then it may be necessary to fit an attenuator in the aerial lead. If the set had been working satisfactorily in that location without alteration to the aerial then it is unlikely that the signal strength would suddenly increase to cause overloading in this way. It is possible, if a sensitivity control is fitted, that this may have been turned up accidentally by the user. If a new aerial has been fitted or a new set installed then the signal strength may be too great and need the attenuation as described. The a.g.c. system on most modern sets has a sufficient range to take care of all except the very highest signal levels, so the more likely explanation in such a case would be a fault in the a.g.c. system itself. As the contrast control is often tied up closely with the a.g.c. system, it can be checked by operating the control to see whether the picture can be turned right down. If the contrast control makes little difference to the picture then a fault in the a.g.c. system would be indicated.

A similar fault to this is sync on sound, caused by synchronising pulses, particularly the field pulses, getting into the sound stages. Normally this can only be caused by some components or valves that are common to both circuits. Some early Philips receivers employed an ECL80 triode pentode with the pentode as the sync separator and the triode connected as a diode sound detector. Interaction between these two sections led to sync pulses being injected into the sound detector circuit. Often several new valves had to be tried before one was found that would be free from the trouble, so a modification was used whereby a germanium diode was used

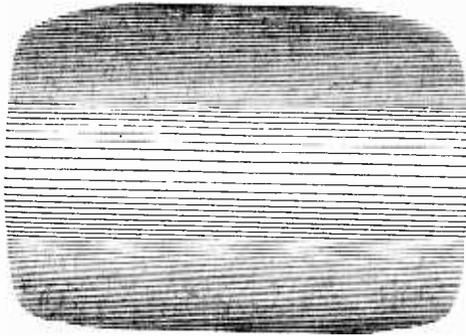


Fig 3 Hum on field.

in place of the triode. Sometimes sound and sync circuits may have a common decoupling capacitor which, if it goes open circuit, will lead to unwanted coupling between the two.

A fault which has a very similar sound is that caused when the sound is modulated by field pulses. It can very easily be distinguished from vision on sound or sync on sound by altering the field speed control. If the buzz is due to the field circuit the pitch of the note will alter immediately. Most likely cause of this trouble is open circuit h.t. decoupling.

### GRID HUM

Yet another type of hum is that known as grid hum. This is due to there being no d.c. path between the grid and cathode leaving the grid "up in the air". This means that the impedance of the grid circuit is now infinity and under these conditions will be very sensitive to any stray hum fields that are about. Open circuit grid leaks are mainly responsible, although anything that is open circuit in the grid path, including dry soldered joints, will give this same effect. Hum from this source tends to be more harsh than normal although not so much of a buzz as that caused by sync, vision or field pulses reaching the sound circuit as described earlier. Grid hum can also appear in both vision and sound circuits and will give very similar symptoms to that already described.

It can be seen that there is far more to curing hum than just changing the smoothing capacitor. If the circuits affected are carefully observed then a speedy diagnosis and cure should result.

### AERIAL RIGGERS' INTERCOM

December issue 1966

There is an error in Fig. 1 on page 120. The battery connections to tags 5 and 6 are shown inadvertently interchanged. This may be corrected by swopping over the two battery leads, also the tag numbers 5 and 6 at the connections to the printed circuit board.

## Book Reviews

**COLOUR TV TROUBLE CLUES**  
By the PF Reporter Editorial Staff. Published by Foulsham-Sams Technical Books Ltd. 128 pages, 8 1/2 in. x 5 1/2 in. Price 18s.

THIS book is written entirely from the practising serviceman's angle, citing actual cases of colour-TV troubles, including some really tricky ones, describing the symptoms, the tests made, the instruments that make them, and the clues to particular faults.

It is a painless method of instilling knowledge and to be recommended, provided the British reader always bears in mind that the eventual system on this side of the water will differ in some respects from the trans-Atlantic model.

Even if one has no intention of touching a colour-TV set—at least until familiarity has taken the edge off apprehension—the technique of imparting knowledge by passing hints and off-beat tips that this experienced group of writers has adopted should be of benefit to any television enthusiast.

Long live George, Herb and John, who appear to be blokes just like us, not some strange race of colour-gifted super-servicemen.—MAQ.

**SERVICING TRANSISTOR TV**  
By Robert G. Middleton.  
Published by Foulsham-Sams Technical Books Ltd.  
223 pages, 8 1/2 in. x 5 1/2 in. Hard covers. Price 30s.

THIS book, despite its transatlantic origin, has the advantage of topicality. A growing number of receivers are employing transistors and the wholly transistorised TV will be the norm as certainly as the solid-state set has ousted the valved radio from its pride of place. Most of the TV circuitry is applicable to UK designs, and the servicing advice that Mr. Middleton gives is universal.


After one chapter on general considerations, i.e. typical circuitry, transistor circuit testing, expected voltages, Test Card analysis and a look at the special cathode ray tubes employed, he goes systematically through the transistor TV circuit, from tuner to power supply in ten well-written chapters.

Each chapter begins with a section describing the stage of the receiver under the spotlight, then enters into a general discussion of its peculiarities, proceeding to describe fault symptoms and tests in commendable detail, and concluding with a short questionnaire on the whole chapter.

This method is maintained throughout, helped by the generous amount of circuits, waveforms and picture symptom photographs that we have come to expect from this author.

The book is thus a useful reference volume as well as an easily-read text for the television engineer or spare-time enthusiast who has not yet had the opportunity of handling these quite different circuits—but knows he most certainly will.

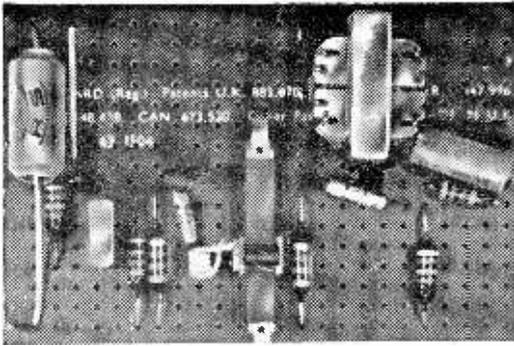Forewarned is forearmed, and this volume is as good as any we have seen to help build up one's stock of specialised knowledge.—MAQ



# TELEVISION PRE-AMP

## Baby Alarm

By A. Thomas

THE circuit described has been in constant use, with germanium transistors, for the past four years. Now that silicon transistors are easily obtainable and are relatively inexpensive, the author recommends that use is made of them. The original circuit has, in fact, been modified to accommodate them on a piece of Veroboard, which can be mounted almost anywhere on the television chassis. One should, however, be careful to keep the preamplifier away from components working at high temperature.

### CIRCUIT DESCRIPTION



Figure 1 shows the final circuit. As it can be seen, the microphone input is fed via a miniature transformer which isolates the microphone from the television chassis. In some instances the TV chassis may be at mains voltage. If this is the case the L and N leads should be reversed. The microphone used by the author was a low impedance balanced armature type (a telephone earpiece, but any low impedance microphone with

a reasonable output may be used). One can use a high impedance microphone if the circuit is modified; by including an emitter follower in the input to carry out impedance matching, as shown in Fig. 2.

The first stage employs a common emitter low current amplifier as does the second stage which has a potentiometer as a volume control in its collector. Output from the final stage, also a common emitter, is fed via a d.c. blocking capacitor and a high value resistor to a suitable audio point on the television set. The high value resistor

Fig. 1 (below): Circuit diagram of pre-amplifier.

Fig. 2 (right): Impedance matching unit that can be added to the standard circuit to enable a high impedance microphone to be used.

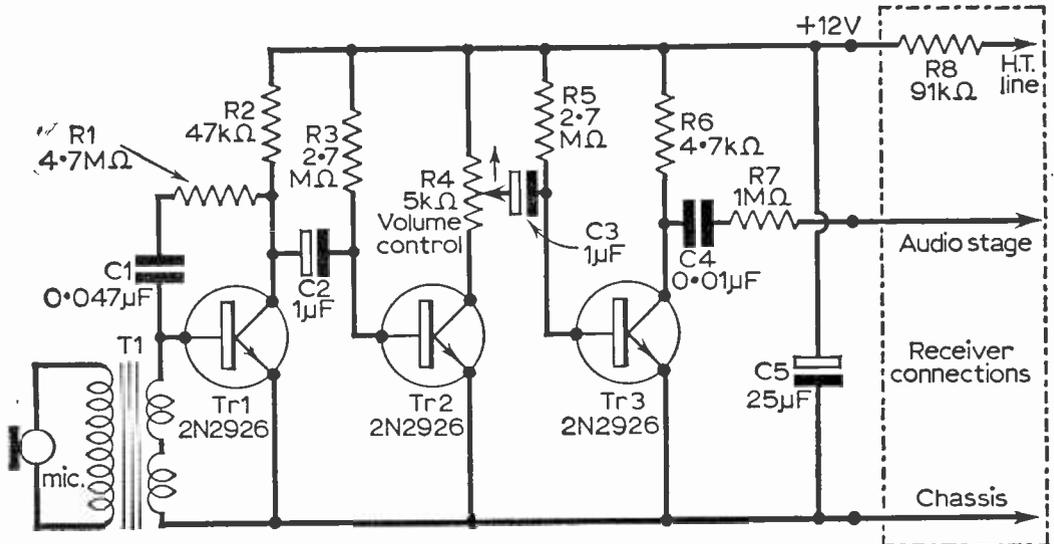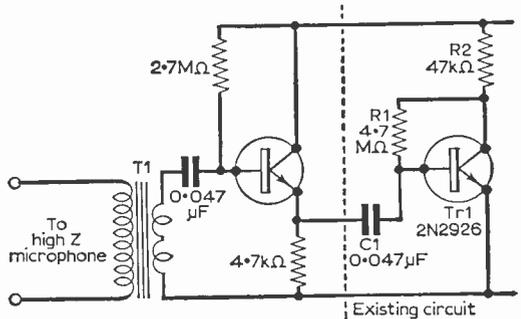

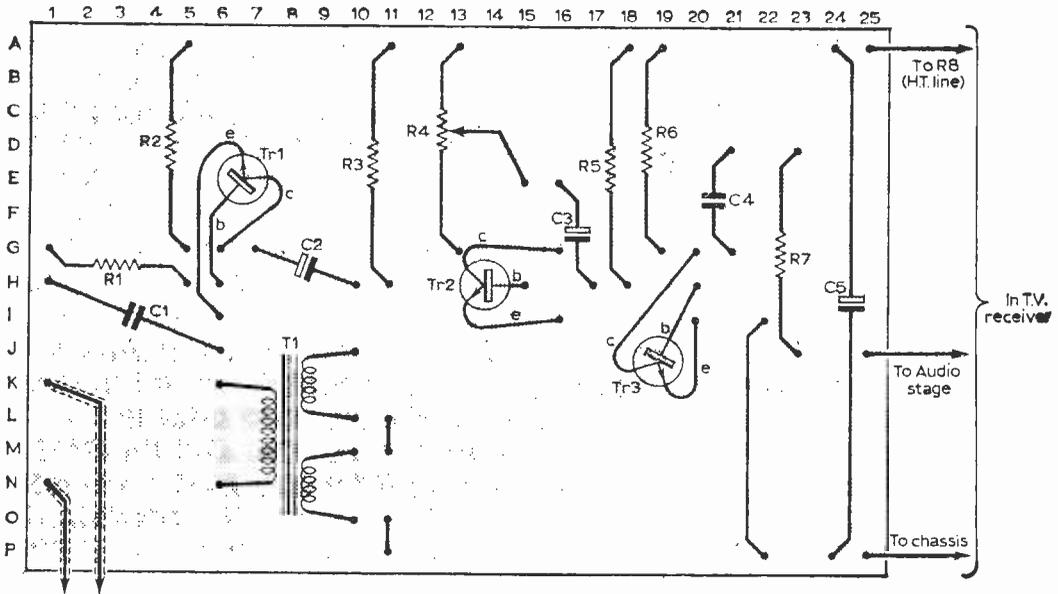


Fig. 3: Suggested component layout of the standard circuit using Veroboard

prevents the transistor amplifier from loading the normal television sound signal, but because of it a greater output voltage is required from the amplifier than would otherwise be the case.

On the author's set, a KB SV30FM, the most convenient point to inject the signal is on the wiper of the sound volume control. A general ruling cannot be given on the best place to inject the amplifier output, but the grid of the output stage

is a good starting point on an unknown set. If a circuit diagram is available then the place may be chosen with ease. The signal connection from the amplifier to the set must be screened to prevent spurious signals being fed to the output stage.

The power to feed the amplifier can be taken from the main h.t. line of the set and fed via a dropping resistor to a decoupling capacitor. The drain from the h.t. line will be in the order of 2.5mA and will not adversely affect the television receiver. The h.t. may be tapped at any convenient point, the main smoothing capacitor often being the most suitable since one could go onto the boosted h.t. line by mistake. For the sake of safety, the dropping resistor R8 should be inserted at the h.t. end to ensure that high voltages do not appear on the Veroboard.

A 12V Zener diode may be used as a voltage regulator but is not thought necessary as the regulation of the transistor line voltage will not adversely affect the amplifier or the transistors.

If the Light programme or Home Service is heard in the output, this is due to it being picked up by the long microphone lead; it may be removed by putting a 0.01µF capacitor between the base and emitter of the first transistor.

**CONSTRUCTION**

As previously mentioned, the amplifier is constructed on a piece of Veroboard as shown in Fig. 3. No difficulty should be encountered as there are only sixteen components.

The microphone input lead may be terminated in a coaxial plug, with a coaxial socket be mounted on the back cover of the TV. This can then be disconnected when not required. An on/off switch may be wired into the 12V power supply, but this was not thought necessary by the author. ■

**COMPONENTS LIST**

**Resistors:**

- |                         |          |
|-------------------------|----------|
| R1 4.7MΩ                | R5 2.7MΩ |
| R2 47kΩ                 | R6 4.7kΩ |
| R3 2.7MΩ                | R7 1MΩ   |
| R4 5kΩ (preset, slider) | R8 91kΩ  |

**Capacitors:**

- C1 0.047µF, 400VW
- C2 1µF, 15VW
- C3 1µF, 15VW
- C4 0.01µF, 250VW
- C5 25µF, 25VW

**Transistors:**

Tr1-Tr3 2N296 (Green Spot)

**Miscellaneous:**

Radiospares transformer type T/T3, microphone (see text), Veroboard, screen lead, etc.

# THE WORLD OF SERVICE

Part 3:  
THE  
SPECIALIST  
ENGINEER

By G.R. Wilding

**B**ECOMING a service specialist represents the easiest way for the competent service engineer to branch out on his own, for in the radio and television business it is becoming increasingly difficult for the small man with limited capital to compete with the national companies as a "selling" dealer. To the utter disbelief of the general public, no one makes a mint from pure service work, or at least no one the writer knows after lifetime of experience. It is easy, of course, for the layman to form that idea, and although (as in all trades) overcharging *does* occur, the customer is apt to overlook that additional to the time spent by the service engineer in his home attending to his set, there are the overheads of shop or workshop premises, van or car running costs, time travelling to and from the service call, phone bills and instrument upkeep. Conversely I know many "company" outside service engineers making up to 15 calls a day who think on the lines of "If only I made a clear pound from each call, that would add up to £75 a week for five days' work".

The problem with this presumption is that to get an average of 15 paying calls per day, due to the high incidence of TV rental, one would require a bigger area of coverage than the average shop has. Furthermore, most receivers owned by possible clients are far from new, since most dealers offer two years' free maintenance with new sets: neither are set owners prepared—nor indeed is it good economics—to spend much time and money on sets whose life expectancy is limited.

Most set owners only want minimum servicing to keep the set working "till they get a new one". The slogan used to be "till the new lines come out," but now as TV is losing its grip and BBC-2 holds little attraction, in many instances, customers who don't like renting, consider that the general level of programmes fails to merit buying a new set. Also many sets are owned by pensioners and other people in the "lower income groups", to whom one is compelled to charge what may well be considered uneconomic rates.

There is no false charity about this work. If after being called to see a TV, and finding it old and in need of extensive repairs, circumstances sometimes compel one to make a nominal charge to cover whatever replacements and service work is unavoidable to produce acceptable results. The alternative is to waste the time and expense involved making the call at the house. It is far better to accept each individual case on its merits—at least cover working costs and leave the set owner well disposed. At the other extreme,

exorbitant charges are the surest way of losing goodwill, no matter how high the income group of the customer.

While service work on average will produce a satisfactory income, *the cream comes from the sale of new receivers to those customers who over a period of time have found you to give good and attentive service.* You will be expected to take their old receiver in part exchange, but there is seldom any real objection to this as there is always a ready market for good used models, especially to your own clients happy to accept your personal assurances.

## RECONDITIONING

The most lucrative part of being a service specialist is reconditioning used television receivers. As the number of service calls varies constantly, to keep fully occupied one must always have sets in the workshop awaiting attention. So at regular intervals you go around all the larger Rental Companies and buy their part-exchange stock, usually *en masse* and at what might seem ridiculously low prices, i.e. £5 for a complete car or van load. Many sets will be fit only for scrap, but as it can be quite a problem disposing of old receivers, most companies are prepared to sell you a bulk lot very cheaply so long as you *do* take the lot. There will always be some very good buys among them, and the beauty of reconditioning receivers is that once you know the types that give little trouble, you get the equivalent of the selling price for repairing it, since individually they cost no more than £1 when bought in bulk.

By spending some time on a known good type and possibly changing several valves plus, say, the rectifier, a few capacitors, any doubtful sections on the breakdown resistor and possibly a few pre-set controls, one can obtain up to £15 for them easily. It never pays to transfer seemingly tolerable valves from scrap sets to those you are about to recondition. Unless valves are obviously new and have been fitted by the set owner in a last minute attempt to solve the defects, discard them. Putting a new replacement in a reconditioned model where required will save a subsequent journey to the customer's home and having to change it there, apart from eliminating the customer's complaint.

There are many service engineers who say that they never seem to make any worth while money out of reconditioned receivers, but I have always found them to be the best part of the business.

Some independent service engineers run their own maintenance schemes, generally averaging about 3s. 6d. a week for 17in. or 19in. receivers

following a complete overhaul at owner's expense. Possibly the most characteristic factor about TV service is that whoever wants it, and for whatever reason, wants it right away. If you mention car repairs or even servicing to a garage proprietor, they invariably murmur something about being free to look at it next Thursday or Friday. This is not so with TV repairs. Any request for TV service carries the unspoken assumption that it will be that day, and that you have been waiting their call to jump into action: so much so that if you don't advertise "Same Day Service" or "Radio Controlled Vans", you won't get much business.

## MOBILE WORKSHOP

The "ABC Mobile Workshop" type of approach which more or less guarantees to do any TV repair "on the spot" finds considerable favour. "After all", argue set owners, "if rental customers can get same day, on the spot attention—why not private set owners?" Many set owners accept some pretty low reception standards, undoubtedly caused by the insidious nature of many set faults. For instance, after replacing a line circuit valve and restoring vision, you will possibly find vertical linearity way out, a badly contacting channel selector, maladjusted fine tuner or sensitivity control, focus off optimum and considerable variation in gain as the coaxial lead is moved about or the cabinet is knocked. On drawing the owner's attention to these faults, the reply usually takes the form of "we never noticed" or "we thought the set was getting worn out". I have seen wooden chips jammed under channel selector knobs to improve ITA reception, rasters that take up to half an hour to fill the screen, EY86's so low in emission that scene changes constantly changed picture size and focus, intolerable sound-on-vision and vision-on-sound and focus so poor it was impossible to distinguish the individual lines.

All these faults and many more like them are tolerated by the owners for long periods, but ultimately lead to the set going off altogether. In the vast majority of cases, far from the set being "worn out", an hour or so of quite simple servicing will completely restore the set.

## TOP OVERHALL

This is where (to borrow a phrase from the motor industry) the "top overhaul" comes in. This means cleaning and adjusting the channel selector, setting the fine tuner where fitted so that both stations are received with the same knob setting, changing (probably) the field output pentode, r.f. amplifier, video pentode or sync separator where tests so indicate, cleaning the volume control and the pins of all valves which produce picture or sound variations when "rocked", adjusting for optimum focus, balancing Band I/III reception, checking leads and plugs, setting subsidiary gain controls for best sensitivity with freedom from inter-modulation of sound and vision, and finally setting up on Test-Card "C".

The price charged need not amount to more than a few pounds, depending on the number of valves used, but on seeing the transformation that such basically simple work produces, the owner

will often assure you of his continued patronage and consider you a TV genius: so long as it doesn't go off again!

Unfortunately customers have the idea that once a service has been performed it automatically invalidates any further failures for at least six months. Change a video pentode and a subsequent fuse-blowing PY33 will be deemed your personal responsibility and in some way entirely entirely your fault. "After all—I paid you 35/- the other week". Often a customer's idea of a week in this respect is about a month, a month equates to six calendar months, and "some time ago" is undoubtedly a couple of years.

## NEW VALVES

Quite often when called to service a set, you will notice one or two gleaming new valves, and it usually transpires that the owner took all the valves to the nearest radio shop for testing. Obviously in any receiver after some years of use, every valve will have depreciated in emission to some extent. Many valves, such as those in the sound section, can reduce to 50% efficiency and still give adequate output, but set owners optimistically believe that any valve indicated by the testing machine as being below par will automatically cure whatever complaint the set has. Attempts by the shop assistant to clarify the indication are often regarded as pure guile. Try and convince a customer that replacement of a low emission PL82 will fail to make any difference to poor BBC reception!

Similarly, customers buy new valves because they suspect run "too hot" or "too cold" or quite honestly for reasons I am never able to discover. I would say that on average, seven out of ten valves bought over the counter by the layman are completely unnecessary and inapplicable to the curing of the complaint.

In America hardly 1% of television receivers are rented, giving the TV repairman the whole field open to his services. However in this country the situation is almost reversed and the larger the city, the higher the incidence of rental customers.

## PRACTICAL ELECTRONICS

MARCH ISSUE

### PHOTOFLASH SLAVE UNIT

A small synchroniser for remote operation of more than one flashgun


### PROXIMITY DETECTOR

A highly sensitive photo-electric 'early warning' device with a variety of applications in the house, garage, garden, etc.

PLUS

### THE OSCILLOSCOPE AND ITS APPLICATIONS

ON SALE NOW—2/6

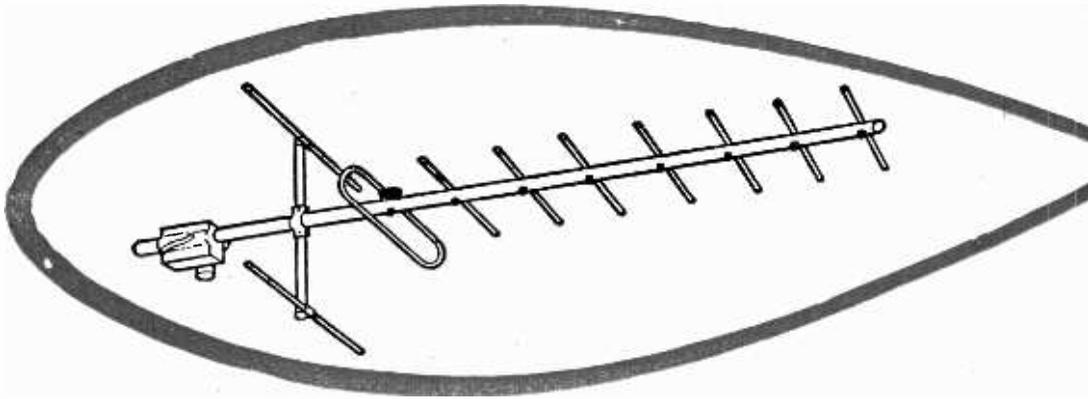

**T**HERE are more than three times as many usable channels in the u.h.f. television bands than there are in the v.h.f. television bands. Each local reception area will eventually have a group of four u.h.f. channels: these groups have already been established. To start with, only one of the u.h.f. channels in these groups is used for BBC-2. Later the other three allotted channels will be put into use, probably to radiate colour-TV, ITV-2 and educational-TV (ETV).

If an aerial for each u.h.f. channel were needed, each household would at some time in the future require four u.h.f. aerials plus the ordinary v.h.f. aerials. Fortunately, this impossible situation will never arise because the majority of groups of four channels will run from co-sited stations and the u.h.f. aerial should have sufficiently wide bandwidth to embrace the frequency spectrum of the group of four channels as a whole.

Grouping of the u.h.f. channels has been arranged so that in most areas the four channels come within an 11-channel grouping, thus the aerial requires a maximum bandwidth of 88Mc/s. In a few areas of the country it has been impossible to maintain this ideal pattern, and in these places of special channel allocations there is a wider frequency span.

Table I

ELEMENT LENGTH AND SPACING DATA IN INCHES	FORMULA, WHERE f IS FREQUENCY IN Mc/s
Dipole	$5616/f$
Reflector	$5976/f$
First Director	$5400/f$
Subsequent Directors	Progressive 2.5% red.
Reflector/Dipole Spacing	$3052/f$
Director/Dipole Spacing	$1546/f$
Director/Director Spacing	$1546/f$

It has been agreed among makers of u.h.f. aerials that the u.h.f. spectrum be divided into three groups of channels. These channel groups are lettered "A", "B" and "C" and colour-coded

Table II

U.H.F. TELEVISION CHANNELS, FREQUENCIES IN Mc/s

Group "A"			Group "B"			Group "C"		
Channel	Sound	Vision	Channel	Sound	Vision	Channel	Sound	Vision
21	477.25	471.25	39	621.25	615.25	52	725.25	719.25
22	485.25	479.25	40	629.25	623.25	53	733.25	727.25
23	493.25	487.25	41	637.25	631.25	54	741.25	735.25
24	501.25	495.25	42	645.25	639.25	55	749.25	743.25
25	509.25	503.25	43	653.25	647.25	56	757.25	751.25
26	517.25	511.25	44	661.25	655.25	57	765.25	759.25
27	525.25	519.25	45	669.25	663.25	58	773.25	767.25
28	533.25	527.25	46	677.25	671.25	59	781.25	775.25
29	541.25	535.25	47	685.25	679.25	60	789.25	783.25
30	549.25	543.25	48	693.25	687.25	61	797.25	791.25
31	557.25	551.25	49	701.25	695.25	62	805.25	799.25
32	565.25	559.25	50	709.25	703.25	63	813.25	807.25
33	573.25	567.25	51	717.25	711.25	64	821.25	815.25
34	581.25	575.25				65	829.25	823.25
						66	837.25	831.25
						67	845.25	839.25
						68	853.25	847.25

# POINTS ABOUT U.H.F. AERIALS

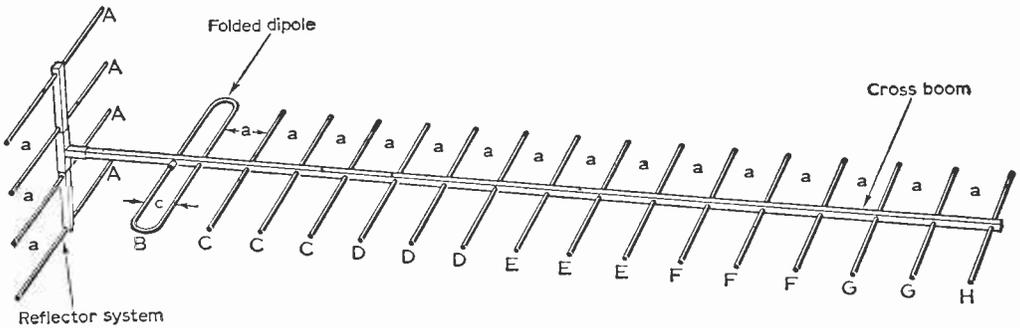


Table III

DIMENSIONS IN INCHES

CHANNEL GROUPS	A	B	C	D	E	F	G	H	a	b	c
"A"	10.9	10.8	9.5	9.0	8.9	8.3	8.0	7.8	4.45	4.45	0.7
"B"	10.4	8.45	7.4	7.1	7.0	6.5	6.3	6.1	3.5	3.5	0.7
"C"	9.15	7.15	6.25	6.0	5.9	5.5	5.2	4.8	2.95	2.95	0.7

Fig. 1: Eighteen-element 'in-line' Yagi. From the dimensions given in Table III, it is a simple matter to construct a 'Group' aerial for u.h.f. reception.

red, yellow and green respectively. Group "A" takes in all the channels of Band IV (channels 21 to 34), while Groups "B" and "C" together cater for all the channels in Band V (channels 39 to 51 and channels 52 to 68 respectively). This grouping of channels means that an aerial or aerial amplifier purchased for the reception of BBC-2 in any given reception area will also respond to the other channels of that area's group when they become active. Some early u.h.f. aerials and amplifiers were 'peaked' to the first channel to go on the air (carrying BBC-2), and this applies especially to home-made equipment.

## WIDEBAND AERIALS

Wideband aerials do not rapidly fall away to zero response outside their designed spectrum so it is possible that a fairly powerful signal outside the group would be received reasonably well on the originally installed aerial. In areas such as these, and there are not very many, aerial manufacturers will probably design units with bandwidth in excess of the normal channel groups. Already it is possible to get aerials with a wider bandwidth than the normal channel group.

Enthusiasts will always want to try for reception of distant u.h.f. channels, and already this is happening in places distant from the u.h.f. stations

at present on the air. The author, for instance, has been receiving Channel 24 from the Isle of Wight over a distance of 100 miles. This cannot be considered as 'normal' reception, for a u.h.f. station does not consistently 'illuminate' an area extending much more than about 30/35 miles. Nevertheless, u.h.f. DX activities are likely to become popular as more and more u.h.f. stations go on the air and for this a 'peaked' or single channel aerial is best.

Most constructors, in fact, design their own aerials for a specific frequency, and formulae for determining the optimum lengths for the elements and spacings are given in Table I. To assist with the construction of such aerials, Table II gives the sound and vision frequencies of all the u.h.f. channels. Note: channels 35, 36, 37 and 38 are not yet allocated for television broadcasting in the United Kingdom.

Wideband aerials are far more difficult to design than single-channel units, as one has to achieve consistent matching, polar response, gain and so forth over the spectrum. It is not just the matter of working out element lengths and spacings. Much more is involved during basic development work dealing with tests of directivity, polar response and matching while the actual aerial is being 'tailored'. There are no 'standard' formulae available for determining these parameters and a

considerable amount of trial-and-error work is involved.

A wideband u.h.f. aerial has to be developed as a complete unit, with a little added to the reflector, for instance, and a little taken from the directors as the practical development progresses until the end product satisfies all the various factors mentioned. There is more than one way of achieving the requirements, and it is for this reason that element lengths, spacings and so on of aerials of different manufacturers and home-designs rarely seem to be consistent.

The elements may differ a little in length and the spacings may not be the same; some makers may stipulate a balun in the aerial between the dipole and coaxial downlead and others may not; some makers may adopt specially-shaped dipoles while others stick to the conventional design seen in v.h.f. arrays.

As more and more u.h.f. channels become active, the possibility of co-channel interference will become very real. Protection from this interference is possible only at the aerial, and the front-to-back pickup ratio of the aerial will become important. The Post Office recommendation to manufacturers is for a front-to-back ratio of at least 16dB.

## EXPERIMENTAL ARRAY

While u.h.f. aerials are not unduly expensive, enthusiasts will almost certainly want to make one. Table III gives experimental statistics for wideband arrays in Groups "A", "B" and "C" relative to the eighteen-element 'in-line' Yagi shown diagrammatically in Fig. 1.

The aerial has one reflector system, folded dipole and fifteen directors. The reflector system can be made up of four spaced elements, as shown in Fig. 1, or of a piece of metal mesh whose square is equal to the dimensions given in column "A" of Table III.

It is not intended here to detail actual methods of aerial construction since these have been given on numerous occasions. The aerial can be made for either outdoor or attic mounting,  $\frac{1}{2}$ -in. diameter aluminium or alloy tubing being highly suitable in either case. The reflector and directors are not connected to anything electrically, though their centre points may be in contact with a metal boom. Similarly, the unbroken side of the folded dipole may be connected to a metal boom at its centre, but, of course, the two ends across which the feeder is connected must be insulated from each other and from the metal cross boom.

This sort of aerial will have a relatively high gain, a good front-to-back ratio and will be highly directional. This latter factor makes it necessary to orientate the aerial very carefully on a transmission for maximum signal pickup.

If this is done on a receiver, the line hold control on 625 lines should be carefully adjusted so that the picture is just slipping out of line lock. The aerial should then be rotated first one way and then the other for the maximum pickup, indicated by the picture pulling into line lock.

It is not usually possible to orientate on picture strength proper, as this is ironed out by the set's a.g.c. systems. One could probably orientate for minimum picture grain, but small variations in grain (i.e., picture noise) are not easily discernible. ■



## CAN ANYONE REMEMBER?

**SIR,**—I wonder if any of your readers could cast their minds back to the days of medium wave television using the original Baird system and, in the light of their experience, help me to obtain some data I require to assist in the building of a photographic type of facsimile recorder for use with the American weather satellites, *Essa II* and *Nimbus II*. At present I am using a direct recording process which, though simple and convenient, cannot reproduce the finer gradations of the picture.

The information I require is (a) the type of lens system used to project a minute spot of light at a distance of some few inches and (b) details of a device which I believe was called a "Kerr Cell" which was used to modulate a fixed source of light with the picture information.

Although only a schoolboy when the 30-line TV system was in use I can remember some of the details, but I have really no idea where to start making inquiries.—**J. B. TUKE, GM3BST** ("Torbank", *McMasters Road, Stranraer, Scotland*).

## VIEWMASTER COILS

**SIR,**—Can any reader of this journal supply me with details of Channel 1 coils for a Viewmaster TV? The original coils were made by *Wright and Wearie Ltd., London and South Shields*, and were *Wearie iron-cored coils* (Channel 3). I want to change to Channel 1.—**ALEX CAMPBELL** (1 *Lochaber Road, Kinlochleven, Argyll*).

## ISSUES REQUIRED

**SIR,**—Could any readers sell or lend me a copy of the December, 1964, edition of *PRACTICAL TELEVISION* or the article containing details of the *P.T. Videoscope* from that issue?

I am willing to pay the full price of the issue plus any postage expenses that may be incurred.—**R. M. DUNKLEY** (80 *Third Avenue, Dagenham, Essex*).

**SIR,**—I would like to buy or borrow some copies of *PRACTICAL TELEVISION* so that I may get them photostatted. They are *January, 1964* (I have *February, 1964*) and any of the following issues which contained the articles on the *Flying Spot Transparency Scanner*, also *December, 1964*, and any issues containing articles dealing with the *Olympic II Transistor TV Receiver*.—**B. CAMERON** (84 *Pownall Street, Masterton, New Zealand*).

*The Editor does not necessarily agree with any of the opinions expressed by his correspondents.*



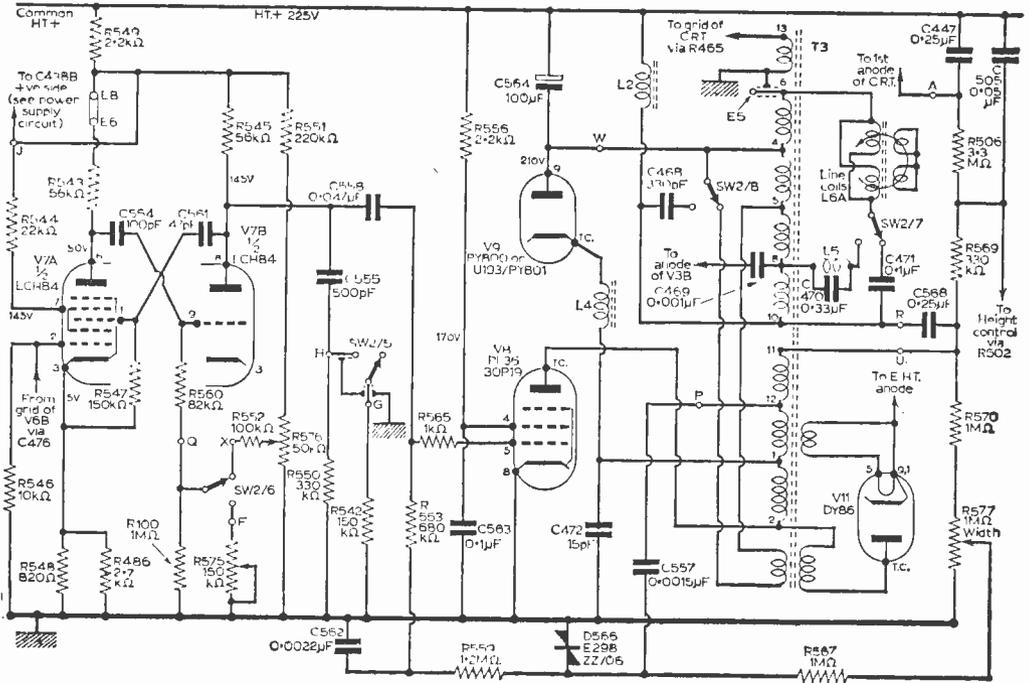


Fig. 5: Circuit of the line timebase

the brilliance control but that there is no picture modulation. The first suspect here is the video amplifier V3 (PCL84). Even though this valve may be defective a replacement will not always restore normal conditions if the faulty valve had an inter-electrode short. The diode (0A70) contained in II-TV3 may be damaged as a result. Secondary casualties may be resistors R123 and R152. Check all others for correct value, R115, R109, R122, R124 (18k $\Omega$ ) can change, causing incorrect operating conditions for V3, resulting in poor sync and incorrect contrast. Damage may occur to 122 etc., with a virtual h.t. short once R123 2.2k $\Omega$  can no longer tolerate the heavy current flow, and itself changes value.

### The field timebase

V10 (PCL85) is the field oscillator-output valve. A horizontal straight line across the centre could well mean that the valve has failed altogether, but if the valve is not at fault, voltage readings should be taken at pins 1 and 6 to ensure that these are present. Low or no voltage at pin 6 should direct attention to the field output transformer primary. Absence at pin 1 indicates the necessity to check R503 (680k $\Omega$ ), and height control, R502 (470k $\Omega$ ). C505 (0.05 $\mu$ F) could be shorted, thus dropping the available voltage not only to the height control but also to the c.r.t.

1st anode (pin 3) where the low voltage would still be sufficient to resolve a fairly bright straight line.

### Bottom compression

This is a fairly frequent fault which can usually be attributed to a failing PCL85 or an open circuited capacitor C501 (500 $\mu$ F).

However, it is sometimes the case that neither is at fault, and when this is so, capacitor C511 0.0022 $\mu$ F should be checked, together with other linearity circuit components. The bottom compression may be accompanied by actual fold-over showing that the PCL85 is being driven into grid current. In this case check the PCL85 then capacitors C507 (0.003 $\mu$ F) and C511 (0.0022 $\mu$ F) for leakage.

### Weak sync

Where it is difficult to lock both holds i.e., the picture tends to roll up or down and be erratic in a horizontal direction, attention should be directed first to V6 (ECH84) and associated components, particularly resistor R531 (680k $\Omega$ ). Check video stage resistors if necessary. If only the vertical hold is affected check V6 pin 8 and pin 9 components and the interlace diode 0A79 (D526).


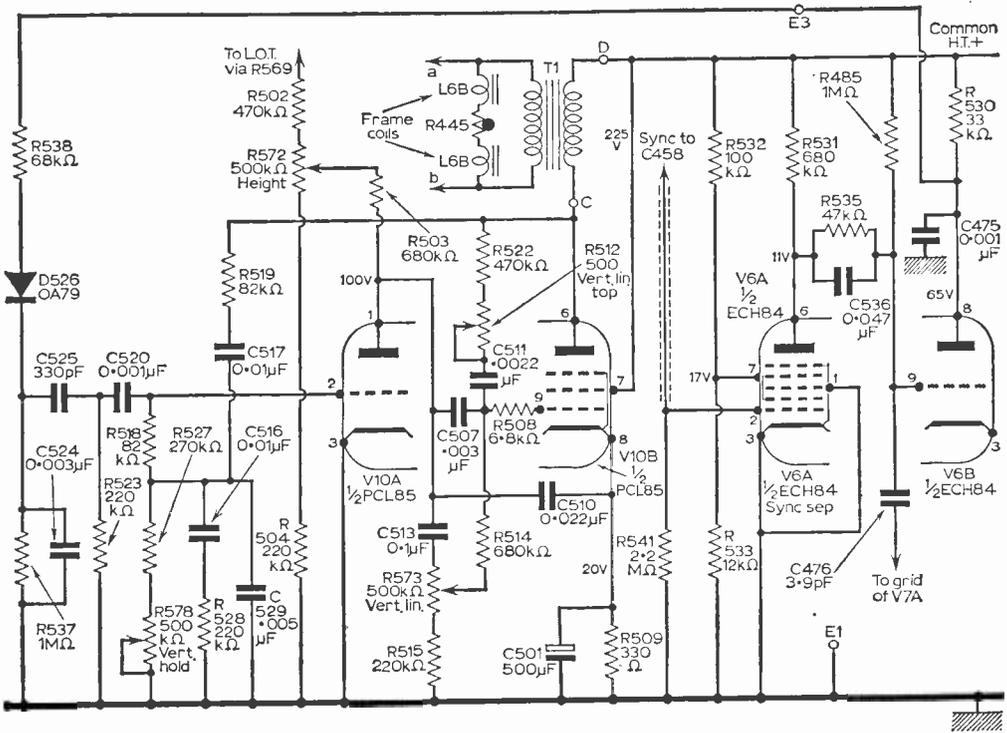


Fig. 6 (above): Field timebase circuitry.

output transformer primary (T2) can go open circuit resulting in no h.t. at pin 6 of V5.

Fig. 7 (below): Waveforms at various points in the field timebase circuitry.

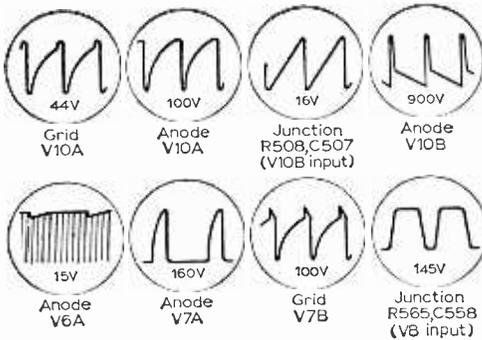

**The sound stages**

On the 405-line standard the sound i.f. amplifier is V4 EF184 (or 6F30). While this is also an i.f. amplifier on the 625 standard it should be remembered that both V1 (EF183) and V2 (EF80) function as common vision and sound amplifiers, the sound then being picked off at the video amplifier. V5, PCL82 (or 30PL12) is the audio-output valve. Check this stage if no sound at all can be heard when the picture is normal. The

**Distorted sound**

If all signals are distorted, check V5 and capacitor C106 (0.01μF). If only 405 signals are affected particularly on a strong signal, the effect minimised as contrast is reduced, check resistor R150 (5.6MΩ) which can "go high".

**The a.g.c. system**

The triode section of V3 is a pulsed a.g.c. amplifier which samples the video signal either from V3A anode (on 405) or V3A cathode (625), dependent upon the setting of SW1. Control of contrast is achieved by variation of V3B grid voltage, while balance of contrast between the two standards is achieved by means of the preset control R117 (5kΩ), adjustment being made on 405 line operation at low level of contrast (20V peak-to-peak). A.G.C. relay is obtained by the delay diode M3 (D135) and the 10MΩ resistor R132 connected to the contrast control slider.

**Loss of height**

If the lack of field scan is even top and bottom, check the height circuit resistors R502 (470kΩ), R503 (680kΩ), and R569 (330kΩ) (boost line).

# DX TV

A MONTHLY FEATURE  
FOR DX ENTHUSIASTS

by Charles Rafarel

**T**HE period 20/12/66 to 22/1/67 has run true to form for Sporadic E reception under winter conditions, with long periods of inactivity enlivened by some brighter spells in January.

The earlier part of the period was poor for tropospheric reception as well, but showed remarkable improvement on all bands from 28/12/66 onwards, including some good u.h.f. results.

I believe that Boxing Day also provided reasonable openings according to my more temperate DX pals, but I must confess that I was a bit too involved at that particular moment!

At New Year I spent three days with L. C. Styles, an old DX friend, at Ingatestone, Essex. He is now exclusively a u.h.f. DXer, and it was a great pleasure for me to see N.T.S. Holland via Lopik, Goes, and Roermond u.h.f. once again, after many months. Even in his favourable location conditions were far from good, but at least I returned home realizing that it was not necessary to tear my own gear apart to look for low-gain faults.

The brightest spot for Sporadic E was the 6, 7, and 8th January, with openings to T.V.E. Spain on E2, E3, and E4; the E3 on the 8th was first class and of long duration.

The tropospherics, including u.h.f., really opened up from 12th January onwards and I hope you have all done well since then.

## NEWS

Rumania has been received via Bacau on Ch R1 (now 3.0kW up from 600 watts as originally used). Reception reported by F. Smales of Pontefract, and Cpl. Maden of Cyprus.

Cpl. Maden reports reception on 4/12/66 at 14.30 to 15.00 test card as per Data Sheet No. 7, and 15.30 to 16.00 GMT test card as per Data Panel No. 15. The transmission opened at 16.00 GMT, with clock and "Bucuresti" caption and this could well be a new one for most of us when the coming SPE/DX season opens.

France; O.R.T.F. has now commenced regular colour test transmissions as from 21/11/66 on u.h.f. bands 2nd chain all transmitters. Times as follows for Monday, Tuesday and Wednesday each week:—

16.45 to 17.30 (French time) Test cards etc.

17.30 to 18.00 (French time) Films and still photos in colour.

There is a colour transmitter now operating at

the Paris Buttes Chaumont TV studios on Ch 28, at the following times:—

09.30 to 18.00 (French time) on Monday, Tuesday, Wednesday, and Thursday with Test cards, test patterns, and films or stills in colour.

Power details of this station are not yet known, but it is probably fairly low, as the service area is destined for the Paris region only, but there is always a chance! I myself have a tentative reception of this one already on 16/1/67.

Holland Colour transmissions also scheduled to commence in the Autumn of 1967.

## METEOR SHOWER REFLECTED SIGNALS

As a follow-up to last month's notes on E2 layer reflections, I think that some notes on meteor shower (M.S.) reflections may be of interest. We have mentioned this previously in connection with the fairly recent Leonid and Geminid showers, but we will now deal with the subject in a little more detail.

When meteors travel through the E layer they are capable of leaving an ionized trail in a similar manner to the action of the sun's rays, the main difference being that the duration of the ionization is much shorter.

It is, however, often of sufficient intensity to enable a TV signal to be reflected back to the earth's surface from heights of 60 to 70 miles up, but it must be remembered that meteors are often of very small dimensions (like grains of sand), and the majority will not produce sufficient ionization for reflection to take place.


These random meteors fall throughout the 24 hour period at all times of the year, but it is usually only when they fall in showers that reflection is possible.

These meteor showers are predictable, and those falling in the Northern Hemisphere arrive at the following approximate dates:—

Quantarids	early Jan.	Perseids	mid August
Lyrids	mid April	Giacobinids	early October
May Aquarids	early May	Orionids	mid-late Oct.
Cetids	mid May	Leonids	mid-late Nov.
Delta Aquarids	end July	Geminids	early-mid Dec.

DATA PANEL-19

SVERIGES RADIO (S.R.)

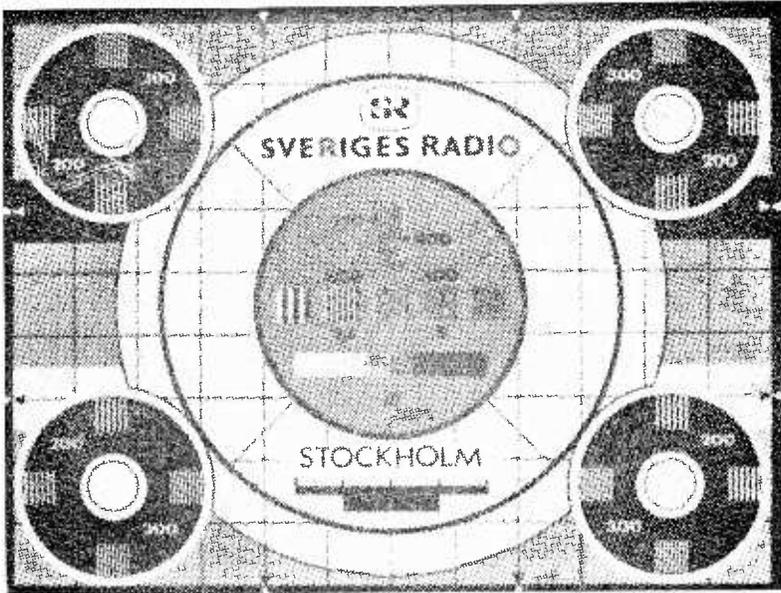

**Test Card:** As photo (see notes below). There are some variations to the above test card in use.

- (1) Some versions have a crown with arrows at the top of the inner circle.
- (2) At times there is a rectangle containing a written caption across the lower part of the inner circle, the wording can be in various languages including English, and is in fact the title of the music accompanying the test card.
- (3) At times (only too rarely!) the lower half of the card carries the name of

the actual transmitter, ie, Vännäs, Boden, or Orebro, etc.

**Channels:**

**Band 1:** E2, Hörby, Vännäs, Orebro; E3, Skovda, and Sveg; E4, Stockholm, Boden, and Ostersund. All well received in the U.K.

**Band III:** Sweden is also occasionally received by tropospheric propagation in the North of the British Isles.

**U.H.F.:** U.H.F. Hörby has been received in East Anglia by one DXer.

Reflections of TV signals are generally possible in Band I only, and are better towards the l.f. end of the band. Yes! I know that our radio amateur friends get reception on 144Mc/s by this method, but remember that the bandwidth is very small in comparison with TV standards. The distances over which reception is possible is about the same as short-medium Sporadic E, i.e. 500 to 1,100 miles.

There are certain clearly defined characteristics to be noted with M.S. reception. The signals received are of very short duration, or subject to very rapid changes in strength over several seconds, multi-path propagation with subsequent "smearing" of the image is also often present.

There is, of course, a problem here for short duration erratic signals are also characteristic of

Sporadic E reception under certain conditions, and it can be very difficult to distinguish between this and M.S. reception. There is no hard and fast rule and I can only suggest that if during meteor shower periods we get sudden "flash-ups" of signals of about one second or less duration, these are probably M.S. reflections.

**READERS' REPORTS**

Still not much activity here; not surprising in view of recent poor conditions, but things appear to be better now, so we are awaiting news of your current successes, and will see what we can find for the Post Bag next month.

## BBC-ITV collaboration

CHRISTMAS viewers were unanimous in their preference for BBC-1 programmes, according to TAM and other audience measurement ratings which normally show ITV as the leaders. Perhaps the best single effort, from many points of view, was the joint ITV and BBC production "The Royal Palaces of Britain". This documentary was a fine example of collaboration artistically and technically, having an engrossing commentary by Sir Kenneth Clark and magnificent editing by Roy Fry of superb shots and background music. Thanks also to David Windlesham and Anthony de Lotbiniere: it was a delightful presentation of history as well as of bricks and mortar.

## The 'whiter-than-white' paper

It is not surprising that the cheerful faces of executives of the television industry have become worried during the past few weeks—in fact, since the Government's White Paper on Broadcasting was published. "It takes a worried man to sing a worried song" might well be the musical background to an epitaph for a would-be progressive industry.

The Government's terms of reference have turned out to have the same theme as the Pilkington-Hoggart Committee's report; as down-beat and discouraging to independent broadcasting as it was (and still is) to independent television.

Competition is essential in show business. "Give the public what it wants—within reason" say the successful showmen. To give the BBC a monopoly for colour television for at least three years has caused dismay in many quarters (including some in the BBC) and especially among the manufacturers of television receivers.

Many people looked forward to a whiter-than-white Government White Paper; as bright as a barrage of rockets. Instead, it turns out to be a nine-page damp squib. The BBC will soldier on against fearful odds, hedged in on u.h.f. by mountains of skyscrapers, gas-holders and pylons. Nevertheless, when every lamp-post in the land is fitted with a miniature satellite u.h.f. transmitter, every man, woman and child in the land will be able to watch colour television—that

# UNDER NEATH



## THE DIPOLE

will be really good!!! If the Greater London area already needs 34 u.h.f. transmitters of varying power to satisfy BBC-2 viewers in the black spots, how many transmitters will they have to install in the Lake District, Scotland or other hilly areas? Lamp-posts still have to be erected in some villages!

## TV backroom melodrama

Old-fashioned melodrama faded from the theatrical stage generations ago, when the brothers Melville and Walter Howard presented "The Bad Girl of the Family", "The Midnight Wedding" and "The Female Swindler". Those were the days when the heroes were heroes (cheers! white spotlights) and villains were villains (hisses, supported by green limes). In this sophisticated day and mass-produced age every character seems to be villainous, down-beat and offensive. Of course, they are not all like that. Nevertheless, melodrama persists even in the modern idiom of

theatrical plays, cinema films and TV technical areas.

"The Sins of Brema" is not, as you may think, a Restoration period play. It might well be an evangelical approach to the charms of d.c. restoration or Mothersole circuitry in television receivers, performed annually by representatives of the British Radio Equipment Manufacturers' Association (BREMA) before the Engineering Committees of the ITA, ITCA and BBC.

## BSC & BREMA

The British Society of Cinematographers, that rather exclusive body of technicians generally referred to as Lighting Cameramen in film studios, who are responsible for the photography of large and small feature films for the cinema or for television, is not a large society. Its membership is limited (by invitation) to fully-qualified technicians. These gentlemen are agast at the poor quality of the reproduction of their photography on the average domestic television receiver. They are mollified somewhat when they view their films on a television studio monitor on which the picture quality black-and-white (and sometimes in colour) is quite satisfactory. Because of this they refer to today's TV sets as having "beautiful reproduction easily made awful", the initials of which coincide, by mere chance, with those of the BREMA!

The British Society of Cinematographers refuses to be put off with the excuses *there is no demand for quality in television sets. The most important thing is the cabinet. The public will not buy sets which may require knob-twiddling. The viewers cannot tell good quality when they see it so why waste the money? The carpets and curtains are more important than the television set which should match them.* They are appalled to see the faces of their artists turn from light to dark skins rapidly according to the background behind them and many other of the horrors of "losing the mood" and making darkness into fog, etc. The BSC's idea of giving an award or medal to those sets which pass the test of giving reasonably good picture quality is a very good one and they are actively engaged in persuading members of BREMA to take notice.

## Laugh, please laugh!

It is not easy for a solo comedian to be funny. He stands there alone with an audience waiting for him to be funny. How he waits! And sometimes still waits—for the slightest sign of approval or a chuckle, a giggle, or bless his heart, a big laugh! More difficult still is it for him to put on the same act in a sound broadcasting studio or a television studio, minus the audience. No reassuring chuckles encourage him and if the studio acoustics are lacking in reverberation like the first BBC "padded cell" at Savoy Hill, he may take fright and rush for the exit. A responsive audience in a studio is a valuable stimulant for just one laugh from just one of them can be contagious. If he tailors his funny gags to the laughter created by the previous wisecrack by accurate timing he can build up the comic atmosphere.

## Double acts

Some of the most successful have been double comic acts. The classic combination of a "straight" man feeding a comedian goes back to characters in Shakespeare, to the first minstrels and to Evans' Supper Rooms. We remember affectionately Burns and Allen, Laurel and Hardy and more recently, Flanagan and Allen. Who will forget the splendid Tony Hancock and Sidney James team, who have never been singly quite so funny as they were in their classic double act situation comedy series. Equally successful were Steptoe and Son, whose character names are better known than their own; Wilfred Brambel and Harry H. Corbett.

Probably the most successful double act on television during 1966 has been Morecambe and Wise, whose split-second timing of well-written gags, physical as well as verbal, promotes laughter with the greatest of ease.

In this case, both are funny men who act as feed for the other, though Eric Morecambe inevitably seems to be the butt, whether in a television sketch or in a full-length feature film. In *The Magnificent Two*, a feature film production being made at Pinewood Studios, a television studio setting was built, complete with image orthicon cameras, video tape monitors and control



Attention for Parazuellian National Anthem! Ernie Wise, camera men and crew watch their president Eric Morecambe, make his presidential address.

Left: Eric and Ernie playing about with one of the Teleprompters.

tions are now arising during the production of feature films for the cinema, especially if they involve a mixture of film cameras, television cameras, monitors and lighting for colour. For the television studio scenes in *The Magnificent Two* the motion picture cameras had to be run at 25 frames per second (instead of the usual 24) so that they could be synchronised with the pictures on television monitors in the scenes. By using a motion picture camera with a mirror-shutter at that speed, the camera operator can observe the "hum bar" (which looks like the frame-line between each picture on a film). This enables him to check the synchronisation and phasing, and ensures that one of the interlace fields is (almost) completely photographed. Also he has to balance the intensity of the monitor picture with the rest of the scene. Further complications arise when video tape is played off and reproduced by monitors in a scene.

Morecambe and Wise have no difficulty in maintaining their pace and timing perfectly without needing laughs from an audience. But they are well aware of the difficulty the technical crews have in stifling their laughs during the shooting of many of the scenes.

rooms. It represented the new President of a South American republic, Parazuellia, which was played by Eric Morecambe, making a speech to "his people". This television studio was actually a reproduction of the Westward Studio at Plymouth. Plenty of slapstick fun was made with the aid of Teleprompter, pedestals, cameras, microphone booms and other equipment as props, aided by a vociferous "Parazuellian" technical crew.

Many new technical complica-

*Icons*

# IDEAS FOR.....


# amateur TV

M. D. BENEDICT.
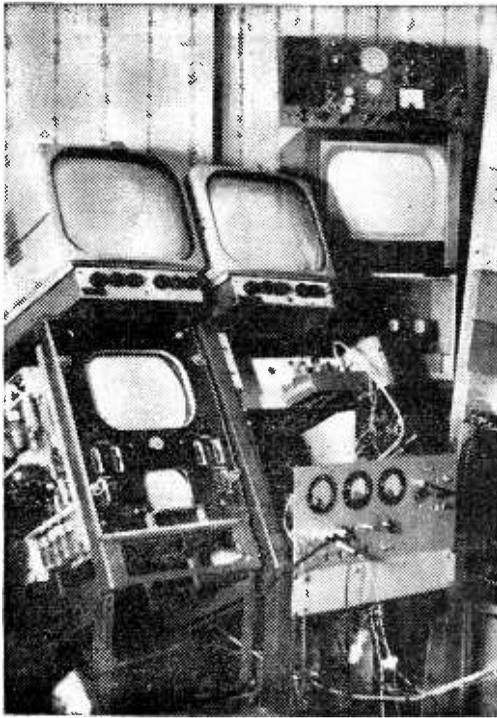
## Part IX

from the mixer control panel. Faders are, unfortunately, expensive to buy as they are high quality stud contact switches with two rows of about 30 studs connected to high stability resistors in a bridged "T" configuration. Capacitors are also used to improve the high frequency response. The B.A.T.C. might be able to assist in obtaining second-hand faders, but they are in great demand. As with all other mechanical devices, flashing due to dirt on the fader contacts is a considerable problem.

Fortunately, simple transistor circuits have been developed which vary their gain in response to d.c. applied from a potentiometer. Instead of obtaining the bias from the usual rotary potentiometer, a linearly operated potentiometer could be used. These potentiometers have only recently been introduced into this country and are remarkably cheap. Their linear movement makes them ideal for use in sound and vision mixers where swift operation is required. The neat appearance of these is also an asset. They are obtainable from F. W. O. Bauch, Holbrook House, Cockfosters, Herts, at about 15/- each, by quoting Type No. 62ZW. In the range of potentiometers available, are log and linear



**L**AST month we were discussing cut amplifiers and a further circuit for inter-field cutting is shown below.

A very compact layout of cut amplifiers has been achieved by using the plastic "buttons" used to protect B9A valve pins on new valves. The small components are mounted between "pins". These are "wires" that are fitted through the holes in these buttons. The whole assembly can then be plugged into a valve base. Numbers on Fig. 51 (last month) refer to the pin connections used. The partially completed bank of cut amplifiers are mounted on a 19in. rack panel; two fade amplifiers and a stabilising amplifier are also mounted to form the complete vision mixer controlled from a remote panel.

In order to fade vision, a potentiometer could be used but it would need to be integrated with an amplifier, as if co-ax cables were used to remote it, the potentiometer would not match the impedance of these cables. A constant impedance potentiometer system is commonly used and these are called faders. The quadrant fader used has a 75 ohm input and output impedance. This means it can be used with coaxial cables to feed the video to and

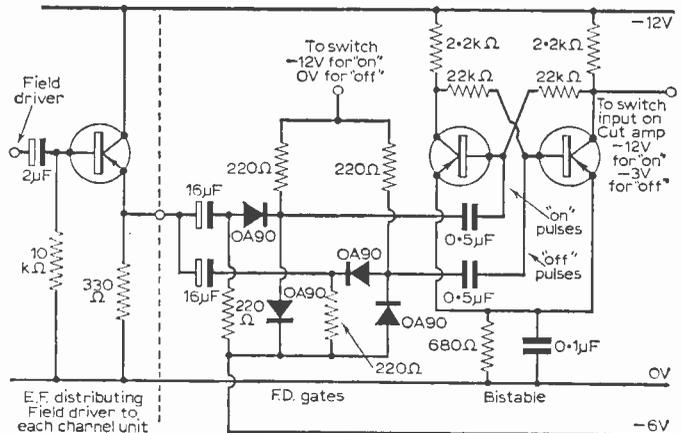


Fig. 52: Additional circuitry for inter-field cutting.

types in a wide variety of values; however, the potentiometer used here is a 10kΩ linear type.

The bias from this potentiometer is fed to the bases of a long tailed pair of 2N711's. Varying the bias alters the gain, and most of the non-linearity inherent with this process is eliminated by the difference amplifier action of this circuit. This circuit (Fig. 53) can be used as a cut amplifier by switching the bias to it. A maximum gain of about 10 is obtained and so the input must be about 0.1 volts of video. The losses in the cut amplifier conveniently compensate for most of this gain.

### VISION MIXERS

Two types of vision mixers using these cut and fade amplifiers are shown in Figs. 54 and 55. Many other types of vision mixers are used, mostly consisting of combinations of these two basic types. Figure 54 shows A/B mixer with two banks of cut buttons, the output of each bank feeds a video fader. Each source appears on both banks so if Camera 1 is selected on the A bank, Camera 2 can be selected by cutting, simply by depressing its button on the A bank, or can be mixed to by selecting it on B bank and fading A bank down and B bank up. Obviously, by this means, any source can be cut to or mixed to any other (providing they are both synchronous). For convenience the potentiometers controlling A bank and B bank faders are wired in an opposite sense so movement of the two potentiometers together effects a mix. The output of the fader amplifiers are combined and feed a stabilising amplifier where syncs. are re-inserted, as the syncs. through the fader amplifier will vary in


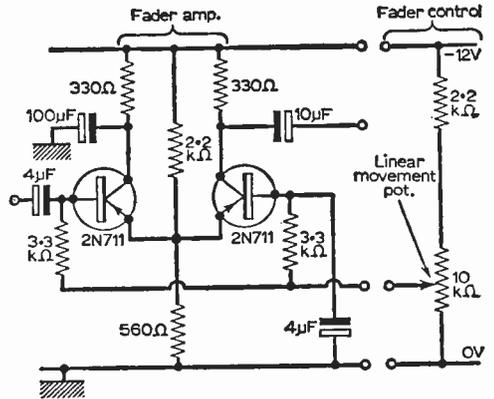


Fig. 53: Circuit of the fader amplifier.

amplitude along with the vision. This circuit will be dealt with later.

Unfortunately, non-sync. sources, i.e. those from another pulse generator, which have not been genlocked to, cannot be treated in this way as their syncs. will not coincide. Neither can two sources not in exact synchronism be mixed one with the other or even faded down (without sync. separation, re-generation and re-insertion!). Non-sync. sources, then, are selected after the output of the stabilising amplifier by cut amplifiers and these cut amplifiers, along with the sync. source cut amplifier, are combined to feed an output amplifier. There is absolutely no point in using inter-frame cutting for these amplifiers as field drives are unlikely to occur during the field

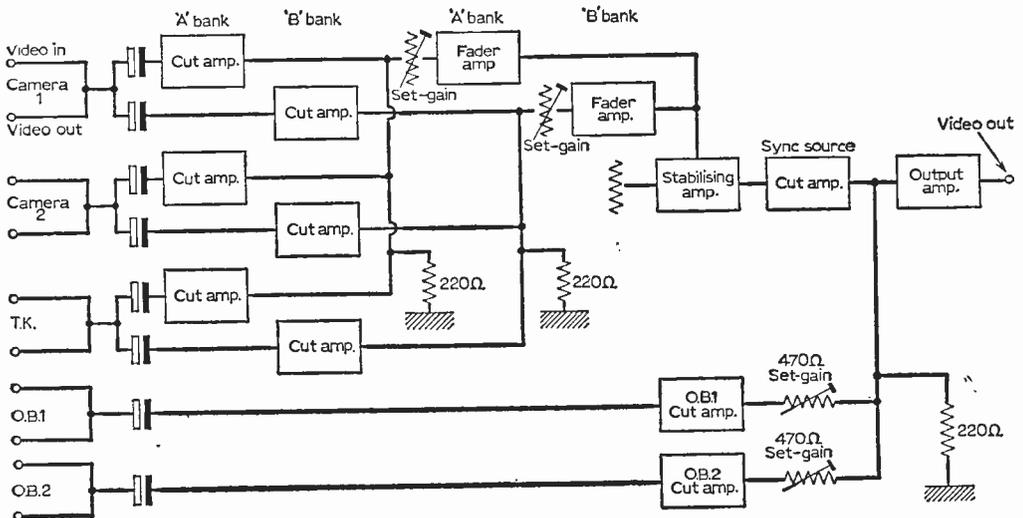

[Fig. 54: A/B vision mixer chain.

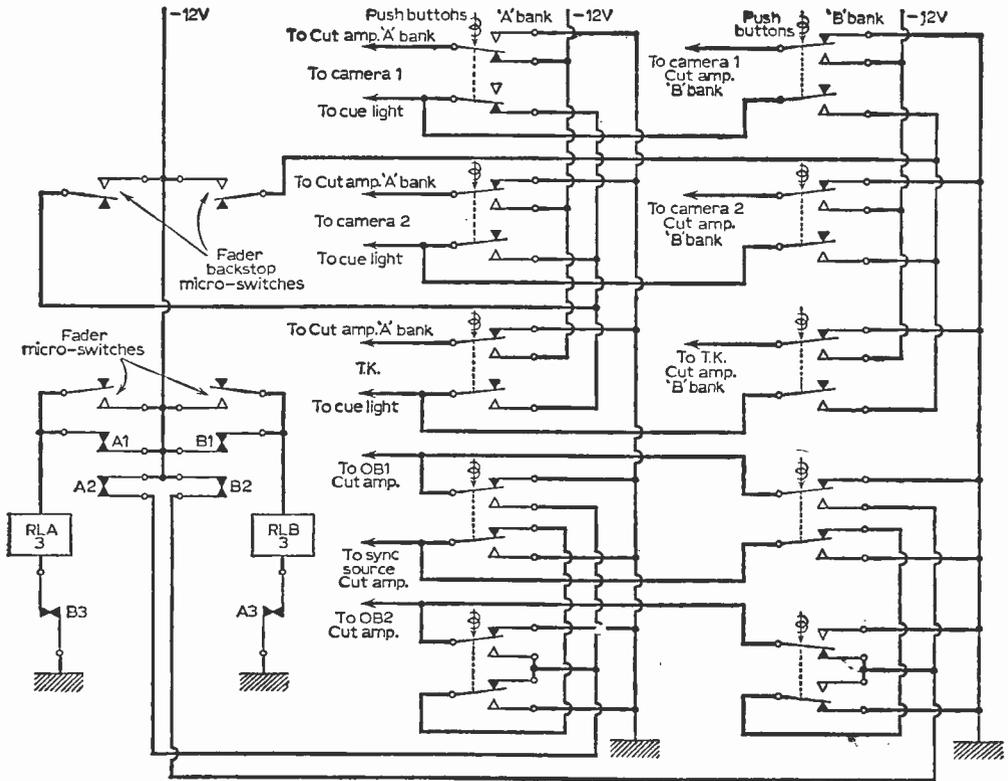


Fig. 55: A/B mixer d.c. switching.

period of the remote syncs., and in many cases a scan disturbance is unavoidable when cutting to non-sync. sources.

The d.c. control circuitry for the A/B mixer is shown in Fig. 55. Micro-switches operated at the fader full up position energise a latched relay which in turn energises non-sync. source buttons on the bank corresponding to that fader. Latching is interrupted by the other fader so that the non-sync. source button of which ever bank is faded up are operative. A second set of micro-switches on the faded down position on each fader feed cue lights via the push buttons. On fading up either bank the micro-switches operate and feed the cue lights of the camera selected. The two non-sync. sources are usually referred to as O.B.'s., and labelled O.B.1, O.B.2, etc. Although cue lights are not usually fed to O.B.'s., it is common practice to arrange an indication of the source selected either by an illuminated sign adjacent to the transmission monitor or on the vision mixer control panel or both. If this is required, the feed to the

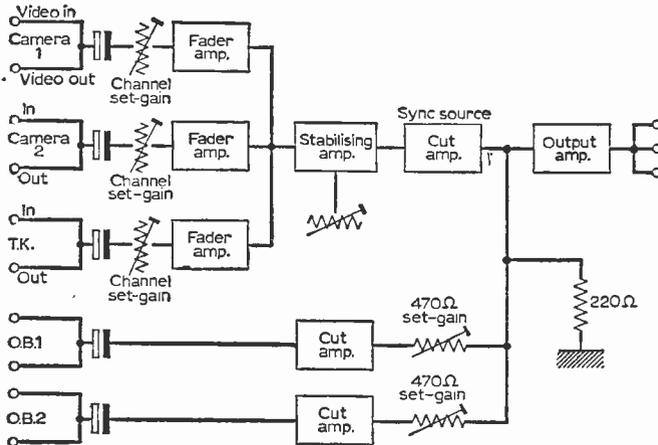


Fig. 56: Vision schematic for cut/fade vision mixer.

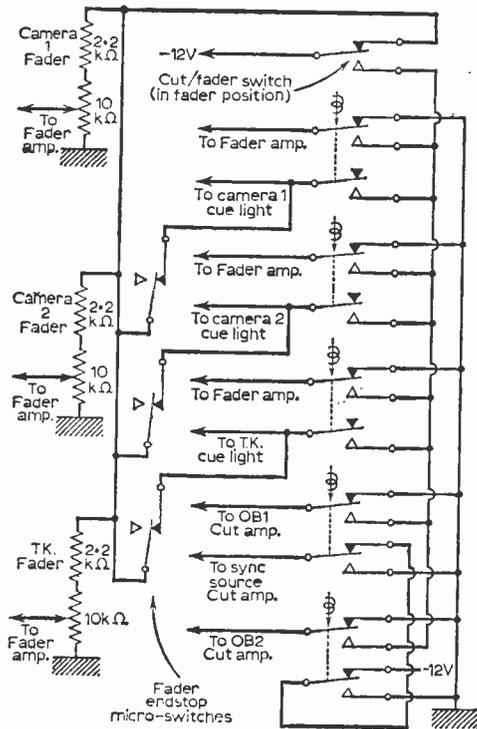


Fig. 57: D.C. control of cut/fade vision mixer

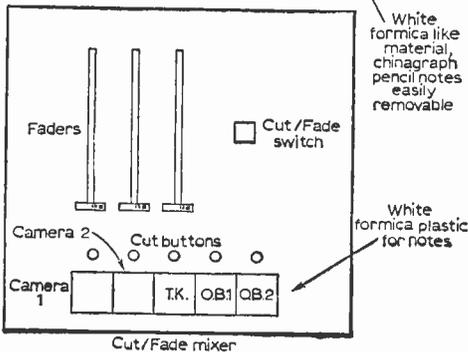
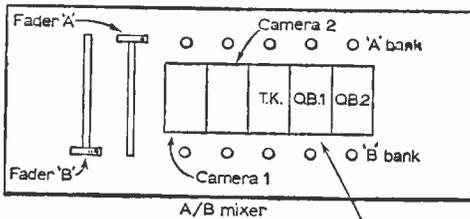


Fig. 58: Layout of mixer control panels.

O.B. cut amplifier can be used to control a relay operating these lights.

Potentiometers (1kΩ) are used to adjust the balance between the two banks and a 470Ω series potentiometer sets the gain of each non-sync channel in respect to the sync. source output. The approximate gain of a fader amplifier is a maximum of 10, so about 0.1 of a volt video should appear at the input. This is set exactly with the amplifier faded up by adjusting the set gain to exactly 1 volt at the output of each amplifier. The non-sync. channels are also set to give a similar amplitude sync. sources at the output of the cut amplifiers. Sawtooth is used for lining these channels up. A suitable layout for the control panel is shown in Fig. 58, along with the other type of mixer, known as the cut/fade mixer (Fig. 56). The layout is very important as the method of operation should be obvious to the operator. Both these control panel layouts are commonly used in professional equipment and hence are proved. Temporary notes can be made with a chinagraph pencil on a white formica type plastic placed near or below the rows of cut buttons, allowing a special identification of sources. The vision control panel should be mounted at least 9in. from the near edge of the desk to enable scripts or notes to be placed on the control desk without obstructing the controls.

With this type of mixer each sync. channel has a fader control and cut button. Non-sync. sources cannot easily be faded, as mentioned previously, so that only cut button selection is provided. The sync. sources are fed to a fader amplifier which is controlled by bias from the cut buttons or from the faders depending on the position of the cut/fade switch. This is followed by a stabilising amplifier then the sync. source cut amplifier. This cut amplifier and the non-sync. source cut amplifiers select sync. or non-sync. sources and feed it to the output amplifier. As before, the set gains of the sync. channels are adjusted to give 1 volt of video at the output of each fader amplifier when faded fully up. Non-sync. channels are adjusted as before. The d.c. control circuitry which is considerably simpler than for the A/B mixer is shown in Fig. 57.

Although for simplicity both mixers are shown as having three sync. and two non-sync. channels, it is advisable to build a more complicated mixer, say 6 sync. inputs and 4 non-sync. inputs, although not all of these channels need be constructed until required. This large capacity allows for use in exhibitions with cameras belonging to other amateurs, as well as other facilities to be described, such as Inlay.

The A/B mixer only allows two sources to be superimposed simultaneously and may appear more complex, but it has the advantage of being very convenient to use with Inlay equipment, to be described. Cut/Fade mixers allow the superimposition of any number of sync. sources. Professional equipment often features a combination of both types of mixer, for example, many BBC studios use an 8 channel cut/fade mixer as each bank of an A/B mixer, with facilities for cutting between either bank. Many other types exist, and it is for the constructor to decide on the type and complexity of the mixer he may wish to use.

TO BE CONTINUED

# Gas in valves and tubes

by K. T. Wilson

**T**HE home experimenter encounters the gassy valve usually in the form of a blue glow in the sound output valve, sometimes accompanied by severe audio distortion and ending up in fuse blowing. To the professional valve-maker, gas is a subject of great concern, signifying a faulty pump system, in which case several pump-loads of valves may have to be rejected; worse, it may mean faulty seals in a batch of several thousand valves and subsequent mass scrapping.

The gas, of course, is usually ordinary air, for the valve-maker calls gas anything which isn't solid, liquid or vacuum. In the case of a newly pumped valve at the factory, the gas, or lack of vacuum, may be due to factors outside the valve, such as a leak in the pump system. In the case of a valve which has passed factory tests and gone out to the customer, the gas must be due either to leaks in the valve itself or to gas generation inside the valve.

## GLASS-TO-METAL SEAL

The leak is the most common fault. The modern valve has a number of glass-to-metal seals forming the electrical leads into the valve. These seals consist of metal and glass which are carefully chosen so that they expand and contract at the same rate; if it were otherwise the seal, which is formed at a temperature at which the glass is molten, would crack and be useless as it cooled.

During the heating process in which the glass is melted round the metal pins to form the seal, the metal oxidises, and the oxide which forms dissolves in the molten glass, causing a distinctive colouration. An expert can judge the goodness of any glass-to-metal seal by looking at the colour of the dissolved oxide.

There are some things which the most expert eye cannot see, however. If there should be a minute scratch down the pin before sealing, the glass will not penetrate to this portion, and a path will be left along which air can trickle into the finished valve.

If this leak is large, it will be detected by the processes to be described later; if it is very small, it will probably pass undetected, to cause a "gas" failure later on in the life of the tube. As fate would have it, this often happens just outside the guarantee time!

## PINS

The remedy for this sort of thing is very great care with the pins at all stages. Valve-makers insist that the material of the pins be tested for purity, that it should be machined only in certain ways (for example, by centreless grinding), that it should be finished to a very high degree of surface smoothness that it must not touch anything which might corrode it (even the oils used during machining must be special non-corrosive types), and that the finished pins must be carefully inspected, and accepted only if less than a very small percentage of a sample is found defective.

With continual care, then, the valve-maker tries to keep down the number of leaks. Some will always get past, for he cannot afford to inspect and test everything; besides, he has no way of testing for very small leaks and must rely on the care which he takes in the selection of his materials.

## GENERATION OF GAS

So much for leaks; what of internal generation of gas? Internal gas can come from any part of the valve, and can be caused by either incomplete outgassing of the components or poor cathode processing. Let me explain what these phrases mean.

As far as the amounts of gas which worry the valve-maker are concerned, all materials are to some extent spongy. Most of this sponginess is just at the surface of the metal or glass or ceramic, though it goes in layers in mica. All the parts of a valve have therefore soaked up gas in quantities enough to cause trouble, and something must be done about this before the valve can be assembled and pumped.

In the case of the metal parts, this "something" is hydrogen furnacing. The metal is heated to a very high temperature, often 800—1,000 degrees Centigrade, in a furnace filled with hydrogen. Providing that the metal has been thoroughly cleaned before the furnacing, this has a remarkable cleaning effect, removing stains and oxidation, and, more important for our purpose, replacing the various gases which have soaked into the metal by pure hydrogen.

It may seem a bit pointless, heating up the metal to remove the mixture of gases it has absorbed, and then letting it soak up hydrogen as it cools down, but there is sound reasoning behind it all. If the metal were heated in a vacuum to remove the mixture of gases, it would simply soak up the gas again during the assembly of the valve, which cannot be done in vacuum. If, on the other hand, it is allowed to saturate itself with hydrogen then very little of any other gas will be absorbed during the time that the parts are exposed to the air.

Furthermore, hydrogen is the lightest of all gases, and we can easily extract all the hydrogen from the metal parts by giving them a break during the time when the valve is being pumped out. This break will also remove the water vapour from the glass of the valve, another source of gas. To make sure of complete gas removal from the metal parts, they are often heated to a dull red heat by induction heating from outside the valve during pumping.

## ACTIVATION OF CATHODE

The activation of the cathode is what turns an assembly of parts in a vacuum into a working valve. The cathode of most of the valves commonly encountered consists of metal oxides, those of the metals barium, strontium, and sometimes calcium coated on a nickel cylinder inside which the heater

wire is inserted. The trouble is that the oxides cannot be put on the cathode cylinder beforehand, they must not be exposed to air if they are to emit electrons properly; they are therefore formed within the valve.

To do this, the carbonates of the metals are coated on to the cathode cylinder, and these are converted to the oxides, while the valve is pumping, by applying volts to the heater. The carbonates are then converted to the oxides and the gas, carbon dioxide, is liberated in the reaction known to all schoolboy chemists as the burning of lime.

This process releases an enormous amount of gas, which must be pumped completely away before the valve can be sealed up and removed from the pump.

## THE GETTER

It can be seen that there are many sources of gas inside a valve, and these would make valves useless if we did not use a getter. The getter is a film of a highly absorbent metal which can soak up thousands of times its own volume of gas.

Since the getter is not heated by the heater or struck by electrons, it does not heat up to any great extent and releases this gas, and valvemakers are careful to place the getter, which is released inside the valve by induction heating after the valve is sealed, in a cool part of the valve.

The getter will soak up gas in a valve until it is exhausted, after which the valve will be useless. This is usually what happens in the case of a slow leak. If the gas comes from inside the valve, however, as often happens when a valve is used after a long period of disuse, the gas which is released rapidly will be steadily mopped up by the getter.

It is this effect which is the cause of so many puzzling failures. The equipment is switched on, and the heating of the large cathode of an output valve, always the worst offender, releases some gas. This, as will be shown later, produces excessive current in the valve, causing overheating, which releases more gas, until the excessive current blows a fuse or causes some other breakdown.

Once the rush of gas is over, though, the getter can cope with the job of mopping up, and by the time the puzzled owner of the equipment has removed the valve and tested for gas, the valve seems perfectly sound. This can happen several times until substitution of a new valve proves that hot gassing is the cause.

## ELECTRON BEHAVIOUR

So much for the causes of gas in the valves. The effects are better known, though the reasons for them are not. The root of the trouble is that electrons in valves travel in vacuum. Large, slow moving particles of gas constitute an obstruction to the small fast electrons and reduce their average speed.

In the presence of gas particles, electrons in a valve or c.r.t. travel from one collision to another on their way from cathode to anode, and each of these collisions mean that the electrons must start accelerating all over again.

Physicists have a term, "Mean Free Path", which means the average distance which an electron can travel before colliding with a gas particle (or molecule), and as you would expect, this Mean

Free Path is longer as the vacuum is better, since there will be fewer gas molecules to collide with.

The importance of this idea can be seen by comparing a c.r.t., where the electrons have to travel many inches on their way from cathode to screen, and a u.h.f. triode, where the distance from cathode to anode is measured in thousandths of an inch.

The collisions of electrons and gas molecules have consequences even more serious than the lengthening of the means free path. Each time an electron strikes a gas molecule at high speed, it breaks it up, first into atoms, then further into ions and more electrons.

The ions, being positively charged and heavy, drift lazily toward the cathode, but the electrons are accelerated toward the anode like any other electrons. Each of these electrons can in turn strike a gas molecule and cause further breaking-up, or ionisation, as it is called.

When large numbers of extra electrons are created in this way, the current flowing to the anode is no longer controlled by the grid, and can reach destructive proportions, unless it is limited by external impedances, as is the case in circuits designed for gas-filled valves.

Even if the ionisation does not proceed to the point of complete breakdown, the cathode of the valve can be destroyed by the bombardment of the positive ions which are attracted to it; such cathodes usually show a brown discolouration.

## ION BURNS

Negative ions can be produced also; they are of little consequence in valves, but can lead to rapid discolouration and loss of brightness of the screen, since they are attracted to the positive element. Being heavy, negative ions are not so readily deflected by the scans as electrons, so the ion burn in a c.r.t. usually consists of a brown spot or blob in the centre of the screen.

We have known for a long time how to avoid this affect, either by aluminising the screen (aluminium being fairly porous to fast electrons but opaque to the large slow ions) or by tilting the electron gun and straightening up the electron beam by means of a magnet. In this case the ions are not deflected and strike the walls of the tube harmlessly.

The formation of the positive ions in a valve also accounts for another feature of a gassy tube. On their way to the cathode, the ions encounter electrons, and if they encounter electrons which are not travelling too fast, they may recombine to form atoms of gas again. Energy had to be absorbed to ionise the atoms in the first place, and the same amount of energy must therefore be given up when recombination takes place.

This energy is given out as light, and the amount of energy determines the colour of the light, usually blue. This is the explanation of the well-known blue glow in gassy valves.

## ION GAUGES

The formation of positive ions in a gassy valve has a very practical use, however, apart from deliberately gas-filled valves, for it enables us to measure the pressure of the gas which is causing the bother; and in the pumping of valves, the ion

current may be used as the measure of the vacuum of the system.

Special valves, known as ion gauges, are made for this purpose, and used when a very high degree of vacuum has to be measured with precision. These gauges are of a simple construction (see Fig. 1.) and consists of a hairpin-shaped filament, a spiral of thin wire around it to act as a collector grid, and a pin or another hairpin filament to act as anode.

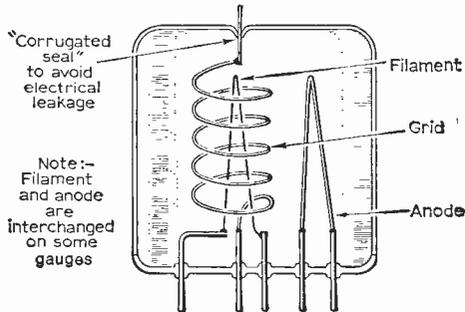


Fig. 1: Electrode structure of an ion gauge.

Arrangements are often made for all the elements of the gauge to be heated red hot by passing current through them; this drives off any gas which may be absorbed in the metal of the gauge, as it would be pointless to try to measure the vacuum in a pumping system if the gauge were giving off more gas than the rest of the system.

The wire used is usually Tungsten or Molybdenum. In either case it has a very high melting point and can stand high temperatures. In use, the anode hairpin is put at about 100V positive and the grid at a few hundred volts negative.

The filament is then heated until electrons are emitted and a fixed anode current, say of 25 milliamps, is reached. The negative current at the grid then consists entirely of positive ions (dis-counting leakage resistance) and can be directly measured, usually in microamps or less. The gauges are usually calibrated against other types of gauge of known accuracy. (See circuit, Fig. 2.)

In a form of this gauge, known as the Philips Gauge, no hot filament is used. Instead, the cathode is of pure metal, and a grid at a potential of a thousand volts or so is placed very close to it.

The electron emission from such a system is very small, and so a magnet is used to make the path of the electrons into a long spiral where their chance of knocking into several gas atoms is greatly increased.

## ION PUMP

A development of the ion gauge is the Ion Pump. We have seen that the negative current at the grid consisted of negative ions, but what happens to them when they reach the grid?

First of all, they must give up their negative charge to the grid; they then become single atoms. In their normal state, however, these gases are molecules, two atoms linked together, and when they are in the single atom state they desperately want to combine with something else.

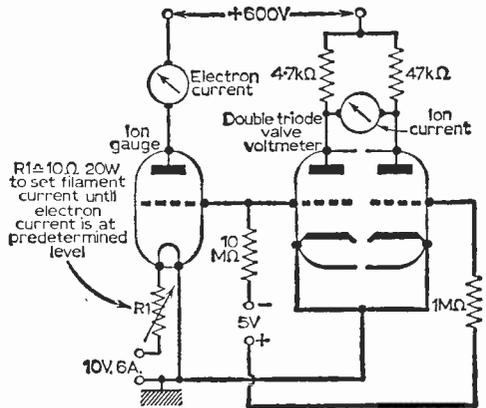


Fig. 2: Method of setting up ion gauge.

The nearest thing available is the metal of the grid, and combination with this takes the atoms out of the gaseous state. They can be recovered only by heating, which is why we heat up the electrodes of the gauge before allowing it to start its work.

In one form of this ion pump, the ions are gathered on a freshly prepared getter surface, the favourite material being Titanium; this form is known as the Getter-Ion Pump.

Every valve testing meter incorporates a test for gas, and the same method is used. In this case, of course, we cannot attach an ion gauge to the valve, and we have to use the valves own electrodes as the electrodes of the ion gauge.

Some testers pass current by making the grid positive and the anode negative, just as if the valve were an ion gauge; the more usual method is to run the valve with a very high grid resistor and measure the grid current.

This grid current will be made up of both electrons and ions, but for a given anode current, the grid current is roughly proportional to the ion current and hence to the gas.


This phenomenon is the reason for the warning in the valve manuals about the maximum grid resistor which may be used, especially in the case of power valves where positive ions landing on the grid and not being discharged to earth by a fairly low value resistor may charge the grid positive and cause excessive anode current.

Gas, then, is one of the valve and c.r.t. manufacturers greatest headaches. It is very much a tribute to his methods of dealing with it that it is not a major problem to the users of valves. ■
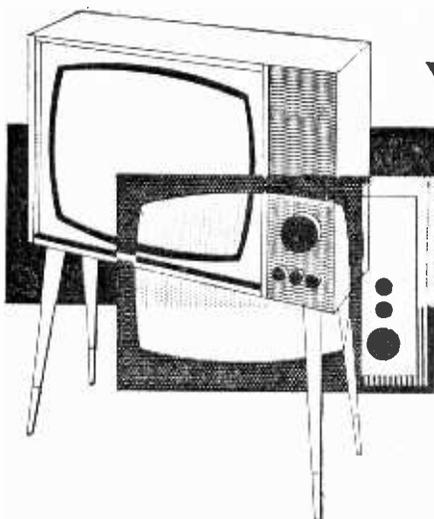
## TELEVISION EASI-BINDER

The Practical Television Easi-binder holds 12 issues. Please state volume number required or a blank cover will be sent. The price is 12s. 6d. inclusive of postage.

Order your binder from: Binding Department, George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.



# Your Problems Solved

*Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from page 284 must be attached to all queries, and a stamped and addressed envelope must be enclosed.*

## **FERGUSON 407**

The boost diode failed. I changed this and the vision returned. Shortly after, a smear appeared on the picture and in the background there were vertical bars shaded black and white extending to about the centre of the picture.—K. Colwill (Torrington, Devon).

Check V17 and V18 (6F80 and 6CC81) also the 0.01 $\mu$ F capacitors associated with the oscillator-sync transformer. Check also the 1.5k $\Omega$  resistor wired across the width coil.

## **VIEWMASTER**

I have just put in a new metal rectifier and whilst the picture and sound are good, there is a clicking noise from some part of the set, which I am unable to trace.—W. H. Jarvis (Barnet, Hertfordshire).

We would suggest you check the e.h.t. section for signs of arcing, resulting from poor soldering, protruding wire ends, dust etc.

## **MURPHY V879U**

The following symptoms developed over a period of three weeks. The sound was normal throughout. (1) After switching on, the picture shrank slightly about 1in. in from the screen edges. (2) Later the centre of the picture took longer to appear than the rest. Eventually, the whole picture took about 7 minutes to appear and was very dim. (3) On increasing the brightness control, the picture enlarged, grew dimmer and then disappeared. This last symptom apparently indicated low emission of the e.h.t. rectifier.

Before I obtained the replacement valve, the symptom had become a vertical white line only down the centre of the screen. Subsequent replacement of the e.h.t. rectifier produced no change.

The line whistle is clearly audible. The PY88 and the PL36 appear to be overheating.—J. W. Gilbert (Whitefield, Lancashire).

The PL36 is likely to be at fault. Check the valve and associated components: line drive to the control grid etc.

## **BUSH TV145U**

Can you suggest how to connect a meter so as to compare signal strengths in order to adjust the aerial and its siting?—J. D. Akroyd (Weymouth, Dorset).

If you wish to meter the signal strength at the receiver itself, it is a comparatively simple job to connect a voltmeter across the a.g.c. line and adjust for maximum negative voltage. Any other means of reading, say at the diode with a voltmeter or milliammeter, will necessitate shorting the a.g.c. line to chassis.

The best reception is not always obtained at the point of maximum signal particularly where ghosting is experienced.

## **PYE V830A-16W**

This set gives no picture—just full brightness without any sound. Adjusting the contrast does not make any difference to the brightness of the screen. Adjustment of the horizontal hold darkens the picture and reduces the screen top and bottom but the full brightness remains and no picture appears. The vertical hold diminishes the screen to 6in. in depth.—W. Prescott (Wirral, Cheshire).

There appears to be a fault on the tuner. Common causes of the symptoms you describe are: broken coils on the tuner rotor, a faulty local oscillator valve, or low h.t. due to a defective h.t. rectifier.

## **ULTRA 1980C**

The trouble is cramping at the top of the picture.

Can you please tell me if the safety glass can be removed to clean the tube face without withdrawing the chassis.—W. Fraser (Herne Bay, Kent).

You should check the 30PL14 field output valve and the components associated with pin 6 to the vertical form circuit.

The chassis must be removed from the cabinet for cleaning purposes.

# LAWSON BRAND NEW CATHODE RAY TUBES



The rapidly increasing demand for a complete range of new tubes of the very highest quality is now being met by the new Lawson "CENTURY 99" range of television tubes.

**SPECIFICATION:**

The new "Century 99" range of C.R.T.s are the products of Britain's premier C.R.T. manufacturers. All types are exact replacements, manufactured to the original specification but incorporating the very latest design improvements to give superb performance, coupled with maximum reliability and very long life.

"Century 99" C.R.T.s, available as direct replacements for the following makes and types

MULLARD		MAZDA		BRIMAR		EMISCOPE & EMITRON		GEC & COSSOR also ENGLISH ELECTRIC	
MW43/69	AW36-80	CRM121	CME1901	C12FM	C17SM				
MW43/64	AW36-21	CRM123	CME1902	C14M	C19/7A	4/14		141K	
MW36/24		CRM122	CME1903	C14GM	C19/16A	4/15		171K	
MW31/74		CRM124	CME2101	C14HM	C19/10AD	4/15G		172K	
MW31/16	<b>Twin Panel Types</b>	CRM141	CME2104	C14JM	C19AH	5/2		173K	
MW43/80		CRM142	CME2301	C14LM	C19AK	5/2T		212K	
MW36/44	A47-13W	CRM143	CME2302	C14PM	C21/1A	5/3		7102A	
MW53/80	A59-16W	CRM144	CME2303	C171A	C217A	5/3T		7201A	
MW53/20	A59-13W	CRM153		C174A	C21AA	14KP4		7203A	
MW43/43		CRM171	<b>Twin Panel Types</b>	C175A	C21HM	17ARP4		7204A	
AW59-91		CRM172		C177A	C21KM	17ASP4		7205A	
AW59-90		CRM173		C17AA	C21NM	17AYP4		7401A	
AW53-89		CRM211	CME1906	C17AF	C21SM	21CJP4		7405A	
AW53-88		CRM212	CME2306	C17BM	C21TM	SE14/70		7406A	
AW53-80		CME141		C17FM	C23-7A	SE17/70		7501A	
AW47-91		CME1402		C17GM	C23-7A			7502A	
AW47-90		CME1702		C17HM	C23AG			7503A	
AW43-89		CME1703		C17JM	C23AK			7504A	
AW43-88		CME1705		C17LM				7601A	
AW43-80		CME1706		C17PM				7701A	

12"	...	£4.10.0
14"	...	£5.10.0
17"	...	£5.19.0
19"	...	£6.19.0
21"	...	£7.15.0

Terms:  
C.W.O.  
Carr. and  
Ins. 10/-

**2 YEARS' FULL REPLACEMENT GUARANTEE**  
Complete fitting instructions supplied

**LAWSON TUBES**  
STATION ESTATE, MALVERN.  
Offices  
18 CHURCHDOWN ROAD,  
MALVERN, WORCS. MALVERN 2100

## More specialist know-how for practical men

Follow through into the allied fields of electronics and radio with the help of these up-to-the-minute 'Practical' magazines. Both bring you the same detailed expert know-how and constructional opportunities that you find month by month in 'Practical Television'.



**PRACTICAL WIRELESS**

Covers the complete field for the radio amateur and experimenter, with new designs for sponsored receivers and other how-to-make features. Monthly, 2/6.

**PRACTICAL ELECTRONICS**

All you want to know about all branches of electronics — new ideas — new methods — how-to-build instructions for a wide range of electronic devices. Monthly, 2/6.

**PLACE A REGULAR ORDER WITH YOUR NEWSAGENT !**

**BUSH 138RU**

This set is troubled by some form of interference on BBC-2. There appears to be a band of light about 3 to 4 in. wide, which travels up the screen and makes the picture sway as if it were affected by a light breeze.

The u.h.f. tuner is transistorised, although the maker's instruction book quotes the tuner as being a valve one.

I have an inside aerial and the picture is quite good. The form of interference I get does not affect 405-line pictures.—G. Barnett (Leeds, 8).

This effect could well be caused by some defective fluorescent lighting or other type of tube, gas filled, lighting operating nearby. We do not recognise the fault as originating in the receiver.

**PETO-SCOTT 738**

The line hold drifts after the set has been working for about an hour. The plug adjustment is set for fringe working at the moment. When this control is set to normal, the picture verticals are ragged.

The sync separator, line output valve and oscillator valve have been checked for emission, and the set was found to have a good 3Mc/s response on both channels 1 and 9. There is no evidence of 50c/s hum or interference on the raster and the frame hold is functioning perfectly.—L. R. Whieldon (Elstead, Surrey).

While the emission of the line generator valve may check normal, it is possible that a drift in its characteristics takes place when it increases in temperature. This valve should be checked by substitution with this kind of symptom. If the valve is OK, check by substitution, the components in the time-constant circuits of the line oscillator and the resistor(s) in the line hold control circuit.

**EKCO TC268**

The fault is a very loud buzzing on both ITV and BBC. The valves in the tuner unit have been changed and so have the coils for both channels. The fine tuner affects the noise very little.

The trouble seemed to coincide with the changing of the line output transformer.—G. Metcalf (Halifax, Yorkshire).

You should check the smaller 16 $\mu$ F electrolytic capacitors associated with the i.f. strip.

**SOBELL ST282**

The valve V6 (PCL84) burned out—it had a short from cathode to filament. After replacing this valve with a new one, the picture was pale and delayed. I then changed over PCL84 (V10) with PCL84 (V6). The sound was then delayed and when it did appear it was very crackly.—T. Edwards (Swansea, South Wales).

It seems as though the new PCL84 is faulty. However we would suggest that you check the resistors which are associated with the originally faulty PCL84—particularly the cathode bias resistor.

**MURPHY V929U**

The field hold is critical, particularly on 625. Also the top of the picture is elongated but this is not accompanied by cramping at the bottom. The field linearity control will not reduce the top of the picture, even at the end of its range. The interlace control is also at the end of its range and any increase in either direction here also stretches the top of the picture.

I have renewed the diodes in the flywheel circuit because out-of-phase with manual control. The picture was not correctly on raster then. This line trouble was caused by the renewal of these diodes but the field trouble started long after this repair.—J. F. Grindley (Oswestry, Salop).

We would advise you to try the interlace diodes, which are similar rectifiers to the ones which you have already replaced. In the circuit these are designated 3MR3 and 3MR4.

**EKCO T345**

The picture has slowly faded away over the last year and I have purchased a new CME 1703 c.r.t. I have some basic electronic knowledge and would appreciate some notes about the installation of the new tube.—E. L. Thomas (Marham, Norfolk).

Once the chassis is out of its cabinet, there is little left to be done. Remove the tube base socket and the neck clamps etc. Remove the e.h.t. lead from the side of the tube. Then slacken the front clamping band and remove the tube.

**FERGUSON 305**

This set has three faults: (1) The picture rolls for five minutes when first switched on, but can be stopped by adjusting the horizontal hold. After a few minutes the picture is gradually displaced to one side but can be centred by re-adjusting the horizontal hold to its original position. (2) The picture gradually creeps up from the bottom of the screen. (3) The contrast control makes no difference to the picture whatsoever.

It may help you to know that this set, although used very little, has been stored for several years, probably in damp conditions.—G. Tawn (Wisbech, Cambridgeshire).

You should check V17 (EF80) and V18 (ECC81) by replacement. Also check V16 (PCL82). Testing these valves proves very little.

Check 0.5 $\mu$ F a.g.c. line capacitor, also V11 (PCF80).

**FERGUSON 546T**

The left half of the screen is much more brilliant than the right. The scan is good with the exception that after approximately one hour there is a foldup of approximately  $\frac{3}{4}$  in. at the bottom.—A. Hills (Haslington, Crewe).

There is a 0.25 $\mu$ F capacitor which decouples the "A" supply to pin 3 of the c.r.t. base. Check this capacitor (C112) preferably by replacement. Also check the lower PCL82 and the 0.01 $\mu$ F capacitor C97.

**COSSOR 950**

The sound on this set is OK. There is a bright line across the screen. Recently the PL84 and ECC82 have been changed but no improvement was obtained.—A. D. Burge (Highfields, Leicester).

If the effect is a collapse of raster to a bright horizontal line, as distinct from the line being present actually on the raster, then the field timebase has failed. If the field timebase valves are in order, a systematic check of the associated components should be made, along with voltage tests to check the goodness of the resistors, coils and transformer windings. It is possible that the primary of the field output transformer has failed or even that the connections have broken between the secondary of this transformer and the field scanning coils.

**PHILIPS U.H.F. TUNER**

I have purchased a Philips u.h.f. tuner and i.f. panel for adapting Philips and associated TV receivers for BBC-2. The type number is Mk. 84006. I would appreciate some information as to the type numbers of the sets for which this particular tuner and i.f. panel are suitable.—E. M. A. Barrell (Holland-on-Sea, Essex).

The conversion kit is intended for use with the Philips models 19TG142A—9142, 23TG121A—3121, 9121, 9122, 9123 and 9125. Stella models are: ST1049A, ST1089A, ST1043A. The Peto-Scott model is TV945.

**EKCO T345**

The screen has a black band top, bottom and sides which is about  $\frac{1}{2}$  in. wide.—W. H. Goodman (Allestree, Derby).

It would appear that the h.t. rectifier is failing. This is the large valve situated above the width settings. Try a new PY33.

**EKCO T371**

Please could you inform me how to remove old tube and fit a new one, advising on adjustments and precautions.—G. O'Neill (Belfast, N. Ireland).

Remove the rear cover. Rotate the fine tuner and expose channel switch knob shank grub screws. Loosen these and remove the knobs. Remove panel screw and pass control panel into cabinet. Pull off loudspeaker leads and remove the four bottom chassis fixing screws. The chassis should now come out if the front of the tube is not stuck too fast to the front mask. Some force may have to be used to break this adhesion. Remove the tube base socket and clamp etc. Remove e.h.t. lead from the side of the tube. Slacken the front clamps and remove the tube.

**QUERIES COUPON**

This coupon is available until MARCH 23rd, 1967, and must accompany all Queries sent in accordance with the notice on page 281.

PRACTICAL TELEVISION, MARCH, 1967

**TEST CASE -52**

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions, but are based on actual practical faults.

After a repair in the power supply input circuit, an experimenter was presented with a single-standard receiver exhibiting severe hum bars on the picture. Although the residual hum on sound did not appear to be abnormally high, slant tests were made with electrolytic capacitors across the main reservoir and smoothing capacitors in the set, but this had no effect whatever on the symptom.

The vision valves were tested for heater/cathode insulation and eventually tested by substitution, but the trouble was not to be found here. Short-circuiting the control grid of the video amplifier valve left the hum bars as before, but a slight decrease in intensity was noted by connecting the tube control grid to chassis through an  $0.1\mu\text{F}$  capacitor.

What was a likely cause of this symptom? The answer will be given in next month's PRACTICAL TELEVISION along with a further item in the Test Case series.

**SOLUTION TO TEST CASE 51  
Page 237 (last month)**

If the experimenter had adjusted the cores in the sound i.f. transformers with the fine tuning control adjusted for the best possible picture he would probably have found that the tuning was very peaky and probably towards the end of the travel of the cores. This would have indicated positive feedback in the sound i.f. stages of sufficient magnitude to peak the response yet insufficient to promote real instability and oscillation. The most likely cause of this trouble is open-circuit of a screen grid decoupling capacitor. Apart from inducing mild positive feedback, depending on the circuit design, trouble of this kind can also detune the stages, giving the symptom fully described last month.

The enthusiast shunted each screen decoupling capacitor in turn with a similar value capacitor, using the shortest possible lead-outs. On shunting the faulty capacitor the sound returned to normal with no apparent peaking of the i.f. tuning.

**SITUATIONS VACANT**

**RADIO AND TV Exams.** and Courses by Britain's best home study School. Coaching by Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Certificate etc. Free brochure from British National Radio School Russell Street, Reading.

**ALDERMASTON COURT POSTAL TRAINING** for B.Sc. (Eng.) Part 1, A.M.I.F.R.E., A.M.S.E., City and Guilds, G.C.E., etc. prepares you privately for high pay and security as Technician or Technologist, Thousand of Passes. For details of Exams and Courses in all branches of Engineering, Building, Electronics, etc. (including latest information on C.Eng.) write for 132-page Handbook—FREE. Please state interest. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 171K), Aldermaston Court, Aldermaston, Berks.

**EDUCATIONAL**

**TV and Radio, City & Guilds R.F.E.B. Certs.**, etc. on "Satisfaction or Refund of Fee" terms. Thousands of passes. For full details of exams and home training Courses (including practical equipment in all branches of Radio, TV, Electronics, etc.) write for 132-page Handbook—FREE. Please state subject. **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY** (Dept. 172K), Aldermaston Court, Aldermaston, Berks.

**BECOME "Technically Qualified"** in your spare time guaranteed diploma and exam. home-study courses in radio, I.V. servicing and maintenance. T.I.F.B., City and Guilds, etc.; highly informative 120-page Guide—FREE. **CHAMBERS COLLEGE** (Dept. 858K), 148 Holborn, London, E.C.1.

**TECHNICAL TRAINING**

**CITY & GUILDS** (electrical, etc.) on "Satisfaction or Refund of Fee" terms. Thousands of passes. For details of modern courses in all branches of electrical engineering, electronics, radio, T.V. automation, etc., send for 132 page handbook—FREE. **B.I.E.T.** (Dept. 173K) Aldermaston Court, Aldermaston, Berks.

**MISCELLANEOUS**

**CONVERT ANY TV SET** into an Oscilloscope. Instructions and diagrams 12/6. **REDMOND**, 42 Dean Close, Portlisle Sussex.

**FOR SALE**

**VALVE CARTONS** at keen prices. Send 1/- for sample and list. **J. & A. BOX-MAKERS** 75a Godwin Street, Bradford 1.

**METAL RECTIFIERS**

**RECTIFIERS—CONTACT COOLED**  
14RA259/FC101, 13/6; 14R12281 PC124FW, 13/6;  
K31 13/-; FC118 7/6; 14RA1263 FC31 see Silicon.  
**RECTIFIERS—PIN TYPES**  
Equivs. for KM4 9/6; KM5 17/6; 14A97 13/6;  
14A98 10/6; EK2 17/6; EK6 17/6; 14A99 10/-;  
14W16 19/-; LW7 19/-; 14A100 19/-; 14A99 10/-;  
FW251A 5/-; 2A 7/-; 4A 10/6.  
**SILICON TV 6/6** or with instr. resist. cond. 7/6.  
**MULTIMETERS** from 32/-.  
Stamped envelope for full latest selection and bargain offers in cheap meters, Radios, Baby Alarms Inter-coms and Walkie-Talkies.  
**LINE O.P. TRANS.** ALL 30/- EACH. Murphy V350-V250, Cosmor 948, Philips 1440/145 and 1746/145 with EY31.  
Under £1 P. & P. 6d. Over £1 Post Free. NO C.O.D.

**DURHAM SUPPLIES**

175 DURHAM ROAD, BRADFORD 8, YORKS.

**RATES:** 4/- per line or part thereof, average five words to line, minimum 2 lines, Box No. 1/- extra. Advertisements must be prepaid and addressed to: Advertisement Manager, "Practical Television", Tower House, Southampton Street, London W.C.2.

**WANTED**

**NEW VALVES WANTED** . . . EY51, FY86, PL84, FCC84, PCF80, PCL82, PCL83, FY81, R19, 30P19, U25, etc. Best cash price by return. **DURHAM SUPPLIES**, 175 Durham Road, Bradford 8, Yorks.

**WANTED—Popular Brand New Valves—**R.H.S., Stamford House, 538 Great Horton Road, Bradford 7.

**SERVICE SHEETS** purchased. **HAMILTON RADIO**, Western Road, St. Leonards, Sussex.

**WANTED I.F. panel assembly** for G.E.C. model. B.T. 347. BEST, "Kendor", Tower Close, Liphook, Hants.

**DAMAGED AVO METERS WANTED.** Models 7 and 8. Any condition. Any quantity. **HUGGETTS LTD.**, 2-4 Pawson's Road, West Croydon. Send for packing instructions.

**AERIALS**

**TV AERIALS**

Band I, H. Mast Fitting . . . . £1 15 0  
Band III, 5 Ele Mast Fitting . . . . £1 10 0  
Band IIII, S/D and 4-Array . . . . £1 15 0  
Band IV, 9 Ele Array . . . . £1 10 0  
Band IV, 18 Ele Array . . . . £2 18 0  
Lashing Kits from 10/-; Poles, Co-ax 6d., Grade "A" 1/4. Plugs 6d., C.W.O., S.A.E. for list.

**TELEINDUSTRIES LTD.**

**BREAKSPEAR ROAD, RUISLIP, Middlesex**

**SETS & COMPONENTS**

**OLYMPIC II TV, S.A.E.** for itemised price list. **AJAX ELECTRONICS**, 18a Rumbold Road, Fulham S.W.6.

**A.1 POST FREE BARGAINS**

Guaranteed reclaimed valves

6C0L2	6/3	EB01	1/-	PL38	6/-
6F1	1/7	EBF80	2/6	PL82	3/-
6FL3	4/9	EC041	3/6	PL83	4/-
6FL4	4/9	EC082	3/-	PY80	2/-
6FL5	5/6	EC180	1/6	PY82	1/6
6FL7	5/-	EF42	4/-	PY84	1/6
6LL18	5/6	EF50	1/3	PY33	5/-
10C2	4/7	EF80	1/1	PY800	4/9
10F1	1/7	EPF5	4/6	F41	3/-
10F13	2/6	EPF91	1/3	U31	2/6
20D1	1/9	EP184	5/-	U25	9/-
20P2	4/3	EY86	3/9	U231	4/9
20P1	2/6	KT01	3/-	U281	5/-
20P3	4/-	LE3	2/-	U282	5/-
20P5	6/-	N37	3/-	U301	5/-
30F5	4/6	N29	10/-	U301	7/-
30FL1	6/-	PCF80	2/-	U41	5/-
30P5	5/-	PCF86	6/6	UF42	4/-
30P1	4/3	PCL83	3/-	U8	8/-
B36	3/9	PL28	2/6	W239	7/3
EB41	3/6	PL26	3/9	Z66	3/-

10% discount on order for 8 or more valves  
Salvage Valves 30/- per 100 (our choice)

**A.1 RADIO COMPONENTS**

14 The Borough, Canterbury, Kent.

**BI-PAK—VALUE PAKS**

NEW—UNMARKED—UNTESTED

- 120 **GLASS SUB-MIN. GERM. DIODES 10/-**
- 20 **MIXED VOLTS. ZENERS 10/-**  
UP TO 16 WATTS SILICON NPN 200 M/C/S
- 25 **TRANSISTORS 10/-**  
SUB-MIN 200 MA
- 60 **SILICON DIODES 10/-**
- 20 **GERM. RECTIFIERS 10/-**  
1 AMP. TOP HAT 750 MA
- 16 **SILICON RECT. 10/-**
- 50 **MIXED TRANSISTORS 10/-**  
STUD TYPE 1 AMP
- 10 **SILICON RECT. 10/-**

**TESTED NEW VALUE PAKS**

- 6 **BY100 TYPE RECTIFIERS, 20/-**  
800 PIV 550mA
- 3 OC139 Trans. NPN Mullard . . . . 10/-
- 2 Infr Trans. 2N1225 100 M/C/S . . . . 10/-
- 6 Matched Trans. OC84/450/18119 . . . . 10/-
- 4 OA10 Diodes Mullard . . . . . 10/-
- 15 Red Spot AF Trans. PNP . . . . . 10/-
- 15 White Spot RF Trans. PNP . . . . . 10/-
- 4 Sil. Rects. 3A 100/400 PIV . . . . . 10/-
- 4 NPN Genra. Switching Trans. . . . . 10/-
- 2 10 Amp. Sil. Rect. 500/100 PIV . . . . . 10/-
- 8 Diodes 4 OA70 1 OA79 . . . . . 10/-
- 1 5 AMP SCR 100 PIV . . . . . 10/-
- 3 Sil. Trans. 28503 PNP . . . . . 10/-
- 5 GERT 884 Trans. Eqt. OC34 . . . . . 10/-
- 10 Assorted Computer Diodes . . . . . 10/-
- 4 Zeners 5 to 12 vits. Mixed . . . . . 10/-
- 4 20447 Trans. Eqt. AF11077 . . . . . 10/-
- 2 200 M/C/S Sil. Trans. BS92677 . . . . . 10/-
- 2 Bi-directional Trans. BS92677 . . . . . 10/-
- 4 High Current Trans. OC32 . . . . . 10/-
- 2 Power Trans. OC2635 . . . . . 10/-
- 5 Sil. Rects. 400 PIV 250mA . . . . . 10/-
- 3 OC71 Trans. Mullard . . . . . 10/-
- 2 4P7s Mullard . . . . . 10/-
- 3 NPN Sil. Trans. 50 M/C/S . . . . . 10/-
- 1 Power Trans. OC20 100 Vits . . . . . 10/-
- 3 OA47 Gold Bonded Diodes . . . . . 10/-
- 4 OA202 Sil. Diodes Sub-Min . . . . . 10/-
- 3 OC77 Trans. Mullard . . . . . 10/-
- 8 OA11 Diodes CV448 . . . . . 10/-
- 3 Sil. Rects. 400 PIV 500 mA . . . . . 10/-

**FREE** One 10/- Pack at your own choice with orders valued £4 or over. **FREE**

- 3 High vit. AF Trans. PNP ACY17 . . . . 15/-
- 5 Sil. Rect. 750mA 100 PIV 6X45A . . . . 15/-
- 3 BS95A Sil. Trans. SFC . . . . . 15/-
- 3 Sil. Trans. OC200 Mullard . . . . . 15/-
- 2 Sil. Power Rect. 6 Amp. 200 PIV . . . . 15/-
- BZ13 . . . . . 15/-
- 1 100V GERM. TRANS. 20 M/C/S . . . . . 15/-
- 1 Sil. Power Trans. 100 M/C/S NPN TK201A . . . . . 15/-
- 6 Zener Diodes 3-15vits. Mixed 400mW . . . . . 15/-
- 5 OA5 Gold Bonded Diodes Eqt. . . . . 15/-
- 1 2N132 PNP PLANAR Trans. Sil . . . . . 15/-
- 2 2N697 NPN PLANAR Trans. Sil . . . . . 15/-
- 4 GERM. Power Trans. eqvt. OC16 Mullard . . . . . 15/-
- 1 UNFUNCTIONING Trans. 2N3640 G.E. . . . . 15/-
- 2 Sil. Trans. 60VCB 200 M/C/S ZTS304 . . . . . 15/-
- 1 Sil. PLANAR Trans. BS925 NPN 100 M/C/S . . . . . 15/-
- 1 Sil. Trans. 18104 160 M/C/S BEF 200 NPN . . . . . 15/-
- 2 SCR's 50 PIV 1 Amp. TO-5 can . . . . . 15/-
- 1 Tunnel Diode IN370 (TD-5) G.E. . . . . 15/-
- 1 2N2160 UNFUNCTIONING Trans. TO-5 can . . . . . 15/-
- 2 Sil. Rect. 5 Amp. 400 PIV Stud . . . . . 15/-
- 1 Tunnel Diode AEY 11 1000 M/C/S . . . . . 15/-
- 3 GERM. Power Trans. OC2829 . . . . . 15/-
- 2 Zeners 5W. 15 and 25 vits . . . . . 15/-
- 1 400 PIV SCR 7 Amp. . . . . 15/-
- 8 Sil. Rect. 400 PIV 500mA . . . . . 20/-
- 1 Transistor Manual by G.E. 648 pp. . . . . 30/-
- 1 Silicon Controlled Rect. Manual G.E. . . . . 30/-
- 25 Marked & GERM. Trans. New & Marked . . . . . 30/-
- 40 Mixed Semiconductor New Marked 40/-
- 1 Logic Module Handbook & Cat. 17/6

**MINIMUM ORDER 10/- CASH WITH ORDER PLEASE.** Add 1/- post & packing PER ORDER. Full Lists 100's Bargains 6d. in stamps

**BI-PAK SEMICONDUCTORS**

(DEPARTMENT T)  
8 Radnor House, 93-97 Regent St., London, W.1. Mail only.



**SETS & COMPONENTS**

(continued)

TV SPARES, fully guaranteed Makers' Parts. Telephone orders sent same day C.O.D. Line O.P. Trans: Murphy V270/280 99/6, Ekco T311, 330, 221, 231, 327 series and Pye VI4 etc., all 62/6. Most types stocked. Send S.A.E. for quote. Add 4/- p.p. Ekco/Ferr. Plastic Hsgs, 15/- KING'S (ORPINGTON) LID., 8 Cray Parade, Main Road, St. Paul's Cray, Kent. Orpington 30566.

**STOP**

**FULLY GUARANTEED L.O.P.T. REWINDING SERVICE**

A few of the types are listed below:—

- BUSH TV 53-86.
- K.B.P.V.P.20, etc.
- PHILIPS 1768U, 17TG100U, etc. All at 50/-

**NEW FROM STOCK**

- U25 Type EKCO, state model. PYE 200-400.
- FERGUSON 306-308 305-307 All at 45/-
- FERGUSON 406, 408, 416, 36, 438
- S.A.E. Enquiries P. s P. 4/-, C.O.D. 6-

**WITWORTH TRANSFORMERS Ltd.**  
26 All Saints Road, North Kensington  
W.11 Telephone BAY 9071

**GUARANTEED IDEAL FOR ANY RECORDER**

**TAPE** World Famous make. PRICES SLASHED. APPROX. HALF PRICE!

By enormous purchase we can offer you fully tensilised Polyester/Myia and P.V.C. tapes of identical Hi-Fi wave range recording characteristics as top grade tapes. Quality control manufacture. Not standard in any way. TRY One for YOURSELF. They are TRULY WORTH A FEW MORE COPPERS.

STANDARD PLAY		DOUBLE PLAY	
3"	150'	3"	300'
4"	300'	4"	600'
5"	600'	5"	1200'
5 1/2"	900'	5 1/2"	1800'
7"	1200'	7"	2400'
LONG PLAY		TRIPLE PLAY	
3"	225'	4"	600'
4"	450'	5"	1800'
5"	900'	5 1/2"	2400'
5 1/2"	1200'	7"	3600'
7"	1800'	QUADRUPL PLAY	
		3"	600'

Postage 1/- per rec.,  
Post free and less 5% on three.  
Trade and quantity enquiries welcome.

**TECHNICAL TRADING CO.**

All Mail Orders to Brighton Please.  
Devonian Court, Park Crescent  
Place, Brighton 689722, 67606  
350/352 Fratton Road, Portsmouth 22034  
72 East Street, Southampton 25851  
132 Montague Street, Worthing 2639

**SERVICE SHEETS**

SERVICE SHEETS (75,000) 4/- each. Callers welcome. ALWAYS OPEN. 5 South Street, Oakenshaw, Bradford.

**SERVICE SHEETS**

For all makes of Radio, Television, Tape Recorders, 1925-1967. Prices from 1/-. Catalogue of 6,000 models, 2/6. Free fault-finding guide with all Service Sheets. Please send Stamped Addressed Envelope with all orders and enquiries.

**HAMILTON RADIO**

Western Road, St. Leonards, Sussex

**SERVICE SHEETS**

(continued)

SERVICE SHEETS. Radio, TV 5,000 models. List 1/-, S.A.E. enquiries. TELRAY, 11 Maudland Bk, Preston.

**SERVICE SHEETS**

4/- each, plus postage

We have the largest supply of Service Sheets for all makes and types of Radios and Televisions, etc. in the country (speedy service).

To obtain the Service Sheet you require please complete the attached coupon:

Name: .....

Address: .....

.....

To: S.P. DISTRIBUTORS

35/36 Great Marlborough Street, London, W.1

Please supply Service Sheets for the following:

Make: .....

Model No..... Radio/TV...

Make: .....

Model No..... Radio/TV

Make: .....

Model No..... Radio/TV

I also require new 1967 List of Service Sheets at 1/6 plus postage

(please delete items not applicable)

enclose remittance of.....

(which includes postage)

MAIL ORDERS ONLY (Mar. PT.)

**PADGETTS RADIO STORE**

**OLD TOWN HALL**

**LIVERSEDGE, YORKSHIRE**

Telephone: Cleckheaton 2866

Pye VI4, 14" TV set 13 Channel fitted with brand new Tube, condition of cabinet fair. Good working order. £51.0.0. Plus carriage 10/-

19 Sets with outer case. Receiver section complete with valves.  
Parts Removed: 500 micro-amp meter, all transmitter part. Relay and 805 valve. Condition fair. No dry rot, 10/5. Carriage 10/-.  
Reclaimed Tubes, Six months' guarantee. AWB080, 30/-, MW3080, 30/-, MW4000, 50/-, CRM172, 30/-, CRM182, 17/-, 12in. Tube at 10/-, 17in. Tubes perfect but without guarantee, 17/- each. Carriage on any Tube in G.B. 10/-. Specially Selected Nearly New Valves, 6 months' guarantee

PY5	6/-	A.P.1	1/0	11.5	5/-
PCC84	5/6	CC120	7/6	10.4	4/-
PCP80	5/6	PCC63	5/-	6.57	1/8
PL81	5/6	PCC82	4/6	2.82	1/8
47	5/-	EP91	2/-	18.8T	8/6

Single Valves. Post 7d.

**VALVE LIST**

Ex. Equipment, a months' guarantee. Single Valves. Post 7d.

EP80	1/6	PCC86	2/-	10P13	2/6
EC120	1/6	PCC84	2/-	10P16	5/-
EP81	5d.	PCL82	4/-	20D1	3/-
EB81	5d.	PCL83	3/-	20L1	5/-
EP80	3/-	PCL85	3/-	20P1	4/-
ECC81	3/-	U250	5/-	20P4	8/6
ECC82	3/-	PY81	1/6	U250	5/-
ECC83	4/-	PY82	1/6	U801	8/6
EL84	5/-	PL81	4/6	U301	5/-
EP80	1/6	PL36	5/-	U391	5/-
EX36	5/-	PY33	5/6	U281	5/-
6K25	5/-	6B8	1/6	U282	5/-
6P1	5/-	6P1	1/-	U25	5/-
6P25	5/-	6P14	5/-		
KT36	5/-	10Y	5/-		

Breaking up 19 Sets.  
Relays 100 Ohm Coil 2/-, Post 2/6. 1 Doz. 20/-, Post Paid. Jack Sockets 7/6 doz. Post Paid.

Toggle Switches 7/6 doz. Post Paid. Pointer Knobs 7/6 doz. Post Paid. Top Grade Diodes 3/6 doz. Post Paid. No duty.

Perfect Speakers, removed from TV sets. Goodmans 7 x 4, 5/-, Goodmans 8 x 5, 7/6, 6 x 4 and 5in. 3/-, Plus Post on any Speaker, 4/-.

New 12 inch Speakers, with built-in tweeter, 28/6, 3 or 4 Coil, 25/6, Post Paid. New 24 volt Miniature Model Makers Motor will run from 6 volts, 6/6. Post Paid. Motors Single Phase Quarter H.P., 26/-, Sixth H.P., 15/-, Ex Washing Machines, Fully guaranteed. Plus Carriage 10/-. Type 46 Set. Complete with valves. Send receive switch removed, 12/6, Post Paid.

**RAPID SERVICING OF TRANSISTOR EQUIPMENT**


GORDON J. KING

160 pages, 90 line and half-tone illustrations Directed to the service technician changing from valves to transistors, students starting a career in electronics, and the enthusiastic amateur, it describes semiconductors and transistors their operating principles and circuitry, together with basic test procedures, and then concentrates on fault diagnosis in the various fundamental types of circuit—audio and video amplifiers, R.F. circuits and oscillators—each section concluding with a Fault Diagnosis Summary Chart. Chapters are devoted to the ordinary transistor portable receiver and practical advice on repair procedures.

160 pp. 90 line and half-tone illus. 30s. FROM ALL BOOKSELLERS or in case of difficulty, 32s by post from

**NEWNES,**

Tower House, Southampton Street, W.C.2

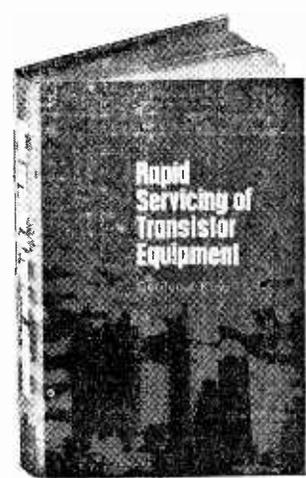

Less than HALF list price!

# SUPERB LUSTRAPHONE MOVING COIL MICROPHONE

Guaranteed brand new in maker's box... offered at below cost, list price £3.7.6. Your opportunity while surplus stocks last. This high quality microphone is complete with 9ft. cable and standard co-axial plug. Frequency response **ONLY 26/-** POST FREE IN U.K.



70-12,000 cycles/sec., sensitivity —75 db(m). Medium impedance, nominal 600 ohms. Lead can be extended up to 100ft. without loss of quality. FREE! Circuit for low-cost transistor pre-amplifier for matching to high-impedance input. **RUSH YOUR ORDER NOW!**

**ANDREW MERRYFIELD LTD**

Dept. PT/811 29 Wright's Lane, Kensington, London, W.8.

## TELEVISION RECEIVER THEORY: Part I

A Textbook for Students and Technicians  
G. H. Hutson 35s. net

The first of two volumes which together provide a systematic course in television receiver theory, including a study of both positively and negatively modulated systems and embracing both valve and transistor circuitry.

## ELECTRICAL SCIENCE FOR ELECTRICAL INSTALLATION STUDENTS: Part I

J. A. Myers 12s. 6d. net

The first of two volumes written to cover the syllabus of Electrical Science for Electrical Installation Course 'B' of the City and Guilds of London Institute. It is also suitable for students preparing for Course 'A' and for other courses where a practical approach to the subject of Electrical Science is required together with an emphasis on calculations.

A catalogue containing information on all technical publications can be obtained on request from the publisher.

**EDWARD ARNOLD**

41 MADDOX STREET, LONDON W.1

### NEW RANGE U.H.F. AERIALS FOR BBC 2 (625) line transmissions

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
**Loft Mounting Arrays, 7 element, 35/-, 11 element, 42/6, 14 element, 50/-, 18 element, 57/6. Wall Mounting with Cranked Arm, 7 element, 60/-, 11 element, 67/-, 14 element, 75/-, 18 element, 82/6. Mast Mounting with 2in. clamp, 7 element, 42/6; 11 element, 55/-; 14 element, 62/-; 18 element, 70/-; Chimney Mounting Arrays, Complete, 7 element, 72/6; 11 element, 80/-; 14 element, 87/6; 18 element, 95/-.** Complete assembly instructions with every unit. **Low Loss Cable, 1/6 yd. U.H.F. Preamps, from 75/-.** State clearly channel number required on all orders.

### BBC · ITV · FM · AERIALS



**BBC (Band 1).** Telescopic loft array, 25/-, 5 element, 35/-, Wall mounting, 3 element, 35/-, 5 element, 45/-.  
**Combined BBC/ITV.** Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.  
**NIF** transistor preamps, 75/-.

**F.M. (Band 2).** Loft S/D, 12/6, "H", 30/-, 3 element, 52/6. External units available. Co-ax cable, 8d. yd. Co-ax plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 5/-.

Send 6d. stamps for illustrated lists. Quotations for special arrays available on request

**K.V.A. ELECTRONICS (Dept. P/T)**  
27 Central Parade, New Addington Surrey  
LOD 2266

### NEW VALVES

Guaranteed Set Tested  
24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET OF 4, 15/9.  
DAF96, DF96, DK96, DL96, SET OF 4, 23/6.

1R5	5/-	EABC80	5/6	PCL83	8/3
1S5	3/9	EAF42	7/-	PCL84	7/3
1T4	2/8	EBF41	6/6	PCL85	7/9
3S4	4/3	EBF30	5/6	PL26	9/-
3V4	5/-	EBF89	5/9	PL81	6/3
5V4G	7/9	ECC81	3/3	PL82	6/9
6F1	6/3	ECC82	4/6	PL83	5/11
6K7G	7/3	ECC83	4/6	PL84	6/-
6K8G	3/3	ECC85	5/3	PY32	8/3
6L19	7/3	ECH35	5/9	PY33	8/3
6V6G	3/-	ECH42	8/9	PY81	5/-
10C2	11/3	ECH81	5/-	PY82	4/9
10F1	9/6	ECL30	5/9	PY83	5/3
10P13	8/3	ECL32	8/-	PY800	5/11
20F2	10/3	ECL86	7/6	R19	6/6
20P1	8/9	EF39	3/6	U25	8/9
20P3	8/9	EF41	5/9	U26	8/6
20P4	12/6	EF90	4/3	U81	10/-
30F5	9/9	EF95	5/-	U301	11/6
30P4	11/6	EF86	6/-	U801	16/-
30P19	11/6	EF89	4/9	UABC80	5/-
DA C32	6/9	EL33	6/3	UAF42	6/11
DAF91	3/9	EL41	8/-	U81	10/-
DAF96	5/11	EL84	4/3	UBF89	5/9
DF33	7/6	EY51	5/11	UC84	8/-
DF91	2/9	EY86	5/3	UCC85	6/-
DF96	5/11	EZ40	5/6	UCF80	8/6
DK32	7/-	EZ30	3/6	UC82	5/6
DK91	5/-	EZ81	4/3	UCH81	5/9
DK96	6/3	GZ32	8/9	UYL82	6/9
DL33	6/6	KT61	6/3	UYL83	8/6
DL35	4/9	N78	14/6	UF41	7/9
DL92	4/3	PCF84	5/3	UF89	5/6
DL94	5/-	PCF89	9/9	UL41	7/9
DL96	5/11	PCF80	8/3	UL84	5/3
DY86	6/3	PCF82	5/9	UY41	4/9
EY87	6/3	PCL82	6/3	UY85	4/9

Postage on 1 valve 9d. extra. On 2 valves or more, postage 8d. per valve extra. Any parcel insured against damage in transit 6d. extra.

Office address, no callers.

### GERALD BERNARD

83 OSBALDESTON ROAD  
STOKE NEWINGTON  
LONDON N.16

### FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and TV. Let us show you how.

#### FREE GUIDE

The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.I.E.R.E. Guide also gives details of range of diploma courses in Radio/TV Servicing, Electronics and other branches of engineering, together with particulars of our remarkable terms of

#### Satisfaction or refund of fee

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES

#### CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)  
(Dept. 884V), 148 HOLBORN  
LONDON, E.C.1

# REBUILT TUBES !

*You're safe when you buy from RE-VIEW !*



- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for two years against all but breakage.
- ★ Each tube is delivered free anywhere in the U.K. and insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

## HERE IS WHAT YOU PAY:

12in. . . . .	£4.15.0
14in. . . . .	£5. 0.0
15in. . . . .	£5. 5.0
17in. . . . .	£5. 5.0
19in. . . . .	£5.15.0
21in. . . . .	£7. 5.0

*Cash or cheque with order, or cash on delivery*

**Discount for Trade**

*Old Tubes Purchased*

## RE-VIEW ELECTRONIC TUBES

237 LONDON ROAD, WEST CROYDON, SURREY. Tel. THOrnton Heath 7735

*J. P. Hawker's new book  
— planned as the standard guide . . .*

# OUTLINE OF RADIO AND TELEVISION

This introductory book starts with clear explanations of electric currents, radio and audio waves and electronic components, and continues through to the most advanced items of equipment such as u.h.f. television tuners, multiplex stereo systems and colour television receiver techniques. A must for your reference bookshelf. *408 pages, over 300 diags., 30s.*

*From all booksellers or by post 32s. 6d. from George Newnes Ltd.*

**NEWNES** Tower House, Southampton Street, W.C.2

## BBC2, TV, RADIO & TAPE REC. SPARES

UHF/625. Modify your set to BBC2. 1953 to 1963 models covered. Selection of new manufacturers conversion kits and tuners at reduced prices. List available. **SPECIAL OFFERS: FERGUSON** 625 1F amp. chassis, NEW, incl. 6 valves 39/8 (less valves, 19/8). Circuit and instr. 3/6, p/p 4/6. **PHILIPS** 625 conversion kit, incl. tuner, 1F amp., valves, circuits etc. £2.10.0, p/p 6/-. **GEC/BOBELL** dual 405/625 1F amp. and output chassis, NEW 45/-, p/p 4/6. **UHF TUNERS**. NEW, with valves, 30/-. **PHILIPS** transistorised 70/-, p/p 4/6. **TV SIGNAL BOOSTER UNITS**. Sens. gain all stations. PVE/LABGEAR trans'd. BBC1/ITA or UHF Battery "plug in", 75/-. UHF Mains "plug in", 97/8. UHF Method 105/-. Post free. **FIREBALL TUNERS**. New/tested (KB, RGTN, RGD, PVE, ULTRA, PILOT, etc.) suitable for other models, 75/-, p/p 4/6. **TURRET TUNERS**. New, Cydon C, 38 Mc/s 20/-. Brayhead 10, 16, 38 Mc/s 25/-. KB 16 Mc/s, KB MV/F 38 Mc/s, 10/-. EKCO 16 Mc/s 10/-, p/p 4/6. Many others available. Tech. Repl. service for special types incl. Pve, Ferguson, Sobell, Philips, GEC, McMich. Large selection Channel Coils, etc. **CRTs**. Rebuilt, 12 mths. guar. 17 in. 70°, 90°, 85/-; 17 in., 19 in. 110°, 105/-, callers only.

**LINE OUTPUT TRANSFS.** Popular types available, brand new exact replacements fully guar. A selection which can be supplied:—

<b>PHILIPS</b> 1768, 177G, <b>STELLA</b> 8617, 1017 range . . . . .	98/8	<b>LOPT Inserts</b> p/p 2/-
<b>EKCO</b> 221 to 331 (125) types . . . . .	42/6	<b>Cossor</b> 930 to 947 . . . . .
<b>FERRANTI</b> 1001 to 1011 (125 types) . . . . .	42/6	<b>Bush</b> TV53 to 69 . . . . .
<b>EKCO/FERRANTI</b> (126 types) 70°/90° . . . . .	58/8	<b>Emerson</b> 700 range . . . . .
<b>FERGUSON</b> 306, 308, 42/6; 406, 506 range . . . . .	58/8	<b>Ferranti</b> 203 to 246 . . . . .
<b>FERG/HMV/MARCONI/ULTRA</b> 800 850 series . . . . .	58/8	<b>Ferranti</b> 1475 to 1778 33/5
<b>MARCONI</b> VT157, 159, 160, 164, 58/6; others . . . . .	72/6	<b>Peto Scott</b> 1419 to 1724 35/-
<b>GEC</b> 1252, 1748, 2745 range 52/6 later models . . . . .	72/6	<b>Pye</b> V4, V7 range . . . . .
<b>HMV</b> 1865, 1869, 42/6; 1870/6, 1890/6 . . . . .	58/6	<b>RGD</b> Deep 17 . . . . .
<b>BOBELL</b> T817, 346 48/6; other models . . . . .	72/6	<b>RGD</b> 580 range . . . . .
<b>PVE, PAM, INVICTA</b> from . . . . .	62/6	<b>Reg.</b> 10-17 range . . . . .

Also, **ALBA, COSSOR, KB, McMICH, PHILCO, P/SCOTT, REG. RGD, ULTRA** etc. Postage and Packing for L.O.Ts 4/6. C.O.D. 3/6 extra. **SCAN COILS**. Frame off frame use, transf., width/linearity coils, sound o/p transf., mains droppers, control knobs, dual vol., controls, line osc. transf., resistors, condensers, etc. **TAPE RECCHANGERS**. Drive Belts, Heads Pinch Wheels, Hiders, Motors for most British (incl. WALTER) and Continental. **SALVAGED COMPONENTS**. Large selection for popular models, clean, serviceable condition, tuners, transformers, etc. ENQUIRIES invited, quotations given. C.O.D. despatch available.

## MANOR SUPPLIES

64 GOLDERS MANOR DRIVE, LONDON, N.W.11

(Callers: 589b, HIGH ROAD (nr. Granville Road), N. Finchley, N.12)  
Open all week inc. Sat., HIL 9118 (Day) SPE 4032 (Evg.)

# No.1 Just Out!

A NEW MAGAZINE FOR  
EVERY HOME HANDYMAN



No.1 OF THE *NEW* HOW-TO-DO-IT MAGAZINE  
**PRACTICAL** MARCH 1967  
**Decorating & Building**  
PRICE 2/6

**FREE!**

**QUANTITY  
CALCULATOR**  
for Glass,  
Cement, Paint,  
and wallpaper

**EXTRA!**

8-page  
Supplement  
**ALL ABOUT  
CEMENT &  
CONCRETE**

**EXTRA!**

Fold-out  
Data Sheet on  
**FITTING WINDOWS**



Backed by the full resources of Newnes famous 'Practical' group, PRACTICAL DECORATING AND BUILDING has been planned to bring every type of decorating and building job, however extensive or difficult, within the scope of the home handyman. Month by month it will include clear how-to-do-it instructions on a wide range of projects indoors and out . . . all about the latest techniques, ideas, tools and materials . . . and expert guidance on a hundred and one aspects of modern home improvement that will save you pounds on every job. In short, it's a must for every handyman. Go for No. 1, now!

**Packed with new ideas and  
detailed know-how on major  
home improvements**



**Hurry — Make  
sure of your  
copy NOW 2/6**