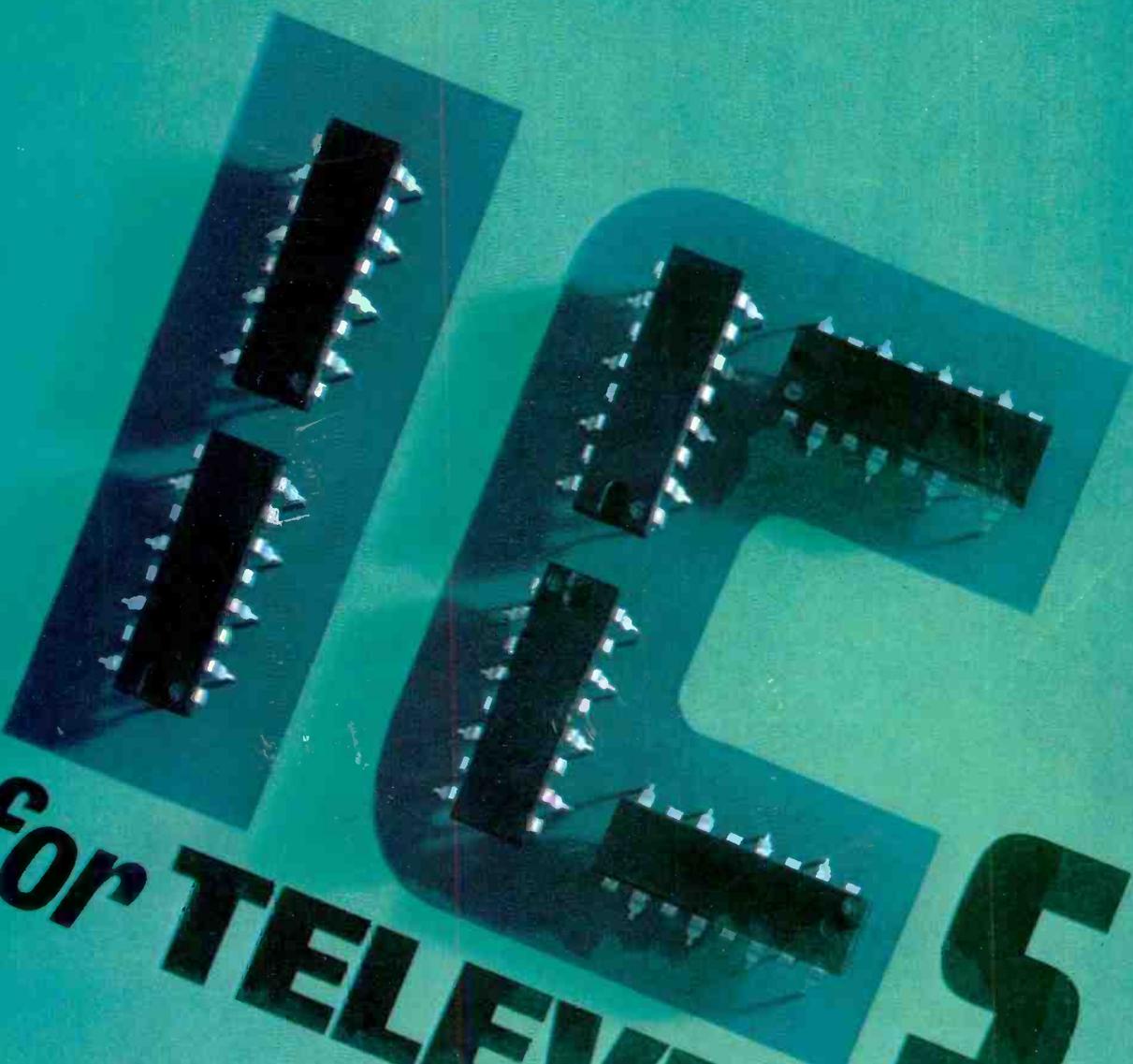


# TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

20p

SEPTEMBER  
1971



**U S**

**for TELEVISION**

**also:**  
THE CROWN 7TV105 PORTABLE  
SERVICING THE SOBELL ST195/ST282 SERIES  
TRANSISTORISED VIDEO/SYNC CIRCUITS for the constructor

# The largest selection

## BRAND NEW FULLY GUARANTEED DEVICES

AC107 15p	AF115 17p	BC140 35p	BCY31 22p	BF272 80p	EC403 15p	ORP60 40p	2N918 30p	2N2714 25p	2N3704 15p
AC113 20p	AF116 17p	BC141 35p	BCY32 25p	BF273 30p	GET880 27p	ORP61 40p	2N929 22p	2N2904 25p	2N3705 15p
AC115 23p	AF117 17p	BC142 45p	BCY33 17p	BF274 30p	MAT100 15p	ST140 12p	2N930 25p	2N2904A 30p	2N3706 15p
AC125 17p	AF118 30p	BC143 40p	BCY34 20p	BF308 35p	MAT101 17p	ST141 17p	2N1131 20p	2N2905 25p	2N3707 13p
AC126 17p	AF124 21p	BC145 45p	BCY70 17p	BF309 37p	MAT120 15p	T1543 40p	2N1302 22p	2N2905A 30p	2N3708 8p
AC127 17p	AF125 20p	BC147 20p	BCY71 30p	BF316 75p	MAT121 17p	UT46 27p	2N1302 22p	2N2906 25p	2N3709 8p
AC128 17p	AF126 20p	BC148 12p	BCY72 15p	BFW10 55p	MPF102 43p	V405A 25p	2N1303 17p	2N2906A 27p	2N3710 10p
AC141K 17p	AF127 20p	BC149 17p	BCZ11 20p	BFX29 27p	MPF105 43p	V410A 45p	2N1304 20p	2N2907 30p	2N3711 10p
AC142K 17p	AF139 33p	BC150 17p	BD121 85p	BFX85 27p	OC19 30p	2G302 19p	2N1305 20p	2N2907A 30p	2N3819 40p
AC151 15p	AF179 50p	BC151 20p	BD124 75p	BFX86 22p	OC22 30p	2G303 19p	2N1306 22p	2N2923 13p	2N3820 11p
AC154 15p	AF179 50p	BC152 17p	BD125 75p	BFX87 22p	OC23 33p	2G304 20p	2N1307 22p	2N2924 13p	2N3903 25p
AC155 17p	AF180 50p	BC153 27p	BD131 80p	BFX88 22p	OC24 33p	2G306 35p	2N1308 27p	2N2925 13p	2N3904 27p
AC156 17p	AF191 50p	BC154 30p	BD132 80p	BFY50 20p	OC25 25p	2G308 35p	2N1309 27p	2N2926 12p	2N3905 25p
AC157 17p	AF186 45p	BC157 20p	BDY20 11p	BFY50 20p	OC26 25p	2G309 35p	2N1711 20p	2N2926 11p	2N4058 15p
AC165 17p	AF239 37p	BC158 17p	BF115 22p	BFY51 20p	OC26 25p	2G309 35p	2N1711 20p	2N2926 11p	2N4059 15p
AC166 17p	AF211 37p	BC159 20p	BF117 45p	BFY52 20p	OC28 40p	2G339 17p	2N1889 35p (Y)	2N2926 11p	2N4060 12p
AC167 20p	AF212 45p	BC167 13p	BF118 60p	BFY53 17p	OC29 40p	2G339A 15p	2N1890 45p	2N2926 11p	2N4061 12p
AC168 20p	AF102 85p	BC168 13p	BF119 70p	BSX19 15p	OC35 33p	2G344 15p	2N1893 37p (O)	2N2926 11p	2N4062 12p
AC169 14p	AL103 85p	BC169 13p	BF152 35p	BSX20 15p	OC36 40p	2G345 15p	2N2160 60p	2N3010 80p	2N4062 12p
AC176 23p	ASV26 25p	BC170 12p	BF153 35p	BSY25 15p	OC41 20p	2G371 10p	2N2147 75p	2N3011 20p	2N5172 12p
AC177 20p	ASV27 30p	BC171 13p	BF154 35p	BSY26 15p	OC42 22p	2G371B 10p	2N2148 60p	2N3053 20p	2N5459 43p
AC187 30p	ASV28 25p	BC172 13p	BF157 45p	BSY27 15p	OC44 15p	2G374 17p	2N2192 30p	2N3054 50p	25034 75p
AC188 30p	ASV29 25p	BC173 13p	BF158 25p	BSY28 15p	OC45 12p	2G377 27p	2N2193 30p	2N3055 63p	25031 30p
AC177 20p	ASV29 25p	BC174 13p	BF159 30p	BSY29 15p	OC70 15p	2G378 15p	2N2194 27p	2N3056 63p	25032 45p
AC188 30p	ASV30 25p	BC175 22p	BF160 30p	BSY38 15p	OC72 12p	2G401 30p	2N2218 25p	2N3057 63p	25033 45p
AC189 30p	ASV31 25p	BC176 17p	BF161 30p	BSY39 15p	OC73 12p	2G414 30p	2N2219 27p	2N3058 63p	25034 75p
AC190 30p	ASV32 25p	BC177 17p	BF162 35p	BSY40 30p	OC74 12p	2G417 25p	2N2220 22p	2N3059 63p	25035 45p
AC191 23p	ASV33 25p	BC178 17p	BF163 35p	BSY41 35p	OC75 15p	2G417 25p	2N2221 22p	2N3060 63p	25036 45p
AC192 30p	ASV34 25p	BC179 17p	BF164 35p	BSY42 35p	OC76 15p	2N388 30p	2N2222 27p	2N3061 63p	25037 45p
AC193 30p	ASV35 25p	BC180 20p	BF165 35p	BSY43 35p	OC77 25p	2N388A 30p	2N2223 27p	2N3062 63p	25038 45p
AC194 30p	ASV36 25p	BC181 20p	BF166 35p	BSY44 35p	OC78 15p	2N404 22p	2N2268 17p	2N3063 63p	25039 45p
AC195 30p	ASV37 25p	BC182 10p	BF167 35p	BSY45 35p	OC81 15p	2N404A 30p	2N2269 15p	2N3064 63p	25040 45p
AC196 30p	ASV38 25p	BC183 10p	BF177 35p	C400 30p	OC82 15p	2N524 55p	2N2369 15p	2N3405 45p	25322A 50p
AC197 30p	ASV39 25p	BC184 10p	BF178 35p	C401 25p	OC83 15p	2N527 60p	2N2411 50p	2N3414 20p	25323 60p
AC198 30p	ASV40 25p	BC185 10p	BF179 35p	C402 25p	OC84 20p	2N697 15p	2N2415 50p	2N3415 20p	25324 60p
AC199 30p	ASV41 25p	BC186 10p	BF180 30p	C425 40p	OC85 20p	2N697 15p	2N2616 55p	2N3417 37p	25325 11p
AC200 30p	ASV42 25p	BC187 27p	BF181 30p	C426 30p	OC139 15p	2N698 24p	2N2711 22p	2N3525 74p	25326 11p
AC201 30p	ASV43 25p	BC188 27p	BF182 30p	C428 20p	OC140 17p	2N699 55p	2N2712 22p	2N3526 74p	25327 11p
AC202 30p	ASV44 25p	BC189 10p	BF183 30p	C441 27p	OC170 15p	2N706 7p	2N2714 25p	2N3703 12p	25328 11p
AC203 30p	ASV45 25p	BC190 10p	BF184 25p	C442 35p	OC171 15p	2N706A 8p			
AC204 30p	ASV46 25p	BC191 10p	BF185 30p	C444 30p	OC172 15p	2N708 12p			
AC205 30p	ASV47 25p	BC192 10p	BF186 30p	C450 17p	OC201 27p	IN709 45p	AA119 8p	BY130 15p	OA10 22p
AC206 30p	ASV48 25p	BC193 10p	BF187 30p	C451 17p	OC202 27p	IN711 40p	AA120 8p	BY130 15p	OA47 7p
AC207 30p	ASV49 25p	BC194 10p	BF188 30p	C452 17p	OC203 25p	2N171 42p	BA116 22p	BY211 32p	OA79 7p
AC208 30p	ASV50 25p	BC195 10p	BF189 30p	C453 17p	OC204 25p	2N172 42p	BA126 22p	BY212 32p	OA80 7p
AC209 30p	ASV51 25p	BC196 10p	BF190 30p	C454 17p	OC205 25p	2N173 42p	BY100 15p	BY213 25p	OA81 7p
AC210 30p	ASV52 25p	BC197 10p	BF191 24p	C722 25p	OC206 25p	2N174 42p	BY101 12p	BY216 35p	OA85 7p
AC211 30p	ASV53 25p	BC198 10p	BF192 30p	C742 17p	OC207 25p	2N175 42p	BY105 15p	BY217 35p	OA90 6p
AC212 30p	ASV54 25p	BC199 10p	BF193 30p	C744 17p	OC208 25p	2N176 42p	BY114 12p	BY218 30p	OA91 7p
AC213 30p	ASV55 25p	BC200 10p	BF194 23p	C745 17p	OC209 35p	2N177 42p	BY126 15p	BY219 35p	OA95 7p
AC214 30p	ASV56 25p	BC201 11p	BF195 24p	C760 17p	P346A 17p	2N727 27p	BY127 17p	OAS 17p	OA200 6p
AC215 30p	ASV57 25p	BC202 11p	BF196 30p	C762 17p	P397 45p	2N743 17p			
AC216 30p	ASV58 25p	BC203 11p	BF197 35p	C764 60p	OC71 43p	2N744 17p			
AC217 30p	ASV59 25p	BC204 11p	BF198 30p	EC401 15p	ORP12 43p	2N914 17p			
AC218 30p	ASV60 25p	BC205 11p	BF199 30p						
AC219 30p	ASV61 25p	BC206 11p	BF200 40p						
AC220 30p	ASV62 25p	BC207 11p	BF201 40p						
AC221 30p	ASV63 25p	BC208 11p	BF202 40p						
AC222 30p	ASV64 25p	BC209 11p	BF203 40p						
AC223 30p	ASV65 25p	BC210 11p	BF204 40p						
AC224 30p	ASV66 25p	BC211 11p	BF205 40p						
AC225 30p	ASV67 25p	BC212 11p	BF206 40p						
AC226 30p	ASV68 25p	BC213 11p	BF207 40p						
AC227 30p	ASV69 25p	BC214 11p	BF208 40p						
AC228 30p	ASV70 25p	BC215 11p	BF209 40p						
AC229 30p	ASV71 25p	BC216 11p	BF210 40p						
AC230 30p	ASV72 25p	BC217 11p	BF211 40p						
AC231 30p	ASV73 25p	BC218 11p	BF212 40p						
AC232 30p	ASV74 25p	BC219 11p	BF213 40p						
AC233 30p	ASV75 25p	BC220 11p	BF214 40p						
AC234 30p	ASV76 25p	BC221 11p	BF215 40p						
AC235 30p	ASV77 25p	BC222 11p	BF216 40p						
AC236 30p	ASV78 25p	BC223 11p	BF217 40p						
AC237 30p	ASV79 25p	BC224 11p	BF218 40p						
AC238 30p	ASV80 25p	BC225 11p	BF219 40p						
AC239 30p	ASV81 25p	BC226 11p	BF220 40p						
AC240 30p	ASV82 25p	BC227 11p	BF221 40p						
AC241 30p	ASV83 25p	BC228 11p	BF222 40p						
AC242 30p	ASV84 25p	BC229 11p	BF223 40p						
AC243 30p	ASV85 25p	BC230 11p	BF224 40p						
AC244 30p	ASV86 25p	BC231 11p	BF225 40p						
AC245 30p	ASV87 25p	BC232 11p	BF226 40p						
AC246 30p	ASV88 25p	BC233 11p	BF227 40p						
AC247 30p	ASV89 25p	BC234 11p	BF228 40p						
AC248 30p	ASV90 25p	BC235 11p	BF229 40p						
AC249 30p	ASV91 25p	BC236 11p	BF230 40p						
AC250 30p	ASV92 25p	BC237 11p	BF231 40p						
AC251 30p	ASV93 25p	BC238 11p	BF232 40p						
AC252 30p	ASV94 25p	BC239 11p	BF233 40p						
AC253 30p	ASV95 25p	BC240 11p	BF234 40p						
AC254 30p	ASV96 25p	BC241 11p	BF235 40p						
AC255 30p	ASV97 25p	BC242 11p	BF236 40p						
AC256 30p	ASV98 25p	BC243 11p	BF237 40p						
AC257 30p	ASV99 25p	BC244 11p	BF238 40p						
AC258 30p	ASV100 25p	BC245 11p	BF239 40p						
AC259 30p	ASV101 25p	BC246 11p	BF240 40p						
AC260 30p	ASV102 25p	BC247 11p	BF241 40p						
AC261 30p	ASV103 25p	BC248 11p	BF242 40p						
AC262 30p	ASV104 25p	BC249 11p	BF243 40p						
AC263 30p	ASV105 25p	BC250 11p	BF244 40p						

# LAWSON BRAND NEW TELEVISION TUBES



**SPECIFICATION:** The Lawson range of new television tubes are designed to give superb performance, coupled with maximum reliability and very long life. All tubes are the products of Britain's major C.R.T. manufacturers, and each tube is an exact replacement. Tubes are produced to the original specifications but incorporate the very latest design improvements such as: High Brightness Maximum Contrast Silver Activated Screens, Micro-Fine Aluminising, Precision Aligned Gun Jigging, together with Ultra Hard R.F. High Vacuum Techniques.

## DIRECT REPLACEMENTS FOR MULLARD-MAZDA BRIMAR GEC, ETC.

A21-11W (P)	AW47-91 (M)	C19/AK (M)	CME1902 (M)	173K (M)
A28-14W	MW43-64 (M)	C21/1A (M)	CME1903 (M)	212K (M)
A31-18W (P)	MW43-69 (M)	C21/7A (M)	CME1905	7205A (M)
A47-11W (P)	MW43-80 (M)	C21/AA (M)	CME1906	7405A (M)
A47-13W (T)	MW52/20 (M)	C21/AF (M)	CME1908	7406A (M)
A47-14W (M)	MW53/80 (M)	C21/KM (M)	CME2101	7502A (M)
A47-17W (P)	AW47-97 (M)	C21/SM (M)	CME2104 (M)	7503A (M)
A47-18W (P)	AW53-80 (M)	C23/7A (M)	CME2301 (M)	7504A (M)
A47-26W (P)	AW53-88 (M)	C23/10 (M)	CME2302 (M)	7601A (M)
A59-11W (P)	AW53-89 (M)	C23/AK (M)	CME2303 (M)	7701A (M)
A59-12W (P)	AW59-90 (M)	CME1101 (P)	CME2305 (P)	CRM121 (M)
A59-13W (T)	AW59-91 (M)	CME1201 (P)	CME2306 (T)	MW31-74 (M)
A59-14W (T)	C17/1A (M)	CME1402 (M)	CME2308 (M)	A50-120W/R (P)
A59-15W (M)	C17/5A (M)	CME1601 (P)	CRM172 (M)	
A59-14W (T)	C17/7A (M)	CME1602 (P)	CRM173 (M)	
AW36-80 (M)	C17/AA (M)	CME1702 (M)	CRM212 (M)	
AW43-80 (A)	C17/AF (M)	CME1703 (M)	CRM211 (M)	
AW43-88 (M)	C17/FM (M)	CME1705 (M)	23SP4 (M)	
AW43-89 (M)	C17/5M (M)	CME1706 (M)	171K (M)	
AW47190 (M)	C19/10AP (T)	CME1901 (M)	172K (M)	

## REBUILT TUBES

**LAWSON "RED LABEL" CRTS** are particularly useful where cost is a vital factor, such as in older sets or rental use. Lawson "Red Label" CRTS are completely rebuilt from selected glass, are direct replacements and guaranteed for two years.

	Brand New Tubes	Red Label Rebuilt	Carr. Ins.
CME 1601	£8-50	£4-25	12" - 19" } 62p
17"	£6-25	£4-87	
19"	£7-25	£5-25	
21"	£8-50	£6-87	
23"	£9-75	£7-25	20" - 23" } 75p
19" Twin Panel	£10-25		
23" Twin Panel	£15-50		
19" Panorama	£9-38		
20" Panorama	£9-50		
23" Panorama	£11-95		

**LAWSON TUBES**  
18 CHURCHDOWN ROAD,  
MALVERN, WORCS.  
Malvern 2100

## 2 YEARS' GUARANTEE FULL TUBE FITTING INSTRUCTIONS

Tubes are despatched passenger train, road or goods taking far too long for customer satisfaction.

## NEW RANGE U.H.F. - TV - AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.  
Loft Mounting Arrays: 7 element, £2-25; 11 element, £2-62; 14 element, £3-00; 18 element, £3-50. Wall Mounting with Cranked Arm: 7 element, £3-25; 11 element, £3-75; 14 element, £4-12; 18 element, £4-50. Chimney Mounting Arrays, Complete: 7 element, £4; 11 element, £4-37; 14 element, £4-75; 18 element, £5-25. Complete assembly instructions with every aerial. Low loss co-axial cable, 81p yd. King Teleboosters-Labgear U.H.F. Boosters from £3-75. Belling Lee 'Concord' all Band V.H.F./U.H.F. mains operated pre-amp., £7-50. State clearly channel number required on all orders. P.p.: Aerials, 40p; accessories, 15p. C.W.O. or C.O.D.

## BBC - ITV - FM AERIALS

BBC (Band 1): Loft, £1-25; wall S/D, £1-62; 'H' array, £3-00. ITV (Band 3): 5 element loft array, £2-25; 7 element, £2-75; wall mounting, 5 element, £3-25. Combined BBC/ITV: Loft 1+5, £2-75; 1+7, £3-37; wall mounting 1+5, £3-37; chimney mounting 1+5, £4-50. Pre-amps from £3-75. Combined BBC/ITV/BBC2 Aerials: 1+5+9, £4-00; 1+5+14, £4-50; 1+7+14, £5-00. Available loft only.

FM Radio: Loft S/D, 87p; 'H', £1-92; 3 element array, £2-87. Standard co-axial cable, 5p yd. Co-ax plugs, 81p. Outlet boxes, 50p. Diplexer crossover boxes, 87p. P.p.: Aerials, 40p; accessories, 15p; C.W.O. or C.O.D. (min. C.O.D. charge 17p). 5p for fully illustrated lists.

CALLERS WELCOMED.  
OPEN ALL DAY SATURDAY.

## K.V.A. ELECTRONICS (Dept. P.T.)

40-41 Monarch Parade

London Road, Mitcham, Surrey

01-648 4884

## Learn at home... First Class Radio and TV Courses



After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

### FREE GUIDE

Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.S.E. (Elec.). Guide also gives details of range of certificate courses in Radio/TV Servicing. Electronics and other branches of engineering, together with particulars of our remarkable terms of Satisfaction or refund of fee


Write now for your copy of this valuable publication. It may well prove to be the turning point in your career.

Founded 1885 Over 150,000 successes

## CHAMBERS COLLEGE

(Incorp. National Inst. of Engineering)  
(Dept. 844V) Aldermaston Court, Reading, RG7 4PF
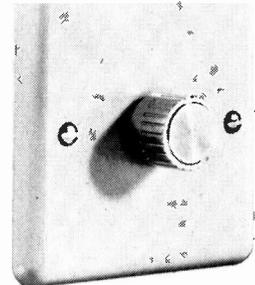
## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w. of all lights except fluorescents at mains voltages from 200-250v. 50Hz. The DIMMASWITCH has built-in radiator:

600—£3-20 Kit Form £2-70  
300—£2-70 Kit Form £2-20

All plus 10p. post and packing.  
Please send C.W.O. to:—

## DEXTER & COMPANY

3 ULVER HOUSE, 19 KING STREET,  
CHESTER CH1 2AH. Tel: 0244-25883

As supplied to H.M. Government Departments, Hospitals, Local Authorities, etc.

# WILLOW VALE ELECTRONICS LIMITED

The Service Department Wholesalers

Compare our prices

e.g. NEW 19" C.R.T's . . . OUR PRICE £7.95 Plus 65p carriage

Please note: Components are sold in packs, quantities per pack are shown under each heading. Prices are per piece of each value.

### TUBULAR CAPACITORS

(5's)			
-001	400v.	£0-04	
-0022	600v.	£0-04	
-0033	600/1500v.	£0-04	
-0047	600/1500v.	£0-04	
-01	400v.	£0-04	
-022	600v.	£0-05	
-033	600v.	£0-05	
-047	600v.	£0-05	
-1	600v.	£0-05	
-22	600v.	£0-10	
-47	600v.	£0-14	
-01	1000v.	£0-06	
-022	1000v.	£0-06	
-047	1000v.	£0-09	
-1	1000v.	£0-09	
-22	1000v.	£0-14	
-47	1000v.	£0-19	
-001	1500v.	£0-08	

### WIRE-WOUND RESISTORS

(5's)			
10 watt rating, suitable for mains dropper sections.			
1	Ohm	£0-09	
10	Ohms	£0-09	
13	"	£0-09	
25	"	£0-09	
33	"	£0-09	
50	"	£0-09	
87	"	£0-09	
100	"	£0-09	
150	"	£0-09	
220	"	£0-09	
330	"	£0-09	
1K	"	£0-09	
2.2K	"	£0-09	
3.3K	"	£0-09	
4.7K	"	£0-09	

### PULSE CERAMICS (5's) 12KV

100pf	22pf	£0-06
120pf	47pf	£0-06
180pf	68pf	£0-06
250pf		£0-06

Tubular type for use in Scan correction circuits and Line Outputs.

### CERAMICS (6's)

500pf	22pf	£0-03
680pf	47pf	£0-03
820pf	68pf	£0-03
1000pf	100pf	£0-03
1500pf	120pf	£0-03
3000pf	180pf	£0-03
5000pf		£0-03

### BIAS ELECTROLYTICS (5's)

25mfd	25v.	£0-07
50mfd	25v.	£0-08
100mfd	25v.	£0-10
250mfd	25v.	£0-15
500mfd	25v.	£0-19
1000mfd	12v.	£0-30
1000mfd	30v.	£0-30
2000mfd	25v.	£0-35
2500mfd	30v.	£0-45
3000mfd	30v.	£0-47
5000mfd	30v.	£0-55
25mfd	50v.	£0-08
50mfd	50v.	£0-10
100mfd	50v.	£0-13
250mfd	50v.	£0-18
500mfd	50v.	£0-24
2000mfd	50v.	£0-47
2500mfd	50v.	£0-55

### SMOOTHING ELECTROLYTICS

Wire ended, 450v. working.			
1mfd		£0-07	
2mfd		£0-08	
4mfd		£0-11	
8mfd		£0-13	
16mfd		£0-16	
32mfd		£0-23	
50mfd		£0-25	
8/8mfd		£0-19	
8/16mfd		£0-25	
16/16mfd		£0-26	
16/32mfd		£0-27	
32/32mfd		£0-27	
50/50mfd		£0-42	
50/50/50mfd		£0-52	

### CANNED ELECTROLYTICS

100/200mfd	£0-63
100/400mfd	£0-83
200/200mfd	£0-85
200/200/100mfd	£0-95
200/400/32mfd	£0-95
100/300/100/16	£0-95
100/400/32mfd	£0-95
100/400/64/16	£1-07

### SKELETON PRE-SETS (5's)

25K	Vertical	£0-07
50K	"	£0-07
100K	"	£0-07
250K	"	£0-07
500K	"	£0-07
1 meg	"	£0-07
2 meg	"	£0-07
500K	Horizontal	£0-07
680V	"	£0-07
1 meg	"	£0-07

### SUB-MINIATURE ELECTROLYTICS (5's)

1mfd	18v.	£0-09
2mfd	18v.	£0-09
4mfd	18v.	£0-09
5mfd	18v.	£0-09
8mfd	18v.	£0-09
10mfd	18v.	£0-09
16mfd	18v.	£0-09
25mfd	18v.	£0-09
32mfd	18v.	£0-09
50mfd	18v.	£0-09
100mfd	18v.	£0-09
200mfd	18v.	£0-09

### THERMISTORS (5's)

Miniature	£0-08
THI	£0-13

### RECTIFIERS

Silicon Mains (5's)	
Westinghouse S10AR2	£0-33
BY127 Mullard	£0-26
BY327	£0-25

### CONTACT COOLED FULL WAVE

75ma	£0-60
100ma	£0-70
150ma	£0-86

### CO-AXIAL PLUGS

Bakelite top	£0-04
Egen metal	£0-08
Single point (car radio)	£0-10

### SLIDER PRE-SETS (3's)

100K	£0-08
1 Meg	£0-08
2.2 Meg	£0-08

### JACK PLUGS

Chrome standard	£0-20
Standard	£0-15
3.5mm. metal	£0-15

### DIN PLUGS (2's)

3-pin	£0-10
5-pin	£0-11
Sockets	£0-06

### DOUBLE DIODE RECTIFIERS

(5's)	
Bush/Murphy/BRC, etc.	
Line/frame timebases etc.	
3 leg	£0-31
4 leg	£0-31
5 leg	£0-31

### RADIO/TV GLASS FUSES

1 amp, 1.5 amp, 2 amp, 3 amp.	
Per dozen	£0-15

### MAINS FUSES

2 amp, 3 amp, 5 amp, 13 amp.	
Per dozen	£0-25

### TERMINAL STRIPS

2 amp	£0-12
5 amp.	£0-14
15 amp	£0-29

### CARBON FILM RESISTORS

½ watt, 1 watt and 2 watt. The following values are packed in cartons of six of each value.

ohm		
10	1.2K	150K
12	1.5K	180K
15	1.8K	220K
18	2.2K	270K
22	2.7K	330K
27	3.3K	390K
33	3.9K	430K
39	4.3K	470K
43	4.7K	560K
47	5.6K	680K
56	6.8K	820K
68	8.2K	1M
82	10K	1.2M
100	12K	1.5M
120	15K	1.8M
150	18K	2.2M
180	22K	2.7M
220	27K	3.3M
270	33K	3.9M
330	39K	4.3M
390	43K	4.7M
430	47K	5.6M
470	56K	6.8M
560	68K	8.2M
680	82K	10M
820	100K	12M
1K	120K	15M

All the above values are available in both ½ watt, 1 watt and 2 watt versions. \*Special for Philips TV's: 8.2M 2-watt, 23p per pack. Price ½ watt -10, 1 watt -13, 2 watt -23

### VOLUME CONTROLS

Standard spindle with flat.	
Double pole switch	£0-25
Without switch	£0-19
(One per pack)	
5K, 10K, 25K, 50K, 100K, 250K, 500K.	
1 meg, 2 meg.	

MOBILE STORES VANS IN LONDON, WEST COUNTRY, WALES AND SCOTLAND

### RECORD PLAYER CARTRIDGES

ACOS: GP67/2g.	High gain general purpose Mono	£0-83
GP91/3C.	Stereo-compatible replacement	£1-10
GP91/3SC.	High gain version of above	£1-10
GP94/1SS.	Stereo cartridge	£1-89

GENERAL PURPOSE REPLACEMENT FOR TC8's etc. High gain, plenty of output (Jap.) Stereo version

### SERVISOL AND ELECTROLUBE PRODUCTS (Nett trade)

Servisol aerosol can	£0-63 nett
Electrolube 2AX aerosol	£0-70 nett
Servisol Freezit	£0-47 nett
Electrolube No. 1 Snorkel	£0-90 nett
Electrolube 2GX Grease	£0-42 nett
Servisol Aero-Clene for tape heads	£0-53 nett
Servisol Aero-Duster	£0-53 nett

### REPLACEMENT STYLII

TC8	£0-23
GCB	£0-23



# “NO



## I'D RATHER HAVE A MINITEST™

The SEI MINITEST has made a remarkable impact in the pocket-sized multi-range meter market, by making itself a firm favourite with discerning people in the industry. Let's look into the reasons why.

First, the appearance. Diminutive, neat, wipe-clean cyclac case with shock and magnetic field proof steel liner. Controls are simple and easy to use.


Second, the range. The Minitest measures a.c. and d.c. voltages d.c. current and resistance over 20 ranges to a sensitivity of 20,000 and 2,000 ohms per volt d.c. and a.c. respectively.

Third, high voltage probes. These extend the range to 25 or 30kV d.c. Little wonder the Minitest is preferred!

**SALFORD ELECTRICAL INSTRUMENTS LTD**  
 Peel Works, Barton Lane, Eccles, Manchester M30 0HL  
 Telephone 061-789 5081 Telex 667711  
 A Member Company of GEC Electrical Components Ltd.



## REBUILT TUBES!

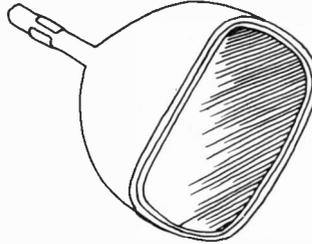

**YOU'RE SAFE WHEN YOU BUY FROM RE-VIEW!**

### HERE IS WHAT YOU PAY:

12in.	..	..	£4-75	19in.	..	..	£5-87
14in.	..	..	£5-00	21in.	..	..	£7-25
15in.	..	..	£5-25	23in.	..	..	£8-50
17in.	..	..	£5-25	19in. Twin Panel	..	..	£7-50
23in. Twin Panel £10							

Cash or cheque with order, or cash on delivery

### COLOUR TUBES AVAILABLE

#### Discount for Trade

- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for two years against all but breakage.
- ★ Each tube is delivered free anywhere in the U.K. and insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

**RE-VIEW ELECTRONIC TUBES**  
 237 London Road, West Cropton, Surrey  
 Tel. 01-689/7735

## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1R5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94  
 Set of 4 for £1.02. DAF96, DF96, DK96, DL96, 4 for £1.48.

1R5	-28	25U4GT	-57	DY86	-26	EL500	-62	PCL82	-36	UABC80	-33
1R5	-22	30C1	-30	DY87	-26	EM50	-41	PCL83	-60	UAF42	-51
1T4	-16	30C15	-63	DY802	-40	EM81	-41	PCL84	-37	UBC41	-52
3B4	-28	30C17	-80	EABC80	-32	EM84	-33	PCL85	-45	UBF80	-34
3V4	-37	30C18	-67	EAF42	-50	EM87	-37	PCL86	-41	UBF89	-33
5U4G	-26	30F5	-76	EB41	-40	EY51	-32	PCL88	-72	UCC84	-35
5V4G	-37	30FL1	-63	EB91	-11	EY86	-32	PCL800	-77	UCC85	-36
5Y3GT	-30	30FL12	-72	EBC33	-40	EZ40	-43	PENA4	-42	UCF80	-36
5Z4G	-37	30FL14	-72	EBC41	-54	EZ41	-43	PEN36C	-70	UCH42	-62
6/30L2	-58	30L1	-32	EBC90	-22	EZ80	-23	PFL200	-63	UCH81	-32
6AL5	-11	30L15	-62	EBP80	-32	EZ61	-24	FL36	-49	UCL82	-35
6AM6	-13	30L17	-73	EBP89	-31	GZ30	-37	PL81	-48	UCL83	-55
6AQ5	-26	30P4	-65	ECC81	-18	GZ32	-43	PL81A	-51	UF41	-56
6AT6	-22	30P12	-77	ECC82	-20	GZ34	-50	PL82	-33	UR89	-33
6AU6	-22	30P10	-65	ECC83	-35	KT41	-77	PL83	-35	UL41	-60
6BA6	-22	30P11	-63	ECC85	-28	KT61	-55	PL84	-32	UL44	£1-00
6BE6	-23	30PL13	-75	ECC804	-60	KT66	-81	PL500	-84	UL84	-35
6BJ6	-42	30PL14	-70	ECP80	-30	LN319	-63	PL504	-64	UM84	-22
6BW7	-55	30PL15	-90	ECP82	-30	LN329	-72	PM84	-37	UY41	-41
6CD6G£1-10		35L8GT	-45	ECH35	-30	LN339	-63	PX25	£1-17	UY85	-28
6F14	-45	35W4	-28	ECH42	-63	N78	-87	PY32	-56	VP4B	-77
6F23	-71	35Z4GT	-25	ECH81	-29	P61	-50	PY33	-55	Z77	-25
6F25	-62	80T	-43	ECH83	-41	PABC80	-35	PY81	-27	Transistors	
6K7G	-12	6063	-62	ECH84	-37	PC86	-51	PY82	-27	AC107	-17
6KR6	-17	AC/VP2	-77	ECL80	-32	PC88	-51	PY83	-28	AC127	-18
6Q7G	-28	B349	-65	ECL82	-33	PC96	-42	PY88	-35	AD140	-37
6RN7GT	-30	B729	-62	ECL86	-36	PC97	-40	PY800	-37	AP115	-20
6V6G	-23	6CH35	-67	EPF39	-35	PC990	-37	PY801	-37	AP116	-20
6V6GT	-32	CV31	-33	EP41	-60	PC884	-30	R19	-32	AP117	-20
6X4	-23	DAF91	-22	EP80	-24	PC885	-30	R20	-65	AP118	-48
6X6GT	-28	DAF96	-36	EP85	-31	PC888	-45	U25	-68	AP125	-17
7B7	-38	DF53	-38	EP86	-81	PC889	-47	U26	-65	AP127	-17
10P13	-60	DF91	-16	EP89	-27	PCC189	-51	U47	-68	OC26	-25
13A8A£2-25		DF96	-36	EP91	-13	PC8605	-65	U49	-65	OC44	-12
13A8T	-13	DH77	-22	EP183	-24	PCF80	-29	U501	-39	OC45	-12
12AU6	-23	DK32	-37	EP184	-32	PCF82	-32	U52	-31	OC71	-12
12AU7	-23	DK91	-28	EH90	-42	PCF86	-47	U78	-24	OC72	-12
12AX7	-23	DK92	-42	EL33	-55	PCF800	-67	U191	-62	OC75	-12
19B6G6	-87	DK96	-38	EL34	-49	PCF801	-33	U193	-42	OC81	-12
20P2	-87	DL35	-35	EL41	-55	PCF802	-45	U251	-72	OC81D	-12
20P3	-85	DL92	-23	EL43	-24	PCF803	-67	U301	-39	OC82	-12
20P4	-92	DL94	-37	EL90	-26	PCF806	-60	U329	-72	OC82D	-12
26L8GT	-25	DL96	-38	EL95	-33	PCF808	-72	U801	-98	OC170	-22

**READERS RADIO**  
 85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX.  
 Tel. 01-550 7441

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra.  
 Any Parcel Insured against Damage in Transit 3p extra.

# TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

VOL 21 No 11  
ISSUE 251

SEPTEMBER 1971

## NO HOLDS BARRED!

The trade battle for the colour television receiver market is now really hotting up. The latest manufacturers' home delivery figures from BREMA are impressive, showing a continued acceleration. During the first five months of this year 231,000 colour receivers were delivered to the trade, representing a rise of 52% over the same period in 1970 (152,000 receivers). Deliveries of monochrome sets continue to fall—now at around the 13% level. So people are decidedly beginning to switch to colour.

Manufacturers are also now making a strong effort to fight off the threat from imported products. Examples of this awakening are the new BRC 8000 series 17in. model at a recommended retail price of only £189.75 (less than anything comparable from overseas) and the new low prices of the GEC 19in. range. These and other moves are encouraging signs but it would be foolish for the industry to indulge in premature euphoria. RBM for instance have introduced a new monochrome portable (the TV300) which is being built in Japan, presumably working on the principle of "if you can't beat 'em, join 'em". And coming fast on the news of the BRC 8000 colour chassis with its advanced solid-state design with 41 transistors, 3 i.c.s and other features, and bearing in mind the Philips 520 with its 5 i.c.s, we learn that Toshiba have developed a 20in. colour receiver in which 75% of the circuitry has been accommodated in no less than 15 i.c.s. The secret of this design is said to be a technique which makes it possible to manufacture i.c.s with superior linear operating characteristics and low noise figures.

At the moment the situation is developing into a gigantic game of leapfrog or industrial one-upmanship. Competition is a stimulus of course and keeps manufacturers on their toes but the vicious atmosphere which is becoming part and parcel of modern commercial life can react against the interests of the consumer by way of shoddy products—as it can be seen to have done in many industries already.

Let us hope therefore that the colour TV battle, which is now joined, will not result in a lowering of the high standards to which we have become accustomed.

W. N. STEVENS, *Editor*


## THIS MONTH

Teletopics	486
ICs for Television—Part 1 Intercarrier Sound ICs	<i>by K. T. Wilson</i> 488
TV Test Report	<i>by E. M. Bristol</i> 491
Basic Circuits for the Constructor—Part 3 Transistor Video and Sync Separator Circuits	<i>by J. W. Thompson</i> 492
Super 8 and Super 16—Developments in Films for TV	<i>by Baynham Honri</i> 496
Workshop Hints	<i>by Vivian Capel</i> 498
The Rainbow Revolution—Part 3	<i>by I. R. Sinclair</i> 500
Servicing Television Receivers—Sobell ST282 series	<i>by L. Lawry-Johns</i> 503
Colour Receiver Circuits—Primary-Colour Tube Drive Circuits cont.	<i>by Gordon J. King</i> 506
Service Notebook	<i>by G. R. Wilding</i> 510
Long-Distance Television	<i>by Roger Bunney</i> 515
A Look at Imported Sets—The Crown 7TV105 Mains-Battery Portable	<i>by H. K. Hills</i> 518
Your Problems Solved	521
Test Case 105	523

**THE NEXT ISSUE DATED OCTOBER  
WILL BE PUBLISHED SEPTEMBER 22**


**Cover:** Grateful acknowledgements this month to Mullard Ltd. who provided us with the TV i.c.s shown in our cover photograph.

# TELETOPICS

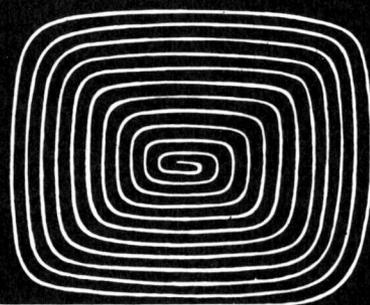
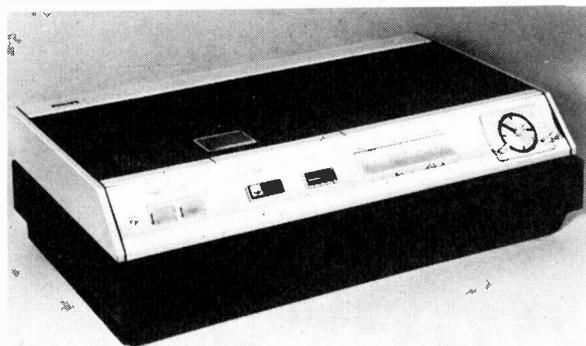
## FIRST VIDEOCASSETTE RECORDER

Philips have announced preliminary details of their videocassette recorder Model N1500 which is due for release towards the end of this year with full-scale production starting next year. The recorder contains a built-in tuner unit so that recording can be done automatically on plugging in an aerial. In this way the viewer can record and watch his ordinary TV set at the same time. The recorder contains a u.h.f. modulator to enable its output to be played back via the aerial socket of an ordinary TV set. Fully



*The Philips N1500 videocassette recorder.*

compatible recordings can be made in colour or monochrome and the UK version will be to the PAL standard. There is no reduction in playing time for colour. The whole unit will cost around £280 with 60-minute blank cassettes costing about £12 each.

## DIFFICULT UHF RECEPTION

Writing in *Electrical and Electronic Trader* recently B. Sykes, Group Chairman, J Beam Aerials Ltd., comments on u.h.f. reception problems in what he calls "diffused-signal areas". These are poor-signal areas where the symptom is found that no improvement can be obtained with a high-gain Yagi in comparison to a much smaller type of aerial. The geographical situation is that a hill obscures the direct signal path from the transmitter, the only signal available consisting of reflected and diffracted signals arriving from different directions and in different phases. The basic conundrum is that because of the diffuse nature of the signal, increased aerial gain cannot be obtained by using a narrow-beamwidth aerial, i.e. as already noted a high-gain Yagi does not improve matters. A solution however is to reduce the vertical aerial beamwidth while leaving the horizontal beamwidth wide. This can be done by using two

aerials stacked vertically: when two identical aerials are stacked vertically the horizontal beamwidth is unaltered but the vertical beamwidth is halved and the gain doubled. The J Beam Multibeam aerial of course uses a configuration of vertically stacked director elements and is suggested as a help in such situations. B. Sykes continues: "As much as a three-to-one variation in signals between channels using a single, flat Yagi, with one or more channels completely useless, becomes almost identical signal strength on each channel when the Multibeam is used. Further gain can be obtained by stacking two Multibeams vertically but any attempt at horizontal stacking with the consequent reduction in horizontal beamwidth produces no improvement in gain whatsoever."

## ADVANCES IN ICs FOR TV

Plessey Microelectronics have announced that they have succeeded in squeezing the entire chroma signal processing circuitry for a PAL colour receiver into just two i.c.s.—most other firms active in this field use some five i.c.s. to perform the same functions. The two i.c.s are now in full-scale production at Plessey's Swindon plant and we understand that the initial production will be used in Rank-Bush-Murphy sets for which they were custom designed (Plessey and RBM have been working together in this field for some time with Plessey producing the i.c.s used in RBM colour sets).

Meanwhile Toshiba in Japan has announced the development of a 20in. colour set in which 75 per cent of the circuitry is incorporated in 15 integrated circuits. The new set, the IC1, also uses 17 ordinary transistors and 49 diodes. Toshiba claim that their advances in crystal device technology have enabled them to achieve this degree of integration in a TV set.

## BELGIAN TV CONDITIONS

We have received an interesting letter from a reader in Belgium who describes the very different television conditions there. He comments that DX-TV is part of the normal way of life because of the possibility of receiving extra programmes from foreign transmitters at "ultra-fringe" distances—facilitated by the relatively flat terrain and the use of common languages. The normal sets on the market are designed to operate on the French 819- and 625-line standards, the Belgian v.h.f. 625-line standard, Luxembourg 819 lines and the v.h.f. and u.h.f. 625-line standards adopted in the rest of continental West Europe, with standards switching sometimes incorporated in the channel selector, sometimes semi-automatic and in other sets by means of independent pushbuttons (so we thought *dual-standard* sets rather a complication!).

In Brussels the most popular foreign programme is ORTF-1 from Lille on ch. F8A. ORTF-2 from the same site can also be received but being on a higher channel, ch. 21, satisfactory reception—at 127km.—is more difficult. Dutch speakers can watch NOS-1 and -2 from Goes on chs. 29 and 32 at about 75km. though some are equipped to receive NOS-1 on ch. 4 from Lopik at 133km. On the higher ground in the eastern suburbs of Brussels Band IV aerials can be seen directed towards Aachen WDR-1 ch. 24 (125km.) or Monschau ZDF (ch. 21, cochannel with ORTF-2) while in other parts of Belgium other distant transmitters are used depending on linguistic interest and propagation characteristics. In Flanders rotatable aerial rigs are popular, generally carrying Band III and IV/V horizontal Yagis. Dover is received by some coastal viewers despite the low e.r.p. of this station, the offshore direction of transmission and the need for 6MHz intercarrier sound adaptors—which are available commercially to enable Belgian sets to get the UK sound signal.

There are in Brussels several municipal and private cable distribution systems which offer up to ten different programme services (ORTF-1 and -2, RTB/BRT, NOS-1 and -2, ARD-1 and -3, ZDF and Luxembourg) either on the original standards (but different channels) or remodulated to facilitate distribution and reception. Our correspondent uses a system that converts all signals to the CCIR standard B with PAL colour: Luxembourg is brought in via a microwave relay link but all the other signals are received off-air by aerials mounted on the roofs of tall buildings. Similar systems exist or are being built in other major towns and cities.

## TRADE NOTES

The latest BREMA figures for TV set deliveries—for May—show the continuing rise in colour set production and corresponding now marked fall off in monochrome set deliveries. Colour set deliveries for the month at 41,000 were up by over 17% compared to the same month last year while monochrome set deliveries at 91,000 fell by over 33%.

As mentioned in our Show notes last month ITT have reintroduced the **RGD** brand: so far there are two monochrome models, the RV237 a 20in. single-standard set at £74 and a 24in. version, Model RV337, at £82.50. These sets are fitted with the ITT VC200 chassis. **Dynatron** have a remote control unit for use with their colour Models CTV9 and CTV11: we understand that this is the first time in the UK that remote control has been applied to models fitted with varicap tuners. Two **Nivico** models have been introduced by Denham and Morley (Overseas) Ltd., a spherical, rotatable 9in. mains-battery model, the Videoglobe, with visor to conceal the screen when the set is not in use, at £69.45, and a 14in. mains-battery portable model at £77.

Next year's Radio and TV Trade Shows will again be held during the spring in London, from May 21st to May 25th.

## ITA's DIGITAL STANDARDS CONVERTER

The ITA's experimental digital line-store standards converter (see *Teletopics*, June 1971) was demonstrated at a recent Royal Television Society meeting. To enable the converter to interpolate over a range of four lines three line stores are used in the inter-

polator, each store having a capacity of 770 8-bit "words"—sufficient to store one line of video information sampled at three times the colour subcarrier frequency, i.e. 13.3MHz. The converter has been assembled from a number of basic component modules which were designed initially for the computerised monitoring equipment which forms part of the ITA's automation programme. These modules however are equally suitable for use in colour synchronisers and *field-rate* converters. The work being carried out by the ITA on conversion is the subject of several patent applications.

## SOLID-STATE IMAGE CONVERTER

A solid-state device for converting optical images directly to a sequential digital output has been developed by Optonetics Inc., of Teterboro, New Jersey. The optical image is focused on to a photosensitive layer of semiconductor material. This is backed by a crossgrid of thin electrical conductors each intersection of which is addressed in turn to obtain a signal corresponding to the image brightness at that point. Using electronic circuitry to scan the entire crossgrid matrix in this way an optical image can be converted into 90,000 to 360,000 points per square inch. The crossgrid of conductors is part of a multilayer sandwich with electroluminescent phosphor laminated to the back of the photosensitive semiconductor layer. Whilst this has been developed with applications such as computer use and character recognition in mind it nevertheless shows up the possibilities that may some day lead to a radically different form of picture display device in TV.


## NEW LIGHT-EMITTING MATERIAL

A new company has been set up in the UK to develop what it claims to be an important advance in the field of light-emitting semiconductor material for solid-state displays. The generation of devices about to enter the stage of large-scale production are based on gallium arsenide phosphates but the new company claims advantages in using a new material for this purpose, zinc selenide, which has an attractive band gap for light emission. New processing techniques to obtain pure zinc selenide have been developed and with the evaporation of a thin translucent layer of gold on the zinc selenide chip a light-emitting Shottky diode is obtained. The efficiency of the new material in terms of lumens per watt is apparently already comparable with the best gallium arsenide phosphide lamps while the driving voltages are i.c. compatible at 15V.
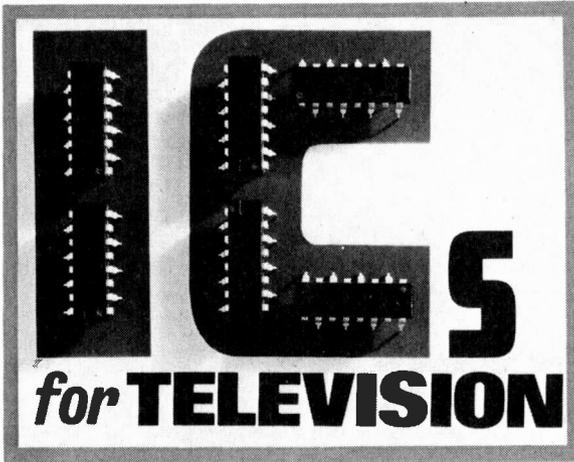
## TRANSMITTER NEWS

ITA transmissions on u.h.f. from **Durriss**, Kincardineshire carrying Grampian Television programmes in black-and-white have now started. The full colour service is to start on September 30th. The channel is 25, polarisation horizontal and a Group A receiving aerial is required.

The BBC has announced the start of engineering tests for the BBC-1 service from the **Sheffield** relay station on channel 31 (receiving aerial Group A, vertically polarised) and for the BBC-2 service from the **Wharfedale** relay station on channel 28 (receiving aerial Group A, vertically polarised).



## PART I

K. T. WILSON

## INTERCARRIER SOUND I.C.s

Hardly have we got used to all-transistor colour receiver chassis than we find the first designs incorporating integrated circuits being introduced. This is a trend which is certain to continue in colour sets since so many of the stages are low-level pulse circuits which are readily adaptable to the use of i.c.s; the trend is also showing in monochrome receivers as the volume of production of i.c.s increases and the range of functions they can carry out also increases. In this series of articles we shall examine some of the i.c.s now available or shortly to be available for use in TV sets, how they are employed and the receiver circuitry used around them.

One of the first i.c.s to be widely used in TV sets was the Mullard TAA570 which is encapsulated in a 10-lead TO-74 casing. It is used in the Pye 169 single-standard monochrome chassis, the GEC-Sobell 2047-1047 series of monochrome sets and the Philips G8 single-standard colour chassis to carry out the operations of intercarrier sound i.f. amplification, limiting, demodulation and preamplification of the audio signal. The output of this i.c. can be fed directly to an audio output stage which requires an input for maximum delivered power of around 0.5V. Mullard suggest a Class A single-ended push-pull circuit using a BC158 and two BD131 transistors but it can also be used to drive a triode-pentode such as the PCL86.

## The Circuit

The internal circuit of this complex i.c. will not be reproduced here and in any case would not be useful to the service engineer since only a few points in the circuit are accessible at the external pins. Because active stages are as easy or easier to form in i.c.s than passive components, the "circuit design" of an i.c. tends to be more complex than that of the transistor circuits which it replaces. Another factor is that cross-couplings and distributed resistance and capacitance exist which cannot be represented in a conventional circuit diagram. For these reasons we shall show the block diagrams of most of the i.c.s to be covered rather than the detailed internal circuitry.

The block diagram of the TAA570 is shown in Fig.

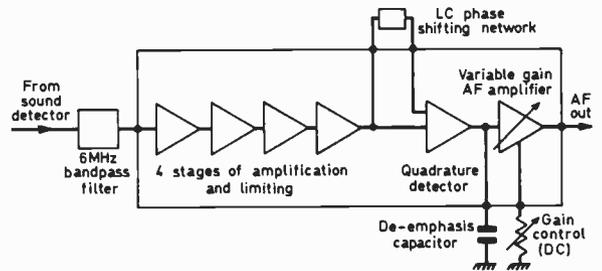


Fig. 1: Block diagram of the TAA570 intercarrier sound i.f. amplifier, limiter and detector i.c. There are 32 transistors and seven diodes in this i.c.

I along with the associated external components it requires. The separated intercarrier sound signal at a centre frequency of 6MHz is fed to the input which presents an impedance approximating  $4k\Omega$  in parallel with 13pF. The first four stages provide amplification and limiting of the 6MHz signal, using long-tailed pair balanced amplifiers. The signal then takes two routes, one directly to a quadrature detector and the other via an external  $90^\circ$  phase-shift network whose output is then fed into the other input of the quadrature phase detector. The a.f. signal from the detector is de-emphasised by an externally-connected capacitor and passes to an audio preamplifier.

The gain of the preamplifier can be controlled by applying a steady voltage to this section of the i.c. (at pin 4). Alternatively audio gain can be controlled in the normal way by a potentiometer in the signal path at the output of the i.c. D.C. control of gain is particularly useful if remote control is desired, and a minimum control range of 60dB is quoted. The output resistance of the final stage is around  $5.6k\Omega$ .

## Quadrature Detection

As the principle of quadrature detection of an f.m. signal is not as well known as that of the commonly used ratio detector a few notes on this will be given. The most important point about a quadrature detector

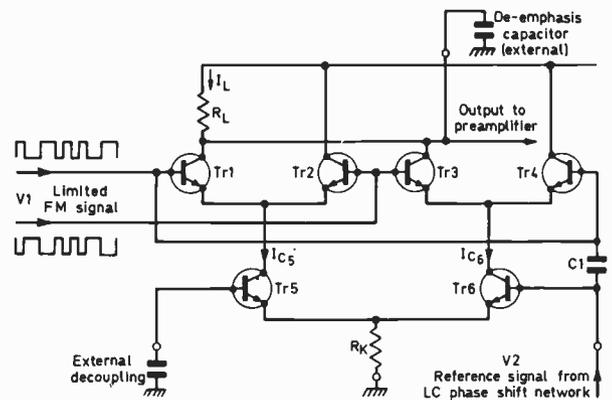


Fig. 2: The quadrature detector circuit. The external LC phase-shift network is driven by the signal fed to it via C1. The sine-wave signal from the phase-shift network drives Tr6 base and by emitter-follower action appears across its emitter resistor  $R_k$ . Thus Tr6 is driven at its base and Tr5 is driven at its emitter by the same basic waveform. This of course amounts to paraphase drive and Tr5 and Tr6 provide antiphase squarewave outputs.

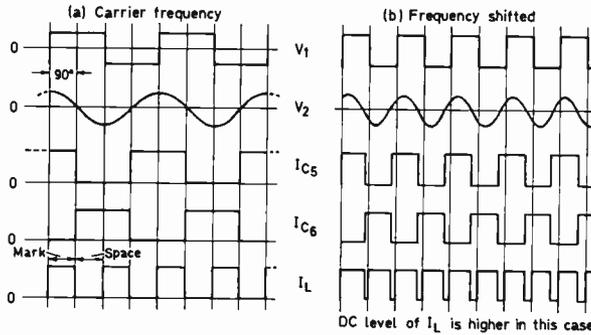


Fig. 3: Quadrature detector waveforms.

is that it uses no inductors in the signal path: this alone makes it desirable for use in an i.c. since the use of a ratio detector circuit would entail having a pin on the i.c. for each transformer connection. In addition this circuit has excellent a.m. rejection and is very easy to set up, the only adjustment necessary being to the phase-shift network which is simply tweaked until the a.f. output is a maximum (with input signal adequate to produce the limiting action).

Figure 2 shows the quadrature detector circuit used in the i.c. Tr1 and Tr2, Tr3 and Tr4, Tr5 and Tr6 are long-tailed pairs. The upper set Tr1-Tr4 is fed with the limited (i.e. clipped or squared) f.m. signal in paraphase and the lower pair with a reference sinewave signal—again in paraphase—whose phase is 90° different from the phase of the f.m. carrier. This reference signal is obtained from the external LC phase-shift network. Thus the inputs to Tr1, Tr2 and Tr3, Tr4 are antiphase squarewaves which are frequency modulated while the inputs to Tr5 and Tr6 are antiphase sinewaves which are *phase modulated* since the 90° phase-shifting circuit smooths out the squarewave carrier fed to it and shifts its phase as the frequency varies.

Figure 3 shows the waveforms at different signal frequency conditions. At (a) there is an exact 90° phase shift between V1 (the squarewave signal from the limiter section) and V2 (the 90° shifted sinewave). At (b) the frequency has shifted slightly (increased).

Taking the collector currents in Tr5 and Tr6 as  $I_{C5}$  and  $I_{C6}$  respectively we can see that these currents flow only when the voltage waveform V2 switches these transistors on; and since V2 is applied in paraphase the output currents  $I_{C5}$  and  $I_{C6}$  flow alternately. The signal voltage V1 is fed in paraphase to the upper pairs Tr1, Tr2 and Tr3, Tr4 so that  $I_{C5}$  flows alternately via Tr1 and Tr2 and  $I_{C6}$  flows alternately via Tr3 and Tr4. We can construct a table (Fig. 4) showing under what conditions current will flow in the load  $R_L$  which is common to the collectors of Tr1 and Tr3 and we can thus predict the current  $I_L$  in the load.

Now examine the case—Fig. 3(b)—where V2 has been slightly phase shifted as well as changed in frequency. Following the same procedure we can see that the frequency of the output signal has changed, and its mark-space ratio has also changed. We have thus produced a rectified signal consisting of a series

V1	V2	$I_{C5}$	$I_{C6}$	$I_L$
+	+	ON	ON	ON
+	-	OFF	OFF	OFF
-	-	OFF	ON	ON
-	+	ON	OFF	OFF

Fig. 4: Voltage and current conditions in the quadrature detector circuit.

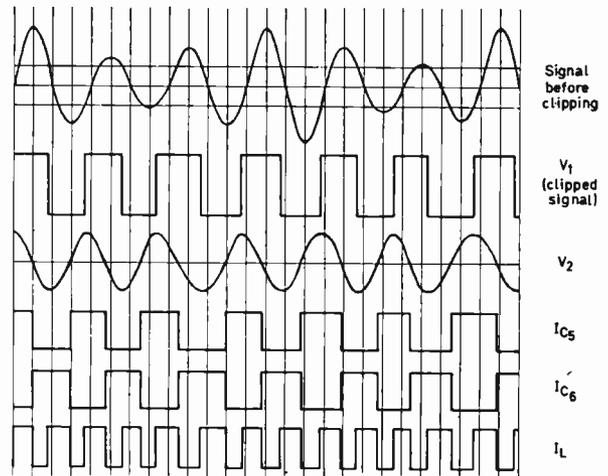


Fig. 5: The effect of amplitude modulation: although  $I_L$  consists of pulses of differing widths, the spaces alter in proportion so that a constant d.c. level is preserved. In this way a.m. produces no output.

of pulses whose frequency and mark-space ratio vary as the original signal varies in frequency. The load resistor  $R_L$  forms with the de-emphasis capacitor an integrating circuit which adds the pulses, providing an output signal which varies in amplitude as the signal frequency changes, which is what is wanted.

### A.M. Suppression

The effect of a.m. in the signal is shown in Fig. 5. When a signal which has become amplitude modulated (because of interference or rapid fading) is clipped the output from the limiter is a squarewave which varies in width at the frequency of modulation. Following the waveforms in Fig. 5 we can see that the width modulation of V1 merely shifts the pulses in the output load to-and-fro without affecting the mark-space ratio over a number of cycles so that good a.m. rejection is achieved.

Another incidental advantage of this form of quadrature detection is that the waveform which is finally rectified is at double the intercarrier frequency, i.e. 12MHz. This is of particular importance in an i.c. in which it may be difficult to prevent feedback from one stage to an earlier one, since it means that feedback will be at a harmonic, which causes much less chance of instability.

The performance of this detector circuit is impressive and is a clear example of the advantages of using i.c.s. With discrete components it would hardly be economic to use a detector circuit which required six transistors and an LC circuit in addition to the complications of paraphase drive!

### D.C. Gain Control

Internal a.f. gain control is achieved by another long-tailed pair in a circuit whose principle is shown in Fig. 6. The input signal is fed to the base of Tr3 which drives the emitters of Tr1 and Tr2. The collector current of Tr3 thus flows through Tr1 and Tr2 and by varying the bias on the bases of these two transistors the proportion of Tr3's collector current passing through each can be adjusted. At low Tr2 base bias very little signal current will pass through Tr2 and



# TV TEST REPORT

E. M. BRISTOL

## THE WELLER AUTO-HEAT SOLDERING IRON

AN almost bewildering array of soldering irons of various shapes and sizes is now available. Few of these have the facility of thermostatic control yet this is a most desirable feature for workshop use where soldering irons must be ready for instant use and so are usually left on all day.

An iron that does possess this facility is the Weller TCPI which has a number of novel features. Heat control is by means of a thermal-magnetic element associated with the actual soldering bit thus ensuring that it is always at the correct temperature. The principle of operation relies upon the fact that iron ceases to have any magnetic attraction when its temperature is raised above a certain level known as its Curie point.

### *Principle of Operation*

The bit is made of copper (for maximum heat transfer), iron-plated and aluminised for long life and easy tinning, and incorporates a small iron disc at its base. This is inserted along with the shank of the bit into the barrel of the iron. Next to this disc in the barrel is a bar magnet which is connected by a rod to a switch in the handle. This rod passes through a magnetic tube at the end of the magnet farthest from the bit. There is thus a form of tug-of-war for the magnet between the end of the tube and the disc next to the bit.

When the iron is cold the magnet is attracted to the disc and the rod closes the contacts of the spring-loaded switch. On attaining the desired temperature the disc reaches its Curie point and there is no further attraction for the magnet which is then attracted to the end of the tube. Assisted by the spring action of the switch, it moves down the barrel and the rod opens the switch contacts. On cooling to just below the Curie point the iron disc resumes its attraction and the magnet moves back to close the switch contacts again.

The iron discs can be made with various Curie points enabling interchangeable bits to be made for specific temperatures. In fact Weller have had four different temperature bits available, for 500, 600, 700 and 800 degrees, but I understand that the demand for the 500 degree bit is small so that it is being dropped. Any of these bits can be used with the basic

iron and changed at will to give the desired operating temperature.

### *Range*

The range of bits is extensive as they are available in numerous widths, shapes and lengths. There are five different widths from 1/32 to 3/16in. and 10 different types in each temperature rating. Long life is claimed for the bits and the iron cladding is partly responsible for this. Solder has a natural affinity for copper and absorbs minute amounts from an ordinary copper bit resulting after a while in the familiar cavities. The iron cladding is not subject to this effect. Also as the correct temperature is maintained the scaling which is common with ordinary irons is prevented. It should however be mentioned that while these bits are undoubtedly longer-lasting than ordinary copper ones continual workshop use takes its toll and replacements are not infrequent—which can be rather expensive at 50p a time.

The bit should not be filed or cleaned with any abrasive material. A damp rag or the damp sponge which is part of the transformer/stand is all that is needed. Bits are easily removed by unscrewing a ring at the base of the barrel and sliding off the outer casing liberating the bit at the same time. When refitting the ring must be screwed only finger-tight. It has been found over a period of use in the workshop with a couple of these irons that the outer casing tends to escape occasionally from the retaining ring and slide off on to the floor. Flattening out the flange at the base of the casing gives more for the ring to grip and usually keeps the casing in place. All the bits are stamped with their temperature, the 700 degree one being the best for general workshop use.

Irons are available with either four or eight feet of cable, the longer one adding 60p to the cost. The cable is covered in silicon-rubber which is claimed to be burn-proof, and indeed placing the hot bit on the cable for several minutes failed to produce any damage. As almost every workshop iron burns its lead at one time or another this is a useful advantage.

The iron operates from 24V. The original models were rated at 40W but this has been uprated to 48W. A transformer can be supplied which is rated at 60W, this giving ample reserve. With the original 40W models it was possible to operate two irons from the same transformer as the load is intermittent due to the thermostatic controls. With the uprated models this is no longer recommended.

A conical spring fixed at an angle at the back of the transformer affords a parking place for the iron when not in use and of course the weight of the transformer is sufficient to ensure that it is not knocked over. A compartment at the front of the transformer houses a flat sponge pad which must be kept moist so that the bit can be wiped on it when needed. If other stands are used they must not contain steel otherwise the magnetic action of the thermostat may be upset.

### *Use*

In use the first impression is the lightness of the tool. Weight including lead is only 2.5oz. When idling in the stand the iron switches on for between 3-5 seconds and is then off for about 15 seconds. When in use the on periods are longer depending on

—continued on page 512

# BASIC CIRCUITS FOR THE CONSTRUCTOR

## THIS MONTH: TRANSISTOR VIDEO AND SYNC SEPARATOR CIRCUITS

THE video amplifier is perhaps the weakest link in nearly every domestic television receiver and few manufacturers can feel justly proud of the video circuits they have produced. Mean-level a.g.c., attenuation of the d.c. level and in some receivers blatantly uncompensated a.c. coupling have all conspired to produce pictures which can cause considerable annoyance to the more discerning viewer. Briefly the basic problems are that a.c. video coupling causes the overall picture brightness to change with picture content while d.c. coupling results in interdependence of the brightness and contrast controls which makes optimum adjustment rather difficult.

In this month's article the constructor is given the option of using d.c. coupling, a.c. coupling or a combination of the two. There can be no doubt that d.c. coupling gives the best results, even up to studio monitor standard, but it has several drawbacks. There is the problem just mentioned of brightness and contrast control interdependence and also that a greater beam current must be supplied by the tube when the picture content is predominantly white. It is thus essential to have a modern tube with good emission and an e.h.t. supply with reasonable voltage regulation.


### Video Circuits

On 405 lines pin 1 (Fig. 1) of the final 405 i.f. transformer is decoupled to chassis by C31 and C32. A small d.c. bias is tapped off from VR31, passes through the final i.f. coil and the detector diode to pin 3 to set up the operating point of Tr32 and ultimately Tr34. The detected vision signal at pin 3 of the final 405 i.f.t. is passed to the base of Tr32 through a low-pass i.f. filter (L31, C35). The signal is transformed to a lower impedance by Tr32 and is developed across R34 with the picture information positive-going. Similarly the 625 signal is developed across R240 (see Fig. 3, July issue), but with sync pulses positive-going.

Selection of the 405/625 signals is accomplished by relay contact RLY31A and the output from this passes to the base of Tr34. This is a high-voltage transistor specifically designed for use in video output stages and can easily provide the 100V peak-peak vision signal required to drive a modern tube. The frequency response of the video stage is tailored by C39 and L33 and the deleterious effects of stray capacitance are reduced to an absolute minimum by the use of Tr35 as a buffer stage before applying the video signal to the c.r.t. R315 and L34 provide a significant degree of protection from high-voltage flashover within the tube.
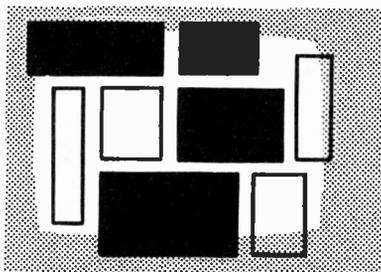
### Tube Modulation

Because of the differing polarities of the 405- and 625-line signals a relay mounted at the base of the tube (RLY32) is arranged so that the tube is modulated at the cathode on 405 lines (conventional practice) and from the grid on 625 lines. This system



J.W. THOMPSON

works extremely well even though 30% more drive is required for grid modulation. Note that the brightness control will work *backwards* on 625 lines and if this is likely to cause confusion the matter can be easily rationalised at the expense of an additional relay.

### Blanking and Sync Separation

The problems introduced by switched tube modulation are two-fold. First the field flyback blanking pulses have to be of opposite polarity for each standard (see Fig. 2). Secondly there is the problem of separating the sync pulses from the vision information. Relay contact RLY31B carries out the necessary switching, taking the signal for the sync separator Tr36 from the video driver Tr32 via R36 an C38 on 405 lines and from the video output emitter-follower Tr35 via R314/C311 and C312 on 625 lines. In both cases the sync pulses are negative-going with positive-going video. A positive bias develops across C313 the level of which is determined by the setting of the presets VR32 (405) and VR33 (625). By suitable adjustment, Tr36 is held cut-off except on the sync tips when it conducts heavily. The system is self-adjusting within a wide range of signal strengths.

The following transistor Tr37 is an npn type and is thus turned on by the positive-going pulses at Tr36 collector. High-amplitude negative-going sync pulses are developed across R318 and are suitable for driving valve or transistor oscillators. The field sync integrating circuit (D32 etc.) provides an output suitable for feeding to the pentode grid of a PCL85 field oscillator-output valve through a 1k $\Omega$  limiter resistor (as for example used in the Bush TV135 series). Adjust the value of C321 for optimum sync; if it is too large field bounce will occur.

### Output Transistor Rating

For the benefit of readers who cannot wait until the end of the series to try this circuit a few comments about power supplies and transistor breakdown voltages will be given. The manufacturer's data on the D40N1 transistor indicates that the maximum safe h.t. voltage in this circuit is 240V and at no time must the h.t. be allowed to rise above this level. On a domestic receiver however the h.t. can sometimes rise to as much as 300V during the warm up period. Power supplies for high-voltage transistors are thus rather a headache for the set designer and there are no less

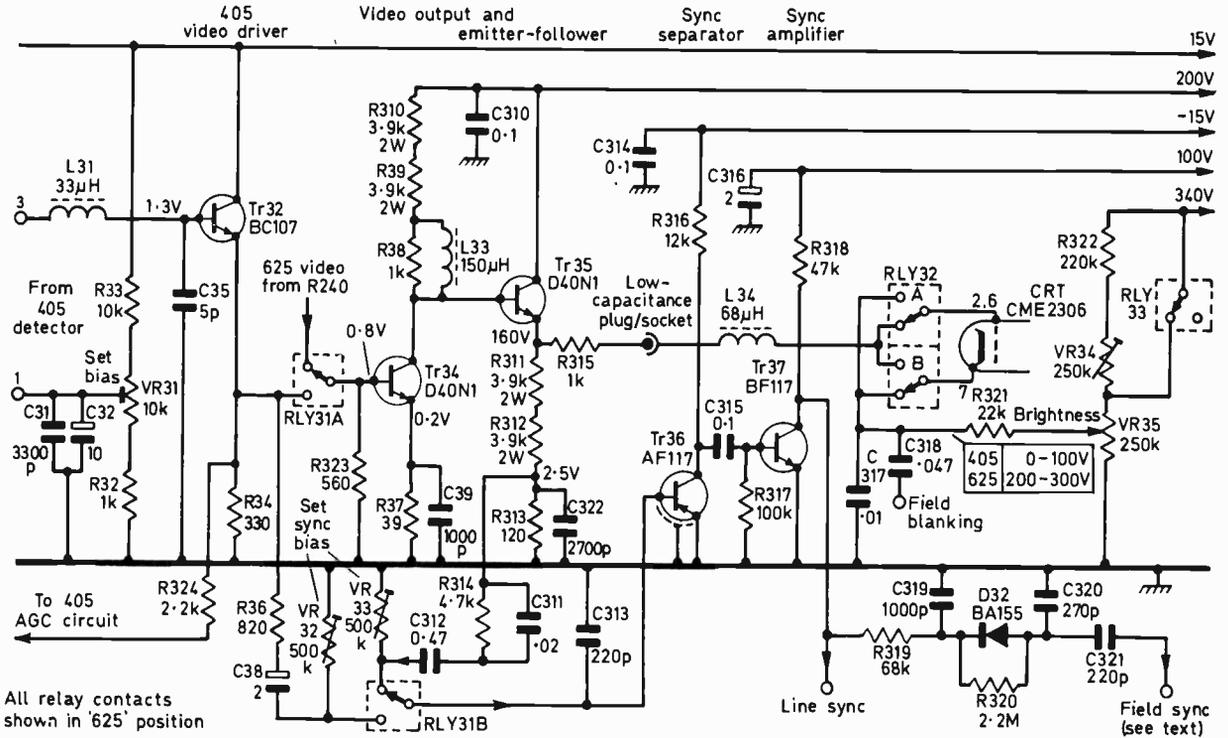


Fig. 1: The video and sync circuits. All relay contacts are shown in the 625-line position. The approximate voltages shown were measured with no signal, the line timebase operational and the video bias presets correctly adjusted, using a meter with an impedance of  $10k\Omega/V$ .

than four solutions to the problem: (1) Use a transistor with a higher voltage rating. There is a transistor (D40N3) which will take 300V and we understand that this is available from the supplier mentioned at the end of this article. (2) Stabilise the main power supply. This is a costly solution and will not be considered here. (3) Connect a  $15k\Omega$  3W resistor from the collector of Tr34 to chassis: even if the h.t. reaches 350V the breakdown voltage of Tr34 will not be exceeded. Tr35 is still in danger however, so this method can only be used with the circuit shown in Fig. 4(b). (4) Use a partially loaded mains transformer (this method is used in the prototype receiver). The h.t. for the entire receiver is obtained from a transformer with 190V no-load a.c. output, providing 210V d.c. at 0.25A through a silicon bridge rectifier. At no time does the h.t. exceed 240V: a resistor chain across it ( $3k\Omega$  plus  $3k\Omega$ ) draws a continuous current of about 30mA and serves the dual purpose of limiting the peak h.t. value and of producing at the junction of

these two resistors a 100V h.t. line for the medium-voltage transistors (e.g. Tr37 which has a maximum  $V_{CER}$  of 140V).

**Recommended Solution**

The fourth solution is recommended because it permits the use of an earthed chassis. Note that the + and -15V supplies may be readily obtained from a low-voltage transformer with suitable rectification

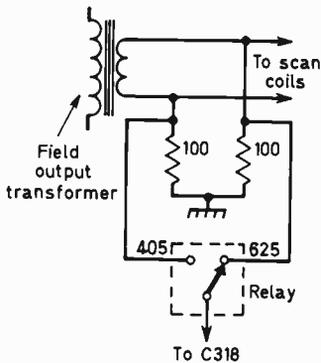


Fig. 2 (left): Because of the switched drive to the c.r.t. it is necessary to invert the polarity of the field blanking pulses on the two systems. The arrangement shown here provides the necessary blanking pulse inversion.

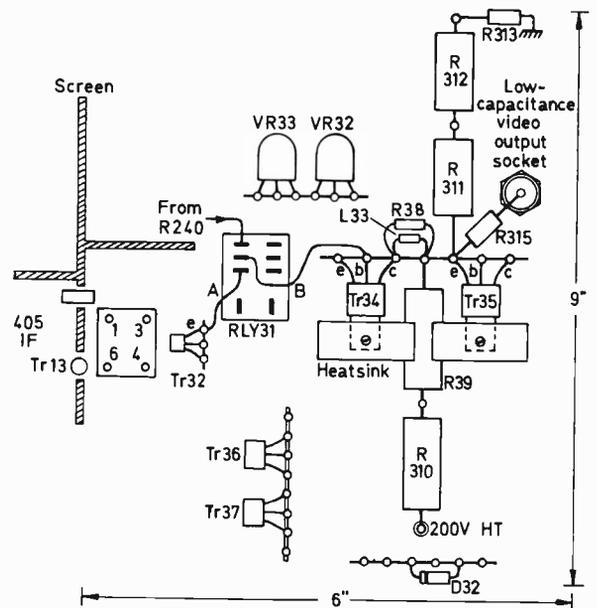


Fig. 3 (right): Suggested layout—as used in the prototype.

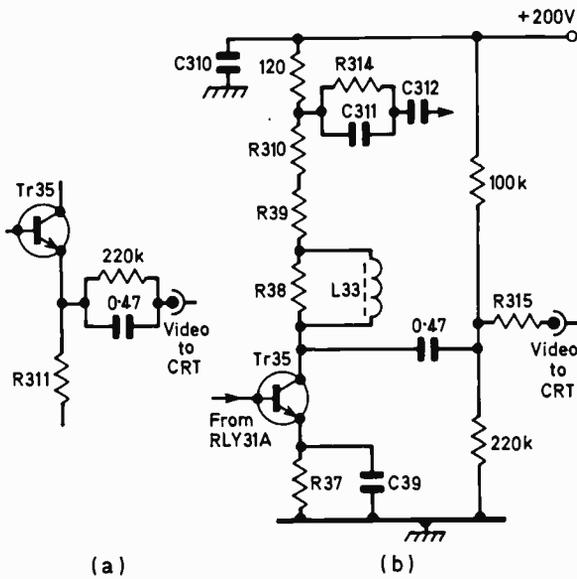


Fig. 4: Optional modifications to the basic circuit. (a) Circuit to reduce aircraft flutter. (b) A.C. coupling to the c.r.t., with the emitter-follower Tr35 omitted.

and smoothing while the 340V line is derived direct from mains live through a BY127 rectifier and 100 $\mu$ F parallel smoothing capacitor.

### Layout

The layout (Fig. 3) is not critical so only a rough overall plan is given. It is advisable to keep all signal-carrying leads as short as possible and on the same side of the chassis as the transistors. The d.c. leads may be as long as necessary and it is a good idea to have as many of them as practicable on the other side

of the chassis, feeding the circuit through nylon lead-through tags.

The transistors themselves should be mounted on low-capacitance tagstrip (e.g. porcelain stand-off type) and the two video output transistors will each need to be bolted to at least 6 sq. cm. of black painted aluminium. The heat sink tags on these transistors are connected to the collector so the heatsinks should be well away from all stray capacitances and must not touch the chassis. The body of relay RLY31 is on the opposite side of the chassis to the transistors and should be mounted on a squared, inverted U-shaped clamp. The relay tags protrude through a rectangular hole cut in the chassis. RLY32 is mounted on the tube base with due regard to stray capacitance. RLY33 may be mounted almost anywhere.

### Setting Up

Turn VR31, VR32, VR33 and VR201 (Fig. 3, July issue) to their mid-positions and polarise the relays for 625-line operation. Do not plug in the aerial yet. Turn the brightness control so that the slider is at the most positive end of its track and attach a meter (250V range) to Tr35 emitter. Switch on the receiver, allow five minutes for it to warm up completely and adjust VR201 to give a reading of 160V on the meter. Any faults at this stage should be apparent from measuring voltages at the points marked in Fig. 1.

Next plug in the aerial and adjust the contrast and brightness to give a well-balanced 625-line picture. All being satisfactory at this stage adjust VR33 for optimum sync conditions. Then switch to 405 lines, set VR31 to give 160V at Tr35 emitter and adjust VR34 and the contrast control for correct grey scale. Adjust VR32 for optimum 405 sync. The value of C321 may need changing, as previously mentioned, for the best field sync conditions.

If the picture is streaky either the vision i.f. is misaligned or there is excessive stray capacitance in

## ★ components list

### Resistors:

R32	1k $\Omega$	R39	3.9k $\Omega$ 2W	R315	1k $\Omega$	R321	22k $\Omega$	VR31	10k $\Omega$	VR35	250k $\Omega$
R33	10k $\Omega$	R310	3.9k $\Omega$ 2W	R316	12k $\Omega$	R322	220k $\Omega$ 1W	VR32	500k $\Omega$		Linear potentiometer
R34	330 $\Omega$	R311	3.9k $\Omega$ 2W	R317	100k $\Omega$	R323	560 $\Omega$	VR33	500k $\Omega$		
R36	820 $\Omega$	R312	3.9k $\Omega$ 2W	R318	47k $\Omega$	R324	2.2k $\Omega$	VR34	250k $\Omega$		
R37	39 $\Omega$	R313	120 $\Omega$	R319	68k $\Omega$		Carbon film 5% $\frac{1}{2}$ W		Linear preset		
R38	1k $\Omega$	R314	4.7k $\Omega$	R320	2.2M $\Omega$		unless o'wise stated				

### Capacitors:

C31	3,300pF 160V P	C310	0.1 $\mu$ F 400V P	C315	0.1 $\mu$ F 160V P	C320	270pF SM
C32	10 $\mu$ F 15V E	C311	0.02 $\mu$ F 160V P	C316	2 $\mu$ F 150V E	C321	220pF SM
C35	5pF SM	C312	0.47 $\mu$ F 160V P	C317	0.01 $\mu$ F 400V P	C322	2,700pF SM
C38	2 $\mu$ F 15V E	C313	220pF SM	C318	0.047 $\mu$ F 400V P		E electrolytic; P polyester
C39	1,000pF SM	C314	0.1 $\mu$ F 160V P	C319	1,000pF 160V P		10%; SM silver mica 5%

### Inductors:


L31	33 $\mu$ H	L33	150 $\mu$ H	L34	68 $\mu$ H		Painton chokes, epoxy encapsulated.
-----	------------	-----	-------------	-----	------------	--	-------------------------------------

### Semiconductors:

Tr32	BC107	Tr34	D40N1	Tr35	D40N1	Tr36	AF117	Tr37	BF117	D32	BA155
------	-------	------	-------	------	-------	------	-------	------	-------	-----	-------

### Relays:

RLY31	RLY32	RLY33	Omron type MH2, 6V, double-pole changeover. (Home Radio).		
-------	-------	-------	---	--	--

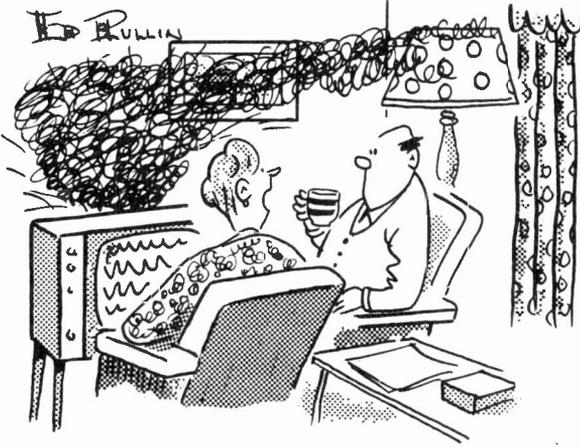

"Is it us or them do you think?"

the video circuit, most likely around the collector lead of Tr34.

### Modifications

In the writer's opinion the video amplifier stage of a receiver can be the most entertaining stage to play around with, perhaps because the picture is so directly influenced by the smallest adjustment. Having built this circuit the reader will probably want to experiment with different component values. For this purpose it is as well to know the "key" components. These are grouped below in terms of their effect on the video amplifier's performance.

**Gain:** Basically set by the value of R37. This resistor may need to be increased to reduce the gain if the circuit is driven from a valve i.f. amplifier. Reduction below  $22\Omega$  is inadvisable.

**Bandwidth:** The ultimate limitation on frequency response is the cut-off frequency  $f_r$  of Tr34 and Tr35. The upper limit can be increased at the expense of gain by reducing the value of R39 and R310 combined, but not below  $4.7k\Omega$  or the transistors will overheat. L33 acts as a peaking coil and may be adjusted.

**Pulse response:** The time-constant C39, R37 is the main factor determining the pulse response of the circuit. If C39 is too small, pulse edges will be rounded; if it is too large, overshoot will occur. It should ideally be adjusted for critical damping. Do not forget to alter its value if R37 is changed.

**D.C. attenuation:** A small degree of attenuation can be a positive advantage in areas of low field strength where aircraft flutter is troublesome. Fig. 4(a) shows a suitable network; the picture black level however will be slightly spoilt. For domestic purposes, and especially if an old tube is being used, viewers may be prepared to put up with a.c. coupling. Fig. 4(b) is the ultimate in cheap and nasty circuitry and regrettably has been used on occasion by several television manufacturers. Let us say no more about it.

### Component Supplies

In case of difficulty the transistors for every circuit in this series are stocked by A. Marshall & Son Ltd., 28 Cricklewood Broadway, London, N.W.2. The video circuit coils may be obtained from ITT Electronic Services, Edinburgh Way, Harlow, Essex.

**TO BE CONTINUED**

**NEXT MONTH IN**

# TELEVISION

## 20MHz PULSE SCALER

This versatile instrument using mainly i.c.s can be used on its own as a self-excited or externally-triggered wide-range pulse generator but has been designed principally to serve as a front-end adaptor for our recently published digital frequency meter. Used with this it extends the frequency range up to 20MHz.

## SECRETS OF THE SONY COLOUR SET

The Sony colour receiver is now being widely distributed in the UK and its performance has left a good impression with engineers. It is not however a PAL-D—or a PAL-S—set! Just what does go in this remarkable receiver will be revealed in detail next month.

## CIRCUITS FOR THE CONSTRUCTOR

Two circuits this month. First a three-stage 38.15MHz sound i.f. strip for the 405-line system to complement the vision i.f. strip given in our June issue. Secondly a fine-gated a.g.c. circuit to provide a control potential related to the signal black level to control the 405 vision i.f. strip.

## TROUBLE-TRACING CHART

A clearly presented list of fault conditions with the checks to make in order to pinpoint quickly the source of trouble. All types of monochrome receiver—single- and dual-standard, valve, transistor and hybrid—have been taken into account in compiling this chart. Of particular value to the newcomer to television receiver servicing.

## PLUS ALL THE REGULAR FEATURES

**ORDER YOUR COPY ON THE FORM BELOW**

TO.....  
(Name of Newsagent)

*Please reserve/deliver the OCTOBER issue of TELEVISION (20p), on sale SEPTEMBER 22, and continue every month until further notice.*

NAME.....

ADDRESS.....

.....



## DEVELOPMENTS in FILMS for TV

THE width of film gauges varies considerably. There are 70mm., 35mm., the CinemaScope and Vistavision variations of 35mm., 17.5mm., 16mm., super sixteen, 9.5mm., 8mm. and super eight. In Britain the BBC and ITV companies use the film print 35mm. standard and 16mm. standard gauges both of which have the long-established Academy aspect ratio of 1.33:1 width to height. This is acceptable to their telecine equipment and of course the screens of television receivers which present that aspect ratio, though many have the squarer shape of 1.25:1. But photography for television is also much concerned with the smaller areas of  $2\frac{1}{4} \times 2\frac{1}{4}$ in. (for slides) and 8mm. film. With both 16mm. and 8mm. film the photographic area for each frame of picture is relatively small because so much space is occupied by the optical sound track alongside the picture and by the perforations.

When sound-on-film pictures started in the cinema in 1928 an area was sliced off one side of the picture to accommodate the sound track. The resulting picture was square and ugly and was very soon restored to a more artistic shape—to fit the  $4 \times 3$  shaped cinema screens—by masking off small sections of the top and bottom of the picture in the film-gate of the motion-picture camera. This naturally thickened the frame line between successive pictures, further reducing the relative picture area in the cause of achieving a more acceptable screen shape. This expedient didn't seem to worry anybody at that time but doesn't look so good today.

### Sound Films for Television

From the very start of television the BBC used 35mm. film for telecine and continue to use this gauge for feature films however old they may be and whether in colour or black-and-white. Gradually, however, for newsreels, magazine items and documentaries the BBC started using 16mm. film, and the BBC has lately been venturing into the use of

colour 16mm. film for photographing exterior sequences or even complete productions which can be made on location.

### Faults with Small Film Gauges

Nearly all British television documentaries and exterior drama sequences cut into colour videotaped interiors are now photographed on 16mm. colour negative or reversal stock, with considerable success in matching the colour balance between film and videotape. What is the next step? But first what is the difference in the picture obtained from a 16mm. colour film compared with a 35mm. one—apart from the extra cost of film stock and processing? My own colour set—which has been very carefully adjusted—reveals the following faults on 16mm. colour film prints: (1) the grain of the photographic emulsion is more noticeable; (2) the dust, dirt and scratches are more conspicuous; and (3) the picture is slightly less steady. I hastily add that these faults are generally quite slight and scarcely discernible on the majority of colour receivers.

A return to the use of expensive 35mm. colour film for this type of television production could not be justified; but there are ways of achieving a big improvement with 16mm. colour film. This has been achieved in Sweden in the super sixteen system devised by Rune Ericson, lighting cameraman and founder of the Swedish Society of Cinematographers. His objective however was to achieve 35mm. film quality prints for use in wide-screen cinemas by making more efficient use of 16mm. gauge film and camera equipment.

### Super Sixteen

Following experiments financed by the Department of Technical Research, Stockholm a 16mm. film camera was modified to photograph an extended frame picture with an area about 40% larger than the standard 16mm. film frame. The principal change is for the picture in the camera to make use of the former sound track area on single-perforated 16mm. film. Several other changes have had to be made, such as moving the optical axis of the lens to a new central position, enlarging the camera aperture plate, replacing the lens with one capable of covering the larger area without vignetting, modifying the reflex mirror-shutter and viewing ground-glass, also the magazines and so on. It wasn't just a matter of doing

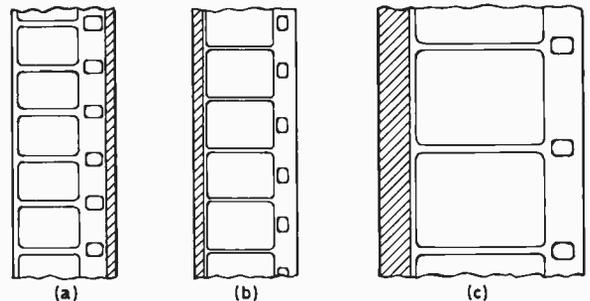


Fig. 1: Comparative picture areas—to same scale—of (a) standard 8mm. film, (b) super-8mm. and (c) 16mm. film, all with sound tracks on the prints. Super-8 has 52% greater area than standard 8.

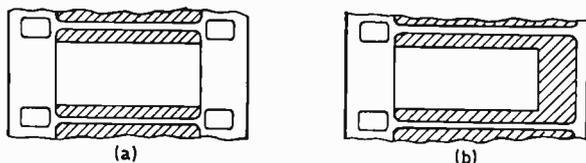


Fig. 2: Making the most of the 16mm. gauge. (a) Double-perforated 16mm. film—shaded area indicates loss of picture area when projected on a 1-85:1 cinema screen. (b) Single-perforated 16mm. film with sound track omitted, showing (shaded) the additional area available for photographing a 1-65:1 frame for television or a 1-85:1 frame for cinema release.

without the sound track therefore. The sound can be separately recorded on  $\frac{1}{4}$ in. tape (with an accompanying synchronising pulse), transferred to 16mm. magnetic sound film for editing and played off on telecine in sepmag form.

In Rune Ericson's experiments the original negative was blown up to 35mm. Eastmancolour reversal internegative film type 5249 from which large numbers of 35mm. colour prints were struck off. The same basic system however should be entirely suitable for top-quality 16mm. colour telecine play-off use.

It is not many years ago that 16mm. film was called "sub-standard" and was the special province of amateurs. Since then black-and-white photographic emulsions have improved enormously and good reversal colour film stocks have been introduced. It is now fully professional with millions of feet used by television organisations, educational authorities, industry, etc., while its use for advertising is expanding.

### Super Eight

When the professional cameramen of television news and magazine items moved into the 16mm. gauge manufacturers of professional film cameras, lenses, tripods and accessories moved too. Industrial and educational films then adopted the gauge as standard, particularly as 16mm. colour film is so much less expensive than the 35mm. gauge they had been using in black-and-white for years.

At this time a large number of amateurs moved out of 16mm. into the "standard" 8mm. gauge. It was a logical development, splitting the 16mm. gauge in half and retaining the same sized perforations—on one side. These perforations now seemed very large in relation to the size of the picture and dirt and scratches became more conspicuous.

### Film Hire

Many film libraries hire out 16mm., 8mm. and super eight gauge films. Their 16mm. films are frequently used by BBC and ITV stations without much complaint but the condition of copies for professional hire and use has to be closely watched. The worry really commences however when it comes to the hire of 8mm. standard gauge or super eight. The super eight gauge has over 50% more picture area than standard 8mm. but the perforations are smaller calling for very tight tolerances in the design and manufacture of the film transport mechanisms: dirt and scratches are less noticeable on super eight but the perforations are more easily damaged.

### Super 8 Cameras

Nevertheless the manufacturers are starting to make high-precision super eight cameras and projectors for professional use in US regional TV stations, the first being by the Fairchild Co. of Los Angeles in collaboration with the Eumig Company in Europe. An astonishing high-precision super eight camera has been announced by the French Beaulieu Company, associated with the American Hervic Corporation. The Beaulieu cameras have a range of extra refinements available: an infinitely variable speed range from 2 to 70 f.p.s. and an Angenieux zoom lens capable of focusing from infinity to half an inch, retaining focus throughout a zoom of 10 to 1. The Bauer super eight camera includes provision for making lap-dissolves in the camera by mechanically overlapping the fade-out of one shot into the fade-in of another. This facility might be important because contact film printing and optical dissolves and effects cannot at present be carried out in labs from such small negatives.

### Projection and Telecine

In addition to the major sprocket-hole changes there is with super eight an increase in the pitch of the film pull-down from frame to frame. Four and a half frames of super eight picture cover the area previously occupied by five frames of standard 8mm. This necessitates a major change in the claw mechanism for transporting the film. There are further complications if a sound track is added and recorded on the original film in the 8mm. camera. Complications thus include the matter of film transport speed—whether the 8mm. film is to be photographed at 16, 24 or 25 f.p.s.—whether the sound is to be recorded on optical or magnetic sound track in the film camera and what is to be the differential position of sound recording—in front or behind the relative position of its corresponding film frame. These points are being fought over in the USA by the many manufacturers interested in 8mm. film.

### The Professional Angle

In the amateur field there are projectors in which it is possible to change gear from 8mm. standard pull-down to super eight. For professional use in television in the USA at present the sound is either (a) added later or (b) separately recorded on  $\frac{1}{4}$ in. magnetic tape with a synchronising pulse on a parallel sound track. In the USA these differences of standards are dealt with by using the appropriate 8mm. film projectors multiplexed and presented to a photoconductive type telecine machine with a long delay time to cope also with amateur filming at 16 f.p.s. The quality is usually poor but the use justified by the news value of the material. ■

### BINDERS FOR YOUR "TELEVISION"

You can keep your copies of TELEVISION safe in a binder which holds a year's issues and is available at 75p from the Binding Department, IPC Magazines Ltd., Carlton House, Great Queen Street, London, WC2.

# Workshop

## HINTS

by VIVIAN CAPEL

THIS time our title is somewhat of a misnomer as we are going outside the workshop for a change to give a few hints and tips to help the outside service engineer. Many problems arise with outside service work that are not found in the workshop and some attention to these can make the outside engineer's day that much easier.

### Route Planning

First the engineer must actually get to the call before he can start the repair. It is surprising how many firms rely on a very haphazard arrangement in assigning service calls to their engineers. Often when the engineer reports he is handed a batch of calls situated at all points of the compass.

No service department should be without a large street plan of the area normally covered and as building and new streets are continuously progressing in many areas this map must be kept up to date. This can be done by obtaining new editions as they are published (some workshops have grimy maps on their walls that are ten years or more out of date). In between any new roads that are discovered can be drawn in; these need not be accurate or to scale.

When requests for service are received they should be put together with those in the same area and different areas or collections of calls then assigned to different engineers. If there are only one or two engineers working outside assign a group of calls in one general area each time. The engineer can then report back when these calls are finished and can next be given those calls in another area. It is possible that in the meantime other calls may have come in for the second run and these would otherwise have been missed if all calls had been assigned in the first place.

Thus a rough sorting out should be done by the service manager to start with. Next the engineer himself should work out in advance a route giving a sequence of calls involving the least time and travelling between. A few minutes spent doing this, consulting the map if need be, will be more than made up in the savings accomplished. There will of course always be the few awkward calls that have to be done at specified times which will throw the spanner in the works, but it may still be possible with slight rearrangement to work these in.

It is a good idea to brief the person taking in the requests for service to avoid special times if at all possible. In the majority of cases it has been found that these can be almost eliminated by suggesting that the key be left with a neighbour or concealed at

some prearranged place. The former is the preferable arrangement as there is then no risk of unauthorised persons entering the house by discovering the key and suspicion falling on the engineer if anything is missing.

Routes should be further planned to avoid busy roads or thoroughfares during rush periods.

### "Not Homes"

Even when customers have stated that someone will be at home on a certain day and in some cases special times have been set engineers sometimes call to find that there is no one at home. To simply call again the next day—unless the van is passing the road—will very likely be a waste of time because a call will not be expected then and a further "not home" will be recorded. On finding no one at home then a note should be left stating that the engineer called at a certain time. An odd scrap of paper or the back of a cigarette packet is *not* the most businesslike reminder to leave of the visit. Printed or duplicated slips are by far the best.

Such slips should state that in response to their request for service an engineer called at (here leave a space for the time). The onus should then be placed on the customer to make a further arrangement. The wording could run this way: "Please let us know which day would be convenient for a further call to be made and whether someone will be home during the morning or afternoon or both." It should avoid being more specific than stipulating morning or afternoon for reasons we have already mentioned. If different from the shop the phone number of the service department should be included.

When leaving a not-home slip make sure that it is well pushed through the letter box or under the door and that no part is accessible or visible to the outside. If this is not done it could well prove an open invitation to housebreakers who are on the watch for such signs of an owner's absence.

### Plastic Foam Van Mats

Much of the engineer's time is spent in transporting television receivers to and fro. Modern slim-line receivers give rise to problems in the van. It needs only a slight jolt—a sharp corner or an emergency stop—to send the set tumbling about with disastrous results to the cabinet and probably internal damage too. Some vans are equipped with straps fixed to the sides and sets are duly strapped in place when in transit, with blankets or other means of padding to prevent the straps chafing at the edges of the cabinet. This is quite an effective method of preventing damage but it is rather time consuming if a number of sets are to be carried.

A better idea which has proved very successful in practice is to equip the van with a number of large foam plastic mats which should be about two inches thick. The receiver is placed face downward on the

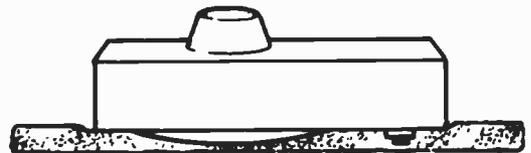


Fig. 1: Slim-line sets lie securely on a plastic foam mat which moulds to their contours.

mat and no other securing is needed (Fig. 1). The mat readily takes the contours of the front of the set and a suction is formed to the c.r.t. face or implosion shield. A grip is also exerted on the floor of the van by the foam under pressure from the weight of the set.

It will be found almost impossible to slide either the mat or the set upon it along the floor. It has in fact proved almost too effective inasmuch as if room must be found in the van for another set after it has been loaded it is not possible to move them all up closer.

### Soldering Irons

While it is common practice for soldering irons to be left on all day in the workshop this cannot of course be done by the outside engineer. This being so he must wait for his iron to warm up each time he needs it, and to cool down again before packing it away afterwards. Because of the time taken by conventional irons to do this a considerable amount of time can be wasted each day. Many outside engineers find one of the several transformer-type irons now readily available very suitable for outside servicing work. These are low-voltage models and as a result heat up very quickly—in just a matter of seconds—and cool in much the same time. Some are cylindrically shaped like a normal iron and have separate transformers. While these are more convenient for workshop use they are less so for outside work as there are two objects to carry and pack and also two leads.

Those irons incorporating the transformer in the iron itself are as good as any for this type of work. Admittedly they have drawbacks, for example being heavy and hence tiring to use for protracted periods. Also the bits are short-lived, being usually made of a loop of copper wire which forms the actual element. These though are not serious snags to the outside engineer because the use of a soldering iron is usually much less than in the workshop.

### Mains Plugs and Adaptors

A variety of mains sockets are likely to be encountered by the outside engineer in various homes and this raises problems as to what plugs to fit to the soldering iron, crosshatch generator and other test equipment. There are multi-type plugs obtainable which will correct to almost any size or type: although quite ingenious and useful for many applications they have been found to be unsuited for outside service work. Some have been found to be not sufficiently robust to stand the hard use—and often abuse—normal in day-to-day service in the field. If the selecting plate gets buckled or out of line, or if the retractable pins get jammed, selecting the right pins can be quite time consuming and fiddling. Their size is also something of a drawback.

After considerable experimentation the best arrangement has been found to be as follows. A 5A two-pin plug of the round Clix type is fitted to the lead of the iron or test equipment. These plugs will in addition to fitting 5A 2-pin sockets spread slightly to fit also the 5A three-pin socket. A shaver-adaptor in the tool-kit will enable a quick connection to be made to 13A sockets which are by now the most widely used sockets. If however another type is found for which there is no adaptor, a 5A-to-BC

adaptor will allow the plug to be used from the nearest lampholder. The iron lead needs to be fairly long to enable this to be done without difficulty.

Thus a single small plug on the lead and two adaptors will care for nearly all eventualities. As for test equipment such as crosshatch and signal generators, many excellent models are now on the market that run from batteries. These are well suited for outside work and eliminate among other things the mains-plug problem.

### Coaxial Plugs

It is often found when investigating complaints of low or intermittent signal strength that the trouble lies in the coaxial connector. Slight movement of the plug brings things back to normal. On investigating further the centre conductor is discovered to be lying in the centre pin without any solder and of course the copper wire has over a period oxidized and thus forms only intermittent contact. It seems to be common practice among aerial installers not to solder the centre conductor or to arrange any mechanical contact whatsoever but to leave things as described with the inevitable contact trouble in due course.

The real remedy of course is to solder the connection, but if for any reason this should prove inconvenient there is a method whereby a sound mechanical joint can be made without solder. This consists of simply nipping the base of the coaxial centre pin with the conductor inside using a pair of sidecutters. Fig. 2 shows that the walls of the pin grip and cause

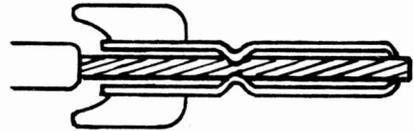


Fig. 2: Coaxial plug inner connector with pin pinched at the base to grip the inner conductor.

an indentation in the solid centre cable conductor. If the cable uses stranded wire this may have to be bent back to double the thickness as it is necessary for there to be no empty space in the pin. If this is not done the pinch will not grip the wire.

The danger in nipping the centre pin is that too much pressure is used so that the pin is nipped right off. There is a knack in getting the pressure just right, as too little will not grip the wire. Do not get the pin too near the joint of the cutter as it is here that the maximum force is exerted and the possibility of severing the pin is the greatest. If there are some old coaxial plugs about it may be as well to practise on them first.

Not all sets exhibiting the symptoms described turn out to have poor connections in the coaxial plugs. Often the trouble is associated with the aerial socket. Repeated removal of the aerial plug over a period for service, cleaning, decorating or just moving to another room can cause bad connections to develop. A common source of trouble is the rivets holding the body of the socket to the paxolin panel. These tend to work loose and as they carry the braid connections this leads to trouble. The most satisfactory way of dealing with them is to run solder over the rivet heads and the base of the socket. Often the print connecting either the body of the socket or the centre pin becomes fractured giving a similar effect. It always pays to check these points.

# THE RAINBOW REVOLUTION!

## 1951-1971 TWENTY YEARS OF COMPATIBLE COLOUR TV

### PART 3

I. R. SINCLAIR

WE have seen that the development team working on display tubes had considered every possible suggestion which had been made for colour tubes, and had settled on beam shadowing as the most feasible method, a choice encouraged by the new methods of photoetching which had been developed for use with printed circuitry. Both three-gun and single-gun versions of the shadowmask tube were demonstrated to the FCC in March and April 1950. The technical description of these tubes is interesting as it shows how right the RCA engineers were at the time to pursue this method.

#### Shadowmask Tube Construction

The shadowmask principle is now well known. The phosphors are laid on the screen in dots, grouped in threes in RGB triad sets (see Fig. 1). The tube shown in 1950 had about 117,000 groups (351,000 dots total) and was aluminised. The phosphors used were: willemite, the traditional green phosphor which was one of the earliest phosphors known; a complex calcium magnesium silicate, titanium doped, for the blue; and a manganese doped cadmium borate for an orange-red. Since the last was not close enough to a true red, a special yellow-rejecting glass filter was placed in front of the tube face to correct the red colours. And because of the inefficiency of the red phosphor the output from the other two phosphors had to be reduced by feeding attenuated signals to the B and G guns.

The shadowmask was made of an alloy of 70 per cent copper and 30 per cent nickel, of thicknesses from 0.002 in. to 0.004 in. (0.05-0.1 mm). It had one accurately located hole for each group of phosphor dots, a total of 117,000 holes, each held to a tolerance of 0.0005 in. (0.0125 mm). The holes in the mask were lined up with the phosphor dots by an elaborate hand-operated stencilling technique and the shadowmask was hot when assembled with the screen so that it was stretched slightly at normal temperatures and would not expand noticeably when it heated under

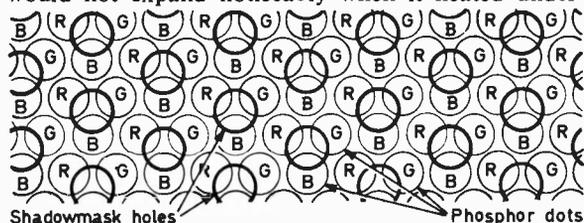


Fig. 1: Alignment of the holes in the shadowmask with the groups of phosphor dots on the screen.


electron bombardment. The scanning coils were wound in sections and carefully assembled and wired to give a suitable convergence pattern.

The shadowmask tubes shown in 1950 (see Fig. 2) must have been incredibly expensive and could never have formed the basis of a colour receiver whose price would have been within the range of the public, even in the USA. The subsequent development of the tube is a classic study of how intelligent engineering for mass production can make an extraordinarily complex article for low cost. At today's prices a shadowmask tube is cheaper than most 35mm. cameras of any quality yet the standard of construction and complexity is many orders greater. The investment made by RCA in the tube ran into many millions of dollars and the profits took a long time to come: every cent of profit made now has been richly earned.

#### Later Development

The resolution of the early tubes was judged to be insufficient so the total number of dots was increased to 585,000. An improved red phosphor based on manganese doped zinc phosphate was introduced and this made the yellow-rejecting glass filter unnecessary. A new blue phosphor was also used as the original one had a rather long persistence resulting in a blue edge to moving objects. (Modern tubes use considerably improved phosphors based on what are known as the rare-earth elements.) The brightness of the picture was increased by the use of these phosphors and also by improvements in mask processing which enabled the beam energy to be increased by two and a half times without creating expansion problems (expansion would make the mask move out of register with the phosphor dots).

The later mask-screen assembly departed from the earlier hand-matching procedures and enabled any shadowmask to be married up with any screen. The shadowmask holes, alignment slits and clamping holes were made in one photoetching operation to ensure uniformity and a system of locating the mask to the screen was devised. This consisted of three pins with collars fitted in a frame to which the shadowmask was bolted. Each pin had a hemispherical, off-centre tip which located exactly in a V groove in the phosphor plate (see Fig. 3). Screwing the collars into the frame had the effect of changing the separation between the shadowmask and screen while rotating the pins moved the phosphor plate round slightly so that the alignment of the mask with the screen could be adjusted.

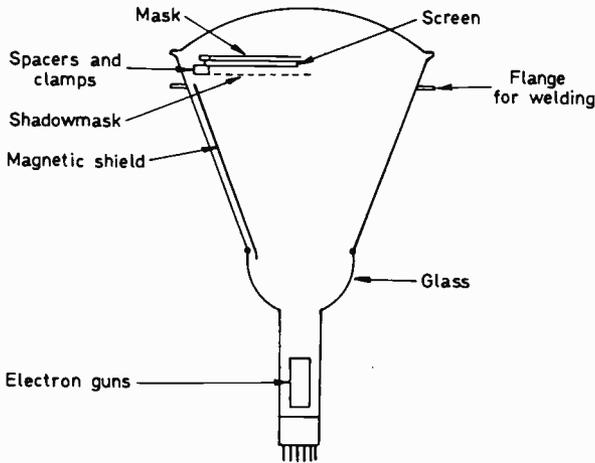


*Fig. 2: The early shadowmask tube. The glass face of the tube was not the screen but simply a transparent cover sealed to a metal ring on which were mounted the phosphor-dot screen and the shadowmask. This assembly was in turn welded to a metal cone to which the stem carrying the guns was sealed. The whole tube was adapted from the 16in. metal-cone tube used for black-and-white television for a considerable time (the same as the monochrome tube made in the UK at the time by English Electric).*

The method of printing the phosphor dots was also being steadily improved but was unchanged in principle. By projecting light from sources positioned as though they were the guns of a tube a photographic plate was printed with the shadowmask dot pattern. One plate was made (carefully lined up to the mask) for each light position R, G and B and stencils were made from the photographic plates and used to mask the screen as the phosphors were allowed to settle. In practice the phosphors are mixed with a sodium silicate solution, with various additives to control the grain size of the powder, and allowed to settle on the glass on which the silicate acts as a binder. This technique proved very satisfactory at the time.

Improvements in the deflection system included continuously wound coils to replace the elaborate built-up assemblies and the use of "field compensating tabs"—small strips of nickel alloy which could be bent to form a fine adjustment to the magnetic field.

A meeting was held between RCA engineers and TV set manufacturers in New York City on 19th and 20th June, 1951. The operation and manufacture of the shadowmask tube were fully described and each receiver manufacturer was offered a free gift of a shadowmask tube and deflection components. Tube manufacturers were offered a free set of parts for the

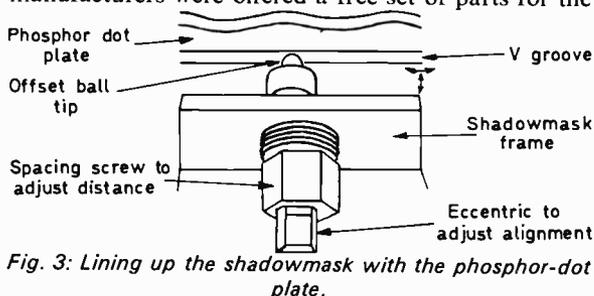

*Fig. 3: Lining up the shadowmask with the phosphor-dot plate.*

tube if they wished to consider making it under licence. Altogether 152 tubes were given away then and by March 1953 477 tubes had been supplied to 177 companies. Pilot production of tubes was running at 10-15 per day by late 1951 and planning was in hand for a production capacity of 2,000 tubes per month within a period of nine months. These were 16in. tubes and a 21in. version was also being developed using 969,000 phosphor dots. This tube size was first shown in July 1951 and in a later version in April 1953.

## Receivers

Another section of RCA, the RCA Victor Division, was coping with the design of receivers using the NTSC signal and the shadowmask tube. Earlier receivers (Trinoscopes) had used separate c.r.t.s with colour filters and projection screens. The first shadowmask model started life in April 1950 and 35 receivers had been made by December of that year. This model used the 16in. shadowmask tube, 45 valves and had two separate chassis. The second prototype shadowmask receiver used 54 valves and incorporated colour phase alternation, with a sub-carrier at 3.58MHz. Six were built and tested in New York during April 1951. The third prototype model used a 3.89MHz subcarrier and CPA, thirty-five were built but at this time the alternative to CPA in the form of I and Q signals of different bandwidths was crystallising. The fourth model started life in December 1951 using 35 valves on a single chassis within a cabinet comparable in size to the black-and-white sets of the time. CPA was still used in the early stages but this was changed in October 1952 to the specification adopted by the NTSC in February 1953. Twenty-one sets were made and demonstrated to the FCC in April and May 1953.

The last prototypes built before FCC approval contained a u.h.f. tuner, a colour hue control, an inter-carrier 41.25MHz i.f. strip, crystal controlled sub-carrier and colour killer circuits. These sets were the model for the types which went into production immediately FCC approval was obtained for the colour standards.

## Picture Quality

In addition to the public opinion surveys RCA also asked qualified TV engineers—their own and NBC employees—to give their opinions on picture quality. These could be given anonymously if wished and no conferring was permitted while the questionnaires were being filled in. The opinions on general picture quality were high, matching the views given by the public, but the engineers particularly noticed mis-registration and colour fringing when these were present.

Tests were also conducted with nontechnical staff to find what fault levels would be acceptable to observers. The first set of tests was of cochannel interference—where two stations working on or near the same frequency cause interference. Every combination of possible effects had to be tested and it was found that this form of interference was no worse with colour signals than with monochrome ones. In general an interfering signal 40dB down was just detectable and one 30dB down was just tolerable. The next set of tests was on random noise and sinewave interference and here the observers found that colour

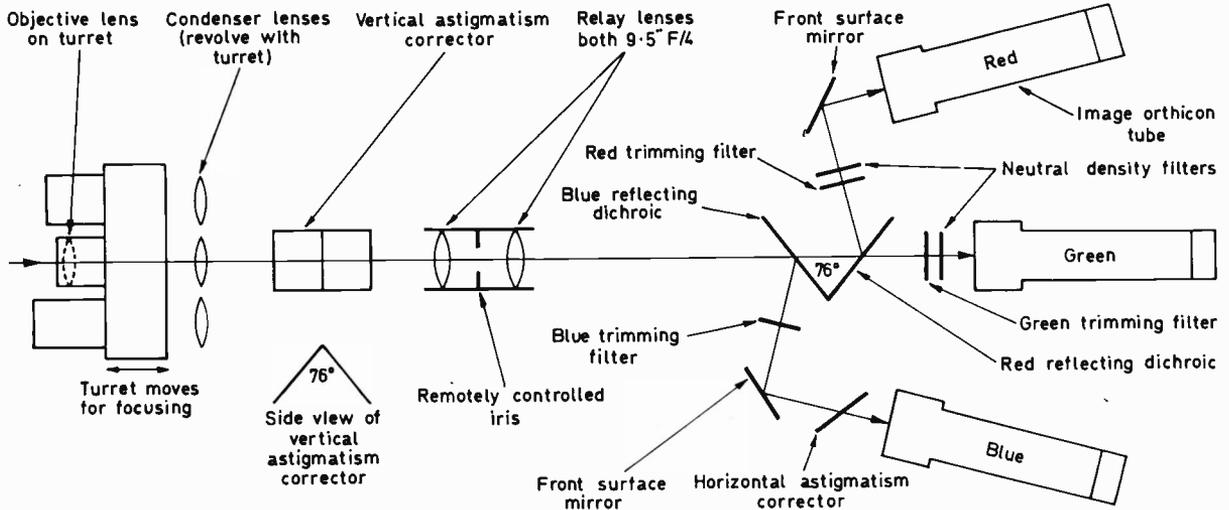


Fig. 4: The optical system used in the three-tube colour television camera developed by RCA.

signals were about 1dB more susceptible to random noise and much more susceptible to sinewave interference near subcarrier frequency compared to black-and-white.

Multipath reception was more troublesome however with colour signals as much as 2.7dB down compared with similar effects on black-and-white signals. There was some doubt as to how far this test could be related to actual field experience for the amplitude of the reflection used was very large, only 8 dB down for the main signal, and then did not simulate the continuous colour change caused by reflection from a moving object. The most serious objections to the NTSC system have always arisen from this type of problem and it was because of this that the phase-alternation principle was revived in the new form of PAL. The extra price paid in Europe for the greater complexity of the PAL system is a measure of how strongly the complaints about colour shifts in the NTSC system affected the Post Office committee which decided in favour of the PAL system in this country.

### Studios and Transmission

Considerable changes were of course necessary in studio and transmission equipment in order to handle colour. Sync generators had to be more closely controlled in frequency and had to incorporate a sub-carrier generator and burst gate for adding the colour burst to the back porch of the line sync pulse.

The cameras used three image orthicon tubes with the light from a single lens split so as to project an image on to the face of each tube (see Fig. 4). Registration of the three images was the main problem here, along with the enormous size and mass of the camera. The camera viewing tube was a monochrome one since small colour tubes were not available.

Monochrome monitors were used, with switching so that the signal from the R, B or G channel could be viewed separately. The separate RGB channels were maintained throughout the video system and this was also done in other pickup devices such as slide and movie scanners. A new device, the colourplexer, was used to mix the colour signals, to form the  $I'$  and  $Q'$  signals and to modulate them on to the subcarrier. Colour monitors were of two types, one using the

separate RGB signals and the other decoding the  $I'$  and  $Q'$  signals.

Transmitters had to be modified so that their phase-frequency characteristics did not appreciably change the colour information of the signal and the amplitude linearity had to be good. In general however the requirements for transmitter equipment were much easier to meet than those for studio equipment, so meeting the claim that RCA colour would not add greatly to the cost of the radio station operator who did not run his own studio.


### Approval

All the evidence so meticulously assembled was condensed into one document of 697 pages and presented to the FCC. A few copies of this document still exist and are a priceless piece of history. The outcome of the petition was as near a foregone conclusion as can be imagined and the RCA system became the colour-broadcasting system for the USA and later for Japan, Canada, Puerto Rico and Mexico. Hundreds of manufacturers took out licences to build colour sets and components, yet sales dragged and continued to drag for years. RCA had to wait ten more years before seeing any prospect of breaking even financially on their huge investment, but they did have the satisfaction of knowing that their engineering ability would keep them ahead of the game for the foreseeable future.

The NTSC system is still in use, unchanged except in minor detail. Improvements in receiver design have greatly reduced the problems of colour stability as well as greatly reducing the price of sets and there is no likelihood of the system being replaced in the US by any other system of transmission. It provided the world's first viable colour TV service and it is ironical that after much deliberation Europe adopted a variant which, in a primitive form, was tried and discarded.
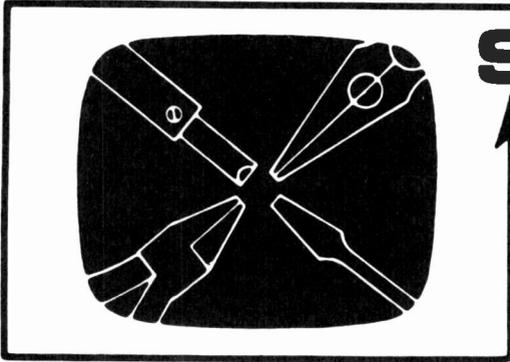
### Acknowledgements

The author wishes to acknowledge gratefully the help given him in the preparation of this series by RCA and also by the Librarian of the English Electric Valve Co. Ltd. who located one of the few copies of the 1953 petition available in this country. ■



# SERVICING television receivers

L. LAWRY-JOHNS

SOBELL ST282 SERIES

A large number of these receivers are now available on the secondhand market and properly serviced provide an admirable second set. The basic models covered are the Sobell ST195, ST282, ST283, ST284, ST285 and ST286 and also the GEC BT452 and McMichael MT762 and MT763, with many near relatives. We will set out this article on the basis that one of these sets has been obtained secondhand with no known history.

## Mains Adjustment

Assuming that the locality has a 240V mains supply the first essential is to check the voltage setting adjustment. In far too many cases this will be found at too low a setting, not to suit the mains voltage but to avoid replacing a faulty dropper section. It is a great pity that this should be done because it does seriously shorten the life of the tube and valves. Revert the setting if incorrect to the 245V position and make checks on the nearer dropper sections (top) which feed the anode of the PY33. In most cases it will be the 17 $\Omega$  section R87 which is affected or one of the 23 $\Omega$  sections R85 or R86. These values are not critical and replacement is quite easy using wired-ended or Radiospares dropper sections.

It is often suggested that the PY33 be replaced with a silicon power diode. We do not agree with this in a receiver which has been used to the slow voltage build up of the valve rectifier. The reliability of the receiver will be maintained by retaining the PY33.

## Common Troubles

Assuming that the receiver is working, with the heaters lighting and h.t. at the smoothing choke (Ch1), the common troubles with their symptoms are as follows.

### No Sound, Vision or Raster

Although total absence of h.t. is invariably due to an open-circuit dropper section (R85, R86 or R87) there is often full h.t. at the choke along with some evidence of overheating in the line output stage. This should immediately direct attention to the sub-h.t. line resistor R80 (150 $\Omega$ ). If this is burnt out or is otherwise open-circuit, the line oscillator cannot function and there is no supply to the i.f. stages.

The trouble should be looked for on the left side panel and some signs of the source may easily be seen around the vision i.f. stage V4. A shorted decoupling capacitor (often C45) starts the trouble, burning out R30 and perhaps damaging the panel.

This type of damage may not be as serious as it looks and can be cleared away quite quickly with the new components wired on the print side if this is more convenient.

The valves should not be above suspicion. Remove these in turn, starting with the two PCL84s, to see if the meter needle swings up to a higher resistance reading when any one is removed. EF80 valves do not as a rule suffer from internal shorts but frame-grid valves such as the EF184 and EF183 most certainly do.

## Line Timebase

When the short has been cleared and a new 150 $\Omega$  resistor fitted the line timebase should start oscillating and e.h.t. should be present. If it isn't either

## VOLTAGE AND CURRENT DATA

The readings given below were measured with a 240V mains input and a weak signal just sufficient to lock the timebases, with the contrast control set for zero voltage across MR1 and all other controls adjusted for a normal picture, using a 20,000 $\Omega$ /V meter. HT1 210V; HT2 202V; HT3 190V; HT4 173V; boost voltage (C97 to chassis) 700V; total h.t. current 292mA.

Valve	Anode volts	Screen volts	Cathode current (mA)	volts
V3	160	106	11	1.3
V4	172	172	12.6	1.9
V5b	—	—	—	90*
V6a	138	173	11	4
V6b	45	—	—	—
V7a	35†	—	—	—
V7b	189	202	48.7	19
V8	215 a.c.	—	292	210
V9	175	175	12.5	1.5
V10a	92	—	—	—
V10b	190	190	18	2.1
V11a	182	—	1.3	4.3
V11b	127	—	4	4.3
V12	—	130	115	—
V13	202	—	—	—

\* With P11 set for minimum suppression. † Dependent on the setting of the height control.

C.R.T. voltages: Cathode 135V; first anode 580V; e.h.t. 15.5kV.


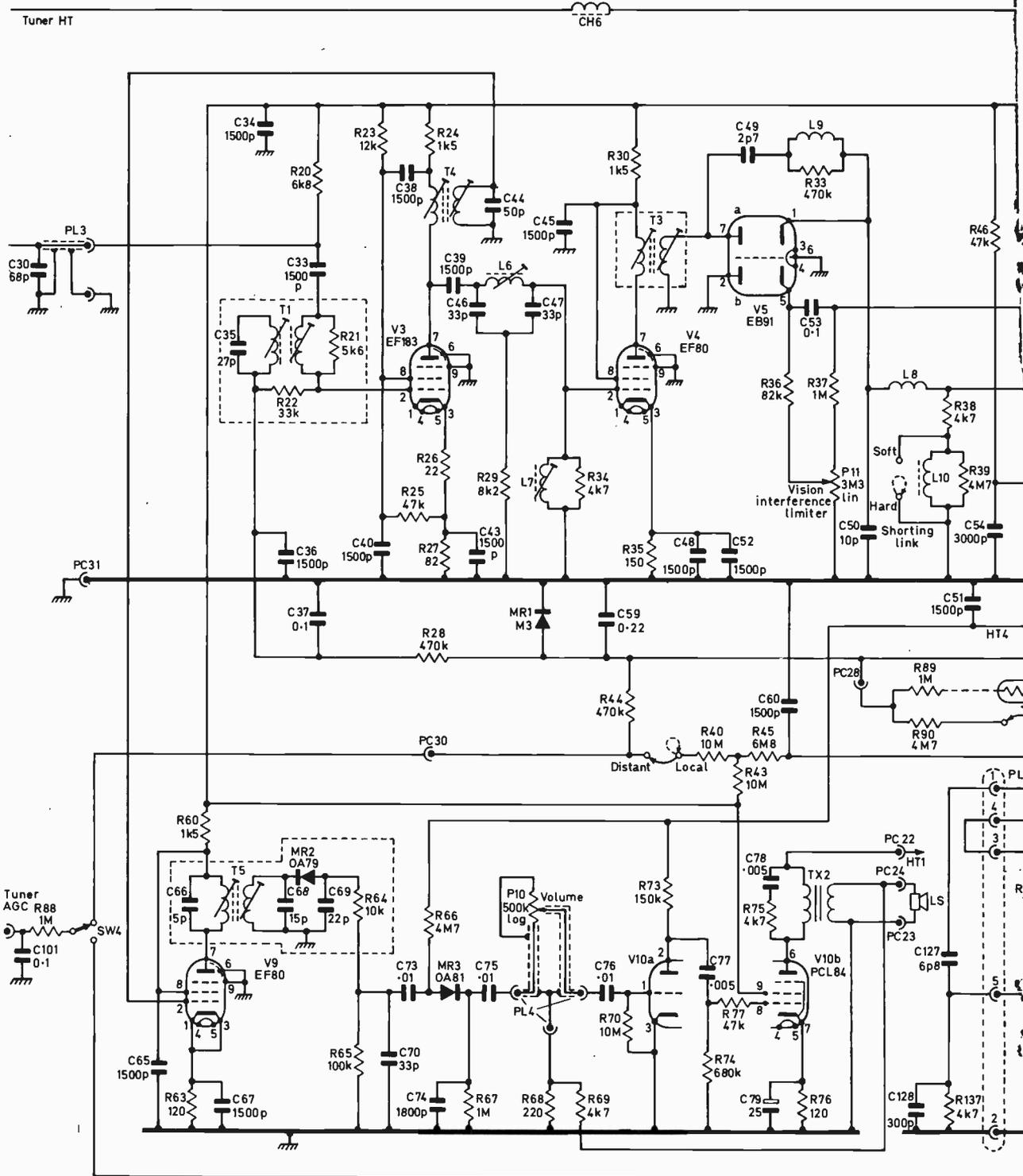


Fig. 1: Circuit diagram, Sobell ST282 series 625-line convertible models. CH6 is only present when a push-button

the PY81 or the PL36 may have suffered damage due to the overheating and the glass of the latter valve may well be cracked.

If the valves are not at fault it is essential to check the screen feed to the PL36. Whilst R134 does not often give trouble it may well overheat. This is

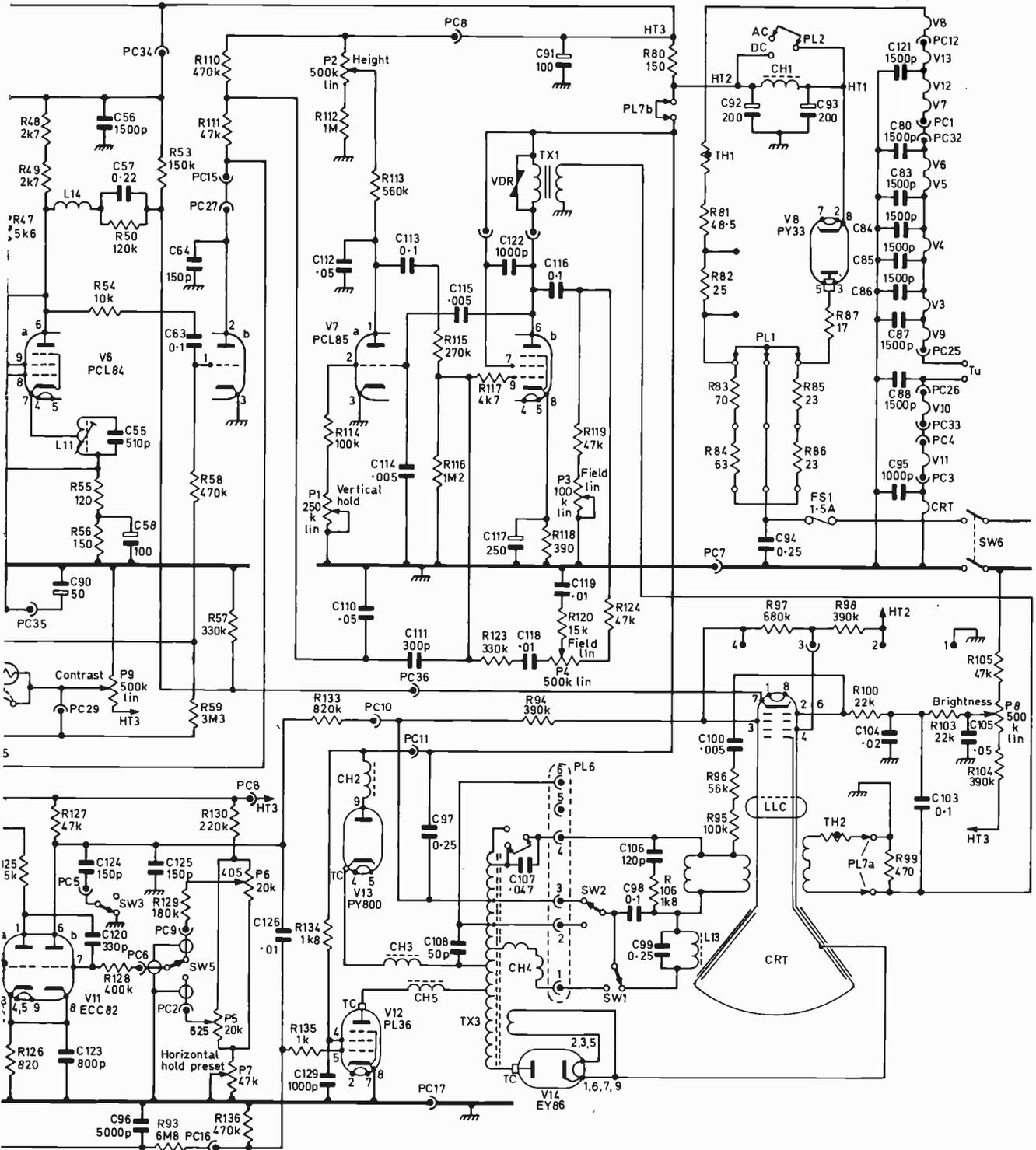because C129 often shorts. This 0.001µF capacitor is in an extremely awkward position and it is quite possible to cut the track across from it and the lower end of the resistor to the PL36 base. With the track removed it becomes possible to wire the resistor from the upper h.t. point to the PL36 valve base, omitting



tuner is used. 19in. models are fitted with an AW47-91 tube, 23in. models with an AW59-91 tube.

the capacitor.

The timebase should then run normally if the ECC82 is in order. If there is still no e.h.t., with no clear whistle, remove the PY81 top cap. If this seems to restore some sort of working replace the boost line capacitor C97 0.25 $\mu$ F. This is over the back

of the tag panel where R80 is located, i.e. out of sight behind the rear centre tagstrip.

Apart from the EY86 becoming faulty this is the sum total of the normal line output troubles.

**CONTINUED NEXT MONTH**

# COLOUR RECEIVER CIRCUITS

PRIMARY-COLOUR TUBE DRIVE CIRCUITS—*cont.*

GORDON J. KING

WHEN primary-colour drive is employed the red, green and blue signals are usually fed to the appropriate cathodes of the picture tube (not to the grids). The grids are then connected together (as in effect are the cathodes in receivers using colour-difference drive) and suitably biased for the correct black level.

Cathode primary-colour drive is preferred because the in circuit picture tube has a greater effective sensitivity at the cathodes than at the grids. This eases the drive level requirement for maximum contrast and saturation—indeed when colour-difference drive is adopted an allowance for an extra 30 per cent drive signal from the colour-difference amplifiers must be made. The first anode comes into the sensitivity equation because the effective potential on this is relative to the cathode, not to the supply negative line or chassis.

Last month we looked at the offset luminance system used in the BRC 3000 chassis for beam limiting and brightness control. The Rank-Bush-Murphy chassis employs a modified arrangement for this. However, before we look at the circuits involved here a run-down on the video circuits would be desirable.

## RBM Circuits

This chassis uses the primary-colour drive technique in conjunction with transistor amplifiers which incorporate black-level stabilising (see Fig. 3). The three primary-colour signals are obtained from a silicon integrated circuit. This device is fed with the U and V chroma signals from the PAL decoder and also the luminance Y signal from an emitter-follower (3VT5) which is driven from a luminance amplifier in the i.f. channel via the Y delay line. Other inputs are a supply of 18V, the U and V subcarrier reference signals and a brightness pulse signal.

The device is designed to demodulate the U and V chroma signals to obtain the R—Y and B—Y signals, to matrix these to obtain the G—Y signal and then to matrix all three colour-difference signals in conjunction with the Y signal to produce the red, green and blue primary-colour signals. The Y signal input is to pin 10 and the red, green and blue primary-colour outputs at pins 13, 12 and 7 respectively feed the appropriate primary-colour amplifiers (3VT12/3VT15 for the red channel, 3VT13/3VT16 for the green channel and 3VT14/3VT17 for the blue channel) each of which has an input level preset for signal balancing.

The appropriate primary-colour signal is applied to the base of the first transistor of the pair, is d.c. coupled from the emitter of this to the base of the second transistor of the pair, and the collector signal of this then drives the appropriate cathode of the picture tube. Fig. 1 shows the connections to the tube cathodes. The series resistors (4R9/4R10/4R11) are

feed hold-offs which work in conjunction with the spark gaps (4SG6/4SG7/4SG9) in blocking any flash-over discharge energy from the amplifier transistors. It will be noticed that the collector of the final transistor of each pair is fed effectively from a potential divider (3R85/3R94 in the red channel for example). This enables the stage to be fed from the 200V supply rail.

A very important aspect of the design of primary-colour amplifiers is the need for high black-level stability. Poor black-level performance in monochrome receivers encourages the display of grey when black is being transmitted and depending on the nature of the signal leads to dark-key scenes dropping below the natural black level. Poor black-level stability in colour sets tends to alter the saturation of the colours. This is compensated to some extent when colour-difference drive is used because a black-level drift on the signal applied to the cathodes (i.e. the Y signal) has the opposite effect to a similar drift on the colour-difference signals applied to the grids. With primary-colour drive however the colour-difference and Y signals are matrixed prior to the tube and since only one electrode of each gun is modulated any drift tendency is emphasised. Receivers using primary-colour drive are more sensitive therefore to changes in d.c. level than their counterparts using colour-difference drive. For this reason, primary-colour drive receivers employ special circuits to hold a very stable d.c. black level reference both under conditions of changing picture information and long-term drift of parameters.

There are two factors involved. One is the d.c. level with respect to the operating point of the amplifier itself and the other the d.c. reference with respect to the black level of the signal. We can now return to the circuit in Fig. 3 to see how Rank-Bush-Murphy tackled the problems.

## Black-level Regulation

The scheme is based on the use of clipped pulses obtained from the line flyback pulses in the line output stage. These clipped pulses are a.c. coupled to a diode whose cathode is connected to the collector—and hence the picture tube cathode—of the primary-colour amplifier output transistor. It will be seen that there is a diode and an RC coupling circuit for each primary-colour amplifier. The coupling components for the red stage for example are 3R97/3C61 and the diode is 3D19. Now the clipping action is arranged to give the pulses an essentially rectangular form and a positive excursion which is equal to the required black level for the cathodes of the tube — 120V above chassis.

It will be seen that the base circuit of each primary-colour input transistor also receives the pulses

# STEPHENS

**ELECTRONICS,  
P.O. BOX 26,  
AYLESBURY, BUCKS.**

**SEND S.A.E. FOR LISTS  
GUARANTEE  
Satisfaction or money  
refunded.**

## GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE

**1 YEARS GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS**

A231 50p	ECF80/2 47p	EL803 85p	PC885 42p	PY83 50p	UL41 57p	6A85 32p	6EJ7 35p	6SK7 32p	12BB6 32p	30PL1 77p
A250 80p	ECF86 57p	EL821 55p	PC888 70p	PY88 41p	UL84 55p	6A86 32p	6EW6 32p	6SL7GT 32p	12BH7 32p	30PL13 90p
CB11 80p	ECH35 67p	EL830 75p	PC889 61p	PY500 £1.00	UM90/4 45p	6A85 35p	6F1 70p	6SN7GT 30p	12B7 30p	30PL14 85p
CB131 55p	ECH42 65p	EM34 80p	PC8189 81p	PZ30 80p	UY29 55p	6A7G 80p	6F8 40p	6SQ7 40p	12K3 50p	35A3 55p
CY31 35p	ECH81 51p	EM71 82p	PCF80 51p	QQU02-622-10 85p	UY85 34p	6A7G 45p	6F8G 25p	6SR7 37p	12J7GT 37p	35A5 65p
DAF91 41p	ECH83 40p	EM80 40p	PCF82 52p	QQU03-10 85p	U25 75p	6A6 29p	6F11 32p	6T8 32p	12Q7 25p	35B5 65p
DAF96 41p	ECH84 47p	EM81 42p	PCF84 47p	U26 75p	U26 75p	6A6 30p	6F12 22p	6U4GT 62p	12SG7 25p	35C5 35p
DF91 45p	ECL80 40p	EM84 37p	PCF86 61p	QV3-12 85p	U191 72p	6BA6 47p	6F13 35p	6U8 35p	12SG7 25p	35D5 65p
DF96 45p	ECL82 49p	EM87 55p	PCF200/1 81p	R19 80p	U193 41p	6BE6 40p	6F14 60p	6V6GT 32p	12SH7 25p	35L6GT 47p
DK91 57p	ECL83 57p	EN91 32p	PCF801 61p	R20 75p	U301 85p	6BH6 42p	6F15 55p	6X4 25p	12SJ7 25p	35V4 25p
DK96 57p	ECL86 46p	EY51 40p	PCF802 61p	SU2150A 75p	W729 55p	6F18 40p	6X5GT 27p	6Y3GT 40p	12SK7 40p	35Z3 55p
DL92 37p	ECL890 46p	EY80 45p	PCF805 65p	TT21 £2.40	Z759 £1.22	6BK7A 50p	6P22 32p	6X8 50p	12SL7GT 40p	35Z4G 25p
DL94 37p	EF39 £1.50	EY81 40p	PCF806 61p	TT22 £2.50	0A2 32p	6BL8 35p	6P23 77p	6Y6 80p	12SN7GT 40p	35Z5GT 37p
DL96 46p	EF39 52p	EY83 55p	PCF808 67p	U18/20 07p	0A3 45p	6BN5 42p	6P24 67p	6Y7 40p	12SQ7 40p	50A5 65p
DM70 32p	EF80 40p	EY86 40p	PCH200 70p	U20 67p	0B2 32p	6BN6 40p	6P25 75p	6B6 42p	12SR7 32p	50B5 35p
DY67/7 40p	EF83 50p	EY87 42p	PL82 51p	U25 75p	0B3 50p	6BQ5 25p	6P26 35p	10C2 50p	1487 80p	50C5 35p
DY92/2 45p	EF86 41p	EY88 42p	PCL83 61p	U26 75p	0C3 35p	6BR7 60p	6P28 70p	10D1 45p	50L6GT 40p	50P 90p
E55L £2.75	EF86 65p	EZ35 27p	PCL84 51p	U31 45p	0D3 32p	6BR8 65p	6P29 32p	10D2 40p	20L1 £1.00	50A2 37p
E88C 40p	EF89 40p	EZ40 45p	PCL85 52p	U37 £1.50	3Q4 40p	6BW6 82p	6P30 35p	10F1 90p	20P1 50p	50A2 37p
E130L £4.50	EF91 42p	EZ41 45p	PCL86 51p	U50 30p	384 35p	6BW7 65p	6J4 47p	10F9 50p	20P3 60p	90A £2.40
E180F 95p	EF92 50p	EZ80 27p	PD500 £1.52	U52 30p	3V4 30p	6BX6 25p	6J5GT 30p	10F18 40p	20P4 £1.00	90C1 80p
EABC80 52p	EF93 47p	EZ81 27p	PL200 74p	U76 25p	5R40Y 55p	6BZ6 32p	6J7 42p	10L1 40p	20P5 £1.00	90C2 £1.25
EA42 50p	EF94 77p	EZ90 25p	PL86 84p	U78 25p	5U4G 30p	6C4 30p	6K6GT 50p	10L11 55p	25C5 45p	807 47p
EBC33 55p	EF95 62p	GS10C £5.00	PL88 90p	U191 75p	5U4GB 37p	6C5GT 35p	6K7 32p	10P13 55p	25L6GT 37p	811A £1.50
EBC41 47p	EF183 55p	GY501 80p	PL81 51p	U201 35p	5V4G 40p	6CD6G £1.40	6K8G 30p	10P14 £1.00	25Z4Q 30p	612A £2.25
EBC81 32p	EF184 35p	GZ30 37p	PLA1A 62p	U281 40p	5Y3GT 30p	6CA4 27p	6K23 50p	12A5 50p	2526GT 80p	813 £2.75
EBC90 47p	E280F £2.10	GZ31 30p	PL82 38p	U282 40p	5Z3 45p	6CA7 52p	6K25 75p	12AC6 37p	30A5 40p	866A 70p
EBF86 40p	EF800 £1.00	GZ32 47p	PL83 61p	U301 57p	5Z4GT 40p	6CBC 27p	64GT 45p	12AD6 37p	30AF3 40p	866B 60p
EBF83 40p	EF804 £1.00	GZ33 60p	PL84 41p	U403 50p	6Z02 75p	6CDGGA £1.15	6L7 32p	12AE5 40p	30B13 55p	5642 70p
EBF89 40p	EF811 52p	GZ34 55p	PL500 82p	U404 37p	6A4 32p	6CQ7 45p	6L8 40p	12A15 40p	30C17 80p	6080 £1.37
EB91 26p	EL34 75p	HK90 32p	PL504 85p	U801 £1.00	6AF4A 47p	6CH6 55p	6LD20 32p	12AQ5 40p	30C18 75p	6146 £1.50
EC53 50p	EL36 47p	HL92 35p	PL505 £1.45	UABC80 52p	6AG7 37p	6CL6 60p	6N7GT 35p	12A76 25p	30F5 85p	6146B £2.37
EC86 60p	EL41 55p	HL94 40p	PL508 £1.00	UBF89 40p	6AH6 50p	6CW4 62p	6P1 60p	12A76 75p	30FL1 70p	6287 32p
EC88 60p	EL42 57p	KT86 £1.37	PL509 £1.84	UBC41 48p	6A18 28p	6CY5 40p	6P25 £1.05	12A76 35p	30FL2 92p	6360 £1.25
EC90 30p	EL43 50p	KT88 £1.66	PL892 85p	UCC85 46p	6AK5 30p	6C7 40p	6P28 62p	12A76 60p	30FL3 55p	6360 £1.25
EC92 32p	EL83 41p	N78 £1.05	PL805 86p	UCH42 48p	6AK6 57p	6D3 40p	6Q7 37p	12A77 45p	30FL4 77p	6399 £2.10
EC93 47p	EL85 42p	PAC80 40p	PY33 82p	UCH81 54p	6AL3 42p	6DC6 67p	6H7G 35p	12A7X 70p	30L1 45p	7199 75p
ECC81 40p	EL86 42p	PAB86 51p	PY80 32p	UCL82 51p	6AL5 16p	6DK6 42p	682 40p	12A7Y 67p	30L15 85p	7390 £1.80
ECC82/3 42p	EL90 32p	PC95 38p	PY81 41p	UCL83 81p	6AM5 25p	6DQ6B 60p	684A 55p	12BA4 50p	30L17 85p	7586 £1.25
ECC84/5 42p	EL91 25p	PC97 41p	PY800 41p	UP41/2 55p	6AM6 22p	6D94 75p	6847 37p	12BA6 32p	30P12 80p	7862 32p
ECC88 55p	EL92 35p	PC97 41p	PY801 41p	UF80/5 37p	6AQ5 32p	6E48 35p	68G7 37p	12BA7 32p	30P13 35p	9002 32p
E88C 62p	EL360 £1.15	PC84 46p	PY82 35p	UF89 41p	6AQ6 50p	6EH7 50p	6S7 37p	12BA7 32p	30P19 75p	9003 50p

### CATHODE RAY TUBES

New and Budget tubes made by the leading manufacturers. Guaranteed for 2 years. In the event of failure under guarantee, replacement is made without the usual time wasting forms.

Type	New	Budget	Type	New	Budget
MW36-20	£4.50	£4.50	A50-120W/R	CME2013 £10.95	£8.25
MW36-21	£4.50	£4.50	AW53-80	CME2101 £29.93	£26.25
MW43-69Z	CRM171 £8.60	£4.62	AW59-90	CME2203 £9.58	£7.20
MW43-80Z	CRM172 £8.60	£4.62	A59-15W	CME2301 £29.58	£7.20
AW43-80Z	CRM173 £8.60	£4.62	A59-11W	CME2305 £13.65	£10.97
	CME1702 £8.60	£4.62	A59-13W	CME2306 £13.65	£10.97
	CME1703 £8.60	£4.62	A59-16W	CME2306 £13.65	£10.97
	CME1706 £8.60	£4.62	A59-23W	CME2305 £12.60	£10.50
	C17AA £8.60	£4.62	A59-23W/R	CME2343 £13.60	£10.50
	C17AF £8.60	£4.62	A61-120W/R	CME2413 £13.60	£10.50
	CME1705 £8.60	£4.62	A65-11W	CME2501 £16.50	£14.50
AW43-88	CME1705 £8.60	£4.62	<b>COLOUR TUBES</b>		
AW47-90	A47 14W £5.95	£4.87	A49-191X	19 inch £52.50	
AW47-91	A47 14W £5.95	£4.87	A56-120X	22 inch £57.50	
A47 14W	CME1901 £5.95	£4.87	A63-11X	25 inch £62.50	
	CME1902 £5.95	£4.87	<b>PORTABLE SET TUBES</b>		
	CME1903 £5.95	£4.87	C19AH	£11.50	
	CME1905 £10.27	£8.50	T8D217	£11.50	
	CME1906 £8.86	£7.00	T8D282	£11.50	
	CME1907 £8.86	£7.00	A28-14W	Not supplied	
	CME1908 £7.75		CME1601	£7.75	
	CME1913R £9.33		CME1602	£8.00	

A discount of 10% is also given for the purchase of 3 or more tubes at any one time. All types of tubes in stock. Carriage and insurance 75p anywhere in Britain.

### TRANSISTORISED UHF TUNER UNITS

NEW AND GUARANTEED FOR 3 MONTHS

Complete with Aerial Socket and wires for Radio and Allied TV sets but can be used for most makes.

Continuous Tuning, £4.50; Push Button, £5.00.

### SERVICE AIDS

Switch Cleaner, 55p; Switch Cleaner with Lubricant, 55p; Freeze 62p. P. & p. 77p per item.

### PLUGS

Jack Plugs and Sockets £19p  
Standard Plugs 12p  
Standard Sockets 12p

Co-Axial Plugs  
Bellong Lee (or similar type) 61p  
Add 2p per doz. p. & p.

### LINE OUTPUT TRANSFORMERS

G.E.C. BT454	£4.75	G.E.C. 2028	£4.75
G.E.C. BT456	£4.75	G.E.C. 2041	£4.75
G.E.C. 2010	£4.75	G.E.C. 2000 Series	£4.75
G.E.C. 2013	£4.75	Phillips 19TG	£4.75
G.E.C. 2014	£4.75	Pye Mod. 36	£4.75
G.E.C. 2018	£4.75	Pye Mod. 40	£4.75
G.E.C. 2043	£4.75	Thorn 800-850	£4.75
G.E.C. 2048	£4.75		

### STYLI—BRITISH MANUFACTURED

All types in stock.			
Single Tip "S"	13p	Double Tip "S"	33p
Single Tip "D"	37p	Double Tip "D"	47p
"S" = Sapphire		"D" = Diamond	

## CARTRIDGES

Inc. P.T. each	B.B.B.	Inc. P.T. each	ROHETTE	Inc. P.T. each
GP79	£1.06 3X8	8/8	106	8/8
GP91-18c	£1.06 3X8	8/8	106	8/8
GP91-28c	£1.06 3X8	8/8	DC400	8/8
GP91-38c	£1.06 3X8	8/8	DC4008C	8/8
Available to replace TC3	£1.06 3X8	8/8	£1.11 106	D/8
GP92	£1.26 3X8H	8/8	£1.11 106	D/8
GP93-1	£1.26 3X8H	D/8	DC400	D/8
GP94-1	£1.56 3X8H	D/8	DC4008C	D/8
GP94-5	£1.90 3X8H	D/8	£1.96	
GP95	£1.24 GOLDRING			
GP96	£1.57 860			
GC05	8800	£5.25	8TA	D/8
	GC00E	£1.20	9TA	D/8
	GC800 Super E	£10.50	9TARC	D/8

SEMICONDUCTORS BRAND NEW MANUFACTURERS MARKINGS NO REMARKED DEVICES					
2N385A 63p	3N3704 23p	AF116 25p	BC118 23p	BF115 25p	TI343 40p
SN697 20p	SN3705 20p	AF117 20p	BC134 55p	BF117 48p	
2N698 25p	SN4061 23p	AF118 20p	BC135 P/A	BF163 35p	DIODES &
SN706 13p	SN4062 23p	AF124 13p	BC136 P/A	BF167 25p	RECTIFIERS
SN706A 13p	SN4286 18p	AF125 20p	BC137 P/A	BF173 33p	1N914 8p
SN930 28p	SN4291 15p	AF128 20p	BC138 P/A	BF178 33p	1N915 10p
SN1132 13p	RCA	AF127 18p	BC142 30p	BF179 75p	BA102 23p
SN1303 18p	402538 P/A	AF129 38p	BC143 P/A	BF180 75p	BA115 23p
SN1305 23p	40398 P/A	AF128 45p	BC147 18p	BF181 33p	BA114 13p
SN1306 25p	40438 P/A	AF129 45p	BC148 15p	BF184 25p	BY100 23p
SN1307 25p	AC107 30p	AF180 53p	BC149 18p	BF191 23p	BY125 20p
SN1610 58p	AC118 60p	AF181 43p	BC152 15p	BF195 47p	BY127 23p
SN3826 30p	AC126				

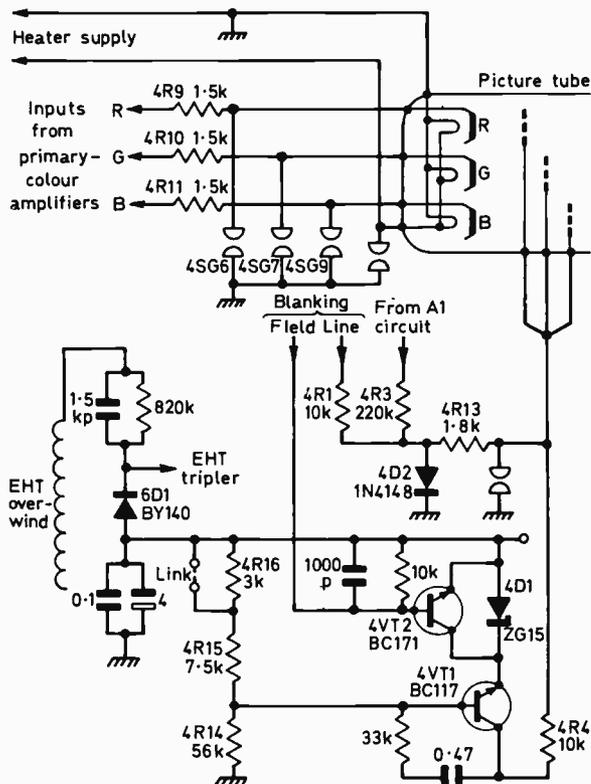


Fig. 1: The picture tube grid clamping, beam current limiting and line and field flyback blanking arrangements.

(through 3R82 and 3R73 in the red channel). Each input transistor however passes a fairly high current because of the other resistor in the base potential-divider arm which is returned to the 18V rail (3R76 in the red channel). Since the emitter of the input transistor is d.c. coupled to the base of the second transistor, the collector current of the latter is controlled by the base current of the former and under no-signal conditions the collector current of the second transistor is thus fairly high. A substantial voltage is thus dropped across the collector load (3R85 in the red channel) and if it is assumed for a moment for the sake of description that the lower circuit of the base potential-divider of the input transistor (3R82/3R73 in the red channel) is open-circuit then the potential at the collector of the second transistor of each pair would be about 30V relative to chassis. The subsequent description relates to the red channel but the other two channels work in exactly the same way.

The cathode of 3D19 is thus at 30V positive which means that between pulses it is non-conducting. It is turned on each time a pulse occurs however because the pulse amplitude (120V) at the anode over-rides the positive cathode voltage. The result of this is that the coupling capacitor 3C61 charges negatively. The charge is conveyed to 3C55 through 3R82, this capacitor thus also charging negatively and counteracting a portion of the forward bias at 3VT12 base applied by 3R76. The result is that 3VT15 collector current falls causing its collector voltage to rise.

On succeeding pulses the same process occurs but with each pulse more charge is added to that already

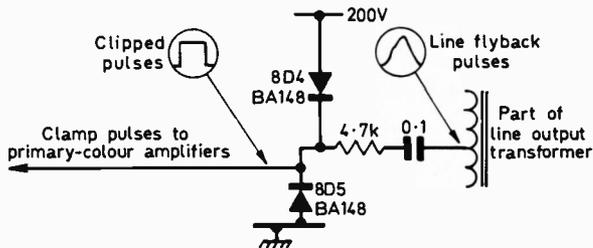


Fig. 2: Method by which the clamping pulses are obtained by clipping the line flyback pulses.

in 3C55 until eventually after a few lines 3VT15 collector potential rises to that of the pulse amplitude (120V) which corresponds to the black-level voltage. The degree of 3D19 conduction during all subsequent pulses is very small and corresponds to that required to maintain a steady charge in 3C55.

### Stability

The stability of this circuit is very high (better than 1 per cent) because with the feedback arrangement between 3VT15 collector and 3VT12 base, coupled with the loop gain of the d.c. coupled stage (about 50), only a small change in 3VT12 base bias conditions is required to reflect a larger change at 3VT15 collector. Thus even very small departures from black level are corrected. The heavy effective negative feedback occurring during the period of the pulses acts as a very efficient d.c. stabilising system without inhibiting the gain during the lines of the picture—since during these periods there are no pulses and hence no feedback! The pulses which operate the circuit are timed to occur during the back porch periods and the circuit from which the pulses are derived is shown in Fig. 2.

Because the cathodes of the picture tube receive the drive signals the primary-colour signals are negative-going on picture information and positive-going on sync, relative to the black level. The black level is established by the flyback pulses during the black-level porches and the clamp diodes will fail to conduct when the sync pulses are present because these represent a *positive-going* signal at the cathodes of the clamp diodes. The sync pulses thus tend to hold the clamp diodes away from the conducting level.

### Gain and Bandwidth Characteristics

To conclude this discourse on primary-colour drivers it is worth noting that in addition to having stable black-level regulation each amplifier must have balanced gain stability and balanced bandwidth. Owing to spreads in transistor parameters the gain should as far as possible be tied to the passive circuit components rather than to the active devices. The same applies to bandwidth consistency. If the bandwidth of one of the primary-colour channels is wider than that of the others the signal will pass through this one more quickly and horizontal colour fringing will occur at points on the picture corresponding to sharp changes in signal level.

In Fig. 3 the network 3C58/3R91 across the second transistor's emitter resistor increases the gain at high frequencies (because the reactance of the capacitor falls as the frequency increases, thereby reducing the total impedance and hence the current feedback in the

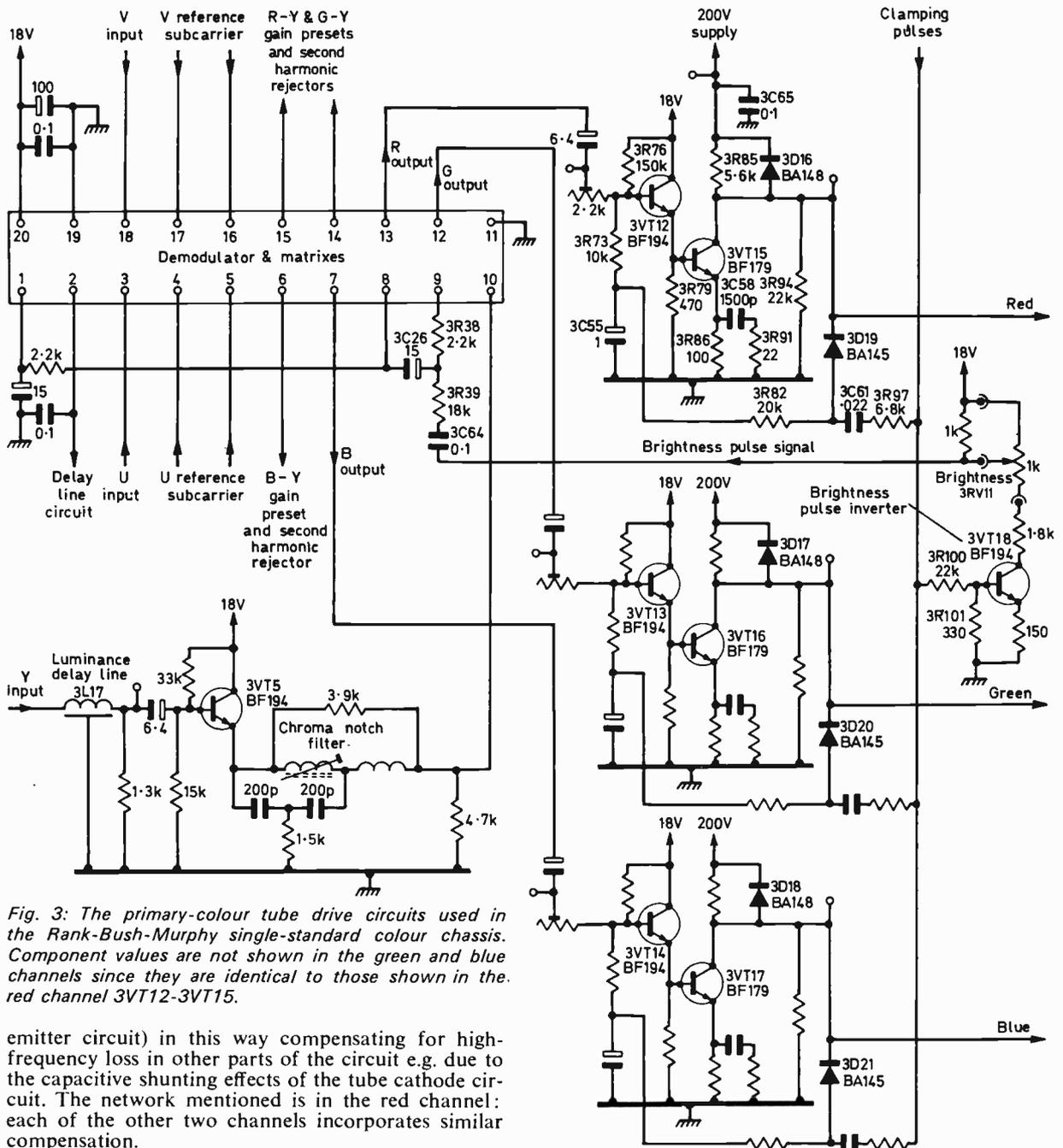


Fig. 3: The primary-colour tube drive circuits used in the Rank-Bush-Murphy single-standard colour chassis. Component values are not shown in the green and blue channels since they are identical to those shown in the red channel 3VT12-3VT15.

emitter circuit) in this way compensating for high-frequency loss in other parts of the circuit e.g. due to the capacitive shunting effects of the tube cathode circuit. The network mentioned is in the red channel: each of the other two channels incorporates similar compensation.

### Brightness Control

The brightness control works in conjunction with the black-level clamping system. It will be seen (Fig. 3) that the clipped clamping pulses are also fed to 3VT18 base via the potential-divider 3R100/3R101. The collector of this transistor is loaded in part by the brightness control 3RV11 and the pulses appear across this in inverted form after being phase reversed by the transistor. From the slider of the brightness control the pulses are fed through 3C64/3R39/3C26 to pin 8 of the i.c. in which they are mixed with the decoded signal. Since the primary-colour clamping pulses and these "brightness" pulses coincide, the

setting of the brightness control which adjusts the amplitude of the inverted pulses fed to the i.c. determines the nominal black-level potential to which the primary-colour stages are clamped and hence the brightness of the picture.

The remainder of the picture-tube circuit relating to the modulation electrodes is shown in Fig. 1. The three grids are connected together and clamped to chassis by reason of the steady 700 $\mu$ A of bleed current which flows through 4R3 and diode 4D2 from the first anode circuit which is energised from the boost h.t. supply. 4D2 is thus held heavily conducting and presents a low impedance to chassis thereby ensuring

—continued on page 512





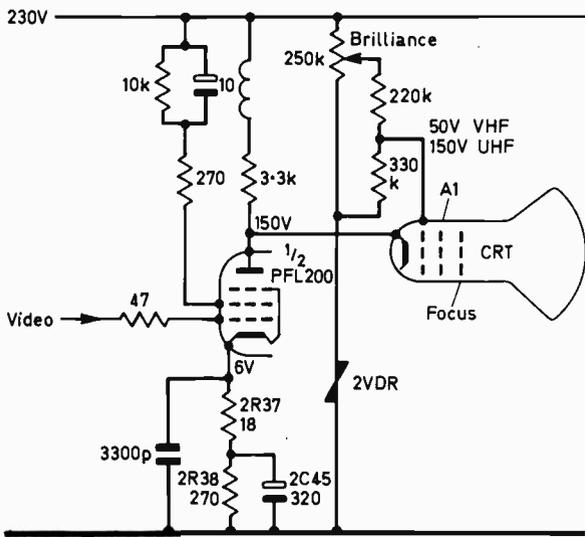


Fig. 4: Video output stage used in the Bush-Murphy TV161U-V1910U series. 2VDR provides switch-off spot suppression: as the h.t. falls on switch-off its resistance rapidly falls thereby quickly reducing the c.r.t. grid voltage.

found this valve and nearby feed resistors severely over-heating. A replacement valve produced similar results and also over-heated quickly. On making voltage tests at the cathode we obtained only a marginal meter deflection instead of the normal 6V. A resistance test then indicated slightly over 20Ω to chassis instead of the normal 288Ω formed by the series resistors 2R37 and 2R38. Reference to the circuit showed that the only cause of the low reading could be a short-circuit in 2C45, the 320µF capacitor decoupling 2R38, leaving 2R37 (18Ω) as the sole cathode resistor. Replacing this electrolytic restored a normal picture but it was found necessary to change the two screen feed resistors and the anode load resistor as they were all discoloured and slightly reduced in value.

The weak contrast had been caused by negligible bias on the video pentode while inability to reduce the brightness normally was due to the valve's anode voltage and therefore the c.r.t. cathode voltage being abnormally low.

TO BE CONTINUED

## COLOUR RECEIVER CIRCUITS

—continued from page 509

the correct black-level operation relative to the drive signals at the cathodes.

### Beam Limiting

Beam-limiting control is applied to the grids via 4VT1. The base of this transistor receives a negative control voltage, derived from diode 6D1 which rectifies sample line output stage signal, via the potentiometer network 4R14/4R15/4R16. Under low beam current conditions the transistor is non-conducting due to the biasing. With increasing beam current however the negative base bias decreases turning on increasing 4VT1 collector current which flows via 4R13/4R4 and the bleed network. Since 4VT1 collector current flows in opposition to the bleed current there comes a time when 4VT1 current predominates. This switches off 4D2 and causes the grids to go negative, thereby automatically pulling back the beam current.

The circuit component values are arranged for 4VT1 current to cancel the bleed current when the beam current exceeds 1mA in 19 in. models. In the 22 and 25 in. models the base potential-divider resistor 4R16 is shorted out by a link and the changeover point then occurs at 1.5mA beam current.

### Flyback Blanking

The picture tube grids also receive the flyback blanking pulses. Field blanking utilises 4VT2. Positive-going flyback pulses from the field timebase are fed to the base of this transistor, causing heavy conduction. During the pulse periods therefore 4VT2 collector-emitter impedance is very low so that the zener diode 4D1 is virtually shorted across. Since this diode is in 4VT1 emitter circuit the current through this transistor rises sharply and the resulting negative-going pulses at its collector are communicated to the grids of the tube thereby cutting the tube off during the flyback period.

The line blanking is less complicated: negative-going pulses from the line output transformer are fed through 4R1/4R13 direct to the grids, resulting in the same sort of blanking action.

NEXT MONTH: PAL CODING AND DECODING

## TV TEST REPORT

—continued from page 491

the nature of the work. These figures were noted with the older 40W irons.

An advantage with all low-voltage irons is their rapid warming up time. The Weller TCP1 is ready to solder less than 25 seconds after plugging in. Heat recovery time is also very fast and solder can be made to run freely on a chassis even with the 700-degree bit. It thus does the job of both a normal instrument iron and a heavy-duty one. Most low-voltage irons have a spring-loaded trigger or switch so that continual pressure is needed when soldering. This can be very tiring and it is not always easy to judge the right temperature for the job. The automatic control on this iron takes the fatigue and guesswork out of low-voltage iron soldering.

Care must be taken when unsoldering components not to use the bit to unpick joints or lever back bent-over terminal tags as this may damage the protective coating and so greatly shorten its life.

The overall length of the iron is 8in. and the distance from bit tip to handle just 3in. This is rather short for some applications and I would have liked at least another inch on the barrel length. The many good features however outweigh these minor disadvantages and make this a worthwhile addition to the equipment of any workshop and indeed a useful tool for the home constructor.

Prices are £5.50 for the iron alone with 4ft. of mains cable and £6.10 for one with an 8ft. cable. The combined price of iron, 4ft. cable and transformer is £11.10. The instrument is made in Canada and the UK distributors are Weller Electric Corporation, Horsham, Sussex.

# NEW LINE OUTPUT TRANSFORMERS

**ALBA** 655, 656, 717, 721 £3-75, 890-895, 1090, 1135, 1195, 1235, 1395, 1435 £5-00.

**ARGOSY**, 17K10, 17K11, 17K12, 17K14, 19K17, 17K43 £4-00.

**BAIRD**. All models price £5-90. From model 600 quote part no. normally found on TX base plate.

**BUSH** TV53 to TUG69 £2-00, TV91 to TV139 £4-75. (From Model TV123 an alternative Square Tag Panel was fitted on Main Bobbin, please state if required.) TV141 to TV176 please state part number £4-50, TV75 to TV86 14-75 (except TV80).

**COSSOR** 904 to 957 Rewind £4-50, CT1700U to CT2378A £5-00.

**DECCA** DM1, DM3C (90°), DM4C (70°), DR1, DR2, DR121 £4-50, DR95, DR100, DR101, DR202, DR303, DR404, DR505, DR606 £4-50.

**DEFIANT** 7P20 to 7609. Prices on request.

**DYNATRON** TV30, TV35, TV36, TV37, TV38, TV39, TV40, TV41, etc £4-00.

**EKCO** T231, T284, TC267, T283, T293, T311, T326, T327, T330, TMB272, T344, T344F, T345, TP347, T348, T348F, TC347, TC349, TC356, T368, T370, TC369, T371, T372, TP373, TC374, T377A, T393, T394, 433, 434, 435, 436, 437 all at £4-00, 503, 504, 505 506 £4-75.

**FERGUSON** 306T, 308T, 406T, 408T, 416, 436, 438, 506, 508, 516, 518, 536, 546, 604, 606, 608, 616, 619, 636, 646, 648, 725, 726, 727, 3600, 3601, 3602, 3604, 3611, 3612, 3614, 3617, 3618, 3619, 3620, 3621, 3622, 3623, 3624, 3625, 3626, 3627, 3629 £4-00. Jelly Pots: please state colour: red, black or white.

**FERRANTI** T1001, T1002, T1002/1, T1004, T1005, T1023, T1024, T1027, T1027F, TP1026, T1071, T1072, T1121, TC1122, TC1124, T1125, TC1126 £4-00, 1154, 1155 £4-75.

**G.E.C.** BT302, BT342 £3-50, BT454DST-456DST, 2012, 2013, 2014, 2012, 2000DS, 2001DS, 2002DS £4-50.

**H.M.V.** 1865, 1869, 1870, 1872, 1874, 1876, 1890, 1892, 1894, 1896. All models to 2645 £4-00.

**KB** OV30, NF70, NV40, PV40, QV10, QV30, RV10, RV20, RV30, PVP20 £4-50. Featherlight £4-50. Chassis No. VC1-VC2-VC3-VC4 £4-50.

**MASTERADIO** 4013 DST, D500 DST, D507 DST £4-50.

**MARCONI** VT153, VT155, VT156, VT157, VT159, VT161, VT163, VT165, VT170, 4611, 4800, 4801, 4803, 4615 £4-00.

**MURPHY** V310 to 929 £4-75.

**PAM** 600S to 5106 £4-00.

**PETO SCOTT**. Prices on request.

**PHILCO** 1019, 1020, 2021 £4-13, 1029, 1030, 1035, 1036, 1040, 1050, 1060 £4-13.

**PHILIPS** 11TG190 to 24T301 £5-00, 1768U to 2196U. Rewind £4-75 (old unit required).

**PILOT** PT450, 452, 455, 650, PT651, P60A, P61 £4-00.

**PYE** V200, V400, 200LB, 210, 220, 300F, 300S, 310, 210S, 410, 510, 530, 600, 620, 630, 700 A or D, 710 A or D, 830 A or D or LBA £4-00, 11U Series, 11U-P/NO, AL21003, 21F to 61. Part Nos must be given when ordering Pye LOPTS £4-00.

**REGENTONE** 197-198, 298, TV402, TV401, TV501, TV502 £4-50, 10-4-10-6 10-21 17-18, 10-12, 191-192 £4-00.

**R.G.D.** 626, 627, 628, 726, RV202, RV302 £4-50, 519-619-620-621C, 723 £4-00.

**SOBELL** 1000DS, 1002DS, 1005DS, 1010DST, 1012, 1013, 1014, 1018, 1019, 1020, 1021, 1032, 1033, 1038, 1039 £4-50.

**STELLA** T1011U to 2149A £5-00.

**ULTRA** 1770, 2170, 1772, 1782, 2172, 1771, 2171, 1775, 2175, 1774, 2174, 1773, 2137, 1980c, 1984c, 100c, 200c, 2380, 2384, 1984, 1985, 1986, 1980, 1980a, 1780, 2180, 2181, 2183, 2182, 1871, 1783, 6600, 6625, 6626, 6628, 6632, 6642 etc. £4-00.

We can rewind most LOPT £4-75.

*Post and Packing 26p. C.O.D. 30p extra.*

## LINE OUTPUT TRANSFORMER INSERTS ONLY

**BUSH** TV92-TV93, TV94-TV95-TV96-TV97, TV98, TV100, TV101, TV103, TV104, TV105, TV106, TV108, TV109, TV110, TV113, TV115, TV115R, TV115c, 123, 125, 128 £2-75. Complete with heater windings. TV75, TV85 £2-75.

**DECCA** DR95, DR101, DR202, DR303, DR404, DR505, DR606 £2-75.

## RETURN OF POST SERVICE ON ALL STOCK ITEMS

CALLERS WELCOME. But to avoid disappointment please phone to check that the items you require are in stock.

All new components inserts are guaranteed for three months from the date of invoice subject to the breakdown being due to faulty manufacture or materials. S.A.E. all enquiries.

**Dept. "R" D.&B. TELEVISION (WIMBLEDON) LTD.  
80 MERTON HIGH STREET, S.W.19 01-540 3513**

# BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1  
THE VALVE SPECIALISTS Telephone 01-722-9000

0A2	0.30	6AX4	0.39	6B7GT	0.38	10P14	1.10	30C1	0.28	1821	0.63	DK96	0.35
0B2	0.30	6BBG	0.13	6K7G	0.10	12A6	0.48	30C2	0.60	5702	0.80	DL32	0.37
0Z4	0.23	6BA6	0.20	6K7GT	0.23	12AC6	0.40	30C17	0.77	5763	0.50	DL92	0.25
1A3	0.23	6BC8	0.50	6K8G	0.16	12AD6	0.60	30C18	0.60	6060	0.30	DL94	0.32
1A5	0.25	6BE6	0.21	6L1	0.98	12AE6	0.48	30F5	0.70	7193	0.53	DL96	0.35
1A7GT	0.33	6BH6	0.43	6L6GT	0.39	12AT6	0.53	30FL1	0.60	7475	0.70	DM70	0.30
1B3GT	0.37	6B96	0.39	6L7	0.53	12AT7	0.16	30FL2	0.60	A134	1.40	DM71	0.38
1D5	0.38	6BQ5	0.22	6L8	0.45	12AU6	0.21	30FL12	0.70	A2134	0.98	DM74	0.30
1D6	0.48	6BQ7A	0.38	6L19	1.38	12AU7	0.10	30FL14	0.68	A3042	0.75	DM75	0.38
1FD1	0.35	6BR7	0.79	6LD20	0.48	12AV6	0.28	30L1	0.29	ACO44	1.16	DY87/6	0.25
1G6	0.30	6BR8	0.63	6N7GT	0.40	12AX7	0.22	30L15	0.68	AC2/PEN		DY89/2	0.37
1H5GT	0.33	6BR7	1.25	6P28	0.59	12AY7	0.68	30L17	0.69			E80F	0.98
1L4	0.13	6BW6	0.72	6Q7	0.43	12B46	0.30	30P4M	0.95	AC6PEN		E83F	1.20
1LD5	0.30	6BW7	0.55	6Q7G	0.27	12B65	0.30	30P12	0.69			E86CC	0.60
1LN5	0.40	6BZ6	0.31	6R7	0.55	12BH7	0.27	30P16	0.30	AC2/PEN/		E92CC	0.40
1NSGT	0.37	6C6	0.19	6R7G	0.85	12E1	0.85	30P19/		DD		E180F	0.90
1R5	0.27	6C9	0.73	6SA7GT	0.35	12J7GT	0.33	30P4	0.58	AC/PEN(7)		E182CC1	1.13
1R4	0.22	6C17	0.63	6SA7	0.35	12K5	0.50	30P11	0.59			E1148	0.58
1R5	0.20	6CB6A	0.28	6SCTG70	0.33	12K7GT	0.34	30P13	0.75	AC/THIO50		EA30	0.13
1U4	0.29	6CD6G	1.08	6SNG7GT	0.38	12Q7GT	0.28	30P14	0.65	AC/TP		EA76	0.88
1U5	0.48	6C08A	0.60	6SH7	0.53	12SA7GT		30P15	0.69	AD60	0.78	EACB90	0.30
2D21	0.35	6C16	0.36	6S7	0.35	6SA3	0.50	AR3	0.35	ATP4	0.12	EAF42	0.48
3A7	0.20	6C16A	0.43	6SK7GT	0.23	12S2C	0.35	35A5	0.75	AZ1	0.40	EB34	0.20
3B7	0.25	6CL8A	0.50	6SQTGT	0.38	12S2G	0.23	35D5	0.70	AZ1	0.40	EB34	0.20
3D6	0.19	6C05	0.50	6U4GT	0.60	12S2H	0.15	35L6GT	0.42	AZ31	0.46	EB91	0.11
3Q4	0.38	6CW4	0.63	6U7G	0.53	12S2J	0.23	35W4	0.23	AZ41	0.53	EB41	0.48
3Q5GT	0.35	6D6	0.15	6V6G	0.17	12S2K	0.24	35Z3	0.50	B36	0.33	EB21	0.33
3R4	0.27	6D7	0.50	6V6GT	0.31	12S2QGT		35Z4GT	0.24	CL33	0.90	EB29	0.30
3V4	0.38	6D76A	0.50	6X4	0.20		0.50	35Z5GT	0.30	CY6	0.63	EB21	0.30
3R4GY	0.53	6E16	0.55	6X5GT	0.25	1A47	0.48	50B5	0.35	CY1C	0.63	EBF80	0.30
5V4G	0.35	6F1	0.59	6Y6G	0.55	1A87	1.15	50C5	0.32	CY31	0.31	EBF83	0.38
5Y3GT	0.28	6F6	0.63	6Y7G	0.63	19A05	0.24	50C6D62	1.17	D63	0.25	EBF89	0.27
5Z3	0.45	6F6G	0.25	7B6	0.58	19G9	1.45	50E15	0.55	DAC32	0.38	EBL21	0.60
5Z4G	0.35	6F13	0.33	7B7	0.35	19H1	2.00	50L6GT	0.45	DAF91	0.20	EC54	0.50
6P00L2	0.55	6F14	0.43	7C6	0.30	20D1	0.65	50P1	0.35	DAF96	0.33	EC86	0.63
6A0C	0.33	6F15	0.65	7F8	0.88	20D4	1.05	85A2	0.43	DD4	0.53	EC88	0.60
6AC7	0.15	6F18	0.45	7H7	0.28	20F2	0.65	85A3	0.40	DF33	0.37	EC90	0.25
6AG5	0.25	6F23	0.68	7R7	0.65	20L1	0.98	90A0	3.38	DF91	0.14	EC92	0.35
6AK5	0.25	6F24	0.68	7V7	0.25	20P1	0.88	90A3	3.38	DF96	0.33	EC93	1.50
6AK6	0.30	6F25	0.58	7Z4	0.30	20P3	0.82	90CC	1.70	DF97	0.63	EC93	1.50
6AM6	0.17	6F28	0.70	9B3W				90CV	1.65	DH33	0.27	EC94	0.80
6AMA	0.50	6F32	0.15	917	0.75	20P3	1.00	90C1	0.69	DH76	0.28	EL34	0.48
6AN8	0.49	6G18A	0.50	10C1	1.25	25A6G	0.29	150B2	0.58	DH77	0.18	EL35	1.00
6AQ5	0.22	6G07	0.50	10C2	0.50	25L6G	0.22	301	1.00	DH81	0.58	EL35	1.00
6AR6	1.00	6H6GT	0.15	10D7	0.50	25Y5	0.38	302	0.83	DH107	0.90		
6AT6	0.18	6J5G	0.19	10F9	0.45	25Y5G	0.43	303	0.75	DK32	0.33		
6AU6	0.20	6J5GT	0.29	10F18	0.35	25Z4G	0.30	305	0.65	DK40	0.55		
6AV6	0.30	6J6	0.15	10LD11	0.53	25Z5	0.40	306	0.65	DK91	0.27		
6AW8A	0.54	6J7G	0.24	10P13	0.54	25Z6GT	0.43	807	0.58	DK92	0.38		

ECC81	0.16	EL37	0.87	IW4/350	0.38	PCL83	0.58	Q875/20		UR1C	0.53
ECC82	0.18	EL41	0.53	IW4/500	0.38	PCL84	0.34	Q895/11	0.63	U9	0.58
ECC83	0.20	EL42	0.54	KT2	0.75	PCL85	0.38	Q895/11	0.49	U19	0.40
ECC84	0.28	EL81	0.50	KT8	1.75	85	0.41	Q8150/15	0.63	U21	0.55
ECC85	0.25	EL83	0.38	KT41	0.98	PCL86	0.38	QV04/70	0.63	UY1N	0.50
ECC86	0.40	EL84	0.22	KT44	1.00	PCL88	0.65			UY21	0.55
ECC88	0.35	EL85	0.40	KT63	0.25	PCL8000	0.75			UY41	0.38
ECC189	0.48	EL86	0.38	KT66	0.80	PCL8010	0.59			UY85	0.25
ECC804	0.55	EL91	0.23	KT74	0.63	PCL8010	0.59			R10	0.45
ECC807	0.20	EL93	0.24	KT76	0.63	PCL805	0.38			R11	0.98
ECF90	0.27	EM34	0.90	KT81	2.00	PEN45	1.38			R12	0.75
ECF92	0.27	EM80	0.38	KT88	1.70	PEN45	0.35			R17	0.68
ECF96	0.65	EM81	0.39	KTW610	0.63	PEN48	0.75			R18	0.50
ECF9042	1.00	EM83	0.75	KTW620	0.63	PEN48	0.20			R19	0.30
ECH21	0.63	EM84	0.31	KTW630	0.63	PEN48	0.20			R20	0.56
ECH42	0.61	EM87	0.35	M162	0.63	PEN48	0.20			R22	0.35
ECH81	0.27	EY51	0.33	M14000	0.74	PEN48	0.20			RG1/204	0.25
ECH83	0.39	EY81	0.35	MHLA	0.75	PEN48	0.20			R26	1.98
ECH84	0.34	EY83	0.55	N78	2.05	PEN48	0.20			RK34	0.38
ECL80	0.30	EY84	0.60	N108	1.40	PEN48	0.20			SP42	0.75
ECL82	0.30	EY87/6	0.30	N308	0.95	PEN48	0.20			SP61	0.33
ECL83	0.52	EY88	0.43	N399	0.44	PEN48	0.20			TH4B	0.50
ECL84	0.55	EY91	0.53	N359	0.44	PEN48	0.20			TH233	0.98
ECL85	0.55	EZ35	0.25	P61	0.48	PEN48	0.20			TFB20	0.98
ECL86	0.36	EZ40	0.40	PABC80	0.33	PEN48	0.20			UAB30	0.49
EEL80	0.70	EZ41	0.42	PC86	0.48	PEN48	0.20			UAB30	0.49
EZ22	0.63	EZ80	0.21	PC88	0.48	PEN48	0.20			UAF42	0.49
EZ81	0.22	EZ85	0.53	PC88	0.48	PEN48	0.20			UBC91	0.40
EZ90	0.20	PC97	0.38	PC89	0.45	PEN48	0.20			UBC91	0.40
FW4/500		PC90	0.34	PC89	0.45	PEN48	0.20			UHF80	0.29
FW4/800		PC85	0.28	PC88	0.48	PEN48	0.20			UHF89	0.30
GZ30	0.35	PC89	0.45	PC88	0.48	PEN48	0.20			UBL21	0.55
GZ32	0.41	PC8189	0.48	PC89	0.45	PEN48	0.20			UC92	0.35
GZ33	0.70	PC8050	0.58	PC89	0.45	PEN48	0.20			UCC84	0.34
GZ34	0.48	PC8060	0.60	PC89	0.45	PEN48	0.20			UCC84	0.34
GZ37	0.75	PC8090	0.28	PC89	0.45	PEN48	0.20			UCC84	0.34
HABC80		PC8090	0.28	PC89	0.45	PEN48	0.20			UCC84	0.34
HL23DD		PC8090	0.28	PC89	0.45	PEN48	0.20			UCF80	0.34
HL41DD		PC8090	0.28	PC89	0.45	PEN48	0.20			UCF80	0.34
HL42DD		PC8090	0.28	PC89	0.45	PEN48	0.20			UCF80	0.34
HN309		PC8090	0.28	PC89	0.45	PEN48	0.20			UCF80	0.34
HVR2	0.18	PC8090	0.28	PC89	0.45	PEN48	0.20			UCF80	0.34
HVR2A053		PC8090	0.28	PC89	0.45	PEN48	0.20			UCF80	0.34
IW3	0.38	PCL82	0.33	PC89	0.45	PEN48	0.20			UCF80	0.34

All valves are unused, boxed, and subject to the standard 90-day guarantee. Terms of business: — Cash or cheque with order only. Post/packing 0.03 per item, subject to a minimum of 0.09. Orders over 5.00 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 0.03 extra per order. Complete catalogue with conditions of sale price 0.07 post paid. Business hours Mon. - Fri. 9.5-3.30 p.m. Sat. 9-1 p.m. We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for a reply.



## EX RENTAL TV's

19" — £29.95  
23" — £39.95

All Channels 405/625  
2 Years Guarantee.  
Free List by return.

19" Slim line TV's £14.95. Guaranteed 2 years. Send for List. Carr. & Ins. all sets £1.95. Daily demonstrations to personal shoppers.

### TEAK HI-FI STEREO CABINETS £14.95

Brand New 44" wide x 16" deep x 18" high with Legs. A superb piece of furniture. Carr. £1.00

Transistor Gang Condensers 30p, Miniature AM, post 5p, Precision Tape Motors £1.95. 200/200V, post 20p.

### TRANSISTOR Radio Cases: 25p each.

Size 9 1/2" x 6 1/2" x 3 1/2" P. & P. 15p.  
SPEAKERS 50p 25 802 BRAND NEW P & P. 5p.

### TRANSISTORS Post Free

AC 126	AF 179	OC 81
AC 128		OC 81D
AF 114	OC 45	
AF 117	OC 71	15p each

### POTENTIOMETERS 23p each

Double & Switched	500 KΩ 500 KΩ	3 1/2" shaft
Double & Switched	500 KΩ 100 KΩ	2" shaft
Double & Switched	1 MEG 100 KΩ	1 1/2" shaft

Post. & Pack. 5p. — 4 for 10p

### KNOBS 100,000 to clear (Brand New)

100 assorted Radio & T.V. knobs  
50p. Postage 25p.

# LONG-DISTANCE TELEVISION

## ROGER BUNNEY

THE excellent conditions experienced during May have largely continued into June except for a short lull at the beginning of the month. It certainly looks as though this year will have one of the best Sporadic E seasons for possibly seven years and we have every reason to think that conditions will remain active for some time yet! In view of the amount of reception logged here I will limit my report as last month to periods of sustained Sporadic E only.

- 1/6/71 TVP (Poland) R1, R2; ORF (Austria) E2a; DFF (East Germany) E3, E4.
- 2/6/71 RAI (Italy) IA, IB; TVE (Spain) E2, E3, E4; NRK (Norway) E2, E3.
- 5/6/71 Switzerland E2; TVE E2.
- 6/6/71 TVP R1, R3; USSR R2; MT (Hungary) R1, R2; RAI IA, IB; JRT (Yugoslavia) E3, E4; ORF E2a, E4; WG (West Germany) E2; ORTF (France) F2; plus unidentified signals.
- 7/6/71 TVE E2; JRT E3; plus unidentified signals.
- 9/6/71 NRK E2 (twice), E3.
- 13/6/71 DFF E4; TVE E2, E3, E4; JRT E3, E4; RAI IA, IB; Switzerland E3; plus unidentified signals.
- 14/6/71 TVE E2, E3, E4; RAI IA, IB; ORTF F2, F4.
- 15/6/71 SR (Sweden) E2; NRK E2; Denmark E3, E4; RTP (Portugal) E2, E3; RAI IA; ORTF F2, F4; CT (Czechoslovakia) R1; TVP R1, R2; plus unidentified signals.
- 16/6/71 USSR R1, R2; DFF E3; NRK E2, E3; RAI IA; TVE E2, E3, E4; RTP E3; plus unidentified signals.
- 17/6/71 RTP E2, E3; TVE E2, E3, E4; RAI IA; MT R1; TVP R1.
- 18/6/71 USSR R1 (twice), R2; CT R1; TVP R2; DFF E4; NRK E2; RAI IA; ORTF F2, F4.
- 19/6/71 TVE E2, E3, E4; RTP E3; RAI IA; Switzerland E3; WG E2; JRT E3, E4, TVP R1.
- 20/6/71 USSR R1; CT R1 (twice), R2; WG E2; JRT E3 (twice), E4; RAI IA; RTP E2, E3; MT R1, R2.
- 21/6/71 ORF E2a; RAI IA; ORTF F2; plus unidentified signals.
- 22/6/71 TVP R1; CT R1; RAI IA; JRT E3, E4.
- 23/6/71 USSR R1; TVE E2; RAI IA.
- 26/6/71 CT R2; ORF E2a; WG E3, E4; RAI IA; TVE E2, E3; plus unidentified signals.
- 27/6/71 USSR R1, R2; TVP R1, R2; plus unidentified signals.
- 28/6/71 SR E2, E3; NRK E2; RAI IA; JRT E4; plus unidentified signals.
- 29/6/71 TVE E2, E3.

Excellent openings which I unfortunately missed were also noted on the 11th, 24th, 25th, 28th, 29th while on certain of the days above the Sp. E openings were well under way when I switched on. Good tropospherics were noted in many parts of the UK at the beginning of the month, brought about by the sustained fine weather, with signals from France, Belgium, Holland and West Germany—notably on u.h.f. Of particular interest here was my reception of Leige E3 via tropospherics—a difficult one due to an extremely strong local signal on ch. B3.

In an opening here on 15/6/71 Denmark was noted using the old Test Card G—with "Danmarks Radio" identification—prior to the ORF type electronic card the latter with no identification. With Austria on ch. E4 with the similar card care is called for when logging this station.

The same Sp. E opening brought forth an interesting

event on ch. E2 with NRK Norway. Within the space of 10 minutes they were noted to change from Test Card G to the ORF type electronic card (with identification) and then to the electronic card used by SWF (West Germany) and Finland (see June DX-TV column for photograph). The latter card carried the identification NRK in the central black rectangle. With Finland also using this distinctive card on both the TV1 and TV2 networks obvious precautions need to be taken. (We have heard that the TV2 ch. E2 Finnish transmitter at Tampere was off the air 1/6/71-15/6/71.)


The USSR has been noted to change the identification on their test card. Usually it carries the number "0249" within the central circle but at times this is replaced with the letters "СССР". Possibly the former originates from the transmitter itself while the latter version indicates a network transmission card.

With recent reception favouring the South East, Yugoslavia has been well received and has brought about a number of queries. There are three main networks in this country: Zagreb (using the Telefunken card and checkerboard pattern); Ljubljana (using the Retma card, with identification, and EBU pattern); Beograd (using the Retma card, no identification, and EBU pattern). Often one network will be transmitting a programme while the others are on test patterns. Yugoslavia has also been noted in the recent openings using numerous patterns on E3 and E4—various grey scales, contrast wedges etc.
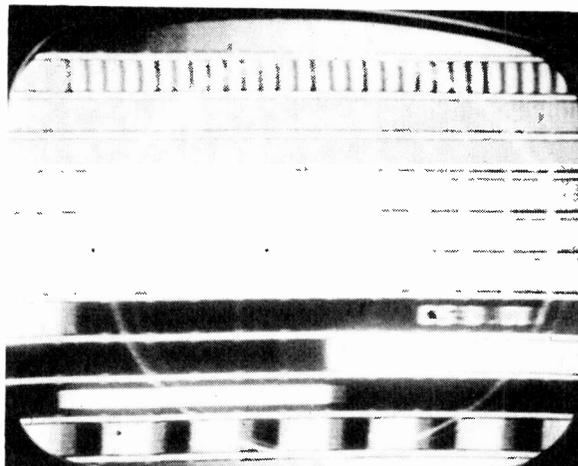
### From our Correspondents


A number of enthusiasts have from time to time noted the DFF (East Germany) test pattern, which usually carries the identification "DFF Berlin", carrying other wording often too small to be deciphered. Keith Hamer (Derby) has sent us the answer to the problem. The wording is "DFF UBERNIMMT DAS PROGRAM VON RADIO DDR". Keith tells us that this means basically that the DFF TV network is taking the sound from Radio DDR and relaying it over the television transmitters. (This is similar to ORTF who relay the France Inter radio programme during the TV test transmissions.) Our grateful thanks to Keith for clearing up this mystery which has puzzled more than one person!

P. Watts (Grimsby) has written with a log of stations




The "CS U 01" Czechoslovakian test pattern.


## DATA PANEL 2—2nd series

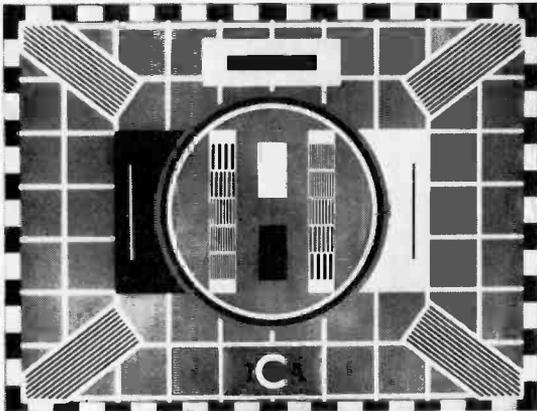

Test Card C

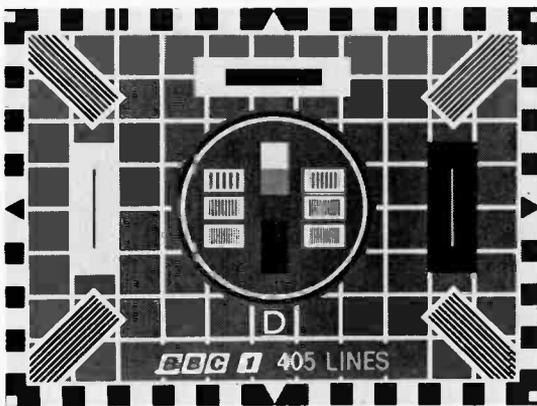


Test Card D

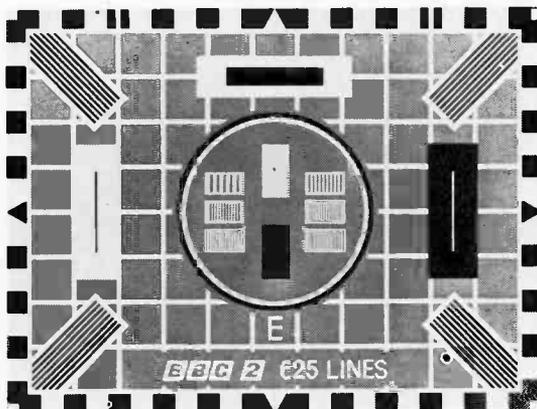


Test Card E


## STANDARD PATTERNS

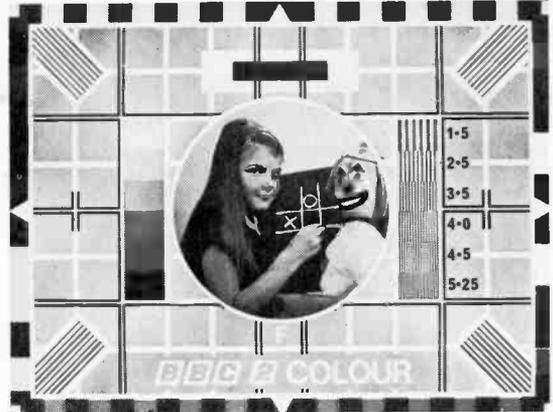

Test Card F

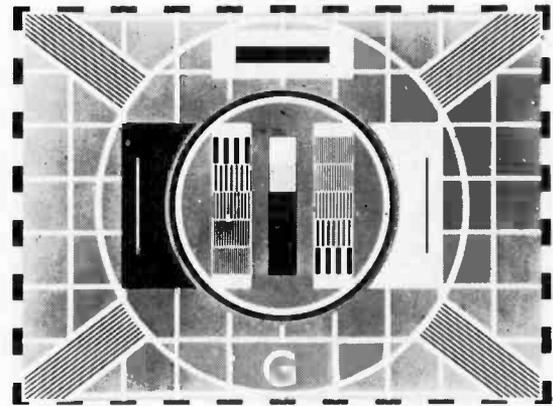

Test Card G

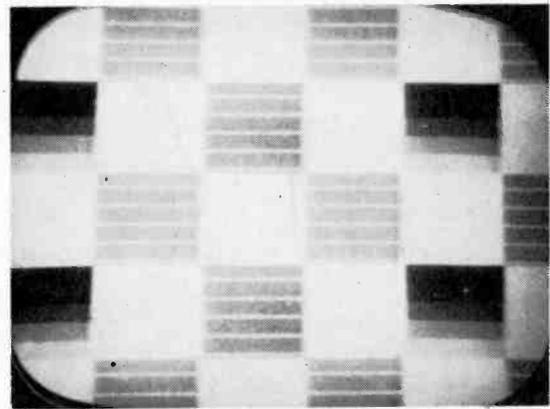

Checkerboard Pattern

*Photographs by courtesy of ITA, BBC, BREMA, S. Wedge and P. D. Van der Kramer.*

he received during the recent good conditions. He too has noted the tendency for reception to the South East and has also received the Hungarian test pattern with the new identification in the black rectangle (see last month's column). The new Czechoslovakian test pattern was also received at good strength, and we are most fortunate to be able to feature this pattern with the column this month.

P. D. van der Kramer has sent us a photograph of the

Czechoslovakian "CS U 01" test pattern as received by him in Slikerveer, Holland. He too has been most active with reception on most days throughout May and June. In his letter he mentions that Belgium has used the ORF (Austria) type electronic card which confirms the observations of Mr. Bunyan of Sittingbourne Kent, mentioned in the April DX-TV column. P. D. van der Kramer goes on to say that he organises a small DX-TV club currently active in the Low Countries. This includes publication

of a monthly bulletin in Dutch. If there is sufficient interest he is considering an English version. Readers interested should write to him direct (with an I.R.C.) at Europese Testbeeldjagers, Diepenbrockstraat 2, Slikkerveer 3210, Holland.

Our friends Lothar Scholt (Ziegelroda, East Germany) and Seppo J. Pirhonen (Lahti, Finland) have both written to us with latest news. They report excellent conditions prevailing in their respective countries. Lothar has seen openings on most days since May 14th although he is unfortunately unable to resolve the BBC-1 405-line signals that are often received there. Seppo tells us that he has been looking in the early mornings with his aerials to the South East and as early as 0515 BST has logged weak signals on ch. R1 which he suspects—and I agree—may have originated in the Central Asian part of the USSR!

To complete the list of Italian transmitters featured in the May DX-TV column the following information is now to hand: No. 19, Gambarie, ch. D; No. 28, Badde Urbara (Sardinia), ch. D.

**News**

**Luxembourg:** We now have more detailed information about the changes at Tele-Luxembourg. As mentioned last month a changeover to 625 lines with positive video will take place from September 1st 1971 and test transmissions are already in progress. A new 300 metre mast is under construction and in the Spring of next year higher gain ch. E7 transmitting aerials will be brought into service at the 260 metre level. During Summer 1972 a 1000kW ch. E21 transmitter will come into service with transmitting aerials at the full 300 metre height. The studio will be capable of colour transmissions using the SECAM system (similar to ORTF-2).

**Monaco:** Tele Monte-Carlo is to construct a 1000kW u.h.f. transmitter in the Alps—North of Tenda on Mount Bec Rouz—to transmit programmes in Italian to Northern Italy along the Po Valley and Tuscany. Another transmitter is planned for Corsica with a coverage into Rome. Both transmissions will be using the SECAM system.

**Sunspot Counts:** Predictions of the smoothed monthly counts: June 64, July 62, August 60, September 58, October 56, November 54. Courtesy Swiss Solar Observatory.

**New Transmitters**

**France:** Toulouse/Pic Du Midi ch.24 500kW horizontal.  
Autun (Central France) ch.51 500kW horizontal.

**Lebanon:** Jounieh ch.E2 1kW horizontal.  
This station is virtually impossible but has been listed as showing an encouraging sign of possible further stations in Band I in an area where Band III tends to be used in preference to other frequencies.

**Sweden:** Halmstad ch.24 1000kW horizontal (approximately 70 miles north of Copenhagen).  
Boden ch.36 increase of e.r.p. to 1000kW horizontal from 100kW.

**Denmark:** Copenhagen ch.31 has been taken out of service.

**Holland:** Goes ch.E7 has been taken out of service.

**DX-TV Pamphlet**

We decided some while ago to produce a small pamphlet giving basic information on DX-TV. Due to Charles Rafele's untimely death this was held up but is now however complete, containing information on vision standards, propagation, aerials and amplifiers, receiver requirements and modifications, interference rejection, photography, etc. To cover costs it is necessary to make a charge of 15p. Postal orders should be made out to R. Bunney and sent care of Television, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD.




**High Salary  
A Dream House  
A New Car  
And A Secure Future**  
Get into the Computer Industry the fast and easy way.

Now for the first time, anybody (no special qualifications are needed) can train outside the computer industry for an exciting career as a **computer operator in only 4 weeks** — and can earn £2,000 ++ p.a.

How? We are the only commercial training organisation in the U.K. permitted to use the famous 'Eduputer'.

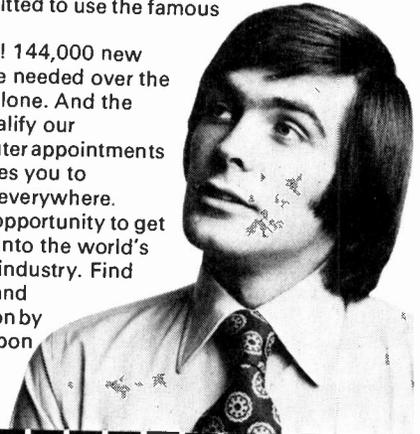**JOBS GALORE!** 144,000 new operators will be needed over the next five years alone. And the moment you qualify our exclusive computer appointments bureau introduces you to computer users everywhere. This is your big opportunity to get out of a rut and into the world's fastest growing industry. Find out more FREE and without obligation by posting this coupon TO-DAY.



**London Computer Operators Training Centre**

D68 Oxford House, 9/15, Oxford Street, London, W1.  
Telephone: 01-734 2874  
127/131 The Piazza, Dept. D68 Piccadilly Plaza, Manchester 1. Telephone: 061-236 2935.

Please send me your FREE illustrated brochure on exclusive Eduputer 'hands on' training for computer operating.

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel \_\_\_\_\_

# a look at Imported SETS....

## The Crown 7TV105 mains/battery portable

H.K.HILLS

It is always interesting and informative and for the service engineer frequently essential to become conversant with the often very different circuits and design ideas used in the many foreign sets now being imported into this country. Getting to grips with these circuits is however hampered for the busy service engineer by the fact that, certainly in the case of the many single-standard monochrome portable sets around, the service manuals seldom contain circuit notes while the circuit diagram draughting is usually completely different to the accepted UK style. The aim of this new occasional series therefore is to highlight and explain the many interesting technical features to be found in the various types of imported sets. To start the ball rolling we shall first take a look at a typical Japanese mains-battery portable model, the Crown 7TV105. This single-standard, solid-state monochrome model is fitted with a 7in. tube and uses 21 transistors and 19 diodes. It is a compact set weighing just 6·6lb.

### Vision Receiver

The receiver stages up to the point where the video and 6MHz intercarrier sound signals are separated are shown in block schematic form in Fig. 1. Looking first at the tuner we immediately see a complete contrast between current UK and Japanese practice, for this tuner uses just one transistor, as oscillator, whose output together with the aerial signal is coupled to a diode mixer. Two tuned lecher lines provide the required pre-mixer selectivity and the i.f. output is taken to a single-stage "bandpass amplifier" mounted on a separate printed-circuit board. The tuned input and output circuits of this stage are centred on 36·8MHz and the amplified output is then

taken to a three-stage vision i.f. strip. As the receiver can give a usable picture from a 40 $\mu$ V input signal, absence of an r.f. amplifier stage implies low-noise conversion by the mixer diode.

The first two vision i.f. amplifier stages are both gain controlled and are shown together with the associated a.g.c. circuitry in Fig. 2. The collector coils of these two stages are series tuned, also to 36·8MHz, by the associated 15pF capacitors. The base feed to the following transistor is in each case taken from the junction of the coil and the 68 $\Omega$  resistor—R107 or R113—which also forms part of the total collector load. This series arrangement is quite different from the conventional parallel-tuned circuit in which the coil, capacitor and loading resistor are all shunted together with the feed to the following stage taken either from the collector or a coil tapping point to suit the input impedance of this stage. The final i.f. stage in this receiver however has a parallel tuned collector load, tuned to 35·35MHz, which is capacitively linked to a tapped coil tuned to 38·15MHz which feeds the vision detector diode.

Overall, therefore, there are five i.f. coils tuned to 36·8MHz, only the final pair of coils being stagger tuned. In the input circuit to Q1 a bridged-T filter is tuned to 40·9MHz to eliminate the adjacent channel sound while an acceptor trap tuned to 32·9MHz deletes the adjacent channel vision. The overall vision i.f. response, shown inset in Fig. 1, locates the vision carrier at 38·9MHz midway down the h.f. flank and the sound 6MHz lower at 32·9MHz.

### AGC Circuits

A common feed from the a.g.c. amplifier Q6 controls the gain of Q1 and Q2 while a delayed a.g.c. line con-


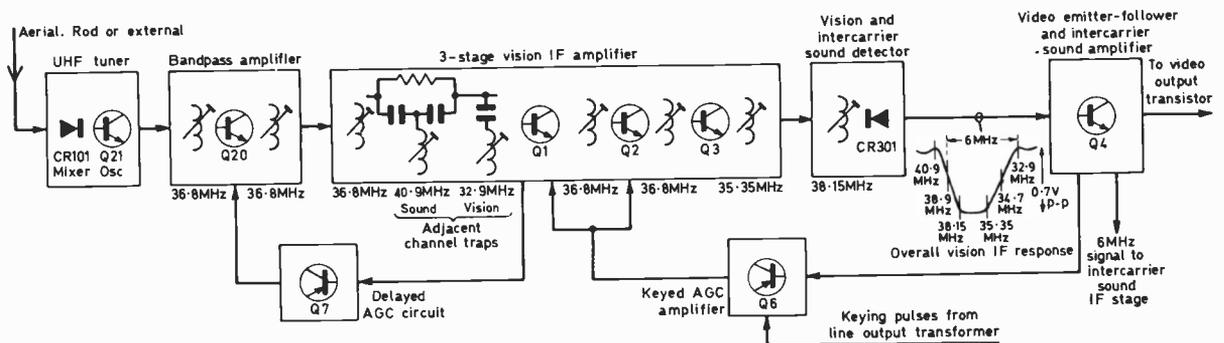


Fig. 1: Block diagram of the vision receiver sections of the Crown 7TV105 portable model.

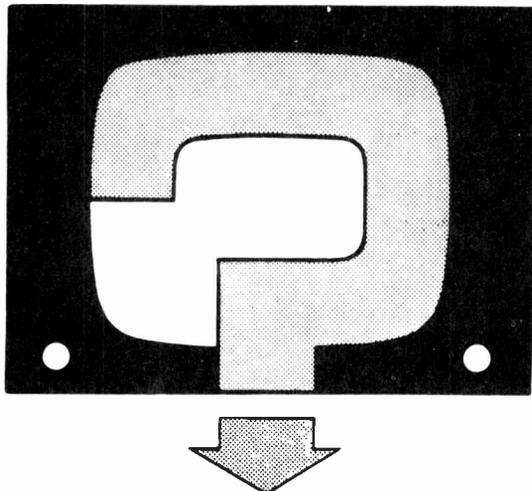





# YOUR PROBLEMS SOLVED

★ Requests for advice in dealing with servicing problems must be accompanied by a 10p postal order (made out to IPC Magazines Ltd.), the query coupon from page 523 and a stamped, addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets or answer queries over the telephone.

## **PYE CT78**

There is an intermittent buzz on sound though the picture and colour are not affected in any way. The buzz is sometimes present on switching on and can occur two or three times a night. It can be completely cured for a time by touching TP3 with a metal object. The buzz can also be reduced to almost zero by placing a finger on top of transistor VT3. Otherwise the sound is OK but is very occasionally reduced and slightly distorted when the buzz is present. Thinking that the trouble could be frequency drift in the tuner the a.f.c. voltage was checked but found to be correct even when the buzz is present.—G. F. Young (Corby).

The symptoms suggest a dry-joint in the sound i.f. section—around T2, T4 and the integrated circuit—which should be carefully examined for this likelihood. Check also the tuning of the slope detector circuit by adjusting L19 for optimum sound.

## **FERRANTI T1046**

The picture has moved to the left—the picture only, not the raster. By moving the line hold control the picture can be moved to the right and the foldover on the left gets very small. As however the picture approaches the correct position it breaks up. This set does not have flywheel sync yet there appears to be a phase shift in the line synchronisation.—G. Penrose (Burton).

This picture shift can occur on sets such as this where the feedback to the line oscillator stage is tapped from the line output transformer and sometimes indicates that the line output transformer is ageing. However, first check the line oscillator and output valves, the cross-coupling capacitors C90, C94 and C89, the sync coupler C99 and the grid resistors.

## **PAM L123A**

The sound is OK but there is no picture, only a thin horizontal line across the screen. The field timebase valves have been replaced without effecting a cure.—R. Jackson (Welwyn).

A frequent cause of this trouble is the VA1054 thermistor inside the field scan coil assembly. The fault could however be almost anywhere else in the field timebase; a check with an oscilloscope would quickly reveal it.

## **REGENTONE 195**

The fault on this set is no raster, sound OK. The voltages on the PL36, PY800 and ECH84 are correct and the line whistle can be heard. A  $\frac{1}{2}$ in. spark can be drawn from the DY86 anode and about  $\frac{1}{4}$ in. from its cathode. The boost voltage is correct at the test point.—G. Barth (Greenford).

The e.h.t. section appears to be in order so we suggest you check the tube base voltages particularly that at pin 3 (first anode) where you might find the 0.02 $\mu$ F decoupler shorted.

## **MURPHY 929U**

The height of the picture and the spacing between the lines increases, the picture also rolling. If the set is switched off for about twenty seconds the trouble goes and the set functions correctly for the rest of the evening. The timebase valves have been replaced without overcoming the difficulty.—T. Downing (Bristol).

We have come across the odd Murphy 929U receiver where this fault is due to shorting turns on the field output transformer. Normally however it is simply due to poor h.t. smoothing. Check therefore the main reservoir and smoothing electrolytics 3C43 and 3C42, then 3C46 which smooths the supply to the field timebase and the other electrolytics in this block—the common fault with these multiple electrolytics is leakage between the sections in the same can, virtually short-circuiting the effect of the smoothing resistors. If these electrolytics are OK check the field output valve cathode decoupler 3C35 500 $\mu$ F from pin 8 of the PCL85.

## **PYE 62**

One of these sets which are fitted with the Pye 368 chassis is suffering from vertical jitter and pulling on whites. The jitter starts on mainly white pictures. The PCL85, PFL200 and ECC82 have been replaced and the capacitors in the field timebase checked. The preset contrast and width controls have also been adjusted.—J. Maundy (Cardiff).

Check that the l.t. feed to the tuner—a sleeved yellow wire running above the system switch—has not got too near the line linearity choke.

**HMV 1893**

There is cramping at the bottom and stretching at the top of the picture. The field timebase valve (PCL82) has been replaced and all components to the valve checked and found to be OK. The linearity controls and associated components also seem to be OK. The ECC82 which forms the other part of the field generator has also been replaced. Apart from this fault the picture is perfect.—L. Warner (Bristol).

Check the  $22k\Omega$  anode load resistor (R113) of the field generator section of the ECC82 and the  $0.01\mu\text{F}$  capacitor C97 behind the linearity control.

**MURPHY V510**

A picture is only obtained by putting the contrast control hard over but the picture is then negative. As the contrast control is adjusted the picture gradually becomes less negative until a point is reached where the picture becomes positive. At this point, however, the picture and sound—with no further movement of the contrast control—suddenly go off (the tube stays on). Both picture and sound can be brought back as before by putting the contrast control hard over again.—H. Redman (Blyth).

The abrupt action of the contrast control denotes a fault in the a.g.c. circuit. This is a rather involved circuit consisting of a 6-30L2 valve coupled to the common i.f. amplifier stage and the tuner unit. Check the 6-30L2 valve then the 30L15 on the tuner and the 30F5 common i.f. amplifier before getting involved if necessary with the components associated with the 6-30L2.

**FERGUSON 3602**

The sound is very distorted though if the volume control is turned fully up the distortion clears. The distortion returns a few minutes after turning the volume control down to a reasonable listening level. The volume control and audio valve have been replaced without improving matters.—B. Cox (Birmingham).

There are two  $0.02\mu\text{F}$  capacitors (C106 and C109) behind the PCL82 audio valve on the upper left-hand side. Change these capacitors: one of them appears to be leaky. Also check the loudspeaker.

**BUSH TV97**

There is excessive width on this model even though the width tapping adjustment has been set to its lowest setting.—G. Truecott (Axminster).

Check the setting of the line linearity sleeve under the deflection coils (make sure that it has not at some time been removed). If this does not solve the problem check C123 ( $0.25\mu\text{F}$ ) and C124 ( $0.1\mu\text{F}$ ). These are the S-correction capacitors in series with the line scan coils. One of them may be short-circuit.

**PHILIPS 19TG158A**

This set has developed uncontrollable brilliance and having checked out all the associated circuits I am forced to the conclusion that the tube is at fault. Are there any steps I can take that may make a new tube unnecessary?—D. Docker (Perth).

A voltage check at pin 2 or pin 6 (grid) of the

AW47-91 will probably show approximately the same voltage as at pin 7 (cathode) whatever the setting of the brilliance control. Short across the base socket heater pins 1 and 8 and note what happens to this voltage when the c.r.t. base is removed. If the voltage now follows the setting of the control the tube has a cathode-grid short. Leave off the base socket and with pins 1 and 8 still shorted to maintain heater line continuity connect pin 7 of the tube base to chassis. Connect a well-insulated lead to pin 6 and touch its other end momentarily to the top cap of the line output valve. This should result in a slight discharge inside the tube and this should clear the short. Repeat if necessary, taking care not to give yourself a little of the same treatment.

**FERGUSON 3703**

There is an intermittent fault on this set. A very severe vertical line of patterning about  $\frac{1}{2}$  in. wide suddenly appears on the right side of the screen, accompanied by lesser patterning all over the screen and also noise. This sometimes lasts only a minute or so while at other times it lasts up to half an hour after which it suddenly disappears. It can always be cured by switching the set off and on again. The fault affects all channels and usually occurs during the first hour. Otherwise the picture is perfect.—G. Lorrimore (Chester).

The trouble is most likely to be in the tuner unit and is probably caused by improper contact between the tuning gang spindle, the earthing clips on the spindle and the tuner bulkheads (the divisions between the sections). Cleaning these clips may be effective or the tuner can be replaced.

**STELLA ST1017U**

There is heavy snow present on all the Band I channels but after about two hours' viewing this slowly disappears until only very faint snow is visible. The trouble has been slowly getting worse. Band III is not affected in this way.—F. Moorfield (Bath).

Since the Band III channels are not affected it appears that the trouble is in the Band I coil biscuits. Remove these and resolder the connections as there seem to be one or more dry-joints or other faulty connections. Also check the PCC89 r.f. amplifier valve.

**GEC 2039**

Sound and vision on u.h.f. suddenly went completely. About the same time the ITV picture started to pull badly to one side in the middle while a week or so later ITV sound and vision also went completely. BBC-1 vision and sound are still excellent. Having had some trouble with the Band switching on the v.h.f. tuner I opened this up and cleaned the switch contacts. After this ITV sound was obtained again but still no vision and no response on u.h.f. A new u.h.f. tuner has been tried with no improvement.—R. Green (Clerkenwell).

The u.h.f. tuner i.f. output is taken to the v.h.f. tuner where it is amplified by the mixer section of the PCF801. If as seems likely the loss of ITV and absence of u.h.f. are due to a common cause this is likely to be in the screen feed to the PCF801 mixer section. Check R7,  $22k\Omega$ , to pin 7 of the valve base.

### PHILCO 1030

The picture is displaced to the left leaving a 3in. wide black vertical band on the right. There is also intermittent picture break-up which necessitates very careful adjustment of the line hold control. This requires further attention from time to time. The following valves have been replaced: PL81, EY86, PY32, PY81.—E. Gunn (Swansea).

You do not mention the two ECC82 valves V12 and V13. These must be checked together with their associated components. There is no direct sync on this model, locking being determined by the line sync comparator valve V13 which is the first suspect.

### EKCO T231

The fault is that the picture is darker, or "shaded", over about one third of the screen on the left-hand side. Could this be due to a failing h.t. metal rectifier and if so could this be replaced by a BY100 silicon rectifier? The set is fitted with spot-wobble: can you tell me the purpose of this?—R. Wise (Aberdeen).

The shading trouble is due to a faulty field flyback suppression capacitor. This 0.001 $\mu$ F capacitor is below the chassis near the main smoothing components and feeds flyback suppression pulses from the field oscillator circuit to the tube grid circuit. You can use a BY100 rectifier with series surge limiter to replace the metal h.t. rectifier if you wish. There is a switch which brings the spot-wobble circuit into operation. This consists of an oscillator coupled to

the scanning assembly and moving the spot as it scans the line so as to diffuse the line structure. It is unfortunately liable to cause patterning on the set next door.

### EMERSON E704

The set operates correctly for about five minutes after which the width of the lines at the top of the picture increases, those at the bottom remaining the same. Adjusting the linearity control helps a little but the effect is still prominent. The field hold control keeps needing adjustment as well.—R. Blackwell (Birmingham).

Check the PCL82 field output valve and its associated components, including the biasing which in this circuit is applied to the grid from the triode oscillator section. The bias is sometimes cancelled by leakage through C77 the 0.01 $\mu$ F coupler from the oscillator triode.

### QUERIES COUPON

This coupon is available until September, 22, 1971, and must accompany all Queries sent in accordance with the notice on page 521.

Don't forget the 10p postal order!

**TELEVISION SEPTEMBER 1971**

## TEST CASE



## 105

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

? A Rank-Bush-Murphy colour receiver came into the workshop with the complaint of incorrect colour displays but with the blue and yellow hues the least affected. The receiver was set up in the workshop from an off-air signal and it was discovered that while the reproduction was normal on a monochrome transmission and on a colour one with the colour control turned right down the symptom of incorrect colours occurred when the colour control was advanced on a colour transmission. The symptom was accompanied by Hanover bar interference (i.e. horizontal lines across the picture, fairly closely spaced).

The receiver was then operated from a PAL-encoded colour-bar generator. At normal viewing distance the white bar appeared white, the yellow bar green-yellow, the cyan bar light blue, the green bar gold-yellow, the magenta bar blue-towards-magenta,

the red bar dirty-red or brown, the blue bar blue-towards-magenta and the black bar black. What area in the receiver would be at fault and what particularly would be most likely to cause incorrect hue displays of this nature? See next month's TELEVISION for the solution and for a further Test Case item.

### SOLUTION TO TEST CASE 104

Page 474 (last month)

On changing from one channel to another the line timebase tends momentarily to fall out of synchronism. This change in generator repetition frequency results in a change in the flyback pulse potential and hence a change in the e.h.t. and boost voltages. There can also be small differences in the sync/blanking signals of different stations which can reflect minor line timebase potential changes.

Now as the field oscillator anode is fed from the boost line a mild fault in the field generator could be aggravated by the change in boost voltage when changing channel and under certain conditions this could lead to loss of field lock as described last month.

Since the technician discovered that the symptom could be influenced by shorting the anode of the field oscillator triode to chassis the next check should have been of the components in the anode circuit. The resistors were found to be without fault but the voltage-dependent resistor used in the set in question to stabilise the height was found to be passing excessive current and thus starving the triode anode circuit. Replacement of this component completely cleared the fault.

# TELEVISION CLASSIFIED ADVERTISEMENTS

The pre-paid rate for classified advertisements is 4p a word (minimum 12 words), box number 7½p extra. Semi-display setting £2.50 per single column inch. All cheques, postal orders, etc., to be made payable to TELEVISION and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, TELEVISION IPC Magazines Ltd., Fleetway House, Farrington Street, London, EC4A 4AD, for insertion in the next available issue.

## EDUCATIONAL

**ENGINEERS**—get a technical certificate. Exam. and Certificate Postal Courses in all branches of Engineering, Electronics, Radio and TV. Computers, Draftings, Building, etc. Write for helpful **FREE BOOK**. B.I.E.T. (Dept. H.6), Aldermaston Court, Reading, RG7 4PF.

**BECOME** "Technically Qualified" in your spare time, guaranteed certificate and exam Home Study courses in Radio, TV, servicing and maintenance, R.T.E.B., City & Guilds, etc., highly informative **FREE Guide**.—Chambers College (Dept. 858K), Aldermaston Court, Reading, RG7 4PF.

**RADIO AND TV Exams and Courses** by Britain's finest home study School. Coaching for Brit.I.R.E., City and Guilds Amateur's Licence, R.T.E.B., P.M.G. Certificate, etc. Free brochure from British National Radio School, Russel Street, Reading.

**MEN!** You can earn £50 p.w. Learn Computer Operating. Send for **FREE** brochure—London Computer Operators Training Centre, C98 Oxford House, 9-15 Oxford Street, London, W.1.

## TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how ICS can help you in your career.

**ICS, DEPT. 560, INTERTEXT HOUSE, STEWARTS ROAD, LONDON SW8 4UJ.**

## FOR SALE

**NEWNES** "Radio & TV Servicing." Complete Set. 15 Vols., 1 to 1964-65, good condition, £50 o.n.o. 15 Tyndale Road, Woodfield, Dursley, Glos.

## LADDERS

**VARNISHED TIMBER LADDERS** from manufacturer, **LOWEST PRICES** anywhere: 15½ ft ext. £6-20; 17 ft ext. £6-50; 20 ft ext. £7; 21½ ft ext. £7-75; 24½ ft ext. £8-90; 29 ft ext. £10-25; 31½ ft triple ext. £12-25; 36 ft triple ext. £16. Carr. 80p. Free Lists. Also Aluminium Ext. and Loft Ladders. **CALLERS WELCOME.** Dept. PTT, HOME SALES, BALDWIN ROAD, STOURPORT, WORCS. Phone 02-993 2574/5222. Placing order on C.O.D.

## MISCELLANEOUS

**RECORD TV** sound using our loud-speaker isolating transformer. Provides safe connection to recorder. Instructions included. 70p plus 10p P&P. Crowborough Electronics (T), Eridge Road, Crowborough, Sussex.

## 17" BBC/ITV TELEVISIONS £5

Working Perfectly.

Plus P. & P. £1 CWO.

Suitable for any area.

3 Channel 19" D/S TVs. ITV, BBC 1, BBC2, £25 inc. carriage. 17" 13 Channel, Complete but untested £1-50 each plus £1 P. & P. CWO.

## SPEAKERS

6" x 4", 7" x 4" 3Ohm, 20p plus 8p P. & P. each. CWO.

Regular deliveries throughout England & N. Ireland

## TRADE TV'S

407 Thornton Road, Gillington, Bradford 8, Yorks.

19 IN. SLIME BBC, ITV TVs. £14. BBC £2, £25, working perfect, plus postage and insurance, £1. Also trade enquiries welcome. Marco Services, 126 Wilmslow Road, Manchester 14. Tel. -061-225-0773.

## TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded.

All at 9p each or

Any 25 transistors for only £1-90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee. P. & P. 10p

**J. M. KING (Z)**

17 Buckridge, Portpool Lane, London, ECI

## AERIALS

**BAKER and BAINES for UHF Aerials** These aerials are suitable for both colour and black and white. Supplied with tilt clamp which will take up to a 2 in. mast. 10 ele £2-10, 12 ele £2-20, 14 ele £2-36, 18 ele £3-25, 22 ele £3-75.

Combined 405 aerials Dipole and 5 £2-70, D and 8 £3-10, Loft Special D and 5 £2-10 complete with loft pole for ease of mounting in the loft space. Lashing Kite—Co-ax—Diplexers and Triplexers—Clamps and couplers. UHF Pre-Amps, £3-75, p. & p. 124p. Please state channel numbers when ordering. Payment paid on all aerials inland. Accessories postage by weight. S.A.E. will bring our full lists.

11 Dale Crescent, Tupton, Chesterfield

## AERIALS

**UHF:** Set Tops £2-10, Outside: 9 ele £1-25, 10 ele £1-90, 11 ele £2-50, 12 ele £2-55, 18 ele £3-25, 20 ele £3-50. Multi-beam 46 and Supremes £5-50.

All aerials supplied with clamps.

**ANTIGHOST:** Troubleshooters/Log-beams £5.

**FM/VHF:** H £2-25, 3 ele £3-25, 4 ele £3-75. Stereo 6 ele £6.

Motorized Units: Semi Auto £20, Auto £25.

All Aerials by leading makers.

**ELECTRONICS, ACCESSORIES:** Incl. Masts, Lashings, Plugs, Amps., Headphones, Meters, Stereo Cartridge Players, Cassettes, Tapes, etc., etc.

**COAXIALE:** Standard 100 Mtrs. £4-50. Low Costs £7, or per Mtr.

State channels for all TV Aerials/Amps. FM state wide band or channelized. **TERMS:** CWO, COD, P & P 32½p. Send 2½p stamps for lists. Callers Welcome.

**OVERSEAS** customers welcome. Note New Zealand/Australia by sea, 7 weeks min. By Air quotations given.

## JEFFRIES SERVICES

31 Hambrook St., Portsmouth. Tel. 28354

## SERVICE SHEETS

## TRADER SERVICE SHEETS

40p each plus postage

We can supply Trader Service Sheets for most makes and types of Radios, Tape Recorders and Televisions—Manuals for some.

Cheques and open P.O.s returned if sheets not available.

## OAKFIELD ENTERPRISES

LIMITED

29 CHURCH ROAD, TUNBRIDGE WELLS, KENT

Make	Model	Radio/TV

1971 List now available at 10p plus postage

If list is required indicate with X

From.....

Address.....

enclose remittance of..... (and a stamped addressed envelope) s.a.e. with enquiries please **MAIL ORDER ONLY** (May T)

## SERVICE SHEETS (continued)

## Service Sheets &amp; Manuals

LARGE RANGE OF MODELS AVAILABLE FOR RADIO TELEVISION TAPE RECORDERS R PLAYERS ETC  
FROM 25p EACH S.A.E. WITH ENQUIRIES PLEASE 1971 LISTS ARE AVAILABLE 13p

MULLARD TRANSISTOR AUDIO AND RADIO CIRCUITS	PRICE £1	63p
T.V. FAULT FINDING BOOK by DATA PUBLICATIONS LTD		55p
MULLARD VALVE & SEMI CONDUCTOR DATA BOOK		23p
MAZDA VALVE & PICTURE TUBE DATA BOOKLET		23p
BRIMAR VALVES & TELE TUBE DATA LIST		20p
RESISTOR COLOUR CODE INDICATOR DISC		13p

Sets of Brand New Valves supplied for most makes of Radio T.V. etc. Prices on request

Post free

**BELLS TELEVISION SERVICES**  
Albert Place Harrogate Yorkshire Tel 0423-86844

### QUICK, EFFICIENT, UNIQUE SERVICE SHEET SERVICE

Very Large Stock  
TVs, Radio, Amps, Test Gear.  
Special Telephone Service available to Trade Customers.  
Colour TV and Test Gear Circuits.  
Exchange Service.  
Full details with first Order.  
List price 10p Post Free.  
State Make and Model Number.  
Large S.A.E. and 25p unfilled P.O.  
Mail Order Only.

**A.S.L., 21c Dryden Chambers,  
119 Oxford Street,  
London, W1R 1PB**

### LARGE SUPPLIER of SERVICE SHEETS

(TV, RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 25p each. Manuals from 50p  
PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES AND ORDERS.  
Otherwise cannot be attended to.  
(Uncrossed P.O.'s please, original returned if service sheets not available.)

### C. CARANNA 71 BEAUFORT PARK, LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.  
MAIL ORDER ONLY

### SERVICE SHEETS

(1925-1971) for Radios, Televisions, Transistors, Radiograms, Car Radios, Tape Recorders, Record Players, etc.  
By return post with

FREE FAULT FINDING GUIDE  
PRICES FROM 5p

Over 8,000 models available.  
Catalogue 13p.

Please send stamped addressed envelope with all orders and enquiries.

### Hamilton Radio

54 London Road, Bexhill, Sussex  
Telephone Bexhill 7097

RADIO, TELEVISION, over 3,000 models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Road, London, W.6. SHE 8441.

SERVICE SHEETS. Radio, TV, etc. 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS with Free Fault Finding Chart 35p, plus stamped addressed envelope. LESMAR, 15 Conholt Road, Andover, Hants.

### SETS & COMPONENTS

### SPARES

From used TVs. S.A.E. your enquiries. Complete but untested TVs. 19 in. 405 lines, £5, 19 in. dual standard, E.G., Ekco 402, Sobell, 1000 series, Thorn 850, etc., £8 (less U.H.F. tuner). 19 in. dual standard with U.H.F. tuner, £12. Carriage and packing, £1.50. Lists. S.A.E.

### LINAYALE RADIO LIMITED

48 Hoe Street, London, E.17,  
01-520-7546.

### CHROMASONIC ELECTRONICS

#### LOW NOISE HI-STABS

½ watt 5% all E24 values, 3 for 2p, plus p & p 6p for up to 50 resistors + 1p for each additional 50  
Skeleton Presets 0.1 watt 5p, 0.25 watt 7p.  
5µF 64v; 16µF 40v, 6p; 100µF 40v, 9p; 640µF 25v, 18p. Polystyrenes 5p each.  
Silver Micas 7p each up to 220pf. C280, 0.1µF 250v 3p. Feedthrough Ceramic 1000pf 5p.

BC107 12p	BC187 27p	OA90 7p
BC108 11p	BF194 17p	OA95 7p
BF167 25p	BF195 17p	2N1613 22p
BF173 25p	BF196	TAA700 £2
BF184 25p	(BF239) 15p	AC128 17p
BF180 42p	BF197 15p	
	BU105 £2.75	

BZY88 range 15p each.

TTL Decade Counter 7490 87p

Coax Socket 8p. Switch 2 pole 3 way 25p

FREE CATALOGUE P & P 3p.

P & P on all orders other than Resistors 6p  
Dept. 'T', 56 Fortis Green Rd., London,  
N10 3HN

### RADIO SPARES EQUIPMENT

Now available for enthusiasts and amateurs. Callers by appointment. S.A.E. MUST accompany all enquiries.

**SONAR GROUP (Dept. T.)**

24 Fordway Avenue, Blackpool, Lancs.  
Telephone 0253 (Blackpool) 32819.

### TELEVISION TUBE SHOP

BRAND NEW TUBES AT  
REDUCED PRICES

A28-14W (A28-13W)	£12.75
A31-18W	£12.50
A47-11W	£9.95
A47-13W	£12.50
A47-14W	£8.25
A47-26W	£10.75
A50-120WR	£12.50
A59-11W	£12.95
A59-13W	£13.50*
A59-15W	£9.95
A59-16W	£13.50*
A59-23W	£14.75
A61-120WR	£16.00
AW36-21, 36-80	£5.75
AW43-80	£6.95
AW43-88, 43-89	£6.75
AW47-90, 47-91	£7.50
AW53-80	£7.50*
AW53-88, 53-89	£8.25
AW59-90, 59-91	£9.00
C17LM, 17PM, 17SM	£6.50
CME1201	£12.50
CME1402	£5.75
CME1601	£10.50
CME1602	£12.00
CME1702, 1703	£6.75
CME1705	£7.75
CME1713/A44-120	£14.50
CME1901, 1903	£7.50
CME1906	£12.50
CME1908	£7.75
CME2013	£12.50
CME2101, 2104	£8.25
CME2301, 2302, 2303	£9.00
CME2305	£14.75
CME2306	£13.50*
CME2308	£9.95
CME2413R	£16.50
CRM93, 124	£5.50*
CRM141, CRM142	£5.50
CRM171, CRM172	£6.50
CRM211, CRM212	£7.50*
MW36-24, 36-44	£5.50
MW43-69	£6.75
MW43-80	£6.75
MW53-20, 53-80	£7.5*
TSD217, TSD282	£14.00†
13BP4 (Crystal 13)	£14.00†
190A134	£9.25
230D134	£11.25

†Rebuilt tubes also,  
at £7.00 plus bulb

\*These types are FULLY rebuilt.

ALL TUBES ARE TESTED AND GUARANTEED FOR A MINIMUM OF 12 MONTHS

ADD 75p FOR CARRIAGE AND INSURANCE

#### COLOUR TUBES

19 in. and 22 in. having slight marks or scratches at £35 each

### TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD,  
LONDON, S.W.11. BAT 6859

WE GIVE GREEN SHIELD  
STAMPS

NEW MOSTLY BVA VALVES! Huge range by post service well known to the trade. Brief list of television types herewith, full list S.A.E. All types ex stock!

DY86/7	43p	PCF86	63p	PY82	50p	20L1	95p
EB91	25p	PCF801/2	62p	PY800/1	50p	20P4	£1.00
ECC82	42p	PCF805	87p	R19	85p	30C15	90p
ECL80	50p	PCF808	85p	U25	95p	30C17	95p
EF80	42p	PCL82	51p	U26	95p	30F5	95p
EF85	45p	PCL83(S)	60p	U37	75p	30FL1 & 2	65p
EF183/4	57p	PCL84	60p	U191	90p	30L15	95p
EH90	55p	PCL805/85	66p	U193	48p	30L17	90p
EY51	60p	PCL86	66p	U251	95p	30P12	95p
EY86/7	43p	PL36/8	87p	U301	90p	30PL1	90p
PC86 & 8	75p	PL81	80p	U801	£1.25	30P4MR	£1.25
PC97	45p	PL83	85p	6/30L2	90p	30P19	87p
PC900	55p	PL84	65p	6AT6	55p	30PL13	£1.00
PCC84	50p	PL500	90p	6BW7	82p	30PL14/5	£1.10
PCC89	62p	PL504	90p	6CD6G	95p	etc.	etc.
PCF80	52p	PY81	50p	6F23	95p	Trade prices	

DEDUCT 5% FROM AUGUST '97!

POST FREE OVER £3.00. 2½p PER VALVE BELOW £3.00

LATEST NEW BY100/127 type silicon rectifier 15p. 33Ω res 5p!

Large bulb Imported PCF80 32p! Note. Ask for separate component and Philips PCL805/85 57p!

## LOOK! Nearly every type in stock now !! NEW TELEVISION TUBES!

TWO YEAR FULL REPLACEMENT GUARANTEE

SEE THE DIFFERENCE A NEW TUBE CAN MAKE TO YOUR VIEWING—LATEST SCREENING TECHNIQUES INCLUDING TINTED SCREENS ON MOST 19" and 23" TYPES

Large stocks by British leading manufacturers, why buy cheap rebuilds. Two year warranty!

COLOUR! FOUR (yes 4) years guarantee: 19" £49.00; 22" £53; 25" £57. Enquiries welcomed.

Special offer! 19" mono rebuilds. 2 year guarantee £5.50! 23" £7.50

12" £3.00 (not 110") 20" 14" to 16" (not 110") £4.75

17" £5.87 A50/120W £10.50

19" mono tubes—all £6.87. Carriage all 60p. All 21" mono tubes—£7.87  
23" mono tubes £9.50. Carriage 75p, also 24" and 25" available.

Prices on application. Quality before price!

RIMBANDS. 19" £8.50; 23" £11.50 } Carriage

TWIN PANELS. 19" & 23" £10.12 & £15.00 } 75p

Bulk enquiries welcomed. GIRO 34.361.4006

### PHILIP H. BEARMAN

(Suppliers to H.M. Govt. etc.)

## 6 POTTERS ROAD, NEW BARNET, HERTS.

Closed Thurs. & Sat. afternoons  
(Adjacent to Post Office)

TEL. 01-449/1934 & 1935  
(Robophone)

### AERIAL BOOSTERS £2.95 EACH

We make four types of transistorized aerial pre-amplifiers. These take only seconds to install.

1. L45 625 TELEVISION (U.H.F.).

2. L12 405 TELEVISION (V.H.F.).

Please state channel numbers.

3. L11 V.H.F. F.M. RADIO.

4. L10 WIDEBAND RADIO.

This covers M/W and S/W to 20 MHz.

PRICE EACH

L45, L12 and L11 £2.95; L10 £1.95.

S.A.E. FOR DETAILS

MONEY BACK GUARANTEE

P. & P. 10p ALL ORDERS

### VALVE BARGAINS

Any 1—10p, 5—45p, 10—70p.

EB91, EBF89, ECC82, EY86, ECL80, EF80, EF85, EF183, EF184, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF800, PCL82, PC97, PCL84, PCL85, PL36, PL81, PL83, PY32, PY33, PY81, PY82, PY800, PY801, 30FL1, 30F5, 30L15, 30C15, 6F23, 6-30LZ. TESTED, WITH 3 MONTH GUARANTEE VALVES 20p EACH

BY100 TYPE RECTIFIERS with Surge-resistor on bracket, 12½p each.

MAINS DROPPERS 3 SECTIONS 33-33-33 OHMS 9p each.

## VELCO ELECTRONICS

62c Bridge Street, Ramsbottom, Bury, Lancs. Tel. 3036

## TV's TV's TV's

### SPECIAL OFFER—LIMITED PERIOD ONLY

Thorn 800 Chassis. 13 channel slim TV's. Good working order. Polished cabinets. Only £9.50 PLUS £1.50 Carr.

### EX-RENTAL TV'S

Complete with 13 channel tuners. Good cabinets. Carriage £1.50 extra.

17" Semi Slim (90° Tube) ... £2.50

17 1/2" Slim (110° Tube) ... £4.50

19" Slimline ... £6.50

23" Slimline ... £8.50

19" BBC2 Sets ... £14.50

### PERFECT SPEAKERS EX T.V.

Phi 3 ohm (minimum order two) 5 in. round, 8 in. by 2 in. rectangular—12½p each. Add 7½p per speaker p. & p.

### VALVES EX EQUIPMENT

EB91	5p	30P4	12½p	PL81	17½p
EBF89	12½p	PC97	17½p	PY81	15p
ECC82	12½p	PCF86	17½p	PY800	15p
ECL80	7½p	PC84	7½p	PY82	7½p
EF80	12½p	PCF80	7½p	PY33	22½p
EF85	12½p	PCC89	12½p	U191	17½p
EF183	12½p	PCL85	22½p	6P23	17½p
EF184	12½p	PCL85	17½p	30PL1	22½p
EY86	17½p	PCL82	17½p	30P12	20p
30PL13	20p	PCL86	17½p	30F5	10p
630LZ	12½p	PCL83	12½p		
30L15	12½p	PL36	22½p		

Add 2½p per valve p. & p., orders over £1 p. & p. free

### UHF TUNERS

To suit Ferguson 850 900 chassis £2.50, p. & p. 50p

### SLOT METERS—SPECIAL OFFER

Smiths Mk. 11 6d. Convertible to 5p. (Smiths Kit cost) 35p) £1 each inc. p. & p. or 10 for £3 inc. p. & p.

Please write with SAE for quotations on any spares

### TRADE

### DISPOSALS (Dept. T.S.)

Thornbury Roundabout, Leeds Ed., Bradford  
Telephone 665870

### WITWORTH

### TRANSFORMERS LTD.

Dept. P.T., 236 SANDYCOMBE ROAD.

RICHMOND.

SURREY.

Telephone: 01-940 8146. 9 a.m. till 5 p.m.

### TELEVISION LINE

### OUTPUT

### TRANSFORMERS

PRACTICALLY ANY MAKE OR MODEL SUPPLIED OR REWOUND

EKCO, FERRANTI, DYNATRON Replacement cases £1.00 each, please state model.

S.A.E. for return of post quotation. TERMS: Cash with order or C.O.D., please add 20p for postage.

C.O.D. orders will be charged 30p extra. Transformers fully guaranteed. (98)

EKCO FERRANTI LOPTS. All types, £2.50, transistors U.H.F. tuners, £4. All post free. C.W.O. 1 Old Shoreham Road, Southwick, Sussex.

### PORTABLE TELEVISIONS

Battery or Mains. We stock over eleven different models. BIG Money Saving Offers. Trade supplied with Full Trade Discounts. All enquiries with S.A.E. please.

Ross Electric,

1 Church Street, Ainsworth, Bolton.  
21408/51956.

## SETS &amp; COMPONENTS (continued)

## SOUTHERN VALVE COMPANY (Valve Specialists)

44 Earls Court Road, London, W.8

We do not claim the cheapest, but quality first!

ALL valves boxed and brand new, some BVA! Send s.a.e. for free lists.

DY87 37p	PC868 50p	PCL805 44p	U193 35p	30L17 75p
DY802 45p	PC97 40p	PCL86 37p	U251 62p	30P12 70p
EB91 15p	PCF80 32p	PL36 52p	6/30L2 60p	30PL1 60p
ECC81 37p	PCF86 52p	PL81 46p	6BW7 60p	30P4MR 95p
ECC82 30p	PCF801 50p	PL84 55p	6CD6G 90p	30P19 70p
ECL80 40p	PCF802 50p	PL500/4 65p	6F23 75p	30PL13 75p
EF80 27p	PCF805 50p	PY81 35p	6F28 48p	30PL14 75p
EF183 37p	PCF808 60p	PY800 35p	20L1 85p	etc., etc.
EF184 37p	PCL82 37p	PY801 35p	20P4 90p	
EH90 45p	PCL83(s) 50p	U25 65p	30C15 70p	
EY51 50p	PCL84 37p	U26 60p	30FL12 75p	
EY86/7 37p	PCL85 44p	U191 65p	30L15 75p	

Post free £2.00 and over. Mail order only.

[932]

**NOTE**  
 BY100/BY127  
 equiv only 20p  
 with resistor.

## TOWERBY LTD

For Line Outputs and Deflector Coils

We have the Country's largest stock of Manufacturer's Original (or Authorised Replacement) Line Output Transformers for many "difficult" makes, including Ambassador, Baird, Cossor, Decca, Dynatron, Ekco, Ferguson, G.E.C., H.M.V., K.B., Masteradio, Peto-Scott, Philips, Regentone, RGD, Sobell, Ultra, etc. Also deflector coils output and oscillator transformers, inc. Alba, Bush, Murphy. Examples: L.O.P.T. Murphy 350/410/540/659/759, £7-35; Bush, TV80, TV95, TV96, £7-35; Cossor 950, £3-87; Ferguson 306/308, £3-97; Philips 1768U L.O.P.T. assembly, £6-75; Ultra 1984-200c, £5-06. Rewind most L.O.P.T., £4-50.

## SPECIAL OFFER

Ekco improved type for Models T221, 231, 310, all at £2-25; Ferranti 1474 series inserts, £1-25; Philco 1019/1021, £2-62; Terms: C.W.O. or C.O.D. (171p), post-packing 30p; 2 or more L.O.P.T.s post/packing free. All enquiries answered but regret no lists available. Same day delivery on most types.

## TOWERBY LTD

MAIL ORDER DIVISION OF T.C.S. LTD.  
 70 STREATHAM HILL, LONDON, SW2  
 Tel.: 01-674 2185.

## T.V. SPARES

**OIL FILLED MURPHY LOPT's** U26 type. Model number not known. £1-25 each plus 25p p.p.

**BAIRD/FERGUSON V.H.F. TUNERS.** Uses PC97 and 30C18 valves. Fits 620 to 650 series models, complete with all coils, supplied less valves, £1-75 each plus 25p p.p.

**BRC 960 I.F. PANELS.** Complete and unused, less valves. Dual standard V.H.F./U.H.F. 405/625. Absolute bargain at £2-50 plus 25p p.p.

**FERGUSON/EKCO PLUG IN MAINS LEADS.** Moulded two-pin connector type. 6 for £1-50 plus 25p p.p.

**LATE G.E.C./SOBELL 625 405, etc.** Dual Standard 405/625 I.F. Panels, complete with switching for direct replacement in this popular Radio and Allied receiver. £1-75 plus 25p p.p.

**TIMEBASE PANELS** to fit Sobell 195, 282, 283, 284, 285, 286, 287, 288 (and DS models), McMichael MT762, 763, 765, P405. Complete and new for direct replacement, £1-75 each plus 25p p.p.

**V.H.F. ROTARY TUNER UNITS** to fit McMichael, Sobell, G.E.C. New and unused, £1-75 each plus 25p p.p.

**FERGUSON 800/850 series TIMEBASE PANELS,** complete and unused in original packing. £2-25 each, plus 25p p.p.

**SCAN COILS,** 110° type will fit most makes, after modification. Originally manufactured for Pye but we have used them in BRC, Philips, etc. with good results. £1-50 plus 25p p.p.

## WILLOW VALE ELECTRONICS LTD.

4 & 5 The Broadway  
 Hanwell, London, W.7

Tel: 01-567 2971 and 5400  
 01-579 3582

Terms cash with order or C.O.D. 27p extra  
 S.A.E. all enquiries. Catalogue 20p

**TV COMPONENTS** (send S.A.E. for list), e.g.: Resistors in packs of 5, all values supplied. Price per pack as follows: 1 watt—10p, 2 watt—19p, 10 watt wire wound—40p, BY127 Silicon Rectifiers—20p each, Thermistors TH1—10 p each. Instant Heat Soldering Gun, only £3-25. Orders despatched within 24 hours (stocks permitting). For urgent orders telephone Doncaster 49874. Please add 15p for P. & P. (orders of £5 or over P. & P. free). TRIDENT TELEVISION SERVICES, 29 Richmond Road, Scawsby, Doncaster, Yorks.

**TELEVISIONS.** Fantastic Reductions. 100 Guaranteed Sets £5 to £10. New Portables BAT/MAINS £48-£50 (Save £21). New UHF 23" £55! Transistor Radios, Record Players at Trade Prices! All Eagle Equipment—Huge Discounts. T.V. Bargain Centre, 47 Goldhawk Road, Shepherds Bush, W.12. 01-743 3050. Open till 7 pm.

## R &amp; R RADIO

51 Burnley Road, Rawtenstall  
 Rossendale, Lancs

Tel.: Rossendale 3152

TESTED VALVES—  
 3 MONTHS' GUARANTEE

EBF80 15p	PCC84 15p	PY800 171p
EBF89 171p	PCF80 15p	PY801 171p
ECC82 15p	PCL82 20p	U191 221p
ECL80 15p	PL36 25p	30C15 25p
EF80 10p	PY33 25p	PCF86 25p
EF85 15p	PY81 171p	PCL85 25p
EY86 20p	PY82 15p	PCL84 25p

Copper Laminate Board, for etching, 1p per sq.in. Double sided 11p per sq.in. Any size cut, min. order 50p plus 10% P. & P.

Postage on Valves: one valve 4p, up to 6 21p over 6 post paid.

**TOP 20 TV Valves,** 10p; PL504, PL36, PY33, 15p, P&P 4p per valve, over 12 valves post free. Guaranteed tested ex-equipment, individually boxed. Resistors and capacitors all values and sizes. Leading manufacturers components and hi-fi equipment, 10% or more off. 13A plugs, 12p. Mains fuses, 20p for 10. Tools, etc., P&P extra on all items. Trade enquiries welcomed, discount for quantity. S.A.E. for list. L & D Components Ltd., 71 Westbury Avenue, Wood Green, N.22. 01-888 2701.

**LARGE** quantities of used TV spares for most models, 1952-64. Lopts, Tuners IF Strips, Time Base Panels Scan Coils, Frame Transformers, Knobs, cabinet Trim, etc. New manufacturers replacement parts, can be supplied, for more modern sets on receipt of an order deposit. S.A.E. for quotations. C.W.O. to TV Dismantlers, Foxhole, Whitstone, Holsworthy, Devon.

## VALVES, VALVES, VALVES

Any ten of your choice 72p, post 5p.  
 100 £5-50, post paid.

EF85, EF80, EB91, EBF89, ECL80, EF183, EY86, PCF80, PCC84, PL36, PY81, PCL82, PCL83, PCC89, PY33, PY82, PY800, PY801, PY88, PCL84, 30F5, 6BW7, PY801.

## BOB'S,

2 St. James Street, Rawtenstall  
 Rossendale, Lancs.  
 Mail order ONLY.

Brand New  
HARTLEY OSCILLOSCOPES  
C.T.316

In original packing. Miniature valves.  
 Band width up to 5 Megs.

Mains supply.

£40, plus £1-50 post and packing.

C.W.O. Carriage charges mainland only.

## A. H. THACKER

Radio Dept, High Street, Cheslyn Hay,  
 Nr. Walsall, Staffs.

**120 NEW ASSORTED** Capacitors, Electrolytic, Mica, etc., and Resistors, 1/20W, 85p, Post Free. Whitsam Electrical, 33 Drayton Green Road, London, W.13.

## WANTED

**WANTED** August and September, 1969 issues "PRACTICAL TELEVISION" Card, 27 Scarborough Road, Lytham-St-Annes, Lancs, FY8 3ER.

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London. W.7. 01-567 5400/2971.

**SERVICE SHEETS** purchased, HAMILTON RADIO, 54 London Road, Bexhill.

## TOP PRICES PAID

for new valves, popular  
 TV & Radio Types

## KENSINGTON SUPPLIES

(A), 367 Kensington Street  
 Bradford B, Yorks

**WANTED!** New valves especially TV types. Cash waiting. Bearman, 6 Potters Road, New Barnet, Herts. Tel. 449/1934.

**NEW VALVES AND TRANSISTORS** wanted. Payment by return. Johnsons (Radio), St. Martins Gate, Worcester.

# B.R.C. LINE OUTPUT TRANSFORMERS

PLEASE STATE  
MAKE & MODEL

\*  
REDUCTION FOR  
QUANTITY

only  
**£1.50** p&p  
each 25p

**CHILTMead LTD.**  
**7 & 9 Arthur Road**  
**Reading**

Tel. No. Reading 582605

## DON'T BE CAUGHT OUT!

Colour television is already here, but 1971 is a big year for colour television with a number of single standard colour sets coming on to the market, engineers with a knowledge of colour television will obviously be in great demand.

## SO DON'T DELAY

We have developed a colour television course geared for the service engineer which will enable him to tackle any problem in colour television.

The course consists of 10 lessons on colour mixing, Pal colour system, colour receivers, decoders, IF circuits, time-bases, convergence, waveforms, set-up procedures, test equipment, fault finding, typical circuits. Fee for complete course 10 gns. Write for details without obligation to:

**DAYLIN ELECTRONICS**  
(Dept. A) 1a Avebury Road  
SOUTHEND-ON-SEA

T.V. TUBES **"VIDEOCHROME"** T.V. TUBES  
FOR BRILLIANCE & DEFINITION



17" £5.00  
19" £5.50  
21" £7.00  
23" £7.50

19" PANORAMA £6.25  
23" PANORAMA £8.25

CASH OR CHEQUE WITH ORDER

TRADE SUPPLIED  
ALL TUBES PRECISION REBUILT AT OUR OWN  
FACTORY BY SKILLED CRAFTSMEN ● EACH TUBE  
BENCH AND SET TESTED TO A VERY HIGH  
STANDARD BEFORE DESPATCH

2 YEARS GUARANTEE ● FREE  
DELIVERY ANYWHERE IN THE U.K.

**VIDEOCHROME TUBES LTD.**  
25 BELLEVUE AVENUE  
RAMSGATE, KENT. Tel. THANET 52914

## NEW VALVES!

Guaranteed and Tested

24-HOUR SERVICE

1R5	-26	DOC90	-80	EF86	-30	PCL85	-40
1S6	-21	DF91	-14	EF89	-24	PCL86	-35
1T4	-14	DF96	-35	EF91	-12	PFL200	-52
384	-26	DK91	-26	EF183	-26	PL36	-47
3V4	-37	DK92	-40	EF184	-29	PL81	-45
5Y3GT	-27	DK96	-36	EL33	-54	PL82	-30
6J30L2	-56	DL92	-26	EL84	-22	PL83	-32
6AQ5	-24	DL94	-37	EY61	-34	PL84	-30
6BW7	-55	DL96	-36	EY86	-30	PL900	-62
6F1	-60	DY86	-24	EZ80	-21	PL504	-63
6F23	-69	DY87	-24	EZ81	-22	PY81	-24
6F25	-55	DY802	-38	GZ37	-70	PY82	-24
6SN7GT	-28	EABC80	-30	KT61	-54	PY800	-33
25L6GT	-20	EB91	-10	KT66	-80	PY801	-33
30C15	-60	EBC33	-38	N78	-85	R19	-30
30C18	-62	EBF89	-29	PC86	-47	U25	-64
30F5	-67	ECC81	-16	PC88	-47	U26	-58
30FL1	-60	ECC82	-19	PC97	-38	U191	-59
30FL14	-69	ECC83	-22	PC900	-32	U261	-65
30L15	-58	ECP80	-27	PCC84	-30	U329	-65
30L17	-68	ECF82	-26	PCF89	-45	UBF89	-31
30P4	-60	ECH85	-27	PCC189	-48	UC85	-34
30P19	-60	ECH81	-27	PCF80	-28	UCH81	-30
30PL1	-60	ECL80	-31	PCF86	-44	UCL82	-33
30PL13	-77	ECL82	-30	PCF801	-30	UCL83	-49
30PL14	-65	ECL86	-35	PCF802	-43	UF89	-29
CCH35	-65	EP39	-35	PCF805	-62	UL84	-31
DAP91	-21	EP80	-22	PCL82	-32	UY85	-26
DAP96	-35	EP85	-27	PCL84	-34	Z77	-18

Postage on 1 valve 6p on 2 or more valves 3p per valve extra. Any parcel insured against damage in transit 3p extra. Office address, no callers.

**GERALD BERNARD**  
83, OSBALDESTON ROAD  
STOKE NEWINGTON,  
LONDON, N.16

# for men of vision rebuilt T.V. tubes

## Current types

17"	£4.75	21"	£5.50
19"	£5.00	23"	£6.00

## Panorama & Rimguard types

19"	£7.00	23"	£9.00
-----	-------	-----	-------

## Twin panel

19"	£7.50	23"	£9.50
-----	-------	-----	-------

Cash or P.O. with order no C.O.D. Free delivery in U.K.

Each tube fitted with new electron gun assembly. Fully guaranteed for two years against any fault except breakage.


Special terms for Hospitals, Orphanages, Old People's homes.

Manufactured in our own factory backed by over 20 years' experience in the field of electronics. Callers always welcome (by appointment) at

# k.s.t. ltd.

Providence Mills, Viaduct Street,  
Stanningly, Nr. Leeds, Yorks.
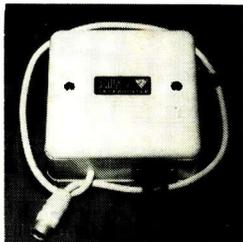
## THE NEW UM4 "COLOURBOOSTER" UHF/625 LINE



**CAN PRODUCE  
REMARKABLE  
IMPROVEMENTS IN  
COLOUR AND  
PICTURE QUALITY  
IN FRINGE OR  
DIFFICULT AREAS  
WITH SIGNIFICANT  
REDUCTION IN  
NOISE (SNOW).**

HIGH GAIN—VERY LOW NOISE  
FITTED FLY LEAD—INSTALLED IN SECONDS  
HIGHEST QUALITY COMPONENTS  
IVORY PLASTIC CASE 3½ x 3½ x 1½ CORK BASE  
CHANNELS: Group A, Red code 21-33  
Group B, Yellow code 39-51  
Group C-D, Green code 52-68

EQUALLY SUITABLE FOR BLACK AND WHITE

### Also the M4 DUAL BAND VHF UNIT

BOOSTS ALL BAND III and ANY SPECIFIED  
BAND I CHANNEL SIMULTANEOUSLY  
NOMINAL GAIN 17-18 DB BOTH BANDS

#### PRICES BOTH TYPES:

£3.75 Battery model or £5.87 Self-contained mains version  
Postage and Packing 13p

### TRANSISTOR DEVICES LIMITED

6 ORCHARD GARDENS, TEIGNMOUTH, DEVON  
Telephone: Teignmouth 4757

## UHF. COLOUR AND TELEVISION SPARES

COLOUR PLESSEY SCAN COILS £5.75 p.p. 35p, CONVERGENCE COILS £3.80 p.p. 25p, BLUE LATERAL £1.25 p.p. 9p, or Complete Set £10 p.p. 50p, MULLARD TYPE, SCAN COILS £3.50 p.p. 35p, CONVERGENCE COILS £1.75 p.p. 25p, LUMINANCE/CHROMINANCE PANEL £1 p.p. 25p, INTEGRATED TRANSISTORISED DECODER UNIT including Circuits £1.25 p.p. 10p, LINE OUTPUT TRANSFORMER including EHT and FOCUS ASSEMBLY £3.50 p.p. 35p. (Shop customers only, assortment Colour Panels of various makes). ALSO COLOUR TV CAMERA UNITS.

COLOUR TV MONITOR PANELS Designed to highest BBC standards. PAL filter & delay £8.00, Chrominance £8.00, Luminance £4.50, Encoded Video Input £2.50 incl. circuit, p.p. 30p. UHF 625 conversion kits and tuners available at reduced prices. Lists available.

UHF Integrated transistd. 6 position push button tuners, leading British makers surplus £4.50 p.p. 35p. Transistd. IF panels (salvaged) £2.50 p.p. 25p.

MURPHY 600/700 series UHF conversion kits in cabinet plinth assembly can be used as separate UHF receiver £7.50 p.p. 50p. 625 IF amplifier incl. 5 valves and circuit £3 p.p. 35p.

SOBELL/GEC Dual 405/625 IF amp and o/p chassis incl. circuit £1.50 p.p. 30p. ULTRA 1980 C to 2384 625 IF amp & switch incl. circuit £1.50 p.p. 30p. PHILIPS 625 P/C IF panel incl. circuit £1 p.p. 25p. GEC 2015 Series Dual 405/625 IF Panel incl. circuit data £1.95 p.p. 30p.

UHF tuners transistd. incl. S/M drive, knobs £3.95, or push button £5.25. Valve type, cyldon £1.75 p.p. 25p.

EKCO/FERRANTI UHF tuner kit, incl. valves, slow motion drive, knobs, leads, aerial panel £5.50 p.p. 30p.

TV SIGNAL BOOSTER UNITS Latest PYE/LABGEAR all station UHF/VHF transistd. "Set back" mains operated £5.90 UHF Masthead £4.25, Power Unit £3.25 pp., 25p.

FIREBALL TUNERS Ferg., HMV, Marconi, New £1.90 p.p. 25p. PUSH BUTTON Plessey, Ekco, Ferranti £1.00 p.p. 25p.

TURRET TUNERS, AB Dual Standard Suitable, Ferguson, Baird, KB etc. 75p, Cyldon C 75p, Ferguson MT7 £2.75, GEC 2018/9 £4.50 p.p. 25p. Large selection channel coils.

LINE OUTPUT TRANSFORMERS. Popular types available, brand new replacements, fully guar. A selection which can be supplied p.p. 25p, C.O.D. 25p.

MURPHY 470 to 530 (oilfilled) ..	£3.75	Bush TV75/85 ..	£2.50
MURPHY 849 to 939 ..	£4.50	Bush TV95/99 ..	£2.50
PHILIPS 17TG100 Range ..	£3.50	BUSH 141, 148, 15KV ..	£2.50
STELLA 1011/1029 ..	£3.50	Murphy 149 ..	£2.50
PHILIPS 19TG111/12 ..	£4.00	159, 15KV ..	£2.50
PHILIPS 19TG121 to 156 ..	£4.50	REG 10-6, 10-17 ..	£2.50
PHILIPS 19TG170, 210 series ..	£4.50	REG 191, 192, 17-18 ..	£2.50
BUSH TV53 to 69 £1.75 105 to 135 ..	£4.50	REGD 610, 711 ..	£2.50
EKCO 221 to 331 (U25 or U26) ..	£3.50	RGD 619, 620 ..	£2.50
FERRANTI 1001/19 (U25 or U26) ..	£3.50		
EKCO 342 to 394, FERRANTI 1021 to 1065 ..	£3.75		
EKCO, FERRANTI 418, 1093 etc. ..	£3.50		

DECCA DM17. 3, 4 (70) DR95, 101/806 DR1. 2, 3, 121, 122 ..	£3.95	LOPT Inserts p.p. 15p	
FERG 305 to 436, 505 to 727 ..	£3.75	Alba 655, 656 ..	£1.75
FERG, HMV, MARCONI, ULTRA, PHILCO 3600, 2600, 4600, 6600, 1100, Jellypot ..	£3.75	Bush 125 to 135 (Round Tag Panel) ..	£2.50
KB QV20, PVP20, VC1 to VC11 ..	£4.00	Coscor 933 to 950 ..	£1.75
MARCONI VT157 to 172 ..	£3.75	Ekco TP308 ..	£1.75
GEC 302 to 346, £2.50, 448 to 452 ..	£3.25	Emerson 700/711 ..	£1.75
GEC 454/6, 2000 series ..	£4.50	KB, NF70, OV30, PV40, PVP20, QV10, 20, 30 ..	£1.75
HMV 1865/9, 1870/6, 1890/1924 ..	£3.75	KB/RGD VCII Featherlight ..	£2.50
PYE C/M/CW series (printed circuit) 17/21, 17S, 110 to 510, 700, 830, 11U to 48 ..	£3.50	KB/RGD VC1-9 ..	£1.75
PAM, INVICTA equiv. LOPTS to above PYE ..	£3.50	Murphy 849 to 939 (Round Tag Panel) ..	£2.50
PETO SCOTT 1419 to 1725 ..	£1.75, 733 to 738 ..	Philco 1961, 1030 series ..	£1.75
SOBELL/McMICHAEL TPS 173, 180, T23, 24, 178, 278, SC24, 270, MP17, 18, M72, M74 ..	£2.50	Philips 17TG100 range ..	£1.75
TPS 781, 279, SC34, 370, MP27, M75, 76, 93, T25, 280, TPS710 ..	£3.25	Pye, VT4, VT7 ..	£2.15
195, 282 to 288, 762, 763 ..	£3.25	RGD D17, 590 to 619 ..	£1.75
SOBELL 196/7, 1000 series ..	£4.50	REG 10-4, 10-17 ..	£1.75
PHILCO 1010 to 1021 ..	£2.25	to 192 ..	£1.75
ULTRA 1770 to 2834 ..	£3.75	Ultra 1770, 1780 ..	£1.75

### PRACTICAL TV 625 RECEIVER

Integrated push button transistorised tuner ..	£4.50	p.p. 25p
Transistorised IF panel ..	£4.75	p.p. 25p
850 line output transformer ..	£3.75	p.p. 25p
850 field output transformer ..	£1.62	p.p. 15p
850 scan coils ..	£3.90	p.p. 25p

(p.p. on complete set of 5 items 50p)

VALVE BASES B9D for PL500 series and colour 12½p p.p. 5p  
SPECIAL OFFER Leading British makers surplus 625 single standard 625 TV chassis, latest design, almost complete, includes transistorised IF stages, frame and line time bases, transformers, etc., incl. circuit £8.65 p.p. 50p.

## MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6

(Near W. Hampstead tube stn; 28, 59, 159 Bus Routes) 01-794 8751

MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11

Staff Holidays: Aug. 16th to 30th

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering ...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

### Mechanical

A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

### Draughtsmanship

A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

### Electrical & Electronic

A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

### Radio & Telecomms.

C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

### Auto & Aero

A.M.I.M.I.  
MAA, IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

### Management & Production

Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

### Constructional

A.M.S.E. (Civ)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

### General

C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

### General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier."—Case History G/321.

"In addition to having my salary doubled, my future is assured."—Case History H/493.

"Completing your Course meant going from a job I detested to a job I love."—Case History B/461.

## FIND OUT FOR YOURSELF

These letters—and there are many more on file at Aldermaston Court—speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B1 Aldermaston Court, Reading RG7 4PF.

## POST THIS COUPON TODAY

To: B.I.E.T., Dept B1, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name ..... Age .....

Address .....

Occupation .....

(Write if you prefer not to cut this page)

