

TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

20p

APRIL
1972

Construct
TELEVISION'S

COLOUR RECEIVER



ALSO:

TWEAKING THE OLDER SET

ALIGNING PAL DECODERS

RENOVATING THE THORN 800/850 CHASSIS

WILLOW VALE



BY RETURN WHOLESALE SUPPLIERS OF:

COMPONENTS

Dubilier capacitors. Erie wire-wound resistors. $\frac{1}{2}$, 1 and 2 watt carbon film hi-stabs. Sprague bias and smoothing electrolytics. Egen presets. AB metal volume controls. Smoothing electrolytics. Printed circuit aerial panels. Valve bases. Belling and Egen co-axial plugs, Din Plugs and sockets. Thermistors (ITT).

TRANSISTORS AND SEMI-CONDUCTORS

Full range of current colour transistors. AC, AF, BC, BF, BD, OC, etc., types always in stock. Rectifiers and VDERS. Full trade discount. Reputable makes. Mullard, Siemens, Valvo, etc.

VALVES

Entire range of entertainment types in stock at 41 per cent or 48 per cent discount. See catalogue for details. *Twelve months' guarantee.*

C.R.T.'s

Full range of monochrome and colour tubes. Rebuilt and new. 2-year and 4-year guarantees. All sizes from 17 in. to 25 in. stocked. Panorama, Rimguard, Mono and Twin-Panel.

LINE OUTPUT TRANSFORMERS

All makes supplied. Exchange units or new replacement transformers. *(Subject to availability.)* Bush, Philips, Pye, Ekco, Sobell/G.E.C., Ferguson, Philco, Ferranti, Peto-Scott, etc., etc.

SERVICE AIDS

Electrolube, Servisol, Multicore Solders, tools, multi-meters in stock.

WE ARE THE ONLY SPECIALIST WHOLESALE TO THE SERVICE ENGINEER

TWO DEPOTS:

Excellent Trade Discounts. Purchase our catalogue, 20p in stamps please. Refunded on first order. Strictly trade only.

OUR REPRESENTATIVES COVER THE COUNTRY AND WILL BE PLEASED TO CALL

4 & 5 THE BROADWAY, HANWELL, LONDON, W.7

Telephones: 01-567 5400 01-567 2971 01-579 3582

42 WEST END, STREET, SOMERSET 045-84 2597

PHILIP H. BEARMAN, A LEADING NAME IN VALVES AND TUBES

Suppliers to H. M. Government

LARGE STOCKS BY LEADING BRITISH AND FOREIGN MANUFACTURERS
TUBES GUARANTEED 2 YEARS, COLOUR 4 YEARS! ALL EX STOCK

Every tube tested before it leaves our premises. Open Saturday mornings

FOR EXAMPLE:

CME1702, AW43-80, CRM173, MW43-80, MW43-69*, CRM172, AW43-88, AW43-89, CME1705, CME1703, C17AF	17"	£5.87p	Cge. 55p
CME1903, CME1902, CME1901, AW47-90, AW47-91, A47-14W, C19AH	19"	£6.87p	60p
CME2101, AW53-88, AW53-89, CRM211, CRM212, MW53-20, MW53-80, CME2104	21"	£7.87p	65p
CME2303, CME2301, AW59-90, AW59-91	23"	£9.50p	65p

* Rebuilds only usually

COLOUR TUBES

4 YEAR GUARANTEE

- * 19" A49.11X, A49.120X £49.00 plus £1 carriage
- * 22" A55.141X, A56.120X £53.00 plus £1 carriage
- * 25" A63.11X, A63.200X £57.00 plus £1 carriage

All prices net trade, old glass not required.

We endeavour to maintain prices but all are subject to alteration without notice

6 POTTERS ROAD, NEW BARNET, HERTS. TEL: 01-449/1934 (Robophone) and 449/1935

TSD282	11"	£12.50
A28-14W	11"	£10.50
MW31-74	12"	£3.00
TSD290	12"	£9.80
13BP4	13"	£14.00
MW36/24 & 44	14"	£4.75
CME1601	16"	£7.50
CME1602	16"	£10.15
CME1906	19"	£10.12
A47-13W		
A47-11W	19"	£9.50
A50-120W	20"	£10.50
CME2306	23"	£15.00
A59-13W		
A59-11W	23"	£11.10
CME2413	24"	£13.00

Plus carriage, but if sea journey, 50p extra

rebuilt T.V. tubes for men of vision

Current types

17"	£4.75	21"	£5.50
19"	£5.00	23"	£6.00

Panorama & Ringuard types

19"	£7.00	23"	£9.00
-----	-------	-----	-------

Twin panel

19" £7.50

Cash or P.O. with order no C.O.D. Carriage free in England, Scotland, Wales. Add 75p for carriage Northern Ireland. For all enquiries please send S.A.E. Each tube fitted with new electron gun assembly. Fully guaranteed for two years against any fault except breakage.

T.V. Aerials U.H.F & Colour.

5 elements £1.25p, 10 elements £1.50p,

17 elements £2.25p, add 32½p p & p.

Please state channel or group.

Each aerial fitted with mast clamp.

Enquiries for other aerials welcome.

k.s.t. ltd.

Providence Mills, Viaduct Street,
Stanningly, Nr. Leeds, Yorks.

DON'T BE CAUGHT OUT!

Colour television is already here, but 1972 is a big year for colour television with a number of single standard colour sets coming on to the market, engineers with a knowledge of colour television will obviously be in great demand.

SO DON'T DELAY

We have developed a colour television course geared for the service engineer which will enable him to tackle any problem in colour television.

The course consists of 10 lessons on colour mixing, Pal colour system, colour receivers, decoders, IF circuits, time-bases, convergence, waveforms, set-up procedures, test equipment, fault finding, typical circuits. Fee for complete course 10 gns. Write for details without obligation to:

DAYLIN ELECTRONICS
(Dept. A) 1a Avebury Road
SOUTHEND-ON-SEA

LINE OUTPUT TRANSFORMERS

ALBA 1090, 1135, 1195, 1235, 1395, 1435 **£5-00.**
ARGOSY 17K10, 17K11, 17K12, 17K14, 19K17, 17K43 **£4-00.**
BAIRD All models price **£5-90.** From model 600 quote part no. normally found on TX base plate.
BUSH TV53 to TUG69 **£2-00.** TV91 to TV139 **£4-75.** TV141 to TV186 please state part number **£4-50.** TV75 to TV86 **£4-00** (except TV80).
COSSOR CT1700U to CT2378A **£5-00.**
DECCA DM4C (70°), DR1, DR2, DR121 **£4-50.** DR95, DR606 **£4-50.**
DEFIANT 9A40 to 9A63. Prices on request.
DYNATRON TV30, TV35, TV36, TV37, TV38, TV39, TV40, TV41, etc. **£4-00.**
EKCO T231, T284, TC267, T283, T293, T311, T326, T327, T330, TMB272, T344, T344F, T345, TP347, T348, T348F, TC347, TC349, TC356, T368, T370, TC369, T371, T372, TP373, TC374, T377A, T393, T394, 433, 434, 435, 436, 437 all at **£4-00.**
FERGUSON 306T, 308T, 406T, 408T, 416, 436, 438, 506, 508, 516, 518, 536, 546, 604, 606, 608, 616, 619, 636, 646, 648, 725, 726, 727, 3600, 3601, 3602, 3604, 3611, 3612, 3614, 3617, 3618, 3619, 3620, 3621, 3622, 3623, 3624, 3625, 3626, 3627, 3629, **£4-00.**
FERRANTI T1001, T1002, T1002/1, T1004, T1005, T1023, T1024, T1027, T1027F, TP1026, T1071, T1072, T1121, TC1122, TC1124, T1125, TC1126 **£4-00.** 1154, 1155 **£4-75.**
G.E.C. BT302, BT342 **£3-50.** BT454DST-456DST, 2012, 2013, 2014, 2015, 2000DS, 2001DS, 2002DS **£4-50.**
H.M.V. 1865, 1869, 1870, 1872, 1874, 1876, 1890, 1892, 1894, 1896. All models to 2645 **£4-00.**
KB OV30, NF70, NV40, PV40, QV10, QV30, RV10, RV20, RV30, PVP20 **£4-50.** Featherlight **£4-50.** VC1-VC2-VC3-VC4 **£4-50.**
MASTERADIO 4013 DST, D500 DST, D507 DST **£4-50.**
MARCONI VT153, VT155, VT156, VT157, VT159, VT161, VT163, VT165, VT170, 4611, 4800, 4801, 4803, 4615 **£4-00.**
MURPHY V310 to 2149 **£4-75.**
PAM 600S to 5106 **£4-00.**
PETO SCOTT. Prices on request.
PHILCO 1019, 1020, 2021 **£4-13.** 1100, 1110, 5600, 5601, 5602, **£4-00.**
PHILIPS 11TG190 to 24T301 **£5-00.**
PILOT PT450, 452, 455, 650, PT651, P60A, P61 **£4-00.**
PYE V200, V400, 200LB, 210, 220, 300F, 300S, 310, 210S, 410, 510, 530, 600, 620, 630, 700 A or D, 710 A or D, 830 A or D or LBA **£4-00.** 11U Series, 11U-P/NO, AL21003, 21F to 61. Part Nos must be given when ordering Pye LOPTS.
REGENTONE 197-198, 298, TV402, TV401, TV501, TV502 **£4-50.** 10-4-10-6, 10-21, 17-18, 10-12, 19-11-192 **£4-00.**
R.G.D. 626, 627, 628, 726, RV202, RV302 **£4-50.** 519-619-620-621C, 723 **£4-00.**
SOBELL 1000DS, 1002DS, 1005DS, 1010DST, 1012, 1013, 1014, 1018, 1019, 1020, 1021, 1032, 1033, 1038, 1039 **£4-50.**
STELLA T1011U to 2149A **£5-00.**
ULTRA 1770, 2170, 1772, 1782, 2172, 1771, 2171, 1775, 2175, 1774, 2174, 1773, 2137, 1980c, 1984c, 100c, 200c, 2380, 2384, 1984, 1985, 1986, 1980, 1980a, 1780, 2180, 2181, 2183, 2182, 1871, 1783, 6600, 6625, 6626, 6628, 6632, 6642 etc. **£4-00.**
Post and Packing 26p. C.O.D. 30p extra. SAE ALL ENQUIRIES.

Dept. "R" E. J. PAPWORTH AND SON LTD.
80 MERTON HIGH STREET, S.W.19 01-540 3513

01-540 3955

VALVES

SAME DAY SERVICE
NEW! TESTED! GUARANTEED!

SETS 1R5, 185, 1T4, 384, 3V4, DAF91, DF91, DK91, DL92, DL94, Set of 4 for **£1-02.** DAF96, DF96, DK96, DL96, 4 for **£1-48.**

1R5	-28	30C15	-58	EABC80	-82	EM80	-38	PCL83	-57	UAF42	-50
185	-22	30C17	-76	EAF42	-50	EM81	-38	PCL84	-34	UBC41	-52
1T4	-16	30C18	-61	EB91	-10	EM84	-32	PCL85	-38	UBF80	-34
384	-26	30F5	-64	EBC33	-40	EM87	-34	PCL86	-38	UBF89	-32
3V4	-37	30FL1	-61	EBC41	-54	EY31	-33	PCL88	-65	UCC84	-32
3U4G	-31	30FL12	-89	EB99	-22	EY86	-29	PCL89	-75	UCC85	-35
5V4G	-35	30FL14	-68	EBF80	-32	EZ40	-43	PEN44	-77	UCP80	-32
5Y3GT	-26	30L1	-29	EBF89	-29	EZ41	-43	PEN36C	-70	UCH42	-58
5Z4G	-35	30L15	-57	ECC81	-17	EZ80	-28	PFL200	-52	UCH81	-32
6J30L2	-54	30L17	-67	ECC82	-20	EZ81	-28	PL36	-49	UCL82	-32
6AL5	-11	30P4	-57	ECC83	-35	EZ30	-34	PL81	-44	UCL83	-55
6AM6	-13	30P12	-72	ECC85	-34	EZ32	-46	PL81A	-47	UP41	-58
6AQ5	-22	30P19	-57	ECC804	-54	EZ34	-48	PL82	-31	UP89	-30
6AT6	-20	30PL1	-60	ECF80	-31	KT41	-77	PL83	-33	UL41	-57
6AU6	-20	30PL13	-89	ECF82	-26	KT61	-55	PL84	-30	UL84	-30
6BA6	-20	30PL14	-65	ECH35	-55	KT66	-78	PL600	-63	UM84	-22
6BB6	-21	35L6GT	-45	ECH42	-59	LN319	-68	PL504	-63	UY41	-39
6B36	-41	35W4	-25	ECH81	-29	LN329	-78	PM84	-33	UY85	-25
6BW7	-53	35Z4GT	-25	ECH83	-40	LN339	-63	PX25	-95	VP4B	-77
6F14	-40	807	-45	ECH84	-38	N78	-87	PY32	-55	W77	-43
6F23	-68	AC/VP2	-77	ECL80	-30	PABC80	-34	PY33	-55	Z77	-22
6F25	-53	B349	-65	ECL82	-31	PC86	-47	PY81	-25	Transistors	
6J7G	-24	B729	-62	ECL86	-35	PC88	-47	PY82	-25	AC107	-17
6K7G	-12	CCH35	-67	EP39	-38	PC86	-42	PY83	-28	AC127	-18
6K9G	-17	CV31	-30	EP41	-60	PC87	-38	PY88	-38	AD140	-37
6Q7G	-35	DAF91	-22	EP80	-23	PC90	-31	PY800	-34	AF15	-20
68N7GT	-30	DAF96	-36	EP85	-28	PCC84	-25	PY801	-34	AF116	-20
6V6G	-28	DF33	-38	E786	-30	PCC85	-25	R19	-30	AF117	-20
6V6GT	-28	DF91	-18	EP89	-26	PCC88	-40	R20	-56	AF118	-48
6X4	-33	DF96	-38	EP91	-13	PCU9	-45	U25	-58	AF125	-17
6X5GT	-28	DH77	-20	EP92	-20	PCC189	-48	U26	-56	AF127	-17
10P13	-58	DL92	-33	EP84	-63	PCF80	-36	U47	-84	OC26	-26
12AT7	-17	DK91	-28	EP18F	-28	PCF80	-25	U49	-58	OC44	-12
12AU7	-20	DK92	-38	EP184	-31	PCF82	-33	U52	-81	OC45	-12
12AX7	-22	DK96	-38	EH90	-35	PCF86	-48	U78	-24	OC71	-12
19B6G6	-80	DL35	-40	EL33	-55	PCF80	-58	U191	-59	OC72	-12
20P2	-67	DL92	-28	EL34	-46	PCF801	-28	U193	-42	OC75	-12
20P3	-77	DL94	-37	EL41	-54	PCF802	-40	U251	-54	OC81	-12
20P4	-92	DL96	-38	EL84	-23	PCF805	-81	U301	-38	OC81D	-12
25L6GT	-19	DY86	-24	EL90	-28	PCF806	-58	U329	-68	OC82	-12
28U4GT	-57	DY87	-24	EL95	-32	PCF808	-68	U801	-80	OC82D	-12
30C1	-28	DY802	-33	EL500	-62	PCL82	-32	UABC80	-32	OC170	-23

READERS RADIO

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Minimum post/packing on 1 valve 7p., on each additional valve, (3p. per valve extra)

Any parcel insured against damage in transit 3p extra.

TV'S 19" NOW £11.95

TWO YEARS GUARANTEE ALL MODELS
405/625: 19" £25-95, 23" £35-95

FREE CATALOGUE

DAILY DEMONSTRATIONS FOR PERSONAL SHOPPERS
 carr. £1-95



COMPONENTS

MUST BE CLEARED

Transistor Radio Cases: 25p each. Size 9 1/2" x 6 1/2" x 3 1/2". Post 15p.

Speakers: 35p. 2 1/2" 8Ω. Brand new. Post 15p.

Press Button Switching Units 4 Banks 25p 6 Banks 35p P. & P. 5p.

Precision Tape Motors: £1-95, 200/250V. Famous German manufacturer. Post 20p.

Transistor Gang Condensers: 20p. Miniature AM. Post free.

Modern Gang Condensers: 30p. AM/FM or AM only 20p. Post 10p.

Record Player Cabinets: £3-75. Designed for the modern auto-changer size 17 x 15 x 7 1/2 PP 55p.

Valve ELL80 50p. Only stock in the country.

Pots: 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg./100 KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg.

COLOUR TV'S

25" £185-00


19" £145-00

A selection of recent years models. U.K. manufacture.

Regret personal shoppers only.

TV TUBES REBUILT

GUARANTEED 2 YEARS

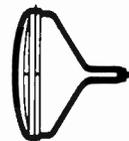

14" £3-95; 17" & 19" £5-95; 21" & 23" £6-45
 Exchange Bowls carr. 55p.

DUKE & CO. (LONDON) LTD.

621/3 ROMFORD ROAD, MANOR PARK, E12

Phone 01-478 6001-2-3

Stamp for Free List

LAWSON BRAND NEW TELEVISION TUBES

SPECIFICATION: The Lawson range of new television tubes are designed to give superb performance, coupled with maximum reliability and very long life. All tubes are the products of Britain's major C.R.T. manufacturers, and each tube is an exact replacement. Tubes are produced to the original specifications but incorporate the very latest design improvements such as: High Brightness Maximum Contrast Silver Activated Screens, Micro-Fine Aluminising, Precision Aligned Gun Jigging, together with Ultra Hard R.F. High Vacuum Techniques.



DIRECT REPLACEMENTS FOR MULLARD-MAZDA BRIMAR GEC, ETC.

A21-11W (P)	AW47-91 (M)	C19/AK (M)	CME1902 (M)	173K (M)
A28-14W (P)	MW43-64 (M)	C21/1A (M)	CME1903 (M)	212K (M)
A31-18W (P)	MW43-69 (M)	C21/7A (M)	CME1905 (M)	7205A (M)
A47-11W (P)	MW43-80 (M)	C21/AA (M)	CME1906 (T)	7405A (M)
A47-13W (T)	MW52/20 (M)	C21/AF (M)	CME1908 (M)	7406A (M)
A47-14W (M)	MW53/80 (M)	C21/KM (M)	CME2101 (M)	7502A (M)
A47-17W (P)	AW47-97 (M)	C21/SM (M)	CME2104 (M)	7503A (M)
A47-18W (P)	AW53-80 (M)	C23/7A (M)	CME2301 (M)	7504A (M)
A47-26W (P)	AW53-88 (M)	C23/10 (M)	CME2302 (M)	7601A (M)
A59-11W (P)	AW53-89 (M)	C23/AK (M)	CME2303 (M)	7701A (M)
A59-12W (P)	AW59-90 (M)	CME1101 (P)	CME2305 (P)	CRM121 (M)
A59-13W (T)	AW59-91 (M)	CME1201 (P)	CME2306 (T)	MW31-74 (M)
A59-14W (T)	C17/1A (M)	CME1402 (M)	CME2308 (M)	A50-120W/R (P)
A59-15W (M)	C17/5A (M)	CME1601 (P)	CRM172 (M)	
A59-14W (T)	C17/7A (M)	CME1602 (P)	CRM173 (M)	
AW36-80 (M)	C17/AA (M)	CME1702 (M)	CRM212 (M)	
AW43-80 (M)	C17/AF (M)	CME1703 (M)	CRM211 (M)	
AW43-88 (M)	C17/FM (M)	CME1705 (M)	23SP4 (M)	
AW43-89 (M)	C17/5M (M)	CME1706 (M)	171K (M)	
AW47190 (M)	C19/10AP (T)	CME1901 (M)	172K (M)	

LAWSON TUBES

18 CHURCHDOWN ROAD,
MALVERN, WORCS.
Malvern 2100

2 YEARS' GUARANTEE FULL TUBE FITTING INSTRUCTIONS

Tubes are despatched day of order by passenger train, road or goods taking far too long for customers satisfaction.

REBUILT TUBES

LAWSON "RED LABEL" CRTS are particularly useful where cost is a vital factor, such as in older sets or rental use. Lawson "Red Label" CRTS are completely rebuilt from selected glass, are direct replacements and guaranteed for two years.

	Brand New Tubes	Red Label Rebuilt	Carr. Ins.
17" (M)	£6-25	£4-97	12" - 19" 62p
19" (M)	£7-25	£5-25	
21" (M)	£8-50	£6-95	
23" (M)	£9-75	£7-25	
19" Twin Panel (T)	£10-25	N.A.	20" - 23" 75p
23" Twin Panel (T)	£15-50	N.A.	
19" Panorama (P)	£9-38	£6-95	
20" Panorama (P)	£10-50	£7-50	
23" Panorama (P)	£11-95	£8-75	
16" Panorama (P)	£8-50		

COLOUR TUBES STANDARD TUBES

METAL BAND TUBES

TWIN PANEL TUBES

Rebuilt with new Electron Guns at under 50% normal list price

SUFFOLK TUBES

LIMITED
261 CHURCH ROAD,
MITCHAM, SURREY
01-640 3133

Britain's largest INDEPENDENT TV Tube rebuilder

Learn at home... First Class Radio and TV Courses



After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

FREE GUIDE


Our Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., A.M.S.E. (Elec.). Guide also gives details of range of certificate courses in Radio/TV Servicing, Electronics and other branches of engineering.

Write now for your copy of this valuable publication. It may well prove to be the turning point in your career.

Founded 1885 Over 150,000 successes
CHAMBERS COLLEGE
(Incorp. National Inst. of Engineering)
(Dept. R58) Aldermaston Court, Reading. RG7 4PF

U.H.F. TV AERIALS

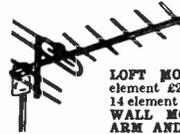Suitable for Colour and Monochrome Reception



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS. 7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75. **WALL MOUNTING e/w WALL ARM AND BRACKET.** 7 element £3-25. 11 element £3-75. 14 element £4-25. 18 element £4-75. **CHIMNEY MOUNTING ARRAYS e/w MAST AND LASHING KIT.** 7 element £4. 11 element £4-50. 14 element £4-75. 18 element £5-25. **MAST MOUNTING arrays** only 7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75. Complete assembly instructions with every aerial. **LOW LOSS** coaxial cable 9p yd. **KING TELEBOOSTERS** from £3-75. **LAGGEAR** all band V.H.F.-U.H.F.-F.M. radio mains operated pre-amps £7-50. State clearly channel number required on all orders. P.p. on all aerials 50p. Accs. 15p. C.W.O. Min. C.O.D. charge 25p.

BBC-TV-FM AERIALS

BBC (band 1) Wall S/D £2. LOFT Inverted 'T' £1-25. EXTERNAL 'H' array only £3. ITV (band 3) 5 element loft array £2-50. 7 element £3. COMBINED BBC-TV loft 1+5 £2-75. 1+7 £3-50. **WALL AND CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from £3-75. **COMBINED U.H.F.-V.H.F. aerials** 1+5+9 £4. 1+5+14 £4-50. 1+7+14 £5. **FM RADIO** loft S/D £1. 3 element £3-25. 4 element £3-50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P.p. all aerials 50p. Accs. 30p. C.W.O. Min. C.O.D. charge 25p. Send 5p for fully illustrated lists.**

CALLERS WELCOMED

OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS

40-41 Monarch Parade
London Road, Mitcham, Surrey
01-648 4884

STEPHENS

**ELECTRONICS, Dept. T,
165 BICESTER ROAD,
AYLESBURY, BUCKS.
Tel: AYLESBURY 84619**

**SEND S.A.E. FOR LISTS
GUARANTEE
Satisfaction or money
refunded.**

GUARANTEED VALVES BY THE LEADING MANUFACTURERS BY RETURN SERVICE

1 YEAR'S GUARANTEE ON OWN BRAND, 3 MONTHS' ON OTHERS

AZ31 50p	ECF80/2 47p	EL1803 85p	PCCR85 42p	PY83 50p	UL41 57p	6AR5 35p	6EJ7 35p	12RE6 32p	30PL1 77p
AZ60 80p	ECF86 55p	EL1821 85p	PCCR88 70p	PY88 41p	UL84 45p	6AR6 32p	6EW6 60p	12BH7 32p	30PL13 90p
CB11 80p	ECH35 67p	EL180 75p	PCCR89 61p	PY500 £1.00	UM80/4 45p	6A85 35p	6F1 70p	12BY7 50p	30PL14 35p
CB13L1 85p	ECH42 66p	EM34 80p	PCCR189 61p	PZ30 80p	UY41 40p	6ASTG 30p	6F8 40p	12K5 50p	35A3 50p
CY31 35p	ECH81 51p	EM71 62p	PCCF80 51p	QUU02-6E210 82p	UY85 34p	6AT6 45p	6F6G 20p	6SR7 37p	35A5 50p
DAF91 41p	ECH83 40p	EM80 40p	PCCF82 52p	QUU03-10 82p	U25 75p	6AU6 29p	6F11 32p	6T8 32p	12Q7G 25p
DAF96 41p	ECH84 47p	EM81 42p	PCF84 47p	U18-20 61p	U26 75p	6AU6 30p	6F12 22p	6U4GT 62p	25p 35C5 35p
DF91 45p	ECL80 40p	EM84 40p	PCF86 61p	QVO3-12 65p	U191 72p	6BA6 47p	6F13 35p	6U8 35p	12SH7 25p
DF96 45p	ECL82 49p	EM87 40p	PCF200/1 81p	R19 85p	U183 41p	6BE6 60p	6F14 60p	6V0GT 32p	35L6GT 47p
DK91 57p	ECL83 57p	EN91 37p	PCF801 81p	R20 75p	U301 85p	6BH6 42p	6F15 55p	6X4 25p	12SJ7 25p
DK92 57p	ECL86 49p	EY51 40p	PCF802 61p	SU2150A 75p	W729 55p	6BJ6 42p	6F18 40p	6X5GT 27p	12SK7 40p
DL96 37p	ECLM900 45p	EY80 45p	PCF805 65p	TT21 22.40	Z759 £1.22	6BK7A 50p	6F22 32p	6X8 55p	12SL7GT 40p
DL94 37p	EY80 45p	EY81 40p	PCF806 61p	TT22 22.50	OA2 32p	6BL8 35p	6F23 77p	6Y0G 80p	12SN7GT 40p
DL96 46p	EF39 52p	EY83 55p	PCF808 67p	U18-20 67p	OA3 45p	6BN5 42p	6F24 67p	7Y4 80p	12SQ7 40p
DM70 32p	EF80 40p	EY86 40p	PCH200 70p	U26 67p	OB3 32p	6BN5 40p	6F25 75p	9B5W6 42p	12SR7 32p
DY86/7 40p	EF83 50p	EY87 42p	PCL82 61p	U25 75p	OB3 50p	6BQ5 25p	6F26 35p	10C2 50p	14S7 80p
DY802 42p	EF85 41p	EY88 42p	PCL83 61p	U26 75p	OC3 35p	6BR7 75p	6F28 70p	10D1 40p	20D1 45p
E55L £2.75	EF86 66p	EZ35 27p	PCL84 51p	U31 45p	OD3 32p	6BR8 95p	6F29 32p	10D2 40p	20L1 £1.00
ER8CC 40p	EF89 40p	EZ40 45p	PL85 52p	U37 £1.50	3Q4 40p	6BW6 82p	6F30 35p	10F1 90p	20P1 50p
EL10L £4.50	EF91 42p	EZ41 45p	PL86 51p	U50 30p	3R4 35p	6BW7 69p	6J4 47p	10F9 50p	20P3 80p
EL10F 85p	EF92 50p	EZ20 27p	PL800 £1.52	U52 30p	3V4 40p	6BW6 25p	6J6GT 30p	10F18 40p	20P4 £1.00
EA3C80 52p	EF93 47p	EZ81 27p	PL200 74p	U76 25p	5R4GY 35p	6BZ6 32p	6J7 42p	10L1 90p	20P5 £1.00
EAF42 50p	EF94 77p	EZ90 25p	PL36 61p	U78 25p	5U4G 30p	6C4 30p	6K7 32p	10LD11 55p	25C5 45p
EBC33 55p	EF95 62p	GS10C 25.00	PL38 90p	U191 75p	5U4GR 37p	6C5GT 35p	6K7 32p	10L13 55p	25L6GT 37p
EBC41 47p	EF183 56p	GY501 80p	PL81 51p	U201 35p	5V4G 40p	6CD6G £1.40	6K8G 30p	10P14 £1.00	25Z4G 30p
EBC81 32p	EF184 35p	GZ30 37p	PL81A 62p	U281 40p	5V3GT 30p	6CA 27p	6K23 50p	12A85 50p	25Z6GT 50p
EBC90 47p	EF20F £2.10	GZ31 30p	PL82 36p	U282 40p	5Z3 45p	6CA7 52p	6K25 75p	12AC6 37p	30A5 40p
EBF80 40p	EF80 £1.00	GZ32 40p	PL83 51p	U301 57p	5Z4GT 40p	6CB2 27p	6G4GT 45p	12AD6 37p	30FL3 50p
EBF83 40p	EF84 £1.00	GZ33 40p	PL84 51p	U403 50p	6B3L2 75p	6CD6GA £1.15	6L7 32p	12AE7 37p	30FL4 77p
EBF89 40p	EF811 75p	GZ34 55p	PL500 82p	U404 37p	6A4 32p	6CC7 45p	6L18 30p	12A15 40p	30C17 80p
EB91 26p	EL34 52p	HK90 32p	PL504 85p	U801 £1.00	6AF4A 47p	6CH6 55p	6LD20 32p	12AQ5 40p	30C18 75p
EC53 50p	EL36 47p	HL92 35p	PL605 £1.45	UABC80 52p	6AG7 37p	6CL6 50p	6N7GT 35p	12AT6 25p	30F5 85p
EC86 60p	EL41 55p	HL94 40p	PL608 £1.00	UBF89 40p	6AH6 50p	6CW4 62p	6P1 60p	12AU6 75p	30FL1 55p
EC89 60p	EL42 57p	KT66 £1.37	PL509 £1.54	UBC41 49p	6A18 29p	6CY5 40p	6P25 £1.05	12AV6 30p	30FL2 92p
EC90 30p	EL41 50p	KT88 £1.86	PL802 80p	UCB5 46p	6AK5 30p	6CY7 60p	6P28 62p	12AV7 45p	30FL3 50p
EC92 32p	EL43 41p	N78 £1.05	PL805 88p	UCH42 89p	6AK6 57p	6D3 40p	6Q7 37p	12AV8 45p	30FL4 77p
EC93 47p	EL45 42p	PABC80 40p	PY33 62p	UCH81 54p	6AL3 42p	6D0C 67p	6R7G 35p	12AX7 30p	30L1 45p
EC98 40p	EL46 42p	PBC8/S 51p	PY80 32p	UCL82 51p	6AL5 48p	6DK6 42p	6S2 40p	12AY7 67p	30L15 85p
EC98/2 3 42p	EL90 32p	PC95 36p	PY81 41p	UCL83 61p	6AM5 25p	6DQB 60p	6S4 60p	12BA4 50p	30L17 80p
EC98/4 5 42p	EL91 25p	PC97 41p	PY800 41p	UF41/2 55p	6AM6 22p	6D84 75p	6S7 37p	12BA6 32p	30P12 85p
EC98/5 6 42p	EL95 35p	PC97 41p	UF801 41p	UF80/5 37p	6AQ5 32p	6E8A 55p	6S7 37p	12BA6 32p	30P15 35p
ER8CC 52p	EL950 £1.15	PC984 46p	UF82 35p	UF89 41p	6AQ6 50p	6EH7 32p	6S7 37p	12BA7 32p	30P19 75p

CATHODE RAY TUBES

New and Budget tubes made by the leading manufacturers. Guaranteed for 2 years. In the event of failure under guarantee, replacement is made without the usual time wasting forms.

Type	New	Budget	Type	New	Budget
	£	£		£	£
MW35-20		£4.50	A50-120W/R	CME2013	£10.85
MW35-21		£4.50	AW35-80		£8.93
MW43-69Z	CRM171	£6.60	AW35-88	CME2101	£8.93
	CRM172	£6.60	AW59-90		£7.20
MW43-80Z	CRM173	£6.60	AW59-91	CME2303	£9.58
AW43-80Z	CME1702	£6.60	A59-15W	CME2301	£7.20
	CME1703	£6.60		CME2302	£9.58
	CME1706	£6.60	A59-11W	CME2303	£13.65
	C17AA	£6.60	A59-13W	CME2306	£10.97
	C17AF	£6.60	A59-16W	CME2305	£12.60
AW43-88	CME1705	£6.60	A59-23W	CME2305	£10.50
AW47-90			A59-23W/R		£12.60
AW47-91	A47 14W	£5.95	A61-120W/R	CME2413	£13.50
A47 14W		£5.95	A65-11W	CME2501	£16.50
	CME1902	£5.95	A49-191X		£5.50
	CME1903	£5.95	A56-120X		£6.50
	C19AH	£5.95	A63-11X		£6.50
147 13W	CME1906	£10.27			
A47-11W	CME1905	£8.86			
A47-26W	CME1906	£8.86			
A47-26W/R	CME1913R	£9.33			

A discount of 10% is also given for the purchase of 3 or more tubes at any one time. All types of tubes in stock. Carriage and insurance 75p anywhere in Britain.

TRANSISTORISED UHF TUNER UNITS NEW AND GUARANTEED FOR 3 MONTHS

Complete with Aerial Socket and wires for Radio and Allied TV sets but can be used for most makes.

Continuous Tuning, £4.50; Push Button, £5.00.

SERVICE AIDS

Switch Cleaner, 55p; Switch Cleaner with Lubricant, 55p; Freezes 82p. P. & p. 7p per item.

PLUGS

Jack Plugs and Sockets Co-Axial Plugs
Standard Plugs 19p Belling Lee (or similar type) 61p
Standard Sockets 12p Add 2p per doz. p. & p.

LINE OUTPUT TRANSFORMERS

G.E.C. BT454	£4.75	G.E.C. 2028	£4.75
G.E.C. BT456	£4.75	G.E.C. 2041	£4.75
G.E.C. 2010	£4.75	G.E.C. 2000 Series	
G.E.C. 2013	£4.75	Philips 19TG	£4.75
G.E.C. 2014	£4.75	Pye Mod. 36	£4.75
G.E.C. 2018	£4.75	Pye Mod. 40	£4.75
G.E.C. 2043	£4.75	Thorn 800-850	£4.75
G.E.C. 2048	£4.75		

STYLI—BRITISH MANUFACTURED

All types in stock.
Single Tip "S" 13p Double Tip "S" 35p
Single Tip "D" 37p Double Tip "D" 47p
"S" = Sapphire "D" = Diamond

CARRIDGES

ACOS	Inc. P.T.	each	B.S.R.	S/S	each	RONETTE	Inc. P.T.	each
GP79	£0.63	X3M	S/S		105	S/S	90p	
GP91-18c -1	£1.05	X3H	S/S		106	S/S	99p	
GP91-28c	£1.05	X3M	S/S		DC400	S/S	70p	
GP91-38c	£1.05	X3M	S/S		DC400SC	S/S	70p	
Suitable to replace		X3H	S/S		105	D/S	£1.11	
TC8		X3M	D/S		106	D/S	£1.11	
GP92	£1.32	X3H	D/S		DC400	D/S	84p	
GP93-1	£1.24	X4N	D/S		DC400SC	D/S	84p	
GP94-1	£1.55							
GP94-5	£1.80							
GP95	£1.24	850						
GP96	£1.57	6800						
ACOS		6800E						
104	1-10	£2.09	6800 Super E					

SEMICONDUCTORS BRAND NEW MANUFACTURERS MARKINGS NO REMARKED DEVICES

2N388A	80p	8N3704	23p	AF116	25p	BC118	33p	BF115	25p	T1843	40p
8N697	20p	8N3705	20p	AF117	25p	BC134	58p	BF117	48p		
2N598	25p	8N4061	23p	AF118	60p	BC135	P/A	BF163	35p	DIODES & RECTIFIERS	
2N704	13p	8N4062	18p	AF119	15p	BC136	P/A	BF167	25p		
8N706A	13p	8N4280	18p	AF125	20p	BC137	P/A	BF173	33p	1N914	8p
8N830	28p	8N4291	18p	AF126	20p	BC138	P/A	BF178	35p	AA119	10p
8N1132	33p	RCA	AF127	18p	BC142	30p	BF179	73p	BA102	23p	
8N1303	18p	40253	P/A	AF139	38p	BC143	P/A	BF180	35p	AA115	9p
8N1305	28p	40398	P/A	AF178	45p	BC147	18p	BF181	35p	BA114	13p
8N1306	25p	40458	P/A	AF179	45p	BC148	15p	BF184	25p	BY100	23p
8N1307	25p	AC107	30p	AF180	53p	BC149	18p	BF191	23p	BY126	23p
8N2614	30p	AC117	60p	AF181	43p	BC152	18p	BF195	25p	BY127	23p
8N3826	30p	AC126	20p	AF186	67p	BC158	18p	BF196	43p	BY288	
8N4905	P/A	AC127	25p	AF239	43p	BC169B	14p	BF197	32p	(Series)	33p
8N4911	P/A	AC128	20p	AF238	28p	BC169C	15p	BF200	37p	OA5	13p
8N4912	25p	AC175									

TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

VOL 22 No 6
ISSUE 258

APRIL 1972

CONSTRUCTORS' COLOUR

THIS month we introduce a project which has long been promised to readers—a colour set for the constructor. The receiver is capable of the highest standards of performance, featuring automatic frequency, chrominance and gain control, RGB tube drive with effective black-level stabilisation, colour and contrast controls which track together and if the constructor wishes the latest varicap type tuner unit (other tuners can be used instead). In addition care and thought have been given to the design of a suitable cabinet so that you can at the end have a set the whole family can live with.

While the set uses high-performance circuitry we do not however make any claims to originality in this respect. That would not have been the object of the exercise. What is required is circuitry of proven performance and reliability, so the set is based on well-known circuits with an established reputation. This does not mean that we are adverse to novel ideas, and we hope to publish further circuits—in fact the venturesome will have seen many other approaches described by our regular contributors—at a later date. To start with however it is obviously best to keep to a well-trodden path: we can hardly ask you to spend not a little time and money on such a project without being certain of its basic soundness. Slight modifications to the original circuits have however been undertaken with a view to making them less critical and consequently better suited to one-off construction.

There is everything to be said for learning from experience and we hope and expect that this project will open up the subject to many newcomers to colour. With this in mind the constructional details will be accompanied by full circuit descriptions.

As readers of Part 1 will find out considerable thought has been given to devising ways to help those who get into difficulties. That said however we must nevertheless emphasise that this project is not one to be undertaken lightly. While the individual backroom genius may find he can put the set together with no trouble at all this is unlikely to be everyone's experience. Perhaps for those who are used to mulling matters over with their friends a joint approach would be best to start off with.

But however you decide to tackle it, we wish you every success and hours of happy viewing at the end. To provide a speedy check on whether any snags arise in practice a couple of further prototypes are being constructed using the specified components. With this "monitoring" we expect to be able to iron out any last minute problems.

W. N. STEVENS, *Editor*

THIS MONTH

Teletopics	246
Long-Distance Television	<i>by Roger Bunney</i> 248
A Closer Look at PAL—Part 5—Aligning PAL Decoders	<i>by E. J. Hoare</i> 251
Renovating the Rentals—Part 2—Thorn 800 and 850 Chassis	<i>by Caleb Bradley, B.Sc.</i> 258
For the Service Engineer	263
The TELEVISION Colour Receiver—Part 1	264
Servicing Television Receivers—Bush TV103/TV105 Series—continued	<i>by L. Lawry-Johns</i> 268
TV Test Report—The Antiference AK10 Aerial Kit	<i>by E. M. Bristol</i> 270
Service Notebook	<i>by G. R. Wilding</i> 272
Tweaking the Older Set	<i>by Vivian Capel</i> 273
Colour Receiver Circuits—The Burst Channel	<i>by Gordon J. King</i> 276
Your Problems Solved	280
Test Case 112	282

**THE NEXT ISSUE DATED MAY
WILL BE PUBLISHED APRIL 17**

Errors: Some gremlins seem to have got into our issue last month. In addition to one or two mis-spellings there was the unfortunate howler on page 215 where the heading should have read "Bush TV103/TV105 Series," not "Sobell ST282 Series—cont." This was due to the wrong heading being inserted at the platemaking stage, after passing for press. There is no connection between the RBM and Sobell-GEC groups. Our apologies to all,

TELETOPICS



START OF SATELLITE TV

The first experimental TV broadcasting service from a satellite direct to TV receivers is due to start in mid-1973 in the Rocky Mountain area of the USA, with transmissions at 2500MHz. The service will provide educational programmes to some 500 communal receivers in schools, public broadcast stations, cable networks and so on, though it has been stated that there is nothing to prevent individuals buying converters with parabolic aerials (at \$150-200) to pick up the transmissions direct. The satellite is the one intended later for a stationary orbit over India to provide direct educational TV for communal sets there.

SERVICING CAREER AND WAGE STRUCTURE

With the aim of providing a career and wage structure the Scottish installation contracting industry's Joint Industry Board has introduced a system of grading and standardised rates of pay for service engineers in two sections of the industry, those carrying out audio/TV work and those repairing electrical appliances. The scheme is an extension of the already established graded rates for electrical installation operatives and the Scottish JIB has sent a circular to employers of audio, TV and domestic appliance servicemen all over Scotland inviting firms and their engineers to join the scheme.

In the audio/TV section there are three pay grades for qualified technicians, with apprentices getting an increasing percentage of the rate for trained men as they progress. The top rate of 80 pence an hour goes to technicians aged at least 27 years who have experience of supervision and are capable of completing 55 service calls a week. The qualification required for this grade is the complete C & G course 48, course 433 or equivalent. The rate for grade 2 technicians is 74 pence per hour. To qualify for this grade technicians must be at least 22, able to make 50 calls a week and have the C & G course 48 part 1, course 433 part 2 or equivalent. For grade 3 a technician must be aged 20 or over, capable of 45 weekly calls, have completed a recognised apprenticeship or equivalent course and have gained C & G course 433 part 1 or equivalent. Aerial installers are also included: the rate for qualified riggers is 54 pence per hour and for grade 2 riggers 49 pence an hour.

These ideas of the Scottish electrical contracting industry have been criticised by the RTRA, the Scottish branch of which claims to have been working for some time on a plan based on job description and minimum rather than fixed rates. The English RTRA

has expressed strong reservations about the job-description gradings and even more about the fixed-rate idea. It seems however that the Scottish contractors have stirred things up and induced some sense of urgency. To us it seems high time that the undoubted skills of service engineers received due recognition and recompense.

TRANSMITTER NEWS

The BBC-1 u.h.f. service from the **Windermere** relay station has now started, on channel 51 with vertical polarisation (receiving aerial group B). Three more ITA relay stations have been brought into service: **Kilvey Hill** (Swansea) carrying HTV Wales programmes on channel 23 (receiving aerial group A, vertical polarisation); **Fenton** (Stoke-on-Trent) carrying ATV programmes on channel 24 (receiving aerial group A, vertical polarisation); and **Halifax** carrying Yorkshire Television programmes on channel 24 (receiving aerial group A, vertical polarisation).

The broadcasting authorities appear to be in a bit of a pother just now, having discovered that their u.h.f. transmitters are giving about 25% more service area than expected: good news for those of you able to get extra programmes as a result, but there could be co-channel interference problems as more stations are brought into operation.

RANGE OF HELICAL AERIALS

A range of helical u.h.f. aerials has been introduced by Precision Electro Mechanical Services Ltd., 12b Grove Road, London E3. The Enterprise range features a spiral active element and circular grid reflector. Advantages claimed are high power gain, high front-to-back ratio and less susceptibility to fading caused by multipath reception and wind movement. There are two group A versions, the A6 with a six-turn active element and the A9 with a nine-turn active element, and group B and C versions which both have nine-turn active elements.

TELEFUNKEN FIRST WITH 110° COLOUR

The first colour receiver with a 110° c.r.t. has now been introduced in the UK. This is a 26in. model from **Telefunken** and has a cabinet depth of only 18in. The chassis is a hybrid one employing 47 transistors, one i.c. and 5 valves. Valved timebases have been adopted rather than the solid-state techniques described in our pages last month. Features include five slider-type user controls and a varicap tuner. The price is £398.

Two new monochrome models have been introduced by **Alba**, the T1520 which is fitted with a 20in. tube and the 24in. Model T1924. It is interesting to note that these models use the BRC 1500 chassis: Alba have been using Philips chassis since they ceased producing their own in 1965.

A new 24in. monochrome receiver fitted with the Pye group 169 chassis has been introduced in the Pye and Ekco ranges. The **Ekco** version is Model T543 at £89, the **Pye** version model 161 at £88.

Reports of a high level of business come from the rental organisations who say that four out of every five colour sets at present going into people's homes do so on a rental basis.

THE VIDEOCASSETTE STANDSTILL

We have received further information on the reasons behind the standstill in videocassette development in the US. Apparently the Federal Communications Commission (FCC), which has power to control interference-causing r.f. radiation, has suggested a maximum output voltage of 2mV r.m.s. for devices such as videotape recorders, videocassette players, CCTV cameras and so on which provide an output consisting of an r.f. carrier modulated with a TV signal for feeding to the 300Ω (US standard practice) aerial input socket of a TV set, and has also proposed limits for spurious radiation from such equipment. Since many of the devices available or under development have outputs of 1V or more something of an impasse has been created.

SPECIAL SETS FOR CATV?

A report from Macclesfield Relay of difficulties encountered in using standard colour receivers for wired TV systems reminds us of a report in the US journal *Radio-Electronics* last September of just such problems there. The basic difficulty is inadequate i.f. selectivity and adjacent channel rejection. Macclesfield Radio comment that severe patterning on colour is caused by beating between certain ITA vision and BBC sound channels, and say that some chassis are affected far more than others. To overcome the problem Macclesfield Relay is to reduce the frequency of its BBC-1 channel by 1.75MHz. Since the Minister of Posts and Telecommunications is at present giving encouragement to the setting up of wired systems this is a problem that could be of increasing importance. In the US, the National Cable TV Association has asked the FCC to set standards for special receivers for cable TV systems and we understand that some US setmakers are developing special sets for use with wired TV distribution systems.

DEVELOPMENTS

The tubeless TV camera is of course the corollary of the flat TV set you hang on the wall. Both may eventually become practicable with advances in semiconductor technology though the well-tried thermionic devices seem in no danger for the foreseeable future. As a step towards the tubeless TV camera RCA Laboratories have released details of their work on a solid-state sensor consisting of a silicon integrated circuit with 1,408 photo-sensitive elements. When light is focused, using an ordinary camera lens, on this structure the elements take up a charge of strength proportional to the intensity of the light reaching

them. These charges are read out in sequence using shift-registers. The present experimental device is said to be capable of providing a recognisable picture, especially of alphanumeric characters. To reach broadcast picture standards an array with some half a million elements would be needed. The next stage in RCA's programme is to develop an array of 10,000 elements.

Meanwhile Laser Video Inc. in the US are developing wide-screen laser-driven colour TV receivers. The model being worked on has a screen diameter of approximately 56in., is wall-mounted and approximately 9-10in. deep.

OFFICIAL STATEMENTS

The Minister of Posts and Telecommunications Christopher Chataway has stated in the House of Commons that he is "not persuaded that the time has yet come to allocate the fourth TV network". He has however "decided to end the restriction on hours of television broadcasting".

Christopher Chataway has also revealed that an extra 100,000 new television licences have been taken out since the TV licence Anti-Evasion Campaign was started last October. This represents additional revenue of about £1¼ million.

NEWS FROM MAZDA

Mazda have completed their annual review of valve and tube types to be included in their lists, and some more old friends go. Valve types 6F24 and 10LD3 are now obsolete, though the GZ34 has been added. Picture tube types CME1702, CME1705, CME1902, CME2101, CME2104, CME2301 and CME2302 are now classified as obsolescent, which means that they will continue to be available as long as stocks last but that there will be no further production. It makes us feel old: surely it was just the other day that the 19in. tube arrived on the scene?! And whatever happened to those CRM types? It does of course mean more scope for the dabbler in finding ways of keeping those old sets the local shops won't look at going!

Mazda also say their *Mazda Book of PAL Receiver Servicing* sold out in just six weeks but that a further reprint is expected shortly. This seems to confirm our own high opinion of the book.

AERIAL INSTALLATION ADVICE

Commenting on the work of the Antiference Mobile Research Unit Ralph Stallworthy has made a number of worthwhile points about current aerial installation problems. For instance, even with low-loss cable a great deal of signal can be lost through too heavy stapling, extra care being needed with semi-airspaced types. Cable kinking can also cause losses. The provision of a drip loop where the feeder enters the aerial junction unit is advised to prevent the connections being regularly wetted and eventually breaking down. For receiving extra ITV stations separate downleads with an aerial switch are recommended to prevent signal break-through in relatively inefficient combining units. Aerial amplifiers are apparently quite often badly installed, with bad connections (loose or completely unconnected braiding for example) and damaged components (especially misplaced coils).

LONG-DISTANCE TELEVISION

ROGER BUNNEY

JANUARY has been a very quiet month. The improved Sporadic E openings noted during December continued into the first two weeks of January as several ever vigilant enthusiasts can confirm. It seems that medium distance skip was prevalent as the West German/Czechoslovakian directions were preferred, particularly on the 8th January over the late morning period. Since that date reception seems to have been confined to the more usual forms of Meteor Shower (MS). My own log for the period reflects the rather depressed conditions. It is possibly significant to note that on most days reception of sorts is possible, though mainly of short-duration bursts. For anyone despairing of the apparent lack of signals I suggest tuning to an empty Band I channel, accurately setting the line and field hold controls, increasing the receiver gain to maximum—with of course an aerial amplifier—and waiting patiently. Eventually some short bursts of signal will be seen, if not on the first day then on the second. The best period to operate in this mode is the early morning period between 0730-0900 when MS activity is at its best. The other advantage is that many of the European broadcasters are on earlier than the UK transmitters—as most of Western Europe keeps to CET rather than GMT, CET being +1 hour GMT.

Now on to my own log:

- 1/1/72 DFF (East Germany) E4; TVP (Poland) R1—(both MS).
- 2/1/72 RAI (Italy) IB (MS); NOS (Holland) E4 (trops).
- 4/1/72 NRK (Norway) E3; SR (Sweden) E2—(both MS).
- 5/1/72 SR E2 (MS); BRT (Belgium) E2 (trops).
- 7/1/72 NRK E3; SR E2, 3—(both MS).
- 8/1/72 DFF E4; SR E4; RAI IB—(all MS).
- 9/1/72 SR E4 (MS); BRT E2 (trops).
- 11/1/72 Switzerland E2; WG (West Germany) E2; SR E2—(all MS).
- 12/1/72 NRK E3 (MS).
- 13/1/72 DFF E4 (MS).
- 15/1/72 DFF E4 (MS); NOS E4; BRT E2—(both trops).
- 16/1/72 NOS E4; BRT E2—(both trops).
- 17/1/72 DFF E4 (MS).
- 20/1/72 NRK E3; SR E2—(both MS).
- 21/1/72 WG E4; NRK E3—(both MS); TVP R1 (Sp.E).
- 22/1/72 NOS E4 (trops).
- 23/1/72 NOS E4; BRT E2 (both trops).

- 24/1/72 SR E3; ORF (Austria) E2a (both MS).
- 25/1/72 Unidentified Sp.E pulse and bar pattern, long duration but weak, thought to be CT (Czechoslovakia) 0835-0844.
- 26/1/72 SR E3, 4 (MS).
- 29/1/72 DFF E4 (MS); NOS E4 (trops).
- 31/1/72 WG E2 (MS).

In the December column we reported some very long-haul u.h.f. DX signals in the United States. The WTFDA, Milwaukee has now sent us some detailed information of this rather epic reception. It appears that our old friend and veteran TV-DX enthusiast Bob Cooper of Oklahoma City, Oklahoma has been successful in the reception of two u.h.f. stations at distances over 1,200 miles. To quote the words of Bob himself as detailed in his report: "Tropical storm 'Beth', sitting off the New England shore, sucked up moisture from the Gulf Coast of Texas, and dead NE along a stalled NE/SW front, setting up a *super duct* that will long be remembered. Reports have it Oklahoma was too far West for the action, except between 0730-1030 August 17th. Then we had it, as you shall see. Net results: u.h.f. like never before, including snow-free WBJA-34 at 1,245 miles, weak but loggable (thanks to a clear channel) WSBK-38 at 1,491 miles and much more." The ch.A34 WBJA transmitter is located at Binghamton, NY, and ch.A38 WSBK at Boston, Mass. I am sure you will all agree that this reception is quite a fantastic distance for the frequencies involved. It shows what can be received by the ever vigilant DX enthusiast. Our congratulations to Bob Cooper.

Sun Spots


Predictions for the next six months, courtesy Swiss Federal Observatory: January 52, February 50, March 48, April 47, May 45, June 44. Solar activity during December remained at quite a high level and on several days the individual count reached over the 100 mark. Indeed on the 17th December the count reached as high as 131.

News

Yugoslavia: We recently indicated that JRT-Yugoslavia would be starting a u.h.f. service and now have news of the first transmitters. Situated in the Serbian part of the country, the second programme—in PAL colour—radiates from Avala ch.E22; Crveni Cot ch.E24; Jastrebac ch.E27. All the transmitters radiate with 1,000kW e.r.p., with believed to be horizontal polarisation.


Finland: Our good friend Seppo J. Pirhonen from Lahti advises of test transmissions. The TV1 network uses the electronic card (SWF type) and the TV2 network the familiar test card G. Test transmission times are: weekdays 0700-1400; Saturday 0700-1200. The TV1 network on Wednesdays has a shortened test transmission from 0700-1200. All times GMT.

Belgium: It appears that Belgium is now carrying the electronic test card type PM5544 on all v.h.f./u.h.f. transmitters. The card carries identification indicating either the BRT or RTB network but no other identification at present. We do not know if this is to be permanent, i.e. replacing the other cards that have been used up to the time of writing. Peter van der Kramer of the Europese testbeeldjagers has sent a photograph of the Schoten transmitter using this type of card just after the transmitter had opened. It is interesting to note that during the good tropospheric conditions that occurred at the

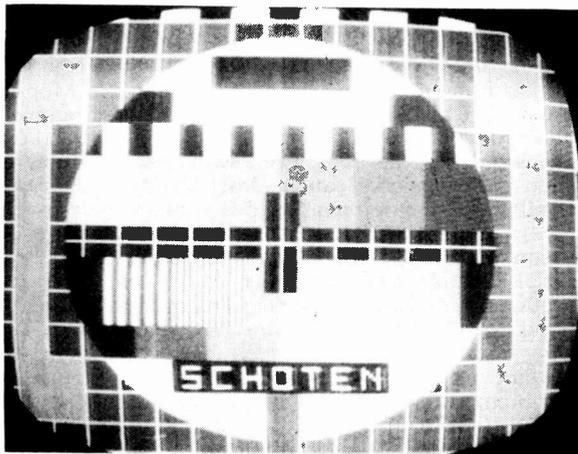


PM5544 electronic test card, Schoten, Belgium. Courtesy P. D. van der Kramer.

DATA PANEL 9—2nd series

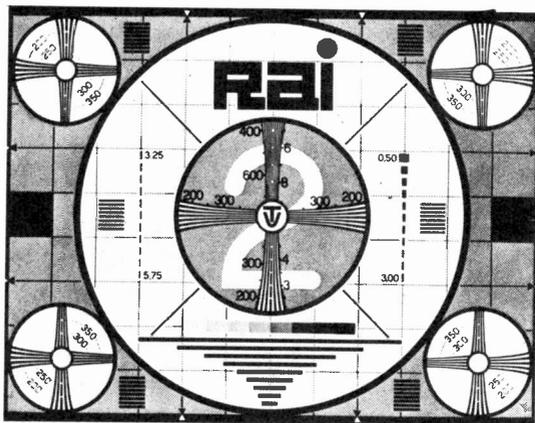

Italy—RAI—Radiotelevisione Italiana

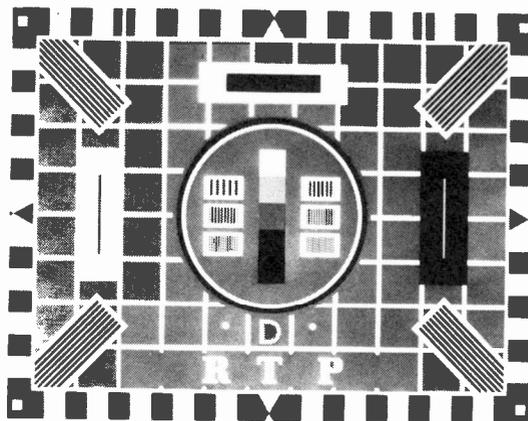

Portugal—RTP—Radiotevisao Portuguesa

Italy: Two basically similar test cards are in use. The 1st National Programme transmitters on v.h.f. use a card similar to that shown above left except that the letter N is superimposed within the centre circle. The 2nd Programme transmitters use the test card as shown. The main transmitters of the National Programme carry an identification number within the centre of the top right-hand circle. The list of these transmitters was given in the May, 1971 DX-TV column, page 310. Additions are: Gambarie Ch. D (19) and Badde Urbara Ch. D (28).

Portugal: Either test card D or E is used, as shown (above right). The checkerboard pattern (see Data Panel 2 of this series) is also extensively used. Test card D courtesy Keith Hamer, Derby.

time of the transmitter opening the identification machine that electronically inserts the station name was faulty, the "Scho" of Schoten flashing on and off. This effect was reported over a wide area.

Spain: From time to time we receive reports of the TVE transmitter at Guadalcanal ch.E4 using the EBU test pattern with an identification "Guadcanal". Apparently this is used for Eurovision purposes when programmes are being relayed to certain North African countries.

Monte Carlo: In connection with the reports of activity with Tele Monte Carlo and a proposed coverage from a high-powered transmitter in the Alps over parts of Northern Italy we have now heard from our correspondent in Bergamo, Northern Italy about the situation there: he personally has seen no signals! A friend of his at Marseille advises that there is a high-powered transmitter "in a very favourable place on the Alps and this must cover North Italy as far as the Adriatic." An official letter from TMC headquarters to our Italian contact advises that only a low-powered transmitter is located on Mt. Agel (their existing v.h.f. transmitter site) and that it can only be received to the West of the Riviere Ligure. The channel used is E35. It seems that the area is part of the target coverage of a high-powered RAI (Italian) transmitter on ch.E34. As we seem to have covered this matter rather extensively in recent issues I propose to drop it until signals are being received: further speculation can only lead to greater confusion!

The EBU tell us that the subscription for the 17th edition of the "List of Television Broadcasting Stations" will be increased from 200 to 300 Belgian Francs. The new edition will commence from March 1st, 1972, with the usual main list, six bimonthly supplements and a map. This excellent list is available from The European Broadcasting Union, 32 Avenue Albert Lancaster, B-1180, Bruxelles, Belgium.


Data Panels

A letter has come from John Wood of Evesham who wishes to correct an error that crept into Data Panel No. 7 relating to the Radio Telefis Eireann test card. Test card


E has now been dropped and a completely different type is now in use bearing the identification "RTE". We have written again to the broadcasting authorities there and hope that they come up with a current photograph of the card concerned. This will be included as soon as possible. In passing if readers spot any errors in the column please let us know so that we can keep accurate records. This is particularly important as items from the column are sometimes used by other organisations.

Letters

There have been a number of letters this month which is unusual for the rather quiet conditions prevailing at the moment. L. Berle of Roehampton, London SW15, has queried the identification of a number of ORTF (France) transmitters that he received during the improved tropospheric conditions of December. Using a Bush Model TV105 he noted excellent signals from Lille ch.F8a, Rouen ch.F10 and Le Havre ch.F7. The usual split image was

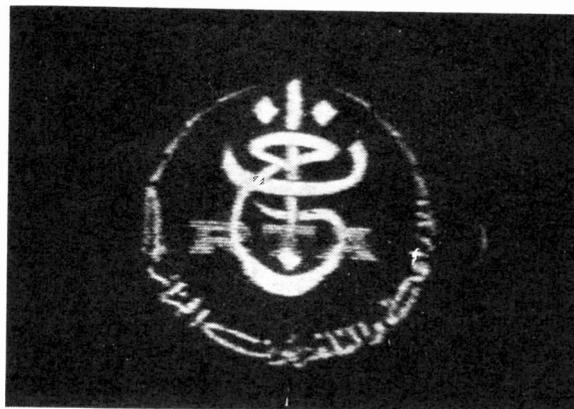

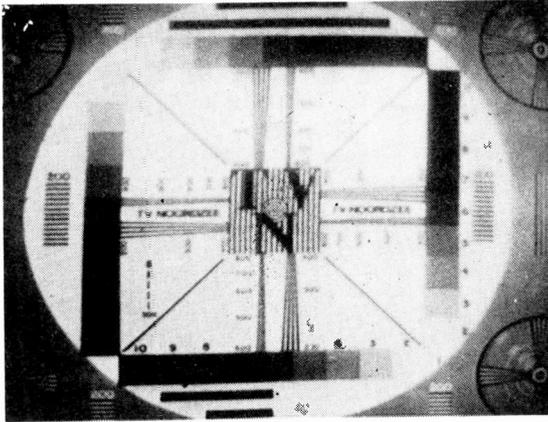
Reception of Algerian TV in Italy—see letters.



TV Noordzee test card.



TV Noordzee identification slide.

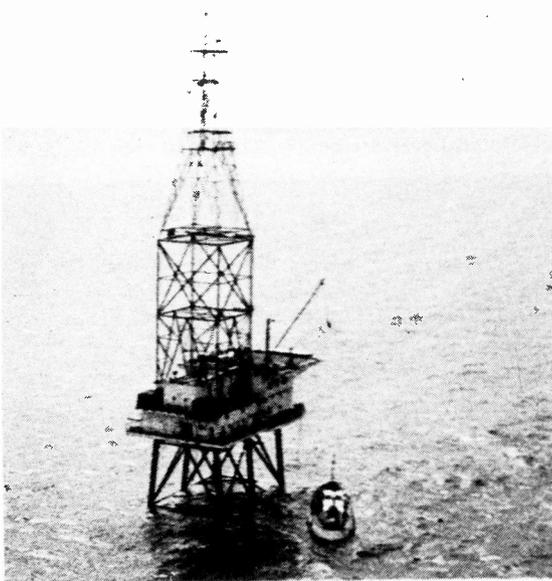

REM Island from the air.

noted—due to receiving the 819-line signal with a 405-line timebase—and signals at high levels lasted for some considerable time.

Michele Dolci at Bergamo, Northern Italy, in a recent letter reports his reception via Tropospheric propagation of Algeria on ch.E5. As with many enthusiasts elsewhere this occurred during the enhanced period over the 14-17th December. Interesting to note that his reception on 16th December between 2000-2345 GMT of the Algerian station was using his ch.E4 three-element array. Michele included a photograph of his reception showing the station identification crest. News too of the Greek television network—they are to build 17 stations of powers between 10-30kW. Unfortunately for us, though at some distance from Greece, they will be all in Band III.

We have heard from Wallace Roome of Pietersburg, South Africa, that despite the lack of television transmitters for many hundreds of miles he has had some limited successes. Although his letter is dated in December he comments that in the previous March-April period he received a Spanish station on ch.E2. Apparently the vision suffered from double images and tended to be snowy. We feel that the reception was from TVE Madrid ch.E2 via F2. Wallace goes on to say that the lack of signals is very frustrating: indeed if that was the only reception between April and December I personally would become somewhat desperate!

TV Noordzee


From time to time we are asked about transmitters that have ceased to operate for one reason or another and recently a query came in asking about TV Noordzee. As few people seem to have heard of this now defunct transmitter and in view of the interest it caused amongst TV-DX enthusiasts we decided to look into the happenings at TV Noordzee.

In 1964 activity was growing in the field of the so-called pirate radio, with floating radio transmitters of various powers and names anchored around the English and Dutch shores. Obviously if a TV transmitter could be put into use considerable advertising revenue would be obtained, especially in the Dutch area where television advertising is somewhat restricted. For such an undertaking however a ship could not be used successfully due to its movement. Eventually a complete floating island was constructed in the harbour at Cork, Eire and towed to a position off the Dutch coast near Nordveik Anglais. The island was known as the REM Island after the Dutch company Reclame Exploitatie Maatschappij. Initially there were radio transmissions on 1403kHz. These were followed on Saturday August 15th by the first programme of TV Noordzee at 1830 CET on ch.E11. The popularity of the programmes grew throughout the reception area and aerials, amplifiers and converters quickly sold out. Coverage was confined to West Holland and parts of Belgium with programmes between 1830-2000 CET and 2200-2330 CET.

The Dutch authorities however were less than enthusiastic! Legislation was undertaken to curb the transmissions and an anti-REM law was passed on December 1st, 1964. It became operative on the 12th. On the same day REM announced that the radio and TV apparatus had been taken over by a foreign company; in fact a London company—High Seas Television Ltd.—had the use of the transmitters. Despite these last-minute moves the authorities landed on board the REM Island during the morning of December 17th and put the transmitting apparatus out of action.

During the few months of its activities TV-DX enthusiasts anxiously tried to receive the signals and a number were fortunate in this quest. The transmitter on ch.E11 was thought to be between 5-10kW e.r.p. We have included several photographs showing the REM Island, test card and identification slide. Our thanks to Heerema Engineering Service; Bob Quanger (Benelux DX club); Dich van Schenk Brill (Pirate Radio News); Peter van der Kramer.

A CLOSER LOOK AT

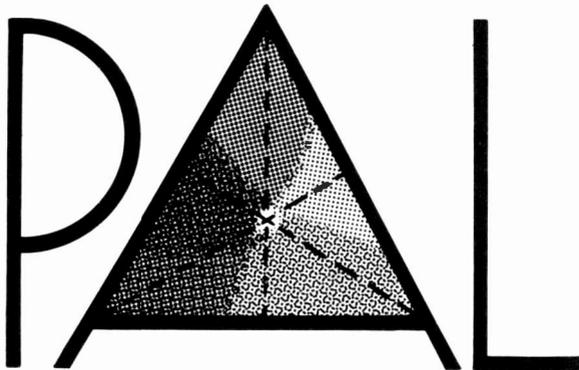

PART 5

E.J. HOARE

ALIGNING PAL DECODERS

It is on the basis of circumstantial evidence and intuitive reasoning that we expect PAL decoders to be sympathetic towards new techniques for carrying out the basic circuit alignment processes. The cancellation effects produced by V axis switching, which we have already discussed and demonstrated in earlier articles of this series, must surely provide scope for the exercise of ingenuity by the experts. It ought for example to be possible to arrange matters so that the delay line matrix and demodulator phases can be adjusted for some sort of null condition, or for minimum blinds or a combination of both. And so it is. There are a variety of possible techniques and doubtless more will be invented.

What we aim to do now is to describe some procedures for aligning the decoder circuits and to delve a bit into the principles on which they are based. Circuits vary a great deal in detail so we cannot give explicit instructions for different receivers. Let us try instead to stimulate some thinking about the subject in general in order to encourage experiments with new ideas.

TELEVISION would be glad to hear from readers who have their own pet methods of aligning the matrix and demodulator circuits—whether they use special test gear or rule of thumb techniques. It might be useful to spread this information through the industry, and perhaps in a later article to explain more fully the principles involved. This suggestion is prompted by an almost abortive hunt through some of the setmakers' service manuals. There seems to be a strange lack of guidance on the subject of decoder alignment. One or two manuals contained nothing at all; others merely suggested rather vaguely that the demodulators should be trimmed for maximum output. What about the delay line?

Let us first run through a few ideas which to be honest are intended as curtain raisers to the more sophisticated and accurate methods we will describe later. These simple approaches have their merits in particular circumstances and in any case may prove interesting to experiment with in slack moments.

Delay Line Matrix

A properly adjusted delay line and matrix circuit accepts the combined chrominance subcarrier and provides completely separated pure U and V outputs by the well known sum and difference process. An incorrectly adjusted delay line circuit on the other hand does not separate the U and V signals properly. As a result blinds occur on the picture and these are aggravated by inaccurate reference carrier phasing in the demodulators.

An obvious method of alignment is to adjust the amplitude and phase controls for minimum blinds, or rather no blinds, repeating the process several times in order to set the controls to the middle of the null region. This is not a particularly good method but with practice it can produce acceptable results. It can after all be argued that if no blinds can be seen then the alignment is sufficiently accurate not to cause visible distortion of the PAL signal. The contrary point of view is to the effect that the PAL immunity to errors is being used up in a poor adjustment procedure instead of being passed on to the viewer.

Another method, which seems a little unexpected at first sight, is to a.c. couple an R—Y reference carrier to the input to the delay line circuit. The injection point must be common to both the direct and delayed paths and in many decoders the base of the delay line driver stage is a suitable point. The output of the local oscillator is usually in R—Y phase and if the a.p.c. loop has been correctly adjusted this is a suitable source provided a low-impedance stage such as an emitter-follower is chosen.

The essence of the method is that an R—Y input to the delay line circuits should produce full output to the R—Y channel and none to the B—Y channel. If an oscilloscope is connected to these output points in turn the delay line can be adjusted for maximum R—Y and minimum B—Y. The receiver must of course be operated on a colour signal in order to lock the local oscillator in its correct phase, and care must be taken to ensure that no appreciable loading of the oscillator or chrominance circuits occurs as phase changes may be introduced which will degrade the accuracy of adjustment.

Demodulation Phasing

We have three methods to suggest here—one interesting and two useful.

Assuming that the delay line circuit is properly aligned then we have two outputs of pure U and V respectively. Nothing we do to the demodulators will alter this simple fact. Now suppose we display a normal colour pattern and then interchange the feeds to the two demodulators so that the V demodulator gets a U signal and vice versa. What is the result? Yes, you are right—no colour.

If colour is in fact present it is due to misalignment of the demodulators or to crosstalk in the decoder circuitry between the U and V channels. All that is required is to adjust the phase of the reference carrier to each demodulator in turn to produce minimum colour output. Ideally you need a pattern with R—Y and B—Y bars but any colour signal will serve although there will be some degree of interaction between the adjustments. These should be repeated several times in very small steps.

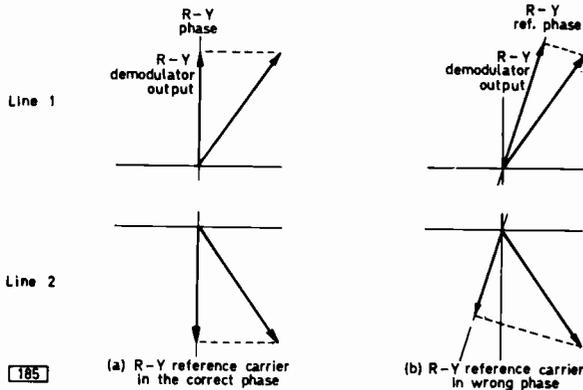


Fig. 1: With Simple PAL decoding a demodulator phase error causes different outputs on alternate lines and hence blinds on the display.

This is an interesting method and in theory is critically accurate. In practice its delightful simplicity is sometimes spoilt by crosstalk which makes it impossible to obtain no colour at all.

Our next suggestion is to connect an oscilloscope to each demodulator output in turn and to adjust its reference signal phase very carefully for maximum output. You cannot get more than the correct output: only less. This is not a very accurate method but it is adequate for most purposes and involves no interference with the circuitry.

Now we come to the Simple PAL technique. If the outputs of the delay line matrix are shorted together we get no signal separation and the original combined chrominance subcarrier will be applied to both demodulators. Fig. 1 shows what happens when this signal is applied (a) to the correctly adjusted and (b) to the incorrectly adjusted R-Y demodulator. You can see immediately that incorrect adjustment, even if quite minor, causes a difference in output on alternate lines, i.e. blinds on the picture. Any hue not on the B-Y axis will produce this effect. So all that needs to be done is to adjust both demodulators for minimum blinds.

Incidentally this method illustrates rather well why Simple PAL decoders are rarely used. It is almost impossible to tune out blinds altogether. Even the smallest phase error will cause a noticeable increase.

Vectorscope Displays

If one could display the decoder outputs corresponding to a known colour test pattern signal input on a vectorscope it would be a simple matter to check whether the decoder alignment was correct. Unfortunately vectorscopes are expensive pieces of equipment and are normally used only for monitoring purposes in broadcast studios and by the makers of test equipment.

It may not be generally realised that a comparatively ordinary oscilloscope can serve very well indeed for aligning decoders by means of a similar type of display. Furthermore the method is very accurate and shows clearly what type of alignment errors are present. The type of 'scope needed is one with access to the X plates in addition to the normal Y input terminals. The bandwidth required is only a few hundred kHz and the sensitivity such that near full deflection is obtained with an input corresponding


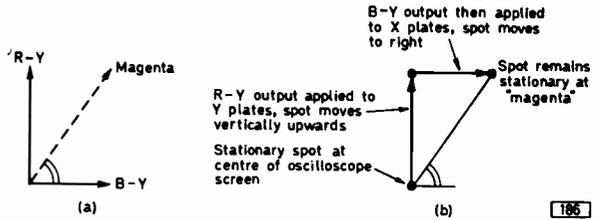


Fig. 2: (a) The R-Y and B-Y components of a magenta hue. (b) If the R-Y component is fed to the Y plates and the B-Y component to the X plates of an oscilloscope with its internal timebase stopped, the display shown here will be obtained.

Fig. 3 (right): An X-Y oscilloscope display for a normal colour-bar test pattern with the receiver operating correctly.

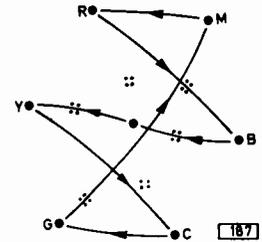

to the R-Y and B-Y outputs from the two colour demodulators. It is possible to buy oscilloscopes that meet these requirements near the bottom end of the price range so this poses no particular problem.

The essence of the technique is delightfully simple. Take say a magenta hue as shown in Fig 2(a). This has R-Y and B-Y components on the V and U axis. In other words R-Y and B-Y demodulator outputs at these amplitudes will when displayed on a colour c.r.t. (with the derived G-Y component applied as well of course) produce a light output of magenta hue.

If the R-Y demodulator output is applied to the Y plates of the 'scope with the timebase stopped the stationary spot will move vertically upwards, i.e. it will move up the R-Y (or V) axis of the conventional phasor diagram as shown in Fig. 2(b). If we now connect the B-Y demodulator output to the X plates the spot will move to the right, parallel to the B-Y (or U) axis, as shown. The spot will then be stationary at a point that subtends the subcarrier phase angle corresponding to magenta.

Thus a stationary spot will appear on the oscilloscope for each individual area of colour in the picture. If the standard colour-bar test pattern signal is applied to the receiver for example six dots will be displayed on the oscilloscope, corresponding to the three primary colours and the three complementaries. This is illustrated in Fig. 3 together with the faint lines between the dots caused by the path traced out by the electron beam as it switches from hue to hue.

Alignment by Vector Display

The vector display that we have just described can be used to best advantage when the receiver reference oscillator is out of lock. The a.p.c. loop should be disabled so that the oscillator is running free and the frequency should then be adjusted by means of the usual trimmer so that it is slipping at a rate of a few cycles a second. It is convenient to disable the colour killer also. The slip frequency can then be judged by observing the colour drifting in and out of synchronism on the screen of the picture tube. The

Now...here's a do-it-yourself aerial kit!

It's an exciting first... from Antiference! Aerialkit comes complete with everything you need except coaxial cable.* Assemble and install it in an hour or so... up in the loft, or on an outside wall or convenient woodwork. When you've completed your installation, the full-sized ten element yagi array will give you broad-band coverage of all your UHF 625 line channels in 'normal' reception areas, for colour or black-and-white.

Reception you'll be proud of! Aerialkit is designed by Antiference, pioneers in TV reception, to the same high professional specification that leading aerial riggers choose. Ask your local dealer about Aerialkit - it could be ideal for you!

**Measure up your cable need and buy it from your dealer.*

Antiference Aerialkit

Powerful ten element yagi array, tuned to A, B or CD channel groups.

Unique Antiference dipole gives more even response over all channels.

'Man-sized' easy-connecting junction box, weatherproofed with captive cap.


'Supaseal' cable entry takes any size cable, keeps a weathertight seal.

'Hi-angle' reflector keeps out interference and aids even response over all channels.

Clever universal mounting enables aerial to be aimed at transmitter, from almost any position.




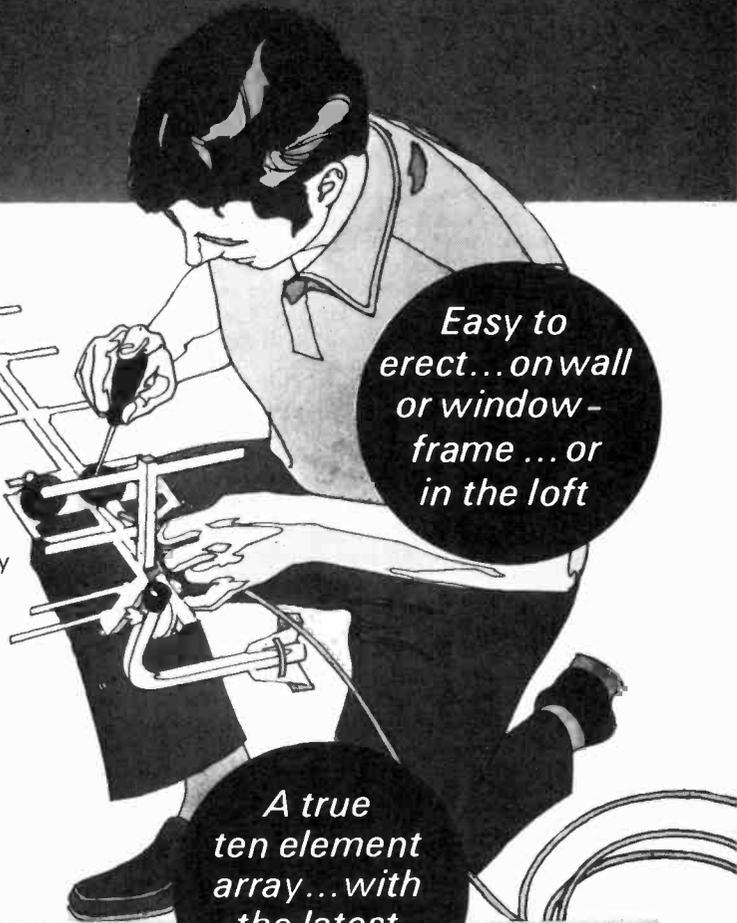Antiference Limited, Aylesbury, Bucks. Tel: 82511



Easy to erect... on wall or window-frame... or in the loft

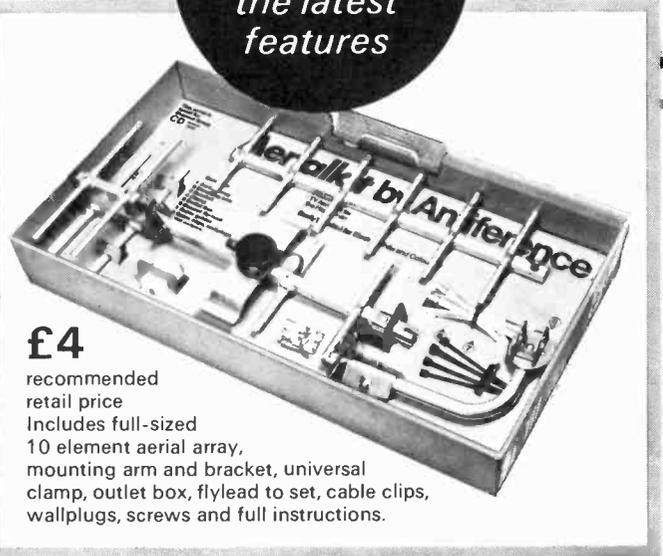A true ten element array... with the latest features



£4

recommended retail price

Includes full-sized

10 element aerial array,

mounting arm and bracket, universal

clamp, outlet box, flylead to set, cable clips,

wallplugs, screws and full instructions.

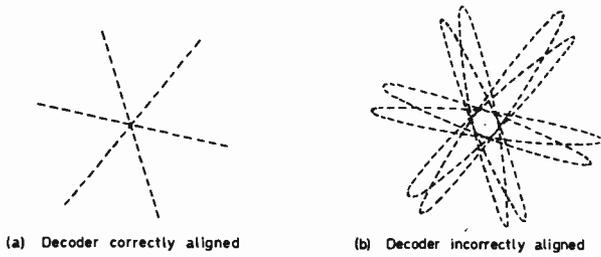


Fig. 4: X-Y oscilloscope display under the same conditions as in Fig. 3 but with the decoder reference oscillator not in lock.

display that will be obtained is shown in Fig. 4 for correctly and incorrectly aligned decoders. Before proceeding further it may be helpful to describe what is appearing on the screen of the oscilloscope.

If you consider the red and cyan bars of the standard colour-bar test pattern for example the conventional phasor diagram will be as shown in Fig. 5(a). If we choose an instant in time when the free running oscillator happens to be in its correct phase—and if the decoder is correctly aligned—the reference carriers to the R-Y and B-Y demodulators will also be correctly in their respective V and U axis phases. Thus we get an output corresponding to say the red hue. This will be displayed as a dot. When the hue changes an instant later to cyan we get another dot. If we take another instant in time several lines later the reference oscillator will have drifted away from its correct phase with the result that the R-Y and B-Y reference carriers are now on new axis as shown in Fig. 5(b). This means that both demodulator outputs are reduced in the same proportion. So the two dots move closer to zero: i.e. closer together along the line R-C.

If, repeating the process, we move on to the instant shown in Fig. 5(c) there will be no output at all from either demodulator because the reference carriers to each demodulator are 90° out of phase. The dots are now coincident at the zero point. The result of all this is that we get a dotted line R-C as shown earlier in Fig. 4(a).

The point of interest to consider now is what happens to this line when decoder alignment errors are present. Take the case of a phase error in the delay

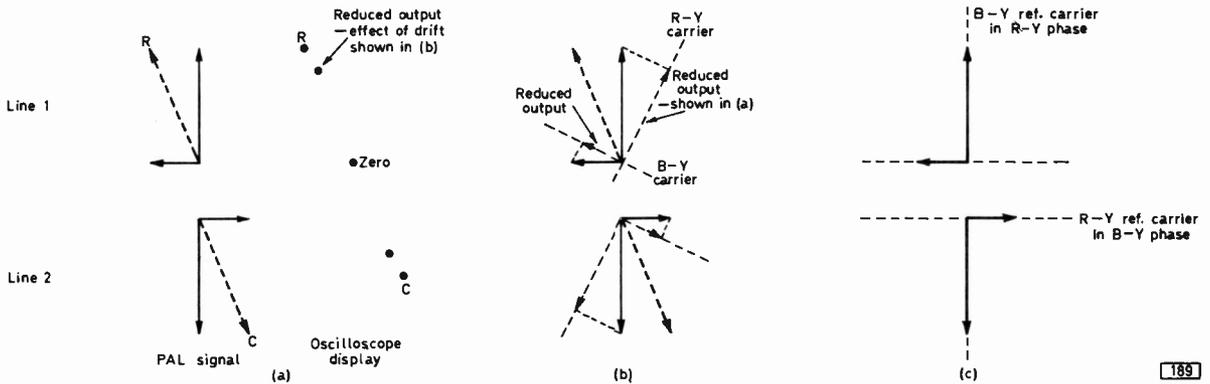


Fig. 5: The dotted lines shown in Fig. 4 (a) are produced as the reference oscillator drifts through one complete cycle. (a) Oscillator reference carriers in correct phase. (b) Both carriers here have drifted away from their correct phases, giving reduced output. (c) When both reference carriers have drifted 90° out of phase there is zero output from both demodulators: the spot is then at the centre of the screen.

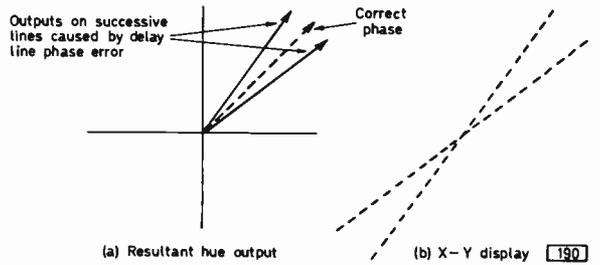


Fig. 6: A delay line phase (time) error produces different hues on successive lines and this is shown clearly on the X-Y display (b).

line circuitry. We saw in a previous article of this series that the resultant of the R-Y and B-Y outputs varied from line to line as shown in Fig. 6(a). We would therefore expect to see this same pattern on the oscilloscope. Happily for the author and his previous analysis we do in fact get a pair of dotted lines separated by an angle dependent upon the phase error introduced by the delay line, as shown in Fig. 6(b).

Referring again to the earlier article (with a little more confidence this time!) we concluded that an amplitude error in the delay line matrixing process would cause crosstalk in both U and V outputs as illustrated in Fig. 7(a). What happens to our vector-scope display?

We can see this fairly easily without going into too much detail. The reference carriers supplied to the R-Y and B-Y (or V and U) demodulators are in quadrature (90° apart) and are slowly rotating about the U and V axis. See Fig. 7(b). When the R-Y reference carrier is at 90° to the R-Y sub-carrier signal the B-Y reference carrier is *not* at 90° to the B-Y signal carrier. Thus when there is no R-Y output there will still be some B-Y output. So the straight line that we get with correct alignment becomes an ellipse. See Fig. 7(c) and (d).

The same argument applies if the two demodulator reference carriers are not in quadrature. We still get an ellipse.

Overall Phase

The only other adjustment with which we are concerned here is the overall phase of the two reference

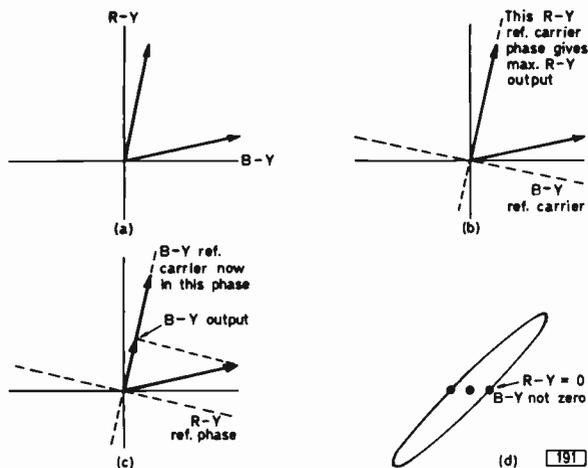


Fig. 7: Crosstalk between the R-Y and B-Y channels causes an ellipse on the X-Y display. (a) These signal components are the result of incorrect delay line amplitude adjustment. (b) This phasing corresponds to a point almost at the tip of the ellipse. (c) No R-Y output, but there is still some B-Y output so the result is an ellipse. (d) An ellipse is formed if the R-Y and B-Y outputs are not zero simultaneously.

carriers. In most cases this is the static phase of the reference oscillator itself, controlled by the a.p.c. loop. If you look more closely at the oscilloscope display when the reference oscillator is properly locked you will see clusters of faint dots as shown in Fig. 3. These are usually called "half-amplitude dots" and are caused by the outputs of the two demodulators at the instant when the hue is changing from one colour bar to the next. On one line the information is say yellow and on the next magenta. When the information from these two lines is added and subtracted in the delay line matrix the electronic averaging process obviously breaks down and we get dots corresponding to this spurious signal. In the case of yellow and blue the information before and after respectively contains no chrominance because it represents a white or a black bar. Thus the matrix outputs into the V and U channels are correct for hue but of half their proper amplitudes. Hence the half-amplitude dots. The spacing of these dots is a minimum when the overall or static phase is correct.

Vector Display Alignment Procedure

We can now list the full procedure for decoder alignment using a vector display.

- (1) With a colour-bar signal or any pattern with large areas of colour first obtain a normal picture display.
- (2) Connect the X and Y plates of the oscilloscope to the B-Y and R-Y demodulator outputs.
- (3) Disable the a.p.c. loop and the colour killer. Bias back the a.c.c. circuit if the saturation is too high.
- (4) Check and if necessary adjust the reference oscillator for slow slip.
- (5) Adjust the gain of the oscilloscope to give a display which fills about two-thirds of the screen. You should now have the display of Fig. 4 or its equivalent depending upon the colour test pattern.
- (6) Adjust the reference carriers' quadrature condition and the delay line matrix amplitude control to turn all ellipses into straight lines.

(7) Adjust the delay line matrix phase control to swing pairs of lines together to form single lines.

(8) Repeat (6) and (7) as necessary.

(9) Enable the a.p.c. loop and adjust the overall phase for close coincidence of the half-amplitude dots on the yellow/blue axis.

No decoder is perfect and if the ellipses cannot be closed completely it usually means that there is some U/V crosstalk built into the circuit. Good results will be obtained on the picture even if the ellipses are appreciably open, because this is a very accurate method of alignment. Furthermore it shows very clearly the type and extent of any errors present.

If more gain is needed the oscilloscope can be connected farther down the channels: for example at the outputs of the colour-difference amplifiers. The disadvantage of doing this is that any crosstalk or other spurious signals will tend to distort the display.

Split-screen Pattern Generator

A very convenient method of aligning decoders involves the use of a pattern generator made by sssh (you know who!) which gives a clear visual indication of any decoding errors. It is the so-called split-screen display and is of special interest because apart from being a good method it also once again makes use of the unique properties of the PAL technique. It is worthwhile describing in detail because it illustrates PAL principles rather well and in any case few engineers would wish to use a piece of test gear without understanding how it works.


For the adjustment of delay line phase and amplitude a pattern is used which has four vertical bars. The fourth bar is pure luminance, with no chrominance at all. The other three bars have hues corresponding to phase angles of 146° , 180° and 90° on the conventional R-Y and B-Y phasor diagram. This chrominance information is NTSC encoded: that is to say no switching is carried out on alternate lines, except for the burst which alternates in the normal PAL sequence. The three chrominance vectors are shown in Fig. 8 and these will be the same on all lines because of the unswitched encoding.

You will see immediately that these three bars have been carefully chosen. Bar 2 is pure - (B-Y), bar 3 is pure + (R-Y) and bar 1 is a straight mixture of bars 2 and 3. Thus bars 1 and 3 have equal amounts of + (R-Y) and bars 1 and 2 have equal amounts of - (B-Y).

The key to understanding how this pattern can be used to display delay line amplitude and phase errors lies in the effect of PAL delay line matrixing upon an NTSC encoded signal. Fig. 9 shows the three bars individually on two successive lines of a field. Note that the PAL sum and difference processes in the delay line matrix are carried out completely normally but on an abnormal signal.

The result of this unexpected combination of techniques is a little surprising. If the matrixing is correct there is no output from the matrix into the R-Y

Fig. 8: The three chrominance signals used for three of the four vertical bars of the special test pattern. Note their relationship.

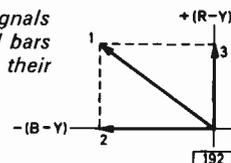

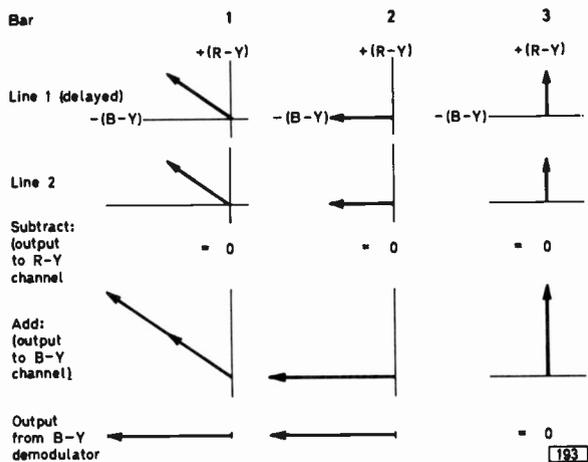


Fig. 9: When decoded an NTSC signal produces no R-Y output, only B-Y. Bar four has luminance only.

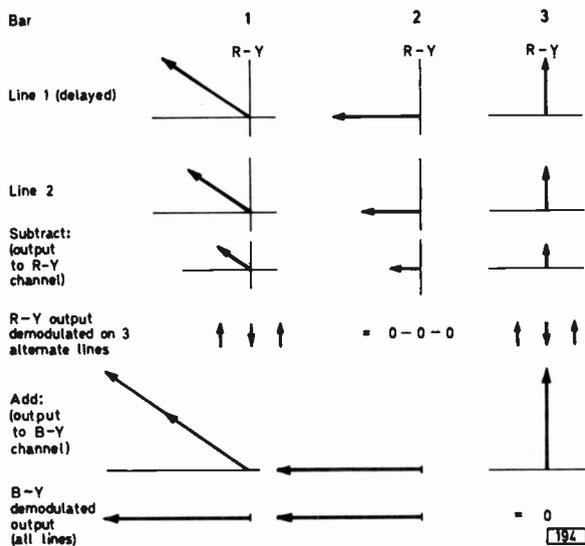


Fig. 10: Decoding the NTSC signal (with switched burst) when the direct and delayed path signals are unequal. Note the alternating outputs in bars one and three, causing blinds on the display.

channel! Whatever the chrominance signal input may be (NTSC encoded) there is no R-Y output from the decoder: this is because we are subtracting delayed and undelayed signals which are identical, so there can be no resultant.

If we look at the sum output from the matrix, feeding the B-Y demodulator, things are more normal. We get twice the amplitude of the chrominance signal (delayed + undelayed) in the B-Y channel. But note the catch for the unwary. Bar 2 has pure - (B-Y) and so we get a - (B-Y) output. Bar 1 has + (R-Y) and - (B-Y) components but only the - (B-Y) component produces an output: the + (R-Y) component is in quadrature and so produces no output from the B-Y demodulator. Bar 3 is pure + (R-Y) and likewise produces no output.

The result of all this on the screen is as follows:

- Bar 1. - (B-Y).
- Bar 2. - (B-Y): same amplitude as bar 1.

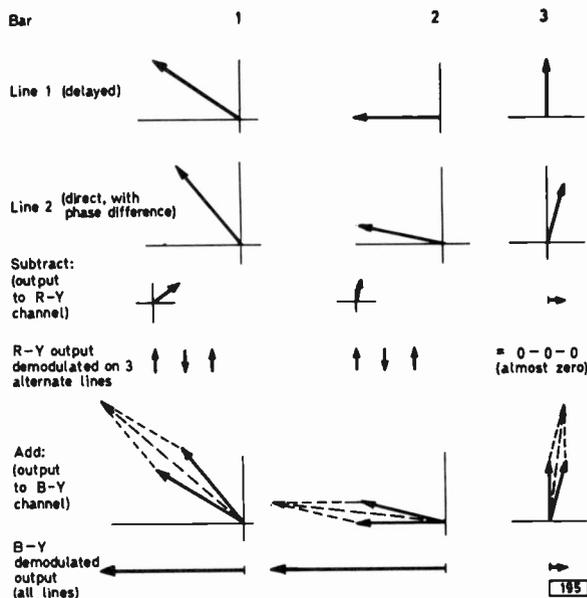


Fig. 11: The same decoding process as in Fig. 10 but this time with a phase difference between the direct and delayed path signals. Switched R-Y outputs are present on bars one and two, causing blinds.

- Bar 3. No colour output, only luminance.
- Bar 4. Luminance as bar 3.

The hue produced by - (B-Y) is greenish. So the first two bars will be of this colour and the other two bars will be light grey.

Delay Line Adjustments

An amplitude error in the delay line circuitry, causing the delayed and undelayed signals to be unequal, will produce the effects shown in Fig. 10. Subtracting these unequal signals will produce an output to the R-Y channel for each of the first three bars. The output for bar 2 will be pure - (B-Y) and so the R-Y demodulator will not "see" it. Thus bar 2 is unchanged apart from a small difference of saturation. Bar 1 will have an R-Y component and so will bar 3. As however the bursts are switched in the normal PAL manner the reference carrier to the R-Y demodulator will also be switched and so these spurious R-Y signals will reverse in phase from line to line: thus blinds will be seen in bars 1 and 3.

Turning now to a delay line phase error we get the results shown in Fig. 11. Following a similar analysis to that just used for amplitude errors we see that there will be only a very small spurious switched R-Y output in bar 3. Bars 1 and 2 however have quite a serious error causing blinds. It is interesting to note that bar 2 has this spurious R-Y signal in spite of the fact that no R-Y information is present in the generated signal. This is a function of delay line PAL decoding.

Summarising our results so far we get:

- Amplitude error: Blinds in bars 1 and 3.
- Phase error: Blinds in bars 1 and 2.

In making any adjustments of phase or amplitude it is necessary to ignore any changes in hue and to align the decoder purely for minimum blinds—repeating the adjustments several times as required. If sub-

stantial errors are present the switched R-Y component will be sufficiently large for the hue differences between sequential lines to be recognized. One line will have + (R-Y), a bluish red. The next line will have - (R-Y), a greenish blue. These hues will of course show up more clearly in the light grey of bar 3 than the greenish bar 2.

Demodulator Adjustment

The colour pattern for adjusting the R-Y and B-Y demodulators has the same chrominance and luminance information as before but is encoded differently and thus displays different hues on the screen of a colour TV receiver. The upper half of the pattern is PAL encoded. So instead of producing decoder outputs of - (B-Y), i.e. greenish, in the first two bars and grey in the other two we get hues corresponding to the subcarrier phase angles. Thus bar 1 is 146° = orange/yellow; bar 2 is - (B-Y) = greenish; bar 3 is + (R-Y) = rose; bar 4 is grey.

The lower half of the pattern is also PAL encoded but chrominance information is transmitted only on alternate lines, the others being luminance only. This means that the delay line matrixing process is put out of action and we get the results shown in Fig. 12(a). You will see that the same signal is applied to each demodulator.

Now if the reference carriers to the two demodulators are both correct we shall get the outputs shown in Fig. 12(b) which will give the same hues as on the upper half of the screen. The Simple PAL decoding of the lower half will give the same result as the delay line PAL decoding of the upper half.

Figure 12(c) shows the effect of reference carrier phase errors in the R-Y and B-Y demodulators. You will see that an R-Y phase error will produce a spurious output in bar 2 which has no R-Y signal. The hue will therefore be distorted. Similarly a B-Y phase error produces a spurious output in bar 3 which has no B-Y signal. Again the hue is distorted. No blinds occur in either case because there is no switched component when alternate lines contain no chrominance information.

The process of demodulator phase adjustment is very simple. Each demodulator is adjusted in turn to give identical hues on both halves of the pattern: bar 2 for the B-Y demodulator, bar 3 for R-Y. In many decoders there is some degree of interaction and so the usual procedure is to repeat the adjustment as necessary.

The split-screen technique provides a very critical indication of correct demodulator phase adjustment and in practice it will be found that different pattern generators give slightly different answers. This is perfectly acceptable because of the tolerance of the PAL system to small errors.

Oscilloscope Measurements

The same colour pattern described above can also be used for adjusting decoders by means of the c.r.t. drive waveforms displayed on an oscilloscope. This procedure is described and illustrated in the manual provided with the pattern generator and there is no particular point in repeating it here. Suffice it to say that the method is based on producing an oscilloscope display such that successive lines of a field are superimposed on each other. Any spurious switched com-

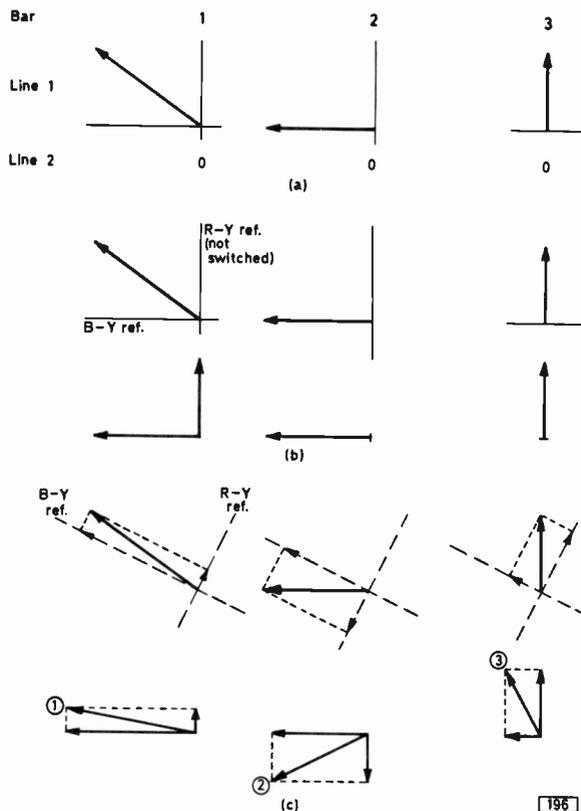


Fig. 12: The split-screen test pattern provides a very sensitive visual indication of demodulator errors by hue changes in bar two for R-Y and bar three for B-Y. (a) Delay line processing of a signal with chrominance on alternate lines only: either adding or subtracting gives outputs identical to line one above, thus the same signal is applied to each demodulator—this is equivalent to Simple PAL decoding. (b) If the reference carriers to the R-Y and B-Y demodulators are in the correct phases the original R-Y and B-Y signal components are obtained. (c) Note how the resultant chrominance phases have been changed in amplitude and phase angle by incorrect demodulation.

ponent present in the output, caused by misadjustment of the delay line or demodulators, will have opposite polarity on alternate lines and so will result in the two superimposed waveforms being separated. The appropriate preset controls are adjusted until only a single trace is obtained on the oscilloscope.

On the whole this method is probably not quite as accurate as using the TV screen display, if only because most engineers have to work with oscilloscopes that give rather a coarse trace. It may however prove useful if the decoder is very seriously out of alignment and difficulty is experienced in interpreting the colour display.

Concluding The Series


We began this series by making the point, to which few people will object, that in PAL we have chosen the right system. Engineers with experience in the field will agree that although not all our customers receive perfect pictures the quality on the whole is very good. Certainly it is better than reports from countries using the well-established NTSC system had

—CONTINUED ON page 279

Renovating the RENTALS

CALEB BRADLEY B. Sc.

② THORN 800 & 850 CHASSIS

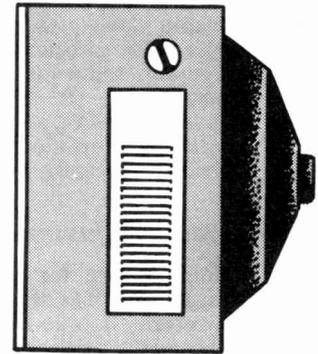

THESE dual-standard capable chassis are found in a wide range of Thorn group (Ferguson, HMV, Ultra, Marconiphone) sets, a few Decca models (DR61 and DR71) and also in sets made specially for rental. The latter may carry the name DER or the name of the rental company. Thousands of the sets are still being rented and thousands more are available on the ex-rental market (see end of article). In general their attractive styling, up-to-date screen sizes (19 and 23in.) and suitability for dual-standard use make them a good buy for reconditioning for either own use or resale.

Common Features

The "800" began way back in 1961 with the Ferguson 705T. This was basically a 405-line set with provision for conversion to dual-standard operation although in those days no one was certain just what the second standard would be. A 405-625 knob at the side of the cabinet operated switches in the line timebase and at the video and sound amplifier grids, but there were no circuits connected to the 625 side of the switches! An interesting proposal at the time was that new programmes on u.h.f. could be accommodated simply by fitting higher frequency coils in the v.h.f. tuner. This worked up to a point but could not give the sensitivity of a purpose-built u.h.f. tuner as used today.

Stripped of some of its gimmicks, such as motor-driven channel selection and remote control, the basic 705T chassis continued as the 800 and was made in large numbers—see photograph and Fig. 1. It established the Thorn pattern of a lightweight steel frame carrying the timebase components on a board at the bottom with the i.f. strip on a slanting board at the top. Accessibility and ventilation are both fairly good with this arrangement and the boards are covered with printed annotations making them almost as easy to understand as circuits. Conductors are helpfully printed in colour on the boards according to the following code: **white** heaters and a.c.; **blue** earth; **blue and white** cathode connections; **green** grid connections and a.g.c.; **red and green** screen grid connections; **red and white** anode connections; **red** h.t.; **broken red** decoupled h.t. Later red and blue were used for boost h.t. conductors.

The 850 Chassis

The foregoing features were retained in the 850 chassis which was introduced in 1963-64. There are two distinct versions of this: a convertible version

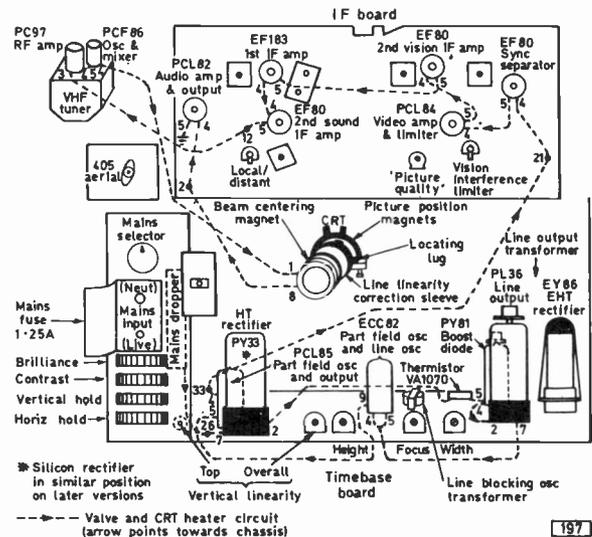


Fig. 1: Layout of the Thorn 800 chassis. The i.f. board has been tilted up and the line output stage shield removed for clarity.



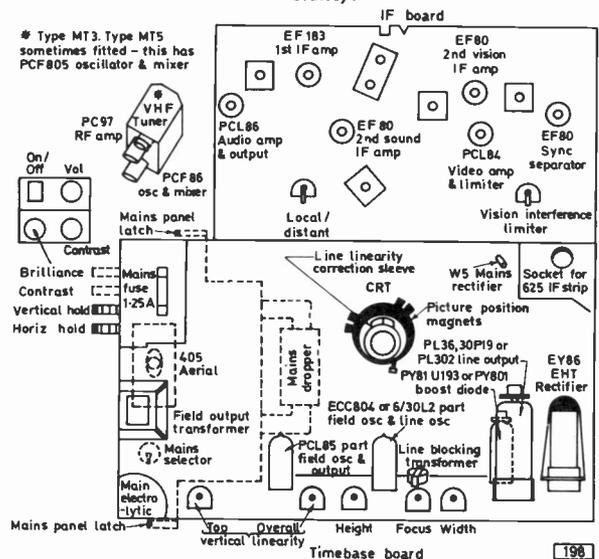


Fig. 2: Layout of the convertible Thorn 850 chassis. The heater circuit is similar to the 800. On some sets the controls, mains dropper and fuse are repositioned.

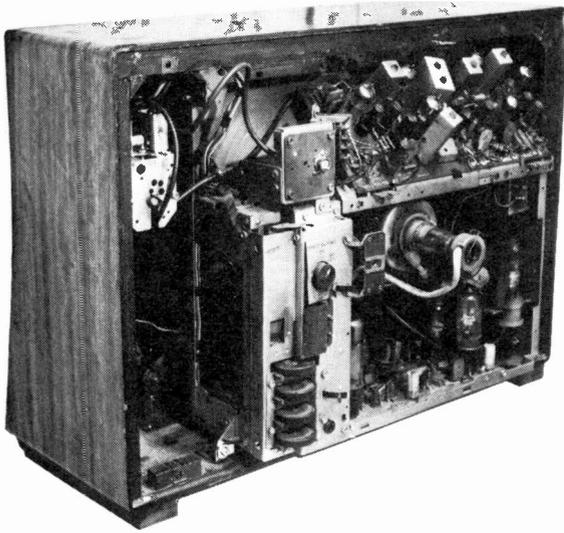

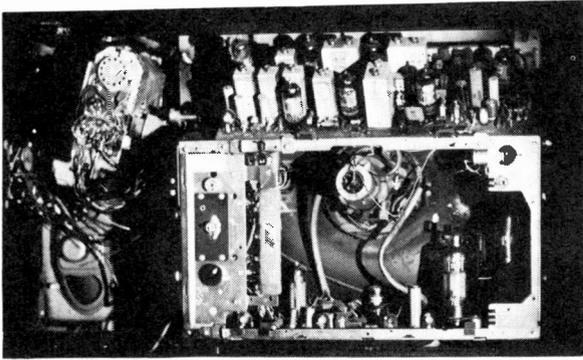A Thorn 800 chassis: hinges at the right enable the chassis to be swung out almost 90° after removing two screws at the left, giving access to both sides.



A dual-standard Thorn 850 chassis, fitted in the wide cabinet of an Ultra Bermuda model.

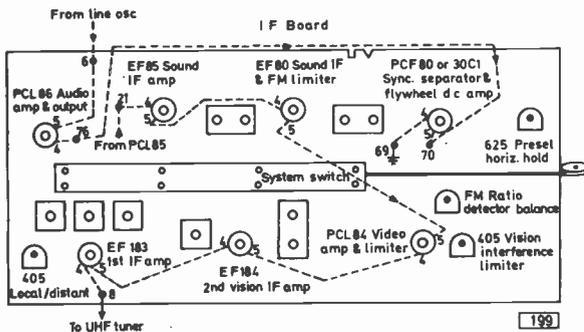


Fig. 3: Layout of the i.f. board used in the dual-standard 850 chassis. This chassis is otherwise similar to Fig. 2 except that the 625 i.f. strip socket is not required.

(Fig. 2) and a dual-standard version (Fig. 3 and photograph). The latter version needs only the addition of a u.h.f. tuner for 625-line use while the convertible version needs both a u.h.f. tuner and an additional 625 converter i.f. strip (same as the 800). The suppliers listed at the end of the article state that they have limited stocks of the manufacturers' original

converter strips and tuners and adding these can be quite straightforward as will be described.

Tuner Faults

Component failures in the v.h.f. and u.h.f. tuners are rare except for occasional loss of gain (low contrast) due to ageing of the valves, particularly the r.f. amplifier. "Scratchy" v.h.f. channel switching can usually be cured by springing off the tuner cover and wiping the coil studs with switch cleaner.

Two types of v.h.f. tuner have been used. One has a dual-concentric spindle the outer of which is used for fine tuning. Sometimes the plastic collar which holds the outer sleeve breaks and some careful rebuilding with Araldite is called for. The panel carrying the tuner, edgewise volume control and press-type on-off switch is easily removed by loosening the main knob grub screw, removing the knobs and then removing a large nut at the rear. This nut clamps the tuner to the side of the cabinet by means of a small right-angled bracket. After long use the panel may move too far back for easy use of the controls because this bracket has become distorted. Also the on-off switch frequently breaks; usually the button has simply shattered. When reassembling it is worth smearing some soap between the tuner knobs to reduce friction as the fine tuner knob is rather hard to grasp.

The second type of v.h.f. tuner has separate knobs for channel switching and fine tuning. The fine tuner is pressed to engage a small plastic sprocket-screw for the channel in use; this in turn presses on a fine tuner bar. The cast disc which carries the sprockets is clamped to the tuner shaft by a grub screw ($\frac{1}{4}$ in. hexagonal core): if this loosens the fine tuning becomes erratic.

A point to note about both v.h.f. tuners is that the fine tuning range is not very great so that adjustment of the local oscillator cores may be necessary. This entails removing the tuner from the cabinet since the core for the channel in use is accessible through a hole in the front of the tuner. Use a non-metallic screwdriver to set the core for an optimum picture with the fine tuner set midway.

The Heater Chain

We dealt with the general unreliability of mains dropper resistors last month and this chassis is no exception. Where failure of the valves to glow is due to an open-circuit heater, the heater routing shown on the chassis layouts will help in tracking it down. The heater arrangement used in these (and other) BRC chassis is unusual in that the c.r.t. heater is not connected directly to chassis as is the general practice.

Note that all common E prefix and P prefix valves should show heater continuity between pins 4 and 5 (B9A range) or pins 3 and 4 (B7G range) when checked out of the set on an ohmmeter. ECC81/2/3 valves also have a heater centre tap at pin 9.

Valve Shorts

Local screen, anode and/or cathode resistor burn-ups can result from shorts inside any of the i.f. strip valves but the PCL84 video amplifier is particularly prone to this. Even after replacing the valve and all the obviously cooked resistors vision may not return.

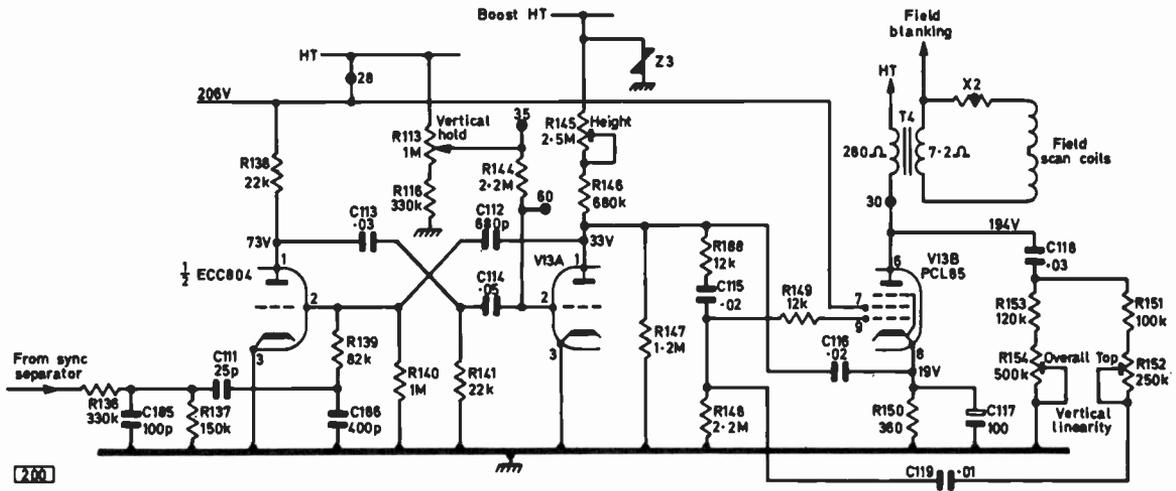


Fig. 4: The field timebase circuit. This is as used in the 850 dual-standard chassis but the earlier 800s and 850s are very similar. Early 800s had v.d.r.s (voltage dependent resistors) in series with R147 (on this circuit) and across T4 (field output transformer) primary winding.

This is because the vision detector diode has also blown. It is an OA70 located inside the rectangular can to the left of the PCL84.

Field Timebase Faults

Two valves are involved in the field timebase, a PCL85 and an ECC82 or ECC804. Either may fail and the voltages shown in Fig. 4 should be obtained on replacement if no components have changed value. Several components in this section can give trouble. When field lock is lost suspect R138 behind the ECC804; this runs warm and may have changed value so use a 1W replacement. Also suspect R144 or either C113 or C114 of being leaky. When vertical linearity is spoilt by top or bottom cramping check the PCL85 pentode cathode voltage. An incorrect reading may be due to R150 changing value or C117 going leaky. Bottom compression can also be caused by C119 or C118 leaking.

HT Smoothing

The large three-way electrolytic used for h.t. smoothing often loses capacitance and the resulting ripple on the h.t. line causes intermittent field sync, S-shaped verticals and brightness variation down the picture. It is located at the bottom left of the frame and there is enough room to fit substitute components if the proper replacement cannot be obtained or if it is only wished to replace one section. When replacing do not attempt to remake the special wire-wrap connections used in this and other parts of the set but use ordinary soldered joints.

White Flashing on Screen

White flashing on the screen can be caused by poor contact between the tube flare coating and the earthing spring with sparking visible in darkness. Cleaning will cure this. Other causes are breakdown of the scan coils, necessitating replacement, or arcing between the scan coils and the linearity sleeve. A possible cure in this case is to withdraw the sleeve and turn it round so that the puncture is at the rear, keeping the sleeve

at the same angle to avoid affecting linearity.

Line Stage Chokes

There are rather fragile square cross-section air-cored chokes glued to the top cap connectors of the line output and boost diode valves and either of these going open-circuit causes loss of picture. In fact if these are simply shorted across performance is still fairly good although the picture may suffer from vertical striations.

The 625 Converter Strip

The 625-line converter i.f. strip is secured to the rear top rail of the chassis with connections as detailed in Fig. 5. The circuit of the strip is shown in Fig. 6 and its layout in Fig. 7. The main features are a flywheel sync circuit with amplified control voltage output—effective on both standards—an f.m. detector without balancing preset and video drive to the tube by a cathode-follower.

Before adding the strip cut out the following (see Fig. 5):

- Links X on slide switch S12.

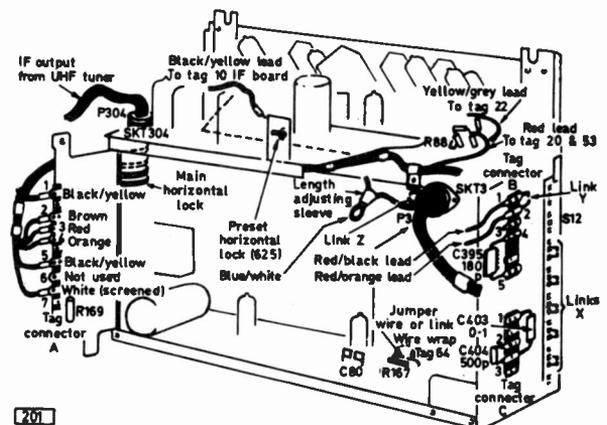


Fig. 5: Connection details for the 625 converter i.f. strip.

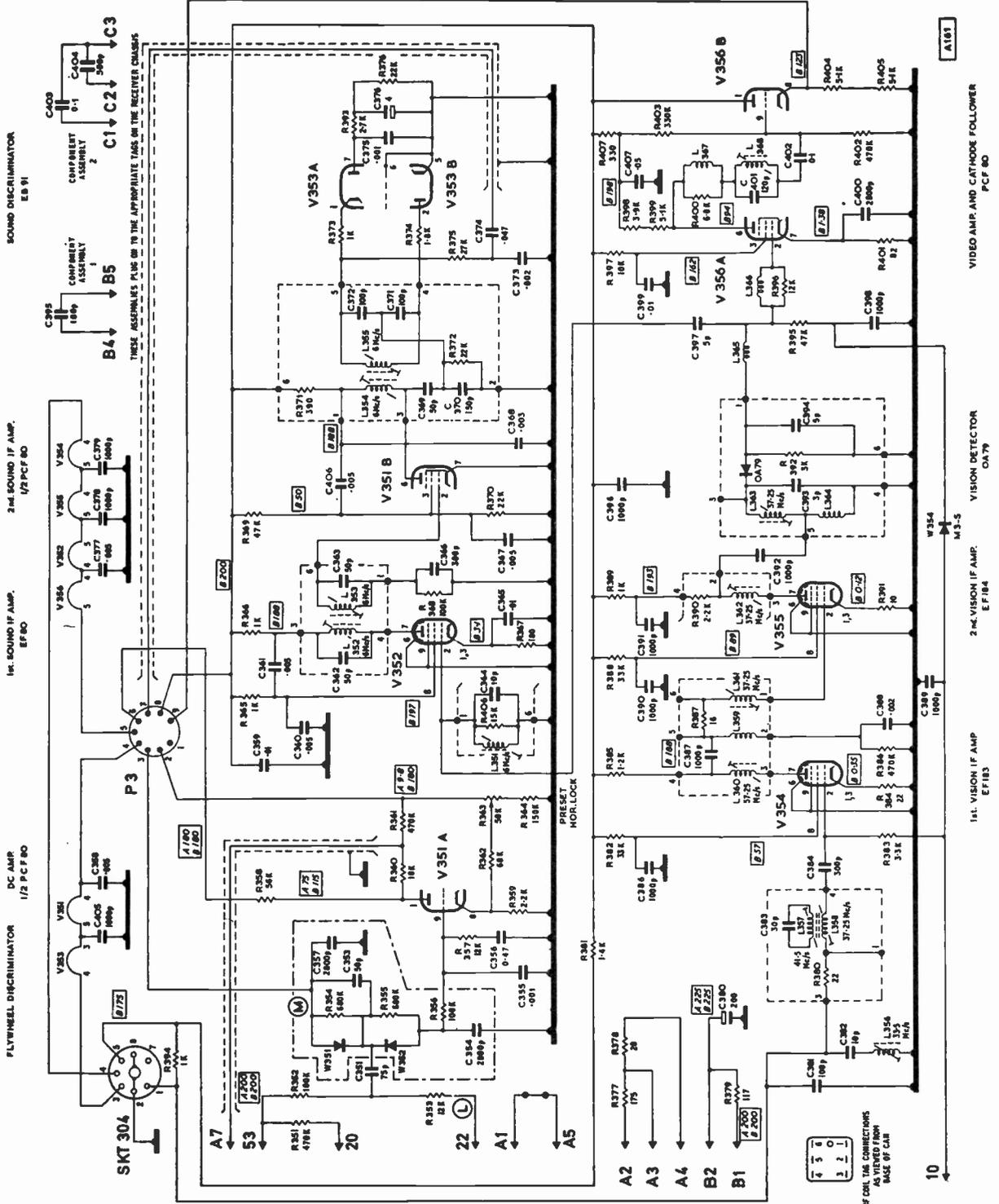


Fig. 6: Circuit of the 625 converter i.f. strip for the 800 and 850 (convertible version) chassis.

Link Y on tag connector B.
 Link Z on SKT3.
 The jumper wire parallel to R167 (4.7kΩ) on the timebase board.
 R88 (120kΩ) in lower right-hand corner of the i.f. board.
 R169 (390kΩ) on tag connector A on the mains

input panel.
 C80 (25pF) adjacent to the ECC82/ECC804 on the timebase panel.
 The three separate capacitors C395, C403 and C404 are connected as shown in Figs. 5 and 6. The i.f. strip has a plug lead to fit the socket on the right-hand of the chassis—colour-coded leads to be connected as

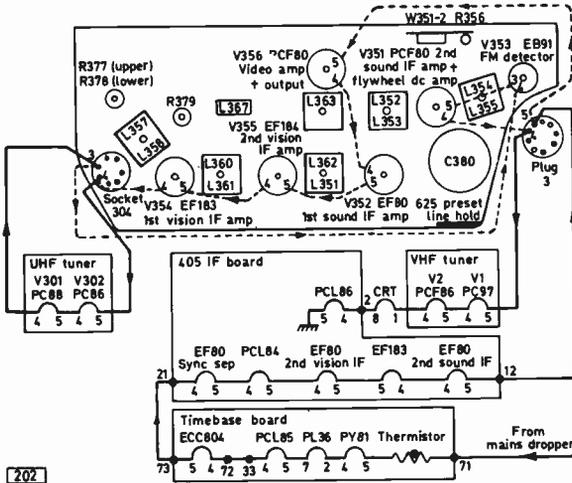


Fig. 7: Layout of the 625 convertor i.f. strip, with the complete heater chain after conversion (arrows point towards chassis).

shown in Fig. 5—and a socket for the u.h.f. tuner.

The new board has a preset 625-line hold control which is set up as follows: Short the top end of R356 (100k Ω —see Fig. 7) to chassis thereby disabling the flywheel sync discriminator. Set the main horizontal hold control for correct or near correct lock on 405 then switch to 625. Set the preset similarly for lock and then remove the short.

UHF Tuners

We gather that the sliderule-scale type of u.h.f. tuner intended for the Ferguson Model 3605 and others is not readily available but that the 3604-type with an indicator knob can be satisfactorily fitted in its place. A high-performance transistor tuner which plugs directly into the convertor strip is also available. Contact the supplier listed at the end of the article for details of what is available for particular sets. The Murphy conversion plinth which was described in our November 1970 issue has also been successfully used with the 800 and 850 chassis although a suitable adaptor lead has to be made up.

Back Panel

The original back panel will no longer fit the set after the convertor strip has been added. If the manufacturer's intended replacement panel cannot be obtained the stout cardboard box in which the strip was supplied can be used to extend the panel. Adequate ventilation holes must be made and of course no internal metal parts must be accessible.

This Month's General Fault: Blank Screen, Sound OK

This is a common symptom and unless the c.r.t. or its electrode voltages are at fault usually means that the e.h.t. is absent. The working sound channel tells us that h.t. is present. Listen hard for a line whistle since this indicates that the oscillator is working. The line output, boost diode, e.h.t. rectifier and line oscillator valves can quickly be checked by substitution

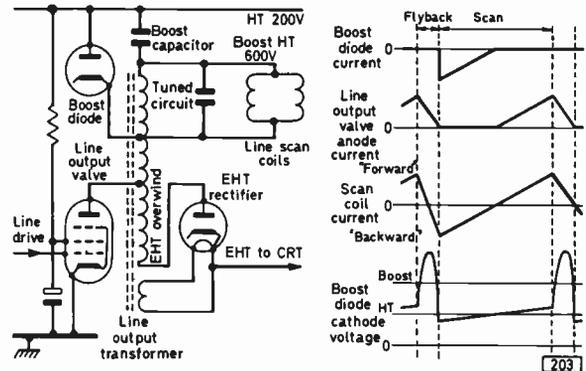


Fig. 8: Basic elements of the line output stage, with the associated waveforms.

(switch set off first!). If these bring no improvement check the screen voltage of the line output valve since the screen resistor often cooks, and the drive at its grid. There should be about 10V a.c. here with a negative d.c. level. If there is drive the remaining easy suspects are the boost h.t. capacitor and the transformer tuning capacitors. After eliminating these there is little left but the line output transformer itself which is comparatively expensive to replace. On some models it is possible to save money by buying a new winding insert only but the replacement involves more work.

When there is no grid drive the line output valve usually glows red hot inside. The fault may lie anywhere in the line oscillator circuit but first check the flywheel sync diodes if fitted, the coupling capacitor to the output valve and for a short- or open-circuit in the line oscillator transformer (if fitted).

The concept of generating the e.h.t. and boost h.t. from the flyback energy in the line output transformer is often forgotten as the breakthrough which made domestic television economic and the action of the circuit is not as well known as it should be. The essentials are shown in Fig. 8. Consider the state just before the end of the line scan. The line output valve is passing a large current which is flowing "forwards" in the tuned circuit comprising the scan coils. The valve then cuts off abruptly. Since the transformer is an inductive load a great positive peak forms at the valve anode. The peak rises and decays according to the resonant frequency of the tuned circuit. As it decays, current flows "backwards" in the scan coils, charging up the boost capacitor *more positively* than the h.t. rail. When the new scan starts the boost diode passes "forward" current into the tuned circuit immediately; the line output valve does not conduct until the *net* current in the scan coils is "forward", i.e. some way through the scan. At this point the source of current becomes the boost h.t. instead of the h.t. rail, giving the circuit higher efficiency. The boost diode prevents the boost capacitor discharging into the h.t. rail. Small currents can be taken from the boost supply thus generated to feed other parts of the set, typically the c.r.t. first anode and focus electrodes and the field oscillator for which a high voltage source gives better linearity. A servicing point is that the value of the boost capacitor is far from critical; both paper and electrolytic types are used in different designs, but it must have a high pulse working voltage.

A many-turned overwind, usually on a separate limb of the transformer and encapsulated in pitch,

and a small diode valve provide the e.h.t. supply to the c.r.t. inner coating. Although the supply is in pulses the capacitor formed with the outer earthed coating of the c.r.t. and the high source impedance provide adequate smoothing. In the chassis described this month the e.h.t. cable is in addition looped several times to act as an r.f. choke.

The problem of heater-cathode insulation in the e.h.t. rectifier, which at 15kV or so would be almost insurmountable, is avoided by powering the heater from a few turns of heavily insulated wire wound on the line output transformer.

A final warning about e.h.t.: cathode-ray tubes form excellent e.h.t. capacitors and there is usually nothing in the television circuit to discharge them when the set is switched off. A nasty surprise can be had when handling a c.r.t. even several days after use. Do not rely on momentarily discharging the e.h.t. connector since many tubes will build up a potential again after an hour or so. To be certain leave a shorting link in place for at least five minutes and preferably all the time that servicing operations are being carried out.

Suppliers

For Ferguson Model 506T receivers and spares for this chassis (covered in *Renovating the Rentals* last month) contact: Padgetts Radio Store, Old Town Hall, Liversedge, Yorks. Tel. Heckmondwike 4285.

Sets fitted with the Thorn/BRC 800 and 850 chassis are widely available but in particular try: Thornbury Trade Disposals, Thornbury Roundabout, Leeds Road, Bradford, Yorks. Tel. 0274-665670.

For 625 conversion kits for the 800 and 850 chassis and u.h.f. tuners contact: Manor Supplies, 172 West End Lane, London NW6. Tel. 01-794 8751. (Mail order: 64 Golders Manor Drive, London NW11.)

FOR THE SERVICE ENGINEER

A new pocket-sized multimeter has been introduced by Avo. The Avometer Model 72 has an impedance of 20,000 Ω /V and a frequency response to 30kHz. Ranges are 150mV-1kV d.c.; 10V-1kV a.c.; 50 μ A-1A d.c.; 1 Ω -20M Ω .

A new range of screwdrivers which hold screws firmly at all angles has been introduced by IXP Ltd. The Self-grip is available for both slot and cross-cut screws. Sizes range from 2.5mm to 6mm blade diameter with length from 75-175mm, and cross-slot sizes 0, 1 and 2 with a length from 125-175mm.

Adcola have introduced a thermal cable stripper incorporating a length stop device. The thermally-controlled blade temperature is specifically designed for stripping p.v.c. and polythene and cables up to $\frac{3}{8}$ in. thick can be handled. There are two models, the R400 and a bench mounted version the R310.

An extra-pressurised aerosol cleaner, the Preclene, is now available to the trade from Electrolube. The price of a single 12oz. aerosol is 63p.

ITT-KB SERVICE DEPARTMENT MOVES

The Service Department of the ITT-KB group is now located at Eldonwall Industrial Estate, Paddock Wood, Tonbridge, Kent.

NEXT MONTH IN

TELEVISION

PAL DECODER

Next month we start on the construction of the TELEVISION Colour Receiver and go straight to the heart of things—the PAL-D decoder. This is built on a conveniently sized printed circuit board and uses well tried and tested circuitry. The board can of course be used as a separate module with other equipment if the reader wishes. In building this decoder you will have a real opportunity to learn about colour signal decoding through practical experience.

RENOVATING THE RENTALS

The last Pye/Ekco valve chassis, the 11U/T418 dual-standard series, will be covered next month.

WIDEBAND BAND I AERIALS

Essential for DX use but not commonly available is the wideband Band I aerial. Along with details of practical designs Roger Bunney also presents information on the fundamentals of wideband television aerial design.

SERVICING TELEVISION RECEIVERS

The next chassis to have its common faults described in this series is that used in the Philips 19TG108 series. With a look also at the earlier, similar 17TG100U series.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW



TO.....
(Name of Newsagent)

Please reserve/deliver the MAY issue of TELEVISION (20p), on sale APRIL 17, and continue every month until further notice.

NAME.....

ADDRESS.....

The **TELEVISION** COLOUR

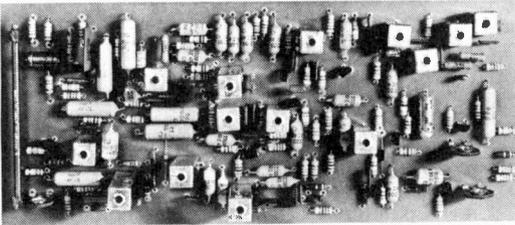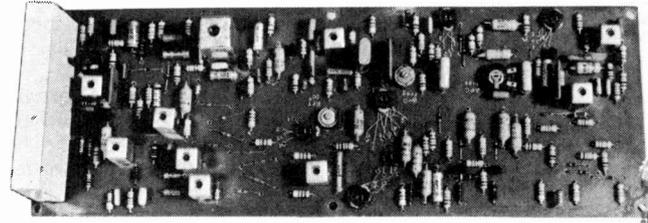

RECEIVER

THIS is the most ambitious project we have ever covered in TELEVISION. In response to the requests of many readers we have arranged the construction of a colour receiver in a way that we hope many people will be able to tackle.

But we feel we must also warn the reader: this is not the kind of project that you can afford to start without some thought. As we will see later there is a fair amount of money involved and of course the project can consume a considerable amount of the reader's time. The purpose of this introductory article is to outline some of the techniques and facilities that the receiver itself and the magazine are offering towards the construction.

A certain amount of skill is needed in the construction. This is inevitable with a project of the relative complexity of a colour receiver, and although we believe we have reduced the chances of building errors to extremely small proportions we would be way out in assuming that there are not going to be some errors made. This has to be and has been taken into account.

Method of Construction

The receiver construction is arranged in modules the size of each having been chosen so as to be a complete section of the receiver without being too large or cumbersome. Each of the main modules is on a printed circuit panel and these are mounted in the receiver so that they can be swung out for easy servicing—all the panels that is except the power supply.

The individual modules will be described in turn in the magazine and complete constructional and assembly details given; the modules will then be assembled in the cabinet—which will also be described—and the whole receiver harness wired up and the unit made to operate correctly. We will proceed at not too fast a pace, allowing the reader to follow the articles on a monthly basis whilst he is constructing the panels. In that way readers can have a completed receiver within one month of the final article appearing.

At this stage it is sufficient to indicate the general

facilities and methods used in the receiver: individual circuits will be described in full along with the constructional procedures. We would also point out at this stage that no claims are made to circuit originality: to design a completely new receiver system is unnecessary because we believe that what readers basically require is a product whose performance and reliability have been well tested. There are however a number of little "twists" of our own that have been introduced to improve the facilities and performance without impinging on the overall cost and we feel that these will be welcomed.

Block Diagram

The block diagram shown in Fig. 1 is very basic and serves only to show the general arrangement of the receiver and in particular the number of circuit modules involved.


The u.h.f. tuner (which may be a push-button, conventional or varactor type) has automatic frequency control (a.f.c.) fed to it from a discriminator at the output of the i.f. strip. A.f.c. is not just a desirable feature on a colour receiver, it is almost essential to enjoyable viewing to ensure that the saturation of the colour picture does not drift with small changes in tuned frequency. If a conventional tuner is being used and is not already fitted with a.f.c. facilities it can be suitably and simply modified.

The tuner output goes to a three-stage i.f. amplifier in which the majority of the out-of-band and v.s.b. shaping is undertaken by a filter arrangement at the input. The amplifier itself is basically broadband and is designed with forward a.g.c. facilities.

Two detectors are used for the main signals—one for luminance and one for chrominance and inter-carrier sound—and separate feeds are taken off for the a.f.c. discriminator and the a.g.c. detector.

The intercarrier amplifier in the receiver uses a silicon integrated circuit on the grounds of cost and efficient circuit action. A second silicon integrated circuit is used to provide the audio output. The prototype receiver uses a 3W output stage driving a 16 Ω 8 \times 5in. loudspeaker in the cabinet. For those who want higher quality audio reproduction a low-level output is also provided to drive an external hi-fi amplifier system.

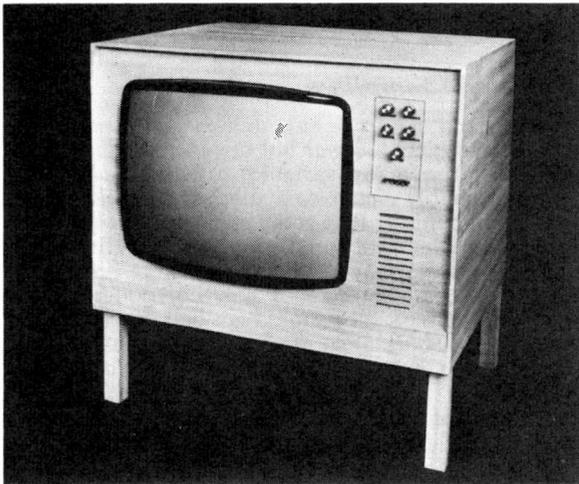The decoder used for the chrominance information is of the PAL-D type and is a straightforward design



of conventional form providing R-Y and B-Y outputs. The decoder forms a separate module by itself.

The luminance path consists of a preamplifier driving the luminance delay line and a phase splitter to give an output feed for the luminance matrixing and a feed for the sync separator.

The drive to the shadowmask tube is in RGB form and the matrixes and output amplifiers are designed to be extremely stable, well matched and under-rated. Feedback clamping is used to both

stabilise the black level and provide brightness control on the reproduced picture.

The timebases form another complete module with only the line output transformer and e.h.t. tripler not being mounted on the printed circuit panel. The line timebase uses flywheel sync of course and the line oscillator and line output stages use the only three valves in the receiver. A great deal of consideration went into the decision to use valves for these stages and much as it would have been pleasant to have had a fully solid-state receiver the importance of ensuring reliability—particularly in a home-built receiver—outweighed the wish to be technically “with it”. A low-voltage overwinding with an e.h.t. tripler is used and fifth harmonic tuning of the transformer employed. The generator is of the sinewave oscillator type for greatest stability.

The field timebase is solid-state with a silicon controlled switch (s.c.s.) oscillator and a transistor transformerless output stage. Feeds from both the line and field timebases provide the convergence waveforms and are fed to a separate module.

The separate power supply unit uses isolated chassis, transformer inputs and provides three sets of voltages, h.t., stabilised l.t. and heater volts. The additional safety afforded with an a.c. isolated chassis is not expensive to provide and must be considered very worthwhile.

An optional extra which can be fitted to the receiver is a crosshatch generator giving a built-in alignment source. This uses transmitted syncs and breaks into

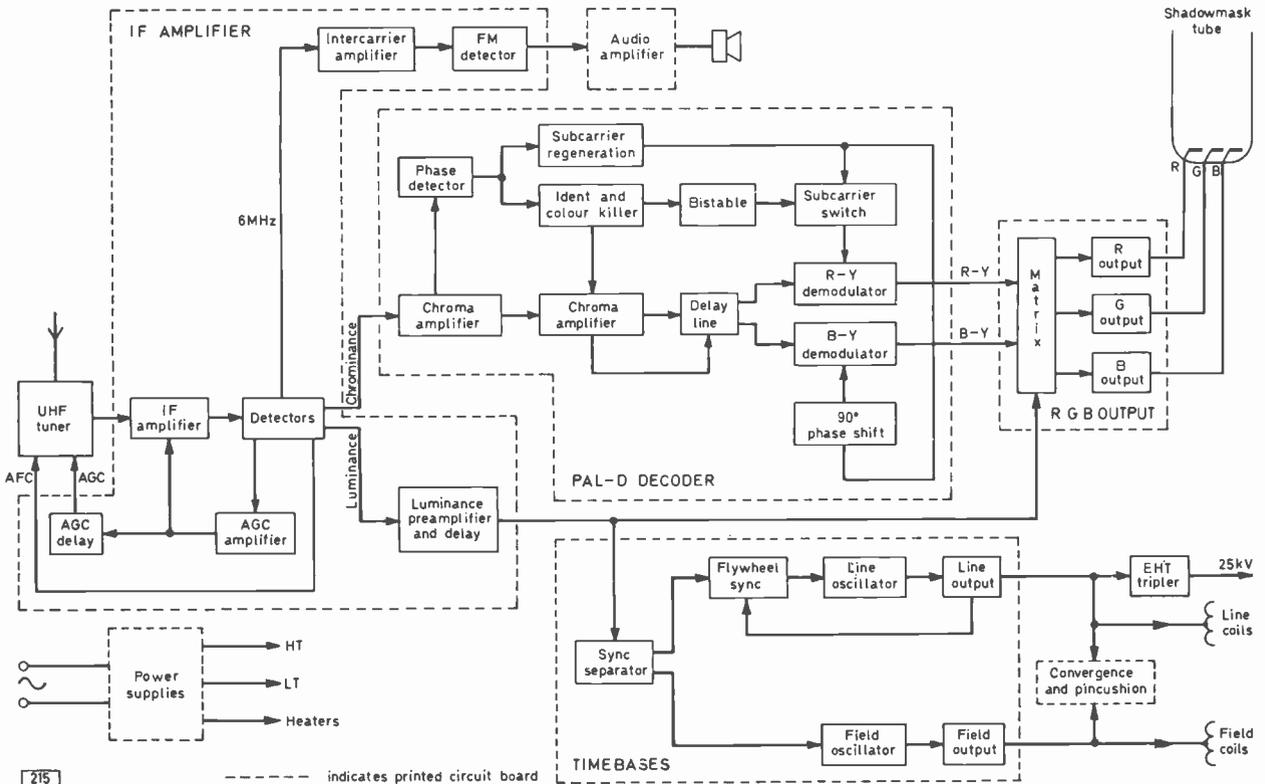


Fig. 1: Basic block diagram of the colour receiver project. Most of the components are mounted on the seven printed circuit boards indicated above. A conventional, push-button or varactor (varicap) tuner unit may be used but the latter type, which is now readily available, is recommended.

the luminance feed in the receiver whilst disabling the colour-difference feeds from the decoder.

The Cabinet

It would be a very great pity to spend a fair amount of money on the construction of a colour receiver only to have it sitting on the floor of your lounge in an open, Meccano-like condition. Apart from the dangers associated with the high-voltage circuits it is far more likely that the woman of the house will be persuaded to allow the rather inevitable mess during receiver construction provided she is guaranteed a reasonable piece of furniture at the end. Full constructional details will therefore also be given of a cabinet to go with the receiver. Indeed the cabinet played an important part in a number of the decisions associated with the design.

Cabinet size is dictated to a very large extent by the dimensions of the shadowmask tube and the other forward-facing components—basically the tuner and loudspeaker: a reasonably compact cabinet has been built around these size-determining elements. The problem in designing a cabinet for the home constructor is to keep the joinery simple while still giving strong construction and a presentable appearance. The extent to which we have achieved this can be judged from the photographs in this issue. Individual deviations by the constructor can of course be made and more (or less) frill attached. For the prototype receiver we had to decide which size tube is the most acceptable to the majority of viewers and from the sales figures of commercial colour receivers this seems to be the 56cm. (22in.) size. This is indeed a nice compromise between the small and the large and the price is a nice average as well. Details will however be given of the modifications required for the smaller and the larger tubes should these be wanted by some readers.

The strength of the cabinet has been put into the legs. They in fact continue to the top of the receiver beneath the external finish and form the basis of a main frame. Commercial designs rely heavily on proprietary processed boards so that they can be produced cheaply in bulk and also because these can have a surface finish already provided. For the amateur cabinet maker however these materials are expensive when thick enough to be reasonably strong and are difficult to work using hand tools. The design evolved therefore uses a timber frame to provide the strength with a thinner form of board to give the outer appearance. Even so one can sit on the prototype and there is no give in the surface.

The prototype receiver had to match in a roomful of high-quality mahogany furniture: the surface was therefore veneered in mahogany and when the series has been completed it will be polished to match the other furniture. The constructor may not need or want such a finish and alternative details will be given for finishing the cabinet without using veneer.

Space has been left in the cabinet for an 8×5in. loudspeaker and either a push-button assembly for varactor tuner control or a conventional push-button tuner can be incorporated.

But one of the nicest little extras we have provided in the receiver is at the bottom of the cabinet. The bar of wood across the front is in fact the front of a drawer in which all the convergence and basic set-up controls are fitted. This enables all facilities except

of course static convergence to be easily adjusted from the front of the receiver.

Costs and Suppliers

We would like to be able to give a precise price list for the complete receiver but this is unfortunately not practical; too many variables are involved and we cannot possibly dictate to a supplier that the price he charges for this or that component must remain fixed from this point until completion of publication. What we can however say is that the absolute limit of the cost for a complete set of new components and a new shadowmask tube should not be more than about £135. If you care to shop around—particularly in the case of the tube—this total may be considerably reduced.

A supplier has been arranged for *every* electrical component in the receiver. This includes not only the standard resistors, capacitors, transistors etc. but also items of major importance in the project: coils (either wound and ready for use or in a kit for home winding), printed circuit boards, convergence components and so on. For each component or batch of components in any module the supplier, the price, postage charges and other relevant data will be given. You will not be left out in the cold unable to obtain the components necessary to complete the project. Should any supplier let us down—and this is unlikely because we have screened them carefully—we will make alternative arrangements with all haste to fill the gap that is left.

Some readers are obviously going to deviate from the published design. In general we cannot guarantee to be able to assist such readers because the nature of the modifications tried out may be basically in error or may differ strikingly from the receiver requirements. For example a reader may opt to use a 625-line i.f. strip that he already possesses so as to save the cost of building a new one; in some cases this may be quite all right but in many others the modifications necessary to make the strip suitable for use with the rest of the receiver may be considerable.

One final word relating to the named suppliers seems in order. We have had to estimate how many readers will construct the project: we could be grossly in error with our guesswork and the demand for components could therefore be much larger than we expect. If this should happen we hope you will have a little patience with all concerned.

Alignment and Testing

Some parts of a colour receiver are very difficult to set up. Whilst alignment can be done without the use of specialised test gear the results can rarely be perfect and there are unfortunate occasions when the initial adjustments are so far out that there is no output with which to observe the results! This can be especially true of i.f. strips. We have reduced to an absolute minimum the number of variables that might be encountered and the printed circuit boards have undergone a number of design stages to reduce possible problems.

We will therefore give two distinct sets of procedures: instructions will be given on the setting-up using virtually no test equipment and a different set of instructions will be given for professional setting-up. We realise that with this system there are some

readers who although capable of the constructional side of the receiver will be deterred through having no test gear and an inbred—and very natural—fear of alignment. Mainly for these readers we are arranging an alignment service to which the completed circuit boards can be sent for alignment. This service must of course be charged for but the costs will amount to little more than the alignment time required and will certainly not be made at a “deterrent” level.

This same service will also be available for faulty units where the reader has made an error he cannot trace or where through no fault of his own components may be faulty. These things do happen and whilst we cannot possibly hope to prevent them we can at least offer this service to help readers out of any difficulties. Fault-finding of this nature (particularly in a module such as an i.f. strip) can be very long winded and without the proper test equipment may even be impossible if the unit is also misaligned. Even with professional equipment and techniques however some of these faults can still be difficult to trace and we must therefore charge the reader an economic rate for any work carried out on these lines.

We should also point out to the intending constructor that although these services will be available it would be foolish to construct the receiver without one particular piece of test equipment—a multimeter of preferably $20k\Omega/V$. Without making very basic checks with a multimeter on the final construction considerable damage may be done.

For those who feel able to perform their own alignment, using either their own or borrowed test equipment, the essentials (in addition to the multimeter) are: (1) An oscilloscope (6MHz bandwidth, line and field triggering). (2) A signal generator (with accurate frequency calibration and at least i.f. and intercarrier outputs and preferably a u.h.f. output). (3) A colour pattern generator. It is also advisable to have some sweep equipment available (again preferably u.h.f. but i.f. will do).

For the reader who plans to use our alignment service or the alignment-without-instrument instructions the optional crosshatch generator should be built into the receiver so that convergence can be set up in the absence of a commercial generator. The only other process that cannot be fulfilled without external equipment is external degaussing and details will be given for the construction of a degaussing coil.


Normal problems of misunderstanding or misinterpretation will be covered in the usual way by our Query Service under the normal conditions.

Towards the end of the series we will publish full circuit voltage details and signal waveforms in a correctly operating receiver to assist the constructor in any future servicing that may be needed.

Making a Start

There is quite a lot of information about the receiver construction contained in this short introductory article: you should spend some time familiarising yourself with the points we have raised.

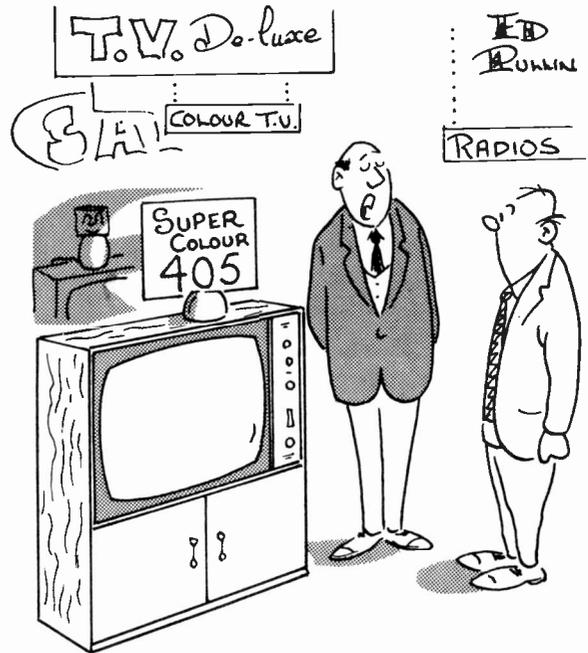Additionally check that you have the basic tools necessary for the construction of the first few modules of the receiver: (1) long-nose pliers; (2) small sidecutters; (3) soldering iron suitable for transistor work; (4) small hand drill with standard set of twist drills plus a $\frac{1}{32}$ in. twist drill.



"That's not the lines, it's the price!"


If you intend making your own printed circuit boards as well (details will be given) you could obtain the necessary etching material. We would recommend that you obtain a 1kg bottle of Ferric Chloride (hydrated, technical) manufactured by for example BDH Chemicals of Poole (product 26093). Most retail chemists will order this for you.

A Final Warning

Let us be blunt: have you understood this introductory article on the colour receiver project? If you have then you are probably in fairly good readiness to understand the whole series. If you have not followed this article then we must advise you to be extremely cautious about whether you proceed any further. We will go as far as it is possible for us to go in helping any reader who gets into trouble but we must be cautious about the degree of assistance that we can afford to give—we cannot after all be expected to build, rebuild or complete a receiver that a reader has abandoned. In addition do make sure that you can afford the project.

We are certainly not trying to dissuade you from the project: we would not have gone to the very considerable troubles that have arisen in presenting this work just to end up by putting people off but we do nevertheless feel a considerable obligation to ensure that readers do not start on a path they cannot finish. Each person knows his individual capacity and patience better than we can guess it. To those of you who decide to follow us through the project we wish a happy and successful constructional period—the results of which will be a high-quality colour receiver in an attractive cabinet and a furthering of your colour television receiver knowledge.

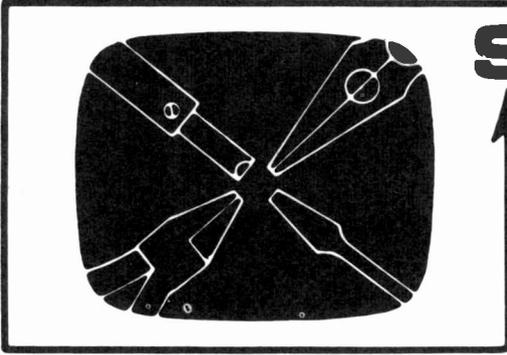Next month we build the first module of the receiver—the PAL decoder panel.



SERVICING television receivers

L. LAWRY-JOHN

BUSH TV103/TV105 SERIES—cont.

The line output transformer can give trouble and this is usually indicated by the resistor R98 ($2.7M\Omega$) wired on the rear end overheating. If this is found to be the case disconnecting R98 will cause arcing from the transformer core to chassis thus denoting a breakdown of insulation. A new transformer must then be fitted.

Field Timebase

The field output valve V11 is a PL84 with an ECC82 V10 acting as the oscillator. Either can become defective to cause either poor scanning, loss of height and hold or complete failure with a white line across the screen.

In these receivers a white line normally indicates valve failure, the ECC82 being responsible in the majority of cases. The PL84 is more likely to cause fold-up at the bottom or a similar condition.

Where one is more likely to be fooled for a while is when there is very poor linearity and the output valve is in order as is its bias resistor R84 and bias electrolytic C89, the controls and so on. With monotonous regularity we have found C82 to be at fault. This is conveniently mounted from one linearity control to the other in an obvious position thus making replacement extremely easy.

When searching for a cause of poor linearity, particularly at the bottom, do not forget to check the h.t. electrolytics especially C85 which decouples the screen of the PL84.

Hold troubles usually centre around the ECC82, either the valve itself or an associated resistor. Where the hold is weak however the ECC83 sync separator V9 can be responsible and it should be appreciated that an ECC82 will not function properly as a replacement.

Sound Faults

Whilst the valves, mainly the PCL82 V8, can be responsible for loss of sound complete absence is often due to lack of h.t. supply. R107 $2.2k\Omega$ is the supply resistor usually responsible with the habit of becoming open-circuit. There are times when it can be burnt out, either by a faulty valve or by a shorted electrolytic C125.

Distorted sound is another thing altogether. This can be due to a number of factors. If the distortion is worse on a strong signal check R48 and R49. These can go high-resistance, virtually shutting off the interference limiter MR4. If the distortion is present all the time or develops after the set has been on for a period the PCL82, its bias resistors R55 and R56

and, occasionally responsible, the coupler C67 should all be checked.

The Vision Strip

We have already mentioned the habit of R31 changing value to cause chaos and confusion. There is another unhappy fault which happens now and then. This is when the PCF80 video amplifier V5 develops an internal short: the screen feed resistor R32 then burns up and the cathode bias resistor R35 is not long in following suit. Should R32 be found burnt up therefore replace the PCF80 and check R35. Due to the presence of C124 the detector diode escapes damage and will rarely be found defective.

While the vision i.f. amplifier V4 seems to carry on working for ever and is rarely suspected we have found on some occasions that when it does lose emission the resulting symptoms can be confusing. The symptoms may well be persistent vision-on-sound and some degree of sound-on-vision. One would normally check the tuning and the a.g.c. circuit to find the cause of this sort of trouble but a good deal of time can be saved by checking the cathode voltage of V4. If this is less than 1.5V the valve should be changed and the trouble should be clear without further ado. This sort of trouble is usually however caused by a faulty EF85 in the V3 position or possibly a defective PCC89 on the tuner, either valve developing leakage to cancel the a.g.c., or by a shorted a.g.c. line capacitor which will give the same effect. These are more common causes and the repairer should normally check them first.

Tuner Unit

Apart from the necessity to clean the slider contacts at regular intervals the tuner as a rule does not give a lot of trouble. The PCC89 has a habit of losing emission to give a weak and grainy picture and either valve can cause the symptoms of no signals at all.

There are however times when the tuner is known to be at fault but the valves are also known to be in order. In this event it will be necessary to check the voltage supplies to each valve base. This may not be easy but it is often necessary. The screen feed resistor R9 ($12k\Omega$) of the mixer V2 (pin 9) can go high-resistance leading first to a weak reception condition and then to a condition of no signal at all except perhaps in areas of high signal strength.

There are very few faults which will not be revealed by a careful check of the switch contacts, valve base contacts, voltages and resistors for correct value.

TV TEST REPORT

E. M. BRISTOL

ANTIFERRENCE AK10 AERIAL KIT

THIS month we are departing from our usual test equipment report to take a look at a u.h.f. aerial kit that has been produced for the do-it-yourself TV owner. The continued expansion in u.h.f. monochrome viewing plus the boom in colour TV is resulting in the welcome disappearance of unsightly v.h.f. aerials from the roof-tops and the substitution of the less conspicuous u.h.f. array. The result has been a lot of extra work for the aerial riggers. Now while most of these make a good job of erecting an aerial this is not always the case. Some use inferior aerials to cut the cost of the installation, do not try for optimum results—being content to aim the aerial in the general direction of the transmitter—and are not too fussy about damaging or misplacing tiles.

As a u.h.f. array is less of an armful than a v.h.f. one many owners are tempted to have a go at installing one themselves and have the bonus of saving a pound or two in the process. Aerials of all sorts and sizes are readily available at local dealers and so are most of the bits and pieces needed to go with them. If you are like me however you will probably find that you have forgotten some necessary item when you are halfway through the job and then have to drop everything and go out to get it—only to find that the shops have closed!

The Antiferrence AK10 is a complete kit containing all that is necessary to install the aerial except the coaxial downlead. Obviously the length of the coaxial lead needed will vary considerably from one installation to the next so it would be impractical to include this in a kit. All one needs to do is measure up the length of coaxial cable needed, add two or three yards to be on the safe side and then buy the resultant length along with the kit.

Kit Contents

First let us see what is contained in the kit. The aerial itself is the Antiferrence TC10, a ten-element Yagi with folded dipole, and is part of the normal Antiferrence range of aerials. Next there is a mounting arm which consists of a tube with a right-angled bend, and a clamp for securing the aerial to the arm with a bracket for fixing the arm to its mounting place. Three plastic pull-through-and-lock cable securing straps are also supplied for holding the downlead firmly to the aerial.

Coming now to the bottom end of the installation we have a white outlet box, a two-yard jumper lead fitted with coaxial plugs at both ends and a supply of cable-clips with nails for running the downlead along the skirting board to the outlet box. Also supplied are screws for the outlet box and aerial bracket and a couple of wall plugs. Last but certainly not least there are printed on the box step-by-step installation instructions and eight very clear diagrams. Although installation is a simple operation there are pitfalls for anyone who has not fitted an aerial before: these instructions however make everything perfectly clear. When dressing the cable for example the amount of conductor, insulation and braiding to be exposed is usually estimated by guesswork; often it is found that one has bared too much or not enough. Here the exact amounts for top and bottom ends of the coax are given.


So much for the contents of the kit: we will now take a closer look at the individual items. Most important of course is the aerial itself. U.h.f. aerials are commonly available with from 6 to 18 elements, usual combinations being 6, 10, 13 and 18. The greater the number of elements (other features of the design being carefully adjusted) the greater the gain and the more directional the aerial. High-gain aerials are needed for monochrome reception in the fringe areas and also for colour reception in the medium ranges but low-gain arrays are satisfactory for medium-range monochrome and short-range colour reception. Local topography may of course modify these general rules.

Now it may at first thought appear that a kit should include a high-gain aerial and thus be suitable for all areas. There are snags however. High gain in good service areas can mean input stage overloading and cross-modulation. This could of course be cured by using an attenuator but then the question would arise of whether to supply one with the kit and whether the extra expense would be justified. A further factor is that high-gain aerials can be very sharp in their directivity so that a few degrees outside the normal acceptance angle will actually give a lower signal than a lower-gain aerial similarly off direction. As the aerial is intended for inexperienced fitting it may well end up several degrees away from the optimum. High-gain aerials should in fact be fitted by experienced riggers and are not suitable for a do-it-yourself kit. A 6-element aerial on the other hand would only be suitable for use in very good reception areas so that a kit with such an array would be of limited appeal. By using a 10-element array a compromise has been reached giving reasonable signal strength over most of the service area with a fair latitude in positioning.

Report

The aerial tested was a group C/D one and was tried out on channels 58, 61 and 64. The acceptance angle for this is $\pm 23^\circ$ —for an 18-element array by the same firm the acceptance angle is $\pm 18^\circ$.

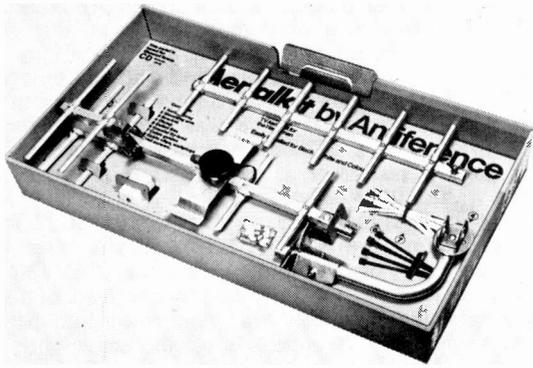The gain of the aerial on channel 58 is 11.5dB, on channel 61 11.8dB and on channel 64 11.6dB. Thus to all practical intent the gain is constant over the three channels. In fact over the whole range of the aerial (embracing 19 channels for group C/D) the maximum deviation was only 0.9dB. The front-to-back ratio is about 30dB average for the three channels.



The Antiference AK10 aerial kit.

While there must be a compromise between low and high gain for a kit I think that of the two medium-gain arrays, 10- and 13-element, on balance a 13-element one would have been better. Colour sets need a good signal to avoid noise on saturated chrominance areas and undoubtedly many of these kits will be used with colour sets. In addition as the kits are intended for fascia-board or window-sill mounting rather than chimney mounting we may expect a somewhat lower signal due to shielding by nearby walls and other buildings. Hence a few extra microvolts would have been an asset: the decrease in acceptance angle would not be too great and the extra directional properties could be useful in dealing with ghosting.

Having said this on behalf of prospective users in poorer signal areas I must add that I found the noise on a colour receiver operating in a medium-range area to be quite acceptable with the aerial mounted in the attic and ordinary coaxial downlead used—not low-loss as recommended.

As to construction the aerial and the arm are made of aluminium to avoid rusting, and to prevent the usual black deposits on the hands when handling and also to prevent corrosion due to acid in the atmosphere the aluminium has been chromate-dipped. We found that it can indeed be handled without any trace of soiling. The brackets and clamps are of steel treated

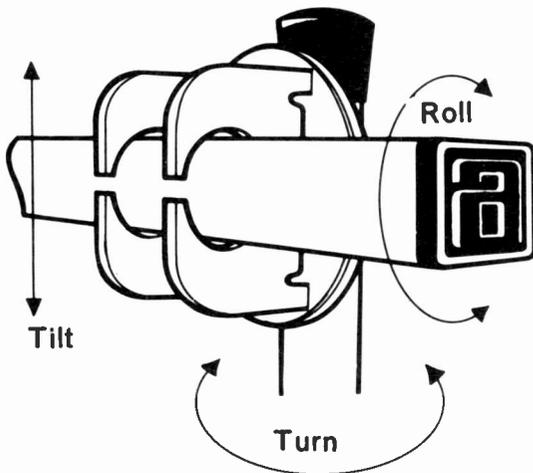


Fig. 1: The ingenious aerial clamp.

to avoid electrolysis action between dissimilar metals. The life-expectancy of the aerial is of course an unknown quantity but it can be mentioned that Antiference have a good reputation in the trade for long-lasting aerials and there are still many old Antiference v.h.f. aerials up and going strong while the aerials of many other makes of the same vintage have long since fallen apart.

Assembling the aerial is straightforward. The reflector which consists of four elements mounted on two brackets is packed flat but clicks into position without removing or fitting a screw and is locked by tightening a wing nut. A boom-arm supporting the first 6 directors is separate but slots into the main arm and is secured by tightening another wing nut. Just a minor point here, the boom can be fitted upside down by someone who doesn't bother to read the directions: I know they should do but some folk like to try first and read about it afterwards. Actually the instructions could be missed (as in fact I did!) because they are printed on the bottom of the box: on or inside the lid would have been a better position.

The clamp for holding the aerial to the arm is one of those delightfully simple devices which are really highly ingenious. It is shown in Fig. 1. By means of it the aerial can be tilted up or down, rolled from dead vertical or horizontal, or turned. All these movements are solidly locked by tightening just a single wing nut. Thus the mounting bracket can be fixed to the house in almost any position and on any convenient support and the aerial can then be swung to the right direction. Top marks for this!

As already mentioned the mounting bracket is designed for fixing to a wooden fascia, window-sill or brickwork—hence the wall plugs supplied. There is no chimney lashing. Here again thought has been given to the prospective installer: few householders relish the prospect of clambering over the roof to the chimney stack (though this is the standard fixing position for the professional rigger) but a ladder up to the guttering is within the capabilities of most. Before fixing though, heed the instructions by trying different positions both vertically and horizontally. At u.h.f. quite amazing differences in signal strength can be found only a foot or so apart.

The outlet box and jumper lead are standard items. One advantage of the latter is that the plugs are fitted and soldered. It has been found that amateurs often make rather a mess of fitting a coaxial plug. Either they don't solder them (and this goes for many aerial riggers too), relying on a press fit between the cable centre conductor and the centre pin of the plug and thereby sowing the seeds of future trouble, or they melt the plastic inner insulator by holding the iron on too long. Often too they manage to get a short from the centre pin to the braid. All these problems are eliminated by having the lead ready made.

Finally the cost has to be considered. The retail price of the kit is £4. If we add the cost of the equivalent aerial from the Antiference list and all the bits and pieces we come to a figure very little less. But with the kit we have the advantage of all the things we need for the installation in one package plus the valuable set of instructions and diagrams.

Kits are available for group A (channels 21-34), group B (channels 39-51) and group C/D (channels 49-68). I would then recommend this kit for use in all except fringe areas and difficult locations where the services of aerial specialists should be obtained.

SERVICE NOTEBOOK

by G. R. Wilding

No Picture

THERE was absence of line whistle on a GEC Model 2017 and the overheating PL500 and PY800 clearly indicated lack of line drive. A new PCF802 line generator/reactance valve failed to produce results and on making voltage tests it was found that there was zero potential at the screen of the pentode section. This was due to R124, which is connected from one end of the oscillator coil to the pentode screen grid, being open-circuit. On replacing this resistor line whistle and a normal picture developed, although it was found necessary to readjust the core of the oscillator coil for optimum locking. The line output pentode appeared to be none the worse for its temporary overload but as tapping the envelope of the PY800 produced an occasional splutter this was replaced.

During the subsequent soak test it was noticed that sound quality gradually deteriorated. A new PCL84 failed to improve matters but although the 120Ω pentode cathode resistor was of unchanged value the cathode voltage was over 4V instead of 3.1-3.0V on v.h.f. and u.h.f. respectively. This naturally indicated excessive anode and/or screen current but as the screen is directly returned to the HT3 rail the most likely cause of the excessive cathode bias voltage was a slight leak in the coupling capacitor from the triode section anode. On changing this capacitor the cathode voltage of the pentode remained constant at 3V and the sound was undistorted.

No Colour

THERE was normal monochrome but no colour on a dual-standard Bush Model CTV25—even after disabling the colour-killer by applying forward bias to the delay line driver transistor 5VT2 by means of an 18kΩ resistor from its base to the positive l.t. rail. This strongly suggested absence of reference oscillator output and this was confirmed by 'scope application to Test Point E4 (Fig. 1).

Voltage tests then showed that the collector potential of the reference oscillator transistor 6VT3 was 15V—equal to l.t. rail supply—while the base and emitter potentials were virtually nil whereas they should have been 2.7V and 2.5V respectively. Our

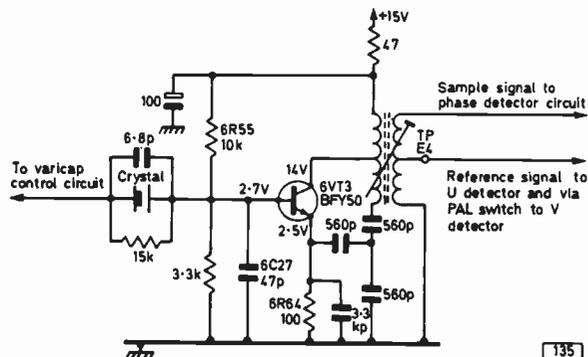


Fig. 1: The decoder reference oscillator circuit used in the Bush-Murphy dual-standard chassis.

first suspicion was that the base bias supply resistor 6R55 was open-circuit or that there was an internal base-emitter short in the transistor as either of these would remove the forward bias and cut off the collector current. Ohmmeter tests showed however that 6R55 was OK but that there was almost a perfect short-circuit from 6VT3 base to chassis. This clearly ruled out the transistor as its emitter is returned to chassis via the 100Ω resistor 6R64.

The only possible cause was a short in 6C27 the 47pF capacitor from 6VT3 base to chassis (used to reduce the effect of the input capacitance of 6VT3 on the crystal tuning). On unsoldering one lead of this component the diagnosis was confirmed and after replacing it colour reappeared on the screen but it was naturally found necessary to run through the reference oscillator phase discriminator setting up procedure to establish optimum colour lock.

Unusual Short-Circuit

On switching on a Bush Model TV115L a section of the mains dropper began to grossly overheat and glow. A short-circuit of such severity is usually caused by a heater-cathode short in the line output pentode or the boost rectifier, both being placed at the top of the heater chain, or by a short in the h.t. rectifier resulting in the a.c. supply to its anode being passed via the electrolytics to chassis.

We switched off before the valves had time to warm up but were unable to see the line output valve and boost rectifier as they are enclosed in the usual protective can. As the original finned h.t. rectifier had been replaced by a BY100 conveniently mounted at the bottom of the chassis however we decided to check this first and found a dead short with the ohmmeter connected in either direction. On unsoldering one lead we found that this component was perfect and on then unsoldering one lead of the shunting protective capacitor we found this to be perfect also. Furthermore when any valve was removed from the circuit the resistance reading across the mains lead became almost infinity so that if there was a heater-cathode short-circuit in the line valves it wasn't present when they were cold. Most heater-cathode failures of course develop only when the valves concerned get hot so we next changed both the line output valve and the boost rectifier since it appeared that one or the other must be at fault.

On switching on again however the results were as before, a section of the dropper resistor overheating but no valves warming up. There was obviously something unusual about this fault or the circuit, and on noticing a large 0.5μF capacitor mounted close to the PL36 we applied an ohmmeter to it and found it to be completely short-circuit. On snipping it out of circuit the valves warmed up normally, there was no sign of overheating at the dropper resistor and on resoldering the h.t. rectifier back in circuit the h.t. reappeared and the set worked normally. On inspecting the circuit diagram we found that this capacitor is connected between the a.c. mains supply and the h.t. rail thus shunting the h.t. rectifier: its purpose is to apply a small a.c. to the d.c. supply to improve the hum level by cancelling the residual ripple. All of which goes to show that even in the simplest receiver subcircuits—the h.t. and heater current supplies—there can be surprising circuit variations which if not known can cause much needless testing.

Tweaking the



VIVIAN CAPEL

MOST workshops get their share of ancient TV sets which for one reason or another must be kept going for a little while longer. Many of them need expensive repairs which are not economically worthwhile so that quick, short-cut methods have to be employed to get the set working to a reasonable standard. Often the fault complained about by the owner is put right whereupon a smeary picture with poor definition appears on the screen. This may not have been mentioned in the original complaint—in fact it may not have been recognized as a fault condition by the owner who may have accepted the condition for a considerable period.

I.F. alignment seems to be required but the engineer knows that a complete realignment by the book will be a lengthy and hence uneconomical procedure considering the age of the set. The only thing to do is to attempt to obtain some improvement by adjusting the cores on a test card.

Check the Video Circuits First

Before doing this however the conditions at the video stage should be checked as a fault here can considerably modify the video response. The d.c. operating conditions can be checked with a meter, and in particular the small-value capacitors that are generally to be found shunted across all or part of the cathode bias resistor should receive attention. The function of these capacitors is to bypass the bias resistor and therefore to reduce the current negative feedback taking place across it. Because of the small value of these capacitors they are effective only at high frequencies at which they thus produce increased gain. This helps overcome the h.f. losses that may be occurring elsewhere in the video circuit and it can be seen that should they go open-circuit the result will be poor h.f. response.

Another possible cause of poor h.f. response in the video stage is the peaking coil(s) often found in series with the anode load. These present a high im-

pedance at high frequencies and thus increase the anode load and the gain at these frequencies. They are usually shunted by a resistor and in fact are often wound over the body of the resistor. Thus if the coil goes open-circuit the h.t. feed to the video amplifier anode is maintained and this may lead one to look elsewhere for the cause of the trouble. The most common place for such coil(s) to go open-circuit is at the end where the winding is soldered to the resistor lead-out wire. A spot of corrosion here or even a dry-joint from the time of manufacture may take many years to show up. A check with the ohmmeter, which should give a fairly low reading if the coil is OK, and a visual inspection should reveal the fault if present. Similar coils are often included in the grid feed as well.

Forming the IF Response

Having eliminated the video stage by these few tests attention must be turned to the alignment. Although recommended alignment methods vary tremendously from one set to another—as a glance at a few service manuals will confirm—the basic principle is the same. The standard 405-line vision i.f. is 34.65MHz. As only one sideband is necessary to carry the signal information single-sideband operation is used and the response below 34.65MHz is therefore eliminated. Above 34.65MHz the response is extended as evenly as possible to 37.65MHz, 3MHz higher, where it falls off rapidly to a dip at 38.15MHz: this is the 405-line sound i.f. where it is essential to have the response at a minimum to avoid sound-on-vision effects. The typical response curve is shown in Fig. 1.


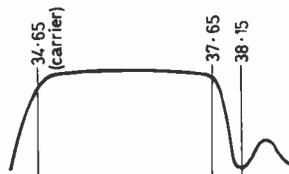



Fig. 1 (left): Typical 405-line vision i.f. response curve.

Fig. 2 (right): How the various individual stagger-tuned responses add to give the overall response. The sharp dip is due to the sound rejector.

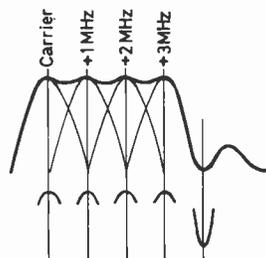

In order to achieve a flat response extending over 3MHz the individual i.f. coils are stagger-tuned, that is each is tuned to a different frequency within the passband. The effect of this is shown in Fig. 2 where there are four different tuning frequencies: each peak is arranged to fill in the gap in the passband left by the others. Individual sets vary as to the number of different peaks used to obtain the overall curve, depending on the number of tuned circuits in the i.f. strip and the width of each one. In order to minimise the bumps and dips across the top of the complete curve caused by the individual peaks, the individual responses are broadened or flattened either by damping the coils with shunt resistors or by employing loose coupling in the i.f. transformers. The final transformer is well damped by the detector diode.

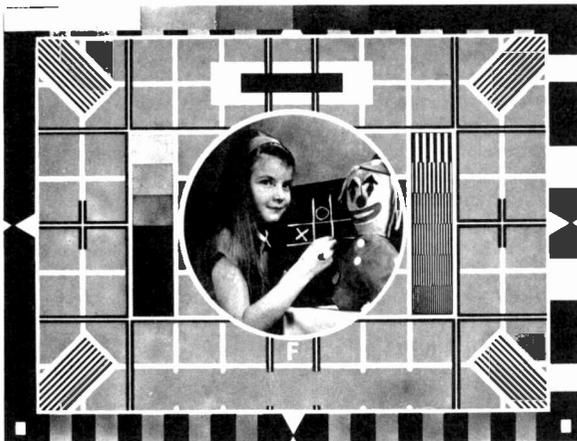The rapid drop at the upper end of the curve is caused by the sound rejector circuit(s). The response given by these is not broad like the passband response



Test card F as radlated on the 405-line v.h.f. channels. The frequency gratings are to the right of the centre circle. As the card is originated on the 625-line standard and converted down to 405 lines the gratings represent (from the top) 1 MHz, 1.6MHz, 2.25MHz, 2.6MHz, 2.9MHz and 3.4MHz. The latter two are likely to be indistinct on most 405-line receivers due to the removal from the transmitted signal of colour information (which is at the h.f. end of the channel bandwidth) to avoid degradation of the converted 405-line picture. Test card F is the joint copyright of the BBC, BREMA, EEA and ITA.

peaks but is made as sharp as possible in order to give the maximum rejection at the sound i.f. This is indicated at the right of Fig. 2.

Mistuned IF Stages

Having digested the basic theory—or refreshed our minds on it as the case might be—let's see what happens when things go wrong. In theory once a coil has been tuned and the core set it should never again need adjustment. In practice however this is not so: cores become loose and shift and stray capacitances which help to tune the circuits alter as a result of valve and component replacements. Thus realignment becomes necessary.

Unless the set has been in the hands of someone who has recklessly twiddled all the cores in sight—and this is unfortunately not an uncommon experience—one can assume that not all the cores need adjustment. In fact only one or two might require resetting and even these should not be too far out. The question is, which ones?

One method of finding out without going through the process of complete realignment is to systematically turn each core in the vision i.f. strip a couple of turns each way. Note carefully the starting position and return the core to it if no improvement is obtained. This should be done with the test card being displayed. Watch the h.f. response as indicated by the frequency gratings and the i.f. response as shown by a clear presentation of the black bar at the top of the card without smearing on the right. Also look for signs of ringing—the appearance of an outline to the right of the frequency gratings.

It will sometimes be found possible to improve one of these three factors at the expense of one of the others. This indicates that we are on the wrong track and the core should be returned to its previous posi-

tion and another one tried. Each core that is tried should be returned to its original position *before* the next one is adjusted. If on adjusting a core improvement is noted in any respect without detriment to the others the core can be left in the best new position found and the others tried for further improvement.

It may not however be necessary to try each core in this manner. It may in fact not be possible because over a period of time some cores have a habit of jamming tight so that no amount of persuasion will shift them.

Assessment by Test Card

Let us assume then that one of the i.f. coils has shifted its tuning point by a moderate amount; what will the likely effect be? This depends of course on which one it is. If it is a coil which contributes one of the inner peaks a sideways movement will produce on the overall response curve a dip where it should have tuned and a higher peak where it is now tuning because it has become partially superimposed on one of the other peaks; a typical example is shown at Fig. 3. The result is an excessive response at some modulation frequencies and a reduction at others. On test cards this will appear as a flaring or ringing after one set of frequency gratings accompanied by a loss of resolution at the adjacent one.

Fig. 3: If one of the circuits is off tune the result is a dip where its peak should have been and a peak where it is superimposed on another.



In the curve shown in Fig. 3 the displaced peak has moved towards the low-frequency end of the pass-band so we would expect flaring after the 1.5MHz gratings and loss of definition at the 2MHz gratings. The higher frequencies would in this case be unimpaired. Had the peak moved the other way however there would have been a dip at around 2MHz as before but flaring at 2.5MHz. If one of the other peaks had moved there would be a corresponding indication in the frequency gratings.

It can be seen therefore that if it is known which core affects which part of the response (this can be ascertained from the service manual by looking up in the alignment procedure the frequency differences from the centre 34.65MHz vision i.f. given for the various coils) then by looking at the test-card frequency gratings the core to adjust can be selected right away.

In our illustration (Fig. 3) the peak that is responsible for the response at around 2MHz has moved to a lower frequency (discovered from the effect on the test card). If we have the manual we can check therefore to see which core must be adjusted to affect the response at $34.65 + 2.0 = 36.65\text{MHz}$ or thereabouts: this is the one to attack! We can even tell which way to turn it because if it is tuning too low we must decrease the inductance so as to tune higher, which means bringing the core out of the coil, while if it is tuning too high we must increase the inductance by screwing the core in.

Even though one of the tuned circuits has gone off tune to give the response shown in Fig. 3 and the effect can be seen on the test-card frequency gratings it is unlikely that the fault will be too noticeable on a picture provided the deviation is not too great. This

is especially the case in old sets where there are likely to be other faults as well—such as a not-too-bright tube.

Mistuned Sound Rejector

Look now at the response curve shown in Fig. 4. Here the higher frequencies are completely killed off by a sharp dip that has appeared and the result on the screen is a very poor-definition picture. That sharp dip and its position at the h.f. side of the curve should give you a clue as to its origin if you didn't already know: yes, it's the sound rejector that is off tune.



Fig. 4: The result of the sound rejector being off tune is sharp h.f. loss.

It follows from this that a mistuned rejector has a far worse effect on the picture than an off-tune i.f. coil; furthermore because it is sharply tuned the setting is much more critical. One turn of the core of an i.f. coil may have little observable effect on the picture but just try it with the rejector! Not only is there a marked loss of h.f. but there will probably be signs of sound-on-vision on heavy sound passages as well. It is quite likely however that if the core is not too far off tune the rejection at the sound i.f. will be sufficient to reduce the sound interference to an almost unobservable level with average sound modulation. This will be especially so if there is another rejector that is on tune in the circuit.

Where there is poor definition therefore, whether sound-on-vision is present as well or not, it always pays to try the rejector(s) first. The rejector(s) can be identified from the manual as the core(s) which must be adjusted for *minimum* output at 38.15MHz. Adjustment must be for minimum sound-on-vision and the easiest method is to use the fixed note that is occasionally transmitted with the test card. After tuning the fine tuner for maximum sound the rejector is adjusted to give minimum ripple. If the note is not present (they rarely seem to transmit what you want when you want it!) it is possible to use the accompanying music if it is not too soft. Owing to the varying nature of the music a null point is not always easy to find: the best way is to tune slightly to one side until sound-on-vision just appears on sound peaks, then to tune to the other side for a similar effect and finally to set the core to the halfway point between the two positions.

The method recommended in manuals is, of course, to use a signal generator to inject a 38.15MHz signal. The sound i.f. coils must however be tuned to the same frequency and as they may be a little off tune using the signal generator method means lining up the sound i.f. stages first. By using the transmitted signal and tuning the oscillator (fine tuner) to maximum sound however, one is sure to tune the rejector(s) to the same frequency. Once the correct setting has been made the video definition should be restored.

Adjacent Channel Rejectors

More often than not in such cases it is found that adjustment of the rejector(s) is all that is required and that further attention to the i.f. cores brings very

little improvement. Some sets, particularly fringe models, have rejectors tuned to the adjacent sound and vision carrier frequencies. Thus there is an adjustment for minimum response at 33.15MHz (adjacent channel sound) and less often at 39.65MHz (adjacent channel vision). These are well outside the vision passband and should not cause any trouble—except to allow adjacent carrier sound or vision through—even if they have drifted a bit.

Jammed Cores

Jammed cores are always a problem. One can go to a great deal of trouble to remove a core, probably breaking it in the process, only to find on fitting a replacement that little or no improvement can be made by adjusting it so that the old one must have been in the correct position all the time. By diagnosing which core is most likely to effect an improvement in the manner outlined here any others that are jammed can be left alone.

Most cores even in older sets are of the hollow type with a hexagonal hole for insertion of a suitable trimming tool. Trying to turn these with anything other than the proper tool will almost certainly break them if they are a little stiff. Even the correct tool becomes rounded at the corners with frequent use and then fails to turn the core. A supply of these tools should be kept by the engineer (they are quite cheap) and they should be discarded as soon as they exhibit signs of wear.

Fortunately such cores if they jam or break can be removed without too much trouble by being broken up inside the coil former. A small-bladed screwdriver is used to break off pieces of the core which will fall through to the bottom end of the former. If this is done a piece at a time it is not long before the complete core is broken up and the coil former is clear. Make sure to clean the thread of any remaining pieces before fitting a new core or this too might jam. A smear of thick grease will help to prevent it jamming yet will lock it against working loose from vibration.

Sound/Vision Beat Patterns

Another effect often seen on older sets is the appearance of a fine pattern of dots over the screen. This is caused by a 3.5MHz beat pattern and a trap to eliminate it is often found somewhere around the video amplifier, usually in the cathode circuit. Often this is a single unscreened coil. The core should be set to give minimum patterning but it is often found to be off tune. Although the pattern is not always instantly noticeable it is surprising how much cleaner the picture looks when the pattern is removed.

Conclusion

The methods we have outlined here for lining up the i.f. tuned circuits on the test card should not be used on modern sets, especially dual-standard models. Wobbulator alignment is the only sure way of getting the desired response with these models: even the spot-frequency method painstakingly and laboriously carried out often yields disappointing results. For a quick job to bring about passable video response on an otherwise uneconomic repair there is, however, nothing to beat knowledgeable core adjustment on test card. ■

COLOUR RECEIVER CIRCUITS

GORDON J. KING

THE BURST CHANNEL

LAST month we looked at some active reference generator circuits—the type using a crystal oscillator and a.p.c. loop. This month the plan is to go on to investigate the passive type of reference generator. Since, however, with this type of generator the signal is derived directly from the bursts let us first look at the circuits in which the bursts are extracted from the chroma signal. We shall consider the burst channel first as used with conventional active reference generators and then pass on to the passive generator system.

We saw last month how with an active generator circuit the phase detector produces a variable control potential to vary the bias applied to a capacitance-diode in the crystal oscillator circuit. To do this the phase detector must receive both the bursts and a sample signal from the reference generator.

Block Diagram

The bursts form a part of the chroma signal, which is usually extracted from the composite transmitted vision signal by a high-pass filter. For correct operation the bursts, which occur during the back porch of the sync pulse, have to be extracted from the chroma signal and furthermore the chroma channel has subsequently to be blanked so that the bursts are not present at the output of the chroma channel. Fig. 1 shows in block diagram form the processes involved.

Burst Gating

As the bursts are present on the rear porches of the line sync pulses it is a relatively simple matter to extract them from the chroma signal by "gating" at line frequency. The separated bursts are then amplified and passed to the phase detector. The gating transistor may operate as the amplifier as well and the stage is designed to be non-conductive (i.e. biased to cut off) during the lines of picture information. Pulses at line frequency rate are applied to the stage to make it conduct and pass the signal during the period of the bursts only. Exact pulse timing is thus important.

Typical Circuit

The circuit used in dual-standard Decca receivers is shown in Fig. 2. Here Tr1 is the first chroma amplifier stage which feeds signal to the second chroma amplifier and also the burst gate/amplifier Tr2. The signal for the burst amplifier is filtered out by the 4.43MHz tuned circuit L1/C1—with damping provided by R1—and is coupled to Tr2 base through C2. There is no fixed bias at Tr2 base while a reverse bias is applied to its emitter via R3. It is thus normally non-conducting. To gate it on during the

bursts correctly-timed positive-going pulses are fed to the base via R2. The transistor thus switches on during these periods and amplified bursts appear across L2 which is the input to the phase detector.

The Burst Signal

The bursts can be regarded as a 4.43MHz carrier wave with 100% squarewave modulation of mark-space ratio approximating 1:28—see Fig. 3. In other words the burst signal consists of the 4.43MHz carrier wave with upper and lower sidebands corresponding to the line frequency and its harmonics plus sideband components of $\pm\frac{1}{2}$, $\pm 1\frac{1}{2}$, etc. of the line frequency due to the swinging bursts (the $\pm 45^\circ$ alternate line phase shifts used for ident purposes). The half line-frequency components arise because the swinging bursts return to the same phase every second line. The bursts in other words are also effectively modulated by a frequency of half 15,625Hz, generally

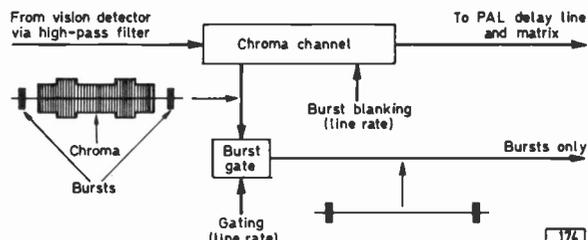


Fig. 1: Block diagram showing the burst gating action.

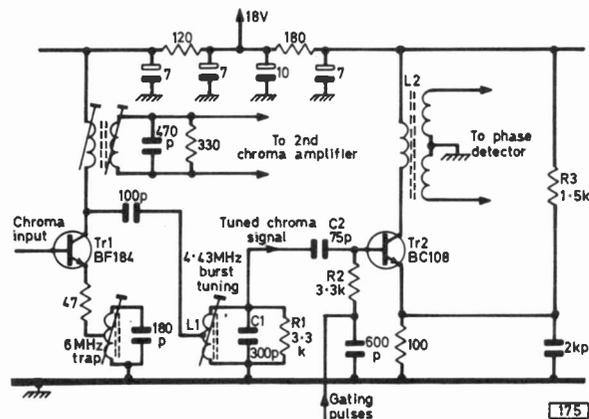


Fig. 2: Representative circuit (Decca dual-standard): Tr2 is the burst gate/amplifier which drives the phase detector transformer L2. It is fed with chroma signal from the chroma amplifier Tr1 via the tuned circuit L1, C1 and is gated on during the bursts by pulses fed via R2 from the pulse generator stage shown in Fig. 5.

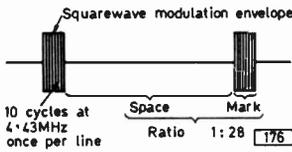


Fig. 3 (left): As the bursts occur once each line (during the back porch period) they can be considered as a 4.43MHz sinewave 100% modulated by a squarewave at line frequency.

Fig. 4 (right): As a result the burst signal consists of the 4.43MHz subcarrier plus sidebands at line frequency as shown here. There are also sidebands at half line frequency because in the PAL system the bursts are alternated in phase line by line. These sidebands are shown in broken line. The bandwidth of the burst signal extends $\pm 1\text{MHz}$ each side of 4.43MHz.

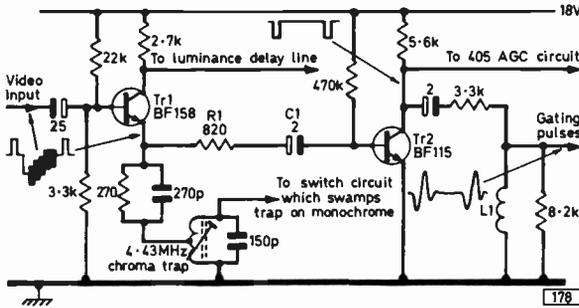
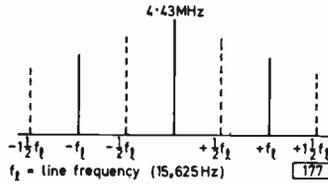


Fig. 5: The pulse generator used in Decca dual-standard models to produce the pulse to switch on the burst gate. An output with positive-going sync pulses is taken from the luminance preamplifier Tr1 and fed to the base of Tr2. As a result Tr2 produces negative-going pulses which are fed to L1. This coil rings, producing a positive-going overshoot which is coincident in time with the bursts and is used as the burst gating pulse (fed to Tr2 in Fig. 2).

referred to as 7.8kHz. The spectrogram in Fig. 4 shows the immediate sidebands of the bursts and to avoid distortion of the bursts the bandwidth of the burst channel must accommodate all the sidebands up to about the twentieth, corresponding to about 650kHz.

Gating Pulses

The gating pulses are sometimes derived from a separate gate pulse generator stage which is activated by either the line flyback pulses or the line sync pulses. It is important that the burst gate opens only during the periods of the bursts and closes completely during the lines of picture information: if these conditions are not satisfied colour distortion appears on the picture.

The pulse generator and associated circuits of the Decca set are shown in Fig. 5. Tr1 is an amplifier transistor in the luminance channel and Tr2 the pulse generator transistor. The video input at Tr1 base has negative-going picture signal and positive-going sync pulses and signal of the same polarity also appears at the emitter. This is fed via R1 and C1 to Tr2 base. Consequently Tr2 is cut off during the negative-going picture signal but passes current pulses

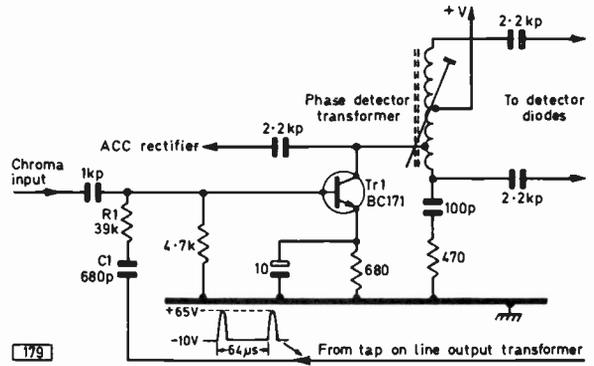


Fig. 6: The burst gate amplifier used in the ITT-KB CVC5 single-standard colour chassis. This is gated by flyback pulses from the line output stage. The collector circuit is rather unusual in comprising a series tuned circuit, the coil driving the discriminator diodes in the normal manner.

when triggered on by the positive-going line sync pulses. These current pulses appear as negative-going pulses at Tr2 collector. Positive-going pulses are required however for the gating action. These are obtained by using the negative-going pulses to make L1 "ring", the positive-going overshoot of each ringing pulse being employed to switch on Tr2 in Fig. 2. This technique ensures that the gate opens only during the bursts—which are on the sync pulse back porch—and not during the line sync pulses themselves. The pulses at Tr2 collector are also used for 405-line a.g.c. gating.

ITT-KB Circuit

The gated burst amplifier circuit used in the single-standard ITT-KB CVC5 series chassis is shown in Fig. 6. The chroma signal input is taken from the chroma amplifier channel (see Fig. 1, page 221, previous issue) and fed to the base of the burst gate/amplifier transistor Tr1. Being an npn type this transistor requires positive-going pulses to switch it on during the periods of the bursts. These pulses are obtained from the line output transformer (flyback pulses as shown in the inset waveform) and a suitable degree of delay is provided by the RC coupling circuit R1/C1 so that the transistor switches on at the times corresponding to the bursts proper. R1 also ensures that the switch-on current is limited to a safe value for the transistor.

Two-stage Circuit

A circuit employing two stages is shown in Fig. 7 (Baird 700 series). Burst gating is accomplished at the input stage Tr1, the action being as follows. During lines of picture signal there are no gating pulses and Tr1 is cut-off, its base being negative with respect to its emitter as its base is at chassis potential (through P1 and R1) while its emitter is taken to a small positive potential at the junction of the potential-divider formed by R2 and R3. The positive potential from the supply line cannot reach Tr1 base via D1 because the cathode of this is connected to supply positive—it is thus reverse biased. During line flyback however a 60V pulse is applied to the anode of D1 through R5 and simultaneously to Tr1

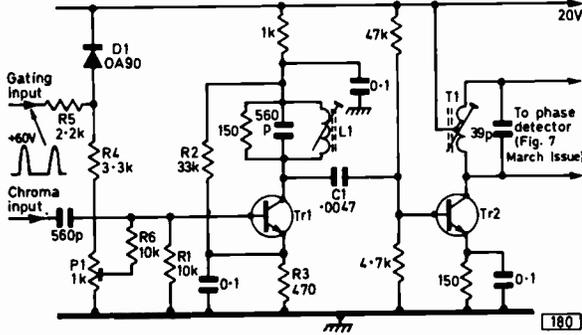


Fig. 7: Two-stage burst channel used in dual-standard Baird colour sets. Line flyback pulses clamped to the 20V l.t. rail by D1 gate the base of Tr1.

base through R4, P1 and R6. This pushes Tr1 hard into conduction while at the same time switching on D1 which effectively clamps Tr1 base to +20V from the supply line. The bursts then develop across L1 in Tr1 collector circuit and are coupled via C1 to Tr2 base. This transistor acts as an amplifier and a loading device to the phase detector input transformer T1. P1 regulates the bias applied to Tr1 base during the periods of the bursts for best gating effect.

Passive Subcarrier Regenerator

Before going on to PAL switching and V-chroma line identification circuits we must conclude the reference generator department by examining the passive type of subcarrier regenerator. This type of circuit differs from the active circuits described last month in that the reference signal is not generated by an active oscillator stage. Instead the reference signal required by the chroma detectors is obtained direct from the bursts.

As we showed in Fig. 4 the bursts consist of a 4.43MHz carrier wave and sidebands or side frequencies spaced either side of the carrier wave at half line frequency and multiples thereof. From this it follows that by feeding the bursts through a very narrow passband filter all the side frequencies will be removed and the original carrier wave only will be obtained. This is in fact just how the passive reference generator system works.

The narrow passband filter consists of a quartz

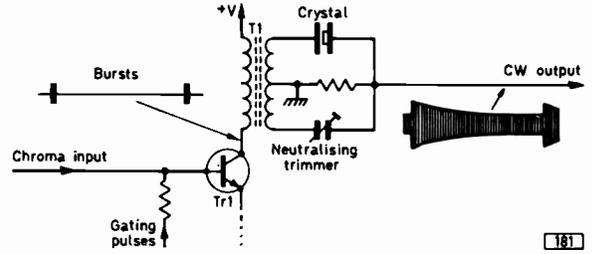


Fig. 8: The basic passive subcarrier regenerator circuit. The crystal acts as a high Q filter which removes the sidebands from the burst subcarrier to provide a 4.43MHz c.w. output.

crystal and the basic scheme of operation is shown in Fig. 8. The bursts at the collector of the gating/amplifier transistor Tr1 are developed across the primary of the filter input transformer T1 the secondary of which is loaded into the crystal proper. The circuit here is akin to a bridge, with the crystal in one arm and a trimming capacitor in the other. It is the purpose of the capacitor to balance out or neutralize the capacitance of the crystal and when this is achieved the circuit acts as a very narrowband filter. The filter circuit neatly removes the side frequencies of the bursts, leaving the 4.43MHz carrier wave (or subcarrier) as shown by the output waveform. The filter in other words effectively "unmodulates" (as distinct from the action of demodulation) the squarewave modulation!

In spite of the effective Q of the circuit being in excess of 10,000 however the selectivity is still not sharp enough to attenuate adequately the half line-frequency components adjacent to the carrier frequency. For this reason PAL receivers employing the passive reference generator scheme incorporate an extra artifice which deletes the burst phase swings so that the crystal filter is presented with "phase constant" bursts having spectral lines corresponding

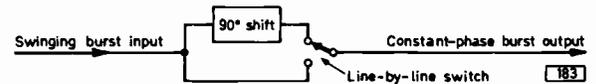


Fig. 10: Diodes D1 and D2 in Fig. 9 in conjunction with the transformer T1 form a 90° phase shift switch to remove the alternate line phase swings from the bursts.

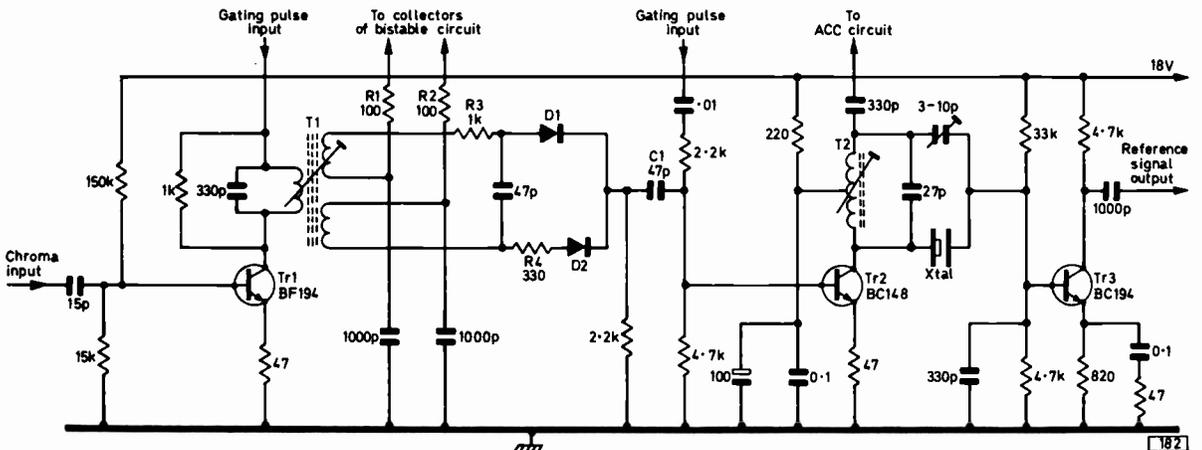


Fig. 9: The burst channel, with passive subcarrier regenerator, used in the RBM single-standard chassis.

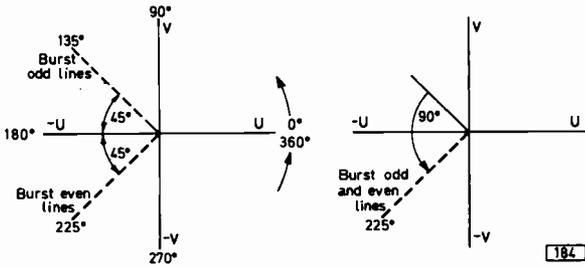


Fig. 11 (left): How the transmitted bursts swing $\pm 45^\circ$ with respect to the $-U$ axis on alternate lines.

Fig. 12 (right): When the 90° switch is correctly synchronised the bursts settle at 225° on all lines. If the switching is out of synchronism the bursts on alternate lines cancel so that there is no reference signal. This feature is used in the RBM chassis for ident purposes as we shall see in a later instalment.

only to the line frequency and its harmonics. The latest crystals well and truly reject these side frequencies—just as they do when used for the same purpose in American NTSC receivers.

Rank-Bush-Murphy Circuit

The single-standard Rank-Bush-Murphy chassis features a passive reference signal generator of this kind as shown in Fig. 9 (later chassis use the integrated version covered in the November 1971 TELEVISION).

The composite chroma signal is fed to the base of Tr1 which is the first gating/amplifier stage. The collector of this stage is fed with clipped positive-going line flyback pulses and as these pulses occur only during the burst periods the transistor is switched on only when the bursts are present.

The burst input swings $\pm 45^\circ$ in phase relative to the $-U$ chroma axis line-by-line in the conventional PAL manner and it is the job of diodes D1, D2 and the associated components to delete these phase swings and thus convert the bursts to a constant phase. What happens is that the diodes in conjunction with transformer T1 shift the phase of the bursts on every other line by 90° as shown in Fig. 10. The switching action occurs as the result of line-by-line alternate conduction of the two diodes, the switching waveform being obtained from the collectors of a pair of transistors in a bistable multivibrator circuit.

On one line for example the potential at R1 is positive and as this is reflected through the top winding of T1 secondary and R3 to D1 anode this diode switches on and the burst at the end of that line is conveyed via C1 to Tr2 base at the phase dictated by the top secondary winding. The other diode is switched off under this condition. On the next line the voltages at the collectors of the multivibrator transistors reverse so that D2 switches on while D1 is switched off. The burst then passes from the bottom secondary winding of T1 via C1 to Tr2 base. The phasing of the transformer windings is such that the burst on one line is shifted 90° in phase relative to the burst on the next line (just as in Fig. 10 in fact). Bearing in mind that the burst phase is also alternating between 135° (odd lines) and 225° (even lines) as shown in Fig. 11 it will be appreciated that the 90° switching just described will counteract the PAL

swings and make the input to Tr2 base phase constant. The operation is shown in Fig. 12 where it will be seen that the 90° phase shift occurs on the odd lines so that the burst phase at Tr2 base settles at a constant 225° .

Tr2 is the second gate/amplifier and the pulses for gating it are obtained from an overshoot ("ring") derived from a tuned and suitably damped circuit which is stimulated by line flyback pulses. This ensures that the gate pulse timing is correct. The arrangement is similar to that employed in the Decca chassis (Fig. 5).

Tr2 collector is loaded by the crystal filter input transformer T2 and the action here is just as explained in relation to Fig. 8. The constant-phase subcarrier is amplified and limited by Tr3 before being processed for application to the chroma detectors.

This chassis also incorporates an interesting method of PAL V-chroma switching identification. We shall be looking at this later. Next month we shall start on PAL V switching and "ident".

COLOUR SERVICING FILM

Zaar Films Ltd. of 339 Clifton Drive South, St. Annes-on-Sea, Lancashire, have released three teaching films on colour television servicing and installation. They are available in 8 or 16mm. form and are in full colour with a magnetic or optical sound track and have been produced with the co-operation of several well-known firms in the TV industry. The three films are Part 1 "The Colour Signal", Part 2 "The Receiver Decoder" and Part 3 "Receiver Installation", and have running times of 30, 20 and 25 minutes respectively.

A CLOSER LOOK AT PAL


—continued from page 257

led us to fear and expect. Theory predicts that hue errors will not arise in the PAL system and practice confirms it. Any errors that do occur are caused primarily by inaccurate adjustment of the display system, particularly by the grey-scale tracking and purity.

In this series we have tried to show why it is that PAL serves us well. We have discussed the reasons why signal phase distortions are largely cancelled; why distorted sideband working fails to produce the ill effects so common with NTSC; and we have demonstrated the high degree of immunity to decoder alignment errors.

Of comparable importance in our search for higher average colour quality in customers' homes is the fact that PAL decoders lend themselves to a variety of simple alignment procedures. These are based on critical visual display techniques and not in any sense upon measurements. PAL decoders also have a built-in facility for instant checking of alignment accuracy—blinds.

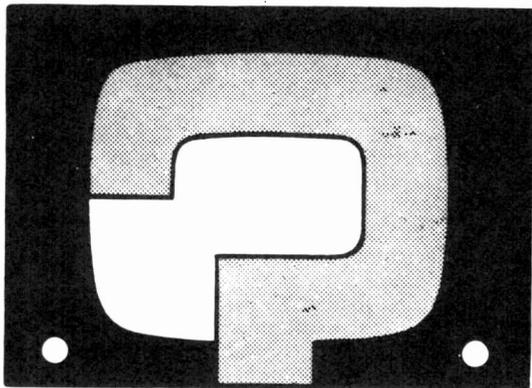With the coming of high-performance integrated circuits and all solid-state receivers we are poised for a major breakthrough in terms of performance, complexity of component assemblies, receiver size, reliability and cost. Who would have thought four years ago that colour TV would travel so far and so fast?



YOUR PROBLEMS SOLVED

★ Requests for advice in dealing with servicing problems must be accompanied by a 10p postal order (made out to IPC Magazines Ltd.), the query coupon from page 282 and a stamped, addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets or answer queries over the telephone.

PHILIPS G6 CHASSIS

The trouble is the blue convergence. On a crosshatch pattern the blue horizontal lines are bowed upwards. Reasonable convergence can be obtained at the centre of the screen but it is very poor at both sides. The blue convergence controls L1614, R1237 and L1605 have no effect on the blue pattern at all.—I. Carter (Rugby).

First check carefully the plugs and sockets from the coils to the convergence panel then check that the system switch is over correctly and making proper contact. If the red and green patterns are not correctly converged, re-converging them may enable the blue pattern to be brought into registration. If the line convergence controls you mention have no effect check the coils and controls for continuity and also C1205, R1240 and C1210 in the horizontal convergence circuit. Also check and adjust the blue field convergence controls R1259 and R1265 as the effect of these in conjunction with the others and the static controls may help. We feel however that the trouble is most likely to be a loose plug or connection.

BUSH TV161

There is loud hum on this set though the picture is not in any way affected. Disconnecting the aerial makes no difference. Also after the set has been on for about two hours the sound becomes very distorted and weak. The PCL82 audio valve has been replaced without improving matters.—H. Aarenson (Erith).

Check the PCL82 valveholder as there may be leakage between pins 3 and 4 (pentode grid and heater). This could also cause the distortion. Apart from this check the PCL82 voltages.

FERGUSON 3624

The trouble is lack of field hold. There are two complete pictures and moving the hold control only makes the picture revolve. The field timebase and video/sync valves have been replaced without any improvement.—J. Pinney (Birkenhead).

Check the value of the 470kΩ resistor R98 in series with the field hold control. Then check C80 (0.01μF) and C79 (0.003μF high-voltage) which couple back to the triode grid of the field timebase valve.

PYE 62

There is reduced width on this three-year-old model. The line output and efficiency diode valves have been changed. The width preset controls are both at the extreme end of their travel.—R. Davies (Swansea).

There are two 3.9MΩ resistors R155 and R156 in the width control circuit. The most likely cause of the trouble is that one or both of these has changed value.

PHILIPS 19TG173

The trouble is that the 625 sound is very poor and distorted although the picture is good. On 405 the picture is very shaky at times and flickers quite a bit. I have tried to clear this fault by adjusting the fine tuner but this makes no difference.—H. Dean (Manchester).

The poor 625 sound could be due to inaccurate tuning of the 625-line sound i.f. coil cores, faulty OA79 detector diodes (in L211 can), a faulty ratio detector balance control R228 or the 4μF electrolytic C219 in this circuit. The shaky picture could be due to excessive contrast, a faulty a.g.c. line clamp diode X206 (BA115) or flywheel line sync valve V401 ECC82.

DEFIANT 9A50

The field hold is rather erratic, the picture sometimes remaining stable for an hour or two but sometimes for no more than five minutes. Sometimes the slip is slow but it usually speeds up and can nearly always be reset with the hold control. Sometimes the picture rolls for a minute or so and then suddenly stops. The trouble occurs on both 405 and 625 lines. Also on 405 lines there is heavy sound-on-vision.—G. Harris (Glencoe).

Check the PCL85 field timebase valve and the resistors associated with the field hold control as one or more may have changed value. Also check the resistors in the video stage where the 18kΩ bias stabilising resistor—made up of 10kΩ and 8.2kΩ in series—may be changing value. To clear the sound-on-vision check the setting of the preset contrast control near the PCL84 and if necessary reset the sound rejector.

PYE CT72

This set gives very good colour pictures but after running for some time it goes black-and-white. This always seems to occur on a camera change. On return to the first camera the picture is perfect again. The fault occurs more with cartoons and such like. Sometimes the colour does not go altogether but is very pale with horizontal bands of colour, green and pink, about $\frac{3}{8}$ in. wide. Always on switching back to another camera the colour is perfect again.—S. Hickson (Cheltenham).

There are two large coils on the decoder panel to the left of the delay line, i.e. to its right as you look in the back. The largest of these is L27, the 7.8kHz ident coil. Unscrew this on a test card until the colours reverse then screw it back one turn. Then adjust the other coil for maximum voltage at TP17 by D22.

FERGUSON 3703

The trouble is loss of line hold and picture break up after the set has been switched on from cold and has been in operation for about 15-30 minutes (field hold is not affected). The picture returns to normal after a period varying between 2 and 20 minutes and generally the trouble does not then recur. Occasionally however the break up and recovery repeat themselves before the picture reaches a stable state for the rest of the time the set is switched on. Varying the tuning has no effect on the broken-up picture.—R. Sanders (Driffield).

The fault you describe is usually due to a dry-joint or other improper connection in the flywheel line sync discriminator, d.c. amplifier or line oscillator stage. Disturbing the components in turn should reveal where the trouble is and the joint that has to be remade.

PHILIPS 19TG172

There is an intermittent fault on this receiver, the picture and sound fading a short time after switching on. A quick flick of the channel change or a thump on the side of the set restores the picture.—J. Heath (Braintree).

The most likely source of the trouble is the plug and socket connection on the lower part of the left-side panel. This terminates a screened lead from the tuner unit. Remove the plug, clean and tighten up. There are two pins plus a locating plug.

HMV 2620

On 405 lines the picture is not very bright and the sound poor though if the tuner is rotated the sound and vision are momentarily good. On 625 lines the picture is good and the sound loud, but after about five minutes both sound and vision begin to fade and then disappear completely leaving nothing but mush on the screen. The switches have been cleaned and the video valve replaced.—D. Read (Northampton).

It seems that R22, the 3.9M Ω resistor from the slider of the 405-line contrast control to the a.g.c. line, has gone high-resistance. It is situated in a convenient position at the rear centre of the chassis. To cure the u.h.f. trouble we suggest you change both u.h.f. tuner valves—the PC86 and PC88.

BUSH TV125

There is no e.h.t. present and the efficiency diode and heater dropper 3R58 are overheating. The line output transformer was replaced after which the set appeared to work normally for about three weeks except that 3R58 was still overheating slightly. The raster has now completely gone. The efficiency diode and e.h.t. rectifier were replaced at the same time as the line output transformer.—H. Boyle (Andover).

The PY88 efficiency diode usually overheats if the boost capacitors 3C23 or 3C24 short so these should be checked. Then check if necessary for corrosion at the e.h.t. rectifier base.

PYE 11

Choke L23 in the h.t. line is burnt out: could you let me know the value? Also I have fitted a u.h.f. tuner and it is working well but I would like to know how to tune out noise on the u.h.f. sound.—L. Graig (Sidmouth).

L23 is an ordinary i.f. choke of value about 30 μ H. We don't think it is very critical so you may find that if the core is intact you can rewind it—using 40 s.w.g. enamelled wire. To tune up the u.h.f. sound adjust L28, the 6MHz oscillator coil beside the EH90.

MURPHY V530

Adjusting the line hold control results at best in two pictures side by side. There is insufficient width and pincushion distortion some of the time. The sound quality is also only fair.—G. Burnhill (Peterborough).

A common cause of your troubles is low h.t. due to a worn mains rectifier. Change this. Then check the 30P4 line output valve as this may be low emission. Also check the value of the 150pF coupling capacitor from pin 6 to pin 2 of the 6/30L2 line oscillator valve.

McMICHAEL MT762

After adding a u.h.f. tuner this set gave perfect performance on both systems. However although the sound has remained OK the picture gradually deteriorated until it is now rather faint with poor definition. The vision strip valves and voltages are all OK. The fault is common to both systems.—P. Larkin (Maidstone).

We are inclined to suspect the tube first anode supply (pin 3 of the tube base). This supply is derived from the boost line via a 390k Ω resistor which is decoupled to the h.t. line by an 0.1 μ F capacitor. If the voltage at pin 3 is little higher than the 200V h.t. rail change this capacitor.

PHILIPS 19TG170A

The width is inadequate and the sound distorted although the height is sufficient. When the brilliance is reduced the width increases.—G. Cox (Leamington).

The width trouble is normally due to the two 8.2M Ω resistors above the preset width controls (lower right) on this model changing value. Apart from this the PL500 (PL504) line output valve may be loosing emission. The distorted sound is probably due to the PCL82 audio valve being faulty, but you should also check its 470 Ω cathode bias resistor and the 2.7M Ω resistor (R234) connected to pin 9 (triode anode).

HMV 1893

There is lack of field hold and reduced height. The picture becomes steady after the set has been on for a few minutes but the line hold is then very critical. The field timebase and video/sync valves have been replaced.—**J. Burns (Deal)**.

The reduced height and field roll are due to the 22k Ω load resistor R113 of the ECC82 section of the field multivibrator stage changing value. The poor sync is most likely to be due to a fault in the video stage and we suggest you check the value of the bias stabilising resistor R55 (47k Ω) and the bias electrolytic C54 (50 μ F).

BUSH TV125

On 405 the picture displays considerable overshoot with definite deterioration of the bandwidth. On advancing the contrast control the trouble is aggravated while parts of the picture tend to pull to the right. The picture on 625 is OK in every respect. No amount of careful tuning helps. The video amplifier and its anode load resistor and the tuner unit valves have been replaced.—**G. Duneven (Porchester)**.

This chassis uses separate vision detector diodes for the two systems. On 405 the detector is 2MR1, with 2MR4 as noise limiter. You will have to check all the components associated with these diodes—the diodes themselves, the small capacitors and resistors and the coil connections.

TEST CASE**112**

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

? A portable receiver fitted with the Thorn 950 chassis was brought in by the field technician with the complaint that after about thirty minutes operation the bottom of the picture would start to creep up, ultimately leaving a gap of about a couple of inches at the bottom of the screen. The technician had tried a replacement field output pentode at the customer's home, but to no avail. He had also removed the field circuit subchassis and visually investigated the components, being aware that a scorched resistor with changed colours often signified an open-circuit or changed value, but in this case there was nothing to indicate the whereabouts of the fault.

In the workshop the valve and its cathode resistor were checked first of all but both were clear of trouble. It was noticed though that as the bottom

DECCA DR123

The sound and picture are OK except that there is pulling from side to side on the picture, vertical lines being wavy and bent. The video and vision i.f. valves have been changed.—**R. Thomson (Tring)**.

Line synchronisation on this as in most Decca sets is controlled by an ECL80 phase comparator valve, V15 on this model. Change it.

INVICTA 7193

The picture suddenly faded away as though the set had been switched off although the sound remained perfect. The line output stage valves have been replaced but there is still no e.h.t.—**C. Speer (Crewe)**.

Check the right-side PCL84, the triode section of which is the line oscillator, and the 0.01 μ F coupler C87 from this to the line output valve. Check the boost capacitor C97 (0.1 μ F). The line output transformer could unfortunately be suspect.

QUERIES COUPON

This coupon is available until April 17, 1972, and must accompany all Queries sent in accordance with the notice on page 280. Don't forget the 10p postal order!

TELEVISION APRIL 1972

contraction increased a degree of correction was possible by operating the height control, the control eventually being at maximum setting.

At this point the technician switched off, removed a field timebase component and found that the height was excessive when next switching on. Readjustment corrected this and protracted running indicated that the fault condition no longer existed. The technician then fitted a new component in place of that previously removed, once more readjusted the height and finally made sure that the set worked normally for several hours before conveying it to the delivery bay. What was the most likely cause of the trouble and the component responsible? See next month's TELEVISION for the solution and for a further item in the Test Case series.

SOLUTION TO TEST CASE 111*Page 235 (last month)*

The resistor was a 1.2M Ω one in series with the height control and had increased in value. Older sets are very susceptible to change in potential at the field oscillator anode, the effect being first a reduction in height and then non-linearity.

The Ekco T433 series chassis employs a high-level contrast control in the video amplifier output circuit. Thus overloading (leading to crushing on whites) as a result of high input drive cannot be corrected by this control. A preset contrast control is however provided to take care of this situation and was the control adjusted by the technician.

The largest selection

BRAND NEW FULLY GUARANTEED DEVICES

AC107 15p	AF115 17p	BC140 35p	BCY31 22p	BF272 80p	EC403 15p	ORP60 40p	2N918 30p	2N2714 25p	2N3704 15p
AC113 20p	AF116 17p	BC141 35p	BCY32 22p	BF273 30p	CE780 27p	ORP61 40p	2N929 22p	2N2904 25p	2N3705 12p
AC115 23p	AF117 17p	BC142 45p	BCY33 17p	BF274 30p	MAT100 15p	ST140 12p	2N930 25p	2N2904A 30p	2N3706 12p
AC119 17p	AF118 30p	BC143 30p	BCY34 17p	BF275 30p	MAT101 17p	ST141 47p	2N1131 25p	2N2905 25p	2N3707 13p
AC126 17p	AF124 21p	BC145 45p	BCY70 15p	BF309 37p	MAT120 15p	TIS43 40p	2N1132 25p	2N2905A 30p	2N3708 8p
AC127 17p	AF125 20p	BC147 17p	BCY71 30p	BF316 75p	MAT121 17p	UT46 27p	2N1302 17p	2N2906 25p	2N3709 8p
AC128 17p	AF126 20p	BC148 12p	BCY72 15p	BF316 75p	MF102 43p	V405A 25p	2N1303 17p	2N2906A 27p	2N3710 10p
AC141K 17p	AF127 20p	BC149 17p	BCZ11 20p	BFX29 27p	MPF105 43p	V410A 45p	2N1304 20p	2N2907 25p	2N3711 10p
AC142K 17p	AF139 33p	BC150 17p	BD121 85p	BFX84 20p	OC19 30p	2G301 19p	2N1305 20p	2N2907A 30p	2N3819 40p
AC151 15p	AF178 50p	BC151 20p	BD123 85p	BFX85 27p	OC20 50p	2G302 19p	2N1306 22p	2N2923 13p	2N3820 41
AC154 15p	AF179 50p	BC152 17p	BD124 75p	BFX86 22p	OC22 30p	2G303 19p	2N1307 22p	2N2924 13p	2N3903 25p
AC155 17p	AF180 50p	BC153 27p	BD131 80p	BFX87 25p	OC23 33p	2G304 20p	2N1308 27p	2N2925 17p	2N3904 27p
AC156 17p	AF191 50p	BC154 30p	BD132 80p	BFX88 22p	OC24 25p	2G306 35p	2N1309 27p	2N2926 12p	2N3905 25p
AC157 17p	AF186 45p	BC157 20p	BDY20 41	BFY50 20p	OC25 25p	2G308 35p	2N1613 17p	(G)	2N3906 27p
AC165 17p	AF239 37p	BC158 17p	BF115 22p	BFY51 20p	OC26 25p	2G309 35p	2N1711 20p	2N2926	2N4058 15p
AC166 17p	AFZ11 37p	BC159 20p	BF117 45p	BFY52 20p	OC28 40p	2G339 17p	2N1889 35p	(Y)	2N4059 10p
AC167 20p	AFZ12 45p	BC167 13p	BF118 60p	BFY53 17p	OC29 40p	2G339A 15p	2N1890 35p	2N2926	2N4060 12p
AC168 20p	AL102 85p	BC168 13p	BF119 70p	BKX19 15p	OC35 33p	2G344 15p	2N1893 37p	(O)	2N4061 12p
AC169 14p	AL103 85p	BC169 13p	BF152 35p	BKX20 15p	OC36 40p	2G345 15p	2N2160 60p	2N3010 80p	2N4062 12p
AC176 23p	ASV26 23p	BC170 12p	BF153 35p	BSY25 15p	OC41 20p	2G371 15p	2N2147 75p	2N3011 20p	2N5172 41
AC177 20p	ASV27 30p	BC171 13p	BF154 35p	BSY26 15p	OC42 22p	2G371B 10p	2N2148 60p	2N3053 20p	2N5459 43p
AC187 30p	ASV28 25p	BC172 13p	BF157 45p	BSY27 15p	OC44 15p	2G374 17p	2N2192 30p	2N3054 50p	25034 75p
AC188 30p	ASV29 25p	BC173 13p	BF158 25p	BSY28 15p	OC45 15p	2G377 27p	2N2193 30p	2N3055 63p	25031 50p
AC189 14p	AL103 85p	BC174 13p	BF159 30p	BSY29 15p	OC70 12p	2G378 15p	2N2194 27p	2N3391 17p	2502A 45p
AC198 20p	ASV51 25p	BC175 22p	BF160 35p	BSY38 17p	OC71 12p	2G379 15p	2N2195 27p	2N3391A 19p	25024 41
AC199 22p	ASV52 25p	BC177 17p	BF162 30p	BSY39 15p	OC72 12p	2G401 30p	2N2218 25p	2N3392 17p	25033 60p
ACY20 20p	ASV54 25p	BC178 17p	BF163 35p	BSY40 30p	OC74 12p	2G414 30p	2N2219 27p	2N3393 15p	25034 41
ACY21 20p	ASV55 25p	BC179 17p	BF164 35p	BSY41 35p	OC75 15p	2G417 25p	2N2220 22p	2N3394 15p	25035 41
ACY26 19p	ASV56 25p	BC180 20p	BF165 35p	BSY95 12p	OC76 15p	2N388 30p	2N2221 22p	2N3395 20p	25036 41
ACY27 18p	ASV57 25p	BC181 20p	BF167 25p	BSY95A 12p	OC77 15p	2N388A 30p	2N2222 27p	2N3402 23p	25037 41
ACY28 19p	ASV58 25p	BC182 10p	BF173 22p	BU105 43	OC81 15p	2N404 22p	2N2368 17p	2N3403 22p	25038 60p
ACY29 30p	ASV58 25p	BC182L 10p	BF176 35p	CI11E 60p	OC81D 15p	2N404A 30p	2N2369 15p	2N3404 32p	25039 60p
ACY30 25p	ASZ21 40p	BC183 10p	BF177 35p	C400 30p	OC82 15p	2N524 55p	2N2369A 15p	2N3405 45p	25040 45p
ACY31 25p	ASZ17 10p	BC184 13p	BF178 45p	C407 25p	OC82D 15p	2N527 60p	2N2411 50p	2N3414 20p	25041 45p
ACY34 18p	BC108 10p	BC184 13p	BF179 35p	C424 35p	OC83 25p	2N596 50p	2N2412 50p	2N3415 20p	25042 41
ACY35 18p	BC109 11p	BC184L 13p	BF180 30p	C425 40p	OC84 20p	2N697 15p	2N2616 55p	2N3417 37p	25043 41
ACY36 30p	BC113 25p	BC186 27p	BF181 30p	C426 30p	OC139 15p	2N698 24p	2N2711 22p	2N3525 74p	25044 41
ACY40 15p	BC114 30p	BC187 27p	BF182 30p	C428 20p	OC140 17p	2N699 55p	2N2712 22p	2N3702 12p	25045 41
ACY41 18p	BC115 30p	BC188 11p	BF183 30p	C441 27p	OC170 15p	2N706 50p	2N2714 25p	2N3703 12p	
ACY44 35p	BC116 35p	BC209 11p	BF184 30p	C442 35p	OC171 15p	2N706A 8p			
AD140 40p	BC117 35p	BC209 11p	BF185 30p	C444 37p	OC200 25p	2N708 12p			
AD142 40p	BC118 25p	BC212L 11p	BF188 30p	C450 17p	OC201 27p	IN709 45p	AA119 8p	BY130 15p	OA10 22p
AD149 43p	BC119 45p	BC213L 11p	BF194 32p	C720 12p	OC202 27p	2N711 40p	AA120 8p	BY120 35p	OA47 7p
AD161 42p	BC125 35p	BC214 11p	BF195 24p	C721 25p	OC203 27p	2N717 42p	EA116 22p	BY121 32p	OA70 7p
AD162 35p	BC126 35p	BC214L 12p	BF196 30p	C740 15p	OC204 25p	2N718 24p	BA126 25p	BY122 30p	OA79 7p
AD161/162(MP) 63p	BC132 25p	BC225 25p	BF197 35p	C742 17p	OC205 35p	2N718A 50p	BY100 15p	BY123 25p	OA81 7p
ADT140 50p	BC134 30p	BC226 35p	BF200 45p	C744 17p	OC309 35p	2N726 27p	BY101 12p	BY126 35p	OA85 7p
ADZ11 42p	BC135 30p	BC317 12p	BF222 80p	C760 17p	P146A 17p	2N727 27p	BY105 15p	BY127 35p	OA90 7p
ADZ12 42-10p	BC137 35p	BC318 12p	BF257 35p	C762 37p	P157 45p	2N743 17p	BY106 15p	BY128 30p	OA91 6p
AF114 17p	BC139 45p	BCY30 20p	BF270 35p	C766 60p	OP71 45p	2N744 17p	BY126 17p	BY129 25p	OA95 7p
			BF271 17p	EC401 15p	ORP12 43p	2N914 17p	BY127 17p	OA5 17p	OA200 6p

DIODES & RECTIFIERS

AA119 8p	BY130 15p	OA10 22p
AA120 8p	BY120 35p	OA47 7p
EA116 22p	BY121 32p	OA70 7p
BA126 25p	BY122 30p	OA79 7p
BY100 15p	BY123 25p	OA81 7p
BY101 12p	BY126 35p	OA85 7p
BY105 15p	BY127 35p	OA90 7p
BY106 15p	BY128 30p	OA91 6p
BY126 17p	BY129 25p	OA95 7p
BY127 17p	OA5 17p	OA200 6p

74 Series T.T.L. I.C.-s

DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed



BI-PAK Order No.	Price and qty. prices 1-24 25-99 100 up	BI-PAK Order No.	Price and qty. prices 1-24 25-99 100 up
2p	1p	2p	1p
BP00-SN7400	0-15 14 0-12	BP51-SN7451	0-15 14 0-12
BP01-SN7401	0-15 14 0-12	BP52-SN7452	0-15 14 0-12
BP02-SN7402	0-15 14 0-12	BP53-SN7453	0-15 14 0-12
BP03-SN7403	0-15 14 0-12	BP60-SN7460	0-15 14 0-12
BP04-SN7404	0-15 14 0-12	BP70-SN7470	0-29 26 0-24
BP05-SN7405	0-15 14 0-12	BP72-SN7472	0-29 26 0-24
BP07-SN7407	0-18 17 0-16	BP73-SN7473	0-37 35 0-32
BP08-SN7408	0-18 17 0-16	BP74-SN7474	0-37 35 0-32
BP09-SN7409	0-18 17 0-16	BP75-SN7475	0-47 45 0-42
BP10-SN7410	0-15 14 0-12	BP76-SN7476	0-43 40 0-38
BP13-SN7413	0-29 28 0-24	BP78-SN7478	0-67 64 0-58
BP16-SN7416	0-43 40 0-38	BP81-SN7481	0-97 94 0-88
BP17-SN7417	0-43 40 0-38	BP82-SN7482	0-97 94 0-88
BP20-SN7420	0-15 14 0-12	BP83-SN7483	1-10 10 0-95
BP23-SN7423	0-15 14 0-12	BP86-SN7486	0-32 30 0-28
BP40-SN7440	0-15 14 0-12	BP90-SN7490	0-67 64 0-58
BP41-SN7441	0-67 64 0-58	BP91-SN7491A	0-67 64 0-58
BP42-SN7442	0-67 64 0-58	BP92-SN7492	0-67 64 0-58
BP43-SN7443	1-95 185 1-75	BP93-SN7493	0-67 64 0-58
BP44-SN7444	1-95 185 1-75	BP94-SN7494	0-77 74 0-68
BP45-SN7445	1-95 185 1-75	BP95-SN7495	0-77 74 0-68
BP46-SN7446	0-97 94 0-88	BP96-SN7496	0-77 74 0-68
BP47-SN7447	0-97 94 0-88	BP98-SN7498	1-75 155 1-55
BP48-SN7448	0-97 94 0-88	BP104-SN74104	0-97 94 0-88
BP30-SN7450	0-15 14 0-12	BP105-SN74105	0-97 94 0-88

BP107-SN74107	0-40 0-38 0-36	BP161-SN74161	1-80 1-70 1-60
BP110-SN74110	0-53 0-53 0-50	BP164-SN74164	2-00 1-90 1-80
BP111-SN74111	1-25 1-15 1-00	BP165-SN74165	2-00 1-90 1-80
BP112-SN74112	1-25 1-15 1-00	BP181-SN74181	2-75 2-60 2-40
BP119-SN74119	1-35 1-25 1-10	BP182-SN74182	0-97 0-94 0-88
BP121-SN74121	0-87 0-84 0-58	BP188-SN74188	3-50 3-25 3-00
BP141-SN74141	0-67 0-64 0-58	BP190-SN74190	3-50 3-25 3-00
BP145-SN74145	1-50 1-40 1-30	BP191-SN74191	3-50 3-25 3-00
BP150-SN74150	1-80 1-70 1-60	BP192-SN74192	2-10 1-95 1-75
BP151-SN74151	1-00 0-95 0-90	BP193-SN74193	2-10 1-95 1-75
BP153-SN74153	1-20 1-10 0-95	BP195-SN74195	1-10 1-05 0-95
BP154-SN74154	1-80 1-70 1-60	BP196-SN74196	1-80 1-70 1-60
BP155-SN74155	1-40 1-30 1-20	BP197-SN74197	1-80 1-70 1-60
BP158-SN74158	1-00 0-95 0-90	BP198-SN74198	5-00 5-00 4-00
BP160-SN74160	1-80 1-70 1-60	BP199-SN74199	5-00 5-00 4-00

PRICE-MIX. Devices may be mixed to qualify for quantity prices. PRICES for quantities in excess of 500 pieces mixed, on application. Owing to the ever increasing range of TTL 74 Series, please check with us for supplies of any devices not listed above, as it is probably now in stock. WARE 3442

★ STOP PRESS ★ NOW OPEN! BI-PAK'S NEW COMPONENT SHOP

A wide range of all types of electronic components and equipment available at competitive prices.

18 Baldock St. (A10), Ware, Herts. Tel.: 61593
OPEN 9.15-6 Tues. to Sats. FRIDAYS UNTIL 8 p.m.

ANOTHER BI-PAK FIRST!

THE NEW S.G.S. EA 1000 AUDIO AMPLIFIER MODULE

* Guaranteed not less than 3 Watts RMS.

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio response provides unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

TELEVISION CLASSIFIED ADVERTISEMENTS

The pre-paid rate for classified advertisements is 5p a word (minimum 12 words), box number 10p extra. Semi-display setting £3 per single column inch. All cheques, postal orders, etc., to be made payable to TELEVISION and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, TELEVISION IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD, for insertion in the next available issue.

EDUCATIONAL



COLOUR TELEVISION TRAINING

11 WEEKS' COURSE for men with Mono experience. Shorter appreciation courses by arrangement. Hours 10 a.m. to 1 p.m. Monday to Friday. Next course commences May 1st. Prospectus from: London Electronics College, Dept. C/4, 20 Penywern Road, London, SW5 9SU. Tel. 01-373 8721.

FULL-TIME COURSES in ELECTRONICS and TELEVISION. These are nine-month courses, starting next September, which lead to City & Guilds certificates. Extensive laboratory work is included, and there are, in most cases, no fees for those under 18 at enrolment. Full details from: Section 434, Electrical and Electronic Engineering Department, Southall College of Technology, Beaconsfield Road, Southall, Middlesex.

TRAIN FOR SUCCESS WITH ICS

Study at home for a progressive post in Radio, TV and Electronics. Expert tuition for City & Guilds (Telecoms Techn's Cert. and Radio Amateurs') R.T.E.B., etc. Many non-exam courses incl. Colour TV Servicing, Numerical control & Computers. Also self-build kit courses—valve and transistor.

Write for **FREE prospectus** and find out how ICS can help you in your career.

ICS, DEPT. 560, INTERTEXT HOUSE, STEWARTS ROAD, LONDON SW8 4UJ.

BECOME "technically qualified" in your spare time. Home study courses in Radio, TV, Servicing and Maintenance, RTEB, City & Guilds, etc. Informative **FREE** guide—Chambers College (Dept. R.105), Aldermaston Court, Reading RG7 4PF.

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Building, etc. **FREE** book from: BIET (Dept. H.6), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

WANTED

CASH PAID for New Valves. Payment by return. **WILLOW VALE ELECTRONICS**, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

SERVICE SHEETS purchased. **HAMILTON RADIO**, 54 London Road, Bexhill.

WANTED (continued)

TOP PRICES PAID for new valves, popular TV & Radio Types
KENSINGTON SUPPLIES
(A), 367 Kensington Street
Bradford 8, Yorks

WANTED! New valves especially TV types. Cash waiting. Bearman, 6 Potters Road, New Barnet, Herts., Tel. 449 1934.

AERIALS

BAINES for HIGH FREQUENCY AERIALS

Postage paid on all aerials inland
MULTIBEAMS UHF
MBM 10 £1-90, MBM 18 £2-65, MBM 30 £3-60, MBM 38 £5-10, MBM 46 £5-50, 2MBM 46 £12-50, 4MBM 46 £28-50.
VHF AERIALS
BBC Dipole £1-75, H £2-50, BBC ITA Dipole and 5 £2-70, ITA 5 Element £2-00, ITA 8 Element £2-70, FM H £2-00.
ACCESSORIES: SAE for full List.
Pre-amps: Masthead mains £6-00, Colourbooster £3-88, Co-Ax. 5p and 9p, UHF Diplexers 65p.
Please state channels on all orders.
R. BAINES, 11 Dale Cres., Tupton, Chesterfield.

AERIALS (continued)

Direct from the Manufacturers
U.N.E. AERIALS
EASY ASSEMBLY KITS
10 Element **SAVE 40%**
£1.25 (on normal retail price)
14 Element **£1.50** 18 Element **£1.75**
Ready assembled add 20p. allow 32½p. carriage and packing. Please state which channels or group.
TRADE SUPPLIED, SEND FOR LIST
APEX AERIALS (T.V.)
ALBAN WORKS, MARY ST., JOHNSTONE, RENFREWSHIRE

UHF 8c £1-90, 14e £2-35, 18e £3-25, 22e £3-75. BBC1 I £1-75, H £2-40, X £2-15, 3e £5-20, 4e £6-90. ITA 5c £1-95, 8e £2-70, 11e £3-30, 13c £4-05. BBC/ITA 1+5 £2-70, 1+8 £3-10, H+5 £4-10, H+7 £4-50. Loft 1+5 with pole, swivel and clamps £2-10. Coax plugs 8p. FM dipole £1-13, 2c £2-00, 3c £3-75, 4c £5-00. Lashing kits, 6" £0-90, 12" £1-15, double £1-65. Diplexers 50p. Triplexers 80p. UHF/VHF diplexers £1-10 pair. Masts 2", 10' £2-20, 16' £3-30, 20' £4-40, 1" 5' 60p, 6' 72p. UHF preamps, battery, £3-75, mains £5-87. Coax, 6p and 10p a yd. Aerials p. paid, clamps provided. Access. Carriage depends on weight.

BAKER, BONTNEWYDD, CARDS., SY23 4JH

SERVICE SHEETS

QUICK, EFFICIENT, SERVICE SHEET SERVICE

Stocks now cover over 10,000 Makes and Models. TV's Mono and Colour, Amplifiers, Tapes, Record Players, Test Gear, etc.

SERVICE SHEETS 25p plus large S.A.E.

MANUALS covering many Makes and Models. Enquiries welcome but S.A.E. please

CATALOGUE covering TV's, Mono and Colour, including Fault Finding Chart and Vouchers. Value 20p.

Price 20p plus S.A.E.—Radio, etc. catalogue also 20p.

— MAIL ORDER ONLY —

A.L.S. 21c Drydon Chambers, 119 Oxford Street, London W1R 1PB

SERVICE SHEETS (continued)

★ SERVICE SHEETS • MANUALS • BOOKS ★

ON RADIOS, TELEVISIONS, AMPLIFIERS, SERVICING DATA AND FAULT FINDING ETC.
SERVICE SHEETS 40p EACH. 1972 SERVICE SHEET CATALOGUE 20p. SEND S.A.E. WITH ENQUIRIES.

NEW BOOKS & PUBLICATIONS	PRICE + P.&P.
COLOUR TELEVISION SERVICING by G.J. King, 332 pages	£4.40 30p
COLOUR TELEVISION PICTURE FAULTS by K.J. Bohman, illustrated in colour	£4.50 20p
MAZDA BOOK OF PAL RECEIVER SERVICING by D.J. Seal, FS.ERT.MRTS. 288 pages	£3.50 30p
TELEVISION SERVICING HANDBOOK by G.J. King, 358 pages	£3.80 30p
T.V. FAULT FINDING BOOK by Data Publications Ltd. 405/625 Edition. 124 pages	£0.50 10p
PAL COLOUR TV by Mullard Ltd. How Colour Works. 100 pages	£0.65 10p
HOW TO RECEIVE FOREIGN TV PROGRAMMES ON YOUR SET by W.J. West	£0.33 7p
PRINCIPLES OF PAL COLOUR TELEVISION by H.V. Sims, C.Eng.M.I.E.E. F.I.E.R.E. 154 pages	£2.00 20p
UNDERSTANDING TELEVISION by J.R. Dawes, 512 pages	£2.10 15p
PRACTICAL TELEVISION CIRCUITS by R.F. Street, 376 pages	£1.40 15p
TELEVISION ENGINEER'S POCKET BOOK by J.P. Hawker, 304 pages	£1.75 15p
COLOUR RECEIVER TECHNIQUES by T.D. Powers, MBE.M.A.B.Sc.M.I.E.E. AMI.E.R.E. 96 pages	£1.75 15p

Send S.A.E. for 'FREE' List of Practical and Technical Books on Radio & Television now available to:-

BELL'S TELEVISION SERVICES
Albert Place, Harrogate, Yorkshire. Telephone 0423-86844

LARGE SUPPLIER of SERVICE SHEETS

(TV, RADIO, TAPE RECORDERS,
RECORD PLAYERS, TRANSISTORS,
STEREOGRAMS, RADIOGRAMS,
CAR RADIOS)

Only 40p each.

PLEASE ENCLOSE LARGE S.A.E. WITH
ALL ENQUIRIES AND ORDERS.

Otherwise cannot be attended to.

(Uncrossed P.O.'s please, original
returned if service sheets not available)

C. CARANNA

71 BEAUFORT PARK,
LONDON, N.W.11

We have the largest supplies of Service
Sheets (strictly by return of post).
Please state make and model number
alternative.

Free TV fault tracing chart or TV list on
request with order.
MAIL ORDER ONLY.

SERVICE SHEETS

(1925-1971) for Radios, Televisions,
Transistors, Radiograms, Car Radios,
Tape Recorders, Record Players, etc.

By return post with

FREE FAULT FINDING GUIDE

PRICES FROM 5p

Over 8,000 models available.
Catalogue 13p.

Please send stamped addressed envelope
with all orders and enquiries.

Hamilton Radio

54 London Road, Bexhill, Sussex
Telephone Bexhill 7097

RADIO, TELEVISION and Tape Re-
corders, 50 mixed odd sheets, 50p, also
large stock of obsolete and current
valves. John Gilbert Television, 1b Shep-
herds Bush Road, London, W.6. 01-743
8441. S.a.e. enquiries.

SERVICE SHEETS. Radio, TV, etc.
8,000 models. List 10p. S.A.E. enquiries.
TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS with Free Fault
Finding Chart 35p, plus stamped
addressed envelope, LESMAR, 15
Conholt Road, Andover, Hants.

FOR SALE

VALVES EX. TV from 5p, 3p postage,
speakers from 37½p, postage 10p. Valve
cartons. Globe Electronics, 151a Brighton
Road, Surbiton, Surrey. 01-399 7333.

NEW. MAZDA GOLD SEAL. C.M.E.
1901. Tube, with guarantee card, £5.
Collect. 32 Hensford Gardens, Syden-
ham, S.E.26.

RADAR C R TUBE & Tester and
U.S.A. Dumont Scope, £25 the two.
Stark & Son, 43 Thicketford Road,
Bolton, Lancs.

25" COLOUR TELEVISION for sale.
Home constructed; requires IF strip. £95.
Box 92.

MISCELLANEOUS

RECORD TV sound using our loud-
speaker isolating transformer. Provides
safe connection to recorder. Instruc-
tions included. £1 post free. Crowborough
Electronics (T), Eridge Road, Crow-
borough, Sussex.

FLICKDIM SWITCH. Dim up to 500
watts at a flick. A must for TV, chil-
dren's bedrooms, etc. White unit easily re-
places lighting switch. Only 70p, with
money back guarantee. 5p postage. E.
Griffiths, 6 Stanway Close, Alkington,
Middleton, Manchester.



LADDERS

LADDERS. 24ft., £9-80, carr. 80p.
order C.O.D. Phone 02-993 5222. (Dept.
PTT) Home Sales, Baldwin Road, Stour-
port, Worcs. Callers welcome. Ansafone
installed.

SETS & COMPONENTS

TV SCOOP PURCHASE!

★ FREE CIRCUIT DIAGRAM WITH EVERY SET

3 Channel BBC2 TVs 19" Slimline
(110° Tube). Despatched tested and
in working order. £20.

Only while present stocks last.
Complete, untested TV sets.

3 Channel—only require UHF
tuner for BBC2. 19" Slimline
(110° Tube) £8

2 Channel (with 405/625 timebase)
19" (110° Tube) £6

2 Channel 405 only, 17" (110°
Tube) £3

(Carriage & Packing, £1-50 extra,
all models.) Despatched at pur-
chasers' risk. Special discounts for
quantity. (S.A.E. for quote) TWO
sets of the same model supplied
if requested. (Deduct £1 from total
price!!). Ideal 2 into 1 plus lots of
spares for future use—you can't
go wrong at these prices!

TRANSISTOR RADIO SCOOP!

Superhet with push-pull output
to internal loudspeaker. Complete
with carrying case, earphone and
PP3 battery. These sets are BRAND
NEW and complete, but may
require slight attention. Hence
bargain price of £1-50, plus 20p P. & P.

SUMIKS, 7 High St., Langley,
Warley, Worcs.

CALLERS WELCOME.

BEAT THIS FOR VALUE!!

New. Marked and Guaranteed.
BC107. 8p; 25/up. 7p; BC109. 9p;
25/up. 8p; 2N1303. 10p; 25/up.
8p; OC74/AC128 10p; 25/up. 8p;
ASY32. 10p; 25/up. 8p. Cash with
order. Post and package 10p.
Many others at low prices—send
Wants.

R. I. RICHARDSON, Dept. T.,
50 Hayes Street, Bromley,
BR2 7LD.

WITWORTH Transformers

LINE OUT-PUT TRANSFORMERS

Manufacturers of the largest range
in the country. All makes supplied.
Free catalogue.
Modern

BAIRD, BUSH, GEC, PHILIPS.

Replacement types ex-stock.

For 'By-return' service, contact your
nearest Depot:

London: 01-948 3702

Tidman Mail Order Ltd., Dept. PT.
236 Sandycroft Road, Richmond,
Surrey, TW9 2EQ.

Birmingham: 021-643 2148

Hamond Components,
89 Meriden Street,
Birmingham 5.

Valves, Tubes, Condensers, Resis-
tors. Rectifiers and Frame out-put
Transformers also stocked.

CALLERS WELCOME

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1
THE VALVE SPECIALISTS Telephone 01-722-9090

0A2	0-30	6AT6	0-18	6F28	0-60	7Y7	0-25	20P3	0-79	90AV	3-38	DH63	0-27
0B2	0-30	6AV6	0-20	6F32	0-15	7Y4	0-60	20P4	0-89	90CG	1-70	DH76	0-28
0Z4	0-25	6AV6	0-28	6G18A	0-60	7Z4	0-50	20P5	1-00	90CV	1-58	DH77	0-18
1A5	0-25	6AX4	0-54	6GK5	0-60	8B9W6	0-50	26A9G	0-28	90C1	0-89	DH81	0-58
1A7GT	0-38	6B8G	0-13	6H6GT	0-15	10C2	0-49	25Y3	0-38	301	1-00	DK32	0-33
1B3GT	0-38	6BA6	0-20	6J3G	0-19	10D7	0-50	25Y3G	0-43	302	0-83	DK40	0-55
1D5	0-38	6BC8	0-50	6J5GT	0-29	10F1	0-75	25Z4G	0-28	303	0-75	DK91	0-26
1D6	0-48	6BE6	0-21	6J6	0-18	10F9	0-45	25Z5	0-50	305	0-83	DK92	0-35
1PD1	0-33	6B9G	0-105	6J7G	0-24	10F18	0-35	25Z6GT	0-43	306	0-85	DK96	0-35
1G6	0-30	6BH6	0-43	6J7GT	0-38	10LD11	0-53	30A5	0-44	807	0-59	DL33	0-35
1HG7	0-38	6B36	0-38	6J8A	0-50	10P15	0-54	30C1	0-28	1821	0-53	DL92	0-25
1L4	0-13	6BK7A	0-50	6K7G	0-10	10P14	1-08	30C15	0-80	5702	0-80	DL94	0-32
1LD5	0-30	6BQ7A	0-22	6K7GT	0-23	12A6	0-63	30C17	0-77	5763	0-50	DL96	0-35
1LN5	0-40	6BQ7A	0-38	6K8G	0-12	12AC6	0-40	30C18	0-60	6060	0-30	DM70	0-30
1NSGT	0-37	6BR7	0-79	6L1	0-98	12AD6	0-40	30P5	0-65	7193	0-53	DM71	0-38
1R5	0-28	6BR8	0-63	6L6GT	0-39	12AE6	0-48	30P11	0-60	7475	0-70	DW4/500	
184	0-22	6BS7	1-25	6L7	0-38	12A76	0-23	30P12	0-80	A1834	1-00		0-38
185	0-20	6B9W6	0-72	6L8	0-44	12A77	0-16	30P12	0-68	A2134	0-98	EY87/6	0-24
1U4	0-29	6B7W	0-54	6L19	1-38	12AU6	0-21	30P14	0-68	A3042	0-75	DL92	0-35
1U5	0-48	6BZ6	0-31	6LD20	0-48	12AU7	0-19	30P15	0-29	AC044	1.16	E80P	1.20
2I21	0-35	6C4	0-28	6N7GT	0-40	12AV6	0-28	30P15	0-58	AC2/PEN		E83P	0.60
2GK5	0-30	6C6	0-19	6P28	0-59	12AX7	0-22	30P17	0-67		0-88	E88CC	0.60
3A4	0-25	6C9	0-73	6Q7	0-43	12BA6	0-30	30P18	0-95	AC6PEN	0.38	E92CC	0.40
3B7	0-25	6C17	0-63	6Q7G	0-27	12BB6	0-30	30P12	0-69	AC2/PEN		E190F	0.90
3D8	0-19	6CB6A	0-38	6R7	0-58	12B17	0-27	30P18	0-30	1D	0.98	E19CC100	
3Q4	0-38	6CD6G	1-08	6R7G	0-35	12J5GT	0-30	30P19		AC/PEN(7)		E198	0.53
3Q5GT	0-35	6CG8A	0-50	6RA7GT	0-35	12J7GT	0-33	30P4	0-58		0-98	E198	0.53
384	0-25	6CH6	0-38	6A7	0-35	12K5	0-50	30P11	0-59	ACTH10-50		E198	0.53
3V4	0-32	6CL6	0-43	68C7GT0-33	12K7GT	0-34	50P13	0-75	AC/TP	0-98	E198	0.53	
4C8	0-50	6CL5A	0-50	68C7GT	0-33	12K7GT	0-33	50P14	0-65	AL90	0-78	E198	0.53
5C8	0-50	6CM7	0-50	68H7	0-53	128GT	0-40	50P15	0-87	AR3	0-35	E198	0.53
5R4GY	0-53	6CU5	0-30	68J7	0-35	128C7	0-35	50P15	0-48	ATP4	0-12	E198	0.53
5V4G	0-34	6CW4	0-63	68K7GT	0-23	128G7	0-23	50P15	0-75	AZ1	0-40	E198	0.53
5Y3GT	0-28	6D3	0-38	68Q7GT	0-38	128H7	0-15	50P15	0-70	AZ31	0-46	E198	0.53
5Z5	0-45	6D6	0-15	6U6GT	0-60	128J7	0-23	50P16GT	0-42	AZ41	0-53	E198	0.53
5Z4G	0-34	6D7	0-50	6U7G	0-33	128K7	0-24	53W4	0-23	B36	0-33	E198	0.53
630L2	0-55	6D7A	0-50	6V9G	0-17	128Q7GT	0-50	53Z3	0-50	CL33	0-90	E198	0.53
6A8G	0-33	6E6W	0-55	6V8GT	0-30	14H7	0-48	53Z4GT	0-24	CV6	0-53	E198	0.53
6AC7	0-15	6F1	0-59	6X4	0-20	1487	0-75	53Z5GT	0-30	CY1C	0-53	E198	0.53
6AG5	0-25	6F6	0-63	6X5GT	0-25	19A5G	0-24	50B5	0-35	CY31	0-31	E198	0.53
6AK5	0-25	6F6G	0-65	6Y6G	0-65	19B6G	0-85	50C5	0-32	Y83	0-25	E198	0.53
6AK8	0-30	6F13	0-33	6Y7G	0-63	19G6	0-50	50C6GT	0-17	DAC2	0-33		0-34
6AM6	0-17	6F14	0-42	7B6	0-58	19H1	2-00	50EH5	0-55	DAF91	0-20		0-34
6AM8A	0-50	6F15	0-55	7B7	0-32	19I1	0-49	50L6GT	0-45	DAF96	0-33		0-34
6AN8	0-48	6F18	0-45	7C6	0-30	20D4	1-05	72	0-33	DD4	0-53		0-34
6AQ5	0-22	6F23	0-68	7F8	0-88	20F2	0-65	85A2	0-43	DP23	0-37		0-34
6AL5	0-30	6F24	0-68	7H7	0-28	20P1	0-98	85A3	0-40	DF91	0-14		0-34
6AR6	1-00	6F25	0-54	7R7	0-65	20L1	0-50	90AG	3-38	DF96	0-34		0-34

All valves are unused, boxed, and subject to the standard 90-day guarantee. Terms of business—Cash or cheque with order only. Post/packing 3p per item, subject to a minimum of 5p per order. Orders over £5 post/packing free. Same day despatch by first class mail. Any parcel insured against damage in transit for only 3p extra per order. Complete catalogue with conditions of sale price 7p post paid. Business hours Mon.-Fri. 9.30-5.30 p.m. Sat. 9.1-1 p.m.
We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for a reply.

LUBECK ENGINEERING CO. NEW TV TUBES

- 19" Monopanel = (A47/14W—CME 1908) £6.50
- 19" Rimband = (A47/26W—CME 1913) £7.00
- 20" Rimband = (A50/120W—CME 2013) £8.75
- 23" Monopanel = (A59/15W—CME 2308) £8.50
- 23" Rimband = (A59/23W—CME 2313) £10.50
- 24" Rimband = (A61/120W—CME 2413) £12.50
- (19" A47/2813W Plus Kit = 19" Twin Panel) £10.00
- (23" A59/2316W Plus Kit = 23" Twin Panel) £13.00

(NO MODIFICATIONS REQUIRED)
Full range available—Bulk user discounts.
Also rebuilt CRT'S with 2 year g'tee from £4.00
16 LIMES ROAD, CROYDON, SURREY
01-689 0193
Reverse charge telephone calls accepted from anywhere.
Free Delivery South London.
LESS 10% IF YOU COLLECT. LESS 10% IF YOU BUY 25 OFF. 1521

AERIAL BOOSTERS 19" TV £6-50

We make four types of Aerial Boosters. L45 625 U.H.F., L12 V.H.F. TV, L11 V.H.F. Radio, L10 M/W & S/W. Price L45, L12 and L11 £2.95, L10 £2.45.

VALVE BARGAINS
Any 5—45p, 10—70p:
8CC82, ECL50, EF80, EF85, EF183, EF184, EBF89, EB01, EY86, PCC84, PCC89, PC97, PCF80, PCF88, PCL82, PCL83, PCL84, PCL85, PL36, PY33, PY82, PY800, PY801, 30L15, 30C15, 6-30L2.

PRINTED CIRCUIT BOARD
2-8 ins. by 4 ins. boards complete with etching compound and instructions. 40p.


500MFD CAPACITORS
500mf/25v/w Brand New Electrolytic with long leads. 11p each.

POST AND PACKING: Under £1. 5p. Over £1, 10p. S.A.E. for leaflets on all items. Money back guarantee if not completely satisfied.

VELCO ELECTRONICS

62A Bridge Street, Ramsbottom, Bury, Lancs.

REBUILT TUBES!

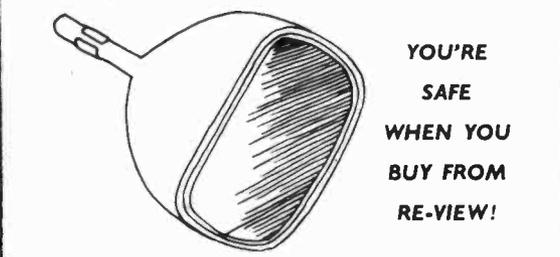

- YOU'RE SAFE WHEN YOU BUY FROM RE-VIEW!
- | | | | |
|---------------|-------|-----------------------|--------|
| 12in. | £4-75 | 21in. | £7-25 |
| 14in. | £5-00 | 23in. | £8-50 |
| 15in. | £5-25 | Twin Panel & Rimguard | |
| 17in. | £5-25 | 19in. | £8-00 |
| 19in. | £5-87 | 23in. | £10-50 |

Cash or cheque with order, or cash on delivery
COLOUR TUBES AVAILABLE

- Discount for Trade**
- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
 - ★ Each tube comes to you with a guarantee card covering it for two years against all but breakage.
 - ★ Each tube is delivered free anywhere in the U.K. and insured on the journey.
 - ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

RE-VIEW ELECTRONIC TUBES
237 London Road, West Croydon, Surrey
Tel. 01-689/7735

T.V. TUBES

"VIDEOCHROME"

T.V. TUBES

FOR BRILLIANCE & DEFINITION



17" £5-00
19" £5-50
21" £7-00
23" £7-50

19" PANORAMA £6-25
23" PANORAMA £8-25

CASH OR CHEQUE WITH ORDER


TRADE SUPPLIED

ALL TUBES PRECISION REBUILT AT OUR OWN FACTORY BY SKILLED CRAFTSMEN ● EACH TUBE BENCH AND SET TESTED TO A VERY HIGH STANDARD BEFORE DESPATCH

2 YEARS GUARANTEE ● FREE DELIVERY ANYWHERE IN THE U.K.

VIDEOCHROME TUBES LTD.
25 BELLEVUE AVENUE
RAMSGATE, KENT. Tel. THANET 52914

THE NEW UM4 "COLOURBOOSTER" UHF/625 LINE

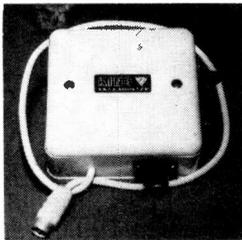

CAN PRODUCE REMARKABLE IMPROVEMENTS IN COLOUR AND PICTURE QUALITY IN FRINGE OR DIFFICULT AREAS WITH SIGNIFICANT REDUCTION IN NOISE (SNOW).

HIGH GAIN—VERY LOW NOISE
FITTED FLY LEAD—INSTALLED IN SECONDS
HIGHEST QUALITY COMPONENTS
IVORY PLASTIC CASE 3¼ x 3¼ x 1½ CORK BASE
CHANNELS: Group A, Red code 21-33
Group B, Yellow code 39-51
Group C-D, Green code 52-68

EQUALLY SUITABLE FOR BLACK AND WHITE

Also the M4 DUAL BAND VHF UNIT BOOSTS ALL BAND III and ANY SPECIFIED BAND I CHANNEL SIMULTANEOUSLY NOMINAL GAIN 17-18 DB BOTH BANDS

PRICES BOTH TYPES:

£3.75 Battery model or £5.87 Self-contained mains version
Postage and Packing 13p

TRANSISTOR DEVICES LIMITED
6 ORCHARD GARDENS, TEIGNMOUTH, DEVON
Telephone: Teignmouth 4757

UHF. COLOUR AND TELEVISION SPARES

SPECIAL OFFER VARICAP UHF tuner ELC 1043, for electronic tuning, incl. data £4-50 p.p. 25p.
COLOUR DELI CHROMINANCE DELAY UNIT £1-95 p.p. 25p.
LUMINANCE DELAY UNIT £1-35 p.p. 15p. **PLESSEY SCAN COILS £5-75** p.p. 35p. **CONVERGENCE COILS £3-80** p.p. 25p. **BLUE LATERAL £1-25** p.p. 9p, or Complete Set £10 p.p. 50p. **MULLARD TYPE, SCAN COILS £3-50** p.p. 35p. **CONVERGENCE COILS £1-75** p.p. 25p. **LUMINANCE/CHROMINANCE PANEL £1** p.p. 25p. **INTEGRATED TRANSISTORISED DECODER UNIT** including Circuits £1-25 p.p. 10p. **LINE OUTPUT TRANSFORMER** including EHT and FOCUS ASSEMBLY £3-50 p.p. 35p. (Shop customers only, assortment Colour Panels of various makes.) ALSO COLOUR TV CAMERA UNITS.

COLOUR TV MONITOR PANELS Designed to highest BBC standards. PAL filter & delay £8-00, Chrominance £8-00, Luminance £4-50, Encoded Video Input £2-50 incl. circuit, p.p. 30p. **UHF 625 conversion kits and tuners** available at reduced prices. Lists available.

UHF tuners transistd. incl. S/M drive, indicator £3-95, or push-button £5-25. **CHF/VHF transistd. basic tuner, latest type, incl. circuit £3-95.** Cydon valve type, £1-50 p.p. 25p.

MURPHY 600/700 series UHF conversion kits in cabinet plinth assembly can be used as separate UHF receiver £7-50 p.p. 50p. **SOBELL/GEC Dual 405/625 1F amp and o/p chassis incl. circuit £1-50** p.p. 30p. **PHILIPS 625 P/CIF panel incl. circuit £1** p.p. 25p. **EKCO/FERRANTI UHF tuner kit, incl. valves, slow motion drive, knobs, leads, aerial panel £5-50** p.p. 30p.

TV SIGNAL BOOSTERS. Latest **PYE/LABGEAR** all station UHF/VHF transistd. 3 outlet Amplifier £6-50, UHF Masthead £4-85, Power unit £3-25. p.p. 25p.

FIREBALL TUNERS Ferg., HMV, Marconi, New £1-90 p.p. 25p. **PUSH BUTTON** Plessey, Ekco, Ferranti £1 p.p. 25p.

TURRET TUNERS. KB "Featherlight" VC11, Philips 170 series, GEC2010 £2-50, AB Dual Standard Suitable Ferguson, Baird, KB etc. 75p, Cydon C 75p, Pye 110/510 Pam, Invicta, Miniature, incremental £2-50. Peto Scott 960, Cossor 1964, Decca 95/606 £2-00 pp 25p.

LINE OUTPUT TRANSFORMERS. Popular types available, brand new replacements, fully guar. A selection which can be supplied p.p. 25p. C.O.D. 25p.

MURPHY 470 to 530 (oilfilled) .. £3-75
MURPHY 849 to 939, 153 to 179 .. £4-50
PHILIPS 1768/2168, 1796/2196 .. £4-50
PHILIPS 17TG100 Range .. £3-90

STELLA 1011/1029 .. £3-90
PHILIPS 19TG111/12 .. £4-00
PHILIPS 19TG121 to 156 .. £4-50
PHILIPS 19TG170, 210 series .. £4-50

BUSH TV53 to 69 £1-75 105 to 178 .. £4-50
EKCO 221 to 331 (U25 or U26) .. £3-75
FERRANTI 1001/19 (U25 or U26) .. £3-75
EKCO 342 to 394, FERRANTI .. £3-90

1021 to 1065 .. £3-90
EKCO, FERRANTI 418, 1093 etc. .. £3-90
DECCA DM17, 3, 4 (705) DR95, 101/606 .. £3-95

FERG 305 to 436, 606 to 727 .. £3-90
FERG, HMV, MARCONI, ULTRA, PHILCO 3600, 2600, 4600, 6600, 1100, Jellypot .. £3-75
KB RV20, SV20, VC1 to VC11 .. £4-00
MARCONI VT157 to 172 .. £3-90

GEC 302 to 346, £2-50, 448 to 452 .. £3-25
GEC 454/6, 2000 series .. £4-50
HMV 1805/9, 1870/6, 1910/1924 .. £3-90
PYE (TM/CW series (printed circuit) 17/21, 17/S, 110 to 510, 700, 830, 1, 2, 3, 11U to 48 .. £3-90

PAM, INVICTA equiv. LOPTS to above PYE .. £3-90
SOBELL/McMICHAEL TPS 173, 180, T23, 24, 178, 278, SC24, 270, MP17, 18, M72, M74, M247 .. £2-50

TPS 781, 279, SC34, 370, MP27, M75, 76, 93, T25, 280, TP8710 .. £3-25
195, 282 to 288, 762, 763 .. £3-25
SOBELL 196/7, 1000 series .. £4-50
PHILCO 1010 to 1021 .. £2-25
ULTRA 1770 to 2834 .. £3-90

ALBA 655, 656 .. £1-75
Cossor 933 to 950 .. £1-75
Ekco TP308 .. £1-75
Emerson 700/711 .. £1-75
KB, NETO, OV30, PV40, PVP20, QV10, 20, 30 .. £1-75

KB/RGD VC11 Featherlight .. £2-50
KB/RGD VC1-9 .. £1-75
Philco 1030 series .. £1-75
Philips 17TG100 range .. £1-75
Pye, VT4, VT7 .. £2-15
RGD 610, 711 .. £2-50
RGD 619, 620 .. £2-50

LOPT Inserts p.p. 15p
Alba 655, 656 .. £1-75
Cossor 933 to 950 .. £1-75
Ekco TP308 .. £1-75
Emerson 700/711 .. £1-75
KB, NETO, OV30, PV40, PVP20, QV10, 20, 30 .. £1-75

KB/RGD VC11 Featherlight .. £2-50
KB/RGD VC1-9 .. £1-75
Philco 1030 series .. £1-75
Philips 17TG100 range .. £1-75
Pye, VT4, VT7 .. £2-15
RGD 590 to 619 .. £1-75
REG 10-4, 10-12 to 192 .. £1-75
Ultra 1770, 1780 .. £1-75

PRACTICAL TV 625 RECEIVER. Integrated push button transistorised tuner .. £4-90 p.p. 25p
Transistorised IF panel .. £4-75 p.p. 25p
850 line output transformer .. £3-75 p.p. 25p
850 field output transformer .. £1-62 p.p. 15p
850 scan coils .. £3-90 p.p. 25p

(p.p. on complete set of 5 items 50p)
THORN 850 Time Base Panel, Dual Standard £1 p.p. 30p
THORN 850 Mains Droppers 25p, pp 10p (state approx. values)
VALVE BASES B9D for PL500 series and colour 12p p.p. 5p

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6

(Near W. Hampstead tube stn; 28, 59, 159 Bus Routes) 01-794 8751
MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11

In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering . . .

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast—makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

WHICH SUBJECT WOULD INTEREST YOU?

Mechanical

A.M.S.E. (Mech.)
Inst. of Engineers
Mechanical Eng.
Maintenance Eng.
Welding
General Diesel Eng.
Sheet Metal Work
Eng. Inspection
Eng. Metallurgy
C. & G. Eng. Crafts
C. & G. Fabrication

Draughtsmanship

A.M.I.E.D.
Gen. Draughtsmanship
Die & Press Tools
Elec. Draughtsmanship
Jig & Tool Design
Design of Elec. Machines
Technical Drawing
Building

Electrical & Electronic

A.M.S.E. (Elec.)
C. & G. Elec. Eng.
General Elec. Eng.
Installations & Wiring
Electrical Maths.
Electrical Science
Computer Electronics
Electronic Eng.

Radio & Telecomms.

C. & G. Telecomms.
C. & G. Radio Servicing
Radio Amateurs' Exam.
Radio Operators' Cert.
Radio & TV Engineering
Radio Servicing
Practical Television
TV Servicing
Colour TV
Practical Radio & Electronics (with kit)

Auto & Aero

A.M.I.M.I.
MAA IMI Diploma
C. & G. Auto Eng.
General Auto Eng.
Motor Mechanics
A.R.B. Certs.
Gen. Aero Eng.

Management & Production

Computer Programming
Inst. of Marketing
A.C.W.A.
Works Management
Work Study
Production Eng.
Storekeeping
Estimating
Personnel Management
Quality Control
Electronic Data Processing
Numerical Control
Planning Engineering
Materials Handling
Operational Research
Metrication

Constructional

A.M.S.E. (Civ.)
C. & G. Structural
Road Engineering
Civil Engineering
Building
Air Conditioning
Heating & Ventilating
Carpentry & Joinery
Clerk of Works
Building Drawing
Surveying
Painting and Decorating.
Architecture
Builders' Quantities

General

C.E.I.
Petroleum Tech.
Practical Maths.
Refrigerator Servicing.
Rubber Technology
Sales Engineer
Timber Trade
Farm Science
Agricultural Eng.
General Plastics

General Certificate of Education

Choose from 42 'O' and 'A' Level subjects including:
English
Chemistry
General Science
Geology
Physics
Mathematics
Technical Drawing
French
German
Russian
Spanish
Biology
B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.

WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.

Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.

THEY DID IT—SO COULD YOU

"My income has almost trebled . . . my life is fuller and happier."—Case History G/321.

"In addition to having my salary doubled, my future is assured."—Case History H/493.

"Completing your Course meant going from a job I detested to a job I love."—Case History B/461.

FIND OUT FOR YOURSELF

These letters—and there are many more on file at Aldermaston Court—speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

Free!

Why not do the thing that really interests you? Without losing a day's pay, *you* could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you . . . but it could be the best thing you ever did.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B1, Aldermaston Court, Reading RG7 4PF.

Accredited by the Council for the Accreditation of Correspondence Colleges.



BIET

(Write if you prefer not to cut this page.)

POST THIS COUPON TODAY

To: B.I.E.T., Dept. B1, Aldermaston Court, Reading RG7 4PF
Please send me book and details of your Courses in

Name Age

BLOCK CAPITALS PLEASE

Address

Occupation

B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE