

# TELEVISION

20p


SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

JULY  
1973

**RENOVATING THE  
PHILIPS G6  
COLOUR CHASSIS**

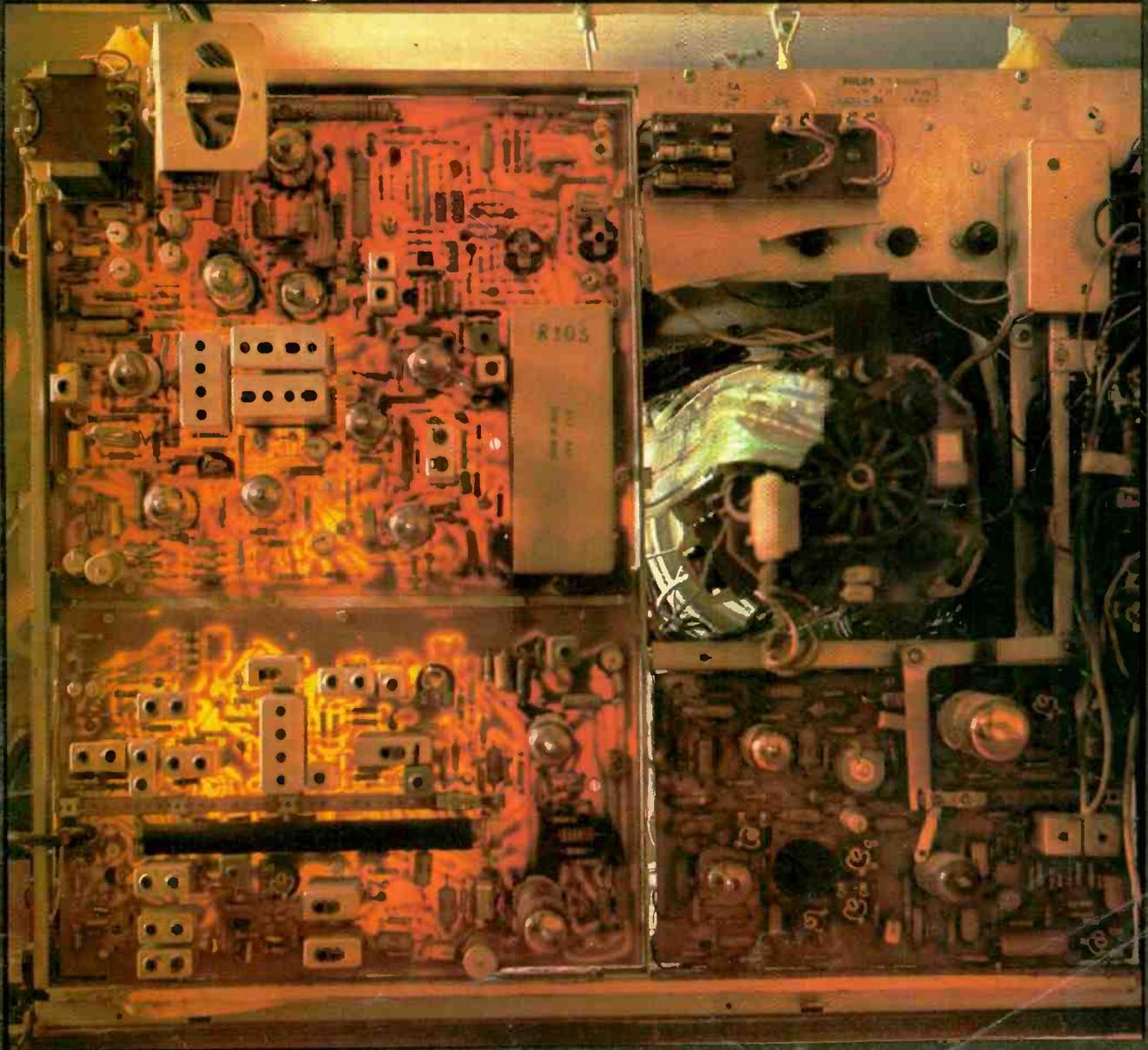**ALSO:**

DC RESTORATION CIRCUIT  
COLOUR RECEIVER INSIGHT  
FAULT FINDING - BUSHTV141 IF PANEL



## COLOUR, UHF AND TELEVISION SPARES

"TELEVISION" Constructor's Colour Set. Demonstration Model, now working and on view at 172 West End Lane, N.W.6. Already seen by hundreds of constructors. Complete your set with MANOR SUPPLIES COMPONENTS. Call, phone or write for up to date information colour lists.

SCAN PACK No. 21. Mullard or Plessey Scan Coils, Convergence Yoke, Blue Lateral, complete set for £10.00 p.p. 40p.

PRINTED CIRCUIT BOARDS. Convergence, 3 for £2.50 p.p. 30p. Decoder, I.F. amp, Time Base £1.25, Power £1.50 p.p. 25p, R.G.B. 70p p.p. 17p, Varicap, C.R.T. Base 66p p.p. 11p. Complete Set £8.25 p.p. 35p. Audio Panel & P.A.263 £1.95 p.p. 15p.

PACKS (incl. p.p.). No. 2 £4.90, No. 5 £1.05, No. 9 45p, No. 12 31p, No. 13 35p, No. 14 £9.90, No. 15 £2.28, No. 16 £10.95, No. 17 £2.72, No. 19 £2.30, No. 21 £10.40, No. 22 £2.20. C.R.T. Base 30p, C.R.T. Shields £2.05 p.p. 55p, Varicap ELC1043 £4.50, TAA550 62p, AE Isolpanel 30p. Pack No. 23 £2.95.

MAINS TRANSFORMER for Colour Receiver, guaranteed to give correct outputs under actual load conditions, plus additional 6.3V C.R.T. heater tapping £9.50 p.p. 50p.

C.R.T. HEATER TRANSFORMERS 6.3V 1 amp £1.10 p.p. 25p. SPECIAL OFFER I.F. Panel, leading British maker, similar design to "Television" panel. Now in use as alternative, incl. circuit, £8.90 p.p. 35p.

G.E.C. Colour decoder oanel (for parts) incl. DL20, crystal and approx. 50% of resistors. Conds., diodes, transist., etc. for "Television" decoder £3.50 p.p. 30p.

PHILIPS G6 single standard convergence panel, incl. 16 controls, switches etc. and circuits £5.00 p.p. 30p.

PHILIPS G8 decoder panel part complete incl. I/C £2.50. I.F. Panel part/compl incl. modules £2.50 p.p. 30p.

BUSH CTV25 timebase units, line frame, E.H.T. surplus £4.50 p.p. 80p. Mk. III Quadrupler Trays/E.H.T. £8.25 p.p. 25p.

VARICAP/VARACTOR ELC 1043 UHF tuner (for "Television" colour receiver) £4.50. VHF Varicap tuners for band 1 & 3 £2.85, Varicap tuners salvaged £1.50 p.p. 25p.

UHF 625 kits and tuners. Lists available at reduced prices. UHF tuners, transist., £3.10, incl. s/m drive, indicator £3.85; 6 position pushbutton £4.95. UHF/VHF transist. tuner, latest type, incl. circuit £3.25. Cylcon valve type £1.50 p.p. 30p.

MURPHY 600/700 series UHF conversion kits in cabinet plinth assembly, can be used as separate UHF receiver £7.50 p.p. 50p.

SOBELL/GEC Dual 405/625 I.F. amp and o/p chassis incl. circuit £1.50 p.p. 30p. PHILIPS 625 I.F. panel incl. cct £1 p.p. 30p.

FIREBALL TUNERS. Ferg. HMV, Marconi. New £1.90 p.p. 25p. TURRET TUNERS, KB "Featherlight" VC11, Philips 170 series, GEC 2010 £2.50, AB Dual Stand, suitable Ferguson, Baird, KB etc.

75p, Cylcon C 75p, Pye 110/510-Pam, Invicta, Miniature, increm. £1.95, Peto Scott 960, Decca 95/606 £1.50 p.p. 30p.

LINE OUTPUT TRANSFORMERS. Popular types available, brand new replacements, fully guar. A selection which can be supplied p.p. 30p. C.O.D. 28p.

MURPHY 849, 939, 153 2417S	£4.90	SPECIAL OFFERS	
PHILIPS 1768/2168, 1796/2196	£4.90	BUSH TV53/86	... £1.75
PHILIPS 17TG/100 Range		BUSH TV95/99	... £2.50
STELLA 1011/1029	... £4.30	EKCO 380 to 390	... £2.50
PHILIPS 19TG111/112	... £4.40	EKCO 407/417	... £2.50
PHILIPS 19TG121 to 156	... £4.90	FERR 1057 to 1068	... £2.50
PHILIPS 19TG170, 210 series	... £4.90	FERR 1084/1092	... £2.50
BUSH TV92, 93, 105 to 186SS	£4.90	FERG. 506 to 546	... £1.50
EKCO 221 to 394, FERRANTI		HMV 1890 to 1896	... £1.50
1001 to 1065	... £4.30	P/SCOTT 1419 to	
EKCO, FERR. 418, 1093 etc.	£4.30	1725, 733 to 738	... £1.75
DECCA DR95, 101/606, DR1,		REG 10-6, 10-17	... £2.50
2, 3, 121/123, 20/24, 2000	... £4.70	REG 191/2, 17-18	... £2.50
FERG 305 to 436, 606 to 727	... £4.30	RGD 519, 606, 610,	
FERG, HMV, MARCONI		612, 619, 620, 711	... £2.50
ULTRA, PHILCO 3600, 2600,		PHILCO 1010/21	... £2.25
4600, 6600, 1100 series, Jell pot	£4.70		
KB VC1 to VC11	... £4.40	LOPT Inserts p.p.	... 17p
MARCONI VT157 to 172	... £4.30	KB NF70, OV30, PV40,	
GEC 302 to 456, 2000 series	... £4.90	PVP20, QV10, 20, 30	... £1.95
HMV 1865/9, 1870/6, 1910/1924	£4.30	KB/RGD VCH	
PYE 17/21, 17/S, 110 to 510,		Featherlight	... £2.75
700, 830, 1, 2, 3, 11U to 64	... £4.30	KB/RGD VC1-9	... £1.95
PAM, INVICTA equiv. LOPTS			
to above PYE	... £4.30	PHILCO 1030/50	... £1.95
SOBELL 195/282/1000 series	... £4.90	PHILIPS 17TG100...	... £4.95
Transistorised I.F. panel (salvaged)			... £2.50 p.p. 25p
850 field output transformer	... £1.80		p.p. 20p
850 scan coils	... £4.40		p.p. 30p
THORN 850 Time Base Panel. Dual Standard	£1 p.p. 30p.		
THORN 850 Mains Droppers 30p p.p. 15p (state approx values)			

CALLERS WELCOME AT SHOP PREMISES

## MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6  
(Near W. Hampstead tube stn; 28, 59, 159 Bus Routes) 01-794 8751  
Mail Order: 64 GOLDERS MANOR DRIVE,  
LONDON, N.W.11

CLOSED FOR STAFF HOLIDAYS, JULY 18th to AUG. 1st incl.

## A. MARSHALL & SON (LONDON) LTD.,

SEMICONDUCTOR SPECIALISTS

42 CRICKLEWOOD BROADWAY, LONDON, N.W.2

Telephone: 01-452 0161/2 Telex: 21492 Cable: Coninst London

NEW LOW PRICES LARGEST RANGE BRAND NEW  
FULLY GUARANTEED

★

We Supply

COMPLETE KITS for the following units:

Television Kit No. 1 **£8.02**

PAL Decoder

Television Kit No. 4 **£7.87**

I.F. Strip

Television Kit No. 8 **£6.35**

R.G.B. Board

Television Kit No. 10 **£7.15**

Time-Base

No increase in prices ! !

## STOP PRESS:

New catalogue available at 15p.

## 100-watt Guitar Amplifier—complete

kit with case and all components **£23.50**

## "SCORPIO"

Capacitor discharge ignition system (as described in *Practical Electronics*, Nov. 1971).

COMPLETE KIT £10.00 P. & P. 50p.

We Stock Full Range of:

Motorola consumer I.C.s

RCA Cos-Mos

Signetics popular I.C.s

★

ALL PRICES EXCLUSIVE  
OF V.A.T.

<p><b>Branded TTL I.C.'s</b></p> <table border="0"> <tr> <td>7400 25p</td> <td>7475 55p</td> <td>7418 24p</td> </tr> <tr> <td>7413 20p</td> <td>7476 55p</td> <td>7419 45p</td> </tr> <tr> <td>7420 25p</td> <td>7480 75p</td> <td>7423 55p</td> </tr> <tr> <td>7473 40p</td> <td>7482 75p</td> <td>7414 55p</td> </tr> <tr> <td>7414 40p</td> <td>7483 75p</td> <td>7416 55p</td> </tr> </table> <p><b>I.C. Sockets</b> Dead-in-line or Zig-Zag 14 and 16 pin Our Price 1p per pin.</p>	7400 25p	7475 55p	7418 24p	7413 20p	7476 55p	7419 45p	7420 25p	7480 75p	7423 55p	7473 40p	7482 75p	7414 55p	7414 40p	7483 75p	7416 55p	<p><b>VDR's &amp; Thermistors</b></p> <table border="0"> <tr> <td>A15B 75p</td> <td>GL23 £1.00</td> <td>VA1005 15p</td> </tr> <tr> <td>AC176 15p</td> <td>R53 £1.32</td> <td>VA1026 13p</td> </tr> <tr> <td>C24 13p</td> <td>R54 £1.46</td> <td>VA1033 13p</td> </tr> <tr> <td>CZ13A 13p</td> <td></td> <td>VA1040 10p</td> </tr> <tr> <td>E298 ED/A258 10p</td> <td></td> <td>VA1053 10p</td> </tr> <tr> <td>E298 ZZ/06 10p</td> <td></td> <td>VA1055S 10p</td> </tr> <tr> <td>GL16 £1</td> <td></td> <td>VA1034 10p</td> </tr> </table>	A15B 75p	GL23 £1.00	VA1005 15p	AC176 15p	R53 £1.32	VA1026 13p	C24 13p	R54 £1.46	VA1033 13p	CZ13A 13p		VA1040 10p	E298 ED/A258 10p		VA1053 10p	E298 ZZ/06 10p		VA1055S 10p	GL16 £1		VA1034 10p	<p><b>Potentiometers</b></p> <table border="0"> <tr> <td>5KΩ</td> <td>50KΩ</td> <td>500KΩ</td> </tr> <tr> <td>10KΩ</td> <td>100KΩ</td> <td>1MΩ</td> </tr> <tr> <td>25KΩ</td> <td>250KΩ</td> <td>2MΩ</td> </tr> <tr> <td>log or lin less switch (&amp; 1KΩ lin)</td> <td></td> <td>12p</td> </tr> <tr> <td>log or lin with switch</td> <td></td> <td>24p</td> </tr> <tr> <td>dual less switch</td> <td></td> <td>40p</td> </tr> <tr> <td>dual with switch 10K, 100K &amp; 1M</td> <td></td> <td>52p</td> </tr> <tr> <td>log only</td> <td></td> <td>40p</td> </tr> <tr> <td>10K log - 10K antilog less switch</td> <td></td> <td></td> </tr> </table>	5KΩ	50KΩ	500KΩ	10KΩ	100KΩ	1MΩ	25KΩ	250KΩ	2MΩ	log or lin less switch (& 1KΩ lin)		12p	log or lin with switch		24p	dual less switch		40p	dual with switch 10K, 100K & 1M		52p	log only		40p	10K log - 10K antilog less switch			<p><b>Capacitors</b></p> <p><b>Ceramic - plate</b> 63V (C333)</p> <table border="0"> <tr> <td>1-8pf</td> <td>8-2pf</td> <td>33pf</td> <td>120pf</td> </tr> <tr> <td>2-2pf</td> <td>10pf</td> <td>39pf</td> <td>150pf</td> </tr> <tr> <td>3-3pf</td> <td>12pf</td> <td>47pf</td> <td>180pf</td> </tr> <tr> <td>3-9pf</td> <td>15pf</td> <td>56pf</td> <td>220pf</td> </tr> <tr> <td>4-7pf</td> <td>18pf</td> <td>68pf</td> <td>270pf</td> </tr> <tr> <td>5-6pf</td> <td>22pf</td> <td>82pf</td> <td>330pf</td> </tr> <tr> <td>6-8pf</td> <td>27pf</td> <td>100pf</td> <td></td> </tr> <tr> <td>all 5p. each</td> <td></td> <td></td> <td></td> </tr> </table> <p><b>mylar film</b> 100V</p> <table border="0"> <tr> <td>1000pf</td> <td>2p</td> <td>-01μF</td> <td>3p</td> <td>-068μF</td> <td>4p</td> </tr> <tr> <td>2000pf</td> <td>2p</td> <td>-02μF</td> <td>3p</td> <td>-11μF</td> <td>4p</td> </tr> <tr> <td>5000pf</td> <td>2p</td> <td>-04μF</td> <td>3p</td> <td>-2μF</td> <td>5p</td> </tr> <tr> <td></td> <td></td> <td>-05μF</td> <td>3p</td> <td></td> <td></td> </tr> </table> <p><b>metallised polyester</b> 250V (C280)</p> <table border="0"> <tr> <td>-01μF</td> <td>3p</td> <td>-068μF</td> <td>3p</td> <td>-47μF</td> <td>8p</td> </tr> <tr> <td>-015μF</td> <td>3p</td> <td>-11μF</td> <td>4p</td> <td>-68μF</td> <td>11p</td> </tr> <tr> <td>-022μF</td> <td>3p</td> <td>-15μF</td> <td>4p</td> <td>1μF</td> <td>13p</td> </tr> <tr> <td>-033μF</td> <td>3p</td> <td>-22μF</td> <td>5p</td> <td>1.5μF</td> <td>20p</td> </tr> <tr> <td>-047μF</td> <td>3p</td> <td>-33μF</td> <td>6p</td> <td>2.2μF</td> <td>24p</td> </tr> </table> <p><b>metallised polyester</b> 400V (C281)</p> <table border="0"> <tr> <td>-01μF</td> <td>4p</td> <td>-047μF</td> <td>6p</td> <td>-22μF</td> <td>10p</td> </tr> <tr> <td>-015μF</td> <td>4p</td> <td>-068μF</td> <td>6p</td> <td>-33μF</td> <td>14p</td> </tr> <tr> <td>-022μF</td> <td>4p</td> <td>-11μF</td> <td>7p</td> <td>-47μF</td> <td>15p</td> </tr> <tr> <td>-033μF</td> <td>5p</td> <td>-15μF</td> <td>8p</td> <td></td> <td></td> </tr> </table> <p><b>mixed dielectric</b> 600V</p> <table border="0"> <tr> <td>-01μF</td> <td>7p</td> <td>-047μF</td> <td>7p</td> <td>-22μF</td> <td>18p</td> </tr> <tr> <td>-022μF</td> <td>7p</td> <td>-068μF</td> <td>8p</td> <td>-47μF</td> <td>24p</td> </tr> <tr> <td>-033μF</td> <td>7p</td> <td>-11μF</td> <td>8p</td> <td>1μF</td> <td>33p</td> </tr> </table> <p><b>mixed dielectric</b> 1000V</p> <table border="0"> <tr> <td>1000pf</td> <td>6p</td> <td>6800pf</td> <td>9p</td> <td>1μF</td> <td>12p</td> </tr> <tr> <td>2200pf</td> <td>6p</td> <td>01μF</td> <td>9p</td> <td>-22μF</td> <td>20p</td> </tr> <tr> <td>3300pf</td> <td>6p</td> <td>-022μF</td> <td>9p</td> <td>-47μF</td> <td>30p</td> </tr> <tr> <td>4700pf</td> <td>6p</td> <td>-047μF</td> <td>12p</td> <td></td> <td></td> </tr> </table> <p><b>Ceramic</b> 12KV d.c.</p> <table border="0"> <tr> <td>100pf</td> <td>9p</td> <td>200pf</td> <td>9p</td> <td>1000pf</td> <td>5p</td> </tr> <tr> <td>15pf</td> <td>9p</td> <td>220pf</td> <td>9p</td> <td>1500pf</td> <td>5p</td> </tr> <tr> <td>22pf</td> <td>9p</td> <td>250pf</td> <td>9p</td> <td>2000pf</td> <td>5p</td> </tr> <tr> <td>68pf</td> <td>9p</td> <td>270pf</td> <td>9p</td> <td>3000pf</td> <td>5p</td> </tr> <tr> <td>82pf</td> <td>9p</td> <td>500pf</td> <td>9p</td> <td>5000pf</td> <td>5p</td> </tr> <tr> <td>100pf</td> <td>9p</td> <td>750V DISC</td> <td>10,000pf</td> <td>5p</td> <td></td> </tr> <tr> <td>120pf</td> <td>9p</td> <td>470pf</td> <td>5p</td> <td>feed-</td> <td></td> </tr> <tr> <td>140pf</td> <td>9p</td> <td>1000pf</td> <td>5p</td> <td>through</td> <td></td> </tr> <tr> <td>150pf</td> <td>9p</td> <td>5000pf</td> <td>5p</td> <td></td> <td></td> </tr> <tr> <td>180pf</td> <td>9p</td> <td>10,000pf</td> <td>5p</td> <td>1000pf</td> <td>5p</td> </tr> </table>	1-8pf	8-2pf	33pf	120pf	2-2pf	10pf	39pf	150pf	3-3pf	12pf	47pf	180pf	3-9pf	15pf	56pf	220pf	4-7pf	18pf	68pf	270pf	5-6pf	22pf	82pf	330pf	6-8pf	27pf	100pf		all 5p. each				1000pf	2p	-01μF	3p	-068μF	4p	2000pf	2p	-02μF	3p	-11μF	4p	5000pf	2p	-04μF	3p	-2μF	5p			-05μF	3p			-01μF	3p	-068μF	3p	-47μF	8p	-015μF	3p	-11μF	4p	-68μF	11p	-022μF	3p	-15μF	4p	1μF	13p	-033μF	3p	-22μF	5p	1.5μF	20p	-047μF	3p	-33μF	6p	2.2μF	24p	-01μF	4p	-047μF	6p	-22μF	10p	-015μF	4p	-068μF	6p	-33μF	14p	-022μF	4p	-11μF	7p	-47μF	15p	-033μF	5p	-15μF	8p			-01μF	7p	-047μF	7p	-22μF	18p	-022μF	7p	-068μF	8p	-47μF	24p	-033μF	7p	-11μF	8p	1μF	33p	1000pf	6p	6800pf	9p	1μF	12p	2200pf	6p	01μF	9p	-22μF	20p	3300pf	6p	-022μF	9p	-47μF	30p	4700pf	6p	-047μF	12p			100pf	9p	200pf	9p	1000pf	5p	15pf	9p	220pf	9p	1500pf	5p	22pf	9p	250pf	9p	2000pf	5p	68pf	9p	270pf	9p	3000pf	5p	82pf	9p	500pf	9p	5000pf	5p	100pf	9p	750V DISC	10,000pf	5p		120pf	9p	470pf	5p	feed-		140pf	9p	1000pf	5p	through		150pf	9p	5000pf	5p			180pf	9p	10,000pf	5p	1000pf	5p
7400 25p	7475 55p	7418 24p																																																																																																																																																																																																																																																																																				
7413 20p	7476 55p	7419 45p																																																																																																																																																																																																																																																																																				
7420 25p	7480 75p	7423 55p																																																																																																																																																																																																																																																																																				
7473 40p	7482 75p	7414 55p																																																																																																																																																																																																																																																																																				
7414 40p	7483 75p	7416 55p																																																																																																																																																																																																																																																																																				
A15B 75p	GL23 £1.00	VA1005 15p																																																																																																																																																																																																																																																																																				
AC176 15p	R53 £1.32	VA1026 13p																																																																																																																																																																																																																																																																																				
C24 13p	R54 £1.46	VA1033 13p																																																																																																																																																																																																																																																																																				
CZ13A 13p		VA1040 10p																																																																																																																																																																																																																																																																																				
E298 ED/A258 10p		VA1053 10p																																																																																																																																																																																																																																																																																				
E298 ZZ/06 10p		VA1055S 10p																																																																																																																																																																																																																																																																																				
GL16 £1		VA1034 10p																																																																																																																																																																																																																																																																																				
5KΩ	50KΩ	500KΩ																																																																																																																																																																																																																																																																																				
10KΩ	100KΩ	1MΩ																																																																																																																																																																																																																																																																																				
25KΩ	250KΩ	2MΩ																																																																																																																																																																																																																																																																																				
log or lin less switch (& 1KΩ lin)		12p																																																																																																																																																																																																																																																																																				
log or lin with switch		24p																																																																																																																																																																																																																																																																																				
dual less switch		40p																																																																																																																																																																																																																																																																																				
dual with switch 10K, 100K & 1M		52p																																																																																																																																																																																																																																																																																				
log only		40p																																																																																																																																																																																																																																																																																				
10K log - 10K antilog less switch																																																																																																																																																																																																																																																																																						
1-8pf	8-2pf	33pf	120pf																																																																																																																																																																																																																																																																																			
2-2pf	10pf	39pf	150pf																																																																																																																																																																																																																																																																																			
3-3pf	12pf	47pf	180pf																																																																																																																																																																																																																																																																																			
3-9pf	15pf	56pf	220pf																																																																																																																																																																																																																																																																																			
4-7pf	18pf	68pf	270pf																																																																																																																																																																																																																																																																																			
5-6pf	22pf	82pf	330pf																																																																																																																																																																																																																																																																																			
6-8pf	27pf	100pf																																																																																																																																																																																																																																																																																				
all 5p. each																																																																																																																																																																																																																																																																																						
1000pf	2p	-01μF	3p	-068μF	4p																																																																																																																																																																																																																																																																																	
2000pf	2p	-02μF	3p	-11μF	4p																																																																																																																																																																																																																																																																																	
5000pf	2p	-04μF	3p	-2μF	5p																																																																																																																																																																																																																																																																																	
		-05μF	3p																																																																																																																																																																																																																																																																																			
-01μF	3p	-068μF	3p	-47μF	8p																																																																																																																																																																																																																																																																																	
-015μF	3p	-11μF	4p	-68μF	11p																																																																																																																																																																																																																																																																																	
-022μF	3p	-15μF	4p	1μF	13p																																																																																																																																																																																																																																																																																	
-033μF	3p	-22μF	5p	1.5μF	20p																																																																																																																																																																																																																																																																																	
-047μF	3p	-33μF	6p	2.2μF	24p																																																																																																																																																																																																																																																																																	
-01μF	4p	-047μF	6p	-22μF	10p																																																																																																																																																																																																																																																																																	
-015μF	4p	-068μF	6p	-33μF	14p																																																																																																																																																																																																																																																																																	
-022μF	4p	-11μF	7p	-47μF	15p																																																																																																																																																																																																																																																																																	
-033μF	5p	-15μF	8p																																																																																																																																																																																																																																																																																			
-01μF	7p	-047μF	7p	-22μF	18p																																																																																																																																																																																																																																																																																	
-022μF	7p	-068μF	8p	-47μF	24p																																																																																																																																																																																																																																																																																	
-033μF	7p	-11μF	8p	1μF	33p																																																																																																																																																																																																																																																																																	
1000pf	6p	6800pf	9p	1μF	12p																																																																																																																																																																																																																																																																																	
2200pf	6p	01μF	9p	-22μF	20p																																																																																																																																																																																																																																																																																	
3300pf	6p	-022μF	9p	-47μF	30p																																																																																																																																																																																																																																																																																	
4700pf	6p	-047μF	12p																																																																																																																																																																																																																																																																																			
100pf	9p	200pf	9p	1000pf	5p																																																																																																																																																																																																																																																																																	
15pf	9p	220pf	9p	1500pf	5p																																																																																																																																																																																																																																																																																	
22pf	9p	250pf	9p	2000pf	5p																																																																																																																																																																																																																																																																																	
68pf	9p	270pf	9p	3000pf	5p																																																																																																																																																																																																																																																																																	
82pf	9p	500pf	9p	5000pf	5p																																																																																																																																																																																																																																																																																	
100pf	9p	750V DISC	10,000pf	5p																																																																																																																																																																																																																																																																																		
120pf	9p	470pf	5p	feed-																																																																																																																																																																																																																																																																																		
140pf	9p	1000pf	5p	through																																																																																																																																																																																																																																																																																		
150pf	9p	5000pf	5p																																																																																																																																																																																																																																																																																			
180pf	9p	10,000pf	5p	1000pf	5p																																																																																																																																																																																																																																																																																	
<p><b>Transistors</b></p> <table border="0"> <tr> <td>AC128 15p</td> <td>BC172 18p</td> <td>BF184 25p</td> </tr> <tr> <td>AC176 15p</td> <td>BD115 67p</td> <td>BF185 25p</td> </tr> <tr> <td>AF239 30p</td> <td>BD124 £1.01</td> <td>BF194 15p</td> </tr> <tr> <td>AF239 30p</td> <td>BD131 70p</td> <td>BF195 15p</td> </tr> <tr> <td>BC107 10p</td> <td>BD132 70p</td> <td>BF196 15p</td> </tr> <tr> <td>BC108 10p</td> <td>BD131/2M.P. £1.48</td> <td>BF197 15p</td> </tr> <tr> <td>BC109 10p</td> <td>BF115 25p</td> <td>BF272 53p</td> </tr> <tr> <td>BC147 10p</td> <td>BF167 20p</td> <td>BFY50 24p</td> </tr> <tr> <td>BC148 10p</td> <td>BF173 20p</td> <td>BRY39 36p</td> </tr> <tr> <td>BC149 10p</td> <td>BF180 25p</td> <td>BSX21 26p</td> </tr> <tr> <td>BC171 21p</td> <td>BF181 30p</td> <td>BU105 £2</td> </tr> </table>	AC128 15p	BC172 18p	BF184 25p	AC176 15p	BD115 67p	BF185 25p	AF239 30p	BD124 £1.01	BF194 15p	AF239 30p	BD131 70p	BF195 15p	BC107 10p	BD132 70p	BF196 15p	BC108 10p	BD131/2M.P. £1.48	BF197 15p	BC109 10p	BF115 25p	BF272 53p	BC147 10p	BF167 20p	BFY50 24p	BC148 10p	BF173 20p	BRY39 36p	BC149 10p	BF180 25p	BSX21 26p	BC171 21p	BF181 30p	BU105 £2	<p><b>Resistors</b></p> <p>½ watt 5% Carbon Film - low noise</p> <p><b>Hi-Stabs</b> All E24 values 1p each plus p. &amp; p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value.</p> <p>1W 10% Carbon Composition 3p each</p> <p>2W 10% Carbon Composition 6p each</p> <p>2½W 5% Wire wound 9p each</p> <p>5W Wire wound 9p each</p> <p>10W Wire wound 10p each</p> <p>plus p. &amp; p. 7p for up to 25 resistors plus 1p for each additional 25.</p>	<p><b>TV Electrolytics</b></p> <table border="0"> <tr> <td>1; 2; 4; 8μF</td> <td>450V</td> <td>14p</td> <td>32μF</td> <td>450V</td> <td>20p</td> </tr> <tr> <td>16μF</td> <td>450V</td> <td>15p</td> <td>50μF</td> <td>350V</td> <td>20p</td> </tr> <tr> <td>8-8μF;</td> <td>450 V.W.</td> <td>18p</td> <td>32-32μF;</td> <td>350 V.W.</td> <td>25p</td> </tr> <tr> <td>8-16μF;</td> <td>450 V.W.</td> <td>20p</td> <td>32-32μF;</td> <td>450 V.W.</td> <td>43p</td> </tr> <tr> <td>16-16μF;</td> <td>450 V.W.</td> <td>25p</td> <td>50-50μF;</td> <td>350 V.W.</td> <td>35p</td> </tr> <tr> <td>16-100-100-300μF;</td> <td>275 V.W.</td> <td>£1.23</td> <td></td> <td></td> <td></td> </tr> <tr> <td>32-100-125-200μF;</td> <td>275 V.W.</td> <td>£1.23</td> <td></td> <td></td> <td></td> </tr> <tr> <td>32-100-200-200μF;</td> <td>300 V.W.</td> <td>£1.23</td> <td></td> <td></td> <td></td> </tr> <tr> <td>100-100-100-150-150μF;</td> <td>320 V.W.</td> <td>£1.68</td> <td></td> <td></td> <td></td> </tr> <tr> <td>175 (400V)-100-100μF;</td> <td>350 V.W.</td> <td>£1.66</td> <td></td> <td></td> <td></td> </tr> <tr> <td>60-100-200μF;</td> <td>300 V.W.</td> <td>93p</td> <td></td> <td></td> <td></td> </tr> <tr> <td>100-200μF;</td> <td>275 V.W.</td> <td>75p</td> <td></td> <td></td> <td></td> </tr> <tr> <td>100-200-200μF;</td> <td>300 V.W.</td> <td>£1.11</td> <td></td> <td></td> <td></td> </tr> <tr> <td>100-400μF;</td> <td>275 V.W.</td> <td>£1.90</td> <td></td> <td></td> <td></td> </tr> <tr> <td>200μF;</td> <td>275 V.W.</td> <td>50p</td> <td>300-300μF;</td> <td>300 V.W.</td> <td>£1.90</td> </tr> </table>	1; 2; 4; 8μF	450V	14p	32μF	450V	20p	16μF	450V	15p	50μF	350V	20p	8-8μF;	450 V.W.	18p	32-32μF;	350 V.W.	25p	8-16μF;	450 V.W.	20p	32-32μF;	450 V.W.	43p	16-16μF;	450 V.W.	25p	50-50μF;	350 V.W.	35p	16-100-100-300μF;	275 V.W.	£1.23				32-100-125-200μF;	275 V.W.	£1.23				32-100-200-200μF;	300 V.W.	£1.23				100-100-100-150-150μF;	320 V.W.	£1.68				175 (400V)-100-100μF;	350 V.W.	£1.66				60-100-200μF;	300 V.W.	93p				100-200μF;	275 V.W.	75p				100-200-200μF;	300 V.W.	£1.11				100-400μF;	275 V.W.	£1.90				200μF;	275 V.W.	50p	300-300μF;	300 V.W.	£1.90	<p><b>Eliminators</b></p> <table border="0"> <tr> <td>9 volt (in 20mA (PP3))</td> <td>£1.25</td> </tr> <tr> <td>6 volt (in 50mA)</td> <td>£1.50</td> </tr> <tr> <td>9 volt (in 50mA)</td> <td>£1.50</td> </tr> <tr> <td>6-5 volt; 50mA</td> <td>£2.50</td> </tr> <tr> <td>9-9 volt; 50mA</td> <td>£2.50</td> </tr> <tr> <td>7½ volt for cassette recorders</td> <td>£2.00</td> </tr> <tr> <td>6, 7½ or 9 volt</td> <td>£3.00</td> </tr> <tr> <td>3, 4½, 6, 7½, 9, 12 " 500mA</td> <td>£3.99</td> </tr> </table> <p>Car Battery Converter fully stabilised to provide 6, 7½ or 9 volts (£4.99 (p. &amp; p. 15p on all types))</p>	9 volt (in 20mA (PP3))	£1.25	6 volt (in 50mA)	£1.50	9 volt (in 50mA)	£1.50	6-5 volt; 50mA	£2.50	9-9 volt; 50mA	£2.50	7½ volt for cassette recorders	£2.00	6, 7½ or 9 volt	£3.00	3, 4½, 6, 7½, 9, 12 " 500mA	£3.99																																																																																																																																								
AC128 15p	BC172 18p	BF184 25p																																																																																																																																																																																																																																																																																				
AC176 15p	BD115 67p	BF185 25p																																																																																																																																																																																																																																																																																				
AF239 30p	BD124 £1.01	BF194 15p																																																																																																																																																																																																																																																																																				
AF239 30p	BD131 70p	BF195 15p																																																																																																																																																																																																																																																																																				
BC107 10p	BD132 70p	BF196 15p																																																																																																																																																																																																																																																																																				
BC108 10p	BD131/2M.P. £1.48	BF197 15p																																																																																																																																																																																																																																																																																				
BC109 10p	BF115 25p	BF272 53p																																																																																																																																																																																																																																																																																				
BC147 10p	BF167 20p	BFY50 24p																																																																																																																																																																																																																																																																																				
BC148 10p	BF173 20p	BRY39 36p																																																																																																																																																																																																																																																																																				
BC149 10p	BF180 25p	BSX21 26p																																																																																																																																																																																																																																																																																				
BC171 21p	BF181 30p	BU105 £2																																																																																																																																																																																																																																																																																				
1; 2; 4; 8μF	450V	14p	32μF	450V	20p																																																																																																																																																																																																																																																																																	
16μF	450V	15p	50μF	350V	20p																																																																																																																																																																																																																																																																																	
8-8μF;	450 V.W.	18p	32-32μF;	350 V.W.	25p																																																																																																																																																																																																																																																																																	
8-16μF;	450 V.W.	20p	32-32μF;	450 V.W.	43p																																																																																																																																																																																																																																																																																	
16-16μF;	450 V.W.	25p	50-50μF;	350 V.W.	35p																																																																																																																																																																																																																																																																																	
16-100-100-300μF;	275 V.W.	£1.23																																																																																																																																																																																																																																																																																				
32-100-125-200μF;	275 V.W.	£1.23																																																																																																																																																																																																																																																																																				
32-100-200-200μF;	300 V.W.	£1.23																																																																																																																																																																																																																																																																																				
100-100-100-150-150μF;	320 V.W.	£1.68																																																																																																																																																																																																																																																																																				
175 (400V)-100-100μF;	350 V.W.	£1.66																																																																																																																																																																																																																																																																																				
60-100-200μF;	300 V.W.	93p																																																																																																																																																																																																																																																																																				
100-200μF;	275 V.W.	75p																																																																																																																																																																																																																																																																																				
100-200-200μF;	300 V.W.	£1.11																																																																																																																																																																																																																																																																																				
100-400μF;	275 V.W.	£1.90																																																																																																																																																																																																																																																																																				
200μF;	275 V.W.	50p	300-300μF;	300 V.W.	£1.90																																																																																																																																																																																																																																																																																	
9 volt (in 20mA (PP3))	£1.25																																																																																																																																																																																																																																																																																					
6 volt (in 50mA)	£1.50																																																																																																																																																																																																																																																																																					
9 volt (in 50mA)	£1.50																																																																																																																																																																																																																																																																																					
6-5 volt; 50mA	£2.50																																																																																																																																																																																																																																																																																					
9-9 volt; 50mA	£2.50																																																																																																																																																																																																																																																																																					
7½ volt for cassette recorders	£2.00																																																																																																																																																																																																																																																																																					
6, 7½ or 9 volt	£3.00																																																																																																																																																																																																																																																																																					
3, 4½, 6, 7½, 9, 12 " 500mA	£3.99																																																																																																																																																																																																																																																																																					
<p><b>Diodes &amp; Rectifiers</b></p> <table border="0"> <tr> <td>AA119 9p</td> <td>BA156 15p</td> <td>BY176 £1.50</td> </tr> <tr> <td>AA120 9p</td> <td>BA243 56p</td> <td>BY182 £1.50</td> </tr> <tr> <td>AA129 9p</td> <td>OA47 10p</td> <td>BY250 23p</td> </tr> <tr> <td>BA102 25p</td> <td>OA73 9p</td> <td>IN4001 6p</td> </tr> <tr> <td>BA115 17p</td> <td>OA90 7p</td> <td>IN4002 7p</td> </tr> <tr> <td>BA130 10p</td> <td>OA91 7p</td> <td>IN4003 8p</td> </tr> <tr> <td>BA145 20p</td> <td>OA200 10p</td> <td>IN4004 8p</td> </tr> <tr> <td>BA148 20p</td> <td>BY100 15p</td> <td>IN4005 10p</td> </tr> <tr> <td>BA154 13p</td> <td>BY126 15p</td> <td>IN4006 12p</td> </tr> <tr> <td>BA155 14p</td> <td>BY127 15p</td> <td>IN4007 15p</td> </tr> </table>	AA119 9p	BA156 15p	BY176 £1.50	AA120 9p	BA243 56p	BY182 £1.50	AA129 9p	OA47 10p	BY250 23p	BA102 25p	OA73 9p	IN4001 6p	BA115 17p	OA90 7p	IN4002 7p	BA130 10p	OA91 7p	IN4003 8p	BA145 20p	OA200 10p	IN4004 8p	BA148 20p	BY100 15p	IN4005 10p	BA154 13p	BY126 15p	IN4006 12p	BA155 14p	BY127 15p	IN4007 15p	<p><b>Power Sections</b></p> <p>ohms</p> <table border="0"> <tr> <td>7, 9, 10, 12, 14, 17, 5, 20</td> <td>in 700mA 20p</td> </tr> <tr> <td>22, 25, 28, 30, 33, 36</td> <td>in 700mA 25p</td> </tr> <tr> <td>40, 47, 52, 56, 60, 63, 66</td> <td>in 300mA 20p</td> </tr> <tr> <td>75, 87, 100, 120, 140, 160</td> <td>in 300mA 25p</td> </tr> <tr> <td>180, 200, 220, 250, 270</td> <td>in 300mA 25p</td> </tr> <tr> <td>300, 350, 400, 470, 560</td> <td>in 120mA 20p</td> </tr> <tr> <td>726</td> <td>in 150mA 25p</td> </tr> <tr> <td>1KΩ</td> <td>in 100mA 20p</td> </tr> <tr> <td>2KΩ</td> <td>in 70mA 25p</td> </tr> </table> <p>plus p. &amp; p. 7p per section.</p>	7, 9, 10, 12, 14, 17, 5, 20	in 700mA 20p	22, 25, 28, 30, 33, 36	in 700mA 25p	40, 47, 52, 56, 60, 63, 66	in 300mA 20p	75, 87, 100, 120, 140, 160	in 300mA 25p	180, 200, 220, 250, 270	in 300mA 25p	300, 350, 400, 470, 560	in 120mA 20p	726	in 150mA 25p	1KΩ	in 100mA 20p	2KΩ	in 70mA 25p	<p><b>Presets</b></p> <p>Vertical or Horizontal</p> <table border="0"> <tr> <td>0.25 watt 5p</td> <td>0.25 watt 7p</td> </tr> <tr> <td>100</td> <td>1K</td> </tr> <tr> <td>100</td> <td>10K</td> </tr> <tr> <td>250</td> <td>2.5K</td> </tr> <tr> <td>500</td> <td>5K</td> </tr> <tr> <td></td> <td>50K</td> </tr> <tr> <td></td> <td>100K</td> </tr> <tr> <td></td> <td>250K</td> </tr> <tr> <td></td> <td>500K</td> </tr> <tr> <td></td> <td>1M</td> </tr> <tr> <td></td> <td>2.5M</td> </tr> <tr> <td></td> <td>5M</td> </tr> </table>	0.25 watt 5p	0.25 watt 7p	100	1K	100	10K	250	2.5K	500	5K		50K		100K		250K		500K		1M		2.5M		5M	<p><b>Presets</b></p> <p>Vertical or Horizontal</p> <table border="0"> <tr> <td>0.25 watt 5p</td> <td>0.25 watt 7p</td> </tr> <tr> <td>100</td> <td>1K</td> </tr> <tr> <td>100</td> <td>10K</td> </tr> <tr> <td>250</td> <td>2.5K</td> </tr> <tr> <td>500</td> <td>5K</td> </tr> <tr> <td></td> <td>50K</td> </tr> <tr> <td></td> <td>100K</td> </tr> <tr> <td></td> <td>250K</td> </tr> <tr> <td></td> <td>500K</td> </tr> <tr> <td></td> <td>1M</td> </tr> <tr> <td></td> <td>2.5M</td> </tr> <tr> <td></td> <td>5M</td> </tr> </table>	0.25 watt 5p	0.25 watt 7p	100	1K	100	10K	250	2.5K	500	5K		50K		100K		250K		500K		1M		2.5M		5M																																																																																																																																																																																			
AA119 9p	BA156 15p	BY176 £1.50																																																																																																																																																																																																																																																																																				
AA120 9p	BA243 56p	BY182 £1.50																																																																																																																																																																																																																																																																																				
AA129 9p	OA47 10p	BY250 23p																																																																																																																																																																																																																																																																																				
BA102 25p	OA73 9p	IN4001 6p																																																																																																																																																																																																																																																																																				
BA115 17p	OA90 7p	IN4002 7p																																																																																																																																																																																																																																																																																				
BA130 10p	OA91 7p	IN4003 8p																																																																																																																																																																																																																																																																																				
BA145 20p	OA200 10p	IN4004 8p																																																																																																																																																																																																																																																																																				
BA148 20p	BY100 15p	IN4005 10p																																																																																																																																																																																																																																																																																				
BA154 13p	BY126 15p	IN4006 12p																																																																																																																																																																																																																																																																																				
BA155 14p	BY127 15p	IN4007 15p																																																																																																																																																																																																																																																																																				
7, 9, 10, 12, 14, 17, 5, 20	in 700mA 20p																																																																																																																																																																																																																																																																																					
22, 25, 28, 30, 33, 36	in 700mA 25p																																																																																																																																																																																																																																																																																					
40, 47, 52, 56, 60, 63, 66	in 300mA 20p																																																																																																																																																																																																																																																																																					
75, 87, 100, 120, 140, 160	in 300mA 25p																																																																																																																																																																																																																																																																																					
180, 200, 220, 250, 270	in 300mA 25p																																																																																																																																																																																																																																																																																					
300, 350, 400, 470, 560	in 120mA 20p																																																																																																																																																																																																																																																																																					
726	in 150mA 25p																																																																																																																																																																																																																																																																																					
1KΩ	in 100mA 20p																																																																																																																																																																																																																																																																																					
2KΩ	in 70mA 25p																																																																																																																																																																																																																																																																																					
0.25 watt 5p	0.25 watt 7p																																																																																																																																																																																																																																																																																					
100	1K																																																																																																																																																																																																																																																																																					
100	10K																																																																																																																																																																																																																																																																																					
250	2.5K																																																																																																																																																																																																																																																																																					
500	5K																																																																																																																																																																																																																																																																																					
	50K																																																																																																																																																																																																																																																																																					
	100K																																																																																																																																																																																																																																																																																					
	250K																																																																																																																																																																																																																																																																																					
	500K																																																																																																																																																																																																																																																																																					
	1M																																																																																																																																																																																																																																																																																					
	2.5M																																																																																																																																																																																																																																																																																					
	5M																																																																																																																																																																																																																																																																																					
0.25 watt 5p	0.25 watt 7p																																																																																																																																																																																																																																																																																					
100	1K																																																																																																																																																																																																																																																																																					
100	10K																																																																																																																																																																																																																																																																																					
250	2.5K																																																																																																																																																																																																																																																																																					
500	5K																																																																																																																																																																																																																																																																																					
	50K																																																																																																																																																																																																																																																																																					
	100K																																																																																																																																																																																																																																																																																					
	250K																																																																																																																																																																																																																																																																																					
	500K																																																																																																																																																																																																																																																																																					
	1M																																																																																																																																																																																																																																																																																					
	2.5M																																																																																																																																																																																																																																																																																					
	5M																																																																																																																																																																																																																																																																																					
<p><b>EHT Rectifier Trays</b></p> <p>(5 stick version) for BRG Chassis i.e. Ferguson, Ultra, Marconiphone &amp; HMV - 950 Mk.II, 960, 970 &amp; 1400 chassis Our Price £3.50 plus p. &amp; p. 20p</p>	<p><b>Mains Droppers</b></p> <table border="0"> <tr> <td>(1) 37Ω - 31Ω - 97Ω - 26Ω - 168Ω</td> <td>50p</td> </tr> <tr> <td>(2) 14Ω - 26Ω - 97Ω - 173Ω</td> <td>50p</td> </tr> <tr> <td>(3) 30Ω - 125Ω - 2.85KΩ</td> <td>50p</td> </tr> </table> <p>plus p. &amp; p. 7p per dropper.</p>	(1) 37Ω - 31Ω - 97Ω - 26Ω - 168Ω	50p	(2) 14Ω - 26Ω - 97Ω - 173Ω	50p	(3) 30Ω - 125Ω - 2.85KΩ	50p	<p><b>Eliminators</b></p> <p>9 volt (in 20mA (PP3)) £1.25</p> <p>6 volt (in 50mA) £1.50</p> <p>9 volt (in 50mA) £1.50</p> <p>6-5 volt; 50mA £2.50</p> <p>9-9 volt; 50mA £2.50</p> <p>7½ volt for cassette recorders £2.00</p> <p>6, 7½ or 9 volt £3.00</p> <p>3, 4½, 6, 7½, 9, 12 " 500mA £3.99</p> <p>Car Battery Converter fully stabilised to provide 6, 7½ or 9 volts (£4.99 (p. &amp; p. 15p on all types))</p>	<p><b>MAIL ORDERS</b> Where no p. &amp; p. charge is shown, a minimum of 7p applies. p. &amp; p. on overseas orders is charged at cost.</p> <p><b>ADDRESS TO:</b> TV Component Dept. 56, Fortis Green Road, London, N10 3HN. Telephone: 01-883 3705</p>																																																																																																																																																																																																																																																																													
(1) 37Ω - 31Ω - 97Ω - 26Ω - 168Ω	50p																																																																																																																																																																																																																																																																																					
(2) 14Ω - 26Ω - 97Ω - 173Ω	50p																																																																																																																																																																																																																																																																																					
(3) 30Ω - 125Ω - 2.85KΩ	50p																																																																																																																																																																																																																																																																																					

**CHROMASONIC electronics**

PLEASE ADD V.A.T.

MAIL ORDERS Where no p. & p. charge is shown, a minimum of 7p applies. p. & p. on overseas orders is charged at cost.

ADDRESS TO: TV Component Dept. 56, Fortis Green Road, London, N10 3HN. Telephone: 01-883 3705

**COLOUR TUBES  
STANDARD  
TUBES**

**METAL BAND  
TUBES**

**TWIN PANEL  
TUBES**


Rebuilt with new Electron Guns to British Standard 415/1/1967.

**SUFFOLK TUBES  
LIMITED**

261 CHURCH ROAD  
MITCHAM, SURREY CR4 3BH  
01-640 3133/4/5

Britain's Largest Independent TV Tube Rebuilder

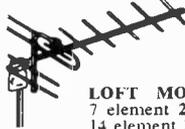**U.H.F. T.V. AERIALS**  
SUITABLE FOR COLOUR AND MONO-CHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

**LOFT MOUNTING ARRAYS**  
7 element 2.25, 11 element 2.75, 14 element 3.25, 18 element 3.75.

**WALL MOUNTING c.w WALL ARM & BRACKET**  
7 element 3.25, 11 element 3.75, 14 element 4.25, 18 element 4.75.

**CHIMNEY MOUNTING ARRAYS c.w MAST & LASHING KIT.** 7 element 4.00, 11 element 4.50, 14 element 4.75, 18 element 5.25.

**MAST MOUNTING arrays only.** 7 element 2.25, 11 element 2.75, 14 element 3.25, 18 element 3.75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd. KING TELEBOOSTERS from 3.75.

**LABGEAR PRE-AMPS 4.25.**

**BELLING LEE CONCORD BOOSTER** V.H.F., F.M., U.H.F., mains operated 8.20. State clearly channel number required on all orders P. p. on all aerials 50p, Accs. 15p. C.W.O. Min. C.O.D. charge 25p.

**F.M. Radio Aerials**

F.M. RADIO loft S/D 1.00 3 element 3.25, 4 element 3.50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P.p. all aerials 50p, Accs. 30p. C.W.O. Min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED  
OPEN ALL DAY SATURDAY

**K.V.A. ELECTRONICS**  
40-41 MONARCH PARADE, LONDON ROAD, MITCHAM, SURREY  
Telephone 01-648 4884

**REBUILT  
COLOUR TUBES**

19"	£22.50	22"	£25.00
25"	£27.00	26"	£28.00

Exchange prices: Tubes supplied without exchange glass at extra cost, subject to availability.

Colour Tubes demonstrated to callers. Carriage extra all types.

New RCA Type A49-15X: £30.00

Full range of rebuilt mono tubes available, Standard, Rimband and Twin Panel

- \* Complete new gun fitted to every tube.
- \* 2 years' guarantee mono-chrome, 1 year colour.
- \* 15 years' experience in tube rebuilding.
- \* Trade enquiries welcomed.

**N.G.T. ELECTRONICS LTD.**  
(Nu Gun Teletubes)

22-24, Anerley Station Road, London S.E.20.

Telephone: 01-778 9178.

# LAWSON BRAND NEW TELEVISION TUBES



**SPECIFICATION:** The Lawson range of new television tubes are designed to give superb performance, coupled with maximum reliability and very long life. All tubes are the products of Britain's major C.R.T. manufacturers, and each tube is an exact replacement. Tubes are produced to the original specifications but incorporate the very latest design improvements such as: High Brightness Maximum Contrast Silver Activated Screens, Micro-Fine Aluminising, Precision Aligned Gun Jigging, together with Ultra Hard R.F. High Vacuum Techniques.

## DIRECT REPLACEMENTS FOR MULLARD-MAZDA BRIMAR GEC, ETC.

A47-11W	MW43-69	C21/KM	CME2302	7601A
A47-13W	MW43-80	C23/7A	CME2303	7701A
A47-14W	MW52/20	C23/10	CME2305	A50-120W/R
A47-17W	AW47-97	C23/AK	CME2306	MW36/24
A47-18W	AW59-90	CME1601	CME2308	MW36/44
A47-26W	AW59-91	CME1602	CRM172	CRM141
A59-11W	C17/1A	CME1702	CRM173	
A59-12W	C17/5A	CME1703	CRM211	
A59-13W	C17/7A	CME1705	23SP4	
A59-14W	C17/AA	CME1706	171K	
A59-15W	C17/AF	CME1901	172K	
A59-14W	C17/FM	CME1902	173K	
AW43-80	C17/5M	CME1903	212K	
AW43-88	C19/10AP	CME1905	7405A	
AW43-89	C19/AK	CME1906	7406A	
AW47-90	C21/1A	CME1908	7502A	
AW47-91	C21/7A	CME2104	7503A	
MW43-64	C21/AF	CME2301	7504A	

## REBUILT TUBES

**LAWSON "RED LABEL" CRTS** are particularly useful where cost is a vital factor, such as in older sets or rental use. Lawson "Red Label" CRTS are completely rebuilt from selected glass, direct replacements and guaranteed for two years.

	New Tubes £	Red Label £	Colour Tubes old glass not required
14"	3-85	—	
17"	6-87	5-47	19" £43-45
19"	7-97	5-77	
21"	9-35	7-65	22" £47-85
23"	10-70	7-97	
19" Twin Panel	11-28	9-07	25" £52-25
23" Twin Panel	17-05	10-72	
16" Panorama	9-35	—	26" £54-45
19" Panorama	10-32	7-65	
20" Panorama	11-55	—	carr. £1-65
23" Panorama	13-15	9-63	

### LAWSON TUBES

18 CHURCHDOWN ROAD,  
MALVERN, WORCS.  
Malvern 2100

### 2 YEARS' GUARANTEE FULL TUBE FITTING INSTRUCTIONS

Tubes are despatched day of order by passenger train, road or goods taking far too long for customers satisfaction.

Carriage/Insurance: 14"-19" 68p. 20"-23" 82p  
All the above prices include V.A.T.

TO CLEAR

# MUST GO!

NEW BOXED  
VALVES  
GUARANTEED

Cheapest  
Available  
Anywhere

**PCC84**  
EBF80  
ECC40  
30C17

**20p**  
EACH  
plus  
5p p. & p.  
OVER 2  
POST  
FREE

PC86  
PC88  
PY82  
PL84  
EBF89  
ECL80  
6F23  
6AK5  
ECC91

**25p**  
EACH  
plus  
5p p. & p.  
OVER 2  
POST  
FREE

EF92  
PC97  
PCF201  
PC95  
PL81  
PCC805  
PCF806

**25p**  
EACH  
plus  
5p p. & p.  
OVER 2  
POST  
FREE

SEND PO, CHEQUE or MO to:

100 OF ABOVE ASSORTED T.V. VALVES £10.00 + 50p P. & P.  
MINIMUM ORDER £1.00

**SOUTHERN MACHINE SERVICES** DEPT 285 MORLAND ROAD  
PT CROYDON, SURREY, CRO 6HE

Telephone 01-653 4863  
or 01-656 0374

# BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX  
All prices inclusive of V.A.T. Telephone 6743

0A2	0-30	6AQ5	0-21	6F18	0-45	7AN7	0-27	19H1	2-00	3S25GT	3-00	CV63	0-53
OB2	0-30	6AR5	0-30	6F23	0-65	7B6	0-58	20D1	0-49	50B5	0-35	CY1C	0-53
OZ4	0-25	6AR6	1-00	6F24	0-68	7B7	0-32	20D4	1-05	50C5	0-32	CY31	0-29
LA3	0-23	6AT6	0-18	6F25	0-51	7B8	0-88	20P2	0-65	50C6D6G2	1-7	D43	0-20
LA5	0-25	6AU6	0-19	6F28	0-60	7H7	0-28	20L1	0-88	50E8	0-55	DAF91	0-20
LAGT	0-22	6AV6	0-28	6F32	1-15	7B7	0-25	20P1	0-50	50L5GT	4-5	DAF92	0-20
LB3GT	0-35	6AW8A	0-54	6G85A	0-30	7V7	0-25	20P3	0-78	72	0-33	DAF96	0-33
LD5	0-38	6AX4	0-39	6GK5	0-50	7Y4	0-60	20P4	0-89	85A2	0-43	DC90	0-60
LD6	0-48	6B8G	0-13	6GU7	0-50	7Z4	0-50	20P5	1-00	85A3	0-40	DD4	0-53
LG6	0-30	6BA6	0-19	6HG6T	0-15	9BW6	0-50	25A6G	0-29	90AG	3-38	DF33	0-37
LH5GT	0-33	6BC8	0-50	6J6G	0-19	9D7	0-78	25L6G	0-20	90AV	3-38	DF96	0-34
LL4	0-13	6BE6	0-20	6J6GT	0-29	10C2	0-49	25V5	0-38	90CG	1-70	DH76	0-28
LLD5	0-30	6BG6G	1-05	6J75	0-18	10D5T	0-50	25V5G	0-43	90CV	1-68	DH77	0-18
LLN5	0-40	6BI6	0-43	6J7G	0-24	10F1	0-75	25Z4G	0-28	90F1	0-59	DH81	0-58
LN5GT	0-37	6BI6	0-39	6J7M	0-38	10F9	0-45	25Z5	0-40	150B2	1-58	DK32	0-32
LR5	0-26	6BR7A	0-50	6J7U8A	0-50	10I18	0-35	25Z6GT	4-3	301	1-00	DK40	0-55
LR4	0-22	6BQ5	0-21	6K7G	0-12	10LD11	0-53	25D7	0-34	302	0-83	DK91	0-28
LR5	0-20	6BQ7A	0-38	6K8G	0-33	10L13	0-54	30A5	0-44	303	0-75	DK92	0-49
LU4	0-29	6BR7	0-79	6L1	0-98	10L14	1-08	30C1	0-26	305	0-83	DK96	0-43
LU5	0-48	6BR8	0-63	6L6GT	0-50	12A6	0-63	30C15	0-55	306	0-65	DL33	0-35
LD21	0-35	6BR7	0-43	6J7G	0-24	10F1	0-75	25Z4G	0-28	90F1	0-59	DL92	0-23
2K5	0-50	6BW6	0-72	6L12	0-32	12AD6	0-40	30C18	0-69	1821	0-53	DL96	0-35
2A4	0-25	6BW7	0-50	6L18	0-44	12AE8	0-48	30F5	0-61	4033X	1-25	DM70	0-30
3B7	0-25	6BZ6	0-31	6L19	1-38	12AT6	0-23	30FL1	0-58	5702	0-80	DM71	0-50
3D6	0-19	6C4	0-28	6LD12	0-29	12A77	0-16	30FL2	0-60	6060	0-30	DW4/500	0-38
3Q4	0-38	6C6	0-19	6LD20	0-48	12AU7	0-21	30FL12	0-67	7193	0-53	DY87/6	0-22
3Q5GT	0-35	6C9	0-73	6NT6T	0-40	12AU7	0-19	30FL13	0-47	7475	0-70	E80C	1-65
3S4	0-26	6C12	0-25	6P15	0-21	12A76	0-44	30L14	0-74	807	0-59	E80F	1-20
3C8	0-50	6C17	0-63	6P28	0-59	12AX7	0-21	30L1	0-27	A2134	0-98	E80F	1-20
3C9	0-50	6CB6A	0-26	6Q7G	0-35	12BA6	0-30	30L15	0-65	A3042	0-75	E80F	1-20
5R4GY	0-53	6CD6G	1-06	6Q7M	0-43	12BE6	0-27	30L17	0-65	AC2/PEN	0-98	E80F	1-20
5T4	0-30	6CG8A	0-50	6Q7GT	0-43	12BH7	0-27	30P4MR	0-95	0-98	0-98	E80F	1-20
5U4G	0-30	6CL6	0-43	6R7	0-55	12J6GT	0-30	30P12	0-69	AC6PEN	0-38	E80F	1-20
5V4G	0-33	6CLA	0-50	6R7G	0-35	12J7GT	0-33	30P16	0-28	AC2/PEN	0-98	E80F	1-20
5Y3GT	0-30	6CM7	0-50	6RAT	0-35	12K5	0-23	30P17	0-4	TD	0-98	E80F	1-20
5Z2	0-45	6CJ5	0-30	6S7GT	0-33	12K7GT	0-34	30P4	0-65	AC/PEN	0-7	E80F	1-20
5Z4G	0-33	6CW4	0-63	6S8G	0-33	12Q7GT	0-28	30PL1	0-57	0-98	0-98	E80F	1-20
5Z4GT	0-38	6D3	0-38	6SH7	0-35	12SA7GT	0-40	30PL12	0-29	AC/TH1	0-5	E80F	1-20
6/30L2	0-35	6D6	0-15	6S7	0-35	12SC7	0-35	30PL13	0-75	AC/TP	0-98	E80F	1-20
6A8G	0-33	6DE7	0-50	6SK7GT	0-23	12S6GT	0-23	30PL14	0-75	AL69	0-78	E80F	1-20
6AC7	0-15	6DT6A	0-50	6S7GT	0-38	12S7H	0-15	30PL15	0-67	ARF3	0-35	E80F	1-20
6AG5	0-25	6E9W6	0-55	6S4GT	0-60	12S7	0-23	35E1	0-6	ATP4	0-40	E80F	1-20
6AH6	0-50	6E5	0-55	6U7G	0-63	12S7K	0-24	35A3	0-48	AZ1	0-40	E80F	1-20
6AJ5	0-75	6F1	0-59	6V6G	0-17	12SQ7GT	0-50	35A5	0-75	AZ31	0-40	E80F	1-20
6AK5	0-25	6F6	0-63	6V6GT	0-27	14H7	0-48	35D5	0-70	AZ41	0-53	E80F	1-20
6AK6	0-30	6F6G	0-35	6X4	0-20	14H7	0-75	35L6GT	0-42	B36	0-30	E80F	1-20
6AM6	0-17	6F13	0-33	6X5GT	0-25	19A9G	0-24	35W4	0-23	B319	0-27	E80F	1-20
6AM8A	0-50	6F14	0-40	6Y6G	0-55	19B9G	0-80	35Z3	0-50	CL33	0-90	E80F	1-20
6AN8	0-49	6F15	0-65	6Y7G	0-63	19G6	0-50	35Z4GT	0-24	CV6	0-53	E80F	1-20

EB34	0-20	EF83	0-54	GZ33	0-70	PCF87	0-74	PY301	0-65	UU12	0-20		
EB91	0-10	EF85	0-25	GZ34	0-47	PCF200	0-67	PY800	0-31	UY41	0-38		
EBC41	0-48	EF86	0-27	GZ37	0-67	PCF800	0-55	PY801	0-31	UY85	0-23		
EBC81	0-29	EF89	0-23	HABC80	0-44	PCF801	0-28	PZ30	0-48	U10	0-45		
EB90	0-18	EF91	0-17	HL23DD	0-40	PCF802	0-37	QQV03/1	0-12/14	0-38	0-38		
EB91	0-28	EF92	0-29	HL45D	0-38	PCF805	0-62	R16	1-30	U16	0-70		
EBF80	0-30	EF97	0-55	HL4DD	0-50	PCF806	0-55	QF75/20	0-63	U17	0-85		
EBF83	0-38	EF98	0-65	HN309	1-40	PCF808	0-65	Q895/10	0-48	U19	0-75		
EBF89	0-26	EF183	0-25	HVR2	0-53	PCH200	0-62	QCL80/15	0-19	U20	0-78		
EBL21	0-60	EF184	0-27	HVR2A	0-53	PCL82	0-29	0-63	U22	0-39	0-39		
EC34	0-50	EFP60	0-50	IW3	0-38	PCL83	0-54	QV04/7	0-63	U25	0-65		
EC68	0-59	EH90	0-34	IW4/350	0-38	PCL84	0-32	R11	0-98	U26	0-60		
EC82	0-20	EM92	0-27	IW4/500	0-38	PCL805/19	0-37	R20	0-60	U27	0-60		
EC92	0-34	EL34	0-48	KT6	0-25	0-37	R17	0-88	U33	1-50	1-50		
ECC32	1-50	EL35	1-00	KT8	1-75	PCL86	0-36	R18	0-50	U35	0-83		
ECC33	1-50	EL37	0-74	KT41	0-98	PCL88	0-75	R19	0-28	U37	1-75		
ECC35	0-95	EL41	0-53	KT44	1-00	PCL800	0-75	R20	0-60	U45	0-78		
ECC40	0-68	EL81	0-50	KT63	0-35	PCL801	0-57	R52	0-33	U47	0-65		
ECC81	0-16	EL83	0-38	KT66	0-80	PD400	1-44	RK34	0-38	U49	0-60		
ECC82	1-19	EL84	0-21	KT74	0-63	0-98	U48	SP61	0-75	U50	0-60		
ECC83	0-21	EL85	0-38	KT76	0-63	1-38	TH4B	0-50	U52	0-30	0-30		
ECC84	0-28	EL86	0-38	KT81	2-00	PEN45	0-40	TH233	0-98	U76	0-24		
ECC85	0-32	EL91	0-23	KTW61	0-63	PEN46	0-20	TP2620	0-98	U78	0-20		
ECC86	0-40	EL95	0-32	KTW62	0-63	0-75	UABCR30	0-30	U191	0-65	0-65		
ECC88	0-35	EL360	0-48	KTW63	0-50	PEN46	0-20	UAF42	0-49	U193	0-31		
ECC89	0-48	ELL80	0-75	LZ339	0-55	PEN46	0-20	UBC41	0-45	U251	0-62		
ECC804	0-53	EM80	0-37	M8182	0-63	PEN483DD	0-98	UBC81	0-40	U281	0-30		
ECC807	1-00	EM82	0-37	M8184	0-75	0-98	U80	UB81	0-35	U282	0-40		
ECCF80	0-27	EM83	0-75	MHL06	0-75	PEN4A	0-98	UB81	0-33	U301	0-40		
ECCF82	0-25	EM84	0-31	MX40	0-50	PEN/DD/	0-98	UB21	0-55	U403	0-33		
ECCF86	0-64	EM85	1-00	N308	0-95	4020	0-88	UC92	0-35	U404	0-38		
ECCF804	0-20	EM87	0-49	N339	0-40	PFL200	0-50	UC84	0-33	U801	0-76		
ECH21	0-63	EY51	0-35	N359	0-42	PL33	0-38	UC80	0-33	U920	0-38		
ECH35	0-50	EY81	0-35	P61	0-40	PL36	0-46	UCF85	0-31	U1392	0-35		
ECH42	0-57	EY83	0-35	PKC80	0-42	PL81	0-42	UCF80	0-30	VP23	0-40		
ECH81	0-25	EY84	0-50	PC86	0-44	PL81A	0-48	UCH49	0-57	VP41	0-38		
ECH83	0-38	EY87/6	0-27	PC88	0-44	PL82	0-28	UCH81	0-29	VT61A	0-35		
ECH84	0-34	EY88	0-40	PC85	0-53	PL83	0-30	UCL82	0-30	UV111	0-44		
ECL80	0-28	EY91	0-53	PC97	0-38	PL84	0-28	UCL83	0-54	UV120	0-60		
ECL82	0-28	EZ35	0-25	PC90	0-29	PL302	0-65	UP41	0-50	UV120A	0-80		
ECL83	0-52	EZ40	0-40	PCC84	0-57	PL504/500	0-60	UP42	0-60	UV133	0-35		
E92CC	0-40	EZ41	0-60	PC85	0-24	0-60	U80	U80	0-35	W1	0-34		
E180F	0-90	EZ80	0-19	PCC88	0-39	PL508	0-90	UF85	0-34	W107	0-50		
E182CC	1-00	EZ81	0-20	PCC89	0-42	PL820	0-75	UF86	0-63	W279	0-60		
E148	0-53	E800	0-60	PW4/500	0-75	PCC8189	0-46	PM84	0-31	UF89	0-27		
EA50	0-27	EF22	0-63	0-75	PCC805	0-55	PY33/2	0-50	U41	0-54	X63	0-33	
EA76	0-88	EF40	0-49	FW4/800	PCC806	0-65	PY80	0-33	UL84	0-28	X66	0-50	
EAC80	0-29	EF41	0-58	0-75	PCF80	0-58	Y81	0-24	UM50	0-33	X65	0-50	
EAC31	0-38	EF42	0-33	0-33	GY501	0-37	PY82	0-30	URIC	0-53	XH15	0-48	
EAF42	0-48	EF73	0-75	GZ30	0-33	PCF84	0-40	Y83	0-28	UY	0-38	Z329	0-61
EAF801	0-50	EF80	0-										

# Service Engineers



GLASGOW  
041-887 4949

WHEREVER YOU ARE FOR BY  
RETURN DESPATCH. WILLOW  
VALE IS AS NEAR AS YOUR  
PHONE. . . .



SOMERSET  
045-84 2597

LONDON  
01-567 5400  
01-567 2971

## STOCKISTS OF GENUINE MANUFACTURERS SPARES FOR:-

RANK BUSH MURPHY LTD. C.E.S. LTD. PYE.  
PHILIPS INVICTA. PAM. EKCO. FERRANTI.  
BRITISH RADIO CORPORATION. FERGUSON.  
ULTRA. MARCONI. HIS MASTERS VOICE.

STOCKISTS OF "TELEPART" SPARES FOR:-  
DECCA. K.B. GEC. SOBELL. MASTERADIO.  
R.G.D. etc.

LINE OUTPUT TRANSFORMERS  
EHT RECTIFIER TRAYS  
SCAN COIL ASSEMBLIES  
FRAME AND SOUND OUTPUTS  
DROPPER SECTIONS

MONOCHROME & COLOUR



HUGH RANGE OF:-

ENTERTAINMENT VALVES up to 48% DISCOUNT  
TRANSISTORS AND INTEGRATED CIRCUITS  
COMPONENTS. CAPS. RESISTORS. V/CONTROLS. PRESETS.  
VALVE BASES. SLIDERS. A/E PANELS. BIAS and SMOOTHING  
ELECTROLYTICS. etc.

CATHODE RAY TUBES. NEW and REBUILT. MONO and  
COLOUR FROM TVETTE TO 26" COLOUR. ALL TYPES.

METERS AND TEST EQUIPMENT. Servisol, Electrolube,  
Multicore, Service Tools.

FOR "BY RETURN" SERVICE CONTACT  
THE SPECIALIST WHOLESALERS:-

## willow vale electronics ltd

4&5 THE BROADWAY, HANWELL, LONDON W7

or

74 MAXWELLTON RD, PAISLEY, RENFREW

or

42 WEST END, STREET, SOMERSET

I would like a free copy of your catalogue

NAME .....

ADDRESS .....

P.T.

HOT LINES: LONDON 01 -567 5400  
GLASGOW 041-887 4949  
SOMERSET 045-84 2597

NO RETAIL ENQUIRIES  
SEND FOR FREE COPY OF OUR 64-PAGE CATALOGUE  
STRICTLY WHOLESALE ONLY

# TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

VOL 23 No 9  
ISSUE 273

JULY 1973

## RTRA's BOURNEMOUTH JAUNT

SEVERAL topics that I have commented on in recent issues inevitably raised their heads at the recent Radio and Television Retailers' Association symposium, conference and exhibition at Bournemouth. From the consumer's angle one of the main problems is ability to receive programmes in difficult areas, and although the rapid erection of some hundreds of main transmitters and relay stations for the u.h.f. bands is providing the predicted coverage this seems as if it will be limited to about 96 per cent of the population. There appears to be some disagreement over the exact proportion of the population that will not be catered for by the present predicted service but at four per cent this amounts to more than two million people and in the region of five million pounds' worth of colour license revenue or three million pounds in monochrome terms. The areas mainly concerned are of course in Scotland, Wales, Northern Ireland and rural England and it is good news that the government has decided to set up a study group to report on this. But it seems rather late in the day to be doing so.

The Conference produced a number of other interesting forecasts. In particular a rapid escalation in the use of i.c.s in colour receivers seems likely in the immediate future, while UK setmakers now seem poised ready to switch over to colour chassis designed around 110° tubes.

The servicing and servicing aids exhibition RadTelDex '73 held in conjunction with the RTRA conference was a worthwhile idea well supported by the industry. It does not however seem to have received the interest expected amongst dealers, which is a pity. Does this mean they don't have any problems, or that they are not interested in them? We hope the latter is not the case.

Perhaps one reason for the lack of support is the number of exhibitions occurring at roughly the same time. Following the RTRA's Bournemouth jaunt we have had the RECMF Components Exhibition and the annual Trade Shows running concurrently in London. All this is a bit much to digest in such a short period and indicates the need for some urgent liaison between conference/exhibition organisers. There is only a limited time that those in the trade can take off to attend these various activities and everyone loses out if they are heaped on top of each other at a busy period of the year.

M. A. COLWELL, *Editor*

## THIS MONTH

Teletopics	390
Colour Receiver Insight—Korting 51763 Series <i>by S. George</i>	392
Fault Finding Guide—5: IF Panel, Bush TV141 Series <i>by John Law</i>	396
DC Restorer Circuit <i>by Keith Cummins</i>	399
Service Notebook <i>by G. R. Wilding</i>	400
The TELEVISION Colour Receiver—Part 16— Module Interconnections	402
Renovating the Rentals—Part 15—Philips G6 Colour Chassis Part I <i>by Caleb Bradley, B.Sc.</i>	406
Workshop Hints:Tuning Capacitor Gangs <i>by Vivian Capel</i>	410
Letters	412
Long-Distance Television <i>by Roger Bunney</i>	413
Servicing Television Receivers—BRC 1580 Chassis continued <i>by L. Lawry-Johns</i>	416
Sizing up the Electron <i>by I. R. Sinclair</i>	420
Your Problems Solved	423
Test Case 127	425

THE NEXT ISSUE DATED AUGUST  
WILL BE PUBLISHED JULY 16

Cover: Our cover photograph this month shows a section of the Philips G6 colour chassis, with the decoder board above left and the i.f. board below left.

# TELETOPICS



## INSTANT NEWS VIA TV

It looks as if the time when the broadcasting authorities will provide an instant news service during their normal TV transmission times may not be far off. This seems to us a most worthwhile extension of the TV service. The basic idea is that information is transmitted in digitally coded form during certain field blanking periods. A receiver attachment decodes and stores the information which consists of a number of pages that can be individually selected and fed to the c.r.t. for display in alphanumeric form on the screen. The viewer can thus at the touch of a button display on his screen a wide selection of news reports which are being continually updated. The first such system to be announced was the BBC's Ceefax system which we mentioned in this column last January. We have now heard that IBA engineers have developed and demonstrated a similar system which they call "Oracle". This system would enable the viewer to receive up to 50 different pages of information, each page containing up to 880 characters or roughly 120 words. When a page is selected by means of a control unit it is automatically "written" on the screen of the receiver. Neither Oracle nor Ceefax affect normal television programme reception.

The IBA has been radiating its Oracle experimental digital data transmissions on line 16 of each field in the London area since early April, and reports that development has now reached the stage of constituting an "experimental working system". This includes a receiver adaptor unit, though it is understood that this would require simplification to become a commercial proposition for mass production. Line 16 of each field should not of course be visible given a correctly adjusted set. Some viewers have however noticed the presence of the data transmissions in the form of twinkling dots, due either to the picture being underscanned so that line 16 is displayed at the top of the screen or to foldover at the top of the picture. Adjusting the appropriate timebase controls should remove the dots.

Oracle draws heavily on the techniques developed by the IBA for its Slice system which enables picture sources to be identified—a problem with complex networking using signals from numerous sources—by inserting identification coding in the field flyback period. The dramatic reduction in recent years in the price of complex digital i.c.s suitable for data storage is the underlying factor that has prompted research—similar work is said to be going on throughout the world by a number of broadcasting authorities—into such public data transmission services.

Since it takes only 1.8 seconds to transmit one Oracle page the entire 50 pages—each possibly providing an entirely different information service—could be rewritten (updated) in less than two minutes.

Two line (64 $\mu$ sec) periods in each period of 625 lines

have been set aside by international agreement for data transmission—though not specifically for public data transmission. The Oracle system transmits one "segment" of display information—representing up to ten characters plus the necessary "address code"—during each 64 $\mu$ sec period. The "address" indicates to the receiving unit the particular page and the exact page/screen position of each information segment: it takes the form of a "run-in code" (5 binary digits—i.e. bits), a "start code" (8 bits), a "line number" (5 bits), a "page number" (6 bits) and a screen position indication (8 bits). At the receiver installation the timing sequences necessary to get the information segments displayed at the correct time are controlled by pulses obtained from the line timebase—as with colour decoding this implies the need for stable line timebase operation.

The Oracle adaptor separates the data signal from the television signal and passes the 64 $\mu$ sec information segments into an intermediate store; when the viewer operates his control unit to select one of the pages the address code is used to insert the appropriate information for display at precisely the correct moment into the main store which thus has to hold only one of the 50 complete pages being transmitted. This means that the main store has to be capable of holding 5,280 bits of information—the store consists in practice of a recirculating shift register in i.c. form. When another page is selected the appropriate segments of information are fed into the main store and displayed on the screen, the previous segments being "lost". Each character on the screen is based on a matrix of 7  $\times$  5 dots.

A computer is used at the studios to code the information available for display and insert it into the television waveform at the appropriate moments. It is intended that the first line of each page would carry an identification, date and time, thus giving the viewer using the service the equivalent of a highly accurate digital clock.

The basic Oracle equipment at the transmission end is said to be likely to cost around £20,000, a modest enough sum for such a useful service. The cost of the receiver adaptor/control unit could lie somewhere in the range £35-£120—current developments in i.c. technology have a considerable bearing on this. Advances in large-scale integration for example could result in the main store consisting of a single i.c., a second i.c. containing most of the control electronics.

## VISION MEMORY UNIT

While on the subject of data storage, Hitachi have recently demonstrated a unit which stores TV frames for replay and also by incorporating a continuous recording facility—using a 4in. diameter magnetically-sensitive disc revolving at a speed of 3,600 r.p.m.—enables frames seen up to four

minutes previously to be stored for subsequent viewing. The equipment can be used with off-air or CCTV signals, both monochrome and colour, and is called a "Multi-Channel Disc Memory". As new signals are recorded on the continuous recording disc the oldest are automatically erased. A total of 15 magnetic heads pick up the signals from the disc and can be set to automatically store frames at set intervals up to 17 seconds apart.

## UHF SERVICE EXTENSIONS

The following two main and three relay stations are now transmitting the BBC-Wales service:

**Moel-y-Parc** channel 52, receiving aerial group E horizontally polarised.

**Llanddona** channel 57, receiving aerial group C horizontally polarised.

**Bethesda** channel 57, receiving aerial group C vertically polarised.

**Betws-y-Coed** channel 21, receiving aerial group A vertically polarised.

**Conway** channel 40, receiving aerial group B vertically polarised.

The following IBA transmitters are now in operation:

**Blaen Plwyf** carrying HTV Wales programmes on channel 24. Receiving aerial group A horizontally polarised.

**Blaenavon** carrying HTV Wales programmes on channel 60. Receiving aerial group C vertically polarised.

**Windermere** carrying Granada programmes on channel 41. Receiving aerial group B vertically polarised.

## US TV SCENE

The US Electronic Industries Association has announced the figures of TV set deliveries to the US market last year: colour set deliveries were 20% up at nearly 8,850,000 and monochrome deliveries almost 8% up at nearly 8,250,000. These figures include imports, but it's getting hard for the US customer to decide what exactly is and isn't an import. For instance there are no longer *any* monochrome chassis in large-scale production in the USA: those sold under well known US brand names are made mainly in Taiwan, Japan and Mexico. Some US firms are also getting their colour chassis manufactured abroad—for example Admiral in Taiwan. On the other hand several large Japanese setmakers now have plants in the USA. Sony's San Diego plant is expected to be turning out 20,000 colour sets a month by the end of the year. National Panasonic has recently added a colour set production line to its Puerto Rico plant, and Hitachi is producing colour sets near Los Angeles. To further complicate matters what goes into a set wherever it is assembled may today come from here, there or almost anywhere. This latter is increasingly the case in Europe as well—witness TCE's use of a number of Japanese scanning units.

The different timing of the introduction of developments in different countries is interesting. The US were first with 110° colour sets for example, some years ago now, but it is only this year that the all solid-state colour chassis is expected to take a substantial portion of the market. The marketing strategy is also curious. In the UK you wouldn't get away with sticking a higher price on a solid-state chassis, presenting it as a new development worth paying extra for, yet this is exactly the approach being adopted by US setmakers. Some US setmakers claim that solid-state chassis are more expensive to produce and less reliable than hybrid ones, points which have not been borne out by experience on this side of the Atlantic. In fact we wonder whether this late move to the solid-state chassis is more indicative of disarray in the US TV industry which has

been under the onslaught of massive cheap imports for several years.

The Federal Communications Commission has set new standards for TV tuner units—these are mandatory upon setmakers. One feature is that all tuners will have to incorporate a.f.c. from July next year. US setmakers are not yet using varicap tuners, because of the problems of operating at both v.h.f. and u.h.f.

## THE NEW COLOUR TUBE

Thorn's new precision in-line colour tube which we described in detail last month was officially unveiled at the London Electronic Components Show. The first tube of this type in the Mazda range will be the A51-160X which is expected to be available from setmakers in Autumn 1974. No marketing date for a smaller version, the A42-100X, has been announced. The concept of a colour tube with integral scanning components—as embodied in these new tubes—enables most setting up adjustments to be eliminated, in particular tedious dynamic convergence routines.

## UK TRADE SCENE

Some statistics prepared by the EIAJ (Electronics Industry Association of Japan) show that of total UK colour set imports of 334,000 in 1972 (an increase of 3.4 times the 1971 figure) rather less than half, 156,000 (up 3.5 times), came from Japan. It also seems however that towards the end of last year total set imports from Japan, i.e. both colour and monochrome, accounted for some 25% of the UK market. It looks as if Thorn at any rate are making a determined effort to adapt to the way in which the market is fast developing—a mixture primarily of colour sets and monochrome portables. Following their recent announcement of plans to substantially increase colour set production (by "at least 40%") TCE now say they will be increasing the production of monochrome portables at their Gosport plant from 80,000 last year to 200,000 this year. Priority is to be given to exports, and it is interesting that TCE will be introducing shortly in their **Ultra** range a seven-channel 12in. portable designed to operate "in any EEC country"—the price is expected to be about £66.

**Decca** have announced a new 22in. de luxe colour set, Model CS2233, featuring concealed controls and electronic tuning by means of seven piano keys. **Alba** have announced an 18in. colour set, Model TC2319, fitted with the BRC 8000 chassis. Two monochrome models announced by **Pye** are fitted with a new chassis, the Pye group 173 series chassis: they are the 20in. tube Model 170 with suggested VAT-inclusive price of £72.29 and the 24in. tube Model 171 priced at £80.52—both models are fitted with varicap tuners.

## HANDS OFF BBC-1!

We commented in an editorial last January on the campaign being conducted by the Institute of Practitioners in Advertising and others to convert BBC-1 into an advertisement-supported service—"to make the BBC lift its ban on commercials" as the Institute puts it. Since then such suggestions have received a rather dusty answer from the government. The latest development consists of a blatant effort at scaremongering lead by the Institute's president Jack Wynne-Williams who is reported to have said recently that "unless our proposals for financing BBC-1 by advertising are accepted the licence fee could soon double—indeed a 50p a week licence will inevitably be with us". The Institute's attempt to grab BBC-1 is beginning to sound rather desperate.



### KORTING 51763 SERIES

THE chassis used in the Korting 51763/51765/52665/52666/52865/52866 series of 22 and 26in. models employs four valves and two i.c.s in addition to 36 transistors. The valves are used in the field (PCL805) and line (PCF802, PL509 and PY500A) timebases while the two i.c.s are a TAA640 intercarrier sound amplifier/discriminator and a TAA630 in the decoder to provide chrominance demodulation and burst blanking, PAL switching, G — Y matrixing and colour-difference signal preamplification. In common with most Continental setmakers Korting employ colour-difference tube drive on this chassis.

#### IF Strip

The signal from the six push-button integrated u.h.f./v.h.f. tuner is fed via a response-shaping bandpass circuit to a three-stage broadband i.f. strip. The use of this shaping at the input enables fixed wideband (approximately 15MHz) tuned coils to be used between the first and second and second and third i.f. stages. The other advantage of this now well-established practice is that the adjacent channel signals are removed whilst at low amplitude, a help since transistors are generally more susceptible than valves to cross-modulation. The final i.f. stage feeds the luminance/chrominance detector via a further bandpass circuit to suppress the 33.5MHz sound i.f. signal and thus prevent sound/chrominance beat patterning. A separate shunt detector produces the 6MHz intercarrier sound signal. Forward a.g.c. is applied to the first i.f. stage, the signal coupling to this stage being light (by means of a 10pF capacitor) so that the variations in input impedance produced by changes in the a.g.c. bias do not result in alteration of the response.

#### Luminance Channel

The complete four-stage luminance channel circuit is shown in Fig. 1. The first stage T105 receives a positive-going (negative video) output from the luminance/chrominance detector and drives the luminance delay line from its collector and the a.g.c. circuit and decoder from its emitter. The base bias of the second stage T201 is set by the "black porch" preset R203. The principle here is that R203/R202/T201/R205 form one side of a bridge with R209/R210 the other side. When R203 is correctly set the voltages at each side of the contrast control R705 are equal.

Variations in the contrast control setting do not alter the base bias applied to the d.c. coupled third luminance stage T150 therefore, and in consequence the black level is not affected. On monochrome D201 is non-conductive and L201 is tuned by C203 to 6MHz. On colour reception a positive potential from the colour-killer circuit is applied to D201 anode, switching it on and effectively connecting C202 across the rejector to lower its frequency to 4.43MHz. In this way the subcarrier is removed from the luminance channel on colour while the full video bandwidth is maintained on monochrome.

The high-amplitude luminance signal swing (about 130V peak-to-peak) required to drive the tube cathodes is developed by T150 and applied to the tube via the emitter-follower T151. The use of an emitter-follower in this position gives two advantages. First the tube's capacitive loading—about three times that of a monochrome tube—is removed from the collector circuit of T150, markedly improving the gain/bandwidth performance of this stage, while secondly the low-impedance output provided by T151 prevents interaction between the brightness setting and the luminance signal. As usual the full luminance output is applied to the red cathode of the tube while the green and blue cathodes are fed via presets which with approximately 170V at each side do not affect the d.c. working conditions of the tube.

#### Beam Limiting

The beam limiting action occurs at T150 emitter. The beam limiter circuit itself is shown in Fig. 2. T205 is linked to the cathode of the line output valve via R224. When the potential at T205 base exceeds that set by the beam current limiter preset R223 at its emitter T205 begins to conduct. The negative-going voltage at its collector in turn increases the conduction of T204 and as a result T204's collector voltage rises. This increased voltage appears at T150 emitter, reducing the conduction of this stage and in consequence the picture brightness. The use of two transistors in the beam limiter circuit ensures a sharp transition into the limiting state so that the beam currents can be allowed to run right up to the maximum permitted values.

#### Colour-difference Amplifiers

Having examined the luminance drive to the tube cathodes, let's see how the colour-difference signals are applied to the appropriate grids. The three colour-difference output stages are of course almost identical. The R — Y output stage is shown in Fig. 3. The output transistor T728 receives its input from pin 4 of the TAA630 i.c., its output being a.c. coupled via C754 and the LR peaking combination to the red grid of the tube. The emitter voltage of T728 is held sensibly constant by the potential divider action of R773 and the emitter resistor R772, while the series connected components C752 and R774 increase the gain at the higher frequencies by eliminating the negative feedback at h.f. across the emitter resistor. As capacitive coupling is used the drive to the tube's grid must be clamped in order to maintain constant black level. This is achieved by the two diodes D724 and D725 which are switched on once each line during the back porch period by pulses from the line output stage, thereby charging the coupling capacitor C754 to the potential set by the brightness control R707. The coupling capacitors in each colour-difference signal feed are charged to an identical potential once each line, establishing a d.c. "base" on which the colour-difference signals are superimposed. The relatively long time-constant of the

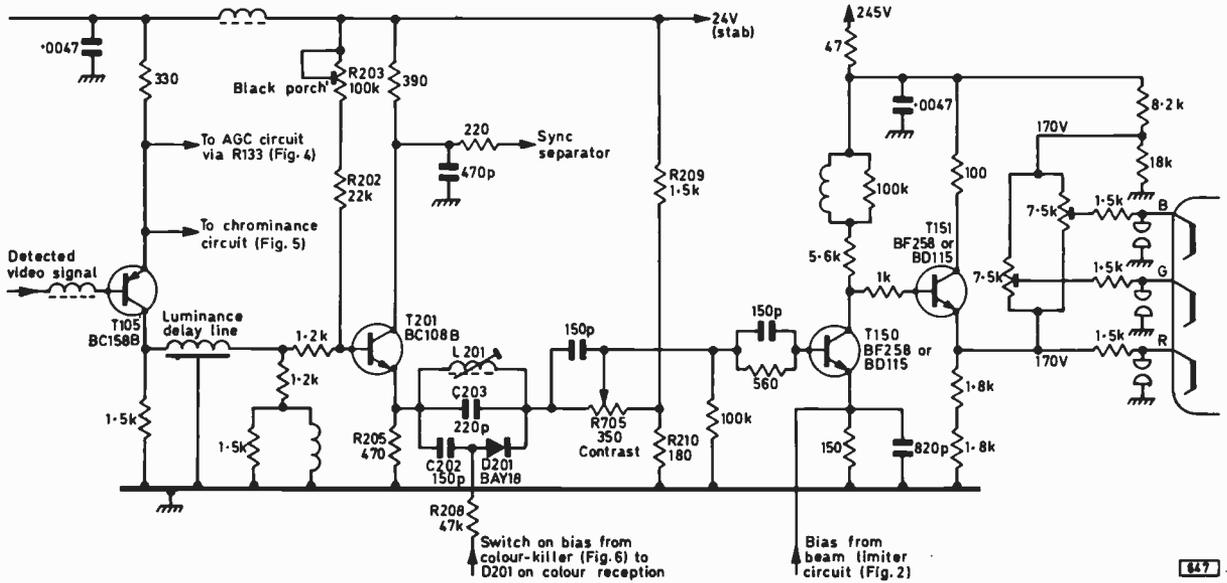


Fig. 1: Complete luminance channel circuit, which is d.c. coupled throughout.

circuit maintains the d.c. level with negligible sag throughout the line period.

**Tint Control**

The tint control R711 which is connected in parallel with R794 and the corresponding resistor in the clamp circuit in the B - Y output stage adjusts the relative d.c. voltage at the red and blue grids so that the picture background tint can be varied slightly between reddish and bluish.

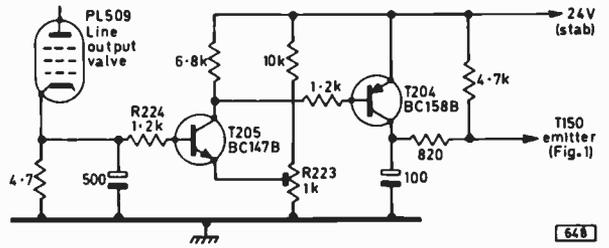


Fig. 2: The beam limiter circuit.

**Brightness Circuit**

As we have seen, the average tube cathode potential is 170V (at T151 emitter). The c.r.t. grids must therefore be at a considerable positive potential to provide the correct working bias. The voltage for the brightness control is

obtained, as shown on the right in Fig. 3, by rectifying the field flyback pulses. This provides tube protection since if the field output fails there is no brightness voltage and the screen is blacked out, thereby preventing damage to

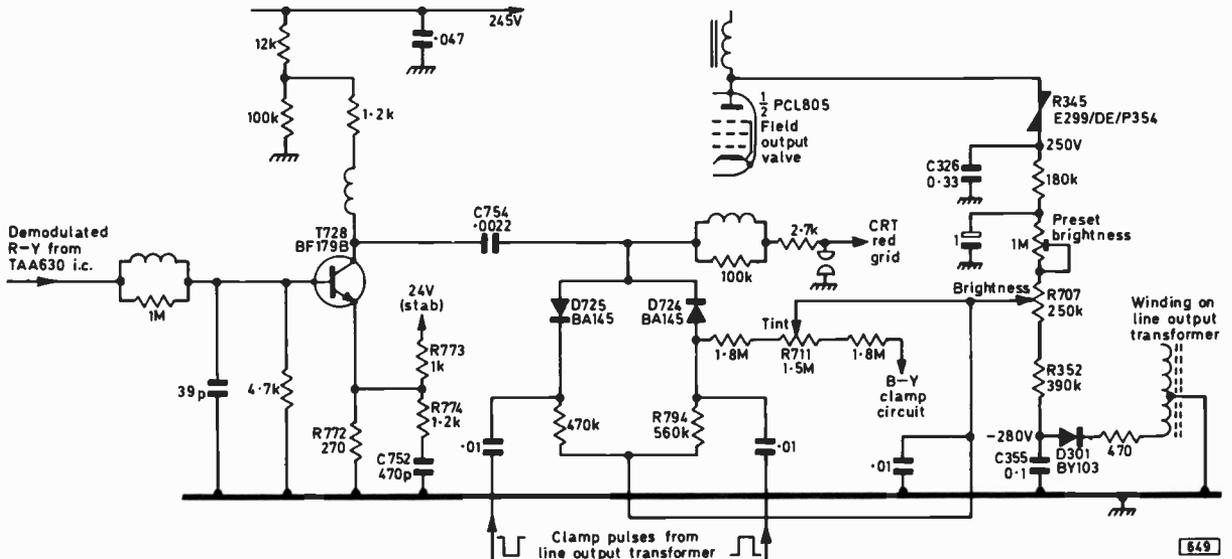


Fig. 3: Circuit of the R-Y colour-difference output stage together with the brightness and tint control arrangements. Tube protection is afforded by deriving the brightness potential from the field output valve.



rising to too great a value on weak signals by clamping T721 base to the potential (8.6V) at the junction of R723 and R722.

## Ident Stage

The heart of any decoder is the ident stage which usually as here controls the colour killer. Instead of the usual LC tuned amplifier the ident stage (see Fig. 6) consists of a synchronised RC oscillator (T748). This gives improved performance in the presence of noise. Synchronisation is achieved by applying the burst ripple appearing at the burst discriminator output to the base of T748 via C811. The frequency of the oscillator can be adjusted by means of the preset R887 while R883 controls the amplitude of the output. To synchronise the PAL switch the ident signal is fed via C824 and C825 to pin 1 of the TAA630 i.c.

## Colour-killer Circuit

The ident sinewave is also fed via C818 to the rectifier D746. This produces a negative bias potential which cuts off the colour-killer transistor T747 (otherwise biased on by the potential tapped from R876). The colour killing action takes place in the TAA630 i.c. The rise in T747's collector voltage when a colour transmission is received is applied to pin 10 of the TAA630 via the potential divider R843/R842. The colour-killer transistor output is used for two other purposes. Its collector is connected via R208 (Fig. 1) to the anode of diode D201 in the luminance channel and this results, as we have previously seen, in the tuning of the filter in the luminance channel being reduced from 6MHz to 4.43MHz on colour. The junction of the potential divider R867/R866 is connected to the anode of diode D745 which connects the earthy end of the RC time-constant filter in the decoder reference oscillator control circuit to chassis via C806. As D745 only switches on when the chrominance signal reaches a certain level the effect of this is to remove the time-constant filter from the reference oscillator control circuit when the set is switched on, thereby widening the pull-in range of the control circuit during the warm-up period.

Switch S2 mounted on the front control panel enables the colour to be killed by overriding the negative bias provided by D746 and thus switching T747 on.

## Decoder Miscellany

There are two saturation control potentiometers: one is ganged to the contrast control so that the two track to-



*"To be honest Lady, a new tube would kill it!"*

gether while the other enables the saturation to be adjusted independently. The controls are incorporated in the collector circuit of the second chrominance amplifier stage and set the amount of signal fed to the chrominance delay line/matrix circuit.

The burst take-off is via an emitter-follower buffer stage which is driven by the second chrominance amplifier stage. Both the buffer stage and the burst amplifier stage are gated, the gating pulses being rather ingeniously shaped so as to coincide exactly with the burst period. The technique involves producing a negative-going spike and adding this to the relatively broad positive-going flyback pulse obtained from the line output stage.

The rest of the decoder consists of a conventional crystal/varicap diode controlled reference oscillator and the TAA630 i.c. whose functions were listed at the beginning of this article.

## Conclusion

D.C. static convergence by means of preset potentiometers is employed—but there are static magnets as well! These latter should be repositioned only if major correction is necessary.

All in all a well made chassis with many interesting circuit features.

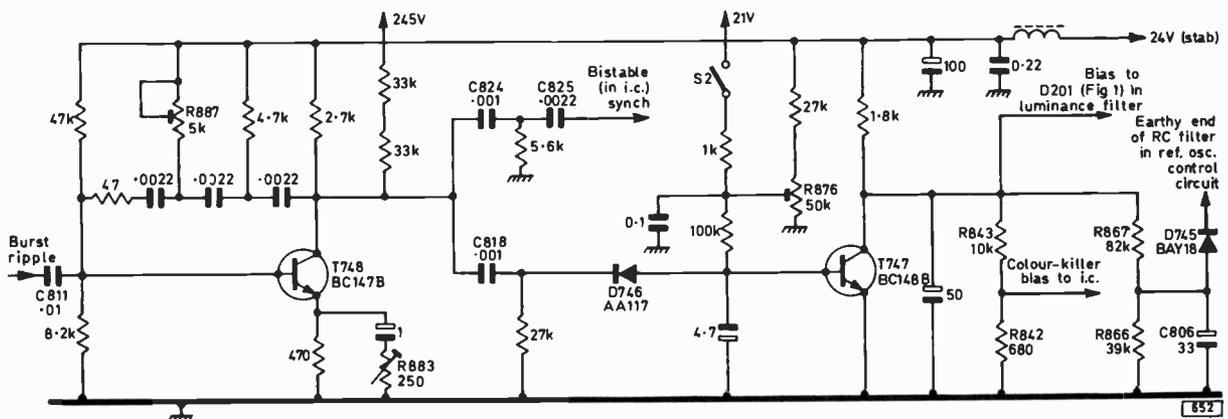


Fig. 6: The RC oscillator ident stage and colour-killer circuitry.

# FAULT FINDING GUIDE

5

John Law

## BUSH TV141 SERIES IF PANEL

IN the early 1960s the Bush TV141/Murphy V159 series were among the best selling TV sets available. They are still around in large numbers and are easily recognisable by their rather austere box-like appearance. The main chassis is a vertical frame mounted at the rear of the cabinet: the i.f. panel (left) and timebase panel (right) are screwed to this frame. The panels can be unplugged and removed separately for replacement or repair. For servicing the chassis hinges down on a length of chain after the system switch has been disconnected: most repair work can be readily carried out with the chassis in this position. Separate v.h.f. and u.h.f. tuners are fitted to the side of the cabinet. The system switching, controlled by two push-buttons, operates through a bowden cable and centre-mounted switch lever.

The present article is concerned with faults in the i.f. panel which in addition to the i.f. stages also contains the video and sound output valves and associated components. The circuit is shown in Fig. 2 and the layout in Fig. 1.

The i.f. signal on u.h.f. is passed to the v.h.f. tuner where the mixer stage then operates as an i.f. amplifier. On both systems therefore the input to the i.f. panel is from the v.h.f. tuner. A.G.C. is applied to the first i.f. stage 2V1: the second stage 2V3 feeds the video detector 2MR4 (OA90) which operates on both systems. The detector diode is mounted inside the can with 2L17/18/19 and polarity switching between the two systems is effected by 2S1d and 2S1e—giving a positive-going output on 405 lines and a negative-going output on 625 lines, with "positive video" in both cases of course. The necessary bias adjustment in the video amplifier 2V4a is effected by 2S1f which switches the cathode voltage from 4.3V on 405 lines to 0.5V on 625 lines—it also earths the intercarrier sound take-off capacitor 2C29 on 405 lines. The second section of the PFL200 (2V4b) is the sync separator.

On 405 lines the sound i.f. signal passes from the anode of the common vision and sound i.f. stage 2V1 to the sound only i.f. amplifier 2V2 via 2L6/7. The 405 detector is 2MR1 and the sound signal then passes via the interference limiter diode 2MR6 and the volume control to the triode section of the audio valve 2V5. On 625 lines the inter-carrier sound signal developed by the vision detector is amplified by the video amplifier and passed via 2C29 etc. to 2V2. On this system a ratio detector is used comprising 2MR2/3. Switching between 405- and 625-line operation in the sound channel is effected by 2S11.

The mean-level a.g.c. bias for the controlled i.f. stage and the r.f. amplifier in the v.h.f. tuner is derived from the grid circuit of the sync separator and is backed off by the contrast controls.

Beside going on to fault finding mention must be made of the c.r.t. and valve heater protection system. In common with many chassis the heaters are fed with a pulsed d.c. voltage which is obtained from a rectifier (3SR2, BY101) in series with the heaters. This is done to reduce heat dissipation within the cabinet. The screen grid of the sync separator receives its supply via 2R38 from a point along the heater chain. Smoothing is effected by 2C43.

A short-circuit can and sometimes does develop in the rectifier 3SR2, putting a.c. across the heaters. This higher voltage overruns the heaters, with eventual permanent damage if the fault isn't traced quickly. The increased

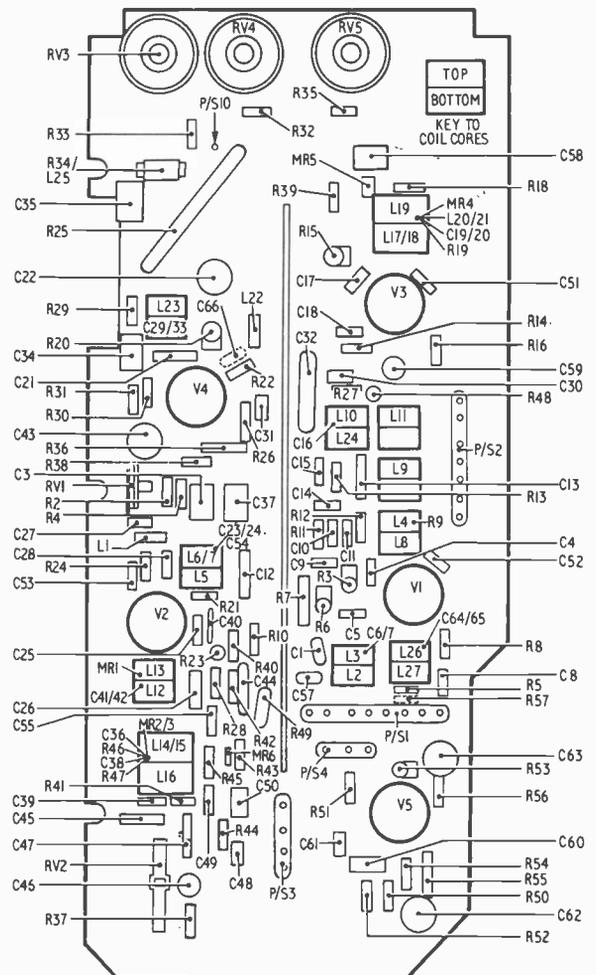


Fig. 1: Layout of the i.f. unit.

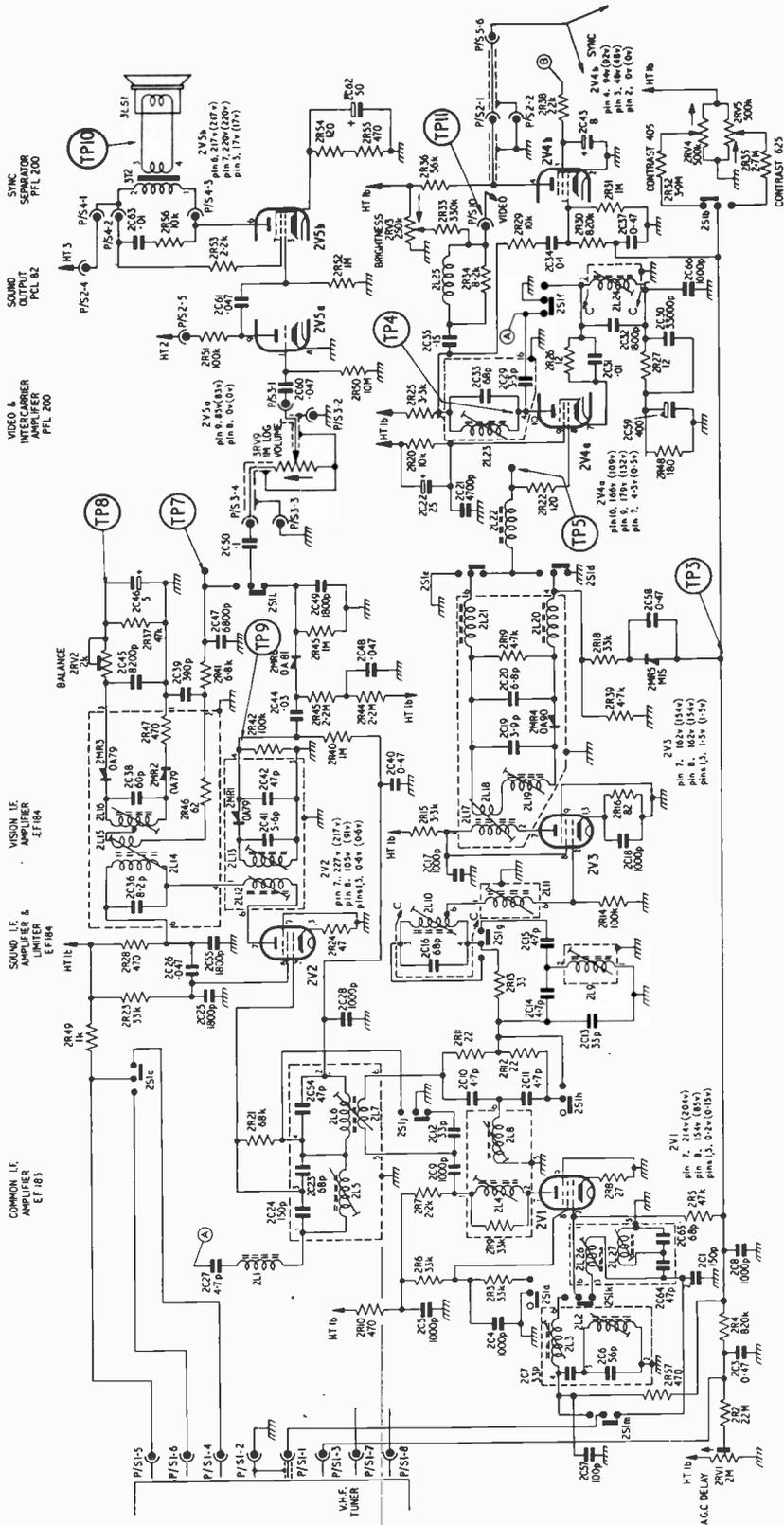


Fig. 2: Circuit diagram of the i.f. unit used in the Bush TV141 and Defiant 901 and 301. Point B is fed from the heater line.

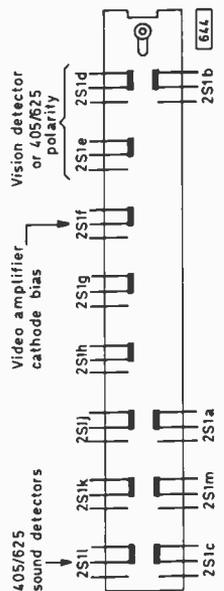


Fig. 3: I.f. panel system switch, shown in 405-line position.

brightness of the valves and c.r.t. can be seen—but the customer is not normally peering into the back of his set! The a.c. will also appear at the screen grid of the sync separator however, resulting in field roll. Thus any suggestion of sync trouble should immediately call attention to the heater rectifier 3SR2: a meter resistance check across it should show about  $1k\Omega$  one way and some  $100k\Omega$  the other.

## Common Faults

The normal fault finding rules—close physical inspection followed by valve replacement and voltage measurements as necessary—apply to the Bush TV141 series as to any other chassis. Seek out particularly discoloured or burnt resistors, leaky electrolytic capacitors or bulging paper capacitors. The printed panels tend to discolour after some years and look burnt, especially under the PFL200. When this happens the print can peel away from the panel and crack, leaving an intermittent or completely broken connection. Always use your eyes before your soldering iron therefore.

In one case in the workshop much time was spent on a Bush chassis changing valves, checking voltages, adjusting rejectors etc., in an effort to trace the source of sound-on-vision. Eventually the cause was traced to the main smoothing electrolytic 3C42. Closer initial inspection would have shown that the can had been leaking excessively over a period and that the capacitor had dried up therefore. A further clue suggesting that the fault was not due to video or rejector trouble was an increase in the severity of the sound-on-vision whenever the volume was turned up. Replacement of the double  $300\mu F$  can completely cured the fault and gave a crisper picture than before.

The h.t. decoupling resistor 2R15 in the second i.f. stage 2V3 sometimes changes value. This can be due to a fault in the EF184. If a fault is traced to this stage the value of 2R15 ( $3.3k\Omega$ ) should always be checked.

## Sync Troubles

True sync faults as distinct from breakdown of the 3SR2 rectifier should be sought in the vicinity of the video section of the PFL200. The valve itself is the first suspect. If the symptoms are confined to 625-line operation suspect the screen decoupling electrolytic 2C22. This is  $25\mu F$  in some sets,  $10\mu F$  in others. The higher value is usually found in older receivers. Note that it is connected between the screen grid and h.t. positive, not between screen and earth as is the usual fashion. This means that the negative terminal goes to the screen grid and the positive one to h.t.: connecting the replacement the wrong way round will ruin it. Loss of capacitance in the cathode electrolytic 2C59 ( $400\mu F$ ) can also impair the sync signals—this capacitor is shorted out on 625 lines by 2S1f.

The screen grid decoupler 2C43 in the sync section of the PFL200 can also fail: as we have seen this is the reservoir for 3SR2. Leakage in the grid coupling capacitor 2C34 will put a positive potential on the grid, upsetting the valve's operating conditions and altering the shape of the sync pulses. A voltage check at pin 1 of the valve will detect this fault. If an oscilloscope is available the sync pulse distortion can be readily seen.

## Blank Raster (405)

Normal sound on 405 lines accompanied by a blank raster suggests absence of the vision signal and often indicates breakdown of the vision detector diode 2MR4.

This is mounted in the final i.f. can but can be tested at 2R22 which is adjacent to 2V4. Connect the meter between the junction 2L22/2R22 and chassis: with the leads one way round a reading of less than  $500\Omega$  should be obtained while reversing the leads should give a reading in excess of  $1M\Omega$ . No reading indicates that the diode is open-circuit, a short-circuit is obvious. Replacement requires removal of the can but this is not a difficult job.

## AGC Troubles

A set with a picture on 625 lines accompanied by wavy lines running down the edges was traced to failure of the anti-lockout diode 2MR5. In another case this symptom was caused by breakdown in 2C22—see sync fault above. Loss of emission in either of the i.f. valves 2V1 or 2V3 will cause a reduction of the a.g.c. bias leading to overloading in the early stages. The symptoms will be a combination of sound-on-vision and vision buzz on sound, depending on how seriously the a.g.c. voltage is effected. It can be cancelled completely by grid leak in 2V1.

When checking valves by substitution take care that the EF183 and EF184 valves are not accidentally interchanged: the former is a variable- $\mu$  type and the latter a straight pentode and interchanging them can give a picture with symptoms suggesting an a.g.c. fault.

A defective valve can give sound-on-vision. An unusual case with sound-on-vision as the symptom came up recently. Replacement of the first i.f. valve 2V1 brought no improvement but a quick check of the voltages around the base revealed absence of anode voltage. Incidentally the voltages on the bases can be measured without lowering the chassis by replacing the positive test prod with a sewing needle: the fine point will contact the pins where they extend from the steatite base and pass through the printed panel. In the case in question further testing revealed that the anode decoupling resistor 2R7 was open-circuit—replacement cured the fault. One might have expected complete absence of picture with no voltage at the anode but in this case the picture was still viewable.

## Sound Faults

Sound troubles are frequently due to the PCL82 valve. Heater-cathode leakage will give distortion accompanied by a higher than normal voltage across the series-connected cathode resistors 2R54/55. Leakage in the grid coupling capacitor 2C61 will also result in distorted sound. Weak sound has been caused by increase in the value of the triode anode load resistor 2R51.

If intercarrier buzz on 625 lines appears check that the discriminator balance potentiometer 2RV2 has not been disturbed.

There is a separate h.t. line to the sound output pentode: where hum on sound is experienced the smoothing electrolytic 3C44—part of the block 3C44/5/6—can be responsible.

## Summary

To sum up, faults in the i.f. panel should be no more difficult to trace than defects in the timebase, tuners, etc. Fortunately coils in cans seldom give trouble except for the occasional dry-joint. Inspect carefully for discoloured resistors, leaky or swollen capacitors, cracks in the printed panel and loose or corroded plugs and sockets where the two panels in this chassis are interconnected.

The system switches on both panels have some play which can become excessive. After repairs have been completed check that the central control lever has sufficient throw to ensure solid make and break on both panel switches.

# DC RESTORER CIRCUIT

Keith Cummins

SYNC tip or line-gated automatic gain control circuits are used in most single-standard 625-line receivers. As a result a stable video signal is produced at the video detector, the black level at this point in the receiver being constant.

## DC Restoration Techniques

Unfortunately a.c. coupling is then frequently employed in the video stages and in consequence the d.c. level is lost. The d.c. level can be restored however, thereby preserving accurate representation of the grey scale. D.C. restoration can take place before the video output stage, which must then of course be d.c. coupled to the tube, or at the tube itself. This latter approach has been adopted in the circuit to be described. It has the advantage of minimal drift, does not affect the synchronising or intercarrier sound, and can be easily incorporated in almost any receiver which uses an a.g.c. system as specified above.

## Prototype Circuit

The prototype circuit was developed using a BRC 1500 chassis. The original tube cathode coupling circuit used in this chassis is shown in Fig. 1 while Fig. 2 shows the basic d.c. restoration circuit first tried—D1 is the d.c. restorer diode. C1 is added from the slider of the brightness control to chassis in order to complete the a.c. path to the diode. The incoming signal is positive-going with the sync pulses representing the maximum positive signal excursion. The sync pulses cause the diode to conduct, thereby setting the video signal on a pedestal voltage set by the brightness control. Since the sync pulse amplitude is constant the picture black level remains at the level set by the brightness control.

The prototype circuit did not operate ideally unfortunately for one simple reason: the tube cathode current flows through the d.c. restorer circuit and the brightness control. This is in effect negative d.c. feedback and offsets the d.c. restoration action so that while the video presentation is improved the d.c. restoration is only about 50% effective.

## Final Circuit

The final circuit evolved is shown in Fig. 3. A buffer transistor Tr1 connected as an emitter-follower is interposed between the d.c. restorer and the tube. The tube's cathode current now flows through the emitter resistor R2 instead of through the d.c. restorer circuit. As a result the d.c. restorer's action is affected only by the small base current of the BF179 transistor. The effect of this is very slight and the action of the whole circuit shows a 95% restoration of the d.c. level.

The component values and reference numbers shown on the circuits apply to the BRC 1500 chassis. It will be seen

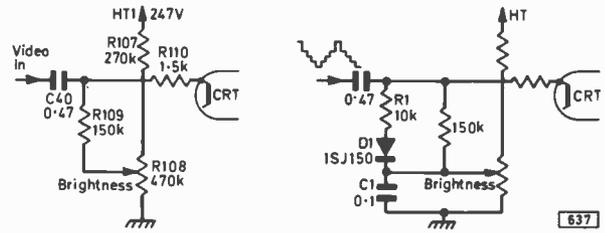


Fig. 1 (left): The video signal is a.c. coupled by C40 to the cathode of the c.r.t. in the BRC 1500 chassis. The two video stages are also a.c. coupled. Since a signal passed through a capacitor loses its reference level, this form of coupling means that the black level of the video signal is no longer stable but varies with alterations in average signal amplitude.

Fig. 2 (right): Simple d.c. restorer diode circuit first tried out. This proved to be only about 50% effective due to the tube cathode current passing through the circuit.

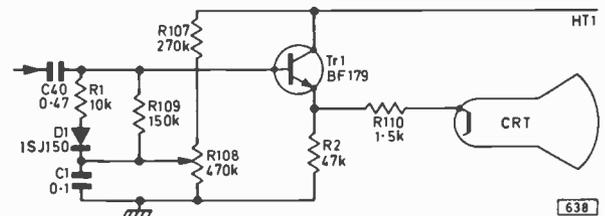


Fig. 3: Circuit finally adopted, with buffer stage Tr1. The diode (D1) is a Radiospares type 1S150: a near equivalent is the OA202.

that one diode, one transistor, one capacitor and a couple of resistors are the only extra components required to provide a stable black level. The advantages in picture presentation seem great compared to the cost of these five components.


It should be possible to adapt the circuit for use with other receivers, but those that use mean-level a.g.c. are not suitable for this modification.

## Assembly Details

The extra components can be easily accommodated on the BRC 1500 chassis. D1 and R1 can be wired in series, sleeved up and soldered on to the printed side of the board across R109. The c.r.t. cathode lead is removed from its tag on the chassis, soldered to the emitter lead of Tr1 and then sleeved up. The base lead of Tr1 is connected to the point vacated by the c.r.t. lead. Tr1 collector is connected to the h.t. line, R2 wired across the tube base panel—between the video lead input point and tag 22 (c.r.t. pin 5 connection)—and finally C1 connected from the slider of the brilliance control to earth, behind the controls.
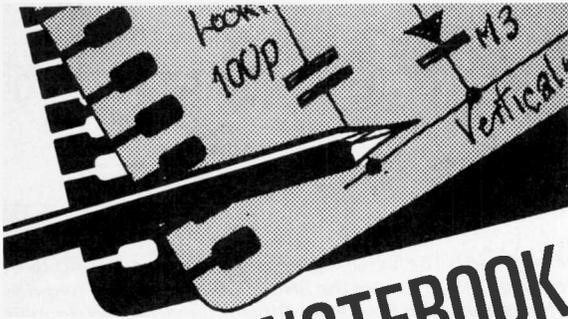
## Results

Altogether the modification is well worth while. For comparison two sets fitted with the 1500 chassis were operated side by side, one as standard production and the other incorporating the modification described. The sets were tuned to the same programme of course. The modified receiver's performance outstripped that of the production model by providing freedom from "milky" scenes, sharp captions against a black background, etc.—thus proving the success of the operation.



# SERVICE NOTEBOOK

G. R. WILDING

## Bottom Cramping

Cramping at the bottom of the picture is generally due to one or more of the following causes: (1) a low-emission output valve; (2) reduced value output valve cathode bias resistor; (3) loss of capacitance in the output valve cathode decoupling electrolytic capacitor. In the case of a 12in. Ferguson portable fitted with the Thorn/BRC 980 chassis that came our way recently however the last two causes had to be immediately ruled out since the field output pentode in this chassis is biased by returning its grid to a suitable voltage point along the negative rectified heater chain. This method of biasing the valve is used as a safety precaution: if the heater chain rectifier goes short-circuit thus greatly over-running the valves and c.r.t. an a.c. voltage will be applied to the field output valve grid constantly tripping the field hold and making viewing impossible.

The circuit is shown in Fig. 1. A new 30PL14 failed to restore a normal raster and it was clear that the cause of the trouble was insufficient grid bias due to a leak in a grid circuit capacitor. This was eventually traced to a leak approaching  $2M\Omega$  in C61, the  $0.3\mu F$  capacitor which smooths the grid bias. On fitting a replacement normal linearity and height were obtained. The leaky capacitor had formed in conjunction with the smoothing resistor R85 a potential divider which reduced the normal grid bias by about a third.

As the rectified heater current is a half-wave supply it

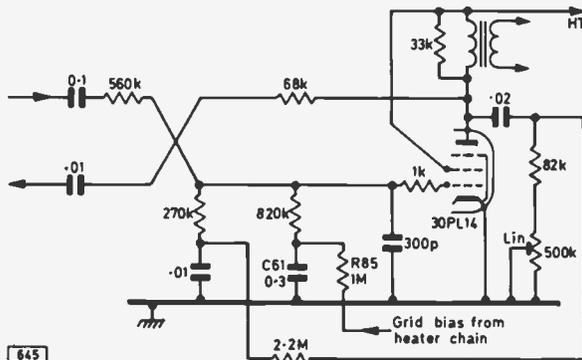


Fig. 1: Field output stage used in the BRC 980 chassis, with grid bias obtained from the heater chain.

might be wondered how a capacitor as small as  $0.3\mu F$  can remove the a.c. component to leave a pure d.c. voltage as the negative grid bias. The answer of course is the high value of R85: the resistance of this is so very much greater than the reactance of the capacitor (approximately  $10k\Omega$ ) at 50Hz that virtually the entire a.c. component is developed across R85—with zero d.c. voltage drop across it since there is zero current—leaving the full d.c. voltage across C61 as grid bias.

## Faint Horizontal Line

The complaint with a 19in. dual-standard Defiant receiver (Plessey chassis) was the presence on the screen of only a faint horizontal line. This was obviously due to lack of output from the field timebase but with this fault the line is usually sufficiently bright to cause screen burn if the set is left on long enough. The back of the set was removed and on inspection a charred resistor was seen near the e.h.t. can. This proved to be a decoupling resistor in the boost feed to the tube's first anode, focus electrode, and the triode anode circuit of the PCL85 field timebase valve. There was a dead short from the feed end of this resistor to chassis—thus robbing the tube of first anode voltage and greatly reducing the brightness of the horizontal white line. The associated decoupling capacitor proved to be OK so we concluded that the short must be caused by a breakdown in the printed-circuit panel insulation—this frequency develops in these early dual-standard models.

The printed wiring leading to the height control was then cut; a resistance test proved that the fault was in this part of the circuit but there was no short at the height control h.t. tag. Further investigation then showed that the wiring from the feed resistor had arced over to an earthed point, the resulting burn disconnecting the printed feed to the height control. Normal results were obtained after replacing the resistor, cutting away the charred panel surrounding the shorted print and replacing this with a jumper lead.

When you find a short-circuit in a printed panel it always helps—particularly if you haven't the service sheet to hand—to cut through feeds to narrow down the area for detailed testing. But first make sure that the trouble isn't a valve internal short.

## Transposed Reds and Greens

The reds and greens would occasionally be transposed on a 19in. Hitachi colour receiver, clearly indicating that the bistable circuit which drives the PAL switch was not being firmly synchronised. Without synchronisation there is of course on any PAL set only a 50-50 chance that the bistable will operate in the correct phase, but as the fault developed only occasionally on this set it appeared that the ident signal from the second ident stage (Tr1008, Fig. 2) was intermittently missing, greatly attenuated or even phase shifted—misadjusted ident tuning coils frequently produce this last fault in many makes of receiver.

Suspicion was first centred on diode CR1006 which couples the ident signal (and the line-frequency trigger pulses) to Tr1009, one of the bistable transistors, but a resistance test proved it to be OK. There appeared to be no dry-joints in the coupling circuitry and as there was colour with even the weakest signal input it seemed that Tr1008 was developing normal output—as the circuit shows an output is taken from the stage to activate the colour-killer circuit and also the a.c.c. circuit. This supposition was strengthened by the fact that the voltages

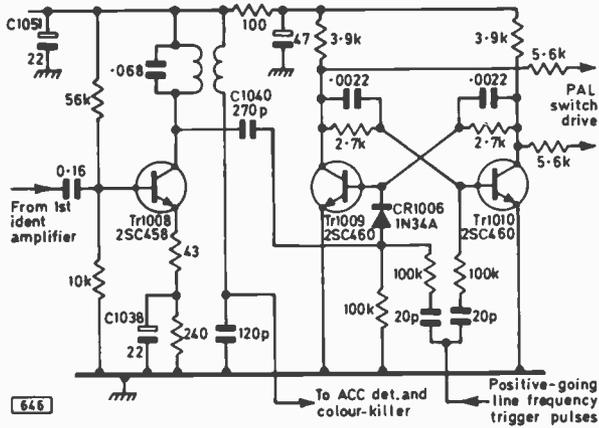


Fig. 2: Second ident stage and bistable circuit used in the decoder section of Hitachi colour sets. Poor bistable synchronisation was due to C1040 being faulty.

everywhere were normal, including those at the a.c.c. detector stage. To be on the safe side as the fault only appeared occasionally and the receiver had had prolonged use we decided to replace the two electrolytic decouplers in the second ident stage—C1038 in the emitter circuit and C1051 in the collector supply line—in case they had to some extent dried up or developed poor power factor.

During a prolonged test run the colours always stayed correct but just as we were about to refit the back the symptom once again appeared. There seemed little else to try but replacement of the ident coupling capacitor C1040 although it appeared to be perfectly all right. This measure resulted in complete removal of the fault symptoms.

### Smell of Burning

A smell of burning was the complaint with a Philips Model 23TG132A though the owner said there was a good picture and perfect sound. This was surprising since a smell of burning is usually accompanied by some evidence on the picture or sound. On switching the set on a full-size picture was obtained though it wavered about somewhat, especially at high brilliance settings, in a manner suggesting a faulty e.h.t. rectifier. On removing the back the cause of the trouble was immediately apparent: the lead to the top cap of the DY86 e.h.t. rectifier from the overwinding on the line output transformer had burnt away for almost half an inch, a vivid arc maintaining the a.c. feed to the anode of the rectifier. Yet there were no signs of arcing on the screen! On fitting a short length of e.h.t. cable perfect results were obtained.

TO BE CONTINUED

### LATE PUBLICATION

We apologise for the delay in publishing this issue of *Television*, due to printing problems. We hope to be back to normal next month but this cannot at present be guaranteed.

NEXT MONTH IN

# TELEVISION

## RECEIVER DEBUGGING

When you've built a TV receiver and tested it you will probably find all sorts of faults present. The aim of this new series is to run through the likely faults and to pinpoint the areas where action needs to be taken. The series will aid the understanding of fault-finding generally of course, and is a follow up to our series earlier this year on assessing receiver performance. In the first part the operation of the timebases is considered and the reasons for non-linear scanning outlined.

## UHF FAULTS

When a dual-standard set is first switched over to 625-line operation all sorts of unsuspected faults are often encountered. George Wilding runs through the common ones and their causes, and the action necessary. Reception on u.h.f. has proved to be rather more troublesome generally than at v.h.f.

## VALVE AND TRANSISTOR SUBSTITUTION GUIDE

It is not always necessary, and sometimes impossible, to fit exact valve and transistor replacements. This guide has been compiled to indicate generally what can and can't be done, list numerous helpful substitutes and lay down guidelines for the more difficult situations.

## SERVICING TELEVISION RECEIVERS

Next month Les Lawry-Johns deals with problems on the final GEC group dual-standard chassis, the GEC/Sobell 2032/1032 series.

## SBF AERIAL FOR BAND V

Following the great interest shown in his short back-fire aerial for the lower u.h.f. channels Reg Roper presents a design suitable for the higher channels.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW

TO .....  
(Name of Newsagent)

Please reserve/deliver the AUGUST issue of TELEVISION (20p), on sale JULY 16, and continue every month until further notice.

NAME.....

ADDRESS.....

# THE 'TELEVISION' COLOUR RECEIVER

## PART 16

# MODULE INTERCONNECTIONS

THE aim this month is to list the module interconnections in detail and indicate the recommended wiring system to be adopted. Also to clarify the line output transformer, e.h.t. tripler and focus unit connections. A component pack of components associated with the line output transformer is being prepared. A warning however: it is most important to get the earthing arrangements around the c.r.t. correct in order to prevent damage due to flashovers—see later.

### Wiring

The inter-module wiring of the receiver is listed in Table 1. It is suggested that stranded wire such as 7/0.2mm is used except where detailed below. Wires should be run round the frame of the cabinet after leaving a module and tied into forms to keep them tidy and the receiver uncluttered. 6–9 inches extra length should be allowed on all runs to modules which are movable so that they can be withdrawn with no hindrance. This extra length can be formed into a "hump" at the back of the module. All connections should be taken to one end of each module.

Different coloured sleeveings could be used for the numerous wires and it is suggested that the cable ends are marked with their board destination codes (1A, 1B, etc.) as they are placed in position before soldering. This is probably most easily done with a piece of Sellotape wrapped round the wire, with an identifying slip of paper trapped under a Sellotape fold.

The following cables should be screened:

<i>I.F. Module:</i>	2B	I.F. input, with screen connected to chassis at 2J.
	2D	Chroma output with screen connected to chassis at 2J.
	2E	Luminance output, contrast slider. Screen of both leads to 2J.
	2F	A.F.C. with screen to 2G.
	2H	Contrast potentiometer bottom with screen to 2J.
	2I	Contrast potentiometer top with screen to 2J.
	2K	Tuner a.g.c. output with screen connected to chassis at 2J.
	Pin C	of L124/5 assembly with screen to pin E of this assembly.
<i>Audio:</i>	9C	Volume control top with screen to 9J.

The following should use twisted wire:

<i>I.F. Module:</i>	2C	Audio output—twisted with earth wire from 2J.
<i>Degaussing:</i>	7A and 7B	twisted together.
<i>C.R.T. Base Panel:</i>	9D and 9E	twisted together.

Standard three-core mains coded cable of 5A r.m.s. capacity should be used into the receiver to the mains

switch and thence to the power supply unit. The earth should be looped around the switch. The lead leaving the receiver should be secured at some point to prevent pull on the switch connections.

### Line Output Transformer

The line output transformer tags are identified in Fig. 1 this month while Fig. 2 shows all the feeds taken from the transformer. Connections to the e.h.t. tripler unit are shown in Fig. 3: the unit must be mounted a minimum of 20mm clear of any metal work (except of course the fixing bolts). There are three connections to the Erie type focus unit: these are marked A, V and E on the unit itself. A is the input from the e.h.t. tripler (see Fig. 3), V is the output to 9F on the c.r.t. base board and E the chassis connection (to 6C on the power supply unit). There is also a connection point marked B which should be insulated with sleeving. The wires to the focus unit must first be soldered to the Pressac connectors provided and the contacts then pushed on to the focus unit pins: on no account should the wires be soldered directly to the focus unit pins as this will damage the unit.

Arrangements are at present being made for the supply of a component pack (Pack 24) for the components—boost capacitor C602 etc.—associated with the line output transformer. It should meanwhile be noted that the capacitors (C601–3) are either high-voltage or pulse types; R605 is rated at 1W and R606 at 5W. The components can be mounted on the line output transformer itself provided they are  $\frac{1}{2}$ -in. clear of the transformer.

### CRT Outer Coating

The Aquadag c.r.t. outer coating has to be earthed of course as with a monochrome receiver. This should have been dealt with when we described the degaussing arrangements in Part 11 (February). Two long springs or lengths of braiding with springs at one end to provide tension should be fixed at each side of the c.r.t. magnetic shield on the inside so that when the shield is mounted over the c.r.t. the springs/braiding rest against the c.r.t. bowl. It is important that the springs/braiding make good electrical contact with the magnetic shield which in turn must be earthed by running a lead from the degaussing component tagstrip to 9E on the c.r.t. base panel.

### Modifications & Corrections

**Flyback Blanking:** The flyback blanking circuit has been modified as shown in Fig. 4. The field blanking pulses now come from point 4E on the timebase board as

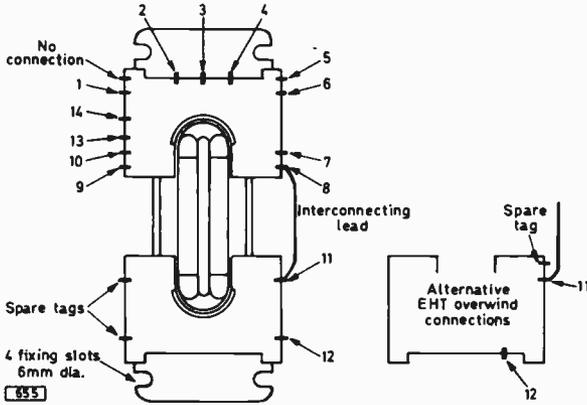


Fig. 1: Line output transformer tag identification.

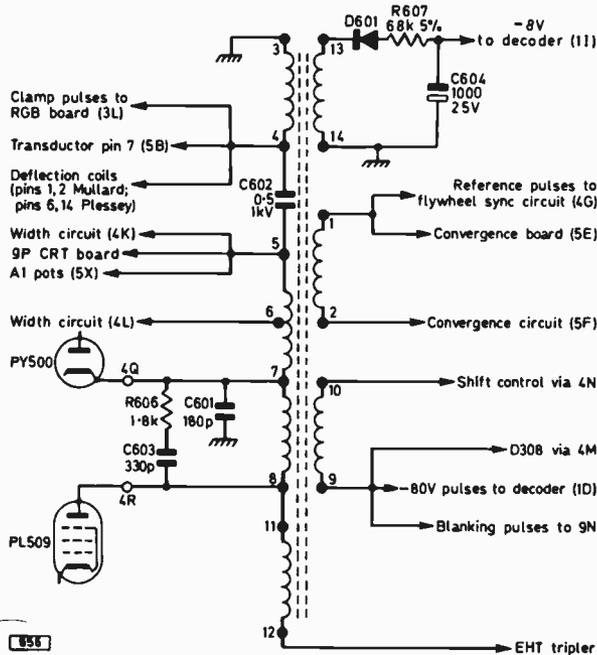


Fig. 2: Line output transformer circuit, showing all feeds to and from the various windings. Connect the earthed pins 3 and 14 to 6C on the power supply board. R605 is connected from the tripler (see Fig. 3 this month and Fig. 3, page 17, November 1972) to either pin 1, pin 3 or pin 4 of the line output transformer, giving e.h.t. level adjustment. Any low-power silicon diode can be used as the -8V rectifier D601, e.g. 1N4148 or 1N914. D601, R605-7 and C601-4 will be in Component Pack 24—details next month.

originally intended. The line blanking pulses are taken from tag 9 on the line output transformer and fed via a new capacitor (C704) and R709 to the junction R712/R708. The c.r.t. base panel arrangements need to be modified as follows: C704 replaces R709 on the board (see Fig. 2, May 1973), R709 being connected instead on the print side of the board from C704 to the junction C703/R712/R708. The print connection on the board between R710 and the original position of R709 must be broken. Despatch of Pack 22 was held up while these modifications were being sorted out and we acknowledge the help given us by Forgestone Components in making these changes.

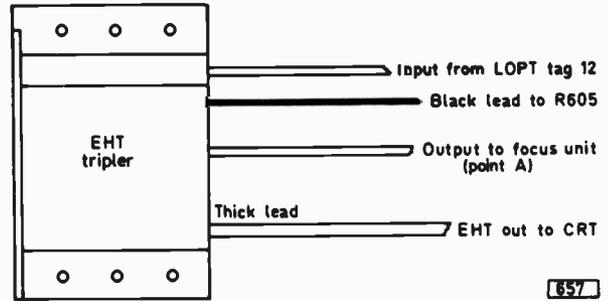


Fig. 3: Connections to the e.h.t. tripler.

**Degaussing Coils:** Anyone winding their own degaussing coils should note the following correction. The gauge of wire specified in the February issue for use with coils for the smaller sizes of tube (19-22in.) should have been given as 34 s.w.g., not 30 s.w.g. If the wrong wire is used the circuit resistance on switch-on will be too low.

**Line Oscillator Tuning:** The value of the line oscillator tuning capacitor C322 was incorrectly specified as 0.0033 $\mu$ F. It should be four times greater, i.e. 0.0132 $\mu$ F. To get the line oscillator to operate at the correct frequency an 0.01 $\mu$ F capacitor should therefore be added in parallel with C322. This capacitor has been given the reference number C332 and will be included in Pack 24. Good oscillator stability is essential in a colour receiver since pulses from the line timebase are used in the decoder and elsewhere and their timing is vital. C332 should therefore be a good quality component, e.g. RS  $\pm 2\frac{1}{2}\%$ , polystyrene.

**V.H.F. Varactor Tuners:** Mullard type ELC1042 v.h.f. varactor tuners are available from Forgestone Components, Ketteringham, Wymondham, Norfolk at £4.95 including postage to Eire. Other overseas constructors requiring this tuner should write to Forgestone for a postage quotation.

**Convergence Clamping Transistors:** There have been several slightly different batches of the NKT279T. In each case however they are coded with a red spot which indicates the collector lead.

**Ident Coil:** It seems that in a few cases the wrong core has been supplied with the ident coil (L4 on the decoder board). The result is low-amplitude ident output and of course no colour since the ident sinewave is rectified to provide the chrominance channel turn-on bias. Constructors who have reached an advanced stage should bear this in mind. We are seeking information on how this point can be checked. The circuit works perfectly with the correct core.

**Line Output Valve Screen Resistor:** The 6W line output

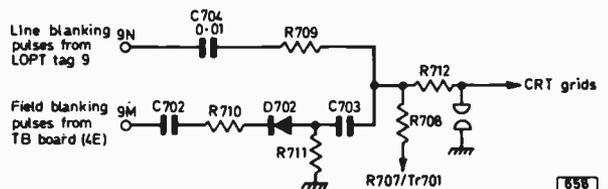


Fig. 4: Modified flyback blanking circuit.

valve screen resistor R351 runs hot and should be mounted off the board therefore, say by 10mm. Those constructors who have mounted this resistor close to the board could insert a small piece of asbestos beneath it. There is otherwise the possibility of damage to the board.

**Power Supply:** The problem with the mains transformer is being investigated.

We shall be providing a recommended switch-on procedure and clearing up other outstanding matters next month.

**Table 1: Module Interconnections.**

In the following table the individual module connection points are listed first, followed by the lead destination. The following abbreviations are used: Dec (decoder); IF (i.f. panel); Au (audio module); RGB (RGB board); TB (timebase board); Con (convergence board); PS (power supply unit); Deg (degaussing circuit); Tu (tuner/preamplifier board); CRT (c.r.t. base panel); LOPT (line output transformer).

**Decoder**

1A 6N (PS)  
1B Saturation control slider  
1C 2L (IF)  
1D 4M (TB)/LOPT tag 9  
1E 3E (RGB)  
1F 3D (RGB)  
1G 2D (IF)  
1H 2M (IF)  
1I R607/C604 (LOPT)  
1J 6C (PS), 2J (IF)

**IF Panel**

2A 6P (PS)  
2B 8K (Tu)  
2C 9B (Au)  
2D 1G (Dec)  
2E 3C (RGB), contrast control slider  
2F 8F (Tu)  
2G 8G (Tu)  
2H Contrast control (bottom)  
2I Contrast control (top)  
2J 6C (PS)/9J (Au)/8D (Tu)/1J (Dec)/3J (RGB)/control panel metal  
2K 8A (Tu)  
2L 1C (Dec)  
2M 1H (Dec)  
2N 4D (TB)  
L124/5 pin C 8L (Tu)  
L124/5 pin E 8M (Tu)

**RGB Panel**

3A 6N (PS)  
3B 6H (PS)  
3C 2E (IF)  
3D 1F (Dec)  
3E 1E (Dec)  
3F 5BB (Con)  
3G 5DD (Con)  
3H 5FF (Con)  
3J 6C (PS), slider and bottom of brightness control, 2J (IF)  
3K Top of brightness control  
3L LOPT tag 4

**Timebase Board**

4A 6I (PS)  
4B 6J (PS)  
4C 6G (PS)  
4D 2N (IF)  
4E 9M (CRT)

4F Deflection coils 6 or 3' (Mullard), 1 or 11 (Plessey)  
4G 5E (Con)/LOPT tag 1  
4H 9Q (CRT)  
4J 6C (PS)  
4K LOPT tag 5  
4L LOPT tag 6  
4M LOPT tag 9, 1D (Dec), 9N (CRT)  
4N LOPT tag 10  
4P 5A (Con)  
4Q LOPT tag 7  
4R LOPT tags 8/11  
4S 6D (PS)  
4U 6E (PS)

**Convergence Board**

5A 4P (TB)  
5B Deflection coils 1 or 2 (Mullard), 6 or 14 (Plessey)  
5C Deflection coils 1' (Mullard), 13 (Plessey)  
5D Deflection coils 2' (Mullard), 7 (Plessey)  
5E LOPT tag 1, 4G (TB)  
5F LOPT tag 2  
5G-5K Line radial dynamic convergence. See November, April and May issues as appropriate  
5L 6C (PS)  
5M Deflection coils 6' (Mullard), 4 (Plessey)  
5N Deflection coils 3' (Mullard), 8 (Plessey)  
5P 6J (PS)  
5Q-5T Field dynamic convergence. See November, April and May issues as appropriate.  
5U 9C (CRT)  
5V 9B (CRT)  
5W 9A (CRT)  
5X LOPT pin 5  
5AA 6H (PS)  
5BB 3F (RGB)  
5CC 9L (CRT)  
5DD 3G (RGB)  
5EE 9K (CRT)  
5FF 3H (RGB)  
5GG 9H (CRT)  
S401/2 L404. See Fig. 7, April 1973

**Power Supply**

6A Line (mains) from mains switch  
6B Neutral (mains) from mains switch  
6C Earth (mains), board earths, 9E (CRT), saturation control (bottom)  
6D 4S (TB), 7B (Deg)  
6E 4U (TB)  
6F 7A (Deg)  
6G 4C (TB)  
6H 3B (RGB), 5AA (Con)  
6I 4A (TB)  
6J 4B (TB), 5P (Con), 8J (Tu)  
6K 8I (Tu)  
6L 9A (Au)

6M 8B (Tu)  
 6N 1A (Dec), 3A (RGB), saturation control (top)  
 6P 2A (IF)  
 6Q 9D (CRT)

#### Degaussing

7A 6F (PS)  
 7B 6D (PS)

#### Tuner/Preamplifier Board

8A 2K (IF)  
 8B 6M (PS)  
 8C Tuner control unit (see Fig. 6, March 1973)  
 8D 2J (IF), tuner control unit (see Fig. 6, March 1973)  
 8E Tuner control unit (see Fig. 6, March 1973)  
 8F 2F (IF)  
 8G 2G (IF)  
 8H Tuner control unit (see Fig. 6, March 1973)  
 8I 6K (PS)  
 8J 6J (PS)  
 8K 2B (IF)  
 8L Pin C of L124/5 (IF), tuner control unit (see Fig. 6, March 1973)  
 8M Pin E of L124/5 (IF), tuner control unit (see Fig. 6, March 1973)

#### Audio Board

9A 6L (PS)  
 9B 2C (IF)  
 9C Volume control (top)  
 9E Loudspeaker (line)  
 9J 2J (IF), LS (chassis), volume control slider and bottom

#### CRT Base Panel

9A 5W (Con)

9B 5V (Con)  
 9C 5U (Con)  
 9D 6Q (PS)  
 9E 6C (PS)  
 9F Focus unit (point V)  
 9G Solder tag on blue lateral coil clamp  
 9H 5GG (Con)  
 9J 6C (PS)  
 9K 5EE (Con)  
 9L 5CC (Con)  
 9M 4E (TB)  
 9N LOPT tag 9/4M (TB)  
 9P LOPT tag 5  
 9Q 4H (TB)

#### Tuner Control Unit

See Fig. 6, page 232, March 1973.

#### Line Output Transformer, EHT Tripler and Focus Unit

See diagrams and text this month.

#### Controls

Volume: top 9C (Au)  
 slider and bottom 9J (Au)  
 Brightness: top 3K (RGB)  
 slider and bottom 3J (RGB)  
 Saturation: top 6N (PS)  
 slider 1B (Dec)  
 bottom 6C (PS)  
 Contrast: top 2I (IF)  
 slider 2E (IF)  
 bottom 2H (IF) } Connect screens of these  
 leads to metal of control  
 panel.  
 Mains switch: in, line and neutral from mains,  
 out, line to 6A (PS) neutral to 6B (PS)  
 Loop earth lead across switch to 6C  
 (PS)

## COLOUR RECEIVER PROJECT: ACKNOWLEDGEMENTS & ADVISORY SERVICE

Referring back to Part I of this series we did point out to readers that to embark on the design, engineering and construction of a colour television receiver is indeed an ambitious project, all the more so when it is carried out on a part-time basis. We have been pleased and flattered therefore at the interest shown in the project—this surpassed all expectations.

We would like to acknowledge the valued assistance and suggestions that have been made from time to time during the series, and in particular the lengthy and helpful discussions that have taken place between our designer, the magazine and the various component suppliers.

In a project of this magnitude it is inevitable that personal circumstances which make it difficult to keep up progress can arise; the pressures on us at this end have been great, but we have done our best to keep the problems to the minimum.

Not the least of our difficulties has been the component supply situation. In a market which has been turned upside down during the past couple of years, with manufacturing and trading policies altered, we have had amongst other things to contend with rapid and substantial price increases. The percentage of im-

ported components in electronic equipment today is not always appreciated and nothing can be done about price rises in this area. We would like to thank those in the component supply trade who have been directly involved in the project for their patience and co-operation in making available as quickly as possible the designer-specified components.

We are grateful for the encouragement given by the many readers who have written to us on this project, especially those who started with a full understanding of the involvement from reading Part I. In several cases it has been possible for us to incorporate constructive suggestions in the articles.

We have received a large number of letters from readers who have presented us with their particular problems and are answering these as fast as we can. Constructors will doubtless welcome the idea of some of the more common problems being answered in the magazine itself, and to this end we are setting up an advisory service. We will be publishing more details of this in the next instalment. Meanwhile we strongly recommend constructors to await the publication of full instructions before writing to us for advice.

# RENOVATING the RENTALS

## 15 PHILIPS G6 CHASSIS

CALEB BRADLEY B Sc

PART 1

ALTHOUGH this colour chassis dates back to the very beginning of colour television in the UK and has passed through many stages of modification including "pruning" from dual- to single-standard operation it has always been noted for its good picture quality when correctly set up. Some work may be needed to achieve this though since the circuit is elaborate—using no less than 21 valves and 17 transistors—and is festooned with far more components per stage than modern designs. Sets are readily available on the ex-rental market at fair prices, almost always in the version shown in the photograph, and are a good prospect for renovating. We are covering the dual-standard version of the G6.

The cabinet is supported on four legs that extend up each corner and are fitted with keyhole plates which hook on to bolts projecting from the cabinet corners. If the set is used without legs it looks rather strange unless the corners are covered in matching veneer. There is usually no knob present on the back where "tint" is stencilled; this control is often cut out as unnecessary on a properly adjusted set. Its function was to vary slightly the relative gains of the R - Y and B - Y output stages.

### Access to Chassis

Chassis accessibility is fair, the three printed panels (i.f., decoder and timebase) being mounted in a vertical frame which can be swung out at the top after removing two plastic pegs. This reveals the track sides of the panels, the power supply components at inside bottom and untidy hanks of wire going everywhere. The chassis hinge at bottom left is formed by a bolt which can be removed to

allow the frame to be withdrawn from the cabinet—this is the only way to get at some of the line output stage components. The intermittent plug and socket troubles that plague some monochrome sets of this make are mostly avoided on the G6 where the printed panels are wired in, although this increases the possibility of trouble due to dry joints. The convergence and A1 (background colour) controls are mounted on a shallow box which after removing four screws can be slid out of the set and stood on top of the cabinet for adjustment. Take care not to upset all your careful adjustments when sliding it back in!

### Tuner

The tuner is an integrated u.h.f./v.h.f. push-button type. The system for each button is set by rotating a slotted knob on the rear of the tuner with the button unlatched. The embossed arrows on these knobs are easier felt than seen. If an explorative child succeeds in latching down all six buttons at once they can be released by pressing the top one farther in.

### IF Panel


The circuit of the i.f. panel is shown in Fig. 2 and its layout in Fig. 1. There are so many tuned circuits that it is vital to refrain from twiddling, though it is not difficult to get a single core back to its correct position after a repair. Cores with the original factory sealant (a reddish goo) intact should certainly be left alone.

### Weak Contrast/Blank Raster

Weak contrast or a completely blank raster are common fault symptoms on this chassis and the tuner is usually wrongly suspected. Check both the r.f. and oscillator supplies to the tuner (12V 'A' and 'B') since it still works weakly if the former is missing, i.e. the r.f. transistor continues to work with the a.g.c. bias. Check the emitter voltages of the i.f. transistors T2142 and T2143—about 2.4V with no signal. These transistors can be faulty but most stock faults lie around the a.g.c. amplifier.
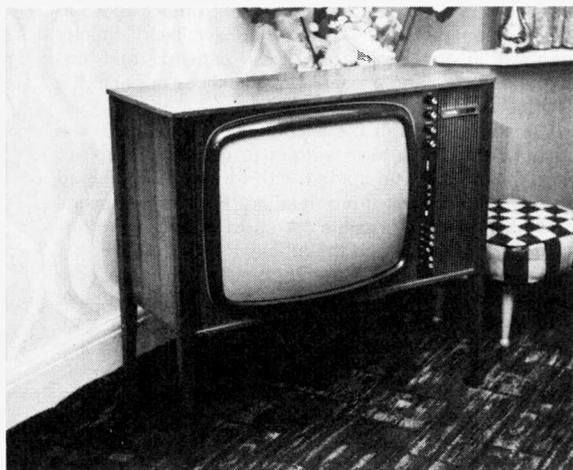
### AGC Circuit

The a.g.c. circuit operates as follows. T2145 is normally held on by bias from R2098 and the tuner a.g.c. voltage across C2040 is low. When a strong signal is received, the negative-going sync tips at T2144 collector draw current via X2153 so that the mean voltage on C2041 is reduced and in consequence T2145 collector voltage becomes more positive. The gains of the tuner and i.f. stages are thus reduced by the increased forward a.g.c. bias. X2151 prevents the i.f. a.g.c. bias rising above the voltage set by the potential divider R2161/2. The a.g.c. control R3485,



*The Philips Model G25K500, a 25in. receiver fitted with the G6 dual-standard colour chassis.*

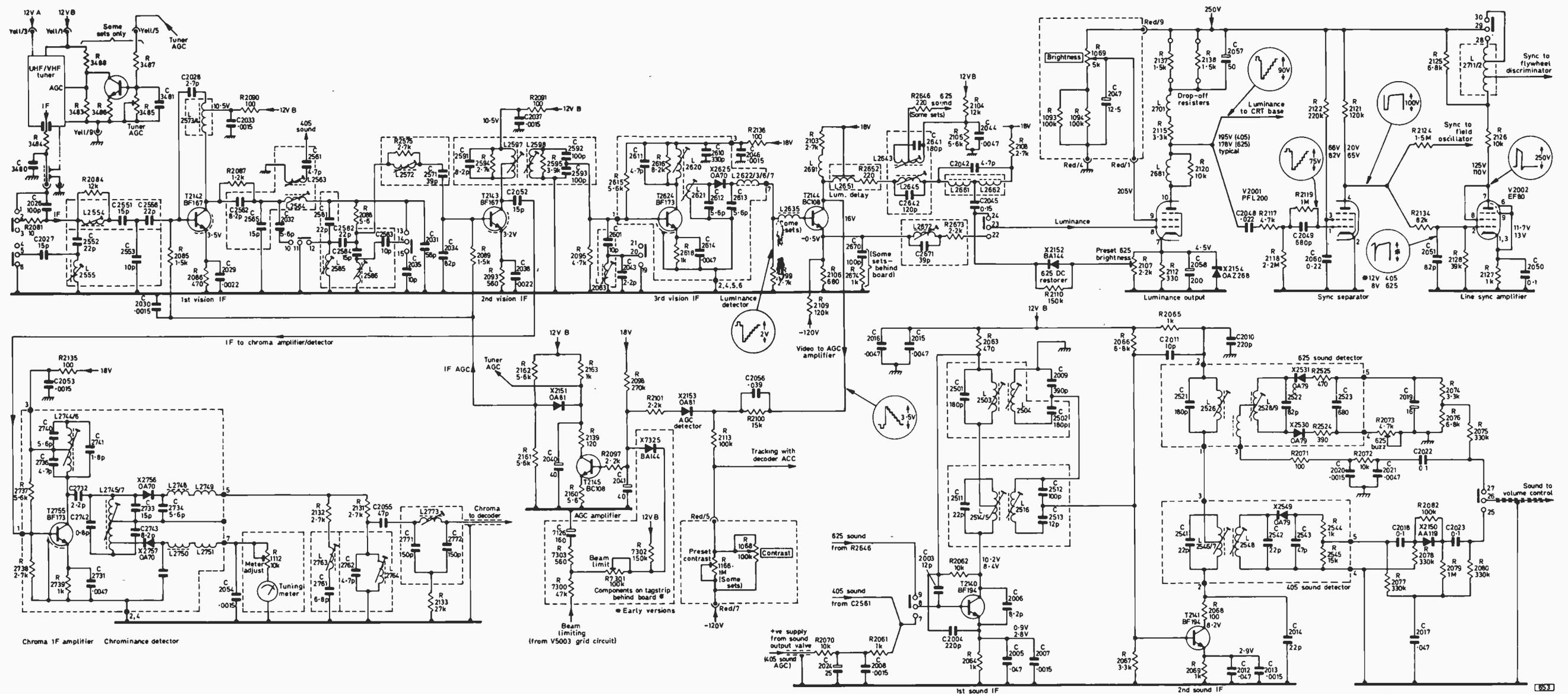


Fig. 2: Circuit diagram of the i.f. panel, which incorporates the luminance channel, sync separator and a.g.c. circuits in addition to the main i.f. channel and the sound and chrominance i.f. sections. The 405/625 system switch is shown in the 625 position. Where two voltage readings are shown the upper one applies on 405 lines and the lower one on 625 lines. During the long life of this chassis a number of modifications were introduced. These were mostly minor component value amendments. Modifications worth noting on the i.f. board are as follows: in later versions T2142 and T2143 are both type BF196, the tuning meter and R1112 are removed, and C2051 is changed to 5.6pF and connected in parallel with R2128; in earlier versions the screen grid of the sync separator V2001 is fed from a potential divider, R2122 being changed to 33k $\Omega$  and R2123 10k $\Omega$  occupying the position of C2060. With this latter arrangement the anode voltage of the sync separator is 85V and the screen grid voltage 57V. Also on earlier versions the switching on L2711/2 was omitted.

if fitted on the tuner, can be set as follows: adjust receiver for 0V across X2151 then set R3485 for 4.5V across R3488. Take care not to short-circuit R3488 since T3495 (top left above, marked "some sets only") may suffer.

The signal gain is also reduced by two other means: negative current from the contrast control(s) or conduction of the beam-limiter diode X7325 (X1165 in some circuits). The beam limiting supply is obtained from the grid of the e.h.t. shunt regulator valve and the effect is that if the c.r.t. beam current becomes excessive due to over-advanced contrast and brightness the contrast is reduced by a.g.c. action to prevent tube damage. The onset of limiting is set by R7301 (or R1161) and should only be adjusted after the e.h.t. regulator V5003 current has been correctly set. Adjust R7301 so that the regulator cathode

voltage (across R5054) cannot be driven below 0.1V by misuse of the viewer controls. A curious result of this arrangement is that incorrect line output stage adjustment can cause apparent i.f. faults due to false beam limiting.

Common faulty parts in this area are X2153, C2041, T2145 and X2151.

In the luminance signal chain, loss of picture can be due to the detector diode X2625 (or the chokes in the same can) going open-circuit, or faulty L2635 or T2144. Note that T2144 and T2145 collectors are connected to their cases, and that the BC109 is a superior replacement. Other blank raster culprits are dry joints on the luminance delay line L2651—this can give double-image effects which look like gross misalignment—and of course the luminance output valve V2001. Two similar looking cases of

intermittent luminance were found to be caused by very different things: faulty C2592/3 in one case and a broken pin on V2001 socket in the other. The springs in this socket tend to weaken since V2001 is a tall valve mounted horizontally without support.

Brightness on 625 lines is preset by cathode-to-grid d.c. feedback via R2107 and the d.c. restorer diode X2152 which conducts only on sync tips. A convenient injection point for our crosshatch generator (see TELEVISION September 1972) is at X2152 cathode. Variable brightness level can be due to the zener diode X2154 being open-circuit. The viewer brightness control R1069 varies V2001 screen voltage and has a very restricted range. Thus R2107 must be set carefully. Uncontrollable brightness is caused by R1069 going open-circuit. Smearly luminance

with poor field hold can be due to C2047 being faulty: on the single-standard G6 chassis the same symptom can be caused by the black-level clamp transistor T2146 (not shown in Fig. 2).

Intercarrier buzz on 625 sound, most noticeable on pictures with large white content, can be minimised by adjusting R2073. If necessary trim L2526/9 also, using a narrow plastic screwdriver.

The chrominance i.f. amplifier/detector stage T2755 is generally reliable though C2736/C2740 can be responsible for intermittent colour. The vast majority of colour stock faults lie on the decoder panel which will be dealt with in a later part.

CONTINUED NEXT MONTH

# Workshop HINTS

by VIVIAN CAPEL

TUNING capacitors in transistor radio receivers tend to be in sealed units a fraction of the size of the older air-spaced gang that was a familiar part of every valve radio receiver. A fault therefore usually means replacing the unit—little can be done in the way of repairs. To offset this snag however the protection provided by the casing means that faults are not all that common. This type of gang has been made possible because of the much lower stray capacitance in the input and oscillator circuits of the miniature layout, and simplified wiring to the wavechange switch.

## Shorts

The service engineer still encounters many of the older type sets in the course of a week's work however. A not uncommon fault with these is a short across one section of the gang. The trouble is easily identified because the receiver works at one part of the tuning scale—usually the high-frequency, low gang capacitance end—then as the tuning knob is rotated the stations disappear amid a loud crackling sound. This latter effect indicates that the gang is responsible rather than oscillator cessation which sometimes occurs at different parts of the tuning range.

Clearing the short can be tricky as it is not always possible to see just where it is taking place while there are several possible causes. The most common cause is a bent moving vane, usually one of those on the outside of the assembly. The first step therefore is visual examination of the outside plates, especially at about the place where the crackling starts. The culprit can often be spotted and a cure effected by gently bending it back to the straight position.

## Bearing Faults

Sometimes however no deformation of the outer plates can be seen and further examination is necessary. Often the bearings of the moving vanes come loose, resulting in fore-and-aft movement. With the narrow clearances between the fixed and moving vanes shorts then inevitably occur. The fault in this case will be of an intermittent nature: sometimes it will be possible to traverse the whole tuning range without trouble while at other times shorts will occur at different spots on the dial each time the tuning knob is swung through its range. The diagnosis can be confirmed by gently pulling and releasing the tuning spindle: play if present will then be apparent.

Adjustment is by means of a large screw at the back of the gang in the same plane as the spindle (see Fig. 1). First loosen the locking nut, then screw in the bearing

adjustment screw until some resistance is felt. Do not over-tighten as this will make the tuning unduly stiff, causing unnecessary wear, and may push the vanes too far forward causing shorts on the other sides. When you think the adjustment is about right try the spindle for play and undue stiffness: if there is still some play the screw needs a fraction of a turn more but if the spindle is tight to turn the screw needs to come back a shade. Having got the adjustment right keep the screwdriver in the slot to hold the screw in the correct position and then tighten the locking nut. If this procedure is not followed the screw may turn with the nut. Then check again for play and stiffness: sometimes the effect of tightening the locking nut is to pull the adjusting screw back against one wall of its thread, especially if it is rather slack in the housing. This will introduce play again and the only way to overcome the problem is to readjust after once again slackening off the locking nut. This time slightly over-tighten the screw (an eighth of a turn or less is usually sufficient). Then when the locking nut is tightened the adjustment will come right. This incidentally is a ploy that must sometimes be used on bearings other than in the tuning gang.

## Fixed Vane Mounting

Another cause of shorting vanes is rather more difficult to put right. The fixed vanes are usually mounted to the metal frame by means of ceramic pillars. If one or more of these breaks the fixed vanes are no longer fixed! This fault is not easy to diagnose unless one is looking for it: I have more than once observed repairmen spending much time and nervous energy trying to clear shorts by bending the moving vanes when it was the fixed ones that were at fault through being loose in this way.

Here again the effect will be intermittent with the shorts appearing at irregular positions and sometimes not at all. Inspection of the ceramic posts will in most cases soon reveal the break, but not always. Sometimes a pillar will shear off where it enters the hole in the frame and everything will look perfectly sound from the outside. The only means of telling where the trouble lies is to gently move the terminal tag of each set of fixed vanes in turn. It will then be seen if and where the vanes move as well. If the problem is a broken pillar and it is not obvious from a visual examination which one is faulty further gentle movement of the vanes will reveal the offending one. A pair of tweezers is useful for doing this. They can grip various parts of the vane assembly and also prevent too much force being used and one of the sound pillars being broken as well.

After identifying the broken pillar we must effect a repair: this is best done with one of the epoxy-resin


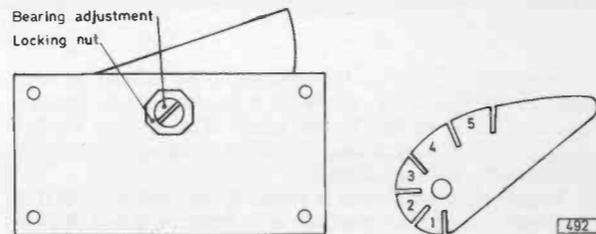


Fig. 1 (left): Gang capacitor rear view, showing the bearing adjustment screw and locking nut.

Fig. 2 (right): End plate of moving vane, showing slots which enable sections to be bent for optimum alignment over the whole tuning range. The correct order of adjustment is as shown (1-5).

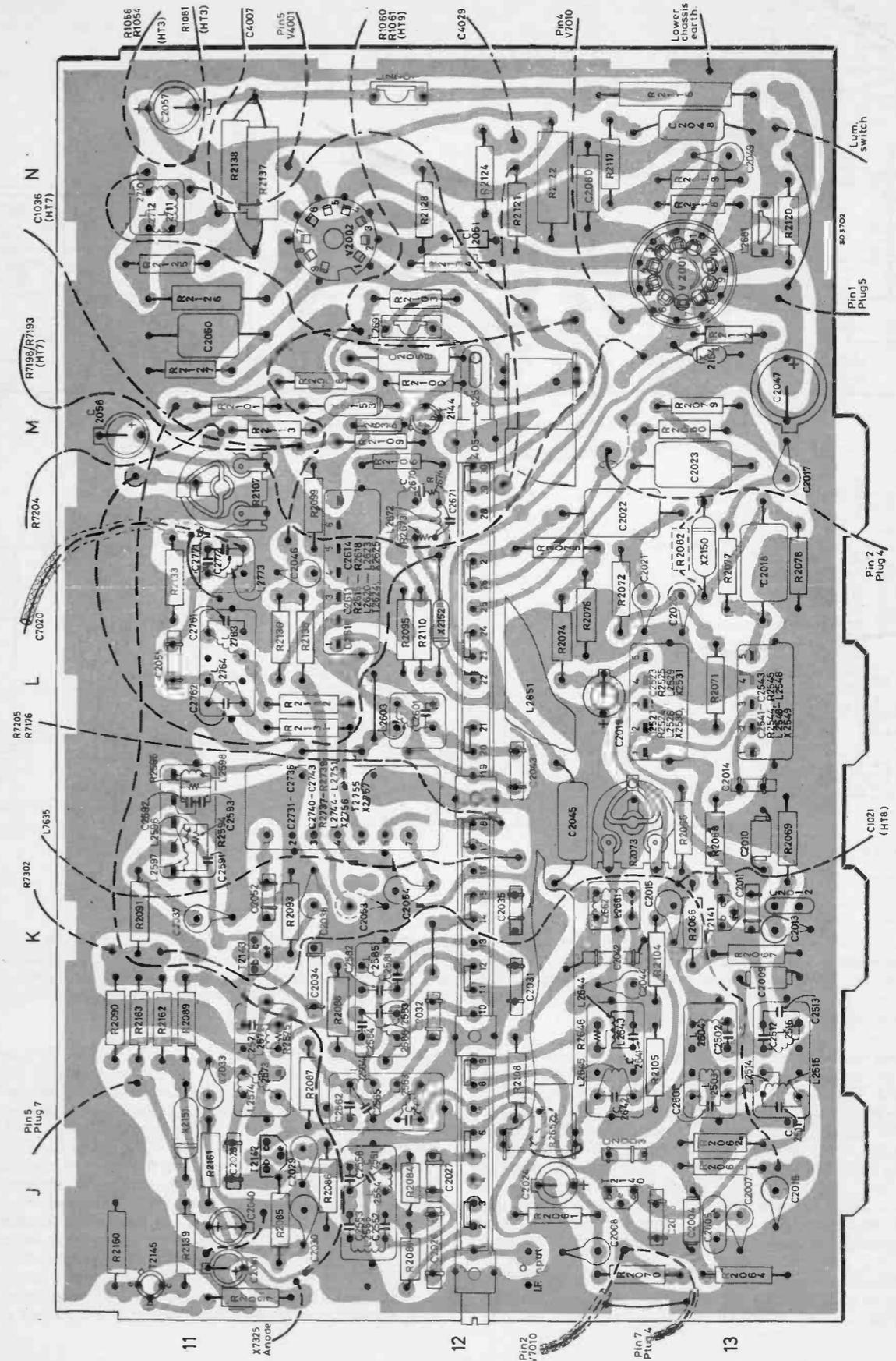

adhesives such as Araldite as this will surround the break and strengthen the actual pillar. It may not be possible to use a conventional adhesive as these need application to the broken faces. Also it may not be possible to force the pillar apart without breaking the others in order to do so. The use of epoxy-resin adhesives makes a longer job of it as they take a number of hours to set—though the process (and the strength) can be increased by application of heat. The main thing to watch out for is that the vanes set in the right position. This means not only putting them so to start with but also ensuring that any vibration or jolt while they are setting does not displace them. To prevent this happening the gang can be fully closed and a few strips of thin card placed between the vanes to hold them in the central position. It may be that the gap is too small even for thin card in which case feeler gauges should do the trick.

### Deformed Inner Plates

Especially with older receivers shorts on the gang are sometimes traceable to deformed inner plates among the moving or even the fixed vanes. It is not always possible to examine these and as a result identification of the offending one can be difficult. First we must establish which set of plates is giving the trouble, the oscillator or the r.f. ones. A meter switched to the lowest resistance range will usually identify the faulty set. In some cases there will be a parallel resistance consisting of the oscillator or r.f. coils. This can be low but in most cases will exceed several ohms. When the vanes are rotated the short will be observed as a lower reading. If in doubt or if the available meter does not read low enough to distinguish between a short and the low coil reading the lead to the gang can be unsoldered and a reading taken without the external circuit.

Having decided which set of vanes is at fault the next thing is to locate the offending one. This may be easier said than done. Look down from the top as the vanes enmesh: if this does not reveal the trouble look along the side with the gang at eye level and note whether all the vanes are parallel. Finally if all else fails make up a test circuit consisting of a battery and a suitable lamp and connect it in series with the gang, disconnecting the receiver lead. As the vanes enmesh the lamp will light when the short appears; but, more helpfully, there will be a minute spark between the shorting vanes. If one looks down or along the vanes viewed in subdued light this spark will be visible and indicate immediately which vane is responsible and where. All that then remains is to bend or prise the vane as appropriate.

After bending any of the vanes leave the gang for a short while before completing the job. Sometimes if the metal is at all springy the vane will return to its former position or something near it and the short will recur. In this case it may be necessary to bend the vane beyond the correct position so that it ends up where it should.

### Alignment

Having dealt with the gang check the alignment and ganging over the tuning range as good alignment may not now be present over the whole scale. Tracking can be restored by bending the split end-plates of the r.f. moving vanes (see Fig. 2).

This is a problem that sometimes occurs with u.h.f. television tuners, especially in areas that can receive two groups of transmissions. Normally the three u.h.f. stations are close together on the scale so that the tuner

does not have to operate over a wide range. Hence any alignment that may be required can be carried out on the frequencies of the local stations. Where two groups of channels can be received it is a different matter: alignment must then be at an optimum at least over the range covered by the two groups.

U.H.F. tuner gangs being small and rigid rarely suffer from shorts but sometimes the tracking over the tuning range is not as good as it could be and it is found that when alignment is carried out around the frequencies of one group of channels it is poor on the other and vice versa.

As with radio tuning gangs split end plates are usually provided to take care of these problems. In either case it is essential to start at the high-frequency end of the scale, that is with the gang fully out. Align by bending the plates for optimum results. Then proceed by meshing the gang and lowering the frequency, bending the sections that have just come into mesh if the alignment of the channels at that point is not at optimum. If you start at the lower-frequency end, with the gang meshed, any alterations subsequently made to the high-frequency channels with the gang partially disengaged will affect what has been done before because retuning to the lower frequencies will bring in the same vane portions that have been bent to affect the higher frequencies. Going the other way, from high to low, does not have this effect because the vane portions bent to align the lower frequencies do not have any effect on the high ones which have already been aligned.

The actual bending is not as precise a method of alignment as could be desired since the capacitance of the bending tool will obviously have a major effect. A long insulated object such as the ubiquitous knitting needle can be used to push the plate inward. If the alignment becomes worse obviously the plate needs to be bent outwards to reduce the capacitance but if it improves then some idea of the amount can be obtained by pushing harder until the gain goes beyond optimum and starts to fall again. The optimum position can be noted and the vane permanently bent to it. If an optimum setting cannot be obtained then other alignment factors must be investigated. The split plates have only a limited capacitance variation and are not a substitute for external trimmers and core tuning. These should be tried first in the normal alignment procedure: only if optimum ganging cannot be obtained should the split vanes be adjusted.

It is not unknown for shorts in radio receiver tuning capacitors to be caused by conductive material between the plates. Lumps can sometimes be seen adhering to the inner surfaces. If this is the case do not try to flush them out with cleaning fluid as the alignment will be upset and the fluid will take a long time to dry out. If realignment is attempted in these conditions it will drift off as the gang dries. Instead dry clean with card strips passed down between the vanes. It is not necessary for the gang to be meshed to do this; in fact it is easier to do if the gang is not meshed.

Finally while on this subject it is worth mentioning a fault that although not common can be extremely baffling. This is an open-circuit earth to the gang. The chassis connection is one of those things one tends to take for granted, especially after years of servicing wired chassis in which the gang is in physical contact with the chassis. Grommet mounting and printed circuits necessitate a separate earth connection and on at least two occasions I recall being led a merry dance by an open-circuit lead. Now whenever faced with a fault in the r.f. side that doesn't respond to the usual tests I always make a resistance test from the gang frame to earth!

# LETTERS

## LINE SYNC TROUBLES

With reference to your servicing article on the Bush TV181S/Murphy V2019 series I would like to comment that in 99% of cases where we have experienced line drift, line flicker and the line timebase being right off speed (too fast) in these models the cause has been the 10 $\mu$ F electrolytic 3C31 which smooths the supply to the line oscillator being in various stages of open-circuit.

In *Your Problems Solved* (May) Mr. Cork mentions the problem of three pictures side-by-side following width control trouble (burn up) in a set fitted with the BRC 950 chassis. He will probably find that when the width control burnt out it carbonised the flywheel line sync panel which is situated directly above the width control on this chassis: this gives the effect of three pictures side-by-side, i.e. line right off speed. I have personally experienced this fault and there was much head-scratching before I realised what had happened!—**R. Bettison** (*Boston*).

## FIELD SLIP: BRC 1500 CHASSIS

Since the appearance of your article on servicing the BRC 1500 chassis last August we have noticed that a lot of sets fitted with this chassis have been coming in with the complaint that the field keeps slipping. This is associated with a hum bar on the picture, and pulling. The cause has in all cases been the smoothing capacitor C56 (400 $\mu$ F) in the h.t. feed (HT6) to most of the transistor stages being open-circuit.—**P. Parrock** (*Gravesend*).

## BRC 1400 CHASSIS MODIFICATIONS

THERE are a couple of problems that seem to keep coming up on this chassis, picture pulling when changing channels or on peak whites, and buzz on sound. As a TV engineer who is well aware of the problems on this chassis I would like to draw your readers' attention to the following modifications which will solve most of the trouble.

**Pulling:** Remove the sync coupling components R44 (10k $\Omega$ ) and C40 (0.1 $\mu$ F) and insert in their place a single 3,000pF capacitor.

**Buzzing:** Change the video amplifier screen grid resistor R36 from 3k $\Omega$  to 8.2k $\Omega$ . It is also a help to convert the set to u.h.f. only operation by disconnecting one end of the 405 vision detector diode W4: although a reverse bias is

applied to W4 on 625 it nevertheless tends to have a varactor effect on the final vision/sound i.f. circuit on this system. Careful adjustment of the intercarrier sound coil L27 for minimum buzz, also the ratio detector balance control R87, should improve matters. Some buzz is picked up by the coil assembly L27/L28 from the field scan coils and a factory modification is to fit a metal shield over the can. This is usually bolted into the formers but can be soldered to the can.

Another useful modification to this chassis is to add a 100pF capacitor across the line sync pulse coupling capacitor C43: this increases the locking range of the line hold control, a source of trouble in some receivers.

These modifications really work. Unfortunately in some sets the i.f. coils will be found to have been altered as the buzz sounds like an alignment problem. I modify every 1400 that comes my way in this manner and it only takes a minute.—**L. E. Francis** (*Stourport, Worcs.*)

**Editorial comment:** To counter the effect of the 405 vision detector on 625 lines another modification is to increase the reverse bias applied to it on 625 lines from 12V to 20V. The bias feed resistor R35 is taken to a potential divider connected across the system-switched h.t. line to provide the required 20V. We must apologise for an error in *Your Problems Solved* recently when dealing with the problem of 625 sound buzz on this chassis (see page 330 of the May issue). The local/distant control R11 is of course operative on 405 lines only: it can be used to remove buzz on this system in strong signal areas.

## TELEVISION COLOUR RECEIVER

I would be interested to hear from any constructors (preferably residing locally) who are building the "Television" colour receiver, with a view to corresponding in connection with minor constructional problems, most economical sources of components, etc. Would any correspondents be kind enough to enclose a stamped, addressed envelope. Some years ago I offered through your columns to give away old copies of the magazine and ended up with some 400 letters and expenses totalling over £8 for returning POs and buying stamps to reply to those I was unable to help.—**J. F. Hitchcock** (*86 Reigate Avenue, Sutton, Surrey*).

**Editorial note:** We would be interested at the magazine in hearing in due course from readers who have successfully completed construction of the set: our main concern at present is to obtain a set of *average* circuit voltages since those obtained from the prototypes known to us could be misleadingly to one side of the tolerance ranges.

## TELEVISION AND PRACTICAL WIRELESS AT THE BERLIN RADIO SHOW

**Television and Practical Wireless** are to take part in an overseas exhibition for the first time at the end of August. The **International Radio and TV Exhibition** to be held in Berlin from August 31st to September 9th is one of the largest exhibitions of its kind. Of special significance this year is the celebration of the 50th anniversary of the official commencement of transmissions from the first German radio station. There will be 23 exhibition halls and four pavilions as well as extensive open-air grounds. Over 20 countries are participating.

The displays will cover all types of electronic home entertainment systems and also servicing, studio and transmission equipment. There will be television transmissions from the main hall.

**Television and Practical Wireless** will be participating in the technical press section. Visitors will be able to see much of the recent work published in the two magazines and get an idea of the exciting new projects to be featured in future issues.

If you are in Berlin at the time of the exhibition we recommend a visit.

# LONG-DISTANCE TELEVISION

## ROGER BUNNEY

APRIL 1973 was a most eventful month. We normally expect an improvement in Sporadic E conditions at this time as a prologue to the main season which starts in May and there have certainly been improving conditions. The spectacular news however revolves around two other events.

On April 1st in the late afternoon a large Aurora was observed producing the usual interference and disturbance throughout Band I and extending into Band III—I noted various effects up to 220MHz. Reports on this particular Aurora have come in from the UK and Europe—all credit is due to those vigilant enthusiasts who were active on what appeared to be just another quiet day. I noted the Auroral effects—rumbling, hum and other noises not unlike short-wave radio—on switching on at 1720 BST and must confess that at first I thought a preamplifier had gone unstable. On changing amplifiers however, there was no result other than a continuation of the interference so the aerials were rapidly turned towards the north, a noticeable peak being found towards the north east. Signals were certainly trying to get in but with the patterning at high levels it was all but impossible to resolve anything. Just after 1800 however there were several short bursts of signal—unfortunately programme material which could not be identified. The interference died down and eventually disappeared at 1930. A check for the second phase of the Aurora revealed very low-level “noises” until just after 2400 so the afternoon phase was certainly the strongest.

The second spectacular news is of reception which may be either 100% F2 propagation or partial F2/SpE occurring in the UK—more on this later!

Several Sporadic E openings have been noted and although they cannot be compared with the big openings of the main season it is certainly a pointer to better things to come. The period around the 19th was particularly active and Graham Deaves noted ORF (Austria), TVP (Poland), and CST (Czechoslovakia). The tropospherics also showed a lift, with u.h.f. active towards the end of the month—specifically the 25–27th. The Lyrids meteor shower was expected to peak on April 22nd and during the morning/evening periods activity was noted particularly on chs. R1/2

My own log for the period—deleting Belgium ch.E2 (as previously mentioned)—is as follows:

- 1/4/73 CST (Czechoslovakia) ch.R1—SpE; WG (West Germany) ch.E2—MS; also unidentified signals via Aurora.
- 5/4/73 CST R1—MS; NOS (Holland) E4—trops.
- 6/4/73 CST R1—MS.
- 8/4/73 DFF (East Germany—GDR) E4—MS.
- 9/4/73 CST R1—MS.
- 10/4/73 DFF E4—MS.
- 12/4/73 TVP (Poland) R1—MS; NOS E4—trops.
- 13/4/73 WG E2—SpE.
- 14/4/73 SR (Sweden) E2—MS—see later; unidentified programme on ch.R1 0745 SpE.
- 15/4/73 WG E2—MS; unidentified sports programme ch.E2 1800—suspect TVE (Spain).
- 16/4/63 NOS E4—trops.
- 18/4/73 NOS E4—trops.

- 19/4/73 CST R1; RAI (Italy) IA, IB; TVE E2. All SpE, opening for 1 hour late morning.
- 20/4/73 WG E2; CST R1; Switzerland E2; TVP R1—all short SpE; BRT (Belgium) E8, 10—trops.
- 21/4/73 WG E2; CST R1—both MS.
- 22/4/73 TVP R1—MS.
- 23/4/73 NOS E4—trops.
- 25/4/73 CST R1; SR E2—both MS.
- 26/4/73 ORTF-2 (French 2nd network at u.h.f.)—various transmitters via trops.
- 27/4/73 SR E2—MS; NOS E4—trops.
- 28/4/73 TVP R1—SpE.
- 29/4/73 RTP (Portugal) E2—SpE.

On April 14th the Swedish TV1 network was received on test card but with a variation—the PM5544 has struck again! Since then other reports which suggest that various identifications are being used have come in. Certainly the lower black rectangle carries the identification “Sverige” while the upper rectangle has “TV1” as an identification with possibly another word.

Over Easter the receiving system was completely changed, from the old Bush TV62s to Murphy types 849/879 (Bush TV125 series). The new receivers have been modified somewhat, the existing tuners being demoted to act as i.f. preamplifiers. Tuning is by means of external varicap units—the frequency is displayed on a 4in. meter. The system gain is extremely high—perhaps too high. Never have I been so well equipped for a coming season! Since this particular chassis (Bush) seems well suited to DX use I shall be preparing an article shortly detailing the modifications and also the varicap tuner arrangements.


Radio Nordsee International (6205kHz) 0900 GMT Sundays and Radio Nederland (6085, 6020kHz) 1830–1950 GMT Thursdays (DX Jukebox) are both at present running TV DX courses. The latter organisation provides a series of typed lessons. We have seen the first half of the 13-lesson course and can recommend it. The object is to encourage more listeners of course. Unfortunately by the time this appears in print it will probably be over. The address of Radio Nederland however is Radio Nederland Wereldomroep, PO Box 222, Hilversum, Holland—write care of DX Jukebox. The frequencies given are for the 49-metre band in Europe.

Good homes (TV DX homes that is!) are required for the following sets. John Penruddocke of Dean Hill Farm, West Dean, Salisbury, Wilts has a 19in. CCIR system B set with fully loaded tuner (E2-11) and high gain (three vision i.f. stages) made by Westinghouse for export to Africa. This is a modern, compact valved receiver. T. C. Bray of Sparkes Place, Womersley, Nr. Guildford, Surrey has a Murphy Model 849U (ideal for DX TV) with video detector switching split from main “gang”. If anyone is interested in these sets please write to the owners (not to us, please) enclosing a s.a.e. Collection must be arranged.


### News Items

*Jordan:* Following recent comments on colour plans we understand that an English company is to install a 15kW (not e.r.p.) transmitter and new aerial system “outside Amman”. Our Cyprus friend Mr. Papaeftychiou who has


**DATA PANEL 24—2nd series**

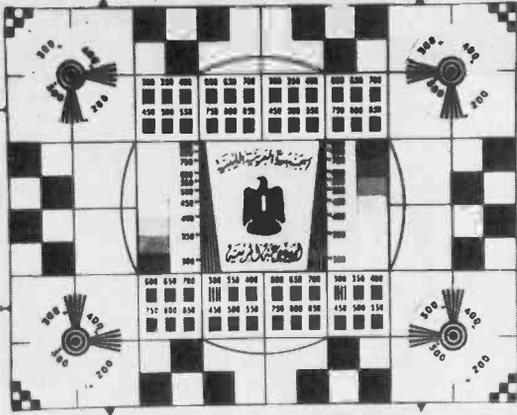

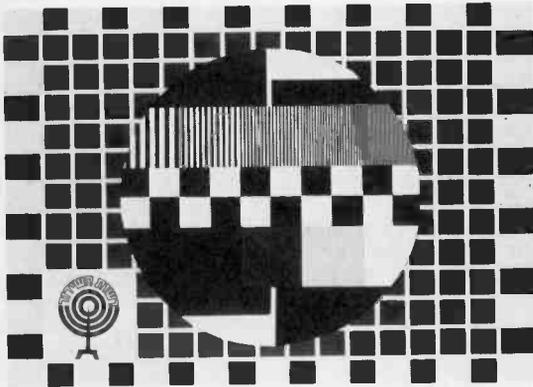
Test cards used by the Libyan Broadcasting and Television Service, courtesy Libyan broadcasting authorities and Michael Dolci. The "official version" is that shown on the left: the eagle appears to be the common factor.



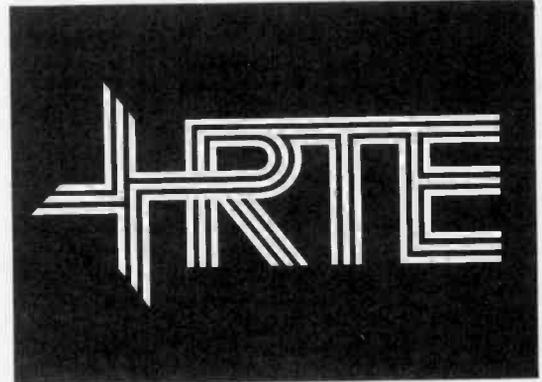PM5540 test card as used by the Israel Broadcasting Authority. Courtesy the Authority, Jerusalem, and Keith Hamer.



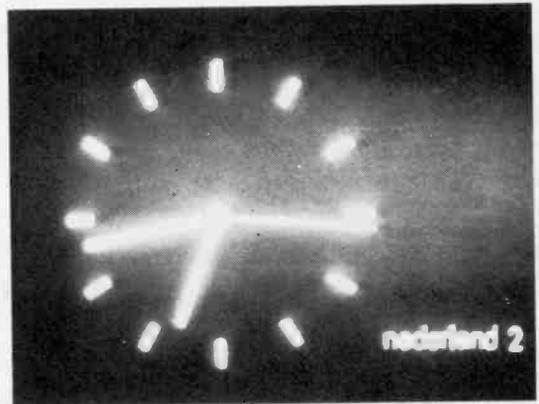Station identification slide used by Radio Telefís Éireann. Photograph courtesy of Keith Hamer.



Clocks: Czechoslovakian clock left, received by Ryn Muntjewerff in Holland. Right: clock used by NOS (Holland). The NOS-1 one is similar. Courtesy Europese Testbeeldjagers.

been monitoring Amman ch.E3 has noted captions advising viewers to switch to ch.E8 for their foreign pro-

grammes. Previously the ch.E6 transmitter carried foreign programmes—there is split programming from Jordan

Television for some hours in the evening.

*Greece:* Increasing activity at u.h.f. is indicated in the latest World Radio-TV Handbook. The Greek Armed Forces Television Service (YENED) is planning as follows: Thessaloniki ch.E30, Thassos Is. ch.E23 (both 1,000kW) and Thira Is. ch.E29 to be operating in 1973. Several of their lower-powered Band III transmitters are to be increased to 60kW e.r.p.

*East Germany—GDR:* Our contact here advises that Brocken ch.E34 increased power on April 2nd to possibly 1,500kW (at present listed as 1,000kW). It is indicated that the transmitter is 1190 metres a.s.l. (3,370 feet). Test and programme times are as follows: DFF-1 test transmissions 0700-0745, programmes 0745-2300, weekdays and Saturdays; 0800-0815 and 0815-2300 respectively on Sundays; DFF-2 test transmissions 1300-1845, programmes 1845-2230, daily. (All times GMT.)

*Dubai-Trucial States:* Keith Hamer tells us that this station is using the Philips PM5540 test card (see column April 1973). We understand that this state/country is called United Arab Emirates.

*International Waters:* From the Europese Testbeeldjagers we hear rumours about a pirate TV station called "Radio King": radio and TV commercial programmes are said to be about to start.

## Exotic Reception

On April 24th I received an urgent 'phone call from Hugh Cocks of Mayfield, Sussex. It seemed that something rather unusual was being received. Hugh had noted the familiar checkerboard on ch.E2 at 1542 (BST) with smeary video—assumed to be RTP (Portugal). At 1600 the RTP ch.E2 signal was covered with a "rumbling effect"—a black bar covered the lower part of the picture. Hugh switched off at 1630, assuming RTP via SpE. When operational again at 1655 a programme was found. At 1700 the same ch.E2 programme was noted carrying the news in *English*. The sound channel was monitored for some time and the accent indicated a similarity to the South African "Dutch type English". The 'phone call to yours truly at 1720 (at my place of work) hurried me to the Eddystone v.h.f. receiver. Certainly on ch.E2 vision (48.25MHz) a weak vision carrier could be heard, fading slowly into the noise. Unfortunately an ever strong ch.B3 local made attempts to resolve the sound channel (53.75 MHz) unsuccessful. By the time I had arrived home some 90 minutes later nothing was left of course!

I feel certain that this was an "exotic", bearing in mind that the signal was from a southerly direction and in the English language. The fact that some four weeks earlier Solar activity was at a high level—resulting in a flare and Aurora—coupled with the 27 days for the Sun's rotation could well mean some form of F2 reception (slightly too early in the day for TE). The sound tape Hugh sent included an Arabic musical programme—probably a harmonic from a radio transmitter—indicating that this too was "picked up" on one of the hops. The point is whether F2 conditions exist sufficiently north of the Equator to propagate a signal into North Africa after which the signal could be propagated into the UK via SpE—hence the arrival of the Arabic harmonic that would have originated in North Africa. We are awaiting word from our Mediterranean friends to check whether anything was noted by them during this period. I feel our congratulations are due to Hugh for this extremely interesting and intriguing reception—certainly this could be one of the longest TV DX hauls for several years.

I regret that space (lack of) means that letters are held over this month.

## For the Beginner to DX— concluding instalment

Aerials for Band III and higher frequencies are much more critical than those for Band I regarding bandwidth, matching and gain performance. To obtain the best performance at these frequencies it is unwise to attempt home construction. There are a number of manufacturers who devote considerable finance to aerial research. The outcome is that they have aerials that give excellent performance unlikely to be bettered by a home constructed array.


As mentioned last month we have a bandwidth problem—in the case of Band III we must cover 174-220MHz (chs.E5-11 vision) while at u.h.f. the coverage needed is 470-860MHz (chs.E21-68). Fortunately a number of wideband Band III receiving arrays are available, notably the J Beam Astrabeam, in versions with up to 11 elements or more when arrays are stacked. It is also possible to obtain certain West German wideband Band III aerial arrays such as the Fuba ones. The u.h.f. frequencies present a problem in that to obtain full coverage with high gain at least two arrays are required, namely for Band IV (chs. E21-37) and Band V (chs.E39-68). In the UK the use of a group A and a group E array would provide the necessary bandwidth. An alternative approach is to use a lower gain array with an extreme bandwidth—over the whole u.h.f. band—such as a log-periodic aerial. We understand that Fuba market a 27-element wideband u.h.f. array covering both Bands IV and V. There is a considerable number of high-gain u.h.f. arrays available and we suggest that the prospective purchaser investigates the literature available from Aerialite, Antiference, and J Beam Aerials.

Over the past few years a variation of the normal Yagi array featuring a more complicated director structure has appeared. This considerably increases the gain of the aerial system by enlarging the capture area. The structure can be seen in the May column where the J Beam MBM70 was illustrated.

Aerials for tropospheric work should be erected as high as possible and the best quality feeder used to avoid undue loss of the very weak signals that will be encountered. It is advisable to mount aerials at least 3ft apart to minimise unwanted absorption, mismatching and other effects. A slight upward tilt to the array can be beneficial and as with Band I horizontal polarisation is the order of the day.

Aerial preamplifiers are essential for tropospheric reception and in these days of very low-noise transistor preamplifiers it is possible to work down to signals of a few  $\mu V$  at u.h.f. There have been several articles in these pages over the past three years giving details of aerial preamplifiers suitable for DX use at the various TV frequencies. Masthead preamplifiers can be used to advantage, particularly at u.h.f. There are several commercial ones available giving part coverage of the u.h.f. spectrum or indeed the whole u.h.f. bandwidth. These are powered "up the download" and are most effective in overcoming cable losses and improving weak signal performance. The one disadvantage is that in the unlikely event of a fault considerable difficulty may be experienced in reaching and repairing the unit.

Tropospheric reception is one of the more difficult modes because of the weaker signals encountered. Great care is required therefore in installing (and selecting) aerials for this work. Provided care is taken the results will justify the effort put in, giving impressive and distant reception at frequencies that would otherwise produce only mediocre signals. Such reception is dependent on tropospheric conditions of course, but given the best aerials optimum results will be obtained.

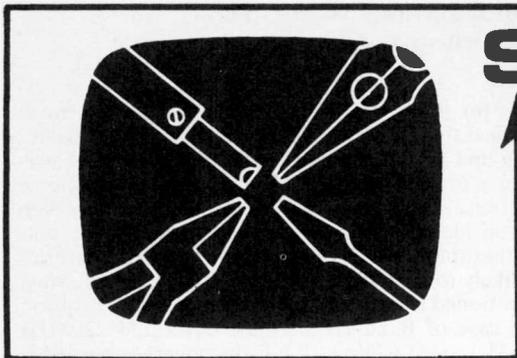

# SERVICING television receivers

L. LAWRY-JOHN'S

**BRC 1580 CHASSIS—cont.**

## EHT Tray

The clip-on e.h.t. tray gives little trouble in receivers with low e.h.t. but in the event of one stick becoming defective (symptoms, poor focus and ballooning coupled with lines across the screen when the brilliance is advanced) both should be replaced as a complete tray.

## AGC Circuit

Part of the video signal at VT5 emitter is passed to VT8 base via the preset contrast control. VT8 only conducts during the line flyback period when it is switched on by a negative-going pulse of about 30V fed from the line output transformer via C55 and W5. This ensures that VT8 conducts only during the sync pulse part of the video signal, C55 then charging to a level determined by the size of the negative-going sync pulse at VT8 base (the size of the sync pulse depends of course on signal strength and the setting of the preset contrast control). When VT8 is switched off (at the end of the flyback) the positive charge on C55 is fed via a smoothing network to VT2 base. This forward bias *increases* the conduction of VT2 and thus VT1 (since the base of the latter is returned to the emitter of VT2) and the resulting voltage drop at the collectors causes a reduction of gain.

## Forward AGC Action

Some may wonder why the control voltage is not negative-going so as to drive the transistors towards cut off—as is done with controlled valves. The answer is that the gain reduction is smoother as the control voltage is increased from the point of maximum gain which is obtained with approximately 6V at VT2 base. Control through decreasing the voltage would cause a more drastic reduction of gain and this is not what is required (what is wanted is a controlled reduction not a switch-like action).

The purpose of W5 is to prevent the a.g.c. transistor being affected by the positive control voltage across C55 (otherwise its collector-base junction would conduct).

## Video Channel

The vision detector (W1) output is fed to a buffer stage (VT5) which also acts as an amplifier for the 6MHz sound signals (with prelimiting by W12). The video signals are taken from the emitter (as is the a.g.c. drive) and are capacitively coupled by C32 to the video amplifier VT6. C31 and L10 forming an acceptor filter for the 6MHz component which must be made to feel unwanted in the

video stage. We have already mentioned the habit of C32 suddenly becoming open-circuit so we will not labour this point further.

The video amplifier itself (VT6) works hard, being operated from the h.t. line with a nominal voltage of 85V at its collector rising to produce the positive tube drive (towards cut-off at the cathode on the sync pulses) as its base is swung negative by the picture information and sync pulses. This swing at the collector is tapped off by R36 which gives high-level contrast control, the sync pulses being divided by R37-R38 and passed to VT7 which functions as the sync separator with a protection diode (W2) in its emitter lead. A suitable replacement for VT6 is a BF178 and for VT7 a BC117.

## Sound Faults

In order to reduce the heat in the cabinet as much as possible a low-dissipation sound output stage is employed, drawing only some 10mA or so. With a loudspeaker of the size used the quality isn't too bad until the speech coil starts to rub (as it tends to do after a period) or the PCF80 output valve starts to draw grid current. The difference in the distortion is apparent to the experienced ear but is difficult to describe. If in doubt check the voltages at pins 7 and 1: pin 7 should show about 3V with respect to chassis and pin 1 about 20V. If the pin 7 voltage is higher than say 3.5V either the valve is faulty, R90 is the wrong value or C68 is leaky; if there is a positive voltage at pin 2 suspect the valve or C68. If the pin 1 voltage is low check the value of R83 which should be about 220kΩ. If the resistor is in order check C65 for leakage. If the pin 1 voltage is high, check R82 which can go high-resistance and thus bias off the triode section. If these voltages are correct and the distortion is more obvious at low volume levels suspect the loudspeaker.

## Distortion at All Levels

Distortion at all volume levels is more likely to be due to a fault in the ratio detector stage (check W6, W7, R85 setting and C67) or in the alignment of L11-L12.

## Tuner Unit

Quite a bit has been written on the subject of the tuner unit employed in this and other BRC chassis such as the 1500 series. It is difficult for us to advise readers whether to service the units themselves or return them to the nearest maker's depot. It all depends upon the aptitude of the

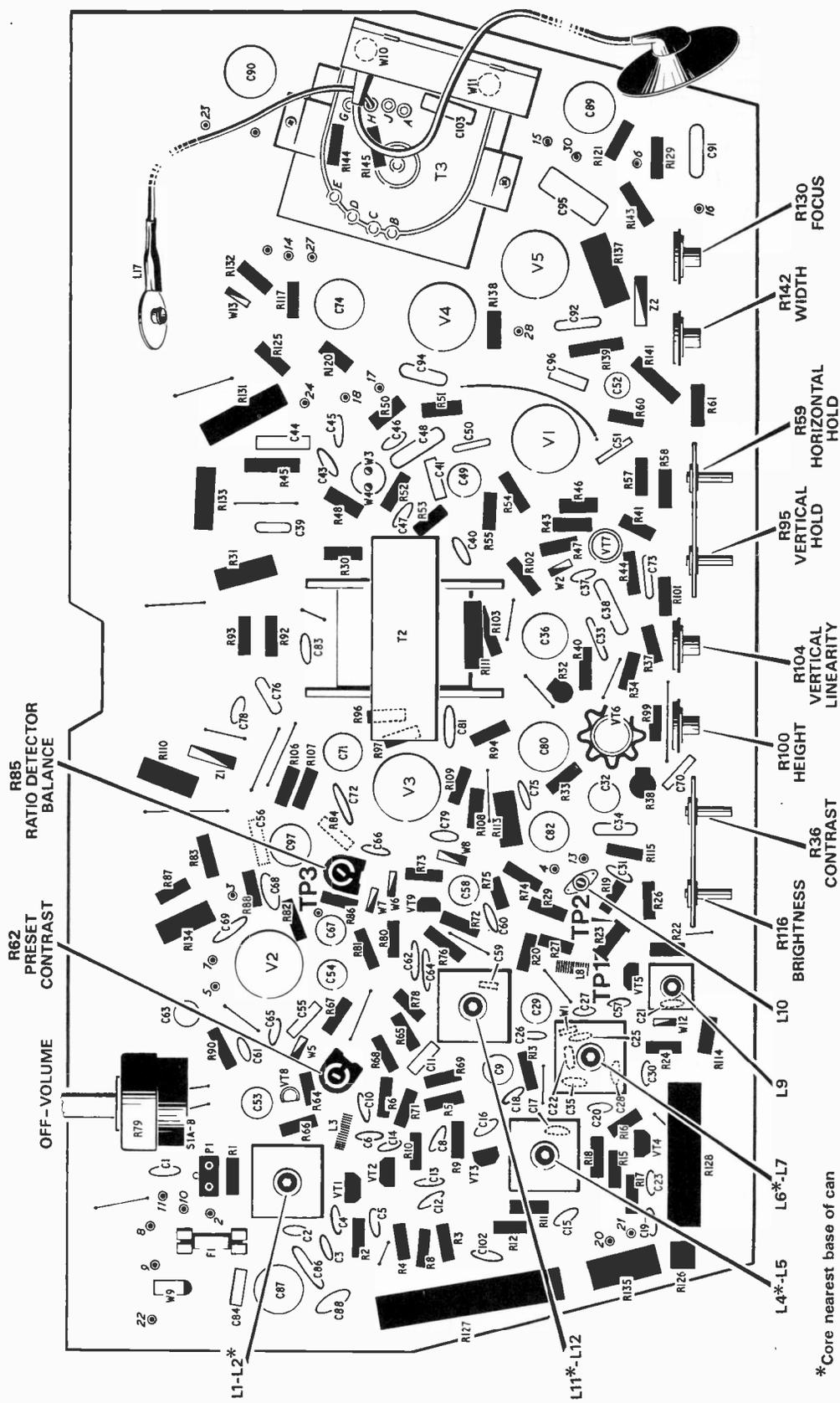


Fig. 2: Component layout on the main chassis assembly.

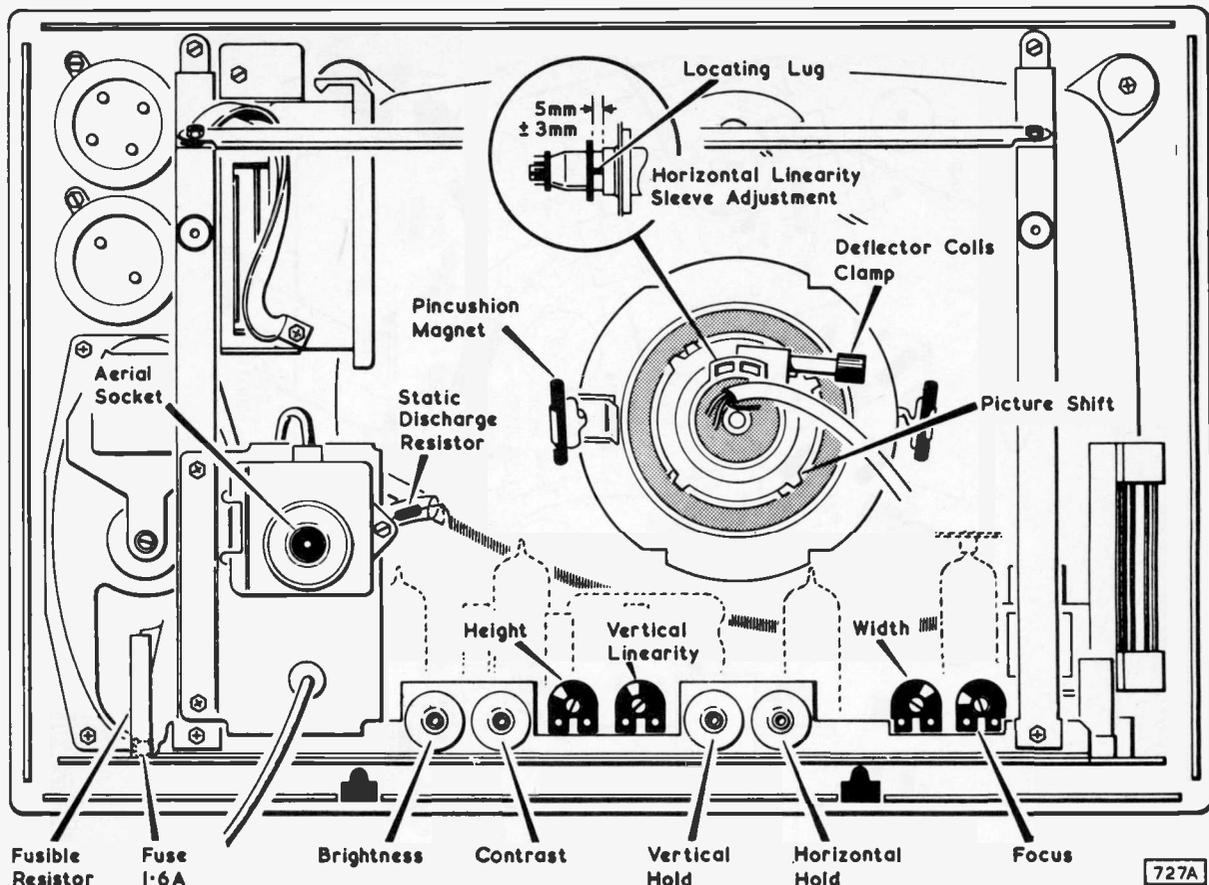


Fig. 3: Rear chassis view showing preset adjustments.

reader. If you don't know exactly what it is all about leave the unit alone and let someone who does know do it. For those who feel quite capable but would like a little guidance we would make the following points.

If the quality of the picture is good but the tuning is inaccurate, the push buttons tending to require frequent resetting, first ensure that the mechanical side is in order. If so it is reasonable to assume that the defect is inside the tuner. The trouble is most likely to be due to surplus grease, which prevents good electrical contact, on the tuning spindle leaf springs. This is not a signal for switch cleaner to be sprayed willy-nilly all over the spindle and tuning vanes: if this is done it will be a considerable time before the tuner will function properly again and the fault will not be removed.

Only the leaf springs require attention. The grease can be removed with a small brush and grease solvent. When the grease has been removed apply switch cleaner lightly to the contact surfaces of the springs. The springs can be removed if desired using a heavy-weight iron or gun—a 15 or 25W iron with a pencil bit is not much use for this job.

### Transistor Faults

Low gain, where the picture is very grainy, if not due to a faulty aerial or plug/socket connection is most often due to failure of the first stage transistor in the tuner—type AF239. If the gain is found to be the same or better with the signal applied between the stages it is safe to fit a

new transistor. Lack of voltage drop across its 1kΩ emitter resistor is another indication that it is not performing.

The second transistor—type AF139—can well be at fault if one programme can be tuned in but not another (the transistor being reluctant to oscillate at a lower frequency). On more than one occasion we have fitted a new transistor in this position only to find that it is no more willing to oscillate than the one taken out.

Before suspecting any transistor however always make sure the supply line is up to specification—12V at the tuner and 20.5V at HT5. Low voltage could indicate a fault in the field timebase, in a supply resistor, or leakage through a smoothing or decoupling capacitor.

### Hum Bars

If the picture is heavily shaded together with loss of field hold suspect C82 and shunt a test electrolytic from the 20.5V line to chassis. The test capacitor should have a capacitance of over 100μF and a rating of 25V or more.

### Modifications

C11 may be 0.047μF; C365 in the tuner unit may not be fitted; R102 may be 120kΩ; R111 15kΩ and R355 in the tuner 2.7kΩ (or 2k7 if you like it put that way).

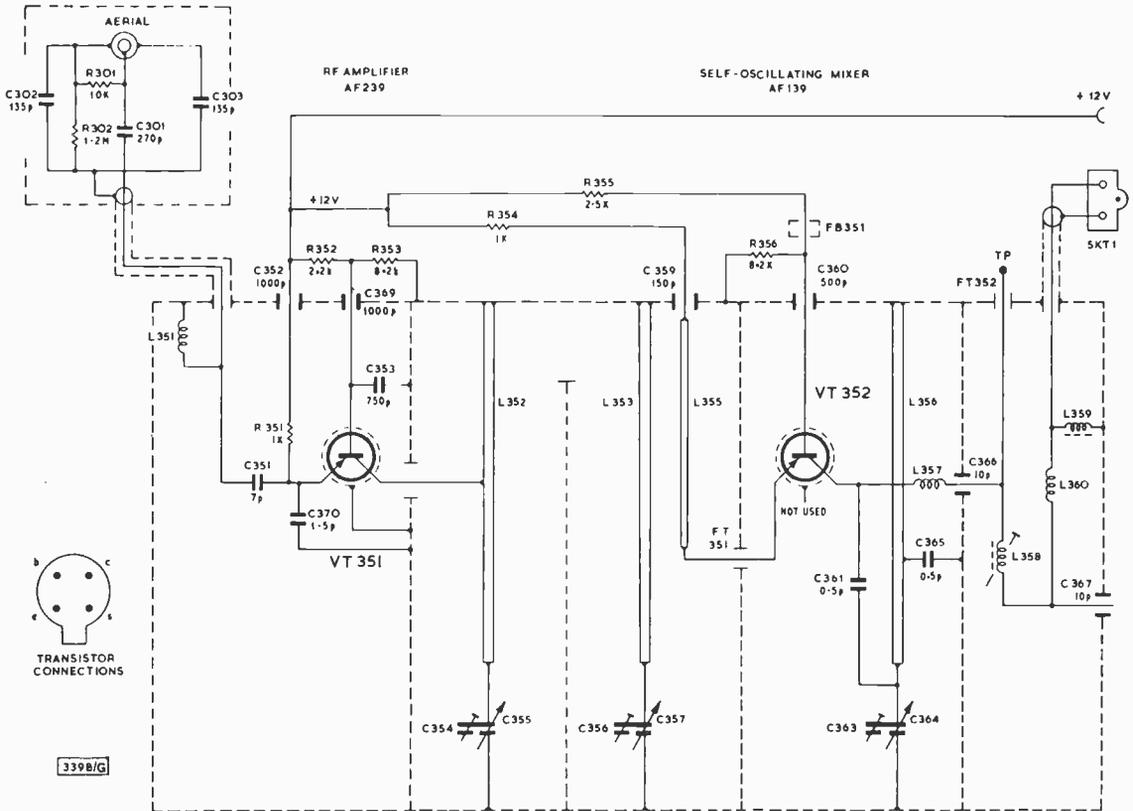


Fig. 4: Tuner type T20 used in the BRC 1580 chassis.

# Strike a new note with Audio


Britain's exciting new-style magazine in music and hi-fi, AUDIO is about every important aspect of the modern sound scene—from the make-up of sound, to the latest means of reproducing it . . . the equipment, its installation and its operation. AUDIO examines new trends, looks at the latest discs and tapes, shows you how to get the most for your money—in clarity, definition and craftsmanship.

## AUDIO

Monthly 20p

THE HI-FI MAGAZINE FOR LEISURE LISTENING

## REBUILT TUBES!

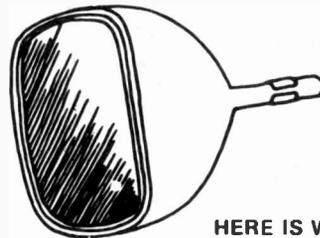

YOU'RE  
SAFE  
WHEN YOU  
BUY FROM  
RE-VIEW!

HERE IS WHAT YOU PAY:


	Mono	Rimband & Twin Panel	Colour
15-17"	£5.00	19" £7.00	19" £25.00
19"	£5.50	23" £9.00	22" £27.50
21"	£6.50	24" £10.00	25" £30.00
23"	£7.50		26" £32.50

Exchange Basis  
Carriage 75p (carriage-ins. £1.50)

Cash or cheque with order, or cash on delivery

- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for Colour Tubes, one year against all but breakage.
- ★ Each tube is insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

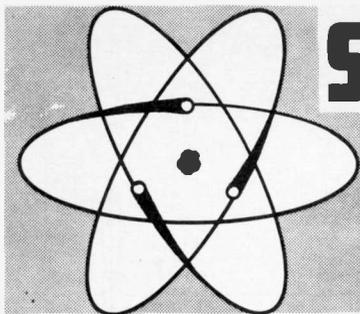**RE-VIEW ELECTRONIC TUBES**  
237 London Road, West Croydon, Surrey  
Tel. 01-689 7735



# Sizing up the Electron

I.R.SINCLAIR

THE word *electron* entered our language at the end of the last century but has become really well established only in the last fifteen years or so. Nowadays we all use the word and its relation *electronics* as a matter of course, but few know on what evidence we base our ideas of what the electron is and its size.

To the ancient Greeks *electron* was the word for amber, the first-known substance which, when rubbed with fur, has the power of attracting small particles of insulators. For centuries *electricity* meant the study of these effects which we now group under the heading *electrostatics*. Electrostatics hardly advanced beyond this stage until Coulomb proved that the force of attraction was proportional to the quantity called electric charge and inversely proportional to the square of distance. Soon after this the modern foundations of the subject, now important to the understanding of semiconductors, were laid by the mathematician Gauss. By this time the original word *electron* had been almost forgotten. The first stage of its recall to active service came as a result of some work by Michael Faraday in the 1830s.

By that time chemists were convinced of the existence of atoms, the basic units of all substances. Faraday was conducting experiments on electrolysis (Fig. 1) to try to find out what amount of electricity was required to deposit unit mass of a material in an electroplating solution. In the course of a series of carefully conducted experiments he found that the mass of the material moved depended on the current and the time for which it was passed. Now the current in amperes multiplied by the time in seconds is the electric charge in coulombs, so Faraday was able to work out the amount of electric charge needed to shift unit mass of any material.

For some time chemists had used the idea of *atomic weights*, the weight of any given atom compared to the weight of the lightest atom, hydrogen, and they had known that in a chemical reaction the weights of substances reacting are in proportion to their atomic weights divided by some whole number (nearly always 1, 2 or 3). These figures of weight put into grams are called gram-equivalent weights, and chemists had a lot of evidence to show that the number of atoms in this weight (32 grams for copper, 108 grams for silver) is the huge figure of  $6 \times 10^{23}$ . Faraday worked out what electric charge would be needed to transfer one gram equivalent of a substance and found that this was the same amount for all the substances which he tried, 96,500 coulombs. This could only mean that a definite quantity of electric charge was needed for each atom, an amount of  $1.6 \times 10^{-19}$  coulombs. He had without realising it measured the charge of the electron.

At that time there was no great interest in this latter measurement. No one was ready for the idea that like matter itself electric charge might exist only in units of definite size. Curiously enough no one ever seems to be

ready for such ideas, i.e. the application of accepted ideas to regions where they do not seem relevant, and when Planck seventy years later put forward the idea that all energy, heat, light etc. was also composed of small units of this sort he was met with the same disbelief as had greeted his predecessors. Faraday's discoveries were quickly put to work in the form of the electroplating industry, and no one for some time worried very much about units of electric charge.

From the 1870s onwards physicists became interested in the effects produced when electricity is passed through gases at low pressures. The most interesting parts of these experiments were those produced when the pressure of the gas was very low, as near to a vacuum as could be produced at the time, and the gas had ceased to glow. In these conditions there appeared in the tube a beam of radiation coming from the negative electrode and heading to the positive one; this effect was named *cathode rays*.

Because any gas used in a discharge tube gives rise to similar "cathode rays" but consisting of different and heavier charged particles (ions) and travelling in the opposite direction, the suspicion grew that the cathode rays were particles and a number of ingenious experiments (see *The Discovery of Cathode Rays*, PRACTICAL TELEVISION, March 1969) showed beyond all doubt that they consisted of negatively charged particles travelling at very high speeds. The next step was obvious—to try to measure the charge, mass and speed of these particles. If they were fragments of an atom—as all the evidence suggested—this was going to be a set of measurements unlike any for determining mass, speed and charge ever carried out before. The first honours fell to a physicist working at Cambridge, J. J. Thomson, who measured the speed of the electron and the ratio of its charge to its mass by what must now be described as electronic measurement. Thomson has another claim to fame—he called the particles *electrons*.

To make any sense of the electron we have to assume that it obeys the same laws of physics as any larger particle. We must, for example, assume that a steady force applied

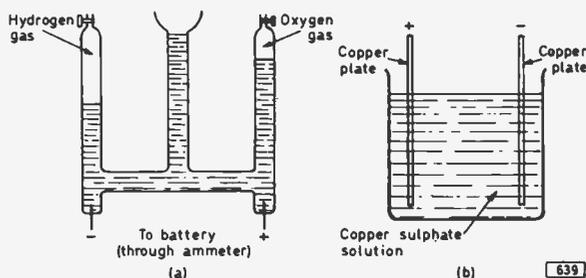


Fig. 1: (a) Electrolysis of water. Water consists of the gases hydrogen and oxygen chemically combined. Electrical energy can be used to separate them, the mass of each gas obtained depending on the amount of electric charge (current  $\times$  time) passed. (b) Electrolysis of copper sulphate. Copper is dissolved from one plate (the positive or anode plate) and deposited on the other (the negative or cathode) plate. The weight of copper transferred depends on the quantity of electric charge passed.

to an electron will make it accelerate, and that the amount of force needed for its acceleration will depend on its mass and on nothing else. Put in the shorter language of mathematics this comes out as  $F = ma$  where the force  $F$  is measured in newtons, the mass  $m$  in kilograms and the acceleration  $a$  in metres per second per second.

Another assumption is that the electron behaves like any other charged particle in an electric field. An electric field exists between any two conductors at different voltages and causes a negative particle to be attracted to the positive conductor. The force of attraction is found by multiplying the charge on the particle  $q$  by the size of the electric field  $E$ . The size of the electric field is given by the voltage difference divided by the distance between the conductors— $V/d$ , see Fig. 2. The quantity  $qE$ , which equals  $q \times V/d$ , is a force and is again measured in newtons.

This force is steady and does not alter because of the movement of the electron. The effect of the force is to accelerate the electron towards the positive plate (see Fig. 3). If an electron is moving very slowly it might be deflected sufficiently in the time it spent near the plates to land on the positive plate; if it is moving rapidly the time it spends between the deflection plates is very small and the deflecting force acts on it for only a short time thus producing only a small deflection. If a particle is accelerated in a direction in which it was not previously travelling the distance covered in time  $t$  (seconds) is given by multiplying the acceleration by half the square of time ( $d = \frac{1}{2}at^2$ ). The three equations we have mentioned can be put together and coupled with the forward movement of the electron to find the velocity from the deflection.

A magnetic field has no effect on a stationary electron but can cause deflection of a moving electron. The force exerted on the electron depends on its speed—the faster it is moving the greater is the force of the magnetic field on it. The important equation here is  $F = Bqv$  where  $F$  is force, again in newtons,  $q$  is the charge on the electron and  $v$  the velocity (speed in a specified direction) of the electron at right angles to the magnetic field (Fig. 4):  $B$  is the strength of the magnetic field—usually provided by a coil—measured in webers per square metre. This quantity can be calculated with some difficulty from the dimensions of the coils used to create the field and the value of current in amperes passed through the coils. The main difficulty here is to produce a magnetic field which has a constant value

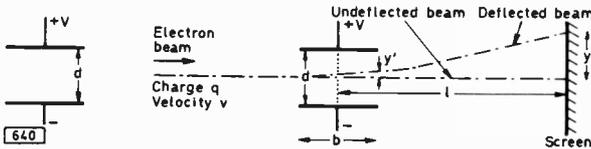


Fig. 2 (left): If  $V$  is the voltage between the plates and  $d$  the spacing between them, the electric field =  $V/d$  volts per meter, e.g. with 300V between plates 1cm (0.01m) apart, field =  $300/0.01 = 30,000V/m$ .

Fig. 3 (right): Electrostatic deflection. Force on an electron during its time between plates =  $q(V/d)$  minus electron mass. Force =  $m \times a$ , thus  $a = (q/m) \times (V/d)$ . Distance sideways =  $\frac{1}{2}at^2$  during time between plates. From the geometry of plates and screen, distance moved sideways between plates =  $y' = y \times (\frac{1}{2}b/l) = y \times (b/2l)$  where  $b$  is plate length and  $l$  is plate-to-screen distance.  $v =$  forward velocity of electron =  $b/t$  where  $t$  is time spent between plates. Thus  $t = b/v$ , Combining,  $yb/2l =$  side distance =  $\frac{1}{2} (qV/md) \times (b^2/v^2) \times$  time<sup>2</sup>. Rearranging,  $v^2 = (q/m) \times (V/d) \times (lb/y)$ , or  $q/m = v^2 \times (d/V) \times (y/lb)$ . So  $q/m$  can be found if  $v$  can be found.

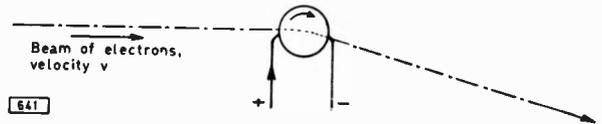


Fig. 4: Magnetic deflection. Deflection force =  $Bqv$ . For a simple Bkt coil,  $B = (6.28/107) \times (nl/a)$  Wb  $m^{-2}$  where  $n$  is the number of turns,  $l$  the current in amperes and  $a$  the radius of the coil.

over the portion of the tube where measurements will be taken.

The arrangement used by Thomson in his measurements on electrons is shown in Fig. 5. The electrons were generated in a gas-filled tube, accelerated and beamed into a bulb where both electrostatic and magnetic deflection could be applied and the deflection measured. Care was taken that the average potential between the electrostatic plates was the same as the final anode potential in the "electron gun" so that the speed of the electron in the bulb was steady before any deflections were applied. The magnetic deflection coils were arranged so that they deflected the electron beam in the same direction as the electrostatic deflection plates (or, of course, in the opposite direction, depending on the direction of the current in the coils). Before the tube had been assembled the dimensions of the deflection plates were carefully measured and the plates fixed at a known distance from the screen. The deflection coils outside the tube were lined up with their centres in line with the centre of the space between the plates.

The position of the electron beam on the screen with voltages applied to the tube but with both the deflection plates at the same voltage and no current in the deflection coils was first noted. This was not easy: the electron beam was wide—not the finely focused spot with which we are familiar in modern cathode-ray tubes—since no way of effectively focusing an electron beam had at that time been found.

A voltage was then applied between the deflection plates and the deflection at the screen measured. As we saw earlier this enables us to find a value for  $q/m$  if the velocity of the electron can be found. It was realised later that the sideways velocity given to the electron in this experiment was at the expense of its forward velocity, making the result slightly inaccurate, but this error is small compared to the errors involved in measuring the deflection of the beam at the screen and so could be neglected. In any case the error is small so long as the deflecting voltage applied to the plates is small compared to the voltage between cathode and anode which gives the electrons their forward velocity.

To find this forward velocity the magnetic field was applied by the coils in such a direction that the electron beam was forced back to the position on the screen where it rested before any deflections were applied. When this

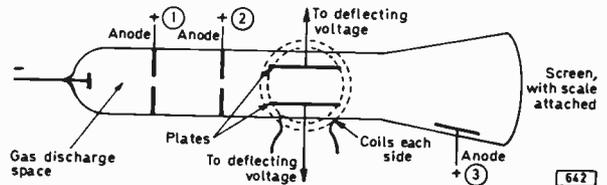


Fig. 5: Thomson's apparatus. The voltages on all anodes are equal. Electric field as before (Fig. 3). Magnetic field added so that beam is deflected back:  $Bqv = q(V/d)$ . Thus  $v = (V/dB)$ . Combining,  $q/m = (V^2/d^2B^2) \times (d/V) \times (y/lb) = Vy/dB^2lb$ .

happens the deflection caused by the magnetic field,  $Bqv$ , must be equal and opposite to the deflection  $Vq/d$  caused by the voltage  $V$  applied to the deflection plates. When we equate the two the charge  $q$ , being on each side of the equation, cancels out and we are left with  $v = V/Bd$ . We can easily find this value of velocity because we know the values of the magnetic field  $B$ , the plate voltage  $V$ , and the distance between the plates  $d$ . Using this value of velocity and substituting it into the other equation in Fig. 3 enables us to find  $q/m$ .

The value found is  $1.76 \times 10^{11}$  coulombs per kilogram, implying that if it were possible to gather together a kilogram of electrons—with nothing else present—the charge would be 176,000,000,000 coulombs, an almost unimaginably large charge. By comparison a 1,000 $\mu$ F capacitor charged to 1,000V stores only 1 coulomb while a 35AH car battery fully charged stores in the form of chemical energy some 1,260,000 coulombs and weighs a darn sight more than 1 kilogram. There seems no doubt that the electron is the “atom” of electricity which Thomson was looking for.

Thomson's experiment not only measured this important quantity but also laid the foundations for the use of magnetic and electrostatic deflection in cathode-ray tubes. Better ways have since been devised to measure the  $q/m$  ratio, but Thomson's remains the best-known because it was the first—history has a habit of forgetting the others. Notice incidentally the relation between the beam velocity and the ratio of the electrostatic deflecting voltage to the magnetic field for the same deflection. This accounts for the use of magnetic deflection in tubes using large anode voltages—the voltage required between the deflection plates for electrostatic deflection would be excessive. We can get round this problem nowadays however by deflecting a low-voltage beam and then accelerating it by a high voltage—the technique called *post-deflection acceleration* (p.d.a.).

If the ratio  $q/m$  is known we need only find the mass to be able to calculate the charge; or if we can find the charge we can calculate the mass. Since the value of  $q/m$  indicates that the charge is large compared to the mass it seems reasonable to expect that the charge of the electron should be easier to measure than its mass. Though there were very good reasons for supposing that the value which Faraday had obtained was in fact the charge of one electron, a direct measurement had to be made to confirm this. This was not achieved for some time after Thomson's experiments, and Faraday's value was used though with a nagging uncertainty.

The idea used by Millikan (who was awarded the Nobel Prize in 1923 for his work) to measure the charge is ingenious and yet startlingly simple. To understand it let us use an analogy. Suppose that we have a set of parcels each containing a different number of identical metal blocks and that we are asked to find the weight of one block without undoing any of the parcels. Suppose that we weigh one parcel and find that its weight is 6kg. Put another parcel on the balance with the first one and we find a weight reading of 10.5kg. Take the first parcel off, and the balance reads 4.5kg. If we know that each block is the same weight and that there are no half blocks we can easily find the weight of a block—it must be the largest number which will divide evenly, with no remainder, into the weight figures we have. Moreover as we have no part blocks it must divide an integral (whole number) number of times.

The largest number suitable in our example is 1.5kg and we could conclude that this is the weight of a block. It could be of course that the weight was 0.75kg and that the blocks go about in twos, but if we did the experiment often enough we should find the weight of the unit block

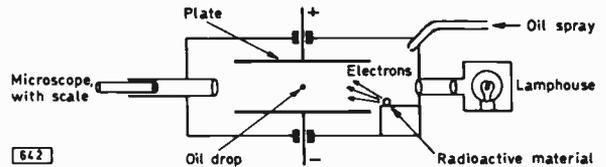


Fig. 6: Millikan's apparatus.

since the pairing would not last forever unless the blocks were welded together—in which case they could not truly be called single blocks. The whole point of this analogy is that the size of a single item can be found without ever seeing a single item so long as the effects can be accurately measured.


The apparatus used by Millikan was as shown in Fig. 6. Two metal plates are arranged one above and parallel to the other and insulated so that a voltage can be applied between them. The space between the plates is brightly illuminated and contains a scale which can be viewed by a microscope. A nozzle is arranged so that very small drops of oil can be blown into the space between the plates where their movements can be followed by the observer using the microscope. A source of electrons, usually a radioactive metal, is placed in one corner of the space between the plates.

To find the electron's charge we use the principle that a force is exerted on an electron in an electrostatic field. Since the charge of the electron is so large even a comparatively large oil drop will move in an electrostatic field if it has one spare electron on it: the radioactive material will provide electrons to land on the oil drops. The first step is to observe a drop and to measure the time it takes to drop some distance (compared with the scale) with no electrostatic field applied. The time taken depends on the size of the drop and the resistance of the air. We can work out the size of the drop from the speed at which it falls. While the drop remains between the plates however it will be gaining electrons from the radioactive material—and losing them again because of the slight conductivity of the air which is slightly ionised by the electrons.

If a voltage is now applied between the plates, with the top plate positive, the drop may move down much more slowly, may hang suspended or may move upwards according to how many electrons are present on it at the time and on the voltage applied. If the same oil drop is watched over a period, its speed can be seen to change as it gains or loses electrons and its speeds with various numbers of electrons aboard can be measured. We do not know of course how many electrons are on the oil drop at any time, but we can work out how much charge is present because the speed of the drop tells us what force is being applied. The charge can be obtained from the formula  $F = q \times V/d$  where  $F$  is force,  $q$  the total charge,  $V$  the voltage between the plates (a few hundred volts) and  $d$  the distance between the plates.

As with the problem of the metal blocks we can now find the unit of charge, because the values of charge on the oil drop which we find are whole-number multiples of the electron charge. The quantity which Millikan found by this method was  $1.6 \times 10^{-19}$  coulombs, identical to the value found by Faraday's experiment. Oddly enough the first attempt at this experiment gave a very different answer, not because of the remarkable delicacy of the measurement but because the value of the resistance of the air to a falling drop had never been measured sufficiently accurately.

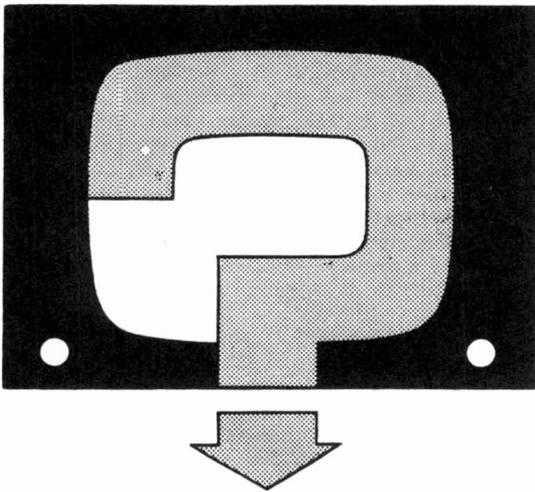These then were the two men and the two experiments which changed the world, moving us from the electric into the electronic age. ■



# YOUR PROBLEMS SOLVED

★ Requests for advice in dealing with servicing problems must be accompanied by an 11p postal order (made out to IPC Magazines Ltd.), the query coupon from page 425 and a stamped, addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets or answer queries over the telephone.

## FERGUSON 3618

We have two of these models each with the same fault. The picture has excessive contrast, as if a preset contrast control has been set too high, while the background is grainy, as if the signal is inadequate. The brilliance control has to be set at maximum and the picture can only be viewed in a darkened room. The i.f. and video valves, the vision detector and the diodes and decoupling capacitors in the a.g.c. line have all been replaced without producing any improvement.—L. Marsh (Rotherham).

The problem is not uncommon with models fitted with this chassis (BRC 850 dual-standard) and is due to C8, a coupling capacitor in the circuit between the tuner unit and the first i.f. amplifier, being leaky. This cancels the a.g.c. at the first vision i.f. stage and leads to excessive a.g.c. being applied to the tuner unit.

## REGENTONE TEN-4

The set works normally when switched on. However if, after it has warmed up, it is switched off and then while still hot switched on again only the sound comes on. If it is allowed to cool down it will work normally again when switched on. I suspect a capacitor in the line output stage going short-circuit after being in operation for a while as the line output valve gets very hot and the e.h.t. rectifier heater does not light up when the fault condition is present.—T. Oliver (Barnet).

The trouble you are experiencing is quite common on these sets. It is due to the fact that the line output stage also forms one half of the line multivibrator. The other section of the multivibrator consists of the triode half of V5 (PCF80). We suggest you replace this PCF80 and then if necessary try another PL81 line output valve. The cross-coupling capacitors could be faulty: they are C42 (0.001  $\mu$ F) and C45 (10pF, 6kV). C40 (40pF, 750V) is another suspect component.

## FERGUSON 725T

To improve results on this old set the tuner valves were replaced but then after about a quarter of an hour R47 associated with the vision i.f. stage V4 burnt out. A picture was obtained by replacing R47 but we were unable to check

the correct value—5.6k $\Omega$  was used. Also the sound became distorted. After a further half an hour both the picture and sound went leaving just a bright light on the screen.—T. Upton (Margate).

The correct value for R47 is 1k $\Omega$ . This resistor provides the h.t. feed to V4 and if after fitting the correct value you find it overheats then the valve and the associated 1,200pF decoupler C45 (use an 0.002 $\mu$ F replacement if more convenient) should be checked. C45 should be replaced anyway as there appears to be instability—also check the decoupler (C32, 0.001 $\mu$ F) in the common vision and sound i.f. stage V3. Common causes of sound distortion are the PCL82 audio valve and change of value of the sound interference limiter bias resistor R106 (3.9M $\Omega$ ). If the PCL82 has to be replaced its 470 $\Omega$  cathode bias resistor R111 should be checked.

## KB PVP20 Royal Star

The problems with this set are that the height can't be reduced while the width is in at both sides of the screen. There is also creeping at the bottom of the raster. The line timebase valves have been renewed.—T. Dixon (Ormskirk).

First the line timebase. We suggest you check the value of the line output pentode screen grid feed resistor (R132, 2.2k $\Omega$ ), the blocking oscillator anode feed resistor (R128, 82k $\Omega$ ) and the coupling capacitor to the line output pentode (C96, 0.003 $\mu$ F). In the field timebase we suggest you try a new PCL82, check the pentode cathode components (R97 380 $\Omega$ , C82 50 $\mu$ F) and if necessary the resistors in the height control circuit—in particular R98 1.8M $\Omega$  to the slider.

## EKCO T407

There is line pairing in this set and I intend to replace the selenium T3/4 interlace diode fitted. These however seem difficult to obtain. Would a Q3/4 selenium rectifier do or possibly a germanium or silicon diode?—K. George (Bangor).

A Q3/4 selenium rectifier could certainly be used. Alternatively a silicon rectifier such as a BA155 could be used.

**PYE 36**

When the contrast is increased there is motor-boating and flashing on the screen. There is no picture but brilliance is still present. If the contrast control is retarded the picture can be resolved and at very low levels will sometimes remain, though with weak sync. The PFL200 video/sync valve has been replaced and the continuity of the contrast control track checked.—T. Brady (Shoreham).

The symptoms suggest instability due to lack of decoupling somewhere. We suggest you check the following electrolytics: C72 (10 $\mu$ F) on the main panel in the contrast control circuit and C32 (10 $\mu$ F) and C34a (64 $\mu$ F) on the i.f. panel in the a.g.c. circuit.

**McMICHAEL M723T**

After about half an hour the field linearity alters, the top of the picture stretching while the bottom shrinks by about 1 $\frac{1}{2}$  in. The picture also loses contrast. All the valves and the main electrolytics have been replaced, also the field output valve bias resistor and the field charging capacitor.—R. Thomson (Bury).

The principal suspect is C73 (0.01 $\mu$ F) in the field linearity feedback loop. However we have also known the v.d.r. wired across the primary of the field output transformer cause this sort of trouble. We presume that the h.t. voltage has been checked, and that it remains steady. The field output pentode cathode decoupling electrolytic and the various coupling and feedback capacitors in the field timebase may have to be checked. Check the 1.8M $\Omega$  resistor to the slider of the contrast control.

**FERGUSON 3802**

The problem with this set is intermittent vision—the sound and raster always remain when the picture goes. Touching the line output valve or boost diode top cap restores the picture. The set runs for several days sometimes without any trouble while on other occasions the picture goes several times in an evening.—J. Middlefield (Manchester).

The cause of the problem follows the video driver stage since the sound take-off is in this stage; the symptoms suggests a faulty capacitor. The electrolytic coupler C37 (64 $\mu$ F) to the video output transistor VT9 should be changed—it is a fairly frequent source of trouble in this chassis. (BRC 1500 chassis.)

**COSSOR 1972A**

This set has given good service but there is now a strong hissing noise. The effect produces broken vertical lines on the screen slightly off centre to the left. After 2 $\frac{1}{2}$  hours or so the effect is not so noticeable but is still there in the form of fuzzy edges. The trouble seems to originate from the vicinity of the line output transformer. Removing the aerial connection makes no difference. The interference can however be removed by advancing the contrast control setting but the picture then suffers. There is a faint smell of burning.—G. Wilson (Manchester).

It is essential that the leads and components associated with the line output transformer are kept away from the transformer windings. Check the top cap connections of the valves in the line output stage, including the e.h.t. rectifier. Note whether the hissing effect is still present with the e.h.t. rectifier removed. It should be possible to see some sort of discharge, identifying the source of the trouble, when the line output stage is viewed in a darkened room. (Philips 19TG152A series.)

**GEC 2012**

There is some sound-on-vision on 405-line operation; it can be reduced but not eliminated by reducing the contrast. Also the sound level can sometimes be increased by switching on the wall lights in another room. On 625 lines reception starts to fade after about ten minutes from cold. The picture can be restored momentarily by increasing the contrast setting but not for long—all that is left is the raster. The transistors in the tuner unit have been replaced without improving matters. The preset contrast control has been replaced by a couple of resistors in parallel—should I restore the circuit to its original condition?—T. Exeter (Bourne).

Replacing the PFL200 video valve will almost certainly cure the 625 signal fade out and will probably reduce the 405 sound-on-vision by ensuring that the full a.g.c. is developed for application to the r.f. amplifier. It would certainly be wise to replace the preset contrast control. Increased volume when lights are switched on usually indicates a dry soldered joint or a badly contacting system switch—also sometimes a faulty coupling capacitor.

**BRC 1500 CHASSIS**

We have two receivers, a Marconiphone and an Ultra one, fitted with this chassis. Reception is good here but the Marconiphone model gives very poor results on the correct BBC-2 button and also on the spare button when we attempt to tune in on this one.—H. Watkins (London SE1).

You should remove the tuner unit and check the clearance of the tuning vanes as they close towards channel 33. Close inspection may reveal a partial short in one section towards the r.f. end. Clean the spindle washers and reassemble, checking the bar sockets (soldered) and spring tension.

**EMERSON E700**

This set has been out of use for several years. It appears to be in good condition but we are unable to get a raster. All valves are operating and the h.t. is normal but drops to about 165V after a time. Similar trouble was cured once in the past by replacing the line output transformer.—R. Eves (Stevenage).

Unfortunately the line output transformer was a weak link in this chassis and it is quite likely that the replacement has failed. Before fitting a new one however check the line timebase valves (PCF80, PL36, PY81), the 4.7k $\Omega$  PL36 screen grid feed resistor, the boost reservoir capacitor C91 (0.1 $\mu$ F) by removing the PY81 top cap to see whether this restores some life to the line timebase, and the high-voltage 100pF tuning capacitor C93 connected across the line output transformer.

**FERGUSON 3618**

This set suffers from foldover at the left-hand side of the screen. The line oscillator, line output and boost diode valves have been replaced without improving matters. The line timebase voltages have been checked and are all close to those specified in the manual.—B. Carter (Peterfield).

The thing to ascertain is whether the raster with no picture present folds over or whether the picture folds. If the former is the case the line output stage is at fault and will require further checking. If the foldover occurs only with a picture present the fault is in the flywheel line sync discriminator circuit. (BRC 850 chassis.)

## PHILIPS G20T300

This set suddenly developed hum the source of which we are having difficulty tracing. The hum decreases when the volume control is turned up and increases when the volume is reduced.—B. Lane (Stafford).

There are only two likely causes of the hum described. The first is poor contact between the right-side electrolytics and their clip (and earthing wire)—a common fault on this chassis—and the second a faulty PCL82 audio output valve. (Philips 300 series.)

## DECCA CTV25

On peak beam current there is severe arcing between the metal shield around the tube and the c.r.t. outer coating. This can be stopped by reducing the setting of the brightness control. There does not appear to be any arcing around the line output transformer but I have been told that this is likely to be the component responsible for the trouble. Another fault is that the verticals are slightly bent. The set

is working very well in every other respect.—G. Bishop (Edinburgh).

We suggest you first check the GY501 e.h.t. rectifier by replacement. Then if necessary remove the one turn heater winding on the line output transformer and replace with heavily insulated cable—retaining the 1.5Ω resistor in series with the heater. The transformer itself should not have to be replaced. For the bent verticals check the PCF802 line oscillator valve and the 2μF electrolytic C324 in its cathode circuit—this component is a frequent cause of troubles in the oscillator circuit.

## QUERIES COUPON

This coupon is available until July 16, 1973, and must accompany all Queries sent in accordance with the notice on page 423. Don't forget the 11p (inc. VAT) postal order!

## TELEVISION JULY 1973

# TEST CASE

# 127

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

? The complaint with a KB CVC2 colour receiver was intermittent loss of colour which could sometimes be corrected either by rotating the colour control rapidly from minimum to maximum a few times or by switching the receiver off and then on again a few minutes later. On-site examination by the field technician yielded no material clues and although the colour faded once during the examination it reappeared without assistance and did not fade again. Consequently the receiver was brought into the workshop for more detailed investigation.

A soak test revealed that the complaint was well founded, for after about two hours running the saturation started to "flicker" with the colour disappearing completely at intervals. After the receiver had been allowed to cool right off the soak test was recommenced. As before the colour was unaffected for an hour or so, after which the symptoms recurred. During this time however it was noticed that on a deep saturation fade the colour lock failed, the colour still present forming zig-zag lines across the picture.

To check the signal in the chrominance channel a 'scope was used to monitor the chrominance signal feeds to the synchronous detectors but even when the colour faded these remained essentially constant. The bench technician concluded—correctly—that the fault was temperature sensitive and eventually—after performing one other test with the

'scope—isolated one critical component. What was this most likely to be? See next month's TELEVISION for the solution and for a further item in the Test Case series.

## SOLUTION TO TEST CASE 126

(Page 377 last month)

The disposition of the vision, chrominance and sound carriers relative to the i.f. passband depends on the front-end tuning. The three carriers are always correctly spaced of course, but as the tuning is adjusted they move *en bloc* in the i.f. passband.

Since the various rejectors necessary are located in the i.f. channel the carriers must be correctly placed to ensure correct signal processing—by the rejectors in particular. With the carriers situated too far towards one side of the i.f. passband the definition is impaired while if they are too far towards the other side the definition is enhanced—ultimately leading to beating between the chrominance and sound carriers which causes patterning.

It is clear therefore that in the receiver in question the a.f.c. was pulling the tuning away from the correct carrier placement instead of "locking" the tuning correctly. A Foster-Seeley a.f.c. discriminator fed with a sample i.f. signal via an a.f.c. amplifier stage is used in the Pye Model CT70 to produce a positive- or negative-going output depending on the direction of mistuning. This output adjusts the bias on a varicap diode in the tuner oscillator circuit so as to keep the tuning correct. If the discriminator itself is incorrectly tuned however the phase-lock-loop will stabilise at an off-tune frequency, detuning instead of correctly tuning the front-end.

This in fact was the trouble and was overcome simply by adjusting the core of the a.f.c. transformer secondary—the a.f.c. circuit being situated on the i.f. board. Pye give a special procedure for doing this but tuning the coil for optimum results is almost as good. It should be borne in mind that as in any other i.f. circuit a drift in the value of an associated component could be the cause of the detuning.

# TELEVISION CLASSIFIED ADVERTISEMENTS

Classified advertisements 6p. per word (minimum 12 words). Box No. 20p. Semi-display setting £3.50 per single column inch. Advertisements must be pre-paid and addressed to Classified Advertisement Manager, TELEVISION, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to TELEVISION and crossed "Lloyds Bank Ltd."

## AERIALS

**GENUINE FULL SIZE 18 element TV aerial** as used by leading TV companies

ITV, BBC 1 & 2 B/W & Colour. Guaranteed Perfect Pictures. Save ££s. We supply this genuine U.H.F. aerial for only £2.20. can be fitted outside or inside. Quality made, technically advanced design. Precision grid reflector eliminates ghosting. Complete with clamp, instructions, advice Money Back Refund. Wati/Caravan Bracket 25p Low Loss Cable 10p per yard. Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters. Send direct to Dept. F.10 219 Mansfield Rd. Nottingham.

**£2.20** incl. VAT + 35p cart

**IMPERIAL TRADING (AERIALS) LTD.**  
the quality Aerial Specialists

### BAINES for High Frequency Aerials.

UHF Multibeams by J. Beam  
MBM 10, £2.20 MBM 18, £2.90  
MBM 30, £3.90 MBM 46, £6.00  
MBM 70, £11.00

### VHF FM Aerials

Dipole £1.40 FM/H £2.00 FM3 £3.00  
FM4S £5.55 FM6S £7.80

### Masterhead Pre-amps

Single Stage £6.00 Two-Stage £8.00  
Wideband £7.00

Accessories: SAE for full list.

Co-ax. 5p Low-loss 9p

Prices do not include VAT. 10% must be added to all orders.

11 Dale Cres., Tupton, Chesterfield S42 6DR

### U.H.F. T.V. AERIALS

MBM46, quality 46 element yagi, max. gain approx. 17dB, available for Groups A-B or CD, £5.75. COLOUR KING flat yagi, covers all UHF channels, max. gain approx. 15.5dB, £6.35 (Two for £11.50). Caravan aerial all channels £8.00.

(Please add sufficient postage)

H. WOOD, 1, Halkyn Hall Estate,  
Pentre Halkyn, Flintshire,  
North Wales. Tel.: 035 288 572

## WANTED

NEW BVA valves of popular types, PCL805, PY800/1, PL504, etc. Cash varying. Bearman, 6 Potters Road, New Barnet, 449/1934-5.

SERVICE SHEETS purchased. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

TELEVISION issues June 1972 to Feb. 1973 to borrow for week against payment, G. L. Berger, 25 Fountain Street, Macclesfield SK10 1JW.

WANTED—One TV Receiver adapted to DX use on C.C.I.R. System "B", and 819 lines system "E". Will pay up to £20, including carriage. Reply:— M. P. Ward, c/o H. Taylor and Son Ltd., Bridge St., Walsall.

**SUPER Stereo** from Electronics today, £5.00. Capacitor Discharge Ignition system Wireless World, 2 off, £20. Heathkit solid state Ignition Analyser, CO 1015, £65. Audio Generator, model AG 9U, £12. AVO Electronic Testmeter, £15. For Sale Television colour receiver components and boards, one of Pal-D Decoder IF Strip, Audio Module RGB Module. Time Case board Pack 14, Pack 15. Convergence boards Power supply, cost £102, offers, B. Rodriguez, "Oakleigh", Forest Road, Wokingham, Berks. Tel. Bracknell 29680 after 6 p.m.

**PRACTICAL TELEVISION.** Complete from No. 1 to No. 255 (Jan. 72)—the lot £12.50 o.n.o. Reply to 238 Chester Road, Helsby, Warrington.

"TELEVISION Colour Receiver". Decoder P.C. Board ready drilled plus packs 1, 2, 3 unused.—£16.75. Back issues "Television" April '72-March '73—£2.75. J. Douglas, 16 Wicks Crescent, Formby, Lancs.

## BOOKS AND PUBLICATIONS

**DIGITAL COMPUTER LOGIC** and Electronics. Four volume self-instructional course. £2.95 including p. & p. Money back assurance.—Cambridge Learning (T), 8a Rose Crescent, Cambridge.

"RADIO AND TV SERVICING" all volumes available. S.A.E. for pricelist. Markonics, 327 Tildesley Road, London S.W.15.

## SERVICE SHEETS

**SERVICE SHEETS MANUALS BOOKS**

**SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 20p**  
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS, RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

**NEW BOOKS & PUBLICATIONS**

	PRICE
RAPID TV REPAIR by G.W.Heath. 224 pages. 107 Illustrations.....	£1.30
EASY WAY TO SERVICE RADIO RECEIVERS by L.Sands. 176 pages.....	£1.00
HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS by B.Brown & P.Lawrence ...	£1.30
ELECTRONIC PUZZLES AND GAMES by M.Mandl. 128 pages.....	£1.20
TV DIAGNOSIS AND REPAIR by The PF REPORTER Editorial Staff. 96 pages ...	£1.00
TV TECHNICIANS BENCH MANUAL by G.R.Wilding. 187 pages. 127 Illustrations	£2.50
NEWNES COLOUR TELEVISION SERVICING MANUAL by G.J.King. 240 pages ..	£4.90
UNDERSTANDING ELECTRONIC CIRCUITS by I.R.Sinclair. 204 pages.....	£3.50
UNDERSTANDING ELECTRONIC COMPONENTS by I.R.Sinclair. 218 pages.....	£3.50
TUNERS AND AMPLIFIERS by John Earl. 187 pages. 127 Illustrations.....	£2.10
TAPE RECORDERS by H.W.Hellier. 239 pages. 254 Illustrations.....	£2.25
GUIDE TO PRINTED CIRCUITS by G.J.King. 140 pages. 95 Illustrations.....	£2.50
BEGINNERS GUIDE TO COLOUR TELEVISION by G.J.King. 2nd Edition.....	£1.95

★ SPECIAL OFFER AT THE REDUCED PRICE OF £1.50 POST FREE  
1972 EDITION OF "WORLD RADIO TV HANDBOOK" Usually £2.80 ★

NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good price paid.  
Send large S.A.E. for FREE booklists and book pamphlets on Radio, Television & Electronics.

NOTE. Postage on all books is now 5p in the £1. Orders over £5.00 POST FREE. (U.K. only)

**BELL'S TELEVISION SERVICES**  
ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

## A.L.S. SERVICE SHEET SERVICE

OUR STOCKS NOW COVER OVER 10,000 MAKES AND MODELS

1973 list covering mono and colour—TV, Radio, Tape, Record Players, etc. List price 25p, plus SAE.

Service Sheets—Service price 30p plus LARGE SAE.

Manuals for many makes. Enquiries welcome but please—a SAE.

Always state make, model number and whether TV, radio, tape, etc.

### 1973 COMPREHENSIVE COLOUR TELEVISION MANUAL

By McCourt. £2.00 including post and packing.

Money refund if dissatisfied.

We can also supply Manuals for many sets, including Colour TVs by such makers as Bush, B.R.C., Murphy, Ferguson, H.M.V., Decca, Sony, Hitachi, Sanyo, etc. Prices on Request.

NEW SERVICE SHEETS, Magazines and Newsletter. SAE brings details and free sample.

### BARGAIN CORNER

Metal box containing Heavy Duty 12V 2PCO Relay OC35 (type) transistor and other components (originally fluid level control unit) price 50p.

MAIL ORDER ONLY

A.L.S.

21c Dryden Chambers, 119 Oxford Street, London W1R 1PB

## LARGE SUPPLIER of SERVICE SHEETS

(TV, RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

Only 40p each.

PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES AND ORDERS.

Otherwise cannot be attended to.

(Uncrossed P.O.'s please, original returned if service sheets not available)

### C. CARANNA 71 BEAUFORT PARK, LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free TV fault tracing chart or TV list on request with order.

MAIL ORDER ONLY  
or Phone 01-458 4882.

### SERVICE SHEETS

(1925-1973) for Radios, Televisions, Transistors, Radiograms, Car Radios, Tape Recorders, Record Players, etc. with

FREE FAULT FINDING GUIDE

PRICES FROM 5p

Over 10,000 models available.  
Catalogue 15p + SAE

Please send stamped addressed envelope with all orders and enquiries.

### Hamilton Radio

47 Bohemia Road, St. Leonards,  
Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

### SETS & COMPONENTS

#### COLOUR COLOUR COLOUR

19in. & 25in. Colour Televisions  
DECCA, BUSH, BRC, PHILIPS etc.  
19" Working £100 25" Working £140  
11" Portables £80

All Good Tubes. Tested before  
Despatch. Delivery can be arranged  
Non-Workers — From £80

S.A.E. Details Please.

T.E.S.T., P.O. Box 1, Kirkham,  
Preston PR4 2RS

TELEVISION'S Colour Receiver  
Epoxy Glass P.C.B.'s, Drilled and  
Tinned, Decoder, I.F. Strip, Time-  
base, Power Supply £2.00 each.  
R.G.B. Module £1.25 each. Conver-  
gence Boards £3.25 per set. I.F.  
Pre-Amp, C.R.T. Base £1.00 each.  
Add V.A.T. to above prices.  
Cash with order.

#### ELECTRONIC DESIGN SERVICES LTD.,

Bothok Works, Walsaw Road,  
Bury, Lancs.

AVOs and all types of meters repaired.  
Postal service. Free estimates. Guar-  
anteed. — Instrumentation Services, 23  
Hallam Road, Clevedon, Somerset.

## TV'S COLOUR TV'S

Reserviced. Perfect working order.  
Repolished.

19in DECCA ..... £110  
19in. GEC 2028 ..... £115  
19in. THORN 2000 £120  
25in. DECCA ..... £125  
25in. RBM PHILIPS £130  
25in. THORN 2000 £135

One month comprehensive written  
guarantee. These are cash and collect  
prices. Delivery quotations by phone.

### MONO U.H.F.

Fabulous TVs. No rubbish, from  
good source. Repolished cabinets.  
Many working. Recent transistorised  
models, including:

BUSH TV 148 U, TV 166, TV 176  
PHILIPS style 70 and 210  
PYE & EKCO 868 chassis  
THORN 950 1400, GEC Concorde  
FROM £12 EACH

Valve u.h.f. models include:

BUSH push-button, THORNE 850,  
SOBELL 1000, etc. FROM £5

### U.H.F. TUNERS

For FERGUSON 850, 900 chassis but  
adaptable for most D/STD chassis  
£2.50 each, c.w.o. postage included.  
Send s.a.e. for lists of Tubes, TVs,  
Valves, etc. For England:

TRADE DISPOSALS, 1943 Leeds Rd.,  
Bradford. Tel: Bradford 665670  
For Scotland:  
TRADE DISPOSALS, Unit 5, Peacock  
Cross INDUSTRIAL ESTATE, 32  
Burnbank Road, Hamilton.  
Tel: Hamilton 29511/2

BZ988 Type Zener Diodes Unmarked  
Untested, 100 for 50p.

OA91 Unmarked Untested, 100 for  
50p.

BA144 Unmarked Untested, 100 for  
50p.

50 NPN Silicon Planar Unmarked  
Untested Transistors Similar to  
ZTX300, ZN3708/9, BC107/8/9,  
BC168/9, etc. 50p.

50 PNP Silicon Planar Unmarked  
Untested Transistors Similar to  
ZTX500, ZN3702/3, BCY70, etc.  
50p.

100 1/2W Carbon Film, Metal Oxide  
Resistors, 50p.

IN4007 Rectifiers 1200V Peak 1A  
Mean Current, 10p each, 10 for 70p.  
4-Digit Counters 500Ω Magnetic, 25p  
each.

Monofilament Unsheathed Light  
Guide 1/8mm Diameter, 10p per meter,  
postage 5p.

S.A.E. for Capacitor and Resistor  
Lists.

J. FULTON, DERRYNASEER,  
DROMORE, CO-TYRONE.

### TOP PRICES PAID

for new valves, popular  
TV & Radio Types

### KENSINGTON SUPPLIES

(A), 367 Kensington Street  
Bradford 8, Yorks

#### TRANSISTORS (For THORN 3000)

R2008 output transistor.  
R2010 chopper transistor.  
Singles £1 each inc. p. & pkg.  
Any twelve for £10 inc. p. & pkg.  
C.w.o. to:—

TRADE DISPOSALS (T/O)  
1043 Leeds Road, Bradford 3.

150 NEW Capacitors/Resistors/Silicon  
Diodes, Electrolytic, Mica, Ceramic,  
Carbon. Oxide etc. £1 Post Free.  
Whitsam Electrical, 33 Drayton Green  
Road, London, W.13.

### TRANSISTORISED UHF TUNERS

6 assorted £15.50 (incl. p. & p.)

### BARGAIN T.V.'s

Slim Line

23" 3 channel with UHF tuner £9.00  
19" 3 channel with UHF tuner £8.00  
23" 2 channel £5.00  
19" 2 channel £3.50

All sets working. Personal callers  
welcome.

Carriage can be arranged.

Open Fridays - Mondays inclusive.

SUNDAYS: 1.30—4.0 p.m.

and by appointment.

### PLASGWYN WAREHOUSE,

Caernarvon Road, Fourcrosses,  
Pwllheli, Caernarvonshire.  
Tel.: Pwllheli 2800.

### EX-RENTALS

ALL SETS complete with UHF

Tuners, many working:—

19" BBC2 Sets at £3

23" BBC2 Sets at £7

Working Sets to Order.

All Sets Re-polished. Calls Only.  
TV DISPOSALS, The Grove, Bristol  
Tel: Bristol 290239

### CHEAPER T.V. SETS

405—19"/23" ..... 50p to £2.50  
D/S—19"/23" ..... £2.50 to £6

625—19"/24" ..... £4.00 upwards

Thousands of T.V. sets always in  
stock. Colour also available. Mon/  
Sat, 9.00 to 5.30.

### WORKING SETS AVAILABLE TO ORDER

Enquiries to:—

Premier Warehouse, Bridge Works,  
East Farleigh, Maidstone.

For quality Hi-Fi Equipment, records  
and Colour Television. Visit  
HANSFAL'S AUDIONICS

488 Lady Margaret, Southall, 01-578  
2258; 54 St. Anns Road, Harrow, 01-  
863 3400. 24 hours Autophone Service.  
Marantz, Pioneer, Sansui, Akai, Rotel,  
Nikko, Lux, Telefunken, Sony, Sanyo,  
Tandberg, Hitachi, Grundig, Scan-Dyna,  
KEF, TEAC, National, Quad, Tele-  
funken, Hitachi, Sony and Grundig  
Colour T.V. Always in stock.

Up to 5 years Colour Tube guaranteed  
and 1 year Free Servicing and Labour.  
Late evening: Friday until 7.00 p.m.

EXCELLENT CREDIT FACILITIES

### COLOUR TV BARGAINS

19" Working £90 25" Working £125

Non Workers from £75

11" Portable Working £75

Various Makes available. Non-  
workers from £80. S.A.E. for details.

### THE TV CENTRE,

83 Upper Aughton Road,  
Southport, Lancs.  
Telephone Southport 68695.

SCOPES. Very special offer. All serv-  
iced by Telequipment, and in perfect  
condition. S43 Single beam 15 Mc.  
bandwidth £75, D51 Double beam 6+3  
Mc. Bandwidth £65, D52 Double beam  
6 Mc. bandwidth £88, D43 Double  
beam 15 Mc. bandwidth £90. Phone  
01-886 9666.

LADDERS, 24ft. £9.80, carr. 80p.  
(Please add 10% V.A.T.). Leaflet. Callers  
welcome. Home Sales Ladder Centre  
(PTT2) Haldane, Halesfield (1) North,  
Telford, Salop. Tel. 0952-586644.

**EX-RENTAL,  
UNTESTED**

BBC2 TV's

Thorn 850-900  
£7.50

Murphy 159U  
Transistor Push Button  
£14

U.H.F. Tuners Suitable for  
Thorn 850-900, adaptable for  
most makes. £2.50

All prices inc. P. & P.

Quantity Discount to Trade

**PENCOYS TV CENTRE**

"Pencoys", Four Lanes,  
Redruth, Cornwall.  
Tel. Redruth 6579.

**New TV Valves**

Top Quality

Direct from Factory

DY 86/7	.23	PCF 801	.30
ECC 82	.22	PCL 82	.30
EF 80	.22	PCL 84	.33
EF 183	.26	PCL 86	.37
EF 184	.27	PL 36	.48
EY 86/7	.28	PL 81A	.48
PC 86	.44	PL 504	.62
PCC 84	.28	PL 509	1.38
PCF 80	.30	PY 81	.25

post and packing 3p per valve

**ACORD ELECTRONICS LTD.,**  
5 High St., Guildford, Surrey.

**TVs TVs TVs !!! 19" TVs**

All in Working Order

Bush, Murphy, Ferguson, Pye,  
Marconi, Thorn, etc.

£11.50 plus £2.00 Carriage

**COLOUR - COLOUR - COLOUR**  
All Working

19" Various Makes ...	£100.00
22" Various Makes ...	£140.00
26" Various Makes ...	£150.00
11" Colour Portables ...	£75.00

Delivery Arranged

S.A.E. LISTS  
ENG. 919301

**LINAVALLE RADIO LTD.,**  
48 Hoe St., London E17 4PG.  
01-520 7546

**EX RENTAL  
TV's BARGAIN**

23" 3 Channel with U.H.F. Tuner	£7.50
19" & 25" Colour from	£60.00
19" 3 Channel with U.H.F. Tuner	£4.50
19" 2 Channel	£1.00

All sets complete. Callers only.

**EDWARDS & SONS**

103 Goldhawk Road, London W.12.

**Top 20 Plus Tested TV Valves**

PL504	18p	PCL84	10p
PC86	15p	PCL82	10p
30L15	15p	PFL200	10p
PL36	15p	ECC82	10p
PCL805/85	15p	EH90	10p
30FL1/2	15p	30PL13	15p

**Colour Valves Fully Tested**

PL509	30p	PY500/A	30p
PL508	30p	PL802	30p

Many others available including  
Mazda Types.  
P. & P. 4p per valve, over 12 2½p  
per valve, orders over £3 post free.  
Prompt service.

S.A.E. for free list.

**L. & D. COMPONENTS LTD.,**  
71 Westbury Ave., London N22 6SA.  
Tel. 01-888 2701.

**TELEVISIONS 50p**

19" V.H.F. from 50p  
23" V.H.F. from £1.00  
19" Convertible from £1.50  
19" 3 Channel from £1.50  
Working Monochrome  
3 Channel from £6.00  
Working Colour from £55.00  
Untested Colour from £40.00

**John Carter Wholesale**  
198, Cator Lane,  
Chilwell, Nottingham.

0602 256358      0602 252908

**1000 COMPONENTS—£3**

Ideal mixtures for service engineers,  
etc., containing carbon, carbon film,  
metal oxide and a few wirewound  
resistors, 1, 2, 5%, ¼, ½, 1, 2W  
types. Also ceramic, mica, paper,  
electrolytic, polystyrene capacitors. At  
least 1000 components £3 + 30p post.  
**GREENWELD (TI)**  
24 Goodhart Way, W. Wickham, Kent

**£90 COLOUR TV £135**

- \* Fully Serviced
- \* Accurate Decoder Set Up
- \* Attractive Cabinets

Also:—  
23" UHF Mono. Working. £10

Telephone : 01-845 2036

**COMPONENTS GALORE.** Pack of 500  
mixed components manufacturers sur-  
plus plus once used. Pack includes  
resistors, capacitors, transistors, diodes,  
I.C., gang, pots, etc. Tremendous  
value. Send £1 plus 10p P. & P. C.W.O.  
to Caledonian Components, Fosterton  
Firs, Strathore Road, Thornton, Fife.

**EX RENTAL TELEVISION**

Stimline Dual Standard with

U.H.F. Tuners. Complete—Untested

19" THORN 850	£4
19" COSSOR 962	£6
19" K.B. VV	£8
23" THORN 850	£10
23" K.B. VV	£12

Collect or Send £2.00 p.p.

162 Kettering Road, Northampton.  
90 Tavistock Street, Bedford.

**TELEVISION TUBE SHOP**

**BRAND NEW TUBES AT  
REDUCED PRICES**

A31-18W	£12-50
A47-11W	£9-95
A47-13W	£12-50
A47-14W	£8-25
A47-26W	£10-75
A50-120WR	£12-50
A59-11W	£12-95
A-59-13W	£13-50*
A59-15W	£9-95
A59-23W	£14-75
A61-120WR	£16-50
AW43-80	£6-95
AW43-88, 43-89	£6-75
AW47-90, 47-91	£7-50
AW53-80	£7-50*
AW53-88, 53-89	£8-25
AW59-90, 59-91	£9-00
CME1201	£12-50
CME1601	£10-50
CME1602	£12-00
CME1705	£7-75
CME1713/A44-120	£14-50
CME1901, 1903	£7-50
CME1906	£12-50
CME1908	£7-75
CME2013	£12-50
CME2101, 2104	£8-25
CME2301, 2302, 2303	£9-00
CME2305	£14-75
CME2306	£13-50*
CME2308	£9-95
CME2413R	£16-50
MW43-80	£6-75
MW53-20, 53-80	£7-50
TSD217, TSD282	£14-00†
13BP4 (Crystal 13)	£14-00†
190AB4	£9-25
230DB4	£11-25

\* These types are fully rebuilt.

† Rebuilt tubes also, at £7.00 plus  
carriage and old bulb.

**COLOUR TUBES NEW R/B**

	£	£
A49-15X	35	-
A49-120X	45	-
A56-120X	72	48
A61-15X	78	52
A63-11X	-	52
A66-120X	82	55
A67-120X	85	-

**SHOP-SOILED COLOUR TUBES**  
19", 22" & 26" NOW AVAILABLE  
Brand new, with slight scratches.  
Prices from £30. Callers only.

Add Carriage and Insurance: Mono-  
chrome 75p, Colour £1.50.

ALL PRICES SUBJECT TO V.A.T.

**TELEVISION TUBE SHOP**

48 BATTERSEA BRIDGE ROAD  
LONDON, S.W.11.      BAT 6859  
WE GIVE GREEN SHIELD STAMPS



# COLOUR TELEVISION TRAINING

11 WEEKS' COURSE for men with Mono experience. Hours 2 p.m. to 5 p.m. Monday to Friday. Next course commences Sept. Prospectus from: London Electronics College, Dept. T.7, 20 Penywern Road, London, SW5 9SU. Tel. 01-373 8721.

**FULL TIME COURSES IN ELECTRONICS AND TELEVISION.** These are nine month courses, starting September 1973 leading to City & Guilds certificates. Extensive laboratory work is included, and there are, in most cases, no fees for those under 18 at enrolment. Full details from: Section 272, Electrical and Electronic Engineering Department, Southall College of Technology, Beaconsfield Road, Southall, Middx.

## COLOUR T.V. SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV technician, and approved by leading manufacturer.

Full details from ICS, (D.750P) Intertext House, London SW8.

**ENGINEERS**—Get a technical certificate. Postal courses in Engineering, Electronics, Radio, T.V., Computers, Draughtsmanship, Building, etc. Free book from: BIET (Dept. ZC BTV 19), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

### MISCELLANEOUS

**PATTERN GENERATOR**, Labgear CM 6004 PG Crosshatch, Dots & Grey-Scale. Current Model, complete with hand-book, £26. Also set of 4 Radio & TV Servicing Manuals 1965-69, £10. 01-889 6166.

### AERIAL BOOSTERS—£3.25

We make three types of Aerial Boosters: B45-UHF 625, B12-VHF 405, B11-VHF RADIO

#### VALVE BARGAINS

Any 5—50p, 10—75p, 50—£3.30:— ECC82, ECL80, EB91, EBF89, EF80, EF85, EF183, EF184, EY86, PCC84, PCC89, PCC189, PC97, PCF80, PCF86, PCF805, PCF808, PCL82, PCL83, PCL84, PCL85, PFL200, PL36, PL81, PL504, PY33, PY82, PY800, PY801, 30L15, EH90.

#### 19" UHF/VHF (BBC2)—£6.00

Thorn-850 or Pye. with set of spare valves. Carriage £2.00 (Untested).

#### 100 MIXED RESISTORS—65p

½ to 2 watt—10 ohms to above 1m-ohms (our choice) 100 mixed Capacitors up to 500MFD—£1.10 (our choice).

#### BARGAIN PARTS

Transistor UHF Tuners—£2.00, 500K-ohms V/C with Switch—20p, 50 mixed Tuner Valves—£2.25, Brand New Transistors (BF115, BF173, BC171, BC153, BC135, BC113, BC117, BC115, BA102, BA129. All 10p each.

All prices include V.A.T. p. & p. 10p per order. Money back refund, S.A.E. for leaflets.

#### ELECTRONIC MAILORDER (BURY) LTD.

62 Bridge St., Ramsbottom, Bury, Lancs. Tel. Rams 3036

Build the Mullard C.C.T.V. Camera Kits are now available with comprehensive construction manual (also available separately at 76p) Send 5" x 7" S.A.E. for details to **CROFTON ELECTRONICS** 15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

19" AND 23" Murphy Astra U.H.F. Conversion Plinths (Tuner + I.F.s etc.) £7 each, £13 the two. I.F. Chassis only £3. Two push button Ekco U.H.F. Tuners £4 each. Six transistor push button tuners (faulty) £10. Four rotary tuners £5. Four various U.H.F. I.F. chassis (unused) £5. Four Perdio Audio Amp Panels £2.50. Various S/H Murphy V410 spares £2.—£40 the lot, collected. Carr. extra. Colour, Bush/Murphy decoders and Frame/Line Panels for recent sets, £10 each.—Tricker, High Street, Cavendish, Sudbury, Suffolk. Tel. Glemsford 424.

**BRAND NEW 26" Colour TV Cabinets.** Slight seconds without backs. All with doors in Dark Teak. Delivered by return for £10. C.W.O. to Trade Disposals (ctv cab) 1043 Leeds Road, Bradford 3.

**ALUMINIUM SHEET** to individual sizes or in standard packs, 3p stamp for details. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warks.

## SOUTHERN VALVE CO. P.O. Box 144 BARNET, HERTS.

All new and boxed, Mazda & Mullard wherever possible. Lists sae. Mail order only

AZ31 62p	EY86/7 35p	PL38 90p	U193 31p	30P19 70p
DY86/7 34p	EZ40/1 40p	PL81 45p	U404 40p	30PL1 60p
DY802 40p	EZ80 35p	PL81A 48p	U801 90p	30PL3 75p
EB91 15p	EZ81 25p	PL82 37p	Y3 35p	30PL4 80p
ECC81 34p	GY501 75p	PL83 45p	YZ4 35p	30PL15 80p
ECC82 25p	GZ30 40p	PL84 45p	6/30L2 60p	30P4MR 88p
ECC83 25p	PC86 46p	PL500 } 58p	6AT6 30p	25W4 35p
ECC85 36p	PC88 46p	PL504 } 58p	6BW7 60p	30CD6G £1.25
ECC88 45p	PC97 38p	PL508 70p	6CD6G 80p	etc. etc.
ECH42 70p	PC900 45p	PL509 £1.40	6F24/5 60p	
ECH81 34p	PCC84 33p	PL802 85p	6F28 60p	
ECH84 50p	PCC85 35p	PL805 78p	6K7/8 35p	
ECL80 40p	PCC88 60p	PY32/3 47p	6V6 35p	
ECL82 45p	PCC89 45p	PY81 31p	6X4 30p	
ECL83 57p	PCC189 48p	PY88 33p	6X5 35p	
ECL86 40p	PCF80(L) 28p	PY800 31p	6Y7 40p	
EF80 24p	PCF80(Br) 38p	PY801 31p	10C2 75p	
EF85 36p	PCF82 50p	PY800 80p	10F1 45p	
EF86 50p	PCF86 48p	UBF89 35p	10P13 70p	
EF89 30p	PCF200 45p	UCH85 40p	12BA6 40p	
EF183 32p	PCF801 48p	UCH42 50p	20L1 80p	
EF184 32p	PCF802 45p	UCH81 40p	20P3 80p	
EH90 45p	PCF805 55p	UCL82 40p	20P4 80p	
EL34 54p	PCF806 55p	UCL83 55p	20P5 95p	
EL41 50p	PCF808 50p	UF41 50p	30C1 38p	
EL42 47p	PCH200 55p	UF85 35p	30C15 75p	
EL84 30p	PCL82 32p	UF89 35p	30C18 50p	
EL86 38p	PCL83 45p	UL41 55p	30F5 75p	
EL90/1 40p	PCL84 32p	UL84 42p	30FL1 50p	
EL95 40p	PCL85 40p	UY41 35p	30FL2 50p	
EM34 99p	PCL805 } 40p	UY85 30p	30L1 35p	
EM80/1 40p	PCL86 32p	U25 62p	30L15 75p	
EM84 40p	PFL200 55p	U26 60p	30L17 70p	
EYS1 45p	PL36 52p	U191 60p	30P12 70p	

The above types, and many others, are in stock at time of going to press. These are new lower prices, assuming V.A.T. at 10%. Transistor lists s.a.e. All valves new and boxed but we cannot always guarantee any specific make. Postage: 3p per valve / post free over £3.00. Tel. (Office): 440 8441

# PHILIP H. BEARMAN

(VALVE SPECIALISTS) SUPPLIERS TO H.M. GOVT. Etc.

NEW valves by Mullard, Mazda, Telefunken etc.,

IMMEDIATE POSTAL DESPATCH, LISTS S.A.E., DISCOUNT PRICE

PRICES FROM 1.4.1973 (INCL. V.A.T.)

DY86/7 33p	PC88 61p	PCL86 53p	6/30L2 80p	30PL13 95p
DY802 37p	PCF80 43p	PL36 70p	6BW7 66p	30PL15 95p
EB91 23p	PCF86 53p	PL81 62p	6CD6 88p	etc. etc.
ECC81 40p	PCF801 53p	PL84 53p	6F23 85p	
ECC82 37p	PCF802 55p	PL500/4 70p	6F28 60p	
ECL80 43p	PCF805 73p	PY81 40p	20L1 88p	
EF80 37p	PCF808 70p	PY800 40p	20P4 88p	
EF183 49p	PCL82 41p	PY801 40p	30C15 84p	
EF184 49p	PCL83 53p	U25 80p	30FL1/2 60p	
EH90 46p	PCL84 49p	U26 80p	30L15 84p	
EY51 60p	PCL85 } 53p	U191 80p	30L17 84p	
EY86/7 33p	PCL805 } 53p	U193 80p	30P12 84p	
GZ34 63p	PCL805 (non BVA) 44p	U251 83p	30P11 66p	
PC86 61p				





POST FREE OVER £3, BELOW THIS add 3p per valve

Large PCF80 30p. Sorry, no 10C1, X78, X79 or 12AH8. (some equivs available) See separate Component, CRT and Transistor Lists. Many obsolete types available.

(Adjacent to Post Office) **6 POTTERS RD., NEW BARNET HERTS.** Tel: 449/1934-5 any time.

Local Agents: MANOR SUPPLIES, 172 WEST END LANE, LONDON NW6 Tel: 794/8751. (Near West Hampstead Tube Station)

# COLOUR TV

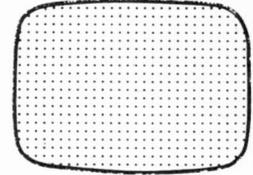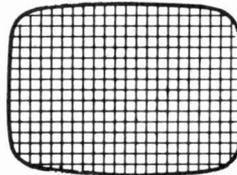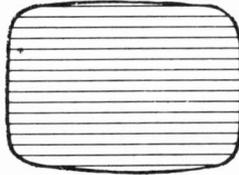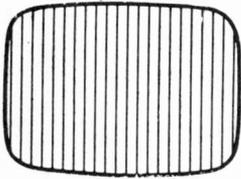

## CROSS HATCH GENERATOR

Complete kit for Cross Hatch Generator as described in "TELEVISION" September issue

The only way to obtain 100% convergence of colour guns in any colour TV

### £3.85

(INC. 10% VAT)

COMPLETE KIT POST PAID

Please send me the free BI-PRE-PAK Catalogue  
Please send me kits of parts for Cross Hatch Generator  
I enclose cheque/P.O./M.O. for

Name \_\_\_\_\_  
Address \_\_\_\_\_

## BI-PRE-PAK LTD

DEPT. G. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.  
TELEPHONE: SOUTHEND (0702) 46344

Reg. No. 820919

### CUT PRICE T.V. AERIALS

**U.H.F. Aerialite supreme** (fringe model) £5.50; Set Top 6 ele. £1.60, 10 ele. £1.50, 18 ele. £2.00; J. Beam MBM30 £3.80, MBM46 £5.50.

**STEREO RADIO** 2 ele. £2.50, 3 ele. £4.00, 4 ele. £4.40, 6 ele. £6.80.

**COAX. CABLE** Low loss random lengths, 2 yds.—12 yds., 5p yd.; cut lengths 8p yd., standard cable 5p yd.

**AMPLIFIERS:** Pye/Labgear. Distribution 6+2 outlets £16.20, 1 outlet £10.50; Mast head/power unit £8.50. Set back batt. op. £3.75.

**ACCESSORIES:** Coax plug 9p, surface socket 30p, flush socket 50p, line connector 14p, Diplexers v.h.f. band 1/3 50p, u.h.f. gp. A/B-CD or A-B/CD 75p, splitters 90p, plastic tape 24 yds. x 1/2" 25p, cable clips 7mm 30p 100, 5mm 25p 100.

**LASHING EQUIPMENT:** Universal clamps 45p, lash kit 1"—1 1/4" masts £1.00, wall-mounting bracket 75p, loft-mounting kit 55p. Please add 10% V.A.T. to all items. Please state ch. gp. clearly.

P.+ P.: Aerials 50p; other items 30p. C.W.O. to:

**H. A. ELECTRIC**  
Dept. P.T.  
2 & 4 BARDEN LANE  
BURNLEY. LANCs.

### COLOUR T.V.

19" £125 25" £160

Completely overhauled. (Not to be confused with 'workers'.) Variety of makes and models available, cash'n'carry discounts given where possible.

#### MONOCHROME

**UHF SINGLE-STANDARD** 19" T.V.'s completely refurbished with pushbutton UHF tuner, etc. Can be seen working at our Langley showroom. £28.50 (carr. £2.50). (Also some requiring attention £20).

**UHF—working and overhauled** BBC2 T.V.'s £20, carr. £2. State if VHF operation required.

**VHF—available cheap!**

**PUSH-BUTTON** type UHF transistorised tuners **BRAND NEW** untested £5, inc. carr.

### TV STANDS



To suit: DECCA CTV19/25 BUSH CTV25 series

THORN 2000, 3000

PYE CT70 etc. etc. . . .

**ALL MONOCHROME and COLOUR SETS**—Slim, attractive yet robust stands—crafted in selected woods—double dowel.

led joints for strength—the finishing touch to any set. Send £3.25 S0p carr. and state length and depth of set. Supplied "in the white" or stained and polished to your order at no extra charge.

All prices include V.A.T.  
**SUMIKS, 7 High Street, Langley, Warley, Worcs.**  
(Near turn-off No. 2, M5 Motorway)  
Trade enquiries welcome.

### PLEASE MENTION TELEVISION WHEN REPLYING TO ADVERTISEMENTS

#### rebuilt T.V. tubes for men of vision

	Current types	
17"	£4.00	21" £5.00
19"	£4.00	23" £5.00

	Panorama & Ringuard types	
19"	£6.00	23" £8.00

	Twin panel
19"	£7.50

Cash or P.O. with order, no C.O.D. Carriage 50p in England, Scotland, Wales. Add 75p for carriage Northern Ireland. For all enquiries please send S.A.E. Each tube fitted with new electron gun assembly. Fully guaranteed for two years against any fault except breakage.

k.s.t. Ltd.

Providence Mills, Viaduct St., Stanningly, Nr. Leeds, Yorks. Tel. Pudsey 78177

TERMS Retail mail order subject to £1.00 minimum order.  
Cash with order only. Trade and educational establishments  
M/AC on application (minimum £5.00).


Postage 10p inland, 25p, Europe

GUARANTEE: All goods carry full manufacturer's  
warranty. Get in touch today for a complete  
run-down of devices available from SCS (include SAE).



SCS COMPONENTS, P.O. Box 26,  
Wembley, Middlesex HA0 1YY  
The 'Professional' Amateur Supplier

## device of the month ZN414

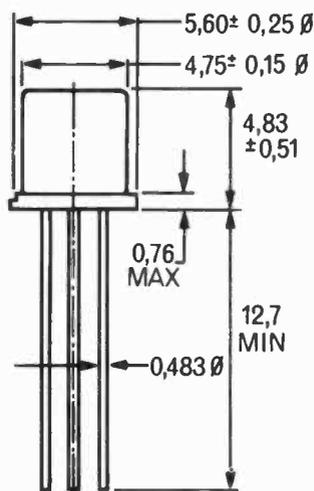


The Ferranti ZN414 is a complete a.m. radio circuit which operates from 1.1 to 1.8 volts and requires only battery, earphones and antenna plus a tuning capacitor and two decoupling capacitors. The ZN414 features: medium and long waveband, good stability on assembly, no setting up of IF coils, plus much more.

a complete a.m radio circuit for just

£1.20  
+ VAT

## compatible device MFC4000B

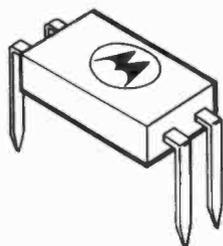

The Motorola  $\frac{1}{4}$ -Watt Audio Amplifier is designed for the output stage of battery powered portable radios.

- \* 250 mW of Audio Output Power
- \* Low Standby Current – 3.5 mA typical
- \* Low Harmonic Distortion
- \* Reduces Component Count in Portable Radios by Two Transformers and Two Transistors
- \* Eliminates Costly Component Matching Requirements

motorola 1/4 watt audio amplifier MFC4000

50p  
+ VAT

# TV LINE OUTPUT TRANSFORMERS

ALL MAKES SUPPLIED PROMPTLY by our  
**RETURN OF POST MAIL ORDER SERVICE**

All Lopts at the one price

**£4.40 TRADE £4.95 RETAIL (INCLUDING V.A.T.)**

Except

BUSH MODELS TV53 to TV67 TV94 to TV101  
EKCO MODELS TC208 to TC335, TV407 to TV417  
FERGUSON MODELS 405 to 438, 506 to 546.  
FERRANTI MODELS 1084 to 1092.

Post and Packing 28p COD 33p  
HMV MODELS 1876 to 1878, 1890 to 1896, FR 20.  
MURPHY MODELS 653X to 789 OIL-FILLED  
REGENTONE MODELS 10-4 to 10-21, 1718, R2, R3, 191, 192.  
RGD 519-621, 710, 711.

ALL AT £2.75 + 28p P&P

**EHT TRAYS SUPPLIED - MONO & COL.**  
All Lopts NEW and GUARANTEED for SIX MONTHS

E. J. PAPWORTH AND SON Ltd.,  
80, MERTON HIGH ST., LONDON, S.W.19

01-540 3955  
01-540 3513

## PHILIP H. BEARMAN, 6 POTTERS RD., NEW BARNET, HERTS.

One of the finest range of new and makers rebuilt tubes in the country; every tube is tested before it leaves the premises. Delivery usually ex stock and sent securely packed daily. Commonwealth deliveries arranged.

### FOR EXAMPLE: NEW TUBES TWO-YEAR GUARANTEE

	Cge.	(including insurance Mono)
CME1702, AW43-80, CRM173, MW43-80, SE17/70 (£5.50) CRM172, AW43-88, AW43-89, CME1705, CME1703 17" C17AF	<b>£6.46</b>	55p
CME1903, CME1902, CME1901, AW47-90, AW47-91, A47-14W, C19AH 19"	<b>£7.56</b>	60p
CME2101, AW53-88, AW53-89, CRM211, CRM212, MW53-20, MW53-80, CME2104 21"	<b>£8.66</b>	65p
CME2303, CME2301, AW59-90, AW59-91 A59-15W, CME2308 23"	<b>£10.45</b>	65p

(NOTE new SE17/70 will replace MW43/69 with mods.)

### Makers Rebuilt Tubes:

CME1908 } £6.05	CME2308 } £8.25
" 1903 } £6.05	" 2303 } £8.25
AW47-91 } £6.05	AW59/91 } £8.25
A47-14W } £6.05	A59/15W } £8.25

### MAKERS COLOUR TUBES

17" available.	4 YEAR GUARANTEE	
19" A49.11X, A49.191X	<b>£53.90</b>	PLUS £1.50 Cge. packing and breakage insurance
20" A51.110X 90%	<b>£55.00</b>	
22" A55.14X, & A56.120X	<b>£58.30</b>	
25" A63.11X, use A63.200X	<b>£62.70</b>	
26" A67.120X, A66.120X	<b>£64.90</b>	

USUALLY EX STOCK EXCEPT A66.120X (short supply) please enquire

NOTE: Above prices from 1st April 1973 include 10% V.A.T.

**10% V.A.T. HAS  
BEEN INCLUDED  
FROM 1/4/1973!**

RIMBAND & TWIN PANELS  
COMPLETE WITH BSI  
415/1972 (implosion safety)

ALL SEA  
JOURNEYS  
50p EXTRA

EIRE E2  
EXTRA FOR  
CUSTOMS  
CLEARANCE

### NEW TUBES (1601 as available)

*TSD282 (TSD217)	<b>£13.75</b>
A28-14W (Mullard)	<b>£12.10</b>
MW31-74	<b>£3.30</b>
TSD290/CME1201	<b>£10.78</b>
A31/120W-CME1220	<b>£10.78</b>
*13BP4	<b>£15.40</b>
MW36/24 & 44	<b>£5.23</b>
CME1602	<b>£11.00</b>
CME1713	<b>£13.20</b>
CME1906 }	<b>£12.10</b>
A47-13W }	<b>£12.10</b>
A47-11W & 26W	<b>£9.35</b>
A50-120W/CME2013	<b>£11.55</b>
†CME2306 }	<b>£16.50</b>
A59-13W }	<b>£16.50</b>
A59-11W & 25 or 23W	<b>£12.65</b>
CME2413/A61, 120W	<b>£14.30</b>

carriage up to 17" 55p.

\* Two Year Guarantee Except TSD282 and 13BP4 1 year.

NOTE: A47-11W and A59-11W makers rebuilds sometimes available at £1.00 off new prices.

† Rebuilt T/Panel (£13.20 (when available))

Telephone enquiries welcomed.  
MONO QUALITY DISCOUNTS IN CERTAIN CASES

OPEN SATURDAY MORNINGS  
CLOSED THURSDAY AFTERNOONS

TELEPHONE: 01-449 1934/5. ALL ENQUIRIES SAE PLEASE

# WITWORTH TRANSFORMERS

TV Line out-put transformers  
(Discounts to Trade)

## ALL ONE PRICE

### £5.17 EACH V.A.T. & CARRIAGE PAID

ALBA	
T1090	TI435
T1095	TD1420
T1135	TD1435
T1195	TD1824
T1235	TS 1320
T1395	TS 1724

BAIRD		
600	628	662 674
602	630	663 675
604	632	664 676
606	640	665 677
608	642	666 681
610	644	667 682
612	646	668 683
622	648	669 685
624	652	671 687
625	653	672 688
626	661	673

Please quote part No. normally found on tx. base plate; 4121, 4123, 4140 or 4142.

COSSOR		
CT1700u	CT1975a	CT1962-77*
CT1910a	CT1976a	CT1954-77*
CT1911u	CT2100u	CT1964-78*
CT1921a	CT2310a	
CT1922a	CT2311a	
CT1935a	CT2321a	
CT1937a	CT2331a	
CT1938a	CT2332a	
CT1972a	CT2373a	
CT1973a	CT2375a	
CT1974a	CT2378a	

\*Two types fitted one has pitch a/w, the other has plastic moulded overwind—please state which type required as they are not interchangeable.

KB				
PV270	QV30 (90°)	WV90	SV20	KV055 KV136
WV05	QV30FM (110°)	MV100/1	SV30	056 138
KV001	QV30-1	QF100	SV042	065 155
KV002	30	PV100	SV048	066 156
KV005	NV40	KV101	SV054	113 165
KV006	NF60	KV105	SV142	114 166
RV10	RV60	KV107	SV143	124
O15	V15	115	SV148	125
TV15	XV60	117	MV818	126
O17	NF70 or FM	119	MV819	127
QV20	PV70	KT400A	MV903	134
WV20-1	QV70			
RV20	RV70	KT405A		
TV20	VV70	by chassis No.—		
WV20	WV70	VC1 VC4 VC52	VC200	
QVF20	WV75	VC2 VCS VC53		
QV30	QF80	VC3 VCS1 VC100		

MURPHY					
V310	V430	V520	V879 or C*	V789	V20155S
V310A	V430C	V530	V923*	V153	V20167
V310AD	V430D	V530C	V939 or L*	V159	V20175
V310AL	V430K	V530D	V973C*	V173	V2310
V310CA	V440	V539	V979*	V179	V2311C
V320	V440D	V540	V653X	V1910	V2414D
V320 or D	V440K	V540D	V659	V1913	V2415D
V330F or L	V470	V649D	V683	V1914	V2415S
V410	V480	TM2 Chassis	V739	V2014	V24155S
V410C	V490	V843*	V753	V2014S	V2416D
V410K	V500	V849*	V783	V2015D	V2416S
V420	V510	V873*	V787	V2015S	V2417S
V420K	V519				

\*Two types fitted. One has pitch overwind, the other has plastic moulded overwind. Please state which type required as they are not interchangeable.

FERGUSON, ULTRA, MARCONI, H.M.V. (BRC, Jellypots). ALL MODELS IN STOCK.

#### E.H.T. RECTIFIER TRAYS

Suitable for: FERGUSON, ULTRA, MARCONI, H.M.V.			
Series	Series	Series	1500 Series
850	900 MKII	980	3 stick £3.52 each
900	960	981	5 stick £4.29 each
911	970	982	
950 MKI	1400		
£3.52 each	£4.29 each	£3.52 each	When ordering, model number and series must be quoted.
(Prices include Carriage & V.A.T.)			

FIXING: Direct BRC replacement, will clip into existing transformer.

BUSH		
TUG versions	TV125	
TV75 or C	TV125U	
TV76 or C	TV128	
TV77	TV134	
TV78	TV135	
TV79	TV135R	
TV83	TV138	
TV84	TV138R	
TV85	TV139	
TV86	TV141	
	TV145	
TV91	TV148	
TV92	TV161	
TV93	TV165	
TV94	TV166	
TV95 or C	*TV171	
TV96 or C	TV175	
TV97	TV176	
TV98C	TV178	
TV99 or C	1B15	
TV100	1B3	
TV101C	1B3D	
TV102C	1B3S	
TV103 or D	1B3SS	
TV105 or D or R	1B55	
TV106	1B6	
TV107	1B6D	
TV108	1B6S	
TV109	1B6SS	
TV112C	1915	
TV113	191D	
TV115 or C or R	193S	
TV118	193D	
TV123		
TV124		

From model TV123 to TV139 there have been two types of transformer fitted. One has pitch overwind, the other has plastic moulded overwind. Please state which type required as they are not interchangeable.

PYE	
1	
2	
3 or u	

11u Series	
12u	
13u	State Pt. No. required—
14u	AL21003 or 772494
15u	
20u	

SP17	62
21f or uf	63
22uf	64
23uf	68
24uf	75
31uf	76
35uf	77
36	80
37	81
40f	83
48	84
49	85
53	86
58	95
59	96
60	
61	

PV110	State Pt. No. required—
V110	771980 or 772013

V210 or A	
V220	
V410 or A	State Pt. No. required—
V420A	771927 or 771920
V430A	
V510	
V530	

V200 or LB	
V300s	
V310 or s	
V400	
V600	
V620	
V630	

V700 or A or D	State Pt. No. required—
V710 or A or D	772444 or 771935

GEC									
BT302	BT314	BT321	BT336	BT449	2000	2015	2022	2043	2064
BT303	BT315	BT322	BT337	BT450	2001	2017	2033	2044	2065
BT304	BT316	BT324	BT342	BT451	2010	2018	2032	2047	2066
BT305	BT318	BT326	BT346	BT452	2012	2019	2033	2048	2082
BT308	BT319	BT328	BT347	BT455	2013	2020	2038	2063	2083
BT312	BT320	BT329	BT448	BT456	2014	2021	2039		

DECCA									
DR20	DR34	DR71	DR505						
DR21	DM35	DR95	DR606						
DR23	DM36	DR100	666TV-SRG						
DR24	DM39C	DR101	777TV-SRG						
DR29	DR41	DR121							
DR30	DM45	DR122	MS1700						
DM30	DR49C	DR123	MS2000						
DR31	DM55	DR202	MS2001						
DR32	DM56	DR303	MS2400						
DR33	DR61	DR404	MS2401						

EKCO									
TC403	TC437	T513	531						
404	T442	514	T532						
406	T500	515	533						
T418	TC501	520	535						
TC419	T502	521	536						
T420	503	524	540						
TC421	504	525	541						
T422	505	526							
433	506	527							
434	510	528							
TC435	511	529							
T436	512	530							

FERRANTI									
1075	TC1122	1163	1155	1175					
1080	1123	1164	TC1157	1176					
1081	1124	1165	1158	TC1181					
1082	1125	1174	1159	TC1182					
1083	TC1126	1175	TC1160	TC1185					
1093	1137	TC1135	1162	TC1186					
1094	TC1154	1136	1163						
1095	TC1155	1137	TC1164						
1096	1157	1138	TC1165						
1097	1159	1140	TC1173						
1121	1160	TC1154	1174						

PHILLIPS		
1768u		19TG122a
1792u	Exchange	19TG123a
1796u	Units	19TG125a
2168u		19TG133a
2192u		19TG142a
2196		19TG148a
		19TG152a
		19TG153a
		19TG154a
		19TG155a
		19TG156a
		19TG158a
		19TG164a
		19TG170a
		19TG171a
		19TG172a
		19TG173a
		19TG175a
		19TG176a
		19TG177a

177G100		
177G102		
177G106		
177G200		
177G300		
19TG108u		
19TG111a		
19TG112u		
19TG114u		
19TG116u		
19TG121a		
19TG179		

21TG100u	G19T210	G23T210
21TG102u	G19T211	G23T211
21TG106u	G19T212	G23T212
21TG109u	G19T213	G24T230
23TG107u	G19T214	G24T232
23TG111a	G19T215	G24T236
23TG112a	G20T230	G24T238
23TG121a	G20T232	G24T300
23TG122a	G20T236	G24T301
23TG131a	G20T238	G24T302
23TG142a	G20T300	G24T306
23TG152a	G20T301	G24T307
23TG153a	G20T302	G24T308
23TG156a	G20T306	G24T307
23TG164a	G20T307	
23TG170a	G20T308	
23TG171a		
23TG173a		
23TG175a		
23TG176a		
23FG632		

ALL MAKES OF COLOUR TRANSFORMERS IN STOCK

Every item listed stocked. Many newer and older models in stock. S.A.E. for quotation For by-return service contact your nearest depot.

Tidman Mail Order Ltd., Dept. NA.  
236 Sandycombe Road,  
Richmond, Surrey.  
London: 01-948 3702 or 01-940 8146

Hamond Components (Midland) Ltd., Dept. NA.  
89 Meriden Street,  
Birmingham 5.  
Birmingham: 021-643 2148

#### SPECIAL

L.O.P. Transformer as specified for "Television" Colour Set only. £5.17 ea. V.A.T. & Carriage Paid

# FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained thousands of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B.; Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.


"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BTVO6 Aldermaston Court, Reading RG7 4PF.

Everything you need to know about **TV maintenance and repairs**. Save £££'s on maintaining your own TV.

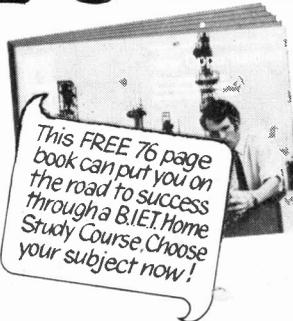A spare time income can be yours or study up to City & Guilds for a **career** that can change your whole future.



#### CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

<b>MECHANICAL</b>	<input type="checkbox"/> Man. Prod.—cont.	<input type="checkbox"/> Constructional-cont.
A.M.S.E. (Mech.)	<input type="checkbox"/> Quality Control	<input type="checkbox"/> Building
Boiler Inspect.	<input type="checkbox"/> Salesmanship	<input type="checkbox"/> Building Drawing
& Operation	<input type="checkbox"/> Storekeeping	<input type="checkbox"/> Build. Foreman
C & G Eng. Crafts	<input type="checkbox"/> Work Study	<input type="checkbox"/> Carpentry & Join.
C & G Fabricat.	<input type="checkbox"/> Works	<input type="checkbox"/> Civil & Municipal
Diesel Eng.	<input type="checkbox"/> Management	<input type="checkbox"/> Engineering
Eng. Inspection	<input type="checkbox"/> A.M.I.E.B.	<input type="checkbox"/> Constructional
Eng. Metallurgy	<input type="checkbox"/> Draughtsmanship	<input type="checkbox"/> Engineering
Inst. Eng. & Tech.	<input type="checkbox"/> Design of Elec.	<input type="checkbox"/> Construction
Inst. Motor Ind.	<input type="checkbox"/> Machines	<input type="checkbox"/> Surveyors
Mainten. Eng.	<input type="checkbox"/> Die & Press Tool	<input type="checkbox"/> Institute
Mechanical Eng.	<input type="checkbox"/> Design	<input type="checkbox"/> Clerk of Works
Sheet Metal Work	<input type="checkbox"/> Electrical	<input type="checkbox"/> Council Eng.
Welding	<input type="checkbox"/> Draughtsmanship	<input type="checkbox"/> Geology
	<input type="checkbox"/> Gen. Draughtsmanship	<input type="checkbox"/> Health Eng.
	<input type="checkbox"/> Jig & Tool Des.	<input type="checkbox"/> Hydraulics
	<input type="checkbox"/> Tech. Drawing	<input type="checkbox"/> Inst. of Builders
<b>ELECTRICAL &amp; ELECTRONIC</b>	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS	<input type="checkbox"/> Highway Sup.
A.M.S.E. (Elec.)	<input type="checkbox"/> Colour TV	<input type="checkbox"/> Painting & Dec.
C & G Elec. Eng.	<input type="checkbox"/> C & G Radio/TV/	<input type="checkbox"/> Public Hygiene
C & G Elec. Inst.	<input type="checkbox"/> Electronics	<input type="checkbox"/> Road Engineer.
C & G Elec. Tech.	<input type="checkbox"/> C & G Telecomm.	<input type="checkbox"/> Structural Eng.
Computer Elect.	<input type="checkbox"/> Tech.	<input type="checkbox"/> Surveying
Elec. Maths	<input type="checkbox"/> Prac. Rad. Elec.	<b>GENERAL</b>
Elec. Science	<input type="checkbox"/> (with kit)	<input type="checkbox"/> Agricultural Eng.
Electronic Eng.	<input type="checkbox"/> Radio Amateurs	<input type="checkbox"/> Council of Eng.
Electrical Eng.	<input type="checkbox"/> Exam.	<input type="checkbox"/> Inst.
Install. & Wiring	<input type="checkbox"/> Radio Servicing	<input type="checkbox"/> Farm Science
Meters	<input type="checkbox"/> & Repairs	<input type="checkbox"/> General Educat.
& Measuring	<input type="checkbox"/> Radio & TV Eng.	<input type="checkbox"/> Gen. Plastics
Instruments	<input type="checkbox"/> Trans. Course	<input type="checkbox"/> Pract. Maths
	<input type="checkbox"/> TV Main. & Serv.	<input type="checkbox"/> Pract. Slide Rule
<b>MANAGEMENT &amp; PRODUCTION</b>	<input type="checkbox"/> AUTO & AERO	<input type="checkbox"/> Pure & Applied
Auto Control	<input type="checkbox"/> Aero Eng.	<input type="checkbox"/> Maths
Computer Prog.	<input type="checkbox"/> A.M.I.M.I.	<input type="checkbox"/> Refrigeration
Electronic Data	<input type="checkbox"/> A.E.C. Cert.	<input type="checkbox"/> Rubber Tech.
Processing	<input type="checkbox"/> Auto Engineer.	<input type="checkbox"/> Sales Engineers
Estimating	<input type="checkbox"/> Auto Repair	<input type="checkbox"/> Tech. Report
Foremanship	<input type="checkbox"/> C & G Auto. Eng.	<input type="checkbox"/> Writing
Inst. Cost & Man	<input type="checkbox"/> Garage	<input type="checkbox"/> Timber Trade
Accountants	<input type="checkbox"/> Management	<input type="checkbox"/> University Ent.
Inst. Marketing	<input type="checkbox"/> MAA/IMI Dipl.	
Management	<input type="checkbox"/> Motor Vehicle	
Metrication	<input type="checkbox"/> Mechanics	
Motor Trade Man.	<input type="checkbox"/> CONSTRUCTIONAL	
Network Plan.	<input type="checkbox"/> A.M.S.E. (Civil)	
Numerical Cont.	<input type="checkbox"/> Architecture	
Operational		
Research		
Personnel Man.		
Planning Eng.		
Production Eng.		

Coaching for many major exams. including ONC, C & G, etc.

**G.C.E.**  
58 'O' & 'A'  
LEVELS SUBJECTS  
Over 10,000  
group passes

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BTVO6 Aldermaston Court, Reading RG7 4PF

NAME  Block Capitals Please ADDRESS

OTHER SUBJECTS  AGE

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY