

DECEMBER 1977

Australia 75c
New Zealand 75c

South Africa 70c
Malaysia \$2.25

50 p

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS

Ten Years of

COLOUR



ALSO:

CRT FAULTS;

ACTIVE CO-CHANNEL INTERFERENCE FILTER;

VCR SERVO FAULTS

ARE YOU IN THE DARK?
...ABOUT OUR



COLOUR T.V. PANEL EXCHANGE REPAIR SERVICE

FULL RANGE OF
THORN · RBM · PHILIPS · PYE · INVICTA
GEC · DECCA · TELPRO
AND MANY OTHER MAKES

90 DAY GUARANTEE ON ALL REPAIRS, SAME DAY POSTAL SERVICE

We employ a large skilled Staff, who utilise some of the most sophisticated Test equipment available, inclusive of AUTOMATIC FAULT FINDING COMPUTERS together with specially designed SERVICING JIGS which in short means to you:—

HIGH QUALITY REPAIRS – AT LOW COST



ONE OFF OR



100 OFF · NO ORDER TOO
LARGE OR SMALL

SEND FOR PRICE LIST

SEND FOR CATALOGUE
BLOCK DISCOUNTS FOR TRADE CONTRACTS

TO

Campbell Electronics Ltd.

Factory Unit E5, Halesfield 23, Telford, Shropshire TF7 4QX

Telephone: Telford ((0952) 584373, Ext. 2. Telex 35191 Chamcon

RADIO AND TV SPARES ALL COMPONENTS BRAND
NEW. CASH WITH ORDER ONLY. P & P 35np. ALL
PRICES INCLUDE VAT. AT 12½%

MAIL ORDER ONLY.
CALLERS BY APPOINTMENT
ONLY.

PHD COMPONENTS DEPT 3, UNIT 7,
CENTENARY ESTATE, JEFFERIES ROAD,
ENFIELD, MIDDX. 01-805 4060. TELEX 261295.

MULTISECTION CAPACITORS

Description	Price
400-400/350	3 00
200-200-150 50/300	2 50
1000-2000/35	80p
600/300	1 90
600/250	1 55
200 300/350	2 05
1000-1000/40	1 00
2500-2500/30	1 30
300 300/300	2 25
200 200-75-25/350	2 40
100-300-100-16/275	1 60
150 100-100 100-150/320	2 60
150-150-100/350	1 50
175 100-100	2 35
220/100	32p
2500-2500/63	1 70
700/200	1 30
400/350	1 55

DROPPER SECTIONS 16p each

MAINS DROPPERS		Price
Pye 11062		75p
Pye 11009		1 20
BRC Mono 1400		80p
BRC Mono 1500		75p
BRC Colour 3000/3500		75p
BRC Colour 8000		75p
BRC Colour 8500		75p
Phillips G8		50p
Phillips 210 (with link)		55p
Phillips 210		65p
RR1 Mono 141		75p
RR1 Mono 161		80p
GEC 27840		75p
GEC 2000		75p
Phillips G9		35p

DIODES

OA81 11p	BA102 24p	BAX13 5p
OA85 11p	BA130 35p	BAX16 6p
OA90 6p	BA145 16p	BAY38 10p
OA91 6p	BA148 16p	IN4148 4p
OA95 6p	BA154 12p	BY206 30p
OA202 11p	BA155 15p	
BA100 14p	BA164 17p	

RECTIFIERS

BY100 21p	IN4001 4p	TUNER ELC1043/05 5 50 each
BY126 15p	IN4002 5p	
BY127 15p	IN4003 6p	CRYSTAL 4 43 MHz 1 90 each
BY133 22p	IN4004 7p	
BY182 2 00	IN4005 8p	
BY238 40p	IN4006 9p	
BYX10 14p	IN4007 10p	

THYRISTORS

2N4443 1 20	
TV106 1 80	
BR101 45p	
BRV39 45p	
BR100 35p	

Bridge Rectifiers

BY164 50p
BY179 65p

High Voltage

TV20 1 90 each

INTEGRATED CIRCUITS

MC1307P 1 50	SL901B 5 00
MC1310P 2 50	SL917B 7 00
TAA350 1 90	SN76003ND 1 70
TAA550 50p	SN76013N 1 80
TAA630S 4 00	SN76013N07 1 80
TBA120S 1 50	SN76013ND 1 60
TBA120SQ 1 50	SN76023N 1 85
TBA520Q 3 00	SN76023ND 1 60
TBA530Q 2 50	SN76033N 2 75
TBA540Q 3 00	SN76655N 2 50
TBA550Q 4 00	CA3065 2 50
TBA560CQ 4 00	MC1358P 2 50
TBA750Q 2 20	MC1327P 2 00
TBA800 1 60	MC1327PQ 2 50
TBA920Q 4 00	MC1330P 1 50
TBA990Q 4 00	MC1351P 1 20
SN76003N 2 75	MC1352P 1 60

TRANSISTORS

AC107 33p	AF124 23p	BC142 29p
AC126 23p	AF125 23p	BC143 34p
AC127 30p	AF125 23p	BC147 12p
AC12701 50p	AF127 23p	BC148 11p
AC128 23p	AF139 34p	BC149 13p
AC12801 50p	AF178 53p	BC153 19p
AC141 24p	AF179 55p	BC154 19p
AC141K 40p	AF180 53p	BC157 14p
AC142 24p	AF181 49p	BC158 12p
AC142K 25p	AF186 39p	BC159 14p
AC153 23p	AF239 39p	BC171 14p
AC176 24p	AL102 1 05	BC172 13p
AC17601 50p	AU107 1 05	BC178 21p
AC187 23p	AU110 1 85	BC179 19p
AC187K 24p	AU113 2 20	BC182L 10p
AC188 24p	BC107 10p	BC182LB 10p
AC188K 40p	BC108 10p	BC183L 10p
AC193K 29p	BC109 10p	BC183LB 10p
AC194K 31p	BC113 12p	BC184L 10p
AD140 45p	BC114 19p	BC186 24p
AD142 50p	BC115 19p	BC187 26p
AD143 50p	BC116 19p	BC203 15p
AD145 50p	BC117 19p	BC204 15p
AD149 1 00	BC118 28p	BC205 15p
AD161 45p	BC119 28p	BC206 15p
AD162 45p	BC125 21p	BC207 15p
AF114 50p	BC126 19p	BC208 11p
AF115 23p	BC136 19p	BC209 15p
AF116 23p	BC137 19p	BC212L 11p
AF117 19p	BC138 19p	BC213L 11p
AF118 48p	BC139 19p	BC214L 11p
		BC225 15p

BC237 15p	BF118 25p
BC238 11p	BF121 24p
BC251A 16p	BF152 30p
BC301 32p	BF154 30p
BC303 59p	BF157 30p
BC307 11p	BF158 24p
BC308 9p	BF163 24p
BC327 12p	BF167 24p
BC328 12p	BF173 24p
BC337 15p	BF177 29p
BC547 12p	BF178 32p
BD115 64p	BF179 32p
BD116 60p	BF180 34p
BD124 79p	BF181 32p
BD131 44p	BF182 43p
BD132 49p	BF183 43p
BD133 49p	BF184 25p
BD134 49p	BF185 25p
BD135 39p	BF194 14p
BD136 45p	BF195 14p
BD137 47p	BF196 14p
BD138 49p	BF197 14p
BD139 80p	BF198 19p
BD144 2 10	BF199 24p
BD155 74p	BF200 34p
BD157 74p	BF240 19p
BD183 55p	BF241 21p
BD235 74p	BF256LC 44p
BD237 74p	BF257 48p
BD238 74p	BF258 65p
BDX32 2 50	BF271 15p
BF115 19p	BF273 15p

BF274 15p	BF336 34p
BF337 34p	BF338 34p
BF458 59p	BFX29 29p
BFX84 24p	BFX85 25p
BFX88 23p	BFX89 30p
BFY50 22p	BFY51 22p
BFY52 22p	BU105/01 1 90
BU105/02 1 90	BU105/04 2 50
BU108 3 00	BU126 2 90
BU204 1 90	BU205 1 90
BU206 1 90	BU208 3 00
MJE340 65p	MJE520 80p
AF126 1 10	MJE3055 73p
MPSU05 65p	MPSU05 1 25
R2008B 3 00	R2009 3 00
R2010B 3 00	RIP31A 60p
TIP31A 60p	TIP32A 60p

REPLACEMENT COMPONENTS


Aerial Isolators	1 00 each
Loft Korting	10 00 each
BRC 3500 Cutouts	1 60 each

VALVES

DY86/87 50p	PCL82 75p
DY802 50p	PCL84 1 00
ECC82 50p	PCL85 90p
EF80 45p	PCL86 90p
EF183 46p	PL200 85p
EF184 46p	PL36 90p
EH90 90p	PL84 70p
PCC89 1 20	PL504 1 20
PCC189 1 60	PL508 2 00
PCF80 75p	PL509 3 00
PCF86 1 50	PL519 3 00
PCF801 60p	PY500A 1 90
PCF802 1 50	PY800 65p
	PL802 4 00

EHT TRIPLERS (Priced each)

BRC950 2 65	Pye CT205 5 50
BRC1400 2 65	Pye 731 8 25
BRC1500 (17") 2 61	Decca 2030 6 60
BRC1500 (24") 3 01	GEC 2028 7 10
BRC3500 6 60	GEC 2110 7 10
BRC8000 2 90	ITT CVC5 6 60
BRC8500 5 50	RR1 111/174 10 00
BRC9000 7 75	RR1 823 7 70
Decca CS190 7 10	Korting 90° 7 10
Phillips G8 7 30	Tanberg 7 10

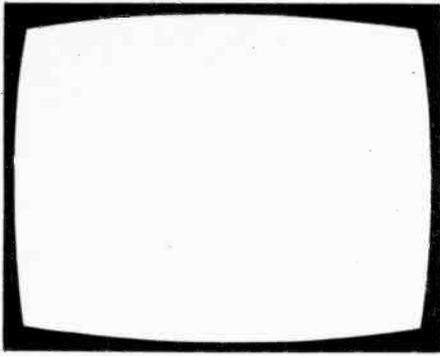

TELEVISION

December
1977

Vol. 28, No. 2
Issue 326

COPYRIGHT

© IPC Magazines Limited, 1977. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. All other correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

BINDERS AND INDEXES

Binders (£2.85) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders add 60p to cover despatch and postage.

BACK NUMBERS

Some back issues, mostly those published during the last two years, are available from our Post Sales Department (address above) at 70p inclusive of postage and packing to both home and overseas destinations.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Your Problems Solved".

this month

- 61 **Ten Years of Colour**
- 62 **Teletopics**
News, comment and developments
- 64 **Choice of Colour System** *by Pat Hawker*
An account of the attempt to agree to a common colour system for Europe and its failure, leading to the adoption of PAL and SECAM by different countries.
- 69 **Colour Servicing and Receiver Developments** *by E. Trundle*
How the advent of colour affected servicing, and the evolution of colour sets over the last decade.
- 73 **Next Month in Television**
- 74 **Colour Set Production** *by Harold Peters*
The various problems that have beset colour setmakers over the past ten years, as rapid development has taken place while demand soared then fell away.
- 77 **Letters**
- 78 **TV Teletext Decoder Update** *by Steve A. Money, T.Eng. (C.E.I.)*
A summary of amendments and modifications.
- 79 **Co-Channel Interference Filter** *by Allan J. Latham*
Co-channel interference can ruin a picture. With the frequency offset system used by the UK broadcasting authorities however it can be substantially reduced by using a sharp notch filter. An active RC filter for the purpose is described.
- 80 **It Won't Take You a Minute . . .** *by Les Lawry-Johns*
An unfortunate encounter with an Hitachi monochrome portable whose sound slid out . . . and some less trying experiences.
- 82 **The Television Monochrome Portable, Part 3** *by Keith Cummins*
Description of the timebase circuits, plus full details of the printed circuit board.
- 88 **Servicing the Rank A823 Colour Chassis, Part 2** *by R. W. Thomson*
Fault finding in the complex line generator and line output stage circuits.
- 91 **Service Notebook** *by G. R. Wilding*
Notes on faults and how to tackle them.
- 92 **TV Servicing: Beginners Start Here . . . Part 3** *by S. Simon*
How television c.r.t.s are operated and the things that can go wrong with them.
- 95 **The Plemi 103-element Aerial** *by Hugh Cocks*
A review of this impressive high-gain u.h.f. Yagi array.
- 96 **Long-Distance Television** *by Roger Bunney*
Reports on DX reception and conditions, and news from abroad. Also, the effects of Auroras on reception.
- 99 **Readers' Printed Board Service**
- 100 **VCR Servo Fault Finding** *by S. R. Beeching, T.Eng. (C.E.I.), A.M.I.E.R.E.*
Servo systems are used in VCRs to control the head and capstan speed so that correct synchronisation is achieved. An outline of the control technique used in the Philips N1500 series is given, together with an account of logical fault finding.
- 102 **Your Problems Solved**
- 104 **Test Case 180**

OUR NEXT ISSUE DATED JANUARY WILL BE
PUBLISHED ON DECEMBER 19

EX-EQUIPMENT SPARES

MONO TUBES (tested) 19" Rimguard £4.50 23" Rimguard £6.00 20" Rimguard £6.00 24" Rimguard £7.50 + £3.00 p.p.	MONO TUNERS 6 - button integrated all at £6.50 U.H.F. P/Button D/S £4.50 U.H.F. P/Button S/S £6.50 Rotary £3.00 + £1. p.p.	MONO LOPTS All D/Standard Lopts at £4.00 + £1. p.p. All S/Standard at £4.00 + £1. p.p.	MONO PANELS i.e. Philips, Bush etc. £3.50 + £1 p.p. Quotations for complete S/Hand chassis if required. (Diff prices)	MISC. S/Output Trans. £1 + VAT + £1 P&P F/Output Trans. £1.25 + VAT + £1. P&P Scancoils £1.50 + VAT + £1. P&P. Other spares available, please write or phone for details.
---	---	---	--	---

VALVES (MONO & COLOUR)

PCL82 0.10	PCF802 0.10	PCC86 0.10	EY86/7 0.10	30PL1 0.10	PL509 0.50
PCL83 0.10	PCF805 0.10	PC97 0.10	EY8/7 0.10	30PL13/4 0.10	PY500 0.50
PCL84 0.10	PCF806 0.10	PC900 0.10	DY802 0.10	30P12 0.10	GY501 0.50
PCL85 0.10	PCF808 0.25	EF80 0.10	PY800/1 0.10	30FL1/2 0.25	PL508 0.50
PCL86 0.10	PCF80 0.10	EF85 0.10	PL36 0.25	ECC82 0.10	PCH200 0.50
PFL200 0.10	PCC189 0.10	EF183 0.10	PL504 0.25	ECC81 0.10	PCF200 0.50
PCF801 0.10	PCC86 0.10	EF184 0.10	PL81 0.10	ECH81 0.10	CEY51 0.15
30C1 0.10	30C15 0.10	6BW7 0.10	6/30L2 0.10	ECL80 0.10	
30C17 0.10	30C18 0.10	ECC85 0.10	U26 0.10	ECL82 0.10	
PL83 0.10	PL84 0.10	EH90 0.10			

Please note there is 25p p.p. per order

D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUTPUT	POWER	L/TB	F/TB
Bush/Murphy	6.50	6.50	6.50	—	—	6.50	1.50	6.50	—	—
GEC/Sobell	6.50	7.50	—	—	—	6.50	—	—	—	7.50
Philips	6.50	9.50	—	—	—	7.50	—	—	—	6.50
Decca	6.50	12.50	12.50	—	—	6.50	2.00	8.00	—	6.00
							(19" only)			
Thorn 2000	6.50	7.50	7.50	6.50	6.50	7.00	—	8.00	9.50	6.50
Pye	7.50	7.50	9.50	—	—	6.50	—	—	—	4.00
Baird	6.50	8.50	8.50	—	—	6.50	—	—	—	6.00

Postage & Packing £1.25

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	20.00	—	8.00	6.00	20.00	—
GEC Hybrid	9.50	9.50	15.00	—	6.00	—	—	12.00
Philips G6 S/S	9.50	—	15.00	—	9.00	—	—	10.00
Thorn 3000	10.00	9.00	18.00	10.00	6.00	20.00	20.00	10.00
Pye 691/693	15.00	7.50	18.00	—	15.00	—	28.00	7.50
Thorn 3500	10.00	9.00	18.00	10.00	10.00	20.00	20.50	10.00

Korting and other foreign panels available on request.

Postage & Packing £1.25

COLOUR TUBES 19" 18.00 19" A49.192 £20 20" 20.00 22" 25.00 25" 18.00 26" 32.00 Plus P & P £4	COLOUR TUNERS Bush 6.50 GEC 6.50 Philips G6 S/S 6.50 Thorn 3000 6.50 (£8 new) Pye 691/697 7.50 Some new tuners in stock can supply on request. Many Foreign Tuners also available on request. Plus P & P £1	COLOUR LOPTS Most lopts available from £7.00. Both British & Foreign makes. Please ring or write. P & P per lopt £1	MISC. S/Output transformer from £1.50 F/Output from £1.25 Scancoils from £5.00 P & P £1 Other spares available on request.	CABINETS Many British & Foreign cabinets available. Please state. Speakers, masks, etc., available on request. Please phone or write.
--	--	--	--	--

T.V.'s (MONO)

Rotaries	P/Button	P/Button	S/Standard
GEC 5.00	Thorn 1400 9.00	20" 24"	20" 24"
Thorn 950 5.00	Bush 161 9.00	Bush 11.00	Bush 15.00
K.B. Trans-tuners 5.00	Baird 9.00	GEC 11.00	GEC 15.00
Pye 5.00	Philips 210 9.00	Philips 11.00	Philips 15.00
etc.	Pye 9.00	Pye 11.00	Pye 15.00
	etc.	etc.	Thorn 15.00
			etc.

COLOUR T.V.'s

D/S Colour	S/S Colour
19", 25" from £30	19", 20", 22", 24" from £50
i.e. GEC, Bush, Philips, Baird etc.,	Working from £65
	includes many makes as well as foreign models.

REDUCTION ON QUANTITIES

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED.
 PLEASE ADD 12½% V.A.T. TO ALL ITEMS AND OVERSEAS AT COST. CASH WITH ALL ORDERS.

BRIARWOOD TELEVISION LTD.
 Legram Mills, Summerville Road, Bradford, West Yorkshire BD7 1NS Tel (0274) 22046.

BRIARWOOD TELEVISION LTD.

Lagrange Mills, Summerville Road, Bradford, West Yorkshire
BD7 1NS. Tel: (0274) 22046.

All transistors, IC's, offered are new and branded. Manufactured
by Mullard, I.T.T., Texas, Motorola etc.

P & P U.K. 25p per order, overseas allow for package and
postage. Cash with all orders.

Please add 12½% VAT to all items and overseas at cost.

All prices subject to alteration without notice.

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	E.H.T. TRAYS MONO	
AC107	0.23	BC109	0.12	BC307A	0.12	BF218	0.12	OC810	0.14	950 MK2 1400	2.26
AC113	0.17	BC113	0.12	BC308A	0.12	BF219	0.12	OC82	0.20	1500 18" 19" stick	2.37
AC115	0.17	BC114	0.12	BC309	0.14	BF220	0.12	OC820	0.13	1500 24" 5 atick	2.48
AC117	0.24	BC115	0.12	BC547	0.09	BF222	0.80	OC83	0.22	Single stick Thorn TV	
AC125	0.20	BC116	0.12	BC548	0.11	BF221	0.21	OC84	0.28	11.16K 70V	0.75
AC126	0.18	BC117	0.12	BC549	0.11	BF256	0.37	OC85	0.13	TV 20 2 MT	0.75
AC127	0.18	BC119	0.24	BC557	0.11	BF258	0.34	OC123	0.20	TV20 16K 18V	0.75
AC128	0.18	BC125	0.15	BD112	0.50	BF259	0.34	OC169	0.20		
AC131	0.13	BC126	0.11	BD113	0.65	BF260	0.24	OC170	0.22		
AC141	0.23	BC136	0.14	BD124	1.00	BF262	0.32	OC171	0.27		
AC141K	0.33	BC137	0.14	BD131	0.39	BF263	0.25	OA91	0.06		
AC142K	0.33	BC138	0.30	BD132	0.39	BF271	0.28	BRC4443	0.85		
AC151	0.17	BC139	0.20	BD133	0.39	BF273	0.17	R2008B	1.80		
AC165	0.16	BC140	0.25	BD135	0.30	BFX84	0.27	R2010B	1.80		
AC166	0.16	BC141	0.22	BD136	0.30	BFX85	0.27	R2305	0.38		
AC168	0.17	BC142	0.24	BD137	0.30	BFX88	0.24	RY126	0.09		
AC176	0.18	BC143	0.23	BD138	0.30	BFY37	0.22	8Y127	0.11		
AC186	0.26	BC147	0.09	BD139	0.40	BFY51	0.20				
AC187	0.21	BC148	0.09	BD140	0.34	BFY52	0.21				
AC187K	0.35	BC149	0.09	BD222	0.50	BFY53	0.27				
AC188K	0.37	BC153	0.12	BDX22	0.73	BFY55	0.27				
AD130	0.50	BC154	0.12	BDX32	2.30	BHA0002	1.90				
AD140	0.65	BC157	0.09	BDY18	0.75	BR100	0.32				
AD142	0.70	BC158	0.11	BDY60	0.80	BSX20	0.23				
AD143	0.70	BC159	0.11	BF115	0.23	BSX76	0.23				
AD145	0.70	BC160	0.28	BF121	0.30	BSY84	0.36				
AD149	0.75	BC161	0.27	BF154	0.16	BT106	1.10				
AD161	0.45	8C167	0.13	BF158	0.20	BU105/04	2.25				
AD162	0.45	BC168	0.13	BF159	0.20	BU126	1.40				
AD161	1.30	BC169C	1.00	BF160	0.27	BU208	2.45				
AD162	0.42	BC171	0.11	BF163	0.27	OC22	1.10				
AF106	0.42	BC172	0.11	BF164	0.20	OC13	1.30				
AF114	0.22	8C173	0.15	BF167	0.21	OC24	1.30				
AF115	0.22	BC177	0.16	BF173	0.23	OC25	0.45				
AF116	0.22	BC178	0.12	BF177	0.28	OC26	0.40				
AF117	0.22	BC179	0.12	BF178	0.33	OC28	0.60				
AF118	0.58	BC182L	0.09	BF179	0.29	OC35	0.45				
AF121	0.55	BC183L	0.09	BF180	0.31	OC36	0.58				
AF124	0.33	BC184L	0.09	BF181	0.33	OC38	0.43				
AF125	0.33	BC186	0.20	BF182	0.35	OC42	0.45				
AF126	0.33	BC187	0.20	BF183	0.33	OC44	0.18				
AF127	0.33	BC209	0.14	BF184	0.27	OC45	0.18				
AF139	0.39	BC212	0.13	BF185	0.27	OC46	0.35				
AF151	0.24	BC213L	0.09	BF186	0.30	OC70	0.22				
AF170	0.29	8C214L	0.09	BF194	0.10	OC71	0.28				
AF172	0.20	BC240	0.31	BF195	0.10	OC72	0.35				
AF178	0.58	BC281	0.24	BF196	0.12	OC74	0.35				
AF180	0.68	BC262	0.20	BF197	0.12	OC75	0.35				
AF181	0.60	BC263B	0.20	BF199	0.14	OC76	0.35				
AF239	0.43	BC267	0.19	BF200	0.28	OC77	0.50				
BC107	0.12	BC301	0.26	BF216	0.12	OC78	0.13				
BC108	0.12	8C302	0.30	BF217	0.12	OC81	0.20				

TYPE	PRICE £	TYPE	PRICE £
SN76013N	1.48	SN76013ND	1.20
SN76023N	1.50	SN76023ND	1.20
SN76226DN	1.50	SN76227N	1.00
TBA341	0.97	TBA520Q	1.75
TBA520Q	1.75	TBA530Q	1.55
TBA540Q	1.75	TBA560CQ	1.90
TBA570Q	1.75	TBA800	1.12
TBA810	1.50	TBA920Q	2.00
TBA990Q	1.85	TCA270SQ	1.75
TCA270SA	1.50	TD13278	1.10

TYPE	PRICE £	TYPE	PRICE £
DY87	0.40	EF183	0.50
DY802	0.48	EF184	0.50
ECC82	0.42	EF180	0.60
EF80	0.40	PC86	0.70
PC86	0.70	PCB8	0.70
PC88	0.70	PCC89	0.55
PCC89	0.55	PCC189	0.60
PCF80	0.50	PCF80	0.50
PCF86	0.58	PCF86	0.58
PCF801	0.60	PCF802	0.70
PCF802	0.70	PCL82	0.60
PCL82	0.60	PCL84	0.55
PCL84	0.55	PCL86	0.60
PCL86	0.60	PCL805	0.60
PCL805	0.60	PLF200	0.70
PLF200	0.70	PL36	0.85
PL36	0.85	PL84	0.62
PL84	0.62	PL504	0.90
PL504	0.90	PL509	1.75
PL509	1.75	PY88	0.52
PY88	0.52	PY500A	1.00
PY500A	1.00	PY801	0.50
PY801	0.50		

E.H.T. TRAYS COLOUR		PRICE £
Pye 691	693	4.81
Decca (large screen)	CS2030/2232/2630/2632/2230/2233/2631	5.67
Philips G8	520/40/50	5.66
Philips G9		5.79
GEC C2110		5.97
GEC Hybrid CTV		5.57
Thorn 3000/3500		5.50
Thorn 8000		2.42
Thorn B500		5.23
Thorn 9000		6.10
GEC TVM 25		2.50
ITT/KB CVC 5/7/B/9		5.96
RRI (R8M) AB23		5.89
Bang & Olufsen 4/5000 Grundig 5010/5011/5012/6011/6012/7200/2052/2210/2252R		6.60
Autovox		6.60
Grundig 3000/3010		6.60
Saba 2705/3715		6.80
Telefunken 709/710/717/2000		6.80
Korting		6.80

P & P on all trays 70p



ELECTRONICS

22 Newland Street, Kettering, Northants.

Mail order, phone Kettering 83922.

All other enquiries Kettering 520910.

Shop open, Monday to Saturday 9.00 to 6.00.

Early closing Thursday 1.00 p.m.

Closed daily for lunch 1.00 to 2.00.

PROBABLY THE LARGEST ALL
ELECTRONICS STORE IN THE
UK WITH 1000's OF SQUARE
FEET DEVOTED TO THE BEST
IN CONSTRUCTIONAL
ELECTRONICS.

TELETEXT DECODER

TEXAS INSTRUMENTS XM-11

TELETEXT DECODER MODULE NOW AVAILABLE ON THE AMATEUR MARKET

Special arrangements with Texas now make this purpose designed decoder available to the non-professional user.

DAILY TELETEXT DEMONSTRATIONS NOW RUNNING IN OUR SHOWROOM.

DECODER FEATURES:

- Character rounding
- Alphanumerics
- Graphics
- Flashing display
- Update facility
- Date and Time on screen
- Boxed display
- Sound muting
- Seven colour display
- Upper and lower case characters

Full colour teletext decoding for less than the cost of discrete - Black and White only - designs.

£132.00 + 12½% VAT

Send SAE for further details. Installation advice and assistance freely available.

FULL COLOUR T.V. GAMES

NATIONAL'S FULL COLOUR TV GAME

CHIP SET SK 1122

Why settle for Black and White games or 'quasi colour' when the real thing is here now?

Six exciting colour video games on ordinary colour TV receivers as featured in this magazine.

Balls, paddles, scores, borders and background are each presented in their own vivid colour, with different combinations for each game; hit, border and scoring sounds are also generated during operation for greater realism.

Chip Set Complete.....£21.00 + 12½% VAT includes the three game chips, plus selected voltage regulator, plus all other semiconductors.

Send 30p for further details of the chips and colour TV game kit.

LOW COST CMOS

THE AWAITED BREAKTHROUGH IN CMOS PRICES IS HERE!

Brand new full spec devices fully guaranteed at prices you'll not believe. And an SAE brings details of even lower quantity mix prices and functional details of all the super MSI and LSI devices that are available.


CMOS data book available with pin outs, diagrams and circuits etc. Hundreds of pages for only £4.25

4000 .16	4044 .93	4440 13.93
4001 .16	4046 1.23	4450 3.22
4002 .16	4049 .39	4451 3.22
4006 1.00	4050 .39	4490 7.83
4007 .16	4051 .85	4501 .16
4008 .91	4052 .86	4502 .81
4011 .16	4053 .85	4503 .67
4012 .16	4066 .57	4507 .34
4013 .39	4068 .16	4508 2.27
4014 .94	4069 .16	4510 1.14
4015 .94	4070 .16	4511 1.42
4016 .43	4071 .16	4512 1.06
4017 .94	4072 .16	4516 1.14
4018 .94	4073 .16	4517 3.37
4020 1.04	4075 .16	4521 1.78
4021 .94	4076 1.21	4522 1.31
4022 .85	4077 .16	4526 1.11
4023 .16	4078 .16	4527 1.49
4024 .69	4081 .16	4528 .98
4025 .16	4082 .16	4529 1.08
4027 .46	4093 .57	4530 .64
4028 .84	4160 1.08	4536 3.30
4032 .94	4161 1.08	4541 1.27
4035 1.02	4162 1.08	4543 1.47
4038 .99	4163 1.08	4553 3.96
4040 1.03	4174 .98	4557 3.81
4042 .69	4175 .90	4566 1.32
4043 .93	4194 1.07	4583 .70
		4584 .56

MANOR SUPPLIES

COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

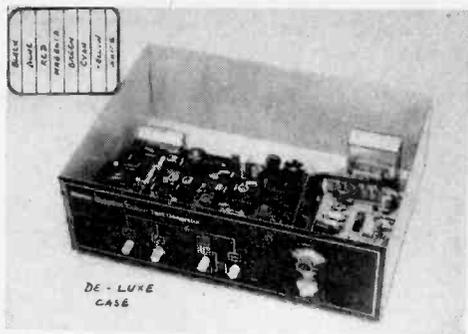

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars, all R-Y, B-Y and Lum. Combinations.
- ★ Plus cross hatch grey scale, peak white and black levels.
- ★ Push button controls, small, compact battery operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £35.00 + 8% VAT + £1.00 P/Packing.

CASES, ALUMINIUM £2.40, DE-LUXE £4.80, BATT. HOLDERS £1.40. ADD 8% VAT TO ALL PRICES!

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £25.00 + £1.00 p.p. CASE EXTRA £1.40. BATT. HOLDERS £1.40. ADD 8% VAT TO ALL PRICES.



- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed.

ALSO NOW AVAILABLE

MK4 DE LUXE (BATTERY) BUILT & TESTED £58.00 + 8% VAT + £1.20 P/Packing.

ALTERNATIVE MAINS SUPPLY KIT £5.78 + 8% VAT + 65p P/P. VHF MODULATOR (CH1 to 4) FOR OVERSEAS £3.50. INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.

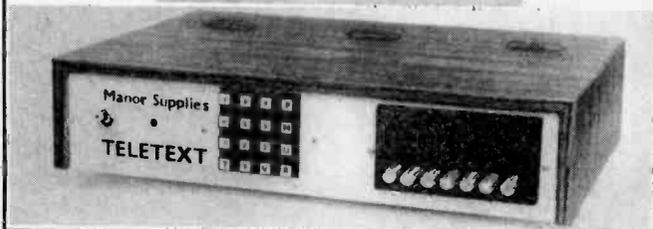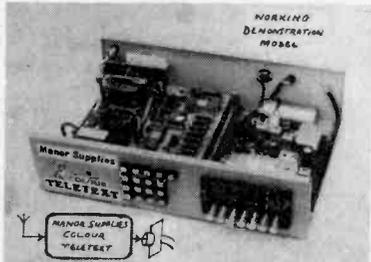MANOR SUPPLIES TELETEXT 77 KIT (incl TEXAS DECODER). Full facilities in colour. External unit. AE input to set. Write or call for further information. See working demonstration model!



COLOUR, UHF & TELEVISION SPARES

T.V. PORTABLE PROJECT LOPT, SCAN COILS, DRIVER £12.50. EHT RECTIFIER £1.20; VIS GAIN, VIS SELECT (TESTED) £3.80 p.p. 85p. MANY OTHER PARTS AVAILABLE.

TELETEXT 77, MANOR SUPPLIES NEW "EASY TO ASSEMBLE" KIT, INCL. TEXAS DECODER, AERIAL INPUT, COLOUR, MIXED T.V. PROGRAMME & TELETEXT, NEWSFLASH, UPDATE, AND MANY SPECIAL FEATURES NOT FOUND IN OTHER UNITS. DEMONSTRATION MODEL IN OPERATION AT 172 WEST END LANE, N.W.6. CALL OR WRITE FOR FURTHER INFORMATION.

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR, BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £11.00 + 45p. p.p.* (ALUM. CASE £2.00 p.p. 75p.*) COMPLETE TESTED UNITS, READY FOR USE (DE-LUXE CASE) £19.00 p.p. 90p.* ADDITIONAL GREY SCALE KIT £2.90 p.p. 30p.*

"NEW TYPE" UHF SIGNAL STRENGTH METER KIT £18.00 p.p. 90p. (VHF VERSION £18.80 p.p. 90p.)* CRT TESTER & REACTIVATOR PROJECT FULL KIT £18.80 p.p. £1.30.*

"TELEVISION" COLOUR SET PROJECT. MARK II DEMONSTRATION MODEL WITH LATEST IMPROVEMENTS. WORKING AND ON VIEW, SPARE PARTS STILL AVAILABLE.

"TELEVISION" PROJECT CROSS HATCH KIT £3.60 p.p. 20p.*

VIDEO PRE-AMP MOD. KIT (Oct. '75 Article) £1.20 p.p. 20p.

SPECIAL OFFER I.F. Panel, leading British maker, similar design to "Television" panel. Now in use as alternative inc. circuit and connection data, checked and tested on colour, full details, £19.80 p.p. 95p.

"FIVE in ONE" PANEL replaces Tuner IF, Decoder, RGB, and sound boards of original project. Tested on colour, with all data. £35.00 p.p. £1.20.

MAINS TRANSFORMER 280W for "T.V." Colour Set £11.50 p.p. £1.50. TRIPLER £6.00 p.p. 75p, ERIE FOCUS £2.20, p.p. 30p, NEW AUDIO UNIT £2.60 p.p. 35p.

STABILISER UNITS, "add on" kit for either 40V or 20V, £2.80 p.p. 35p.

GEC 2040 Surpl Panels, ex-rental, Decoder £5.00, T.B. £5.00 p.p. 90p.

BRC 3000 Surplus/Salv Panels, Decoder £7.50, Video £7.50 p.p. 90p.

DECCA Colour T.V. Thyristor Power Supply, HT, LT etc. £3.80 p.p. 95p.

BUSH CTV25 Power Supply Unit £3.20 p.p. £1.50.

PYE 697 Line T.B. P.C.B. for spares, £1.50 p.p. £1.00.

MULLARD AT1023/5 convergence yoke. New £2.50 p.p. 75p.

DLIE delay line. New 90p p.p. 40p. AT1025/06 blue lat. 75p p.p. 30p.

PHILIPS G6 single standard convergence panel, incl. 16 controls, switches etc., and circuits £3.75 p.p. 85p, or incl. yoke, £5.00. PHILIPS G8 panels for spares, decoder £2.50 p.p. 85p.

VARICAP, Mullard ELC1043 UHF tuner £4.50, ELC1043/05 £5.50, G.I. type (equiv. 1043/05) £3.50 p.p. 35p. Control units, 3PSN £1.25, 4PSN £1.80, 5PSN £2.20. Special offer 6PSN £1.00, 7PSN £1.80 p.p. 35p.

TAA 550 50p p.p. 15p.

VARICAP VHF PHILIPS £3.80, ELC1042 £4.80, p.p. 35p, ELC1042 on PYE P.C.B. £5.40, p.p. 65p.

VARICAP UHF/VHF ELC 2000S £12.50 p.p. 65p.

UHF/625 Tuners, many different types in stock. Lists available. UHF tuners transistd. incl. s/m drive, indicator £3.85; 6 posn. or 4 posn. push-button £4.20 p.p. 85p. Integrated tuners BUSH, PYE 40 6 posn. £4.50 p.p. £1.20. AE ISOL 30p p.p. 20p.

TRANSISTORISED 625 IF for T.V., sound tested (as featured in Practical Wireless, Nov. '75). £6.80 p.p. 65p.

PHILIPS 625 I.F. Panel incl. cct 50p p.p. 50p.

TURRET TUNERS, KB "Featherlight" VC11, Philips 170 series, GEC 2010 £2.50. GEC 2018, 2019, 2038, 2039 5 position £4.20 p.p. 85p.

TBA "Q" I.C.s. 480, 530, 540, £2.20, 550, 560C, 920 £3.20 p.p. 15p.

HELICAL POTS, 100K. 4 for £1.20 p.p. 20p.

BRC 1500 Mains Droppers, two for 90p p.p. 50p.

LINE OUTPUT TRANSFORMERS. New guar. p.p. 85p.

BUSH 105 to 186SS, etc. £6.80

DECCA DR1, 2, 3, 121/123, £6.40

20/24, MS1700, 2001, 2401 £6.40

DECCA MS2000, 2400 £5.80

FERG. HMV, MARCONI, £7.30

ULTRA 850, 900, 950 Mk. 1 £5.90

950II, 1400, 1500, 1590 £5.90

GEC 2000, 2047 series, etc. £6.40

INDESIT 20/24EGB £6.40

ITT/KB VC2 to 53, 100, 200, 300 £6.20

MURPHY 849 to 2417, etc. £6.80

PHILIPS 19TG121 to 19TG156 £4.80

PHILIPS 19TG170, 210, 300 £6.40

PYE 11U, 368, 169, 769 series £6.40

PYE 40, 67 series (36 to 55) £3.80

PAM, INVICTA, EKCO, £6.40

FERRANTI equivalents as above. £6.40

SOBELL 1000 series £6.40

STELLA 1043/2149 £6.40

SPECIAL OFFERS

BUSH TV53/86, 95/99 £1.00

EKCO 380 to 390 £1.00

EKCO 407/417 £1.00

FERR. 1084/1092 £1.00

FERG. 506 to 546 £1.00

GEC 448/452 £2.50

KB VCI, VCH (003) £2.80

P/SCOTT 733 to 738 £1.00

REG 10-6, 10-17 etc. £1.00

SOBELL 195/282/8 £2.50

MANY OTHERS STILL AVAILABLE

COLOUR LOPTS p.p. £1.00.

BUSH 182 to 1122 etc. £9.80

MURPHY Equivalents £7.60

DECCA "Bradford" £7.80

(state Model No. etc) £9.20

GEC 2028, 2040 £16.80

PYE 691, 693, 697 £8.80

THORN 8500 £8.80

THORN 850 Time Base Panel, Dual Standard 50p p.p. 80p.

MULLARD Scan Coils Type AT1030 for all standard mono 110° models, Philips, Stella, Pye, Ekco, Ferranti, Invicta £2.00 p.p. 85p.

PHILIPS G8 Tripler (1174) £6.00 p.p. 75p. Others available.

6-3V CRT Boost Transformers £2.90 p.p. 75p.; Auto type £1.80 p.p. 45p.

CALLERS WELCOME AT SHOP PREMISES

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE NOT NORMALLY ADVERTISED


MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

(Near W. Hampstead tube stn: 28, 59 159 Bus Routes) 01-794 8751

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

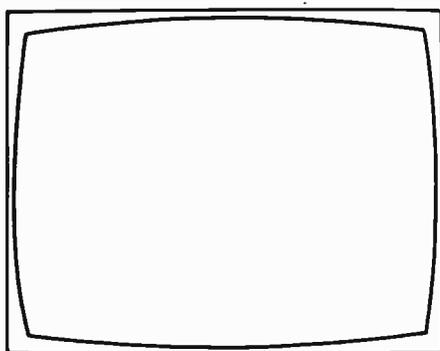PLEASE ADD 12½% VAT TO PRICES (EXCEPT * 8%)



TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTS MANAGER

Roy Smith

CLASSIFIED ADVERTS

Colin R. Brown

01-261 5762

Ten Years of Colour

During mid and late 1967 we had been running a series of articles entitled "Colour is Coming". With the December issue we proclaimed "Colour is Here!": December 2nd marked the official start of the BBC's colour service on BBC-2. That date is possibly arguable – as are so many historical "starts" and "firsts" when you try to pin them down – since there had been regular colour transmissions since Wimbledon in the summer of 1967, while the service after December 2nd was not a full colour one. Nevertheless, the BBC had been preparing the public for colour, and getting the trade used to what this would involve, and on December 2nd released its plans for extensive colour programming.

It was a proud moment, and those of us who had been watching the early colour transmissions were impressed by their quality. But most of us probably held our breath. Would the public be interested? Would it pay up? And more to the point for us, how on earth were we going to sort out the problems and faults that were going to come our way? A whole new dimension had been added to television and, it seemed, was going to double at least the problems of servicing.

The reputation that colour had established for itself in N. America didn't help. We laughed at the joke about the serviceman moving into the spare room when the colour set was installed in the lounge, but at the same time were deeply uneasy. We thumbed through the US magazines – particularly Jack Darr's famous Service Clinic in *Radio-Electronics* – and wondered how we were going to be able to make head or tail of the strange things that could apparently happen to the colour display. We then noted that PAL was more complex, with things like a PAL switch which could stop, Hanover blinds, and so on – and pushed the whole matter as far as possible to the backs of our minds while attending to the present crop of open-circuit dropper resistors.

Then we thought of all the heat generated by those early NTSC colour sets – there had been a few around in the UK for experimental purposes – bristling as they did with mighty valves, and of the e.h.t. voltage in the region where X-ray radiation starts to increase rapidly. There'd been reports of US colour sets having to be recalled by the manufacturers for safety modifications. . . .

But even if there have been many headaches, in the event things turned out to be a lot easier than anyone to start with dared hope. For one thing the PAL decoder is a very logical arrangement, and therefore ideally suited for making a few quick key checks. Then again most wrong colour faults turned out to be a simple enough matter – once you'd got used to the three primaries and how they add or should add up. Then, as with monochrome, the majority of faults turned out to be of the burnt dropper, no e.h.t., horizontal white line variety with which we were familiar enough. And the industry was rapidly moving over to transistors, with their cool operation. We had to get used to transistors at the same time that we got used to colour of course, and this didn't exactly help. Nor did dual-standard operation.

Two years later however saw the duplication of BBC-1 and ITV at u.h.f., in colour. Dual-standard colour sets were suddenly a thing of the past, and a new, simpler breed of sets started to appear. At the same time public interest began to perk up, and when the next consumer boom was unleashed in late 1972 colour suddenly became a feature of most people's living rooms.

This month we've departed slightly from our usual formula, in order to commemorate what in the event has turned out to be quite a success story. Looking back over those ten years – did they go that quickly because colour has in one way or another kept us so busy? – I think we are all entitled to a pat on the back. Early apprehensions proved unfounded. The public has been well served – to a considerable extent by service engineers who picked it all up as they went along! The broadcasting authorities have maintained a very high standard. Right then, are you all ready for what's in store for you next – teletext, video discs and the domestic TV as a home computer VDU?!

CORRECTION

There was an error in Fig. 1 on page 21 last month. There should be no electrical connection between S1a and S1b/S2 which are in parallel. The arrangement is shown correctly in Fig. 3.

FRONT COVER

The two sets shown contrast a typical 1967 colour receiver, a bulky Bush CTV25 dual-standard hybrid set with 25in. tube, and one of the very latest releases, a Bang and Olufsen Model 4402 which features a 26in. 20AX tube and ultrasonic remote control. The Bush CTV25 is still going strong after ten years' use!

Teletopics

HOME TV COMPUTER

Digital computer techniques have been gradually finding their way into the domestic TV set. First came digital methods of controlling the varicap tuner. Next came TV games, which use digital techniques with the TV set acting as a VDU (visual display unit). More recently we've had the advent of teletext, and the prospect of Viewdata. Along with these, setmakers are already producing elaborate remote control systems using digital techniques. The latest handheld remote control transmitters resemble the pocket calculator, with their rows of buttons to tell the TV set what to do – to change channels, display one of the several hundred teletext pages, turn the sound or brightness up/down and so on. A set with all this digital hardware in it is already half way to being a simple computer, so it's not surprising that someone's decided to go the whole way and convert it into being just that – in addition to its normal functions of course. Just to remind ourselves of what's involved, Fig. 1 shows the basic elements of a simple digital computing system. The control section enables us to tell the computer what we want it to do. What it can do for us is stored in the programme memory as a number of programmes. Once the control system has told the programme memory which programme is required, and the computing memory the numbers involved, the memories take over, using the counter to do the donkey work. Once the computation is complete, the computing memory feeds the result to the display unit.

The main element that's missing from our latest TV sets is the all important programme memory – the expensive part of a computer. The necessary step to fill this gap has now been announced by General Instrument Microelectronics Ltd. who, in conjunction with EMI Tape Ltd., have developed an inexpensive method of providing a computer data store. This consists of conventional audio tape cassettes and a standard audio cassette mechanism or deck. The technique, for which patents have been obtained, enables 1.6 million data bits to be stored on each side of a conventional thirty minute per side C60 audio cassette, and offers a one hundredfold increase in storage capacity in comparison with ROM microcircuit cartridges, at a quarter of the price. The technique also allows voice and digital data to be stored on the same cassette.

GIM and EMI see the widespread availability of

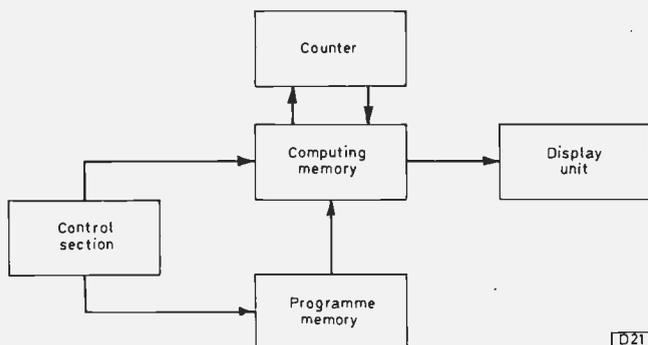


Fig. 1: Basic elements of a simple digital computing system. The counter and computing memory functions are commonly combined in a microprocessor i.c.

inexpensive hardware for the storage and playback of computer programmes as the key requirement in developing the domestic TV set into a computer system which can be used for such purposes as programmed learning, an information terminal and as a centre for TV games of a far more elaborate kind than those currently available. The two companies are collaborating in the development of programme material, with EMI taking responsibility for producing and distributing the tapes. The first products likely to become available – through normal tape/record shops – are ranges of TV games and educational programmes.

The possible range of programmes is virtually unlimited. By plugging a suitable cassette programme into a cassette deck contained in a TV games unit, the TV set can be transformed into a scientific or business calculator display in which every stage of calculation is displayed on the TV screen. Insert another cassette and the TV set can be transformed into a games terminal on which games of the complexity of chess can be played. Alternatively, language tapes could be made available combining on-screen text with the spoken word. Another big market is considered to be children's educational games, including arithmetic and spelling games in which the terminal's instant response to question and answer quizzes provides both entertainment and education.

The development of the programmable television terminal could lead to the growth of a major new software industry for educational and entertainment programmes. To avoid a proliferation of incompatible hardware, an industry standard for recording cassette data is required. The joint EMI/GIM technique for recording data on to cassettes, combined with the EMI patented watermark technique for protecting tape material copyrights, could become the standard.

An "electronic interface" which provides data retrieval and error checking, and which can be used with standard cassette recorder heads to play back the EMI/GIM record data, is to be marketed by GIM. It will form part of a complete programmable television terminal microcircuit chip set.

A key element in this system is the microprocessor, which incorporates in a single microcircuit package all the computing memory/counting functions of a complete computer. Costing one hundredth to one thousandth the price of a conventional computer, the microprocessor is already incorporated in GIM's decoder system for teletext and Viewdata.

GIM have in an advanced state of development a set of compatible MOS microcircuits for interfacing the television to its CP1600 microprocessor family. Modular in concept, these interface circuits can be used by the setmaker to offer a wide range of optional extras on the standard TV set, culminating in a complete home computer system. These interface circuits are also suitable for receiving the Viewdata and teletext services. Provision is made for remote armchair control, and for interfacing to the cassette mechanism for the playback of TV games and educational programmes.

It's important to emphasise that the system is still under development. We suspect that it will be some time before the chip set becomes available to anyone other than setmakers

and systems manufacturers, but as soon as it does . . . watch this space!

PHILIPS LAUNCH THE N1700

Philips have now officially launched their N1700 130-minute VCR in the UK and expect deliveries to start reaching dealers towards the end of the year. The machine, which can record for over two hours on a single VC60 cassette, will be the only VCR which Philips promote on the domestic market. The N1502 will continue in production alongside the N1700, but will be available only through audio/visual specialist distributors. Philips say that the longer playing time of the N1700 is much more suitable for general consumer use, since many TV programmes run for longer than an hour. Schools, training establishments, industry, etc. on the other hand do not require such long recordings. These users can save about £250 by purchasing the N1502. The price of the N1700 is likely to be around £750 including VAT. Philips state that there are around 35,000 VCRs in use in the UK at the present time, and they expect to more than double this figure in N1700 sales. The company has a 600 strong dealer network, but it's not planned to expand this in the near future. Philips have retained the modular method of construction, and initial tests have shown the recorder to be reliable. Servicing is said to be no more complicated than with the N1502.

Philips have also announced a monochrome camera for use with the N1700. The price of this is likely to be around £450.

RIC SUMMIT

Leading figures in the radio and television industry spoke at the recent Radio Industries Club convention called to discuss the depressed state of the industry. Thorn's group chairman and MD Sir Richard Cave suggested that Thorn would have sunk on TV alone: he commented that Thorn's results had not been satisfactory since the year ending March 1974, with the return on capital at less than the Bank Rate, and with their TV plant operating at only 60 per cent capacity – a figure which applies to the industry as a whole – since April 1975. TV setmakers have managed to remain in business only by being parts of larger industrial groups. Sir Richard said "we are selling very good equipment very much too cheaply: the UK customer is certainly getting a very good buy".

It seems that due to the highly competitive marketing in the UK the prices of domestic electronic equipment are markedly cheaper than in other parts of the world. The result may be good for the consumer, but makes the profitability of setmakers, component manufacturers and distributors such that their future is uncertain. Mullard's MD Jack Ackerman pointed out that the UK is currently importing over 90 per cent of the i.c.s used, 75 per cent of other semiconductor devices and 60 per cent of passive components. He called for increased investment, comparable to that in other advanced countries, if the UK's electronics industry is to survive.

Sir Richard spoke about the greatly improved reliability of the latest UK produced sets – a theme we've mentioned before in these pages. Interestingly, he mentioned that they would have to reduce the time at present required on inspecting and repairing faults, since this takes three times as long as their competitors.

US VCR SCENE

Some fifteen companies are planning to introduce new two- and four-hour VCRs on the US domestic market towards the end of the year. The number of basic systems now seems to

have been reduced to three. The Matsushita VHS system gets up to four hours' on to a $\frac{1}{2}$ in. tape by using the skip-field principle – since each stripe on the tape consists of a complete field, the bandwidth can be considerably reduced by recording only alternate fields and playing these back twice. This reduces the vertical resolution of course, but still provides acceptable quality. You get the best of both worlds with switchable machines that operate either normally or in the skip-field mode to give either two or four hours' playing time. The Matsushita (National Panasonic) VHS system has been adopted by RCA, Sylvania and Magnavox amongst others. The latter is intriguing, since Magnavox is owned by Philips.

Philips plan to launch their video disc in the US within a matter of weeks.

SINCLAIR INCREASE MICROVISION PRODUCTION

Sinclair have announced that as a result of the success of their multi-standard 2in. Microvision miniature portable TV receiver production is to be increased from 2,000 to 4,000 a month. The main market for the set is in the USA.

STATION OPENINGS

The following relay transmitters are now in operation:

Dolgellau (Gwynedd) BBC Wales channel 55, ITV (HTV Wales) channel 59, BBC-2 channel 62. Receiving aerial group C/D.

Ivybridge (Devon) BBC-1 channel 39, ITV (Westward Television) channel 42, BBC-2 channel 45. Receiving aerial group B.

Llwyn Onn (Gwynedd) BBC Wales channel 22, ITV (HTV Wales) channel 25, BBC-2 channel 28. Receiving aerial group A.

Machynlleth (Powys) BBC Wales channel 57, ITV (HTV Wales) channel 60, BBC-2 channel 63. Receiving aerial group C/D.

Sennybridge (Powys) BBC Wales channel 40, ITV (HTV Wales) channel 43, BBC-2 channel 46. Receiving aerial group B.

DECCA'S QUALITY CONTROL

Decca have invested more than half a million pounds in new test facilities and quality control at their Bridgnorth television factory. Every colour set now has a 24-hour soak test, which includes cycling on/off periods and mechanical bump tests, while passing along a 1,000ft. conveyor system. After repair, faulty sets receive a further 24-hour soak test. Decca comment that this test is equivalent to at least a week's use by the customer, and enables those irritating faults that occur early in a set's life to be avoided – especially as the components causing such troubles can be pinpointed and measures taken with suppliers.

TV GAMES: NO HAZARD

Videomaster have commented that there is no evidence to show that TV games can harm TV sets, pointing out that with modern vacuum techniques of tube manufacture there is no danger of static images being left on the screen. Their research suggests that a game would have to be played for 2,000 hours before any damage occurred. Videomaster now take extra precautions to ensure that their games cannot be displayed too brightly on the screen, and feel that as a result a Videomaster game could be played for 4,000 hours before having an adverse effect. It seems that such damage as has been experienced has been mainly due to the misuse of games: the advice given by Thorn (see *Teletopics*, October 1977) is worth noting.

TEN YEARS OF COLOUR

1: Choice of Colour System

Pat Hawker

ENGINEERING, industrial, administrative and political factors all became hopelessly intertwined in the long but eventually unsuccessful attempt to establish a single colour-encoding system for Europe. From 1962-67 the struggle oscillated wildly between the three main systems – the American NTSC, the French SECAM and the German PAL. There were also many variations within the SECAM and PAL systems, plus some outsiders such as NIIR, FAM, TSC, SEQUIN, LEP, and counter ideas such as the Post Office's pilot-tone reference system for NTSC, suggested by Dr N. W. J. Lewis in 1964.

In February 1965 the official UK delegation went to the CCIR Study Group XI meetings at Vienna firmly committed to support NTSC – yet before the end of that year it had swung over equally firmly to support PAL. Indeed for much of 1964 and 1965 the only *public* support in the UK for either PAL or SECAM came from a few technical journalists and the small engineering team at ABC, Teddington. At that period the British industry, through BREMA, was solidly behind NTSC. The BBC's then Director of Engineering, Sir Francis McLean, wrote in March 1965 that "the NTSC system is much to be preferred". The PMG made a statement in the House of Commons on February 3, 1965 in favour of NTSC. Yet today almost everyone in British broadcasting circles sincerely believes that the UK made the right choice in opting for PAL. Even in the United States, the birthplace of NTSC, one finds a belief that European television benefits from having chosen PAL or SECAM, though clearly many of the original problems in handling and, particularly, in tape recording NTSC have now been largely overcome.

Why did it take skilled engineers and administrators so long to come to what, with hindsight, may seem the obvious choice? And why are we still left with all three systems in general use?

History of Colour

Baird, in his disconcerting manner of rushing on to the next problem before solving the last one, demonstrated low-definition colour in the 1920s. Less well known was his later war-time demonstration of relatively good quality electronic colour, and his development of the two-gun and three-gun Telechrome picture tubes.

In the 1930s there had also been proposals by the Frenchman Georges Valensi that a compatible colour system, i.e. capable of being received also as black-and-white, might be based on the concept of luminance and chrominance.

But much of the early work on colour was based on sequential, non-compatible systems. CBS in America demonstrated a 343-line 120-field sequential colour system in 1940 and, after the war ended in 1945, developed a 525-line, 144-field sequential system which required a 12MHz channel – this system was even used operationally for a

time, during the course of 1951.

But in 1949 the FCC decided that for colour to be used generally it must be capable of fitting within the standard American 6MHz channel, and began a series of hearings. The industry formed the National Television System Committee, whose purpose was to assist the FCC and bring together the ideas then being pursued separately by different firms.

This period also saw the development by RCA, under a crash programme, of the Tricolour shadowmask display tube. This was an immensely important development, since it made obsolete the spinning colour discs used in sequential systems and the then possible alternatives – the costly projection systems based on Schmidt optics, or the bulky three orthogonally mounted cathode-ray tubes viewed through diachroic mirrors. The shadowmask tube drew on the ideas of W. Flechsig, Dr A. N. Goldsmith, A. C. Schroeder and others. The key problem – how to line-up accurately several hundred thousand tiny holes with an equal number of phosphor-dot triplets – was solved by Harold Law with his "lighthouse" technique, using light to simulate the electron beams. In 1950 the first shadowmask tube was demonstrated.

During 1950-52 NTSC emerged as a "system", drawing freely on the work of several firms and including the colour-dot sequential and other ideas of RCA. One of the ideas that was considered but not adopted was "colour phase alternation" (CPA), which was proposed by B. D. Loughlin of Hazeltine. It was later the genius of Dr Walter Bruch to join the potential advantages of CPA with the electrical memory introduced by Henri de France for SECAM in order to form the basis of PAL – but we are running ahead of our story.

Although it is often said that a camel is a horse designed by a committee, the NTSC standard that emerged from all this was undoubtedly a work of genius. It solved each of the problems it had been set: a fully-compatible system, in the standard channel bandwidth; good reverse-compatibility (display of black-and-white pictures on a colour set); excellent potential colour fidelity with an absence of crawling patterns (other than the degree of cross-colour inherent in any system using frequency interleaving), and virtual absence of colour dots on black-and-white displays.

The FCC authorised NTSC colour transmissions from January 1, 1954, and NBC (the broadcasting company affiliated with RCA) was particularly prominent in promoting the system.

But the growth of colour set sales was slow. Early sets were expensive and unreliable; colour cameras were bulky, required intense light, and were prone to drift. And the whole system was soon found to be susceptible to differential phase and differential amplitude problems, particularly when networked across the country. The user needed to compensate for phase variations by means of a hue control, and it was soon clear that many viewers found it difficult to adjust both the saturation and hue controls.

TTIs by TEXAS		C-MOS ICs		OP AMPS		Linear ICs		TBA651 275p		8FX86/7/8 30p		2N3053 22p		VOLTAGE REGULATORS (Plastic) Fixed	
7400 16p	74105 60p	4000 21p	1458 75p	10A800 100p	8FX60 22p	2N3054 85p	187K 25p	8FX50 22p	2N3055 85p	1 Amp +ve	1 Amp -ve	5V 7805 130p	5V 7905 200p	12V 7812 130p	12V 7912 200p
74HD0 30p	74107 36p	4001 21p	301A 40p	3130 100p	8FY5 22p	2N3056 85p	AC187K 25p	8FY6 22p	2N3057 85p	2N3702/3 14p	2N3704/5 14p	15V 7815 130p	15V 7915 200p	18V 7818 150p	18V 7918 200p
74L5DD 32p	74110 70p	4002 21p	3140 105p	3140 105p	8FY2 22p	2N3058 85p	AC126/7 20p	8FY3 22p	2N3059 85p	2N3706/7 14p	2N3708/9 14p	24V 7824 150p	24V 7924 200p		
74SD0 48p	74111 80p	4007 22p	3900 70p	3900 70p	8RY39 45p	2N3060 85p	AC126/8 20p	8RY40 45p	2N3061 85p	2N3710/11 14p	2N3712/13 14p				
7401 18p	74112 80p	4009 67p	LM324N 130p	LM339N 225p	8S19/20 20p	2N3062 85p	AC141/2 20p	8S19/20 20p	2N3063 85p	2N3714/15 14p	2N3716/17 14p				
7402 18p	74113 80p	4011 21p	709 40p	709 40p	8S19/20 20p	2N3064 85p	AC176 20p	8S19/20 20p	2N3065 85p	2N3718/19 14p	2N3720/21 14p				
7403 18p	74114 80p	4012 21p	747 70p	747 70p	8S19/20 20p	2N3066 85p	AC187/8 20p	8S19/20 20p	2N3067 85p	2N3722/23 14p	2N3724/25 14p				
7404 24p	74115 80p	4013 21p	748 40p	748 40p	8S19/20 20p	2N3068 85p	AC187K 25p	8S19/20 20p	2N3069 85p	2N3726/27 14p	2N3728/29 14p				
74H04 40p	74116 220p	4007 22p	748 40p	748 40p	8S19/20 20p	2N3070 85p	AC187K 25p	8S19/20 20p	2N3071 85p	2N3730/31 14p	2N3732/33 14p				
7405 25p	74117 80p	4009 67p	748 40p	748 40p	8S19/20 20p	2N3072 85p	AC187K 25p	8S19/20 20p	2N3073 85p	2N3734/35 14p	2N3736/37 14p				
7406 45p	74118 90p	4011 21p	748 40p	748 40p	8S19/20 20p	2N3074 85p	AC187K 25p	8S19/20 20p	2N3075 85p	2N3738/39 14p	2N3740/41 14p				
7407 45p	74119 80p	4012 21p	748 40p	748 40p	8S19/20 20p	2N3076 85p	AC187K 25p	8S19/20 20p	2N3077 85p	2N3742/43 14p	2N3744/45 14p				
7408 25p	74120 95p	4013 21p	748 40p	748 40p	8S19/20 20p	2N3078 85p	AC187K 25p	8S19/20 20p	2N3079 85p	2N3746/47 14p	2N3748/49 14p				
7409 27p	74121 32p	4014 21p	748 40p	748 40p	8S19/20 20p	2N3080 85p	AC187K 25p	8S19/20 20p	2N3081 85p	2N3750/51 14p	2N3752/53 14p				
7410 18p	74122 53p	4015 120p	748 40p	748 40p	8S19/20 20p	2N3082 85p	AC187K 25p	8S19/20 20p	2N3083 85p	2N3754/55 14p	2N3756/57 14p				
74H10 30p	74123 73p	4016 54p	748 40p	748 40p	8S19/20 20p	2N3084 85p	AC187K 25p	8S19/20 20p	2N3085 85p	2N3758/59 14p	2N3760/61 14p				
7411 28p	74124 76p	4017 110p	748 40p	748 40p	8S19/20 20p	2N3086 85p	AC187K 25p	8S19/20 20p	2N3087 85p	2N3762/63 14p	2N3764/65 14p				
7412 28p	74125 70p	4018 120p	748 40p	748 40p	8S19/20 20p	2N3088 85p	AC187K 25p	8S19/20 20p	2N3089 85p	2N3766/67 14p	2N3768/69 14p				
7413 28p	74126 76p	4019 54p	748 40p	748 40p	8S19/20 20p	2N3090 85p	AC187K 25p	8S19/20 20p	2N3091 85p	2N3770/71 14p	2N3772/73 14p				
7414 96p	74127 81p	4020 95p	748 40p	748 40p	8S19/20 20p	2N3092 85p	AC187K 25p	8S19/20 20p	2N3093 85p	2N3774/75 14p	2N3776/77 14p				
7416 35p	74128 90p	4021 100p	748 40p	748 40p	8S19/20 20p	2N3094 85p	AC187K 25p	8S19/20 20p	2N3095 85p	2N3778/79 14p	2N3780/81 14p				
7417 40p	74129 81p	4022 100p	748 40p	748 40p	8S19/20 20p	2N3096 85p	AC187K 25p	8S19/20 20p	2N3097 85p	2N3782/83 14p	2N3784/85 14p				
7420 18p	74130 81p	4023 21p	748 40p	748 40p	8S19/20 20p	2N3098 85p	AC187K 25p	8S19/20 20p	2N3099 85p	2N3786/87 14p	2N3788/89 14p				
7421 43p	74131 81p	4024 75p	748 40p	748 40p	8S19/20 20p	2N3100 85p	AC187K 25p	8S19/20 20p	2N3101 85p	2N3790/91 14p	2N3792/93 14p				
7422 27p	74132 81p	4025 21p	748 40p	748 40p	8S19/20 20p	2N3102 85p	AC187K 25p	8S19/20 20p	2N3103 85p	2N3794/95 14p	2N3796/97 14p				
7423 36p	74133 81p	4026 220p	748 40p	748 40p	8S19/20 20p	2N3104 85p	AC187K 25p	8S19/20 20p	2N3105 85p	2N3798/99 14p	2N3800/01 14p				
7425 33p	74134 81p	4027 81p	748 40p	748 40p	8S19/20 20p	2N3106 85p	AC187K 25p	8S19/20 20p	2N3107 85p	2N3802/03 14p	2N3804/05 14p				
7427 40p	74135 81p	4028 152p	748 40p	748 40p	8S19/20 20p	2N3108 85p	AC187K 25p	8S19/20 20p	2N3109 85p	2N3806/07 14p	2N3808/09 14p				
7430 18p	74136 81p	4029 120p	748 40p	748 40p	8S19/20 20p	2N3110 85p	AC187K 25p	8S19/20 20p	2N3111 85p	2N3810/11 14p	2N3812/13 14p				
7432 34p	74137 81p	4030 59p	748 40p	748 40p	8S19/20 20p	2N3112 85p	AC187K 25p	8S19/20 20p	2N3113 85p	2N3814/15 14p	2N3816/17 14p				
7437 37p	74138 81p	4031 59p	748 40p	748 40p	8S19/20 20p	2N3114 85p	AC187K 25p	8S19/20 20p	2N3115 85p	2N3818/19 14p	2N3820/21 14p				
7438 37p	74139 81p	4032 21p	748 40p	748 40p	8S19/20 20p	2N3116 85p	AC187K 25p	8S19/20 20p	2N3117 85p	2N3822/23 14p	2N3824/25 14p				
7440 18p	74140 81p	4033 59p	748 40p	748 40p	8S19/20 20p	2N3118 85p	AC187K 25p	8S19/20 20p	2N3119 85p	2N3826/27 14p	2N3828/29 14p				
7441 85p	74141 85p	4034 59p	748 40p	748 40p	8S19/20 20p	2N3120 85p	AC187K 25p	8S19/20 20p	2N3121 85p	2N3830/31 14p	2N3832/33 14p				
7442 75p	74142 85p	4035 59p	748 40p	748 40p	8S19/20 20p	2N3122 85p	AC187K 25p	8S19/20 20p	2N3123 85p	2N3834/35 14p	2N3836/37 14p				
7443 130p	74143 85p	4036 59p	748 40p	748 40p	8S19/20 20p	2N3124 85p	AC187K 25p	8S19/20 20p	2N3125 85p	2N3838/39 14p	2N3840/41 14p				
7444 130p	74144 85p	4037 29p	748 40p	748 40p	8S19/20 20p	2N3126 85p	AC187K 25p	8S19/20 20p	2N3127 85p	2N3842/43 14p	2N3844/45 14p				
7445 108p	74145 90p	4038 29p	748 40p	748 40p	8S19/20 20p	2N3128 85p	AC187K 25p	8S19/20 20p	2N3129 85p	2N3846/47 14p	2N3848/49 14p				
7447 90p	74146 120p	4039 95p	748 40p	748 40p	8S19/20 20p	2N3130 85p	AC187K 25p	8S19/20 20p	2N3131 85p	2N3850/51 14p	2N3852/53 14p				
7448 90p	74147 275p	4040 100p	748 40p	748 40p	8S19/20 20p	2N3132 85p	AC187K 25p	8S19/20 20p	2N3133 85p	2N3854/55 14p	2N3856/57 14p				
7450 18p	74148 173p	4041 110p	748 40p	748 40p	8S19/20 20p	2N3134 85p	AC187K 25p	8S19/20 20p	2N3135 85p	2N3858/59 14p	2N3860/61 14p				
7451 18p	74149 135p	4042 100p	748 40p	748 40p	8S19/20 20p	2N3136 85p	AC187K 25p	8S19/20 20p	2N3137 85p	2N3862/63 14p	2N3864/65 14p				
7453 18p	74150 135p	4043 100p	748 40p	748 40p	8S19/20 20p	2N3138 85p	AC187K 25p	8S19/20 20p	2N3139 85p	2N3866/67 14p	2N3868/69 14p				
7454 18p	74151 77p	4044 100p	748 40p	748 40p	8S19/20 20p	2N3140 85p	AC187K 25p	8S19/20 20p	2N3141 85p	2N3870/71 14p	2N3872/73 14p				
7460 20p	74152 77p	4045 100p	748 40p	748 40p	8S19/20 20p	2N3142 85p	AC187K 25p	8S19/20 20p	2N3143 85p	2N3874/75 14p	2N3876/77 14p				
7470 32p	74153 92p	4046 150p	748 40p	748 40p	8S19/20 20p	2N3144 85p	AC187K 25p	8S19/20 20p	2N3145 85p	2N3878/79 14p	2N3880/81 14p				
7472 32p	74154 164p	4047 110p	748 40p	748 40p	8S19/20 20p	2N3146 85p	AC187K 25p	8S19/20 20p	2N3147 85p	2N3882/83 14p	2N3884/85 14p				
7473 36p	74155 97p	4048 68p	748 40p	748 40p	8S19/20 20p	2N3148 85p	AC187K 25p	8S19/20 20p	2N3149 85p	2N3886/87 14p	2N3888/89 14p				
7474 37p	74156 97p	4049 110p	748 40p	748 40p	8S19/20 20p	2N3150 85p	AC187K 25p	8S19/20 20p	2N3151 85p	2N3890/91 14p	2N3892/93 14p				
7475 48p	74157 96p	4050 54p	748 40p	748 40p	8S19/20 20p	2N3152 85p	AC187K 25p	8S19/20 20p	2N3153 85p	2N3894/95 14p	2N3896/97 14p				
7476 37p	74158 120p	4051 54p	748 40p	748 40p	8S19/20 20p	2N3154 85p	AC187K 25p	8S19/20 20p	2N3155 85p	2N3898/99 14p	2N3900/01 14p				
7480 54p	74159 135p	4052 54p	748 40p	748 40p	8S19/20 20p	2N3156 85p	AC187K 25p	8S19/20 20p	2N3157 85p	2N3902/03 14p	2N3904/05 14p				
7481 108p	74160 120p	4053 54p	748 40p	748 40p	8S19/20 20p	2N3158 85p	AC187K 25p	8S19/20 20p	2N3159 85p	2N3906/07 14p	2N3908/09 14p				
7482 85p	74161 120p	4054 54p	748 40p	748 40p	8S19/20 20p	2N3160 85p	AC187K 25p	8S19/20 20p	2N3161 85p	2N3910/11 14p	2N3912/13 14p				
7483 96p	74162 120p	4055 120p	748 40p	748 40p	8S19/20 20p	2N3162 85p	AC187K 25p	8S19/20 20p	2N3163 85p	2N3914/15 14p	2N3916/17 14p				
7484 103p	74163 120p	4056 145p	748 40p	748 40p	8S19/20 20p	2N3164 85p	AC187K 25p	8S19/20 20p	2N3165 85p	2N3918/19 14p	2N3920/21 14p				
7485															

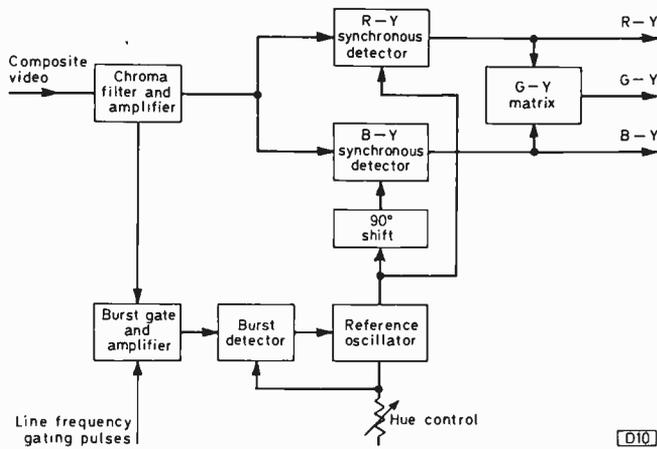


Fig. 1: Basic NTSC decoder. Detection takes place on the tips of the reference signal. Since the phase of the signal determines the colour, if the signal phase shifts spuriously incorrect colours are detected. The hue control enables the reference signal to be shifted to compensate.

For the broadcaster a new and unexpected problem soon arose. In 1956 Ampex started the television world with the first successful videotape recorders. But the early VTR machines introduced linear phase errors which made their performance on colour at best marginal (even when the recording heads were sent with the tapes for playback). If NTSC had been drawn up *after* the development of the VTR, it is highly likely that more attention would have been given to the idea of phase alternation.

A combination of factors – high receiver price, limited amount of colour programming, variable colour fidelity, VTR problems etc. – kept demand for colour sets in the United States low. At one period only NBC were regularly transmitting colour. It took almost ten years for colour sales to reach one million a year (1963, with 1.4 million, was the turning point). Europe was in no hurry to start colour under those conditions.

Some European engineers felt that the slow start to colour in the USA was influenced by the unnatural hues seen due to the susceptibility of NTSC to small phase errors. There were two ways out of this problem: to develop better studio equipment and tighten the specification of distribution links; or to develop a new system less susceptible to phase errors.

Start of SECAM

Henri de France proposed a system which he called SECAM (“sequential and memory”). This encoded the colour without using quadrature modulation for the two colour-difference signals: instead, he proposed that at any given moment only one chroma signal would be transmitted, and introduced the idea of storing the signal temporarily by means of a delay line. This would then provide him with both signals simultaneously, but with reduced vertical colour resolution, a matter of little practical importance. He originally proposed to carry the chroma information on an amplitude-modulated subcarrier, but the system was soon redesigned for frequency-modulation of the subcarrier. In both systems, unlike NTSC, the subcarrier is continuously present (NTSC uses suppressed-carrier quadrature amplitude modulation for the two colour-difference signals.) Henri de France’s ideas were adopted by a French company, CFT, which was set up by two large French firms, the electronics company CSF and the large glass manufacturer Saint-Gobain.

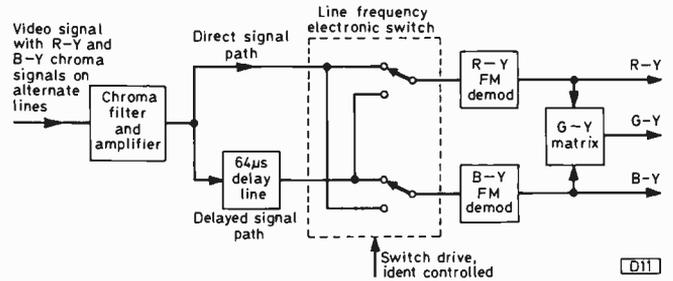


Fig. 2: Simplified SECAM decoder. The R-Y and B-Y colour-difference signals are transmitted on alternate lines. The combination of the delay line and the switch enables the lines to be repeated, the demodulators detecting alternate lines twice. The reduced vertical colour resolution is of little practical significance, the great advantage of the system being that detection is not phase sensitive. The switching has to be synchronised, so that the correct signals are fed to the two demodulators, and for this purpose positive- and negative-going sawtooth signals are transmitted during the field flyback blanking interval to provide the necessary identification – because of the odd number of lines per picture, the first line of each alternately carries R-Y and B-Y chrominance signals.

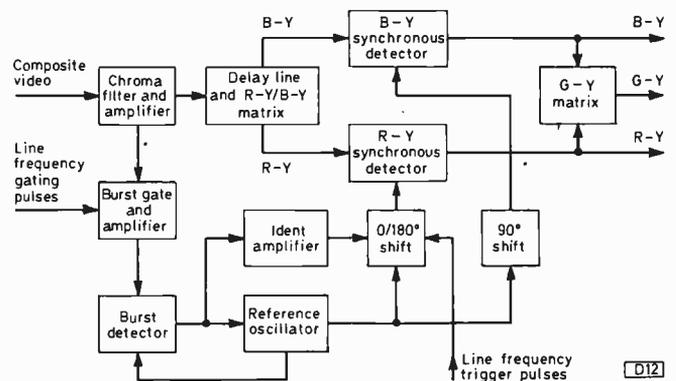


Fig. 3: Basic PAL-D decoder. The use of a delay line and a matrix circuit enables the two transmitted colour-difference signals to be separated prior to detection. To make this arrangement work, the polarity of one of the colour-difference signals (in practice R-Y) has to be reversed, i.e. its phase shifted by 180°, on alternate lines. This means that a 0/180° phase shift switch is required in the decoder, with ident to synchronise its operation with the switching at the transmitter. By processing the signals in the delay line/matrix circuit, the effect of spurious phase shifts is converted into a slight loss of saturation.

Henri Peyroles of CFT became extremely active in propagating the ideas of SECAM, and his engineering team included the redoubtable Pierre Cassagne. It was also clear that behind CFT stood the active support of President De Gaulle, and indeed a Government minister was for a time directly concerned with promoting SECAM.

Birth of PAL

In Germany Dr Walter Bruch of Telefunken, who had been concerned with television for many years, shared the view of Henri de France that colour was being held back by the phase problems of NTSC. For a time he worked on SECAM, with its electronic memory, but he was equally attracted by the quadrature modulation suppressed-carrier techniques of NTSC. In 1962 he married the two, and so was born PAL (phase alternation line), using the phase alternation ideas of CPA, the basic techniques of NTSC, and also the delay-line memory of SECAM.

But the other systems had both had some years in which to sort out their problems. PAL came just in time to be

adopted as a serious contender by the EBU, but its parameters had virtually to be optimised during the investigation – giving rise to the tag “Pray and Learn”. SECAM also continued to offset problems as they were uncovered, by changing its basic parameters (SECAM I, II, III and IV). It became known as the “Supreme Effort Contre les Americains”! NTSC in turn was dubbed “Never Twice the Same Colour”.

The Battle

Looking back through a pile of fading press clippings, I find that the battle between the systems began in earnest at the beginning of 1963. It reached London that summer during a series of demonstrations, and became a war of attrition throughout 1964 when CFT began production of a few SECAM receivers. The Post Office rescued NTSC from its dependence on high-grade microwave links by devising a pilot-tone reference system, and the controversy rose to fever pitch at Vienna in 1965. It finally collapsed in failure to agree at Oslo in April 1966.

Rome and Moscow were also battlefields, and the PAL system was demonstrated to the press for the first time only in February 1965, in Berlin. This led me to forecast then that “PAL could be the compromise system for Europe”. The EBU ad hoc Committee published massive reports in October 1963 and February 1965, based on extremely intensive investigations by a whole series of groups. Both reports were crammed full of engineering facts.

But nobody was prepared collectively to pick a single system as “the best”: each had advantages and disadvantages. SECAM was rugged and easiest to record and distribute over long distances and could use steel delay lines. NTSC was tried and tested and showed every promise that with better cameras and VTRs it would give good quality. PAL came in the middle, with more pros than cons but still posing the problem – could precision glass delay lines be made at low cost in mass production? At the time they were high cost, specialised radar components. Telefunken guaranteed to supply them to West German manufacturers for less than DM20, but what about the rest of Europe?

The BBC co-operated with Ampex in improving colour video recording, and this led to the development of high-band recorders that gave good performance on all three systems (indeed the 8-field sequence adopted for PAL has tended to make this the most difficult system to record). They also presented a rather questionable demonstration that highlighted SECAM's vulnerability to “silver fish” beyond the service area, due to the f.m. threshold.

The ABC team, on behalf of ITV, developed – under Howard Steele – methods of transcoding between systems, and also improved the “mixing” of SECAM signals in the studio. ITV in fact became the only group to transmit NTSC, PAL and SECAM in 405-lines.

BREMA produced a report to show that the extra “hue” control on a NTSC receiver would not often require adjustment by the user. By a tactical error they issued only part of the report to the press, and that part appeared to prove that NTSC *did* involve user problems!

Philips in Eindhoven – with their own colour systems out of the running – quietly went on developing the Plumbicon camera tube. This arguably played an even greater part than any encoding system in improving the standard of colour.

RCA, misjudging the European mood, issued a series of highly partisan booklets in support of NTSC. Several British engineers were dissuaded from speaking in Moscow about SECAM!

Some firms were by now convinced that colour was unlikely to appeal to a mass audience until the prices came down, and were quite content to stand by and watch the infighting. Several ceased development work on colour, though Bush was an exception.

Some continental firms were so uncertain which way the fight would go that, for example, I was shown excellent SECAM receivers by one international firm in France only on the explicit understanding that I would not disclose which firm I was writing about!

The Chairman of the EBU ad hoc Committee, the late Dr. Richard Theile, due to report on the work of the Committee at the 1965 Montreux Symposium, withdrew his paper at the last moment.

At Oslo in 1966 it was even thought that one way out of the impasse was, instead of changing the parameters, simply to change the name. PAL almost became SEQAM, or alternatively “The Oslo system”. There was a move to insist that all countries should look at SECAM IV/NIIR while shelving further work on other systems.

The administrators and telecommunications people at Oslo fell out bitterly with the broadcasters, whom they dismissed as a troublesome clique, prone to “political rigging and manoeuvring”.

In the end it was agreed that the parameters of the three colour systems should be registered by the CCIR, but that individual countries should make up their own minds. So failed the attempt to choose a colour system for Europe. But it left the UK free to adopt PAL, and there are few regrets. Somehow, almost by accident one feels, we chose the right system.

In the UK however that was not the end of the controversy. ITV wanted a chance to start colour as quickly as possible – and that meant 405-line colour on v.h.f. Why and how they lost that struggle is another story.

In the end the BBC was authorised to begin its colour service on BBC-2 by the end of 1967. On July 27, 1967 the PMG announced that ITV could begin 625-line u.h.f. colour “early in 1970”. In fact colour on BBC-1 and ITV began on November 15, 1969.

Table 1: Some system comparisons

	NTSC	SECAM	PAL
Tolerance to differential phase errors	±12°	±40°	±40°
Tolerance to differential gain errors	30%	65%	30%

PAL improvements on NTSC

Horizontal resolution and vertical edge effects when transmitted on European “G” standard; tolerance to distortions of upper sideband of chroma signal; sensitivity to multi-path echoes.

PAL disadvantages to NTSC

Basic receiver cost; compatibility on black-on-white; adaptability to single-gun tube; experience.

Loosely based on the EBU ad hoc Committee reports of 1963-65.

Subcarrier frequencies

625-line PAL	4.43361875MHz
625-line NTSC	4.4296875MHz
625-line SECAM	4.4375MHz (f.m. ± 770 kHz)
525-line NTSC	3.579545MHz
405-line NTSC	2.6578125MHz

TEN YEARS OF COLOUR

2: Servicing and Receiver Developments

E. Trundle

IT seems incredible that regular colour transmissions in the UK have been going on for ten years now – that ten years has flown! It was on December 2nd 1967 that the regular BBC-2 colour service started – heralded by lots of little kangaroos. This was not the first time that colour had been seen by the UK public, as for several months test programmes had been transmitted while for some years previously most setmakers had mounted displays at the annual Radio Show (in those far off days when it was at Earl's Court, and the public was allowed in as well!). I remember a row of darkened booths, each one painted matt black and containing a 21in. circular RCA shadowmask tube displaying locally generated demonstration films with varying degrees of fidelity. Purity and convergence left a bit to be desired in some cases, but it was nevertheless very impressive. The BBC and ITA (as it then was) had already been active in the colour field for some time before 1967, with experimental 405-line colour using NTSC and other systems.

First Experiences

My first introduction to colour was when a huge 25in. dual-standard colour console receiver was delivered to the workshop for setting up. It was a Philips G6, bristling with valves and presets, and what on earth was that relay on the c.r.t. base for? We all had a go at purity adjustments, and each engineer spent about a day on the convergence, after which it was almost as good as when it was unpacked.

I left the employ of that firm shortly afterwards, but not before being taken to one side by Jim. Now Jim had had dealings with projection equipment years before, and solemnly told me of the evil effects of X-ray radiation upon the human frame. Certain extremities of a confidential nature, said Jim, were likely to drop off under the influence of X-rays. . . . To this day I have been hesitant to approach GY501s and especially PD500s closely, but all is well, Jim, as I write this.

I then secured a post seven doors down the road as one-man-band in the TV service department of the local branch of a well-known divi-giving national store. My arrival coincided with that of their first colour set, a dual-standard GEC model with a vast cabinet, a 19in. screen and a colour beacon to proclaim to the world that its purpose in life was being fulfilled. It was humped up three flights of stairs, through the furniture and accounts departments to my lair at the top of the building (why are TV workshops always upstairs?) where it was pored over and played with before being borne in triumph to the showroom, there to be degaussed and meticulously pointed due East in glorious demonstration.

Complete Colour Capability?

As we started to rent and sell colour receivers, so my

worries increased. Like most of the trade at that time, I was grossly under equipped, boasting only a Bemix crosshatch generator in addition to monochrome TV servicing gear, and living in fear of the under-manager's regular refrain: "Mr. Wigg's set's gorn again!" Large areas of the colour set were still shrouded in mystery – how I wished that the Complete Colour Capability of my Mullard PL802s and PL509s extended to the man who fitted them! Many readers will remember, perhaps with some affection, the demonstration films shown on BBC-2 in the early days. Our favourite was the colour installation cartoon film. How confidently did the little technician degauss and converge that TV! How readily did the pert little housewife accept the shortcomings of her indoor aerial! I could swear that the technician winked as he pulled closed the curtains preparatory to setting up the c.r.t.

For two years or so, colour sets were quite thin on the ground. It seems that they were the province of the better-off, with the vast majority of people being interested, but waiting for the price to come down (!). It never did in terms of pounds, but in real terms colour TV is getting cheaper all the time: what other commodity can claim to have held its price virtually steady for almost ten years? As the trade was still feeling its way on the servicing side, in retrospect the gradual introduction of colour was a good thing for both setmaker and dealer.

The Early Sets

On the technical side there was much of interest. Mullard had published, quite early on, a sort of Bible for setmakers, with suggested circuits using their hardware and a very good basic design for a dual-standard colour receiver. Many setmakers adopted the Mullard approach, and this accounts for the similarity between early models from such makers as Decca, Rank, Pye, and GEC. The latter firm was amongst the first to employ an e.h.t. tripler instead of a thermionic rectifier, in an otherwise conventional receiver. Thorn were the great innovators in the early days: they never built a hybrid colour receiver at all, but plunged boldly into solid-state technology from the word go. An example of the 2000 series dual-standard chassis occupies a well deserved place in the National Science Museum as the world's first production all transistor colour receiver. Looking at a 2000 now, it seems very involved and complex in comparison with the 8500 chassis from the same stable.

Colour Adaptor

In the first year or two much thought was given to the possibility of getting colour out of monochrome sets. There was a sort of colour filter marketed very cheaply. It adhered to the front of the c.r.t. screen, was divided into three horizontal sections, with the lower band red-brown, the

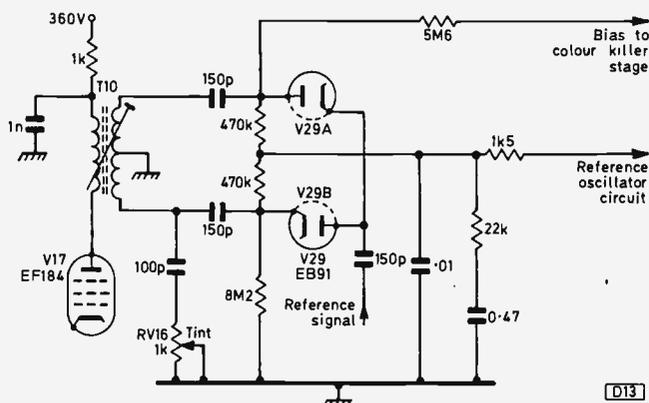


Fig. 1: The control you never had to use. RV16 is the tint (hue) control in this circuit from the Ekco Model CT100, an NTSC, v.h.f./u.h.f. 21in. set. V29 is the burst detector – very similar to the circuit commonly used in subsequent production chassis, except for the use of a valve. RV16 altered the tuning of the burst detector transformer T10, giving a phase shift of approximately 90°.

middle band green and the upper one blue – not very inspiring surperimposed on Crossroads or the newsreader! A more serious attempt was made by a firm which marketed an apparatus consisting of a decoder and TRITCH (TRIPLE sequential swITCH). This operated a system of tinted translucent perspex shutters in front of the c.r.t. screen, with subliminal lighting from miniature bulbs hidden behind the frame of the front shutter. RGB signals were sequentially switched to the c.r.t. cathode in synchronism with the gyrations of the shutter gear. This equipment foundered on the twin rocks of mechanical problems and colour flicker – notwithstanding the subliminal lighting.

An Experiment

Inspired by contemporary articles in *Practical Television* I took to my garden shed, wherein lived a vidicon camera. This was fitted with a three-section rotating colour wheel in front of the lens, the wheel having three magnets to excite an adjacent tape head to produce trigger pulses. Said pulses were processed in the inevitable tritch, which culminated in three triodes arranged to switch in sequentially the first anodes of a recently acquired Pye dual-standard colour set.

The camera output was fed via a modulator to the Pye set's aerial input socket, and this very hairy equipment fired up. It worked, although there was only one chance in three of getting the right colours at switch-on, and results were much marred by colour flicker and the lag of the vidicon camera tube. These experiments were abruptly terminated one day when the colour wheel came adrift while rotating at full pelt, and stuck quivering in the wooden wall of the shed. The inventor/operator staggered white-faced from the shed – the colour wheel had almost succeeded where the X-rays had failed!

Colour on all Channels

With experience came growing confidence, and this was just as well, because November 1969 saw the simultaneous introduction of colour on BBC-1 and most of the ITV network. As anticipated, this led to greatly increased sales of colour receivers, and the welcome introduction of single-standard sets. Far and away the best of these sets was the Danish Bang and Olufsen, as pointed out by Keith Cummins in a recent issue.

Initially, most British setmakers brought out a single-standard version of their current dual-standard design, perhaps fitting a tripler in place of the hot and bulky, but very effective, e.h.t. rectifier valve/shunt stabiliser arrangement. These seemed to perform better than their predecessors. In 1969 a new type of c.r.t. was introduced, marking the beginning of the end for the ungainly 19in. and 25in. types. This was the square 22in. size, and its push-through presentation gave a very pleasing and modern appearance to the first UK single-standard colour set – the Philips 511, with the single-standard G6 chassis.

Two important solid-state chassis made their first appearance in 1969. The Rank A823 chassis had some very original thinking, with a purpose-designed i.c. at the back-end of the decoder (see last month), and an unusual passive subcarrier regenerator. The A823 chassis and its later derivatives proved to be a long-lived and successful design.

Thorn released what is probably the most numerous TV chassis around, the 3000. It was similar to the 2000 series in many ways, but introduced the chopper concept in the power supply, the first application of this principle in television receivers and an approach which many other manufacturers followed in the fullness of time. In spite of the introduction of the 8000, 4000 and 9000 series, the larger-screen version of the 3000 chassis (series 3500) has continued in honourable service for many years and is only now being phased out.

The Sony Trinitron


In the early days we had to look to Japan for the really unconventional, and the 13in. Sony Trinitron receiver had everything! It seems Sony decided that if a decoder could be devised that did not decode in the normal PAL manner, it would not be necessary to obtain a licence from the Telefunken Company of Germany, the holders of the PAL patents. The result was a decoder which deleted alternate lines of the chroma signal, substituting the chroma from the previous line by means of a delay line. Two local oscillators in the decoder drove two synchronous detectors, leading up to the crowning glory, the Trinitron c.r.t. How many of us were fooled into thinking that that big knob on the e.h.t. tripler was a focus control?

With hindsight, the Trinitron c.r.t. was a harbinger: in-line guns and simple convergence adjustments – familiar now, but the Trinitron was around in 1971! With the exception of the Trinitron, the 90° delta-gun shadowmask c.r.t. reigned supreme for many years.


Varicap Tuning

Varicap tuning is used exclusively these days. It's a mixed blessing, and while it has eliminated the problems inherent in mechanical tuners, it has brought with it a whole crop of problems of its own – chop the pliers in for a digital voltmeter, substitute the circuit diagram for the vice, and we're in business again! The changeover happened just when the fiendish Heath-Robinson style mechanical tuner had given way to the simple and almost foolproof slide-bar mechanism, of which the Thorn four-button tuner is a good example. Philips were first in the field with varicap tuning, in the G8 single-standard chassis in late 1970.

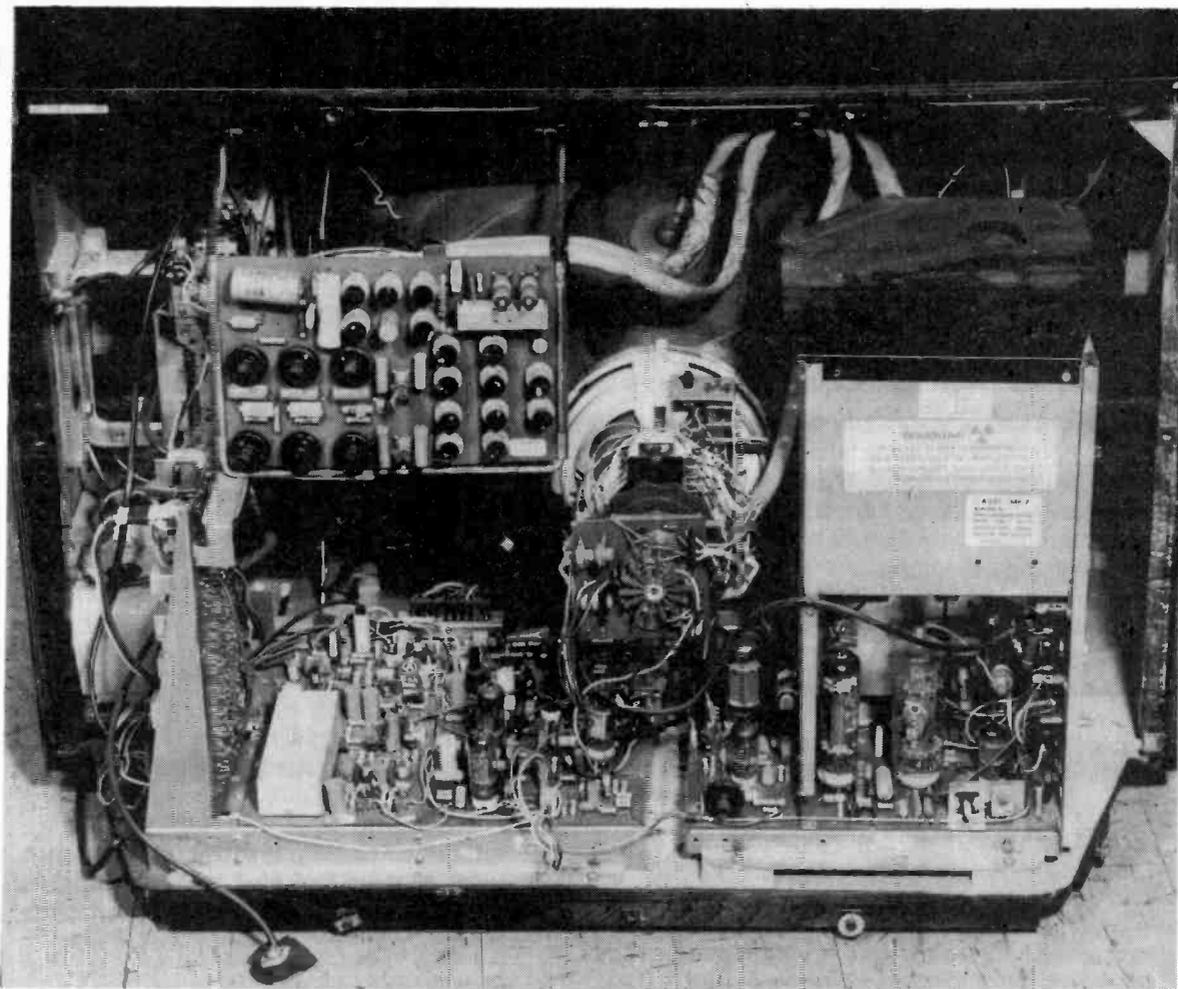We often feel that we would as lief be without varicap tuning as with. Tuning drift always seems to be intermittent and elusive when electronic tuners are involved, and there are so many possibilities when it does happen! The situation was not helped by a certain European component manufacturer who turned out thousands of tuner control



The contrast inside those sets shown on the front cover. Above, the dual-standard Bush Model CTV25, a hybrid chassis with valves in all the high voltage and power sections. The e.h.t. valves are in the screened section on the right. Note the clutter around the c.r.t. neck – and almost everywhere else! The convergence panel is at the top left. By contrast, below the Bang and Olufsen Model 4402 with its 20AX tube: the few convergence tolerance controls are on the small panel at the top left. All the timebase circuitry is on the right-side vertical panel, with a diode-split line output transformer. The signals section on the left includes the remote control system.

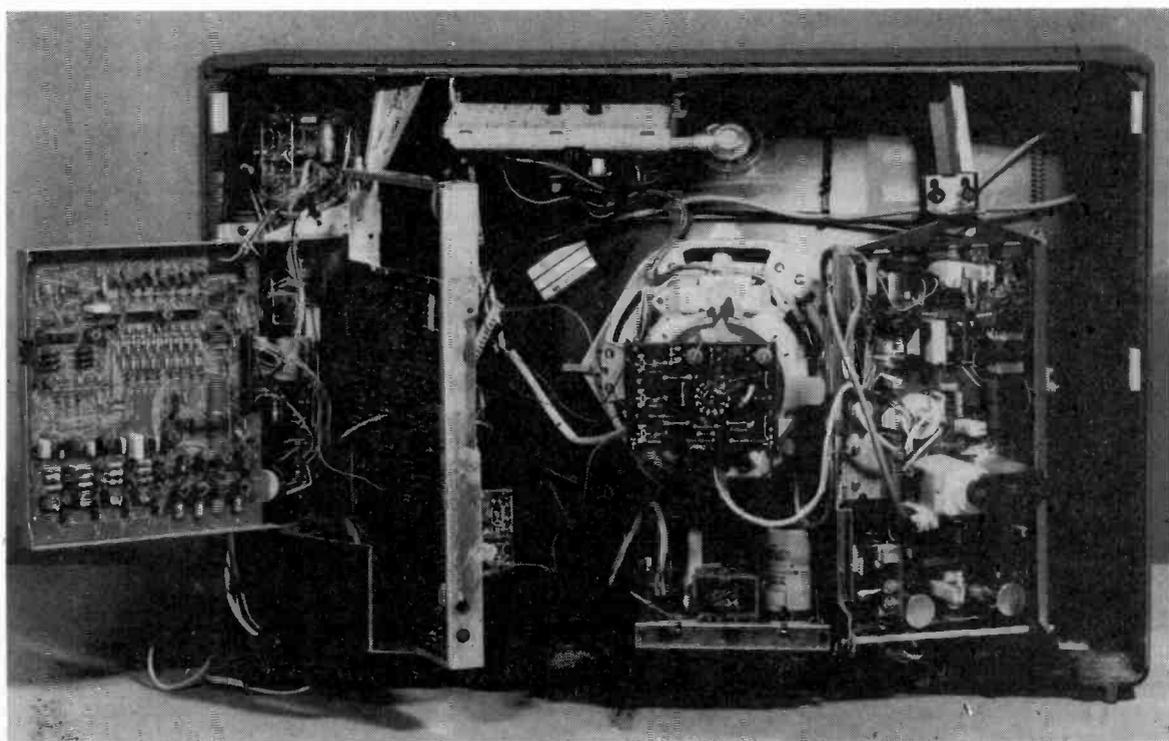

units whose resistive elements changed value on a regular basis! Touch-tuning came next, ranging from a delightfully simple transistor-plus-neon arrangement by Rank to an incredibly involved 24 transistor set-up in the ITT Feathertouch 100. Like many other functions of a TV receiver, touch-tuning (and remote control switching) is becoming the exclusive province of integrated circuits.

Came the Boom

From the low set sales up to 1969; sales of colour sets then gradually went into top gear, and in 1972-3 a peak was reached. All manufacturers were going flat out to meet the demand. Apart from the economic boom, demand was fuelled by the rapid spread of colour throughout the UK as new transmitters were opened, sometimes at the rate of several a week by each authority. One or two small setmakers sprang up in the UK, and imports of large-screen (20in. and upwards) models from Europe blossomed. As far as this engineer was concerned, this was a definite pain in the neck. The situation often arose that a handful of each of several obscure makes were purchased by his firm, and from then on these had to be serviced, spares stocked, manuals and training made available to each field engineer and so on. The ludicrous thing was that for some models we had to obtain more service manuals than we had sets if each engineer was to be able to service them in the field!

The 110° Tube

In 1972 came the 110° tube. As yet it was still in the form of a delta-gun thick-neck device, needing prodigious deflection power and elaborate high-power convergence and raster-correction arrangements. Some European setmakers introduced 110° models immediately, others sat on the fence, as did the public and the dealers – not surprising, in view of the considerable complexity of the sets, which often produced a picture no better and in some respects (like purity, focus and convergence) sometimes markedly poorer than their contemporary 90° counterparts. All this for 3 in. or so off the cabinet depth! Some customers did not even realise at the time of purchase that they had bought or rented a 110° set; certainly the sales staff did not make it a big selling point – perhaps they were unaware too!

The arrival of 110° deflection did not make a big impact in my part of the world. Probably the most elaborate wide-angle set was the 3400 model from Bang and Olufsen. This receiver boasted ten valves, 104 transistors and 89 diodes, with two PL509s providing line deflection/e.h.t. Other features were dynamic (line-rate) focusing and a separate class B push-pull output stage for each set of horizontal dynamic convergence coils. Thirty convergence controls and six raster-correction adjustments were provided in a set which vies with Thorn's 2000 model for the distinction of being the most involved colour receiver ever to be released on the domestic market.

Receiver Developments

As colour receiver technology advanced, the field timebase shrank even faster than the pound. In the beginning, the norm was a PL508 valve working with at least one triode, feeding a big output transformer. After a few years that old standby, the PCL85/805, was to be found manfully scanning a 90° shadowmask tube in some makes, the alternative being a pair of BD124s or something similar in solid-state and some hybrid models. With the new in-line gun c.r.t. types came the tiny 12-pin class B i.c. type

TDA1170, and now here we are on the brink of class D i.c.s for field deflection.

All sections of the colour receiver have undergone this shrinking process, not least the low-level signal stages, which are most amenable to integrated circuit techniques. In 1977 transistors are starting to become rare in the i.f. stages, and now that the SAW filter is with us (see the October 1976 issue) i.f. strips will change beyond all recognition.

Early decoders using discrete components certainly took up more room, but given an oscilloscope, a colour signal and a crocodile clip with which to override the colour killer, diagnosis of faults was a pleasure unsullied by inter-i.c. loops with their attendant chicken-and-egg problems. Modern three- and four-i.c. decoders, while undeniably capable of consummate performance, are in my experience more confusing to service than the conglomeration of BC108s, OA90s and little transformers of yore. The latter, I might add, generally stayed wrong when they went wrong (with one or two notable exceptions!) whereas today's chipped decoders seem to show frustrating intermittent effects when troubles develop.

Due to multiple-reflection techniques, chrominance delay lines are getting smaller too – I've got a big old DL1E gathering dust in my stores, and likely to stay there now.

Have you noticed how the number of adjustments necessary (and hence maladjustments possible) in a colour set has shrunk? The i.c. decoder removed many of the setting-up trimmers associated with the colour circuitry, while modern c.r.t.s have few or no convergence controls. The arrival of the SAW filter deletes virtually all the i.f. response adjustments, and that doesn't leave much!

The Line Timebase

Turning to the line timebase, the growing pains have been greater here than anywhere. The earliest transistors capable of the onerous duties of line deflection and e.h.t. generation were low-voltage types working from an h.t. line in the region of 60V. Most manufacturers at this time were using the Volks-valve, the PL509, in an arrangement that differed little, except in power output, from monochrome practice.

On the semiconductor front, the next generation was the BU105 type, fine for monochrome but with a p.i.v. rating that meant two were needed in series for colour TV applications when working from an h.t. line of 180V or so. All very well as long as the two drive waveforms were correctly adjusted and the tuning capacitors held out! Development work was going on apace however, and soon the BDX32 and BU206 appeared, capable of servicing a 90° c.r.t. by themselves. We come up to date with the current favourite, BU208A, which can control a vast amount of energy. For an A66-140X for instance, the line scan current is in excess of 6A peak-to-peak with a maximum e.h.t. power consumption in the region of 30W. Add to this the fact that several other stages of the receiver are powered from the same department, and this represents quite an achievement! The other contender in the line deflection stakes, the thyristor system, has not become as widespread as it might – possibly because of the cost of the special wound components and capacitors needed.

Mains Consumption

Mains consumption has gone down steadily. Some early receivers sucked 350-400W from the mains. The norm for modern receivers is nearer 120W, and even this is markedly affected by beam current. The switch-mode power units

now generally used are capable of operating at as low as 160V. This low mains consumption and wide voltage tolerance is good not only from an energy conservation point of view. Out here in the sticks we have seasonal influxes of caravanning types with invertors – as well as hillbilly-style homesteads powered by generators. Even with a mains supply laid on, we have known a cold winter's evening to reduce the mains voltage to less than 200V in cases where a farm or group of cottages are at the end of the line. If Jarge invests in the latest model, he'll no longer have to switch the electric fire off to watch TV!

A Profusion of CRTs

For those who have to maintain a component store, an increasing headache is the profusion of colour c.r.t.s now in use. Time was when one of each of the popular sizes of 90° delta-gun tube would cover virtually any set one encountered, with only the Mazda-type mutations (A55- and A67-series) to cloud the horizon. With six or more types of tube, and at least seven sizes, today's customers will have to wait while the glassware is ordered, probably at great expense – should not our re-gun man be looking to the future instead of nonchalantly rebuilding yet another A56-120X?

The Present Day

Recession followed the boom, setting in during late 1974. But while customers may have been lacking, technical innovation certainly has not. I have just encountered my first diode-split line output transformer (described in the February 1977 issue), in a Bang and Olufsen receiver. D.C. coming straight out of an overwind will take some getting used to! Here's hoping it will be as reliable as promised – that transformer looks very expensive!

Bang and Olufsen are well known for their comprehensive remote-control systems, and other manufacturers have followed this trend, ranging from simple mute-and-sequential-channel-change (ITT, Rank and Thorn) to sophisticated systems offering infinite control over all functions, like the Tandberg Model TV133. This can be awkward in the showroom – when selecting ITV on a B and O switches off the Bush and mutes the ITT! Other refinements currently available are sets which incorporate TV games, and the Grundig which offers digital readout of TV channel and time – we've come a long way since 1967!

Finally, I must congratulate the UK broadcasting authorities. The other day, I heard a television critic being interviewed on the radio. He was apparently a widely travelled man and gave it as his considered opinion that British audiences did not know what bad TV was. He was referring, of course, to programme standards and presentation quality, but this is no less true of the engineering standards maintained by the two UK television authorities. Mrs. Perkins telephones for help if Ena Sharples' face is a bit on the orange side. "I'm very disappointed with it," says she. She should be so lucky! – her American counterpart can rotate her vectors through the best part of 360° (what are vectors, Dad?). There seems to be no doubt that the decision to adopt the PAL system was the right one, although it is probably fortunate that most of us have never met a PAL-S receiver.

What will the next ten years bring? Possibly stereo sound with TV, almost certainly a fourth channel. It seems that the design of TV receivers will not fundamentally change until the flat screen arrives, and by all accounts this is still a long way off.

next month in Television

● THIRTY-CHANNEL REMOTE CONTROL

Remote control of channel changing has been a feature of some TV sets for many years, sometimes along with remote control of sound, brightness and colour. More recently however fifteen and thirty channel remote control systems have been featured on some imported sets and some export models. These are based on a set of CMOS i.c.s, and the use of these more elaborate systems is likely to spread in the near future since they can accommodate the functions required for teletext page selection. The operating principles of this type of remote control will be described, and examples of typical peripheral circuitry given.

● DECODER SERVICING

A general guide to the operation of PAL decoders, the faults that occur in them and trouble-shooting procedures, also mentioning some of the more important variations between different designs.

● TELETEXT EYEHEIGHT

What? Well, the transmission of digital teletext signals involves many differences from the well known problems of transmitting and receiving normal TV picture signals. For example, with a conventional TV signal the picture worsens gradually with reduction in signal strength, whereas with teletext reception there is an abrupt transition from correct reception to the decoder producing "scribble". It's important therefore to be able to assess the quality of a teletext signal, and for this purpose the BBC now inserts teletext test signals on lines 20 and 330. These can be scoped, and the eyeheight of the digits observed. Harold Peters explains.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:-

TO.....
(Name of Newsagent)

Please reserve/deliver the JANUARY issue of TELEVISION (50p), on sale December 19th, and continue every month until further notice.

NAME.....

ADDRESS.....

.....
.....

TEN YEARS OF COLOUR

3: Producing the Sets

Harold Peters

THE previous article, by the middle man of the “we make them, they break them, he mends them” trinity, just about sums up the first decade of PAL colour TV. Although my viewpoint was a little different, my feelings are about the same but if, as I suspect, you are either an enthusiast or in retailing, it may interest you. It may even explain why set-makers do some of the things they do, and if you end up understanding us a little better then it will have done more than just entertain.

The Beginning

To get a set into its carton, with serial no. 00001 on it, takes about ninety weeks' preparation. So it doesn't take much imagination to realise that we began about mid 1966 to prepare sets for “opening night”. At that time there was very little detail, material, or know-how to draw upon. The only sets were those left over from the NTSC 405-line “Ally Pally” experiments, and they were huge things, bristling with valves, and with a round 16in. tube with a metal cone anode, the protection for which has given us the name coneshield for today's tin degaussing coil holder.

To our surprise, the components we were offered for our PAL prototypes were 90° rectangular tubes and fully transistorised small signal stages. The Mullard Bible mentioned in the previous article was ours as well, only we read it in draft form, badly copied – for there were no zeroes (zeroxii?) then. Slide rules whizzed like trombones – we had no calculators either – and the skill of our monochrome production line was creamed off to form a small, rather elite colour crew. Each final test operator had her individual cubicle, and a lot of personal attention was lavished on every set we made. We still marvel today at the early basic Mullard design, which proved itself so dependable right through the boom years that came with the duplication of BBC-1 and ITV. What we didn't like about those early sets was all the dual-standard switching and the rather lethal shunt stabiliser e.h.t. arrangement, which for some obscure reason was known as the smokestack. Sighs of relief all round therefore when we switched to our single-standard version – but even that was not all smooth sailing. The demand for sets brought about by service duplication caused colour production to displace much of our monochrome line. This was a pity, for we had just turned out a quite handsome and dependable single-standard monochrome chassis. We eventually moved this into a separate building hitherto used as a store, but it all took time and for some years we were a little cramped to say the least.

Economies

Parallel with the activity on the factory floor, our technical staff were trying to keep the price of the set down – a crazy situation really when you consider that every setmaker was able to sell all the sets he could turn out. If you had bought a set for “opening night” it would have set you back about £350: the minivan which delivered it would have cost the same price. Today the set would still be in the £350 price range, but the delivery minivan is close to

£2,000. Ironically our industry is currently struggling to survive, the minivan is state-assisted.

As far as knocking a fiver off the price of the set, we were not given a very large area to explore. If you completely remove *our* bit – the chassis – from the set, what remains, apart from falling face down, comprises four large items which we buy in: the c.r.t., cabinet, speaker, and deflection yoke. These add up to over half the price of the set, so we knew that even if we performed a minor miracle the total price would never reflect a proportional reduction. Somehow we managed however.

ICs

The single-standard set, needing only intercarrier sound, was a sitting duck for device makers to “throw in their hat” with an i.c., and we handled our first TAA350 as if it was the Cullinan Diamond, observing to the letter all the ritual requirements of heatsinks, non-static clothing and quick soldering. Familiarity soon bred contempt, and by 1976 we were plugging them in and out like EF80s. In 1976 came the touch tune circuits with MOSFETS in them, and it was back to square one with static-free areas, cotton clothing, conductive pads and all the rest. Then last week a teletext demonstrator calmly changed programme by swapping over two 24-pin MOSFETS in the coder without even turning off the supply – and he got away with it!

By comparison with the old ratio detectors, the alignment of i.c. sound strips was too simple to be true, but because all the gear and expertise were at hand we methodically checked out all the device parameters, such as limiting point, a.m. rejection and output, even though we realised that the thing either worked or it didn't. To the dismay of some device makers the habit persists today. Should they think we are too fussy, some of our best customers live down by the river where the signal is low.

A twinge of nostalgia overcame me as we said goodbye to valves. Troublesome they might be, but when since have you been able to get instant fault diagnosis at the expense of a scorched handkerchief?

Where i.c.s were concerned a lot of heartsearching went into the problem “to be pluggable or not”. An i.c. is so reliable once reposing in its correct circuit that a holder, if fitted, became the most unreliable part. It's like digital watches, where the trouble is nearly always with the battery rather than the watch itself. In the main our i.c.s are soldered straight into the board, but as an exception we fit holders on circuitry which requires an elaborate pre-test, because the wide i.c. tolerance spreads do not permit us to work with as narrow a window of acceptance as we would like.

Test Features

It surprised me, in preparing these notes, when I saw how much some of our testing had changed, and how little the rest had changed. To begin with items like decoders and i.f. strips were laboriously plugged up and progressively aligned by hand, using test probes applied to the board by solder blobs. Tuners were married to i.f. strips and were serialised

in case they got split up. Coils left the winding factory "rough aligned" with such precision that one of them had to be deliberately mistuned to ensure that alignment of the strip was fully carried out. We still do it this way, but with sufficient experience to be able to issue units or pretuned modules to the service trade so that fitting in the field will not involve realignment.


The synchronous vision detector (TCA270 in our case) was the i.c. which caused us most headaches. It isn't a true synchronous demodulator since it has no separate phase-locked oscillator, using the residual i.f. signal carrier, suitably limited and phase shifted, instead. This is variously called a quasi-synchronous demodulator, or an exalted carrier demodulator, depending on whether you are for or against it. Whatever you call it, its mode of operation caused it to defy sweep generator alignment of the conventional type, and forced us to abandon overnight the habits of a lifetime.

By the time the sales boom of 1972-3 hit us, i.f. and decoder alignment had become a press-button affair. The panel was clamped into a frame and its copper side impaled by sharp, spring-loaded pins through which the appropriate test signals were applied via relays enabled by a diode matrix. If the presence of a pin affected alignment or produced any form of undesired loading, it was pulled down by a solenoid when not required. From then on, modifications involving work on the copper side were out. One frustrating effect of this streamlined testing was, and is, to be able to go down the production line and see a girl align a set better in twenty seconds than you could in an hour.

1975 saw us extend this pin-jig feature further. By the addition of more pins to the jig, and more test pads to the copper side of the board, it became possible to test panels for correct component values prior to alignment. This was done by comparison with a standard set of components within the test gear. If you think this is unimportant, just mix up six 1.2k Ω resistors with six like type 12k Ω ones, and see how accurately you can sort them out in ten seconds starting now.

As technology moved us forward, so the Health and Safety at Work Act backpedalled us a bit. Our latest test benches guard the work (more strictly the operator) with heavy perspex covers, through which protrude spring-loaded adjustment tools which sometimes line up with their intended preset. Rather like you would expect to handle a radioactive railway ham sandwich. We now have a full-time safety officer, and to our credit have had only two small fires since the act has been in force. We didn't have any previously.

At the point where the chassis meets its tube, the final test area, the amount of test equipment per operator position has been greatly reduced. The majority of our involved setting-up procedure is carried out by subjective assessment of a variety of test patterns radiated over the factory signals system. Our mainstay is the ubiquitous PM5544 coloured circle pattern, with which we check just about everything, even the 4.43MHz reference oscillator by swinging the pattern's subcarrier. Signals at the ends of the bands ensure complete tuner coverage, and the centre cross pinched from the PM5544 is overlaid on the convergence crosshatch. We distribute at u.h.f. through high-quality feeders and terminate in variable attenuators, providing an accurate signal from 10 μ V to 30mV to up to 500 simultaneous positions. A far cry from the beginning when, in default of a satisfactory cable distribution system, we radiated the signal down each production line and collected it at the test points on small aerials. The factory fabric absorbed most of the

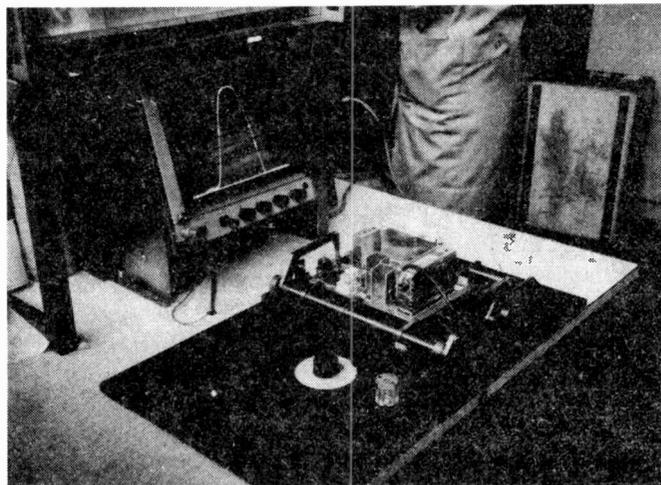

The modern method of factory alignment, with the i.f. board mounted on a pin jig through which signals are injected and extracted and power supply connections made. The large knob on the left is the signal attenuator. Each step is selected by a push button. As the monitor screen shows, a text book i.f. trace is obtained every time! (Courtesy Pye, Lowestoft.)

stray radiation, to the annoyance of neighbours hoping to set up their newly acquired sets.

Soak Testing

The size of the early sets made us glad to get them into their cartons and out of the factory as quickly as we could. Today we give every set two long soak periods before the dealer gets it. The first happens as soon as it has been assembled, but before any setting up is done. At this stage the pictures are unbelievably grotesque, but we accrue the advantage of spotting trouble before too much work has been done on the adjustments. Imagine what it feels like to set everything up carefully, only to find that the c.r.t. is dud. . . .

Power supplies

Soaking sets for long periods means that several hundred will be fired up at the same time. As well as making demands on our transmitters, the mains supply comes in for a caning too. We knew that our 110° delta-gun c.r.t. set would have a single thyristor power supply as well as the new tube, so each set would take a huge gulp of mains, all at the same time, and all at the back end of the positive mains half cycle. This lowers the r.m.s. level of the positive half cycle, or put it another way pushes negative d.c. back up the mains (Fig. 1). This d.c. will saturate any isolators interposed for safety, which means that their rating must be twice what you would expect from the wattage printed on the back of the set.

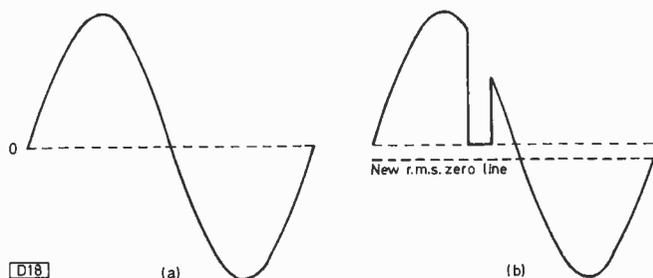


Fig. 1: (a) The normal mains waveform. (b) The mains waveform showing the chunk extracted by a thyristor controlled power supply: since the waveform is now asymmetrical, the r.m.s. zero line shifts, producing a negative d.c. component.

We accordingly asked the Electricity Board to provide for this, which they did, and at the same time they carried out a number of tests here and elsewhere to study the effects that large numbers of these sets would have upon the supply waveform. The results were rather frightening, with a set of oscillograms looking like the Fourier analysis of the last chord of "Rite of Spring". Their report suggested that too many of this type of power supply used too close to a computer installation (for example) could affect its performance due to waveform distortion. Please don't try it or you will get me into trouble. Our latest sets have a full-wave rectifier system, which pleases the Board but leaves servicemen with a half mains potential chassis.

Covergence and Purity

Initially purity, covergence, degaussing, and grey-scale tracking were taken to be part of the dealer's installation procedure. Where perfection is required, they still are. Discount warehouse marketing of latter years however has demanded a set which, when unboxed by the user, will give a reasonably good picture without any adjustment at all.

We first stumbled on this requirement when we sent our export models into W. Europe and Scandinavia. In remote areas, buying a TV set is usually a mail order affair, with the chosen model being delivered halfway up a mountain side by the Postbus. The need for extra precision would have to coincide with the advent of 110° deflection, which bothered us anyway.

To see the problem, imagine a line drawn two inches in from the edge of the screen on the tube face. If all that is within the line represents the area of a 90° set, the part outside is the additional area needing purifying etc. on a 110° set. No doubt you are familiar with the way purity on 90° sometimes makes it only just. If so you can appreciate the problem posed by the extra angle of the 110° tube.

Imagine our dismay when we realised that in order to cover the Postbus requirement we had not only to tackle the extra screen area but also to ensure that the beam landings were in the middle of their respective phosphor dots, not just hitting them somewhere.

Today's in-line guns give better results with considerably less trouble, so with that hurdle behind us for keeps you would expect to find us reasonably happy. But no, TV setmakers are like farmers: nothing seems to please them. "Self-convergence" makes the set easier to assemble, with fewer components, but requires a rather special convergence/scanning yoke. The total difference to the shop price is small, the difference being where the work is done. Europe's gain is one of our lines lost, and at the same time the control of the manufacture of that bit of the set passes out of our hands.

The same applies with the surface acoustic wave filter, which removes any control we have of the i.f. response but does not save us a mint. Despite the assertions of SAW suppliers, the group delay response of the average hand-crafted i.f. strip is not too bad, and when it comes to teletext it's the transmission system which worsens the eyeheight more than anything, as you would expect when you squeeze a 6.9 megabit quart into a 5.5 megahertz pint pot.

Safety

More progress has been made in the safety field than anywhere. I doubt if there is a non-BEAB approved set on sale today. We were lucky enough to get some experience of the requirements with our export range, which had to satisfy the similar requirements of the various European inspectorates, or "Test Houses" as we call them. These vary slightly from country to country, and if anything the BEAB

tests are the most demanding of them all. Without realising it, this fact has contributed to stability of design, since a setmaker thinks twice about putting in a modification which will involve him trailing the length and breadth of Europe to get it approved. A domestic grey area which thankfully has never been put to the test is when a BEAB approved set is repaired using a non-approved part and as a consequence later causes damage or injury. It could easily happen.

Service and Serviceability

Right from the start we knew that a colour set was going to be the most complex item any industry had let loose inside the homes of the general public. So we made sure that our service manuals were as comprehensive as possible. At the same time our Technical Manager toured the country imparting know-how.

In the years that followed we have forged links with a number of dealers upon whom we can count for an unbiased report, and have set up a group comprising factory, spares, and service personnel so that information coming back can be quickly acted upon. By comparison with monochrome the serviceability of early sets was poor, but it's got better. We still have to convince the production staff of the need for change, but happily the majority of service improvements benefit them as well. The only outstanding, and possibly insoluble, difference is that production like their panels big, but service prefer them to be small isolated boards, each one an entity itself.

The Japanese

Strenuous efforts were made prior to the boom to keep out Oriental imports. The PAL patents were invoked, the European test houses were very stringent, and all manner of discouragement was put in their way. The boom changed all that, because setmakers needed a certain amount of oriental components and tubes in order to maintain their share of the market. The dependability of the complete receivers supplied by Japan is now history, and arose from their strenuous efforts to satisfy all the test houses with a common chassis. It caused our Quality Assurance Department to switch its sights from the German attainment to the Japanese – possibly a false promise, since their quality is rooted in conception as well as design and execution. I have heard that the only place not troubled much by oriental competition is France, who insist on all imports being capable of resolving the 819-line system as well as 625. Why didn't we think about deploying 405 lines that way?!

Where now?

Traditionally we should end up with a peep around the corner into the future. Not this time! Successive Governments have used our trade so readily as a convenient economic regulator that we are no longer masters of our own destiny. So instead I am going back in time, past this decade, past the two previous years when "Late Night Line Up" went into colour and only a handful knew, past the 405-line midnight tests from Ally Pally, right back to an evening in 1935, just after the last jubilee, when my mother scorched my rugby shorts.

The occasion was the burning down of the original Crystal Palace – and from our house we had a grandstand view. I recall my mother's words at this final Brocks Benefit. "I suppose it's that Mr. Baird and his Colour Television Experiments." To set the record straight, it wasn't: his equipment and the nearby South Tower were just about all that remained, but you can see that I was biased from an early age.

LETTERS

SPLICING VIDEOTAPES

In your October issue reference is made to splicing videotapes (VCR Notes). Some two years ago I tried the butting method suggested, but found that the splice lasted for only a short time. I also believe, but can't prove, that the splice accelerated head wear since the head failed approximately 30 hours after starting to use the spliced tape (with the spliced tape itself in use for about ten hours), giving a total head life of approximately 300 hours.

It seems to be very difficult to make a satisfactory butt joint. I did not initially use the spliced tape with the new head, but when this head reached 500 hours' use I decided to try again – particularly as by then I had another broken tape. This time I overlapped the broken end portions and stuck them together. The splices have not parted so far, and with three tapes (two spliced) in use more or less in succession the second head is still in use after 800 hours. I cut the ends perpendicularly, smear adhesive (Dunlop Thixofix) thinly on to the outer side of the leading tape end portion for some two inches, and before the adhesive dries press the two portions together and leave for a few minutes. Any exposed adhesive must be carefully removed with methylated spirit, though if the splice is carefully done this will be on the outer (non-head) side of the tape only. To avoid head wear, the head side edge must be the trailing edge of the splice. A line or lines will pass down the picture as the splice passes round the head, but this is tolerable. I also use Thixofix for sticking on stop foils cut from aluminium foil.

Regarding distortion of the tape edge portions at the beginning of the tape, repositioning the stop foil, as suggested, won't cure it for long. The distortion is caused by the flange at the lower end of the upper of the two white guide rollers of the cassette. This flange is presumably intended to position the tape correctly, but in practice what happens after a few uses of the tape is that it folds over a part of the lower edge portion of the tape, thus doubling the thickness for about $\frac{1}{16}$ in. at the lower edge portion. When this thicker portion is wound on to the reel it slightly distorts the corresponding edge portion of at least the next layer of tape, making it easier for the flange to fold it next time the tape is used. Thus a bit more is folded every time the tape is used.

It's possible to remove the folds by hand, although the tape will remain creased lengthwise and hence be likely to fold again. It's better to cut out the bad portion and splice the tape as described above, adding a new stop foil. In an attempt to avoid this trouble, I've tried changing over the two rollers in the cassette. This seems to work better. The tape edge portion can still become folded over on the cassette case, but not so readily. – W. H. Hammond, *Gravesend, Kent.*

DON'T SPLICE VIDEOTAPES!

As an engineer with considerable experience in the video field I was surprised to read some of the statements made on the subject of VCRs in your October issue. First, I can say with great confidence that anyone who tries to splice cassette tape together and anyone who attempts to wind on other tapes is doomed to failure. It is *not* folk lore that

splicing tape will "strip the heads in one go": it takes approximately one and a half seconds for a vertical splice to go around a head drum revolving at 1,500 r.p.m., so this gives each head some 40 goes at shattering, not such good odds. The splicing tape eventually stretches anyway, thus widening the gap with time: worse odds now!

Scotch Guardsman tape is part of a family, and I assume the reference is to type 8173 — $\frac{1}{2}$ — 3550: this is thin low-energy (density) tape designed for time-lapse machines or extended playing time on the Sony CV2100. Although it's nearly as thin as VC60 tape it's certainly not chrome oxide (Philips, BASF, Memorex), nor is it cobalt (Scotch), so it's use on a VCR will cause it to saturate, resulting in a low f.m. signal on replay. This will show up most frequently as replay colour drop out. All of this does not take into account chewed tapes which stick as a result of many greasy finger marks.

While agreeing in principle that saving money is a good idea, remember that new VCR heads, fitted, will cost about £55-£60. What price then do you pay for cheapness? This also applies to the use of computer tape (this was not recommended in the original article – *Editor*) or high-energy tape on normally low-energy machines, when bills of £250-£350 can result for new drums and guides – poor performance and incompatibility are suffered long before the wear is noticed.

The new Philips N1700 is a special machine. Professional engineers are fed up with being asked to modify N1500s and /01s and are not going to be plagued by requests to convert N1502s into N1700s, because they are not the same thing. On an N1700 the head gaps are oppositely inclined, with no guard band between the tracks: the principle is that if one head scans the other's track there will be little or no output. As for skip field principles, due to the PAL four-field sequence anyone who goes about chopping this up ad lib will end up with intermittent colour drop out and gross phase errors at the top of the picture as the PAL squarewave loses continuity. The Sony VO2850 and Philips N1520 ignore this when editing, but quad machines do not.

As to the bit about disconnecting the N1520 edit clearing button relay, if an N1520 releases edit buttons during an edit it does so for a reason, even if it is a fault condition: the cause should be cured rather than the symptom removed. The release relay is there to stop any normal recordings being done in any edit mode. Someone at Mr. Matthewson's establishment is going to complain that a tape replay won't track, probably because there's no control track as someone did a recording in the insert edit mode due to someone removing a wire from the pushbutton release relay. – S. R. Beeching, T. Eng (CEI), A.M.I.E.R.E., *B & B Electronics, Newark, Notts.*

JOSTYKIT HF385 VHF/UHF AMPLIFIER

We regret that Jostykit electronic kits are no longer being distributed by Jostykit (UK) Ltd., Middlesbrough. The above amplifier, featured in our August issue, is not currently available in the UK therefore.

We will be featuring a wideband aerial amplifier for the constructor in a future issue.

TV Teletext Decoder Update

Steve A. Money, T. Eng. (CEI)

DURING the series on constructing the *Television Teletext decoder* there were a few omissions and errors. Whilst the more important of these have already been dealt with it was felt that for the sake of completeness all these errors should be collected together and presented, along with one or two hints on construction and some recommended modifications to improve the operation of the decoder.

INPUT LOGIC CARD

Since there were no errors in the power supply module we shall start by dealing with the input logic card which was described in the April and May issues. The circuit diagram in the April issue should be modified as follows:

(1) On IC1c the pin numbers are incorrect. The input should be pin 13 and the output should read pin 12.

(2) The inverter between IC6 pin 5 and IC13 pin 12 is section f of the 7404 IC10.

(3) Resistor R5 was omitted from the circuit diagram and should be inserted between pin 9 of IC8 and pin 1 of IC5a, as shown in Fig. 1.

(4) For more reliable operation, pins 2 and 4 of the 7485 IC24 should be connected to 0V.

In the table of top soldered connections to the ICs, printed in the May issue, the number of connections to IC2 should be 6 and not 7 as printed. This makes the total number of top soldered connections on the board 114.

On the soldered layout diagram, capacitors C6 and C7 are incorrectly numbered. The capacitor near IC1 should be labelled C7 and that near IC5 should be C6.

The component layout for this card does not show the positions of the decoupling capacitors C1 and C2. Capacitor C1 is connected across the +5V and 0V supply input tracks running from pads 14 and 17 of the edge connector. It is convenient to use the leads of this capacitor to form the through board links on these two supply tracks. The second capacitor C2 is connected between pins 5 and 10 of the 7493 IC7 and is mounted on the track side of the board.

Pins 2 and 4 of the 7485 IC24 should be connected to 0V. This is simply done by linking them with short wires to the track running alongside them from pin 8 of the i.c.

It has been found that the latest version of the i.f. card gives slightly different clock timing from the original prototype design, and that for optimum decoder operation capacitor C7 on the input logic card should be removed from the circuit.

DISPLAY LOGIC CARD

Since there are no errors on the memory board the next card to be dealt with is the display board described in the July and August issues.

Some readers have been puzzled by the fact that on the mother board there are tracks carrying -5V and -12V supplies to the display board edge connector whereas there is no mention of either of these supplies on the display

board circuit or printed board layout. These supplies were required for the 2513 character generator ROM originally used on the display board, but when the circuit was updated to use the Texas SN74S262 ROM these supplies were no longer required since the newer device runs from +5V only.

In the process of changing the ROM however an error slipped into the graphics/alpha switching logic. In the circuit diagram the connection from pin 11 of IC6d should go to the DB4 input and not to DB5 as shown. Unfortunately this error also occurs in the printed board layout, and will be present on some of the early PCBs supplied to readers. It is quite easy to modify the board to correct this error. Cut the track from IC6d pin 11 at a point just short of its junction with pin 4 on IC3, then link the open end of the track across to pin 11 on IC3 with a short piece of wire. This modification is shown in Fig. 2.

There were one or two errors on the layout diagram, Fig. 5. Pin 7 of IC5 and IC7 require top soldering, pin 1 of IC13 doesn't.

Some problems have been experienced with the loading operation of the 74165 shift register IC1. The circuit uses the input impedance of the 74165 to produce a differentiating action and thus generate a short load pulse for the shift register.

Because of variations in the input characteristics of different makes of 74165, and even between different batches of the same make, this circuit does not always work correctly. The recommended modification to the display board to ensure reliable operation is shown in Fig. 3. Capacitor C1 is removed from the board. Gate IC8b was

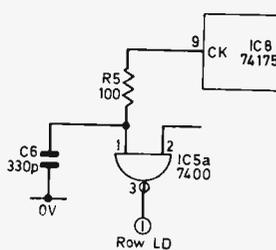


Fig. 1 (left): Position of resistor R5 in the circuit of the input logic card.

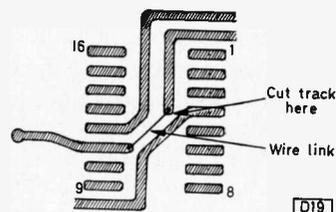


Fig. 2 (right): Modification to the display board.

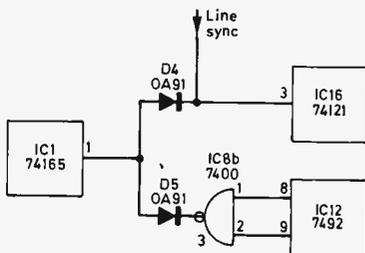


Fig. 3 (left): Modified 74165 (IC1) load circuit on the display board.

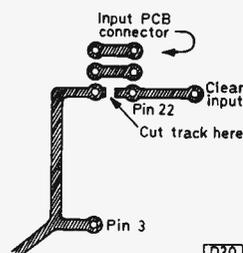


Fig. 4 (right): Modification to the mother board.

originally used with the 2513 ROM and produces a pulse at the end of each symbol period. Diodes D4 and D5 act as an OR gate which ensures that the shift register is loaded by either an end of symbol pulse or the line sync pulse. If the line sync pulse was not included, the first symbol of each row of text would not get loaded into the shift register and would not be displayed on the screen. The two diodes are mounted on the component side of the board directly from pin 3 of IC8 and pin 3 of IC16 to the track leading to pin 1 of IC1.

MOTHER BOARD

On the mother board described in the September issue the sound feed for the text mode was omitted. There should be a link from pin 3 of the i.f. board to pin 3 of the display board. This should be made by joining these two points with a length of insulated wire.

There is an incorrect link on the board and this must be cut. It occurs at pin 22 of the input board connector, where the input from the Clear Page switch is connected. The short link to this pin should be cut so that only the Clear input connects to pin 22. This is shown in Fig. 4.

IF BOARD

Since the design was published, the package used for the surface wave filter has been modified. PCBs will be supplied to suit the new version of the SW150 filter.

In addition to the amendments listed on page 39 last month, we have omitted to show pin 13 of the CA3046 on the circuit diagram. This pin must be earthed. The p.c.b. is also shown incorrectly in this respect, although boards purchased from the Readers' PCB Service will be correct.

Modifications giving more reliable i.f. board performance under different signal conditions are being tested and details will be given next month.

THROUGH BOARD LINKS

A. S. Denby of Alcester has an interesting tip for inserting the through board links on the logic cards. He uses a length of 10A fuse wire and threads it back and forth through all the link holes before putting any other components on the board. Then each link is soldered on both sides and finally the surplus wire is cut away. This approach could certainly be much quicker than inserting the linking wires individually. ■

Co-Channel Interference Filter

Allan J. Latham

THE author lives approximately the same distance from Crystal Palace (70 miles) and Stockland Hill (80 miles). Because the location is on the western side of a hill, we are shielded from Crystal Palace and Stockland Hill is usually the stronger signal. Since the ITV transmissions from both stations are on channel 23, co-channel interference is a serious problem: at times it can make both stations unwatchable, although Stockland Hill is usually reasonable. The filter described was devised to reduce the interference.

The vision carriers of U.K. u.h.f. TV transmitters are offset from their nominal frequency in order to reduce the visible effects of co-channel interference. The offsets used are 0, + 5/3 and -5/3 of the line frequency. This results in differences of 0, 5/3, or 10/3 of the line frequency. The visual effect is of diagonal lines which are very nearly horizontal (zero difference is rarely used since in practice a beat frequency of tens or hundreds of cycles would result, and the visual effect would be very disturbing).

The notch filter (see Fig. 1) was built into the luminance channel of the author's set, immediately before the black-level restorer circuit. The circuit consists of an RC notch filter followed by an amplifier to increase the Q of the circuit. The overall gain of the circuit is a little less than

unity (at other than the notch frequency) because all the output voltage is subtracted from the input to the f.e.t. gate. At the notch frequency the gain is the notch depth plus the open-loop gain of the f.e.t./transistor combination - it should be about -30dB, but was not measured.

The unit was constructed on Veroboard, and no stability problems were encountered. The frequency control potentiometer R4 must be a multiturn trimpot type because tuning at the h.f. end is very critical. The other potentiometer is not so critical. The prototype used a BC213L transistor (Tr2) but any pnp plastic general purpose type with a gain of about 100 could be used. The power supply was taken from the set: two rails were available, 30V and 12V, and either worked satisfactorily.

Setting up and Use

The setting up procedure is very easy. Adjust R4 for minimum interference (the 50kHz notch is with the slider near the capacitors). Then adjust R2 for minimum interference, and finally readjust R4.

It should be possible to completely remove the offending interference. One thing that will become apparent however is slight smearing of some parts of the picture due to phase shifts of video components near the notch frequency. This is worse at 50kHz (10/3 line frequency), and when a grey raster is being transmitted three faint vertical bars are apparent due to the phase error at 45kHz. This is a small price to pay for the removal of co-channel interference however and is much less objectionable.

The unit was arranged so that it could be switched in or out as required. The phase errors are not visible on channels not suffering co-channel interference therefore.

The author would be interested to hear from others who have experimented with methods of co-channel interference rejection. ■

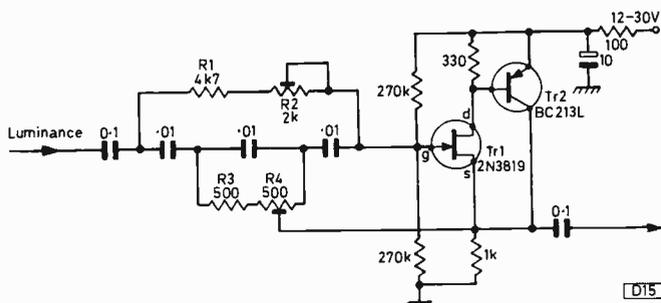


Fig. 1: Circuit of the active notch filter.

It won't take you a minute . . .

Les Lawry-Johns

THERE are days when everything goes with a swing: there are others when you are on a roundabout which keeps bringing you back to where you started from. Not only do you get nowhere, but the damned thing starts going backwards and you end up hate filled, bitter and frustrated. Much like that ladybird I was watching the other day walking round and round the top of an empty bowl, not realising that it kept coming back to where it started. But then ladybirds can fly off and escape from that type of torture. For me there was no escape when that Hitachi monochrome portable arrived for its three day stay which I thought was going to be a couple of hours at the outside. You could call it a mother-in-law, and it behaved in much the same way.

A Good Start

It (the day) had started off quite well really: three colour sets polished off in minutes each. The first, an Ultra with a 3500 chassis, simply needed a red button cut-out because it had cut out and wouldn't come back. Twist, twist (the tabs), unsolder two leads, plonk the new one in and that was that.

The second was a Decca with the Bradford chassis. Poor focus, width o.k., check the resistors associated with the focus unit (two 4.7M Ω resistors, one from the tripler to the focus unit, the other from the unit to chassis) and find one high. Snip snip and Bob's your auntie.

The third was an ITT CVC5 with no sound (PCL86) and an initially rolling picture (PCL805). It doesn't happen very often like that but there they were, three in a row and I was smiling. Then in walked Stan.

The Hitachi Portable Arrives

"Just have a look at this portable will you, you did it a couple of years ago and it took only a few minutes, probably the same thing again. I'm going to have a haircut - collect it on the way back". Before I could think of a cutting remark he had gone, leaving his Hitachi P32 monochrome portable for me to wave my magic wand over.

Although there were several other things to be attended to I thought I'd try to oblige. Screw either side and two underneath, pull off the side contrast and brightness knobs and lift off the cabinet shell. Plug in aerial and switch on. Still tuned in as sound came on full strength, but no picture. E.H.T. o.k. Tube base voltages: first anode pin 7 o.k., grid pin 5 near enough right, cathode pin 2 high at 100V (should be about 54V).

Well that looks easy enough: video output transistor not drawing any current. Where is it? There, with a heatsink on it: check collector, 100V; base 2.5V; emitter 2V. Switch off and cold check the transistor. Reads right and as the base should be at 4.2V check back through the contrast control to the emitter of the video emitter-follower. Voltage low here too, and the base low at about 2V (should be 4.95V). Where

does it get its bias from? Check bias network, having removed the screening covers (soldered on in several places) to get at the print. These and other components seemed to be blameless.

Some time had gone by and back came Stan. "Done it?" he enquired cheerfully. "No", I growled. "If you think it's that easy, do the bloody thing yourself".

Only the Sound's Slipped Out

"Don't be like that", said Stan. "It's only that the sound slipped out".

"Slipped out, slipped out", I croaked. "I suppose the picture slips in when the sound slips out?"

"Yes, that's right. The knob's probably loose", said Stan helpfully. This was too much for me. Putting the set back upright, I asked him to give me a demonstration. He turned the tuner knob slightly and the sound slipped out and some sort of picture slipped in. I clutched at a straw.

"You haven't just come back from a wine tasting trip to Germany have you, and had this thing seen to out there?"

Stan looked at me as if I'd gone loony.

"I don't drink wine if that's anything to go by, and I haven't been to Germany or Timbuktu, and if I had I wouldn't have taken this with me, so what are you on about?"

"Never mind, I only thought . . . Oh well", I floundered.

I returned to the tuner. Tuned in correctly, there was no illumination on the screen at all. Detuned, the screen lit up and the sound naturally slid off. The possibilities were endless and my mind went numb. "Better leave it with me Stan, there's nothing easy about this one".

Stan departed, mystified that such a small thing could take so long to put right. He said he'd call in when he finished work on Monday evening, leaving us the weekend. When he had gone there were several other sets to see to before we could get back to the mystery. When we did get back to it however we didn't get very far.

The AGC Circuit

It was now obvious that when a full-strength signal was tuned in there was insufficient output from the detector to drive the video emitter-follower. Without an aerial at all, the set behaved itself and a grainy picture could be tuned in with almost normal sound. This naturally directed attention to the a.g.c. line, which was checked through bit by bit as the circuit (see Fig. 1) is not all that easy to follow from the manual. The two transistors appeared to be in order on a cold test, the capacitors had capacity, and the resistors were right. With the set on again, everything was in order! Therefore all the testing had been in vain, since the fault was not present. After some time however the picture started fluttering and back we were to square one. After some more fruitless checking we put it down until the next day.

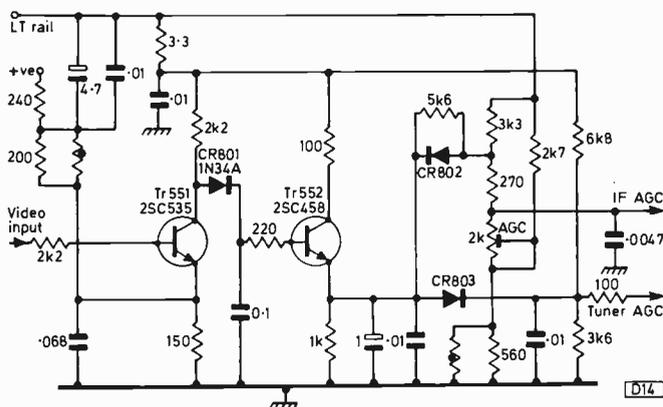


Fig. 1: A.G.C. circuit, Hitachi monochrome portable Model P32.

The next morning we started again. So did the set. Fine for a few minutes, and then the overloading started. Without turning off, we returned to the testing. Still the low detector output, so we worked back along the i.f. strip.

The a.g.c. applied to the first two i.f. stages seemed very small and varied little as the aerial was withdrawn. There was a good swing at the base of TR551, but not at the base of TR552. This directed attention to both transistors and CR801. The latter checked out o.k., and bearing in mind the fact that we had already had some hanky panky with the fault coming and going we replaced both transistors with BC107 types (for convenience) and were rewarded with a steady, unblinking picture with normal sound.

Many hours had been spent tracing this simple fault but there had been several interruptions to distract us. When Stan returned his comment was "I knew it wouldn't be very much. Fancy it taking you all that time to do it". Our reply was unprintable.

A Very Grainy Picture

Hardly had we sorted this one out when a Pye 180 arrived. Picture very grainy indeed, suggesting a poor aerial socket, or perhaps a defective tuner. This solid-state Pye monochrome set uses the same i.f. selectivity/gain module as the CT200 and the Philips 570 series. It's been a constant source of trouble, due to defective soldering to the capacitors and coils in the unit. We disregarded the tuner etc. therefore and without further ado set about removing the i.f. module. Using a solder sucker or desoldering braid, this can be done in a matter of minutes, so we soon had the suspect stripped out of its can.

There are several possible trouble spots with this unit, as we have mentioned before in previous issues. We always go straight to the components on the print, which are soldered on both sides. Lifting the small capacitors a fraction with the solder melted ensures that the legs get the solder and not the cement. This is normally all that is required, and once again this seemed so as a normal picture appeared when the unit was replaced. After twenty minutes however the same symptoms returned and the whole process had to be repeated, this time with lasting success.

A Rigonda Starlet

Then followed a long, involved tussle with a Rigonda Starlet 603. We do not normally handle these, but this set belonged to a close relative so with bad grace we got down to it. The complaint was that it would function for a time and then intermittently go off as though switched off.

As the owner was a first class poacher (not really, he does get permission from the farmer), I suggested that a nice fresh rabbit would come in handy, skinned and dressed of course. He readily agreed but complained that the rabbiting was not so good of late because his wife had been petting one of his ferrets. The result was that as soon as it was released at the rabbit hole instead of going down it would roll over on its back to have its belly tickled. This is not at all the idea, so until he could break the habit the catch would be reduced. I found this hard to believe because every ferret I've ever met seemed to have had but one desire, to bite my fingers off. Since these were very young ferrets however I presumed that they would develop their more ferocious habits later. Ah yes, the Rigonda.

Now these are made up in slabs which can be separately detached – top, bottom and sides. Since the power pack is at the bottom we removed the four screws and then the bottom slab. This gave us partial access, at least enough to confirm that although the supply voltages were reaching the base and emitter of the regulator transistor its collector was shutting down with monotonous regularity. At first sight the regulator looked very much like an AD149 or similar, except that it had three legs in the same configuration as the more common smaller drivers etc. Never to be accused of wasting an opportunity, we stuck a 10Ω dropper section between the emitter and the collector to bring it more into line with what we are used to. The thing then worked and regulated correctly. Remove the resistor and it reverted to its hysterical behaviour. Check the transistor and it read o.k. Replace the resistor and the thing worked for an hour with the resistor taking only a small amount of current.

I suppose the resistor kept the emitter voltage just that little bit over the base voltage so that the transistor continued to conduct, but the appearance of the control panel persuaded us not to argue with the other three control transistors over the matter. In our tattered nervous condition we did not feel inclined to delve deeper, so we replaced the power slab and called it a day, rabbit or no rabbit.

If it comes back I'll fit an AD149 and see if that cures the condition, but so far everyone appears to be happy.

TV TELETEXT DECODER

TROUBLE-SHOOTING AND REPAIR SERVICE

To assist constructors who may encounter difficulties with this project, *Television Technical Services* are offering a trouble-shooting and repair service for the various modules. The charges are as follows: modulator £2; input card £4.50; memory card £3.50; display card £4.50; i.f./data recovery card £4.50 (including alignment). These charges include the cost of replacing minor components, and return postage. Any expensive replacement parts needed will be notified to constructors. Modules should be sent with remittance and package able to withstand return mailing. Write or phone for a quotation if you wish to send all four boards for testing.

Television Technical Services,
PO Box 29,
Plymouth, Devon.

Tel: 0752 813245

The Television MONOCHROME PORTABLE RECEIVER

Part 3

Keith Cummins

LAST month we covered the signal circuits in the receiver. It's time now to turn to the timebases, starting with the SN76544N i.c. which contains a sync separator, noise gate, and the line and field generators. First of all a couple of corrections. C36 (0.1 μ F) was unfortunately omitted from the circuit diagram: it decouples the feed from R79 to the tuning voltage pin of the varicap tuner. Tr8 and Tr10 should have been shown on the circuit as type BC212L: the pin connections to the BC212 are different. The volume control RV1 was shown as 25k Ω on the circuit diagram and 5k Ω in the components list: either will do but the latter value gives a better control range. The correct value for C62 is 22nF (0.022 μ F) – shown incorrectly on the circuit and in the components list. A chassis connection should have been shown to the tuning head (Fig. 2), and pin 8 of IC103 should have been shown connected to chassis. C16 is 0.47 μ F as on the circuit diagram, not 4.7 μ F as listed in the components list.

Sync/Timebase Generator IC

The SN76544N i.c. (IC105) is a 16-pin device and all its pins are used. The makers state that the individual connections are short-circuit proof to their adjacent neighbours, and also short-circuit proof to earth. It's better of course if the constructor does not put this to the test. It's certainly *not* true of the SN76001N audio i.c. I write from rueful experience: the AVO prod slipped!

A block diagram of the SN76544N i.c. is shown in Fig. 6. It requires a d.c. supply of course, at 11V, and this is

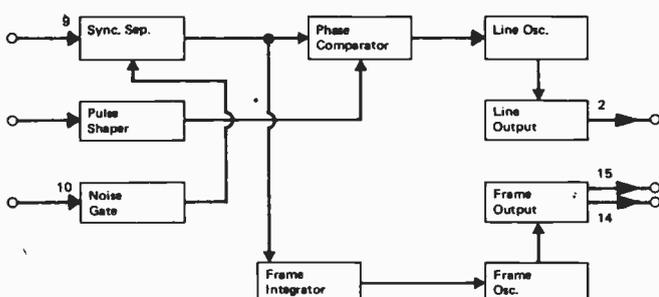


Fig. 6: Block diagram of the SN76544N i.c.

filtered by R30, C19 and C33. Its inputs consist of the output from the first sync separator Tr10, an input from the video distribution point to the noise gate, and finally a sample pulse from the line output stage for phase comparison in the flywheel sync circuit. The outputs consist of drive pulses for both the line and field timebases. Complementary pulses are available at field rate: the positive-going one is used for field flyback blanking, by injection at the tube cathode as described earlier.

It's probably best to take the i.c. connections pin by pin, and describe the circuits connected to each one. Pin 1 has the frequency-determining resistive network for the line oscillator connected to it, with RV4 the line hold control. The line stability is very good, and once set the control should not need readjustment.

The output to the line driver stage appears at pin 2. Pin 3 is a supply input. Pins 4 and 5 have the line oscillator timing capacitor C18 connected across them. The flywheel sync reference pulse is fed in at pin 6. Pin 7 is connected to the horizontal a.f.c. line, and has the usual "flywheel" type network – C16, C17 and R19 – connected to it.

The flywheel sync comparison ramp is generated across C15, which is connected to pin 8. The sync separator input is pin 9, and in our case is fed with sync pulses from the first sync separator.

The noise gate circuit is connected to pin 10. D15 acts as a threshold diode. Normal amplitude video, negative-going, is applied to it via R21 and C13. The positive-going sync tips cause D15 to conduct only slightly once C13 has charged to a stable value. Large noise pulses drive D15 into heavy conduction however, and the input which results to pin 10 turns off the sync separator. By this means, spurious sync pulses are eliminated. The circuit works well under conditions of simulated interference. The whole circuit appears to be able to cope with interference signals in an efficient and rugged manner. Pin 11 is a general earth connection.

The field timing components are connected to pin 12. These consist of the capacitor C20 and R24, RV5 and R25. Different samples of the SN76544N require slightly different values of timing resistor, and to avoid having too high a value field hold control R24 is included. It can be shorted out if the total resistance is too high.

Pin 13 is another supply point, and in our circuit is

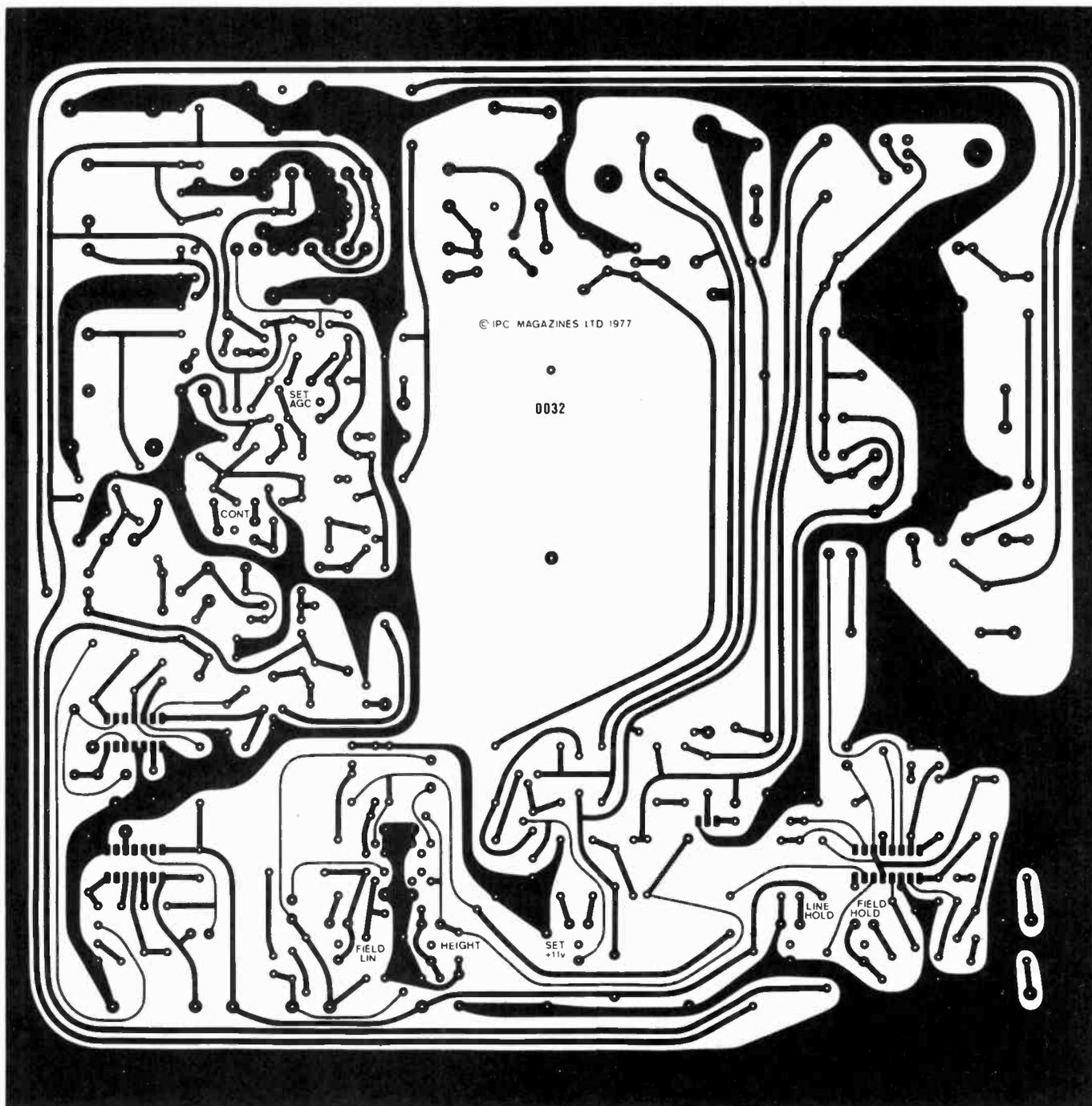


Fig. 7: Printed board print pattern (not to scale). The actual size is $11\frac{3}{4} \times 11\frac{3}{4}$ in.

connected directly to pin 3. The field blanking output, mentioned earlier, is taken from pin 14.

A negative-going pulse from pin 15 is used to discharge the field charging network.

Pin 16 is another earth connection.


Line Driver Stage

We shall now deal with the line driver stage Tr5. The output from pin 2 of IC105 is fed via the current limiter R28 to the base of Tr5, with C31 providing integration to clean up the waveform. Note that since we are using a driver transformer to match the low impedance of the output transistor's base-emitter junction, the flux in the driver transformer core will reverse as the driver stage turns on and off, thereby producing both turn-on and turn-off current for the output transistor. This latter is very


important for the correct operation of the line output stage. Note that turning *on* the driver stage produces the change of flux necessary to produce the turning *off* current for the output transistor.

The turn-on waveform from IC105 to the driver Tr5 has a steep edge. Also, Tr5, working into a mainly inductive load, produces steep transients at the instant of turning on.

The line output transistor acts as a switch, earthing pin 2 of the line output transformer when it switches on some way into the forward scan. It's switched off at the end of the line to give the flyback. The line output transistor does not turn off instantaneously however, taking about $10\mu\text{sec}$ to do so. This means that the line driver transistor has to be turned on about an inch before the end of the scan, at the right-hand side of the screen. The size of the transients developed across the line driver transformer is limited by the inclusion of the damping network R29/C22. The driver transistor is supplied from the 25V boost rail via R31, with C21

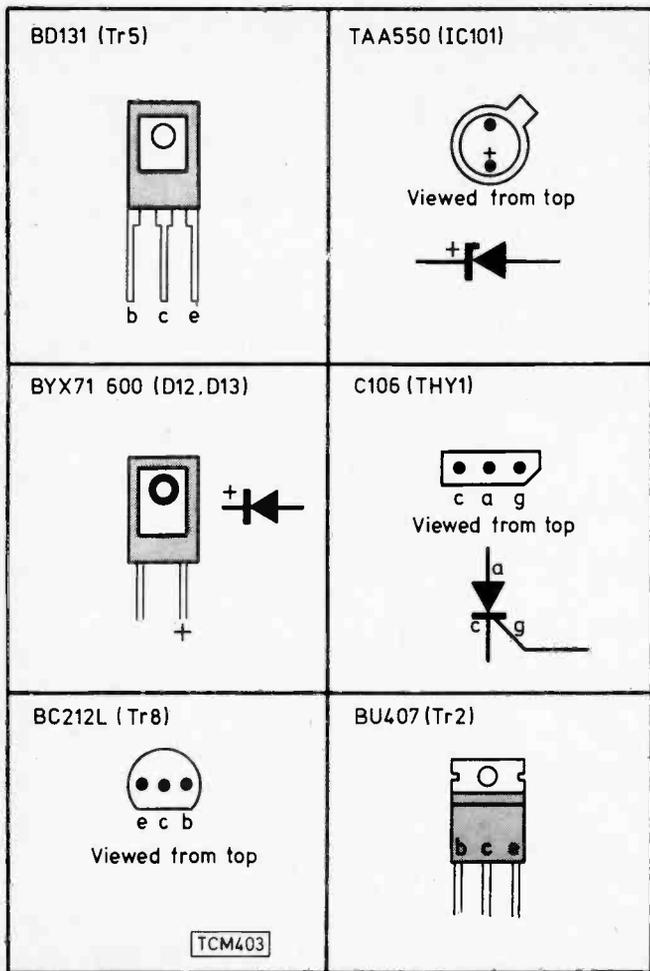

Rear view of Tuning Head

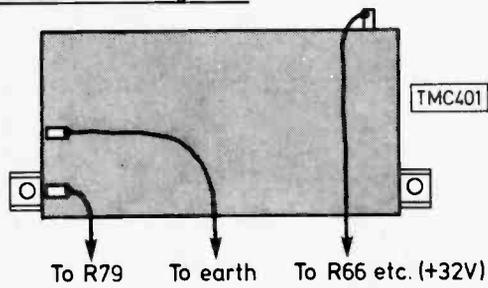

To C27, R41 etc. To R40, C25 etc.

Rear view of scan coils


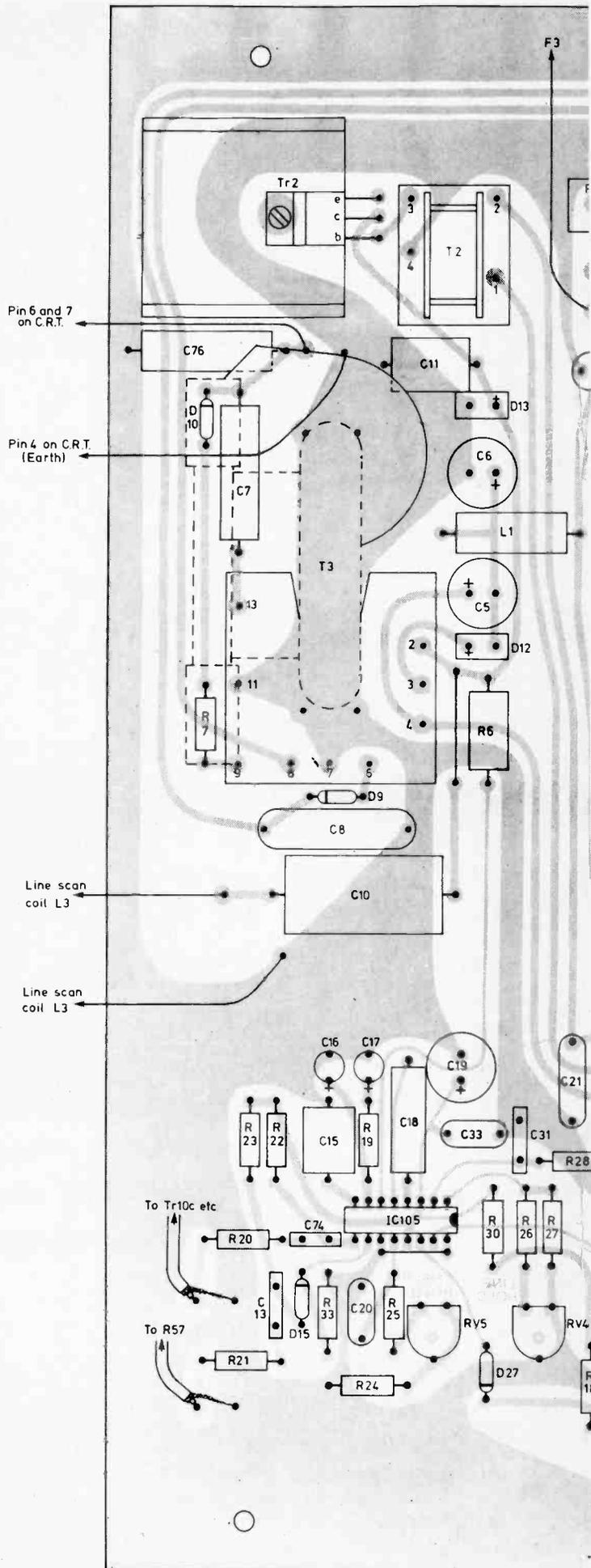
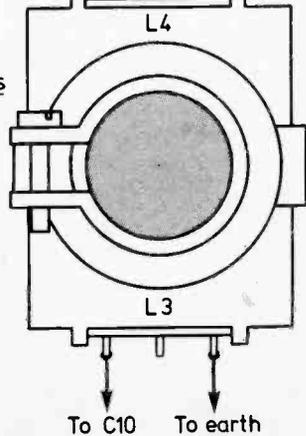


Fig. 8: Component layout and connections.

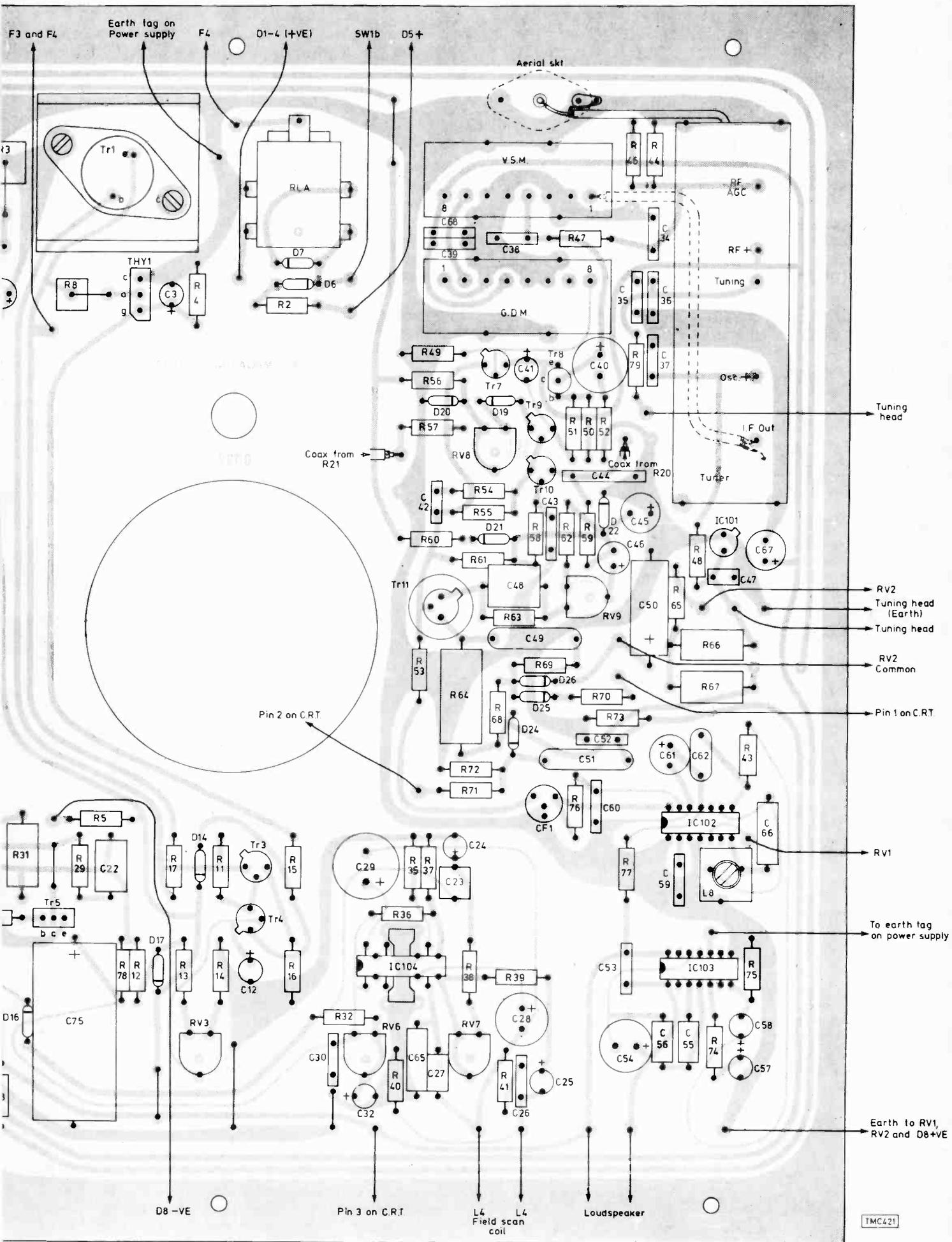

providing decoupling. We will deal with the line output stage itself later.

Field Timebase

The field output stage is built around the well-known TBA800 audio i.c. A field-frequency sawtooth voltage waveform is generated by charging C23 from the boost rail via RV6 and R32, and then discharging it through diode D16 and IC105. The cathode of D16 is normally at 8V: when the field drive pulse arrives from pin 15 of the SN76544N i.c. this voltage drops to near zero. Consequently C23 is discharged. The ratio of RV6 and R32 to R35 defines the charge which is developed across C23, and therefore the amplitude of the sawtooth voltage. R35 also provides scan correction by reducing the "aiming" voltage so that the curvature of the charging waveform is increased at the end of the scan. For the moment we are ignoring the linearity correction feedback which is applied to the junction of C23/C24.

The i.c. is fed from the 25V boost rail, with R78 and C75 providing filtering. Rhythmic expansion and contraction of the field scan was experienced before R78 was added. C30 provides h.f. decoupling to ensure stable i.c. operation.

During the forward field scan the scan coils appear predominantly resistive. The i.c. takes the sawtooth voltage generated across C23, amplifies it and delivers it to the scan coils from a low source impedance, thereby producing the scanning current.

During the field flyback the inductive component of the scan coils becomes dominant, due to the higher frequency compared to the forward scan. This inductance would introduce a large negative spike on the sawtooth voltage appearing across the scan coils. Since the coils are always connected to the i.c. however, the spike is clamped to earth, the remaining energy being dissipated in the i.c. This type of circuit is for obvious reasons called a "clamped" circuit. Its main disadvantage is that the i.c. has to dissipate this extra energy. Therefore with this type of circuit the power capability of the i.c. needs to be greater than if we could isolate the scan coils from the i.c. during the flyback.

One way of doing this is to place a transistor in series with the output from the i.c. and to arrange its bias so that it

switches off when the flyback pulse arrives. This leaves the coils open-circuited, so we need to put a capacitor across them (usually $2.2\mu\text{F}$, depending on the inductance of the coils) so that during the flyback the coils and the capacitor form a resonant circuit which defines the frequency (i.e. duration) of the flyback and consequently its amplitude. This is called an "unclamped" circuit. Its main disadvantage lies in the fact that it requires a medium power transistor, a rather bulky capacitor, plus several biasing components.

In this particular circuit the cost advantage of a clamped system using the TBA800 and the space saving compared to an unclamped system made the choice easy.

Most transistor field charging circuits differ slightly from the one used here in that C32 is normally absent, so that the combined resistance of R32 and RV6 (at any given setting) determine the charging rate. In this design, at high-resistance settings of RV6 C32 acts as a reservoir capacitor whose voltage is determined by RV6 in conjunction with the current drawn by the remainder of the circuit. The charging rate is therefore determined by R32. At low-resistance settings of RV6 C32 has little or no effect. Its purpose is to ensure that the charging voltage source is cleaned of any unwanted signals which may interfere with the charging circuit.

The output from the i.c., at pin 12, is coupled to the field scan coils by C29. C28 is a bootstrap capacitor which ensures that a symmetrical waveform is obtained from both "halves" of the quasi-complementary output stage within the i.c. The capacitors connected to pin 5 (C27 and C65) prevent the circuit from oscillating, by feeding back a phase-shifted signal at higher frequencies. R41 and C26 are also used to ensure stability, by compensating for the inductive nature of the coils.

A small sawtooth voltage is developed across R40 and is fed back to the inverting input of the i.c. via C25 and R39. These components define the closed-loop gain of the amplifier. Field linearity is corrected by feeding back part of this signal (adjusted by RV7) via R38 to the junction of C23/C24. As a result, a parabolic waveform is developed across C24. The combination of this parabola and the sawtooth voltage across C23 provides a scan-corrected drive waveform (necessary because of the wide deflection angle of the c.r.t.). The value of C23 is much less than that of C24: as a result, the charging current in C23 has little effect on the charging of C24. Further correction is provided by R35 as mentioned earlier.

Resistors R36 and R37 provide a bias voltage for pin 7 of the i.c. This puts a d.c. shift on the quiescent output voltage, which is normally sitting at half the supply voltage. This ensures that most of the scanning current is provided by the upper of the two output transistors in the i.c., thus allowing sufficient margin for the flyback pulse to be developed at the required amplitude.

Line Output Stage

The final section of the receiver to investigate is the line output stage. The stabilised 11V supply is fed to the line output stage via choke L1, which is decoupled by C6. The purpose of this arrangement is to prevent line-frequency pulses reaching the other parts of the receiver via the 11V rail. The supply reaches the transformer via the boost diode D12, which operates in exactly the same way as in a valved receiver, charging the boost reservoir capacitor C5 to produce a 25V supply for the line output stage and other sections of the receiver. There is also a shunt efficiency diode (D13) which we'll come to shortly.

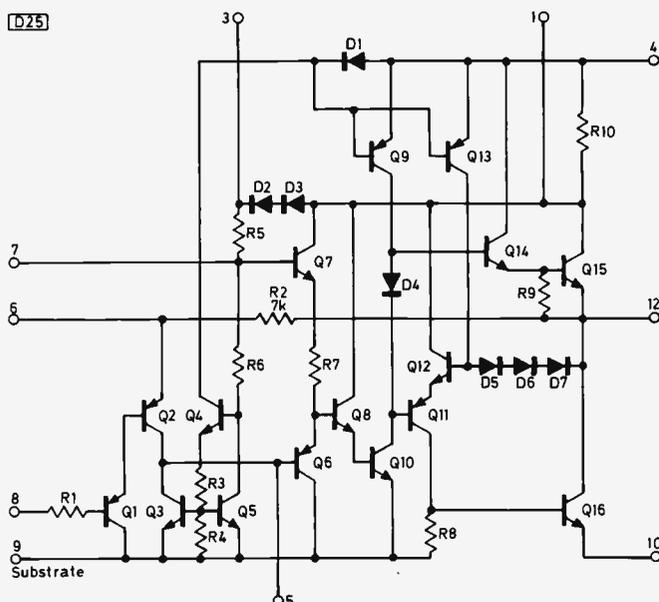


Fig 9: Internal circuit of the TBA800 i.c.

The BU407 silicon npn line output transistor acts as a switch, again in the conventional manner, connected across the flyback tuning capacitor C11. It's switched on some way into the forward line scan, at the end of the energy recovery period at the start of the scan.

We have to produce a sawtooth current (scan-corrected as in the case of the field scanning current) in the line scan coils, which at line frequency are predominantly inductive. It may not seem immediately obvious, but the scan coils are in effect connected in parallel with the primary winding (tags 2-4) of the line output transformer – the a.c. path is via T3 4-2, C10, L3, C6 and C5. The d.c. resistance of the transformer's primary winding is very low, and is less than that of the coils. When Tr2 is turned on, there is a d.c. path from the boost rail to chassis, via the transformer's primary winding and the transistor. Applying a voltage across an inductance (which, as we've pointed out, also includes the scan coils) results in a linear rise in current flow. This completes the scan and, when the spot is at the right-hand side of the screen, the line output transistor is switched off by the drive waveform provided by T2.

When Tr2 turns off, the flux in the scan coils and the transformer collapses, producing the familiar positive pulse voltage – the flyback pulse. The inductive components form a resonant circuit during this time in conjunction with the tuning capacitor C11. At the end of the pulse, the spot has returned to the left-hand side of the screen in order to commence the next line. The energy in the circuit during this half-cycle of oscillation is first stored in the tuning capacitor C11 and is then returned to the inductive components. The circuit tries to continue to oscillate, but as the voltage reverses so the boost diode D12 switches on, transferring energy to the boost capacitor C5. The clamping action of D12 and C5 result in a linear current decay through the coils and the transformer, so moving the scan from the left-hand side of the screen towards the centre. When about a third of the screen has been scanned in this way, Tr2 is switched on again. The current flow first falls to zero (middle of screen), then increases linearly in the opposite direction to complete the scan.

The efficiency diode D13 also conducts during the first part of the scan. It's included mainly to remove spurious line output transformer resonances however, contributing little in practice to the operation of the circuit. It could possibly be omitted, or the cheaper BYX55-350 used: the latter is not suitable for D12 however – the function of the boost diode is very rigorous and only the type specified should be used.

In order that the charge stored in the base of the line output transistor at the point when it's switched off can be efficiently removed, its base circuit requires a series inductance. This is built into the driver transformer in the form of the correct leakage inductance, providing a means of shifting the charge from the capacitance of the transistor to the inductance. By this means we avoid turning the transistor off slowly while its collector voltage is rising – a condition which would result in excessive dissipation and breakdown of the transistor.

C10 in series with the scanning coils provides scan correction as well as acting as a d.c. block. Scan correction is required in order to slow down the start and the finish of the scan, where for a given deflection angle there is a greater movement across the nearly flat face of the tube. C10 resonates with the inductance of the coils to superimpose a sinusoidal waveform upon the sawtooth.

A line linearity coil was included in an early prototype but, despite being correctly damped, seemed to produce ringing at the end of the scan. The linearity was found to be

perfectly satisfactory after removing it however so it was left out of the final circuit.

As we have seen, C11 tunes the circuit, determining the flyback time and hence the rate of change of flux in the transformer. This in turn determines the flyback pulse amplitude and hence the e.h.t. C64 contributes towards the tuning, but is also there to protect the line output transistor against pulses which may be developed across the coils in the event of a flashover in the tube.


Scan-derived Supplies

The line output transformer also provides various supplies for other sections of the receiver. The usual e.h.t. overwinding provides a positive pulse which is rectified by D11, charging the tube capacitance to the required e.h.t. potential. D9 charges C8 to approximately 95V to provide a supply for the video output transistor, the 32V stabiliser, etc. D10 charges C76 to approximately 550V for the c.r.t. first anode and focus electrodes. The negative-going pulse at tag 13 is coupled to this feed via C7 to provide line flyback blanking. C7 initially fulfilled both functions – blanking pulse coupling and reservoir for D10, but it was found that without C76 transformer resonances produced vertical striations across the screen.

Finally, winding 7-8 produces the -8V pulse required for a.g.c. gating and to produce a -5.6V supply in the video circuits.

In the concluding article next month we'll be giving constructional notes, the setting up procedure, and some fault finding advice.

CONTINUED NEXT MONTH

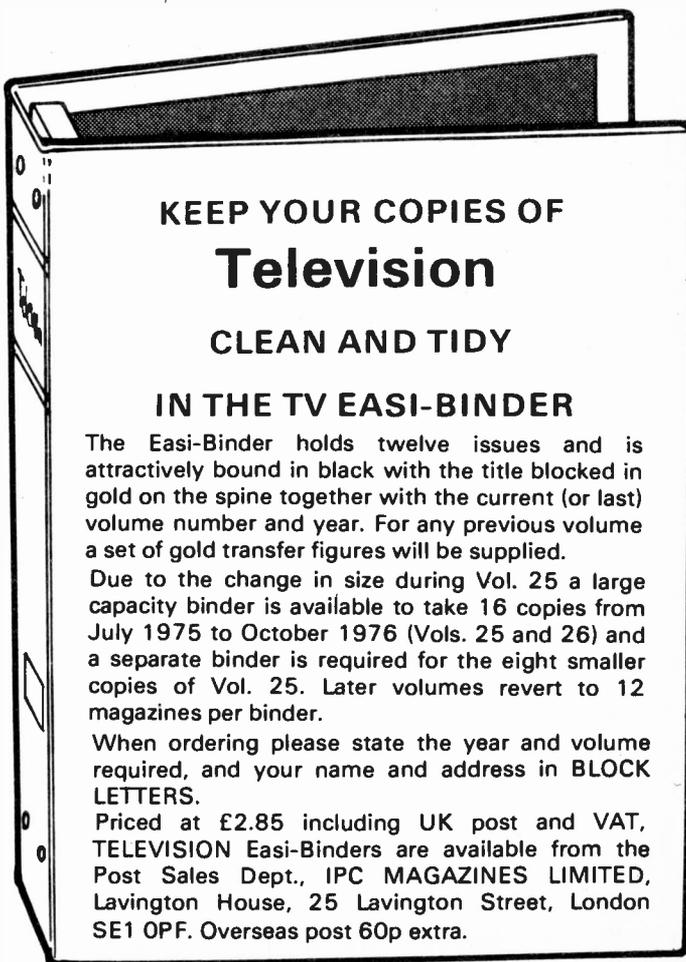

KEEP YOUR COPIES OF
Television
CLEAN AND TIDY
IN THE TV EASI-BINDER

The Easi-Binder holds twelve issues and is attractively bound in black with the title blocked in gold on the spine together with the current (or last) volume number and year. For any previous volume a set of gold transfer figures will be supplied.

Due to the change in size during Vol. 25 a large capacity binder is available to take 16 copies from July 1975 to October 1976 (Vols. 25 and 26) and a separate binder is required for the eight smaller copies of Vol. 25. Later volumes revert to 12 magazines per binder.

When ordering please state the year and volume required, and your name and address in **BLOCK LETTERS**.

Priced at £2.85 including UK post and VAT, TELEVISION Easi-Binders are available from the Post Sales Dept., IPC MAGAZINES LIMITED, Lavington House, 25 Lavington Street, London SE1 0PF. Overseas post 60p extra.

Servicing the Rank A823 Colour Chassis

Part 2

R. W. Thomson

THE timebase panel, type A803, is situated at the extreme right of the chassis and contains the sync separator, the field oscillator and output stages, the flywheel line sync and line oscillator stages and the line driver transistor. The latter drives the two series-connected BU105 line output transistors, which are housed within the can screening the line output transformer, the e.h.t. tripler and the focus unit. Fig. 4 shows the sync separator and line generator circuits.

Sync Circuit

5VT1 is the sync separator, which is biased during the scan period to a point just beyond cut-off. The arrival of a sync pulse drives 5VT1 into conduction, pulling the collector voltage down far enough to cut-off 5VT2 whose base is d.c. connected to the collector of 5VT1. The fast interruption of current through the primary of 5T1 causes this inductance to "ring", similar waveforms being generated in the secondary winding 5L2. 5C7 tunes the primary 5L1, and a sinewave of approximately 50V p-p is developed across the secondary 5L2 as a reference waveform for the discriminator diodes 5D2 and 5D3. The "hot" end of 5L2 is connected to the junction of these two diodes. When 5VT1 returns to the cut-off state, 5VT2 turns on again, taking diode 5D1 into conduction and damping any further oscillation in 5T1 until the next sync pulse arrives.

Positive and negative pulses from the line output transformer are fed to the outer ends of diodes 5D2/3. The resultant phase comparison of the two pulses with the sinewave from 5L2 creates a voltage across the balance control 5RV2 which, when correctly adjusted, supplies the correct voltage conditions for varicap diode 5D4.

Line Oscillator and Driver

Any change in the capacitance of 5D4 is multiplied by the reactance multiplier 5VT4, varying the reactance across 5T2, thus keeping the frequency and phase of the line oscillator in strict relationship with the sync pulses. The line oscillator transistor 5VT5 is driven hard on and off by the feedback pulses from 5C21, and in consequence a rectangular waveform appears across 5C23 to drive 5VT6/7. 5D5 protects the base-emitter junction of 5VT5, while 5D6 d.c. restores the waveform at the base of 5VT6. The emitter-follower 5VT6 drives the base of 5VT7 at low-impedance, ensuring that the latter is effectively bottomed by the drive pulse. This keeps the dissipation in 5VT7 low, hence the absence of a heatsink on this BD131, a transistor which usually runs very hot in other types of circuit.

Line Generator Faults

It will be noted that the primary of the driver transformer 6T1 is shunted by the damping network 5C25 and 5R35. This is essential to avoid the back-e.m.f. from the primary destroying 5VT7. These two components, particularly the

capacitor 5C25, should be checked in all cases of BD131 failure since this is a prime cause for the failure of this transistor, an event which is regularly encountered in these sets. The result is no e.h.t. of course, but since 5VT7 usually goes short-circuit the l.t. fuse 8F1 blows and there is no sound either – in fact nothing except the tube heater glowing. Also check the connections to 2R35/2C25 should 5VT7 have failed since a dry-joint here can be responsible. The BD131 can also go open-circuit of course, but this time the fuse doesn't fail.

The capacitors in this area can be troublesome. 5C14, 5C20, 5C21 and 5C23 have all been found responsible for no e.h.t. Intermittent loss of e.h.t. has been traced to 5C7, 5C17 and 5C18 – also 5D6, which can be checked with freezer. Loss of line sync can be caused by 5C14, 5C20 (also check whether it's dry-jointed), 5C21 and 5C23; also the flywheel sync discriminator diodes, usually 5D2. Intermittent loss of sync can be 5C17/18 or the line oscillator coil (5T2) former warping. Intermittent line jitter can be 5C17/18 again. Finally 5C22 can be responsible for bent verticals, maybe intermittent.

If false line lock is experienced with early sets, look at 5T1 and see whether it bears a green spot. If it doesn't, replacing it with a modified transformer will cure this fault. Later transformers had a green spot to indicate that the phase of the primary/secondary had been changed.

Line Output Stage

As with other early solid-state designs there are two line output transistors, connected in series in order to share the line flyback pulse between them. Loss of e.h.t. (with 8F3 blown) due to failure of the line output transistors is not common. When it does happen the cause is lack of balance between the two: if the base drive waveforms are not adjusted so that the two transistors switch off at the same time, the first one to switch off will have the full flyback pulse voltage across it. To prevent this, chokes 6L4 and 6L5 are included in the base drive circuits: one has a movable core which is adjusted to equalise the decay of the base currents and ensure that the two transistors switch off at the same instant. The way of doing this is described below – the method for later versions differs because with these both coils are adjustable.

The e.h.t. tripler and focus arrangements follow the normal lines in this type of chassis, but a point worth mentioning is the extremely high reliability of the line output transformer. The only one I've had to replace didn't fail of its own accord but due to a non-soldered joint that somehow missed the factory's inspection department. So in cases of no e.h.t., the line output transformer is the last thing to suspect.

In cases of no e.h.t. where 6R6 is of the fusible type check whether this has gone open-circuit. If so, check the line output transistors and the flyback tuning capacitors 6C5 and 6C6. The main cause of line output stage failure in early sets was these two polystyrene capacitors, so much so

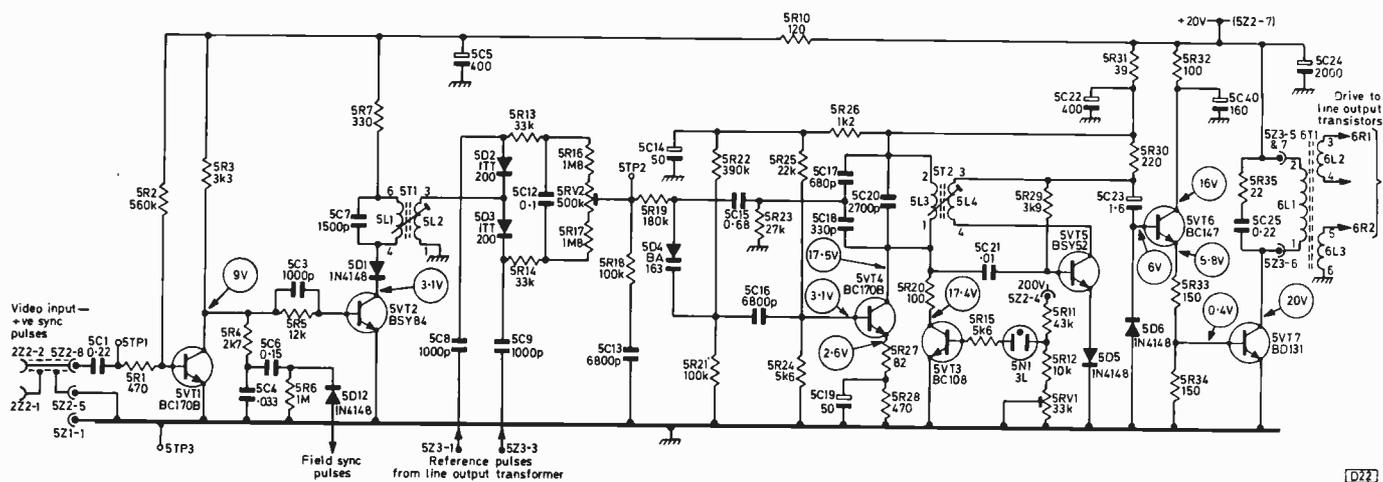


Fig. 4: Sync separator and line generator circuits. See Fig. 7 for modifications. 5TP4 (not shown) is a chassis connection.

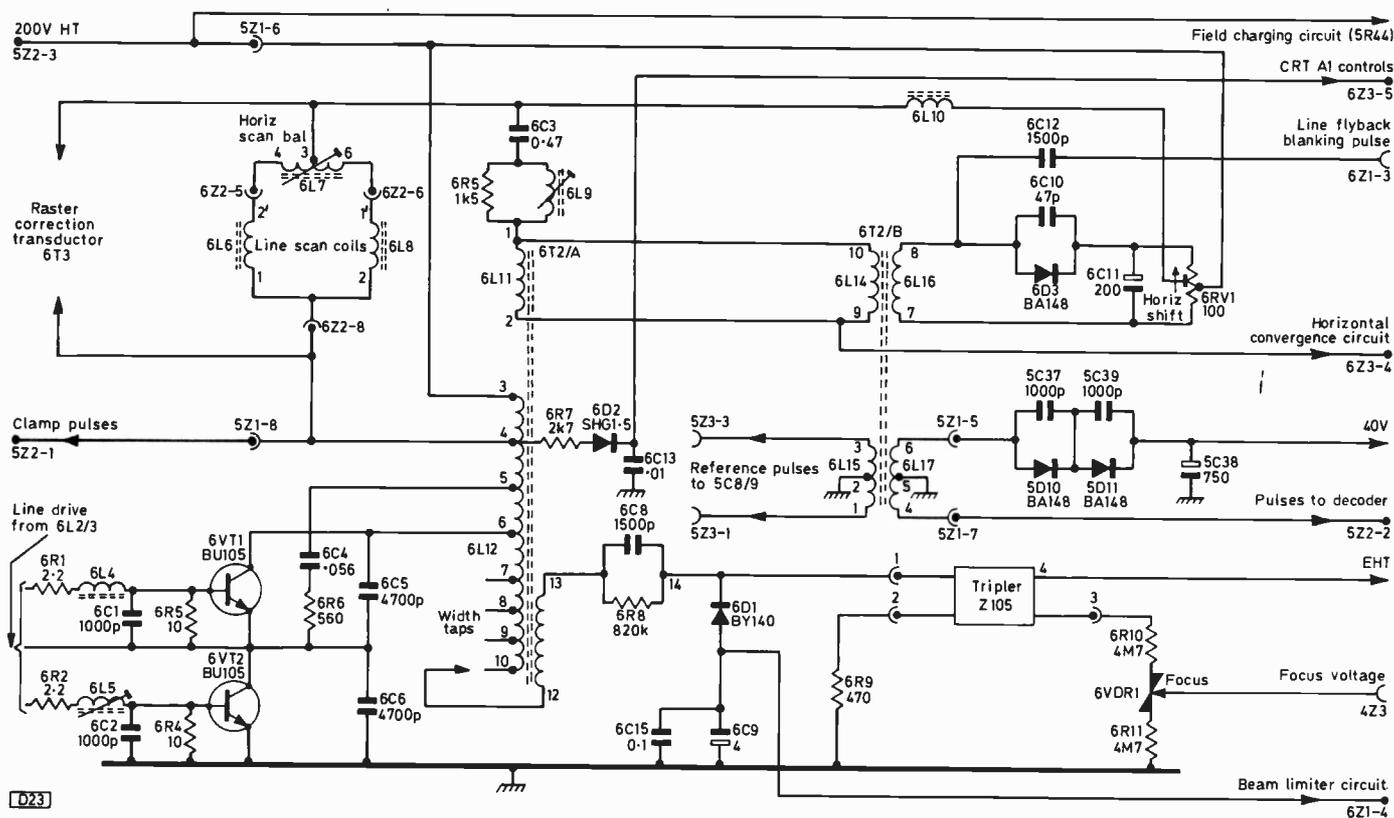


Fig. 5: Line output stage circuit. See Fig. 7 for modifications.

that many engineers automatically replaced them with alternative types before putting sets into service. The capacitors chosen were the tubular types supplied at the time by RS Components – listed as 800V a.c. buffer types. Subsequently Rank themselves started to use these capacitors. Although they are not close tolerance types, they worked and still do.

Adjustments

Balancing the line output transistors is, as you've now gathered, highly important. The writer checks this every time a receiver comes into the workshop, no matter for what reason. Perhaps this is the reason why the failure rate of line output transistors has been so low in the receivers I've handled. It doesn't take long to rebalance the stage, which *does* go out of balance over the years. The procedure for early versions is as follows:

- (1) Note the voltage at 8F3 on the power panel, then switch off the set.
- (2) Solder a 390kΩ resistor in parallel with 8R9. Switch on and set 8RV1 to give 100V at 8F3.
- (3) Tune the set to a test card or pattern generator or other stationary picture source, relock the line hold if necessary, and switch off again.
- (4) Swing the scan output panel out on its hinges, and connect the meter's negative lead to the pin carrying two red wires on the scan control panel. Connect the positive meter lead to the fuse 8F3. Switch on again and adjust 6L5 for minimum reading on the meter, starting with the 250/300V range and progressively changing downwards until on the 10V range. A reading of less than 3.5V should be obtained. This will be the point at which the circuit is working most efficiently, with both transistors driven equally.
- (5) Switch off and remove the meter leads and bridging

resistor. Check that 8R9 is a good, sound 390k Ω resistor. Replace the panel and the job's done.

If adequate width is obtainable with 200-210V at 8F3 all is well, but if the width is excessive or insufficient the tapping at tags 7, 8, 9 or 10 on the line output transformer should be selected for correct picture size in the horizontal direction, adjustment of field balancing being necessary if any change is made.

The line oscillator is easily adjusted by shorting pins 5TP2 and 4, then adjusting the core of 5L3/4 until a near stationary picture is obtained. 5RV2 should be adjusted to the centre-point between break-up in either direction, and if the displayed picture is not right in relation to the raster the core of 5T1 should be used to correct this.

Overvoltage Protection

Overvoltage protection of the line output transistors is provided to avoid over-running and possible destruction of these components, plus the avoidance of excessive e.h.t. This is done by having a normally non-conducting transistor 5VT3 shunted across the line oscillator coil 5L3. If the h.t. rises above a voltage preset by 5RV1, neon 5N1 strikes and 5VT3 switches on, effectively shorting 5L3. This stops the oscillator and switches off the output transistors. The circuit remains in this condition until the set is switched off and the neon is extinguished.

To set this stage accurately, two spare resistors, of 220k Ω and 270k Ω , should be connected in series across 5R11. A temporary short is then made across the 270k Ω resistor, the receiver switched on, and 5RV1 adjusted until the neon strikes. After switching the set off and removing the temporary short across the 270k Ω resistor, switch the set on again and the neon should, if properly set, remain unlit. If it does strike, either the procedure has been carried out too roughly or there is a fault in the circuit. The overvoltage circuit should be reset whenever the set h.t./e.h.t. control 8RV1 has been adjusted.

Note that a diode was added in place of 5R20 fairly early on in the life of the A823 chassis. This was to allow the use of low-gain transistors for 5VT3.

If the overvoltage neon keeps striking despite correct setting up, check the transistor 5VT3 and the value of 5R11. The neon itself can be faulty, striking to produce loss of raster a short while after switching on.

Modifications

Various modifications were made in the line output stage before the introduction of the later A823A version of the chassis. Fig. 7 shows the changes, which include adjustable coils in the drive to each line output transistor. The procedure for balancing the output transistors is in this case as follows:

- (1) Switch off, remove fuse 8F1 and fit an additional 390k Ω resistor in parallel with 8R9.
- (2) Switch on and reduce the h.t. to approximately 100V by means of 8RV1.
- (3) Switch off, replace 8F1 and set the cores of 6L4 and 6L5 to be flush with the top ends of their formers. Connect a meter on the 250V a.c. range across 6R6.
- (4) Switch on and rotate the core of 6L5 clockwise, by no more than three turns, for minimum reading on the meter (after three turns the reading will not change due to the coil inductance being at maximum). If the adjustment results in an increased reading on the meter, return the core to the flush position and then rotate the core of 6L4 inwards. When the minimum reading has been obtained with either

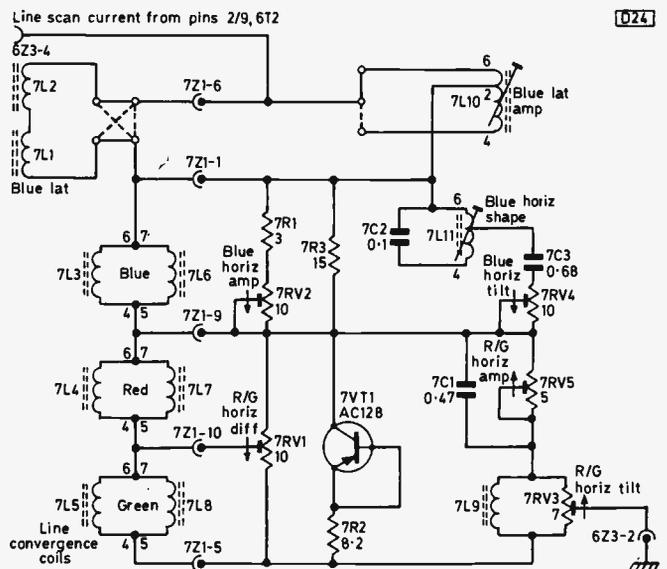


Fig. 6: Horizontal convergence circuit.

coil the other must then be adjusted to finally achieve balance. Rotate the cores slowly, because the minimum reading may be missed due to the damping in the meter. Reduce the meter range as adjustment proceeds, making the final adjustment on the 10V range.

(5) Return the h.t. voltage to normal by removing the added 390k Ω resistor and resetting 8RV1.

Fault Summary

It's possible for the line output stage to work after a fashion with only one of the line output transistors operational. This will result in an unusually large raster due to the low e.h.t. In addition to balancing the line output transistors, their base circuit series resistors 6R1/2 should be checked since they tend to change value. It's best to change line output transistors in pairs.

In addition to the line output transistors going short-circuit, several other components in the line output stage can cause the h.t. fuse 8F3 to blow. One is the tuning capacitors (6C5/6) previously mentioned, another is the c.r.t. first anode supply rectifier 6D2 and/or its reservoir capacitor 6C13 (in either case 6R7 will probably be burnt). Other causes are the horizontal shift circuit rectifier diode 6D3 and its reservoir capacitor 6C11, the scan-correction capacitor 6C3, shorting turns in the pincushion distortion correction transductor 6T3 (which may smoke!), and, not so common, short-circuit scan coils.

The tripler gives its share of trouble, from ballooning when the brightness control is advanced to no e.h.t. Depending on what's wrong within it, 6R9 may be found in a charred condition.


A not uncommon fault is a narrow picture (may be about 2in. wide), with smoke from the convergence board. The cause is the R/G horizontal tilt control 7RV3 on this board burning up – the line scan current returns to chassis via this control.

The old fault of striations across the screen is due to the usual cause – the linearity coil damping resistor, in this case 6R5. The striations are usually down the left-hand side of the screen only.

Focusing

Focus is effected in the now well-established manner, using a tapping on the tripler to supply a resistor chain

Fig. 7: Line driver and output stage modifications. In addition, 5R20 replaced by a 1N4148 diode, 5C43 (390pF) added from 5VT1 base to chassis, 6C9 changed to 5µF and 6D1 to type BY182, and 6L25 added between 6L17 pin 6 and 5Z1-5.

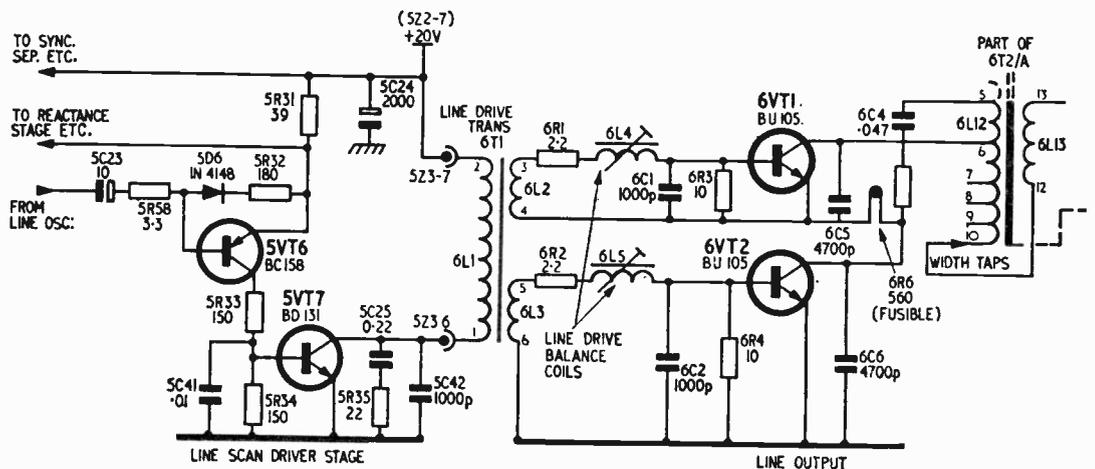

consisting of two 4.7MΩ resistors, 6R10 and 6R11, at either side of a variable focus unit comprising a VDR and a sliding contact tapping from it. The faults in this system are well-established too! If the top resistor in the chain (6R10) goes high, focus is lost and is outside the range of the control; whereas if the other one (6R11) gives up, the full

output from the tripler is allowed to reach the c.r.t. unattenuated, usually causing the spark gap 4SG3 to burst into flame and melt. Occasionally the series resistor 4R8 goes high, and this should always be checked when investigating focus faults.

TO BE CONTINUED

Service Notebook

G. R. Wilding

Fuse Failure

After working normally until switch off the previous evening, a Philips colour set fitted with the G8 chassis was found to be completely dead the next day. This is common enough of course, and is usually due to the switch-on surge blowing an elderly fuse or causing an ageing component in the power supply to break down and blow the fuse. Inspection showed that the 3.15A mains fuse was open-circuit and blackened internally, but the usual cause of this in these models, the BT106 thyristor rectifier, was o.k. No other fuses were blown, and there were no signs of any damaged components nor of any short-circuits, so we replaced the fuse and switched on. The result was a good picture and sound. The static and dynamic convergence were somewhat away from optimum however, and as a test card transmission had conveniently commenced we spent quite some time adjusting the magnets and presets.

As usual with a fault of this nature, we then switched the set off and on several times to see whether the new fuse might blow. We then switched off and replaced the back. On switching on again — no results! The mains fuse had blown, but as before there were no signs of a short in the BT106 or anywhere else. Since these thyristors do commonly break down after some years' service however we fitted a replacement. Some weeks later there has been no further call for service so it seems that the original must have been shorting intermittently.

Loss of Sound

One of the few stock faults on Decca hybrid colour receivers (series 10 and 30) is complete loss of sound from the PCL82 audio circuit. In most cases it will be found that the valve is running quite cool, due to the wirewound resistor R82 on the power supply panel being open-circuit.

The resistor is not of the same value, nor used for the same purpose, in the various versions of these chassis however. In the 17in. Model CS1730 and the 10 series chassis it's 12kΩ and supplies the pentode section's screen grid and the triode anode's 220kΩ anode load resistor. In the later 30 series chassis, with the vertically mounted tuner, R82 is 1.8kΩ and feeds the screen grid and both anodes. The best way to change the resistor is first to unclip the vertically mounted timebase panel, after which it will be found readily accessible on the horizontally mounted power supply panel.

Failure of this resistor is generally due to ageing, but in several cases I've found that after replacing it and retesting the sound quality soon deteriorated. The cause was a leak in the 0.1µF coupling capacitor (C82) between the two sections of the valve. As a result it was also necessary to change the valve and the pentode section's bias resistor.

Philips 210 Chassis

A dual-standard Philips monochrome set fitted with the 210 hybrid chassis produced a very elongated picture, especially in the top half of the screen. The main and top field linearity controls had only marginal effect, so clearly there was something wrong with the negative feedback loop used to provide field linearity. There are several components involved here, the source of the feedback being a tertiary winding on the field output transformer. Unfortunately the winding turned out to be open-circuit, necessitating a replacement transformer.

There are many tens of thousands of these sets still in service and, apart from the two droppers which develop open-circuit sections more than most, they've proved very reliable. The right-hand section of the left-hand dropper, R1544, is particularly vulnerable since it consists of many turns of fine wire to give a resistance of 2.85kΩ. It's used to drop the h.t. supply to a voltage suitable to feed the transistor circuits. In cases of an unmodulated raster with no sound therefore, first check R1544. I find it's worthwhile carrying exact replacements for both droppers: there's no temporary substitute possible for R1544, while there's insufficient room under the heat dissipating plate to satisfactorily mount those resistors which are usually so useful for bridging open-circuit dropper sections.

TV Servicing: Beginners Start Here...

Part 3

S. Simon

HAVING looked at how valves use a controlled flow of electrons to provide amplification, we will now take a look at the heart of a TV set, which is of course the cathode ray tube. This again makes use of a flow of electrons, but this time to provide a visual display. The idea is to find a material which will glow when struck by a beam of electrons, and to coat this on to the inside of the front of an evacuated glass envelope. This can be of any size, but as we are all familiar with domestic TV we need not describe the appearance of the front end since this is what we look at for a good deal of our lives (for better or worse). We can call this the display end.

Several things are necessary to obtain a readily identifiable picture on such a screen. First we need and have got a thing called persistence of vision. This simply means that we see light for a fraction of a second after it has actually gone. Thus we can "see" a complete image or picture which is actually made up of a quickly moving series of "pieces", be they dots, lines or one of those seaside pier peep shows of what the butler saw. In our case a concentrated beam of electrons is required to produce a glowing spot on the screen, and this spot must be moved rapidly across the screen to produce a line, then flying back to repeat the process a fraction lower down the screen and so on until the whole screen has been scanned.

This produces a nice bright plain raster of lines quickly enough to enable the process to be repeated with another set of lines interlaced between the first set, so that you have to look carefully in order to see the line structure. You may say why not make the spot bigger so that you cannot see the scanning lines. The snag with this is that detail would be lost. In other words, the definition would be impaired. So you must have a small spot and it must work overtime in order to produce a well defined picture.

Now bear in mind that to start with we are talking about a monochrome or black and white picture. The actual white depends upon the chemicals on the screen face and the number of electrons which hit them at any given moment. Thus by reducing the number of electrons we can obtain varying shades of grey down to black, where no electrons hit the screen at all. Just as in the valve, we heat a cathode which emits electrons which speed toward any electrode which is positive (lacking electrons). In this case however we require a concentrated spot, so we want an electrical "lens" which will converge the electron beam on a particular point at a particular time, while at the same time being varied in intensity to give the light output required from each part of the screen.

Instead of a control grid in the form of a wire mesh, we need a disc with a hole in it or a tube with a hole so that, as we vary the potential on this disc or tube with respect to the cathode, the number of electrons passing through the hole is controlled (see Fig. 1).

Then we need an accelerator to speed things up a bit (this

is normally called the first anode), a focusing electrode to get the beam down to the right size by the time it reaches the screen, and a final anode with a very high potential to really fling the electrons at the tube face. There is room for variation in the design of this gun assembly, but this is a very crude idea of the general pattern of events from the cathode to the tube face.

Deflection

At the same time that all this is going on, we must move the electron beam horizontally to produce the lines and more slowly from the top to the bottom. When the spot has been deflected to one side it has to flyback at a high speed as we said before. Also, when it reaches the bottom it must flyback quickly to the top. Thus we have a line flyback and and field or frame flyback. Obviously the spot would cause a visible line which is not required while flying back, and this is suppressed either by reducing the grid voltage at this time, raising the cathode voltage (which amounts to the same thing), or by turning off the first anode. You could call it flyback suppression or blanking if you will.

You could now say that we have left out the electrodes which deflect the spot horizontally and vertically. This is true, and indeed there are such electrodes in some types of tube used mainly in oscilloscopes (this is electrostatic deflection). We have enough to think about with our domestic TV however, so we will not go into specialist tubes. Our type of deflection is obtained electromagnetically, from a slab of coils on the tube neck secured well up to the bowl of the tube. The rising and falling currents through these scan coils produce electromagnetic fields which deflect the beam horizontally and vertically.

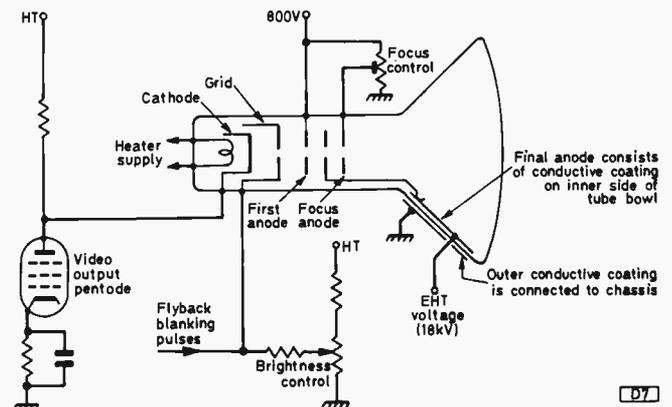


Fig. 1: The electrodes in a monochrome tube, and a simple drive circuit. The output pentode is direct coupled to the c.r.t.'s cathode, with the grid returned to the brightness control which sets the bias applied to the tube. It should be adjusted to give the correct black level: the brightness range will then be correct. The flyback blanking pulses are negative-going to cut off the beam at the grid.

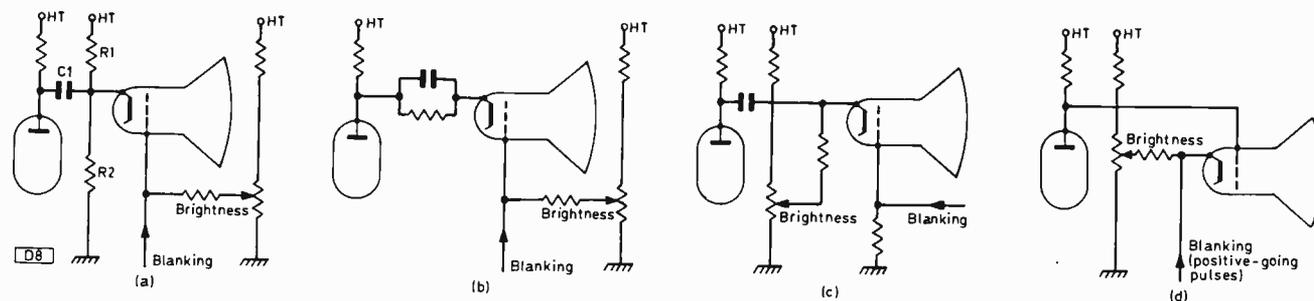


Fig. 2: Alternative tube drive arrangements to that shown in Fig. 1. (a) A.C. coupling (C1) to the cathode, with a fixed potential divider (R1/R2) to set the d.c. voltage level: the a.c. drive signal is superimposed on this d.c. level. The tube's bias is determined by R1/R2 in conjunction with the brightness control. (b) Partial a.c. coupling to the cathode. (c) A.C. cathode coupling, with the brightness control this time setting the d.c. voltage at the cathode and the grid used for blanking. When not being blanked, the grid is at chassis potential. (d) Applying the video drive signal to the grid, with the brightness control in the cathode circuit.

The current flowing must build up in a linear manner and collapse very rapidly, hence the use of a sawtooth waveform as mentioned last month.

Operating Voltages

We've mentioned the electrodes which make up the gun assembly, now what about voltages? The final anode must have a very high potential in order to get the electron beam moving at the high speed necessary. If this voltage falls, the beam will slow down and the picture will appear larger and lifeless. The final anode potential is called the e.h.t. or extra high tension voltage. A typical figure for a monochrome tube with a tube face diagonal of some 50 centimetres or 20in. is about 18kV or 18,000V. We shall see how this high voltage is obtained later.

Now voltages like this can jump about a bit, and this is why the e.h.t. connection is in an isolated position on the tube bulb with nothing but plain glass around it. This connection can retain a high voltage when the source is no longer working: it must be discharged therefore before any attempt is made to touch it. A lead or other conductor should be connected from the outer graphite coating to the cavity connector on the tube, preferably more than once. The reason for the retention of voltage at this point is the capacitance formed by the inner and outer graphite coatings of the tube bulb. This capacitance is necessary in order to smooth the e.h.t. which would otherwise have a fairly high-frequency ripple on it.

The first anode does not require such a high potential but is potent nevertheless. A figure of some 600V-1kV is fairly typical and this can be connected to the tube base, say to pin 3, without much risk of it jumping across to an adjacent pin.

There is often a spark gap between this (and other connections) and a chassis point however, in order to discharge any sudden increase of voltage (caused by say a spark from the final anode inside the tube). This spark gap is much narrower than the distance between the tube pins, so as to provide a more inviting path. The other side of the gap not only goes to a chassis point but also as a rule directly back to the outer coating of the tube, in order to provide the shortest route back to the source. This avoids the possibility of damage to some sensitive components which might not like the less direct chassis route. Readers may think that this is unnecessarily fussy, but bitter experience has shown that funny and nasty things can happen when the e.h.t. or a small part of it suddenly appears where it shouldn't.

The voltages at these anodes must be kept steady for good picture presentation, and obviously so should the

focus voltage. In order to vary the beam current (to provide our picture information) however there must be a corresponding variation of potential between the grid and the cathode. If the grid is held steady at say zero voltage – except for flyback blanking pulses – the cathode must be made to vary say above and below some 100V which is its bias voltage. Below this it will be approaching the grid voltage and therefore the screen will be brighter at that point (the grid will be less negative with respect to the cathode, and more electrons will pass). As the cathode is swung higher so the beam current is reduced as the grid is then more negative compared to the cathode. The picture at that moment becomes darker therefore. It's all a matter of timing you see.

The alternative is to keep the cathode at a steady voltage and apply the picture information voltage swings to the grid, and if you don't get the direction of the voltage swings right you have a lovely negative, i.e. black shirts and faces, with white suits and hair (except for blondes that is).

One method of driving the tube is shown in Fig. 1: some alternatives are shown in Fig. 2.

Tube Defects

Having had a brief look at the inside of the everyday monochrome tube we can discuss some of the things which stop it working properly. One sure way of stopping it working completely is to crack the glass. It is pretty difficult to crack the front. When this goes it really goes and you shouldn't be around when it does because thick, razor edged glass flying at high speed is pretty lethal.

There is a tendency for modern sets to be front heavy, and they don't need a lot of push therefore to make them fall forward. Normally this doesn't crack the face (don't bet on it though): instead, the tube is pushed violently back into the cabinet and it is the fragile base end which is broken. When this happens there is a violent rush of air into the tube, and this often destroys the coating on the inside of the tube face. You are then privileged to look through the front into the innards. This is all pretty obvious however so we won't dwell upon it.

Another less common defect is when an electrode (usually the grid or cathode) becomes internally disconnected. This usually results in a very dim raster which cannot be controlled. Some makes of tube seem, or seemed, to suffer from this defect more than others, and although attempts may be made to weld the connection by applying a high pulse voltage this approach is usually doomed to failure and the only answer is to have the tube rebuilt with a new gun assembly.

Far more common is loss of emission as the cathode

surface becomes coated with impurities which harden over the emitting surface. As a general rule this happens in tubes which do not possess the high degree of vacuum that others do. Anyone concerned with servicing over a period of years can specify the life expectancy of various makes of tube. He may well be wrong sometimes, but nine times out of ten he will be right. This all revolves around care in manufacture.

Whatever the merits of this however, it doesn't help when one is faced with a tube that is not very old but displays the classic symptoms of blurred and pearly whites which can be helped only by turning down the brightness to reduce the demand on the emitting ability of the cathode. The blurring occurs due to the lower vacuum leaving traces of gas which impede the electron beam and defocus it.

Several designs of tube reactivator have been described in these pages at various times, but basically there are two methods. One is simply to overrun the tube heater by say 20%, either by using a separate transformer or in some cases by connecting a resistor from the supply mains to one pin of the tube heater. The other involves applying a fairly high voltage to the grid for a very short period so that this attracts a fairly heavy current from the cathode. The idea is to "pulse" the cathode surface and uncover a fresh emitting surface. Although this does not help the lack of hardness of vacuum, i.e. the tube is still basically soft, the electron emission is improved however – perhaps for only a short period – and the picture quality is therefore improved.

A fault which can give rise to the same (or very similar) symptoms is a defective heater element, where part of it shorts across to another part thereby lowering its effective resistance and thus developing a correspondingly lower voltage. The visible sign, looking at the heater, is that it does not glow at its normal intensity. The net result is that it is no longer able to heat the cathode sufficiently and therefore the electron emission is drastically cut. A sharp tap on the tube neck will often clear the short, albeit for a short period (or a long one if you are lucky), and the picture then comes up just as bright and crisp as ever as the electron flow is restored. Again however the only sure remedy is tube replacement.

Once in a while we still encounter yet another fault which at one time was very common. This is a cathode to heater short-circuit. Since the heater is at a low voltage (quite often one of the heater pins is connected direct to chassis), the cathode is not only robbed of its picture information (assuming that the cathode and not the grid is fed with the video signal) but it also loses its positive bias and there is therefore no control of the electron beam, leaving a bright white raster if the e.h.t. supply can cope with this current demand. If it can't, the result could be a large defocused and dim raster with a dark patch in the centre, or simply no raster at all. Once again, a voltage check on the tube base will reveal the absence of cathode voltage.

There are several ways of coping with this, one being to change the method of tube bias and signal feed. We will not go into this however as it's of limited interest and there is a simpler alternative. This is to supply the heater from a separate transformer with a very low capacitance between its two windings. The primary winding must be suitable for 240V a.c. input, with the secondary wound to give the required tube heater voltage (say 6.3V, but with perhaps an extra tapping for a 20% boost should this be required). The existing heater leads are removed from the base and joined together to preserve the heater chain continuity. The transformer secondary is connected to the tube's heater pins and the cathode can then be directly connected or left as it is with a resistor (say 100kΩ) wired to the heater to keep the heater winding at the same voltage as the cathode. With the

voltage difference removed the short may no longer occur, but this is of little consequence since the low capacitance between the windings will not rob the cathode of its picture signals. An ordinary close-wound transformer has a large capacitance between its windings and this would have the same effect as wiring a capacitor from the cathode to chassis, i.e. it would short-circuit the varying picture signal voltages above a certain frequency and result in a very smeared and unacceptable picture. All this may be of limited interest as you may never encounter this type of fault, but it's as well to cross the tees and dot the eyes (oh dear) as it may help in the basic understanding of how tubes work and why they sometimes don't.

Colour Tubes

We don't wish to jump the gun as it were and get too complicated at this stage, but it's logical to have a brief look at colour tubes next. A short while ago only one type need have been described, but the scene has changed and there are now so many that we don't propose to attempt to describe the basics of them all.

Instead of the one gun required to scan the monochrome tube face, we need three separate cathodes, each to activate one basic primary-colour phosphor on the tube face (see Fig. 3). The phosphors (red, green and blue light emitting) can be deposited on the inside of the tube face either as groups of dots or in vertical stripes.

It's obvious that one particular cathode must have its beam directed to one particular colour only, and must not overlap on to another. This is no easy task. To put it another way, if we switch off two of the beams, say blue and green, the colour produced by the remaining beam must be red only, with no patches of impurities anywhere on the screen. To achieve this, steering (purity) magnets are provided to accurately direct the beams through certain holes or slots in a mask (the shadowmask) which is mounted just behind the screen. This ensures that only the correct phosphors are activated. Similar magnets are found on monochrome tubes, just behind the deflection coils, in order to move the picture vertically or horizontally. They are in the form of discs which can be rotated with respect to each other. Picture shifting has to be done by other means in colour receivers.

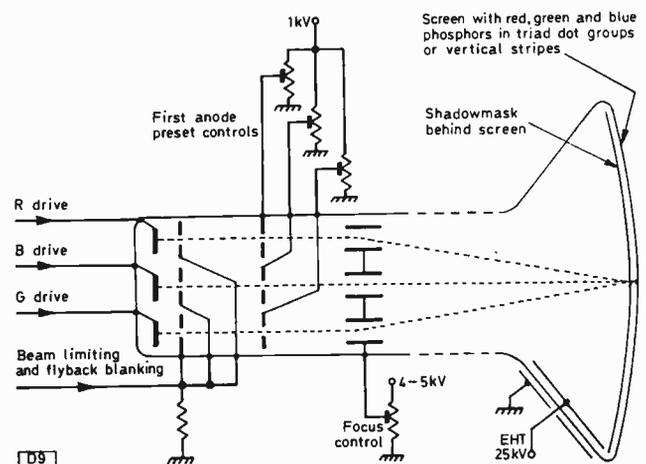


Fig. 3: Basic colour-tube drive arrangements, excluding the deflection and convergence systems. In some tubes the grids and the first anodes are connected together internally. Some smaller tubes operate with a lower focus voltage. In some earlier receiver designs video signals were applied to the cathodes and to the grids as well.

It will be clear that the electron beams in a colour tube have a much harder life since not all the electrons find their way through the holes in the shadowmask. In fact most of them hit the mask, their energy being expended in the form of heat. This is not only a waste but as the heat distorts the mask the problems are compounded. More can get through slots to activate vertical stripes than through holes to activate dots: that's why this newer type of tube has a higher light output although the detail is not quite so good.

Now this is only the start of the troubles. You cannot have three guns in exactly the same position. With the dot formation the guns are mounted in a triangular formation and for the stripe formation they are side by side horizontally. Since the guns are not in the same position, the beams will have to travel along different paths to reach different parts of the screen. Unless correction is applied, the resultant red, green and blue pictures will not be correctly superimposed. This means that there must be quite a bit of beam bending, slowing up and speeding up and other correction, in order to get reasonable convergence. In the case of the triad tube, which has been the norm until

recently, this is a formidable task needing many convergence controls and circuits. A good deal of interaction takes place, and complete convergence setting up is an operation that requires a lot of patience and a fair amount of experience if acceptable results are to be obtained. A glow of self satisfaction is well deserved when a good black and white picture can be displayed on the screen of a colour tube. We will delve a little deeper into this, and into grey-scale tracking etc., later in the series.

The more recent receivers with in-line gun tubes do not require such a high degree of correction and therefore life is a little easier although, as we shall see, it gets far more complicated in some other respects.

Colour tubes are heavier than monochrome ones and require more care in handling. They also have more external hardware, such as degaussing coils to demagnetise the shadowmask (otherwise the mask itself will deflect the electrons, which are supposed to pass through it), very carefully designed scan coils, and other devices varying according to the type of tube.

TO BE CONTINUED

Aerial Review: Plemi 103-element Array

Hugh Cocks

I recently had the opportunity to test a 103-element u.h.f. aerial made by the Dutch firm Plemi. The 103-element aerial consists of 25 multiple director units, a dipole, reflector and launch director.

Our test aerial covered channels 21 to 51, but the gain did not fall off until channel 57. It was a massive aerial indeed, being some 12ft. 3in. long. Various groups are available, matching the British groups A, B and C, plus a wideband version. Peak gain is claimed to be 18.9dB, which on our aerial occurred between channels 40 and 50. Due to the size of the array two support booms are used. The aerial is surprisingly light for its size however, due no doubt to the light gauge metal elements employed. The large grid-type reflector used results in an extremely good back-to-front ratio, and the aerial also has a very narrow beam width.

The results obtained with the aerial were very encouraging. With most of the aeriels tried here the French television transmissions from Le Havre on channel 40 are almost swamped by the vertically polarised signal from


Weymouth. The Plemi aerial gave the best results seen to date on this channel. Even on a test pole about 10ft. above ground the Channel Islands transmitters were pulled in at a similar strength to the main aerial at 35ft.

The aerial elements are pale green in colour and the reflector matt black. Once installed on the roof with the sun shining on it the aerial is a sight to behold!


Our only criticism is of the dipole insulation box which would tend to let water in over a long period. We would recommend thoroughly greasing the inside of the box and taping it over thoroughly outside in order to avoid the demon moisture. But I would certainly advise anyone in the market for a good high-gain aerial to consider this new product.

Pricewise the aerial competes well with UK produced aeriels. Plemi also produce smaller versions of the aerial. Those interested can obtain further details from: Eastern Antennae, 87 Norwich Road, Ipswich, Suffolk IP1 2PR.

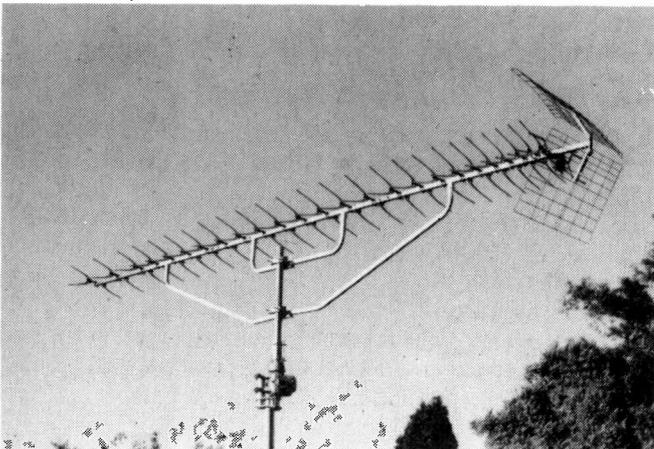The Plemi aerial range has a five-year guarantee against faulty materials/workmanship and normal weather hazards.



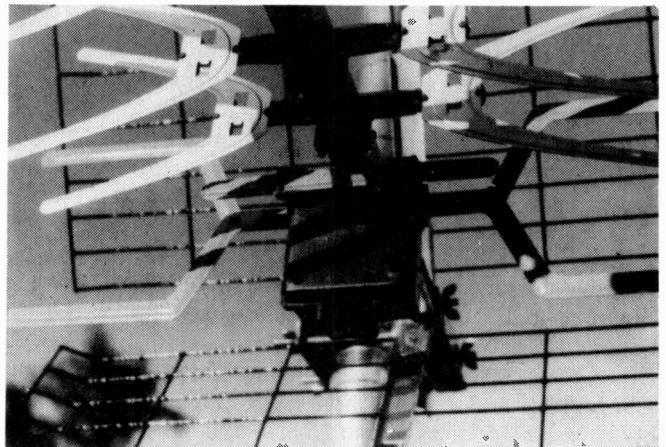The Plemi 103-element u.h.f. aerial has 25 multiple directors, a launch director, X-dipole and reflector.



Close up view of the dipole and the feeder connection box. The launch director is just in front of the dipole.

LONG-DISTANCE TELEVISION

ROGER BUNNEY

SEPTEMBER is traditionally good for tropospheric reception. This year there was a good opening into central Europe from the 10th to the 14th. A relatively static high pressure system provided the right conditions, and from reports coming in it seems that signals were mainly from southerly and south-eastern directions.

Several East Anglian DXers have reported reception from Switzerland and Austria. Clive Athowe logged the Pfander ORF (Austria) transmitter on Band III and at u.h.f. on the 13th, along with many Swiss stations. The signals continued on the 14th, with yet more Swiss ones and DFF (East Germany). David Martin (Dorset) and High Cocks (Devon) had similar successes, but with reception from RTVE (Spain) at both v.h.f. and u.h.f. Hugh logged an RTVE transmitter on ch. E6 – the only high-powered one below 40°! Hugh seems ideally placed for Spanish reception, since he received the ch. E3 and E4 transmitters on an omnidirectional Band I array. David logged RTVE on the 11th, during the morning, on chs. E3, 4, 5, 7 and 11, followed by strong Swiss u.h.f. signals.

It's interesting that W. Germany, usually a good source of strong signals during a tropospheric opening, was generally absent, all reception of consequence coming from the south/south east following the prevailing isobar pattern. David is now using a u.h.f. double-backfire array which was previously on my own mast. It was erected at Shaftesbury to reduce the effects of a new source of interference – a nearby relay operating in the group A section of the u.h.f. spectrum. The side-stacked backfire is working very well, giving deep lobes so that weak signals can be received and also providing a wide capture area. This is often a greater asset than using a single long, high-gain Yagi, with its high gain concentrated in a reduced capture area.

RTVE ch. E4 was logged here at Romsey on the 10th, a difficult signal for me since any tropospheric signals from this direction are effectively screened by the Abbey, its recently reroofed roof providing an efficient signal screen! Although I carefully tuned over Band III and the u.h.f. channels on the 11th there was no sign of RTVE, but several W. German Band III and u.h.f. signals were noted. On the 14th there were strong TDF (France) Band III and u.h.f. signals, giving the usual identification problems.

There was little Sporadic E reception during the month. TSS (Russia) and MTV (Hungary) chs. R1 and R2 were present on the 3rd, while TSS was also present on the 7th and SR (Sweden) ch. E2 on the 8th.

Reception here is at present being disrupted due to re-arrangement and construction of a DX-TV room. This should ease domestic problems, and I hope to be operational again within three weeks. Monitoring during the early morning period has ceased until the new lines are ready.

News Items

Satellites: The first OTS 12GHz experimental satellite was unfortunately destroyed on take-off. The replacement isn't due to be launched until early Spring.

Poland: The Krakow TV centre is now producing SECAM programmes – previously only Warsaw provided network colour. It is anticipated that most of the country will have TVP-2 coverage by 1980.

Spain: RTVE is extending its u.h.f. coverage with four new transmitters. A high-powered transmitter at Mijas will come into service in 1978 to relay programmes to Southern Spain and North Africa.

Bahamas: Radio Bahamas will be opening a new station (on ch. A13, system M) at Nassau in Autumn 1977 to establish the first colour service in this area. Its coverage will include the neighbouring islands of New Providence and part of the Family Islands. RCA have been awarded the main contract for studio equipment through to the transmitters.

In Brief . . .

Caen, TF1 France on ch. F2 has been noted using 625-line tests with PAL colour information . . . Sendz Components (2, Wood Grange Close, Thorpe Bay, Essex) is selling a brand new varicap v.h.f. tuner of Telefunken origin with coverage from below ch. E2 to approximately 105MHz in Band I and with a Band III coverage from 140-230MHz. These were apparently made for the Australian market. This is obviously the answer for DXing and for coverage of the elusive Band II TV spectrum and chs. R3, 4, 5 and IC. Previously coverage of Band II has been either via an upconverter or a Mullard ELC2000S tuner. The price is around £1.50 + VAT. Apart from a 12V supply, the gain control feed needs 8V for maximum gain down to 3V. I expect these will soon sell out!

New Dutch Programme Network

The NOS-3 network is to commence in 1980. The channel allocations (thanks Gosta V.D. Linden) are as follows:

Goes ch. E7 (formally NOS-1)	Smilde ch. E44 (1000kw)
Lopik ch. 30 (1000kw erp)	Arnhem ch. 58
Roermond ch. 34	Markelo ch. 51
Wieringermeer ch. 42.	


There are also plans for a large number of relays for both the NOS-3 service and the existing NOS-2 network, mainly low powered except for Den Helder on ch. E10.

Algeria

Pierre Godou (Rennes) has kindly sent us information on



**WHEN
PERFORMANCE MATTERS!**

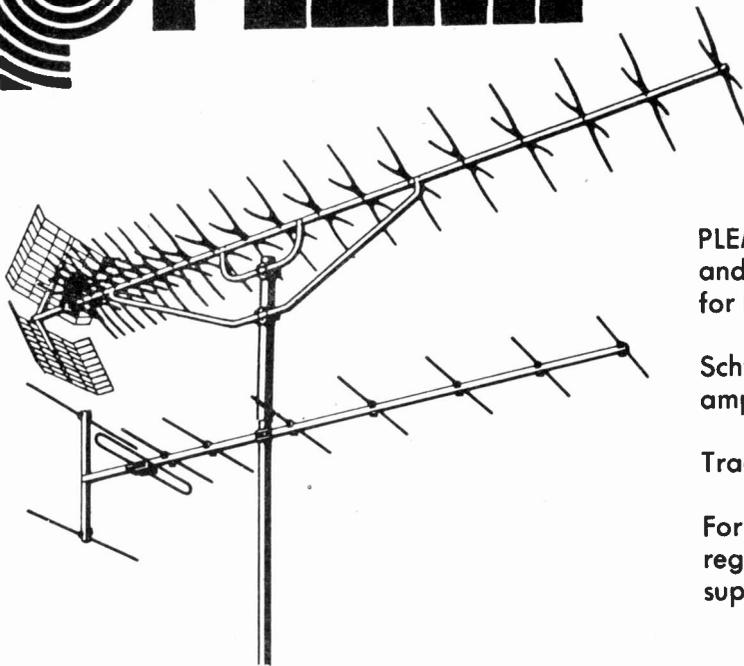

PLEMI 'color cross' UHF Tv, Bands I & III, and FM stereo aeriels – all guaranteed for FIVE YEARS!

Schwaiger mast-head & distribution amplifiers and accessories.

Trade & Wholesale enquiries welcome.


For full literature, prices, and details of regional stockists and Mail Order suppliers contact the UK distributor:

**EASTERN 87 Norwich Road, Ipswich, Suffolk IP1 2PR
ANTENNAE Tel: 0473 217217**

CATRONICS FOR ALL THE LATEST COMPONENTS

for the **Television**

TELETEXT DECODER

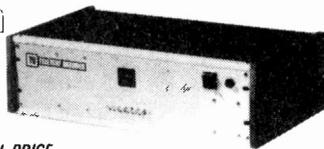

SPECIAL PRICE
COMPLETE KIT

£215

+ £2 P & P.

★ ALL THESE
SPECIAL PRICES
INCLUDE VAT!

★ All the kits for this project are now available from CATRONICS all backed by Catronics Ltd. exclusive FOUR-STAR SERVICE.

Catronics Guaranteed kits contain all components required for the specific unit, INCLUDING A REPRINT OF THE ORIGINAL ARTICLE, plus the PCB as indicated.

Kit	Incl. PCB	Less PCB	P & P
POWER SUPPLY UNIT	£26.75	£23.80	£1.00
INPUT LOGIC CARD	£25.85	£16.05	20p
MEMORY CARD	£30.80	£22.90	20p
7 sockets for 2102 i.c.s. – extra £1.60			
DISPLAY CARD	£34.65	£26.65	20p
MOTHERBOARD etc. ex. mod.	£29.75	£24.50	20p
MODULATOR Pre-aligned and tested		£17.00	20p
I.F. CARD	£34.00	£28.00	20p
CABINET – Ready Punched		£21.30	£1.25

Components are also available separately:

Thumbwheel Switch – £7.00; Push Button Switch Assy – £4.20; 32 way Edge Connector – £1.95; 47K 20T Cermet Pot – £1.10; ELC1043/05 Tuner – £9.15; SAW Filter – £2.85; SFE6 OMA Filter – 93p; BYZ13 – 70p; 1A Bridge Rectifier – 40p; 10,000mfd 16V capacitor – £2.75; Illuminated Mains Switch – £1.40; Mains Transformer – £6.25 (+ £1.00 p & p); 7805 – £1.50; 7812 – £1.50; 2102 – £2.65; 74S262N – £17.00. Please add minimum 20p P & P.

See Price List for details of other components, incl. 7400 series i.c.s.



CATRONICS LTD. (Dept. 762),
COMMUNICATIONS HOUSE,
20, WALLINGTON SQUARE,
WALLINGTON, SURREY SM6 8RG.
Telephone: 01-669 6700.

SYSTEMS PLANNED FOR TV & FM SHOP DISPLAYS,
HOUSE SYSTEMS, SMALL BLOCKS OF FLATS.
ALL PARTS SUPPLIED (PARTS EXCHANGEABLE)
10% OFF ALL AERIALS, ACCESSORIES & ROTATORS.
AFTER SALES ADVICE – ORDER OVER £25
CARRIAGE FREE.

A really personalised
mail order service but
S.A.E. PLEASE!

Stockists of:
FUBA TV & FM aeriels also
AM/FM aeriels (W. Germany)
PLEMI TV aeriels (Holland)
JAYBEAM TV & FM aeriels
ANTIFERENCE TV & FM aeriels
UKW FM aeriels (E. Germany)



The amazing PLEMI TV aeriels
now stocked. High gain,
anodised, yet no dearer than
home produce.

ASTRA (D.I.Y.) AERIALS

GENUINE D.I.Y. AERIAL SPECIALISTS FOR ALL BAND TV RECEPTION
ALSO FM/stereo RECEPTION: AM TOO
Backed by 23 years' practical aerial rigging experience

We can advise you of aeriels needed for the entire U.K. Give us five minutes and we can advise you on which Band, which Channel, which aerial for any country in the world. We stock all ancillary parts to match. Also amplifiers to suit all Bands.

AERIALS & PARTS EXCHANGEABLE UNTIL SATISFIED.
WHOLESALE SUPPLIERS TO THE TV & FM TRADE.

Over 2,500 aeriels stocked: All Bands: also Set-Tops: Masts: Lashings: Wall Brackets: Rotators: Televertas: Diplexers & Triplexers (specially imported) for mixing variously. Bands 1, 2, 3, 4 and 5: Distribution and mast-head amplifiers: 2/3/4 way splitters: Padded outlets: Directional splitters: all types coax cable: quality 300 ohm cable.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON



Nr. Gloster Pub & Garage
Open 9.30-5.30 MON-SAT
Open lunchtime

Tel: 01-684 4300

01-684 5262

24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY

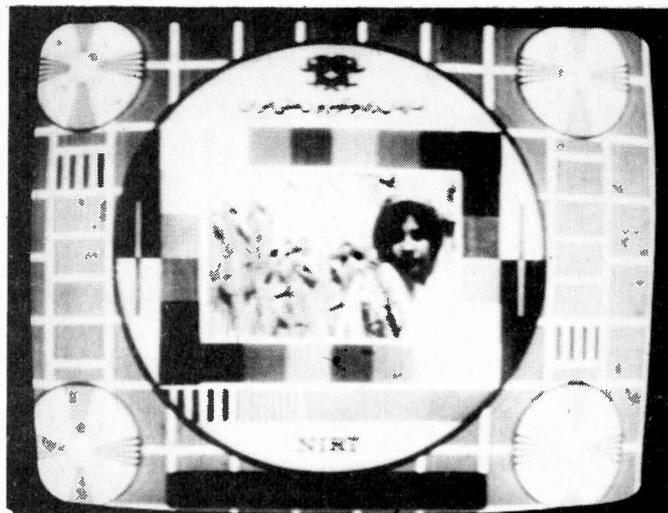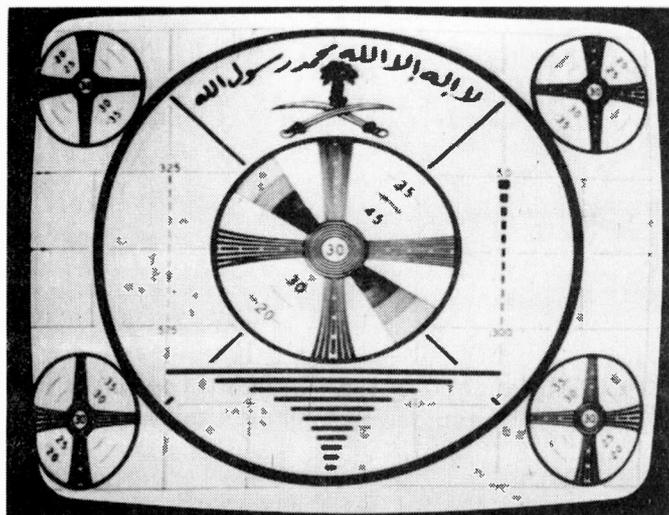

Further test cards received by Allan Latham during his recent visit to Abu Dhabi. Left, the Dahrn ch. A2 station HZ22 Indian Head test card – with arabic identification replacing the Indian Head. Right, the NIRT, Iran test card used on chs. E8, E3 and E4.

the Algerian TV Service (RTA). System B is used, in Band III, and colour tests are being made with both SECAM and PAL. Almost all the country is served, helped in part by a satellite telecommunications network based on an Atlantic Intelsat leased channel. More relays have brought TV to the south of the country. RTA transmits 65 hours of programmes a week, in both Arabic and French. At the end of 1975 410,000 TV receivers were in use.

FM Video Demodulator

Several enthusiasts had great success with the video signals from the ATS-6 Indian satellite in late 1975/76. In the June 1976 column we published a circuit using the Signetics NE561B phase-locked loop i.c. as built by Steven Birkill. Ian Smith has now sent us information derived from a Signetics application note. This enables the operating frequency of the device to be extended to 60MHz. The modification – see Fig. 1 (a) – is relatively simple, consisting of two 10kΩ resistors from pins 2 and 3 to chassis. Adding a further 5kΩ potentiometer as shown in Fig. 1 (b) provides a degree of fine tuning. Although there are at present no suitable satellite transmissions available, the PLL may form the basis of a 12GHz f.m. video demodulator when experimental transmissions start in 1980.

From our Correspondents . . .

Robin Williams (Stratford-upon-Avon) has been extremely active this Summer, using a Sony colour Model KV1800UB and the upconverter featured in the September

1976 issue. He has received signals from most of Europe via Sporadic E, his aerial being a simple ch. B4 two-element one. He also uses the surplus Plessey “radar” i.c. amplifier. He’s also received various W. German tropospheric Band IV signals. This is encouraging since Robin lives relatively deep inland and uses no masthead amplification at u.h.f. A useful tip from Robin is that tourist areas often sell foreign newspapers which contain details of overseas television programmes and timings.

Desmond Hellier has been receiving DX-TV signals at his Hampstead flat using a modified Bush Model TV125 and a Pye Model 40F. We have sent modification notes to Desmond since the latter receiver tended to have poor field lock on weak signals. Desmond suggests (and we agree) that it would be a good idea for enthusiasts to send in details of any receivers they have modified as alternatives to the popular Bush TV125 series.

A. Jaques (Urmston, Manchester), a licensed radio amateur (G3PTD, formally G6ACW/T), has suggested that it may be possible for DX-TV enthusiasts to receive the various amateur transmissions (TV) in the 433-450MHz band either by tuning to the l.f. end of a conventional u.h.f. tuner or by slight adjustment of the tuned circuits. He says that TV Hams will be pleased to receive reception reports from DX-TV enthusiasts. If you decide to cover this band do not adjust the normal DX tuner but obtain another for realignment.

Brian Fitch (Scarborough) tells us that Swaziland is to commence TV transmissions next year from its capital town Mbabane. Either system B or I will be used, with mainly European equipment. Programmes will consist of local productions and British film/tape.

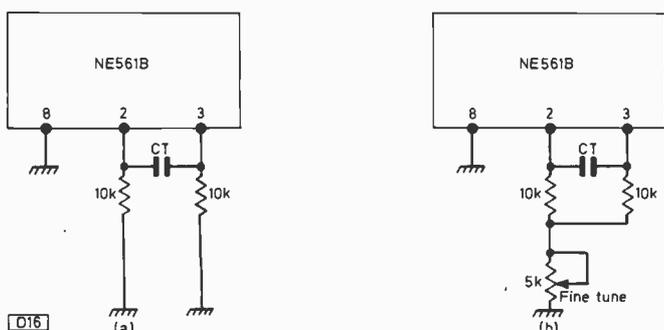


Fig. 1: Modifications to extend the operating frequency of the NE561B f.m. video demodulator circuit to 60MHz.

Auroral Reception

In a previous column I gave details of F2 propagation/reception since, with increasing sunspot activity as we continue along the upward part of the new sunspot cycle, there is an increasing chance of this. Such propagation depends on solar radiation, and can give reception over greatly enhanced distances. An associated phenomenon consists of an aurora, which produces variations in signal propagation and shows up visually as a coloured display in the night sky towards the north – appropriately known as the “Northern Lights” – or the south in the southern hemisphere. The display consists of a

continually changing pattern of rays in colours from red to green, white and yellow, and from isolated rays to "great bundles of different colours".

The visual effect is as often as not obscured by cloud, but the secondary effect of v.h.f. back scatter can make reception possible up to Band III. The phenomenon is caused by solar storms, as a result of which a steady flow of ionised particles spiral outwards from the sun. They take about 24 hours to reach the Earth, and when they arrive they concentrate at the magnetic poles, causing severe disturbance to the Earth's outer radiation belts.

An aurora can occur at any time during a sunspot cycle, but there's a greater possibility of one during the more active periods, particularly at the equinoxes when the Sun's poles tilt towards the Earth. The equinoxes occur every six months, in early April and early October.



A characteristic of auroral openings is the two-phase effect, with an afternoon period and a late evening one. Either period may be the stronger, or both may be similar. Within each period there may be a tendency for the reception distance to gradually decrease and then increase again.

Unfortunately auroral reception gives poor quality signals. Due to the continually fluctuating state of the auroral currents, the signal may be diffused and reflected from several points, resulting in a poor quality video signal with multiple images and hum. There has been successful

auroral reception in the UK from Finland and Sweden and stations in W. Europe however. The aerial must be pointed towards the north, $\pm 45^\circ$.

Reception in Band I is easiest, and we've had one report in the past of transatlantic reception of a ch. A2 signal with the aerial pointing toward the north west. An intense aurora may allow propagation in Band III. Carefully monitoring the sound channel (a.m. if possible) should then reveal numerous rumbling and "zipping" noises. If an aurora is suspected at midnight when most European stations are off air, check carefully to the north west for possible reception of a Canadian signal.

The signals during an aurora sometimes tend to be concentrated in a particular direction rather than being a general, diffused back scatter from NW through to NE. With the aerial pointing north, a station to the east of the receiving site may be present. The main factor in successful auroral reception is vigilance: during peak periods, keep a careful check for such propagation by monitoring an empty local channel for evidence of the Scottish BBC-1 v.h.f. stations or rumbling noises as just mentioned. A check on the sun itself will reveal whether there are active areas, but we must again emphasize that instant eye damage will be caused by direct viewing with the naked eye or through a telescope or binoculars. If you can mount a telescope on a tripod, you can project the sun on to a white card in order to observe its surface clearly and safely.

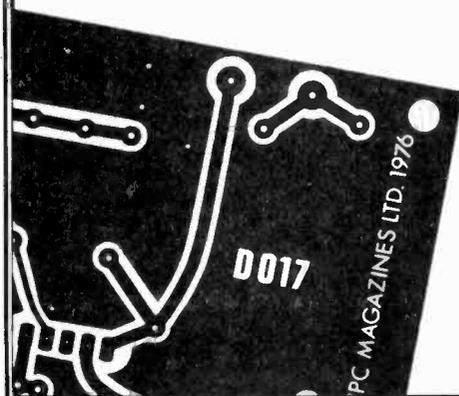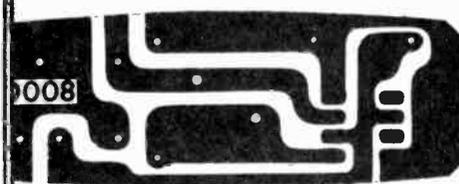

TELEVISION

READERS PCB SERVICE

Issue	Project	Ref. no.	Price
April/May 1976	Video Effects Generator	DN0799A	£4.25
April/May 1976	Video Effects Generator-Fader only	DN0780A	£1.58
July 1976	Opto-coupled Audio Extractor	D001	£1.35
November 1976	Ultrasonic Remote Control	D007/D008	£2.95 per set
December 1976	IC Sound Circuits for the Constructor	D009	£1.25
		D017	£1.25
		D018	
Jan/Feb/March 1977	TV Pattern Generator	{ + u.h.f. mod. board }	£3.90 per set
March 1977	Teletext Decoder Power Supply	D022	£2.95
May 1977	Teletext Decoder Input Logic	D011	£9.80
May 1977	Single-chip SPG	D030	£3.00
June 1977	Wideband Signal Injector	D031	£0.65
June 1977	Teletext Decoder Memory	D012	£7.90
July/Aug 1977	Teletext Decoder Display	D013	£8.00
July/Aug 1977	TV Games in Colour	D034	£3.80
August 1977	Logic State Checker	D038	£1.50
September 1977	Teletext Decoder Switch Board	D021	£1.25
September 1977	Teletext Decoder Mother Board	D027	£4.00
September 1977	Touch Tuning System	D051/D052	£4.00 per set
October 1977	Teletext Decoder IF Board	D041	£6.00
December 1977	Monochrome Portable Receiver	D032	£15.00

All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned. Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.

To:- Readers' PCB Services Ltd. (TV), P.O. Box 11, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____
 ADDRESS _____
 Post Code _____

VCR Servo Fault Finding

S. R. Beeching, T.Eng. (CEI), AMIERE

A PHILIPS N1500/15 videocassette recorder was brought into the workshop recently by a local TV shop which normally does its own repairs. It was said that the machine had been dropped, and whilst the physical damage had been tidied up there was a capstan servo fault which they'd been unable to resolve. To make matters worse, the owner's brother, who was a TV repairman, had also had a look at it...

I asked whether the servo lock fault was evident in the playback or record mode or both, and was told that the audio/sync head had been changed, the servo output transistors changed, etc., all to no avail. Some of this was evident at a quick glance at the butchered printed circuit board. I got no answer however to my question as to which mode the fault occurred in, but it was probably playback I thought as otherwise why would the sync head have been changed – the pulses from the sync track lock the machine during playback. The chances, now at least, were that the sync head was out of alignment.

Basic Principles

For those who don't know much about VCR servos, a brief description of the principles of operation of the system seems appropriate. The idea is shown in Fig. 1, and it will be seen from this that the servo has two inputs and one output – as with flywheel line sync. The reference pulses dictate the basic motor speed, the feedback pulses being used to hold the speed within fine limits. The output, which is proportional to the relationship between the reference and the feedback pulses, controls the actual motor speed. In the Philips VCR the two (head and capstan) motors are of the synchronous type and free run slightly faster than the required "locked in" speed (say 1,510 r.p.m. for a locked speed of 1,500 r.p.m.). The servo systems drive current into the two braking coils, on the basis of more current, more braking.

In the record mode, the reference pulses are the field sync pulses from the off-air signal, the feedback pulses coming from the appropriate motor flywheel. Hence the speed is synchronised with the incoming video signal, any motor speed fluctuations being compensated for by the action of the servos in comparing the reference and feedback pulses from the flywheels. At the same time, 25Hz pulses (40msec apart) are recorded on the upper edge of the tape for replay purposes.

In the playback mode, the reference pulses are derived from the mains in order to synchronise the machine to a stable frequency source. The feedback pulses are those recorded on the sync track, picked up by the same sync head that recorded them. As the feedback pulses are derived from the moving tape, any speed changes will affect the timing of these pulses. As a result the servo systems will initiate the required compensating action. With the recorded sync pulses synchronised to the video signal and the tape speed locked to a 50Hz source (the mains), the video is replayed at the 50Hz field rate. Note that if a 60Hz

reference say is used, the replayed video would be 625 lines at a field frequency of 60Hz. Hence the reason for not using something like a multivibrator, which may drift, as the playback reference source.

The Faulty Machine

Now back to the machine with the faulty capstan servo. On switching on I found that the reason for not getting an answer to my question as to whether the servo was unlocked in play or record was that there was no off-air signal due to a cracked tuner board! The previous repairs had had to be done in the playback mode therefore, resulting in the incorrect diagnosis of a faulty audio/sync head.

Initial Tests

When faced with a VCR servo problem, first do two important checks. Identify test point TP221 in the capstan servo circuit and test point TP220 in the head servo circuit. During operation, each should show a sawtooth or ramp waveform with a sample pulse on it (see Fig. 2) when checked with an oscilloscope. Put the machine in the record mode and tune in, with a cassette inserted. Do a short recording. If the pulses sit steadily on the slopes of the ramps the servos are o.k. Replay the recording and again check whether the pulses sit still on the ramps at the two test points. Any deviation discovered during these checks will indicate where the problem area is – capstan or head servo, on play or record.

In this particular case, having repaired the tuner board we found that all was well at the head servo test point. At the capstan servo test point TP221, well... First, there were two pulses instead of one (see Fig. 3); secondly they were running up the ramp and falling over the edge. This confirmed that the machine had indeed been got at. Experience counts here, and we knew the reason for the double pulses – someone had reversed the wiring on the

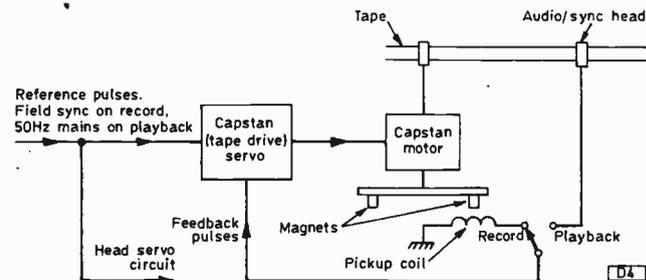


Fig. 1: Block diagram showing in simplified form the basic elements of the Philips N1500 VCR's capstan servo system. On playback the feedback pulses come from the tape via the audio/sync head. On record, the feedback pulses are obtained from magnets attached to the capstan flywheel: these induce a pulse voltage in the pickup coil.

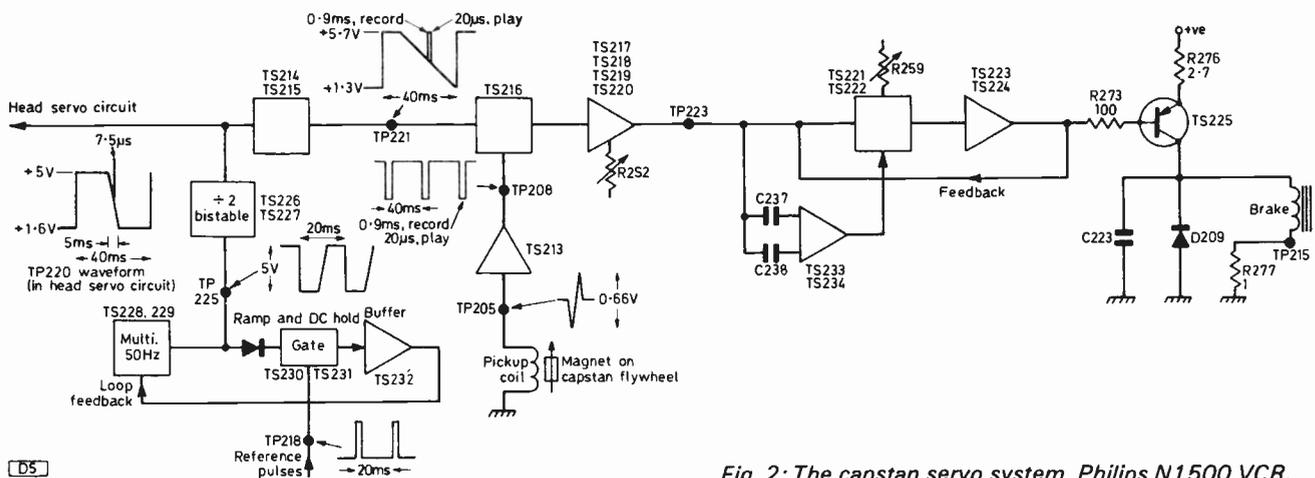


Fig. 2: The capstan servo system, Philips N1500 VCR.

capstan motor flywheel pickup coil/head. A quick rewire restored the single pulse, but it still ran up the ramp. Now the ramp is derived from the sync pulse and is steady, while the pulse comes from the capstan motor flywheel: the fact that it was running up the ramp showed that the motor was running fast, i.e. no servo braking.

Tracing the Fault

A more precise measurement is required next. First, check whether the ramp and the sync pulses coming in at TP218 (see Fig. 2) are synchronised by comparing the waveforms at TP221 and TP218 on a dual-beam scope. If they are not synchronised, the trouble is in the 50Hz multivibrator and its phase locked loop, or the divide-by-two bistable circuit. In our particular case the waveforms were synchronised, thus eliminating these areas.

The next point to check is TP223. The feedback pulse samples the reference ramp derived from the sync pulse and provides a d.c. voltage, buffered by the sample and hold circuit TS217-TS220, at TP223. With our fault conditions you would expect to find here a d.c. voltage that slowly rises and suddenly falls, representing the pulse running up the ramp and falling off the top. No reading would indicate a fault in the sample-and-hold circuit. Don't twiddle R252, as it can be set only when the servo is properly operational. The same goes for R259. There was a rising and falling voltage at TP223, so everything was all right up to there.

Due to the voltage conditions in the following section it's more difficult to see anything much, even when the servo is working. The main part consists of two d.c.-coupled differential amplifiers TS221-TS224 which are used for the small phase changes required. There is partial bypassing by TS233-TS234, which are a.c. coupled and are sensitive to the large changes in level when the servo is well out of lock, such as at switch on. They drive hard into the locked condition. The pulse falling off (or leaping up) the edge of the ramp is a large enough change, so this part of the circuit can be temporarily eliminated by disconnecting C237/C238.

Having done this however the fault was still present and the d.c. level change noted at TP223 continued through from TS221 to the output transistor TS225. This was removed and checked, but turned out to be all right. Continuity through the brake coil was checked, then D209

and C223, but all were cleared. To summarise the situation: all transistors were o.k., the voltage and current variations seen at TP223 appeared at the collector of TS225 and, although small, across R277 via which the brake coil is returned to chassis. So the servo was working: why no lock? I decided to measure the brake current, which turned out to be 89-98mA, not enough. In the VCR setting up procedure provided by Philips, voltages of around 150mV are mentioned across R277 (measured at TP215). It was a fair guess therefore ($V = IR$) that the current should be in the 120-170mA region. This lack of brake current was obviously the cause of the motor running too fast.

So what was the very last thing I checked? Yes, R276 (2.7Ω). The one I removed read 13Ω. Replacing R276 with a 2.7Ω resistor restored lock at last. Reconnect C237 and C238, then adjust R252 for minimum ripple at TP223 and R259 to sit the feedback pulse half way up the ramp. Further work was required to reset the audio/sync head.

Other Servo Faults

A couple of other servo faults have caused headaches. The first I encountered some time ago: the capstan servo would not lock and on following the procedure just outlined lock was obtained on removing C237 and C238. The problem turned out to be a larger than normal ripple pulse at TP223. This kept kicking the servo out of lock via the lock-in circuit. The trouble was eventually traced to the pulse from the flywheel pickup coil. It should be 0.66V peak-to-peak at TP205 but was about 1.5V peak-to-peak, thus overdriving the servo. The cause was wear in the lower capstan flywheel bearing, as a result of which the magnets on the flywheel were lower than they should be and closer to the pickup coil, thus increasing its output.

The second fault, a more frequent one, is no capstan servo lock, with the feedback pulse running down the ramp, indicating that the motor is running too slowly. With slow running, if there is no electronic fault such as TS225 going short-circuit, see whether disconnecting the eddy current brake increases the motor speed. If the pulse is still running down the ramp, the motor is still running slow. The trouble has been overcome by replacing the motor, which seems to lose power though I've not established why.

If the feedback sample pulse is not present during playback the cause is often the sync part of the audio/sync head being defective. Other faults, such as open-circuit or short-circuit brake drive transistors with or without open-circuit emitter resistors, are fairly obvious to trace due to the lack of voltage variations at specific points and incorrect d.c. voltages.



Fig. 3: The fault condition: waveform monitored at TP221.

Your PROBLEMS solved

Requests for advice in dealing with servicing problems must be accompanied by a 50p postal order (made out to IPC Magazines Ltd.), the query coupon from page 104 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

Thorn 1500 Chassis

An otherwise excellent picture is marred by faint vertical striations on the left-hand side of the screen, covering the first two inches or so. The effect resembles that caused by a line linearity coil ringing – but this circuit doesn't use a line linearity coil.

First check C98 which decouples the screen grid of the PL504 line output valve. Then if necessary check the pulse winding ED on the line output transformer, and the components between it and the c.r.t. control grid.

Philips G8 Chassis

The raster is green when the set is switched on, and remains like this for approximately half an hour before correcting itself. Colour is then normal for the rest of the evening.

There have been various versions of the G8 chassis, so we don't know which one you have. There should be no difficulty however in finding the green output transistor, which is the centre one of the three heatsinked transistors where the coloured leads are taken to the c.r.t. base. The fault is probably nothing more than a dry-joint around the BD115 or BF337 transistor, its 5.1k Ω collector load resistor or the associated 47k Ω resistor. If necessary check the transistor by substitution and examine the print around it. The preceding i.c. (TBA530) could be at fault if the green output transistor's base voltage is in excess of 1.3V: also check if necessary the connections to the filter coil in the G–Y signal path between the TBA520 and the TBA530.

GEC 2010 Series

On u.h.f. reception the sound seems to be modulating the contrast: loud sound passages result in the picture going grey, while very loud sound detunes the picture altogether. The PFL200 video/sync valve has been replaced, also the EF183 first i.f. stage, but the fault persists. I am not in a position to be able to check the conditions on v.h.f.

There is a 32 μ F electrolytic behind the PFL200: this decouples a sub-h.t. line which feeds the video pentode's screen grid and the anode of the EH90 quadrature detector valve, and can be responsible for this sort of trouble when defective. If the effect is noticeable only when the volume control is advanced however the 32 μ F capacitor is not at fault and the 150 μ F electrolytic (dual 150 plus 50 μ F can) which smooths the HT3 line should be checked, also ensuring that the associated filter resistor R143 is intact (i.e. that it hasn't been shorted out).

Philips 170 Series

There is foldover at the top of the raster on this Philips dual-standard monochrome set. Altering the setting of the top linearity control makes very little difference – about 1cm. from one extreme to the other. When the height control is varied, the picture expands at the bottom only, the picture remaining where it is at the top – about two inches from the top of the screen. A new PCL805 has been tried without success, and the surrounding components checked.

Top foldover on these sets is unfortunately usually due to shorted turns in the field output transformer. Before condemning this however take a closer look at the preset linearity controls. They often have a poor rivetted connection (tag to track).

Decca CTV25

The focus deteriorated over a period and then the picture suddenly disappeared, leaving only a dimly lit raster on which the brightness control had no effect. It was found that the focus potentiometer was burnt out at one end, and that the focus rectifier had broken down, reading only about 1k Ω on an Avo Model 8. The control and rectifier were replaced and various checks made, but within a short time after switching on the rectifier blew and the control again started to burn out. Since then I've again replaced these components, also the focus reservoir capacitor C416, and in addition tried a new line output transformer primary winding, but to no avail.

The most common cause of the TV6.5 rectifier failing is C416: make sure that your replacement is a disc type rated at 8kV or more. Then check the insulation of the rectifier's cathode tag, and the insulation of the lead to pin 9 of the c.r.t. and the focus spark gap.

Philips T-Vette 11TG190AT


On v.h.f. it's impossible to tune in good sound and vision together: each can be obtained separately, but the other is then lost. There is also virtually no field sync, while the picture tends to pull to the right. The OC44 sync separator has been replaced and all resistors and capacitors in this circuit have been checked. The video output transistor has also been replaced as it had a broken lead.

Provided the aerial can provide an adequate signal on 405 lines the most likely cause of the sound and vision separation is a broken fine tuning slug. This can be removed by unscrewing it through C3022 on the tuner, using a fine screwdriver. Lightly oil the replacement before screwing it into position. If the core is not broken, try replacing the tuner transistors, which can be prised gently from their sockets on the top of the tuner. For the poor field sync replace the field sync clipper diode X4019 and check the associated components. For the line pulling suspect the smoothing electrolytics, check the line sync diodes X4018 (gating) and X4011/2 (flywheel sync discriminator) and ensure that the voltages on the reactance and line oscillator transistors T2022/3 are correct.

Philips G8 Chassis

The problem is that R4483 on the timebase panel is overheating and going up in smoke. What's causing this?

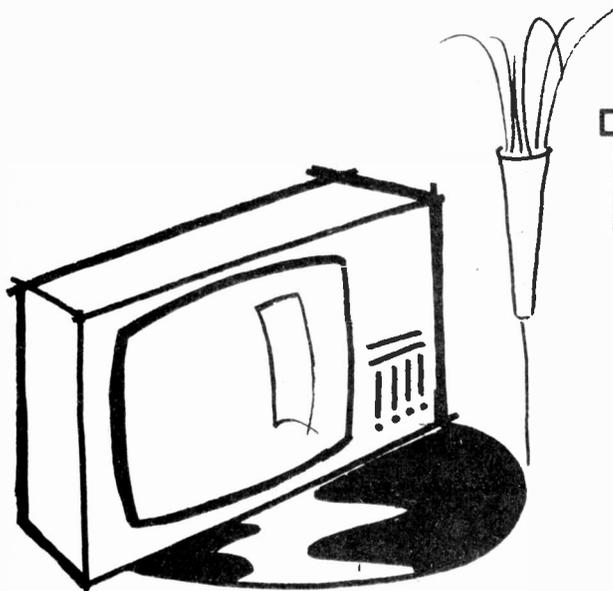R4483 is in parallel with the pincushion distortion correction transducer. Disconnect plug H (red) from the panel – the set will function pretty well without this fitted – thus removing the line drive to the transducer. If this stops the overheating, replace the transducer.



It's easy to build your own

TELEVISION

PORTABLE

- ★ Perfect for bedroom, car, caravan, camping.
- ★ Top picture quality from the latest 15 inch tube.
- ★ What a wonderful present!

ORDER THE TUBE NOW FROM US – £15.75 plus VAT 12½%

12 month guarantee – carriage free.

RB-TV Services

82 North Lane – East Preston – Sussex.

SONY KV1810UB Mk II

After about ten minutes the picture starts to twitch and appears to be on the verge of collapsing, i.e. the height and width momentarily reduce. The raster does not collapse completely however. It seems that the h.t. voltage is lost for a split second. The sound is not affected, though there is the click you would expect to hear when the fault occurs. The fault does not clear, and switching the set off and on again has no effect.

We agree that the fault appears to be in the power supply, which is a fairly complex gate-controlled switch chopper circuit (see July 1977 issue). We particularly suspect the 4.7µF electrolytic C620 which decouples the feed to the monostable transistors Q606/Q607. Other possibilities are C616 (0.47µF electrolytic) which decouples the emitter of the error detector/amplifier transistor Q608, and its reference zener D610 which is returned to chassis via Q601.

THORN 1580 CHASSIS

Here's one that may be of help to others. On switching on from cold there was about two inches of line scan at the centre of the screen. Then after about two minutes the thermal resistor in the h.t. line would open. If the resistor was reconnected and the set then switched on again a perfect picture would appear. We spent hours on this one, and changed everything relevant including the line output transformer – but still no good. The trouble turned out to be leakage between the pins under the PL81A line output valve base. This was loading the line output stage – Thorn tell us they've had quite a few like this!

Many thanks for passing this one on to us.

PYE 368 CHASSIS

I have the same fault on two of these sets. When the picture content is mainly peak white the line sync is weak, though the field sync, resolution and contrast are good. The fault may not appear for a whole evening, but on the odd scene with about 90% white background the picture has a wavy edge – with no signs of break up however. I've changed the sync separator and flywheel sync phase-splitter valves, and replaced the coupling capacitor to the control grid of the sync separator. The main reservoir/smoothing electrolytics have also been replaced.

It seems to us that the video output pentode's bias is not quite right. This could well be due to the input video coupling capacitor C68 (2.5µF) being slightly leaky.

THORN 1590 CHASSIS

The problem is horizontal splitting of the picture – not like loss of sync, but consisting of a bright line division at two or three points horizontally, the picture pulling along the light lines. This occurs only after several hours' use, and is sometimes accompanied by rolling. Switching off and allowing the set to cool restores normal operation.

Your first concern should be that the voltage from the regulator is not rising unduly. The regulator transistor is usually an AD149, mounted on the left side aluminium panel. Its body (the collector) should be at 11.5V. If this voltage is found to rise, check the regulator transistor, the error sensing transistor VT22 and the control R104, which should be set for 5V at the base of VT22. If the supply voltage is constant, check the reservoir electrolytic C85 as the tags of this do not always make proper contact with the capacitor's rivets.

Decca Series 10 Chassis

The problem is no raster. There is sound until the PL509 line output valve glows cherry red. The valves have all been replaced and a new line output transformer and e.h.t. tripler fitted. The resistors on the timebase panel appear to be all right, with no signs of burning or shorting.

The cherry red line output valve suggests that line drive is absent. Check for $-70V$ on pins 1 and 8 of the PL509. If absent, check the voltages and components in the line oscillator (PCF802) stage. If you disconnect R465 (the PL509's screen grid feed resistor) you can investigate the line oscillator circuit without risk of overheating. If drive is present, disconnect the tripler from the line output transformer and if the line output stage comes back to life check whether C451 in the corner of the convergence board is leaky. This is the field flyback blanking pulse coupling capacitor and, if leaky, it places a high positive voltage on

the c.r.t. grids. The result is very low e.h.t. and a very unhappy tripler. The reason for the sound going off is due to the action of the beam limiter, which works on the a.g.c. system.

GEC 2114 Junior Finline

About a minute after switching on, a horizontal band about an inch wide which distorts the picture to the right starts to move up the screen. When it gets to the top the whole picture jumps for about five seconds. After it stops jumping the band reappears at the bottom.

This sort of thing is quite common with portables using an encapsulated bridge rectifier. It's almost certainly due to the rectifier being faulty. Remove the case and the four screws which hold the bottom centre power pack. The four-legged bridge rectifier is at the rear of this. Replace it and all should be well. If not, check the reservoir capacitor C410.

TEST CASE

180

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

An ITT colour receiver fitted with the CVC8 chassis arrived in the workshop with the complaints of weak colour and "rippling" colour intensity following any sharp change in colour. These symptoms were confirmed on the test bench, and even with the saturation control at maximum the colour intensity was only about one third of normal. Using the signal from a colour-bar generator, it was noted that distinct "rings" were present at points of colour change.

This chassis uses a Motorola MC1327 i.c. for colour demodulation and matrixing, driven by the delay line and its driver. In front of this there is a two-stage chroma amplifier (BC172X and BF241 transistors). The chroma signal coupling to the delay-line driver transistor (BC171B) is via a pair of varicap diodes which are arranged in a bridge circuit and are biased by a potential-divider and a potentiometer which serves as the saturation control. The strength of the chroma signal let through to the delay-line driver depends on the degree of diode bridge imbalance. This is adjustable by the saturation control.

When the bridge is in perfect balance there is very little chroma coupling, so it was decided to check this part of the circuit first. The saturation control circuit is complemented by a second potentiometer which is ganged to the contrast control so that good colour balance is maintained regardless of the contrast control setting. These potentiometers and the associated resistors and diodes (which were changed) all appeared to be okay however.

An oscilloscope test of the chroma signal amplitude at the base and then at the collector of the second chroma

amplifier transistor (BF241) revealed barely any gain in the stage. It was also noticed that the chroma at the collector was of distorted and asymmetrical envelope shape, though there was no distortion on the signal at the base. The BF241 was changed and the d.c. voltages measured, but no static fault could be detected.

What was the most likely cause of the symptoms? See next month's Television for the solution and for a further item in the Test Case series.

SOLUTION TO TEST CASE 179

— Page 49 last month —

The line oscillator in the Thorn 1500 chassis consists of the triode section of a 30FL2 valve in a blocking oscillator circuit. The oscillator transformer provides coupling between the anode and grid. It was found that by applying light pressure to the outer windings with the flat of a screwdriver a significant change in the line oscillator frequency was produced.

The transformer is mounted towards the top of the printed panel, not far from the mains dropper. Consequently it rises in temperature, due to the heat from the dropper. The result is that the wire expands slightly, altering the transformer's parameters sufficiently to move the line oscillator frequency outside the range of the line hold control.

Sometimes it's possible to minimise the effect by binding the transformer. For a permanent cure however the transformer should be replaced.

QUERY COUPON

Available until 19 December 1977. One coupon, plus a 50p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 102.

TELEVISION DEC 1977

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Pacesetters, London SE1. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R 0NE. Sole Agents for Australia and New Zealand - Gordon and Gotch (A/sia) Ltd.; South Africa - Central News Agency Ltd. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

TV LINE OUTPUT TRANSFORMERS

ALL MAKES SUPPLIED
PROMPTLY by our

**RETURN OF POST
MAIL ORDER SERVICE**

All Mono Lopts at the one price

**£6.20
TRADE**

£6.75 RETAIL
(V.A.T. INCLUDED AT 12½%)
Postage and Packing 70p

All Lopts NEW and GUARANTEED
for SIX MONTHS

**PAPWORTH
TRANSFORMERS**
80 MERTON HIGH STREET,
LONDON,
S.W.19 **01-540 3955**

T.V's! T.V's! T.V's!

Special clearance of 25" dual std. Philips G6. Thorn 2000 and RBM C.T.V's from only **£16.00**

19" GEC S/STD from only **£24.00**. Working from **£40.00**
(limited number without tubes at only **£16.00**)
22" Philips 511 S/STD from only **£28.00**. Working from **£44.00**
22" Pye Hybrids from only **£32.00**. Working from **£48.00**
22"/26" Pye Varicaps from only **£48.00**. Working from **£64.00**
19"/22"/26" Bush Integrated. Beautiful sets all prices.
20"/22"/26" Thorn 3500 - working or not. Lots of choice.
26" EMO Eurosonic 110° tube. Slimlines from **£60.00**

Hundreds of Mono T.V's - all makes - all sizes.

Colour Tubes - Ex equipment tested 25" **£16.00**
19" **£20.00**. 20"/22" **£24.00**. 26" **£28.00**. Plus **£4 P & P**

New tubes from **£40.00**

Mono tubes any size all at **£5.00 + £3 P & P**

ALL PRICES PLUS VAT

Please write for quotations on any set or spares.
Quality discounts. Callers welcome. Deliveries arranged.



WEST Unit 4A, Bulwark Industrial Estate, Chepstow, Nr. Bristol. Tel. Chepstow (02912) 8652	SOUTHERN Watling Street, Hockcliffe (3 miles north of Dunstable on A5). Tel. Hock- cliffe (052521) 788	NORTHERN Thornbury Roundabout, Leeds Road, Bradford 3. Tel. (0274) 865670	SCOTLAND Peacock Cross Industrial Estate, Burnbank Road, Hamilton. Tel. (06982) 28511
--	--	---	---

A. P. ELECTRONICS

Manufacturers & Distributors of Electronic Components
**3 MILDMAY ROAD, ROMFORD, ESSEX
RM7 7DA.**

Telephone: ROMFORD 28882

BONANZA

4 MILLION RESISTOR'S Brand new. A fabulous range of ¼ Watt, ½ Watt, 1 Watt and 2 Watt. Carbon Film Resistor's. 1,000 mixed values. For the lowest price ever, VAT included **£3.50** only.

This is a bargain you cannot miss, only from A. P. ELECTRONICS. Count by weight. Post & Pack only **45p**.

½ A MILLION MINIATURE CERAMIC PLATE CAPS. 200 for only **£1.25**. Mixed values all brand new VAT included. Post & Pack **25p**. Count by weight.

¼ OF A MILLION MULLARD C296 POLYESTER'S. Many values, 75 for only **£1** VAT included. Post & Pack **30p**. Brand new. Count by weight.

MULLARD C280 75 mixed values for only **£1** VAT included. Post & Pack **20p**. Count by weight.

A FABULOUS PACK OF HARDWARE. Self tappers, nuts, bolts, washers, spacers, grommet's, etc. etc. **£1** VAT included. Post & Pack **40p**.

200 METRES CONNECTING WIRE. Mixed colours, stranded and single only **£1.25**. Post & Pack **25p**.

50 ELECTROLYTICS CAPACITORS. Mixed values for only **£1** VAT included. Post & Pack **25p**.

50 WIREWOUND RESISTORS. From 2.5 Watt. Mixed values for only **£1** VAT included. Post & Pack **30p**. Count by weight.

OVERSEAS POST AT COST.

EX-STOCK. Transistors, Diodes, I.Cs, C.MOSs, Thyristors, Knobs, Pre-sets, Resistors, Capacitors, Tant's, Bridge-Rectifiers, Transformers.

Open all day from 9am till 5.30pm.

Open all day Saturday.

TELEVISION ELECTRONIC DISTRIBUTION (SPARES) LTD.

412a Hanworth Road, Hounslow, Middlesex
Telephone: 01-572 4668

PANEL REPAIR/EXCHANGE SERVICE

TRADE ONLY

THORN 2000 Series, 3000/3500 Series,
8000/8500 Series.

GEC Solid State 2110 Series.

PHILIPS G8

RBM A802/823

DECCA Solid State 80 Series

GRUNDIG 6010 GB

VERY COMPETITIVE PRICES. 3 MONTHS' WARRANTY FROM DATE OF OUR INVOICE. PRICES ON APPLICATION. DISCOUNT FOR BULK PANEL ORDERS. 10 MIXED LESS 10%, 15 MIXED LESS 12½%, 25 MIXED LESS 15%, 100 MIXED LESS 20% - NO DISCOUNT ON REPRINTS. 48 HOUR SERVICE WHEREVER POSSIBLE. ALSO VERY COMPREHENSIVE RANGE OF MULLARD TV COMPONENTS, CATALOGUE AVAILABLE ON REQUEST.

COLOUR T.V.'s UNTESTED

Most Dual-standard; R.B.M., Philips G6, Decca, Pye, etc., from £25 + VAT.

Single-standard from £35 + VAT. Most makes available.

Monochrome from £3 + VAT. 'Square screen' from £6 + VAT. Circuit Diagrams available most sets £1 extra.

All working sets demonstrated. All untested sets can be fully inspected before purchase.

Ring or send s.a.e. for current prices and stock.

Usually scrap sets of many makes available from £10 + VAT.

Fresh stock of Castor Stands just in!

West Midlands TV Trade Sales

1532 Pershore Road (Main A441)

Stirchley, Birmingham, B30 2NW

('Phone 021-458 2208)

Open all day Mon, Tues, Thurs, Fri, Sat. Half day Wed.

TV's TV's TV's

DEALERS, NOW IS THE TIME TO STOCK FOR THE CHRISTMAS RUSH
We are the largest stockists in the south of Ireland
of clean used T.V. sets.

BUSH - PHILIPS - FERGUSON - PYE

Mono D/S from £15.00 each

Colour from £110.00 each

Transistor Radios from £8.00 each

Visit our warehouse and see for yourself.

Fresh Stocks Weekly.

T.V. WHOLESALE DISTRIBUTORS LTD.

E.D.I. HOUSE,

Kylemore Park West Industrial Estate, Dublin 10. Tel. 364139.

COLOUR TUBES STANDARD TUBES

METAL BAND TUBES

TWIN PANEL TUBES

Rebuilt with new Electron
Guns to British Standard
415/1972.

SUFFOLK TUBES LIMITED

214, PURLEY WAY
CROYDON, SURREY
01-686 7951

Britain's Largest Independent
TV Tube Rebuilder

REBUILT TUBES!

YOU'RE SAFE WHEN YOU
BUY FROM RE-VIEW!

HERE IS WHAT YOU PAY:

MONO

19" £10.00
23" £12.00

RIMBAND & TWIN PANEL

16", 17", 19" £10.00
20" £12.00
23" £14.00
24" £15.00

Carriage £2.70 inc. V.A.T.

COLOUR

17", 18", 19" £31.00
20" £32.00
22" £34.00
25" £36.00
26" £40.00

Exchange Basis £5 Deposit Returnable
Old Tube (Colour)
(carriage-ins. £3.25 inc. V.A.T.)

Guarantee 1 year

Cash or cheque with order,
or cash on delivery

Add 12½% V.A.T. to all orders

INQUIRIES S.A.E. PLEASE

RE-VIEW ELECTRONIC TUBES

237 LONDON ROAD,
WEST CROYDON, SURREY
Tel: 01-689 7735

ELECTRONIC MAILORDER LTD. VALVE BARGAINS

Any 5-64p, 10-£1.20, 50-£5.00. Your
choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80,
PCF802, PCL82, PCL84, PCL85, PCL805,
PL504, PY81/800, PY88, 30PL14, 6F28,
PFL200.

Colour Valves - PL508, PL509, PL519,
PY500/A. All tested. 35p each.

Aerial Splitters - 2 way, 75 OHMS, Inside
Type, £1.50

AERIAL BOOSTERS

Aerial boosters can produce remarkable
improvements on the picture and sound, in
fringe or difficult areas.

B11 - For the stereo and standard VHF/FM
radio.

B12 - For the older VHF television - Please
state channel numbers.

B45 - For Mono or colour this covers the
complete UHF Television band.

All boosters are complete with battery with
Co-ax plugs & sockets. Next to the set fitting.
£4.20

100 - C280/1 CAPACITORS. Values from
.01uF to 1.5uF, 250v/w. Price £1.50 (mixed
packs).

100 - ELECTROLYTICS from 1uF to above
500uF. Mixed voltages. Price £2.00 (mixed
packs)

ALL PRICES INCLUDE VAT. P&P 30p PER ORDER. PLEASE
SEND UNCROSSED P.O. OR CHEQUES FOR RETURNING IF
WE ARE OUT OF STOCK OF CAPACITOR BARGAIN PACKS.
EXPORTS WELCOME AT COST.

62 BRIDGE STREET, RAMSBOTTOM,
BURY, LANCs.
TEL: RAMS (070 682) 3036.



LINE OUTPUT TRANSFORMERS

All items new and guaranteed

MONO TRANSFORMER £7.00ea
(No Extra for Carriage)

VAT @ 12½% 86p

DISCOUNT FOR TRADE. TOTAL £7.86

BUSH	TV128	TV183 or D
TV102C	TV134	TV183S
TV103 or D	TV135 or R	TV183SS
TV105 or D	TV138 or R	TV185S
TV105R	TV139	TV186 or D
TV106	TV141	TV186S
TV107	TV145	TV186SS
TV108	TV148	TV191D
TV109	TV161	TV191S
TV112C	TV165	TV193D
TV113	TV166	TV193S
TV115 or C	TV171	TV198
TV116R	TV175	TV307
TV118	TV176	TV313
TV123	TV178	TV315
TV124	TV181 or S	
TV125 or U		

DECCA	DM35	DR123
DR1	DM36	DR202
DR2	DM39	DR303
DM3	DR41	DR404
DR3	DR45	DR505
DR20	DR49	DR606
DR21	DM55	666TV-SRG
DR23	DM56	777TV-SRG
DR24	DR61	MS1700
DR29	DR71	MS2000
DR30	DR95	MS2001
DR31	DR100	MS2400
DR32	DR101	MS2401
DR33	DR121	MS2404
DR34	DR122	MS2420

MURPHY	V843
all models to	
V979	
V153	
V159	
V173	
V179	
V1910	
V1913	
V1914	
V2014 or S	
V2015D	
V2015S	
V2015SS	
V2016S	
V2017S	
V2019	
V2023	
V2027	
V2310	
V2311C	
V2414D	
V2415D	
V2415S	
V2415SS	
V2416D	
V2416S	
V2417S	
V2419	
V2423	

PHILIPS	19TG100u	19TG170a...	21TG106u
19TG102u	all models to	21TG107u	
19TG106u	19TG179a	21TG109u	
19TG200u	G19T210a		
19TG300u	G19T211a	23TG111a...	
19TG320u	G19T212a	all models to	
	G19T314a	23TG164a	
	G19T215a		
19TG108u...		23TG170a...	
all models to		all models to	
19TG164a	G20T230a...	23TG176a	
	all models to		
	G20T328		
		G24T230a...	
		all models to	
		G24T310	

PLEASE QUOTE PART NO. NORMALLY FOUND ON TX. BASE PLATE 4133, 4123, 4140 OR 00062.

BAIRD	600	628	662	674
	602	630	663	675
	604	632	664	676
	606	640	665	677
	608	642	666	681
	610	644	667	682
	612	646	668	683
	622	648	669	685
	624	652	671	687
	625	653	672	688
	626	661	673	

GEC	BT454
	BT455
	BT455DST
	2000DST...
	all models to
	2044
	2047...
	all models to
	2084
	2104 or/1
	2105 or/1

KB-ITT	By Chassis:	
	VC1	VC52
	VC2	VC52/1
	VC3	VC100
	VC4	VC100/2
	VC11	VC200
	VC51	VC300
	Or quote model No.	

INDESIT	20EGB
	24EGB

PYE	11u	40F	58	64	81	93	161
	31F	43F	59	68	83	94	150
	32F	48	60	75	84	95/4	151
	36	49	61	76	85	96	155
	37	50	62	77	86	97	156
	39F	53	63	80	92	98	160

SOBELL	ST196 or DS
	ST197
	ST290
	ST297
	1000DS...
	all models to
	1102

Tidman Mail Order Ltd.,
236 Sandycroft Road,
Richmond, Surrey.
Approx. 1 mile from Kew Bridge.
Phone: 01-948 3702

MON-FRI 9 am to 12.30 pm.
1.30 pm to 4.30 pm.
SAT 10 am to 12 noon.

Hamond Components (Midland) Ltd.,
416, Moseley Road,
Birmingham B12 9AX.
Phone: 021-440 6144.

MON-FRI 9 am to 1 pm.
2 pm to 5.30 pm.

COLOUR TV LINE OUTPUT TRANSFORMERS E.H.T. RECTIFIER TRAYS (Prices on application)

BENTLEY ACOUSTIC CORPORATION LTD.
The Old Police Station, Gloucester Road, LITTLEHAMPTON, Sussex.
PHONE 6743
ALL PRICES INCLUSIVE OF V.A.T. AT 12½%. NOTHING EXTRA TO PAY


OA2 0.85	6CU5 0.90	30C15 1.00	ECC8072.80	EZ81 0.40	PY82 0.40
OB2 0.40	6DE7 0.90	30C17 0.90	ECC808.60	PY88 0.60	
1B3GT 0.55	6DT6A 0.85	30F5 0.70	ECF82 0.50	GY501 1.25	PY500A 1.56
2D21 0.55	6E5 1.00	30L15 0.75	ECF86 0.80	GZ32 1.00	PY800 0.60
3CG8 0.75	6EW6 0.85	30L17 0.70	ECH35 2.00	HN309 1.70	PY801 0.60
SR4GY 1.00	6FI 0.80	30P12 0.74	ECH42 1.00	KT66 3.00	PZ30 0.50
SU4G 1.00	6F18 0.60	30P19 0.90	ECH81 0.55	KT88 6.75	QQV03/10
5V4G 1.00	6F23 1.00	30PL1 1.25	ECH84 0.75	P61 0.60	2.00
5Y3GT 0.65	6F28 0.85	30PL13 1.30	ECL80 0.55	PC86 0.80	QV06/20
5Z3 1.40	6GH8A 0.80	30PL14 1.50	ECL82 0.50	PC88 0.80	4.70
5Z4G 0.75	6GK5 0.75	50CD6G	ECL83 1.50	PC92 0.55	R10 5.00
6/30L2 0.90	6GK6 2.00		ECL86 0.64	PC97 0.75	R19 0.75
6AC7 0.70	6GU7 0.90	85A2 1.40	EF22 1.00	PC90 0.65	UABC80
6AG7 0.70	6HGT 0.50	807 1.10	EF40 1.00	PCC84 0.39	0.45
6AH6 0.70	6J5GT 0.65	5763 2.75	EF41 1.00	PCC85 0.47	UAF42 0.70
6AK5 0.45	6J6 0.35	AZ31 1.00	EF80 0.40	PCC89 0.49	UBC41 0.70
6AMB8A 0.70	6J8A 0.90	AZ41 0.50	EF83 1.70	PCC1890.60	UBC81 0.55
6AN8 0.70	6K7G 0.50	DY51 2.00	EF85 0.45	PCF80 0.80	UBF80 0.50
6AQ5 0.68	6K8G 0.50	DY86/7 0.45	EF89 0.50	PCF82 0.45	UBF89 0.39
6AR5 0.80	6L6GC 1.75	DY802 0.50	EF91 0.70	PCF86 0.57	UC92 0.50
6AT6 0.60	6L7GM 1.50	E80CF 6.00	EF92 0.70	PCF200 1.35	UCC85 0.45
6AU6 0.50	6Q7G 0.75	E88CC 1.20	EF183 0.45	PCF201 1.00	UCF80 0.80
6AV6 0.65	6SA7 0.70	E188CC 4.50	EF184 0.45	PCF801 0.49	UCH42 1.00
6AW8A 1.15	6SG7 0.70	EASO 0.40	EH90 0.65	PCF802 0.75	UCH81 0.50
6AX4 0.75	6V6G 0.50	EABC80	EL34 1.25	PCF805 2.25	UCL82 0.55
6BA6 0.45	6X4 0.95		EL41 1.00	PCF806 0.70	UCL83 1.00
6BC8 0.90	6X5GT 0.50	EAF42 1.00	EL81 1.00	PCH200 1.00	UF41 0.70
6BE6 0.60	9D7 0.70	EAF80 1.50	EL84 0.41	PCL82 0.54	UF42 1.00
6BH6 1.00	10C2 0.70	EB91 0.25	EL86 0.60	PCL83 0.75	UF80 0.40
6BJ6 0.75	10DE7 0.80	EBC41 1.00	EL95 0.80	PCL84 0.46	UF85 0.50
6BK7A 0.85	10F1 0.67	EBC81 1.00	EL360 2.50	PCL86 0.65	UF89 0.52
6BN8 1.00	10F18 0.65	EBF80 1.00	EL509 2.50	PCL805 0.65	UL41 0.90
6BQ7A 1.40	10I3 0.80	EBF89 0.40	EL509 2.50	PCL805 0.65	UL41 0.90
6BR7 1.00	10P14 2.50	EC86 0.84	EM80 1.00	PCL805 0.65	UL41 0.90
6BR8 1.25	12AT6 0.45	EC88 0.84	EM81 1.00	PCL805 0.65	UL41 0.90
6BW6 3.50	12AU6 0.50	EC92 1.00	EM84 1.00	PCL805 0.65	UL41 0.90
6BW7 0.65	12AV6 0.60	ECC33 2.00	EM87 1.45	PCL805 0.65	UL41 0.90
6BZ6 1.50	12BA6 0.50	ECC35 2.00	EY51 0.65	PCL805 0.65	UL41 0.90
6C4 0.50	12BE6 0.85	ECC40 1.00	EY81 1.50	PCL805 0.65	UL41 0.90
6C9 2.00	12BH7 0.55	ECC81 0.48	EY83 1.50	PCL805 0.65	UL41 0.90
6CB6A 0.65	13D8 2.00	ECC82 0.48	EY87/6 0.45	PCL805 0.65	UL41 0.90
6CD6G 4.00	19AQ5 0.65	ECC83 0.48	EY88 1.00	PCL805 0.65	UL41 0.90
6CG8A 0.90	19G6 6.50	ECC84 0.50	EY500 1.45	PCL805 0.65	UL41 0.90
6CL6 0.75	19H1 4.00	ECC85 0.50	EZ40 1.00	PCL805 0.65	UL41 0.90
6CL8A 0.95	20P1 1.00	ECC86 2.00	EZ41 1.00	PCL805 0.65	UL41 0.90
6GM7 1.00	20P4 0.84	ECC88 0.72	EZ80 0.35	PCL805 0.65	UL41 0.90

All goods are unused and boxed, and subject to the standard guarantee. Terms of business: Cash or cheque with order only. Despatch charges: Orders below £25, add 50p extra per order. Orders over £25 post free. Same day despatch. Terms of business available on request. Any parcel insured against damage in transit for only 5p extra per parcel. Many other types in stock. Please enclose S.A.E. with any enquiries. Special offer of EF50 VALVES, SOILED, BUT NEW AND TESTED £1 EACH.

ORCHARD ELECTRONICS ! SERVICE SECOND TO NONE - TRY US AND SEE ! SUPPLIERS TO U.K.A.E.A. D.O.E. UNIVERSITIES, ETC.

ARE YOU GETTING THE BEST SERVICE?

TRANSISTORS	c p	I/C LINEAR	c p	TRANS-		TV SPARES	c p
BU126	2.50	708 (7089)	0.35	FORMERS		LOPTS	
BU208	3.00	708 (8 PIN DI)	0.40	6-0-6-100mA	1.20	GEC Solid State Colour	9.00*
25C1172	3.00	741 (8 PIN DI)	0.28	9-0-9-75mA	0.87*	GEC Hybrid Colour	9.00*
AU113	2.20*	AY-5-1224	3.75	9-0-9-75mA	1.20	GEC 2047 Single Stand Mono 7.00*	
MJE340	0.76	CA3130	0.87*	9-0-9-75mA	3.20	GEC 2043 Dual Stand Mono 7.00*	
AF138	0.34	LM301AN	0.86	9-0-9-75mA	0.86	GEC 2114	7.00*
AF239	0.48	LM309K	2.00	12-0-12-50mA	1.30	TRIPLETS	
BC108	0.12	LM324	2.06	12-0-12-12A	1.29*	ITT TS2511TDC Solid State	8.25*
BC148	0.09	LM380/SL60745	1.29*	12-0-12-12A	2.75	ITT 11T2B Hybrid	8.00*
BC300	0.38	LM381N	2.00*	min O/P for		Oscillator Coils for Hybrid	1.15*
R2010B	3.00	LM723	0.89	OC71/2 use 0.25		Line Sync Trans 2043 Series	0.70*
BY126	0.16	LM3900N	2.85	6-0-6-280mA	2.40	Line Sync Trans 2100 Series	0.70*
BY127	0.16	MC1310	1.38*	12-0-12-12A	2.40	TUNERS	
BY133	0.20	MC1332P	0.75*	12-0-12-12A	2.40	UHF with Tuning Drive -	
BY164	0.40	MC1350P	0.75*	150mA	2.40	replacement for BRC, BUSH,	
1N814	0.05	NE555	0.49	MGT 700 OP		GEC, 2018, PYE, PHILIPS	8.00*
1N4148	0.05	NE568	1.90*	P-1K2		Variacap 4 Push Button with	
BAK18	1.40	NE567	2.70*	80 200 MW	0.60	window	9.00*
QA47	0.09	SN76003N	2.80*	1N4007	0.08	H/B Silicone 2100 series	8.00*
1N4004	0.08	SN76013ND	1.80*	OFFER		ELC 1043/05	5.00*
1N4007	0.11	SN76013N	1.75*	RED LED's 125		Telefunken Variacap (High quality	
		SN76023ND	1.80*	10 for £1		replacement for 1043)	5.50*
THYRISTORS		SN76033N	2.75*	RED LED's 2		ELECTROLYTIC CAPACITORS	
60V 1A 0.25		SN76860	0.90*	10 for £1		1000-2000 35V	0.80*
100V 1A 0.38 TAG 1 100		SN76860	0.90*	10 for £1		300-300+100-50+150 350VDC	3.00*
200V 1A 0.60 TAG 1 200		TAA550	0.90*	100 for £8		200-200-150-50 300V	2.50*
600V 1A 0.80 TAG 1 800		TAA550	1.30*	2N 3702		THYRISTORS	
700V 1A 1.40 BT 106		TBA120AASO	1.25*	3704		TH303/VA8850	0.80*
400V 4A 0.85 C106D1		TBA4800	1.70*	100 for £9		TV DRIVER RESISTORS	
500V 6A 1.85 BT 109		TBA5200	1.90*	100 for £9		TCE (BRC) 56-1 K+47-12 1.08*	
CERAMICS 50V		TBA5300	2.06*			TCE (BRC) 200-20+148-1.5K+317	1.23
2.2, 4.7, 6.10, 22, 33, 39,		TBA5400	3.40*			TCE (BRC) 100-1+6	1.08*
47, 100, 200, 470, 580,		TBA5500	2.30*			GEC 2047	0.85*
1000, 1500, 2200, 3000pF,		TBA5600Q	2.56*			Philips 30+125+2.85K	0.84*
4700, 10000, 47000pF,		TBA641	1.90*			Philips 118-148	0.88*
1 MFD 10V, All at 8p*		TBA750	2.20*			Philips 2.2+88	0.69*
each. 1MFD33V 8p*.		TBA800Q	1.35*			RR1 (RBM) 250+14+156	0.78*
TANTALUM BEAD		TBA81DSQ	1.49*			RR1 (RBM) 56-68	1.07*
15 MFD/35V 13p*		TBA8200	1.20*			15-23-26	0.85*
47 MFD/35V 13p*		TBA920Q	2.80*			37-31-97-168	0.85*
1 MFD/15V 13p*		TBA990Q	2.20*			37-31-97-030	0.85*
6.80 MFD/35V 13p*		TCA270Q	2.20*			26-35-97-59-30	0.85*</

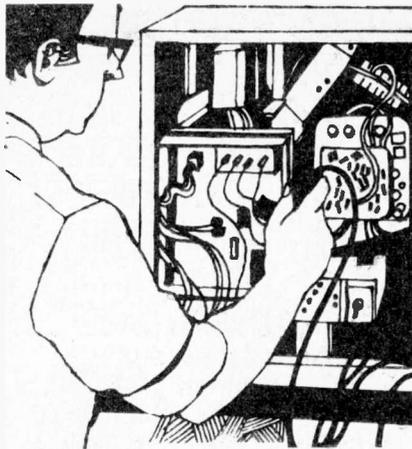

SMALL ADS

The prepaid rate for classified advertisements is 16p per word (minimum 12 words), box number 60p extra. Semi-display setting £3.20 per single column centimetre. All cheques, postal orders, etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

NOTA BENE

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

SETS & COMPONENTS

ELECTRONICALLY TESTED TV VALVES

DY86/7	15p	PC88	15p	PCL805/85	20p
ECC82	15p	PC97	15p	PFL200	25p
EF183	15p	PCF802	15p	PL504	20p
EF184	15p	PCL82	15p	PL506	15p
PC86	15p	PCL84	15p	U26	20p

SPECIAL OFFER - 12 PCL805/85 £2.50 post free

COLOUR TYPES

PL509	45p	PL508	40p	PY500/A	40p
-------	-----	-------	-----	---------	-----

Many others available, please send list of types required with a.e. for quotation. All valves subject to availability. P. & P. 11p first valve, thereafter 7p each, max. 90p. Orders over £12 post free.

Mail order only.

L. & D. COMPONENTS LTD.

71 WESTBURY AVE., LONDON N22 6SA

TIRRO ELECTRONICS the mail order division of RITRO ELECTRONICS UK offers a wide range of components for the amateur enthusiast. Large S.A.E. or 20p brings list. Grenfell Place, Maidenhead, Berks. SL6 1HL.

VALVE BARGAINS

ANY 1-12p, 5-60p, 10-£1.00, 50-£4.50

ECC82, ECH84, EH90, DY86/7, EF80, EF183, EF184, PC86, PC88, PCF80, PCF802, PCL82, PCL84, PCL85/805, PCL86, PY81, PY800, PY88, PL36, PL504, 6F28, 30PL14.

COLOUR VALVES 30p EACH

PY500/A, PL508, PL509.

Postage & Packing 25p, no VAT

VELCO ELECTRONICS

9 Mandeville Terrace, Hawthorn, Via Bury, Lancs.

74H00 20p, 2102 £1.85, BC108C 10p, MJE3055 50p, TIL209 + Clip 15p, BF195 10p, BC213 10p, BC183 10p, OCP70 20p, 10p P/P.
LB ELECTRONICS, 43 Westcott, Hayes, Middx.

BRC 2000, 3000, 3500, 8000, 8500.

Philips G8, Pye 691, 697, 713.

Bush Murphy 802, 823.

G.E.C. 2100 Single Standard Hybrid Panel Repair/Exchange Singles or Bulk.

MODULAR ELECTRONICS

160 Brabazon Road, Hounslow, TW5 9LP.
Telephone 01-897 0976.

SETS & COMPONENTS

BARRON ELECTRICAL WHOLESALE IN IRELAND NOW OFFER QUALITY USED

TV's TV's TV's TV's

MONO: THORN 950's, 1400's, PYE 169's, 368's, ALL SIZES FROM £12.50.

COLOUR: BUSH, PHILIPS, PYE, FROM £100, CLEAN CABINETS. BULK DISCOUNTS AVAILABLE.

VIEW AT OUR WAREHOUSE, STOCK CHANGING CONTINUALLY.

COMPONENTS: VALVES, RESISTORS, CAPACITORS, TRANSISTORS, REGUNNED TUBES. THIS MONTH'S SPECIAL - LABGEAR "TELE-VERTA'S" £20 inc. VAT. UHF MULLARD ELC1043, EX-EQUIP. £2. G8 Tuners on P.C. £4. FUBA H/G AERIALS XC391 GROUP A, NOW ONLY £16.70 ON VAT 20%. P.P. £1. NO VAT FOR UK BUYERS PERSONAL CALLERS WELCOME. S.A.E. FOR PRICE LISTS.

57 RIVERVIEW ESTATE, GLASHEEN, CORK, IRELAND.

PHONE NO. 021-45465.

COLOUR TV's

Many working for disposal, trade only. All sizes and makes available. Mono sets also available.

INGERTONE (LONDON)

24 Dames Road, Forest Gate, London E7.

Tel: 01-555 5569.

INGERTONE (BRISTOL)

28 St. Thomas St., Bristol 1.

Tel: 0272-211179 (5063)

TV TUBE REBUILDING PLANT

Western-Whybrow TV Tube Rebuilding Plant was selected by two of U.K.'s largest TV Rental Firms as being "Vastly Superior" and "unquestionably better" than any other equipment available in Europe.

Staff can be fully trained before installation of Plant. Design and manufacture is backed by twenty years experience of tube rebuilding, and extensive USA experience.

If you can afford the best, contact Western Whybrow Engineering, Praa Sands, Cross Roads, Penzance. (073 676 2265).

4lbs BRAND-NEW COMPONENTS! Transistors, Diodes, Wire-wound/Carbon Resistors, Volume Controls, Presets, Electrolytic/Silver-Mica/Polyester/Polystyrene Capacitors Etc. Well assorted. £5. Inclusive. Milward, 369 Alum Rock Road, Birmingham B8 3DR.

VALVE LIST

ALL VALVES FULLY TESTED

Five valves or over postage paid
Under five valves postage 6p each

DY86/87	15p	PC900	8p	PCL85/805	20p
EB91	12p	PCC84	8p	PL36	20p
ECC82	10p	PCC85	20p	PL504	25p
ECL80	8p	PCC89	8p	PY32/33	15p
EF80	8p	PCC189	8p	PY81/800	15p
EF85	8p	PCC805	15p	PY801	20p
EF183	10p	PCF80	8p	U191	15p
EF184	10p	PCF86	15p	6F23	15p
EH90	13p	PCF805	20p	6/30L2	15p
EY86/87	13p	PCL82	15p	30F5	10p
PC86	15p	PCL83	15p	30FL1	20p
PC88	15p	PCL84	15p	30PL14	15p

AND MANY MORE AVAILABLE

S. W. ELECTRONICS

114 Burnley Road, Rawtenstall, Rossendale, Lancs.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement.

EX RENTAL TV

19" UHF 625 £4.50

23" UHF 625 £6.00

Colour from £40.00

EDWARDS & SONS

103 Goldhawk Road, London W12

Tel: 01-743 6996

MAINS DROPPERS

Philips G8 475	40p
Philips G8 2-2-680	60p
Philips 210 118-148-Loop	70p
Philips 210 30-125-2K85	70p
Philips GT23 6-124-84	70p
Thorn 3500 6-1-100	70p
Thorn 1500 350-20-148-1500-317	85p
Thorn 8000 56-1K-47-12	85p
Pye 725 27-56	60p
R.B.M. TV161 250-14-56	65p
GEC 2108 8-15-17-70-63-188	85p
Thorn 800/850 37-31-97-26-168	60p
Thorn Dual 14-26-97-173	60p
14-26-97-160	60p
15-19-20-70-63-28-63	60p
TV Condenser - 200 + 200 + 100 mfd	80p each
300 V	

Post Free, Cash with order, VAT paid.

Durham Supplies

367 Kensington Street, Bradford 8, West Yorkshire

TV SPARES PHILIPS · TCE · GRUNDIG TELEVIEW

01-994 5537

194 ACTON LANE,
LONDON W.4.

TELEVISION TELETEXT - Input Logic Board, built, untested; Transformer; 10,000mF Capacitor; cost £35; all for £22 including post; Telephone Hawarden 533556.

SURPLUS STOCK

COLOUR TUBES used from	£10
S/S COLOUR TUBES new from	£25
S/S P.I.L COLOUR TUBES new from	£25
PORTABLE TUBES Mono Available	
CABINETS, COLOUR, MONO, from	£2
S/S COLOUR SETS MURPHY from	£60
S/S & D/S MONO, from	£5

RING:- JEFFRIES 01-845 2036.

LADDERS

ALUMINIUM Roof Crawlers. Sizes 12ft - 24ft. Also make aluminium ext. up to 62ft. Leaflets. The Ladder Centre (TEL) Halesfield (1), Telford. Tel: 586644. Callers welcome.

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS, RECORD PLAYERS, TAPE RECORDERS, ETC.

SERVICE SHEETS 75p PLUS S.A.E. SERVICE SHEET CATALOGUE 50p

BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

SOLID STATE COLOUR TELEVISION CIRCUITS by G. R. Wilding	£6.20
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 1	£8.60
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 2	£8.60
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 3	£8.60
COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition	£7.30
COLOUR TELEVISION THEORY by G. H. Hutson	£6.80
COLOUR TELEVISION PICTURE FAULTS by K. J. Bohlman	£2.90
COLOUR TV WITH REFERENCE TO THE PAL SYSTEM by G. N. Patchett	£5.70
MAZDA BOOK OF PAL RECEIVER SERVICING by D. J. Seal	£5.60
TELEVISION (COLOUR & MONOCHROME) Part 3 by G. N. Patchett	£4.35
TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition	£6.10
BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition	£2.65
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition	£2.65
CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett	£4.00
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition	£5.35
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. Revised Edition	£5.25

(SEND LARGE S.A.E. FOR FREE BOOK LISTS)

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.
FROM VOLUME ONE UP TO 1976-77 EDITION. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 25p POSTAGE PER COPY.

P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, R. CONSTRUCTOR, ELECTRONICS TODAY, ELEKTOR.

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

COLOUR TV MANUALS

COVERING FOLLOWING MAKES

ALBA, BRC, BUSH, DECCA, GEC, DEFIANT, MARCONI, EKCO, PYE, FERGUSON, DYNATRON, NATIONAL, HITACHI, INVICTA, ITT/KB, RGD, GRUNDIG, SOBELL, STELLA, SONY, MURPHY, PHILIPS, HMV, ULTRA.

PLEASE SEND S.A.E. FOR QUOTATION

"COMPREHENSIVE TV REPAIR MANUALS" by McCourt. In 7 Volumes

These unique Books save time and money on repairs and cover most British Colour & Mono sets. Price £4.00 per volume plus 45p POST, or complete 7 volumes for only £27.00 POST FREE. SEND FOR FREE LEAFLET.

LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS

TV, RADIO, TUNERS, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS. ALL AT 75p EACH EXCEPT COLOUR & CAR RADIOS.

PLEASE STATE IF CIRCUIT WILL DO, IF SERVICE SHEET NOT IN STOCK. LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS OTHERWISE CANNOT BE ATTENDED TO. UNCROSSED P.O.s OR CROSSED P.O.s RETURNED. IF SERVICE SHEETS ARE NOT AVAILABLE. ALL SERVICE MEN, PLEASE NOTE. WE OPERATE A SAME DAY RETURN SERVICE. ALL CLAIMS OF NON-DELIVERY SHOULD BE MADE WITHIN SEVEN DAYS. NO OVERSEAS MAIL PLEASE. MAIL ORDER ONLY OR PHONE 01-458 4882. FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER.

C. CARANNA, 71 BEAUFORT PARK, LONDON, NW11 6BX.
NO CALLERS PLEASE

SERVICE SHEETS - COLOUR TV SERVICE MANUALS

Service Sheets for Mono TV, Radios, Record Players and Tape Recorders 75p.

Please send large Stamped Addressed Envelope.

We can supply manuals for most makes of Colour Television Receivers by return Post.

**B.R.C. PYE EKCO PHILIPS ITT/KB SONY G.E.C. HITACHI BAIRD ULTRA INVICTA
FERGUSON H.M.V. MARCONI AND MANY MORE. LET US QUOTE YOU.**

Please send a Stamped Addressed Envelope for a prompt reply.

COMPREHENSIVE TV REPAIR MANUALS BY J. McCOURT

Mono Volumes 1, 2, 3 and 4. Colour Volumes 2, 3 and 4.

A must for the repair man, loaded with faults and cures, all at £4.00 each plus 40p post.

Build yourself "The Colour TV Signal Injector", manual £1.45. Manual with printed circuit £2.30 post paid.

The McCourt circuit diagram manuals Mono and Colour. Send S.A.E. for full details.

Export enquiries welcome. International Reply Coupon please.

G. T. TECHNICAL INFORMATION SERVICE

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA
MAIL ORDER ONLY

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo etc. With free fault-finding guide, from 50p and S.A.E. Catalogue 25p and S.A.E. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio, TV, etc., 10,000 models. Catalogue 24p plus S.A.E. with orders/enquiries. Telray, 154 Brook Street, Preston, PR1 7HP.

BOOKS & PUBLICATIONS

SIMPLIFIED TV Repairs. Full repair instructions individual British sets £4.50, request free circuit diagram. Stamp brings details unique. TV Publications, (Auset) 76 Church Street, Larkhall, Lancashire.

AERIALS

WRIGHT'S AERIALS

High gain arrays: Antiference XG8 £15.00, XG14 £25.00, XG21 £36.00. Jaybeam MBM48 £13.90, MBM88 £25.30. Full installation instructions. Labgear UHF mast-head amplifiers with mains power supply £22.80. Wideband or grouped. Send large SAE and 14p in loose stamps for lists, details, technical advice, etc. Very wide range of aerials and accessories in stock. Prices include mainland carriage and VAT. Semi airspaced coax cable 16p/metre (p. & p. 50p if ordered separately).

3 CHELTENHAM RISE,
SCAWSBY, DONCASTER, S. YORKS.

AERIALS FOR FM & TV

Types for all Bands I to V available

TV UHF - Fuba XC 391 £38.90, DX87 Ch21-60 £22.75, DX43 Ch21-68 £14.50, Exa08 Panel Ch21-68 £11.25.

FM - Fuba Uka St. 8 £33.33, DX8-H £22.75, DX7-H £19.00, DX5-H £12.50.

All above have anodised alloy finish.

Cables, Rotators, Masts, Lashings, M/H Amps, Dist Amps etc.

Carriage free mainland UK orders above £25. Carr. £1 otherwise.

Audio Workshops Ltd., 33 London Road, Southborough,

Tunbridge Wells, Kent, TN4 0PB. Tel: Tun. Wells (0892) 39222.

Access/Barclaycard.

FOR SALE

Radio & TV Servicing 1972-1976 Volume Library (Four Books, Brand New). All for £15. Telephone: 01-743 8565.

BARGAINS GALORE, genuine new T.V. spares at prices you can't afford to miss, immediate despatch. Absolutely thousands in stock. E.g. transistors, panels, scan coils, diodes, multi-section electrolytics, condensers, pulse ceramics, disc ceramics, cables, plugs, connectors, lamp holders, etc. Free detailed lists. S.A.E. please. P.H.S., 18 Digby Avenue, Mapperley, Nottingham. MAIL ORDER ONLY PLEASE.

COMPLETE 22" Project Colour Receiver in cabinet. Needs setting up. Also, cross-hatch generator and relevant copies of 'Television'. First reasonable offer secures. Telephone: Telford 461308.

FOR SALE



TOP U.K. SOURCE FOR QUALITY USED T.V.

10,000 mono & 5,000 CTV always available

Stable competitive prices – delivery arranged – generous quantity discounts – used spares always in stock.

TRADE ONLY Colour from £15.00 Mono from £2.00

**Colour Televisions From £25.00 VAT inc.
D/S Mono From £4.00 VAT inc.
S/S Square Screens From £12.00 VAT inc.**

**VISIT OUR WAREHOUSE AND SEE FOR YOURSELF.
WE HAVE 4 DELIVERIES OF FRESH STOCK WEEKLY.**

TELECARE

BRITAIN'S LARGEST USED T.V. DISTRIBUTOR.

**Unit B.1, Eley Road, Eley Estate,
Edmonton, London N18.
Tel: 01-807 5908/9 807 5900.**

"TELEVISION" COLOUR RECEIVER. Panels assembled/aligned. 25" shadow mask tube. Good cabinet. Nearly completed. £65. Folkestone 76598.

Owing to bereavement coloured television parts, tools, tubes, leaflets, television books from 1963. Liphook 724380.

WANTED

GRUNDIG Remote control colour Television wanted. Model 6010 or 6011. Working or not. Telephone 0782 535898.

SURPLUS??? Turn it into cash. Phone 0491-35529 (Oxon).

WANTED – New Valves, Transistors. Top prices, popular types. Kensington Supplies (A), 367 Kensington Street, Bradford 8, Yorkshire.

**WANTED FOR CASH
COLOUR & B/W T.V.'s ANY
QUANTITY – WILL COLLECT
SHEFFIELD PANEL REPAIRS
RING 0742 745168.**

NEW VALVES and CRT's required. PCL805, PL504, PL509, PY500A etc. Cash waiting. Bearman, 6/8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

EDUCATIONAL

**BETTER JOB!
BETTER PAY!**

**GET QUALIFIED WITH ICS IN:
COLOUR & MONO TV SERVICING
COLOUR & MONO TV ENGINEERING
COLOUR & MONO TV MAINTENANCE**

PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,

NEW: Self-build radio courses with free kits
Train in your own home, in your own time with ICS, the world's most experienced home study college.

RETURN THIS COUPON TODAY FOR FREE BROCHURE!

ICS Int Correspondence Schools
800P Intertext House Stewarts Rd
London SW8 4UJ. Tel: 01-622 9911

Name

Address

TELEVISION TRAINING

12 MONTHS' full-time course in Radio & TV for beginners. (GCE – or equivalent – in Maths. and English.)

26 WEEKS' full-time course in Mono & Colour TV. (Basic electronics knowledge essential.)

13 WEEKS' full-time course in Colour TV. (Mono TV knowledge essential.)

These courses incorporate a high percentage of practical training.

NEXT SESSION starts on January 3rd.

PROSPECTUS FROM:
London Electronics College, Dept. TT12
20 Penywern Road, London SW5 9SU.
Tel. 01-373 8721.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for insertions. I enclose Cheque/P.O. for £
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME

ADDRESS

Send to: Classified Advertisement Manager,
TELEVISION,
G.M.G. Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846.
Rate
16p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Get a great deal from Marshall's

A. MARSHALL (LONDON) LTD. Dept: TV
LONDON - 40-42 Cricklewood Broadway, NW2 3ET
Tel: 01-452 0161/2 Telex: 21492
LONDON - 325 Edgware Road, W2. Tel: 01-723 4242/3.
GLASGOW - 85 West Regent St., G2 2OD. Tel: 041-332 4133
BRISTOL - 1 Straits Parade, Fishponds Rd., BS16 2LX. Tel: 0272 654201
Call in and see us 9-5.30 Mon.-Fri., 9-5.00 Sat. Trade & export enquiries welcome
NEW CATALOGUE 77
2nd edition for Autumn with over 8,000 line items. Plenty of new products and ideas.
35p post paid (25p to callers).

Our range covers over 8,000 items. The largest selection in Britain.

TOP 200 IC's TTL LINEARS

CA3018	0.81	LM380N-8	0.90	LM1845N	1.35	SN76008KE	2.50	TA4320A	1.15
CA3018A	1.08	LM380N14	0.98	LM1848N	1.80	SN76013N	1.70	TA4350A	2.48
CA3020	1.78	LM381AN	2.45	LM3900N	0.75	SN76013ND	1.57	TA4521	1.00
CA3020A	2.29	LM381N	1.60	LM3909N	0.68	SN76018KE	2.50	TA4522	1.90
CA3021	2.18	LM382N	1.25	MC1303L	1.47	SN76023N	1.90	TA4550	0.60
CA3022	1.83	LM384N	1.45	MC1304P	1.85	SN76023ND	1.57	TA4570	2.30
CA3023	1.78	LM386N	0.80	MC1305P	1.85	SN76033N	2.55	TA4818	1.85
CA3036	0.87	LM387N	1.05	MC1308P	1.00	SN76110N	1.48	TA4821	2.15
CA3041	1.48	LM388N	1.00	MC1310P	1.91	SN76115N	1.87	TA4861A	1.32
CA3042	1.49	LM389N	1.00	MC1312P	1.98	SN76116N	2.06	TA4861B	1.32
CA3043	2.01	LM555CH	0.48	MC1327P	1.54	SN76131N	1.30	TA4700	3.91
CA3044	1.54	LM555CN	1.30	MC1350P	0.75	SN76131M	1.30	TA4930A	1.00
CA3046	0.89	LM701C	2.80	MC1351P	1.20	SN76228N	1.94	TA4930B	1.05
CA3046	2.23	LM702A	2.80	MC1352P	0.97	SN76228N	1.75	TA0100	1.95
CA3052	1.82	LM702C	0.75	MC1357P	1.45	SN76228N	1.75	TA0120	0.85
CA3064	1.84	LM703LM	1.05	MC1414L	1.20	SN76530N	0.91	TB231	1.20
CA3065	1.74	LM709	0.85	MC1430P	2.20	SN76532N	1.50	TB4000	1.50
CA3066	3.02	LM709-9	0.45	MC1431P	3.00	SN76533N	1.30	TB4500	2.21
CA3067	3.13	LM709-14	0.46	MC1433G	3.00	SN76544N	1.44	TB4500	2.30
CA3068	3.48	LM711CN	0.55	MC1435G	1.80	SN76545N	2.05	TB4510	2.21
CA3070	2.49	LM726	5.38	MC1437L	1.80	SN76549N	1.44	TB45100	2.30
CA3071	2.31	LM733CN	1.46	MC1438R	7.48	SN76550-2	0.41	TB4520	2.21
CA3072	2.37	LM741C	0.85	MC1439G	1.45	SN76552-2	0.65	TB45200	2.30
CA3075	1.88	LM741C-8	0.48	MC1458G	1.55	SN76570N	2.08	TB4530	1.98
CA3078	1.93	LM741C-14	0.50	MC1458G	2.20	SN76570N	2.08	TB45300	2.07
CA3086	0.51	LM747CN	0.90	MC1495L	4.70	SN76580N	1.10	TB4540	2.21
CA3086F	1.50	LM748-8	0.50	MC1496G	1.10	SN76600N	0.60	TB4550	3.13
CA3089E	2.52	LM748-14	0.50	MC1529G	8.50	SN76688N	0.92	TB4560CC	3.22
CA30900	3.80	LM1303N	1.47	MC1530G	8.50	SL414A	2.35	TB4570	1.29
LM301AH	0.87	LM1304N	1.85	MC1531G	8.50	SL415	2.50	TB4641B	2.50
LM301-B	0.44	LM1305N	1.85	MC1531G	8.50	SL810C	2.35	TB4700	1.52
LM308H	1.82	LM1307N	1.10	MC1545L	6.75	SL611C	2.35	TB4720AD	2.30
LM308N	1.17	LM1351N	1.20	MC1545L	6.75	SL612C	2.35	TB4750	1.98
LM370N	3.00	LM1310N	1.91	MC1550G	0.80	SL820C	3.50	TB4800	1.20
LM371H	2.25	LM1458N	0.91	MC1552G	8.40	SL821C	3.50	TB4820	1.03
LM372N	2.15	LM1498N	0.91	MC1553G	8.40	SL823C	5.75	TB4920	2.80
LM373N	2.25	LM1800N	1.78	MC1553G	8.40	SL830C	2.35	TB4940	1.82
LM374N	2.25	LM1808N	1.92	MC1590G	3.75	SL840C	4.00	TCA180A	1.61
LM377N	1.76	LM1820N	1.10	SAS570	2.50	SL841C	4.00	TCA280A	1.30
LM378N	2.25	LM1841N	1.75	SN76003N	2.55	SL701C	2.00	TCA290A	3.13
LM379S	3.95	LM1828N	1.75			TAA263	1.25	TCA740	2.78
						TAA300	1.89	TC4800	3.13

WHY NOT PAY US A VISIT AT OUR NEW CENTRAL LONDON BRANCH AT 325 EDGWARE ROAD, W2, ABOUT 100 YARDS NORTH OF THE WESTWAY FLYOVER. EXTENSIVE STOCK RANGE. MANY SPECIAL OFFERS TO PERSONAL SHOPPERS ONLY.

TELEVISION TELETEXT DECODER

We can supply from stock complete kits of parts -

POWER SUPPLY EXCLUDING TRANSFORMER AND P.C. BOARD £12.50 + 65p P&P + 8% VAT.

INPUT LOGIC CARD UNIT EXCLUDING P.C. BOARD £15.50 + 50p P&P + 8% VAT.

MEMORY CARD KIT £32.00 + 60p P&P + 8% VAT.

DISPLAY CARD KIT £18.50 + 40p P&P + 8% VAT.

TV GAMES IN COLOUR - as featured in the July issue of this magazine. We can now offer complete kits of parts excluding the P.C. Boards at £35.00 delivered including VAT and p&p. Alternatively sets of TV Games Chips only, at £17.00 per set delivered including VAT and p&p.

We also carry a comprehensive range of transistors, diodes, bridges, thyristors, diacs, opto components, all kinds of integrated circuits, capacitors, resistors, plugs and sockets. ALL MANUFACTURERS BRANDED PRODUCTS.

Prices correct at 19 October, 1977, but please add VAT, p&p 40p.

TRAIN for SUCCESS

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs - they can do the same for *you*.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians' Radio TV Electronics Technicians' Electrical Installations Technicians' Electrical Installation Work Radio Amateurs'

MPT Radio Communications Cert.

EXAMINATION STUDENTS - GUARANTEED COACHING UNTIL SUCCESSFUL

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including: Electronic Engineering & Maintenance Computer Engineering/Programming Radio, TV & Audio Engineering & Servicing Electrical Engineering, Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

Occupation

ICS

Accredited by CACC
Member of ABCC

To: International Correspondence Schools, Dept. 283P Intertext House, LONDON SW8 4UJ or phone 01-622 9911 (all hours)

LOOK!

Phone: LUTON, BEDS. 38716

OPPORTUNITIES TRADE SALES

START AT £25 INC. VAT!!

FOR D/S COLOUR TV's
G.E.C., Philips, Murphy, Decca, Ferguson

S/S COLOUR TV's
Philips, G.E.C., Telefunken, Decca, Ferguson

FROM £40 INC. VAT!!

MONO TV's, all makes from
£5 INC. VAT

SQUARE SCREEN, all models
£12 INC. VAT!!

Deliveries arranged if necessary.

HUNDREDS OF SETS EACH WEEK TO BE
DISPOSED OF AT GIVE-AWAY PRICES.

LUTON 38716

9.30-6.00 p.m. Weekdays
10.30-1.00 p.m. Sundays

SIDS Components

FAST, RELIABLE AND COMPETITIVE

SIDS full stock + price list available -
Just telephone 061.480 8244 or write to
- SIDS (Electronic Components) Ltd.
251, Wellington Road South, Stockport,
Cheshire.

TV Replacement Mains Droppers

MANUFACTURER	CHASSIS	MAKERS CODE	VALUES	SIDS ORDER CODE	SIDS PRICE EACH (p)
T.C.E.	1400	06E5.016	128R+16R+1K7+118R+462R+126R	C121	85
	1500	06E5.018	350R+20R+148R+1K5+317R	C113	63
	3000/3500	00E5.071	6R+1R+100R	C105	53
	8000	90E5.006	56R+1K+47R+12R	D123	59
	8500	90E5.007	50R+40R+1K5	D127	70
PHILIPS	210	50501	30R+125R+2K85	D112	49
	210	50511	118R+148R+L00P	D108	41
	G8	50811	47R	C103	24
	C10	50832	2R2+68R	C102	39
PYE	725	PL10662	27R+56R	O106	44
		PL10664			
G.E.C.	2018	27840	8R+15R+17R+70R+63R+188R	OS114	55
R.R.I.	TV161	AP48928	250R+14R+156R	D109	39
	A823		56R+68R	D150	63

POWER WIREWOUND RESISTORS - DROPPER SECTIONS
OVAL SECTIONS 25mm x 25mm x 7mm
WATTAGE 12W
ORDER CODE F104/VALUE REQUIRED
VALUES 4R7 7R5 10R 12R 15R 18R 22R 24R 27R 33R 39R 47R 51R 56R 68R 75R 82R 100R 120R 150R 180R 200R 220R

PRICE 0.25p EACH

Diodes

TYPE	PRICE (p)
BA 115	16
BA 145	18
BA 148	18
BA 154/201	12
BA 155	14
BAX 13	5
BAX 16	9
BY 126	12
BY 127	13
BY 133	20
BY 199	25
BY 206	18
BYX 10	14
OA 47	10
OA 90	6
OA 91	7
OA 95	7
OA 202	9
IN 914	5
IN 4001	6
IN 4002	6
IN 4003	7
IN 4004	8
IN 4005	6
IN 4006	10
IN 4007	10
IN 4148	4

Valves

TYPE	PRICE EACH (p)
DY 87	56
DY 802	57
ECC 82	46
EF 80	40
EF 183	46
EF 184	46
EH 90	46
PC 86	69
PC 88	57
PC 900	56
PCF 189	57
PCF 80	49
PCF 86	55
PCF 801	60
PCF 802	62
PCL 82	63
PCL 85	57
PCL 84	63
PCL 86	60
PCL 86	60
PFL 200	75
PL 36	69
PL 84	51
PL 504	99
PL 508	105
PL 509	195
PL 519	270
PY 88	52
PY 500A	137
PY 800	52

ORDER NOW!

Integrated Circuits

At New Low Prices following Bulk purchase of New Plessey and Toshiba Stocks.

TYPE	PRICE (p)
MC 1349	160
ML 2318	230
ML 2328	230
SL 414A	240
SL 415A	280
SL 1310	160
SL 1327	115
SL 3046	82
SL 76544	140
SN 76003N	180
SN 76013N	140
SN 76013ND	124
SN 76023N	140
SN 76023ND	124
SN 76033N	180
SN 76110N	142
SN 76226N	180
SN 76227N	140
SN 76532N	160
SN 76533N	140
SN 76544N	150
SN 76550N	120
SN 76660N	70
SN 76666N	100
TA 7050P	125
TA 7051P	140
TA 7072P	170
TA 7047P	150
TA 7141AP	120
TA 7171P/SAS	186
TA 560S	186
TA 7172P/SAS	186
TA 7173P	160
TA 7176P	120
TAA 550	45
TAA 570	185
TAA 661B	100
TAA 700	165
TBA 120AS	80
TBA 120S	100
TBA 440	300
TBA 4800	140
TBA 5200	170
TBA 5300	130
TBA 5400	150
TBA 5500	200
TBA 5600Q	210
TBA 7500	150
TBA 800	120
TBA 9200	210
TBA 9900	180
TCA 2700	225
TCA 800	225
TDA 440	310

NO MINIMUM ORDERS!
CASH WITH ALL ORDERS
ADD 12% VAT PLUS 25p POSTAGE.

EHT Trays

TYPE	DESCRIPTION	PRICE EACH (p)
101/TH	Thorn 950 Mk 11 1400	2.35
102/TH	Thorn 1500 3 Stick	2.30
103/TH	Thorn 1500 5 Stick	2.50
104/TH	Thorn 1500 Stick	40
105/IT	ITT Philips Mono Large Screen	72
106/RA	Rank Z 718	1.82
107/TH	Thorn 3000/3500	6.00
108/TH	Thorn 8000	2.30
109/TH	Thorn 8500	4.40
110/TH	Thorn 9000	6.60
111/OE	Decca Doubler	3.20
112/OE	Decca 30 Series	5.30
113/OE	Decca 80 Series	5.80
114/GE	G.E.C. Hybrid	5.30
115/GE	G.E.C. Solid State	5.80
116/IT	ITT CVC 1-5	5.30
117/IT	ITT CVC 20	5.80
118/PH	Philips G8	5.30
119/PH	Philips 550	5.30
120/PV	Pye 691/693	4.40
121/PY	Pye 731	5.80
122/RA	Rank A823	5.30
125/KO	Korting	5.30
126/MU	Telefunken/Carnival/Hamilton Sceptophone	5.30
128/PH	Philips G9 T25 DB	5.80
129/DE	Decca 100 T30 AV	5.80

Subject to 10% Discount - 5 of any one type or 10 mixed types.

Resistors

Power Wirewound	Price (p)	Trade Pack Qty.
10 Watt		
Style Axial Leads - cement coated		
Range 10R 12R 25R 33R 39R 47R 50R 68R 75R 82R 100R 120R 150R 180R 220R 250R 270R 330R 400R 470R 500R 550R 1K0 2K2 3K3 6K0 8K0 10K	60	(5)
5 Watt		
Style Radial Leads - cement coated		
Range 10R 15R 25R 33R 47R 68R 82R 100R 120R 150R 180R 220R 270R 330R 390R 470R 560R 680R 820R 1K 1K2 1K5 1K8 2K2 2K7 3K3 3K9 4K7 5K6 6K8 8K2 10K 12K	60	(5)
2.5 Watt		
Style Radial Leads - cement coated		
Range R22 R33 R50 1R0 1R5 2R2 2R7 3R3 3R9 4R7 5R6 6R8 8R2 10R	60	(5)

RESISTORS: High Stability Carbon Film E.12 Range
Power Ratings: 0.5W 1.0W & 2.0W watts.
0.5W rated at 70°C.
1.0W & 2.0W rated at 40°C.
Tolerance 5%.
Style - Axial Leads
Values 10R 12R 15R 18R 22R 27R 33R 39R 47R 56R 68R 82R 100R 120R 150R 180R 220R 270R 330R 390R 470R 560R 680R 820R 1K 1K2 1K5 1K8 2K2 2K7 3K3 3K9 4K7 5K6 6K8 8K2 10K 12K 15K 18K 22K 27K 33K 39K 47K 56K 68K 82K 100K 120K 150K 180K 220K 270K 330K 390K 470K 560K 680K 820K 1M 1M2 *M5 1M8 2M2 2M7 3M3 3M9 4M7 5M6 6M8 8M2 10M

Price Trade Pack Qty.
0.5W .19 (10)
1.0W .32 (10)
2.0W .52 (10)

Capacitors

Electrolytic: Axial Leads	Value	Vvkg	Dimensions	Price	Trade Pack Qty.
25V WKG Range					
22uF	25	10 x 6mm	0.35 (5)		
47uF	35	18 x 8mm	0.60 (5)		
100uF	25	19 x 8mm	0.40 (5)		
220uF	25	21 x 11mm	1.20 (5)		
470uF	35	32 x 13mm	1.25 (5)		
1000uF	35	40 x 16mm	1.26 (3)		
2200uF	25	39 x 21mm	0.90 (3)		
63V WKG Range					
47uF	63	13.6 x 6.6mm	0.48 (5)		
22uF	70	18 x 7mm	0.50 (5)		
47uF	70	17 x 12mm	0.68 (5)		
100uF	70	32 x 10mm	0.90 (5)		
220uF	63	38 x 13mm	1.20 (3)		
470uF	70	38 x 16mm	1.20 (3)		
1000uF	70	38 x 24mm	1.35 (3)		
450V WKG Range					
1uF	450	28 x 12mm	0.80 (5)		
2.2uF	450	27 x 13mm	0.95 (5)		
4.7uF	450	32 x 13mm	1.05 (5)		
10uF	450	32 x 16mm	1.20 (5)		
15uF	450	40 x 19mm	1.40 (5)		
32uF	450	52 x 26mm	1.75 (5)		

CAPACITORS: Mixed Electric 1000V WKG
New 660 Capacitors (moulded in flame retardant material)

Value	Voltage	Price (p)	Trade Pack Qty.
0.01uF	1000	45	(3)
0.022uF	1000	54	(3)
0.033uF	1000	40	(2)
0.047uF	1000	40	(2)
0.1uF	1000	45	(1)
0.22uF	1000	38	(1)
0.47uF	1000	55	(1)
0.1uF	1250	35	(1)

CAPACITORS: Polyester 600V
Sprague Pum Range 416P Filmits

Value	Dimensions	Price (p)	Trade Pack Qty.
0.01uF	18.2 x 4.8mm		
0.022uF	18.2 x 4.8mm		
0.033uF	18.2 x 5.2mm	50	(5)
0.047uF	18.2 x 5.0mm		
0.1uF	21.4 x 6.9mm		
0.22uF	22.2 x 9.5mm		
0.33uF	25.4 x 10mm	60	(5)
0.47uF	31.8 x 10.2mm		

Multi Section Capacitors

MANUFACTURER	CHASSIS Nos.	CAPACITANCE mfd	VOLTAGE	SIDS ORDER CODE	SIDS PRICE EACH (p)
T.C.E.	1500	150 150 100	350	CMS/5	115
	3000/3500	175 100 100	400/350	CMS/3	185
	8000	1000	63	CMS/4	168
	3000	2500.2500	63	CMS/5	65
R.R.I.	A823	2500.2500	30	CMS/7	115
	A823	600	300	CMS/8	155
PYE	691	200.300	350	CMS/10	180
	697 & 723				
PHILIPS	G8	600	300	CMS/8	155
DECCA	CS1910	400.400	350	CMS/14	245
G.E.C.	02110	600	300	CMS/8	155

YOU'LL GO A LONG WAY FOR A BETTER DEAL

ALL NEW AND BRANDED ITEMS

Semi Conductors

TYPE	PRICE (p)	BC 113	12	BC 213	15	BF 160	30	BRY 52	33
AC 107	28	BC 114	15	BC 213L	13	BF 167	26	BT 106	120
AC 126	27	BC 115	16	BC 214	13	BF 173	24	BT 108	132
AC 127	27	BC 116	16	BC 214L	13	BF 178	30	BT 116	120
AC 128K	33	BC 116A	30	BC 237	15	BF 179	32	BU 105/02	190
AC 141	27	BC 117	17	BC 238	12	BF 180	33	BU 106	200
AC 141K	37	BC 118	17	BC 301	30	BF 181	32	BU 108	160
AC 142	20	BC 119	28	BC 303	31	BF 182	35	BU 204	160
AC 142K	33	BC 125	16	BC 327	20	BF 183	34	BU 205	160
AC 151	31	BC 125B	18	BC 328	18	BF 184	30	BU 206	210
AC 154	20	BC 126	15	BC 337	15	BF 185	28	BU 208	245
AC 155	20	BC 132	15	BC 338	18	BF 186	36	BU 208/02	264
AC 156	31	BC 135	18	BC 546	15	BF 194	12	BU 69B	275
AC 176	24	BC 136	18	BC 547	12	BF 195	12	BU 69A	300
AC 176K	38	BC 137	15	BC 548	10	BF 196	12	E 1222	42
AC 187	20	BC 138	20	BC 549	12	BF 197	13	MJE 340	44
AC 187K	40	BC 139	24	BC 550	15	BF 197A	18	NJE 520	50
AC 188	27	BC 140	38	BC 557	14	BF 198	19	2N 696	25
AC 188K	42	BC 141	26	BC 558	13	BF 199	20	2N 706	16
AC 193K	40	BC 142	24	BCV 72	20	BF 200	30	2N 3053	22
AC 194K	39	BC 143	24	BD 115	60	BF 218	56	2N 3054	72
AD 140	78	BC 147	12	BD 116	60	BF 224	30	2N 3055	60
AD 142	74	BC 147A	12	BD 124	70	BF 240	20	2N 3702	16
AD 143	300	BC 147B	12	BD 131	44				

3500 Thorn Triplers	£3.50	TIP112	25p	VHF Varicap Units		BA159	10p	
LP1193/1Mallard	£2.50	TIP115	25p	New	£2.50	BY184	25p	
TK25KC15BL	£1.50	TIP117	25p	VHF Varicap Units		TAA550	30p	
Ex Panel				New. 49.00-219.00 MHZ	£1.50	TBA510	£1.00	
TS2511TBD	£4.00	100 Mixed Electrolytics				TBA480Q	£1.00	
TS2511TBK	£4.00	1000 MFD to 4 MFD	£2.50	Reject VHF Varicap		TBA550Q	£1.50	
TS2511TDT	£4.00	120 Mixed Pack of		Units	50p	TBA720A	£1.50	
TS2511TBQ	£1.50	Electrolytics & Paper		AE Isolating Socket &		TBA790B131	£1.00	
TS2511TCE	£3.00	Condensers	£1.20	Lead	45p	TBA800	95p	
TS2511TCF	£3.00	100 Green Polyester		6 Position 12.5k		TBA920	£2.00	
TS2511TBH	£3.00	Condensers		V/Resistors Units for		TAA700	£2.00	
1730 Decca	£3.00	Mixed Values	£2.00	Varicap	50p	TBA530Q	£1.00	
Mains Droppers		.1 MFD 2000v	15p	EHT Rectifiers Sticks		TBA550	£2.00	
169R + 161R	20p	.1 MFD 1000v	} EACH	Used in Triplers		SN76544N	50p	
147R + 260R	20p	.01 MFD 1000v			x80/150	12p	SN76640N	£1.00
Thorn Mains Droppers		.047 MFD 1000v			CSD118xMH	12p	SAAS70	50p
6R + 1R + 100R	35p	.0047 MFD 1000v			CSD118xPA	15p	TBA120A	50p
Thorn Mains On/Off		200+200+100M 325v		40p	3 Off G770/HU37		TCA270Q	£2.00
Switches	15p	470+470M 250v	40p	Silicone	15p	TCA270SQ	£2.00	
Thorn 2000 & 3000		100+200M 325v	30p	Bridge Rectifiers		Star Aerial Amps	£4.00	
Series Hearing Aid		200+200+100+32M		1A 100v	20p	CHANNEL B+C	EACH	
External Loudspeaker		350v	70p	2A 100v	25p	TV18	40p	
Unit	£2.00	150+200+200M 300v	50p	3A 100v	50p	TV20	50p	
Focus Unit 3500 Thorn	£1.00	800M 250v	20p	W005M	20p	Rectifier Sticks & Lead		
4 Push Button Unit		600M 300v	£1.00	BY127	10p	BU105	£1.00	
UHF Thorn	£3.50	400M 400v	£1.00	IN4007	20 for £1.00	BU105/04	£1.50	
D.P. Audio Switch	7½p	800+800M 250v	60p	IN4005	20 for £1.00	BU205	£1.90	
4 Push Button Unit for		200+100+100+50M		BYX94 1200v 1 Amp.	15 for £1.00	BU208	£2.00	
Varicap	£1.00	300v	45p	BB105		2N3055	45p	
7 Push Button Unit for		200+200+150+50	£1.00	BA182	Varicap Diodes	BRCD1603	80p	
Varicap	£1.50	100M 450v	25p		12 for £1.00	Thorn		
RIZ243619 Replacement		47M 450v	25p	BY133	12p	BD138	20p	
for ELC 1043		680M 100v	25p	BYX55/350	10p	BD252	20p	
UHF Varicap new	£2.50	6800M 40v	35p	BY210/400	5p	Audio O/P Trans.		
BF127 BC350	} EACH	100M 350v	20p	BY206	15p	RCA16572	} 40p	
BF264 BF178		22M 350v	20p	BT106	95p	RCA16573		} PAIR
BF180 BF121		33000 10v	30p	BT116	95p	BU105 Ex. Panel	} 50p	
BF181 BF257		15000 40v	50p	12 Kv Diodes 2M/A	30p	BU126 Ex. Panel		} EACH
BF182 BF137		220M 10v	} EACH	18 Kv BYF3123 Silicone	30p	5A-300	} 25p	
BF300 BC161		2.2M 100v		180PF 8Kv	10M 350v	TIC106 Thyristors		} EACH
AC128 BF185		22M 100v		1000PF 10Kv	100M 50v	RCA40506 Thyristors	50p	
2N2222		22M 100v		1200PF 10Kv	330M 10v	BC108	7p	
2N3566	4.7M 63v	1000PF 12Kv		330M 25v	BC188	10p		
BC198	1000M 10v	160M 25v	330M 35v	BC149C	7p			
2N1305	4700M 25v	220M 25v	330M 50v	Aerial Amp Power				
MJE2021 90V 80V	15p	1000M 16v	330M 63v	Supplies 15 volts	£1.50			
SJE5451 5A	EACH	300M 100v	330M 10v					
90V 80V 5A NPN	} 28p	330M 10v	470M 25v					
PNP		1000M 63v	220M 35v	470M 35v				
1N5349 Diode	} 10p	3300M 25V	220M 40v	470M 40v				
12v Z/Diodes		1000M 40v	220M 50v	470M 25v				
Mullard UHF T/Units	£1.50	1000M 50v	22M 315v	EACH				
300 Mixed Condensers	£1.50	1500M 25v						
300 Mixed Resistors	£1.50	1000M 10v						
30 Pre-Sets	50p	1500M 40v						
100 W/W Resistors	£1.50	1000M 25v						
40 Mixed Pots	£1.50	1500M 50v						
20 Slider Pots	£1.50	4700M 16v						
		1000M 16v						
		100M 63v						

SENDZ COMPONENTS

2 WOOD GRANGE CLOSE,
THORPE BAY, ESSEX.

Reg. Office only -
No personal callers. Thank you.
Free Postage applies in U.K. only.

PLEASE ADD 12½% VAT