

SEPTEMBER 1979

Australia 95c; Malaysia \$2.75; New Zealand 95c

55p

TELEVISION

SERVICING VIDEO CONSTRUCTION DEVELOPMENTS




**SERVICING PYE SOLID-STATE
COLOUR RECEIVERS
RECEIVING FRENCH TV
NEW TELETEXT SIGNAL PANEL
THE V2000 VCR SYSTEM**

PHD COMPONENTS
RADIO & TV COMPONENT DISTRIBUTORS
UNIT 7 CENTENARY ESTATE
JEFFRIES RD ENFIELD MIDDX
MAIL ORDER ONLY TELEX 261295

ALL COMPONENTS OFFERED SUBJECT TO AVAILABILITY. WE RESERVE THE RIGHT TO SUBSTITUTE REPLACEMENTS SHOULD THE ORIGINAL PART BE OUT OF STOCK OR UNAVAILABLE!
PLEASE ADD 0.35p per parcel post and packing.

SEMICONDUCTORS

AA113	0.16	BC117	0.20	BU208.02	3.00
AA116	0.16	BC118	0.20	BU3265	1.50
AA117	0.16	BC125	0.50	BU406	2.00
AA119	0.16	BC126	0.20	BU407	2.50
DA91	0.12	BC136	0.20	BU407D	2.50
DA95	0.12	RC137	0.20	R2008B	2.50
OA202	0.18	BC138	0.40	R20108	2.50
BA100	0.18	BC139	0.40	R2940	3.00
BA102	0.10	BC140	0.40	ME402	0.20
BA130	0.15	BC142	0.40	ME402	0.20
BA154	0.10	BC143	0.40	ME4003	0.15
BA155	0.20	BC147	0.15	ME6002	0.20
BA164	0.12	BC148	0.10	ME8001	0.20
BA163	0.16	BC149	0.15	MJE2295	1.50
BAX16	0.08	BC153	0.15	MJE3005	1.30
BAY38	0.16	BC154	1.00	MP8113	1.00
BY206	0.20	BC157	1.00	MPSU05	0.15
IN4148	0.04	BC158	0.15	MPSU55	1.20
BY126	0.20	BC159	0.15	TIP2955	1.30
BY127	0.15	BC160	0.40	TP3055	1.30
BY133	0.22	BC161	0.40	TIS90M	0.60
BY164	0.50	BC170	0.15	TIS91M	0.50
SKB2.08	1.00	BC171	0.15	2N2904	0.50
BY238	0.15	BC172	0.20	2N2905A	0.20
BYX10	0.18	BC177	0.40	2N2905	0.50
IN4001	0.10	BC178	0.20	2N3053	0.50
IN4002	0.10	BC179	0.20	2N3703	0.20
IN4003	0.12	BC182L	0.15	2N3705	0.20
IN4004	0.12	BC183L	0.15	2N3710	0.20
IN4005	0.12	BC184L	0.15	2N3755H	0.75
IN4006	0.14	BC184L.C	0.20	TAA350	0.80
IN4007	0.16	BC186	0.30	TAA550	0.60
IN5407	0.33	BC187	0.30	TAA570	1.80
BR100	0.50	BC203	0.15	TAA611	1.75
BR101	0.60	BC204	0.15	TAA6305	2.50
BRV39	0.60	BC205	0.15	TAA661B	2.00
TIC1160N	1.50	BC206	0.15	SN76540N	1.50
BT119	2.50	BC207	0.15	TAD100	2.00
BT120	2.50	BC208	0.15	TBA120AS	0.75
BYX 71 600	0.80	BC209	0.15	TBA231	2.20
2N444	1.50	BC212L	0.15	TBA480Q	2.20
TV106 2	1.50	BC213L	0.15	TBA520Q	2.00
BYX89C2V7	0.10	BC214L	0.15	TBA530	2.00
BZV88 3V0	0.10	BC225	0.40	TBA530Q	2.00
BZV88 3V3	0.10	BC227	0.15	TBA540	2.20
BZV88 3V6	0.10	BC238	0.15	TBA540Q	2.20
BZV88 3V9	0.10	BC251A	0.15	TBA550	3.00
BZV88 4V3	0.10	BC301	0.40	TBA560C	3.00
BZV88 4V7	0.10	BC303	0.50	TBA560Q	3.00
BZV88 5V1	0.10	BC307	0.15	TBA560CCO	2.20
BZV88 5V6	0.10	BC308	0.15	TBA570	2.50
BZV88 6V2	0.10	BC327	0.15	TBA570Q	2.50
BZV88 6V8	0.10	BC328	0.15	TBA6418X	1.80
BZV88 7V5	0.10	BC337	0.15	TBA641811	1.00
BZV88 8V2	0.10	BC338	0.15	TBA651	3.00
BZV88 9V1	0.10	BC547	0.15	TBA720A	1.50
BZV88 10V	0.10	BC141.10	0.80	TBA730	1.50
BZV88 11V	0.10	BD115	0.50	TBA750	2.00
BZV88 12V	0.10	BD124	2.00	TBA750Q	2.00
BZV88 13V	0.10	BD131	0.70	TBA800	1.00
BZV88 15V	0.10	BD132	0.60	TBA810S	1.50
BZV88 18V	0.10	BD133	0.70	TBA820	1.50
BZV88 20V	0.10	BD134	0.70	TBA920	2.00
BZV88 22V	0.10	BD144	2.50	TBA920Q	2.00
BZV88 27V	0.10	BD159	0.80	TBA990	2.00
BZV88 33V	0.10	BD238	0.50	TBA990Q	2.00
BZV88 39V	0.25	BD380	0.70	TCA2705A	3.00
BZV88 47V	0.25	BD441	0.70	TC9800	3.00
BZV88 51V	0.25	BD537	0.70	TC9A90	2.00
BZV88 56V	0.25	BD538	0.70	TDA1170	2.00
BZV88 61V	0.25	BD507	0.70	TDA1200	3.00
BZV88 62V	0.25	BD508	0.75	TDA1270	4.00
BZV88 67V	0.25	BD511	1.20	TDA1412	1.00
BZV88 72V	0.25	BD512	1.20	TDA2020	4.00
BZV88 75V	0.25	BD709	1.00	SN76115N	1.20
BZV88 81V	0.25	BD710	1.00	SN76227N	1.20
BZV88 86V	0.25	BD711	0.70	SN7630P	1.00
BZV88 91V	0.25	BD712	0.50	SN76551N	1.50
BZV88 96V	0.25	BD713	0.60	SN76003N	3.00
BZV88 101V	0.25	BF118	0.60	SN76013N	2.00
BZV88 106V	0.25	BF152	0.40	SN76013ND	2.00
BZV88 111V	0.25	BF154	0.20	SN76013ND	2.00
BZV88 116V	0.25	BF155	0.70	SN76023N	2.00
BZV88 121V	0.25	BF156	0.40	SN76023ND	1.00
BZV88 126V	0.25	BF157	0.60	SN76033N	2.00
BZV88 131V	0.25	BF163	0.60	SN76110N	2.00
BZV88 136V	0.25	BF164	0.50	SN76225ND	2.00
BZV88 141V	0.25	BF173	0.50	SN76227N	2.00
BZV88 146V	0.25	BF177	0.50	SN76532N	1.20
BZV88 151V	0.25	BF179	0.50	SN76533N	2.00
BZV88 156V	0.25	BF180	0.50	SN76544N	2.00
BZV88 161V	0.25	BF181	0.60	SN76604	1.00
BZV88 166V	0.25	BF182	0.50	SN76655N	1.50
BZV88 171V	0.25	BF183	0.50	SN76666N	1.20
BZV88 176V	0.25	BF184	0.50	SL910	6.00
BZV88 181V	0.25	BF185	0.50	SL917B	5.00
BZV88 186V	0.25	BF194	0.15	TBA356Q	2.00
BZV88 191V	0.25	BF195	0.15	TDA440	2.50
BZV88 196V	0.25	BF196	0.15	SN76001N	1.50
BZV88 201V	0.25	BF197	0.15	TBA520	2.00
BZV88 206V	0.25	BF198	0.15	TBA120S	1.00
BZV88 211V	0.25	BF199	0.15	UA7824	0.50
BZV88 216V	0.25	BF200	0.15	TBA396	2.00
BZV88 221V	0.25	BF224	0.15	TCA2705O	2.00
BZV88 226V	0.25	BF240	0.15	TDA2030	2.00
BZV88 231V	0.25	BF241	0.15	TDA2140	6.00
BZV88 236V	0.25	BF255L.C	0.50	TDA2150	6.00
BZV88 241V	0.25	BF257	0.50	TDA2160	6.00
BZV88 246V	0.25	BF258	0.50	TDA1230	3.00
BZV88 251V	0.25	BF271	0.60	TDA308	5.00
BZV88 256V	0.25	BF273	0.20	TDA1054M	2.00
BZV88 261V	0.25	BF274	0.25	MC1349P	1.50
BZV88 266V	0.25	BF336	0.50	SAA661	0.60
BZV88 271V	0.25	BF337	0.50	SAS560S	2.00
BZV88 276V	0.25	BF338	0.50	SAS705S	2.00
BZV88 281V	0.25	BF355	0.80	SN7400N	1.80
BZV88 286V	0.25	BF458	1.00	SN7413N	0.40
BZV88 291V	0.25	BF459	0.50	SN7437S	0.90
BZV88 296V	0.25	BF473	0.50	SN74141N	1.00
BZV88 301V	0.25	BFX29	0.50	TBA395	1.80
BZV88 306V	0.25	BFX84	0.50	TBA395Q	1.80
BZV88 311V	0.25	BFX88	0.50	TBA950	4.00
BZV88 316V	0.25	BFY89	0.50	TCAB00	4.00
BZV88 321V	0.25	BFY90	0.50	TCAB90Q	4.00
BZV88 326V	0.25	BFY92	0.50	TDA1180	3.00
BZV88 331V	0.25	BFY93	0.50	TDA1190	3.30
BZV88 336V	0.25	BFY94	1.20	TDA2002H	3.60
BZV88 341V	0.25	BF381	0.50	TDA2590Q	5.00
BZV88 346V	0.25	BF393	0.30	TDA2600	5.00
BZV88 351V	0.25	BF381	0.30	TDA2640	3.30
BZV88 356V	0.25	BF381	0.30	TDA2640	3.30
BZV88 361V	0.25	BF381	0.30	TDA2640	3.30
BZV88 366V	0.25	BF381	0.30	TDA2640	3.30
BZV88 371V	0.25	BF381	0.30	TDA2640	3.30
BZV88 376V	0.25	BF381	0.30	TDA2640	3.30
BZV88 381V	0.25	BF381	0.30	TDA2640	3.30
BZV88 386V	0.25	BF381	0.30	TDA2640	3.30
BZV88 391V	0.25	BF381	0.30	TDA2640	3.30
BZV88 396V	0.25	BF381	0.30	TDA2640	3.30
BZV88 401V	0.25	BF381	0.30	TDA2640	3.30
BZV88 406V	0.25	BF381	0.30	TDA2640	3.30
BZV88 411V	0.25	BF381	0.30	TDA2640	3.30
BZV88 416V	0.25	BF381	0.30	TDA2640	3.30
BZV88 421V	0.25	BF381	0.30	TDA2640	3.30
BZV88 426V	0.25	BF381	0.30	TDA2640	3.30
BZV88 431V	0.25	BF381	0.30	TDA2640	3.30
BZV88 436V	0.25	BF381	0.30	TDA2640	3.30
BZV88 441V	0.25	BF381	0.30	TDA2640	3.30
BZV88 446V	0.25	BF381	0.30	TDA2640	3.30
BZV88 451V	0.25	BF381	0.30	TDA2640	3.30
BZV88 456V	0.25	BF381	0.30	TDA2640	3.30
BZV88 461V	0.25	BF381	0.30	TDA2640	3.30
BZV88 466V	0.25	BF381	0.30	TDA2640	3.30
BZV88 471V	0.25	BF381	0.30	TDA2640	3.30
BZV88 476V	0.25	BF381	0.30	TDA2640	3.30
BZV88 481V	0.25	BF381	0.30	TDA2640	3.30
BZV88 486V	0.25	BF381	0.30	TDA2640	3.30
BZV88 491V	0.25	BF381	0.30	TDA2640	3.30
BZV88 496V	0.25	BF381	0.30	TDA2640	3.30
BZV88 501V	0.25	BF381	0.30	TDA2640	3.30
BZV88 506V	0.25	BF381	0.30	TDA2640	3.30
BZV88 511V	0.25	BF381	0.30	TDA2640	3.30
BZV88 516V	0.25	BF381	0.30	TDA2640	3.30
BZV88 521V	0.25	BF381	0.30	TDA2640	3.30
BZV88 526V	0.25	BF381	0.30	TDA2640	3.30
BZV88 531V	0.25	BF381	0.30	TDA2640	3.30
BZV88 536V	0.25	BF381	0.30	TDA2640	3.30
BZV88 541V	0.25	BF381	0.30	TDA2640	3.30
BZV88 546V	0.25	BF381	0.30	TDA2640	3.30
BZV88 551V	0.25	BF381	0.30	TDA2640	3.30
BZV88 556V	0.25	BF381	0.30	TDA2640	3.30
BZV88 561V	0.25	BF381	0.30	TDA2640	3.30
BZV88 566V	0.25	BF381	0.30	TDA2640	3.30
BZV88 571V	0.25	BF381	0.30	TDA2640	3.30
BZV88 576V	0.25	BF381	0.30	TDA2640	3.30
BZV88 581V	0.25	BF381	0.30	TDA2640	3.30
BZV88 586V	0.25	BF381	0.30	TDA2640	3.30
BZV88 591V	0.25	BF381	0.30	TDA2640	3.30
BZV88 596V	0.25	BF381	0.30	TDA2640	3.30
BZV88 601V	0.25	BF381	0.30	TDA2640	3.30
BZV88 606V	0.25	BF381	0.30	TDA2640	3.30
BZV88 611V	0.25	BF381	0.30	TDA2640	3.30
BZV88 616V	0.25	BF381	0.30	TDA2640	3.30
BZV88 621V	0.25	BF381	0.30	TDA2640	3.30
BZV88 626V	0.25	BF381	0.30	TDA2640	3.30
BZV88 631V	0.25	BF381	0.30	TDA2640	3.30
BZV88 636V	0.25	BF381	0.30	TDA2640	3.30
BZV88 641V	0.25	BF381	0.30	TDA2640	3.30
BZV88 646V	0.25	BF381	0.30	TDA2640	3

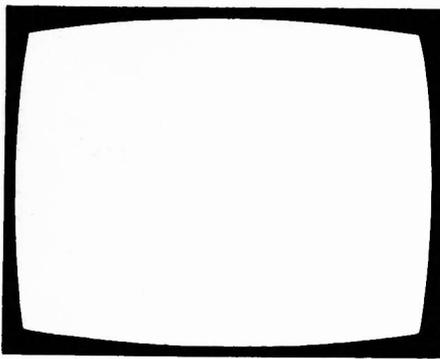

TELEVISION

September
1979

Vol. 29, No. 11
Issue 347

COPYRIGHT

© IPC Magazines Limited, 1979. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

SUBSCRIPTIONS

An annual subscription costs £9.50 in the UK, £10.50 overseas (\$21 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£2.85) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 70p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Your Problems Solved". Send to the address given above (see "correspondence").

this month

- 567 Leader**
- 568 Teletopics**
News, comment and developments.
- 570 Receiving French TV** *by Hugh Cocks*
In favourable locations along the south and east coasts French TV can be received on a permanent basis. Advice is given on transmitters to try for and the equipment required.
- 574 The V2000 VCR System**
Technical features of the new Philips/Grundig VCR system, which could become a new world standard.
- 576 No Clock Display** *by Steve Beeching, T.Eng. (C.E.I.)*
Another nasty VCR fault. This time a Sony Betamax VCR which wouldn't give a clock display.
- 577 All Slog and No Grog . . .** *by Les Lawry-Johns*
Part of this month's column is set to music. Whatever next? At least the Red Baron hasn't put in an appearance. Not yet.
- 579 Next Month in Television**
- 580 Restricted Brightness Range** *by George Wilding*
Quite a lot of things can be responsible for restricting the range of operation of a set's brightness control, and these depend on circuit design. A survey of possible causes is provided.
- 582 New Teletext Signal Panel** *by Alan Kitching*
This new signal panel has been designed as a direct replacement for the original one in the *Television* teletext decoder, using the same components. The use of an adaptive data slicer circuit gives improved performance under adverse signal conditions. The layout has been improved, and a sound i.f. preamplifier added.
- 586 Readers' PCB Service**
- 587 Servicing Pye Solid-State Colour Receivers, Part 1** *by Mike Phelan*
Dealing with faults on the Pye 713, 715, 717, 725, 731, 735, 737 and 741 chassis. This part covers the power supply and timebase circuits used in the larger-screen chassis.
- 592 Long-Distance Television** *by Roger Bunney*
Reports on DX reception and conditions, and news from abroad. Also the start of a new series giving advice to those thinking of making a start with experimental DX reception.
- 595 Tuners for DX Reception** *by Hugh Cocks*
A useful new v.h.f./u.h.f. tuner has become available on the surplus market.
- 596 TV Troubles** *by Robin D. Smith*
More notes on fault conditions. Also some of the problems that can arise when customers decide to have a go.
- 598 TV Servicing: Beginners Start Here . . . Part 24** *by S. Simon*
Now we really come to grips with colour! The basic colour mixing techniques are described, and things to look for listed when dealing with wrong colours or a poor grey scale on sets with colour-difference drive.
- 601 Letters**
- 602 Your Problems Solved**
- 604 Test Case 201**

OUR NEXT ISSUE DATED OCTOBER WILL BE
PUBLISHED ON SEPTEMBER 17

THE UNBEATABLE BRIARWOOD SERVICE

EX-EQUIPMENT SPARES

MISC. S/Output Trans.
£1 + VAT + £1 P&P
F/Output Trans.
£1.25 + VAT + £1 P&P.
Scancoils £1.50 + VAT
+ £1 P&P. Other
spares available, please
write or phone for details.

MONO TUBES
(tested)
19" Rimguard £3.00
23" Rimguard £4.00
20" Rimguard £5.00
24" Rimguard £6.00
+ £4.00 P.&P.

MONO TUNERS
6-button integrated all
at £4.00
U.H.F. P/Button D/S
£4.00. U.H.F. P/Button
S/S £4.00. Rotary £3.00
+ £1 P&P.

MONO LOPTS
All D/Standard Lopts
at £4.00 + £1 P.&P.
All S/Standard at
£4.00 + £1 P.&P.

MONO PANELS
i.e. Philips, Bush etc.
£3.50 + £1 P.&P.
Quotations for
complete
S/hand chassis if
required. (Diff. prices)

PLEASE ADD 15% V.A.T.
TO ALL ITEMS AND
OVERSEAS AT COST.
CASH WITH ALL ORDERS.

VALVES (MONO & COLOUR)

PCL82	0.10	PCF802	0.10	PCC86	0.10	EY86/7	0.10	30PL1	0.25	PL509	1.00
PCL83	0.25	PCF805	0.25	PC97	0.20	EY8/7	0.10	30PL13/4	0.10	PY500	1.00
PCL84	0.10	PCF806	0.10	PC900	0.10	DY802	0.10	30P12	0.10	GY501	1.00
PCL85	0.10	PCF808	0.25	EF80	0.10	PY800/1	0.10	30FL1/2	0.25	PL508	0.50
PCL86	0.10	PCF80	0.10	EF85	0.10	PL36	0.25	ECC82	0.10	PCH200	0.50
PFL200	0.10	PCC189	0.10	EF183	0.10	PL504	0.25	ECC81	0.10	PCF200	0.50
PCF801	0.10	PCC86	0.10	EF184	0.10	PL81	0.10	ECH81	0.10	CEY51	0.15
30C1	0.10	30C15	0.10	6BW7	0.10	6/30L2	0.10	ECL80	0.10		
30C17	0.10	30C18	0.25	ECC85	0.10	U26	0.10	ECL82	0.10		
PL83	0.10	PL84	0.10	EH90	0.10						

Please note there is 25p Postage and Packing per order.

WE DO NOT SELL RUBBISH
AT BRIARWOOD TV

D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUTPUT	POWER	L/TB	F/TB
Bush/Murphy	6.50	6.50	6.50	—	—	6.50	1.50	6.50	—	—
GEC/Sobell	6.50	7.50	—	—	—	6.50	—	—	—	7.50
Philips	6.50	9.50	—	—	—	7.50	—	—	—	6.50
Decca	6.50	9.00	9.00	—	—	6.50	2.00 (19" only)	8.00	—	6.00
Thorn 2000	5.00	5.00	5.00	6.50	6.50	6.00	—	6.50	10.00	6.50
Pye	7.50	7.50	9.50	—	—	6.50	—	—	—	7.50
Baird	6.50	8.50	7.00	—	—	6.50	—	—	—	6.00

Postage & Packing £1.25

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	7.50	—	12.00	—	8.00	6.00	12.00	—
GEC Hybrid	7.50	6.50	10.00	—	6.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	6.00	—	—	6.00
Thorn 3000	6.50	6.50	8.00	6.50	6.00	20.00	20.00	6.50
Pye 691/693	6.50	6.50	10.00	—	6.50	—	15.00	6.50
Thorn 3500	6.50	6.50	8.00	6.50	7.50	20.00	20.50	6.50

Postage & Packing £1.25

Korting and other foreign
panels available on request.

COLOUR TUBES

19"	£18.00
19" A49, 192	£20.00
20"	£20.00
22"	£22.00
25"	£18.00
26"	£28.00

Plus P&P £4.

NEW
Rebuilt tubes
available on request.

COLOUR TUNERS

Bush	£6.00
GEC	£6.00
Philips G6 S/S	£6.00
Thorn 3000	£6.00
Pye 691	£6.00

Some new tuners in stock,
can supply on request. Many
Foreign Tuners also available
on request. Plus P&P £1.

COLOUR LOPTS

Most Lopts available
from £7.00. Both
British & Foreign
makes. Please ring
or write.
P&P per Lopt £1.

MISC.

S/Output transformer
from £1.50.
F/Output from £1.25.
Scancoils from £5.00.
P&P £1.
Other spares available on
request.

G8 PANELS

SPECIAL OFFER
CHROMA £12.00

THORN 1500 TUNERS
NEW SPECIAL OFFER
AT £8.00

Postage & Packing £1.00

MAIL ORDER T.V.s. IN GOOD WORKING ORDER

		COLOUR		MONO	
Pye	19"	£60.00	22" £65.00	26" £75.00	
GEC	19"	£60.00	22" £65.00	26" £75.00	
Bush	19"	£80.00	22" £80.00	26" £90.00	
Philips	G6	—	22" £63.00	26" £70.00	

Many other makes & models available.

Please ring or write for information.

**PERSONAL CALLERS
WELCOME.**

		MONO	
20" & 24" S/S	£16.00	Pye, GEC, Bush etc.	
20" & 24" D/S	£14.00	Pye, GEC, Bush etc.	
19" & 23" D/S	P/button £12.00	Pye, GEC, Bush etc.	
19" & 23" D/S	Rotary £8.00	Pye, GEC, Bush etc.	

Please note there is 15% V.A.T. on all the above prices.
Plus £8 P&P. England, Wales & Scotland for colour T.V.'s.
Inland N. & S. Ireland P&P £15. P&P £5 for mono T.V.'s
to England, Wales & Scotland. Inland N. & S. Ireland £7
per set.

Briarwood T.V. Limited
Britain's Mail Order
T.V. Specialists

BRIARWOOD

THE PROFESSIONAL CHOICE. NATIONWIDE

NEW SPARES

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	DIODES	E.H.T. TRAYS MONO
AC107	0.20	AF170	0.25	BC172	0.08	BD222/T1P31A	0.37	BF260	0.24	OC45	0.20	1N4001	950 MK2 1400 2.00
AC113	0.17	AF172	0.20	BC173	0.12	BD225/T1P31A	0.39	BF262	0.28	OC48	0.35	1N4002	1500 18" 19" stick
AC115	0.17	AF178	0.49	BC177	0.12			BF263	0.25	OC70	0.22	1N4003	2.37
AC117	0.24	AF180	0.60	BC178	0.12	BD234	0.34	BF271	0.20	OC71	0.28	1N4004	1500 24" 5 stick 2.48
AC125	0.20	AF181	0.30	BC179	0.12	BD222	0.73	BF273	0.12	OC72	0.35	1N4005	Single stick Thorn TV
AC126	0.18	AF186	0.29	BC182L	0.09	BDX22	0.73	BF336	0.28	OC74	0.35	1N4006	11.16K 70V
AC127	0.19	AF239	0.43	BC183L	0.09	BDX32	1.98	BF337	0.24	OC75	0.35	1N4007	TV20 2 MT
AC128	0.17	AU113	1.29	BC184L	0.09	BDY60	0.80	BF338	0.29	OC76	0.35	1N4148	TV20 16K 18V
AC131	0.13			BC186	0.18	BDY1B	0.75	BF342	0.26	OC77	0.50	1N4751A	
AC141	0.23	BA130	0.08	BC187	0.18	BDY60	0.80	BF434	0.24	OC78	0.13	1N5401	IC's
AC142	0.19	BA145	0.14	BC209	0.11	BF115	0.24	BFY43	0.27	OC81	0.20	1N5404	SN76013N 1.20
AC141K	0.29	BA148	0.17	BC212	0.09	BF121	0.21	BFX84	0.27	OC810	0.14	1N5406	SN76013ND 1.00
AC142K	0.29	BA155	0.08	BC213L	0.09	BF154	0.12	BFX85	0.27	OC82	0.20	1N5408	SN76023N 1.20
AC151	0.17	BA158	0.08	BC214L	0.09	BF158	0.19	BFX88	0.24	OC820	0.13		SN76023ND 1.00
AC165	0.16	BA165	0.08	BC237	0.07	BF159	0.24	BFY50	0.15	OC83	0.22		SN76226DN 1.50
AC166	0.16	BC107	0.10	BC240	0.31	BF160	0.23	BFY51	0.15	OC84	0.28		SN76227N 1.20
AC168	0.17	BC108	0.10	BC2B1	0.24	BF163	0.23	BFY52	0.15	OC85	0.13		TBA341 0.97
AC176	0.17	BC109	0.10	BC262	0.18	BF164	0.17	BFY53	0.27	OC123	0.20		TBA520Q 1.10
AC176K	0.28	BC113	0.09	BC263B	0.20	BF167	0.23	BFY55	0.27	OC169	0.20		TBA530Q 1.10
AC178	0.16	BC114	0.12	BC267	0.19	BF173	0.21	BHA0002	1.90	OC170	0.22		TBA540Q 1.45
AC186	0.26	BC115	0.10	BC301	0.22	BF177	0.26	BR100	0.20	OC171	0.27		TBA550Q 1.40
AC187	0.21	BC116	0.10	BC302	0.30	BF178	0.24	BSX20	0.23	QA91	0.05		TBA560CQ 1.50
AC188	0.20	BC117	0.11	BC307	0.10	BF179	0.28	BSX76	0.23	BRC4443	0.65		TBA570Q 1.00
AC187K	0.30	BC119	0.22	BC337	0.11	BF180	0.30	BSY84	0.36	R200BB	1.50		TBA800 1.00
AC188K	0.30	BC125	0.12	BC338	0.09	BF181	0.34	BT106	1.18	R2010B	1.50		TBA810 1.50
AD130	0.50	BC126	0.09	BC307A	0.10	BF182	0.30	BT108	1.23	R2305	0.38		TBA920Q 1.50
AD140	0.65	BC136	0.12	BC308A	0.12	BF183	0.29	BT109	1.09	R2305/BD222	0.37		TBA990Q 1.50
AD142	0.73	BC137	0.12	BC309	0.14	BF184	0.23	BT116	1.23	SCR957	0.65		TCA270SQ 1.45
AD143	0.70	BC138	0.21	BC547	0.09	BF185	0.29	BT120	1.23	TIP31A	0.38		TCA270SA 1.45
AD145	0.70	BC139	0.21	BC548	0.11	BF186	0.30	BU105/02	1.50	TIP32A	0.36		TCA1327B 1.00
AD149	0.64	BC140	0.24	BC549	0.11	BF194	0.09	BU105/04	2.00	TIP3055	0.53		E.H.T. TRAYS COLOUR
AD161	0.40	BC141	0.22	BC557	0.11	BF195	0.09	BU126	1.40	T1590	0.19		Pye 731 5.20
AD162	0.40	BC142	0.19	BD112	0.39	BF196	0.12	BU205	1.20	T1591	0.19		Pye 691/693 4.50
AD161	1.00	BC143	0.19	BD113	0.65	BF197	0.10	BU208	1.60	TV106	1.09		Decca (large screen)
AD162	1.00	BC147	0.07	BD115	0.30	BF198	0.11	BY126	0.09				CS2030/2232/2630/
AF106	0.42	BC148	0.07	BD116	0.47	BF199	0.14	BY127	0.10				2632/2230/2233/
AF114	0.23	BC149	0.07	BD124	1.30	BF200	0.28						PL36 0.90
AF115	0.22	BC153	0.12	BD131	0.32	BF216	0.12						PL84 0.74
AF116	0.22	BC154	0.12	BD132	0.34	BF217	0.12						PL504 1.10
AF117	0.30	BC157	0.10	BD133	0.37	BF218	0.12						PL509 2.45
AF118	0.40	BC158	0.11	BD135	0.26	BF219	0.12						PL82 0.67
AF121	0.33	BC159	0.11	BD136	0.26	BF220	0.12						PCL84 0.75
AF124	0.33	BC160	0.22	BD137	0.26	BF222	0.12						PCL86 0.78
AF125	0.29	BC161	0.22	BD138	0.26	BF221	0.21						PCL805 0.75
AF126	0.29	BC167	0.09	BD139	0.40	BF224	0.12						PLF200 1.00
AF127	0.29	BC168	0.09	BD140	0.28	BF256	0.37						PL36 0.90
AF139	0.39	BC169C	0.09	BD144	1.39	BF258	0.27						PL84 0.74
AF151	0.24	BC171	0.08	BD145	0.50	BF259	0.27						PL504 1.10

All transistors, IC's offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc. Please add 15% VAT to all items and overseas at cost P & P U.K. 25p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

TELEVISION SALE DISCOUNT FOR QUANTITY

Please note all mono sets sold as 100% comp. Working Mono £3.00 extra. No broken/masks, no broken panels etc. Working Colour £15.00 extra. Colour sets sold with good c.r.t.s and 100% comp. Supplied in 1's or 100's.

MONO Rotaries 19" & 23"

GEC	£3.00
Thorn 950 etc.	3.00
K.B.	3.00
Pye	3.00
Thorn 1400	4.50

D/S P/B 19" 23"

Thorn 1400	7.00
Bush 161 etc.	7.00
Baird 660 etc.	7.00
Philips 210 etc.	7.00
Pye Olympic etc.	7.00

D/S P/B 20" 24"

Bush	10.00
GEC	10.00
Philips	10.00
Pye	10.00
Thorn	10.00

S/S 20" 24"

Bush 313 etc.	£12.00
Pye 169 chassis	12.00
Thorn 1500	12.00
GEC series 1 & 2	12.00
Decca MS series	12.00

S/S COLOUR

	19"	20"	22"	25"	28"
	£	£	£	£	£
GEC	40	40	40	40	40
Philips	—	—	40	40	40
Thorn	55	—	60	45	65
Korting	—	—	55	—	60
Pye Mechanical	40	—	40	40	40
Pye Varicap	45	—	45	45	45

MAINS DROPPERS

Mono

Bush 161	60p
Philips 210 30+125+2K85	50p
Philips 210 118R+148R	48p
Thorn 1400	75p
GEC 2018	58p
Thorn 1500	70p

Colour

Bush A823	72p
Pye 723 27Q+56Q	57p
GEC 2110-41Q	45p
GEC 2110-12R5+12R5	47p
GEC2110-27R5	45p
Thorn 3500	58p
Thorn 8000	58p
Thorn 8500	54p
Philips G8 47R	30p
Philips G8 2.2+68	42p

All plus VAT at 15%

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED.

EXPORT COLOUR & MONO T.V.s AVAILABLE READY FOR USE OVERSEAS

E.H.T. TRAYS COLOUR	
Pye 731	5.20
Pye 691/693	4.50
Decca (large screen)	
CS2030/2232/2630/	
2632/2230/2233/	
PL36	0.90
PL84	0.74
PL504	1.10
PL509	2.45
PY88	0.63
PY500A	1.60
PY81/800	0.57
SPECIAL OFFER	
Philips PL802	2.55

RRI (RBM) A823	5.10
5.00	
Bang & Olufsen	
4/5000 Grundig	
5010/5011/5012/	
6011/6012/7200/	
2052/2210/2252R	
Tandberg (radionette)	
Autovox	6.60
Grundig 3000/3010	
Saba 2705/3715	
Telefunken 709/710/	
717/2000	6.80
Korting	8.80

TELEVISION

Briarwood House Preston Street
Bradford West Yorkshire BD7 1NS
Tel. Bradford 306018 (STD code 0274)



THE LARGEST STOCKS OF GENUINE PART-EXCHANGED COLOUR T.V.'s IN THE COUNTRY — UNDER ONE ROOF.

REGULAR LARGE DELIVERIES EVERY WEEK INCLUDE—


Philips 511/512/G8 etc., Bush, Murphy, Thorn 3000/3500/8000/8500, GEC all models, Pye Varicap, Grundig, Telefunken, Saba, Decca Bradford, Nordmende, B. & O., Emo, Finlux, Luxor, Korting, Hitachi, Sanyo, Toshiba, etc., etc., etc.

SPECIAL LOW SUMMER PRICES

Now in operation

DUAL STANDARD FROM **£5 + VAT**


SINGLE STANDARD FROM **£20 + VAT**

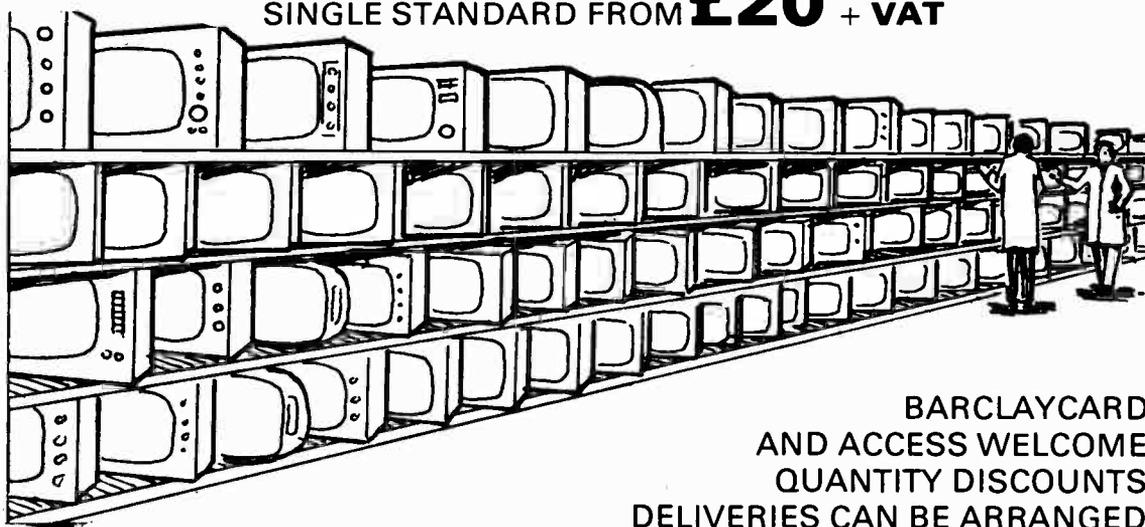

BARCLAYCARD AND ACCESS WELCOME
QUANTITY DISCOUNTS
DELIVERIES CAN BE ARRANGED

SUPERB TESTING FACILITIES AVAILABLE

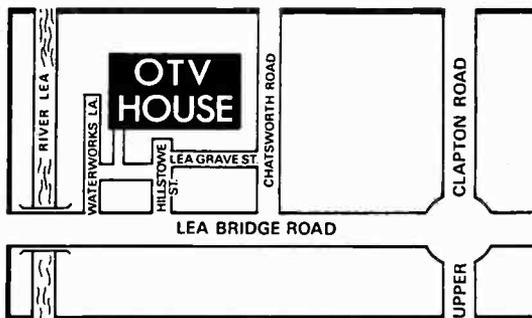**OTV TELEVISION LTD,
144A Lea Bridge Rd,
London E5 9RB.
Tel: 01-985 6111/8687**



We specialise in Export

Enquiries invited from the Middle East and Third World Countries.

ARE YOU IN THE DARK?..
..ABOUT OUR



COLOUR T.V. PANEL EXCHANGE REPAIR SERVICE

FULL RANGE OF
THORN · RBM · PHILIPS
PYE · INVICTA · GEC
DECCA · TELPRO
AND MANY OTHER MAKES

90 DAY GUARANTEE ON ALL REPAIRS
SAME DAY POSTAL SERVICE

We employ a large skilled Staff, who utilise some of the most sophisticated Test equipment available, inclusive of AUTOMATIC FAULT FINDING COMPUTERS together with specially designed SERVICING JIGS which in short means to you -

HIGH QUALITY REPAIRS - AT LOW COST



ONE OFF
OR



100 OFF · NO ORDER TOO
LARGE OR SMALL

SEND FOR PRICE LIST

SEND FOR CATALOGUE
BLOCK DISCOUNTS FOR TRADE CONTRACTS

TO

Campbell Electronics Ltd.

Factory Unit E5, Halesfield 23, Telford · Shropshire · TF7 4QX
Telephone · Telford (0952) 584373. Ext. 2 · Telex 35191 Chamcon


S & R. BREWSTER

LIMITED Ref:TV

86-88 UNION ST.
PLYMOUTH

TELEPHONE
0752-65011

Manufacturers of

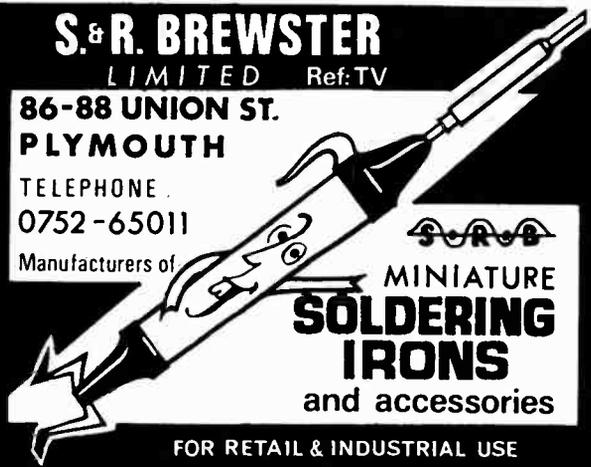

MINIATURE
SOLDERING
IRONS
and accessories

FOR RETAIL & INDUSTRIAL USE

QUALITY USED TV's AT GIVE AWAY PRICES

S.S. MONO FROM £12
D.S. MONO FROM £5
S.S. COLOUR FROM £40
PRICES PLUS V.A.T.

ALL WORKERS, FRESH STOCKS WEEKLY,
QUANTITY DISCOUNTS, DELIVERY ARRANGED.
TRY US YOU WILL NOT BE DISAPPOINTED.

TELETRADERS

We have moved to our new Warehouse where we have much bigger stocks.

St. Leonard's Warehouse, St. Leonard's Road,
Newton Abbott, Devon.
Telephone (0626) 60154

Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs - and they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

City and Guilds Certificates:-

Telecommunications Technicians,
Radio, TV and Electronics Technicians,
Electrical Installation Work,
Technical Communications,
Radio Amateur,
MPT General Radio Communications
Certificate.

Diploma Courses:-

Electronic Engineering,
Electrical Engineering,
Computer Engineering,
Radio, TV, Audio Engineering, Servicing and
Maintenance (inc. Colour TV)
New Self-Build Radio Courses with Free Kits.

Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful - at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name.....


Address.....

..... Phone No:

ICS International Correspondence Schools,
Dept. L285, Intertext House,
LONDON SW8 4UJ. Tel 622 9911
(all hours)

TRANSISTORS, ETC.

Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.48	AU103	2.40	BC22	0.56	BC377	0.66	BD234	0.66	BF222	0.51	BPX29	1.62	MPSU05	0.66
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.39	BD235	0.63	BF224 & J	0.22	BR101	0.83	MPSU06	0.76
AC126	0.48	AU110	2.40	BC205*	0.39	BC440	0.82	BD236	0.63	BF240	0.32	BR103	0.84	MPSU55	1.26
AC127	0.54	AU113	2.60	BC206*	0.37	BC441	0.59	BD237	0.66	BF241	0.31	BR303	1.06	MPSU56	1.32
AC128	0.46	BC107*	0.16	BC207*	0.39	BC461	0.78	BD238	0.66	BF244*	0.51	BR303	1.06	MPSU60	0.82
AC128K	0.55	BC108*	0.15	BC208*	0.37	BC477	0.30	BD253	1.58	BF245	0.43	BR339	0.80	MPCU131	10.59
AC141	0.55	BC109*	0.16	BC209*	0.39	BC478	0.25	BD410	1.65	BF254	0.48	BR356	10.44	OC26	1.90
AC141K	0.70	BC113	10.22	BC211*	0.36	BC479	0.33	BD433	0.65	BF255	0.58	BS527	0.92	OC28	1.49
AC142K	0.80	BC114	10.22	BC212*	0.17	BC547*	10.13	BD435	0.70	BF256*	0.49	BT106	1.90	OC29	1.80
AC151	0.31	BC116*	0.28	BC213*	0.17	BC548*	10.13	BD436	0.71	BF257	0.44	BT108	1.90	OC35	1.28
AC152	0.38	BC117	10.20	BC213*	0.16	BC549*	10.18	BD437	0.74	BF258	0.62	BT116	1.45	OC36	1.25
AC153	0.42	BC118	10.24	BC214*	0.18	BC550	10.24	BD438	0.76	BF259	0.62	BT119	5.18	OC42	0.90
AC153K	0.82	BC119	10.34	BC214*	0.18	BC556	10.23	BD519	0.88	BF262	0.73	BU102	2.85	OC44	0.68
AC154	0.41	BC125*	0.30	BC225	0.42	BC558*	0.17	BD520	0.88	BF263	0.88	BU105	11.80	OC45	0.63
AC176	0.45	BC126	10.30	BC237*	0.16	BC559*	0.18	BD599	0.87	BF270	0.47	BU105/02	11.85	OC70	0.66
AC178	0.51	BC132	10.20	BC238*	0.15	BCY10	0.30	BD600	1.23	BF271	0.42	BU108	12.98	OC71	0.75
AC179	0.85	BC134	10.22	BC239*	0.22	BCY30A	1.06	BD663BR	0.68	BF272A	0.80	BU126	12.91	OC72	0.73
AC187	0.56	BC135	10.21	BC251*	0.25	BCY32A	1.19	BDX12	1.58	BF273	0.33	BU204	12.90	OC81	0.83
AC187K	0.85	BC136	10.22	BC252*	0.26	BCY34A	1.02	BDX32	2.85	BF274	0.34	BU205	12.78	OC81D	0.85
AC188	0.52	BC137	10.30	BC253*	0.28	BCY34A	1.02	BDY16A	0.83	BF275	0.63	BU206	13.09	OC139	1.30
AC188K	0.81	BC138	10.35	BC253*	0.28	BCY34A	1.02	BDY18	1.55	BF337	0.65	BU208	13.09	OC140	1.35
AC193K	0.74	BC140	10.35	BC282A*	0.28	BD123	0.80	BDY20	2.25	BF338	0.65	BU407	11.38	OC170	0.80
AC194K	0.74	BC141	10.35	BC283*	0.28	BD124	1.55	BDY28	1.38	BF355	0.72	BU477	2.50	OC171	0.82
AC197	1.20	BC142	10.35	BC287*	0.20	BD124	1.55	BF115	0.48	BF362	10.49	C106D	0.80	OC200	3.90
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF117	0.45	BF363	10.49	C106F	0.43	OC201	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF120	0.55	BF367	10.29	C111E	10.46	OC202	2.40
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF121	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF122	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF123	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF124	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF125	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF126	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF127	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF128	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF129	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF130	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF131	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF132	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF133	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF134	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF135	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF136	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF137	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF138	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF139	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF140	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF141	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF142	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF143	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF144	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF145	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF146	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF147	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF148	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF149	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF150	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF151	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF152	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF153	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF154	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF155	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF156	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF157	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF158	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF159	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF160	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF161	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF162	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF163	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF164	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF165	0.55	BF367	10.29	C111E	10.46	OC205	3.95
AC197	0.95	BC143	10.38	BC288*	0.28	BD131	0.58	BF166	0.55	BF367	10.29	C111E			

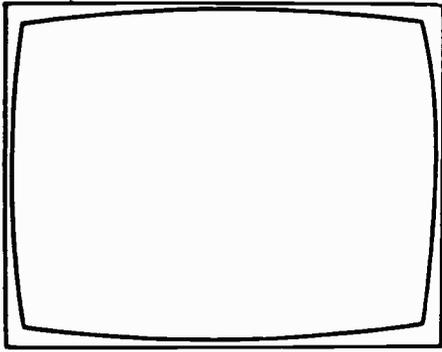

TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTS MANAGER

Roy Smith

01-261 6671

CLASSIFIED ADVERTS

Colin R. Brown

01-261 5762

A decade of the VCR

The 70s have seen the development of the domestic VCR from initial laboratory prototypes to an established consumer product. At the start of the decade, there were numerous intimations that a number of firms had development projects under way. There were also proposals for other domestic video systems, both disc (Teldec) and film (EVR), that subsequently fell by the wayside. The first domestic VCR system to appear, Cartrivision, was introduced in the USA in mid-1972. It was not a success. It appears to have lasted for about a year, by which time Ampex had also decided to drop its proposed Instavideo system. Though RCA continued work on various proposed systems, including discs and a holographic system using cheap plastic film, US firms then seem to have lost interest.

The main development was continued by Philips in Europe and various Japanese firms, in particular JVC and Sony. Philips were first to introduce a successful system in launching the N1500 on the European market in 1973. It gave an hours' recording/playback time. Up-dated versions were introduced in 1975 (N1501) and 1976 (N1502), and the N1700 with its two hours' (later two and a half hours') record/playback time was launched in late 1977. Philips never seem to have been keen to enter the US market with an NTSC version.

The Japanese video manufacturers battled it out over the years 1976-7 in their own and the US markets. Several systems came and went, and at the end of it all Sony's Beta II and JVC's VHS systems had become firmly established. During 1978, PAL versions were launched in the UK, giving three hours' playing time. Improved versions have already appeared, the main items receiving manufacturers' attention being timers with extended operating periods, facilities for locating particular parts of the recorded material quickly and easily, and the provision of pause controls.

There is no doubt that many leading international TV firms regard domestic video as the key to their future. The colour TV markets in the developed world have reached saturation point – the markets are now mainly first-time buyers and replacement ones – while it's likely that countries such as Korea, Taiwan and Singapore will scoop third world TV markets as they open up. So video is an obvious thing for Japanese and European TV firms to go for.

Seeing the growing dominance of the Japanese video firms, Grundig decided to develop a variant on the N1700 system with more sophisticated features such as search-

tuning. Its SVR system, giving four hours' playing time, was launched in 1978.

Which brings us close to the end of the decade and the recent announcement of the joint Philips/Grundig V2000 system. You might have thought that there were enough non-compatible VCR systems already. True enough, but if a major technical breakthrough has been achieved then yet another system is justified. All the systems so far use $\frac{1}{2}$ in. tape. What Philips and Grundig have succeeded in doing is to get up to eight hours' playing time (with a corresponding reduction in tape costs) from a cassette, by making use of the tape twice over. In fact it's a $\frac{1}{2}$ in. recording system on $\frac{1}{2}$ in. tape, the arrangement being similar to the standard audio cassette. This involves the use of some sophisticated techniques, in particular dynamic track following, in order to maintain correct head/track alignment. We shall have to wait to see whether the system is accepted in practice however. As they say, the proof of the pudding is in the eating. Philips and Grundig are nevertheless to be congratulated on their successful development of the new system, and it's refreshing to find that the European TV industry is not prepared to play second fiddle to you know who.

The situation is unlikely to end at this point however. Other systems are under development. Funai Electric of Japan for example intends to introduce a system using a $\frac{1}{2}$ in.-tape cassette, and there is some emphasis on the development of light-weight portable machines – the present generation of VCRs is hardly acceptable for portable use, being intended mainly as time-shift devices (seeing the programmes when you want to rather than when the broadcasting schedules dictate).

The intense competition in the video field has given the consumer the benefit of very reasonable VCR prices. Manufacturers can hardly have made much out of their VCR efforts to date. What are the prospects? We still incline towards pessimism. Do people have the time or inclination, even if they have the spare cash, to dabble with yet another piece of domestic technology? It's one thing to pick up the paper or switch on the radio or telly, another to organise yourself so that you can decide what you want to see and when a week or more in advance, and then arrange everything accordingly. And of course the marketing effort will be against a background of forecast deepening world economic recession.

Correction: The value of R9 in the class AB video circuit featured in the monochrome monitor conversion article last month should have been shown as 47k Ω , not 27k Ω .

Teletopics

TELETEXT TROUBLE

Setmakers, through BREMA, have expressed concern over the slow growth of the teletext service and are understood to be seeking government assistance. Production of teletext-equipped sets has failed to reach anything like the expected levels. The industry had originally hoped to sell about 40,000 teletext-equipped receivers by the end of 1977, but to date only some 20,000 sets have been sold. Production potential is said to be around 50,000 sets a year, but only half this number is at present being produced. The industry is blaming the price of teletext-equipped sets – around £700 for a 26in. model. It's felt that the public will begin to buy in large numbers only when teletext sets are available at an extra £60 to £70.

Apparently some i.c. manufacturers have encountered problems in getting the chips to operate at the frequencies involved. The price of sets of teletext i.c.s is certainly appreciable at present, accounting for much of the high price premium of teletext sets. Setmakers feel that a major breakthrough would occur if the price of the sets of chips could be brought down to around £10 to £15. This is one of those awkward chicken and egg problems however. Low production means high prices, and until volume production commences the prices will remain high.

With a saturated TV market, increased public demand for teletext sets will come mainly through replacement sales. Whilst replacement buyers frequently go up market, the present premium seems to be a deterrent to many purchasers.

DOMESTIC SATELLITE TV RECEPTION STARTS IN THE US


Satellites have been in use for some time now in the USA for coast-to-coast TV programme distribution, and have in particular benefited cable system operators in enabling them to increase substantially the number of channels

available to their subscribers. So why not set up your own backyard terminal, and link yourself to the satellite TV distribution system? Well cost for one thing. Until recently, it seems.

As we go to press with this issue a Satellite Private Terminal Seminar (SPTS-79) is being held in Oklahoma City, co-ordinated by Bob Cooper who is well known for his DX-TV activities and as the former editor-in-chief of the CATJ magazine. Four years ago a satellite receiver terminal would cost you over \$100,000. The cost a year ago was \$25,000, and has now fallen to under \$8,000. If you have the knowledge to build and set up your own terminal however, the cost can be in the region of \$500 to \$1,000, depending on how much surplus equipment you can obtain to incorporate in the installation. Those attending the seminar were provided with two complete sets of plans for building a satellite terminal – the Coleman Conversion and the Howard Terminal.

EXTENDED PLAY VIDEODISCS

The battle of the VCR systems raged mainly around how many hours' playing time you could get out of the cassette. Now that Philips are test marketing their videodiscs in the USA (in Seattle and Atlanta initially) a similar contest seems to be looming up. The basic Philips videodisc, which we described in some detail in our June 1975 issue, has a playing time of an hour – half an hour per side. This is rather wasteful of disc space however if you think about it. The laser scans the disc from the centre outwards, each rotation of the disc giving a complete picture, i.e. two fields. This means that at the end of the disc (outer edge) a field takes up far more space than at the centre. Much more information could be crammed on the disc if the length of track occupied by a field was kept constant from the centre to the outer edge, with the disc speed being reduced accordingly as the scan proceeds. This is the proposal put

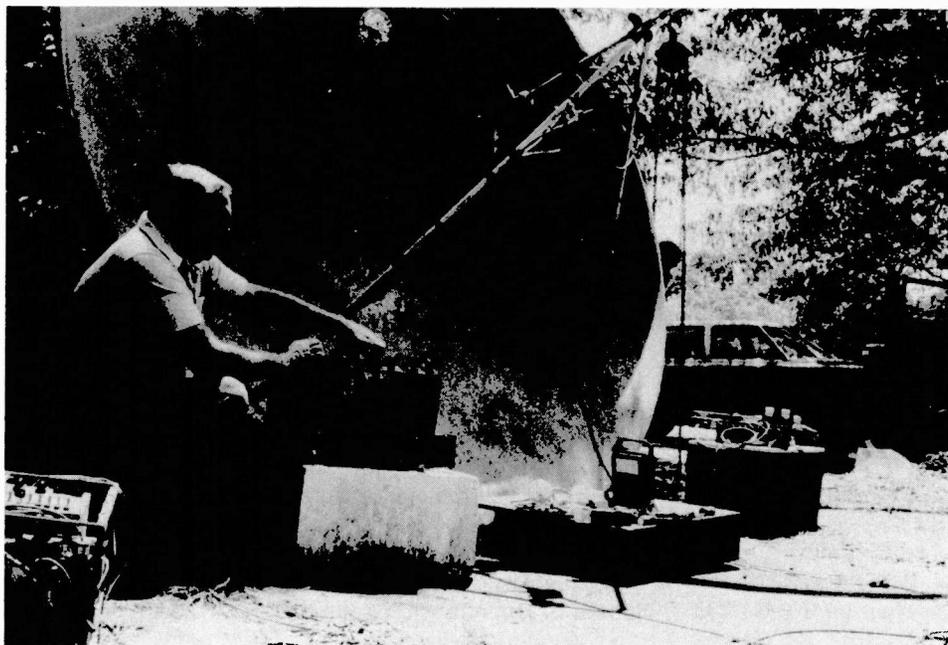

Robert Coleman of South Carolina with his \$200 satellite TV receiver terminal. Surplus equipment which Robert obtained over a six-month period enabled the cost to be kept to a minimum. Robert Coleman is believed to be the first individual working privately to design and bring into operation state-of-the-art gallium-arsenide f.e.t. low-noise amplifiers for this service. Coleman's receiver electronics cost him less than \$50 to assemble and put together: he was one of the programme instructors at the recent Satellite Private Terminal Seminar held in Oklahoma City.

forward by Philips for their Extended Play videodisc. There would be one complete picture per disc rotation at the centre, as with the Standard Play disc, and three complete pictures per rotation at the outer edge, the speed being progressively decreased from 1,800 r.p.m. at the centre to 600 r.p.m. at the outer edge.

Sony, who have also demonstrated a working optically-scanned videodisc system, have put forward an alternative suggestion – halving the disc speed to double the playing time.

TV4

The Government is to introduce a bill during the next parliamentary session extending the life of the IBA and giving it responsibility, "subject to strict safeguards", for the fourth TV programme. If all goes ahead as at present planned, TV4 is expected to open as a commercial network under IBA control in late 1982 or early 1983. The previous Government had authorised the IBA to commence engineering work for the new network.

MARKET FORECASTS

Mackintosh Consultants have issued a prediction that by 1982 72 per cent of Western European homes will have a colour receiver – this compares with 47 per cent last year. There is considerable variation between countries at present. Whilst the W. German, UK and Swedish markets are virtually saturated for example, only 15 per cent of Spanish homes have a colour receiver. The Spanish market is not likely to provide opportunities for hard-pressed German and UK setmakers however, since the Spanish TV industry enjoys a considerable measure of protection while per capita income is likely to prevent a rapid growth of sales.

As a result of excess production by W. German setmakers over a million sets are now estimated to be held in stock. Prices have fallen by a quarter, and some plants are working on short time.

The total European VCR market last year reached 225,000. BREMA figures suggest that UK imports had risen from 22,000 in 1977 to 95,000 last year. Mackintosh suggest that if the average VCR retail price falls below £600, European sales this year could reach 450,000.

The Henley Centre for Forecasting has also been looking at its crystal ball. Predictions here are that UK VCR sales could reach 150,000 this year, and that the market value of video systems will show an increase of over 1,000 per cent over the period 1978-84.

STATION OPENINGS

The following relay transmitters are now in operation:

Brushford (West Somerset) BBC-1 ch. 21, Westward Television ch. 24, BBC-2 ch. 27. Receiving aerial group A.

Claonaig (Kintyre) BBC-1 ch. 55, Scottish Television ch. 59, BBC-2 ch. 62. Receiving aerial group C/D.

Dowlais (Mid-Glamorgan) BBC-Wales ch. 58, HTV Wales ch. 61, BBC-2 ch. 64. Receiving aerial group C/D.

Faversham (Kent) BBC-1 ch. 22, Southern Television ch. 25, BBC-2 ch. 28. Receiving aerial group A.

Grantown-on-Spey (Highland) Grampian Television ch. 41, BBC-2 ch. 44, BBC-1 ch. 51. Receiving aerial group B.

Ireshopeburn (Co. Durham) BBC-1 ch. 55, Tyne Tees Television ch. 59, BBC-2 ch. 62. Receiving aerial group C/D.

Oban (Strathclyde) Scottish Television ch. 41, BBC-2 ch. 44, BBC-1 ch. 51. Receiving aerial group B.

Walthamstow (London) BBC-1 ch. 45, Thames/London

Weekend Television ch. 49, BBC-2 ch. 66. Receiving aerial group E.

All the above transmissions are vertically polarised.

The latest (May, 1979) issue of the IBA's invaluable pocket guide to transmitting stations has now been published. Copies can be obtained from the IBA Engineering Information Service, Crawley Court, Winchester, Hants, S021 2QA.

JAPANESE BUY UK CHIPS

Matsushita has placed an order with Plessey for 200,000 1GHz divide-by-256 CMOS i.c.s for use in a frequency synthesiser tuning system to be incorporated in up-market Panasonic TV receivers. The Plessey chip has been selected because it's the only 1GHz divider that can drive CMOS metal-gate logic directly without the need for low-power Schottky interfacing.

SUPERTITLING

Amongst the systems under development at the IBA's engineering headquarters is a new process called "Supertitles" to help the hard-of-hearing follow TV programmes. The system operates on the same principles as teletext, boxed captions appearing at the bottom of the screen. One problem is the fact that most people speak at a rate of around 160 words per minute, while few typists or machines can handle much over 80 words per minute. Southampton University is collaborating with the IBA on the project.

FLAT-SCREEN TV FROM SINCLAIR?

At a recent press conference Clive Sinclair announced that his company is in the final stages of developing a flat-screen TV receiver. The initial model would be a 3in. portable the size of a small paperback, but the principle can apparently also be used for large-screen models. What exactly the principle is remains something of a mystery, the only fact to emerge being that the screen is 3/8in. thick. Sinclair Radionics is unable to finance the establishment of a production line for the new development however, and is looking for a partner willing to provide the required investment. Meanwhile production of the present Microvision model is being moved from the company's St. Ives factory, where 160 redundancies have been announced, to a new and so far undisclosed location.

THE PYE STORY

A twenty page booklet marking the fiftieth anniversary of the formation of Pye Radio Limited is available to members of the public on application to Pye Ltd., Publications Department, 137 Ditton Walk, Cambridge. This fascinating little publication, entitled "*The Story of Pye Wireless*", traces the history of Pye receivers from the early twenties (the Pye Unit System of 1922) to the present day. TV sets, from 1936 on, naturally also feature in the story. Many of the early sets are illustrated.

An intriguing part of the story is the creation of Pye village industries throughout East Anglia during the 1939-45 war. The Government had suggested that Pye build a giant shadow factory. Instead however Pye took work to the villages in order to make use of the vast productivity potential of the area. By the end of the war the most complicated electronic equipment was being made in every corner of East Anglia, many people working at home. Pye had over 14,000 employees in village industries at the time.

Receiving French TV

Hugh Cocks

FRENCH TV can be received on a permanent or semi-permanent basis over quite a large area of England (apologies to those in Scotland, N. Ireland and Wales). Signals are present all the time along the entire south coast and a fair way up the east coast, and extend some way inland. During settled weather conditions, very strong signals are present over much of the country. There are three French TV networks, Television Francaise 1, Antenne 2, and France Regions 3. They can provide a refreshing change from our local programmes, especially the late night films! Language is not too great a problem: it's surprising how one tends to pick it up after watching for a while, though fast-spoken French in films can be a problem.

French TV System

As in the UK, all three networks use the same transmitter sites at u.h.f. The old 819-line system, used by TF-1 at v.h.f., is becoming obsolete and dates for the closedown of this service are being suggested, giving way to a new 625-line v.h.f. service (where have we heard that before?!).

The u.h.f. network uses system L. This has positive-going vision modulation, a.m. sound spaced 6.5MHz above the vision carrier, and SECAM colour with the subcarriers (two) at roughly the same frequency as our one subcarrier. Needless to say, a UK system I TV receiver won't think very much of the French transmissions, producing a somewhat jumbled negative picture with mostly buzzing from the loudspeaker. A system I set can be used to line up the aerials in the first place however, before you get too committed with system L receivers.

Which Transmitter?

The first thing to decide is which transmitter to try to receive. The map shown in Fig. 1 indicates the transmitters most favourably received in the UK. Those marked with an asterisk are lower powered ones, but can be well received under good conditions. A problem that has to be taken into account is UK transmitters on the same or adjacent channels. The channel groupings correspond to our own (the channel numbers are exactly the same) with the exception of Boulogne where a wideband aerial will be required.

As a very approximate guide to the "UK service area" of these transmitters, Lille is strongest up the east coast and inland areas; Boulogne in east Kent and south east Sussex; Caen from mid-Sussex to east Devon; Brest in the south west; and Rennes in the Channel Islands. Obviously the local terrain and UK relay transmitters may make the final selection of a transmitter somewhat different from this rough guide.

Care is required in receiving Caen in central southern England, as the aerial will be pointing more or less at Rowridge, Isle of Wight, which is only one channel away. Extra i.f. and aerial filters may be required therefore in order to get good results – to say nothing of high-gain aerials with a sharp forward pickup lobe. Sideways stacked aerials are

recommended, especially in this area, in order to narrow the forward pickup lobe – the problem in most locations will be not so much the strength of the received signal as the level of interference from UK transmitters.

Receivers

As regards receivers, there are several options open to the budding French TV viewer. The obvious one, though expensive, is a quick trip to Boulogne, where a set can be purchased at a price in excess of UK TV prices plus a large dose of French VAT (33%!) to say nothing of UK customs duty. Certain setmakers, notably the German ones, can supply SECAM sets in the UK. It's worth making enquiries.

Perhaps the easiest solution, to start off with anyway, is to convert a UK monochrome TV receiver. Late dual-standard sets are the best, in particular the Bush TV161 series. Modifications are relatively simple with a dual-standard set, as the French system L is a mixture of our 405- and 625-line systems. As a bonus, the set can still be kept dual-standard, switching between the UK and French u.h.f. systems.

Typical Conversion

As an example then we'll take the Bush TV161, though other dual-standard chassis will doubtless serve just as well.

First disconnect the switching linkage between the i.f. and timebase panels, and solder the timebase panel for operation on 625-lines only.

Connect switches 2S1a, b and c on the i.f. panel permanently in the 625-line position. This is best done at the rear of the panel, by breaking the "405" print to the switches and linking the "625" contacts together. To cater for the 6.5MHz spaced French sound, the old 405 sound i.f. needs to be moved from 38.15MHz to 33MHz. This is easily accomplished by increasing the value of C24 in the 2VT2 transistor can from 3.9pF to approximately 5.6pF,


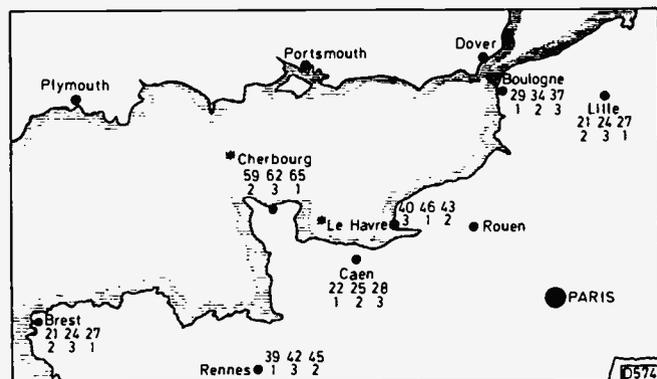


Fig. 1: French TV transmitters which can be received in the UK. Those marked with an asterisk provide a strong signal in good reception conditions only. Cherbourg, Le Havre and Boulogne have an e.r.p. of 100kW, all others an e.r.p. of 1MW. Rouen is also a 1MW transmitter, but the channels are the same as Crystal Palace. The network number is shown beneath the channel number.

MANOR SUPPLIES

PAL COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

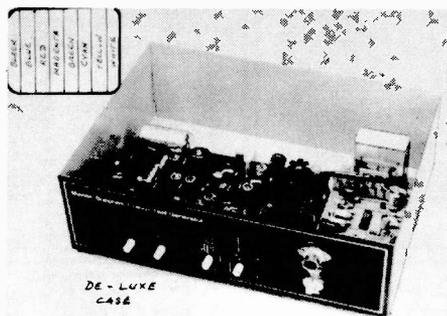

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £40.25 + £1.10 P/Packing. DE-LUXE CASE £5.55. ALUMINIUM CASE £2.95, BATT HOLDERS £1.70, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.55.

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £28.75 + £1.15 p.p. CASE EXTRA £1.75. BATT. HOLDERS £1.70.

- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed.

MK4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.35 P/Packing.

VHF MODULATOR (CHI to 4) FOR OVERSEAS £4.00.

INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.

(ABOVE PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT KIT (incl. TEXAS DECODER). Wide range of facilities in colour. External unit. AE input to set. Write or call for further information. See working demonstration model! Easy to build and results guaranteed for every completed unit.


Texas XM11 Decoder £149.50 p.p. £1.10.

Auxiliary Units £101.00 p.p. £1.65.

De-Luxe Case £17.00 p.p. £1.10. (or total p.p. £2.95).


Prices include 15% VAT

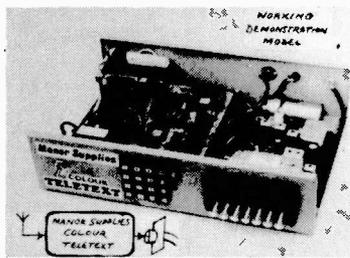Separate Price List for Individual Units available.



Changes from Teletext to picture without switching aerials.

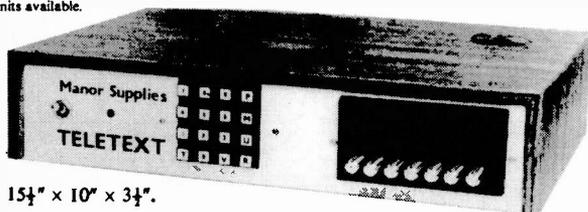Armchair control of Teletext and T.V. stations.



15½" x 10" x 3½".

Now available ex stock **NEW MULLARD TELETEXT DECODER MODULE 6101 VML**, complete and tested. Details on request.

COLOUR. UHF & TELEVISION SPARES

NEW 'TELEVISION' COLOUR RECEIVER PROJECT PARTS BEING SUPPLIED. POWER, SIGNAL & TIMEBASE. SEND OR PHONE FOR LIST. WORKING DEMONSTRATION SET NOW ON SHOW.

NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.80 p.p. £1.10. T.V. PORTABLE PROJECT PARTS AVAILABLE. SEND OR PHONE FOR LIST. WORKING MODEL AT 172 WEST END LANE, NW6.

TV TEST GENERATOR UHF MODULATOR £4.00 p.p. 40p.

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £12.65 p.p. 50p. (ALUM CASE £2.30 p.p. 80p.) COMPLETE TESTED UNITS, READY FOR USE (DE LUXE CASE) £25.00 p.p. £1.10.

ADDITIONAL GREY SCALE KIT £3.35 p.p. 35p. STAB MAINS POWER SUPPLY FOR ABOVE £5.50 p.p. 80p. UHF SIGNAL STRENGTH METER KIT £19.40 (ALSO VHF VERSION) ALUM CASE £1.75, DE-LUXE CASE £5.60 p.p. £1.10.

CRT TESTER & REACTIVATOR PROJECT KIT £24.00 p.p. £1.45 "TELEVISION" COLOUR SET PROJECT (1974) SPARE PARTS STILL AVAILABLE. ALTVE. IF COMPL. & TESTED £16.80 + £1.10 p.p. PHILIPS 300 Series IF Panels £2.90 p.p. £1.10.

PHILIPS 210, 300 Series Frame T.B. Panels £1.15 p.p. 75p. PHILIPS 19TG 170 Series Timebase Panels £2.90 p.p. £1.00. BUSH A823 CONVERGENCE PANEL £7.60 p.p. £1.00.

BUSH A823 (A807) Decoder Panel £8.65 p.p. £1.10. BUSH A823 SCAN CONTROL PANEL £2.90 p.p. 80p. BUSH A823 IF PANEL (EXPORT VERSION) £3.25 p.p. 95p.

BUSH BC6100 IF PANEL (EXPORT VERSION) £5.75 p.p. 80p. BUSH A816 IF PANEL (SURPLUS) £2.90 p.p. 80p. BUSH 161 TIMEBASE PANEL A634 £4.40 p.p. £1.00.

GEC 2010 SERIES TIMEBASE PANEL £1.15 p.p. 95p. GEC 2040 Surplus Panels, ex-rental. Decoder £5.75 p.p. £1.00. GEC 2040 Convergence Control Panel £2.90 p.p. £1.00.

DECCA CTV25 Single Stand. IF Panel £4.40 p.p. 75p. DECCA Colour T.V. Thyristor Power Supply. HT, LT etc. £4.40 p.p. £1.10. BUSH TV 312 IF Panel (Single I.C.) incl. circuit £5.75 p.p. 75p.

BUSH TV Portable Eleven Volt Stab. Power Supply Unit £4.40 p.p. £1.10. PYE 697 Line T.B. P.C.B. for spares, £2.80 p.p. £1.10. THORN 3000 VID, IF, DEC, FTB SALVAGED £5.75 ea. p.p. £1.00.

THORN 8000/8500 POWER/SALV. SPARES £2.88 p.p. 60p. THORN 8000/8500 TIME BASE, SALV., SPARES £5.52 p.p. 90p. THORN 9000 LINE T.B. SALV., SPARES £8.62 p.p. £1.38.

MULLARD AT1022 Colour Scan Coils £6.90 p.p. £1.30, AT1023/05 Convergence Yoke £2.90 p.p. 95p, AT1025/06 Blue Lat. 90p p.p. 40p, Delay Lines, DL1E £1.00, DL20, DL50 £4.00 p.p. 80p.

PHILIPS G9 Signal Board Panels for small spares £4.80 p.p. £1.00. PHILIPS G6 single standard convergence panel, inc. 16 controls, switches etc., and circuits £4.25 p.p. 95p, or incl. yoke, £5.65. G8 Decoder panels salvaged £4.25. Decoder panels for spares £2.00 p.p. 95p.

VARICAP UHF MULLARD U321 £8.97, ELC1043/05 £6.35 p.p. 40p., G.I. type (equiv. 1043/05) £4.00 p.p. 40p. Control units, 3PSN £1.40, 4PSN £1.75, 5PSN £2.00, 6PSN £2.10, Special offer 6PSN £1.15 p.p. 40p. TAA 550 58p p.p. 20p. Salv. UHF varicap tuners £1.75 p.p. 40p.

BUSH "Touch Tune" assembly, incl. circuit £5.75 p.p. 85p. VARICAP UHF-VHF ELC 2000S £9.80 p.p. 75p. VHF ELC 1042 £6.90 p.p. 40p.

UHF/625 Tuners, many different types in stock. UHF tuners transisted. incl. s/m drive, £3.28. Mullard 4 position push button £2.88 p.p. £1.00, Ae Isol 70p p.p. 25p.

TRANSISTORISED 625 IF for T.V., sound, tested. £7.82 p.p. 75p. HELICAL POTS, 100K. 4 for £1.40 p.p. 25p.

RBM 774 250R Mains Droppers, four for £1.15 p.p. 40p. LINE OUTPUT TRANSFORMERS. New guar. p.p. 95p.

BUSH 145 to 186SS series £8.05
BUSH, MURPHY A816 series £9.80
DECCA DR 121/123, 20/24, MS1700, 2001, 2401 £7.85
DECCA MS2000, 2400 £6.70
FERG., HMV, MARCONI, ULTRA 900, 950, Mk. 1 950II, 1400, 1500, 1580 £6.80
GEC 2000, 2047 series, etc £7.85
INDESIT 20/24EGB £7.85
ITT/KB VC2 to 53, 100, 200, 300 £7.85
MURPHY 1910 to 2417 series £8.05
PHILIPS 19TG170, 210, 300 £7.85
PYE 368, 169, 769 series £7.85
PYE 40, 67 series (36 to 55) £7.85
PAM, INVICTA, EKCO, FERRANTI equivalents as above.
SOBELL 1000 series £7.85
STELLA 1043/2149 £7.85

SPECIAL OFFER

BUSH TV 125 to 139 £3.25
GEC 2114J/FINELINE £5.50
GEC 448/452 £1.75
THORN 1590/1591 £5.50
KB VCI, VCII (003) £3.25
MURPHY 849 to 939 £3.25
COLOUR LOPTS p.p. £1.10.
BUSH CTV 25 Mk3 £9.45
BUSH 182 to 1122 etc £11.30
MURPHY Equivalents £11.30
DECCA "Bradford" (state Model No. etc) £10.15
GEC 2028, 2040 £11.30
GEC 2110 Series £12.20
ITT CVC 5 to 9 £7.80
PYE 691, 693, 697 £20.50
PHILIPS G8 £10.15
THORN 3000/3500 (Scan or EHT) £7.85
THORN 8500 £12.50

THORN MONO SCAN COILS (850 to 1500) £3.25 p.p. 95p. THORN 950 3 Stick Tray £2.75 p.p. 55p. Others Available. 6-3V CRT Boost Transformers £3.70 p.p. 85p., Auto type £2.10 p.p. 50p.

CALLERS WELCOME AT SHOP PREMISES (Tel: 01-794-8751)

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE NOT NORMALLY ADVERTISED

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Sta. (Bakerloo & Jubilee)

W. Hampstead British Rail Sta. (Richmond, Broad St.) (St. Pancras, Bedford) Bus Routes 28, 159

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

ALL PRICES INCLUDE VAT AT 15%

**QUARTZ LCD
5 Function**

Hours, mins., secs., month, date, auto calendar, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch.

Very slim, only 6mm thick.



M1

**QUARTZ LCD
7 Function**

Hours, mins., secs., month, date, auto calendar, back-light, seconds STOP WATCH.

£9.65

Guaranteed same day despatch.

Very slim, only 6mm thick.



M2

**QUARTZ LCD
11 Function** SLIM CHRONO

6 digit, 11 functions. Hours, mins., secs., day, date, day of week, 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calendar. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£12.65 Thousands sold!

Guaranteed same day despatch.



M3

**QUARTZ LCD
ALARM 6 Function**

Hours, mins., secs., month, date, back-light, 24 hour ALARM. Adjustable stainless steel bracelet. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

**QUARTZ LCD
ALARM 7 Function**

Hours, mins., secs., day, date, alpha day, back-light, auto calendar. Adjustable stainless steel bracelet. Only 9mm thick.

£15.95

Guaranteed same day despatch.



M5

**QUARTZ LCD Alarm
Chronograph with Dual
Time Zone Facility**

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£22.65



M6

**SOLAR QUARTZ LCD
Chronograph with Alarm
Time Zone Facility**

Constant LCD display of hours and minutes, plus optional seconds or date display, plus day of the week and am/pm indication. Perpetual calendar, day, date, month and year. 24 hour alarm with on/off indication. 1/10 second chronograph measuring net, lap and first and second place times. Dual time zone facility night light. Only 9mm thick.

£25.65



M7

**QUARTZ LCD
Alarm Chrono**

22 function, 6 digit. Hours, mins., secs., date, day of week, stopwatch, split time, alarm, second watch (dual time), back-light. FRONT BUTTON OPERATION.

£22.65

Guaranteed same day despatch.

METAC ★ PRICE



M8

**SOLAR QUARTZ LCD
Chronograph**

6 digit, 11 function. Hours, mins., secs. 1/100, 1/10 secs., mins. Split and lap modules. Auto calendar and back light. Powered from solar panel with battery back-up.

£13.95



M9

SEIKO Alarm Chrono

LCD, hours, mins., secs., day of week, month, day and date, 24 hour Alarm, 12 hour chronograph, 1/10th secs., and lap time. Back light, stainless steel, HARDLEX glass. List Price £130.00 METAC PRICE

£105.00



M10

SEIKO Chronograph

LCD, hours, mins., secs., day of week, month, day, date, 12 hour chronograph, 1/10th secs. and lap time. Back light, stainless steel water resistant, HARDLEX glass. List Price £85.00 METAC PRICE

£68.00



M11

**SOLAR QUARTZ LCD
5 Function**

Genuine Solar Solar panel with battery back-up. Back light and auto calendar. Hours, mins., secs., day, date. Quality metal bracelet.


£8.95

Guaranteed same day despatch.



M12

**HANIMEX
Electronic
LED Alarm Clock**

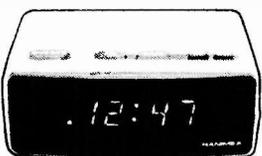

Features and Specification:
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indication. Repeatable 9-minute snooze. Display bright/dim modes control. Size: 5.15" x 3.93" x 2.36" (131mm x 11mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

£9.65 Thousands sold!

Guaranteed same day despatch.

M13

**QUARTZ LCD
Ladies Slim Bracelet**

5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.

£15.95

Guaranteed same day despatch.



M14

**QUARTZ LCD
Ladies 5 Function**

Only 25 x 20mm and 6mm thick. 5 function. Hours, mins., secs., day, date and back light and auto calendar. Elegant metal bracelet in silver or gold. State preference.


£9.95

Guaranteed same day despatch.



M15

**DIGITAL
LED CLOCK**

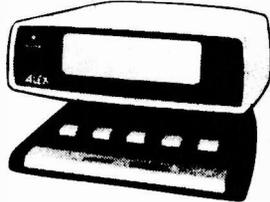

Automatic brightness control. Weekend alarm cancel.

Features and Specification:
Hour/minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on/off control. Display flashing for power loss indicator. Repeatable 9-minute snooze. Automatic brightness control. Weekend alarm cancel.

£10.95

Guaranteed same day despatch.

M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and the order details clearly, enclose 30p for post and packing or the amount stated. We do not wait to clear your cheque before sending the goods so this will not delay delivery. All products carry 1 year guarantee and full money back 10 day reassurance. Battery fitting service is available at our shops. All prices include VAT.

Trade enquiries: Send for a complete list of trade prices - minimum order value £100. Telephone Orders: Credit card customers can telephone orders direct to Daventry or Edgware Rd., 24 hour phone service at both shops: 01-723 4753 03272-76545.

CALLERS WELCOME
Shops open 9.30 - 6.00.




Metac ELECTRONICS & TIME CENTRES

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

increasing the value of C54 in the 2VT5 transistor can from 47pF to 82pF, and increasing the value of C61 in the 2VT6 transistor can from 33pF to 47pF. In the 405-line position the i.f. panel switching now corresponds to the French system, while the 625-line position remains as required for UK reception.

Alignment

When it comes to alignment, no alteration to the UK side of things is required of course. Switch the i.f. strip to the French position, and tune in a French transmission. Sound of sorts should be heard immediately, probably accompanied by buzzing.

Starting with the sound take-off coil L11, adjust for maximum sound and least buzz. Then adjust the first and second sound i.f. coils L26 and L30 for the same results. Go back to L11, and repeat the procedure once or twice. This should produce buzz-free sound. Note that the contrast control (405/French) should not be over advanced, or sound-on-vision and vision-on-sound may result (the old 405-line system complaint!). When satisfied with the sound alignment, tweak L10 (2VT2 can) in the vision channel on test card (yes, the French radiate the PM5544 pattern all afternoon on the third channel!) for optimum frequency response. You should now have a highly sensitive French/UK TV receiver.

Single-standard Sets

Single-standard sets can also be modified, but require a great deal more work – not so much in providing for demodulation of the positive vision signal, but in arranging for the a.m. sound. An approach I've used is to employ the ubiquitous surplus Philips G8 gain and vision selectivity modules (see Fig. 2).

Three modules are required, two selectivity ones and a gain module. Insert one selectivity module immediately after the tuner, diplexing the output from this to the main i.f. strip and to the second selectivity module. The output from the latter goes to the gain module, whose video output pin provides the audio signal. By suitably aligning all the Philips cores, good sound can be obtained.

The correct vision signal sense can be obtained by using a phase-splitter stage in the main i.f. strip, following the vision detector diode. A suitable transistor is often present anyway as an emitter-follower, the simple course then being to take the signal from its collector. Beware of any d.c. coupling. If this is present, a.c. coupling will have to be introduced. You might think that simply reversing the detector diode would do the trick, but this will totally upset the a.g.c. circuit and any d.c. coupling present. No interaction occurs incidentally between the Philips units and the existing i.f. strip.

As it stands of course this results in a single-standard (French) TV receiver. By adding switching (a relay is best) however the sound and vision can be switched back to the UK standard: use the existing 6MHz feed for the sound, and tap the emitter of the phase-splitter transistor for the vision – also cut the supply voltage to the a.m. sound i.f. system.

Colour

The more adventurous reader may ask what scope there is for modifying a UK colour set for SECAM reception. Modifying an existing PAL only board would be a formidable task unfortunately. SECAM is a completely

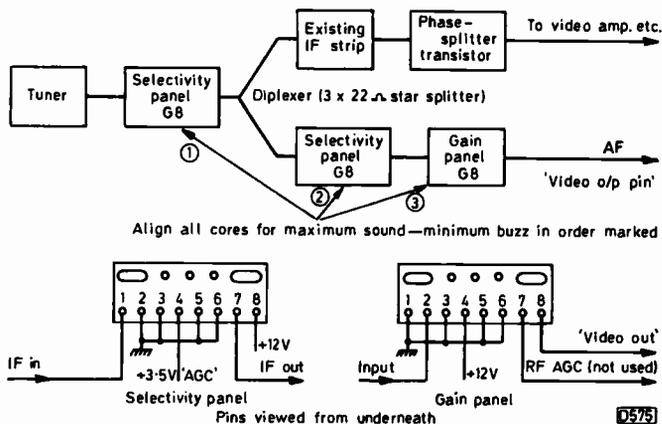


Fig. 2: Block diagram of a single-standard receiver converted for reception of French TV.

different system up to the matrixing of the luminance and colour-difference signals. One or two UK setmakers have produced export versions of their chassis, often with a PAL/SECAM decoder. The latter is a clever one with electronic switching between the two systems. I've seen such a board for the Thorn 3000 chassis. The situation with this is somewhat complicated by the fact that the board was made in Belgium and not by Thorn themselves, who cannot supply it.

Results

Providing there's a clear take-off in the French direction, and interfering signals are at a low level, signals of sorts should be seen at up to 150 miles from a 1MW French u.h.f. transmitter. Needless to say, high-gain aerials mounted as high as is practical should be used, particularly the farther inland one is. As mentioned earlier, the main problem will come from UK transmitters on the same or adjacent channels. If several French transmitters seem likely to be received, a wideband aerial on a rotator could be employed. During enhanced tropospheric conditions the signals become very strong indeed – often with stations from the south of France causing co-channel interference.

If you obtain a SECAM colour receiver, you'll obviously need a higher signal level than for monochrome reception. Below a certain signal level, colour noise increases rapidly with the SECAM system, due to the f.m. threshold effect. This happens only at quite low signal levels however, and in practice SECAM can provide a better signal-to-noise ratio than PAL under mediocre signal conditions. Noise tends to appear as long streaks with SECAM and can be irritating.

It would be possible to build a monochrome French to UK system converter. The French signal would have to be demodulated and then remodulated to the UK standard on a spare UK u.h.f. channel. I can somehow envisage a few G8 modules in the French i.f. strip!

One inconvenient point is that you can never be too sure what programmes are being shown on French TV until the day of the transmission. The French TV guide is published well in advance: it can be ordered through large newsagents.

It should be possible to obtain a teletext decoder or modify a UK one to receive the French Antiope system (different again, needless to say!) and have pages of French information in good signal areas.

Finally, my thanks to many friends in the south of the country who have helped with advice on suitable transmitters for different areas. And my apologies to anyone who is well and truly out of range of French TV... ■

The V2000 VCR System

THE new V2000 VCR system which has been jointly developed by Philips and Grundig represents a major advance in VCR technology. The compact cassette, roughly $7 \times 1 \times 4\frac{1}{4}$ in., is capable of providing up to eight hours' playing time. It achieves this by using a quarter-inch video recording system, i.e. there are two sets of video tracks (see Fig. 1) one above the other on the $\frac{1}{4}$ in. tape. The arrangement is the same as that used with audio cassettes: when one track length has been used, the cassette is withdrawn, turned over, and the second section of track is used. With each track section providing up to four hours' playing time, the total playing time is a maximum of eight hours.

The greatly extended playing time – and thus tape economy – has been achieved by cramming yet more information on to the tape. The speeds used are much the same as with other current machines, but the track width is the narrowest yet. As a comparison:

System	Tape Speed	Read/write speed*	Track Width
N1700	6.56cm/sec	8.1m/sec	84 μ m
SVR (Grundig)	3.95cm/sec	8.2m/sec	51 μ m
VHS	2.339cm/sec	4.83m/sec	49 μ m
Betamax	1.873cm/sec	6.6m/sec	30 μ m
V2000	2.44cm/sec	5.08m/sec	22.6 μ m

*Taking head and tape movement into account.

So the increased information packing density has been attained by using quarter-inch recording and very narrow tracks, laid down side by side. This implies the need for great accuracy in the head/track alignment, and for this purpose a new technique has been adopted – dynamic track following (DTF).

The video heads (see Fig. 3) are mounted on small plates of piezoelectric ceramic material which are in turn attached to the upper section of the head drum. Since piezoelectric material bends when a voltage is applied to it, this enables the heads to be moved vertically. The control voltage is obtained from the head as it follows the track, so that the alignment of the head with the track can be continuously maintained. The use of this technique has other advantages: interchangeability of cassettes between machines is guaranteed, while slow-motion, fast-motion and still-frames can be obtained with good picture quality and without interference.

The self-correcting video head system (dynamic track following) operates during both record and playback. The usual control track is dispensed with. As shown in Fig. 1 there are audio tracks at each side of the tape, both capable of stereophonic recording/reproduction, and cue tracks in the centre. These latter are not used in the initial production VCRs, but will be employed in later development of the system. For control purposes, DTF signals are laid down on the track during recording at frequencies below the 625kHz chrominance subcarrier (see Fig. 4). These vary between adjacent tracks, following the sequence (Fig. 5) 102kHz (f1), 117kHz (f2), 164kHz (f4), 149kHz (f3). Frequencies f1

and f4 are recorded by one head (K1), frequencies f2 and f3 by the other (K2).

Dynamic Track Following

During playback, the relevant video head scans the recorded tracks. In addition to the video signal and the track's DTF signal there will also be, due to crosstalk, difference frequencies is compared, to find out in which signal frequencies on adjacent tracks. Say head K1 is scanning a track with a 102kHz DTF signal (f1). Adjacent tracks will carry 117kHz (f2) and 149kHz (f3) signals. The two difference-frequency signals produced will thus be 15kHz and 47 kHz ($117 - 102\text{kHz} = 15\text{kHz}$, $149\text{kHz} - 102\text{kHz} = 47\text{kHz}$). The relative amplitude of these two difference-frequencies is compared, to find out in which direction the head is tending to move away from the correct track, and as a result a correction signal is obtained for application to the piezoelectric plate. This then pulls the head back into alignment with the track. The difference

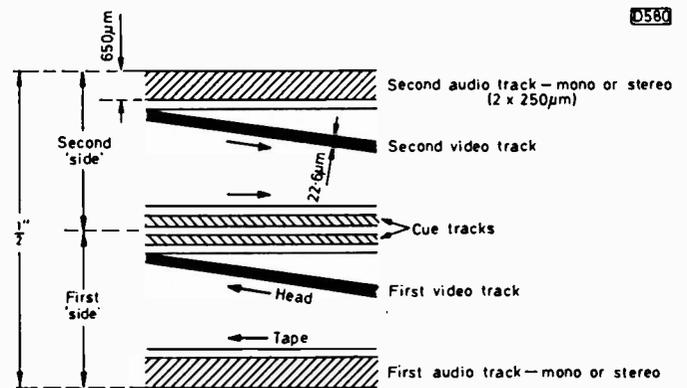


Fig. 1: Arrangement of the tracks on the tape.

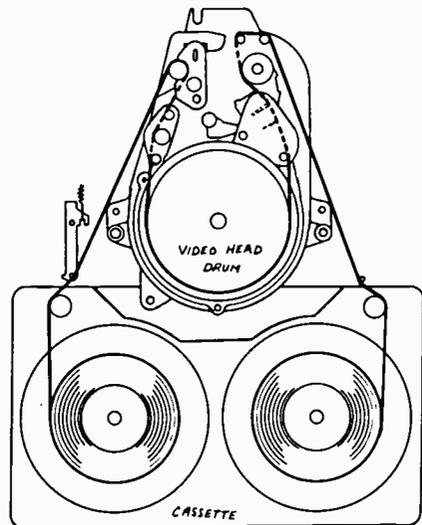


Fig. 2: The M-wrap tape path in the recorder.

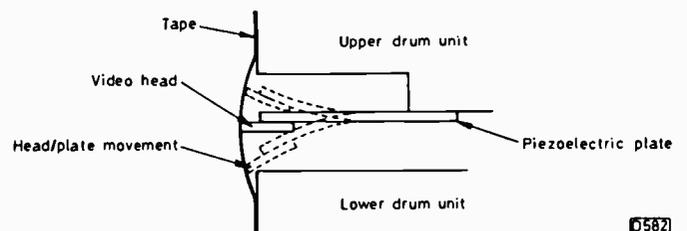


Fig. 3: The heads are mounted on servo-controlled piezoelectric elements to provide dynamic track following.

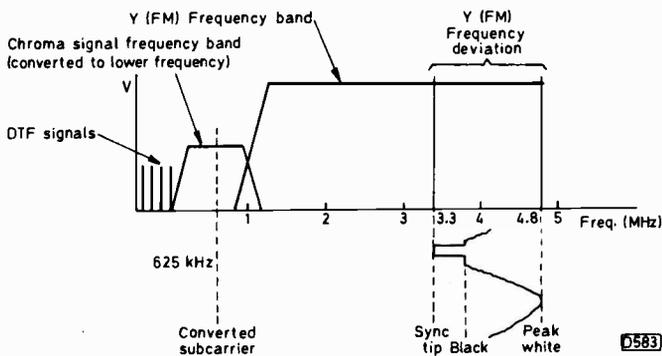


Fig. 4: The signal positions within the bandwidth.

frequencies are 15kHz and 47kHz whatever the track, as some addition and subtraction exercises will show.

During the period when a video head is not in contact with the tape, i.e. between fields, its piezoelectric carrying plate is restored to the position it had at the commencement of the previous track. When the head returns to contact with the tape therefore it's in the correct starting position.

The head drum is specially heated in order to reduce to a minimum the effect of any mechanical changes during the scanning of the tape. By keeping the drum at a constant temperature, its diameter hardly alters. Wear on the head and frictional losses due to the tape sticking to the drum are thus reduced to a minimum.

If the two heads show an equal deviation in the same direction during playback, the effect is remedied by moving the tape. For this action, the control voltage from the DTF discriminator is fed to the tape servo. The result is that the tape is moved relatively to the heads, restoring the correct alignment. This is termed automatic tracking (see later).

During recording, the heads must be lined up in exactly the correct position with respect to each other, since the video tracks are laid down side by side with no guard band. Due to tolerances however, for example the hysteresis characteristics of the piezoelectric head carrying plates, there is no permanent static condition. This means that dynamic control is necessary during recording as well as during playback.

This is done by placing one head in the nominal position and including the other in a control loop. An additional reference signal, at 223kHz, is recorded on the track for a one and a half line period during the field flyback. During the following one and a half lines, no signal is recorded on the track (see Fig. 6). This enables the signal on the adjacent track to be read in order to provide the required control voltage.

Servo Systems

The tape runs through the recorder at a constant speed of 2.44cm/sec. For this purpose the capstan is directly connected to the capstan motor spindle, on which a 216-pole tachogenerator is mounted. The motor speed is 116.4 r.p.m. Speed control during recording is achieved by comparing the phase of the signal from the tachogenerator with that of a fixed 419.376Hz signal produced by a crystal oscillator. During playback, the previously mentioned automatic tracking system is used to move the tape into the required position instead of using phase comparison.

The head drum is also directly driven, with the motor connected to a 125-pole tachogenerator. The speed of the head drum is 1,500 r.p.m. For phase comparison purposes a phototransistor, coupled to the head drum, produces one

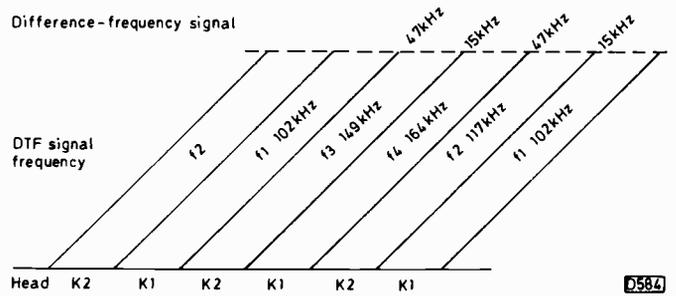


Fig. 5: The sequence of the dynamic track following signals. Read from the right, this is f1, f2, f4, f3.

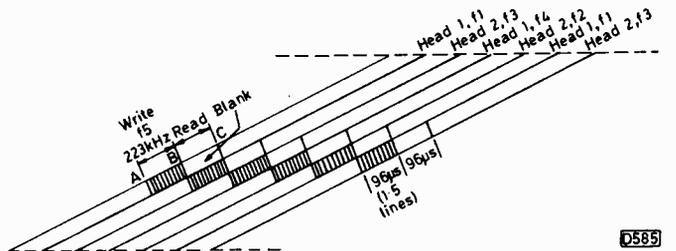


Fig. 6: For dynamic head position correction during recording, a signal is laid down during a 96µsec period while the field flyback is occurring. Recording ceases during the following 96µsec period, the head then reading the crosstalk signal from the previous track. The resultant signal initiates the servo control action.

pulse per revolution (25 pulses per second). These are compared to a 25Hz reference frequency. During recording the reference frequency is produced by division from the field frequency; during playback it's produced by a crystal oscillator.

The scanning unit, which consists of the microchassis and the integrated head drum motor/video head drum assembly, has been designed so that it can be automatically preadjusted in the factory. The scanning unit can be exchanged without difficulty in either the factory or the service department. The same interchangeability applies to the following parts of the scanning unit: the head drum motor (with or without head drum), the head drum, the audio head, and the erase head.

Signal Handling

As with the N1700 system, the slant-azimuth technique (the two heads are angled at +15° and -15° with respect to each other) is used to avoid luminance crosstalk between adjacent tracks. To avoid crosstalk between the lower frequency chrominance signals, a comb filter consisting of a 128µsec delay line and an adder circuit is used. This of course is a similar idea to the basic PAL arrangement. These techniques are said to ensure good picture quality during playback, while good sound quality is achieved by a new system developed by Philips - "dynamic noise suppression".

Operation

The VCR has been designed for simple, foolproof operation. Search tuning is employed, as in the Grundig SVR system (see *Television*, July). Once the search button has been pressed, the recorder automatically scans all the TV bands. Accurate, automatic tuning occurs immediately a station is found. The tuned-in frequency can then be stored in the memory, by operating the "store" command followed by a channel number chosen by the user. A maximum of 26 channels can be stored in the memory.

The Philips VR2020 VCR has five memory blocks for storing recording instructions. Each block stores the required starting time, stopping time, day of recording and the relevant channel number. Programming can be done up to 16 days in advance. Once the recorder has been programmed in this way, anyone using the recorder in between is warned by the indication "attention timer". The cassette lift opens if there is no cassette or a protected cassette in the machine, drawing the user's attention to the fact that he cannot record under these circumstances.

There's a separate switch, which can be set in either of two positions, for each side. In one position recording is possible: in the other, marked by a red indicator, recording and erasure are not possible. This provides protection against unintentional erasure.

If the auto-rewind button is pressed at the end of the pre-programmed recordings, the recorder automatically winds back to the beginning of the tape.

The VR2020 is equipped with a four-digit electronic tape counter. To go back to a certain tape position quickly, the go-to button is pressed and the required counter number is keyed in on the keyboard. The recorder then winds forward or backwards to the position requested. The counter is

automatically set to zero at the beginning of the tape. It can also be set to zero manually if required.

An infra-red remote control system provides remote channel selection and control of all the tape drive functions.

The use of an advanced microprocessor makes operation very simple. If any key is pressed at random, a check is first of all made by the microprocessor's programme to see whether the requested operation is permissible – for example in the case of recording with a protected cassette in the machine. The recorder is completely safeguarded against incorrect operation therefore.

As a result of using microprocessor control, it's possible to switch over directly from wind to play or from off to record for example: all the necessary intermediate steps are automatically carried out by the recorder.

If the electricity supply is interrupted, the channels stored in the memory are retained for about three months. Also, once the supply has been restored any interrupted operation continues.

The recorder contains a wideband aerial amplifier which passes the off-air or VCR signal to the TV set without loss. It's not necessary therefore to switch the recorder over between off-air and playback when the VCR and the TV set are used alongside. ■

No Clock Display

Steve Beeching, T.Eng. (C.E.I.)

THE problem with a Sony Betamax SL8000 VCR we had in recently was that on switching on the clock didn't show any digits. The first thing I did of course was to check that the supplies were reaching the timer board – these are 10V, -20V and 2.5V a.c. They all seemed to be o.k., making the checks with my oscilloscope since any further testing would probably require its use to check on the presence or absence of pulse waveforms. So on we went to check the waveforms around the timer i.c. IC3101. There seemed to be a general absence of pulses, except for pins 1 and 42 which had 400kHz pulses and pin 36 which had a 50Hz squarewave – at the correct levels.

There are five enable lines to the display board (four figures plus colon), on pins G1 to G5. Enable is 10V, otherwise the lines are biased to -20V via 100kΩ resistors. Each figure consists of a seven-segment arrangement, a to g, and each part of the colon has its own input. Without any input pulses there's no illumination – the digits are multiplexed, G1 to G5 being strobed in turn and each set of segments altered digit by digit at a fast rate to produce a constant display.

It seemed at the time a good idea to change the timer i.c., no mean feat since it has 42 soldered pins and is a CMOS

type at that. So the new one went in with me chained to earth. Switch on and . . . oh dear, no lights! Still no pulses anywhere either. My workshop has dents in the wall that match my forehead after previous VCR nasties, so I added a few more.

A closer look was needed since something had obviously been missed. Check i.c. pin voltages carefully. All correct except for pin 7, the reset pin, which is connected to the collector of Q3001 (see Fig. 1). This transistor should have been turned hard on, with its collector at 0V. Instead, it was at 7.5V. Drastic measures were called for, so I earthed the collector – and got lots of pretty green lights from the display. I then discovered that the 10V line was in fact also 7.5V.

Now Q3001 resets all the timer i.c. functions when the VCR is switched on, or in the event of a mains interruption, thus eliminating any false timer action. At switch on, Q3001 is biased off by the -20V rail. The 10V rail rises slowly, due to the large values of the decouplers and the action of C8104 (see Fig. 2) in the 10V regulator circuit. As the 10V rail rises, the voltage at the collector of Q3001 increases and, at a point just over 8V, the timer i.c. is powered but held reset. At about 8.2V, zener diode D3001 switches on, applying a positive voltage to the base of Q3001 which also switches on. Its collector voltage falls to 0V, thus removing the reset.

So if the 10V rail is lower than 8V, the i.c. is held reset and nothing happens. The fault was clearly in the power supply, and swapping the timer or display boards would have had no effect on the fault. The trouble was in fact due to an open-circuit joint on the 10V supply reservoir capacitor C8106. The effect of the rest of the circuit was to produce a well-smoothed 7.5V supply.

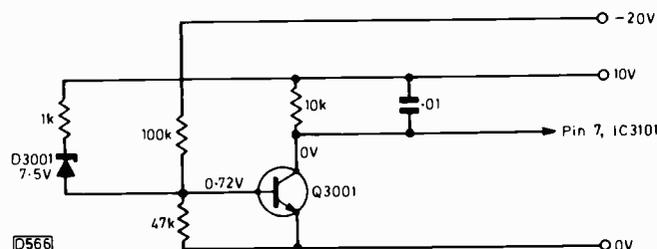


Fig. 1: Timer i.c. reset circuit.

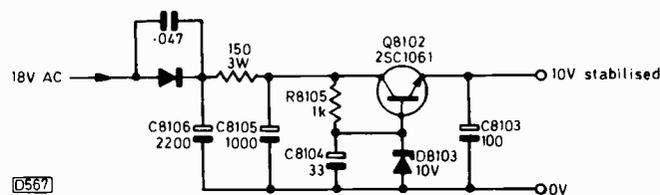


Fig. 2: 10V supply circuit.

All Slog and No Grog . . .

Les Lawry-Johns

THERE'S absolutely no rest for us busy boys lately. Even when we finish you can bet your life some joker will spoil your pint with "I don't want to bother you, but . . .". You escape from that and settle down at home with a bite to eat and a quick glimpse of the telly before bedtime and the thing changes channels all on its own. So you give up and go to bed and dream about sets that won't go right or women that won't go wrong or something. Look at yesterday for instance. It started with colourless sets.

First an 8500 (Ferguson) with the complaint that the colour had been intermittent but had now gone beyond recall.

Dealing with Lack of Colour

I suppose we all have our own pet ways of making a start when tackling faults that can have various possible causes. I always like to start on this one by proving the presence of timing pulses from the line output stage. These are applied to connection 3/2 on the decoder panel on the 8000 series chassis, and can be measured at TP9 in the burst gate circuit. Finding little activity here we nipped smartly over to the timebase panel and had a look at TP28, which again was lifeless. It was a short step from here to R404 (33k Ω) which was found to be open-circuit.

Nice going we thought. Keep it up and we might regain some of our lost confidence which has taken a bashing lately due to persistent wrong diagnoses, er diagnostics, er, jumping to the wrong conclusions, with the consequent hours lost plodding toward the right conclusions.

And the Next Gent Please

Of course the next case just had to be loss of colour again. Apparently Mr. Earlybirth had had a spot of trouble with his Philips G8 of late, and was dissatisfied with the service he had received from the original suppliers of the set. He produced massive repair bills to prove it. Horrific would perhaps be a better word. Since the last one was very recent and was incurred in the quest for lost colour, I suggested that he returned the set to the repairers for their approbation. "I'm too scared" he said. "It'll probably be a hundred quid this time." I couldn't quite see how this could happen, but as he was clearly adamant about not going back with it I didn't press the point further.

"O.K. Mr. Earlybirth, leave your phone number and we'll ring you when it's sorted out."

Clearly this was one to approach with caution. It was one of the separate panel type, and it was obvious that some work had been done on both the signal and the decoder panels.

So we decided to cut across the usual routine and fit a known good decoder panel which we just happened to have lying around. With this in there was still no colour, so we did something daft. We refitted the original panel and then checked for the positive and negative pulses at pins 8 and 1 respectively at the rear edge connector. The negative pulses were there but there was no joy at pin 8 (TP39). So over we went to the timebase (line scan) unit and checked at pin 1 of

plug U. Nothing here so follow the track along to R576 (4.7 Ω , or 4R7 if you like that better). It didn't look well, and indeed proved to be open-circuit. A replacement of the same small wattage did not overheat, and the positive pulses were now present on my little diode probe.

Sadly however there was still no colour (and I hadn't left the colour control turned down like I did on that one some time ago, chasing all over the place before I realized it).

So out came the decoder panel again and in went the test one. Full colour. Suspecting hanky-panky, we looked with care at the removed panel. The core of the reference oscillator coil looked decidedly out of place, whilst all the other cores were still sealed. So back went the panel and careful adjustment to the suspect core restored almost normal results except that the grey scale was out and the picture was too bright with the brightness right down.

Resetting the blue d.c. level control R297 restored normal brightness, and a touch up on the green and red level controls restored the grey scale to very nearly perfect. All that remained was to converge the set. This was easier said than done, since R1933 on the convergence panel had seen better days. A new 10 Ω potentiometer put this right, and we were quite pleased with the result.

"Mr. Earlybirth. Your set's ready. Bring a couple of hundred quid with you, ha, ha."

It was a bit premature really because I suddenly became aware that there was no sound when I turned it up to hear what the tennis scores were (I can't read).

The rear cover had to come off again, and the sound returned on its own. This proved to be nothing more than a poor contact on the audio plug, so we weren't all that upset.

Put the back on again, having wangled the control knobs through, and that was that. We didn't really sting him. He got change from three fivers, and was happy.

Only No Sound

"Not a lot wrong" he said. "Not a lot. Just no sound." As this was an ITT CVC5, it came as no surprise and of course we made straight for the PCL86. Giving it a quick clout with a screwdriver handle restored the sound with a sharp crack. In went a new valve and we waited for the sound to burst forth. It didn't. Applying the voltmeter, we found rather more h.t. than we expected. Not too much voltage you understand, but what there was was in too many places.

As usual, my mind went completely blank. I knew I should have h.t. on pin 6, the output pentode anode, but I couldn't remember what pin the screen grid voltage should be on. So we had 200V on pins 6, 8 and 3, and 100V on pin 9. Looking it up, we should have had 200V on pins 6 and 3, but pin 8 was the control grid. Not to be bothered with niceties, the valve was whipped out and the voltage on pin 8 vanished. Another duff new valve, but what had happened to the cathode bias resistor? Nothing apparently. It still read 120 Ω and the 50 μ F decoupler was also in one piece. Another new valve restored the sound.

"While you're at it" said Mr. Ratchet (christian name I presumed was Paul, as it said P on the job sheet), "you

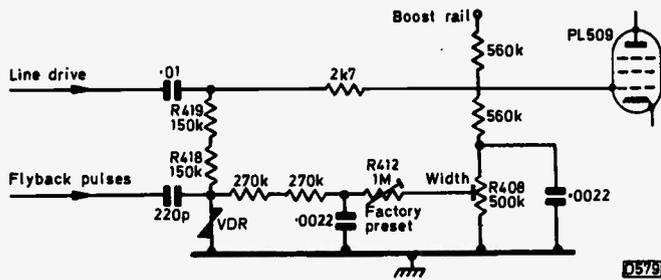


Fig. 1: The width control circuit used in the ITT CVC5 and subsequent hybrid colour chassis. The design is conventional, but care has been taken over its implementation. Pairs of resistors are used to reduce the voltage stress across the individual resistors, and the 0.0022 μ F decoupling capacitors are included to protect the factory and dealer preset width controls against high pulse voltages.

might have a quick look at the picture as there's a line down the left side." There was indeed. It looked like brushing of some sort, and the width only just made it. Just to put us on the wrong track (tracking?) there was a sharp crack of discharge from inside the line output section.

Off came the screening and we peered suspiciously at the tripler and focus assembly. Nothing seemed out of place, and the discharge did not recur. Bearing in mind Eugene's good advice from earlier in the year, we looked hard at the line output transformer subpanel for signs of dry-joints etc. Everything seemed in order.

Looking again at the picture, the line scan did not seem all that even. We concluded however that once the left side dribble was cured everything else would fall into line as it were. For want of something better to do, we changed the PL509. This made matters a damn sight worse, so we changed the PY500 as well. This didn't alter things at all.

Since the width was only just making it, we reset the "dealer width" control R408 (see Fig. 1) which didn't do anything. Neither did the "factory width" control R412, which seemed most peculiar. A meter applied to the PL509's control grid showed that there was adequate drive, and incidentally shot out the width. "Ah ha" we said (not being able to think of anything better).

So off went the supply and we got down to checking the resistors in the width circuit. All seemed in order until we came to the series resistors R418 and R419. They should have been something like 150k Ω each. R419 read o.k., but R418 didn't read at all. A new resistor in this position enabled us to set up the width correctly, with a nice even line scan and no dribble.

"Took a long time to find that, didn't it?" commented Mr. Ratchet. "My name's not Trundle" I protested (sorry Eugene). "My name is the one over the door and I am a well known ditherer. Always have been and it's a bit late to change now. If I was any good at this job I wouldn't be doing it." Now there's a profound thought. I must think about that.

So the Day Wore On

Just for a change we thought we'd have a go at a Ferguson audio effort. "Won't play the records it won't." This was a relief, as we'd had a bit of trouble of late with the cassette side of one of one of these and didn't relish another bout for a time. BSR deck, funny noise, and dead slow on 45 r.p.m.

Take off the turntable and clean up the centre post and bush. Rough up the idler wheel, and a drop of oil into the top motor bearing. Reassemble and check. Nice, quiet and

only slightly fast on the strobe (as usual). Switch to 33. Turntable stops. Do it again. O.K. on 45, stops on 33.

Take off turntable and check on idler wheel. Clunks nicely on to the drive spindle on 45, doesn't want to be pulled across fully on 33. Conclude that there's friction on swing spindle in the 33 position. Oil and try again. No better. Take out unit and check on nylon assembly and notice that swing arm has to come down a shade out of its true position which would make the idler contact the motor spindle. Why? Don't know.

Note that there's movement to spare on the assembly when in the 45 position, but none in the 33 position (determined by a nylon ratchet rotating the cog teeth of the nylon speed selector drum). Think. "If the ratchet is pushing the cog drum too far round, why not move it back one tooth?" Ease out the ratchet and allow the drum to advance one tooth. Instant success. Now plays 33 as well as 45.

Question: how did the ratchet and cog get out of sync in the first place? Never mind, plod on.

Think about calling it a day and cashing up. Not difficult as there is no cash in till other than that wrested from Mr. Earlybirth and Mr. Pawl, sorry Mr. Ratchet. Will have to reduce fluid intake until our monetary affairs improve.

Later

We had only a couple of halves, and that was spoilt by someone wanting to know something I didn't know anything about. And so to bed.

Funny it keeps changing channels like that. I'll have to see if it's the i.c. Never mind. Think about it tomorrow. Wonder what I can chat about in the next article? Twenty five years with the September issue, seems only yesterday.

Thirty years ago: wrestling with old prewar Cossor 1210 with the funny sync separator. Two top caps at 90 degrees, one for line, the other for frame (not field then). Bloody great 15in. tube.

Thirty five years, thirty six or so . . . I can still hear the boys singing Lily Marlene.

"There's a desert squadron
Somewhere in the blue,
No one there that matters
To tell 'em what to do.

About nine miles this side of Alexandria, well past the stinking tannery, is a small village called Fayid.

We had an airfield there, right on the Med, only the coast road between. Our main war effort was making sailing dinghies to play with out in the bay on our make and mends (afternoons off). Fleet requirement unit they called us, 775 squadron.

And so to Sleep

There was a panic on. The skipper was going barmy. He called Sub-Lt. Thompson in at the double.

"Listen Thompson. Something's up. Jerries are flying Ju 52s across to Benghazi carrying secret loads of I don't know what, but the army's going mad and the Admiral has been on the blower. He wants 'em shot down. Trouble is they're not ordinary Ju 52s, they're Ju 52Ms. The M is for metal. Bloody great lengths of corrugated iron right the way along 'em.

Machine guns are no good, 20mm. cannon shells are deflected back and shoot down or own Seafires - deflected back by the grooves of the corrugated iron. Only one thing to do. We've had a 70mm. gun mounted on a Hurricane and that'll knock a hole in anything. The recoil when the

thing goes off will knock you back a hundred knots, so you must go in at two hundred to avoid stalling.

We know your reputation for missing the target every time Thompson, but this time you mustn't miss. All the other pilots have shot themselves down."

Sub-Lt. Thompson,
Second in command,
Couldn't find the target,
Too much bloody sand.
He dropped all his bombs out in the blue,
Too bloody true, and so would you.
If you had seen Benghazi,
If you had seen B.G.

So off went our hero, out into the blue, flying the Hurricane burdened with the enormous gun.

Approaching Benghazi, he could see the distant speck of the three-engined Ju 52 out over the Med. He could see other flying things as well. Large birds called Shite Hawks, wheeling about the sky, hungry for prey. Peculiar birds. The only ones that fly in herds. Lots of cows and only one big bull. He was so wrapped up in what was before him that he didn't see what was behind. An Italian Macchi 42 was slowly coming up astern.

The Ju 52 came lumbering in over the coast line as our Subby closed in to attack. He could plainly see the corrugated side of the big jerry transport looming large.

Before he could get into the firing position, he saw the transport dropping its secret cargo. Hundreds of cones falling, each with their little parachute. Cornets from the toe of Italy. So that was it. Cornettoes. What a devilish scheme, seeing that allied troops held Benghazi at the moment.

They bomb Benghazi every night,
And when they're not,
They're getting tight.

He fired his mighty gun. Crash it went. Bash came the recoil, and the Hurricane practically stood still. Unfortunately, the Macchi had closed up for the kill and couldn't avoid hitting the Hurricane. Bang, they went.

The impact shot Subby Thompson clean out of his cockpit, and he'd forgotten his parachute. Whizz he went, through the crisp North African air. The big Shite Hawk saw his chance and moved in, grasping Subby firmly in his enormous talons. The 70mm. shell tore into the Ju 52 and down it went. Boom. The tangled mass of the Hurricane and the Macchi spiralled into the sea off the coast. Leaving our hero suspended as usual by Bull Shite.

Footnote to a Previous Epic

Footnote to the saga of Lt-Commander Pragham-Wright who attacked the whole Italian 7th fleet in the Straits of Messina (see July issue).

Nineteen ships were sunk that day by one torpedo. The twentieth ship was rammed by the lone Swordfish, whose pilot was heard to shout just before impact "one more for the pot."

We've had several enquiries, you see.

NEW TELEPART CATALOGUE

The new 152-page Telepart trade catalogue, listing over 5,000 items, is now available from Willow Vale Electronics Ltd., Old Hall Works, Arborfield Road, Shinfield, Reading, Berks. (Telephone: Reading (0734) 884444.)

next month in

TELEVISION

● COLOUR RECEIVER OPTIONS

Most constructors who embarked on the colour receiver project we started a year ago should by now either be receiving pictures on their set or be very close to finishing construction of the basic receiver.

Next month we start on the various options mentioned earlier in the series, starting with the addition of teletext reception facilities. For this purpose the Texas Instruments XM11 teletext decoder module is used, together with a very simple interface board and an inexpensive cable linked keypad. This approach provides the simplest possible solution to the provision of teletext, and the whole thing can be built and working within a matter of hours.

In subsequent issues we will describe how to add remote control to the basic receiver: this will be followed by the ultimate option, the addition of teletext and remote control – the remote control system operating both the receiver controls and the teletext functions. This last option will enable constructors to build a receiver which compares favourably with up-market commercial sets.

● SECAM COLOUR

Following our feature on receiving French TV this month, we thought it would be a good idea to take a look at the way in which the French colour system (SECAM) works. Keith Cummins describes the system, its pros and cons, and reports on his observations of the results off-screen.

● TACKLING MAINS/BATTERY PORTABLES

With their need to be able to operate from a 12V supply as well as the mains, portables present their own problems. A dead set can be a very dead one indeed – no signs of life at all. John Law describes how to tackle this sort of problem, with particular reference to the Thorn 1590/1591 chassis.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the OCTOBER issue of TELEVISION (55p), on sale September 17th, and continue every month until further notice.

NAME.....

ADDRESS.....
.....
.....

while if a resistor on the chassis side increases in value it may become impossible to black out the screen — assuming that the brightness control is in the c.r.t.'s grid circuit.

Fig. 1(b) shows the brightness control arrangement used, with a.c. video coupling, in the Thorn 1500 chassis. In this example the control grid is taken to chassis and is thus at 0V d.c., serving simply as a suitable point at which to apply the negative-going flyback blanking pulses. The brightness control sets the positive d.c. voltage at the cathode — range from 0 to about 90V. This is equivalent to varying the control grid between 0 and -90V of course.

If in doubt as to whether advancing the setting of the brightness control reduces the tube bias sufficiently, a simple test is to momentarily short the grid and cathode together. This should not significantly increase the brightness of the raster with the brightness control well advanced. If it does, either the c.r.t.'s cathode voltage is too high or its grid voltage too low.

On occasion, you might find that as the brightness control is advanced to increase the c.r.t. grid voltage, so the cathode voltage tends to follow suit. This is a sure indication of grid-cathode leakage in the tube. It can sometimes be cured by flashing techniques, but usually means that a replacement tube will be needed.

Hybrid Colour Sets

When we come to hybrid colour sets using colour-difference drive, we find a very similar situation to monochrome receivers using d.c. coupling. The luminance output pentode is d.c. coupled to the three c.r.t. cathodes, and all the considerations of changed value screen grid and cathode resistors etc. still apply. In addition however it will be found that brightness control is effected by varying the output pentode's negative control grid bias, while this bias may also be affected by the action of the beam limiter circuit. When operating correctly, excessive e.h.t. current will result in the beam limiter increasing the bias on the luminance output pentode. A fault in the beam limiter circuit may change the bias in either direction however. In total therefore many components could be responsible if you find that the luminance output pentode's anode voltage cannot be swung between the normal limits.

An interesting example of such a fault came our way recently, the set being an Ekco one fitted with the Pye hybrid chassis. Although the tube was undoubtedly of low emission, appraisal of the test card showed that all three darkest sections of the grey scale were at about the same darkness level, and couldn't be separated by juggling with the contrast and brightness controls. Probably the most common cause of excessive luminance output pentode anode voltage (lack of brightness) and thus high tube cathode voltage is a low-emission PL802 luminance output valve. A replacement brought no improvement this time however. The beam limiter threshold control RV16 was found to have no effect, while the tube's first anode preset controls were as near maximum as possible consistent with obtaining a relatively untinted raster.

The brightness control circuit used in this chassis is shown in Fig. 2. It acts in conjunction with the d.c. restorer diode D39 which conducts on the tips of the negative-going sync pulse tips. When this happens, C39 is charged to the voltage at the slider of the brightness control, which is connected between 20V and -20V rails via R213, R212 and R202. The brightness control thus sets the d.c. level at the control grid of the PL802 luminance output valve, providing a smooth transition from minimum to maximum brightness. It also provides a means for the beam limiter to act — when the beam limiter transistor VT35 conducts, at

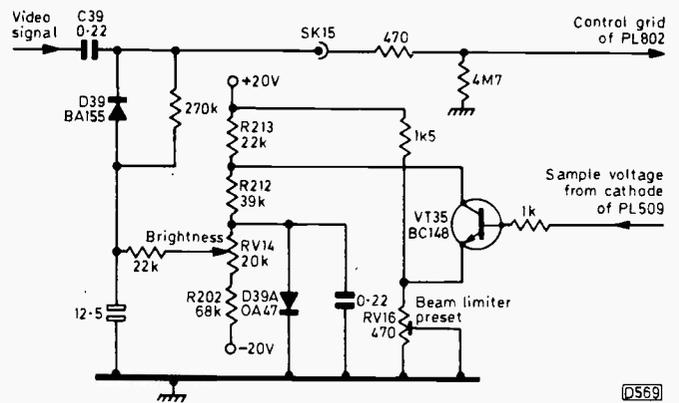


Fig. 2: Brightness control circuit used in Pye hybrid colour receivers. The d.c. restorer diode D39 conducts on the tips of the negative-going sync pulses, returning the coupling capacitor C39 to the d.c. voltage set by the brightness control. The beam limiter also acts on this circuit. With excessive beam current, the line output valve's cathode voltage increases and the beam limiter transistor VT35 switches on. Its collector current, flowing through R213, alters the voltages along the resistive chain R213/R212/RV14/R202. The voltage at the slider of the brightness control is thus pulled back, and the beam current reduced to a safe level.

maximum beam current, the voltage at the junction of R212/R213 is reduced.

Withdrawing the small white plug from socket 15 on the colour-difference amplifier panel removes both the luminance signal feed and the control bias from the control grid of the PL802. When this was done, with the brightness control at maximum, there was an immediate and most pronounced increase in brightness level. Clearly then the brightness control was failing to reduce the bias on the PL802 sufficiently, and on making voltage checks along the resistor network R213, R212 etc. R212 was found to be open-circuit. Replacing R212 also restored normal beam limiter action.

Restricted brightness control range on hybrid colour sets using colour-difference tube drive can also of course be caused by incorrect tube control grid voltages. The colour-difference signals are a.c. coupled to the grids, with clamps to establish the correct d.c. conditions. These are usually driven by line-frequency pulses, so absence of the pulses will remove the clamp action. This is quite rare however: more common is drift or variation in the d.c. level from one gun to another due to a component value change. With the Pye hybrid chassis however the tube will be completely or almost completely biased off should either R389 or R393 on the CDA panel go open-circuit. The effect of this is to remove the clamp voltage, so that the voltages at the anodes of the clamp triodes fall to a very low figure instead of the correct 100V or so.

The diversity of brightness control arrangements used in receivers using RGB drive is such that we can't go into them here. Fortunately they don't in practice give much trouble.

Preset Controls

Often the trouble is simply an incorrectly adjusted preset control. Preset brightness controls are to be found in sets of all types, and operate in a variety of ways. In the GEC hybrid chassis there's a background control which sets the colour-difference signal clamping level. In addition you'll often find in a colour set a beam limiter threshold control. It's vital that all controls that affect the brightness level of the picture are correctly set up. This is especially so when the tube is ageing, since wrongly adjusted presets accentuate the effects of low tube emission. ■

New Teletext Signal Panel

Alan Kitching

SOMETIME ago I built up the original version of the *Television* teletext decoder. I found however that under certain signal conditions an unusually high number of errors was present on the display. These could usually be eliminated by adjusting the slice level, the tuning and the clock frequency slightly, but the main difficulty seemed to lie in the critical nature of the data recovery section used in the original design. To overcome this problem, a new signal panel was designed. This uses the original i.f. strip along with a new adaptive data recovery section which is able to cope with quite large variations in signal strength and noise levels. Improvements were also made to the i.f. strip earthing arrangements, to overcome certain problems with the original.

The circuit of the new section of the board is shown in Fig. 1. The video input is taken from the positive-going video output of the TDA440 i.c. (pin 12). The new section also includes a 6MHz sound preamplifier as some problems were experienced in the original design at low sound modulation levels.

Buffer Stage

The positive-going video output from pin 12 (which was left disconnected in the original design) of the TDA440, at about 3V peak-to-peak, is a.c. coupled to the base of the emitter-follower Tr1. This provides a low-impedance source to drive the sync and data separator circuits. A parallel tuned

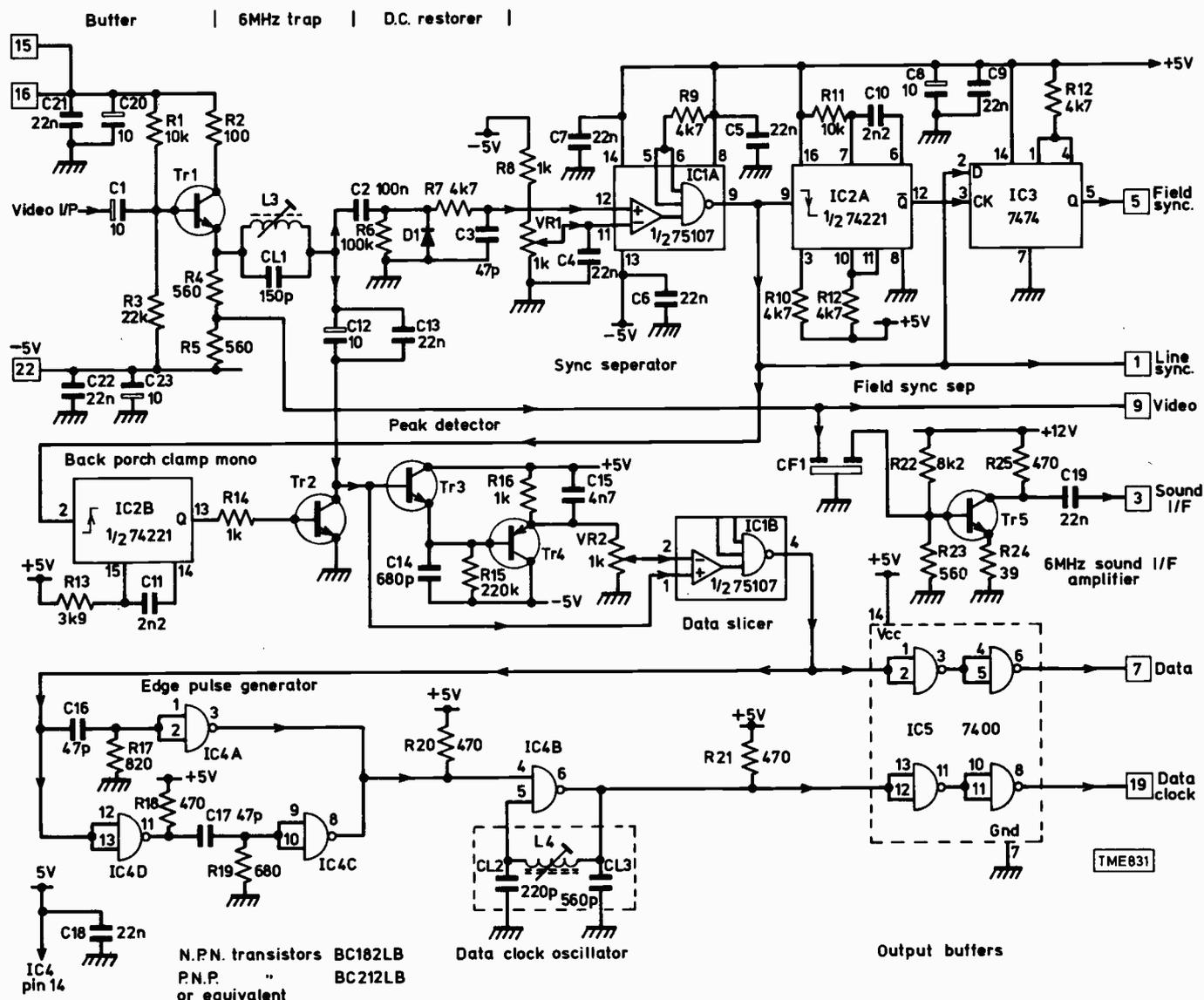


Fig. 1: Circuit diagram of the revised data recovery section. The i.f. section remains unchanged. R12 shown twice in error.

circuit (L3/CL1) removes the 6MHz intercarrier sound signal, which would otherwise upset the operation of the data clock – this is very close to 6MHz.

Tr1 has a split emitter-load resistor (R4/R5), so that a high-amplitude video signal is available to drive the sync and data separators and a low-amplitude video output is available to drive the modulator and the sound i.f. preamplifier Tr5. This split emitter load also provides isolation between the external circuit connected to the video output edge connector pin 9 and the internal data separation circuitry, thus reducing the number of errors caused by locally generated interference.

Sync Separator

We will deal first with the sync separator section of the circuit. The composite video at the emitter of Tr1 is a.c. coupled via C2, with D1 providing d.c. restoration, clamping the sync pulses at about -0.6V. R7 and C3 form an h.f. filter, removing the chroma information and the remaining video signal from the feed to the positive input (pin 12) of the comparator IC1a. The negative input (pin 11) of the comparator is connected to a voltage between -5V and 0V: this sets the level at which the composite video is sliced. The level is set to approximately half-way through the sync pulse portion of the waveform. TTL mixed sync appears at the output pin 9.

The negative-going leading edges of the sync pulses trigger the monostable IC2a, which switches state for 18μsec. The Q output then returns to logic 1. This rising edge clocks the D-type flip-flop IC3, the Q output of which takes up the state of the D input which, during the field sync period, is at logic 0. We thus have negative-going field sync pulses at the Q output of IC3. These are taken out to edge connector pin 5, while the line sync pulses are brought out to pin 1, maintaining compatibility with the original board.

Adaptive Data Slicer

Turning now to the data separation section of the circuit, the positive-going trailing edges of the sync pulses trigger monostable IC2b. This produces a short, positive-going pulse of about 2μsec duration during the back porch period. The pulse switches Tr2 on, clamping the black level of the video signal, which is a.c. coupled via C12/C13, at approximately 0V regardless of the average level of the signal. The slice level is set by using a peak detector to detect the data amplitude. The resultant information is used to set the slice level midway between the positive data peaks and black level. Let's see how this operates.

Tr3 and C14 form the positive data peak-detection circuit, with R15 providing the time-constant to set the decay time. The time-constant is fairly long compared to the data bytes, to prevent too much decay during the worst-case condition of fourteen consecutive zeros. Tr4 offsets the base-emitter voltage drop of Tr3, while the shorter time-constant of C15, R16 increases the rise time of the peak-detector circuit to reduce the effect of large noise spikes.

The slice level can be adjusted by means of VR2 over the range from 0V to the positive data-peak level. The voltage from the slider of VR2 is applied to the negative input (pin 2) of the second comparator IC1b, the video signal being fed directly to its positive input (pin 1). The output, at pin 4, is a TTL signal representing the sliced serial data. This is buffered by half the 7400 i.c. IC5.

Data Clock

The serial data from pin 4 of the data slicer i.c. is also fed to the clock generator section. The differentiating network C16, R17 produces a positive-going output to turn on gate IC4a, forcing its output to the low state coincident with the positive-going edge of the data bits. IC4d inverts the serial

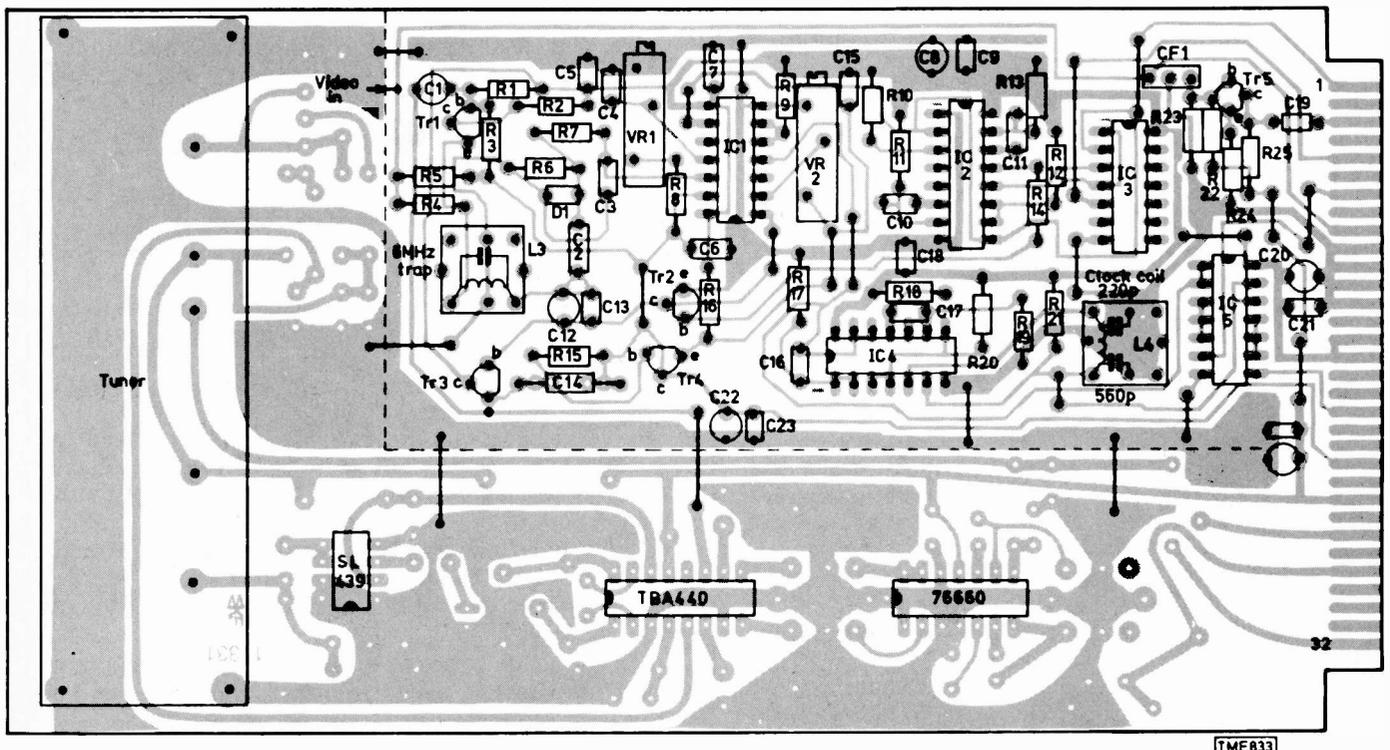


Fig. 2: Component location diagram of the new signal board. The component location diagram for the i.f. section is given in the October 1977 issue.

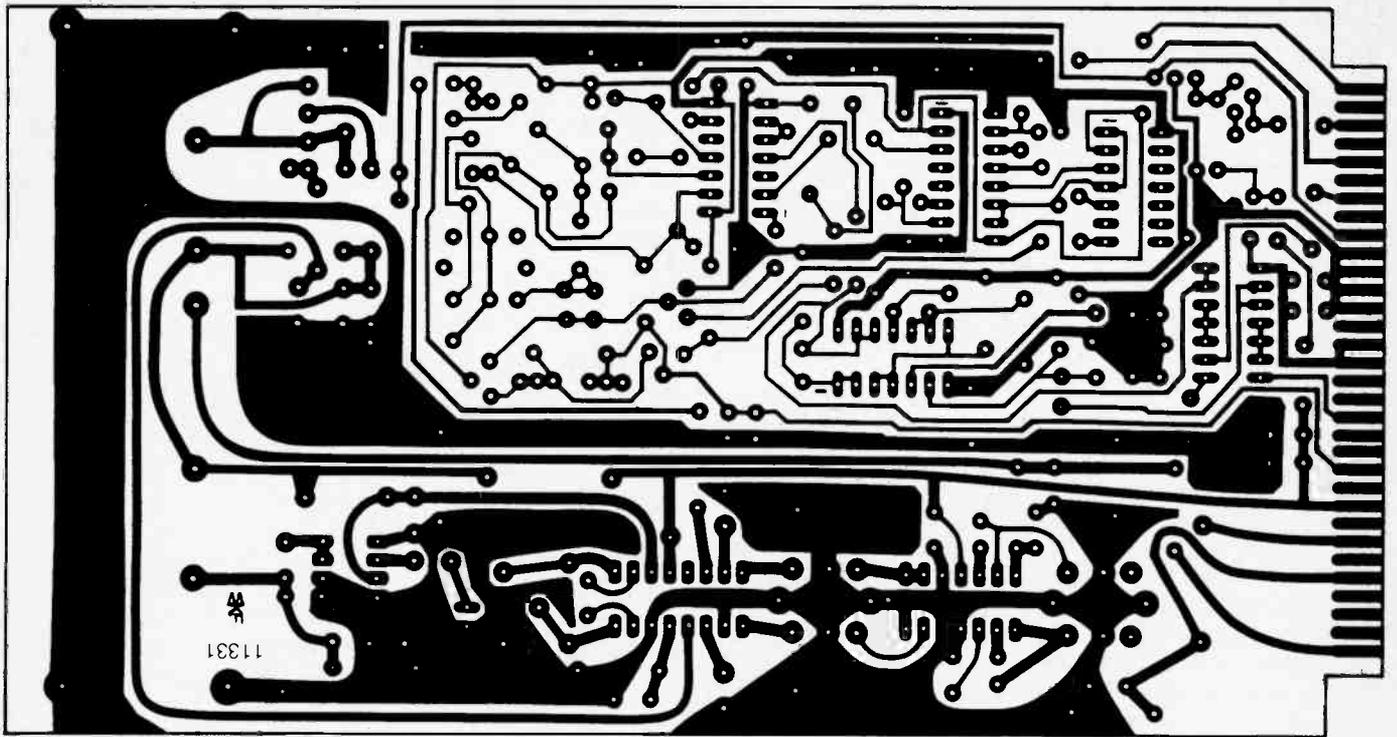


Fig. 3: Copper pattern of the new signal board. The board is available from our Readers PCB Services, reference 11331. Note that the actual size of the board is 386mm x 205mm.

★ components list
(new data recovery section only)


Resistors:

R1	10k
R2	100Ω
R3	22k
R4	560Ω
R5	560Ω
R6	100k
R7	4k7
R8	1k
R9	4k7
R10	4k7
R11	10k
R12	4k7
R13	3k9
R14	1k
R15	220k
R16	1k
R17	820Ω
R18	470Ω
R19	680Ω
R20	470Ω
R21	470Ω
R22	8k2
R23	560Ω
R24	39Ω
R25	470Ω
All ¼W 5% carbon film	
VR1	1k
VR2	1k
½in. cermet multiterm	
Semiconductors:	
IC1	75107
IC2	74221
IC3	7474
IC4	7403
IC5	7400
D1	1N4148
Tr1	BC182L
Tr2	BC182L

Capacitors:

C1	10μF 25V
C2	100n
C3	47p
C4	22n
C5	22n
C6	22n
C7	22n
C8	10μF 10V
C9	22n
C10	2n2
C11	2n2
C12	10μF 10V
C13	22n
C14	680p
C15	4n7
C16	47p
C17	47p
C18	22n
C19	22n
C20	10μF 10V
C21	22n
C22	22n
C23	10μF 10V
CL1	150p polystyrene
CL2	220p polystyrene
CL3	560p polystyrene
All electrolytics tantalum bead.	
All capacitors not otherwise specified ceramic plate.	
Tr3	BC182L
Tr4	BC212L
Tr5	BC182L
Coils etc:	
L3	25 turns
L4	30 turns
both 36swg, ecw on 4mm formers with cores and screens.	
CF1	SFE6.0MB Murata

Fig. 4: Constructional details of coil L4.

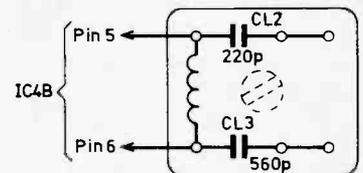

data and drives another differentiating network C17, R19. This, with IC4c, operates in the same way as IC4a/C16/R17, producing a short negative-going pulse coincident with the negative-going edge of the data bits. The outputs from IC4a and IC4c are connected in the wired-or mode, with R20 forming a common load resistor. Consequently a series of short, negative-going pulses coincident with the positive- and negative-going data transitions is fed into one input of the data clock oscillator formed by IC4b with L4 and the associated tuning capacitors. The pulses serve to lock the oscillator in the correct phase and frequency as the incoming data. The free-running frequency of the oscillator is set by the core in L4 to the data clock frequency (6.9MHz).

The data clock output is buffered by half the 7400 i.c. IC5 and is then brought out to edge connector pin 19.

Construction

If the new signals board is to be constructed using components from the original board, these can be transferred on a one-to-one basis – the component layout is identical. If the circuit is to be built from scratch however the constructional details given in the October 1977 issue should be followed and alignment carried out as described in the November 1977 issue.

Construction of the new section of the board is straightforward, following the component layout shown in Fig. 2. The only component requiring any special consideration is the clock coil L4, which differs slightly from the original. It can be wound on the same former however after removing the old winding (see details in components list). Take care to

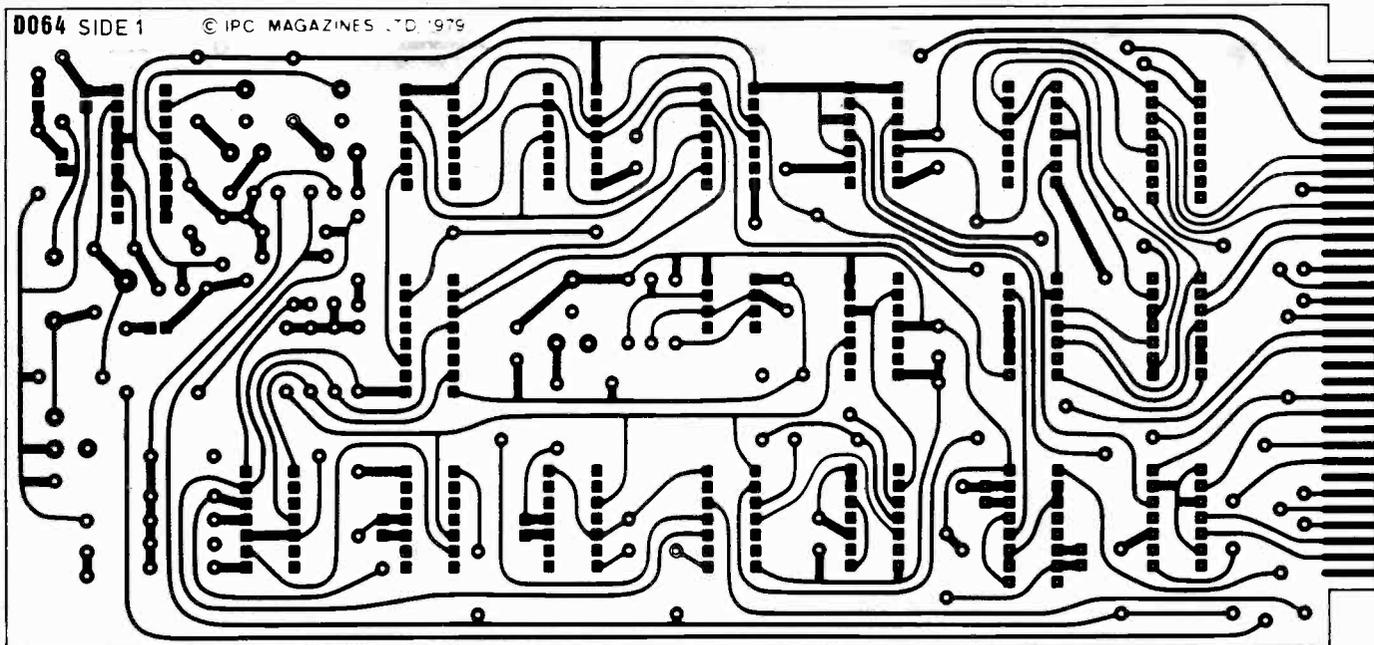


Fig. 5: Underside copper pattern for the teletext options card (see last month), ref. D064.

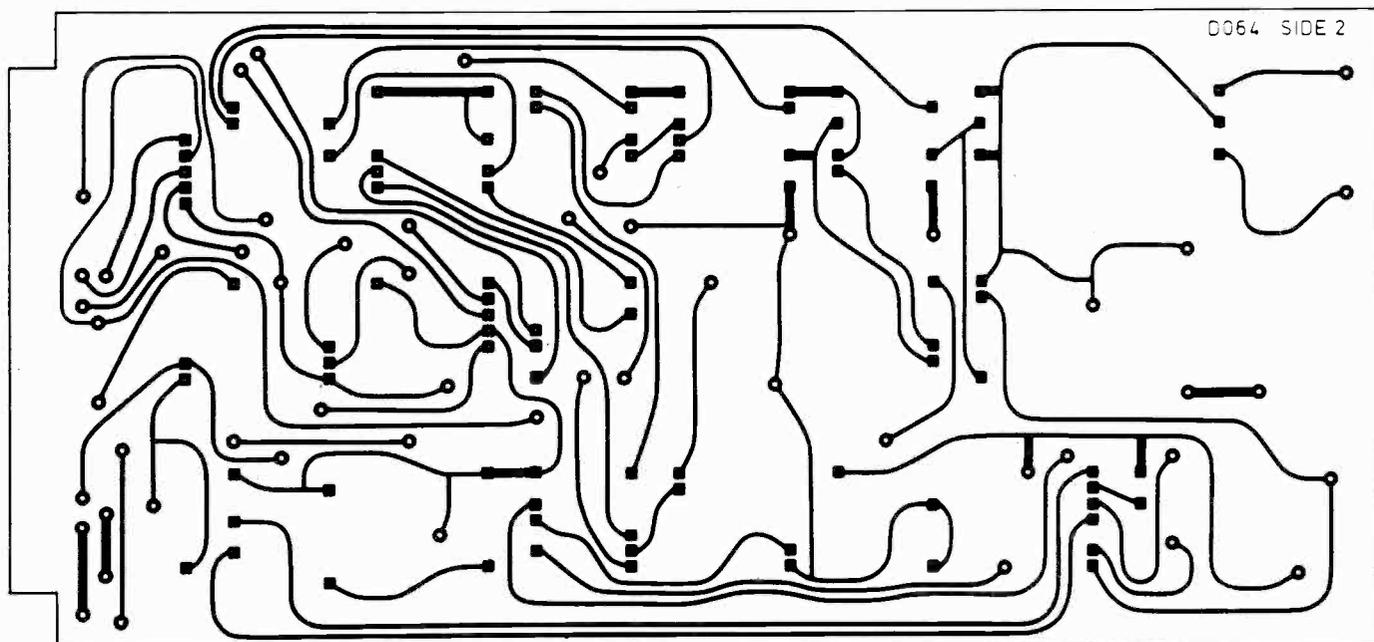


Fig. 6: Topside copper track of the options card D064. Note that the actual board size is 438mm x 205mm.

connect the decoupling electrolytics on the negative supply rail the correct way round, i.e. positive to chassis.

Alignment

Assuming that the alignment and the 6MHz sound trap have been set up in accordance with the instructions given in the November 1977 issue, and that a good picture which includes a teletext transmission is being received, the new data recovery section should be set up as follows. Switch to the text mode and connect a scope to pin 9 of IC1a. Adjust VR1 to produce TTL composite sync at this point. Check that TTL field sync pulses are present at pin 5 of IC3: if not, check the timing components and connections around IC2a and IC3.

Select the page roll mode and whilst watching the screen adjust VR2 for the most rapidly changing display of characters. When this point has been reached, adjust L2

slowly until the text is as free of errors as possible and complete pages are seen to roll through. Repeat these last two steps if necessary.

Finally switch off page roll and select the clock-cracker page. Adjust L4 a quarter of a turn at a time until complete pages of error-free text are produced. Check on all the other channels. ■

MONOCHROME MONITOR CONVERSION

One of the fundamental requirements for a monitor is that it is isolated from the mains. We neglected to mention this point in our article last month, and it's important that constructors incorporate a mains isolating transformer adequately rated for the set being converted. A suitable transformer is the RS Components type 207-469 which is rated at 500VA. Where the power consumption does not exceed about 150W, the 200VA type 207-021 can be used.


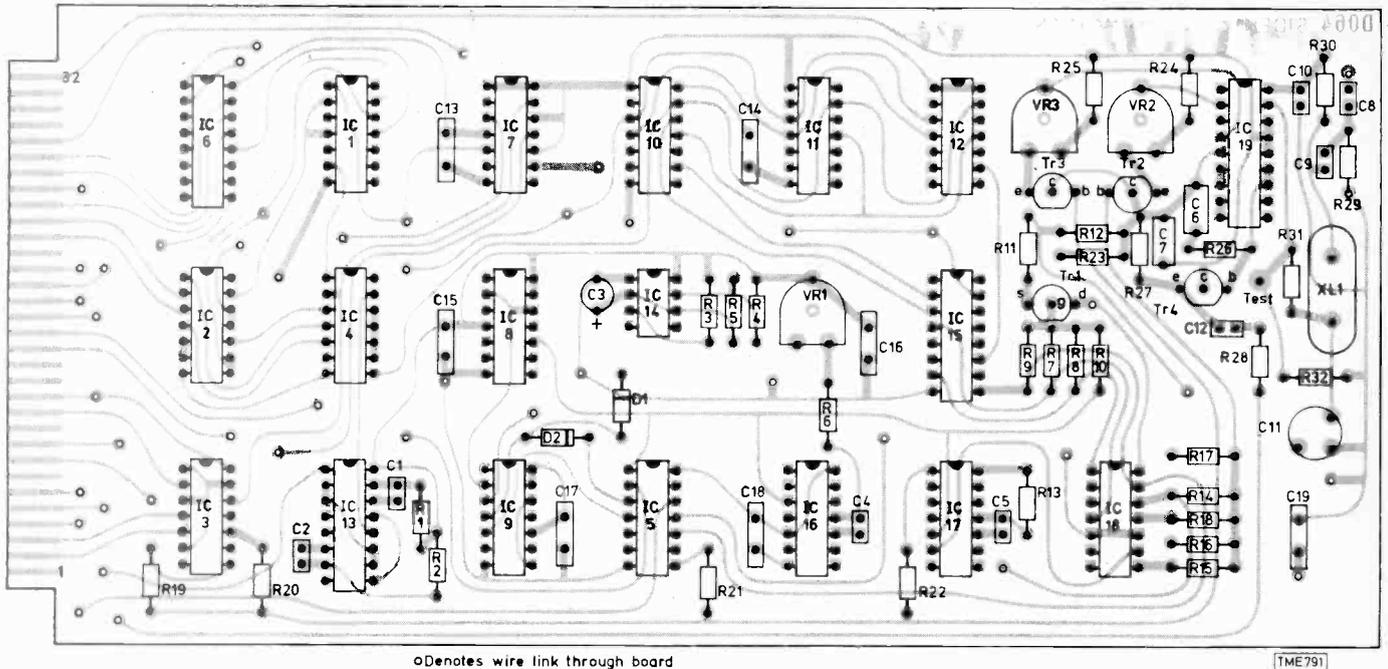


Fig. 7: Component location diagram for the options board.

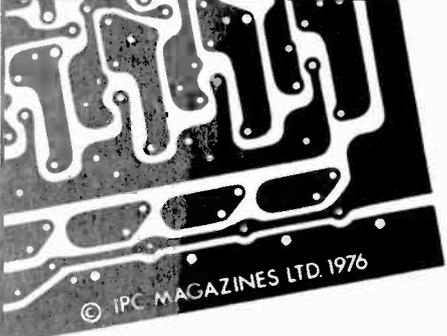

All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.



TELEVISION

READERS PCB SERVICE

<p>Issue</p> <p>November 1976 December 1976</p> <p>March 1977 May 1977 May 1977 June 1977 June 1977 July/Aug 1977 August 1977 September 1977 September 1977 October 1977 Feb/March 1978 April/May 1978 May/June 1978 Aug/Sept 1978 October 1978 January 1979 February 1979 March 1979 July 1979</p> <p>September 1979 August 1979 August 1979 September 1979</p>	<p>Project</p> <p>Ultrasonic Remote Control IC Sound Circuits for the Constructor</p> <p>Teletext Decoder Power Supply Teletext Decoder Input Logic Single-chip SPG Wideband Signal Injector Teletext Decoder Memory Teletext Decoder Display Logic State Checker Teletext Decoder Switch Board Teletext Decoder Mother Board Teletext Decoder IF Board On-Screen Clock CRT Rejuvenator Test-Pattern Generator Diagnostic Pattern Generator Colour Receiver PSU Board Colour Receiver Signals Board Commander-8 Remote Control System Colour Receiver Timebase Board Colour Pattern Generator</p> <p>Teletext Decoder Options Board Teletext Decoder New Mother Board Simple Sync Pulse Generator New Teletext Signal Panel</p>	<p>Ref. no.</p> <p>D007/D008 D009 D017 D022 D011 D030 D031 D012 D013 D038 D021 D027 D041 D045 D046 D048 D051 D052 D053 D054/S D049 D062 D063 D064 D065 D067 11331</p>	<p>Price</p> <p>£3.24 per set £1.44 £1.44 £3.24 £10.53 £3.30 £0.79 £8.51 £8.62 £1.70 £1.43 £4.36 £6.50 £7.03 £2.76 £9.15 £8.62 £3.83 £10.75 £5.43 per set £17.13 £13.50 £9.15 £8.50 £5.00 £4.00 £8.00</p>
---	--	--	--

To:- Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____

ADDRESS _____

Post Code _____

Servicing Pye Solid-State Colour Receivers

The 713, 715, 717, 725, 731, 735, 737 and 741 Chassis

Part 1

Mike Phelan

THIS series of articles will cover all the Pye solid-state colour chassis produced up to, but excluding, those sets using the G11 chassis. First we shall deal with the large-screen models. The 18 and 20in. sets used a chassis with certain similarities but a completely different layout: these (the 713, 715 and 717) will be discussed later.

Chassis Numbering

Now to sort out the confusing mixture of chassis numbers. The original was the 731 chassis, using a 26in. tube and an SN76544 combined line and field oscillator i.c. To make the sets VCR compatible, the i.c. was altered to a TBA920 with the field oscillator redesigned using discrete components: the chassis number became 737. Putting the tuning controls in a drawer separate from the push-buttons changed the number to 735! Later models using an A66-410X quick-heat tube had their chassis designated 741; and a "pruned" version fitted with a 20 or 22in. 90° tube was numbered 725.

Despite this complicated system of numbering, most of the panels are interchangeable; the exceptions of course are the line timebase and convergence panels, which differ for 90° and 110° models; the field timebase panel (which can be changed if three components are altered); the c.r.t. base panel; and finally power supplies coded 4A4 cannot be changed for different types.

Accessibility and Layout

Accessibility is quite good, most of the panels being held in three vertical plastic frames which slide on runners, two on the left of the c.r.t. looking from the back and one on the right. The latter holds the convergence, power supply and field timebase panels; for access, lift the plastic latch at the bottom rear corner, draw the panel to the rear until it clicks, then swing it out and lock it in position with the plastic peg at the top. In this position, the convergence controls are accessible from the front of the set. For greater access push the panel, while it's still at an angle, back into the cabinet to free it from the runners. The top runner can be freed from its guide with a strong pull, allowing the panel to be laid on its back.

The extreme left-hand frame carries the chroma panel (top) and a bottom panel containing the tuner, i.f. module, vision detector and sound stages. This frame can be pulled along its runners after the top and bottom latches have been released. When in the nearest position, the panels swing out to the left. The frame on the left nearest the c.r.t. contains one large board with the line timebase and raster correction circuitry on it, and is attached to the cabinet in the same way as the right hand frame – it's necessary to swing out the chroma/i.f. panel however before removing or turning the line timebase. The plastic moulding on the large i.f. can is to prevent shorts to the line timebase print when

both panels are out, but beware of the i.f. panel shorting against a metal aerial plug (I found this out the hard way!).

Power Supply Circuit

Starting with the power supply, a blown mains fuse will in most cases mean either that the mains rectifier thyristor D888 is short-circuit or that the mains filter capacitor C915 (0.22 μ F) is short-circuit. If C915 has shorted it will usually have blown one of its ends off. It should be replaced by a component rated at 1kV working. Early power supplies used a 16472 thyristor, later ones a 2N4444 or BT106. Beware of devices coded TV106 – an OT112 seems to be about the most reliable replacement.

The thyristor can suffer from leakage as an alternative to going completely short-circuit: this causes the h.t. flutter familiar to most of us (though this symptom can have other causes as well). First try setting up the h.t. Adjust RV916 (h.t. fine) to mid-position, and RV917 (h.t. coarse) fully anti-clockwise. With the meter on the dropper tag marked "185V", adjust RV917 for 195V, then adjust RV879 (overvolts) until the picture *just* starts to pulsate. Finally adjust RV917 for 185V.


Another cause of h.t. flutter is a faulty diac, particularly if of the black plastic D3202Y type. A BR100 is a suitable replacement, but in an emergency reversing the diac sometimes works. Often this device will go open-circuit, sometimes intermittently, but an intermittent diac can usually be persuaded to give up the ghost altogether when sprayed with freezer.

Early panels had a diac/thyristor arrangement for overvoltage protection: this was later altered to a more conventional circuit using a transistor – similar to that in the Philips G8 chassis. As mentioned before, the earlier and later panels are interchangeable – unless the board is a very early one coded 4A4.

A fairly common fault on this set, as in the G8 chassis, is a dry-joint on the mains filter choke L909. Those of us used to the G8 may think that a quick clean-up and re-solder will get the set going again within minutes. But no – the beast will usually be found to be very dead on switching on again. The reason is that the tag on the choke burns quite a hole in the print before the receiver packs up altogether, and the heat produced destroys D884 (7.5V zener) in the overvoltage circuit.

Measuring the voltages on the diac can be revealing in cases where a.c. is reaching the thyristor but nothing is coming out. First however make sure nothing is on the cathode: a very low a.c. reading means that the power supply is working but R978 (3.3 Ω) is open-circuit. Confusing, but quite logical – if the thyristor's cathode is not connected to the rest of the set, it will follow the gate via R885, and the gating pulse must be between gate and cathode.

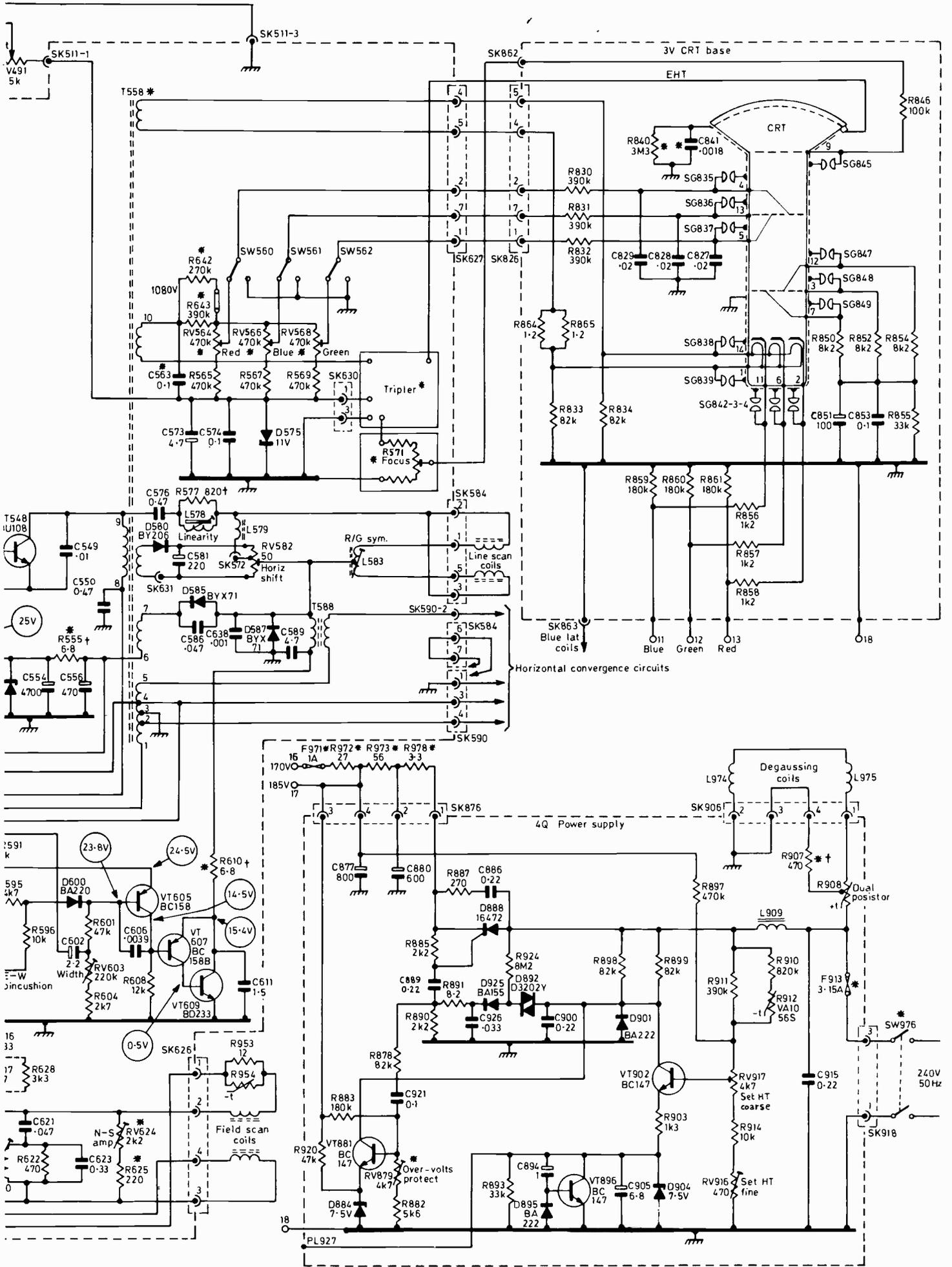Back to the diac: there should be 11.5V positive on one



† component to be replaced only by same type or manufacturers approved alternative. † Fusible

connected from pin 2 of the line output transformer, via an 18kΩ resistor (R632), and is used for a.g.c. gating in the TCA270Q i.c. in the i.f. strip.

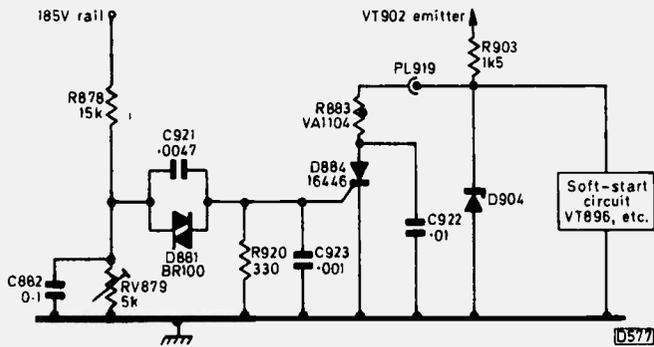


Fig. 2: The over-voltage protection circuit used in early models. On very early versions, PL919 is taken to the cathode of the mains rectifier thyristor: this gives a crowbar action, blowing the mains fuse in the event of excessive h.t. voltage.

side and 8V negative on the other – no positive voltage means either a fault in the overvoltage protection circuit or D901 (BA222) short-circuit; a very low voltage means VT896 (BC147), VT902 (BC147) or D904 (7.5V zener) short-circuit, or possibly C905 defective (can result in a very low h.t. rail if leaky). VT881 and VT896 can be temporarily removed just to check, but remove the h.t. fuse first (situated bottom centre). Lack of negative voltage normally means a defective diac.

Up to now the dropper has behaved itself, apart from the aforementioned R978, which may either be part of the dropper or a separate resistor mounted above. If of the latter type, the correct replacement must be used otherwise mysterious hum bars may be produced. Dry-joints on C880 and C877 (h.t. reservoir/smoothing) can also be the cause of hum bars. As yet we haven't had to replace either of these capacitors, but sooner or later they will begin drying up to cause low h.t.

R911 can change value to cause low h.t. As with other solid-state chassis, it's advisable to check that the h.t. is correctly adjusted whenever one of these sets is serviced.

The Line Timebase

The line timebase is fairly conventional, using a BU108 output transistor. A feature to note is the method of deriving the boost voltage for the tube first anodes. The e.h.t. tripler contains the now usual clipper diode to remove the rings on the input pulse and improve the e.h.t. regulation. If the overwinding is not connected to anything else d.c.-wise, it assumes a potential of about 1kV above chassis. The "bottom" end is decoupled by C563 (0.1μF), and supplies the first anodes. C563 in fact is the bête noire of this chassis. When it goes short-circuit it gives the symptoms of a faulty tripler – disconnect the tripler, and the line timebase starts up. Later sets use an 0.22μF, 1.25kV working capacitor. If the set is left on in this condition, the demise of the tripler, sometimes followed by the BU108 and the line output transformer, can result before the h.t. fuse blows. Where the h.t. fuse F971 has blown, C563 should be the first check therefore. C563 should also be checked whenever the tripler fails.

The 90° and 110° transformers are not interchangeable, the 90° one having more tags. Also, later replacement transformers from the manufacturer have the shift winding incorporated in the primary bobbin instead of being wound externally on to the core: a slight modification is needed on fitting, but full details are supplied with each transformer – a 2.7Ω resistor is required in series with the cathode of D580.

The next most common fault must be failure of C514, the line oscillator timing capacitor (with the TBA920 i.c.). The

result is a dead set, which often springs to life if any voltage measurements are taken round the line driver stage, leaving doubt as to the cause of the fault. If the set manages to stay off, it will be found that the collector of the driver transistor VT541 is at h.t., with no negative voltage at its base. Another prod with the AVO shows that the voltage at pin 2 of the TBA920 is approximately correct – so we jump to the wrong conclusion and replace the BF355. After this disturbance the set may work, but sooner or later will fail again when C514 goes open-circuit and the line oscillator tries to run at about 3MHz. Replace with a polyester – not ceramic – type. Twice we have replaced C514 and the fault recurred a few weeks later due to the driver transistor developing an open-circuit base-emitter junction. The policy therefore is to replace both components at the same time.

C586 in the EW modulator circuit can be responsible for lack of width. Again a polyester type must be used. The focus unit can go up in smoke, but that's an obvious one.

The c.r.t. first anode preset controls used in these sets are prone to alteration in value, giving changes in grey scale. The series resistors R565, R567 and R569 (470kΩ) are also suspect for this. What seems to happen is that the presets fall in value while the series resistors go high, until a situation is reached where it is impossible to turn the presets down sufficiently. Sometimes it's necessary to replace R642 (270kΩ) and R643 (390kΩ) which feed the first anode potentiometers from the boost rail. They tend to go high resistance, causing a dark picture, though they can also fall in value, giving excessive brightness. The grey-scale setting up procedure will be given later, as it's necessary to adjust the d.c. levels on the decoder first.

The rest of the line timebase has proved quite reliable. One fault we've encountered once or twice on the 110° chassis has been intermittent droop at the top of the raster, caused by a bad spot on the track of RV624 (NS amplitude). The early 110° panel with the SN76544 has the latter and its associated components mounted on a small subpanel.

The Field Timebase

The field timebase uses a single-ended class A output stage with choke loading, similar to the Thorn 3500 chassis. The field oscillator, except on the early 731 chassis which uses part of the SN76544 for the purpose, employs a complementary pair of transistors on the line timebase panel. These are connected as a silicon controlled switch which gives an output consisting of negative-going pulses that forward bias D650 to produce the flyback. This discharges the field charging capacitor C652, which during the forward scan charges from the unstabilised 28V rail via R653, R655 and R656. VT660 amplifies the waveform produced by C652, its gain being variable for control of height by varying the emitter resistor's value. VT660's collector waveform is integrated by C663 and R665, R664, R666 and the linearity control RV659. The remainder of the timebase consists of three d.c.-coupled transistors, VT678, VT684 and VT688, the latter being mounted on a large heatsink. The choke load T687 is actually a transformer, but the secondary supplies a convergence waveform only.

This panel seems to be reasonably reliable, most cases of intermittent field collapse being due to faulty plugs and sockets – either SK704 near the output choke, or one of the plugs at the top of the line timebase. Attention should be directed to these when the field timebase has been proved working – either by a measurable a.c. voltage on the output transistor's collector or an audible buzz from T687.

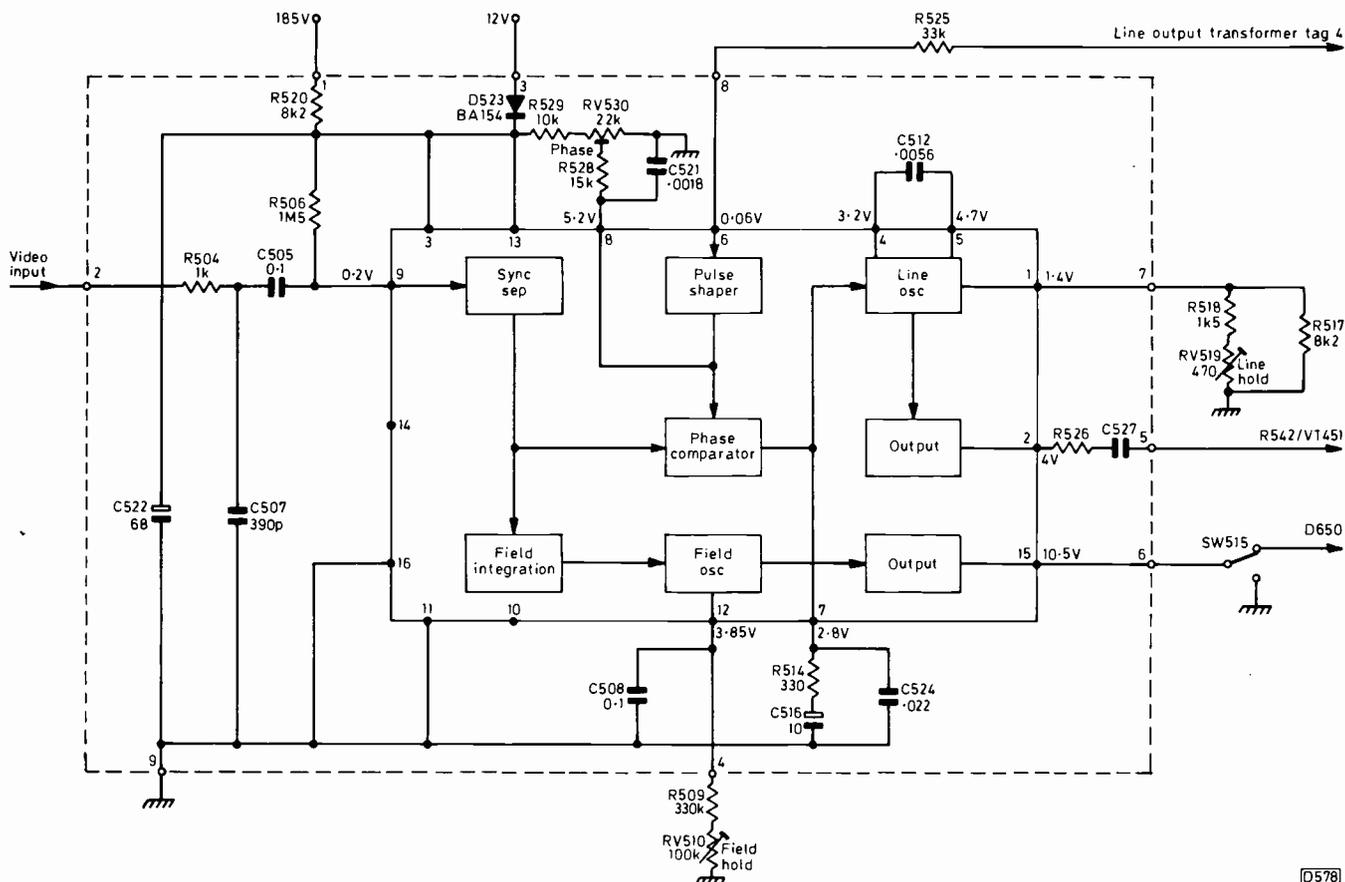


Fig. 3: The 731 chassis uses an SN76544N07 i.c. as the sync separator and line and field oscillator. It's mounted, along with certain associated components, on a subpanel, as shown above. R526 and C527 values as in Fig. 1.

A 3in. high scan with no video has nothing to do with the timebases but is caused by R555 (25V supply filter resistor) springing open. Why did it spring open? H.T. too high, probably because the thyristor in the power supply was leaky.

Both VT678 and VT684 (BC158 and BC338 respectively) can be responsible for field collapse, sometimes intermittent. The output transistor VT688 can be replaced by a 2N3055. It doesn't fail often, but can go leaky causing a progressive reduction in height as it warms up. Always check the setting of RV675 (bias) after any replacements in the field timebase. Start with the control fully clockwise, and turn anticlockwise until the slight compression about a third of the way down the raster disappears and VT688's emitter voltage is no more than 0.5V.

The various electrolytics in the field timebase cause different fault symptoms. Up to now most failures have been due to leakage, but no doubt as these sets age more of the electrolytics will have to be replaced because they've dried up. By far the most common electrolytic to give trouble is C672, in which slight leakage gives reduction of height, but still with a linear scan. C668 gives lack of height, with a band of compression at the centre of scan. We have had to replace a dried up C693 (1,000 μ F) once or twice, as it was giving severe lack of height with cramping at centre and bottom of the scan. Leakage in C941 causes weak field sync, which can also be caused by C194 (tuner a.g.c. smoothing) on the signals panel.

The 90° and 110° panels are interchangeable, provided three components are changed in value as follows: R661 is 1k Ω for 90°, 470 Ω for 110°; R703 is 1.5k Ω for 90°, 10k Ω for 110°; C663 is 0.68 μ F for 90°, 0.47 μ F for 110°. Failure to carry out these changes will result in excessive

height if a panel from a 110° set is fitted to a 90° chassis. The converse applies if the field timebase from a 725 chassis is fitted to a 110° set.

Convergence Circuitry

The convergence circuitry in both the 90° and 110° chassis has been quite free of trouble. This is in no small measure due to the good design, avoiding controls with low values and high dissipation (which inevitably become noisy and intermittent). The field convergence circuit is driven from the aforementioned secondary winding on the output transformer T687, and is of the active variety, using four transistors in a waveform amplifying and shaping circuit. These occasionally go faulty, usually with open-circuit emitter-base junctions – maybe intermittently. The result depends on which transistor is faulty, but you'll usually find gross convergence errors, the static convergence being so far out that purity is also affected. As a quick check, pull the plugs off the convergence yoke and switch on: though there will obviously be no dynamic convergence, the static convergence should be reasonable.

Other convergence faults have been few and far between, and mostly of the type that respond to tapping – for example an intermittent contact on one of the plugs, or a coil leadout wire dry-jointed.

When adjusting the convergence on the 110° sets, don't forget that there are two three-position switches which can be adjusted in conjunction with the R/G tilt and blue tilt controls. The centre positions give nil correction. As well as this, the blue lateral coil has four tappings on to which the flying lead can be plugged.

CONTINUED NEXT MONTH

Long-distance Television

Roger Bunney

THE Sporadic E season continued into June, with signals at fair levels, and many enthusiasts have remarked on the quite dramatic signals received from Scandinavia — Norway (NRK) in particular. Since NRK includes the transmitter identification on the PM5544 test pattern, establishing the exact transmitter received when the signal is clear enough is relatively easy. With conditions as they have been however, at least two NRK patterns may be received simultaneously on each channel, making identification difficult. Iceland has also been received at good strength on chs. E3 and E4: following recent advice, one DXer tried RUV reception very late — and succeeded in noting system M signals from the NW. These must obviously have originated from somewhere in the Americas!

My own log for the month has been pretty full, though there was no really dramatic reception. The following loggings were all via SpE.

- 2/6/79 TSS (USSR) chs. R1, 2; NRK E2, 3 and 4 (two on each channel); SR (Sweden) E2, 4. This developed into an all-day opening that jammed Band I.
- 3/6/79 NRK E3, 4; SR E3; DR (Denmark) E3, 4; also unidentified signals.
- 4/6/79 RAI (Italy) IA (twice), IB; TVP (Poland) R1; CST (Czechoslovakia) R1; MTV (Hungary) R1; TSS R1, 2.
- 5/6/79 DFF (East Germany) E4.
- 6/6/79 SR E2, 3; RAI IA; plus many unidentified R1, 2 signals.
- 8/6/79 TSS R1, 2.
- 10/6/79 TSS R1.
- 16/6/79 NRK E2, 3; unidentified R1, 2 signals.
- 17/6/79 TSS R1 twice; RAI IA.
- 19/6/79 TSS R1, 2; RAI IA.
- 21/6/79 RAI IA; TSS R1, 2; unidentified R1, 2, 3 signals; plus a mystery signal at 0800 consisting of a pulse and bar pattern followed by a non-identified FUBK test card, weak from the SE, between the E2, R1 carriers.
- 22/6/79 SR E2, 3, 4; CST R1, 2; TSS R2; unidentified signals.
- 25/6/79 TVP R1, 2; unidentified R1, 2 signals.
- 26/6/79 RAI IB; RTP (Portugal) E2.

One point is clear: signals from RTVE (Spain) have been lacking this season. There was an improvement in tropospheric reception during the 18-20th — even W. Germany at u.h.f. was noted!

Hugh Cocks (E. Sussex) reports reception of "JTV AMMAN" (identification on PM5544 test pattern) on Sunday the 10th at 1620. There have been several reports that the RAI PM5544 pattern has been seen with the identification "RAY 1" instead of the usual "RAI 1". Mike Allmark (Leeds) received the Tele Oristano (Sardinia) ch. IB electronic test pattern on the 1st — it resembles the W. German circular type pattern of the late 1960s, with the identification "Teleor Can B UHF". Kevin Jackson (Leeds)

and Hugh Cocks report reception of another ch. E3 Italian "free" station early in the period, with the "NCT" caption. Gwelo, Rhodesia ch. E2 was received at good strength on May 29th. Geoff Perrin (Dubai) also reports good SpE conditions — he received Pakistan ch. E4 using the PM5544 pattern with the identification "Pakistan" at the top and "Television" at the bottom.

During the early hours of June 12th, Cyril Willis (Cambridge) attempted to receive RUV (Iceland). Starting at 0115, he received for twenty minutes rolling pictures that were out of both field and line sync. This suggests a system M signal. Cyril reports that the signals were "in the middle of the tuner, at around ch. E3", i.e. ch. A2. No sound was present unfortunately, so the origin of the signals will never be known. I feel that they are most likely to have come from the eastern seaboard, since they were picked up from a westerly direction.

A correction to the July column incidentally. On page 475 the Lopik channel should have been given as E4, not E3.

News Items


Luxembourg: CLT is using a 1,000kW transmitter at Dudelange to facilitate reception in Belgium and W. Germany. It's the first time that the same programmes have been transmitted on different standards from co-sited transmitters.

Albania: A new transmitter in Tirana is operating on ch. E10, providing a superior signal to the ch. C outlet.

Eire: New EBU listings: Cork ch. IG 100/50kW vertical; Sligo ch. IG 100/10kW horizontal; Gort ch. IH 100/50kW vertical; Kilkenny ch. IJ 100/50kW vertical — all RTE-2. Three Rocks RTE-1 ch. 29, 25kW horizontal. The Dublin ch. B3 and B7 and Sligo ch. B11 transmitters have now closed down.

The 30-50MHz Band

With the exception of ch. B1 and TV from ch. E2 upwards, the band 30-50MHz is empty in the UK — apart from i.f. radiation of course. In other parts this spectrum is used for medium-haul ground-wave communications, and of course for forward-scatter communications in Eastern Europe. When F2 propagation is increasing, this band can be used to advantage to see how high the maximum usable frequency has reached. Signals you may receive can come from Indian- or African mobile radio transmitters, Russian communications, or US Highway Patrol and paging

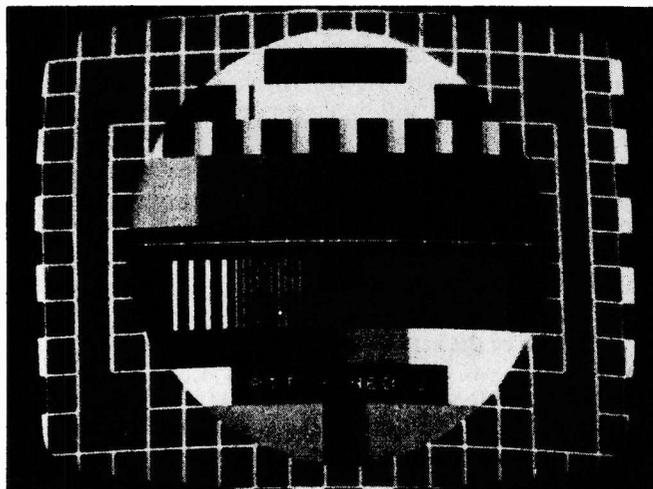

The NOS (Holland) PM5544 test pattern, received by Gareth Price (Lowestoft) on ch. 27.

stations. Short-wave radio harmonics abound of course.

Covering this spectrum is a problem unfortunately, since apart from specialised communications receivers (the Eddystone 770R etc.) there's little equipment available. I've approached the problem in various ways over the years, and do at present have a means of covering this spectrum accurately.

During the last sunspot cycle I modified the coils of a government surplus RF26 unit, feeding its i.f. output into a short-wave receiver. The next approach was to use a home-built tunable converter, covering 25-55MHz, using EF80/ECF80/EF80 valves and Denco coils. The Denco range of v.h.f. coils, reaching to about 80MHz, is still available and could probably be used with f.e.t. circuitry. Subsequently I obtained through *Practical Wireless's* VHF Bands columnist Ron Ham an historical (circa 1939) Hallicrafters S21 receiver covering 25-66MHz. Later types, including the S36, cover 26-150MHz and are available at low cost. Unfortunately, impressive though these receivers look they use elderly valves which by today's standards have low gain and poor noise performance. For the wealthy in our midst, Eddystone manufacture both v.h.f. and u.h.f. radio units (990 series).

Perhaps the easiest and cheapest way of covering the spectrum, assuming that you have a short-wave receiver covering 10-7MHz, is to use the tuner head available from Ambit International (Brentwood, Essex). Their 5402 varicap tuned head unit is available covering 30-50MHz and features a BF256 f.e.t. input amplifier driving a TFK1062 v.h.f. i.c. with an output at 10-7MHz. There's a pin diode a.g.c. system, but the only voltage requirements are a 12V supply and the tuning voltage. The cost (early June) is £14.75 plus VAT, and delivery approximately four weeks.

Coverage of 30-50MHz can also be obtained by using imported transistor radio receivers intended for the American market and for police monitoring. They are imported by Allan Electronics, 21 Ocean View, Whitley Bay, Tyne and Wear, NE26 1AL, and several models are available. I invested in the cheapest one, which is a Radioshak model with the Realistic emblem, made in Taiwan for export to Tandy in Canada. The "Patrolman 50" I'm using covers 30-50MHz, 108-174MHz and 450-512MHz with f.m. demodulation and squelch provision, and the broadcast bands 88-108MHz and MW. The electronics, including the miniature u.h.f. tuner, are mounted on a single board. Switching from band to band connects the aerial to the appropriate tuner, separate tuners being provided for each band with a common ganged tuning capacitor. The gain is good and the overall quality better than expected. Being intended for the American market, the mains transformer is for 120V a.c. input, though the importers say that 240V adaptors are available.

The set I ordered came via a Canadian air cargo flight and was held for a considerable time by the customs at Heathrow. Apparently there are now ample stocks however. Unfortunately, recent price and VAT increases have made this a less attractive proposition than last winter, but it does provide the quickest way of monitoring the required band with minimum effort. In its original form (120V a.c. and 6V battery operation) the Patrolman 50 costs £80.44, or £85 with 240V in-line adaptor, inclusive of postage and VAT.

Any other ideas from readers on covering the 30-50MHz band would be welcome.


F2 Propagation

Ian Roberts (South Africa) reports that an s.s.b. two-way

**CONTINENTAL AERIAL SPECIALISTS, RETAIL AND TRADE.
GOLDEN ANODISED, WEATHER PROTECTED, SUPERB ARRAYS.
GUARANTEED BY US FOR FIVE YEARS.
GOLDEN QUALITY IN A PLASTIC AGE.
ALL PARTS (EXCEPT COAX) EXCHANGEABLE FOR 7 DAYS.
10% DISCOUNT OFF MOST AERIALS
SPECIAL PROMOTION OFFER
15% + DISCOUNT ON PLEMI RANGE**

For new glossy, highly graphic lists & brochures send 40p & stamp only. 40p credit on 1st order.

AGENTS FOR
FUBA & PLEMI

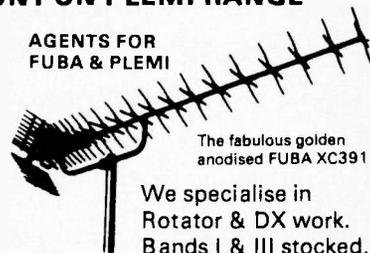

Stockists of the finest aerials available in Britain:

STOLLE FM aerials (W.Ger.)
FUBA TV & FM aerials (W.Ger.)
PLEMI TV aerials (Hol.)
UKW FM aerials (E.Ger.)
ANTIFERRENCE TV & FM aerials (U.K.)

The fabulous golden anodised FUBA XC391

We specialise in
Rotator & DX work.
Bands I & III stocked.

ASTRA (GOLDEN D.I.Y.) AERIALS

A friendly family firm. Our 25th. Jubilee Year.

D.I.Y. AERIAL SPECIALISTS FOR ALL DOMESTIC TV & FM RECEPTION

Weather exposed part of U.K.? Scotland, Wales, West Country etc. Gales, salt air corrosion problems? Want to install your aerial and forget it?

The continental aerial range from Germany and Holland having proved so fantastically successful, we are in future recommending continental aerials (especially Fuba) as our first choice for customers. In short we offer quality in a plastic age.

Anodised against corrosion, guaranteed for five years, robust, high gain, easy to assemble, eye-catching superb aerials, what else, in truth could we recommend?

Over 3,000 aerials stocks: All Bands: Masts: Lashings: Wall Brackets:

Rotators: Televertas: Diplexers and Triplexers: You can now mix Band 4 and Band 5, or lower Band 5 with higher Band 5, or mix FM with either,

1-5db loss approx.: Padded outlets: Directional splitters: Coax, white or brown: 300 ohm cable.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Gloster Pub & Garage

Tel: 01-684 4300

Open 9.00-5.30 MON-SAT.

01-684 5262

Closed 12.30-1.30 But Open ALL day Sat.

24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY

LOOK! Phone: LUTON
BEDS. 38716

**OPPORTUNITIES
TRADE SALES
ALL SETS GUARANTEED
COMPLETE**

**HUNDREDS OF SETS
IN STOCK EACH WEEK**

Pye 20T, Philips G8;
Ferguson 3-3k5, etc.

All from

£35.00 £50.00

Square Screen, Mono's from

£5.00

Sets for spares from

£2.00


All include VAT

OPPORTUNITIES

9A, Chapel Street, Luton, Beds.

LUTON 38716

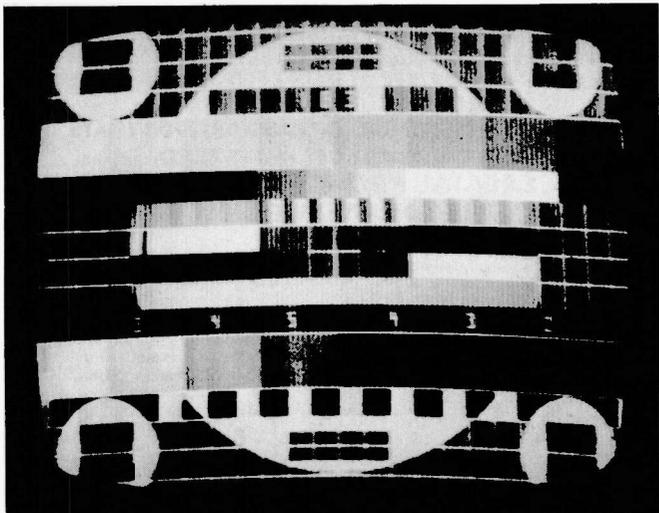9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.



The Russian electronic test pattern received on ch. R2 via SpE by Gareth Price.

contact has taken place at 144MHz between Italy and Luderitz (S.W. Africa), setting a new world record. Texas TV DXer Pat Dyers received ch. A2 (at up to 58MHz) from Venezuela on April 17th, the first time in this cycle. Jerry Pulice (Staten Island, USA) reports that during good F2 conditions in February the UK ch. B2 could be received at high levels, though with no sign of ch. B1 at 45MHz. On other days during February ch. B1 was generally very, very strong!

From our Correspondents . . .

The many letters I've received this month indicate that SpE reception has been experienced throughout the country. Mike Gaskin (Croydon) has been using a JVC 3050 portable TV set with excellent results, despite being only two miles from Crystal Palace. His loggings include Denmark chs. E3 and E4 via a very short skip path, and a 200W 88MHz RUV (Iceland) f.m. station.

Frank Jimenez (Clapham) has logged SR, NRK and RUV with only a small aerial sticking out of the window. He too has received short-skip signals from Denmark. John Lees (Cheltenham) has noted the RAI test card with "RAY 1" identification, and two West German transmitters at Ochsenkopf and Kreuzberg, using an indoor aerial. Gareth Price (Lowestoft) has sent us an excellent photograph of the Russian electronic test pattern, received on ch. R2.

Long-distance TV for the Beginner

The Long-distance Television column and its predecessor DX-TV have been running monthly in this magazine since the early 1960s. There have been many changes over the years: colour is now often a feature of long-distance (DX) reception; there has been a vast increase in the number of transmitters (all seemingly using that plague – for identification purposes – the PM5544 test pattern); but perhaps the change that has become the greatest problem is the increase in the number of programme hours, with the corresponding reduction in test card transmission time, making station identification increasingly difficult. The technology has also changed: u.h.f. DX-TV reception is now firmly established, while some enthusiasts have already sampled the delights of satellite TV. And with advances in tuner and aerial technology, it's possible to achieve reception at very low signal levels. To cater for newcomers, it's necessary from time to time to go over the basic techniques of DX-TV reception, so here we go again. My



An example of reception during a period of enhanced tropospheric propagation – photo by Gareth Price.

apologies to those who already know it all: I'm sure they will understand.

Perhaps most viewer's first introduction to DX-TV reception comes when they find on their screen a signal that hasn't come from one of the local transmitters. This may happen while tuning between the usual stations, and may lead to an exploration over the whole u.h.f. TV band. This will probably reveal further unexpected signals.

The quality of distant TV signals varies from day to day, and the signals may last for a few hours or less. Warm, settled weather is best. There may in some locations be distant signals of sorts present every day, stronger on some days than on others. U.H.F. signals are particularly dependent on weather conditions. Remember the "old 405-line days" however, when the BBC signal would sometimes be upset during the summer months by weird patterning and Spanish voices, leading to the familiar "foreign interference" announcements. That's another form of DX-TV reception, but at distances of 500 miles or more, actual signal strength being very strong and receivable even on an indoor aerial.

The potential DX-TV enthusiast will obviously wish to minimise his initial expenditure until he can assess the possibilities that expensive aerials and ancillary equipment might bring at his location. Fortunately it's possible to use a standard u.h.f. TV receiver (preferably one with full dial tuning rather than push-buttons for channel selection) for both v.h.f. and u.h.f. DX reception – more on that next month.

Considering first long-distance u.h.f. reception, we've already pointed out that the number of transmitters that can be received and the quality of the signals is related to the weather. This is determined by the conditions in the troposphere – the region from the Earth's surface upwards to some 25,000ft. (8,000m.). For obvious reasons, this type of reception is called tropospheric reception. Pointers to the likelihood of such reception are the slow-moving high-pressure systems that give us our sunny, cloudless summer days, with a rapid fall in temperature at night due to the clear skies. This results in the signals improving during the evening, falling off next morning as the Sun heats the Earth's atmosphere again. Fog is another effect that's often present during such conditions, and during the autumn you'll often find that remarkable tropospheric reception is possible during foggy conditions. Sometimes, when a moving weather system produces abrupt pressure changes along the isobars, a form of signal ducting occurs – *along*

the line of the isobar. So it pays to keep an eye on the weather maps.

You don't need a vast or complicated installation to start experimenting with DX u.h.f. reception. Obviously an aerial is required, and a basic rule of aerials is the larger the system the higher the gain, i.e. a big aerial captures more signal. Fortunately however the advent of low-noise aerial preamplifiers has made it possible to achieve reasonable DX reception using a compact array.

The bandwidth of u.h.f. aerials (and preamplifiers) varies. Most aerials sold for normal domestic reception of local transmissions are grouped, i.e. designed to receive particular groups of channels – group A, channels 21-34; group B channels 39-53; group C/D channels 48-68. There are also wideband u.h.f. aerials – for channels 39-68 (group E); channels 21-48 (usually suffixed K); and the /W type which covers the entire u.h.f. bandwidth (channels 21-68). To minimise outlay, a single /W aerial is a sensible purchase. Since gain falls with increase in bandwidth however, improved results will be obtained by employing a group A and group E aerial or by employing three aerials (group A, B and C/D) to cover the bandwidth. For a given type of aerial, the greater the number of elements the higher the gain and the more directional the response (assuming that the system is correctly designed of course).

Gain is specified in decibels (dBs), the basic half-wave dipole being assumed to have zero gain. Add a reflector rod and perhaps a couple of director rods and the aerial gain is increased, at the same time making the system more directional, i.e. restricting the forward pickup angle (helpful in reducing interference from unwanted signals). An aerial with a 3dB gain has twice the signal output of a single half-wave dipole, i.e. there's a power gain. A four times increase is 6dB, an eight times increase 9dB, a sixteen times increase 12dB – in fact a 3dB power gain every time the output doubles. If you want to go into aerial theory in greater depth, it would be worth consulting Gordon J. King's "Practical Aerial Manual", 2nd edition, published by Newnes-Butterworths. If I may include a commercial break at this point, you'll also find much information on aerials in my own book "Long-Distance Television (DX-TV) for the Enthusiast", published by Babani Publishing at £1.45. There's far more information there than I can include here.

So you buy your aerial, and we'll assume you don't live within five miles or so of a high-power transmitter (if you do, you've got problems!). The next thing is where to point it, since there are signals in all directions. It's obviously best to be able to rotate the aerial. Aerial rotators are available, but again this involves expense. If you have access to a wall and ground however you can erect the aerial on a scaffold pole mounted on a large ball bearing. Support the pole with wall brackets and thrust/ballrace/bearings – so long as the friction is low and the aerial clears the roof, it can be turned by hand (for further details see the article by Keith Hamer and Gary Smith in the March 1978 issue of *Television*).

An aerial preamplifier is helpful – essential in some locations, but occasionally a problem (less than five miles from a local transmitter). It can be used indoors where the feeder run is very short (say less than 30ft.) and very low-loss, high-quality coaxial cable is used. If a long length of cable is necessary however the preamplifier must be mounted at the aerial end. Select a medium- to high-gain preamplifier, with low noise and good cross-modulation performance, i.e. it can withstand a high-level local signal without overloading (producing interference on other channels). Wideband preamplifiers can be obtained with noise figures of less than 3dB and gains of 22dB minimum (voltage gain, not power gain) over the entire bandwidth.

It's worth taking a look at the Labgear and Wolsey ranges.

Turning to aerials again, if minimum outlay is essential I'd suggest giving thought to a stacked bowtie system, such as the Wolsey Colour King and other variants, or a multiple Yagi aerial such as the /W versions in the Antiference XG range. Fuba also have a range of wideband aerials with a high reputation.

If interference from a local channel is a problem, a simple filter can be made to attenuate such channel(s). If preamplifier overloading is taking place however the filtering will have to be done prior to the preamplifier. Hugh Cocks covered the whole subject of filtering in the November 1977 issue of *Television*.

Tropospheric signal propagation can result in u.h.f. reception over many hundreds of miles, at high signal levels. In the eastern coastal areas of the UK, signals have been received from as far away as Poland, the USSR, Sweden, Czechoslovakia, Austria and Switzerland. On a more local note, in most areas a good aerial installation should provide at least one additional IBA channel.

Tuners for DX-TV

Hugh Cocks

For some time the ELC2000 tuner has been much sought after by DXers. This tuner covers the v.h.f. and u.h.f. bands, with the advantage of an extended low-band coverage (Bands I and II) up to approximately 90MHz, enabling the OIRT and Italian/Albanian Band II channels to be received. The disadvantage of the tuner is its price, also its availability, though the latter has improved recently.

I recently came across a cheaper solution which also has a marginally improved frequency coverage – the ELC2060 tuner. This is physically identical to the ELC2000, the difference in coverage being that the low band extends to over 100MHz, enabling channel R5 to be received (not possible with the ELC2000). The ELC2060 is intended for use in sets destined for the Australian market, which accounts for the extended frequency range.

A minor advantage of this tuner is that on Band III it's aligned down to 138MHz, the Australian channel 5A. Coverage in practice extends well below this, down to about 110MHz, making possible reception of a multitude of non-TV signals. The ELC2000 also has this band coverage, but the tuned circuits are aligned only as far as the bottom of the European Band III (approximately 175MHz).

The ELC2060's u.h.f. coverage is good – from below channel 21 to well above channel 68.

The tuner is available from Sendz Components, 2 Woodrange Close, Thorpe Bay, Essex. The price at the time of writing is £4.50, including VAT and postage.

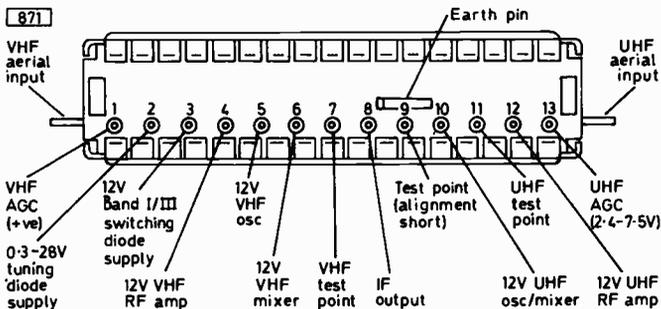


Fig. 1: ELC2000/ELC2060 u.h.f./v.h.f. varicap tuner pin connections. The output from the u.h.f. section of the tuner is coupled to the v.h.f. mixer.

TV Troubles

Robin D. Smith

Rank A823 Chassis

A six year old set fitted with the Rank A823 chassis was in need of a general overhaul. It came in initially because the customer complained of a "ticking" noise which we never heard. We decided to fit a new tube and while the chassis was out had a good look around. The h.t. reservoir/smoothing capacitors 8C9/10 had leaked badly over the chassis, so had to be replaced, but we doubted whether this could have had anything to do with the "ticking". Close inspection in the e.h.t. compartment then revealed that the focus stick 6VDR1 had crumbled badly, so we assumed that this was the cause of the complaint.

With the new tube fitted and the e.h.t. set up correctly there was a reasonable picture but not one of the quality that should have been present with a new tube in the set. Attention was turned to the two-chip decoder therefore, and the U reference signal at 3TP7 adjusted for 600mV by means of the preset colour control 2RV6 (see my notes in the July 1978 issue, page 465). The general colour still appeared to be desaturated however. A new decoder panel produced the results we were after, so we realigned the original following the instructions in the manual. We found that by setting up the matrix amplitude control 3RV3, the V reference phase coil 3L5, the U reference phase coil 3L10 and the matrix phase coil 3L7 our troubles were completely cured.

We've since had several of these decoders in with similar alignment errors.

The customer himself had had a go on one of the later A823B versions of this chassis. Finding the l.t. voltages to the decoder and i.f. unit low, he'd decided to check the smoothing electrolytics 8C3/4 in the power supply. He came to the conclusion that they were both leaky, but as he didn't have a replacement he decided to refit the panel while obtaining a new can. He forgot to refit the screws securing the panel to the chassis however, and on switching the set on there was a loud bang. When he'd sorted that out, he discovered he'd got no picture. This is where we came on the scene.

The l.t. was low but e.h.t. was present. We then advanced the c.r.t.'s first anode controls to maximum, obtaining a negative picture. It's my experience that this is generally due to the SL901B i.c. on the decoder panel, so I came to the conclusion that he'd destroyed it when the power supply earthing had been incorrect. I decided to leave this however until the l.t. supply was correct. It was about 3V down, with hum at minimum volume and a hum bar. 8C3/4 were checked but seemed to be all right, so the other two electrolytics 8C1/2 came under suspicion. Muck had started to leak out, but a replacement block still didn't cure any of the faults.

So if the power supply panel and 8C1/2 weren't the cause of the trouble, what was? I remembered a similar fault that took me an age to find many years ago. There's a tagstrip near 8C1/2/9/10, secured to chassis by two screws which provide the necessary earth connections for the components

mounted on the strip. On examination, one of these screws was found to be very loose. It was tightened, with a little difficulty, the chassis assembled and the set switched on. L.T. now correct, no zero volume hum, no hum bar. Replace the SL901B, reset the chroma reference signal level, generally converge and the results were excellent.

Intermittent Signals

The trouble on an ITT colour set fitted with the CVC9 chassis was intermittent loss of sound and picture – the sound and vision would cut out, leaving just a snowy raster. This suggested a fault in the i.f. strip, not uncommon on these sets. We noticed however that the picture geometry was not quite correct when the fault appeared, and felt that maybe the fault was in the line output stage. Now the small panel on the line output transformer is prone to dry-joints, so instinct told us to look there first. Luckily we found the fault quickly – at the pulse winding earth pin 3 – and resoldering cleared the trouble. Why did this remove the signals? Well the 75V pulse from pin 4 of this winding is used to gate the a.g.c. circuit. With no pulse present, there's no a.g.c. action and the first two i.f. transistors are driven into saturation, removing the signals.

Signal Cramping

A customer brought in a Bush monochrome set (TV161 series) with the fault weak field lock. He'd been having a go himself, having fitted a regunned c.r.t. and checked the field timebase thoroughly. On switching on I noticed that the picture was not as good as it should have been with a replacement tube, indicating a fault in the video circuitry. The voltages around the PFL200 video output/sync valve were all correct, so I moved back to the video phase-splitter transistor 2VT4. The collector was at the l.t. rail voltage, while both the base and emitter read 0.7V. Clearly the transistor was short-circuit base-to-emitter, and a replacement gave a sharp picture with good field lock. From experience, I've found that tube flashover is usually the cause of the failure of this transistor – remember that a new tube had been fitted.

2VT4 acts as an emitter-follower on 625-lines incidentally, with no gain but a high input and low output impedance. The short-circuit would load the detector circuit therefore, clipping the sync and video information.

Terrible Striations

The same customer, a bit of a TV cowboy, subsequently brought in a Philips dual-standard monochrome set (210 chassis) with the worst vertical striations I'd ever seen – alternate black and white bars, about 2in. wide, right across the screen. This time he'd fitted a new line output transformer – and after some time spent checking the connections, we found he'd got them wrong. The moral here is always to make a drawing before removing any part which has multiple connections, in particular noting the destinations of any wires with the same colour coding.

Line Drive Trouble

Back in February I described an awkward fault on a Decca Bradford chassis – the picture getting darker after the set had been on for a while. The trouble then was due to the feedback capacitor (C427) in the line oscillator stage being of the wrong value, as a result of which the line drive

waveform was incorrect. The set was back with us recently with similar trouble – low amplitude line drive, as a result of which the line output valve was overheating, eventually blowing the 500mA h.t. fuse. Checking the voltages in the line oscillator circuit didn't reveal any major errors, but then meters aren't always that accurate when it comes to oscillator stages. This time the fault was traced to the pentode's anode load resistor R444, which had changed value from 33k Ω to something more like 3.3k Ω .

Yet More Cowboys

The 'phone rang one morning recently. "Have you a 13A to 15A fuse for a colour TV set?" "There's no such thing" we replied. "Well the one fitted was 13A, and a 13A mains fuse blows." So we had the set in and duly noted a 13A fuse in the mains fuse holder. It turned out to be a Bush set, fitted with the A823A chassis. Checks revealed that the thyristor rectifier was short-circuit, the series thermistor shattered, and the associated print blown apart. After making the necessary repairs, fitting the correct fuses (none of them correct) and setting up we awaited the return of this other cowboy. When he came in we asked him what made him think the fuse was rated at 13A? "Well the old one was marked T3-15A" he said, "and I took this to mean 13-15A."

Another A823A chassis had received the attentions of the son of the house. He'd started a job in electronics and, after four months, thought he could repair colour television sets. He'd apparently found the l.t. fuse blown, due he discovered to a short-circuit l.t. rectifier, but on replacing these still had no picture. We first checked the h.t., which was found to be high at 240V. This indicated the reason for the absence of e.h.t. – the over-voltage protection circuit had tripped, stopping the line oscillator. So we turned the set e.h.t./h.t. control 8RV1 to minimum, then advanced it to read 200V at the h.t. fuse 8F3. Still no picture, because the tube heaters were not alight, but a healthy oscillation could be heard and the hairs on the back of a hand placed close to the tube face confirmed the presence of e.h.t. The absence of the heater supply was simply a plug-and-socket fault, soon put right.

It's very easy to move 8RV1 accidentally when working on the power supply panel, which was presumably why the h.t. was high and the over-voltage trip had operated. We always turn it to minimum before switching on after carrying out any repairs in this area.

Anyway, we now had a picture – but it was negative, with flyback lines. From experience we concluded that the SL901B demodulator/matrixing i.c. on the decoder panel was faulty, and a replacement produced a normal picture.

We gave the budding apprentice a short talk, and I expect he got a thick ear when his father received our bill for £17. Shame!

A Pye Hybrid Colour Set

We were caught again the other day by a stock fault on the Pye hybrid colour chassis – lines across the top of the picture due to a defective pincushion correction potentiometer, RV41 – though the fault had taken eight years to put in an appearance. The cause of the trouble was a dead spot on the wirewound track – the fault disappeared when the preset was moved. Cleaning and refitting the control cleared the problem. Another fault on the set was that the green first anode control couldn't be adjusted, due to its series 1.5M Ω resistor R465 being open-circuit.

While setting the receiver up, R389 (3.3k Ω) on the CDA panel started to glow like a bulb. This resistor supplies the

screen grids of the PCL84 colour-difference output valves, also the tuning voltage for the varicap tuner. It's decoupled by a 4 μ F electrolytic, which was our first suspect, but the trouble turned out to be due to a screen grid-cathode short in one of the PCL84 valves.


On making some further adjustments we had the set working very well for its age.

20AX Tube Fault

The complaint on a set fitted with the ITT CVC32 chassis was lack of brightness. The set was only four weeks old, so we thought that adjusting a preset was probably all that would be required. On inspecting the test card however we found that the focus and convergence were very poor at the edges – in fact the picture was poor generally. It turned out to be a faulty tube – our first defective 20AX type. Very easy to change and set up on this chassis.

All Part of the Service . . .

The customer complained that the sound on his GEC C2110 series receiver cut out after a couple of hours. Fitting a replacement sound panel cured the problem – these panels are not worth repairing by us – but a week or so later the customer phoned to say that the trouble had returned, along with varying brightness. On examination, we found the set to be thoroughly wet, with the e.h.t. sparking away. We brought it into the workshop to dry it out, after which it performed correctly. All this had to be done free of charge, since the set was under guarantee. All we could do was to give some advice on heating and hope for the best.

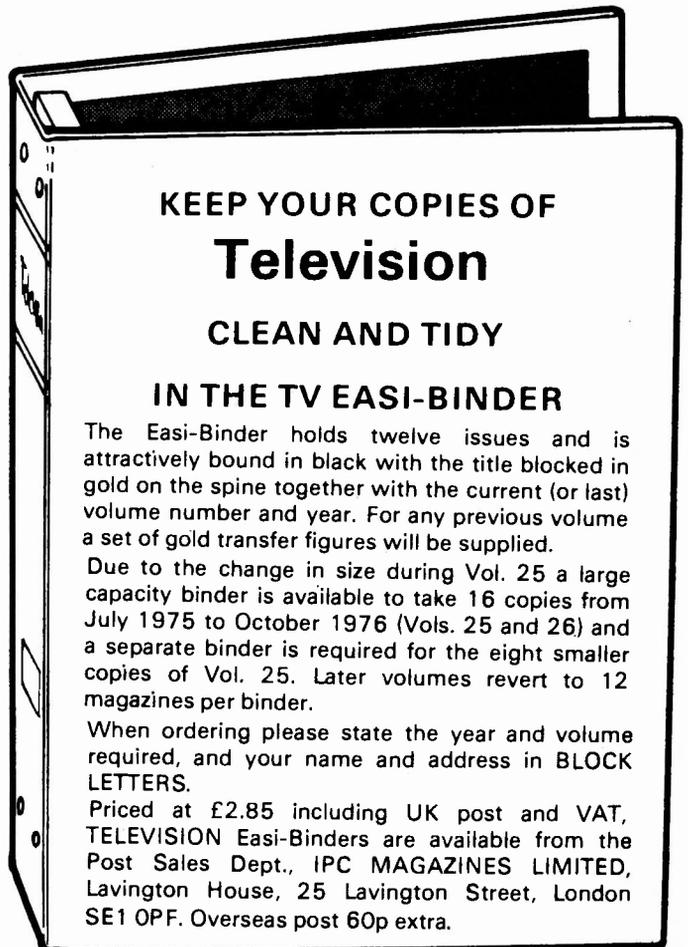

**KEEP YOUR COPIES OF
Television
CLEAN AND TIDY
IN THE TV EASI-BINDER**

The Easi-Binder holds twelve issues and is attractively bound in black with the title blocked in gold on the spine together with the current (or last) volume number and year. For any previous volume a set of gold transfer figures will be supplied.

Due to the change in size during Vol. 25 a large capacity binder is available to take 16 copies from July 1975 to October 1976 (Vols. 25 and 26) and a separate binder is required for the eight smaller copies of Vol. 25. Later volumes revert to 12 magazines per binder.

When ordering please state the year and volume required, and your name and address in **BLOCK LETTERS**.

Priced at £2.85 including UK post and VAT, TELEVISION Easi-Binders are available from the Post Sales Dept., IPC MAGAZINES LIMITED, Lavington House, 25 Lavington Street, London SE1 0PF. Overseas post 60p extra.

TV Servicing: Beginners Start Here . . .

Part 24

S. Simon

LAST month we tiptoed into the shallow end of colour receiver servicing, and found that the power supply and line timebase sections of a hybrid colour set present little in the way of problems that we've not already met in dealing with monochrome receivers. We must now wade into slightly deeper water.

The next part of the set – sticking with Pye hybrid chassis – we're going to look at is the CDA panel – CDA standing for colour-difference amplifier. Why colour-difference? Well, remember first that there are three beams in a colour tube, to activate the red, green and blue phosphors, and that the luminance signal will drive the colour tube to produce a monochrome display just as with a monochrome set – in fact the luminance signal in a colour set is exactly the same as the video signal that drives the c.r.t. in a monochrome set. Clearly then to get colour on our colour tube we require something in addition to the luminance signal. That something consists of three colour-difference signals, one each for the three primary colours, red, green and blue. They may be positive- or negative-going, so as to add to or subtract from the luminance signal applied to each gun. Say we want to turn our display from monochrome to red. Obviously we have to turn up the red beam, but at the same time we have to turn down the blue and green beams, in order to preserve the correct brightness level. This is what the colour-difference signals do.

Colour Mixing

This is obviously a mixing process. We mix the luminance signal (Y) with the colour-difference signals (B – Y, R – Y and G – Y) in order to get the correct colour in the display. Now this mixing can be done in several ways. It can be done by a simple resistor network before application of the signals to the c.r.t., or as in most recent chassis in an i.c., or alternatively, as in many hybrid chassis including the Pye ones, by feeding the Y signals to the c.r.t. cathodes and the colour-difference signals to the tube's control grids (see Fig. 1). This latter technique is for obvious reasons called colour-difference tube drive; the alternative arrangement, in which the tube is driven (almost always at its cathodes) by RGB signals, is for equally obvious reasons called RGB tube drive. Note that for a monochrome display the colour-difference signals simply disappear, the tube being driven by the luminance signal only.

Grey Scale

As you'd expect, there are some complications. Since the human eye has an uneven colour response, the signal levels have to be adjusted to take this into account. The correction required is done at the transmitter. To take into account receiver circuit tolerances, and differences between the characteristics of different tubes, highlight presets are incorporated in the tube drive circuits while the tube's first

anodes are provided with low-light presets that set the cut-off levels of the three guns (since the PIL type of tube has a common first anode structure, the low-light presets with this type of c.r.t. must act on the tube's biasing). When everything is set up correctly, we should have a tint-free grey scale from bright white through to dark grey.

This is all very nice, but alas tubes age and the emission of the three guns tends to vary over a period of time, with the result that the displayed picture may show decided colour tints at different brightness levels. Assuming that the tube's emission is good however, the grey scale should not be too difficult to set up, if indeed this is necessary at all. The point to bear in mind is that if a good black-and-white picture cannot be resolved with the colour off, it will be impossible to obtain correct colours when colour is restored to the display. You have the first basic rule of colour receiver servicing therefore: first get it right in black and white.

CDA Circuitry

RGB drive to the tube's cathodes is the more efficient system, since the cathodes are being swung with respect to steady voltages on the first anodes and control grids, i.e. if the cathode is driven negatively, this is the same as both the control grid and the first anode being driven positively, whereas when a colour-difference signal is applied to the grid the voltage difference between the cathode and the first

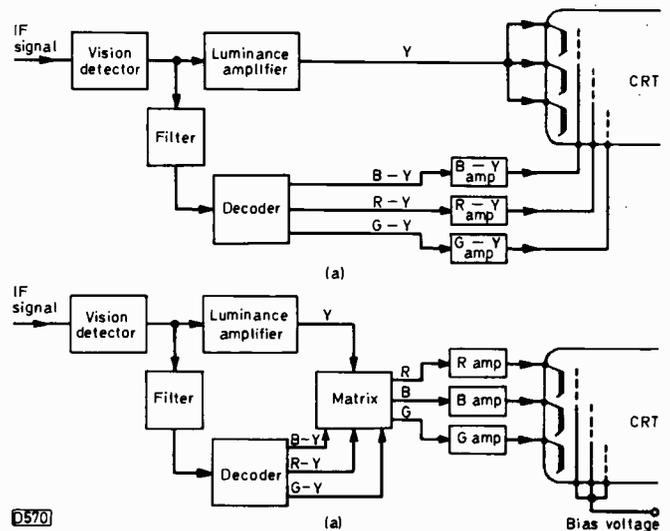


Fig. 1: Methods of driving a colour tube. (a) Colour-difference drive, with the luminance signal (Y) applied to the three cathodes and the three colour-difference signals applied to the grids. The tube then carries out the RGB matrixing, the phosphor screen being activated by the three primary-colour signals. (b) RGB drive. In this case matrixing is carried out prior to the tube, the RGB signals being applied (almost always) to the three cathodes.

anode remains the same, so that a larger signal swing is required. This large signal swing requirement persuaded most designers of early sets to opt for valve colour-difference amplifiers. If the signal voltage swing required to drive a beam from full on to full off is 150V, this must be developed across a resistor of some 10kΩ from a supply line of over 200V. A valve with a fairly good mutual conductance figure (change of anode current with change of grid voltage) is required to provide the current necessary to produce this swing across the 10kΩ load resistor. So it's quite common to find three colour-difference amplifier valves of the PCL84 type driving the three tube control grids, while a PL802 luminance output pentode drives the three tube cathodes. This valve line-up is not universal however: in the Philips G6 chassis for example you'll find a PFL200 used as the luminance output valve and three PCF200 valves as the colour-difference amplifiers.


The PCL84 and PCF200 valves are triode-pentodes, the pentode sections being the high-gain amplifiers which drive the c.r.t. grids, while the triodes are used as clamps to keep the d.c. conditions at the tube grids correct (because the pentodes are a.c. coupled to the grids). The basic idea is shown in Fig. 2. The drive signal developed across R1 is coupled via C1 to the c.r.t. grid. The triode clamp is driven hard on at the end of each line by a pulse derived from the line output stage. As a result, the junction of C1 and R2 is restored once each line to the voltage set by the potential divider R3/R4, thus stabilising the d.c. conditions.

The clamp triode's anode resistor is of a high value, typically 10MΩ, and it's not uncommon to find one of these (remember that three such circuits are required, one for each c.r.t. control grid) open-circuit or very high in value, thus allowing the relevant tube grid to drift, rendering the grey scale quite wrong. Note that as a result of the a.c. coupling a faulty pentode anode load resistor (R1) will not affect the grey scale (there's no colour signal swing) but will really upset the colour rendering.

Poor Grey Scale

Inability to obtain a good grey-scale with a tube that's known to be good must direct attention to the tube base voltages, checking that the first anode voltages are roughly equal (say 450V at each first anode pin), that the cathodes are at whatever is stated in the service data for the set (say 220V) while the grids are at around 80-100V (assuming colour-difference tube drive). If the application of the voltmeter to one cathode drastically changes the colour, check the preset drive control associated with that cathode (see Fig. 3). If the grid voltages are not roughly the same, check the clamp triode and its associated components, particularly the high-value anode resistor. Also remember this: the grids of the three clamp triodes are connected together, so that a fault in one triode will affect the others. PCL84 valves are particularly prone to developing faults in their triode sections, and one faulty one will affect the other two.

The Pye hybrid sets are also particularly prone to developing troubles on the CDA panel itself, due mainly to decomposition of the plastic panel material (the heat from the four valves being conducted down on to it by the base contacts). Thus incorrect colours may well be due to cracks in the panel, leakage through the panel material, and poor earthing to the rear clips. The earthing is made by spring wires which pass through loops of metal, and it's the loops that are soldered to the panel earth. Poor contact between the wire and the loop therefore will result in a poor earth connection to the main frame. This is one cause of colour

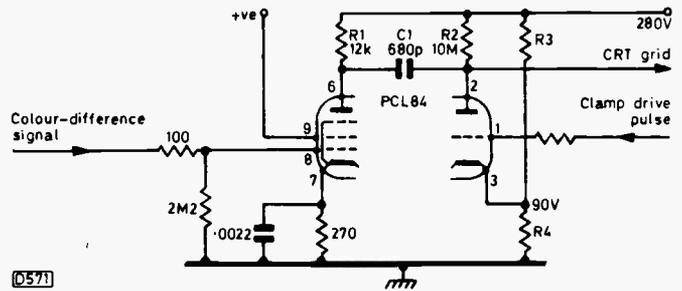

0571

Fig. 2: A typical colour-difference output stage, with triode clamp. C1 couples the signal to the c.r.t.'s grid, with the triode setting the d.c. conditions at the grid. The black level is set by the potential divider R3/R4.

shading from the left to the right of the screen (say green to the right and blue to the left). The remedy is to solder the wires to the loops, or connect a flying lead from the panel earth to a screwed earth on the main frame. Speaking generally, many strange effects can be displayed on almost any make of colour set as a result of poor earthing, and the connection of a lead from the main frame to the various panel earths can be a rewarding exercise.

Signals in a Colour Set

Now let's just briefly consider the various signals we're concerned with in a colour set. There are three colour-difference signals plus the luminance signal, and when these are mixed, either before the c.r.t. or by application to the c.r.t. electrodes, we get R, G and B primary-colour signals to activate the colour phosphors on the screen. The luminance signal is the same as the video signal in a monochrome set, and has the full video bandwidth, i.e. the picture detail is contributed by the luminance (Y) signal, exactly as in a monochrome receiver. In addition, two colour-difference signals are transmitted. Only two, you may ask? Yes, because if you look at the mathematical relationships between the two transmitted colour-difference signals (R - Y and B - Y) and the luminance signal (Y), i.e. their relative amplitudes, you'll find that the third colour-difference signal (G - Y) can be obtained quite simply in the receiver by adding together certain preset proportions of B - Y and R - Y. This is done in the G - Y matrix, which may consist of a couple of resistors or be something that in more recent sets goes on within an i.c. The two transmitted colour-difference signals have a much narrower bandwidth than the luminance signal, since the human eye is not sensitive to colour detail, and are carried on a common subcarrier which fits within the channel bandwidth. The various signals are separated out in the receiver by filters, and sent to the appropriate parts of the set.

The chrominance signal, as the transmitted colour-difference signals when modulated on to their subcarrier is called, passes from the video detector (or a separate detector) to the colour decoder, whose function is to process and demodulate the chrominance signal and present to the video output circuits either RGB signals or the luminance and three colour-difference signals depending on receiver design. The colour-difference signals are adjusted in amplitude at the studio to correspond with the sensitivity of the human eye, and are further weighted to avoid overloading the transmitter. The latter is corrected in the receiver simply by presetting the relative gains of the R - Y and B - Y amplifiers. The PAL system introduces some clever twists to overcome the effects of signal distortion in the transmission process - but we'll have to leave a look at that side of things until we come to the decoder. Our main

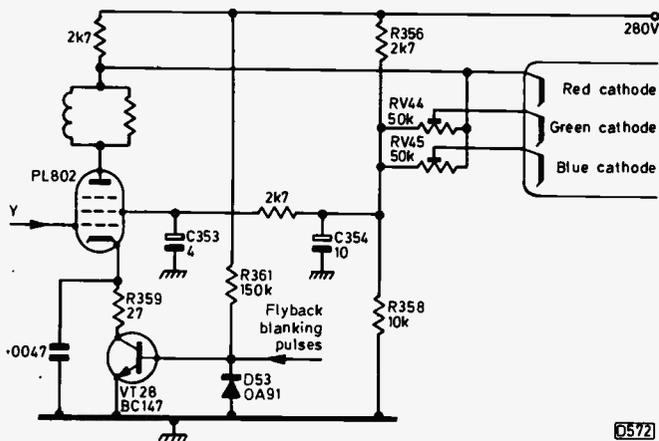


Fig. 3: A typical pentode luminance output stage. In some receivers there are preset controls in all three c.r.t. cathode circuits. The luminance signal is a.c. coupled to the PL802's control grid, and the brightness control acts here via a d.c. restorer. Beam limiting is also generally carried out at this point in hybrid colour receivers.

current (i.e. the e.h.t. current) is reduced to a safe level. RV16 in the transistor's emitter circuit sets the operating level of the beam limiter circuit. Thus the setting of the beam limiter, on the power unit, is closely related to the brightness control on the front panel. (See Fig. 2, page 581).

Dark Picture

In practice the beam limiter circuit is relatively trouble free. Complaints of a dark picture, with the brightness control up full, are nearly always due to failing emission in the PL802 valve, which can nowadays be replaced by a solid-state equivalent which is marketed under the same type number except that it carries a suffix such as T to indicate that it's different.

Flyback Blanking

Another operation that's carried out in the luminance output stage is flyback blanking – cutting the tube off when the spot is returning from the right-hand side of the screen to the left-hand side or from the bottom to the top. Blanking can be effected by raising the c.r.t.'s cathode voltages with respect to its grid voltages, or by dropping the grid voltages with respect to the cathodes. On most sets employing colour-difference drive the former is the chosen method, the luminance output valve being cut off during the flyback times. This raises the anode voltage and thus the c.r.t. cathode voltage to the full h.t. voltage.

concern at this stage is to get clear the idea of three tube beams being separately driven and that errors in the drives, due to incorrectly adjusted preset controls or component faults, will result in incorrect colours in the display.

Luminance Output Stage

One of the main trouble spots in a hybrid set with colour-difference drive is the luminance output stage. This usually features a PL802 valve, though as we've already pointed out the Philips G6 uses a PFL200 for the purpose. Since we're taking the Pye hybrid chassis as our example however, we'll stick with the PL802. Fig. 3 shows a simplified circuit of the PL802 luminance output stage used in the Pye chassis. Its anode is directly coupled to the c.r.t.'s red cathode, while preset controls are incorporated in the drives to the green and blue c.r.t. cathodes. These presets enable the circuit to be set up for correct (untinted) white. Since d.c. coupling is used between the PL802 and the c.r.t. cathodes, it's obvious that the voltage at the cathodes depends upon the current passed by the valve. As the valve's emission falls, its anode voltage and the voltages at the tube cathodes rise and the picture gets darker and darker. This fault does not have to be due to the valve losing emission however. The same effect will be produced if its control grid becomes too negative with respect to its cathode, or its cathode becomes too positive with respect to its control grid, which is the same thing though the causes are different.

Quite apart from the signal swinging the PL802's control grid voltage up and down, the beam limiter and the brightness control also operate on the control grid. So we need to know how the beam limiter functions. It's quite simple, really. If the e.h.t. current demand is excessive, which doesn't do the tube, the tripler or the line output transformer much good, the PL509 line output valve will be asked to pass excessive current. If we connect a resistor in its cathode lead, the voltage developed across this will be proportional to its cathode current and we can thus monitor the conditions in the line output stage. This voltage is applied to a sensing circuit which consists of a transistor and a few resistors, including a preset control (RV16). When the voltage across the PL509's cathode resistor exceeds a certain level, the transistor conducts and reduces the voltage applied to the brightness control. In consequence the PL802 passes less current, and the c.r.t.

In our specimen chassis the cathode of the PL802 is returned to chassis via a small resistor (R359) in series with a transistor (VT28). When the transistor is fully conductive, the resistor provides the only bias and the PL802 works away normally. During the flyback periods however the transistor is turned off by the blanking pulses, and the valve is thus also turned off. Its anode voltage rises, cutting off the c.r.t. In the absence of flyback blanking pulses, the transistor is held conductive by R361 (150k Ω). While the blanking circuit is normally reliable, the valve is sometimes blamed when in fact R361 has gone high in value, the transistor has gone open-circuit, or the associated base protection diode D53 has gone short-circuit.

One also has to take into consideration the possibility that the blanking circuit is in order but the beam limiter is faulty, biasing back the valve's control grid. "Oh dear" you may say, "what do we do?" Well, eliminating the blanking circuit from the list of possibilities is quite simple. You simply short out the blanking circuit by taking the bias resistor R359 direct to chassis, noting the effect. If the brightness returns to normal, the blanking circuit is proved faulty and one checks the transistor, resistor and diode. These items need not be wholly short- or open-circuit: degrees of defectiveness can result in poor picture definition plus distinct striations (vertical rulings) down the left half of the screen, though we hasten to add that the most common cause of the latter fault is that the resistor which damps the line linearity coil has gone high in value. This resistor (R228) should be 1.5k Ω , but as it's a carbon one it tends to cook up. The result is that it goes high in value and fails to damp linearity coil which rings, causing the striations.

Other CDA Faults

There are lots of other items that can play tricks on the CDA panel, such as open-circuit electrolytic decoupling capacitors which can mess things up colour wise, open-circuit resistors, and missing supply lines. The latter problem is not necessarily due to an open-circuit resistor

since, as we've already mentioned, deterioration of the panel occurs: as a result, the fact that the h.t. is present at the panel input point does not mean that it gets to where it's supposed to be. Cracks in the tracks you see, something to bear in mind.

Later versions (693, 697) of the Pye hybrid chassis employ a varicap tuner which requires a stabilised 30V tuning line. This is obtained from the h.t. line through a resistor or resistors on the tuner panel. The h.t. is not taken direct from the power supply however, but is derived from a point on the CDA panel. Deterioration of the panel can thus result in the absence of the tuning voltage, with the result that the tuner cannot select any signals and simply produces noise. The tuning voltage also disappears when R389 goes open-circuit, but as this also removes the supply to the

c.r.t.'s control grid clamp circuits the result is no or very little screen illumination and no sound signals of course. The trick is to know what voltage to expect and where to expect it. Almost back where we started, aren't we?

Summarising

In conclusion this time we'd mention that whilst the colour decoder, which we've yet to consider, is far more complex than the colour tube's drive circuitry (the luminance and colour-difference amplifiers), the fact is that the vast majority of colour faults are due to something amiss in the c.r.t. drive/biasing arrangements. There are also convergence and purity to consider, though the results of faults here are mainly self-evident.

Letters

EW TINTING

I've read with interest the comments in *Television* on EW tinting with the Pye hybrid colour chassis. The fault has come my way only once, and what I can't understand is how switching the c.r.t. first anodes on and off could have cured it, even temporarily.

I arrived at the cause of the trouble after giving it some thought. What was obviously happening was that one of the guns was being turned on progressively harder as its beam scanned across the screen. This was verified by using the scope to monitor the c.r.t. cathode waveforms and also by observing the three rasters separately. This threw suspicion on the colour-difference output/clamp circuits, and the 12k Ω pentode anode load resistor was found to be open-circuit (R391 in the G - Y channel in this case). I've since been told that the fault is quite common on these chassis. The sure-fire way of checking this is to disconnect the lead supplying the 47V pulses to the clamps: this stops the clamp action, and if the tint disappears the pentode anode load resistor is the cause of the trouble.

I'd also like to take this opportunity to agree with your contributors who have commented on the low standards of performance most people are prepared to accept from their TV sets, even when new.

Gerald Messent, North Cornelly, Bridgend, Glamorgan.

Editorial comment: Since the pentode anode load resistors sometimes go open-circuit intermittently, it would seem that the first anode switching business is coincidental.

BIONIC PYES

We read with interest the article entitled *Bionic Pyes* in your June issue, covering certain of our products specifically designed as replacement units for use in Pye hybrid colour receivers. We appreciate the fair presentation and recommendations, but would like to add a few comments.

First the CDA panel on which your tests were made was an early production one. Although many thousands of these are now in use, the only modification we have found to be desirable is to change the colour-difference output transistors from type BF259 to type BF459 so that we can use a different type of heatsink. There is nothing wrong with the BF259 as such, but the tall heatsink we used with it makes it top heavy and vulnerable to damage, especially

when sent through the post. Rough handling could result in the transistor leads being pulled out of the board, and this could have been the cause of the dry-joint trouble referred to in your article. There have been very few cases of this reported to us, but we decided to prevent it by changing to the BF459 with its lighter heatsink - this was some eight months ago.

The audio module, like the CDA panel, has also been very successful and well received by users. We have found however that the supply of the SN76013ND i.c. in production quantities is too erratic, though it is readily available for replacement purposes. Being unable to find a suitable alternative i.c., we decided to redesign the module using discrete components which we can get in sufficient quantities to maintain production. The new module is still a direct replacement for the LP1162, and of course we've used silicon transistors which make it more reliable than the original Mullard LP1162 unit.

Your readers may be interested in our new 915 module, which has been designed as a direct replacement for the i.f. selectivity/gain unit used in the Pye 713, 725, 731, 735, 737 and 741 chassis and the Philips 570 chassis. The original units have proved troublesome due mainly to the use of a number of through board connections and double-sided print. Our replacement unit uses a SAWF to provide the bandpass response and an i.c. to provide the gain, and as a result we've managed to achieve a single-sided print layout.
W. Kennedy, LEDCo, Thornton Heath, Surrey.

LEDCo CDA PANEL

Having been plagued for some time by drifting grey-scale and other problems in an ageing Pye hybrid colour set (697 chassis), I decided some while ago to fit the LEDCo CDA panel reviewed in your June issue. For nine months or so the board has performed admirably in eliminating these defects, and looks like adding several years to the life of the set. I was surprised however that you omitted to mention a rather obvious shortcoming in the design of the solid-state circuit. This is that the components which bias the base of the luminance input transistor (VT701) upset the action of the d.c. restorer D39, causing the black level to float up and down with the picture content as if the luminance was a.c. coupled. I must say however that this is far less annoying than the effects of tired valves.

Alan Pemberton, Sheffield.

P.S. Poor field lock on this set turned out to be the field sync pulse integrating capacitor C41 (0.0047 μ F) open-circuit, replacement curing the trouble. I've not seen this one mentioned in your columns before. It's mounted on the i.f. panel, along with the sync separator.

Your PROBLEMS solved

Requests for advice in dealing with servicing problems must be accompanied by a 50p postal order (made out to IPC Magazines Ltd.), the query coupon from page 603 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

TELEFUNKEN 709 CHASSIS

The set will work perfectly all evening provided the channel is not changed. If another channel is selected after the set has been on for some time, it's impossible to obtain a picture. The situation is the same on all channels. The set works normally when first switched on from cold.

The tuning voltage stabiliser diode GR971 (ZTK33) has a tendency to cause slight tuning drift when warm, since it then stabilises at a slightly different voltage. This effect is often sufficient to throw the set off tune when a different channel is selected. Another area that gives trouble on this chassis is the gated a.g.c. circuit. This is on the main signal board, alongside the i.f. unit. Operation of the circuit can become very critical when, as the set warms up, either of the transistors T171 (BC237A) or T172 (also BC237A) starts to break down, reducing the voltage at pin 3 of the i.f. strip so that overloading occurs. Under these conditions it's extremely difficult to tune the receiver to any station at all.

GEC C2002H

There's a dynamic convergence problem with this set. The colours are correct at the centre of the screen. The top left-hand side is all green however and the bottom red, the right-hand side being the same but with the colours reversed. The colouring tends to vary with the brightness.

The most likely cause of this would seem to be a defect associated with the horizontal R/G symmetry coil L905 on the convergence panel. There must be d.c. continuity, since the line scan current flows through this coil. Try setting it up, and if this fails fit a replacement.

THORN 3500 CHASSIS

The set will work perfectly for perhaps a few hours, then the cutout will operate. If this is reset, the set will again work satisfactory for a while but will eventually trip. This can happen several times in the course of an evening. A possible clue is that R609, which is in series with the chopper transistor, tends to burn out. The tripping continues after replacing this resistor. The cutout itself has been replaced, and everything else appears to be in order.

The cutout operates when the crowbar thyristor W621 fires, shorting R609 to chassis in the process. It seems therefore that there is repeated crowbar action. Suspects in this area are the crowbar thyristor W621, the sensing zener diode W617, and C618 (100 μ F) which is present in this circuit to suppress transients. Alternatively, the h.t. supply could be rising so that the trip operates. Disconnect the feedback amplifier by removing R621: this should give a

small picture, with the h.t. supply falling to about 30V. If the trip still operates, the chopper transistor is probably faulty. If the h.t. is rising due to the monostable being held on too long, check W615. Make sure the print around W621 is clean – the electrolytics tend to leak.

DECCA 30 SERIES

This Decca 30 series chassis is actually in a Telefunken model. The picture is very good once the set settles down after the first few minutes, but some odd things occur initially. After switching on, one usually gets to start with a very dark, diffused picture, mainly in blues and greens. Then the screen becomes almost entirely white, with very pale colours here and there. Eventually a vague picture is seen, then a hissing noise occurs accompanied by dark lines across the screen. Then the picture comes up much clearer.

It seems to us that the most likely cause of these symptoms is simply that either the PL509 or PY500 line output stage valve is lazy. Alternatively, it could be that the c.r.t. is loading the e.h.t. generator due to its being driven hard as a result of a fault on the decoder panel. This would show up as an abnormally low voltage on all three cathodes, and could be due to a faulty MC1327P demodulator/matrixing i.c. or a fault in the luminance emitter-follower (TR204) circuit.

CHECKING CAPACITORS

Reference is often made in your magazine to leaky capacitors. Can you advise on the equipment and method of checking this? What I do is to use a scope to trace the signal, then use a multimeter to check for open- and short-circuit capacitors when the scope indicates that a fault is present. Some capacitors check out o.k. however, though replacement produces an improvement. Other capacitors look as if they're defective but perform satisfactorily.

We cannot suggest any improvement upon your method of checking suspect capacitors. The only additional factor we tend to rely on is that some types of capacitor are more prone to failure than others. Other than this if in doubt, chuck it out.

ITT CVC8 CHASSIS

The trouble with this set is loss of colour. I managed to restore the colour by replacing the delay line driver transistor T29, using a BC107, but the colour went again after a couple of days. Using the correct BC171B transistor produced no results. The voltages seem to be correct, except for those at the output pins 1, 2 and 4 of the MC1327 i.c. These are 7.5-8V instead of 6V. I've changed the varicap diodes in the saturation control circuit, also C161 which couples the signal to the base of T29.

First check that the bistable transistors are working – the collector voltages of the two transistors (T36/37) should be 9-10V with a colour signal. Then check C165 which decouples the emitter of T29 and C162 which smooths its base bias. These are both 4.7 μ R tantalum electrolytics. There are three other capacitors of this type in the chroma amplifier circuit, C155, C153 and C151. All may need to be checked – observe correct polarity if any need to be replaced. The chroma amplifier transistors T27 and T28 are also suspect. Loss of colour is commonly due to faults in the burst/reference oscillator section, such as oscillator drift, but this would be betrayed by a rainbow pattern as the fault comes and goes. If necessary, check that the output from the ident stage is adequate – there should be 11V across C218 with a colour signal.

THORN 1500 CHASSIS

The problem with this set is wavy verticals, from the bottom to the top of the screen, slightly more noticeable on the right-hand side. There is no buzz on sound however.

In spite of the absence of hum, the main electrolytic block C88/91/101 could be faulty. Check its connections to the printed board before condemning it. A more likely suspect however is C102 which smooths the h.t. rail used by the line generator and sync circuits. Other suspects are C98 which decouples the line output valve's screen grid, C32 which smooths the video driver transistor's base bias, C56 and C58 which smooth the l.t. supplies, or possibly heater-cathode leakage in the PY801 boost diode.

TELEFUNKEN 634E

Recently, after the set has been switched on the picture appears first as a slot across the centre of the screen. The picture then "flicks", and during the next couple of minutes expands vertically. It never quite reaches the top and bottom of the screen however.

This set is in fact fitted with the Decca hybrid colour chassis, and consequently the same fault-finding approach is required. The most common culprit causing sluggish opening out of the field scan is simply the PL508 field output valve, which may be taking rather a long time to reach full emission. When this valve starts to fail, its cathode bias resistor R413 (560 Ω) and screen grid feed resistor R415 (3.9k Ω) tend to cook, so these should also be checked. The PCF80 (triode section) which forms part of the field oscillator is usually reliable, though it's emission has been known to fall, giving similar results. Lack of height is commonly due to the resistors in the height control circuit changing value. Check R402 (820k Ω) and R405 (270k Ω).

PYE 691 CHASSIS

A band, approximately 1½ in. wide, passes through the picture. It varies in speed and direction, sometimes going from the top of the screen to the bottom, then changing direction. At other times it's almost stationary. The main smoothing block C306/315 has been changed and other capacitors in the smoothing section checked by substitution. Voltage checks show a slight variation in the voltage at the collector of the field output transistor VT27, in sympathy with the band. The verticals in the band bend to the left, but there's no change of colour. Both the line and field locking are good.

It could be tricky trying to find the source of this hum problem. As a start we suggest you double check the smoothing electrolytics, especially the 1,250 μ F ones (C307/313/308/309). If these are satisfactory, the inter-connecting plugs and the chassis bonding connections will have to be checked. Remember that the i.f. strip's l.t. smoothing capacitors are on the top of the i.f. panel itself.

THORN 1500 CHASSIS

The trouble is that the field hold cannot be held for any length of time before it drifts away again. I've tried a new PCL805 field timebase valve without success.

This sort of trouble is often due to the circuit between the anode of the output pentode section of the valve and the triode grid. There are two resistors (R101 and R102) that tend to change value. Check that they are still 18k Ω . If it's necessary to replace them, use 1W types. Then check the associated capacitors, particularly C75, since these can become leaky. Also check the sync separator's screen grid feed resistor R44 (47k Ω), again replacing if necessary with a 1W type.

BUSH TV300

When the set has not been in use for a while, a normal picture is obtained after switching on. This lasts for half an hour to an hour, then the white parts of the picture begin to streak to the right and eventually, even with the contrast control at minimum, the picture goes almost totally white. Try the set within three days and the streaking is still pretty bad: leave it a week or so and a normal picture is obtained again. The resistors and electrolytics in the video output and contrast control circuits have been checked, and the video output transistor TR10 changed, but the trouble persists. The voltage at the collector of the video output transistor is very low with the fault present.

The low collector voltage on TR10 is the key factor. The supply comes from the line output stage, and is smoothed by C519 and C520 (both 1 μ F). Every time we've come across these symptoms, one or other of these electrolytics has turned out to be responsible. It's possible that the rectifier concerned (D505), the filter resistor R515, or the discharge resistor R234 could be at fault however.

TELETON VX1110

The raster collapses, as though the set has been switched off, reappearing a few seconds later. This can happen two or three times, then the set will settle down with no further trouble. There's also intermittent loss of field hold, and poor field linearity (top elongated).

For the loss of e.h.t. (picture collapse), open the right side compartment flap to expose the 3AT2 e.h.t. rectifier and check with a neon tester — the neon should light up when brought near (not touching) the valve. You should also be able to see the glow of this valve's heater. If the neon remains alight when the picture goes off, see if the heater fades out. If it does, make sure that the e.h.t. is discharged and then remove the valve base to check the heater contacts and the 2.2 Ω series resistor. If the neon goes out, check the line timebase valves and voltages. The line output valve is a 31JS6A and the boost diode a 17DW4A. The field trouble should respond to a new 17JZ8 field output valve. If necessary, check its cathode bias components and those in the linearity network.

PHILIPS 210 SERIES

There's an odd sound fault on this set. After switching on, the sound comes on at full volume, with a trace of hum, even with the volume control at minimum. After about half an hour however the conditions stabilise and the volume control operates normally.

The volume control is returned to chassis via a 2.5 μ F electrolytic capacitor (C1503). Either the volume control itself is defective, the capacitor is defective or improperly connected, or the earthing is not being made to chassis. Note that the positive side of C1503 goes to chassis, the negative side to the volume control.

QUERY COUPON

Available until 17th September, 1979. One coupon, plus a 50p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 602.

TELEVISION SEPT. 1979

TANDBERG CTV2

The original fault with this set was loss of raster, with the power supply module going into its "purring" mode. The cause was found to be a defective horizontal shift choke (L752), and replacing this restored the sound and picture. There are still a couple of faults however. First the picture is of reduced width, the width control R860 (in the EW modulator circuit) having no effect at all. The voltage at the supply end reads 30V instead of 25V. Secondly, although the 6.8V reference zener diode D975 in the switch-mode power supply control circuit has been changed (to cure picture size variations) the h.t. supply cannot be set any higher than 150V (should be 160V). The set h.t. control R976 can be used to reduce the h.t. below 150V however. Whilst checking around the circuit I noticed that the EW modulator diodes D750 and D751 seem to have been running hot, as the board is slightly scorched in the vicinity.

All your problems are likely to be resolved by replacing

the EW modulator diodes, plus the EW modulator output transistors Q853/852 if necessary. Also check whether the horizontal shift control R772 is burnt.

THORN 980 CHASSIS

The trouble with this set is very critical line hold, which has to be constantly adjusted – every three to four minutes. A new line oscillator valve has been tried but has not improved matters.

The fault could be in the flywheel line sync circuit, where the discriminator diodes W3/4 are the first suspects. A very likely possibility however is a fault in the video output stage. You will find a bias stabilising resistor (R26, 39k Ω , 1W) connected between the screen grid and the cathode of V5. This commonly falls in value, upsetting the bias conditions in the stage and therefore severely clipping the sync pulses. The sync separator's screen grid and anode load resistors would also be worth checking.

TEST CASE

201

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

An ASA Model CT6000 colour receiver had been working satisfactory for at least four years – with good sound and bright pictures – at a site within six miles visible range of a low-power transmitter. Being a worker with "unsociable hours", the owner decided to try out a video cassette recorder, and for the first week or so was happy with the results. The pictures were crisp and the colours accurate, both off-air (through the machine's "monitor" mode) and off-tape.

As the days went by however, the early morning viewer of the previous night's programmes became less enchanted. He found the recorded pictures getting less sharp, though the colour accuracy was unaffected. The distaff side started to complain that it was necessary to turn down the brightness and sometimes the contrast, and to darken the room, in order to achieve acceptable viewing from the set. It was discovered that the pictures could be improved by altering the position of the set-top aerial so that it was broadside on to the distant, though visible, transmitting aerial, whereas previously the best pictures had been obtained with the aerial pointing at the transmitter.

Since the colours remained accurate, the technician investigating the problem concluded that the e.h.t. tripler was at fault, especially after one or two measurements revealed that the focus potential at pin 1 of the tube was lower than normal even with the focus preset at maximum setting.

Unfortunately, tripler replacement failed to solve the

problem. The picture was still weak and not properly in focus at any point on the range of the preset focus control, though at full brightness setting the overall screen illumination was quite reasonable. Replacing the focus preset gave no improvement, and it was then concluded that video crushing was responsible. Detailed tests in the colour-difference and video amplifier stages failed to shed any light on the problem however.

What was the most likely cause of the trouble, and why was the fault seemingly aggravated by the use of a VCR? See next month for the solution and for a further item in the series.

SOLUTION TO TEST CASE 200

– page 550 last month –

It will be recalled that the Decca CTV25 mentioned in last month's test case was suffering from two faults, weak field sync and slight variations in height accompanied by an audible sizzle. The weak field sync was not a difficult problem to solve. The field sync pulses are applied to one of the control grids of the ECC82 cathode-coupled field multivibrator via an OA81 interlace diode (D301) whose cathode is biased by a potential divider consisting of a 3.3M Ω resistor (R302) connected to the h.t. rail and a 150k Ω resistor (R303) to chassis. With age, the higher-value resistor in the network tends to rise considerably in value, and the fault was completely cleared by replacing R302.

The field amplitude jitter was located less scientifically! Had it not been for the "reflected spark", diagnosis would have been more protracted. In the event, it was discovered that the spark was concentrated around the positive tag of the 400 μ F h.t. reservoir capacitor C2705 in the power pack. The tag had developed a high-resistance contact to its termination, and the result was a tendency to spark across due to the heavy ripple current. C2705 was still providing capacitance, but the ripple discharge was affecting the field scan more dramatically than any of the other sections of the receiver fed from the h.t. rail.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R 0NE. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £9.50, Overseas £10.50 per annum payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

★ NEW ★

COLOUR BAR GENERATOR

U.H.F. AERIAL INPUT PATTERN GENERATOR CPG6-RF

All Facilities of our PG6RF



PLUS COLOUR BARS.

Produces 7 invaluable patterns.

**Robust, Battery Powered, Pocket Sized Unit,
Plugs Straight into Aerial Socket.**

W H I T E	Y E L L O W	C Y A N	G R E E N	M A G E N T A	R E D	B L U E	B L A C K
-----------------------	----------------------------	------------------	-----------------------	---------------------------------	-------------	------------------	-----------------------

FEATURES:

- ★ CROSSHATCH GRID
- ★ DOT MATRIX
- ★ VERTICALS
- ★ HORIZONTALS
- ★ WHITE RASTER
- ★ GREYSCALE
- ★ PLUS PAL COLOUR BARS;

ONLY 3 SIMPLE ADJUSTMENTS.

- ★ PG6RF OWNERS; Buy Add-On 'C6' Unit!

ORDER NOW!

PG6RF KIT £25.87 BUILT £33.35 – As per TV Review, Jan. 1979

C6 KIT £18.98 BUILT £26.45 – Add-on Colour to PG6RF

CPG6RF KIT £42.55 BUILT £63.25 – Both above combined.

These prices INCLUDE P & P and 15% VAT. Export VHF versions available.

In response to demand we have produced an add-on Colour Bar unit C6 to upgrade the PG6RF to PAL COLOUR. A MUST for TV construction or servicing! Available as a KIT or BUILT & TESTED. Kit includes all components and ready built modulator etc. Full 12 month guarantee on built units.

MAIL ORDER ONLY

Quantity Discount on application

ACCESS ORDERS WELCOME

ALSO AVAILABLE:

TECS: TECHNLOGICS EXPANDABLE COMPUTER SYSTEM.

Full Colour Teletext; full facility Microprocessor-based, Aerial Input Decoder with extensive computing facilities. The most versatile decoder on the market. Expandable from a simple teletext decoder to a full professional computer/information centre. Send large S.A.E. for details.

SEND ALL ORDERS OR ENQUIRIES TO TECHNLOGICS LTD. (DEPT. TV)

8 EGERTON STREET, LIVERPOOL L8 7LY.

TV LINE OUTPUT TRANSFORMERS

by FAST RETURN OF POST SERVICE

MONO LOPTS

Most makes supplied

£6.90 TRADE

£7.50 RETAIL

p&p 75p

COLOUR LOPTS

Philips G8, ITT CVC5-9, Decca Bradford series 10 & 30

£8.35 TRADE

£9.50 RETAIL

p&p 75p

WINDINGS

Bush colour. (Hybrid quadrupler version)

£6.25

Decca CTV19/25 (non-tripler version)

Primary £6.25

EHT £7.20

Phillips G6 (dual & single standard)

Primary £6.25

(EHT winding on exchange basis only)

EHT £7.20

Pye 691, 693 & 697 (please state which)

Primary £4.60

EHT £3.10

EMO 90 degree

Primary £6.25

PRICES INCLUDE 15% VAT

S.A.E. all enquiries

All lopts and windings are new and guaranteed for 6 months.

PAPWORTH TRANSFORMERS

80 Merton High Street
London SW19 1BE

01-540 3955

ARE YOU

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling used colour televisions from home in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "How to Deal Successfully in Used Colour Televisions" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can succeed immediately.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure certain success. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail – for both televisions and new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. Plus FREE on-going advice and FREE regular updating service.

You can start tomorrow – but you'll need our guide. The latest big illustrated edition is out now, and costs just £4.95 – a small price to pay for financial independence!

SAME DAY SERVICE

CITY PUBLISHING, HAYWORTH ROAD, SANDIACRE, NOTTINGHAM NG10 5LL

To: City Publishing, Hayworth Road, Sandiacre, Nottingham NG10 5LL.
Please send by return post "How to Deal Successfully in Used Colour Televisions".
I enclose cheque/p.o. for £4.95.

NAME

ADDRESS

.....

**BIG NEW EDITION
OUT NOW!**

TV LINE OUTPUT TRANSFORMERS (Prices include VAT at 15%)

Post and Packing
70p

BUSH	MURPHY	DECCA	PYE	GEK	COLOUR TRANSFORMERS	
TV123 TV124 TV125 or U TV128 TV134 TV135 or R TV138 or R TV139 TV141 TV141 TV145 TV148 TV161 TV165 TV166 TV171 TV175 TV176 TV178 TV181 or S TV183 or D TV183S TV183SS TV185S TV186 or D TV186S TV186SS TV191D TV191S TV193D TV193S TV198 TV307 TV313 TV315	V843 all models to V979 V153 V159 V173 V179 V1910 V1913 V1914 V2014 or S V2015D V2015S V2015SS V2016S V2017S V2019 V2023 V2027 V2310 V2311C V2414D V2415D V2415S V2415SS V2416D V2416S V2417S V2419 V2423 A774	MS1700 MS2000 MS2001 MS2400 MS2401 MS2404 MS2420 Price £7.36 PHILIPS 23TG170a all models to 23TG176a G24T230a... all models to G24T310 19TG170a... all models to 19TG179a G19T210a G19T211a G19T212a G19T314a G19T215a G20T230a Price £7.36 INDESIT 20EGB 24EGB Price £7.85	58 64 59 68 60 75 61 76 62 77 63 80 81 93 83 94 84 95/4 85 96 86 97 92 98 150 161 151 170 166 170/1 156 171 160 171/1 Price £7.36 KB-ITT By Chassis: VC1 VC2 VC3 VC4 VC11 VC51 VC52 VC52/1 VC100 VC100/2 VC200 VC300 Price £8.48	BT454 BT455 BT455DST 2000DST... all models to 2044 2047... all models to 2084 2104 or/1 2105 or/1 Price £7.36 SOBELL ST196 or DS ST197 ST290 ST297 1000DS... all models to 1102 Price £7.36 THORN GROUP Ferguson, H.M.V., Marconi, Ultra. By Chassis: 800, 850, 900, 950/3, 960, 970, 950/1, 950/2, 1400, 1500, 1500, 1580, 1590, 1591, 1612, 1600, 1712 Or quote model No. Price £8.48	DECCA CS1730, 1733, 1830, 1835 DECCA 30 Series Bradford Chassis DECCA 60, 80, 100 Series GEC Dual STD Hybrid GEC Single STD Hybrid GEC Single STD Solid State ITT CVC 1 to CVC 9 ITT CVC 20 ITT CVC 30, CVC 32 PYE/EKCO 725 Chassis PYE/EKCO 731, 735, 737, 741 Chassis PYE/EKCO 713, 715 Chassis PHILIPS G8, G9 Chassis PHILIPS 570 Chassis THORN 3000, 3500 EHT and SCAN THORN 8000, 8000A, 8500, 8800 THORN 9000 TELPRO All Models	£9.51 £9.51 £9.51 £11.59 £11.59 £9.51 £9.51 £9.51 £10.53 £9.51 £9.51 £9.51 £10.53 £8.48 £10.02 £10.02 £9.51
Price £7.36					PYE EKCO 691, 692, 693, 697 Chassis Wired in version of above Price on Application Printed Circuit Version of above £15.26	
BUSH MURPHY A816 Chassis TV309 TV311 V2029 V2427 Price £10.30					EHT Winding PYE 691 to 697 Chassis* £3.07 Primary Winding PYE 691 to 697 Chassis* £4.60 *Please state Printed Circuit version or Wired version.	

Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702	MON-FRI 9 am to 12.30 pm. 1.30 pm to 4.30 pm. Closed Wednesday afternoon	Hamond Components (Midland) Ltd., 416, Moseley Road, Birmingham B12 9AX. Phone: 021-440 6144.	MON-FRI 9 am to 1 pm. 2 pm to 5.30 pm.
--	--	---	---

Contact your nearest depot for service by-return. Callers welcome. Please phone before calling.

STANDERD T.V. TUBE

HIGH QUALITY COLOUR AND MONO-CHROME REPLACEMENT TUBES AT COMPETITIVE PRICES.

- ★ Complete New Gun fitted to every Tube.
- ★ Two year Guarantee
- ★ Every Tube Electrically Tested.
- ★ Every Tube Picture Tested.
- ★ Supplier to Major Rental Companies.

19", 20"	£22
22"	£25
25", 26"	£28


**11-29, Fashion Street,
London E1**

**Ring Standerd T.V. Tube Reguner
Tel. 01-247 3097**



schub ASM 5007

A NEW APPROACH TO T.V. TESTING

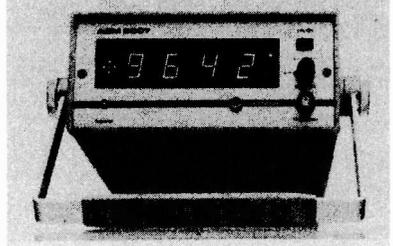

50kV PROOF + AUTO RANGE + MEMORY DISPLAY
Withstands EHT mistakes!

VOLTS DC
9-999 99-99 999-9V ± 0.08% ± 1 digit

VOLTS AC
9-999 99-99 999-9V ± 1% ± 1 digit to 20KHz

OHMS
9-999 99-99 999-9K ± 0.02% 9999K ± 1%

FREQUENCY
9-999 99-99 999-9KHz

Tone indication of new reading. Sample + Hold facility.
High brilliance 16mm display. 220/110V 50/60Hz 10W.
Fast Reading 12/sec.

£290 + VAT + Carriage

ADRETTA LTD, TEL (082 347)
NORTH STREET 3535
WELLINGTON, SOMERSET

MAIL ORDER PROTECTION SCHEME

The Publishers of *Television* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Television* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—
‘Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered’. Classified and catalogue mail order advertising are excluded.

CAMPBELL ELECTRONICS Limited

Unit E5, Halesfield 23
Telford, Salop
TF7 4QX
Tel: Telford (STD 0952)
585799/584373
Telegrams: CAMELEC
Telex: CHAMCOM 35191

WHOLESALE DISTRIBUTORS OF SPECIALISTS SPARES TO RADIO & TELEVISION SERVICE DEPTS; NATIONWIDE

SEND FOR OUR FULL CATALOGUE AND PRICE LIST

Your source to better components

TRANSISTORS

part		part		part		part		part		part		part		part					
AC127	26	AF239	50	BC119	25	BC173	14	BC464	60	BD150B	40	BF123	23	BF222	50	BF450	24		
AC128	25	AF2795	79	BC125	12	BC178	17	BC465	60	BD150C	84	BF154	18	BF214	18	BF458	38	BU117Y	230
AC141	26	AL102	150	BC126	14	BC179	20	BC547	09	BD163	70	BF156	29	BF240	18	BF459	45	BU126	120
AC142	27	AL113	150	BC135	16	BC182L	10	BC548	09	BD166	46	BF158	18	BF241	09	BF459	30	BU204	134
AC153	36	AU103	210	BC136	12	BC183L	10	BC549	09	BD181	77	BF160	22	BF255	09	BF459	30	BU205	134
AC176	28	AU106	166	BC137	15	BC184L	10	BCX31	20	BD182	70	BF167	35	BF256	40	BF459	30	BU206	134
AC187	27	AU107	166	BC139	25	BC186	21	BCX32	20	BD183	78	BF173	27	BF257	25	BF459	30	BU207	220
AC188	27	AU108	207	BC140	28	BC187	19	BCX33	20	BD187	65	BF177	45	BF258	27	BF459	30	BU208	220
AD149	67	AU110	150	BC141	28	BC212L	10	BCX34	30	BD201	80	BF178	19	BF259	28	BF459	30	BU209	134
AD181	37	AU111	217	BC142	23	BC213L	11	BCX36	26	BD222	48	BF179	22	BF262	37	BF459	30	BU210	134
AD162	35	AU112	217	BC143	25	BC213L	11	BCY70	17	BD225	48	BF180	29	BF263	37	BF459	30	BU211	134
AF115	28	AU113	158	BC147	10	BC214L	11	BCY71	16	BD232	45	BF181	24	BF271	20	BF459	30	BU212	134
AF116	28	AU110	129	BC148	09	BC237	12	BCY72	17	BD233	47	BF182	29	BF273	12	BF459	30	BU213	134
AF117	28	BC107	11	BC149	11	BC238	11	BD115	36	BD234	45	BF183	28	BF274	13	BF459	30	BU214	134
AF118	68	BC108	10	BC153	11	BC239	10	BD116	55	BD237	50	BF184	22	BF274	13	BF459	30	BU215	134
AF125	36	BC109	11	BC154	11	BC307	12	BD131	37	BD238	50	BF185	27	BF336	27	BF459	30	BU216	134
AF126	37	BC113	13	BC157	10	BC327	12	BD132	43	BD435	65	BF194	10	BF337	27	BF459	30	BU217	134
AF127	37	BC114	13	BC158	09	BC337	12	BD133	39	BD437	45	BF195	09	BF338	27	BF459	30	BU218	134
AF139	48	BC115	14	BC159	11	BC338	12	BD135	36	BD509	55	BF196	09	BF355	40	BF459	30	BU219	134
AF178	86	BC116	13	BC160	26	BC384LC	21	BD136	30	BD514	40	BF197	11	BF362	40	BF459	30	BU220	134
AF180	158	BC117	11	BC170B	20	BC641	27	BD140	39	BDX32	170	BF198	17	BF363	40	BF459	30	BU221	134
AF181	168	BC118	13	BC171	10	BC642	65	BD144	136	BF115	29	BF199	18	BF422	34	BF459	30	BU222	134
				BC172	13	BC643	65	BD150A	40	BF121	21	BF200	27	BF423	34	BU110	294	OC76	75

THYRISTORS, SILICON SWITCHES, DIACS

part	part	part	part
BF142	35	BT109	116
BF143	33	BT110	116
BR100	19	BT116	116
BR101	30	BT119	295
BRC4443	72	BT120	199
BRV39	39	CI06D	46
BT106	116	OT112	120
BT108	130	TIC46	39

BRIDGE RECTIFIERS

part	part	part	part
B40	54	KB501	74
BY154	40	W02	29
BY179	156	W04	27
BYW24	232	W06	35
BYW61	305	BR1	26
BYW62	317	BR2	37
BYW64	397	BR3	43
ITT3CD	38	BR4	42

DIODES AND RECTIFIERS

part	part	part	part
AA112	12	BA115	11
AA116	14	BA145	16
AA117	13	BA155	11
AA119	06	BA156	09
AA143	10	BA202	09
AA144	07	BA219	08
AY102	154	BA316	20
AY106	141	BA317	20
BA102	33	BAX13	04
BAX16	05	BY126	10
BY207	20	BY127	10
BY210/400	21	BY133	12
BY210/800	29	BY176	124
BY227	28	BY251	20
BY251	20	BY252	20
BY255	24	BY258	24
BY258	24	BY259	24
BY298	40	BY299	40
BY299	40	BY299	40
BYX10	14	IN4007	07
IN4007	07	IN4148	03
IN4448	17	IN4448	17
IN4001	05	IN5401	13
IN4002	05	IN5404	15
IN4003	05	IN5408	16
IN4004	06	IT144	04
IN4005	07	ITT2002	13
IN4006	07		

ZENER DIODES

part	part	part	part
400M BZY88 TYPE	10	Values 2.4V - 62V	
1W BZX61 TYPE	13	Values 3.3V - 200V	
10W (STUD MOUNTING)	1.28	Values 4.7V - 200V	

INTEGRATED CIRCUITS

part	part	part	part
BRCM200	334	SN72733L	168
BRCM300	342	SN76003N	140
BRC1330	80	SN76013N	110
BT1782	5.21	SN76013ND	105
BT17801B	1.97	SN76023N	130
CS500	2.67	SN76023ND	105
CA270AE	2.85	SN76033N	140
CA270BI	2.70	SN76110N	160
CA505	1.30	SN76226ND	179
CA758E	3.40	SN76227N	108
CA920AE	1.96	SN76228N	186
CA2121	1.80	SN76530P	147
CA3099E	3.40	SN76532N	138
CA3090D	1.45	SN76533N	150
ET15016	2.10	SN76544N	140
ET176016	2.10	SN76546N	2.89
LM1351	1.58	SN7666E	1.27
LM1370	1.78	TA450A	189
MC1310P	1.69	TA450B	27
MC1310P	1.11	TA450C	27
MC1527A	2.67	TA450D	27
MC1527P	1.20	TA4570	180
MC1310P	66	TA4591	198
MC1349P	1.99	TA4611B	248
MC1351P	1.20	TA4610S	340
MC1352P	1.20	TA4661B	180
MC1358P	1.20	TA4700	230
MC1724CP	1.36	TA4721	129
ML237B	1.97	TA420A	460
SA4570	1.98	TA4325	157
SA4700	3.91	TA4395	185
SA5605	1.75	TA4396	160
SA5705	1.75	TA4400	333
SA5800	2.25	TA440N	3.33
SA5900	2.45	TA4500	3.33
SA5960	3.41	TA4500	1.65
SA5670	3.41	TA4510	1.65
SC9503P	1.00	TA4520	1.95
SC9504P	1.45	TA4530	1.23
SC9506P	2.69	TA4540	1.24
SL437F	5.99	TA4550	1.80
SL901B	4.60	TA4560C	2.00
SL917B	5.95	TA4570	1.50
SL918A	4.56	TA45A12	1.65
SN16848N	1.99	TA45B11	2.70
SN16851N	1.99	TA4618X1	2.95

EHT MULTIPLIER TRAYS

part	part	part	part
TCE1400 (5 Stick)	3.08	TCE3000 3500	5.55
TCE1500 (3 Stick)	2.47	TCE 4000	5.20
TCE1500 (5 Stick)	3.08	TCE 8000	2.76
ITT CVC 5.7 B & 9	4.80	TCE 8500	5.50
ITT CVC 20.30	5.40	TCE 9000	6.35
GEC 2028 1040	4.80	RR1 Dual Standard CTV	6.50
GEC 2110	4.80	RR1 A823	5.70
GEC 2100	5.95	RR1 A823B	4.85
GEC 2200	4.80	RR1 219	4.80
PYE 691 693	4.49	GRUNDIG 5010/6010/HA0	4.95
PYE 731 (4 lead)	4.90	GRUNDIG 3000	4.95
PYE 731 (5 lead)	4.85	KORTING	4.95
PYE 713 15 17	5.50	SIEMENS TVK31 51Z	4.75
PHILIPS 520.540.550	4.80	SABA/TFK SITA/DORIC	4.75
PHILIPS 550 (long lead)	4.80	TANBERG TV2, TVC MG	4.95
PHILIPS 69	4.80	EUROTRAY	4.65
DECCA CS1730 1830	3.65	CONVERSION BRACKET A	25
DECCA CS2030.2230 etc.	4.80	CONVERSION BRACKET B	25
DECCA CS1910 2213	4.80	TV18EHT STICK	92
DECCA 80100 Teletex	5.20		

VARIAC TUNERS, DELAY LINES, CRYSTALS, etc.

part	part	part	part
ELC 1043 05	7.40	ELC 1043 06	7.40
U321 (Philips G11)	7.00	Delay line DL50	2.00
Delay line DL60	3.00	Delay line DL60	3.00
Luminance Delay Line For TBA560	1.50	Transducer AT4041/37	1.68
Linearity Coil AT4047/02	1.00	Linearity Coil AT4042/04	1.00
Colour Crystal 4.433619 MHz	1.18	Focus Resistor (Thick Film)	80
10M, 30M, 47M			

TEST EQUIPMENT

part	part	part	part
POWER SUPPLY 0.30V		0 1A PS301	48.50
POWER SUPPLY 5-18V		0 2A PS302	48.50
POCKET SIGNAL INJECTOR (Requires U7 Type Battery)	1.90		

REPLACEMENT DROPPERS

part	part	part	part
PHILIPS GB	45	PHILIPS GB (47R)	35
PHILIPS 210	54	TCE 1500	78
GEC 2018	58	RR1 640	51
RR1 640	51	TCE 8000A	57
TCE 8000A	57	DECCA 70	1.03
DECCA 70	1.03	PYE 73	96
PYE 73	96	TCE 1400	81
TCE 1400	81	RR1 A823	70
RR1 A823	70	GEC 2110 (41R)	41
GEC 2110 (41R)	41	GEC 2110 (2R5 - 12R5)	47
GEC 2110 (2R5 - 12R5)	47	TCE 3500	65

REPLACEMENT COLOUR TUBES

part	part	part	part
17" A44 271X 90°	32.50	25" A83 200X 90°	37.00
18" A47 342X 90°	32.50	26" A86 120X 90°	37.00
19" A49 11X 90°	32.50	26" A86 140X	

T.V. REPLACEMENT CAPACITORS PLASTIC FILM CAPACITORS

250v AC Mains filter type. To meet the requirements of BS 2135 (Class X suppression applications) Life tested at 375v AC at 85 deg. C.

0.047mfd	35p	0.1mfd	40p
0.33mfd	55p	1.0mfd (three wire type)	60p

1000v. DC. General purpose type. Metallised polypropylene, encapsulated. Axial leads.

0.047mfd	27p	0.1mfd	34p
0.22mfd	46p	0.47mfd	62p

2kV Peak Flyback capacitors. Encapsulated, with axial leads.

1500pF	40p	4700pF	40p
5200pF	40p	8200pF	50p

ELECTROLYTIC CAPACITORS

Solder Tag and P.C. Type

800mfd 250v.	G8	150p
800mfd 300v.	G8	182p
800mfd 300v.	GEC	175p
800mfd 300v.	A823	162p
800mfd 300v.	Z179	160p
800mfd 300v.	G9	160p
400mfd 350v.	8000	154p
470mfd 250v.	G11	132p
800mfd 250v.	G9	167p
200 + 300mfd 350v.	891	205p
300 + 300mfd 300v.	A640	190p
400 + 400mfd 350v.	Decca	280p
150 + 150 + 100mfd 300v.	1500	160p
175 + 100 + 100mfd 400/350v.	3500	204p
200 + 400 + 50mfd 325v.	A816	230p
200 + 200 + 150 + 50mfd 300v.	GEC	200p
300 + 300 + 100 + 32 + 32mfd 300v.	Z148	243p
300 + 300 + 300 + 150 + 100 + 50mfd 325v.	GEC	300p
1000mfd 63v.	3500	62p
2200mfd 63v.	G9	95p
1250mfd 50v.	169	60p
4700mfd 25v.	1590	73p
1000 + 1000mfd 40v.	Pye	82p
1000 + 2000mfd 35v.	GEC	97p
2500 + 2500mfd 30v. (PC)	A823	107p

The above prices are for single items. Quantity discounts allowed.
CASH WITH ORDER PLEASE!

All the above prices include postage and VAT at 15%.

P.E. WHITE 22 York Road, Camberley,
Surrey. GU 15 4HR.

TELEVISION ELECTRONIC DISTRIBUTION (SPARES) LTD.

412a Hanworth Road, Hounslow, Middlesex
Telephone: 01-572 4668

PANEL REPAIR/EXCHANGE SERVICE TRADE ONLY

BERRYVISION 510

EMO

THORN 2000 Series, 3000/3500 Series,
8000/8500/8800/9000 Series.

GEC Solid State 2110 Series.

PHILIPS G8 G9

RBM A802/823 AV (Ultrasonic)

DECCA Solid State 80 Series/Hybrid 30 Series.

GRUNDIG 5010/6010 GB

PYE 691, 697, 713, 723, 731

SONY 1800UB

TRADE REPAIRS ON ALL SONY COLOUR T.V.'s
VERY COMPETITIVE PRICES.

3 MONTHS WARRANTY ON PANELS FROM
DATE OF OUR INVOICE.

DISCOUNT FOR BULK PANEL ORDERS.
CATALOGUE AVAILABLE ON REQUEST.

SOUTHERN IRELAND DEALERS

We are the largest stockists in the south of Ireland
of clean used T.V. sets.

**PYE - BUSH - PHILIPS - FERGUSON - KORTING
DECCA ETC.**

UHF/VHF Mono from **£18.00** each

Colour from **£125**

All Sets Tested & Cabinets Polished.

Over 2,000 sets in stock.

Visit our warehouse and see for yourself.

Delivery can be arranged.

T.V. WHOLESALE DISTRIBUTORS LTD.

**E.D.I. House, Kylemore Park West Industrial Estate,
Dublin 10. Tel. 364139 or 791995.**

Irish stockists for the new 'Tyne' colour sets.

PLEASE MENTION

TELEVISION

WHEN REPLYING
TO ADVERTISERS

EX RENTAL COLOUR TV's. THE BEST DEAL IN LONDON

OVER 2,000 in STOCK. MANY WORKING.

THORN BUSH DECCA PYE GEC PHILIPS KORTING GRUNDIG

Delivery arranged ★ Working sets available ★ Complete lorry loads available

★ Excellent stocks of Mono ★ Export our speciality.

Low, Low prices for genuine trade buyers, call and see for yourself, we would like to meet you
or phone 01-997 8833/2298

Colin Butler TV Wholesale, Servier House, Horsenden Lane South, Perivale, Middx.
(New industrial estate behind Perivale underground station)

Manufacturers Surplus Components FIT THE RIGHT PART

300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt resistors £1.50
 150 mixed 1 and 2 watt resistors £1.50
 300 mixed **Capacitors**, improved pack, most types £3.75
 100 mixed **Electrolytics** £2.20
 300 mixed **Printed Circuit** mounting **Components** for various TVs, resistors, caps etc. £1.50
 300 printed circuit **Resistors** $\frac{1}{2}$ to 4 watt £1.00
 100 **High Wattage** TV resistors, **Wirewound** etc. £2.75
 100 mixed miniature Ceramic and Plate Caps £1.50
 100 mixed polystyrene capacitors £2.20
 25 mixed **Pots and Presets** £1.20
 25 mixed **TV Presets** £1.00
 20 assorted **TV VDRs** and **Thermistors** £1.20
 10 assorted **TV Convergence Pots** £1.00
 20 assorted **TV knobs**, includes push button, chrome, control types etc. Mostly Thorn and ITT £1.00
 10 assorted **Valve Bases**, B9A, ceramic, EHT, etc. £1.00
 20 assorted **Sync Diodes** blocks for various TVs £1.00
 25 assorted **Pulse Caps** high voltage £1.25
 10 **Spark Gaps** £1.00
 20 assorted **Zener Diodes** 1 watt and 400MW £1.50
 100 **Mixed Diodes**, includes zener, power, bridge, varicap, germanium, silicon etc. All full spec. £4.95

NEW
 4-433 C.T.V. Crystals
 Long Leads £1.00 each
 3 for £2.50

New Improved Transistor Packs
 100 **New and Marked Transistors** including. BC148, BC154, BF274, BC212L, BF200 and lots of others only £4.95

200 Transistors as above and including 2N3055, AC128, BD131, BFY50, BC238, BC184L only £9.95

Why Buy Expensive Triplers?
 Repair your old 5 and 3 sticks at a **Fraction of the Cost.**
 10 Replacement Rectifier Sticks (Thorn). £1.00

Special TV Bargain Parcels
 Lots of useful parts including damaged panels, tuners, components etc. 10lb for £7.50
Hardware Pack
 Includes BA nuts and bolts, nylon, posidrive, self-tapping "P" clips, cable markers, clamps, fuse holders etc. £1 per lb.

THORN SURPLUS

8500 LOPT. windings £3 pair
 3500 Series **Scan Coils**, new and boxed, complete with convergence yoke, purity assembly, static controls, leads and sockets £5.25
 3500 **Focus** units with metrosil £1.50
 3500 "625" line **VHF Kit** for wired systems £9.50
 4 **Knobs** black with chrome caps to fit ITT, Thorn, GEC and most small diam. shafts 60p per set
 950 rotary transistor tuner with leads and slow motion drive £3.00
 950 bottom panel complete with i.f.'s switch etc. £3.00
 950 line transformer (not Jellypot) £2.50
Convergence Pots with knobs. 5 Ω , 10 Ω , 20 Ω , 30 Ω . 8 of 1 type £1.00. 8 of each £3.50

SAVE THAT TUBE.
 Fit our **C.R.T. Isolating Transformer**. Ideal for HTR./Cath. Shorts. 200-220-240 inputs. 750-900 MA outputs with thermal cutout. Made for **Thorn 4000 C.T.V.** but works O.K. on other sets. £2.00 each 3 for £5.00

MISCELLANEOUS

Philips G8 Tube Base Panels
 Complete, but PCB's cracked, ok for spares. Focus, base leads, plugs etc. 2 for £1

Bush CTV 25 Quadrupler Remo type Q25B. equiv. to ITT. TU25 30K. with mounting brackets. £4.25 each. 3 for £10

GEC single standard, hybrid chassis. convergence panel. Brand new, complete with plugs and leads £2.50

Focus unit with lead, for above chassis £1.50

ITT Featherlight Super. Side Chassis, with controls. V. Cap Tuning Panel, Regulator, P/Button Switches, Bridge Rec. etc., etc. £4.95
 I.C. for above £1.00

SPECIAL OFFER

GEC transistor rotary tuners with slow drive, AE Skt. and leads **2010** Series £2.50

KB VC3 VHF tuner with valves £1.50

KB VC3 transistor tuner "UHF" £1.50

ITT VC200 transistor tuner (Philips type) £1.50

ITT CVC5 power panel. New but five resistors never fitted £1.50

Pye 697 line and power panels, damaged or some bits missing but invaluable for spares £2.00

Pye mono mains droppers with fusible link. 147 Ω + 260 Ω 50p 3 for £1.00
 69 Ω + 161 Ω 50p 3 for £1.00

Decca "Bradford" C.T.V. triplers 25KV £3.00 each 4 for £10

Portable TV EHT Sticks "Siemens TV 18 KV". Fit most portables 50p each 3 for £1.00

Pye 18" CT200 V. Cap P/B Assembly with leads and plug £1.20

EMO. On/off switch £1.00

G.E.C. S/S Hybrid Focus Assembly with lead £1.50

2 x **Coax Sockets** on plates suitable for various Continental T.V.s 50p

White Ceramic TV Resistors 20 Ω 16W, 180 Ω 11W, 13 Ω 11W. 10 of any one type £1.20
 10 of each type £3.00

2-2k fusible, vertical mounting **Screen Feed** resistors 9 watt 8 for £1.00

0-47 Ω $\frac{1}{2}$ watt emitter resistors 40 for £1.00

10 μ F 400V modern Small Type 8 for £1.00

4.7 μ F 63V 20 for £1.00

1000 μ F 16V 10 for £1.00

Bias Caps 330 μ F 25V 10 for £1.00

470 μ F 25V 10 for £1.00

4,500 μ F 35V cans 80p each

Avoid Lethal Shocks
 Buy our specially designed **EHT Probe**, removes high voltage charges from tubes, caps, etc. Heavily insulated with lead and earth connector 60p each

B9A P.C. valve bases 20 for £1.00

EY87/DY87 EHT bases 10 for £1.00

PL509/PY500 ceramic bases 10 for £1.00

C.T.V. Tube bases 5 for £1.00

20mm Antisurge Fuses. 800MA, 1A, 1.25A, 1.6A, 12 for £1.00

2A, 2.5A, 3-15A 100 for £7.00

TH1 thermistors 6 for £1.00

TH3 thermistors 10 for £1.50

Aluminium **Coax Plugs** 8 for £1.00

Metal Coax Couplers 8 for £1.00

200V 1A Diodes 10D2 (equivalent to 1N4003) 20 for £1.00

Miniature "Terry" clips ideal for screwdrivers and small tools etc. 40 for £1.00

Low profile 14 pin quill **I.C. Sockets** (to fit most "Q" series I.C.) 12 for £1.00

Cassette Motors self regulating, 9V, make unknown type 9FM 90p

Rediffusion/Doric Mk 13 5 stick Triplers can be modified for other sets £1.00

Portable T.V. Batt. Leads with Croc Clips and flat 2 pin socket £1.20

Miniature Level/Batt. Meters as fitted to many cassette recorders 90p

LOUDSPEAKERS

2 $\frac{1}{4}$ " Round 8 Ω 70p
 2 $\frac{1}{4}$ " Round 20 Ω 90p
 2 $\frac{1}{2}$ " Round 8 Ω 80p
 6" x 4" Elliptical 8 Ω £1.25
 5" x 3" Elliptical 12.5 Ω £1.00
 4 $\frac{1}{4}$ " x 2 $\frac{3}{4}$ " Elliptical 8 Ω for R.B.M. Mono T.V. £1.30

ZENERS

400MW. 4.3V, 4.7, 6.8, 7.5, 30V 10 of one type 80p
 10 of each type £3.00
 1-3W. 12V, 13V, 18V. 10 of one type £1.00
 10 of each type £2.50
 6 for £1.00

DIACS BR100

STABILIZERS

TAA550 4 for £1.00

GEN. PURPOSE DIODES

IN4000 30 for £1.00 IN4003/10D2 20 for £1.00
 IN4002 25 for £1.00 IN4148 20 for £1.00

ULTRASONIC TRANSDUCERS

Transmitter and receiver. 40 kHz 14 mm diam. £4.25 pair

PROTECT YOUR PROPERTY

Buy a "SENTINEL" **Smoke and Gas Detector**. Uses TGS105 plug in sensor, housed in 3 $\frac{1}{2}$ " diameter diecast box. 24V. Convertible to 12V. Will activate lamp or relay.

With Data and Circuit £16.95

Suitable 24V Relay £1.00

De Luxe Fibre Glass Printed Circuit Etching kits
 Includes 150 sq. ins. copper clad F/G. board. 1 lb ferric chloride 1 dalo etch resist pen. Abrasive cleaner. Etch tray plus instructions.
Special Price £4.95.
 1 lb F.E. C1 To mil. spec. £1.25
 5 lb F.E. C1. To mil. spec. £5.00
 150 sq. in. **Single sided** board £2.00
 150 sq. in. **Double sided** board £3.00

500 Watt Dimmer Switch
 Toroidal mains suppression, fused with satin aluminium knob, white.

ONLY £3.45.

Send **40p P. & P.** on all above items; send Cheque or P.O. with order to:-

SENTINEL SUPPLY DEPT. TV

149a Brookmill Rd., Deptford, London SE8

(Mail Order address only. Callers by appointment)
 Trade enquiries for quantity welcome.

Surplus stocks purchased for cash.

TV'S TV'S TV'S

THOUSANDS OF MONO TV'S IN STOCK

All makes - all sizes from £1.15. Square screens from £6.90. Clearance of 25" D/STD CTV'S (Philips 500 and GEC 2028 only). Checked complete £16.10 each, add £8 p/pkg. Earlier model S/STD (Philips 511, GEC 2040, Pye Hybrid etc) Singles tested tube & checked complete £39.10.

Quantities from £27.60 each
Singles working £48.30 each
Add £6 p/pkg

More recent S/STD CTV'S always in stock (Pye Varicaps, Bush Integrated, Thorn 3500/8000, Decca Bradford, GEC 2100, Korting, Grundig, Luxor, Japanese etc). Sold with tube tested from £46, working from £64.40.

Ring for quotations

EX-TV SPARES

RANK BUSH MURPHY 184 SERIES ETC

Decoder (Single IC) or Line Board £13.80
I.F. Panel or Power Panel £9.20
Convergence Panel £6.90
Tuners £6.90
Complete EHT Stack £20.70

GEC HYBRID 2040/1 SERIES AND PYE HYBRID CHASSIS

Decoder or DCA (Inc. Valves) £13.80
I.F. Panel or Convergence Panel £9.20
Line Panel £16.10
Tuners £6.90

PHILIPS 511

I.F. Panel £9.20
Tuners £6.90
Lopt £9.20

Any above add £1.60 postage & packing
RING FOR QUOTATIONS ON OTHER SPARES

COLOUR TUBES

(fully tested)
25" £18.40
19" £20.70
22" £25.30
26" £29.90
Plus £4.00 p/pkg.

MONO PANELS/TUNERS

Most types £3.45
£1 p/pkg.

VEGA MONOCHROME TUBES

(Brand new USSR Manufacture in Maker's Box with 12 months Guarantee)
20" Size £15.53
24" Size £17.83
Add £2.50 p/pkg.
Discounts for orders over five.

MULLARD COLOUREX/MAZDA NEW LIFE TUBE REBUILDS

(Callers only)
One year guarantee.
Any size only £30.65 plus old glass.

SPECIAL OFFER

20"/24" Single/STD PYE/EKCO/PHILIPS TYPE 230 (Plastic back) Re-furnished with good cabinet and brand new USSR tube (12 month guarantee).
20" Model £32.20
24" Model £34.50
Add £4.00 p/pkg.

ALL PRICES ARE INCLUSIVE OF VAT.

TRITEL GROUP

NORTHERN

Therbury
Roundabout
Leeds Road
Bradford 3.
Tel: (0274) 665670

SCOTLAND

Peacock Cross
Industrial Estate,
Burnbank Road
Hamilton.
Tel: (0698) 282141

LONDON

Kingsley House
Off Avonmore Rd.
(Opp Olympia)
Hammermith Rd.
LONDON W14.
Tel: (01) 602 2982

LONDON

395/397 Albany Road
Off Walworth Road
LONDON SE5
Tel: (01) 703 4040

WEST

Unit 4a
Bulwark Industrial
Estate, Chopetow,
Nr. Bristol.
Tel: Chopetow
(02912) 8652

MIDLAND

48/52 Parshore
Street,
Birmingham 5.
Tel: (021) 622 1023

SOUTHERN

Wading Street
Hockcliffe, North
Dunstable (on A5)
Tel:
Leighton Buzzard
(0525) 210768

MAIL ORDER SEND CWO (CHEQUES OR UNCROSSED PO'S) TO ANY BRANCH

EX-EQUIPMENT SPARES (NONE CHEAPER)

Valves - Colour and Mono

PCL82	£0.08	PCF802	£0.10	PCC86	£0.08	EY86/7	£0.08
PCL83	£0.20	PCF805	£0.20	PC97	£0.18	EY8/7	£0.08
PCL84	£0.08	PCF806	£0.08	PC900	£0.08	DY802	£0.08
PCL85	£0.08	PCF808	£0.08	EF80	£0.08	PY890/1	£0.08
PCL86	£0.08	PCF80	£0.08	EF85	£0.08	PL36	£0.08
PFL200	£0.08	PCC189	£0.08	EF183	£0.08	PL504	£0.20
PCF801	£0.08	PCC86	£0.08	EF184	£0.08	PL1	£0.08
30C1	£0.08	30C15	£0.08	8BW7	£0.08	8/30L2	£0.08
30C17	£0.08	30C18	£0.20	ECC86	£0.08	U26	£0.08
PL83	£0.08	PL84	£0.08	EH80	£0.08	30PL1	£0.25
30PL13/4	£0.08	30P12	£0.08	30FL1/2	£0.20	ECC82	£0.08
ECC81	£0.08	ECH81	£0.08	ECL80	£0.08	ECL82	£0.08
PL509	£0.95	PY500	£0.95	GY501	£0.95	PL508	£0.48
PCH200	£0.48	PCF200	£0.48				

PLEASE NOTE - 25p Postage and Packing

SPEAKERS

£0.75 each

State oval or round with order.
Postage and Packing £0.25

COLOUR TUBES

(FULLY TESTED)

19" £17.00
19" A49/192 £18.00
20" £18.00
22" £20.00

Plus Postage/Packing
£8.00 per tube

MAIL ORDER COLOUR TELEVISIONS

(GOOD WORKING ORDER)

GEC	19"	£55.00	22"	£80.00	Postage/Packing Per set G.B. £8.00
BUSH	19"	£70.00	22"	£75.00	Ireland £15.00

OTHER MAKES AND MODELS AVAILABLE - All prices inclusive of V.A.T.

Cash with order please to:-

Scarborough T.V. Trading Ltd.
Ridings House,
Depot Lane,
Seamer Road,
Scarborough,
North Yorkshire.
Tel. 0723 68087

OR N.W. Electronics (Bfd) Ltd.
Boilingbrooke Buildings,
Boilingbrooke Street,
Bradford 5.
Tel. 0274 390121.

We're giving away

Trade secrets

FOR EX-RENTAL COLOUR AND MONO TELEVISION

West Midlands TV
Trade Sales Ltd.
021-444-6464

92 HIGH STREET
KINGS HEATH
BIRMINGHAM B14 7JZ

★ NOW OPEN ★
New Warehouse at
37-39, Jamaica St.
Bristol.
0272-48266

Why not call in and see us...
A relaxed friendly atmosphere, together with a choice of hundreds of sets at low, low prices. Colour from £15. Mono from £2. Also stands, spares, etc. Send an S.A.E. or phone, for our current price lists and area map showing how to find us. Export enquiries welcome.

N.G.T. COLOUR TUBES

First Independent Rebuilder with

B.S.I. CERTIFICATION

(Certificate No. 004)

12 month's guarantee: 4 year option

Tubes are processed using high temperature pumping schedules giving high definition and long life. They are then fitted with an implosion safety system approved by the British Standards Institution.

N.G.T. ELECTRONICS LTD.,

120, SELHURST ROAD., LONDON S.E.25

Phone: 01-771 3535.

20 years experience in television tube rebuilding.

TELEVISION TUBE SHOP

NEW TUBES AT CUT PRICES

EUROPEAN TYPE Nos.

	Price £	VAT £
A28-14W.....	18.95	2.37
A31-19W/20W.....	19.95	2.49
A31-120W/300W.....	17.95	2.24
A31-410W/510W.....	17.95	2.24
A34-100W.....	18.50	2.31
A38-160W.....	17.50	2.19
A44-120W.....	18.75	2.34
A50-120W.....	17.95	2.24
A59-23W.....	18.95	2.37
A61-120W.....	18.95	2.37

U.S.A./JAP. TYPE Nos.

9AGP4.....	19.50	2.44
190AB4/C4.....	17.50	2.19
230ADB4.....	28.50	3.56
230DB4/CT468.....	24.00	3.00
240AB4A.....	17.95	2.24
CT507.....	17.95	2.24
CT512.....	27.50	3.44
310DGB4/DMB4.....	23.00	2.88
310EUB4.....	19.95	2.49
310EYB4.....	18.75	2.34
310FDB4.....	19.95	2.49
310FXB4.....	17.50	2.19
310GNB4A.....	23.50	2.94
310HCB4.....	23.50	2.94
340AB4.....	19.50	2.44
340AYB4.....	25.25	3.15
340Rb4/CB4.....	24.50	3.06
340AHB4.....	24.50	3.05

Some Rebuilt Japanese & European Types Available at £14.00 + VAT £1.75

COLOUR TUBES (New & Colourex)

12VARP22.....	62.50	7.81
330AB22.....	65.00	8.12
470FUB22B.....	85.00	10.62
A44-271X.....	65.00	8.12
A47-342X.....	69.50	8.89
A47-343X.....	69.50	8.89
A49-191X.....	59.50	7.44
A51-220X.....	64.00	8.00
A56-120X.....	69.50	8.89
A63-120X.....	69.50	8.89
A66-120X.....	75.00	9.37
A66-140X/410X.....	70.50	8.81
A67-120X.....	82.00	10.25
A67-140X/200X.....	69.50	8.89
A67-150X.....	75.00	9.37

ALL TUBES TESTED BEFORE DESPATCH & GUARANTEED FOR 12 MONTHS! 4 YEAR GUARANTEES AVAILABLE ON MOST TYPES

CARRIAGE

Mono £3.00 Colour £4.00
Mainland only. Overseas Rates on Application.

TELEVISION TUBE SHOP LTD.
52 BATTERSEA BRIDGE RD., LONDON, SW11.
Tel. 228 6859/223 5088

PHILIP H. BEARMAN

(VALVE SPECIALISTS)

SUPPLIERS TO H.M. GOVT. Etc.

Closed 12.30-2pm.

NEW valves by Mullard, Mazda, etc, we cannot supply these makes with warranty. (See our lists for explanation). Kindly verify current prices.

"QUALITY" BRANDED VALVES ONLY CARRY THE 90 DAY GUARANTEE. SEE OUR LISTS.

IMMEDIATE POSTAL DESPATCH

LISTS S.A.E.

QUOTED PRICES INCLUDING 0% ALLOWANCE IN LIEU OF GUARANTEE ON EVA VALVES

IMMEDIATE POSTAL DESPATCH		LISTS S.A.E.		PRICES FROM AUG. 1979 INCL. 15% VAT	
DY31 75p	EZ40 & 41 68p	PCF802 £1.05	PL36 £1.26	U25 63p	30P12 73p
DY86/7 78p	GY501 £1.68	PCF805 £1.83	PL84 63p	30P15 P.O.A.	
DY802 84p	PC86 99p	PCF808 £1.83	PL504 £1.57	6F23 63p	30PL14 £1.26
ECC81 78p	PC88 99p	PCH200 £1.31	PL508 £1.62	6F28 £1.05	30PL15 £1.15
ECC82/3 78p	PC97 84p	PCL82 £1.05	PL509 £3.15	20P4 73p	Also 3AT2,
ECL80 75p	PCC84 36p	PCL83 POA	PL802 £3.05	30C1 94p	17DW4A & 40KD6
EF80 69p	PCC89 78p	PCL85 POA	PY81/83 94p	30C17 78p	12HG7, 31JS6A
EF183 84p	PCC189 78p	PCL85 } £1.20	PY800 94p	30FL1 } £1.20	BY 100/127 etc.
EF184 84p	PCF80 99p	PCL85 } £1.20	PY801 94p	30FL2 } £1.20	all 22p each
EH90 68p	PCF86 99p	PCL805 } £1.20	PY500 78p	30L15 } £1.20	with 10W
EY51 89p	PCF200 £1.73	PD500 £3.88	PY500A } £1.83	30L17 } £1.20	resistor.
EY86/7 52p	PCF801 94p	PFL200 £1.68	PY500A } £1.83	30L17 } £1.20	

Our suppliers vary prices, our prices correct at time of going to press ONLY. MINIMUM ORDER 80p!

ENQUIRIES WELCOMED ON OUR VAST RANGE

TELEPHONE ENQUIRIES WELCOMED & ALSO CALLERS

HUNDREDS OF OTHER TYPES AVAILABLE, VAST STOCKS.

See separate Component, CRT and Transistor List. Many obsolete types available. I.R.C. or S.A.E. or International Reply Coupon with enquiries please.

Overseas Post @ Cost. U.K. Post 15p per valve under £25.00 (max. 80p) but 2p extra larger valves/ADDITIONAL VALVES 7p).

SEND SAE FOR COLOUR

TRIPLER LIST (BRC)

ALSO LATEST COMPONENTS LIST.

(Near Sub Post Office)

6 POTTERS RD., NEW BARNET

Production 30PL1 discontinued

STOP PRESS PC92/96, PCL200, PL95, PL519. Also some Television types & EY500A, EL509, EL519.

Herts. Tel: 01/449-1934/5 (Tel. recording service 449/1934 only)

Note: Actual makers of NEW MICRO ALL GROUPS UHF AERIAL (625-) 3" x 1 1/4", amazing results. £3.70 all incl. SAE DETAILED LEAFLET (Tech reports 50p extra)

SOUTHERN VALVE COMPANY

Second Floor, 8 Potters Road, New Barnet, Herts.

Telephone 01-440/8641

Noon to 2 pm excepted

MAIL ORDER ONLY

MINIMUM ORDER 80p

Some leading makes available.

VAT invoices issued on request.

ALL NEW & BOXED, "QUALITY" BRANDED VALVES GUARANTEED 3 MONTHS. BVA ETC. ARE OFTEN AVAILABLE WITHOUT ANY GUARANTEE (SEE OUR LISTS). QUOTES ON REQUEST.

PROBABLY THE BEST VALUE ANYWHERE

NOTE: We regret some increases, Correct only at time of going to press.

DY86/7 57p	EF86 57p	PC86 84p	PCF802 86p	PL36 £1.26	PY500A £1.89
DY802 57p	EF89 78p	PC88 84p	PCF805 £1.90	PL81A 73p	UBF89 53p
ECC81 63p	EF183 57p	PC97 78p	PCF804 78p	PL82 31p	UCR85 58p
ECC82 66p	EF184 57p	PC90 68p	PCF808 £1.90	PL83 48p	UCH81 63p
ECC83 66p	EH90 63p	PCC84 36p	PCL82 68p	PL84 53p	UCL82 78p
ECC85 58p	EL41 £1.05	PCC85 55p	PCL83 POA	PL500 } £1.26	UCL83 POA
ECH81 58p	EL509 £3.15	PCC89 52p	PCL84 73p	PL504 } £1.26	UF89 58p
ECH84 89p	EM84/87 94p	PCC189 57p	PCL85 } 89p	PL508 £1.78	UL41 99p
ECL80 55p	EY86/7 50p	PCF80 99p	PCL805 } 89p	PL509 £3.20	UL84 94p
ECL82 78p	EY500A £1.68	PCF86 63p	PCL86 89p	PL802 £3.05	UY41 63p
ECL86 75p	EZ80 45p	PCF80 84p	PCL200 £1.51	PY88 94p	UY85 63p
EF80 43p	EZ81 47p	PCF200 £1.68	PD500 £3.88	PY800 73p	U25/26 63p
EF85 47p	GY501 £1.47	PCF801 63p	PFL200 £1.41	PY801 73p	Also 3AT2, 40KD6 etc.

One valve post 15p, each extra valve 6p. MAX 80p LISTS & ENQUIRIES. S.A.E. PLEASE! (OR INTERNATIONAL REPLY COUPON) Large valves 2p extra. VAT INCLUDED IN PRICES NO CALLERS AGENTS NEW UHF "MICRO" AERIAL! Only 3" x 1 1/4". WIDE BAND. PRICE £3.70 INCL. POST & VAT. (625 UHF).

EMO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES ETC., ETC. ● ALL SPARES READILY AVAILABLE ● REBUILT TUBES CREDIT AVAILABLE - TRADE ONLY

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc. NEW - COMBI LOPTX NOW AVAILABLE.

YOU CAN BE 95% SURE WE CAN SUPPLY ANY TV COMPONENT BY RETURN IF YOU NEED SPARES FAST - RING NOW!

ACCESS AND BARCLAYCARD ACCEPTED.

S.A.E. FOR FREE SERVICE CATALOGUE.

TELE-PORT (WTON) THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 773121

PHILIP H. BEARMAN

NEW MONO TUBES. Usually 2 Year Guarantee. Tested prior sale. BUY NOW - PRICES MUST INCREASE SHORTLY.

A31/410W Mullard	£18.90
A31/120 - CME1220	(A31/300)*
A34/100 - CME1420	£20.50*
A38/160 - CME1520	£20.00*
A44/120WR - CME1713	£20.50*
A50/120WR - CME2013	£18.90*
A61/120WR - CME2413	£22.10*

Note* less £1 for 1 year guarantee.

A31/510W 8A34/570W. POA.

COLOUR TUBES. Prices on application. SAE all enquiries please!

Prices correct at time of going to press but subject to alteration without notice.

Telephone enquiries welcome. 19", 20" £63; 22" £73 £10 allowance old CRT. (Subject acceptability)

6 POTTERS ROAD, NEW BARNET, HERTS. Tel: 01-449 1934/5. (Answering machine 1934 only)


PRICES INCLUDE 15% VAT. (Callers welcome)

MAKES INCLUDE TOSHIBA, HITACHI, VEGA, MAZDA, BRIMAR & MULLARD. CARRIAGE £2.50 (Mainland); £3.50 colour; £1.75 for EXTRA Short Sea Journey. Eire Extra. NEW STOCKS ARRIVING REGULARLY. BRAND NEW! Also A59, 15W, £11.55. MULLARD A48-26WR £17.00! MULLARD. TUNGSRAM available SHORTLY.

All Mullard 2 year (NOT 1 year) GUARANTEE. (UNREPEATABLE AT THESE PRICES!)

NOTE - JUST ARRIVED - NEW MAZDA A47-13W £15.75 (limited stocks)

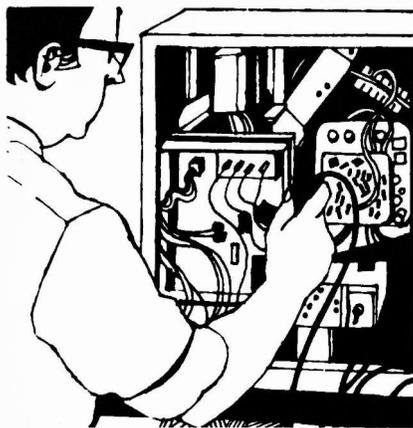COLOUR TUBES. Prices on application. SAE all enquiries please!



SETS & COMPONENTS

RE-BUILT COLOUR TUBES

19" £29.50 MONO 20" £30.50
 22" £32.50 20" 24" 25" £34.50
 26" £38.50 £16

One Year Guarantee.

MATRIX TV LTD.,

112 Essex Road, London N1. Tel: 226 1111

ANOTHER FIRST

from

LEDCo

THE PANEL PEOPLE

Specialists in the design, manufacture and servicing of TV panels

Module 915: A state of the art replacement for the IF Filter/Gain Module used in the Philips 570 & Pye 713-725-735 and similar chassis. **£11.45** each

Solid State CDA Panel

for Pye Hybrid **£21.50**

Solid State PL802 **£2.45**

LP1162 Equivalent **£6.60**

As featured in June issue of this magazine.

Prices include VAT & Carriage Discounts for five or more.

Send for details of these and our TV panel repair service.

LEDCo. 189a Livingstone Road, Thornton Heath, Surrey CR4 8JZ
 Tel. 01-653 7575

COLOUR TV's

Many working for disposal, trade only. All sizes and makes available. Mono sets also available.

Ingartone (London)

24 Dames Road, Forest Gate, London E7. Tel: 01-555 5569

Ingartone (Bristol)

28 St. Thomas St., Bristol 1. Tel: 0272 211179

SMALL ADS

The prepaid rate for classified advertisements is 21p per word (minimum 12 words), box number 60p extra. Semi-display setting £4.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

CONDITIONS OF ACCEPTANCE OF CLASSIFIED ADVERTISEMENTS

1. Advertisements are accepted subject to the conditions appearing on our current advertisement rate card and on the express understanding that the Advertiser warrants that the advertisement does not contravene any Act of Parliament nor is it an infringement of the British Code of Advertising Practice.
2. The publishers reserve the right to refuse or withdraw any advertisement.
3. Although every care is taken, the Publishers shall not be liable for clerical or printers' errors or their consequences.

VALVE BARGAINS

ANY 1-20p, 5-80p, 10-£1.25, 50-£5.50

ECC82, ECH84, EH90, PFL200, EF80, EF183, EF184, PCF80, PCF802, PCL82, PCL84, PCL85/805, PY81, PY800, PY88, PL36, PL504, 6F28, 30PL14.

COLOUR VALVES 50p EACH

PY500/A, PL508, PL509, PL519.

Postage & Packing 30p, no VAT

VELCO ELECTRONICS

9 Mandeville Terrace, Hawkeshaw, Via Bury, Lancs.

S/S Colour £30, Mono Push Button £3. Plus VAT. Phone Southend 559895. Any time.

TR500 UNIVERSAL T.V. TUBE TESTER

TESTS:—

- ALL COLOUR AND MONO TUBES
- EMISSION (Moving Coil Meter)

PLUS:—

- REACTIVATION
- STABILIZED HEATER AND TEST VOLTAGES
- PROFESSIONAL WORKSHOP OR FIELD INSTRUMENT
- SUPPLIED WITH FULL INSTRUCTIONS AND GUARANTEE

COSTS:—

ONLY £26.62 Incl. VAT

CASH WITH ORDER PLEASE TO

NEW DIMENSION TELEVISION

12 BUXTON ROAD, HEAVILEY, STOCKPORT, CHESHIRE

Send stamped addressed envelope for details.

CALLERS WELCOME

COLOUR PANEL EXCHANGE SERVICE

BRC 3000 - 3500 8000 - 8500
 Philips G8 and GEC 2110 series.

Free delivery in London area on Exchange Panels. Large stock of BRC 3500 series spares. New and S/H BRC Panels for sale. Immediate exchange on repairable panels.

Catalogue available on request.

KAY JAY TV SERVICE

34, Clauson Avenue, Northolt. Phone 864 0350.

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
 194, Acton Lane, London W.4.

REBUILT COLOUR AND MONO TUBES IN

South Wales

All tubes are guaranteed for 12 months. Colour tube guarantee extendable to 4 years.

Colour	Price examples
18", 19"	£31.00
20", 22"	£33.00
25"	£35.00
26"	£36.00

20AX and P.I.L. tube prices available on application.

Mono	Price
20"	£11.00
24"	£12.00

Add V.A.T. @ 15% to all the above prices.

Prices are based on a sound tube for tube exchange.

For further details, contact:

C.R.T. Services

Telephone: Newport (0633) 412112
 And Llanwern 2112

ELECTRONIC COMPONENTS. Send S.A.E. For List. Special Offers monthly. Radnor Supplies, 23 Arbury Road, Nuneaton, Wark's.

TELEVISIONS

LARGE STOCK OF COLOUR & MONO TV'S MOST MAKES AND SCREEN SIZES, WORKERS & NON WORKERS, SUITABLE SALE OR RE-RENT TESTING FACILITIES AVAILABLE, QUANTITY DISCOUNTS.

GENERAL FACTORS

Union Street

(off St. Sepulchre Gate West Doncaster)

0302 - 49583 & 68416

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS,
RECORD PLAYERS, TAPE RECORDERS, ETC.

SERVICE SHEETS £1.00 PLUS S.A.E. SERVICE MANUALS ON REQUEST.

BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

- TVT '78 TRANSISTOR EQUIVALENT & DATA BOOK. (A TO Z). 272 Pages£2.75
- TVT '78 TRANSISTOR EQUIVALENT & DATA BOOK. (2N. 2S. ETC.). 392 Pages£3.80
- NEWNES COLOUR TELEVISIONS SERVICING MANUAL by G. J. King. Vol. 1£7.20
- NEWNES COLOUR TELEVISIONS SERVICING MANUAL by G. J. King. Vol. 2£7.20
- NEWNES COLOUR TELEVISIONS SERVICING MANUAL by G. J. King. Vol. 3£8.60
- COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition£7.30
- COLOUR TELEVISION THEORY by G. H. Hutson£6.80
- LONG DISTANCE TV RECEPTION FOR THE ENTHUSIAST by R. Bunney£1.70
- COLOUR TV WITH REFERENCE TO THE PAL SYSTEM by G. N. Patchett£6.20
- VIDEOTAPE RECORDING: THEORY AND PRACTICE by J. F. Robinson 2nd Edition. £7.80
- TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition£6.10
- BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition£2.65
- BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition£2.65
- CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett£4.00
- SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition£5.35
- TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. Revised Edition£5.95

(SEND LARGE S.A.E. FOR FREE BOOK LISTS)

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.
FROM 1965-66 EDITION UP TO DATE. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 20p POSTAGE PER COPY.
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, R. CONSTRUCTOR, ELECTRONICS TODAY, ELEKTOR.

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. (HALF DAY WEDNESDAY) PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS

TV Mono, Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E.,
except Colour TV and Car Radios. **MAIL ORDER**

State if Circuit will do, if sheets are not in stock. All TV Sheets are full length 24 x 12, not in Bits & Pieces. All other Data full lengths.
Free Fault Finding Chart or TV Catalogue with order. Crossed PO's Returned if Sheets Not in Stock.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882.

SERVICE SHEETS, Radio, TV, etc., 10,000 models.
Catalogue 24p plus SAE with orders/enquiries.
TELRAY, 154 Brook Street, Preston, PR 1 7HP.

SERVICE SHEETS from 50p and S.A.E. Catalogue
25p and S.A.E. Hamilton Radio, 47 Bohemia Road,
St. Leonards, Sussex.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for
insertions. I enclose Cheque/P.O. for £
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME.....
ADDRESS.....
.....

Send to: Classified Advertisement Manager,
TELEVISION
G.M.G., Classified Advertisement Dept., Rm. 2337,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-281 5848.
Rate
21p per word, minimum 12 word, Box No. 80p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

EDUCATIONAL

TELEVISION & VIDEO SYSTEMS SERVICING

15 MONTHS full-time Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO & COLOUR TELEVISION
- CLOSED CIRCUIT TELEVISION
- VIDEO CASSETTE RECORDING
- DIGITAL TECHNIQUES
- TELETEX & TV GAMES

Shortened courses for applicants with suitable electronics background.

Next session starts September 17th.

(Also available 2½ year course in Marine Electronics & Radar for employment as ships Radio Officer.)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept. TT9, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

BETTER JOB! BETTER PAY!

GET QUALIFIED WITH ICS IN: COLOUR & MONO TV SERVICING
COLOUR & MONO TV ENGINEERING
COLOUR & MONO TV MAINTENANCE
PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,

NEW: Self-build radio courses with free kits

Train in your own home, in your own time with ICS, the world's most experienced home study college.

RETURN THIS COUPON TODAY FOR FREE BROCHURE!

ICS Int Correspondence Schools
L284 Intertext House, Stewarts Rd.
London SW8 4UJ. Tel: 01-622 9911

Name

Address

FOR SALE

TEXAS/TIFAX XM11 Teletext Decoder Module plus Keyboard. Perfect working order. £100.00. Luton 598928.

NEW BACK ISSUES of "TELEVISION" available 70p each post free. Open P.O./Cheque returned if not in stock - BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

75 EX-BROADCAST 2 inch VIDEO TAPES (Ampex Type). Mixed Memorex and EMI. Offers. All letters answered. Box No. 149.

CCTV BARGAINS. EMI Camera Type 8. Min. Mains/Batt. Video/RF. £140. Siemens Industrial CCIR System £160. Vidicons £15. Plumb/Cons £25. All articles in Good Used condition. Enquiries after 7 p.m. Tel: 01-855 8892.

SEVERAL SELECTED S/STANDARD B & White T.V.'s. Tested and serviced. For sale or rental. Reasonable offer accepted. Tel. 0332-27460. After 6pm.

TWO MULLARD A65-11W Tubes Brand New Boxed, also Decca Projection Set. Offers. Telephone Worcester 27989.

TV TUBE REBUILDING - for everything from a complete plant to sundry materials, training, electron guns etc. **WESTERN WHYBROW ENGINEERING,** Penzance. (073 676) 2265. DEMONSTRATION PLANT AT LONDON BRANCH.

WANTED

NEW VALVES and CRT's required, PCL805, PL504, PL509, PY500A etc. Cash waiting. Bearman, 6/8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

LADDERS


ALUMINIUM Roof Crawlers. Sizes 12ft.-24ft. Also aluminium ext. up to 62½ft. Leaflet. Ladder Centre (TEL2), Halesfield (1), Telford. Tel: 586644. Callers welcome.

MISCELLANEOUS

C.T.V. Panels Ect lists S.A.E. No Callers. Sole, 37 Stanley St., Ormskirk, Lancs. L39 2DH.

RIGONDA AGENTS. For all spares and repairs. Fast dispatch Trade Services available. 01-476 1928. Star Radio, 272 Barking Road, London E13.

BELLS AND SIRENS

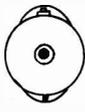

6 to 12v D.C.



12v D.C.

CARTERS SIREN £5.95
INDUSTRIAL SIX INCH BELL £8.95
PRICES INCLUSIVE.
SEND CHEQUE. P.D. to:
CWAS ALARM
 11 Denbrook Walk,
 Bradford BD4 0QS
 SAE for full price list of Professional Burglar Alarm Equipment.

VIDEORECORDER SERVICE and Technical consultancy - B & B Electronics, Newark 76895. Call Steve Beeching.

VIDEO, VCR, and STUDIO SOUND EQUIPMENT REPAIR, conversion and installation. The VIDEO-Workshop Chelsea, Studio 352 3800 Home 603 9649.

NOTICE TO READERS

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

VIEW WELL WITH WELLVIEW TV TUBE REBUILDS

Exchange Mono

	our price	+VAT 15%	total price
CME 1601-1602	£9.30	£1.39	£10.69
A44/120WR	£9.30	£1.39	£10.69
A50/120WR	£9.30	£1.39	£10.69
AW59/23W	£11.00	£1.65	£12.65
A61/120WR	£11.00	£1.65	£12.65

Exchange Colour

	our price	+VAT 15%	total price
A44/270X-271X	£27.00	£4.05	£31.05
A47/342X-343X	£27.00	£4.05	£31.05
A49/120X	£27.00	£4.05	£31.05
A51/110X	£27.00	£4.05	£31.05
A55/14X	£32.00	£4.80	£36.80
A56/120X	£32.00	£4.80	£36.80
A63/120X	£36.00	£5.40	£41.40
A66/120X	£36.00	£5.40	£41.40
A67/120X	£36.00	£5.40	£41.40
A67/200X	£36.00	£5.40	£41.40

18 month full guarantee (Established ten years).

Send cash or cheque together with old tube with your order.

Carriage=£4.50 including VAT

ALSO YOUR VALVE SUPPLIER NEW AND BOXED (inclusive of VAT)

DY802=74p	ECC82=64p	EF183=78p
EF184=64p	PCC89=72p	PCF802=98p
PCL82=78p	PCL84=92p	PCL805=97p
PEL200=£1.15	PCL86=97p	PC504=£1.38
PL509=£2.82	PL519=£2.92	PY88=70p
PY800=70p		PY500Y=£1.52

Postage and Packing 10p per valve. All orders over £10 Free of charge.

WELLVIEW TUBES LTD.,

Unit 7, KING ROAD,
CHARFLEET INDUSTRIAL ESTATE,
CANVEY ISLAND,
ESSEX
TELEPHONE CANVEY ISLAND 65372

COLOUR TUBES STANDARD TUBES METAL BAND TUBES

Rebuilt with new Electron Guns to British Standard 415/1972. Clause 18.2.

SUFFOLK TUBES LIMITED

214, PURLEY WAY
CROYDON, SURREY
01-686 7951

Britain's Largest Independent TV Tube Rebuilder

ELECTRONIC MAILORDER LTD.

VALVE BARGAINS

Any 5-80p, 10-£1.50, 50-£6.00 Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PL504, PY81/800, PY88, 30PL14, 6F28, PFL200.

Colour Valves - PL508, PL509, PL519, PY500/A. All tested. 55p each.

Aerial Splitters: - 2 way, 75 OHMS, Inside Type, £2.50

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11 - For the stereo and standard VHF/FM radio.

B12 - For the older VHF television - Please state channel numbers.

B45 - For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. Price £4.70 each.

STEREO HEADPHONES

Black - Freq. 30-18000HZ.
SAVE ££'s - PRICE £3.50

ALL PRICES INCLUDE VAT P & P 30p PER ORDER. EXPORTS WELCOME AT COST

62 BRIDGE STREET, RAMSBOTTOM,
BURY, LANCS.
TEL: RAMS (070 682) 3036.

CALEY TUBES

17-35 Bangor Road,
Edinburgh EH6 5JY.
031-554 4200.

Callers Welcome.

Rebuilt T.V. tubes from Scotland's oldest established rebuilder, all fitted with top quality gun mounts and hot pumped for maximum life.

COLOUR 2 YEAR GUARANTEE.

12" + 14" + 16" Teleton & Hitachi etc. portable types.	£29.50
18" A47 - 342x, A47 - 343x, 470 DUB 22, 470 DKB 22, 470 EMB 22 etc.	£29.50
18" Toshiba 470 ERB 22 etc. P.I.L.	£37.50
19" A49 - 11x, A49 - 120x, A49 - 191x, A49 - 192x, CTA 1950, CTA 1951, 490 AXB 22, 490 BKB 22 (A+B) 490 BTB 22 (A), 490 BUB 22, 490 CJB 22, 490 CUB 22	£29.50
20" A51 - 110x, A51 - 220x, 510 AEB 22A, 510 ARB 22, 510 AUB 22 (A), 510 BMB 22	£29.50
22" A55 - 14x	£33.00
22" A56 - 120x, A56 - 140x, A56 - 410x	£33.00
22" A56 - 500x etc.	£41.00
25" A63 - 11x, A63 - 120x, A63 - 200x etc.	£37.50
26" A66 - 120x, A66 - 140x, A66 - 410x, A67 - 120x, A67 - 150x, A67 - 200x	£37.50
26" A66 - 500x	£45.50

MONO 2 YEAR GUARANTEE.

All portable thin neck types incl. Japanese.	£14.00
Up to and including 20"	£10.00
23" and 24"	£12.00
Ex equipment 24" A61-120W. Tested as new, guaranteed 3 months.	£8.50

Usually same day despatch or your old tube rebuilt and despatched within 48 hours of receipt.

Please enquire for any type not listed as we can rebuild almost anything including V.D.U. and industrial types.

All prices quoted assume the return of your old envelope in rebuildable condition with your order.

Old CRT and cash or cheque with order. Carriage + packing £2.75 inc VAT anywhere on mainland, or advance replacement by special arrangement.

Please add VAT at 15% to all orders.

VALVES ALL NEW AND BOXED

10C2	50p	10F1	50p	10P14	£1.00
20D1	25p	20F2	25p	20L1	25p
20P4	50p	20F5	50p	30P12	25p
30C15	50p	30L1	25p	PCCB4	25p
PCL83	£1.00	PL83	25p	PY33	25p
U25	50p	U191	25p	U301	50p
U141	50p				

V.A.T. inclusive.

P & P 15p one valve plus 5p per valve.

Price includes 10% discount in lieu of guarantee.

All valves tested before despatch.

DISPLAY ELECTRONICS

COLOUR TUBES MONOCHROME TUBES VDU/RADAR TUBES

REBUILT IN OUR
OWN FACTORY
IN N.W. LONDON

Customers are asked to note that as a result of the continuing high demand for our products we have moved to a new purpose built factory in UXBRIDGE and the old factory at West Drayton is now closed.

The new address is:—

96/100 WATERLOO ROAD,
UXBRIDGE, MIDDX.
TELEPHONE:
UXBRIDGE 55800

COLOUR T.V. SPARES

Most parts of Decca's stocked

LOPT		
DECCA	10/30	£10.80
	80/100	£10.20
	Mono	£12.00
PHILIPS G8		£12.90
ITT	20/25/30	£10.90
BUSH	A774	£15.00

TUNER CONTROL UNITS

DECCA	
4 Button	£6.70
6 Button	£8.90
7 Key	£14.00

Send for catalogue (16p). Hundreds of correct spares listed.

Complete 3000 Models
£79 collected.

Ex-equip panels

3000 - Power £20. LTB £20. F/S
£8.50 Conver. £8.50 IF £10.
Video £12. Chr. £12.

Bradford

10 Decoder £16. 30 Decoder £18.
Prices include 15% VAT

Package/Posting 30p per order but Transformers and Panels 75p.

BOTTOMLEY'S TELEVISION

11 Leeds Road, Hipperholme,
HALIFAX (0422) 202979

Callers Phone first. Exit 26 M62

Ex-equipment panels are complete and working but are sold on condition that they may require attention due to age.

BIRMINGHAM AND DISTRICT DEALERS/ENGINEERS

NEWS FLASH

HIGH VACUUM
QUALITY
REBUILT TELEVISION
PICTURE TUBES

COMPETITIVE PRICES

CONTRACT TERMS
AVAILABLE

2 YEAR GUARANTEE

E.G.		
17" 18" 19"	£29.50 + VAT	£4.43
20"	£32.50 + VAT	£4.86
22"	£34.00 + VAT	£5.10
25"	£37.00 + VAT	£5.55
26"	£40.00 + VAT	£6.00

PIL Tubes our speciality.

All Prices For Tubes available on a Sound "Glass for Glass" basis otherwise £20 surcharge

C.W.O. Carr./Ins. £6.50

"Old Glass Purchased"

TUBESURE LTD.

Unit 111, Middlemore Industrial Estate,
Middlemore Road, Smethwick,
West Midlands. Telephone: 021-558 7777.

3 amp 1½ Fuses 2p	EHT S.Stick 18 or 20KW Triplers (ITT) £1.50 new	EHT Lead & Anode Cap 75p
Long wires	3 amp Diodes approx. voltage 1200V 7p each	Star Aerial Amps £4.00
300 Mixed Carbon Film Resistors	3500 6 push button units for Thorn 3500 Varicap tuning £1.00	Channel B or C
5 of each type ¼ Watt 1R to 2 Meg - ITT £1.50	Varicap F.M. Tuner	2200/35 15p
Red & Green L.E.D.s mixed large and small 14 for £2.00	Tuning range 78.5 to 108MHz £2.00	2000+2000/35 25p
Convergence Panel for GEC 2040 11 pots 5 coils 2 Resistors E.T.C. New £1.50	(I.F. Panel with circuit) £2.00	2500+2500/63V 50p
(Reject Varicap Units) ELC1042/ELC1043 50p	6 position 12.5K V/Resistor Unit for Varicap 50p	4700/25 25p
ELC2000 £1.00	Thorn Mains Lead & ON/OFF switch & Control Panel with Slider Pots 75p	4700/30 35p
10 Watt LP1173 £1.00	TBA 120A 30p	4700/40 50p
IF LP1170 50p	TBA 120B 30p	1250/50 10p
AM/FM T/Unit (Seconds) 50p	TBA 120AS 30p	33/350 6p
AT1025/08 Blue Lateral Ass. 15p	TBA 120SB 30p	100/63 8p
10 Watt Mullard Amps New £2.00		10/350 8p
BD 207 30p		47/50 5p
TIP 31 20p	4.7NF5KV 10p	1500/40 10p
TIP 2955 50p	6200PF/2000V 10p	.005/1500V 5p
2N3583 250V/1A Output Transistor 40p	180PF/8KV 10p	47/100V 8p
BD 252 20p	1000PF/10KV 10p	.05/100 3p
(MJE2021) NPN 80V/5A 15p	1000PF/12KV 10p	4.7/50V 5p
(SJE5451) 15p	1200PF/12KV 10p	4/350 5p
(661 pair 80W/5A pair 28p	270PF/8KV 10p	1000/25 10p
(660 90V 28p	160PF/8KV 10p	4.7/100 6p
40V 2A O.P. Trans B0375/6 pair 20p	.1MFD 400V 5p	2.2/100 6p
BZV 15/12R PYE 50p	.1MFD 800V 8p	1000/10 5p
BD226 25p	.1MFD 2000V 15p	8/350 5p
BD238 25p	.1MFD 1250V 15p	1/250 5p
MJE 1661 25p	.01MFD 600V 5p	1/100 5p
XTALS T/V 4.433.610KHz 50p	.01MFD 1000V 8p	6MHz Filters 25p
BYX 38/600R 50p	.0047/500V 8p	3300/40 15p
BT138 Triacs 10a/600V 65p	.0022 1500V 8p	3300/25 5p
RCA40506 Thyristors 50p	.47 250 A/C 8p	1500/25 10p
MJE 2955/15A 50p	.47 1000V 35p	1/350 5p
TIP 41A-42 pair 40p	.047 1000V 8p	220/10 5p
G11 Phillips Thyristors 60p	.22/250AC 8p	680/100 10p
PYE Thyristors 85p	1500/100V 25p	220/16 5p
2N4444-0T112 BT116 85p	10/500V 15p	47/63 5p
SP8385 Thorn 25p	.47/100V 5p	33/63 5p
5 amp 300V Thyristors 25p	330/25V 5p	2.2/63 5p
BRC 4443 65p	680/40V 8p	22/100 8p
SCR 957 65p	22/350V 7p	4.7/63 5p
BD561-2 pair 30p	330/100V 10p	1000/40 10p
BC 365 10p	15/450V 10p	100/450 30p
BD 131 25p	47/450V 12p	22M 350V 20p
BD 183 50p	470/16V 8p	33.000 20p
AC187-8K pair 40p	470/25V 8p	PUA758PC £1.00
	470/40V 10p	MC1349P 50p
	470/63V 15p	TCEP100 £1.00
	470/100V 15p	TCE120CQ £1.00
	220/25V 6p	
	220/40V 6p	
	220/63V 10p	
	160/25V 5p	
	330/16V 5p	
	100/16V 5p	
	2.2/160V 5p	
	10/40V 5p	
	TBA 920 £1.00	
	TBA 920Q £1.50	
	TBA 480Q £1.00	
	TBA 550Q £1.50	
	TBA 540 £1.00	
	TBA 5400 £1.00	
	TBA 530Q £1.00	
	TBA 990 £1.00	
	SBA 550B £1.50	
	SN76003 £1.00	
	No Heat Sink	
	SN 76003 £1.75	
	SN 76033 £1.50	
	TBA 800 60p	
	TBA 810S £1.00	
	TCA 270 £1.00	
	TCA 270Q £1.00	
	TCA 275Q £1.00	
	CA 270 £1.00	
	TBA 720A £1.50	
	TBA 510Q £1.50	
	SN76115N 50p	
	TAA 700 £2.00	
	TAA 570 £1.50	
	TBA 396 £1.00	
	SAS 570S £1.50	
	SN76666 £1.00	
	SN76660 50p	
	SN76227 50p	
	SN76544N 75p	
	TBA641BX1 £1.50	
	CA920 AW £1.00	
	TBA 750 £1.00	
	TAA 550 20p	
	SN76131N 50p	
	SN76001 £1.00	
	TBA560CQ £1.00	
	SN76530P 50p	
	SN76650N 50p	
	TDA1170 85p	
	BT822 £1.50	
	BT8224 £1.50	

SENDZ COMPONENTS
2 WOODGRANGE CLOSE,
THORPE BAY, ESSEX.
Reg. Office Only.
Callers by appointment only.
Add 15% VAT.
Add postage for all overseas parcels.

100 mixed 20mm Fuses £2.00	100 Mixed Transistors 75p	UHF Varicap Units + VHF	BY 127 10p
3500 Thorn Triplers £3.50	1 Lbs Mixed Components £1.50	NEW	IN4005 4p
Triplers TS2511TDT THORN £2.50	BU 105/04 £1.00	ELC 1043/05 £4.00	IN4006 5p
Triplers TS2511TBQ PYE £1.50	BU 205 £1.00	ELC 1043/06 £4.00	BY210/400 5p
1730 DECCA £1.00	BU 108 £1.00	THORN Varicap UHF 3.500 £3.50	BY210/800 10p
GRUNDIG 3000/3010 SIEMENS TVK52 Triplers £3.00	BU 208 £1.75	New EQV ELC1043/05	BY176 50p
Triplers - DECCA £3.00	BU 500 £1.75	DECCA UHF Varicap New eqv EIC 1043/05 £4.00	BY133 10p
CS 2030 CS 2230	BU 126 £1.00	VHF/UHF AEG Varicap (New) £3.50	BA159 10p
CS 2232 CS 2233	R2008B £2.00	G8 PHILLIPS £3.50	BY184 25p
CS 2630 CS 2631	R2010B £1.25	UHF Varicap replacement	BY187 50p
CS 2632	EHT Rectifier BY212 10p	NEW VHF/UHF on panel ELC2060 £4.50	TV 20 50p
THORN - Needs Mod No 1400 . 1500 Stud Multipliers £1.50	3 OFF G770/HU37 EHT 10p	Phillips T/Units UHF New £2.00	TV 18 40p
Triplers - PHILLIPS 520.540.550 £3.00	12KV 2 M/A Small 20p	VHF/UHF AEG Varicap NSE Removed from new panels £2.50	Rectifier Sticks & lead & Anode Cap
Triplers - ITT CVC5 CVC7 CVC9 CVC20/25/30 CVC8 £3.00	12KV 2 M/A Large 30p	VHF Varicap Units NSF AEG removed from Print Panels £1.00	BYF3214 20KV Rectifier Sticks 25p each
LP1174/33 DECCA LP1194/42 PYE Triplers £4.00	EHT REC USED IN THORN 1400.1500 Triplers (x80/150) 10p	New 49.00 21.900MHz	BYF3123 18KV Wire ends 25p
G2100 GEC Tripler TVM25 £2.00	CSD 118xMH Rec THORN 3500 10p	VHF Varicap (NSF) AEG New 49.00 21.900MHz £2.00	BA 248 6p
THORN 3500 THORN 8500 Focus Unit DECCA 8500 Focus Unit (Large or small) £1.00 each	220M/450V THORN 50p	4 Push Button T/Units UHF MULLARD £2.00	BSS 68 20p
4 Push Button Units 1400-1500 THORN £3.50	700M/250V THORN 35p	AE Isolating Sockets UHF & Lead PYE & THORN 40p	BYX55/350 10p
4 Push Button Unit 8500 THORN £3.50	175+100+100 350V 3500 THORN £1.50	DECCA 1730 Doubler £1.00	BY 206 10p
300 Mixed condensers £1.50	400+400.350V DECCA 80p	Transistor UHF Units with AE Socket and leads GEC 2000 Rotary type NEW £2.00	BT106 S/Type 50p
300 Mixed resistors £1.50	470+470.250V 40p	7 button Varicap tuning heads Variable Resistor with Fascia Plate 7 Lamps £3.00	BT106 95p
30 Pre-Sets £0.50	100+200 325V 40p	PYE 6 push button unit for Varicap Tuning £2.50	BT116 95p
100 W/W Resistors £1.50	200+200+100+32 350V 70p	4 push button unit (for Varicap Tuning) 20K New £0.60	BT119 95p
40 Mixed Pots £1.50	150+200+200.300V 70p	DECCA Bradford Tuner 5 Button New £2.75	BT109 70p
20 Slider Pots £1.50	731 PYE 600/300V & BUSH 75p each	BB 105 UHF 5p each	BT146 750V 25p
10 Different Types	200+200 350V 60p	BA 182 Varicap diodes BTY80 20p	Thyristors 8A/800V 2N6399A 30p
Mixed Electrolytics 150 £2.00	300+300+100/32/32 £1.00	3 amp Diodes 300V 10p	Thyristors 8A/400V 52600D 30p
DP Push Button Switch ON/OFF 10p	400M 400V 40p	3 amp Diodes 100V 7p	Y827 Diodes 30p
Mains ON/OFF Push Button T/V 20p	400M 350V 50p	1 amp Bridges 100V 20p	Bridge Rec
Mains ON/OFF Rotary T/V 12p	800M 250V 30p	1 amp 400V 20p	B30C 600A6 12p
Mains Dropper THORN 6R+1R+100R 35p	AE Power supplys 15V £1.00	3 amp Bridge 25p	B30C 500 12p
Mains Droppers AD 161 AD 162 PAIR 60p	Flush Mounted Diplexer White 2 Coax Sockets T/V F.M. 35p	W005M Bridge 15p	BC147C 2N3566
147+260 PYE 40p	BF 127 BC 303		BC148B BF198
(731) 3R+56R+27R 50p	BF 264 BRC 2108		BC149C BF274
100 Mixed Diodes £1.00	BF 180 BC 336		BC195 BSY79
	BF 181 BF 157		BC108 BC327
	BF 182 BC 161		BC107 BC213LA
	BC 300 BC 460		BF594 BC212LT
	AC 128 BC 350		BC158 BF195
	BF 178 BSY95A		2N2222 BC182L
	BF 257 BFT 43		2N390 BF594
	BF 137 with heat sink		2N4355 BC183
	BF 185 TIP 29A		T1591 BC238A
	BF 200 TIP 32		
	AC 153K 20p each		
	GEC Sound O.P. Panel I.C. O.P. £2.50		

7p each
Add 15% VAT.

SENDZ COMPONENTS

2 WOODGRANGE CLOSE,
THORPE BAY, ESSEX.

Reg. Office Only.
Callers by appointment only.

Add postage for all overseas parcels.