

NOVEMBER 1979

Australia 95c; Malaysia \$2.75; New Zealand 95c

55p

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS

FIELD SERVICING PART I



NI700 VIDEO OUTPUT
SERVICING THE PYE CT200
USING DIGITAL ICs

PHD COMPONENTS
RADIO & TV COMPONENT DISTRIBUTORS
UNIT 7 CENTENARY ESTATE
JEFFRIES RD ENFIELD MIDDX
MAIL ORDER ONLY TELEX 261295

ALL COMPONENTS OFFERED SUBJECT TO AVAILABILITY. WE RESERVE THE RIGHT TO SUBSTITUTE REPLACEMENTS SHOULD THE ORIGINAL PART BE OUT OF STOCK OR UNAVAILABLE!
PLEASE ADD 0.35p per parcel post and packing.

SEMICONDUCTORS

AA113	0.16	BC117	0.20	BU208/02	3.00
AA116	0.16	BC118	0.20	BU326S	1.50
AA117	0.16	BC119	0.50	BU406	2.00
AA119	0.16	BC125	0.20	BU406D	2.50
QA91	0.12	BC126	0.20	BU407	2.00
QA95	0.12	BC136	0.20	BU407D	2.50
QA202	0.18	BC137	0.20	R208B	2.50
BA100	0.18	BC138	0.40	R2010B	2.50
BA102	0.10	BC139	0.40	R2540	3.00
BA130	0.15	BC140	0.40	ME0402	0.20
BA154	0.10	BC143	0.40	ME0412	0.40
BA155	0.12	BC147	0.20	ME4003	0.15
BA164	0.12	BC148	0.10	ME8001	0.20
BA164	0.16	BC149	0.15	MJE2995	1.50
BA164	0.08	BC153	0.15	MJE3005	1.30
BA164	0.16	BC154	0.10	MP8113	1.00
BY206	0.20	BC157	0.15	MPSU05	1.20
IN4148	0.04	BC158	0.15	MPSU55	1.50
BY126	0.15	BC159	0.15	TIP2955	1.30
BY127	0.22	BC160	0.40	TIP3055	1.30
BY133	0.10	BC161	0.40	TIS80M	0.60
BY164	0.50	BC170	0.15	TIS91M	1.20
SKB2.08	1.00	BC171	0.15	2N2904	0.50
BY238	0.15	BC172	0.20	2N2905A	0.50
BYX10	0.18	BC177	0.20	2N2905	0.50
IN4001	0.10	BC178	0.20	2N3053	0.50
IN4002	0.10	BC179	0.20	2N3703	0.20
IN4003	0.12	BC182L	0.15	2N3705	0.20
IN4004	0.12	BC183L	0.15	2N3710	0.20
IN4005	0.12	BC184L	0.15	2N3055H	0.75
IN4006	0.14	BC184LC	0.20	TAA350	0.80
IN4007	0.16	BC186	0.30	TAA550	0.60
IN5407	0.33	BC187	0.30	TAA570	1.80
BR100	0.50	BC203	0.15	TAA611	1.75
BR101	0.60	BC204	0.15	TAA630S	2.00
BR139	0.60	BC205	0.15	TAA661B	2.00
TYC1160N	1.50	BC206	0.15	TN7550M	1.50
BT119	2.50	BC207	0.15	TAD100	2.00
BT120	2.50	BC208	0.15	TBA120AS	0.75
BYX 71 600	0.80	BC209	0.15	TBA231	1.20
2N444	1.50	BC212L	0.15	TBA4800	2.20
TV106 2	1.50	BC213	0.20	TBA5200	2.00
BYX88C2V7	0.10	BC214L	0.15	TBA530	2.00
BZ98 3V0	0.10	BC225	0.40	TBA5300	2.00
BZ98 3V3	0.10	BC237	0.15	TBA540	2.20
BZ98 3V6	0.10	BC238	0.15	TBA540Q	2.20
BZ98 3V9	0.10	BC251A	0.15	TBA550	2.00
BZ98 4V7	0.10	BC301	0.10	TBA550Q	2.00
BZ98 4V7	0.10	BC303	0.50	TBA560C	2.20
BZ98 5V1	0.10	BC307	0.15	TBA560CQ	2.20
BZ98 5V6	0.10	BC308	0.15	TBA570	2.50
BZ98 6V2	0.10	BC327	0.15	TBA570Q	2.50
BZ98 6V8	0.10	BC328	0.15	TBA641B	3.00
BZ98 7V5	0.10	BC337	0.15	TBA641B11	4.00
BZ98 8V2	0.10	BC338	0.15	TBA651	3.00
BZ98 9V1	0.10	BC547	0.15	TBA720A	1.50
BZ98 10V	0.10	BC141 10	0.80	TBA730	1.50
BZ98 11V	0.10	BD115	0.50	TBA750	2.00
BZ98 12V	0.10	BD124	2.00	TBA7500	2.00
BZ98 13V	0.10	BD131	0.70	TBA800	1.00
BZ98 15V	0.10	BD132	0.60	TBA810S	1.50
BZ98 18V	0.10	BD133	0.70	TBA820	1.50
BZ98 20V	0.10	BD134	0.70	TBA920	2.00
BZ98 22V	0.10	BD144	2.50	TBA9200	2.00
BZ98 27V	0.10	BD159	0.80	TBA990	2.00
BZ98 33V	0.10	BD238	0.50	TBA990A	2.00
BZ61 7V5	0.25	BD380	0.70	TC2705A	3.00
BZ61 8V2	0.25	BD441	0.70	TC900	1.00
BZ61 9V1	0.25	BD537	0.70	TC940	2.00
BZ61 10V	0.25	BD538	0.70	TDA1170	2.00
BZ61 11V	0.25	BD507	0.70	TDA1200	3.00
BZ61 12V	0.25	BD508	0.75	TDA1270	3.00
BZ61 13V	0.25	16181	1.20	TDA1412	1.00
BZ61 15V	0.25	16182	1.20	TDA2020	4.00
BZ61 16V	0.25	BD709	1.00	SN76115N	2.00
BZ61 18V	0.25	BD710	1.00	SN76227N	1.20
BZ61 20V	0.25	BD442	0.70	SN76530A	1.00
BZ61 22V	0.25	BD379	0.50	SN76551N	1.50
BZ61 24V	0.25	BF115	0.60	SN76003N	0.60
BZ61 27V	0.25	BF118	0.60	SN76013N	0.60
BZ61 30V	0.25	BF152	0.40	SN76013ND	2.00
BZ61 33V	0.25	BF154	0.40	SN76013ND	2.00
BZ61 36V	0.25	BF157	0.70	SN76023N	1.00
BZ61 39V	0.25	BF158	0.40	SN76023ND	2.00
BZ61 47V	0.25	BF160	0.60	SN76033N	2.00
BZ61 72V	0.25	BF163	0.60	SN76110N	2.00
AC107	0.50	BF167	0.50	SN76228DN	2.00
AC127	0.50	BF173	0.50	SN76227N	1.20
AC127 01	0.60	BF177	0.50	SN76532N	2.00
AC128	0.60	BF179	0.60	SN76533N	2.00
AC128 01	0.60	BF180	0.50	SN76544N	2.00
AC141	0.50	BF181	0.60	SN76654N	1.50
AC141K	0.60	BF182	0.50	SN76655N	1.50
AC142	0.40	BF183	0.50	SN76666N	1.20
AC142K	0.60	BF184	0.50	SL191B	6.00
AC176	0.60	BF185	0.50	SL191B	6.00
AC176 01	0.60	BF189	0.15	TBA336Q	2.00
AC186	0.40	BF195	0.15	TDA440	2.50
AC187	0.40	BF196	0.15	SN76001N	1.50
AC187K	0.60	BF197	0.15	TBA520	2.00
AC188	0.40	BF198	0.15	TBA120S	1.00
AC188K	0.60	BF199	0.15	UA7824	0.50
AD140	1.50	BF200	0.15	TBA396	2.00
AD142	1.50	BF224	0.15	TC2705O	2.00
AD143	1.50	BF240	0.15	TDA2030	8.00
AD145	1.50	BF241	0.15	TDA2140	6.00
AD146	1.00	BF256LC	0.50	TDA2150	6.00
AD161 2	1.50	BF257	0.50	TDA2160	6.00
AD162	0.70	BF258	0.50	TDA1230	6.00
AD262	1.50	BF271	0.60	TDA 3389	2.00
AF114	0.60	BF273	0.25	TDA1054M	2.00
AF115	0.60	BF274	0.25	MC1349P	1.50
AF116	0.60	BF336	0.50	SAA661	0.60
AF117	0.80	BF337	0.50	SAS560S	2.00
AF118	0.60	BF338	0.50	SAS570S	2.00
AF121	0.60	BF350	0.60	SN74000N	0.40
AF125	0.60	BF458	1.00	SN7413N	0.90
AF125	0.60	BF459	1.00	SN74122N	1.00
AF126	0.60	BF473	0.50	SN74141N	1.00
AF127	0.60	BFX29	0.50	TBA396	1.80
AF139	0.60	BFX84	0.50	TBA396Q	1.80
AF139	1.00	BFX88	0.50	TBA950	4.00
AL102	3.00	BFX89	0.50	TC800	4.00
ALU107	3.00	BFY50	0.50	TC800Q	4.00
ALU110	3.00	BFY51	0.50	TDA1180	3.00
ALU113	3.00	BFY52	0.50	TDA1190	3.00
AL103	3.00	BFY90	1.20	TDA2002H	3.60
AY102	3.00	BF381	0.50	TDA25900	5.00
BC107	0.20	BF399	0.30	TDA2600	5.00
BC108	0.20	BF399	0.30	TDA2640	3.00
BC109	0.20	BF381	0.30	TDA2850	3.00
BC113	0.15	BF389	0.15	TAA621 AX1	3.30
BC114	0.15	BF259	0.25	TBA625X5	2.00
BC115	0.20	BDX32	2.50	TC830S	2.00
BC116	0.20	BU206	1.60	TDA2020/ A2	5.00

TDA2020P	5.00
TD2020V	3.60
TD2010/BD2	4.50
TD2002V	5.00
TC940E	3.00

VALVES - ALL VALVES
'MAZDA' BRAND

DY 86/87	1.20
DY902	1.20
ECB2	1.10
ECB4	1.35
ECH83	1.00
ECH84	2.00
ECL80	1.50
ECL82	1.30
ECL86	1.50
EF80	1.20
EF95	0.70
EF183	1.10
EF184	1.10
EL34	3.00
EL84	1.40
GY501	2.40
PC97	1.60
PC900	1.75
PCF80	1.50
PCF802	1.50
PCF806	2.50
PCL82	1.50
PCL84	1.50
PCL86 805	1.50
PCL86	1.50
PD500 510	5.00
PLF200	3.00
PL36	2.00
PL81	2.00
PL504	1.60
PL508	2.40
PL509	3.50
PL519	5.00
PL802	3.00
PY88	1.80
PY800A	2.40
PY800/801	1.40
UCL82	1.60
30FL2 1	1.60
PCF805	1.00
PCF808	1.50

DIRECT REPLACEMENT PARTS

173 Tuner (Repl Eic 1043 05)	8.00
4.443MHz Crystals	2.00
Cut Out TCE 3500	2.00
Cut Out GEC	2.00
Cut Out TCE 8500	2.00
TV18 Rectifier Stick	2.00
TV20 Rectifier Stick	2.00
Va 1104 Thermister	0.60
Transductor TCE 3000	1.00
AEG Tuner (Repl Eic 1043 06)	9.00
Aerial Isolator Kit	1.20
Philips GB Lopt	12.00
PYE 691 697 Lopt	14.00
Bush A 774 Lopt	18.00
Decoder Panel Autovox 2282	10.00
Degaussing Panel Autovox 2282	2.00
Sound O/P Panel Autovox 2282	4.00
FS Panel Autovox 2282	6.00
Comp Control Unit Autovox 2282	2.00
Field TB Panel Autovox 2282	5.00
IF Tuner Assembly Autovox 2282	7.50
TCE 850 Lopt	1.00
TCE 900 Half Wave	0.50
Delaware SDL 141	0.40
Pye 95 Tuner	1.50
GCE 2110 Degauss Panel	1.50


EHT MULTIPLIERS

TCE950 Doubler	2.00
TCE950/1400 Tripler	4.00
TCE1400 (Fixed System Only)	6.00
TCE1500 Doubler	4.00
TCE1500 Tripler	4.50
TCE1600 1/2 Wave	3.00
DECCA CS 1730/1830 Doubler	4.00
DECCA CS 1910/2213 Tripler	5.50
DECCA 30 Series Tripler	6.50
DECCA 80 Series Tripler	8.50
DECCA 100 Series Tripler	6.50
GEC Hybrid 2028 Tripler	6.50
GEC 2110 Tripler PRE JAN77	7.00
GEC 2110 Tripler Post JAN77	6.50
ITT CVC 5 8/9 Tripler	6.50
ITT CVC 20 25 30	6.50
Philips 520 Tripler	6.50
Philips 550 Tripler	6.50
Philips G9 Tripler	6.50
PYE 691/693/697 Tripler	5.50
PYE 731/725 Tripler	6.50
RRI 2179 823	6.50
TCE 3000/3500 Tripler	7.00
TCE 4000 Tripler	8.00
TCE 8000 Doubler	3.00
TCE 8000 Tripler	6.00
TCE 9000 Tripler	7.00
TVK 76 13 Continental Sets	5.00
TVK 52 ITT Replacement	6.50
Korting 90% Tripler	6.50
Autovox 2282 Tripler	6.50
Rediffusion MK 1 Tripler	8.00
RRI TV 25 Quadripler	8.00
Tripler Mounting Kit	1.50
RRI T20	6.50

PHD COMPONENTS

MULTISECTION CAPACITORS

DECCA 400-400/350	3.72
DECCA 80/100-400-350/800/250	4.00
GEC 200 200-150-50-350	3.00
GEC 1000 2000 35	1.90
GEC/Philips GB 600-250	2.10
GEC/Philips GB 600-300	2.10
ITT CVC 20 200-400	3.00
Philips G11 470-250	2.20
PYE 691 200-300-350	2.80
PYE 1000 1000-40	0.90
PYE 731 800-250	2.50
RRI 2500 2500-30	1.30
RRI 600-300	2.50
RRI 300-300-300	2.50
TCE 950 100-300-100-16	1.00

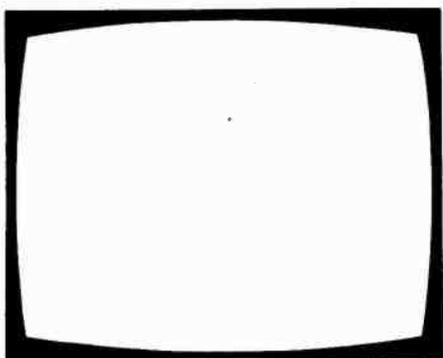

TELEVISION

November
1979

Vol. 30, No. 1
Issue 349

COPYRIGHT

© IPC Magazines Limited, 1979. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

SUBSCRIPTIONS

An annual subscription costs £9.50 in the UK, £10.50 overseas (\$21 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perry Mount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£2.85) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 70p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Your Problems Solved". Send to the address given above (see "correspondence").

this month

- 9 **Leader**
- 10 **Teletopics**
News, comment and developments.
- 12 **Letters**
- 15 **Don't Ask Why** *by Les Lawry-Johns*
All sorts of daft questions keep arising during the daily servicing round.
- 18 **Servicing in the Field, Part 1** *by George Wilding*
For optimum efficiency the field service engineer should deal with as many repairs as possible in customers' homes. This calls for a somewhat different approach to servicing than that adopted on the bench. A guide to speedy diagnosis of basic faults.
- 23 **Adding Video and Audio Out to the Philips N1700 VCR**
by David Matthewson, B.Sc., Ph.D. and Ian Howarth
The Philips N1700 VCR is intended as a domestic model and does not provide audio and video outputs. These can be easily added however, using simple matching amplifiers that can be built up on a small PCB (details included).
- 24 **Of TTL and CMOS Gates and Cabbages and Kings . . . Part 1**
by Andrew Parr, B.Sc., C.Eng., M.I.E.E.
There are certain simple rules and precautions that have to be observed when using digital i.c.s. A practical guide to basic requirements, starting with TTL.
- 27 **Servicing Pye Solid-State Colour Receivers, Part 3** *by Mike Phelan*
In this concluding instalment in his series Mike Phelan deals with the smaller-screen (18in.) models using the 713, 715 and 717 chassis.
- 30 **Long-Distance Television** *by Roger Bunney*
Reports on DX reception and conditions and overseas developments. The beginners' section this month deals with Band III DX reception.
- 33 **Readers' PCB Service**
- 34 **Colour Receiver Options Part 2: Adding Remote Control**
by Luke Theodossiou
Ultrasonic remote control of brightness, colour, volume, channel selection and receiver switch off. The compact interface board uses two ITT i.c.s.
- 38 **TV Servicing: Beginners Start Here . . . Part 26** *by S. Simon*
This time a detailed look at convergence, purity and degaussing, and how to tackle faults and adjustments.
- 42 **Next Month in Television**
- 43 **Your Problems Solved**
- 45 **Test Case 203**

OUR NEXT ISSUE DATED DECEMBER WILL BE
PUBLISHED ON NOVEMBER 19

THE UNBEATABLE BRIARWOOD SERVICE

EX-EQUIPMENT SPARES

MISC. S/Output Trans.
£1 + VAT + £1 P&P
F/Output Trans.
£1.25 + VAT + £1 P&P.
Scancoils £1.50 + VAT
+ £1 P&P. Other
spares available, please
write or phone for details.

MONO TUBES
(tested)
19" Rimguard £3.00
23" Rimguard £4.00
20" Rimguard £5.00
24" Rimguard £6.00
+ £5.00 P.&P.

MONO TUNERS
6-button integrated all
at £4.00
U.H.F. P/Button D/S
£3.50. U.H.F. P/Button
S/S £4.00. Rotary £3.00
+ £1 P&P.

MONO LOPTS
All D/Standard Lopts
at £4.00 + £1 P.&P.
All S/Standard at
£5.00 + £1 P.&P.

MONO PANELS
i.e. Philips, Bush etc.
£3.50 + £1 P.&P.
Quotations for
complete
S/hand chassis if
required. (Diff. prices)

PLEASE ADD 15% V.A.T.
TO ALL ITEMS AND
OVERSEAS AT COST.
CASH WITH ALL ORDERS.

VALVES (MONO & COLOUR)

PCL82	0.10	30C1	0.10	PCC189	0.10	EF183	0.10	PL504	0.25	ECL80	0.10
PCL83	0.25	30C17	0.10	30C15	0.10	EF184	0.10	6/30L2	0.10	PL509	1.00
PCL84	0.10	PCF802	0.10	30C18	0.25	6BW7	0.10	30PL1	0.25	PY500	1.00
PCL85	0.10	PCF805	0.25	PC97	0.20	EH90	0.10	30PL13/4	0.10	GY501	1.00
PCL86	0.10	PCF806	0.10	PC900	0.10	DY802	0.10	30FL1/2	0.25	PL508	0.50
PFL200	0.10	PCF808	0.25	EF80	0.10	PY800/1	0.10	ECC82	0.10	PCF200	0.50
PCF801	0.10	PCF80	0.10	EF85	0.10	PL36	0.25	ECC81	0.10	EY51	0.15

Please note there is 25p Postage and Packing per order.

WE DO NOT SELL RUBBISH
AT BRIARWOOD TV

D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUTPUT	POWER	L/TB	F/TB
Bush/Murphy	5.00	5.00	6.50	—	—	5.00	1.50	5.00	—	—
GEC/Sobell	5.00	5.50	—	—	—	5.00	—	—	—	7.50
Philips	5.00	7.00	—	—	—	5.00	—	—	—	5.00
Decca	5.00	9.00	9.00	—	—	5.00	2.00 (19" only)	6.00	—	5.00
Thorn 2000	5.00	5.00	5.00	6.50	6.50	7.00	—	6.50	10.00	5.00
Pye	7.00	6.00	7.00	—	—	5.00	—	—	—	5.00
Baird	6.50	8.50	7.00	—	—	5.00	—	—	—	5.00

Postage & Packing £1.25

S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	12.00	—	6.00	6.00	12.00	—
GEC Hybrid	6.00	6.50	9.00	—	5.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	5.00	—	—	6.00
Thorn 3000	6.00	6.00	6.00	—	5.00	20.00	20.00	6.00
Pye 691/693	6.00	6.00	8.00	—	5.00	—	15.00	5.00
Thorn 3500	6.00	6.00	6.00	6.50	7.50	20.00	20.50	6.00

Postage & Packing £1.25

COLOUR TUBES

19"	£18.00
19" A49, 192	£20.00
20"	£20.00
22"	£22.00
25"	£18.00
26"	£28.00

Plus P&P £5.00

NEW

Rebuilt tubes
available on request.

COLOUR TUNERS

Bush	£5.00
GEC	£5.00
Philips G6 S/S	£5.00
Thorn 3000	£5.00
Pye 691	£5.00

Some new tuners in stock,
can supply on request. Many
Foreign Tuners also available
on request. Plus P&P £1.

COLOUR LOPTS

Most Lopts available
from £7.00. Both
British & Foreign
makes. Please ring
or write.
P&P per Lopt £1.

MISC.

S/Output transformer
from £1.50.
F/Output from £1.25.
Scancoils from £5.00.
P&P £1.
Other spares available on
request.

THORN 1500 TUNERS

NEW SPECIAL OFFER
AT £8.00

Postage & Packing £1.00

MAIL ORDER T.V.s. IN GOOD WORKING ORDER

		COLOUR				
Pye	19"	£60.00	22"	£65.00	26"	£75.00
GEC	19"	£60.00	22"	£65.00	26"	£75.00
Bush	19"	£80.00	22"	£80.00	26"	£90.00
Philips	G6	—	22"	£63.00	26"	£70.00

MONO

20" & 24" S/S	£16.00	Pye, GEC, Bush etc.
20" & 24" D/S	£14.00	Pye, GEC, Bush etc.
19" & 23" D/S P/button	£12.00	Pye, GEC, Bush etc.
19" & 23" D/S Rotary	£8.00	Pye, GEC, Bush etc.

Please note there is 15% V.A.T. on all the above prices.
Plus £8 P&P. England, Wales & Scotland for colour T.V.'s.
Inland N. & S. Ireland P&P £15. P&P £5 for mono T.V.'s
to England, Wales & Scotland. Inland N. & S. Ireland £7
per set.

Many other makes & models available.
Please ring or write for information.

**PERSONAL CALLERS
WELCOME.**

Briarwood T.V. Limited
Britain's Mail Order
T.V. Specialists

BRIARWOOD

THE PROFESSIONAL CHOICE. NATIONWIDE

NEW SPARES

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	DIODES	E.H.T. TRAYS MONO
AC107	0.20	AF170	0.25	BC172	0.08	BD222/T1P31A	0.37	BF260	0.24	OC45	0.20	1N4001	0.04
AC113	0.17	AF172	0.20	BC173	0.12		0.37	BF262	0.28	OC46	0.35	1N4002	0.04
AC115	0.17	AF178	0.49	BC177	0.12	BD225/T1P31A	0.39	BF263	0.25	OC70	0.22	1N4003	0.06
AC117	0.24	AF180	0.60	BC178	0.12		0.39	BF271	0.20	OC71	0.28	1N4004	0.07
AC125	0.20	AF181	0.30	BC179	0.12	BD234	0.34	BF273	0.12	OC72	0.35	1N4005	0.07
AC126	0.18	AF186	0.29	BC182L	0.09	BD222	0.73	BF336	0.28	OC74	0.35	1N4006	0.08
AC127	0.19	AF239	0.43	BC183L	0.09	BDX22	0.73	BF337	0.24	OC75	0.35	1N4007	0.08
AC128	0.17	AU113	1.29	BC184L	0.09	BDX32	1.98	BF338	0.29	OC76	0.35	1N4148	0.03
AC131	0.13			BC186	0.18	BDY18	0.75	BF42	0.26	OC77	0.50	1N4751A	0.11
AC141	0.23	BA130	0.08	BC187	0.18	BDY60	0.80	BF43	0.24	OC78	0.13	1N5401	0.12
AC142	0.19	BA145	0.14	BC209	0.11	BF115	0.24	BF44	0.27	OC81	0.20	1N5404	0.12
AC141K	0.29	BA148	0.17	BC212	0.09	BF121	0.21	BF45	0.27	OC810	0.14	1N5406	0.13
AC142K	0.29	BA155	0.08	BC213L	0.09	BF154	0.12	BF46	0.24	OC82	0.20	1N5408	0.16
AC151	0.17	BAX13	0.05	BC214L	0.09	BF158	0.19	BF47	0.22	OC820	0.13		
AC165	0.16	BAX16	0.08	BC237	0.07	BF159	0.24	BF48	0.15	OC83	0.22		
AC166	0.16	BC107	0.10	BC240	0.31	BF160	0.23	BF49	0.15	OC84	0.28		
AC168	0.17	BC108	0.10	BC281	0.24	BF163	0.23	BF52	0.15	OC85	0.13		
AC176	0.17	BC109	0.10	BC282	0.18	BF164	0.17	BF53	0.27	OC123	0.20		
AC176K	0.28	BC113	0.09	BC263B	0.20	BF167	0.23	BF55	0.27	OC169	0.20		
AC178	0.16	BC114	0.12	BC267	0.19	BF173	0.21	BHA0002	1.90	OC170	0.22		
AC186	0.26	BC115	0.10	BC301	0.22	BF177	0.26	BR100	0.20	OC171	0.27		
AC187	0.21	BC116	0.10	BC302	0.30	BF178	0.24	BSX20	0.23	OA91	0.05		
AC188	0.20	BC117	0.11	BC307	0.10	BF179	0.28	BSX76	0.23	BRC4443	0.65		
AC187K	0.30	BC119	0.22	BC337	0.11	BF180	0.30	BSY84	0.36	R2008B	1.50		
AC188K	0.30	BC125	0.12	BC338	0.09	BF181	0.34	BT106	1.18	R2010B	1.50		
AD130	0.50	BC126	0.09	BC307A	0.10	BF182	0.30	BT108	1.23	R2305	0.38		
AD140	0.65	BC136	0.12	BC308A	0.12	BF183	0.29	BT109	1.09	R2305/BD222	0.37		
AD142	0.73	BC137	0.12	BC309	0.14	BF184	0.23	BT116	1.23	SCR957	0.65		
AD143	0.70	BC138	0.21	BC547	0.09	BF185	0.29	BT120	1.23	TIP31A	0.38		
AD145	0.70	BC139	0.21	BC548	0.11	BF186	0.30	BU105/02	1.50	TIP32A	0.36		
AD149	0.64	BC140	0.24	BC549	0.11	BF194	0.09	BU105/04	2.00	TIP3055	0.53		
AD161	0.40	BC141	0.22	BC557	0.11	BF195	0.09	BU126	1.40	T1590	0.19		
AD162	0.40	BC142	0.19	BD112	0.39	BF196	0.12	BU205	1.20	T1591	0.19		
AD161	1.30	BC143	0.19	BD113	0.65	BF197	0.10	BU208	1.60	TV106	1.09		
AD162	1.30	BC147	0.07	BD115	0.30	BF198	0.11	BY126	0.09				
AF106	0.42	BC148	0.07	BD116	0.47	BF199	0.14	BY127	0.10				
AF114	0.23	BC149	0.07	BD124	1.30	BF200	0.28						
AF115	0.22	BC153	0.12	BD131	0.32	BF216	0.12	OC22	1.10				
AF116	0.22	BC154	0.12	BD132	0.34	BF217	0.12	OC23	1.30				
AF117	0.30	BC157	0.10	BD133	0.37	BF218	0.12	OC24	1.30				
AF118	0.40	BC158	0.11	BD135	0.26	BF219	0.12	OC25	1.00				
AF121	0.33	BC159	0.11	BD136	0.26	BF220	0.12	OC26	1.00				
AF124	0.33	BC160	0.22	BD137	0.26	BF222	0.12	OC28	1.00				
AF125	0.29	BC161	0.22	BD138	0.26	BF221	0.21	OC35	1.00				
AF126	0.29	BC167	0.09	BD139	0.40	BF224	0.12	OC36	0.90				
AF127	0.29	BC168	0.09	BD140	0.28	BF256	0.37	OC38	0.90				
AF139	0.39	BC169C	0.09	BD144	1.39	BF258	0.27	OC42	0.45				
AF151	0.24	BC171	0.08	BD145	0.50	BF259	0.27	OC44	0.20				

DIODES	PRICE £
1N4001	0.04
1N4002	0.04
1N4003	0.06
1N4004	0.07
1N4005	0.07
1N4006	0.08
1N4007	0.08
1N4148	0.03
1N4751A	0.11
1N5401	0.12
1N5404	0.12
1N5406	0.13
1N5408	0.16

VALVES	PRICE £
DY87	0.52
DY802	0.64
ECC82	0.52
EF80	0.40
EF183	0.60
EF184	0.60
EH90	0.60
PC86	0.76
PC88	0.76
PCC89	0.65
PCC189	0.65
PCF80	0.70
PCF86	0.68
PCF801	0.70
PCF802	0.74
PL82	0.67
PCL84	0.75
PCL86	0.78
PCL805	0.75
PLF200	1.00
PL36	0.90
PL84	0.74
PL504	1.10
PL509	2.45
PY88	0.63
PY500A	1.60
PY81/800	0.57

SPECIAL OFFER	PRICE £
SL901B	3.50
SL917B	5.00

SPECIAL OFFER	PRICE £
Philips PLB02	2.55

E.H.T. TRAYS MONO	PRICE £
950 MK2 1400	2.00
1500 18" 19" stick	
1500 24" 5 stick	2.48
Single stick Thorn TV	
11.16K 70V	0.75
TV20 2 MT	0.75
TV20 16K 18V	0.75

IC's	PRICE £
SN76013N	1.20
SN76013ND	1.00
SN76023N	1.20
SN76023ND	1.00
SN76226DN	1.50
SN76227N	1.20
TBA341	0.97
TBA520Q	1.10
TBA530Q	1.10
TBA540Q	1.45
TBA550Q	1.40
TBA560CQ	1.50
TBA570Q	1.00
TBA800	1.00
TBA810	1.50
TBA920Q	1.50
TBA990Q	1.50
TCA270SQ	1.45
TCA270SA	1.45
TCA1327B	1.00

E.H.T. TRAYS COLOUR	PRICE £
Pye 731	5.20
Pye 691/693	4.50
Decca (large screen)	
CS2030/2232/2630/	
2632/2230/2233/	
2631	5.00
Philips G8 520/40	5.30
Philips 550	5.30
GEC C2110	5.50
GEC Hybrid CTV	5.10
Thorn 3000/3500	5.00
Thorn 8000	2.42
Thorn 8500	4.75
Thorn 9000	5.50
GEC TVM 25	2.50
ITT/KB CVC 5/7/8/9	5.10
RRI (RBM) A823	5.00

All transistors, IC's offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc. Please add 15% VAT to all items and overseas at cost P & P U.K. 25p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

TELEVISION SALE DISCOUNT FOR QUANTITY

Please note all mono sets sold as 100% comp. No broken masks, no broken panels etc. Colour sets sold with good c.r.t.s and 100% comp.

Working Mono £3.00 extra. Working Colour £15.00 extra. Supplied in 1's or 100's.

MONO Rotaries 19" & 23"	PRICE £
GEC	£3.00
Thorn 950 etc.	3.00
K.B.	3.00
Pye	3.00
Thorn 1400	4.50

S/S 20" 24"	PRICE £
Bush 313 etc.	£12.00
Pye 169 chassis	12.00
Thorn 1500	12.00
GEC series 1 & 2	12.00
Decca MS series	12.00

S/S COLOUR	19"	20"	22"	25"	26"
GEC	40	40	40	40	40
Philips	—	—	40	40	40
Thorn	55	—	60	45	65
Korting	—	—	55	—	60
Pye Mechanical	40	—	40	40	40
Pye Varicap	45	—	45	45	45

MAINS DROPPERS

Mono	PRICE
Bush 161	60p
Philips 210 30+125+2K85	50p
Philips 210 118R+148R	48p
Thorn 1400	75p
GEC 2018	58p
Thorn 1500	70p

Colour	PRICE
Bush A823	72p
Pye 723 27Q+56Q	57p
GEC 2110-41Q	45p
GEC 2110-12R5+12R5	47p
GEC2110-27R5	45p
Thorn 3500	58p
Thorn 8000	58p
Thorn 8500	54p
Philips G8 47R	30p
Philips G8 2.2+68	42p

All plus VAT at 15%

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED.

EXPORT COLOUR & MONO T.V.s AVAILABLE READY FOR USE OVERSEAS

TELEVISION

Briarwood House Preston Street
Bradford West Yorkshire BD7 1NS
Tel. Bradford 306018 (STD code 0274)


BRIARWOOD TELEVISION LTD

Britain's Mail Order TV Specialists

BRITAIN'S LARGEST SUPPLIERS OF
BRITISH AND CONTINENTAL
LINE OUTPUT TRANSFORMERS

12 Months Guarantee. Please add 15% VAT
to all items. P & P £1.00.

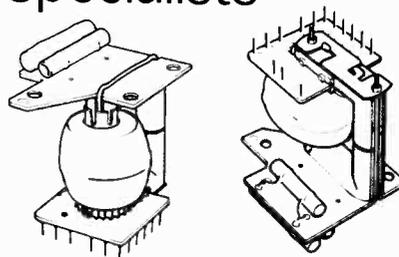Various other models available on request



Set Manufacturer	Chassis/Model	Price £	Set Manufacturer	Chassis/Model	Price £
Pye	731	12-50	Scantic	2621-1/2621-2	12-50
Philips	G8	9-50	Scantic	Chassis 32.631 - Series 2	
Philips	K70			2635-1/2635-3/ 2636/2636-2/ 2636-4/2637/ 2638/2639/ 2645/1805-6482	12-50
Decca	30 (Bradford)	9-25	B & D (Beovision)	3100/3300/3400	13-00
Decca	1730	9-25	B & O (Beovision)	3100/3300/3400 EHT Transformer	14-50
Decca	80	9-00	B & O (Beovision)	3500/3600/4000/ 5000/6000	12-50
Decca	100	9-00	Tandberg	CTV 1/2/2-2/ Colour 102/103/ 104/105/106 CTV 55552	12-50
Decca Mono	MS1700/2020/ 2001/2401	8-00	Telefunken	Chassis 711A	12-00
Korting	51763/51765 - 22" 52665/52666 - 26" 52865/52866 - 26"	12-00	Autovox 90°	Chassis 2682/2683/ 2684/2282/2283/ 2284	12-00
Korting	53701/02/08/09 54701/02/07/08/547 55606/55700/02/ 711/735/747	11-20	Autovox 110°	Chassis 2693/2694	12-00
ITT	CVC25/30/32	9-00	Siemens	2221-1/222-2/ 2621-1/2621-2/ 2622-1/2622-2/ 2623-1/2623-2/ 2624-1/2624-2	12-50
Grundig	1500/2000/2500/ 3000/3010	12-50	Zanussi	B2222-2/3 B2223-2/3	11-20
Grundig	5010	13-00	Baird	27" 110°	11-20
Grundig	5010 EHT Transformer	14-50	Salora	BP-CTV 225 & 265 BP-7-663291/ BP-7-663691	12-00
Grundig	Series 5005/ 2222/6000/6010/8000	12-50	Indesit Mono	ED/B24 EG/B	8-50
Luxor	Chassis 32.617 - Series 2 2031-1/2031-2/ 2227-1/2227-2/ 2229-1/2229-2 Chassis 56.307 - Series 1 & 2 22307/22309/22317 26305/26307 Chassis 56347 - Series 1	12-00			
Luxor	TV 22347-2217-1 22349-2219-1 26345-2615-1 26347-2617-1 26349-2619-1 26347-2227-1 Chassis 32.621 - Series 1	12-50			

6 MONTH GUARANTEE

p & p 1-00

INSERTS (WINDING)

PYE 691 or 697	Small	3-65	Decca CTV 25	(Non Tripler Type)	
PYE 691 or 697	Large	5-10		Overwind	8-50
Bush CTV 25 Mk 3	Underwind	7-25	Philips G6 S/S or D/S	Underwind	7-25
Philips K70	Underwind	8-00		Underwind	7-90
				Overwind	8-50
				Philips G6 Overwind on Exchange basis only	
			EMO 90° Winding		7-90

MONO

Bush 161V Series	8-45	Philips 210, 300	8-45
Bush 313 Series	8-45	PYE 368	8-45
Decca DR1 to DR24	8-45	PYE 169 or 569	8-45
GEC Series 1-2	8-45	BUSH 816	12-00
ITT K13 VC 200	8-45		

Briarwood House, Preston Street, Bradford
West Yorkshire BD7 1LU
Tel: (0274) 306018

ARE YOU IN THE DARK?
...ABOUT OUR



COLOUR T.V. PANEL EXCHANGE REPAIR SERVICE

FULL RANGE OF
THORN · RBM · PHILIPS
PYE · INVICTA · GEC
DECCA · TELPRO
AND MANY OTHER MAKES

90 DAY GUARANTEE ON ALL REPAIRS
SAME DAY POSTAL SERVICE

We employ a large skilled Staff, who utilise some of the most sophisticated Test equipment available, inclusive of AUTOMATIC FAULT FINDING COMPUTERS together with specially designed SERVICING JIGS which in short means to you —

HIGH QUALITY REPAIRS — AT LOW COST



ONE OFF
OR



100 OFF · NO ORDER TOO
LARGE OR SMALL

SEND FOR PRICE LIST

SEND FOR CATALOGUE
BLOCK DISCOUNTS FOR TRADE CONTRACTS

TO

Campbell Electronics Ltd.


Factory Unit E5, Halesfield 23, Telford Shropshire TF7 4QX
Telephone: Telford (0952) 584373, Ext. 2. Telex 35191 Chamcon

S & R. BREWSTER LIMITED Ref: TV

86-88 UNION ST.
PLYMOUTH

TELEPHONE
0752-65011

Manufacturers of

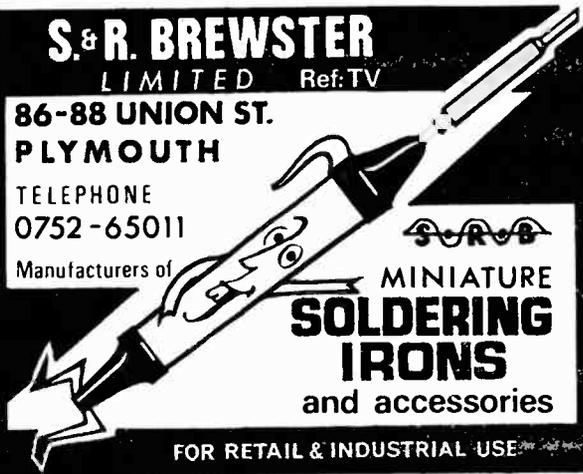

MINIATURE
**SOLDERING
IRONS**
and accessories

FOR RETAIL & INDUSTRIAL USE

QUALITY USED TV'S AT GIVE AWAY PRICES

S.S. MONO FROM £12
D.S. MONO FROM £5
S.S. COLOUR FROM £40
PRICES PLUS V.A.T.

ALL WORKERS, FRESH STOCKS WEEKLY,
QUANTITY DISCOUNTS, DELIVERY ARRANGED.
TRY US YOU WILL NOT BE DISAPPOINTED.

TELETRADERS

We have moved to our new Warehouse where we have much bigger stocks.

St. Leonard's Warehouse, St. Leonard's Road,
Newton Abbott, Devon.
Telephone (0626) 60154

Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs — and they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

City and Guilds Certificates:-

Telecommunications Technicians,
Radio, TV and Electronics Technicians,
Electrical Installation Work,
Technical Communications,
Radio Amateur,
MPT General Radio Communications
Certificate.

Diploma Courses:-

Electronic Engineering,
Electrical Engineering,
Computer Engineering,
Radio, TV, Audio Engineering, Servicing and
Maintenance. (inc. Colour TV)
New Self-Build Radio Courses with Free Kits.

Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful — at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name.....

Address.....

..... Phone No:

ICS International Correspondence Schools,
Dept. N285, Intertext House,
LONDON SW8 4UJ. Te 622 9911
(all hours)

**QUARTZ LCD
5 Function**

Hours, mins, secs., month, date, auto calender, back-light, quality metal bracelet.

£6.65

Guaranteed same day despatch. Very slim, only 6mm thick.




M1

**SOLAR QUARTZ
LCD 5 Function**

Genuine solar panel with battery back-up. Hours, mins., secs., day, date. Fully adjustable bracelet. Back-light. Only 7mm thick.

£8.65

Guaranteed same day despatch.

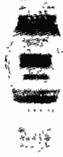

M2

**QUARTZ LCD
11 Function. SLIM CHRONO**

6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calender. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£10.65 Thousands sold! Guaranteed same day despatch.



M3

**QUARTZ LCD
ALARM 7 Function**

Hours, mins, secs., month, date, day. 6 digits, 3 flags plus continuous display of day and date or seconds. Back-light. Only 9mm thick.

£12.65

Guaranteed same day despatch.



M4

**MULTI ALARM
6 Digits 10 Functions**

- Hours, mins., secs.
- Months, date, day.
- Basic alarm.
- Memory date alarm.
- Timer alarm with dual.
- Time and 10 country zone.
- Back-light.
- 8mm thick.

£18.65

M5



**FRONT-BUTTON
Alarm Chrono
Dual Time**

6 digits, 5 flags, 22 functions. Constant display of hours and mins., plus optional seconds or date display. AM/PM indication, month, date. Continuous display of day. Stop-watch to 12 hours 59.9 secs., in 1/10 second steps. Split and lap timing modes. Dual time zones. Only 8mm thick. Back-light. Fully adjustable open bracelet. Guaranteed same day despatch

£22.65

M6



**SOLAR QUARTZ LCD
Chronograph with Alarm
Dual Time Zone Facility**

6 digits, 5 flags, 22 functions. Solar panel with battery back-up. 6 basic functions. Stop-watch to 12 hours 59.9 secs., in 1/10 sec. steps. Split and lap timing modes. Dual time zones. Alarm. 9mm thick. Back-light. Fully adjustable bracelet.

£27.95

M7



**ALARM CHRONO
with 9 world time zones**

- 6 digits, 5 flags.
- 6 basic functions.
- 8 further time zones.
- Count-down alarm.
- Stop-watch to 12 hours 59.9 secs.
- in 1/10 sec. steps.
- Split and timing modes.
- Alarm.
- 9 mm thick.
- Back-light.
- Fully adjustable bracelet.

£29.65

M8



**SOLAR QUARTZ LCD
Chronograph**

Powered from solar panel with battery back-up. 6 digit, 11 functions. Hours, mins., secs., day, date, day of week. 1/100th, 1/10th, secs., 10X secs., mins. Split and lap modes. Back-light, auto calender. Only 8mm thick. Stainless steel bracelet and back. Adjustable bracelet. Metac Price

£13.65

Guaranteed same day despatch.

M9



**QUARTZ LCD
Ladies Day Watch**

Only 25 x 20mm and 6mm thick. Hours, minutes, seconds, day, date, backlight and auto calender. Elegant metal bracelet in silver or gold fully adjustable to suit very slim wrists. State colour preference.

£9.95

Guaranteed same day despatch.

M15



**QUARTZ LCD
Ladies Fashion Watch**

Elegant bracelet in bronze/gold finish or silver colour. Hours, mins, secs, day, date, backlight and auto calender. Adjustable for the slimmest of wrists. State colour preference.

£14.95

Guaranteed same day despatch

M17




**QUARTZ LCD
Ladies Cocktail Watch**

Highly functional watch which also suits those special occasions. Beautifully designed with a very thin bracelet which retains strength as well as elegance. Hours, mins, secs, day, date, backlight and auto calender. Bracelet fully adjustable to suit slim wrists. State gold or silver finish.


£19.95

Guaranteed same day despatch

M18

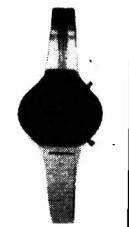

**HANIMEX
Electronic
LED Alarm Clock**

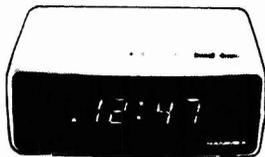

Features and Specification
Hour minute display. Large LED display with p.m. and alarm on indicator. 24 Hours alarm with on off control. Display flashing for power loss indication. Repeatable 9 minute snooze. Display bright dim modes control. Size: 5 1/2" x 3 9/32" x 2 3/8" (131mm x 111mm x 60mm). Weight: 1.43 lbs (0.65 kg). AC power 220V.

£10.20 Thousands sold!

Mains operated.

Guaranteed same day despatch

M13

**EXECUTIVE ALARM
WATCH**

6 Functions plus Alarm: Conference signal, 5 minute snooze alarm. Conference signal sounds 4 secs. before main alarm to give advance warning and an option to cancel. Snooze sounds 5 mins. after main alarm and is always preceded by the conference signal.

£14.95

M60



**MACY QUARTZ
ANALOGUE**

Automatic Calendar Day and Date infinite bracelet. This mans watch has elegance as well as the robust appearance provided by a watch with traditional features. Accuracy is provided by a quartz crystal powered by a long life miniature battery.

£24.95

M21



Metac price breakthrough for an Alarm Chronograph with Dual Time only

£18.95



OUTSTANDING FEATURES

- **DUAL TIME.** Local time always visible and you can set and recall any other time zone (such as GMT). Also has a light for night viewing.
- **CALENDAR FUNCTIONS** include the date and day in each time zone.
- **CHRONOGRAPH/STOPWATCH** displays up to 12 hours, 59 minutes, and 59.9 seconds.
- On command, stopwatch display freezes to show intermediate (split/lap) time while stopwatch continues to run. Can also switch to and from timekeeping and stopwatch modes without affecting either's operation.
- **ALARM** can be set to anytime within a 24 hour period. At the designated time, a pleasant, but effective buzzer sounds to remind or awaken you!

Guaranteed same day despatch. M16

HOW TO ORDER

Payment can be made by sending cheque, postal order, Barclay, Access or American Express card numbers. Write your name, address and order details clearly, enclose 40 pence per single item for post and packing or the amount stated in the advert. All products carry 1 year written guarantee and full money-back 10 day reassurance. Battery fitting and electronic calibration service is available to customers at any Metac shop. All prices include VAT currently at 15%.

Metac Wholesale:

Trade enquiries - send for a complete list of prices for all the goods advertised plus many more not shown also minimum order details.

Telephone orders: Credit card customers can telephone orders direct to Daventry (03272) 76545 or Edgware Rd. 01-723 4753 24 hours a day.



Service Enquiries 03272-77659

CALLERS WELCOME Shops open 9-30am-6.00

Metac

**ELECTRONICS
& TIME CENTRES**

North & Midlands
67 High Street, DAVENTRY
Northamptonshire
Telephone: 03272 76545

South of England
327 Edgware Road
LONDON W.2
Telephone: (01) 723 4753

OTV

THE LARGEST
STOCKS OF
GENUINE PART-EXCHANGED COLOUR
T.V.'s IN THE COUNTRY
— UNDER ONE ROOF.


**REGULAR LARGE DELIVERIES EVERY WEEK
INCLUDE—**

Philips 511/512/G8 etc., Bush, Murphy, Thorn 3000/3500/8000/8500, GEC all models,
Pye Varicap, Grundig, Telefunken, Saba, Decca Bradford, Nordmende, B. & O., Emo, Finlux,
Luxor, Korting, Hitachi, Sanyo, Toshiba, etc., etc., etc.

**STOCK UP NOW FOR THE COMING
BUSY PERIOD.**

SINGLE STANDARD T.V.'s
FROM **£20** + VAT

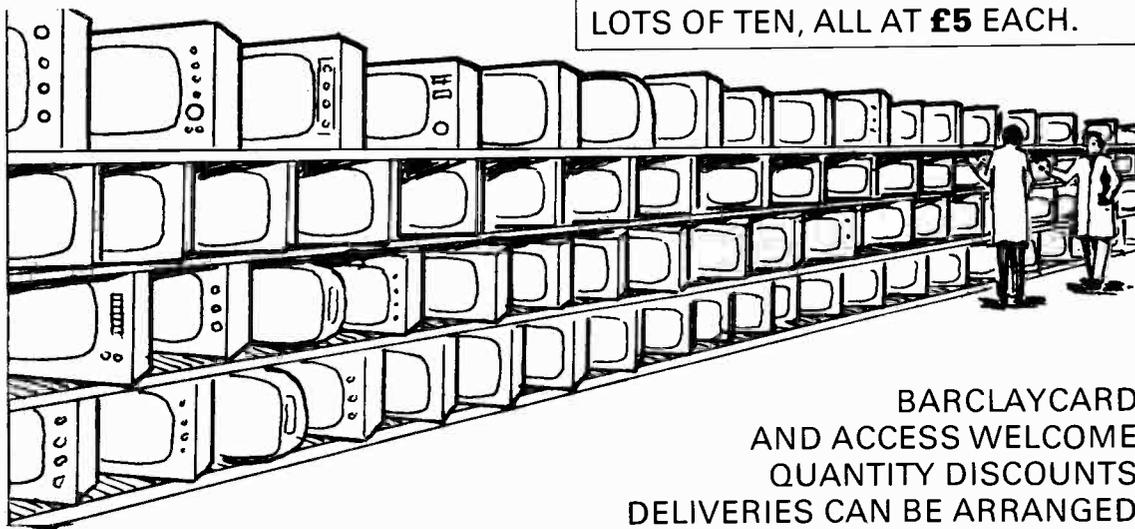SPECIAL OFFER WHILE STOCKS
LAST. ASSORTED DUAL
STANDARD COLOUR T.V.'s IN
LOTS OF TEN, ALL AT **£5** EACH.




BARCLAYCARD
AND ACCESS WELCOME
QUANTITY DISCOUNTS
DELIVERIES CAN BE ARRANGED

SUPERB TESTING FACILITIES AVAILABLE


**OTV TELEVISION LTD,
144A Lea Bridge Rd,
London E5 9RB.
Tel: 01-985 6111/8687**

OPEN MON.-SAT.

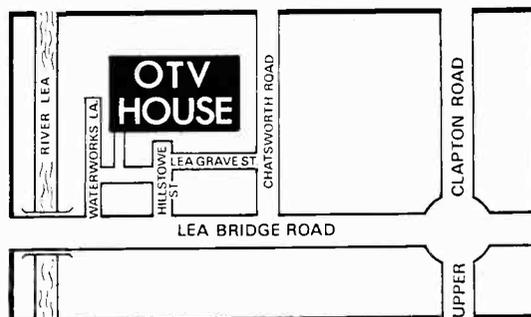

We specialise in Export

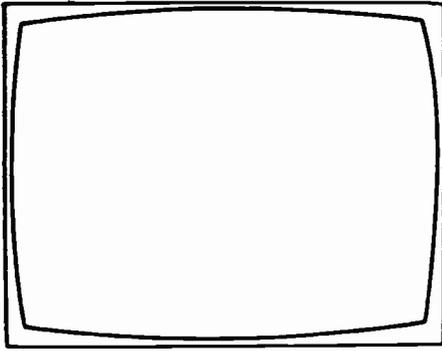Enquiries invited from the Middle East and Third World Countries.



TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTS MANAGER

Roy Smith 01-261 6671

CLASSIFIED ADVERTS

Colin R. Brown 01-261 5762

What to do with ITV-2

In the past we have supported the idea of setting up a separate, independent authority – the OBA, as recommended by the Annan Committee – to run the UK's fourth TV network. The problem with that idea was always how it would have been financed, a point on which the Annan Committee was rather vague. Be that as it may, the idea died along with the last government, the present government promising in the Queen's Speech to set up TV4 under the control of the IBA, with finance provided through advertising. The danger of this of course is yet more of the same, with the new network striving to achieve maximum audience ratings. Not an inspiring prospect, but one appealing to the advertising industry which has more prospective advertising than can be fitted into the present single commercial network.

The comments on ITV-2 made by the Home Secretary, William Whitelaw, during a speech at the opening of the Royal Television Society's recent convention are most reassuring therefore. TV4 will not it seems be allowed to become "just ITV-2". In running TV4, the IBA will be charged with preventing the two commercial channels engaging in a battle for high ratings, and also with preventing the present Big Five ITV companies from dominating the new network.

These are strong words, and in enlarging upon the "strict safeguards" mentioned in the Queen's Speech Mr. Whitelaw spelt out clearly what the government expects of the new service. We quote: "The IBA will be expected to develop a distinctive service . . . (which) should be designed to give new opportunities to creative people in British TV and add new and greater satisfaction . . . for the viewer. It will be expected to make arrangements for the largest practicable proportion of programmes . . . to be supplied by organisations and persons other than the companies contracted to provide programmes on ITV-1." To ensure this, the new network should have its own controller and its own income. The IBA will be expected to ensure "that the budget for the fourth network is adequate to achieve the sort of service described," while this finance would not necessarily be determined by the revenue obtained from advertisements shown on the network," implying that the IBA will be able to use revenue from ITV-1 to finance ITV-2.

This could lead to something very close to what the Annan Committee proposed, and a worthwhile addition to the present services. Let's hope that the expectations Mr. Whitelaw has raised will in due course be met.

European Shivers

As 1980 approaches, the economic outlook is far from reassuring. The seventies have not turned out to be a particularly successful decade economically, and we seem far indeed from the optimism of the late fifties (remember "you've never had it so good"?) and sixties. The end of the era of cheap fuel played a major part in this of course, but one feels that an important contributory factor has been the lack of any significant new industrial developments to act as economic stimulants in the way that electronics and chemicals did in the sixties.

Against this sombre background, the European TV industry is also faced with excess capacity and, with the ending of the PAL patent restrictions, growing competition from Japan. This is the likely reason for some of the interesting company realignments announced in recent months. Earlier this year France's largest setmaker, Thomson-Brandt, took a majority shareholding in one of the largest German setmakers, NordMende. More recently the continent's largest electronics concern, Philips, set up a joint operation with Grundig, which holds a substantial share of the German market. Close technical ties between the two companies had already been established, in particular with the joint development of the V2000 VCR system. Another interesting tie up is that between Italy's largest setmaker Zanussi and Hitachi, who have entered into an agreement for marketing and technical co-operation in all their manufacturing fields.

There has also been rationalisation in colour tube manufacturing, with the announcement that Thomson-Brandt and AEG-Telefunken are to set up a joint subsidiary to be known as Europacolour. Thomson-Brandt's tubes are produced by Videocolour, which was set up jointly with RCA in 1971 and holds about 20 per cent of the European market: Telefunken tubes have been made under a Philips licence which is due to expire.

One can't help but feel that further mergers and realignments amongst the still rather fragmented European domestic electronics manufacturers are to be expected.

OCTOBER COVER

Our cover last month featured the latest *Television* colour receiver, photographed using a fish-eye lens, in a special case made of Perspex. The use of this material results in a very smart cabinet, but working with Perspex is not recommended unless you have experience and the necessary equipment.

Teletopics

CHANGES AT SINCLAIR

News about changes at Sinclair Radionics, which manufactured test equipment, pocket calculators and the Microvision pocket TV set and is owned by the NEB, seems to have leaked out in dribs and drabs. First came the report, mentioned in these pages a couple of months ago, that a new pocket TV set with a flat-screen c.r.t. had been developed and that production of the 2in. Microvision Model TV1B, which uses a conventional electrostatically-deflected instrument tube, had ceased. Next came an announcement that Binatone International Ltd. had taken over Sinclair's calculator and TV interests, which had been operating at a loss.

The picture that eventually emerged was a three-way split up of Sinclair Radionics' interests, though there are several complications in the final arrangements. The three-way split divides up the profitable instrument division, which remains with the NEB as Sinclair Electronics Ltd., a subsidiary of the holding company Sinclair Radionics Ltd.; the pocket calculator and Microvision TV1 interests, which have been bought by Binatone International Ltd.; and Sinclair Research Ltd., which will continue development work on the flat-screen pocket TV receiver project and will also work on other development projects. Complications on the flat-screen TV side arise in that Sinclair Research will develop the receiver under subcontract to Sinclair Radionics which is in turn under contract to the NRDC. The NRDC has already provided £300,000 for the project, and is committed to a total of over £500,000. It's understood that the NEB and Sinclair Radionics are seeking partners to take on manufacture of the flat-screen tube and assembly and marketing of the sets. Mullard has been suggested as a possible partner on the tube side. Work on the project is continuing, but it's unlikely that the flat-screened set will be launched before Christmas 1982.

Binatone, which exports its products to over 50 countries and is said to be the largest privately owned UK electronics company, is to start production of the TV1 at its Wembley headquarters while seeking a Department of Industry grant to build a factory for the purpose in Tyneside. The advantage to Binatone is that by promoting the Microvision TV1 alongside its numerous other products, which include TV games, clock radios and music centres, marketing costs can be kept down. There are likely to be three versions, the UK only TV1B, the TV1C for the US market and the TV1D for Europe. The original multi-standard TV1 was discontinued by Sinclair Radionics in 1978.

Clive Sinclair, who founded Sinclair Radionics in July 1961, also owns Science of Cambridge Ltd. which may take on the marketing of products developed by Sinclair Research. Just to confuse the situation further, Sinclair Research is hoping to obtain a contract to develop a new pocket TV set using a conventional tube.

VIDEO DEVELOPMENTS

Europe's largest annual domestic electronics exhibition, the Berlin Radio and Television Show, is the obvious place in Europe to launch new products and preview new developments. True to form, several new video systems put

in an appearance there this year. Toshiba's fixed-head VCR, which we described in *Teletopics* last month, was on show and the long-awaited BASF system was also displayed. There are significant differences between these two LVR (longitudinal video recording) systems however. The Toshiba system uses an endless loop of $\frac{1}{2}$ in. (12.7mm.) tape with 220 tracks on it to give an hour's playing time. In the BASF system on the other hand the tape moves to and fro between a take-up spool in the recorder and the spool in the cassette: the tape is 8mm. wide, and carries 72 tracks. The 114 x 116 x 17mm. BASF cassette has a maximum playing time of 180 minutes, but will also be available in 60 and 120 minute versions. When we first mentioned the BASF LVR system in the September 1977 *Teletopics* it was reported that the aim was to have the machine on the market by Christmas 1979. BASF don't seem to be far off target – a UK version is expected to be launched in about a year's time. The simplified mechanics of these systems would seem to offer advantages, though considerably higher tape speeds are involved. BASF claim an improved frequency response compared to helical-scan systems, and both BASF and Toshiba point out the advantage of high-speed tape duplication.

Also on view was Grundig's first video disc player. This pre-production machine is based on the Philips system.

INTERNATIONAL PRESTEL

The PO is to carry out an international trial of its Prestel system, involving users in the UK and up to six other countries – Australia, W. Germany, Holland, Sweden, Switzerland and the USA. A wide variety of up-to-the-minute business information from many parts of the world will be made available to those taking part, the aim being to assess whether a full international Prestel service would be a viable proposition.

TUBELESS CTV

Toshiba is understood to have developed a successful flat-screen colour display system employing a liquid crystal matrix. Initial sets will be in small screen sizes and are planned for introduction in about a year's time. The main problem with this type of display is understood to be achieving adequate definition due to the writing speed attainable.

DR ELECTRONICS EXTEND RANGE

Several interesting additions have been made to the range of solid-state replacement modules produced by DR Electronics. In addition to the PL802/T replacement for the PL802 luminance output pentode, mentioned in these pages before, there is now a replacement CDA panel for use in Pye group hybrid colour receivers, an i.f. selectivity/gain module for use in Pye solid-state colour chassis (713, 725, 731 etc.), also a.c. and d.c. replacement motor speed control modules for use in Hoover washing machines. DR's products are sold mainly through wholesalers, including Belvoir Components, Lloyd Electronics, S.E.M.E. Ltd.,

Swansea Aerials Ltd., Cooper Electronics (Dublin), Pinnacle Electronics Ltd., Vision Spares (Dublin) and J.A.T.A. DR Electronics' address is 5 Bradgate Lane, Asfordby, Melton Mowbray, Leicestershire.

The i.f. selectivity/gain module consists of a Plessey SW153 SWAF to define the bandwidth, driven by a BF197 transistor and followed by a two-transistor (BF196/BF197) amplifier to provide the gain. The CDA panel has several different features from the LEDCo panel reviewed in our June issue. In particular the colour-difference outputs are a.c. coupled to the c.r.t. grids, which are clamped at 80V. DR Electronics say this system avoids colour drift and makes setting up particularly simple, with only the green and blue presets to balance if necessary.

GREECE CHOOSES SECAM

Greece is to be the twenty fourth country to adopt the French SECAM colour system – an initial £9 million pound contract for the supply of equipment has now been signed. It's understood that the particularly mountainous Greek terrain played a part in the decision to adopt SECAM. A separate agreement has been reached between French and Greek setmakers for the production of 20,000 colour receivers annually.

NEOSID SMALL ORDERS

Neosid Ltd., a major supplier of ferrite components, coil assemblies and plastics coil formers for both professional and consumer electronics use, has established a mail order department to assist constructors and service engineers to obtain these items in small quantities. A broad selection of the company's products is included in the small order catalogue, which is available from Neosid Small Orders, PO Box 86, Welwyn Garden City, Herts AL7 1AS (please enclose stamped, addressed envelope). The range includes ferrite components such as beads, screw cores, rods, E, I and U cores, coil assemblies, plastic formers and trimming tools.

PRERECORDED VIDEO TAPES

One thing that could boost the sale of VCRs would be the availability of prerecorded tapes of well known feature films. Magnetic Video Ltd. has now jumped in to fill this role, with an initial range of 27 films including *Soldier Blue*, *The Sound of Music*, *Blue Hawaii* and *The African Queen*, on both VHS and Betamax format cassettes. The recommended price for a two-hour film on tape is £29.96 including VAT, and Magnetic Video say they have many more titles to follow.

AUSTRALIAN SATELLITE TV

As mentioned before, Australia is planning to use Satellite transmissions in order to reach the remote outback areas of the continent. The latest news is that a Canadian satellite is to be used to carry out a series of tests. Television programmes – and telephone calls – will be beamed from Ottawa via the Canadian Hermes satellite to 47 test sites in New South Wales and Queensland. The satellite is being moved to a position off the west coast of Canada so that it "sees" Ottawa and the eastern Australian states at the same time.

CEEFAX SUBTITLING AIDS THE DEAF

The BBC has carried out experimental programme transmissions using a subtitling system designed to help

deaf viewers to follow programmes. The subtitles were transmitted as part of the BBC's teletext system (Ceefax) and can be received on a normal teletext-equipped TV receiver. The Ceefax system includes provision of a subtitling control bit which, when "set", indicates that the associated Ceefax page is to be displayed in the form of a boxed caption superimposed on the picture.

Experience with foreign film subtitling has shown that the timing of subtitles must be accurate to within four television pictures (four film frames), i.e. one sixth of a second. Since a full teletext page can take up to a quarter of a second to transmit, when subtitles are included it will often be necessary to break into the transmission of a normal data page to synchronise the subtitles with the picture. The BBC's Ceefax transmission equipment at the Television Centre has been designed to make this possible. Interrupting the transmission of the normal Ceefax data pages to insert subtitle pages increases the overall magazine transmission time, but the effect is minimal – transmission of a two-row subtitle every second increases the overall magazine transmission time by less than 5%.

The BBC's computer subtitling system, which is normally used for subtitling foreign films, holds the subtitles in a floppy disc store. They are read out to an electronic character generator under time-code control. To use the system with Ceefax, the data from the floppy disc is "reformatted" and fed to the Ceefax computer-video terminal. The BBC has also devised a caption system which can be used where only a limited number of subtitles are required in a programme. Neither system is suitable for use with live broadcasts of unscripted programmes. The BBC is working with Leicester Polytechnic however on a project aimed at exploiting the Palantype system of mechanical shorthand so that subtitles can be generated and transmitted almost instantaneously – the BBC has designed an electric Palantype keyboard, whose output is transcribed by the Polytechnic's computer, giving a quality of script which shows great promise.

The IBA has been working on similar arrangements (don't the two of them always?), in conjunction with Southampton University.

STATION OPENINGS

The following relay stations are now in operation.

Bishop's Castle (Salop) BBC-1 ch. 39, BBC-2 ch. 45, ATV ch. 49. Receiving aerial group B.

Bleachgreen (Cumbria) BBC-1 ch. 57, Border Television ch. 60, BBC-2 ch. 63. Receiving aerial group C/D.

Briton Ferry (West Glamorgan) BBC-2 ch. 40, HTV Wales ch. 43, BBC Wales ch. 46. Receiving aerial group B.

Church Stretton (Salop) ATV ch. 41, BBC-2 ch. 44, BBC-1 ch. 51. Receiving aerial group B.

Kirkcudbright (Dumfries and Galloway) BBC-1 ch. 21, Border Television ch. 24, BBC-2 ch. 27. Receiving aerial group A.

Pencader (Dyfed) HTV Wales ch. 23, BBC-2 ch. 26, BBC Wales ch. 33. Receiving aerial group A.

Rothbury (Northumberland) BBC-1 ch. 55, BBC-2 ch. 62, Tyne Tees Television ch. 65. Receiving aerial group C/D.

Skipton (Yorkshire) BBC-1 ch. 21, Yorkshire Television ch. 24, BBC-2 ch. 27. Receiving aerial group A.

Storeton (Liverpool and Birkenhead) BBC-1 ch. 22, Granada Television ch. 25, BBC-2 ch. 28. Receiving aerial group A.

West Brunton (Wensleydale) BBC-1 ch. 40, Tyne Tees Television ch. 43, BBC-2 ch. 46. Receiving aerial group B.

All the above transmissions are vertically polarised.

Letters

IMPROVED AGC

There are still a lot of dual-standard sets around capable of giving excellent performance – especially in areas where there's a strong signal. Their main shortcoming is the use of mean-level a.g.c., which alters the gain with variations in picture content despite the signal amplitude remaining constant. As is well known, a sync-tip a.g.c. system gives much better performance during scenes that are darker or lighter than average.

Mean-level a.g.c. was the only economical way of handling both 405- and 625-line signals. Nowadays 405-line reception is required in only a very few areas. In most areas

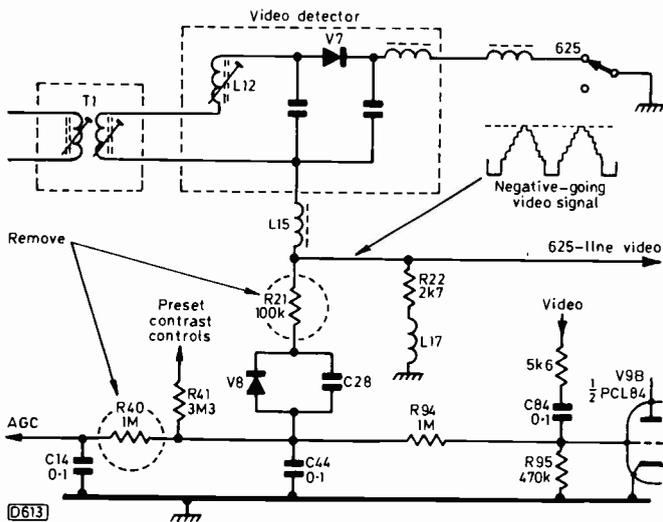


Fig. 1: The original mean-level a.g.c. circuit used in the Pye 11U series receivers. Removing R40 disconnects the controlled stages from the existing a.g.c. circuit; removing R21 or V8 and C28 eliminates unnecessary loading on the video detector diode V7.

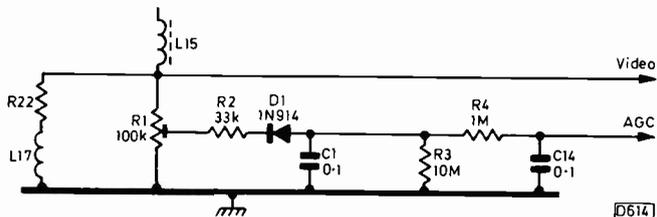


Fig. 2: Suggested sync-tip a.g.c. circuit for use in the Pye 11U series. Except for R21 and R40, the original a.g.c. circuit components can be left in place.

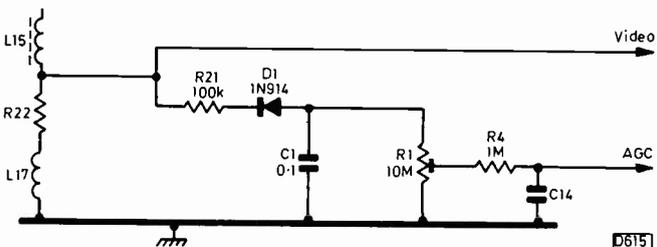


Fig. 3: Suggested alternative circuit. In this case leave R21 in place and disconnect V8 and C28.

a dual-standard set can be left in the 625-line position permanently and modifications can be made to improve the 625-line reception. It's very easy to change the a.g.c. circuit to a sync-tip one – which operates on the principle that the sync tip represents maximum signal amplitude.

Details will vary from chassis to chassis of course. The example given here is the chassis used in the Pye 11U series of all-valve sets produced over the period 1963-5 – there was a vast number of models bearing many brand names.

The original a.g.c. arrangement is shown in Fig. 1. The negative voltage at the grid of the triode sync separator V9B was used as the a.g.c. potential, filtered by R94/C44/R40/C14 – diode V8 provides overload action on 625-lines, conducting when the d.c. component of the rectified video signal exceeds the a.g.c. voltage and thus supplementing the mean-level a.g.c. action.

The original a.g.c. circuit can be disabled simply by removing R21 and R40. The sync-tip circuit shown in Fig. 2 can be built up on a tagstrip mounted very close to L15 (except for R4 which should be close to C14). If the alternative circuit shown in Fig. 3 is used, remove V8 and C28 instead of R21. The preset potentiometer R1 now acts as a preset contrast control. Set it for a slightly overmodulated picture with the manual contrast control at maximum (a higher setting gives rise to more buzz, due to intermodulation in the video amplifier). These sets are slightly unusual in using a high-level manual contrast control in the anode circuit of the video output pentode incidentally.

The sync-tip circuit couldn't be simpler. Diode D1 acts as a peak rectifier, charging C1 on the sync pulses. It doesn't discharge significantly through the large-value resistor R3 before the next pulse arrives. The video signal input is about 3V peak-to-peak.

I. L. Heynemann,
London NW1.

THORN 1600 CHASSIS

When servicing the Thorn 1600 chassis, engineers should always check the condition of R157 (39Ω) which is part of the mains dropper. If R157 is open-circuit, the voltage regulator is inoperative. The set will still function, with slight overscan, but the condition will lead to eventual failure of a major component. Since the fault is not obvious to the viewer, can you suggest an over-voltage protection circuit that could be incorporated?

Peter Crosby,
Oldham, Lancs.

Editorial note: When R157 is open-circuit, the 29V supply to the field output stage rises to about 36V. RS Components have an over-voltage protection i.c. (stock no. 307-890) which operates in conjunction with a crowbar thyristor and can be adjusted over the range 2.6-45V. This could possibly be used, though we've not tried it. Anyone else care to comment on this problem?


SERVICING HEADACHES

A couple of servicing problems have caused me headaches recently. The first fault was on a Pye colour set fitted with the 697 chassis. The verticals over the top three-four inches of the screen were slightly bent to the right. The field locking was excellent, and the line lock very good except when a fast moving object such as a tennis or football moved rapidly across the screen – the whole raster would then shimmer. Otherwise both timebases were o.k. All likely culprits in the

MANOR SUPPLIES

PAL COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

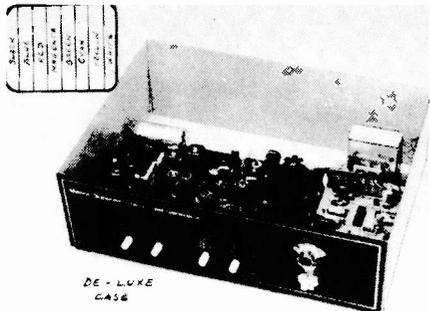

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £40.25 + £1.25 P/Packing. DE-LUXE CASE £5.95. ALUMINIUM CASE £2.95, BATT HOLDERS £1.70, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.55.

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £28.75 + £1.15 p.p. CASE EXTRA £1.75. BATT. HOLDERS £1.70.

- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed.

MK4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.50 P/Packing.

VHF MODULATOR (CHI to 4) FOR OVERSEAS £4.00.

INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.

(ABOVE PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT KIT (incl. TEXAS DECODER). Wide range of facilities in colour. External unit. AE input to set. Write or call for further information. See working demonstration model! Easy to build and results guaranteed for every completed unit.


Texas XM11 Decoder £149.50 p.p. £1.30.

Auxiliary Units £101.00 p.p. £1.65.

De-Luxe Case £17.00 p.p. £1.40. (or total p.p. £3.00).


Prices include 15% VAT

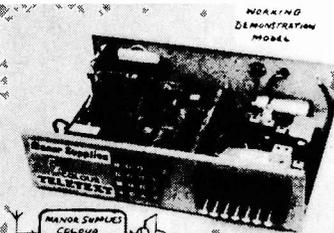Separate Price List for Individual Units available.



Changes from Teletext to picture without switching aerials.

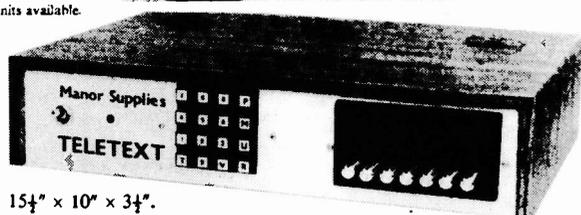Armchair control of Teletext and T.V. stations.



15 1/2" x 10" x 3 1/2".

Now available ex stock **NEW MULLARD TELETEXT DECODER MODULE 6101 VML**, complete and tested. Details on request.

COLOUR. UHF & TELEVISION SPARES

NEW 'TELEVISION' COLOUR RECEIVER PROJECT ALL PARTS AVAILABLE AT PRESENT. POWER, SIGNAL & TIMEBASE. SEND OR PHONE FOR LIST. WORKING DEMONSTRATION SET NOW ON SHOW.

NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.80 p.p. £1.10. T.V. PORTABLE PROJECT PARTS AVAILABLE. SEND OR PHONE FOR LIST. WORKING MODEL AT 172 WEST END LANE, NW6.

TV TEST GENERATOR UHF MODULATOR £4.00 p.p. 40p.

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £12.65 p.p. 50p. (ALUM CASE £2.30 p.p. 80p.) COMPLETE TESTED UNITS READY FOR USE (DE LUXE CASE) £25.00 p.p. £1.25.

ADDITIONAL GREY SCALE KIT £3.35 p.p. 35p.

STAB MAINS POWER SUPPLY FOR ABOVE £5.50 p.p. 80p.

UHF SIGNAL STRENGTH METER KIT £19.40 (ALSO VHF VERSION)

ALUM CASE £1.75, DE-LUXE CASE £5.60 p.p. £1.25.

CRT TESTER & REACTIVATOR PROJECT KIT £24.00 p.p. £1.60.

"TELEVISION" COLOUR SET PROJECT (1974) SPARE PARTS STILL AVAILABLE. ALTVE. IF COMPL. & TESTED £16.80 + £1.25 p.p.

PHILIPS 210 300 Series IF Panels £2.90 p.p. £1.25.

PHILIPS 210, 300 Series Frame T.B. Panels £1.15 p.p. 75p.

PHILIPS 19TG 170 Series Timebase Panels £2.90 p.p. £1.25.

BUSH A823 CONVERGENCE PANEL £7.60 p.p. £1.25.

BUSH A823 (A807) Decoder Panel £8.65 p.p. £1.25.

BUSH A823 SCAN CONTROL PANEL £2.90 p.p. 80p.

BUSH A823 IF PANEL (EXPORT VERSION) £3.25 p.p. 95p.

BUSH 2718 IF PANEL (EXPORT VERSION) £5.75 p.p. 80p.

BUSH A816 IF PANEL (SURPLUS) £2.90 p.p. 80p.

BUSH 161 TIMEBASE PANEL A634 £4.40 p.p. £1.25.

GEC 2010 SERIES TIMEBASE PANEL £1.15 p.p. 95p.

GEC 2040 Surplus Panels, ex-rental. Decoder £5.75 p.p. £1.25.

DECCA CTV25 Single Stand. IF Panel £4.40 p.p. 75p.

DECCA Colour T.V. Thyristor Power Supply. HT, LT etc. £4.40 p.p. £1.40.

BUSH TV 312 IF Panel (Single I.C.) incl. circuit £5.75 p.p. 75p.

BUSH TV Portable Eleven Volt Stab. Power Supply Unit £4.40 p.p. £1.10.

PYE 697 Line T.B. P.C.B. for spares £3.68 p.p. £1.25.

THORN 3000 VID, IF, DEC, FTB SALVAGED £5.75 ea. p.p. £1.00.

THORN 8000/8500 POWER/SALV. SPARES £2.88 p.p. 60p.

THORN 8000/8500 TIME BASE, SALV., SPARES £5.52 p.p. 90p.

THORN 9000 LINE T.B. SALV., SPARES £8.62 p.p. £1.38.

MULLARD AT1022 Colour Scan Coils £6.90 p.p. £1.30, AT1023/05

Convergence Yoke £2.90 p.p. 95p, AT1025/06 Blue Lat. 90p p.p. 40p, Delay

Lines, DL1E £1.00, DL50 £4.00 p.p. 80p.

PHILIPS G9 Signal Board Panels for small spares £4.80 p.p. £1.00.

PHILIPS G9 Signal Board Panels for small spares £4.80 p.p. £1.15.

etc., and circuits £4.25 p.p. £1.20, or incl. yoke, £5.65. G8 Decoder panels

salvaged £4.25. Decoder panels for spares £2.00 p.p. £1.15.

VARICAP UHF MULLARD U321 £8.97, ELC1043/05 £6.35 p.p. 40p.,

G.I. type (equiv. 1043/05) £4.00 p.p. 40p. Control units, 3PSN £1.40, 4PSN

£1.75, 5PSN £2.00, 6PSN £2.10, Special Offer 6PSN £1.15 p.p. 40p.

TAA 550 58p p.p. 20p. Salv. UHF varicap tuners £1.75 p.p. 40p.

BUSH "Touch Tune" assembly, incl. circuit £5.75 p.p. 85p.

VARICAP UHF-VHF ELC 2000S £9.80. p.p. 75p.

VHF ELC 1042 £6.90 p.p. 40p.

UHF/625 Tuners, many different types in stock. UHF tuners transisted. incl.

s/m drive, £3.28. Mullard 4 position push button £2.88 p.p. £1.10 Ae Isol

70p p.p. 25p.

TRANSISTORISED 625 IF for T.V., sound, tested. £7.82 p.p. 75p.

RBM 774 250R Mains Droppers, four for £1.15 p.p. 40p.

LINE OUTPUT TRANSFORMERS. New guar. p.p. 95p.

BUSH 145 to 186SS series £8.50
 BUSH, MURPHY A816 series £9.80
 DECCA DR 121/123, 20/24, MS1700, 2001, 2401 £8.50
 DECCA MS2000, 2400 £6.70
 FERG., HMV, MARCONI, ULTRA 900, 950, Mk. 1 950II, 1400, 1500, 1580 £6.80
 GEC 2000, 2047 series, etc. £8.50
 INDESIT 20/24EGB £8.50
 ITT/KB VC2 to 53, 100, 200, 300. £8.50
 MURPHY 1910 to 2417 series £8.50
 PHILIPS 19TG170, 210, 300. £8.50
 PYE 368, 169, 769 series £8.50
 PYE 40, 67 series (36 to 55) £7.85
 PAM, INVICTA, EKCO, FERRANTI equivalents as above.
 SOBELL 1000 series £8.50
 STELLA 1043/2149 £8.50

SPECIAL OFFER

BUSH TV 125 to 139 £3.25
 GEC 2114J/FINELINE £5.50
 GEC 448/452 £1.75
 THORN 1590/1591 £5.50
 KB VCL, VCII (003) £3.25
 MURPHY 849 to 939 £3.25
 COLOUR LOPTS p.p. £1.10.
 BUSH 182 to 1122 etc. £11.30
 MURPHY Equivalents £11.30
 DECCA "Bradford" (state Model No. etc) £10.15
 GEC 2028, 2040 £11.30
 GEC 2110 Series £12.20
 ITT CVC 5 to 9 £7.80
 PYE 691, 693, 697 £20.50
 PHILIPS G8 £10.15
 THORN 3000/3500 (Scan or EHT) £7.85
 THORN 8500 £12.50

OTHERS AVAILABLE. PRICES ON REQUEST.

THORN MONO SCAN COILS (850 to 1500) £3.25 p.p. 95p.

THORN 950 3 Stick Tray £1.15 p.p. 55p. Other Available.

6-3V CRT Boost Transformers £3.70 p.p. 85p., Auto type £2.10 p.p. 50p.

CALLERS WELCOME AT SHOP PREMISES (Tel: 01-794-8751)

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE NOT NORMALLY ADVERTISED

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Sta. (Bakerloo & Jubilee)

W. Hampstead British Rail Sta. (Richmond, Broad St.) (St. Pancras, Bedford) Bus Routes 28, 159

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

ALL PRICES INCLUDE VAT AT 15%

CAMPBELL ELECTRONICS Limited

Unit E5, Halesfield 23
Telford, Salop
TF7 4QX

Tel: Telford (STD 0952)
585799/584373

Telegrams: CAMELEC

Telex: CHAMCOM 35191

WHOLESALE DISTRIBUTORS OF SPECIALISTS SPARES TO RADIO & TELEVISION SERVICE DEPTS; NATIONWIDE

SEND FOR OUR FULL CATALOGUE AND PRICE LIST

Your source to better components

TRANSISTORS											
each		each		each		each		each		each	
AC127	26	AF239	70	BC119	25	BC173	14	BC464	60	BD150B	40
AC128	25	AF2795	59	BC125	12	BC178	17	BC465	60	BD150C	80
AC141	26	AL102	150	BC126	14	BC179	20	BC547	09	BD163	70
AC142	27	AL113	150	BC135	16	BC182L	10	BC548	09	BD166	46
AC153	36	AU103	210	BC136	17	BC183L	10	BC549	09	BD181	77
AC176	28	AU106	166	BC139	25	BC184L	10	BCX31	27	BD182	70
AC187	27	AU107	166	BC139	25	BC186	21	BCX32	20	BD183	78
AC188	27	AU108	207	BC140	28	BC187	10	BCX33	20	BD187	65
AD149	87	AU110	150	BC141	28	BC212L	10	BCX34	30	BD201	80
AD161	35	AU111	217	BC142	23	BC213L	11	BCX36	26	BD222	48
AD162	35	AU112	217	BC143	25	BC213L	11	BCY70	17	BD225	48
AF115	28	AU113	158	BC147	10	BC214L	11	BCY71	16	BD232	45
AF116	28	AU110	129	BC148	09	BC237	12	BCY72	13	BD233	47
AF117	28	BC107	11	BC149	11	BC238	11	BD115	36	BD234	45
AF118	68	BC108	10	BC153	11	BC239	10	BD116	59	BD237	50
AF125	36	BC109	11	BC154	11	BC307	12	BD131	37	BD238	50
AF126	37	BC114	13	BC158	11	BC338	12	BD135	36	BD509	55
AF127	37	BC114	13	BC158	11	BC338	12	BD135	36	BD509	55
AF139	48	BC116	13	BC160	26	BC384LC	21	BD136	30	BD510	40
AF178	85	BC116	13	BC160	26	BC384LC	21	BD136	30	BD510	40
AF180	158	BC117	13	BC170B	20	BC461	27	BD140	39	BDX32	170
AF181	160	BC118	13	BC171	10	BC462	65	BD144	136	BF115	29
				BC172	13	BC463	65	BD150A	40	BF121	21

THYRISTORS, SILICON SWITCHES, DIACS

BFT42	35	BT109	1.16
BFT43	33	BT110	1.16
BR100	19	BT116	1.16
BR101	30	BT119	2.95
BRC4443	72	BT120	1.99
BRY39	39	CT106D	46
BT106	1.16	OT112	1.20
BT108	1.30	TC146	39

BRIDGE RECTIFIERS

BY164	40	KBS01	74
BY179	58	WO2	29
BYW21	1.96	WO4	27
BYW24	2.32	WO6	35
BYW61	3.05	BR1	26
BYW62	3.17	BR2	37
BYW64	3.97	BR3	43
ITT3CD	38	BH4	42

DIODES AND RECTIFIERS

AA112	12	BA115	11
AA116	14	BA145	16
AA117	13	BA155	11
AA119	06	BA156	09
AA143	10	BA202	09
AA144	07	BA219	08
AY102	1.54	BA316	20
AY106	1.41	BA317	20
BA102	33	BA313	04
BAX16	05	BY206	15
BY129	10	BY207	20
BY210	400	BY210/800	21
BY176	1.24	BY227	28
BY182	87	BY251	20
BY184	30	BY255	24
BY187	70	BY298	40
BY199	26	BY299	40
BY199	26	BY299	40

ZENER DIODES

IN4007	07
IN4148	03
IN4448	17
IN5400	13
IN5404	15
IN5408	16
IT144	04
ITT2002	13

400mW BZ88 TYPE 10"
1W BZX61 TYPE 13"
Values 3.3V 200V
10W (STUD MOUNTING) 1.28
Values 4.7V 200V

INTEGRATED CIRCUITS

BRCM200	3.34	SN7273L	1.68	TBA651	2.97
BRCM300	3.42	SN76003N	1.40	TBA673	2.10
BHC1330	80	SN76013N	1.10	TBA690	2.80
BTT782	5.21	SN76013ND	1.05	TBA700	1.60
BT76018	1.97	SN76023N	1.10	TBA720A	2.40
C590	2.67	SN76033N	1.05	TBA750	1.39
CA270AE	2.86	SN76033N	1.40	TBA800	1.00
CA270BE	2.70	SN76110N	1.60	TBA810AS	1.38
CA505	1.30	SN76226DN	1.79	TBA810S	2.22
CA75BE	3.40	SN76227N	1.08	TBA820	95
CA920A	1.96	SN76228N	1.85	TBA890	3.94
CA121	1.80	SN76530P	1.47	TBA920	2.20
CA3089E	3.40	SN76532N	1.38	TBA940	3.09
CA3090Q	1.45	SN76533N	1.50	TBA9502A	3.07
ET76016	2.10	SN76544N	1.40	TBA970	2.94
ETT76016	2.10	SN76546N	2.89	TBA990	1.65
LM1351	1.95	SN7666E	1.27	TBA144X	3.33
LM1370	1.78	TAA350A	1.89	TBA144	3.33
MC1307P	1.69	TAA550A	27	TC4270	1.95
MC1310P	1.11	TAA550B	27	TC4270S	2.24
MC1327AP	2.67	TAA550C	27	TC4290A	3.23
MC1327P	1.20	TAA570	1.80	TC4420A	2.04
MC1330P	65	TAA591	1.98	TC4440	1.98
MC1349P	1.99	TAA611B	2.48	TC4640	2.97
MC1351P	1.20	TAA630S	3.40	TC4650	3.42
MC1352P	1.20	TAA661B	1.80	TC4730	3.32
MC1388P	1.20	TAA700	2.90	TC4750	2.43
MC1724CP	1.36	TBA731	1.29	TC4800	2.20
ML237B	1.97	TBA240A	4.60	TC4820	2.27
SA4570	1.98	TBA325	1.57	TC4830S	2.13
SA4700	3.91	TBA395	1.85	TC4900	1.48
SA560S	1.75	TBA396	1.60	TC4910	1.80
SA5570S	1.75	TBA440C	3.33	TC4940	1.48
SA5880	2.45	TBA440N	3.33	TC4900P	3.54
SA5990	2.45	TBA480	1.00	TD4440	3.30
SA5960	3.41	TBA500	1.65	TD4440N	3.33
SC9503P	1.41	TBA511	1.65	TD41170	3.31
SC9504P	1.45	TBA520	1.95	TD41412	1.10
SC9506P	2.69	TBA540	1.23	TD42521	2.66
SL437F	5.99	TBA540	1.40	TD42530	2.20
SL9018	4.60	TBA550	1.80	TD42560	2.15
SL917B	5.85	TBA560C	2.00	TD42590	2.18
SL918A	4.56	TBA570	1.50	TD42600	2.74
SN16848N	1.99	TBA641A12	1.65	TD43950	2.57
SN16851NG	1.99	TBA641B11	2.70	TMS3848NC	4.37
		TBA641B1X	2.25	TK33A	77

EHT MULTIPLIER TRAYS

TCE1400 (5 Stick)	3.08	TCE3000 3500	5.55
TCE1500 (3 Stick)	2.47	TCE4000	5.20
TCE1500 (5 Stick)	3.08	TCE8000	2.76
ITT CVC 5,7,8 & 9	4.80	TCE9000	5.10
ITT CVC 20,30	5.40	TCE9000	6.45
GEC 2110	4.80	RR1 Dual Standard CTV	6.50
GEC 2100	5.95	RR1 A823	5.70
GEC 2200	4.80	RR1 2718	4.80
PYE 691,693	4.49	GRUNDIG 5010/6010 B&O	4.95
PYE 731 (4 lead)	4.90	GRUNDIG 3000	4.95
PYE 731 (5 lead)	4.85	KORTING	4.95
PHILIPS 520 540,550	5.50	SIEMENS TVK31, 512	4.75
PHILIPS 550 (long lead)	4.80	SABA/TFK/SITA/DORIC	4.75
PHILIPS 59	4.80	STANBERG TV2, TVC M6	4.90
DECCA CS1730 1830	3.65	EUROTRAY	4.65
DECCA CS2030 2230 etc.	4.80	CONVERSION BRACKET A	25
DECCA CS1910 2213	4.80	CONVERSION BRACKET B	25
DECCA 80/100 Teletip	5.20	TV18 EHT STICK	92

VARICAP TUNERS, DELAY LINES, CRYSTALS, etc.

ELC 1043 05	7.40
ELC 1043 06	7.40
U321 (Philips G11)	7.00
Delay line DL50	2.00
Delay line DL60	3.00
Luminance Delay Line For TBA560	1.50
Transductor AT4041/37	1.68
Linearity Coil AT4042/02	1.00
Linearity Coil AT4042/04	1.00
Colour Crystal 4 433619 M Hz	1.18
Focus Resistor (Thick Film)	80
10M 30M 47M	80

SERVICE AIDS

SERVISOL	66
FREEZER	66
AIR SPRAY CLEANER	75
FOAM CLEANER	65
SILICONE GREASE	69
SOLDER MOPS	60

TEST EQUIPMENT

POWER SUPPLY 0-30V	
0 1A PS301	48.50
POWER SUPPLY 5-18V	
0 2A PS202	48.50
POCKET SIGNAL INJECTOR (Requires U7 Type Battery)	1.90

REPLACEMENT DROPPERS

PHILIPS G8	45
PHILIPS G8 (47R)	35
PHILIPS 210	54
TCE 1500	78
GEC 201B	58
RR1 640	51
TCE 8000A	57
DECCA 20	1.03
PYE 731	66
TCE 1400	81
RR1 A823	70
GEC 2110/41R	41
GEC 2110/12RS + 12RS	47
TCE 3500	65

REPLACEMENT COLOUR TUBES (Two year guarantee)

17" A44 271X 90°	32.50	25" A63 200X 90°	37.00
18" A47 342X 90°	32.50	26" A66 120X 90°	37.00
19" A49 11X 90°	32.50	26" A66 140X 110°	40.00
19" A49 191X 90°	32.50	26" A67 120X 90°	37.00
19" A49 200X 90°	32.50	26" A67 150X 110°	42.50
20" A51 110X 90°	32.50	SPECIALS TO ORDER	
22" A55 14X 90°	32.50		
22" A56 120X 90°	32.50	NEW MONOCHROME TUBES	
25" A63 11X 90°	37.00	20"	13.00
25" A63 120X 90°	37.00	24"	14.00

IN OUR OPINION THESE ARE ONE OF THE HIGHEST QUALITY RE-PROCESSED TUBES AVAILABLE. THEY INCORPORATE A HARD CATHODE OFFERING HIGH DEFINITION, LONG LIFE AND RELIABILITY.

COLOUR TELEVISIONS DECONTROLLED (Guaranteed)

RANK A823 SERIES	60.00 TO 70.00
RANK A823A SERIES	75.00 TO 80.00
RANK A823AV SERIES	84.00 TO 94.00
DECCA SERIES 10,30	75.00 TO 83.00
THORN 3000-9000 SERIES	70.00 TO 95.00

Other makes are available to order and quantity discounts may be arranged.
T.V. Trolley Stand 22" - 594mm 26" - 662mm. Suit all makes. £7.50.
SERVICE AND SOAK TESTED BEFORE DESPATCH. THESE RECEIVERS ARE OF THE HIGHEST QUALITY AVAILABLE AND ARE GUARANTEED FOR THREE MONTHS - New cathode ray tubes fitted if specified, however original C.R.T. must meet our high standards of specification compatible with the age of the receiver, before despatch.
THESE ARE READY TO BE INSTALLED IN YOUR CUSTOMERS HOMES. (Delivery service mainland U.K.)

Telephone - TELFORD STD (0952) 585799/584373

ORDER VALUES LESS THAN £10.00 PLEASE ADD 40P P & P.
ALL PRICES QUOTED ARE NET. EXCLUSIVE OF VAT. PLEASE ADD AT 15% (ANYTIME)


flywheel sync/line oscillator circuits were replaced, but the fault persisted. I then decided to take a look at the sync separator circuit, which is on the i.f. panel. It turned out that the high-value ($4.7\text{M}\Omega$) bias resistor R33 between the base of the sync separator transistor and the 205V line had gone open-circuit.

The other fault was on a Thorn 1500 chassis which displayed a perfect picture except that approximately two inches from the bottom of the raster two or three lines were paired, with a peculiar small kink which looked like a triangular pulse about three-quarters of the way along the paired lines (see Fig. 4). The culprit turned out to be C37 ($64\mu\text{F}$) which couples the video signal to the base of the video output transistor. It seemed all right on test however, charging up perfectly via an Avo 8 on the times 100 range – a nice, smooth steady climb to $10\text{M}\Omega$ or thereabouts.

*D. Hewitt,
Havant, Hants.*

Editorial note: The high-value resistor is included in the sync separator's base circuit to ensure that it's driven to saturation by the sync pulses. The trouble given by the video coupling electrolytic capacitor could possibly be due

Fig. 4: Unusual fault condition experienced on the Thorn 1500 chassis. Linearity otherwise perfect.

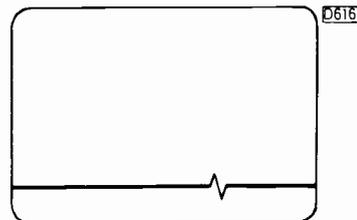

to its inductance – or has anyone any other ideas on this one?

PYE SOLID-STATE COLOUR CHASSIS

Further to Mike Phelan's comments on the Pye large-screen solid-state colour chassis (731 etc.), I've found that a leaky field output transistor (VT688) can cause a very rapid reduction of the scan down to two-three inches, with a linear scan. If the field scan reduces in this way, check the field output transistor's heatsink: if the temperature is high, the transistor is suspect.

*S. J. Humphreys,
Welwyn, Herts.*

Don't Ask Why

Les Lawry-Johns

WHEN women start asking questions, they never stop. Take the other night for instance.

"Why is it warmer in the summer than in the winter?"

Now I'm not going to be taken in by a simple question like that. There just has to be something behind it. But I thought I'd play along.

"Because the earth tilts and we see more of the sun up this end. In other words, it comes up earlier and goes down later and they see less of it down South America way, until it's our winter and then it's their turn to see more of it and we see less, you see."

"When do we start seeing less of it?"

"Oh about the middle of June or something – you know, the longest day."

"Well, if we see less of it after that, why does it always seem warmer two months later, in August?"

"Er, well, you see, by then the sun has warmed up the places which were cold when it arrived. So whichever way the wind blows, it's always warm until these places start cooling down again. Say in September, when it starts getting a bit nippy. Something to do with Arctic Terns so they say."

"So the best time to buy a new coat is in the Autumn then, say about now?" I might have known. So I thought it was my turn to ask silly questions and during the day, instead of concentrating on the work, I was trying to dream up something daft.

It's All Yellow

It was a Thorn 8500 chassis with the complaint of "previously changing colours, now all yellow" (i.e. no blue). So naturally we leapt at the blue output stage to see whether the voltages there could tell us anything. They couldn't. The base, emitter and collector readings were more like those in

the red and green stages than they were themselves . . . well, you know what I mean. They couldn't be faulted. So we leapt where we should have leapt in the first place, to the tube base, and checked the first anodes. If anything, the blue first anode was slightly higher than the other two. Check the cathodes we said, and did. Instead of being high, the blue cathode voltage was slightly low, which should have meant more blue on the screen.

My mistake of course was not looking in the mirror when I took the readings. But I had my glasses off to peer closely at the meter, and when I put them back on to look up the test prod was no longer on the blue cathode.

To my befuddled mind it now seemed that the tube had lost emission on the blue gun, so I bunged on the tube tester. Not too good it said, but not too bad either. About the same as the green and red guns. What more do you want?

I was rapidly getting fed up, and when my honey bunny asked what I wanted for lunch I snapped nastily "a turkey egg".

This was it, the daft question I'd wanted since last night. "Don't be silly" she said. "Whoever heard of a turkey egg for lunch?"

"I'll have it tonight then."

"Don't be stupid, you can't buy turkey eggs."

"Why not? There are millions of turkeys around doing nothing until some bank holiday – except gobbling food and making funny noises."

"Well I've never seen them for sale. You deserve beans on toast."

So back we went to the 8500 and its missing blue. This time I happened to look in the mirror as I took the voltage readings on the cathodes. Red o.k., green o.k., blue slightly low and the screen became blue and remained so until the meter prod was removed.

Moving back to the output transistors, the blue collector was correct and the meter made no difference. Obviously the choke between the collector and the tube's cathode was open-circuit. It wasn't. But there was no continuity from the choke to connector 7/3 which takes the blue drive to the tube. My bleary eyes couldn't see any crack in the print, but a jump lead restored normal working.

Voltage readings can be misleading if you don't look in the mirror at the same time to see the effect of the meter on the circuit. The trouble with looking in the mirror of course is that you stand a chance of seeing yourself peering over the top of the set. Then you know just how dozy you look when you're trying to concentrate. Not a pretty sight.

More on the Pye Hybrids

Every time we look round there seems to be a Pye 691, 693 or 697 needing attention. One caught me nicely the other day. It came in for "wrong colour". This was putting it mildly. The grey scale seemed reasonable enough, but when the colour was turned on it was horrible beyond description.

Checking the PCL84 colour-difference output valves didn't produce much joy, although one was definitely low-emission – and leaky to boot. A check on the 12kΩ pentode anode load resistors then revealed that two of the three were open-circuit, which was a promising start. We were out of 12kΩ wirewounds of course as I'd forgotten to order any, but as we seemed to have plenty of other values we decided to fit three 10kΩ resistors and see what the picture then looked like.

At first sight it didn't seem too bad, but when the colour was turned up much the newsreader's face turned green and looked decidedly sick due to a horrible hum bar. So we checked the earthing of the panel, screening of leads, and everything except the right thing of course. We had already checked for the presence of clamp pulses at the yellow plug on the CDA panel – only briefly, in view of the fair grey scale. In the end we took a closer look at the d.c. clamping, and found that although the pulses were arriving at the yellow plug there was a poor contact between the socket and the series capacitor C372, thus leaving the triodes virtually unclamped. With the clamping restored, we could turn up the colour and only maximum contrast would produce hum bars of any mention.

Another Silly Question

We had to call on Mrs. Allnutty whose Doric was dicey (no raster). The line output stage was overheating, and this proved to be a faulty tripler. Whilst we were struggling to fit the new one, Mrs. Allnutty carried on with her decorating and was engaged in mixing paint, or rather was preparing to mix some. She had a fine tin of white satin gloss which she tipped into a large tin. As she did this, she chatted.

"I'm not keen on brilliant white paint. I much prefer a touch of colour, and I do like a very delicate green tint in the white to contrast with the Avacado. Trouble is, I'm right out of green paint. Do you think this emulsion will mix in all right?"

You could have knocked me down with a feather. Mix emulsion with paint?

"You can't do that Mrs. Allnutty. They just won't mix, and if they do they'll separate afterwards. Oil and water you see."

"What do you mean, separate afterwards?" Mrs. Allnutty asked in a worried voice.

"Well, if you painted that door with it, the white would

go to the top and the green would go to the bottom, so you'd have a two toned door."

"That sounds a bit daft to me" said Mrs. Allnutty. "I painted the door and skirting in the other room with it yesterday, and it's still all right."

"It might be all right now Mrs. A" I explained, being an expert on telling my wife how she should decorate our own place. "You wait until er, well, you wait. They don't call me Lowery for nothing you know."

"Well I'm going to mix it, and I'm going to paint the woodwork in here with it like I did in the other room, whatever you say."

She did. And it looks all right.

A New Servicing Hazard

Jeff phoned the other day to acquaint me with a hideous new aspect that's entered upon the servicing scene. You know how touch tuner channel selectors and their attendant circuitry can often present problems due in some part to the high impedances involved? Obviously any additional conductive material will do the circuitry no good at all.

Apparently Jeff had a Thorn 9000 in for service which included fitting a new tube. The job finished, the set was placed on the lowest storage rack to await collection. His dog inspected the various sets and finding that the 9000 carried a challenging smell he naturally cocked his leg and sprayed the touch tuner, then with a sniff trotted off without telling Jeff.

Some time later the set was put on the bench for a pre-delivery check. The full horror of what had happened burst on Jeff as soon as he saw the front of the tuner selectors. Needless to say they were totally inoperative. Thinking that it was just a matter of cleaning the sensors and drying out, Jeff merely kicked the dog and told him not to hiss over the sets anymore or he would be seen to. Alas a thorough cleaning of the touch tuner panel resulted in no improvement at all. The internal works had received a lethal dose of whatever it is that spells doom to touchy components and printed panels. No amount of cleaning and drying out restored reliable selection, and Jeff had no option but to replace all affected parts.

Particularly beware of ladies with two small dogs on leads. We know only too well that they attempt to outdo each other against any vertical surface in a strange place, and our shop is certainly a strange place. Fortunately there were no touch tuners around at the time. The fact that she had recently purchased a new unit audio and a colour set from us saved the dogs from our wrath. When I had occasion to call at their home recently I resisted the temptation to . . .

Too Fast, too Slow

A Ferguson studio something or the other music centre came in with the complaint that the records played too fast and the tapes too slow, with the weird result that records could be taped reasonably but the radio recordings were hopelessly wrong, records sounded like the Chipmunks and prerecorded cassettes of Maria Callas sounded like Paul Robeson.

Being used to funny things and people, we were not disturbed and immediately dealt with the record fault by clearing off the rubber deposit on the motor spindle. This restored its original diameter. The cassette section however was a different kettle of fish (why fish?).

We noticed that when fast forward or rewind was selected, it started at high speed and then slowed and

stopped. A meter showed that the motor voltage fell to zero, although the input to the motor control board remained constant. So we attacked the control board, in the wrong way of course as is our wont or natural bent you might say. Hang on a second. We are not naturally bent, I didn't mean that of course, I mean we usually do things wrong because logic is not one of our strong points. Our strong points are muddle, chaos and panic, in that order.

So we checked the three transistors cold and of course they read right. We then did it right and set the thing going. When it slowed we sprayed each transistor with freezer, and when one received a cooling draft the speed immediately increased. Replacing this restored normal operation.

In other words, a job which should have been done in ten minutes took an hour. Maria Callas now sounded like Maria Callas and on record Jim Reeves sounded like, well, Jim Reeves. I'm not keen on servicing these things: TVs seem so straightforward from a handling point of view.

Bear with Us

One of the nice things about running a personal business is that you deal directly with the customer and the customer deals directly with you (never mind about Laura Lovitt, we're not going into that . . . I mean, we need not discuss our flights of imagination just now). Although this is not always a good thing, in the main it is.

One unexpected facet is that we often receive small gifts as tokens of appreciation – bunches of flowers, pot plants, vegetables in season, the odd bottle of Bell's and lots of other nice things, quite often from people we thought we had upset or who had upset us, which all goes to prove that the milk of human kindness should be spread out even to those you can't stand the sight of at first. However, we received something recently which really shook us, and not only us, but the dog and cat as well.

To be honest I must say that this was from someone in the family, so perhaps it doesn't qualify as from a "customer". It was an enormous teddy bear, over 4ft. tall and 3ft wide (paw to paw), with a head perhaps too large for the body – the sort of thing most people like and most females love (why?). This could not be said for our cat and dog however. The cat took one look, arched her back with every hair extended, spat in defiance and then fled for dear life. Ben came in to see what all the fuss was about and was confronted with an enormous head a few inches away from him as he skidded to a halt. He looked away as if the bear wasn't there, which we took to be a gesture of submission, and slowly slunk away.

Thus our brave animals proved their worth when confronted by Ted, and instead of threatening them with the vet we've now only to say the magic word Ted to obtain instant obedience or at least their temporary absence. Which brings us back to our daily work.

Caught Again

We had a Thorn 3500 that lead us a merry dance the other day. The report was that it had suffered from the "twitters" for some time, the twittering being audible while visually the effect was of corrugated verticals. Someone had been in to fix it and had left it free from the twitters, but within a day or two the whole thing had gone off, the cut-out popping out as soon as the set was switched on. So we collected it and started.

There were no apparent shorts, so we started by unhooking the tripler. The set then came on and stopped on for a while, during which time we checked the 30V line and then

the 60V line which read more like 70V. Before we could do anything else, several things seemed to happen at once, with some smoke and the cut-out coming to the rescue as my reactions are so slow that they cannot be relied on to switch a set off quickly.

The 15Ω resistor in series with the chopper looked sick, while the chopper transistor itself was short-circuit. These items were replaced and the supply lines checked for shorts. The line output transistor was a dead short, and was also replaced. Just to be sure, we wound back the set e.h.t. control so that the 60V line would be under this. The set then functioned up to a point, but the line timebase was still taking too much current – measured by checking the voltage across the beam limiter sensing resistor R907 which was very hot though of the right value.

We eventually changed the e.h.t. transformer, which had shorted turns, only to find that the restoration of full timebase working resulted in severe arcing in the field timebase panel at C434 which is in the c.r.t. grid bias circuit. This resulted in the loss of three transistors and one diode. To cut a very long story short, this transpired to be due to our accidentally moving a capacitor in the line output section up against a tag on the e.h.t. transformer when the latter was replaced.

After this harrowing and self-inflicted experience, we set up the supply lines correctly, noting that the original twittering whistle had returned. We then considered connecting the original tripler, but decided to do this with caution. Rather than clipping the pulse lead on, we left the set on and advanced the clip to it. There was a vicious arc of flame when it got near. So out went the tripler.

With a new one fitted we had a fair picture, but it was marred by the corrugated effect whenever the brightness was turned down. We also noted that it got worse when the 60V line was reduced, and faded away when the 60V line was increased to an unacceptable level. This then was how it had been "cured" by the someone who advertised his services by only a phone number – by setting the 60V line too high. Apart from my bungling with the capacitor against the transformer tags, the "cure" had resulted in the loss of a lot of expensive bits and pieces.

So now we had to find the cause of the twitter and silence it. Something nagged in the back of my atrocious memory. This was a known fault. Surely not the core of a coil? No it wasn't. Check here, there and almost everywhere. Something started saying 0-01, 0-01 in the back of my mind. C631 in the chopper driver transistor's collector damping network was changed and the twitter stopped. Of course! We'd had the same trouble some years ago, but I'd forgotten it so easily. Why don't I jot these things down? Even if I did, I'd probably lose the thing I jotted them down on.

And Yet Again

It was inevitable that the next set would be a similar model (3000 chassis) with corrugated verticals that came and went. A fool to the last, we immediately whipped out the power pack and in a trice had fitted a new 0-01μF capacitor in the C631 position. With a leer of self-confidence, the power pack was replaced in another trice and the set switched on . . . the raster was still rippled of course. We shone a light on the decoder board and there was the core from L502 (h.t. supply choke in the line timebase) just lying there doing nothing – not even shorting anything out. A dab of adhesive and back it went and away went the ripple, hopefully never to return. Why didn't I do that first?

Servicing in the Field

Part 1

George Wilding

FEW vocations can be as demanding technically as that of the TV service engineer, especially if you work for a retailer or specialist repair business. You can be called upon to repair anything from an old all-valve, v.h.f.-only monochrome set to the latest imported solid-state colour receiver which may employ a new and unusual power supply arrangement, remote control and what have you. On top of this, when confronted with one of these latest pieces of electronic wizardry in the customer's home you will be expected to make an instant diagnosis and put whatever's wrong right with a deft adjustment or at most replacement of one or two small components . . . In truth it might take you some time even to find out which stage is which.

If you fish out a service manual and start to study it, even to check up on expected voltages, you'll be thought to be an inexperienced upstart with no real experience of TV sets. After all, "when the set went off next door leaving a white line across the screen the man fixed it in minutes." The present fault may be "only very minor, because the set works fine for about an hour then the colours go funny."

If you persuade the customer that the set requires bench attention, he'll probably expect it to be away for some days and will be quite happy with the use of a loan set. But once you've got the back off in the living room, you're expected to get cracking.

So it pays to give some thought to the best fault-finding procedure to adopt in the field. After many years of practice and experience, I'd say that the following three factors summarise the best approach. First, carefully observe all symptoms, and check for any damaged or overheating components – spotting a discoloured resistor can often save hours of time spent checking voltages etc. Secondly, make the fewest possible simple tests to prove or disprove the operation of suspect sections of the receiver. Finally, check possible faults in order of probability, keeping all service action, in particular component snipping and transistor changing, to the absolute minimum. Servicing efficiency is determined by how few tests are required to trace the faulty component(s).

So what to do? We'll concentrate on older models, since these are the ones most likely to require attention.

No Results

One of the most common faults is a "dead" set, i.e. no sound or raster. Let's say the set is an all valve or hybrid one. First note whether there's any abnormality at switch on – mains switches, whether linked to the volume control or separate, frequently go open-circuit in one or both poles. This is particularly so with earlier Bush/Murphy monochrome sets.

Secondly note whether the valves light up. If not, either no a.c. is reaching the set or there's a break in the heater supply. Don't waste time checking the mains plug fuse. If

there's been a short across the mains input, the set's internal mains fuse will have blown. Again, if this is not readily accessible, don't waste time looking for it – it may well be all right, and in any case it's simpler to make a d.c. continuity check across relevant points. If it can be seen however and has a blackened interior – due to a severe short – you'll probably find that the mains filter capacitor is short-circuit or that there's a heater-cathode short in the boost rectifier or line output pentode. On replacing the fuse, if the resistance across the mains input is just less than the ohmmeter's zero reading the filter capacitor is almost certainly short-circuit. If some resistance is recorded however the boost diode or line output pentode is more likely to be at fault. Mains filter capacitors can sometimes fool one by breaking down when subject to the mains voltage but not when checked by the meter's low test voltage: if in doubt therefore, disconnect it.

A dead short in the mains rectifier's reservoir capacitor or across the rectifier itself will also blow the mains fuse of course, but these are rare occurrences. H.T. shorts usually develop in a circuit fed from the h.t. reservoir capacitor via a resistor, which if of the fusible type may have sprung open to show you conveniently where the fault lies. If not, look for a heat damaged or burnt component. This could well be the screen grid feed resistor of a pentode valve which has an internal short-circuit between its screen grid and the control grid or cathode.

A short-circuit in the line output stage can also blow the mains fuse, though it's more likely to have open-circuited the h.t. feed to the line output stage, giving the "no results" or "sound, no raster" symptoms depending on the circuitry used in the particular model. We'll return to this fault later, but as a quick check to eliminate the line output stage before switching on after replacing the fuse, measure the resistance from the top cap of the boost diode to chassis. A reading of at least 200k Ω should be obtained.

If there's no d.c. continuity reading across the mains plug in either direction – check with the meter connected both ways in case there's a diode in the heater circuit – first ensure that there is d.c. continuity between one of the leads from the plug and chassis, with the mains switch on. This should be the neutral lead of course, but many a mains plug is incorrectly wired. If there's no continuity from either lead to chassis, there's either a break in the appropriate lead or the switch's neutral contacts are failing to make.

Assuming that there's d.c. continuity on the neutral side, place one ohmmeter lead on the live mains plug pin and the other on the highest voltage mains dropper tag or the fuseholder – whichever is most accessible. The odds are that the fuse will be intact, and that moving along the dropper will reveal that one of the sections is open-circuit.

In some sets there's a surge limiting thermistor whose connections may have come away: this is most easily checked simply by putting a little pressure on the thermistor, which may then completely disintegrate.

Complete loss of h.t. in hybrid monochrome and colour sets is thus a simple matter to cure, since the h.t. supply is a simple arrangement consisting of a half-wave rectifier plus smoothing. Sound may still be present if the h.t. feeds to the sound circuits and timebases are separate.

Hum

Unless there's a fault in the set that causes excess current to be drawn, low h.t. voltage accompanied by an increased hum level indicates a low capacitance h.t. reservoir capacitor. Near normal h.t., but with a high hum level, poor field lock, impaired definition and in severe cases a visible hum bar indicates loss of capacitance in the smoothing electrolytics.

Thermal Cut-outs

While the usual method of protection against excessive current demand in the receiver is to use fuses and fusible resistors, one occasionally encounters a thermal cut-out. The one used in Rediffusion/Doric hybrid colour sets is resettable, and operates if either the mains current or the line output valve's cathode current is excessive, breaking the live mains connection to the set. To reset the cut-out, press in and release the button. The cut-out used in GEC hybrid colour sets is connected in series with the line output valve's cathode, removing the supply to the stage when it goes open-circuit as a result of excess current. This gives the no e.h.t. symptom of course, to which we must turn next. Note that cut-outs can themselves be faulty.

No EHT

Perhaps the most common fault with receivers of all types is sound but no raster. This can be due to loss of c.r.t. first anode voltage, or incorrect cathode/grid voltages. The usual cause however is zero or inadequate e.h.t.

We'll take monochrome sets first. The first check should be to see whether you can obtain the usual small arc at the anode of the line output valve – if the anode is beginning to glow visibly red however first change the line oscillator valve. If the line output valve is abnormally cool, try another in case it has very low emission or an internal screen grid or cathode disconnection – if there's an anode disconnection, the screen grid winding in the valve will visibly glow due to its taking several times its normal current, while if the control grid is disconnected the valve will grossly overheat due to lack of bias.

If a replacement valve fails to produce a normal arc at the anode, check that there is ample screen grid voltage. Depending on the siting of the valve and its accessibility, this check can be made with the valve in place or removed. With it removed the voltage recorded should be virtually the h.t. rail voltage instead of the working screen grid voltage of course.

Inability to obtain a normal arc from the pentode's anode, with a known good valve and the screen grid and drive voltages present, could be due to several possibilities. Let's assume for the time being however that such an arc can be obtained, but there's no e.h.t. The next step is to hold the tip of the screwdriver blade just under the top cap cover of the e.h.t. rectifier. This should produce both corona discharge and a really good long arc. Changing the rectifier will usually restore the e.h.t. and picture.

If the arc obtained at the rectifier's anode is little larger than at the pentode's anode however there's either a short across the rectifier's heater, thus overloading the line output transformer, or the transformer's e.h.t. overwinding has shorting turns, preventing it from providing the normal

transformer action. If removing the rectifier results in a bigger than usual arc at its anode cap, then clearly the rectifier itself is at fault and a replacement will restore results.

On occasions you may get a very good arc from the anode cap of a known good rectifier, but only the slightest of sparks from the e.h.t. lead to the tube, the cause being an open-circuit connection to the rectifier's heater inside its insulated valveholder. On still rarer occasions you may find that removing the anode cap from the tube shows that there's ample e.h.t. there, but there's still no e.h.t. when the anode cap is replaced. This means that there's a heavy leak within the tube.

When a tripler is used instead of an e.h.t. rectifier valve, the snap-on connection point is equivalent to the valve's anode, but the pulse waveform supplied to this point will be very much less. Tripler failure in monochrome sets is usually due to breakdown of the stick rectifiers. This produces a characteristic odour. If on the other hand one of the capacitors in the tripler goes short-circuit, the resultant heavy loading on the line output transformer will give the impression that this rather than the tripler is at fault.

Remember that two different types of e.h.t. multiplier are used in the Thorn 1500 chassis, a doubler which gives 15kV and is coded with a pink or green sticker, and a tripler giving 20kV and having a white sticker. It's possible to fit the wrong type: when the 15kV type is fitted in a 20kV chassis the picture is too big, while using a 20kV type in a 15kV chassis produces the opposite effect, often accompanied by an occasional spark over from the tray to the adjacent electrolytic can.

Colour Sets

When dealing with sound but no raster in a hybrid colour set, the first move should again be to check for the presence of a pulse waveform (spark) at the anode of the line output valve. If this is normal, check at the feed point to the tripler. Adequate tripler input but no output usually means that the tripler is defective, but missing c.r.t. first anode voltages, excessive cathode voltages or inadequate grid voltages caused by a fault in the clamping circuitry in the colour-difference output stages will also black out the screen. As with monochrome receivers however the probability is that the cause of the blank screen is zero or inadequate e.h.t.

This can be indirectly checked by shorting together the grid and cathode pins of any one of the c.r.t.'s guns to remove the bias: if the e.h.t. and first anode voltages are present, this will produce an all red, green or blue raster as the case may be. The red gun pins are probably easiest to use for this purpose – cathode pin 2, grid pin 3 and first anode pin 4, all well away from the high voltage which should be present at the focus pin 9.

If you want to prove positively that e.h.t. is being applied to the tube's final anode and you don't have a pukka probe, the quickest and safest thing to do is to disconnect the anode cap, position it firmly so that it is well clear of earthed points etc., and note the corona. Alternatively, strip about $\frac{1}{4}$ in. from the end of a short piece of stiff e.h.t. cable, coat with solder and shape it into about three-quarters of a circle: push this under the anode connector, and note the corona at the other end.

Naturally such testing should be limited to the shortest possible amount of time, and in fact ample evidence that e.h.t. is present will be provided well before the valves have even warmed up fully. Remember too that the tube's capacitance can hold a considerable charge for a long time after the set has been switched off!

In practice the line output transformers of hybrid colour sets only rarely break down (the most frequent offender

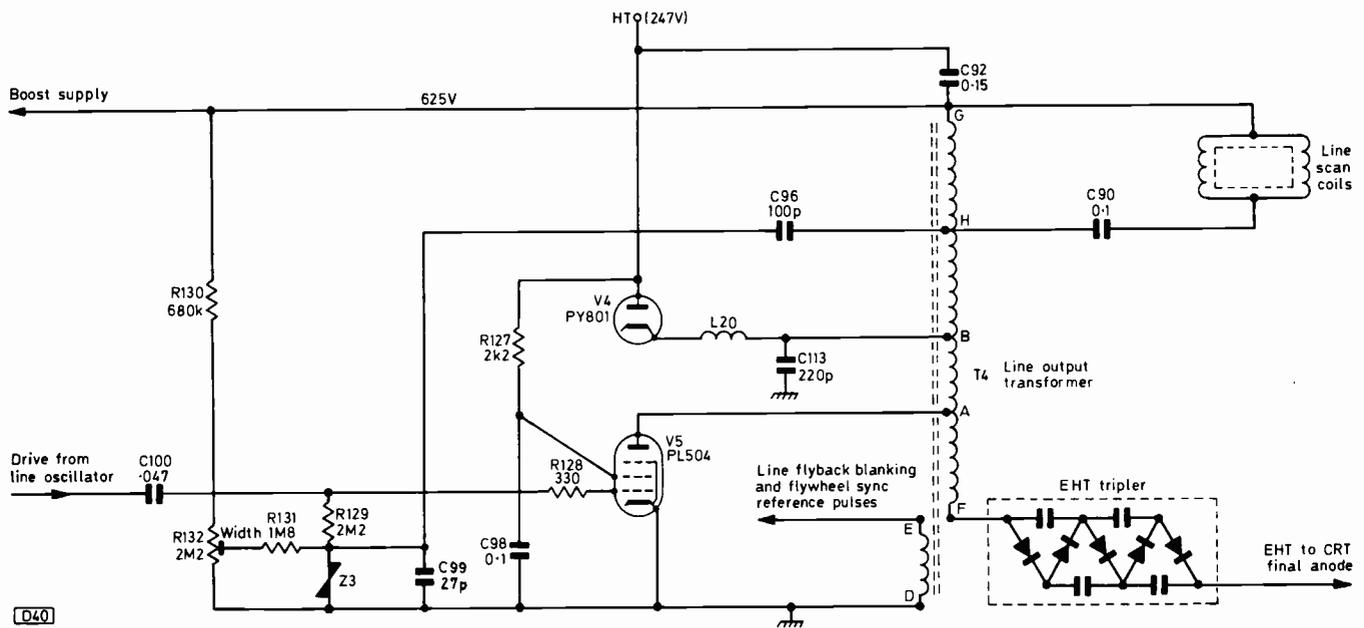


Fig. 2: Typical monochrome receiver line output stage (Thorn 1500 chassis, 20kV version). Check the line output transformer tuning capacitor C113 if a resistance check from the cathode of the boost diode to chassis reveals a short-circuit. This would open R124 (see Fig. 1). The boost capacitor C92 is returned to the h.t. rail and will thus give the sound, no raster symptom when it goes short-circuit.

being the Pye chassis), boost capacitors and 8 or 12kV ceramic tuning capacitors (and the first anode supply reservoir capacitor in the Pye chassis) giving the most trouble. The ITT chassis are particularly prone to tuning capacitor failure. Never replace 8kV disc types with the tubular varieties – they always break down. Use 12kV types wherever possible. It's important to use exact value

replacements. Apart from causing reduced or excessive width, incorrect value transformer tuning capacitors can lead to excessive flyback pulse amplitude with possibly damaging effects upon the transformer and the tripler.

As with monochrome receivers, the line scan coils very rarely give trouble. When they do develop shorted turns, the symptom is much more likely to be readily recognisable raster distortion rather than loss of e.h.t.

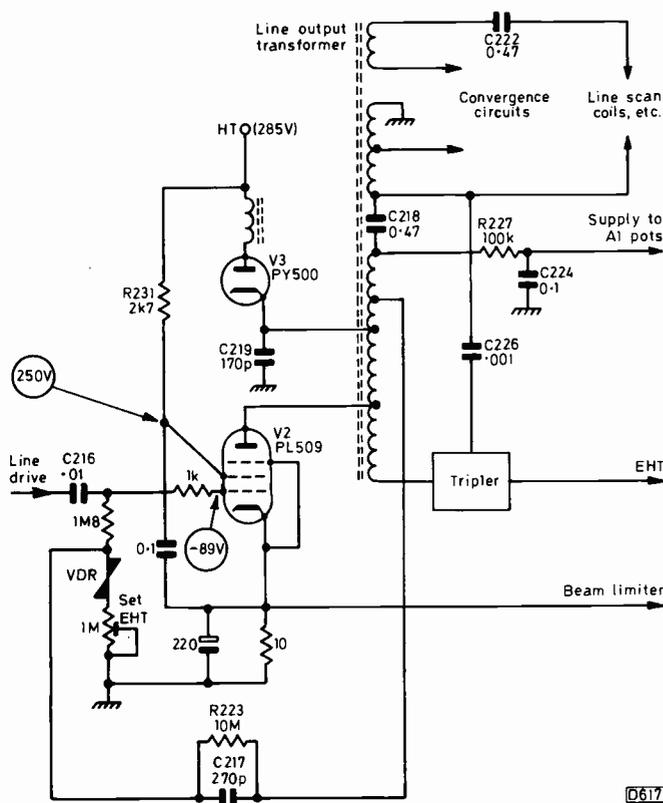


Fig. 3: Simplified circuit of the line output stage used in Pye hybrid colour chassis. This time the boost capacitor (C218) is returned to chassis. There is no h.t. fuse in this chassis, nor any fusible resistors in the h.t. supply. As a result, a short-circuit in C219, C218 or C224 will blow the mains fuse.

Lack of Width

Particularly in monochrome receivers, lack of width is usually caused by a major increase in the value of one of the high-value resistors in the width circuit which biases the control grid of the line output valve. The quickest way to check suspects, which will typically be 4.7MΩ, 8.2MΩ or even 10MΩ, is to shunt them with the meter (20kΩ/V) switched to the 250V or 500V range – it will then be equivalent to a 5MΩ or 10MΩ resistor. Even without a manual, it should be easy to spot these resistors in the v.d.r. circuit. If shunting one of them with the meter set to a range giving a comparable resistance value greatly increases the width, the resistor is almost certainly at fault. Even if the resistor hasn't increased in value, shunting it with the meter will increase the width to some slight extent of course, but a marked increase in width is a sure indication of value change, which will be confirmed by fitting a replacement. In Decca hybrid sets (10 and 30 chassis) check R453 (330kΩ) which tends to fall in value.

On occasion, insufficient width can be due to the line generator valve producing an output pulse of insufficient amplitude or incorrect shape. If a new valve fails to cure the trouble, the working voltages in the stage will be found to be below normal.

Field Timebase Faults

Valve field timebase circuits in monochrome receivers are responsible for almost as many service calls as the line timebase circuits, though they are usually much easier and inexpensive to put right. The valve field timebase circuits

used in hybrid colour receivers on the other hand are very reliable.

Probably the most common complaint is intermittent or complete field collapse due to a defective PCL805 field timebase valve: if the horizontal white line displayed has some curvature to it however, resembling a flattened sinewave, then the scan coils are probably disconnected at a plug and socket or the miniature v.d.r. in series with them is open-circuit.

The next most common complaint is possibly weak field hold, the oscillator valve (again probably the PCL805) being the first suspect. Should a replacement fail to effect a cure, the interlace diode feeding the sync pulses to the stage, impaired h.t. smoothing, or inadequate video output valve or sync separator screen grid decoupling must be considered. Check too for discoloured resistors around the video output stage – being carbon types and passing considerable current, they often change value in older sets. This alters the stage's d.c. conditions, usually showing up as distortion of the sync pulses. If the resistors are unblemished, they can be taken to be of the correct value.

In many old ITT monochrome sets weak or non-existent field lock is often due to R63 (330kΩ) going high resistance or open-circuit. This resistor feeds the sync separator's screen grid and the field sync pulse amplifier's anode. Even when it's open-circuit, depriving the sync separator of screen grid voltage, the line hold remains good!

Other causes of weak field sync are a slightly soft i.f. amplifier valve of the EF183/EF184 type, inadequate decoupling of a transistor i.f. stage or strip, or a faulty a.g.c. circuit. When the timebase causes of weak field sync in a hybrid set have been eliminated and suspicion falls on the transistor i.f. and/or video stages the problem, unless a replacement panel is to hand, really becomes a bench job.

In ITT hybrid colour receivers the OA91 interlace diode D46 is worth bearing in mind: it quite often goes short-circuit to give complete loss of field sync, or open-circuit to give no field scan.

If the base of the raster is cramped, first try a new field output valve. If this doesn't correct the fault, check its cathode bias resistor and/or decoupling electrolytic, either of which may have fallen in value. Very often the valve and its cathode bias resistor must be replaced, a fault in one accentuating the deterioration of the other. Top compression can be due to an increase in the value of the cathode bias resistor. In cases of poor linearity, try the presets and if these are in order suspect a component in the feedback loop: if the resistors are unblemished, there is probably a leaky capacitor. Excessive picture size with bad linearity in many Philips hybrid monochrome sets is due to the negative feedback winding on the field output transformer going open-circuit.

A common fault is insufficient height, and in 90% of cases it's due to increase in the value of one of the high-value resistors in series with the height control. This leads to inadequate voltage at the anode of the field oscillator triode. The feed is from the boost rail, and the offending resistor is sometimes in the line timebase section of the receiver. In ITT many monochrome receivers a sudden reduction in height to about two-thirds of the screen is often due to C134 (0.1μF) going short-circuit: the result is that the height circuit is fed from the h.t. instead of the boost supply.

Next Month

So much then for those basic power supply and timebase faults which should be easily dealt with in the field. In the next instalment we'll take a look at the signal side of things.

★ NEW ★ COLOUR BAR GENERATOR

U.H.F. AERIAL INPUT PATTERN GENERATOR CPG6-RF

All Facilities of our PG6RF

PLUS COLOUR BARS.

Produces 7 invaluable patterns.

**Robust, Battery Powered, Pocket Sized Unit,
Plugs Straight into Aerial Socket.**



W H I T E	Y E L L O W	C Y A N	G R E E N	M A G E N T A	R E D	B L U E	B L A C K
-----------------------	----------------------------	------------------	-----------------------	---------------------------------	-------------	------------------	-----------------------

FEATURES:

- ★ CROSSHATCH GRID
- ★ DOT MATRIX
- ★ VERTICALS
- ★ PLUS PAL COLOUR BARS;
ONLY 3 SIMPLE ADJUSTMENTS.
- ★ PG6RF OWNERS; Buy Add-On 'C6' Unit!
- ★ HORIZONTALS
- ★ WHITE RASTER
- ★ GREYSCALE

ORDER NOW!

PG6RF KIT £25.87 BUILT £33.35 – As per TV Review, Jan. 1979


C6 KIT £18.98 BUILT £26.45 – Add-on Colour to PG6RF

CPG6RF KIT £42.55 BUILT £63.25 – Both above combined.

These prices INCLUDE P & P and 15% VAT. Export VHF versions available.

MAIL ORDER ONLY

Quantity Discount
on application

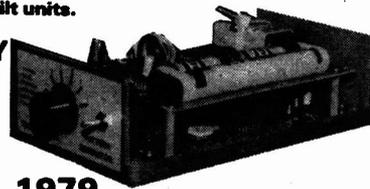

**ACCESS
ORDERS
WELCOME**

ALSO AVAILABLE:

TECS: TECHNALOGICS EXPANDABLE COMPUTER SYSTEM.

Full Colour Teletext; full facility Microprocessor-based, Aerial Input Decoder with extensive computing facilities. The most versatile decoder on the market. Expandable from a simple teletext decoder to a full professional computer/information centre. Send large S.A.E. for details.

**SEND ALL ORDERS OR ENQUIRIES TO TECHNALOGICS LTD. (DEPT. TV)
8 EGERTON STREET, LIVERPOOL L8 7LY. Tel: 051-724 2695.**

Video and Audio Out from the Philips N1700 VCR

David K. Matthewson, B.Sc., Ph.D., and Ian Howarth

REGULAR readers of this magazine will know that students are often taken on in my workshop to give them industrial training experience. One of the present batch has been coming up with some very bright ideas. His latest suggestion was that we add video and audio output facilities to the Philips N1700 VCR. This machine is intended of domestic use, and provides an output at u.h.f. to feed the aerial socket of an ordinary TV set.

We use several of these VCRs for recording long runs of Open University programmes over the weekends, copying the programmes required on to other tapes for the local OU group (yes, we do have a recording licence!). Better quality can obviously be obtained by copying or editing at video levels than at u.h.f., so this modification makes good sense. It also enables the VCR to be used with a video monitor, so that the best possible quality picture is displayed. The sound can be fed to a separate amplifier for use in a large room etc.

So, after putting our heads together, here's the design we came up with (see Figs. 1 and 2). The audio circuit is quite straightforward, consisting of a simple emitter-follower (Tr4) giving an output of about 1V into 10k Ω . The video side is rather more of a problem, since it must provide 1V into 75 Ω (the standard level for TV equipment). There's no suitable point in the N1700 to tap off the required signal, hence the use of a two-transistor amplifier (Tr1-2) with an emitter-follower output stage (Tr3).

The amplifiers require a 12V supply. This, along with the sound and vision signals, can be taken from panel 51 of the VCR - the 12V from pin 3 of socket L1, and 0V from pin 4 of socket L3 or any convenient point on the earth print. The video feed to the amplifier is taken from point M1 and the audio from pin 1 of socket L1.

As we had several of these VCRs to modify, a PCB was designed. This is shown full-size in Figs. 3 and 4. We leave it to the individual to decide upon the type of output sockets to use. Note however that if BNC and DIN sockets are used suitable holes are already provided in the rear of the case. There's plenty of room inside the VCR to fit the PCB, though some minor metal work may be required in order to provide suitable mounting brackets.

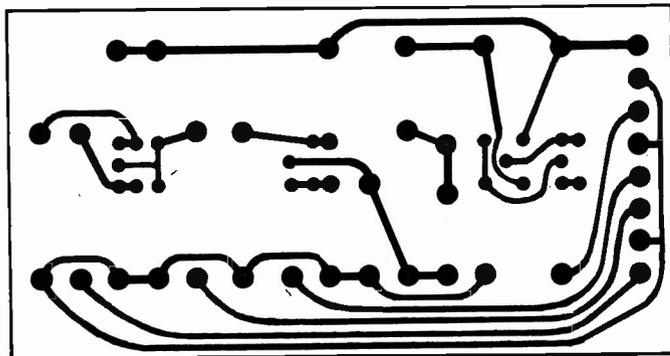


Fig. 4: Full size board layout.

Finally, though the video circuit was designed for use with the N1700 it can be employed wherever an amplifier with a gain of two and an output at 75 Ω is required. ■

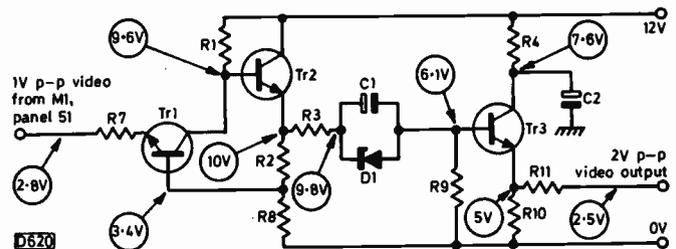


Fig. 1: The video out amplifier.

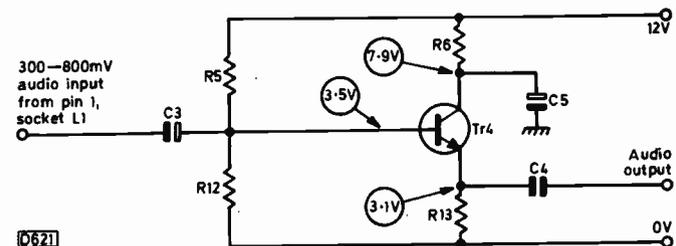


Fig. 2: The audio out amplifier.

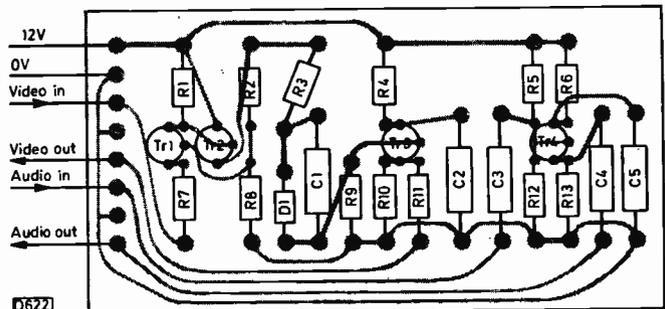


Fig. 3: Component layout on the board.

★ Components list

Resistors:

R1	3.9k Ω
R2	470 Ω
R3	68 Ω
R4	100 Ω
R5	39k Ω
R6	1.8k Ω
R7	330 Ω
R8	270 Ω
R9	2.2k Ω
R10	2.2k Ω
R11	68 Ω
R12	22k Ω
R13	1.8k Ω
All $\frac{1}{4}$ W carbon film	

Capacitors:

C1	47 μ F
C2	220 μ F
C3	22 μ F
C4	22 μ F
C5	22 μ F
All 16V electrolytic	

Semiconductor devices:

Tr1	BC109
Tr2	BC109
Tr3	BC109
Tr4	BC109
D1	BZY88 4V7

Of TTL and CMOS Gates and Cabbages and Kings . . .

Part 1

Andrew Parr, B.Sc., C.Eng., M.I.E.E.

EARLY in 1965 I was given a 7400 TTL chip by my employers and told to find out what it could do. The chip lasted just two days before I managed to destroy it. This started a love/hate relationship with digital logic that's lasted to the present day.

Digital logic is now established in most fields of electronics, and television engineering is a particularly fruitful source of applications. The "Language of Logic" series in the October to December issues of *Television* 1978 provided an introduction to the basic ideas of digital circuits. This article is a follow up, giving practical details of the two most popular logic families, TTL and CMOS.

TTL LOGIC

In the early 1960s the space race was in full flight and it was becoming obvious that electronics would play a vital part in any (hopefully hypothetical) future war. This led to a sudden burst of frontier pushing and, along with Teflon saucepans, the world was presented with TTL. Incidentally, it has been said that two things gave the USA their lead in military electronics: TTL and the management tool called Critical Path Analysis. That's another story however.

TTL emerged commercially in 1964, introduced by a small firm called Texas Instruments. Although logic chips (RTL and DTL) had been around for some time, the performance of TTL was so vastly superior that it swept aside all alternative techniques and rapidly became an industry standard. It still holds that position, which is a tribute to the original design.

Basic NAND Gate Circuit

With the adverts and the history lesson over, we can look at a TTL gate and see what makes it tick. Fig. 1 shows the circuit of a typical TTL gate. At first sight the multiple emitter transistor looks odd, but this is really a shorthand way of drawing the multiple transistors shown in Fig. 2. The circuit is actually quite a good model for anyone who wants to experiment with the innards of a TTL gate.

With both inputs high, current flows through the base-collector junctions of TR1a/b, turning on TR2 and hence TR4. To appreciate this, consider the diode analogy shown in Fig. 3. The output goes to 0V therefore. With any one in-

put low, TR1 acts as a transistor, pulling the base of TR2 down to 0V. TR2 turns off, and TR3 acts as an emitter-follower taking the output high.

Thus with both inputs high, we get a low output; with one input low, we get a high output. The circuit is thus a positive NAND gate.

The output stage is particularly interesting. The so called totem-pole output gives active drive with either a 1 (high) or 0 (low) output. When logic circuitry is being driven at speed, the main constraint is stray capacitance: the active output allows capacitive outputs to be driven with ease.

Logic Families

TTL is actually a common name for a wide range of TTL type gates, the circuit shown in Fig. 1 being the "standard" gate. The main features of a logic system are usually considered to be: (a) speed; (b) power consumption; (c) noise immunity; and (d) simplicity in use.

As mentioned above, stray capacitance is the major restriction on speed. To increase speed, it's necessary to reduce the value of the resistances in the circuit. This increases the power consumption. Initially, TTL was made available in three versions – low power, standard and high speed. Improved techniques have enabled Schottky diodes to be used in the circuit, and as a result two more types have been added. The speed of a gate is defined as the propagation delay, which is the time a signal takes to go from a gate's input to its output. The characteristics of the five TTL families can best be summarised as shown in Table 1.

Which type of gate you choose depends on the application, but the standard series is adequate for most circuits (it's also the cheapest!).

TTL is specified by a multipart code as follows:

- Manufacturer's code. SN is Texas Instruments.
- Specification. 74 is industrial, 0° to 70°C; 54 is Military –55°C to +125°C.
- Type code as in Table 1.
- Device reference: 04 is an inverter, 00 is a quad NAND gate etc.
- Package. N = plastic dual in line.

Work out then what a device coded SN74LS04N is.

TTL in Use

TTL runs on a 5V supply rail, and this is subject to a tight tolerance of $\pm 0.25V$. The supply can rise to 7V before damage will occur, but operation at this voltage is neither recommended or guaranteed.

The nominal value of a "1" output is 3.3V, and in this state the gate can provide a current drive ("source") of 0.5mA. The nominal value of a "0" is 0.25V, and it can draw ("sink") 16mA. This high drive capability allows simple interface circuits to be used when TTL is connected to the

Table 1: TTL Characteristics.

Type	Code	Power consumption	Propagation delay	Speed
Low power	L	1 mW	33nS	3MHz
Standard	–	10 mW	10nS	35MHz
High speed	H	22 mW	6nS	50MHz
Low-power Schottky	LS	2 mW	9nS	45MHz
Standard Schottky	S	19 mW	3nS	125MHz

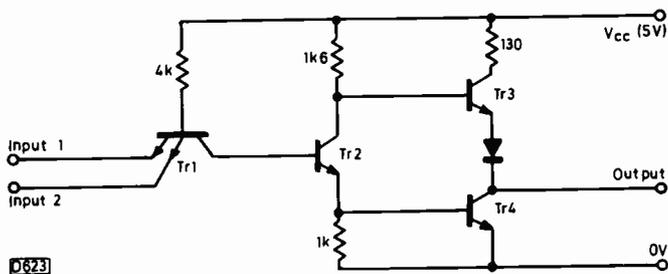


Fig. 1: Standard TTL gate circuit.

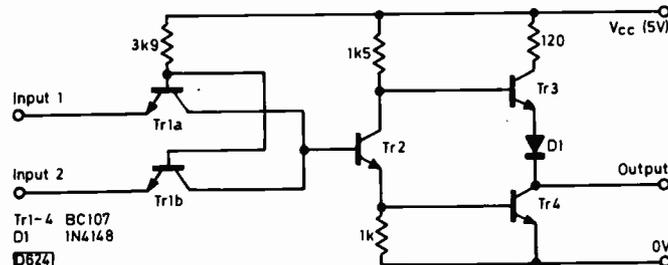


Fig. 2: Discrete component version of the TTL gate.

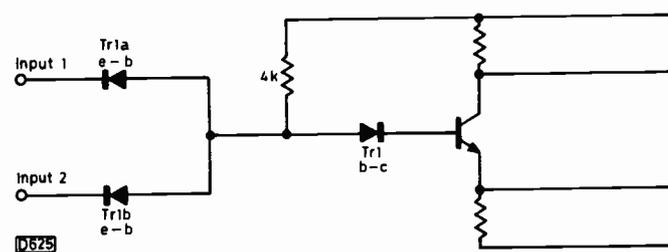


Fig. 3: Diode analogy of the action of Tr1 in Fig. 1.

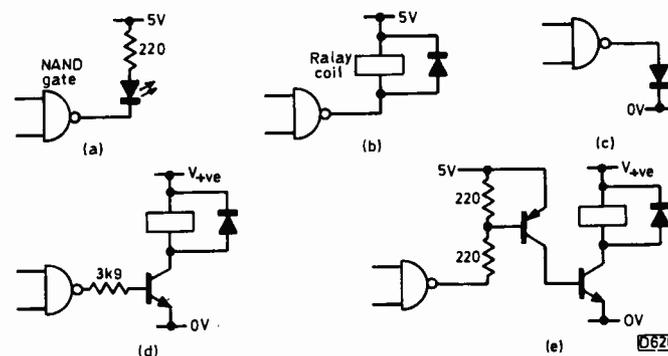


Fig. 4: Interfacing between a TTL gate and an external device. (a) Driving a LED. (b) Direct drive to a reed relay. (c) Alternative LED drive. (d) Driving a high-voltage relay. (e) Driving high current loads.

outside world. Examples are shown in Fig. 4.

TTL is relatively bullet proof, and in my experience will stand having its output shorted to either supply rail for extended periods without harm. There are however several ways of killing the gates.

The first is to let the supply go over 7V. If you are using large amounts of TTL, don't use a simple series regulator which could fail. Use an i.c. regulator or a commercial supply with an over voltage trip. Running TTL on an adjustable supply is asking for trouble – that's how I killed my first gate back in 1965.

The second foolproof method of killing a gate is to take the inputs outside the supply rails. This causes breakdown of the substrate, but is a problem only when you are mixing TTL with circuits operating with higher voltage supplies.

A common problem with all digital systems is noise. This causes memory devices to set, counters to count and monostables to fire – all at the most inconvenient moments.

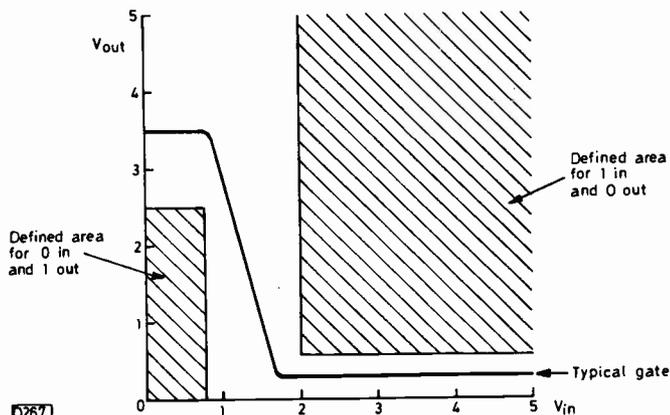


Fig. 5: TTL gate transfer characteristic.

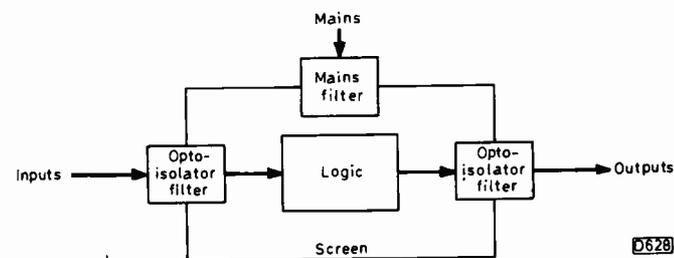


Fig. 6: Last ditch screening to eliminate external noise.

Noise can come from several sources: (a) supply born external (e.g. your deep freeze thermostat); (b) supply born internal, due to current spikes; (c) crosstalk between parallel lines; (d) reflections in long lines.

Before describing these and how to deal with them, we must define noise immunity. We have stated that a typical value for 1 is 3.3V and for 0 0.25V. We must define the lowest possible worst case 1 and the highest possible worst case 0. These are, respectively, 2.4V and 0.4V. We next establish how high we can take a 0 input without the corresponding 1 output going below 2.4V. The data sheet gives the value of 0.8V. If the maximum conceivable 0 level is 0.4V but it can rise to 0.8V we have 0.4V of noise immunity.

Similarly, the lowest value of a 1 is 2.4V, but an input can go down to 2V before the corresponding 0 output rises above 0.4V. Thus at the 1 level we also have 0.4V noise immunity.

The transfer characteristic is shown on Fig. 5.

A noise immunity of 0.4V does not sound a lot, but there are two points to remember. First this is an absolute worst case, with the worst gate at the minimum power supply voltage driving the maximum load. Secondly, the power required to switch the gate is quite large, as the TTL gate is a low-impedance device.

Dealing with Noise

Taking our four sources of noise, how can we deal with them? The first, external noise, is a question of filtering the mains and in extreme cases putting the whole circuit in a Mumetal screen as shown in Fig. 6. Opto-isolators should be used for the inputs and outputs.

The second source, internally generated noise, is interesting. As a TTL gate switches, for a brief time both TR3 and TR4 in Fig. 1 are on together. This causes a large current pulse on the supply. The pulse has very sharp edges, thus generating large transient voltages across the inductance of the supply leads.

Computer manufacturers use multilayer boards, with a

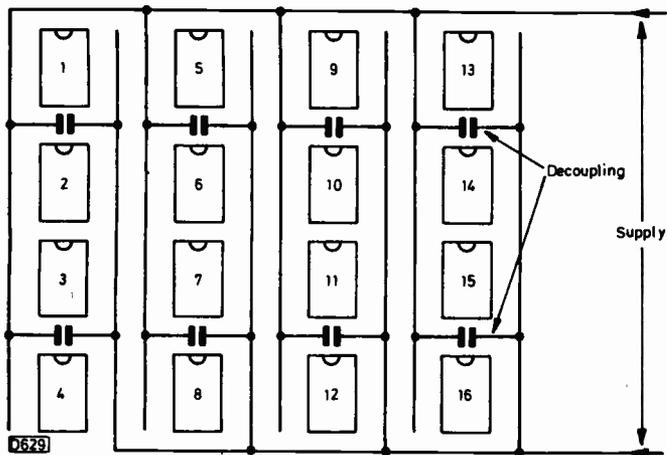


Fig. 7: Supply arrangements with TTL - a typical general-purpose PCB layout.

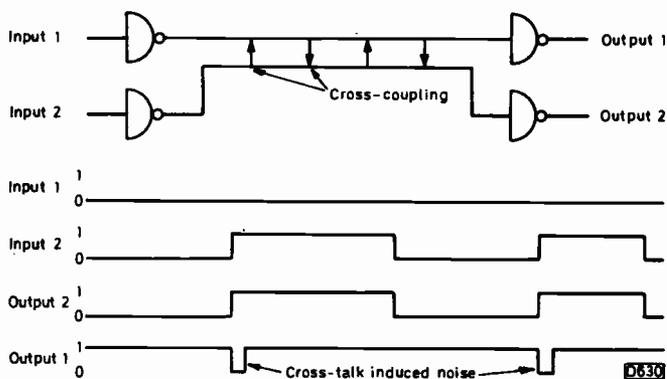


Fig. 8: Crosstalk due to coupling between adjacent tracks.

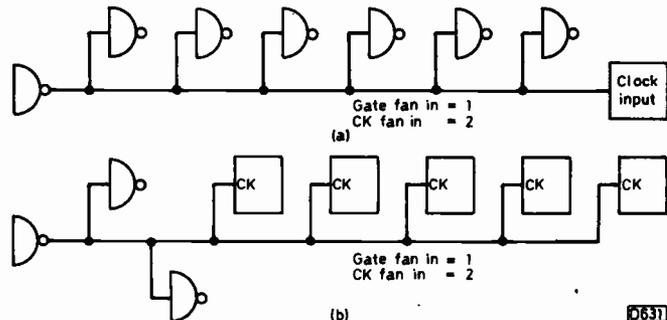


Fig. 9: Fan out and fan in. (a) An allowable configuration - the gate at the left has a fan out of 10, driving a total fan in of 8. (b) Non-allowable configuration. The gate, with its fan out of 10, is linked to 12 fan ins.

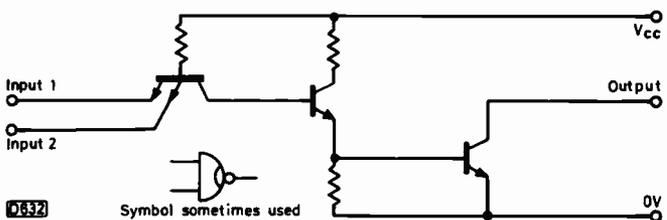


Fig. 10: Open-collector gate circuit.

sheet for the supply and another for 0V. This is not feasible for us poor cost conscious individuals, but we can overcome the problem with a sensible supply layout and liberal use of decoupling capacitors. Fig. 7 shows a commonly used general purpose board.

Manufacturers recommend the use of one $0.01\mu\text{F}$ disc ceramic for every five i.c.s. I'm a pessimist and use one

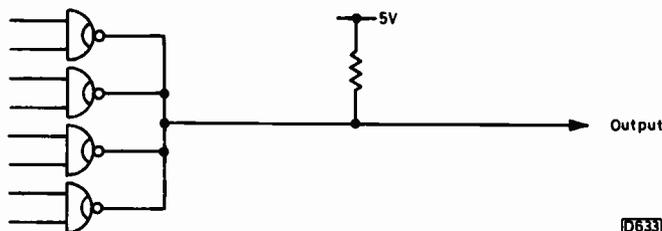


Fig. 11: Use of open-collector gates to provide the "wired-OR" logic function.

$0.01\mu\text{F}$ for every two simple i.c.s and for every i.c. that's vulnerable to noise, such as a memory, counter, etc.

The last two sources (crosstalk and reflection) have similar causes. The waveform edges in TTL are very fast, typically a nS or so. At this speed the edge time is faster than the time taken for the signal to travel along a wire more than a foot (sorry, 30cm) in length.

Crosstalk is coupling between one pair of gates and another (see Fig. 8). Its cure is simply not to run wires close together for runs longer than 30cm or so.

Reflections arise because the interconnecting wires behave like a transmission line - and all TV engineers know that transmission lines need terminating. Normal interconnecting wires have a characteristic impedance of around $300 - 600\Omega$, and need a corresponding terminating resistor. This is beyond the capabilities of normal gates, but special line driver i.c.s are available. The rule is: keep line length below 60cm for normal gates; above this use line drivers and terminate the lines.

Fan in/Fan out

There's a practical limit to the number of gate inputs a gate can drive. A TTL output is defined as having a fan out - usually ten unit loads. An input is defined as having a fan in, usually one unit load although some clock inputs are higher. To see if a gate can drive the inputs you want, total all the fan in loads and check that it comes to less than the output fan out. Fig. 9(a) is thus allowable (fan out 10, fan in 8), but Fig. 9(b) is not (fan out 10, fan in 12).

Unused Inputs

Unused gate inputs present a problem. They can be left floating, but are then prone to noise. The recommended solutions are: to tie them to the supply rail via a $1\text{k}\Omega$ resistor; to tie them to a logical 1 defined by two resistors across the supply rail; or finally to parallel inputs. Spare inputs on OR type gates should of course be tied to 0V or connected in parallel.

Open-collector Gates

Some TTL gates have the totem pole output replaced by a single transistor, as shown in Fig. 10. These gates are called "open-collector gates", and are usually designed so that the collectors can be taken to a high voltage such as 15V or 24V. This makes them suitable for lamp driving etc.

In addition, they can be used to provide a cheap OR function. If several collectors are connected together as shown on Fig. 11, when any output goes to 0 the common line will go to 0. This is known as a "wired-OR". A single resistor is needed to take the line to 1 when all transistors are turned off. Under no circumstances should the outputs of normal totem pole TTL gates be connected together. The wired-OR operation is slower than using a TTL NOR gate.

Servicing Pye Solid-State Colour Receivers

Part 3: 713, 715 and 717 Chassis

Mike Phelan

IN the final instalment in this series we'll deal with the small-screen (18in.) solid-state Pyes, using the 713, 715 and 717 chassis. There is also a Philips version, known as the 570 or A4 chassis. Perhaps the best known model is the Pye CT200, the first all solid-state Pye colour set, which was introduced in late 1972. Other models include the Pye CT200/1 and CT218, the Ekco CT818, the Invicta CT7018 and CT7018/1 and the Philips G18C570. The original version (713 chassis) was fitted with a similar tube to that employed in the Thorn 8000 chassis. It requires a relatively low focus voltage which is derived from the boost rail: a flylead on the tube base provides adjustment, plugging into one of three pins with little variation in the result. The later 715 and 717 (and 570) chassis employ a tube which uses the normal higher focus voltage: this is obtained from the e.h.t. doubler via a focus control on the tube base.

The four main printed panels are held in plastic runners attached to the cabinet base and sides, accessibility being fairly good. The convergence panel is on the right, and can be taken out and placed on top of the set. The top left panel is the decoder, which is virtually identical to the one used in the larger screen models and described last month. Below this is the i.f. panel, which is also much the same as that used in the 725/731 chassis. The large panel at the bottom has on it the power supplies and timebases, some parts of it being a little difficult to get at. When sliding this panel back on its runners, make sure that no leads are trapped behind it – otherwise it will be impossible to replace the back of the set. The latter is held on by the same fixings as were used on the later Pye hybrid sets. They suffer from the same problem, i.e. breaking very easily. Replacements can be glued and screwed to the cabinet with small self-tappers.

Starting again with the power supply, the main differences compared with the larger-screen models are the use of a bridge rectifier prior to the thyristor controlled rectifier, and the use of a BR101 silicon controlled switch instead of a diac to trigger the thyristor. The use of a bridge rectifier means that the chassis is at half-mains potential of course.

The anode of the SCS is fed with a sawtooth waveform

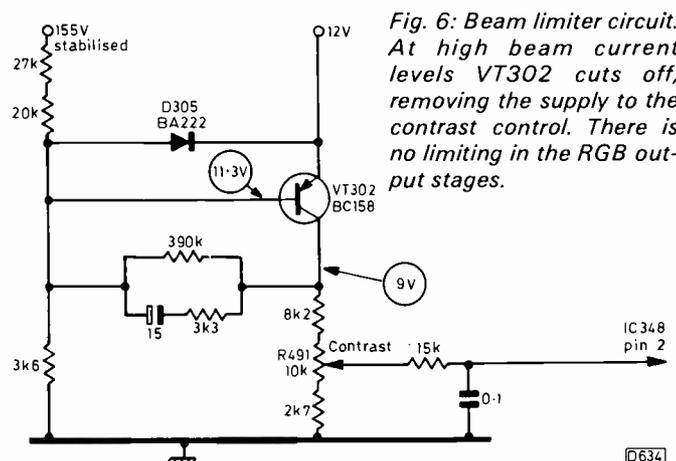


Fig. 6: Beam limiter circuit. At high beam current levels VT302 cuts off, removing the supply to the contrast control. There is no limiting in the RGB output stages.

©634

which is produced by R519/C521. When this reaches the same voltage as the 100Hz half-cycle fed to the anode gate from the junction of R524/R522, the SCS fires, producing a pulse across R533. This is fed to the gate of the thyristor via C532. For over-voltage protection there's a glow switch (537). Should the h.t. rise above a safe value, the gas in the glow switch ionises and the bimetallic contact strips bend, shorting out the h.t. and blowing the mains fuse F526.

When confronted with a blown mains fuse, replace it, switch on and observe the glow switch. If it glows briefly before the fuse blows again, the h.t. is too high. Likely causes are a short-circuit thyristor or the 7.5V zener diode D518 being open-circuit. If the fuse blows instantly without the glow switch operating, check the diodes in the bridge (D503/5/7/9) for leakage. The mains filter capacitor C501 is also not above suspicion.

These sets have a habit of blowing their fuses for no reason at all – both the mains fuse and the h.t. fuse F541 (630mA). A mains fuse that blows at odd times may mean that the h.t. is slightly too high and that the glow switch is striking when the set is warm or when a slight surge occurs on the mains. Note that the mains fuse is the 1.6A one: the 3.15A fuse next to it feeds the degaussing circuit.

Another common fault on this power supply is dry-joints on the filter choke L525. It's worth checking this even if the set is working – if left, dry-joints here rapidly become large holes in the board.

If it seems that the thyristor is not being switched on, but has voltage at its anode, check whether R524 (15k Ω or 10k Ω in earlier production sets) is open-circuit before getting too involved in the power supply circuit. This is the large green or brown resistor on legs near the thyristor, and is often the cause of a dead set.

We've had little trouble with the dropper, but if the 3.5 Ω section R544 goes open-circuit the symptoms are misleading. The cathode of the thyristor is then no longer decoupled by C535, so no gate current flows, giving no h.t. at the cathode and leading one to suspect a fault elsewhere in the power supply.

The line timebase is very reliable – the only components that we've ever had to replace are the e.h.t. doubler, the line output transistor (VT654) and the flyback tuning capacitor C656 (0.0024 μ F or 0.0027 μ F). Note that there are two types of doubler – one with four and one with five leads, depending on the type of tube fitted.

The field timebase is very simple, using an SCS oscillator (D711) and a class B complementary-symmetry output stage. The output transistor pair VT751/VT754 is the cause of most troubles, either both going short-circuit and blowing F678 or one or other of them going intermittently open-circuit. Be sure to replace the insulating washer under VT751 when repairing this part of the set. The driver transistor VT741 (BC337) occasionally plays up, usually giving a very non-linear field scan. The only electrolytic that has occasionally given trouble is C732 (4.7 μ F). Symptoms have been poor linearity and spasmodic height/linearity variations.

There are two extra adjustments in the field timebase,

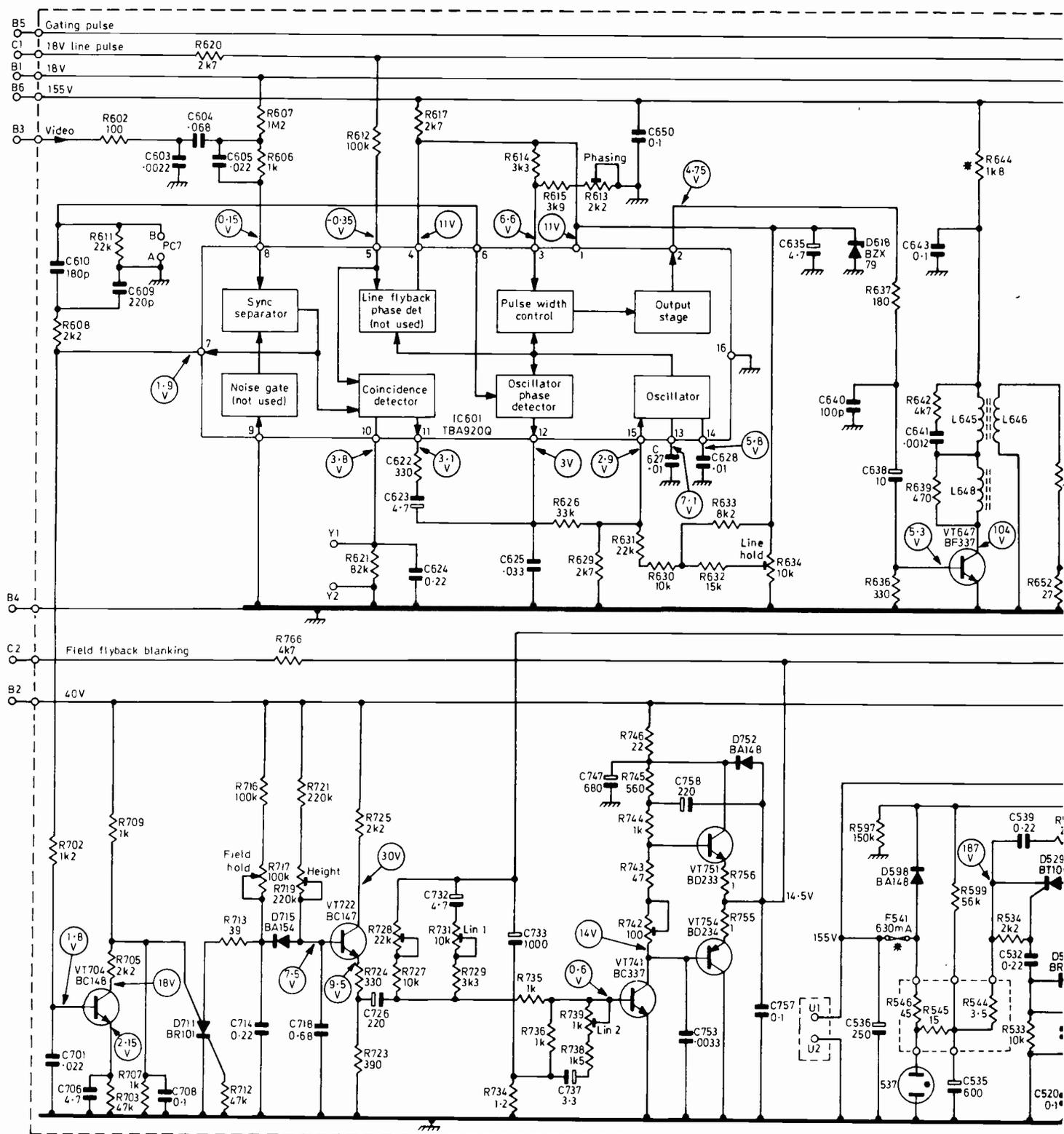


Fig. 7: Power supply and timebase circuits, Pye 715 and 717 chassis.

and these must not be altered indiscriminately. They are the mid-point setting control R728 and the output stage bias control R742. Both settings should be checked after replacing any components in the driver or output stages. Set R728 for 14.5V at the junction of R755 and R756. R742 should be turned fully anti-clockwise, then turned slowly clockwise until the bright line in the centre of the field scan just disappears. The line is caused by crossover distortion, as in an audio amplifier.

Some of the tuning push-buttons fitted to these sets give rise to a fair amount of trouble. They can be repaired in the same way as those of the Pye sets mentioned last month.

The tuner/i.f. panel is almost the same as that used in the bigger brethren, but a 12V filter transistor (VT210) is incorporated. This is also employed as a beam current limiter – in addition to the one (VT302 and associated components) that operates on the contrast control. The rest of the panel is more or less the same as that of the 731 series, and suffers from the same faults – the main one again being dry-joints in the i.f. module.

The decoder is also basically the same as that used in the 731 chassis, but there are one or two differences. There's no switch for turning off the luminance, and the beam current limiter (see Fig. 6) senses the fall in the l.t. supply – this is

Long-Distance Television

Roger Bunney

CONTRARY to expectations, Sporadic E signal propagation during August was extremely active. Unlike June/July, the openings didn't last long but nevertheless gave a selection of signals from most countries in Europe. A well established high pressure system at the end of the month (from about the 26th on) started to provide enhanced tropospheric propagation – the weather consisted of the characteristic clear, cloudless days and nights, with early morning mist/fog. My log for the period, omitting MS (meteor scatter) signals, is as follows:

- 3/8/79 YLE (Finland) ch. E2.
- 5/8/79 MTV (Hungary) R1.
- 6/8/79 Switzerland E2.
- 7/8/79 TSS (USSR) R1, 2; SR (Sweden) E2.
- 9/8/79 RAI (Italy) IA; unidentified R1 signal; Gwelo, Rhodesia E2 (see later).
- 11/8/79 CST (Czechoslovakia) R1; MTV R1; ORF (Austria) E2a; unidentified R1 signals. A long SpE opening.
- 12/8/79 CST R1, 2; many unidentified R1/2 signals. Another prolonged but bitty SpE day. The period 1300-1400 produced an unusual fluttery SpE signal – not unlike MS variations.
- 14/8/79 TSS R1, 2; TVP (Poland) R1 – the signal reached 800 μ V straight from a dipole!; SR E2; DFF (East Germany) E4; RAI IB.
- 19/8/79 MTV R1; several unidentified signals.
- 21/8/79 TSS R1; TVP R1, 2 (strong signals again); DFF E4.
- 27/8/79 TSS R1, 2; SR E2, 4; YLE E2.

One point noted was that DFF have a new identification across their electronic pattern. Reception of Gwelo, Rhodesia was initiated by Hugh Cocks (E. Sussex) who phoned at 1800 to report very strong signals. With careful tuning I could resolve only weak video however. David Martin (Shaftesbury) was active at the time but nothing at all was visible there! It seems that this early evening TE

(transequatorial skip) type signal is only just reaching the south coast. Hugh lives inland from Hastings, on high ground with a clear take-off to the sea some ten miles away. My own location is on low ground, with the Isle of Wight (and its two ranges of high hills) in the way. David Martin is similarly thirty miles from the open sea. Thus when TE is just making it, only south coast DXers will benefit.

Clive Athowe has recently returned from a visit to the United States (see later). He also noted the new DFF identification, and is the first DXer in the UK to receive the new RTL (Luxembourg) ch. E27 transmitter (625 lines with negative video) – congratulations! He comments that the YLE-2 ch. E2 Fubk card has no concentric circle, though the YLE-1 card does include this feature.

Last month I mentioned another Ryn Muntjewerff "first", reception in Holland of RTA (Algeria) ch. E5 via SpE. Fortunately his photograph of the female announcer came out well (see illustration – note the local Dutch ch. E5 floating signal in the background). I also reported last month suspected reception of Gabon ch. E3 – by T. van Dalen in Holland. The photograph of this suspected reception shows a test card similar to the old Czechoslovakian one with the light background (see *Guide to World-wide Television Test Cards*). This reception was at 1000 GMT on June 29th. Any suggestions?


A final comment on August reception. Ray Davies (Norwich) reports receiving a Jordanian ch. E3 signal on the 5th, from 1730-1745, with Arabic news. At fade out (1745) Ray returned to ch. E2 and received ten minutes of programme and credits from Gwelo!

DX Photos

Prints of off-screen photographs returned from the processors seldom seem to do justice to one's DX reception. This is due to the use of mass production printing techniques which employ a system not unlike mean-level a.g.c. – o.k. for Aunt Flo on the beach, but not for a PM5544



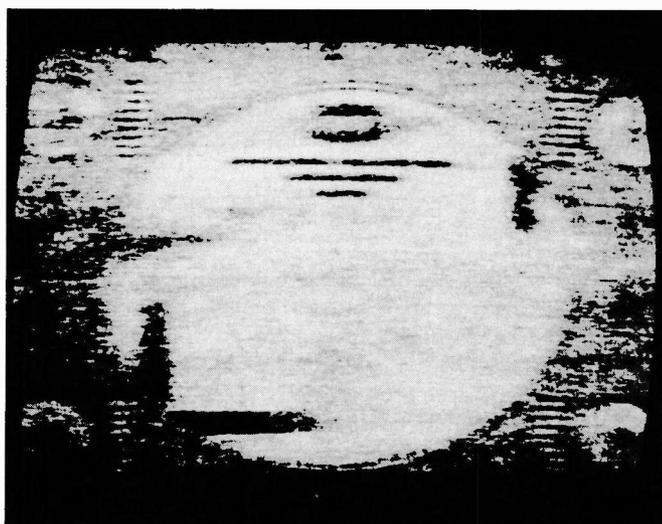Ryn Muntjewerff's reception of Algerian TV ch. E5 via SpE in Holland.



Could this be Gabon ch. E3? Test card received by T. van Dalen in Holland.

pattern with "JTV Amman" identification! Hand printing from the labs can also (from my experience) prove a disappointment due to incorrect framing etc. If you know of a DXer/film expert you're fortunate. Gareth Price has recommended Paul Godfrey of John Wells Photo and Audio Ltd., 44 London Road North, Lowestoft, Suffolk (tel. 3742) who he says can work wonders with doubtful exposures. Being a radio amateur as well, he understands what DX-TV is all about and can, I'm assured, deal with most shots that come along. Developing is 75p, with hand printing for a 5 x 3½ shot at 23p, postage 20p extra - these prices were before the latest increases in postal charges however, so send an s.a.e. for latest details.

Automated DX

In the June issue of the WTFDA magazine *VHF/UHF Digest* Peter Sawatzky of Guelph, Ontario describes an automated set-up for f.m. DXing. Though this column is concerned with TV DXing only, some of the techniques used give food for thought. The system monitors the 100 allocated f.m. channels in the 88-108MHz spectrum over a 24-hour period. Digital information corresponding to the channels in the f.m. band is loaded, via toggle switches, into a memory which, via a digital-to-analogue converter, controls a varicap tuner. The entire f.m. band is scanned once every five seconds. During this process digital signals corresponding to the a.g.c. levels across the band, i.e. whether or not signals are present, are stored in another 100 locations in the memory. The system compares the a.g.c. levels with another set of data signals already programmed into the memory. When the off-air a.g.c. exceeds the programmed level, scanning stops for a predetermined period of time while a tape recorder records what the system has decided is a DX signal! The frequency can also be noted on the tape, though this part of the system has not so far been brought into operation.

The system is reported to work well with SpE signals, but has shortcomings with MS and tropospheric signals. A Mk. II system based on an Intel 8085 microcomputer is being developed to overcome these shortcomings. The tuner is part of a Heathkit AJ15 receiver. As the system operates on a 24-hour basis seven days a week, no opening is missed.

Whilst the system works well for US radio signals, I feel that in Europe the lack of radio and TV signal identifications for much of the time would be a decided drawback. A UK system could perhaps recover VITS information to give a form of identification, but unfortunately many a truly exotic DX signal does not include VITS, while distortion with F2 propagation could be destructive of such information.

Nevertheless, full marks to Peter! Such a system would be ideal for ionospheric research, but strikes me as being not quite in the spirit of true DXing. Any comments?


New Aerial System

I've recently been testing a new stacked bowtie wideband u.h.f. aerial system. The gain, particularly in groups B and C/D, is most encouraging compared to other versions I've used in the past. Comparative tests of the new Vorta system and a similar stacked bowtie array at both Romsey and Shaftesbury have shown that whilst the group A gain is similar there's a 2dB lift at the h.f. end of group B and a peak improvement of 3dB in group C/D. I also noted a 2dB improvement in the front-back ratio, though the forward lobe is similar and quite broad. Individual measurements were made at two different locations in order to confirm the

**CONTINENTAL AERIAL SPECIALISTS, RETAIL AND TRADE.
GOLDEN ANODISED, WEATHER PROTECTED, SUPERB ARRAYS.
GUARANTEED FOR FIVE YEARS.
GOLDEN QUALITY IN A PLASTIC AGE.
ALL PARTS (EXCEPT COAX) EXCHANGEABLE FOR 7 DAYS.
10% DISCOUNT OFF MOST AERIALS
SPECIAL PROMOTION OFFER
15% + DISCOUNT ON PLEMI RANGE**

For new glossy, highly graphic lists & brochures send 40p & stamp only. 40p credit on 1st order.

AGENTS FOR
FUBA & PLEMI

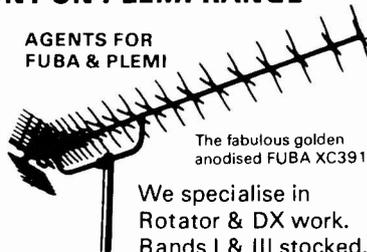

The fabulous golden anodised FUBA XC391

Stockists of the finest aerials available in Britain:
STOLLE FM aerials (W.Ger.)
FUBA TV & FM aerials (W.Ger.)
PLEMI TV aerials (Hol.)
UKW FM aerials (E.Ger.)
ANTIFERRENCE TV & FM aerials (U.K.)

We specialise in
Rotator & DX work.
Bands I & III stocked.

ASTRA (GOLDEN D.I.Y.) AERIALS

A friendly family firm. Our 25th. Jubilee Year.

D.I.Y. AERIAL SPECIALISTS FOR ALL DOMESTIC TV & FM RECEPTION

Weather exposed part of U.K.? Scotland, Wales, West Country etc. Gales, salt air corrosion problems? Want to install your aerial and forget it?

The continental aerial range from Germany and Holland having proved so fantastically successful, we are in future recommending continental aerials (especially Fuba) as our first choice for customers. In short we offer quality in a plastic age.

Anodised against corrosion, guaranteed for five years. robust, high gain, easy to assemble, eye-catching superb aerials, what else, in truth could we recommend?

Over 3,000 aerials stocked: All Bands: Masts: Lashings: Wall Brackets: Rotators: Televertas: Diplexters and Triplexers: You can now mix Band 4 and Band 5, or lower Band 5 with higher Band 5, or mix FM with either.

1.5db loss approx.: Padded outlets: Directional splitters: Coax, white or brown: 300 ohm cable.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Gloster Pub & Garage Tel: 01-684 4300

Open 9.00-5.30 MON-SAT. 01-684 5262

Closed 12.30-1.30 But Open ALL day Sat. 24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY

LOOK! Phone: LUTON
BEDS. 38716

OPPORTUNITIES TRADE SALES

**ALL SETS GUARANTEED
COMPLETE**

OVER SIX HUNDRED SETS

ALWAYS IN STOCK

Pye 20T, Philips G8;

Ferguson 3-3k5

Murphy, Bush, Decca, GEC

All from

£35.00 £50.00

Square Screen, Mono's from

£5.00 ALL MODELS

Sets for spares from

£2.00

All include VAT

OPPORTUNITIES
9A, Chapel Street, Luton, Beds.
LUTON 38716

9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.

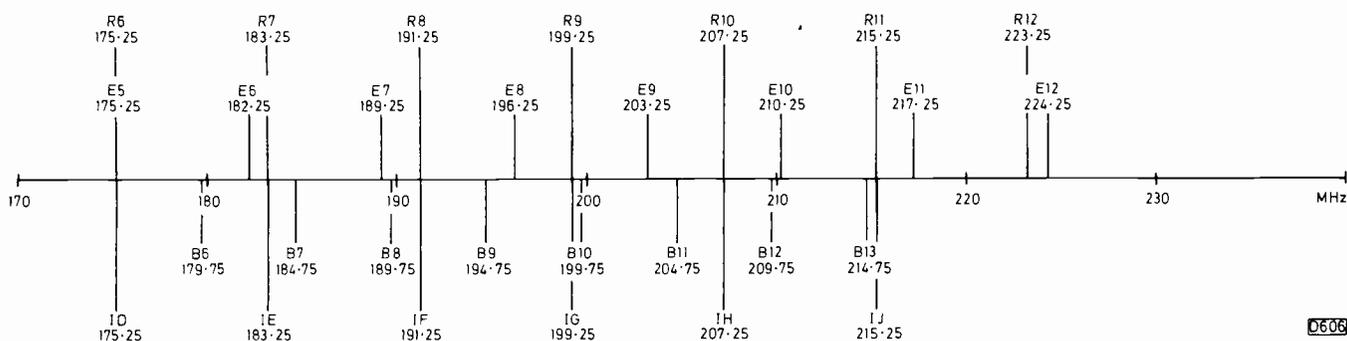


Fig. 1: European Band III vision carrier frequencies. The R channels are used in East Europe, with 6.5MHz sound/vision spacing (system D); the E channels in West Europe with 5.5MHz sound/vision spacing (system B); the I channels in Eire with 6MHz sound/vision spacing (system I); and the B channels in the UK with 3.5MHz sound/vision spacing (system A). System A has 405 lines and positive vision modulation, all the other systems 625 lines with negative vision modulation.

results and check with different signals.

The reason for the improved performance is uncertain, since the new Vorta array is if anything slightly smaller than the other similar one. Matching into 75Ω from the Vorta's balanced system is done by a small ferrite-loaded transformer – the other system uses tuned lines etched on a PCB. Personally I suspect that the improvement is entirely due to the method of matching. The Vorta aerial is known as the Duplex DX4/4 and is "competitively" priced – though at the time of writing I don't have an exact price.

From our Correspondents . . .

Brian Fitch sends us the following Swiss Solar Observatory sunspot predictions: July 153, August 155, September 154, October 152, November 150, December 148. So it would seem that August was the peak in the current cycle.

Robert Copeman (Sydney, Australia) reports more potential DX fields to explore. During 1980 additional u.h.f. stations will be opened at King's Cross (ATN ch. 46, TCN 49, TEN 52) and North Head (ATN 47, TCN 50, TEN 53), with a new Ethnic Television station on ch. 29.

While Clive Athowe was staying in New Jersey, twenty miles from New York, he didn't see a single test card! – all the stations were on air before he rose. Many of the available channels are occupied, and in the f.m. band there's a station every 100kHz. Many householders use rotor systems.

P. Layton (Deal, Kent) reports remarkable success at u.h.f. using a Stolle multiple-director wideband aerial and amplifier (plus rotor). Many Dutch and Belgian u.h.f. signals are "regular".

Jim Cook (Newcastle) has received many Russian signals since erecting an Antiference combined Band I/III MH308 array. A good catch was the Italian free station NCT on ch. E3, with a tuning caption displaying a reclining lady of the *Sun* page 3 variety!

Feedback from John Lannigan (Gainsborough) on the subject of planning permission. When he applied for permission to erect aerials on an 18ft. alloy mast at the rear of his house he was asked to provide exact specifications of each aerial and the method of fixing etc. When permission was granted it was with the proviso that the specification given be followed exactly and preferably erected by a professional engineer. This seems to contradict my suggestion that it's best to be vague about the aerials, merely stating something like "domestic u.h.f. aerial". The aerials are as follows incidentally: from the top down, a five-element 144MHz array, an 18-element array for amateur TV at 430MHz – both using a rotor – a group B Antiference XG aerial, an 18-element group C/D aerial facing north east, a three-

element f.m. aerial, a 10-element group A aerial for Belmont, and a group B array from Emley Moor.

DX-TV for the Beginner – 3

Band III covers 164-230MHz. In the UK it's used for the IBA's 405-line transmitters – rumour has it that some of these now operate at reduced power in the interests of conserving the remaining stock of spare valves, which are now impossible to obtain. Long-distance television reception in Band III is mainly due to tropospheric signal propagation, i.e. is dependent on weather conditions – see remarks in the September column. From time to time there are reports of SpE reception in Band III, but this is relatively unusual. Somewhat more frequent are reports of meteor shower reception in Band III – we'll go into this type of signal propagation in a later article.

There's considerable scope for good tropospheric reception in Band III: UK enthusiasts have logged many stations in Sweden, the Iron Curtain countries, Austria and down into Spain. During a good tropospheric opening there will normally be both Band III and u.h.f. signals. Sometimes results in Band III will be better, while at other times the u.h.f. signals will be stronger. Those living in the north east of the UK have limited scope unfortunately due to the intervening terrain – generally, distant UK and Irish stations will be the only ones to put in an appearance.

A prime requirement for a Band III aerial is a good gain/bandwidth product. Though there's not much call for v.h.f. aerials in the UK today, some companies still produce a selection for either single channel or broadband operation. Antiference and Jaybeam make several wideband Band III systems for fringe reception, with a forward gain of 11dB for an eleven-element version. Antiference have several arrays with multiple-element reflector assemblies, giving improved front-back ratio. Premier Industries (Cheltenham) also make several narrow and wideband Band III aerials. A narrow-band aerial should be used where optimum performance at a given frequency is required, e.g. if you wish to receive a particular distant channel regularly, or for MS work on a particular channel. For DX purposes in general however an efficient wideband aerial is the most cost effective solution. Whereas in Band I there are SpE, F2 or MS signals most days, in Band III and at u.h.f. there are long periods when things are dead. It's possible that in a bad year only a couple of good openings may occur, so a general-purpose wideband aerial is the wisest choice. The same thinking applies at u.h.f., especially as installation costs rise with increasing frequency.

When designing an aerial system from scratch on a limited budget, I'd suggest starting off with a Band I aerial,

then adding a wideband u.h.f. array with preamplifier, and finally a Band III aerial. From personal experience at my particular location I'd say that the use of good, low-loss coaxial feeder makes the use of a Band III masthead amplifier unnecessary – in a built up area, the amplifier will tend to aggravate interference problems. If on the other hand the location is free of interference from ignition systems, thermostats etc. then by all means use an amplifier.

As with u.h.f. aerials, a Band III aerial must be mounted as high as possible and clear of obstructions. When stacking the aerials on the mast therefore the u.h.f. one will be at the summit, with the Band III aerial beneath it, at least 3ft. away, and lower down the Band I aerial, again with the same spacing. Point all aerials in the same direction, since if propagation from say the east is good at u.h.f. it follows that Band III propagation from the same direction will probably be enhanced.


To start with, concentrate Band III effort on tropospheric reception – attempts at MS reception using the wideband i.f. strip employed in an unmodified receiver will be discouraging because of the weak signals involved and the high noise/low gain of the strip. With experience, you will find it possible to reduce the bandwidth of the i.f. strip, achieving higher gain with improved selectivity. This allows very weak signals that would be masked by noise in an unmodified

receiver to be displayed.

Fig. 1 shows the Band III channels in use in western and eastern Europe, including Eire and UK carrier frequencies which can be used for marker purposes. French allocations have been excluded since the receiver used is unlikely to be able to resolve positive-going video signals, let alone 819 lines.


Having briefly covered Band III reception and aerials, there remains the problem of supporting the aerials. Unlike Band I where one can if necessary mount the aerial in the roof space, u.h.f. and Band III aerials should be erected as high as possible in the open. A 30ft. mast with a means of rotation can be erected for only a few pounds (with rotation by hand). The subject was covered in some detail by Garry Smith and Keith Hamer in the March 1978 issue of *Television*. The average house is some 30ft. high, so that a wall bracket/mast combination at the apex of an end wall, or fixed by means of a substantial chimney lashing, will give a height of about 35ft., which is adequate for TV-DX operations.

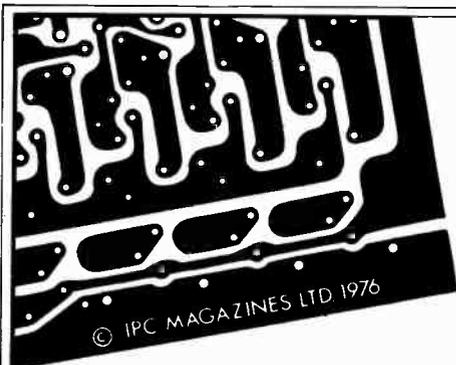Finally, having changed my aerials twice a year on average over the past 16 years and encountered most of the problems associated with DXing, I'd be happy to advise newcomers on proposed structures and/or equipment – but please enclose an s.a.e.



All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

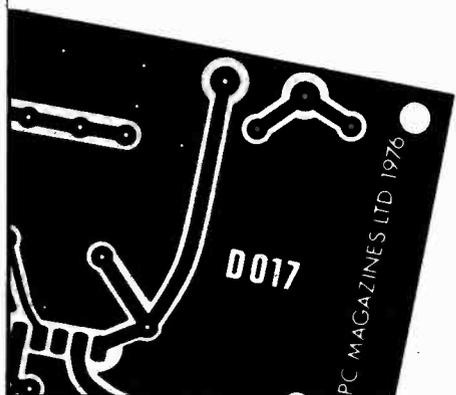Any correspondence concerning this service must be addressed to **READERS' PCB SERVICES LTD**, and not to the Editorial offices.



TELEVISION READERS PCB SERVICE

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£3.24 per set
December 1976	IC Sound Circuits for the Constructor	D009	£1.44
		D017	£1.44
March 1977	Teletext Decoder Power Supply	D022	£3.24
May 1977	Teletext Decoder Input Logic	D011	£10.53
May 1977	Single-chip SPG	D030	£3.30
June 1977	Wideband Signal Injector	D031	£0.79
June 1977	Teletext Decoder Memory	D012	£8.51
July/Aug 1977	Teletext Decoder Display	D013	£8.62
August 1977	Logic State Checker	D038	£1.70
September 1977	Teletext Decoder Switch Board	D021	£1.43
September 1977	Teletext Decoder Mother Board	D027	£4.36
October 1977	Teletext Decoder IF Board	D041	£6.50
Feb/March 1978	On-Screen Clock	D045	£7.03
April/May 1978	CRT Rejuvenator	D046	£2.76
May/June 1978	Test-Pattern Generator	D048	£9.15
Aug/Sept 1978	Diagnostic Pattern Generator	D051	£8.62
October 1978	Colour Receiver PSU Board	D052	£3.83
January 1979	Colour Receiver Signals Board	D053	£10.75
February 1979	Commander-8 Remote Control System	D054/5	£5.43 per set
March 1979	Colour Receiver Timebase Board	D049	£17.13
July 1979	Colour Pattern Generator	D062	£13.50
		D063	£9.15
September 1979	Teletext Decoder Options Board	D064	£8.50
August 1979	Teletext Decoder New Mother Board	D065	£5.00
August 1979	Simple Sync Pulse Generator	D067	£4.00
September 1979	New Teletext Signal Panel	11331	£8.00
October 1979	Teletext Keyboard	D057	£3.50
October 1979	Teletext Interface Board	D058	£5.00
November 1979	Colour Receiver Remote Control	D066	£5.00

To:- Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME _____

ADDRESS _____

Post Code _____

Colour Receiver Options 2: Adding Remote Control

Luke Theodossiou

IF you add this month's remote control only option to your basic receiver, you'll have sixteen functions which you can control from your armchair. These functions are as follows: choice of any one of eight preselected stations; volume adjustment up or down; brightness adjustment up or down; adjustment of colour saturation levels up or down plus a "normalise" command; and full set switch-off. We've decided to use a commercial remote control transmitter (ITT) rather than a DIY unit, since the commercial variety looks a little more attractive. The circuit diagram is shown in Fig. 1.

Briefly, the transmitter operates as follows. When a button is pressed, two address pins on the SAA1024 are grounded. Which two pins out of eleven depends on the command required. Thirty "channels" are available with this system, though in our application only sixteen are used. These input signals from the keypad are then converted into five-bit words in the i.c., and are applied to a variable-frequency divider which generates the correct frequency from the 4.43MHz crystal-controlled oscillator for driving the ultrasonic transducer.

The receiver circuit is shown in Fig. 2. The signal is picked up by the ultrasonic transducer, which is connected across terminals 1 and 2 of connector A. It's then amplified by Tr1, Tr2 and Tr3, and fed to pin 15 of the SAA1130. Frequency selective feedback is applied from the emitter of Tr3 to the base of Tr2 to reduce the gain of the amplifier at frequencies outside the wanted range.

The SAA1130 measures the frequency of the incoming signal by counting the number of cycles during a fixed interval determined by the 4.43MHz crystal. All commands are converted into a coded five-bit output signal. A block diagram of the SAA1130 is shown in Fig. 3. It contains a 4.43MHz oscillator which provides all the necessary timing

signals. Decoding is achieved by counting the number of cycles present in the ultrasonic signal.

The channel information is stored in the "programme store" and comes out at pins 13, 14, 6 and 7. The code is shown in Table 1.

When "high" the voltage is around +18V and is potted down to +5V by resistors before being supplied to IC2, a 1-of-10 decoder. In our application only the first eight channels are used. Each of the outputs drives a transistor switch (Tr6-Tr13) which has a helical multiturn potentiometer as its collector load. The wipers of these pots are connected to a buffer via hold-off diodes.

The analogue control signals (brightness, colour and volume) come out of the SAA1130 at pins 2, 3 and 4 in the form of 17.5kHz squarewaves, whose duty factor is variable in 62 steps between 1:62 and 62:1. The signal is integrated by capacitors on the signals board of the receiver: this results in a d.c. voltage whose amplitude is proportional to the required control level. On switch on or when the "ideal" button is pressed, the duty factor is 32:31. The potentiometers VR1, VR2 and VR3 are set to correspond to a "normal" picture and volume setting. The i.c. takes 8.5 seconds to sweep the entire range of control.

The mains-off circuit drives a triac (SCR1) which activates the solenoid of the on-off switch. Unlike a "standby" condition, this method actually isolates the set from the mains. We consider it an important safety feature.

On switch on, the SAA1130 goes into "standby" mode. Tr5 with its associated components hold pin 5 positive for a sufficient period to enable normal operation.

Construction

The complete circuit is built on a single p.c.b., reference number D066. The copper print pattern is shown in Fig. 4, while Fig. 5 shows the component locations. The only component which is not on the board is the ultrasonic receiver capsule, which has to be mounted on the front of the cabinet and connected to the interface board (at A1 and A2) by a length of screened cable. The remaining connections are listed in Table 2.

Table 1: Programme code

Programme number	Code			
	PA	PB	PC	PD
1	L	L	L	L
2	H	L	L	L
3	L	H	L	L
4	H	H	L	L
5	L	L	H	L
6	H	L	H	L
7	L	H	H	L
8	H	H	H	L
9	L	L	L	H
10	H	L	L	H
11	L	H	L	H
12	H	H	L	H
13	L	L	H	H
14	H	L	H	H
15	L	H	H	H
16	H	H	H	H

L = low, H = high.

Table 2.

B1	→	A5	on signals board
B2	→	A6	on signals board
B3	→	A9	on signals board
B4	→	A12	on signals board
B5	→	A18	on signals board
C1	→	F2	on PSU board
C2	→	F1	on PSU board
C3	→	F4	on PSU board

In addition, the mains switch solenoid cell is connected to E1 and E2 on the power supply board.

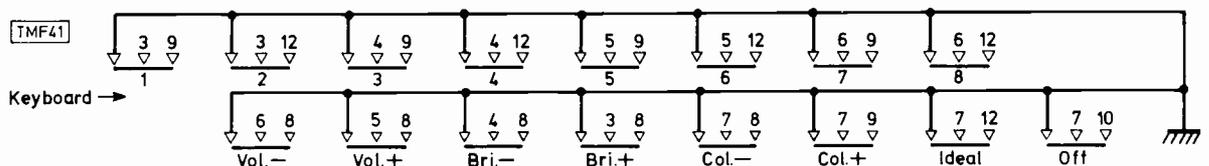
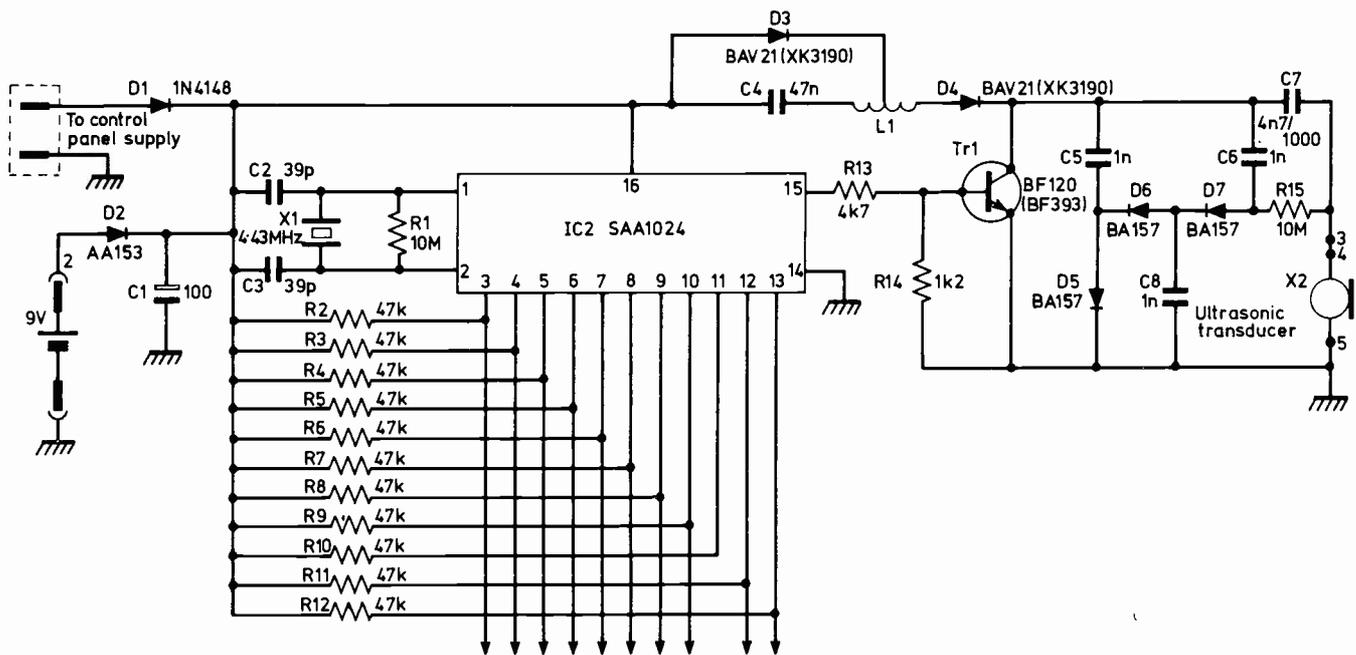


Fig. 1: Complete circuit diagram of ITT remote control transmitter. Note that the plug labelled "to control panel supply" is not used in our application.

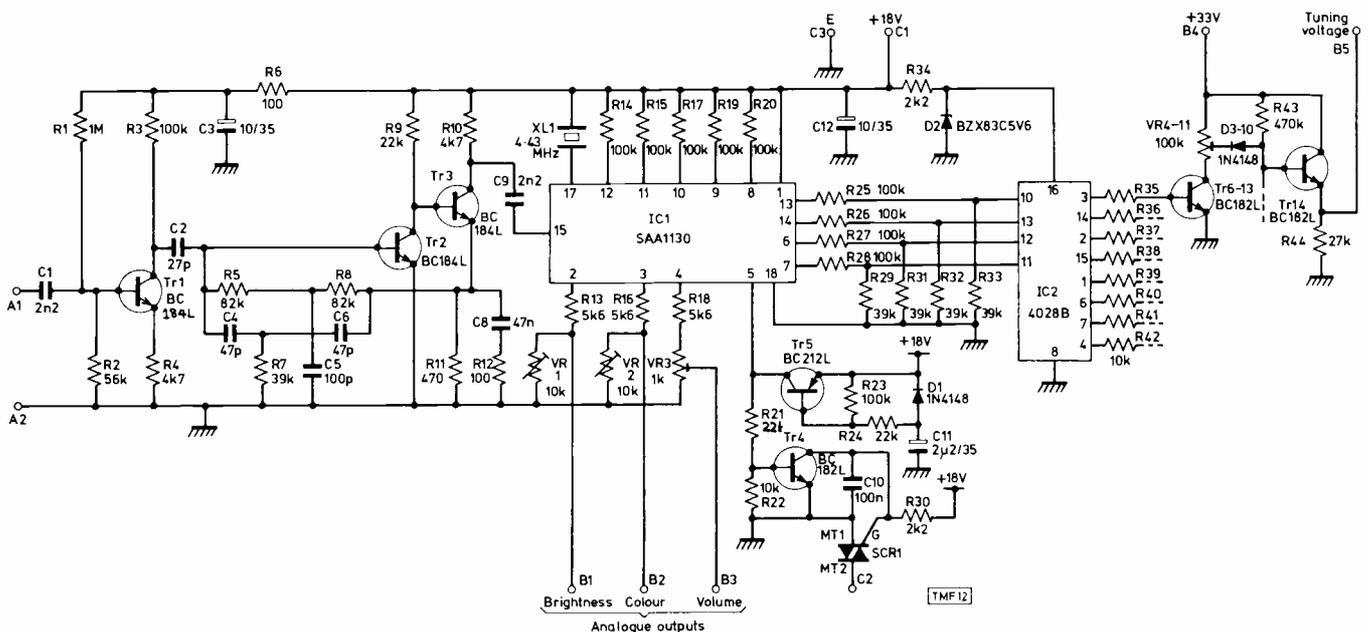


Fig. 2: Circuit diagram of interface board.

Setting Up and Faultfinding

Setting up merely involves switching the receiver on (it will automatically select channel no. 1) and tuning in VR4 to the local station. Then select channel 2 on the remote control transmitter, adjust VR5, and so on.

Next adjust VR1, VR2 and VR3 (without having touched any of these analogue controls on the transmitter) for what you feel is an "ideal" picture and a comfortable

listening level. This is the picture and sound you will now obtain on switch on or when pressing the "ideal" button on the transmitter. Note that you will have to press the "off" button on the transmitter for a few seconds before it's activated, due to a built-in delay circuit which prevents inadvertent operation.

Faultfinding is straightforward. If the unit fails to respond to any commands from the transmitter, first of all

★ Components list

Capacitors:

C1	2n2 ceramic plate
C2	27p ceramic plate
C3	10/35V tantalum bead
C4	47p ceramic plate
C5	100p ceramic plate
C6	47p ceramic plate
C7	not used
C8	47n polyester
C9	2n2 ceramic plate
C10	100n polyester
C11	2 μ 2/35V tantalum bead
C12	10/35V tantalum bead

Semiconductors:

D1	1N4148
D2	BZX83 C5V6
D3-D10	1N4148
Tr1-Tr3	BC184L
Tr4	BC182L
Tr5	BC212L
Tr6-Tr14	BC182L
IC1	SAA1130
IC2	4028B
SCR1	TR1400-0.35 triac (RS Components stock no. 262-028)

Resistors:

R1	1M
R2	56k
R3	100k
R4	4k7
R5	82k
R6	100
R7	39k
R8	82k
R9	22k
R10	4k7
R11	470
R12	100
R13	5k6
R14	100k
R15	100k
R16	5k6
R17	100k
R18	5k6
R19	100k
R20	100k
R21	22k

R22	10k
R23	100k
R24	22k
R25	100k
R26	100k
R27	100k
R28	100k
R29	39k
R30	2k2
R31	39k
R32	39k
R33	39k
R34	2k2
R35	10k
R36	10k
R37	10k
R38	10k
R39	10k
R40	10k
R41	10k
R42	10k
R43	470k
R44	27k

VR1	10k
VR2	10k
VR3	1k
VR4-VR11	100k

} subminiature horizontal presets

} 20 turn helical tuning potentiometers

Miscellaneous:

Ultrasonic receiving transducer

RS Components stock no. 307-367

P.c.b.

Readers PCB Services reference no. D066

Remote control transmitter

ITT Consumer Products type CMC33 (stock no. 16-4-99)

XL1

4.43MHz crystal

Molex 0.2in. connectors

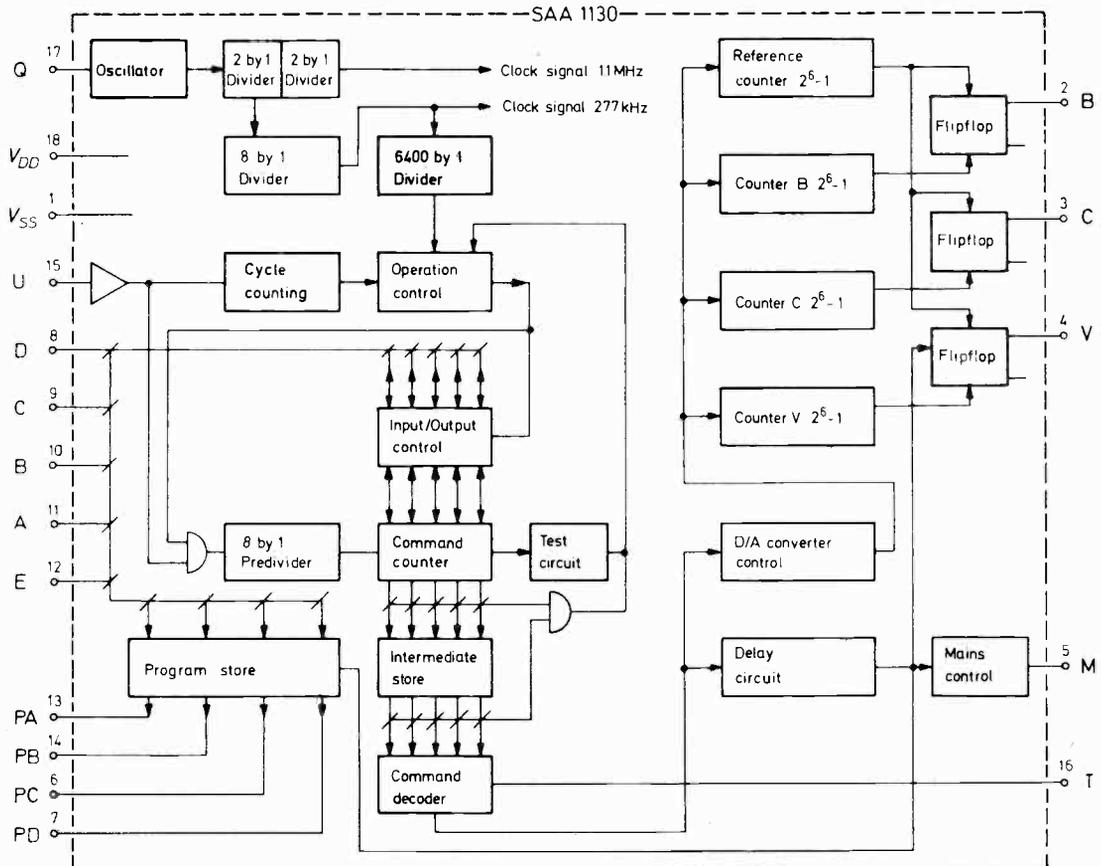


Fig. 3: Block diagram of the SAA1130.

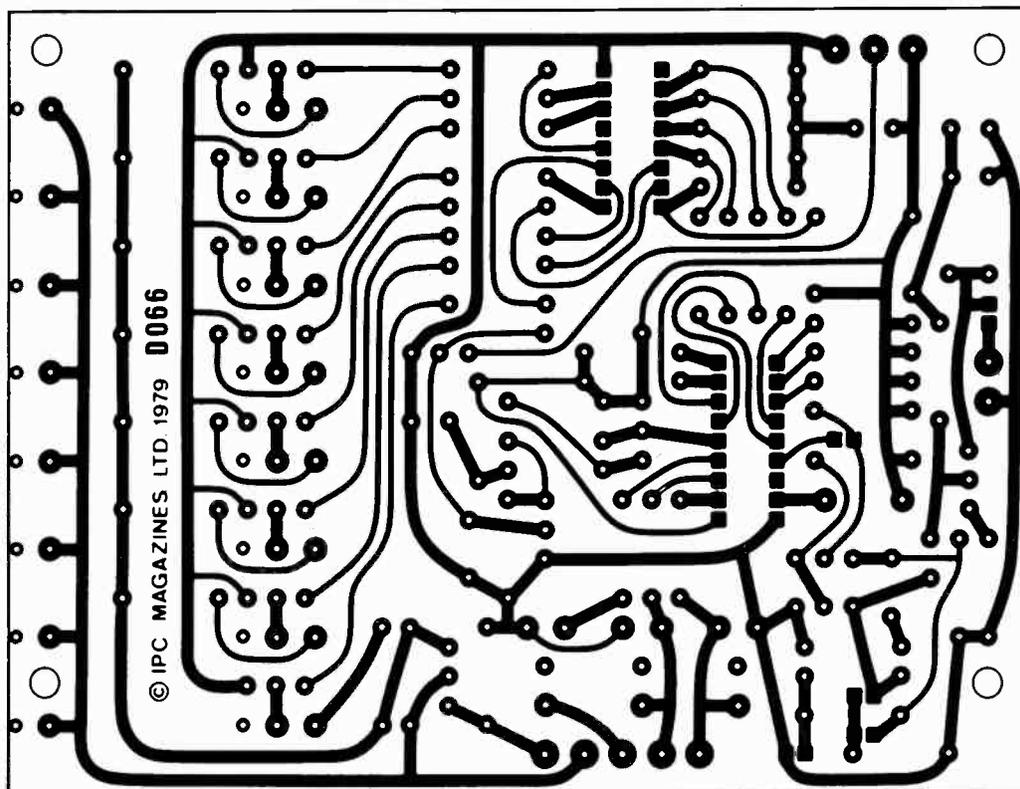


Fig. 4: Copper print pattern for interface board ref. D066.

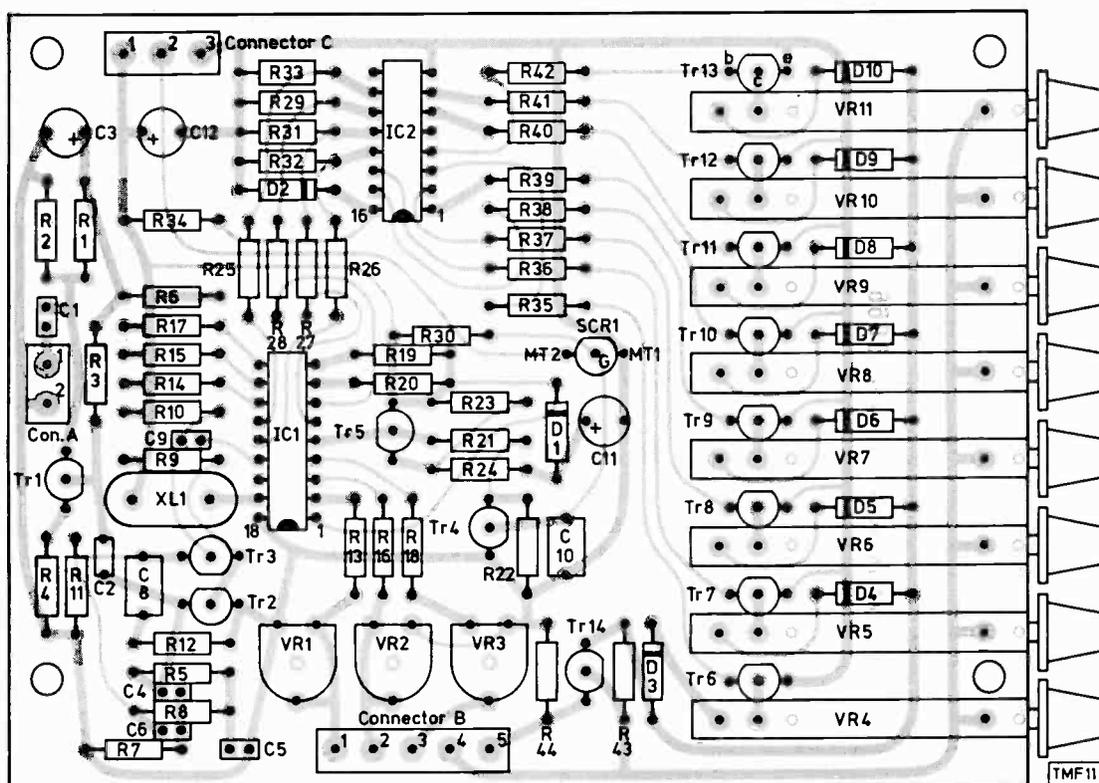


Fig. 5: Component location diagram.

check the battery in the transmitter. If this is in order, check with a scope (while pressing say a channel button on the transmitter) that a signal is present at the collector of Tr3. If all is well, suspect the SAA1130. If the unit fails to change channels but otherwise operates correctly, switch off – then

switch on again to reset channel 1, and check the voltages on pins 13, 14, 6 and 7 of IC1 (see Table 1). If they are correct and respond when changing to another channel, then it's probably IC2 which is at fault, though Tr14 or the connections to the signal board may also be responsible.

TV Servicing: Beginners Start Here . . .

Part 26

S. Simon

IN the last two instalments we've described colour tube drive circuits and the faults they give rise to. These are basically excess or lack of one or more colour(s), brightness faults or maybe shading across the screen. There are other types of colour fault however. No or intermittent colour, un-locked colour (colour bars across the screen), green faces or Hanover bars for example. These are due to faults in the decoder (though missing pulses from the line timebase can be responsible for some of these faults) and will have to wait till we get around to that part of the colour receiver. Another group of faults consists of patchy colour or mis-registered colour, i.e. the blue, green and red components of the picture are not correctly superimposed, giving rise to medal ribbon effects when really bad. These are due to purity and convergence problems, and are next on the agenda. We'll take convergence first.

In the not too distant future convergence will not be a problem to worry about. This is because the present generation of colour tubes, with their in-line guns and striped phosphor screens, are self-converging.

Mounting the guns horizontally in line reduces the need for convergence, while designing the scan coils to predistort the three beams removes the need for anything other than maybe a couple of factory preset adjustments. For the moment however most of the colour sets you'll have to deal with will be fitted with the older generation of colour tubes. These have the three guns mounted in the neck of the tube in a triangular configuration (or delta arrangement as it's called) – see Fig. 1. As a result, the three rasters produced will, without correction, tend to be as shown in Fig. 2. The required correction is provided by the convergence system, and by considering Fig. 2 you'll see why incorrect convergence will result in misregistration of the three primary colours on the screen.

How is convergence achieved then? A little thought suggests that placing a magnet over each gun will result in the beams being deflected inwards. If the three magnets are carefully adjusted, the three beams can be brought into registration, i.e. converged, at a point in the centre of the screen. This takes care of the centre area, but still leaves severe problems when the beams are deflected towards the edges and corners of the screen.

Centre convergence is called *static* (i.e. beams un-deflected) *convergence*. Permanent magnets can be and generally are used for this purpose. Alternatively we can employ a coil wound on a soft iron core, passing through the coil a current (d.c.) preset by a variable resistor, i.e. using an electromagnet instead of a permanent magnet to produce the same effect. Coils and presets were favoured by some continental set designers.

Let's stick with permanent magnets however and bring up the next point. If the blue gun is mounted at the apex of the triangle, two magnets will be required to converge the blue beam with the other two beams – see Fig. 3 – one to move it vertically so that it's brought to the same vertical position as the other two beams, and the other to move it

laterally so that its horizontal position coincides with the other two beams. The red and green beams are simply moved radially until they coincide. In practice the two magnets make it easy to adjust the static blue convergence, but red and green are not so easy to converge. They have to be done first therefore (switch off the blue gun).

Once the red and green images have been accurately overlaid at the centre of the screen by means of the red and blue static convergence magnets, it's a simple matter to converge the blue beam so that blue falls on top of red and green (yellow) to give white. While the blue vertical static magnet shares the same convergence housing with the others, the blue lateral magnet is mounted on a clamp on the neck of the tube towards the rear (see Fig. 4). It must obviously be aligned with the blue gun. This is at the top in most sets, at the bottom in some (e.g. the Thorn 3000/3500 chassis), depending on which way up the tube is put in – we'll assume that it's at the top, which means that the e.h.t. cavity connector is at the top of the cabinet and not at the bottom. If the blue lateral magnet is rotated or allowed to rotate on the tube neck it will influence the red and green beams as well – you'll have enough trouble without letting this happen!

Having achieved good centre convergence, a lot more correction is required to produce good convergence in the outer areas of the screen. We can't use permanent magnets for this purpose, because the amount of convergence correction required varies as the beams travel across the screen and up and down. We have to employ coils fed with varying current waveforms so that the correction can be varied as required while the scans progress. We can combine sawtooth and sinewave current waveforms to achieve the desired results, varying their amplitudes and proportions by means of a group of preset controls – the *dynamic convergence* controls. By carefully adjusting the controls to tailor the waveforms, we can converge the three (red, green and blue) rasters into one with no distracting fringing to the images (except maybe in the corners). The waveforms required will be at line and field frequency, and can thus be obtained from the two timebases, with the shaping effected by the coils, presets, capacitors and a few other bits and pieces which you will mostly find mounted on the convergence panel.

Purity

We've talked about converging the three beams at the screen. This is not quite accurate. Colour tubes employ a metal screen (the shadowmask) which is mounted just behind the screen and serves to ensure that when everything is set up correctly the beams fall on the colour dots (stripes in more recent tubes) of the correct colour phosphor. The point at which the beams converge is the shadowmask, not the screen itself. This introduces a further complication.

Suppose the beams are accurately converged but, after passing through the mask, they fall partially on dots/stripes of the wrong colour? We'll get incorrect colours

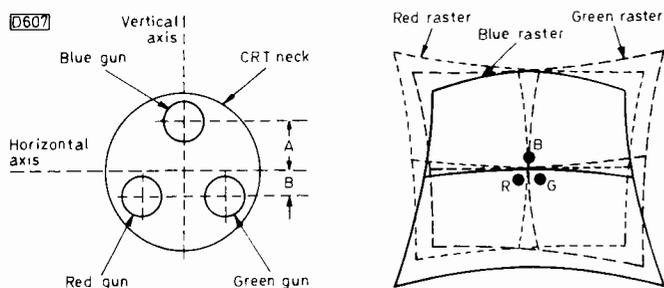


Fig. 1 (left): Arrangement of the electron guns in the neck of a delta-gun tube. Note that distance A along the vertical axis is roughly twice distance B, so that a greater current is required in the blue dynamic convergence coils than in the red and green coils.

Fig. 2 (right): Without convergence correction, the three rasters produced by the three guns in a delta-gun tube take on the approximate shapes shown here.

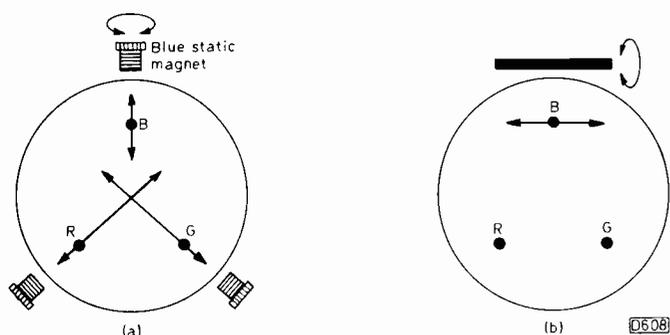


Fig. 3: Radial movements (a) of the three beams, under the influence of adjustable permanent magnets, to converge the beams at the centre of the screen (static convergence). (b) The blue beam requires horizontal as well as radial movement in order to align it with the red and green beams.

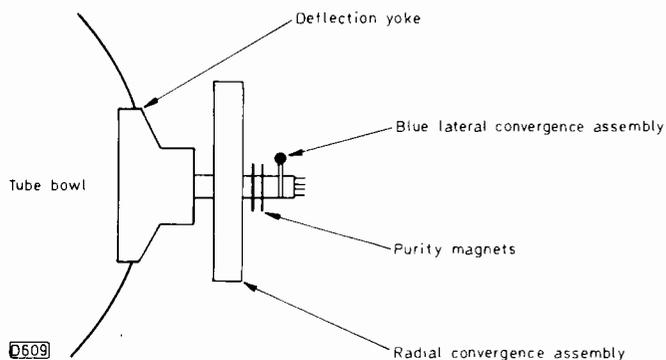


Fig. 4: Positions of the various correction assemblies on the neck of a delta-gun shadowmask tube.

of course – in practice a patchy colour effect. We can't move the shadowmask of course, so to get correct beam "pass through", i.e. colour purity, correction is carried out at the gun assembly end of the tube. This means yet more magnets (two) mounted on the neck of the tube. They take the form of rings which can be rotated relatively to each other – much the same as with the picture shift rings used in a monochrome set. The action of the magnets is to rotate the beams slightly to ensure that the beams pass through the shadowmask apertures accurately and then strike the appropriate phosphors.

It may be thought that all these magnets will react with each other to some extent. Indeed they do. And we are not finished yet. The position of the scan coils on the tube neck has a profound effect on beam landing, which is why they have to be moved along the tube neck in addition to the

more obvious rotational adjustment to correct for any tilt. All this interaction may appear to be somewhat frightening, and up to a point it is. If the convergence and tube neck components have been seriously tampered with (and we all encounter this from time to time) a lot of patience and a degree of expertise is called for to regain an acceptable display. What to do?

The first move should be to get the purity right. This can be done in several ways and we all have our pet method. One can have all three guns in operation, and examine the plain white raster for signs of colour patches that shouldn't be there. Or one can switch off two of the guns and examine the colour of the remaining raster (say red). If there are patches of incorrect colour (anything other than red), loosen the plastic wing nuts at either side of the deflection coils and pull them back. Then rotate the purity rings in relation to each other until the centre of the screen is pure red. Next move the scan coils forward to spread the correct red out to the edges. After this, check the separate green and blue rasters and ensure that the purity is correct, readjusting if necessary until the required purity is obtained. When purity has been achieved, the convergence can be tackled: don't try convergence first, because resetting the purity magnets will affect the convergence.

Static Convergence Adjustment

As previously mentioned, red and green static convergence should be done first, aiming for perfect overlay at the centre of the screen – preferably using a pattern of squares from a crosshatch generator or the crosses of test card F. Don't be too fussy at this stage, even though we said "perfect overlay", since if adjustments to the dynamic convergence controls are required these will affect the centre registration. If you are very lucky, only small adjustments will be required to produce an acceptable picture. Once the red and green have been centred up, switch on the blue gun and see how far out the blue static convergence is. The static blue magnet moves the blue image up and down, the blue lateral magnet moving it horizontally. So this is a very quick adjustment.

At this point it's a good idea to check the purity again, to see whether the static convergence adjustments have produced any purity errors. If so, do it all again.

Dynamic Convergence

After this has been done one tackles the far more involved business of dynamic convergence. This calls for some explanation.

Different setmakers have used different convergence arrangements. This means that unless one is handling only a limited range of models difficulties can arise for even the experienced engineer. On some chassis a card covering the convergence board shows the intended effect of each control. This is of course most helpful. On other chassis the controls may be given only a circuit reference number, so that the relevant manual is required in order to find out what they are supposed to do.

Convergence Circuit Faults

Let's, as we've done in some past instalments, take the circuit used in the Pye 691 chassis as an example (see Fig. 5). Before doing so however we must make one point clear. If the set has not been interfered with and the convergence suddenly becomes wrong although it was previously right, no attempt should be made to reconverge

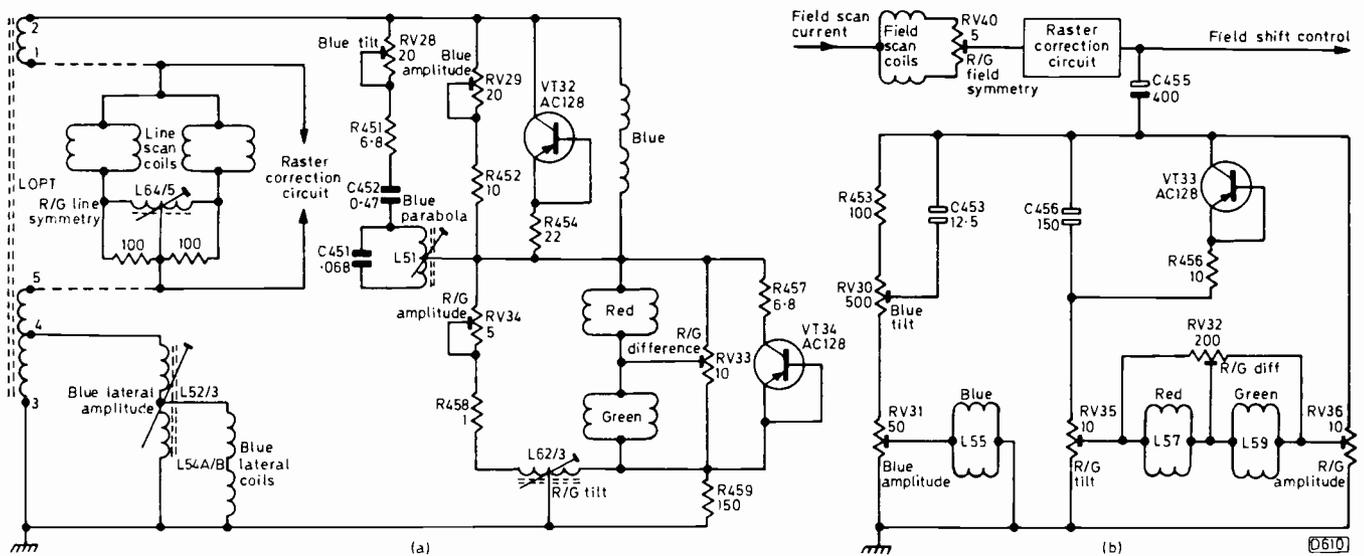


Fig. 5: The line (a) and field (b) convergence circuitry used in Pye hybrid colour sets. The line convergence circuitry is connected in series with the line scan coils via windings 3-5 and 1-2 on the line output transformer.

using the controls unless only one control on the board is suspect, i.e. the exercise is not to reconverge the set but to locate a faulty preset which may have been damaged by heat. Such presets often carry or are asked to carry more current than their wattage rating warrants, or are run near the maximum, which leads to overheating and eventual damage to the track and wiper. The appearance or "feel" often identifies the suspect: by feel we mean that slight adjustment is difficult and feels "grindy".

Some convergence circuit paths are shunted by fairly high value wirewound resistors which can go open-circuit, leaving diodes and/or presets carrying a load for which they are unsuited. As a result several components may be found damaged, with perhaps a burnt board to add to the confusion. The moral here is that if a component is found damaged, be it a preset control or fixed resistor, check the official circuit diagram to see whether the original cause could have been failure of a shunt component or circuit path. Convergence circuitry usually involves several parallel (shunt) paths, and an ohmmeter is of dubious value unless the components to be measured are isolated from the rest for this purpose.

The convergence panel used in the Pye 691 chassis uses three transistors connected as diodes (bases and emitters connected together) plus a number of low value resistors and presets, coils and so on. If a low value resistor is suspected, disconnect one end from the board in order to be able to check for certain whether or not it's open-circuit. With care, a faulty component can be identified and replaced, restoring normal convergence, whereas if an attempt at reconvergence is made with the faulty component still in circuit not only will acceptable convergence be unobtainable but the whole lengthy procedure will have to be repeated when the faulty component is eventually located and replaced. This can mean hours of frustration.

Typical Circuitry

What sort of current flows through the convergence coils, and where is it obtained? Remember that we are not talking now about centre convergence but about bending the three beams vertically and horizontally at the top, bottom and sides of the screen and whilst they are being deflected. This calls for a fair amount of current. More in fact for the blue beam since if you look at Fig. 1 carefully you'll observe that the blue gun is farther from the centre along the vertical axis

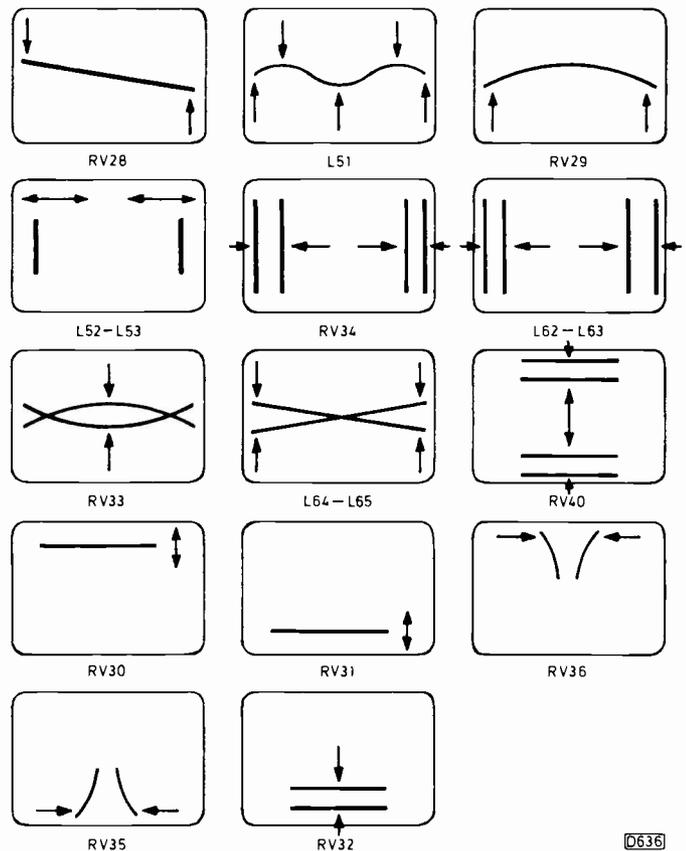


Fig. 6: The effects produced by the various convergence controls in the circuit shown in Fig. 5.

than the other two guns.

The following short account describes how dynamic convergence is achieved in the 691 chassis. Since we need currents which vary along the horizontal and vertical axes, we can use line and field frequency sawtooth waveforms obtained from the currents flowing in the respective deflection circuits. We can in fact use the currents flowing in the deflection coils, by wiring the convergence circuits in series with them, tapping off the required amount of current (say one tenth) and shunting the rest away (hence the heat problems previously mentioned).

Since the red and green guns are equally spaced at either side of the vertical axis, they'll require equal but opposite

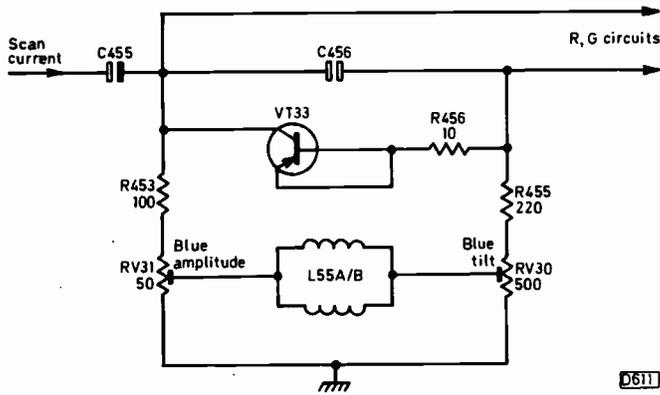


Fig. 7: Modified blue vertical convergence circuit used in later versions of the Pye hybrid chassis.

correction. The correction current will be only about half that required by the blue beam's convergence coils. About 200mA peak-to-peak is required for the red and green horizontal (line frequency) convergence coils and about 400mA peak-to-peak for the blue. The actual current flowing in the convergence coils depends on the amount of correction required: where the convergence is naturally good – at the centre of the screen – no correction current is required. As the distance travelled by the beams becomes greater, so does the possible convergence error and therefore a greater correction is required.

Since the blue gun is mounted centrally, a parabolic convergence waveform is required to give horizontal correction. The line scan current is of sawtooth form: the inductance of the convergence coils tends to alter this to a parabolic form, but nowhere near enough. A capacitor in series with a fixed and a variable resistor are wired across the blue horizontal convergence coils therefore (C452, R451 and the blue tilt control RV28). This alone is still not enough however, additional shaping being required to prevent the blue raster drooping alarmingly at the extreme sides of the screen. The correction required is provided by the parallel connected components C451/L51, the coil being labelled blue parabola. See Fig. 6.

These components affect the shape of the current waveform but not its amplitude. To adjust this, the shunt preset control RV29 (with series resistor R452) are incorporated in the circuit. RV29 is labelled blue amplitude of course. This resistive path shunts away the required amount of power, and can thus change an upward curl at the edges relative to the centre into a downward droop. So that the centre convergence (static) is not upset by this variation at the sides, VT32 is added connected as a clamp diode.

It's quite common for trouble to develop in this particular circuit – it will often be found that the blue horizontal lines cannot be converged with the red and green lines at the left and right-hand sides (droop). The items to check carefully are RV29 and its series resistor R452, and VT32 with its series resistor R454. These are wirewound resistors. The coils and capacitors are rarely at fault.

We've already referred to the need for separate blue lateral convergence – carried out by the separate magnet clamped on the tube neck at the rear. Dynamic blue lateral correction is also required – so that the sides of the blue raster can be adjusted independently. For this purpose a sawtooth current is passed through a small coil wound on the magnet, thus explaining the two leads that go to it. The effect produced can be reversed by swapping over the leads or push-on connectors, and adjusted by means of L52/3.

To summarise so far, we've seen that we can move the edges (left and right-hand sides) of the blue raster up and

down and in and out relative to the red and green rasters. The operation has also to be done with the red and green rasters, but as the two guns are in line with one another only a single set of controls is required so that the rasters can be moved relatively to each other. Once again there's a clamp diode (transistor VT34), with a series resistor, to keep the centre convergence steady. The R/G amplitude and tilt controls (RV34 and L62-3) enable the red and green rasters to be brought into registration at the sides. The R/G difference control RV33 removes bowing of the red and green horizontals while L64-5 enables the red and green horizontals to be tilted to remove the crossover effect.

This then is a condensed version of what horizontal convergence is all about: coils of wire associated with static magnets, and timed/shaped currents. This is only the half of it however. What's necessary to achieve correct registration at the sides is also necessary to get the top and bottom right. So we have more convergence coils, this time wired in series with the field scan coils.

In effect, we break the field scan current return path and insert some wirewound resistors of the variable slider type to enable us to tap off the required field frequency sawtooth voltages that push the necessary currents through L57 (red), L59 (green) and L55 (blue). RV40 varies the current flowing in each half of the field scan coils, and is labelled field (frame actually) symmetry. R453 is in series with two variable controls RV30 (blue tilt) and RV31 (blue amplitude). Similarly we have two variables for red and green, RV36 and RV35. The red and green vertical convergence coils are connected to the sliders of the R/G tilt and amplitude controls, with an additional control RV32 wired across them to vary the current in one with respect to the other.

Due to the inductance of all these coils, the sawtooth waveforms are changed into graceful parabolic curves to enable us to raise and lower and straighten up the images. A modification to the blue vertical convergence circuit (see Fig. 7) made it more like the red/green arrangement, and this is more likely to be met in practice.

Degaussing

Now for another complication. We've previously pointed out that patches of incorrect colour will be present if the purity is not accurate. To this end it's essential that the shadowmask itself is free of magnetism. Any large metal surface can easily become magnetised, and the shadowmask is no exception.

To prevent this, coils (called *degaussing coils*) are fitted around the tube bowl (they are actually mounted on the degaussing shield – something you won't find with later types of tube). Each time the set is switched on, a high

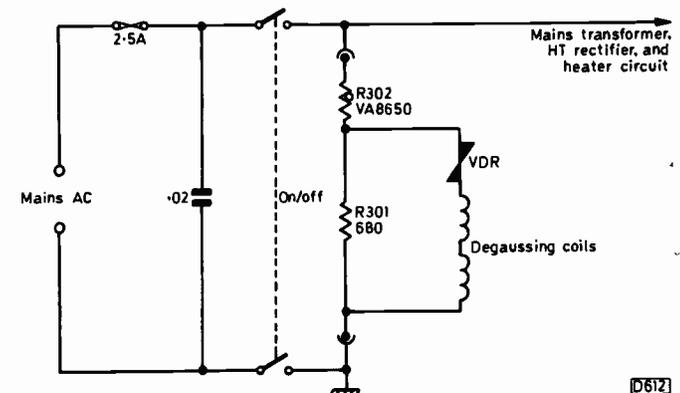


Fig. 8: The tube degaussing (demagnetising) circuit used in Pye hybrid colour receivers.

next month in

TELEVISION

● INTRODUCTION TO VDUs

The TV and computer worlds have been moving closer together in recent times. The c.r.t. has long been a way of presenting a computer's output, but the domestic TV set has now started to take on this role. The more sophisticated TV games units use microcomputers, and as an extension of this some systems can handle educational material as well. So it's time to start thinking of the TV set as a VDU – visual display unit.

There are two main aspects to linking a TV set with a computer: providing suitable interfacing circuitry with a memory to store the data, and conversion of the data into a form that can be handled by the set and displayed on the screen. This type of circuitry was one specialised, but has become commonplace with the advent of i.c.s designed for teletext use.

Various developments are leading to the era of the cheap domestic computer, and several articles and projects are planned to enable you to understand and make use of these new opportunities. As a start, next month the basics of the VDU are explained.

● SERVICING FEATURES

The second instalment of servicing in the field deals with the signal side of things – no signals, weak signals, contrast and brightness troubles and so on – while our beginners series tackles the circuitry used in colour receivers to decode the PAL colour signal.

● VINTAGE TV

Malcolm Burrell has been renovating a Bush TV22 and has made out of it a handy second set. This leads to some reflections on the way in which TV receiver design has evolved over the years – the TV22 dates from 1951.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO.....
(Name of Newsagent)

Please reserve/deliver the DECEMBER issue of TELEVISION (55p), on sale November 19th, and continue every month until further notice.

NAME.....

ADDRESS.....
.....
.....

current (a.c.) is passed through the coils to demagnetise the shadowmask and the associated metalwork. The presence of the positive temperature coefficient resistor (thermistor) R302 (see Fig. 8) ensures that the current rapidly decays to virtually zero.

If patches of impurity are evident, the connections to this circuit are more likely to be at fault than one of the components themselves. In some chassis however a thermistor which is liable to disintegrate is used, and this is a possibility you may have to check. This is especially the case with the double-thermistor used in hybrid GEC colour chassis for example.

Hints on Convergence Adjustments

Having discussed the circuitry involved and what it does, we need only a few hints on using the controls. We can't provide a rigid convergence routine because there really isn't one. There's no substitute for practice, and it's an education to see a hopelessly misconverged test card or crosshatch pattern quickly corrected by an experienced person. If there's a pretty coloured card over the controls to illustrate the effect of each, there's little to be added except to warn that some interaction is to be expected. Static convergence for central beam registration should be carried out first, but one must return to this several times to correct any static misconvergence introduced as a result of adjusting the dynamic convergence controls. If there's no picture guide, the controls will be labelled R/G diff, Blue amp etc. or will simply have circuit reference numbers which will have to be checked with the appropriate service manual.

The basic idea is to start by getting the centre right (approximately) with the static magnets. First switch the blue gun off (by means of the relevant first anode switch) and converge red and green into a single yellow. Then switch the blue gun on. Raise and lower the blue beam by means of the blue static magnet, then bring the blue into horizontal convergence, using the blue lateral magnet, to obtain white.

Switch off the blue gun again and look at the top and bottom to see how far the R/G vertical controls are out of adjustment. If difficulty is experienced in getting good results, aim instead for the same error all the way down the centre vertical lines, appreciating that the static R and G magnets produce an opposite angular movement – try to cater for this. Switch on the blue gun, and recheck the blue static convergence now you've adjusted the R/G vertical controls.

Having done this a few times, you should start to get the feel of each control. When a respectable vertical registration of the three rasters has been achieved, note the positions of the horizontal convergence controls (R/G amplitude, R/G difference, R/G tilt and the corresponding blue controls). Adjust the R/G amplitude control to converge the left-hand verticals, and the R/G tilt control to bring the right side to a nice yellow if separate red and green verticals can be seen. If the red and green horizontal lines cross over, straighten them up with the R/G line symmetry control, and again reset the static convergence if necessary.

Remember that the vertical (field/frame) convergence controls adjust the top and bottom verticals down the centre line, and the top and bottom horizontals (R/G frame difference and R/G frame symmetry for the horizontals, R/G frame amplitude and R/G frame tilt for the verticals). The line controls adjust the sides.

If we've had one recurring trouble with convergence of the 691 chassis, it's been with the shape of the "blue droop" at both sides. If the horizontal blue amplitude control RV29 has no effect, the 10Ω series resistor R452 will be found open-circuit.

Your PROBLEMS solved

Requests for advice in dealing with servicing problems must be accompanied by a 50p postal order (made out to IPC Magazines Ltd.), the query coupon from page 45 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

DECCA 30 CHASSIS

Is there any way of increasing the effect of the pincushion phase coil L404 on this chassis? At optimum adjustment there is still a dip in the lines at the top centre of the screen, while the sides of the raster tilt outwards slightly from the bottom to the top.

We have often found that better control over the pincushion correction can be achieved by replacing the 10 Ω resistor R481 with a 25 Ω or 50 Ω potentiometer. Adjusting such a potentiometer in conjunction with L404 may well clear your trouble.

SONY KV1800UB

When a camera switches to a new shot with more than a minimal amount of red content in it the whole screen suffuses with red/orange, taking about five-fifteen seconds before the colour balance returns to normal. The fault occurs only at the red end of the spectrum, and is not affected by the a.f.c. action.

This is an unusual fault. It would seem that either a transistor in the red video channel is leaky, or that the R - Y chrominance amplifier is going unstable. The transistors in the red channel are Q159/Q160/Q165. Oscillation in the R - Y chrominance amplifier circuit could be due to failure of the collector supply decoupling capacitor C407 (0.01 μ F) or leakage in the emitter decoupling capacitors C404 (10 μ F) or C405 (0.047 μ F). If you are very unlucky, the tube could have interelectrode leakage in its red gun.

THORN 1500 CHASSIS

The picture on this set is very good, but is slightly dark even with the brightness at maximum. Is there any way of increasing the brightness level?

First make sure that R115 (3.9M Ω) which feeds the tube's first anode has not increased in value, and that its decoupling capacitor C82 (0.01 μ F) is not leaky. If these components are in order, the brightness can be increased by adding a high-value resistor between pin 2 (control grid) of the c.r.t. and the h.t. line.

GRUNDIG 5011

The picture size sometimes judders for short periods, and on one occasion the cutout operated. A one inch foldover is present - though not always - on the left-hand side of the screen. There are also very prominent Hanover bars. Attempts at readjustment seem to have no effect on these.

We suggest a careful check on the joints in the line oscillator section and around the wound components in the

line output stage. The judder could be due to R509, R508 or R507 which set the bias conditions in the width circuit. Check also R504 and Di504, which are in series with the width control transducer. When these points have been cleared, set up the line hold control R426 ("Z"). Hanover bars are uncommon on these Grundig sets. The TBA510 and TAA 630 i.c.s in the decoder are suspect if the fault cannot be cleared by adjusting controls LZ and DV in the delay line circuit.

SONY KV1810UB

Every three to four months this set blows the chopper device Q603 on the power supply board and the line output device Q510 on the timebase board. The set works normally after replacing these devices (type SG6533), then the same thing happens three-four months later.

This is a nasty, expensive habit your set has acquired! We have it on good authority that the sync/timebase oscillator i.c. IC501 (CX104A) or the main smoothing electrolytic C606 (120 μ F) can be responsible, and have also known it to be due to the line flyback tuning capacitor C542 (0.018 μ F, 1.5kV).

GEC C2110 SERIES

The main trouble with this set is high e.h.t. With the set h.t. control set correctly, i.e. for 190V at the junction of R58/R59, the e.h.t. is 27kV. If the h.t. is set to reduce the e.h.t. to 25kV the voltages throughout the set are low, giving poor contrast, width etc. With the e.h.t. at 27kV there's defocusing on peak whites, while at 25kV there's smearing etc. There's also a loud caption buzz.

This is clearly an early model - the resistors in the h.t. supply were rearranged in later production. If the e.h.t. is high with P701 set for the correct h.t. voltage and 40V at the emitter of the line output transistor, it's likely that the flyback tuning capacitor C52 is faulty. It should be replaced with the correct type from GEC. Replacing C119 (220 μ F) which decouples the 12V supply to the TCA270 in the i.f. strip should cure the smearing, while fitting an extra 470 μ F capacitor across C187 on the sound board should overcome the caption buzz.

THORN 8800 CHASSIS

This set, which I recently acquired, has obviously been operating in a damp environment. When I first switched on there was no raster, due to the e.h.t. lead to the tube shorting to earth - the insulation had broken down. I managed to cut off four inches and remade the connection to the tube, and also replaced the focus potentiometer (full of green mould!), but there are now random flashes across the tube face when a programme is being broadcast. I can't see any signs of arcing around the e.h.t. section however.

In view of the conditions under which it has been operating, we feel that a new e.h.t. stick should be fitted to start with. This may cure the problem, but if not it could be that corrosion has attacked the signals panel. If so, washing it with methylated spirit may do the trick.

ITT CVC30

There's excessive sibilance on sound, but only on BBC-1, the other two channels being perfect. The picture quality is excellent on all three channels.

Very slight adjustment of the quadrature coil L312 adjacent to the TBA120S intercarrier sound i.c. (IC302) will clear this trouble.

DECCA CTV25

This old colour set gives excellent results except for limited colour and an unsynchronised PAL switch. Tuning for maximum ident signal at the emitter of the ident emitter-follower Tr603 with the ident coil L602, the burst coil and VR602 (discriminator balance) produces a signal of about 7V peak-to-peak and about 8.5V across the colour-killer reservoir capacitor C609. This gives reasonable but intermittent colour, but the PAL switch runs unsynchronised – in fact it seems to favour green faces! Reducing the amplitude of the ident signal results in correct PAL switching but loss of colour.

You don't seem to have enough ident signal. There should be about 10V peak-peak at the emitter of Tr603, with L602 adjusted for slightly less than maximum ident signal. We'd suggest you check by substitution the two electrolytics in the ident circuit, C611 and C614, both 10 μ F. The ident should be improved by replacing the ident diode D604 – use an OA91 – and its coupling capacitor C615 (0.22 μ F).

THORN 2000 CHASSIS

When this set comes on the picture and sound are good. It takes up to half an hour for this to happen however, and afterwards it sometimes goes off again for a second, leaving a dim raster. The picture and sound come on gradually. The picture appears in monochrome at first, then the colour gradually comes up. The signals always return gradually following the occasional dim raster.

As all signals are involved it seems that either a supply line is going intermittent (monitor the 30V lines with a meter during the fault) or there's a fault in the i.f. or a.g.c. sections of the set. For the latter possibility, start by checking the voltage across the a.g.c. decoupler C56 in the i.f. strip. This should be about 12-14V with a strong signal. If the a.g.c. line is working correctly, check voltages in the i.f. strip. If not, check back to the a.g.c. stages VT9/10: the electrolytics C54/5 (both 50 μ F) could be playing up.

KÖRTING 51765

The raster on this set flashes white two or three times then stays white, with the picture in the background and prominent flyback lines. The brightness control has no effect on the white screen.

The trouble is often due to heater-cathode leakage in the tube in these sets. To check this, measure the three cathode voltages on the tube base. If these are low, remove the tube base and see whether the voltages on the base return to normal. If so, the tube is almost certainly at fault, and fitting a 6.3V heater isolating transformer will overcome the problem. If the tube is not at fault, check the two transistors (luminance output) on the right side of the tube base and the associated voltages.

THORN 8800 CHASSIS

This set has been troubled with the same problems from new. The symptoms are that the red content of the picture changes to mauve, followed by total loss of colour, and when changing channels the picture appears in monochrome for three-four seconds before colour appears. Adjusting the set oscillator frequency control R210 and trimmer C188, both associated with IC5, seems to make no difference. IC5 (SC9506/TBA395) has been replaced.

Some batches of TBA395 i.c.s were suspect for thermal effects, but since this item has been replaced and the

symptoms remain it seems clear of suspicion. We suggest you replace the crystal and the two electrolytics C186 (6.8 μ F) and C187 (1 μ F) associated with R210. It's not beyond possibility that the following SN76227 demodulator/PAL switch/matrixing i.c. (IC4) is faulty.

TELETON TA12

Picture wobble on this portable has got worse. There's a white hum bar on the screen but no hum on sound, and at most times the field is unlockable.

Despite the absence of hum on sound, it would seem that there is excessive 50Hz ripple on the supply. This is probably due to failure of one of the rectifier diodes D601/2 connected to the mains transformer, or to loss of capacitance in the associated reservoir capacitor C603 (2,200 μ F, 25V).

SONY TV9-90UB

The trouble on this monochrome portable is white streaking across the whole screen from any very black picture content, and black streaking from very white picture content. The fault is present on v.h.f. only, u.h.f. operation being all right.

This sounds like a form of i.f. instability. We suggest you check the small ceramic decoupling capacitors such as C324, C337 and C332 in the i.f. strip, and if necessary the electrolytics – C314, C333 and C334. It's possible, though unlikely, that the v.h.f. tuner or the video output transistor Q503 could be responsible.

THORN 2000 CHASSIS

This set has given several years trouble free viewing. It's now developed the following fault however. Every few minutes the colours unlock, forming not so much Hanover blinds as Venetian blinds. The trouble can be temporarily cured by pushing lightly on the push-button tuner for the particular station. The tuner has been repaired, so I assume it's a decoder fault.

Decoder problems with the 2000 chassis are quite rare. From your description, it seems that the reference oscillator is drifting off lock. Suspect components are the electrolytics C3 and C7 (both 4 μ F) in the burst gate/amplifier circuit, the OA91 diodes (W1-4) in the burst detector circuit, the BC107 d.c. amplifier transistor VT3, and the crystal. Since these components are inexpensive, we'd replace the lot then adjust R13 (detector balance) and R15 (oscillator frequency) as described in the manual.

THORN 1591 CHASSIS

The original trouble with this set was field collapse, the cause being traced to VT16. The original transistor had no marking however, other than a couple of dots, and is marked on the circuit as type TVT15. None of this means much to me, but I found that the set could be got working again by fitting a BC147 in this position. The only trouble now is field judder, mostly at the bottom of the picture. I've checked the height and linearity controls, and both are in order. Could the transistor I fitted be responsible?

VT16 is the field linearity amplifier and TVT15 is a Thorn classification, which includes types BC149, BC208B, BC183LB, BC183LC and BC349B. The BC149 is probably most readily available. We suggest you fit one of the approved devices then, if the fault persists, check the field output coupling capacitor C78 (1,000 μ F) and its connections and if necessary the output transistors VT19/VT20. If C70 is 0.002 μ F, change it to 0.01 μ F.

JVC 7170GB

The problem with this set is that the picture moves to the right, then line sync is lost. The fault rights itself after a while. The field hold is in order and can be adjusted on a normal picture.

Suspect components are the flywheel line sync discriminator diodes D01 and D02 (type 1N34A), and the electrolytics in this part of the circuit, C06 (4.7 μ F) and C07 (47 μ F). The line oscillator transistor TR03 is another possibility. There's a rather unusual stage that inverts and shapes the waveform fed back from the line output transformer to the flywheel sync discriminator circuit. The transistor involved (TR02) and the coupling capacitor C13 (1 μ F) are further suspects. Check D01/2 first though.

GEC C2110 SERIES

When the picture first appears, there's a bright horizontal band, about $\frac{1}{2}$ in. deep, at the bottom. This disappears after a couple of minutes. The picture is then normal except that the very lowest of captions are half lost below the bottom of the screen. This later fault was apparent before the bright band first started to appear.

The bright band is foldover when the field timebase first comes into operation, and the general problem seems to be lack of field linearity. Make sure that the field output stage mid-point voltage control P454 is correctly set, then check the thermistor TH451 (VA1034) in the output stage emitter bias network and the field charging capacitors C457 (47 μ F) and C458 (22 μ F).

TEST CASE

203

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

We took in part exchange a console Decca colour receiver fitted with the later version of the CTV25 series chassis. Although there was no raster, the set was in astonishingly good condition for its age – a nice clean chassis, and a good quality audio section. We decided therefore to correct the line timebase fault, run over the chassis generally, and place the set on the market at a fair price.

The line output stage fault was simply a short-circuit boost capacitor. This was replaced, and as we'd had trouble with the high-voltage capacitors in the line output stage in these sets we decided to go the whole hog and replace all dubious looking components in this area. Following these replacements and complete readjustment of the video, chroma, timebase and convergence sections the results were really very good. Although the tube was the original one, the picture was quite bright with good colour, free from any blurring or colour imbalance over the full range of the grey scale.

The set was put on the market and was bought by a young couple who had only recently married and taken up residence on a new housing estate. Having little spare cash, they were delighted to have acquired such a handsome set at a low price, particularly in view of the good quality sound. This latter feature was particularly appreciated by the young man, who was a hi-fi enthusiast. Less than a week later however they were back in the shop, all apologetic but obviously very concerned. "The set's working fine" they reported, "but we can't keep it on for long because of the ringing it causes in our ears."

This was a new one on us, so we despatched our trusted senior technician, who had been in the business since the

days of 9in. Marconiphone sets, to see what was going on. After spending a few hours (yes!) listening with the couple he reported that he couldn't understand the problem since the sound seemed excellent to him, with no ringing, yet the set was obviously causing the couple distress.

Have you any idea what the trouble was? See next month for the answer and another case in the series.

SOLUTION TO TEST CASE 202

– page 661 last month –

You will recall that the problem was no raster on a set fitted with the Pye hybrid colour chassis, and that after extensive tests it was discovered that all three tube guns were excessively biased, with low grid voltages. Now a triode is used as a clamp in each grid circuit, the cathodes of the three clamp triodes being connected together and returned to the clamp voltage source. A fault common to all three clamps would suggest trouble somewhere in the common cathode circuit therefore.

The three cathodes are returned to chassis via R397 (8.2k Ω), which forms a potential divider with R393. The latter is also 8.2k Ω , and the voltage at the junction of these two resistors – the clamp voltage – is smoothed by a 4 μ F electrolytic (C371). If the clamp voltage falls, the voltages at the three c.r.t. grids will also fall, thus reducing the brightness of the picture – to black out if the voltage falls sufficiently. Possible causes of low voltage would be C371 leaky or short-circuit, R393 high in value or open-circuit, or loss of the supply to R393 (via R389, decoupled by another 4 μ F capacitor, C367). The fault was eventually traced to R393 having increased significantly in value.

QUERY COUPON

Available until 19th November, 1979. One coupon, plus a 50p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 43.

TELEVISION NOV. 1979

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R 0NE. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/Sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £9.50, Overseas £10.50 per annum payable to IPC Services, Oakfield House, Perymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

TV LINE OUTPUT TRANSFORMERS (Prices include VAT at 15%)

Discount to Trade

Post and Packing 70p

BUSH TV123 TV124 TV125 or U TV128 TV134 TV135 or R TV138 or R TV139 TV141 TV143 TV145 TV148 TV161 TV165 TV166 TV171 TV175 TV176 TV178 TV181 or S TV183 or D TV183S TV185S TV186 or D TV186S TV186SS TV191D TV191S TV193D TV193S TV198 TV307 TV313 TV315 Price £8.50	MURPHY V843 all models to V979 V153 V159 V173 V179 V1910 V1913 V1914 V2014 or S V2015D V2015S V2015SS V2016S V2017S V2019 V2023 V2027 V2310 V2311C V2414D V2415D V2415S V2415SS V2416D V2416S V2417S V2419 V2423 A774 All complete with valve base Price £8.50	DECCA MS1700 MS2000 MS2001 MS2400 MS2401 MS2404 MS2420 Price £8.50 PHILIPS 23TG170a all models to 23TG176a G24T230a ... all models to G24T310 19TG170a ... all models to 19TG179a G19T210a G19T211a G19T212a G19T314a G19T215a G20T230a Price £8.50 G24T324 G24T326 G24T329 Price £10.00	PYE 58 64 59 68 60 75 61 78 62 77 63 80 61 93 83 94 84 95/4 85 96 86 97 92 98 150 161 151 170 155 170/1 156 171 160 171/1 Chassis 189, 173 RV293B 388 589, 573 789 Price £8.50 KB-ITT By Chassis: VC1 VC2 VC3 VC4 VC11 VC51 VC52 VC52/1 VC100 VC100/2 VC200 VC300 Price £8.50	GEC BT454 BT455 BT455DST 2000DST ... all models to 2044 2047 ... all models to 2084 2104 or /1 2105 or /1 Price £8.50 SOBELL ST196 or DS ST197 ST290 ST297 1000DS ... all models to 1102 Price £8.50 THORN GROUP Ferguson, H.M.V., Marconi, Ultra. By Chassis: 800, 850, 900, 950/3, 960, 970, 950/1, 950/2, 1400, 1500, 1500, 1580, 1590, 1591, 1612, 1712 Or quote model No. Price £8.50 1600, 1615 1690, 1691 Price £10.20	COLOUR TRANSFORMERS DECCA CS1730, 1733, 1830, 1835 £9.51 DECCA 30 Series Bradford Chassis £9.51 DECCA 60, 80, 100 Series £9.51 GEC Dual STD Hybrid £11.59 GEC Single STD Hybrid £11.59 GEC Single STD Solid State £9.51 ITT CVC 1 to CVC 9 £9.51 ITT CVC 20 £10.53 ITT CVC 30, CVC 32 £9.51 PYE/EKCO 725 Chassis £9.51 PYE/EKCO 731, 735, 737, 741 Chassis £9.51 PYE/EKCO 713, 715 Chassis £9.51 PHILIPS G8, G9 Chassis £9.51 PHILIPS 570 Chassis £10.53 THORN 3000, 3500 EHT and SCAN £8.48 THORN 8000, 8000A, 8500, 8800 £10.02 THORN 9000 £10.02 TELPRO All Models £9.51 RANK A823, A823A, A823B £11.35 TANDBERG CTV 2-2 £9.51 PYE/EKCO 691 to 697 Printed circuit type £15.26 PYE/EKCO 691 to 697 Wired Type P.O.A.
BUSH MURPHY A816 Chassis TV309 TV311 V2029 V2427 Price £10.30	INDESIT 20EGB 24EGB with rectifier holder Price £9.51	WINDINGS Post & Packing 40p BUSH Colour Hybrid Quadripler type £6.25 RANK T20A, 2179 chassis £6.83 PHILIPS G6 EHT Overwind £7.20 PHILIPS G6 Primary £6.00 PYE 691 to 697 EHT Overwind* £3.07 PYE 691 to 697 Primary Winding* £4.60	*Please state Printed Circuit version or Wired version.		

Tidman Mail Order Ltd.,
 236 Sandycombe Road,
 Richmond, Surrey.

MON-FRI 9 am to 12.30 pm.
 1.30 pm to 4.30 pm.
 Closed Wednesday afternoon

Approx. 1 mile from Kew Bridge.
 Phone: 01-948 3702

Hamond Components (Midland) Ltd.,
 416, Moseley Road,
 Birmingham B12 9AX.

MON-FRI 9 am to 1 pm.
 2 pm to 5.30 pm.

Phone: 021-440 6144.

Contact your nearest depot for service by-return. Callers welcome. Please phone before calling.

ARE YOU

USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling used colour televisions from home in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "How to Deal Successfully in Used Colour Televisions" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can succeed immediately.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure certain success. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail - for both televisions and new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. Plus FREE on-going advice and FREE regular updating service.

You can start tomorrow - but you'll need our guide. The latest big illustrated edition is out now, and costs just £4.95 - a small price to pay for financial independence!

SAME DAY SERVICE

CITY PUBLISHING, HAYWORTH ROAD, SANDIACRE, NOTTINGHAM NG10 5LL

To: City Publishing, Hayworth Road, Sandiacre, Nottingham NG10 5LL.
 Please send by return post "How to Deal Successfully in Used Colour Televisions".
 I enclose cheque/p.o. for £4.95.

NAME
 ADDRESS

**BIG NEW EDITION
 OUT NOW!**

New Spares Service from W.M.T.V. Ltd.

Tested Ex-Equipment

Valves	
DY802/86/87	10p
ECC82	10p
ECL80	8p
EF80	8p
EF85	8p
EF183	8p
EF184	8p
EY86/87	10p
PCC85	15p
PCF80	10p
PCF802	12p
PCL82	12p
PCL84	15p
PCL85/805	15p
PFL200	15p
PL36	20p
PL504	25p
PL508	30p
PL509	80p
PL519	£1.00
PL802	£1.20
PY500	40p
PY800/81/801	15p
6F23	20p
30FL1/2	25p

Many more available.
 15% V.A.T. to be added to
 prices shown.

Postage paid on orders
 over £2.00.
 Orders under £2.00,
 please add 10p per
 valve, p&p.
 Discount of 10% on
 orders over £20.00.
 Large quantities of
 untested valves sold,
 prices on request.

Ex-Equipment Colour

Tubes	
19" A49 12ox	£18.00
20" A56-12ox	£20.00
25" A63-12ox	£15.00
26" 90°	£24.00

Please add £4.00 p&p
 per C.R.T.
 Please add 15% V.A.T.
 to all items ordered,
 then add postage indicated.

MANY MORE SPARES
 AVAILABLE
 PLEASE WRITE OR PHONE
 NOW.

**PERSONAL CALLERS
 WELCOME.**

W.M.T.V. TRADE SALES LTD.
 92, High Street, Kings Heath,
 BIRMINGHAM, B14 7JZ

Manufacturers Surplus Components FIT THE RIGHT PART

300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt resistors £1.50
 150 mixed 1 and 2 watt resistors £1.50
 300 mixed **Capacitors**, improved pack, most types £3.75
 100 mixed **Electrolytics** £2.20
 300 mixed **Printed Circuit** mounting **Components** for various TVs, resistors, caps etc. £1.50
 300 printed circuit **Resistors** $\frac{1}{2}$ to 4 watt £1.00
 100 **High Wattage** TV resistors, **Wirewound** etc. £2.75
 100 mixed miniature Ceramic and Plate Caps £1.50
 100 mixed polystyrene capacitors £2.20
 25 mixed **Pots** and **Presets** £1.20
 25 mixed **TV Presets** £1.00
 20 assorted **TV VDRs** and **Thermistors** £1.20
 10 assorted **TV Convergence Pots** £1.00
 20 assorted **TV knobs**, includes push button, chrome, control types etc. Mostly Thorn and ITT £1.00
 10 assorted **Valve Bases**, B9A, ceramic, EHT, etc. £1.00
 20 assorted **Sync Diodes** blocks for various TVs £1.00
 25 assorted **Pulse Caps** high voltage £1.25
 10 **Spark Gaps** £1.00
 20 assorted **Zener Diodes** 1 watt and 400MW £1.50
 100 **Mixed Diodes**, includes zener, power, bridge, varicap, germanium, silicon etc. All full spec. £4.95

NEW

4-433 C.T.V. Crystals
 Long Leads £1.00 each
 3 for £2.50

New Improved Transistor Packs

100 New and Marked Transistors including: BC148, BC154, BF274, BC212L, BF200 and lots of others only £4.95

200 Transistors as above and including 2N3055, AC128, BD131, BFY50, BC238, BC184L only £9.95

Why Buy Expensive Triplers!
 Repair your old 5 and 3 sticks at a Fraction of the Cost.
 10 Replacement Rectifier Sticks (Thorn). £1.00

Special TV Bargain Parcels

Lots of useful parts including damaged panels, tuners, components etc. 10lb for £7.50
Hardware Pack
 Includes BA nuts and bolts, nylon, posidrive, self-tapping "P" clips, cable markers, clamps, fuse holders etc. £1 per lb.

THORN SURPLUS

3500 Series **Scan Coils**, new and boxed, complete with convergence yoke, purity assembly, static controls, leads and sockets £5.25
 3500 **Focus** units with metrosil £1.50
 3500 "625" line **VHF Kit** for wired systems £9.50
 4 **Knobs** black with chrome caps to fit ITT, Thorn, GEC and most small diam. shafts 60p per set
 950 rotary transistor tuner with leads and slow motion drive £3.00
 950 bottom panel complete with i.f.'s switch etc. £3.00
 950 line transformer (not Jellypot) £2.50
Convergence Pots with knobs. 5 Ω , 10 Ω , 20 Ω , 30 Ω . 8 of 1 type £1.00. 8 of each £3.50

SAVE THAT TUBE.

Fit our **C.R.T. Isolating Transformer**. Ideal for HTR/Cath. Shorts. 200-220-240 inputs. 750-900 MA outputs with thermal cutout. Made for **Thorn 4000** C.T.V. but works O.K. on other sets. £2.00 each 3 for £5.00

MISCELLANEOUS

Philips G8 Tube Base Panels
 Complete, but PCB's cracked, ok for spares. Focus, base, leads, plugs etc. 2 for £1

Bush CTV 25 Quadrupler Remo type 'Q25B. equiv. to ITT. TU25 3QK. with mounting brackets. £4.25 each. 3 for £10

GEC single standard, hybrid chassis. convergence panel. Brand new, complete with plugs and leads £2.50

Focus unit with lead, for above chassis £1.50

ITT Featherlight Super. Side Chassis, with controls, V. Cap Tuning Panel, Regulator, P/Button Switches, Bridge Rec. etc., etc. £4.95
 I.C. for above £1.00

SPECIAL OFFER

GEC transistor rotary tuners with slow drive, AE Skt. and leads **2010** Series £1.50

KB VC3 VHF tuner with valves £1.50

KB VC3 transistor tuner "UHF" £1.50

ITT VC200 transistor tuner (Philips type) £1.50

ITT VCVS power panel. New but five resistors never fitted £1.50

Pye 697 line and power panels, damaged or some bits missing but invaluable for spares £2.00

Pye mono mains droppers with fusible link. 147 Ω + 260 Ω 50p 3 for £1.00
 69 Ω + 161 Ω 50p 3 for £1.00

Decca "Bradford" C.T.V. triplers 25KV £3.00 each 4 for £10

Portable TV EHT Sticks "Siemens TV 18 KV". Fit most portables 50p each 3 for £1.00

Pye 18" CT200 V. Cap P/B Assembly with leads and plug £1.50

EMO. On/off switch £1.00

G.E.C. S/S Hybrid Focus Assembly with lead £1.50

2 x **Coax Sockets** on plates suitable for various Continental T.V.s 50p

1-9 **Amp T.V. Cutouts** Suitable for DECCA and THORN sets. 60p each. 3 for £1.50

White Ceramic TV Resistors
 20 Ω 16W, 180 Ω 11W, 13 Ω 11W. 10 of any one type £1.20
 10 of each type £3.00

2-2k fusible, vertical mounting **Screen Feed** resistors 9 watt 8 for £1.00

0-47 Ω $\frac{1}{2}$ watt emitter resistors 40 for £1.00

10 μ F 400V modern Small Type 8 for £1.00

4.7 μ F 63V 20 for £1.00

1000 μ F 16V 10 for £1.00

Bias Caps 330 μ F 25v 10 for £1.00

470 μ F 25V 10 for £1.00

4,500 μ F 35V cans 80p each

100 μ F, 32 μ F, 300V 2 $\frac{1}{2}$ " x 1 $\frac{3}{8}$ " 50p

Avoid Lethal Shocks
 Buy our specially designed

EHT Probe, removes high voltage charges from tubes, caps, etc. Heavily insulated with lead and earth connector 60p each

B9A P.C. valve bases 20 for £1.00

EY87/DY87 EHT bases 10 for £1.00

PL509/PY500 ceramic bases 10 for £1.00

C.T.V. Tube bases 5 for £1.00

20mm **Antisurge Fuses**. 800MA, 1A, 1.25A, 1.6A. 12 for £1.00

2A, 2.5A, 3 15A 100 for £7.00

TH1 thermistors 6 for £1.00

TH3 thermistors 10 for £1.50

Aluminium **Coax Plugs** 8 for £1.00

Metal Coax Couplers 6 for £1.00

200V 1A **Diodes 10D2** (equivalent to 1N4003) 20 for £1.00

Miniature "Terry" clips ideal for screwdrivers and small tools etc. 40 for £1.00

Low profile 16 pin quill

I.C. Sockets (to fit most "Q" series I.C.) 12 for £1.00

Cassette Motors self regulating, 9V, make unknown type 9FM 90p

Rediffusion/Doric Mk 13 5 stick **Triplers** can be modified for other sets £1.00

Portable T.V. Batt. Leads with Croc Clips and flat 2 pin socket Fits BRC sets £1.50

Miniature Level/Batt. Meters as fitted to many cassette recorders 90p

Also:- **Miniature Mains Transformers** 4-5V-0-4-5V at 250Ma 90p each. 3 for £2.50

LOUDSPEAKERS

2 $\frac{1}{4}$ " Round 8 Ω 70p
 2 $\frac{1}{4}$ " Round 20 Ω 90p
 2 $\frac{1}{2}$ " Round 8 Ω 80p
 6" x 4" Elliptical 8 Ω £1.25
 4 $\frac{1}{4}$ " x 2 $\frac{3}{4}$ " Elliptical 8 Ω for R.B.M. £1.30
 Mono T.V.

PROTECT YOUR PROPERTY

Buy a "SENTINEL" **Smoke and Gas Detector**. Uses TGS105 plug in sensor, housed in 3 $\frac{1}{2}$ " diameter diecast box. 24V. Convertible to 12V. Will activate lamp or relay.

With Data and Circuit £16.95
 Suitable 24V Relay £1.00

De Luxe Fibre Glass Printed Circuit Etching kits

Includes 150 sq. ins. copper clad F/G. board. 1 lb ferric chloride 1 dalco etch resist pen. Abrasive cleaner. Etch tray plus instructions.

Special Price £4.95.

1 lb F.E. C1 To mil. spec. £1.25

5 lb F.E. C1 To mil. spec. £5.00

150 sq. in. **Single sided** board £2.00

150 sq. in. **Double sided** board £3.00

500 Watt

Dimmer Switch

Toroidal mains suppression, fused with satin aluminium knob, white.

ONLY £3.45.

ZENERS

400MW. 4-3V, 4-7, 6-8, 7-5, 30V 10 of one type 80p

1-3W. 12V, 13V, 18V, 10 of each type £3.00

10 of one type £1.00

10 of each type £2.50

6 for £1.00

DIACS BR100 4 for £1.00

STABILIZERS TAA550 4 for £1.00

GEN. PURPOSE DIODES

IN4000 30 for £1.00 IN4003/10D2 20 for £1.00

IN4002 25 for £1.00 IN4148 20 for £1.00

BY476 (BY176) 18kV. 2.5Ma EHT REC 60p each 3 for £1.50

ULTRASONIC TRANSDUCERS

Transmitter and receiver. 40 kHz 14 mm diam. £4.25 pair

Send **40p P. & P.** on all above items; send Cheque or P.O. with order to:-

SENTINEL SUPPLY DEPT. TV

149a Brookmill Rd., Deptford, London SE8

(Mail Order address only. Callers by appointment)
 Trade enquiries for quantity welcome.

Surplus stocks purchased for cash.

TV'S TV'S TV'S

THOUSANDS OF MONO TV'S IN STOCK

All makes - all sizes from £1.15. Square screens from £6.90. Clearance of 25" D/STD CTV'S (Philips 500 and GEC 2028 only). Checked complete £16.10 each, add £8 p/pkg. Earlier model S/STD (Philips 511, GEC 2040, Pye Hybrid etc) Singles tested tube & checked complete £39.10.

Quantities from £27.60 each
Singles working £48.30 each
Add £6 p/pkg

More recent S/STD CTV'S always in stock (Pye Varicaps, Bush Integrated, Thorn 3500/8000, Decca Bradford, GEC 2100, Korting, Grundig, Luxor, Japanese etc). Sold with tube tested from £46, working from £64.40.

Ring for quotations

EX-TV SPARES

RANK BUSH MURPHY 184 SERIES ETC

Decoder (Single IC) or Line Board £13.80
I.F. Panel or Power Panel £9.20
Convergence Panel £6.90
Tuners £6.90
Complete EHT Stack £20.70

GEC HYBRID 2040/1 SERIES AND PYE HYBRID CHASSIS

Decoder or DCA (Inc. Valves) £13.80
I.F. Panel or Convergence Panel £9.20
Line Panel £16.10
Tuners £6.90

PHILIPS 511

I.F. Panel £9.20
Tuners £6.90
Lopt £9.20

Any above add £1.60 postage & packing

RING FOR QUOTATIONS ON OTHER SPARES

COLOUR TUBES

(fully tested)
25" £18.40
19" £20.70
22" £25.30
26" £29.90
Plus £4.00 p/pkg.

MONO PANELS/TUNERS

Most types £3.45
£1 p/pkg.

VEGA MONOCHROME TUBES

(Brand new USSR Manufacture in Maker's Box with 12 months Guarantee)
20" Size £15.53
24" Size £17.83
Add £2.50 p/pkg.
Discounts for orders over five.

MULLARD COLOUREX/MAZDA NEW LIFE TUBE REBUILDS

(Callers only)
One year guarantee.
Any size only £30.65 plus old glass.

SPECIAL OFFER

20"/24" Single/STD PYE/EKCO/PHILIPS TYPE 230 (Plastic back) Re-furnished with good cabinet and brand new USSR tube (12 month guarantee).
20" Model £32.20
24" Model £34.50
Add £4.00 p/pkg.

ALL PRICES ARE INCLUSIVE OF VAT.

TRITEL GROUP

NORTHERN

Thornbury
Roundabout
Leeds Road
Bradford 3
Tel: (0274) 685670

SCOTLAND

Peecock Cross
Industrial Estate,
Burnbank Road
Hamilton.
Tel: (0698) 282141

LONDON

395/397 Albany Road
Off Waltham Road
LONDON SE5
Tel: (01) 703 4040

WEST

Unit 4a
Bulwark Industrial
Estate, Chopetow,
Nr. Bristol.
Tel: Chopetow
(02912) 6652

MIDLAND


48/52 Pershore
Street,
Birmingham 5.
Tel: (021) 822 1023

SOUTHERN

Walling Street
Hockcliffe, North
Dunstable (on A5)
Tel:
Leighton Buzzard
(0525) 210768

MAIL ORDER SEND CWO (CHEQUES OR UNCROSSED PO'S) TO ANY BRANCH

NOW AT LAST . . .

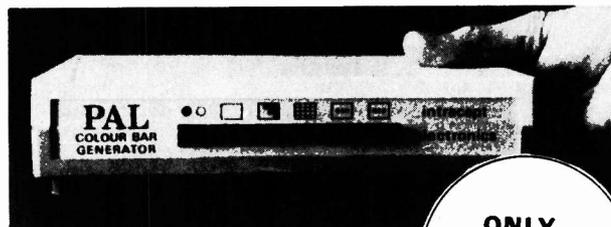

A TRULY PORTABLE COLOUR BAR GENERATOR KIT!

ONLY
£59.50
INCLUSIVE

- * Yes, truly portable - runs (for up to 10 hours) on its own built-in rechargeable battery OR direct from mains via Power Unit supplied.
- * Small enough to be carried in a Tool Case, it measures only 205mm x 143mm x 40mm, and weighs a mere 500g.
- * Push button selection provides:
 - Peak White Raster.
 - Linearised Grey Scale.
 - Crosshatch.
 - Standard 75% Saturated 100% Amplitude Colour Bars.
 - Red Raster.
- * Modulated UHF Output fixed at Channel 45 (Approx). Just send £59.50 INCLUSIVE for a complete kit including a professionally finished Case, Ready Built Power Unit/Charger, Ni-Cad Battery Drilled & Tinned P.C.B., Crystal, 11 I.C.'s & Holders, Push-Button Switch Assy., Resistors, Capacitors, Transistors, Diodes, Sockets, Wire, Nuts & Bolts.

to: **INTRACAPT ELECTRONICS LTD.,**
203 Picton Road, Liverpool L15 4LG.
Tel. 051-733 3042.

PLEASE ALLOW 28 DAYS FOR DELIVERY

SOUTHERN IRELAND DEALERS

We are the largest stockists in the south of Ireland of clean used T.V. sets.

PYE - BUSH - PHILIPS - FERGUSON - KORTING DECCA ETC.

UHF/VHF Mono from **£18.00** each
Colour from **£125**

All Sets Tested & Cabinets Polished.
Over 2,000 sets in stock.

Visit our warehouse and see for yourself.

Delivery can be arranged.

T.V. WHOLESALE DISTRIBUTORS LTD.

E.D.I. House, Kylemore Park West Industrial Estate, Dublin 10. Tel. 364139 or 791995.

Irish stockists for the new 'Tyne' colour sets.

MAIL ORDER PROTECTION SCHEME

The Publishers of *Television* are members of the Periodical Publishers Association which has given an undertaking to the Director General of Fair Trading to refund monies sent by readers in response to mail order advertisements, placed by mail order traders, who fail to supply goods or refund monies owing to liquidation or bankruptcy. This arrangement does not apply to any failure to supply goods advertised in a catalogue or in a direct mail solicitation.

In the unhappy event of the failure of a mail order trader readers are advised to lodge a claim with *Television* within three months of the date of the appearance of the advertisement, providing proof of payment. Claims lodged after this period will be considered at the Publisher's discretion. Since all refunds are made by the magazine voluntarily and at its own expense, this undertaking enables you to respond to our mail order advertisers with the fullest confidence.

For the purpose of this scheme, mail order advertising is defined as:—

'Direct response advertisements, display or postal bargains where cash had to be sent in advance of goods being delivered'. Classified and catalogue mail order advertising are excluded.

THE FAMOUS BI-PRE-PAK

CROSS HATCH GENERATOR

THOUSANDS SOLD!



LIMITED STOCKS - SO ORDER PROMPTLY

In kit form with instructions.
Inc. V.A.T.

£12.25

Ready built and tested (less
batts) but inc. V.A.T.

£14.95

**NO EXTRA TO PAY IF YOU
ORDER BY POST IN U.K.**

To pay by Access or Barclaycard just phone in your number.

More than ever these days, a cross hatch generator is absolutely essential to TV engineers, etc. It is the only accurate way to align all three guns in colour TV. The proven reliability, small size, easy operation and stability of this truly famed instrument is such that we are offering it once again, but this time, when stocks have been sold, it is not likely that supplies will be available again at anywhere near present prices. With improvements incorporated - plug-in I.Cs for example - it is going to be wanted more than ever. Many thousands are in regular use by TV renters and suppliers, etc. As this Generator is a VIDEO FEED UNIT and NOT R.F., it can be used anywhere overseas without having to worry about frequency matching. Operates from its own self-contained standard batteries.

- ★ FOUR STANDARD PATTERN SELECTOR SWITCH GIVING VERTICALS, HORIZONTALS, DOTS AND CROSS HATCH
- ★ TOUGH FIBRE GLASS CASE 5½" x 3" x 3"
- ★ OPERATES FROM SELF-CONTAINED BATTERIES
- ★ VERY EASY TO CARRY AROUND - REQUIRES NO EXTERNAL POWER SOURCE
- ★ PLUG-IN I.Cs AND SENSITIVE SYNC PICK-UP CIRCUIT
- ★ FUNCTIONS TO FULL PROFESSIONAL AND COMMERCIAL REQUIREMENTS
- ★ FOR PROMPT, NO DELAY DELIVERY
- ★ IN KIT FORM OR READY-BUILT, TESTED AND GUARANTEED

Orders by post to:

STIRLING SOUND,
37, Vanguard Way, Shoeburyness, Essex.
Telephone (03708) 5543

Personal Shoppers:

BI-PRE-PAK LTD., 222-224 West Road,
Westcliff-on-Sea, Essex SS09DF.
Telephone Southend (0702) 351048.

For those who appreciate Quality

a complete high quality colour television receiver kit

The Forgestone 500 New Generation 20AX System

- 20AX Hi-Bri tube
- Pin diode tuner
- Full technical construction manual
- Glass epoxy printed circuit panels
- Eleven integrated circuits
- Ready built and aligned I.F. module
- All solid state
- A Teletext decoder kit is available for the Forgestone 500 which includes assembled and tested L.S.I. module, power unit, interface, keypad and complete instructions
- Modern cabinets
- Fully isolated and protected power supply
- Latest diode split L.O.P.T.
- Low consumption

Buy as you build. All Forgestone Kits are for the constructor of today. Sections of the Kit are available separately. Please send stamp for further details of these quality products.

Forgestone Colour Developments Limited

Ketteringham, Wymondham, Norfolk, NR18 9RY
Telephone: Norwich 810453 (STD 0603)

Telephone or Mail Orders accepted on
Barclaycard/Access



TV LINE OUTPUT TRANSFORMERS

by FAST RETURN OF POST SERVICE

MONO LOPTS

Most makes supplied

£7.90 TRADE

£8.50 RETAIL

p&p 70p each item

COLOUR LOPTS

Philips G8, ITT CVC5-9, Decca Bradford series 10 & 30

£8.35 TRADE

£9.50 RETAIL

p&p 70p each item

WINDINGS p. & p. 50p each item

Bush colour. (Hybrid quadrupler version)

£6.25 p&p 70p each item

Decca CTV19/25 (non-tripler version)

Primary £6.25

EHT £7.20

Philips G6 (dual & single standard)

Primary £6.25

(EHT winding on exchange basis only)

EHT £7.20

Pye 691, 693 & 697 (please state which)

Primary £4.60

EHT £3.10

EMO 90 degree

Primary £6.25

PRICES INCLUDE 15% VAT

S.A.E. all enquiries

All lopts and windings are new and guaranteed for 6 months.

PAPWORTH TRANSFORMERS

80 Merton High Street
London SW19 1BE

Barclaycard and
Access welcome



01-540 3955

TELEVISION ELECTRONIC DISTRIBUTION (SPARES) LTD.

412a Hanworth Road, Hounslow, Middlesex
Telephone: 01-572 4668

PANEL REPAIR/EXCHANGE SERVICE TRADE ONLY

BERRYVISION 510

EMO

**THORN 2000 Series, 3000/3500 Series,
8000/8500/8800/9000 Series.**

GEC Solid State 2110 Series.

PHILIPS G8 G9

RBM A802/823 AV (Ultrasonic)

DECCA Solid State 80 Series/Hybrid 30 Series.

GRUNDIG 5010/6010 GB

PYE 691, 697, 713, 723, 731

SONY 1800UB

**TRADE REPAIRS ON ALL SONY COLOUR T.V.'s
VERY COMPETITIVE PRICES.**

**3 MONTHS WARRANTY ON PANELS FROM
DATE OF OUR INVOICE.**

DISCOUNT FOR BULK PANEL ORDERS.

CATALOGUE AVAILABLE ON REQUEST.

T.V. REPLACEMENT CAPACITORS PLASTIC FILM CAPACITORS

250v AC Mains filter type. To meet the requirements of BS 2135 (Class X suppression applications) Life tested at 375v AC at 85 deg. C.

0.047mfd	35p	0.1mfd	40p
0.33mfd	55p	1.0mfd (three wire type)	60p

1000v. DC. General purpose type. Metallised polypropylene, encapsulated. Axial leads.

0.047mfd	27p	0.1mfd	34p
0.22mfd	46p	0.47mfd	62p

2kV Peak Flyback capacitors. Encapsulated, with axial leads.

1500pF	40p	4700pF	40p
5200pF	40p	8200pF	50p

ELECTROLYTIC CAPACITORS

Solder Tag and P.C. Type

600mfd 250v.	G8	150p
600mfd 300v.	G8	182p
600mfd 300v.	GEC	175p
600mfd 300v.	A823	162p
600mfd 300v.	Z179	160p
600mfd 300v.	G9	160p
400mfd 350v.	8000	154p
470mfd 250v.	G11	132p
800mfd 250v.	G9	167p
200 - 300mfd 350v.	691	205p
300 - 300mfd 300v.	A640	190p
400 - 400mfd 350v.	Decca	260p
150 - 150 - 100mfd 300v.	1500	160p
175 - 100 - 100mfd 400/350v.	3500	204p
200 - 400 - 50mfd 325v.	A816	230p
200 - 200 - 150 - 50mfd 300v.	GEC	200p
300 - 300 - 100 - 32 - 32mfd 300v.	Z146	243p
300 - 300 - 300 - 150 - 100 - 50mfd 325v.	GEC	300p
1000mfd 63v.	3500	62p
2200mfd 63v.	G9	95p
1250mfd 50v.	169	60p
4700mfd 25v.	1590	73p
1000 - 1000mfd 40v.	Pye	82p
1000 - 2000mfd 35v.	GEC	97p
2500 - 2500mfd 30v. (PC)	A823	107p

The above prices are for single items. Quantity discounts allowed.
CASH WITH ORDER PLEASE!

All the above prices include postage and VAT at 15%.

P.E. WHITE 22 York Road, Camberley,
Surrey. GU 15 4HR.

We're giving away

**Trade
secrets**

**FOR EX-RENTAL COLOUR
AND MONO TELEVISION**

**West Midlands T.V.
Trade Sales Ltd.**

021-444-6464

92 HIGH STREET
KINGS HEATH
BIRMINGHAM B14 7JZ

★ **NOW OPEN** ★
**New Warehouse at
37-39, Jamaica St.
Bristol.**
0272-48266

Why not call in and see us. . .
A relaxed friendly atmosphere, together with a choice of hundreds of sets at low, low prices. Colour from £15. Mono from £2. Also stands, spares, etc. Send an S.A.E. or phone, for our current price lists and area map showing how to find us. Export enquiries welcome.

N.G.T. COLOUR TUBES

First Independent Rebuilder with

B.S.I. CERTIFICATION

(Certificate No. 004)

12 month's guarantee: 4 year option

Tubes are processed using high temperature pumping schedules giving high definition and long life. They are then fitted with an implosion safety system approved by the British Standards Institution.

N.G.T. ELECTRONICS LTD.,

120, SELHURST ROAD., LONDON S.E.25

Phone: 01-771 3535.

20 years experience in television tube rebuilding.

EX RENTAL COLOUR TV's. THE BEST DEAL IN LONDON

OVER 2,000 in STOCK. MANY WORKING.

THORN BUSH DECCA PYE GEC PHILIPS KORTING GRUNDIG

Delivery arranged ★ Working sets available ★ Complete lorry loads available

★ Excellent stocks of Mono ★ Export our speciality.

Low, Low prices for genuine trade buyers, call and see for yourself, we would like to meet you
or phone 01-997 8833/2298

Colin Butler TV Wholesale, Servier House, Horsenden Lane South, Perivale, Middx.

(New industrial estate behind Perivale underground station)

PHILIP H. BEARMAN (VALVE SPECIALISTS)

SUPPLIERS TO H.M. GOVT. Etc.
NEW valves by Mullard, Mazda, etc, we cannot supply these makes with warranty. (See our lists for explanation). Kindly verify current prices.

"QUALITY" BRANDED VALVES ONLY CARRY THE 90 DAY GUARANTEE, SEE OUR LISTS.

IMMEDIATE POSTAL DESPATCH	LISTS S.A.E.	QUOTED PRICES INCLUDING 6% ALLOWANCE IN LIEU OF GUARANTEE ON BVA VALVES
DY51 85p	EZ40 & 41 60p	PCF802 £1.05
DY86/7 78p	GY501 £1.75	PL36 £1.30
DY802 85p	PC86 95p	PL83/4 60p
ECC81 78p	PC88 95p	U25 60p
ECC82/3 78p	PC97 80p	U26 60p
ECL80 73p	PC90 80p	6F23 60p
EF80/85 70p	PC99 75p	PL508 1.75
EF183 85p	PCC89 75p	6F28 £1.05
EF184 85p	PCC89 75p	20P4 60p
EH90 60p	PCC189 75p	30P4/19 £1.30
EY51 85p	PCF80 95p	30C15/17 75p
EY86/7 50p	PCF86 95p	30FL1 } £1.26
	PCF200 £1.75	30L15 75p
	PCF801 90p	30L17 75p
		resistor.

HUNDREDS OF OTHER TYPES AVAILABLE, VAST STOCKS.

See separate Component, CRT and Transistor List. Many obsolete types available. I.R.C. or S.A.E. or International Reply Coupon with enquiries please.

Overseas Post & Cost. U.K. Post 18p per valve under £25.00 (max. 80p) but 2p extra larger valves/ADDITIONAL VALVES 7p)

6 POTTERS RD., NEW BARNET
Herts. Tel: 01/449-1934/5 (Tel. recording service 449/1934 only) Any excess paid will be refunded.

Note: Actual makers of NEW MICRO ALL GROUPS UHF AERIAL (625) - 3" x 1 1/4", amazing results. £3.70 all incl. SAE DETAILED LEAFLET (Tech reports 50p extra)

VIEW WELL WITH WELLVIEW TV TUBE REBUILDS

Exchange Mono

	our price	+VAT 15%	total price
CME 1601-1602	£9.30	£1.39	£10.69
A44/120WR	£9.30	£1.39	£10.69
A50/120WR	£9.30	£1.39	£10.69
AW59/23W	£11.00	£1.65	£12.65
A61/120WR	£11.00	£1.65	£12.65

NEW MONO TUBES
20" = £15.80 inc. VAT 24" = £17.20 inc. VAT

Exchange Colour

	our price	+VAT 15%	total price
A44/270X-271X	£27.00	£4.05	£31.05
A47/342X-343X	£27.00	£4.05	£31.05
A49/120X	£27.00	£4.05	£31.05
A51/110X	£27.00	£4.05	£31.05
A55/14X	£32.00	£4.80	£36.80
A56/120X	£32.00	£4.80	£36.80
A63/120X	£36.00	£5.40	£41.40
A66/120X	£36.00	£5.40	£41.40
A67/120X	£36.00	£5.40	£41.40
A67/200X	£36.00	£5.40	£41.40

18 month full guarantee (Established ten years).

Send cash or cheque together with old tube with your order.
Carriage=£4.50 including VAT
ALSO YOUR VALVE SUPPLIER NEW AND BOXED (inclusive of VAT)

SOUTHERN VALVE COMPANY

Second Floor, 8 Potters Road, New Barnet, Herts. Telephone 01-440/8641 Noon to 2 pm excepted

"QUALITY" BRANDED VALVES GUARANTEED 3 MONTHS. BVA ETC. ARE OFTEN AVAILABLE WITHOUT ANY GUARANTEE. (SEE OUR LISTS). QUOTES ON REQUEST.

ALL NEW & BOXED.	PROBABLY THE BEST VALUE ANYWHERE	NOTE:
DY86-7 62p	EF86 60p	We regret some increases, correct only at time of going to press.
DY802 62p	EF89 85p	
ECC81 66p	EF183 60p	
ECC82 68p	EF184 60p	
ECC83 68p	EH140 50p	
ECC85 65p	EL41 £1.20	
ECH81 62p	EL509 £2.25	
ECH84 95p	EM84/87 £1.00	
ECL80 55p	EY86/7 50p	
ECL82 90p	EY500A £1.75	
ECL86 80p	EZ80 55p	
EF80 43p	EZ81 55p	
EF85 47p	GY501	

One valve post 17p, each extra valve 6p. MAX £1.00 LISTS & ENQUIRIES S.A.E. PLEASE! (OR INTERNATIONAL REPLY COUPON)

Large valves 2p extra. VAT INCLUDED IN PRICES NO CALLERS AGENTS NEW UHF "MICRO" AERIAL Only 3" x 1 1/4" DIAM. BAND. PRICE £3.70 INCL. POST & VAT. (625 UHF).

MAIL ORDER ONLY
MINIMUM ORDER £1.00
Some leading makes available. (A.I. invoices issued on request.)

We offer same day postal despatch

CWO ONLY. No C.O.D. NO CREDIT CARDS
Post free over £25.00.
£6 to £25 - £1.00 (max.) (insured parcel £1)

Items in stock at time of going to press but subject to possible market fluctuations if unavoidable.

WELLVIEW TUBES LTD.,
Unit 7, KING ROAD,
CHARFLEET INDUSTRIAL ESTATE,
CANVEY ISLAND,
ESSEX
TELEPHONE CANVEY ISLAND 85372

EMO - EUROSonic - GRUNDIG - TELETON + ALL BRITISH MAKES ETC., ETC. ● ALL SPARES READILY AVAILABLE ● REBUILD TUBES CREDIT AVAILABLE - TRADE ONLY

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc.
NEW - COMBI LOPTX NOW AVAILABLE.

YOU CAN BE 95% SURE WE CAN SUPPLY ANY TV COMPONENT BY RETURN IF YOU NEED SPARES FAST - RING NOW!

ACCESS AND BARCLAYCARD ACCEPTED. S.A.E. FOR FREE SERVICE CATALOGUE.

TELE-PORT (WTON) THE TELECENTRE, WORCESTER ST., WOLVERHAMPTON (0902) 773121

COLOUR TUBES STANDARD TUBES METAL BAND TUBES

Rebuilt with new Electron Guns to British Standard 415/1972. Clause 18.2.

PHILIP H. BEARMAN

6 POTTERS ROAD, NEW BARNET, HERTS. Tel: 01-449 1934/5, (Answering machine 1934 only) PHONE FOR SHOP HOURS.

NEW MONO TUBES. Usually 2 Year Guarantee. Tested prior sale.

BUY NOW - PRICES MUST INCREASE SHORTLY.

A31/410W Mullard	£18.90	CARRIAGE £2.75 (Mainland); £3.50 colour; £1.75 for Extra Short Sea Journey. Eire Extra.
A31/120 - CME1220	A31/300*	MULLARD A59/15 (AW59/91) BRAND NEW £11.55.
A34/100 - CME1420	£21.00	FEW MULLARD A47-26WR £18.00. All Mullard 2 year (NOT 1 year) guarantee. (UNREPEATABLE AT THESE PRICES!)
A38/160 - CME1520	£20.00*	MULLARD A31/5/0W £18.90 & A34/510W £21.00!
A50/120WR - CME2013	£18.90*	NOTE - JUST ARRIVED - NEW MAZDA A47-13W £15.00 (limited stocks)
A61/120WR - CME2413	£22.10*	

Note* less £1 for 1 year guarantee.

A31/510W £19; A34/510W £20.50

COLOUR TUBES. Prices on application. SAE all enquiries please!
Price correct at time of going to press BUT SUBJECT TO ALTERATION WITHOUT NOTICE
Telephone enquiries welcome. New 19" £60. Up to £10 old CRT (Colour)
(Not 19" or 25" please)

SUFFOLK TUBES LIMITED

214, PURLEY WAY
CROYDON, SURREY
01-686 7951

Britain's Largest Independent TV Tube Rebuilder



SETS & COMPONENTS

MAINS DROPPERS AND CAN CONDENSERS

Philips G8 47Ω	43p
Philips G8 2-2-68Ω	63p
Philips 210 118-148-LoopΩ	63p
Philips 210 30-125-2K85Ω	74p
Philips GT23 6-124-84Ω	74p
Thorn 3500	74p
Thorn 1500 350-20-148-1500-317Ω	90p
Thorn 1400	80p
Thorn 8000 56-1K-47-12Ω	90p
Pye 725 27-56Ω	63p
R.B.M. TV161 250-14-156Ω	70p
GEC 2010 8-15-17-70-63-188Ω	90p
2010 Covers 2013 2014 2017 & Sobell 1010 10A 13 & 1014	
Bush TV165 166-171-175-176-178	70p
Murphy V1910-1913-1914-2014-2310-2311-2312 2314	70p
Bush A823 68-56Ω	90p
TV Condensers: - 200 + 200 ± 100 mfd 300V	45p each
150-100-100-100-150M 325V	£2.00
150-150-100M 300V	£1.60
175M 400V 100-100M 350V	£2.05
400-400M 350V	£2.65
All 2500-2500m 30V	80p
2500-2500m 63V	£1.45
Can 4700m 25V	85p
1500m 70V	80p
Cond 2200m 40V	65p
1000m 63V	63p
BDX32	£1.98
PL802T Special	£3.50
100-300-100-10m 300V	£1.70
Post Free, Cash with order, VAT paid.	

Durham Supplies

367 Kensington Street, Bradford 8, West Yorkshire

DXTV EQUIPMENT of all kinds supplied. Overseas enquiries welcome. Hugh Cocks, Bre Cottage, Staplecross, Robertsbridge, E. Sussex. Tel. 058083-317.

URGENT TRADE NOTICE

Large quantities of good quality mono and colour TV receivers for sale, at competitive prices.

WHY not come to us where your custom will be welcomed and appreciated.

WE supply receivers to all parts of the UK and to EIRE. All export enquiries welcomed.

TV WHOLESALE SUPPLIES

35 Shipston Road, Stratford-on-Avon.
TEL: 0789 4424

ELECTRONIC COMPONENTS. Send S.A.E. For List. Special Offers monthly. Radnor Supplies, 23 Arbury Road, Nuneaton, Wark's.

MULLARD MIXED CAPACITOR BARGAIN PACKS

150-C2801/1 Capacitors, values from .01 F to 1.5 F, 250V/W. Very good mixed selection.

PRICE £2.00 Inclusive.

VELCO ELECTRONICS

9 Mandeville Terrace, Hawshaw, Via Bury, Lancs.

SMALL ADS

The prepaid rate for classified advertisements is 21p per word (minimum 12 words), box number 60p extra. Semi-display setting £4.00 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

Publishers Announcement

Due to increases which may have taken effect since this issue went to press, we strongly advise readers to check with advertisers the prices shown, and availability of goods, before purchasing.

TELEVISIONS

LARGE STOCK OF COLOUR & MONO TV'S MOST MAKES AND SCREEN SIZES, WORKERS & NON WORKERS, SUITABLE SALE OR RE-RENT TESTING FACILITIES AVAILABLE, QUANTITY DISCOUNTS.

GENERAL FACTORS

Union Street

(off St. Sepulchre Gate West Doncaster)

0302 - 49583 & 68416

LOOK!

THORN 3000/3500 TRIPLERS

High Quality Silicon Replacement Units
One Year Guarantee: Same Day Despatch
ONLY £3-95 inc. P.P. Add 59p V.A.T.

Quotes for larger quantities on request.

WING ELECTRONICS
13 Middle Road, Harrow HM, Middx.

ANOTHER FIRST from

LED Co

THE PANEL PEOPLE
Specialists in the design and manufacture of TV panels

Module 915: A state of the art direct replacement for the IF Filter/Gain Module used in the Philips 570 & Pye 713-725-735 and similar chassis. £11.45

Solid State CDA Panel for
Pye Hybrid TV £20.50
Solid State PL802 £2.45
LP 1162 Equivalent £6.60

As featured in June issue of this magazine.

VAT included in price. Carriage free by 1st class post. C.W.O.

Send for details of these tried and proven components as used by the major companies.

LED Co. 189a Livingstone Road,
Thornton Heath, Surrey CR4 8JZ
Tel. 01-653 7575

S/S Colour £30, Mono Push Button £3. Plus VAT.
Phone Southend 559895. Any time.

QUALITY REBUILT TUBES HIGH TEMPERATURE PUMPING Colour (2 year guarantee) from £32 Mono (including thin necks) from £12

Send or phone for full list and terms
OPEN MONDAY-SATURDAY

WELTECH PICTURE TUBES

5 Masons Avenue, Wealdstone, Harrow, Middx.
01-427 5063.

VALVE LIST

ALL VALVES FULLY TESTED

Five valves or over postage paid
Under five valves postage 6p each

DY86/87	15p	PC900	8p	PCL85/805	20p
EB91	12p	PCC84	8p	PL36	20p
ECC82	10p	PCC85	20p	PL504	25p
ECL80	8p	PCC89	8p	PY32/33	15p
EF80	8p	PCC189	8p	PY81/800	15p
EF85	8p	PCC805	15p	PY801	20p
EF183	10p	PCF80	8p	U191	15p
EF184	10p	PCF86	15p	6F23	15p
EH90	13p	PCF805	20p	6/30L2	18p
EY86/87	13p	PCL82	15p	30F5	18p
PC86	15p	PCL83	15p	30FL1	20p
PC88	15p	PCL84	15p	30PL14	15p

AND MANY MORE AVAILABLE

S. W. ELECTRONICS

114 Burnley Road, Rawtenstall, Rossendale, Lancs.

DX-TV AERIALS & EQUIPMENT

serials manufactured to your own designs

suppliers of mats, lashing & cables

Premier vpx22 wide band aerial uhl	£29.00
Antiferance xg21 wide band aerial uhl	£38.00
Wolsey colour ring wide band aerial uhl	£13.00
FX16 high gain beam for stereo aerial	£28.00
Euro logarithmic 14element wide band vhf band III	£18.00
Stolle 2060 rotor (uses 3 core cables)	£42.00
Wolsey supanova amp & p/unit w/b uhl	£38.00
Wolsey supanova amp & p/unit w/b vhf	£20.00
Wolsey s/nova high gain amp & p/u w/b uhl	£82.00
Antiferance u12 vhf/uhf diplexer	£2.80
Labgear 8030/8040 wide band amplifiers	£22.00
Labgear 8001 power unit (for aovs)	£11.80

All prices include p&p etc. cash with order please.

For price quotations on other items a.s.a. to:

AERIAL CONTRACTORS (SOUTHERN)

28 Cuffield Road, Shoeburyness, Essex.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

COLOUR PANEL EXCHANGE SERVICE

BRC 3000 - 3500 8000 - 8500
Philips G8 and GEC 2110 series.

Free delivery in London area on Exchange Panels. Large stock of BRC 3500 series spares. New and S/H BRC Panels for sale. Immediate exchange on repairable panels.

Catalogue available on request.

KAY JAY TV SERVICE

34, Clauson Avenue, Northolt. Phone 884 0360.

REBUILT CATHODE RAY TUBES IN

S. WALES

All tubes are now guaranteed for 2 years	Exchange Price	V.A.T. @ 15%
A44 270X-A44 271X	£30.00	£4.50
A47 342X-A47 343X	£30.00	£4.50
A49 120X-A49 192X	£30.00	£4.50
A51 110X-A51 220X	£30.00	£4.50
A55 14X	£33.00	£4.95
A56 120X-A56 140X	£33.00	£4.95
A63 120X-A63 200X	£36.00	£5.40
A66 120X-A66 140X	£36.00	£5.40
A67 120X-A67 150X	£36.00	£5.40

20AX and P.I.L tube prices are available on application.

For further details contact: **C.R.T. Services**
Tel. Llanwern (0633) 412 112

TV TUBE REBUILDING

Faircrest Engineering Ltd., manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

Willis Road, Croydon CR0 2XX
Tel: 01-689 8741 01-684 1422/3

P. V. TUBES

12 months guarantee

Colour tubes supplied on a 'glass for glass' basis
Callers ring to arrange to bring your glass for on the spot exchange from our stocks
Lancashire/W. Yorks. deliveries by arrangement
Carriage costs per tube: Portables £1-80; Mono £3-50; Colour £4-50; incl. VAT

REBUILT MONO	REBUILT COLOUR	NEW MONO
A28-14W 11" (Pencil) £14	17" 18" 19" 20" £28	
A31-410W 12" £14	22" £30	
A31-120W 12" (Pencil) £14	25" 26" £34	
A31-18W 12" £14	26" 110" £36	
A34-100W 14" (Pencil) £14		
A38-160W 15" (Pencil) £14	A31/510 12" £17	
A44-120WR 17" £14	Replaces A31/120 Mullard 2 year warranty	
A59-23W 23" £14	A31/410	
A50-120WR 20" £11		
A61-120WR 24" £11	A34/510 14" £18-50	
	Replaces A34/100	
	A50/120WR 20" £12	
	A61/120WR 24" £13-50	

Glass is required for portable rebuilt mono please.
All tube prices subject to 15% VAT

NEW MULLARD COLOUREX TUBES ALL SIZES IN STOCK SEND S.A.E. FOR PRICE LIST NEW VALVES

Type	Price	Valve prices include 15% VAT	Type	Price	
30FL1/2	£1.28	Type	Price	PL36	82p
DY802	89p	EF184	83p	PC885	82p
DY86/7	80p	EH90	77p	PC889	87p
ECC81	53p	EL34	£1.84	PCC189	87p
ECC82/3	83p	EL84	52p	PCF80	83p
ECC85	51p	EL509	£2.56	PCF86	87p
ECC88	74p	EY86/87	52p	PCF200	£1.83
ECC80	87p	EY500A	£1.53	PCF801	81p
ECF82	87p	EZ80	51p	PCF802	83p
EC81	56p	EZ81	51p	PCF805	87p
EC84	£1.02	GY501	£1.43	PCF806	71p
ECL80	82p	GZ34	£1.79	PCF808	£1.74
ECL82	82p	KT66	£3.58	PCH200	£1.23
ECL86	77p	PC86	77p	PCL82	75p
ECF86	83p	PC88	77p	PCL84	83p
EF80	41p	PC92	85p	PCL805/85	87p
EF85	41p	PC97	77p	PCL86	87p
EF86	82p	PC900	77p	PD500	£3.37
EF183	83p	PCC84	31p	PFL200	£1.28
				U191	48p

ALL VALVES ARE UNUSED - BOXED - AND GUARANTEED

Post & Packing charges 14p for 1 valve - 7p for each
Additional valve - 2p extra for large valves - max. 80p.
Post free orders over £20 - any parcel insured extra 10p.

P. V. TUBES Regd. Office
38A Water Street, Accrington, Lancashire. BB5 6PX
Tel. (0254) 38521 and answering service.
V.A.T. No. 291-1937-45.

COLOUR/MONO Televisions available to the Trade.
Large stocks at good prices. Phone Solway TV
Trading Carlisle 0228 38307. Currock Works,
Currock Road, Carlisle.

COLOUR TV's

Many working for disposal, trade only.
All sizes and makes available.
Mono sets also available.

Incertone (London)

24 Dames Road, Forest Gate,
London E7. Tel: 01-555 5569

Incertone (Bristol)

28 St. Thomas St., Bristol 1.
Tel: 0272 211179

LLOYD ELECTRONICS

63 North Parade, Grantham,
Lincolnshire

PL802/T Top Quality Solid State Valve @
£2.50 each.
Solid State C.D.A. Panel for 'Pye' 203/205
series @ £19 each.
I.F. Gain module for 'Pye' 713/731-series @
£9.50 each.
Motor speed control module for 'Hoover'
washing machines. Types 3234/5/43 D.C. @
£9.50 each.

VAT & P/P included
QUANTITY DISCOUNTS

RE-BUILT COLOUR TUBES

19" £29.50 MONO 20" £30.50
22" £32.50 20" 24" 25" £34.50
26" £38.50 £16

One Year Guarantee.

MATRIX TV LTD.,

112 Essex Road, London N1. Tel: 226 1111

TELEVISION AERIALS

The full range of quality BASIC aerials, amplifiers, lashing kits, cables, masts, rotators and accessories can be supplied at extremely competitive prices, normally from stock. Representative examples are shown. For quotations on specific items, or general and technical application queries, please write enclosing S.A.E. with all enquiries. Comprehensive price lists on request.

VORTA DX 4/4 UHF Wideband Aerial (style of the 'Colour King')	£13.30
WOLSEY Nova High Gain (19dB) UHF Wideband Amplifier	£13.77
ANTIFERRENC MH473 High Gain Wideband 1/111 DX Aerial	£26.70
VORTA 14 element Wideband Band III Aerial	£21.88
CHANNELMASTER Heavy Duty Rotor, inc. Control Box	£54.87

All prices include VAT & post & packing

The proprietor **Roger Bunney** and his associate **David Martin** will be happy to advise on specific installations and allied problems, drawing on their in depth knowledge of reception engineering. A mains powered version of the single channel amplifier (JULY Television) is now available to order at £18.80 inclusive of VAT post and packing. Send S.A.E. for details.
BASIC Aerialite, Antiferrence, Jaybeam, Maxview, Wolsey, Premier Industries.

SOUTH WEST AERIAL SYSTEMS
10 Old Boundary Road, Shaftesbury, Dorset. Tel. (0747) 4370

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

COLOUR TUBES

Rebuilt with new electron gun, to British Standard.
High temperature pumping.

Here is what you pay.

17-18-19 inch.....	£29.00
20 inch.....	£30.00
22 inch.....	£32.00
25 inch.....	£34.00
26 inch.....	£38.00

Guarantee 2 years.

Exchange basis.

Prices negotiable for contracts.

Old Colour tubes purchased.

Carriage £5-00.

TELESTAR TUBES

575c Moseley Road, Birmingham B12 9BS.
Tel: 021-440 5712.

20 AX & P.I.L. TUBE

Colour Tubes.....	from £25
20 AX all sizes.....	from £25
Toshiba P.I.L. All Sizes.....	from £25
S/S COLOUR SETS.....	from £60
S/S & D/S MONO.....	from £5

RING: JEFFRIES 01-845 2036

TELEVISIONS to the Trade. Large quantities of Mono from £2.00; Square Screen from £6.00. Colour T.V.s Working from £65. R.B.M. GEC, Pye, Thorn etc. Phone Scarborough 0723-68087-65451. Scarborough T.V. Trading, Ridings House, Depot Lane, Seamer Road, (A64) Scarborough.

TELECARE T.V. DISTRIBUTION LTD. BRISTOL AND NORTHERN IRELAND

Due to a New Policy in purchasing we are able to OFFER most makes of Colour & Mono at Lower Prices than ever before.

We can supply any quantity, nothing too big or too small. Trade only.

TELECARE BRISTOL

Unit 3 Whitby Road,
Brislington,
Bristol.
Phone 0272 712569

NORTHERN IRELAND

Bellanaleck
Co' Fermanagh,
Northern Ireland.
Phone Florencecourt 388

PLEASE
MENTION

TELEVISION

WHEN
REPLYING TO
ADVERTISEMENTS

SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS,
RECORD PLAYERS, TAPE RECORDERS, ETC.

SERVICE SHEETS £1.00 PLUS S.A.E. SERVICE MANUALS ON REQUEST.

BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

TVT '78 TRANSISTOR EQUIVALENT & DATA BOOK. (A TO Z). 272 Pages	£2.75
TVT '78 TRANSISTOR EQUIVALENT & DATA BOOK. (2N. 2S. ETC.). 392 Pages	£3.80
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 1	£7.20
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 2	£7.20
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 3	£8.60
COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition	£7.30
COLOUR TELEVISION THEORY by G. H. Hutson	£6.80
LONG DISTANCE TV RECEPTION FOR THE ENTHUSIAST by R. Bunney	£1.70
COLOUR TV WITH REFERENCE TO THE PAL SYSTEM by G. N. Patchett	£6.20
VIDEOTAPE RECORDING: THEORY AND PRACTICE by J. F. Robinson 2nd Edition	£9.70
TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition	£6.10
BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition	£2.65
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition	£2.65
CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett	£4.00
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition	£5.35
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. Revised Edition	£5.95

(SEND LARGE S.A.E. FOR FREE BOOK LISTS)

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.
FROM 1965-66 EDITION UP TO DATE. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 20p POSTAGE PER COPY.
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, ELECTRONICS TODAY, ELEKTOR

BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. (HALF DAY WEDNESDAY) PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

LARGE SUPPLIERS OF SERVICE SHEETS AND COLOUR MANUALS

TV Mono, Radios, Tuners, Tape Recorders, Record Players, Transistors, Stereograms, all at 75p each + S.A.E.,
except Colour TV and Car Radios.

State if Circuit will do, if sheets are not in stock. All TV Sheets are full length 24 x 12, not in Bits & Pieces. All other Data full lengths.
Free Fault Finding Chart or TV Catalogue with order. Crossed PO's Returned if Sheets Not in Stock.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882. MAIL ORDER

G.T. THE TECHNICAL INFORMATION SERVICE 76 CHURCH STREET, LARKHALL, LANARKS ML9 1HE.

Over 200 different colour T.V. service manuals in stock.
1000's of other manuals in stock for immediate delivery.

S.A.E. brings quotations, newsletter,
bargains, details these and other T.V. offers
by return. Any service sheet £1 + large s.a.e.
by return.

FREE £4 OFF VOUCHERS
send very large s.a.e. and £2 for our
2 GIANT SERVICE SHEETS &
MANUALS CATALOGUES

NEW PUBLICATIONS FROM T.V. TECHNIC . . . plus extra manuals.

Complete British Colour T.V. Repair System **£52** (£65 abroad).
(3 Repair Manuals & 3 Giant Circuit Diagram/layout collections in luxury
binders).
Complete Mono T.V. Repair System **£42** (£53 abroad).
(4 Repair Manuals & 2 Giant Circuit Diagram/layout collections in luxury
binders).

SERVICE SHEETS from 50p and S.A.E. Catalogue
25p and S.A.E. Hamilton Radio, St. Leonards,
Sussex.

SERVICE SHEETS, Radio, TV, etc., 10,000 models.
Catalogue 24p plus SAE with orders-enquiries.
Telray, 154 Brook Street, Preston, PR1 7HP.

LADDERS

ALUMINIUM Roof Crawlers, 12ft. - 24ft.
Aluminium ext. up to 62½ft. Leaflets. Ladder Centre
(TEL3) Halesfield (1) Telford. Tel: 586644. Callers
Welcome.

BOOKS & PUBLICATIONS

FULL REPAIR data any named T.V. £5.30, with cir-
cuits, layouts, etc. £7. (AUST) 76 Church Street,
Larkhall, Lanarks ML9 1HE.

FOR SALE

NEW BACK ISSUES of 'Television' available 75p
each post free. Open P.O./Cheque returned if not in
stock - BELL'S TELEVISION SERVICES, 190
Kings Road, Harrogate, N. Yorkshire. Tel: (0423)
55885.

NEW 22" Colour Tube. Complete Set "Television"
Receiver Components. Cabinet. Cross Hatch
Generator. £20. 0283 63767.

TELETEXT "Television" type with new Signal Panel
£110 o.n.o. also "Wireless World" Decoder (Full
Specification) £200 o.n.o. Tel: Gt. Ayton 3060.


OSCILLOSCOPE 4D10 Scopex Dual trace as new
£120 o.n.o. 36 Broadacre, Killay, Swansea, W/Glam.
0792299268.

WANTED

NEW VALVES and CRT's required, PCL805,
PL504, PL509, PY500A etc. Cash waiting. Bearman,
6/8 Potters Road, New Barnet, Herts. Tel:
01-449 1934/5.

PRE-WAR or early post-war TV Sets or parts in any
condition required by enthusiast. Write Box 150.

MISCELLANEOUS

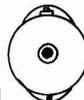BELLS AND SIRENS		
	CARTERS SIREN £5.95	
	INDUSTRIAL SIX INCH	
	BELL £8.95	
	PRICES INCLUSIVE.	
	SEND CHEQUE. P.O. to:	
	CWAS ALARM	
	11 Denbrook Walk.	
8 to 12v D.C.	Bradford BD4 0QS	12v D.C.
SAE for full price list of Professional Burglar Alarm Equipment.		

C.T.V. Panels Ect lists S.A.E. No Callers. Sole, 37
Stanley St., Ormskirk, Lancs. L39 2DH.

VIDEORECORDER SERVICE and Technical consultancy - B & B Electronics, Newark 76895. Call Steve Beeching.

3000-3500 TEST SET

This unit enables the 3000-3500 Power supply and Line T.B. boards to be run up for testing and fault finding entirely independent of the T/V set. The informative Led indicators show immediate presence or absence of the 6.3v 30v. and 58-65v. lines using the integral line pulse generator, or simply plug in the Line T.B. and check up to EHT pulse output. Has Neon warning of connection to mains and overload cut-out. Highly praised and recommended by Thoms own Technical Service Dept. Measures 4 1/2" x 4" x 2" in black case with gold lettering. £12.50 plus 50p post & packing. CWO.

J. Baker & Co.
1, Old Shoreham Road, Southwick
Sussex. BN4 4RD Tel. Brighton 593315

EDUCATIONAL

TELEVISION & VIDEO SYSTEMS SERVICING

15 MONTHS full-time Diploma course to include a high percentage of practical work.

- ELECTRONIC PRINCIPLES
- MONO & COLOUR TELEVISION
- CLOSED CIRCUIT TELEVISION
- VIDEO CASSETTE RECORDING
- DIGITAL TECHNIQUES
- TELETEXT & TV GAMES

Shortened courses for applicants with suitable electronics background.

Next session starts January 7th.

(Also available 2 1/2 year course in Marine Electronics & Radar for employment as ships Radio Officer.)

Prospectus from:

LONDON ELECTRONICS COLLEGE

Dept; TT11, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

SITUATIONS VACANT

TELEVISION SERVICE ENGINEER

We have a vacancy for an experienced Television Service Engineer to join our enthusiastic team in Guildford. A five day week with two day weekend is worked. An estate car will be available and, accordingly, a valid driving licence is essential. A self contained modern flat could be made available if required. Our Service Department is well and fully equipped, on the ground floor, and working conditions are excellent.

Please apply to:

MERROW SOUND LTD.,
21-22 Tunsgate, Guildford.

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser both prices and availability of goods before ordering from non-current issues of the magazine.

STANDERD T.V. TUBE

HIGH QUALITY COLOUR AND MONO-CHROME REPLACEMENT TUBES AT COMPETITIVE PRICES.

- ★ Complete New Gun fitted to every Tube.
- ★ Two year Guarantee
- ★ Every Tube Electrically Tested.
- ★ Every Tube Picture Tested.
- ★ Supplier to Major Rental Companies.

19", 20" £22
22" £25
25", 26" £28

**11-29, Fashion Street,
London E1**

**Ring Standard T.V. Tube Reguner
Tel. 01-247 3097**

TELEVISION TUBE SHOP

NEW TUBES AT CUT PRICES

EUROPEAN TYPE Nos.

	Price £	VAT £
A28-14W	18.95	121%
A31-19W/20W	19.95	2.37
A31-120W/300W	17.95	2.49
A31-410W/510W	17.95	2.24
A34-100W	18.50	2.24
A38-160W	17.50	2.31
A44-120W	18.75	2.19
A50-120W	17.95	2.34
A59-23W	18.95	2.24
A61-120W	18.95	2.37

U.S.A./JAP. TYPE Nos.

9AGP4	19.50	2.44
190AB4/C4	17.50	2.19
230ADB4	28.50	3.56
230DB4/CT468	24.00	3.00
240AB4A	17.95	2.24
CT507	17.95	2.24
CT512	27.50	3.44
310DGB4/DMB4	23.00	2.88
310EUB4	19.95	2.49
310EYB4	18.75	2.34
310FDB4	19.95	2.49
310FXB4	17.50	2.19
310GNB4A	23.50	2.94
310HCB4	23.50	2.94
340AB4	19.50	2.44
340AYB4	25.25	3.15
340Rb4/CB4	24.50	3.06
340AHB4	24.50	3.06

Some Rebuilt Japanese & European Types Available at £14.00 + VAT £1.75

COLOUR TUBES (New & Colourex)

12VARP22	62.50	7.81
330AB22	65.00	8.12
470FUB22B	85.00	10.62
A44-271X	65.00	8.12
A47-342X	69.50	8.89
A47-343X	69.50	8.89
A49-191X	59.50	7.44
A51-220X	64.00	8.00
A56-120X	69.50	8.89
A63-120X	69.50	8.89
A66-120X	75.00	9.37
A66-140X/410X	70.50	8.81
A67-120X	82.00	10.25
A67-140X/200X	69.50	8.89
A67-150X	75.00	9.37

ALL TUBES TESTED BEFORE DESPATCH & GUARANTEED FOR 12 MONTHS! 4 YEAR GUARANTEES AVAILABLE ON MOST TYPES

CARRIAGE

Mono £3.00 Colour £4.00

Mainland only. Overseas Rates on Application.

TELEVISION TUBE SHOP LTD.
52 BATTERSEA BRIDGE RD.,
LONDON, SW11.
Tel. 228 6859/223 5088

ELECTRONIC MAILORDER LTD.

VALVE BARGAINS

Any 5-80p, 10-£1.50, 50-£6.00 Your choice from the list below.

ECC82, EF80, EF183, EF184, EH90, PCF80, PCF802, PCL82, PCL84, PCL85, PCL805, PL504, PY81/800, PY88, 30PL14, 6F28, PFL200.

Colour Valves - PL508, PL509, PL519, PY500/A. All tested, 85p each.

Aerial Splitters: - 2 way, 75 OHMS, Inside Type, £2.50

AERIAL BOOSTERS

Aerial boosters can produce remarkable improvements on the picture and sound, in fringe or difficult areas.

B11 - For the stereo and standard VHF/FM radio.

B12 - For the older VHF television - Please state channel numbers.

B45 - For Mono or colour this covers the complete UHF Television band.

All boosters are complete with battery with Co-ax plugs & sockets. Next to the set fitting. Price £5.70 each.

STEREO HEADPHONES

Black - Freq. 30-18000HZ.
SAVE ££'s - PRICE £3.50

ALL PRICES INCLUDE VAT. P & P 30p PER ORDER. EXPORTS WELCOME AT COST

62 BRIDGE STREET, RAMSBOTTOM,
BURY, LANCS.
TEL: RAMS (070 682) 3036.

DISPLAY ELECTRONICS

COLOUR TUBES 2 YEAR GUARANTEE

Up to 19"	£29.50
20"	£31.50
22"	£33.50
25"	£35.50
26"	£37.50

The above prices are for standard 38mm Delta Gun Types. Prices on application for P.I.L. Tubes etc. Some types available without pre-supply of glass.

MONO TUBES

2 YEAR GUARANTEE

19"/20"	£11.00
23"/24"	£13.00

Carriage/Packing £3.00 on mainland.
Please add 15% VAT to all orders.

BIRMINGHAM AND DISTRICT DEALERS/ENGINEERS

NEWS FLASH

HIGH VACUUM
QUALITY
REBUILT TELEVISION
PICTURE TUBES

COMPETITIVE PRICES

CONTRACT TERMS
AVAILABLE

2 YEAR GUARANTEE

E.G.	
17" 18" 19"	£29.50 + VAT £4.43
20"	£32.50 + VAT £4.86
22"	£34.00 + VAT £5.10
25"	£37.00 + VAT £5.55
26"	£40.00 + VAT £6.00

PIL Tubes our speciality.
All Prices For Tubes available on a Sound "Glass for Glass" basis otherwise £20 surcharge

C.W.O. Carr./Ins. £6.50
"Old Glass Purchased"

TUBESURE LTD.

Unit 111, Middlemore Industrial Estate,
Middlemore Road, Smethwick,
West Midlands. Telephone: 021-558 7777.

CALLERS WELCOME

Late night Thursdays until 8pm
Saturdays until midday.

N.B. Customers intending to collect orders are requested to telephone in advance:— even popular types may be out of stock for short periods.

V.D.U./RADAR TUBES

We have supplied British and Foreign Airlines with rebuilt V.D.U. Tubes for several years and also have Radar Display Tubes operating on British Airfields.

Home and export enquiries for Radar Display Tubes manufactured from new (with phosphors to specification) are invited.

**WATERLOO ROAD,
UXBRIDGE,
MIDDLESEX**

Telephone: Uxbridge 55800

COLOUR T.V. SPARES

Most parts for Decca's stocked

LOPT

DECCA 10/30	£10.80
80/100	£10.20
Mono	£12.00
PHILIPS G8	£12.90
ITT 20/25/30	£11.90
BUSH A774	£15.00

TUNER CONTROL UNITS

DECCA	
4 Button	£7.90
6 Button	£8.90
7 Key	£14.50

Complete working
THORN 3000 models
£79 (callers only)

Ex-equip panels
for 3000 and BRADFORD
See our *NEW Catalogue*
for details.

Hundreds of correct
spares listed.
Send stamp for
free copy.

New 1590 or 1591 speakers £4.90.
Prices include 15% VAT

Package/Posting 30p per order but Transformers
and Panels 80p.

BOTTOMLEY'S TELEVISION

11 Leeds Road, Hipperholme,
HALIFAX (0422) 202979

Callers Phone first. Exit 26 M62

PLEASE
MENTION

TELEVISION

WHEN
REPLYING

TO
ADVERTISERS

BD253 £1.25	EHT S.Stick 18 or 20KW Triplers (ITT) £1.50 new	EHT Lead & Anode Cap 75p
3 amp 1½ Fuses 2p	3 amp Diodes approx. voltage 1200 7p each	Star Aerial Amps £4.00
Long wires	3500 6 push button units for Thorn 3500 Varicap tuning £1.00	Channel B or C 15p
300 Mixed Carbon Film Resistors	Varicap F.M. Tuner £2.00	2200/35 25p
5 of each type ¼ Watt 1R to 2 Meg - ITT £1.50	Tuning range 78.5 to 108MHz (I.F. Panel with circuit) £2.00	2000+2000/35 50p
Red & Green L.E.D.s mixed large and small 14 for £1.00	6 position 12.5K V/Resistor Unit for Varicap 50p	2500+2500/63V 25p
Convergence Panel for GEC 2040 11 pots 5 coils 2-Resistors E.T.C. New £1.50	Thorn Mains Lead & ON/OFF switch & Control Panel with Slider Pots 75p	4700/25 35p
(Reject Varicap Units)	TBA 120A 30p	4700/30 50p
ELC1042/ELC1043 50p	TBA 120B 30p	4700/40 10p
ELC2000 £1.00	TBA 120AS 30p	1250/50 6p
10 Watt LP1173 £1.00	TBA 120SB 30p	33/350 8p
IF LP1170 50p	TIP 161NPN 50p	100/63 8p
AM/FM T/Unit (Seconds) 50p		10/350 8p
AT1025/08 Blue Lateral Ass. 15p		47/50 5p
10 Watt Mullard Amps New £2.00	.01MFD 1000V 8p	DE Solder Pumps £6.00
BD 207 30p	.0047/500V 8p	.05/100 3p
TIP 31 or TIP 31A 20p	.0022 1500V 8p	4.7/50V 5p
TIP 2955 50p	.47 250 A/C 8p	4/350 5p
2N3583 250V/1A Output Transistor 40p	.47 1000V 35p	1000/25 10p
BY190 (MJE2021) NPN 80V/5A 40p	.047 1000V 8p	4.7/100 6p
(SJE5451) pair 28p	.22/250AC 8p	2.2/100 6p
(661 pair 80W/5A pair 28p	1500/100V 25p	1000/10 5p
(660 90V	10/500V 15p	8/350 5p
40V 2A O.P. Trans 20p	.47/100V 5p	1/250 5p
B0375/6 pair 20p	330/25V 5p	1/100 5p
BZV 15/12R PYE 30p	680/40V 8p	6MHz Filters 25p
BD226 25p	22/350V 7p	3300/40 15p
BD238 25p	330/100V 10p	3300/25 5p
MJE 1661 25p	15/450V 10p	1500/25 10p
XTALS T/V	47/450V 12p	1/350 5p
4.433.610KHz 50p	470/16V 8p	220/10 5p
BYX 38/600R 50p	470/25V 8p	680/100 10p
BT138 Triacs 10a/600V 65p	470/40V 10p	220/16 5p
RCA40506 Thyristors 50p	470/63V 15p	47/63 5p
MJE 2955/15A 50p	470/100V 15p	33/63 5p
TIP 41A-42 pair 40p	220/25V 6p	2.2/63 5p
G11 Phillips Thyristors 60p	220/40V 6p	22/100 8p
PYE Thyristors 85p	220/63V 10p	4.7/63 5p
2N4444-0T112 BT116	160/25V 5p	1000/40 10p
SP8385 Thorn 25p	330/16V 5p	100/450 30p
5 amp 300V Thyristors 25p	100/16V 5p	22M 350V 20p
BRC 4443 65p	2.2/160V 5p	33.000 20p
SCR 957 65p	10/40V 5p	PUA758PC £1.00
BD561-2 pair 30p	TBA 920 £1.00	MC1349P 50p
BC365 10p	TBA 920Q £1.50	TCEP100 £1.00
BD 131 25p	TBA 480Q £1.00	TCE120CQ £1.00
BD 183 50p	5 x 3 Speaker 80R or 50R 50p	
AC187-8K pair 40p	G9 Speakers 70R £1.00	
6 Way Ribbon Cable 20p per meter	TBA 625 £1.00	
4.7NF5KV 10p	TBA 550Q £1.50	
6200PF/2000V 10p	TBA 540 £1.00	
180PF/6KV 10p	TBA 5400 £1.00	
1000PF/10KV 10p	TBA 530Q £1.00	
1000PF/12KV 10p	TBA 990 £1.00	
1200PF/12KV 10p	SBA 550B £1.50	
270PF/8KV 10p	SN76003 £1.00	
160PF/8KV 10p	No Heat Sink	
.1MFD 400V 5p	SN 76003N £1.75	
.1MFD 800V 8p	SN 76023N £1.50	
.1MFD 2000V 15p	SN 76033 £1.50	
.01MFD 600V 5p	TBA 800 60p	
	TBA 810S £1.00	
	TCA 270 £1.00	
	TCA 270Q £1.00	
	TCA 275Q £1.00	
	CA 270 75p	
	TBA 720A £1.50	
	TBA 510Q £1.50	
	SN76115N 50p	
	TAA 700 £2.00	
	TAA570 £1.50	
	TBA 396 £1.00	
	SAS 570S £1.50	
	SN76666 £1.00	
	SN76660 50p	
	SN76227 50p	
	SN76544N 75p	
	TBA641BX1 £1.50	
	CA920 AW £1.00	
	TBA 750 £1.00	
	TAA 550 20p	
	SN76131N 50p	
	SN76001 £1.00	
	TBA560CQ £1.00	
	SN76530P 50p	
	SN76650N 50p	
	TDA1170 85p	
	TBA 651 75p	
	BTT822 £1.50	
	BTT8224 £1.50	
	22/40 5p	
	1500/40 10p	
	.005/1500V 5p	
	47/100V 8p	
	BU124 Portable T/V Line Scan 50p	

SENDZ COMPONENTS

2 WOODGRANGE CLOSE,
THORPE BAY, ESSEX

Reg. Office Only.

Callers by appointment only.

Add 15% VAT.

Add 30p P. & P.

Add postage for all overseas parcels.

Belling Lee CO AX Plug Non Solder Type 14p	BU 205 £1.00	NEW VHF/UHF on panel ELC2060 £4.50	IN4006 5p
100 mixed 20mm Fuses £2.00	BU 108 £1.00	Phillips T/Units UHF New £2.00	IN4007 5p
3500 Thorn Triplers £3.50	BU 208 £1.75	VHF/UHF AEG £2.50	BY210/400 5p
Triplers TS2511TDT THORN £2.50	BU 500 £1.75	Varicap NSE Removed from new panels	BY210/800 10p
Triplers TS2511TBQ PYE £1.50	BU 126 £1.00	VHF Varicap Units	BY176 50p
1730 DECCA £1.00	R2008B £2.00	NSF AEG removed from Print Panels £1.00	BA159 10p
GRUNDIG 3000/3010 SIEMENS TVK52 Triplers £3.00	R2010B £1.25	New 49.00 21.900MHz	BY184 25p
Triplers-DECCA £3.00	EHT Rectifier BY212 10p	VHF Varicap (NSF) AEG New 49.00 21.900MHz £2.00	BY187 50p
CS 2030 CS 2230	3 OFF G770/HU37 EHT 10p	4 Push Button T/Units UHF MULLARD £2.00	TV 20 50p
CS 2232 CS 2233	12KV 2 M/A Small 20p	AE Isolating Sockets UHF & Lead	TV 18 EHT 40p
CS 2630 CS 2631	EHT RECS 30p	PYE & THORN 40p	Rectifiers Sticks & lead & Anode Cap
CS 2632	EHT RECS	DECCA 1730 Doubler £1.00	BYF3214 20KV Rectifier Sticks 25p each
THORN-Needs Mod No 1400. 1500 Stud	EHT REC USED IN THORN 1400.1500 Triplers (x80/150) 10p	Transistor UHF Units with AE Socket and leads	BYF3123 18KV Wire ends 25p
Multipliers £1.00	CSD 118xMH Rec THORN 3500 10p	GEC 2000 Rotary type NEW £2.00	BA 248 6p
Triplers-PHILIPS	220M/450V THORN 50p	7 button Varicap tuning heads Variable Resistor with Fascia Plate 7 Lamps £3.00	BSS 68 20p
520.540.550 £3.00	700M/250V THORN 35p	PYE 6 push button unit for Varicap Tuning £2.50	BYX55/350 10p
Triplers-ITT	175+100+100 350V 3500 THORN £1.50	4 push button unit (for Varicap Tuning) 20K New 50p	BY 206 10p
CVC5 CVC20/25/30	400+400.350V DECCA 80p	DECCA Bradford Tuner 5 Button New £2.75	BT106 S/Type 50p
CVC7 CVC8	470+470.250V 40p	BB 105 UHF	BT 106 95p
CVC9 £3.00	100+200 325V 40p	BB 103 VHF	BT 116 95p
LP1174/33 DECCA	200+200+100+32 350V 70p	BA 182	BT 119 95p
LP1194/42 PYE	150+200+200.300V 70p	Varicap diodes 5p each	BT 109 70p
Triplers £4.00	731 PYE 600/300V & BUSH 75p each	BTY80 20p	BT 146 750V 25p
G2100 GEC Tripler	200+200 350V 60p	3 amp Diodes 300V 10p	Thyristors 8A/800V 2N6399A 30p
TVM25 £2.00	400M 400V 40p	3 amp Diodes 100V 7p	Thyristors 8A/400V 52600D 30p
THORN 3500	400M 350V 50p	1 amp Bridges 100V 20p	Y827 Diodes 30p
THORN 8500 Focus Unit	800M 250V 30p	1 amp 400V 20p	Bridge Rec
DECCA Focus Unit (Large or small) £1.00 each	AE Power supply 15V £1.00	3 amp Bridge 25p	B30C 600A6 12p
4 Push Button Units 1400-1500 THORN £3.50	Flush Mounted Diplexer White 2 Coax Sockets T/V F.M. 35p	W005M Bridge 15p	B30C 500 12p
4 Push Button Unit 8500 THORN £3.50	BF 127 BC 303	194-N30 Replacement for BU204 75p	BC147C 2N3566
300 Mixed condensers £1.50	BF 264 BRC 2108	121-1015 Replacement for BU208A £1.00	BC148B BF198
300 Mixed resistors £1.50	BF 180 BC 336	200+200+100 325V 70p	BC149C BF274
30 Pre-Sets £0.50	BF 181 BF 157	BY 127 10p	BC195 BSY79
100 W/W Resistors £1.50	BF 182 BC 161	IN4005 4p	BC108 BC327
40 Mixed Pots £1.50	BC 300 BC 460		BC107 BC213LA
20 Slider Pots £1.50	AC 128 BC 350		BF594 BC212LT
10 Different Types	BC 350 E1222		BC158 BF195
Mixed Electrolytics	BF 178 BSY95A		2N2222 BC182L
150 £2.00	BF 257 BFT 43 with heat sink		2N390 BF594
DP Push Button Switch ON/OFF 10p	BF 137 TIP 29A		2N4355 BC183
Mains ON/OFF	BF 185 TIP 32		T1591 BC238A
Push Button T/V 20p	BF 200 TIP 32		2SK30A BC454
Mains ON/OFF	BD 253 AC 153K		BC455
Rotary T/V 12½p	20p each		7p each
Mains Dropper THORN 6R+1R+100R 35p	GEC Sound O.P. Panel I.C. O.P. £2.50		
Mains Droppers 69R+161 PYE 40p	AC 176K		
AD 161 AD 162	AC 153K		
Pair 60p	Pair 40p		
147+260 PYE 40p	UHF Varicap Units+VHF NEW		
(731) 3R+56R+27R 50p	ELC 1043/05 £4.00		
100 Mixed Diodes £1.00	ELC 1043/06 £4.00		
Mixed Bulbs 45p	THORN Varicap UHF 3.500 £3.50		
RCA 16572	New EQV ELC 1043/05		
RCA 16573	DECCA UHF Varicap New eqv E1C 1043/05 £4.00		
O/P Trans Pair 40p	VHF/UHF AEG Varicap (New) £3.50		
ZTK 33B 6p	G8 PHILLIPS £3.50		
100 Mixed Transistors 75p	UHF Varicap replacement		
1 LBs Mixed Components £1.50			
BU 105/04 £1.00			

SENDZ COMPONENTS

2 WOODGRANGE CLOSE,
THORPE BAY, ESSEX

Reg. Office Only.

Callers by appointment only.

Add 15% VAT.

Add 30p P. & P.

Add postage for all overseas parcels.