

FEBRUARY 1981

70p

# TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS


## VIDEO MIXER



**CAPACITOR  
FAULTS**

**MOSFET BAND III  
PREAMPLIFIER**



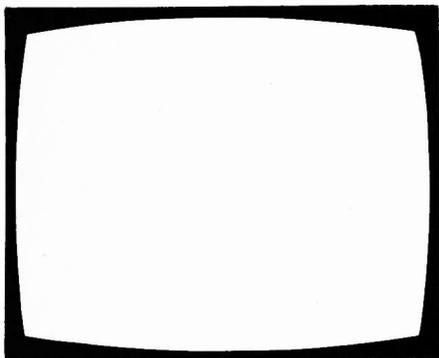

# TELEVISION

February  
1981

Vol. 31, No. 4  
Issue 364

## COPYRIGHT

©IPC Magazines Limited, 1981. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

## SUBSCRIPTIONS

An annual subscription costs £10 in the UK, £11 overseas (\$24.20 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

## BINDERS AND INDEXES

Binders (£4.40) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

## BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 85p inclusive of postage and packing.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.


Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").
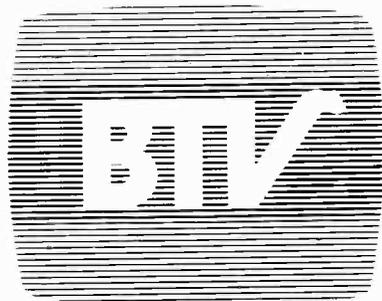
## this month

- 177 **Leader**
- 178 **Mosfet Band III Preamplifier** *by Hugh Cocks*  
The problem with bipolar transistor wideband amplifiers is the possibility of intermodulation problems in the presence of strong local signals. The use of a mosfet provides a solution.
- 179 **Readers' PCB Service**
- 180 **Letters**
- 183 **Video Mixer** *by Malcolm Burrell*  
A simple design allowing four or more monochrome video sources to be mixed. An effects circuit can be added and will be described in a later article.
- 186 **The Complementary Transistor Switch** *by S. George*  
Applications of the complementary transistor switch circuit in TV sets.
- 188 **Teletopics**
- 190 **VCR Clinic** *by Steve Beeching, T.Eng. (C.E.I.)*  
Further VCR faults and their causes.
- 192 **Servicing Notes on the Siemens Model FC365** *by Mike Dutton*  
Not a very common set this, but worth spending some time on. Notes on faults encountered to date.
- 193 **Practical TV Servicing: Capacitor Defects** *by S. Simon*  
Capacitors are responsible for a large proportion of faults in TV sets. A guide to common capacitor problems.
- 195 **Next Month in Television**
- 196 **Video Report: The Sony HVS2000P Effects Unit** *by David K. Matthewson, B.Sc., Ph.D.*  
A versatile unit at a very reasonable price. What it does and how it does it.
- 198 **Vintage TV: The Baird Everyman** *by Vivian Capel*  
This set, introduced in the late 40s, was an interesting exercise in economical design.
- 199 **Service Notebook** *by George Wilding*  
Notes on faults and how to tackle them.
- 200 **TV Tussles** *by Nick Lyons*  
A counter-attack by some Thorn sets plus notes on the Rediffusion Mk. I colour chassis.
- 202 **Long-distance Television** *by Roger Bunney*  
DX reception and conditions, and a review of the JVC Model 3040UKC.
- 205 **Test Report: The Thandar PFM200 Digital Frequency Meter** *by Eugene Trundle*  
There are quite a few uses for a frequency meter, and this one is remarkably cheap.
- 206 **Fault Report** *by Derek Snelling*  
Problems with the Tandberg CTV2-2 chassis and EW modulator faults on the Pye/Philips G11 chassis.
- 208 **Two-channel TV Sound** *by Harold Peters*  
Methods of obtaining two-channel sound, receiver considerations plus a note from Andrew Flockton on pseudo stereo.
- 210 **Active Sound Filter** *by Keith Cummins*  
A filter unit designed to remove the effects of beats between a sound recorder's bias oscillator and other signals above the basic audio spectrum.
- 211 **Service Bureau**
- 213 **Test Cast 218**

OUR NEXT ISSUE DATED MARCH WILL  
BE PUBLISHED ON FEBRUARY 18





**Can you afford NOT to switch to  
the fantastic BRIARWOOD TV trade offer?**

**100's of colour TVs  
100% complete - as they arrive - in batches of ten  
ONLY £13.00 per set**

**COLOUR TVs WITH TESTED TUBES  
GUARANTEED 100% COMPLETE**

	IN 10's	In 20's	GOOD WORKING in 10's
PYE 691	£18.00 each	£15.00	£33.00
PYE 697	£21.00 each	£18.00	£38.00
GEC 2040	£18.00 each	£15.00	£33.00
BUSH 184	£23.00 each	£20.00	£38.00
THORN 3000 19"	£28.00 each	£25.00	£43.00
THORN 3000 25"	£23.00 each	£20.00	£38.00
THORN 3500 26"	£28.50 each	£25.00	£43.00
DECCA BFD - 30's	£28.00 each	£25.00	£43.00
KORTING	£25.00 each	£22.00	£45.00
TELPRO	£23.00 each	£20.00	£38.00

Please note there is 15% VAT on all the above prices.

Foreign makes of TV's i.e. Skantic/Luxors, ASA's, Mitsubishi, Teleton, Grundigs, Saba's etc., in batches of 10's @ £40.00 each


Later types of sets i.e. G8, Thorn 3500 Varicap, ITT/KB, Thorn 8500, GEC 2100 etc., in batches of 10's @ £50.00 each.

**OPENING TIMES MON-FRI 9.00-12.00/1.00-5.45 (CLOSE 4.30 SAT)**

**CASH & CARRY SPECIAL SERVICE TO THE TRADE  
OR ASK ABOUT SPECIAL DELIVERIES ON LARGE QUANTITIES**

BRIARWOOD TELEVISION  
Briarwood House, Preston Street  
BRADFORD, West Yorkshire ND7 1LU  
Tel: (0274) 306018

**BRIARWOOD TELEVISION LIMITED**

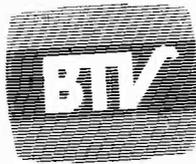

# BRIARWOOD

## QUALITY SELECTED EX EQUIPMENT SPARES

**MISC S/Output Trans. £1 + VAT + P&P**  
**F/Output Trans. £1.25 + BAT + £1 P&P**  
**Scancoils £1.50 + VAT + £1 PIP. Other spares available, please write or phone for details.**

**MONO TUNERS**  
 6 button integrated all at **£4.00**  
 U.H.F. P/Button D/S **£3.50**. U.H.F. P/Button S/S **£4.00**. Rotary **£3.00** + **£1 P&P**

**MONO TUBES**  
 (tested)  
 19" Ringuard **£3.00**  
 23" Ringuard **£4.00**  
 20" Ringuard **£5.00**  
 24" Ringuard **£6.00**  
 + **£5.00 P & P**

**MONO LOPTS**  
 All D/Standard Lopts at **£4.00 + £1 P&P**.  
 All S/Standard at **£4.00 + £1 P&P**.

**MONO PANELS**  
 i.e. Philips, Bush, etc. **£3.50 + £1 P&P**.  
 Quotations for complete S/hand chassis if required. (Diff. prices)

**PLEASE ADD 15% V.A.T. TO ALL ITEMS AND OVERSEAS AT COST CASH WITH ALL ORDERS.**

### VALVES (MONO & COLOUR)

PCL82	0.10	30C1	0.10	PCC189	0.10	EF183	0.10	PL504	0.25	ECL80	0.10
PCL83	0.25	30C17	0.10	30C15	0.10	EF184	0.10	6/30L2	0.10	PL509	1.00
PCL84	0.10	PCF802	0.10	30C18	0.25	6BW7	0.10	30PL1	0.25	PY500	1.00
PCL85	0.10	PCF805	0.25	PC97	0.20	EH90	0.10	30PL13/4	0.10	GY501	1.00
PCL86	0.10	PCF806	0.10	PC900	0.10	DY802	0.10	30FL1/2	0.25	PL508	0.50
PFL200	0.10	PCF808	0.25	EF80	0.10	PY800/1	0.10	ECC82	0.10	PCF200	0.50
PCF801	0.10	PCF80	0.10	EF85	0.10	PL36	0.25	ECC81	0.10	EY51	0.15

Please note there is 25p Postage and Packing per order.

**WE DO NOT SELL RUBBISH AT BRIARWOOD TV**

### D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUPUT	POWER	L/TB	F/TB
Bush/Murphy	5.00	5.00	6.50	—	—	5.00	1.50	—	—	—
GEC/Sobell	5.00	5.50	—	—	—	5.00	—	5.00	—	—
Philips	5.00	7.00	—	—	—	5.00	—	—	—	—
Decaa	5.00	9.00	9.00	—	—	5.00	2.00 (19" only)	—	—	7.50
Thorn 2000	5.00	5.00	5.00	6.50	6.50	7.00	—	6.00	—	5.00
Pye	7.00	6.00	7.00	—	—	5.00	—	—	—	5.00
Baird	6.50	8.50	7.00	—	—	5.00	—	6.50	10.00	5.00
										5.00
										5.00

Postage & Packing £1.25

### S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	12.00	—	6.00	6.00	12.00	—
GEC Hybrid	6.00	6.50	9.00	—	5.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	5.00	—	—	6.00
Thorn 3000	6.00	6.00	6.00	—	5.00	20.00	20.00	6.00
Pye 691/693	6.00	6.00	8.00	—	5.00	—	15.00	5.00
Thorn 3500	6.00	6.00	6.00	6.50	12.00	20.00	20.50	6.00

Kotring and other foreign panels available on request.

Postage & Packing £1.25

### COLOUR TUBES

17"	£15.00
18"	£15.00
19"	£15.00
19" A49/192	£18.00
20"	£18.00
22"	£20.00
25"	£15.00
26"	£22.00

Plus P&P **£6.00**  
**New rebuilt tubes available on request.**

### COLOUR TUNERS

Bush	£5.00
GEC	£5.00
Philips G6 S/S	£5.00
Pye 691	£5.00
Thorn 3000	£5.00

Some new tuners in stock, can supply on request. Many Foreign Tuners also available on request. Plus P&P **£1**.

### COLOUR LOPTS

Most Lopts available from **£5.00**. Both British & Foreign makers. Please ring or write. P&P per Lopt **£1.00**

### MISC.

S/Output transformer from **£1.50**. F/Output from **£1.25**. Scancoils from **£5.00**. P&P **£1.00**. Other spares available on request.

**THORN 1500 TUNERS**  
**NEW SPECIAL OFFER**  
**AT £8.00**

Postage & Packing **£1.00**

## NEW PRODUCTS!

**£2.50** each  
 £1.00 p&p




**SUPER VALUE - SUPER QUALITY**

Wide band aerial for all UHF TV transmissions

**£5.95** each  
 £1.75 p&p

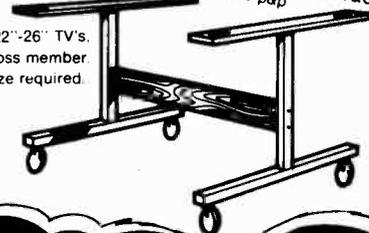Fits 22"-26" TV's.  
 wood finished cross member.  
 State size required.



# TV scores with quality

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED

## NEW SPARE SELECTION

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £
AC107	0.24	AF170	0.92	BC173	0.12	BD132	0.36	BF199	0.14	OC25	1.00	2N2219	0.40
AC113	0.22	AF172	1.00	BC177	0.12	BD133	0.37	BF200	0.28	OC26	1.00	2N2646	0.40
AC115	0.23	AF178	1.00	BC178	0.12	BD135	0.30	BF216	0.12	OC28	1.30	2N2926	0.15
AC117	0.30	AF180	1.00	BC178A	0.12	BD136	0.30	BF217	0.12	OC35	1.00	2N3053	0.21
AC125	0.23	AF181	1.00	BC179	0.12	BD137	0.30	BF218	0.12	OC36	0.90	2N3054	0.60
AC126	0.23	AF186	0.90	BC182L	0.09	BD138	0.31	BF219	0.12	OC38	0.90	2N3055	0.60
AC127	0.22	AF239	0.46	BC183L	0.09	BD139	0.40	BF220	0.12	OC42	0.45	2N3442	1.00
AC128	0.22	AU113	1.40	BC183LA	0.10	BD140	0.37	BF221	0.21	OC44	0.60	2N3702	0.15
AC131	0.13	BA130	0.08	BC183LB	0.10	BD144	1.39	BF222	0.12	OC45	0.50	2N3703	0.12
AC141	0.24	BA145	0.14	BC184L	0.09	BD145	0.50	BF224	0.18	OC46	0.39	2N3704	0.18
AC142	0.24	BA148	0.21	BC186	0.21	BD177	0.50	BF256	0.37	OC70	0.39	2N3705	0.18
AC141K	0.31	BA155	0.08	BC187	0.21	BD178	0.50	BF258	0.30	OC71	0.39	2N3706	0.14
AC142K	0.31	BAX13	0.05	BC209	0.11	BD203	0.40	BF259	0.30	OC72	0.39	2N3707	0.14
AC151	0.21	BAX16	0.08	BC212	0.09	BD204	0.70	BF260	0.25	OC74	0.39	2N3708	0.14
AC165	0.21	BC107	0.11	BC212L	0.09	BD222	0.73	BF262	0.28	OC75	0.39	2N3772	2.00
AC166	0.21	BC108	0.11	BC213L	0.09	BD233	0.36	BF263	0.25	OC76	0.39	2N3773	2.50
AC168	0.22	BC109	0.11	BC214L	0.09	BD234	0.34	BF271	0.27	OC77	0.50	2N3619	0.30
AC176	0.22	BC113	0.11	BC237	0.09	BD237	0.44	BF272	0.27	OC78	0.23		
AC176K	0.28	BC114	0.11	BC238	0.09	BD238	0.44	BF273	0.16	OC81	0.26		
AC178	0.23	BC115	0.11	BC240	0.31	BDX22	0.73	BF336	0.30	OC810	0.14	DY87	0.52
AC186	0.26	BC116	0.11	BC249	0.35	BDX32	1.98	BF337	0.29	OC82	0.26	DY802	0.64
AC187	0.23	BC117	0.12	BC251	0.22	BDY18	0.80	BF338	—	OC820	0.20	ECC82	0.52
AC188	0.23	BC119	0.24	BC257	0.20	BDY60	0.80	BF479	0.29	OC83	0.30	EF80	0.50
AC187K	0.30	BC125	0.15	BC262	0.18	BF115	0.30	BFT	0.27	OC84	0.30	EF183	0.70
AC188K	0.30	BC126	0.15	BC263B	0.20	BF12*	0.29	BFT	0.27	OC85	0.28	EF184	0.70
AD130	0.58	BC136	0.15	BC267	0.19	BF154	0.12	BFX84	0.27	OC123	0.25	EH90	0.75
AD140	0.60	BC137	0.17	BC281	0.24	BF158	0.19	BFX85	0.27	OC169	1.20	PC86	0.85
AD142	0.80	BC137	0.23	BC300	0.27	BF159	0.24	BFX	0.30	OC170	1.20	PC89	0.85
AD143	0.70	BC139	0.23	BC301	0.27	BF160	0.23	BFY37	0.22	OC171	0.92	PCC89	0.65
AD145	0.70	BC140	0.24	BC302	0.30	BF163	0.30	BFY50	0.21	OA91	0.07	PCC189	0.70
AD149	0.64	BC141	0.27	BC303	0.27	BF164	0.30	BFY51	0.21	BRC4443	0.65	PCF80	0.80
AD161	0.42	BC142	0.27	BC307	0.11	BF167	0.30	BFY52	0.21	R2008B	1.50	PCF86	0.72
AD162	0.42	BC143	0.27	BC307A	0.11	BF173	0.21	BFY53	0.27	R2009	1.30	PCF801	0.70
AD161)		BC147	0.10	BC308A	0.12	BF177	0.26	BFY55	0.33	R2010B	1.50	PCF802	0.78
AD162)	1.00	BC148	0.10	BC309	0.14	BF178	0.24	BFX		R2265	1.50	PCL82	0.70
AF106	0.42	BC149	0.10	BC337	0.12	BF179	0.28	BHA0002	1.90	R2305	0.38	PCL84	0.75
AF114	0.37	BC153	0.12	BC338	0.15	BF180	0.30	BSX20	0.23	R2305	0.38	PCL86	0.81
AF115	0.37	BC154	0.12	BC487	0.20	BF181	0.34	BSX76	0.23	BD222	0.37	PCL805	0.82
AF116	0.37	BC157	0.12	BC547	0.10	BF182	0.30	BSY84	0.36	R2540	2.50	PLF200	1.00
AF117	0.40	BC158	0.12	BC548	0.11	BF183	0.29	BU105	1.00	S2802	—	PL36	0.90
AF118	0.45	BC159	0.12	BC549	0.11	BF184	0.27	BU105 02	1.50	SCR957	0.65	PL84	0.74
AF121	0.37	BC160	0.26	BC557	0.12	BF185	0.29	BU105 04	2.00	TIP31A	0.38	PL504	1.15
AF124	0.43	BC161	0.26	BCX33	0.10	BF186	0.32	BU126	1.40	TIP32A	0.36	PL508	1.50
AF125	0.30	BC167	0.11	BD112	0.39	BF192		BU205	1.20	TIP3055	0.53	PL509	2.45
AF126	0.30	BC168	0.11	BD113	0.65	BF194	0.15	BU206	1.60	TIP31B	0.39	PL509	2.45
AF127	0.30	BC169	0.11	BD115	0.32	BF195	0.13	BU208	1.60	TIS90	0.23	PL802	2.55
AF139	0.40	BC171	0.10	BD116	0.47	BF196	0.13	OC22	1.10	TIS91	0.25	PY88	0.75
AF150	0.27	BC171A	0.10	BD124	1.30	BF197	0.13	OC23	1.30	TV106	1.09	PY500A	1.60
AF151	0.30	BC172	0.10	BD131	0.36	BF198	0.12	OC24	1.30	MJE340	0.50	PY81 800	0.65
										MJE520	0.45		

### E.H.T. Trays

TYPE	PRICE £
Pye 691 693	4.50
Pye 715/731/735	5.50
Pye 737	5.40
Decca (Large Screen)	
CS2030/2232/2630/2632/2230/2233/2631	5.00
Decca 80	5.30
Decca 100	5.30
Philips G8	
520/540	5.30
Philips G9	5.50
Philips 550	5.30
GEC C2110	5.50
GEC Hybrid	
CTV	5.10
Thorn 3000/3500	5.00
Thorn 800	2.42
Thorn 8500	4.75
Thorn 9000	5.50
GEC TVM25	2.50
ITT KB CVC	
5/7/8/9	5.10
ITT KB CVC	
20/25	
30/32	5.50
Bush CTB25	
Mk3	
Quadrupler	8.00
Bush X179	4.50
RR1 (RBM)	
A823	5.00
Bang & Olufsen	
4/5000 Grundig	
5010/5011/5012/6011/6012/7200/2052/2210/2252R	
Tandberg (radionette)	
Autovox	6.60
Grundig	
3000/3010	
Saba 2705/3715	
Telefunken	
709/710/717/2000	6.80
Korting	6.80

All transistors, IC's offered are new and branded. Manufactured by Mullard, I.T.T. Texas, Motorola etc. Please add 15% VAT to all items and overseas at cost. P & P U.K. 50p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice.

## MAIL ORDER TV BARGAINS

PYE 691	22" @ £55.00
PYE 691	26" @ £55.00
PYE 697	22" @ £65.00
PYE 697	26" @ £65.00
BUSH 184	19" @ £70.00
BUSH 184	22" @ £70.00
BUSH 184	26" @ £70.00
GEC 2040	19" @ £55.00
GEC2040	22" @ £55.00
GEC 2040	25" @ £55.00
GEC 2040	26" @ £65.00
KORTING	22" @ £70.00
KORTING	26" @ £80.00
THORN 3000	19" @ £70.00
THORN 3000	25" @ £60.00
Good working mono's Pye, GEC, Bush etc.	
20" & 24" S/S	£15.00
20" & 24" D/S	£14.00
19" & 23" D/S P/Button	£12.00
19" & 23" D/S Rotary	£ 8.00

Cheques, P.O. or Cash with orders Please. Please note there is 15% VAT on all the above prices. Plus £10.00 p & p for colour TV, £5.00 for mono. ENGLAND, WALES and SCOTLAND. Inland N & S IRELAND £15.00 for colour. £7.00 for mono.

### TYPE PRICE £

#### IC's

BTT6018	1.00
CA3605	1.20
MC7/c	
MC14016	0.50
SN76003N	1.40
SN76013N	1.20
SN76013ND	1.00
SN76023N	1.20
SN76023ND	1.00
SN76110N	1.00
SN76226DN	1.50
SN76227N	1.20
SN76532N	1.30
SN76550N	0.30
SN76666N	0.70
TAA570	1.38
TBA120AS	1.00
TBA120S	0.75
TBA120SQ	0.75
TBA395	2.20
TBA341	0.97
TBA520	1.40
TBA520Q	1.10
TBA530Q	1.10
TBA540	1.30
TBA540Q	1.45

TBA550Q	1.40
TBA560C	1.50
TBA560CQ	1.50
TBA570	1.00
TBA570Q	1.00
TBA800	1.00
TBA810	1.50
TBA920	2.00
TBA920Q	1.50
TBA990Q	1.50
TCA270SQ	1.45
TCA270SA	1.45
TCA270Q	—
TCA1327B	1.00
TCA800	2.00
TDA1010	—
TDA1327B	1.00
SBA750	1.75
SC9503P	1.20
SC9504P	1.20
SL901B	3.50
SL917B	5.00
DIODES & THYRISTORS	
OA47	0.06
OA81	0.06
OA90	0.06
OA91	0.07
BA130	0.10
BA145	0.16
BA148	0.18
BA154	0.18
BA155	0.10
BAX13	0.08
BAX16	0.10
BY126	0.10
BY127	0.10
BY164	0.40
BY179	0.57
BY226	—
BY227	0.12
BYF206	0.14
1N4001	0.04
1N4002	0.05
1N4003	0.06
1N4004	0.07
1N4005	0.07
1N4006	0.08
1N4007	0.08
1N4148	0.05
1N4751	0.14
1N5401	0.12
1N5403	0.12
1N5404	0.14
1N5405	0.14
1N5406	0.14
1N5408	0.25
BR100	0.22
BR101	0.28
BT106	1.19
BT108	1.23
BT109	1.09
BT116	1.60
BT120	1.60
2N4444	0.90

### E.H.T. TRAYS

#### MONO

950 MK2	
1400	2.50
1500 18" 19" stick	2.75
1500 24" 5 stick	2.85
Single Stick	
Thorn TV	
11. 16K 70V	0.75
TV 20 2 MT	0.75
TV 2016K	
18V	0.75
BUSH 718	1.30

EXPORT COLOUR & MONO TV'S AVAILABLE READY FOR USE OVERSEAS

# BRIARWOOD TELEVISION LTD

Briarwood House, Preston Street, Bradford West Yorkshire BD7 1LU  
Tel: (0274) 306018

## Manufacturers Surplus Components FIT THE RIGHT PART

**20 assorted Tantalum capacitors**  
£1.20

300 mixed  $\frac{1}{2}$  and  $\frac{1}{4}$  watt resistors £1.95  
150 mixed 1 and 2 watt resistors £1.95  
300 mixed **Capacitors**, improved pack, most types £3.95  
100 mixed **Electrolytics** £2.95  
300 mixed **Printed Circuit** mounting **Components** for various TVs, resistors, caps etc £1.95  
300 printed circuit **Resistors**  $\frac{1}{2}$  to 4 watt £1.45  
100 **High Wattage** TV resistors, **Wirewound** etc. £2.95  
100 mixed miniature Ceramic and Plate Caps £1.50  
100 mixed polystyrene capacitors £2.20  
25 mixed **Pots and Presets** £1.20  
25 mixed **TV Presets** £1.00  
20 assorted **TV VDRs** and **Thermistors** £1.20  
10 assorted **TV Convergence Pots** £1.00  
20 assorted **TV knobs**, includes push button, chrome, control types etc. Mostly Thorn and ITT £1.00  
10 assorted **Valve Bases**, B9A, ceramic, EHT, etc. £1.00  
20 assorted **Sync Diodes** blocks for various TVs £1.00  
10 **Spark Gaps** £1.00  
20 assorted **Zener Diodes** 1 watt and 400MW £1.50  
100 **Mixed Diodes**, includes zener, power, bridge, varicap, germanium, silicon etc. All full spec. £4.95  
12 assorted **I.C. Sockets** £1.00  
20 Gen. purp. **Germ. Diodes** £1.00

**GRUNDIG**  
**UHF/VHF Varicap Tuners.**  
Fit 1500 GB, 3010 GB.  
Brand new £12.50

### PUSH BUTTON KNOBS

**Type 1** 15mm long x 11mm diam. Brushed Aluminium Finish  
10 for £1

**Type 2** 10mm long x 10mm diam. Chrome Finish 10 for £1

Both types fit standard  $3\frac{1}{2}$ mm square shafts as used on most music centres etc. 100 for £7  
1000 for £50

### SPECIAL SCOOP PURCHASE OF MULLARD CAPACITORS

Spillages, Floor Sweepings, Cosmetic Imperfects etc. All mixed up. Factory clearance.

#### UNREPEATABLE OFFER

**Polyester C280's** (Licuorice Allsorts) 100 mixed £2. 1000 mixed £12  
**Miniature Electrolytics** (Blue Type) 150 mixed £2. 1000 mixed £10

**De Luxe Fibre Glass Printed Circuit Etching kits**  
Includes 150 sq. ins. copper clad F/G. board, 1 lb ferric chloride, 1 etch resist pen. "Tweezers", Abrasive cleaner. Etch tray plus instructions. **Special Price £5.95.**

**1 lb F.E. C1** To mil. spec. £2.25  
150 sq. in. **Single sided** board £2.00  
150 sq. in. **Double sided** board £3.00

**33V Varicap Tuner Regulators.**  
Equivalent to TAA550, SN76550, ZTK33 etc. Only 8 for £1

**Why Buy Expensive Triplers!**  
Repair your old 5 and 3 sticks at a **Fraction of the Cost.**  
10 Replacement Rectifier Sticks (Thorn). £1.00

Ultrasonic 40 kHz remote control receiver with 20" Coax lead and Phono Plug.  
Thorn: £1.20 each 3 for £3

### Hardware Pack

Includes BA nuts and bolts, nylon, posidrive, self-tapping "P" clips, cable markers, clamps, fuse holders etc. £1 per lb.

**ITT CTV. SCAN COILS** complete with conv. yoke. Plessey type. £3.95

### TRANSISTOR MOUNTING KITS

**TO3** (BU208 etc) 8 for 60p  
**TO220** (TIP 33 etc) 10 for 60p  
**TO77** (BD131 etc) 12 for 60p  
Pack of each £1.50  
**All include Mica insulators and relevant washers.**

### I.C. SOCKETS

**DIL 14 pin** 10 for £1  
**Quil 16 pin.** 12 for £1  
**Dil to Quil 16 pin** 10 for £1

### CASSETTE MAINS LEAD

7' lead with Fig. 8 Plug. 75p each, 4 for £2

### ITT BLUE LATERAL

Assembly (single knob type) 60p  
3 for £1.50

**ITT Spun Aluminium Control Knobs.**  $\frac{1}{2}$ " diam.  $\frac{1}{4}$ " shaft 4 for £1

### SAVE THAT TUBE.

Fit our **C.R.T. Isolating Transformer.** Ideal for HTR./Cath. Shorts. 200-220-240 inputs. 750-900 MA outputs with thermal cutout. Made for **Thorn 4000 C.T.V.** but works O.K. on other sets. £3.00 each 2 for £5.00

**Pye 697 Line + Power Panels.** Damaged with some components missing but ideal for spares. Good value £2.20 each 3 for £6

### SPECIAL OFFER

Thyristors, **SS106.** Like **BT106.** 60p each 3 for £1.50  
10 for £4.00

**3A 200V Diodes** 8 for £1.00  
**2A 800V Metal Diodes** 12 for £1.00  
**3A 1000V Diodes** 6 for £1.00

### FOCUS UNITS

Rotary type. As fitted in "Thorn 8500", solid state **G.E.C.** and lots of other sets. £1.20 each 3 for £3.

### VIDEO GAME BOARDS

All new but incomplete. Hundreds of useful modern components. **C.M.O.'s** I.C.'s, Transistors, Diodes, Sockets, Switches, etc. 5 Assorted Boards £2.50.

**Degaussing V.D.R.'s** (Red, Orange, Black), fit most sets. 5 for £1.

**Bush CTV 25 Quadrupler** Remo type Q25B. equiv. to ITT. TU25 3QK. with mounting brackets. £3 each. 2 for £5

**GEC single standard**, hybrid chassis. convergence panel. Brand new, complete with plugs and leads £2.50

**G.E.C. S/S Hybrid Focus** Assembly with lead and VDR Rod £2.00

### SPECIAL OFFER

**GEC** transistor rotary tuners with slow drive. AE Skt. and leads **2010 Series £1.95 each 3 for £5**

Line linearity coils. 50p each, 3 for £1  
**4 Knobs** black with chrome caps to fit ITT, Thorn, GEC and most small diam. shafts 60p per set  
**ITT CVC5** power panel. New but five resistors never fitted £1.50

**4 P/B UHF TUNER** suitable for **VC200** and some Pye and Philips sets. 3 hole fixing. £2.75  
**Pye** mono mains droppers with fusible link. 147 $\Omega$  + 260 $\Omega$  50p 3 for £1.00  
69 $\Omega$  + 161 $\Omega$  50p 3 for £1.00

**R2010B** £1 each

### Portable TV EHT Sticks

"Siemens TV 18 KV". Fit most portables 50p each 3 for £1.00

**Pye 18" CT200 V. Cap/P/B** Assembly with leads and plug £3.90

**Miniature Mains Transformers** 4-5V-0-4 5V at 250Ma 90p each. 3 for £2.50

**BD131 4 for £1.** **BD132 4 for £1**  
**2N3055H** 60p each 3 for £1.50  
**FOCUS RODS** ( $2\frac{3}{4}$ " V.D.R.) £1.20 each 3 for £3

**BB105B** U.H.F. Varicap Diodes 20 for £1

### Telescopic Aerials

Chrome on Brass, 9 Section. 2'1" Extended. Plugs in to any 3.5mm skt. Ideal for portables. £1.00 each, 3 for £2.50.

### UHF MODULATOR

**VIDEO IN - UHF OUT** Calibrated to Channel 36. Housed in metal box  $2\frac{1}{2}$ " x 2" x  $\frac{1}{2}$ " Complete with 9" coaxial lead and plug. With connection data. only £2.50 each, 3 for £6

**Thorn 1500** Bias Caps. 160uF 25v 20 for £1.50

**ZENERS**  
**400MW.** 2-7V, 4-3V, 4-7, 5-6, 6-2V, 6-8, 7-5, 27V, 30V  
10 of one type 80p. 10 of each type £6.00  
10 of each type £5.50  
**1.3W.** 12V, 13V, 18V, 10 of one type £1.00  
10 of each type £2.50

**DIACS** BR100 6 for £1.00

**GEN. PURPOSE DIODES**  
IN4000 30 for £1.00 IN4003/10D2 20 for £1.00  
IN4002 25 for £1.00 IN4148 20 for £1.00  
BA158 10 for £1.00

## TRANSISTOR PACKS

Our Transistor Packs are even better than before! **100 NEW AND MARKED TRANSISTORS** including BC238, ME0412, BF274, BC148, BC183L, BC338 and, or other similar types. A random analysis of these packs yielded between 98 and 106 transistors of 17 to 20 different types with an average total retail value of £14 - £16. **OUR PRICE ONLY £4.95**

**200 transistors** as above but including BD131, 2N3055, AC128, BFY50, BC154, BF394, BC184L, etc. **ONLY £9.95**

Send 60p P. & P. on all above items; send Cheque or P.O. with order to:-

### SENTINEL SUPPLY DEPT. TV

149a Brookmill Rd., Deptford, London SE8

(Mail Order address only. Callers by appointment)  
Trade enquiries for quantity welcome.

Surplus stocks purchased for cash.

**NEW**  
**4-433 C.T.V. Crystals**  
Long Leads £1.00 each  
3 for £2.50

**Miniature Push to make Switches.**  
Red knob 8 for £1  
**Sub. Min. S.P.C.O. Slide Switches** 10 for £1

**2-2k** fusible, vertical mounting  
**Screen Feed** resistors 9 watt 8 for £1.00  
**0-47 $\Omega$**   $\frac{1}{2}$  watt emitter resistors 40 for £1.00  
**10 $\mu$ F 400V** modern Small Type 8 for £1.00  
**4.7 $\mu$ F 63V** 20 for £1.00  
**1000 $\mu$ F 16V** 10 for £1.00  
**330 $\mu$ F 25v** 10 for £1.00  
**470 $\mu$ F 25V** 10 for £1.00  
**4,500 $\mu$ F 35V** cans 80p each  
**2,200 $\mu$ F 40V Cans** 60p; 3 for £1.50  
**4,700 $\mu$ F 40V Cans** 80p; 3 for £2.00  
**RBM/ITT. Capacitor 220uf 400v** £1.00 each, 3 for £2.50.

**VIDEO O.P. TRANSISTORS**  
BF257A 10 for £1.00  
BF338 10 for £1.50

**Avoid Lethal Shocks**  
Buy our specially designed **EHT Probe**, removes high voltage charges from tubes, caps, etc. Heavily insulated with lead and earth connector 60p each

**B9A** P.C. valve bases 20 for £1.00  
**EY87/DY87 EHT** bases 10 for £1.00  
**C.T.V.** Tube bases 5 for £1.00

**20mm Antisurge Fuses.** 630Ma 800Ma, 1A, 1-25A, 1-6A, 2A, 2-5A 3-15A 12 of ONE Type £1  
Pack of Each £7  
60p 3 for £1.50

**TBA 800Q** 10 for £1.50  
**TH3** thermistors 10 for £1.50  
Miniature "Terry" clips ideal for screwdrivers and small tools etc. 40 for £1.00

**Convergence Pots** with knobs. 5 $\Omega$ , 10 $\Omega$ , 20 $\Omega$ , 30 $\Omega$ , 50 $\Omega$ , 100 $\Omega$ , 200 $\Omega$ , 1K. 8 of 1 type £1.00. 8 of each £7

**Decca Bradford Tuners.** 5 button (4 push, one tune) £2.75 each, 5 for £10.50. Also fit **Indesit** mono TV.

**EHT Cable** 30p per metre 10 metres £2.50  
**Anti Corona Caps** 3 for £1.00  
**Miniature Level/Batt. Meters** as fitted to many cassette recorders 90p  
Miniature **Reed Switches** 20 for £1.00. 100 for £2.95.  
**Rediffusion/Doric Mk 13** 5 stick **Triplers** can be modified for other sets £1.00


# MANOR SUPPLIES

## PAL COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)



3RD SUCCESSFUL YEAR

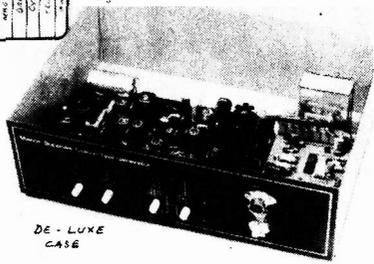

DE-LUXE CASE

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

**PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £40.25 + £1.40 P/Packing, DE-LUXE CASE £5.95, ALUMINIUM CASE £3.30, BATT HOLDERS £1.70, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.55.**

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £28.75 + £1.40 p.p. CASE EXTRA £2.00. BATT. HOLDERS £1.70.

- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed. Technical back-up service.

MK 4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.60 P&P.  
 MK 4 DE LUXE (MAINS) BUILT & TESTED £80.50 + £1.60 P&P.  
 VHF MODULATOR (CHI to 4) FOR OVERSEAS £4.60.  
 INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.  
 (ALL PRICES INCLUDE 15% VAT)


# MANOR SUPPLIES

## TELETEXT KIT (MK2)

(INCORPORATING MULLARD DECODER 6101VML)

BACKED BY YEARS OF EXPERIENCE

INFRA RED REMOTE CONTROL

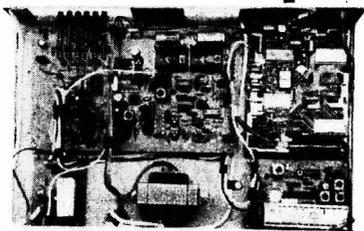

- EXTERNAL UNIT, PLUGS INTO AERIAL SOCKET OF TV RECEIVER.
- LATER SPEC (DOUBLE HEIGHT, BACKGROUND COLOUR ETC).
- INFRA RED REMOTE CONTROL (MULLARD 3000 SYSTEM) STATION SELECTION, TEXT, MIX, TIME, DOUBLE HEIGHT, HOLD, CLOCK, REVEAL RESET ETC, ETC.
- INCLUDES COMPLETE & TESTED 6101 VML (MULLARD) DECODER, SAW FILTER IF PANEL & 32 BUTTON REMOTE CONTROL HANDSET.
- SUITABLE FOR BBC DEAF SUB-TITLE TRANSMISSIONS-REMULATES PICTURE.
- CONVERTS ANY UHF RECEIVER TO STATION SELECTION REMOTE CONTROL AND TELETEXT. (SIMPLIFIED KIT AVAILABLE FOR REMOTE CONTROL ONLY).
- FACILITIES FOR VIDEO OUTPUT, MONITORS, CCTV ETC.
- AUDIO OUTLET FOR EXTERNAL HI-FI AMPLIFIER.
- EVERY KIT EASY TO ASSEMBLE & FULLY GUARANTEED. TECH. BACK-UP SERVICE.
- DE-LUXE CASE MEASUREMENTS APPROX. 154 x 104 x 34.
- WORKING MODEL AT 172 WEST END LANE, N.W.6.

FURTHER DETAILS ON REQUEST

ALSO, MANOR SUPPLIES TELETEXT MK1 KIT (TEXAS) NOW WITH REMOTE CONTROL PRICE £193.20 P/P £2.80.

## TELETEXT & TELEVISION SPARES

"TELEVISION" NEW MONITOR PARTS AVAILABLE.  
 "TELEVISION" NEW PORTABLE RECEIVER PARTS AVAILABLE.  
**WORKING MODEL & PANEL TEST SERVICE.**  
 NEW CTV SIGNALS BOARD PARTS NOW AVAILABLE.  
**SPECIAL OFFER TEXAS XMII TELETEXT MODULE NEW & TESTED, LIMITED QUANTITY AT HALF PRICE £69.00 p.p. £1.40.**  
**"TELEVISION" COLOUR RECEIVER PROJECT ALL PARTS AVAILABLE AT PRESENT. POWER, SIGNAL & TIMEBASE. SEND OR PHONE FOR LIST. WORKING MODEL ON SHOW WITH TELETEXT. (PANEL TEST SERVICE NOW AVAILABLE).**  
 NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.80 p.p. £1.10.  
 TELETEXT 5V STABILISED MAINS POWER SUPPLY (FOR TEXAS OR MULLARD DECODERS) £6.70 p.p. £1.00.  
 TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE £11.30 p.p. £1.00. XM11 INTERFACE PANEL (THORN) £2.10 p.p. 75p.  
**CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £12.65 p.p. 50p. (ALUM CASE £2.60 p.p. 80p.)**  
 ADDITIONAL GREY SCALE KIT £3.35 p.p. 35p.  
 TV TEST GENERATOR UHF MODULATOR £4.60 p.p. 40p.  
**UHF SIGNAL STRENGTH METER KIT £20.00 (VHF VERSION £21.60). ALUM CASE £2.00 DE LUXE CASE £5.95 p.p. £1.60.**  
**CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO £25.80 p.p. £2.00.**  
**THORN 9000 FACIA INCL. CHANNEL SELECTOR, INDICATOR SET CONTROLS, ETC. £5.50 p.p. £1.80.**  
**PHILIPS 210, 300 Series Frame T.B. Panels £1.15 p.p. 75p.**  
**BUSH Z718, BC6100 SERIES SURPLUS LINE T.B. PANEL Z904, INCL. LOPT, EHT STICK, FOCUS ETC. 18" £17.25 p.p. £2.00.**  
**BUSH Z718 BC6100 SERIES IF PANEL £5.75 p.p. 80p.**  
**BUSH A816 IF PANEL (SURPLUS) £1.90 p.p. 80p.**  
**BUSH 161 TIMEBASE PANEL A634 £3.25 p.p. £1.40.**  
**GEC SERIES 1 MONO PANELS £2.10 p.p. £1.30.**  
**GEC 2110 DECODER, RGB PANELS £5.75 EACH p.p. £1.00.**  
**GEC 2010 SERIES TIMEBASE PANEL £1.15 p.p. 95p.**  
**GEC 2040 (TYPE) CDA PANEL £2.88 p.p. £1.25.**  
**GEC 2040 CONVERGENCE PANEL £2.88 p.p. £1.30.**  
**PYE 697 Line T.B. P.C.B. type salvaged £4.80 p.p. £1.50.**  
**THORN 3000 LINE TB PCB £5.75 each p.p. 85p.**  
**THORN 3000 VID, IF, DEC, Ex Rental £5.75 each p.p. £1.30.**  
**THORN 8000/8500 IF/DECODER PANELS salvaged £5.52 p.p. £1.60.**  
**THORN 8000/8500 POWER/SALV. SPARES £2.88 p.p. 60p.**  
**THORN 9000 LINE T.B. (incl. LOPT etc.), SALV., SPARES £8.62 p.p. £1.60.**  
**MULLARD AT1022 Colour Scan Coils £6.90 p.p. £1.60, AT1023/05 Convergence Yoke £2.90 p.p. 95p, AT1025/06 Blue Lat. 90p p.p. 40p.**  
**PHILIPS G9 Signal Board Panels for small spares £4.80 p.p. £1.00.**  
**PHILIPS G6 Single standard convergence panels £2.90 p.p. £1.20.**  
**G8 Decoder panels salvaged £4.25. Decoder panels for spares £2.00 p.p. £1.35.**  
**VARICAP, U321, ELC 1043/06 £7.82, ELC 1043/05 £6.35 p.p. 45p., G.I. type (equiv. 1043/05) £4.00 p.p. 40p. Control units, 3PSN £1.40, 4PSN £1.75, 5PSN £2.00, 6PSN £2.10, Special Offer 6PSN £1.15 p.p. 40p.**  
**BUSH "Touch Tune" assembly, incl. circuit £5.75 p.p. 85p.**  
**VARICAP UHF-VHF ELC 2000S £9.80. BUSH TYPE £9.00 p.p. 85p.**  
**VARICAP VHF MULLARD ELC1042 £7.95 p.p. 45p.**  
**UHF/625 Tuners, many different types in stock. UHF tuners transisted, incl. s/m drive, £3.28. Mullard 4 position push button £2.88 p.p. £1.30.**  
**TRANSISTORISED 625 IF for T.V., sound, tested. £7.82 p.p. 75p.**  
**MULLARD EP9000 Audio Unit incl. LP1162 Module £4.38 p.p. 85p.**  
**LINE OUTPUT TRANSFORMERS. New gear. p.p. £1.00.**

BUSH 145 to 186SS series.....	£8.80	COLOUR LOPTS p.p. £1.25.	
BUSH, MURPHY A816 series.....	£9.80	R.B.M. A823.....	£6.60
DECCA 20/24, 1700, 2000, 2401.....	£8.50	R.B.M. 2179.....	£6.70
FERG., HMV, MARCONI, ULTRA		DECCA Bradford (state Model No.).....	£10.15
850 to 1580.....	£6.80	DECCA 80, 100.....	£9.50
GEC 2000, 2047 series, etc.....	£8.50	GEC 2028.....	£7.82
INDESIT 20/24EGB.....	£8.50	GEC 2040.....	£11.30
ITT/KB VC1 to 53, 100, 200, 300.....	£8.50	GEC 2110 Series.....	£12.20
MURPHY 1910 to 2417 series.....	£8.50	ITT CVC 5 to 9.....	£10.15
PHILIPS 19TG170, 210, 300.....	£8.50	ITT CVC 30 Series.....	£10.15
PYE, INVICTA, EKCO, FERR.		PYE 691-697.....	£20.50
368, 169, 569, 769 series.....	£8.50	PYE 697 PC.....	£20.50
<b>SPECIAL OFFER</b>		PYE 713-715.....	£7.85
GEC 2114/FINELINE.....	£5.50	PHILIPS G8, G9.....	£10.15
PYE 40, 67.....	£5.50	PHILIPS 570.....	£7.85
THORN 1590/1591.....	£5.50	THORN 3000/3500 SCAN, EHT.....	£7.85
THORN 3000/3500.....	£3.25	THORN 8000/8500.....	£14.80

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.T.S.  
 THORN 950 3 Stick Tray £1.15 p.p. 55p. Most others available.  
 THORN 3000/3500, 8000, 8500, MAINS TRANSF. £10.15 p.p. £1.60.  
 6-3V CRT Boost Transformers £5.00 p.p. 95p.

Telephone  
 01-794 8751/7346

CALLERS WELCOME AT SHOP PREMISES

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE  
 NOT NORMALLY ADVERTISED, ENQUIRIES INVITED

## MANOR SUPPLIES


172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159 pass door  
 W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)  
 W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.  
 ALL PRICES INCLUDE VAT AT 15%

**TRANSISTORS, ETC.**

Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)		
AC107	0.48	AU103	2.40	BC192	0.86	BC377	0.29	BD234	0.88	BF222	0.81	BFX29	1.62	MPSU05	0.66	MTX500	0.18	2N3819	0.47
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.39	BD235	0.83	BF224 & J	0.22	BR101	0.53	MPSU06	0.76	MTX502	0.22	2N3820	0.72
AC126	0.36	AU110	2.40	BC205*	0.39	BC440	0.52	BD236	0.83	BF240	0.32	BR103	0.64	MPSU55	1.32	MTX504	0.28	2N3866	1.08
AC127	0.54	AU113	2.60	BC206*	0.37	BC441	0.88	BD237	0.83	BF241	0.31	BR103	1.06	MPSU56	1.26	2N404	1.30	2N3904	0.20
AC128	0.46	BC107*	0.16	BC207*	0.39	BC461	0.78	BD238	0.68	BF244*	0.81	BRCA4443	1.76	MPSU60	0.82	2N698	0.46	2N3905	0.20
AC128K	0.55	BC108*	0.15	BC208*	0.37	BC477	0.30	BD239	1.58	BF245*	0.43	BRY39	0.60	MPU131	0.59	2N697	0.46	2N3906	0.20
AC141	0.86	BC109*	0.16	BC209*	0.39	BC478	0.28	BD410	1.65	BF254	0.48	BRYS6	0.44	OC26	1.49	2N706A	0.33	2N4036	0.94
AC141K	0.70	BC113	0.22	BC211*	0.39	BC479	0.33	BD433	0.65	BF255	0.88	BSS27	0.92	OC28	1.90	2N706	0.29	2N4123	0.17
AC142	0.60	BC114	0.22	BC212*	0.17	BC547*	0.13	BD436	0.70	BF256L*	0.49	BT108	1.50	OC29	1.80	2N814	0.32	2N4124	0.17
AC142K	0.68	BC115	0.24	BC212L*	0.17	BC548*	0.13	BD438	0.68	BF257	0.44	BT109	1.95	OC35	1.25	2N816	0.46	2N4126	0.17
AC151	0.31	BC116*	0.25	BC213*	0.16	BC549*	0.16	BD437	0.74	BF258	0.82	BT108	1.48	OC36	1.25	2N818	0.54	2N4236	2.20
AC152	0.36	BC117	0.30	BC213L*	0.16	BC550	0.24	BD438	0.76	BF259	0.82	BT119	5.18	OC42	0.50	2N830	0.29	2N4289	0.32
AC153	0.42	BC118	0.24	BC214*	0.18	BC556	0.23	BD439	0.88	BF262	0.73	BU102	3.35	OC44	0.88	2N1164	8.29	2N4292	0.32
AC153K	0.52	BC119	0.34	BC214L*	0.18	BC557*	0.16	BD520	0.68	BF263	0.88	BU105	1.80	OC45	0.83	2N1304	1.40	2N4416	0.85
AC154	0.41	BC125*	0.30	BC225	0.42	BC558*	0.16	BD599	0.87	BF270	0.47	BU105/02	1.96	OC70	0.85	2N1305	1.29	2N4444	1.00
AC176	0.45	BC126	0.30	BC237*	0.16	BC559*	0.17	BD600	1.23	BF271	0.42	BU108	2.98	OC71	0.73	2N1306	1.49	2N4921	0.80
AC178	0.81	BC132	0.20	BC238*	0.16	BCY10	0.30	BD663BR	0.86	BF272A	0.80	BU126	2.91	OC72	0.73	2N1307	1.32	2N5042	1.65
AC179	0.85	BC134	0.22	BC239*	0.22	BCY30A	1.06	BDX18	1.55	BF273	0.33	BU204	2.80	OC81	0.83	2N1308	1.53	2N5060	0.28
AC187	0.86	BC135	0.21	BC251*	0.25	BCY32A	1.19	BDX32	2.95	BF274	0.34	BU205	2.88	OC81D	0.95	2N1711	0.47	2N5081	0.30
AC187K	0.86	BC136	0.25	BC252*	0.26	BCY34A	1.02	BDY16A	0.63	BF336	0.83	BU206	2.99	OC139	1.30	2N1893	0.52	2N5084	0.63
AC188	0.52	BC137	0.15	BC253*	0.38	BCY72	0.27	BDY16B	0.63	BF337	0.88	BU206	2.71	OC140	0.87	2N1912	0.71	2N5085	0.49
AC188K	0.61	BC138	0.25	BC261A*	0.28	BD115	1.35	BDY20	2.29	BF338	0.88	BU407	1.98	OC170	0.80	2N2017	0.55	2N5087	0.80
AC193K	0.70	BC140	0.36	BC262A*	0.28	BD123	1.50	BDY36	1.38	BF355	0.72	BU77	2.50	OC171	0.80	2N2216	0.38	2N5208	0.89
AC194K	0.74	BC141	0.44	BC263*	0.26	BD124	1.85	BF115	0.48	BF356	0.49	CI06D	0.80	OC200	3.25	2N2219	0.42	2N5294	0.86
ACY17	1.20	BC142	0.35	BC267*	0.20	BD130Y	1.66	BF117	0.45	BF363	0.49	CI06F	0.43	OC201	3.95	2N2221A	0.26	2N5296	0.68
ACY19	0.95	BC143	0.38	BC268*	0.28	BD131	1.66	BF120	0.55	BF367	0.29	CI11E	0.46	OC202	2.40	2N2222A	0.41	2N5298	0.68
ACY28	0.88	BC147*	0.12	BC286	0.40	BD132	0.88	BF121	0.85	BF451	0.43	D40N1	0.64	OC205	3.95	2N2389A	0.40	2N5322	1.16
ACY39	2.02	BC148*	0.12	BC287	0.49	BD133	0.70	BF123	0.48	BF457	0.46	E300	0.42	OC271	1.98	2N2401	0.80	2N5449	0.18
AD140	1.79	BC149*	0.13	BC291	0.27	BD135	0.37	BF125	0.88	BF458	0.49	E1222	0.47	ON236A	0.94	2N2484	0.35	2N5457	0.46
AD142	1.90	BC152	0.42	BC294	0.37	BD136	0.38	BF127	0.81	BF459	0.82	E5024	0.19	RM028B	2.72	2N2570	0.74	2N5458	0.40
AD143	1.79	BC153*	0.42	BC297	0.36	BD137	0.40	BF127F	0.78	BF459A	0.16	GE18	0.48	R2010B	2.79	2N2646	0.82	2N5459	0.88
AD149	1.42	BC154	0.41	BC300*	0.62	BD138	0.42	BF152	0.62	BF594	0.16	GE18	0.48	R2010B	2.79	2N2646	0.82	2N5459	0.88
AD161	0.66	BC157*	0.13	BC301	0.38	BD139	0.46	BF158	0.25	BF597	0.27	MF040A/02	0.18	R2323	0.85	2N2889	2.08	2N5496	1.08
AD161/162	1.22	BC158*	0.12	BC302	0.86	BD140	0.50	BF159	0.27	BF599	0.30	ME6001	0.18	ST2110	0.48	2N2894	0.45	2N6207	0.55
AD162	0.71	BC159*	0.14	BC303	0.64	BD144	2.24	BF160	0.20	BF640	0.28	ME6002	0.18	ST6120	0.48	2N2904*	0.40	2N6107	0.71
AF114	0.35	BC160	0.52	BC304	0.44	BD145	0.75	BF161	0.84	BF641	0.30	MJ2955	1.30	TIC44	0.25	2N2905*	0.39	2N6122	0.60
AF115	0.35	BC161	0.58	BC307*	0.17	BD150A*	0.81	BF163	0.65	BF642	0.29	MJ3000	1.58	TIC46	0.35	2N2906*	0.38	2N6178	0.70
AF116	0.41	BC167B	0.15	BC308*	0.14	BD155	0.90	BF164	0.95	BF652	0.33	MJ340A	0.88	TIC47	0.45	2N2926G	0.15	2N6180	1.39
AF117	0.42	BC168B	0.14	BC309*	0.18	BD167	0.81	BF166	0.80	BF652	0.29	MJ341	0.72	TI29A	0.47	2N2926G	0.14	2N6211	2.74
AF118	0.88	BC169C	0.15	BC310*	0.15	BD168	0.78	BF167	0.35	BF662	0.28	MJ370	0.74	TI30A	0.80	2N2926Y	0.14	2N6211	4.28
AF121	0.88	BC170*	0.15	BC315*	0.15	BD169	0.98	BF173	0.35	BF679	0.30	MJ371	0.79	TI31A	0.81	2N2955	1.12	2N6458C	0.78
AF124	0.58	BC171*	0.15	BC319*	0.19	BD169	2.89	BF177	0.55	BF680	0.29	MJ372	0.87	TI31C	0.87	2N3052	0.48	2N6458C	2.28
AF125	0.38	BC172*	0.14	BC320	0.17	BD183	0.67	BF178	0.48	BF681	0.30	MJ521	0.95	TI32A	0.86	2N3054	0.66	2N6458C	1.80
AF126	0.36	BC173*	0.22	BC321A&B	0.18	BD165	0.86	BF179	0.58	BF688	0.42	MJE2955	1.20	TI32C	0.72	2N3055	0.72	2N6459	1.45
AF127	0.86	BC174A & B	0.26	BC322	0.28	BD166	0.86	BF180	0.53	BF741	0.48	MJE3000	1.95	TI33A	0.77	2N3250	0.52	2N61172Y	3.55
AF139	0.58	BC176	0.20	BC323	1.15	BD175	0.85	BF181	0.53	BF743	0.55	MJE3055	1.22	TI34A	0.84	2N3254	0.58	2N6234	1.48
AF147	0.52	BC177*	0.22	BC327	0.18	BD177	0.58	BF182	0.44	BF744	1.02	MPF102	0.40	TI41A	0.70	2N3391A	0.38	3N128	1.60
AF149	0.45	BC177*	0.20	BC328	0.16	BD178	0.92	BF183	0.52	BF745	0.92	MPS3702	0.33	TI42A	0.82	2N3633	0.80	4050	0.98
AF178	1.35	BC178*	0.22	BC337	0.17	BD181	1.94	BF184	0.44	BF746	0.19	MPS3705	0.30	TI2955	0.77	2N3703	0.17	40251	1.14
AF179	1.38	BC179*	0.28	BC338	0.17	BD182	2.10	BF185	0.42	BF747	0.20	MPS6521	0.38	TI2955	0.88	2N3704	0.19	40257	0.87
AF180	1.35	BC182*	0.15	BC340*	0.19	BD183	1.34	BF186	0.42	BF748	0.88	MPS6523	0.38	TI543	0.44	2N3705	0.17	40361	0.48
AF181	1.33	BC182L*	0.15	BC347*	0.17	BD187	2.30	BF187	0.14	BF749	0.38	MPS6566	0.44	TI590	0.33	2N3706	0.16	40362	0.50
AF186	1.48	BC183*	0.14	BC348A & B	0.18	BD187	2.30	BF195*	0.13	BF754	0.38	MPSA05	0.30	TI590	0.33	2N3707	0.16	40410	0.94
AF202	0.27	BC183L*	0.14	BC349B	0.17	BD188	1.28	BF196	0.14	BF750	0.38	MPSA06	0.32	TI591	0.28	2N3708	0.17	40429	0.88
AF239	0.73	BC184*	0.15	BC349B	0.17	BD189	0.71	BF197	0.15	BF751	0.37	MPSA55	0.43	ZTX108	0.14	2N3715	1.70	40530	0.79
AF240	1.40	BC184L*	0.15	BC350*	0.22	BD222	0.91	BF198	0.29	BF752	0.36	MPSA56	0.46	ZTX109	0.16	2N3771	2.09	40595	1.39
AF279S	0.91	BC185	0.36	BC351*	0.24	BD225	0.91	BF199	0.29	BF753	0.36	MPSA93	0.56	ZTX213	0.23	2N3772	2.08	40603	1.13
AL100	1.30	BC186	0.25	BC352A*	0.24	BD232	0.												

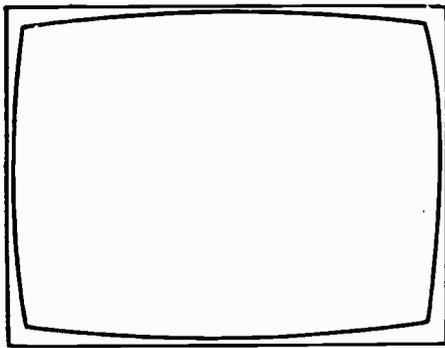

# TELEVISION

## EDITOR

John A. Reddihough

## ASSISTANT EDITOR

Luke Theodossiou

## ART EDITOR

Roy Palmer

## ADVERTISEMENT MANAGER

Roy Smith

01-261 6671

## CLASSIFIED ADVERTISEMENTS

Colin R. Brown

01-261 5762

## THE LLJ COLUMN

The good folk of Gravesend – and their TV sets – kept Les Lawry-Johns rather busy during the Christmas period, when this issue was being put together. Never fear, he'll be back again next month.

## We don't need no educashun

Education is one of those things about which everyone claims to be something of an authority. After all, we all get involved in it at least once in our lives. It's not a subject we often comment upon in these pages, though when we do we usually receive a few quick brickbats since one of the things teachers seem to have plenty of time for is writing letters to editors. That should get a few of 'em going for a start.

OK, so what business is it of ours? Well, we're concerned with industry and its welfare, things on which the state of the country largely depend, and education/training are key aspects in industrial development. A number of questions can be put to the educationalists then. How, for a start, do you manage to turn out a proportion of illiterates after several years' schooling? That's an unfair question perhaps, since the educational industry's input must inevitably include some rather unpromising material.

"Educational industry?" Well yes, it's one of the service industries really, isn't it? Certainly there's an input and an output, a lengthy and rather expensive process intervening between the two. So the real questions are does society get value for the investment it makes, and is the product wanted/relevant/usable?

Oh dear, oh dear! That's not the way to look at it at all, is it? Education is an end in itself, something to which we all have a right – advanced education too, according to a car sticker I saw only the other day. That's the extreme opposite view, and we'd go along with it to some extent, emphasizing only that a balance has to be struck between these ways of looking at things, and that if education really is as all important as those involved in it are apt to maintain then its effects on our society and economy are things that must be kept under review.

So, are we directing our investment in education to the best advantage? Does the educational process cost too much and take too long? Are we getting the right mix of arts/science/management etc. output? One thing that has never ceased to stagger me personally is the number of people who attain high qualifications in some subject or another and then go on to do something totally different, sometimes though not always due to limited opportunities. This isn't a case of one or two isolated examples: it seems to happen quite often, and leads one to ask whether something somewhere might be a little wrong? You can't get the equation exactly right of course. Only in a rather nasty sort of totalitarian society could you decide exactly who studied what for how long, then ensure that professions are followed come what may. It wouldn't work very well either. But it does tend to raise the question as to what education is *for*?

These questions are not new of course. So long as I can recall there's been concern about too many/few scientists, doctors, arts graduates and so on. One thing that everyone's been sure about is that we've always produced too few engineers. It would be ironical if we got this right just when there's little engineering left to be done as a result of our economic decline.

It's easy to ask awkward questions and to point out deficiencies. Technical magazines tend to have something of a vested interest in the educational system's shortcomings, since they survive in part through filling the gaps in the formal educational system. In fact there exist side by side formal and informal educational systems, technical journalism forming part of the latter. This means that journalists share some of the educationalists' problems – in acquiring and putting over knowledge, especially where a fast developing technology is concerned. One advantage the journalist possibly has is that through operating in an informal way he can see these common problems in a different light.

Let's consider educational taste for example. Educational what? Well, taste plays a major role in most aspects of life, so why not in education? Some, especially the extroverted, find that they do best in a class, learning on a group basis. Interaction and questioning and so on and so forth. Others may find it difficult to get anywhere unless left largely to their own devices. Between these extremes there no doubt lies a wide range of educational tastes, and the problem is can a formal educational system even begin to cater for them?

This and our other questions are not the sorts to which simple answers are possible. They are nevertheless worth asking. Especially as one has this feeling that education could and should have been doing rather better than it has, and that some at any rate of our misfortunes are due to educational failings that have persisted over a very long period of time. Shove up the shutters someone quick, and let's see what response we get!



instability goes, well and good. If not, check the screening between the input and output circuits – ensure that the soldering to the tinplate subchassis is good at all points. It should go without saying that all connections should be kept as short as possible.

### Results

In these days of low-noise tuners, a preamplifier makes a less dramatic improvement than in the days of PCC84/PCF80 tuners-cum-noise generators (for DX use they didn't need a preamplifier so much as a predriver). A good increase in sensitivity/decrease in picture noise was nevertheless noted. Using an audio tone from a good quality signal generator, the signal could be heard down to  $0.5\mu\text{V}$  without the preamplifier: with the preamplifier in circuit, the tone could still be heard very weakly at  $0.1\mu\text{V}$ ! The tuning peak is fairly broad, and no problems should be found when tuning across Band III in a hurry.

Although the prototypes were built for set-side use, a masthead version could be employed, with suitable weatherproofing to house the unit. A third wire will have to be run up the mast for the tuning voltage – ensure good

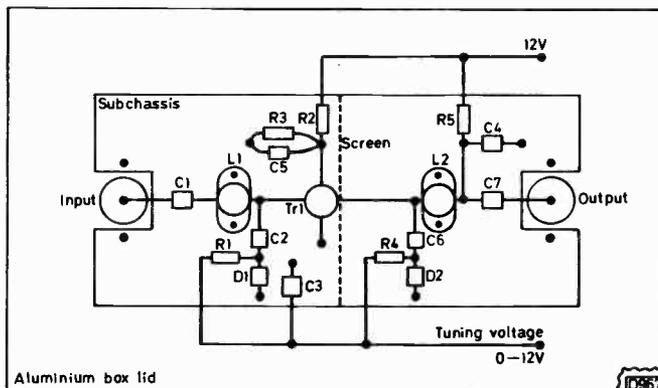


Fig. 3: Suggested layout.


decoupling of the tuning voltage at the amplifier end, as the line can be a source of hum/shortwave breakthrough.

Band III is rather neglected by DXers, which is a great pity. Using a good aerial, it's surprising what can be received on a daily basis over the noise – let alone what can be received when the conditions are good. A colleague observed Arabic SpE signals in Band III last July. ■



All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.

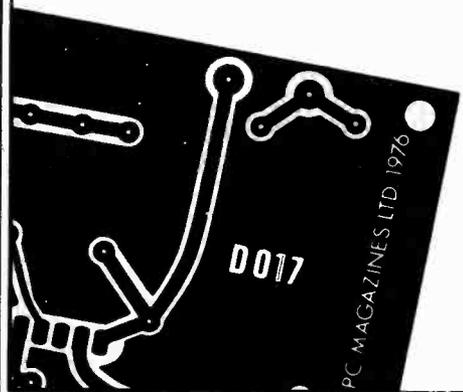Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.



# TELEVISION READERS PCB SERVICE

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£3.85 per set
March 1977	Teletext Decoder Power Supply	D022	£3.75
May 1977	Teletext Decoder Input Logic	D011	£12.50
June 1977	Wideband Signal Injector	D031	£1.00
June 1977	Teletext Decoder Memory	D012	£10.50
July/Aug 1977	Teletext Decoder Display	D013	£11.00
September 1977	Teletext Decoder Switch Board	D021	£1.75
April/May 1978	CRT Rejuvenator	D046	£3.00
October 1978	Colour Receiver PSU Board	D052	£4.00
January 1979	Colour Receiver Signals Board	D053	£10.75
February 1979	Commander-8 Remote Control System	D054/5	£6.00 per set
March 1979	Colour Receiver Timebase Board	D049	£17.13
July 1979	Colour Pattern Generator	D062	£14.50
		D063	£9.15
September 1979	Teletext Decoder Options Board	D064	£8.50
August 1979	Teletext Decoder New Mother Board	D065	£6.00
August 1979	SimpleSync Pulse Generator	D067	£4.00
September 1979	New Teletext Signal Panel	11331	£8.00
October 1979	Teletext Keyboard	D057	£3.50
October 1979	Teletext Interface Board	D058	£5.00
November 1979	Colour Receiver Remote Control	D066	£5.00
January 1980	Remote Control Preamplifier	D061	£3.75
February 1980	Teletext/Remote Control Interface	D070	£9.50
February 1980	LED Channel Display	D071	£4.00
March 1980	Improved Sound Channel	D072	£3.25
May 1980	Monochrome Portable Signals Board	D074	£6.25
June 1980	Monochrome Portable Timebase Board	D075	£7.75
July 1980	Monochrome Portable CRT Base Board	D076	£1.00
Sept/Oct 1980	New CTV Signals Panel	D077	£9.50
January 1981	Small-screen Monitor Board	D078	£8.50
December 1980	Video Camera Pulse Generator Board	D079	£4.50
December 1980	Video Camera Video/Field Timebase Board	D080	£5.50
January 1981	Video Camera Power Supply Board	D082	£2.00
January 1981	Video Camera Line Timebase/H.T. Board	D083	£4.00

To: Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.

Please supply p.c.b.(s) as indicated below:

Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Post Code \_\_\_\_\_

# Letters

## TRANSISTOR TESTS

In connection with S. Simon's comments in the January issue on carrying out conduction tests on transistors, I'd like to point out that not everyone will be using an AVO Model 8 and that different meters, even if of a similar specification to the AVO 8, can give totally different results. For example, with my USSR made  $20k\ \Omega/V$  meter on the low-resistance range all silicon transistors read open-circuit, regardless of polarity. Forward biased junctions of typical germanium transistors such as the AC128/AC178 etc. all read about  $70\ \Omega$ . On the next resistance range, normal silicon transistors read  $100\ \Omega$  for the BC108 etc.,  $120\ \Omega$  for the BF194/5/7 types and  $250\ \Omega$  between the emitter and collector of a BF196.

None of this matters as long as you know your meter, but the beginner could easily be confused, especially if he takes S. Simon's notes to mean for instance that a BF196 which does not read between  $50\text{-}100\ \Omega$  is therefore faulty.

Alan J. Gamble,  
Ormskirk, Lancs.

*Editorial note:* The AVO Model 8 was quoted because it's generally regarded as a sort of "standard" for television servicing. Alan Gamble's warning is important, and we suggest that those using other meters regularly should try them out on known good transistors of various types in order to check on the sorts of readings they should expect to get when making such tests.

## VINTAGE MATTERS

Writing about the pre-war HMV Model 901 in the *Letters* column in your December issue, E. Kendal says "there were no ferrites that could operate at 45MHz in those days". There were dust cores however, and these were a neater solution than brass eddy-current slugs. I expect that many readers now approaching retirement age will remember the Pye r.f./i.f. 45MHz strips which, by coincidence, were mentioned by Chas E. Miller in the same issue. The coil formers used in these strips – also available separately – were in my opinion the most convenient the experimenter ever had. They were grooved to keep the turns of the winding at a constant spacing, and had two full-length fins drilled with holes to secure the ends of the winding(s). As long as we had these formers, I almost enjoyed winding v.h.f. coils.

I was told, and think it to be true, that the Pye strips were originally designed as vision r.f. strips for use with the pre-war Alexandra Palace TV transmissions, and were called up as it were for wartime service as radar i.f. strips – hence the frequency.

The EF50 was certainly a notable valve. Unlike later styles of all-glass valves the pins were stiff, and after a period of use it was common to find cracks radiating from them. I don't recall finding one that had lost its vacuum however. The original EF50s were painted red, but the VR91 services equivalent was usually unpainted. Another still remembered war-winner was the VR65, a 6.3V version of the Mazda SP41. Both the VR65 and the VR91 were used in large quantities, supplies being reinforced by

manufacture in the US and Canada – if I remember correctly, the US-made VR91s were marked Sylvania. The nearest US type was the 6AC7/1852, a metal valve. But US radar equipment, unlike British, contained a lot of twin triodes – the 6SN7GT. As Chas E. Miller says, British practice was to use high-slope pentodes in as many positions as possible. This was partly in pursuance of the policy of using high gain and feedback to obtain predictable and accurate performance. The immediate successor to both of these British high-slope pentodes was the CV138, which later became known commercially as the EF91 etc. This type, and improved versions of it, remained an Inter-Service standard until the end of the valve era.

E. F. Good,  
Darlington, Co. Durham.

## PUSH BUTTON REPAIRS

S. Simon's article on tuning troubles in the November issue prompts me to write regarding the repair of the push buttons used on certain Rank TV sets. The point made about these buttons in the article is that the star shaped hole in the plastic wears to become a round hole, with the result that the button can no longer be used to rotate the spindle for tuning purposes. The answer to this problem is very simple, and doesn't require sticky adhesives which can leave an awful mess. Go to your nearest stockist of plastic Rawlplugs. You'll find that the ends of these are star shaped while the body diameter is tapered. So all you need to do is to cut off the required length and push it into the hole in the button, which is then as good as new. Ten plugs cost about 10p – they must be of the type that's star shaped at the end.

Roy Martin,  
Belfast.

## MISLEADING SYMPTOMS

A recent fault we had on an ITT colour set fitted with the CVC9 chassis and Feathertouch tuning could cause confusion. The fault itself was simple enough – the 100mA fuse F1c in the 12V stabiliser circuit (see Fig. 1) on the Feathertouch panel had gone open-circuit. But the symptoms were a dim picture with excessive sound and vision noise. Channel changing was not affected. The cause of these misleading symptoms was the fact that some voltage was still present on the 12V line – obtained from the 20V l.t. line via R1c, T1c and the base-emitter junction of T2c. So before you start chasing around the aerial, tuner and a.g.c. departments when you come across this situation, check the fuse. The set does give one clue: the channel indicator lamps don't light up.

A. Mole,  
London, W4.

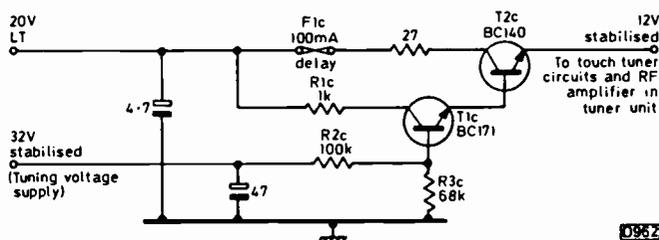


Fig. 1: The 12V stabiliser circuit on the Feathertouch tuning panel used in some versions of the ITT CVC9 chassis. When F1c goes open-circuit there's still some voltage on the 12V rail, via R1c, T1c and the base-emitter junction of the series regulator transistor T2c. This can cause misleading symptoms. There are two fuses with the reference number F1c in these sets, the other one being the mains fuse.

ARE YOU IN THE DARK?  
...ABOUT OUR

## COLOUR T.V. PANEL EXCHANGE REPAIR SERVICE



FULL RANGE OF  
THORN · RBM · PHILIPS  
PYE · INVICTA · GEC  
DECCA · TELPRO  
AND MANY OTHER MAKES

90 DAY GUARANTEE ON ALL REPAIRS  
SAME DAY POSTAL SERVICE

We employ a large skilled Staff, who utilise some of the most sophisticated Test equipment available, inclusive of AUTOMATIC FAULT FINDING COMPUTERS together with specially designed SERVICING JIGS which in short means to you –

HIGH QUALITY REPAIRS – AT LOW COST



ONE OFF  
OR



100 OFF · NO ORDER TOO  
LARGE OR SMALL

SEND FOR PRICE LIST

SEND FOR CATALOGUE  
BLOCK DISCOUNTS FOR TRADE CONTRACTS

TO

**Campbell Electronics Ltd.**

Unit 5, Heath Hill Estate, Dawley, Telford, Shropshire TF4 2RH.  
Telephone: Telford (0952) 502422. Telex 35191 Chamcon

BUILD  
AND LEARN

Kits which have PROVED themselves!

## Forgestone 500 TELETEXT

High quality colour television receiver


NEW INFRA-RED FULL FEATURE REMOTE CONTROL TELETEXT

- ★ Pin diode tuner
- ★ Glass epoxy printed circuit panels
- ★ Full technical construction manual
- ★ Hi-Bri tube
- ★ Eleven integrated circuits
- ★ Ready built and aligned IF module
- ★ High quality components
- ★ Modern cabinets
- ★ All solid state
- ★ Fully isolated and protected power supply
- ★ Diode split L.O.P.T.
- ★ Low consumption

THE ULTIMATE in large screen 22" and 26" television receiver kits. Deluxe full spec. Teletext, 7 channel + VCR. Also video and audio in/out. 6 models in the 500 range.

Buy as you build. All Forgestone Kits are for the constructor of today, sections of the Kit are available separately. Please send stamp for further details of these quality products.

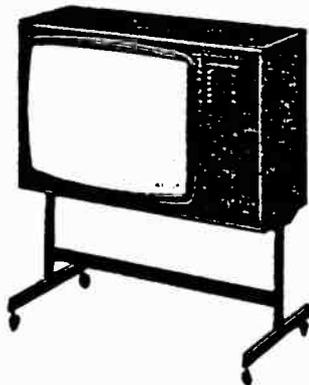Telephone or Mail Orders accepted on Access/Barclaycard



**forgestone  
colour developments  
limited**

Ketteringham, Wymondham,  
Norfolk, NR18 9RY  
Telephone: Norwich (0603) 810453

# Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs – and they can do the same for you.

Fill in the coupon below and find out how!

**There is a wide range of courses to choose from, including:**

### City and Guilds Certificates:-

Telecommunications Technicians,  
Radio, TV and Electronics Technicians,  
Electrical Installation Work,  
Technical Communications,  
Radio Amateur,  
MPT General Radio Communications  
Certificate.

### Diploma Courses:-

Electronic Engineering,  
Electrical Engineering,  
Computer Engineering,  
Radio, TV, Audio Engineering, Servicing and  
Maintenance. (inc. Colour TV)  
New Self-Build Radio Courses with Free Kits

### Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

### The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful – at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name .....

Address.....

..... Phone No: .....

**ICS**

International Correspondence Schools,  
Dept. 285D, Intertext House,  
LONDON SW8 4UJ. Tel 622 9911  
(all hours)

# P.V. TUBES

38A WATER STREET  
ACCRINGTON LANCs BB5 6PX

SUPPLIERS OF TELEVISION COMPONENTS

Telephone: Accrington (0254) 36521

TRADE COUNTER OPEN MON-FRI 9a.m.-4.30p.m.  
SAT. MORN. 9.30a.m.-12 NOON.

PLEASE ADD 15% VAT TO ALL PRICES

### NEW MONO TUBES

Mullard A31/510 12" 110"	£17 00
Mullard A34/510 14" 110"	£18 50
Hitachi A31/300 12" 110"	£15 00
Vega 12" 90"	£15 00
Vega A50/120 20" 110"	£13 50
Vega A61/120 24" 110"	£15 00

1 year warranty except Mullards which have 2 years warranty.

### REBUILT COLOUR TUBES

17" 18", 19" 20"	£28 00
22"	£30 00
25", 26"	£34 00
26" 110"	£36 00

Glass for glass exchange  
2 year warranty.

### MULLARD COLOUREX/OR THORN NEW LIFE

18"	£54.50
19"	£46.00
20"	£50.00
22"	£40.00
25"	£52.00
26"	£55.00
26" 110"	£55.00

Glass for glass exchange  
1 year warranty & 4 year optional.  
Carriage incl. VAT on carriage

**MONO** £5 00  
**COLOUR** £5 00  
**PORTABLE** £3 50

### NEW VALVES

30FL2	121	EY86/7	68	PCL84	81
DY802	72	EY50DA	133	PCL85/805	79
DY86/7	66	E280/1	56	PCL86	81
ECC81	60	GY501	145	P0500	293
ECC82	60	G234	156	PL200	135
ECC83	60	KT66	698	PL36	115
ECC84	80	KT88	1000	PL81	94
ECC85	98	PC86	81	PL82	46
ECC88	135	PC88	81	PL83	143
ECC89	80	PC92	80	PL84	84
ECC92	88	PC97	114	PL95	100
ECH81	104	PC90	80	PL504	132
ECH84	113	PC84	70	PL508	143
ECL80	84	PC85	85	PL509	239
ECL82	77	PC88	82	PL519	278
ECL86	84	PC89	79	PL802	215
ECL88	78	PC189	102	PY33	61
EFR80	68	PC805	140	PY88	81
EFR85	68	PCF80	75	PY50DA	140
EFR86	119	PCF86	113	PY800/1	69
EFR89	148	PCF200	123	UCF80	67
EF183	68	PCF800	138	UCH81	143
EF184	88	PCF801	113	UCL82	84
EH90	102	PCF802	86	ULC83	94
EL34	163	PCF805	163	UL84	102
EL81	86	PCF806	130	U26	130
EL84	68	PCF808	163	U191	95
EL90	82	PCH200	145	6F23	85
EL509	222	PCL82	78	UY85	80
		PCL83	200		

All valves are now based - guaranteed.  
Please add 15% VAT to ALL items

### RECTIFIER TRAYS

Thorn 950	£4 25	GEC 2110 before Jan '77	£6 95
Thorn 1500/1580	£3 85	GEC 2110 after Jan '77	£6 85
Thorn 1500 5 stuck	£4 25	GEC 1028, 2028, 1040	£5 64
Thorn 1800	£3 45	ITT/KB CVC5/7/8/9	£5 35
Thorn 3000/3500	£6 89	ITT/KB CVC20/25/30	£5 35
Thorn 1400	£3 85	Korting (similar to Siemens TVK1)	£6 65
Thorn 8000	£3 51	Philips 3113 550/1/3	£5 85
Thorn 8000/8800	£5 40	Philips 68	£5 85
Thorn 9000	£7 43	Philips 69	£6 33
Decca CIV 19/25	£5 35	Pye 691/25	£5 13
Decca CS1730/3, CS1830/5	£3 68	Pye 731/25	£5 40
Decca 1910 Bradford	£5 92	Rank BM A823/2179	£5 78
Decca 80	£5 92	Rank BM A823 A/V	£6 09
Decca 100	£6 28	Rediffusion MK1	£6 84
	£6 04	RRC 2000	£6 80
		"Universal Tripler"	£5 60

### TRANSFORMERS

#### LINE OUTPUT TRANSFORMERS

Type	Price (p)
Bush A774	£11.75
Replacement Tripler for A774	£10.75
Decca 80	£8.58
Decca 100	£8.58
Decca 1730	£8.58
Decca 2230	£8.58
GEC 2040	£9.20
GEC 2110	£8.59
ITT CVC 25/30/32	£7.80
Philips 68	£10.00
Philips 69	£7.15
Philips G11	£13.50
Pye 691/693	£14.00
Pye 697	£14.00
Pye 731	£10.15
Thorn 3500	£5.00
Scan AC EHT Transformer	£9.00
Thorn 8000	£10.00
Thorn 8500	£10.00

#### MAINS TRANSFORMER

Type	Price (p)
Thorn 3000/3500	£10.50

#### PYE LABGEAR

Most Head Amp WB 12V	£12.25
28db gain	£1.00
Power Unit for above	£11.25
Behind the Set second set amp	£10.08
Behind the Set UHF amp (mains)	£10.73
Teletext Adaptor (Colourcast)	£28.00
VHF/UHF 8-1 distribution amp	£32.35

### MAINS CROPPERS

Type	Price (p)
Decca 20 Decca 20 Series	£1 10
GEC 2018	70
Philips 210/5050	66
Philips GB 5081	35
Philips GB 5083	56
Pye 725	53
RBM 161	55
RBM A823	77
Thorn 1500	96
Thorn 2500	68
Thorn 8000	86
Thorn 8500	83

### PREFERRED VALUES RESISTORS

WIREWOUND	Price Each (p)
4 watt 1 ohm-1.5kohm	15
2.2k 3.3k	17
4.7k 6.8k	19
10k	24
7 watt 1 ohm-4.7kohm	16
5.6k 12k	17
15k 22k	18
1 ohm-6.8kohm	20
10k-15k	23
22k	20
17 watt 1 ohm-10kohm	26
15k, 22k	27

### SEMICONDUCTORS

Type	Price (p)	Type	Price (p)	Type	Price (p)
AC126	22	BC212	9	BF160	27
AC127	22	BC212L	9	BF167	24
AC128	20	BC213	9	BF173	22
AC128K	32	BC213B	10	BF178	26
AC141K	34	BC213L	9	BF179	28
AC142K	30	BC214	9	BF180	36
AC176	25	BC214L	10	BF181	36
AC176K	32	BC237	9	BF182	30
AC187	26	BC238	8	BF183	30
AC187K	28	BC251A	12	BF184	30
AC188	25	BC251B	15	BF185	30
AC188K	37	BC252A	12	BF194	11
AD140	75	BC252B	12	BF195	10
AD143	82	BC261A	18	BF196	10
AD149	79	BC261B	15	BF197	11
AD161	42	BC262A	15	BF198	15
AD161/2	£15	BC262B	15	BF199	15
AD162	42	BC300	30	BF200	30
AF124	34	BC301	28	BF224	16
AF127	32	BC303	28	BF241	21
AF139	42	BC307	28	BF242	46
AF239	45	BC307A	10	BF258	26
AL102	£20	BC327	11	BF259	26
AL103	£20	BC328	8	BF271	12
AL110	£20	BC337	11	BF273	12
AL113	£14	BC338	9	BF274	13
BC107	11	BC546	30	BF336	36
BC107A	12	BC547	7	BF337	30
BC107B	13	BC547A	10	BF338	34
BC108	11	BC548	10	BF355	37
BC108A	12	BC549	7	BF362	37
BC108B	12	BC550	7	BF363	37
BC108C	14	BC557	7	BF371	30
BC109	11	BC558	7	BF457	23
BC109A	14	BC772	13	BF458	24
BC109B	13	BD115	30	BF459	35
BC109C	11	BD116	65	BF472	28
BC114	12	BD124P	60	BF473	27
BC116A	12	BD124=2N3054		BFW10	60
BC140	32	BF131	33	BFX29	30
BC141	26	BF132	35	BFX84	27
BC142	21	BF133	40	BFX85	28
BC143	24	BF135	28	BFX86	28
BC147	9	BF136	27	BFX88	25
BC148	9	BF137	23	BFY50	23
BC149	9	BF138	23	BFY51	20
BC157	11	BF139	28	BFY52	20
BC158	9	BF140	30	BFY90	75
BC159	10	BD144	£120	BR100	17
BC180	25	BD182	70	BR101	30
BC181	28	BD183	65	BR4443	80
BC1708	10	BD201	85	BRX46 (TIC46)	40
BC171	9	BD202	80	BRY39	30
BC171A	10	BD203	80	BT106	£100
BC171B	10	BD204	84	BT108	£124
BC172	9	BD222	46	BT116	£121
BC172A	10	BD225	47	BU104	£200
BC172B	10	BD232	45	BU105	£125
BC172C	10	BD233	35	BU105/02	£165
BC173B	12	BD234	31	BU108	£150
BC174B	10	BD235	31	BU108	£180
BC182	9	BD236	31	BU124	£130
BC182LB	10	BD237	31	BU128	£149
BC182A	12	BD238	33	BU204	£150
BC183LA	10	BDX32	£150	BU205	£134
BC184	9	BDY20	20	BU208	£180
BC184LA	10	BF115	35	BU208	£180
BC204	9	BF127	26	BU208A	£165
BC208	13	BF154	12	BU208/02	£200
BC209	10	BF158	18	BU308	£175

### SEMICONDUCTORS

Type	Price (p)	Type	Price (p)	Type	Price (p)
CA3026A	£1 42	CA3065/ET76016/	£2 20	TBA120U	£1 00
BU407	£1 25	ML2328	£2 20	TBA396	£1 00
E12222	28	ETTR8016/	£1 00	TBA4800	£1 25
MJE340	44	ML2318	£2 20	TBA510	£3 00
MJE520	40	MC1307	£1 00	TBA5200	£1 20
OC71	27	MC1327	£1 00	TBA5300	£1 20
OC79	15	MC1349	£1 20	TBA5300	£1 28
R20088	£1 80	MC1351	£1 00	TBA5400	£1 49
R20108	£1 80	MC1352	£1 00	TBA5500	£1 58
R2265	£1 40	SAS5005	£1 80	TBA5600D	£1 59
R2322	58	SAS5705	£1 80	TBA5700	£1 00
R2323	67	SL9018	£4 45	TBA7500	£1 39
R2461	10	SL9178	£6 25	TBA8000	89
R2540	£2 80	SL1310	£1 80	TBA810AS	£1 35
RCA16334	90	SL13270	£1 20	TBA920	£1 80
RCA16335	80	SN7603N	£1 75	TBA9200	£1 99
TIP29C	43	SN76013N	£1 15	TBA9900	£1 49
TIP30C	43	SN76013N0	£1 15	TCA2700	£1 20
TIP31C	41	SN76023N	£1 45	TCA2700S	£1 25
TIP32C	42	SN76023N0	£1 53	TCA800	£1 99
TIP41C	28	TIP41C	46	TCA940	£1 60
TIP42C	47	SN76110N	89	TOA1170	£1 99
TIP2955	90	SN76131N	£1 30	TOA2030	£2 80
TIP3055	12	SN76228N	£1 50	TD2522	£2 40
(SEP3055)	63	SN76227N	£1 10	TD2640	£2 50
TV106/02	£1 20	SN76532N	£1 50	TD2690	£1 00
2N696	21	SN76533N	£1 30	TBA841/B11	£1 50
2N7905	22	SN76544N	£1 35	TBA950	£2 40
2N3054	60	SN76650N	70	TBA2532	£2 95
2N3055	60	TAA550	28	TD2600	£3 25
2N3702	11	TAA570	£1 80	TD2540	£3 15
2N3703	10	TAA881B	£1 20	TD2560	£2 95
2N3704	10	TAA700	£1 30	TD2591	£2 75
2N3705	10	TBA120B	£1 70	SN76220N	95
2N3706	10	TBA120S	69	TA717P	£1 80
2N5294	38	TBA120AS	£1 20	TA7172P	£1 80
2N5296	48	TBA120SQ	79	TA7173P	£1 44
2N5298	38			TA7074P	£1 00
2N5496	53			TA7178P	75
ZSC643A	£1 50			TA300	56
ZYSC1172Y	£2 20			TA310	50

### SOCKETS

Crystal	20	8 pin	24
4.43MHZ	£1 30	14 pin	18
		16 pin	20
		14 Out/Dual	24

### THERMISTORS

VAT104	52	14 Oh/Dual	24
VAB850	45		

### WELLER

Hot Gun	£10.50
Hot Gun Kit	£13.00
Min. Sold Iron	£5.20
Cordless Solder	
Iron	£22.00

### SOLDER

50/40 Alloy	18SWG	£8.85
Hot Gun	£10.50	
Hot Gun Kit	£13.00	
Min. Sold Iron	£5.20	
Cordless Solder		
Iron	£22.00	

### ELECTRONIC TUNERS and ASSEMBLIES

AG/MSF equivalent to ELC1043/05	£7 10
ELC1043/06	£7 10
4 way P/B for Decca etc	£5 80
4 way P/B for Decca etc	£7

# Video Mixer

Malcolm Burrell

ONE of the prime ambitions of the amateur video enthusiast must be to build a control desk to enable different video sources to be selected as required. One often progresses no further than a plug and socket, or at best a row of toggle switches. The aim of the present project has been to design a very simple system which the enthusiast with limited finances can easily build. It'll give his efforts that little extra polish.

## Design Considerations

The mixer was designed to complement the simple video camera featured in recent issues of the magazine. Depending on the quality of the cabinet used, the constructor who shops around might be able to build a two or three camera monochrome outfit for about the cost of a single commercially built domestic camera.

I've called it a simple system, but the word "simple" refers to the electronics. As the system grows, so do the number of interconnecting units, cables and plugs and sockets. Then there comes the need for a monitor to enable you to preview the pictures at your disposal. So we end up with a system that's less portable and not exactly for the living room, rather for the "den", spare room or garage.

Flexibility really is the keynote of the "Studio 80" series. The ideas are tried and tested and can be taken up or discarded at will.

This mixer, in conjunction with two or more video sources which must share a common source of sync pulses, enables "live" programmes, lectures etc. to be produced. Those with a video recorder will be able to make large chunks of or even complete productions, using different cameras and mixing shots as necessary without having to stop the machine - with the inevitable picture disturbances that this produces. The lone amateur on the other hand could sit before a fixed camera with one hand on the mixer to enable him to add a little "finesse" with captions, test cards or general shots.

## Operation

A-B channel mixing is used, i.e. a single fader control selects the input from either of two banks of switches (see Fig. 1), depending on its position. With the fader in the A position, operating the top switch buttons will give black level, camera 1, camera 2, camera 3, camera 4 or effects if this feature (to be described in a later article) is incorporated. The bottom row of switches gives the same results with the fader in the B position. A fade-in can be accomplished with say the fader in position B and black level selected on the bottom row of switches and camera 1 selected on the top row. Moving the fader upwards will then fade in the camera 1 picture. Moving the fader down again will fade out the picture.

Mixing between two video sources is also possible. Say camera 2 is selected on the top row and camera 4 on the bottom row of switches. Moving the fader from A to B will result in the pictures first dissolving into each other, finally leaving the camera 4 picture on the screen. With the fader in this position, a cut to camera 1 is produced simply by

operating the camera 1 switch on the bottom row. The next shot involving the use of the fader can then be selected at the top.

This arrangement provides enough facilities for most purposes. Crude superimposition of titles is possible if a "contrasty" background is used. The lettering should be white on a black background. By moving the fader to about half way into the dissolve mode, the title should be discernible, though the relative brightness of the overall picture will be reduced. I shall be covering this in greater detail when we get to the special effects unit.

The mixer is tolerant of deviations from the ideal 1V peak-to-peak video signal, and it's possible to mix composite (video plus syncs) and non-composite (video only) signals as well as colour and monochrome signals. In the latter case however the output obtained will always be in monochrome due to the loss of the original sync pulses, the burst and all signals below the black level (this includes part of the chrominance with dark colours such as red and blue).

The video inputs should be of 75Ω impedance, and in addition to the input socket an extra socket is provided for looping through (see Fig. 2) to monitors etc. If the signal is not to be fed to another piece of equipment, a switch can be incorporated to introduce a terminating resistor or the cheaper solution of using a "stuffer" can be adopted. The latter is simply a suitable plug containing a 75Ω resistor.

The sync pulse generator has been built into the unit to save on extra casing, power supplies and cables. The four outputs available are mixed syncs, mixed blanking and line and field drive. These can be taken to a five-pin DIN plug. As with the original circuit published in the May 1977 issue,

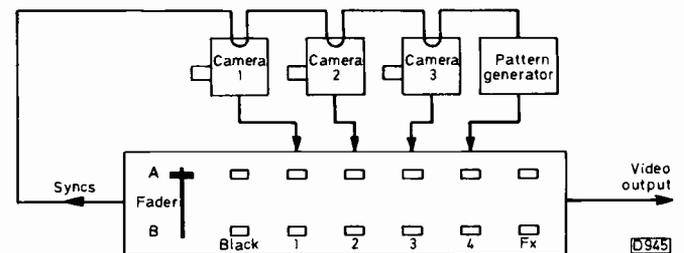


Fig. 1: Fader, switches and general arrangement of the inputs. Position 4 can be used for a pattern generator or a fourth camera.

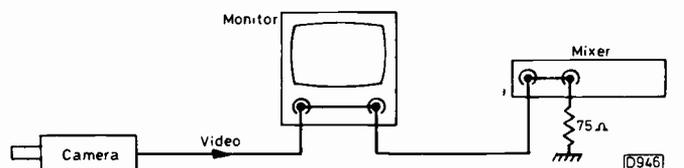


Fig. 2: Looping through.

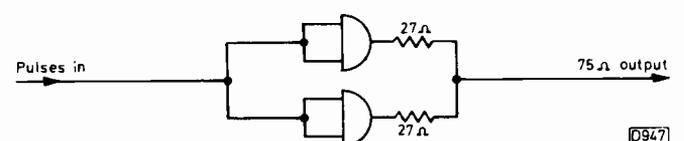


Fig. 3: Use of extra gates to obtain 75Ω outputs.

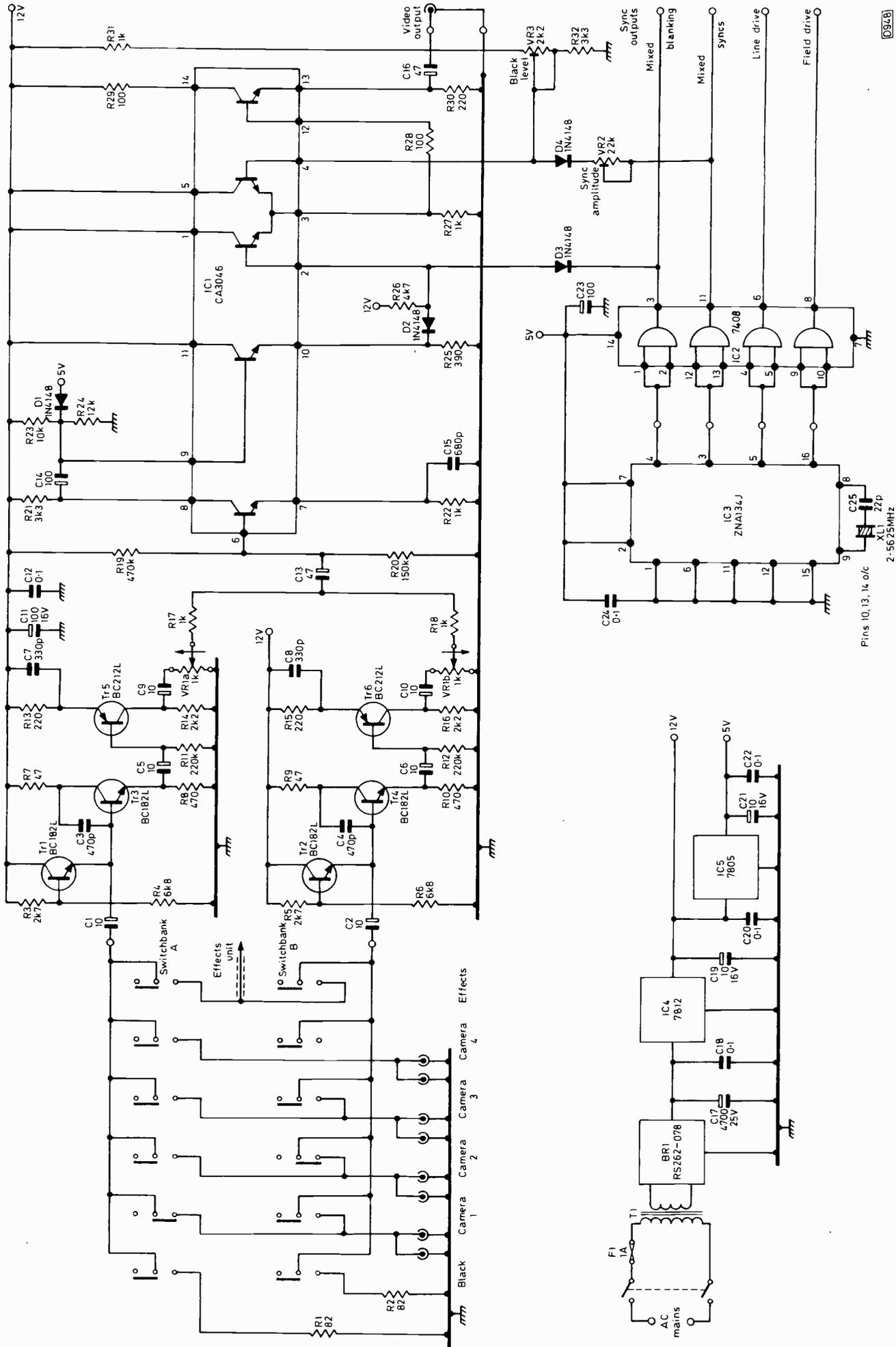


Fig. 4: Complete circuit of the video mixer unit.

these are at TTL level. The perfectionist (who won't build this unit anyway!) will probably throw up his hands in horror, though a limited number of video sources will work happily with these medium-impedance pulses. The use of extra gates will give you 75 Ω outputs (see Fig. 3).

The selector buttons used are those marketed by Maplin. They can be arranged in rows ranging from one to ten. For convenience, two banks of six are employed, but if a simpler video system is to be used and no expansion is envisaged a smaller number can be used.

### Circuit Description

The channel A and B amplifiers are identical, so the A one only will be described (see Fig. 4). The input selected by the switchbank is a.c. coupled by C1 to the emitter-follower transistor Tr3. Since selecting different video signals whose mean level may vary widely can produce picture disturbances with a large-value coupling capacitor, a d.c. restorer transistor (Tr1) is used to provide a stable base bias. The alternative approach (using a lower value coupling capacitor) would result in an unacceptable l.f. response. C3 is included to prevent instability.

A.C. coupling is again used to the fader amplifier transistor Tr5. The fader control itself, VR1a/b, is a dual-slider control with each track connected in the opposite sense. Since this control tends to be noisy, at least until it's worn in, a.c. coupling (C9) is used between the control and the collector of Tr5. The use of large-value coupling capacitors preserves most of the l.f. response.

The output from the fader is a.c. coupled by C13 to the first transistor in the CA3046 transistor-array i.c. — this is

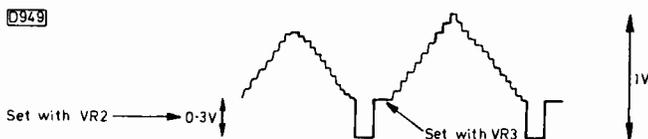


Fig. 5: Setting up the sync and black level controls.

used to reduce the transistor count in the circuit. The first stage is an inverter, which is a.c. coupled with d.c. clamping (D1) to the following emitter-follower stage. The use of a.c. coupling with d.c. restoration at this point was found to give a very significant improvement to the performance of the mixer. The addition of C15 in the emitter circuit of the inverter stage improved the vertical edges.

The blanking and sync pulses are added at the following differential-amplifier stage, with VR2 setting the sync level and VR3 the black level (see Fig. 5). The blanking removes any sync pulses in the original signal. The final stage is a further emitter-follower which provides a 1V peak-to-peak output at 75 Ω.

The well-known ZNA134J sync pulse generator i.c. has been used as the sync source, the outputs being buffered by IC2. The cheap and cheerful circuit shown in the August 1979 issue should work reasonably well as a cheaper alternative.

### Setting up

To set up the mixer, feed in the output from a camera, adjusted to 1V peak-to-peak. With the output from the mixer viewed on a scope, adjust VR2 for a sync amplitude of about 0.3V, then set VR3 so that the darkest parts of the

## ★ Vision mixer components list

### Resistors:

R11	220k	R22	1k		
R1	82	R12	220k	R23	10k
R2	82	R13	220	R24	12k
R3	2k7	R14	2k2	R25	390
R4	6k8	R15	220	R26	4k7
R5	2k7	R16	2k2	R27	1k
R6	6k8	R17	1k	R28	100
R7	47	R18	1k	R29	100
R8	470	R19	470k	R30	220
R9	47	R20	150k	R31	1k
R10	470	R21	3k3	R32	3k3

0.25W, 5% carbon film

VR1	1k+1k lin.
VR2	22k miniature horizontal skeleton preset
VR3	2k2 miniature horizontal skeleton preset

### Capacitors:

C1	10 16V radial electrolytic	C13	47 16V radial electrolytic
C2	10 16V radial electrolytic	C14	100 16V radial electrolytic
C3	470p ceramic plate	C15	680p ceramic plate
C4	470p ceramic plate	C16	47 16V radial electrolytic
C5	10 16V radial electrolytic	C17	4700 25V can electrolytic (e.g. RS 102-774)
C6	10 16V radial electrolytic	C18	0.1 ceramic disc
C7	330p ceramic plate	C19	10 16V radial electrolytic
C8	330p ceramic plate	C20	0.1 ceramic disc
C9	10 16V radial electrolytic	C21	10 16V radial electrolytic
C10	10 16V radial electrolytic	C22	0.1 ceramic disc
C11	100 16V radial electrolytic	C23	100 16V radial electrolytic
C12	0.1 ceramic disc	C24	0.1 ceramic disc
		C25	22p ceramic plate

### Miscellaneous:

Switchbanks	See text.
F1	1A anti-surge with holder
XL1	2.5625MHz crystal
Heatsink	RS 401-497 for IC4-5
T1	240V primary, 15V 3A secondary
Mains on-off switch	
Input/output sockets as required.	

The crystal is available from:

Senator Crystals,  
36 Valleyfield Rd.,  
London SW16 2 HR

IC3 is available from:

Semicomps Ltd.,  
Willington Rd.,  
London Colney,  
St. Albans, Herts.

### Semiconductors:

Tr1-4	BC182L
Tr5-6	BC212L
D1-4	1N4148
IC1	CA3046
IC2	7408
IC3	ZNA134J
IC4	7812
IC5	7805
BR1	RS262-078

video waveform just touch the black level. If a scope is not available, view the picture on a monitor, setting VR2 for a steady locked picture then VR3 so that the darkest parts of the picture begin to blend with the dark grey areas. Then back VR3 off slightly to give a satisfactory contrast range.

### Miscellaneous Matters

The mixer and the effects generator to be described can be housed in the same cabinet, sharing the same power supply. Whether or not the mixer is used with the camera design previously described, it should provide a cheap solution to amateur TV production problems. Surplus, even ex-broadcast, equipment can be obtained by the amateur from time to time, and although the mixer is not of broadcast quality it should work well with most video equipment.

Many cameras, such as the Crofton design, can be adapted for separate sync operation. There are many however, especially those of the surveillance variety, which can be difficult to operate in this way without extensive modification. This is mainly because they obtain their field scan by shaping the mains supply waveform. All need not be lost if you have one of these, since with some ingenuity the sync can be separated from the video and used to drive other units.

Mixing colour signals is a complex business, with the need to avoid phase errors, preserve the burst and lock the subcarrier and ident on all units in use. There's no reason however why an RGB system could not be used with a mixer circuit like the present design in triplicate, feeding a common colour encoder.

A PCB for the project is in preparation and will be shown next month.

# The Complementary Transistor Switch

S. George

IT'S common to explain the action of a thyristor by drawing an analogy with a complementary pair of transistors. Fig. 1 shows the idea. As we should know by now, provided the thyristor's anode is positive with respect to its cathode, then by applying a positive-going pulse to its cathode gate to make this positive with respect to its cathode the thyristor will conduct. It will then remain conductive so long as the current flowing through it is sufficient to hold it on. In the circuit shown in Fig. 1(a) the thyristor will switch on and discharge capacitor C1 – which would have charged previously from the positive rail via R1. If the value of R1 is such that the hold-on current is insufficient once C1 has discharged, the thyristor will switch off. By timing the pulses so that C1 charges periodically via R1 and is then discharged via the thyristor, a sawtooth output can be obtained at the junction of R1/C1.

Why does the thyristor remain conductive after the cessation of the switch-on pulse? The two-transistor analogy explains the action – see Fig. 1(b). By switching Tr2 on, the base of Tr1 is made negative with respect to its emitter, so that it too switches on. Tr2's collector current flows via the base-emitter junction of Tr1, while Tr1's collector current flows via the base-emitter junction of Tr2. So provided the current flowing through the transistors is sufficient, the pair remain conductive. When a thyristor or a pair of complementary transistors switch on, the voltage across them falls to a very low level, in the region of 1V. This is the base-emitter saturation voltage of one transistor plus the collector-emitter saturation voltage of the other.

A complementary pair of transistors is in fact quite widely used in TV receiver circuitry. The use of a pair of transistors may be cheaper than a thyristor, while having both bases available for biasing gives the arrangement greater versatility. There are several possible applications.

### Protection circuits

One is in protective circuitry. A good example is the overload protection circuit used in the Rank Z718 chassis – see Fig. 2. 5VT1 is the line driver transistor, and the idea is to remove the drive to it in the event of an overload in the line output stage. With no drive applied to the line output stage, the set shuts down. To this end, 5VT4/5 act as a

shorting switch across the line driver transistor's base circuit.

During normal operation, 5VT4/5 remain cut off, since the positive voltage tapped from the slider of the set overvoltage trip potentiometer 5RV3 is insufficient for the 8.2V zener diode 5D7 to conduct. The line output transistors' emitter current flows via 5R8, so that the voltage developed across this resistor – and the combination 5RV3/5R15 – is proportional to the load on the line output stage. An excessive load will increase the voltage at the slider of 5RV3 to the point where 5D7 and thus 5VT4/5 conduct. In order to restart the set, it must be switched off for a minute or so for the h.t. to decay. If the overload was transient, the set will then start up. An overload due to a fault in the set will reactivate the trip. 5R16 and 5C22 provide a time-constant to prevent the trip responding to switch-on surges and momentary transients. A similar circuit is used in the later T20 chassis, though the overload sensing arrangement is different.

### Low-voltage Protection

In contrast, Fig. 3 shows the complementary transistor switch circuit used in the Panasonic Model TC333G 13in. battery/mains colour portable to switch the set off in the event of the battery voltage falling to a low figure. This is done in the interests of both the set and the battery. A LED

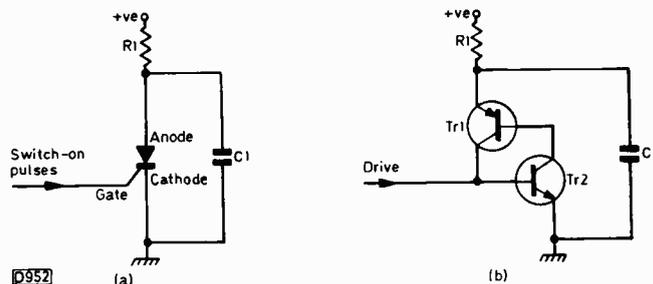


Fig. 1: Analogy between a thyristor (a) and a complementary transistor switch (b). Both operate in the same manner, the thyristor acting like a pair of pnp/npn transistors with their bases and collectors d.c. coupled. The discrete transistor circuit gives greater flexibility in application.

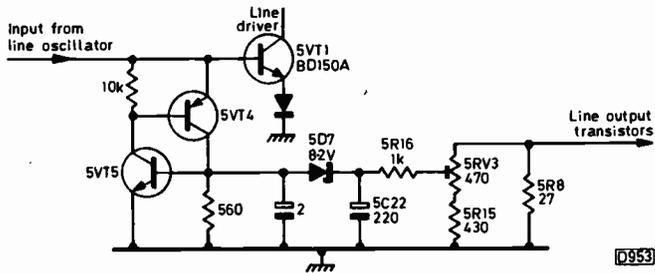


Fig. 2: Use of a complementary transistor switch circuit as an overload trip in the Rank Z718 chassis. In the event of excessive current being drawn by the line output stage, the trip operates to remove the input to the line driver stage.

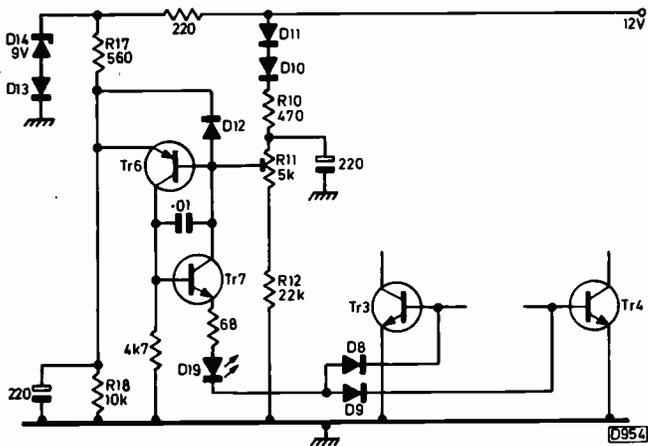


Fig. 3: The complementary transistor switch circuit Tr6/7 in the Panasonic Model TC333G 13in. battery/mains colour portable comes into operation when the voltage from the battery falls to a low level.

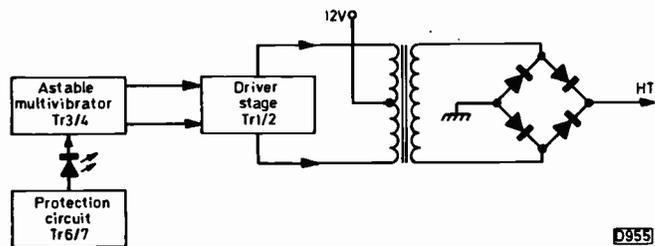


Fig. 4: Block diagram of the battery power supply arrangement used in the Panasonic Model TC333G. In the event of the 12V battery voltage falling to a low level, the protection circuit shuts down the multivibrator oscillator.

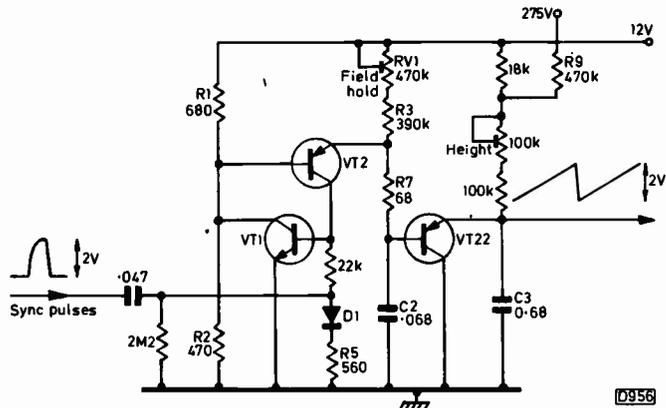


Fig. 5: Use of a complementary transistor switch (VT1/2) as the field oscillator in the Rank Z718 chassis. The circuit is timed by C2 in conjunction with RV1 and R3. The field sawtooth is generated in the following stage, as C3 charges from the 275V h.t. rail via R9 and the height control etc.

comes on at the same time to show that the battery is in need of a recharge.

Fig. 4 shows in block diagram form the arrangement used to obtain the h.t. supply on battery operation. Briefly, the outputs from an astable multivibrator circuit are fed to a driver stage which produces a 20V peak-to-peak squarewave across the primary winding of a step-up transformer. The output from the secondary winding is rectified by a bridge rectifier circuit to provide the h.t. supply.

Tr6/7 form a complementary transistor switch which is normally cut off. There's no current through the LED indicator D19 therefore, and the astable multivibrator transistors Tr3/4 oscillate at line frequency. Tr6's emitter voltage is set by the fixed potential divider R17/18 across the 9V zener diode D14, its base voltage being determined by the setting of the "battery undercut" preset R11 which is connected across the 12V supply in series with R12, R10 and diodes D10 and D11. If the voltage from the battery falls sufficiently, Tr6's base voltage will fall below its emitter voltage (which is held steady by the zener diode). In consequence Tr6/7 will switch on, current flowing via the LED, the two isolating diodes D8/9 and the base-emitter junctions of the two multivibrator transistors Tr3/4. With both Tr3 and Tr4 held conductive, there's no output to the driver stage and the power supply shuts down. Diodes D10/11/12/13 are included to provide temperature compensation.

The flexibility of the complementary transistor switch circuit is highlighted by the fact that in the first example given the switch is operated by applying a positive voltage to the base of the npn transistor whilst in this second example the switch is operated by applying a negative-going voltage to the base of the pnp transistor.

### Field Oscillator Circuit

Our final example takes us back to the Rank Z718 chassis, where a complementary transistor switch is used as the field oscillator. This illustrates two other aspects of the circuit, control via the emitter of the pnp transistor, with the switch reverting to the off condition after the discharge of a capacitor.

The circuit is shown in Fig. 5 and depends for its basic operation on the timing circuit RV1/R3/R7/C2. The base of VT2 is biased at about 5.2V by the fixed potential divider R1/2, its emitter voltage rising at field rate as C2 charges via R7/R3/RV1. When VT2's emitter voltage rises above its base voltage, the two transistors switch on, discharging C2 via R7. Once C2 has been discharged, the two transistors switch off, the comparatively high-value resistors R3/RV1 being unable to provide a hold-on current. The oscillator is synchronised by applying positive-going pulses to the base of the npn transistor. D1 and R5 rectify the sync pulses, producing a negative bias to hold VT1 cut off until the next field sync pulse arrives. The stage is triggered just before the natural switch-on time set by the timing circuit is reached.

Whilst the oscillator could be used to produce the basic field scan ramp waveform, this is done by the following "field waveform generator stage" comprising VT22 and the associated components. When C2 is discharged, the base-emitter junction of VT22 is forward biased. As a result it switches on, in turn discharging C3 across which the field ramp is generated.

The complementary transistor switch is a versatile circuit then, and once you recognise it for what it is the circuit action becomes clear. ■

# Teletopics

## **VLP now LaserVision**

Philips have decided to adopt the name LaserVision in place of VLP for their video disc system. The term VLP (video long play) had been employed since the original laboratory demonstrations of the system in 1972. Two other terms are being introduced to make the system easier for consumers to understand. For marketing purposes, the CLV discs will be known as Long Play discs and the CAV ones as Active Play discs. The constant linear velocity/long play versions of the disc have a playing time of an hour per side, while the constant angular velocity/active play discs have a playing time of 36 minutes per side but in addition offer still frame, slow motion, reverse motion and frame indexing facilities. The same player can operate with both types of disc.

The LaserVision disc system is understood to be on schedule for its launch on the UK market in mid-1981. The system is now on sale in all major market areas in the USA, following various initial test market trials, with players produced by Magnavox (Philips) and Pioneer. Philips are expressing confidence in the successful launch of the system in the UK on two counts, first the technical superiority of the system and secondly the fact that it will be available ahead of its RCA and JVC rivals. Discs for the European markets will be produced at Blackburn, where the installation of the disc-pressing plant is well on target – trial production started in October 1980.

The initial disc catalogue will include over 100 titles and will be expanded to 250 by the end of the year. Rank have agreed to make films available, joining Magnetic Video/20th Century Fox, MCA/Universal and Paramount. Philips envisage sales of LaserVision players in the UK rising from tens of thousands in the first year to 150,000 in 1983 and 700,000 in 1986, and regard these estimates as "conservative". The players are expected to sell at around £500, with the discs averaging £15.

The name LaserVision is to be used world wide, all players and discs made to the Philips optical system carrying the term in addition to any other brand name.

## **High-voltage Line Scan Darlington**

The use of a Darlington line driver/output transistor pair in a common encapsulation is now well established in monochrome portables. Matsushita have now announced in Tokyo the successful development of a high-voltage version for use in large-screen colour sets. As with the low-voltage devices, the pack also includes the shunt efficiency diode and a speed-up diode.

## **Grundig's 2x4 Plus Launched in UK**

Grundig have now launched on the UK market what they call their "second generation" VCR using the joint Grundig/Philips V2000 format. It's the 2 x 4 Plus, which offers still pictures plus fast and slow motion. We first mentioned it in this column last November after it had been on show at the Cologne Photokina exhibition. Grundig comment that with the dynamic track following that's a feature of the V2000 system, the excellent picture quality achieved in normal operation is maintained in the new operating modes, providing clear, interference-free pictures. The slow motion is at a third of normal speed, with fast forward at three times the normal speed.

Another new feature of the machine is the provision of video input/output sockets. An "A" indication lights up in the LED display to show that the machine is in the AV mode. Like the standard 2 x 4, an automatic programme finder (APF) records a signal on the tape at the beginning and end of each recording. When the cassette is run in the fast forward or rewind modes with the tape threaded round the drum, the machine automatically stops at each signal. The timer can be programmed to record four programmes on separate channels over a period of ten days.

The new machine has been taken up by Visionhire, and will be available initially through their 140 branches in the south east.

## **ITV Changes**

The main changes following the IBA's franchise review are as follows: Television South is to take over the south and south east region from Southern Television, while Television South West will take over the Devon/Cornwall area from Westward Television. ATV Midlands is to be restructured, with Lord Grade's Associated Communications Corporation holding no more than 51 per cent of the shares, and Yorkshire Television and Tyne Tees Television must be run separately. The new contracts take effect from January 1982. Breakfast TV is to start some time in 1983 and will be run by TV-AM, which is headed by Peter Jay. In addition to news reports there'll be current events programmes, analyses, features and entertainment. Transmissions will be from 6.15 a.m. to 9.15 a.m. TV4 starts in late 1982. The BBC is also considering breakfast TV, with a possible launch date in early 1982.

## **The Turbo Trinitron**

Sony's latest release on the UK market, their 27in. Model KV2704UB colour set, incorporates some interesting features. For a start there's the 27in., 114° tube, the largest to be used in a domestic colour set. Secondly there's the use of velocity modulation, which is employed to give enhanced picture sharpness. The technique, which Sony call "Turbo modulation", alters the scan speed fractionally when there's a sudden change in picture content. Sony say that the use of this technique enables the sharp pictures obtained with small-screen tubes to be obtained on the new large-screen tube. A sharpness control is provided to enable the viewer to set the degree of picture sharpness to suit his own taste. A third technical feature of interest is the use of a quasi-parallel sound system. This appears to mean that the sound signal is tapped off at an earlier than usual point in the i.f. strip, thus obtaining better results than with the conventional intercarrier sound technique. To make full use of the improved quality sound signal, there's a 10W audio amplifier with independent bass and treble controls and a loudspeaker mounted in its own acoustic enclosure within the main cabinet.

The set's up-market specification includes electronic tuning by voltage synthesis, full-function infra-red remote control and comprehensive input/output facilities. The recommended retail price of the set, which is being produced at Sony's Bridgend factory in S. Wales, is £650.

## **Death of Sir Jules Thorn**

One of the best known names in our industry, Sir Jules Thorn, died on December 12th last, aged 82. Sir Jules was still president of Thorn-EMI, having handed over as chairman in 1976. He was born in Vienna in 1898 and came to England in the early 20s, his first venture being into the import and supply of electric light bulbs and radio valves. When import tariffs were introduced, he started to

manufacture his own bulbs. That was in 1932. His Electric Light Service Co. had been formed in 1928, and in 1936 he bought the Enfield based radio receiver manufacturer Ferguson. The combined company was named Thorn Electrical Industries Ltd.

During the war Thorn bought DER (Domestic Electrical Rentals), laying the foundation of the future TV rental business. TV manufacture started after the war, and in 1958 the British Radio Corporation was set up in conjunction with EMI, giving Thorn the rights to manufacture and sell sets under the HMV and Marconiphone brand names. Shortly after this the Ultra Electric Ltd. radio and TV interests were taken over, giving Thorn two more brand names – Ultra and Pilot. The long series of acquisitions before and after these included AEI's lighting division, Radio Rentals in 1968, and both electrical and gas appliance manufacturers. Well known Thorn brand names include Ferguson, Kenwood, Mazda, Tricity, AVO and Taylor.

Over the years the business expanded in many directions, including hire purchase finance and mechanical engineering. The largest divisions remained TV manufacture/rental and lighting however. The most recent move was Thorn's takeover of EMI in 1979.

Sir Jules was knighted in 1964. He was president of the Radio Industries Council in 1966 and of BREMA from 1964-8. Today Thorn is one of the UK's largest companies, with sales of £1.75 billion and pre-tax profits of £125 million in the last financial year. Sir Jules himself played the major role in building up this massive enterprise.

### **Video Round up**


Hitachi have come up with an interesting VCR in their new Model VT8000, combining as it does the latest video technology with a suggested retail price of only £549 including VAT. Features include pause, still picture, frame-by-frame advance and forward or reverse playback at five times the normal speed to give visual search. A wired remote control unit comes as standard, and the timer can be set to record any programme up to ten days in advance. The size of the motor drive system has been reduced by using a direct drive capstan and a direct drive drum motor system. This gives a very compact, lightweight machine. To assist in setting the machine up initially, a test signal generator has been built in.

Sharp have also announced new video products – two VCRs and a colour camera. The VCRs are the VC7700H and VC7300H, both to the VHS standard, the former being a full-specification machine and the latter a down market model selling at some £200 less. Features of the VC7700H include pause, frame-by-frame advance and half and double speed, automatic programme location by searching for a signal laid down when the record button is pressed, and infra-red remote control. The XC33H camera has a ×6 f1.4 manual zoom lens, a through-the-lens viewfinder and a suggested retail price of around £500.

The new Marconi MV402 all solid-state miniature TV camera was on show at the latest Video Tradex International exhibition. This UK-made, matchbox-size battery-operated camera is primarily intended for industrial surveillance purposes.

Rediffusion have announced the opening of 22 video centres to provide customers with a comprehensive video service. Rediffusion are also launching a videocassette library, with the cassettes for sale or rental. The scheme is to be extended to several hundred of the group's 450 shops.

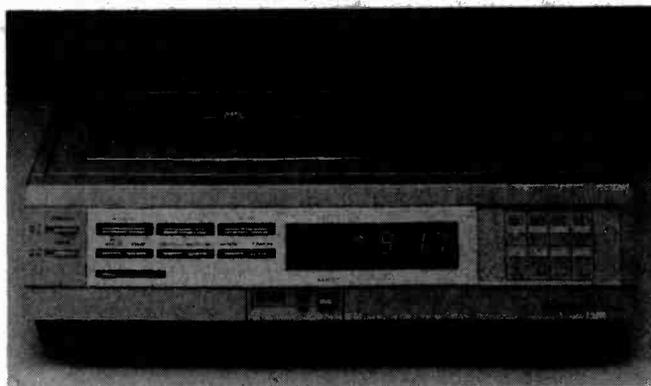A somewhat different type of projection TV receiver has been announced by Sanyo – a back-projection colour set



*The new Hitachi VT8000 VCR.*

with 45in. screen. The two speakers deliver 10W per channel.

A gadget called the Editor has been introduced in the USA to enable VCR users to remove the advertisements from their recordings – this is something of a problem for US users since on average something like 15 minutes in every hour is devoted to adverts. The device, which is manufactured by the Shelton Video Company, works by detecting the short no-signal periods that, in accordance with FCC regulations, must precede all advertisements. The Editor then switches the recorder off for 32 seconds after which, if another black cue doesn't follow, the recorder is switched on again. Apparently only two per cent of commercials slip through – the proportion of missing bits of programme is the same. Shelton are doing further work with the hope of achieving 100 per cent effectiveness.

### **Prestel Developments**

British Telecom's Prestel service is to become international this July, following a successful trial run throughout last year. The latter involved over 300 businesses in seven countries. The full service is expected to follow the pattern found most successful during the trial, with information for specific business sectors, including shipping movements, investment statistics and commodity prices, plus "closed user" segments giving organisations exclusive use of certain parts of the information bank for intra-company use. The database used will be quite separate from the one used for general purposes in the UK.

Prestel International will be restricted initially to the seven trial countries – Australia, Holland, Sweden, Switzerland, W. Germany, the USA and UK, plus Hong Kong – though access will be possible from anywhere in the world. The first database, a GEC 4080 computer, will be sited in London, a second one in the USA being due to come into operation towards the end of the year. Databases will be brought into service in other countries as required.

Meanwhile on the domestic user front various adaptors at under £200 have been announced (Tangerine, Radofin, Zycor), though it's not quite certain what the status of these adaptors is – whether they are still in prototype form etc. It seems that the development of specialised i.c.s for the purpose is likely to have a dramatic effect on costs.

Access to Prestel-type database systems and page selection by means of voice control has been demonstrated, for the first time, at a conference held by the National Maritime Institute at the IEE. It would form part of a radio Prestel system for marine use, enabling ships at sea to replace much of the printed documentation currently used.

### **Videotape Warnings**

Warnings about the use of cheap, imported videocassettes have been issued by Granada TV Rentals, Hitachi and

JVC. Granada comment that a shortage of videotape in the UK last year led to a flood of cheap imports, while JVC mention "obscure brands of VHS cassettes which don't meet the company's technical standards". The tape can be abrasive and shed oxide which causes clogging and damage to the heads. One point to watch out for is tapes prefixed with the letter "T" instead of the European "E". "T" tapes are manufactured for use with the US NTSC television system, which is less critical than the PAL system for recording purposes.

### **Revised Panel Prices**

Philips Service have announced revised prices for two of their replacement panels. The 212 27327 CDA panel for use in Pye hybrid colour receivers now costs £17.00, while the 212 27314 rear-mounted convergence panel for use in later versions of the Philips G8 chassis is available as a new unit only at £17.85. These prices do not include VAT.

### **Roberts-Dynatron Link**

Roberts Video, the TV section of Roberts Radio, has bought the Dynatron TV interests from Philips. This will keep the brand name alive in the TV field, and will give Roberts the advantage of being able to offer dealers up-market sets in cabinet styles varying from modern to traditional.

### **Trade Round up**

Japanese colour receiver production is expected to reach a record level of over eleven and a half million sets in 1980 – production exceeded one million for the first time in any month in November 1980. A further increase in 1981 is anticipated.

Meanwhile European problems worsen. The Italian TV/consumer electronics industry is the latest to get into difficulties, as a result of which a proposal for joint operations between Indesit, Voxon and Emerson has been put forward. Indesit is at present under "special supervision" – an Italian form of receivership. Voxon is expected to apply for this status, while Emerson appears to be anticipating bankruptcy. The three companies are hoping that government financial guarantees will enable a holding company to be set up. This would form one of the largest electronic concerns in Italy, and with pooled development,

purchasing and marketing would provide considerable cost savings. Italian Grundig and Zanussi have both announced substantial lay-offs.

Colour tube production has ended in Finland with the closure of the Finnvalco plant. After three years' operations, losses exceeded £24 million. We were always rather puzzled by this venture, which was started shortly after Thorn withdrew from tube production in the UK. It seems that the problems of starting from fresh in a greenfield site in a rather remote area – selected to help deal with local unemployment – were too great at a time of excess world-wide tube making capacity.

### **A Bit of Fun**

The new generation of more complex video games certainly seems to be doing good business in pubs and clubs across the land. One problem is that customers eventually get bored and require something new. The ingenuity of manufacturers in you know where is apparently rising to meet the challenge however. One of the games that's not so far appeared in the UK features babies being flung from the roof of a burning building. The idea is to catch them before they land on the ground. If you miss, the baby goes "splat" on the sidewalk and a tiny angel appears and moves slowly up the screen. Our more erudite readers might like to devise a steam-hammer and editor game. The idea would be to splat the editor with the steam-hammer, when a small fountain pen would appear on the screen and . . . Never mind.

### **Station Openings**

The following relay transmitters are now in operation:

**Alton** (Hants) BBC-1 ch. 49, TV4 ch. 52, Southern Television ch. 59, BBC-2 ch. 62.

**Baltasound** (Shetlands) BBC-1 ch. 39, Grampian Television ch. 42, BBC-2 ch. 45, TV4 ch. 49.

**Brightstone** (Isle of Wight) Southern Television ch. 41, BBC-2 ch. 44, TV4 ch. 47, BBC-1 ch. 51.

**Bristol (Barton House)** BBC-1 ch. 21, HTV-West ch. 24, BBC-2 ch. 27, TV4 ch. 31. Polarisation horizontal.

**Mallaig** (Inverness) Scottish Television ch. 40, BBC-1 ch. 43, BBC-2 ch. 46, TV4 ch. 50.

**Ravenscraig** (Strathclyde) BBC-1 ch. 21, Scottish Television ch. 24, BBC-2 ch. 27, TV4 ch. 31.

Polarisation is vertical unless otherwise stated.

---

# **VCR Clinic**

November was fun time. Amidst the rubble and wiring, work progressed at a slow pace whilst I tried to sort out my little shop. A few interesting faults have come along, sent by various dealers who had problems and saw no reason why I shouldn't be burdened with them.

### **Replay Wobble**

First came a JVC HR4100 portable VCR. It replayed known good recordings with no problem at all. When it made its own recordings and replayed them however the verticals wobbled at the top and bottom of the screen – the centre vertical line was stable. The effect was similar to that produced by displaced video heads, so we changed them. This was a waste of time. Well I thought, the problem can't

**Steve Beeching, T.Eng.(C.E.I.)**

be mechanical, since replay of a known good recording is fine. So I tried a recording made by the machine on another one. The fault then showed up, indicating that the wobble was due to something being recorded by the machine on the tape.

Experience led me to deduce (think up) that the problem was being caused by the head drum changing speed, which in turn suggested a drum servo fault. But the drum employs the same components for both record and replay – or does it?

Inspecting the motor drive voltage in both the record and replay modes revealed a lump on the d.c. voltage in the record mode – a parabolic lump. So further investigation was called for, tracing back along the servo system from the motor. The voltage from the error detector circuit was level

and steady (pin 12 of IC3), but on the other side of the non-linear circuit (see Fig. 1) there was this parabola. The problem was thus due to X9 or its associated circuitry.

Now X9 is part of the still circuit. The aim is to hold the drum servo voltage at a fixed value, near the true working level, during a pause. During normal play, pulses from the tracking control monostable in IC3 are fed to the base of X8, turning it on and off sequentially. As a result, C52 is kept discharged via D15 and X8. In the pause mode however X7 switches on to remove the pulses from the base of X8, which is thus kept cut off. The result is that C52 charges via R60, X9 turning on to clamp the servo motor voltage at the level set by R62.

So what was happening in the record mode and not on playback? Answer, X8's collector voltage was not falling to zero, since it was not being turned on fully by the pulses from the monostable. Now the pulse duration on record is shorter than on playback, and these short pulses were not turning X8 fully on. In consequence C52 was not being fully discharged and X9 was turning on, producing the offending parabola.

During playback the monostable which produces the pulses to switch X8 on is timed by the tracking control, the timing period being fairly long. In record the timing is done by the crossover point adjuster R28, the timing period being short. The record crossover point was in fact a bit high, occurring some eight lines before field blanking instead of three and a half lines. Adjusting R28 to the correct point cured the wobble. A good one, isn't it?!

### No Drum Servo Lock

Another of these portables came along a little while later, this time a Ferguson version. The fault reported was no drum servo lock – the dealer's engineer had tried various possibilities without success. All the circuitry up to the non-linear bit worked, but after this there were lumps on the drum motor drive voltage. Now as you know Beeching is not one to be caught twice, so R28 was adjusted. The effect was astounding. The servo still didn't lock. Check with scope and find the lumps present at both the collector and base of X9. Hello, hello, hello – on the base which is decoupled by a nice electrolytic? A nice blue tant – in fact a nice blue open-circuit tantalum capacitor! Stick in a new 4.7µF capacitor and the servo works.

### Picture Fault

The next machine was yet another one sent in by a bald dealer (due to tearing his hair out). The accompanying note said that the machine replayed known good tapes but would

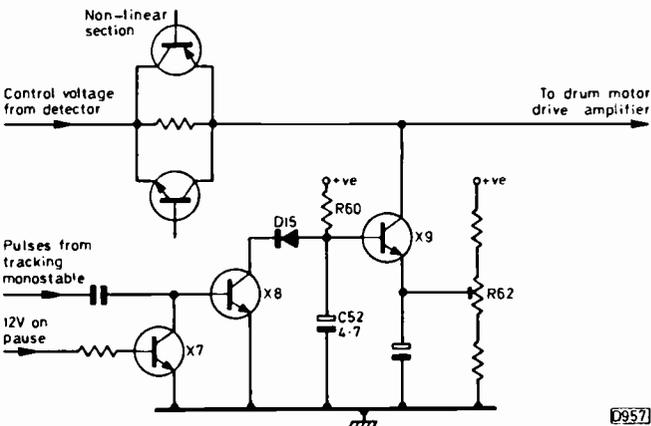


Fig. 1: Part of the pause circuit in the JVC portable Model HR4100. During a pause transistor X9 switches on, clamping the drum servo voltage at the level set by R62.

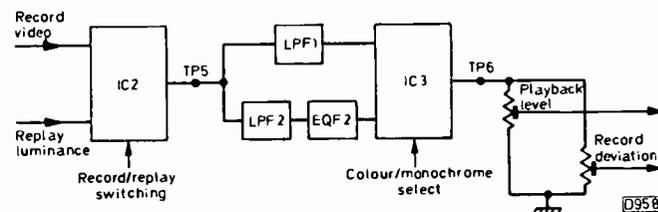


Fig. 2: Luminance signal path in the JVC Models HR3330 and HR3660.

neither record nor play its own. So I checked it out, and found that the replay of its own recordings was diabolical – very low level and fuzzy, with lots of ringing on the edges. I then tried a known good tape. The replay was better, but there was still some ringing.


The next step was to check the record carrier f.m. deviation and level. These were a bit odd, but could be set up all right. The level was a bit out, but this was put down to previous twiddlings. The results were still bad.

I next tried playing a recording from the machine on another one. The results were reasonable. Not good: reasonable. This led me to conclude that whatever was causing the problem was obviously in both the record and replay paths. The ringing on the edges of transients was tolerable when a known good recording was being replayed, and when the defective machine's tapes were replayed on another machine, but when the machine was used to replay its own recordings the results were terrible.

I put on a test tape and started to check around, somewhat puzzled. It was around IC3 (see Fig. 2) that I came across some slight discrepancy. The signal level at TP5 was about 2V peak-to-peak on replay, but at TP6 there was only about 250mV instead of 1.2V peak-to-peak. So being a bit dim I changed IC3, which made no difference.

Switching the rear selector switch to monochrome gave a black-and-white picture with increased video levels. So it must be IC3 – there's not much else except filters. Just for interest, I did a recording and replay and discovered that the signal level in the monochrome mode was considerably greater. Hmmm. Since there was ringing, I replaced low-pass filter 2. No difference. Change equalisation filter 2 and the fault is cleared. So this was the cause of the trouble – a partial internal short to chassis in the filter.

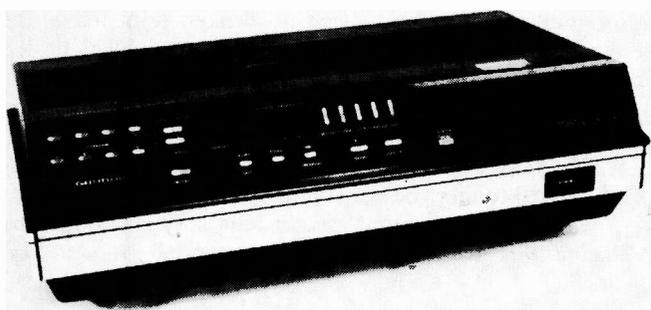In writing the above I've deliberately missed out the other components that were removed and checked before the filter was proved to be the cause of the fault. Naturally a replacement filter had to be ordered from Japan – because they don't go wrong, do they?



The latest VCR from Grundig, the 2x4 plus, uses the V2000 format. For further details see page 188.

# Service Notes on the Siemens Model FC365

Mike Dutton

THE Siemens Model FC365, a 90° colour set, is one of the few foreign receivers imported during the colour boom I'd not come across until recently. Over the past three months however some fifty of these sets, bought ex-rental, have passed through the workshop.

The most common problem we've had has been failure of the tuning selector unit. It's of the push button type, with phosphor bronze spring contacts. These snap off or go weak, causing non-operation of the particular button or poor tuning reset accuracy. The units can be returned to the Siemens Service Agent for repair – new units are not available.

The set is typically German in design, with a large horizontal main panel and four plug-in panels for the power supply control circuitry, RGB output, decoder and field timebase. The main panel contains the luminance, line oscillator, thyristor line output stage and the rest of the power supply circuitry. The panel can be taken out of its slides and parked vertically on the hook provided: this gives excellent access to both sides. The plug-in panels can also be plugged into the back of the main panel, giving access to both sides. A separate side panel contains the sound circuitry, a plug-in i.f. panel and plug-in tuner.

The controls are mounted in a block which can be easily removed after releasing four fastenings. The convergence panel is mounted along the top of the chassis and hinges upwards to enable adjustments to be made from the front of the set. Excellent convergence can be obtained, with extra controls provided for corner convergence correction.

The power supply is slightly unusual. Fig. 1 shows the main essentials. Thyristor D601 provides a regulated h.t. supply and, with D536, C536 and C539, is incorporated in what's basically a voltage doubler circuit. An overload trip is incorporated in the power supply – it operates when the return current flow via R612 exceeds a certain limit or the beam current is excessive, disabling the trigger pulse circuit. To reset the trip, the set must be switched off then on again.

The set's reliability is good, and with a new tube the picture quality is excellent. Much the same chassis is used in the following models: FC366, FC370, FC371, FC373, FC375, FC376, FC379, FC385 and FC388.

The most common fault is a dead set, and the 4A anti-surge mains fuse S1201 (at the left back of the main panel)

will usually be found blown. The usual cause of this is that D536 is short-circuit. The original type had a metal body – a BY133 is a suitable replacement. Lift out the power supply control panel – D536 will be found mounted on the main panel, under where the power supply control panel sits. In only one case have we found the thyristor D601 to be faulty.

Lack of width with bottom foldover is due to low h.t. (the U1 line). The cause may be a faulty preset (R614 on the power supply control panel) or loss of capacitance in C536 (470 $\mu$ F) – when this electrolytic goes completely open-circuit the effect is a dead set. It's always advisable to check the power supply adjustments when servicing one of these sets. Set R607 to minimum, then adjust the U1 supply (R614) for 238V (at pin 1 of plug II). Finally adjust R607 to bring the U1 supply up to 240V. In the l.t. department, adjust R651 for a reading of 24V on the U9 rail (emitter of the series regulator transistor V555).

If the set's dead but the h.t. supply is present, suspect failure of the line oscillator (V590 – BC238B – and associated components), the emitter-follower driver transistor V596 (BC337-25), or the line drive coupling capacitor C598 (0.22 $\mu$ F).

The thyristor line output stage seems to suffer few faults. The only dry-joints I've met have been under R1157 (220  $\Omega$ , 17W). This resistor carries the line scan current, and is associated with the line frequency windings on the EW correction transducer T1155. A case of power supply tripping was traced to one of the line output stage tuning capacitors, C1151 (0.22 $\mu$ F) – it had split open. A faulty tripler (type TVK52S) will also cause the power supply to trip.

Field timebase faults have been confined to dirty preset controls and field collapse due to failure of the emitter-follower transistor V1035 (BC237A).

A bright screen with flyback lines was caused by C702 (5 $\mu$ F) on the RGB panel. The customer had complained of a gradual increase in brightness until eventually the picture disappeared, leaving a blank screen. The capacitor had a heavy leak.

A case of no sound was also traced to a capacitor. This time C199 (10 $\mu$ F) had gone dead short, removing the bias from the base of the audio preamplifier transistor. Loss of sound can also be due to failure (base-emitter open-circuit) of the driver transistor V210 (BC328-25).


I've had two cases of no colour. The first was due to R326 (1k  $\Omega$ ), which sets the reference oscillator frequency, being faulty. The second was due to C320 (0.1 $\mu$ F), which decouples the slider of R326, being leaky. The result of this was that R326 didn't have enough control range to pull in the reference oscillator.

Convergence adjustment is all electronic, with no mechanical static convergence adjustments. Gross misconvergence can be caused by broken print inside the convergence assembly on the tube neck. Coil L843 on the convergence panel burns up, causing various effects.

The first anode presets are mounted together on the main chassis and can be responsible for grey scale drifting.

R270 (33k  $\Omega$ , 2W – it's R547 on some sets), which feeds the TAA550 tuning voltage stabiliser from the U1 rail, runs very warm. I've found that greater reliability is obtained by replacing this with a component mounted on stand-off pillars.

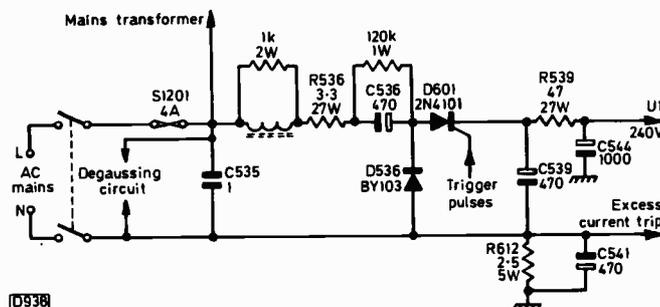Finally, the on/off switch control knob breaks off. With care however the control can be stripped down and the knob glued. In general I've found that these sets are capable of producing a good quality picture and sound, and are well worth renovating. ■



093B

Fig. 1: Simplified circuit showing the mains input and h.t. rectifier circuits.

# Practical TV Servicing: Capacitor Defects

S. Simon

THERE'S no doubt that defective capacitors are responsible for a large percentage of the breakdowns that occur in domestic electronic equipment. Whilst we're primarily interested in TV servicing here, the fact is that at some time or another we probably all get called upon to attend to radio receivers, stereo units, cassette recorders and the like, so a few words here and there about such items may perhaps save the reader some time and heartache – particularly if he's not normally involved in servicing audio equipment.

Let's start at the shallow end, as usual, by considering what should by now be well known, in order to go on to what may not be so well known. When a hybrid TV set is encountered with an open-circuit mains fuse and the fuse is not blackened to suggest a direct short, due say to a short-circuit h.t. rectifier or filter capacitor, we've often advised readers to check with an ohmmeter the reading from the top cap of the PY500 boost rectifier in the line output stage to chassis. If the boost supply is in order, a reading of something over 200k $\Omega$  can be expected. Anything much less should give us food for thought before proceeding further.

A reading of 100k $\Omega$  for example may well suggest that the boost feed to the tube's first anode circuit is at fault, and investigation may prove that a decoupling capacitor in this area is short-circuit. Such a reading will be obtained only when the 100k $\Omega$  (say) feed resistor which the capacitor decouples has maintained its value despite the heavy current flow due to the short-circuit capacitor. It's rather doubtful whether the resistor would have retained its value however, since the usual rating is only about 1W. In fact the overheated resistor would probably have already indicated its distress by sending up smoke signals.

Let's suppose that the reading obtained is say 3k $\Omega$ , which you may say is a rather funny figure. Not so really, because it could mean that the 100k $\Omega$  feed resistor has fallen in value as a result of the overload and is now only 3k $\Omega$ . It could. But in fact this doesn't often happen because when the 100k $\Omega$  filter resistor we're considering changes value it usually does so in no uncertain manner, ending up with a very low resistance. So much then for the boost supply filter in the feed to the c.r.t.'s first anode circuit, and as regular readers will have recognised we were thinking in particular of the Pye hybrid colour chassis in the foregoing comments.

Let's get back to our discovery of a lower reading than 200k $\Omega$  between the top cap of the PY500 (or whatever) and chassis. What do you do next? You get a nice bright light and examine the high-voltage capacitors associated with the line output stage. The ones you'll usually find are round disc types with a value of some 200pF and a voltage rating of 8kV or 12kV. If one of these is responsible for the low resistance reading, it will usually have a blackened area on it – if it's not in fact more severely damaged.

One might have thought that with such a deterioration there'd be a direct short, and you could be right about this. More often however you'll find a resistance reading of

several thousand ohms when checking cold, and this is what you should generally expect under the circumstances. The purpose of these capacitors is to contribute to the shaping of the line flyback pulse, and the original type and capacitance value must be maintained. The tubular type of pulse capacitor is not so reliable, and discs are to be preferred. A few sets do use the tubular type however – in the ITT VC200 hybrid monochrome chassis for example there are three in a row, and it's extremely common to find one of them burnt up, presenting a short-circuit across the boost line.

So here are two types of capacitor that often cause trouble in TV sets – the ceramic (disc or tubular) types used for tuning in the line output stage, and the paper/polyester types used to decouple the c.r.t.'s first anode supply. These are all high-voltage types of capacitor.

## Leaky Couplers

Ceramic capacitors will also be found in most low-voltage circuits, and these are of a different construction. They are normally (considering the vast quantities used) very reliable, as also are the equally widespread polyester ones of the gaily coloured variety. They are not above suspicion however.

Let's revert to the Thorn 1500 hybrid monochrome chassis which we mentioned so often in the previous *Beginners' Guide* series. The audio department here consists of a PCL82 valve and associated components, with the triode used as a voltage amplifier and the pentode as the power output stage to drive the loudspeaker. The output developed across the triode's anode load resistor is coupled to the pentode's control grid by a capacitor, so that the a.f. signal appears at the pentode's control grid but not the high d.c. voltage at the anode of the triode. If a positive d.c. voltage does reach the pentode's control grid, it will pass excessive current and the sound will be badly distorted. There are two ways in which the pentode's control grid can become positive – either leakage in the coupling capacitor, or a defect in the valve itself. If the positive voltage is still present at pin 3 (pentode control grid) when the valve has been removed, the coupling capacitor is leaky and should be replaced. This is a common enough fault, and serves to illustrate that leaky capacitors are not found only in the high-voltage sections of the receiver.

## Open-circuit Capacitors

Leaky capacitors are usually pretty obvious, since they disturb the d.c. conditions and can therefore be detected using a meter. Open-circuit capacitors on the other hand just sit there and do nothing except cause trouble. If the open-circuit capacitor is a large electrolytic one, the effect is usually quite dramatic and fairly easy to trace.

Say the main h.t. reservoir capacitor becomes open-circuit – something one must expect to encounter quite often. There will be a drop in the h.t. voltage, which should

be revealed without much ado by checking with the meter. Provided one knows what the h.t. voltage should be of course.

In a recent case we were asked to repair a solid-state GEC colour set (C2110 series). The customer's complaint was that the sides of the picture had come in and that the colour had failed, leaving a blue picture (not movie). This could have been a confusing set of symptoms, but a meter check at the top right-hand side power resistors revealed that the h.t. was only about 130V instead of 186V. So we removed the bottom centre power unit and unsoldered the connections to the h.t. reservoir/smoothing electrolytics (they are separate on this chassis, instead of being the more common multiple unit). The left-hand reservoir capacitor moved the meter's pointer to a certain reading (actually 300k $\Omega$ ) where it remained steady – instead of the pointer swinging over to give a low reading, then recovering to a fairly high reading as the capacitor charged. Replacing the reservoir capacitor restored the h.t., the width and the colour signals, though it didn't do much for the predominantly blue cast since this was due to a worn tube. Resetting the grey scale made an immense improvement however, producing quite an acceptable picture.

All pretty obvious you may say, but the essential point is that once the effect of low h.t. due to an open-circuit h.t. reservoir capacitor is appreciated the repair can be carried out with a minimum of checks and disconnections. The effect of an open-circuit h.t. smoothing capacitor is also well known, the symptoms varying from curved verticals and impaired sync to complete loss of any recognisable picture – depending upon the amount of extra smoothing and decoupling used in the set (more capacitance further along the supply lines). Some sets employ quite an elaborate h.t. supply network, with separate supply lines, each separately decoupled by a fair sized electrolytic, going to various parts of the set. With such a set the failure of the main h.t. smoothing electrolytic will not have such drastic results as in a set which relies on one single large electrolytic to provide the majority of the smoothing. In the latter type of set, loss of the one electrolytic section will produce many varied and confusing symptoms.

To check whether an h.t. smoothing/reservoir electrolytic is open-circuit, simply shunt the suspect with another one of similar value. Note however the charging effect of the test capacitor if the circuit is working, i.e. fit it before switching on, so that it charges normally. This check will nearly always prove the point. Remember to discharge the test capacitor if the test is not conclusive, preferably via a resistor to avoid the heavy spark which occurs when the tags of a charged electrolytic are shorted across.

### Low-voltage Electrolytics

Electrolytics are not confined to power supply smoothing applications of course. For a.g.c. purposes we require a d.c. control voltage, i.e. the signal variations present at the source of the a.g.c. voltage must be smoothed out before the

a.g.c. potential is applied to the controlled stage. This again may be fairly obvious, but the fact is that an open-circuit a.g.c. line smoothing capacitor can be responsible for apparently baffling symptoms, and that much time can be saved by remembering to check this at an early stage in the fault finding procedure.

Let's consider next the effect produced by an open-circuit decoupling capacitor in an ordinary transistor audio amplifier stage – we rarely mention this sort of thing in these pages. Many preamplifier stages used in audio equipment employ small electrolytics to prevent negative feedback, and it's instructive to consider the simple circuit shown in Fig. 1.


The transistor is an npn type of the BC109 variety (low noise, high gain). The input signal is applied to its base, while the output signal is taken from its collector, being developed across its collector load resistor R3 as a result of the variation in the current flowing through the transistor. If a resistor (by itself) is connected in the transistor's emitter lead, this will also develop a signal voltage – since the transistor's emitter current is also its collector current. The signal voltage at the emitter will cancel the input signal voltage at the base (negative feedback), which defeats the whole purpose of the exercise. So in designing such a stage we can do either of two things – we can omit the resistor in the emitter circuit, or we can decouple it with a capacitor (C3 in our circuit) which smooths out the signal voltage variations in the emitter circuit so that the transistor is left with a d.c. voltage at its emitter.

If you are faced with an amplifier that fails to amplify despite the voltages around it being apparently correct, spare a thought for the fact that negative feedback might be cancelling the input signal, i.e. check the capacitor which decouples the emitter resistor. You will almost certainly find that it's open-circuit, which will be proved by shunting a suitable replacement across it.

You may say that one rarely comes across this type of audio preamplifier circuit in a TV set. All the more reason to draw attention to it, since it's the "one off" jobs with unfamiliar circuitry that are the most time consuming. Just to emphasize the main facts here, a hum test or a signal injector should produce a certain level of output when applied to the collector of the transistor, a much greater response when applied to the base, and no response when applied to the emitter. If the test produces approximately the same response at the collector, base and emitter, it can be assumed that the emitter decoupling capacitor is open-circuit.
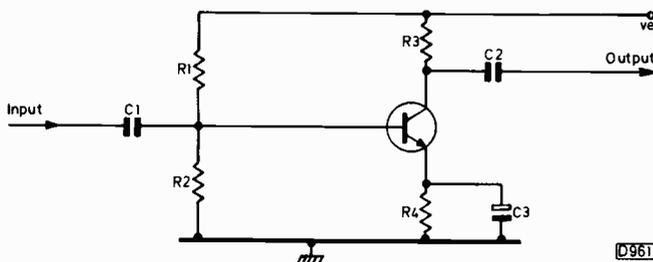
### Polystyrene

Polystyrene is a word that strikes terror in the heart of the busy engineer. Capacitors using polystyrene as the insulating material are normally high-stability types employed in parts of the TV set where frequency stability is essential – for example in the colour decoder reference oscillator circuit or in the line oscillator circuit. Such capacitors all too often become open-circuit, with the result that the oscillator runs at the wrong frequency (it usually continues to oscillate due to the natural capacitance of the coil and the presence of stray capacitance). The situation is aggravated when the defect is intermittent. The only sure remedy is to replace any suspects, using exact replacements or silver mica types of the same capacitance value (these are also high-stability components). Typical values found in line oscillator circuits are 390pF and 820pF. We don't want to give the impression that line hold problems should direct attention first to the small capacitors in the line oscillator



©961

Fig. 1: Simple transistor audio amplifier stage.

circuit however: the well known trouble spots should be checked first.

For example, say you have a Pye hybrid colour set which is giving trouble with unobtainable or varying line hold. If you immediately changed the polystyrene capacitors in the line oscillator circuit, you'd almost certainly be disappointed – because the trouble is likely to lie elsewhere. Our oft repeated advice on dealing with this problem on this chassis should be followed.

In short, you'd first check the 47k $\Omega$  resistor which feeds line pulses back to the flywheel sync discriminator circuit – simply by looking at it. If it's still smart and colourful, there's little cause for concern. If it's in an obviously distressed state, change it and check the nearby discriminator diodes – these often go short-circuit when the resistor has allowed too much current to pass. Next, if necessary, look at the 100k $\Omega$  resistor in series with the line hold control – disconnect one end and check its value. If everything's in order here, move over to the left-hand side i.f. panel where you may find that the sync separator's 4.7M $\Omega$  base bias resistor is high in value. Ah, you may say: in this case the field locking would also be weak. Ah, we reply, weaker than usual, though it may not be too obvious, so watch it! If these points check out o.k., turn attention to the 16 $\mu$ F capacitor which decouples the oscillator's h.t. supply, and the PCF802 valve itself. When all this has been done – and the routine takes only a few minutes – one may fairly view the polystyrene capacitors in the line oscillator circuit with suspicion.

### Leaks and leaks . . .

What exactly does one mean by a leaky capacitor? Leaky like a dripping tap? Possibly, in a way that might surprise you. Otherwise what we mean is that the capacitor has lost its d.c. insulation. We've already mentioned the audio circuit in the Thorn 1500 chassis, where the coupling capacitor can become leaky with the result that the operating conditions in the output side of the circuit are upset. Many other such examples could be quoted, but we don't wish to labour this rather obvious condition. It's the other aspect of the leaky condition that requires a little explanation.

It applies only to electrolytics, but can spell havoc on a crowded circuit board. Once upon a time one could shake an electrolytic capacitor and actually hear the electrolyte sloshing about inside. Since those days the electrolyte has thickened up a bit, so you can't slosh it about. It can still leak out however, and does. The trouble is that the capacitor can go on functioning, since it retains its capacitance even though it's leaking.

"What's this on the carpet under the TV set dear?"

"It must be the cat."

The cat might be quite continent, but the picture on the TV set may be doing funny things – like getting progressively darker as the conductive fluid spreads into the beam limiter circuit say, causing transistors to conduct when they shouldn't.

When your TV set or audio unit is doing funny things, shine a light on to the end of the electrolytics to see if they are moist. If they are, look to see where the fluid has spread (or dripped). Many items may have to be removed in order to clear the effects of the leakage, or perhaps a whole panel may have to be replaced if your patience doesn't run to removing the multipin sockets etc. in addition to the more run of the mill resistors, capacitors and transistors in order to clean out every trace of the conductive chemicals, wet or dry . . .

# next month in

# TELEVISION

## ● SERVICING THE THORN 4000 CHASSIS

The 4000 colour chassis is a very interesting one – Thorn's design for driving 110° delta gun tubes. It has an up-market specification, having been designed primarily as an export model. In addition to the UK, it's been produced in quantity in Australia and S. Africa. Technical features include a parallel chopper circuit, separate line output and e.h.t. generator stages (the latter with regulation), and the use of a number of thick-film units. It can give an excellent picture, though the high dissipation can cause reliability problems.

Elsewhere in our servicing coverage, Les Lawry-Johns returns to the scene, reporting amongst other things on an encounter with a Thorn 9800 chassis – another one we've not mentioned previously.

## ● SIMPLE UHF PREAMPLIFIER

One of the most common requests we receive is for practical preamplifier details. This latest design is extremely simple yet capable of excellent results, using as it does a transistor (type BFQ85) which has a high gain (21dB at 500MHz) and a very low noise figure (1.6dB at 200MHz).

## ● FUN AND GAMES

Malcolm Burrell reports on the TV games boom in pubs, clubs and other public places. He's had an opportunity to examine the innards of many of them, having recently completed a maintenance stint.

## ● IN-CIRCUIT TRANSISTOR TESTER

Also checks transistors out of circuit, in fact a very handy device that uses only four components plus a switch and a couple of batteries. The idea is to check whether the transistor being tested will oscillate. It rejects transistors with low gain, low-frequency cut-off, leaks or open-circuit junctions, and identifies pnp and npn types. The 3V supply means that damage is avoided if the tester is connected incorrectly. The only limitation on in-circuit testing is where the base-emitter circuit impedance is very low (e.g. with line output devices).

**PLUS ALL THE REGULAR FEATURES**

**ORDER YOUR COPY ON THE FORM BELOW:**

TO.....  
(Name of Newsagent)

**Please reserve/deliver the March issue of TELEVISION (70p), on sale February 18th, and continue every month until further notice.**

NAME.....

ADDRESS.....

# Video Report: The Sony HVS2000P Effects Generator

David K. Matthewson, B.Sc., Ph.D.

THE Sony HVS2000P camera power unit, switcher and colouriser is a remarkable release on the domestic video market. This small box – only some 4 × 10 × 10in. – acts as a 12V d.c. power supply unit for one monochrome and one colour camera (the Sony HVM100CE monochrome and HVC2000P colour cameras say) and allows the user to cut synchronously between the two cameras. The latter means that the cutting is done during the field blanking period, so that no interference appears on the screen. A monochrome picture can also be faded in and superimposed on top of the colour one, and even artificially colourised at the touch of a button. These features should make the switcher interesting enough to the domestic or low-budget industrial/educational video user, but a further feature should clinch the deal – the suggested retail price, including VAT, is only £72!

At this price, which is little more than the SRP of the power unit alone for the HVC2000P colour camera, Sony admit that they are not making a profit out of the unit. The hope is that it will encourage the sales of cameras and the wider use of video equipment. Sony also comment that most of the development costs have already been recovered, as many of the i.c.s employed in the unit were originally designed for use in various pieces of more expensive professional equipment.

## Features

Before we take a look at how it works, let's consider in a bit more detail what it does.

The unit is housed in a sloping fronted case and weighs around seven pounds. At the rear are the various connectors, including two of the new K type 14 pin sockets for power out/video in, and two BNC video output sockets. One of these sockets is for feeding a VCR and the other for feeding a monitor. Although both outputs may appear to be identical, only the VCR output is controlled by the blanking

switcher: the monitor output gives asynchronous cuts, and should not therefore be used to feed a VCR.

Other sockets provide an audio output (this supplies the signal from the colour camera's built-in microphone to the VCR), a remote control jack to allow the colour camera's trigger to stop and start the VCR, and a tally jack which enables the "tape run/stop" button on the HVS2000P's front panel to do the same thing.


The front panel has two banks of vision selector switches, one for monitor output – a sort of preview, which allows you to examine an effect before selecting it for recording – and one to select the video output fed to the VCR for recording. These two banks of switches enable either the colour camera signal or the monochrome camera signal to be selected for recording or, when the superimpose button is operated, a number of special effects can be carried out. In the simplest mode this enables you to mix (fade) monochrome pictures with colour ones, or to key them into colour ones – keying is a form of non-additive mixing. This effect for example enables you to superimpose in monochrome the name of a man shown talking in the colour picture – this sort of thing is often done by broadcasters during news programmes. With the artificial colouriser switched on, the keyed in item can be superimposed in colour – in either yellow, cyan, green, magenta, red or blue. By operating the normal/reverse button the opposite effect is obtained – in other words a coloured field with the caption keyed into it, through which the colour camera's picture is visible.

## Use

All in all then it's a very versatile piece of equipment. Colour cameras other than the HVC2000P can be used, connected via suitable adaptor leads. Off-air TV signals or off-tape video can also be fed in (see Fig. 1), so that titles can be added to a prerecorded tape for example. A word of warning here. Much of the signal processing within the switcher is timed by the incoming colour video signal, and it's essential that this is of the highest possible quality and quite stable – nth generation rolling video tapes will produce very unsatisfactory results.

The monochrome camera recommended by Sony for use with the unit is their HVM100CE, which can be switched to operate with its own internal sync pulses or locked to an external sync source. It must be used in the latter mode with the HVS2000P, its syncs being derived from the incoming colour video signal. Hence the need for stability. Rather awkwardly, Sony have chosen to supply the monochrome camera with a mixed sync signal with the horizontal drive positive-going and the vertical drive negative-going, the whole waveform being about 2.8V peak-to-peak, instead of a standard 2V or 4V mixed syncs signal or separate line and field drives on two wires. This makes the use of other monochrome cameras difficult, since it's essential that both video sources are synchronised.

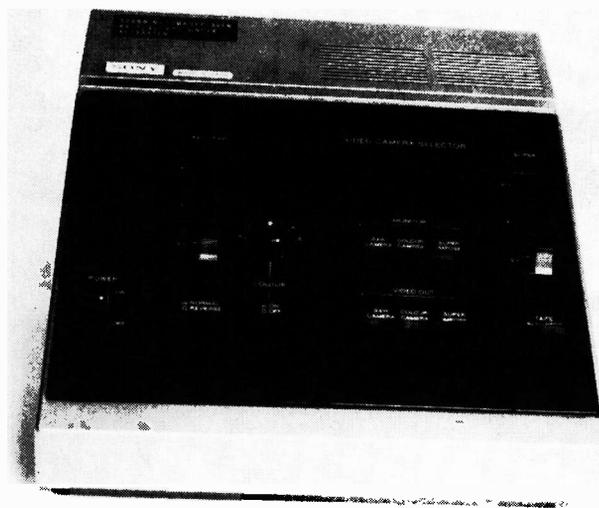Difficult certainly, impossible no. The sample mixer I had for review came along with an HVC2000P colour camera but no monochrome one, so I devised a method of



The Sony HVS2000P effects unit, showing the layout of the controls on the sloping front panel.

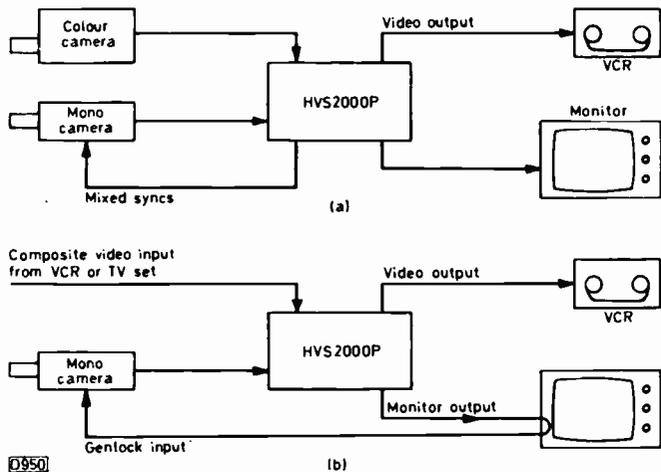


Fig. 1: Using the Sony HVS2000P effects unit. (a) Normal use. (b) Alternative ways of using the unit.

testing it out that may be of interest to others. I had a National monochrome camera that could be genlocked to an external video signal (for those not familiar with video techniques, genlocking is a way of synchronising a camera's or a vision mixer's sync pulse generator to an external video signal so that the two operate synchronously: they can thus be mixed etc.). By selecting the colour camera's output on the monitor switch bank and feeding this to the National camera's genlock input socket, I was able to feed synchronous signals from the National camera to the HVS2000P switcher and thus do mixes etc.

## Results

Even when compared with units costing several thousand


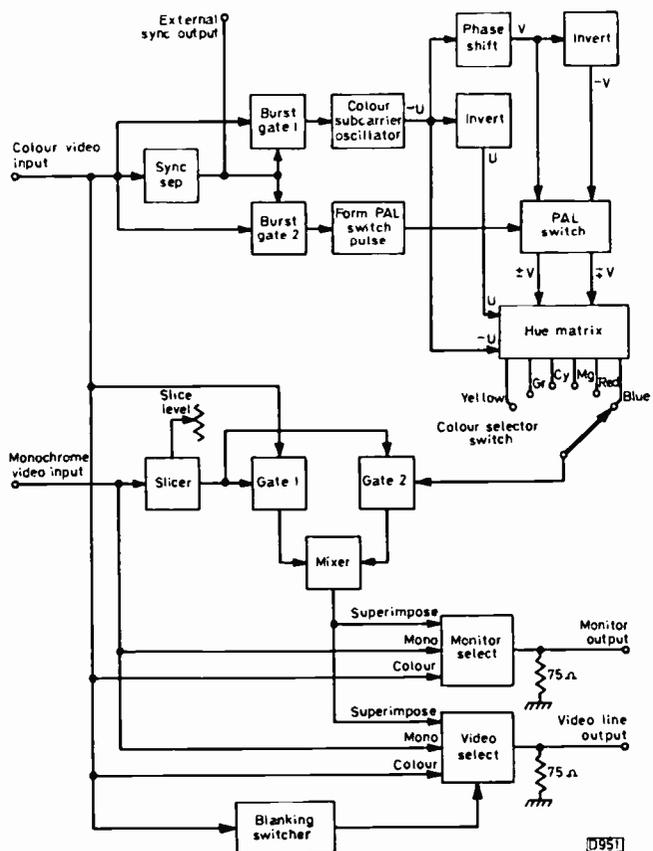


Fig. 2: Simplified block diagram of the Sony HVS2000P effects unit, which also provides regulated power supplies for the two cameras.

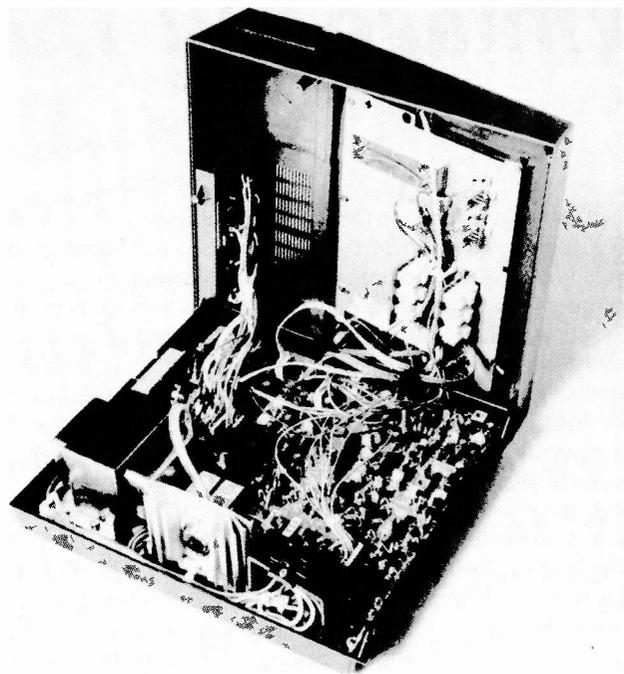

Innards of the HVS2000P effects generator unit.

pounds the Sony HVS2000P switcher was found to perform very well indeed. The only slight complaint I have is that the synthesized colour field does not completely overlap the colour camera one. On some TV sets this may appear as a small margin of colour picture at the top and right-hand side of the synthesized picture. The effect is not present when captions are superimposed on a colour signal. Quite why this problem arises I'm not sure, but it's obviously supposed to happen since it's mentioned in the users' handbook.

The synthesized colours were well saturated and impressive, judged subjectively. The keying and mixing facilities worked well, and lighting the captions to be keyed in, something that's always a problem, was not too difficult. For anyone who wants the facilities this unit offers, I can quite unhesitatingly recommend it.

One has learnt not to expect much for £70 in the video world. It came as a considerable surprise therefore when I lifted the top off the switcher and counted some thirteen i.c.s and over 90 transistors, all arranged on a neat pcb. The presets are clearly labelled, and there are plenty of test points.

The operating principles are quite straightforward, as the block diagram (Fig. 2) shows. The basic waveforms required, including the U and V subcarriers and the PAL alternate line phase shift for colourising, are all derived from the incoming colour video signal. The incoming signal from the monochrome camera is sliced, i.e. the signal level above a preset level is considered to be white, that below the preset level black (no greys), the white portion then being used to gate the monochrome signal into the colour one at the mixer.

Though the unit is intended for the home video market, I'm sure it will find wider applications in education and industry. It doesn't conform to broadcast standards, but nevertheless works very well. With these features at this price, it's a must for everyone seriously interested in video programme production.

Finally (oops) a correction to my review of the Hitachi GP4/VKC750 colour camera last month. The Sony colour camera referred to was the HVC2000P of course. ■

# Vintage TV: The Baird Everyman

Vivian Capel

THE cost of a receiver in the early days of television amounted to a high proportion of the average income. Some models were not greatly different in price from present day ones, but incomes then were only around a tenth of what they are today. So sets were few and far between, and only the affluent could afford to gaze at the wonders on the 9in. screen in their living rooms. Thus it was that several manufacturers tried to beat the price barrier and bring TV to a much wider audience. For this purpose, sets cut down to the barest essentials were the order of the day.

A noteworthy example was the Baird Everyman. There were two basic models. The first to appear was the T29A, which was for use on a.c. mains supplies only. The reason for this was that a small transformer was used to feed the c.r.t.'s heater. The rest of the heaters were connected in series across the mains, with a dropper resistor, in the usual manner. The arrangement rather belied the name Everyman, since a number of areas then had a d.c. mains supply. So the second version, the T29U, appeared. This was fitted with a GEC 6505A c.r.t. instead of a Mazda CRM92, and as this tube had an 0.3A heater it could be connected in the series heater chain, dispensing with the transformer.

To call it a series heater chain is not entirely accurate since two of the valve heaters were connected in parallel. The valves concerned were the 20P1 line timebase valve and the 10P14 field output valve. The former had an 0.2A heater and the latter an 0.1A heater, so they could be connected in parallel in the heater chain. It was a bit risky however, since if one of these heaters went open-circuit the other would be considerably overrun. The rest of the valves would still be working, with the sound present, so there was the possibility that the owner would leave the set on to hear the rest of the programme.

The most interesting feature of the set however was the fact that it used only eleven valves, plus the c.r.t. This was before the days when multiple valves became commonplace, and in fact the only multiple valve was the 6D6 double diode (vision and sound detectors). The sets were of the t.r.f. variety, with three r.f. stages. One provided both sound and vision r.f. amplification, the other two providing sound and vision r.f. amplification respectively. Further saving was achieved by using the sound r.f. amplifier in the reflex manner – as an audio amplifier as well. All this meant that there was not a great deal of gain, but the sets were quite adequate for areas where the signal strength was reasonably good. The 6F12 pentode used in the r.f. amplifier stages was also used in the video output, sync separator and even the audio output positions, so the engineer needed to carry only a few valves to have a complete range for the set.

There were two versions of both models, one for the London region (channel 1) and the other for the Birmingham area (channel 4). The alignment of the latter version was rather critical, sound rejection in particular needing very careful adjustment.

## Focusing

The standard method of focus adjustment, which eventually came to be used in almost all monochrome receivers, consisted of two magnetic rings on the neck of the tube. One was fixed while the other could be moved by means

of a lever. It was quite common in very early sets to use a form of electrical focusing however, sometimes adjustable by varying the current through a focusing coil.

Two methods of varying the focusing were used in the Everyman. The main focusing was provided by means of a permanent magnet. There was also a fine focusing control however which varied the e.h.t. around the nominal value of 7kV. This was done by including a 200Ω potentiometer in the h.t. feed to the one-valve line timebase. Reducing the h.t. supply decreased the e.h.t. and also the line scan power. Since the deflection sensitivity of the tube is dependent on the e.h.t. however, the sensitivity increasing as the e.h.t. falls, the focus control had little effect on the width. To ensure that the height was not affected, the focus control also varied the h.t. supply to the field timebase.

## Line Timebase

The line output stage circuits used in sets of the time were always comparatively simple. The single-valve line timebase used in the Everyman really did reduce things to a minimum however (see Fig. 1). There were three windings on the transformer (plus the e.h.t. rectifier's heater winding of course). The secondary provided feedback to the 20P1's control grid, and also drove the scan coils. A single RC time-constant network set the frequency (one or two extra components were added to this part of the circuit in some sets). The valve's screen grid feed resistor was also the sync separator's anode load resistor – the screen grid voltage was thus modulated by the line sync pulses. The usual overwinding fed an EY51 rectifier to provide the e.h.t.

## Field Timebase

A rather more complex field timebase circuit was used (see Fig. 2), though there were circuit economies here as well. The two valves employed were a 6F12 in the blocking oscillator circuit and a 10P14 for the output. The charging circuit

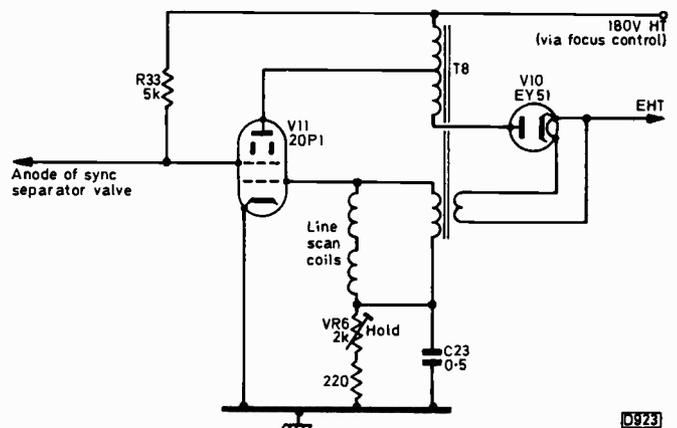


Fig. 1: The single valve line timebase used in the Baird Everyman. In addition to driving the scan coils, the secondary winding on the line output transformer T8 provides feedback to the 20P1's control grid. The self-oscillating circuit was synchronised by applying the line sync pulses to the valve's screen grid. There was no efficiency diode in this early form of line timebase, the output valve conducting throughout the scan while the flyback energy was dissipated as heat.

R27/C26 generated the basic field scan waveform, C26 being periodically discharged by the oscillator valve. The field hold control circuit consisted of just three resistors and a wire link to short out sections as required. The manual rather optimistically stated that "the frame hold is fixed before leaving the makers and will not normally require resetting". As engineers who were active in the trade in those days will recall, the field hold control was in most models the most likely one to need adjustment. In fact with some sets good interlace could be obtained only at certain critical hold control settings. Other sets would start rolling as soon as they warmed up, so that the control had to be set near the opposite limit of its hold range, the idea being that the set would drift into rather than out of lock! The danger of course was that the field would be out of lock when the set was switched on.

The field output stage also had some unusual features. Instead of an output transformer, the load consisted of a choke, the scan coils being connected between the valve's anode and cathode via the 100 $\mu$ F electrolytic C24. The height was controlled by means of a variable resistor in the cathode circuit. This didn't control the bias, since doing that would have affected the linearity as well. With the control grid returned to the top end of the control, the h.t. applied to the stage was being varied instead. Linearity was controlled by means of the 5k $\Omega$  variable resistor VR7 in series with the anode choke. This was not a user accessible control, being mounted underneath the chassis. The comparatively low value (150 $\Omega$ ) screen grid resistor R29 was returned to the

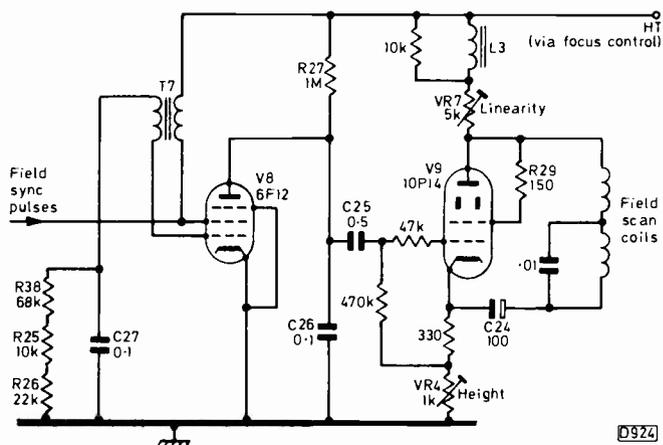


Fig. 2: The Baird Everyman's field timebase circuit. The network R38/25/26 forms a fixed field hold control, resistors being shorted out as required. The output valve is operated as a triode, with the scan coils a.c. coupled via C24.

valve's anode, so the valve was being operated as a triode.

All in all then the set was an interesting exercise in circuit economy. Given more modern valves, the count could have been further reduced. With a single field timebase valve, a combined video/sync valve, a stick e.h.t. rectifier and germanium diodes for signal detection, the count would have been little more than that of a contemporary radio receiver!

# Service Notebook

George Wilding

## HUM PROBLEM

The problem with an ITT hybrid colour receiver (CVC8 chassis) was a broad hum bar plus a pronounced hum from the speaker. This suggested either impaired smoothing or an open-circuit diode in the l.t. supply bridge rectifier. The 1N4001 bridge rectifier diodes all proved to be in order, so the next move, after taking the usual precautions, was to stab a 25 $\mu$ F electrolytic with long wire leads across each of the h.t. smoothing electrolytics. These range in value from 25 $\mu$ F to 200 $\mu$ F in this chassis, but if shunting a 200 $\mu$ F electrolytic with a 25 $\mu$ F one results in any diminution of the fault you can be reasonably sure you've located the culprit.

Before shunting the various electrolytics I checked with a meter to see which tags carried h.t. — discharging the test capacitor to an earthed point would produce a big and possibly damaging spark. While doing this I found a reading of about 11V on one of the tags under a multiple electrolytic can. This tag turned out to be the common earth one for the unit. The print path across the panel was followed and found to be terminated by a large soldering tag, and just touching this with the positive test prod produced some sparking. Anyway a touch with the soldering iron cured all signs of hum.

## EHT FAILURE

The raster had suddenly disappeared on a Philips Model G20T300, leaving the sound unaffected. Failure of the e.h.t. of course, and the likely suspects were the line timebase valves, the boost capacitor C2064 and the line output transformer. On removing the back, we noticed a small

solder blob near the top leadout wire of the boost capacitor, which is vertically mounted on the panel. This suggested that the line output transformer had almost certainly been changed recently and could be eliminated from the list of suspects. This proved to be the case, a new PL504 line output valve restoring the e.h.t. Now why did that solder blob give us a clue?

Well, if you can obtain only a very small spark at the anode of the PL504, the next step should be to remove the boost diode's top cap and see whether h.t. is still present at the anode of the PL504. If so, and in the event you'll probably get a hearty arc, then either the boost capacitor is short-circuit or, as happens quite often in these sets, there's a short between the secondary windings L5022/3 on the line output transformer and the primary winding. The easiest and quickest way of deciding which is at fault is to eliminate the capacitor — it's soldered at both ends to connection points on the i.f./line timebase panel, so you can simply cut the top leadout wire. If h.t. is still present at the PL504's anode, the transformer's insulation has broken down. It was clear then that someone had investigated a no e.h.t. fault recently and, having found that the boost capacitor was o.k., had resoldered its lead and replaced the transformer.

## PICTURE DEFECTS

The picture on a Pye hybrid colour set was said to "go into lines" after about twenty minutes, while at other times it would tend to fade and become "fuzzy". On switching on, quite a good picture was obtained, but after some minutes the picture was suddenly blotted out by a black-and-white check pattern. The pattern looked as though a signal generator had been applied, but vanished within seconds. Ten minutes later the picture started to fade away, with at the same time a steadily increasing type of noise being superimposed on it — not the usual grainyness you get with

inadequate aerial input, but more like minute horizontal streaks.

The nature of the noise suggested that it was subject to high amplification, implying a fault in the tuner or the first i.f. stage. The picture then improved, and within some minutes was tolerable. Well, the i.f. panel in these sets is extremely reliable, so it had to be the tuner. It's mounted on a small, easily removable panel at the side of the cabinet, so even I could change it reasonably quickly.

Changing varicap tuners with their five leadout wires and four lugs can be irritating and time consuming in some sets, so I usually get young Ian (the chip off the old block!) to do it for me. He can do it with incredible speed, and the secret of fitting the replacement is apparently first to repeatedly drive a stiff piece of wire through all the PCB holes. Then check that all the leadout wires are straight and parallel, and make sure that they are vertical, or if anything very, very slightly inclined towards the opposite edge of the tuner. You must now position the board so that you can see beneath the tuner. First fit one lug on the side nearest the leadout wires, insert the nearest wire in its hole, and continue along the board. If any wire is slightly nearer to the opposite edge than it should be, it can easily be pushed back and into its hole using a long, thin screwdriver. Don't waste your time, and risk repeatedly bending the leadout wires, by attempting to position the wires and lugs precisely and then drive the tuner home.

Anyway, the new tuner in the Pye set cured the symptoms and produced a fine, grain-free picture.

### CURIOUS SYMPTOMS

The picture and sound on an ITT hybrid colour set (CVC8 chassis) would intermittently vanish, leaving a very strange visual display and only an unusual type of "vision buzz" from the speaker. The raster would become green, with no modulation or noise except for about six two-inch

multicoloured bars near the left- and right-hand edges of the screen. The set might revert to normal operation within a few seconds, or remain in the fault condition for an hour or so.

Simultaneous loss of the sound and vision suggested a fault in the i.f. or a.g.c. circuitry. There are one or two fairly well known faults that occur on the signal side. The TAA550 voltage stabiliser i.c. for example can go short-circuit or develop less than the normal voltage, giving complete loss of signals (though sometimes sound from a foreign radio station can be heard). Then a faulty a.g.c. transistor (T41) or diode (D45) can result in an overloaded picture with weak or no sync. The clue in this case is incorrect voltage across the a.g.c. smoothing capacitor C114 (50 $\mu$ F). Neither of these faults would produce the bizarre symptoms present this time however.

A start had to be made somewhere, so we checked the voltage across C114. This should be 1V with no signal and about -1.1V with an average strength signal. We measured several volts however, so clearly the a.g.c. circuit wasn't operating normally. Both the transistor and the diode were o.k., while replacing the gating pulse coupling capacitor C235 made no difference. This pulse comes from tag 4 on the line output transformer, so it seemed logical to remove the line output stage cover and take a look at the connections to the pulse winding. There are five tags in a row near the bottom of the transformer subassembly board - and all were almost bereft of solder! Resoldering all five tags restored normal results.

When discussing the matter with ITT, we were told that the most common cause of troubles in this area is when tag 3, the chassis connection to the pulse winding, is dry-jointed or open-circuit. The earthing wire from the transformer's subassembly board to a tag on the transformer's core fixing clamp can also be dry-jointed. In addition it's advisable to check the transformer assembly clamp fixing nuts which hold the transformer to the cage assembly.

# TV Tussles

Nick Lyons

THERE are times when I seriously wonder whether TV sets have some inbuilt evil intelligence. You may think this a strange statement, but it's made after careful consideration of the evidence. Haven't you noticed for example how sets can smell a public holiday a mile off, then start dying en masse? Then a mere word of praise as to a set's reliability will immediately provoke clouds of smoke and pungent odours from within.

With all this in mind, it came as little surprise when after my last attack on Thorn sets the species launched an all out assault on me. I won't go into the full details, merely mention a couple of examples.

"The picture's dwindling away" the customer mournfully told me on the phone. On arrival the picture had dwindled to oblivion, and had clearly been en route there for some weeks. The set in question was a transportable fitted with the 1400 chassis. Off came the back and a PL504 with its top a most singularly pure white was revealed. In with another, switch on, and wait. Eventually a narrow picture with rather poor horizontal linearity presented itself, then dragged itself out to full width over the following two-three

minutes. Changing the PY801 boost diode improved matters, but the line oscillator's frequency moved around quite a bit once the set had warmed up, so in went a new 30FL2 as well.

### Problem with a Plastic Case

I'll digress at this point to tell you that when a set's at a convenient level with the back off I frequently lift it by putting my hand under the back edge of the top. It's very easy to lift a set an inch or two off the bench in this way, and to swivel it around to look at the back or the front.

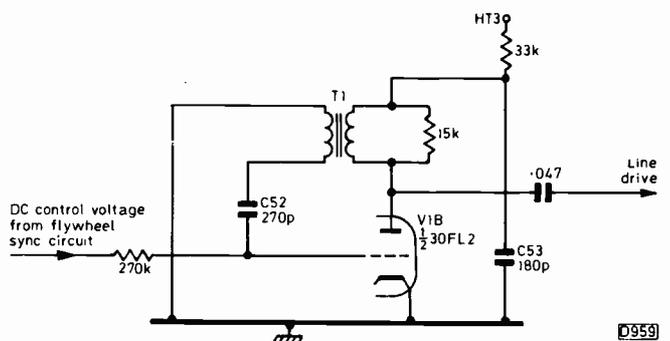


Fig. 1: The line blocking oscillator circuit used in the Thorn 1500 chassis. The weak spot here is the charging capacitor C53, which can cause intermittent line tearing when leaky.

With some sets, such as the Thorn 1400 under consideration, there's a handle on top to make this easier still. So I was rather astounded when, after fitting the new 30FL2, I picked up the set to swivel it around and look at the picture and, with the set half way round, there was this distinct crash. The set had fallen the two or three inches to the table top. Butterfingers you're thinking. Well, not quite, because I was still holding the top part of the set. The rest of it had now assumed a more stable, though fractured, pose on the table – the case looking like a half peeled banana. And all this in front of the customer!

What else to do but dive into the tool box in search of Araldite? No luck of course. But the customer, when he'd recovered from shell shock, managed to produce a tube of Bostik, with which I hastily glued the thing back together. Mercifully it had come apart at the joints only – the so-called dovetails that hold the top on – and when the repair was completed you couldn't see the join.

### Explosions

I supplied another customer, a noted bad payer, with a reconditioned 1500 on the cheap. So I was a little wary when she called to say that it had blown up. I replaced the offending mains filter capacitor, but was told it couldn't possibly be that as the set had gone off with such a loud bang. I switched the set on, and it produced a picture. Then, just as I was about to leave, the line oscillator dived off lock and next ceased to oscillate at all.

"I told you" she moaned, then repeated the description of the Hiroshima like explosion the set had apparently produced. The PL504 was now overheating of course, and an Avo connected to its control grid confirmed the lack of line drive. The anode of the line oscillator mustered just 2V, due to the 180pF charging capacitor C53 being virtually short-circuit (see Fig. 1).

### The Rediffusion Mk. I Chassis

So much for Thorns then. The Rediffusion Mk. I chassis is not something you very often find in private ownership, and those not connected with Rediffusion might find it a little strange. I've only recently inherited a pair of them, and hope that my follies when trying to recondition one of them may serve as instruction for others. The basic problem was that the set had more than one fault, and that I kept making dubious assumptions.

For those not familiar with the chassis I should perhaps first outline the basic features. It's a hybrid design, with just two valves (PY500A and PL509). Most of the rest of the circuitry uses discrete transistor stages, there being only one chip (TBA750 for intercarrier sound). There's a mains transformer for the l.t. supply and the valve and tube heaters.

So now to the reconditioning exercise. Switch on and get sound (lovely tone – two speakers and a tone control) but not much by way of a raster, though the e.h.t. rustled up. Find internal preset brightness control, on timebase board, but adjusting this produced no more than a mid-grey, totally unmodulated raster (it sets the bias applied to the c.r.t. grids). Next, my first mistake. The RGB output transistors are all of the BF337 variety, fed from the 200V h.t. rail via 6.8k $\Omega$  load resistors. I measured the collector voltage of each using, second mistake, an Avo. There was 200V or so at each collector. First misleading and time-consuming assumption: there must be something wrong with the drives. Much fruitless stabbing around was undertaken before I did what I should have done in the first

place – get out the scope. On looking at the output stages, all was revealed. There was no h.t. at the collectors at all! So what was the 200V the Avo stubbornly displayed? The scope revealed this also – a great line rate pulse of about 600V amplitude. If I'd looked at the circuit more carefully I would have foreseen this. There's feedback clamping in the RGB driver/output stages you see, and the Avo was simply giving average value readings of the clamp pulse voltages. The moral I suppose is to spy out the territory first, and to treat meter readings with suspicion where pulses abound. In the event, all that was wrong was that the 1.2k $\Omega$  power resistor R602 was open-circuit, removing the 200V h.t. line.

Having replaced the power resistor (R600 + R602) we were rewarded with rather a nice picture – but in monochrome. After my initial dismal efforts however I felt that tea was in order, and decided to take advantage of the monochrome picture to set up the convergence. Anything to avoid getting into a tussle with the decoder. The convergence set up very well, and as the tea ran out I'd no more delaying tactics.

I must have convinced myself that something complex was wrong, because instead of simply going through the chroma circuits with a scope I resumed picture diagnosis. Weak colour could in fact be obtained by careful tuning and turning the colour control to maximum. So a considerable time was spent setting up the decoder. Almost adequate saturation was obtained, but with the colour control still flat out.

Bring out the scope again. Pin 6 of module 4 on the i.f. strip (chroma take-off point) showed a healthy chroma envelope, as did TP12 (collector of the second chroma amplifier) on the decoder board. The same could not be said when the check was made at the collector of the third chroma amplifier transistor TR205. In fact the transistor had failed. It's a BF194, but I never have any of these. So a BF597 went in instead and proved to be an excellent replacement – vast levels of chroma were now available, and my problems were at last at an end.

The picture quality that can be obtained on these sets is good – the equal I'd say of my favourite of the era, the ITT CVC5 chassis. "In house" components are not generally used, good quality, well known semiconductor devices being the order of the day. BF337s, BF194s, 1N4148s etc, making replacements simple. The chassis doesn't seem to rely desperately on the parameters of particular devices however, and seems to be very tolerant of any substitutions that are made. This is not true of some chassis, and is important I think with sets of this age, since the fewer the components that have to be kept in stock the cheaper the sets are to repair and the less likely you are to end up with unwanted bits and pieces when the sets are eventually scrapped.

The construction of the set is reasonably good, though there are many panels dotted about at various levels and angles to one another. This is not as bad as it sounds, since the boards are for the most part easy to get at, and unclip and unplug for easy swapping about. The hardest bit to find is the power supply. It's behind the main chassis, which must be removed for easy access. There's a cut out in series with the mains fuse: it carries the line output valve's cathode current, operating when the line output stage is overloaded. There were various versions, some standard aerial ones, others video monitors and CATV ones for carrier distribution systems.

*Editorial note:* Some fault notes on this chassis were published in a letter in our December 1978 issue (page 72). ■

# Long-distance Television

Roger Bunney

THE events since the last column was written have certainly been dramatic! Australian ch. A0 signals have been received in the UK on several occasions, and there's a suggestion that New Zealand ch. 1 may have been received just above the noise.

The day after the last column was posted to the magazine Hugh Cocks rang to report that weak line syncs were visible on ch. A0 (this was at 0825GMT on October 28th). Here at Romsey unfortunately considerable Russian interference meant that only the basic sync information was visible. There was sufficient however to confirm the presence of a video signal. The programme content subsequently noted at Hugh's E. Sussex location consisted of a newsreader. Information that Anthony Mann has sent suggests that the signal was from ABMNO (Wagga Wagga, NSW). Channel A0 was received by Hugh on the 1st, 3rd and 21st of November during the morning period, and a definite identification of the new Australian ethnic service was achieved – a light entertainment programme in French.

My own *pièce de résistance* during the period occurred on October 29th, when a weak vision buzz, i.e. the vision carrier, was logged at an aerial heading of NEN at 0855GMT on 42.25MHz – the New Zealand ch. 1 allocation. The signal was audible only on a narrow-band radio receiver, attempts to display the video using a narrow-band TV receiver proving fruitless – all efforts were nullified by very strong adjacent frequency Russian communications signals. The 42.25MHz signal was steady but just above the noise level. It was present for some fifteen minutes, then faded – it hasn't been logged since!

Though Hugh Cocks is only some 100 miles to the east of my Hampshire location, we often find when comparing logs that particular signals varied considerably in quality (and even presence). Russian ch. R1 F2 signals for example generally rise above the noise earlier at my location, which is farther from the transmitter site, while the fade out times at the end of an opening also vary.



Reception of Chinese TV in Holland? This Asiatic newsreader was received by Henny Demming on ch. R1.

Russian F2 signals were less active during November than during the same month last year. During some periods, particularly after the middle of the month, nothing was present on ch. R1. Generally the openings have started later than in 1979, with earlier closing down. On October 29th there was F2 reception up to ch. R2 vision, and for the first few days during November reception from Russia was good. Farther into the month reception became erratic.

On the 15th there were strong Russian ch. R1 and Dubai ch. E2 signals. F2 reception improved again on the 21st, with ch. R1 and ch. A0. The long awaited ch. A2 System M signals from N. America first appeared on the 25th – at Hugh Cocks's location for two minutes at 1555GMT. They were preceded by an odd audio signal, CBC (Canada) at 50.7MHz. This is 4.5MHz below the ch. A2 vision carrier – the sound should be at 59.75MHz! Unfortunately 50.7MHz is saturated with interference here at Romsey. The 26th however was better for me, with two audible 55.25MHz carriers just above the noise level producing a difference beat of about 4kHz. The video couldn't be locked however due to the marginal signal level. What was very evident was a blockbusting Canadian amateur, V1ABX, calling CQ on the American 50MHz amateur band during the afternoon period.

F2 reception has been widely reported by readers, Cyril Willis (Ely) getting his first sight of Gwelo ch. E2 (Zimbabwe) on October 28th.

Sporadic E propagation also had its moments during the period, specifically on the 3rd, 16th, 18th and 20th – with sustained signals from RAI (Italy) on the 16th. There were also two small tropospheric openings. Signals were received from Switzerland and Germany (both East and West) on November 1st, in Band III and at u.h.f. Activity was noted around midday in the south and south east of the UK. The second opening was on the 20th, with a greater number of Swiss and German signals, DFF (E. Germany) being particularly prominent. The opening was widely reported throughout southern and eastern England.

The Leonids meteor shower produced signals during mid-November, with sustained Band I signals on the night of the 14th. Andrew Tett (Surbiton) received signals from as far as DFF, ch. E34. He's troubled with very strong Crystal Palace signals, requiring considerable filtering to minimise cross modulation from adjacent channels.

Conditions overseas have been excellent. Sustained F2 and TE (transequatorial skip) signals have been received in S. Africa, with openings lasting for many hours on many days, the signals at times being as high as chs. E4 and R2. David Maden (Vereeniging) received RTVE (Spain) chs. E2 and 3, RTP (Portugal) chs. E2 and 3, and RTVE Izana (Canary Isles) ch. E3, plus heavy interfering signals on chs. R1, 2 and E4. The openings sometimes commenced in the afternoon (around 1530) and continued until well after the local sunset (2200).

Anthony Mann (Perth) and Robert Copeman (Sydney) in Australia have been logging Chinese ch. R1 signals, while on the 6th and 8th of November, during the period 0900-1030GMT, Anthony received ch. B1 sound and vision. He notes that when the BBC ch. B1 audio or the TDF (France) ch. F2 audio is received after 1100GMT it has a characteristic TE flutter.

Solar activity was particularly high during the first week of November, with a count of over 300 on the 6th.

## News Items

USSR: A ch. R33 transmitter for the fifth programme, which is due to start in 1983, is being installed at the

Ostankino Tower in Moscow. The first programme is also to be transmitted at u.h.f.

**W. Germany:** Alexander Wiese comments that with the opening of BFBS-TV in W. Berlin there are now transmissions on five different standards in the city – systems B/G PAL, I PAL, L Secam, G Secam and M NTSC. The Canadian forces are likely to have their own TV service later this year.

**Belgium:** Dieter Scheiba reports irregular pirate TV transmissions on ch. E22. The video quality in the Brussels area is good.

**Australia:** As reported last month, the new ethnic/multicultural TV service has started in the Sydney and Melbourne areas, on chs. A0 and 28. Robert Copeman points out that the Sydney ch. A0 vision carrier frequency is offset at 46.26MHz. F2 DXers note!

**USA:** The Satellite Corporation of America is proposing a multi-channel direct transmission system to home viewers, operated on a subscription basis. Two channels would be used for nationwide coverage, with a further two channels serving selected areas via spot beams. Subscribers would rent/buy a decoder to unscramble the coded video. Receiving units with 1m dish aeriels are suggested. Thanks to Brian Fitch for this information.

### Satellite News

The Anglo-Swiss Telsat group hopes to start a satellite TV service on January 1st 1984, two launchings for the craft having been reserved. The venture is a joint British (45%) and Swiss (55%) one. Initially services in German, French and Italian are planned. "Excellent" reception should be possible in Switzerland, France, the Netherlands, Austria, most of Germany and North Italy, while considerable interest has been expressed in Holland/Belgium where there are extensive cable systems. Three of the Swiss channel allocations in the 12GHz band would be used. The RTL (Luxembourg) satellite, about which there's been considerable speculation in recent months, is likely to be delayed until the late 80s.

### From our Correspondents . . .

Mike Allmark (Leeds) has received many signals of all types during the past few months – signals from most of Europe, and recently from Russia and the UAE via F2. The fine test grid he's seen during afternoons to the south on ch. E2 comes from Ghana! During the excellent October tropospherics he received ORF (Austria) at u.h.f. – possibly a record distance. On June 30th on ch. E3 he observed a cartoon film and a second programme – the presentation of diplomas – on ch. E3. These signals were also received by Ryn Muntjewerff (amongst others) in Holland. The diploma presentation was by King Hussein via Jordan Television, Amman, while the cartoon film came from the Dhahran Aramco transmitter in Saudi Arabia. The latter station, often known at HZ22, recently changed from system M (525 lines) to system B (625 lines).

Gareth Price (Isleworth, Middlesex) has constructed an impressive wideband log-periodic array covering Band I through to Band III. We hope to see an article on it in the magazine in due course. For u.h.f. he uses a Vorta VPX22 wideband array. He visited the far east during October and reports that Malaysia uses the PM5544 test pattern on both networks, with no identification. The letters "RTM" are shown between programmes and during the news. When programmes are networked however two clocks are shown side by side, since part of the country is half an hour ahead of the rest (GMT + 7½ and +8 hours). The Singapore card

### GOLDEN ANODISED AERIALS: SUPERB ECONOMY AMPLIFIERS; ALL PRICES INCLUDE VAT.


Masthead Amps	Type	Gain	Price
Astrax 1456	A:B:C/D (TV)	10dB	£8.88
Astrax 1450 LN	Bands 4&5 (TV)	28dB	£15.49
Astrax 1455	Bands 1&3 (TV)	25dB	£16.81
Astrax 1470	Band 2 (FM)	25dB	£11.89
Astrax 1520	power unit for above amps		£9.15
i.e. An Astrax 1456 needs an Astrax 1520 =			£18.03

**IMPORTANT Quote TVM**  
For highly graphic lists and Brochure Send 52p. Refund of 30p on 1st purchase over £5.

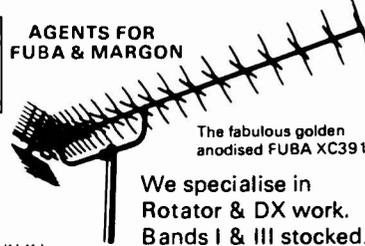**AGENTS FOR FUBA & MARGON**

Stockists of the finest aeriels available in Britain:

STOLLE FM aeriels (W.Ger.)  
FUBA TV & FM aeriels (W.Ger.)  
MARGON TV aeriels (Hol.)  
UKW FM aeriels (E.Ger.)  
ANTIFERRENCE TV & FM aeriels (U.K.)



The fabulous golden anodised FUBA XC391

We specialise in Rotator & DX work. Bands I & III stocked.

### ASTRA (GOLDEN D.I.Y.) AERIALS

A friendly family firm. Our 25th. Jubilee Year.

SOME OF OUR SUPERB TV & FM AERIALS.

Name	Group:W/Band	Gain dB	Price	Discounted
Margon 103 (TV)	both	19.5/21.5	£61.41	£52.19
Margon 91 (TV)	both	18.5/20.5	£44.16	£37.53
Fuba 91 (TV)	both	18.5/20.5	£48.61	£43.75
Optimax 14 (FM)	Band 11 W/B	14	£57.50	£48.88
Optimax 8 (FM)	Band 11 W/B	9.5/10.5	£32.54	£29.29
Fuba 8 (FM)	Band 11 W/B	10.5	£40.85	£36.77

Over 3,000 aeriels stocked, all transmitters, poles, lashings, rotators, clamps, wall brackets, amplifiers, duplexers, triplexers, notch filters, coax white or brown.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON, SURREY.


Nr. Spurgeons Bridge Tel: 01-684 4300  
Open 9.00-5.30 TUE-SAT. 01-684 5262

Closed 12.30-1.30 Closed All Day Mon. 24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY
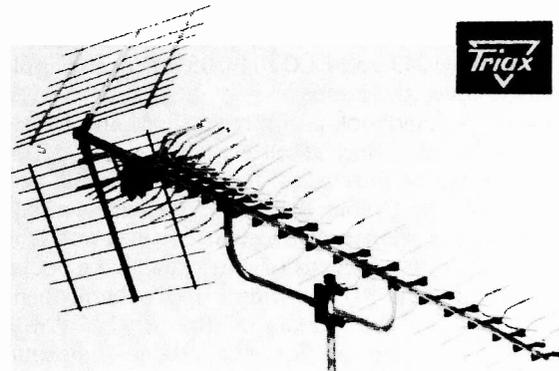
### South West Aerial Systems

10 OLD BOUNDARY ROAD,  
SHAFTESBURY, DORSET.  
SP7 8ND tel.0747 4370



This aerial is new. It looks like most Continental style systems – but it's different! Made in Denmark by the TRIAX A-S company, it features superior construction, more robust and 'solid' to handle with easier assembly. The director units are hinged, clip-in mountings; the dipole box is strong and condensation free; the reflector a 'slide-in' positive fixing; and gold anodised throughout. The Fuba company catalogue their classic XC391 at 16dB gain. Triax catalogue their Unix 92 at 16.5dB. With better performance, better construction, better price, TRIAX A-S have set a new standard in aerial technology.

Fuba XC391 (groups A, E/W, K) 16dB gain	£47.55
Triax Unix 92 (groups A, E/W, K) 16.5dB gain	£38.55
Triax Unix 44 (groups A, E/W, K) 14dB gain, rear mounting	£29.85

The above prices include VAT, packing and carriage.  
Our 1981 catalogue costs 40p. Include SAE with all enquiries.

(the PM5544 of course) has "SBC COLOUR" across the bottom – transmissions are in Band III only. Thailand uses System M and System B PAL, with no duplication of services on the two standards. In Bangkok an extra sound channel is available in Band II – this is often used to transmit the original sound track of a film that's been dubbed into Siamese. Dual-standard receivers with 14-channel turrets are available in the System M areas. On November 2nd, Gareth received G4CRJ using an ELC2060 tuner and his Vorta aerial.

T. S. Nanda Kumar (Madras, India) has had great success with Band I DXing. Various Indian and Pakistani stations have been received, plus Dubai and suspected Thailand.

Petri Pöppönen (Finland) received a ch. E2 signal via F2 on November 7th at 0935, possibly Malaysia. The blank PM5544 pattern, with no VITS, was followed by a programme at 1000GMT. Considerable F2 backscatter has been noted on ch. B1 – severe multiple images etc. Nicholas Brown's July 14th reception (see November column) has been confirmed as coming from Finland – "Hetkinen" means "just a minute please". J. Abbott (S. Africa) has received the Russian Stat T satellite (714MHz) using a 5ft diameter dish aerial with a head amplifier featuring 38dB gain and a noise figure of only 1.8dB. I'm hoping to devote some space next month to S. African reception of the satellite's 714MHz signals. Finally, Henny Demming (Holland) has sent in a large quantity of photos of F2 reception. Included are several of Asiatic newsreaders. These were received on ch. R1, at 0900-0912GMT on October 22nd, and are suspected Chinese signals.

### **Amateur TV**

Our mention of amateur TV activities in the 430MHz band produced quite a response. ATV transmissions lie within the spectrum 434-440MHz, with the vision carriers at 435 or 436MHz, and are often to the full PAL specification. Activity is rather sparse unfortunately, with pockets of active amateurs in London and the South East, East Anglia and the Birmingham areas. When conditions are good, signals from French, Belgian, Dutch and German amateurs may be picked up, with the call signs starting F, ON, PA and D respectively. The ELC2060 tuner will tune directly to 430MHz, as will receivers in the Bush TV161 series. The ELC1043 and ELC1043/05 tuners can easily be modified to cover the band.

A new ATV handbook is in preparation, and I hope to review this shortly. Specialised aerials for the 430MHz (70cm) band can be purchased, but some domestic aerials, such as the Wolsey Colour King, give reasonable results at these frequencies. Activity is irregular however and is most likely to be noted at weekends (if you know that a pocket of ATVers is not too far off) or during a tropospheric opening.

Our thanks to the editor of the British Amateur Television Club journal for the above information. Enquiries about membership of the BATC should be sent to Mr. B. Summers, 13 Church Street, Gainsborough, Lincs. – with an SAE please.

### **The JVC Model 3040UKC**

In the August issue last year I reviewed the Panasonic Model TR5030G, a small-screen dual-standard receiver offering scope for DX use. I propose to review two other sets offering similar facilities, the JVC Model 3040 this month and the Plustron Model TVR50 at a later date. Our main interest in reviewing these sets is to report on their suitability for TV-DXing in simple installations.

The JVC 3040 is a 5in. v.h.f./u.h.f. receiver with switching between System B/G sound (5.5MHz) and System I sound (6MHz). Coverage of the v.h.f. Bands I and III is provided by a varicap tuner, a mechanically tuned three-gang tuner covering u.h.f.

The JVC set is more attractive and convenient to operate than the Panasonic one, with the variable tuning controls for both tuners accessible on the front control panel. The band-switching and volume controls are also forward facing, likewise the loudspeaker. The v.h.f. tuning scale is circular and clearly visible, the ch. E2-4 spectrum covering 150° of the scale and chs. E5-12 a further 180°. The u.h.f. tuning calibration is visible through a small window, with channel number indications every two channels.

Attractive though the JVC set is, its suitability for TV-DXing is questionable. The gain at u.h.f. is good, the tuner's i.f. output passing via the v.h.f. tuner to the two-stage i.f. strip. At v.h.f. however the two i.f. stages do not provide sufficient gain to make the set suitable for DX use (something it wasn't designed for of course), particularly since the small number of tuned circuits make for a relatively unselective bandpass characteristic. As a result, there's considerable adjacent channel interaction – when for example ch. E2 and R1 vision carriers are both present. The lack of gain at v.h.f. could well lead to the unwary using a preamplifier, which would cause a further deterioration of the adjacent channel performance. The system switching introduces an 11.5MHz oscillator for 5.5MHz operation – its output is fed to a 6MHz tuned circuit, creating a 5.5MHz difference frequency.

Strangely, there's no brightness control, the screen illumination being adjusted by means of the high-level contrast control, which of course affects the video gain.

The aerial input to each tuner is via external screw terminals. The input impedance at v.h.f. seems to be 75Ω unbalanced (though no indication of the chassis connection is given), but at u.h.f. is 300Ω balanced, i.e. intended for use with ribbon feeder. So for optimum performance at u.h.f. the correct (300/75Ω balanced/unbalanced) transformer must be used (it can be obtained in the UK), while for v.h.f. use the correct chassis connection for the screen of the coaxial cable must be determined.

Field and line synchronisation on weak signals is good. The set can be operated off dry cells (nine 1.5V HP2 etc.) which fit in a compartment beneath. A whip aerial is fitted on the upper side of the case, with a spade terminal connection emerging adjacent to the rear aerial connection terminals.

The basic version of the set has little to recommend it for DX use at v.h.f., though it does have potential at u.h.f. (assuming that an aerial input matching transformer is used). The lack of a separate brightness control is a decided handicap.

In conclusion then, the 3040UKC receiver we tested is suitable for normal domestic use and, with reservation, for u.h.f. DX work. With modification, say an additional i.f. amplifier (this would certainly make it a "hot" u.h.f. receiver) and the addition of a rear mounted brightness control, the receiver could be a useful feature in a DX-TV installation, particularly as the tuning controls are well placed for easy operation. The use of a wideband i.f. system for DX reception presents problems however, as I've pointed out in the past (see the August 1980 column for example, page 556). Anyone buying one of these sets with a view to DX use should bear these shortcomings in mind.

My thanks to JVC for supplying a set for test and evaluation.

# Test Report: Thandar PFM200 Digital Frequency Meter

Eugene Trundle

ONLY a few years ago a frequency counter would have been considered to be an expensive and fussy laboratory instrument with no business on the service workbench. The situation has been changed by the all-conquering silicon chip, which has now come up with inexpensive and accurate digital counters. Of those currently available, we selected a Thandar (Sinclair Electronics Ltd.) PFM200 for evaluation.

## Frequency Meter Applications

Some of you may still regard a counter or frequency meter as an expensive luxury in the radio and TV workshop. With the exotic equipment we are called upon to service nowadays however such test gear finds many applications. Here are some of them:

Setting up the tape speed in audio tape recorders and decks, in conjunction with a standard test tape.

Checking local oscillator frequencies in a.m. and f.m. superhet receivers.

Setting transmitter frequencies for amateur radio, model control, etc.

Adjusting infra-red and ultrasonic remote control transmitter and receiver units. These are very widely used in TV sets nowadays, and the idea of remote control is beginning to spread to certain makes of audio equipment.

Setting up timebases and subcarrier oscillators in TV receivers.

The applications for a frequency counter with VCRs include setting the f.m. deviation for video record f.m. modulators, the carrier frequencies in the colour signal processing circuitry, and the capstan speed. With VHS machines, the final check on the capstan speed consists of verifying a 3kHz tone on the VHS video test tape.

Calibrating and checking test equipment and signal sources.

Identifying quartz crystals.

Checking the clock frequencies in computer and other digital circuitry.

## The PFM200

In appearance the Thandar PFM200 looks rather like a large pocket calculator. In place of the keypad there's a single four-position slider switch which sets the gate time or sampling rate and a single slider switch for function setting. The readout consists of an eight-digit LED display which indicates the applied frequency in kHz, with automatic digital point placement.

A very wide frequency range (20Hz to 200MHz) is covered without range switching apart from the two-position function switch. The sensitivity is typically 10mV, with a safe input level approaching 1kV at frequencies below 1kHz. Accuracy, the most important factor in a frequency counter, is typically  $\pm 2$  p.p.m./ $\pm 1$  count, a very acceptable figure. The instrument is portable indeed, weighing less than  $\frac{1}{2}$ lb (200gm) and being powered by a PP3 type battery (operation from an a.c. adaptor is possible). Test leads are provided, along with an operator's

manual and a protective wallet.

Inside the PFM200 there are four i.c.s and nine transistors. The circuitry is based on a 10MHz crystal clock oscillator, a 28-pin jumbo chip containing all the counters, timebases, decoders and drivers for the LED display. With the low signal levels and "quiet life" that this sort of instrument enjoys, electrical failure is unlikely and a long trouble-free life can be expected, provided that care is taken in handling it and that expired batteries are removed.


We were sufficiently convinced of the virtues of the PFM200 to purchase one for the workshop. This has enabled us to evaluate the instrument at leisure, with no deadline for its return.

In the general m le of television field servicing a counter is seldom required. In other electronic fields it could be an important tool – for the mobile man concerned with transmitters, data links and industrial electronics for example. It could also we imagine be a boon to the friendly Post Office engineers who minister to radio amateurs and trace interference for radio and television users.

Many applications were found for the PFM200 in the workshop – in the audio, video and TV departments. On receipt, our first action after fitting a battery was to connect the meter to the best frequency standard we know – the locked reference oscillator of a working colour TV set. Up came the display at 4433.617 – not bad at all! A slight tweak of the calibration trimmer brought up 4433.619, and this calibration has held steady over a period of six weeks to date. Tongue in cheek we then used the instrument to check



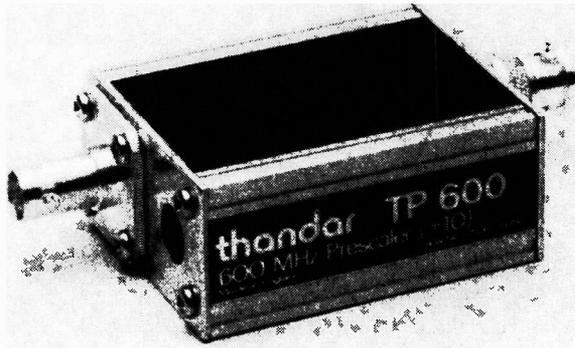The Sinclair/Thandar PFM200 digital frequency meter.



The Thandar TP600 frequency prescaler can be used to extend the upper frequency limit of most frequency meters, including the PFM200, to 600MHz. The sensitivity is better than 10mV r.m.s. and the suggested price £37.50 plus VAT.

the parameters and calibration of some of our workshop test equipment – and discovered some surprising and embarrassing inaccuracies (in the equipment, not the PFM200!).

The instrument works basically by counting the zero crossings of the test waveform, and it's important to bear this in mind when checking sources containing beat frequencies or heavy harmonic distortion. It would be a bit naïve for example to connect the counter to the i.f. input of the working envelope vision detector of a TV receiver and expect to see a readout of the i.f. at 39.5MHz without further filtering. We found generally that it helped to know in advance roughly what frequency was to be expected.

Many of the applications we found for the counter didn't call for anything like the full accuracy of the instrument. For these a shorter gate time can be selected, giving the advantage of a quick settle-down time. Many short cuts were discovered in applications where equipment manufacturers' setting up procedures were based on the assumption that a counter was not available. This has resulted in much time saving. When looking at low-level

signals from a high source impedance we found that an oscilloscope type 10:1 probe was useful in reducing circuit loading and avoiding misleading readings, though this type of probe will not work up to the counter's full 200MHz capability. Since its arrival in the workshop the counter has been much in demand, spending its time shuttling between the TV, audio and video sections.

We found our instrument better than its sensitivity specification at 1kHz, and at the other end of the scale we were quite happy to plug the test prods straight into the mains socket. Donning our executioner's hat, we next subjected the poor little counter to a source of 800V line flyback pulses, using the attenuated input. We were rewarded by a rock-steady reading of 15.625kHz with no signs of distress.

If the instrument is in fairly constant use in the workshop a suitable a.c. adaptor would probably pay for itself – PP3 batteries must be about the most expensive form of energy going in terms of pence per milliampere-hour, and the current consumption of the PFM200 (20-60mA) is rather hard on these little batteries if used for prolonged periods. Most of this energy is spent lighting the LED display, which is perfectly readable even within a foot of a 100W bulb and reflector. The visibility is aided by a tilted display and purple filter, the viewing angle being wider than that of a pocket-calculator readout.

### Conclusion

Nobody could say that a 200MHz counter at under £60 is not good value for money! The Thandar PFM200 seems to be a very good counter, though we must admit that our previous experience of digital frequency meters is rather limited. An LCD display would have reduced the battery consumption considerably, but no doubt there were good reasons for adopting the LED system. The frustration and time we've saved since investing in the PFM200 is considerable, and we regard it as money well spent. The PFM200 is available from Thandar stockists at £57.27 including VAT. ■

# Fault Report

*Derek Snelling*

## TANDBERG TROUBLES

The problem with a Tandberg colour set (CTV2-2 chassis) started a few weeks back. The report was of reduced width, and sure enough on inspection there was a lin. gap at either side of the screen. This could be removed by adjusting the width control, which sets the bias in the EW raster correction circuit. A quick check on the associated resistors revealed nothing amiss, so the control was left at its new setting. A week later however the set was back again with the same fault, and this time the width control couldn't be adjusted for a full width picture.

Nothing amiss could be found in the width circuit, so we thought maybe the line output transistor's gain was low. A new line output transistor had no noticeable effect however, so the transistors in the EW raster correction circuit were checked. This got us nowhere, so rather belatedly we checked the e.h.t. – the height was normal, but the field scan tracks the e.h.t. since the supply for the height circuit is

obtained by rectifying pulses obtained from the line output transformer. On switching on again, the e.h.t. went off the scale (over 30kV). I switched off hastily and wondered what X-ray dosage I might have received. What could be wrong? The h.t. was correct, so the next thought was that maybe the flyback tuning capacitor C754 was doing something funny – I remembered from a lecture I'd attended that it was a special component. Anyway, a replacement cured the problem, and it's worth noting that only the correct type, obtained from Tandberg, should be used. In fact it's several capacitors in one, hence the width reducing in stages.

A week later another of these sets came in. This time the card said "set dead". Switching the set on produced loud arcing noises from the back however. Not exactly my idea of "dead", so we hastily switched off. Next we switched it on and off briefly whilst looking in the back, and noticed flashes from the power supply can. A ha! I thought, a dry-joint in the power supply (it's happened to me a couple of times). Now in this chassis the power supply is enclosed in a metal can, which is fixed with awkward non-standard screws with vaguely hexagonal heads. They usually call for the use of a pair of pliers. A five minute struggle revealed the power supply – but no sign of arcing.

Another brief switch on revealed the awful truth. What I'd taken for arcing in the power supply had in fact been a reflection in the metalwork of arcing higher in the set – coming from the scanning yoke in fact. Very unusual.

Removal of the blue convergence segment revealed a small burnt patch and, worse still, a corresponding hole in the neck of the tube. Luckily the customer had a four year tube guarantee, with six months left, so all we had to do was to persuade the manufacturer that the broken tube neck was not the result of a blow with a blunt instrument.

The replacement tube arrived four weeks later, and in it went together with a new convergence segment. Switching on produced a few loud bangs followed by a high-pitched buzz/whistle. This sound meant either a heavy load on one of the outputs from the power supply (it's of the blocking oscillator chopper type, as in the Rank T20 chassis), or a fault in the power supply itself. The latter proved to be the case, so two new transistors and a new trigger thyristor were fitted.

I decided this time to power the set from a variac, slowly increasing the mains voltage whilst monitoring the line output stage h.t. and e.h.t. supplies. By the time the h.t. had reached 100V (the normal line output stage h.t. voltage is 160V), the e.h.t. had already risen to 25kV. The cause of the original tube failure was now clear – excessive e.h.t. – and remembering the previous set a new flyback tuning capacitor was fitted.

This cured the basic problem, but a glance at the screen revealed a bright raster with flyback lines. Obviously the arcing had damaged other components. So we checked the RGB output stages, where we found the red output transistor short-circuit. We also found the TBA530 matrixing i.c. faulty. These were replaced, but on switching on the only noticeable difference was a slight picture in the background. In an effort to reduce the excessive brightness, the beam limiter and c.r.t. first anode controls were turned to minimum, producing a viewable if slightly bright picture.

At this point the height began to decrease, and a wiff of smoke came from R816. This is the surge limiting resistor (47  $\Omega$ ) in series with the rectifier (D806) which produces the negative supply for the height circuit. D806 was short-circuit. Replace D806 and R816. Switch on once more and closely inspect the picture. Lack of width, pincushion

distortion, and severe convergence errors. Adjustment made no difference, and in the end we cleared the first two problems by replacing the EW modulator driver transistor Q853 (2N5298) and the latter one by replacing all four transistors in the R/G vertical convergence circuit (the set has a 110° delta gun tube).

This left me with the "minor" problem of excessive brightness. The first anode voltages were correct, and the matrix i.c. had been changed earlier. This suggested something amiss in the luminance/beam limiter circuits. Unfortunately the circuit gives few voltages in this area, so that fault-finding is not easy. I decided that the TBA500 luminance i.c. was the most likely suspect, since i.c.s are rather susceptible to high-voltage spikes. Not this time however: all the voltages were substantially correct. So out came the scope, which revealed that the signal was being lost somewhere around the i.c. Perhaps the beam limiter, which acts on pin 6 of the i.c., was responsible? A closer look in this area revealed that R248 (15k  $\Omega$ ) was open-circuit (see Fig. 1). This would result in the c.r.t.'s grids being at a much higher than normal voltage. There's a moral here of course: when dealing with excessive or inadequate brightness, don't forget the tube's grids.

So there it was. After replacing R248 we had the set working correctly. But why the failure of C754 had on this occasion produced such dramatic results compared to the earlier occasion remains open to speculation.

## EW FAULTS ON THE G11

Just recently I've been plagued by Philips/Pye G11 chassis with EW raster correction faults. They fall into two categories: the easy ones, where the fault is due to a dry-joint on the modulator transformer L3137 (usually pin 3) or failure of the EW driver transistor T2150 (BD238) on the timebase panel, and the ones you get on the twelfth floor of a block of flats (that's where I encountered the next one anyway). A quick check showed that T2150 was short-circuit, and thinking that this would be all that was required I replaced it and switched on. The new transistor lasted a few seconds, then failed, accompanied by the smell of burning. Oh dear.

The burning smell seemed to come from the line output stage panel, and a quick check here revealed that L3134, which is in series with T2150, had melted, while the modulator transformer L3137 looked a bit charred. I didn't have either with me of course, so back I came next day. Replace T2150, L3134 and L3137 and switch on. Lack of width and another dead T2150. Check the diodes in the modulator circuit, and discover that D3132 is short-circuit. I didn't have one, but I did have a replacement line output panel – twelve floors below in the car. In due course the replacement panel was installed and yet another BD238 was fitted, and the fault had been cleared. Back to the workshop with the faulty line output panel.

D3132 was replaced and with the panel on the bench a dry-joint was spotted on pin 14 of the line output transformer. After repairing this the panel worked satisfactorily. I've had the problem three times since and, whilst L3137 usually survives and D3132 doesn't always go short-circuit, L3134 always melts, T2150 always fails – and there's always a dry-joint around pin 14 of the line output transformer (usually on the wire link connecting the transformer to C3128). So it pays to resolder these joints when working on the line output panel.

Finally the other diode (D3133) in the modulator circuit often goes short-circuit, blowing the 1A h.t. fuse (FS4037). Unfortunately it usually blows T2150 as well.

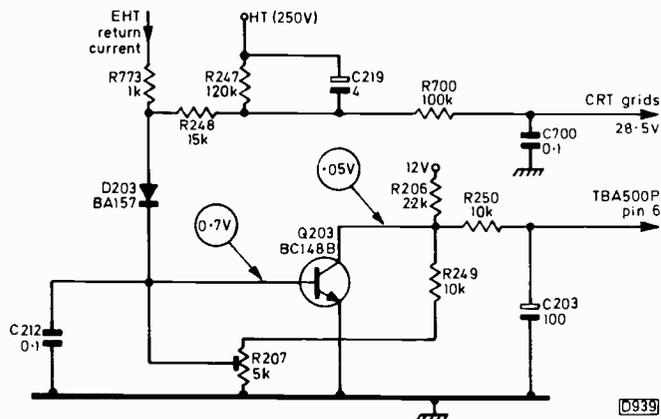


Fig. 1: Beam limiter circuit used in the Tandberg CTV2-2 chassis. The e.h.t. current returns to chassis via R773, D203 and R207, D203 being forward biased via R247 and R248. There are two modes of beam limiting. Transistor Q203 senses the voltage at the slider of R207. If this swings negatively, Q203 will begin to turn off, applying beam limiting to pin 6 of the TBA500P luminance i.c. This reduces the contrast, then the brightness. Should the beam current exceed the bias current flowing via R207, D203, R248 and R247, D203 will cut off. The beam current will then flow via R773, R248 and R247 to h.t., and the voltage at the junction of R248/7 will swing negatively. This negative voltage is applied to the c.r.t. grids via R700, thus reducing the beam current. R207 should be set for 1.1V across R773. This is equivalent to an average beam current of 1.1mA.

# Two-channel TV Sound

Harold Peters

COMING close on the heels of a superlative "Last Night of the Proms", which was "simulcast" to give stereo sound, Pat Hawker's November 1980 article on "Developments in TV Sound" has stimulated enough interest for some readers to want to know more about two-channel TV sound. Let's first recap on the basic requirements that have been laid down, and on the four techniques that have been developed to date.

The requirements are first that the quality of the sound should be to high fidelity standards – of the order expected from LP discs and v.h.f./f.m. radio, i.e. a flat frequency response to 15kHz. Secondly that in addition to stereo sound it should be possible to use the two sound channels for totally different signals, for example transmissions in two languages, with minimum crosstalk between the two channels. Thirdly there should be no reduction in the service areas of the transmitters. And finally there should be complete compatibility with the existing transmission system so that viewers with single-channel sound TV equipment are not aware of any change.

The first two-channel system, the pilot-tone technique used for stereo f.m. radio broadcasting, is a non-starter for TV since it's suitable only for stereo, the channel separation being inadequate for use with a two-language programme.

The second system is the f.m.-f.m. one currently used in Japan. In this system the second sound signal frequency modulates a subcarrier at twice the line frequency, i.e. 31.25kHz with a 625-line system. The two signals are then added, the resultant multiplex signal frequency modulating the r.f. sound carrier.

A totally different approach is to use digital techniques, with the sound signals interposed in unused sections of the line or field flyback blanking periods. The broadcasting authorities have been using a "sound in sync" system to distribute the present single sound channel TV signals for many years now. The sound signal is first compressed then converted from an analogue to a digital one. The resultant digital signal is inserted in the line sync pulse interval. At the receiving end, the signal is converted back to an analogue one, then expanded. All this presents compatibility problems, so that any system of this sort is only likely to come into use along with a new broadcasting system, for satellite TV for example.

The fourth system is the two-carrier one, with a second sound carrier spaced 242kHz from the present one. This system is currently on trial in W. Germany, which now insists that all future broadcasting equipment is capable of handling it, and seems the most likely one to be adopted elsewhere in W. Europe.

Another desirable feature is that the system should tell the receiver whether the sound being transmitted is monophonic, stereophonic or bilingual. The f.m.-f.m. and two-carrier systems both provide this feature by including in addition a pilot tone at 3.5 times the line frequency. The codes used differ however. The Japanese amplitude modulate the pilot tone at 922.5Hz to indicate a bilingual and at 982.5Hz to indicate a stereo transmission. The W. Germans frequency modulate the tone at 274.1Hz to

indicate a bilingual and at 117.5Hz to indicate a stereo transmission. In both cases mono is indicated by the absence of the pilot tone control signal.

## Dual-channel Receivers

It's the receiver side of things that's the main interest to readers of this magazine however, so without further ado we'll move on to this aspect of the subject. The following comments relate to experience to date with the two-carrier system.

Simple adaptors can be designed – and may well form the basis of future constructional articles. Trials to date however show that sets specifically designed for the job provide a worthwhile improvement in the results obtained.

The major snags experienced with trial receivers have been vision buzz and poor separation of the two sound channels – especially in the case of bilingual broadcasts, where the presence of a second commentary in the background is annoying. These problems occurred with sets using intercarrier sound however – the current convention. Changing to a "split-carrier" system was found to provide a cure to these problems – i.e. taking a separate sound i.f. signal direct from the tuner, as in many of the old 405-line only designs. With intercarrier sound, the separation of the two sound signals was 44dB at best. Using split carriers improves the separation to 56dB. A separation of 40dB is considered to be adequate (i.e. a little crosstalk can be heard if you listen closely), so intercarrier systems may yet turn out to be feasible, and could easily be improved using careful alignment and modern techniques. The same modern techniques however have made the split-carrier system less of a bogey than it has been.

Intercarrier sound has ruled the roost for so long because it's cheap to produce and because it's free from the effects of detuning caused by local oscillator drift – since you detect the *difference* between the sound and vision signals (6MHz), and because this difference is crystal controlled at the transmitter, the sound is always on tune provided the picture is locked in. Tuner drift is of the order of 1-2MHz, and the use of a separate 33.5MHz sound i.f. could have lost the sound signal during the first hour of viewing. The coming of colour made the problem worse, since the tuning of the colour subcarrier is as critical as that of the sound signal. Most sets now use a.f.c. therefore – while a.f.c. is mandatory for good teletext data capture.

The a.f.c. signal is normally taken from a detector tuned to the vision carrier: it produces a d.c. output proportional to the difference between the carrier fed to it and 39.5MHz. This is then applied to the tuner in the right phase to pull the oscillator back on to tune. The 6MHz intercarrier signal cannot be used for this purpose, despite what some textbooks suggest, because no matter how much the oscillator drifts the difference between the sound and vision signals remains the same – 6MHz. With a split-carrier i.f. system however it's possible to produce a very steep-sided a.f.c. action in the sound channel. This can be merged with the vision-signal derived a.f.c. to provide a stable tuning action.

The sound i.f. bandwidth requires careful tailoring. At present a sound i.f. bandwidth of  $\pm 200$ kHz is acceptable and can be achieved by using single tuned circuits of high *Q* or ceramic filters. For two-channel work however the bandwidth needs to be 200+242+200kHz, i.e. 642kHz, which can be easily achieved by simple tuning with a 33.5MHz split-carrier system but would require very careful bandpassing with an intercarrier system.

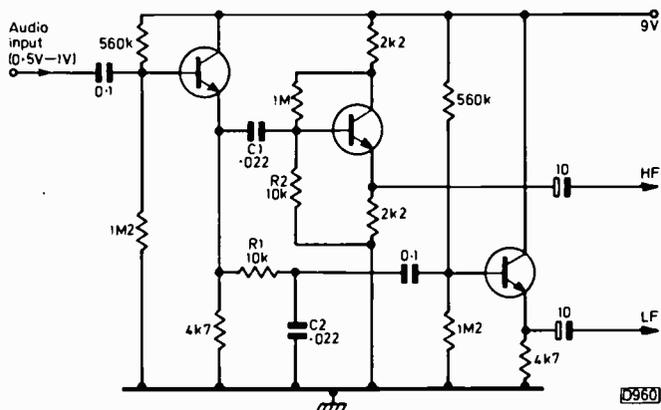


Fig. 1: Pseudo-stereo sound filter circuit – C1/R2 and R1/C2 filter out the h.f. and l.f. components of the sound.

Conventional detector circuits can be used, though the de-emphasis components need to be moved over to the other side of the decoding circuit. What's this? Well, for stereo operation L+R is transmitted on the main sound channel and L-R on the subsidiary channel. So to recover the L and R signals we have to do the same sorts of things we do in a colour decoder with the colour-difference signals, i.e. adding L+R and L-R gives us 2L etc. Once a system has been agreed upon, purpose designed i.c.s will take care of all this.

Having gone to all this trouble, if the set is specially designed for dual-channel sound it's worth arranging the audio circuits more along the lines of a high fidelity unit. Why not have tape input and output jacks, with a function switch to select mono/stereo/channel 1/channel 2 and a full tone control system?

Experience with the Philips K12 chassis shows that a

compact bass reflex enclosure with twin speakers is practical without running into purity and degaussing problems. One snag however is the typical size of the TV cabinet, which would separate the stereo loudspeaker system by only the width of the c.r.t. This is no problem with monophonic or bilingual programmes, but for stereo a greater sound spread is preferable. One way round this problem is to feed the h.f. component of one channel, suitably phase shifted, into the other channel. This gives the same effect as putting a phase switch in one speaker lead and appears to spread the sound. Not all programmes would need this treatment, so a switch marked "stereo extra" or something similar can be incorporated. All these arrangements can be d.c. controlled using i.c.s, which means that they can all come under the control of the remote armchair handset.

Moving the de-emphasis farther downstream permits the ingress of clicks and bangs from appliances, so transient suppression is required somewhere along the line.

*Andrew Flockton adds:* A synthetic form of stereo has been offered with some US TV receivers. They have loudspeakers at either side of the screen, driven by separate audio output stages, the TV sound signal being artificially processed to give a pseudo-stereo effect – rather like those records marked "mono recording electronically reprocessed to give a stereo effect".

The technique used is to split the signal at a certain frequency, sending all the signal above this frequency to one side and all the signal below to the other side. Apparently consumer response has been mixed – some find it worthwhile while others find it annoying. Interesting, but no substitute for true stereo. If anyone wants to try this out, Fig. 1 shows a suitable circuit. ■

**The Professional**


# COLOUR BAR GENERATOR kit

**TRULY PORTABLE**

**ONLY**

**£59.50**

*inclusive*

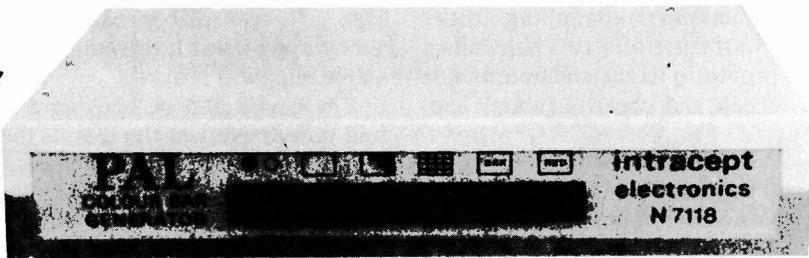

**Intracept electronics**  
N 7118

\*Compare the specifications with any kit or manufactured Colour Bar Generator on the market. Then compare the price. See Test Report in April 1980 Issue of Television.

**\*SPECIFICATION**

(a) Line Frequency: 15,625 Hz±0.1%

(b) Field Frequency: 50 Hz±0.1%

(c) Interlace: 2:1

(d) Subcarrier Frequency: 4.43361875 MHz

(e) Colour System: PAL

(f) Standard 75% Saturated 100% Amplitude Colour Bars, left to right: White, Yellow, Cyan, Green, Magenta, Red, Blue, Black

(g) Size 8" x 5½" x 1½" and weighs a mere 500g

\*Push Button Selection provides:

- (i) Peak White Raster
- (ii) Linearised Grey Scale
- (iii) Crosshatch
- (iv) Colour Bars
- (v) Red Raster

\*Direct connection to Television Aerial Socket

\* All kits are complete with a **PROFESSIONALLY FINISHED** Case, tinned, drilled and screen-printed P.C.B., step by step assembly instructions, and a simple setting up procedure (only **TWO** adjustments)

\* No extras to buy, not even Batteries. It comes complete with its own re-chargeable battery and charger (Approx. 10 hours running time per charge)

\* The backing of our After Sales Service Department

\* V.H.F. Modulator also available

\* Ready-built, aligned and tested for only £88.25, with a full twelve months guarantee

Also available with additional 1 volt p.p. 75 ohm video output. S.A.E. for details.

Prices inclusive of V.A.T. and Postage



**INTRACEPT ELECTRONICS LTD.,**

STOP PRESS. 5-5-6 mhz add on FM sound module now available.

203 PICTON RD, LIVERPOOL L15 4LG

Tel: 051-733 3042

# Active Sound Filter

Keith Cummins

THE circuit described in this article was adopted following problems with recording the sound from a television set (the famed *Television 625-line Receiver*) using an elderly Revox G36 audio tape recorder. Now the performance of this recorder is excellent – it can produce tapes that are virtually beyond reproach. It's input circuits do not include low-pass filters however, making things difficult when you want to record from a stereo tuner or a TV set.

In the former case the stereo difference signal, centred on 38kHz, can produce beat signals by mixing with the bias oscillator signal. The second harmonic of the stereo signal, at 76kHz, can do the same thing. Similar problems arise with the harmonics of the line timebase in a TV receiver, since they fall at approximately 31, 46, 62 and 78kHz. A TV set produces a lot of energy at line frequency, and when attempting to record the sound I found that a permanent whistle was present in the background. This was due to the difference frequency between the line harmonics and the recorder's bias oscillator falling within the audio passband. Only a small amount of line frequency signal mixed with the receiver's audio output is sufficient to produce a whistle.

## Filtering Arrangements

My first effort at dealing with the problem consisted of adding a simple RC filter. This was effective in reducing the whistle, but also reduced the audio response very noticeably at the top end. It was obvious therefore that a basic single-pole filter was not the answer: something more sophisticated was required. So the use of a two-pole active filter was investigated, and proved to be the solution. It was built around the popular, cheap and cheerful (about 25p) 741 operational amplifier i.c.

Fig. 1 shows the basic low-pass active filter using an operational amplifier. It will be seen that the output is fed back directly to the amplifier's inverting input. This means

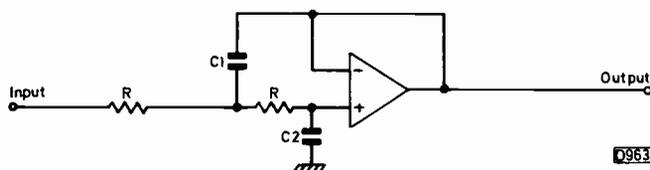


Fig. 1: Two-pole active low-pass filter, using an operational amplifier i.c.

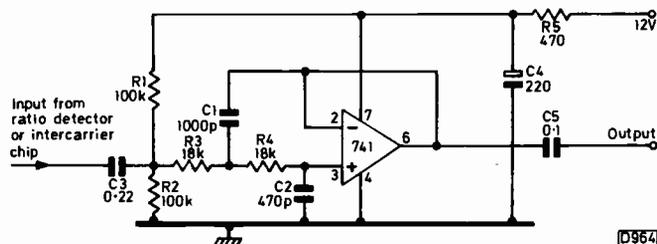


Fig. 2: Practical circuit, using a 741 i.c. The filter components R3/C1/R4/C2 give a corner frequency of 12.6kHz. If the impedance being fed is less than 50kΩ, the value of C5 should be increased to 4.7µF.

that there's 100 per cent negative feedback, the basic stage gain being one. The first step that has to be taken is to select the "corner frequency", i.e. the frequency at which the roll-off attains -3dB. For this type of filter a smooth roll-off at 12dB/octave is obtained by applying the formula  $f = 1/(2\sqrt{RC})$ . R is the value of the two resistors used in the circuit, while C1 equals  $C/\sqrt{2}$  and C2 equals  $C/\sqrt{2}$ . It follows that the value of C2 is twice that of C1. The corner frequency decided upon was about 12kHz – sufficiently high to cause minimal audio degradation while being significantly lower than the line frequency (15.625kHz). Making the value of R 18kΩ, C1 0.1µF and C2 470pF gives us a corner frequency of 12.6kHz.

The addition of the filter will ensure that line frequency harmonics likely to beat with the bias oscillator will be attenuated by about 30dB. Assuming that they are down 20dB to start off with, this gives a total of -50dB. Even a level of -40dB would probably be acceptable.

## Practical Circuit

The circuit shown in Fig. 2 was built up, with the operational amplifier biased at half-rail voltage by R1/2 since there's only one supply line. The output from the i.c. is of low impedance, which assists in preventing line-frequency pick up on the audio output cable following the i.c. The result of taking the signal via the filter was an instant success, the whistle completely disappearing. As a test, C1 was disconnected. The whistle then returned, though at a lower level than previously. So the effectiveness of the filter was proved.

The circuit can be built on a small piece of Veroboard, and positioned near the rear of the set, close to the take-off point. Note that the arrangement is safe only when the TV set has an isolated chassis (as the 625-line Receiver has). There's no reason however why the filter should not be used to drive a small audio isolating transformer directly, with the transformer suitably screened to avoid line pick up! In this case the circuit acts as a filter and buffer.

The filter is also worth consideration when the TV set is used to feed a high-fidelity sound system. Intercarrier sound systems often contain very high-order harmonics of both the line and field pulse frequencies. These can be responsible for a rattling kind of sound when passed through a wideband audio system. In reducing these harmonics the filter also reduces the bandwidth for out-of-band noise, thus improving the overall signal-to-noise ratio without drastically reducing the audio bandwidth itself. It can be argued that the de-emphasis network reduces such signals. This is undoubtedly true, but the filter described makes a much better job of it.

The supply voltage is shown as 12V. This is not critical, and the circuit would probably work quite satisfactorily if operated at 9V. There's no need to exceed 12V however – if necessary, increase the value of R5 to reduce the voltage applied to the i.c.

For those interested, a pair of these circuits can be used to filter the output from a stereo decoder should the 38kHz signal cause problems with a tape recorder. ■

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a 75p postal order (made out to IPC Magazines Ltd.), the query coupon from page 213 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## **RANK Z718 CHASSIS**

The problem with this set is that we can't balance the line output transistors. The initial fault was that the overload protection circuit would shut down intermittently. This situation continued after replacing the two line output transistors, so the output transformer was replaced. We then had the set going again, but when we tried to balance the transistors the voltage obtained across 5R6 was 20-15V a.c. instead of 1V or less.

Inability to balance the two halves of the line output stage is often due to failure of one of the flyback tuning capacitors 5C9/10, which should be replaced with Rank approved types. If necessary, check the condition of 5R6 (68 $\Omega$ ) as well and the components in the base circuits of the output transistors.

## **SONY KV1800UB**

The problem we have with this set is that the "horizontal converter" transistor Q802 (2SC1316) and the two transistors Q851/2 (2SA678 and 2SD291) in the e.h.t. regulator circuit have all gone short-circuit. Since the converter stage drives the tripler, with the regulator in the converter transistor's emitter circuit, we're wondering whether the fault is due to a tube flashover. Also, are there any equivalents?

These transistors seem to fail for their own reasons, and we doubt whether tube flashover is responsible – assuming that the h.t. has been set at the correct level (110V at the emitter of Q902). There are no equivalents for the 2SC1316, and the equivalents for the others are as obscure as the originals. The correct types should be readily available from Sony or their agents.

## **THORN 9000 CHASSIS**

The picture collapses to a single vertical white line, only momentarily and intermittently. The problem is worse when the brightness is turned up, but disappears at maximum or very low brightness settings.

The trouble is most likely to be due to one or more dry-joints on the line output transformer pins – some batches of these sets suffered from this problem. Also check the connections to the line scan coils, the Syclops transistor's emitter resistor R710 and the scan-correction capacitor C724.

## **PYE HYBRID COLOUR CHASSIS**

This dual-standard set has given good service for many years. For a long time however it has suffered from an irritating fault which varies in intensity from day to day for

no obvious reason. It consists of a pattern superimposed on the picture. If the a.f.c. control is muted and the tuning adjusted manually, the pattern can be tuned out, while still retaining colour, but as soon as the a.f.c. is restored the pattern returns.

First ensure that the various (braid) earthing leads are properly connected to the tuner and i.f. panel, and that the a.g.c. preset RV3 is not over advanced. If this does not solve the problem, the a.f.c. circuit will probably have to be realigned following the instructions in the manual. It's possible, though unlikely, that one or more of the small i.f. transistor emitter decoupling capacitors C10/20/27 etc. is open-circuit.

## **HITACHI CNP190**

The picture is perfect apart from about half an inch of foldover at the bottom of the raster.

We suggest you adjust the field output transistor's base bias. This is done by connecting a milliammeter between the 120V h.t. line, say at pin K5 of the deflection board socket or the positive side of C713, and the negative side of C607 in the field output transistor's collector circuit, then adjusting R617 for a reading of 64mA. If the fault persists, check the field output transistor TR37 (2SC936), its base input coupling capacitor C606 (100 $\mu$ F) and the driver transistor TR36 (2SA15V).

## **THORN 9000 CHASSIS**

Two faults have appeared simultaneously on this set. First, when the set has been on for about half an hour field flyback lines appear on the picture. Secondly the picture takes on a green cast – this comes and goes. No incorrect voltages can be found.

Field flyback blanking is carried out in the SN76227N colour demodulator/matrixing i.c., the blanking pulses being applied to pin 6. The first problem seems to be due either to loss of these pulses or the i.c. developing a fault when its operating temperature rises. Check for loss of pulses when the fault occurs – the problem could be a loose pin in socket 22 (pin 1) or socket 4 (pin 6). If this doesn't help, replace the i.c., which could also be responsible for the green cast fault since there's d.c. coupling from its outputs up to the c.r.t. cathodes. If the intermittent green cast fault persists, the set green bias potentiometer R194 could have a noisy track. This would affect the d.c. conditions in the green output stage. Other things to check if necessary are the green output stage transistors VT106/9 and the green gain potentiometer R190.

## **GEC HYBRID COLOUR CHASSIS**

The original fault we had with this set was that the picture would revert to black-and-white, no amount of adjustment of the fine tuning restoring the colour. On checking the a.c.c. circuit we found that the cause was the preset P401 having increased in value from 100k $\Omega$  to some 200k $\Omega$ . We next found that R704 on the pincushion correction panel had burnt out. This was replaced, using a higher wattage component, but then R705 cooked and burnt out. These components are on the line scan side of the correction transducer. What's causing this excess current flow? – there's no short across the transducer, the line output stage does not appear to be drawing excessive current, and voltage checks have shown no great discrepancies.

Your problem should be resolved by replacing the transducer. These components do develop shorted turns, which will not show up as a direct short-circuit. Thank you for the information on the colour drop-out fault.

### **ITT CVC20 CHASSIS**

The problem is intermittent foldover at the bottom of the screen – covering the bottom inch or so. Is there a common cause of this?

The main suspects are the field output transistors T9 and T10. First however check the output stage biasing network R62/R63/D7/R65, and for dry-joints in the field timebase – particularly around the NS phase control L7A.

### **SHARP 12P17H**

There's sound but no raster on this portable, so I suspect the 2SB468 line output transistor. There's 12V across it and an efficiency diode which reads o.k. on an ohms check. Is there an equivalent for the 2SB468?

The direct equivalent for the 2SB468 is the AU106, though the more generally available AU113 should do just as well. Since there's apparently been no fuse blowing or signs of distress however the output transistor would not be our first suspect. We suggest you check the supply to the line driver transistor – there are two  $\frac{1}{2}$ W resistors here, R717/8, both 56 $\Omega$ , and one will probably be found open-circuit. They are deliberately under-rated as a protective measure.

### **THORN 8500 CHASSIS**

The trouble was intermittent loss of colour, so a disturbance check was carried out on the chroma section of the signals panel. When C160 was moved, the colour reappeared and has remained. What action should I take if it goes off again?

The best procedure would be to override the colour-killer by shorting the base and emitter of VT113. This will give you an idea as to exactly where the fault is. You will probably get coloured bars on the screen, indicating that the reference oscillator is running out of lock. C160 tunes the oscillator output circuit and is often the cause of this problem. It can also be caused by the transistor (VT111) and the 4.43MHz crystal – the crystals used in this chassis tend to go off frequency. Complete absence of colour could mean that the burst gating pulses are not reaching the decoder due to the feed resistor R404 on the timebase panel having cooked up and gone open-circuit. There could on the other hand be chroma amplifier trouble. Check the transistors (VT115 and VT117), see whether the delay amplitude control R198 is open-circuit, and check C171 and C180 as these capacitors tend to go open-circuit intermittently. The MC1327P demodulator chip could be responsible for complete loss of colour, but this is rare indeed – the chip usually causes loss of one colour when defective. Another possibility is a defective d.c. amplifier transistor in the reference oscillator control loop – the f.e.t. VT110 – since this will upset the oscillator.

### **SONY KV1810UB**

The picture horizontals are correct, but there's quite severe vertical pincushion distortion – the verticals are being pulled into the corners as if the deflection magnets are all out of position. These are o.k. however.

The EW modulator transistor Q586 (2SC1124) is almost certainly faulty. It would also be worth checking D592 in Q586's base circuit.

### **INDESIT T24EGB**

The problem is lack of brightness – the picture is only slightly visible with the brightness control at maximum. The voltage at the c.r.t. grid is around 47V and varies little with rotation of the brightness control. The neon in the tube's

grid circuit remains on all the time, while the voltages in the video output stage are correct. Shorting the tube's grid and cathode produces a bright raster, so the tube is not suspect.

The neon is included to provide switch-off spot suppression, and should remain alight – it's in series with the feed between the c.r.t.'s grid and the brightness control circuit. The most likely cause of the trouble is simply that R230, which is in series with the brightness control, has changed value, though C215 could be leaky. Make sure that the spark gap associated with the c.r.t. grid is clean.

### **THORN 3500 CHASSIS**

I'm reconditioning one of these sets and, in the interests of reliability, would like your suggestions on what components to replace as a matter of course.

As with any chassis, the line timebase and the power supply give rise to the majority of faults. There are also some items on the video panel worth renewing. We suggest you replace the following:

**Power supply:** The h.t. electrolytics C602/3/6, the 30V supply electrolytics C607/9, and the chopper output electrolytic C619.

**Line timebase:** R528 in the h.t. feed, and the electrolytics C506/8/11 in the line generator circuit. It would be worth replacing the sensing resistor R907 on the beam limiter board.

**Video panel:** The clamp circuit electrolytics C215/27/31, C221 in the clamp bias circuit and the h.t. decoupler C222.

Clean the tracks of all the preset controls, and set up the receiver throughout, following the procedure laid down in the manual.

### **SONY KV1810UB**

This set has given good service, but recently the chopper and line output gate-controlled switches Q603/Q510 both went short-circuit, blowing the mains fuse F602. I can't find any fault that could have contributed to the demise of these rather expensive components. Any suggestions?

The only reasonably sure way we've found of avoiding a recurrence of this unfortunate fault is to replace all the following items: the mains on/off switch; the CX104A line/field oscillator chip; the electrolytics C624 (47 $\mu$ F) and C620 (4.7 $\mu$ F) on the power regulator board; the line drive coupling electrolytic C538 (0.47 $\mu$ F) and the flyback tuning capacitor C542 (1,800pF, 1.5kV) on the timebase board; and the two gate-controlled switches of course, making sure that you replace the mica washer on the chopper Q603. Check the condition of R608 and R642 on the power regulator board.

### **DECCA 30 CHASSIS**

There's an excellent picture on this set, but with some captions you get horizontal pulling – this happens mainly with film titles etc. I assumed it to be a sync fault, but replacing the valve and checking the bias components have made no difference.

There are two sync separator stages on this chassis, the first consisting of transistor TR202 on the decoder panel. Check its input coupling electrolytic C207 (1 $\mu$ F), and try adding a 6.8pF capacitor between its collector and base. Also check the video coupling electrolytic C200 (33 $\mu$ F). The beam limiting action takes place in the video circuit, the sensing point being the cathode of the line output valve. Its cathode decoupler C434 (100 $\mu$ F) is worth checking therefore. In this respect, you should get a reading of 2.2V at R37 on the i.f. panel. The problem could be in the line oscillator stage, and the PCF802 valve and its associated electrolytics C419/23/25 should be in good condition.

## GEC C2110 SERIES

When the set's first switched on there's a bright, non-linear picture about an inch high. The raster opens up to normal size after about ten-fifteen minutes.

The 40V line could be developing slowly. If so check the reservoir capacitor C601. Various components in the field timebase are suspect: the charging capacitors C457/8, the bootstrap capacitor C462, the bias stabilising thermistor TH451, R471 (220  $\Omega$ ) in the bias network and the output transistors. Make sure that the mid-point voltage is set for 23V at the junction of R466/7.

## SABA CHASSIS F

**There's lack of brightness on this set, even though the brightness and preset brightness controls are at maximum. There's plenty of contrast and colour, but the picture is dark.**

The main suspect is the PL802 luminance output pentode. Another possibility in the luminance output stage is the flyback blanking transistor T313 (BC238) – it tends to go open-circuit, with the result that the PL802's cathode voltage rises. If the PL509 line output pentode is conducting heavily, the voltage across the beam limiter control P632 in

## QUERY COUPON

Available until 18th February, 1981. One coupon, plus a 75p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 211.

## TELEVISION FEB. 1981

its cathode circuit will be excessive. This turns the beam limiter transistor T631 on, pulling down the PC92 luminance preamplifier triode's grid voltage. Check the setting of P632 therefore and ensure that the line output stage is operating normally. The other main possibility is that the c.r.t.'s first anode voltages are low. There should be about 800V at the top ends of the first anode preset controls P581-3. If this voltage is low, check the decoupling capacitor C724 (0.01  $\mu$ F) on the line output transformer panel. It sometimes goes leaky, pulling the voltage down.

# TEST CASE

## 218

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trix questions but are based on actual practical faults.

Many tales about fault-finding in the Pye Hybrid colour chassis can be told. Ours this month concerns a 693 chassis with the no colour fault symptom. The decoders used in these chassis are very reliable, so it was confidently expected that either the tuning had drifted off or that slight adjustment was required to the reference oscillator frequency control RV10. When we came face to face with the set however the tuning was found to be spot on while no amount of adjustment to RV10 would bring any colour to the picture.

RV10 was carefully returned to its original position therefore, and a check was made with the meter to ensure that the -20V and 15V supplies were reaching the decoder panel, also that a voltage from the colour control potentiometer was arriving at SK11. All seemed well, so a source of 2.5V was found and applied to TP21 to override the colour-killer. This made not a scrap of difference to the monochrome picture.

Out came the oscilloscope! With some difficulty, as we'd almost forgotten our way around this decoder, we established that the chroma signal was present at SK6, that the reference oscillator was running, that a good 10V peak-peak ident signal was present at the collector of the ident

amplifier VT18 – and that U and V chroma signals were emerging from the delay line! All the connections to the decoder panel were again checked, but no fault could be discovered on the decoder panel. So where lay the cause of this puzzling symptom? Answer next month, along with another item in the series.

## SOLUTION TO TEST CASE 217

– page 156 last month –

Last month we described a battle with a recalcitrant Tandberg CTV2-2 which would produce virtually no signals after having been fitted with a new u.h.f. tuner. Not once – two new tuners were tried.

The solution to this obscure problem lay in the band-switching arrangements. In this chassis a pair of BA182 switching diodes, D1 and D2, are inserted in the i.f. output feeds from the v.h.f. and u.h.f. tuners on the tuner/i.f. panel. The band switching applies a d.c. bias to the appropriate diode, thus turning it on so that the i.f. output from the selected tuner is passed to the i.f. strip, the other output being isolated. For u.h.f. reception, the relevant diode is D2, which is switched on by a d.c. voltage from the band switch via R5.

Now in the Mullard ELC1043/05 u.h.f. tuner unit originally fitted – the one that was replaced due to the drift problem – there's an internal blocking capacitor in series with the i.f. output pin. In the replacement Elpro tuner however the i.f. output is developed across a small choke which provides continuity to chassis at the tuner's i.f. output. This was shunting away the switching diode's bias, which thus remained off, robbing the i.f. circuits of their input signal.


This is the first and only instance we've had where this new type of tuner has proved to be incompatible: in all other models designed for use with the Mullard type of tuner it's worked well.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R 0NE. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £10, Overseas £11 per annum payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

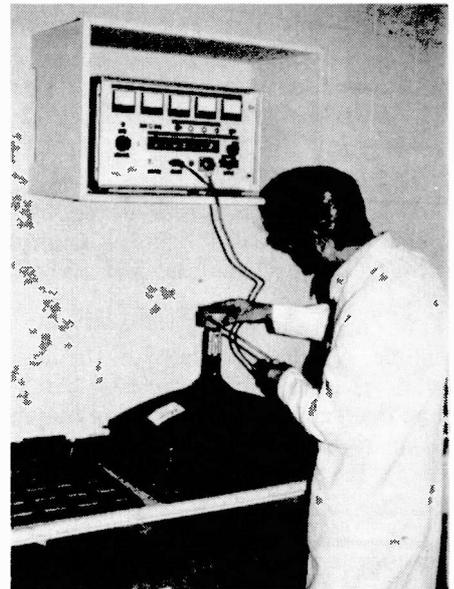
# TOP QUALITY REBUILT TV TUBES

Rebuilt on the most modern equipment to original manufacturers specification

- ★ HIGH FOCUS
- ★ LONG LIFE
- ★ FULLY TESTED
- ★ FULLY GUARANTEED



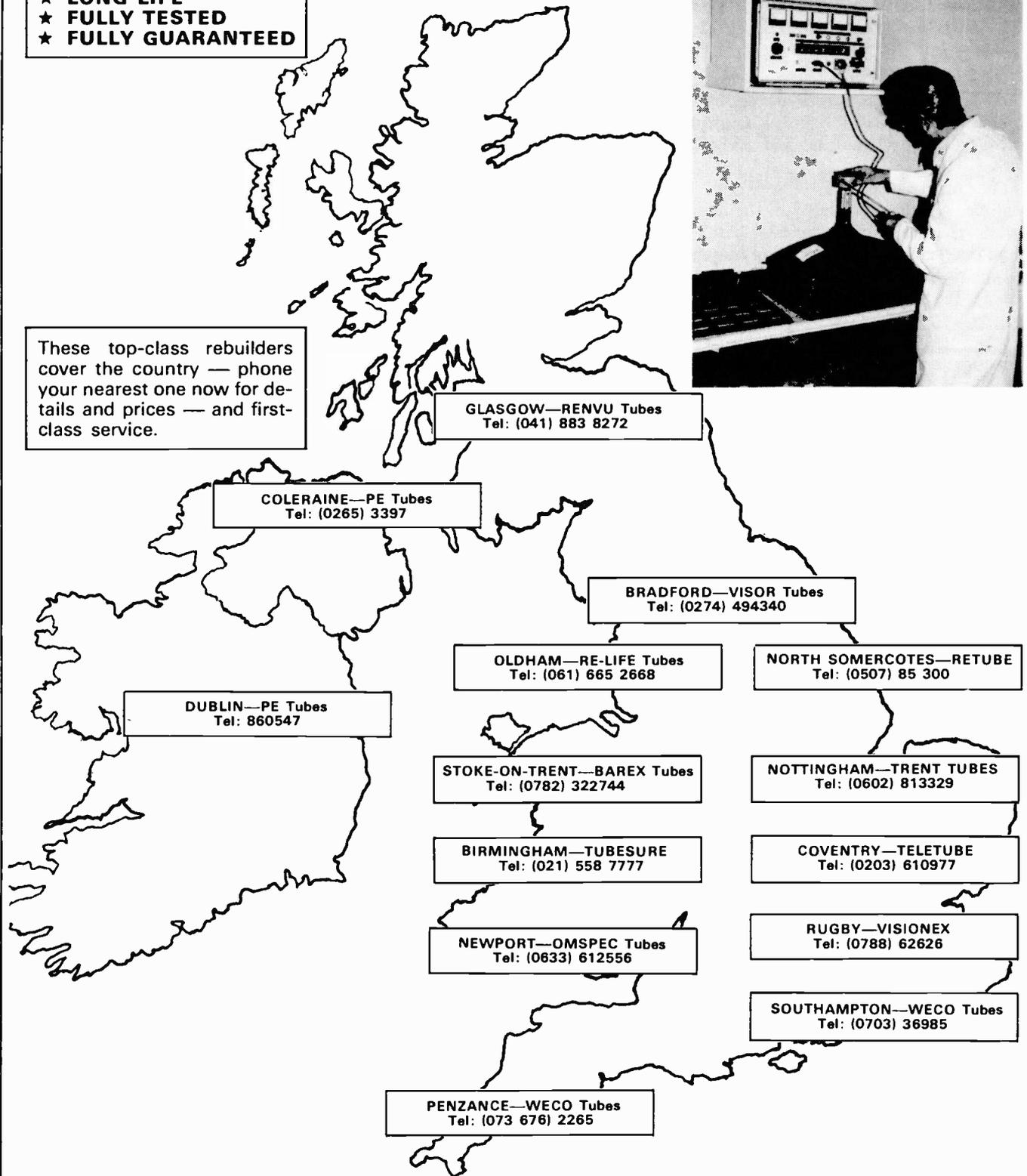These top-class rebuilders cover the country — phone your nearest one now for details and prices — and first-class service.



All these top-class rebuilders use plant and equipment manufactured by Western-Whybrow Engineering — acknowledged as the best available, and the product of more than twenty years' experience of rebuilding colour tubes in U.K. and U.S.A. There is a constant interchange of information to ensure the highest standard of rebuilt tube.

★ NEW ★

# COLOUR BAR GENERATOR

U.H.F. AERIAL INPUT PATTERN GENERATOR CPG6-RF



All Facilities of our PG6RF

## PLUS COLOUR BARS.

Produces 7 invaluable patterns.

**Robust, Battery Powered, Pocket Sized Unit,  
Plugs Straight into Aerial Socket.**

W H I T E	Y E L L O W	C Y A N	G R E E N	M A G E N T A	R E D	B L U E	B L A C K
-----------------------	----------------------------	------------------	-----------------------	---------------------------------	-------------	------------------	-----------------------

## FEATURES:

- ★ CROSSHATCH GRID
- ★ DOT MATRIX
- ★ VERTICALS
- ★ HORIZONTALS
- ★ WHITE RASTER
- ★ GREYSCALE
- ★ PLUS PAL COLOUR BARS;  
ONLY 3 SIMPLE ADJUSTMENTS.
- ★ PG6RF OWNERS; Buy Add-On 'C6' Unit!

## ORDER NOW!

**PG6RF KIT £25.87 BUILT £33.35 – As per TV Review, Jan. 1979**

**C6 KIT £18.98 BUILT £26.45 – Add-on Colour to PG6RF**

**CPG6RF KIT £42.55 BUILT £63.25 – Both above combined.**


These prices INCLUDE P & P and 15% VAT. Export VHF versions available.

In response to demand we have produced an add-on Colour Bar unit C6 to upgrade the PG6RF to PAL COLOUR. A MUST for TV construction or servicing! Available as a KIT or BUILT & TESTED. Kit includes all components and ready built modulator etc. Hundreds sold, reliable design.

**Full 12 month guarantee on built units.**

## MAIL ORDER ONLY

Quantity Discount  
on application

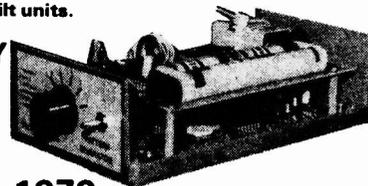

**ACCESS  
ORDERS  
WELCOME**

PLEASE NOTE OUR NEW ADDRESS. ORDER FROM:—  
**TECHNALOGICS LIMITED (DEPT. TV)**  
WINDMILL WORKS, STATION ROAD,  
SWINTON, MANCHESTER M27 2BU.  
TELEPHONE: 061-793 5293

## TV LINE OUTPUT TRANSFORMERS

by FAST RETURN OF POST SERVICE  
PRICES INCLUDE P. & P. & 15% VAT

### COLOUR TRANSFORMERS

DECCA	CS1730, 1733, 1830, 1835
DECCA	30 series Bradford Chassis
DECCA	80, 100 series
ITT	CVC 5 to CVC 9
ITT	CVC 20, CVC 30, CVC 32
PHILIPS	G8, G9 Chassis
PHILIPS	K80 (Rewind only – old unit required – £12)

**£10  
RETAIL**

**£9  
TRADE**

(Trade Orders only)

### WINDINGS

BUSH	Colour Hybrid quadrupler type	£6.00
RANK	T20A chassis	£6.00
PHILIPS	G6 EHT Overwind (exchange basis only)	£7.00
PHILIPS	G6 Primary	£5.00
PYE	691 to 697 EHT Overwind	£3.00
PYE	691 to 697 Primary Winding	£4.00
★ please state which		
EMO	90 degrees	£7.00

### MONO LOPTS

Most British & Foreign  
makes supplied.  
**£9 RETAIL £8 TRADE**  
Separate windings  
also available.

### REWINDS

Rewind Service Available  
Mono or Colour  
SAE all enquiries.

Open Mon. – Fri. 9 to 5.30 pm Callers Welcome.

All lopts and windings are new and guaranteed for 6 months.

**PAPWORTH  
TRANSFORMERS**  
80 Merton High Street  
London SW19 1BE

Barclaycard and  
Access welcome



01-540 3955

# ARE YOU

## USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "How to Deal Successfully in Used Colour Televisions" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail – for both televisions **and** new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular updating service.**

**You can start tomorrow – but you'll need our guide.** The latest big illustrated edition is out now, and costs just **£4.95** – a small price to pay for financial independence!

ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, OARLEY ABBEY MILLS, DERBY.

To: Globus Industries Ltd., Unit 18, Oarley Abbey Mills, Derby.

Please send by return post "How to Deal Successfully in Used Colour Televisions".  
I enclose cheque/p.o. for **£4.95**.

NAME .....

ADDRESS .....

## TV LINE OUTPUT TRANSFORMERS (ALL NEW AND FULLY GUARANTEED)

(Prices include VAT at 15%)

Discount to Trade Post and Packing 85p

### RANK BUSH MURPHY

Z146 A640 dual std mono	9.48
Bush A792, A793 single std mono	9.48
A774 single std mono	9.48
A816 solid state mono	10.43
Z712 T16a T16b mono portable	10.43
A823 A823b A823av colour	11.98
Z179 Z722 series colour	18.06
Z718 18" series	24.57
Z718 20" 22" 26" series	24.57
T20a T22 series colour	16.00

### DECCA

MS2000 MS2400 mono	6.80
MS1700 2001 2020 2401 mono	9.26
MS2404 2420 2424 mono	9.26
1210 1211 1511 portable	11.09
GYPSY portable	10.24
CS1730 1733 colour	10.00
CS1830 1835 colour	10.00
'30' series BRADFORD colour	10.00
80 series colour	10.00
100 series colour	10.00

### G.E.C.

2000 to 2064 dual std mono	9.50
2047 to 2105 3112 to 3135	9.50
"GAIETY" FINELINE	9.50
2114 portable mono	9.50
3133 3135 M1501H portable mono	9.50
DUAL STD hybrid colour	11.59
SINGLE STD hybrid colour	11.59
SINGLE STD solid state 90° or 110°	10.00

### INDESIT

20EGB 24EGB mono	9.90
------------------	------

### PHILIPS

170 series dual std mono	9.20
210 300 series mono	9.20
320 series solid state mono	10.00
G6 single std colour	19.88
G8 series colour	10.35
G9 series colour	10.35
G11 series colour	17.36

### KB-ITT

VC2 to VC10 VC12 to VC100	9.20
VC200 VC205 VC207 mono	9.20
VC300 VC301 VC302 portable	9.20
CVC1 CVC2 colour	10.35
CVC5 CVC7 CVC8 CVC9 colour	10.35
CVC20 series colour	10.74
CVC30 CVC32 series colour	10.00
CVC40 series	15.90

### GRUNDIG

HYBRID 717 1500 3010 colour	12.57
5010 6010 5011 6011 6022	
2222	12.57
1510 2210 2252 5012 colour	12.57

### PYE

169 173 569 573 769 series	9.26
RV293B 368 series	9.20
691 692 693 697 series colour	
Two types see below	
Wired in version	21.41
Printed circuit version	15.26
713 715 570 series colour	12.32
731 735 737 741 colour	10.10
725 colour	9.51

### FERGUSON HMV MARCONI ULTRA THORN

950 mk2 1400 mono	8.50
1500 20" 1500 24" 1580 mono	8.50
1590 1591 1592 1593 mono	8.50
1612 1613 1712 mono	8.50
1600 1690 1691 mono	11.85
1615 series mono	14.64
3000 3500 EHT or SCAN	8.50
8000 8000a series colour	12.14
8500 8800 series colour	12.14
9000 series colour	12.14
9800 series colour	23.85

TELPRO all models	10.00
TANDBURG CTV 2-2 colour	10.00
NORDMENDE solid state	10.00
TELEFUNKEN 637 647	10.00
ZANNUSI	10.71

## WINDINGS

### WIRED TO TAG PANELS

Post & Packing 40p

<b>RANK BUSH MURPHY</b>	
Colour hybrid quadrupler type	5.60
T20a T22 Z719 Z722 Pry & Sec	6.83
Z718 series primary	5.60
Z718 series EHT overwind	7.20

<b>PHILIPS</b>	
G6 eht overwind	7.20
G6 primary	4.60
<b>KORTING hybrid series</b>	7.80
<b>WALTHAM 125 EHT overwind</b>	3.00

<b>PYE</b>	
691 to 697 EHT overwind*	3.07
691 to 697 primary*	4.60
*Please state printed circuit or wired version	

<b>FERGUSON HMV MARCONI ULTRA THORN</b>	
8000 8000a primary	4.50
8500 8800 primary	4.50
8500 8800 EHT overwind	6.00

Contact your nearest depot for service by return.  
Callers welcome. Please phone before calling.  
If the Transformer you require is not listed please phone.

**Tidman Mail Order Ltd.,**  
236 Sandycombe Road,  
Richmond, Surrey.  
Approx 1 mile from Kew Bridge.  
Phone: 01-948 3702


Mon-Fri 9 am to 12.30 pm.  
1.30 to 4.30 pm.  
Sat 10 am to 12 pm.

**Hamond Components  
(Midland) Ltd.,**  
416, Moseley Road,  
Birmingham B12 9AX.  
Phone: 021-440 6144.

Mon-Fri 9 am to 1 pm.  
2 pm to 5.30 pm.
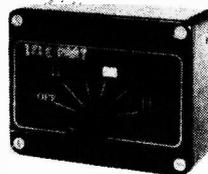
# TELEPART

13 WORCESTER ST.,  
WOLVERHAMPTON,  
WV2 4LJ  
Tel: (0902) 773122  
Telex: 336810



### Telepart Pattern Generator

- Exceptionally light and durable
- Pocket size for outside service
- PP3 battery power source
- Five different test patterns for colour and mono TV
- Cross hatch grid
- Dot matrix
- White raster
- Horizontals
- Vertices

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customer's home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)



### Telepart Colour Bar Generator

- Exceptionally light & durable
- Compact 13x17.5x5.5 cms
- Battery powered for mobility
- Cross hatch grid
- White raster
- Grey scale
- Colour bars
- Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.)

## Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

## AERIAL SPLITTERS

Two way in white box with three black insulated co-ax sockets. Completely made up with two spare co-ax plugs.  
Price only £1.70 EACH.

### CALLERS WELCOME

Large stock of capacitor, resistors, P.C.B. etching compound, TV valves, loft aerial and co-ax cable.  
Open for Callers: Tuesday, Thursday, Friday and Saturday morning.

**SIGNAL INJECTORS** with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts dc. Complete with leads £5.70 each.  
All prices include VAT at 15%. P&P per order 30p. S.A.E. for leaflets. Access cards.

## ELECTRONIC MAILORDER LTD,

62 Bridge Street, Ramsbottom,  
Via Bury, Lancs. BL0 9AGT. Tel. Ramsbottom (070 682) 3036.

## QUALITY TV'S ALWAYS AVAILABLE

GOOD STOCKS OF MODERN COLOUR  
PLENTY OF SINGLE STANDARD MONO  
VERY COMPETITIVE PRICES  
COME TO THE BEST IN THE WEST

## TELETRADERS

ST. LEONARDS WAREHOUSE  
ST. LEONARDS ROAD, NEWTON ABBOT, DEVON  
Telephone: (0626) 60154

# WMTV LTD. – THE TV PROFESSIONALS



## THE BEST DEAL IN TV's

- ★ Britain's most reliable source of Quality T.V.'s.
- ★ Hundreds of working polished T.V.'s.
- ★ Full customer testing facilities.
- ★ Thousands of untested S/S Colour T.V.'s from **£10.**
- ★ Quantity deliveries arranged anywhere in Britain or the World.

### Special Deals

- ★ Mixed 25" 4 for **£30**
  - ★ GEC 19" 10 for **£100**
  - ★ BRC 26" 10 for **£250**
  - ★ Pye 691 22" **£12** each
  - ★ PYE 205 22" 10 for **£199**
  - ★ Personal collection only
- All above prices are plus 15% V.A.T.*

**RING 021-444 6464 FOR DETAILS OF QUANTITY DISCOUNTS**

### MAIL ORDER TV's – Working Colour TVs supplied by Mail Order and fully tested before despatch.

- ★ GEC 2100 22" **£45** ★ PYE 205 22" **£60**
- ★ BRC 22"/26" **£70** ★ BUSH 184 22" **£40**
- ★ BRC 8000 17" **£65** ★ BUSH A823 22"/26" **£60**

*Above MAIL ORDER prices include V.A.T. but please add £12 p & p/T.V. Set.*

- ★ New T.V. Stands.
- ★ Fully adjustable.
- ★ **£6.25** plus £1.75 p & p.
- ★ Quantity discounts.
- ★ Price inc. V.A.T.



## EXPRESS MAIL ORDER SPARES

### ★ Ex-equipment Panels

	Con	Power	Line	Decoder	Video	IF	Frame	Tripler	LOPTX
<b>RBM 823</b>	7.00	6.00	14.00	14.00	—	6.00	9.00	3.00	3.00
<b>BRC 3000</b>	6.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
<b>BRC 3500</b>	9.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
<b>GEC 2100</b>	6.00	—	—	8.00	6.00	6.00	10.00	5.00	5.00
<b>PYE 205</b>	6.00	—	12.00	8.00	7.00	6.00	5.00	5.00	7.00

Postage & packing **£1.25** Panels **50p** Triplers

### Ex-Equipment Valves

	Tested	Untested
ECC82	20	10
PCF80	20	10
PCF802	18	9
PCL82	20	10
PCL84	20	10
PCL85/805	18	9
PCL86	20	10
PFL200	20	10
PL36	23	10
PL504	23	10
PL508	35	18
PL509	90	30
PL519	£1.00	40
PL802	£1.35	—
PY500	45	20
PY800/81	20	10
PY801/88	20	10
30FL1/2	30	20

- ★ p & p paid but minimum order of £3.00 please.
- ★ Deduct 10% discount on orders over £20.00.

### Ex-Equipment Colour Tubes

All fully tested

17" (A44-271X)	<b>£18.00</b>
18" (A47-342X)	<b>£18.00</b>
18" (A47-343X)	<b>£18.00</b>
19" (A49-191X)	<b>£18.00</b>
20" (A51-120X)	<b>£25.00</b>
22" (A56-120X)	<b>£17.00</b>
25" (A63-200X)	<b>£10.00</b>
26" (A66-120X)	<b>£20.00</b>
26" (A67-120X)	<b>£17.00</b>

Please add £5.00 p & p per C.R.T.

### Equipment Spares

\*Always available

- ★ Colour and Mono Scan Coils **£1.50** + £1.00 p & p.
- ★ Tuners for all makes of Colour and Mono **£4.00** + £1.00 p & p.
- ★ Mono tubes fully tested. All Sizes – please state size on order **£3.00** - £4.00 p & p.
- ★ Reconditioned 50p meters **£92.00/Box of 10** incl. p & p.
- ★ PLESSEY SL918 colour ICs with ● circuit for substitution of SL917 **£2.00** + 25p p & p.
- ★ NEW VHF/UHF Varicap Tuners with circuit and full data **£1.25** + 75p p & p.

**WE ARE OPEN MON-SAT 9.30-5.45**

**PLEASE NOTE – ALL THE ABOVE MAIL ORDER PRICES INCLUDE 15% V.A.T.**

**WMTV LTD. 92 HIGH ST (A435) KINGS HEATH B'HAM B14 7JZ TEL. 021-444 6464  
021-444 2575**

THE FAMOUS BI-PRE-PAK

# CROSS HATCH GENERATOR

THOUSANDS SOLD!



**DESIGNED SPECIALLY FOR  
COLOUR T.V. CONVERGANCE**

- **EASY BUILD KIT** with instructions **£14.50**
- **READY BUILT AND TESTED** (Less Batteries) **£16.75**

Prices include V.A.T. and postage in U.K.

- **LIMITED STOCKS SO PLEASE ORDER PROMPTLY.**

More than ever these days, a cross hatch generator is absolutely essential to TV engineers, etc. It is the only accurate way to align all three guns in colour TV. The proven reliability, small size, easy operation and stability of this truly famed instrument is such that we are offering it once again, but this time, when stocks have been sold, it is not likely that supplies will be available again at anywhere near present prices. With improvements incorporated – plug-in I.C.s for example – it is going to be wanted more than ever. Many thousands are in regular use by TV renters and suppliers, etc. As this Generator is a VIDEO FEED UNIT and NOT R.F., it can be used anywhere overseas without having to worry about frequency matching. Operates from its own self-contained standard batteries.

- ★ VERTICAL/HORIZONTAL/DOT/CROSS HATCH PATTERNS
- ★ FOUR POSITION PATTERN SELECTOR SWITCH
- ★ TOUGH FIBRE GLASS CASE 5¼" x 3" x 3"
- ★ OPERATES FROM SELF-CONTAINED BATTERIES
- ★ VERY EASY TO CARRY AROUND – REQUIRES NO EXTERNAL POWER SOURCE
- ★ PLUG-IN I.C.s AND SENSITIVE SYNC PICK-UP CIRCUIT
- ★ FUNCTIONS TO FULL PROFESSIONAL AND COMMERCIAL REQUIREMENTS
- ★ FOR PROMPT, NO DELAY DELIVERY
- ★ IN KIT FORM OR READY-BUILT, TESTED AND GUARANTEED

ORDER DIRECT FROM  
**BI-PRE-PAK LTD.** 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS0 9DF  
Telephone (0702) 351048 – Shop Hours 9.30 am–6.00 pm.

## TENREC

Tenrec Electronic Engineers Ltd  
502 Bearwood Road  
Warley, West Midlands  
021 429 8150

### Thorn 8000/8500 CTV's

Full working order from £65 + p.&p.

### LCD Watches

from £5.85 + £1 p.&p.

SAE for Complete List.

\*A31-410, 12" Mono Tube New. Special Price for Current  
A38-160W, 15" "Television" Feature; £19. P&P-£2.

**Plenty of used colour panels working. S.A.E. for  
list. 50p p. & p.**

Trade enquiries welcome

(All prices include VAT)

(T.I.)

## APOLLO

### HIGH TEMPERATURE PUMPED COLOUR TUBES

Orders accepted by phone, same day delivery. Manchester area £3.50. Mail Order anywhere by request, fitting while you wait £15 extra.

18"	A47 – 342 x 343 x	£33.00
19"	A49 – 120 x /192 x	£33.00
20"	A51 – 220 x /110 x	£33.00
22"	A56 – 120 x /123 x	£36.00
25"	A63 – 120 x	£39.00
26"	A66 – 120 x A67 – 120 x	£39.00

These tubes replace many Toshiba types.

Callers welcome, please phone first.

**061 799 0854**

Reg Office:

**43 Clarke Cres, Little Hulton,**

**Nr. Manchester M28 6XM.**

While stocks last – 3 hour conversion kits for Philips 1500  
Video's £99 inc. P. & P.

# CELTEL

WARNERS MILL  
SOUTH STREET  
BRAINTREE  
ESSEX  
(0376) 26384

UNIT 5A,  
KEMPS SHIPYARD,  
QUAYSIDE ROAD,  
BITTERNE,  
SOUTHAMPTON  
0703 331899

COLOUR & MONO TV's  
WORKERS & NON-WORKERS,  
EX EQUIPMENT TUBES & PANELS  
**RE-BUILT COLOUR TUBES**

REBUILT CATHODE RAY TUBES IN

## SOUTH WALES

NEWPORT

CARDIFF

NEATH

### C.R.T. SERVICES

274 Chepstow Road, Newport, Gwent.

Tel Newport 272005.

TUBES ALSO AVAILABLE FROM OUR STOCKISTS IN

CARDIFF

NEATH

Dependable TV, 9 Crwys Rd.  
Tel. Cardiff 44006

Sureview, 89 Windsor Rd.  
Tel. Neath 57676

#### CURRENT PRICE LIST

A44-271X, A47-342X/343X	£30	470ERB22, 470FTB22	£40
A49-120X, A51-110X	£30	A51-161	£40
A56-120X, A56-140X	£33	A56-500X, 560HB22	£43
A63-120X, A66-120X	£36	A66-500X	£46
A66-140X, A67-120X/150X	£36	Add 15% VAT to all prices.	

Prices are based on a type for type exchange tube  
suitable for reprocessing.

**TWO YEAR GUARANTEE ON ALL TUBES**

**LOOK!** Phone: LUTON  
BEDS. 38716

**OPPORTUNITIES  
TRADE SALES**

**ALL SETS GUARANTEED  
COMPLETE**

**OVER SIX HUNDRED SETS**

**ALWAYS IN STOCK**

Pye 20T, Philips G8;

Ferguson 3-3k5

Murphy, Bush, Decca, GEC

All from

**£35.00 £50.00**

Square Screen, Mono's from

**£5.00 ALL MODELS**

Sets for spares from

**£2.00**

All include VAT

**OPPORTUNITIES**

**9A, Chapel Street, Luton, Beds.**

**LUTON 38716**

9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.

**N.G.T. COLOUR TUBES**

*First Independent Rebuilder with*

**B.S.I. CERTIFICATION**

*(Certificate No. 004)*

**2 year guarantee: 4 year option**

All Colour Tubes are debanded, high temperature pumped and rebanded using new adhesives and new tension band.

19" £30, 20" £32, 22" £33, and 26" £38.

*Exchange prices: add VAT at 15%*

**N.G.T. ELECTRONICS LTD.,**

120, SELHURST ROAD., LONDON S.E.25

**Phone: 01-771 3535.**

*20 years experience in television tube rebuilding.*

**EMO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES  
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●**

**CREDIT AVAILABLE — TRADE ONLY**

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX -  
EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY  
TV COMPONENT BY RETURN**

**IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

S.A.E. FOR FREE WALL CHART

**TELEPART (WTON) THE TELECENTRE, WORCESTER ST.,  
WOLVERHAMPTON (0902) 773122**

**TELEVISION TUBE  
SHOP**

*NEW TUBES AT CUT PRICES*

**EUROPEAN TYPE Nos.**

	Price £	VAT £	15%
A28-14W.....	21.95	3.29	
A31-19W/20W.....	19.95	2.99	
A31-120W/300W.....	17.95	2.69	
A31-410W/510W.....	17.95	2.69	
A34-100W.....	18.50	2.77	
A38-160W.....	17.50	2.63	
A44-120W.....	27.00	4.05	
A50-120W.....	17.95	2.69	
A59-23W.....	21.50	3.22	
A61-120W.....	19.95	2.99	

**U.S.A./JAP. TYPE Nos.**

9AGP4.....	21.82	3.27
190AB4/C4.....	23.00	3.45
230ADB4.....	28.50	4.28
230DB4/CT468.....	26.60	3.99
240AB4A.....	17.95	2.69
CT507 equiv.....	21.95	3.29
CT512.....	27.50	4.12
310DGB4/DMB4.....	23.00	3.45
310EUB4.....	19.95	2.99
310EYB4.....	18.75	2.81
310FDB4.....	23.50	3.52
310FXB4.....	17.50	2.62
310GNB4A.....	23.50	3.52
310HCB4.....	23.50	3.52
340AB4.....	22.50	3.38
340AYB4.....	30.00	4.50
340RB4/CB4.....	26.00	3.90
340AHB4.....	26.00	3.90

**Some Rebuilt Japanese  
& European Types  
Available from  
£14.00 + VAT £2.10**

**COLOUR TUBES**

**New and Mullard Colourex\***

12VARP22.....	62.50	9.37
330AB22.....	73.50	11.03
470FUB22B.....	97.50	14.63
A44-271X.....	65.00	9.75
A47-342X.....	69.50	10.42
A47-343X.....	69.50	10.42
A49-191X.....	59.50	8.92
A51-161X.....	67.00	10.05
A51-220X.....	64.00	9.60
A56-120X.....	58.50	8.77
A63-120X.....	69.50	10.42
A66-120X.....	65.00	9.75
A66-140X/410X.....	70.50	10.57
A67-120X.....	65.00	9.75
A67-140X/200X.....	69.50	10.42
A67-150X.....	75.00	11.25

**\*Old Bulb Required for Colourex\***

**ALL TUBES TESTED BEFORE  
DESPATCH & GUARANTEED  
FOR 12 MONTHS. 4 YEAR  
GUARANTEES AVAILABLE ON  
MOST TYPES**

**CARRIAGE**


Mono £3.00 Colour £5.00

**Mainland only. Overseas Rates on  
Application.**

**TELEVISION TUBE SHOP LTD.**

**52 BATTERSEA BRIDGE RD.,  
LONDON, SW11.**

**Tel. 228 6859/223 5088**

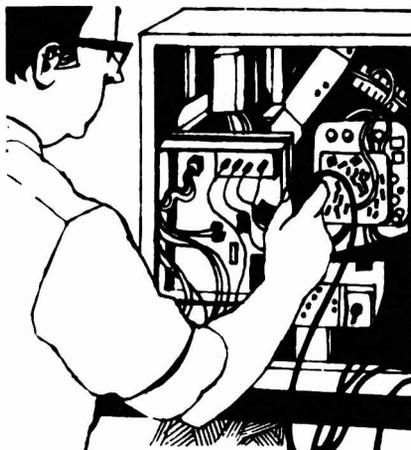

## SETS & COMPONENTS

### TV DX.

High Quality, proven equipment supplied by an expert in the TV DX field.

**Wideband Band I preamplifier module.** Gives approx 20dB gain, low noise-IC used. 12V supply required. **£6.00.**

**Upconverter.** This is an ideal way to start TV DXing. The unit converts band I/III to UHF-A tuned RF stage ensures low noise and cross modulation, a feature which many models lack, 12V supply required. **£10.00.**

**Band I notch filter.** This attenuates the sound and vision frequencies of your local band I channel (please state which) whilst passing with low insertion loss the rest of the band. **£17.95.**

**Philips G8 selectivity modules.** One or two of these placed between the tuner and IF strip of your TV gives reduced bandwidth essential for serious DX work. **£1.10.**

**FM DX!** 88-108MHz tunable Mosfet pre-amplifier. Reduces local signal overload. **£25.95.**

**TV DX receivers** available. Please send sae for my product list to:

**H. COCKS,**

**Cripps Corner,  
Robertsbridge, Sussex TN32 5RY.**

**Phone 0580 83317.**

*The above prices include post/packing. Overseas enquiries welcome. Callers welcome. Please telephone first.*

### Southern Valve Co.,

2nd Floor, 8 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability, all popular valves stocked. **NO CALLERS, SAE Lists.** Cash with order. Same Day Postal Despatch. (Lunch 12.30-2p.m.)

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter or MAIL ORDER. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 6 Potters Road, New Barnet, Herts.

Tel: 01-449 1934/5 (1934 Recording Machine).

Please phone for opening hours.

### TV PATTERN GENERATOR

UHF output, plugs straight into aerial socket, provides cross-hatch and peak white and 8 bar grey scale. Size 100 x 75 x 40mm.

**£17.75**

price includes battery, P&P, and VAT.

Further details of this and our other products on request.

**C. L. JERVIS,**

15 Mercer Grove,  
Wolverhampton, WV11 3AN.  
TEL (0902) 736606.

### LOOK!

**THORN 3000/3500 & 9000 TRIPLERS**

High Quality Silicon Replacement Units

T3500 only **£4.95** inc. P.P. Add 74p V.A.T.

T9000 only **£5.45** inc. P.P. Add 82p V.A.T.

Quotes for 50+.

1 Year Guarantee

**WING ELECTRONICS**


15, Waylands, off Tudor Road, Hayes End,  
Middlesex.

## SMALL ADS

The prepaid rate for classified advertisements is 25p per word (minimum 12 words), box number 60p extra. Semi-display setting £4.80 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).
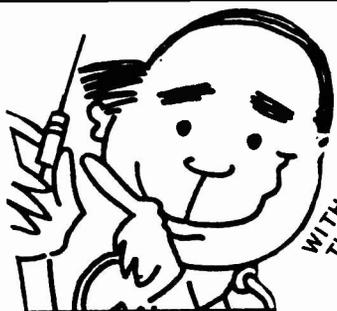
### NOTICE TO READERS

*Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.*



## WERNETH

**ELECTRONICS LIMITED**  
**FREEPOST.**

**P.O. BOX 9, MARPLE, STOCKPORT, CHESHIRE. SK6 6YE.**

WERNETH ELECTRONIC PRODUCTS · WINNINGTON RD · MARPLE · STOCKPORT · CHESHIRE

### "Just what the doctor ordered!"

**TUBE TEST INSTRUMENTS**

TX 80 PROFESSIONAL £48.85

TX50 LOW COST SERVICE TESTER £29.50

TX50 COMPLETE KIT OF PARTS £21.00

### Get to the point: fast! IN-CIRCUIT TRANSISTOR TESTER

Designed for fault finding in Solid State circuits, this tester uses C-MOS technology to detect faulty transistors and diodes in or out of circuit.

Also identifies PNP & NPN base-emitter-collector leads.

Supplied complete with full instructions (less PP3 battery) **£15.60** inc.

*C.W.O./S.A.E. for product details.*

### TELETRONIC (NORTH EAST) LIMITED.

"SEE-VU" Works,  
Strangford Road,  
Seaham, Co. Durham.  
Tel. (0783) 812142

Competitive - Reliable  
**REBUILT COLOUR TUBES**  
Hot pumped and Rebanded  
Two year guarantee - Four Year Available  
ENQUIRIES WELCOME

Ask for our list of sixty types JAPANESE 'IN LINES' and 20AX.

The North-East's largest rebuilder.  
Established 1957

Mono tubes also available.

**TURN YOUR SURPLUS** capacitors, transistors, etc. into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

### COLOUR TUBES

Rebuilt with new electron gun, to British Standard. High temperature pumping.

	Here is what you pay.	VAT
17-18-19 inch.....	£29	4.35
20 inch.....	£30	4.50
22 inch.....	£31	4.65
25 inch.....	£34	5.10
26 inch.....	£35	5.25

Guarantee 2 years.  
Exchange basis.

**CALLERS ONLY**

### TELESTAR TUBES

575c Moseley Road, Birmingham B12 9BS.  
Tel: 021-440 5712.

## TV WHOLESALE SUPPLIES LTD THE SPECIALISTS FOR

Good quality colour and Mono TVs. Fresh stocks in every week. Why not call and see our selection of PX, re-possession and ex rental TVs.

- ★ **COMPETITIVE PRICES**
- ★ **FULL TEST FACILITIES.**
- ★ **DELIVERY ARRANGED IF NECESSARY.**
- ★ **SPARES FOR MOST MAKES OF MODERN RECEIVERS.**
- ★ **PLUS REGUNN TUBES AT COMPETITIVE PRICES.**
- ★ **ALSO EXPORT OUR SPECIALITY.**

### TV WHOLESALE SUPPLIES LTD.

**35 SHIPSTON ROAD, STRATFORD-UPON-AVON, WARWICKS.**

**TELEPHONE (0789) 4424.**

**Open 9.30 till 6.30 6 days a week.**

**On the main A34 Oxford road.**

# SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.  
Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBANDED TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAINS LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

## COLOUR PANEL EXCHANGE SERVICE

BRC 3000/3500, 8000/8500  
GEC 2110 series  
Philips G8, G9 and G11

Three months guarantee on all Exchange Panels.  
Free delivery in London area.

Also Ex-Equipment Panels Thorn 3500 for sale.

All guaranteed Perfect Working Order.  
Phone or send SAE for Catalogue.

### KAY JAY TV SERVICE,

34, Clouston Avenue,  
Northolt, Middlesex.  
Phone 864-0350.

EXCELLENT QUALITY  
USED COLOUR TV's  
CHOOSE UNTESTED  
OR FIRST CLASS  
WORKERS ENGINEERED  
IN OUR WORKSHOP.

**TELFURB T.V. LTD.**  
WHEATLEY  
08677 3849

# STS

FOR  
QUALITY  
USED T.V.s

200 EX RENTAL  
COLOUR AND MONO TVs  
ARRIVING WEEKLY  
GOOD CLEAN CABINETS

**Bush ★ Decca ★ GEC**  
**Pye ★ Philips ★ Thorn**  
**Grundig ★ Sanyo ★ ITT Etc**

TROLLEY STANDS AND  
ALL SIZE REGUN TUBES.

DELIVERY IF REQUIRED

Call or phone now to:

**SOUTHERN TRADE SERVICES**  
21 COLINDALE AVE.,  
LONDON NW9  
TEL 01-200-7337.

## QUALITY REBUILT TUBES

HIGH TEMPERATURE PUMPING

COLOUR (2 year Guarantee)

90° up to 19"	£32
90° 20" - 22"	£34
90° 25" - 26"	£36
110° and PIL	£38

MONO (including thin necks) from  
£12.

All prices + VAT

Delivery UK Mainland £6.

4 year Optional Guarantee

Send or phone for full list and terms.

**WELTECH PICTURE TUBES**  
Unit 3-10 Wembley Commercial Centre,  
East Lane, Wembley, Middx.  
01-908-1816

# TELEVISION

# R A D E

## FREE WINE AND LOW LOW PRICES

**YES** we are giving away free bottles of wine with every £100 spent, **PLUS** our special **LOW LOW** price spring offers. You'll need the wine to celebrate your good fortune. Don't delay, call and see us, we will do you a **SUPER DEAL**, on the spot.

*(PS. Don't forget your cash)*

Most makes colour or mono with good cabinets

## GENERAL FACTORS

GOOD MOTORWAY ACCESS  
EXPORT ENQUIRIES

UNION ST, DONCASTER DN1 3AE  
TELEPHONE (0302) 49583-68416

WINE OFFER ENDS 30TH APRIL 1981

## IRISH TV DEALERS

Call now for a full range of colour and mono TVs. All sets sold working. Delivery can be arranged to any part of Ireland. Call write or phone:

### TELESCREEN

Bellanaleck Quay, Near Enniskillen,  
Co Fermanagh, N. Ireland  
Tel: Florencecourt 388.

When replying to Television Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

G6 SPARES. ELECTRONICS. SAE. Early radios.  
Sole. 37, Stanley Street, Ormskirk, Lanes.

EXPORT MONO TELEVISIONS used 24" for  
CCIR-B system suitable for most African countries.  
Also colour available Parako T.V. 6, Greenfell Road,  
Maidenhead, Berks. 0628 34717.

# IRELANDS LARGEST DISTRIBUTORS OF COLOUR AND MONO TELEVISIONS

Mono from £5, Colour from £20,

*Delivery can be arranged. Working sets to order.*

ALSO DISTRIBUTORS OF SERVICE EQUIPMENT, COMPONENTS AND TOOLS, AERIALS, VIDEO RECORDERS, RADIOS AND CASSETTES ETC.

**TELETRONICS, SESKINORE, OMAGH, CO. TYRONE. TEL: FINTONA 389 (STD 066 284)**

## WANTED

NEW VALVES and CRT's required, PCL805, PL504, PL509, PY500A etc. Cash waiting, Bearman, 6/8 Potters Road, New Barnet, Herts. Tel: 01-449 1934/5.

WANTED C.R.T. 5642/200P31 for telequipment storage scope DM 64. Phone Flintwick 5897.

WANTED. Transistor oscilloscopes dual trace 10mV, 10MHz. 7 Firtree Road, Hastings. (Tel. 0424 427374).

## EDUCATIONAL

### BETTER JOB! BETTER PAY!

GET QUALIFIED WITH ICS IN:  
COLOUR & MONO TV SERVICING  
COLOUR & MONO TV ENGINEERING  
COLOUR & MONO TV MAINTENANCE  
PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,

**NEW: Self-build radio courses with free kits**

Train in your own home, in your own time with ICS, the world's most experienced home study college.

**RETURN THIS COUPON TODAY FOR FREE BROCHURE!**

**ICS** Int. Correspondence Schools  
284D Intertext House, Stewarts Rd.  
London SW8 4JJ. Tel: 01-622 9911

Name .....

Address .....

## TELEVISION COMPUTER & RADAR SYSTEMS SERVICING

**TWO YEAR full-time Modular Diploma course to include a high percentage of practical work.**

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS
- RADAR

Each of the above Modules are 12 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £430 per Module. - Computer Module £500.

Next session starts April 21st.

(Also available 2½ year course in Marine Electronics & Radar.)

Prospectus from:

### LONDON ELECTRONICS COLLEGE

Dept: TT, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721.

## FOR SALE

EARLY R + T.V. Servicing Books. 12 books from Vol. 1 to 1961. Offers. 03272 77436.

NEW BACK ISSUES of 'Television' available 90p each post free. Cheque or uncrossed P.O. returned if not in stock. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

COLOUR TV PORTABLE PANELS. UHF Varicap Tuner & Touchtone panel, Vis. & Sound IF, Spund output. Chroma Decoder on panel 250x200mm. Send Cheque/P.O. £17.50 to 'Vision On', 171 South Ealing Road, London W.5.

TUBE REGUNNING PLANT complete system. Loads of extras. Full training given. Bargain! Box No. 158.

## MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest Discount catalogue out now. Phone C.W.A.S. Alarm. 0274 682674.

RIGONDA AGENTS. For all spares and repairs fast dispatch trade service available. 01-476 1928. Star Radio, 272 Barking Road, London E.13.

## VETERAN & VINTAGE

### "SOUNDS VINTAGE"

The only magazine for all vintage sound enthusiasts, packed with articles by top writers covering gramophones, phono graphs, 78s wireless, news, history, reviews, etc.

B. monthly. Annual subscription £6.00 (airmail extra). Send 75p for sample copy.

28 Chestwood Close, Billericay, Essex

## BOOKS & PUBLICATIONS

ANY SINGLE SERVICES SHEET £1. L.S.A.E. Thousands different repair/service manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E. Newsletter, price lists, quotations. AUS (T). 76 Church Street, Larkhall, Lanarkshire. (0698 883334).

**PLEASE MENTION TELEVISION WHEN REPLYING TO ADVERTISEMENTS.**

## SERVICE SHEETS

### 30,000 SERVICE SHEETS IN STOCK COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios £1.25. Tuners £1. Tape Recorders, Record Players, Transistors and Stereograms + S.A.E. from £1.25 each except Colour TV Circuits £2. Car Radios from £1.25. All Radiograms from £1.25.

State if Circuit will do, if sheets are not in stock. All TV Sheets are full length 24 x 12, not in Bits & Pieces. All other Data full lengths. Free Fault Finding Chart or TV Catalogue with order. Crossed PO's Returned if Sheets Not in Stock.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882.

MAIL ORDER SAE.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

JAPANESE TV service sheet specialists catalogue 25p plus S.A.E. Sandhurst Publications, 49c, Yorktown Road, Sandhurst, Camberley, Surrey.

SERVICE SHEETS, Radio, TV, etc., 10,000 models. Catalogue 24p plus SAE with orders-enquiries. Telray, 154 Brook Street, Preston, PR1 7HP.

Thousands of different full size service sheets Thousands of different manuals of all kinds in stock. (Many of above are unique to us and obtainable nowhere else.)

Updated collection of British colour TV circuits/layouts etc. Contained in 3 huge binders - special price £39.50.

Updated foreign colour TV repair system for £22.50. (2 manuals, 1 binder) chassis from Grundig, Hitachi, Skantic, Luxor, Mitsubishi, Kuba, Zanussi.

Complete set of 10 unique TV repair manuals - only £49.50. Mono + colour from dual standards to latest models, McCourt & Tunbridge.

S.A.E. any quotation, also price lists, newsletter, bargain offers, details of our unique TV repair systems.

£1 + large S.A.E. any single service sheet.

Phone: 0698 883334, anytime. Callers 4-6 pm. weekdays, Saturday from 10 am.

# G.T.

**TECHNICAL INFORMATION SERVICE  
76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.**

# SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS,  
RECORD PLAYERS, TAPE RECORDERS, ETC.

**SERVICE SHEETS £1.00 PLUS S.A.E. SERVICE MANUALS ON REQUEST.**

## BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

TVT '79 TRANSISTOR EQUIVALENT & DATA BOOK. (A TO Z). 272 Pages .....	£3.50
TVT '79 TRANSISTOR EQUIVALENT & DATA BOOK. (2N, 2S, ETC.). 392 Pages.....	£4.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 1 .....	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 2 .....	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 3 .....	£9.75
COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition.....	£9.80
COLOUR TELEVISION THEORY by G. H. Hutson.....	£7.95
LONG DISTANCE TV RECEPTION FOR THE ENTHUSIAST by R. Bunney.....	£1.70
AUDIO EQUIPMENT TESTS by G. J. King.....	£7.50
RADIO CIRCUITS EXPLAINED by G. J. King .....	£6.50
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition.....	£7.20
TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition.....	£7.95
BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition.....	£3.75
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition .....	£3.75
C.C.T. RHOE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett.....	£4.40
TELETEXT AND VIEWDATA by S.A. Money .....	£6.00
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. 2nd Update.....	£10.35

## COLOUR TV MANUALS

COVERING FOLLOWING MAKES  
PLEASE SEND S.A.E. FOR QUOTATION

ALBA, BRC, BUSH, DECCA, GEC,  
DEFIANT, MARCONI, EKCO, PYE,  
FERGUSON, DYNATRON,  
NATIONAL, HITACHI, INVICTA,  
ITT/KB, RGD, GRUNDIG, SOBELL,  
STELLA, SONY, MURPHY,  
PHILIPS, HMV, ULTRA & OTHERS.

## CIRCUIT DIAGRAM MANUALS

We supply circuit diagrams for televisions in Giant Binders,  
covering most British 'Single' and 'Dual Standard' models,  
consisting of 2 volumes on colour and 1 on black & white. Price  
£14.50 each post free or all 3 for £40.50 post free.

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.  
FROM 1971-72 EDITION UP TO DATE. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 25p POSTAGE PER COPY.  
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, ELECTRONICS TODAY, ELEKTOR

## BELL'S TELEVISION SERVICES

**190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885**

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. (HALF DAY WEDNESDAY) PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for .....

insertions. I enclose Cheque/P.O. for £ .....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)


NAME.....

ADDRESS .....

.....

Send to: Classified Advertisement Manager,  
**TELEVISION**  
G.M.G., Classified Advertisement Dept., Rm. 2337,  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Telephone 01-261 5846.  
Rate  
25p per word, minimum 12 words. Box No 60p extra.

Company registered in England. Registered No. 53626 Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS

# DISPLAY ELECTRONICS

**LEADERS  
IN TUBE  
TECHNOLOGY  
SINCE THE 60's.**

## REGUNNED COLOUR TUBES 2 YEAR GUARANTEE

Up to 19".....	<b>£29.50</b>
20".....	<b>£31.50</b>
22".....	<b>£33.50</b>
25".....	<b>£35.50</b>
26".....	<b>£37.50</b>

The above prices are for standard 38mm Delta Gun Types. Prices on application for P.I.L. Tubes etc. Some types available without pre-supply of glass at extra cost.

Carriage/Packing £5 up to 75 miles from works. £6.50 over. Please add 15% VAT

## REGUNNED MONO TUBES 2 YEAR GUARANTEE

20".....	<b>£11.00</b>
24".....	<b>£13.00</b>

Carriage/Packing £4.00 up to 75 miles from works. £5.00 over. Please add 15% VAT.

## BUDGET CORNER

Buy any 5 mixed types Cash 'n Collect - Take 20% discount.

**OR**

Buy any 5 Mono mixed sizes Cash 'n Collect at **£8.50** (20") and **£10** (24").

PLEASE ADD 15% VAT.

## CALLERS WELCOME

Late night Thursdays until 8pm Saturdays until midday.

N.B. Customers intending to collect orders are requested to telephone in advance:— even popular types may be out of stock for short periods.

## V.D.U./RADAR TUBES

Home and export enquiries for Radar Display Tubes manufactured from new (with phosphors to specification) are invited.

**WATERLOO ROAD,  
UXBRIDGE,  
MIDDLESEX**

Telephone: Uxbridge 55800

**BIRMINGHAM AND DISTRICT  
DEALERS/ENGINEERS**

# NEWS FLASH

**HIGH VACUUM  
QUALITY  
REBUILT TELEVISION  
PICTURE TUBES**

**COMPETITIVE PRICES**

**CONTRACT TERMS  
AVAILABLE**

**2 YEAR GUARANTEE**

17" 18" 19"	<b>£31.00 + VAT £4.65</b>
20"	<b>£34.00 + VAT £5.10</b>
22"	<b>£36.00 + VAT £5.40</b>
25"	<b>£40.00 + VAT £6.00</b>
26"	<b>£43.00 + VAT £6.45</b>

**PIL Tubes our speciality.**  
All Prices For Tubes available on a Sound "Glass for Glass" basis otherwise **£20** surcharge

**Built up to a standard  
not down to a price.**

## TUBESURE LTD.

Unit 111, Middlemore Industrial Estate,  
Middlemore Road, Smethwick,  
West Midlands. Telephone: 021-558 7777.

# STANDARD T.V. TUBE

**HIGH QUALITY COLOUR AND  
MONO-CHROME REPLACEMENT  
TUBES AT COMPETITIVE PRICES.**

- ★ Complete New Gun fitted to every Tube.
- ★ Two year Guarantee
- ★ Every Tube Electrically Tested.
- ★ Every Tube Picture Tested.
- ★ Supplier to Major Rental Companies.

18", 19"	<b>£25</b>
20", 22"	<b>£27</b>
25", 26"	<b>£29</b>

All prices quoted assume the return of your old glass rebuildable condition. Old CRT cash/cheque with order. Please add VAT at 15%.

**S.STANDARD TV TUBE CO.**

**11-29, Fashion Street,  
London E1**

Tel. 01-247 3097

**Now at Bridgwater!**

# WELLVIEW

**SERVES THE WEST**

## Exchange Colour

	our price	+ VAT 15%	total price
A44/270X-271X	£27-00	£4-05	£31-05
A47/342X-343X	£27-00	£4-05	£31-05
A49/120X	£27-00	£4-05	£31-05
A51/110X	£27-00	£4-05	£31-05
A55/14X	£32-00	£4-80	£36-80
A56/120X	£32-00	£4-80	£36-80
A63/120X	£36-00	£5-40	£41-40
A66/120X	£36-00	£5-40	£41-40
A67/120X	£36-00	£5-40	£41-40
A67/200X	£36-00	£5-40	£41-40

## New Mono

	our price	+ VAT 15%	total price
A31-120-300	£15-00	£2-25	£17-25
A50-120	£14-74	£2-21	£16-95
A61-120	£15-96	£2-39	£18-35

18 month full guarantee (Established ten years).

*Send cash or cheque together with old tube with your order.*

*Carriage=£4.50 including VAT*

**ALSO YOUR VALVE SUPPLIER  
NEW AND BOXED  
(inclusive of VAT)**

DY802=74p	ECC82=64p	EF183=78p
EF184=64p	PCC89=72p	PCF802=98p
PCL82=78p	PCL84=92p	PCL805=97p
PFL200=£1.15	PCL86=97p	PL504=£1.38
PL509=£2.82	PL519=£2.92	PY88=70p
PY800=70p		PY500A=£1.52

Postage and Packing 10p per valve. All orders over £10 Free of charge.

## Special News Flash

# "TUBE REPLACEMENTS"

53A Exeter Road,

Exmouth. Tel: 6210

ARE OUR AGENTS FOR  
AVON - DEVON - SOMERSET  
THEY OFFER FREE DELIVERY PLUS  
MOST OTHER TV SPARES  
*FREE CATALOGUE ON REQUEST*

## Colour Sets.

600 ex-rental TVs

Good sets good prices

Call and see

*All mail order and  
enquiries to  
Head Office and  
Factory*

**WELLVIEW TUBES  
LTD**

**Unit No1, Monmouth St,  
Bridgwater, Somerset.**

**Tel. 0278 425690-722816**

CVC 9 ITT Control panel. **£4.00**  
 CVC 20 ITT 6 push button unit & Input panel. **£5.00**  
 Philips TV IF Modules 38 Mc/s 1st and 2nd IF. **£1.50**  
 3500 6 push button unit for Thorn 3500. Varicap Tuning. **£1.00**

**VARICAP F.M. TUNER**  
 Range 87.5 to 108MHz. **£2.00** (IF panel with circuit). **£2.00**  
 6 position 12.5KV Resistor Unit for varicap. **50p**  
 GEC IF panel (204C). **£7.50**  
 I.T.T. (CVC 5) 7 push button unit for V/cap tuning **£7.00**  
 New portable T/V chassis. Mono **£16.00**  
 New I.F. panel T/V. 3 I.C. 11 coils etc. **£3.00**  
 ELC 2000M New. **£7.00**  
 GEC VHF/UHF 8CH touch tune units 41C 1xSN 29862N+1xSN 16861NG+2xCBF 16848N. **£5.00**  
 New circuit supplied. CVC panel with pots and main switches 250K, 100K, 423 500K. **£1.00**  
 New (NSF/AEG) UHF/VHF Varicap tuner units. Cost £10. only **£4.00**  
 Convergence panel for GEC 2040, 11 pots, 5 coils, 2 resistors etc. New. **£1.50**  
 PYE 731 6 push button unit and 100KA pots. **£3.00**  
 New circuit supplied with UHF 8ch Light action unit 4 i/c for Varicap tuning GEC C2001/C2201. **£5.00**  
 UHF Mullard 4 push button tuner unit. **£2.00**  
 ITT Control Panel with Mains lead, 4 slider pots, Mains filter. **£2.50**  
 Bush Rank 6 push button Unit for varicap. **£2.50**  
 4 push button unit (for Varicap Tuning) 20K. **50p**  
 4 pots and 6 push button unit for Varicap. Mains on/off switch + Mains filter. I.T.T. **£3.50**  
 Philips T/unit UHF. **£2.00**  
 Transistor UHF units with Ae socket and leads. GEC 2000 rotary type. **£2.00**  
 Thorn UHF tuner unit and panel for 9000 series. **£8.00**  
 Thorn 9000 frame panel. **£9.00**  
 Mullard VHF Tuner V/cap V314. **£5.00**  
 U321 T/unit V/cap. **£6.00**  
 Thorn 3500.  
 Thorn 8500 focus unit. Decca focus unit. Large or small. **£1.00** each  
 4 push button unit. Thorn 1400/1500. **£3.50**  
 4 push button for varicap with pots. **50p**  
 Decca Bradford Tuner, 5 button (4 push). **£2.75**  
 Line O/P Trans. CVC 20. **£5.00**  
 12" TV tube Hitachi A31/300W. **£12.00**

**SPEAKERS**  
 5x3 80r or 50r. **50p**  
 G9 70r. **£1.00**  
 5x3 35 ohm. **75p**  
 6x4 15 ohm. **£1.00**  
 GEC 8 ohm. **70p**  
 GEC 15 ohm. **70p**  
 NE 2B6H 2 small neon lamps used in GEC. **3p**  
 Red and Green LED, 14 mixed. **£1.00**  
 TLR 102 small red LED. **5p**  
 20 small red LED. **£1.00**

**MAINS DROPPERS**  
 GEC mains dropper for models c1441H, c2001H, c2015H, c2110H, c2113H, c2118H, c2136H, c2202H, c2219, c2601H, c2611H. **20p**  
 Thorn 6+1+100r. **35p**  
 Pye 69+161. **40p**  
 Pye 147+260r. **40p**  
 (731) 3+56+27r. **50p**

**CERAMIC FILTERS**  
 5.5 MHz. **15p**  
 6MHz. **25p**  
 3.5mm Jack socket. **7p**  
 FT 3055. **20p**  
 NPN/PNP 60v 5 amp/80w, pair. **20p**  
 6 way ribbon cable, per metre. **20p**

**TV XTALS**  
 4.433; 610 KHz. **50p**  
 6 volt 23 watt soldering iron. **£2.00**  
 Infra-red emitting diode, TIL30. **20p**  
 750 MFD 50V. **10p**

**THERMISTORS**  
 200+200+75+25 4 fuse holder +2BY133+resistors. I.T.T. panel. **£1.50**  
 ITT PT266 3W12 (Thermistor degaussing) fits most sets. **15p**  
 PTH451A or B. **20p**  
 PT 37P. **25p**  
 GEC 4700M/25v. **15p**  
 1000M/63v ITT axle. **15p**  
 22M/375v ITT. **20p**

**THYRISTORS**  
 GEC 122M for Philips G11. **60p**  
 5 amp/300v. **25p**  
 52600D 7amp/400v. **30p**  
 RCA 40506. **50p**  
 PYE 22N4444/OT113/BT116. **85p**  
 MR 501 3amp/100v. **7p**  
 MR 508 3amp/800v. **12p**  
 SCR 957. **65p**  
 SP 8385 Thorn. **25p**  
 ELC 1043 AEG. **£4.00**

**PHILIPS SNIPS:**  
 CUTS MOST THINGS. **£1.50**  
 CO-AX plugs. **12p**  
 UHF Aerial socket and leads, PYE, ITT, THORN. **35p**  
 AE Isolating socket, UHF and lead, PYE, THORN, ITT. **35p**  
 Plug and socket 3+6 pin printed circuit type, pair. **10p**  
 TBA750, SC9503P, MSC9504P GEC aerial T/V socket & lead **35p**  
 GEC Mains and battery switch. **30p**

**FRONT END FOR MUSIC CENTRE**  
**VHF/MW/LW size 13x3 1/2"**

4 push button unit, 7 transistors, V/condenser, 10 coils rod aerial I/C decoder CA 758E (no power supply and output stage). Circuit supplied. **£6.00**  
 Output stage for music centre. **£6.00**  
 Pre-amp panel 4 pots transistor etc. Plugs and sockets. **£1.00**

B9A print V/holder. **5p**  
 PYE 697 long. **15p**  
 TV 18 EHT. **40p**  
 TV 20. **50p**  
 100k 40 turn pots for V/cap tuning. **20p**  
 Mains on/off rotary. **13p**  
 Mains on/off push. **20p**  
 D/P push button on/off. **10p**  
 ITT mains on/off push button. **25p**  
 IF panel. **£1.00**  
 20 watt O/Put stage. **£1.00**

**DE-SOLDER PUMPS.** **£4.00**  
 ORP 12. **40p**  
 LP 1173/10 watt. **£1.00**  
 LP 1170. **50p**  
 AM/FM tuner unit (seconds). **50p**  
 10 watt Mullard amps. NEW. **£2.00**  
 AT 1025/08 Blue lateral. **15p**  
 Thorn hearing aid unit + ext. loudspeaker. **£2.00**  
 AD161/162, pair. **60p**  
 731 PYE 600/300v, also Bush. **75p**  
 EHT rectifier BY212. **10p**  
 3X G770/HU37EHT. **10p**  
 EHT rec 2m/a small. **20p**  
 EHT rec 2m/a large. **30p**  
 Both 12KV.  
 EHT rec used in Thorn 1400/1500. **10p**  
 Triplers x80/150. **10p**  
 CSD 118xMH rec for Thorn 3500. **10p**  
 GEC 8N 2/2000V. **8p**  
 UHF T/V aerial for portable T/V **50p**  
**TRIPLERS**  
 Thorn new type 9000. **£4.00**  
 Thorn TS 25-11TDT. **£2.50**  
 PYE TS25-11TBQ. **£1.50**

TS25 11TBW fits Autovox, Saba, Bang Oulfsen, Grundig Tanberg. **£3.75**  
 GEC 2110 after 27.1.77. **£3.50**  
 GEC G2100 TVM 25. **£2.00**  
 Philips G9. **£3.75**  
 Grundig 3000/3010, Seimens TVK 52. **£3.00**  
 ITT LP 1174/NC. **£3.00**

**MULTI CAPACITORS**  
 1000 + 2000/35v. **25p**  
 2000 + 2000/35v. **30p**  
 2500 + 2500/63v. **50p**  
 470 + 470/250v. **40p**  
 150 + 200 + 200/300v. **70p**  
 200 + 200 + 100/325v. **60p**  
 100 + 200/325v. **40p**  
 200 + 200/350v. **60p**  
 FLC 1043 on panel for I.T.T. CVC 9 175 + 100 + 100/350v to fit 3500 Thorn. **£2.00**

**THORN SPEAKERS**  
 1500 5 1/2 x 2 1/2 3Ω  
 1590 5 x 2 1/2 12Ω  
 3500 5 x 3 80Ω  
 3500 7 x 3 80Ω  
 9000 7 x 3 16Ω  
 5 x 3 loudspeaker for GEC 15Ω **£1.00**  
 UHF Modulator, CCIR. **£3.00**  
 Circuit supplied flush mounting socket. FM/TV **35p**  
 ELC 1042. **£6.50**  
 ELC 1043/05. **£6.00**  
 Mullard. Power supply 30V 1 amp Reg. **£2.00**  
 Small DX Tuner V/cap 48-88 MHz and 175- 220MHz automatic changeover. **£5.00**  
 Transductor AT4041/07. **£1.00**  
 8 Push button switch and 1 to 8 V/Ristor unit 21-68 CH. **£2.00**  
 R2540. **£1.00**  
 BUY 69 (RCA1693). **£1.00**

# SENDZ COMPONENTS

**63 BISHOPSTEIGNTON,  
 SHOEBOURNESS,  
 ESSEX SS3 8AF.**

**Reg. Office only.**

**Callers by appointment only.**

**Add 15% VAT.**

**Add 50p P. & P.**

**Add postage for all overseas parcels.**

Equivalent EQ TCA 270 series	I.C.'s—cont.	Semiconductors—cont.	TIP29C	20p	Various Mixed Packs
CA270CE 50p	SN76227 50p	BF181 20p	TIP29A 20p		10 Thermistor 50p
CA270CW 50p	SN7630P 50p	BF182 20p	TIP30A 20p		20 Slider Pots £1.00
CA3089Q 50p	SN7650N £1.00	BF185 20p	TIP31A/B 20p		30 Presets 50p
CA3090 50p	SN76532 50p	BF195 7p	TIP32 20p		40 Pots £1.50
I.C.'s	SN76533 £1.00	BF198 7p	TIP33B 10A/80V 25p		300 Condenser £1.50
MC476P 50p	SN76544N £1.00	BF200 20p	TIP41A 42 pair 50p		300 Resistor £1.50
MC1349 50p	SN76546 £1.00	BF237B 7p	NPN TIP130 60V/8A 25p		150 Electrolytic £2.00
MC1352P 50p	SN76550 15p	BF240 7p	IN3899 50p		15 bulbs 45p
PLA758PC £1.00	SN76570 50p	BF245A 7p	IN4003 5p		100 diodes £1.00
S7246/N64100 £5.00	SN76650N 50p	BF263P 25p	IN4004 5p		100 20mm fuses £2.00
SAA1020 £6.00	SN76660N 50p	BF264 20p	IN4005 5p		100 W/W resistors £1.50
SAA1021 £5.00	SN76666N 50p	BF273 7p	IN4006 5p		100 ceramic and plate condensers £1.00
SAA1024 £4.00	SN76707N 50p	BF274 7p	IN4007 5p		300 Carbon film 1/4W 1R to 2M 1TT £1.50
SAA1025 £5.00	*Denotes with heatsink.	BF337 24p	Y716 20p		1800/4K V 5p
SAS560 £1.00	Semiconductors	BF355 30p	Y827 30p		4.7NF/5K V 10p
SAS570 £1.00	AC128 25p	BF423 PNP 7p	1 amp/400V 7p		180PF/6K V 10p
SBA750B £1.00	AC153K 25p	BF458 NPN 12p	1 amp/1600V 7p		210PF/8K V 10p
SL901 £3.00	AC176K 25p	BF458T 12p	3 amp/100V 7p		270PF/8K V 10p
SL918 £3.00	AC187/8K pair 50p	BF594 7p	3 amp/300V 10p		330PF/8K V 10p
TAA320A 50p	AF139 25p	BFT43 20p	3 amp/1200V 7p		1000PF/10K V 10p
TAA470 £2.00	AU113 £1.25	BFY50 15p	W04 bridge 15p		1200PF 12K V 10p
TAA550 20p	BA159 7p	BFY90 15p	W05 bridge 25p		210PF/12K V 10p
TAA570 £1.00	BA182 7p	BR100 30p	ITT bridge 1 1/4 A C73 25p		6200PF/2000V 10p
TAA700 £2.00	BA248 7p	BSS68 20p	3 amp bridge 25p		BYW56 1000V 2A BDX32 £1.20
TBA120A 40p	BAV10 7p	BSX20 5p	B30C 600A6 12p		TIC126N Thyristors 800V 12A 65p
TBA120AS 40p	BB103VHF 7p	BSY79 7p	B30C 500 12p		Sale Condensers
TBA120C 40p	BB105UHF 7p	BT100 30p	1 amp/100V 12p		220/10 4.7/63
TBA120SA 40p	BC107 7p	BT106 50p	NK T279, AC 128 12p		330/10 33/63
TBA120SB 40p	BC108 7p	BT106 special 50p	MC 7724CP 40p		4700/10 47/63
TBA120U 40p	BC109 7p	BT109 £1.00	Condensers		100/16 330/63
TBA1441 £1.00	BC116 7p	BT116 £1.00	4700 25 25p		220/16 .01/100
TBA396 £1.00	BC139 7p	BT119 £1.00	220/40 5p		160/25 33/100
TBA480Q £1.00	BC147C 7p	BT138/10A 70p	1500/40 10p		330/25 .47/160
TBA510 £1.00	BC148B 7p	BT146 25p	1250/50 10p		470/25 2.2/160
TBA520Q £1.00	BC149C 7p	BT151/800R 70p	220/63 10p		680/25 22/160
TBA530 £1.00	BC154 7p	BT1822 £1.00	1000/63 15p		33/35 .47/250
TBA540 £1.00	BC157 7p	BTT8124 £1.00	700/250 35p		10/40 1/250
TBA550Q £1.00	BC158 7p	BTT8224 £1.00	800/250 30p		22/40 3.3/250
TBA560CQ £1.00	BC171 7p	BTY80 20p	800/250 30p		47/40 10/250
TBA560Q £1.00	BC171B 7p	BU105 50p	4/350 5p		8/300 10p
TBA570 £1.00	BC173 7p	BU105/04 £1.00	8/350 8p		680/40 .1/400
TBA625 £1.00	BC173C 7p	BU108 £1.00	22/350 8p		1.63 .005/1500
TBA641BX1 £1.50	BC174 7p	BU124 50p	.047/1000 10p		All at 6p each.
TBA651 80p	BC182L 7p	BU126 £1.00	.01/1000 10p		
TBA673 £1.00	BC183 7p	BU137 60p	.47/1000 30p		
TBA720A £1.00	BC183LB 7p	BU204 40p	.0047/1500 10p		
TBA750Q £1.00	BC207 7p	BU205 £1.00	1N8/1500 10p		
TBA800 40p	BC212LT 7p	BU208 50p	2N2/1500 10p		
TBA810S £1.00	BC213LA 7p	BU208A £1.00	.1/2000 15p		
TBA820 £1 each	BC237B 7p	BU208/02 £1.00			
TBA890 £1.00	BC238 7p	BU326 60p			
TBA920 £1.00	BC238A 7p	BU407 50p			
TBA920Q £1.00	BC245 7p	BU500 50p			
TBA950 £1.00	BC250 7p	CA270 7p			
TBA950Q £1.00	BC251A 7p	CA270EW 50p			
TBA990Q £1.00	BC252C 7p	E1222 20p			
TCA270 £1.00	BC257 30p	R2008B £1.00			
TCA270Q £1.00	BC300 30p	R2010B £1.00			
TCA270SQ £1.00	BC303 30p	R2603 50p			
TCA4500A £1.00	BC307 7p	OA90 7p			
TCA640 £1.00	BC308B 7p	OT112 £1.00			
TCA650 £1.00	BC327 7p	MJE51T NPN 300V 4A 25p			
TCA660 £1.00	BC336 20p	MJE2955/15A 50p			
TCA740 £1.00	BC337 7p	MJE1661 25p			
TCA800 £1.00	BC350 20p	BY127 10p			
TCA830S £1.00	BC365 10p	BY133 10p			
TCE82 30p	BC413C 7p	BY176 type 25p			
TCE120CQ £1.00	BC454 7p	BY176 50p			
TCE157 20p	BC455 7p	BY179 35p			
TCE527 20p	BC460 20p	BY184 25p			
TCEP100 £1.20	BC462 7p	BY187/01 10p			
TDA1170 £1.20	BC463 7p	BY190 40p			
TDA1190 £1.20	BC546 7p	BY204/4 7p			
TDA1327 £1.00	BC559 7p	BY206 10p			
TDA1412 50p	BD124 £1.50	BY210/400 7p			
TDA2540 £1.00	BD131 30p	BY210/800 10p			
TDA2640 £1.00	BD132 30p	BY223 5A/1500V 25p			
TDA2680 £1.00	BD136 10p	BY226 10p			
TDA2690 £1.00	BD207 30p	BY296 10p			
TDA3950B £2.00	BD221 20p	BY298 12p			
SN16862AN £1.00	BD228 25p	BY299 10p			
SN16964AN 50p	BD238 20p	BYF3123 wire end 50p			
SN29764 £1.00	BD239 12p	BYF3126 wire end 50p			
SN29848 50p	BD253B 25p	BYF3214 20K v 50p			
SN75108AN £1.00	BD416 35p	BYX36/600 10p			
SN76001 £1.00	BD561 2 pair 30p	BYX38/600 50p			
SN76003 £1.00	BD595 35p	BYX55/350 10p			
SN76003* £1.50	BD596 35p	2N390 7p			
SN76008KE £1.00	BD681 25p	2N2222 7p			
SN76013* £1.50	BD807 10/a 70V 30p	2N3055 35p			
SN76018KE £1.00	NPN 9 watt 25p	2N3566 7p			
SN76023* £1.50	BF127 20p	2N4355 7p			
SN76033 £1.00	BF137 20p	2N4442 60p			
SN76033* £1.50	BF157 20p	2N4444 £1.00			
SN76115 50p	BF180 20p	2N6099 25p			
SN76131 50p		2N6348 50p			
SN76226 £1.00		2N6399A 30p			
Tuner Units Varicap and Mechanical repaired. Please ask for estimate.		2SK30A 7p			

# SENDZ COMPONENTS

63 BISHOPSTEIGNTON,  
SHOEBURYNNESS,  
ESSEX, SS3 8AF

Reg. Office Only.

Callers by appointment only.

Add 15% VAT and 50p P. & P.

All items subject to availability.

Add postage for all overseas parcels.