

APRIL 1981

70p

# TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS



**ARROW GENERATOR**  
**LOCATING INTERMITTENT FAULTS**  
**THE THORN TX10 CHASSIS**  
**plus**  
**ALL THE REGULAR FEATURES**


**PHD COMPONENTS**  
**RADIO & TV COMPONENT DISTRIBUTORS**  
**UNIT 7 CENTENARY ESTATE**  
**JEFFRIES RD ENFIELD MIDDX**  
**SHOP NOW OPEN TELEX 261295**

**ALL COMPONENTS OFFERED SUBJECT TO AVAILABILITY. WE RESERVE THE RIGHT TO SUBSTITUTE REPLACEMENTS SHOULD THE ORIGINAL PART BE OUT OF STOCK OR UNAVAILABLE!**  
**PLEASE ADD 50p per parcel post and packing.**

**SEMICONDUCTORS**

AA113	0.16	AU113	3.00
AA116	0.16	AL103	3.00
AA117	0.16	AY102	3.00
AA119	0.16	BC107	0.20
QA91	0.12	BC108	0.20
QA95	0.12	BC109	0.20
QA202	0.18	BC113	0.15
BA100	0.18	BC114	0.15
BA102	0.10	BC115	0.20
BA130	0.15	BC116	0.20
BA154	0.10	BC117	0.20
BA155	0.20	BC118	0.20
BA164	0.12	BC119	0.50
BAX13	0.16	BC125	0.20
BAX18	0.08	BC126	0.20
BAY38	0.16	BC136	0.20
BY206	0.20	BC137	0.20
IN4148	0.04	BC138	0.40
BY126	0.20	BC139	0.40
BY127	0.15	BC140	0.40
BY133	0.22	BC142	0.40
BY164	0.50	BC143	0.40
SKB2/08	1.00	BC147	0.15
BY236	0.15	BC148	0.10
BYX10	0.18	BC149	0.15
IN4001	0.10	BC153	0.15
IN4002	0.10	BC154	0.15
IN4003	0.12	BC157	0.15
IN4004	0.12	BC158	0.15
IN4005	0.14	BC159	0.15
IN4006	0.12	BC160	0.40
IN4007	0.16	BC161	0.40
IN5407	0.33	BC170	0.15
BR100	0.30	BC171	0.15
BR101	0.60	BC172	0.20
BRV39	0.60	BC177	0.20
TIC1160N	1.50	BC178	0.20
BT119	2.00	BC179	0.20
BT120	2.00	BC182L	0.15
BYX/71/600	0.80	BC183L	0.15
2N444	1.50	BC184L	0.15
TV106/2	1.50	BC184LC	0.15
BYX88 2V7	0.10	BC186	0.30
BZY88 3V0	0.10	BC187	0.30
BZY88 3V3	0.10	BC203	0.15
BZY88 3V6	0.10	BC204	0.15
BZY88 3V9	0.10	BC205	0.15
BZY88 4V3	0.10	BC206	0.15
BZY88 4V7	0.10	BC207	0.15
BZY88 5V1	0.10	BC208	0.15
BZY88 5V6	0.10	BC209	0.15
BZY88 6V2	0.10	BC212L	0.15
BZY88 6V8	0.10	BC213L	0.15
BZY88 7V5	0.10	BC214L	0.15
BZY88 8V2	0.10	BC225	0.40
BZY88 9V1	0.10	BC237	0.15
BZY88 10V	0.10	BC238	0.15
BZY88 11V	0.10	BC251A	0.15
BZY88 12V	0.10	BC301	0.40
BZY88 13V	0.10	BC303	0.40
BZY88 15V	0.10	BC307	0.15
BZY88 18V	0.10	BC308	0.15
BZY88 20V	0.10	BC327	0.15
BZY88 22V	0.10	BC328	0.15
BZY88 27V	0.10	BC337	0.15
BZY88 33V	0.10	BC338	0.15
BZX61 7V5	0.20	BC547	0.15
BZX61 8V2	0.20	BC141-10	0.80
BZX61 9V1	0.20	BD115	0.50
BZX61 10V	0.20	BD124	1.80
BZX61 11V	0.20	BD131	0.70
BZX61 12V	0.20	BD132	0.60
BZX61 13V	0.20	BD133	0.70
BZX61 15V	0.20	BD134	0.70
BZX61 16V	0.20	BD140	2.50
BZX61 18V	0.20	BD159	0.80
BZX61 20V	0.20	BD238	0.50
BZX61 22V	0.20	BD380	0.70
BZX61 24V	0.20	BD441	0.70
BZX61 27V	0.20	BD537	0.70
BZX61 30V	0.20	BD538	0.70
BZX61 33V	0.20	BD507	0.70
BZX61 36V	0.20	BD508	0.70
BZX61 39V	0.20	BD181	1.20
BZX61 45V	0.20	BD182	1.20
BZX61 72V	0.20	BD709	1.00
AC107	0.35	BD710	1.00
AC127	0.50	BD442	0.70
AC127/01	0.60	BD379	0.50
AC128	0.60	BF115	0.60
AC128/01	0.60	BF118	0.60
AC141	0.50	BF152	0.40
AC141K	0.60	BF154	0.20
AC142	0.40	BF157	0.70
AC142K	0.60	BF158	0.40
AC176	0.60	BF160	0.60
AC176/01	0.60	BF163	0.60
AC186	0.40	BF167	0.50
AC187	0.40	BF173	0.50
AC187K	0.60	BF177	0.50
AC188	0.40	BF179	0.50
AC188K	0.60	BF180	0.50
AD140	1.50	BF181	0.60
AD142	1.50	BF182	0.50
AD143	1.50	BF183	0.50
AD145	1.50	BF184	0.50
AD149	1.50	BF185	0.50
AD161/2	0.70	BF194	0.20
AD262	1.50	BF196	0.20
AF121	0.60	BF197	0.20
AF124	0.60	BF198	0.15
AF125	0.60	BF199	0.15
AF126	0.60	BF200	0.15
AF127	0.60	BF204	0.15
AF139	0.60	BF240	0.45
AF202	1.00	BF241	0.50
AL239	3.00	BF258C	0.50
AU107	3.00	BF258	0.50
AU110	3.00	BF271	0.60

BF273	0.20	BF274	0.25
BF336	0.50	BF337	0.50
BF338	0.50	BF355	0.80
BF458	1.00	BF459	1.00
BF459	1.00	BF473	0.50
BFX29	0.50	BFX84	0.50
BFX88	0.50	BFX89	0.50
BFY50	0.50	BFY51	0.50
BFY52	0.50	BFY90	1.20
BFY90	1.20	BF381	0.50
BF381	0.50	BF389	0.30
BF389	0.30	BF399	0.30
BF399	0.30	BF787	0.30
BF787	0.30	BF789	0.30
BF789	0.30	BF791	0.30
BF791	0.30	BF799	0.30
BF799	0.30	BF809	0.30
BF809	0.30	BF819	0.30
BF819	0.30	BF829	0.30
BF2269	0.30	BF2279	0.30
BF2279	0.30		

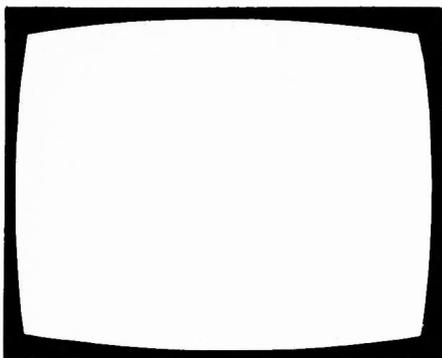

# TELEVISION

April  
1981

Vol. 31, No. 6  
Issue 366

## COPYRIGHT

©IPC Magazines Limited, 1981. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, Lavington Street, London SE1 0PF.

## SUBSCRIPTIONS

An annual subscription costs £10 in the UK, £11 overseas (\$24.20 Canada or USA). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

## BINDERS AND INDEXES

Binders (£4.40) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

## BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 85p inclusive of postage and packing.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month

- 289 **Leader**
- 290 **Teletopics**  
News, comment and developments.
- 292 **Letters**
- 295 **Readers' PCB Service**
- 296 **Dealing with Intermittent Faults** *by Derek Snelling*  
A systematic approach to tracing and repairing intermittent faults.
- 297 **CCTV Arrow Generator** *by Andrew Parr, B.Sc., C.Eng., M.I.E.E.*  
The arrow generated by this circuit can be moved around on the screen using a joystick control and can be displayed in black, white or flashing between the two. A simpler option for a movable spot is also described.
- 301 **Servicing the Thorn 4000 Chassis, Part 2** *by David Robinson*  
Dealing with the field timebase, convergence and remote control units, plus a fault summary from Down Under.
- 304 **The Shooting of Sam Magrew** *by Les Lawry-Johns*  
Les gets involved in getting this "new" Bush set going so that Sam's old mum can watch TV. The consequences were trying to say the least.
- 306 **VCR Clinic** *by Steve Beeching, T.Eng. (C.E.I.)*  
From the N1500 to the latest models, with a Panasonic machine that had received less than expert attention.
- 307 **The Thorn TX10 Chassis** *by Eugene Trundle*  
A review of Thorn's current chassis for driving large-screen 110° colour tubes. The compact chassis has some interesting circuitry, including a highly efficient chopper arrangement. One of these sets was made available for this test report.
- 310 **Practical TV Servicing: Dealing with Unfamiliar Sets** *by S. Simon*  
Most older sets use conventional circuitry which provides many signposts that aid fault diagnosis. What happens however when you come up against a transistor pump circuit, a capacitor start circuit or a self-oscillating chopper? Practical notes on what to expect.
- 313 **Miller's Miscellany** *by Chas E. Miller*  
Fault notes plus a vintage spot dealing with early Vidor TV sets and their circuitry.
- 315 **Next Month in Television**
- 316 **Selected New Products**  
Items worth considering for the workshop.
- 317 **Darlingtons in TV** *by S. George*  
The Darlington pair forms a useful circuit building block that's found numerous applications in TV sets. Its features and uses briefly surveyed.
- 318 **Fault Report** *by Dewi James*  
Faults on a variety of sets, mainly foreigners, plus a look at the EW modulator circuit used in many Sony 13in. colour sets.
- 320 **Long-distance Television** *by Roger Bunney*  
DX reception and conditions, and overseas news.
- 323 **Service Bureau**
- 325 **Test Case 220**



OUR NEXT ISSUE DATED MAY WILL  
BE PUBLISHED ON APRIL 22

# TOP QUALITY REBUILT TV TUBES


Rebuilt on the most modern equipment to original manufacturers specification

- ★ HIGH FOCUS
- ★ LONG LIFE
- ★ FULLY TESTED
- ★ FULLY GUARANTEED

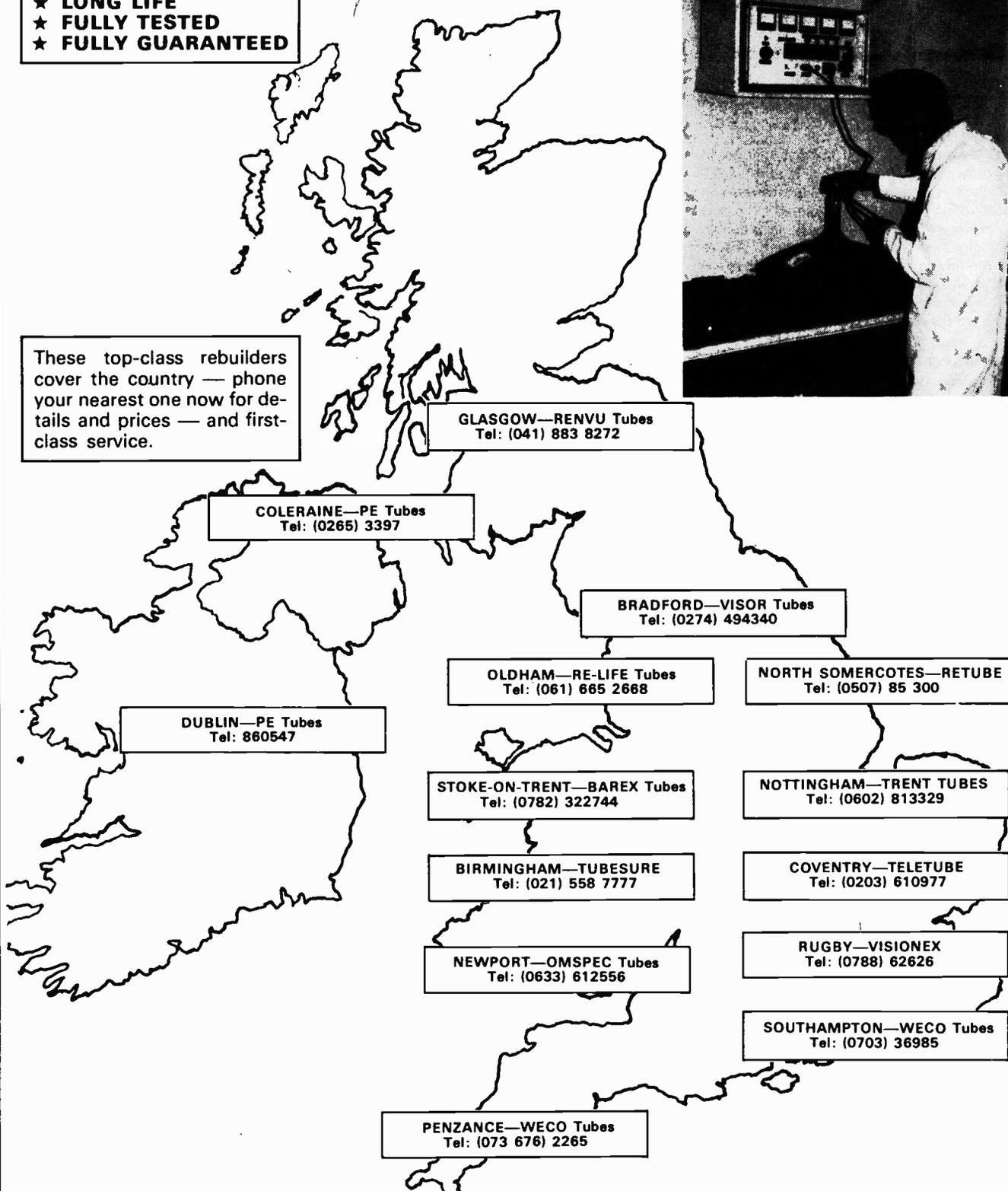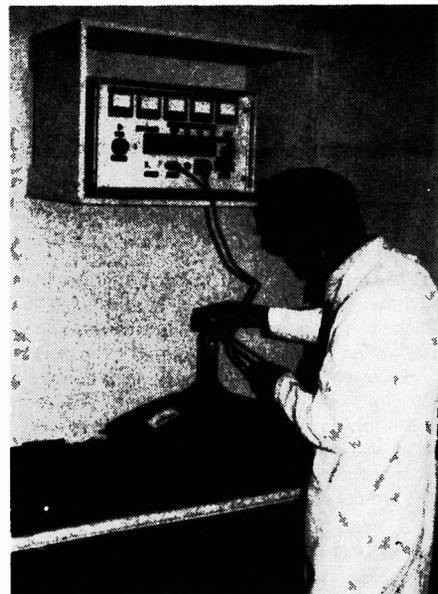These top-class rebuilders cover the country — phone your nearest one now for details and prices — and first-class service.



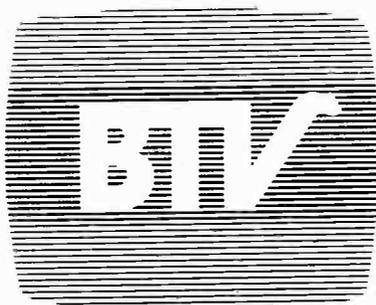All these top-class rebuilders use plant and equipment manufactured by Western-Whybrow Engineering — acknowledged as the best available, and the product of more than twenty years' experience of rebuilding colour tubes in U.K. and U.S.A. There is a constant interchange of information to ensure the highest standard of rebuilt tube.



**Can you afford NOT to switch to  
the fantastic BRIARWOOD TV trade offer?**

**100's of colour TVs  
100% complete - as they arrive - in batches of ten  
ONLY £13.00 per set**

**COLOUR TVs WITH TESTED TUBES  
GUARANTEED 100% COMPLETE**

	IN 10's	In 20's	GOOD WORKING in 10's
PYE 691	£18.00 each	£15.00	£33.00
PYE 697	£21.00 each	£18.00	£38.00
GEC 2040	£18.00 each	£15.00	£33.00
BUSH 184	£23.00 each	£20.00	£38.00
THORN 3000 19"	£28.00 each	£25.00	£43.00
THORN 3000 25"	£23.00 each	£20.00	£38.00
THORN 3500 26"	£28.50 each	£25.00	£43.00
DECCA BFD - 30's	£28.00 each	£25.00	£43.00
KORTING	£25.00 each	£22.00	£45.00
TELPRO	£23.00 each	£20.00	£38.00

Please note there is 15% VAT on all the above prices.

Foreign makes of TV's i.e. Skantic/Luxors, ASA's, Mitsubishi, Teleton, Grundigs, Saba's etc.,  
@ £40.00 each


Later types of sets i.e. G8, Thorn 3500 Varicap, ITT/KB, Thorn 8500, GEC 2100 etc., @ £50.00 each.  
@ £50.00 each.

**OPENING TIMES MON-FRI 9.00-12.00/1.00-5.45 (CLOSE 4.30 SAT)**

**CASH & CARRY SPECIAL SERVICE TO THE TRADE  
OR ASK ABOUT SPECIAL DELIVERIES ON LARGE QUANTITIES**

BRIARWOOD TELEVISION  
Briarwood House, Preston Street  
BRADFORD, West Yorkshire ND7 1LU  
Tel: (0274) 306018

**BRIARWOOD TELEVISION LIMITED**

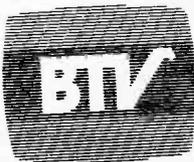

# BRIARWOOD

## QUALITY SELECTED EX EQUIPMENT SPARES

MISC S/Output Trans. £1 + VAT + P&P  
F/Output Trans. £1.25 + BAT + £1 P&P  
Scancoils £1.50 + VAT + £1 PIP. Other spares available, please write or phone for details.

### MONO TUNERS

6 button integrated all at £4.00  
U.H.F. P/Button D/S £3.50. U.H.F. P/Button S/S £4.00. Rotary £3.00 + £1 P&P

### MONO TUBES

(tested)  
19" Rimguard £3.00  
23" Rimguard £4.00  
20" Rimguard £5.00  
24" Rimguard £6.00 + £5.00 P & P

### MONO LOPTS

All D/Standard Lopts at £4.00 + £1 P&P.  
All S/Standard at £4.00 + £1 P&P.

### MONO PANELS

i.e. Philips, Bush, etc. £3.50 + £1 P&P.  
Quotations for complete S/hand chassis if required. (Diff. prices)

PLEASE ADD 15% V.A.T. TO ALL ITEMS AND OVERSEAS AT COST. CASH WITH ALL ORDERS.

### VALVES (MONO & COLOUR)

PCL82	0.10	30C1	0.10	PCC189	0.10	EF183	0.10	PL504	0.25	ECL80	0.10
PCL83	0.25	30C17	0.10	30C15	0.10	EF184	0.10	6/30L2	0.10	PL509	1.00
PCL84	0.10	PCF802	0.10	30C18	0.25	6BW7	0.10	30PL1	0.25	PY500	1.00
PCL85	0.10	PCF805	0.25	PC97	0.20	EH90	0.10	30PL13/4	0.10	GY501	1.00
PCL86	0.10	PCF806	0.10	PC900	0.10	DY802	0.10	30FL1/2	0.25	PL508	0.50
PFL200	0.10	PCF808	0.25	EF80	0.10	PY800/1	0.10	ECC82	0.10	PCF200	0.50
PCF801	0.10	PCF80	0.10	EF85	0.10	PL36	0.25	ECC81	0.10	EY51	0.15

Please note there is 25p Postage and Packing per order.

WE DO NOT SELL RUBBISH AT BRIARWOOD TV

### D/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	EHT	REG	CON	S/OUTPUT	POWER	L/TB	F/TB
Bush/Murphy	5.00	5.00	6.50	—	—	5.00	1.50	5.00	—	—
GEC/Sobell	5.00	5.50	—	—	—	5.00	—	—	—	—
Philips	5.00	7.00	—	—	—	5.00	—	—	—	—
Decaa	5.00	9.00	9.00	—	—	5.00	2.00 (19" only)	—	—	7.50
Thorn 2000	5.00	5.00	5.00	6.50	6.50	7.00	—	6.00	—	5.00
Pye	7.00	6.00	7.00	—	—	5.00	—	—	—	5.00
Baird	6.50	8.50	7.00	—	—	5.00	—	6.50	10.00	5.00
										5.00
										5.00

Postage & Packing £1.25

### S/STANDARD COLOUR SPARE PANELS

	IF	LUM	CHROMA	VIDEO	CON	POWER	L/TB	F/TB
Bush 184	9.50	—	12.00	—	6.00	6.00	12.00	—
GEC Hybrid	6.00	6.50	9.00	—	5.00	—	—	12.00
Philips G6 S/S	9.50	—	10.00	—	5.00	—	—	6.00
Thorn 3000	6.00	6.00	6.00	—	5.00	20.00	20.00	6.00
Pye 691/693	6.00	6.00	8.00	—	5.00	—	15.00	5.00
Thorn 3500	6.00	6.00	6.00	6.50	12.00	20.00	20.50	6.00

Kotring and other foreign panels available on request.

Postage & Packing £1.25

### COLOUR TUBES

17" £15.00  
18" £15.00  
19" £15.00  
19" A49/192 £18.00  
20" £18.00  
22" £20.00  
25" £15.00  
26" £22.00

Plus P&P £6.00  
New rebuilt tubes available on request.

### COLOUR TUNERS

Bush £5.00  
GEC £5.00  
Philips G6 S/S £5.00  
Pye 691 £5.00  
Thorn 3000 £5.00

Some new tuners in stock, can supply on request. Many Foreign Tuners also available on request. Plus P&P £1.

### COLOUR LOPTS

Most Lopts available from £5.00. Both British & Foreign makers. Please ring or write. P&P per Lopt £1.00

### MISC.


S/Output transformer from £1.50.  
F/Output from £1.25.  
Scancoils from £5.00.  
P&P £1.00  
Other spares available on request.

THORN 1500 TUNERS  
NEW SPECIAL OFFER  
AT £8.00

Postage & Packing £1.00

## NEW PRODUCTS!


£2.50 each  
£1.00 p&p

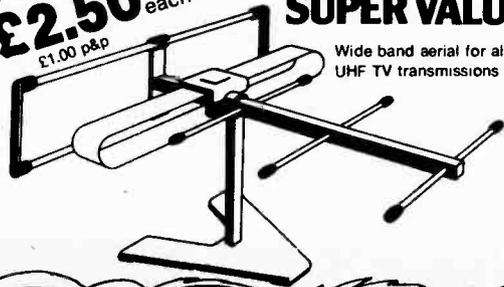

Wide band aerial for all UHF TV transmissions

### SUPER VALUE - SUPER QUALITY

£5.95 each  
£1.75 p&p

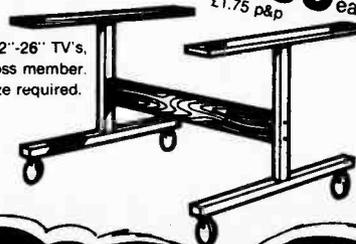

Fits 22"-26" TV's, wood finished cross member. State size required.

# TV scores with quality

WHY NOT TRY OUR EXPRESS MAIL ORDER ON ANY OF THE ITEMS LISTED

## NEW SPARE SELECTION

TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £	TYPE	PRICE £
AC107	0.24	AF181	1.00	BC179	0.12	BD137	0.30	BF218	0.12	OC36	0.90	2N3053	0.21
AC113	0.22	AF186	0.90	BC182L	0.09	BD138	0.31	BF219	0.12	OC38	0.90	2N3054	0.60
AC115	0.23	AF239	0.46	BC183L	0.09	BD139	0.40	BF220	0.12	OC42	0.45	2N3055	0.60
AC117	0.30	AU113	1.40	BC183LA	0.10	BD140	0.37	BF221	0.21	OC44	0.60	2N3442	1.00
AC125	0.23	BA130	0.08	BC183LB	0.10	BD144	1.39	BF222	0.12	OC45	0.50	2N3702	0.15
AC126	0.23	BA145	0.14	BC184L	0.09	BD145	0.50	BF224	0.18	OC46	0.39	2N3703	0.12
AC127	0.22	BA148	0.21	BC186	0.21	BD177	0.50	BF256	0.37	OC70	0.39	2N3704	0.18
AC128	0.22	BA155	0.08	BC187	0.21	BD178	0.50	BF258	0.30	OC71	0.39	2N3705	0.18
AC131	0.13	BAX13	0.05	BC209	0.11	BD203	0.40	BF259	0.30	OC72	0.39	2N3706	0.14
AC141	0.24	BAX16	0.08	BC212	0.09	BD204	0.70	BF260	0.25	OC74	0.39	2N3707	0.14
AC142	0.24	BC107	0.11	BC212L	0.09	BD222	0.73	BF262	0.28	OC75	0.39	2N3708	0.14
AC141K	0.31	BC108	0.11	BC213L	0.09	BD233	0.36	BF263	0.25	OC76	0.39	2N3772	2.00
AC142K	0.31	BC109	0.11	BC214L	0.09	BD234	0.34	BF271	0.27	OC77	0.50	2N3773	2.50
AC151	0.21	BC113	0.11	BC237	0.09	BD237	0.44	BF272	0.27	OC78	0.23	2N3819	0.30
AC165	0.21	BC114	0.11	BC238	0.09	BD238	0.44	BF273	0.16	OC81	0.26		
AC166	0.21	BC115	0.11	BC240	0.31	BDX22	0.73	BF336	0.30	OC810	0.14		
AC168	0.22	BC116	0.11	BC249	0.35	BDX32	1.98	BF337	0.29	OC82	0.26		
AC176	0.22	BC117	0.12	BC251	0.22	BDY18	0.80	BF338	0.29	OC820	0.20		
AC176K	0.28	BC119	0.24	BC257	0.20	BDY60	0.80	BF479	—	OC83	0.30		
AC178	0.23	BC125	0.15	BC262	0.18	BF115	0.30	BFT	0.27	OC84	0.30		
AC186	0.26	BC126	0.15	BC263B	0.20	BF12:	0.29	BFT	0.27	OC85	0.28	DY87	0.80
AC187	0.23	BC136	0.15	BC267	0.19	BF154	0.12	BFX84	0.27	OC123	0.25	DY802	0.64
AC188	0.23	BC137	0.17	BC281	0.24	BF158	0.19	BFX85	0.27	OC169	1.20	ECC82	0.60
AC187K	0.30	BC137	0.23	BC300	0.27	BF159	0.24	BFX	0.30	OC170	1.20	EF80	0.55
AC188K	0.30	BC139	0.23	BC301	0.27	BF160	0.23	BFY37	0.22	OC171	0.92	EF183	0.70
AD130	0.58	BC140	0.24	BC302	0.30	BF163	0.30	BFY50	0.21	OA91	0.07	EF184	0.70
AD140	0.68	BC141	0.27	BC303	0.27	BF164	0.30	BFY51	0.21	BRC4443	0.85	EH90	0.75
AD142	0.80	BC142	0.27	BC307	0.11	BF167	0.30	BFY52	0.21	R2008B	1.50	PC86	0.85
AD143	0.70	BC143	0.27	BC307A	0.11	BF173	0.21	BFY53	0.27	R2009	1.30	PCC89	0.65
AD145	0.70	BC147	0.10	BC308A	0.12	BF177	0.26	BFY55	0.33	R2010B	1.50	PCC189	0.80
AD149	0.64	BC148	0.10	BC309	0.14	BF178	0.24	BFX	—	R2265	1.50	PCF80	0.80
AD161	0.42	BC149	0.10	BC337	0.12	BF179	0.28	BHA0002	1.90	R2305	0.38	PCF86	0.72
AD162	0.42	BC153	0.12	BC338	0.15	BF180	0.30	BSX20	0.23	R2305	—	PCF801	0.70
AD161)	—	BC154	0.12	BC487	0.20	BF181	0.34	BSX76	0.23	BD222	0.37	PCF802	0.85
AD162)	1.00	BC157	0.12	BC547	0.10	BF182	0.30	BSY84	0.36	R2540	2.50	PCL82	0.75
AF106	0.42	BC158	0.12	BC548	0.11	BF183	0.29	BU105	1.00	S2802	—	PCL84	0.80
AF114	0.37	BC159	0.12	BC549	0.11	BF184	0.27	BU105 02	1.50	SCR957	0.65	PCL86	0.85
AF118	0.45	BC160	0.26	BC557	0.12	BF185	0.29	BU105 04	2.00	TIP31A	0.38	PCL805	0.82
AF121	0.37	BC161	0.26	BCX33	0.10	BF186	0.32	BU126	1.40	TIP32A	0.36	PLF200	1.00
AF125	0.30	BC167	0.11	BD112	0.39	BF192	—	BU205	1.20	TIP3055	0.53	PL36	£1.10
AF126	0.30	BC168	0.11	BD113	0.65	BF194	0.15	BU206	1.60	TIP31B	0.39	PL84	0.80
AF127	0.30	BC169	0.11	BD115	0.32	BF195	0.13	BU208	1.60	TIS90	0.23	PL504	0.30
AF139	0.40	BC171	0.10	BD116	0.47	BF196	0.13	OC22	1.10	TIS91	0.25	PL508	1.50
AF150	0.27	BC171A	0.10	BD124	1.30	BF197	0.13	OC23	1.30	TV106	1.09	PL509	2.45
AF151	0.30	BC172	0.10	BD131	0.36	BF198	0.12	OC24	1.30	MJE340	0.50	PL802	0.75
AF170	0.92	BC173	0.12	BD132	0.36	BF199	0.14	OC25	1.00	MJE520	0.45	PY88	0.75
AF172	1.00	BC177	0.12	BD133	0.37	BF200	0.28	OC26	1.00	2N2219	0.40	PY500A	1.60
AF178	1.00	BC178	0.12	BD135	0.30	BF216	0.12	OC28	1.30	2N2646	0.40	PY81/800	0.70
AF180	1.00	BC178A	0.12	BD136	0.30	BF217	0.12	OC35	1.00	2N2926	0.15		

### E.H.T. Trays

TYPE	PRICE £	TYPE	PRICE £
Pye 691 693	4.50	Philips G8	—
Pye 715/731/735	5.50	Philips G9	5.50
Pye 737	5.40	Philips 550	5.30
Decca (Large Screen)	—	GEC C2110	5.50
CS2030/2232/2630/2632/2230/2233/	—	GEC Hybrid	—
2631	5.00	CTV	5.10
Decca 80	5.30	Thorn 3000/3500	—
Decca 100	5.30	Thorn 800	2.42
Philips G8	—	Thorn 8500	4.75
520/540	5.30	Thorn 9000	5.50
Philips G9	5.50	GEC TVM25	2.50
Philips 550	5.30	ITT KB CVC	—
GEC C2110	5.50	ITT KB CVC 5/7/8/9	5.10
GEC Hybrid	—	ITT KB CVC 20/25	—
CTV	5.10	30/32	5.50
Thorn 3000/3500	—	Bush CTB25	—
Thorn 800	2.42	MK3	—
Thorn 8500	4.75	Quadripler	8.00
Thorn 9000	5.50	Bush X179	4.50
GEC TVM25	2.50	RRI (RBM)	—
ITT KB CVC	—	A823	5.00
ITT KB CVC 5/7/8/9	5.10	4/Bang & Olufsen	—
ITT KB CVC 20/25	—	50/100 Grundig	—
30/32	5.50	5010/5011/5012/6011/6012/7200/2052/2210/2252R	—
Bush CTB25	—	Tandberg (radionette)	—
MK3	—	Autovox	6.60
Quadripler	8.00	Grundig	—
Bush X179	4.50	3000/3010	—
RRI (RBM)	—	Saba 2705/3715	—
A823	5.00	Telefunken	—
4/Bang & Olufsen	—	709/710/	—
50/100 Grundig	—	717/2000	6.80
5010/5011/5012/6011/6012/7200/2052/2210/2252R	—	Korting	6.80
Tandberg (radionette)	—		
Autovox	6.60		
Grundig	—		
3000/3010	—		
Saba 2705/3715	—		
Telefunken	—		
709/710/	—		
717/2000	6.80		
Korting	6.80		

All transistors, IC's offered are new and branded. Manufactured by Mullard, I.T.T., Texas, Motorola etc.

Please add 15% VAT to all items and overseas at cost

P & P U.K. 50p per order, overseas allow for package and postage. Cash with all orders. All prices subject to alteration without notice

## MAIL ORDER TV BARGAINS

PYE 691	22" @ £55.00
PYE 691	26" @ £55.00
PYE 697	22" @ £65.00
PYE 697	26" @ £65.00
BUSH 184	19" @ £70.00
BUSH 184	22" @ £70.00
BUSH 184	26" @ £70.00
GEC 2040	19" @ £55.00
GEC2040	22" @ £55.00
GEC 2040	25" @ £55.00
GEC 2040	26" @ £65.00
KORTING	22" @ £70.00
KORTING	26" @ £80.00
THORN 3000	19" @ £70.00
THORN 3000	25" @ £60.00
Good working mono's Pye, GEC, Bush etc.	
20" & 24" S/S	£20.00
20" & 24" D/S	£18.00
19" & 23" D/S P/Button	£15.00
19" & 23" D/S Rotary	£12.00

### TYPE PRICE £ IC's

BTT6018	1.00
CA3605	1.20
MC7/c	—
MC14016	0.50
SN76003N	1.40
SN76013N	1.20
SN76013ND	1.00
SN76023N	1.20
SN76023ND	1.00
SN76110N	1.00
SN76226DN	1.50
SN76227N	1.20
SN76532N	1.30
SN76550N	0.30
SN76666N	0.70
TAA570	1.38
TBA120AS	1.00
TBA120S	0.75
TBA120SQ	0.75
TBA395	2.20
TBA341	0.97
TBA520	1.40
TBA520Q	1.10
TBA530Q	1.10
TBA540	1.30
TBA540Q	1.45

TBA550Q	1.40	BAX13	0.08
TBA560C	1.50	BAX16	0.10
TBA560CQ	1.50	BY126	0.10
TBA570	1.00	BY127	0.10
TBA570Q	1.00	BY164	0.40
TBA800	1.00	BY179	0.57
TBA810	1.50	BY226	—
TBA920	2.00	BY227	0.12
TBA920Q	1.50	BYF206	0.14
TBA990Q	1.50	1N4001	0.04
TCA270SQ	1.45	1N4002	0.05
TCA270SA	1.45	1N4003	0.06
TCA270Q	—	1N4004	0.07
TCA1327B	1.00	1N4005	0.07
TCA800	2.00	1N4006	0.08
TDA1010	—	1N4007	0.08
TDA1327B	1.00	1N4148	0.05
SBA750	1.75	1N4751	0.14
SC9503P	1.20	1N5401	0.12
SC9504P	1.20	1N5403	0.12
SL901B	3.50	1N5404	0.14
SL917B	5.00	1N5405	0.14
		1N5406	0.14
		1N5408	0.25
		BR100	0.22
		BR101	0.28
		BT106	1.19
		BT108	1.23
		BT109	1.09
		BT116	1.60
		BT120	1.60
		2N4444	0.90

Cheques, P.O. or Cash with orders Please. Please note there is 15% VAT on all the above prices. Plus £10.00 p & p for colour TV, £5.00 for mono. ENGLAND, WALES and SCOTLAND. Inland N & S IRELAND £15.00 for colour. £7.00 for mono.

EXPORT COLOUR & MONO TV's AVAILABLE READY FOR USE OVERSEAS

# BRIARWOOD TELEVISION LTD


Briarwood House, Preston Street, Bradford West Yorkshire BD7 1LU  
Tel: (0274) 306018



# MANOR SUPPLIES

## PAL COLOUR BAR GENERATOR

plus CROSS HATCH KIT (Mk. 4)

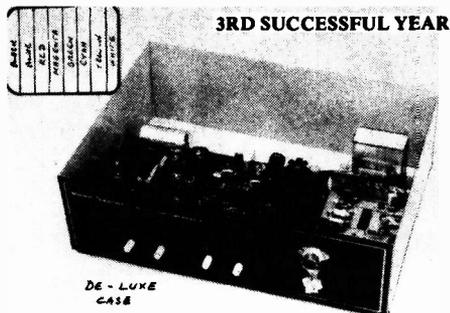

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

**PRICE OF MK4 COLOUR BAR & CROSS HATCH KIT £40.25 + £1.40 P/Packing. DE-LUXE CASE £5.95. ALUMINIUM CASE £3.30, BATT HOLDERS £1.70, ALTERNATIVE STAB. MAINS SUPPLY KIT £5.55.**

ALSO THE MK3 COLOUR BAR GENERATOR KIT FOR ADDITION TO MANOR SUPPLIES CROSS HATCH UNITS. £28.75 + £1.40 p.p. CASE EXTRA £2.00. BATT. HOLDERS £1.70.

- ★★ Kits include drilled P.C. board, with full circuit data, assembly and setting up instructions.
- ★★ All special parts such as coils and modulator supplied complete and tested, ready for use.
- ★★ Designed to professional standards.
- ★★ Demonstration models at 172 West End Lane, NW6.
- ★★ Every kit fully guaranteed. Technical back-up service.

**MK 4 DE LUXE (BATTERY) BUILT & TESTED £66.70 + £1.80 P & P. MK 4 DE LUXE (MAINS) BUILT & TESTED £80.50 + £1.80 P & P. VHF MODULATOR (CHI to 4) FOR OVERSEAS £4.60.**

INFORMATION ON VIDEO TAKE-OFF FOR C.C.T.V.

(ALL PRICES INCLUDE 15% VAT)



# MANOR SUPPLIES

## TELETEXT KIT (MK2)

(INCORPORATING MULLARD DECODER 6101VML)

BACKED BY YEARS OF EXPERIENCE

INFRA RED REMOTE CONTROL

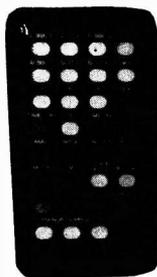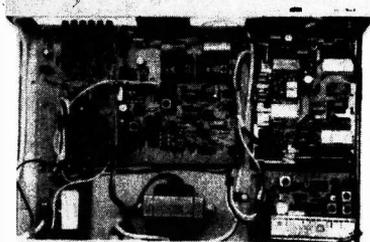

- EXTERNAL UNIT, PLUGS INTO AE SOCKET OF TV RECEIVER.
- LATER SPEC (DOUBLE HEIGHT, BACKGROUND COLOUR ETC).
- INFRA RED REMOTE CONTROL (MULLARD 5000 SYSTEM) STATION SELECTION, TEXT, MIX, TIME, DOUBLE HEIGHT, HOLD, CLOCK, REVEAL RESET ETC, ETC.
- INCLUDES COMPLETE & TESTED 6101 VML (MULLARD) DECODER, SAW FILTER IF PANEL & 32 BUTTON REMOTE CONTROL HANDSET.
- SUITABLE FOR BBC DEAF SUB-TITLE TRANSMISSIONS-REMODULATES PICTURE.
- CONVERTS ANY UHF RECEIVER TO STATION SELECTION REMOTE CONTROL AND TELETEXT. (SIMPLIFIED KIT AVAILABLE FOR REMOTE CONTROL ONLY).
- FACILITIES FOR VIDEO OUTPUT, MONITORS, CCTV ETC.
- AUDIO OUTLET FOR EXTERNAL HI-FI AMPLIFIER.
- EVERY KIT EASY TO ASSEMBLE & FULLY GUARANTEED. TECH. BACK-UP SERVICE.
- DE-LUXE CASE MEASUREMENTS APPROX. 154 x 104 x 34.
- WORKING MODEL AT 172 WEST END LANE, N.W.6.

FURTHER DETAILS ON REQUEST

ALSO, MANOR SUPPLIES TELETEXT MK1 KIT (TEXAS) NOW WITH REMOTE CONTROL PRICE £193.20 P/P £2.80.

## TELETEXT & TELEVISION SPARES

"TELEVISION" NEW MONITOR PARTS AVAILABLE.  
 "TELEVISION" NEW PORTABLE RECEIVER PARTS AVAILABLE.  
 WORKING MODEL & PANEL TEST SERVICE.  
 NEW CTV SIGNALS BOARD PARTS NOW AVAILABLE.  
 SPECIAL OFFER TEXAS XM11 TELETEXT MODULE NEW & TESTED, LIMITED QUANTITY AT HALF PRICE £69.00 p.p. £1.40.  
 "TELEVISION" COLOUR RECEIVER PROJECT ALL PARTS AVAILABLE AT PRESENT. POWER, SIGNAL & TIMEBASE. SEND OR PHONE FOR LIST. WORKING MODEL ON SHOW WITH TELETEXT. (PANEL TEST SERVICE NOW AVAILABLE).  
 NEW SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND TESTED FOR T.V. SOUND & VISION £32.80 p.p. £1.10.  
 TELETEXT 5V STABILISED MAINS POWER SUPPLY (FOR TEXAS OR MULLARD DECODERS) £6.70 p.p. £1.00.  
 TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE £11.30 p.p. £1.00. XM11 INTERFACE PANEL (THORN) £2.10 p.p. 75p.  
 CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET £12.65 p.p. 50p. (ALUM CASE £2.60 p.p. 80p.)  
 ADDITIONAL GREY SCALE KIT £3.35 p.p. 35p.  
 TV TEST GENERATOR UHF MODULATOR £4.60 p.p. 40p.  
 UHF SIGNAL STRENGTH METER KIT £20.00 (VHF VERSION £21.60). ALUM CASE £2.00 DE LUXE CASE £5.95.  
 CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO £28.00 p.p. £2.00.

PHILIPS 210, 300 Series Frame T.B. Panels £1.15 p.p. 75p.

BUSH 2718 BC6100 SERIES IF PANEL £5.75 p.p. 80p.

BUSH A816 IF PANEL (SURPLUS) £1.90 p.p. 80p.

BUSH 161 TIMEBASE PANEL A634 £3.25 p.p. £1.40.

DECCA BRADFORD IF, TB, Power Panels ex Rental £5.52 p.p. £1.20.

GEC SERIES I MONO PANELS £2.10 p.p. £1.30.

GEC 2110 DECODER, RGB PANELS £5.75 EACH p.p. £1.00.

GEC 2010 SERIES TIMEBASE PANEL £1.15 p.p. 95p.

GEC 2040 (TYPE) CDA PANEL £2.88 p.p. £1.25.

PYE 697 Frame T.B. ex Rental £2.88 p.p. 90p.

PYE 697 Line T.B. P.C.B. type salvaged £4.80 p.p. £1.50.

THORN 3000 LINE TB PCB £5.75 each p.p. 85p.

THORN 3000 VID, IF, DEC. Ex Rental £5.75 each p.p. £1.30.

THORN 8000/8500 IF/DECODER PANELS salvaged £5.52 p.p. £1.60.

THORN 8000/8500 POWER/SALV. SPARES £2.88 p.p. 60p.

THORN 9000 LINE T.B. (incl. LOPT etc.), SALV., SPARES £8.62 p.p. £1.60.

THORN 9000 IF/DECODER PANELS Salvaged £8.90 p.p. £1.60.

PHILIPS G8/G9 IF/DECODER Panels for small spares £4.80 p.p. £1.30.

PHILIPS G6 Single standard convergence panels £2.90 p.p. £1.20.

G8 IF Panels for small spares £1.75 p.p. 95p.

G8 Decoder panels salvaged £4.25. Decoder panels for spares £2.00 p.p. £1.35.

VARICAP, U321, ELC 1043/06 £7.82, ELC 1043/05 £6.35 p.p. 60p.;

G.I. type (equiv. 1043/05) £4.00 p.p. 60p. Control units, 3PSN £1.40, 4PSN

£1.75, 5PSN £2.00, 6PSN £2.10, Special Offer 6PSN £1.15 p.p. 50p.

BUSH "Touch Tune" assembly, incl. circuit £5.75 p.p. 85p.

VARICAP UHF-VHF ELC 2000S £9.80. BUSH TYPE £9.00 p.p. 85p.

VARICAP VHF MULLARD ELC1042 £7.95 p.p. 45p.

UHF/625 Tuners, many different types in stock. UHF tuners transisted. incl.

s/m drive. £3.28. Mullard 4 position push button £2.88 p.p. £1.30.

TRANSISTORISED 625 IF for T.V., sound, tested. £7.82 p.p. 75p.

MULLARD EP9000 Audio Unit incl. LP1162 Module £4.38 p.p. 85p.

LINE OUTPUT TRANSFORMERS. new guar. p.p. £1.25.

BUSH 145 to 186SS series ..... £8.80

BUSH, MURPHY A816 series ..... £9.80

DECCA 20/24, 1700, 2000, 2401... £8.50

FERG., HMV, MARCONI, ULTRA

850 to 1580 ..... £6.80

GEC 2000, 2047 series, etc. .... 18.50

INDESIT 20/24EGB ..... £8.50

ITT/KB VC1 to 53, 100, 200, 300 £8.50

MURPHY 1910 to 2417 series ..... £8.50

PHILIPS 19T170, 210, 300 ..... £8.50

PYE, INVICTA, EKCO, FERR.

368, 169, 569, 769 series ..... £8.50

SPECIAL OFFER

GEC 2114J/FINELINE ..... £5.50

PYE 40, 67 ..... £5.50

THORN 1590/1591 ..... £5.50

KB VC ELEVEN (003) ..... £3.25

COLOUR LOPTS p.p. £1.30.

R.B.M. A823 ..... £5.60

R.B.M. Z179 ..... £6.70

DECCA Bradford (state Model No.) ..... £10.15

DECCA 80, 100 ..... £9.50

GEC 2028 ..... £7.82

GEC 2040 ..... £11.30

GEC 2110 Series ..... £12.20

ITT CVC 5 to 9 ..... £10.15

ITT CVC 30 Series ..... £10.15

PYE 691-697 (BOBBINS) ..... £7.60

PYE 713-715 ..... £7.85

PHILIPS G8, G9 ..... £10.15

PHILIPS 570 ..... £7.85

THORN 3000/3500 SCAN, EHT ..... £7.85

THORN 8000/8500 ..... £14.80

THORN 9000 ..... £10.15

OTHERS AVAILABLE. PRICES ON REQUEST. ALSO F.O.PTS.

THORN 950 3 Stick Tray £1.15 p.p. 55p. Most others available.

THORN 3000/3500, 8000, 8500, MAINS TRANSF. £10.15 p.p. £1.80.

6-3V CRT Boost Transformers £5.00, Auto Type £3.20, p.p. 95p.

CALLERS WELCOME AT SHOP PREMISES Telephone 01-794 8751/7346

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE

NOT NORMALLY ADVERTISED, ENQUIRIES INVITED

LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

## MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159 pass door

W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)


W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 84 GOLDERS MANOR DRIVE, LONDON N.W.11.

ALL PRICES INCLUDE VAT AT 15%

**TRANSISTORS, ETC.**

Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.48	AU103	2.40	BC192	0.56	BC377	0.29	BD234	0.68	BF222	0.51	BFX29	1.82	MPSU05	0.66	ZTX500	0.18	2N3819	0.47
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.39	BD235	0.63	BF224 & J	0.22	BR101	0.53	MPSU06	0.76	ZTX502	0.22	2N3820	0.72
AC126	0.36	AU110	2.40	BC205*	0.39	BC440	0.52	BD236	0.63	BF240	0.32	BR103	0.64	MPSU55	1.26	ZTX504	0.28	2N3866	1.08
AC127	0.54	AU113	2.60	BC206*	0.37	BC441	0.59	BD237	0.68	BF241	0.31	BR303	1.06	MPSU56	1.32	2N404	1.30	2N3904	0.20
AC128	0.46	BC107*	0.16	BC207*	0.39	BC461	0.78	BD238	0.68	BF244*	0.51	BR4443	1.76	MPSU60	0.82	2N696	0.46	2N3905	0.20
AC128K	0.55	BC108*	0.15	BC208*	0.37	BC477	0.30	BD253	0.68	BF245*	0.43	BR4939	0.80	MPU131	0.59	2N697	0.46	2N3906	0.20
AC141	0.65	BC109*	0.16	BC209*	0.29	BC478	0.25	BD410	1.65	BF254	0.48	BR556	0.44	OC26	1.90	2N706A	0.33	2N4036	0.94
AC141K	0.70	BC113	0.22	BC211*	0.38	BC478	0.25	BD413	0.65	BF255	0.58	BS27	0.92	OC28	1.48	2N708	0.29	2N4123	0.17
AC142	0.60	BC114	0.22	BC212*	0.17	BC547*	0.13	BD435	0.58	BF256*	0.49	BT106	1.50	OC29	1.60	2N814	0.32	2N4124	0.17
AC142K	0.65	BC115	0.24	BC212L*	0.17	BC548*	0.13	BD438	0.71	BF257	0.44	BT109	1.99	OC35	1.25	2N816	0.54	2N4126	0.17
AC151	0.31	BC116*	0.25	BC213*	0.16	BC549*	0.15	BD437	0.74	BF258	0.52	BT116	1.45	OC36	1.25	2N818	0.52	2N4236	0.20
AC152	0.36	BC117	0.30	BC213L*	0.16	BC550	0.24	BD438	0.75	BF259	0.54	BT119	5.18	OC42	0.90	2N830	0.29	2N4289	0.32
AC153	0.42	BC118	0.24	BC214*	0.18	BC556	0.23	BD519	0.88	BF262	0.73	BU102	3.35	OC44	0.68	2N1164	1.02	2N4292	0.32
AC153K	0.52	BC119	0.34	BC214L*	0.18	BC557*	0.16	BD520	0.88	BF263	0.66	BU105	1.80	OC45	0.83	2N1304	1.40	2N4416	0.85
AC154	0.41	BC125*	0.30	BC225	0.42	BC558*	0.16	BD599	0.87	BF270	0.47	BU105/02	1.95	OC70	0.65	2N1305	1.29	2N4444	1.90
AC176	0.45	BC126	0.30	BC237*	0.16	BC559*	0.17	BD600	1.23	BF271	0.42	BU108	2.98	OC71	0.73	2N1306	1.49	2N4421	0.80
AC178	0.51	BC132	0.20	BC238*	0.15	BCY10	0.30	BD663BR	0.86	BF272A	0.80	BU126	2.91	OC72	0.73	2N1307	1.32	2N5042	1.85
AC179	0.55	BC134	0.22	BC239*	0.22	BCY30A	1.06	BDX18	1.55	BF273	0.33	BU204	2.50	OC81	0.83	2N1308	1.53	2N5080	0.28
AC187	0.66	BC135	0.21	BC251*	0.25	BCY32A	1.19	BDX32	1.95	BF274	0.34	BU205	2.88	OC82	0.95	2N1711	0.47	2N5081	0.30
AC187K	0.65	BC136	0.22	BC252*	0.26	BCY34A	1.02	BDY16A	0.53	BF336	0.63	BU208	2.89	OC130	1.30	2N1893	0.52	2N5084	0.53
AC188	0.52	BC137	0.30	BC253*	0.38	BCY72	0.27	BDY17	1.55	BF337	0.65	BU208	2.89	OC140	1.35	2N2102	0.71	2N5086	0.48
AC188K	0.61	BC138	0.35	BC261A*	0.28	BD115	1.35	BDY20	2.29	BF338	0.68	BU407	1.38	OC170	0.80	2N2217	0.55	2N5087	0.50
AC193K	0.70	BC140	0.36	BC262A*	0.28	BD123	1.50	BDY38	1.38	BF355	0.72	BU477	2.50	OC171	0.82	2N2218	0.38	2N5208	0.59
AC194K	0.74	BC141	0.44	BC263*	0.26	BD124	1.85	BF115	0.48	BF362	0.49	CI06D	0.80	OC200	3.90	2N2219	0.42	2N5294	0.68
AC194K	0.74	BC141	0.44	BC267*	0.20	BD130Y	1.56	BF117	0.45	BF363	0.49	CI06F	0.43	OC201	3.95	2N2221A	0.26	2N5296	0.68
AC194K	0.74	BC141	0.44	BC268*	0.28	BD131	0.58	BF120	0.56	BF367	0.29	CI11E	0.46	OC202	2.40	2N2222A	0.41	2N5298	0.71
AC194K	0.74	BC141	0.44	BC286	0.40	BD132	0.68	BF121	0.85	BF451	0.43	DA0N1	0.64	OC205	3.95	2N2369A	0.40	2N5322	1.16
AC194K	0.74	BC141	0.44	BC287	0.49	BD133	0.77	BF123	0.48	BF457	0.46	E300	0.42	OC271	1.98	2N2401	0.80	2N5449	1.18
AD140	1.79	BC149*	0.13	BC291	0.27	BD135	0.37	BF125	0.85	BF458	0.49	E1222	0.47	ON236A	0.94	2N2484	0.35	2N5457	0.46
AD142	1.90	BC152	0.42	BC294	0.36	BD136	0.38	BF127	0.61	BF459	0.52	E5024	0.19	R2008B	2.72	2N2570	0.74	2N5458	0.40
AD143	1.78	BC153	0.38	BC297	0.36	BD137	0.40	BF137F	0.78	BF459	0.16	GET872	0.46	R2010B	2.79	2N2586	0.82	2N5459	0.88
AD149	1.42	BC154	0.41	BC300	0.82	BD138	0.42	BF138	0.46	BF586	0.17	MG402	0.18	R2322	0.76	2N2784	1.15	2N5494	1.05
AD161	0.66	BC157*	0.13	BC301	0.38	BD139	0.46	BF158	0.25	BF597	0.27	MG404/02	0.18	R2322	0.76	2N2869	0.55	2N5496	1.45
AD161/162	1.22	BC158*	0.12	BC302	0.66	BD140	0.50	BF159	0.27	BF599	0.30	ME6001	0.18	ST2110	0.49	2N2894	0.48	2N6027	0.55
AD162	0.71	BC159*	0.14	BC303	0.64	BD144	2.24	BF160	0.20	BF640	0.29	ME6002	0.18	ST6120	0.48	2N2904*	0.40	2N6107	0.71
AF114	1.32	BC160	0.52	BC304	0.44	BD145	0.75	BF161	0.84	BF641	0.30	MJ2955	1.30	TIC44	0.25	2N2905*	0.39	2N6122	0.60
AF115	1.26	BC161	0.58	BC307*	0.17	BD150A*	0.51	BF163	0.66	BF650	0.29	MJ3000	1.58	TIC46	0.35	2N2906*	0.36	2N6178	1.07
AF116	1.28	BC167B	0.15	BC308*	0.14	BD155	0.90	BF164	0.95	BF652	0.33	MJ340	0.68	TIC47	0.45	2N2926G	0.15	2N6180	1.39
AF117	1.32	BC168B	0.14	BC309*	0.18	BD157	0.51	BF166	0.50	BF653	0.29	MJ341	0.72	TIP29A	0.47	2N2926O	0.14	2N6211	2.74
AF118	0.98	BC169C	0.15	BC317*	0.15	BD158	0.75	BF167	0.38	BF662	0.28	MJ370	0.74	TIP30A	0.50	2N2926Y	0.14	2S8337BP	4.28
AF121	0.68	BC170*	0.15	BC318*	0.15	BD159	0.68	BF173	0.35	BF679	0.30	MJ371	0.79	TIP31A	0.51	2N2955	1.12	2S8458C	0.78
AF124	0.35	BC171*	0.15	BC319*	0.19	BD160	2.69	BF177	0.36	BF680	0.29	MJ520	0.85	TIP31C	0.67	2N3053	0.48	2S8463A	2.25
AF125	0.38	BC172*	0.14	BC320	0.17	BD163	0.67	BF178	0.46	BF681	0.31	MJ521	0.95	TIP32A	0.66	2N3054	0.66	2S8493D	1.80
AF126	0.36	BC173*	0.22	BC321A & B	0.18	BD165	0.66	BF179	0.38	BF688	0.42	MJ2955	1.20	TIP32C	0.72	2N3055	0.72	2N41061	1.05
AF127	0.66	BC174A & B	0.26	BC322	0.28	BD166	0.68	BF180	0.53	BF689	0.41	MJ3000	1.95	TIP33A	0.77	2N3250	0.52	2S81172Z	3.88
AF139	0.58	BC176	0.22	BC323	1.15	BD175	0.90	BF181	0.53	BF693	0.55	MJ3055	1.22	TIP34A	0.84	2N3254	0.58	2S8234	1.45
AF147	0.52	BC177*	0.20	BC327	0.16	BD177	0.58	BF182	0.44	BF694	0.52	MJ3055	1.22	TIP41A	0.72	2N3391A	0.38	3N128	1.60
AF149	0.45	BC177*	0.20	BC328	0.18	BD178	0.92	BF183	0.52	BF695	0.52	MPS3702	0.33	TIP42A	0.80	2N3633A	0.80	400250	0.98
AF178	1.35	BC178*	0.22	BC337	0.17	BD181	1.94	BF184	0.44	BF696	0.19	MPS3705	0.30	TIP2955	0.77	2N3703	0.17	40251	1.14
AF179	1.36	BC179*	0.28	BC338	0.17	BD182	2.10	BF185	0.42	BF697	0.20	MPS6521	0.36	TIP3055	0.58	2N3704	0.19	40327	0.67
AF180	1.35	BC182*	0.15	BC340	0.19	BD183	1.34	BF186	0.42	BF698	0.65	MPS6523	0.36	TIS43	0.44	2N3705	0.17	40361	0.48
AF181	1.33	BC182L*	0.15	BC347*	0.17	BD184	2.30	BF194*	0.14	BF699	0.38	MPS6526	0.44	TIS73	1.36	2N3706	0.16	40362	0.50
AF186	1.48	BC183*	0.14	BC348A & B	0.17	BD187	1.20	BF195*	0.13	BF699	0.42	MPSA05	0.30	TIS90	0.23	2N3707	0.18	40410	0.94
AF202	0.45	BC183L*	0.15	BC349B	0.17	BD188	1.25	BF196	0.14	BF784	0.36	MPSA06	0.32	TIS91	0.28	2N3708	0.17	40429	0.88
AF239	0.43	BC194*	0.15	BC349B	0.17	BD189	0.87	BF197	0.19	BF785	0.37	MPSA55	0.55	TN715	0.70	2N3715	1.70	40430	1.39
AF240	1.40	BC184L*	0.15	BC350*	0.24	BD222	0.91	BF198	0.29	BF786	0.36	MPSA56	0.45	TX109	0.16	2N3717	2.09	40595	1.79
AF279S	0.91	BC185	0.36	BC351*	0.22	BD225	0.91	BF199	0.29	BF787	0.36	MPSA93	0.56	TX123	0.23	2N3722	2.08	40803	1.13
AL100	1.30	BC186	0.25	BC352A*	0.24														

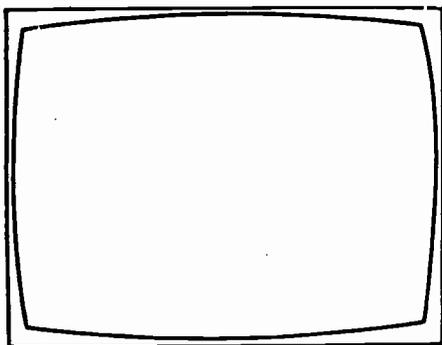

# TELEVISION

## Tackling Technology

### EDITOR

John A. Reddihough

### ASSISTANT EDITOR

Luke Theodossiou

### ART EDITOR

Roy Palmer

### ADVERTISEMENT MANAGER

Roy Smith  
01-261 6671

### CLASSIFIED ADVERTISEMENTS

Colin R. Brown  
01-261 5762

### COVER PHOTO

Our cover photograph this month was provided by Mullard Ltd. and shows an ion implantation machine at their Southampton factory being used in the production of i.c.s for teletext and viewdata applications. Ion implantation allows the doping levels in semiconductor material to be very closely controlled. Mullard Ltd. is currently the largest UK manufacturer of teletext and viewdata chips. Production is expected to reach two million this June, with half exported.

For those concerned with maintaining consumer electronic products, the problems of keeping pace with the developing technology are ever increasing. In such fields as plumbing and car servicing the principles change little while the applications change but slowly. Joe Bloggs Crash Repairs is unlikely to be called upon to service an aeroplane or a guided weapon, nor will anyone phone South Croydon Heating and Plumbing Ltd. because their teleprinter's had a fit. Things of this sort seem to be happening to us all the time however! Complicated, sometimes gimmicky, TV sets, projection models, colour TV cameras, VCRs in six different formats, half of them already obsolete, and, coming shortly, synthesized tuning and video discs. How can even the most conscientious technician keep up to date on all these fronts?

If he's good at his job, well equipped and not too rushed, he'll be able to put right most of the things that come his way. But what happens when he comes up against an obscure intermittent fault in a piece of equipment he only half understands and has never seen before? How does he cope when he doesn't know what standard of performance to expect from a new piece of equipment and is confronted by a demanding customer who's just parted with several hundred pounds? What's he to do with a nice little TV camera which gives a sickly green and grey picture when the poorly designed manual (which he conscientiously ordered as soon as he saw the thing on the shop shelves) hasn't a word of circuit description and calls for heaven knows what in the way of test jigs and equipment?

Some would say that the answer to these very real problems lies in training courses run by manufacturers or maybe the local technical college. The value of such things is not nowadays, we submit, as great as it once was. Human nature being what it is (and we speak from experience in these matters), the details so carefully collated and mentally digested tend to get blurred and forgotten unless one is dealing with the piece of equipment concerned constantly. Five or ten years ago, servicing courses on the Thorn 3000 say or the ITT hybrids were worth their weight in gold, but with the high reliability of the latest sets and their diverse circuitry you all too often find yourself confronted on a service assignment with a product you've never seen before – inside, anyway. Be you the most able engineer in the world, this isn't good for the ego or for customer relations!

So we have to resort more and more often to the manufacturer's Technical Department. Roving technical liaison engineers seem to be getting rarer these days, and their job is to inform and advise – not repair equipment! Now irate customers and problems with showroom displays cannot await the exchange of learned correspondence between the dealer's engineer and the setmaker's technical office, so the telephone is often the only resort available – if you see a glowing telephone line alongside the A21, it'll probably be because a new type of VCR is on the shelves and going wrong on approval in customers' homes, and the manufacturer has yet to get around to distributing service manuals!

When we phone, how greatly our reception varies! How different are the oracles of Sydenham and Shropshire, of Slough and Gloucester! Having circumnavigated the obstacle course presented by separate telephone numbers for different departments, and often had to swallow the considerable financial pill of waiting many minutes on the phone before getting through to the hapless adviser in the technical office, we find a tremendous variation in the service offered – varying from the excellent to the abysmal. We don't mean to knock these gents, most of whom are friendly and helpful souls doing a thankless task, sometimes in very difficult circumstances. It can't be denied that some of their enquiries come from people who shouldn't be dabbling with this sort of equipment at all, and we know from our own experience with the query service that diagnosis from afar is often difficult even with all the necessary information to hand, and sometimes impossible without.

Even so, how many manufacturers and agents can put their hands on their hearts and claim that their technical liaison department does justice to the clever wizards who design the circuits, specify the components and arrange for the lot to be put together? We can think of one, maybe two, amongst the two score or so of setmakers with whom we deal. Some liaison people we reach on the telephone have never worked on the equipment upon which they advise us; some seem to try to get by on clouds of theory; some just frankly admit that they are not conversant with this or that product, and cheerfully suggest we forward it to them for attention – sometimes a totally impractical course.

Is it too much to expect a circuit description in a service manual covering a new and complex product? How many hours, and hard earned pounds, have been spent on endless dialling of engaged numbers in south and south east London, and in waiting for the technical office to become free? No doubt readers will have comments to make and views to express on this difficult subject – maybe even one of the denizens of a technical office would care to give his viewpoint. Over to you!

# Teletopics

## SINCLAIR'S POCKET TV


Sinclair Research Ltd. have announced a £5 million, four-year capital investment programme to put into full-scale production their Model 2700 pocket radio/TV set with its innovatory flat-screen c.r.t. Production of both the tube and the set itself is being subcontracted to the Timex Corporation in Dundee. The manufacturing agreement reached with Timex comes at the end of a five-year, £1 million plus, partly NRDC-backed research and development programme during which the technical aspects of the tube were sorted out and the techniques and methods for automating its production established – the latter include a new method of vacuum forming glassware. The new investment, funded by Sinclair Research with in addition a regional development grant and £1.5 million from the Scottish Economic Planning Department, will result in a tube production capacity of a million a year by the end of phase one in 1982.

The tube's principles have been described in these pages before – see pages 653-4 of the October 1979 issue. In its production form the tube is even smaller than previously envisaged – approximately  $4 \times 2 \times \frac{1}{4}$  in. The set itself will be assembled alongside the tube production line and is designed to retail at around £50. We've been sceptical about mini TV sets in the past, but at this sort of price there should be a substantial market. It will be able to receive transmissions in most parts of the world, tuning as it does over the v.h.f. and u.h.f. bands, and a major USA retail chain is understood to be planning to place a substantial order during the first year of production. The set also incorporates provision for v.h.f./f.m. radio reception. It will measure about  $6 \times 4 \times 1$  in. and weigh only a few ounces.

According to Clive Sinclair, the production subcontract was awarded to Timex because of their experience in designing and making automatic production machinery and reputation for precision engineering. The decision was taken after an exhaustive appraisal of international alternatives –



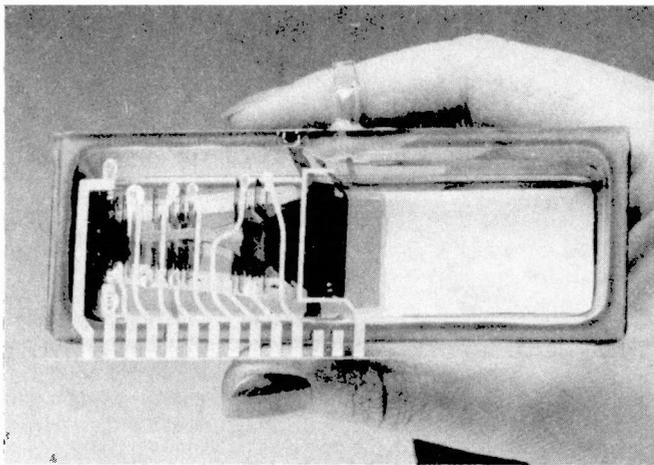The multi-standard Sinclair Microvision pocket TV has a 3in. screen and is expected to be available in 1982.



One of the Sinclair flat-screen tubes produced on the pilot production line at St. Ives, Cambridgeshire.

in particular an in-depth examination of the facilities and finance available in Hong Kong.

The flat-screen tube has its gun to one side, and in addition to vertical and horizontal deflection requires a further deflection field to bend the beam through 90°. The beam strikes the phosphor screen from the same side that the tube is viewed. This latter feature means that the tube is inherently brighter than a conventional one, and Sinclair have in mind its modification for use in projection systems, where tubes have to be driven hard to obtain a bright projected image. Since the tube is flat, the rear side of the screen can be connected directly to a heatsink. Sinclair foresee a three-tube projection set with a 50in. diagonal colour display and the optics and electronics fitting into a unit the size of a shoe box.

## HITACHI VIDEO DISC PLAYER

Hitachi have decided to adopt the RCA CED video disc system and are understood to have started the manufacture of players at their Yokohama plant. The player is to be launched in the US during the summer, at an anticipated price of around £220. The aim is to produce some 10,000 a month initially.

## TATUNG SIGN DECCA DEAL

As forecast last month, the Taiwanese firm Tatung is to buy from Racal the Decca radio and television interests. Tatung will be paying £1.1 million for the Decca TV plant at Bridgnorth, which will give them a foothold within the EEC. TV production at Bridgnorth has been running at 80,000 sets a year recently: Tatung intend to expand this, using advanced technology, and have guaranteed for a year the jobs of 500 of the present 850 labour force. A subsidiary, Tatung (UK) Ltd., will be set up to run the operation, which includes the development laboratory at Bradford, from June 1st.

## STORM IN THE VIDEO TEACUP

The intense rivalry between the VHS and Betamax VCR systems seems to have been the cause of the recent brief storm in the video teacup. It all started with a news item in Japan's financial daily to the effect that Sanyo were to start producing VHS VCRs. Now as you all know, Sanyo are one of the main manufacturers of Betamax machines, so some bright press officer jumped to a conclusion and promptly issued a press release suggesting that Sanyo were about to move from the Betamax to the VHS camp. The facts behind the story turn out to be that the US firm Sears

Roebuck, which is the world's largest retailing organisation and obtains VCRs from Sanyo, had insisted on VHS machines. As a result, Sanyo arranged for the production by its subsidiary firm Tokyo Sanyo of VHS machines specifically for Sears Roebuck, with the stipulation that the Sanyo brand name should not be used on the machines. Sanyo are planning to produce 1.8 million Betamax machines in 1982, and to double production in the following year. Planned production of VHS machines by Tokyo Sanyo is for 200,000 units in 1982, again doubling in 1983.

Meanwhile Cap Ten Industries are planning to introduce in the UK this summer a Betamax VCR, with an advanced specification and at a competitive price, produced by NEC. Sony themselves are planning to produce 1.8 million Betamax machines this year, with production increasing to 2.4 million in 1982. Sony's chairman Akio Morita comments that the boom in VCRs is creating extra demand for colour sets, as a result of which Sony are planning to produce 2.7 million CTVs this year.

### NEW SETS

An extremely versatile set has been introduced by JVC – the CX610GB 6in. v.h.f./u.h.f. portable colour receiver/monitor. It's capable of PAL or SECAM reception, and will operate on any of the following systems – PAL B, G or I, and SECAM B, G, D, K or KI, i.e. the CCIR (W. European) and OIRT (E. European) standards. The colour decoder automatically switches to the correct system, and the corresponding sound i.f. can then be selected. The set's versatility is further enhanced by the four-way power supply option – a.c. mains, ordinary batteries, a 12V car battery or its own rechargeable battery pack. Video sockets enable it to be used with a camera or for off-air recording. The suggested price, including VAT, is £259.

Pye have added a 20in. model to their range of teletext-equipped colour sets. The 3237 comes complete with infra-red remote control and uses the basic Philips KT3 90° chassis.

### TELETEXT/VIEWDATA DELIVERIES

Official estimates for teletext and viewdata receiver and adaptor deliveries have recently been made available for the first time. The figures are as follows:

Year	Teletext/ Prestel				
	Teletext sets	Teletext adaptors	Prestel sets	Prestel adaptors	Prestel sets
1977	2-3,000	—	—	—	—
1978	7,000	—	—	—	—
1979	28,000	2,000	750	—	2,000
1980	75,000	5,000	3,500	1,000	3,500

Of the Prestel registrations in 1979, 1,800 were business and 200 domestic, the figures for 1980 being 7,200 and 800 respectively.

The Department of Industry recently held a conference with the aim of gingering things up a bit.

### SANYO'S NEW COLOUR TUBE

The basic principles of the beam-indexing colour c.r.t. are far from new: a tri-colour phosphor screen, with vertical RGB phosphor stripes, is used with a single electron gun, the RGB inputs to modulate the single beam being switched in RGB sequence. The problems concern the high-frequency switching and the need to synchronise this with the scanning of the beam (this is where the indexing bit comes in). The great advantage is the power saving, with only one gun and no shadowmask to intercept the beam.

The problems are probably not so great using modern circuit techniques, and Sanyo have announced the successful development of a beam-indexing tube which they claim reduces the power consumption by 50 per cent compared with an equivalent shadowmask tube. Sanyo intend to use the tube initially in a 6in. colour set which will have a power consumption of only 12W.

### ANOTHER VIDEO "MOVIE CAMERA"

The next great leap forward in the video world is going to be the portable combined camera/VCR unit. And as usual various non-compatible prototypes are beginning to surface. We've described the Sony Cam-Corder in some detail previously, and also mentioned the Hitachi Mag Camera. The latest version of this species to be announced is Matsushita's "micro video system", which has a two-hour capability using a cassette smaller than a standard audio one. For the record, the sizes of the cassettes used in these prototype systems are as follows:

Sony 56 × 35 × 13mm (recording time 20 minutes)  
Hitachi 112 × 67 × 13.6mm (recording time two hours)  
Matsushita 94 × 63 × 14mm (recording time two hours).

Whilst the Sony and Hitachi units use solid-state image sensors, the Matsushita unit employs a newly developed ½in. colour pickup tube called the Cosvicon. In conjunction with some specially developed i.c.s (several featuring large-scale integration) this has enabled the power consumption to be reduced to only 5W. Matsushita intend to develop the mass production technology required for the system whilst co-operating with other companies in establishing a standard format for this type of equipment. We shall see!

### STATION OPENINGS

The following relay stations are now in operation:  
Cwmaman (Mid-Glamorgan) BBC Wales ch. 39, Welsh fourth programme ch. 42, BBC-2 ch. 45, HTV Wales ch. 49.  
Lampeter (Dyfed) Welsh fourth programme ch. 54, BBC Wales ch. 58, HTV Wales ch. 61, BBC-2 ch. 64.  
Ludlow (Shropshire) BBC-1 ch. 39, ATV ch. 42, BBC-2 ch. 45, TV4 ch. 49.  
Matlock (Derbyshire) BBC-1 ch. 21, ATV ch. 24, BBC-2 ch. 27, TV4 ch. 31.  
St. Bees (Cumbria) TV4 ch. 54, BBC-1 ch. 58, Border Television ch. 61, BBC-2 ch. 64.

All the above transmissions are vertically polarised.

### TRADE WORRIES

A substantial increase in Japanese CTV exports to the EEC during 1980 is expected to be revealed when the final figures are announced – up from some 500,000 sets in 1979 to over 700,000. A particularly large increase has been registered in exports to W. Germany – these rose by almost 100 per cent. Amongst the firms feeling the pinch is W. Germany's largest setmaker Grundig, which plans to close down four consumer electronics factories this year – following two years in which another four plants were closed and 8,000 of the 40,000 staff were laid off.

On the monochrome receiver side the European Commission is holding an investigation into the alleged dumping of South Korean sets, following a complaint from the European Association of Consumer Electronics Manufacturers. According to the Association, some 814,000 12 and 14in. S. Korean monochrome portables were dumped on the European market last year at prices 21

per cent below cost. Exports in 1979 totalled 122,000 sets, S. Korea's share of the EEC market rising from five per cent to 22 per cent between 1979-80.

## TV4

Mr. Ellis Griffiths has been appointed Chief Engineer of the new Channel Four Television Company. His responsibilities will include the design and installation of the network centre for the Channel, and the standards and engineering operations when programmes commence in November 1982. Mr. Griffiths was previously Technical Operations Manager at Thames Television's Euston Studios.

The IBA reports progress with engineering work on the

Welsh fourth programme network – over 50 relay transmitters have already been installed, but cannot be brought into operation until the six main high-power stations come on air in November 1982.

## MORE VIDEO FROM HITACHI

Hitachi have followed up the launch of their VT8000 VCR (see *Teletopics* February) with a further model offering additional features. The new VT8500 VCR has a suggested price of £665 including VAT. Added to the range of colour cameras is the VKC770, a version of the VKC750 with an electronic viewfinder. The suggested price is £517.50 including VAT. For a review of this camera under its Hitachi Denshi label see our January issue.

# Letters

## BALANCING LINE OUTPUT TRANSISTORS

Reading the problem (*Service Bureau*, February) about balancing the line output transistors in the Rank Z718 chassis prompts me to write regarding a recent experience with one of these sets. The symptoms we had were much the same, i.e. to start with the overload circuit shutting down. The two line output transistors were replaced, but on trying to balance them we couldn't obtain a lower reading than 10V across 5R6. We discussed the matter with Rank, who told us that the line output transistors must be a matched pair. These were obtained and fitted, and we then managed to get a near zero reading. The voltage would shoot up however and then drop back to zero. Now John Coombes, writing in your February 1980 issue, reported a similar fault which was found to be due to intermittent shorting turns in the line driver transformer 5T1. Replacing this gave us a zero balance reading with no further trouble – it comes complete with all the associated components (diode, resistors and capacitors) incidentally.

F. H. Stansby,  
Hornchurch, Essex.

## THAT TANDBERG TROUBLE

I was most interested to read Derek Snelling's account (February issue, page 206) of the disastrous Tandberg CTV2-2 breakdown, having had a similar problem some five or six years ago. The set was brought in by one of the field engineers, who delightedly told me that "I was going to love this one". The tube neck was broken, and the whole scanning assembly could be moved about, accompanied by a "scrunching" sound.

Investigation revealed signs of severe arcing where the tube neck had fractured. Unfortunately the customer had not taken out the four year tube guarantee and the set was only about 18 months old – and had not been bought from us. A new tube was fitted, and the rest of the troubleshooting commenced. The self-oscillating chopper power unit had failed, and needed several replacement devices, including the chopper transistor itself. The tripler and the line output transistor had also failed. When all these obvious victims had been replaced, the set was powered up using a variac. The mains supply was gently increased, but the e.h.t. seemed to get very lively at a remarkably low mains voltage. A test showed that it had already risen to 27kV.

This led to replacement of the flyback tuning capacitor, the e.h.t. then being restored to normal. As in Derek's receiver however we next discovered that several of the convergence output transistors had failed, and the EW modulator had also blown. Replacing these items cleared all the faults – it was then "only" a matter of setting everything up properly.

I had already explained to the customer that the situation was pretty disastrous, but they were still shaken by the final extent of what had happened. It ended up with a white-faced husband whose wife was crying on my shoulder. I finally gave them cups of tea and six months' interest-free credit to allow three equal payments in settlement – all because of one capacitor!

Keith Cummins,  
Southampton.

## UNUSUAL DEGAUSSING CIRCUIT

Malcolm Burrell's comment about fuse blowing due to short-circuit diodes in the degaussing circuit (see *Fun and Games*, March) might puzzle some readers. The fact is that the degaussing circuit used in the Electrohome monitor (see Fig. 1) is a bit unusual. The two back-to-back diodes D911/2 allow a.c. through to the coils at switch on and turn off when the posistor R901 has reached its high-resistance state, thus isolating the coils. The diodes can cause mains

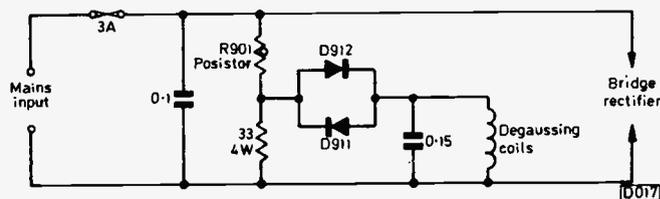


Fig. 1: Degaussing circuit used in the Electrohome monitor.

fuse blowing – I found this out when searching around in a dark pub corner and running out of fuses – but why this should happen is hard to see. Any ideas?

A. Mole,  
London, W4.

## STOLEN VIDEO

On January 26th the following equipment was stolen from a car in Soho:

- 1 Sony DXC1640 colour camera, serial no. 50020.
- 1 Sony VO4800 portable recorder, serial no. 10061.
- 1 Sony power supply unit, serial no. 10077.
- 3 BP60 batteries.

All this equipment was engraved N.F.S. in prominent

# Oscilloscopes

Look  
new  
book

## How to use them How they work

Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models is available. But which is the right scope for a particular application? Which features are essential, which not so important? What techniques will get the best out of the instrument?

Ian Hickman, experienced in both professional and hobbyist electronics, has written this book to help all oscilloscope users – and potential users. After introducing basic principles for readers new to the subject, he explains in detail the features of typical simple and advanced real-time oscilloscopes, plus accessories such as probes and cameras. He advises on how to choose

and operate scopes, and how to avoid common pitfalls; he also describes special-purpose instruments, from small portable scopes to storage scopes and spectrum and logic analysers. Finally, to give readers a better understanding of how oscilloscopes work, he explains the principles of the cathode-ray tube and basic scope circuitry.

Illustrated with many photographs and two-colour diagrams, the book will appeal to everyone who needs to know about oscilloscopes, from the school student to the graduate, from the hobbyist to the technician.

216 x 138mm · 128 pages · Illustrated  
0 408 00472 X · £3.45 · Paperback

Available from your local bookseller or in case of difficulty from the Publisher.

ORDER NOW. Cut out this coupon and return it to Patricia Davies at the address below.

Please send me \_\_\_\_\_ copy/ies of **Oscilloscopes** (Hickman)  
0 408 00472 X @ £3.45 Paperback

I enclose cheque/PO for £ \_\_\_\_\_ in total payment

From \_\_\_\_\_

Address \_\_\_\_\_

(TV 4/81)

## Newnes Technical Books

Borough Green, Sevenoaks, Kent TN15 8PH

### APOLLO

#### HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Just phone for a quotation. Delivery Manchester area £3.50. Two year guarantee. Fitting while you wait £20 extra.

18"	A47 – 342x343x	£37.00
19"	A49 – 120x/192x	£37.00
20"	A51 – 220x/110x	£38.00
22"	A56 – 120x/123x/140x	£38.00
25"	A63 – 120x	£39.00
26"	A66 – 120xA67 – 120x/140x	£39.00

These tubes replace many Toshiba types.

Callers welcome, please phone first.


061 799 0854

Reg Office:

43 Clarke Cres, Little Hulton,  
Nr. Manchester M28 6XM.
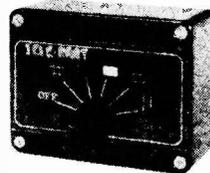
## TELEPART

13 WORCESTER ST.,  
WOLVERHAMPTON,  
WV2 4LJ  
Tel: (0902) 773122  
Telex: 336810



### Telepart Pattern Generator

- Exceptionally light and durable
- Pocket size for outside service
- PP3 battery power source
- Five different test patterns for colour and mono TV
- Cross hatch grid
- White raster
- Horizontals
- Verticles
- Dot matrix

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)



### Telepart Colour Bar Generator

- Exceptionally light & durable
- Compact 13x17.5x5.5 cms
- Battery powered for mobility
- Cross hatch grid
- White raster
- Grey scale
- Colour bars
- Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.)

### Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

## CELTEL

26" G8...£25    22" 3500...£45  
DECCAS all sizes ... £25  
26" 3500...£12    PYE 205 ... £18  
WHITE MURPHY ... £15

Also available: TELEFUNKEN, SABA, JVC, etc.

ALL PLUS VAT @ 15%

WARNERS MILL, SOUTH ST., BRAINTREE, ESSEX (0376) 43685  
UNIT 5A, KEMPS SHIPYARD, QUAYSIDE ROAD  
BITTNER, SOUTHAMPTON 0703 331899

## Manufacturers Surplus Components FIT THE RIGHT PART

20 assorted Tantalum capacitors  
£1.20

300 mixed  $\frac{1}{2}$  and  $\frac{1}{4}$  watt resistors £1.95  
150 mixed 1 and 2 watt resistors £1.95  
300 mixed Capacitors, improved pack, most types £3.95  
100 mixed Electrolytics £2.95  
300 mixed Printed Circuit mounting Components for various TVs, resistors, caps etc £1.95  
300 printed circuit Resistors  $\frac{1}{2}$  to 4 watt £1.45  
100 High Wattage TV resistors, Wirewound etc. £2.95  
100 mixed miniature Ceramic and Plate Caps £1.50  
100 mixed polystyrene capacitors £2.20  
25 mixed Pots and Presets £1.20  
25 mixed TV Presets £1.00  
20 assorted TV VDRs and Thermistors £1.20  
10 assorted TV Convergence Pots £1.00  
20 assorted TV knobs, includes push button, chrome, control types etc. Mostly Thorn and ITT £1.00  
10 assorted Valve Bases, B9A, ceramic, EHT, etc. £1.00  
20 assorted Sync Diodes blocks for various TVs £1.00  
10 Spark Gaps £1.00  
20 assorted Zener Diodes 1 watt and 400MW £1.50  
100 Mixed Diodes, includes zener, power, bridge, varicap, germanium, silicon etc. All full spec. £4.95  
12 assorted I.C. Sockets £1.00  
20 Gen. purp. Germ. Diodes £1.00

**GRUNDIG**  
UHF/VHF Varicap Tuners.  
Fit 1500 GB, 3010 GB.  
Brand new £12.50

### PUSH BUTTON KNOBS

Type 1 15mm long x 11mm diam. Brushed Aluminium Finish  
10 for £1

Type 2 10mm long x 10mm diam. Chrome Finish 10 for £1

Both types fit standard  $3\frac{1}{2}$ mm square shafts as used on most music centres etc. 100 for £7  
1000 for £50

### SPECIAL SCOOP PURCHASE OF MULLARD CAPACITORS

Spillages, Floor Sweepings, Cosmetic Imperfects etc. All mixed up. Factory clearance.

#### UNREPEATABLE OFFER

Polyester C280's (Liquorice Allsorts) 100 mixed £2. 1000 mixed £12  
Miniature Electrolytics (Blue Type) 150 mixed £2. 1000 mixed £10

**De Luxe Fibre Glass Printed Circuit Etching kits**  
Includes 150 sq. ins. copper clad F/G. board, 1 lb ferric chloride, 1 etch resist pen, "Tweezers", Abrasive cleaner. Etch tray plus instructions.  
Special Price £5.95.

1 lb F.E. C1 To mil. spec. £2.25  
150 sq. in. Single sided board £2.00  
150 sq. in. Double sided board £3.00

33V Varicap Tuner Regulators.  
Equivalent to TAA550, SN76550, ZTK33 etc. Only 8 for £1

THORN 1600 Dropper 18 + 320 + 70 + 390 60p each. 3 for £1.50  
"THORN 3,500 Transductor" Fits most sets. £1.50 each 3 for £4

**Why Buy Expensive Triplers!**  
Repair your old 5 and 3 sticks at a Fraction of the Cost.  
10 Replacement Rectifier Sticks (Thorn). £1.00

Ultrasonic 40 kHz remote control receiver with 20" Coax lead and Phono Plug. Thorn: £1.20 each 3 for £3

**Hardware Pack**  
Includes BA nuts and bolts, nylon, posidrive, self-tapping "P" clips, cable markers, clamps, fuse holders etc. £1 per lb.  
ITT CTV. SCAN COILS complete with conv. yoke. Mullard Type CVC 5-9 £3.95

### TRANSISTOR MOUNTING KITS

TO3 (BU208 etc) 8 for 60p  
TO220 (TIP 33 etc) 10 for 60p  
TO77 (BD131 etc) 12 for 60p

Pack of each £1.50  
All include Mica insulators and relevant washers.

TRANSISTORS 90° fit G8 etc. Price: £1.50 each. 3 for £4.00.  
THORN 900, 950 Triplers. £1 each. 3 for £2.50.

### I.C. SOCKETS

DIL 14 pin 10 for £1  
Quil 16 pin. 12 for £1  
DH to Quil 16 pin 10 for £1

### CASSETTE MAINS LEAD

7' lead with Fig. 8 Plug. 75p each, 4 for £2

### ITT BLUE LATERAL

Assembly (single knob type) 60p  
3 for £1.50

ITT Spun Aluminium Control Knobs.  $\frac{3}{4}$ " diam.  $\frac{1}{4}$ " shaft 4 for £1

### SAVE THAT TUBE.

Fit our C.R.T. Isolating Transformer. Ideal for HTR./Cath. Shorts. 200-220-240 inputs. 750-900 MA outputs with thermal cutout. Made for Thorn 4000 C.T.V. but works O.K. on other sets. £3.00 each 2 for £5.00

Pye 697 Line + Power Panels. Damaged with some components missing but ideal for spares. Good value - £2.20 each 3 for £6

### SPECIAL OFFER

Thyristors, SS106. Like BT106. 60p each 3 for £1.50  
10 for £4.00

3A 200V Diodes 8 for £1.00  
2A 800V Metal Diodes 12 for £1.00  
3A 1000V Diodes 6 for £1.00

### FOCUS UNITS

Rotary type. As fitted in "Thorn 8500", solid state G.E.C. and lots of other sets. £1.20 each 3 for £3.

### VIDEO GAME BOARDS

All new but incomplete. Hundreds of useful modern components. C.M.O.'s I.C.'s, Transistors, Diodes, Sockets, Switches, etc.  
5 Assorted Boards £2.50.

L.O.P.T. for R.B.M. 823A Chassis £4.50 each 3 for £10

EHT Lead with Anode CAP (CTV), suitable for Split Diode sets. 1 metre long. 60p each. 3 for £1.50.

Degaussing V.D.R.'s (Red, Orange, Black), fit most sets. 5 for £1.

Bush CTV 28 Quadrupler Remo type Q25B. equiv. to ITT. TU25 30K. with mounting brackets. £3 each. 2 for £5

GEC single standard, hybrid chassis. convergence panel. Brand new, complete with plugs and leads £2.50

G.E.C. S/S Hybrid Focus Assembly with lead and VDR Rod £2.00

### SPECIAL OFFER

GEC transistor rotary tuners with slow drive. AE Skt. and leads 2010 Series £1.95 each 3 for £5

Line linearity coils, 50p each, 3 for £1  
4 Knobs black with chrome caps to fit ITT, Thorn, GEC and most small diam. shafts 60p per set  
ITT CVC5 power panel. New but five resistors never fitted £1.50  
4 P/B UHF TUNER suitable for VC200 and some Pye and Philips sets. 3 hole fixing. £2.75

Pye mono mains droppers with fusible link.  
147 $\Omega$  + 260 $\Omega$  50p 3 for £1.00  
69 $\Omega$  + 161 $\Omega$  50p 3 for £1.00

R2010B £1 each

### Portable TV EHT Sticks

"Siemens TV 18 KV". Fit most portables 50p each 3 for £1.00  
Pye 18" CT200 V. Cap P/B Assembly with leads and plug £4.95

Miniature Mains Transformers 4.5V-0-4.5V at 250Ma 90p each. 3 for £2.50

BD131 4 for £1. BD132 4 for £1  
2N3055H 60p each 3 for £1.50  
FOCUS RODS (2 $\frac{1}{2}$ " V.D.R.) £1.20 each 3 for £3

BB105B U.H.F. Varicap Diodes 20 for £1

### Telescopic Aerials

Chrome on Brass, 9 Section. 21" Extended. Plugs in to any 3.5mm skt. Ideal for portables. £1.00 each, 3 for £2.50.

### UHF MODULATOR VIDEO IN - UHF OUT

Calibrated to Channel 36. Housed in metal box 2 $\frac{1}{2}$ " x 2" x  $\frac{1}{2}$ " Complete with 9" coaxial lead and plug. With connection data. only £2.50 each, 3 for £6

Thorn 1500 Bias Caps. 160uF 25v 20 for £1.50

"TAIYO" 6MHZ Ceramic Sound Filters. 50p each. 3 for £1.

ZENERS 400MW. 2.7V, 4.3V, 4.7, 5.6, 6.2V, 6.8, 7.5, 27V, 30V  
10 of one type 80p. 10 of each type £6.00  
10 of each type £5.50  
10 of one type £1.00  
10 of each type £2.50

DIACS BR100 6 for £1.00  
GEN. PURPOSE DIODES  
IN4000 30 for £1.00 IN4003/10D2 20 for £1.00  
IN4002 25 for £1.00 IN4148 20 for £1.00  
BA158 10 for £1.00

## TRANSISTOR PACKS

Our Transistor Packs are even better than before! 100 NEW AND MARKED TRANSISTORS including BC238, ME0412, BF274, BC148, BC183L, BC338 and, or other similar types. A random analysis of these packs yielded between 98 and 106 transistors of 17 to 20 different types with an average total retail value of £14 - £16. OUR PRICE ONLY £4.95

200 transistors as above but including BD131, 2N3055, AC12B, BFY50, BC154, BF394, BC184L, etc.

ONLY £9.95

Send 60p P. & P. on all above items; send Cheque or P.O. with order to:-

### SENTINEL SUPPLY DEPT. TV

149a Brookmill Rd., Deptford, London SE8

(Mail Order address only. Callers by appointment)  
Trade enquiries for quantity welcome.

Surplus stocks purchased for cash.

**NEW**  
4-433 C.T.V. Crystals  
Long Leads £1.00 each  
3 for £2.50

Miniature Push to make Switches.  
Red knob 6 for £1  
Sub. Min. S.P.C.O. Slide Switches 12 for £1

2-2k fusible, vertical mounting  
Screen Feed resistors 9 watt 8 for £1.00  
0.47 $\Omega$   $\frac{1}{2}$ watt emitter resistors 40 for £1.00  
10 $\mu$ F 400V modern Small

Type 8 for £1.00  
4 $\mu$ F 350V 10 for £1.00  
0.002 $\mu$ F 2000V Axial leads 10 for £1.00  
1000 $\mu$ F 35V Radial 5 for £1.00  
4.7 $\mu$ F 63V 20 for £1.00  
1000 $\mu$ F 16V 10 for £1.00  
330 $\mu$ F 25v 10 for £1.00  
470 $\mu$ F 25V 10 for £1.00  
4,500 $\mu$ F 35V cans 80p each  
2,200 $\mu$ F 40V Cans 60p; 3 for £1.50  
4,700 $\mu$ F 40V Cans 80p; 3 for £2.00  
RBM/ITT. Capacitor 220uf 400v £1.00 each, 3 for £2.50.

BF338 10 for £1.50  
Avoid Lethal Shocks  
Buy our specially designed EHT Probe, removes high voltage charges from tubes, caps, etc. Heavily insulated with lead and earth connector 60p each  
B9A P.C. valve bases 20 for £1.00  
EY87/DY87 EHT bases 10 for £1.00  
C.T.V. Tube bases 5 for £1.00

20mm Antisurge Fuses. 630Ma 800Ma, 1A, 1.25A, 1.6A, 2A, 2.5A 3-15A 12 of ONE Type £1  
Pack of Each £7  
60p 3 for £1.50  
TBA 800Q 10 for £1.50  
TH3 thermistors 10 for £1.50  
Miniature "Terry" clips ideal for screwdrivers and small tools etc. 40 for £1.00  
Convergence Pots with knobs. 5 $\Omega$ , 10 $\Omega$ , 20 $\Omega$ , 30 $\Omega$ , 50 $\Omega$ , 100 $\Omega$ , 200 $\Omega$ , 1K. 8 of 1 type £1.00, 8 of each £7

Decca Bradford Tuners. 5 button (4 push, one tune) £3.50 each, 5 for £15. Also fit Indesit mono TV.

EHT Cable 30p per metre  
10 metres £2.50  
3 for £1.00

Anti Corona Caps 3 for £1.00  
Miniature Level/Batt. Meters as fitted to many cassette recorders 90p  
Miniature Reed Switches 20 for £1.00. 100 for £2.95.  
Rediffusion/Doric Mk 13 5 stick Triplers can be modified for other sets £1.00

"THORN 9000 Tripler complete." On Panel. £4.95 3 for £12.50.

positions. As we're not in a financial position to replace this equipment, we would appreciate hearing from any readers to whose notice it might come.

Peter Wilson, Senior Video Engineer,  
The National Film School,  
Beaconsfield Film Studios, Station Road,  
Beaconsfield, Bucks. HP9 1LG.  
Telephone Beaconsfield 71234.

### TRANSISTOR REPLACEMENTS

I see from the February *Service Bureau* that another reader recently had the identical fault to one I experienced – bottom foldover on the Hitachi Model CNP190. Transistor trouble was suspected, but one problem is that the 2SA, 2SB, 2SC series transistors can no longer be obtained. Marshalls suggested an AF124 as a replacement for the 2SA15V field driver transistor, and this cured the fault. As it's a four-legged device however the screen lead had to be cut off and the other leads carefully sorted out. Towers gives the OC44N and 2N2614 as alternatives, and this would have avoided the complication. Incidentally, I first

tried replacing the 2SC936 field output transistor with a BDX32: it lasted just one day, so the original device was replaced. All is now well.

J. H. Brooks,  
Walworth, London.

### CHRISTIAN VIDEO

In the past eighteen months or so there has been a great increase in the number of VCRs rented or sold. Before long they will no doubt be considered necessities rather than luxuries. Most of the video tapes now on sale are secular in content, the Churches still not being alert to the possibilities that VCRs present.

I would be glad to hear from any of your readers who are interested in a Christian video tape ministry, and who perhaps have their own cameras. Video technology now offers great possibilities for propagating the Christian Gospel.

Michael Byrne, Director, Christian Video Outreach,  
Credenhill Court,  
Credenhill, Herefordshire, HR4 7DL.



© IPC MAGAZINES LTD 1976

# TELEVISION

## READERS PCB SERVICE

**All boards are epoxy glassfibre and are supplied ready drilled and roller-tinned.**

**Any correspondence concerning this service must be addressed to READERS' PCB SERVICES LTD, and not to the Editorial offices.**

Issue	Project	Ref. no.	Price
November 1976	Ultrasonic Remote Control	D007/D008	£3.85 per set
March 1977	Teletext Decoder Power Supply	D022	£3.75
May 1977	Teletext Decoder Input Logic	D011	£12.50
June 1977	Wideband Signal Injector	D031	£1.00
June 1977	Teletext Decoder Memory	D012	£10.50
July/Aug 1977	Teletext Decoder Display	D013	£11.00
September 1977	Teletext Decoder Switch Board	D021	£1.75
April/May 1978	CRT Rejuvenator	D046	£3.00
October 1978	Colour Receiver PSU Board	D052	£4.00
January 1979	Colour Receiver Signals Board	D053	£10.75
February 1979	Commander-8 Remote Control System	D054/5	£6.00 per set
March 1979	Colour Receiver Timebase Board	D049	£17.13
July 1979	Colour Pattern Generator	D062	£14.50
		D063	£9.15
September 1979	Teletext Decoder Options Board	D064	£8.50
August 1979	Teletext Decoder New Mother Board	D065	£6.00
August 1979	Simple Sync Pulse Generator	D067	£4.00
September 1979	New Teletext Signal Panel	11331	£8.00
October 1979	Teletext Keyboard	D057	£3.50
October 1979	Teletext Interface Board	D058	£5.00
November 1979	Colour Receiver Remote Control	D066	£5.00
January 1980	Remote Control Preamplifier	D061	£3.75
February 1980	Teletext/Remote Control Interface	D070	£9.50
February 1980	LED Channel Display	D071	£4.00
March 1980	Improved Sound Channel	D072	£3.25
May 1980	Monochrome Portable Signals Board	D074	£6.25
June 1980	Monochrome Portable Timebase Board	D075	£7.75
July 1980	Monochrome Portable CRT Base Board	D076	£1.00
Sept/Oct 1980	New CTV Signals Panel	D077	£9.50
January 1981	Small-screen Monitor Board	D078	£8.50
December 1980	Video Camera Pulse Generator Board	D079	£4.50
December 1980	Video Camera Video/Field Timebase Board	D080	£5.50
January 1981	Video Camera Power Supply Board	D082	£2.00
January 1981	Video Camera Line Timebase/H.T. Board	D083	£4.00
Feb/March 1981	Video Mixer	D086	£4.50

**To:- Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts.**

Please supply p.c.b(s) as indicated below:


Issue	Project	Ref.	Price

Prices include VAT and post and packing. Remittance with order please.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Post Code \_\_\_\_\_

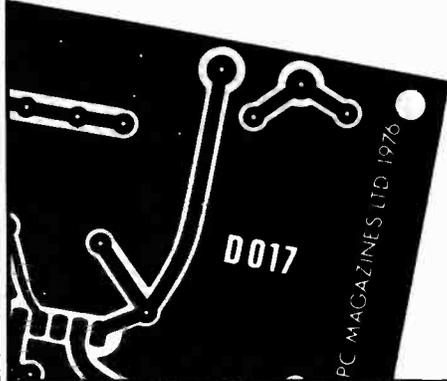

© IPC MAGAZINES LTD 1976

D017

# Dealing with Intermittent Faults

**Derek Snelling**

AS TV sets get more reliable, various intermittent faults are coming to account for an increased proportion of service calls. The first problem with this type of fault is that it's never present when you call at the customer's house. The set can be taken back to the workshop of course, but even then location of the fault can be difficult – while it's always best to carry out the repair in the customer's home if possible.

## **Defining the Fault**

The first thing to do is to try to ascertain from the customer the exact nature of the fault. This requires a certain amount of detective work – the customer's initial description of the fault should not be accepted at face value. I've had the description "no picture" given in cases of field collapse, loss of vision signal, no signals at all, no e.h.t., and loss of line hold for example, which is understandable coming from someone not familiar with the workings of a TV set. Another misleading description I had recently was "poor focus" in a case that turned out to be an intermittent convergence problem.

To overcome this difficulty, try to simulate the fault while the customer watches. By adjusting the height, width, line and field hold and set h.t./e.h.t. controls, removing the aerial connection, and switching off one or more colours as necessary, you should be able to get a reasonable idea of the part of the set in which the fault lies, e.g. the decoder, line output stage, etc.

## **Fault-finding Procedures**

Once you've located the area where the fault lies, the next step is to try to find the cause of the problem. Try tapping the area with the handle of a screwdriver – this should reveal the presence of dry-joints or cracks in the printed tracks. Successively lighter taps should then enable you to narrow the area down to just a few components, when resoldering all the connections in the area and if necessary bridging cracks in the print with wire should eliminate the problem. If the set is an old one, particular attention should be paid to areas subject to heat, such as valvebases, where cracks are common.

If tapping or flexing the panel has no effect, try heating it with a hairdryer or cooling it using a freezer aerosol. This will reveal any components that are sensitive to temperature change – semiconductor devices and resistors are particularly prone to this type of fault. The cure is then simply a matter of replacing the sensitive component. Take care though, as some circuits are sensitive to excessive temperature change when in fact working correctly.

These techniques should sort out a good 75 per cent of intermittent faults. For the rest, check all relevant controls and plugs and sockets for intermittency, and carefully examine the components in the suspect area, changing any discoloured resistors or leaking capacitors. Change any polystyrene capacitors, since these are notorious, also any high-value resistors. If this fails, change any likely semiconductor devices or valves.

In older sets, check for carbonised parts of the board

subject to heat. A carbonised area can be conductive, giving rise to tracking. The only cure for this sort of thing is to drill or cut away the affected area – until you get back to unburnt board – replacing any copper tracks with wire (remember to note where the tracks went before cutting!).

## **Intermittent Fuse Blowing**

We are left with perhaps the most difficult type of fault – intermittent fuse blowing. You visit a dead set, change the fuse and it works perfectly for days or even weeks before the fuse again fails. You're obviously not going to see this fault happen, so some detective work is again necessary.

First examine the fuse. If it's blackened, there was a virtual short-circuit across it at the moment of failure. If the wire has simply parted, the cause could be a small overload over a long period or a gradually increasing overload. Secondly, ask the customer whether anything happened when the fuse blew – was there perhaps a bang or crack from the back of the set, indicating arcing, did the picture go first, did it close in slowly from the sides, etc.? This may enable you to narrow down the possibilities.

If you have a blackened fuse and thus an intermittent short-circuit there are certain likely causes – a valve or the c.r.t. could be sparking (try tapping them), the insulation of some wiring could be faulty, or a transformer could be breaking down. Resistors can be discounted, as they don't go short-circuit intermittently. Similarly capacitors don't normally go short-circuit intermittently, though this is not unknown – mains filter capacitors are notorious for misbehaviour of one sort or another. If a semiconductor device goes short-circuit, again this is usually a permanent rather than an intermittent condition, though they can be susceptible to thermal runaway which can account for the other type of fuse failure.

Two other possibilities to consider on certain types of set are (1) does failure of the line oscillator result in an overloaded line output stage, and (2) is there a crowbar trip which when it fires puts a short across the mains fuse? In the former case, failure of the line oscillator while the set is running will result in the fuse suddenly blowing. Suspects here are capacitors in PCF802 sinewave line oscillator circuits. In the latter case it's necessary to check up on the conditions that cause the crowbar to operate and investigate further.

If the fuse is not blackened, check the setting of the h.t. and e.h.t. supplies – the receiver may appear to work normally with these set incorrectly, but the excessive current may be sufficient to cause the fuse to fail after a time.

Should the line oscillator fail to start, or not start quickly enough, the line output stage current may increase until the fuse blows. This depends on the type of circuit employed – line output transistors remain off in the absence of drive, while line output valves switch on.

Finally, check for any modifications introduced to prevent spurious fuse blowing – this applies particularly to the more modern types of power supply.

These notes should have covered most causes of intermittent faults. Happy hunting! ■

# CCTV Arrow Generator

Andrew Parr, B.Sc., C.Eng., M.I.E.E.

THE unit to be described was designed so that a controllable marker could be inserted on a closed-circuit TV picture. The marker consists of a movable arrow which can be rotated to point in any of four directions – up, down, left or right. The arrow can be displayed in black, white or flashing between black and white at about 1Hz. A cheaper option is also described – a movable (but obviously non-rotatable) spot which can also be displayed in black, white or flashing between the two.

The unit is for connection between the camera and the monitor, and the controls are simple. A joystick positions the arrow on the screen, a four position switch selects the arrow direction, a further four-position mode switch (video, black, white, flash) completing the controls.

## Basic Principles

Drawing an arrow on a CCTV picture involves producing suitable bright-up (or black-out) signals for mixing with the video. The arrow consists of the dot matrix shown in Fig. 1, i.e. 7 × 7 dots which can be moved to anywhere on the screen by altering times T1 and T2. Arrow

rotation is something we'll come back to later (also an option for an arrow with a solid head).

The circuit thus falls naturally into two parts. First a video board which extracts the sync pulses from the incoming video signal and adds the arrow dots to the signal. Secondly the logic which produces the dots for the video board.

The logic required to produce a non-rotatable arrow is shown in simplified form in Fig. 2. The line and field sync pulse inputs come from the video board and are used to trigger the two monostables whose cycles are controlled by the joystick position control. These monostables position the arrow on the screen therefore. They gate the outputs from the two oscillators, inhibiting the outputs until an arrow is called for. The oscillator outputs thus start at the position on each line and field at which the arrow is required.

The oscillator outputs are fed to two four-bit counters. The first three bits from each counter are fed to a decoding matrix to produce the arrow bright-up at the correct times. If we call the horizontal counter X and the vertical counter Y, Fig. 1 shows us that we need bright-up pulses at X4/Y0, X5/Y1, X6/Y2, X6/Y4, X5/Y5, X4/Y6 and Y3/X0-7. The decode matrix looks for these counter states and produces the necessary bright-up pulses. The oscillator frequency thus determines the size of the arrow.

Once started, the counters run to the end of the line or field. They are then reset by the next sync pulse. This means that the decode matrix would produce a set of arrows which would fill the lower right-hand portion of the screen. To ensure that only one arrow is displayed, two flip-flops are used to inhibit the output from the decoding matrix. They are reset at the start of each line/field by the sync pulses, and switch over when the corresponding counter reaches a count of 8. The inhibit flip-flops thus gate the output from the decode matrix, ensuring that only one arrow per field is displayed.

The circuit described so far displays only a right-pointing arrow. To get arrows that point in other directions modifications are required. The first stage is to reverse the arrow, thus giving left- or right-facing arrows, then to add the up/down options.

If the least significant bits of counter 1 are inverted, the counter will appear to count down from 7 to 0. The decode matrix will then produce a left-facing arrow. To obtain left/right selection we must be able to switch the inversion of the counter's output. This can be done using the NEV gate – see Fig. 3(a) – whose truth table is as follows:

Input A	Input B	Output
0	0	0
0	1	1
1	0	1
1	1	0

It will be seen that with 0 at the A input the output is the same as at the B input, while with 1 at input A the output is the inverse of input B. The circuit shown in Fig. 2 is thus modified as shown in Fig. 3(b), SW1 enabling us to select whether the pulses fed to the decode matrix count up or

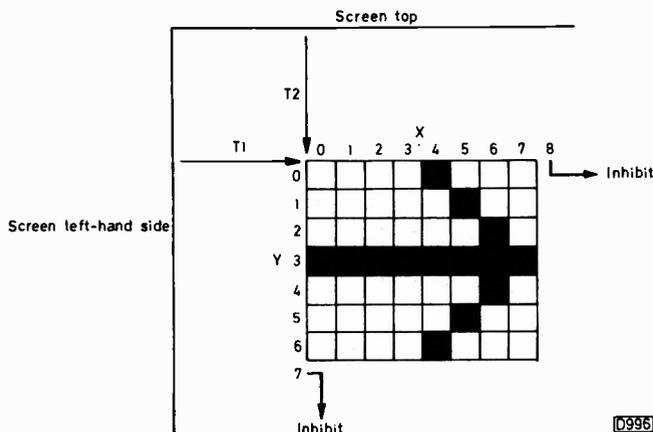


Fig. 1: Arrow format.

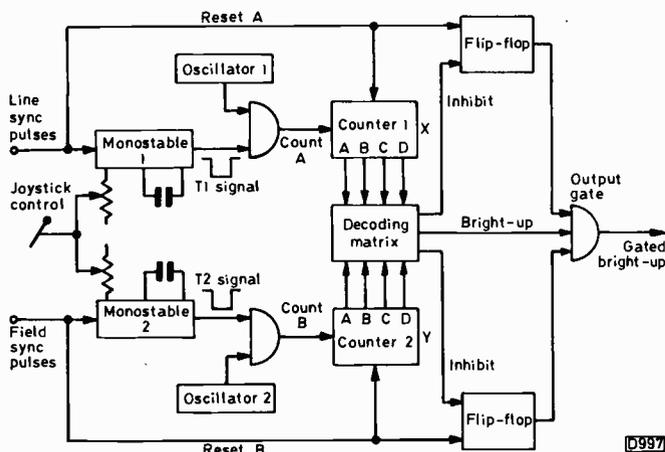


Fig. 2: Simplified diagram showing the logic required to produce a right-pointing arrow.


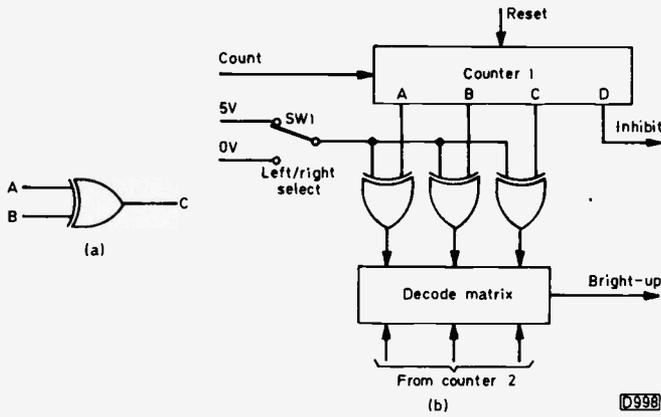


Fig. 3 (above): (a) NEV gate symbol. (b) Modification to the basic system to give left/right pointing arrows.

Fig. 4 (right): Principle of four-direction arrow selection.

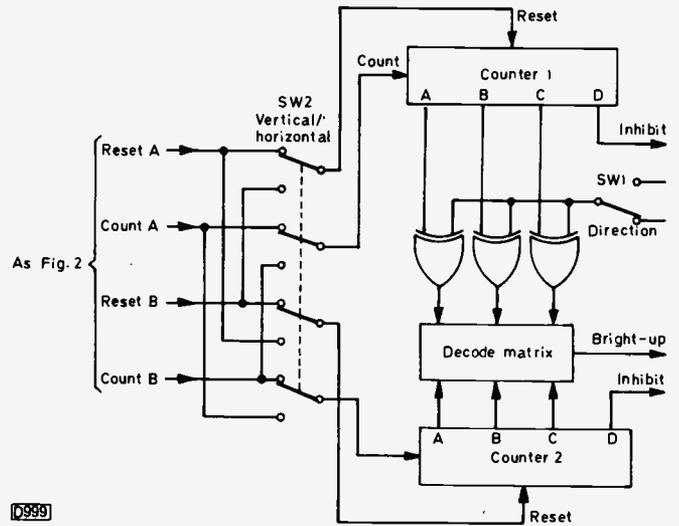

0999

in Fig. 3(b), the other bank for the changeover switches shown in Fig. 4.

### Practical Logic Circuit

The practical circuit (Fig. 5) closely follows the principles outlined above. Line and field sync pulses from the video board (see later) trigger monostables IC1a/b to obtain the line and field delays. Front panel control RV1 thus sets the horizontal position and RV2 the vertical position of the arrow. IC2 contains two monostables which are used as the horizontal oscillator, IC3 similarly providing the vertical oscillator. RV3 and RV4 determine the oscillator frequencies. In the prototype unit these were brought out as

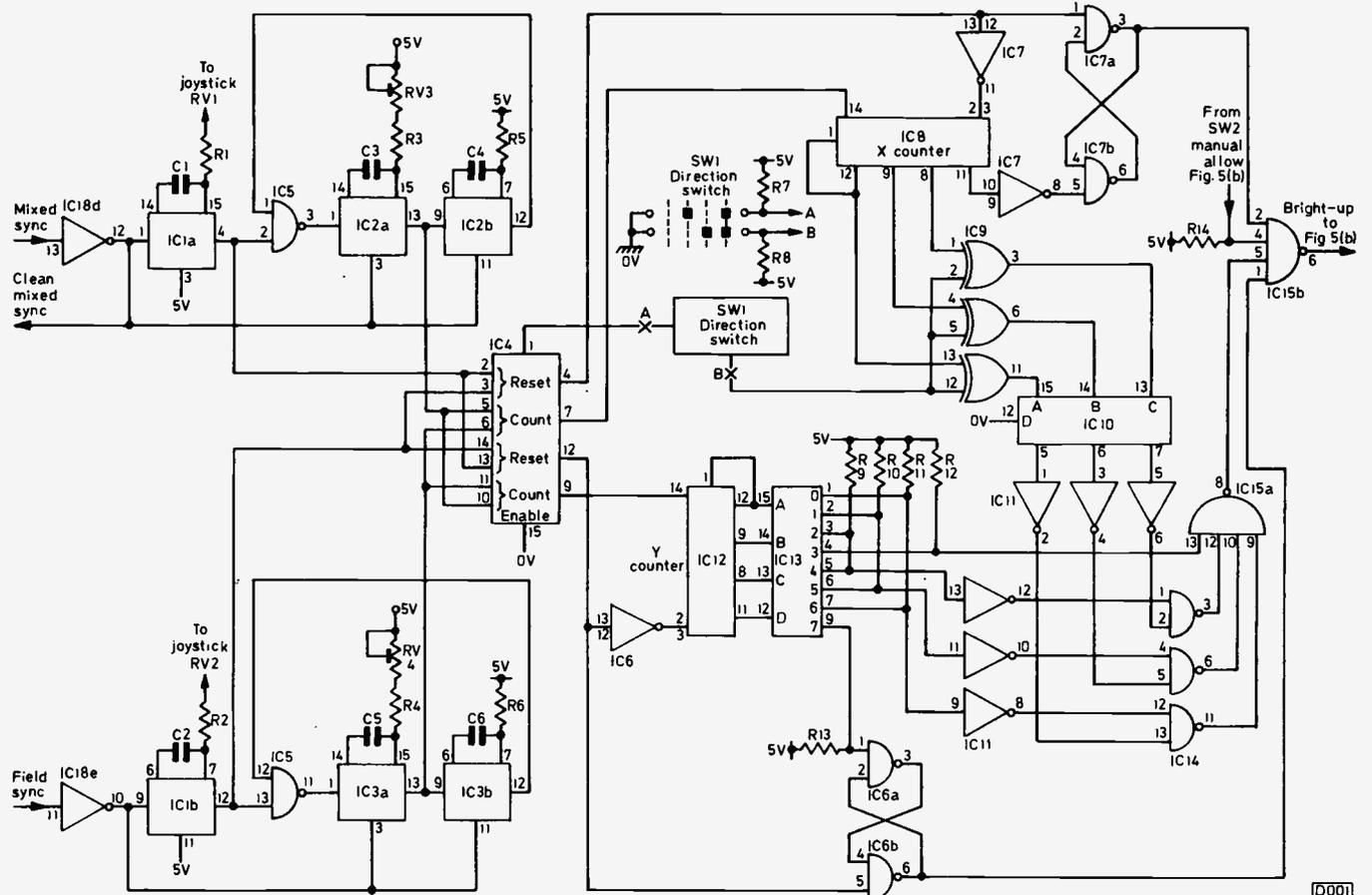


Fig. 5(a): Arrow logic.

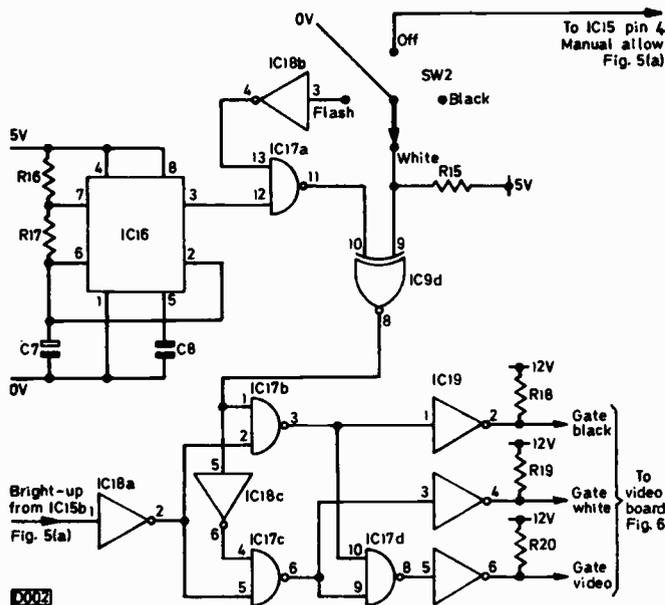


Fig. 5(b): Arrow logic continued.

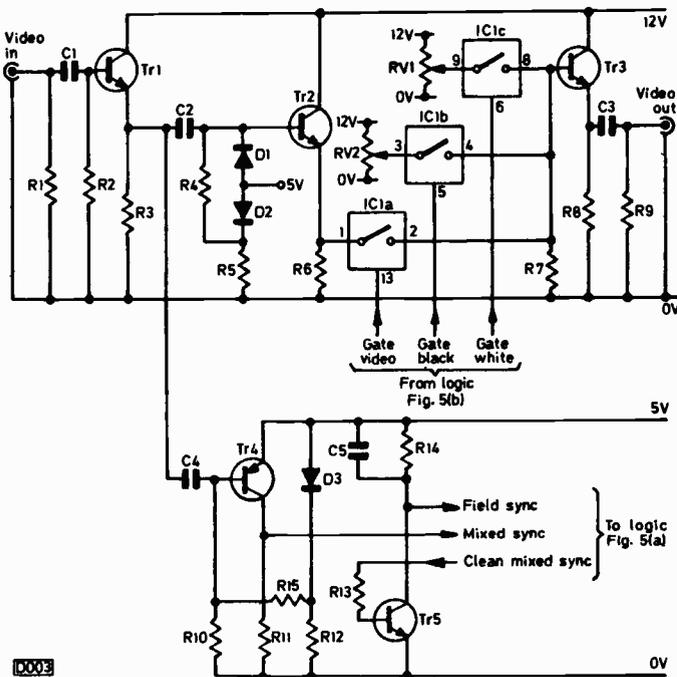


Fig. 6: Circuitry on the video board.

a ganged front panel control labelled "arrow size", but this feature was found to be of little practical use. Presets are recommended therefore. IC5 gates the oscillators.

Vertical/horizontal switching is provided by the 74157 multiplexer IC4. It contains four changeover switches which are controlled by pin 1. For example, pin 4 can be connected to pin 2 or pin 3 depending on the signal at pin 1. Obviously pin 1 is connected to the horizontal/vertical bank on SW1.

The reset and count pulses from IC4 go to the X and Y counters (IC8 and IC12) and the inhibit flip-flops (IC7a/b and IC6a/b). The Y counter is decoded by the 7445 binary to decimal decoder IC13. From Fig. 1 it will be seen that the arrow is symmetrical about a Y count of three. The open-collector outputs on the 7445 allow outputs 0-6, 1-5 and 2-4 to be linked directly.

The X counter output goes to the NEV gates in IC9 as outlined in Fig. 3. The outputs are then decoded by IC10.

Examination of Fig. 1 shows that only counts of 4, 5 and 6 are needed.

The decoding is done by IC11, IC14 and IC15a using brute force methods. The circuit simply tests for each of the conditions given earlier, with IC15a as an output OR gate. The output from IC15a is a 1 whenever an arrow dot is required.

The inhibit flip-flops IC6 and IC7 are reset by the respective reset pulses, and are set by the counter states. The Y counter decoded output 7 is used to set IC6, the X counter most significant bit being used to set IC7. The decoded X counter output cannot be used since IC9 reverses the count direction.

The two inhibit outputs and the manual allow signal are gated at IC15b with the arrow data to produce a low-going signal when an arrow dot is required.

The arrow's "colour" is determined by SW2. Its first position is "arrow off" and goes to IC15b pin 4 to inhibit the arrow dot data. The positions "black" and "white" gate the data via IC17b or c - see Fig. 5(b). If "flash" is selected, oscillator IC16 inverts the data at IC9d to switch between black and white at approximately 1Hz.

### Video Circuit

The video board has three switches which gate the video output. The first two select black and white levels and are controlled by the outputs from IC17b and c. The third gates the video from the camera, and is operated via IC17d when no arrow dots are required.

The circuit of the video board is shown in Fig. 6. This is fairly conventional and straightforward. The video signal is terminated by R1 and buffered by TR1. The output of TR1 is d.c. restored by D1/D2 and fed to switch IC1a via TR2. The two remaining switches, IC1b and c, are fed from potentiometers RV1 and RV2 which set the black and white levels. The three switches are selected by signals from the logic described above. Transistor TR3 provides a low-impedance output at 75Ω.

### Sync Circuit

Transistors TR4 and TR5 extract the sync pulses. TR4 is normally biased off by D3, and is turned on by the negative sync pulses. These mixed sync pulses are squared by the Schmitt trigger IC18d and are used as line sync pulses to trigger monostable IC1a.

The squared mixed sync pulses also turn on TR5, whose output is integrated by C5 and R14. The resulting output

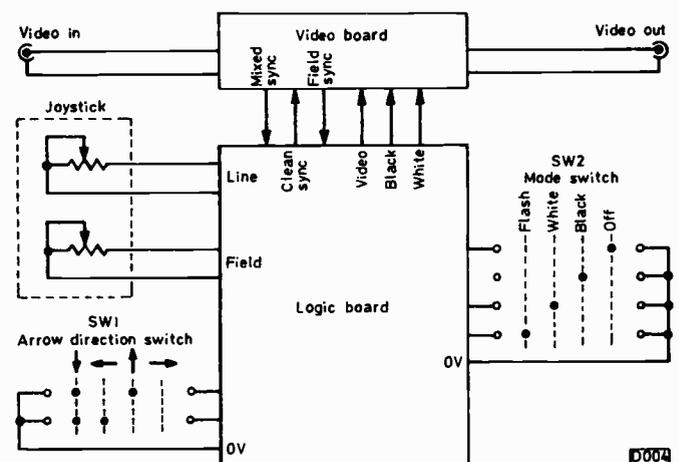


Fig. 7: Interconnections between the video and logic boards.

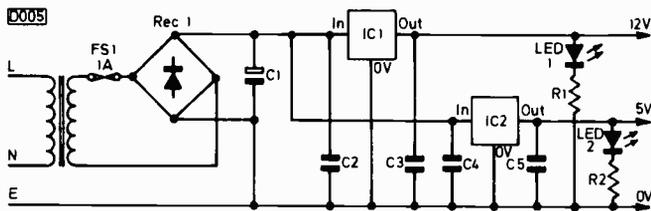


Fig. 8: Power supply circuit.

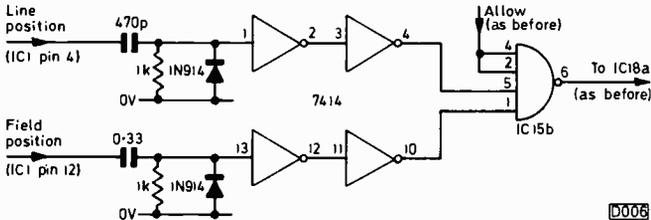


Fig. 9: Modified circuitry giving a movable spot.

consists of field sync pulses which are squared by IC18e and used to trigger monostable IC1b.

### Construction and Setting Up

The prototype was built in two parts – with one board for the TTL logic and another for the video circuitry. A general purpose i.c. board was used for the logic, and standard 0.1in. strip board for the video. No layouts are given, since the wiring is largely pin-to-pin and straightforward. Care should be taken to keep the wiring to the monostables IC1-IC3 as short as possible to prevent faulty triggering. Each i.c. should have an 0.01 $\mu$ F capacitor connected across its supply pins. Fig. 7 shows the board interconnections.

The most fiddly part of the setting up is the mechanical positioning of RV1 and RV2 in the joystick controls. These should be set so that with the joystick at the top left position

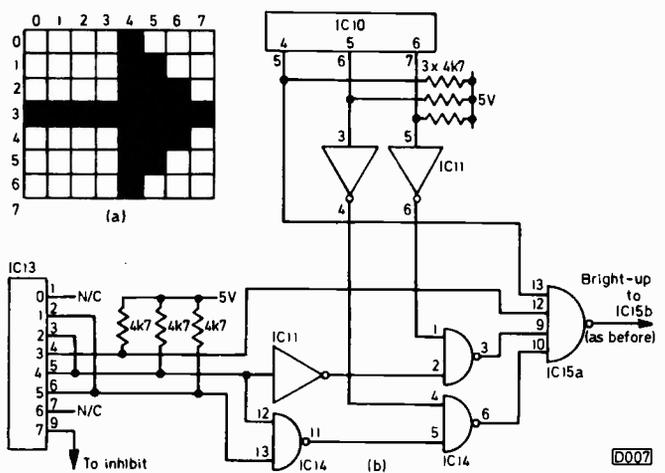


Fig. 10: Decoding circuit for an arrow with a closed head.

RV1 and RV2 are at minimum resistance. In the control used by the author this involved manipulating small coupling pieces with Allen screws arranged in highly inaccessible places.

With RV1 and RV2 set, RV3 and RV4 should be set to mid-range and the system connected between a camera and monitor. "White arrow" and "black arrow" should be selected and the video board presets adjusted to give the required levels. Note that maladjustment of the controls can cause loss of picture sync. RV3 and RV4 can now be set for the required arrow size. A small size is preferable so that the eye can't resolve the dots.

Move the joystick from top left and observe its range. Because of component tolerances, it's unlikely that the arrow will reach the opposite screen boundaries when the joystick reaches the end of its travel. C1 and C2 should therefore be trimmed by adding small value capacitors until the desired travel is obtained. Too large a value will cause

### ★ Components list

#### Logic board

##### Resistors:

R1-15 4.7k  
R16 1k  
R17 10k

##### Capacitors:

C1 0.0022 $\mu$ F ceramic  
C2 1 $\mu$ F polyester  
C3 22pF ceramic plate  
C4 47pF ceramic plate  
C5 0.068 $\mu$ F polyester  
C6 0.033 $\mu$ F polyester  
C7 10 $\mu$ F tantalum  
C8 0.01 $\mu$ F ceramic disc

Plus 19 0.01 $\mu$ F ceramic disc decouplers, one per i.c. across the supply

R18-20 4.7k  
All  $\frac{1}{4}$ W  
RV1-2 250k lin.  
RV3-4 25k lin.

##### Semiconductors:

IC1-3 74123  
IC4 74157  
IC5-7, 14, 17 7400  
IC8, 12 7493  
IC9 7486  
IC10, 13 7445  
IC11 7404  
IC15 7420  
IC16 555  
IC18 7414  
IC19 7406

Note: IC2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12 and 13 are not required for the simple spot alternative.

#### Integrated circuit supply connections

7400, 7404, 7414, 7416, 7420 pin 14 5V, pin 7 chassis  
7445, 74123, 74157 pin 16 5V, pin 8 chassis  
7493 pin 5 5V, pin 10 chassis  
555 all connections shown  
4016 pin 14 12V, pin 7 chassis

#### Video board

##### Resistors:

R1 82 $\Omega$   
R2 4.7k  
R3 680 $\Omega$   
R4 10k  
R5 1k  
R6 680 $\Omega$   
R7 10k  
R8 330 $\Omega$   
R9 1k  
R10 1M  
R11 22k  
R12 680 $\Omega$   
R13 10k  
R14 1k  
R15 22k  
All  $\frac{1}{4}$ W  
RV1/2 5k lin.

##### Capacitors:

C1 22 $\mu$ F 25V electrolytic  
C2 1 $\mu$ F polyester  
C3 47 $\mu$ F 25V electrolytic  
C4, 5 0.1 $\mu$ F polyester

##### Semiconductors:

TR1, 2, 5 BC108 etc.  
TR3 2N3053  
TR4 BC478 etc.  
D1, 2 1N914 etc.  
D3 OA81 etc.  
IC1 4016 (CMOS)

##### Miscellaneous hardware

2-bank, 4-position rotary switch  
1-bank, 4-position rotary switch  
Mains switch  
Joystick assembly  
Video connectors  
Veroboard and case

#### Power Supply

IC1 7812 R2 470 $\Omega$   $\frac{1}{2}$ W  
IC2 7805 C1 4700 $\mu$ F 25V electrolytic  
R1 1k  $\frac{1}{2}$ W C2-5 2.2 $\mu$ F polyester

LEDs, 1A bridge rectifier,  
0-12V 1A secondary mains transformer,  
heatsinks as necessary for IC1/2.

the arrow to vanish off the screen edge and possibly reappear in ghostly form elsewhere on the screen.

The circuit requires a 12V rail for the video board and a 5V rail for the logic board. These are provided by the simple i.c. regulators shown in Fig. 8. Bolt the regulator i.c.s to the case or some other suitable heatsink.

### Variations

A cheaper alternative is to use a non-rotatable dot. This can be obtained using the circuit shown on Fig. 9. A 7414

i.c. produces small pulses at the end of the cycles of IC1a and IC1b. These are gated together at IC15 with the manual allow signal to give a low-going signal to IC18a, as before. This option is "instead of" and not "as well as" the arrow circuit. The component list shows which chips are required for the dot indicator.

The arrow shown in Fig. 1 has an open head. Some users have preferred the closed head shown in Fig. 10(a). This can be obtained by rearranging the wiring of IC11, 14, 15 to that shown in Fig. 10(b). This simply alters the operation of the decode matrix to give a closed arrow head. ■

# Servicing the Thorn 4000 Chassis

## Part 2

David Robinson

It's in the field timebase that the price for using toroidal scan coils has to be paid – the field output stage has to supply a 6A peak-to-peak output, and consumes some 40W in doing so. The NS raster correction system is unusual in that modulation of the field scan takes place at a low level, the line-frequency correction signals being passed through the field output stage. This has a certain elegance about it, but does mean that the output stage's signal handling requirements and hence the dissipation are further increased.

The modulator stage is VT401 (see Fig. 5), which acts as a bidirectional switch. When it's switched on by the line pulse applied to its base, the amplitude of the line pulse output obtained at its collector is determined by the field-frequency sawtooth waveform applied to its emitter. The main collector load is the NS pincushion amplitude control R405, which is returned to chassis. During the first half of the field scan, VT401's collector is negative with respect to its emitter – the transistor works well enough under these conditions, the only proviso being that as the emitter is being used as the collector the 5V reverse voltage rating of this junction must be observed. R404 gives a small offset to the field ramp to compensate for the fact that the red and green guns are below the tube's centre line: in this way curvature of the picture's horizontal centre line is prevented.

The pulse output produced by VT401 is not directly suitable for pincushion correction of course. Integration is required to obtain a line-frequency parabolic waveform, and this is provided by the integrator stage in thick film unit TF401, with a final variable integration by R402 and the input capacitance of the main amplifier. Much of the field timebase circuit is incorporated in two thick-film units.

TF401 also contains the field oscillator circuit (an astable multivibrator), while TF402 contains a two-transistor preamplifier followed by a complementary-symmetry driver stage. The output stage consists of another complementary-symmetry pair, VT402/3, types TCER84 and TCER83 respectively. Suitable replacement types are the RCA 2N6109 in the VT402 position and the RCA 2N5296 in the VT403 position.

Having passed the modulated line parabola through the field output stage, the remaining problem is the high inductance of the field scan coils – this makes passing line-frequency signals through them difficult due to the high-voltage drive required. The problem is solved by including the network L401/C411. C411 forms a series resonant circuit with the scan coils at line frequency, L401 being included to pass the field frequency waveform. In fact as seen by the scan coils, the pincushion correction waveform is larger than the field scan waveform.

The field timebase is generally very reliable, apart from occasional output transistor failure. A slight reduction of height as the set warms up is normal, due I suspect to the presence of the current monitoring resistor R411. Linearity is determined by fixed components: this is not entirely successful in some cases, but for the perfectionist there's space on the panel to fit a potentiometer in series with a fixed resistor in place of R417.

The flyback blanking circuitry is on the field timebase panel. This and the tube protection system (see Fig. 6) linked to the line output stage should be born in mind when investigating no raster faults.

### Convergence System

The convergence system was certainly designed with ease of setting up in mind. It's a pleasant change to have separate controls that don't interact for the top and bottom, and to have the static convergence controls so readily accessible. These are mounted, along with the dynamic convergence controls, in a plastic box with a long cableform that can be unwound to allow the box to be brought round to the front of the set.

Because of the balanced line output stage configuration, the line waveforms required can't easily be derived from the scan coils. An extra winding on the line output transformer is thus used to obtain line-frequency sawtooth waveforms of opposite polarity and also a parabolic line-frequency output. A field-frequency sawtooth is taken from across

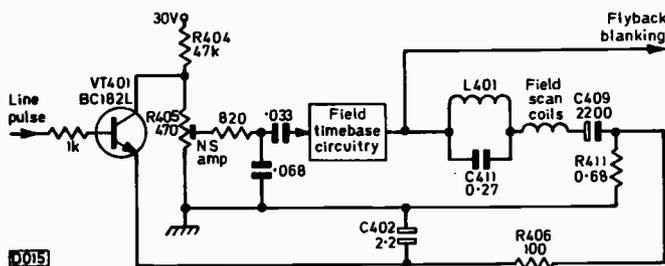


Fig. 5: Simplified circuit showing the way in which NS raster correction is carried out in the Thorn 4000 chassis. The signal developed across R411 is also used as feedback in the field timebase and is fed to the convergence circuits.

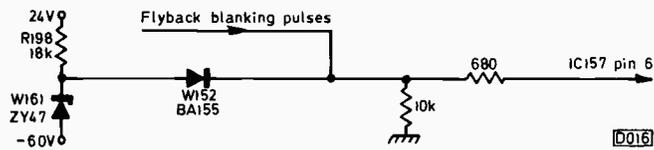


Fig. 6: Circuit used to provide tube protection in the event of line output stage failure. The anode of diode W152 is reverse biased by the network R198/W161, which is connected between 24V and -60V supplies. Since the -60V supply is obtained from the line output transformer, via a voltage doubler circuit, failure of the line output stage will remove this supply. W152 will then be forward biased via R198 and a positive voltage will appear at pin 6 of IC157, removing the c.r.t. drive signals.

R411. These waveforms are fed to the hand-held convergence unit where the field-frequency sawtooth is split into top and bottom sections by thick-film unit TF601. The various waveforms are combined and adjusted by the various controls, giving four outputs for feeding to the convergence neck unit.

The output at 33/13 can be thought of as red + green, as it passes currents equally through the red and green coils, so moving the red and green lines towards each other horizontally. The output at 33/20 is the red - green output which applies opposite currents to the red and green coils, so correcting any vertical red-green separation. The other two outputs are both for blue, one feeding the main blue coil with variable line and fixed field signals, the other feeding variable field signals to the blue static coil.

The main line controls are numbers 7, 11 and 15, feeding line parabola. The sawtooth controls 8, 12 and 16 provide small tilt corrections in either direction.

The neck unit has a matrixing circuit to separate the red and green signals from red + green and red - green, and three power amplifiers (VT501/2/3) to drive the convergence coils. Again the dissipation is rather high, this time due to the amplifiers having to handle the line and field waveforms added together, but at least the usual troublesome high-wattage potentiometers have been avoided. VT501 drives the red convergence coils, VT502 the green coils and VT503 the blue coils (radial).

With convergence faults it's important to interpret the symptoms correctly. For example, it may appear that the red-green convergence is non-existent. But on closer examination, and on trying a few of the controls, you may find that the red lines can be adjusted quite normally but the green lines stay fixed (all the red-green controls except static move the red and green beams by equal amounts). The most usual offenders are the output transistors, although thick-film units TF501 (red-green) and TF502 (blue) can also fail. The RCA 2N5298 can be used to replace the Thorn TCER82 output transistors.

Four dual-resistor units (two TF503s and two TF504s) are used in the static circuit. They often go open-circuit in one half, giving a one-way adjustment. Earlier types are encapsulated in a casing which cracks up with the heat, but this doesn't always spell failure. The edge connectors to both convergence units can become intermittent.

## Tubes

So much for the main receiver. It must be said that the quality of the tubes seems to vary considerably. Some give a nice bright picture with excellent focus right out to the corners. Others look well worn even when almost new, and good grey-scale and resolution may be unobtainable. This doesn't seem to be related to any particular make of tube, but it's a point worth bearing in mind when judging the set's

performance.

Tubes with different heater current requirements have been fitted in these sets. The 20in. A51-152X, 22in. A56-150X and 26in. A67-150X tubes require 900mA at 6.3V, and the heaters should be taken via connections 18/1 and 18/2 to the heater winding on the mains transformer. The 22in. A56-160X and 26in. A67-510X require 750mA at 6.3V and should be connected via 18/1 and 18/3 to the mains transformer heating winding. Note however that a different mains transformer was introduced for use with the low heater current tubes - part number 00D3-082-P01. The original type of transformer (part number 00D3-071-00P-001) must be used with high heater current tubes only.

## Remote Control

The type of remote control unit most likely to be encountered has a seven-button transmitter giving three analogue controls (volume, brightness and colour) plus channel stepping. The analogue settings are retained when the set is switched off by powering the memory i.c. from a rechargeable standby battery. Later versions can in addition switch the set to standby and back again by prolonged operation of the channel change button. With this version the standby battery is dispensed with, all the analogue settings being reset to mid-point at switch on instead. The earlier version can be identified by the analogue reset button on the back of the set (designed to confuse those familiar with the 3500 series!) and the later one by the standby neon on the front panel. Note that the later type will go to standby if powered up with the on-off button already depressed, but will come on if switched on at the button - thanks to the reset contacts at the back of the switch.

The usual remote control fault is incorrect or no remote control action due to drift of the remote control transmitter frequencies. The transmitter can only be set up using a frequency counter. Just pressing the input lead against the transmitter PCB without connection is usually adequate. There are two adjustments, a coil (L951/2) and a trimmer capacitor (C954): the principle is similar to trimming and padding on a radio receiver. Set the trimmer for 44.4kHz on colour down, and the coil for 33.6kHz on channel change. Repeat both adjustments until they are correct. If the transmitter is completely dead, the transducer is almost certainly faulty.

The single most troublesome component on the remote control receiver unit is the bridge rectifier W555. If it's orange in colour, I would recommend replacing it as a precaution. The symptoms are intermittent non-operation of the unit, with incorrect analogue settings (this latter can be misleading if the remote control has been dead for some time and the customer has reset the front panel controls). On the later version the set may suddenly switch to standby, then appear to operate normally for some time afterwards.

Drift of the analogue settings is sometimes caused by the ERC3064 i.c. which stores them. Before condemning this i.c. however connect a scope, preferably synchronised to the line timebase, to the preamplifier output (point 134 on the main panel). Any amount of line-frequency signal here spells trouble. Although care has been taken to use ultrasonic frequencies that lie between line-frequency harmonics, line pickup can still cause erratic remote control operation. To cure this problem, first check that the microphone lead is dressed away from the tube. Then turn down the remote sensitivity control R468, which is accessible through a grommet in the unit's back plate, in

order to reduce the line pickup consistent with maintaining adequate remote control range. To check, ensure that the signal from the transmitter limits at the maximum range to be used.

## AUSTRALIAN REPORT

As we mentioned in Part 1 last month, large numbers of these sets were assembled in Australia and S. Africa. From Australia a correspondent, Frank Klamka, reports as follows.

The chassis is very common here though there are some differences from the UK versions. Instead of touch tuning, there's a simple rotary v.h.f. tuner, while on the mains input side there's a mains isolating transformer – so the rectifier board is different. Here are some stock faults.

### No Results

Dead set, c.r.t. heater alight, chopper transistor VT301 and fuse F301 blown. This can be caused by arcing in the deflection yoke (between the line and field coils), by the h.t. rectifier W364 being short-circuit, or by an overload if the dynamic (excess current) trip is not working. The latter situation arises because with an overload such as a short-circuit line output transistor and the trip out of action the chopper has to take the full load. The trip may not work simply because someone has backed off the setting of R325, or because of out-of-tolerance components in the trip circuit. Dry-joints on the switched-mode module also cause chopper transistor failure. The chopper usually fails for no other reason however, replacement (with the fuse) restoring normal operation. To check the operation of the dynamic trip, just rotate R325. Towards one end of its travel the set should shut down, indicating that the trip is working. Correct setting must be done as described in the manual.

Set squeals for a second or a loud click is heard, then switches off. This is the trip coming into action due to an overload. The usual causes are the e.h.t. tripler, the line output or e.h.t. transistor short-circuit, C342 in the e.h.t. generator stage short-circuit, a defective field driver thick-film unit (TF402), short-circuit field output transistors, or shorted turns in the deflection yoke.

The trip may come into operation without an overload being present if the sensing resistor R363 goes high in value or open-circuit. Its value seems to be very critical.

Repeated failure of the line output transistor is caused by the flyback tuning capacitor C331 going open-circuit.

### Thick-film Units

The thick-film units used in these sets are a source of trouble, TF501 and TF502 in the active convergence circuitry on the neck module being the worst offenders. This latter fault gives all sorts of convergence problems, but it's not worth listing them since you seldom get exactly the same symptoms twice. R517 (10 $\Omega$ ), which is mounted on the print side of the convergence neck module, sometimes goes open-circuit, giving almost no red/green control (this resistor, also R516, was added in later versions using TF501 part number 00S1-039).

TF302 can be responsible for EW correction problems, with some or none of the associated controls working. TF303 is sometimes responsible for the set e.h.t. control not working, with reduced width.

On the field timebase panel TF401 can cause intermittent rolling and NS raster correction problems. TF402 can be responsible for severe scan distortion or collapse,

sometimes when hot. Partial field collapse occurs when one of the output transistors VT402/3 or R411 goes open-circuit.

TF151 on the signals board is a collection of resistors. When the 220 $\Omega$  section (between pins 2 and 3) goes open-circuit the supply to the luminance i.c. (IC155) is removed. The result is a bright raster with no video. Other sections of this unit go open-circuit, but not all that often. Most are associated with IC155, but the 12 $\Omega$  section (pins 1-2) provides the supply to IC157.

Thick-film unit faults are often intermittent, and can usually be made to come and go by moving the unit with the fingers.

### IC Troubles

Many of the i.c.s can give trouble. IC153 (SN76033N) causes no sound or distorted sound; IC101 (TCA270) causes various video problems, sometimes only when hot; IC155 (TBA396) causes no brightness or incorrect operation of the front controls – the brightness control may affect other functions for example; IC156 (SN76228) gives the no colour symptom. The TBA396 is not directly equivalent to the BRCM200 used in earlier production in position IC155.

IC157 and IC301 give the most trouble however. The former (SN76227) causes excessive blue or flyback lines. IC301 (TCEP100) can be responsible for the power supply being inoperative with no line whistle, or for a wildly fluctuating h.t. voltage with the raster coming and going – freezer will usually confirm the diagnosis in this case.

### Fault Summary

The 12V zener diode W151, which stabilises the 12V rail, can go open-circuit when hot. Various symptoms occur – from a snowy picture to horizontal pulling.

W152 in the protection circuit goes leaky, with the symptom of flyback lines on the picture.

C166 which tunes the sound detector quadrature coil can change value, with the result that the sound level drops. Some technicians simply turn up the preset volume control. This restores the sound level, though it's rather noisy with the interesting symptom of a very loud clank from the speaker when changing channels – so loud in fact that it frightened me to death when I first heard it! The reason for this is that the sound channel is responding to noise pulses regardless of frequency while not responding much to the intercarrier sound signal, which is at 5.5MHz here.

C221 (0.1 $\mu$ F), C204 (820pF) and C211 (0.047 $\mu$ F) on the chroma subpanel go leaky or short-circuit, causing no or wrong colour. They are tiny black types and can be tricky to check as the leakage may be intermittent. If in doubt, replace all three. Some panels use other types which are more reliable.

If the e.h.t. sensing resistor R352 (1M $\Omega$ ) goes open-circuit, the e.h.t. rises to around 30kV and the set e.h.t. control has no effect. Always check the value of R352 after replacing the tripler.

If the first anode supply rectifier W308 goes short-circuit the symptoms are no raster and a burning smell. Poor focus is caused by the focus control itself. Intermittent horizontal collapse is likely to be due to the yoke plugs not making proper contact, either on the main board or the line shaper board (top centre).

One of the guns producing a hazy picture is usually due to a heater-cathode short, with the result that the colour concerned is smeared. ■

# The Shooting of Sam Magrew

*Les Lawry-Johns*

HE was a funny sort of fellow. Sort of round, if you know what I mean – five foot tall, five foot wide and five foot deep, with a face proclaiming that the Lord had not been too generous when dishing out the intelligence quota. He had to screw up his watery blue eyes to protect them from the smoke that forever issued from the fag that stuck out of his mouth – it was there the whole time he spoke, which he did incessantly while never really saying anything. He probably kept it there whilst eating as well. I vaguely recognised him as a labourer for a local builder, which perhaps explains why the local pub keeps falling to pieces.

Anyway, he came into the shop one morning, talking before he even got through the door and expecting me to understand exactly what he meant though I'd heard only the half of it. I can't possibly record his exact words, only the gist of it.

Apparently his old TV had finally given up the ghost and had been dispatched to the graveyard. As a replacement, his sister had given him a "new" Bush set which had gone wrong a couple of years previously and had been stored in her loft. He would like it got going again. No, he couldn't bring it in as he didn't have a car. And he'd like it done today otherwise his old mum, who was a cripple, wouldn't have anything to watch. Which is why I nipped up there to see if I could sort things out.

It was a hybrid monochrome set – A774 chassis. Its on/off switch was faulty for a start, and as it had been stored for a couple of years I thought it would be prudent to take it back to the shop. As I prepared to put it in the car, he cheered me up by telling me that I'd been the last one to repair it, and that although his sister thought I was all right her husband hadn't liked me. I thanked him for this interesting bit of information and departed, promising to return before evening so that the old girl could see the night's programmes. Before I left he shouted out that he wanted his name put on the set, because he didn't want it changed over for one that was no good.

"Magrew. Sam Magrew. Anyone round here will tell you." I drove off wishing I hadn't got involved to start with. I couldn't really spare the time away from the shop, and I had this funny feeling . . .

There were several other jobs that had to be done before I could attend to Sam's set, but when I got to it I fitted a new volume control-on/off switch and checked for any obvious shorts. Switch on and the valves lit up, but as soon as the line timebase got going the e.h.t. rectifier's heater winding on the output transformer started arcing. This wasn't surprising, in view of the fact that it had been stored. So I pondered upon the wisdom of either fitting a new transformer or simply replacing the heater winding and keeping my fingers crossed. Totting up the cost of a new transformer, plus the on/off switch etc., I came to the conclusion that the total would be no mean factor to Sam, who'd had the set given to him anyway. So out came the DY802's holder, and some e.h.t. cable in sleeving provided the winding. I knew this was a mistake, but like a fool kept

on. The e.h.t. now came on nicely, and there was good sound. But sync was nowhere in sight. The sync separator transistor is tucked away on the left centre, near the vertical strut. It proved to be open-circuit. On replacing this the picture locked and looked good. So I stuck the set in the car and nipped it back smartly.

"Fifteen quid" bawled Sam, "I could have got a new one for that." The old girl tutted in agreement. Sam pulled out a wad of tenners and fivers and peeled off the fifteen.

"I hope it ain't going to give no more trouble after all this."

I began to loose my cool. "If the set's been stored in the loft for a couple of years, I'm responsible only for what I've just done, not the rest of the bloody thing."

## *Another Visit*

Next morning Sam reappeared. "We saw the telly for just four hours, then it went off again. My mum's not very pleased I can tell you."

So we popped up and found that the line output transformer had given up the struggle. I put a new one in, with a stick rectifier, and carefully checked the drive and operating conditions, shutting my ears to the uncomplimentary conversation that was going on in the background about my abilities as a repairer of tellys. I'd intended to waive the charge on the transformer for the sake of customer relations, but as I could hear that these were already at a low ebb I cheered Sam up by asking for another tenner. This wouldn't put the balance right, but would help a bit. There was immediate uproar, and I think he said something about going to the race relations. This seemed a bit queer, but I eventually got out and beat a hasty retreat.

## *The Final Visit*

You'll never guess who turned up next morning. Hard things were said. Suitably translated, the gist of his comments were to the effect that when he'd paid through the nose for a job he expected it to have been done, not half done. "What about the pub that keeps falling to pieces" I asked? "That's nothing to do with me, I only mix the cement."

So up we went again, and I was shocked to find that the new transformer had a short between windings, as a result of which the smoothing resistor lit up like a firebar. I told him I'd take it down to the shop to check it thoroughly, but he didn't listen because he was moaning about the money he'd already spent. So I counted out the exact sum he'd paid and put it on the table. Like a flash he grabbed it.

"You had the set given to you, and now you've grabbed that you haven't paid a bean. The only looser around here is me." That was my swan-song.

"Leave the set alone" he said unnecessarily. "I'll get Dave around the corner to fix it. He'll do it in no time and won't charge either."

On leaving, I felt I'd done something wrong somewhere. I've shortened the story so as not to bore you – in fact two new line output transformers had had to be fitted, and both had shorted to earth through the windings after some five hours' use. The line drive waveform appeared to be perfectly correct.

It was probably all my fault, but Sam's attitude was less than constructive so it was possibly six of one and half a dozen of the other. If you happen to meet a Bush set with an A774 chassis and a new line output transformer with a short, be careful.

I had a dream that night. Sam Magrew was at the bar

telling everyone that Long John Lawry was a bum. As I entered through the swing doors, Sam went for his gun and I went for mine . . .

### ***It Never Rains***

After that awkward epic, we just had to have another. Nothing complicated, just a Bush colour set fitted with the A823 chassis. No field scan after working normally for a few minutes. So we checked the vertical scan balance control 6RV2 and resoldered the pegs of the pincushion correction phase coil 6L20. No trouble at all, no more field collapse. Run the set for twenty minutes or so, then await collection.

Half an hour later there was a phone call to say that the colour had gone. Back it came. Change decoder panel: still no colour. Change i.f. panel: colour restored. Attack chroma amplifier and change little round transistors, fitting better known ones. Lovely colour. Check for thirty minutes. No loss of colour, no field collapse.

Next day there was a phone call to say that there was now no sound or raster and would I call as they thought that carting the set around was having a bad effect on it . . . So off I went. Blown l.t. fuse due to the BY164 l.t. rectifier being short-circuit. Fit more manly BY225 bridge and new fuse. Sound o.k., picture o.k., colour o.k. Would I mind if they gave the set a few days' trial before popping the money in?

### ***Colour Faults***

Three Thorn colour sets (3500 chassis) appeared in rapid succession. All with colour faults that may be of interest.

The first gave a nice monochrome display, but when the colour control was turned up only blue and green were in evidence. This ruled out a good 80 per cent of the decoder circuitry, so we settled down to check the R - Y channel, from the bridge demodulator onwards. Our first suspect was the small electrolytic which couples the signal to the base of the R - Y preamplifier transistor on the video panel. This turned out to be all right however, so we moved back to the decoder panel. The filter choke L304 between the bridge and the output connection was open-circuit. Repair the choke and full colour is restored.

Feeling pleased about this quick one, we turned to the next. No colour. Check for presence of gating/blanking pulse from line output stage at 12/9. Present. Check at other side of pulse coupling resistor R351. Pulse still there. Check presence of chroma signal from i.f. panel at 12/4. Present and correct. Check for presence of colour turn-on voltage at base of chrominance amplifier transistor VT309. Nothing - there should be 17V at TP2. Check back through the circuit and find that the emitter-follower transistor VT305 is open-circuit, preventing the 4.43MHz reference signal going any place. Replace VT305. Nice colour. Another quicky! Could our luck last? No it couldn't.

The next one was a bitch. It needn't have been, since we'd had the same thing a couple of years previously. But suffering from senile decay as I am, I can never remember these things until I've spent a lot of time rediscovering them. So round and round the decoder we went, looking for the cause of the loss of colour. The basic problem was that the ident signal was missing. Think carefully about the ident stage. The 330Ω emitter resistor is decoupled by an 0.22μF electrolytic. Maybe this had dried up, killing the ident signal through negative feedback action? Bridging it seemed to restore everything to normal, but a replacement failed to make any difference. Tap the stage and the colour came back. Turn the set back upright and the colour went. Then it

dawned on me. Removing the 7.8kHz coil's can revealed a sliver of solder which had obviously fallen into it during the course of a previous line timebase repair. Just as in the case two or three years back.

Why my brilliant, retentive memory keeps failing me like this I don't know. Honey Bunney says it's all these sex books her cousin brings in for me. He has lots of technical books given to him as surplus by someone who collects them from newsagents, and scattered amongst them are these naughty books I find of some small interest. But I don't really think they cause loss of memory.

### ***No Field Scan***

A Philips colour set (G8 chassis) was a little too large for its owner to bring in, so we had to pay it a call. The fault reported was no field scan, and as this can be a little awkward at times we took a spare timebase panel with us. This was as well, since on checking the voltages around the two BD131 output transistors everything seemed to be about right. So we fitted the spare panel, then spent some time on other little jobs that needed sorting out - grey scale, convergence, etc. Having satisfied the lady of the house that the set was now in 100 per cent condition (even though the original complaint had simply been about the field collapse), we took the faulty panel and ourselves back to the shop.

On the bench, the panel was checked. The transistors and the BRY56 s.c.s. all appeared to be in order, but the field charging capacitors C4451 and C4452 were virtually open-circuit. Replacing these electrolytics and applying about 30V to the supply connections F1 and F2 proved that the panel was now working - because of the buzz from the loudspeaker of the signal tracer - but as we didn't have a G8 around we couldn't tell exactly how well the panel was performing. When one did come in, for a new line output transformer, we took the opportunity to check the panel. The height and linearity were not up to standard, and although the BD131 output transistors read all right on a meter new ones had to be fitted to restore some range to the operation of the presets.

### ***Dog Attacks Vicar***

Ben is fairly large as rough coated collies go. Placid too, as far as people are concerned. When it comes to territory and other dogs however, it's a different story. His pet hate is a black dog which comes past with its owner and marks his patch as it were. If he could get out when that dog passes there'd be an awful reckoning. The problem now is that Ben's dislike of that dog appears to have turned into a pathological hatred for all things black. For example, there's a lady who passes with a black shopping basket on wheels. This makes Ben go berserk.

Well the other Sunday morning we'd just returned from our walk and I'd slipped Ben's chain off prior to opening the door when I caught sight of the vicar toddling down the road, supported in the main by his rolled umbrella.

"Morning vicar." I'd hardly got the words out when Ben rushed straight at him, with every hair standing on end. Not a pretty sight. Ben's teeth fastened on the black umbrella, and the vicar was robbed of his support. Fortunately Ben realised his mistake at once, and looked rather sheepish even before I cuffed him round the ear. But the vicar was going round in circles trying to stay on an even keel. I tried to help, with the result that we both gyrated around a couple of times. Profuse apologies were offered and accepted. "It's your umbrella" I explained, "it's black you see."

Needless to say, Ben's been in the dog house ever since.

# VCR Clinic

Steve Beeching, T.Eng.(C.E.I.)

A couple of the older Philips VCRs have been in for repair this month. The first was an N1500 with the complaint of intermittent colour when recording, the little green light not coming on. The little green light indicates that the colour section of the receiver part of the machine is working correctly, being linked as it is to the colour-killer circuit (see Fig. 1). Now transistor TS1407, which drives the light and switches the 25V supply through to the chroma amplifier transistors TS1405/6 when a colour recording is being made, is often known to give trouble. Not this time however.

Working on colour panel 3 without the small extension board that used to be given away with the earlier machines is difficult. If I'd any sense, I'd have changed the panel for the spare one I had in stock. But that's the easy way. Instead, I checked the ident signal at the collector of the ident amplifier transistor (TP307). There should be a large, 24V peak-to-peak 7.8kHz waveform at this point. What I found was 5V, and not at 7.8kHz. The ident stage is preceded by the burst amplifier/discriminator module U1507, which was found to have chroma and 4.43MHz subcarrier inputs. So it should have had the correct output, but hadn't. The answer was obvious: change U1507. So I did this and it didn't work, i.e. the fault was still present. Perhaps the 4.43MHz reference oscillator module U1506 was faulty? Change this and the fault had cleared, but why? Job satisfaction does not come from panel swapping, even at module level. Fortunately the N1500 manual shows the circuitry inside some of the modules. A look at the U1506 module's circuit gave a distinct clue in the form of a BA102 varicap diode, which did indeed prove to be the cause of the trouble.

The second of these machines was an N1501 with another intermittent fault – random switch off. It sat on the bench for some time under test. When the fault occurred, the meter light went out but the head motor was still going. I leapt at the machine, AVO in hand, but the light then came on again. This happened two or three times, the machine sometimes unthreading. Each time the fault would clear, then return.

Various subtle techniques were used – hairdryer, freezer, flame thrower, sacrifice the cat... The problem was

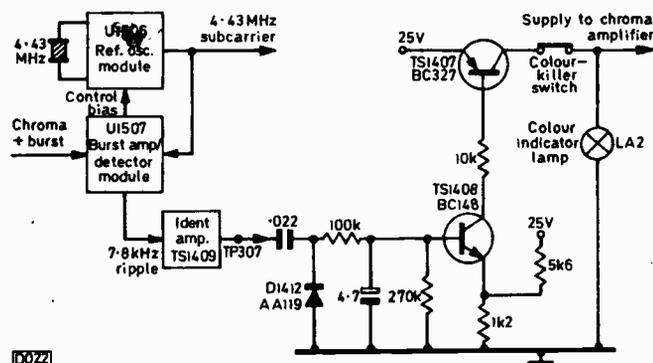


Fig. 1: Ident/colour-killer arrangement used in the Philips N1500 VCR.

eventually traced to the diodes in the 24V bridge rectifier circuit – D101/2/3/4. They are often responsible for troubles in this area. Type OF194 or BY127 may be fitted, but it's best to replace them with 1N5401s, enlarging the board holes to take the thicker leads. The light (LA1) can be extinguished should the diodes go short-circuit, blowing the 3-15A fuse Z101 which is mounted next to them.

## Great Fun?

Great fun was had this month when a large video company sent along a National Panasonic NV8600 video recorder with the complaint that it wouldn't replay in colour. I checked this and there was indeed no colour. As a further check a known good tape was tried, but the symptom was the same. Obviously a no colour fault. Clever, eh?

Some hours and a couple of colour i.c.s later I was getting nowhere. I just couldn't find anything wrong at all. The circuits were all working correctly, but something seemed to be wrong with the phasing of the replay signal, giving the impression that the replay circuits were getting it wrong. If you read your *Television* carefully, you'll know (see May 1980) that with the VHS system one head records the colour on a subcarrier at some 627kHz, the other head doing the same but with the subcarrier retarded by 90° per line (which means that one cycle is missing every four lines). This is all done in the interests of avoiding colour crosstalk between the signals on adjacent tracks. It seemed to me that the replay circuit was trying to replay the head A recording in the head B mode and vice versa. Now VHS recorder pundits will know that this is not possible unless... the video heads are fitted 180° out of phase!

The fault report did not say that the colour had gone after new heads had been fitted, and what's more the top of the machine didn't look as though it had been removed for months. But, mused I, we'd better check. Remove top, look at video heads, bang own head on wall. Fit video heads correct way around and guess what... pretty colours, and much relief. Subsequent enquiries, or rather a red hot phone call asking what class one moron had been mucking about, revealed that the machine had been sitting for some three months on the shelf and that no one knew much about it or was admitting anything. The invoice will have sorted the men from the boys.

## Parts – and Information – Awaited

A Grundig 2 × 4 plus is still awaiting final attention. A new opto-sensor was fitted in the drum unit in order to stabilise the erratic servo so that we could decide whether the audio head was faulty. Well, during a little general discussion with Grundig it turned out that they are not yet releasing certain information on mechanical alignment. This has made it difficult to align the little opto-sensor, and is not going to make life any easier when it comes to audio head replacement – but more of that next month.

Enter a 2 × 4 plus that had been dropped – but only slightly, according to the customer. Anyway, it refused to thread up, except for a short bit. I tried board substitution as a quick check, but this revealed nothing. So I called Grundig, explained the situation, and they promised to call back. As Grundig didn't sound too convincing, I decided to take another look at the mechanics underneath – you know the bits I mean, the ones you can't get any information on. I discovered a small solenoid with a bit of plastic sticking out of it. Not knowing whether it should or shouldn't be there, due to not having any information..., I gave it a wiggle and it came loose. "Oh dear" thought I (at least that's what

I thought in print). But the recorder then threaded up and worked all right (so far). It appears that this solenoid should operate a small switch mounted near it. Anyway, when Grundig rang back to say that they'd no idea what the trouble was I told them.

### More Parts Awaited

Another minor problem arose with a Philips N1700 which had very poor capstan servo lock. A discussion with the customer revealed that it worked all right with older tapes, but not when it now recorded and played back the new tape. The servo was not a million miles off lock, just very so slightly off, what you might call a "soft lock". Our immediate and astounding conclusion was that the audio/sync head was worn on the sync bit. A check with the scope confirmed this, and parts are awaited . . .

### A Batch of VHS Machines

There was a time during January when Andy and I were going through VHS machines at the rate of six a day – we'd had a batch dropped in our laps you see. The faults were

various, including "made in Holland" type drum servo motors with intermittent start characteristics or taking too much current, creating servo problems in some portable VCRs. There was the odd head replacement, along with a pause latching mechanism that wouldn't – wouldn't latch, that is. Also a play key which jumped out of latch after the machine had threaded up. It's the "clunk" from the mechanics that causes the key to jump out of the latch – you can file the key, using a needle file, and put a slope on the lip which sits on the latching bar. This way you don't have to replace the key or its assembly.

### What's Ahead?

Lastly I must say that I'm astounded, if not amazed, at the consistency and reliability of the Toshiba V5470. Someone recently referred to Toshiba as the sleeping giant of video, and I agree. New models are due for release this summer, and you might care to watch for what may come from Ferguson in disguise. In the same vein I have it on good authority (the rep was tortured) that the yet to be announced Grundig machine has so many features on it that they're at a loss to know what to develop next.

---

# The Thorn TX10 Chassis

*Eugene Trundle*

IN THE February 1980 issue we reported in detail on the Thorn TX9 chassis, mentioning amongst other things the economic climate in which it was conceived and born. It's a simple, remarkably compact chassis designed to drive 90° colour tubes of the PIL variety. In our experience the TX9 has proved to be very reliable and has fulfilled its early promise. In fact we've yet to encounter our first fault in one, though we must admit to not having all that many of them in our care. There are now 22in. TX9 sets incidentally.

The other half of Thorn's colour TV master plan consists of the TX10 chassis for driving 110° tubes. For several weeks recently one of these sets, a 22in. Ferguson Model 3765, sat in glory in my living room. I've still not quite recovered from seeing its rendering of Kate Bush in concert!

### Vital Statistics

The TX10 is designed to drive 20, 22 and 26in. tubes of the 30AX type and the similar thin-neck RCA S4 type. There's but one "tolerance" control to match the chassis to the scan yoke. As with the TX9, simplicity is the keynote of the design and the basic chassis can be used with a variety of screen sizes and consumer options – the same chassis can be removed from a basic 22in. set and without any modification fitted into a 26in. remote controlled set with teletext and tone controls. This versatility is a characteristic of the chassis, with its ability to operate with a simple or sophisticated remote control system and sweep tuning, drive an external loudspeaker, provide headphone or hi-fi outputs, incorporate bass and treble controls and accept video inputs. The latter facility embraces many things – teletext, viewdata, TV games inputs, signals from a camera and use as a data display, for example as a VDU with a home computer. To these ends a video/audio input/output socket is fitted and the video bandwidth is no less than 10MHz.

This is far beyond the 5.5MHz capability required for present TV transmissions, giving really crisp data displays. In fact we suspect that in the smaller screen sizes at least the c.r.t. phosphor "dot" size and the 625-line standard are the limiting factors determining the resolution.

The power consumption has been kept low – 70W at zero beam current. This is 28W more than the TX9, an extra 20W being required for 110° scanning plus 8W for peripheral circuitry. While the signal stages and the field timebase are for the most part similar to those used in the TX9, the power supply and line timebase are totally different and the RGB output stages are of the class AB type.

Apart from the i.f. daughter board, the chassis is to all intents and purposes a single board design. The board is in two separate sections (signals and power supply/timebases) in the final chassis assembly, but is cut into two only at a late stage of production. The two sections of the board are then mounted in a hinged steel frame, which results in a slim chassis with easy access for servicing. The metal chassis is isolated from the mains, facilitating the external connections previously mentioned, all the mains-live  try being protected by red plastic covers.

### Signal Processing

There is some complication in the TX10's front end due to the provision of sockets for sweep tuning and remote control. Otherwise the varicap tuner plus i.f. preamplifier/SAWF/TDA2540 i.f. amplifier/demodulator i.c. arrangement follows the pattern set by the TX9. The sound department is also the same, with a single TDA1035T i.c. The loudspeaker is an 8Ω type however. Let's hope that the isolated chassis doesn't result in too many liberties being taken with the external speaker wires –

or we'll need to stock up on these!

The single-chip decoder used is the TDA3560, as in later production versions of the TX9 (earlier production used the quite different  $\mu$ PC1365C). The TDA3560 does not need an external chroma delay line driver stage and operates with an 8.8MHz crystal. As a result of the latter feature, U and V reference signals with the correct phases for demodulation are obtained automatically and no adjustments in this part of the circuit are required.

The most important point about the TDA3560 however is its ability to accept and handle external video input signals. A blanking input is provided, along with the RGB input pins, so that any size or shape of black hole can be inserted in the picture and filled with characters or graphics from an external source. Alternatively the data can be superimposed on the picture, the blanking input then giving a crisper result than would be obtained by simply mixing the data and video signals within the chip. This arrangement also offers versatility in data or graphics presentation, for example the ability to surround characters with white or black edges.

The RGB output stages are also worth mentioning. They are mounted on the c.r.t. base panel to reduce stray capacitance, and consist of three three-transistor configurations – a cascode pair plus an emitter-follower to improve the h.f. performance. The result is a bandwidth of 10MHz with a low current consumption.

### Timebases

The field timebase is similar to the TX9, in that most of the circuitry is within a single i.c., a TDA1044 this time instead of a TDA1170S, but there's an external output stage to provide the additional deflection power required for 110° deflection. The output stage (see Fig. 1) looks rather basic, and at first sight quite impractical since the bases of the output transistors are strapped together – you'd expect crossover distortion from this arrangement! The key to this however is R777, which feeds the scan coils directly from the chip during the part of the field scan (about the centre) when both output transistors (TR772/3) are non-conductive. A further external transistor (TR771) boosts the supply to the output stage during the flyback period. This works as follows. During the forward scan D771 is conductive and the positive plate of C781 is at 26V. When


the flyback occurs, the flyback booster circuit in IC771 feeds a positive-going pulse to the base of the emitter-follower TR771 which switches on. The 26V developed across R786 increases the voltage on both plates of C781 by the same amount, the positive plate rising to 52V. D771 cuts off, and the supply to the external (TR772/3) and internal (within IC771) output stages is thus doubled. C775 and the network R778/C776 are included to prevent instability.

The line processor i.c. is a TDA2576. In addition to the expected sync separator, flywheel line sync and line generator circuits, this i.c. produces the sandcastle pulse required for the decoder i.c. and incorporates a clever teletext blanking circuit. The line oscillator runs at twice the normal speed, so that division of the clock frequency (31.250kHz) by 625, plus a triggering input from the field sync, enables a precisely timed teletext blanking pulse to be generated by counting to lines 21/334. This happens only in the presence, recognised by the chip, of a full-specification broadcast field sync pulse train – so you won't lose the top of your tennis game or camera picture. The teletext blanking waveform emerging from pin 1 of the chip is added to the sandcastle pulse fed to the decoder.

The TX10's line output stage is simplicity itself. Shorn of the responsibility for generating the e.h.t. and most of the other supplies (the chopper circuit provides the e.h.t.), there's simply a BU208B output transistor, a small transformer, a flyback tuning capacitor, scan-correction capacitor, the scan coils and very little else. The line output transformer in fact consists of a small choke, with a secondary winding that provides 60V and -60V pulses.

Since harmonic tuning of the line output transformer is no longer necessary (this is required only when there's an e.h.t. overwinding to complicate matters), the usual EW diode modulator circuit can be dispensed with. Instead, as in the 4000 chassis circuit described last month, an EW modulator transistor is connected in series with the line output transistor – between its emitter and chassis. The EW modulator transistor is a Darlington type (BD677) whose base bias is controlled by the width potentiometer.

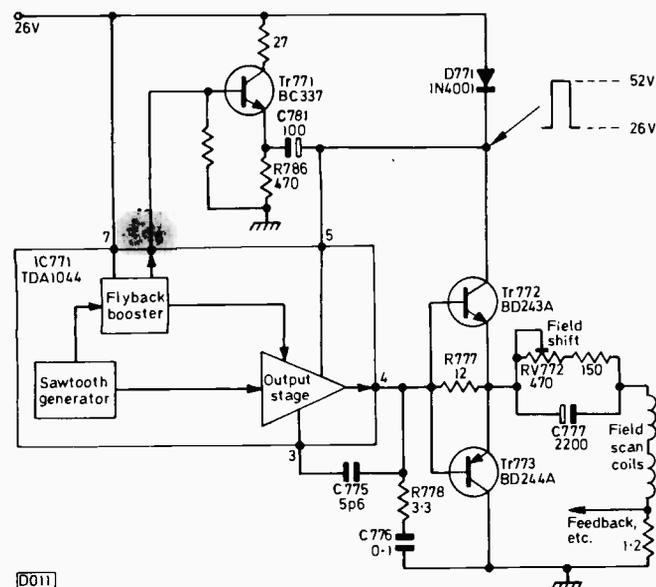Whenever the line scan and the e.h.t. are provided by different stages, there's the risk of danger to the c.r.t. screen should the line scan fail. To prevent this, the c.r.t.'s first anode supply is obtained from a rectifier which is fed from the junction of the scan coils and the scan-correction capacitor.



### Power Supply Circuit

In many ways, power supply circuit design has come round full circle with the TX10. With the power supply providing the e.h.t., an isolated chassis and a very simple line output stage, the basic arrangement is just like that used in the 1938 EMI TV set that lives in the corner of my workshop (the one that David Looser described last October)! The control operations in the TX10 are provided by a TDA2582 chip – the only chips in the EMI set occurred if you dropped the chassis on the rectifier valve and smashed it . . .

The incoming mains supply is fed to a bridge rectifier (D701) which charges its reservoir capacitor C708 to some 320V. This is applied to the collector of the BU208B chopper transistor TR701 (see Fig. 2). A small mains transformer (T702) provides a start-up supply, the supply for the chopper driver transistor, and energy for the remote control receiver (if fitted). The TDA2582 contains a 15.625kHz oscillator which is synchronised to the line oscillator. The output from this passes via a pulse-width

0011


Fig. 1: The TX10's field output stage.

modulator stage within the i.c. to the chopper driver which switches the chopper transistor on and off. The pulse-width modulator varies the mark-space ratio of the chopper transistor's drive waveform, i.e. the on and off times of the chopper, thus regulating the supplies obtained from the chopper transformer T705. These include the e.h.t. and a 150V line for the line output stage. Feedback from the 150V line to the TDA2582 controls the action of the pulse-width modulator, i.e. the regulation. The i.c. also contains slow-start and comprehensive protection circuitry – the latter monitors the chopper current (the ripple flowing via T703), the h.t. and e.h.t. voltages (the latter indirectly) and the beam current.

Apart from the first anode and start-up supplies, the chopper transformer T705 provides all the supply lines in the TX10 – the e.h.t. comes from a diode-split secondary. When the chopper transistor switches off, a "line flyback" pulse is produced. The e.h.t. and the 205V (for the RGB output stages) supplies are obtained by "flyback" rectification, the other supplies being produced by rectifying the "scan" part of the waveform in the chopper transformer in order to achieve good regulation. One of the secondary windings on the chopper transformer provides the drive to the line output transistor.

The operation of the chopper itself is new and worth going into in greater detail. Apart from the chopper transistor TR701 and transformer T705, the components involved are diodes D702/3/4, capacitors C711/2 and coil L702. When TR701 is switched on, current flows via L702 and the primary winding of T705. When TR701 is switched off, the magnetic fields established around the two windings collapse. C712 tunes the primary winding of T705 to provide the "flyback" pulse. At the end of the half cycle of oscillation, D704 conducts, damping the circuit. The action is that of an efficiency diode, C711 being charged by the linear decay of current. C711 is also charged during the chopper transistor's off period by the energy decay in L702, D703 being on during the whole of the chopper transistor's off period.

When TR701 switches on again, D704 and D703 switch off (unless the mains voltage is low, when D704 will remain on briefly). D704 will also be conductive during the slow-start period, before C711 has fully charged. D704 switches off when the charge across C711 is such that its cathode is positive with respect to its anode when TR701 switches on. Now the charge developed across C711 is proportional to the chopper transistor's on/off time, increasing when the

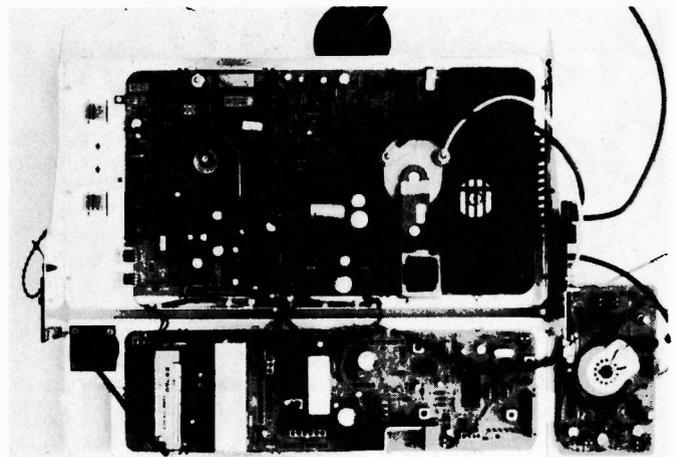

The Thorn TX10 chassis, with the signals section at the bottom in the hinged down position. The mains-live section is beneath the plastic cover shown at the top right.

transistor is on for a longer time. The result of this is that D702 conducts, feeding the surplus energy in C711 back into the supply to improve the efficiency of the circuit.

This all adds up to a very efficient power supply, with an unusually large number of energy stores – C708, C711, L702, T705 and the reservoir capacitors associated with T705's secondary windings. Mains isolation is provided by no fewer than four transformers (T702/3/4/5) plus the network R701/C701, all of which have to comply with BEAB requirements.

## Evaluation

Such is the standard of excellence amongst current TV receiver designs that it's difficult to make any really significant comparisons between the TX10 and its competitors. The picture quality is excellent – but then so is that with all current commercial designs. Like the TX9, the e.h.t. regulation, or more strictly the picture size/brightness performance, is very good – but so is everyone else's! The cabinet and much of the stand is of plastic material – as again are most contemporary sets. Our review model did not incorporate teletext or viewdata, which was a pity since this would have brought out some of the best features of the design.

As with our TX9 Thorn review set, I had to make a little internal adjustment before perfect reception was secured – this time to the a.f.c. and vision detector coils. Again I found that the customer controls were a bit fierce and non-linear. In the review set, the volume and colour controls were the main offenders – only the middle third of the volume control's track had significant effect.

On test card an excellent display was obtained, with good geometry and the teletext truly blanked. Sound was satisfactory from the necessarily small loudspeaker. For a cost-efficient (that's what we call it nowadays!) design, the performance is very acceptable and comparable with anything the opposition (even the expensive Danish and oriental opposition) can offer. The chassis layout is delightfully clean and easy to get at – none of those myriads of plug-in modules that continental setmakers seem to like. Ah, you may say, but mightn't this make field servicing more awkward, since chunks of circuitry can't be substituted? Not really, since the straightforward circuitry employed means that fault-finding should prove to be relatively simple. The engineering elegance of a neat layout lies in the simplified production procedures. In conclusion, well done Thorn – rule Britannia!

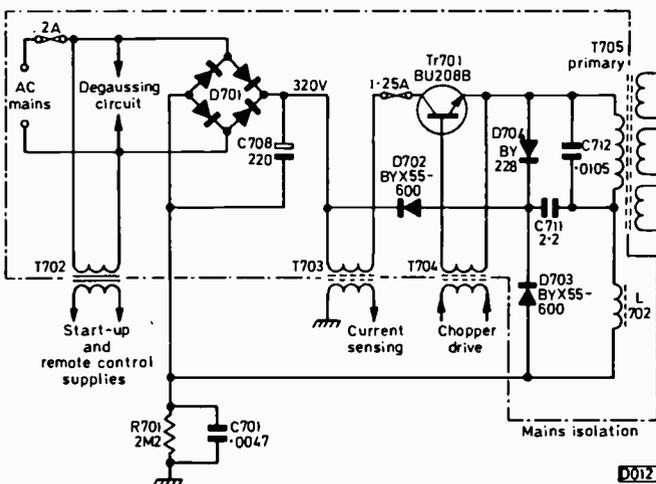


Fig. 2: Simplified circuit showing the mains input and chopper power supply arrangements. The chopper transformer T705 has a diode-split secondary to provide the e.h.t.

# Practical TV Servicing: Dealing with Strangers

S. Simon

TO THE newcomer, all TV sets are unfamiliar. So in dealing with them he must follow the advice of others, or plod through certain established servicing procedures in order to uncover the cause of the problem with which he is confronted. He then has to obtain and fit the necessary parts in order to find out whether or not the full story has been revealed. He may find that there are hidden (to him) factors that led to the breakdown.

Even the experienced engineer is not all that much better off – because it depends on what you mean by “experienced”. A chap may have vast experience of Thorn sets say, and be able to rattle off all the stock faults on these with scarcely a moment’s hesitation. But confront him with a strange set, a Philips G11 say, and he’ll have to pause a while. If the trouble’s not too obvious, the chances are he’ll pick up the phone and consult a friend who is as knowledgeable on Philips sets as he is on Thorn chassis. The friend will probably be able to guide him to the seat of the trouble, be it a faulty diode, a burnt out choke or perhaps a dry-joint in an unexpected place. If he has such a friend that is. If he hasn’t, and he elects to do the job, he too must plod and hope that the fault will not turn out to be too obscure.

We had something to say on this subject in a previous article (“When You Meet a Stranger”), but it seems time to enlarge upon the topic, particularly with respect to certain more up-to-date sets that provide a noticeable lack of simple signposts to aid diagnosis. So as not to leave anyone out, let’s start with a bit of a recap.

## Is there a Mains Transformer?

Most of the earlier colour sets – the ones still most likely to be encountered – used a mains transformer, and it was customary for the tube’s heaters to be supplied by a winding on this. Most monochrome portables also have a mains transformer, to reduce the 240V mains supply (UK) to approximately the same voltage that would be applied to the set from a car battery (12V). There were exceptions amongst portables however, a notable example being the Indesit T12 which employed a switch-mode “pump” circuit. The GEC 3133 and 3135 portables also used this arrangement. Now the problem with these and with many other less familiar circuits is that some sort of start-up system may be required. This was not the case with the first UK chassis to have a switch-mode power supply, the famed Thorn 3000/3500 chassis, because this one did have a mains transformer which powered the l.t. side of things in a conventional way following switch on. Though it caused us all a few grey hairs, it didn’t quite have the mystique that seems to surround some more recent chassis, with their start-up capacitors and resistors and what have you. These need to be approached with some caution, particularly since a set that is apparently “dead” may in fact be very much alive.

Robbed of the mains transformer we can’t, with a colour receiver, rely on the tube heaters providing a visual

indication that power is reaching the set. Nor can the chassis be relied upon to be at neutral potential. In many sets nowadays the chassis is at half mains potential, because the mains input is first fed to a bridge rectifier circuit. The chassis may be connected to the bridge’s negative or positive output, which is something else to think about. We can’t in this short article consider all the various circuit permutations you may encounter: instead we’ll look at one or two of the less common arrangements, from the bench point of view – heavy on the practical aspects, light on theory.

## The Indesit T12LGB Portable

Most of you will by now have come across the Indesit T12LGB portable with its unusual transistor pump circuit. Whilst some of the common faults this set presents – field collapse or no signals for example – are straightforward, there comes a time when one of them is brought in with the comment that it’s dead, though a meter check shows that it’s very much alive. First check whether it works when supplied from a 12V battery. If it does, the start-up circuit will have to be investigated (see Fig. 1).

A d.c. reading of some 300V or more may be obtained around the top right-hand side electrolytics C902/3. A voltage of 220V or so may be found at the collector (the body) of the top right-hand side power transistor TR902 (the pump). If it isn’t, check the wirewound resistors in series with the transistor – R909 is likely to be open-circuit. It’s above the transistor. The other resistor (R908) is on the bottom centre heatsink and is connected via two obvious leads to the top right. By and large then, no trouble so far.

Assuming that the voltage is reaching the pump transistor, the fact that precious little else is happening means that the pump isn’t pumping. Cries of “well I never!” The d.c. voltage at the collector of the pump transistor must not only be high, it must also be smooth. So we double check the reservoir electrolytics C902/3, noting that the main suspect – the second one down, C903 – has its negative side connected to chassis whilst the upper one doesn’t. The start-up supply is obtained from the junction of

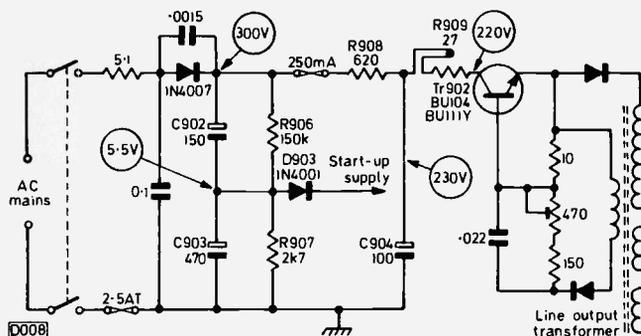


Fig. 1: Power supply arrangements used in the Indesit T12LGB monochrome portable, showing the mains input and rectifier, the start-up circuit and the pump transistor Tr902.



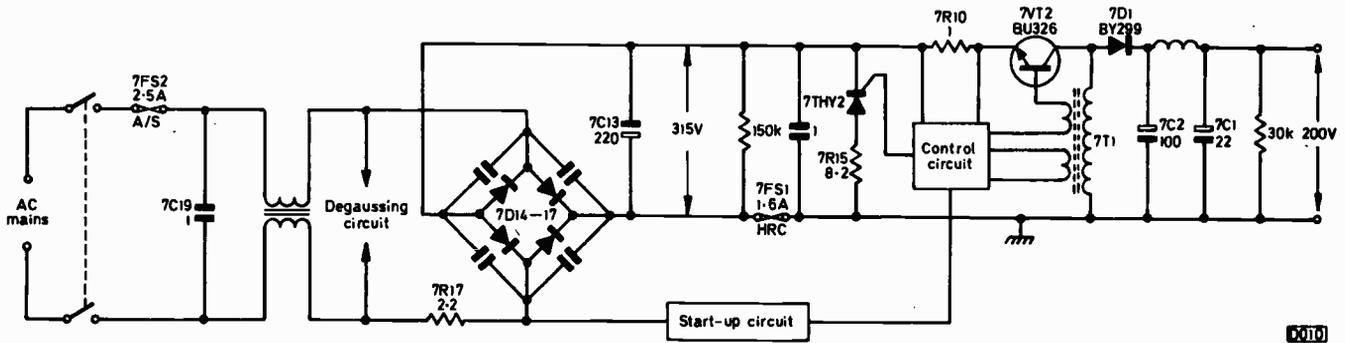


Fig. 3: Simplified diagram showing the way in which a regulated 200V h.t. rail is obtained in the Rank T20, T22 and T26 chassis. The bridge rectifier 7D14-17 produces a supply of approximately 315V across its reservoir capacitor 7C13 – note that this supply is negative with respect to chassis, which is in turn at half mains potential. This negative, 315V supply is applied to the emitter of the chopper transistor 7VT2, which is connected in a self-oscillating circuit with feedback between its collector and base via the chopper transformer 7T1. The control circuit adjusts the chopper transistor's on/off times to provide the voltage regulation. The output developed across the primary winding of 7T1 is rectified by 7D1, which in turn develops a regulated 200V supply across its reservoir capacitor 7C2 – this supply is positive with respect to chassis. Though the chopper is self-oscillating, it requires a start-up circuit to trigger it into action at switch on. This consists of a diode which feeds a positive-going mains pulse, after clamping and shaping, to the base of 7VT2. In the event of excessive output from the chopper due to a fault, the overvoltage protection thyristor 7THY2 will fire, blowing fuse 7FS1.

supply used in the T20 that's more likely to be encountered and more likely to give cause for concern.

Fig. 3 shows the main features. Basically, 7VT2 is a self-oscillating chopper whose on/off times are varied so that a stabilised supply is obtained from the rectifier 7D1. Our main interest however is the set's habits when it turns up on the bench. The mains input is fed to a bridge rectifier (7D14-17) as in the Z718 chassis, but this time the positive output from the bridge is taken to chassis via the 1.6A HRC (high rupture capacity) fuse 7FS1. This is not unusual


today, a similar arrangement being found in solid-state ITC colour sets for example. The 315V negative output from the bridge will be found at various points in the power supply's control circuitry but will not be found in the receiver proper. After the power supply unit, the chassis is the normal current return path for the 200V h.t. line which is positive with respect to it. The chopper transistor's emitter stands at some 315V negative with respect to its collector.

Before making any tests, it's as well to study the full circuit in the manual carefully. Use 7VT2's emitter as the reference point when carrying out voltage checks in the chopper control circuitry.

Possible causes of the dead set symptom in the mains input circuit are the 1.6A (later changed to 2.5A) anti-surge resistor 7FS2 and the 2.2Ω resistor 7R17. If 7FS2 is found blown, the likelihoods are a shorted diode in the bridge rectifier circuit or the mains filter capacitor 7C19 being short-circuit or troublesome. If 7FS1 is found blown, the crowbar thyristor 7THY2 may have switched on, possibly due to a fault in its firing circuit. It normally sleeps unused – and may thus be overlooked.

The usual complaint however is tripping due to excess current. This is nothing to do with the power supply. As in the Z718 chassis, a trip removes the drive to the base of the line driver transistor when the load on the line output stage is excessive. So the answer is again to unload everything that can be unloaded in the line output stage and try again. The tripler is an obvious suspect but, we hate to tell you this, in most cases the trouble is due to shorted turns in the line output transformer – the evidence for which consists of the winding overheating even though the tripler has been disconnected. Sorry.

Oh yes, start-up arrangements. Again, most of the supplies in the set are derived from the line output stage. Since both the line output and line driver stages are powered from the 200V h.t. rail however (the line driver stage via a 1.8kΩ fusible resistor, the line output stage via an 800mA fuse which was removed in later production), only the line oscillator requires a start-up supply. The arrangement used is exactly as in the Z718 chassis, a 10μF capacitor (4C19 this time) charging from the 200V h.t. line. There's a small 100Ω series resistor (4R49), again as in the Z718, and the same remarks apply. The chopper circuit itself is self-oscillating but not self-starting. The start-up circuit has not however given us any trouble.

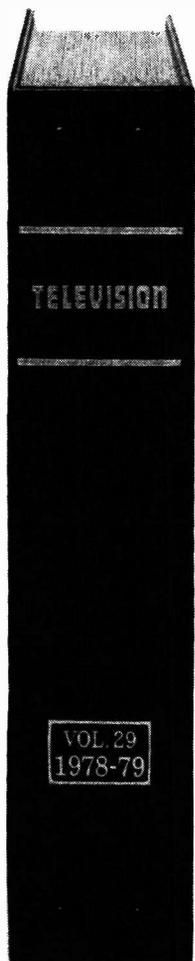

# Bind it

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold approximately 12 issues and is attractively bound and blocked with Television logo. Gold lettraset supplied for self blocking of volume number and years.

Price £4.40 including, postage, packing and V.A.T. Why not place your order now and send the completed coupon below with remittance to:— IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington St., London SE1 0PF.

it's easy with **EASIBIND**

## Order Form

I enclose p.o./cheque value .....

for..... binders

Years required.....  
(BLOCK LETTERS PLEASE)

Name.....

Address.....

.....

.....

Date.....

VOL. 29  
1978-79

# Miller's Miscellany

Chas E. Miller

AS I've said before, particular types of faults seem to turn up in batches. I've recently had this experience once again. This time it all turned out to be to my advantage – it also proves the point that a TV engineer has to have a long, long memory.

The set that started this chain of events off was one of the original ITT, well KB in those days, Featherlight portables – I'd better explain, for newer readers, that the reference is not to a type of surgical goods. Dear me no, it's to a compact all-valve (except for the u.h.f. tuner, which wasn't always fitted initially) transportable set that appeared in the mid-60s. The VC11 dual-standard chassis. The one I had to deal with was one that lacked the u.h.f. tuner, which made it rather less than satisfactory for the job my friend had in mind for it – for use by his son to receive Open University programmes. Had I known this at the start, I probably wouldn't have got involved with it, but you know how difficult it can be to refuse.

I switched on with little enthusiasm – from my recollection, the sets were nothing much to write home about when they were new some sixteen years ago. Up came the sound, but there was no sign of a picture. The timebase was whistling healthily enough however, so I gave it a few minutes. Nothing happened, so I sighed and switched off. By chance I looked at the bench mirror and saw the raster collapse to a bright spot. Something stirred in the back of my mind. Wasn't there a certain resistor that used to fail? I found an ancient manual, blew off the dust, and discovered the faded inscription "if the brightness is low check R167". This 4.7M $\Omega$  resistor is connected between the boost supply and the c.r.t.'s first anode, and was virtually open-circuit.

When a new resistor had been fitted the results were ridiculously good for such an old set. The picture was so bright I could only conclude that the set had been in store for most of its life. It was returned to a delighted owner and might have been forgotten except for another chance happening next day.

This time another acquaintance called in to say that he was on his way to buy a rebuilt colour tube and did I want him to pick up any for myself? So I asked him why he needed a tube himself?

"It's for that Thorn 8000 you repaired for me a month or so ago – it's gone absolutely flat. Everyone says it must be the tube."

Now when I last saw that set it was in excellent fettle, with nary a sign of reduced emission or any other tube fault. So I persuaded him to let me have another look at it before going to all the expense of a new c.r.t.

At first sight it looked as if I'd wasted my time. All the classic symptoms of a bad tube were present – very poor brightness, flaring on highlights and so on. It seemed hardly worth even trying the tube tester on it. But as I switched off there was once again that brilliant spot as the raster collapsed. Wondering whether this was going to be a repeat of the previous day's performance, I measured the c.r.t. base voltages. The grids should have been at about 27V – measured at the junction of R613 and R615, which provides forward bias for the beam limiter diode network. The voltage was virtually zero however, due to R615

having risen from 180k $\Omega$  to a very high value indeed. Replacing this resistor restored the brightness to a very acceptable level.

After this it was certain that a third repair of the same type would be required – it was actually waiting for me in my secondhand set store! I'd been presented with another Thorn colour set, this time a 3000, which was alleged to be completely worn out. When I got around to trying it out I was gratified to find out that the picture wasn't too bad at all. After half an hour or so it had all but disappeared however. Flushed with my recent successes, I again checked the c.r.t. voltages. Grid voltage wrong again, this time due to R451 (910k $\Omega$ ) having changed value as a result of which all the guns were close to cut off. A replacement resistor – it's mounted on the field timebase panel – did the trick, and I was now feeling very self-satisfied indeed. Which is usually the signal for a kick in the pants from fate.

Sure enough an hour or so later, during a test run, the picture began to lose all its red. Not too difficult this one – simply a high-value resistor (R725, 1.5M $\Omega$ ) in the feed to the red first anode preset increasing in value. During a further test run however the picture seemed gradually to lose its crispness – it eventually, and suddenly, went bright green, the luminance information virtually disappearing. It required a session with the scope to fathom this one out. I finally tracked it down to the luminance coupling electrolytic C204 (100 $\mu$ F) on the video panel. It was open-circuit, and must have been failing gradually over a period since a new one brought the picture up to almost "new tube" standard. Well that was some three-four months ago, and the set's given satisfactory service ever since.

## VINTAGE SPOT: VIDOR

Few people nowadays would associate the name Vidor with anything other than batteries. The firm was once one of the UK's largest manufacturers of portable radios however – along with their chief competitor Ever Ready, also of course a battery making concern. And for a few years during the late 40s and early 50s they also produced what they called televisors.

## Early Models

Many of the designs of that time bordered on the eccentric. The Vidor sets featured good design and workmanship however. One of the earliest models was the CN370, which was introduced at the time when the BBC service was being extended to cover the midlands – via the Sutton Coldfield transmitter. This was a difficult period for setmakers, since many of them were committed to t.r.f. designs which couldn't easily be adapted for the new channel 4. Even the superhets of the day weren't always readily tunable – in many cases new sets of aerial and oscillator coils had to be fitted, plus perhaps a few changes made to associated capacitor values. Vidor however opted for a commendably simple approach – a two-channel superhet which could receive either channel 1 or 4 at the turn of a switch.

It was a 12in. console model which had a handsome



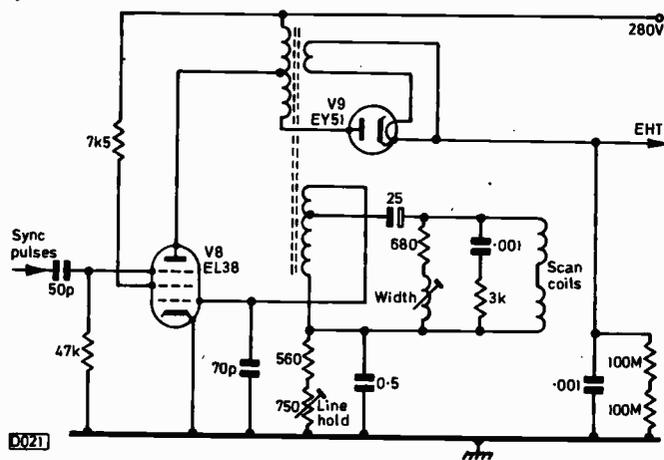


Fig. 2: The single-valve (plus e.h.t. rectifier) line timebase circuit used in the CN390 series.

There were three ECL80s this time – audio, sync amplifier/field blocking oscillator and field output/line oscillator. The remaining thyatron had finally departed from the field timebase, while on the line side a boost diode appeared, the output stage using a more modern PL81/PY80/EY51 configuration. Vidor's name for the boost diode was "primary recovery diode", which seems fair enough as it recovers the energy otherwise wasted in the line output transformer's primary winding.

This time there was an a.c./d.c. power supply – no transformer and with a PY82 replacing the GZ32 that had been used as the h.t. rectifier till then. The series heater chain incorporated the idea, popular at the time, of a thermistor shunted by an ordinary resistor – of 330Ω in this case. As a result, the thermistor's warm-up time was delayed and the valves came up very gradually indeed. So gradually that one sometimes despaired of them ever getting going, especially with the PY80's normal three-minute warm-up time!

## Conversion

These sets gave good service over long periods. The simple and stable i.f. amplifiers were well suited to 13-channel use when a turret tuner was added – the correct procedure was to convert the original mixer valve for use as an extra i.f. amplifier. The previous models were not so easy to convert since their i.f.s were lower than usual – 9.75MHz vision and 6.25MHz sound. Years later however those old 6.25MHz sound i.f. transformers became unexpectedly useful. No doubt many readers will remember how the old Bush twin-chassis sets could be coaxed into operating at 15.62kHz so that with a u.h.f. tuner in place of the v.h.f. one and the vision detector diode reversed quite good 625-line pictures could be obtained. It was not possible to receive the sound without altering the sound i.f. transformers however, and it was here that the Vidor ones came in handy since they were directly interchangeable and easily tuned to the intercarrier sound frequency. It was relatively simple to knock up a modified ratio detector which produced acceptable sound. One of the sets I modified in this way was carted around to all sorts of locations to test signal strength, and after long and useful service ended up as the basis of a DX receiver. But that's another story . . .

## Footnote

A friend who has a Murphy Model CV1917 (Rank A823

# next month in

# TELEVISION

## COLOUR PORTABLE PROJECT

The popularity of colour sets with screen sizes of 20in. or less has increased dramatically over the past three-four years. So we thought we'd see what we could come up with in this area. The result is a portable that offers excellent performance and good value. Design features include:

- Full function infra-red remote control
- Minimum component count with simple construction and setting up
- Pincushion distortion free tube system with black matrix screen plus preset convergence and purity. Choice of tube size (14, 16 or 20in.)
- Line output stage using gate turn-off switch and diode-split transformer
- Switch-mode power supply
- Low power consumption (60W)
- Prealigned i.f. module
- Single-chip colour decoder and class AB video output stages
- VCR compatible

## SONY HVC2000P COLOUR CAMERA

A review of this interesting camera which amongst other things uses a novel pickup tube – the Trinicon.

## SERVICING FEATURES

Fault report from Robin Smith, servicing notes on ASA solid-state colour receivers and Sid Simon on c.r.t. reactivation.

**PLUS ALL THE REGULAR FEATURES**

ORDER YOUR COPY ON THE FORM BELOW:

TO.....  
(Name of Newsagent)

*Please reserve/deliver the May issue of TELEVISION (70p), on sale April 22nd, and continue every month until further notice.*

NAME.....

ADDRESS.....

chassis) rang up to complain that the picture was marred by what sounded like a hum bar. I took some replacement smoothing capacitors with me, including the usual test one with its long flexible leads. For once the fault showed up immediately the set was switched on, so I anchored the negative lead of my test capacitor under a handy screw on the power unit and prepared to bridge the smoothers to see if one had lost capacitance. I borrowed a mirror to observe the results, and guess what – the hum bar had gone. “Oh no” I thought, “not another rotten intermittent fault.” It then dawned on me that the problem had simply been a poor connection between the board and the supporting metal frame – this was confirmed by loosening the screw and tightening it up a couple of times.

Now what do you charge for tightening a screw? The famous railway engineer George Stephenson is supposed to have performed a similar duty for which he charged £10.0.6d – 6d for tightening the screw and £10 for knowing which one to tighten. But I couldn't even claim that small credit, since it had been purely a matter of luck. I hadn't intended to make a charge anyway, so I was spared the mental effort of coming to a decision. The fact remains however that it costs as much to make a call to do a minor servicing job as it does to carry out a major repair. I thought I'd ask my old friend Ike Hodge, whose “Guide to Coarse Servicing” is a byword in such cultural centres as the local pub, what his feelings on the matter were. I'll let you know in the next *Miscellany*.

---

## Selected New Products

### LEADER TEST GEAR

A. Marshall (London) Ltd. have been appointed stockists for the Leader range of test equipment, which is imported by Sinclair Electronics Ltd.

Of particular interest to the TV servicing trade is a dual-trace oscilloscope, Model LBO-508A. The unit features a 10mV/cm sensitivity with a bandwidth of d.c. to 20MHz at a price of £299 (+ VAT). We hope to include a review of the instrument in a future issue of *Television*.

Also of interest in the range is the LBO-80 high-voltage probe. This is a 20k $\Omega$ /V self-contained instrument that can measure e.h.t. up to 40kV with an accuracy of  $\pm 3\%$ . The price is £13 + VAT, and again we hope to include a test report in a future issue.

A. Marshall (London) Ltd., Kingsgate House, Kingsgate Place, London NW6 4TA.

### DIGITAL CAPACITANCE METER

B and K-Precision have recently announced a portable, auto-ranging digital capacitance meter, Model 830. In use, one of ten ranges is automatically selected and the value of the unknown capacitor is shown on the 3½ digit l.c.d. display. The capacitance range is from 1pF to 199.9 $\mu$ F, with a basic accuracy of 0.2%. A “range hold” switch is incorporated. This freezes the instrument in one range to reduce the response time when the capacitors to be measured are within a narrow value range. Battery life is quoted as 20 hours for continuous use, but there is provision for an a.c. mains adaptor. The suggested price tag is around £100 plus VAT.

### INEXPENSIVE SCOPE

Albol Electronic's SB3M scope has a price tag of only £99 + VAT. The bandwidth is d.c. to 3MHz, with automatic timebase triggering, 50mV/cm sensitivity and a calibration accuracy of  $\pm 5\%$ . The input impedance is 1M $\Omega$  in parallel with 30pF.

Albol Electronics and Mechanical Products Ltd., 3 Crown Buildings, Crown St., London SE5 0JR.

### THANDAR DMMS

Two new l.c.d. digital multimeters have been introduced in the Sinclair Electronics Ltd. Thandar range.

The TM352 is a hand-held instrument with a 3½ digit

0.5in. display covering d.c. voltages from 100 $\mu$ V to 1,000V, a.c. voltages from 100mV to 1,000V, direct current from 100nA to 10A, and resistances from 1 $\Omega$  to 20M $\Omega$ . The instrument also features an audible continuity check and a transistor gain measurement facility. Push-button controls give rapid and easy operation, whilst compact size and long battery life make the instrument useful for field servicing. The price of the TM352, complete with battery, test leads and a one-year guarantee, is £49.95 + VAT.

The TM353 is a 3½ digit l.c.d. multimeter for use in the workshop or in the field, its main feature being a battery life in excess of 3,000 hours. Supplied complete with a test lead set and alkaline batteries, the TM353 costs £84 + VAT and carries a one-year guarantee.

Sinclair Electronics Ltd., London Road, St. Ives, Huntingdon, Cambridgeshire PE17 4HJ.

### ALCON LCD MULTIMETERS

Two new Miselco pocket multimeters have been announced by Alcon Instruments Ltd. Designated the “Super 20” and the “Super 50”, they offer sensitivities of 20k $\Omega$ /V and 50k $\Omega$ /V respectively on both the a.c. and d.c. ranges. In addition to voltage, current and resistance ranges, there's a simple semiconductor test facility. A signal injector which is rich in harmonics up to 500MHz is also available.

In addition to the usual fuse protection, the instrument features a novel neon discharge system and a new electronic high-speed cut-out which disconnects the instrument from the circuit under test should a dangerous overload be applied. The “Super 20”, which in our opinion is the more suitable instrument for television work, is available off the shelf at £56.81 including VAT, complete with case, leads and instructions. An optional high-voltage probe extends d.c. range to 30kV.

Alcon Instruments Ltd., 19 Mulberry Walk, London SW3 6DZ.

### NEW SCOPEX SCOPE

Scopex Instruments Ltd. have announced a new low-cost, high-performance scope. The dual-trace instrument offers a 10MHz bandwidth, 2mV/cm sensitivity and a 10 × 8cm display. The price of £230 + VAT includes two high-impedance probes and carriage within the UK mainland.

Scopex Instruments Ltd., Pixmore Industrial Estate, Pixmore Avenue, Letchworth, Hertfordshire SG6 1JJ.

# Darlington's in TV

S. George

ONE of the neatest uses of transistors is the Darlington pair, where one transistor directly drives the base of a second one with no biasing or other components involved in the coupling between the two transistors. The advantage is that the current gain of the combination is approximately the product of the individual gains of the two separate transistors, which means that a high overall gain figure can be achieved using a low-power device to drive a higher-power one. The idea was first put forward by S. Darlington as long ago as 1953, for driver/output stage use in audio amplifiers. Since then, various alternative arrangements have appeared, for example pnp/npn configurations and drive from either the collector or the emitter of the first transistor – also of course output from the collector or emitter of the second one – and there's also been increasing use of Darlington pairs in TV receiver circuitry.

## Voltage Regulator Circuit

One of the earliest uses of the Darlington pair in TV sets was in series voltage regulator circuits. Fig. 1 shows a simple series regulator circuit with Tr1/2 being the Darlington pair. Zener diode D1 stabilises the base voltage applied to Tr2, and the output obtained at the emitter of Tr1 will remain steady at 1.4V less than the voltage at the base of Tr2. The use of the Darlington pair increases the current handling capability of the circuit – compared with the use of

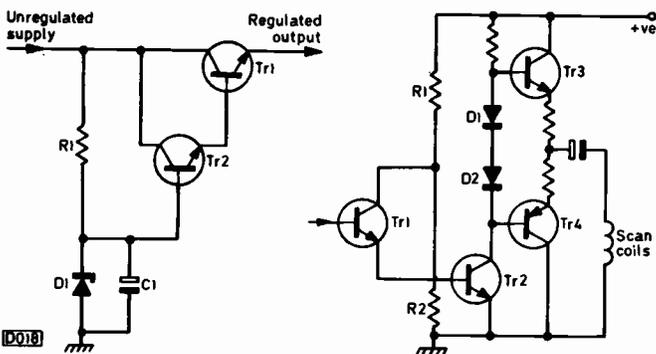


Fig. 1 (left): Darlington pair of transistors in a simple voltage regulator circuit without feedback. The output is stabilised at 1.4V less than the voltage, set by zener diode D1, at the base of Tr1. The circuit acts as an active filter, since the value of C1 is much less than would otherwise be necessary to provide smoothing.

Fig. 2 (right): Use of a Darlington pair of transistors (Tr1/2) as a field driver stage.

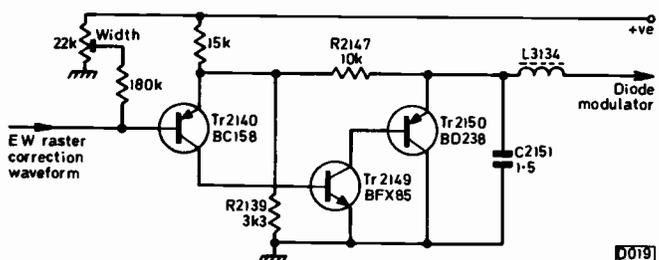


Fig. 3: A triple Darlington configuration, with pnp and npn transistors, used to provide the EW modulator drive with a 20AX tube (Philips G11 chassis).

a single power device in position Tr1 that is. It's interesting to note that the circuit also functions as an active filter, since the capacitance of C1 in Tr2's base circuit is in effect multiplied by the circuit's overall current gain. Switch-on surges are thus minimised, and there's considerable saving in component cost and size. The circuit is widely used, a well-known example being the l.t. regulator in the ITT CVC5/CVC9 series of hybrid colour chassis. In this example the low-power device is a BC170B and the high-power device an AD161.

## Drivers/output Stages

One of the earlier TV uses of a Darlington pair as a waveform amplifier was in the field driver stage of the Thorn 8000 series chassis, where the first transistor is a BC147 and the second a BC142. The circuit is shown in simplified form in Fig. 2. R1/2 are included to limit the voltage swing at the collector of Tr1 and the current flowing in this transistor, while diodes D1/2 develop the forward bias for the bases of the complementary push-pull output pair Tr3/4.

It's quite common nowadays to find the Darlington pair sharing a common encapsulation. Examples include the BU807 line driver/output device used in monochrome portables, the BD677 which is used as the EW modulator in the Thorn TX10 chassis, and the BUW81A which is used as the chopper-plus-driver in the Decca 70 chassis.

## Multiple Darlington Circuits

As mentioned earlier, the Darlington principle has been developed to include pnp/npn combinations – also triple-transistor configurations. Our final example illustrates both these techniques. It's an EW modulator driver circuit widely used with the 20AX colour tube. The example shown in Fig. 3 is used in the Philips G11 chassis.

Here we have a pnp/npn/pnp configuration, with the first two transistors operated in the common-emitter mode and the final transistor in the common-collector (emitter-follower) mode. The result of course is an amplifier with high gain and a low output impedance. The emitter voltage for the final transistor is provided by the diode modulator circuit, while R2147/R2139 are included to provide voltage negative feedback. The output is taken via the low-pass filter L3134/C2151, which has negligible effect at the EW correction waveform's field frequency while preventing line-frequency signals being fed into the circuit. Note that there's phase reversal in the first two stages, since they are operated in the common-emitter mode, but not in the final stage: overall therefore the amplifier's input and output are in phase.

## Semi-Darlington's

The term Darlington pair is sometimes loosely used to refer to a d.c. connected transistor pair where the first transistor has an emitter or collector load resistor. Whilst the gain of such a circuit may approach that of a Darlington pair, correctly speaking the base current of the second transistor in a Darlington circuit is the entire emitter or collector current of the first transistor. ■

# Fault Report


Dewi James

I'M back running my own repair service after doing a stint with one of the large rental chains. The result of course is that all sorts of sets are appearing on the bench instead of just a few chassis. There certainly seem to be quite a few Hitachi sets around here. Let's summarise some recent experiences with them.
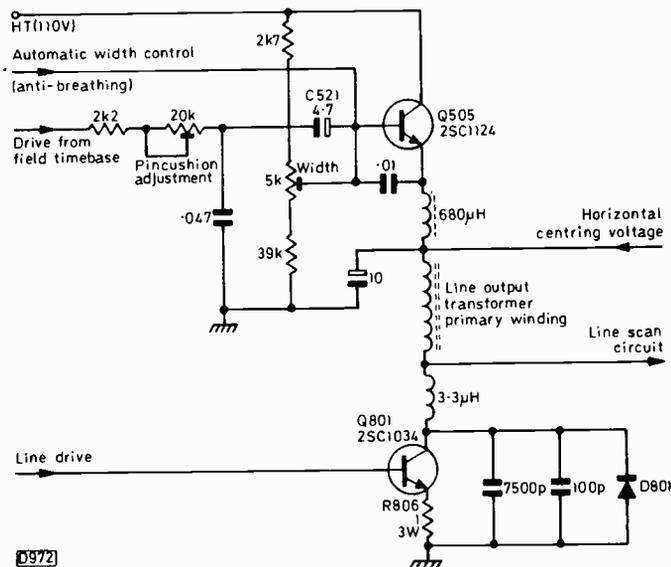
## Hitachi Models

A set fitted with the NP6C chassis had a picture that was becoming narrow intermittently, sometimes returning to normal width almost immediately, at other times remaining narrow for quite long periods. The change was accompanied by a sizzling sound, rather like an e.h.t. discharge. After much searching and voltage checking etc., moving from the line output stage to the switch-mode power supply and back again, the fault was eventually traced to R937 (220Ω) which is connected to pin 5 of module CP902 (type HM9102) in the h.t. voltage sensing section of the power supply.

Failure of sets fitted with the NP6C chassis to start is not uncommon. The usual causes are dry-joints or a defective transistor in the multivibrator start-up circuit. On this occasion however the defective transistor was TR903 (2SC458) which shapes the pulse from the line output stage before applying it to the pulse-width modulator circuit.



D972


Fig. 1: The EW raster correction system used in the Sony 13in. colour portable Models KV1300UB, KV1310UB and KV1330UB. Correction is applied by connecting the modulator transistor Q505 in series with the h.t. feed to the line output transistor Q801. This means that the series chopper transistor Q903 on the power supply panel, the modulator transistor Q505 and the line output transistor Q801 are connected in series. The e.h.t. is obtained from the "converter" stage, which is interposed between the line driver and output stages. In addition to the field-frequency correction waveform fed to the base of Q505 via C521, an anti-breathing correction voltage is applied from the circuit shown in Fig. 2 - Sony called this "automatic zoom correction". A similar circuit to that above is used in the later Model KV1340UB - the very early Model KV1320UB is completely different.

The next set was fitted with the latest NP8C chassis. The only sign of life was a low-frequency buzzing sound coming from the region of the chopper transformer T901. The 108V and 54V rails were present and correct, and there was drive at the base of the line driver transistor Q701. Its collector voltage was high however. Whilst trying to figure out why this was so, and why the line output stage was not working, we discovered that the print to R714 (5Ω, 8W) was open-circuit. So we repaired this and found that far from improving matters we'd now lost the supply rails. Time to take a good look at the circuit. It turned out that R714 is the sensing resistor for the excess-current trip, being connected in series with the line output stage. The fault turned out to be a short-circuit line output transistor (Q702, type 2SC1942). Oh, and you could find this fault in GEC sets, since the same chassis is used in Models C2057H and C2257H.

Two sets with colour problems. The first was an old one (Model CNP860) with the complaint that the colour was all right for the first hour after switching on, colour bars then developing on the screen. Sure enough, after an hour colour lock was lost. Twiddling the reference oscillator transistor's collector coil L1005 restored normal colour - we were tempted to try this because there was already a matchstick sticking in the coil! In the end, replacing the varicap diode CR1003 fixed this bit of nonsense, and we were able to throw the matchstick away. The other set was rather more recent, a CTP202 (PAL-4 chassis). This time the complaint was no colour, and after disabling the colour-killer by linking TP454-5 we discovered that the real problem was no colour sync. The burst signal was present at TP457, i.e. at the burst input to the phase detector circuit, and the set oscillator frequency control R497 had a little effect towards one end of its travel. Not unexpectedly, the cause of the trouble was the phase detector diodes CR454/5.
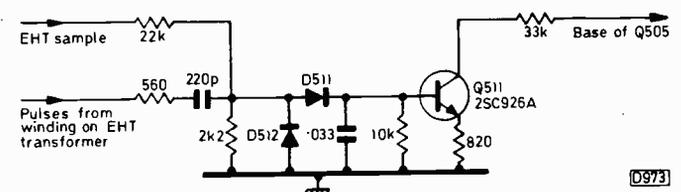
## Sony Colour Portables

Two dead Sony 13in. colour sets. The first was an elderly KV1300UB, with its cut-out open and the 2A mains fuse open-circuit. The chopper transistor Q903 (2SC867) and the pincushion modulator transistor Q505 (2SC1124) were both short-circuit. The second was a slightly later KV1310UB, and again the cut-out was open, due in turn to the chopper transistor Q903 being short-circuit. We replaced the chopper, did a few cold checks, and switched on again. The sound came up perfectly, but there was no field scan. Check and find the vertical output-1 transistor,



D973

Fig. 2: Circuit used to sense e.h.t. variations and apply correction to the base of the EW modulator transistor Q505. The e.h.t. ("flyback") transformer is driven by the converter transistor Q802. The e.h.t. sample is obtained from the tripler circuit.

another 2SC867, short-circuit. Replace and switch on, but still no field scan. The transistor's  $27\Omega$ ,  $\frac{1}{8}W$  feed resistor R566 was open-circuit. Presumably, in view of its low wattage rating, this is a safety resistor. Switch on again and we had some field scan, but it was insufficient and bent over on itself. This was due to the other field output transistor Q509 (type 2SC1124) being short-circuit. I thought a 2SC1127 would do, and in fact it produced some improvement, but it was not until the correct transistor was obtained and fitted that we had normal field scan. Incidentally, someone had also fitted an MJE340 in the audio output position instead of the correct 2SC867, but it seemed to be working correctly so I left it alone.

Unfortunately we still had quite severe pincushion distortion. The width control, which sets the bias applied to the base of the pincushion modulator transistor Q505 (see Fig. 1), was functioning, so we felt that the transistor was likely to be o.k. It turned out that C521 ( $4.7\mu F$ ), which feeds the correction waveform to its base, was open-circuit. That must be it I thought. Wrong! After the set had been on for a few minutes, the brightness began to vary. So did the vertical and horizontal amplitude. So we monitored the 110V rail with a scope, and found large spikes that coincided with the variations. After much head-scratching, some luck and a masterly bit of diagnosis, we traced the fault to the fact that the chopper transformer T601 was breaking down internally. Replacing this item completed the repair, and I must assume that it was the spikes on the h.t. line that had led to the breakdown of most of the other items.

## Sharp C2072

The final set in the Japanese department was a Sharp Model C2072, with a barely visible raster but the sound o.k. Simply low c.r.t. first anode voltage, due to R627 ( $330k\Omega$ ) being open-circuit. There are three of these  $330k\Omega$  resistors in series in this set, so presumably any one of them can become faulty.

## Some Continentals

A Grundig 2210GB appeared in our workshop during a particularly wet Wednesday. Apparently it had "gone off" during Coronation Street. "It must be a valve" the wet apparition at the door said, "I was going to have a look at it for a friend, but I've no time just now." We've all come across these local experts of course. Dry-joints around the line output stage are a common cause of the trip cutting out to give the dead set symptom on these sets, but this one was the exception. Each joint looked perfect. I was going to have to earn my money.

A visual check revealed that the focus VDR had disintegrated, something that can be quite a spectacular occurrence at times. This wasn't the reason for the set being dead however. The cause was traced to R514 ( $2.7\Omega$ , 4W) in the h.t. feed to the line output stage being open-circuit. There were no detectable shorts, so R514 and the focus control were replaced and the set switched on. Everything came on normally and the set's worked correctly ever since.

The Waltham hybrid monochrome Model W125 was a new one to me, but a couple have turned up recently (the circuit was given in the August 1977 issue of *Television* incidentally). The first displayed a blank raster, with neither vision nor sound signals and the 24V and 12V rails at about 5V. D401 produces these supplies, being fed from a winding on the line output transformer, and things were back to normal after fitting a new diode. The second set had an

inoperative brightness control due to a changed value resistor in the brightness circuit.

Another new one to me was the Salora Model 1F3K (F chassis). The set is of Finnish manufacture and had been sold by a large store. The complaint was sound but no picture, though there was obviously e.h.t., as indicated by the sighing of the scan coils and static on the face of the screen. Easy I thought: no c.r.t. first anode voltage. Check at pin 10 and find plenty of voltage, also a hefty focus voltage at pin 1. Cathodes about right at 140V. Brief moment of panic – after all I'd never seen one of these sets before, was in a tiny cottage on the north east coast of Anglesey, twenty miles from base, and it was a cold, wet Saturday afternoon – just two hours before the Wales/England match at Cardiff Arms Park. Before making a dash for it, let's check the grid voltage. Bingo: a large negative voltage, hence the cut-off tube with no brightness. Trace through circuit using diagram found in plastic envelope attached to back of set. The grid bias is derived from the 220V rail, which comes from the line output stage, the feed resistor being RA34 ( $100k\Omega$ ). This was faulty of course, and on replacing it we had 11V positive at the c.r.t. grids and brightness on the screen. The grid circuit is used for flyback blanking incidentally.

This set has many interesting features, one being an automatic search and store system – the set can scan the bands automatically, indicating where it is at any instance by means of a green line on the screen. When it finds a station it stops, and if you want the station you press the store button and the appropriate channel selector button. Once repaired, the set gave an excellent picture. I had an even worse moment of panic later that same afternoon, my sanity being restored this time when Steve Fenwick kicked a penalty just before the end of that match. I'm not sure whether I can take much more of this.

## Home-brewed Troubles

So much for foreigners. On the home front we recently had a Philips G8 that was giving an excellent imitation of a set with a faulty tube, i.e. a misplaced shadowmask. The purity was out, and none of the rasters would converge. These faults turned out to be due to open-circuit resistors however. The purity trouble was due to R1358 ( $1.5\Omega$ ) in the degaussing circuit being open-circuit. It's on the power supply panel. The misplaced rasters were due to R1920 ( $10\Omega$ ), R1933 ( $10\Omega$ , R/G parabola balance) and R1934 ( $10\Omega$ , R/G parabola) in the horizontal R/G convergence circuit all being open-circuit.

The trouble with a Decca set fitted with the 80 chassis was no sound and a bright white raster. The sound problem was easy enough – a new TBA800 audio i.c. put that right. The bright white raster took a little more effort however. Not unexpectedly, the collector voltages of the RGB output transistors were low. So we traced back along the luminance signal path, and discovered that there was no voltage at the emitter of the luminance emitter-follower transistor TR208 (BC157), though there was voltage at its base. Replacing this transistor restored the picture.

Finally, a set fitted with the Rank Z718 chassis. The problem was foldover at the bottom of the screen, and no amount of jiggery pokery with the field timebase controls would get it right. This chassis uses one of those rather complex class AB field output stages, and the biasing conditions can give rise to difficulties of this sort. Sure enough 4R30 ( $13\Omega$ ) was found to be damaged, and after replacing it and the nearby diodes 4D4-7 (to be on the safe side) the fault had been cleared.

# Long-distance Television

*Roger Bunney*

JANUARY is traditionally a poor month for DX-TV reception. Not so this time however. Periods of enhanced reception, via all modes of DX propagation, have been reported by many enthusiasts.

A letter from Arthur Milliken (Wigan) describing reception of suspected Arabic signals on chs. E2 and E3 during the afternoon of December 26th arrived too late to be mentioned in the last column. The ch. E2 signal consisted of a feature film with a floating image of two men talking, dressed in Arabic clothing. The later ch. E3 signal produced an Arabic news announcer with clearly defined letters on the station identification. The signals were also received by Brian Fitch (Scarborough). The mode of signal propagation is unknown.

There was Sporadic E activity on several days during the period under review. December 30th produced a short but interesting lunch time opening, with signals from E. and W. Germany on chs. E2 and E4. The 31st was even more dramatic here, with very strong Polish signals on chs. R1 and 2 and weaker ones on ch. R3. There were also Russian ch. R1 signals, but these tended to be mixed with more distant Russian ch. R1 signals arriving via F2 propagation. The result was rather a lot of interference! There were yet more SpE signals on January 4th – from Norway, Sweden, Finland and Russia. These signals, throughout Band I, were reported by various enthusiasts in the UK.

The best SpE opening seemed to occur on the 9th, during the mid-morning. I logged NRK (Norway) chs. E2/3, SR (Sweden) chs. E2/3/4, TSS (Russia) ch. R1 and YLE (Finland) ch. E2 here at Romsey – most of these signals were very strong. In addition, Brian Fitch logged YLE ch. E3. In the late afternoon of the following day, Mark Baldwin (Rugby) received RUV (Iceland) ch. E3. There was a lull during the following week, then a further spell during which Cyril Willis (Cambridge) noted sustained signals from RTVE (Spain) on chs. E2/3. There were further SpE

signals on the 20th/21st, both Andrew Webster and Arthur Milliken receiving, during two-hour openings, RTVE chs. E2/3/4 and RAI (Italy) chs. IA/B. RTP (Portugal) and NRK were also received in the UK on these days.


Meteor shower/scatter reception was particularly rewarding. Apart from the Quadrantids shower during the first week of January, there was a high level of random MS activity on most days. Mark Baldwin, who has been upgrading his installation, has been successful with Band III MS reception on chs. E5/6, logging numerous signal pings. This is a difficult field. Mark can just receive a weak signal, via tropospheric scattering, from Roermond (Holland) on ch. E5. This serves as a sync reference, with the pings registering "on top". Mark is currently using a home constructed eight-element Band III array, but intends to erect a Jaybeam ABM11 aerial which should increase his Band III capability. He received a Derby amateur TV station (G8VBC), at a distance of some 40 miles, using a Wolsey Colour King aerial!

Tropospheric reception was the most significant during the period however. A high-pressure system at the turn of the year produced enhanced tropospheric propagation from December 29th through to January 1st. Brian Fitch received several German transmitters on the 29th, then more widespread signals to the south and east on the 30th, with French and German Band III and u.h.f. signals. DFF (E. Germany) ch. E34 was noted in Eastern UK, and during the late afternoon Cyril Willis was rewarded with DR (Denmark) ch. E7. There were many signals on the 31st – here at Romsey they tended to be noisy though slow fading. For many enthusiasts in Eastern UK the highlight of the period was CLT (Luxembourg) on chs. E7/21. These signals were still visible on the 2nd, when the others had all faded. There was a smaller tropospheric opening on the 9th, with W. German stations at u.h.f., and at the time of writing (on the 27th) conditions are improving.

F2 reception has been rather lacking unfortunately, and it seems as if the best of the present cycle has now passed. TSS ch. R1 was present via F2 only during the first week of January. The most dramatic F2 reception was of Australia ch. A0 (46.25MHz vision) on January 10th – with possible SpE enhancement at the Australian end. Several UK enthusiasts noted this sustained signal, which lasted for over an hour. Ryn Muntjewerff received the signal weakly in Holland, for over an hour "on and off" with at one time a floater – this is a "first" in Holland. Mark Baldwin had the signal for some twenty minutes from 0846GMT. There was



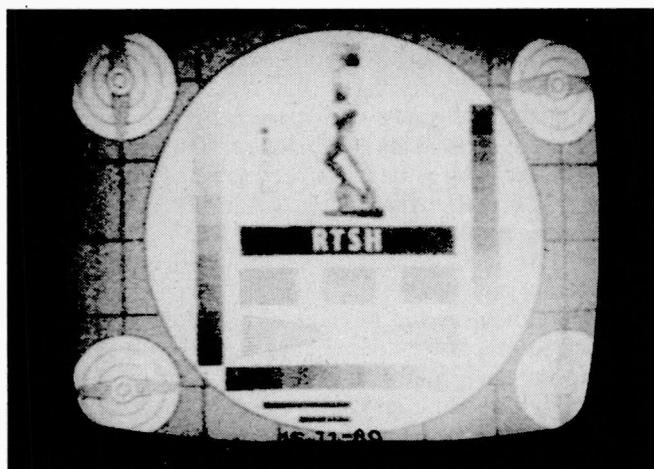*Reception from the Russian Stat-T satellite, at 714MHz, by Ian Roberts in South Africa.*



*The Albanian test card, on ch. IC, received in Holland by Ryn Muntjewerff.*

a weak image for only about three minutes here at Romsey, and at Shaftesbury the signal wasn't even visible!

In all then it's been a very active month for the time of year, and I fear that February/March will be rather quieter.

### Overseas Reports

Petri Pöppönen (Lahti, Finland) reports SpE reception on December 23rd, 27th and 31st and January 4th, 5th, 6th, 8th and 9th. He's logged very weak ch. 51 (714MHz) signals from the south east, with unusually difficult sync problems, and wonders whether this might be direct broadcasting from the Russian Stat-T satellite at 99°E – see later!

From Australia, Anthony Mann, Robert Copeman and Wenlock Burton have all reported a very active SpE season. Double-hop propagation is common, and New Zealand signals as high as ch. 2 (55.24MHz) have been seen in Perth, Western Australia. Anthony Mann travelled some 700 miles north of Perth recently, to Exmouth, where he reports incredible conditions – ch. B1 sound and vision and ch. F2 sound on five of the seven days he was there! Ch. B1 on a hand held portable radio receiver gave "local quality" results. Anthony reports that ABC-TV has just been made available via a 4GHz satellite downlink – being transmitted on ch. 8. This is one of four other similar relay outlets. Other signals he mentions receiving whilst at Exmouth include Malaysia, China and Russia. As an historical note, the Carnarvon beacon (52.32MHz) 500 miles from Perth has been received by G4BPY in Birmingham (UK). From programme guides, it seems that the UK reception of ch. A0 on January 10th came from TVQ0 Brisbane!

### DX-TV Book

The second edition of my DX-TV book "Long Distance Television Reception (TV-DX) for the Enthusiast" has now been published by Babani Publishing Ltd., at £1.95. The catalogue number is BP52. The new edition has been updated and expanded, including a section on satellite reception. It's available from booksellers or by post from South West Aerial Systems at an inclusive price of £2.15.

### ATV Transmissions

Steve Whalley (15 Goodwood Place, Tretmar, Stoke-on-Trent), who holds an ATV licence, reports that several amateur TV stations are active in the Stoke area – mainly on Sunday mornings from 1000 and on Wednesday evenings. Steve has an 8W peak sync transmitter feeding a Jaybeam Parabeam aerial. This produces an e.r.p. of 80W. Others in the region operate at higher powers. Steve would like to hear from readers in the area interested in receiving the 430MHz transmissions or aligning tuners for the purpose.

I've obtained one of the new Microwave Modules ATV converters (Model MMC435/600), which lifts the 430MHz signals to ch. E36, and hope to report further next month.

### News Items

**Spain:** The main Navacerrada ch. E2 transmitter, which serves Madrid and the central region, failed on December 27th due to heavy storm damage. It was back on air within two days.

**Australia:** Discussions on the specification for direct satellite transmissions continue, and tenders for a craft with 4-30W and 11-15W transponders have been invited.

**Holland:** We've shown pictures of pirate Dutch TV

**GOLDEN ANODISED AERIALS: SUPERB ECONOMY AMPLIFIERS;**  
EST. 26 YRS. ALL PRICES INCLUDE VAT. EST. 26 YRS.


### ROTATOR PRICES SLASHED

	old price	new price
Hirschman/Stolle Rotator	£51	£39.95
Cornell Dubilier (Heavy duty) Rotator	£71	£64.95

Also a superb range of Masthead amps.

**IMPORTANT Quote TVM**  
For highly graphic lists and Brochure Send 52p. Refund of 30p on 1st purchase over £5.

Established 26 yrs

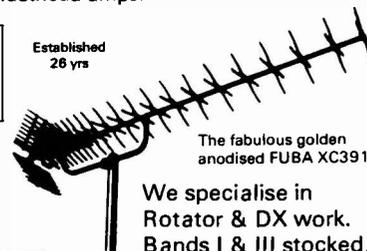

Stockists of the finest aerials available in Britain:  
OPTIMAX (Malta)  
FUBA TV & FM aerials (W.Ger.)  
MARGON TV aerials (Hol.)  
UKW FM aerials (E.Ger.)  
ANTIFERENCE TV & FM aerials (U.K.)

The fabulous golden anodised FUBA XC391

We specialise in Rotator & DX work. Bands I & III stocked.

## ASTRA (GOLDEN D.I.Y.) AERIALS

CB Aerials now stocked. Callers only.

### SOME OF OUR SUPERB TV & FM AERIALS.

Name	Group:W/Band	Gain dB	Price	Discounted
Margon 103 (TV)	both	19.5/21.5	£61.41	£52.19
Margon 91 (TV)	both	18.5/20.5	£44.16	£37.53
Fuba 91 (TV)	both	18.5/20.5	£48.61	£43.75
Optimax 14 (FM)	Band 11 W/B	14	£57.50	£48.88
Optimax 8 (FM)	Band 11 W/B	9.5/10.5	£32.54	£29.29
Fuba 8 (FM)	Band 11 W/B	10.5	£40.85	£36.77

Over 3,000 aerials stocked; all transmitters; poles; lashings; rotators; clamps; wall brackets; amplifiers; diplexers; triplexers; notch filters; coax white or brown.

Many of our customers come from recommendation.

53 WHITEHORSE ROAD, CROYDON, SURREY.

Nr. Spurgeons Bridge Tel: 01-684 4300

Open 9.00-5.30 TUE-SAT.

01-684 5262


Closed 12.30-1.30 Closed All Day Mon.

24 hr. answering service

FM & TV AERIALS AND ROTATORS ON DISPLAY
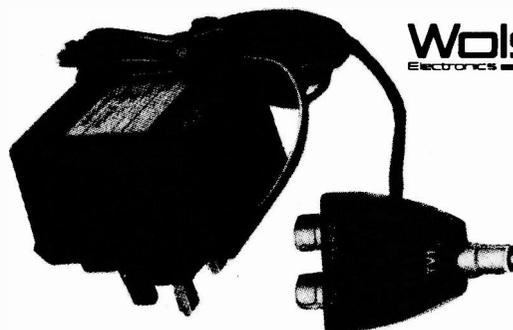
## South West Aerial Systems

10 OLD BOUNDARY ROAD,  
SHAFTESBURY, DORSET.  
SP7 8ND tel. 0747 4370



**WOLSEY**  
Electronics

The Wolsey 'Twin Set' provides 2 wideband UHF amplified outputs (+7dB) with a low noise figure (3.5dB) from a single aerial and is intended for the '2 set household'.

South West Aerial Systems can supply other '1 in, 2 out' amplifiers, and a large range of distribution amplifiers with up to 8 wideband outputs and provision for further splitting on the higher output units.

We carry a vast range of TV/FM aerials, amplifiers and ancillary equipment for the local, fringe or DXing installation – and have the specialist knowledge. Customer consultancy is available to resolve reception difficulties.

Wolsey 'Twin Set' UHF amplifier (2 O/Ps @ +7dB; Noise 3.5dB) £13.85

Antiference XS2U 'XtraSet' UHF amplifier (2 O/Ps @ +4dB;

Noise 6dB) £14.95

Labgear CM7043 'Second Set' UHF amplifier (2 O/Ps @ +4dB;

Noise 6dB) £14.25

Wolsey 'Sapphire 81' 40-860MHz. Distribution amplifier, 1 I/P, 8 O/P


@ +3dB, 1 O/P @ +23dB. Supplies m/head amp. @ 24v. £44.25

All the above operate from 240v. AC.


Babani Publishers – BP52 (Roger Bunney's TVDX book, 2nd edition) £2.15

The above prices include VAT, Postage and Packing.

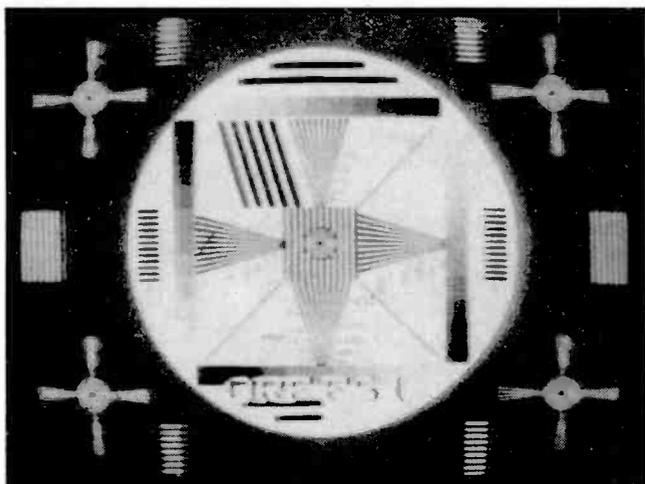Our catalogue costs 45p. Include SAE with all enquiries please.



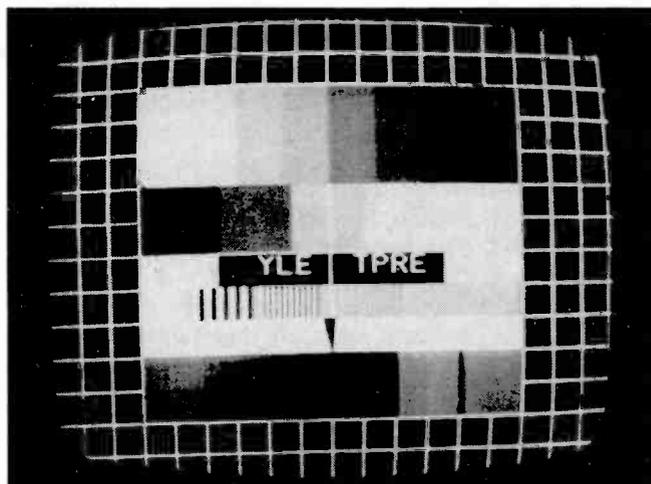
The Telefunken T05 test card used by ORF (Austria). Received on ch. E2a by Andrew Tett (Caversham) using a 7ft. dipole!



Fubk test pattern used by Finland, with Tampere identification (ch. E2). Photo from Petri Pöppönen.



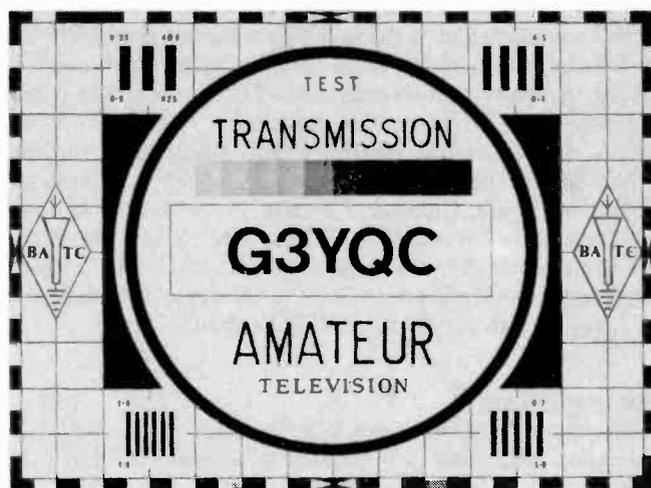Patriotic ATV call sign/pattern used by G3PTU. The 435MHz transmission was received in Holland by Ryn Muntjewerff.



The standard BATC test card, with John Wood's identification (G3YQC). John transmits in the Rugby area.

transmissions in this column from time to time. Gosta van der Linden reports that such activities are much in evidence at present. There are many f.m. radio pirates operating between 100-108MHz and MW pirates operating between 175-190 metres in Eastern Holland. It seems that there is widespread viewing of pirate TV transmissions via cable networks. When the usual transmissions close down, the cable companies insert a colour pattern. If an off-air transmission is received however the system accepts the new signal, e.g. a pirate. So mobile pirates near cable system aerials transmit their own signals on an empty channel, the relay switching the pirate transmission on to the cable network. Favourite channels to use are E35, when ZDF has closed down, and E62 when BRT has closed. One pirate calls himself "Nederland 3"!

#### From our Correspondents . . .

David Burton (Tolworth, Surrey) has bought a 14in. Grundig Model P1421GB. This has a BF907 dual-gate mosfet r.f. amplifier stage which performs very well – on most receivers overloading from Crystal Palace is experienced in this area. The gain is high and the sync performance excellent, even on the weakest signals.

I've received two very long letters from Nanda Kumar Sa of Madras, India, who works as a TV technician. Of particular interest is the fact that he can receive reasonably

good 714MHz signals from the Russian Stat-T satellite on a daily basis, using a Yagi array and a recently added OM337 wideband preamplifier. His home-made aerial has fifteen X-type directors, a straight dipole and a sheet reflector. Programme times are usually 0630-1020 and 1730-2130, Indian time, but vary, evening transmissions sometimes starting as early as 1500. It seems that a long Yagi array with multiple directors, a masthead amplifier with a gain of 30dB and a low-noise u.h.f. tuner are the basic requirements for successful reception from the satellite. The Stat-T2 satellite is expected to be in operation this year, at 754MHz, and may carry the Moscow second programme. Nanda lives 1km from the Madras TV tower (ch. E4, 50kW), which results in DX-TV problems in Band I at times – Madras uses the RETMA test card. Apparently the Stat-T test card photo included in the March 1980 column (page 264) was shown upside down.

#### TV-DX System

We're currently investigating a new, simplified DX-TV receiving system. This uses an external tuner/i.f. unit, with signal processing at i.f./video, followed by remodulation back to r.f. so that the signal can be fed into a standard TV receiver – the object being to be able to use an unmodified TV set. The new Ambit 94420 i.f. strip looks as if it could form the basis of the system.

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a 75p postal order (made out to IPC Magazines Ltd.), the query coupon from page 325 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## **SONY KV1810UB Mk II**

The picture and sound are perfect when the set is first switched on, but after a few seconds a two-inch foldover develops at the top and bottom of the raster. This opens up to cover the full picture, then flickers back to top and bottom foldover.

Check carefully and thoroughly for dry-joints or print problems in the field timebase – by flexing and probing the timebase panel. If nothing turns up, check the field driver/phase-splitter transistor Q502, the output transistors Q503/4, the coupling electrolytic C522 (22 $\mu$ F), the decoupler C559 (1 $\mu$ F), and the output stage biasing components C523 (470 $\mu$ F) and R543 (12 $\Omega$ ) – preferably by substitution.

## **THORN 1580**

The problem with this hybrid portable is that the picture is moving very rapidly from left to right. Also, there appears to be no sound when the line hold control is moved.

First try a new ECC82 line oscillator valve. If the problem persists, check the values of its anode load resistors R54 (22k $\Omega$ ) and R57 (56k $\Omega$ ), and the cross-couplers C50/51 which could be leaky. If everything is in order in this area, check the flywheel sync discriminator diodes W3/4 and the pulse feedback/integrating resistor R45 (68k $\Omega$ ). The sound fault is probably nothing more than a faulty PCF80 audio valve or a dry-jointed audio output transformer.

## **GRUNDIG 5010**

When the set has been on for some time the field collapses to a bright line across the centre of the screen. A slight tap on the cabinet restores the picture. I assume that this is due to a dry-joint or loose connection, but the field output transistor appears to be soundly soldered.

We suggest you check particularly around the NS pincushion distortion correction transducer PTC1. Gentle tapping and probing in this area of the panel should narrow the field of search. Also check the connections between the field timebase subpanel and the main panel.

## **THORN 9000 CHASSIS**

There's an annoying intermittent fault on this set. When it's been on for about half an hour, the height will suddenly reduce at the top and bottom from anything between just perceptible to 1½ in. or so. This is accompanied by a proportional brightness reduction. The effect clears after one-five seconds, and occurs at random thereafter. Since the field timebase and the signal circuits are fed from the 24V

rail, I suspect a fault in this area. When the back is removed however the fault refuses to put in an appearance.

We're inclined to agree with your view that the common 24V line is falling when the fault occurs. Try monitoring the line with the back on and the meter leads passed out. The supply is provided by the EW modulator diodes W711/2, the reservoir capacitor being C725. These are the main suspects, and a squirt of freezer during the presence of the fault should confirm the point.

## **FERGUSON 3787**

The trouble with this colour portable is no sound or raster, with the mains present at the set. I'm a bit puzzled since the chassis does not appear to be of either the 9000 or TX9 type. The only clue as to the cause of the fault is that RU05 is smoking. It's a fusible resistor, but hasn't opened – possibly due to lack of tension or the use of the wrong solder.

This set is of W. German manufacture and is quite different from any other Thorn sets – it uses a thyristor line output stage for one thing. It seems to have been imported as an interim measure whilst the TX9 was under development. RU05 is in the soft-start circuit, and the fact that it's overheating indicates that the overload trip is operating. Check for shorts across the h.t. line, see whether the set works normally with the e.h.t. tripler disconnected, and make sure that all joints in the line output stage are sound – particularly around the combi coil UA01.

## **PHILIPS TS7 CHASSIS**

The fault with this monochrome portable is sound but no raster – no line whistle. Any clues as to where to start?

The fact that you've got sound suggests that the power supply is operative, so there shouldn't be anything drastically wrong in the line timebase. As a check for line drive, see whether you can measure -0.4V at the base of the line output transistor TS29. If not, check back to the driver transistor TS28, paying particular attention to the small 3.3 $\Omega$  safety resistor R231 in its emitter feed circuit, then move back to the oscillator stage TS26/7 as necessary. If line drive is present, the output transistor or the boost diode D22 (U06C) could be open-circuit. A suitable replacement for the boost diode is the BYX71-350.

## **RANK A640 CHASSIS**

The trouble with one of these sets (Bush TV161 series) is that the verticals distort and become wavy when the contrast is increased.

First check the PFL200 video/sync valve and its attendant decoupling electrolytics (2C44, 2C45 and 2C48), then if necessary check the black-level clamp and a.g.c. delay diodes 2MR9 and 2MR2. Note however that this situation is normal on these models with excessive contrast control settings.

## **SONY KV1330UB**

The trouble with this set is pincushion distortion at the sides of the screen. The pincushion control VR504 has no effect but seems to be of the correct value.

The pincushion control adjusts the input to the EW modulator transistor Q505, which is in series with the h.t. supply to the line output stage. The fault is not uncommon in these sets, and is usually due to either the modulator transistor being short-circuit or leaky, or its base signal coupling capacitor C521 (4.7 $\mu$ F) being defective. A further possibility is a faulty automatic width control transistor (Q511, type 2SC926A).

### **VIDEO CONNECTION**

I'd like to feed a standard 1V peak-to-peak video signal from a VTR into a Hitachi CNP192 colour set, bypassing the tuner etc. Any ideas?

Fortunately the Hitachi Model CNP192 contains a double-wound mains transformer, so no isolation problems will arise. A 1V peak-to-peak signal is present at the emitter of the video emitter-follower transistor TR8 (TP1), so you should be able to a.c. couple the video input to this point. If problems arise, we suggest you consult the article on receiver/monitor conversion in the January 1980 issue.

### **ITT CVC8 CHASSIS**

The problem with this set is excessive width. The valves in the line timebase have been replaced and the two width controls are operative, but the width cannot be reduced to provide a normal raster. The h.t. voltage is correct.

We suggest you first check the values of R418/9 (150k $\Omega$  each) which link the line output valve's control grid circuit to the width control network, then if necessary check the sample pulse feedback capacitor C303 by substitution. If the fault persists, check the harmonic tuning capacitor C308 and the damping network C306/R422.

### **RANK A774 CHASSIS**

The original fault was no sound or raster, and was traced to the HT2 smoothing resistor 3R76 being open-circuit. On replacing this there was only a faint, unrecognisable picture – just very faint flickers of light – while the sound seemed to be coming from a foreign station.

The 6MHz "babble" and vague vision flutterings are commonly due to tuner failure or a.g.c. faults. First check that the 20V supply is present across 3C48 – it's derived from the line output transformer. Then check the d.c. voltages in the a.g.c. and i.f. circuits – as a quick check, override the a.g.c. voltage on 3C4. The probable cause of the trouble is failure of one or other of the transistors (3VT2/3) in the a.g.c. circuit or the associated diode 3D3.

### **TANDBERG CTV2-4 CHASSIS**

The power supply is running at a low, clearly audible, frequency, and is producing very low outputs. There's no sound or raster of course.

The switch-mode power supply goes into this "purring" mode when an overload is present. This is usually due to leakage in the field output transistors Q806/7 or an overloaded line output transformer. To check for the latter condition, disconnect the tripler and shift choke L752 one at a time, switching on to see whether the overload has then disappeared. The line output transformer or line output transistor Q751 could be faulty, but this is rare on these sets.

### **GRUNDIG 6011GB**

The cutout operates when the set is switched on. I've replaced the thyristors in the line output stage and checked the diodes and capacitors, but the problem is still present. Disconnecting the scan coils and the e.h.t. tray also made no difference.

This effect can be caused by some most unexpected components in the line timebase! Check the miniature chokes L501 and L515 which feed the gates of the two thyristors. You might find one open-circuit or dry-jointed. Check the associated components R501, R515 and C515, and ensure that there are no dry-joints at the tags of any of the wound components in the timebase. If necessary, check the tuning capacitors C516 and C518 by substitution.

### **THORN 3000 CHASSIS**

The problem is cramping at the top of the raster – it can't be removed by any adjustment of the field timebase controls. The regulated h.t. supply is present and correct.

First check C432 (250 $\mu$ F) which decouples the supply to the field output stage, then check the field output transistor VT424. C429 (16 $\mu$ F) in the damping network across the field output transformer is another possibility, also the field scan coupling capacitor C705 (400 $\mu$ F). The latter is mounted on the convergence panel.

### **BUSH TV161 SERIES**

I've had trouble with the small choke in the boost diode's anode circuit bursting into flames, though everything else seems to be in order. Unfortunately no details of the coil are given in the manual.

The choke's there to prevent parasitic oscillation and can be replaced with almost any small one, e.g. an RS 1A suppressor choke. It shouldn't burst into flames however! Check the PY88 boost diode, the boost capacitor 3C18, which is returned to chassis, and make sure that there are no blobs or burns around the PY88's anode connection (pin 9).

### **THORN 8000 CHASSIS**

The tuning knob has to be adjusted to obtain a picture whenever the channel is changed to ITV. Also the colour control has to be fully advanced to get a picture with reasonably good colour balance. The picture often changes to black and white, with loss of field lock – mainly on ITV.

First check that there's adequate signal from the aerial. If the fault proves to be in the set, the first suspect is the tuner. We've also known this trouble to be due to slight misadjustment of one of the traps at the input to the i.f. amplifier, or alternatively to misalignment of the vision detector coil L108. Don't adjust the traps without the full equipment specified in the manual.

### **GRUNDIG 3010GB**

There's an intermittent fault on this set. The picture is perfect when the set is first switched on, but after anything from five minutes to an hour the picture goes slightly out of focus, a misty band appears across it, and the top three inches of the screen go very dark with flickering. Turning the brightness control to maximum lightens the dark part, but of course the picture then can't be seen. The picture will sometimes return suddenly to normal if the set is left on for three hours or so.

We've traced this fault to C385 (10 $\mu$ F) which decouples the brightness voltage fed to the base of the black-level clamp transistor Tr385. Unfortunately however it could be due to a fault in any one of several semiconductor devices in the clamp and the luminance driver/output section. The use of a freezer aerosol and heat from a hairdryer should help localise the source of the trouble.

### **RANK A816 CHASSIS**

The initial problem was a narrow picture. Then the tube heater went out and a high-pitched whistle came from the vicinity of the line output transformer. Also the HT line is very low, with the dropper resistor getting hot. The sound is normal, and the line oscillator i.c. has been changed.

We suggest you change the flyback tuning capacitor 3C61 (2,200pF), which must be of the approved type. Unfortunately the line output transistor could also have been damaged. The c.r.t. heater is fed from a winding on the line output transformer.

## ITT CVC5 CHASSIS

There are various intermittent troubles with this set. For example loss of line sync at switch on and subsequent loss of signals with strange colour bands. The faults sometimes clear, a slight tap beneath the cabinet often helping.

The four tags which earth the line output transformer to its subpanel are probably dry-jointed. Clean them and resolder and your problems should be over.

## THORN 1400 CHASSIS

There are four separate pictures, equally divided, across the width of the screen. Can you explain the reason for this and the likely cause?

The reason for the display you describe is simply that the line oscillator is running at the wrong speed. The most likely culprit is the 30FL14 flywheel line sync d.c. amplifier valve. Other possibilities are the 30FL2 line oscillator valve, the timing capacitor C53 (250pF, silver mica), the flywheel

sync d.c. amplifier's anode load resistor R60 (56k $\Omega$ ), and the flywheel sync discriminator diodes W5/6.

## HITACHI CNP190

There's no colour for a quarter of an hour or so after switching on from cold, though there's a monochrome picture. The colour then slowly builds up until an excellent colour picture is present.

The first suspects are the initial chroma/burst amplifier transistor TR19 and C503 (10 $\mu$ F, 25V) which decouples its base bias. The a.c.c. amplifier, which biases the emitter of TR19, could also be responsible. The things to check here are the two transistors TR24/25 and the electrolytics C509 (1 $\mu$ F, 50V) and C511 (47 $\mu$ F, 16V). If these stages are in order, you will have to override the colour-killer and follow up whatever clues you obtain. This can be done by connecting an 18k $\Omega$  resistor between the 12V rail and terminal J on the power/signals board.

# TEST CASE

## 220

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

The saga started, as most do, with a telephone call. "A Bang and Olufsen colour set" the voice said, "with no picture at all, though the sound's there." It was a busy time, and to save the expense of a home call the customer agreed to bring the set to the workshop for attention. It turned up half an hour later, and proved to be a Beovision 3400. We were glad this was to be an 'inside' job – no picture on this complex hybrid set can be caused by many things, most of them expensive, while we'd much prefer practising our diagnostic skills in the well lighted and well equipped workshop than crouched behind the set in the chimney corner!

With the back off and the power on, the rustle of the e.h.t. build-up could be heard. Its presence was confirmed by bristling hairs on a hand held in front of the blank screen. The timebase and e.h.t. sections were probably o.k. therefore. Our next suspicion was that the c.r.t. was maybe cut off by excessive voltage at its cathodes. On checking this however a normal reading of 200V or so was obtained. Switch up two ranges on the meter and check the c.r.t.'s first anode voltages – pins 4, 5 and 13. Several hundred volts apiece, so no problems here. Maybe the grids had gone negative? A high-impedance voltmeter proved that each grid was reasonably close to the specified 100V. More and more puzzled, we found an e.h.t. meter and set about checking the focus voltage – complete absence of the focus supply can cut off the tube. 4.7kV was recorded – fiendish set! As the e.h.t. voltmeter was now to hand, we decided to confirm the e.h.t.

at the tube's final anode. Even with the set switched off, a spark leapt from under the plastic e.h.t. "flower" to greet the probe. Under running conditions, 24kV was recorded.

Ten minutes later there was a picture on that set and we were kicking ourselves. What had we overlooked? All will be revealed next month – plus another test case item.

## SOLUTION TO TEST CASE 219

– page 269 last month –

Our line driver stage last month (Thorn 3500 chassis) was failing to turn on the line output stage. We'd discovered that the waveform at the collector of the driver transistor was wildly incorrect – and remained so despite our replacing almost everything in the line driver stage. Disconnecting L505 in the line output transistor's base circuit made no difference either. Had we been wiser, we'd have realised that disconnecting L505 *should* have made a difference to the drive waveform – because of the loading effect of the line output transistor on the secondary of the driver transformer. In fact the cause of the trouble was simply that the line output transistor's base-emitter junction was open-circuit. We won't be caught out by that again!

Incidentally L505 and the associated 47 $\Omega$  resistor are fitted on the 3500 chassis only – on the smaller-screen 3000 version, the line output transistor's base is fed directly from the line driver transformer (though very early production used a two-transistor line output stage).

## QUERY COUPON

Available until 22nd April, 1981. One coupon, plus a 75p (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 323.

## TELEVISION APRIL 1981

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by Carlisle Web Offset, Newtown Trading Estate, Carlisle. Distributed by IPC Business Press (Sales and Distribution) Ltd., 40 Bowling Green Lane, London EC1R 0NE. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £10, Overseas £11 per annum payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# WMTV LTD. – THE TV PROFESSIONALS



## THE BEST DEAL IN TV'S

- ★ Britain's most reliable source of Quality T.V.'s.
- ★ Hundreds of working polished T.V.'s.
- ★ Full customer testing facilities.
- ★ Thousands of untested S/S Colour T.V.'s from **£10**.
- ★ Quantity deliveries arranged anywhere in Britain or the World.

### Special Deals

- ★ Mixed 25" 4 for **£30**
  - ★ GEC 19" 10 for **£100**
  - ★ BRC 26" 10 for **£250**
  - ★ Pye 691 22" 10 for **£120**
  - ★ PYE 205 22" 10 for **£199**
  - ★ Personal collection only
- All above prices are plus 15% V.A.T.*


RING 021-444 6464 FOR DETAILS OF QUANTITY DISCOUNTS

### MAIL ORDER TV's – Working Colour TVs supplied by Mail Order and fully tested before despatch.

- ★ BRC 22"/26" **£70**
- ★ BUSH 184 22" **£40**
- ★ BRC 8000 17" **£65**
- ★ BUSH A823 22"/26" **£60**

*Above MAIL ORDER prices include V.A.T. but please add £12 p & p/T.V. Set.*

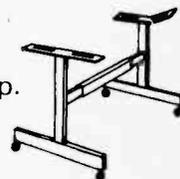- ★ New T.V. Stands.
- ★ Fully adjustable.
- ★ **£6.25** plus £1.75 p & p.
- ★ Quantity discounts.
- ★ Price inc. V.A.T.



## EXPRESS MAIL ORDER SPARES

### ★ Ex-equipment Panels

	Con	Power	Line	Decoder	Video	IF	Frame	Tripler	LOPTX
<b>RBM 823</b>	7.00	6.00	14.00	14.00	—	6.00	9.00	3.00	3.00
<b>BRC 3000</b>	6.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
<b>BRC 3500</b>	9.00	12.00	12.00	6.00	6.00	6.00	6.00	4.00	6.00
<b>GEC 2100</b>	6.00	—	—	8.00	6.00	6.00	10.00	5.00	5.00
<b>PYE 205</b>	6.00	—	12.00	8.00	7.00	6.00	5.00	5.00	7.00

Postage & packing **£1.25** Panels **50p** Triplers

### Ex-Equipment Valves

	Untested
ECC82	10
PCF80	10
PCF802	9
PCL82	10
PCL84	10
PCL85/805	9
PCL86	10
PFL200	10
PL36	10
PL504	10
PL508	18
PL509	30
PL519	40
PL802	—
PY500	20
PY800/81	10
PY801/88	10
30FL1/2	20

- ★ p & p paid but minimum order of £3.00 please.
- ★ Deduct 10% discount on orders over £20.00.

### Ex-Equipment Colour Tubes

All fully tested

17" (A44-271X)	<b>£18.00</b>
18" (A47-342X)	<b>£18.00</b>
18" (A47-343X)	<b>£18.00</b>
19" (A49-191X)	<b>£18.00</b>
20" (A51-120X)	<b>£25.00</b>
22" (A56-120X)	<b>£17.00</b>
25" (A63-200X)	<b>£10.00</b>
26" (A66-120X)	<b>£20.00</b>
26" (A67-120X)	<b>£17.00</b>

Please add £5.00 p & p per C.R.T.

### Equipment Spares

\*Always available

- ★ Colour and Mono Scan Coils **£1.50** + £1.00 p & p.
- ★ Tuners for all makes of Colour and Mono **£4.00** + £1.00 p & p.
- ★ Mono tubes fully tested. All Sizes – please state size on order **£3.00** + £4.00 p & p.
- ★ Reconditioned 50p meters **£92.00/Box of 10** incl. p & p.
- ★ PLESSEY SL918 colour ICs with circuit for substitution of SL917 **£2.00** + 25p p & p.
- ★ NEW VHF/UHF Varicap Tuners with circuit and full data **£1.25** + 75p p & p.

**WE ARE OPEN MON-SAT 9.30-5.45**

**PLEASE NOTE – ALL THE ABOVE MAIL ORDER PRICES INCLUDE 15% V.A.T.**

**WMTV LTD. 92 HIGH ST (A435) KINGS HEATH B'HAM B14 7JZ TEL. 021-444 6464  
021-444 2575**

# TV LINE OUTPUT TRANSFORMERS

by **FAST RETURN OF POST SERVICE**  
**PRICES INCLUDE P. & P. & 15% VAT**

## COLOUR TRANSFORMERS

DECCA	CS1730, 1733, 1830, 1835	} <b>£10.50</b> <b>RETAIL</b> <b>£9.00</b> <b>TRADE</b> <b>(Trade Orders only)</b>
DECCA	30 series Bradford Chassis	
DECCA	80, 100 series	
ITT	CVC 5 to CVC9	
ITT	CVC 20, CVC 30, CVC 32	
PHILIPS	G8, G9 Chassis	
PHILIPS	K80 (Rewind only - old unit required - £12)	

## WINDINGS

BUSH	Colour Hybrid quadrupler type	£6.00
RANK	T20A chassis	£6.00
PHILIPS	G6 EHT Overwind (exchange basis only)	£7.00
PHILIPS	G6 Primary	£5.00
PYE	691 to 697 EHT Overwind*	£3.00
PYE	691 to 697 Primary Winding*	£4.00
	*please state which	
EMO	90 degrees	£7.00

## MONO LOPTS

**Most British & Foreign makes supplied.**  
**£9.50 RETAIL £8 TRADE**  
 Separate windings also available.

## REWINDS

**Rewind Service Available**  
**Mono or Colour**  
**SAE all enquiries.**

Open Mon. - Fri. 9 to 5.30 pm Callers Welcome.

All lopts and windings are new and guaranteed for 6 months.

**PAPWORTH TRANSFORMERS**  
 80 Merton High Street  
 London SW19 1BE

Barclaycard and Access welcome



**01-540 3955**

# ARE YOU

## USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "**How to Deal Successfully in Used Colour Televisions**" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail - for both televisions **and** new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular updating service.**

You can start tomorrow - but you'll need our guide. The latest big illustrated edition is out now, and costs just **£4.95** - a small price to pay for financial independence!

### ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, DARLEY ABBEY MILLS, DERBY.

To: **Globus Industries Ltd., Unit 18, Darley Abbey Mills, Derby.**

Please send by return post "**How to Deal Successfully in Used Colour Televisions**".  
 I enclose cheque/p.o. for **£4.95**.

NAME .....

ADDRESS .....

.....

# Technical Training in Radio, Television and Electronics

Start training TODAY and make sure you are qualified to take advantage of the many opportunities open to trained people. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college has helped thousands of people to move up into higher paid jobs - and they can do the same for you.

Fill in the coupon below and find out how!

**There is a wide range of courses to choose from, including:**

### City and Guilds Certificates:-

Telecommunications Technicians,  
 Radio, TV and Electronics Technicians,  
 Electrical Installation Work,  
 Technical Communications,  
 Radio Amateur,  
 MPT General Radio Communications Certificate.

### Diploma Courses:-

Electronic Engineering,  
 Electrical Engineering,  
 Computer Engineering,  
 Radio, TV, Audio Engineering, Servicing and Maintenance. (inc. Colour TV)  
 New Self-Build Radio Courses with Free Kits.

### Colour TV Servicing

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study courses which are approved by a leading manufacturer.

### The ICS Guarantee

If you are studying for an examination, ICS will guarantee coaching until you are successful - at no extra cost.

POST OR PHONE TODAY FOR FREE BOOKLET.

I am interested in.....

Name .....

Address.....

..... Phone No: .....

**ICS** International Correspondence Schools,  
 Dept. 285F Intertext House,  
 LONDON SW8 4UJ. Tel 622 9911  
 (all hours)

## TV LINE OUTPUT TRANSFORMERS (ALL NEW AND FULLY GUARANTEED)

(Prices include VAT at 15%)

Discount to Trade Post and Packing 85p

RANK BUSH MURPHY	
Z146 A640 dual std mono	9.48
Bush A792, A793 single std mono	9.48
A774 single std mono	9.48
A816 solid state mono	10.43
Z712 T16a T16b mono portable	10.43
A823 A823b A823av colour	11.98
Z179 Z722 series colour	18.06
Z718 18" series	24.57
Z718 20" 22" 26" series	24.57
T20a T22 series colour	16.00

PYE	
169 173 569 573 769 series	9.26
RV293B 368 series	9.20
691 692 693 697 series colour	
Two types see below	
Wired in version	21.41
Printed circuit version	15.26
713 715 570 series colour	12.32
731 735 737 741 colour	10.10
725 colour	10.00

DECCA	
MS2000 MS2400 mono	6.80
MS1700 2001 2020 2401 mono	9.26
MS2404 2420 2424 mono	9.26
1210 1211 1511 portable	11.09
GYPSY portable	10.24
CS1730 1733 colour	10.00
CS1830 1835 colour	10.00
'30' series BRADFORD colour	10.00
80 series colour	10.00
100 series colour	10.00

FERGUSON HMV MARCONI ULTRA THORN	
950 mk2 1400 mono	8.50
1500 20" 1500 24" 1580 mono	8.50
1590 1591 1592 1593 mono	9.50
1612 1613 1712 mono	8.50
1690 1691 mono	11.85
1600 1615 series mono	14.64
3000 3500 EHT or SCAN	8.50
8000 8000a series colour	12.14
8500 8800 series colour	12.14
9000 series colour	12.14
9800 series colour	23.85

G.E.C.	
2000 to 2064 dual std mono	9.50
2047 to 2105 3112 to 3135	9.50
"GAIETY" FINELINE	9.50
2114 portable mono	9.50
3133 3135 M1501H portable mono	9.50
DUAL STD hybrid colour	11.59
SINGLE STD hybrid colour	11.59
SINGLE STD solid state 90° or 110°	10.00

TELPRO all models	10.00
TANBURG CTV 2-2 colour	10.00
NORDMENDE solid state	10.00
TELEFUNKEN 637 647	10.00
ZANNUSI	10.71

### WINDINGS

#### WIRED TO TAG PANELS

Post & Packing 40p

INDESIT	
20EGB 24EGB mono	9.90

RANK BUSH MURPHY	
Colour hybrid quadrupler type	5.60
T20a T22 Z719 Z722 Pry & Sec	6.83
Z718 series primary	5.60
Z718 series EHT overwind	7.20

PHILIPS	
170 series dual std mono	9.20
210 300 series mono	9.20
320 series solid state mono	10.00
G6 single std colour	19.88
G8 series colour	10.35
G9 series colour	10.35
G11 series colour	17.36

PHILIPS	
G6 eht overwind	7.20
G6 primary	4.60
KORTING hybrid series	7.60
WALTHAM 125 EHT overwind	3.00

KB-ITT	
VC2 to VC10 VC12 to VC100	9.20
VC200 VC205 VC207 mono	9.20
VC300 VC301 VC302 portable	9.20
CVC1 CVC2 colour	10.35
CVC5 CVC7 CVC8 CVC9 colour	10.35
CVC20 series colour	10.74
CVC30 CVC32 series colour	10.00
CVC40 series	15.90

PYE	
691 to 697 EHT overwind*	3.07
691 to 697 primary*	4.60
*Please state printed circuit or wired version	

GRUNDIG	
HYBRID 717 1500 3010 colour	12.57
5010 6010 5011 6011 6022	
2222	12.57
1510 2210 2252 5012 colour	12.57

FERGUSON HMV MARCONI ULTRA THORN	
8000 8000a primary	4.50
8500 8800 primary	4.50
8500 8800 EHT overwind	6.00

Contact your nearest depot for service by return.  
Callers welcome. Please phone before calling.  
If the Transformer you require is not listed please phone.

**Tidman Mail Order Ltd.,**  
236 Sandycombe Road,  
Richmond, Surrey.  
Approx 1 mile from Kew Bridge.  
Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm.  
1.30 to 4.30 pm.  
Sat 10 am to 12 pm.

**Hamond Components**  
(Midland) Ltd.,  
416, Moseley Road,  
Birmingham B12 9AX.  
Phone: 021-440 6144.

Mon-Fri 9 am to 1 pm.  
2 pm to 5.30 pm.

**LOOK!** Phone: LUTON  
BEDS. 38716

## OPPORTUNITIES TRADE SALES ALL SETS GUARANTEED COMPLETE OVER SIX HUNDRED SETS ALWAYS IN STOCK

Pye 20T, Philips G8;

Ferguson 3-3k5

Murphy, Bush, Decca, GEC

All from

**£35.00 £50.00**

Square Screen, Mono's from

**£5.00 ALL MODELS**

Sets for spares from

**£2.00**

All include VAT

## OPPORTUNITIES

9A, Chapel Street, Luton, Beds.  
LUTON 38716

9.30-6.00 p.m. Weekdays, 10.30-1.00 p.m. Sundays.

## TENREC

Tenrec Electronic Engineers Ltd  
502 Bearwood Road  
Warley, West Midlands  
021 429 8150

### Thorn 8000/8500 CTV's

Full working order from £65 + p.&p.

### LCD Watches

from £5.85 + £1 p.&p.

SAE for Complete List.

\*A31-410, 12" Mono Tube New. Special Price for Current  
A38-160W, 15" "Television" Feature: £19. P&P-£2.

Plenty of used colour panels working. S.A.E. for  
list. 50p p. & p.

Trade enquiries welcome

(All prices include VAT)

(T.I.)

## QUALITY TV's ALWAYS AVAILABLE

GOOD STOCKS OF MODERN COLOUR  
PLENTY OF SINGLE STANDARD MONO  
VERY COMPETITIVE PRICES  
COME TO THE BEST IN THE WEST

## TELETRADERS

ST. LEONARDS WAREHOUSE  
ST. LEONARDS ROAD, NEWTON ABBOT, DEVON  
Telephone: (0626) 60154

★ NEW ★

# COLOUR BAR GENERATOR

U.H.F. AERIAL INPUT PATTERN GENERATOR CPG6-RF

All Facilities of our PG6RF



## PLUS COLOUR BARS.

Produces 7 invaluable patterns.

**Robust, Battery Powered, Pocket Sized Unit,  
Plugs Straight into Aerial Socket.**

W H I T E	Y E L L O W	C Y A N	G R E E N	M A G E N T A	R E D	B L U E	B L A C K
-----------------------	----------------------------	------------------	-----------------------	---------------------------------	-------------	------------------	-----------------------

## FEATURES:

- ★ CROSSHATCH GRID
- ★ DOT MATRIX
- ★ VERTICALS
- ★ HORIZONTALS
- ★ WHITE RASTER
- ★ GREYSCALE
- ★ PLUS PAL COLOUR BARS;  
ONLY 3 SIMPLE ADJUSTMENTS.
- ★ PG6RF OWNERS; Buy Add-On 'C6' Unit!

## ORDER NOW!

PG6RF KIT £25.87 BUILT £33.35 – As per TV Review, Jan. 1979

C6 KIT £18.98 BUILT £26.45 – Add-on Colour to PG6RF

CPG6RF KIT £42.55 BUILT £63.25 – Both above combined.


These prices INCLUDE P & P and 15% VAT. Export VHF versions available.

In response to demand we have produced an add-on Colour Bar unit C6 to upgrade the PG6RF to PAL COLOUR. A MUST for TV construction or servicing! Available as a KIT or BUILT & TESTED. Kit includes all components and ready built modulator etc. Hundreds sold, reliable design.

Full 12 month guarantee on built units.

## MAIL ORDER ONLY

Quantity Discount  
on application

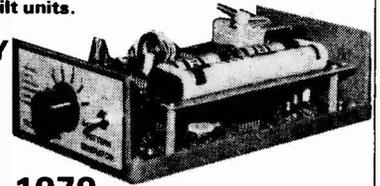

ACCESS  
ORDERS  
WELCOME

LOOK OUT, WE'VE MOVED. ORDER FROM:—  
**TECHNALOGICS LIMITED (DEPT. TV)**  
UNIT 2, TAYLOR ST., INDUSTRIAL ESTATE,  
LIVERPOOL, 5.

**PHILIPS "PRESTEL" 22" COLOUR T.V.**

FULLY REMOTE + TELETEXT

CLEARANCE OFFER PRICE **£695** (MODEL 708 PRESTEL)

OTHER TELETEXT COLOUR T.V. OFFERS

20"	22"	26"
<b>£359.95</b>	<b>£409.95</b>	<b>£459.95</b>

23 WILMSLOW ROAD,  
CHEADLE, CHESHIRE  
061-428-6367  
(Established over 30 years)

### RADIO/TAPES BARGAINS

LW/MW Mains/Battery Radios **£9.00** each (P&P £1.00).  
LW/MW Car Radios with Speaker **£9.00** each (P&P £1.00).  
Small VHF/MW Battery Radios **£7.00** each (P&P 50p).  
8-C60 High Gain Cassettes **£2.00** (P&P 50p).  
5-C90 High Gain Cassettes **£2.00** (P&P 50p).  
Stereo Headphones with Lead & Jack Plug **£4.50** (P&P 50p).

### AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

**B45** – for mono or colour this is tunable over complete UHF television band.  
**B11** – for stereo or standard VHF/FM radio.  
**B12** – for VHF television band 1 & 3.

**All amplifiers are complete and ready to use.**

Battery type PP3 or 8v to 18v dc, next to the set type fitting. Prices **£6.70 each.**

### SIGNAL INJECTORS

with (pre-set) variable AF, which emits RF harmonics into the UHF band. Protected up to 300 volts dc. Complete with leads **£5.70 each.**

All prices include VAT at 15%. P&P per order 30p. S.A.E. for leaflets. Access cards.

## ELECTRONIC MAILORDER LTD,

62 Bridge Street, Ramsbottom,  
Via Bury, Lancs. BL0 9AGT. Tel. Ramsbottom (070 682) 3036.

### REBUILT CATHODE RAY TUBES IN SOUTH WALES

## C.R.T. SERVICES

274 Chepstow Road, Newport, Gwent.  
Tel Newport 272005.

CURRENT PRICE LIST

A44-271X, A47-342X/343X	<b>£30</b>	470ERB22, 470FTB22	<b>£40</b>
A49-120X, A51-110X	<b>£30</b>	A51-161	<b>£40</b>
A56-120X, A56-140X	<b>£33</b>	A56-500X, 560HB22	<b>£43</b>
A63-120X, A66-120X	<b>£36</b>	A66-500X	<b>£46</b>
A66-140X, A67-120X/150X	<b>£36</b>		

Add 15% VAT to all prices.

Prices are based on a type for type exchange tube suitable for reprocessing.

**TWO YEAR GUARANTEE ON ALL TUBES**

## CARDIFF CENTREVISION

### EX RENTAL T/V's

---


\*In stock now. Philips G8 Thorn 3500

---

RBM twin chip and many others from **£15.00**  
Also Mono from **£2.00**

Large range of spares. Call and see our 4000 sq. ft. warehouse, you won't be disappointed.

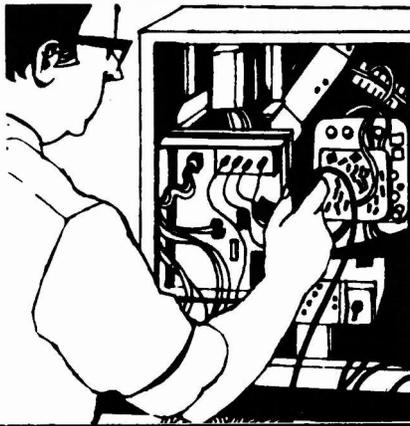Unit 2 corner of Penarth Road and Hatfield Road.  
Tel. Cardiff 0222 44754



**SETS & COMPONENTS**

TURN YOUR SURPLUS capacitors, transistors, etc. into cash. Contact Coles-Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

**T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG**

**TELEVIEW** 01-994 5537  
194, Acton Lane, London W.4.

EXCELLENT QUALITY USED COLOUR TV's CHOOSE UNTESTED OR FIRST CLASS WORKERS ENGINEERED IN OUR WORKSHOP.

**TELFURB T.V. LTD.**  
**WHEATLEY**  
**08677 3849**

**COLOUR T.V.s**

PHILIPS G8 COMPLETE

22" £55 26" £65

DISCOUNT FOR BULK BUYERS

TEL: 965 1230 & 961 3997  
**SMITH**

43-43A, PARK PARADE, HARLESDEN, LONDON N.W.10.

**SMALL ADS**

The prepaid rate for classified advertisements is 25p per word (minimum 12 words), box number 60p extra. Semi-display setting £4.80 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Television, Room 2337, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

**NOTICE TO READERS**

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

**IRELANDS LARGEST DISTRIBUTORS OF COLOUR AND MONO TELEVISIONS**

Mono from £1, Colour from £12. Delivery can be arranged. Working sets to order. NEW STOCK NOW ARRIVING WEEKLY, BUSH, PYE, FERGUSON, SKANTIC, GRUNDIG ETC. 1000 COLOUR TELEVISIONS NOW ON SHOW.

Special Offers:- Ferguson 1400 £4, Bush S/S £4, Bush D/S Minus Tuner £3, Bush 19" Colour 184 £12, Bush 22" & 26" Colour 2 I.C. and 1 I.C. Mixed £25, Low-Loss Co-Axial Cable 100m £11.30, 800 Watts Dimmer Switch £3.95, Set-Top Aerial £2, TV Stand £3, DV27 CB Antenna £4.90, Side Cutters £1.56, PY500A and PL509 £2 for the two. (All prices are for lots of 10).

**TELETRONICS, Radio and Television Wholesale Distributors**  
SESKINORE, OMAGH, CO. TYRONE. TEL: FINTONA 389 (STD 066 284)

**Southern Valve Co.,**  
2nd Floor, 8 Potters Road, New Barnet, Herts.

Tel: 01-440 8641 for current prices & availability. All popular valves stocked. NO CALLERS, SAE Lists. Cash with order. Same Day Postal Despatch. (Lunch 12.30-2pm.) Not Thurs.

Valves, Tubes, Aerials etc by LEADING-MAKERS. Send SAE Lists or Phone for current prices. Counter. NO COD. Speedy Despatch assured. No order under £1.

Philip Bearman, 6 Potters Road, New Barnet, Herts.  
Tel: 01-449 1934/5 (1934 Recording Machine).  
Closed Thurs. Please phone for opening hours.

**COLOUR PANEL EXCHANGE SERVICE**

BRC 3000/3500, 8000/8500  
GEC 2110 series  
Philips G8, G9 and G11

Three months guarantee on all Exchange Panels. Free delivery in London area.

Also Ex-Equipment Panels Thorn 3500 for sale.

All guaranteed Perfect Working Order.

Phone or send SAE for Catalogue.

**KAY JAY TV SERVICE,**

34, Clauson Avenue,  
Northolt, Middlesex.  
Phone 864-0350.

**20 AX & P.I.L. TUBE**

Colour Tubes.....from £25  
20 AX all sizes.....from £25  
Toshiba P.I.L. All Sizes.....from £20  
Top quality Regun 90°. All sizes.....£28

RING: JEFFRIES 01-845 2036

**TV PATTERN GENERATOR**

UHF output, plugs straight into aerial socket, provides cross-hatch and peak white and 8 bar grey scale. Size 100 x 75 x 40mm.

**£17.75**

price includes battery, P&P, and VAT.  
Further details of this and our other products on request.

C. L. JERVIS,  
15 Mercer Grove,  
Wolverhampton, WV11 3AN.  
TEL (0902) 736606.

**WERNETH**

ELECTRONICS LIMITED

FREEPOST.

P.O. BOX 9, MARPLE, STOCKPORT, CHESHIRE. SK6 6YE.

WERNETH ELECTRONIC PRODUCTS · WINNINGTON RD · MARPLE · STOCKPORT · CHESHIRE ·

**TUBE TEST INSTRUMENTS**

TX80 PROFESSIONAL £48.85  
TX50 LOW COST SERVICE TESTER £29.50  
TX50 COMPLETE KIT OF PARTS £21.00

**IN-CIRCUIT TRANSISTOR TESTER £15-60**

C.W.O. / S.A.E. for product details.

**CAMPBELL ELECTRONICS LTD.**

Distributors of specialist spares to radio and television service depts.

We stock semiconductors, I/Cs, special T.V. and audio spares, service aids, rebuilt CRTs etc.

Fast off the shelf delivery of stock items. Send S.A.E. or telephone for full catalogue and price list.

**CAMPBELL ELECTRONICS LTD.,**  
Unit 5, Heath Hill Estate,  
Dawley, Telford, Shropshire.  
Tel-Tophone Telford (0952) 502422.

**STS**

FOR QUALITY USED T.V.s

200 EX RENTAL COLOUR AND MONO TVs ARRIVING WEEKLY GOOD CLEAN CABINETS

Bush ★ Decca ★ GEC  
Pye ★ Philips ★ Thorn  
Grundig ★ Sanyo ★ ITT Etc

TROLLEY STANDS AND ALL SIZE REGUN TUBES.

DELIVERY IF REQUIRED

Call or phone now to:

**SOUTHERN TRADE SERVICES**  
21 COLINDALE AVE., LONDON NW9  
TEL 01-200-7337.

**LOOK!**

**THORN 3000/3500 & 8000 TRIPLERS**

High Quality Silicon Replacement Units  
T3500 only £4.95 inc. P.P. Add 74p V.A.T.  
T9000 only £5.45 inc. P.P. Add 82p V.A.T.

Quotes for 50+.

1 Year Guarantee

**WING ELECTRONICS**

15, Waylands, off Tudor Road, Hayes End, Middlesex.

**PLEASE MENTION TELEVISION WHEN REPLYING TO ADVERTISEMENTS**

# SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.  
Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBANDED TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAINS LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

## QUALITY REBUILT TUBES

HIGH TEMPERATURE PUMPING

COLOUR (2 year Guarantee)

90° up to 19"	<b>£32</b>
90° 20" - 22"	<b>£34</b>
90° 25" - 26"	<b>£36</b>
110° and PIL	<b>£38</b>

MONO (including thin necks) from **£12.**

All prices + VAT

Delivery UK Mainland £6.

4 year Optional Guarantee

Send or phone for full list and terms.

**WELTECH PICTURE TUBES**

Unit 3-10 Wembley Commercial Centre,  
East Lane, Wembley, Middx.  
01-908-1816

NEW PHILIPS 511 G6 SPARES. Pre-war onward valves, wireless. SAE: Sole, 37, Stanley Street, Ormskirk, Lancs L39 2DH.

# TELEVISION

# R A D E

## FREE WINE AND LOW LOW PRICES

YES we are giving away free bottles of wine with every £100 spent, PLUS our special **LOW LOW** price spring offers. You'll need the wine to celebrate your good fortune. Don't delay, call and see us, we will do you a **SUPER DEAL**, on the spot.

*(PS. Don't forget your cash)*

Most makes colour or mono with good cabinets

## GENERAL FACTORS

GOOD MOTORWAY ACCESS  
EXPORT ENQUIRIES

UNION ST, DONCASTER DN1 3AE  
TELEPHONE (0302) 49583-68416

WINE OFFER ENDS 30TH APRIL 1981

### CAMPBELL ELECTRONICS LTD. COLOUR T.V. PANEL EXCHANGE/ REPAIR SERVICE

THORN, RANK, PHILIPS, GEC,  
DECCA, TELPRO, GRUNDIG etc.  
90 Day Guarantee on all repairs - same  
day postal service.

Telephone Telford (0952) 502422  
for catalogue and price list.

CAMPBELL ELECTRONICS LTD.,  
Unit 5, Heath Hill Estate,  
Dawley, Telford, Shropshire.

### VALVE BARGAINS

BOXED & TESTED 30p EACH

ECC82, PFL200, EF184, PCF802, PCL84,  
PCL85/805, PCL86, PY81, PY800, PY88, PL36,  
PL504, 6F28, 30PL14, 30PL13.

COLOUR VALVES 65p EACH

PY500/A, PL508, PL509/519, PL802.

Postage & Packing 30p, no VAT

**VELCO ELECTRONICS**

9 Mandeville Terrace, Hawshaw, Via Bury, Lancs.

### TV DX.

High Quality, proven equipment supplied  
by an expert in the TV DX field.

**Band I/II tunable Mosfet preamplifier.**  
25dB gain. Very low noise/cross modulation  
figure. **£25.95.**

**Upconverter.** This is an ideal way to start  
TV DXing. The unit converts band I/III to  
UHF-A tuned RF stage ensures low noise  
and cross modulation, a feature which many  
models lack, 12V supply required. **£10.30.**

**Band I notch filter.** This attenuates the  
sound and vision frequencies of your local  
band I channel (please state which) whilst  
passing with low insertion loss the rest of the  
band. **£17.95.**

**Philips G8 selectivity modules.** One or  
two of these placed between the tuner and IF  
strip of your TV gives reduced bandwidth es-  
sential for serious DX work. **£1.50.**

**FM DX!** 88-108MHz tunable Mosfet pre-  
amplifier. Reduces local signal overload.  
**£25.95.**

**TV DX receivers** available. Please send sae  
for my product list to:

**H. COCKS,  
Cripps Corner,**

Robertsbridge, Sussex TN32 5RY.

Phone 0580 83317.

*The above prices include post/packing. Overseas enquiries  
welcome. Callers welcome. Please telephone first.*

## T.V.s FOR EXPORT

We have a selection of Bush and Ferguson  
colour T.V.s in good working order.

VHF/UHF suitable for countries using PAL  
system. We also supply The Home Market.

Write:

Tele Spares Ltd.,  
7 Walkinstown Road,  
Dublin 12, Ireland.  
Tel: Dublin 520485.

When replying to Television Classified Advertise-  
ments please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and  
despatching orders with the minimum of delay.

## SERVICE SHEETS

### 30,000 SERVICE SHEETS IN STOCK COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £1.25. Tuners £1.25. Tape Recorders, Record Players, Transistors and Stereograms + S.A.E. from £1.25 each except Colour TV Circuits £2. Car Radios from £1.25. All Radiograms from £1.25.

State if Circuit will do, if sheets are not in stock. All TV Sheets are full length 24 x 12, not in Bits & Pieces. All other Data full lengths. Free Fault Finding Chart or TV Catalogue with order. Crossed PO's Returned if Sheets Not in Stock.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882.

MAIL ORDER  
S.A.E.

JAPANESE TV service sheet specialists. Catalogue 25p plus S.a.e. Sandhurst Publications, 49C, Yorktown Road, Sandhurst, Camberley, Surrey.

SERVICE SHEETS from 50p and S.A.E. Catalogue 25p and S.A.E. Hamilton Radio, 47 Bohemia Road, St. Leonards, Sussex.

SERVICE SHEETS, Radio, TV, etc., 10,000 models. Catalogue 24p plus SAE with orders-enquiries. Telray, 154 Brook Street, Preston, PR1 7HP.

Thousands of different full size service sheets Thousands of different manuals of all kinds in stock.  
(Many of above are unique to us and obtainable nowhere else.)

Updated collection of British colour TV circuits/layouts etc. Contained in 3 huge binders - special price £39.50.

Updated foreign colour TV repair system for £22.50. (2 manuals, 1 binder) chassis from Grundig, Hitachi, Skantic, Luxor, Mitsubishi, Kuba, Zanussi.

Complete set of 10 unique TV repair manuals - only £49.50. Mono + colour from dual standards to latest models, McCourt & Tunbridge.

S.A.E. any quotation, also price lists, newsletter, bargain offers, details of our unique TV repair systems.

£1 + large S.A.E. any single service sheet.

Phone: 0698 883334, anytime. Callers 4-6 pm. weekdays, Saturday from 10 am.

# G.T.

## TECHNICAL INFORMATION SERVICE

76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

## SERVICE SHEETS. SERVICE MANUALS PRACTICAL AND TECHNICAL BOOKS

COVERING COLOUR & MONO TELEVISIONS, RADIOS,  
CASSETTES, MUSIC CENTRES, ETC.

SERVICE SHEETS £1.00 PLUS S.A.E. SERVICE MANUALS ON REQUEST.

### BOOKS

PRICES INCLUDE POSTAGE U.K. ONLY

TVT '79 TRANSISTOR EQUIVALENT & DATA BOOK. (A TO Z). 272 Pages .....	£3.50
TVT '79 TRANSISTOR EQUIVALENT & DATA BOOK. (2N. 2S. ETC.). 392 Pages .....	£4.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 1 .....	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 2 .....	£9.75
NEWNES COLOUR TELEVISION SERVICING MANUAL by G. J. King. Vol. 3 .....	£9.75
COLOUR TELEVISION SERVICING by G. J. King. 2nd Edition .....	£9.80
COLOUR TELEVISION THEORY by G. H. Hutson .....	£7.95
LONG DISTANCE TV RECEPTION FOR THE ENTHUSIAST by R. Bunney .....	£2.35
AUDIO EQUIPMENT TESTS by G. J. King .....	£7.50
RADIO CIRCUITS EXPLAINED by G. J. King .....	£6.50
SERVICING WITH THE OSCILLOSCOPE by G. J. King. 2nd Edition .....	£7.20
TELEVISION SERVICING HANDBOOK by G. J. King. 3rd Edition .....	£7.95
BEGINNERS' GUIDE TO TELEVISION by G. J. King. 5th Edition .....	£3.75
BEGINNERS' GUIDE TO COLOUR TELEVISION by G. J. King. 2nd Edition .....	£3.75
CATHODE-RAY OSCILLOSCOPE AND ITS USES by G. N. Patchett .....	£4.40
TELETEXT AND VIEWDATA by S.A. Money .....	£6.00
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR. 2nd Update .....	£10.35

### COLOUR TV MANUALS

COVERING FOLLOWING MAKES  
PLEASE SEND S.A.E. FOR QUOTATION

ALBA, BRC, BUSH, DECCA, GEC,  
DEFIANT, MARCONI, EKCO, PYE,  
FERGUSON, DYNATRON,  
NATIONAL, HITACHI, INVICTA,  
ITT/KB, RGD, GRUNDIG, SOBELL,  
STELLA, SONY, MURPHY,  
PHILIPS, HMV, ULTRA & OTHERS.

### VCR SERVICE MANUALS

We can supply Service Manuals for the most popular makes  
of Video Cassette Recorders. Please ring for a quote.

WE STOCK NEW AND SECONDHAND EDITIONS OF "RADIO AND TELEVISION SERVICING" BOOKS.  
FROM 1971-72 EDITION UP TO DATE. PRICES ON REQUEST.

BACK ISSUES OF FOLLOWING MAGAZINES AVAILABLE. CURRENT PRICE PLUS 25p POSTAGE PER COPY.  
P. WIRELESS, P. ELECTRONICS, E. ELECTRONICS, TELEVISION, ELECTRONICS TODAY, ELEKTOR

## BELL'S TELEVISION SERVICES

190, KINGS ROAD, HARROGATE, N. YORKSHIRE. TEL. HARROGATE (STD 0423) 55885

OPEN TO CALLERS DAILY 9.00 a.m. TO 5.00 p.m. (HALF DAY WEDNESDAY) PLEASE INCLUDE AN S.A.E. WITH ENQUIRIES

### VETERAN & VINTAGE

#### "SOUNDS VINTAGE"

The only magazine for all vintage sound  
enthusiasts packed with articles by top  
writers covering gramophones, photo-  
graphs, 78s, wireless, news, history,  
reviews etc.  
Bi-monthly. Annual subscription 16.60  
(annual extra). Send 75p for sample copy.  
28 Chestwood Close, Billericay, Essex

### AERIALS

ALMAG INDOOR T.V. AERIAL, new design all  
groups £2.50 + 50p P&P refundable. Murphy,  
6, London Road, Dalkeith, Midlothian.

### SITUATIONS VACANT

#### VIDEO T.V. TECH

Vacancy exists in electronics company based in  
Jeddah, Saudi Arabia. Suitably qualified and  
experienced persons please send C.V. to:

Mr. D. P. Varley, A.A.T.E.,  
POB 1215,  
Jeddah,  
Saudi Arabia.

#### WANTED

NEW VALVES and CRT's required, PCL805,  
PL504, PL509, PY500A etc. Cash waiting. Bearman,  
6/8 Potters Road, New Barnet, Herts. Tel:  
01-449 1934/5.

COMPLETE SLOWSCAN RECEIVING  
EQUIPMENT in good working order preferably  
AM/FM. Full details to P. Sado, Flat 28, 2,  
Mansfield Street, London W.1.

### BOOKS & PUBLICATIONS

COMPLETE FAULT GUIDES with circuits and  
step by step charts for Thorn CTV's 3K-8K-9K  
series. £4 each. Chassis type. Sandhurst Publications,  
49C Yorktown Road, Sandhurst, Camberley, Surrey.

ANY SINGLE SERVICES SHEET £1. L.S.A.E.  
Thousands different repair/service manuals/sheets in  
stock. Repair data your named TV £6 (with circuits  
£8). S.A.E. Newsletter, price lists, quotations. AUS  
(T), 76 Church Street, Larkhall, Lanarkshire.  
(0698 883334).

PLEASE MENTION  
TELEVISION WHEN REPLYING  
TO ADVERTISEMENTS

**PLANT FOR SALE**

**COMPLETE T.V. TUBE REBUILDING PLANT** for sale following company takeover. Inclusive all supplies. Technology, Installation Guidance and training available. Price by negotiation, around £5,000. Substantial enquiries only to: Inpholink Limited, Front Street West, Bedlington, Northumberland.

**FOR SALE**

**12 VIDICONS.** 1 Plumbicon 517 V.C.R. tube 1" Vidicon scan coils. Dual standard Video monitor chassis. Write: Rolls, 23 Brandreth Avenue, Dunstable, Beds.

**NEW BACK ISSUES** of 'Television' available 90p each post free. Cheque or uncrossed P.O. returned if not in stock. Bell's Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel: (0423) 55885.

**COLOUR TV PORTABLE PANELS.** UHF Varicap Tuner & Touchtune panel. Vis. & Sound IF, Spund output. Chroma Decoder on panel 250x200mm. Send Cheque/P.O. £17.50 to 'Vision On', 171 South Ealing Road, London W.5.

**VIDEOCRAFT TELETEXT DECODER.** Infrared control. Ready to insert in colour set. £100. Cheltenham 0242-23638.

**TEXAS TIFAX XM11 TELETEXT MODULE** with connection data. £50. Telephone Farnborough (0252) 516647.

**A SET OF BACK ISSUES** of 'Television' from 1974. £39 including postage. Heathkit oscilloscope and manual. £85. Delivery extra. Maldon (Essex) 740755.

**G.E.C. 2040 EX-TV PANELS** (over 100 available). All 100% complete and undamaged. Untested. I.F., Chroma. Sound. Timebase. Convergence £2.00 each, P&P £1 per order. K. Bailey, 40 Seymour Close, Selly Park, Birmingham 29.

**MISCELLANEOUS**

**RIGONDA AGENTS.** For all spares and repairs fast dispatch trade service available. 01-476 1928. Star Radio, 272 Barking Road, London E.13.

**COMBI/ANTUR LOPTX.** Genuine article small quantity available, SAE for details. M. J. Kyte, 11, Warminster Road, Westbury, Wilts.

**BURGLAR ALARM EQUIPMENT.** Latest Discount catalogue out now. Phone C.W.A.S. Alarm. 0274 682674.

**EDUCATIONAL**

**BETTER JOB!  
BETTER PAY!**

**GET QUALIFIED WITH ICS IN:  
COLOUR & MONO TV SERVICING  
COLOUR & MONO TV ENGINEERING  
COLOUR & MONO TV MAINTENANCE**  
PLUS: Telecommunications, radio, electronics, electrical engineering, technical communications, radio communications, etc., etc.,

**NEW: Self-build radio courses with free kits**

Train in your own home, in your own time with ICS, the world's most experienced home study college.

**RETURN THIS COUPON TODAY  
FOR FREE BROCHURE!**

**ICS** Int. Correspondence Schools  
284F Intertex House, Stewarts Rd.  
London SW8 4JJ. Tel: 01-622 9911

Name .....

Address .....

**TELEVISION  
COMPUTER & RADAR  
SYSTEMS SERVICING**

**TWO YEAR full-time Modular Diploma course to include a high percentage of practical work.**

- ELECTRONIC PRINCIPLES
- MONO TV & CCTV
- COLOUR TV & VCR
- DIGITAL TECHNIQUES
- COMPUTERS & MICROPROCESSORS
- RADAR

Each of the above Modules are 12 weeks in duration. Individual Modules can be arranged for applicants with suitable electronics background.

Tuition fees (UK & Overseas) £430 per Module. - Computer Module £500.

Next session starts April 21 st.

Prospectus from:

**LONDON ELECTRONICS  
COLLEGE**

Dept: TT, 20 Penywern Road,  
London SW5 9SU. Tel: 01-373 8721.

**ORDER FORM PLEASE WRITE IN BLOCK CAPITALS**

Please insert the advertisement below in the next available issue of Television for ..... insertions. I enclose Cheque/P.O. for £ .....  
(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)


NAME.....  
ADDRESS .....

Send to: Classified Advertisement Manager,  
**TELEVISION**,  
GMG, Classified Advertisement Dept., Rm. 2337,  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Telephone 01-261 5846.  
Rate  
25p per word, minimum 12 words, Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

# GENERAL INSTRUMENT

## MICROELECTRONICS

We are in the middle of a major expansion programme in Glenrothes, Scotland.

We are one of the world's leading Semiconductor companies with factories in the USA, Far East and the United Kingdom. Our strategic plans call for many new products and processes to be introduced in the near future. To help us grow as fast as we can, we are looking for the following people:

### APPLICATIONS ENGINEER

We are looking for a Qualified Engineer to assist our customers in Northern Europe in the design and manufacture of electronic systems using our semiconductor products.

Your job will involve working with our Sales Team to:

- Help customers evaluate and design with our products.
- Produce demonstration systems for new products.
- Provide Technical Support to our Distributors in UK, Scandinavia and Benelux.

You must be a Qualified or Chartered Engineer with a Degree or equivalent. You will get a good salary. You will receive in-depth technical training, plus an insight into the micro-electronics industry which will accelerate your learning and personal growth.

### INSIDE SALES ENGINEER

We are looking for a recent graduate or young engineer to help the Northern Europe Sales team, based in our London Office.

Your job will involve:

- helping customers with technical information
- liaison with our Distributors in UK, Scandinavia and Benelux
- co-ordinating Quotations via our Distributors and Sales Engineers
- preparation of statistics and Marketing information.

You will receive regular technical training. You will gain insight into the micro-electronics industry which will accelerate your learning and personal growth. According to your capabilities, this job can become a stepping-stone to becoming a Sales Engineer, Marketing Engineer, Applications Engineer or Micro-chip Design Engineer. This position carries a very competitive salary.

### SALES ENGINEER


We are looking for Sales Engineers to help sell our products to electronics companies in the UK. You will be responsible for co-ordinating our business in a number of key customers, plus sales to all other customers within a geographical area, both directly and via our Distributors.

You must have at least two years experience as a Sales Engineer within the electronics industry.

You will get a good salary and a company car. We operate a Bonus scheme which gives you high additional earnings if you meet your agreed targets. We will give you regular training, both in our products and as a manager of yourself and your business skills.

If you are interested in any of these jobs, and think you are suitable, please write for an Application Form to:

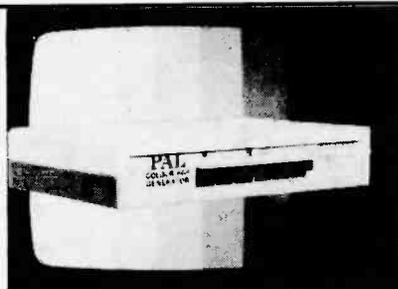**Rufus Greenbaum, Northern Area Manager,  
General Instrument Microelectronics Ltd.,  
Regency House, 1-4 Warwick Street, London W1R 5WB.**



N7118

## COLOUR BAR GENERATOR

- \* Now Available with Sound Modulator
- \* Built-in rechargeable battery PLUS Mains Unit.
- \* Push-Button operation selects: Colour Bars, Red Raster, Crosshatch, Grey Scale and Peak White.
- \* UHF or VHF Output, plus (optional) 1V P to P Video.

COMPARE OUR PRICE & SPECIFICATION AND SEE WHY HUNDREDS OF SERVICE ENGINEERS, BROADCAST ENGINEERS, UNIVERSITIES AND TECHNICAL COLLEGES, WORLD WIDE, CHOSE THE N7118.

### SPECIFICATION

Line frequency: 15.625 Hz  $\pm$  0.1%  
Field Frequency: 50 Hz  $\pm$  0.1%  
Interlace: 2:1  
Colour System: PAL  
Standard 75% Saturated, 100%  
Amplitude Colour Bars

### SOUND

Carrier frequency: 6 MHz or 5.5 MHz  
Modulation: 1 KHz Sinusoidal/Unmod.

### VIDEO

Output: 1V P to P Positive  
into 75 ohms

### EXTRACT FROM APRIL 1980 TELEVISION MAG.

"The N7118 was substituted for our Philips PM5509 and used for some weeks on all bench repair jobs. It worked well, providing over a millivolt of u.h.f. signal without any sign of modulator or receiver overload . . ." "This bar generator really came into its own in field servicing. The ten-hour capability of the internal battery last for many weeks of field servicing . . ."

PRICES	TOTAL
N7118 Kit £49.95 + VAT. & PP	£59.50
N7118 Built & Tested £75.00 + VAT & PP	£88.25
Sound Module (kit) £8.95 + VAT	£10.29
Sound Module (Built) £9.95 + VAT	£11.44
Video Module (kit) £8.95 + VAT	£10.29
Video Module (Built) £9.95 + VAT	£11.44

(Please add 58p Post & Packing if ordering sound or Video module, under separate cover)




**INTRACEPT**

**ELECTRONICS LTD., 203 Picton Road, Liverpool L15 4LG Tel: 051-733 3042**

**Authorised Distributor of Thandar  
Test Equipment.**

**THE VERY LATEST SC110 LOW POWER,  
FULLY PORTABLE OSCILLOSCOPE.**

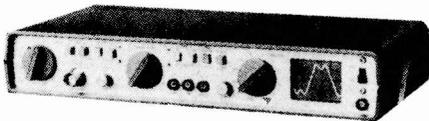The new Thandar SC110 represents a break-through in oscilloscope development. The SC110 is LESS THAN TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. Reviewed in 'Television' August 1980.



**1980 GOLD MEDAL** winner of the B.R.N.O. EXHIBITION, the largest Trade Fair held in Eastern Europe.

**Full Sized Performance**

- \* 10 MHz bandwidth.
- \* 10 mV per division sensitivity.
- \* Full trigger facilities are provided including TV frame, or TV filtering.
- \* Runs on 4 to 10V DC via disposable cells, re-chargeable cells, or AC adaptor.
- \* Size 255mm x 148mm x 50mm.

'Scope **£139.00** + £20.85 V.A.T.  
Carry case **£7.70** + £1.16 V.A.T.  
× 1 Probe **£7.00** + £1.05 V.A.T.  
× 10 Probe **£7.70** + £1.16 V.A.T.  
AC Adaptor **£4.95** + £0.74 V.A.T.

(Overseas purchasers please state voltage.)

Re-chargeable cells **£7.50** + £1.13 V.A.T.

World-wide post free service. Overseas orders welcome. Please deduct U.K. V.A.T. Mail Order only.

Barclaycard/Access orders welcome, Cheque/Bank draft etc., with order please.

Large S.A.E. for technical leaflet and complete Thandar list.

**B. K. ELECTRONICS, Dept. 'T',**

**38 Whitehouse Meadows, Eastwood,  
Leigh-on-Sea, Essex SS9 5TY.  
Tel: (0702) 527572.**

**N.G.T. COLOUR TUBES**

*First Independent Rebuilder with*

**B.S.I. CERTIFICATION**

*(Certificate No. 004)*

**2 year guarantee: 4 year option**

All Colour Tubes are debanded, high temperature pumped and rebanded using new adhesives and new tension band.

19" **£30**, 20" **£32**, 22" **£33**, and 26" **£38**.

*Exchange prices: add VAT at 15%*

**N.G.T. ELECTRONICS LTD.,**

**120, SELHURST ROAD., LONDON S.E.25**

**Phone: 01-771 3535.**

*20 years experience in television tube rebuilding.*

**EMO - EUROSonic - GRUNDIG - TELETON + ALL BRITISH MAKES  
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●**

**CREDIT AVAILABLE — TRADE ONLY**

Almost any TV Component supplied by return "off the shelf" e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc., etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY  
TV COMPONENT BY RETURN  
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

S.A.E. FOR FREE WALL CHART

**TELEPART (WTON) THE TELECENTRE, WORCESTER ST.,  
WOLVERHAMPTON (0902) 773122**

**TELEVISION TUBE  
SHOP**

**NEW TUBES AT CUT PRICES**

**EUROPEAN TYPE Nos.**

	Price £	VAT %
A28-14W.....	21.95	15%
A31-19W/20W.....	19.95	3.29
A31-120W/300W.....	17.95	2.99
A31-410W/510W.....	17.95	2.69
A34-100W.....	18.50	2.77
A38-160W.....	17.50	2.63
A44-120W.....	27.00	4.05
A50-120W.....	17.95	2.69
A59-23W.....	21.50	3.22
A61-120W.....	19.95	2.99

**U.S.A./JAP. TYPE Nos.**

9AGP4.....	21.82	3.27
190AB4/C4.....	23.00	3.45
230ADB4.....	28.50	4.28
230DB4/CT468.....	26.60	3.99
240AB4A.....	17.95	2.69
CT507 equiv.....	21.95	3.29
CT512.....	27.50	4.12
310DGB4/DMB4.....	23.00	3.45
310EUB4.....	19.95	2.99
310EYB4.....	18.75	2.81
310FDB4.....	23.50	3.52
310FXB4.....	17.50	2.62
310GNB4A.....	23.50	3.52
310HCB4.....	23.50	3.52
340AB4.....	22.50	3.38
340AYB4.....	30.00	4.50
340RB4/CB4.....	26.00	3.90
340AHB4.....	26.00	3.90

**Some Rebuilt Japanese  
& European Types  
Available from  
£14.00 + VAT £2.10**

**COLOUR TUBES**

**New and Mullard Colourex\***

12VARP22.....	62.50	9.37
330AB22.....	73.50	11.03
470FUB22B.....	97.50	14.63
A44-271X.....	65.00	9.75
A47-342X.....	69.50	10.42
A47-343X.....	69.50	10.42
A49-191X.....	59.50	8.92
A51-161X.....	67.00	10.05
A51-220X.....	64.00	9.60
A56-120X.....	58.50	8.77
A63-120X.....	69.50	10.42
A66-120X.....	65.00	9.75
A66-140X/410X.....	70.50	10.57
A67-120X.....	65.00	9.75
A67-140X/200X.....	69.50	10.42
A67-150X.....	75.00	11.25

**\*Old Bulb Required for Colourex\***  
ALL TUBES TESTED BEFORE  
DESPATCH & GUARANTEED  
FOR 12 MONTHS. 4 YEAR  
GUARANTEES AVAILABLE ON  
MOST TYPES

**CARRIAGE**

Mono £3.00 Colour £5.00

Mainland only. Overseas Rates on  
Application.

**TELEVISION TUBE SHOP LTD.**

**52 BATTERSEA BRIDGE RD.,  
LONDON, SW11.**

**Tel. 228 6859/223 5088**

# DISPLAY ELECTRONICS

**LEADERS  
IN TUBE  
TECHNOLOGY  
SINCE THE 60's.**

## REGUNNED COLOUR TUBES 2 YEAR GUARANTEE

Up to 19".....	£29.50
20".....	£31.50
22".....	£33.50
25".....	£35.50
26".....	£37.50

The above prices are for standard 38mm Delta Gun Types. Prices on application for P.I.L. Tubes etc. Some types available without pre-supply of glass at extra cost.

Carriage/Packing £5 up to 75 miles from works. £6.50 over. Please add 15% VAT

## REGUNNED MONO TUBES 2 YEAR GUARANTEE

20".....	£11.00
24".....	£13.00

Carriage/Packing £4.00 up to 75 miles from works. £5.00 over. Please add 15% VAT.

## BUDGET CORNER

Buy any 5 mixed types Cash 'n Collect - Take 20% discount.

**OR**

Buy any 5 Mono mixed sizes Cash 'n Collect at **£8.50** (20") and **£10** (24").

PLEASE ADD 15% VAT.

## CALLERS WELCOME

Late night Thursdays until 8pm  
Saturdays until midday.

N.B. Customers intending to collect orders are requested to telephone in advance:— even popular types may be out of stock for short periods.

## V.D.U./RADAR TUBES

Home and export enquiries for Radar Display Tubes manufactured from new (with phosphors to specification) are invited.

**WATERLOO ROAD,  
UXBRIDGE,  
MIDDLESEX**

Telephone: Uxbridge 55800

# STANDARD T.V. TUBE

**HIGH QUALITY COLOUR AND  
MONO-CHROME REPLACEMENT  
TUBES AT COMPETITIVE PRICES.**

- ★ Complete New Gun fitted to every Tube.
- ★ Two year Guarantee
- ★ Every Tube Electrically Tested.
- ★ Every Tube Picture Tested.
- ★ Supplier to Major Rental Companies.

18", 19"	£25
20", 22"	£27
25", 26"	£29

All prices quoted assume the return of your old glass rebuildable condition. Old CRT cash/cheque with order. Please add VAT at 15%.

**S.STANDARD TV TUBE CO.**  
11-29, Fashion Street,  
London E1

Tel. 01-247 3097

**BIRMINGHAM AND DISTRICT  
DEALERS/ENGINEERS**

# NEWS FLASH

**HIGH VACUUM  
QUALITY  
REBUILT TELEVISION  
PICTURE TUBES**

**COMPETITIVE PRICES**

**CONTRACT TERMS  
AVAILABLE**

**2 YEAR GUARANTEE**

17" 18" 19"	£31.00 + VAT £4.65
20"	£34.00 + VAT £5.10
22"	£36.00 + VAT £5.40
25"	£40.00 + VAT £6.00
26"	£43.00 + VAT £6.45

**PIL Tubes our speciality.**  
All Prices For Tubes available on a Sound "Glass for Glass" basis otherwise £20 surcharge

Built up to a standard  
not down to a price.

**TUBESURE LTD.**

Unit 111, Middlemore Industrial Estate,  
Middlemore Road, Smethwick,  
West Midlands. Telephone: 021-558 7777.

## TUBE REPLACEMENTS PROUDLY OFFER

**"WELLVIEW" EXCHANGE COLOUR**

A44-271X	£29
A47-342X	£29
A47-343X	£31
A49-120X	£29
A51-110X	£29
A51-110LF	£31
A55-14X	£33
A56-120X	£33
A63-120X	£38.50
A66-120X	£38.50
A66-140X	£38.50
A67-120X	£38.50
A67-150X	£38.50

**"WELLVIEW" EXCHANGE MONO**

A44-120 WR	£11
A47-26 WR	£12
A50-120 WR	£11
A59-120 WR	£12.50
A61-120 WR	£13.50
NEW A31-300 (18 months guarantee)	£15.00

All above plus VAT @ 15%.  
Carriage £4.50 inc. VAT.

**ALSO YOUR VALVE SUPPLIER  
NEW AND BOXED  
(inclusive of VAT)**

DY802=74p	ECC82=64p	EF183=78p
EF184=64p	PCC=72p	PCF802=98p
PCL82=78p	PCL84=92p	PCL805=97p
PFL200=£1.15	PCL86=97p	PL504=£1.38
PL509=£2.82	PL519=£2.92	PY88=70p
PY800=70p		PY500A=£1.52

Postage and Packing 10p per valve. All orders over £10 Free of charge.

## Colour Sets

1000 ex-rental TVs  
Good sets good prices  
Sets from £10 only  
Bush, Pye, GEC,  
Grundig, ASA, BRC,  
Philips, Shantic

The prices will amaze  
you.

**TUBE REPLACEMENTS**  
Unit No. 1, Monmouth St.,  
Bridgwater, Somerset.  
Tel. 0278 425690-722816

EHT lead for split diode LOPT. £1.00	<b>SPEAKERS</b> 5x3 80r or 50r. <b>50p</b> G9 70r. <b>£1.00</b> 5x3 35 ohm. <b>75p</b> 6x4 15 ohm. <b>£1.00</b> GEC 8 ohm. <b>70p</b> GEC 15 ohm. <b>70p</b>	<b>NEW SONY KV.1400.</b> Chroma Panel cost £60.00 <b>£10.00</b> Tuner unit <b>£3.50</b> Touch button unit with I.C. <b>£3.50</b>
7 push button unit VHF/UHF. £7.00	NE 2B6H 2 small neon lamps used in GEC. <b>3p</b>	<b>FRONT END FOR MUSIC CENTRE</b> VHF/MW/LW size 13x3 1/2". 4 push button unit, 7 transistors, V/condenser, 10 coils rod aerial I/C decoder CA 758E (no power supply and output stage). Circuit supplied. <b>£6.00</b> Output stage for music centre. <b>£6.00</b> Pre-amp panel 4 pots transistor etc. Plugs and sockets. <b>£1.00</b>
CVC 9 ITT Control panel. £4.00	Red and Green LED, 14 mixed. <b>£1.00</b>	Grundig 3000/3010, Seimens TVK 52. <b>£3.00</b>
CVC 20 ITT 6 push button unit & Input panel. <b>£5.00</b>	TLR 102 small red LED. <b>5p</b> 20 small red LED. <b>£1.00</b>	ITT LP 1174/NC. <b>£3.00</b>
Philips TV IF Modules 38 Mc/s 1st and 2nd IF. <b>£1.50</b>	<b>MAINS DROPPERS</b> Thorn 50R-40R-1K5 <b>50p</b> Thorn 6+1+100r. <b>35p</b> Pye 69+161. <b>40p</b> Pye 147+260r. <b>40p</b> (731) 3+56+27r. <b>50p</b>	<b>MULTI CAPACITORS</b> 1000 + 2000/35v. <b>25p</b> 2000 + 2000/35v. <b>30p</b> 2500 + 2500/63v. <b>50p</b> 470 + 470/250v. <b>40p</b> 150 + 200 + 200/300v. <b>70p</b> 100 + 200/325v. <b>40p</b> ELC1043 on panel for I.T.T. CVC 9. <b>£5.00</b>
3500 6 push button unit for Thorn 3500. Varicap <b>£1.00</b>	<b>CERAMIC FILTERS</b> 5.5 MHz. <b>15p</b> 6MHz. <b>25p</b>	175 + 100 + 100/350v to fit 3500 Thorn. <b>£2.00</b>
VARICAP F.M. TUNER Range 87.5 to 108MHz. <b>£2.00</b> (IF panel with circuit). <b>£2.00</b>	3.5mm Jack socket. <b>7p</b>	For T/V Sony Transformer & Lead & Sockets for earpiece. 8 ohms. <b>£1.00</b>
6 position 12.5KV Resistor Unit for varicap. <b>50p</b>	NPN/PNP 60v 5 amp/80w, pair. 660-661. <b>20p</b>	<b>THORN SPEAKERS</b> 1500 5 1/2 x 2 1/4 3 3500 7 x 3 80 1590 5 x 2 1/4 12 9000 7 x 3 16 3500 5 x 3 80 5 x 3 loudspeaker for GEC 15 <b>£1.00</b>
GEC IF panel (204C). <b>£7.50</b> I.T.T. (CVC 5) 7 push button unit for V/cap tuning <b>£7.00</b>	6 way ribbon cable, per metre. <b>20p</b>	UHF Modulator, CCIR. <b>£3.00</b>
New portable T/V chassis. Mono <b>£10.00</b>	TV XTALS 4.433; 610 KHz. <b>50p</b>	Circuit supplied. Flush mounting socket. FM/TV <b>35p</b>
New I.F. panel T/V 3 I.C. TBA 750 & SC950 MSC950 <b>3p</b> <b>4p</b>	6 volt 23 watt soldering iron. <b>£2.00</b>	ELC 1042. Mullard. <b>£6.50</b> ELC 1043/05. Mullard. <b>£6.00</b> Power supply 30V 1 amp Reg. <b>£2.00</b>
ELC 2000M New. <b>£7.00</b>	Infra-red emitting diode. TIL30. <b>20p</b>	Small DX Tuner V/cap 48-88 MHz and 175-220MHz automatic changeover. <b>£5.00</b>
GEC VHF/UHF 8CH touch tune units 41C 1xSN 29862N + 1xSN 16861NG + 2xCBF 16848N. <b>£5.00</b>	750 MFD 50V. <b>10p</b>	Thorn Transductor. <b>£1.00</b>
New circuit supplied. CVC panel with pots and main switches 250K, 100K, 423 500K. <b>£1.00</b>	<b>THERMISTORS</b> 200+200+75+25 4 fuse holder +2BY133+resistors. I.T.T. panel. CVC 9. <b>£1.50</b>	Transductor AT4041/07. <b>£1.00</b> 8 push button switch and 1 to 8 V/Ristor unit 21-68 CH. <b>£2.00</b> R2540. <b>£1.00</b> BUY 69 (RCA 1693). <b>£1.00</b>
New (NSF/AEG) UHF/VHF Varicap tuner units. Cost £10. only <b>£4.00</b>	ITT PT266 3W12 (Thermistor degausing) fits most sets. <b>15p</b> PTH451A or B. <b>20p</b> PT 37P. Fit Pye, Bush etc. <b>25p</b>	ROTARY. Min UHF T/unit for portable Mono T/V. <b>£4.00</b> Sound O/P. Thorn 9000. <b>£1.50</b>
Convergence panel for GEC 2040, 11 pots, 5 coils, 2 resistors etc. New. <b>£1.50</b>	H.T. thermistor neg. <b>35p</b> GEC 4700M/25v. <b>15p</b> 1000M/63v ITT axle. <b>15p</b> 22M/375v ITT. <b>20p</b>	PYE, GEC, THORN, PHILIPS, etc. 15K, 22K, 67K, 100K 40 turn pots for V/cap. <b>20p</b> 400M/400V. <b>40p</b> DL 50. Mullard. <b>£1.00</b> Thorn mains on/off switches. T/V. <b>20p</b> Focus units, I.T.T. etc. <b>80p</b> each
PYE 731 6 push button unit and 100KA pots. <b>£3.00</b>	THYRISTORS Philips G11. G122M. <b>60p</b> 5 amp/300v. <b>25p</b> 52600D 7 amp/400v. <b>30p</b> RCA 40506. <b>50p</b>	
New circuit supplied with UHF 8ch Light action unit 4 i/c for Varicap tuning GEC C2001/C2201. <b>£5.00</b>	PYE 22N4444/OT113/BT116. <b>85p</b> MR 501 3 amp/100v. <b>7p</b> MR 508 3 amp/800v. <b>12p</b> SCR 957. <b>65p</b> SP 8385 Thorn. <b>25p</b> ELC 1043 AEG. <b>£4.00</b>	
UHF Mullard 4 push button tuner unit. <b>£2.00</b>	PHILIPS SNIPS: CUTS MOST THINGS. <b>£1.50</b>	
ITT Control Panel with Mains lead, 4 slider pots, Mains filter. <b>£2.50</b>	CO-AX plugs. <b>12p</b>	
Bush Rank 6 push button Unit for varicap. <b>£2.50</b>	UHF Aerial socket and leads. PYE, ITT, THORN. <b>35p</b>	
4 push button unit (for Varicap Tuning) 20K. <b>50p</b>	AE Isolating socket. UHF and lead, PYE, THORN, ITT. <b>35p</b>	
4 pots and 6 push button unit for Varicap. Mains on/off switch + Mains filter. I.T.T. CVC 20. <b>£3.50</b>	Plug and socket 3+6 pin printed circuit type, pair. <b>10p</b>	
Philips T/unit UHF. <b>£2.00</b>	GEC aerial T/V socket & lead <b>35p</b>	
Transistor UHF units with Ae socket and leads. GEC 2000 rotary type. <b>£2.00</b>	GEC Mains and battery switch. Or stand by. <b>30p</b>	
Thorn UHF tuner unit and panel for 900 series. <b>£8.00</b>	B9A print V/holder. <b>5p</b>	
Thorn 900 frame panel. <b>£9.00</b>	PYE 697 long. <b>15p</b>	
Mullard VHF Tuner V/cap V314. <b>£5.00</b>	TV 11 <b>25p</b> TV 13 <b>25p</b> TV 18 EHT. <b>40p</b> TV 20. <b>50p</b>	
U321 T/unit V/cap. <b>£6.00</b>		
Thorn 3500. Thorn 8500 focus unit. Decca focus unit. Large or small. <b>£1.00</b> each		
4 push button unit. Thorn 1400/1500. <b>£3.50</b>		
4 push button for varicap with pots. <b>50p</b>		
Decca Bradford Tuner, 5 button (4 push). <b>£2.75</b>		
Line O/P Trans. CVC 20. <b>£5.00</b>		
12" TV tube Hitachi A31/300W. <b>£12.00</b>	100k 40 turn pots for V/cap tuning. G9-G11 & Thorn. <b>20p</b>	

# SENDZ COMPONENTS

63 BISHOPSTEIGNTON,  
SHOEBURYNNESS,  
ESSEX SS3 8AF.

Reg. Office only.

Callers by appointment only.

Add 15% VAT.

Add 50p P. & P.

Add postage for all overseas parcels

## VOLTS-OHMS-MILLIAMPERES MULTIMETER



£5.00

1K Ω/V on DC/AC

Equivalent	I.C.'s—cont.	Semiconductors—cont.	2N5983	30p	Various Mixed Packs
<b>EQ TCA 270 series</b>			2N6099	25p	20 Mixed Convergence Pots <b>£1.50</b>
CA270CE 50p	SN7630P 50p	BF127 20p	2N6348 50p		100 Mixed EHT Rectifier Sticks <b>£1.00</b>
CA270CW 50p	SN7650N <b>£1.00</b>	BF137 20p	2N6399A 30p		10 Thermistor <b>50p</b>
CA3089Q 50p	SN76532 50p	BF157 20p	2SK30A 7p		20 Slider Pots <b>£1.00</b>
	SN76533 <b>£1.00</b>	BF180 20p			30 Presets <b>50p</b>
<b>I.C.'s</b>	SN76544N <b>£1.00</b>	BF181 20p	TIP29C 20p		40 Pots <b>£1.50</b>
MC1327 <b>£1.00</b>	SN76546 No. 7 <b>£1.00</b>	BF182 20p	TIP29A 20p		300 Condenser <b>£1.50</b>
MC476P 50p	SN76550 15p	BF185 20p	TIP30A 20p		300 Resistor <b>£1.50</b>
MC1349 50p	SN76570 50p	BF195 7p	TIP31A/B 20p		150 Electrolytic <b>£2.00</b>
MC1352P 75p	SN76650N 50p	BF198 7p	TIP32 20p		15 bulbs <b>45p</b>
MC1748CPI 50p	SN76660N 50p	BF200 20p	TIP33B 10A/80V 25p		100 diodes <b>£1.00</b>
PUA758PC <b>£1.00</b>	SN76666N 50p	BF237B 7p	TIP41A-42 pair 50p		100 20mm fuses <b>£2.00</b>
S7246/N64100 <b>£5.00</b>	SN76707N 50p	BF240 7p	TIP100 30p		100 W/W resistors <b>£1.50</b>
SAA1020 <b>£6.00</b>	TBA820 <b>£1.00</b>	BF245A 7p	TIP2955.S 40p		25 for <b>50p</b>
SAA1021 <b>£5.00</b>	Touch Tune I.C. ML236E <b>£2.00</b>	BF263P 25p	NPN TIP130 60V/8A 25p		200 ceramic and plate condensers <b>£1.00</b>
SAA1024 <b>£4.00</b>	FT3055 20p	BF264 20p			2-7 meg & 4-7 meg 10% resistor 100. OFF <b>50p</b>
SAA1025 <b>£5.00</b>	Thorn 3500 A1 diodes 15p	BF273 7p	IN60 3p		300 Carbon film 1/2W 1R to 2M ITT <b>£1.50</b>
SAS560 <b>£1.00</b>	AD149 <b>£1.00</b>	BF274 7p	IN3899 50p		20 slider knobs <b>£1.00</b>
SAS570 <b>£1.00</b>	BZW70 6-2 10p	BF337 24p	IN4003 5p		1800/4KV 5p
SBA750B <b>£1.00</b>	BD116 25p	BF355 30p	IN4004 5p		4.7NF/5KV 10p
SL901 <b>£3.00</b>	*Denotes with heatsink.	BF234 PNP 7p	IN4005 5p		180PF/6KV 10p
SL918 <b>£3.00</b>		BF458 NPN 12p	IN4006 5p		210PF/8KV 10p
TAA320A 50p	<b>Semiconductors</b>	BF458T 12p	IN4007 5p		330PF/8KV 10p
TAA470 <b>£2.00</b>	AC128 5p	BFR79 15p	XK3123 4000 Thorne Diodes <b>£1.00</b>		1000PF/10KV 10p
TAA550 20p	AC153K 5p	BFT34 20p	IR106 40p		1200PF/12KV 10p
TAA570 <b>£1.00</b>	AC176K 25p	BFT43 20p	Y716 20p		6200PF/2000V 10p
TAA700 <b>£2.00</b>	AC187/8K pair 50p	BFY50 15p	Y827 30p		BYW56 1000V/2A BDX32 <b>£1.20</b>
TBA120A 40p	AF139 25p	BFY90 15p	1 amp/400V 20p		TIC126N Thyristors 800V/12A <b>65p</b>
TBA120AS 40p	AU113 <b>£1.25</b>	BR100 30p	1 amp/1600V 7p		<b>Sale Condensers</b>
TBA120B 40p	BA159 7p	BSS68 20p	3 amp/100V 7p		220/10 4.7/63
TBA120C 40p	BA182 7p	BSX20 5p	3 amp/300V 10p		330/10 33/63
TBA120SA 40p	BA248 7p	BSY79 7p	3 amp/1200V 7p		4700/10 47/63
TBA120SB 40p	BAV10 7p	BT100 30p	W04 bridge 15p		100/16 330/63
TBA120U 40p	BB103VHF 7p	BT106 30p	W005 bridge 25p		220/16 .01/100
TBA1441 <b>£1.00</b>	BB105UHF 7p	BT106 special 50p	ITT bridge 1 1/2 A C73 20p		160/25 33/100
TBA396 <b>£1.00</b>	BC107 7p	BT109 <b>£1.00</b>	3 amp bridge 25p		330/25 .47/160
TBA480Q <b>£1.00</b>	BC108 7p	BT116 <b>£1.00</b>	B30C 600A6 12p		470/25 2.2/160
TBA510 <b>£1.00</b>	BC109 7p	BT119 <b>£1.00</b>	B30C 500 12p		680/25 22/160
TBA520Q <b>£1.00</b>	BC116 7p	BT138/10A 70p	1 amp/100V 20p		33/35 47/250
TBA530 <b>£1.00</b>	BC139 7p	BT146 25p	NKT279, AC128 12p		10/40 1/250
TBA540 <b>£1.00</b>	BC142 15p	BT151/800R 70p	MC7724CP 40p		22/40 3.3/250
TBA550Q <b>£1.00</b>	BC147C 7p	BT1822 <b>£1.00</b>			47/40 10/250
TBA560CQ <b>£1.00</b>	BC148B 7p	BTT8124 <b>£1.00</b>	<b>Condensers</b>		8/300 8/300
TBA560Q <b>£1.00</b>	BC149C 7p	BTT8224 <b>£1.00</b>	4700/25 25p		.1/800 10p
TBA570 <b>£1.00</b>	BC154 7p	BTY80 20p	470/25 10p		.047/1000 10p
TBA625 <b>£1.00</b>	BC157 7p	BU105 50p	220/40 5p		.47/1000 30p
TBA641BX1 <b>£1.50</b>	BC158 7p	BU105/04 <b>£1.00</b>	1500/40 10p		.0047/1500 10p
TBA651 80p	BC171 7p	BU108 <b>£1.00</b>	1250/50 10p		2N2/1500 10p
TBA673 <b>£1.00</b>	BC171B 7p	BU124 50p	220/63 10p		.1/2000 15p
TBA720A <b>£1.00</b>	BC173 7p	BU126 <b>£1.00</b>	1000/63 15p		8 mixed gun switches <b>£1.00</b>
TBA750Q <b>£1.00</b>	BC173C 7p	BU137 60p	700/250 35p		
TBA800 40p	BC174 7p	BU204 40p	800/250 30p		
TBA810S <b>£1.00</b>	BC182L 7p	BU205 <b>£1.00</b>	4/350 5p		
TBA820 <b>£1 each</b>	BC183 7p	BU208 80p	8/350 8p		
TBA890 <b>£1.00</b>	BC183LB 7p	BU208A <b>£1.00</b>	22/350 8p		
TBA920 <b>£1.00</b>	BC207 7p	BU208A/02 <b>£1.00</b>	33/350 8p		
TBA920Q <b>£1.00</b>	BC212LT 7p	BU326 60p	400/350 50p		
TBA950 <b>£1.00</b>	BC213LA 7p	BU407 50p	33/450 10p		
TBA950Q <b>£1.00</b>	BC237B 7p	BU500 <b>£1.00</b>	220/450 50p		
TBA990Q <b>£1.00</b>	BC238 7p	CA270 50p	10/500 10p		
TCA270 <b>£1.00</b>	BC238A 7p	CA270EW 50p	33/500 10p		
TCA270SQ <b>£1.00</b>	BC245 7p	E1222 20p	.1/800 10p		
TCA4500A <b>£1.00</b>	BC250 7p	R2008B <b>£1.00</b>	.047/1000 10p		
TCA640 <b>£1.00</b>	BC251A 7p	R2010B <b>£1.00</b>	.01/1000 10p		
TCA650 <b>£1.00</b>	BC252C 7p	R2603 50p	.47/1000 30p		
TCA660 <b>£1.00</b>	BC257 30p	RC A16573 30p	.0047/1500 10p		
TCA740 <b>£1.00</b>	BC300 30p	OA90 7p	IN8/1500 10p		
TCA800 <b>£1.00</b>	BC303 30p	OT112 <b>£1.00</b>	2N2/1500 10p		
TCA830S <b>£1.00</b>	BC307 7p	MJESIT NPN 300V 4A 25p	.1/2000 15p		
TCE82 30p	BC308B 7p	MJE2955/15A 50p			
TCE120CQ <b>£1.00</b>	BC327 7p	MJE1661 25p			
TCE157 20p	BC336 20p	MJE2801 30p			
TCE527 20p	BC337 7p	BY127 10p			
TCEP100 <b>£1.20</b>	BC350 20p	BY133 10p			
TDA1170 <b>£1.20</b>	BC365 10p	BY176 type 25p			
TDA1190Z <b>£1.20</b>	BC413C 7p	BY176 50p			
TDA1327 <b>£1.00</b>	BC454 7p	BY179 35p			
TDA1412 50p	BC455 7p	BY184 25p			
TDA2540 <b>£1.00</b>	BC460 20p	BY187/01 10p			
TDA2640 <b>£1.00</b>	BC462 7p	BY190 40p			
TDA2690 <b>£1.00</b>	BC463 7p	BY204/4 7p			
TDA3960 7p	BC546 7p	BY206 10p			
SN1682AN <b>£1.00</b>	BC559 7p	BY210/400 7p			
SN16964AN 50p	BD124 <b>£1.50</b>	BY210/800 10p			
SN29764 <b>£1.00</b>	BD131 30p	BY233 5A/1500V 25p			
SN29848 50p	BD132 30p	BY226 10p			
SN75108AN <b>£1.00</b>	BD136 10p	BY296 10p			
SN76001 <b>£1.00</b>	BD207 30p	BY298 12p			
SN76003 <b>£1.00</b>	BD221 20p	BY299 10p			
SN76003* <b>£1.50</b>	BD228 25p	BYF3123 wire end 50p			
SN76008KE <b>£1.00</b>	BD238 20p	BYF3126 wire end 50p			
SN76013* <b>£1.50</b>	BD239 12p	BYF3214 20KV 50p			
SN76018KE <b>£1.00</b>	BD331 25p	BYX36/600 10p			
SN76023* <b>£1.50</b>	BD332 25p	BYX38/600 50p			
SN76033 <b>£1.00</b>	BD253B 35p	BYX55/350 10p			
SN76033* <b>£1.50</b>	BD416 25p	BXY71/350 25p			
SN76115 50p	BD561/2 pair 30p	2N390 7p			
SN76131 50p	BD595 35p	2N2222 7p			
SN76226 <b>£1.00</b>	BD596 35p	2N3055 35p			
SN76227 50p	BD681 25p	2N3566 7p			
Tuner Units Varicap and Mechanical repaired. Please ask for estimate.	BD807 10A/70V NPN 9 watt 25p	2N4355 7p			
		2N4442 60p			
		2N4444 <b>£1.00</b>			

# SENDZ COMPONENTS

63 BISHOPSTEIGNTON,  
SHOEBURYNNESS,  
ESSEX, SS3 8AF

Reg. Office Only.  
Callers by appointment only.

Add 15% VAT and 50p P. & P.

All items subject to availability.

Add postage for all overseas parcels.