

MAY 1983


Australia \$1.74; New Zealand \$2.00; Malaysia \$3.50; I.R. £1.33 (inc. VAT)

90p

# TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS

COLOUR  
PULL-OUT  
SUPPLEMENT

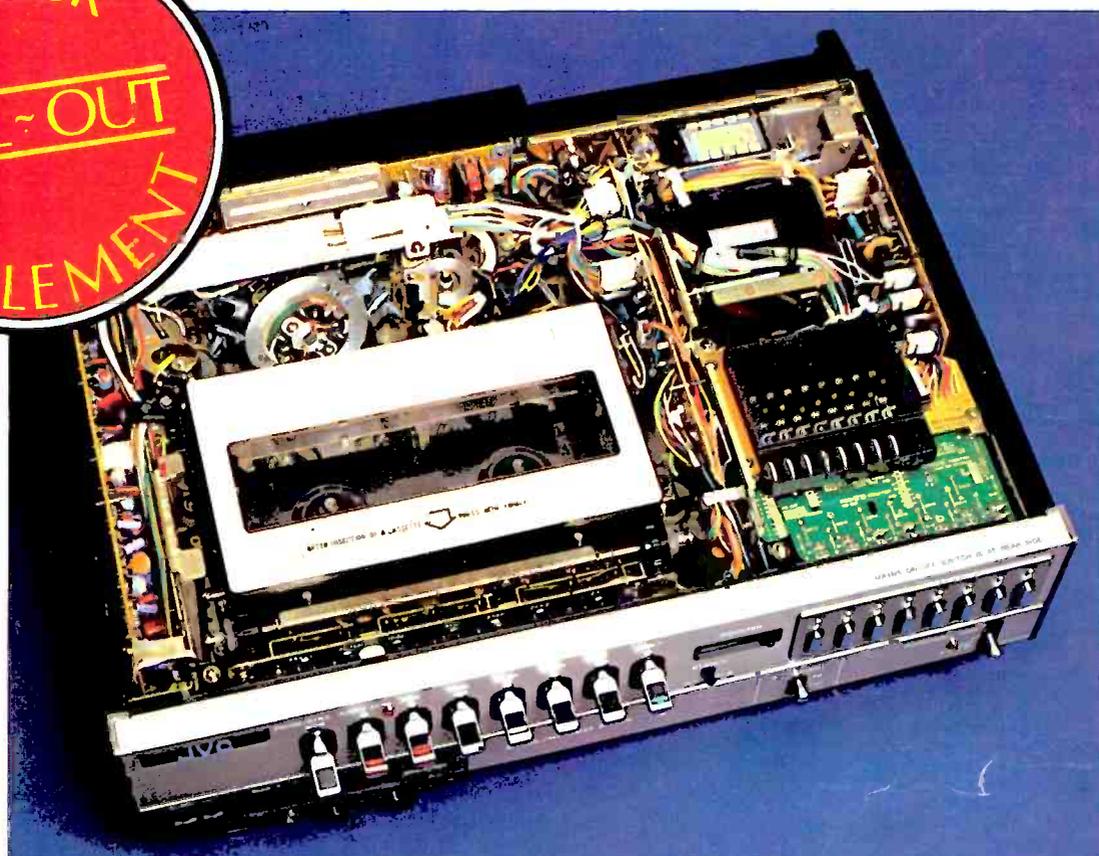

**ILLUSTRATED GUIDE  
TO VCR FAULT SYMPTOMS**

**EXPERIMENTAL 4GHz CONVERTER**

**ROUTINE TESTS:  
THORN 9000 CHASSIS**

**VCR CLINIC**

**NOVEL EHT SYSTEM**

**TEST REPORT**

# Interested in Television Servicing?

## Try a ZED Pack. Effect Repairs at Minimum Cost.

<b>Z1</b>	300 mixed ½ and ¼ watt and miniature resistors	<b>£1.95</b>	<b>Z20</b>	10 Assorted switches including: Pushbutton, Slide, Multiple, Miniature etc. Fantastic Value	<b>£1.20</b>	<b>Z44</b>	TO3 Mounting kits (BU208)	<b>8 for 60p</b>
<b>Z2</b>	150 mixed 1 and 2 watt resistors	<b>£1.95</b>	<b>Z21</b>	100 Assorted Silver Mica caps	<b>£2.20</b>	<b>Z45</b>	TO220 Mounting kits (TIP33)	<b>10 for 60p</b>
<b>Z3</b>	300 mixed capacitors, most types amazing value	<b>£3.95</b>	<b>Z22</b>	10 Mixed TV convergence Pots	<b>£1.00</b>	<b>Z46</b>	TO126 Mounting kits (BD131)	<b>12 for 60p</b>
<b>Z4</b>	100 mixed electrolytics	<b>£2.20</b>	<b>Z23</b>	20 Assorted TV Knobs including: Push Button, Aluminium and Control types	<b>£1.20</b>	<b>Z47</b>	Pack of each Mounting kit. All include insulators and washers	<b>£1.50</b>
<b>Z5</b>	100 mixed Polystyrene Capacitors	<b>£2.20</b>	<b>Z24</b>	10 Assorted Valve bases B9A, EHT, etc.	<b>£1.00</b>	<b>Z48</b>	3a 1000v Diodes (IN5408 type)	<b>8 for £1.00</b>
<b>Z6</b>	300 mixed Printed Circuit Components	<b>£1.95</b>	<b>Z25</b>	10 Spark Gaps	<b>£1.00</b>	<b>Z49</b>	Brushed Aluminium Push Button Knobs, 15mm long x 11mm Diam. Fit standard 3½mm square shafts	<b>10 for £1.00</b>
<b>Z7</b>	300 mixed Printed Circuit resistors	<b>£1.45</b>	<b>Z26</b>	20 Assorted Sync Diode Blocks	<b>£1.00</b>	<b>Z50</b>	Chrome finish 10mm x 10mm Diam as above	<b>10 for £1.00</b>
<b>Z8</b>	100 mixed High Wattage Resistors, wirewounds etc.	<b>£2.95</b>	<b>Z27</b>	12 Assorted IC Sockets	<b>£1.00</b>	<b>Z51</b>	Aluminium Finish. Standard Fitting Slider Knobs. (Decca)	<b>10 for £1.00</b>
<b>Z9</b>	100 mixed Miniature Ceramic and Plate caps	<b>£1.50</b>	<b>Z28</b>	20 General Purpose Germanium Diodes	<b>£1.00</b>	<b>Z52</b>	Decca "Bradford" Control Knobs	<b>10 for £1.00</b>
<b>Z10</b>	25 Assorted Potentiometers	<b>£1.50</b>	<b>Z29</b>	20 Assorted Miniature Tantalum Capacitors. Superb Buy at	<b>£1.20</b>	<b>Z53</b>	Black and Chrome. ¼" Shaft Tuner P/B Knobs, Black and Chrome. Fit most small Diam Shafts, ITT, THORN, GEC etc.	<b>8 for £1.00</b>
<b>Z11</b>	25 Assorted Presets, Skeleton etc.	<b>£1.00</b>	<b>Z30</b>	40 Miniature Terry clips, ideal for small Tools etc.	<b>£1.00</b>	<b>Z54</b>	Spun Aluminium Control Knobs (ITT) ¼" Shaft, suitable for most sets with recessed spindles	<b>8 for £1.00</b>
<b>Z12</b>	20 Assorted VDR's and Thermistors	<b>£1.20</b>	<b>Z31</b>	5 CTV Tube Bases	<b>£1.00</b>	<b>Z55</b>	14 Pin DIL I.C. Sockets	<b>12 for £1.00</b>
<b>Z13</b>	1 lb Mixed Hardware, Nuts, Bolts, Selftappers, "P" clips etc.	<b>£1.20</b>	<b>Z32</b>	10 EY87/DY87 EHT bases	<b>£1.00</b>	<b>Z56</b>	16 Pin Quil I.C. Sockets	<b>12 for £1.00</b>
<b>Z14</b>	100 mixed New and marked transistors, all full spec. includes: PBC108, BC148, BF154, BF274, BC121L, BC238, BC184L and/or Lots of similar types	<b>ONLY £4.95</b>	<b>Z33</b>	20 x PP3 Battery Connectors	<b>£1.00</b>	<b>Z57</b>	16 Pin DIL TO QUIL I.C. Sockets	<b>10 for £1.00</b>
<b>(Z14A)</b>	200 Transistors as above but including power types like BD131, 2N3055, AC128, BFY50 etc.	<b>£9.95</b>	<b>Z34</b>	6 x Miniature "Press to Make" Switches, Red Knob	<b>£1.00</b>	<b>Z58</b>	22 Pin DIL I.C. Sockets	<b>10 for £1.00</b>
<b>Z15</b>	100 Mixed Diodes including: Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec.	<b>£4.95</b>	<b>Z35</b>	12 Sub Min S.P.C.O. Slide Switches	<b>£1.00</b>	<b>Z59</b>	B9A Valve Bases P.C. Type	<b>20 for £1.00</b>
<b>Z16</b>	20IN4148 Gen Purpose Diodes	<b>£1.00</b>	<b>Z36</b>	8 Standard 2 Pole 3 Pos Switches	<b>£1.00</b>	<b>Z60</b>	0.47Ω ¼ Watt Emitter Resistors	<b>40 for £1.00</b>
<b>Z17</b>	20IN4003/10D2	<b>£1.00</b>	<b>Z37</b>	4 x HP11 Batt Holders (2 x 2 Flat type)	<b>4 for £1.00</b>			
<b>Z18</b>	20 Assorted Zeners. 1 watt and 400 mw	<b>£1.50</b>	<b>Z38</b>	3.5mm Jack Sockets, switched, enclosed Type	<b>8 for £1.00</b>			
			<b>Z39</b>	100 Miniature Reed Switches	<b>£2.30</b>			
			<b>Z40</b>	100 Subminiature Reed Switches	<b>£4.20</b>			
			<b>Z41</b>	20 Miniature Reed Switches	<b>£1.00</b>			
			<b>Z42</b>	12 Subminiature Reed Switches	<b>£1.00</b>			
			<b>Z43</b>					

**V.C.R. BATTERY PACKS.**  
**HITACHI PORTABLE V.C.R. Nicad pack.**  
 Type VTBP60E **£20 each.**  
 Brand New and Boxed **3 for £50**

**THORN "VIDEOSTAR" 3V25/26 Nicad pack.** Type VA214. Also suitable for J.V.C. etc. These are untested units which contain 10 x "C" size (HP11) Nicads, which alone would cost in excess of £20. A Real Bargain at **£10 each 3 for £25**

**High quality COAX PLUGS,** silver plated pin, grub screw fixing. **5 for £1**  
**COAX COUPLERS** 5 for £1  
**COAX FLYING SOCKET** 3 for £1

**ELECTROLYTIC**

1µf 63v	20 for £1.00
1µf 350v	10 for £1.00
2.2µf 63v	20 for £1.00
4µf 350v*	10 for £1.00
22µf 16v	20 for £1.00
100µf 25v	20 for £1.20
160µf 25v*	20 for £1.50
330µf 25v	10 for £1.00
400µf 40v*	8 for £1.00
470µf 25v	10 for £1.00
470µf 35v	8 for £1.00
1000µf 35v	6 for £1.00

\* Axial. All others are Radial.

**CAN TYPES**

22µf 375v (3 pin)	50p
50µf 250v (3 pin)	50p
100+200 350v	£1.00
2000µf 100v	£1.00
1000µf 100v	60p
2,200µf 40v	60p
2,200µf 63v	70p
3,500µf 35v	50p
4,500µf 35v	60p
220µf 400v ITT/RBM	£1.00

**THEY'RE BACK**

We can now again offer our special TV BARGAIN PARCELS. These contain all manner of useful bits and pieces. Components, semiconductors, videogame boards etc. which we have accumulated over the past year and must clear as we need the space.

**5kg £9.95 10kg £14.95**

**"RIFA"**  
 0.1µ 1000v Flameproof **5 for £1.00**

**EHT DIODES**  
 Very small. 20kV 2.5ma. 30ma peak  
**50p ea. 3 for £1.00**

**R.B.M. USERS LOOK!**  
 No more messy soldering. 24 pin I.C. sockets for SL901 etc.  
**SPECIAL OFFER: 5 for £1.00 100 for £12.50.**

**SPECIAL OFFERS**  
 100 Assorted Polyester Capacitors. Mullard C296's and others  
 160v-400v only **£2.00**  
 100 Assorted Mullard C280's Cosmetic imperfections etc. **£2.00**  
 200 Mullard Miniature Electrolytics Cosmetic imperfections etc. **£2.00**  
**PACK OF EACH £5.00**

**12V BULBS** on leads. Suitable for most VIDEO RECORDERS.  
**90p each 3 for £2.50**

**BY127** Type diodes. Unmarked, untested, Approximately 90% o.k. **100 for £2.95**  
**AC128** untested **100 for £3.95**

**ZENER DIODES**  
 0v7, 2v7, 4v3, 4v7, 5v6, 6v2, 6v8, 7v5, 27v, 30v. ALL 400mw.  
 10 of one value **80p**  
 10 of each **£6.60**  
 1.3 watt, 12v, 13v, 18v  
 10 of one value **£1.00**  
 10 of each **£2.50**

**DIODES**

25 x IN4002	£1.00
100 for £2.50	
20 x IN4003	£1.00
100 for £3.00	
20 x IN4005	£1.50
100 for £5.00	
20 x IN4148	£1.00
100 for £2.50	
25 x IN4002	£1.00
10 x SK4E2/06 (600v 2a fast switching)	£1.00
12 x BY127	£1.00
8 x BY255 (3A 1000V)	£1.00
10 x BA158 (600v 400ma)	£1.00
IN5402 3a 200v	8 for £1.00
6A. 100V. Bridge Rectifier.	
Very small.	80p ea. 3 for £2.00

**I.C.'s**

CA270AE	£1.00	6 for £5.00
MC1327P	£1.00	6 for £5.00
TBA120SB	50p each, 5 for £2.00	
TBA820	£1 each, 6 for £5.00	
TBA810P	£1.00	6 for £5.00
555 Timer	30p	4 for £1.00
TAA 661B	£1.00	6 for £5.00
SN76660N	50p	5 for £2.00

**THORN SPARES**

"3500" Transductor	£1.20, 3 for £3.00
"3500" Focus Assembly with VDR	£1.50
"8500" Focus Assembly, Rotary type	£1.50, 3 for £4.00
"8500" 0022 2000V Line Capacitor	10 for £1.00
"1590/91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160µf 25v	20 for £1.50
"1500" Jellypot. L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"950" Can. 100 + 300 + 100 + 16µf	£1.00

**THYRISTOR CONVERGENCE POTS**

SS106 (BT106) 75p each	5Ω, 10Ω, 20Ω, 30Ω, 50Ω, 100Ω,
3 for £2.00, 10 for £5.50	200Ω, 1K. 8 of one type £1.00. 8 of each type £6.00.

**REGULATORS**

7812 12v 1a	3 for £1.00
7805 5v 1a	3 for £1.00

**MISCELLANEOUS**


BG100 tripler for CVC45 etc. **only £3.50**  
 Line output transformer for RBM823A **£4.25 each, 3 for £10.00**  
 ITT VC200 4P/B Transistor Tuner. Suitable for some Pye and Philips sets. 3 hole fixing **£2.75 each**  
 Decca Bradford Tuner. **£4.00 each, 4 for £12.00**  
 5 button type UHF Modulator UHF out Video in. Ch. 36. 2½" x 2" x ¼" complete with 9 foot coaxial lead and plug. With connection data **£3.00 each, 2 for £5.00**  
 GEC Hybrid 2040 series Focus Assembly with lead and VDR rod **£2.00 each, 3 for £5.00**  
 Convergence Panel for above. Brand new leads and plug. **£3.00 each**  
 GEC 2010 Transistor Rotary Tuner with AE, SKT, and leads **£1.95 each, 3 for £5.00**  
 Buch CTV 25 Quadrupler type Q25B equivalent to ITT TU25 3QK **£3.00 each, 2 for £5.00**  
 Focus VDR Rods 2½" x ¼". Suitable for GEC, Decca etc. **75p each, 3 for £2.00**  
 Grundig UHF/VHF Varicap Tuner for 1500GB, 3010GB. **£12.50 each, 3 for £30.00**  
 EHT Lead with Anode cap (CTV) suitable for split Diodes sets 1m long **60p each, 3 for £1.50**  
 EHT Cable **30p per metre, 10 metres £2.50**  
 Anti Corona Caps **3 for £1.00**  
 4.433 Mhz CTV Crystals **£1.00 each, 3 for £2.50**  
 Cassette Mains Leads. 7ft with fig 8 plug **60p each, 3 for £1.50**  
 6 MHZ sound filters, ceramic 3 pin "TAIYO" type **50p each, 3 for £1.00**  
 10.7 MHz Ceramic Filters "Vernitron" FM4 **50p each, 3 for £1.00**  
 PYE CT200 Control Knobs **8 for £1.00**  
 Cassette/Calc Leads. 2m long, figure 8 skt. to flat pin. American plug **60p each, 3 for £1.50**  
 3.5mm Jack Plug on 2m of screened lead **5 for £1.00**  
 Degaus VDRs. ¼" diam, for RBM etc. **5 for £1.00**  
 Mains Neons **10 for £1.00**  
 2k2 Screened Resistors. White ceramic, 9 watt, with fusible link. **8 for £1.00**  
 Philips G8 Transductor. **£1.20 each, 3 for £3.00**  
 E.H.T. Discharge probe, with heavily insulated handle, with lead and chassis connector. **60p each, 3 for £1.50**

**GEMINI ELECTRONIC COMPONENTS**  
 Dept. TV, The Warehouse, Speedwell Street, London S.E.8.  
 Please quote ZED code where shown. Send cheque\* or Postal Order. Add 60p P&P and 15% VAT.  
 \*Schools etc. SEND OFFICIAL ORDER. Allow up to 28 days for delivery. Most orders despatched same day.  
**ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8.**  
 Send large S.A.E. for list of Quantity, Prices and Clearance Lines etc.

# TELEVISION

May  
1983

Vol. 33, No. 7  
Issue 391

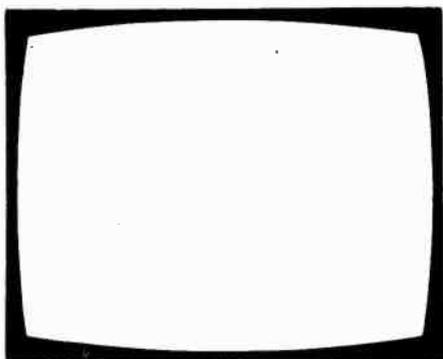

## COPYRIGHT

©IPC Magazines Limited, 1983, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

## SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

## BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

## BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 85p inclusive of postage and packing.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month

- 345 Leader**
- 346 Long-distance Television** *by Roger Bunney*  
Reports on DX reception and conditions and news from abroad. Also an initial investigation into the use of active aerials for DX use.
- 351 The Further Adventures of Tiny Tim** *by Les Lawry-Johns*  
All sorts of things are sent to try Tiny Tim. TV sets seem to be only a part of his troubles.
- 352 VCR Clinic**  
Reports on VCR faults and servicing from Mike Phelan, Richard Roscoe and Michael J. Cousins, T.Eng. (C.E.I.).
- 354 Fault Report**  
TV receiver servicing problems reported by Richard Roscoe, George R. Wilding and Mick Dutton.
- 356 Teletopics**  
News, comment and developments.
- 358 Test Report** *by Eugene Trundle*  
The Bi-Pak LOPT tester is unique in using a dynamic testing technique. It has been tried out on a wide variety of LOPTs, both good and dud, and also in-situ.
- 360 Vintage Video** *by David K. Matthewson, Ph.D., B.Sc.*  
A look at Baird's ideas on the subject of video discs - Phonovision. The discs were on sale for a short period in the early thirties.
- 361 A New EHT Circuit** *by George R. Wilding*  
When Telefunken came to design the 415/615 chassis they wanted to use the simplest possible LOPT. This led to the adoption of an interesting new e.h.t. rectifier arrangement.
- 362 Routine TV Receiver Tests** *by S. Simon*  
How to deal with the Thorn 9000 chassis, with its unique Syclops power/line output circuit.
- VCR Fault Guide**  
Colour supplement illustrating basic VCR fault symptoms. Photographs and text by Mike Phelan.
- 365 Frequency Counter-Timer, Part 2** *by Tony Jenkins, G8TBF*  
A start on the constructional details.
- 367 Next Month in Television**
- 368 Letters**
- 370 Experimental 4GHz Converter** *by Hugh Cocks*  
An experimental single-step converter for the 4GHz satellite band, featuring image rejection.
- 373 VCR Servicing, Part 17** *by Mike Phelan*  
Concluding the account of the mechacon panel in the Ferguson 3V23/JVC HR7700 VCR.
- 376 Service Bureau**
- 377 Test Case 245**

OUR NEXT ISSUE DATED JUNE WILL  
BE PUBLISHED ON MAY 18

# MANOR SUPPLIES

## NEW MKV CHEQUERBOARD & PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE.




- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£80.50**  
 Standard Case (10½" x 6½" x 2½") **£5.50**  
 De Luxe Case (10" x 6" x 2½") **£8.50**  
 Optional Sound Module (6MHz or 5.5MHz) **£4.50**  
 Built & Tested in De Luxe Case including Sound Module **£120.75**


SPECIAL TEST REPORT 'TELEVISION' DEC. 1982

Post/Packing £2.50  
 All above prices include VAT 15%

## PAL COLOUR BAR GENERATOR (Mk 4)

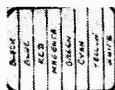

4TH SUCCESSFUL YEAR

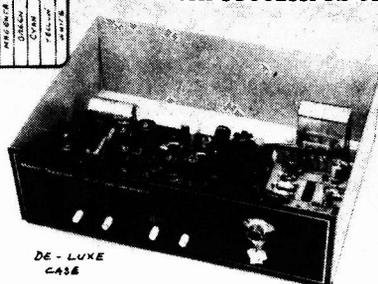

DE-LUXE CASE

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s. on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£34.50**. DELUXE CASE **£8.50**. BATT HOLDERS **£3.20** OR MAINS SUPPLY KIT **£4.80** (Combined P&P **£1.80**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£66.70 + £1.80 P & P**.  
 MK 4 DE LUXE (MAINS) BUILT & TESTED **£80.50 + £1.80 P & P**.  
 VHF MODULATOR (CHI to 4) FOR OVERSEAS **£5.50**.  
 EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

(ALL PRICES INCLUDE 15% VAT)

### MANOR SUPPLIES TELETEXT ADAPTOR KITS

MK 1 (Texas XMII) Cable remote control **£170.20** p.p. **£2.80**  
 MK 2 (Philips/Mullard) Infra-red remote control **£227.70** p.p. **£2.80**.  
 Further details on request.

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

## TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

### TELEVISION MAGAZINE PROJECT PARTS

NEW COLOUR PORTABLE TV  
 TV PATTERN GENERATOR SMALL SCREEN MONITOR  
 MONO PORTABLE TV LARGE SCREEN COLOUR TV  
 PHONE, CALL, OR SEND FOR LISTS  
 WORKING MODELS & PANEL TEST SERVICE AT  
 172 WEST END LANE.

SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND tested for T.V. SOUND & VISION **£32.80** p.p. **£1.20** (SUITABLE FOR USE WITH TELEVISION SIGNAL BOARDS).

TV SOUND IF PANELS, FULLY TESTED **£7.82** p.p. **£1.00**.  
 SPECIAL OFFER TEXAS XMII TELETEXT MODULE NEW & TESTED, AT REDUCED PRICE **£57.50** p.p. **£1.60**

PHILIPS-PYE G11 TYPE TELETEXT DECODERS **£34.50** p.p. **£1.60**.  
 TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE **£7.80** p.p. **£1.20**. XMII STAB. POWER SUPPLY **£4.40** p.p. **£1.20**.

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET **£12.65** p.p. **60p**. (ALUM CASE **£2.60** DE LUXE CASE **£5.50** p.p. **£1.20**).  
 ADDITIONAL GREY SCALE KIT **£3.35** p.p. **45p**.

UHF SIGNAL STRENGTH METER KIT **£21.60** (VHF version also available). ALUM CASE **£2.60** DE LUXE CASE **£8.50** p.p. **£1.80**.

CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO **£29.40** p.p. **£2.00**.

BUSH A823 POWER **£1.00** BASIC PCB. IN FIBREGLASS **£6.40** p.p.

BUSH Z718 BC6100 SERIES IF PANEL **£5.75** p.p. **90p**.

BUSH A816 IF PANEL (SURPLUS) **£1.90** p.p. **90p**.

DECCA "Bradford" T.B. POWER ex rental **£5.75** each p.p. **£1.40**.

DECCA 80, SERIES, IF FRAME T.B. **£5.75** each p.p. **£1.40**.

DECCA 80, 100 LINE T.B. salvaged **£11.50** each p.p. **£2.00**.

GEC 2110 Decoder, RGB panels (ex rental) **£5.75** each p.p. **£1.00**.

GEC 2040 DECODER PANEL **£2.88** p.p. **£1.60**.

THORN TX9 PANELS ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.75** p.p. **£2.00**

THORN TX9 PANELS salvaged ex factory for spares incl LOFT & mains transformers **£11.50** p.p. **£2.80**.

THORN TX10 T.B. PANELS salvaged ex factory for spares **£17.25** p.p. **£3.00**.

THORN 3000 LINE T.B., POWER PCB **£5.75** each p.p. **£1.30**.

THORN 8800 Varicap channel selector & front control unit **£4.37** p.p. **£1.80**.

THORN 8000/8500 IF/DECODER PANELS salvaged **£3.70** p.p. **£1.80**.

THORN 8000/8500 FRAME T.B. PANELS salvaged/spares **£2.88** p.p. **£1.40**.

THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET **£19.32** p.p. **£1.84**.

THORN 9000 IF/DECODER PANELS Salvaged **£5.75** p.p. **£1.60**.

PHILIPS 210, 300 Series Frame T.B. Panels **£1.15** p.p. **80p**.

PHILIPS G8/G9 IF/DECODER Panels for small spares **£1.75** p.p. **£1.40**.

G8 IF Panels for small spares **£1.15** p.p. **95p**.

G8 Decoder panels salvaged **£4.25**. Decoder panels for spares **£2.00** p.p. **£1.40**.

G9 Scan Panel. Basic PCB in fibreglass **£16.68** p.p. **£1.80**.

VARICAP, U321, U322, ELC 1043/06 ELC 1043/05 **£7.82** p.p. **80p**; G.I. type (equiv. 1043/05) **£4.00** p.p. **60p**. MAKERS VARICAP CONTROLS

Pye CT200 4PSN **£8.60**, A823 4PSN **£5.50**, Decca 6PSN **£6.70** p.p. **80p**.

SPECIAL OFFER ELEVEN POSITION VARICAP CONTROL UNIT UHF/VHF **£2.10** p.p. **£1.00**.

BUSH "Touch Tune" Varicap Control Z179, Z718 types **£4.40** p.p. **95p**.

VARICAP UHF-VHF ELC 2000S **£9.80**. BUSH TYPE **£7.82** p.p. **85p**.

VARICAP VHF MULLARD ELC 1042 **£7.95** p.p. **80p**.

UHF/625 Tuners, many different types in stock. DECCA Bradford 5 position **£2.88** p.p. **£1.80** etc.

LOPTS NEW & GUAR. P/P Mono **£1.35p**, Colour **£1.45p**, Bobbins **80p**.

BUSH 161 to 186 (twin panel) ..... **£6.80**

BUSH, MURPHY 774 series ..... **£9.80**

BUSH, MURPHY A816 series ..... **£9.80**

FERR. HMV, MARCONI, ULTRA 950, 1400, 1500, 1580, 1590, 1591 **£6.80**

THORN 1600, 1615, 1690, 1691 **£10.50**

GEC 2000 to 2038 series ..... **£7.80**

GEC series 1 & 2 ..... **£9.20**

INDEST 20/24EGB ..... **£8.80**

ITT/KB VC 200, 300 ..... **£8.80**

MURPHY 1910 to 2414 series ..... **£6.80**

PHILIPS 19TG 170, 210, 300 ..... **£8.80**

PYE, INVICTA, EKCO, FERR. 368, 169, 569, 769 series ..... **£8.80**

SPECIAL OFFER

DECCA 20/24, 1700, 2000, 2401 ..... **£4.40**

GEC 2114J/Junior Fineline ..... **£3.25**

PYE 40, 67 ..... **£2.00**

KB VC ELEVEN (003) ..... **£2.00**

KB VC1 ..... **£3.25**

R.B.M. A823 ..... **£5.60**

R.B.M. Z179 ..... **£11.30**

R.B.M. T20, T22 ..... **£11.30**

R.B.M. T20, T22 Bobbin ..... **£6.44**

DECCA Bradford (state Mod No.) ..... **£10.15**

DECCA 80, 100 ..... **£10.15**

GEC 2028 ..... **£5.60**

GEC 2040 ..... **£6.70**

GEC 2110 Series ..... **£12.20**

ITT CVC 5 to 9 ..... **£11.30**

ITT CVC 20 ..... **£11.30**

ITT CVC25, CVC30 series ..... **£10.15**

PYE 691-697 ..... **£11.50**

PYE 713, 715, 731 to 741 ..... **£7.85**

PYE 725 (90°) ..... **£10.60**

PHILIPS G8, G9 ..... **£10.15**

PHILIPS 570 ..... **£7.85**

THORN 3000/3500 SCAN, EHT **£7.85**

THORN 8000/8500/8800 ..... **£14.80**

THORN 9000 to 9600 ..... **£10.15**

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.TS.

TRIPLERS Full range available. Mono & Colour.

Special Offer: Thorn 1400 5 stick EHT Tray **£1.72** p.p. **65p**.

TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.72** p.p. **60p**.

6-3V CRT Boost Transformers **£5.80**, Auto Type **£3.20**, p.p. **£1.20**.

CALLERS WELCOME AT SHOP PREMISES Telephone 01-794 8751/7346

THOUSANDS OF ADDITIONAL ITEMS AVAILABLE, ENQUIRIES INVITED

LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

## MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door  
 W. Hampstead British Rail Stn. (Richmond, Broad St) (St. Pancras, Bedford)  
 W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

ALL PRICES INCLUDE VAT AT 15%

# BI-PAK BARGAINS

## TRIACS - PLASTIC

4AMP - 400v - T0202 - TAG 136G.	1 OFF	10 OFF	50 OFF	100 OFF
4p	£3.75	£17.50	£30.00	
8 AMP 400v - T0220 - TAG 425	8p	£5.75	£27.50	£50.00

## SLIDER POTENTIOMETERS ALL AT 50p

Plastic 40mm Travel Mono		PER PACK	
SX063 5 x 470 ohm Lin	SX067 5 x 47k Lin		
SX064 5 x 1k Lin	SX068 5 x 47k Log		
SX065 5 x 22k Lin	SX069 5 x 100 Lin		
SX066 5 x 22k Log	SX070 5 x 1 meg Lin		

SX400 250 Silicon Diodes - Switching like IN4148 DO-35. All good - uncoded. Worth double our price 45v 75mA	£1.25
SX411 250 Silicon Diodes - General Purpose, like OA200/202 BAX13/16 Uncoded. 30-100v 200mA DO-7.	£1.25

**OPTO 7-Segment Displays**  
Brand New 1st Quality  
**LITRONIX DL 707R 14-pin**  
Red 0.3" Common Anode Display 0-8 with right hand decimal point TTL compatible 5v DC Supply. Data supplied.

5 pieces £3 (8p each)
10 pieces £5 (5p each)
50 pieces £20 (4p each)
100 pieces £35 (3p each)
1,000 pieces £300 (3p each)

THE MORE YOU BUY - THE LESS YOU PAY

## BI-PAK'S OPTO 83 SPECIAL

A selection of Large & Small size LED's in Red, Green, Yellow and Clear, plus shaped devices of different types. 7 Segment displays, photo transistors, emitters and detectors.  
Types like MEL11, PPT100 etc. Plus Cadmium Cell ORP12 and germ. photo transistor OCP71. TOTAL OF 25 pieces.

O/NO: SX57A  
Valued - Normal Retail £12.00  
Our Price  
£5.00

## "IRRESISTABLE RESISTOR BARGAINS"

Pack No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/2 watt Carbon Resistors	£1
SX12	200	1/2 watt Carbon Resistors	£1
SX13	200	1/2 watt Carbon Resistors	£1
SX14	150	1/2 watt Resistors	£1
SX15	100	22 ohm-2m2 Mixed 1 and 2 watt Resistors	£1

Paks SX-12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 22 meg. Save pounds on these resistor packs and have a full range to cover your projects.  
\*Quantities approximate, count by weight.

## GUARANTEED TO SAVE YOU MONEY

SX27A 60 Assorted Polystyrene Bead Capacitors Type 9500 Series PPD	£1.00
SX28A 50 Assorted Silver Mica Caps 5.6pF-150pF	£1.00
SX29A 50 Assorted Silver Mica Caps 180pF-470pF	£1.00
SX30A 50 High Voltage Disc Ceramics 750V min up to 8KV. Assorted useful values	£1.00
SX31A 50 Wirewound 9 watt (arg) Resistors. Assorted values 1 ohm-12K	£1.00

**AUTO SCREWDRIER DRILL**  
Automatic spiral ratchet. Complete with 2 screwdriver blades, 5 & 6mm. 1 screwdriver cross point No. 1 & three drills - 2, 2.8 and 3.6mm - A MUST FOR ALL HOBBY-BUILDERS & CONSTRUCTORS. Order No. ASD/1 £3.50 each.

## 1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 - 500v - unidirectional - you select for VLTS. All perfect devices - NO duds. Min 50v. 50 for £1.00 - worth double ORDER NO SX76  
Silicon General Purpose NPN Transistors TO-18 Case Lock fit leads - coded CV7644. Similar to BC147 - BC107 - Z789 ALL NEW! VCE 70v IC500mA Hfe 75-250 50 off, 100 off, 500 off, 1000 off. PRICE £2.00, £3.00, £17.50, £30.00  
Order as CV7644  
Silicon General Purpose PNP Transistors TO-5 Case Lock fit leads coded CV9507 similar 2N2905A to BF730 VC 80, IC 600mA. Min Hfe 50 ALL NEW! 50 off, 100 off, 500 off, 1000 off. PRICE £2.50, £4.00, £19.00, £35.00  
Order as VC9507

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors	£1
SX18	100	Miniature Mixed	£1
SX19	100	Mixed Ceramics 1pf-5.6pf	£1
SX20	100	Mixed Ceramics 6.8pf-0.5mf	£1
SX21	100	Assorted Polyester/Polystyrene Capacitors	£1
SX22	60	Mixed C200 type capacitors metal foil	£1
SX23	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics	£1

\*Quantities approximate, count by weight.

## BARGAINS

SX391 20 x Large 2" RED LED	£1
SX42 20 small .125" RED LED's	£1
SX43 10 Rectangular Green LED's 2	£1
SX46 30 Assorted Zener Diodes 250mw-2 watt mixed voltages, all coded. New	£1
SX47 4 Black Instrument Knobs - winged with pointer 1/2". Standard screw. Fit size 29 x 20mm	50p
SX48 20 Assorted Slider Knobs. Black/Chrome, etc	£1
SX50 12 Neons and Filament Lamps. Low voltage and mains - various types and colours - some panel mounting	£1

SX52 6 Black Heatsink will fit TO-3 and TO-220. Ready drilled. Half price value. £1

SX53 1 Power finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design, pre-drilled TO-3 size 45mm square x 20mm high 40p  
SX54 TO-66 size 35mm x 30mm x 12mm 35p  
SX55 1 Heat Efficiency Power Finned Heatsink 80mm x 80mm x 35mm High. Drilled to take up to 4 x TO-3 devices £1.50 each

## IC SOCKETS The lowest price ever.

Pin	10 off	50 off	100 off
8 pin	95p	£3.90	£8.00
14 pin	95p	£3.75	£8.90
16 pin	95p	£4.00	£7.00
28 pin	£2.50	£11.00	£20



## VOLTAGE REGULATORS T0220

Positive +	Negative +
7805 - 50p	7905 - 55p
7812 - 50p	7912 - 55p
7815 - 50p	7915 - 55p
7824 - 50p	7924 - 55p


## SILICON BRIDGE RECTIFIERS

Comprising 4 x 1/2 amp rectifiers mounted on PCB.

VRM - 150 vts IFM - 1.5 Amps Size: 1 inch square

10 off £1.00
50 off £4.50
100 off £7.50

Order No. As:4R1  
BRect.

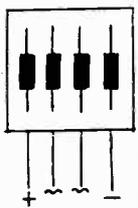

## SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq.Ins.	Price
FB1	4	9x2 1/2"	100	£1.50
FB2	3	11x3"	100	£1.50
FB3	4	13x3"	156	£2.00

## DOUBLE SIDED FIBREGLASS BOARD

FB4 2 14x4" 110	£2.00
-----------------	-------

## SILICON POWER TRANSISTORS - T03

NPN like 2N3055 - but not full spec 100 watts 50v min. 10 for £1.50 - Very Good Value 100s of uses - no duds Order No. SX90

# Time is Money!

We can save you both


**BI-PAK'S REVOLUTIONARY DYNAMIC "LOPT" TESTER**  
Immediately tells the condition of a suspect LOPT without desoldering or removal.

Guaranteed correct analysis in seconds saving you £££'s in Service Engineers TIME!

- \* Invaluable to all T.V. Engineers and unlike anything before.
- \* Small, compact, mains operated size 10 x 7.5 x 4cms.
- \* The D.T.T. is inductively coupled by two loose turns of the test lead around the yoke or over the overwind on the suspect line output transformer (as illustrated).
- \* The DYNAMIC TESTER will give a positive rapid test by giving E.H.T. at the overwind if the transformer is sound. If it is faulty then no E.H.T. will be given off and the transformer can be easily disconnected and replaced with confidence in only minutes.
- \* Designed by a T.V. Engineer and is wholly British Made. Comes complete with instructions. Fully guaranteed.
- \* 10-day satisfaction money-back guarantee BI-PAK will refund your cash in full should you not be completely satisfied and return the unit within 10 days of purchase.

Immediate despatch - Ring Cardholder Hotline 0820-3162 for same day despatch or send cash, cheque, P.O.'s etc. to:

**PRICE £36 each + V.A.T.**

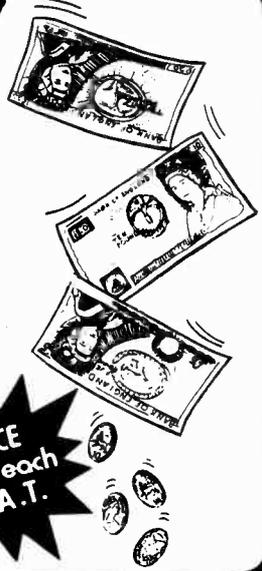

# BI-PAK

Send your orders to Dept 15 BI-PAK PO BOX 6 WARE HERTS SHOP AT BARNDDK ST WARE HERTS  
TERMS: CASH WITH ORDER. SAME DAY DISPATCH. ACCESS BANK/CARD ALSO ACCEPTED. TEL: 0920 319 030 388 2006  
ADD 15% V.A.T. AND 5p PER ORDER POSTAGE AND PACKING



Use your credit card. Buy us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add V.A.T. at 15% to your order.

# P. V. TUBES

Just phone your order through, we do the rest.



Telephone: Accrington (0254) 36521  
Accrington (0254) 32611

**SUPPLIERS OF TELEVISION COMPONENTS**

38A WATER STREET, ACCRINGTON, LANCS BB5 6PX.

**TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m.**

### INTEGRATED CIRCUITS

AN240	3.84	ML926	2.18	TA7074P	1.00	TBA120B	1.30	TCA940	1.95	TDA3560	6.00
AN214Q	3.91	ML928	2.18	TA7108P	3.43	TBA126SB	1.37	TDA440	2.20	TDA3950	2.30
AN7150	3.97	MRF475	2.50	TA7120P	2.43	TBA120U	1.05	TDA1002	1.95	TDA3960	2.95
CA555	4.6	MRF477	10.00	TA7129AP	3.76	TBA395	1.20	TDA1003A	5.50	UPC554	1.34
CA741	25			TA7130P	1.93	TBA396	80	TDA1004A	2.95	UPC1158H	90
CA748	45	MSN5807	7.87	TA7141P	95	TBA440N	2.50	TDA1006A	2.50	UPC1163-H	90
CA3065	1.80	PLL02AG	9.89	TA7193P	5.67	(TBA1441)	2.75	TDA1035	4.70	UPC1181H	1.62
LA4031P	3.21	MS1513L	2.80	TA7171P	1.85	TBA440P	2.50	TDA1044	4.37	UPC1186	90
LA4102	3.57	MS1515L	3.28	TA7172P	1.85	TBA480(Q)	1.50	TDA1170	3.00	UPC1212C	1.34
LA4250	3.57	SAS560	1.89	TA7173P	1.85	TBA510	3.00	TDA1190	3.50	UPC1230H	3.95
LA4400	3.05	SAS560S	1.80			TBA520Q	1.68	TDA1200	2.95	UPC1378H	4.49
LA4422	3.28	SAS570	1.89	TA7176P	2.50	TBA530(Q)	1.28	TDA1270	3.95	UPC1367	3.45
LC7130	5.93	SAS570S	1.80	TA7193P	5.67	TBA540	1.68	TDA1327	1.70	UPC566H	2.95
LC7120	5.87	SAS580	2.90	TA7202P	4.27	TBA550(Q)	2.34	TDA1352B	1.60	UPC575C2	3.40
LC7137	5.50	SAS590	2.90	TA7204P	3.77	TBA560Q	1.59	TDA1412	1.20	UPC1025H	2.95
LM1303N	2.63	SL901B	5.18	TA7205AP	3.72	TBA570	1.79	TDA2002	2.80	UPC1182H	2.95
HA1151	3.89	SL917B	6.50	TA7206P	3.40	TBA590	1.90	TDA2140	4.90	UPC1156H	4.25
MC1307	1.98	SL1310	1.80	TA7220P	6.40	TBA61BK1	3.50	TDA2190	7.70	UPC1350C	4.16
MC1310P	1.80	SL1327Q	1.20	TA7221P	2.52	TBA673	2.45	TDA2020	4.65	UPC1185H	3.86
MC1327	1.70	SL76544	2.05	TA7227P	5.58	TBA700	2.12	TDA2030	4.00		
MC1351P	1.90	SN76003N	2.49	TA7202P	5.98	TBA729AQ	2.64	TDA2521	2.17		
MC1330P	90	= SN76013N		TA7310P	4.78	TBA729Q	2.12	TDA2522	2.40		
MC1349	1.98	SN76023N	2.00	TA7609P	2.39	TBA750	2.98	TDA2523	3.40		
MC1350	1.50	SN76110N	1.15	TA7611AP	2.92	TBA800	1.62	TDA2524	2.25		
MC1351	2.83	SN76115N	2.27	TAA300	5.8	TBA810	1.10	TDA2530	2.70		
MC1352	1.75	SN76131N	2.00	TAA310	2.83	TBA810AS	1.35	TDA2532	2.45		
MC1358P	1.90	SN76226DN	2.00	TAA320	2.80	TBA820	1.70	TDA2540	3.84		
MC1495L	3.00	SN76227N	1.18	TAA350A	6.0	TBA890	3.94	TDA2541	3.84		
MC14011	66	SN76530P	1.47	TAA550	55	TBA920	3.00	TDA2560	3.30		
MC14049B	43	SN76532N	1.50	TAA570	1.99	TBA920(Q)	1.80	TDA2571	2.56		
ML231/RETBA6016	2.20	SN76533N	1.30	TAA630	3.50	TBA950	3.05	TDA2581	3.30		
		SN76033N	1.65	TAA621-AX1	3.00	TBA950(Q)2	2.40	TDA2590	3.25		
MC232	2.20	SN76544N	2.35	TAA8400S1	1.96	TBA970	4.09	TDA2591	2.95		
ML236	5.35	SN76650N	1.05	TAA700B	1.70	TBA990	1.90	TDA2593	2.95		
ML237B	2.96	SN76660N	80	TAA700	1.70	TBA1441	2.75	TDA2600	4.23		
ML238	4.20	SN76666N	80	TAA661B	1.20	TCA180	1.20	TDA2611A	1.95		
ML238B	6.00	STK435	9.06	TBA120A	70	TCA760	2.30	TDA2640	2.92		
ML239	2.50	SW153	2.74	TBA120S	70	TCA270SQ	2.50	TDA2680	3.15		
ML920	4.12	TA7050P	95	TBA120SA	70	TCA440	2.95	TDA2680A	3.40		
ML922	3.29	TA7051P	95	TBA120AS	1.37	TCA800	3.70	TDA2690	1.35		

### T.T.L. 74LS SERIES

74LS00	19	74LS37	19	74LS92	35	74LS160	60	74LS251	54
74LS02	19	74LS38	20	74LS93	35	74LS161	60	74LS253	1.00
74LS03	19	74LS40	20	74LS94	20	74LS162	60	74LS257	53
74LS04	20	74LS42	36	74LS95	27	74LS163	60	74LS258	67
74LS05	19	74LS44	80	74LS96	27	74LS164	65	74LS259	74
74LS08	19	74LS48	80	74LS97	11	74LS165	65	74LS273	80
74LS09	19	74LS49	80	74LS98	27	74LS166	65	74LS283	50
74LS10	19	74LS51	19	74LS99	19	74LS167	65	74LS293	70
74LS11	19	74LS54	19	74LS100	19	74LS168	65	74LS295	1.10
74LS13	37	74LS55	19	74LS101	46	74LS169	65	74LS302	1.54
74LS14	37	74LS56	28	74LS102	46	74LS170	65	74LS303	66
74LS15	19	74LS57	28	74LS103	46	74LS171	65	74LS304	36
74LS16	19	74LS58	28	74LS104	46	74LS172	65	74LS305	36
74LS17	19	74LS59	28	74LS105	46	74LS173	65	74LS306	36
74LS18	19	74LS60	28	74LS106	46	74LS174	65	74LS307	36
74LS19	19	74LS61	28	74LS107	46	74LS175	65	74LS308	36
74LS20	19	74LS62	28	74LS108	46	74LS176	65	74LS309	36
74LS21	19	74LS63	28	74LS109	46	74LS177	65	74LS310	36
74LS22	19	74LS64	28	74LS110	46	74LS178	65	74LS311	36
74LS23	19	74LS65	28	74LS111	46	74LS179	65	74LS312	36
74LS24	19	74LS66	28	74LS112	46	74LS180	60	74LS313	36
74LS25	19	74LS67	28	74LS113	46	74LS181	60	74LS314	36
74LS26	19	74LS68	28	74LS114	46	74LS182	60	74LS315	36
74LS27	19	74LS69	28	74LS115	46	74LS183	60	74LS316	36
74LS28	19	74LS70	28	74LS116	46	74LS184	60	74LS317	36
74LS29	19	74LS71	28	74LS117	46	74LS185	60	74LS318	36
74LS30	19	74LS72	28	74LS118	46	74LS186	60	74LS319	36
74LS31	19	74LS73	28	74LS119	46	74LS187	60	74LS320	36
74LS32	19	74LS74	28	74LS120	46	74LS188	60	74LS321	36
74LS33	19	74LS75	28	74LS121	46	74LS189	60	74LS322	36
74LS34	19	74LS76	28	74LS122	46	74LS190	60	74LS323	36
74LS35	19	74LS77	28	74LS123	46	74LS191	60	74LS324	36
74LS36	19	74LS78	28	74LS124	46	74LS192	60	74LS325	36
74LS37	19	74LS79	28	74LS125	46	74LS193	60	74LS326	36
74LS38	19	74LS80	28	74LS126	46	74LS194	60	74LS327	36
74LS39	19	74LS81	28	74LS127	46	74LS195	60	74LS328	36
74LS40	19	74LS82	28	74LS128	46	74LS196	60	74LS329	36
74LS41	19	74LS83	28	74LS129	46	74LS197	60	74LS330	36
74LS42	19	74LS84	28	74LS130	46	74LS198	60	74LS331	36
74LS43	19	74LS85	28	74LS131	46	74LS199	60	74LS332	36
74LS44	19	74LS86	28	74LS132	46	74LS200	60	74LS333	36
74LS45	19	74LS87	28	74LS133	46	74LS201	60	74LS334	36
74LS46	19	74LS88	28	74LS134	46	74LS202	60	74LS335	36
74LS47	19	74LS89	28	74LS135	46	74LS203	60	74LS336	36
74LS48	19	74LS90	28	74LS136	46	74LS204	60	74LS337	36
74LS49	19	74LS91	28	74LS137	46	74LS205	60	74LS338	36
74LS50	19	74LS92	28	74LS138	46	74LS206	60	74LS339	36
74LS51	19	74LS93	28	74LS139	46	74LS207	60	74LS340	36
74LS52	19	74LS94	28	74LS140	46	74LS208	60	74LS341	36
74LS53	19	74LS95	28	74LS141	46	74LS209	60	74LS342	36
74LS54	19	74LS96	28	74LS142	46	74LS210	60	74LS343	36
74LS55	19	74LS97	28	74LS143	46	74LS211	60	74LS344	36
74LS56	19	74LS98	28	74LS144	46	74LS212	60	74LS345	36
74LS57	19	74LS99	28	74LS145	46	74LS213	60	74LS346	36
74LS58	19	74LS100	28	74LS146	46	74LS214	60	74LS347	36
74LS59	19	74LS101	28	74LS147	46	74LS215	60	74LS348	36
74LS60	19	74LS102	28	74LS148	46	74LS216	60	74LS349	36
74LS61	19	74LS103	28	74LS149	46	74LS217	60	74LS350	36
74LS62	19	74LS104	28	74LS150	46	74LS218	60	74LS351	36
74LS63	19	74LS105	28	74LS151	46	74LS219	60	74LS352	36
74LS64	19	74LS106	28	74LS152	46	74LS220	60	74LS353	36
74LS65	19	74LS107	28	74LS153	46	74LS221	60	74LS354	36
74LS66	19	74LS108	28	74LS154	46	74LS222	60	74LS355	36
74LS67	19	74LS109	28	74LS155	46	74LS223	60	74LS356	36
74LS68	19	74LS110	28	74LS156	46	74LS224	60	74LS357	36
74LS69	19	74LS111	28	74LS157	46	74LS225	60	74LS358	36
74LS70	19	74LS112	28	74LS158	46	74LS226	60	74LS359	36
74LS71	19	74LS113	28	74LS159	46	74LS227	60	74LS360	36
74LS72	19	74LS114	28	74LS160	46	74LS228	60	74LS361	36
74LS73	19	74LS115	28	74LS161	46	74LS229	60	74LS362	36
74LS74	19	74LS116	28	74LS162	46	74LS230	60	74LS363	36
74LS75	19	74LS117	28	74LS163	46	74LS231	60	74LS364	36
74LS76	19	74LS118	28	74LS164	46	74LS232	60	74LS365	36
74LS77	19	74LS119	28	74LS165	46	74LS233	60	74LS366	36
74LS78	19	74LS120	28	74LS166	46	74LS234	60	74LS367	36
74LS79	19	74LS121	28	74LS167	46	74LS235	60	74LS368	36
74LS80	19	74LS122	28	74LS168	46	74LS236	60	74LS369	36
74LS81									

# P. V. TUBES

### REPLACEMENT ELECTROLYTICS

PYE 169 (200/200/100/32)	2.12
PHILIPS 320 (400/400/200V)	2.74
DECCA 30 (400/400/350V)	2.96
OECCA 80 (400/350V)	3.15
DECCA 100 (800/250V)	3.15
DECCA 1700 (200/200/400/350V)	4.83
PHILIPS G8 (600/300V)	2.21
PHILIPS G9 (600/300V)	2.21
PHILIPS G11 (470/250V)	2.90
PYE 691/7 (200/300/350V)	2.39
PYE 731 (600/300V)	2.31
RBM A823 (2500/2500/30V)	1.66
RBM A823 (600/300V)	1.26
RBM Z146 (300/300/350V)	3.15
RR1 T20A (220/400V)	2.00
ITT CVCS/9 (200/200/75/25)	2.47
ITT CVC 20 (220/400V)	2.00
GEC 2110 (600/250V)	1.94
GEC 2040 (1000/2000/35V)	1.19
GEC 2040 (300/300/150/100/50)	4.10
THORN 3500 (400/40V)	30
THORN 950 (100/300/100/16/275V)	1.83
THORN 1400 (150/100/100/150/320V)	2.79
THORN 1500 (150/150/100/300V)	2.01
THORN 1500 (12/300V)	31
THORN 1500 (1591/1691 4700/25V)	1.20
THORN 3500 (175/100/100/400/350V)	2.46
THORN 3500 (1000/63V)	65
THORN 3500 (1000/70V)	84
THORN 8000/8500 (2500/2500/63V)	1.54
THORN 8000/8500 (4700 P/C 25V)	1.20
THORN 8000/8500 (700/250V)	2.31
THORN 8000/8500 (400/350V)	2.56
THORN 9000 (400/400V)	3.05
GEC (200/200/150/50)	2.64

### ELECTRONIC TUNERS AND ASSEMBLIES

Mullard ELC1043/05	8.40
Mullard ELC1043/06	8.40
4 P/B DECCA/GEC/ITT	6.88
6 P/B DECCA/GEC/ITT	7.00
4 P/B PYE	9.00
6 P/B PYE	16.00
PHILIPS G8 Tuner	10.50
PHILIPS G8 Ass. (Square/Early)	13.50
PHILIPS G8 Ass. (Sloping/Late)	13.90
PHILIPS G9 Tuner	10.50
PHILIPS G11 Tuner	9.00
PYE 697 Repair Kits	6.97
ITT 6 way P/B with VCR	8.30
ITT/PYE/GEC 7 Button P/B	13.95
GEC 2110 6 way P/B	7.98
U321 UHF Tuner	7.50
THORN 8800 SELECTOR (HMV Model 2725/6 way round button)	11.40
THORN 9000 SELECTOR U322	7.20
HITACHI 4 way Chan. Selector (Also Rank A823)	10.75
RR1 T20A 6 way Chan. Selector	9.75
RR1 T20/22/26	11.00
PHILIPS 12 way TIP Switch Unit (suitable for all G11)	23.00
KT3 PHILIPS	14.50
KT30 PHILIPS	10.30

### FUSES

1 1/2" QUICK BLOW	Per type	Pack of 10
1Uma		70
250ma-500ma-750ma-1A		60
1.5A-2A-2.5A-3A-5A		60
1" ANTISURGE		1.60
250ma		1.70
500ma, 600ma, 630ma, 750ma, 850ma, 1A, 1.25A		2.50
1.5A, 2A		1.70
2.5A, 3A, 5A		2.50
20mm x 5mm ANTISURGE		4.80
80ma		2.40
100ma		2.20
160ma, 200ma		1.30
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.6A		1.80
2A, 2.5A		1.90
3.15A		1.89
20mm x 5mm QUICK BLOW		60
100ma, 250ma, 500ma, 630ma, 800ma		1.00
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A		1.00
1" MAINS		60
2A, 3A, 5A, 10A, 13A		1.00

### LABGEAR

CM7061 Power Unit 12V	10.70
CM7062 Reg Power Unit 12V	11.67
CM7060 MHA 10db 12V W/B	6.94
CM7065 VHF/AHF MHA W/B 12V	9.71
CM7067 UHF 12V MHA (Specify A-B or C/D)	13.03
CM7068 UHF 12V MHA High Gain (Specify A-B or C/D)	14.47
CM7053 Behind Set UHF Amp (Mains)	11.81
CM7054 Behind Set UHF Amp (Battery e.g. Caravans)	9.45
CM7043 Second Set Amp UHF	11.00
CM7093 Behind Set UHF Amp 3 Sets	13.86
CM7068 Dist. Amp. VHF/UHF 17db/output 12V 20.10	
CM7073 VHF/UHF 821 Dist. Amp.	39.24
CM9700 27mhz CB Suppress	3.88
CM6011 Outdoor Splitter (2 way) W/B	7.10
CM9003 Flush Single Outlet	1.34
CM9010 Flush Twin Outlet	1.78
CM9034 UHF Group Filters with DC Through Pass (state A/B/C/D)	6.90
CM6006 6 Way Passive Splitter	11.52
CM7042 TV Games Combin.	2.56
CM9009 Flush TV/FM Outlet	2.77
CM7069 Tri Star Amplified Set Top Aerial W/B 17.59	
CM7090 Amplified Caravan Aerial 12V DC W/B 15.52	
CM6038 UHF/VHF 625 Pattern Gen.	98.05
CM6052 UHF/VHF PAL Colour Bar Gen.	235.06

### CAPACITORS AXIAL

Volts	Mfd	Price
6V3	33	8
10V	22	8
	47	8
	100	10
	220	12
16V	470	20
	33	11
	68	14
	220	14
	1000	20
25V	10	8
	22	8
	47	10
	100	12
	220	14
	470	24
	1000	38
	2200	48
4700	80	80
40V	10	10
	22	10
	400	48
	5 pin-5 pin Audio Leads	95
63V	1	12
	2.2	12
	4.7	11
	10	11
	15	12
	22	13
	33	12
	47	19
	100	23
	220	37
	470	49
	1000	58
	2200	94
100V	10	13
	22	15
	47	20
	100	29
	220	35
450	1	33
	2.2	30
	10	30
	30	35
	65	35
	22	35
	33	35
	1	32
	10	32
500	1	35
600	1	35

### CONVERGENCE PRE-SETS

3 Watt complete with knob	
5R0-6R8-10R-15R-20R	
50R-100R-200R-500R	60

### METRIC CONVERGENCE POTS

PHILIPS G8	
5R-10R-20R-50R	35

### NEW PRODUCTS ASSTD.

Philips RGB 10G diodes	50
OR 39 3W resistors	60
Switch	2.80
Focus Unit	7.00
Focus Unit	2.70
Focus Unit	2.30
Philips Clock Radios (AS390)	21.39
Fluorescent Torch	6.50
5 pin-5 pin Audio Leads	95
Travel Plugs	3.50
Electrical Circuit Testers	1.50
Video Head Care Kit	3.50
L5 7" x 3 1/2" Speaker 15R	4.25
Ayr Teletext Adaptor	127.00
Battery Chargers Universal	6.75
Gen. Purpose Thyristors THY15/80	2.20
(many applications) THY15/85	
Diodes SKE 49/2/02	1.09
SKE 5F/3/10	1.19
SKE 4G/2/06	90
Video Heads VHS ("Universal")	38.00
Diodes Y723	1.30
Y827	1.42

### BATTERIES

RX6 - HP/NN1500	1.39
RX14 - SP11/HP11/NN1400	2.17
RX20 - SP2/HP2/NN1300	2.34
RX22 - PP3/NN1604	4.69

### VIDEO/AUDIO

VHS E30	3.06
VHS E60	3.66
Scotch E120 Video Tape	5.00
Scotch E180 Video Tape	5.13
BETA L500	4.90
BETA L750	5.80
PHILIPS VCC 240	5.93
PHILIPS VCC 360	8.30
PHILIPS VCC 480	10.21
Green Cassette Cases (Red/Blue/Green/Brown)	80
Scotch Audio Tape C90 Ferric	65
C90 Super Ferric	96

### PANELS + UNITS

AFC UNIT PHILIPS G8	8.82
IF GAIN MODULE (Pye/Philips)	9.00
CDA PANEL (Pye/Invicta/Ecko/Ovynatron)	20.00
REAR CONVERGENCE PANEL (Philips G8)	23.00

### SWITCHES

4A Double Pole On/Off Switch	
General Purpose Push/Push	66
Philips G8 Push On/Off Switch	1.38
4A Double Pole Rotary On/Off	66
A1 Beam Switch (THORN 3500)	70
A1 Controls 5m (THORN 3500)	89
GEC 2110 A1 Control IM5 (Red, Blue, Green)	58
GEC 2040 On/Off Switch	88
On/Off Switch G11/G12	1.58
On/Off Switch GEC/TCE TX9/10	1.06

### SUNDRY TUNER ACCESS.

RANK Tuner P/B	
1 1/2" x 3/4"	35
2" x 3/4" (yes we have some!)	35
2" x 1/2"	35
RANK Drive Cams	10
GEC 2110 Tuner Neons	14

### SUNORIES

Delay Lines DL60	2.20
OL700	2.20
OL50	2.20
EHT Final Anode Cap	53
EHT Cable	25p mtr.
63V CRT Boost Trans.	4.35
13A Plug Set box 12	4.80
Quick Set Adhesive	7.80
Moulded Plastic Hex. 6mm Trim	
Tools	10
Double End 4mm/8mm Trim Tools	20
Focus Rod	1.25
Focus Holder	2.00
Keynector Safe Block (mains)	5.50
Cassette Drive Belts per pack of 5	
44.5mm	1.65
64mm	1.71
74mm	1.70
57mm	1.65
89mm	1.90
Torch (handy for tool box)	42
I.C. Insertor	1.18
SM Neon Screwdriver	40
DIN Plugs 3 pin	22
4 pin	22
5 pin	20
180°	20
Stnd. 5 pin	20
Phono Plugs	12
Car Aerial Plug	18
2.5mm Jack Plug	14
3.5mm Jack Plug	14
Stnd. Jack Plug	20
Stereo Jack Plug	36
5A Connector Block (12)	40
Fuse Wire 5A-15A-30A	28
Battery Plug Thorn TV's	3.25
Gen. Purpose Power Supply 9V 200ma	
12V 200ma	
Mains Connector 4 way 13A	5.00

### MINIATURE SKELETON PRESET POTS

100R-220R-470R-1K0-2K2-4K7-10K-22K-47K-100K-220K-470K-1M0	15p each
---	----------

### STANDARD SKELETON PRESET POTS

100R-220R-470R-1K0-2K2-4K7-10K-22K-47K-100K-220K-470K-1M0-2M2-4M7	15p each
---	----------

### SLIDER POTENTIOMETERS

Lin or Log	
470R	65p
4K7	65p
1K	65p
10K	65p

### MIDGET CONTROLS

Insulated Spindle Length 44mm	
Log or Lin Without Switch	
5K-10K-25K-50K-100K-250K-500K-1M	39p
With D.P.S.T. Switch	
Log: 5K-10K-25K-50K-100K-250K-500K-1M, 2M	81p

### THERMAL CUT OUT

THORN 3000 2A Metal	1.60
THORN 8500 2.5 Plastic	1.60
GEC 2040 Metal	2.50

### MULTITURN POTS

100K	55
GEC TCE	55
PHILIPS G8	55
DECCA, RANK	55

### THICK FILM RESISTOR NETWORK

THORN 3500 (5 pin connection)	1.98
PYE 731 (6 pin connection)	2.20
THORN 9000 (Circuit Ref. R704/7)	1.98

### MINIATURE SKELETON PRESET POTS

Horizontal or Vertical	
100R-220R-470R-1K0-2K2-4K7-10K-22K-47K-100K-220K-470K-1M0	15p each

### STANDARD SKELETON PRESET POTS

Horizontal or Vertical	
100R-220R-470R-1K0-2K2-4K7-10K-22K-47K-100K-220K-470K-1M0-2M2-4M7	15p each

### SLIDER POTENTIOMETERS

Lin or Log	
470R	65p
4K7	65p
1K	65p
10K	65p

### MIDGET CONTROLS

Insulated Spindle Length 44mm	
Log or Lin Without Switch	
5K-10K-25K-50K-100K-250K-500K-1M	39p
With D.P.S.T. Switch	
Log: 5K-10K-25K-50K-100K-250K-500K-1M, 2M	81p

### THERMAL CUT OUT

THORN 3000 2A Metal	1.60
THORN 8500 2.5 Plastic	1.60
GEC 2040 Metal	2.50

### MULTITURN POTS

100K	55
GEC TCE	55
PHILIPS G8	55
DECCA, RANK	55

### THICK FILM RESISTOR NETWORK

THORN 3500 (5 pin connection)	1.98
PYE 731 (6 pin connection)	2.20
THORN 9000 (Circuit Ref. R704/7)	1.98

### EAGLE PRODUCTS

Please send large S.A.E. for full EAGLE Catalogue	
DF615 Full Range Speaker 6"	8.95
Multimetres	
KEW 7N 2.000 opv	5.25
KEW 20	14.50
EM5 5.000 opv	9.95
EM10 10.000 opv	11.50
EM20 10.000 opv	13.95
EM50 50.000 opv	19.95
EMC321 Carrying Case for above	44.50
Digital Meter TS1000	21.95
MM20 20.000 O.P.V.	25.95
MM50 50.000 O.P.V.	36.50
MM100 100.000 O.P.V.	45.00
MM125 100.000 O.P.V.	58.95
MM150 100.000 O.P.V.	1.20
T64 Test Leads	15.95
Case for MM100	6.95
T1206 2 Station Intercom	

### DATA BOOKS (No VAT)

Transistor Equivalent	
TVT 80 A-Z only 3.75	
TVT 80 2N/2S series only 4.00	
TVT 80/80 A-Z and 2N/2S together	7.50
LIN IC Books LIN 1	5.95
LIN 2	5.95


### DISC CERAMIC CAPACITORS

8KV (12Kv Wleg)	
39pF 200pF	each
150pF 220pF	30p
180pF 250pF	

### RECTIFIER TRAYS

THORN 950 MK II	4.25
THORN 1400 3 Stick	4.25
THORN 1500 3 Stick	4.95
THORN 1500 5 Stick	5.29
THORN 1600	3.90
THORN 3000	7.39
THORN 3500	7.90
THORN 8000	5.28
THORN 8500/8800	6.15
THORN 9000	7.93
DECCA 1730/1830	4.48
DECCA 1910/2213 Bradford	5.92
DECCA 30	6.76
DECCA 80	6.60
DECCA 100	6.14
UNIVERSAL ITT or REMO	6.00
GEC 2100	7.40
GEC 2200 (20AX)	6.50
GEC 2040/2028	6.60
GEC 2110 Pre Jan 77	7.00
GEC 2110 Post Jan 77	7.00
PHILIPS G8 Short Focus Lead	6.70
PHILIPS G8 Long Focus 550	6.70
PHILIPS G9	6.37
PYE 691/3/7	6.58
PYE 713/4 Lead	6.90
PYE 713/725	7.60
R.B.M. A823 (plug in) AV	6.70
R.B.M. A823	7.40
R.B.M. T20	

# NOW!

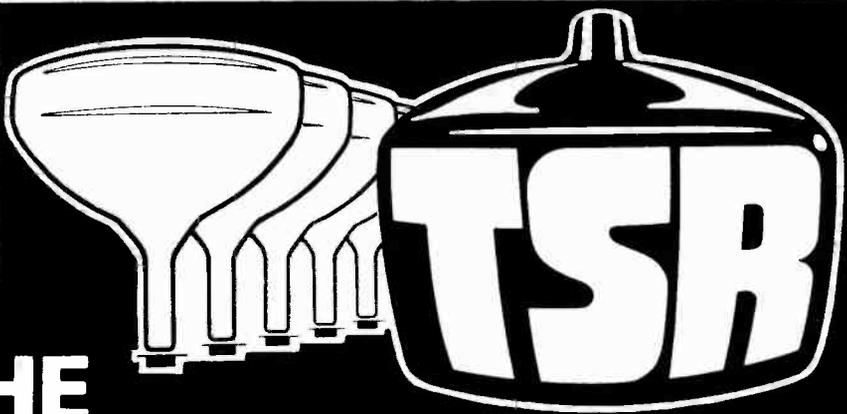

# FOR THE FIRST TIME!

## QUALITY REBUILT CRTs

# ALL SONY CRTs

and PROJECTION SYSTEMS

# ALL HITACHI CRTs

including the 560DZB22 and 510VLB22 series

All In-Line CRTs whatever make.  
All monitor CRTs.  
All gaming machine CRTs.

SONY, HITACHI,  
DZB/VLB glass bought.

**ONE YEAR GUARANTEE  
WITH A FOUR YEAR OPTION**  
★  
**REBANDED FOR MAXIMUM SAFETY**  
★  
**SPECIALIST CRTs REBUILT AT OUR  
SCOTTISH FACTORY**



SCOTLAND & N. ENGLAND  
T.S.R. Vacuonics Ltd.,  
Tom Stewart Lane,  
St. Andrews, Fife,  
Scotland.  
Tel: (0334) 74035

Available **NOW!**  
only from sole distributors

MIDLANDS

**Express T.V. Supplies**  
33 Fortescue Lane,  
Rugeley, Staffs.  
Tel: (08894) 77600

**THE  
OTV  
TUBE SHOP**

LONDON & HOME COUNTIES

OTV House,  
144 Lea Bridge Rd.,  
London E5 9RB.  
Tel: 01-985 6111

SOUTHERN ENGLAND

**Double D. Distributors**  
27 Florence Rd.,  
Parkstone, Poole, Dorset.  
Tel: (0202) 742 347

S.W. ENGLAND

**Torbay Tubes**  
2a Barton Hill Road, Barton Industries,  
Torquay, Devon.  
Tel: (0803) 33035

**Information on all other CRTs available on request**

TOP WINTER VALUE FROM  
BTC-THE TV SPECIALISTS

# You won't better these BTC bargains!

Top quality sets to set you up for the winter televiewing boom.  
Brighten your winter profits with better sets from BTC.

**COLOUR** DECCA BFD 30  
TELPRO  
KORTING  
PYE 697, GEL 2040

**COLOUR** PHILIPS G8's  
2-CHIP BUSH/MURPHY  
GEC 2110, 8500  
3500 VARICAPS  
P/BUTTON HITACHI's  
18" PHILIPS

**COLOUR** 1-CHIP BUSH/MURPHY  
THORN 3000, THORN 8000  
18" PYE's  
ROTARY JAPS

**COLOUR** LATER SETS  
i.e. THORN 9000  
TOUCH TUNE SETS  
ETC.

**MONO** SINGLE STANDARD MONO TV's  
IN BATCHES OF 20 @ £4.00 EACH

## HYBRIDS

UNTESTED  
SINGLES £15.00  
FIVES £12.00  
TENS £9.00

WORKING  
SINGLES £25.00  
FIVES £20.00  
TENS £18.00

## SOLID STATES

UNTESTED  
SINGLES £25.00

WORKING  
SINGLES £35.00

FIVES £20.00

FIVES £30.00

TENS £18.00

TENS £28.00

UNTESTED  
SINGLES £20.00  
FIVES £18.00  
TENS £15.00

WORKING  
SINGLES £30.00  
FIVES £28.00  
TENS £25.00

UNTESTED  
SINGLES £35.00  
FIVES £32.00  
TENS £30.00

WORKING  
SINGLES £45.00  
FIVES £42.00  
TENS £40.00


PLEASE  
NOTE 15%  
VAT ON ALL  
PRICES

# 0274~306018

CASH & CARRY SPECIAL SERVICE  
TO THE TRADE OR ASK ABOUT  
SPECIAL DELIVERIES ON LARGE QUANTITIES.

OPENING TIMES MON-FRI  
9.00-12.00/1.00-5.45  
(CLOSE 4.30 SAT)

## BRIARWOOD TRADING COMPANY

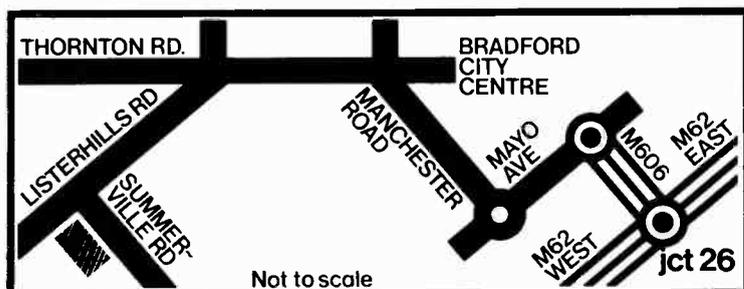

BRIARWOOD TRADING COMPANY  
LEGRAMS MILL, SUMMERVILLE ROAD,  
BRADFORD BD7 1NH

**TRANSISTORS, ETC.**


Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.48	AU103	2.40	BC192	0.86	BC377	0.29	BD234	0.68	BF222	0.51	BPX29	1.62	MPSU05	0.86
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.39	BD235	0.63	BF224 & J	0.22	BR101	0.53	MPSU08	0.78
AC126	0.36	AU110	2.40	BC208*	0.39	BC440	0.52	BD236	0.63	BF240	0.32	BR103	0.64	MPSU55	1.26
AC127	0.48	AU113	2.60	BC208*	0.37	BC441	0.59	BD237	0.68	BF241	0.31	BR103	0.64	MPSU56	1.26
AC128	0.48	BC107*	0.16	BC207*	0.18	BC461	0.78	BD238	0.68	BF244*	0.51	BR4443	1.96	MPSU80	0.82
AC128K	0.55	BC108*	0.16	BC208*	0.37	BC477	0.30	BD239	0.68	BF245*	0.43	BR439	0.60	MPSU131	0.59
AC141	0.65	BC109*	0.16	BC209*	0.39	BC478	0.25	BD410	1.65	BF254	0.48	BR556	0.44	OC26	1.90
AC141K	0.70	BC113	0.22	BC211*	0.36	BC479	0.33	BD431	0.65	BF255	0.58	BSS27	0.92	OC28	1.49
AC142	0.60	BC114	0.22	BC212*	0.17	BC547*	0.13	BD435	0.70	BF256L*	0.49	BT106	1.50	OC29	1.60
AC142K	0.65	BC115	0.24	BC212L*	0.17	BC548*	0.13	BD436	0.71	BF257	0.47	BT109	1.99	OC35	1.25
AC151	0.31	BC116*	0.25	BC213*	0.16	BC549*	0.15	BD437	0.74	BF258	0.62	BT116	1.45	OC36	1.25
AC152	0.36	BC117	0.30	BC213L*	0.16	BC550	0.24	BD438	0.75	BF259	0.54	BT119	1.18	OC42	1.90
AC153	0.42	BC118	0.24	BC214*	0.18	BC555*	0.23	BD519	0.88	BF262	0.73	BU102	2.85	OC44	0.68
AC153K	0.52	BC119	0.34	BC214L*	0.18	BC557*	0.16	BD520	0.88	BF263	0.88	BU105	1.80	OC45	0.63
AC154	0.41	BC125*	0.30	BC225	0.42	BC558*	0.16	BD599	0.87	BF270	0.47	BU105/02	1.95	OC70	0.65
AC176	0.45	BC126	0.30	BC230*	0.16	BC559*	0.17	BF020	1.23	BF271	0.47	BU106	2.98	OC71	0.73
AC178	0.51	BC132	0.20	BC238*	0.15	BCY10	0.30	BD600	0.86	BF273	0.33	BU126	2.91	OC72	0.76
AC179	0.55	BC134	0.22	BC239*	0.22	BCY30A	1.05	BD604	0.86	BF274	0.34	BU204	2.50	OC81	0.83
AC187	0.56	BC135	0.21	BC251*	0.25	BCY32A	1.19	BDX32	2.95	BF275	0.63	BU205	2.58	OC810	0.95
AC187K	0.65	BC136	0.22	BC252*	0.26	BCY34A	1.02	BDY16A	0.63	BF337	0.65	BU206	2.59	OC139	1.30
AC188	0.52	BC137	0.30	BC253*	0.38	CCY72	1.27	BDY18	1.55	BF338	0.68	BU208	2.78	OC140	1.35
AC188K	0.61	BC138	0.35	BC261A*	0.28	BD115	1.35	BDY20	2.29	BF355	0.72	BU407	1.38	OC170	0.80
AC193K	0.70	BC140	0.36	BC262A*	0.28	BD123	1.50	BDY38	1.38	BF362	0.49	C1069	0.80	OC171	0.82
AC194K	0.74	BC141	0.44	BC263*	0.26	BD124	1.65	BF115	0.48	BF363	0.49	C106F	0.43	OC200	3.90
AC197	1.20	BC142	0.35	BC267*	0.20	BD130Y	1.66	BF117	0.45	BF367	0.29	C111E	0.46	OC201	3.95
AC199	0.95	BC143	0.38	BC286*	0.28	BD131	0.58	BF120	0.55	BF451	0.43	D40N1	0.64	OC202	2.40
AC228	0.98	BC147*	0.12	BC288	0.40	BD132	0.68	BF121	0.55	BF457	0.46	E300	0.42	OC205	3.95
AC239	0.98	BC148*	0.12	BC289*	0.49	BD133	0.70	BF123	0.48	BF458	0.49	E1222	0.22	OC207	2.98
AD140	2.02	BC149*	0.12	BC291	0.27	BD135	0.37	BF125	0.48	BF459	0.52	E524	0.47	ON236A	0.98
AD142	1.90	BC152	0.42	BC294	0.37	BD136	0.38	BF127	0.51	BF594	0.15	GET872	1.72	R2008B	2.72
AD143	1.78	BC153	0.38	BC297	0.36	BD137	0.40	BF137F	0.78	BF596	0.17	ME0402	0.18	R2010B	2.79
AD149	1.42	BC154	0.41	BC300	0.62	BD138	0.42	BF152	0.19	BF597	0.27	MF0404/02	0.18	R2322	0.75
AD161	0.66	BC157*	0.13	BC301	0.38	BD139	0.46	BF158	0.25	BF839	0.30	ME6001	0.18	R2323	0.85
AD161/162	1.22	BC158*	0.12	BC302	0.68	BD140	0.50	BF159	0.27	BF840	0.29	ME6002	0.18	ST2110	0.49
AD162	0.71	BC159*	0.14	BC303	0.64	BD144	2.24	BF160	0.20	BF841	0.30	MJ2955	1.30	ST6120	0.48
AF114	1.32	BC160	0.62	BC304	0.44	BD145	0.75	BF161	0.84	BF850	0.29	MJ3000	1.58	TIC44	0.25
AF115	1.28	BC161	0.58	BC307*	0.17	BD150A*	0.51	BF163	0.65	BF852	0.33	MJ341	0.68	TIC46	0.35
AF116	1.26	BC167B	0.15	BC308*	0.14	BD155	0.90	BF164	0.95	BF861	0.29	MJ370	0.72	TIC47	0.45
AF117	1.32	BC168B	0.14	BC309*	0.15	BD157	0.57	BF166	0.50	BF862	0.28	MJ370	0.74	TIC47	0.45
AF118	1.78	BC169C	0.15	BC317*	0.15	BD158	0.75	BF167	0.38	BF872	0.30	MJ371	0.74	TP29A	0.47
AF121	0.69	BC170*	0.15	BC318*	0.15	BD159	0.68	BF173	0.35	BF880	0.29	MJ371	0.74	TP30A	0.50
AF124	0.38	BC171*	0.15	BC319*	0.19	BD160	2.69	BF177	0.36	BF881	0.30	MJ521	0.95	TP31C	0.67
AF125	0.38	BC172*	0.14	BC320	0.17	BD163	0.67	BF178	0.46	BF882	0.42	MJ525	1.20	TP32A	0.56
AF126	0.36	BC173*	0.22	BC321A & B	0.18	BD165	0.66	BF179	0.58	BF883	0.42	MJ53000	1.95	TP32C	0.72
AF127	0.86	BC174A & B	0.26	BC322	0.28	BD166	0.88	BF180	0.53	BF884	0.45	MJ53055	1.22	TP33C	0.77
AF139	0.58	BC176	0.26	BC323	1.15	BD175	0.90	BF181	0.53	BF885	1.02	MJ53055	1.22	TP33C	0.77
AF147	0.52	BC177*	0.20	BC327	0.16	BD177	0.58	BF182	0.44	BF886	0.44	MPF102	0.40	TP34A	0.84
AF149	0.45	BC178*	0.22	BC328	0.18	BD178	0.92	BF183	0.52	BF887	0.19	MPF3702	0.33	TP41A	0.72
AF178	1.35	BC178*	0.20	BC328	0.18	BD178	0.92	BF183	0.52	BF887	0.19	MPF3705	0.30	TP42A	0.80
AF179	1.38	BC179*	0.28	BC338	0.17	BD182	1.20	BF185	0.42	BF888	0.44	MPF6521	0.38	TP2955	0.77
AF180	1.35	BC182*	0.15	BC340	0.19	BD182	1.34	BF186	0.42	BF889	0.38	MPF6521	0.38	TP2955	0.77
AF181	1.81	BC182*	0.15	BC340	0.19	BD184	2.30	BF187	0.35	BF890	0.42	MPSA05	0.44	TP30A	0.50
AF186	1.48	BC183*	0.14	BC348A & B	0.17	BD187	1.20	BF195*	0.32	BF890	0.42	MPSA06	0.32	TP30A	0.50
AF202	0.27	BC183L*	0.14	BC348A & B	0.17	BD188	1.25	BF196	0.14	BF951	0.17	MPSA06	0.32	TP30A	0.50
AF239	0.73	BC184*	0.15	BC349B	0.17	BD189	0.71	BF197	0.15	BF952	0.36	MPSA06	0.32	TP30A	0.50
AF240	1.40	BC184L*	0.15	BC350*	0.24	BD222	0.91	BF198	0.29	BF953	0.36	MPSA93	0.56	TP30A	0.50
AF279S	0.91	BC185	0.36	BC351*	0.22	BD225	0.91	BF199	0.29	BF954	1.98	MPSA93	0.56	TP30A	0.50
AL100	1.30	BC186	0.25	BC352A*	0.24	BD232	0.91	BF200	0.25	BPX25	1.62	MPSU01	0.61	TP30A	0.50
AL103	2.55	BC187	0.27	BC360	0.69	BD233	0.62	BF218	0.42					TP30A	0.50

Alternative gain versions available on items marked\*

For matched pairs add 20p per pair.

**LINEAR IC's**

Type	Price (£)	Type	Price (£)
CA8100M	2.50	SN76023ND	2.52
CA3005	1.85	SN76023N	2.50
CA3014	2.23	SN76115N	1.62
CA3016	0.71	SN76116N	1.78
CA3020	1.89	SN76131N	2.10
CA3028A	0.88	SN76226N	1.60
CA3028B	1.09	SN76227N	2.61
CA3045	3.75	SN76502N	1.92
CA3046	0.70	SN76503P	0.97
CA3065	1.94	SN76544N	1.85
CA3066	1.70	SN76546N	1.85
CA3130S	1.57	SN76570N	1.81
FCJ101	3.32	SN76620AN	0.99
LM309K	1.98	SN76650N	1.48
LM380N-14	1.65	SN76660N	0.66
LM1303N	1.83	SN76666N	0.96
MC1307P	1.02	TA7073P	3.51
MC1310*	2.84	TAA263	3.20
MC1312P	1.34	TAA320	1.10
MC1327P*	0.85	TAA350A	2.48
MC1350P	1.22	TAA370A	3.18
MC1351P	1.42	TAA435	1.70
MC1352P	1.42	TAA450	3.39
MC1357P	2.92	TAA521	1.10
MC1358P*	2.30	TAA522	2.09
MC1458K	1.43	TAA550	0.35
MC1496L	1.15	TAA560	0.20
MC3051P	0.58	TAA611A	1.67
MFC400B	0.85	TAA611B	2.85
MFC4060A	0.98	TAA612AXI	4.71
MIC1P	1.10	TAA630Q	3.95
ML231	3.57	TAA630S	4.18
ML232	3.57	TAA661A	2.39
NE555	0.72	TAA661B	1.75
NE556	1.34	TAA700*	2.80
NE566	1.95	TAA840	0.98
SA11024	5.70	TAA861A	3.35
SA11025	10.35	TAA930B	1.43
SAS570A	2.01	TAA960	3.20
SC9503P	1.40	TAA970	2.81
SL432A	2.52	TAD100	2.66

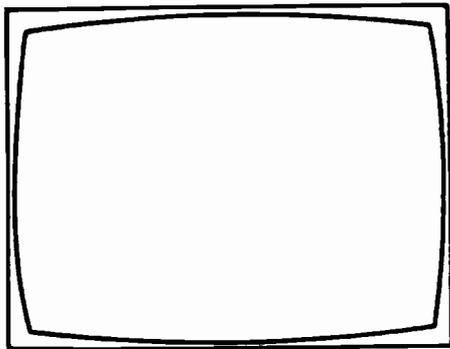

# TELEVISION

## EDITOR

John A. Reddihough

## ASSISTANT EDITOR

Luke Theodossiou

## ART EDITOR

Roy Palmer

## ADVERTISEMENT MANAGER

Roy Smith  
01-261 6671

## CLASSIFIED ADVERTISEMENTS

Barbara Blake  
01-261 5897

## PCB SERVICE

The Readers' PCB Service continues in operation - details as given on page 265 of the February issue. Boards for the Frequency Counter-Timer project will be available, also for the In-Circuit Transistor Tester (see next month).

## Technical Prospects

One thing about television is that it never stands still for long. That prevents us getting either bored or complacent. Even in the days BC (before colour), there was a constant succession of developments - flywheel sync, vision a.g.c., new valve ranges, the use of higher and higher frequencies and so on. AC (after colour) brought solid-state circuitry in many forms, the intrusion of digital techniques for teletext and remote control purposes, and the whole gamut of video technology. What next?

It seems reasonably safe to suggest that digital techniques will play an increasingly large role in TV receivers. The use of digital techniques in the timebase generator stages will give rock-steady sync, while converting the video signal into digital form will enable almost anything to be done to it depending on the amount of digital memory available in the receiver. The BBC have promised us digital sound signals for their DBS services, and are investigating the use of digital sound for terrestrial two-channel transmissions.

A digital field oscillator is already in use, as mentioned in our report on the Thorn 1696/1697 chassis in the February 1983 issue - it's in the Monomax i.c. Some eighteen months ago, in November 1981, we reported on the set of LSI and VLSI chips being developed by ITT in W. Germany to provide digital TV receiver signal processing - the ITT Digivision system. The i.c.s were presented at the 1981 Berlin Radio Show and the 1982 Paris Components Show. Sets using the i.c.s are to be demonstrated at this year's Hanover Fair, Berlin Radio Show and the Great Home Entertainment Spectacular to be held in the UK later this year. Digivision ITT sets are expected to be on sale in the UK early next year. They are likely to be up-market models, though it may be only a matter of time before the technology appears in simple, no-frills receivers. It all depends on relative costs as the production of digital TV i.c.s increases.

ITT are not alone of course in developing chips of this sort. Others treading the same path include Philips, RCA, Sony and Hitachi. How long will it be before most TV chassis use digital signal processing? It's probably relevant to recall the long time it took for discrete component i.f. circuitry to become obsolete. I.F. i.c.s have been around for many years, but it took quite a time before performance and cost swung decisively in favour of the i.c. approach. The digitalisation of TV receiver signal processing is likely to follow a similar pattern.

The conventional analogue approach is perfectly satisfactory of course - so are thermionic valves for that matter! - but just think about what can be achieved once the video signal has been converted to digital form. First it can be regenerated - converted to nice square pulses to remove signal distortion effects. Then features such as picture-within-a-picture, picture zoom, still pictures and slow motion become possible. These are probably rather unnecessary - you don't want to spend your time playing with the set rather than viewing, while reports on VCR use suggest that such features are seldom in practice used. More interesting is the prospect of using digital technology to double the number of lines to give high-resolution pictures. One of the problems here is that a high-resolution tube would be required to display the picture, though computer requirements have already led to much work being done in this field.

In ten years then the average domestic telly could be a precision instrument compared to today's set. What else? Cable/DBS will extend the range of programmes available, though the extent of the likely increase is open to question. The present problems with TV-am underline the fact that merely filling an empty slot in broadcasting time is of questionable worth. You've got to substantially increase the number of programmes made for television if a real increase in choice is to be provided. Programme production is an expensive business however, and since viewing habits long since reached saturation point the more programmes transmitted the smaller the prospective audience for each. It remains to be seen how the economics will turn out, though the difficulties experienced by US cable operators suggest that cable is not going to be the bonanza it's been made out to be in some quarters.

It's also interesting to note that delays in the establishment of cable networks - the necessary legislation will take time, and an election will probably intervene, while the services have yet to be sold to the public - mean that few people will have the cable at their doorsteps before DBS starts. The cable enthusiasts had hoped to get going before the advent of DBS, and to offer the DBS services via cable. As it is, it's more likely that the public will be installing DBS dishes and then finding they've enough choice without cable's offerings - especially with the amount of material available on tape and disc. Much was made of the prospects of selling cable technology abroad during the great cable debate - but we might do just as well by selling dishes and microwave electronics.

This leaves the display device. We've not heard so much about flat-screen displays recently. They seem to be as far off as ever. If high-resolution tubes come into wide use the day of the flat-screen display will recede even further. The c.r.t. may be bulky, but there's no more efficient picture source than a phosphor screen activated by an electron beam.

# Long-distance Television

**Roger Bunney**

FEBRUARY 1983 was a relatively quiet month, the only events of note being a tropospheric lift over the 13-19th (peaking on the 18-19th) and enhanced auroral activity on the 4-5th. A very slow moving high pressure system gave almost two weeks of freezing temperatures during the month, with clear skies – the classic condition leading to tropospheric propagation. As the pressure started to fall, so the signals rose. The midlands/north of the UK seem to have fared better than the south for European TV reception. Indeed Ryn Muntjewerff (Holland) reported “a little tropo” on the 16-17th which would normally have meant reception of a considerable number of stations. In his case Band III and the u.h.f. bands were open, producing CST (Czechoslovakia) chs. R10/R38, while here at Romsey (Hants) there was improved reception from the east (i.e. France and the Low Countries, and just W. Germany), but nothing on the scale of the tropospheric opening in January.

Reports from Cyril Willis (Cambridge), Garry Smith (Derby) and Iain Menzies (Aberdeen) indicate that things were better in the north. Garry Smith for example received several W. German stations and DFF (E. Germany) at good strength from around 2100 onwards on the 15th. Following this peak (15th) things died down until the 18th, when Band III and the u.h.f. bands opened up, giving W. and E. German signals and, at Cambridge, two European ATV stations (DC40N and ON6LM, W. Germany/Belgium). At Derby reception was mainly from Belgium, France, W. Germany and (just) E. Germany (at u.h.f.). The peak occurred on the night of the 18th/early 19th – when Cyril Willis rose at 0500 he was rewarded with TVP (Poland) on ch. R30. Conditions fizzled out during the morning, and by 1200 things were dead. It's interesting to note that several enthusiasts received forces TV stations – AFN ch. E34 (Shape) and various BFBS outlets – during the period, the main ones being on chs. E28/48. Another small lift occurred on the 23/24th, experienced mainly in the north – Iain Menzies reported reception of a large number of NRK (Norwegian) Band III transmitters at good strengths.

Intense auroral activity was logged throughout the UK on the 4/5th, mainly in northern parts, though there was some evidence along the south coast. All the Band I channels were affected and Cyril Willis noted suspected System M signals on chs. A2, 3, 4. Both early and late phases were observed on the 4th, but the 5th was less intense and only the early phase seems to have been seen.

There was the usual meteor scatter reception – short signal bursts of anything from one to ten seconds. The signals generally logged here are from SR (Sweden), CST and TVP (Poland) on chs. E2/R1. For those with no experience of this mode of propagation, the procedure is to leave the set tuned to one of these channels, with the correct line and field settings, and eventually short bursts of picture information will be seen – the best time is early morning, though MS occurs throughout the twenty four hour period.

There were SpE signals on the 7th, during the evening (2100-2300), on chs. E2/E2a/IA/E3. The only identified programmes were from RAI (Italy) on ch. IA, the others showing mainly skiing.

My thanks to Cyril Willis, Iain Menzies, Garry Smith, Arthur Milliken and Ryn Muntjewerff for sending in reports of their reception.

## News Items

**Eire:** A new list of RTE TV transmitters has been issued by RTE (available from Reception Investigation Dept., RTE, Dublin 4). The main transmitters and the relays with over 1kW e.r.p. are as follows.

Main transmitters	RTE-1 channel	RTE-2 channel	Vision e.r.p.
Three Rock (Dublin)	29	33	25
Cairn Hill (Longford)	40	43	800
Kippure	H	—	100
Maghera	B	H (V)	100
Mt. Leinster	F (V)	I (V)	100
Mullaghanish	D (V)	G (V)	100
Truskmore	I	G	100
Clermont Carn (Co. Louth)	52 (V)	56 (V)	250
Holywell Hill (N.E. Donegal)	23	26	20

## Relays

Achill	E	H	1
Cahirciveen	F	I	1
Castlebar	D (V)	F (V)	1
Clifden	D	F	1
Fanad	F	D	2
Monaghan	D	—	1

Polarisation is horizontal unless otherwise indicated (V = vertical).

**Spain:** The “Euskal TeleBista-TV” Basque service is now in operation with studios at Durango (Vizcaya). The Philips PM5544 test pattern with ETB identification in the upper black rectangle is used. Transmitters are: Durangesado ch. E33; Bilbao ch. E35; Vitoria ch. E42; Jaizkibel ch. E51.

**E. Germany:** The Helpterberg ch. E3 DFF-1 transmitter (an old friend of DXers!) has now closed, the service being transferred to ch. E37.

**SEBC:** As mentioned last month, this stands for Southern European Broadcasting Corporation. The mystery of the ch. A2 TV transmissions from the same direction now seems to have been solved. Duncan Fraser reports that there's an AFRTS transmitter at the base in Vicenza, Italy. Readers will recall that ch. A2 transmissions have been received via SpE from this direction for several years, though the AFRTS deny operation in Band I in Europe or the Middle East.

**New EBU listings:** Spain Villadiego RTVE-1 ch. E47, 200kW. The Finish Taivalkoski ch. E2 YLE-1 transmitter has now closed down – yet another old friend of DXers.

## Publications

Newsletters have arrived from Cyril Willis and Dave Launder during the month. The former is called “DXTV News” and is issue number one. It's hoped to publish this monthly at £4.50 for six issues. The publication, on photocopied A4 paper, includes photographs, news items,

details of DX equipment, reception logs and profiles of DXers and their equipment – Iain Menzies and Arthur Milliken are featured in this issue. For further details send s.a.e. to Cyril at 17 Main Street, Little Downham, Ely, Cambs CB6 2ST.

Dave Lauder's "DX-TV Group Newsletter" is published every two-three months on photocopied folded A4 and has a much more technical bias. Items include information on auroral E layer propagation and likely dates, methods of monitoring the TV bands with audio warning of signal onset (a circuit using the MC1310 stereo decoder i.c. tuned to the 15.625kHz line frequency is shown), a test report on a Hugh Cocks' MOSFET preamplifier, satellite information and a brief rundown of reception loggings. A sample can be obtained by sending a SAE to Dave at 18 Burnside Close, Barnet, Herts EN5 5LN.

I feel it's an encouraging sign of the increasing interest in TV-DXing that such newsletters are becoming available. One favourable aspect nowadays is the comparative ease with which equipment for DX use can be obtained – no need to modify old 405-line receivers!

Robert Copeman has sent an Australian list of radio/TV stations entitled "Sound and Television Broadcasting Stations", dated June 30th 1982, edition three, published by the Australian government's Department of Communications. The book costs \$4 from the Australian Government Publishing Service, Canberra. Include sufficient postage – the weight is 175g.

"Build a Personal Earth Station for Worldwide Satellite TV Reception", a Tab book by Robert J. Traister, has been sent by Maplin Electronics. This provides a mainly US approach to the subject and doesn't contain circuitry. It's really a practical guide to the installation and operation of the types of commercial terminal kits available in the USA, at prices now of under \$2,000 for a complete system. As a general guide to 4GHz satellite reception I found it interesting and informative. The book has 296 pages and costs £8.25 in the UK. It concentrates on how the equipment works rather than how to construct boards, feedhorns, etc.

A list of CB filters is available from AKD, 10 Willow Green, Grahame Park Estate, Hendon, London NW9 5GP on receipt of a SAE. The filters are all in-line types for 75Ω coaxial cable use. There are various types with mainly braid/inner break functions – the BB1 for example has a 1:1 transformer braid break only.

### Simple IF Preamplifier

A simple BF254 (or equivalent) transistor wideband i.f. preamplifier circuit has been sent to us by the French TV-DX club AFATELD, see Fig. 1. It's for fitting at the output of a standard u.h.f./v.h.f. tuner. An i.f. transformer could be added at the input to increase the selectivity, but


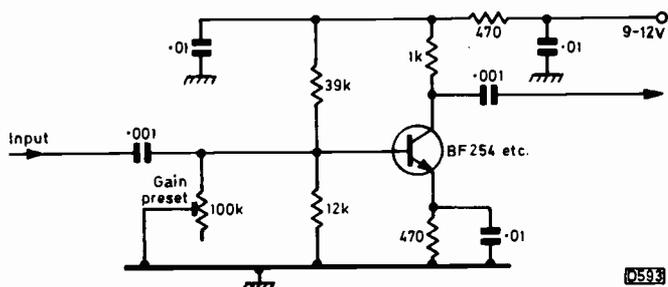


Fig. 1: Simple i.f. preamplifier circuit. A BF254, BF314 or equivalent transistor can be used.
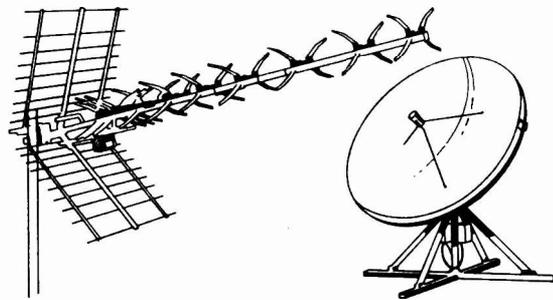
## SOUTH WEST AERIAL SYSTEMS

10 Old Boundary Road, Shaftesbury,  
Dorset. SP7 8ND tel. 0747 4370



SOUTH WEST AERIAL SYSTEMS – TODAY'S AERIAL TECHNOLOGY AT ITS BEST – AND WITH TOMORROW IN MIND.

We provide the consultancy and supply the equipment for ALL receiving installations in the VHF/UHF broadcasting spectra. Our EXTENSIVE RANGES of aeriels, amplifiers, filters and allied components cover Western Europe's most respected companies including Antiference, Jaybeam, Pye/Labgear, RS (Components), Wolsey, Fuba, Triax, Polytron, Teldis, Vorta, Mutek, Channel Master/CDE, Hirschmann and our own exclusive aerial ranges for various VHF options, including a Band I TV-DXing range.

WHETHER YOUR NEED IS FOR LOCAL OR FRINGE RECEPTION, ALTERNATIVE CHANNELS, TV/FM DXING, OR FOR A DISTRIBUTION SYSTEM, SOUTH WEST IS THE 'ONE-STOP' ADDRESS FOR ALL EQUIPMENT AT VERY COMPETITIVE PRICES.

We have the practical experience in resolving reception problems, interference reduction and DXing – our customer consultancy service will end your difficulty. Babani and BATC technical publications supplied.

We can offer a 4GHz TVRO satellite terminal package (and in addition a 2½ metre fibre glass segmented dish suitable to 20GHz) and with 12GHz options available shortly.

SOUTH WEST AERIALS IS UNIQUE – TRY OUR 1983 COMPREHENSIVE CATALOGUE AT 54p. Please include an SAE with all enquiries, customer reception consultancies and for our own VHF aerial and 'Wideband UHF Aerials' leaflets. (Access/Barclaycard welcome).

## TV LINE OUTPUT TRANSFORMERS

If the Transformer you require is not listed please phone.

<b>RANK BUSH MURPHY</b>		
Z146 A640 dual std mono	8.51	
Bush A792, A793 single std mono	8.51	
A774 single std mono	8.50	
A816 solid state mono	9.00	
Z712 T16a T16b mono portable	9.00	
A823 A823b A823av colour	10.00	
Z179 Z722 series colour	10.00	
Z718 18" series	11.00	
Z718 20" 22" 26" series	11.00	
T20a T22 series colour	10.00	
<b>DECCA</b>		
MS1700 2001 2020 2401 mono	8.00	
MS2404 2420 2424 mono	8.00	
1210 1211 1511 portable	9.13	
GYPSY portable	9.13	
CS1730 1733 colour	8.00	
CS1830 1835 colour	8.00	
'30' series BRADFORD colour	8.00	
80 series colour	8.00	
100 series colour	8.00	
<b>PHILIPS</b>		
210 300 series mono	8.00	
320 series solid state mono	8.50	
G8 series colour	8.00	
G9 series colour	8.50	
G11 series colour	13.70	
<b>KB-ITT</b>		
VC200 VC205 VC207 mono	8.00	
VC300 VC301 VC302 portable	8.00	
CVC1 CVC2 colour	9.00	
CVC5 CVC7 CVC8 CVC9 colour	9.00	
CVC20 series colour	9.00	
CVC30 CVC32 series colour	8.00	
CVC40 series	14.56	
<b>L.O.P.T. TESTER</b>		
Total Price		16.79

ADD 15% VAT to ALL prices.

**Tidman Mail Order Ltd.,**  
236 Sandycroft Road,  
Richmond, Surrey.

Approx. 1 mile from Kew Bridge.

Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm.

1.30 to 4.30 pm.

Sat 10 am to 12 pm.

**Hamond Components**  
(Midland) Ltd.,  
416 Moseley Road,  
Birmingham B12 9AX.

Phone: 021-440 6144.

Mon-Fri 9 am to 1 pm.

2 pm to 5.30 pm.

I feel that its merit lies in simplicity and that sufficient selectivity should be available in the later i.f. stages to give adequate DXing performance.

### From our Correspondents . . .

Ian Moody (Sutton) has been TV DXing for three years and is now using a Ferguson 3840 (Thorn 1690 chassis) with good results. He's sent details (see Fig. 2) of modifications to the receiver to cater for French u.h.f. vision signals. Switched, parallel detector diodes are used, the subminiature SPDT toggle switch S1 selecting the video sense. R1 is introduced on system L to reduce the bias applied to the base of the video driver transistor to avoid picture flaring. A 10k $\Omega$  preset could be used in this position, set for optimum results, but the value of 6.8k $\Omega$  works well enough. Ian mentions reception of aircraft scattered French u.h.f. signals due to his proximity to flight paths!

Ian Johnson (Bromsgrove) reports that the Bush Ranger Model BM6714A Mk. III, with its discrete component i.f. stages, is good for DXing - he's got two of them in use and judging by his reception during January they're working very well. MS signals synchronise easily and over the period January 10-26th there was only one day when he failed to log anything.

Since the Thorn 1690/1 series chassis is no longer in production, I would appreciate comments from readers on alternative current models suitable for DX use. The aim is to compile a list of suitable models for future publication.

Mike Ockenden (Pevensey, Sussex) reports that the French version of Nationwide goes out at 1920-1940 local time and includes regional identifications (Nord, Picardie, etc.) which appear behind the newsreader.

John Tellick (Surrey) reports that the Gorizont downlink channel 3 carried Top of the Pops on January 27th just three hours after the UK transmission but with the links (i.e. announcements between numbers) badly edited out! This was followed by the recent King Kong feature film. On subsequent nights various W. European offerings that were flying around the Eurovision links were to be seen.

Chandra de Silva (Colombo, Sri Lanka) is using a standard domestic Tatung monochrome receiver which, with an eight turn indoor helix aerial and no aerial amplifier, is able to resolve the sound and vision signals from the Ekran satellite (714MHz downlink).

### Miniature Active Aerials

For some years I've been interested in compact active aerials, and have experimentally made a ch. E4 (62MHz) system using helically wound "rubber ducks". This, with an amplifier, provides better results than a standard dipole whilst being only 18in. long. The opportunity arose recently to test a commercial active aerial produced in the Far East - one with a combined v.h.f./u.h.f. array and integrated amplifier. The system is so integrated that the riveted PVC container can't be opened - it's not even

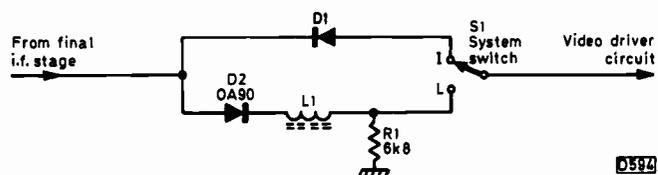


Fig. 2: Switched video detector circuit for the Thorn 1690 chassis.

translucent! The length is some 680mm., the width 470mm. and the thickness 50mm. An optional add-on element extends the coverage via internal filtering to the "hi" band (i.e. Band III), or a larger folded dipole can be added for v.h.f. reception down to 40MHz. The one I've tested has this folded dipole.

The results at u.h.f. have been surprising. I'd expected poor results considering the size of the aerial, which appears to be some form of log-periodic array at u.h.f. The unit was mounted at 41ft above ground level and powered. Comparison tests were then made with an Antiference XG21W and Labgear CM7066 amplifier mounted at 63ft. The measured output from the active aerial system on Crystal Palace ch. E23 was found to be only 5dB down on the XG21W combination. Obviously if the active aerial was lifted to 63ft there would be a corresponding increase in its output. There are possibilities for improvement. For example there's no efficient reflector system (I suspect that the rear mounting clamp is all that gives rear protection): a suitably mounted reflector would increase the forward gain and improve the front-back ratio from the present 6-16dB to a constant 25dB. The beamwidth at the -3dB points resembles that of the Colour King type aerial - around 55-65°.

The Band III performance seemed to be good, at least when compared with an Antiference HC2011R with 12dB gain amplifier. Again improvement could be obtained by adding a reflector - the Band III element is the sole v.h.f. pickup, the front-back ratio being 0dB.

The performance on Band I is poor when compared with a two-element wideband aerial of the WB2 type.

It would appear to be best to exploit the active system for its Band III/u.h.f. coverage. I would expect two units correctly stacked for u.h.f. operation to have a 30° beamwidth at the -3dB points, with a 40-45° beamwidth in Band III when used with a suitable double reflector system.

The amplifier is again a mystery, being hidden away inside, but is obviously mounted directly on to the u.h.f. array, thus obtaining an optimum noise match. The amplifier operates at 12V, 120mA and has a noise figure of 1.7-3.5dB.

Further tests will be carried out to establish the aerial's potential for DX use. It certainly resolves the stronger Band I MS and weakish u.h.f. tropospheric scatter signals, and the results on London u.h.f. (a steady, over the horizon signal here) seem convincing.

### Small-screen Dual-standard Portables


Some time back I reviewed three small-screen (approximately 5in.) monochrome portables featuring v.h.f. and u.h.f. tuners and sound i.f. switching between system B/G (5.5MHz) and system I (6MHz). The one best suited for DX use was the Plustron Model TVR5D, which also has f.m./l.w./m.w. radio coverage. The importers have now discontinued this model unfortunately, so I'm at present investigating possible alternatives. I expect to be able to report back shortly on this subject.

### System L-I Converter

I've received several requests for details from those wishing to wind the coil in the system L-I converter featured in the February issue (see Fig. 2, page 195). The details for L1 are as follows: 7 turns of 22 g. wire wound on a ½in. coil former, spaced over 1in. and tapped at two turns.
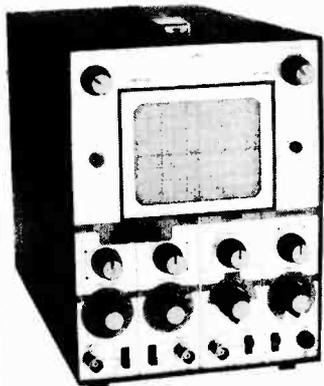
# B.K. ELECTRONICS

**INCREASE YOUR PROFITS - IMPROVE YOUR SERVICE  
WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT**



## SAFGAN DT-420 DUAL TRACE SCOPE 20MHz BANDWIDTH


- SPECIFICATION**
- ★ CH1, CH2: 5mv/div-20v/div
  - ★ Time Base: 1 sec/div-100ns/div
  - ★ XY Facility: Matched XY inputs
  - ★ Trigger: Level control, ± slope selection
  - ★ Auto, normal, TV triggering
  - ★ Z-Modulation
  - ★ CAL output 1V 1KHz
  - ★ Graticule blue ruled 8x10 div (4" CRT). Very Sharp Trace.
  - ★ Size: H215mm, W165mm, D280mm
  - ★ Weight: 4kgs
  - ★ Supply: 200-240V, 40-60Hz
- PRICE £199 + £29.85 VAT**  
Probes as Thandar below.

BRITISH MADE - RELIABLE - 18 MONTH GUARANTEE
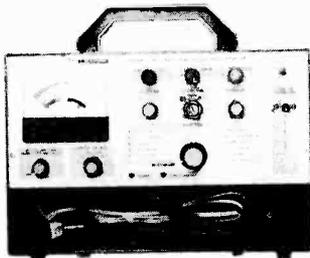
## LEADER LCT-910A C.R.T. TESTER-REJUVENATOR

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.


- ★ Tests for shorts and leakage between electrodes.
  - ★ Tests cathode emission characteristics.
  - ★ Separately checks condition of guns.
  - ★ Removal of shorts and leakage between electrodes.
  - ★ Checks heater warm-up characteristics.
  - ★ Rejuvenation of low emission cathodes with automatic timing.
  - ★ Super rejuvenation with manual control.
  - ★ Complete with tube base adaptors.
- Size: H 230mm W 330mm D 120mm.



PRICE £151 + £22.65 VAT
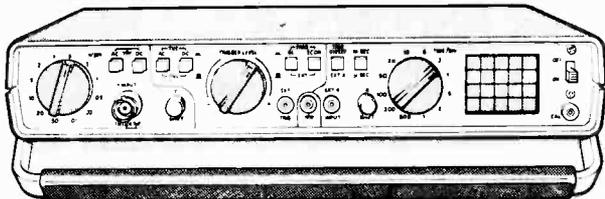
## THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.

The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**



**1980 GOLD MEDAL** winner of the B.R.N.O. EXHIBITION, the largest Trade Fair held in Eastern Europe.

### Full Sized Performance

- 10 MHz bandwidth.
- 10 mV per division sensitivity.
- Full trigger facilities are provided including TV frame, or TV filtering.
- Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- Size 255mm x 148mm x 50mm.

Scope **£149.00 + £22.35 V.A.T.**

Carry Case **£8.95 + £0.89 V.A.T.**

x 1 Probe **£7.00 + £1.05 V.A.T.**

x 10 Probe **£8.00 + £1.20 V.A.T.**

x1/x10 Switched Probe **£9.50 + £1.42 V.A.T.**


Rechargeable Batteries **£11.00 + £1.65 V.A.T.**

AC Adaptor **£6.95 + £1.04 V.A.T.**

(Overseas purchasers please state voltage.)

**BRITISH  
MADE**

**FULLY  
GUARANTEED**

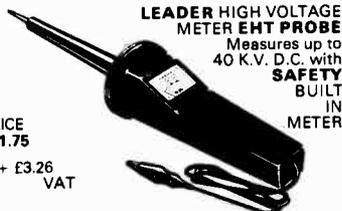

**LEADER HIGH VOLTAGE  
METER EHT PROBE**  
Measures up to  
40 K.V. D.C. with  
**SAFETY  
BUILT  
IN  
METER**

PRICE  
**£21.75**  
+ £3.26  
VAT

**ALSO AVAILABLE**  
Analogue Multimeters  
Digital Multimeters  
Oscilloscopes  
Signal Generators  
Digital Frequency Meters  
Pattern Generators  
CRT Tester/Rejuvenator  
T.V. Field Strength Meter  
LARGE S.A.E.  
FOR COMPLETE LIST.

U.K. Post Paid. Export orders welcome, please deduct V.A.T. and include an additional £5.00 for Overseas carriage. Mail Order only. Callers by appointment. Barclaycard/Access orders welcome, or Cheque, Bank Draft etc., with order please. Large S.A.E. for technical leaflets of complete range.

Delivery normally within 7 days.

**B. K. ELECTRONICS, Dept. 'T',**  
37 Whitehouse Meadows, Eastwood,  
Leigh-on-Sea, Essex SS9 5TY.  
Tel: (0702) 527572.



# Technical Training in Television, Radio and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed".

## CITY AND GUILDS CERTIFICATES

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

**Basic Electronic Engineering (C&G/ICS)  
Radio Amateurs**

## CERTIFICATE COURSES

**TV & Audio Servicing  
TV, Radio and Audio Engineering  
Radio & Amplifier Construction  
Electronic Engineering\*  
Computer Electronics\*  
Industrial Electronics\*  
Radio Frequency Electronics\*  
Electrical Engineering\*  
Electrical Contracting & Installation**

\*Qualify for IET Associate Membership



Approved by CACC



Div. National Education  
Corporation



Member of ABCC

## POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Dept G285  
ICS School of Electronics  
160 Stewarts Road  
London SW8 4JJ



01-622 9911  
(All Hours)

# COLOUR TELEVISION & MUSIC CENTRE

Old Mixon Crescent, Old Mixon Trading Estate,  
Weston Super Mare – (15 mins. past Bristol on M5)

**NOT EX-RENTAL**

## COLOUR TELEVISIONS SOLID STATE

★ **FANTASTIC OFFER** ★

*All in perfect running order*

PYE CHELSEA

18", 6 Button, Sliding Controls,  
Brilliant Condition

**£45.00**  
Inc. VAT

PYE 721

20"-26", could be mistaken for new

**£65.00 each**  
Inc. VAT

FERGUSON 9000

Remote Control, Like New

**£85.00 each**  
Inc. VAT

*Minimum 6 sets*

★ ★ ★

THE ABOVE CHELSEA ARE WORKS MODIFIED FOR ANY PART OF THE WORLD  
VHF - UHF

BIG REDUCTIONS FOR EXPORT ORDERS OVER 200 SETS

ALL OTHER MAKES IN STOCK OFF THE PILE FROM £6

★ ★ ★

**Ring Now**  
**W.S.M. 413537**

# The Further Adventures of Tiny Tim

Les Lawry-Johns

Tiny Tim woke up early in the morning and started to think his usual gloomy thoughts. What was wrong with the world was that there were too many people in it, most of them wanting him to do things that he didn't want to do for them. He killed off a million people mentally. Still too many. So he killed off another million and too many remained. Wouldn't it be nice if there were no people at all?

The animals would be able to go about doing whatever it is that animals do, and the forests would grow nice and big. There would be great big forest fires with no one to put them out. All the animals would be burnt. Oh dear, that wouldn't do. His cat Spock would catch cat flue and die because she wouldn't have had her jab from the vet. Oh dear. Perhaps firemen and vets could live then? Except the vet who was going to bring in his car radio-cassette. This frightened Tim because it was a Philips machine and he had a job to get the cassette drive belt back on when it bounced off as it had a habit of doing. So one vet would have to go and another would have to be found to give Spock her jab to ward off cat flue.

## Pinnacle of Despair

As he lay there he thought of the nasty letter he'd had from one of the wholesalers. If he didn't pay their account they would do nasty things to him. He always paid his accounts on time, but he wasn't going to pay this one because it was daft. He'd ordered six video cassettes for his wife to play with and they'd sent sixty one. As eight were loose he'd decided to keep these and send the rest (53) back. He'd phoned the firm and the girls who'd answered the phone had laughed and said the rep who'd taken the order must have had a shaky hand. So they'd laughed some more. He'd put the phone down but nothing was done about it. The cassettes were collected by a well known firm of carriers who signed the collection note.

Tiny Tim had again phoned the wholesalers to let them know that the cassettes were on their way back to them, but the man at the other end said he didn't know what it was all about. Tim was eventually promised a credit note, but it never came despite several more phone calls. One person had said that they hadn't got back the number specified. This had made Tim angry, and he'd said nasty things that his wife had said he should have been ashamed of saying. So the statement had come in, along with a nasty letter which Tim had returned with a comment to the effect that the liaison between their departments was deplorable. This was much nicer than what he'd said on the phone. So he dug in his tiny heels and waited for the nasty things to happen.

## Daylight

As it was beginning to get light, Tim decided it was time that someone should get up and make the breakfast. So he stirred around enough to wake up his wife and then snored to pretend he was asleep. His wife looked at the clock and heaved a sigh.

"He lays awake all night thinking stupid things and when it's time to get up he goes to sleep. God how I suffer."

Tim snored loudly to ensure that his wife wouldn't go back to sleep, and eventually she got up. Tim smiled at the picture of the tiger on the wall. "We each of us have our own ways of getting our food" he told the tiger.

His wife brought up his breakfast, and Tim noticed that she couldn't burn the scrambled eggs like he did to give them a nutty flavour, but he thought it best not to complain. Something about not tampering with your luck.

He ate his breakfast and drank his tea, then laid back and sort of slipped off to sleep. He was rudely awakened by his wife talking to customers in the shop.

"I'm sorry but he's out with the dog at the moment."

Which was a bit shaky since Ben had been standing with the lead in his mouth for the last half hour or so.

Tim waited for the customers to leave, then crept down the stairs.

"Mr. Crankcase wants a new colour set delivered by ten o'clock. He wants a 22in. without remote control or any trimmings. No later because he's off to America and wants to see it and settle before he goes. So you'd better put your skates on."

"I'll just take the dog for his walk, then I'll get cracking" said Tim.

"Oh excellent" said his wife. "Mr. Crankcase lives at Birling, which is a long way away. You haven't unpacked the set yet and it's now nine fifteen."

"Oh dear" said Tim. "Why didn't I get up earlier? Why did you let me nod off again? I must fly." So he flew, but went in the wrong direction because he'd forgotten where Birling was. He ended up feeling very confused, driving along the M20 towards Maidstone. It all ended happily however, because Mr. Crankcase had delayed his departure.

But Ben was rather peeved. He stopped at a post but missed it, contriving to hit Tim's leg instead. This reminded Tim of the time he'd been standing at the top of Windmill Hill looking out over the river and a big black dog had come and stood beside him. Tim had patted the dog's head, thinking how good he was with dogs, but had suddenly become aware that his leg was soaking wet. It was a very large dog.

Tiny Tim made his way back to the shop, talking to Ben and telling him that in addition to getting rid of all the people in the world the dogs would have to go as well, leaving just a few bitches - they don't cock their legs at every tree, post and leg that happens to be near.

## Trying TVs

When they got back, quite a few jobs were waiting to be done. The first was a GEC set fitted with the 20AX tube (Model C2233H). A note on it said "no results". The right side fuse (on the switch-mode power supply panel) had blown, so Tim looked askance at the BU126 chopper transistor. It was short-circuit. As he fitted a new one Tim was thinking. He'd had this trouble a year or so ago and the new one had died very quickly indeed. Then there was

a note on the same subject in a recent Fault Report item in *Television*. The driver transistor is biased by a nasty 150k $\Omega$  resistor. Now where was it? Ah, just there, R515. Take it out and measure it. Reading about 4M $\Omega$ .

Tim didn't have a 1W, 150k $\Omega$  resistor, so he was a devil and used a 220k $\Omega$  one instead. It worked well enough, so he logged this information in that magnificent computer he has atop his shoulders – another one not to be forgotten.

The next set was an ITT CVC9 that belonged to one of Tim's old school chums (which makes him very old). It had been in several times of late, suffering from loss of colour which seemed to be restored permanently each time Tim did almost anything around the decoder, only to fail again several days later.

Tim had first found that when the base of the 4.43MHz reference oscillator transistor T38 was touched with the test prod the colour returned and couldn't be made to go off again. So he'd changed T38. On the next occasion it had seemed that the crystal was faulty, so Tim had fitted a new one. He'd thought that this was unusual in an ITT set, but concluded that as he was very rarely right about anything it must be the case since the colour stayed and stayed. Here it was again however.

He put the probe on the base of T38 and the colour appeared. He looked at the board and the blue 470pF capacitor (C228) in the oscillator circuit (base-emitter feedback) caught his colour prejudiced eye. He doesn't like blue things. So he changed it and the set has been all right ever since.

### **The Music Centre**

A Fidelity 440 music centre sat there waiting its turn. Its owner, a nice man by the name of Les Woolends, came in just as Tim was about to perform.

"Thought I'd pop in to tell you what's wrong with it. It won't record on one channel."

Tiny Tim scowled at him. "It's a pity you didn't take it back where you bought it."

"I bought it here."

"Just testing, just testing." Tiny Tim was aware of his wife's eyes boring into his back.

Without further ado Tim removed the bottom of the music centre and squirted a jet of Servisol into the record/playback switchbank. Much to his surprise, it now worked on both channels.

Putting on his 'leave it to the master' air, Tim replaced the bottom cover and chatted away to Mr. Woolends about cats and things.

### **Night-time**

That night Tiny Tim had a nasty dream about being eaten by a great big cat. He awoke bathed in perspiration and decided to have a nice wash to freshen himself up a bit. So down to the bathroom he went, and gave himself a good wash down. He dried off and looked for his talcum powder. It was some distance away, at the far end of the bath, so he decided to use some of his wife's instead. But no matter how hard he shook the pink tube nothing would come out. So he tried the green one which had two nice big holes at the top. He shook the powder all over his private places and rubbed it in, noting that it seemed rather coarse for his little body. He tumbled back into bed, thereby waking up his wife.

"Now what are you up to?"

"Just been to the bathroom for a wash. What's the talc in the green tub?"

"That's not talc, you fool. It's shake 'n vac carpet cleaner."

"Oh dear" said Tiny Tim.

# **VCR Clinic**

**Mike Phelan, Richard Roscoe and Michael J. Cousins, T.Eng. (C.E.I.)**

### **Ferguson 3V23**

The fault with a Ferguson 3V23 was noticeable only on a stationary picture. It looked as though there was a slight ripple on the verticals – but only on about the centre third of the picture, the top and bottom being o.k. As the fault was also present on still frame we had a look around the drum motor drive circuit. This is a brushless, direct drive motor, so the pole switching is done by Hall sensors and a magnetic ring (instead of a commutator and brushes).

The sensors drive many transistors, culminating in two power stages which supply current to the two sets of poles. When the head is running we should have an equal sinewave on each pole, but in this case one was missing. As a result, the drive was varying. One very discoloured power transistor gave itself away, but while we were measuring voltages we noticed that the supply to the motor was about 22V instead of 12V – the regulator transistor in the power supply had gone short-circuit. It's surprising that anything worked at all! **M.P.**

### **Ferguson 3V00**

"We've fitted a new head, but can't get the tape guide rollers adjusted" they said. We connected the scope to

TP7 to monitor the video f.m. envelope, and found that while we could get rid of the dip at either end of one channel it was then transferred to the other channel. Now in theory each head follows the same path, so the condition we had shouldn't be – unless the heads were not following the same path, due possibly to the spindle being bent. We removed the head and there it was – a piece of something indescribable, compressed to a few thou and stuck to the mounting flange with the result that the drum tilted fractionally. **M.P.**

### **Ferguson 3V00**

The fault with a Ferguson 3V00 was severe herringbone patterning on the chroma on its own recordings only – prerecorded tapes played back o.k. The chroma record current control R2 on the pre-rec board was set too high. **M.P.**

### **Ferguson 3V29**

There was no capstan servo action with this Ferguson 3V29, and a check showed that there were no off-tape control pulses at TP2 (adjacent to IC2) even with a

prerecorded tape. IC2's supply pin had a 50Hz waveform on it, and this varied if the head was slowed down! The fault was due to the HA13008 head motor drive i.c. drawing excessive current from the supply, though it was otherwise functioning correctly. **M.P.**

### Ferguson 3V29

The problem we had with a Ferguson 3V29 was gradually increasing noise on playback while the playback f.m. signal, monitored at the test point, decayed to zero. The same thing happened when a prerecorded tape was tried, so we changed the head amplifier etc. i.c. (IC202, HA11724). Unfortunately the fault symptoms remained exactly the same.

The HA11724 also contains the record current amplifier. On record the playback paths from the heads are earthed by applying the E-E 9V supply to the switching transistors Q216/7. These transistors should thus be off on playback, but we found that the E-E 9V line, which should then be at 0V, had risen to 1.5V. The E-E 9V line is switched between 0V and 9V by transistor Q102, which turned out to be leaky. **M.P.**

### Toshiba V8600

A Toshiba V8600 would not accept a tape — it ejected the tape instead of threading it up, though very occasionally it would work. Now pin 5 of the microcomputer control i.c. is fed with inputs from the dew detector and the slack sensor and is normally high. The slack sensor reed switch is normally disengaged until play is selected. As pin 5 of the i.c. was low, we checked this switch and found that it was sticking (permanently magnetised?) until disturbed. **M.P.**

### Ferguson 3V22

The problem with a Ferguson 3V22 was intermittent loss of servo action on record. Checks revealed that in the fault condition no control pulses were being recorded. These are derived from the video signal via a sync separator on the servo panel. The video input to this panel seemed to be o.k., so we changed the AN301 amplifier/sync separator i.c. No change. On examining the video input to the panel more closely however we noticed that there was slight distortion in the region of the field sync waveform — like poor l.f. response.

The machine worked all right with a video input signal, so we turned attention to the i.f. panel. The video is fed out at pin 36 of this panel via an emitter-follower buffer stage (X201). The signal coupling to and from this transistor is via 47 $\mu$ F electrolytics, and the one on the input side (C207) turned out to be partially open-circuit. **M.P.**

### JVC HR7200

Failure to record was the fault on a JVC HR7200 (Ferguson 3V29), and a check at the heads confirmed the absence of an f.m. record signal. Tracing farther back, we discovered that the signal disappeared at the point (pin 1) where it enters the HA11724 i.c. There's a switching transistor (Q209) here — the relevant bit of circuitry is shown in Fig. 1. When record is selected, diode D204 conducts. The voltage at its anode is then just under a volt, and as a result the 4.3V zener diode D208 and transistor Q209 are non-conductive, allowing the record signal to pass through to the heads. The problem was that D208

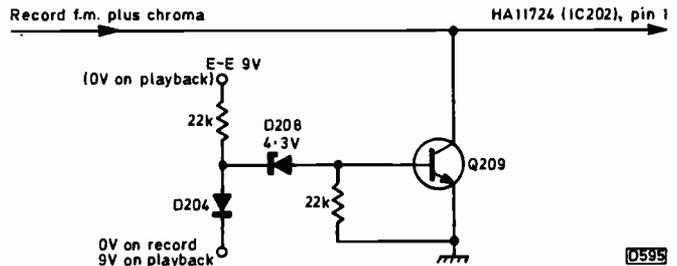


Fig. 1: Record signal muting circuit used in the Ferguson Model 3V29. The circuit is inoperative on playback.

was short-circuit, as a result of which Q209 was conductive. A replacement zener diode restored normal operation. **M.J.C.**

### Grundig 2 x 4 Super

The trouble with a Grundig 2 x 4 Super looked like a servo fault — the picture disappeared into noise every few seconds — and we found that the ramp waveform at the drum servo test point disappeared when the fault occurred. This waveform comes from a PLL which is supplied with a reference frequency from the DTF module. It was quickly proved, by substituting known good panels, that the fault wasn't in either the servo or the DTF sections of the machine.

Our next step was to look at the supply lines with a scope. This revealed that the 20V supply to the servo board had about 0.5V of very high-frequency ripple (at some 20kHz) on it. A 15V supply is derived from the 20V rail via a UA723C/chopper transistor arrangement, and it looked as if some of the switching signal was getting out. The 20V line smoothing was checked to no avail, and we next found that the ripple was of higher amplitude on the output side of the 15V regulator. Whilst making checks in this area we noticed that C455 (100pF), between pins 4 and 13 of the UA723C i.c., had never been fitted. **M.P.**

### Ferguson 3V30

The fault with a Ferguson 3V30 was erratic lines of interference on playback. Now if a normal picture (with tracking lines) was present with pause selected (not freeze frame) then the fault would be in the capstan servo circuit. A check at TP5 on the servo panel showed that the capstan servo trapezoid waveform was present, but there was no sample pulse on the ramp. The off-tape sample/control pulses pass through IC2 and then inverter transistor Q1 before being applied to the HA11711 servo i.c. They were present at the control head but vanished at the base of Q1. Cold checks revealed that C55 (0.01 $\mu$ F), which is connected between Q1's base and chassis, was leaky, measuring some 120k $\Omega$ . Replacing C55 restored the sample pulses and a stable picture. **M.J.C.**

### Ferguson 3V16

A customer brought his Ferguson 3V16 along for repair one wet and windy day — it was encased in a duffle bag. His complaint was that the machine was "completely dead — probably only the fuse". Well this was the longest fuse change I've ever come across. It was indeed a fuse — the thermal fuse buried deep inside that most inaccessible component the mains transformer. A new transformer was ordered and fitted, restoring normal operation, but can

anyone say why JVC in their wisdom bother to have a thermal fuse that can't be reset?  
**M.J.C.**

### **Mitsubishi HS303B**

Last month I mentioned the trouble we'd had with a brand new Mitsubishi HS303B whilst it was still in the showroom. Then we sold it. Last week it came back again. This time when we switched it on the pause and stop lights both came on and eject wouldn't work — we couldn't even load a tape.

We started with the errant pause light. All the function indicators are driven by the MC14174BCP i.c. IC500 under the control of one of the microcomputer i.c.s, IC5A0 (TMS1400/MP7309). The pause light was on because pin 20 of IC5A0, which drives pin 14 of IC500, was high instead of low. Further laborious checking through the rest of the control circuitry (how a good

circuit description in the manual would have helped!) revealed that the other symptom, no eject, was due to the same thing. So we unsoldered pin 20 of IC5A0 to check whether it was the source of the high signal. It wasn't. An internal fault in IC500 was the cause of the trouble.  
**R.R.**

### **Ferguson 3V23**

VCRs don't seem to be prone to stock faults, apart from various mechanical weaknesses (i.e. take-up idlers, motors, etc.). We've recently had three cases of Ferguson 3V23/JVC HR7700 machines with unstable pictures however, and in each case the cause was the 4.433MHz crystal on the servo-2 panel. The output from the crystal oscillator is counted down by IC1 (AN6342) and used to produce the 50Hz reference squarewave for the drum servo circuit.  
**M.J.C.**

# **Fault Report**

*Richard Roscoe, Mick Dutton and  
George R. Wilding*

### **Dead Deccas**

Our winters here in Cornwall always take their toll of triplers and line output transformers — especially in the Decca 80 and 100 series chassis. These sets have a couple of evil and potentially expensive tricks it's worth knowing about. For instance, it's quite common for the tripler to fail and the mains fuse to blow. If you replace the fuse for test purposes it can last just long enough for the faulty tripler to kill the output transformer and often the TBA920 sync/oscillator chip and output transistor as well. So we follow a very strict procedure when we get a call to one of these sets with no sound or raster and the 3.15A mains fuse (on the tuner panel) blown.

First we check the bridge rectifiers D600-3 on the power supply board. One or more of these often goes short-circuit. If they haven't we swing up the main chassis, remove the screen from around the line output transformer (one screw) and disconnect the tripler from the transformer before fitting a new fuse.

We then switch on — keeping our hand on the switch. If the sound comes up and the line output transformer produces a spark, the damage is confined to the tripler alone. Again we breathe a small sigh. If nothing at all happens we fit a new TBA920 sync/oscillator chip and try again. If we hear a hum from the input choke we switch off fast and don't breathe any sighs. The line output transformer will certainly have failed. When replacing the transformer we check the line output transistor and the diodes on the panel, but provided the precautions outlined above have been observed these usually survive — especially the more rugged BU208A transistor used in the 100 chassis.

If the transformer has failed we always change the tripler as well. Even if it seems to be o.k. it won't last long and it will probably kill the new transformer when it does fail. We also carefully check the soldering of all the plug pins on the line output panel, since dry-joints here are often the cause of line output transformer failure in the first place.

This simple procedure takes care of 95 per cent of the cases of blown mains fuses we've had to deal with on these

chassis — and does so at minimum expense in terms of replacement parts.  
**R.R.**

### **Intermittent Hitachis**

We've had trouble with several fairly new Hitachi sets recently — ones fitted with the NP81CQ Mk. II chassis. In each case the symptom has been a tendency to fail to start, though once the set gets going it will run quite happily and can't be induced to stop. John Coombes (Fault Report, December 1982) mentioned dry-joint trouble on the earlier NP81C chassis, which is very similar. We've also had that (dry-joints around the line output transformer), but the situation was slightly different in that the set could be made to start and stop.


The cause of the problem with the more recent sets has been traced to the soldering of the chopper transformer's pins (T901), especially pin 4. It seems that the soldering here must be perfect — any small resistance at this point causes heating as a result of which the joint deteriorates further. Eventually the point is reached where the ability of the power supply to start up is affected, though once it does start the connections are good enough to keep it going.

We've found that the best cure is to remove T901 completely and scrape all the pins clean before carefully resoldering them.  
**R.R.**
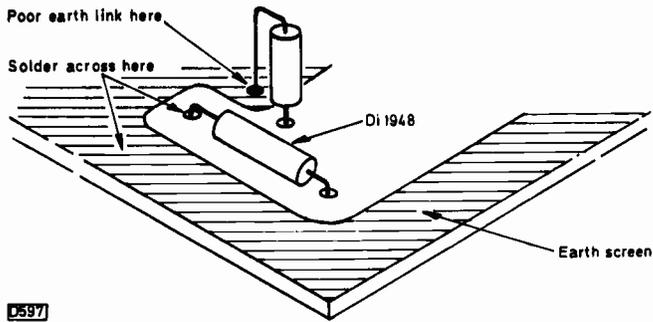
### **Grundig Gremlins**

Here are a couple of faults that crop up time after time with Grundig colour sets. If you get these symptoms it's odds on that the culprit will be the same.

**Sound o.k., blank screen:** This applies to sets fitted with the 29301-046.02 RGB module (Models 8632GB and 8232GB for example). The fault is usually intermittent: the picture will dramatically disappear and reappear at random, and it can be infuriatingly elusive, showing up perhaps only once in a while. The cure is simple however. At the top of the RGB module, above the three output stages, there's a zener diode (Di1948). It's anode is rather poorly connected to earth via the lead of an adjacent



0597

Fig. 1: Location of a very common source of trouble on later Grundig colour-difference output modules.

resistor through the board — this link gets lost. Solder the diode to the top earth screen (see Fig. 1) without removing it from its existing position and you'll experience no further trouble.

**No colour or intermittent colour:** This fault occurs on a large number of models (e.g. 6210GB, 6610GB, 8632GB, 8232GB and 1510B) fitted with colour decoder module type 29301-024.01. The cure is to change both the  $0.1\mu\text{F}$  decoupling capacitors C861 and C863. They cause the fault by going slightly leaky — in fact we've had so much trouble with them that we fit replacements whenever one of these sets comes into the workshop for whatever reason.

We had a 1510B portable however where replacing these capacitors failed to restore the colour — in fact a whole new decoder module failed to do so. The fault turned out to be on the colour-difference output panel. Unlike most modern chassis, this Grundig chassis employs colour-difference drive to the tube's grids/cathodes. The cause of the fault was that the three colour-difference output transistors were cut off due to a break in the track of the preset R587 ( $200\Omega$ ) via which their emitter circuits are returned to chassis. The colour-difference drive coupling capacitors C574/584/594 prevented the altered d.c. conditions affecting the tube's biasing, with the result that it displayed the luminance signal normally. **R.R.**

### Decca 30 Series Chassis

A Decca hybrid set (30 series chassis) would work perfectly for about half an hour after which faces in particular and the picture in general would suddenly turn a ghastly green. The ident amplifier was obviously working, otherwise there would have been no turn-on bias for the chroma channel via the colour-killer transistor TR208. Drift of the ident coil L205 can cause incorrect operation of the PAL switch, which is inside the MC1327P i.c. The coil turned out to be o.k, the fault being cured by changing the chip. **G.R.W.**

### Ekco T554 Portable

An Ekco T554 14in. monochrome portable came in with field troubles — unsteady lock, random jitter and bottom cramping. The voltages in the field timebase seemed to be about right, so we put a scope on the output. Riding on top of the field sawtooth was a lot of random, low-frequency noise — it looked suspiciously like transistor noise.

The field generator circuit is a bit unusual. There are two transistors, TR501 and TR502. TR501 is labelled "vertical oscillator" and provides the discharge action. TR502 acts as a Miller integrator so that the field charging

capacitor C506 produces a linear ramp. Anyway we found that TR502 was faulty, but we didn't have a 2SA609E in stock (who has?). A BC212, carefully fitted the right way round, proved to be a suitable substitute. It cured all the field troubles, but the steadier display revealed that all was not well with the line sync — the verticals were decidedly wavy, though the line lock itself was good.

It's said that lightning never strikes twice, but in this case it did. The sync separator transistor TR209 is another 2SA609E and was also noisy — the noise was passing through the flywheel sync circuit. Another BC212 put an end to that. Incidentally if, like us, you don't have a manual for the T554, you'll find that the circuit for the Teleton TW12BS applies. **R.R.**

### Thorn 1500 Chassis

A Thorn monochrome set fitted with the 1500 chassis produced ample sound, which was undistorted, but the picture — which could barely be locked in either direction for more than a minute — was weak with little definition or tonal graduation. The sound signal is tapped off at the collector of the video emitter-follower transistor VT8, so the obvious conclusion was that the fault was in the following video output stage or the coupling networks between VT8 and the tube's cathode. As a start we checked the voltages in the emitter-follower and output stages. These were correct, so the operating conditions in these stages were normal.

There are two video coupling capacitors, C37 ( $64\mu\text{F}$ ) between the video emitter-follower and output stage and C40 ( $0.47\mu\text{F}$ ) between the video output transistor and the tube's cathode. The latter was ruled out since if open-circuit it would not affect the sync. If C37 had partially dried up on the other hand the h.f. response would still have been acceptable.

Attention was directed to the i.f. strip therefore, and it was discovered that the final i.f. transistor VT7 was open-circuit between its collector and base. This transistor is located just under a small clip-on screening can near the bottom of the chassis — if care isn't taken, the securing clip breaks off. Replacing it restored normal results, with first class timebase locking. The sound signal had obviously managed to get through via the shunt capacitance present, though the video signal had been distorted and attenuated. **G.R.W.**

### Bush BC6338

The problem with a Bush Model BC6338 (Z718 chassis with touch tuning) was that the channel selector was stuck on channel one, with no tuning ability. The touch sensor contacts looked clean, so we decided to change the ETT6016 selector i.c. This enabled us to change channels, with the appropriate neons lighting up, but there was still no tuning ability. The 33V tuning supply was correct, but the voltage on the tuning line was also 33V. A check at the slider of the selected tuning potentiometer showed that it did what it was supposed to do, i.e. vary from zero to approximately 30V, but this voltage was not being applied to the tuning line via the blocking diodes 9D1-11. The voltage at pin 8 of the i.c. was next found to be low, and on checking back we found that the 180V supply at pin 4 of 9Z1 was also low, at approximately 30V. This voltage comes via 1R116 ( $7.5\text{k}\Omega$ ) on the Varicap tuner panel, and a check here revealed that 1R116 was virtually open-circuit. **M.D.**

# Teletopics

## EUROPEAN MERGERS

The proposed link up between Grundig and Thomson-Brandt – as reported in our February issue, the French state-owned electronics giant Thomson-Brandt had signed an agreement of intent to purchase the 75.5 per cent of Grundig not owned by Philips – is now off, having been vetoed by the W. German Federal Cartel Office on the grounds that a Thomson-Brandt/Grundig merger would have 40 per cent of the W. German CTV market and 25 per cent of the W. German VCR market. Instead, Thomson-Brandt now propose to take a 75 per cent controlling interest in Telefunken, whose ailing parent firm AEG-Telefunken has been in a form of receivership. It's not expected that the Thomson-Brandt/Telefunken link up will be vetoed by the Federal Cartel Office, even though it will have some 30 per cent of the W. German CTV market. Thomson-Brandt already own Saba and NordMende, each of which have ten per cent of the W. German CTV market, while Telefunken's share of the W. German CTV market increased from six to ten per cent over the past year.

This leaves Grundig, which has been making substantial losses during the past two years (DM 187m in 1980-81 and DM 35m in 1981-82, though a profit for the year 1982-83 is expected to be announced), in a difficult position. The speculation is that Philips might wish to increase its stake in Grundig, to which it is an important components supplier as well as the two firms being joint developers of the V2000 VCR system, though this might raise fresh problems with the Cartel Office (stringent conditions were imposed when Philips originally acquired 24.5 per cent of Grundig).

The Thomson-Brandt/Telefunken link up has interesting implications in the VCR field. A merger with Grundig would have given Thomson-Brandt an interest in the V2000 system. Telefunken however are part of the J2T joint venture partnership (with Thorn and JVC) manufacturing VHS machines in Europe (in W. Berlin and Newhaven), while Thomson-Brandt have been importing JVC machines for sale in France and had been planning to start assembling VHS machines in about a year's time. The position of the VHS system in the European market has thus been given a considerable and unexpected boost.

In a recent move Thomson-Brandt established the European Electronics Corporation as an umbrella organisation for the activities of Saba and NordMende.

## JAPANESE-EEC VCR AGREEMENT

The agreement between the Japanese Ministry of International Trade and Industry and the EEC Commission to limit the export of VCRs (for one year initially) to Europe and to set "floor" prices for Japanese VCRs has now come into effect. As far as the floor price system goes, three classes of machines (basic, mid-range and top-range) have been established, with floor prices of £195, £240 and £280 respectively f.o.b., i.e. delivered to the docks. Decisions about how the market is to be shared out amongst the various Japanese VCR manufacturers and how the machines will be allocated between countries have not been announced. To meet the requirements of the General Agreement on Tariffs and Trade, all these matters have to

be decided by the Japanese unilaterally.

The net result in the UK, taken in conjunction with the recent fall in the value of the pound, is expected to be a rise of £100 or more in VCR prices with corresponding increases in rental charges. Rental at present accounts for 60 per cent of VCR deliveries to consumers, and it has been suggested that the price increases could boost this percentage. Stocks of machines are low at present, and with distributors anxious to increase profit margins price rises in the short term could be quite sharp. The long term prospects will depend on market conditions, the present excess Japanese VCR manufacturing capacity, whether the V2000 system manages to establish a firm position in the market, and what happens to the agreement under its proposed second and third years of operation.

## THE COMPACT DISC

Not a TV subject perhaps, but one nevertheless very much of interest to dealers and technicians: the compact (4 $\frac{1}{4}$  in.), laser scanned, digitally recorded audio disc which has now been launched in the UK and three other European markets. The system was developed jointly by Philips and Sony – one could say that it's an offspring of LaserVision. The sound is two-channel of course and the discs have a playing time of an hour per side. The players provide an output of some 1.5V at 500Ω. The great advantages are the elimination of mechanical problems on the signal pick-up side and the clean digital signal. A frequency response of 20Hz-20kHz and a dynamic range of greater than 90dB give a rough guide to the excellent quality of which the system is capable.

Players from Philips, Sony, Fisher (Sanyo), Hitachi and Marantz (a Philips subsidiary) have so far been announced in the UK, with prices in the range of roughly £500-£550. Over thirty eight manufacturers worldwide have taken out licences to produce players. The discs cost around £10 each, and an expanding catalogue of titles from several record companies is already available. Sony expect the UK market for players to be around 40,000 during 1983.

Philips are pressing for a special 19 per cent EEC tariff on the players (the tariff on conventional audio equipment is half that), claiming that Far Eastern manufacturers are planning to flood the European market.

## TAPE STORAGE

BASF have issued some simple guidance on video tape storage. The temperature should be 20-22°C and the relative humidity 50-60 per cent. Major temperature fluctuations should be avoided, as of course should be exposure to magnetic fields. Upright storage is best, to prevent slippage, and an extra plastic bag is recommended when tapes are going to be stored for any length of time.

## TSR VACUONICS

The Scottish c.r.t. rebuilding firm TSR Vacuonics Ltd. is particularly interesting in being able to process a very wide range of tubes including Trinitrons, the latest Hitachi tubes, and those used in monitors and games machines. The company assemble their own guns and offer a 7-10 day turn round on an exchange basis, though an off-the-shelf service is envisaged when sufficient glass is available. OTV of OTV House, 144 Lea Bridge Road, London E5 9RB have been appointed distributors in the London area.

TSR are now investigating the possibility of rebuilding VCR heads, and have had talks with a number of large national rental and sales companies who have expressed interest in the idea. The process involves laser cleaning of

the gap and rebonding new ferrite pole pieces. It's hoped to be able to provide such a service by the end of the year, initially offering VHS and Betamax heads at £10-£12 each. If there's sufficient interest, TSR would hope to extend the service to cover V2000 heads.

### **BBC-UNISAT DBS AGREEMENT**

The BBC's satellite TV service, which is due to start in 1986, came a step closer with the signing of an agreement on the provision of the satellites by Bryce McCrirrick, BBC Director of Engineering, and Alan Jeffries, Managing Director of United Satellites Ltd. (Unisat). Unisat is jointly owned by British Telecom, British Aerospace and GEC and will be responsible for building and launching two satellites, the first to be operational and the second an in orbit spare. As an additional safeguard, a third satellite will be made available ready for launch. The service's footprint will cover the UK and parts of W. Europe, and the power output will be suitable for high-quality reception by individual households via suitable receivers and dish aerials of less than one metre diameter. The agreement covers a period of operation lasting at least seven years.

The satellites will carry transmitters for the two BBC DBS services. DBS-1 will be a subscription channel carrying feature films and other attractions. DBS-2 will have an international flavour. There will also be a number of digital sound channels, providing stereo TV sound and some high-quality radio channels.

British Telecom will be using the satellite to provide various facilities, including the distribution of TV programmes and feature films to local cable TV networks. This will be entirely separate from the two high-power channels used by the BBC.

The IBA developed C-MAC colour signal encoding system will be used for the two BBC channels. C-MAC was recently demonstrated by the IBA in W. Germany, at the invitation of the German Post Office. About one hundred senior broadcast and telecommunications engineers saw signals sent from Crawley Court to Darmstadt via the European Test Satellite (OTS). A presentation was also made to representatives of German industry, the Post Office and the broadcasting research institute (IRT).

### **THE BATC**

The British Amateur Television Club will be holding an exhibition of amateur television at the Post House, Leicester, on May 22nd. The doors will be open at 10 a.m., admission is free and all will be welcome. Attractions will include the BATC outside broadcast unit and demonstrations of both fast- and slow-scan television. There will be the usual trade stands plus a comprehensive supply of the Club's books and PCBs. The Post House Hotel provides a reasonably priced Sunday lunch and special half-priced rooms are available for people attending the exhibition.

The latest BATC publication, "TV for Amateurs" by John L. Wood, G3YQC, is available from BATC Publications, 14 Lilac Avenue, Leicester LE5 1FN, at £1.50 plus 25p post and packing. It's main aim is to serve as an introduction to the world of Amateur TV, but in doing so it provides much useful reference material and a lot of practical information (circuits etc.). Excellent value and highly recommended.

### **ELECTRACK**

A new mains plug-socket system that should prove useful where large numbers of mains connections are required, in

workshops and retail showrooms for example, has been announced. Called Electrack, it consists of a slim aluminium track carrying three copper conductors along which plugs can be inserted at intervals of either 100 or 200mm. It's totally enclosed, and the safety aspect is enhanced by the fact that contact with the mains supply is completed only when an Electrack key plug is inserted and rotated through 90°.

The track will be available in various standard lengths from 600 to 3600mm, and can easily be cut to any required length. By adding a clip-on housing it becomes a skirting system. It can also be used as a flush floor distribution system. Apart from the improved safety aspect, the advantages of Electrack include much increased flexibility plus a reduction in installation time and costs.

Electrack will be made available through wholesalers later this year. Details can be obtained from Electrack International Ltd., 45 High Street, Kingston-upon-Thames, Surrey KT1 1LQ (01-546 7799).

### **NEWARK VIDEO CENTRE**

Steve Beeching's eagerly awaited book "Domestic Videocassette Recorders" can be obtained from Steve's Newark Video Centre, 108 London Road, Balderton, Newark, Notts (0636 71475) at £14.50 plus post and packing. You might even be able to get an autographed copy! We hope to review the book shortly.

Steve's two-day weekend VCR servicing courses are still being held from time to time as circumstances permit. The next one is on May 14-15th.

### **TV R & D**

Much work is being done in research departments on methods of processing video signals in digital form for TV receiver applications. Some details of one approach were given in our November 1981 issue. What are the advantages? For one thing the signals can be cleaned up, improving a receiver's performance, the disadvantage (at present) being the added complexity of converting the transmitted signal into a digital one and then converting it back to analogue form to drive the c.r.t. This disadvantage could be eliminated with a fall in the cost of the digital circuitry required. An interesting prospect is the use of digital techniques to increase the number of lines. Converting from 625 to 1,250 lines in the receiver would greatly improve the resolution and could be done using the techniques employed in 525-625 line standards conversion. The idea is to create the extra lines by averaging the information carried by successive pairs of transmitted lines. Eliminating interlace would improve matters further.

Amongst the firms understood to be working on this are ITT, Philips, RCA, Hitachi and Sony. In a recent issue of *Radio-Electronics*, an RCA spokesman was quoted as saying that a compatible high-resolution system would come "in this decade".

The aim of the 5-D Corporation is just that - a 3-D display plus surround sound. The breakthrough claimed is plans for a camera that provides compatible 3-D pictures, i.e. those viewing without special blue/red spectacles see the picture without the usual double image effect. Another step contemplated is receivers that don't require special glasses to be worn by the viewer.

US set maker Zenith has developed a self-converging colour projection TV system. The three (red/green/blue) projection tubes are mounted in line, the outer tubes having angled screens that distort the images to com-

pensate for the distortion introduced by off-centre mounting.

### GLARE

Last month we mentioned a filter to reduce VDU operator eye strain. An alternative approach is to use a spray on treatment. An anti-glare treatment kit called Glarego has been introduced by Vision Products, Unit 10, Wessex Road, Bourne End, Bucks SL8 5DW, and is said to provide a lasting non-reflective surface on TV screens, computer terminals, video games and glass-fronted pictures. It doesn't damage the screen and is easy to remove. The screen is first prepared with Cleanscreen spray, the Glarego spray (which contains anti-static dust repellent) then being applied. The suggested price of the kit, which includes a mask and lint-free cloth and enough spray to treat three screens, is £7.95 plus postage.

### SATELLITE TV LTD

Satellite TV Ltd., which was originally established to provide a European TV service via a spare transmitter aboard the OTS satellite, has been allocated one of the UK transmitters on board the European Communications Satellite ECS-1 which is due to come into operation by the end of 1983. Satellite TV Ltd. is at present in the process

of raising funds from institutional investors for the further development of its service.

### IN BRIEF

Under a deal with J.J. Silber, the company that acquired the Murphy brand name from Rank, the Rediffusion subsidiary Doric Radio will in future be marketing Murphy TV sets . . . ITT Consumer Products is to be taken over by STC, which became independent of its former US parent company ITT last October . . . Sony is due to release its 2in. Watchman flat-screen TV set in the UK shortly. The set measures  $7\frac{3}{4} \times 3\frac{3}{8} \times 1\frac{1}{2}$ in. and is expected to sell at around £200. According to a survey carried out by Oracle, the number of UK homes equipped with teletext sets grew from 300,000 to 800,000 last year, a household penetration of 3.9 per cent. About 16 per cent of sets now being sold/rented are teletext models, the percentage rising with screen size . . . A further round of talks on establishing a new world standard for 8mm video, i.e. for the coming generation of portable "camcorders", took place in Tokyo this March . . . The recently introduced Mitsubishi portable VCR, Model HS700, is unusual in incorporating a tuner/timer. The suggested price is around £500, the weight 16.3 lb and the dimensions  $16.7 \times 9.1 \times 6$ in.

# Test Report

*Eugene Trundle*

A PERENNIAL problem for those involved in television servicing is the difficulty in deciding whether a line output transformer is faulty, especially when short-circuit turns or internal leakage is suspected. The diagnosis can often be proved conclusively only by fitting a known good transformer, so the traditional drill is to eliminate all other suspects (such as the e.h.t. rectifier/tripler, the scan coils and the secondary supply rectifiers) first. This is time consuming, and the heavy loading introduced by a defective transformer can take its toll of line output transistors and the like whilst the necessarily repetitive tests are being made. All this assumes that no cut-out or trip is banging away to confuse the situation further!

Many testers have been devised over the years to overcome this problem. The idea is that they test the line output transformer (or the power supply transformer in switch-mode circuits) independently, usually in situ. They work with varying degrees of success, but none has been infallible. Most of them work by acting as a threshold oscillator, with the suspect line output transformer incorporated in the feedback path: if short-circuit turns are present, the damping this introduces prevents oscillation and the transformer is thus condemned. Because there are so many different types of line output transformer in use however, while the effective load on them in situ varies from model to model, a degree of doubt is inevitable and diagnosis cannot be certain in every case.

### Dynamic Testing

The Bi-Pak line output transformer tester works on a quite different principle. The idea in this case is to energise the transformer in much the same way as when it's working under normal conditions and see how it performs.

Two or three turns of wire are wound around a winding or limb of the suspect transformer to form a primary which is energised from the mains-powered tester. The transformer's windings now all act as secondaries, and the voltages induced in them are proportional to the drive level. A damped transformer will not respond, and will show no signs of life.

### Construction

The Bi-Pak tester is fitted in a small plastic box measuring  $10 \times 7.5 \times 4$ cm. It has a spring-loaded "on" button, a rotary "drive" knob and a pilot lamp, along with two sockets. The lead which forms the "primary" of the transformer being tested is plugged into these two sockets – the lead comes with the tester. There's just over one metre of mains cable.

The tester's precise mode of operation is not immediately obvious for the very good reason that the internal components are partially potted in epoxy resin! Oscilloscope tests suggest that the incoming mains waveform is chopped by some thyristor like device to produce short-duration output current pulse spikes with very fast rise times indeed – I measured 15V peak-to-peak across the ends of the test lead. During the test each spike rings the transformer to produce a series of decaying bursts of oscillation at about 25kHz. This is below the resonant frequency of the transformer itself, and means that there's probably a tuning capacitor inside the mystery box!

### Operation and Tests

Operation is very simple. The lead supplied is looped a couple of times around the windings – or a yoke limb – of the suspect transformer, be it in or out of the set. The go button is next pressed, then the drive control is slowly wound clockwise. A good transformer will respond with signs of life such as whining or buzzing. There will be a healthy corona discharge from the overwinding, and often sparking around the primary winding. A neon held several

millimetres away from the transformer will light up. A dud transformer on the other hand will show no signs of life.

I started off with a good selection of new stock transformers, ranging from types used in small monochrome portables to large multi-winding types used in colour sets. The first thing I discovered was that the tester needs a "stiff" mains supply – it didn't work at all when fed from the bench isolating transformer (a 500W type). On raw mains however the results were satisfactory – the response from most of the new line output transformers was good. I was a little alarmed however to find that even at the minimum drive setting many transformers produced internal and external sparking between points up to 8mm. apart! This happened on pressing and releasing the go button, and I made a mental note to be wary of this when making in situ tests on transistor receivers.

Amongst the stock were jellypot transformers of the type used in many Thorn chassis. These couldn't be tested because of the impossibility of setting up an effective primary winding. The same thing applied to many types of switch-mode power supply output transformers. Most diode-split line output transformers have an exposed ferrite limb, and I had specimens of Mullard, Hitachi and National Panasonic manufacture. Unfortunately on all these the plugs at the end of the lead supplied were too large to go through the gap between this limb and the heavily-sheathed winding block. By improvisation however I was able to set up a test and was rewarded with a beautifully buzzing transformer, with little "snicks" from the e.h.t. and focus connector wells to indicate a good transformer. This required three primary turns and a fairly high drive level, probably due to the foil-type windings used in the particular specimen I chose for the test.

I found that small conventional transformers were very lively, and in the case of a transformer for the ITT VC300 chassis (with e.h.t. rectifier and reservoir capacitor attached) I had no difficulty in raising an e.h.t. output of 15kV (way above normal) with the tester's drive setting at one third – this was with just two turns of the test lead wound on! An ITT FT110 line output transformer produced 10kV pulses (normal operation produces 8.5kV pulses) with modest drive, and 15kV was registered at a high drive level, all with a two-turn primary winding. The transformer used in the Thorn 8500 chassis has a full-voltage overwinding, and with the tester's drive control advanced a little the transformer was lively: at about half drive 4cm. sparks were leaping from inside the e.h.t. connector sleeve to the transformer's metal frame . . . So it's important to heed the warning in Bi-Pak's instructions to avoid excessive drive levels.

Having exhausted the possibilities of testing good transformers out of circuit, I tried introducing short-circuit turns on various types of transformers by winding a loop of wire around the ferrite core and shorting together the free ends. A single short-circuit turn merely called for a higher drive level than before to get the same results. Two short-circuit turns were (in many transformers) betrayed by the need for an abnormally high drive setting before the sparks began to fly. In most cases three short-circuit turns gave an unambiguous dud indication. Strangely enough however an ITT CVC20 transformer could be made very lively at low drive settings with its five-turn c.r.t. heater winding dead short!

The dustbin was next turned out and a rich harvest of dead line output transformers was found. The first, from an ITT CVC32 set, tested dud, but as the drive was wound up the tester's 2A mains plug fuse blew. A 3A replace-

ment fuse was fitted and held out for the remainder of the tests, which confirmed faulty line output transformers from the Decca 100 chassis, the Philips G8 and the Pye 725. The second transformer from a G8 let us down however: it was known to have short-circuit turns in the overwinding, but on test a lively response was seen at the main winding, with sparks in all directions – the overwinding was quite dormant of course.

### In-circuit Testing

We always have plenty of working TV sets on test, and several were tried with the Bi-Pak tester. The short mains lead proved to be very inconvenient – the instrument has to be very close to the transformer under test, and it was not always easy to get the transformer within a metre of the mains socket.

In-circuit testing was possible and fruitful with many sets, and good results were obtained provided normal checks around the line output stage had previously eliminated obvious faults. For example, a leaky BU208 line output transistor (500Ω collector-to-emitter both ways) prevented an o.k. indication with a good transformer, as might be expected. The tester was found to be reasonably tolerant of normal loads such as the scan coils and the tube heaters.

I was unlucky with the majority of Japanese colour sets in at the time, either because the transformer was physically incompatible with this sort of testing, for the reasons described above, or because it was buried inside a substantial and well battened down screening can. A known working Pye CT200 didn't give a good indication for reasons that I don't know, and the neighbouring Thorn 9800 was likewise disinclined to co-operate, maybe due to the foil/diode-split type of transformer used. In both these cases removal of the c.r.t. base (to disconnect the heater load) didn't help matters. I must confess that I shied away from in situ testing on certain sets for fear of component damage, though this is not to say that such damage would have actually happened.

### Conclusion

As mentioned above, there's no such thing as an infallible line output transformer tester. The Bi-Pak tester is no exception to this rule. It's a lively device, perhaps a little too lively, but if used with care it's unlikely that anything untoward will happen. The sorts of transformers it won't test are the ones that generally don't fail anyway. Use of the tester will provide experience of what it can and cannot do, which counts for a lot in interpreting results. One thing is for sure – if it fails for any reason it's irreparable due to the encapsulated circuit.

It's a useful diagnostic tool and is worth having, but if it was mine I'd replace the mains lead with a three metre one before putting it in the toolbox. I can't honestly say that it's more effective than the i.c. oscillator type, and where the transformer under test is not physically suited to this particular mode of testing, or where it's buried in heavy screening, the alternative type of tester has the advantage. It seems rather over priced at £41.40 (including VAT), though there's no doubt that its cost will be saved (in terms of labour time and materials) once a few tests have avoided the need for line output transformer replacement.

The tester is available from Bi-Pak, PO Box 6, Ware, Herts (telephone 0920 3182).

# Vintage Video: Baird's Discs

David K. Matthewson, Ph.D., B.Sc.

"PICTURES from a silver disc" – so runs the Philips advertisement for the LaserVision disc system. The concept of LaserVision involves the use of advanced technology, which Philips and now Pioneer are doing their utmost to exploit. The idea of recording pictures on disc is far from new however. Indeed the history of video discs goes back to the early pioneering days of television. John Logie Baird conceived the idea of storing TV pictures on disc for two reasons. First to have a means of demonstrating television without too much trouble, and secondly to enable viewers to use their televisions – the mechanical TV receivers used in the early thirties – when programmes were not being transmitted.

Baird's original TV system was a mechanical one, using a Nipkow disc at the studio and at the receiver to produce a scanned picture. There were thirty vertical lines and 12½ pictures per second, with no interlacing. A photocell was used to sense the light at the studio end, a neon in the television being modulated at the receiving end.

Because of the small bandwidth of the signal – the maximum frequency was about 13kHz, while for broadcast transmission it was around 9kHz – it could be recorded on a conventional 78 r.p.m. gramophone record. Baird's patent number 289,104, filed on October 15th, 1926, describes a disc cutter and reproducer (see Fig. 1) for use with his proposed TV system. The patent includes details of the disc's groove structure, which was envisaged as consisting of two parallel sections, one carrying the sound and the other the vision signal. A double-headed pickup for reproduction was also described, and Baird coined the name Phonovision for the system. In practice Baird never seems to have developed the double-groove system, the few surviving examples of Baird discs all being single grooved with no sound track.

Problems seemed to have arisen with the disc cutting process when trying to record a signal with a lot of high-frequency content. Other experimenters continued to work on the idea however, and by the mid-thirties it seemed clear that there were two alternatives: using a conventional type of record and player you could have either imperfect reproduction of pictures with a fair amount of detail, or reasonable accuracy if the subject was a simple one. The Major Radiovision Company of London, run by R.O. Hughs, adopted the latter option, and in June 1935 were selling their 30-line TV discs by mail order (at 7/- plus 6d post and packing) and in Selfridge's London store. The subject matter was not particularly inspiring, consisting as it did of ten still cartoons: the "artistes" apparently included Marconi, Harry Lauder, Charlie Chaplin and Stanley Baldwin. The discs were double sided, ran for just six minutes per side, and used different modulation depths on each side to allow the user to experiment with different types of pickup. Major Radiovision also suggested that by reversing the pickup leads you could obtain negative pictures.

Quite a few televisions were around in the mid-thirties. Plessey had produced about 1,000 for the Baird Company, and kits were available from firms such as Peto Scott. There are no sales records for the discs, so we shall never know how popular they were. They were certainly

not a financial success, and Major Radiovision went out of business shortly afterwards.

One of the main problems with Baird's mechanical TV system was poor sync. No sync pulses were transmitted, reliance being placed on the fact that the signal fell to black level at the end of each line and on motor speed controls. Needless to say the discs suffered from similar

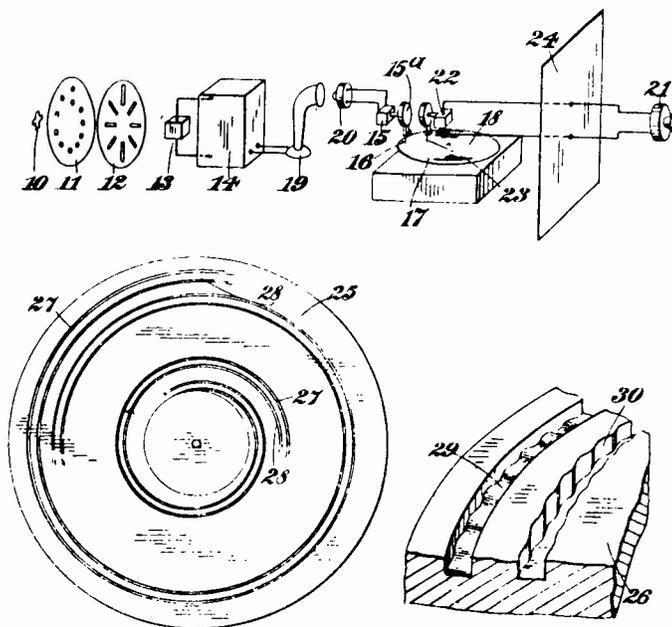


Fig. 1: Baird's 1926 ideas for a video disc recorder and player – Phonovision. The lower part of the diagram shows details of the proposed twin-groove arrangement. (10) Subject matter. (11) Nipkow disc. (12) Light-interrupting device. (13) Photocell. (14) Amplifier. (19) Microphone. (20) Pick-up transducer. (15a/16) Vision signal groove cutter. (21) Sound pick-up microphone. (22/23) Sound signal groove cutter. (18/25/26) Disc. (29) Hill-and-dale modulation for the vision signal. (30) Side modulation for the sound signal.

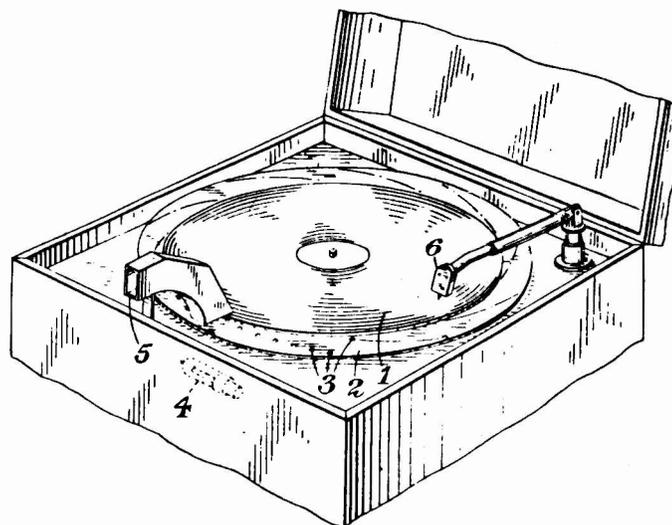


Fig. 2: Baird's 1928 idea for a combined disc player and television. (1) Disc. (2) Combined turntable/Nipkow disc. (3) Scanning holes. (4) Modulated neon light source. (5) Viewing lens. (6) Pick-up.

problems. The television's scanning speed was 750 r.p.m., the disc's 78 r.p.m., and it was necessary to keep the two in step. As with an off-air transmission, this was a tricky and time consuming task.

In April 1928 Baird registered a patent for a complex system in which a disc player and television were linked via a mechanical gear train. It's not known whether he ever built the device, and in October of that year another Baird patent proposed a more elegant solution. This consisted of a combined disc reproducer and viewer, with the record player turntable also acting as the television scanning disc (see Fig. 2). As the turntable/disc were combined, sync could not be lost once it had been set up by carefully

aligning the record with marks on the turntable. The viewer was to watch the pictures, produced by a neon, through a series of lenses. Unfortunately it seems that Baird never built this system either.

In 1966 the BBC "decoded" a Major Radiovision disc, displaying the signal on an adapted oscilloscope. In 1971 the IBA did something similar, this time displaying the output on a renovated television. The 30-line system was finally abandoned for broadcast purposes in September 1935. By August 1936 high-definition television had arrived. The author would like to hear from any readers who may have any further information on Baird type video discs – or even examples!

## A New EHT Circuit

George R. Wilding

THE current Telefunken 415/615 CTV chassis is conventional in most respects, with its self-oscillating chopper power supply which also provides mains isolation, TDA 3560 single-chip decoder, class AB RGB output stages, TDA1670 field timebase i.c. and BU208 line output transistor. The line output transformer is something quite new however.

Line output transformers are nowadays reliable components though a percentage of failures do occur. Tripler breakdown after some years' service is far more common, except in Japanese sets. The transformer is certainly one of the most expensive items in a TV receiver: the pulse windings and secondaries used to provide various supply lines add greatly to the manufacturing cost and increase the insulation problems.

Telefunken decided to do something about this in designing the 415/615 chassis. The aims were to reduce the cost of the transformer, make it as small as possible, mountable without securing screws, and producible by automatic production methods whilst having a power handling capability, reliability and internal resistance equal to or better than conventional designs.

To achieve these aims it was decided to use a half-wave e.h.t. rectifier arrangement. This in itself is not unique of course, but for CTV use the problem of a half-wave rectifier circuit is the high leakage inductance and internal capacitance in the transformer. The result is an e.h.t. system with a high internal resistance.

It was decided therefore to use a transformer with just two windings, the primary and e.h.t. overwinding. The i.t. supplies are derived from the chopper transformer, while a transistor to which the line flyback pulses are fed produces the feedback pulse for the flywheel sync system. The latter is in the TDA1950 sync/line oscillator chip, which also produces the sandcastle pulse used by the TDA3560 decoder i.c. for gating, blanking and clamping.

This decision greatly simplifies the transformer of course, while collaboration with a specialist manufacturer or ferrite cores enabled the cross-sectional area of the core to be reduced by some 25 per cent. The result is a transformer which is extremely compact and light.

The main design advance however is the use of what Telefunken call the "push-pull high-voltage concept". This uses two rectifier diodes, one at each end of the winding as shown in Fig. 1. The action of the circuit is shown in Fig. 2. D1 acts as a conventional peak rectifier when the positive-going flyback pulse arrives at its anode, charging

the e.h.t. reservoir capacitor C2 (tube capacitance). During this time D2 conducts, clamping the bottom end of the e.h.t. overwinding to chassis. At the end of the flyback pulse half cycle the bottom end of the winding swings positively and D2 cuts off. It conducts again when the voltage at its cathode (circuit oscillatory action) tries to swing negatively, thus charging the interwinding capacitance C1. The next time the flyback pulse occurs, D1 sees an enhanced voltage at its anode, i.e. the sum of the flyback pulse and the charge on C1. The circuit thus acts as a voltage multiplier, and the number of overwinding turns can be substantially reduced in comparison with a simple half-wave rectifier circuit.

Even though it's on such a small former the primary winding has only two layers. These terminate in connection pins which together with two snap-on springs hold the transformer securely to the board for soldering. The diodes and the e.h.t. connection are secured to the body of the overwinding and encapsulated in heat hardened epoxy resin.

The focus supply is obtained via a bleed resistor in the tube's anode cap connector. Fig. 3 shows the feedback pulse generator stage.

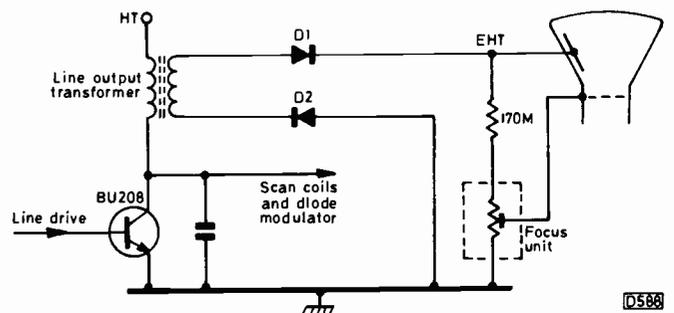


Fig. 1: "Push-pull" e.h.t. rectifier circuit.

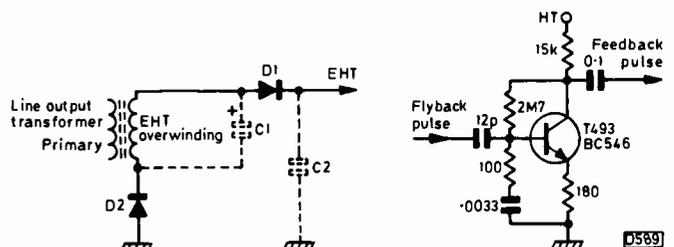


Fig. 2 (left): Operation of the rectifier circuit. Fig. 3 (right): Feedback pulse generator stage.

# DIGITAL VIDEO STORAGE & PROCESSING

**Technology  
Transfer  
California to  
Europe  
via a new  
Waterford  
facility**

An experienced project manager is required for this exciting role.

As our client wants a senior designer with hands-on-experience in real-time digital video processing, exposure to phase-lock loops, micros (Z80 and 8000), 14MHz digital memory and signal processing and control then salary will not be a limiting factor.

Applicants in the first instance to write to Bill Hennessy as adviser to the company:



**E.P.I. CONSULTANTS**  
70 Eccleston Square, London SW1V 1PJ

socket, check back to the line linearity coil L705 and the diode modulator transformer T705. If there's continuity through these points, check the 2.2 $\mu$ F scan correction capacitor C724 which could be open-circuit.

## Field Timebase

The field timebase lives on the right side panel above the Syclops driver etc. A field hold control may or may not be fitted. In the event of field roll, check C406 (47 $\mu$ F) which smooths the supply to the field oscillator.

The field timebase is basically reliable but is inclined to suffer from dry-joints, normally at the transistor connections, i.e. the base, emitter or collector. These poor connections can't always be seen, even under a strong light, so a few moments with the soldering iron may be called for.

The field oscillator consists of a pnp-npn pair (VT401/2) which periodically discharges C405 (0.68 $\mu$ F). The following stage employs a field effect transistor, VT403 (BF256L), the height control being in series with its source connection. The output from this transistor is capacitively coupled to the driver transistor VT404, which has the linearity feedback applied to its base. This is followed by a class AB output circuit which consists of a Darlington pair (VT405/6), a second driver (VT408), the second output transistor (VT407), and the bias diodes W406-8. VT405 is a BC337, VT406 a 16802, VT407 a 16801 and VT408 a BC327. In the event of incorrect or complete loss of height, check these various items.

## Signals Panel

The signals panel closely follows that used in the 8800 chassis, as does the tuner. See the comments made last month. The tuner panel carries the 33V stabiliser (TAA550) and its 10k $\Omega$  feed resistor R15, which takes its supply from the 90V rail. There's no other supply resistor as there is in other models where the source voltage is some 200V.

Grey-scale problems can be caused by the RGB output stage decoupling/compensating capacitors C174/5/7 (560pF later 330pF).

## Beam Limiting

Another similarity with the 8000 series is the beam limiter arrangement. The tube's grids should be at about 23V. If not, check R725 (180k $\Omega$ ) and diode W722 (1N4005). These items can be damaged by a faulty tripler.

## Puzzling Symptoms

Returning to the power supply arrangements, various puzzling symptoms can be produced when the 90V supply smoothing capacitor C715 is defective. If you find that there's marked line pairing ("horizontal lines"), possibly centre foldover and whistling, with intermittent tripping or tripping on channel change, check this item.

## Audio ICs

Finally note that where an i.c. audio output stage is used the i.c. is type SN76033N. These have been in short supply for some time. Any that are available should be snapped up, together with any SN76003s, which are commonly used in various popular stereo units.

# VCR Fault Guide

Photos and text  
by Mike Phelan

## Supplement to 'Television', May 1983

The purpose of this supplement is to illustrate common VCR fault symptoms to assist newcomers with fault diagnosis.

Photo (1) shows the typical effect produced on a VHS or Betamax machine when one of the video heads is not working or there's a fault in the head circuitry. The fault may be on either record or playback: to prove which, check with a prerecorded tape. The cause could be a defective or dirty head or a fault in one of the preamplifiers. If on record only, check the record/playback switch (Beta) or the switching transistors (VHS) – the result is the same, i.e. alternate fields of noise only.

On V2000 machines, also certain early Philips and Grundig VCRs, the drop-out compensator continually reinserts the last line of "good" video, so one head not working gives an overlay of vertical bars as shown in photo (2), due to the last line of video from the good head being repeated throughout the following field.

Similarly, lesser drop-outs due to tape creases, a worn head etc. produce a series of bands of like appearance on these machines, as shown in photo (3).

If the whole picture on a V2000 machine goes into drop-out stripes every few seconds, check on fast search if available – see photo (4). Regularly spaced drop-out or noise bars prove that the dynamic track following is not working – fast search should be noise free, unlike VHS or Beta machines.

### **Incorrect Head Switching**

If the head switching point (controlled by pulses from the head drum or flywheel) is in the wrong place, this will show on the picture as a band of disturbance or, if the switching is too late, the field sync pulses will be mutilated, causing jitter or roll. Photo (5) shows a case where the switching point was way out – it was discovered that the flywheel had been put on in the wrong position.

### **Noise Bars**

Noise bars on a prerecorded tape only – see photos (6) and (7) – point to a fault in the tape path, affecting either the writing angle or the wrap of the tape around the head. Early VHS machines were prone to problems with the mechanical tape loading arm system, as a result of which the tape is not fully wrapped. Troubles on the supply (left-hand) side give a noise bar at the top of the picture and vice versa.

### **Spaghetti**

The fault shown in photo (8), called "spaghetti", can be caused by quite a lot of things, but the basic reason is that the playback f.m. limiter is not coping – due to the f.m. being too low, excessive, noisy or the limiter being misadjusted. Worn heads can give this system, especially with V2000 machines.

### **Worn/dirty Heads**

Worn or dirty heads with VHS and Betamax machines usually produce this symptom – see photo (9). Definition is lost; also the l.f. and h.f. ends of the f.m. spectrum, corresponding to the sync level and peak white respectively, are lost, so we get clogging and "dirty" highlights lacking in

detail. With the cost of replacement heads in mind, a clean is worth a try.

### **Misadjustments**

When a new head has been fitted it's necessary to go through any preamplifier frequency response adjustments – there are usually four with VHS machines, four or six with Betamax machines. If not, the picture may contain excessive f.m. noise as shown in photo (10). It looks like grains of rice on mid-grey areas (spaghetti, rice, what next? – that's nothing to the edible matter with which some customers fill their machines!).

There are also normally adjustments for the f.m. (luminance) and chroma record levels. Excessive f.m. gives a noisy playback picture, possibly with some spaghetti. If greatly excessive the chroma will be affected, as it rides on the edge of the f.m. waveform. See photo (11). Excessive chroma record level will *not alter the saturation*, as the burst and chroma are altered in proportion and the a.c.c. in the TV set compensates. You will however get a diamond pattern effect – see photo (12) – on saturated colours due to cross-modulation between the l.f. chroma and the f.m. If the playback chroma level is too high the effect is different – see photo (13). This time there's a fringe of patterning following all vertical edges – the effect is produced in the r.f. modulator.

### **Unlocked Colour**

When the carrier used for chroma conversion is off frequency, the result is similar to the reference oscillator in a TV receiver's colour decoder being off frequency – see photo (14). A scope is essential for tackling this type of fault.

### **Displaced Colour**

If the chroma is displaced with respect to the luminance, see photo (15), the machine is replaying the wrong number of lines per field. The TV set's flywheel line sync system compensates but the PAL delay line has a fixed period. The cause of the condition can be incorrect tape speed, excessive back tension, a tight head bearing or anything else that loads the head. If the displacement is not steady, suspect the pinch wheel or problems in the tape path. If the head speed is too far out for the TV set to be able to compensate the result is line slip as shown in photo (16). In this case the head servo circuit will have to be checked.


### **FM Modulator Faults**

When confronted with a display such as that shown in photo (17), there are problems in the f.m. sections. In this example the carrier and deviation adjustments in the f.m. modulator had been twiddled. A scope, frequency counter and calibrated power supply are necessary to put things right again.


### **Drum Earthing Problems**

As the head drum rotates in contact with the tape, it becomes charged electrostatically. Random white lines on the picture – see photo (18) – mean that the earthing brush for the drum spindle needs cleaning.


# VCR Fault Guide

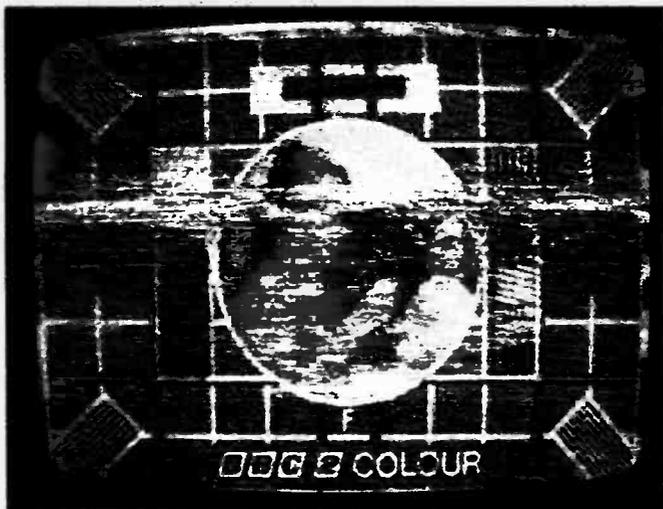

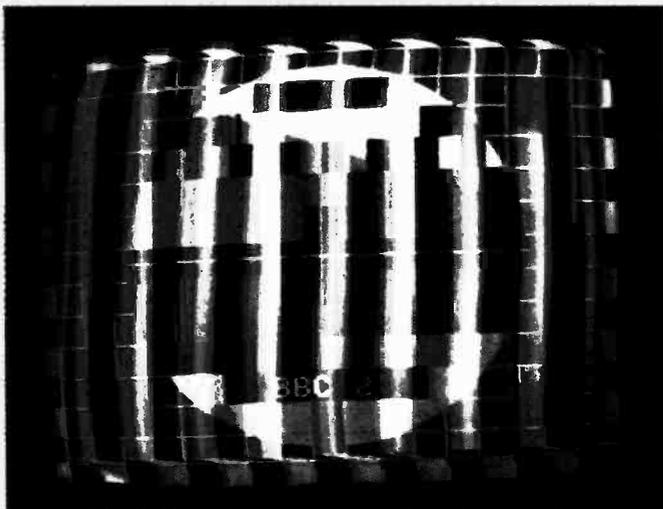
(1) Typical symptom on a VHS or Betamax machine when one head is not working.



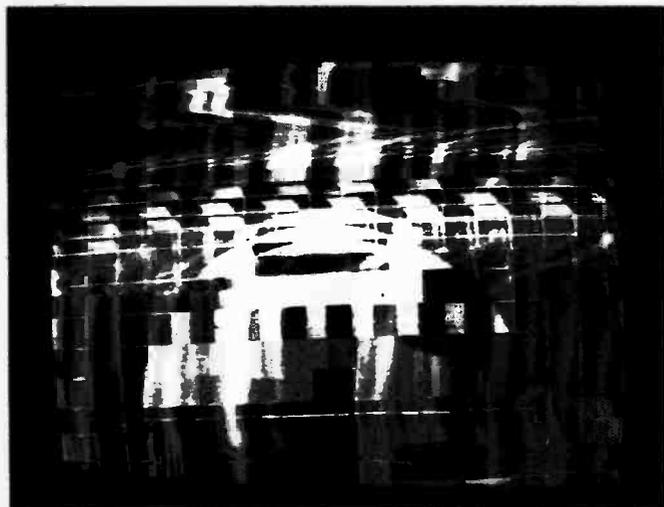(2) The effect when one head is not working on a V2000 system machine.



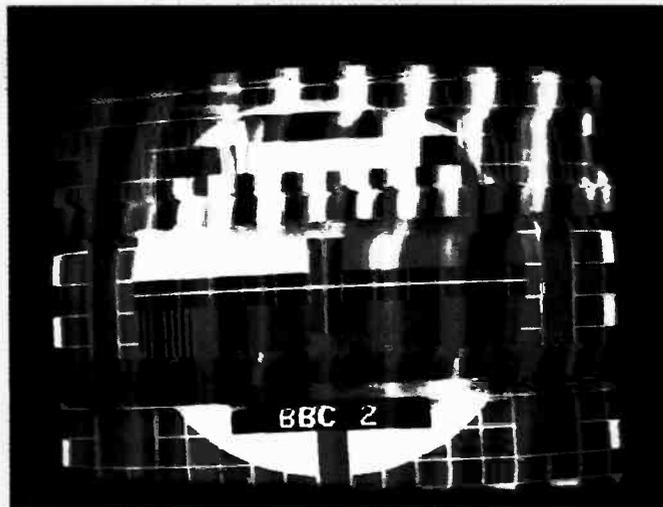(3) The effect produced by minor drop-outs on a V2000 system machine.



(4) Effect when the dynamic track following system is not working on fast search with a V2000 machine.



(5) Effect produced when the head switching point is far out – due here to incorrect flywheel position.



(6) Noise bars at the top and bottom of the picture due to a tape path fault.


# VCR Fault Guide



(7) Noise bar at the bottom of the picture due to a tape path fault on the take-up side.



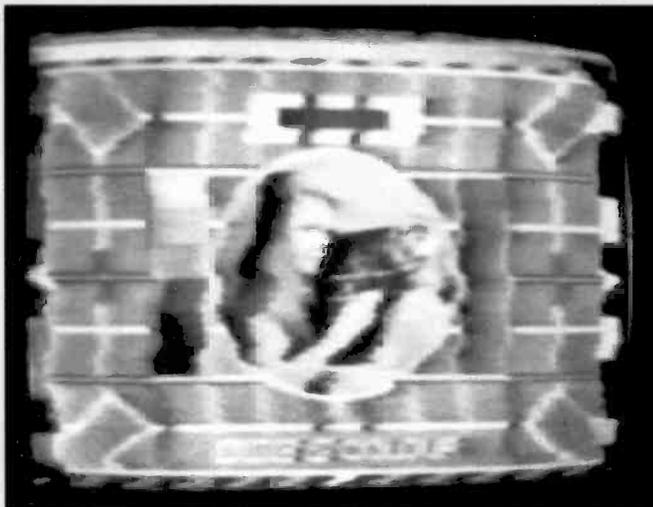(8) If the limiting is inadequate or the f.m. is noisy the result is "spaghetti" as shown here.



(9) Badly worn heads in VHS and Betamax machines produce this type of display.



(10) Effect produced when the head preamplifier  $Q$  and resonance adjustments are incorrect.



(11) Effect produced when the f.m. record current is excessive – noisy playback, possibly with spaghetti.



(12) Effect produced when the chroma record current is excessive – patterning, not excessive saturation.


# VCR Fault Guide




(13) Fringe patterning on vertical edges due to excessive playback chroma signal.



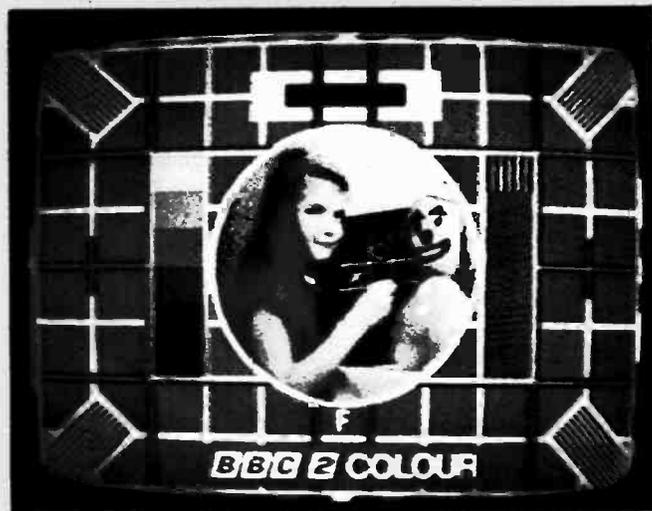(14) An off-lock chroma conversion carrier produces unlocked colour.



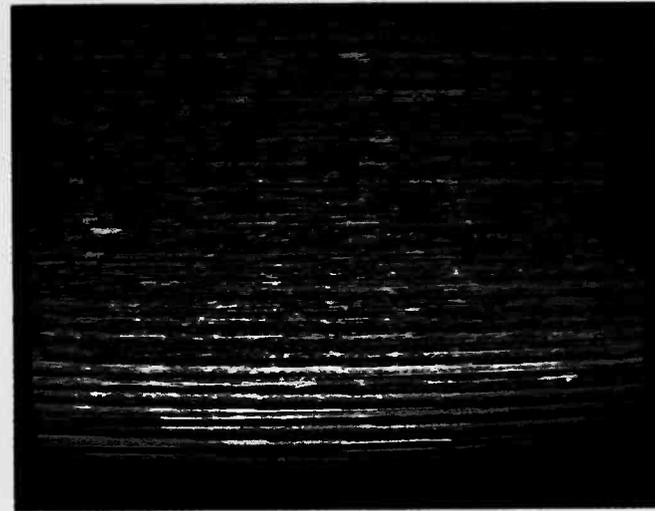(15) Chroma displaced with respect to the luminance, due in this case to incorrect head phase control.



(16) When the drum speed is too far out the result is line slip as shown here.



(17) Type of display produced when the f.m. modulator adjustments are mis-set.



(18) Random white lines will be present when the drum's static discharge system is not working.

# Digital Counter-Timer

## Part 2

Tony Jenkins, G8TBF  
(WKF Electronics)

WE'LL assume that those contemplating the construction of the frequency counter-timer are proficient at wiring and assembly. The aim of the following notes therefore is to ensure that the unit goes together with the minimum of problems, thus saving both time and frayed nerves.

### Construction

Start with the main board. Fig. 7 shows the component layout. First of all fit the two through-board links under IC1 - it's impossible to do so after fitting the i.c. socket.

Now install the i.c. sockets, which must be spaced sufficiently away from the board to allow access to the pins requiring top soldering. We suggest that the four corner pins on each socket are soldered first, with only about 1mm. showing on the underside of the board. Next fit the resistors, capacitors, diodes, crystal, etc., making sure that all top-soldered connections are made. Fit the SIL resistor networks with the dot on the body matched to the "1" shown on the PCB. Then fit the transistor and preset, followed by the regulator i.c. which also needs to be secured to the board by its tab with a short 3mm. screw

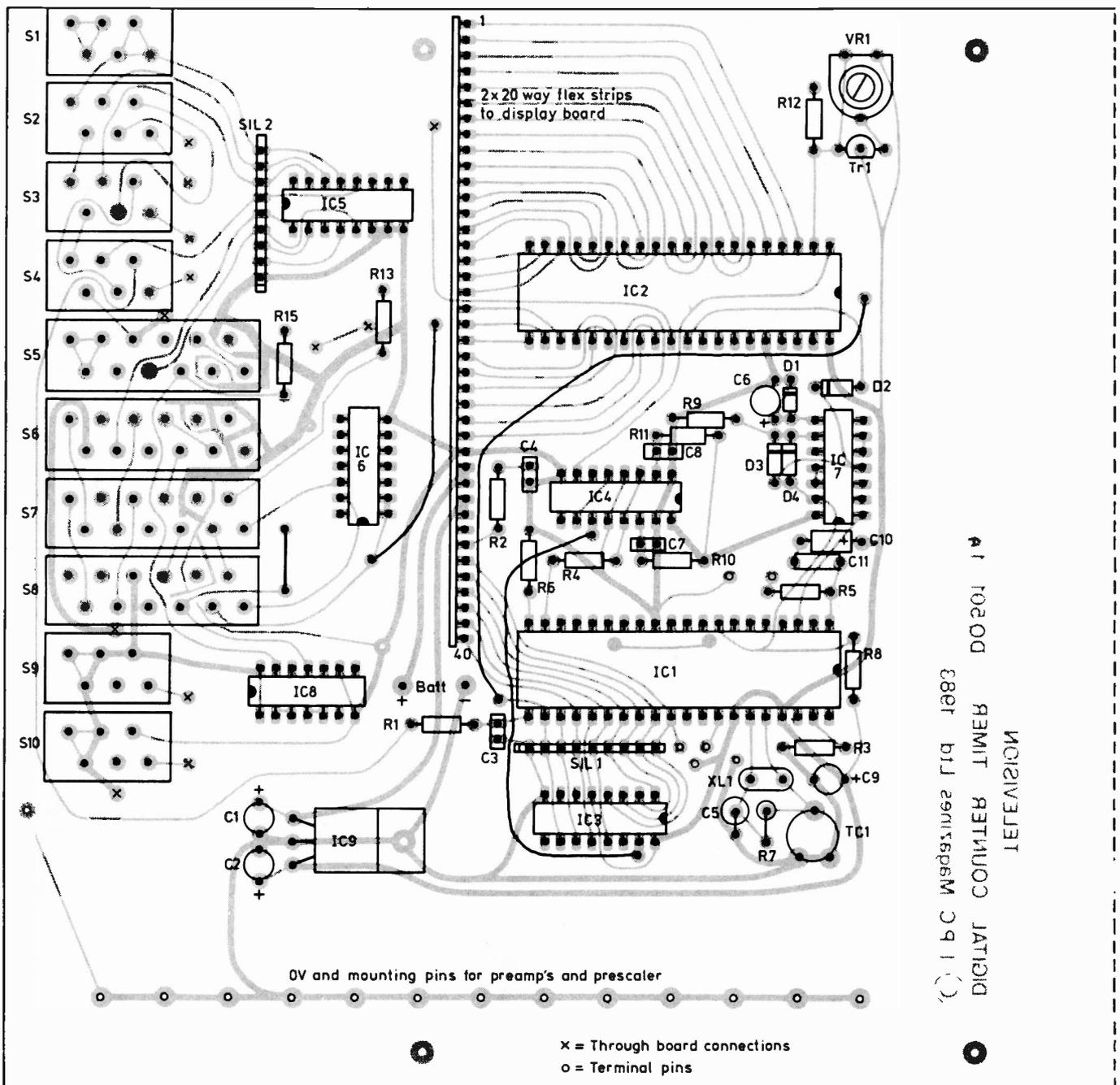


Fig. 7: Main panel component layout.

TMJ905

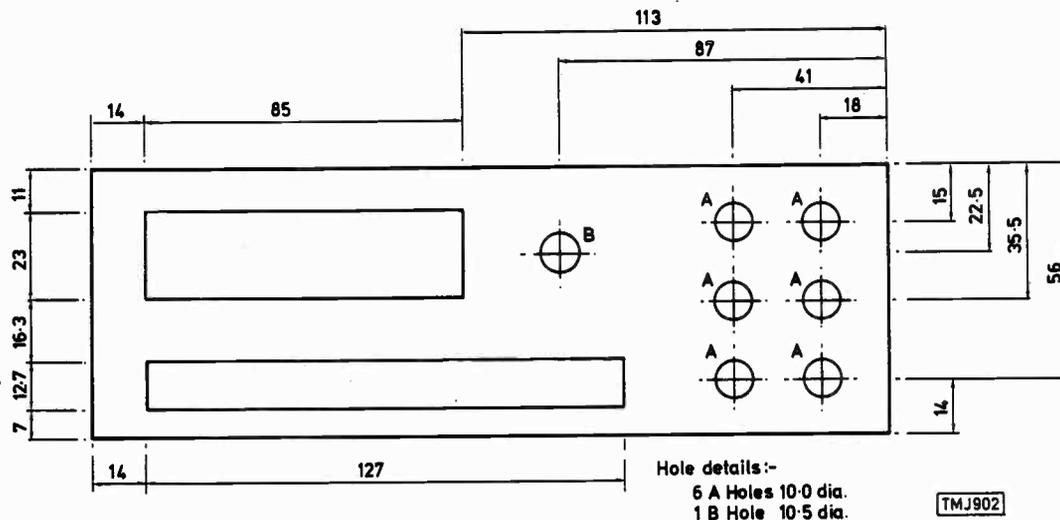


Fig. 8: Front panel cut-outs - dimensions in mm.

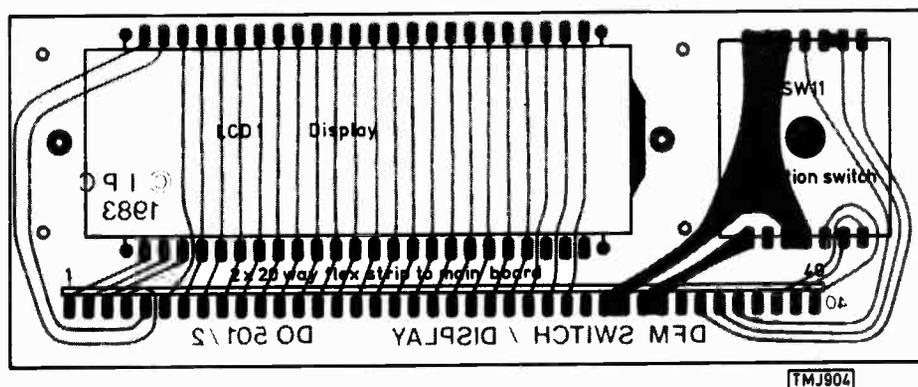


Fig. 9: Display panel layout.

## COMPONENT LIST - 2

### Prescaler One

Resistors: all 0.25W carbon film,  $\pm 5\%$ , except where stated

R1	47R	R5	330R
R2	1k	VR1	10k
R3	10R	miniature horizontal-mounting skeleton preset	
R4	4k7		

### Capacitors:

C1	10n		ceramic plate
C2	22p		ceramic plate
C3-6	10n		ceramic plate
C7-9	1 $\mu$ F	35V	tantalum bead
C10	10n		ceramic plate

### Semiconductors:

Tr1	BC183L	IC2	LM2931-Z5-0
IC1	8629		

### Miscellaneous Items Required:

Set of p.c.b.s	Printed labels for front panel
I.c. sockets:	4 BNC sockets, single-hole mount, 50 $\Omega$
2 40-pin	2 20-way, 85mm Flexstrip jumpers
4 16-pin	Knob for function switch
2 14-pin	Display bezel
1 8-pin	4 3mm screws and washers
Case	PP7 battery

### Preamplifiers (each of two units)

Resistors: 0.25W carbon film,  $\pm 5\%$  except where stated

R1	1M	R10	220R
R2	100k	R11	220R
R3	10k	R12	47R
R4	22k	R13	470R
R5	150R	VR1	1k
R6	470R	subminiature cermet preset	
R7	47R	VR2	1k
R8	2k2	carbon track preset with knob	
R9	10k		

### Capacitors:

C1	100n		polyester
C2	15p		ceramic plate
C3	1 $\mu$ F	35V	tantalum bead
C4	10n		ceramic plate
C5	10n		ceramic plate
C6	10n		ceramic plate
C7	100 $\mu$ F	6V	tantalum bead
C8	10n		ceramic plate
C9	10n		ceramic plate
C10	1n		ceramic plate
C11	1 $\mu$ F	35V	tantalum bead

### Semiconductors:

Tr1	3N201
Tr2	BC183L
Tr3	BC183L
Tr4	BC212L

### Miscellaneous:

L1 One turn e.c.w. on ferrite bead

and nut. Next fit the terminal pins followed by the remaining through-board links (note that there are two between sections of the switch bank). Finally fit the switch bank.

The next stage is to drill and prepare the front panel. Fig. 8 shows the cut-out details which must be adhered to. Readers purchasing PCBs from Readers' PCB Service will receive a paper template which should ease the task. The March cover showed the suggested lettering, which can be done using a suitable style and size of dry transfer lettering. Protect the finished panel with at least two coats of a suitable spray-on laquer. When the front panel is completed, letter the display bezel in the same way, then fit the bezel on to the front panel.

It's necessary to prepare the front panel prior to the display board since the function switch SW11 is not soldered flat to the board but has to be spaced away from it to provide the correct mounting distance from the front panel. More on that later. Fig. 9 shows the display board component layout. The LCD display has 24 connections on each side. The manufacturers supply it with connector strips which have 26 pins, one spare being located at each end. The socket strips to be soldered into the PCB have 25 pins. So the spare pin at one end of the display connector will go into the socket but the spare pin at the other end will be left floating. As the socket strip pins are offset, ensure that they are mounted the same way round and that the display is offset towards SW11. Then insert the display into the socket strips, making sure that it is correctly orientated and fully seated.

Insert SW11 *but do not solder*. Put the shakeproof washer on the spindle and strip off the antirotation pin (otherwise the switch will not mount flush to the front panel). Locate the whole assembly on the bezel studs, using a nut at each side for positioning. Align the board so that the display is parallel to the bezel, leaving a gap of about 1mm. Fit and tighten the securing nut on SW11, then solder the switch to the board.

The whole assembly can now be removed and the two 20-way flex strips soldered to the copper track side of the display board and then through the main board, remembering to solder the top and bottom. The flex strips are supplied cut to size, so don't insert farther than necessary through either PCB or the display may not reach the front panel. After fitting the i.c.s and the battery lead (we suggest using a PP7 battery) the assembly can be tested.

On initially switching on the display should show 00000000 with the "measurement in progress" (MIP) flag flashing. The annunciator flags should change according to the range selected. If all is in order the assembly can be put into the case - after the input sockets and offset controls have been mounted on the front panel.

The earth tags on the input sockets should be linked together, with a short lead attached for connecting to the main board. Likewise the pins at the anticlockwise end of the offset controls.

### Corrections

Finally this month some corrections to Part 1. An i.c. pin number was omitted from Fig. 6: pin 5 of IC4b is connected to pin 10 (the missing number) of IC4a. Incorrect type numbers were given for the two 5V regulator i.c.s: IC9 (incorrectly shown as IC8 in Fig. 6) is type LM2931-T5-0 and IC2 (prescaler 1) type LM2931-Z5-0.

**TO BE CONTINUED**

# next month in

# TELEVISION

## ● IN-SITU TRANSISTOR TESTER

This simple in-circuit transistor tester, designed by Alan Willcox, will also check diodes and thyristors. It's quick and easy to use, giving rapid identification of transistor type (npn/pnp) and condition, diode polarity and so on, possessing good immunity to the in-circuit conditions. Indication of a device's condition (open-circuit/short-circuit/o.k.) is by means of a pair of LEDs which either flash or are extinguished (a dual-timer i.c. provides supply line switching at about 5Hz). There are just two switches, on/off and diode/transistor. Can be built easily and cheaply to give reliable go/no-go testing. Two alternative case arrangements will be shown.

## ● TELEVISION RENTALS

So you've renovated a batch of now sparkling CTVs and want to go in for a bit of DIY renting. What are the problems and pitfalls? There are various legal requirements in addition to the business and technical aspects. Tony Thompson draws on his experiences to provide guidance for those about to start out in the rental field - there's money and satisfaction to be gained from such an enterprise.

## ● TRIPLER CONVERSION

Disaster struck when the e.h.t. overwinding in Keith Cummins' Beovision 2600 developed shorted turns. Since these sets provide excellent pictures, a decision was taken to investigate the possibility of conversion to e.h.t. generation using a tripler. This proved to be highly successful, a neat modification to the regulating circuit restoring the performance to almost the original standard.

## ● SERVICING FEATURES

S. Simon on the Thorn 9600 chassis. VCR Clinic. John Coombes on the Toshiba C800B. Mike Phelan on the 3V23's drum servo system.

**PLUS ALL THE REGULAR FEATURES**

**ORDER YOUR COPY ON THE FORM BELOW:**

TO .....  
(Name of Newsagent)

*Please reserve/deliver the June issue of TELEVISION (90p), on sale May 18th, and continue every month until further notice.*

NAME .....

ADDRESS .....

.....

.....

# Letters

## SONY MODEL KV1810UB

David Botto's article on the Sony Model KV1810UB in the March issue was excellent. The suggested replacement component count for a dead set was very high however, and many service engineers will undoubtedly be reluctant to allocate the time and expense necessary to follow all the recommendations. Few engineers seem to realise that this model can be powered up without using the regulator circuit. The procedure I adopt when the chopper and line output devices (Q603 and Q510) fail is as follows:

- (1) Remove but don't replace the chopper GCS Q603.
- (2) Link across its anode and cathode on the panel.
- (3) Replace the line output GCS Q510.
- (4) Connect an 18V supply to pin 17 on the regulator panel.
- (5) Supply the set from a variac, adjusting this for 125V at pin 22.

The set can now be tested (or soak tested) without fear of Q603 locking on and destroying both GCSs. This test does not give sensible results in terms of visible picture content, but for the majority of faults on these sets this is irrelevant.

The diagnostic procedure to follow on the regulator panel itself is adequately covered in the article, but I think it's important to point out that IC501 rarely (if ever) goes wrong. Also the value of C624 is not critical for test purposes. Higher values (say 100 $\mu$ F) can be used but will cause a line down the centre of the picture: you can fit values as low as 32 $\mu$ F, but this should be done only if the engineer is prepared to monitor the waveform at pin 16 of IC501.

Finally, the protection transistor Q610 is a complete disaster in these sets. If it conducts, the trigger input to the monostable is clamped to chassis. When this happens the chopper Q603 is left without drive and usually remains on. The result is that two more GCSs are destroyed. I remove Q610 and associated components, cut the track, and fit a crowbar circuit – exactly as in the Thorn 3500 chassis but with two zener diodes that come into operation when the 130V line rises to 140V.

*Grahame Danbury,  
Berkhampstead, Herts.*

## FERGUSON 3292 DRUM ASSEMBLIES

In the December 1982 VCR Clinic Derek Snelling raised the point about the interchangeability of replacement head drums, and the need to replace the lower drum assembly, in early versions of the Ferguson 3292. I've found that it's not necessary to replace the lower drum assembly. The replacement head drums are fitted with plastic relay pins which protrude and foul the mounting. They can be removed and carefully exchanged for the PCB and wires from the old head drum – but do take care to maintain the colour identification of heads 1 and 2. This simple modification can save £50 in parts alone.

*Brian Watkins,  
Arun Video, Bognor Regis.*

## THORN TX10 CHASSIS

The problem of the Thorn TX10 chassis blowing its chopper transistor was mentioned in the March Service Bureau. The fault described has a very strong resemblance

to a great number that have passed through our workshop. The trouble is that the focus unit arcs internally. Replace this and fit a new BU208 and no more trouble will be experienced.

*B. Francis, Tech. (C.E.I.), A.M.I.E.E.I.E.,  
Plympton, Plymouth.*

Failure of the chopper transistor in the Thorn TX10 chassis was mentioned in Service Bureau, March. I've found that the usual cause, whether a BU208A or BU208B is fitted, is the focus unit, which tends to arc over to chassis – this sometimes can't be seen or heard, and causes much head scratching.

*David N. Burns,  
Penicuik, Midlothian.*

## WORKSHOPS

Last December Chas Miller commented on the subject of workshops. It's a problem that occurs beyond the UK shores, believe me. My first five years in the trade were spent in Hamilton, Victoria in a workshop that was structurally sound but had a severe lack of test gear, particularly for two-way radio servicing (TV equipment o.k., just). May 1981 saw me up in Cohuna, Victoria. This time the workshop was an old house that was falling down. The floor was uneven, so that CTVs on trolleys ran away to the back wall. There were only four (two double) general purpose 240V outlets plus a million dual adaptors. The roof leaked – into a VCR one evening, but still nothing was done about it! The service vehicle (1968 Holden) had next to no brakes and big, gaping holes in the back. When delivering a new CTV the set got in one hell of a mess if the client lived on a gravel road! Stocks consisted of two triplers, a couple of BU326s, 2SD380s etc. In the summer the workshop temperature went over 40°C whilst in winter it fell to 0°C. In all, it was a dump. I could go on about it, but won't.

That's why I'm now at Tennant Creek, Northern Territory. The workshop here is an ex-cool room, thermally insulated and air conditioned with a constant temperature of 72°F, also with controlled humidity. The inner and outer skin is colourbond steel, providing r.f. shielding, an important aspect according to our Department of Communications requirement for transceiver servicing. Test gear is being purchased as we can afford it – we need about \$10,000 to set up properly – but it's paradise compared to my previous experiences. Les's rusty motor car? – it sounds like a roller to me compared with the heap of rubbish we had to attempt to drive! The moral of all this is to be wary of working for a retailer (we don't retail up here). Retail margins are so narrow that the workshop inevitably suffers.

To close with, here are some fault experiences I've had with the Sony Model KV1800A.

- (1) The 2.2 $\mu$ F RGB output stage h.t. smoothing capacitor C168 goes open-circuit, causing modulation of the raster at line rate – white-going modulation.
- (2) No results – press cutout!
- (3) The line driver transistor shorts, taking out the line driver transformer in a cloud of smoke.
- (4) The line output transistors Q801A and B go short-circuit, taking with them the pincushion output transistor Q604.
- (5) Horizontal tearing/ragged verticals. The line oscillator transistors Q509/Q510 have noisy junctions.
- (6) Varying grey scale. The RGB output transistors or more often the 330 $\Omega$  trim pots in the relevant output stage.

(7) No chroma. The 4.43MHz driver transistor Q306 open-circuit or the ident coil L308 lossy (not open-circuit – possibly shorted turns). The bistable switch transistors Q314 or Q315 open-circuit.

(8) Varying vertical static convergence – replace the HV block (tripler and thick film potentiometer assembly).

(9) The tube occasionally gives trouble – usually the blue or green gun goes down. Take care when removing the e.h.t. cap – the lead is coaxial, with 25kV on the braid and the vertical static convergence voltage on the inner conductor. If the spring on the centre contact of the connector is broken off the c.r.t. will be useless.

Finally, regards to Les, Chas and all.

*Andy Sutherland, VK8KAS,  
Tennant Creek, Northwest Territory, Australia.*

*Editorial comment:* A check with our KV1800UB (UK version) manual suggests that most of the servicing notes above apply to this as well, but the capacitor in item (1) is C161 while a different decoder is used – see item (7).

### PLUG PROBLEM

A further point about the failure of the line output transistor etc. in the Philips G11 chassis due to arcing in the mains plug. I've also experienced this and on occasions have found that it was caused by loose screws in the mains plug. This was in turn due to the tinned ends of the mains lead not being cut off prior to fitting the plug. The solder on the stranded wires "cold flows", and after a few months the screws become loose and the connector arcs.

*Michael Bennett,  
Romford.*

### FERGUSON FEEDBACK

The letter from D. Hazell in your March issue calls for a reply. *Ferguson Feedback* is issued free of charge to all Ferguson dealers: it's also available, on application, to all full-time, bona fide retail or repair operators on the basis of one per retail or repair organisation.

Due to an administrative error, your correspondent was charged for issue 1 and the binder on a retail basis. As a matter of policy we don't supply this particular publication to members of the public, but our internal procedures require that all the items we stock carry a notional retail price tag. Our apologies to Mr. Hazell for having charged him for something he should have received free of charge, and for adding insult to injury by levying the notional retail price. We shall be sending a refund.

*Frank Pack,  
Editor, Ferguson Feedback.*

### VIDEO/AUDIO CONNECTOR

I was interested to read the system L-I converter article in the February issue. Because most UK receivers have only a u.h.f. input, the converter incorporates a u.h.f. modulator. The cost of this and the alignment problems would be avoided if a direct video input could be used. All TV sets now sold in France are equipped with an industry standard "peritelevision" connector, and there are moves to get this adopted throughout W. Europe. This makes interfacing with other video equipment much easier, with better quality than is possible using a u.h.f. modulator. The standard pin connections are as follows:

(1) Audio output B. (2) Audio input B. (3) Audio output A. (4) Audio common earth return. (5) Video B return. (6) Audio input A. (7) Video B. (8) Function

switching. (9) Video G return. (10) Intercom data. (11) Video G. (12) Intercom data. (13) Video R return. (14) Intercom data return. (15) Video R. (16) Blanking. (17) Video return (composite). (18) Blanking return. (19) Video output (composite). (20) Video input (composite). (21) Chassis.

All connectors mounted on equipment are female and various types of cords fitted with male connectors are available. Only sets with mains isolated chassis can be fitted with such connectors of course. It seems to me that you would be doing a service by drawing attention to this new standard.

*(Name and address supplied, omitted for professional reasons.)*

### BACK COPIES WANTED

I've purchased *Television*, *Practical Electronics* and *Practical Wireless* for over eight years, keeping all issues in bound volumes. Unfortunately my house and all that was in it was destroyed during the recent fire storms here in Australia. I'm now seeking any back issues – subjects of particular interest to me are vision mixing and special effects, TV test pattern generators, teletext, audio mixers, and microprocessors (especially the 6800 family). Perhaps other readers could help?

*W. Steinke, c/o 9 Holehouse Street,  
North Sunshine, Victoria 3020, Australia.*

### PLAYING NTSC TAPES

When a member of my family emigrated to Canada and started to send me NTSC VHS video tapes I naturally turned my thoughts to seeing whether a UK VHS machine could be adapted to play them back. Obviously my first concern was with the servo system, so I started with the simplest type of machine, in fact a mechanically controlled Ferguson 3292.

During playback the capstan in this machine is locked to a 475.2Hz reference oscillator whose output is divided down to 3.71Hz, while the drum is locked by the off-tape control pulses. I decided to unlock the capstan and speed it up until I had 30Hz control pulses coming off the tape for drum control. This was done by earthing the gate of the field effect transistor X14, connecting a 1kΩ resistor between its source and drain (the usual method of opening the loop when fault finding), and adjusting the capstan sample position potentiometer to get 30Hz control pulses. Adjustment of the drum sample position potentiometer then gave me locked monochrome pictures. These remain stable due to the drum servo compensating for slight variations in capstan speed as a result of the unlocked capstan servo.

My second effort was with a Ferguson 3V23. During playback the capstan in this machine is controlled by off-tape pulses while a 4.43MHz crystal oscillator provides a common reference for both servos, counted down to 50Hz by IC1 on the servo-2 board and then divided by two to 25Hz in IC3. If pin 6 of IC1 is disconnected the reference output is increased to 70Hz: changing the crystal to a US chroma type (3.579MHz) gives an output at 60Hz, as required. Adjusting the drum and capstan sample position potentiometers then produced perfect monochrome pictures with all the facilities this machine provides.

Getting chroma as well is a different matter of course. Has anyone tried this?

*D. Plummer, 26 Vicarage Road,  
Hastings, E. Sussex.*

# Experimental 4GHz Converter

Hugh Cocks

WHILST most US 4GHz receiver designs use dual conversion down to an i.f. of about 70MHz, single conversion is more convenient and also far less expensive. The problem with single conversion is the image frequency. To put the problem simply, if we mix a 4.07GHz local oscillator signal and an incoming 4GHz signal and select the difference we get an output at 70MHz ( $4.07\text{GHz} - 4\text{GHz} = 70\text{MHz}$ ). If there's an incoming signal at 4.14GHz (the image frequency) this will also produce an output at 70MHz when mixed with the local oscillator signal ( $4.14\text{GHz} - 4.07\text{GHz} = 70\text{MHz}$ ). Unfortunately 140MHz is a very small step away from the wanted signal at 4GHz, and if this image frequency is not sufficiently attenuated the result will be a reduction in the carrier-to-noise ratio of 3dB. That's like throwing away 1.5ft diameter on a 6ft dish! Another possibility is that the two signals could interfere with each other, which is highly undesirable. Hence the need for image frequency rejection with a single conversion receiver, as in the present design. With double conversion to a first i.f. of say 800MHz the image frequency is 1.6GHz away at 5.6GHz.

To keep the cost down, a current-controlled multivibrator is used as the local oscillator in the unit to be described instead of a packaged microwave integrated circuit (MIC) – the latter are expensive for use at these frequencies at one-off prices, especially as they all come from the land of the dollar! The current-controlled multivibrator is a very effective substitute.

Due to the conversion loss, a low-noise amplifier (LNA) is essential. A simple one can be made for under £50 however now that the price of gallium arsenide field effect transistors is falling. The combination of an LNA and the present design provides a very effective down-conversion system. It should be emphasized however that the project is not one for the inexperienced constructor.

## Circuit Operation

The circuit is shown in Fig. 1. The amplified signal from the LNA enters the first hybrid which splits and phase shifts it. The input impedance, as with most microwave gear, is  $50\Omega$ . The two outputs from the hybrid are taken to two further hybrids where the input from the local oscillator, at 70MHz away, is introduced. The outputs are applied to the balanced Schottky diode mixers D1/2 and D3/4, which are forward biased via R8/L6 and R9/L7 respectively for optimum performance. A 4GHz stub at each output removes any trace of microwave signal, the outputs being passed via the high-pass filters L1/C1 and L3/C8 to the two identical common-emitter amplifiers Tr1 and Tr2.

From here the signals are resistively combined via C2 (d.c. block), L2 and R3 on one side and VC1 with R4 on the other side. VC1 is adjusted so that the wanted signals are combined in phase, the 140MHz image signal being out of phase and thus removed. The goodness of the cancelling action depends on the stripline hybrids: cancellation between 18 and 28dB can be obtained across the band. As the circuit will be preceded by a high-gain LNA, strong image signals will be present at the input but will be

of no great consequence.

The signal finally goes to transistors Tr3 and Tr4, which provide amplification and some bandpass filtering, and then leaves the head unit for its trip via coaxial cable to the indoor receiver. Simple, isn't it!

The PCB is the most critical item in the system, being etched from Teflon with a critical dielectric constant of 2.5 (0.8mm. thick). This can be obtained from several sources in the UK but isn't cheap – a piece of the size required will cost several pounds. The 70MHz section of the circuit could be made up on cheaper PCB to reduce the cost, but I've not tried it and can't guarantee it.

## Microwave Oscillators

The current-controlled multivibrator consists of transistors Tr5 and Tr6. They are fed from the 12V line, the two bases being soldered directly to the board. The emitters are fed with a variable tuning voltage, between about  $-1\text{V}$  and  $-15\text{V}$ , via R13 and R14 respectively. The higher this voltage the higher the frequency – the opposite to a varicap system. This is a help with long cable runs from the indoor unit. (Microwave varicap tuned oscillators run at about ten times higher frequency than TV tuner varicap tuned oscillators and give about ten times the trouble with hum pickup, due to the oscillator's voltage/frequency response.) Frequency drift is of little consequence, but a.f.c. derived from the demodulated video can be applied. Diodes D5 and D6 help by giving some thermal tracking in addition to providing reverse voltage protection.

The loop of wire that joins the collectors of the two transistors can be made of coaxial cable inner conductor. Keep about three quarters of the original collector lead lengths on both transistors (they are mounted with the cases almost touching), with the loop having just a slight curve to join the two. With BFR34A transistors the band is tuned across by varying the voltage from  $-6\text{V}$  to  $-10.5\text{V}$ , though this may differ with other transistors. The oscillator is built off the board, secured to the board by the transistor connections. Mount the loop about a quarter of an inch off the board: fine adjustment of the tuning range is done by bending the loop back and forth.

The oscillator's output is picked up by a piece of wire which goes right over the loop and is soldered through to the microstrip on the other side of the board. When finished, this is positioned to give a level response over the band. It helps to solder a small value capacitor from the "dead" end of the wire, about a quarter of an inch beyond Tr6, to the board. Another capacitor can be soldered from one side of the loop to the pickup wire.

If a MIC oscillator is used instead, it can easily be mounted in the space the multivibrator would occupy. Direct connection from the output pin should be taken through to the stripline. Most of these oscillators present a d.c. short-circuit which our forward-biased Schottky diodes won't like, so a small chip capacitor should be inserted in the feed just before the wire joins the microstrip. Remember to change the polarity of C16 and the tuning voltage supply diode D6, as a positive 0-15V

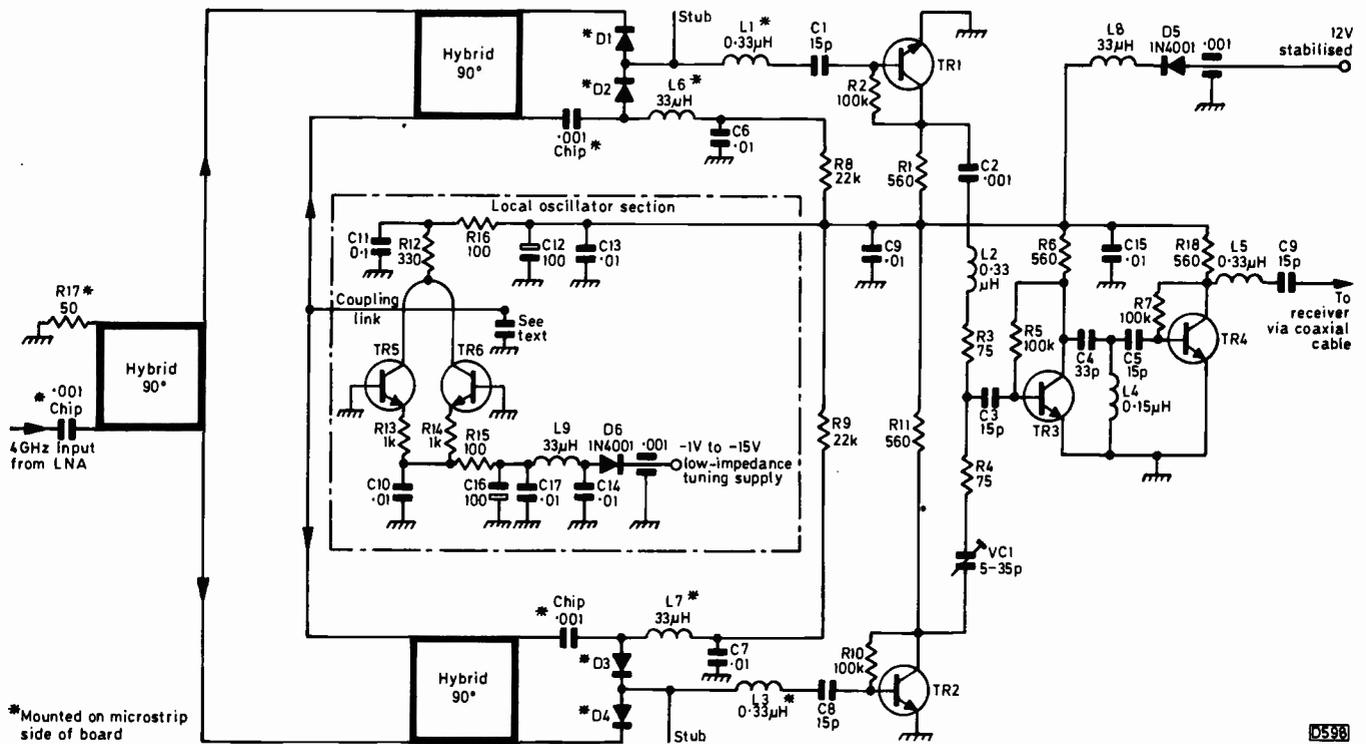


Fig. 1: Complete circuit of the converter.

(sometimes 22V) supply is required – the value of C16 should be reduced to say 2.2 $\mu$ F.

### Construction

The PCB should have a tinplate surround with two feedthrough capacitors in the wall for the supply voltage inputs – the thing looks like a u.h.f. tuner when completed. The LNA may be built directly on to the input in order to do away with the need for expensive microwave connectors. If a US type with a gain of 50dB is used (some reach 57dB, which is not far off a million!) you will find type N output connectors fitted as standard (with waveguide input via a ferrite isolator), so either a chassis mounting plug or socket with back-to-back plug must be used.

Make sure that there's no danger of the coils touching the PCB. The various supply chokes are not critical in value and can be wound over resistors (high value ones!). I used BC109s in positions Tr1-4 – any npn transistor with a cut-off frequency of around 300MHz will do. It may be more convenient to have the trimmer on the same side as the oscillator: this is permissible though it will be a squeeze – check for obvious touching components. Finally put a lid on the top and bottom, with a hole for adjusting VC1.

### Testing

We'll assume that you've some basic DX-TV equipment but no exotic test gear. Tune a TV receiver's tuner to around 70MHz and switch on (leave the oscillator switched off for the moment). There should be a vast increase in the noise seen on the screen. If not, check Tr3 and Tr4. If you can't tune to 70MHz, tune an f.m. radio to 88MHz. Next touch a screwdriver blade on the input ends of L1 and L3. This should produce a further vast increase in noise. If this happens on only one side, check the appropriate signal path.

When the oscillator is powered a "squegging" may be

seen for an instant. This is normal. Check the voltages around the oscillator transistors. The collector voltages will vary as the emitter currents vary, down to about 8V at maximum current. It will certainly be oscillating now.

Those with microwave signal generators will have no problem. A lot of u.h.f. signal generators produce harmonics extending into the GHz range however, so you can at least prove that signals are being mixed. The humble u.h.f. tuner radiates microwave harmonics at its aerial input – the fourth or fifth harmonic can be used.

An LNA is essential. Even the Gorizont spot beam signals will be very low without one. No need to go into the design of one here. Castle Microwave (address later), who are NEC microwave component agents in the UK, have a very good application note for an LNA plus power unit. Alternatively an American LNA can be obtained.

### In Use

With the LNA connected and the converter powered a lot more noise will be seen on the screen, probably varying as the unit is tuned across the band. The feedhorn used could be the same as that described by Roger Bunney in the November 1982 issue of the magazine. If an American LNA is used with waveguide input a matching horn such as the "Chapparral Superfeed" should be bolted on – it costs about \$30.

Turn the receiving dish aerial to the Gorizont co-

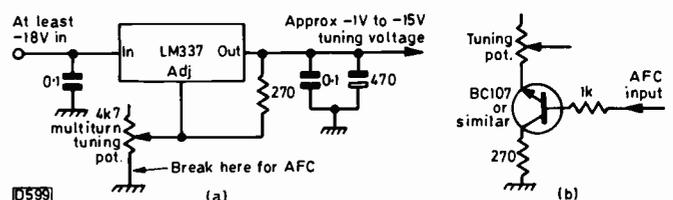


Fig. 2: (a) Method of obtaining a stable negative bias supply for tuning the microwave oscillator. (b) Method of applying a.f.c. to the bias supply.

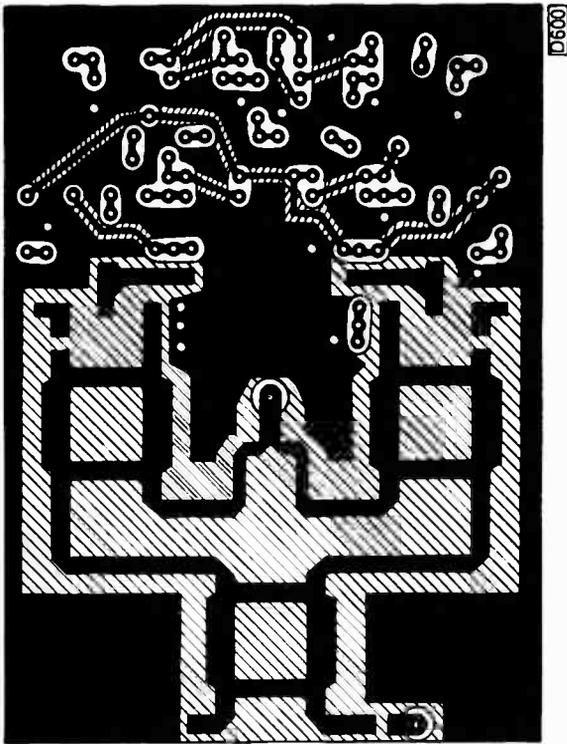


Fig. 3: Print pattern, microstrip side.

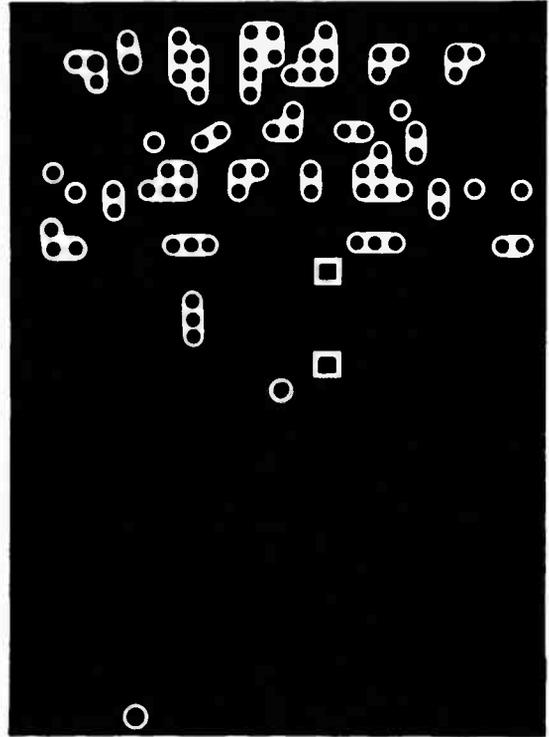


Fig. 4: Print pattern, component side.

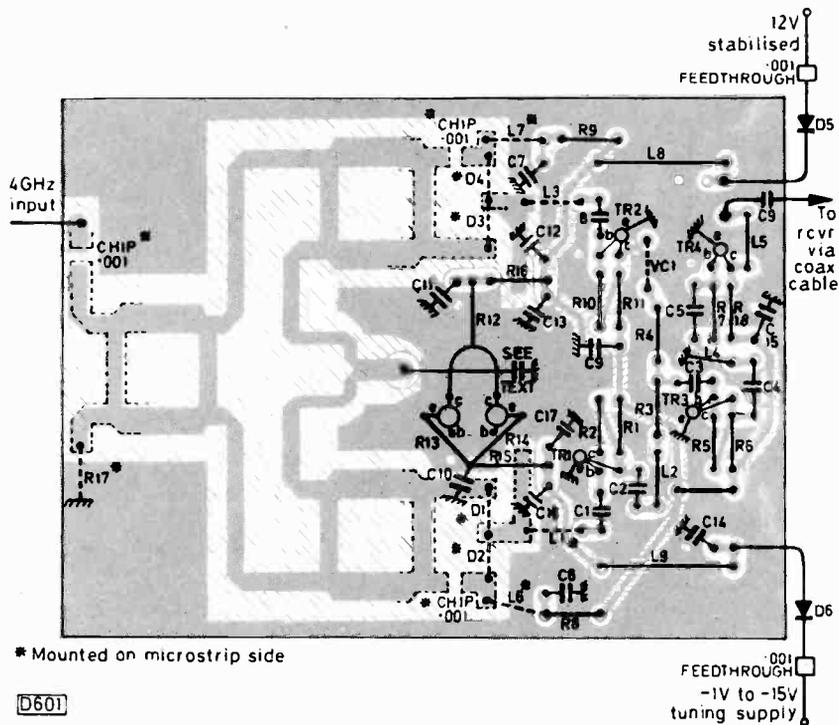


Fig. 5: Component layout. VC1 can be mounted on either side of the board.

ordinates of  $198^\circ$  from north and  $30^\circ$  elevation (reference London – the equatorial position is  $14^\circ\text{W}$ ). The strong  $3.675\text{GHz}$  spot beam should be quickly located, with its characteristic  $2.5\text{Hz}$  flicker due to the energy dispersal waveform which is superimposed on the signal. It's preferable to set the oscillator on the high side of the signal to prevent weak image signals fouling the  $3.825/3.875\text{GHz}$  transponder signals. Tune VC1 on the "lower" tuning position for least signal – you won't lose the image signal completely but it should have a lot less "spread". Confirm that the two weaker transponder signals are present ( $3.825\text{GHz}$  is at present the weakest of the three Gorizont signals and is often off air).

There have been several mentions of f.m. video demodulators in previous issues of the magazine. Phase locked loop i.c.s such as the NE564 (not the NE561) will work at  $70\text{MHz}$  but are happier at  $35\text{MHz}$ . A simple divide by two circuit can be used to convert the signal to  $35\text{MHz}$  (see Long-distance Television, January 1982). An alternative is the quadrature detector type of i.c. such as the MC1357, TAA661 or CA3089 – even the ubiquitous TBA120 can be used at  $70\text{MHz}$  – with the appropriate choice of gain, quadrature coil and damping resistor (quite a low value for f.m. video – a  $470\Omega$  preset is best).

To remove the unwanted energy dispersal, apply a.f.c. to the local oscillator by taking the d.c. component from

the video demodulator plus up to 5Hz or so via an active filter, amplifying this with an operational amplifier or discrete component circuit, and feeding the output into the oscillator's tuning voltage supply. A good d.c. clamp in the video circuit will remove the "turning point" of the waveform so that the flicker is entirely removed.

The converter presented here is very much an experimental design, gleaned from an American source. If anyone builds or improves upon it I'd be interested to hear of their experiences. It certainly represents the lowest cost way of effectively receiving signals at 4GHz. My thanks to Dave Lewis for sorting out the PCB design.

### Sources of Supply

Tr5 and Tr6 can be types BFR90, BFR91, MRF901, BFR34A or anything similar with a 4-5GHz cut off point. Such transistors are available from Ambit, Electrovalue, Maplin, etc.

Teflon PCB (often referred to as PTFE/woven glass laminate) 0.8mm. thick with a dielectric constant of around 2.5 can be ordered from Walmore Electronics, 11-15 Betterton Street, Drury Lane, London WC2 (telephone 01-836 1228). Ready etched boards (and chip capacitors) will be available from Hugh Cocks TV Services, Cripps Corner, Robertsbridge, Sussex (telephone 058-083 317).

The Schottky diodes D1-4 are NEC type ND4981-7E, Ambit part no. 12-49817, or can be obtained as a batch matched set for about £4 from Castle Microwave, 2 Clarence Road, Windsor, Berks. Some experimentation with diode types may prove beneficial.

American LNAs are available on a mail order basis from American Microwave Technology, PO Box 824, Fairfield, Iowa, 52556, USA. A 1.5dB maximum noise type costs about \$360, a 1.3dB maximum noise type about \$400 (120°K and 100°K respectively). The feedhorn required costs \$30.

# VCR Servicing

## Part 17

Mike Phelan

TIME to take a further look at the 3V23's mechacon board. In Part 16 (March) we described how the basic command encoding system works, but there are some loose ends still to tie up – refer back to the block diagram shown in Fig. 68.

The function keys for the clock, tuning etc. are entirely separate from the mechanical function keys that feed ten-bit serial coded command signals to the serial-to-parallel converter IC38 on the mechacon panel – the tuner/timer board has its own key scan system. On remote control however both types of command are initiated by the hand unit, so it's necessary to feed five bits of the eight-bit parallel coded output from IC38 back to the tuner/timer board.

Some of the commands are not processed by the microcomputer IC1 but go from IC38 as four parallel lines to IC12 (a 4028 four to ten lines decoder) and then to the servo and display control panels. These commands are counter reset, frame advance and slow motion forward/reverse, see Fig. 73.

Although IC12 has ten outputs, only four are used here (the reason for this is that the other six output states have

already been used in addressing the data selectors IC23/4/5/6). Starting with the Q0 output, this is inverted to give a low for counter reset. This also occurs at switch on. The Q1 (frame advance) output passes through an AND gate whose other input goes high for still/pause. The Q2 and Q3 outputs (slow forward/reverse) operate in conjunction with the voltage-follower IC36 (part) and C19. These latter items form a storage circuit whose output voltage goes to the servo board. When the Q2 output goes high, this appears as a low (after inversion) at C19 which will discharge via R104. When the Q3 output goes high C19 charges. As there's no load at the input to IC36, C19 retains its charge and the output from IC36 follows the input, varying the slow motion rate via the servo circuit. The "three-in-one" diode D27 acts as a zener diode to set the minimum speed – IC36's output cannot fall to zero.

Another four to ten line decoder (IC11) is used to drive the function LEDs on the front panel (see Fig. 74). This receives its inputs from the microcomputer's C port, while its outputs are passed through inverters. The operational amplifier (part of IC36) shown at the bottom in Fig. 74 is connected as an oscillator whose frequency is about 1Hz.

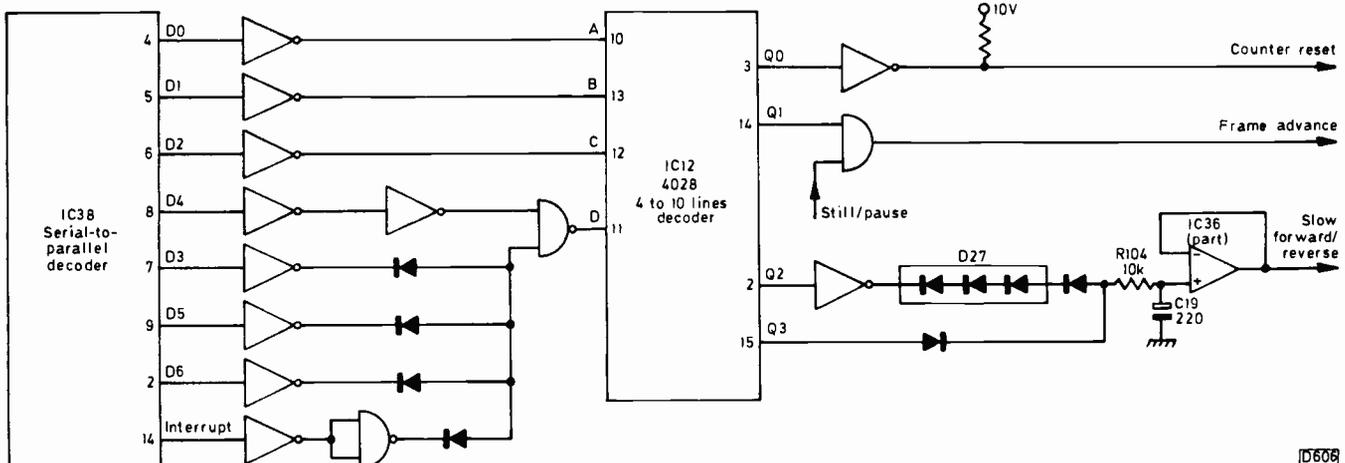


Fig. 73: Counter reset, frame advance and slow forward/reverse control.

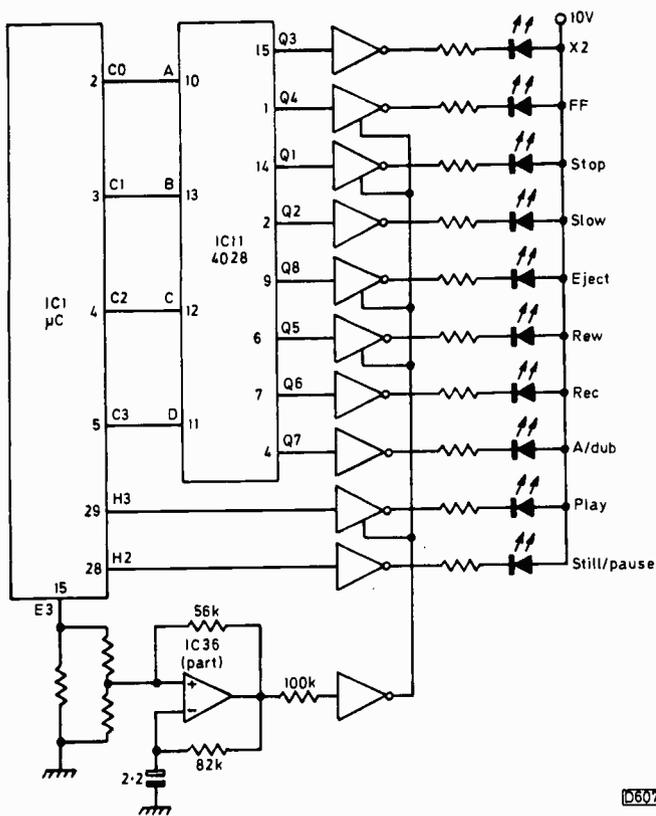


Fig. 74: Function LED drive circuit.

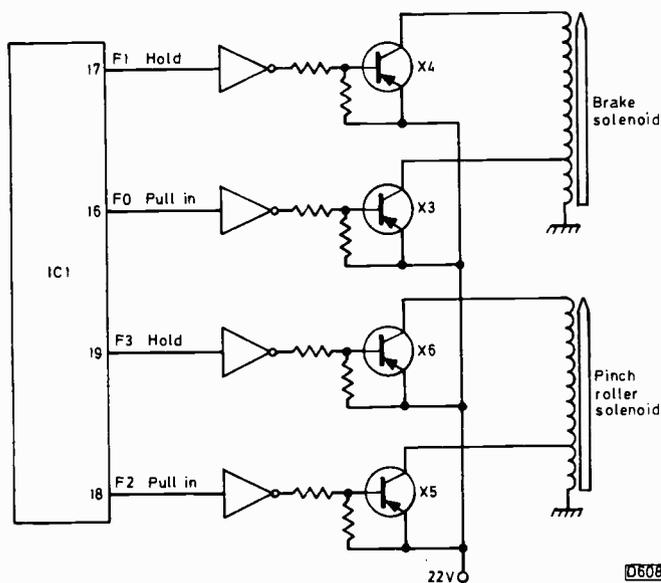


Fig. 75: Brake and pinch roller solenoid control.

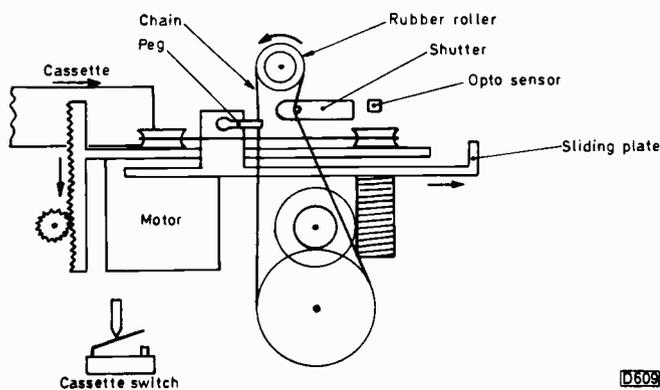


Fig. 76: Cassette housing, shown in the up position.

This is started when the microcomputer's E3 output goes high. Five of the inverters have a third connection. When this goes low, the inverter's output is open-circuit. Thus when the oscillator is running and one of the LEDs is powered it will flash, indicating that the machine is waiting for a previous function to finish or that a fault has developed.

The microcomputer's H1, H2, H3 and E1 outputs control power rail switching transistors via various gates to produce various switched supplies - things like "play 12V", "E-E 12V", "Rec 12V" to name but a few. There are 16 of these rails, which go from the mechacon board to various other boards in the machine.

We'll leave the D port (reel motor drive) until we've covered the servo boards. The remaining microcomputer output ports are F and G.

The F port drives the two solenoids (see Fig. 75), one for the pinch roller and one for the reel brakes. Each solenoid has two inputs: one is fed with a pulse to draw the solenoid in while the other is fed with a hold supply.

### Cassette and Tape Loading Motors

The G2, G3 and H0 outputs control the cassette motor (the one that loads the cassette or ejects it). The loading process is initiated by pushing the cassette into the slot in the front of the machine (refer to Fig. 76). This lifts the rubber roller, tightening the chain and moving the shutter with the result that the opto sensor operates. This, via the data selector and microcomputer i.c., turns the cassette motor on for five seconds. The rollers rotate, drawing the cassette in and pushing the sliding plate to the right so that the peg enters a link on the downwards moving chain, drawing the complete carriage down until the cassette switch closes. The motor runs for a further 300msec, then turns off. If the cassette switch doesn't close within five seconds, eject occurs.

The drive electronics are shown in Fig. 77. It can be seen that the circuit is basically a bridge configuration - this arrangement is often used in VCRs to drive motors that need to be reversed, as in this case. IC1 output H0 goes high to unload the cassette while G2 and G3 go high for loading. If the cassette is pushed back in whilst the machine is trying to eject it, the load mode could be entered while the motor's inertia is still turning it in the eject direction. To overcome this problem G3 goes low to initiate reload: X12 turns off, and the motor drive current flows via X11 whose collector resistor provides current limiting.

The tape loading motor circuit (see Fig. 78) is driven by the G0 and G1 outputs and is very similar. In this case however the supply is switched off by transistor X7 to stop the motor. The motor drives toothed rings which move the tape guide rollers along tracks to pull the tape from the cassette and wrap it round the head drum.

### Tape Guard Circuit

Fig. 79 shows the tape guard circuit, which provides protection in the event of the drum FF pulses being absent (no drum rotation), reel rotation stopping, lamp failure, and still/pause overtime (to prevent tape wear in one place). R154 and C42 form a timer circuit for the latter purpose.

The reel discs are slotted, the peripheries passing through optical sensors which produce signals to indicate that the reels are rotating. Both these signals and the drum

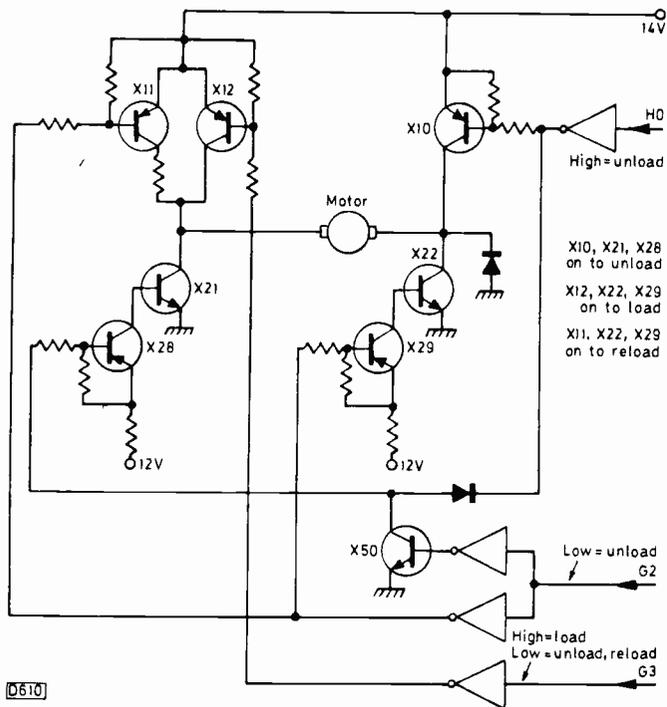


Fig. 77: Cassette loading motor drive circuit.

FF signal go to a three-input gate which is followed by an inverter. The output from this normally keeps C43 discharged. In the event of any of the three inputs not being present however C43 charges via R158 to start the interrupt routine.

If the machine is in the still/pause or slow modes there will be no or interrupted reel rotation. The tape guard signal input to pin 13 of IC24 is therefore blocked via the NAND gate. After five minutes or so in pause C42 charges, the gate opens and the lack of reel rotation is detected with the result that the machine stops.

Failure of the cassette lamp produces the same effect.

The interrupt routine starts when pin 6 of the microcomputer IC1 goes low, even momentarily and irrespective of mode. The following sequence then occurs. The microcomputer checks its A2 input - this is the input

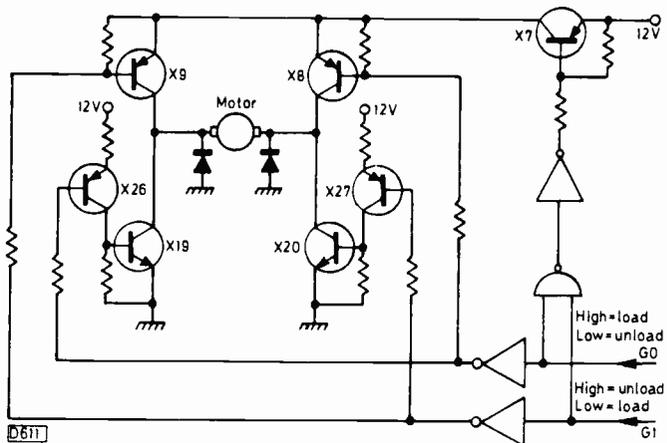


Fig. 78: Tape loading motor drive circuit.

from the data selector (IC24) that checks the unload switch, record safety switch, counter zero and command bit D2. A2 is high for stop and eject, low in all other modes. If the microcomputer finds that A2 is high, the tape guard input (IC24, pin 13) is checked. If this is high, the eject light flashes and the tape guard is rechecked. If A2 is low the machine is in a mode other than stop or eject, the outputs from the microcomputer are all cleared, then checked. This is repeated until A2 goes high, i.e. the machine is in the stop or eject mode. That's just a general idea - to go into the complete routine would require a detailed flowchart.

### The Other Microcomputer

Before leaving the mechacon board, a brief mention of the other microcomputer here, IC2. This receives signals from both reel rotation sensors and from these calculates the relative reel speeds and thus the amount of tape remaining. The output goes to the tuner/timer board in the form of a five-bit code, to be translated into dots on the display. It also drives an up/down counter which operates the digital tape counter via the display control board.

Next time we'll look at the 3V23's servo circuits.

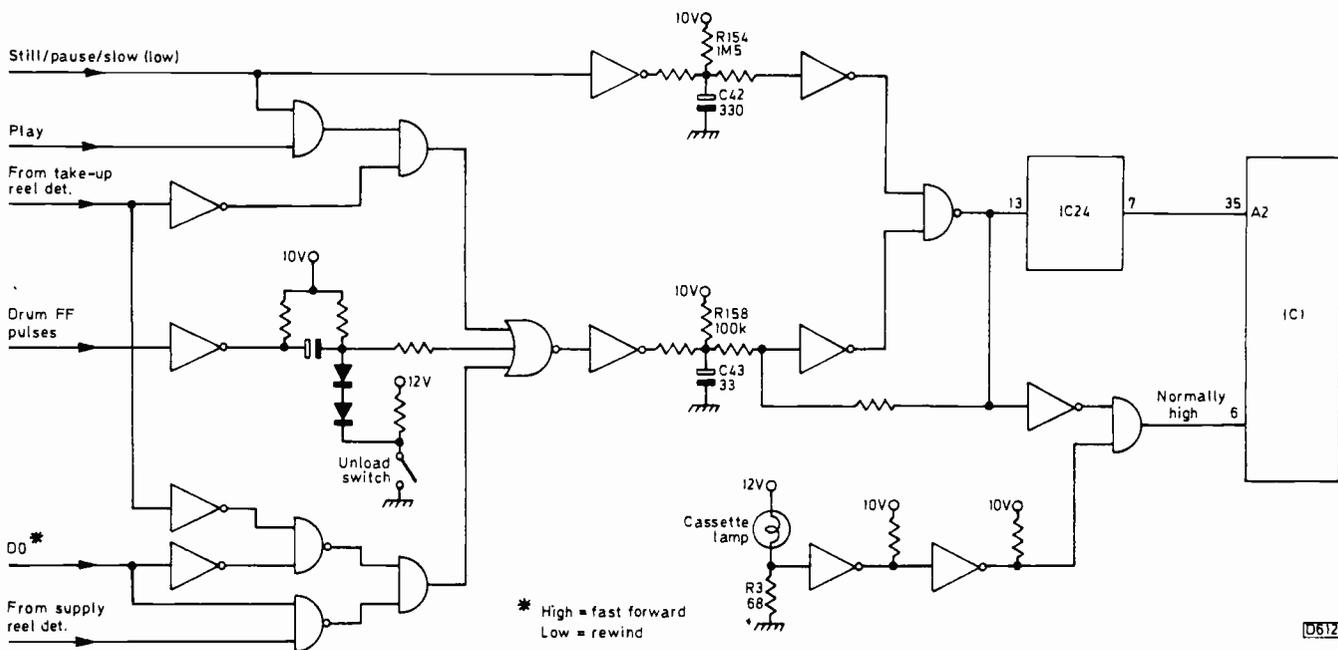


Fig. 79: The tape guard system.

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon from page 377 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## **NATIONAL PANASONIC TC2203**

There are two unusual diodes connected across the 160V stabilised h.t. line. When they go short-circuit the set goes dead, but removing them allows things to start up and appear normal. What's going on?

The two items you mention, D809 and D818, are special diacs, type TVSK1V11. They are designed to go short-circuit when the h.t. voltage is excessive, initiating operation of the excess current trip. The usual cause of this trouble is intermittent failure of the 6V zener diodes D808 and D814 (type TVSQA106SBV) — they go open-circuit intermittently. Replace all four diodes with factory supplied replacements.

## **ITT CVC45/1 CHASSIS**

The problem with this set is no results. There's 300V at the switch-mode power supply output instead of 127V, and there doesn't appear to be any drive to the chopper transistor. R3A in the 187V feed to the control panel has sprung.

This symptom is not uncommon with the CVC45 and derived chassis and is caused by the chopper transistor T807 being short-circuit. Use a TE1233 or BU126 as a replacement. The excessive h.t. voltage shuts down the chopper control circuit, at the same time removing the line drive which comes from the chopper transformer. Don't forget to resolder R3A and adjust R828 for 127V at C11.

## **TELETON C18BS**

The width is excessive on this set — about two inches too wide at each side of the screen. Adjusting the horizontal size tappings has no effect and there doesn't seem to be an e.h.t. preset.

First make sure that the output from the h.t. series regulator transistor is not excessive. There should be 120V across C409, adjustable by VR701. If the h.t. is correct the probability is that the line flyback tuning is incorrect. This is controlled by the tuning capacitors C432/3/4 (0.033/0.033/0.047 $\mu$ F). Replacements should be adequately rated.

## **FERGUSON 3V16**

The plug-in remote control unit's slow-motion button no longer operates — it simply puts the machine into pause, and adjusting the slider has no effect. The slow preset on the servo panel also has no effect when adjusted. The continuity of the remote control system has been checked.

The fact that the tape stops when slow is pressed proves that pin 8 of the control i.c. IC6 on the servo panel is

being earthed via the remote hand unit. The fault would appear to lie between pin 29 of IC6 and the base of X15 in the capstan motor control circuit. First check for a pulse at pin 29 with the slow slider half way (this should show on a meter). The pulse goes via X11 and D22 to pin 5 of IC8, which shortens it. The output at pin 6 goes via D24 to X14. X10 feeds another pulse to add to this, the resultant double pulse being fed via D15 to the base of X15. Likely suspects are IC8 (BA222), X11 and X14. If there's no pulse at pin 29 of IC6, this i.c. is defective. Adjust the slow preset with a tape recorded on the machine, and the slow motion at the minimum rate, for least noise on the picture while the tape is stationary, i.e. between shunts.

## **GRUNDIG 717**

There's distorted sound and no raster on this set. The voltage across the h.t. reservoir capacitors C708/9 is only 80V instead of 294V — when the set is first switched on the voltage is 200V, but it then falls to 80V. Disconnect C708/9 and the following smoothing resistor R702 and the result is the same. The diodes (D1701-4) used in the bridge rectifier circuit (three SKE-1/06 plus one C1780) don't seem to be readily available.

Whilst the bridge rectifier diodes or the reservoir capacitors could be faulty, it's more likely that either the anodes of diodes D1701/703 in the bridge are not earthed, the negative terminal of C708/9 is not properly earthed, or there's a fault in the surge limiter resistors R701/711. BY127s can be used in the bridge rectifier circuit.

## **THORN 8500 CHASSIS**

The bottom of the raster creeps up very slowly — it takes several hours to reduce by about three inches. I've replaced the field driver and output transistors, the bootstrap and scan coupling electrolytics, also C432 (32 $\mu$ F) which decouples the supply to the field oscillator. As the fault develops the supply to the field oscillator falls and the driver transistor gets very hot.

If C432 and its associated smoothing resistor R433 (5.6k $\Omega$ ) are in order we would suspect the 46V supply smoothing electrolytic C714 (2,500 $\mu$ F) on the power supply panel. If the trouble persists, suspect C433 (2.2 $\mu$ F) and W410 in the field charging circuit.

## **ITT CVC5 CHASSIS**

I've seen the following fault on several of these sets — alternate vertical purple and green bars right across the picture. These are not really noticeable at high brightness levels but are pronounced on dark scenes. Changing the 20V line decouplers C152 and C219 in the decoder has failed to provide a cure.

This nasty effect afflicted some early CVC5s. Check the phasing of the subcarrier rejector coils L71 and L72 — these are towards the top of the board and the direction of winding should be clockwise when viewed from above. Ensure that the leads to the convergence box are dressed tightly against the degaussing shield, and that the green lead to the base of the regulator transistor T46 is dressed well away from the filter coil L95.

## **TELEFUNKEN 709 CHASSIS**

The problem with this set is loss of line hold and picture break up when changing channels after the set has thoroughly warmed up. It's necessary to switch off and wait for a couple of minutes before switching on to the

desired channel. The line lock then dithers for a few seconds before settling down. Very occasionally a camera change will trigger loss of line sync, but this will recover after a few seconds. Adjusting the line hold control (oscillator coil) does not seem to make any difference.

First try a new ECH84 line oscillator valve, then if necessary replace the flywheel line sync discriminator diodes (Gr451, in common encapsulation). The latter sometimes go open-circuit intermittently, causing loss of line hold. Another possibility is the coil's tuning capacitor C462 (390pF) which is of a notorious type. Check it for intermittency – the leads sometimes pull loose at the ends. The problem can also be caused by the line output transformer cooking up – when this happens the pulse winding feeding the discriminator tends to go open-circuit, with loss of line hold, usually after an hour or so.

# TEST CASE

## 245

*Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.*

A minor fault can often lurk for years in a set out on rental. On each service call to attend to a more serious problem the visiting technician may notice the defect, but if the trouble is obscure and diagnosis difficult it may well remain there when he's gone! At some stage the set may have to be brought into the workshop. Such faults can then be studied at leisure and, hopefully, cured.

An example of this sort of skeleton in the cupboard condition was provided recently by a 100 series Decca colour set. A major timebase fault had resulted in the set's arrival in the workshop, and when this had been dealt with and the set readjusted the picture was seen to be definitely below par in a difficult to define way – the symptom was rather like that sometimes seen in old monochrome sets when the vision i.f. alignment has been twiddled a bit.

We are fortunate in having a locally generated monochrome test card in the workshop, and when this was displayed the fault condition was better defined. It took the form of an instability effect, with the white verticals of the pattern being reproduced in faint and distorted form at about quarter inch intervals to the right of the main image. As a result, the picture was hazy and badly defined – this sort of thing is sometimes seen on Thorn 3000 series sets when the local-distant control is incorrectly set. The colour reproduction was fair, but not up to the usual standard of this Decca chassis.

Faults like this are never easy to tackle. A start was made by bridging the l.t. supply decoupling capacitors in

the i.f. and tuner departments. This had no effect, and careful checks on the earthing of the tuner and i.f. panels and the braid of the coaxial cable linking them brought nothing to light. The supply to the first i.c. in the i.f. strip is stabilised by a 15V zener diode (D101). This sometimes does odd things, but turned out to be o.k. Suspicion then fell on the two i.f. chips, MC1349 and TCA270, but substitution checks proved that they were blameless. So the set was put to one side until an i.f. panel could be robbed from another set to try in our patient.

In due course a known good panel was fitted – and had no effect on the fault at all! Perhaps the tuner was responsible? Another tuner was fitted and whilst the instability took a slightly different form it was still present. It was now becoming clear why the problem had never been sorted out over the years in the customer's home!

By now many hours had been spent on this set, and nearly all possible approaches to the trouble had been exhausted. The cause of the fault was finally traced however – to a component which by its nature is seldom guilty of failure. It was “no' very big and awfu' shy” as an old Scottish song goes. What was it? See next month.

### ANSWER TO TEST CASE 244 – page 322 last month –

The key to the solution to John's tale of woe recounted last month lay in the e.h.t. meter reading. It will be recalled that the picture on this ITT monochrome set (VC200 chassis) was ballooning very badly, with normal proportions present at only very low brightness levels. All the tests and substitution checks that had been made assumed that the cause of the trouble was faulty e.h.t. stabilisation in the line output/e.h.t. generator circuit. In fact the e.h.t. voltmeter showed that the voltage applied to the tube was correct and rock steady regardless of the setting of the brightness control. This could mean only one thing, that the tube itself was faulty. Such was the case, and good pictures were obtained after fitting a replacement.


It was only the second occasion in many years that we've had this fault with a picture tube. The e.h.t. voltage is linked to the tube's final anode via an internal conductive strip painted on the inside of the flare, and it's likely that this was very high resistance or open-circuit somewhere. We won't send this one back for regunning!

### QUERY COUPON

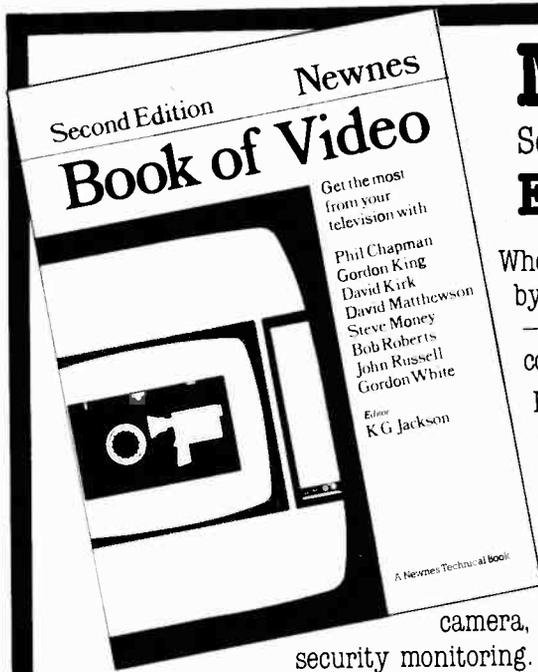**Available until 18th May 1983. One coupon, plus a £1-00 (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice on page 376.**

TELEVISION MAY 1983

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.



# Newnes Book of Video

Second Edition

**Edited by Ken Jackson**

When first published in 1980 **Newnes Book of Video** was described by **Television** as "a handy book to have around as a reference" — now it has been improved and updated to provide the comprehensive survey of television and other video equipment.

Its clear presentation of material and numerous illustrations enable newcomers, enthusiasts and businessmen to understand and choose equipment and assemble systems to their individual requirements.

All the main areas of video are covered, including the TV set itself, as are the various available add-ons — antenna, recorder, camera, game, computer — and extra uses such as teletext reception and security monitoring. For the budding professional, there is a fascinating explanation of programme making with just a single camera. A directory of manufacturers, agents and trade names rounds off this invaluable handbook.

**Contents: The Video Centre • TV Receivers • Tape Recorders • Disc Players • Cameras • Programmes with a Single Camera • Antennas • Cable Distribution • Teletext and Viewdata • TV Games and Computers • Security and Surveillance •**

**Softcover 128 pages 246 x 189 mm Illustrated 0 408 013192 £6.95 May 1983**


**Order from your local Bookseller**

(TV/5.83)

**N** Newnes Technical Books, Borough Green, Sevenoaks, Kent TN15 8PH
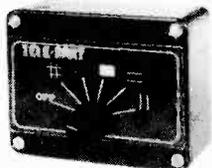
## TELEPART

13 WORCESTER ST.,  
WOLVERHAMPTON,  
WV2 4LJ  
Tel: (0902) 773122  
Telex: 336810



### Telepart Pattern Generator

- \* Exceptionally light and durable
- \* Pocket size for outside service
- \* PP3 battery power source
- \* Five different test patterns for colour and mono TV
- \* Cross hatch grid
- \* Dot matrix
- \* White raster
- \* Horizontals
- \* Verticles

A lightweight, extremely portable and versatile pattern generator for black, white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

**PRICE £14.95 (Subject to V.A.T.)**

POST & PACKING £1.15

### Telepart Colour Bar Generator

- \* Exceptionally light & durable
- \* Compact 13x17.5x5.5 cms
- \* Battery powered for mobility
- \* Cross hatch grid
- \* White raster
- \* Grey scale
- \* Colour bars
- \* Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

**PRICE £49.95 (Subject to V.A.T.)**

POST & PACKING £1.15

### Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

**PRICE £5.50 (Subject to V.A.T.)**

Supplied by return, off the shelf

## COLOUR TV SETS

Philips G8, Pye 222, Decca 30 series, Pye Chelsea, Thorn 3500/8000, ITT, GEC, many others including JAP.

Working hybrids from £15.

Working solid state from £25.

Non-working sets, working panels and tubes available.

**Huge Selection – Quantity Discounts**  
Delivery by arrangement.

**SOUTHBRIDGE TV CENTRE**  
120, Selhurst Rd., London, S.E.25.  
Tel: 01-771 3535.

## A.B.C. TRADE SALES

COLOUR T.V.'s

Philips G8, Pye, Decca 30's,  
Thorn's 3000's, 3500's, 8000's

**Prices start from £12 - Working sets from £20**

Hundreds of Mono T.V.'s from **£2.00**

Jap. sets from **£30.00**

Special prices for quantity

9,000 sq. feet Warehouse

**83 SHOWELL ROAD, BUSHBURY,  
WOLVERHAMPTON, STAFFS.**  
Tel. Wolverhampton 722637

# POST A PART, ELECTRONICS.

AD161	32p	BCX34	11p	PN107	7p
AD182	32p	BD131	30p	R2008	1.00
AF139	30p	BF137	20p	R2010B	1.10
AF239	41p	BF199	15p	R2285	1.30
BC107B	15p	BF240	9p	R2443	25p
BC108A	15p	BF255	10p	RCA16446	30p
BC108B	15p	BF256S	20p	RCA16559	1.25
BC117	21p	BF257	20p	RCA16800	1.40
BC153	16p	BF259	20p	2N3703	20p
BC154	16p	BF274	11p	2N3A473	10p
BC171	9p	BF458	40p	2SC346	10p
BC172	9p	BF487	25p	2SC785R	12p
BC174B	23p	BF742	30p	2SC3820	15p
BC184LC	12p	BF743	30p	2SC388A	20p
BC208	9p	BU105	1.00	R2322	50p
BC237	12p	BU126	1.10	R2323	50p
BC238	9p	BU207	1.05	TIP31	35p
BC251	9p	BU208A	1.15	T9010V	1.45
BC307	10p	BU326A	1.30	T9016V	1.20
BC308	9p	C1172B	9p	T9017V	1.20
BC317	9p	CU1129	9p	T9030V	1.30
BC384	9p	ME904	8p	T9032V	1.30
BC454	9p	ME9412	8p	T9033V	1.30
BC455	9p	ME9002	8p	S2800B	90p
BC460-6	40p	MJE340	50p	S2800C	1.00
BC494	9p	MJE520	65p	S2800D	1.25
BC556	9p	NKT241	8p	S2800E	1.40
BC558	9p	NKT276	20p	S2800M	2.00
BC595	9p	NKT453	1.05		

**ZENER DIODES**

**TOSHIBA 200MV 10p each**  
6.2v, 12v.

**BZY88 10p each**  
3.9v, 5.6v, 12v, 16v, 20v, 30v, 33v.

**TOSHIBA 500MV 10p each**  
5.6v, 6.8v, 7.5v, 8.2v, 11v, 15v.

**BZX61 16p each**  
9.5v, 10v, 11v, 15v, 27v, 72v.

Thorn 10Ω 20W (3500 R751 Safety Resistor 75p  
Pye 713 Speaker 5" x 3" 70Ω 1.00  
Pye 713 Complete Tube Base Panel  
with Focus Slider & Leads 2.75  
Pye 713 Control Knobs 4 for 50p  
Tube Base Socket ITT CVC32 45p  
Tube Base Socket Thorn 3000/8000 etc 50p  
IC Insertor 18 Pin 50p  
Large IC Extractor 50p  
Crystal 4.33MHz 65p  
EHT Lead & Cap for Split Diode Lopt 90p  
Anode Capacitor 47p  
Sanyo Anode Cap Assy + Lead. 12TCD-CT-16 65p  
Degauss Thermistors. PT37P, ITT/GE 35p  
Degauss VDR E2980/HP230 3000/8000 25p  
Castors Set of 4 1.90  
Double Fuse Holder on Small Pax Board  
20mm type 10p  
Single Fuse Holder on Small Pax Board  
20mm type 5p  
Direct Panel Mounting 20mm Fuse Clips (pair) 15p  
Single Fuse Holder on Small Pax Board.  
As per early 3000 mains inout 6p  
EHT Cable (Metre 25p 13A Plugs 12 for 4.80

**THICK FILM RESISTOR UNITS**

3500 Thorn (5 Pin Connection) video 1.70  
4000 Thorn (5 Pin Connection) 1.90

**TANTALUM CAPACITORS**

0.1MFD to 470MFD 6.3v/10v/15v/35v  
£6 per 100

**MINIATURE CERAMIC DISC**

1PF to 10NF 50v/250v/500v  
£2 per 100 or £15 per 1000

**HIGH VOLTAGE DISC**

Most Values Available 2KV to 12KV  
£5 per 100 or £40 per 1000

With these items No Mixed Values in Lots of 100

**SERVICE AIDS**

Amberal MS4 Silicone Grease 12oz 2.15  
Amberal Freezer 12oz 1.90  
Amberal Amberlube 8oz 1.90  
Amberal Ambertron 16oz 1.95  
Amberal Anti-Static Screen Cleaner 7oz 1.95  
Amberal 40+ Protective Lubricant 14.1oz 2.15  
Amberal Amberlens Foaming Cleaner 13oz 2.15  
Amberal Circuit Lacquer 14oz 2.15

**MIXED PACKS**

300 Mixed Resistors 1.50  
300 Mixed Capacitors 1.50  
150 Mixed Electrolytics 2.00  
100 W/W Resistors 1.00  
20 Mixed Conv Pots 1.00  
40 Mixed Pots 1.50  
20 Mixed Sliders 1.00  
40 Mixed Presets 60p  
20 Mixed VDR & Thermistors 1.00  
20 Mixed Ferrite Cores 50p  
100 Mixed Ceramic Discs 1.00

20 Mixed Valve Bases 1.00  
10 Spark Gaps 1.00  
10-16 pin Quil IC Socket 90p  
20 Assorted TV Knobs 1.00  
10-16 pin Quil to Dil IC Socket 90p  
100 Mixed Diodes 1.00  
50 Mixed Mica Washers 65p  
300 Mixed Resistors & Capacitors 1.50  
10-16 pin Dil to Dil IC Socket 1.00  
59 Electrolytics & 50 Capacitors 1.00

**AERIAL SOCKETS**

AE Socket & Lead. Pye, ITT, Thorn 25p  
AE Socket & Lead. GEC 25p  
AE Socket & Lead. (long) GEC 25p  
AE Socket & Lead. Pye 691/693 25p  
AE Socket & Lead. Philips KT3 25p  
AE Socket & Lead. Thorn col. portable 25p  
AE Socket & Lead. (long) Pye 725/731 25p  
AE Socket & Lead. ITT CVC32, etc 25p

UHF TV Aerial for portable 50p  
Indoor Aerial Parabolic Type Reflector  
to Help Combat Ghosting Problems 2.50  
Line Connectors 38p  
Coax Plugs 10 for 1.65  
Band Change Switch Assy, Pye 725 40p  
Flush Mounting TV/FM Diplexer 40p  
Switched Flush Firing Aerial Outlet 1.00

**CAN TYPES**

0.2MFD 250V 50p  
2MFD 250V 50p  
22MFD 275V 50p  
50MFD 275V 50p  
100MFD 150V 85p  
100MFD 250V 70p  
100MFD 450V 75p  
220MFD 400V Thorn 9K 1.30  
220MFD 450V Thorn 4K 2500MFD 30V 85p  
220MFD 450V Thorn 8K 3300MFD 16V 65p  
800MFD 250V Print 4700MFD 16V 72p  
800MFD 250V 80p  
800MFD 250V 70p

1250MFD 40V 50p  
1500MFD 50V 50p  
1500MFD 70V Thorn 3K 50p  
1500MFD 100V 1.05  
2000MFD 30V 50p  
2200MFD 40V Thorn 4K 85p  
2500MFD 35V 85p  
2500MFD 40V 85p  
3000MFD 30V 50p  
3300MFD 25V 60p  
4700MFD 16V 72p  
4700MFD 40V 75p

**CAPACITORS**

3.3PF 350V 3000PF 2KV  
6.8PF 63V 3300PF 250V  
8.2PF 350V 4700PF 400V  
10PF 350V .0047MFD 500V  
12PF 1000V .0075MFD 2KV  
22PF 63V .01MFD 250V  
30PF 63V .01MFD 600V  
47PF 350V .015MFD 400V  
182PF 63V .02MFD 200V  
250PF 2000V .02MFD 250V  
330PF 63V .022MFD 250V  
330PF 160V .047MFD 400V  
330PF 8KV .1MFD 250V  
470PF 250V .1MFD 600V  
560PF 63V .1MFD 2KV  
1000PF 250V .22MFD 400V  
1500PF 250V .33MFD 250V  
1800PF 160V .39MFD 250V  
2700PF 63V .47MFD 250V

Any 10 @ £1.90

**WIRE WOUNDS**

2R 5W Thorn 3K 30p  
2.2R 4W 16p  
3.3R 9W 30p  
10R 9W 18p  
15R 17W 23p  
2.2R 9W Fus. 25p  
2.7R 7W Fus. 25p

36R 17W 23p  
2.2R 9W Fus. 25p  
2.2Ω 7W Fus. (Korting) 30p  
2.7R 5W 18p  
2.7R 7W 23p  
2.7R 17W 23p  
3.3R 5W 15p

3.3R 7W 23p  
3.3R 17W 23p  
1K2 10W Fus. 25p  
2K2 5W Fus. 25p  
2K2 7W Fus. 25p  
2K7 9W Fus. 25p  
3K9 4.5W Fus. 25p

4K7 7W Fus. 25p  
5K1 7W 16p  
8K2 7W 15p  
8K2 9W 8K Thorn 20p  
10K 7W 15p  
10K 9W 16p  
39K 4W 15p

**TRANSFORMER/LOPT**

Thorn Mains TX 3000/3500 10.00  
Thorn Mains TX 8000/8500 10.00  
Thorn S.O.P.T 8000/8500 3.50  
Thorn Scan TX 3000/3500 6.00  
Thorn EHT TX 3000/3500 6.00  
Thorn LOPT 9600 12.00  
ITT LOPT CVC1-9 9.60  
Pye LOPT 713 10.00  
Pye LOPT 725 9.85  
Pye LOPT 169 9.70  
GEC LOPT 3133 7.40  
Diode Split LOPT AT2076/35 14.75  
Sanyo LOPT AM-WM-21 6.75  
Sanyo LOPT AM-WM-4 7.30  
Thorn LOPT 1615 7.25  
Thorn LOPT 1590/91 7.25

**MULTISECTION CAPACITORS**

100+150+150 350V 50p  
220+47 350V 65p  
200+150+50 350V 60p  
200+200+100 350V 55p

16+16 450V 45p  
200+100+100+50 350V 60p

32+32+16 275V 52p  
200+200+100+32 325V 54p  
350V 70p  
100+50+150 350V 58p  
400+400 200V 72p  
32+32+16 350V 52p  
200+32+300+100 350V 70p  
225+25 350V 50p  
200+200+100 350V 70p  
200+100 325V 65p

16+16 450V 45p  
200+200+75+25 350V 60p  
16+16 500V 45p  
50+50+8 300V 55p  
100+50+100 350V 55p  
16+16 350V 45p  
2500+2500 (Thorn 8K) 63V 1.20  
150+150+100 300V 1.80  
200+47 300V 65p

**ELECTROLYTICS**

1MFD 63V 20/£1  
1.5MFD 63V 20/£1  
2MFD 350V 10/£1  
2.2MFD 25V 20/£1  
4MFD 64V 20/£1  
4MFD 350V 10/£1  
6.8MFD 40V 20/£1  
10MFD 40V 20/£1  
10MFD 160V 10/£1  
15MFD 16V 20/£1  
15MFD 63V 20/£1  
22MFD 10V 20/£1  
22MFD 63V 20/£1  
22MFD 160V 10/£1  
32MFD 27.5V 10/£1  
33MFD 40V 20/£1  
33MFD 50V 10/£1  
33MFD 250V 10/£1  
33MFD 350V 10/£1  
47MFD 350V 10/£1  
50MFD 25V 20/£1  
100MFD 18V 10/£1

100MFD 25V 10/£1  
100MFD 160V 10/£1  
150MFD 25V 20/£1  
160MFD 40V 10/£1  
250MFD 16V 10/£1  
250MFD 25V 10/£1  
330MFD 10V 20/£1  
330MFD 35V 10/£1  
330MFD 63V 10/£1  
470MFD 6.3V 20/£1  
470MFD 10V 10/£1  
470MFD 25V 10/£1  
470MFD 40V 10/£1  
680MFD 40V 10/£1  
1000MFD 10V 10/£1  
1000MFD 18V 10/£1  
1500MFD 18V 10/£1  
1500MFD 35V 10/£1  
2200MFD 25V 6/£1  
2200MFD 40V 6/£1

**INTEGRATED CIRCUITS**

BRC/M/200 1.00  
BRC/M/300 1.00  
ML237B 2.00  
MC1358P 1.30  
MC78M24 25p  
SL432A 1.80  
SAS560 2.50  
SN15846N 60p  
SN74123N 65p  
SN74154N 1.40  
SN76013ND/HS 1.80  
SN76023N 1.80  
SN76033N 2.00  
SN76115 2.00  
SN76600N 80p  
SN76544N 1.20

TBA120CQ 70p  
TBA385 1.00  
TBA480Q 1.40  
TBA540 1.10  
TBA1440C 1.00  
TC4270S 1.05  
TDA1035T 3.50  
TDA2540 3.50  
TDA2680 2.80  
TDA2690A 1.50  
TDA3560 8.00  
MC14426P 4.80  
MC14429P 4.50  
MC14514 5.00  
SAA5010 8.00  
TDA1170S 1.50

**DIODES**

AA112 8p  
AA119 8p  
AA143 8p  
BA115 8p  
BA154 8p  
BB103 8p  
BR303 4.60  
BT106 15p  
BY127 12p  
BY204 26p  
BY296 22p  
BYX22/400 30p  
IN60 8p  
IN2070 8p  
IN4001 4p  
IN4002 4p  
IN4003 4p  
IN4004 5p  
IN4005 5p  
IN4006 5p

IN4007 6p  
IN4742A 8p  
IN5254B 8p  
IN5349 14p  
IS025 8p  
IS131 8p  
IS158B 8p  
MR854 45p  
MR854 35p  
SKE102 20p  
MCR406 35p  
TCL106C 40p  
2N4444 1.50  
Y27 90p  
ZX150 15p  
OA91 5p  
MCR106/7 1.80  
MCR106/8 1.50  
TDF600H 3.00  
TDF600R 3.00  
BY255 30p

**MAINS DROPPERS**

Pye 78+161 50p  
Pye 147+260 50p  
Thorn 56+1K+47+12 1.00  
Thorn 50+40+1K5 60p  
RBM 250+14+58 (TV181) 63p  
Pye 3R5+15+45 (713) 90p

**EHT TRAYS**

Thorn 3000 5.50  
Thorn 8000 3.50  
Thorn 8500 5.00  
Thorn 9000 5.00  
Thorn 900/950 3.00  
Thorn 1500 3 stick 3.40  
GEC 2100 5.39  
Pye 713 4 lead 5.83  
Pye 713 5 lead 5.97  
Pye 725 6.35

**THERMAL CUT OUT**

Thorn 3000 Metal 1.45  
Thorn 8/8500 Plastic 1.45

**FUSES**

50MA 10 for 70p  
315MA A/S 10 for 50p  
500MA 10 for 50p  
1A 10 for 50p  
2.5A 10 for 1.00  
3.15A 10 for 1.00

250MA 10 for 65p  
750MA 10 for 65p  
7A 10 for 50p  
10A 10 for 50p  
20A 10 for 50p  
50A 10 for 50p

**SANYO SCAN COIL (mono portable)**

AM-LS-200 2.50  
M-LS 145 2.50  
4-2761-44570 4.50  
Thorn 4000 Coil L401 25p  
Thorn 4000 Coil L701/2/3 40p  
Pye 713 Coil L531/832 12p  
Philips G8 Coil L462 Late Type 65p  
Philips G9 Lums Delay Line 90p  
Pye 713 Lums Delay Line 90p  
Convergence Yoke Assy AT1023/05 5.90

**SWITCHES ETC**

Rank A823 4 P/B Assy 5.80  
Telpro 4 P/B Assy 5.80  
Thorn 3500 6 P/B Assy + Leads 1.75  
ITT CVC9 On/Off Switch + Relay 90p  
Philips G8 On/Off Switch 65p  
Thorn 3/3500 A1 Switch 50p  
Thorn 4000 A1 Switch 50p  
Korting Shift Pot 50Ω 65p  
Thorn 4000 Focus Pot 4.75

## NOW! SAME DAY SERVICE

I wish to pay by Access.

Access No. ....  
Amount .....  
NAME .....  
ADDRESS .....  
Signature .....



**326 FURTHERWICK ROAD,  
CANVEY ISLAND, ESSEX**  
Callers By Appointment

ADD 65p P&P, THEN 15% VAT.  
ADD POSTAGE FOR OVERSEAS ORDERS. ORDERS WITH  
AEROSOLS, PLEASE ADD 25p PER CAN.

# ELECTRONIC EQUIPMENT SERVICING

(TELEVISION/VIDEO)

full-time College course

TRAINING INVOLVES A HIGH PERCENTAGE OF WORKSHOP FAULT DIAGNOSIS ON MONOCHROME & COLOUR TELEVISION EQUIPMENT. CLOSED CIRCUIT TV & VIDEO CASSETTE RECORDER PRINCIPLES ARE INCLUDED IN THE COURSE

## 15 MONTHS COURSE

for beginners to include Electronic Fundamentals

## 6 MONTHS COURSE

for BSc, HND, CGLI, TEC and similar applicants

**COLLEGE  
DIPLOMA  
AND  
TEC**

Next two courses commence on April 25th & September 19th.

Also courses in Computers/Microprocessors, and Radio-communication/Radar leading to College Diploma and Technician Education Council awards.

Prospectus from:

**LONDON ELECTRONICS COLLEGE (Dept T3/4)**  
20 Penywern Road,  
Earls Court, London SW5 9SU  
Tel: 01-373 8721

## N. J. ELECTRONICS

UNITS 82/83/84 STORFORTH LANE TDG. EST. HASLAND  
CHESTERFIELD, DERBYSHIRE S41 0SN.  
TEL CHESTERFIELD 209079

### PUSH BUTTON UNITS

DECCA 30 6 button	£7.96
GEC 2110	£9.00
GEC 2112 7 button	£13.10
GEC 2136/2137	£8.35
ITT CVC 5	£10.50
ITT CVC 8	£14.00
G8 SQUARE (early)	£12.50
G8 SLOPING (later)	£13.55
PYE 713 4 button	£9.15
PYE CHELSEA	£12.98
RRI 823 4 button	£8.74
RRI 823 6 button	£9.45
RRI Z718 6 button	£9.90
TELEPRO 4 button	£8.75

### EHT TRAYS

DECCA 80	£5.95
DECCA 100	£6.00
SEIMENS UNIVERSAL	£6.30
GEC 20AX	£6.70
GRUNDIG 5011	£6.10
KORTING	£7.22
PHILIPS KT3	£6.00
PHILIPS 550	£6.50
PHILIPS 520	£6.50
ITT CVC5	£6.00
ITT CVC45	£7.00

### LOTXs

THORN 1590/91	£9.70
THORN 1615	£9.20
THORN 1690/91	£8.45
RRI T20/22	£11.95
RRI 774	£11.50
PHILIPS G8	£8.50
PHILIPS G9	£9.00
PHILIPS 210	£9.50
PHILIPS G11	£12.75
PHILIPS K30	£14.00
ITT CVC30/32	£8.50
ITT CVC45	£8.50

### ICs

TDA2522	£2.30
TDA2523	£2.40
TDA2540	£2.00
TDA2571	£2.20
TDA2581	£1.70
TDA2600	£4.25
TDA2611	£1.75
TDA2680	£1.85
TDA2690	£1.80
TDA2593	£2.75
TDA1170	£1.80
TDA1190	£2.00
MC11358P	£1.40
MC1327	£1.50
TBA920	£1.90

ADD 65 PENCE POSTAGE + 15% VAT TO ALL ORDERS.

(See CONTRAST U.K. advertisement in this copy, all your component, panel and TV needs under one roof).

## TEST CONNECTORS

Are you using the E-Z Hook Test Connector?

Many T.V. service engineers are.

For full information contact:

**I & J Products Ltd.,**  
7A Christchurch Road,  
Ringwood,  
Hants BH24 1DG.  
Telephone: (042 54) 79974

## APOLLO

### HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Delivery 2-3 days.

Just phone for a quotation. Delivery Manchester area free same day. Two year guarantee. Fitting while you wait or in your home £20 extra. Also PIL types & Toshiba.

18"	A47 - 342x343x	£37.00
19"	A49 - 120x/192x	£37.00
20"	A51 - 220x/110x	£38.00
22"	A56 - 120x/123x/140x	£38.00
25"	A63 - 120x	£39.00
26x	A66 - 120x/A67 - 120x/140x/150	£39.00

17" Ferguson Colour T.V.'s fully serviced, ideal as second set for kitchen, bedroom or caravan. £75 inc. delivery anywhere.

Philips Video Spares Available.

**061 799 0854 24 hour answering service.**  
43 Clarke Cres, Little Hulton,  
Nr. Manchester M28 6XM.

# 1000's OF COMPLETE TV'S TUBES & PANELS ALWAYS IN STOCK

Give us the opportunity to quote for all your requirements. Mixed loads delivered to your door directly from source - at unbeatable prices plus special discounts for bulk purchases.

**JUST ARRIVED!**  
Fresh stocks from our suppliers.



call  
**BRAINTREE**  
**(0376) 43685**  
24 hour service

**G8's**  
from only **£5.00**

AMPLE  
FREE  
PARKING

# CELTEL

OPENING HOURS		BRAINTREE		LONDON	
Mon-Fri	9-6 pm	Mon-Fri	10-5 pm		
Saturday	9-3 pm	Saturday	10-1 pm		

Warners Mill, South St. Braintree, Essex. Tel: (0376) 43685  
10 Shackdewell Rd. London N16. Telephone: 01-249 9265

## TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

<b>RANK BUSH MURPHY</b>		<b>PHILIPS</b>	
Z146 A640 dual std mono	8.50	170 series dual std mono	9.50
Bush A792, A793		210 300 series mono	9.50
single std mono	8.50	G8 & G9 series colour	9.00
A774 single std mono	8.50	<b>PYE 169-173-569-368</b>	<b>8.50</b>
A816 solid state mono	9.00	<b>EKCO RV305-769-725-741</b>	<b>9.00</b>
<b>DECCA</b>		<b>WALTHAM I25</b>	<b>9.00</b>
MS1700 2001 2020 2401 mono	8.00	<b>REWIND SERVICE</b> - available	
MS2404 2420 2424 mono	8.00	for most continental types i.e.	
CS1730 1733 colour	9.00	Kuba, Luxor, Korting, Tyne, Berry	
CS1830 1835 colour	9.00	Skantic, K80 £12. Old lopt required	
'30' series Bradford colour	9.00	<b>WINDINGS</b>	
80 series colour	9.00	<b>RANK BUSH MURPHY</b>	
100 series colour	9.00	T20a T22 Pry & Sec	6.00
<b>FERGUSON HMV MARCONI</b>		Z718 series primary	6.00
1600	9.50	Z718 series EHT overwind	7.00
<b>G.E.C.</b>		<b>ULTRA THORN</b>	
2047 to 2105	8.00	1690 1691 EHT overwind	7.00
2000 to 2084 dual std mono	8.00	1590 overwind	5.00
DUAL STD hybrid colour	11.00	1615 winding	7.50
SINGLE STD hybrid colour	10.00	<b>PHILIPS</b>	
<b>Indesit 20EGB 24EGB mono</b>	<b>9.00</b>	G6EHT	8.00
<b>KB - ITT</b>		G6 primary	6.00
VC200 VC205 VC207 mono	9.00	<b>PYE</b>	
CVC5CVC7CVC8CVC9 col.	9.00	691 to 697 EHT overwind	4.00
CVC20 series colour	9.00	691 to 697 primary	5.00
CVC30 CVC32 series colour	9.00		
<b>PRICES INCLUDE P. &amp; P. &amp; 15% VAT</b>			

All lopts and windings are new and guaranteed

Open Mon - Fri, 9 to 5.30 pm  
Allow 1-2 days for delivery.

**PAPWORTH TRANSFORMERS**  
80 Merton High Street  
London SW19 1BE

S.A.E. all enquiries  
Barclaycard and  
Access welcome



01-540 3955

For orders placed at the post office  
Trans cash  
506 4856

# ARE YOU

## USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling used colour televisions from home in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "How to Deal Successfully in Used Colour Televisions" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can succeed immediately.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure certain success. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail - for both televisions and new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. Plus FREE on-going advice and FREE regular updating service.

You can start tomorrow - but you'll need our guide. The latest big illustrated edition is out now, and costs just £4.95 - a small price to pay for financial independence!

ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, DARLEY ABBEY MILLS, DERBY.

To: Globus Industries Ltd., Unit 18, Darley Abbey Mills, Derby.

Please send by return post "How to Deal Successfully in Used Colour Televisions".

I enclose cheque/p.o. for £4.95.

NAME.....  
ADDRESS.....

# MANTEL

**Manchester's No. 1 in Ex-Rental TVs**  
**Over 2,000 TVs in stock**  
**Special Offer on Working Colour TV's**

All sets are Serviced with repolished cabinets ready for sale

Some Examples of UNTESTED TV's available

Philips G8 550s	22/26	£45
Philips 18"		£40
Philips G8 520s	22/26	£35
GEC S/State	from	£35
Thorn 17" 8000		£30
Decca 30	18/20/22/26	£30
Japanese	from	£30
Many other makes available from £25		

Thorn	10 for	£125
Philips	6 for	£90
Bush	6 for	£80
GEC	6 for	£60
Decca	6 for	£60
Mono TVs avail. s/s		£4 each
New TV trolley stands.		
All sizes		£4.95
All Prices subject to V.A.T.		

Discount on quantity

**Ex Equipment Panels & Tubes Available**

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

**419 Barlowmoor Road, Chorlton, Manchester 21 2ER.**  
**Tel: 061 861 8501**

## TOP TWENTY T.V. SPARES

1. Philips G8 LOPTX (genuine Philips) **£7.50**
2. Decca 30 Series LOPTX (genuine Decca) **£7.00**
3. Decca 100 Series LOPTX (genuine Decca) **£6.50**
4. ITT CVC 25/30/32 LOPTX (genuine ITT) **£7.00**
5. Pye 713/725/731 Vis Gain Module (replaces expensive 212-27327) **£6.50**
6. 5 x Universal Aerial Socket Kit (replaces most UK and Continental skts) **£5.50**
7. 10 x BU208 **£7.50**
8. 10 x BU208A **£8.50**
9. ITT CVC 5/8/9 EHT Tray **£3.00**
10. Grundig 5010/5011 EHT Tray **£3.00**
11. Decca 1730/1830 Doubler **£2.00**
12. Decca 80 Series EHT Tray **£3.00**
13. GEC 2040 (Hybrid) EHT Tray **£3.00**
14. 50X BY127 Diodes **£3.00**
15. Thorn 1500 (5 Stick) EHT Tray **£3.50**
16. Thorn 8000 Doubler **£2.00**
17. Thorn 1400 EHT Tray **£2.00**
18. Thorn 1690/91 LOPTX **£7.00**
19. Philips G9 EHT Tray **£3.50**
20. ITT Universal EHT Tray **£5.25**

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.

Please add 15% VAT and 90p P & P

**QUICK SAVE T.V. SPARES,**  
**Muxton House, Muxton, Telford, Salop.**

REG. OFFICE ONLY  
 CALLERS STRICTLY BY APPOINTMENT  
 UK ONLY

## COLOUR SETS GALORE

Hundreds in Stock.

**From £20. Guaranteed Complete.**

Mono's and non-complete sets from £3.

Most makes available.

**QUALITY COLOUR TUBES**

Reconditioned and used tubes.

**From £10 Guaranteed.**

*Don't delay, ring today.*

**ALPHA TUBES (DUNSTABLE)**

53 Lowther Road, Dunstable.

Tel. (0582) 68934

TRADE

**THE NO. 1 SOURCE  
 IN THE SOUTH**

**GOOD STOCKS OF  
 MODERN COLOUR  
 UNBEATABLE PRICE AND QUALITY  
 DON'T DELAY RING TODAY**

**TELETRADERS**

ST. LEONARDS WAREHOUSE  
 ST. LEONARDS ROAD, NEWTON ABBOT, DEVON

Telephone: (0626) 60154

# NEW



## N7128 COLOUR BAR GENERATOR

### New improved design with additional features.

- ★ Six Standard Test Patterns viz. Colour Bars, Red Raster, Linear Grey Scale, Cross Hatch, Dots, White Raster.
  - ★ All monochrome patterns available with or without burst signal (for checking colour killer action etc).
  - ★ Crystal controlled sub-carrier, Line and Field frequencies.
  - ★ Three outputs to rear panel: Video at 1V P to P into 75ohm, 800Hz (approx), sine wave audio and modulated UHF (VHF available) 4mV at 75ohm.
  - ★ 6MHz (adjustable to 5.5MHz) intercarrier sound.
  - ★ Front panel LED to indicate "Power On".
  - ★ Integral re-chargeable ni-cad battery plus mains unit/charger.
  - ★ Fully built, tested and guaranteed for 12 months.
- PRICE £85.00.

## N7118 COLOUR BAR GENERATOR KIT

- ★ Five Standard Test Patterns viz. Colour Bars, Red Raster, Linear Grey Scale, Cross Hatch and White Raster.
  - ★ Crystal controlled sub-carrier, Line and Field Frequencies.
  - ★ UHF Output (VHF available).
  - ★ Integral Ni-cad Battery and mains unit/charger.
  - ★ Optional integral sound and video board add-on kits available @ £8.95.
- Still available at special price £39.95.

Please add 15% VAT + £2.05 postage and packing per Generator.



**INTRACEPT ELECTRONICS LTD., 203 PICTON ROAD, LIVERPOOL L15 4LG.**  
TEL: 051-733 3042

TELFURB - STS - TELFURB - STS - TELFURB - STS -

## PRECISION VISION LTD

INCORPORATING

STS, LONDON AND TELFURB T.V., OXFORD  
WE NOW OFFER THE VERY BEST IN  
QUALITY USED WORKING TV's. ALL WITH  
GOOD CLEAN CABINETS AT FAIR PRICES.  
WE HAVE FULLY EQUIPPED WORKSHOPS  
AND QUALIFIED EXPERT ENGINEERS.

- ★ EXPORT ENQUIRIES WELCOME ★
- ★ VAN LOADS OF STOCK FROM SOURCE
- ★ AVAILABLE FOR OTHER WHOLESALERS
- ★ GRADED NEW TV's AND VIDEO ★  
AVAILABLE (ORDER NOW)
- ★ NEW AND SECOND HAND TV STANDS,  
TUBES AND PANELS IN STOCK
- ★ DELIVERY ARRANGED FOR BULK ORDERS

WRITE OR PHONE NOW TO THE EXPERTS

HEAD OFFICE:  
MANOR BUILDINGS,  
67 LONDON ROAD,  
HEADINGTON  
OXFORD (0865) 750212



LONDON BRANCH:  
21 COLINDALE AVE.,  
LONDON NW9  
01-200 7337

TELFURB - STS - TELFURB - STS - TELFURB - STS -

TELEVISION MAY 1983

## Switch to the biggest wholesaler of quality late model used TV's

- Thousands of Quality Sets always in stock
- Colour/Mono/VCR's and Audios available
- Murphy/Pye/Philips/Sony/National Panasonic and other big names
- We are big - we buy in bulk - we offer you the keenest prices
- Cash and Carry or we will deliver
- New and used stands always in stock

VISIT OUR NEW SHOWROOM  
TODAY OR RING US ON  
**0562 743735**

**CAMPION THOMPSON**  
ELECTRICAL WHOLESALERS



Incorporating



Campion House, Franchise Street, Kidderminster, Worcestershire DY11 6RE

SPECIAL OFFER SURPLUS STOCK TO CLEAR			
AC127	0.150	BFX88	0.150
AC128	0.150	BFY50	0.140
AC187	0.150	BFY51	0.140
AD149	0.400	BT106	0.900
AD161	0.220	BT116	1.100
AD162	0.220	BT119	1.100
AF139	0.220	BU126	0.700
AF239	0.220	BU205	0.750
AU106	1.000	BU208	0.800
AU110	1.100	BU208A	0.850
BC107	0.070	BU326	0.850
BC108	0.070	BU407	0.750
BC109	0.070	BU526	0.800
BC147	0.055	BY127	0.080
BC148	0.055	BY133	0.080
BC149	0.055	BY164	0.080
BC157	0.055	DA47	0.220
BC159	0.055	DC28	1.000
BD131	0.250	DC29	0.800
BD132	0.250	DC35	1.000
BD135	0.200	R2008B	0.800
BD136	0.200	R2010B	0.800
BD137	0.200	TBA520	0.750
BD138	0.200	TBA530	0.750
BD139	0.200	TBA540	0.750
BD140	0.200	TBA550	0.750
BD144	1.100	TBA560	0.750
BD150	0.300	TBA800	0.350
BD157	0.300	TBA810S	0.600
BD158	0.300	TBA820	0.750
BD159	0.300	TBA820	0.800
BD166	0.300	TBA950	0.800
BD175	0.300	TBA990	0.800
BD177	0.300	TCA800	0.800
BD179	0.320	TCA940	0.850
BD181	0.450	TDA1170	0.900
BD433	0.320	TDA2522	0.800
BD535	0.400	TDA2530	0.800
BD536	0.400	TDA2530	0.750
BD537	0.420	TDA2540	0.700
BD538	0.420	TDA2540	0.700
BDX65	0.800	TDA2583	0.800
BF180	0.160	TDA2640	0.800
BF181	0.180	TIP29	0.150
BF194	0.050	TIP41A	0.220
BF195	0.050	TIP42A	0.220
BF196	0.060	TIP2955	0.340
BF199	0.060	TIP3055	0.340
BF200	0.160	2N3053	0.180
BF258	0.180	2N3054	0.400
BF337	0.200	2N3055	0.320
BF338	0.200	2N3440	0.580
BF362	0.300	2N3442	0.850
BFX87	0.150		
		2N3771	0.500
		2N3772	0.950
		2N3773	1.000
		LM305K	1.000
		7805	0.350
		7812	0.380
		7818	0.380
		7824	0.380
		7905	0.350
		78L05	0.300
		78L12	0.300
		78L18	0.300
		78L24	0.300
		2SC495	1.000
		2SC1306	1.300
		2SC1369	1.000
		2SC2029	1.200
		2SC2078	1.200
		MB3712	1.500
		TA7205	1.500
		UPC575	1.000
		LM380	0.500
		LM381A	0.600
		741C8	0.150
		NE555	0.180
		LM3900	0.250
		7400	0.110
		7401	0.110
		7402	0.120
		7405	0.100
		7407	0.200
		7413	0.190
		7414	0.250
		7425	0.110
		7441	0.300
		7442	0.300
		7447	0.400
		7473	0.190
		7474	0.180
		7475	0.150
		7485	0.300
		7486	0.160
		7489	1.100
		7490	0.220
		7493	0.250
		74123	0.160
		74141	0.250
		74393	0.500
		74LS09	0.120
		74LS164	0.300
		74LS197	0.350
		74LS221	0.420
		74LS240	0.580
		74LS244	0.580
		VALVES	
		DY802	0.450
		ECC82	0.400
		ECC83	0.430
		ECC84	0.400
		ECC85	0.400
		ECH81	0.490
		ECH84	0.520
		ECL80	0.570
		ECL82	0.590
		ECL84	0.570
		ECL85	0.570
		ECL96	0.490
		EF80	0.310
		EF85	0.340
		EF89	0.430
		EY86	0.310
		EY87	0.310
		PC97	1.000
		PCF802	0.570
		PCL81	0.540
		PCL82	0.700
		PCL84	0.500
		PCL85	0.550
		PCL86	0.550
		PL200	0.850
		PL304	0.950
		PY500A	1.600
		SOCKETS	
		8 PIN	0.070
		14 PIN	0.080
		16 PIN	0.090
		18 PIN	0.120
		20 PIN	0.140
		22 PIN	0.160
		24 PIN	0.180
		28 PIN	0.200
		40 PIN	0.250
		LED	
		3mm Red	0.050
		3mm Yellow	0.100
		3mm Green	0.100
		5mm Red	0.050
		5mm Yellow	0.100
		5mm Green	0.100
		ELECTROLYTIC	
		4700UF-	
		16V CAN	0.200

Please add 40p. P&P and VAT at 15%. Govt. Colleges, etc. orders accepted.  
Quotations given for Large Quantities. Please allow 7 days for delivery.  
All brand-new Components. All valves are new and boxed.

**SUNMIT ELECTRONICS**  
9 THE BROADWAY, PRESTON ROAD, WEMBLEY, MIDDLESEX, ENGLAND.  
Telephone: 01-904 2093

## UNIVERSAL PROGRAMME SELECTOR FOR VARICAP TUNING

UK Regd. Design No. 1006611

6 way interlocked d.p. switch 100 K tuning potentiometers


Top quality through hole plated pcb

Dimensions: 5" by 2 1/2" by 1"  
Ideal for replacement when original parts are obsolete or unobtainable.

Template guide supplied for drilling of your own fascia design

Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification

All orders despatched same day

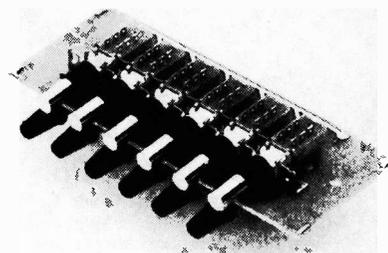

### DIRECT REPLACEMENT FASCIA/MOUNTING KITS

Type 30-80 Replaces 7 piano-key unit as fitted to Decca/Telefunken 30 and 80 chassis

Type 30-C Replaces 7 piano-key unit as fitted to Decca console using long perspex illuminated control panel

Type 100 Replaces 8 position touch tune selector (AEG SAS 660 SAS 670) as used in Decca/Telefunken 100 chassis

Type CVC8-9 Replaces 5 rectangular push button plus thumbwheel as used in ITT

**SELECTOR £11 + VAT**

**FASCIA/MOUNTING KITS (each) £2 + VAT**

**ALDERSON-JAMES LTD**

**160 KINGS ROAD ● HARROGATE ● N. YORKS**

**TEL: HARROGATE (0423) 60058 HG1 5JG**

## CENTREVISION

**NO. 1 IN WALES**

**9000 Sq Ft 2000+ CTV**

- ★ DECCA 18" £18 + VAT
- ★ KORTING 22-26 CTV £14 + VAT
- ★ HITACHI CTV FROM £28 + VAT
- ★ THORN 9000 20" £40 + VAT
- ★ RANK Z719-Z718-T20 VARIOUS PRICES
- ★ PHILIPS 550 22" REMOTE £35 + VAT
- ★ GEC SOLID STATE FROM £28 + VAT
- ★ THE TRADE SAY THE BEST QUALITY SETS ON THE MARKET TODAY
- ★ BULK TERMS TO OTHER WHOLESALERS
- ★ PYE 17" MONO PORTABLES £32.50

(GRADED STOCK) + VAT

DECCA 30 SERIES 22" IN 10'S £16.00

SELECTION OF WORKING SETS

**DONT DELAY PHONE TODAY**

**0222-44754**

**CENTREVISION HOUSE,**  
SLOPER ROAD,  
CARDIFF CF1 8AB.

### HIGH GAIN AERIAL BOOSTERS

#### B45 H/G UHF Television

Tunable over the complete UHF band. Gain above 20dB. noise 2.8dB.

#### B14 - Band 3 VHF Television

Tunable over the complete Band 3 (Channels (E) 5 to 13). Also covers Aircraft & 2 meter Amateur Bands. Gain above 28dB. Noise 2.8dB.

PRICE each £8.70.

### AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 - For Mono or Colour this is tunable over complete UHF television band.

B11 - For stereo or standard VHF/FM radio.

B12 - for VHF television band 1 & 3. All amplifiers are complete and ready to use Battery type PP3 or 8V to 18V DC next to the set type fitting.

PRICES £6-70 each.

### AERIAL SPLITTERS

2 way T-TYPE £2.70 each

Goods despatched on receipt of order.

All Prices Fully Including P & P per Order 30p. S.A.E. for Leaflets. Access Cards.

**ELECTRONIC MAILORDER LTD,**  
62 Bridge St, Ramsbottom, via Bury, Lancs. BLO 9AGW.  
Tel Rams (070 682) 3036.

## M W ELECTRICAL

BROOK PARK AVE. (OFF MARINE RD.)  
PRESTATYN

**"WE DO NOT BOOST TUBES"  
COLOUR TV'S**

COMPLETE FROM £10.00  
TRADE WORKERS FROM £25.00  
MINIMUM OF TEN

G8, DECCA, BUSH, THORN. ALSO MONOS ETC.

NEW & GRADED TVs ALSO AVAILABLE

OPEN SAT MORN, LATE NIGHT THURS 8pm

**TEL: PRESTATYN (07456) 89849/89970**



# VISIONTEL

## BEST QUALITY EX RENTAL SETS FROM £10 HERE IN CENTRAL LONDON!

Hundreds of sets always in stock  
**AT VERY COMPETITIVE PRICES**

For Example:

	Untested	Good Workers
Philips G8	£15	£25
Philips 550	£20	£35
Thorn 3500	£10	£25

ALL PRICES SUBJECT TO VAT

We also have **PYE, DECCA, GEC, ITT, GRUNDIG, JVC, PHILIPS G9 + G11, THORN 9000** and **PORTABLE TVs**

**FOR FURTHER DETAILS TELEPHONE 328 3787  
 OR COME ALONG TO  
 55 KILBURN HIGH ROAD, NW6**

### TV TUBES TUBE POLISHING WORKING TV's WORKING PANELS FREE DELIVERY\*

Quality, High Temperature Reprocessing

Colour Tubes	One year guarantee (optional extension up to three years)	Two year guarantee (optional extension up to four years)
Delta		
90° up to 20"	£26	£29
90° up to 22"	£30	£33
90° up to 26"	£32	£35
110° 26"	£33	£36
(fast heat, narrow neck)		
In Line & PIL		
Up to 20"	£36	£42
Up to 22"	£38	£44
Up to 26"	£40	£46

Please add £12 plus VAT for optional guarantee on any type of colour tube.

MONO TUBES (One Year Guarantee)

A50-120W/R £12, A61-120W/R £13, Mono Portables £16

All tubes exchange glass required.

**FOLLOWING ITEMS CALLERS ONLY**

Solid state working colour TV's, with well view tubes fitted (1 year guarantee on tubes) from Only £45

Working TV Panels at Reasonable Prices

Your good, working tubes with scratches or small chips, can be **POLISHED** with our purpose built polishing equipment. Only £7 per tube.

Delivery Service up to 40 miles from Luton. Fixed Charge £3. \*Free Delivery for tube orders over £50 + VAT.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

Send for a fully comprehensive price list and a wall chart of approx 1700 Colour Tube Types that can be processed by us.

### WELL VIEW

114-134 Midland Rd.  
 Luton, Beds.

Open Mon-Fri 9am-5pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:

Retach Ltd., Northwood, Middx. Tel. 9694-27019  
 West One Distributors Ltd., Gt. Misenden, Bucks. Tel. 024-06-3609  
 Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901  
 Daventry Rentals, Daventry, Northants. Tel. 03272 77436  
 S.S. TV Services, Bradford, Yorks. Tel. 0274-498180

Please note that we have no connections whatsoever with any other business having similar name to ours.

### A.B.C. ELECTRONICS

Rear of 20, HANKINSON ROAD,  
 WINTON, BOURNEMOUTH.  
 TEL: 519542

**TRADE TV's BEST PRICES**  
 Colour From **£12.00 + VAT**  
 B&W From **£2.00 + VAT**

**DISCOUNT ON QUANTITIES**

**ALL MAKES - ALL SIZES - ALL COMPLETE  
 CALL IN OR RING FOR COMPETITIVE QUOTE  
 FULLY REFURBISHED SETS AVAILABLE  
 + DELIVERY SERVICE**

### MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

(1) You have not received the goods or had your money returned; and  
 (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

LONDON'S LARGEST TELEVISION WHOLESALER ...  
with over 4½ thousand sq. feet.

## "TELEMANN"

8-10 RHODA STREET,  
(Off Bethnal Green Road)

LONDON E.2. FREE CAR PARK

TEL: 01-739 2707

ALL MAKES IN STOCK AND GUARANTEED COMPLETE

PYE 22" COLOUR FROM £7.50

PHILIPS 22" G8 (Teak cabinet) PARCEL OF TEN £12

MONO DUAL STANDARD £2

- SINGLE STANDARD £5

FREE DELIVERY TO THE LONDON AREA!

TELEPHONE 01-739 2707 - NOW!

## N.G.T. COLOUR TUBES

First Independent Rebuilder with

**B.S.I. CERTIFICATION**

(Certificate No. 004)

2 year guarantee; 4 year option

All Colour Tubes are debanded, high temperature pumped and rebanded using new adhesives and new tension band.

19" £30, 20" £32, 22" £33, and 26" £38.

No exchange tube required on delta types.

**N.G.T. ELECTRONICS LTD.,**

120, SELHURST ROAD, LONDON S.E.25

Phone: 01-771 3535.

20 years experience in television tube rebuilding. add VAT at 15%

## TVs TVs TVs

### PANELS PANELS PANELS

DECCA 18" 20" 22" 26"	from £25	BUSH A823 22" 26"	from £25
PHILIPS G8 22" 26"	from £25	HITACHI 18"	POA
PHILIPS 570 18"	from £35	THORN 3500 20" 22" 26"	from £25
PYE CT200 18"	from £35	THORN 8800 22"	from £30
PYE CHELSEA 18"	from £40	ITT CVC8 22"	from £40
NAT. PANASONIC 18"	POA		

The above prices are for working TVs, Non workers usually available Please ring for prices.

#### QUANTITY DISCOUNT FOR 10+

Panels for most makes available with 3 month guarantee.  
Add £1.70 per panel for postage + 15% VAT.

(Also see N.J. Electronics advertisements, all your TV spares panels etc. under one roof).

#### CONTRAST U.K.

82/83/84 STORFORTH LANE TDG. EST. CHESTERFIELD, DERBYSHIRE S41 0SW  
Tel. Chesterfield (0246) 209061

EMO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES  
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●

### IMMEDIATE CREDIT AVAILABLE—TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY  
TV COMPONENT BY RETURN  
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

**TELE-PART (WTON) THE TELECENTRE, WORCESTER ST.,  
WOLVERHAMPTON (0902) 773122**

## 1983 PRICE LIST

# DISPLAY ELECTRONICS

### GOLD LABEL COLOUR TUBES

2 YEAR GUARANTEE

90° up to 19".....	£33
90° up to 22".....	£36
90° up to 26".....	£39

The above prices are for standard 38mm Delta Gun Types.

Add £5 Gun surcharge for 20AX Types.  
Other in-line & P.I.L. Types, prices on application.

### GOLD LABEL MONO TUBES

2 YEAR GUARANTEE

19"/20".....	£12
23"/24".....	£14

### GREEN LABEL COLOUR TUBES

12 MONTHS GUARANTEE

90° up to 19".....	£28
90° up to 22".....	£31
90° up to 26".....	£34

Green Label Prices apply only to standard 38mm Delta Gun Types. They will be of particular interest to customers refurbishing ex-rental sets.

### BUDGET CORNER

Buy any 5 mixed types take 20% discount.

Buy any 3 mixed types take 10% discount.

Budget prices apply only to colour tubes. The mix can include Gold & Green Label Types if required.

### CALLERS WELCOME

Late night Thursdays until 8 p.m.  
Saturdays until Midday

N.B. Customers intending to collect orders are requested to telephone in advance:- even popular types may be out of stock for short periods.

UNIT 1  
SWAN WHARF  
WATERLOO ROAD  
UXBRIDGE  
MIDDLESEX

Telephone: UXBRIDGE 55800

**SETS & COMPONENTS**

*The* **VINTAGE**  
**WIRELESS COMPANY**

**NOSTALGIA - COLLECTING**  
1900-1950s

Publishers of The Antique Wireless Newsheet  
(Sample on Request)

Suppliers of: • Valve Radio sets & Amplifiers



- Valves, Components
- Repairs & Restorations
- Service Data & Manuals
- Historical Data
- New and Used Books/Magazines

The complete service for the collector and enthusiast of Vintage Radio.

**THE VINTAGE WIRELESS COMPANY**

64 Broad Street, Staple Hill, Bristol BS16 5NL  
Tel: Bristol (0272) 568472 - 24 hour Ansaphone, Closed Mondays

**TUBE RE-GUNS**  
2 YEAR GUARANTEE

56-120 **£30** inclusive  
Also at £30 A51-110

A49-191, A44-271, A47, 342 or 3.

A66-120, 140, 410, A67-120.  
£35 inclusive.

**SLIGHTLY USED TUBES**  
A56-120, A51-110 £15.00  
A66-120 £19.00

3 month guarantee

**IN-LINE RE-GUNS**  
£48 inclusive

51-161, 66-500, 56-500 and many more  
with 1 year guarantee.

**PROFESSIONAL STICK**

**DE-GAUSSING-COILS**  
£19.50 EACH INCLUSIVE & DELIVERED  
1 Year Guarantee.

No need to spend £5 returning old glass  
if you buy from us (except in-line).  
Tubes delivered and insured within a  
few days of receipt of cheque.

£6 delivery per tube, 2 for £10 including  
Scotland and N. Ireland.  
Discounts for more than 2.

**U-View (Tubes)**  
29 Warmsworth Road, Doncaster,  
Yorks DN4 0RP. 0302 855017.

Open 7 days Callers ring first.

Thorn 3000/3500  
Thorn 9000

**UNIVERSAL**

1 year guarantee

**TRIPLERS**  
**£4.50** inc. p.p.

The UNIVERSAL TRIPLER can be used in most  
G.E.C., I.T.T., Pye, Rank, Decca & Continental  
sets.

**WING ELECTRONICS**  
15 Waylands, off Tudor Rd, Hayes End, Middlesex

**COLOUR TV PANELS** Fully Tested & Working

	IF	CDA	Decoder	LTB	Line Board	Frame Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-	-
DECCA 13/30	3.00	-	5.00	5.00	-	-	4.00
BUSH 'A'	2.00	-	5.00	5.00	2.50	-	2.00
THORN 8-8½"	-	-	7.00	5.00	-	-	3.00
PYE 205	3.00	3.50	5.00	8.00	-	2.00	-
THORN 3+3½K	3.00	-	5.00	8.00	-	-	10.00
G8	6.00	-	8.00	5.00	15.00	-	5.00
BUSH twin chip decoder	10.00	-	-	-	-	-	-

Post & packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

26" CRT's fully tested £10

fitted with  
brand new  
transformer

**LAVITE LTD.,**

Viaduct Mills, Milnsbridge, Huddersfield. Tel: 0484-643273

Callers by appointment only.

# TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £5.64 per single column centimetre (minimum 2.5 cms). Classified advertisements 33p per word

## ARE YOU OVERSTOCKED?

Turn your surplus stocks into cash

**£500,000 AVAILABLE**

for any surplus electrical stocks ie. TV's,  
Video's, Washers etc.

Phone in strictest confidence:

Mr R. Walker,

**Brighthouse (0484) 714413**

## TELEVISION

Trade Supplies of Good  
Quality Colour & Mono  
TV's. Most Makes  
available, suitable for  
Sale or Re-Rent.

## GENERAL FACTORS

UNION STREET  
DONCASTER  
(0302) 49583 68416

GOOD MOTORWAY ACCESS

## MONITOR TUBES

"GREEN"

12" 110°

AW31 - 550GH

MEN-TU ELECTRONICS LTD.

SALTERNS LANE,  
FAREHAM, HANTS.

Tel: 0329 235116.

CASED ISOLATION TRANSFORMERS 500w max,  
suitable TV work £8.00 + £2.85. Working test equip-  
ment Meters, P.S.U's etc. SAE lists: S.H.E. 5, St  
Joseph's Park, Ballycruttle, Downpatrick BT30 7EN.

## CAMPBELL ELECTRONICS LTD. COLOUR T.V. PANEL EXCHANGE/ REPAIR SERVICE

THORN, RANK, PHILIPS, GEC,  
DECCA, TELPRO, GRUNDIG etc.  
90 Day Guarantee on all repairs - same  
day postal service.

Telephone Telford (0952) 502422  
for catalogue and price list.

**CAMPBELL ELECTRONICS LTD.,**  
Unit 5, Heath Hill Estate,  
Dawley, Telford, Shropshire.

## EX RENTAL C.T.V.'s & REGUN TUBES

RBM, THORN, DECCA, PYE GEC,  
GRUNDIG, ITT, PHILIPS G8, G9, G11,  
JAPANESE  
From £10

Also all modules from £4 untested.

**STARLITE ELECTRONICS,**  
80 Como St., Romford, Essex.  
Telephone Romford 752537  
London Code 3.

## TVDX/SATELLITE EQUIPMENT

VHF to UHF Converter. 12v supply required.  
Ideal way to start DXing £13.95. Band I/II  
Mosfet mains preamplifier. High gain, low  
noise £27.50 (Bill available). **SOON TO  
COME** complete 4GHz LNA/downconverter  
for satellite reception £200 (approx.).

SAE data lists:

H. COCKS

Cripps Corner, Robertsbridge, Sussex TN32 5RY.  
Telephone 058063-317

# SERVICE PAGES

(minimum 12 words), box number 60p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

## RANK BUSH MURPHY TV PANELS

REPAIR/SALE SERVICE BY EX RRI EXPERTS. SAME DAY RETURN WITH 3 MONTHS GUARANTEE. GENUINE RBM TECHNOLOGY AT YOUR SERVICE. WE ALSO BUY T20, 22, 718 CHASSIS PANELS, WORKING OR NOT. CASH WAITING. PLEASE CONTACT MONDAY TO SATURDAY 9am to 7pm

T.K. PANELS SERVICE  
Tel: (0438) 61567

31 Bronte Paths, Stevenage, Herts.

Northwood Middx (9684) 27019 01-845 2036

## RETACH LTD.

Rear 78 High Street, Northwood, Middx.

LOOK G11 PHILIPS (inline tube)	£75
Also:	
PHILIPS G8 550 (22 Slant Button)	£35
PHILIPS G8 520 (22 Flat Button)	£25
PHILIPS G8 522 (26 Flat Button)	£18
PHILIPS G8 526 (26 Slant Button)	£25
PHILIPS G9 585 (26 Remote)	£35
RANK T20/22 Series (Incline Tube)	£75
RANK 823 (White Stocks Last)	£10
RANK 718 (Incline Tube)	£45
THORN 9600 (Incline Tube)	£55
MONO:- PYE T184-24" Mono (Solid State)	£18
VIDEOs:- PHILIPS N1700, N1702, videos	£39
TUBES:-	
20" Rebuilt Colour Tube, 2yr Guar.	£29
22" Rebuilt Colour Tube, 2yr Guar.	£33
26" Rebuilt Colour Tube, 2yr Guar.	£35

All Prices+VAT - Callers by Appointment

## T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537  
194, Acton Lane, London W.4.

## CURE VIDEO INTERFERENCE

Stop interference from spoiling your off-air recordings or breaking into your pre-recorded playbacks. Most TVI filters are ineffective; our braid-breaker design really works. They are recommended by Sony and supplied to British Telecom.

For details ring or write:

Elidee Technology, (Dept. TVI),  
Freeport, Lowestoft, Suffolk NR32 3BR.  
Telephone: 0502 68106.  
Trade enquiries welcome

## CAMPBELL ELECTRONICS LTD.

Distributors of specialist spares to radio and television service depts.

We stock semiconductors, I/Cs, special T.V. and audio spares, service aids, rebuilt CRTs etc.

Fast off the shelf delivery of stock items.

Send S.A.E. or telephone for full catalogue and price list.

## CAMPBELL ELECTRONICS LTD.,

Unit 5, Heath Hill Estate,  
Dawley, Telford, Shropshire.  
Telephone Telford (0952) 502422.

# SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.

Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBANDED TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAINS LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

# CLEARANCE SALE

## LARGE QUANTITY OF GOOD CLASS COLOUR TELEVISIONS

BUSH, PYE, GEC, THORN, PHILIPS ETC.

Excellent Cabinet Condition.

Genuine Change Over TV's and Repositionings.

## LARGE QUANTITY SOLID STATE BUSH £10 Each

(Minimum quantity 5)

GEC HYBRID  
£5

PYE HYBRID  
£5

MONO  
£3

100's to choose from!!

We export large quantities of TV's weekly. Can we help you?

Discount on Quantity Orders.

OVER 1,000 MONO TV's IN STOCK FROM £3.

100's colour tubes suitable for reconditioning. Working colour TV's to order ie.

Bush 20"/22" 21C. excellent picture, ready to sell. Only £39.

CALL AND SEE OUR SELECTION

## WHITE GOODS

All types of Washing machines, Vacs, Fridges, Cookers, etc. Hoover Auto's, Servis, Hotpoint, Hoover Uprights, Vacs. 500 always in stock. Fully reconditioned Hoover

Twin Tubs and Upright Vacs, all models. Phone for details.

PAY US A VISIT AND YOU WILL NOT BE DISAPPOINTED.

# N.W. ELECTRONICS

BOLINGBROOKE STREET (PICKFORD BUILDINGS), BRADFORD 5.  
3 minutes from Motorways. Telephone 0484 714413.

GRUNDIG, NORDMENDE, complete sets, circuits, reconditioned panels supplied. Television Magazine, colour manuals wanted. 0785 814643.

## BULK BARGAIN T.V. SERVICE PACK

Contains at least £50 worth of T.V. service components and accessories. Loads of hard to obtain T.V. spares and components. Ideal for the service engineer. Only £12.50, carr. £2.50. Ref. Guar. HAVE YOU SEEN THE GREEN CAT? 1000s of new components, T.V., radio, and electronic items at unbelievably low prices. Probably the cheapest in the country. Send 40p for GREEN CAT and reserve FREE RECORD SPEED INDICATOR.

MYERS ELECTRONICS, Dept. TV2,

12/14 Harper Street, Leeds LS2 7EA.

Next to Union Jack Clothing Store, Leeds LS2 7EA.

Callers welcome at our NEW retail premises.

Open 9 to 5 Mon to Sat. Tel. 452045.

SECOND HAND COLOUR TV SPARES and tubes, most makes. Telephone Southport (0704) 74411. Anytime.

## RANK BUSH MURPHY TRANSFORMERS

### LINE OUTPUT TRANSFORMERS

#### Z718 (T703A, T706A)

(1) New (Complete) £20.50

(3) Less Focus Module and Rectifier £10.50

#### Z718 SPARES (T703A, T706A)

Pri. - £5.50, Sec. - £6.00,  
Rectifier - £3.00, Lead - £2.50

T20, T22 (T705A) £9.00

T26 (T705B) £9.50

### Switch-mode Transformers

T114 A/B £8.00

Genuine RBM Units

Prompt Postal Service.

Add 15% V.A.T. to all Prices.

DISCOUNT For QUANTITIES

### WOODSDALE COMPONENTS MR SKEHAN

34 Field End Road, Eastcote,  
Pinner, Middlesex HA5 2QT.  
01-868 5580

Agents Office, callers by appointment only.

**TRADE COLOUR TV'S**

MOST MAKES & SIZES  
FROM £10. DISCOUNTS  
5% & 10% OFF FOR 5+ & 10+.  
MONDAY-SUNDAY.

Tel: Southampton 814318

# TELEVISION

JAPANESE COLOUR TV's, Hitachi, Sony, Panasonic, Mitsubishi, Toshiba, Sharp. Colourland TV. Trade Only. 0484 863489.

## IRISH T.V. DEALERS

(No. 1 for s/hand T.V.s)

1. 400 sets to choose from.
2. Most leading makes sold.
3. Fresh stocks weekly.
4. Delivery to any part of Ireland.
5. All sets with VHF/UHF tuners.
6. Colour from only £70 mono from £15.

Visit our new spacious warehouse:

**TELE SPARES LTD.**  
Unit 113 Elm Road, Western Ind. Estate,  
Dublin 12.  
Tel: 01 521756/521211.

### EAST ANGLIA BARRY TV SERVICES

Good quality working colour televisions (from £35 plus VAT) straight from our retail shelves, (with good tubes & cabinets). Available at all times - delivery available anywhere.

Contact John, Dave or Steve on  
Cambridge 69215  
or Ely 61462

Your Satisfaction Is Our Concern.

### TRADE TV'S

For the best quality at the cheapest prices in Nottingham.

### CASTLE TV

100s of ex-rental sets in stock.  
S/S colour from £12.50  
S/S mono from £3.00

TV Sales & Spares to the Trade.  
346 Radford Road,  
Nottingham.  
Tel. Mr. Atkins  
Nottingham 785321.

### WE HAVE MOVED TO NEW PREMISES TEST EQUIPMENT

- UHF T.V. Pattern Generators £17.25
- Crosshatch & 4 patterns £18.50
- As above but with Greyscale
- Prices include P&P and VAT.

- Also available:
- PAL COLOUR BAR GENERATOR
- CAPACITANCE METER
- TRANSISTOR TESTER
- S.A.E. for prices and full details.
- The above items are not kits.
- C.M.J. ELECTRONICS
- Unit 8, 16 Union Mill St., Horseley Fields,  
Wolverhampton, WV1 3DW.  
Tel. (0902) 871563

### TELEVISION TUNER

REPAIRS ALL TYPES  
BRITISH, EUROPEAN,  
JAPANESE ETC.

**MEN-TU ELECTRONICS,  
SALTERNS LANE,  
FAREHAM, HANTS.  
Tel: 0329-235116.**

### WIZARD DISTRIBUTORS

MANCHESTER  
SPECIALIST DISTRIBUTORS TO THE TRADE OF  
T.V. & VIDEO SPARES.  
WE STOCK A FULL RANGE OF PARTS &  
COMPONENTS INCLUDING C.R.T.'s  
RANK - THORN - PHILIPS - ITT - DECCA -  
GEC ETC.

THANDER & LEADER STOCKIST  
TRADE COUNTER OPEN: 9-4.30  
CATALOGUE ON REQUEST.  
Mail Order Enquiries Welcomed  
**EMPRESS STREET WORKS,  
EMPRESS STREET,  
MANCHESTER M16 9EN.  
TEL: 061-848 0060**

### JABCO LOPT TESTER

This instrument is now used in hundreds of Service Workshops and Manufacturers with household names all round the world. Saving countless hours in checking Line O.P stages and the unnecessary fitting of new LOPTS.

Mains operated. Straight forward indication of good or bad by Red & Green Leds. No controls to set up.  
Instruction booklet on testing many common Lopts in situ including jellypots.  
£16.50 inclusive. C.W.O. delivery 3 days. £18 overseas post by sea. £21 airmail.

**J. BAKER & CO.**  
1, Old Shoreham Rd., Southwick,  
Sussex BN4 4RD.  
Tel. Brighton 593315.

SEMICONDUCTORS		MODULES	
AC 176	0.25	PL802 Solid State	3.25
BC 142	0.25	Dropper Resistors	
BT 106	1.00	GEC 2018	0.70
BU 105	0.80	Philips G8 5083	1.30
BU 126	1.00	Philips 210/5051	0.90
MC 1327PQ	1.20	RRI A640	1.20
R2008B	1.00	TCE 1500	1.30
R2010B	1.00	TCE 3000/3500	0.90
SL901B	4.00	TCE 8000/A	0.95
SN76013N	2.00	TCE 8500/8800	0.85
SN76131N	0.70	Add 0.50 for postage & packing	
TAA 550	0.25	Add VAT @ 15% to total.	
TBA 120SA	0.50	<b>ACORD ELECTRONICS LTD</b>	
TBA 990Q	1.00	45 Stoke Road, Guildford GU1 4HT	
TDA 1327	1.20		
2N4443	0.80		
2SC643AY	1.50		

### BOOKS & PUBLICATIONS

ANY PUBLISHED, full-sized service sheet by return £2 + L.s.a.e. CTV/Music centres £3. Repair data with all circuits, layouts, etc. Your named TV or Video £8.50. Free 50p mag. all orders, queries: TIS (TV), 76 Churches, Larkhall, Lanarkshire.

### ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for .....

insertions. I enclose Cheque/P.O. for £ .....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)


NAME.....

ADDRESS.....

Send to: Classified Advertisement Dept.

### TELEVISION

Classified Advertisement Dept., Room 2612,  
King's Reach Tower, Stamford Street,  
London SE1 9LS. Telephone 01-261 5848.

Rate  
33p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

MAY/83

# SERVICE PAGES

## FOR SALE

**TUBE REBUILDING PLANT** for sale. Fire salvage in good restorable condition. Offers. Phone 0706 523415.

### TRADE TELEVISIONS

- Wide range of used sets in good cabinet condition.
- Plenty of working sets - try ours!
- Delivery arranged anywhere.

B.T.V., 39 St. Stephen's Road,  
Birmingham B29 7RR.  
Tel: 021-471-3836.

**COMPLETE REGUNNING PLANT** for sale. Five electric ovens. Apply Box No TV 178.

**TWO TELEVISION PROJECT CTV's** one 26" completed, in use 2 years. Good order. Other 22" completed but not assembled. Ideal enthusiast. £60. 01-500 4673.

**JVC HR-4100** portable VHS recorder, little used, with Ferguson 3V20 colour camera. £495. 0482 48900.

## WANTED

**WANTED** Emo, Rigonda, Saba, Telefunken, TV service manuals. Reasonable prices paid. Phone Yateley, Hants. (0252) 876968 evenings.

## WANTED

Modern unused TV components Lopts, Trays, Transistors, Fuses etc. Also VHS spares motors, Clutches, Pinch Wheels, Head Drums etc. Job lots purchased. Cash waiting.

Confidential Service Box No: TV 177

**WANTED PHILIPS/PYE G11** Colour TVs, any quantities. Hornchurch 58513, Mr. Morris.

**WANTED.** 12 good clean working 22" TV's. Either ITT CVC 30, Thorn 9000 or Philips G11. Box No. TV 176.

**WANTED FOR CASH.** Video, TV's, spares, electronic components. Tel: 965 1230. Box No. TV 175.

## SPECIAL CLEARANCE

Colour TV's good working order £25. Offer of the month Philips G8s £25. Any quantities. Most make and sizes available. Complete non workers £10 each. Mono sets £2 each. Spare parts available.

Tel: (0203) 714213 or  
(041) 221-2146.

**TELEVISION 1978 PROJECT** complete in cabinet with remote control board unfinished. Offers: 77 Tedder Road, RAF Halton, Aylesbury, Bucks.

## AERIALS

### AERIALS & ACCESSORIES

QUALITY components at competitive prices. UHF 10 element from £1.10. 18 element from £2.20. FM2 from £2.40. FM4 from £4.95. Lashing Kits from £1.20. Wall Bkts. from 85p. Masts available 2' to 20'. Aluminium coax plugs from 10p. Coax cable from £9.30. Full range of Accessories and Amplification Equipment available.

Comprehensive price list on request.

S.C.S. AERIALS (Aerial Distributors)  
14 Tanners Crescent,  
Hertford, Herts. SG13 8DS  
Tel: 0952 50478

## SERVICES

**VIDEO, HI FL, TELEVISION** Servicing by highly experienced engineers. Trade contracts required. Capital Electronics 01-874 0885.

**TEST EQUIPMENT SERVICED.** Scopes, generators, meters, etc. Telford Communications, 3 Park Road, Much Wenlock, Shropshire. Tel: 0952 727719.

## MISCELLANEOUS

**BURGLAR ALARM EQUIPMENT.** Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 682674.

**BURGLAR ALARM EQUIPMENT.** Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

# ALARMS

## FREE CATALOGUE!



OUR GREAT NEW ILLUSTRATED CATALOGUE IS PACKED WITH INFORMATION ON SUPERB QUALITY, PROFESSIONAL BURGLAR ALARM EQUIPMENT

**AT UNBEATABLE PRICES!**

SEND SAE OR PHONE NOW FOR YOUR COPY

A.D. ELECTRONICS  
DEPT. TV  
217 WARBECK MOOR  
AINTREE LIVERPOOL  
L9 0HU/051 523 8440

THIEFCHECK BURGLAR ALARM D-I-Y SYSTEM MAIN DISTRIBUTOR

When replying to Television Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## SERVICE SHEETS

### TECHNICAL INFORMATION SERVICE

**SERVICE SHEETS:** full size by return - radio, mono, etc. £2 + large sae. CTVs & Music Centres from £3.

**SERVICE MANUALS:** Sole suppliers most obsolete equipment. Everything stocked to latest releases. Fantastic stocks CTVs/Videos. E.g. A823 £6.50; Autovox (early) £6.50. Tyne 5000/6000 Series £7.50.

**COMPREHENSIVE TV REPAIR COURSE** - Complete data almost every fault. - Huge beginners section. - Only £8.50.

**TV REPAIR MANUALS** - All 12 for £75. - Mono portables (new) £6.50. - Early VCR, £10.50.

**CIRCUIT DIAGRAM COLLECTIONS IN HUGE BINDERS:** British CTV (3) £42.50; Foreign CTV (2) £27; Early VHS/Phillips video £15; Mono TV standard + portables £29.

**REPAIR SYSTEMS (REPAIR DATA, CIRCUITS, ETC):** Video 1, £24.50; Foreign CTV, £40; Mono TV, £31.50.

SAVE £12 - BRITISH CTV ONLY £60 - LIMITED TIME; Complete integrated TV Repair System £160.

Quotations/free 50p magazine/price lists/etc for large sae.

£2 plus 8" x 10" S.A.E. for service sheet and manual catalogues with £4 vouchers.

PHONE 0698 883334 FOR FAST QUOTES - Open 4-6 daily, 11-1 weekends.

T.I.S., 76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

### 30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £2.00. Tuners £2.00. Tape Recorders, Record Players £2.00. Transistors, Stereograms & Music Centres £2.00 + SAE. Also Colour Available. Car Radios £3.00 + SAE. All Radiograms £2.00. State if Circuit will do if sheets are not in stock. All TV Sheets are full-length 24x12, not in Bits & Pieces. All other Data full-lengths.

All sheets from £2.00 except Colour. OLD VALVE Radios £3.00 + SAE 9" x 3".

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882

MAIL ORDER  
S.A.E.

### SANDHURST PUBLICATIONS

Television Service Sheet Specialists

Workshop Manuals, large selection of Japanese and European TV Sheets. Callers 5.30-7.00 pm. Upper Floor. Send S.A.E. for Catalogue and Enquiries:

49C Yorktown Road,  
Sandhurst, Camberley, Surrey GU17 7AG.

## COUCHES

**BELL'S TELEVISION SERVICES** for service sheets on Radio, TV, etc. £1.25 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

**CONQUER THE CHIP...** Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C4, Reading, Berks RG1 1BR.

**STEVE BEECHING** will be holding another 2 day training Course, on 14th and 15th May 1983. If you would like details, please ring or send a letter to: NEWARK VIDEO CENTRE, 108 London Road, New Balderton, Newark, Notts. Tel: Newark 71475.

DIODES		Voltage Regulators	
OA 47	10p	BZX 83c33	10p
OA 90	10p	BZX 84c6v8	30p
IN 60	5p	BZX 85c8v2	10p
IN 541	5p	BZY 88c0v7	10p
IN 914	5p	BZY 88c3v9	10p
IN 2069a	10p	BZY 88c4v3	10p
IN 2070	10p	BZY 88c4v7	10p
IN 4001	5p	BZY 88 6.8v	20p
IN 4002	10p	BZY 88 6v2	20p
IN 4004	10p	BZY 88c12	20p
IN 4005	10p	BZY 88c22	20p
IN 4006	5p	CV 8617	10p
IN 4007	7p	Y 716	20p
IN 4148	10p	Y 730	20p
IN 4448	10p	Y 827	30p
IN 4742	10p	Y 860	30p
IN 4722	10p	Y 933	5p
IN 4751	10p	Y 997	30p
IN 5235	10p		
IN 5254	10p	All diodes at 10p in this list 20 of one type	£1.00
IN 5392	10p		
IN 5401	10p	Alternative diodes eg IN 4448/ BY 298 will be sent should we be out of stock.	
IN 5928B	10p		
IA 5401	10p		
IAV 30	10p		
IM 72255	10p	R 1038	50p
IR 106a	20p	R 1039	50p
IR 3051	10p	R 2008b	£1
IS 164	10p	R 2009	£1
IS 921	10p	R 2010b	£1
IS 3011a	10p	R 2210	60p
IS 3072a	10p	R 2257	60p
IS 5024a	50p	R 2323	15p
IS 5030	50p	R 2461	£1
ITT 921	10p	R 2030	£1
ITT 923	10p	R 2443=BD124	40p
ITT 1075	10p	R 2540	£1.25
ITT 2001	10p	R2737=TIP31A	40p
ITT 2002	10p	R2738=TIP41	30p
ITT 4150	10p	R2775=TIP41c	40p
ZE 1.5	10p	R2928=BU 208	60p
ZF 3.0	10p	R 2813	£1
ZF 3.3	10p	R3129=TIP47	40p
ZF 4.3	10p	R 3018	60p
ZF 10	10p	R 3019	60p
ZF 11	10p		
ZF 12	10p	BU 105	75p
ZF 15	10p	BU 105/04	80p
ZF 33	10p	BU 108	£1
ZF 43	10p	BU 124	50p
ZF 47	10p	BU 126	80p
ZF 82	10p	BU 137	50p
ZPD 3.9	10p	BU 180a	65p
ZPD 4.7	10p	BU 204	60p
ZPD 5.6	10p	BU 205	£1
ZPD 10	10p	BU 206	£1
ZPD 47	10p	BU 207	£1
ZPY 8v2	10p	BU 208	60p
ZPY 12	10p	BU 208a	£1
ZPY 16	10p	BU 222	£1
ZPY 24	10p	BU 326	£1
ZPY 43	10p	BU 407	60p
ZPY 47	10p	BU 426V	60p
ZPY 56	10p	BU 500	£1
ZTE 2	10p	BU 526	75p
ZTK 22	10p	BUX 84	50p
ZTK 33	10p	BUW 84	30p
ZTK 33a	10p	BUY 71	£1
ZTX 102c	10p		
ZTX 107	10p	TIC 106a	30p
ZTX 108c	10p	TIC 116d	30p
ZTX 109k	5p	TIC 116n	35p
ZTX 213	10p	TIC 126	40p
ZTX 341	10p	TIC 206m	30p
ZTX 342	10p	TIC 226m	30p
ZTX 384	10p	TIC 236m	30p
ZTX 450	10p	TICV 106D (T092 case 2A/400V)	10p
ZTX 451	10p		
ZTX 550	10p	TIP 29C/A	20p
ZW 13	12p	TIP 30	30p
ZW 27	10p	TIP 31A/B	40p
ZW 43	10p	TIP 32	25p
ZW 310	10p	TIP 33	50p
ZX 68	50p	TIP 34	50p
ZY 47	10p	TIP 35	50p
ZY 72	10p	TIP 36	50p
AA 112	10p	TIP 41	30p
AA 113	10p	TIP 41c	40p
AA 119	10p	TIP 42	40p
AA 143	10p	TIP 47	30p
AA 144	10p	TIP 49	30p
BA 102c	10p	TIP 100	30p
BA 157	8p	TIP 112	30p
BA 159	8p	TIP 117	30p
BA 173	8p	TIP 120	30p
BA 182	8p	TIP 125	35p
BA 201	8p	TIP 130	30p
BA 202	8p	TIP 131	30p
BQ 243	8p	TIP 136	30p
BA 248	8p	TIP 136	30p
BA 316	8p	TIP 640	£1
BAV 10	10p	TIP 2955	40p
BAV 21	10p		
BAW 21	10p	MJE 1300S	30p
BB 103	10p	MJE 2955C3	30p
BB 105A	10p	MV 2209	10p
BB 105B	10p	SP 8385	25p
BB 105G	10p		
BB 121a	10p		
BZX 46c22	15p		
BZX 61c10	6p		
BZX 61c15	6p		
BZX 61c20	6p		
BZX 61c220	10p		
BZX 70c33	8p		
BZX 79c4v7	8p		
BZX 79c5v6	8p		
BZX 79c6v2	8p		
BZX 79c6v8	8p		
BZX 79c8v2	8p		
BZX 79c12	8p		
BZX 79c22	8p		
BZX 79c30	8p		
BZX 79c43	8p		
BZX 79c47	8p		
BZX 83c4v3	10p		
BZX 83c5v6	10p		
BZX 83c8v2	10p		
BZX 83b12	10p		
BRC 83c13	10p		
BZX 83c20	10p		
BZX 83c27	10p		

**PHILIPS DIY HOME SECURITY ALARMS KITS**  
Send for details. Prices £54 to £112.

**MARDAVE MODEL RACING CARS**  
Nickel Cadmium Battery driven  
Please send for details

**Various Tools and Accessories**

Sellotape PVC Black		
25mm x 20M	50p	50mm x 20M 70p
Telescopic aerials (radio)		£1
Xcelite pliers		£3.90
Xcelite snips		£5
Xcelite cutters		£3.90
GKN Supascrew kits; 180 items in box with British made screwdriver.		Was £4.99. ONLY £2.50
VU meter		45p
Pull up large aerial		75p
Portable TV aerial		75p
Neon screwdriver		50p
Phillips snips		£2
2 way baby alarm/intercom with long leads		£5
Phillips universal battery tester/charger, fuse/bulb tester		£5
Volt/ohm test meters 1000 ohm/volt		£5
Eisenmann NICAD CHARGER 5.5V/150 ma		£2
2" x 1/2" microphone/speaker		50p
Continental 2 pin plug with 5ft mains lead (black & blue) 5 for		£1
7" Ferrite rod with LW/MW coils		50p
Front End Music Center. VHF/MW/LW 13" x 3 1/2"		£5
Output Stage for music center		£5
Both items		£9
circuit supplied (as previous ad)		
SONY 1400KV Chroma Panel		£6
SONY 1400KV Tuner unit		£3.50
SONY 1400KV Touch button unit		£3.50
4 books/Electronic Systems/First steps into TV/Guide to Printed Circuits + 1 other		£1.75
<b>Special Offer</b>		
<b>Quantity Reductions</b>		
BY204/4	25 for	£1.00
BY206	25 for	£1.00
BY210/600	25 for	£1.00
BY298 3 amp/fast/R	20 for	£1.50
BD239	20 for	£2.00
MR856	20 for	£1.50
BU126	10 for	£6.00
BU208	10 for	£5.00
BU204	20 for	£8.00
BU205	10 for	£8.00
BU105	10 for	£8.00
25C2122A	10 for	£8.00
BF458	10 for	£1.00
BD136	10 for	£1.25
BF224	20 for	£1.40
OA90	40 for	£1.00
IN4148	40 for	£1.00
IN4448	40 for	£1.00
BYX10	100 for	£4.00
50 High voltage ceramic condensers		£1.50
Mixed Mounting Kit for Power Transistors		50p
300 Condensers		£1.50
300 Resistors		£1.50
150 Electrolytics		£2.00
15 Bulbs		40p
100 Diodes		£1.50
100 Fuses		£2.00
100 W/W Res.		£1.50
20 Slider Knobs		70p
6 Mixed UHF Aerial Isolating Sockets, some with long leads		£1.00
<b>Mixed Packs</b>		
Pack of mixed coloured wire		£1.00
25 LED red/yellow/green		£1.50
201/C Holders		£1.20
20 Large LED Red		£1.00
20 Small LED Red		£1.00
10x20 Turn 100K Pots		£1.00
100 Mixed Transistor		£2.50
20 Convergence Pots		80p
100 Mixed Sticks		£1.00
10 Thermistors		50p
20 Slider Pots		£1.00
30 Presets		50p
40 Pots		£1.50
10 Gun Switches		50p
5 Tube Bases		£1.00
1,000 Diodes, Condensers, Resistors on Bandolier		£3.00
Lucky Dip 600 gram		£1.00

Panel VDP 12/80 D2N 720 Issue 3. Complete with All I.C.'s. Usually £100. ONLY £10.  
**VIEWDATE DECODER PANEL TEXAS**

**SENDZ COMPONENTS**  
63 Bishopsteignton,  
Shoeburyness, ESSEX SS3 8AF  
**SAME DAY SERVICE**  
All items subject to availability.  
**No Accounts : No Credit Cards**  
Postal Order/Cheque with order  
Add 15% VAT, then 50p P+P  
Add Postage for overseas  
**Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992**

# SENDZ COMPONENTS

D. Whitworth,  
63 Bishopsteignton, Shoeburyness,  
Essex SS3 8AF.

Telephone: 0702 332992  
ADD VAT 15%, 50p P&P.

Goods despatched on receipt of order.  
No Credit Cards Taken.  
Shop at 212 London Rd., Southend.

Mains in 110-120-220-240V A.C. 50Hz Adaptor. For black and white camera. Power consumption: 12V A. Output voltage: 14V D.C. Dimensions 150mm (w) x 80mm (h) x 120mm (d).  
Accessories: Mains lead and video/audio remote cable (2 metres)



Transducer Hand Set insert, crystal, transducer, 11C SAA 1124 & lead £3.50	CVC32 ITT £7.50	EHT Split Diode Leads £1.00
THORN 4000 ultra sonic hand set insert with 7 buttons (no case) £5	<b>Triplers</b>	
ECL2060 on panel. New £5	Y1 TEZ Rank £3.00	9000 Thorn £5.00
4.000 Thorn thick film. 00S1 012 E004 £1.00	KT3 £4.00	CVC-20-25-30 £4.00
00S1 012 E002 £1.00	G9 Philips £4.00	GEC 2110 £4.00
00S1 012 010B £1.00	2040 GEC £4.50	9500 Thorn £4.50
00S1 018D £1.00	2040 GEC £3.50	G8 Philips £4.50
Rank/Toshiba preh unit 0354 £9.50	LP1194 Pye 731 £3.50	Decca 80 100 £4.50
4 Push button unit preh £1.00	Grundig TVK 52 £2.50	LP1194 Pye 731 £3.50
6 Push button VHF/UHF for v.cap. GEC-Decca type £7.00	11TBO £3.00	11THY £4.00
7 Push button for CVC3 ITT £7.00	D22 for Pye 18" colour portable £4.00	LP 1193/63 £4.00
6 Push button unit for GEC 2040 and ELC 1043/05 £6.00	BG 100/41 £3.25	BG 100/61 £3.25
<b>Mains Droppers</b>	New Philips Infra Red Transmitter 9ch & Vol. & brightness change £7.00	
Pye 731 3+56+27R 50p	THORN Tuner Panel. 6 Slider pots, Knobs, touch button. Ultrasonic transducer, ICs, components & mains switch £3.75	GEC Portable Line Trans. £3.00
3500 Thorn 6/1/100 60p	Philips Infra-Red (full remote transmitter)	Philips KT3 16C928/20C934 £12
Thorn 50/17/1K5 £1.00	Philips KT3 7228/7324 K12 26C 797/1ST 66K 1826 £12	Transmitter Decca RC11 £14
120/20/20/48/117 £1.00	Transmitter Decca RC12 £14	G11 Tuner Units £6.00
270/10/6 for Thorn 4000 50p	G11 6 Button Key Switch £2.00	G11 E/W Transformer 50p
18/320/70/39 £1.10	G11 Line OSE Tran. 50p	G11 Line OSE Tran. 50p
Thorn 50-40R-1K5 50p	G11 Transient Suppressors 245V 10 for £1.00	G11 Scan Coils £5.00
Aerial Socket and Lead 35p	G11 AE Sockets 25p	KT3 AE Sockets 25p
Pye, Thorn, ITT, Thyristor, Philips G11 122 60p	4000 Thorn Frame Panel £5.00	4000 Thorn Power Supply £3.00
Rank Toshiba Tube Bases 30p	4000 Thorn Line OP Panel £20.00	NPN PNP 80V 6 Amp TO66 O.P. Trans. pair 25p
<b>Speakers</b>	GEC IC CBF16848. SN16861. SN1682 each 50p	Thorn 3500 IF Panel NEW £3.00
6x4G11 25 ohm £1.00	Thorn Tuner Panel 6-100K Pots & Components NEW No Tuner £2.00	6 button 100K pots + cursors on panel for varicap tuning £1.50
5x2 3 ohm £1.00	THORN 1600 mains lead: switch: 3 slider assy. £2.00	5 button touch tuner BBC1/2 ITV1/2 video with ic SAS 560T/570T £7.00
5x3 80 ohm 70p	Control panel 5 sliders + mains lead £1.50	Tube base + base unit for 820 Euro chassis £4.00
5x3 50 ohm 50p	CVC 9 IF panel and decoder £7.00	GEC Line O/P Trans. & Rec Stick for Portable £3.00
5x3 35 ohm 70p	GEC 20/25/30/35/40 decoder panel £10	CVC 20/25/30/35/40 decoder panel (untested) £5
5x3 15 ohm 80p	CVC 40/45 IF panel £5	Mains Panel with switch and lead £1.50
6x4 15 ohm £1.00	Mains Panel with switch and lead £1.50	Thorn 3500 6 push button unit & cable form £1.50
7x3 70 ohm £1.00	International Rectifier EHT Diodes G770/HV34 6KV 3 for 8p	EHT Rectifier wire ends 16Kv 10p
5x3 8 ohm 70p	6A/600V Stud Diodes 20p	25A473 PNP C/P 10p
7x3 16 ohm £1.00	6A/1000V Stud Diodes 20p	
8x5 8 ohm £1.00	SKE 1/02 20p	
2" dia 8 ohm 75p		
3" dia 8 ohm 75p		
<b>Diodes</b>		
BY 127 10p		
BY 133 10p		
BY 134 10p		
BY 164 30p		
BY 176 type 25p		
BY 179 40p		
BY 184 25p		
BY 187 10p		
BY 190 40p		
BY 194 30p		
BY 196 30p		
BY 198 10p		
BY 204/4 8p		
BY 206 8p		
BY 210/400 5p		
BY 210/600 5p		
BY 210/800 10p		
BY 223 50p		
BY 226 15p		
BY 227 15p		
BY 228 30p		
BY 229/400 30p		
BY 237 5p		
BY 254 10p		
BY 255 10p		
BY 296 10p		
BY 298 10p		
BY 299 10p		
BY 527 20p		
F 247 10p		
XK 3123 50p		
Thorn A1 10p		
<b>Line Transformers</b>		
G8 Trans. Philips £7.50		
G11 Split Diode £12.00		
CVC320 Split Diode ITT £10.00		
CVC40 Split Diode ITT £10.00		
GEC 2040 £5.00		
Pye mono £3.00		
Rank mono T704A £3.50		

<b>Rec &amp; Trans</b>	<b>Condensers</b>
G11 Ultrasonic t/text transmitter G26C 674/02 £19	1500/16 20p
G22 C66/02 £19	3300/16 20p
Infra Red (full remote transmitter) Dynatron TV CTV 62, 63, 64 £19	10000/16 20p
40K Transducer 50p	3300/18 20p
PHILIPS NE511N £1.20	470/25 5p
LM337M Reg. 30p	680/25 5p
Thorn T605 1V NPN TO66 80V 6A 10p	1250/25 10p
20 GEC Black Spark Gaps £1.00	1500/25 10p
G11 Line Driver Transmitter 35p	2200/25 10p
2 SD350A BU208A £1.00	3300/25 20p
G11 IF Detector £3.00	4700/25 25p
G11 Teletext Transmitter £19.00	5000/25 25p
BG200/43 Tripler £3.00	1500/30 20p
DECCA IF 80-100 £3.50	3300/30 30p
G11 Time Base Panel £12.00	1500/35 10p
AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670 £3.00	2200/35 25p
Thorn 900 Sound OP Panel NEW £1.00	220/40 5p
U321 T/Unit on Panel Cum 40 ITT £6.00	400/40 25p
Z714 RANK IF Panels 6MHz 1 I.C. SL437F £3.00	680/40 5p
Z909B RANK IF Panels Export 5.5MHz 2 I.C.'s TBA1205B TCA2705Q £2.50	1250/40 20p
Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s TBA750+SC9504P+SC9503P £1.50	2000/40 25p
Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF £2.50	2500/40 25p
G11 dynamic correction panel £6	3300/40 25p
CVC 20 Front panel with sliders + mains input panel £4	6800/40 35p
THORN 3500 Tuner panel (ELC 1043/05 + pots) £7	750/50 10p
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots £14	1000/50 20p
CVC 5 Mains on/off + 5 pots £2	1250/50 25p
GEC Convergence panel (We have 1000's) to clear £1	2000/50 20p
	3000/50 25p
	15/63 5p
	47/63 10p
	2200/63 50p
	250/64 10p
	4.7M/100 5p
	140/100 20p
	470/100 25p
	800/160 50p
	G11 0.91/210 scan coil correction .1/250 25p
	G11 0.47/250 5p
	2.2 250v 10p
	4n7/250 tested 5KV 25p
	22/250 15p
	47/250 10p
	100/250 20p
	500/250 50p
	GEC600/250 60p
	800/250 40p
	8/300 8p
	4/350 5p
	8/350 8p
	12/300 10p
	4.7M/350v 10p
	16/350 25p
<b>Multi-Caps</b>	
Thorn 3500	
175/100/100/350v £2.00	
KT3/200/25/25/385v £1.00	
47/220/350v 60p	
150/150/100/100/100/320v £2.00	
2500/2500/63v 50p	
470/470/250v 50p	
150/200/200/300v 70p	
100/200/325v 40p	
400/200/200/350v £1.50	
200/200/100/300v 60p	
200/350v + 300/100/32/300v £2.00	
200/200/100/32/350v £1.50	
200/47/350v 60p	
100/300/200/100/16/350v £2.00	
200/100/100/375v £2.00	
1000/1000/35v 60p	
150/150/100/100/325v £2.00	
100/350 + 300/200/100/16/275v £2.00	
<b>ITT Panels</b>	
CMA 10 £2.00	
CMA 11 £2.00	
CMA 30 £2.00	
CMA 40 £1.50	
CMC 10/2 £5.00	
CMC 15 £10.00	
CMC 16 £4.00	
CMC 19 £12.00	
CMC 45 £1.50	
CMC 47 £1.00	
CMC 54 £10.00	
CMC 56 £5.00	
CMC 58 £8.00	
CMC 59 £8.00	
CMC 67 £3.75	
CMC 67/2 £4.00	
CMC 68 £4.00	
CMD 12 £10	
CMD 40 £5.00	
CMF 25 £2.00	
CMF 40 £2.00	
CMH 10 £1.50	
CMH 31 £1.50	
CMK 12 (untested) £4.00	
CMN 20 £1.50	
CMN 40 £1.00	
CMP 10 £2.00	
CMP 11 £2.00	
CMP 40 £2.00	
CMS 11 £2.00	
CMS 40 £2.00	
CMU 14 £8.00	
CMU 30 £7.00	
CMU 40 £7.00	
CMU 45 £5.00	
VMC 34 £5.00	
VMC 44 + 45 £4.00	

Tuner Units	
ELC1043/05 Mullard	£6.00
ELC1043 (Ex Panel)	£3.75
ELC1042	£5.00
ELC2000	£7.00
EL2060	£7.00
ELC2060 on panel	
NEW	£5.00
U321 (UHF) Mullard	£6.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
ELC1043/05 Thorn	£5.00

Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00

VHF Rotary Mitsumi	£1.00
--------------------	-------

Portable & rotary Tuners	
Sanyo & Mitsumi UHF	£5.00

Mossfit UHF VHF NSF.	
ET021 DX	£8.00

Sylvania UHF VHF F6013 (Fits Rank)	£4.50
------------------------------------	-------

Sylvania UHF	£3.00
Sylvania VHF	£3.00

Decca Bradford Tuner 5 Button	£4.00
-------------------------------	-------

NSF AEG UHF/VHF	£6.00
-----------------	-------

Small Tuner DX 175-220MHz Auto Changeover	£5.00
---	-------

9000 Thorn Tuner on Panel	£7.00
---------------------------	-------

D.P.D.T. switch Black knob: Chassis or PCB mount	4p
each or 40 for	£1.00

THORN 1400 4P.B. Mechanical Tuner	
THORN 1500 4P.B. Mechanical Tuner	
THORN 3500 4P.B. Mechanical Tuner	
THORN 8000 4P.B. Mechanical Tuner	
THORN 8500 4P.B. Mechanical Tuner	
All new & boxed	£4 each + £1 postage each

Tyne T/V I.C. SN76545N	£3.50
------------------------	-------

VHF 3 Transistor Rotary Tuner Units D.X. TV. NEW	£1.00
--	-------

BFT43	10p	2SC1030	£1.00	BC160	25p
BFT84	8p	2SC1173	£1.00	BC171	10p
BFY11	20p	2SC1617	£1.00	BC172	10p
BFX29	30p	2SC2073	8p	BC173	10p
BFX84	25p	2SC2122A	£1.00	BC174	10p
BFY50	15p	2SC2229	15p	BC182L	10p
BFY90	25p	2SD180 TO3 80v/		BC183	10p
BRX43	15p	6A	15p	BC184	10p
BSY95a	10p	2SD200	£2.00	BC187	10p
BTY80	20p	2SD350A	£1.00	BC204	10p
BSX19	17p	2SK30A	10p	BC207	10p
BSX20	17p	2SN30A	8p	BC212	10p
2N930	5p	FT3055	30p	BC213	10p
2N2221	8p	BC107	10p	BC214	10p
2N2222	8p	BC108	10p	BC237	10p
2N3055	40p	BC109/2N930	5p	BC238	8p
2N3094	15p	BC113	10p	BC239	8p
2N3096	15p	BC114	10p	BC245	8p
2N3703	10p	BC115	10p	BC250	10p
2N3711	10p	BC116	10p	BC251	10p
2N3583	50p	BC125	10p	BC252	10p
2N4355	10p	BC139	10p	BC257	10p
2N4442	£1.00	BC141	25p	BC262	10p
2N4444	£1.00	BC142	25p	BC298	10p
2N5296	40p	BC143	25p	BC300	30p
2N5983	30p	BC147	10p	BC301	30p
2N6099	40p	BC148	10p	BC303	30p
2N6348	20p	BC149	10p	BC307	7p
Z5B-407 Sanyo		BC153	10p	BC308	10p
TO3	10p	BC154	10p	BC309	10p
2SB474	30p	BC157a	10p	BC327	10p
2SB566	10p	BC158	10p	BC328	10p
2SC753	10p	BC159	10p	BC337	10p

## SENDZ COMPONENTS

**D. Whitworth,**  
63 Bishopsteigton, Shoeburyness,  
Essex SS3 8AF.  
Telephone: 0702 332992  
ADD VAT 15%, 50p P&P.  
Goods despatched on receipt of order.  
Callers By Appointment.  
No Credit Cards Taken.

Diodes	
1 Amp 1600v	7p
3 Amp 100v	7p
3 Amp 1200v	10p
9000 Thorn O/P Transistors with Heatsink T903 8v	£1.00
7 Seg Display, Led Red	50p
TA7607	£1.00
TA7609	£1.00
TA7315	£1.00

Delay Lines	
TAU80	£1.00
DL11	50p
DL20A	80p
DL50	£1.00
DL70	£1.00
DL600	£1.00
DL700	£1.00
Luminance Delay Line MDL-CBL Min.	50p
3.15 Fuses	4p

Co-Ax Joint	
Co-Ax Belling Lee Plug	12p
UHF Modulator CCIR	£3.00
Infra Red Emitting Diode	20p
NE286H Small Neon Lamps	
GEC	5p
Mullard 5 Watt Amps. LP1162 New	75p

Tube A31/510	
A31/300	£5.00
12" Tube Hitachi	£12.00
15" Tube Hitachi	£8.00

T.V. Tubes	
A31/510	£5
12" A31/300 Hitachi	£12
15" A38/170W Hitachi	£8
Add £2 P&P each	

Integrated Circuits	
AM25LS23PC	£1.00
BAV40	40p
BRC-M-200	50p
BRC-M-300	60p
BRC 1330	75p
CA270CE	50p
CA270CW	50p
CA3065	50p
CA3089Q	50p
CA3094AE	50p
CA920AE	£1.00

TBA231	75p
TBA395	50p
TBA396	75p
TBA440	£1.00
TBA440C	£1.00
TBA480Q	£1.00
TBA510	£1.00
TBA520	£1.00
TBA530	£1.00
TBA540	£1.00
TBA540Q	£1.00
TBA550Q	£1.00
TBA560CQ	£1.00
TBA560C	£1.00
TBA570	£1.00
TBA641BX1	£2.00
TBA673	£1.00
TBA720A	£1.00
TBA750Q	£1.00
TBA800	40p
TBA810S	70p
TBA820	70p
TBA890	£1.00
TBA920	£1.00
TBA920Q	£1.00
TBA950	£1.00
TBA990Q	£1.00
TMS1943NL	£2.00
SN29848	50p
SN7472N	20p
SN75108AN	£1.00
SN76001	£1.00
SN76003	£1.00
SN76018	£1.00
SN76008	£1.00
SN76023N	£1.50
SN76033	£1.50
SN76115	50p
SN76131	50p
SN76226	£1.00
SN76227	60p
SN76228N	£1.00
SN76530P	60p
SN76532N	50p
SN76533	£1.00
SN76544N	£2.00
SN76546	£1.00
SN76552	£1.00
SN76650	50p
SN76660	40p
SN76620AN	50p
SN76666	50p
SN76707N	75p
SN76708N	75p
ML232R	£1.20
BTJ6016	£1.20
ML236E	£1.50
ML237B	£1.50
ML238B	£3.50
BTT822	£1.00
BIT6018	£1.50
ML237B	£1.50
ML231	£2.00
BTT8124	£1.00
BTT8224	£1.00
TDA2522	£1.00
UA783P3C	40p
UPC1365C	£1.50

KT3 2SD 200 Line Transistor	£2.00
BT100A	30p
BT106	£1.00
BT106 Plastic	50p
BT119	£1.00
BT120	£1.00
BT109	£1.00

Semiconductors	
BT100A	30p
BT106	£1.00
BT106 Plastic	50p
BT119	£1.00
BT120	£1.00
BT109	£1.00

BD116	25p
BD124	50p
BD124 (metal)	£1.20
BD130Y	25p
BD131	30p
BD132	30p
BD135	30p
BD136	30p
BD140	30p
BD176	25p
BD202	60p
BD207	60p
BD221	20p
BD222	30p
BD226	20p
BD233	30p
BD235	30p
BD238	30p
BD239	15p
BD243a	15p
BD250a	30p
BD252B	30p
BD253B	50p
BD231	20p
BD332	20p
BD416	25p
BD433	25p
BD437	25p

BT138/10A	70p
TCA270	£1.00
TCA270Q	£1.00
TCA940	£1.00
TCA4500A	£1.00
TCA640	£1.00
TCA650	£1.00
TCA660	£1.00
TCA270S	£1.00
TCA270SQ	£1.00
TCA740	£1.00
TCA800	£1.00
TCA830	£1.00
TCEP100	£2.25
TDA440Q	£1.00
TDA1003A	£1.00
TDA1010	£1.00
TDA1170	£1.00
TDA1190	£1.00
TDA1327A	£1.00
TDA1412	30p
TDA2010	£1.00
TDA2140	£3.50
TDA2530	£1.00
TDA2532	£1.00
TDA2540	80p
TDA2541	£1.00
TDA2575A	£1.00
TDA2590	£1.00
TDA2593	£1.00
TDA2560	50p
TDA2600	£3.75
TDA2653	£1.00
TDA2002	£1.00
TDA2640	80p
TDA2680	£1.00
TDA2690	£1.00
TDA2593	£1.00
TDA3190	£1.00
TDA3500	£2.00
TDA3560	£3.50
TDA3571Q	£1.50
TDA3950	£1.50
SN74LS 125AN	30p
SN16862AN	£1.00
SN16964AN	50p
SN29764	£1.00
SN297728N	50p
RGP30G	10p
MPSA43	10p
BTY80	20p
BLY49	20p
E1222	20p
MJE511	25p
MJE340	28p
MJE2801	30p
MJE2955	50p

Sanikron Diode	
SKE262/04	30p
SN6550/3R	£1.00

Transistors	
AC121	20p
AC128	20p
AC151	20p
AC131	20p
AC152	30p
AC153K	20p
AC142K	20p
AC176	20p
AC176K	20p
AC187K	20p
AC188	20p
AC188K	26p
ACY21	25p
AD143	50p
AD149	50p
AD161/162	pair 40p
AF139	25p
AF239	25p
AF367	25p
AU113	£1.20

BF468	30p
BF469	30p
BF470	30p
BF480	50p
BF594	10p
BF597	10p
BF694	10p
BF757	30p
BF758	30p
BF761	30p
BF781	30p
BF787	15p
BF791	15p
BF794	10p
BF799	15p
BF823	15p
BF848	30p
BF450	20p
BF457	10p
BF458	30p
BF459	30p
BF468	30p
BF469	30p
BF470	30p
BF480	50p
BF594	10p
BF597	10p
BF694	10p
BF757	30p
BF758	30p
BF761	30p
BF781	30p
BF787	15p
BF791	15p
BF794	10p
BF799	15p
BF823	15p
BF848	30p
BF450	20p
BF457	10p
BF458	30p
BF459	30p

Filters	
5-5MHz	15p
6MHz	25p
BFU455K	5p

Thyristors	
BT119	£1.00
BT120	£1.00
BRC4443	75p
G11 Thyristor	60p
Decca 80-100	60p
G11 Teletext Decoder	
Panel Philips	£30.00

Thermistors	
VA1104	35p
ITTPT266312	15p
PTH451 AOR	15p
PT37P Fits Pye & Bush	25p
PT34	20p
Degaussing Thermistor (fits most sets)	20p
3 Pin Blue Thermistor (fits most sets)	20p
BLY49	50p