

JUNE 1983

Australia \$1.80; New Zealand \$2.10; Malaysia S5.50 (R; £1.15 6p VAT)

90p

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS



IN SITU TRANSISTOR TESTER

TV RENTAL • VCR CLINIC

**Servicing Features :
THORN 9600 CHASSIS
& TOSHIBA MODEL C800B**

SAVE ON THE PRICE OF YOUR COLOUR PRINTS!

NOW ONLY 12p EACH

with the Television Colour Print Service

While prices go up elsewhere, Television makes a bargain offer in its Colour Print Service. Now you can have as many films printed as you like, including Giant Superprints, at only 12p a print. There is no developing charge and just 25p towards postage and packing.

At this new price, the magazine Colour Print Service, already used by hundreds of thousands of readers, is as fast and efficient as ever. Here's all you have to do to enjoy its advantages.

Send any make of colour print film, including disc film, inside the envelope enclosed with this issue. Or fill in the coupon below and send with your colour print film in a strong envelope to:

Television Colour Print Service, FREEPOST, READING RG1 1BR. No stamp is required.

SEND NO MONEY

We are so confident in the reliability of our service and the quality of our prints (each one date-stamped with the month and year of developing) that you don't pay until you've seen them. **LUXURY COLOUR PRINTS**

You will be amazed at the beautiful colours and sheen finish of these prints. They have elegant rounded corners and are borderless to give you maximum picture area. And with the Giant Superprints, you get 30 per cent more picture area than the standard enprints *at no extra cost!*

Offer excludes Black & White, transparency, sub-miniature, C22 & Agfa CNS film. Superprints can only be produced from Kodacolor II, C41 cassette, cartridge and disc film not half frame. Prices correct at time of going to press.

UNBEATABLE VALUE

All you pay for the Colour Print Service is 12p for each good print received plus 25p towards postage and packing. The most you would pay us for processing and printing a 24-exposure film for example is £3.13. Compare that with the price you would pay in the shops.

FREE ALBUM PAGES

With each film we process, you receive an album page voucher. Collect and return three vouchers, and you receive a set of FREE album pages to fit into our specially designed album for any size of print up to 4in. by 6in.

HOW YOU BENEFIT

You benefit in three ways. Firstly, you pay nothing for the actual processing—only for prints and postage and packing. Secondly, you enjoy a personal service with every care taken over each individual order. And thirdly, you pay only for what you get—with no credit vouchers as with many other companies. An invoice comes with your prints, so it is a straight business transaction.

48 HOURS IN-LAB SERVICE

Your films will be processed within 48 hours* of receipt, but please allow for postal delays.


The price of this offer is limited to the U.K.

*C41 Process cassette and cartridge film only.



FILMS AT REDUCED PRICES

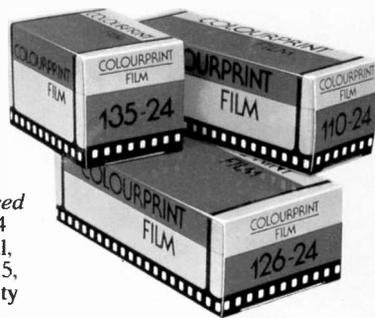Always keep your camera action-ready. Order replacement films at our specially reduced prices: 110/24, 126/24 or 35/24 at £1.20 a roll, or three for £3; disc/15, £1.30 each (no quantity discount).



If you have any queries, contact our Customer Service on Reading (0734) 597332.

Use this label if you have no envelope, or pass it to a friend. It is used to pack your prints.

To: Television Colour Print Service
FREEPOST, Reading RG1 1BR

- Please print my film Superprint size
Standard Enprint size

If film is being ordered ● Please send me _____
of 110/24 of 126/24 of 35/24 of disc/15

- Tick box(es) as required.

From: Television Colour Print Service
FREEPOST, READING RG1 1BR

Mr/Ms _____

Address _____

Postcode _____

TELEVISION

June
1983

Vol. 33, No. 8
Issue 392

COPYRIGHT

©IPC Magazines Limited, 1983, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 85p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope.

Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month


- 401 **Leader**
- 402 **Letters**
- 404 **Teletopics**
News, comment and developments.
- 408 **Routine TV Receiver Tests** *by S. Simon*
Most of the faults experienced with the Thorn 9600 chassis are fairly predictable and easy to trace. In the event of a more tricky situation, diagnostic sockets are included to provide clues.
- 410 **In-circuit Transistor Tester** *by Alan Willcox*
Transistors, diodes, thyristors and diode/thyristor combinations can all be tested by this unit, which has good immunity to the in-circuit conditions, is quick and simple to use, and can be built cheaply. Flashing neons indicate the condition of a device.
- 412 **TV Rentals** *by Tony Thomson*
Running a small rental business presents various problems but can nevertheless increase the services you are able to offer and thus your income. Guidance on the legal, technical and practical aspects, based on personal experience.
- 414 **B and O Tripler Conversion** *by Keith Cummins*
It seemed possible that the 2600 would be a write-off when the e.h.t. transformer failed. As the set's performance is so good however the possibility of using a tripler was investigated. The result is a simple and cheap answer to the problem, with the set's original performance maintained.
- 416 **VCR Clinic**
Reports on VCR faults and servicing.
- 418 **Long-distance Television** *by Roger Bunney*
Reports on DX reception and conditions and news from abroad.
- 420 **TV Fault Report**
Notes on TV receiver faults from Mick Dutton and Richard Roscoe.
- 422 **VCR Servicing, Part 18** *by Mike Phelan*
The Ferguson 3V23 uses dual servo systems, with both speed and phase control. This time the drum servo and the method of controlling the direct-drive motor.
- 426 **Servicing the Toshiba C800B** *by John Coombes*
This 18in. colour set uses straightforward circuitry but nevertheless has one or two features that can cause confusion. Most faults are due to soldering problems between the tracks on both sides of the boards.
- 427 **Next Month in Television**
- 428 **Frequency Counter-Timer, Part 3** *by Tony Jenkins, G8TBF*
Final construction of the basic unit and setting-up instructions.
- 429 **Lords of the Morning Air** *by Les Lawry-Johns*
Mr. Piddlewell, Mr. Lord and Mr. Knight all present problems of one sort or another.
- 431 **Service Bureau**
- 432 **Test Case 246**

OUR NEXT ISSUE DATED JULY WILL
BE PUBLISHED ON JUNE 22

MANOR SUPPLIES

NEW MKV CHEQUERBOARD & PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE

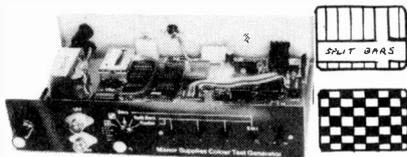

- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£80.50**

Standard Case (10½"×6½"×2½") **£5.50**

De Luxe Case (10"×6"×2½") **£8.50**

Optional Sound Module (6MHz or 5.5MHz) **£4.50**


Built & Tested in De Luxe Case including Sound Module **£120.75**

SPECIAL TEST REPORT TELEVISION DEC. 1982

Post/Packing **£2.50**

All above prices include VAT 15%

PAL COLOUR BAR GENERATOR (Mk4)

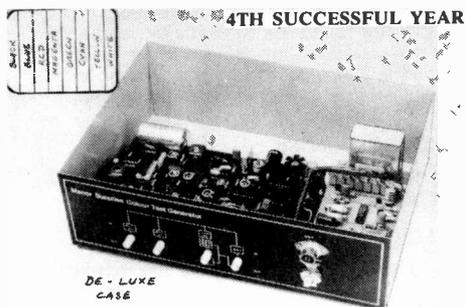

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT £34.50. DELUXE CASE £8.50. BATT HOLDERS £3.20 OR MAINS SUPPLY KIT £4.80 (Combined P&P £1.80).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£66.70 + £1.80 P & P.**
 MK 4 DE LUXE (MAINS) BUILT & TESTED **£80.50 + £1.80 P & P.**
 VHF MODULATOR (CHI to 4) FOR OVERSEAS **£6.60.**

EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.
 (ALL PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT ADAPTOR KITS

MK 1 (Texas XMII) Cable remote control **£170.20** p.p. **£2.80.**
 MK 2 (Philips/Mullard) Infra-red remote control **£227.70** p.p. **£2.80.**

Further details on request.

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS

NEW COLOUR PORTABLE TV
 TV PATTERN GENERATOR SMALL SCREEN MONITOR
 MONO PORTABLE TV LARGE SCREEN COLOUR TV
 PHONE, CALL, OR SEND FOR LISTS
 WORKING MODELS & PANEL TEST SERVICE AT
172 WEST END LANE

SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND tested for T.V. SOUND & VISION **£32.80** p.p. **£1.20** (SUITABLE FOR USE WITH TELEVISION SIGNAL BOARDS).

TV SOUND IF PANELS, FULLY TESTED **£7.82** p.p. **£1.00.**
 SPECIAL OFFER TEXAS XMII TELETEXT MODULE NEW & TESTED, AT REDUCED PRICE **£57.50** p.p. **£1.60.**

PHILIPS-PYE G11 TYPE TELETEXT DECODERS **£34.50** p.p. **£1.60.**
 TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE **£7.80** p.p. **£1.20.** XMII STAB. POWER SUPPLY **£4.40** p.p. **£1.20.**

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET **£12.65** p.p. **60p.** (ALUM CASE **£2.60** DE LUXE CASE **£5.50** p.p. **£1.20.**)
 ADDITIONAL GREY SCALE KIT **£3.35** p.p. **45p.**
 UHF SIGNAL STRENGTH METER KIT **£21.60** (VHF version also available). ALUM CASE **£2.60** DE LUXE CASE **£8.50** p.p. **£1.80.**

CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO **£29.40** p.p. **£2.00.**
 BUSH A823 POWER **£1.00** BASIC PCB. IN FIBREGLASS **£6.40** p.p.
 BUSH Z718 BC6100 SERIES IF PANEL **£5.75** p.p. **90p.**
 BUSH A816 IF PANEL (SURPLUS) **£1.90** p.p. **90p.**

DECCA "Bradford" T.B. POWER ex rental **£5.75** each p.p. **£1.40.**
 DECCA 80, SERIES, IF FRAME T.B. **£5.75** each p.p. **£1.40.**
 DECCA 80, 100 LINE T.B. salvaged **£11.50** each p.p. **£2.00.**

GEC 2100 Decoder, RGB panels (ex rental) **£5.75** each p.p. **£1.00.**
 GEC 2040 Convergence panels **£2.88** p.p. **£1.80.**
 GEC 2040 DECODER PANEL **£2.88** p.p. **£1.60.**

THORN TX9 PANELS ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.75** p.p. **£2.00.**
 THORN TX9 PANELS salvaged ex factory for spares incl. LOPT & mains transformers **£11.50** p.p. **£2.80.**

THORN TX10 T.B. PANELS salvaged ex factory **£17.25** p.p. **£3.00.**

THORN 3000 LINE T.B., POWER PCB **£5.75** each p.p. **£1.30.**
 THORN 8000/8500 IF/DECODER PANELS salvaged **£3.70** p.p. **£1.80.**
 THORN 8000/8500 FRAME T.B. PANELS salvaged/spares **£2.88** p.p. **£1.40.**

THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET **£19.32** p.p. **£1.84.**
 THORN 9000 IF/DECODER PANELS Salvaged **£5.75** p.p. **£1.60.**

PHILIPS 210, 300 Series Frame T.B. Panels **£1.15** p.p. **80p.**
 PHILIPS G8/G9 IF/DECODER Panels for small spares **£1.75** p.p. **£1.40.**
 G8 IF PANELS for small spares **£1.15** p.p. **95p.**
 G8 Decoder panels salvaged **£4.25.** Panels for spares **£2.00** p.p. **£1.40.**

G9 Scan Panel. Basic PCB in fibreglass **£16.68** p.p. **£1.80.**
 VARICAP, U321, U322, ELC 1043/06 ELC 1043/05 **£7.82** p.p. **80p.** G.I. type (equiv. 1043/05) **£4.00** p.p. **60p.** MAKERS VARICAP CONTROLS Pye CT200 4PSN **£8.60.** A823 4PSN **£5.50.** Decca 6PSN **£6.70** p.p. **80p.**

SPECIAL OFFER ELEVEN POSITION VARICAP CONTROL UNIT UHF/VHF **£2.10** p.p. **£1.00.**
 BUSH "Touch Tune" Varicap Control Z179, Z718 types **£4.40** p.p. **95p.**
 VARICAP UHF-VHF ELC 2000S **£9.80.** BUSH TYPE **£7.82** p.p. **85p.**
 VARICAP VHF MULLARD ELC 1042 **£7.95** p.p. **80p.**

UHF/625 Tuners, many different types in stock. DECCA Bradford 5 position **£2.88** p.p. **£1.80** etc.

LOPTS NEW & GUAR. P/P Mono **£1.35p.** Colour **£1.45p.** Bobbins **80p.**

BUSH 161 to 186 (twin panel) **£6.80** R.B.M. A823 **£5.60**
 BUSH, MURPHY 774 series **£9.80** R.B.M. Z179 **£11.30**
 BUSH, MURPHY A816 series **£9.80** R.B.M. T20, T22 **£11.30**
 FERG., HMV, MARCONI, ULTRA R.B.M. T20, T22 Bobbin **£6.44**

950, 1400, 1500, 1580, 1590, 1591 **£6.80** DECCA Bradford (state Mod No.) **£10.15**
 THORN 1600, 1615, 1690, 1691 **£10.50** DECCA 80, 100 **£10.15**
 GEC 2000 to 2038 series **£7.80** GEC 2040 **£6.70**
 GEC series 1 & 2 **£9.20** GEC 2110 Series **£12.20**

INDESIT 20/24EGB **£8.80** ITT CVC 5 to 9 **£11.30**
 ITT/KB VC 200, 300 **£8.80** ITT CVC 20 **£11.30**
 MURPHY 1910 to 2414 series **£6.86** ITT CVC25, CVC30 series **£10.15**
 PHILIPS 19TG 170, 210, 300 **£8.80** PYE 691-697 **£11.50**

PYE, INVICTA, EKCO, FERR. PYE 713, 715, 731 to 741 **£7.85**
 368, 169, 569, 769 series **£8.80** PYE 725 (90°) **£10.60**
 SPECIAL OFFER PHILIPS G8, G9 **£10.15**

DECCA 20/24, 1700, 2000, 2401 **£4.40** PHILIPS 570 **£7.85**
 GEC 2114J/Junior Fineline **£3.25** THORN 3000/3500 SCAN, EHT **£7.85**
 PYE 40, 67 **£2.00** THORN 8000/8500/8800 **£14.80**
 KB VC ELEVEN (003) **£2.00** THORN 9000 to 9600 **£10.15**
 KB VCI **£3.25** THORN 9800 **£21.90**

OTHERS AVAILABLE. PRICES ON REQUEST. ALSO F.OPTS. TRIPLERS Full range available. Mono & Colour.

Special Offer: Thorn 1400 5 stick EHT Tray **£1.72** p.p. **65p.**
 TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.72** p.p. **60p.**
 6-3V CRT Boost Transformers **£5.80.** Auto Type **£3.20.** p.p. **£1.20.**

CALLERS WELCOME AT SHOP PREMISES Telephone 01-794 8751/7346
 THOUSANDS OF ADDITIONAL ITEMS AVAILABLE, ENQUIRIES INVITED

LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Sta. (Jubilee) Buses 28, 159, C11 pass door
 W. Hampstead British Rail Stns. (Richmond, Broad St) (St Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: **64 GOLDERS MANOR DRIVE, LONDON N.W.11.**

ALL PRICES INCLUDE VAT AT 15%
 CLOSED FOR HOLIDAYS JUNE 6th to 18th

BI-PAK BARGAINS



5121 SCREWDRIVER SET
6 precision screwdrivers in hinged plastic case. Sizes - 0.8, 1.4, 2.2, 4.2, 9 and 3.8mm. **£1.75**

5131 NUT DRIVER SET
5 precision nut drivers in hinged plastic case. With turning rod. Sizes - 3, 3.5, 4, 4.5 and 5mm. **£1.75**

5141 TOOL SET
5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers - H 0 and H 1 Hex key wrenches - 1.5, 2 and 2.5mm. **£1.75**

5151 WRENCH SET
5 precision wrenches in hinged plastic case. Sizes - 4, 4.5, 5, 5.5 and 6mm. **£1.75**

BUY ALL FOUR SETS 5121-5151 and get HEX KEY SET FREE
HEX KEY SET ON RING
Sizes 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm
Made of hardened steel
HX/1 **£1.25**



SX52
6 Black Heatsink will fit TO-3 and TO-220. Ready drilled. Half price value. **£1**

SX53
1 Power finned Heatsink. This heatsink gives the greatest possible heat dissipation in the smallest space owing to its unique staggered fin design, pre drilled. TO-3 Size 45mm square x 20mm high. 40p

SX54
TO-66 size 35mm x 30mm x 12mm. 35p
SX55
1 Heat Efficiency Lower Finned Heatsink. 90mm x 80mm x 30mm High. Drilled to take up to 4 x TO-3 devices. **£1.50 each**



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm-2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.

*Quantities approximate, count by weight

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180-240, Inline 3-6 Pin, Speakers, Phono, Jack, Stereo and Mono etc. Valued at well over £3 normally. Order No. SX25.

Our Price **1.50** per pak. Guaranteed to save you money.
SX30A 3 Pcs of 6 pin 240 DIN Plugs and Chassis Sockets **50p**
SX27A 60 Assorted Polystyrene Bead Capacitors Type 9500 Series FPD **£1.00**
SX28A 50 Assorted Silver Mica Caps 5.6pF-150pF **£1.00**
SX29A 50 Assorted Silver Mica Caps 100pF-4700pF **£1.00**
SX30A 50 High Voltage Disc Ceramics 750v min up to 8KV. Assortec useful values **£1.00**
SX31A 50 Wirewound 9 watt (avg) Resistors. Assorted values 10hm 12K **£1.00**

SINGLE SIDED FIBREGLASS BOARD

Order No.	Pieces	Size	Sq. Ins.	Price
FB1	4	9 x 2 1/2"	100	£1.50
FB2	3	11 x 3"	100	£1.50
FB3	4	13 x 3"	156	£2.00

DOUBLE SIDED FIBREGLASS BOARD

FB4	2	14 x 4"	110	£2.00
-----	---	---------	-----	-------

SILICON POWER TRANSISTORS - T03
NPN like 2N3055 - but not full spec 100 watts 50V min. 10 for £1.50 - Very Good Value 100s of uses - no duds Order No. SX90

SOUND with SINCLAIR

MAKE AMAZING SOUND EFFECTS WITH YOUR ZX 81, TIMEX Sinclair 1000 or SPECTRUM

THE ZON X 81

£25.95

incl p&p & VAT.



- The ZON SOUND UNIT is completely self-contained and especially designed for use with the ZX 81, TIMEX Sinclair 1000 and Spectrum Computers. It just plugs in - no dismantling or soldering.
- No power pack, batteries, leads or other extras.*
- Manual Volume Control on panel - ample volume from built-in loud-speaker.
- Standard Sinclair - 16K Rampack or printer can be plugged into ZON X Sound Unit without affecting normal computer operation.
- Huge range of possible sounds for Games, Music, Helicopters, Sci-Fi, Space Invaders, Explosions, Gun-shots, Drums, Planes, Lasers, Organs, Bells, Tunes, Chords, etc., or whatever you devise!
- 8 full octaves. Uses 3-Channel sound chip giving programme control of pitch, volume of tones and noise all with envelope control.
- Easily added to existing games or programmes using a few simple "BASIC" lines or machine code.
- No memory addresses used - 10 mapped.

FULL instructions with many examples of how to obtain effects and the programmes, supplied. Fully guaranteed. British Made.
*Except with Spectrum, you need the Spectrum Extension Board Order No. SE1 - PRICE £6.80 inc. VAT.
Payment may be made by Cheque, P.O. Giro No. 388 7006. Postal Order or Credit Card.
Export orders:- Bank Cheque, International Money Order, U.S. \$ or £ Sterling.

Time is Money!

We can save you both

BI-PAK'S REVOLUTIONARY DYNAMIC "LOPT" TESTER immediately tells the condition of a suspect LOPT without desoldering or removal. Guaranteed correct analysis in seconds saving you £££'s in Service Engineers TIME!



- ★ Invaluable to all TV Engineers and unlike anything before.
- ★ Small, compact, mains operated size 10 x 7.5 x 4cms.
- ★ The D.T.T. is inductively coupled by two loose turns of the test lead around the yoke or over the overwind on the suspect line output transformer (as illustrated).
- ★ The DYNAMIC TESTER will give a positive rapid test by giving E.H.T. at the overwind if the transformer is sound. If it is faulty then no E.H.T. will be

- given off and the transformer can be easily disconnected and replaced with confidence in only minutes.
- ★ Designed by a T.V. Engineer and is wholly British Made. Comes complete with instructions. Fully guaranteed.
- ★ 10-day satisfaction money-back guarantee BI-PAK will refund your cash in full should you not be completely satisfied and return the unit within 10 days of purchase.

IMMEDIATE DESPATCH - Ring Cardholder Hotline 3182 for same day despatch or send cash, cheque, P.O.'s etc. to:

PRICE **£36 each** + V.A.T.

JUST OUT

OUR NEW 1983 CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

We hold vast Stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock.



The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

ORDER YOUR COPY NOW ONLY 75p P + P 25p

BI-PAK


Send your orders to Dept T.6. BI-PAK PO BOX 6 WARE HERTS SHOP AT 3 BALDOCK ST WARE HERTS
TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS, BARCLAYCARD ALSO ACCEPTED. TEL (0920) 3182. GIRO 388 7006 ADD 15% VAT AND 75p PER ORDER POSTAGE AND PACKING



Use your credit card Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your order. Total Postage add 75p per total order.

P. V. TUBES

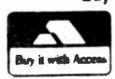Just phone your order through, we do the rest.



Telephone: Accrington (0254) 36521
Accrington (0254) 32611

WHOLESALE SUPPLIERS OF TELEVISION COMPONENTS

38A WATER STREET, ACCRINGTON, LANCS BB5 6PX.

TRADE COUNTER OPEN MON-FRI 9 a.m.-4.30 p.m. SAT MORN. 9.30 a.m.-12 noon.

INTEGRATED CIRCUITS		TA7193P		TBA673		TDA2530		T.T.L. 74LS SERIES	
AN240	3.84	MS1513L	2.80	TA7204P	5.67	TDA2532	2.70	74LS00	19
AN2140	3.91	MS1515L	3.28	TA7205AP	3.77	TDA2524	2.45	74LS02	19
AN7150	3.97	SAS560S	1.80	TA7222	3.72	TBA720Q	2.12	74LS03	20
CA555	46	SAS570S	1.80	TA7310P	2.78	TBA750	2.05	74LS04	20
CA741	25	SAS580	2.90	TA7609P	4.39	TBA800	99	74LS05	19
CA748	45	SAS590	2.90	TA7609P	4.39	TBA810AS	1.35	74LS06	19
CA3065	1.00	SL901B	5.00	TA7609P	4.39	TBA820	1.70	74LS07	19
LA4031P	3.21	SL917B	6.25	TA7609P	4.39	TBA890	3.94	74LS08	19
LC7130	5.93	SL1310	1.20	TA7609P	4.39	TBA920(Q)	1.80	74LS09	19
LC7120	5.87	SL1327Q	1.20	TA7609P	4.39	TBA950(2X)	2.40	74LS10	19
LC7137	5.50	SL7654A	2.05	TA7609P	4.39	TBA970	4.09	74LS11	19
LM1303N	2.63	SN7600GN	2.00	TA7609P	4.39	TBA990	1.49	74LS12	19
HA1151	3.89	=SN76013N	2.00	TA7609P	4.39	TBA1441	2.75	74LS13	19
MC1307	1.50	SN76013ND	2.00	TA7609P	4.39	TCA160	1.96	74LS14	19
MC1310P	1.60	SN76023N	2.00	TA7609P	4.39	TCA170B	1.70	74LS15	19
MC1327	1.70	SN76110N	1.15	TA7609P	4.39	TCA270SQ	1.25	74LS16	19
MC1351P	1.75	SN76115N	2.27	TA7609P	4.39	TCA280	2.15	74LS17	19
MC1330P	90	SN76131N	1.30	TA7609P	4.39	TCA940	1.65	74LS18	19
MC1349	1.20	SN76226(DN)	2.00	TA7609P	4.39	TDA440	2.20	74LS19	19
MC1350	96	SN76227N	1.18	TA7609P	4.39	TDA1002	1.95	74LS20	19
MC1352	1.75	SN76532N	1.50	TA7609P	4.39	TDA1003A	5.50	74LS21	19
MC1358P	1.50	SN76533N	1.70	TA7609P	4.39	TDA1004A	2.95	74LS22	19
MC1495L	3.00	SN76533N	1.65	TA7609P	4.39	TDA1006A	2.50	74LS23	19
MC14011BCP	42	SN76544N	1.35	TA7609P	4.39	TDA1035	4.00	74LS24	19
MC14049UB	43	SN76650N	1.05	TA7609P	4.39	TDA1044	4.37	74LS25	19
ML231/ETTR6016		SN76660N	80	TA7609P	4.39	TDA1170	1.99	74LS26	19
		SN76666N	80	TA7609P	4.39	TDA1190	2.60	74LS27	19
ML232	2.20	SN76666N	80	TA7609P	4.39	TDA1200	2.95	74LS28	19
ML236	2.20	SN76666N	80	TA7609P	4.39	TDA1270	3.95	74LS29	19
ML237	2.50	SN76666N	80	TA7609P	4.39	TDA1327	1.70	74LS30	19
ML238	4.20	SN76666N	80	TA7609P	4.39	TDA1352B	1.60	74LS31	19
ML239	2.50	SN76666N	80	TA7609P	4.39	TDA1412	1.20	74LS32	19
ML290	4.12	SN76666N	80	TA7609P	4.39	TDA2002	2.50	74LS33	19
ML922	3.29	SN76666N	80	TA7609P	4.39	TDA2140	5.95	74LS34	19
ML926	2.18	SN76666N	80	TA7609P	4.39	TDA2190	4.95	74LS35	19
ML928	2.18	SN76666N	80	TA7609P	4.39	TDA2200	4.66	74LS36	19
MRF475	2.50	SN76666N	80	TA7609P	4.39	TDA2300	2.80	74LS37	19
MRF477	10.00	SN76666N	80	TA7609P	4.39	TDA2521	4.17	74LS38	19
MSN5807	7.87	SN76666N	80	TA7609P	4.39	TDA2522	2.40	74LS39	19
PLLO2AG	9.89	SN76666N	80	TA7609P	4.39	TDA2523	2.20	74LS40	19
		SN76666N	80	TA7609P	4.39	TDA2523	2.20	74LS41	19
		SN76666N	80	TA7609P	4.39	TDA2523	2.20	74LS42	19
		SN76666N	80	TA7609P	4.39	TDA2523	2.20	74LS43	19
		SN76666N	80	TA7609P	4.39	TDA2523	2.20	74LS119	19
		SN76666N	80	TA7609P	4.39	TDA2523	2.20	74LS1	

THANDAR PORTABLE TEST BENCH

A wide range of high performance instruments, at prices that are hard to beat, puts professional test capability on your bench.

COUNTERS - TF200 10Hz to 200MHz; TF040 10Hz to 40MHz; PFM200A 20Hz to 200MHz (hand-held model); TP600 prescales to 600MHz; TP1000 Prescales to 1GHz.

MULTIMETERS - TM351 0.1% 3½ digit LCD; TM353 0.25% 3½ digit LCD; TM355 0.25% 3½ digit LED; TM354 0.75% 3½ digit LCD (hand-held model); TM451 0.03% 4½ digit with autoranging and sample hold.

OSCILLOSCOPE - SC110A 10MHz, 10mV sensitivity, 40mm CRT with 6mm graticule divisions.

THERMOMETERS - TH301 -50°C to +750°C, 1° resolution; TH302 -40°C to +1100°C and -40°F to +2000°F, 0.1° and 1° resolution. Both accept any type K thermocouple.

GENERATORS - TG100 1Hz to 100kHz Function, Sine, Square, Triangle Wave; TG102 0.2Hz to 2MHz Function, Sine, Square, Triangle Wave; TG105 5Hz to 5MHz Pulse, Free Run, Gated or Triggered Modes.

LOGIC ANALYSERS - TA2080 8 channel 20MHz; TA2160 16 channel 20MHz.

ACCESSORIES - Bench rack, test leads, carrying cases, mains adaptors, probes, thermocouples etc.

Send for our latest catalogue and price list.
Thandar Electronics Ltd,
London Road, St. Ives,
Huntingdon, Cambridgeshire PE17 4HJ.
Telephone (0480) 64646. Telex 32250.



thandar
ELECTRONICS LIMITED

PUTTING THE BEST WITHIN YOUR GRASP

Switch to the biggest wholesaler of quality late model used TV's

- Thousands of Quality Sets always in stock
- Colour/Mono/VCR's and Audios available
- Murphy/Pye/Philips/Sony/National Panasonic and other big names
- We are big - we buy in bulk - we offer you the keenest prices
- Cash and Carry or we will deliver
- New and used stands always in stock

VISIT OUR NEW SHOWROOM
TODAY OR RING US ON
0562 743735

CAMPION THOMPSON
ELECTRICAL WHOLESALERS

Campion House, Franchise Street, Kidderminster, Worcestershire DY11 6RE.



Incorporating



TVs TVs TVs

PANELS PANELS PANELS

DECCA 18" 20" 22" 26"	from £25	BUSH A823 22" 26"	from £25
PHILIPS G8 22" 26"	from £25	HITACHI 18"	POA
PHILIPS 570 18"	from £35	THORN 3500 20" 22" 26"	from £25
PYE CT200 18"	from £35	THORN 8800 22"	from £30
PYE CHELSEA 18"	from £40	ITT CVC8 22"	from £40
NAT. PANASONIC 18"	POA		

The above prices are for working TVs, Non workers usually available Please ring for prices.

QUANTITY DISCOUNT FOR 10+

Panels for most makes available with 3 month guarantee.
Add £1.70 per panel for postage + 15% VAT.

(Also see N.J. Electronics advertisements, all your TV spares panels etc. under one roof).

CONTRAST U.K.

82/83/84 STORFORTH LANE TDG. EST. CHESTERFIELD, DERBYSHIRE S41 0SW
Tel. Chesterfield (0246) 209081

COLOUR TV SETS

Philips G8, Pye 222, Decca 30 series, ITT, Pye Chelsea, Thorn 3500/8000, GEC, many others including JAP.

Working hybrids from £15.

Working solid state from £25.

Non-working sets, working panels and tubes available.


Quantity Discounts

Delivery by arrangement.

SOUTHBRIDGE TV CENTRE
120, Selhurst Rd., London, S.E.25.
Tel: 01-771 3535.

B.K. ELECTRONICS

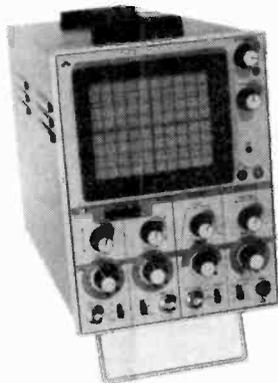INCREASE YOUR PROFITS - IMPROVE YOUR SERVICE
WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT



SAFGAN DT-520 DUAL TRACE SCOPE 20MHz-5" C.R.T.


- SPECIFICATION**
- ★ CH1, CH2: 5mV/div-20V/div
 - ★ Time Base: 1 sec/div-100ns/div
 - ★ XY Facility: Matched XY inputs
 - ★ Trigger: Level control, ± slope selection
 - ★ Auto, normal, TV Triggering
 - ★ Z-Modulation
 - ★ CAL output 1V 1KHz
 - ★ Sweep output
 - ★ Graticule blue ruled 10x8 cm (5" C.R.T.) Very sharp trace.
 - ★ Size: H235mm, W177mm, D360mm.
 - ★ Weight: 6.5Kgs.
 - ★ Supply: 200-240V. 40-60Hz.
 - ★ Price: £210.00 + £31.50 V.A.T.
 - ★ Probes as Thandar below.

BRITISH - NEW MODEL - 12 MONTH GUARANTEE

LEADER LCT-910A C.R.T. TESTER-REJUVENATOR

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T.s.

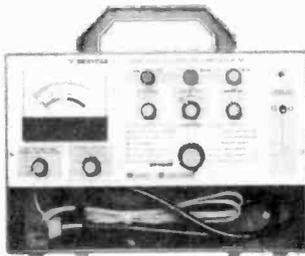
- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors.



PRICE £151 + £22.65 VAT

THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.

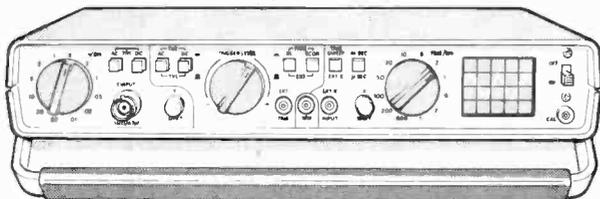The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**



One of the most useful and versatile instruments available.

Full Sized Performance

- ★ 10 MHz bandwidth. * 10 mV per division sensitivity.
- ★ Full trigger facilities are provided including TV frame, or TV filtering.
- ★ Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- ★ Size 255mm x 148mm x 50mm.

* Scope £149.00 + £22.35 V.A.T.

Carry Case £5.95 + £0.89 V.A.T.

x 1 Probe £7.00 + £1.05 V.A.T.

x 10 Probe £8.00 + £1.20 V.A.T.

x 1/10 Switched Probe £9.50 + £1.42 V.A.T.

Rechargeable Batteries £11.00 + £1.65 V.A.T.

AC Adaptor £6.95 + £1.04 V.A.T.

(Overseas purchasers please state voltage.)

BRITISH
MADE

FULLY
GUARANTEED


LEADER HIGH VOLTAGE METER EHT PROBE

Measures up to
40 K.V. D.C. with

SAFETY
BUILT
IN

METER

PRICE
£21.75
+ £3.26
VAT

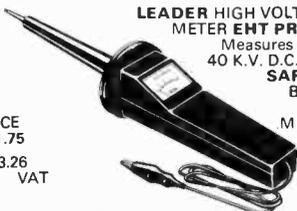

ALSO AVAILABLE

- Analogue Multimeters
 - Digital Multimeters
 - Oscilloscopes
 - Signal Generators
 - Digital Frequency Meters
 - Pattern Generators
 - CRT Tester/Rejuvenator
 - T.V. Field Strength Meter
 - Digital Capacitance Meter
- LARGE S.A.E.
FOR COMPLETE LIST.

U.K. Post Paid. Export orders welcome, please deduct V.A.T. and include an additional £5.00 for Overseas carriage. Mail Order only. Callers by appointment. Barclaycard/Access orders welcome, or Cheque, Bank Draft etc., with order please. Large S.A.E. for technical leaflets of complete range.

Delivery normally within 7 days.

B. K. ELECTRONICS, Dept. 'T',

Unit 5, Comet Way,

Southend-on-Sea, Essex, SS2 6TR.

Tel: (0702) 527572.



FREE CAREER BOOKLET

**Train for success in Electronics
Engineering, T.V. Servicing,
Electrical Engineering—or running
your own business!**

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success

The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

**TICK THE FREE BOOKLET YOU
WANT AND POST TODAY**

ELECTRONICS ENGINEERING

A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.



T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.



ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.



RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.



Name

Address

ICS

ICS
Dept H630,
160 Stewarts Road,
London SW8 4UJ.



01-622 9911
(all hours)


TRANSISTORS, ETC.

Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
AC107	0.48	AU103	2.40	BC192	0.56	BC377	0.29	BD234	0.68	BF222	0.51	BPX29	1.62	MPSU05	0.66
AC117	0.38	AU107	2.75	BC204*	0.39	BC394	0.39	BD235	0.63	BF224 & J	0.22	BR101	0.53	MPSU06	0.76
AC126	0.36	AU110	2.40	BC205*	0.39	BC440	0.52	BD236	0.63	BF240	0.32	BR103	0.64	MPSU55	1.26
AC127	0.54	AU113	2.60	BC206*	0.37	BC441	0.59	BD237	0.68	BF241	0.31	BR303	1.06	MPSU56	1.32
AC128	0.46	BC107*	0.16	BC207*	0.0	BC461	0.78	BD238	0.68	BF244*	0.51	BR34443	1.76	MPSU60	0.82
AC128K	0.55	BC108*	0.15	BC208*	0.37	BC477	0.30	BD253	1.58	BF245*	0.43	BR393	0.60	OCPU131	0.50
AC141	0.65	BC109*	0.16	BC209*	0.39	BC478	0.25	BD410	1.85	BF254*	0.48	BR556	0.44	OC26	1.99
AC141K	0.70	BC113	0.22	BC211*	0.36	BC479	0.33	BD433	0.65	BF255*	0.58	BSS2	0.92	OC28	1.49
AC142	0.60	BC114	0.22	BC212*	0.17	BC547*	0.13	BD435	0.70	BF256*	0.49	BT106	1.50	OC29	1.60
AC142K	0.65	BC115	0.24	BC212*	0.17	BC548*	0.13	BD436	0.71	BF257*	0.47	BT109	1.99	OC35	1.25
AC151	0.31	BC116*	0.25	BC213*	0.16	BC549*	0.15	BD437	0.74	BF258	0.52	BT116	1.45	OC36	1.25
AC152	0.36	BC117	0.30	BC213*	0.16	BC550*	0.24	BD438	0.75	BF259	0.54	BT119	5.18	OC42	0.90
AC153	0.42	BC118	0.24	BC214*	0.18	BC556	0.23	BD519	0.88	BF262	0.73	BU102	2.85	OC44	0.68
AC153K	0.52	BC119	0.34	BC214*	0.18	BC557*	0.16	BD520	0.88	BF263	0.88	BU105	1.80	OC45	0.63
AC154	0.41	BC125*	0.30	BC225	0.42	BC558*	0.16	BD599	0.87	BF270	0.47	BU105/02	1.95	OC70	0.65
AC176	0.45	BC126	0.30	BC237*	0.16	BC559*	0.17	BD600	1.23	BF271	0.47	BU108	2.98	OC71	0.73
AC178	0.51	BC132	0.20	BC238*	0.15	BCY10	0.30	BD663BR	0.86	BF273	0.33	CU126	2.91	OC72	0.73
AC179	0.55	BC134	0.22	BC239*	0.22	BCY30A	1.05	BDX18	1.55	BF274	0.34	BU204	2.50	OC81	0.83
AC187	0.56	BC135	0.21	BC251*	0.25	BCY32A	1.19	BDX32	2.95	BF336	0.63	BU205	2.58	OC139	1.30
AC187K	0.65	BC136	0.22	BC252*	0.26	BCY34A	1.02	BDY16A	0.63	BF337	0.65	BU206	2.59	OC140	1.35
AC188	0.52	BC137	0.30	BC253*	0.38	BCY35	0.87	BDY19	1.55	BF338	0.68	BU208	2.75	OC170	0.80
AC188K	0.61	BC138	0.35	BC261A*	0.28	BD115	1.35	BDY20	2.29	BF355	0.72	BU407	1.38	OC171	0.82
AC193	0.71	BC140	0.36	BC262A*	0.28	BD123	1.50	BDY38	1.38	BF362	0.49	C106D	0.80	OC200	3.90
AC194K	0.74	BC141	0.44	BC263*	0.26	BD124	1.85	BF115	0.48	BF363	0.49	C106F	0.43	OC201	3.95
AC197	1.20	BC142	0.35	BC267*	0.20	BD130Y	1.56	BF117	0.45	BF367	0.29	C111E	0.46	OC202	2.40
AC199	0.95	BC143	0.38	BC268*	0.28	BD131	0.58	BF120	0.55	BF451	0.43	D40N1	0.64	OC205	3.95
AC199K	0.98	BC147*	0.12	BC286	0.40	BD132	0.68	BF121	0.85	BF457	0.46	E300	0.42	OC205	3.95
AC199S	2.02	BC148*	0.12	BC287	0.49	BD133	0.70	BF123	0.48	BF458	0.49	E1222	0.47	OC205	3.95
AD140	1.79	BC149*	0.13	BC291	0.27	BD135	0.37	BF125	0.55	BF459	0.52	E5024	0.19	ON236A	1.98
AD142	1.90	BC152	0.42	BC294	0.37	BD136	0.38	BF127	0.51	BF594	0.16	FB172	0.46	R2008B	2.72
AD143	1.78	BC153	0.38	BC297	0.36	BD137	0.40	BF137F	0.78	BF596	0.17	R20108	0.18	R2108	2.79
AD149	1.42	BC154	0.41	BC300	0.62	BD138	0.42	BF152	0.19	BF597	0.27	MF0A04/02	0.18	R2278	2.78
AD161	0.66	BC157*	0.13	BC301	0.38	BD139	0.46	BF158	0.25	BF599	0.27	ME6001	0.18	R2323	0.85
AD161/162	1.22	BC158*	0.13	BC302	0.86	BD140	0.50	BF159	0.19	BF600	0.29	ME6002	0.18	ST2110	0.49
AD162	1.22	BC159*	0.14	BC303	0.64	BD144	2.24	BF160	0.20	BF601	0.20	MJ2955	1.30	ST6120	0.48
AF114	1.32	BC160	0.52	BC304	0.44	BD145	0.75	BF161	0.84	BF602	0.30	MJ3000	1.58	TIC44	0.25
AF115	1.26	BC161	0.58	BC307*	0.17	BD150A*	0.51	BF163	0.65	BF603	0.23	MJ340	0.68	TIC46	0.35
AF116	1.28	BC167B	0.15	BC308*	0.14	BD155	0.90	BF164	0.95	BF604	0.29	MJ341	0.72	TIC47	0.45
AF117	1.32	BC168B	0.14	BC309*	0.18	BD157	0.51	BF166	0.50	BF605	0.28	MJ370	0.74	TIP29A	0.47
AF118	0.98	BC169C	0.15	BC317*	0.15	BD158	0.75	BF167	0.38	BF606	0.20	MJ371	0.79	TIP296Y	0.50
AF121	0.68	BC170*	0.15	BC318*	0.15	BD159	0.68	BF173	0.35	BF607	0.29	MJ520	0.85	TIP31A	0.51
AF124	0.38	BC171*	0.15	BC319*	0.19	BD160	2.69	BF177	0.36	BF608	0.20	MJ521	0.95	TIP31C	0.67
AF125	0.38	BC172*	0.14	BC320	0.17	BD163	0.67	BF178	0.46	BF609	0.42	MJ525	1.20	TIP32A	0.56
AF126	0.36	BC173*	0.22	BC321A&B	0.18	BD165	0.66	BF179	0.58	BF741	0.48	MJ3000	1.95	TIP32C	0.72
AF127	0.86	BC174A & B	0.26	BC322	0.28	BD166	0.68	BF180	0.53	BF743	0.55	MJ3055	1.20	TIP33A	0.77
AF139	0.58	BC176	0.26	BC327	0.16	BD177	0.58	BF182	0.44	BFW11	1.02	MJ3055	1.20	TIP33A	0.77
AF147	0.52	BC177*	0.20	BC328	0.18	BD178	0.92	BF183	0.52	BFW30	2.58	MJ3055	1.20	TIP33A	0.77
AF149	0.45	BC177*	0.20	BC328	0.18	BD178	0.92	BF183	0.52	BFW59	0.19	MPS3705	0.30	TIP42A	0.80
AF178	1.35	BC178*	0.22	BC337	0.17	BD181	1.94	BF184	0.44	BF606	0.20	MPS6521	0.36	TIP2955	0.77
AF179	1.36	BC179*	0.28	BC338	0.17	BD182	2.10	BF185	0.42	BF607	0.20	MPS6523	0.36	TIP3055	0.58
AF180	1.35	BC182*	0.15	BC340	0.19	BD183	1.34	BF186	0.42	BF608	0.20	MPS6566	0.44	TIS43	0.44
AF181	1.33	BC182L*	0.15	BC347*	0.17	BD184	2.30	BF194*	0.14	BF609	0.20	MPSA05	0.30	TIS73	1.36
AF186	1.48	BC183*	0.14	BC348A & B	0.17	BD187	1.20	BF195*	0.13	BF610	0.20	MPSA06	0.32	TIS90	0.23
AF202	0.27	BC183L*	0.14	BC349B	0.17	BD188	1.25	BF196	0.14	BF611	0.37	MPSA07	0.43	TIS91	0.28
AF239	0.73	BC184*	0.15	BC350*	0.24	BD189	0.71	BF197	0.15	BF612	0.37	MPSA08	0.45	TIS91	0.28
AF240	1.40	BC184L*	0.15	BC351*	0.24	BD190	0.91	BF198	0.29	BF613	0.36	MPSA09	0.45	TIS91	0.28
AF279S	0.91	BC185	0.36	BC352*	0.24	BD191	0.91	BF199	0.29	BF614	0.36	MPSA10	0.45	TIS91	0.28
AL100	1.30	BC186	0.25	BC352A*	0.24	BD192	0.91	BF200	0.25	BF615	0.36	MPSA11	0.45	TIS91	0.28
AL103	2.55	BC187	0.27	BC360	0.59	BD233	0.62	BF218	0.42	BF616	0.36	MPSA12	0.45	TIS91	0.28

Alternative gain versions available on items marked*.

For matched pairs add 20p per pair.

LINEAR IC's		DIODES		VDR's, etc.		VALVES	
Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
SN76023ND	2.52	TBA4800	1.84	BY114	0.60	DYB6/B7	0.75
SN76033N	2.20	TBA500*	2.21	BY116	1.10	DYB02	0.75
SN76110N	1.20	TBA510*	2.21	BY126	1.20	DYB02	0.75
SN76115N	1.62	TBA520*	2.98	AA129	0.28	EC81	0.78
SN76116N	1.78	TBA530*	2.24	AA143	0.18	EC82	0.92
SN76131N	2.10	TBA540*	2.88	AA149	0.18	EC83	0.78
SN76226N	2.80	TBA550*	3.13	AA213	0.42	EC83	0.78
SN76227N	1.81	TBA560*	3.18	AZ15	0.35	EC83	0.78
SN76228N	1.80	TBA570*	2.29	AZ17	0.42	EC83	0.78
SN76502N	1.92	TBA611B	1.68	AY102	3.85	EC83	0.78
SN76503P	0.97	TBA641	4.55	BA100	0.24	EC83	0.78
SN76533N	1.38	TBA6418X1	4.60	BA102	0.36	EC83	0.78
SN76544N	1.85	TBA651	2.42	BA104	0.10	EC83	0.78
SN76546N	1.85	TBA673	2.31	BA110	0.89	EC83	0.78
SN76570N	1.81	TBA700*	2.50	BA111	0.70	EC83	0.78
SN76620AN	1.81	TBA750*	2.18	BA115	0.17	EC83	0.78
SN76666N	0.99	TBA810	2.05	BA116	0.56	EC83	0.78
SN76680N	0.64	TBA810AS	2.00	BA121	0.85	EC83	0.78
SN76686N	0.96	TBA820*	2.80	BA129	0.45	EC83	0.78
SN76700N	1.03	TAA300	3.8F	BA145	0.19	EC83	0.78
SN76710N	1.84	TAA300*	2.90	BA148	0.19	EC83	0.78
SN76720N	2.34	TAA300*	3.55	BA154	0.06	EC83	0.78
SN76730N	1.88	TAA320					

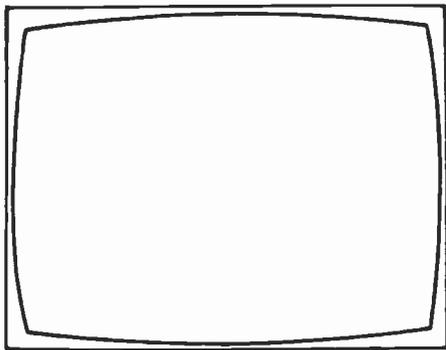

TELEVISION

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

PCB SERVICE

The Readers' PCB Service continues in operation - details as given on page 265 of the February issue. Boards for the Frequency Counter-Timer project are now available, also for the In-Circuit Transistor Tester.

Prospects for Cable

This cable business gets more and more curious - largely because the whole idea was blown up out of all proportion to start with. Let's just backtrack for a moment. The provision of programmes via cable is almost as old as broadcasting itself. At the present time some two and a half million people in the UK are served by cable TV. The problem is that such services are very restricted, being limited (with a few experimental exceptions) to the relay of off-air transmissions in areas where reception is difficult. In Europe, cable systems have proliferated in areas where programmes from different countries can be offered, while in the USA a tremendous boost was given to cable operations by the advent of satellite programme distribution. This rapid expansion of US cable operations seems to have been the factor responsible for the idea that cable could become a big thing in the UK. The Minister of Information Technology became enthusiastic about the prospects, and in January 1982 the government's Information Technology Advisory Panel produced a report on the subject. This came to the conclusion that "a major programme of cable installation was desirable", and that there were "powerful economic and industrial arguments for encouraging cable systems in the United Kingdom." The arguments presented in the report didn't seem all that powerful or convincing to many observers, and to this one the report seemed to be a very confused presentation of various technical, economic and industrial aspects of the subject. The Hunt Committee was then set up to report on technical standards and methods of exercising control, and produced its report on schedule last September. This was to be followed by a government White Paper which was expected early this year but was finally published on April 27th. It seems that the Home Office and the Department of Industry had spent a couple of months arguing about the right balance between ensuring that broadcasting standards are maintained and the industrial advantage to be gained by encouraging cable laying at the earliest opportunity. Between Hunt and the White Paper, the city had been assessing the prospects and getting more and more gloomy.

There is of course no reason why people should be deprived of as wide a choice of programmes as possible, within the constraints imposed by economics and the need to maintain the established programme sources. Cable can provide this wide choice but is expensive. The original ITAP report didn't really seem all that concerned about wide programme choice however: it was more concerned with a starry-eyed view of cable providing a vast increase in information services, backed by arguments that the appropriate technology was now available and should be exploited in order to create jobs and establish leadership in an important new industry.

As expected, the White Paper confirms that cable networks providing extra channels are to be allowed, with a Cable Authority to award franchises to cable operators and ensure a degree of regulation, but little is now being said about the technological prospects and economic advantages. The starry-eyed technical wonder aspect has evaporated. In its place there seems to be greater acknowledgement of the practicalities of the matter, to wit that what people are likely to be prepared to pay for will be a few extra TV channels to increase their choice of programmes. Forget the ideas about linking homes to powerful computers, electronic shopping and all that sort of thing.

Who will benefit from the new services that look as if they will come on offer rather falteringly? We now come to the nitty-gritty. Some very interesting research on the business prospects has been carried out recently. For example, NERA International Inc. have produced a detailed report entitled "Can Cabling Britain be Profitable?" This studied four potential franchises and came to the conclusion that one was "very promising", two were "marginal" and one was "distinctly unattractive". Ah, you might suppose, that "distinctly unattractive" franchise must be some obscure place with all sorts of practical problems. Not at all! It was West London. Now if cable is a distinctly unattractive proposition in a high population density area like Hammersmith/Fulham/Chelsea/Kensington, you might wonder where it would be "very promising". The answer is Glasgow, and the reasons for this seem to be largely demographic, i.e. lots of kids. According to a report in the *Financial Times*, many "cable experts favour council estates and poorer, racially mixed districts over affluent neighbourhoods". Bruce Fireman of investment bank Charterhouse Japhet is quoted as saying that "Mayfair and Worthing will be the last parts of the country to be cabled." The Pearson Longman group did a study of Harrow, N.W. London, and found that the cost of cabling (at between £400 and £500 a house) would be far too high for a service to be economically viable. The general consensus seems to be that careful selection of franchise area and type of audience will be crucial to economic success, and that "it's a very risky investment" (Jeffrey Richardson, of management consultants Deloitte Haskins and Sells, quoted in *The Observer*).

In retrospect it seems sad though inevitable. More soap operas for areas with plenty of children will work all right, but all that brave talk about cable providing a revolution in information technology for the home is just not on. For the present, anyway.

Letters

N1700 SPEED CONVERSION

I have just completed the N1700 speed conversion described in your April issue – a worthwhile and cost-effective modification by Mike Phelan. The quality obtained at the reduced speed is very good. The modification gives only a fifty per cent increase in recording time however rather than doubling it. It appears that the discharge of the 0.047 μ F capacitor in Fig. 2 depends on the value of R21 and the series 680k Ω resistor, so to double the total resistance R21 should be increased to 1.9M Ω – say 1.8M Ω 5 per cent.

On my machine the motor and control circuitry are operating at near the limit at half speed – if R21 is made 2.2M Ω , the capstan motor stalls and restarts at about four second intervals on replay but works smoothly on record.

With the slow-speed modification the best replay is obtained with the tracking control displaced a little to the left of its normal position, probably because of the overlap and consequent over writing of the edges of adjacent tracks. This will displace the best reading position a little with respect to the original record head position.

*Ian Burgon,
Grantham, Lincs.*

NO TO GIMMICKS

Is it really necessary for certain video/TV manufacturers to resort to gimmickry to sell their products? I refer in particular to stereo TV and the recently announced 3D TV.

It's true that dual-channel TV and video is useful for bilingual information, but just whom does the industry think it's fooling when it predicts any sort of future for stereo TV? Creating a stable stereo image is difficult enough, but when there's a visual scene complementing it the task become virtually impossible.

In the case of mono sound, the visual impression dominates and the viewer has no problem in identifying the sound source with wherever the visual information dictates. No one has ever complained that the visual image and the sound source are separated. The distance involved is too small for this. Once stereo sound is introduced however it's a different matter: attention is immediately drawn to an apparently shifting sound source, and the discrepancy between it and the visual scene can only cause confusion.

Leaving aside more subtle discrepancies, take the case of an opera singer moving across the stage, the sound faithfully following him whilst his image remains dead centre as the camera pans him! Are we to assume that this is taken into account, along with a reduced stereo image requirement as the camera closes in on the scene? Furthermore, if any claim to accuracy is made, why the restriction of the sound image in one direction while the TV picture is two-dimensional? Visualise this scene: thousands of disappointed stereo TV owners witnessing the launch of some new space venture, the rocket travelling upwards through the top of the TV set while the roar of

the motors stubbornly remains smack bang in the middle of the screen. And whom do Thorn think they're kidding with their stereo video demonstration tape? The deterioration of sound quality on the "old mono" part compared with the "new stereo" section is obvious even on monophonic equipment! Just what went on when this tape was recorded one can only wonder . . .

But the Gimmick of the Year award must surely go to NordMende/Saba for their introduction of "3D TV". Now obviously there's no way in which the TV set can know what is foreground information and what is background information unless this is transmitted. Practical tests bear this out, showing that the only effect of this "revelation" is to give the impression that the picture is situated in a different plane from the TV screen – and with poor colour at that. Not only is the public expected to swallow this but, through the technical information sent out, it seems that we in the retail and servicing trade are expected to swallow it as well. Well, no thank you.

Any steps taken to improve the picture and sound quality are welcome, but let's avoid these gimmicks please.
*Alan Willcox,
Llanadeyrn, Cardiff.*

TWELVE-HOUR CLOCK CORRECTION

I've not seen a correction yet to an error that occurred in the twelve-hour clock conversion article in the December 1982 issue. This applies to the information given for the Ferguson 3V30, where link B454 should read link B453. Lifting links B453 and B464 alters the clock as intended in the article – I believe link B454 in fact supplies the "first" week indicator.

*P. Jigins,
Grays, Essex.*

PORTABLE LIGHT UNIT

I'd like to make a couple of points about Victor Rizzo's portable light unit (letters, April). First the standard car reversing lamp in the UK is 21W, which would require a 2A transformer. Secondly the method of construction, with an earthed metal box, could be extremely dangerous. Suppose you used it in the corner of a customer's house – now imagine what would happen if you touched a live TV chassis and this earthed box at the same time!

*P. Richards,
Criccieth, Gwynedd.*

Editorial comment: Several readers have written to point out the dangers of the earthed portable light. Our thanks to one and all.

PHILIPS K30 CHASSIS

Here's an interesting problem we had recently with a remote control Dynatron set fitted with the Philips K30 chassis. The set stopped working in the show room and I was asked to look at it. On examination I found that the 285V h.t. supply was reaching the collector of the chopper transistor, but the output at its emitter was pulsating at around 8V. No fault could be found in the power supply, so attention was turned to the line output stage. The line output transistor and the various diodes in the circuit all read o.k., and after making various checks I discovered that conditions returned to normal – with e.h.t. present and the tube's heaters alight – when the scan coils were

disconnected. Further investigation revealed that the print running from the line linearity coil beneath the line output transformer to the scan correction capacitor C1560 was being shorted by the line output transformer's earthed clamping washer. The cure is to cut the print and bridge across with insulated wire. It's worth checking this point on the K30 chassis – could save callbacks.

*M. S. Barakat,
Slough.*

SERIES REGULATOR FAULT

The following fault recently experienced may serve as a warning to others. The set was a Bush Ranger monochrome portable, Model BM6514, the symptoms being that the set was dead – no sound or raster, and the tube's heater out. It didn't take long to see that the fusible resistor R62 (see Fig. 1) was open, thus removing the output from the series regulator – or rather preventing it from starting up. When this resistor was resoldered and the set switched on R62 began to overheat badly and the regulated supply line fell from 11V to 4V.

Quick as a flash I diagnosed an overload and began disconnecting the various sections of the receiver. Sure enough when the print to the line output stage was cut the supply returned to exactly 11V, with sound and the tube's heater alight. The line output stage was carefully checked, but no obvious culprits could be found. "Line output transformer" I muttered, and obtained a replacement which I then confidently fitted. When the set was switched on however the fault symptoms remained exactly as before!

There followed a lot more checking around the line output stage, and I finally disconnected all the leads from the output transformer. Only when the supply lead to the primary winding was disconnected did the fault disappear. So another line output transistor was tried, in vain, and a check on the line drive waveform revealed that this was correct. Dark thoughts about the new transformer began to gather in my mind, and yet another was obtained – with the same results.

Whilst wondering what to do next I tried the effect of adjusting the set volts control RV6 with the line output stage disconnected. Imagine my amazement when I saw the 11V line remain rock steady at exactly 11V when RV6 was adjusted from one end to the other!

The penny then dropped. The series regulator transistor

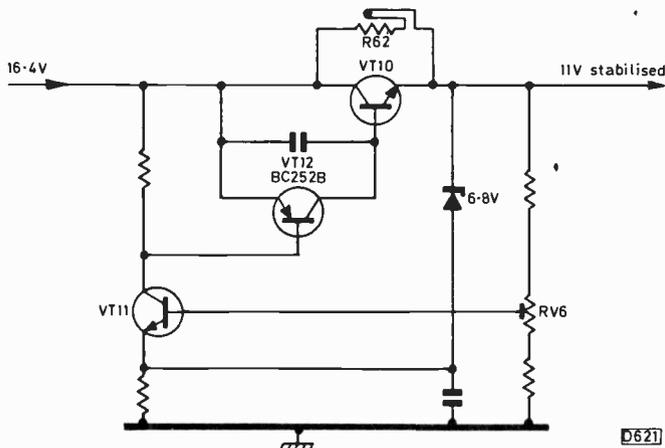


Fig. 1: Series regulator circuit used in the Bush Ranger Model BM6514. With a light load and VT10 non-conductive the output remained at 11V.

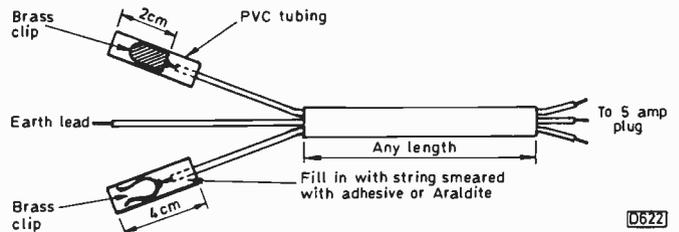


Fig. 2: DIY adaptor for converting a 13A plug for operation from a 5A socket.

VT10 was not conducting, so R62 was overheating, being called upon to handle all the current. By coincidence (or Sod's Law) the supply voltage became exactly 11V on light load with the line output stage disconnected. Had the supply line voltage been anything else I wouldn't have wasted so much time on the line output stage.

Having reached this stage, it didn't take long to discover that the driver transistor VT12 was open-circuit base-to-emitter, a replacement restoring normal service.

*Dennis Apple,
West Bridgford, Nottingham.*

5A ADAPTOR

Most homes are fitted with 13A sockets, but the service engineer still occasionally encounters 5A types. Since the soldering iron is usually fitted with a 13A plug, this means either having to improvise or waste time swapping plugs. The contraption shown in Fig. 2 solves this problem and is safe to use.

The clips in the prototype were made from the terminals of a discarded 4.5V battery – 3cm is a good length. These are bent to fit the 13A plug flat pins (live and neutral only), the clips then being tightly embedded in a length of suitable PVC tubing (about 4cm long). The outer covering of white coaxial cable will do. For safety's sake it's important that the plug pins are completely covered by the tubing. Fill the wire end of the tubing with Araldite (costly) or with a piece of string smeared with adhesive.

For the earth connection I've found that it's better to use a suitable crocodile clip – it's easy to get mixed up, notwithstanding the wire colour coding!

*Victor Rizzo,
Msida, Malta.*

SURGE MODIFICATION

Other readers may be interested in a modification I carried out on the Decca hybrid colour chassis (Bradford chassis) – the version with no thermistor in the heater circuit, resulting in a surge which appears almost too bright for comfort.

An 0.3A thermistor was fitted in series between the heaters of the PCL82 and PCF80 valves, with the normally-open contacts of a relay of some 500Ω coil resistance wired across the thermistor. The relay's coil, with a 60Ω resistor in series, was used to replace the PCL82's 560Ω cathode bias resistor.

This modification eliminates the switch-on surge, and gives a time delay after which the thermistor is shorted out. It's worked with no problems for over a year.

*F. S. Yates,
Bedford.*

Editorial comment: In many of these sets a modified audio circuit is used, the PCL82's cathode bias resistor being 390Ω.

Teletopics

EIGHT-HOUR VHS MACHINES

The VHS system is proving to be very adaptable. We've already had the compact version (VHS-C) – the latest models are described later. Now come two-speed, eight-hour machines. Models so far announced include the JVC HR7655, Ferguson 3V32, Panasonic NV788 and the Hitachi VT17. These are all top of the range models, featuring front loading, infra-red remote control, etc.

The two speeds are 2.34cm/sec and 1.17cm/sec, the later giving up to eight hours' recording time on a standard E240 cassette. Two extra heads are used, the second pair having a narrower gap width for the slower speed (the Panasonic machine has five heads in all, the fifth having a wider gap to give improved still and slow motion pictures with standard tracks). Both standard and long play recordings can be made on the same tape, the machines automatically detecting the type of recording on playback and setting up accordingly.

END OF 405

The Home Secretary announced on April 12th the government's decision to bring forward to the end of 1984 the closedown of the BBC and IBA 405-line transmitter networks. The aim is to allow the Band I/III v.h.f. allocations to be made available sooner for mobile radio. In his statement, the Home Secretary recognised that some 70,000 people in smaller communities scattered throughout the country could still be without a TV service at the end of 1986. Some of these will be catered for in a further phase of transmitter building designed to cover communities down to 200 people where this is economic.

THOMSON-JVC DEAL

Thomson-Brandt and JVC have signed an agreement on the manufacture of VHS equipment. Thomson-Brandt hopes to produce a million VCRs a year and to produce precision mechanical parts, including heads, for use in the J2T (JVC-Telefunken-Thorn) plants in Newhaven and W. Berlin. By boosting the locally made content of VHS machines, the problem of export restrictions on Japanese machines could be avoided.

The initial Thomson-Brandt plans are to set up a plant to produce mechanical parts accounting for some 40 per cent of the value of a VHS machine. This boost to VHS manufacture in Europe, plus the new eight-hour capability of the VHS system, would seem to place a further question mark over the prospects of the V2000 system. Meanwhile the W. German Federal Cartel Office has given Thomson-Brandt approval for the takeover of Telefunken and, in Japan, JVC has launched its VHD video disc system.

BOOM YEAR

1982 was certainly boom year for TV and VCR sales/rentals in the UK. Colour set deliveries totalled 2,934,000, an increase of 14 per cent on 1981 and well in excess of the famed Barber boom year of 1973 when deliveries reached 2,250,000 million. Of the 1982 total, just over two million CTV sets were of the large screen type and just over 900,000 were small-screen sets (16in. and under): 571,000 were equipped for teletext reception.

Import penetration overall increased from 29 to 32 per cent. Monochrome portable deliveries reached 1,012,000.

The VCR total was 2,235,000 compared to 1,035,000 in 1981.

For the present year, sales of large-screen CTVs are expected to remain at much the same level, with an increase in small-screen CTV sales to something like 1,100,000.

The value of CTV imports in 1982 was £156,367 million. CTV exports amounting to £56,440 million were recorded.

Thorn have taken a major step to increase sales of UK made small-screen CTVs with the introduction of the new TX90 chassis – see story later.

EURO SATELLITE TV DISAGREEMENT

Despite an EBU technical committee deciding that a single European standard for satellite TV transmissions is of "paramount importance", and that the standard should be a form of the C-MAC system developed by the IBA, the European Broadcasting Union has failed to reach agreement on a common standard. France is likely to go ahead with SECAM-based transmissions, while W. Germany has declined to accept a common standard unless this is agreed by all parties. UK broadcasters and setmakers are proceeding with the development of C-MAC equipment ready for the start of the BBC's satellite service in late 1986, and since the French and W. German services are due to start in 1985 there's little time left to reach agreement on a common system.

ITT-STC

As mentioned in our leader last month, ITT expects to have TV sets using the new ITT Digivision system on sale in the UK early next year. The system was described in some detail in our November 1981 issue.

Meanwhile STC has decided not to purchase ITT Consumer Products (UK) Ltd. in view of the close integration of the ITT consumer electronics manufacturing operations at Basildon and Borkum in W. Germany. It will however be buying the ITT rental operation Telebank TV Rentals, which operates mainly in the north. ITT has decided to take shares rather than cash for the sale of its UK subsidiaries to STC, which will ensure a continuing strong link between the two companies.

STEREO SOUND TRANSMISSION

The BBC's stereo TV sound test transmissions, using the W. German two-carrier f.m. system, were mentioned in this column last December. The transmissions took place out of normal service hours and were conducted to establish whether the system was compatible with normal UK u.h.f. reception. They were observed by staff from the BBC, ITV companies and receiver manufacturers in the area served by the Crystal Palace transmitter: analysis of the 414 questionnaires returned has now been completed. The results confirm the expectation that crosstalk between the two sound signals is not a problem and that patterning due to beats between the two carriers is acceptable when the amplitude of the main carrier is reduced a little. Buzz on sound can be a problem with existing receivers however, regardless of the level of the second carrier, and this problem is increased when the amplitude of the main carrier is reduced. The buzz is to some extent receiver dependent, but the main factors affecting it were found to be multipath propagation, which can cause the received sound-to-vision ratio to vary by ± 5 dB or more, and the

Interested in Television Servicing?

Try a ZED Pack. Effect Repairs at Minimum Cost.

Z1	300 mixed ½ and ¼ watt and miniature resistors	£1.95	Z20	10 Assorted switches including: Pushbutton, Slide, Multipole, Miniature etc. Fantastic Value	£1.20	Z44	TO3 Mounting kits (BU208)	8 for 60p
Z2	150 mixed 1 and 2 watt resistors	£1.95	Z21	100 Assorted Silver Mica caps	£2.20	Z45	TO220 Mounting kits (TIP33)	10 for 60p
Z3	300 mixed capacitors, most types amazing value	£3.95	Z22	10 Mixed TV convergence Pots	£1.00	Z46	TO126 Mounting kits (BD131)	12 for 60p
Z4	100 mixed electrolytics	£2.20	Z23	20 Assorted TV Knobs including: Push Button, Aluminium and Control types	£1.20	Z47	Pack of each Mounting kit. All include insulators and washers	£1.50
Z5	100 mixed Polystyrene Capacitors	£2.20	Z24	10 Assorted Valve bases B9A, EHT, etc.	£1.00	Z48	3a 1000v Diodes (IN5408 type)	8 for £1.00
Z6	300 mixed Printed Circuit Components	£1.95	Z25	10 Spark Gaps	£1.00	Z49	Brushed Aluminium Push Button Knobs, 15mm long x 11mm Diam. Fit standard 3½mm square shafts	10 for £1.00
Z7	300 mixed Printed Circuit resistors	£1.45	Z26	20 Assorted Sync Diode Blocks	£1.00	Z50	Chrome finish 10mm x 10mm Diam as above	10 for £1.00
Z8	100 mixed High Wattage Resistors, wirewounds etc.	£2.95	Z27	12 Assorted IC Sockets	£1.00	Z51	Aluminium Finish. Standard Fitting Slider Knobs. (Decca)	10 for £1.00
Z9	100 mixed Miniature Ceramic and Plate caps	£1.50	Z28	20 General Purpose Germanium Diodes	£1.00	Z52	Decca "Bradford" Control Knobs Black and Chrome. ¼" Shaft	8 for £1.00
Z10	25 Assorted Potentiometers	£1.50	Z29	20 Assorted Miniature Tantalum Capacitors. Superb Buy at	£1.20	Z53	Tuner P/B Knobs. Black and Chrome. Fit most small Diam Shafts, ITT, THORN, GEC etc.	8 for £1.00
Z11	25 Assorted Presets, Skeleton etc.	£1.00	Z30	40 Miniature Terry clips, ideal for small Tools etc.	£1.00	Z54	Spun Aluminium Control Knobs (ITT) ¼" Shaft, suitable for most sets with recessed spindles	8 for £1.00
Z12	20 Assorted VDR's and Thermistors	£1.20	Z31	5 CTV Tube Bases	£1.00	Z55	14 Pin DIL I.C. Sockets	12 for £1.00
Z13	1 lb Mixed Hardware, Nuts, Bolts, Selftappers, "P" clips etc.	£1.20	Z32	10 EY87/DY87 EHT bases	£1.00	Z56	16 Pin Quil I.C. Sockets	12 for £1.00
Z14	100 mixed New and marked transistors, all full spec. includes: PBC108, BC148, BF154, BF274, BC121L, BC238, BC184L and/or Lots of similar types	ONLY £4.95	Z33	20 x PP3 Battery Connectors	£1.00	Z57	16 Pin DIL TO QUIL I.C. Sockets	10 for £1.00
(Z14A)	200 Transistors as above but including power types like BD131, 2N3055, AC128, BFY50 etc.	£9.95	Z34	6 x Miniature "Press to Make" Switches, Red Knob	£1.00	Z58	22 Pin DIL I.C. Sockets	10 for £1.00
Z15	100 Mixed Diodes including: Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec.	£4.95	Z35	12 Sub Min S.P.C.O. Slide Switches	£1.00	Z59	B9A Valve Bases P.C. Type	20 for £1.00
Z16	20 IN4148 Gen Purpose Diodes	£1.00	Z36	12 Min D.P.C.O. Slide Switches	£1.00	Z60	0.47W ½ Watt Emitter Resistors	40 for £1.00
Z17	20 IN4003/10D2	£1.00	Z37	8 Standard 2 Pole 3 Pos Switches	£1.00			
Z18	20 Assorted Zeners. 1 watt and 400 mw	£1.50	Z38	4 x HP11 Batt Holders (2x2 Flat type)	4 for £1.00			
			Z39	3.5mm Jack Sockets, switched, enclosed Type	8 for £1.00			
			Z40	100 Miniature Reed Switches	£2.30			
			Z41	100 Subminiature Reed Switches	£4.20			
			Z42	20 Miniature Reed Switches	£1.00			
			Z43	12 Subminiature Reed Switches	£1.00			

High quality **COAX PLUGS**, silver plated pin, grub screw fixing. **5 for £1**
COAX COUPLERS **5 for £1**
COAX FLYING SOCKET **3 for £1**

ELECTROLYTIC

1µf 63v	20 for £1.00
1µf 350v	10 for £1.00
2.2µf 63v	20 for £1.00
4µf 350v*	10 for £1.00
22µf 16v	20 for £1.00
100µf 25v	20 for £1.20
160µf 25v*	20 for £1.50
330µf 25v	10 for £1.00
400µf 40v*	8 for £1.00
470µf 25v	10 for £1.00
470µf 35v	8 for £1.00
1000µf 35v	6 for £1.00
1000µf 40v*	5 for £1

*Axial. All others are Radial.

CAN TYPES

22µf 375v (3 pin)	50p
50µf 250v (3 pin)	50p
100+200 350v	£1.00
2000µf 100v	£1.00
1000µf 100v	60p
2,200µf 40v	60p
2,200µf 63v	70p
3,500µf 35v	50p
220µf 400v ITT/RBM	£1.00
6,700µf 70v	£1.00
10,000µf 40v	£1.00

THEY'RE BACK

We can now again offer our special TV **BARGAIN PARCELS**. These contain all manner of useful bits and pieces. Components, semiconductors, videogame boards etc. which we have accumulated over the past year and must clear as we need the space.

5kg £9.95 10kg £14.95

"RIFA"
 0-1µ 1000v Flameproof **5 for £1.00**

EHT DIODES
 Very small. 20kV 2.5ma. 30ma peak
50p ea. 3 for £1.00

R.B.M. USERS LOOK!
 No more messy soldering. 24 pin I.C. sockets for SL901 etc.
SPECIAL OFFER: 5 for £1.00
100 for £12.50.

SPECIAL OFFERS
 100 Assorted Polyester Capacitors. Mullard C296's and others
 160v-400v only **£2.00**
 100 Assorted Mullard C280's Cosmetic imperfects etc. **£2.00**
 200 Mullard Miniature Electrolytics Cosmetic imperfects etc. **£2.00**
PACK OF EACH £5.00

12V BULBS on leads. Suitable for most **VIDEO RECORDERS.**
70p each 4 for £2

BY127 Type diodes. Unmarked, untested, Approximately 90% o.k. **100 for £2.95**
AC128 untested **100 for £3.95**

ZENER DIODES
 0v7, 2v7, 4v3, 4v7, 5v6, 6v2, 6v8, 7v5, 27v, 30v. ALL 400mw.
 10 of one value **80p**
 10 of each **£6.60**
 1.3 watt, 12v, 13v, 18v
 10 of one value **£1.00**
 10 of each **£2.50**

DIODES
 25 x IN4002 **£1.00**
100 for £2.50
 20 x IN4003 **£1.00**
100 for £3.00
 20 x IN4005 **£1.50**
100 for £5.00
 20 x IN4148 **£1.00**
100 for £2.50
 10 x SKE 4F2/06 (600v 2a fast switching) **£1.00**
 12 x BY127 **£1.00**
 8 x BY255 (3A 1000V) **£1.00**
 10 x BA158 (600v 400ma) **£1.00**
 IN5402 3a 200v **8 for £1.00**
 6A, 100V, Bridge Rectifier. Very small. **80p ea. 3 for £2.00**

I.C.'s
 CA270AE **£1.00** **6 for £5.00**
 MC1327P **£1.00** **6 for £5.00**
 TBA120SB **50p each, 5 for £2.00**
 TBA820 **£1 each, 6 for £5.00**
 TBA810P **£1.00** **6 for £5.00**
 555 Timer 3P **4 for £1.00**
 TAA 661B **£1.00** **6 for £5.00**
 SN7660N **50p** **5 for £2.00**

THORN SPARES
 "3500" Transductor **£1.20, 3 for £3.00**
 "3500" Focus Assembly with VDR **£1.50**
 "8500" Focus Assembly. Rotary type **£1.50, 3 for £4.00**
 "8500".0022 2000v Line Capacitor **10 for £1.00**
 "1590/91" Portable metal boost Diode (W11) **5 for £1.00**
 "1500" Bias Caps 160µf 25v **20 for £1.50**
 "1500" Jellypot. L.O.P.T. Pinkspot **£3.50**
 "900/950" 3 stick triplers **£1.00, 3 for £2.50**
 "950" Can. 100 + 300 + 100 + 16µf **£1.00**

THYRISTOR CONVERGENCE POTS
 SS106 (BT106) 75p each **200£. 1K. 8 of one type £1.00. 8 of each type £6.00.**
 5£. 10£. 20£. 30£. 50£. 100£.

V.C.R. BATTERY PACKS.
HITACHI PORTABLE V.C.R. Nicad pack. Type VTBP60E **£20 each.**
 Brand New and Boxed **3 for £5.00**

THORN "VIDEOSTAR" 3V25/26 Nicad pack. Type VA214. Also suitable for J.V.C. etc. Brand new and boxed. **£20 each, 3 for £50.**
THORN "VIDEOSTAR" Nicad packs. Same as above but secondhand, untested. Contain 10 "C" size Nicads (HP11) which can be replaced if necessary. **£10 each, 3 for £25.**

MISCELLANEOUS
 BG100 tripler for CVC45 etc. **only £3.50**
 Line output transformer for RBM823A **£4.25 each, 3 for £10.00**
 ITT VC200 4P/B Transistor Tuner. Suitable for some Pye and Philips sets. 3 hole fixing **£2.75 each**
 Decca Bradford Tuner. **£4.00 each, 4 for £12.00**
 5 button type UHF Modulator UHF out Video in. Ch. 36. 2½" x 2" x ¼" complete with 9 foot coaxial lead and plug. With connection data **£3.00 each, 2 for £5.00**
 GEC Hybrid 2040 series Focus Assembly with lead and VDR rod **£2.00 each, 3 for £5.00**
 Convergence Panel for above. Brand new leads and plug. **£3.00 each**
 GEC 2010 Transistor Rotary Tuner with AE. SKT. and leads **£1.95 each, 3 for £5.00**
 Buch CTV 25 Quadrupler type Q25B equivalent to ITT TU25 30K **£3.00 each, 2 for £5.00**
 Focus VDR Rods 2½" x ¼". Suitable for GEC, Decca etc. **75p each, 3 for £2.00**
 Grundig UHF/VHF Varicap Tuner for 1500GB, 3010GB. **£12.50 each, 3 for £30.00**
 EHT Lead with Anode cap (CTV) suitable for split Diodes sets 1m long **60p each, 3 for £1.50**
 EHT Cable **30p per metre, 10 metres £2.50**
 Anti Corona Caps **3 for £1.00**
 4.433 Mhz CTV Crystals **£1.00 each, 3 for £2.50**
 Cassette Mains Leads. 7ft with fig 8 plug **60p each, 3 for £1.50**
 6 MHZ sound filters, ceramic 3 pin "TAIYO" type **50p each, 3 for £1.00**
 10.7 MHZ Ceramic Filters "Vernitron" FM4 **50p each, 3 for £1.00**
 PYE CT200 Control Knobs **8 for £1.00**
 Cassette/Calc Leads. 2m long. figure 8 skt. to flat pin. **60p each, 3 for £1.50**
 American plug **5 for £1.00**
 3.5mm Jack Plug on 2m of screened lead **5 for £1.00**
 Degaus VDRs. 1½" diam, for RBM etc. **5 for £1.00**
 Mains Neons **10 for £1.00**
 2k2 Screenfeed Resistors. White ceramic, 9 watt, with fusible link. **8 for £1.00**
 Philips G8 Transductor. **£1.20 each, 3 for £3.00**
 E.H.T. Discharge probe, with heavily insulated handle, with lead and chassis connector. **60p each, 3 for £1.50**

REGULATORS
 7812 12v 1a **3 for £1.00**
 7805 5v 1a **3 for £1.00**


GEMINI ELECTRONIC COMPONENTS

Dept. TV, The Warehouse, Speedwell Street, London S.E.8.

Please quote ZED code where shown. Send cheque* or Postal Order. Add 60p P&P and 15% VAT.
 *Schools etc. SEND OFFICIAL ORDER. Allow up to 28 days for delivery. Most orders despatched same day.
ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8.

Send large S.A.E. for list of Quantity, Prices and Clearance Lines etc.

NOW!

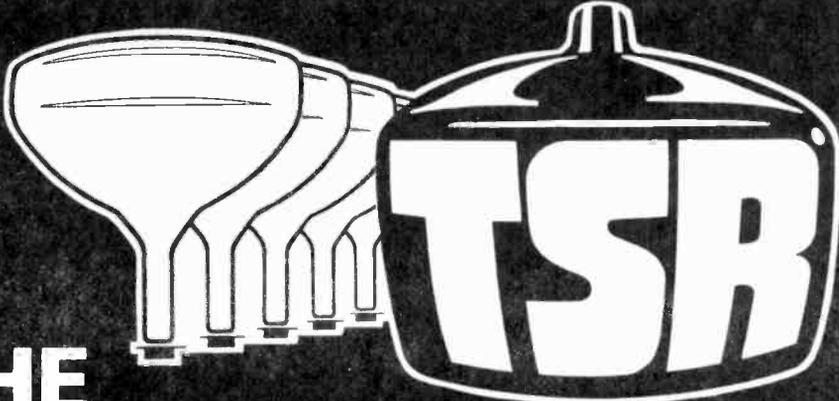

FOR THE FIRST TIME!

QUALITY REBUILT CRTs

ALL SONY CRTs

and PROJECTION SYSTEMS

ALL HITACHI CRTs

including the 560DZB22 and 510VLB22 series

All In-Line CRTs whatever make.
All monitor CRTs.
All gaming machine CRTs.

SONY, HITACHI,
DZB/VLB glass bought.

ONE YEAR GUARANTEE
WITH A FOUR YEAR OPTION
★
REBANDED FOR MAXIMUM SAFETY
★
SPECIALIST CRTs REBUILT AT OUR
SCOTTISH FACTORY



SCOTLAND & N. ENGLAND
T.S.R. Vacuonics Ltd.,
Tom Stewart Lane,
St. Andrews, Fife,
Scotland.
Tel: (0334) 74035

Available **NOW!**
only from sole distributors

MIDLANDS

Express T.V. Supplies
33 Fortescue Lane,
Rugeley, Staffs.
Tel: (08894) 77600

THE
OTV
TUBE SHOP

LONDON & HOME COUNTIES

OTV House,
144 Lea Bridge Rd.,
London E5 9RB.
Tel: 01-985 6111

SOUTHERN ENGLAND

Double D. Distributors
27 Florence Rd.,
Parkstone, Poole, Dorset.
Tel: (0202) 742 347

S.W. ENGLAND

Torbay Tubes
2a Barton Hill Road, Barton Industries,
Torquay, Devon.
Tel: (0803) 33035

Information on all other CRTs available on request

spectral content of the picture.

The general conclusion reached is that a system of this type could provide a largely satisfactory service but alternative possibilities should be investigated. In particular the use of digital sound for DBS transmission makes it important to establish whether a digital package could provide a better alternative for terrestrial propagation than the use of a second f.m. carrier. Preliminary assessments indicate that the digital option would give a better compromise between compatibility and ruggedness. The BBC has started an examination of digital methods and will be carrying out over-air tests in due course.

LARGE-SCREEN MONOCHROME SET

There are not many large-screen monochrome sets on the market at present, so it's worth mentioning a new addition to the Pye range, the 20in. Model 2080, which has a recommended retail price of £110.

THORN'S TX90 CHASSIS

Thorn has developed a new chassis, the TX90, with the aim of increasing Ferguson's share of the small-screen CTV market. Since the new 14in. Model 37140 has been designed to sell at a recommended price of just £169, the firm has every reason to expect success. How has the necessary cost reduction been achieved? First there's a 25 per cent reduction in the component count in comparison to the TX9 – from 410 parts to less than 300. Secondly the chassis has been designed for 75 per cent automatic component insertion initially, rising to 90 per cent when all the robots have been installed at the Gosport plant. Thirdly there's economic arrangement of the chassis and circuitry, with a reduction in scan power of some 20 per cent. There's also a weight saving of 8lb.

The new chassis has been designed specifically to drive a narrow-neck 14in. tube. The chassis is mounted vertically at the left-hand side, and the user controls are all mounted on the main panel. The latter technique, which is also used in the 1790 monochrome portable chassis (see February 1983 *Television*), eliminates the need for a separate control panel with expensive interconnecting plugs/sockets and leads. A version with remote control (Model 37141) is expected to follow in the autumn.

Thorn are also planning to introduce a "unit video" system based on the TX9 chassis. This would consist of a stereo version of the TX9 with separate speakers, a VCR, and a remote control unit for both the TV set and the VCR. The aim is a popular, rather than semi-professional, unit system.

AERIALS LEAFLET

A leaflet giving guidance on wideband u.h.f. aerials is available from South West Aerial Systems, 10 Old Boundary Road, Shaftesbury, Dorset – send a stamped, addressed envelope with requests. The leaflet is a reprint, with minor amendments, of an article by Roger Bunney that originally appeared in our August 1982 issue.

8mm VIDEO

The March meeting in Tokyo on an 8mm video standard agreed on technical standards for the audio signal but left the video signal processing system for more detailed discussion. The meeting was attended by the five leading signatories (Hitachi, JVC, Matsushita, Philips and Sony) of the group attempting to establish a world standard for the system. The Japanese companies agreed that 8mm

video equipment is unlikely to be on the market before the spring of 1984.

HIRWAUN STRIKE

Production staff at the joint GEC-Hitachi TV plant at Hirwaun, South Wales have returned to work after a five-day stoppage in protest over a pay standstill for a third consecutive year and a cut of £6-£7 a week in bonus payments. The plant has been making a loss for the past six years, and recorded its largest ever loss of £5.2 million in the year to March 31st, 1982. There were 800 redundancies last year as part of an attempt to cut costs by 25 per cent – the present workforce is 1,200.

Just four years ago Hitachi joined forces with GEC to re-equip and modernise the plant, increasing production capacity from 150,000 to 300,000 sets a year, but despite boom conditions generally the factory was operating on short-time for a period last year. One of the problems is thought to be the amount of in-house component manufacture.

Meanwhile Toshiba are planning to double CTV production at Plymouth to 160,000 sets a year. VCR production is also under consideration but has been deferred due to uncertainty over the Japanese-EEC VCR import limitation agreement. Hitachi plan to start producing VCRs at Landsberg, W. Germany, this October, at an initial rate of 60,000 units a year.

PORTABLE VIDEO EQUIPMENT

Ferguson have introduced a portable video camera/recorder combination using the VHS-C system. The Ferguson Videostar C video system, Model 3V40, consists of a compact VCR weighing only 5.3lb and a colour camera weighing just 2.75lb. The camera uses a half-inch Saticon tube which can operate at light levels down to 30 lux. The camera's power consumption is 5.5W and the electronic viewfinder acts as a monitor for instant review. A shoulder-mounting carrier is available so that the camera, recorder and power pack can be combined as a single shoulder-operated assembly. There's an extensive range of accessories designed to offer the user the opportunity to exploit to the full the various possible uses of the equipment. An all-in price of around £1,000 is suggested.

A similar portable video system has been introduced by NordMende.

The latest video camera introduced by Hitachi, Model VKC2000, is of interest in using a solid-state image sensor of the MOS type instead of a tube. This has enabled the weight, compared to previous Hitachi models, to be reduced to about 3.75lb. The use of an intricate colour filter is said to greatly improve the colour reproduction. Other performance figures are signal-to-noise ratio better than 45dB and a horizontal resolution of about 300 lines. Consumption is 5.3W on record, 0.1W on standby. An advantage with a solid-state image sensor is that there is no burn-in problem when the camera is pointed at a strong light source.

BOOK NOTICE

Bernard Babani (Publishing) Ltd. have published "An Introduction to Video" by David K. Matthewson. The 86-page book, reference number BP100, is priced at £1.95 and should be available from the larger branches of W.H. Smith and Son Ltd., component shops etc. It provides a basic guide to the whole range of video equipment, with information on the development of the various systems and some useful reference material.

Routine TV Receiver Tests: Thorn 9600 Series Chassis

S. Simon

The Thorn 9000 chassis, which we dealt with last month, was designed to drive 90° PIL tubes. It featured what Thorn call a Syclops transistor, which drives both the chopper and line output transformers. To drive 110° PIL tubes Thorn designed the 9600 chassis, which reverts to the use of separate chopper (VT512) and line output (VT801) transistors. The chopper circuit has its own driver stage, employing transistor VT511, but the line output transistor is driven by a secondary winding on the chopper transformer. The two sections of the receiver thus continue to operate in conjunction with one another, the line oscillator as before driving the chopper control circuit. Because the line oscillator's supply is obtained from the chopper transformer, a start-up oscillator is required. This is on the chopper control panel and is of the Colpitts type, using transistors VT601/2: this is synchronised by the line oscillator when the start-up sequence has been completed. Fig. 1 shows the basic arrangement of the chopper and line timebase circuits in block diagram form.

The line output stage is on the horizontal board beneath the tube, the power supply board being mounted vertically at the right-hand side. With the chassis slid out in the servicing position, the wing nut that secures the screening cover of the right side power panel can be removed and the cover swung back to reveal the printed board. This enables the mains input to be checked up to the h.t. bridge rectifier, the h.t. reservoir capacitor and the h.t. input to the chopper transistor.

It's worth going into this in a little more detail in order to avoid confusion. The mains input is taken first to a 2.5A anti-surge fuse which is located in a separate holder at the bottom left side. It then goes via a filter unit to the on/off switch and thence via a brown and blue pair of leads to a plug and socket on the left side of the main frame. After this it's taken to the right side plug and socket PL511, then passing to the mains filter capacitor C531, the degaussing components and, via the 3Ω surge limiting resistor R511, the bridge rectifier W525. Thus the a.c. part of the circuit.

Basic Faults

If you find the mains fuse shattered, check C531 and W525 which is a fairly small unit and is suspect. Of the four legs viewed from the print side, the right hand leg is the output to the reservoir capacitor C515. This should read low to the other legs only with the red probe applied to it and the black probe applied to one of the other legs. Reversing the probes should produce a much higher reading. A very low reading in either direction will usually indicate a short in the bridge itself or in the reservoir capacitor C515. We say usually because there are other items across the output of the bridge, including the 1μF capacitor C530 and the chopper transistor itself (with the primary winding of the chopper transformer and its 0.75Ω emitter resistor R522 in series). There are thus several possibilities to consider and to check individually. The chopper transistor is quoted as type T9038V but can be

replaced with the usual BU126 or similar.

In common with more recent chassis, most of the troubles revolve around poor connections or dry-joints. Particularly the latter, which seem to be very common under the centre line output section, especially in the area of the scan coils plug and socket (often accounting for the complaint of a white line down the centre of the screen). One or two of the diodes used in the line output stage are also suspect, chief amongst these being W810 (BY298) in the diode modulator circuit – it seems to get burnt up every now and again. The line scan coupling/correction capacitor C809 (4.7μF) is also suspect and will often be found misshapen due to the effect of internal heat.

It's essential to understand the functions of the three secondary supply fuses in the lower corner of the power supply panel, also the top empty diagnostic socket TSB. The centre fuse F511 (500mA) supplies 34V to the 24V regulator. The output from the top fuse F512 (800mA) is also at 34V: it supplies the field oscillator and output stages and, via R520, the TBA920 sync/line oscillator chip. The lower fuse F513 (500mA) supplies 31V to the audio panel. These fuses are all anti-surge types. The diagnostic socket TSB enables various points on the power supply panel to be monitored.

No Field Scan

If the sound is normal but there's no field scan, slide the chassis out to the service position, remove the wing nut and swing open the power supply panel's screening cover. Refit the earth braiding under the wing nut, then check the voltage at pin 1 of TSB. This should be 34V. If this voltage is absent it's a fair bet that F512 is open-circuit and that 34V will be read at only one side of it. If this is so, switch the set off and measure the resistance between pin 1 of TSB and chassis – black lead to pin 1, red to chassis. If the reading is less than 1kΩ, check the field output stage. The field output transistors are mounted at the front of the main timebase panel. If 34V is recorded at pin 1 of TSB we know that F512 is intact and a check should be made at F511 and at pin 10 (80V rail) of the other diagnostic socket TSA on the main, centre timebase panel. The output from the 24V regulator, which provides one of the feeds to the field timebase, can be monitored at pin 2 of TSA. If F511 is blown, measure the resistance between pin 2 of TSA and chassis – black lead to pin 2, red to chassis. The reading should be not less than 150Ω. If the reading is much lower, check the 24V regulator transistor VT812 and its driver VT813. A study of the circuit diagram will show the voltages to be expected at TSB and TSA.

Dead Set Tests

The drill in the event of a dead set is similar to that just described. The first thing to do is to check the voltage at pin 9 of diagnostic socket TSB. If the chopper is working

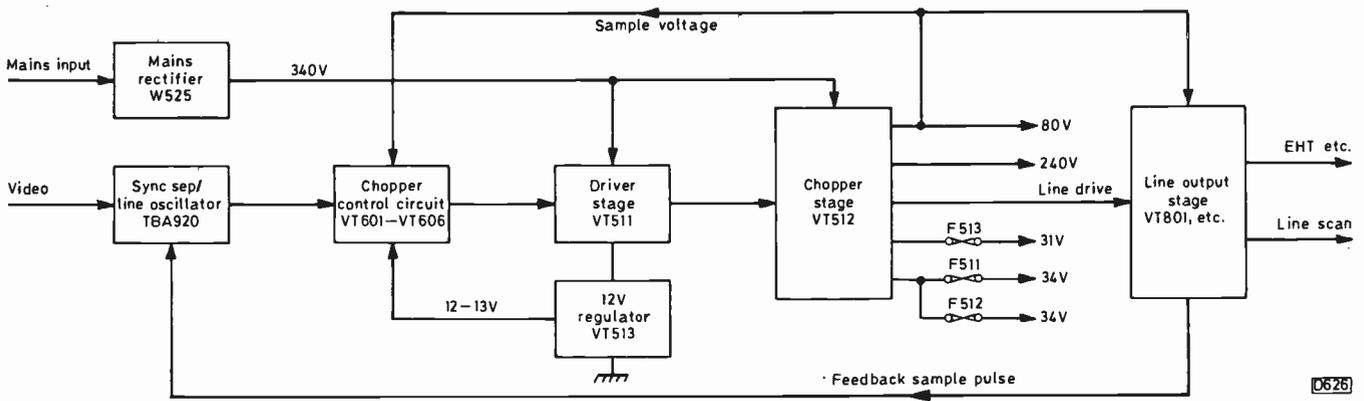


Fig. 1: Power supply/line timebase arrangement used in the Thorn 9600 chassis.

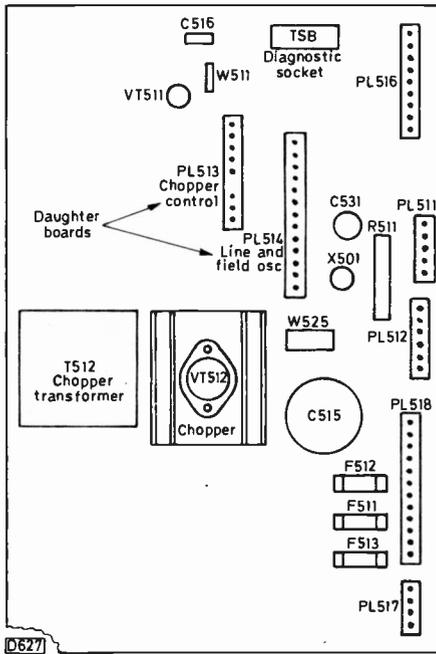


Fig. 2: Items on the right side power supply panel.

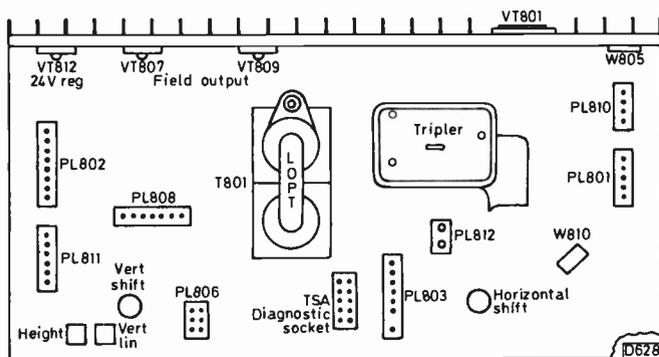


Fig. 3: Main items on the centre horizontal panel, which houses the field and line output stages.

the voltage here should be 580V. Zero voltage suggests an open-circuit between the mains fuse and the chopper circuit, so the circuit to and from the bridge rectifier should be checked. If the voltage is 340V or so the h.t. supply to the chopper circuit is present but the chopper isn't working.

If the voltage at TSB-9 is over 500V, check the 34V and 24V lines as described above.

If the voltage at TSB-9 is about 340V, check for 13V at PL513-2 - this is the supply to the chopper control circuit.

If this voltage is correct, check the chopper drive (see later). If it's low at about 10V, short test point TP601 to chassis. If the voltage rises to 13V, check transistors VT601/2/3. If the voltage is less than 9V, unplug the panel to see whether it rises. If so, check the panel for shorts. If the voltage remains low, check the 12V regulator transistor VT513 and the associated 6.2V zener diodes W529 and W530.

If 340V is present at TSB-9 and 13V at PL513-2, suspect lack of chopper drive. Switch off and allow a minute or so for things to stabilise (capacitors to discharge). Switch the meter to the resistance range and apply the black lead to the collector of the chopper driver transistor VT511 and the red lead to its emitter. If the reading is less than 1k Ω , check VT511 and if necessary W511 and C516. If the reading is over 1k Ω , switch to the voltage range and measure the voltage at the collector of VT511. If, when the set is switched on, the voltage rises to a high value and then falls back to 13V, check the chopper transistor VT512 and the components in its base circuit. If the voltage rises evenly to 13V, there's a fault in the chopper control panel and this should receive close attention. The correct voltage is 82V.

In Conclusion

There are many other check procedures for the 9600 chassis, for example when the set is tripping. Details of these can be found in the field service manual - full data should be to hand if you are going to service any number of these sets.

Such tests are rarely required however, since most fault conditions are due to dry-joints under the timebase panel, a break in the mains supply circuit, or a similarly fairly obvious condition. Unhooking the tripler from the line output transformer is a "must" from time to time, as in most sets, but due to its revised position (away from the metal frame) the tripler in the 9600 does not cause the trouble it does in the 9000 series chassis.

The left side panel contains the tuner and remote control circuit and the audio subpanel. It swings up for service and for access to the signals panel, which is the same as in the 9000 - this swings out for service after the tuner panel has been swung up. As with the power supply panel, a screening plate covers the print side.

Finally, that BY298 diode (W810) in the EW diode modulator circuit. In our opinion the BY298 is not suitable for use in this position. It is our custom to replace it with a BYX71-600, fitting this under the print for convenience, having first correctly identified the cathode connection.

In-circuit Transistor Tester

Alan Willcox

In addition to transistors, the tester to be described also checks diodes and thyristors. The basic principle of the unit is that the device being tested is turned on by a bias from the tester, thereby diverting current from an LED which is thus extinguished. Fig. 1(a) shows the arrangement for checking an npn transistor while Fig. 1(b) shows the equivalent test for a pnp transistor. Reversal of the supply line and of the LED is required in order to test both types. Since it's undesirable to have to operate an npn/pnp switch on an in-circuit tester, the circuit shown in Fig. 1(c) was adopted. The supply line is reversed at about 5Hz, and two LEDs are connected back to back. As it stands, the two LEDs will blink alternately as the supply reverses.

If a good npn transistor is connected, it will conduct on the positive-going supply half cycles, diverting current from LED2 only. LED1 is left flashing. With a good pnp transistor LED1 is extinguished and LED2 continues to flash. The LEDs are thus labelled as shown, so that the LED that continues to flash indicates the type of transistor connected. Both LEDs will continue to flash if the transistor is open-circuit, and both will be off if it's short-circuit.

This basic circuit suffers from certain limitations. For example, if the transistor being tested has a base-emitter or base-collector short-circuit it will act as a diode, conducting on one half cycle and thus extinguishing one LED. This would give an erroneous indication of a good transistor. Also, if there's a low-value resistance across the transistor being tested sufficient current may pass through it to cause both LEDs to turn off, giving an incorrect short-circuit indication.

Diodes are added to the circuit to overcome these drawbacks. Fig. 1(d) shows the set up for testing an npn transistor. The voltage appearing across the collector/

emitter terminals is the forward voltage drop across the LED minus that of the two diodes. This is about 0.4V, which is insufficient to cause a diode connected across the terminals to conduct. The reduced voltage available also means that the tester is less affected by in-circuit resistance – in fact it will tolerate values as low as 50Ω or so before any dimming of the LEDs occurs.

The original circuit before the introduction of the diodes is satisfactory for testing diodes and thyristors with their forward voltage drops of 0.5-1V or so. In the final circuit (see Fig. 2), cancellation of the voltage drops introduced by diodes D1-4 is achieved by supplying power to their junction via R5 when the transistor/diode switch SW2 is in the diode position. For example, on positive half cycles LED2 would be supplied via D3, but if a good diode was connected for test across the collector-emitter terminals the current would be diverted from LED2 via D2: as D2 and D3 are effective in opposite directions, the effect of their voltage drops is cancelled out. If the diode under test was reversed, D4 would conduct on negative half cycles and LED1 would be extinguished.

The diodes could simply be switched out of circuit of course, but the method adopted allows a suitable resistor value (R5) to be switched in at the same time. This lower value ensures that the same tolerance to in-circuit resistance is retained, though at the cost of increased power consumption.

Thyristors can also be tested with the switch in the diode position. To allow for the fact that these are often insensitive devices, gate bias current is supplied from the positive side of the battery via R2. As the gate is not required to be negative with respect to the cathode, reversal of the supply to it is not necessary.

A 556 dual timer i.c. is used to provide supply line reversal at about 5Hz. One section of the i.c. is connected as an astable oscillator with R1 and C1 the timing components. C1 is charged and discharged from the output at pin 9 via R1. The other section of the i.c. has its trigger and threshold inputs (pins 2 and 6) connected to pin 9, with the result that its output at pin 5 follows the square wave present at pin 9 but with reversed polarity. When internal voltage drops are taken into account, the net result is a 14V peak-to-peak squarewave between pins 5 and 9. This forms the supply for the rest of the circuit.

Construction

The PCB is small enough to fit into almost any case that will accommodate the battery, but a larger case will allow for the inclusion of test sockets. The smaller prototype was built into a hand controller box which will take a PP3 battery once some internal struts have been cut away.

The probes consist of short lengths of plastic-covered curtain wire supported in a section of 5A strip connector (an idea suggested by J. Bloor in a letter in the April 1978 issue). Dart points were filed down to a push fit in the ends of the wire, the assembly being bolted to the bottom of the case through the hole in the connecting strip.

The miniature red LEDs were simply push fit and

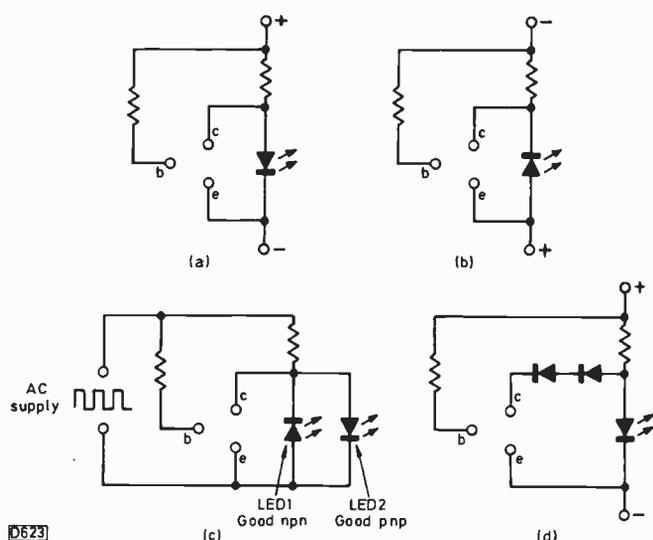


Fig. 1: Basic principles. (a) Arrangement for npn transistors. (b) Arrangement for pnp transistors. (c) Arrangement for testing both types automatically. (d) Addition of two diodes to ensure that only the low saturation voltage of a good transistor will extinguish the LED.

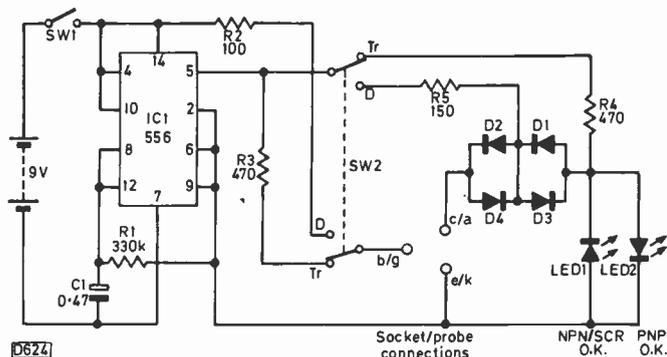


Fig. 2: Complete circuit. Diodes are tested by being connected across the collector-emitter terminals.

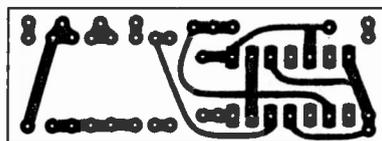


Fig. 3: Printed board layout - 1:1 scale.

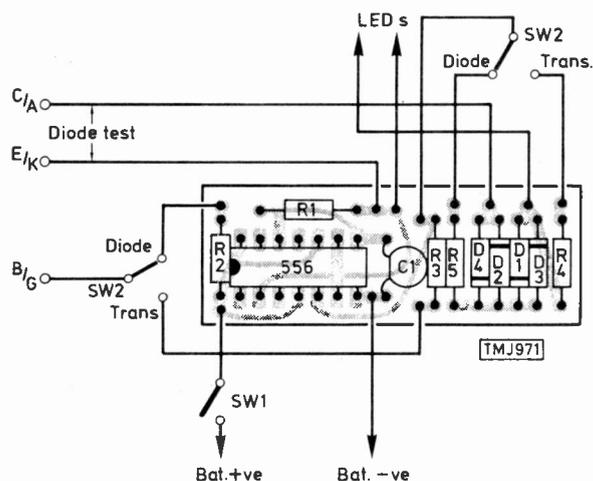


Fig. 4: Component layout.

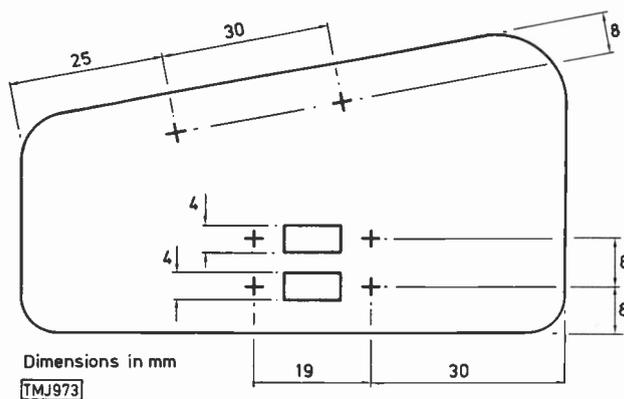


Fig. 5: Small case details.

secured with a spot of glue. The PCB itself is secured with an adhesive pad. The larger version has a red and a green 0.2in. LED, both mounted in holders. The battery is fixed to the case bottom with an adhesive pad.

Tests

Table 1 lists the main possibilities that may be encountered in operation. One LED flashing generally indicates a good device. One of the exceptions is when two diodes are

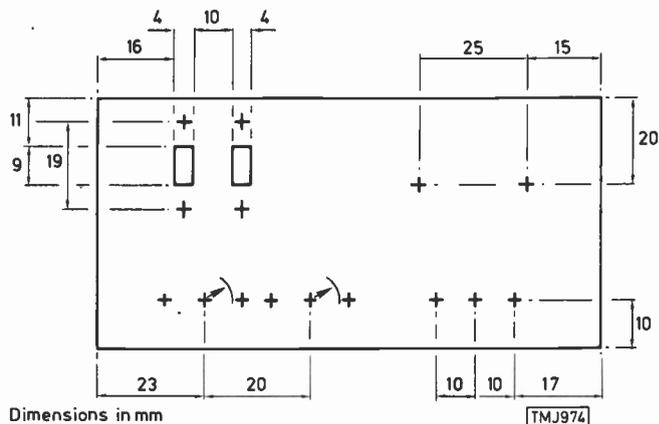


Fig. 6: Large case details.

connected back to back. In this case current flows on both half cycles, turning off both LEDs. If this action is in fact due to normal diode current, this will be confirmed by switching to the transistor test position, whereupon both LEDs will turn on again. If they stay off, at least one of the diodes is short-circuit.

Another example is when testing a thyristor which has either an integral or external diode across its anode and cathode connections. Here again current flow is in two directions, positive half cycles through the thyristor and negative half cycles through the associated diode. Now if the thyristor is good, removal of the gate (base) probe should bring on the pnp LED, the other LED staying off because of the diode across it. In this way both the thyristor and the parallel diode are checked out.

If it's found when using the tester that one LED

Table 1: Test conditions and results

DEVICE CONNECTION	SW2 at #	PNP LED†	NPN LED†	CONCLUSION
	Tr	●	○	Good npn
	Tr	○	●	Good pnp
	Tr	○	○	Faulty: o/c or base s/c
	Tr	●	●	Faulty: c-e s/c
	D	●	○	Good diode ‡
	D	○	●	Good diode ‡
	D	●	●	Switch to transistor
	Tr	○	○	Both diodes good
	Tr	●	●	One or both s/c
	D	●	○	Good thyristor ‡
	D	●	●	Now remove base/gate connection. Base disconnected, thyristor and diode O.K.—see text

* Tr = transistor. D = diode/thyristor (SCR)

† ● = off ○ = flashing

‡ S/c and o/c conditions as for transistors

0625

extinguishes while the other dims somewhat, this would indicate a suspect device – unless there is an unusual circuit configuration.

In Conclusion

Although the tester is basically a go/no go checker, the majority of semiconductor device faults in fact fall within this category. Its main virtues are that it is quick and simple to use, giving rapid indication of transistor types, diode polarity, etc., while possessing good immunity to in-circuit conditions. More subtle faults caused by semiconductor devices not being quite up to specification, e.g. low gain and so on, would require a different fault-finding procedure anyway.

Finally, I've a number of the smaller, hand controller boxes etched as per the prototype (see front cover)

Components list

R1	330k Ω	SW1, SW2 Miniature double pole
R2	100 Ω	Battery PP3 alkaline
R3	470 Ω	
R4	470 Ω	Small version:
R5	150 Ω	1799 Verocase hand controller
All $\frac{1}{2}$ W carbon		with RS 586-447 miniature
film 5%		LEDs (LED1-2)
C1	0.47 μ F	Large version:
tantalum bead		RS509-282 Verocase (100 ×
D1-4	1N4004 or	50 × 40mm.) with 0.2in.
	BA148	LEDs. LED1 green RS
IC1	556	587-838, LED2 red
		RS 587-822

available at £1 each on a first come, first served basis from 33 Hill Rise, Llanedeyrn, Cardiff.

TV Rental

Tony Thompson

There's money and satisfaction to be gained from running a TV rental service. That's a fact, and if you need convincing a look at the number of national outlets, many specialising in rental only, along any high street should be proof enough. These are the big league however, with glossy showrooms, corporate image, massive advertising campaigns and high-technology products, the whole served with considerable style. You can't hope to compete with them in the new set rental market, with their capital expenditure and block discounting, but you can join in by looking for subscribers in the areas where the big guns are weakest – the so-called decontrolled set field.

Those who rent sets in this sector of the market have as their main reasons for doing so (1) the fact that the initial deposit is limited to one month in advance, i.e. no deposit rental, and (2) the fact that the rates are usually lower than with new sets. If you check, you'll find that the major companies make little distinction in their charges between new and not so new sets – the overheads remain the same whatever the set.

Legal Aspects

A number of things have to be done before embarking on a rental scheme, however limited its scale. First, a licence from the Office of Fair Trading is required. This is in fact a licence to offer credit, since that's precisely what you'll be doing. This costs, for a sole trader part or full time, in the region of £90 – about double this amount if you are in partnership. All this for what is bound to start as a mere handful of sets! It will take a few weeks for the department to check you out (they do this before issuing a licence), and it's a waste of time phoning them in an attempt to speed things up. You'll get it when they are good and ready: estimate a couple of months . . .

Once you have the licence you can start to plan the operation. Are you going to work alone or with a partner – or at least someone who is willing and able to help out at least some of the time? Working in partnership with another engineer can be very convenient, as days off are easier to organise, similarly holidays. But there are inherent difficulties too. Financing the scheme for a start. Who

pays for what and when? Who's phone number do you use for adverts? Remember that BT consider that any telephone number used in trade advertising is a business line, and is thus subject to the higher business rate. To be legal you must inform British Telecom – and if you don't, someone else probably will. Another point must be made about partnerships, though it should be obvious: halving the work also halves the individual's profit from the venture.

Your advertisements should make clear that the sets will be demonstrated in the prospective renter's home, unless you've a shop or other trade premises from which to work. This neatly sidesteps the thorny subject of trading from a private address, something that many local councils – and some neighbours – find irritating.

Insurance for the small or part-time businessman can be an expensive affair, yet the fact that you will be putting complex electronic equipment into your renters' homes must be taken into account. Your vehicle may also require modified insurance to cover its use for business purposes, though this need not necessarily involve expense. And finally, legally correct rental agreement forms are essential. Willow Vale amongst others can supply these.

Be Businesslike

It's worth being businesslike – after all, it's a business you're running! You should keep books: a simple income/expenditure type will suffice. You can obtain the Simplex books from most stationers (ask their advice), or you can use something as inelegant but practical as an exercise book.

Open out at a double page spread and on the left chart your income with dates, on the right the same with your expenditure. Use one double page spread a month initially. Keep all bills safely. If you're starting from the ground up you needn't worry about VAT, at least to begin with. Keep a weather eye on your turnover however: presently, if this exceeds £5,000 in any quarter, that quarter is liable to VAT charges. If you get caught unawares you may find yourself paying VAT twice on some goods as, not being registered, you will have paid the VAT upon purchase but you will have to pay it again upon compulsory registration! Remember that the figure quoted refers to turnover, *not* profit! It's worth a chat with a sympathetic accountant, if only to allay any doubts.

Keeping tabs on your renters can be a problem. I suggest that a simple method is to use a card index, again

available from stationers, and using the day of the month as a filing system. Ensure that your renters pay on the date each month. This system works well for a small scale operation, though it's obviously capable of improvement.

Obtaining Sets

There are plenty of sets about, but beware! Many older sets, offered at apparently attractive prices, are unsuited to the purpose we have in mind. My advice is to purchase only solid-state chassis, and as modern as possible. I admit that there are some stylish and fairly reliable valved chassis about, but they are ageing and, as the cost of replacement valves continues to rise, they don't represent a good prospect for long-term rental use.

If you opt to obtain a few sets at a time you may well have to "cash and carry" them from trade sources. These may be many miles from your location, and wasted journeys (in terms of both time and money) are sometimes inevitable. Don't be tempted to buy at all costs just because you've covered a lot of ground getting there. Sigh and keep on looking. If you can find a source through recommendation you will be well advised to use it. Remember that tubes are all too easy to boost undetectably and may well fail on you in a matter of weeks, damaging your profit, reputation and faith in human nature . . . As a start, check around the advertisers in this magazine. And when buying non-workers, check each one carefully for completeness.

Which Sets to Choose?

We all have our preferences about particular chassis, and I'll try not to influence you on this score. By and large however, sets with varicap tuners are preferable to those with the more clumsy mechanical types. But don't go in for touch tune types, especially not the GEC ones, unless you're prepared to fit replacement light-action types. And don't buy ultrasonic remote control sets.

Chassis using the later generation of high-voltage line output transistors (BU208 etc.) are preferable to earlier solid-state chassis. This does, I'm afraid, rule out the ubiquitous Thorn 3000/3500 series – good as they were in their day, they are now getting long in the tooth and good examples with a worthwhile span of trouble-free life still to be expected are becoming rare.

Another thing to consider when purchasing stock is the availability of stands. Most renters will require one. Your best bet is to purchase a batch of adjustable trolley types. These can be attached to most cabinets, though you will probably have to take the feet off first – assuming the feet are still attached! Plastic cabinets pose a problem. With some, the only way to attach a stand is by means of the correct short metal screws. The accent here is on "short" – metal trolleys are conductive.

It's worth remembering that certain parts of sets take a lot of hammer over the years, even in normal use, and it's these parts that you may have to find replacements for – the kind of things I have in mind are the tuner control panel, on/off switches, slider potentiometers, the aerial socket, and of course the knobs themselves.

Whatever you buy, the aim is to get at least two or three years' relatively trouble free service. For this reason, the cheapest initially may not turn out to be so in the end.

Whichever sets you opt for, it's wise to limit your selection to say one or two chassis. This makes servicing much easier, especially if you choose the types (mainly

British) with easily replaceable panels. You can then minimise the time spent in the subscriber's home by carrying a set of serviceable panels that can be maintained during slack periods.

Obtaining Customers

If you've no shop and are working part time, in the evenings, your advertising should stress "NO DEPOSIT COLOUR TV, ONLY £XX.XX MONTHLY. For prompt installation or free home demonstration THIS EVENING, phone . . ." I don't advise offering a free trial as this will mean leaving the set, perhaps for several days. They'll know if they want it once you've demonstrated it – if they don't they won't after a week either.

You can advertise in a local paper, but display advertisements are expensive and frankly unlikely to yield a quick return. A card in the window of a local shop can be just as effective, or more so, at a fraction of the cost. Another good method is to put leaflets through letterboxes. This is particularly effective if you're pushing other lines, such as repairs and sales or aerial work. Such leaflets, often regarded as the poor man's method, can pay long term dividends. Folk often stick them behind the clock on the mantel shelf and fish them out a year or so later.

Some Pitfalls

The bad payer is always with us, and unfortunately you're bound to attract some of these. They'll already have done the rounds of the major firms, who will have repossessed their sets due to the accumulated debts: now it's your turn. How to spot them? Intuition helps, but if you are weak on this sort of thing, as most of us are, it helps to have built-in safeguards.

One technique is to insist on payment by standing order, which is common enough these days. Fill out the form at the time of installation, and post it to the bank yourself. To be certain that the bank will carry out this type of instruction, the renter must have a current account. The form itself can be a simple affair, duplicated from your typed original by photocopying. The wording should be along the lines: "To Bank,(address). Please make monthly payments FROM the account of, account number, the amount of £XX.XX, TO the account of Rentals, Bank, (address). First payment to be on . . ." Leave a space for their signature – both signatures will be needed if the account is a joint one. If the prospective renter has an account but is unwilling to sign such a perfectly acceptable document, you can draw your own conclusions.

Another problem arises when people some distance away rent your sets. My area for example consists of a small market town with numerous villages and hamlets ten or more miles out, plus lots of remote farmsteads. The reliability of your sets is crucial if you are to be cost effective on long-range installations. A breakdown every month or so can be crippling financially, especially at the beginning when every penny counts.

It's been my experience that the older folk are the most reliable payers. It's to these if to anyone that you can issue a small payment card, being reasonably sure that they'll come along regularly. You need patience with this type of customer however. The older folk are often lonely, and tend to keep you trapped whilst the kettle boils, unmindful of your crowded schedule. They can natter, too. At the

other extreme it's been my sad experience that some young married couples and single men make doubtful propositions. Some simply forget to pay, others have no intention of doing so. Stick to standing orders where you can, and bear in mind that the above comments are only generalisations, which are always dangerous.

Servicing Aspects

You'll need manuals or at least circuit diagrams for each type of set you have out on rental. A fair selection of spares should also be carried, including the major valves if you have hybrid chassis, at least a couple of e.h.t. trays (the universal ones if your sets suit), tuner units, aerial sockets, on/off switches, one or more line output transformers, fuses, crystals and the usual assortment of dropers, resistors, small electrolytics and semiconductor devices. Electrolytics present a problem: they do age when simply left, and are rather expensive. It's best to replace them when doing your initial service, prior to installation.

This initial service must be thorough if you are to minimise the failure rate and customer dissatisfaction. I start by cleaning out all debris and dust, with paintbrush and vacuum, then carry out a careful inspection. Cabinets can be tidied up at this point (see my article on Cabinet Renovation in the January 1983 issue). Clean and lubricate all variable resistors and user adjustable presets with Servisol or similar switch cleaner, but don't use this on the mains switch. If this item is rough or uncertain in operation, replace it. Make sure that the mains filter capacitor is in place: if missing, fit one rated at 1kV at least.

Check all presets on the timebase panels, especially the

height and linearity potentiometers, using a spot of switch cleaner or replacing the component as necessary. Check for dry-joints, first visually on the power and timebase panels then, whilst observing the picture, by gentle tapping on the video, chroma, i.f. and tuner panels. Clean dust away from the c.r.t. base panel, checking the spark gaps especially.

You may well find that certain potentiometers on the convergence panel are in an advanced state of decay. These tend to work hard, and replacements should of course be heavy-duty wirewound types.

The main thing is to be thorough and give each set a soak test. When carrying out the installation it's useful to have with you some mains plugs, including the older 5A round pin type, and a few coaxial plugs.

In Conclusion

Running an efficient rental organisation is no picnic. It demands skill and knowledge and, at least to start with, quite a lot of groundwork. There's also the initial outlay, both in terms of time and money, little of which is likely to return quickly – it must be looked upon as a medium-term investment. It's not an easy way to riches, but can make a worthwhile supplement to your earnings, giving an extra string to your bow and a satisfying outlet for your skill.

Finally, rental forms (see earlier) can be obtained from Willow Vale Electronics Ltd, Old Hall Works, Shinfield, Reading, Berks. Literature explaining licence requirements is available from the Office of Fair Trading, Consumer Credit Branch, Bromyard Avenue, London W3.

B & O Tripler Conversion

Keith Cummins

DISASTER struck one evening. The Beovision 2600 had no picture and smoke was emerging from the back. A quick check showed that the e.h.t. transformer's overwinding was overheating – the result of shorted turns. For those not familiar with this particular chassis (90° hybrid) I should perhaps mention that there are separate, linked line output and e.h.t. generator stages, each with its own output transformer. This means that a superbly regulated e.h.t. is provided.

The e.h.t. transformer has always been an expensive item, and now appears to be obsolete. Being reluctant to write off what has always been a very good receiver, I decided to investigate the possibility of using an e.h.t. tripler.

Modification Details

The e.h.t. transformer was removed and the overwinding clamped in a vice. Then, using a hacksaw, I cut down through the overwinding until the saw was just nibbling the ferrite core. Twisting a screwdriver in the slot thus produced cracked the overwinding into two parts. The leads were unsoldered and the whole overwinding was opened out and withdrawn from the core. The third

harmonic tuning coil and an 0.01 μ F capacitor were also removed, so that the transformer was left with just the windings on the opposite leg of the core.

Having done this I replaced the transformer and reconnected those parts remaining. Upon switching the set on, the expected healthy sparks could be drawn from the top caps of the PL509 and PY500A valves, using an insulated screwdriver, thus indicating that the primary winding was operating normally.

There's a pulse of some 8kV at the top cap of the PL509, and the use of a tripler would increase this to 24kV for the c.r.t. The GY501 e.h.t. rectifier and its base were removed, and an ITT replacement tripler, type TS30-11THV, was fitted to the inside of the e.h.t. enclosure just above where the GY501 had been situated.

Fig. 1 shows the connections. The tripler's grey input lead is driven from the anode of the PL509 while the black lead is taken to pin 3 of the transformer – this is the boost voltage point and has the grey leads from the receiver attached to it. Since the focus voltage in this chassis is produced by a separate rectifier driven by the line output stage, the tripler's white focus lead was cut short and sleeved. The red e.h.t. lead was cut and joined to the original lead to the c.r.t., then heavily insulated – this maintains the capacitive feedback used to improve the regulation in these sets. The mauve lead which emerges from the receiver's cableform and goes to the earthy end of the overwinding was cut back to the loom and sleeved, being no longer required.

Both the e.h.t. max and min potentiometers should be rotated fully clockwise (minimum position when observed from the component side of the board). The e.h.t. max potentiometer should be left in this position and not touched again.

Fidelity VCR

A couple of months ago I mentioned the Fidelity VCR, saying that it uses the mechanics from the Hitachi VT8000 series. I've subsequently found that it suffers from the same problem, that of looping the tape at the end of rewind, and consequently requires the same modification, i.e. filing the brake arm (see page 15, November 1982 *Television*). As the electronics differ from the Hitachi machines the electrical modification is not possible. D.S.

Hitachi VT8000

The symptom with an Hitachi VT8000 was that the clock worked but the operate light would not come on and none of the functions worked. A quick check showed that the 15V and 9V rails were not being switched on, though the 18V rail was present! A check at pin 2 (power control) of the microcomputer on the system control panel showed that this device was providing the correct output to switch the power supply on, but a meter check at the collector of the following transistor Q051 produced a reading of zero instead of 16.5V. Checks in the collector circuit of this transistor then revealed that R054 and R055 were open-circuit whilst the 16V zener diode ZD051 was short-circuit. It's amazing how many faults in these machines are due to zener diodes. D.S.

Sanyo VTC9300P

An interesting point arose with a Sanyo VTC9300P I repaired. The original fault was that the machine stopped a few seconds after the play key was pressed though the other functions worked perfectly. A quick inspection showed that the tape was not moving in the play mode because the pinch wheel was not being pulled in by the solenoid. This is operated by a high current via Q810 and is then held in by a small holding current via Q816. If the centre was pushed into the solenoid by hand it held there, showing that the fault was in the pull-in rather than the hold-in part of the circuit – in fact Q810 was open-circuit. I thought that this was the end of the matter – a quick test then back to the customer.

Next day he phoned to say that the machine was dead except for the clock. Just my luck I thought: the 12V regulator transistor would pick this moment to fail. When I got there however I found that although the power light did not come on neither did the wait light when switched to timer, though it will when the regulator transistor fails.

I decided to check the fuses on the power supply panel and found that the first one, F701, was faulty, though you needed good eyesight to spot the break. In with a replacement and the machine was once more o.k. As this fuse is one of the two in the 17V supply, which feeds Q810, I thought that it had been strained by the failure of that transistor and had just waited for an hour or so to fail. Next day however the customer reported that the machine had worked for just forty minutes and then stopped.

Back at the house I decided to check the fuses again. The one I'd fitted the previous day had been of the mica filled variety, which means you have to check it with a

meter, so being idle I decided to check the other one (F702) in the 17V supply first. Sure enough there was a small break in the wire, a replacement restoring normal operation. I came to the conclusion that they'd both been strained and that I should have replaced the two of them at the same time.

Next day the same thing happened again of course, so I lent him a machine and took the 9300 back to the workshop. There I had the brainwave I should have had at the house. Check *both* fuses: both faulty. It turns out that in this machine if either F701 or F702 (they each feed one of the two diodes in a full-wave rectifier circuit) goes open-circuit the machine will continue to work normally but the current flowing through the remaining fuse will be so close to its failure current that it will fail after 30-40 minutes. I've since taken one of these fuses out of a working machine whilst it was playing and was unable to see any noticeable effect despite the 17V supply coming from a half-wave instead of a full-wave rectifier. So be warned! D.S.

Ferguson 3V29

A Ferguson 3V29 replayed prerecorded tapes normally. In the E-to-E mode however the sound was accompanied by a continuous harsh buzz which, unlike the early u.h.f. TV receiver intercarrier buzz problem, was relatively unaffected by the picture content or fine adjustment of the VCR tuning presets. For this reason vision i.f. response problems were not suspected and attention was directed to the sound i.f. section.

Amplification/limiting/detection is carried out by IC2. The 6MHz input enters at pin 8 and the audio output appears at pin 4. The input level appeared to be correct, but in addition to the audio output a combination of line and field rate pulses was present at pin 4. This led us to investigate the muting circuit (see Fig. 1), which operates during channel change or signal loss.

The composite video signal from the i.f. strip is fed to the base of Q10, the positive-going tips of the sync pulses triggering Q10. As a result, a line frequency sinewave is produced at its collector. This is coupled to the base of Q11 by C46, with d.c. restoration by D11, and as a result Q11 is saturated during viewable display conditions, the voltage across C47 falling to only 0.1V. Should the r.f. input signal be lost or an untuned channel selector button be depressed, there's no input to Q10 and Q11 and the

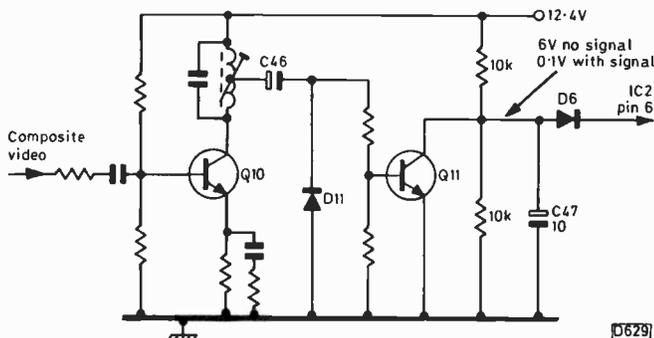


Fig. 1: Sound muting circuit, Ferguson 3V29.

voltage across C47 rises to 6V. This is applied to pin 6 of IC2 to mute the sound. The problem was that C47 was open-circuit, as a result of which the audio signal was being subjected to a sync-rate disturbance. **P.H.D.**

Toshiba V8600

The problem we had with a Toshiba V8600 was tuning drift, and on checking the voltage at the 32V regulator zener diode D004 we found that this was low at only 30V. This voltage comes from a voltage doubler via the stabiliser transistor Q811 on the line filter board. There should be 56V at the collector of this transistor, 48V at its base and 47.4V at its emitter, the base bias being set by two zener diodes (D814/5) and a further diode D816. One of the zener diodes (D815) proved to be leaky. **L.H.**

ITT TR3913A

The ITT TR3913A is very similar to the Ferguson 3V29. The trouble we had on one of these machines was that whilst the picture was o.k. in the E-to-E mode on playback (test tape) the frequency gratings were tearing very badly. The playback f.m. waveform was found to be very "spiky", and whilst making voltage checks around the HA11724 preamplifier etc. i.e. we found that pin 13, which is fed from the E-to-E 9V rail, was at 0.65V instead of zero volts as it should be on playback. We suspected the mode control transistor Q102 since this controls the E-to-E 9V rail, but the 0.65V was present even with Q102 removed from the board. The fault was eventually traced to D407 in the colour circuit being leaky! **L.H.**

Sony C7

The fault we had with a Sony C7 was that the test signal was showing in the play mode. When the test signal switch is operated, the voltage at pin 8 of connector CN1008 on the video panel should be 12V. At other times the voltage here should be 0V. In fact the voltage on the "test 12V" line was 12V during play as well, due to D41 being leaky (disconnecting D41 restored a normal playback signal). Replacing D41 cured the trouble. **M.S.**

Sony C6

The trouble with a Sony C6 was that it would unthread but wouldn't always eject. After making myself dizzy watching the machine thread and unthread I eventually got it to stay in the fault condition. Shorting out the cassette off switch ejected the tape, and on examining the switch I found that the spring had weakened. As a result it sometimes didn't switch over. Replacing the switch and setting up cured the fault. **M.S.**

Mitsubishi HS300B

A Mitsubishi HS300B - an oldie but a goodie - caused us premature greyness recently. The complaint was that very occasionally the machine would refuse to respond to the front panel controls when a tape was loaded. Over a period of about a week we gradually pieced together the following story. First we discovered that the fault occurred only when the tape was at the beginning. This suggested that we should take a look at the start sensor and its associated circuitry, see Fig. 2. Sure enough we found that the fault disappeared when the start sensor phototransistor

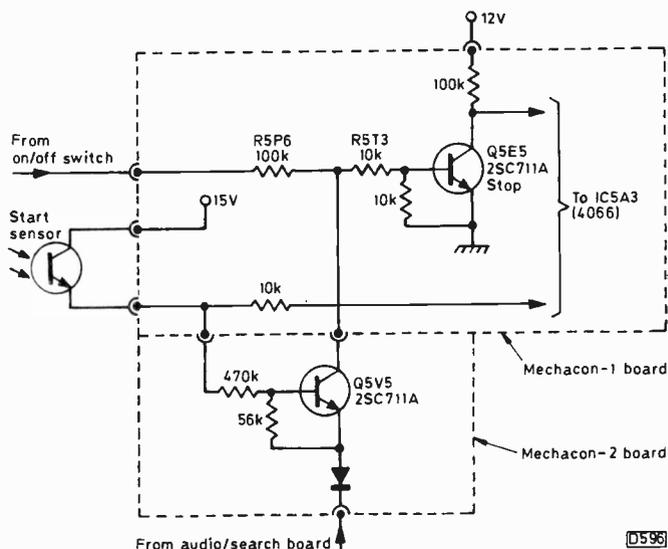


Fig. 2: Start sensor circuit, Mitsubishi HS300B.

was blanked off. The transistor itself seemed to be working correctly, so we went on to check the gate circuit it controls. This is part of a 4066 chip (IC5A3) on the mechacon-1 board. We've had trouble with this type of chip before, but in this case the action was correct. Whilst checking this chip however we discovered that another gate control signal, from the collector of transistor Q5E5, was high when it should have been low. Q5E5 is turned on by a voltage from the front panel on/off switch, via resistors R5P6 and R5T3. The switch-on voltage was being lost at the junction of these two resistors, a point which is also connected to transistor Q5V5 on the machacon-2 board.

The machacon-2 board is unfortunately buried under the capstan motor and a large bundle of cable. It's almost impossible to get at (0 out of 10 for Mitsubishi design here), and is secured to the chassis by the motor drive transistor's heatsink. When we burrowed under all this we discovered that the cable run had pushed Q5V5 over, with the result that its emitter was just touching the heatsink. This was the final link in the chain. Q5V5 is turned on and off by the start sensor transistor. Under normal stop conditions it's base is at a positive voltage but its emitter is floating. Under certain conditions its emitter is pulled down by circuitry on the audio/search board, but with the emitter touching the earthed heatsink this point was at zero voltage even under normal stop conditions.

This possibility is now on our checklist for these machines, and in one or two instances the effort has clearly been just in time. **R.R.**

Sony C6

Here are a couple of faults we've had with the Sony C6UB. First the 3.15A fuse F001 blowing instantly. This was due to a short-circuit in the r.f. converter - an r.f. trimmer capacitor lead had dropped off, shorting the l.t. supply. The offending trimmer is in a subassembly in the converter. It can be repaired or, more expensively, the complete unit can be replaced.

The second fault we had was no fast forward or forward search, though all the other operations were o.k. The trouble was that the fast forward solenoid drive start transistor Q025 was leaky. It's a special Sony Darlington, type 2SD1164. **M.S.B.**

Long-Distance Television

Roger Bunney

March produced another excellent tropospheric opening, from the 7th through to the 9th, with another minor event on the 12th. With the approach of the Sporadic E season (usually around the second week of May), there's been an increasing incidence of short-lived Band I signals – stronger than the usual MS (meteor scatter) pings and of longer duration, at times up to half a minute. SpE signals should be with us again by the time these words are read, though some of the familiar Band I signals will be absent – as previously reported, DFF (E. Germany) ch. E3, YLE (Finland) ch. E2 and SR-1 (Sweden) ch. E4 (Finnveden) have now closed.

The event on the 12th was an aurora from 1530-2100, producing Band I activity. Slight auroral activity was also noted on the 25th and 28th, but in the far north only.

Here at Romsey, Hants, tropospheric conditions began to build up on the 7th, with Band III being particularly active – signals were received during the evening from the low countries and W. Germany. I found the morning of the 8th perhaps best, with many W. German Band III/u.h.f. signals, DFF chs. E6 and E34 and, for my location, an excellent long-haul signal from ORF-2 (Austria) on ch. E24. The latter consisted of the PM5544 pattern, which was unfortunately obliterated at 1000 when the local BBC-2 transmitter came on air. Many enthusiasts reported good reception from RTL (Luxembourg) ch. E7 – the new standard B transmitter. Conditions improved again during the evening, giving mainly W. German signals.

During the evening of the 9th there was a more concentrated offering of Band III and u.h.f. signals from Germany, including DFF chs. E5 and 6. The opening came to an end on the 10th – with rain!

A short-lived tropospheric duct occurred on the 12th, giving excellent reception of Swiss Band III and u.h.f. signals in Holland. The signals lasted for some five hours before fading into the noise.

On both the 6th and the 8th I logged ATV signals from G6CPE, G8FAB/A and G6GXG. It later transpired that the signals came from a common transmitter belonging to the Southampton Amateur Radio Club. At a distance of one mile this hardly represents DX reception, but the signals were noise free and confirm that at least one ET021 tuner can cover the 435MHz amateur band (my other two didn't).

My thanks to Cyril Willis (Cambridge), Hugh Cocks (Robertsbridge), Ian Menzies (Aberdeen), Garry Smith (Derby) and Ryn Muntjewerff (Holland) for sending details of their reception.

News Items

Pirate TV: There's been considerable publicity in the press about a pirate TV station operating in the Birmingham area – it calls itself Second City Vision and uses ch. E40 when the local BBC-2 transmitter goes off-air on Friday/Saturday nights. So far there seem to have been only low-

power test transmissions, but some sort of programming is expected. The service area will undoubtedly be small, and could be around Edgbaston.

Seychelles: The Radio-Television Seychelles (RTS) TV service started on December 31st, with PAL colour and some nine hours of programmes at the weekends (Friday-Sunday). Channel information is not known at present.

Turkey: Colour transmissions (PAL) are to start in July.

Band I Allocation Chart

Letters arrive from time to time asking for explanations of ch. E2, R1 etc. In a monthly summary of DX reception it's obviously impossible to give full frequency details of the various channels. In view of recent changes however Table 1 provides an updated Band I/II channel allocation listing – note particularly the French channels.

New readers may not be familiar with SpE, so for these a brief recap. The phenomenon occurs mainly during the summer months, starting in May and continuing through to late August/early September. SpE openings cannot be predicted, but there are various signs when conditions are about to open up. The openings last anything from five minutes to fifteen hours, producing high-level signals from Band I up to some 100MHz (intense openings can produce signals in Band III).

SpE signal propagation is caused by localised or wide-spread intense ionisation in the E layer, some 70 miles above the Earth's surface. The ionisation causes reflection of v.h.f. signals that would otherwise pass through to

Table 1: Band I/II Channel Allocations

Channel	Vision carrier MHz	Sound carrier MHz	System
B1	45	41.5	A
B2	51.75	48.25	A
B3	56.75	53.25	A
B4	61.75	58.25	A
B5	66.75	63.25	A
E2	48.25	53.75	B
E2A	49.75	55.25	B
E3	55.25	60.75	B
E4	62.25	67.75	B
IA*	53.75	59.25	B
IB*	62.25	67.75	B
IC*	82.25	87.75	B
R1	49.75	56.25	D
R2	59.25	65.75	D
R3	77.25	83.75	D
R4	85.25	91.75	D
R5	93.25	99.75	D
F2†	52.4	41.25	E
F3†	65.55	54.4	E
A‡	47.75	41.25	L
B‡	55.75	49.25	L
C‡	64.75	58.25	L
C'‡	63.75	57.25	L
A	45.75	51.75	I
B	53.75	59.75	I
C	61.75	67.75	I
A2	55.25	59.75	M
A3	61.25	65.75	M

* Italian channels.

† Old French channels.

‡ New French channels.

F.M. radio allocations: 66-73MHz E. Europe, 87.5-108MHz W. Europe.

space. Signal reflection occurs over distances of between 450-1,500 miles, but with multiple reflection (if you're lucky!) the distance is extended. The reflected signals can be of sufficient strength for reception with relatively simple equipment – even an indoor dipole can produce excellent results. An upconverter can be used to receive Band I signals with a u.h.f. receiver – simply add a wideband dipole and you're in business.

Space permitting, a Band III update will be included in next month's column.

Commercial News

The newly published BATC booklet "TV for Amateurs" was mentioned in Teletopics last month. I'd just like to add my own recommendation! With some 52 pages it's excellent value at £1.50 plus 25p post and packing.

If you're contemplating the construction of a 5.5MHz system B/G i.f. strip it's worth knowing that 5.5MHz ceramic filters are available from Marco Trading, The Maltings, High Street, Wem, Salop SY4 5EN at 50p each, or three for £1, plus 35p postage and then VAT.

A free leaflet on wideband u.h.f. aerials is available from South West Aerial Systems. It's a reprint, with minor corrections, of an article of mine that appeared in the August 1982 issue. Include a stamped SAE.

The Future of Band I

For many years Band I has been used exclusively for TV. Things are about to change however. The BBC/IBA 405-line services are to close at the end of next year, and various interests are looking at the bandwidths thus to be made available. UK radio amateurs had an allocation at 50MHz from December 1947 to March 1949, so it's hardly surprising that the RSGB is lobbying for the restoration of this. In fact some 40 licenced amateurs throughout the UK have already received permission for test transmissions in the 50-52MHz band outside TV hours, and a beacon at 50.02MHz (GB3SIX, Anglesey) is now in operation.


It looks as if the 50-52MHz spectrum will be given to amateur radio by early 1985. Being h.f. of ch. R1 vision, the band can be filtered out, though the presence of an amateur operating at high power nearby could prove troublesome, calling for good filtering and equipment with good dynamic signal handling performance.

What is becoming an increasing problem is the cordless phone. Approval has been given for operation at 47MHz, but the UK is being swamped by 49MHz types sold as "approved" for UK use. Most have limited coverage, but the Supaphone CT505 is claimed to have a range of 1km. I've personally been dialled from one and have dialled back to a remote unit via its base at some five miles from base, the base using half-wave dipoles cut to 49/71MHz. I've heard that seven miles can be achieved in East Anglia. So this is the equipment that will cause problems – the various channels used for the 49MHz base transmitter cluster around the 49.6-49.9MHz region, right on top of ch. R1. What can one do?

Garry Smith (Derby), writing in Cyril Willis's *DXTV Newsletter*, reports considerable trouble from this source in his area. He's tracked down owners of the illegal equipment by recording the dialling blip clusters on a tape recorder at 7.5 in/sec, then replaying them at a slower speed, counting the blips in each group to find whom the operator is contacting. To locate the operator himself it's usually necessary to monitor the channel in use when a

SOUTH WEST AERIAL SYSTEMS

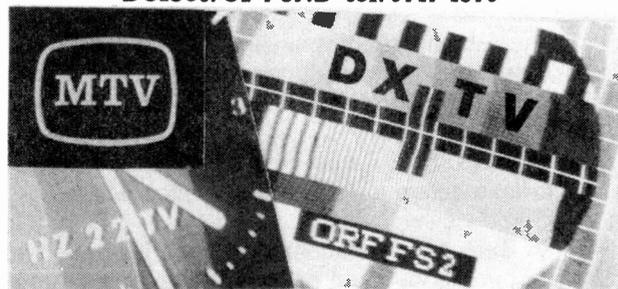10 Old Boundary Road, Shaftesbury,
Dorset. SP7 8ND tel. 0747 4370



As market leaders we supply a comprehensive range of aerial equipment for domestic, fringe, DXing and distribution systems.

We supply a full advisory and after sales backup service.

We supply aerials/equipment for all bands, the big aerials and the small filters – and all the bits in between!

We are active DXers – your guarantee of honest and accurate advice – efficient equipment at competitive prices.

We've listed just some of our DXing aerials below – prices include VAT, packing and Securicor delivery.

S.W.A.S. Wideband Band 1 Aerials 47-68MHz incl. (SAE leaflet)	Wideband Band 3 – 175-230MHz Triax – MTH6 - 6 el., 7.2dB gain	£19.85
WB1 dipole with stub mast	MTH13-13 el., twin refl., high gain 11.9dB	£31.75
WB2 2 element budget array	Jaybeam - Astrabeam 5, 5 el	£19.85
WB3 3 element (very popular)	ABM8-8 el., 9.5dB gain	£25.50
WB4 4 element high gain	ABM11-11 el., 11.6dB gain	£30.50
WB5 crossed dipoles (WB1) for omnidirectional use	Antiference-HC2011R 13 el. twin refl. 11dB gain	£33.25
WB6 as WB5 but with reflectors		

(allow 10-14 days for delivery of stock items)

Combined wideband Band 1/3 Antiference exports available, for details on these and everything else send 54p for 1983 catalogue. Lots of UHF aerials, see next month's advertisement. Access/Barclaycard welcome. SAE all enquiries please and for UHF DXing leaflet.

TV LINE OUTPUT TRANSFORMERS

If the Transformer you require is not listed please phone.

RANK BUSH MURPHY T20a, T22 Pry & Sec 5.51 Z718 Series primary 5.00 Z718 Series EHT overwind 5.00 A774 single std mono 8.50 A816 solid state mono 9.00 Z712 T16a T16b mono portable 9.00 A823 A823b A823av colour 10.00 Z179 Z722 series colour 10.00 Z718 18" series 11.00 Z718 20" 22" 26" series 11.00 T20a T22 series colour 10.00	DECCA MS1700 2001 2020 2401 mono 8.00 MS2404 2420 2424 mono 8.00 1210 1211 1511 portable 11.50 GYPSY portable 11.50 CS1730 1733 colour 8.00 CS1830 1835 colour 8.00 '30' series BRADFORD colour 8.00 80 series colour 8.00 100 series colour 8.00
G.E.C. 2047 to 2105 3112 to 3135 8.00 "GAIETY" FINELINE 8.00 2114 portable mono 8.00 3133 3135 M1501H portable mono 8.00 DUAL STD hybrid colour 11.00 SINGLE STD hybrid colour 10.00 SINGLE STD solid state 90° or 110° 8.50	PHILIPS 210 300 series mono 8.00 320 series solid state mono 8.50 G8 series colour 8.00 G9 series colour 8.50 G11 series colour 14.98
FERGUSON HMV MARCONI 1590 1591 1592 1593 mono 8.00 1612 1613 1712 mono 8.00 1690 1691 mono 8.50 1600 1615 series mono 9.74 3000 3500 EHT or SCAN 8.58	KB-ITT VC200 VC205 VC207 mono 8.00 VC300 VC301 VC302 portable 8.00 CVC1 CVC2 colour 9.00 CVC5 CVC7 CVC8 CVC9 colour 9.00 CVC20 series colour 9.00 CVC30 CVC32 series colour 8.00 CVC40 series 14.56
ADD 15% VAT to ALL prices.	L.O.P.T TESTER Total Price 16.79
Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm. 1.30 to 4.30 pm. Sat 10 am to 12 pm.	Hamond Components (Midland) Ltd., 416 Moseley Road, Birmingham B12 9AX. Phone: 021-440 6144. Mon-Fri 9 am to 1 pm. 2 pm to 5.30 pm.

call is incoming (the dialling tone indicates this). The answer will often reveal either a name or number etc. You can then contact them, report that their total calls are being monitored, and suggest that they obtain an approved 47MHz type from the supplier, using the Sale of Goods act as a lever. Persist if necessary but remain anonymous.

Garry suggests that the normal TV set won't resolve the audio and recommends using a scanner, e.g. an SX200 or the popular Tandy Patrolman 50 (this has been discontinued, though some Tandy shops may still have them in stock). It seems that Radio Services will not be over anxious to take action unless the unit concerned is upsetting a 405-line viewer.

The new Telecommunications Bill, when it's passed and comes into operation, could be the answer. It will amend the 1949/1967 Wireless Telegraphy Acts, increasing the enforcement available. It would seem that any 49MHz apparatus used for transmission will be illegal to operate, own, sell or manufacture, with the police empowered to arrest and search people and property. Those found guilty of such offences would forfeit the illegal equipment.

Such offences were previously known as Summary Offences, but under the new act they'd be tried on indictment at a Crown Court for example, with more severe penalties - maximum fines would rise to £1,000, and those found guilty would carry a criminal record. The Bill should be passed this summer, and will enable you to take action by advising the police.

From our Correspondents . . .

Gosta van der Linden (Holland/BDXC) has sent interesting details of the Moroccan TV service. A system B ch. 34 outlet at Laayoune operates at 180kW e.r.p. and has been well received in the UK via SpE. The PM5544 pattern is transmitted between 1800-1830 GMT, with the identification "RTM" at the bottom and Arabic script at

the top. A portrait of King Hussan II appears at 1830, with a reading from the Koran at 1833. There's a news programme in French at 1915! Arabic programmes last from 1930 until close down at approximately 2330-0015 GMT, preceded with another reading from the Koran.

Bud Lloyd Bennett, who was previously in Saudi Arabia, is now in Northern Nigeria. He reports that with his three-element wideband Band I array and JVC portable he can regularly receive RTM (Morocco) ch. E4 and RTVE (Canary Islands) ch. E3 via night time TE from around 1930 local time onwards. Other stations he receives at times include RTVE Madrid ch. E2 and the Sicilian ch. IA RAI transmitters. Full sound and colour vision is received, though the vision is usually very smeary and with the characteristic multiple images. Local stations are Minna ch. E10, Abuja ch. E5 (170km), and Bida ch. E12 (90km). Kaduna ch. E34 (300km) is received at times. Very weak signals of unknown origin are received on ch. E29. As an interesting aside, 27MHz CB operation is extensively used, due to the remoteness of the site, and it's been possible to work back to the UK on our 40 channels!

Another letter from Gosta van der Linden reports that all NOS (Dutch) TV transmitters are to be equipped with stereo sound facilities, starting with Smilde (ch. E47) and Wieringen (chs. E39/45) this year. The actual transmissions are expected to start in 1985/6. Finnveden SR-1 (Sweden) has now moved to ch. E41 at 1,000kW e.r.p.

Graeme Wilson (Middlesborough) mentions that some cheap and cheerful radios with MW, CB1 (a.m.) and CB2 (f.m.) coverage have come on to the UK market. Graeme's sample, called the Academy AA31, comes from the far east. He says that the 27MHz f.m. section can be realigned to cover 29-32MHz so that the set can be used as an i.f. receiver, with the input from the main tuner taken via an f.e.t. buffer stage. Graeme comments that this arrangement is "very sensitive" - remove the telescopic whip aerial and use the wired connection for the i.f. input.

TV Fault Report

Decca 110 Chassis

The customer's complaint with a Decca Model CV1110 (110 chassis) was that the brightness level had been varying for a while and flyback lines would now appear as the set got warm. We took the set back to the workshop for a soak test, and after being on for a few minutes very small changes in brightness level were visible. The fluctuations were too small to measure however, so we left the set on for a while longer. After a further ten minutes flyback lines began to appear and we were able to measure an increase in the first anode voltage at each of the three guns. The voltages at the "high" side of the first anode presets were nearly 1kV, and there was very little voltage drop across the controls. A check on R913 (22kΩ) at the earthy end of the control network revealed that it was virtually open-circuit, a replacement curing the problem. **M.D.**

Panasonic U1 Chassis

The problem with a National Panasonic Model TC2203 was normal sound but no raster. When the set was

switched on there was a healthy e.h.t. crackle, and on checking the tube base voltages we found that the first anode voltages were present and normal. The cathode voltages were high however.

We operated the service switch and obtained a line across the screen. In the normal mode however the base voltages of the three RGB output transistors were low at 6.2V instead of about 7.8V. The base drives are d.c. coupled from the TDA2530 matrixing/preamplifier i.c. (IC301), and when we checked this i.c.'s supply voltage (pin 9) we found that it was high at 15.4V instead of 11.4V. The supply is taken from the stabilised 12V rail, and on checking at the series regulator transistor Q818 all three legs were at 15V. Two zener diodes (Q818/9) set this transistor's base bias, and D818 turned out to be open-circuit. Replacing this 6.3V zener diode gave correct voltages and restored the picture. **M.D.**

Thorn TX9 Chassis

The fault with a Thorn set fitted with the TX9 chassis was unstable field scanning with black lines on the picture. The field timebase controls all worked correctly, and we suspected internal breakdown in the TDA1170S field timebase i.c. Replacing this made no difference however, so we had to resort to component substitution. The problem was cured when C212 (0.1μF) was replaced - a

check on the original revealed that it was open-circuit. It's in the impedance matching network across the output from the i.c. **M.D.**

Grundig 5010 Series

Intermittent field bounce and occasional field collapse was the problem with a Grundig Model 5012. We found that the fault was heat sensitive and was on the field timebase module. After careful use of freezer and a hairdryer L447 was found to be the culprit – it would alter its resistance with heat, and occasionally go open-circuit. It's in series with the unijunction field oscillator transistor, on the chassis side. **M.D.**

VCR Tuning Problem

We supplied a second-hand Bush colour set fitted with the Z718 chassis, with touch tuning and simple remote control, to a customer who already owned a Ferguson 3V22 VCR. The set was demonstrated in the shop, and we explained how to tune in the VCR. The customer took the set away but phoned a little while later to say that he couldn't get the VCR to work. When we called we found that all four channels being transmitted from Sutton Coldfield could be tuned in correctly, but it was impossible to tune in the output from the VCR (on a lower channel). The problem was eventually traced to the ETT6016 touch tune i.c., replacing this providing a cure. **M.D.**

Philips G8 Chassis

We've had three G8s recently with interesting faults. The problem with the first was flyback lines visible over the top third of the screen when the set was cold, the lines disappearing one by one as the set warmed up. This was eventually traced to C216 (1 μ F) on the combined signals panel. This electrolytic capacitor couples the flyback blanking pulses to pin 8 of the TBA560C i.c. and turned out to be slightly leaky when cold.

The problem with the second set was intermittent power supply flutter. The usual causes were tried – the thyristor, diac and zener diodes, but the fault was eventually traced to breakdown of R1386 (27k Ω) in the trigger pulse charging circuit.

Very intermittent loss of line sync was the problem with the third set – it would run for several days at a time without the fault appearing. Our first suspect was the TBA550Q video/a.g.c./sync i.c., but the fault remained after this had been replaced. It also persisted after fitting exchange i.f. and timebase panels. We eventually found that when the fault was present the feedback pulse to the i.f. panel (flywheel sync circuit) was missing, due to pin 3 on the line output transformer going open-circuit. A new transformer had to be fitted. **M.D.**

Telefunken 712 Chassis

The complaint with a Telefunken set fitted with the 712 chassis was no results. The 4A mains fuse Fu421 had blown and a quick check revealed that the BU208 line output transistor was short-circuit. We replaced these two items and disconnected the tripler in case it was faulty, but nothing happened at switch on. H.T. was present, but it was very high. It seemed that the regulator circuit wasn't

working. We decided to start by disconnecting the line timebase and getting the h.t. right. On checking through the regulator circuit we eventually found that the set h.t. control R429 (500 Ω) was open-circuit at one end of its track. Replacing this enabled us to get the correct 163V h.t. reading.

The line timebase was still inoperative however – h.t. was present at the collector of the BU208, but a high voltage was also present at its emitter, due to R566 (3.9 Ω) having gone open-circuit (it returns the BU208's emitter circuit to chassis). Replacing this restored normal operation. When we returned the set to the customer he commented that for some while the picture had been jittering, presumably due to h.t. variations.

Another of these sets suffered from intermittent field collapse. This was traced to dry-joints around the scan coupling capacitor C836 (1500 μ F) on the scan correction panel (the PIL tube version of the chassis). **M.D.**

Decca 30 Series Chassis

A Decca hybrid colour set fitted with the 30 series chassis was brought into the workshop with the complaint that the picture was too dark and the colour wrong. We switched on and found that the picture was indeed very dark while the colour was mis-identified at the left-hand side of the screen. It seemed likely that the fault was due to lack of the line-frequency pulses that provide clamping etc. in the decoder, and we suspected the area around the MC1327 demodulator/PAL switch/matrixing i.c. The voltages here were all correct, so we moved on to the pulse shaper transistor TR203. With the use of a scope we found that R218 (150k Ω) had gone open-circuit, removing the pulse feed to the base of this transistor. A replacement resistor produced a reasonable picture. **M.D.**

Thorn 1500 Chassis

The traditional method of dealing with a set that suffers from hum is to check the smoothing capacitors by bridging a known good capacitor across each one in turn. The Marconiphone set (Thorn 1500 chassis) we were confronted with had bad hum problems indeed – the picture was very unstable, with a pronounced hum bar, and the line and field hold were both affected. So out with our jumper leads and test electrolytic. No matter where we prodded however the hum remained as bad as ever. For want of anything better to do we replaced the main smoothing block. The hum was still bad, but seemed just a little better. What next?

To cut a long story short, we had to replace all the following before the set was free of hum: the main smoothing block; the l.t. supply smoothers C56, C58 and C12; the video output stage h.t. supply smoothing electrolytic C38; and C32 which smooths the bias applied to the base of the video driver transistor.

You don't expect to find such a mass capacitor failure, and we couldn't understand what had gone wrong. It later turned out that they hadn't all failed at once. We were again witness to the remarkable ability of some people to watch anything that moves, even when it shouldn't. The owner had watched the ailing set for months until eventually the hum had got so bad that it started to affect the sync. Next time you have a bad hum fault, remember to ask how long it's been going on! **R.R.**

Contributions from Mick Dutton and Richard Roscoe

VCR Servicing

Part 18

Mike Phelan

This month we'll start looking at the 3V23's servo system, starting with the drum (head) servo.

To recap momentarily, we saw in a previous instalment that the 3V00 used a straightforward phase-locked loop for each servo, plus compensation for varying loads. This system was carried forward to the 3V16. Ajustment is critical, since maximum gain without the loop going into oscillation is necessary.

This type of servo is always a compromise. If we have a steep trapezoid slope, a small change in phase will produce a great variation in the control voltage, but a large phase change takes the sample pulse off the slope altogether, the system taking a long time to lock up again. Making the slope more gradual alleviates the latter problem, but the locking is not so "solid" since a small phase change will produce only a small change in the control voltage.

Most machines now have dual servo systems. What this means is that each servo (drum and capstan) has two phase-locked loops. One is a speed control fed from a "frequency gear" (FG) on the rotating element. This controls the speed of rotation. There is then the normal phase control loop to lock the system when the speed is right. The 3V23's servos are both of this type.

As with most machines the drum servo (see Fig. 80) is locked to the field sync divided by two on record, and to a crystal oscillator on playback (this machine is capstan controlled, i.e. on playback the off-tape control pulses are applied to the capstan servo). In addition to this, in both modes a 1.5kHz FG on the drum motor feeds a frequency-to-voltage converter which also affects the motor speed - this is the speed control loop.

The 3V23 has a fast search facility of ten times normal speed, forward or reverse. As we saw with the 3V16 in the still, slow or double-speed modes, this alters the relative writing speed and thus the number of lines per field, but the error in these modes is not very great and the TV set's line timebase compensates. At ten times normal speed however the error is about five per cent, and if nothing

was done the set would display line slip or, at best, displaced colour. The only way in which this can be corrected is to vary the drum's speed of rotation so that the relative head-to-tape speed is the same as in playback. The reproduced line frequency will then be 15.625kHz. The field frequency will be incorrect of course, but the error is proportionately small and the set doesn't mind this.

The drum speed is varied by disconnecting the motor control preamplifier from the servo and connecting it instead to one of two voltages tapped from the l.t. rail to make the drum rotate more slowly in reverse search and faster in forward search. Both speeds are adjustable - they are set for minimum chroma displacement. As this is a capstan controlled machine, there is no phase reference for the head on playback - indeed on normal speed playback the phase control loop is really a speed control one since the reference is the free-running crystal oscillator.

We will mention here that the drum motor is a direct drive type, but more on this later.

Now for a closer look at the drum servo system, see Fig. 81. First the speed control loop. The printed FG coil has 60 poles and thus produces a 1.5kHz signal when the rotational speed is correct. The circuit between pins 14 and 8 of IC3 converts the squarewave at the collector of X34 to a voltage which rises if the frequency increases. We won't bother with a timing chart for this process: basically it relies upon the constant width pulses from the monostable multivibrator (MMV) being added to the output, which varies with speed, from the flip-flop (FF), the result being a series of pulses whose width varies with speed. These are integrated, the length of the ramp thus obtained altering with the speed since the slope is constant. A pulse from the MMV samples this ramp, the result being that the output voltage occurs at a position on the ramp depending on the speed of the drum. R39, R38 and C22 form the MMV time-constant, C21 and R37 provide the integration, while C20 acts as the storage capacitor for the sample-and-hold circuit.

Turning next to the phase control loop, sample pulses from the drum pickup head are passed through two back-to-back diodes which remove stray hum and noise pick up, are amplified by transistor X2, and are then processed in IC3 in a similar manner to the machines we've discussed previously. There are the same three adjustments for the

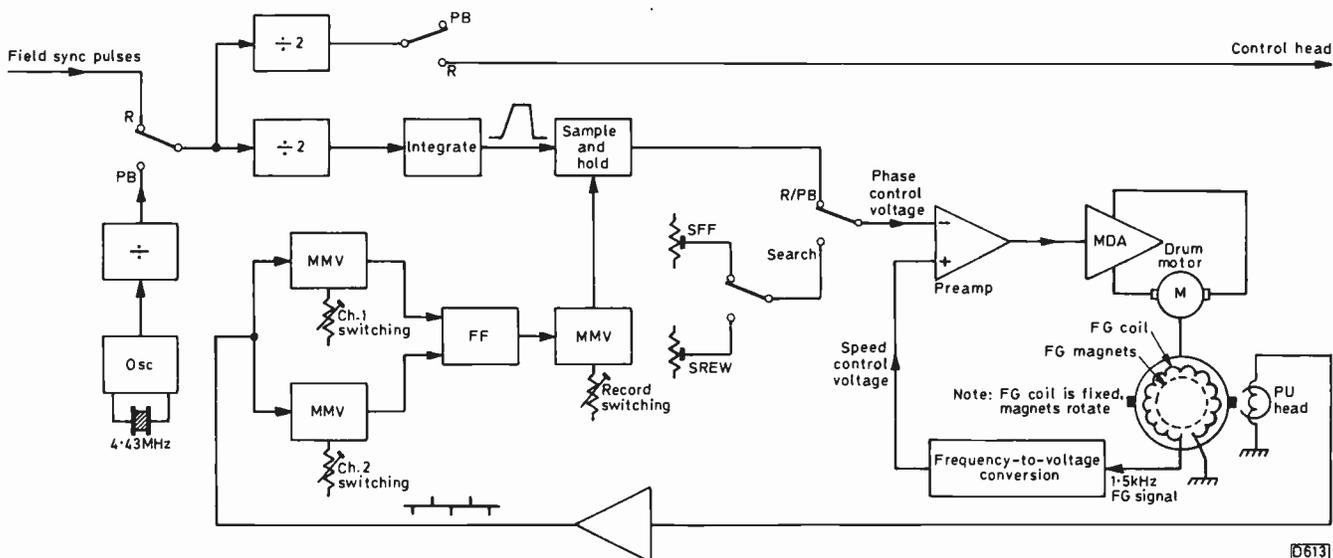


Fig. 80: The drum motor control system used in the 3V23.

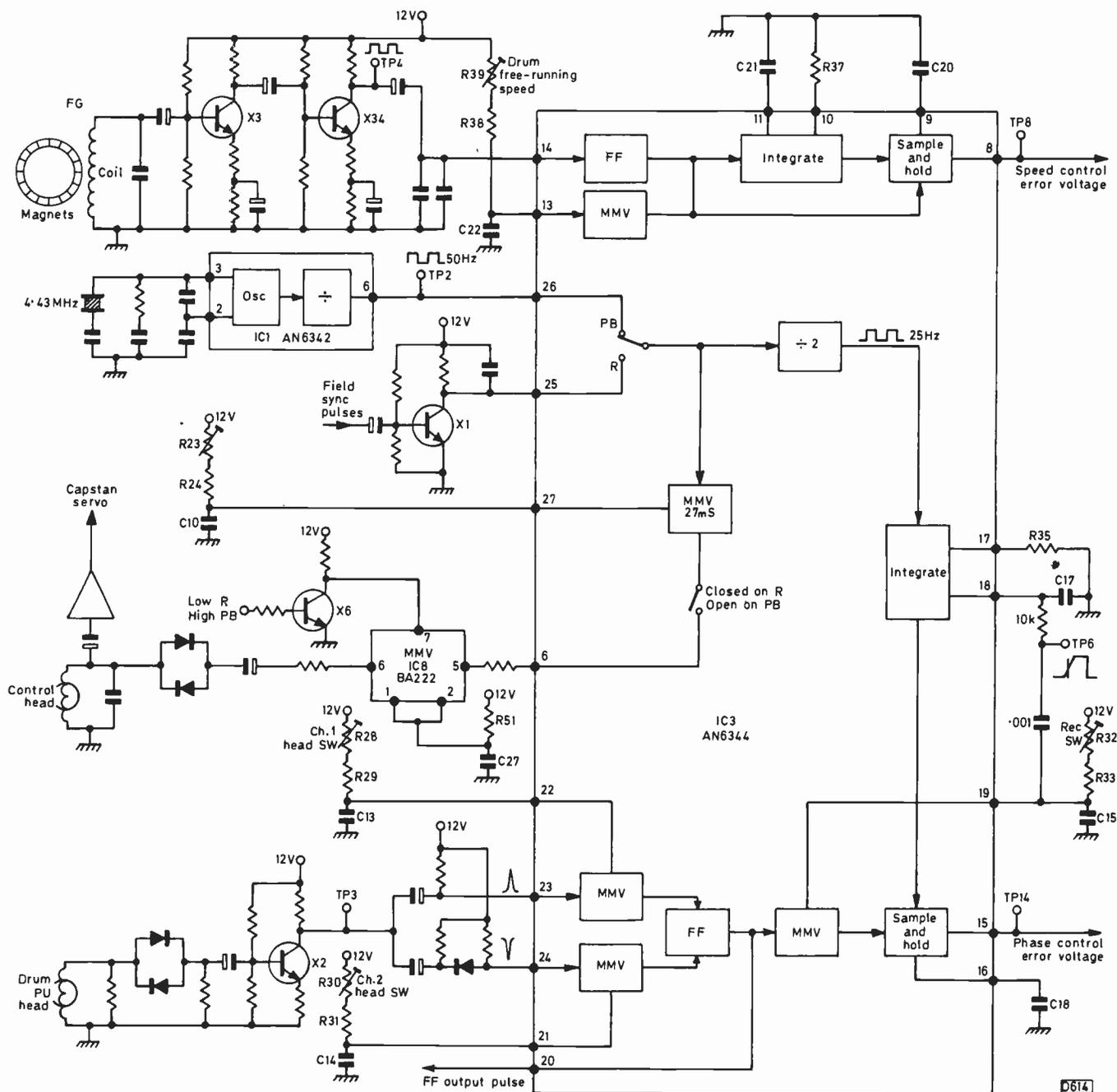


Fig. 81: The servo systems that provide drum speed and phase control.

head switching point.

On record, the reference signal is obtained from the field sync pulses which are amplified by X1 and then fed to pin 25 of IC3 for division by two. The divider is actually a flip-flop. The 1:1 squarewave from the divider is integrated by R35 and C17 to give a trapezoid for the sample-and-hold circuit. Note that this is the reverse arrangement to the 3V00, where the drum FF pulse is converted to a trapezoid and the sync pulse is used to sample this. The RC network connected between pins 18 and 19 has no circuit function: it adds the pulse and the trapezoid to provide a convenient test point (TP6) where both can be viewed simultaneously for the purpose of adjusting R39 in the speed control circuit. Though R39 varies the free-running speed, it can be adjusted so as to place the pulse at the centre of the ramp – you can say that the free-running speed is incorrect then it tries to oppose the phase control, leaving the pulse in the wrong place even if the servo succeeds in locking.

Back to IC3. The field sync pulses from X1 are also fed to a 27msec MMV which effectively provides division by two – the first pulse triggers the MMV whose output stays high until after the second pulse. The resultant 25Hz output passes through an electronic switch which is closed on record only, and emerges from IC3 to be delayed by IC8 (BA222), another monostable. IC8 provides a 28msec wide output pulse which is fed via noise removal diodes to the control head for recording on the tape. X6 is turned on during playback to remove the supply to pin 7 of IC8, thus disabling this monostable and ensuring that pin 6 goes open-circuit and doesn't load the control head – on playback the low-amplitude signal from the head is required for the capstan servo.

On playback it's not necessary to phase control the drum but a 50Hz reference signal must be supplied to IC3 in place of the field sync otherwise the output voltage from the sample-and-hold circuit (at TP14) would be incorrect. IC1 (AN6342) contains a crystal oscillator that operates in

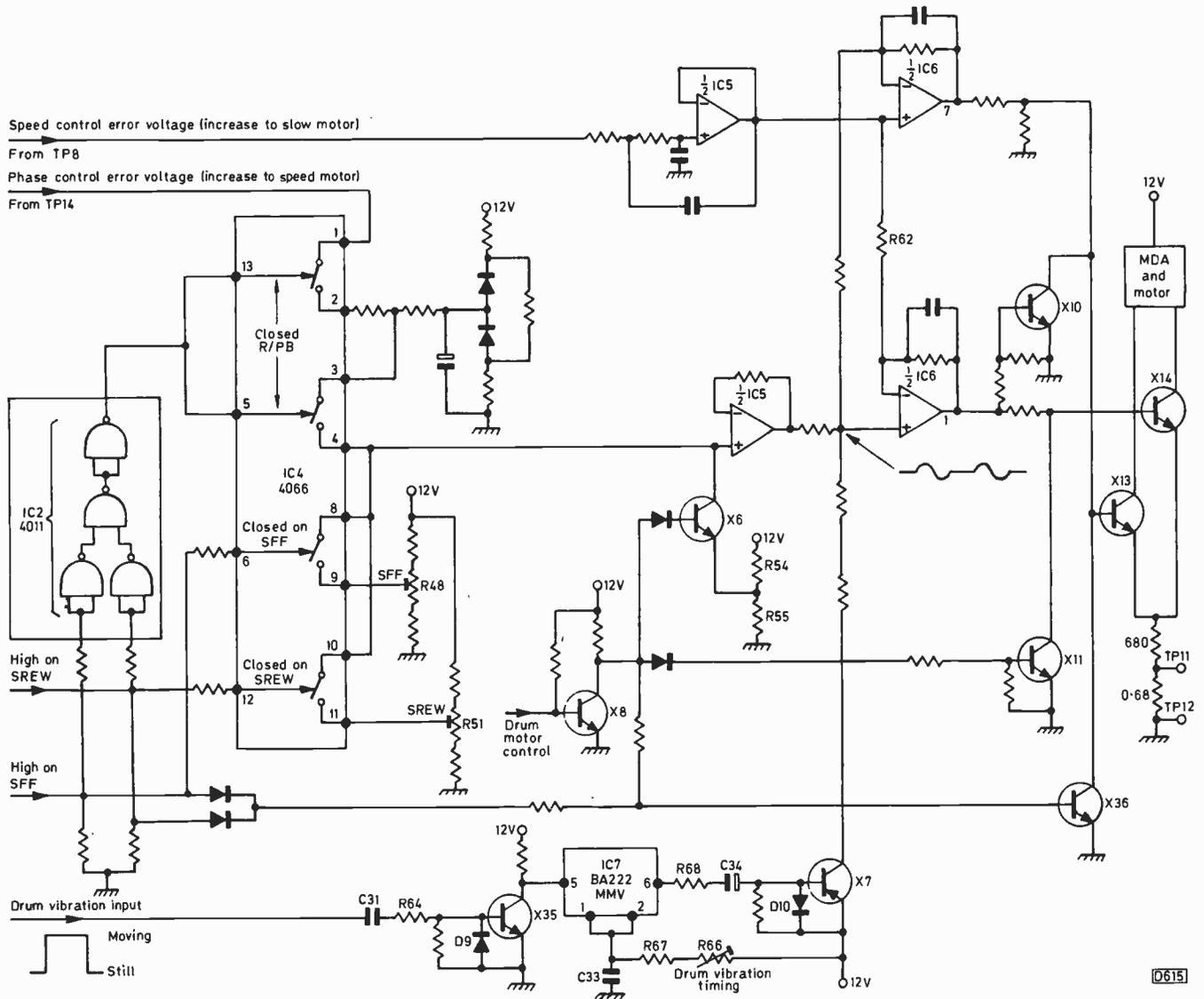


Fig. 82: Drum motor control arrangements.

conjunction with a standard 4.43MHz crystal. This is followed by divide by eight, four and 2,771 stages to get a 50Hz output.

Motor Control

So much for the dual servo loops, which have produced speed and phase control outputs. These have next to be amplified and used to control the motor. Fig. 82 shows the circuitry fed by the outputs at TP8 and TP14. Note that the two output voltages are in opposite sense – the speed error voltage at TP8 will increase with speed, to slow the motor down, while the phase control voltage does the converse.

As Fig. 82 shows, the control voltages are applied to the motor via amplifiers. The final motor drive amplifier (MDA) stages are not shown – we'll discuss them later.

Taking the speed control system first, the error voltage drives the operational amplifier voltage-follower (half of IC5) then, via R62, half of IC6. The upper half of this i.c. supplies the base of X13 and is not used in most modes – more about this later. The non-inverting (+) input to the lower half of IC6 is obtained from the other half of IC5 (also a voltage-follower) which is under the control of the phase error voltage. This latter voltage is routed through two switches in IC4. The first two of these complete the

path through the filter and limiter network between pins 2 and 3 of IC4 and are closed in the absence of either the SFF (search fast forward) or SREW (search rewind) inputs to the gates in IC2. When SFF or SREW is selected, these switches open and one of the other switches closes so that the control voltage is obtained from either R48 or R51.

X8 provides on/off control for the drum motor. When X8 is turned off its collector voltage goes high, turning on X11 which shorts out the base bias for X14. Since X14 amplifies the output from IC6, this action stops the motor. At the same time X6 is turned on, putting a voltage determined by the values of R54 and R55 on the phase control line. The values of R54 and R55 are chosen so that this voltage is the same as that present during normal running, the idea being to eliminate hunting when the motor is restarted.

X14 drives the motor drive amplifier – the motor speed increases with collector current increase. The motor current can be measured at TP11, with TP12 as earth. X13 also drives the drum motor, but does so in the opposite direction. We don't want to do this of course, X13 being used to brake the drum when we go from SFF to playback. At all other times X13 is off.

Due to the construction of the MDA, if X14 and X13 were turned on at the same time the l.t. rail would be

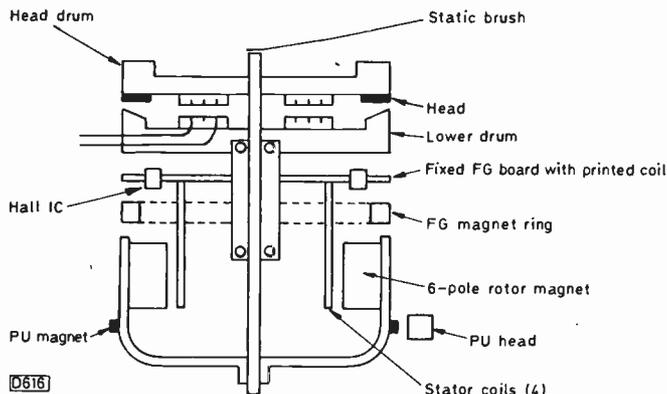


Fig. 83: The head drum/motor assembly.

shorted out. X10 prevents this from happening by removing X13's base bias. In the SFF mode X14 is on and X13 is off, due to X10 conducting. When the machine returns to play as the SFF button is released, the speed control registers excessive drum speed. So X14 and X10 turn off, since pin 1 of IC6 goes low. Pin 7 of IC6 is high, so X13 turns on to brake the motor. As it slows, pin 7 goes lower and pin 1 higher, turning X14 and X10 on and X13 off. During both search modes X36 conducts, providing a safeguard to ensure that X13 cannot turn on. X36 is also driven on when the machine goes to stop, since X8 switches off.

Finally the drum vibration circuit X35, IC7, X7. In the slow motion mode the tape moves for a fixed period and is then stationary for a variable period depending on the setting of the controls. Every time the tape moves the writing speed alters, the result being a horizontal "twitch" of the picture with each tape movement. To avoid this we need to speed up the drum momentarily when the tape moves, then slow it down when the tape stops – the latter is necessary due to the system's mechanical inertia (the drum would take a second or so to slow down of its own accord).

To this end a pulse from the slow drive circuit is fed to

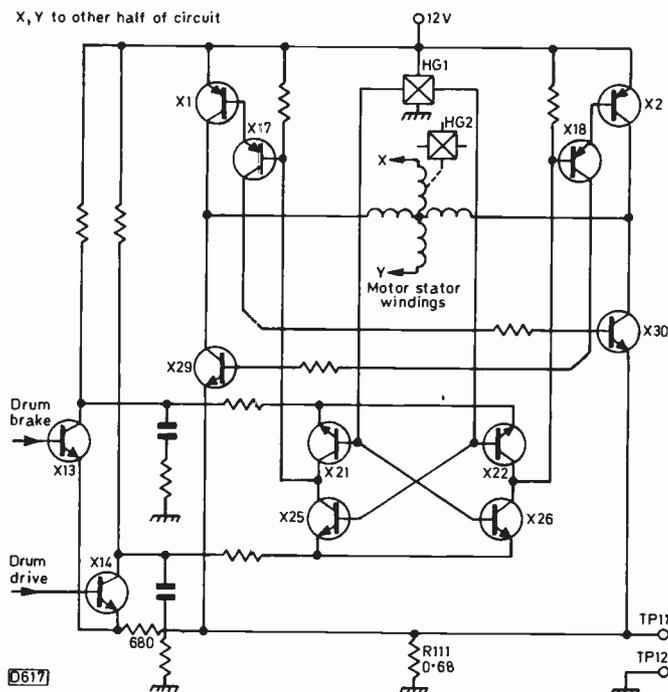


Fig. 84: Motor drive amplifier circuit.

the differentiating circuit C31/R64, with D9 to remove the negative-going excursion at the output. The positive pulse switches X35 on to produce a negative pulse at its collector coincident with the start of tape movement. This pulse triggers the monostable IC7, whose time-constant consists of C33, R67 and R66 – the latter is adjusted for minimum picture disturbance on "slow". The monostable's output is a replica of the slow drive pulse but with the width variable. R68 and C34 provide differentiation of the output, with D10 clipping the positive-going excursion. The negative-going pulse is amplified and inverted by X7 and is then added to the output from IC5. The time-constants are such that X7 conducts slightly when the tape stops.

Motor Drive

The only thing remaining is the drum motor itself. With this machine we come to the concept of a direct drive motor. Previously, most machines used normal d.c. permanent magnet motors, with a wound armature and brushes and a commutator to switch the windings on when they are in the correct juxtaposition to the stationary magnet poles. It would be nice to drive the drum directly without the intervention of a belt and pulleys, but permanent magnet motors don't run evenly at low speeds, due to lack of inertia and the sudden pole switching. If we made the latter electronic, with more gradual switching, it would overcome that problem, but we would still have to get the current to the coils. The answer with direct drive motors is to make the coils stationary with the magnets rotating outside them (see Fig. 83), thus also adding to the inertia. The motor and head drum thus become one compact assembly.

The pole switching is done by two Hall effect i.c.s – remember how one was used in the 3V00 series to sense take-up spool rotation. In this case two are used, 90° apart. The signals induced in them by the six pole motor magnets are amplified to drive the two pairs of coils which are also spaced at 90°. As we've seen, X13 and X14 control the direction of this current. Fig. 84 shows half the circuit – the other half is the same, and all the components are on the servo-2 board, with the drum servo.

X13 or X14, depending on which is conducting, provides an emitter return for two of the transistors X21/22/25/26. When the Hall effect device HG1 is enabled by the rotor magnet, it turns on one of the two transistors selected. Say we are in playback with the motor running. X14 will be partially turned on, providing a ground path for the emitters of X25 and X26 whose bases are alternately forward biased as the magnet poles pass HG1. As each transistor passes current, two of the four transistors X1, X2, X29 and X30 conduct. For example when X26 conducts, X18, X2 and X29 conduct while X17, X1 and X30 are all off. As a result current flows through the winding from the collector of X29 to the collector of X2.

We can now see why it's necessary to have X10 to ensure that X13 and X14 could not both turn on hard – this would turn on all the MDA transistors, stalling the motor and connecting the coils and R111 across the 12V rail, much to their disadvantage.

The other half of the circuit, with HG2, the remaining two coils and associated transistors, is identical – X13 and X14 don't need to be duplicated of course.

Next month we'll deal with the servo-1 board (capstan servo), including the still, slow, double speed, frame advance and assembly edit facilities.

Servicing the Toshiba C800B

John Coombes

The Toshiba C800B is a table model fitted with an 18in. in-line gun tube. It features touch tuning and conventional circuitry, though there are one or two things that can cause confusion. The main power supply arrangements are as follows (see Fig. 1).

The mains autotransformer T802 on the left-hand side of the chassis (viewed from the rear) feeds a bridge rectifier (D801-4) which produces 130V across its reservoir capacitor C810. A secondary winding on the mains transformer supplies the tube's heaters, via a fuse which is part of the transformer. The output from the bridge rectifier is fed via the two h.t. fuses F803 and F804 to a series regulator circuit which produces a stabilised 107V h.t. rail. This supplies the line oscillator and driver stages, also the audio output stage, the tuning voltage circuit and the field flyback switch. D407 in the line output stage produces a boosted 130V supply which is used by the line output transistor and the RGB output stages.

In addition to D407 and the e.h.t. rectifier, the line output transformer feeds four other rectifiers, D403, D405, D409 and DB01. Two of these, D403 and D405, are on the line drive board. D403 produces the supply for the c.r.t.'s first anodes whilst D405, which is separately fused, produces a 15V supply for the low-voltage stages in the receiver. The third rectifier D409, on the mother board, produces a 55V supply for the field driver and class B field output stages. A switching circuit increases the supply to the field output stage to 100V for the field flyback. The fourth rectifier DB01 is on the channel selector board. It produces 19V which is fed to a series regulator that provides a stabilised 15V output.

Before mentioning particular components to check for various faults, it should be pointed out that in practice most faults are caused by dry-joints, due mainly to the metal lugs between the print on each side of the boards. This problem occurs mostly on the daughter boards, though it can also occur on the mother board.

Dry-joints on the vision i.f. panel can be responsible for

a blank raster with low sound, intermittent buzz on sound, intermittent sound, intermittent picture, and intermittent low gain.

Dry-joints on the a.f.c. panel can cause loss of sound with a snowy picture.

Dry-joints on the chroma panel can give intermittent colour or intermittent loss of red or green.

In the event of loss of red/green/blue or loss of picture, check the RGB output panel for dry-joints and check the connections between this and the mother board.

For field collapse, lack of height, intermittent lack of height, bottom cramping or the scan reduced to half an inch, check for dry-joints on the field output transistors Q306 (2SC1448) and Q307 (2SA740) or on the mother board in the vicinity of these transistors.

Fault Summary

Other than dry-joints, our fault experiences with this set have been as follows.

No results: Check the mains fuses F801/2. If blown, check the mains filter capacitors C811/2, the bridge rectifier diodes D801-4 (type 1S1887) and the h.t. reservoir capacitor C810 for shorts.

If the mains fuses are o.k., the tube's heaters should be alright. The next thing to check is the h.t. fuse F803. If this has blown D808 will be reverse biased and the regulator will not start up. Check C807 and D812 (1S1555 - in the error amplifier circuit) for being short-circuit, and Q801 and Q803 (2SC735 - error amplifier transistor) for being open-circuit. Next check the line output transistor Q405 and the line driver transistor Q404 (2SC1447). If these are o.k., suspect the line output transformer T402.

If any of these three fuses has blown and no short-circuit can be found, a replacement fuse restoring normal operation temporarily, replace the mains transformer T802.

No sound or raster can be caused by C408 (0.0043 μ F) in the line oscillator circuit - check by replacement. With this

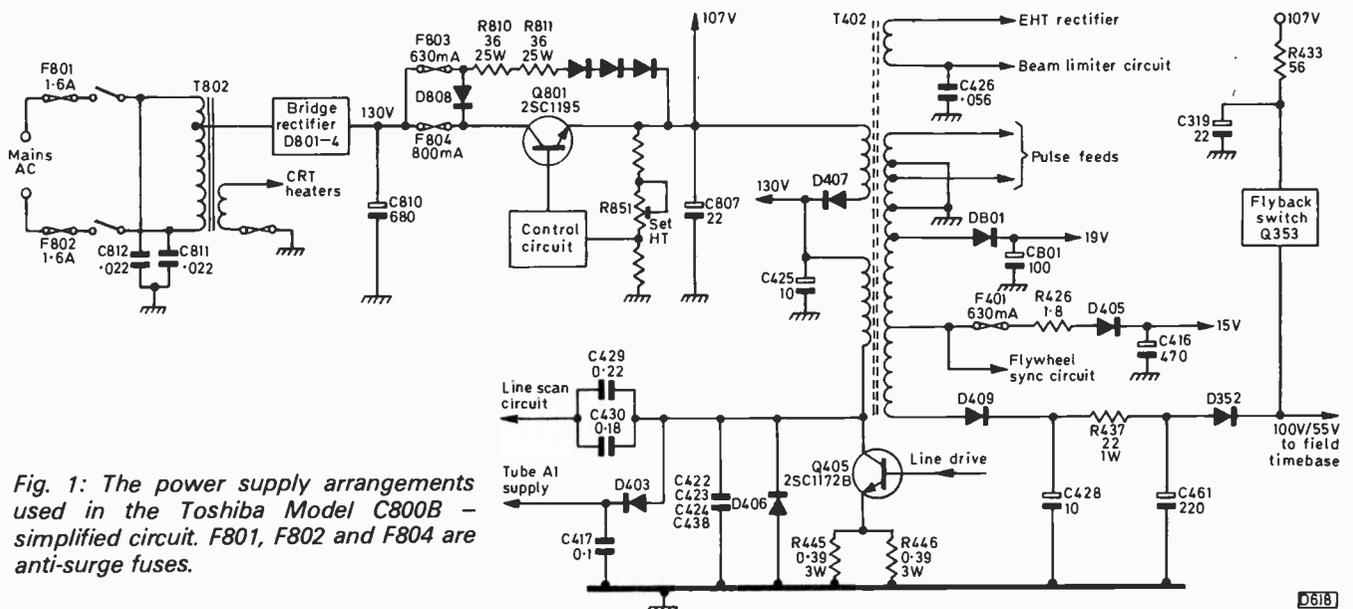


Fig. 1: The power supply arrangements used in the Toshiba Model C800B - simplified circuit. F801, F802 and F804 are anti-surge fuses.

fault the touch sensor neons will flash.

No raster: In the event of no e.h.t., check whether the e.h.t. rectifier D408 (ESPA04-40) is open-circuit. If the diode is all right, check whether C426 at the earthy end of the overwinding is short-circuit.

Focus troubles: The usual cause is the focus unit R452 (22M Ω). This forms part of a potential divider chain across the e.h.t. supply. The other two resistors in the chain, R462 (22M Ω) and R461 (135M Ω), are in the e.h.t. rectifier unit and can also become faulty. It may be necessary to check the decoupler C909 (330pF) and the spark gap Z909 for being short-circuit. If all these items are in order, check the tube base connection (pin 9) and finally suspect the tube.

Striations down one side of the picture: Check the line linearity coil damping resistor R436 (1k Ω).

Sync problems: No sync or intermittent loss of sync is not common but can be caused by the sync separator transistor Q301 (2SA495Y) which should be checked by replacement.

In the event of poor line sync check the flywheel sync discriminator diodes D401/2 (1S1555) which tend to go open-circuit. If necessary check the filter capacitor C406 (3.3 μ F) by replacement.

In the event of poor field sync, check the gating diode D302 (1S1555), the integrating capacitor C305 (0.01 μ F), and if necessary the field oscillator/amplifier chip IC351 (TA7132P) by replacement.

Field jitter: Check the field hold control R351 (150k Ω) then if necessary replace IC351 (TA7132P).

Sound, no picture: The video amplifier transistors can be responsible for this – usually the second one Q202 or the fourth one Q204 (both type 2SC372). Check for an open-circuit or dry-joint on the panel, and if necessary check the luminance delay line W201 which can go open-circuit.

No red/green/blue: The RGB output transistors are Q505 (red), Q507 (green) and Q509 (blue); all type 2SC1447. Check as necessary, also for poor joints on the RGB output board or on the base of the mother board. Also check the connections to the leads between the RGB output board and the c.r.t. base panel.

Excessive R/G/B: Check the spark gaps at the tube's cathodes – Z901 in the event of excessive red, Z902 for excessive green and Z903 for excessive blue.

Intermittent bistable operation: Check D501 (1S1555).

No sound: Check the audio output transistor Q603 (2SC1447) by replacement – if the trouble is intermittent, check for dry-joints at its base and emitter. If this transistor is without collector voltage, check the feed resistor R688 (390 Ω). Check the continuity of the output transformer's primary winding (T661). If necessary check the sound module (U601) for dry-joints and replace the i.c. on this panel – IC601, type TA7146P. On rare occasions the loudspeaker goes open-circuit.

Touch sensors: In the event of channel jumping or sticking in one position, try cleaning the touch sensor pads. The problem can be made worse by the use of spray furniture polish. The remedy is to spray on switch cleaner and then wipe off.

Sticking in one position can also be caused by the neons (GA01/2/3/4) and their driver transistors (QA09/10/11/12). The neons are type NE2D, the driver transistors type 2SC734FA-2.

Associated models: The 20in. Model C2000B uses similar circuitry to the C800B. Differences include the use of i.c.s in the channel selector circuit and a TA7152P in the IC351 position (field oscillator/amplifier).

next month in

TELEVISION

● THORN TX90 CHASSIS

You can always expect something novel in a new Thorn chassis. The TX90 is no exception. The basic power supply circuit is simple – mains isolating transformer plus rectifier – but regulation is achieved by means of a switch-mode boost voltage circuit. There's also an important new i.c., type TDA4500, which incorporates most of the low-voltage circuitry apart from the decoder, and an unusual quiescent current control circuit in the audio output stage. The TX90 is Thorn's highly original answer to small-screen colour portables from the Far East. It's technical features will be described next month.

● AERIALS AND AERIAL FAULTS

Use of an aerial that provides a good, clean signal of adequate strength is important. Aerial systems deteriorate however, giving rise to various problems. The article also covers preamplifiers and faults in this area.

● TELETEXT DECODER UPDATE

Since colour decoding was added to the *Television* teletext decoder in 1979 two developments have occurred – the use of four lines for teletext transmission, and data interleaving in the Oracle system. Steve Money describes modifications to deal with these changes.

● AD CONVERSION FOR VCR CONTROL

Recent VCRs use analogue-to-digital conversion systems to interface the machine's controls with the microcomputer, the aim being to reduce the number of i.c. pins required. Richard Roscoe describes the technique and some faults that can occur.

● SERVICING FEATURES

S. Simon on some less common faults on particular chassis, VCR Clinic, TV Fault Report, etc.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO
(Name of Newsagent)

Please reserve/deliver the July issue of TELEVISION (90p), on sale June 22nd, and continue every month until further notice.

NAME

ADDRESS

.....

.....

Frequency Counter-Timer

Part 3

Tony Jenkins, G8TBF
(WKF Electronics)

This month we'll deal with completion of the construction of the basic unit. Prescaler 2 will be the subject of an article to follow later.

The component layout for the preamplifiers is shown in Fig. 12. When connecting these up the input and output cable screens are connected at the preamplifier PCB only.

Fig. 10 shows the prescaler 1 component layout. The input is fed from the 200MHz input socket via a short length of 50Ω coaxial cable. The screen of the output lead is connected at the prescaler board only.

The final task is to interconnect the whole unit. Fig. 11 shows the interwiring and connection details for the complete assembly, with the exception of prescaler 2 which has to be mounted inside a diecast box. Both preamplifiers and prescaler 1 are mounted by soldering the ground planes to the row of earth pins along the side of the main board. The input and offset grounds are connected to the front pin. Check all wiring carefully before applying power.

Setting up

VR1 on main board: This is the l.c.d. drive control. Adjust for a well contrasted display without the unwanted segments being visible.

TC1 on main board: This sets the counter chip's clock frequency and has to be accurately adjusted with a known frequency source since it determines the accuracy of the unit. The best source available to service engineers is a CTV's reference oscillator when this is locked to an off-air

signal. This is specified by the broadcasting authorities as $4.43361875\text{MHz} \pm 1\text{Hz}$, which is pretty accurate! Adjust the trimmer to give the correct display.

VR1 on the preamplifier boards: This compensates for spreads in the MOSFET's pinch-off voltage (Tr1). Adjust for 2.5V at the collector of Tr2 with the input socket shorted to chassis.

VR1 on the prescaler 1 board: This sets the transistor's operating point. With the 200MHz input shorted to chassis, adjust for 2.5V at the collector of Tr1.

The instrument is now ready for use.

A separate article on prescaler 2 is in preparation. This extends the instrument's capability to around 2GHz. We plan to publish the article in the near future.

WKF Electronics inform us that they are able to supply a complete kit of parts for the project (excluding prescaler 2) for £170.49. Alternatively the instrument can be

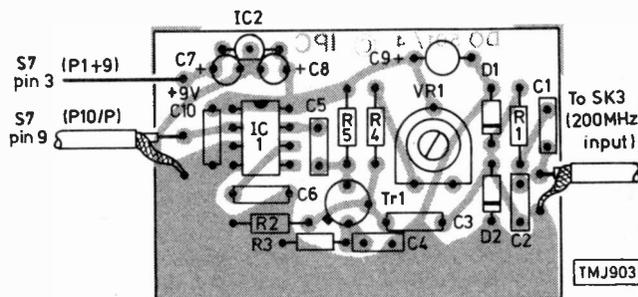


Fig. 10: Prescaler 1 component layout.

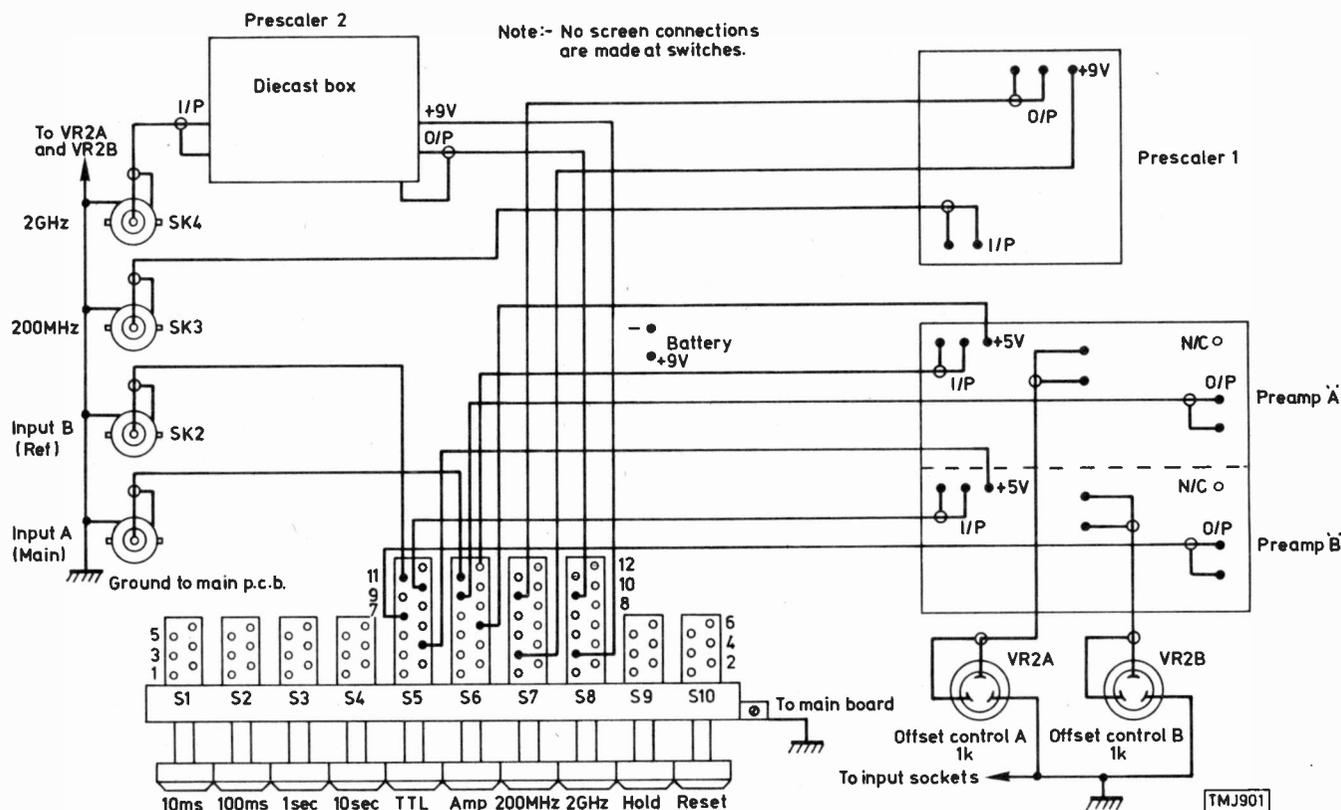


Fig. 11: Interwiring for the complete assembly.

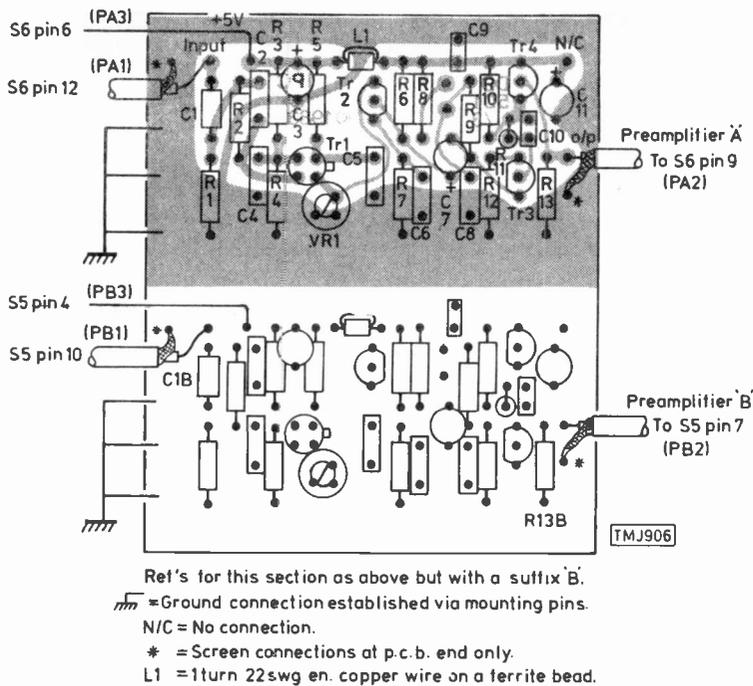


Fig. 12: Preamplifier component layout.

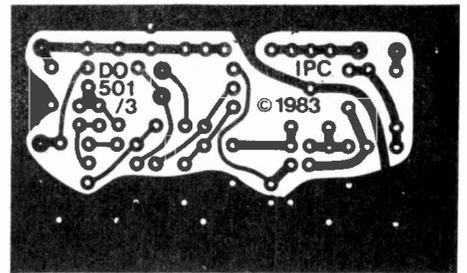


Fig. 13: Preamplifier board pattern.

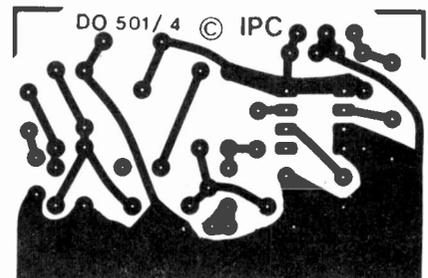


Fig. 14: Prescaler 1 board pattern.

bought fully built and tested for £190.49. Both prices are inclusive of postage, packing and VAT. The main board DO501/1 is available from Readers' PCB Service at £15

while the other boards are available at £1 each. In both cases the address is Fleet House, Welbeck Street, Whitwell, Worksop, Notts.

Lords of the Morning Air

Les Lawry-Johns

MANY years ago, more than I care to admit, I was an avid reader of science fiction magazines. My favourite, if I remember correctly, was *Astounding Stories*. There were some good yarns in it, and the title of one sticks in my mind – it was *Lords of the Morning Air* and was about some superior beings that came to visit earth. They looked like us but were far superior of course, with long fair hair and blue and gold robes to prove the point. Kind they were too, not like us louts.

Anyway it was a bright and sunny morning, and as I took Ben for his stroll we first waved at the drivers of the cars – the ones that came up the road and honked at us – and then went round the back of the flats (two large blocks opposite the shop), continuing to wave at all the occupants who waved at us. One old boy opened his window and bawled out that he'd "let us look at his TV set later". "Thank you, thank you very much" I bawled back, without much conviction in my voice. What he really meant was that I was to be allowed to cart a load of equipment over to the flats, lugging it through the corridors, then performing a miracle on his old set before carting the lot back again. Anyway, we dismissed this diversion from our minds and continued our walk in the morning air, still waving to all and sundry and wishing we didn't have too because our arms were aching. Now we know how royalty feels. Royalty, that's what we were, *Lords of the Morning* . . . until we got back to the shop, when we became surfs once more.

Who should be waiting for us but Mr. Piddlewell – he who'd threatened to cut off our milk supply last time. He didn't even give me time to get the lead off my neck.

"We were watching that science fiction film last night when the picture went off and someone started talking in a foreign language – lots of other voices chattered away too."

"What do you expect if you put the volume full up?" I snarled.

"Well it shouldn't chatter away in a foreign language, should it?"

"It might if it doesn't feel well. It was probably delirious" I replied, looking on the shelf for an MC1330 chip.

"What's that?" demanded Mr. Piddlewell. "It doesn't look much."

"That there does a very difficult job" I explained. "When it stops doing it the set jabbers away in lots of foreign languages and you don't get a picture either."

"Oh" said Mr. P. "How do you know it's that?"

"Because I can feel it in my water" I explained, not wishing to go into detail about previous tests with prods at the input and prods at the output.

So we opened the signals panel of Mr. P's Thorn 8000 chassis, took out the MC1330 from the left-hand side, and fitted the new one. Just for fun I applied the meter's test prod to the chip's output pin and switched the set on. There was an air-splitting garble of voices from the speaker, and Mr. P's eyes widened.

"It's still doing it" he bawled.

"No it ain't" I said, removing the test prod and plugging an aerial in. Soft music accompanied the BBC-2 test pattern.

"You're having a go at me. I know you are."

"Not at all, Mr. P. I was just demonstrating that when the chip goes open-circuit it acts like an aerial for the reception of 6MHz signals and the harmonics thereof" I said, laying it on a bit thick.

"Oh, very genital" said Mr. P, reverting to his coarse upbringing.

"Well pay up, look big and sod off" I advised him, reverting likewise.

Another Lord

Stripe me pink if Mr. Lord didn't walk in carrying a large Philips radio cassette. It was Mr. Lord my accountant.

"What do you want? you robber" I greeted him warmly.

He looked pained. "We don't rob you Les. It's not our fault if you don't charge enough for your services. At least we're realistic."

"I'll start charging realistic fees right now Mr. Lord" I said.

"Don't be impetuous. Rome wasn't built in a day."

"It would never have been built at all if the contractors had charged your fees" I replied, warming to my task.

Mr. Lord crossed his fingers and said "Faye Knights". That put an end to it of course.

"Sorry Mr. Lord. Well now, perhaps I can help you in some way?"

"It's just the cassette section of this thing Les. The pinch wheel is flopping about."

So he left it for me to fiddle with whilst he returned to his office to do his fiddling. I hope he had better luck than I did.

Due to my lack of observation I mucked about with it for ages. Having stripped it down and removed the cassette section I couldn't find any sign of the pinch wheel spring. So I thought I'd try to make one, which I did, having to remove the wheel to fit it. When I refitted the wheel and anchored the free end of the spring the wheel did what it was supposed to do and fitted tightly against the capstan. A little too tightly I thought, but blundered on.

To test the machine the panels had to be reassembled, so I thought I might just as well put the whole thing together anyway, just leaving the rear cover off. I switched on and pressed play. The capstan rotated nicely but the spool carrier didn't move. I tried again but it stayed still and refused to rotate. So I took the panels out again and got the screws thoroughly mixed up whereas I'd previously had them organised for proper replacement.

I stared at the cassette section and pushed down the play button. The plastic carrier went down but when I rotated the flywheel the take-up spool carrier didn't rotate. It would spin freely, but didn't engage with the sprocket which should have driven it. The sprocket is pushed into position by the plastic carrier which didn't seem to be travelling far enough. Perhaps it was because I'd anchored the spring to the carrier? So I took the pinch wheel off and tried again. The sprocket engaged, and the take-up spool carrier rotated with the flywheel.

At this point the cat walked across the bench and sat looking at the rear cover. Something was attracting her attention. It also attracted mine because it was a nice bronze spring caught up in the leads which connect the rear cover to the main unit. "Thank you Spock" I said gratefully as I shoved her off the bench.

So I put the right spring on and checked it carefully.

The pinch wheel fitted tightly against the capstan and the take-up carrier didn't rotate. I felt peeved about this, and once again removed the pinch wheel. The carrier then rotated. I stared at the assembly and then saw what I should have seen earlier. There's a plastic obtusion just above the pinch wheel assembly, and I'd put the assembly back to ride below it, which was why it fitted too tightly against the capstan. Assembled so that it rode above the obtusion, the plastic carrier could ride fully down and the sprocket would engage.

What would have taken any sensible person a few minutes had taken me over an hour, and I was not pleased with myself. No wonder I can't pluck up enough courage to tackle these videos. Just imagine what a mess I'd make. Mind you, some of these audio stack systems seem to be just as inaccessible, with the whole works up front and acres of nothing in the rest of the cabinet. Come back music centres, all is forgiven.

It wasn't my fault that my accountants had advised me to increase my service charges. Sorry Mr. Lord.

More Royalty

What a funny thing. If you get one type of set in you can bet that a whole row of them will follow. In this case it was names however. Next along comes Mr. Knight who wanted his G8 repaired. He also announced that he intended to buy a new set for the lounge, keeping the G8 for the bedroom.

I didn't go along with this idea, and suggested that it would be more convenient to leave the G8 where it was and invest in a 14in. colour portable for the bedroom, with remote control so that if anyone was confined to bed they could change channels, control the volume and switch the set off with the small handset. In addition there would be a considerable saving because a portable was a lot cheaper than a 22in. set. As his wife was with him I added that a portable could easily be moved to the kitchen for the reception of breakfast TV, the set having its own aerial.

Mrs. Knight was immediately convinced and informed her husband that he'd be a fool to buy another large set.

So I showed them a Fidelity CTV14S, and they were most impressed with my demonstration of mirror reflected channel changing, though I couldn't quite see the value of this if you're watching the set anyway and holding the remote unit.

Mr. Knight announced his decision. If I could repair the G8, he'd take the portable. So we checked the G8 and found that there was lack of red. The red BF337 output transistor was o.k., but there was precious little turn on bias at its base. The driver load resistor R7326 (39kΩ) was accused of being high and proved to be so. I looked in vain for a 39kΩ resistor but the nearest I could find was 47kΩ, 2W. Fitting this restored normal operation without any need for adjustment, so we wrapped up the G8 and piled it and the Fidelity portable into the Knight's car, while Mr. Knight wrote out the cheque which was for a lot less than he'd expected when he first arrived.

What an honest chap I am. We haven't been able to get any 22in. remotes for some time . . .

Note on the G11

Finally a note on the h.t. reservoir capacitor (C4029) in the Philips G11 chassis – it came up in the letters column recently. Green ones are just as bad as the red ones – blue or black are o.k.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon printed below and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

BUSH BC6004

The original fault was a dead set. Quite a lot of items had to be replaced: the BU208 line output/chopper transistor, the associated diodes D687/688/725, the mains bridge rectifier D856, the surge limiter resistor R854 and the TDA2560 i.c. in the decoder. No one around here seemed to have replacements for D687/725 so I used BY223s as in the D688 position. The h.t. was correctly set for 122V and everything works, but the BU208 and its heatsink get very hot indeed.

The overheating could be due to the use of incorrect diode types in the D687/725 positions. The specified types (SKE series) should be available from Mastercare or the electrical wholesalers SEME. The BU208 is protected by the snubber network C841 (0.001 μ F) and R841 (560 Ω , 17W) and it would be worth checking these components.

ITT CVC9/1 CHASSIS

There's distortion on the right-hand side of the screen — the upper part bends downwards and the lower part upwards, with a gap at the bottom. A new field timebase valve has made no improvement. The distortion is not constant, the raster being normal at switch on, then distorting, then returning to normal etc.

The pincushion correction is working with a phase error. Adjustment of the NS phase coil L125h might clear the problem, but first check carefully for dry-joints around the pincushion correction transducer and the associated components. This should include C255h and C254h, both 0.033 μ F, which are suspect if correct raster shape cannot be achieved.

THORN TX9 CHASSIS

This set has developed faulty line sync — particularly noticeable on test pattern ETP1 where the verticals exhibit a zigzag effect. The fault also seems to be dependent on the setting of the contrast control. Would you suspect the TDA9503 line processor i.c. IC54 or its associated components?

First check the 12V regulator IC56 by confirming the correct 12V at pin 4 of IC54. If this is right, check the sync separator coupling/bias components C156/R203 (0.33 μ F/1M Ω) and the voltages around the sync inverter transistor VT50 before condemning IC54.

TOSHIBA C81B

The problem was fuse blowing, the cause being a short-circuit line output transistor (2SC1172). Replacing this

with a BDX32 stopped the fuse blowing but failed to restore normal operation. I've now fitted a 2SC1172Y, but in doing so it was necessary to shorten the emitter coil slightly due to a fracture. Is this in order and is there anything else to check?

Slight shortening of the emitter coil should not matter, at least in the short term. It's just possible that the transistor may overrun slightly during prolonged use, though this is unlikely. Other items worth checking are the e.h.t. regulator transistor Q405 (2SC792) and its emitter resistor R438 (5.6 Ω , 1W), also R435 (6.8 Ω , 5W) which is in series with the h.t. feed to the line output stage.

RANK A823 CHASSIS

As the set warms up, the sound starts to buzz and crackle. This can be tuned out with the fine tuner, but then either the picture goes or it has to be watched in monochrome. The crackle is present on all stations.

This is the early version of the chassis fitted with the A809 i.f. panel. It uses a slope detector for sound demodulation, a system that was not very successful. Try adjusting the sound i.f. coils 2L26/7/8 to eliminate the crackle. A very small (less than one turn) adjustment of 2L1 in the i.f. input filter unit may also help. A conversion kit (type 154m) was at one time available from Rank to improve the sound reception. Alternatively the later Z182 panel can be used — it works better.

FERGUSON 3787

The original fault was a burnt out tripler and focus unit. These items were replaced and a new line output transformer was fitted, and after adjusting RZ13 for the correct supply rails the set ran all right for a couple of days. It then went dead. At first there was an intermittent ticking sound but this has now disappeared. All fuses are intact, and the pulse feed resistors (RU15 and RU16) to the electronic trip thyristor DU04 are intact.

If there's no "burst" of energy at switch on to indicate operation of the trip we would suspect that the flyback thyristor DA12 is faulty, though it would be useful to check for drive via CA13 with an oscilloscope. If there is a burst of energy, check the regulator thyristor DU11 and make sure that its gate trigger pulse circuit is intact. It's essential to use the correct thyristor types.

NATIONAL PANASONIC TC85GA

The problem with this set is a dark band on the left-hand side of the screen, extending from the edge for about four inches towards the centre — it looks rather like a shadow. The rest of the picture is all right.

The fault is not uncommon on these sets and is usually due to C514 (4.7 μ F, 350V) drying up — it's the reservoir capacitor for the video output transistors' 220V h.t.

QUERY COUPON

Available until 22nd June 1983. One coupon, plus a £1.00 (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice above.

TELEVISION JUNE 1983

supply, which is derived from the line driver transformer. Other things to check if necessary are the first anode supply reservoir capacitor C518 (0.068 μ F, 1.5kV) and the 24V line reservoir/smoothing capacitors C523/4 (both 330 μ F, 35V). These two supplies are derived from the line output transformer.

THORN 1690 CHASSIS

This set works normally when switched on, but after some five minutes the screen blacks out (no raster), the tube's

heater becomes dull and after a further ten minutes the sound also gradually disappears. Sound and normal tube heater brightness are restored when the e.h.t. connector is removed.

The e.h.t. rectifier stick, which is encapsulated in the line output transformer, is breaking down. As a result a.c. is fed to the c.r.t. anode connector and is shorted via the tube's capacitance, loading down the line output stage. It would be best to fit a new line output transformer assembly, though a stick as used in the 8000 chassis could be wired in series.

TEST CASE

246

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

THE number of service calls to a particular item of domestic entertainment electronics seems to depend largely on whether it's rented (lots of calls at no charge to the customer) or purchased (very few calls after the guarantee has expired!). The care lavished on rented TVs and VCRs also seems to be much less than when the user owns the gear. At the termination of the rental contract the equipment comes into our workshop for checking and refurbishing, and a great deal of time often has to be spent on repolishing, cleaning and replacement of cosmetic items in order to bring the performance and appearance up to scratch.

This month's tale of intrigue concerns an ex-rental Ferguson VCR, Model 3V20. The job ticket conveyed the depressing message that the subscriber had defaulted on his rental payments and that the machine was not working. Plainly the customer's problems were not confined to finance, for a cracked side and deep dents in the bottom cover around the feet betrayed the fact that the VCR had been dropped. When we tested the machine we found that it would lace up and then unlace after a few seconds, reverting to stop. A careful examination of the relevant printed panels and the top of the tape deck was made for signs of cracking or damage, but none were found.

The system control circuitry on this model is quite straightforward, consisting of a single MSM5830 chip on the mechacon panel and a handful of transistors in the interfacing circuitry. The fact that the machine would lace up initially suggested that most of the mechacon system was in order, and we could see that the cassette lamp was working and the head drum was rotating. During the five second period of operation the machine provided, all

seemed to be normal. So our first investigation was centred on the spool rotation detector – if this fails to produce an output, a counter within the mechacon chip shuts the machine down after five seconds.

The spool rotation detector consists of a Hall effect i.c. and a rotating magnet driven from the counter belt – all were present and correct, and there was adequate a.c. input to the mechacon chip. The AL (after load) switch was also found to be working correctly, putting a logic high on pin 13 of the chip at the completion of lacing. There seemed to be no point in checking the memory (counter) and tape end sensor inputs to the chip as these, if giving false signals, would not permit the five seconds' operation available. So we pressed on.

There's one other input to the mechacon system required for normal operation, and here lay the trouble. The oscilloscope led us to another panel, then away again to . . . where? If you haven't already got there, suffice it to say that the machine stopped working from the time it hit the floor – yet nothing internal was broken, and there were no discontinuities in the panels, leads or connections. Time now to enter stop . . . full replay in the next issue!

ANSWER TO TEST CASE 245 — page 377 last month —

Last month we described one of those obscure, minor faults that sometimes afflict TV sets. The set concerned was fitted with the Decca 100 chassis, and the trouble was a slight vision instability effect, showing plainly on only certain types of picture, the standard test card being the favourite. The instability took the form of faint, distorted multiple images to the right of the correct one, as a result of which the picture was somewhat blurred.

After various initial checks we'd fitted a substitute i.f. panel. This had made no difference, so the trouble wasn't there. Another tuner had subsequently been tried, and the fact that the appearance of the symptom was then slightly different encouraged us to concentrate on the area of the tuner.

Bridging the tuning line decoupler C3 with a similar component did nothing, but the same capacitor when placed across C1 completely cleared the trouble! This 0.1 μ F capacitor decouples the tuner's a.g.c. line, and is on the tuner panel. It's a polyester type with a much higher voltage rating than one normally finds used in this position, and was the last thing we'd expected to fail!

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

1000's OF COMPLETE TV'S TUBES & PANELS ALWAYS IN STOCK

Give us the opportunity to quote for all your requirements. Mixed loads delivered to your door directly from source - at unbeatable prices plus special discounts for bulk purchases.

JUST ARRIVED!

Fresh stocks from our suppliers.



call
BRAINTREE
(0376) 43685
24 hour service

NEW STOCKS ARRIVING

AMPLE
FREE
PARKING

CELTEL


OPENING HOURS

BRAINTREE		LONDON	
Mon-Fri	9-6 pm	Mon-Fri	10-5 pm
Saturday	9-3 pm	Saturday	10-1 pm

Warners Mill, South St. Braintree, Essex. Tel: (0376) 43685
10 Shackdewell Rd. London N16. Telephone: 01-249 9265

TELEPART

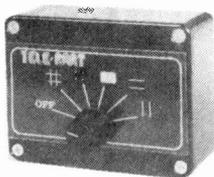13 WORCESTER ST.,
WOLVERHAMPTON,
WV2 4LJ
Tel: (0902) 773122
Telex: 336810



Telepart Pattern Generator

- * Exceptionally light and durable
- * Pocket size for outside service
- * PP3 battery power source
- * Five different test patterns for colour and mono TV
- * Cross hatch grid
- * Dot matrix
- * White raster
- * Horizontals
- * Verticles

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)

POST & PACKING £1.15

Telepart Colour Bar Generator

- * Exceptionally light & durable
- * Compact 13x17.5x5.5 cms
- * Battery powered for mobility
- * Cross hatch grid
- * White raster
- * Grey scale
- * Colour bars
- * Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.)

POST & PACKING £1.15

Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

Supplied by return, off the shelf

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY

Z146 A640 dual std mono	7.00
Bush A792, A793	
single std mono	7.00
A774 single std mono	7.00
A816 solid state mono	9.00

DECCA

MS1700 2001 2020 2401 mono	7.00
MS2404 2420 2424 mono	7.00
CS1730 1733 colour	8.00
CS1830 1835 colour	8.00
'30' series Bradford colour	8.00
80 series colour	8.00
100 series colour	8.00

FERGUSON HMV MARCONI

1600	9.50
------	------

G.E.C.

2047 to 2105	7.00
2000 to 2064 dual std mono	7.00
DUAL STD hybrid colour	11.00
SINGLE STD hybrid colour	10.00

Indesit 20EGB 24EGB mono 9.00

KB - ITT

VC200 VC205 VC207 mono	7.00
CVC5CVC7CVC8CVC9 col.	8.00
CVC20 series colour	8.00
CVC30 CVC32 series colour	8.00

PRICES INCLUDE P. & P. & 15% VAT

PHILIPS

170 series dual std mono	7.00
210 300 series mono	7.00
G8 & G9 series colour	8.00

PYE 169-173-569-368 7.00

EKCO RV305-769-725-741 8.00

WALTHAM I25 9.00

REWIND SERVICE - available for most continental types i.e. Kuba, Luxor, Korting, Tyne, Berry Skantic, K80 £12. Old lopt required

WINDINGS

RANK BUSH MURPHY

T20a T22 Pry & Sec	6.00
Z718 series primary	6.00
Z718 series EHT overwind	7.00

ULTRA THORN

1690 1691 EHT overwind	7.00
1590 overwind	5.00
1615 winding	7.50

PHILIPS

G6EHT	8.00
G6 primary	6.00

PYE

691 to 697 EHT overwind	4.00
691 to 697 primary	5.00

All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Allow 1-2 days for delivery.

S.A.E. all enquiries
Barclaycard and
Access welcome

PAPWORTH TRANSFORMERS

80 Merton High Street
London SW19 1BE

01-540 3955

For orders placed at the post office
Trans cash
506 4856

HUSSAIN CENTRAL TV

Clearance deal to the trade

10,000, yes, 10,000 sets to be cleared at ridiculous prices in ones or hundreds, i.e. Pye 205 £3, GEC Hybrid £3, Philips G8 £5, and mono's £1.50.

Hundreds of modern sets at giveaway prices, i.e. Philips G11, G9, Grundig, Bush 220, Thorn 9800, Solid State ITT, Decca 100 and 80, etc.

Ring us today at our Birmingham depot:
Phone 021 622 1023.
Chepstow depot: 0291 26652.

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded."



LEDU multi-purpose illuminated magnifier

ONLY £52.00 plus VAT

Please send _____ LEDU illuminated magnifier/s at £59.80 each, inclusive of VAT. Total value £ _____

* Please debit my Philips Service account No. _____
My Order number is _____

* I enclose cheque made payable to PHILIPS SERVICE

Deliver to _____
Address _____
Tel. No. _____

Signature _____ * Delete as applicable

PHILIPS SERVICE,
Commercial Sales Office, 604, Purley Way,
Waddon, Croydon CR9 4DR
Please allow 21 days for delivery.

Or order by ringing
01 - 686 - 0505
ext. 240

Service Service Service **PHILIPS**

POST A PART, ELECTRONICS.

AD161	32p	BCX34	11p	PN107	7p
AD162	32p	BD131	30p	R2008	1.80
AF139	38p	BF137	20p	R2010B	1.10
AF239	41p	BF199	15p	R2265	1.30
BC107B	15p	BF240	9p	R2443	25p
BC108A	15p	BF255	10p	RC1A16446	30p
BC109B	15p	BF255S	20p	RC1A16589	1.25
BC117	21p	BF267	28p	RC1A16600	1.40
BC133	16p	BF259	28p	2N3703	20p
BC154	16p	BF274	11p	2SA473	10p
BC171	9p	BF459	40p	2SC346	8p
BC172	9p	BF887	25p	2SC785R	12p
BC174B	23p	BF742	30p	2SC3020	15p
BC184L	12p	BF743	30p	2SC388A	20p
BC208	9p	BU105	1.00	R2322	50p
BC237	12p	BU126	1.10	R2323	50p
BC238	8p	BU207	1.05	TIP31	35p
BC251	8p	BU208A	1.15	T9010V	1.45
BC307	10p	BU326A	1.30	T9016V	1.20
BC308	8p	BU326B	1.30	T9017V	1.20
BC347	8p	BU326C	1.30	T9050V	1.50
BC394	8p	ME0404	8p	T9051V	1.00
BC454	8p	ME0412	8p	T9052V	1.30
BC455	8p	ME0420	8p	T9053V	1.30
BC460-6	40p	MJE340	50p	S2800E	90p
BC549	8p	MJE520	65p	S2800C	1.00
BC556	8p	NKT241	8p	S2800K	1.25
BC559	8p	NKT726	20p	S2800E	1.40
BC595	8p	NKT453	1.65	S2800M	2.00

ZENER DIODES

TOSHIBA 200MV 10p each
6.2v, 12v.

BZY88 10p each
3.9v, 5.6v, 12v, 16v, 20v, 30v, 33v.

TOSHIBA 500MV 10p each
5.6v, 6.8v, 7.5v, 8.2v, 11v, 15v.

BZX61 16p each
9.5v, 10v, 11v, 15v, 27v, 72v.

THORN TX9 main panel complete (no tuner) Ex-factory. **£11.00**

Thorn 10Q 20W (3500) R751 Safety Resistor 75p
Pye 713 Speaker 5" x 3" 70Ω 1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads 2.75
Pye 713 Control Knobs 4 for 50p
Tube Base Socket ITT CVC32 45p
Tube Base Socket Thorn 3000/8000 etc 50p
IC Insertor 16 Pin 50p
Large IC Extractor 50p
Crystal 4.43MHz 65p
EHT Lead & Cap for Split Diode Lopt Anode Capacitor 47p
Sanyo Anode Cap Assy + Lead. 12TCD-CT-1G 65p
Degause Thermistors. PT37P, ITT/GEC 35p
Degause VDR E298D/HP230 3000/8000 25p
Casters Set of 4 1.90
Double Fuse Holder on Small Pax Board 20mm type 10p
Single Fuse Holder on Small Pax Board 20mm type 5p
Direct Panel Mounting 20mm Fuse Clips (pair) 15p
Single Fuse Holder on Small Pax Board. AS per early 3000 mains input 6p
EHT Cable Metre 25p 13A Plugs 12 for 4.80

THICK FILM RESISTOR UNITS

3500 Thorn (5 Pin Connection) video 1.70
4000 Thorn (4 Pin Connection) 1.90

TANTALUM CAPACITORS

0.1MFD to 470MFD 6.3v/10v/16v/35v
£6 per 100

MINIATURE CERAMIC DISC

1PF to 10NF 50v/250v/500v
£2 per 100 or £15 per 1000

HIGH VOLTAGE DISC

Most Values Available 2KV to 12KV
£5 per 100 or from £40 per 1000

With these items No Mixed Values in Lots of 100

SERVICE AIDS

Ambersil MS4 Silicone Grease 12oz 2.15
Ambersil Freezer 12oz 1.99
Ambersil Amberlube 6oz 1.85
Ambersil Ambertron 16oz 1.95
Ambersil Anti-Static Screen Cleaner 7oz 1.95
Ambersil 40+ Protective Lubricant 14.1oz 2.15
Ambersil Amberclens Foaming Cleaner 13oz 1.25
Ambersil Circuit Lacquer 14oz 2.15

MIXED PACKS

300 Mixed Resistors 1.50
300 Mixed Capacitors 1.50
150 Mixed Electrolytics 2.00
100 W/W Resistors 1.00
20 Mixed Conv Pots 1.00
40 Mixed Pots 1.50
20 Mixed Sliders 1.00
40 Mixed Presets 60p
20 Mixed VDR & Thermistors 1.00
20 Mixed Ferrite Cores 50p
100 Mixed Ceramic Discs 1.00
20 Mixed Valve Bases 1.00

AERIAL SOCKETS

AE Socket & Lead. Pye, ITT, Thorn 25p
AE Socket & Lead. GEC 25p
AE Socket & Lead. (long) GEC 25p
AE Socket & Lead. Pye 691/693 25p
AE Socket & Lead. Philips KT3 25p
AE Socket & Lead. Thorn col portable 25p
AE Socket & Lead. (long) Pye 725/731 25p
AE Socket & Lead. ITT CVC32, etc 25p

UHF TV Aerial for portable 50p
Indoor Aerial Parabolic Type Reflector to Help Combat Ghosting Problems 2.50
Line Connectors 38p
Coax Plugs 10 for 1.65
Band Change Switch Assy, Pye 725 40p
Flush Mounting TV/FM Diplexer 1.00
Switched Flush Fitting Aerial Outlet 1.00

CAN TYPES

0.2MF 250V 50p
2MF 250V 50p
22MF 275V 50p
50MF 275V 50p
100MF 150V 65p
100MF 250V 70p
100MF 450V 75p
220MF 400V Thorn 9K 1.30
2500MF 35V 95p
2500MF 40V 65p
3000MF 30V 65p
3300MF 16V 50p
3300MF 25V 60p
4700MF 16V 72p
4700MF 40V 75p

CAPACITORS

3.3PF 350V 3000PF 2KV
6.8PF 63V 3300PF 250V
8.2PF 350V 4700PF 400V
10PF 350V 0047MF 500V
12PF 1000V 0075MF 2KV
22PF 63V 01MF 250V
30PF 63V 01MF 600V
47PF 350V 015MF 600V
182PF 63V 02MF 200V
250PF 2000V 02MF 250V
330PF 63V 022MF 250V
330PF 160V 047MF 400V
330PF 8KV 1MF 250V
470PF 250V 1MF 600V
560PF 63V 1MF 2KV
1000PF 250V 22MF 400V
1500PF 250V 33MF 250V
1800PF 160V 39MF 250V
2700PF 63V 47MF 250V

Any 10 @ £1.00

WIRE WOUNDS

2R 5W Thorn 3K 30p
2.2R 4W 16p
3.3R 9W 30p
10R 9W 18p
15R 17W 23p
22R 9W Fus. 25p
27R 7W Fus. 25p

36R 17W 23p
235R 9W Fus. 25p
220R 7W Fus. (Korting) 30p
270R 5W 15p
270R 7W 16p
280R 17W 23p
330R 5W 15p

4K7 7W Fus. 25p
5K1 7W 16p
8K2 7W 15p
8K2 9W 8K Thorn 20p
10K 7W 15p
10K 9W 16p
39K 4W 15p

10 Spark Gaps 1.00
10-16 pin Quil IC Socket 90p
20 Assorted TV Knobs 90p
10-16 pin Quil to Dil IC Socket 90p
100 Mixed Diodes 1.00
50 Mixed Mica Washers 65p
300 Mixed Resistors & Capacitors 1.50
10-16 pin Dil to Dil IC Socket 1.00
50 Electrolytics & 50 Capacitors 1.00
50 Mixed Poly Capacitors 1.00
30 Mixed Neons & Bulbs 1.00

Thorn Mains TX 3000/3500 10.00
Thorn Mains TX 8000/8500 10.00
Thorn S.O.P.T 8000/8500 3.50
Thorn Scan TX 3000/3500 6.00
Thorn EHT TX 3000/3500 6.00
Thorn LOPT 9600 12.00
ITT LOPT CVC1-9 9.60
Pye LOPT 713 10.00
Pye LOPT 725 9.85
Pye LOPT 169 9.70
GEC LOPT 3133 7.40
Diode Split LOPT AT2076/35 14.75
Sanyo LOPT AM-WM-21 6.75
Sanyo LOPT AM-WM-4 7.30
Thorn LOPT 1615 7.25
Thorn LOPT 1590/91 7.25
Thorn LOPT TX9 9.85
Thorn LOPT 9800 17.00

MULTISECTION CAPACITORS

100+150+150 16+16 450V 45p
200+150+350 350V 50p
220+47 350V 65p
200+150+50 350V 60p
200+200+100 350V 55p
200+200+100 350V 55p
32+32+16 325V 52p
200+200+100+32 275V 52p
200+200+100+32 350V 70p
100+50+150 350V 58p
400+400 200V 72p
32+32+16 350V 52p
200+32+300+100 2500+2500 (Thorn 8K) 63V 1.20
225+25 350V 50p
200+200+100 350V 70p
200+47 300V 1.80
200+100 325V 65p

ELECTROLYTICS

1MF 63V 20/£1
1.5MF 63V 20/£1
2MF 350V 10/£1
2.2MF 25V 20/£1
4MF 64V 20/£1
4MF 350V 10/£1
6.8MF 40V 20/£1
10MF 40V 20/£1
10MF 160V 10/£1
15MF 16V 20/£1
15MF 63V 20/£1
22MF 10V 20/£1
22MF 63V 20/£1
22MF 160V 10/£1
33MF 275V 10/£1
33MF 40V 20/£1
33MF 50V 20/£1
33MF 250V 10/£1
33MF 350V 10/£1
47MF 350V 10/£1
50MF 25V 20/£1
100MF 18V 10/£1

100MF 25V 10/£1
100MF 160V 10/£1
150MF 25V 20/£1
160MF 25V 20/£1
250MF 16V 10/£1
250MF 25V 10/£1
330MF 10V 20/£1
330MF 35V 10/£1
330MF 63V 20/£1
470MF 10V 10/£1
470MF 25V 10/£1
470MF 40V 10/£1
660MF 40V 10/£1
1000MF 10V 10/£1
1000MF 18V 10/£1
1500MF 16V 10/£1
1500MF 35V 10/£1
2200MF 25V 6/£1
2200MF 40V 6/£1

INTEGRATED CIRCUITS

BRC/M/200 1.00
BRC/M/300 1.00
ML237B 2.00
MC1358P 1.30
MC78M24 25p
SL432A 1.80
SAS590 2.60
SN15846N 60p
SN74123N 65p
SN74154N 1.40
SN76013ND/HS 1.80
SN76023N 1.80
SN76033N 2.00
SN76115 2.00
SN76660N 80p
SN76544N 1.20

TBA1200C 70p
TBA395 1.00
TBA480Q 1.40
TBA540 1.10
TBA1440C 1.00
TCA2705 1.05
TDA1035T 3.50
TDA2540 3.50
TDA2680 2.80
TDA290A 1.50
TDA3560 6.00
MC14426P 4.80
MC14429P 4.50
MC14514 5.00
SAA5010 6.00
TDA1170S 1.50

DIODES

AA112 8p
AA119 8p
AA143 8p
BA115 8p
BA154 8p
BB103 8p
BR303 46p
BT106 1.50
BY127 12p
BY204 26p
BY298 22p
BYX22/400 30p
IN60 8p
IN2070 8p
IN4001 4p
IN4002 4p
IN4003 4p
IN4004 5p
IN4005 5p
IN4006 5p
IN4007 6p

IN4007 6p
IN4742A 8p
IN5254B 8p
IN5249 14p
IS025 8p
IS131 8p
IS1658 8p
MR854 35p
MCR702 20p
MCR406 35p
TIC106C 40p
2N4444 1.50
Y827 80p
ZX150 12p
OA91 5p
MCR106/7 1.00
MCR106/8 1.50
TD3F800H 2.80
TD3F800R 3.00
BY255 30p

MAINS DROPPERS

Pye 78+161 50p
Pye 147+260 50p
RBM 250+14+58 63p
Thorn 56+1K+47+12 1.00
Thorn 50+40+1K5 60p
Thorn 250+14+58 (TV161) 63p
Pye 3R5+15+45 (713) 90p

EHT TRAYS

Thorn 3000 5.50
Thorn 8000 3.50
Thorn 8500 5.00
Thorn 9000 5.00
Thorn 900/950 3.00
Thorn 1500 3 stick 3.40
GEC 2100 5.39
Pye 713 4 lead 5.83
Pye 713 5 lead 5.97
Pye 725 6.35

THERMAL CUT OUT

Thorn 3000 Metal 1.45
Thorn 8/8500 Plastic 1.45

FUSES

50MA 10 for 70p
315MA A/S 10 for 50p
500MA 10 for 50p
1A 10 for 50p
2.5A 10 for 1.00
3.15A 10 for 1.00

250MA 10 for 65p
750MA 10 for 65p
7A 10 for 50p
10A 10 for 50p
10A 10 for 50p
50A 10 for 50p

AM-LS-200 Sanyo Scan Coil (mono portables) 2.50
M-LS 145 2.50
4-2761-44570 2.50
Thorn 4000 Coil L401 40p
Thorn 4000 Coil L701/2/3 12p
Pye 713 Coil L831/832 65p
Philips G8 Coil L482 Late Type 65p
Philips G9 Luma Delay Line 90p
Pye 713 Luma Delay Line 90p
Convergence Yoke Assy AT1023/05 5.90

SWITCHES ETC

Rank A823 4 P/B Assy 5.80
Telpro 4 P/B Assy 5.80
Thorn 3500 6 P/B Assy + Leads 1.75
ITT CVC9 On/Off Switch + Relay 90p
Philips G8 On/Off Switch 65p
Thorn 3/3500 A1 Switch 50p
Thorn 4000 A1 Switch 50p
Korting Shift Pot 50Ω 65p
Thorn 4000 Focus Pot 4.75

NOW! SAME DAY SERVICE

236 FURTHERWICK ROAD,
CANVEY ISLAND, ESSEX
Callers By Appointment

ADD 65p P&P, THEN 15% VAT.
ADD POSTAGE FOR OVERSEAS ORDERS. ORDERS WITH
AEROSOLS, PLEASE ADD 25p PER CAN.

If wish to pay by Access.

Access No.

Amount

NAME

ADDRESS

Signature

G.G.L. COMPONENTS

108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY
PHONE (0228) 20358

WHOLESALE COMPONENT STOCKISTS

INTEGRATED CIRCUITS			TRANSISTORS			LINE O/P TR.		NEW VALVES	
TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)	TYPE	PRICE (£)
LC7120	4.30	TBA480Q	1.40	TDA2591	2.50	AC127	.22	BC184L	.11
MC1730	4.50	TBA510	2.30	TDA2593	2.30	AC128	.22	BC208	.12
MC1327A	4.50	TBA520Q	1.00	TDA2600	4.30	AC128K	.30	BC212L	.10
MC1358P	1.80	TBA530Q	1.00	TDA2611A	1.50	AC141K	.30	BC213L	.10
MC1350P	0.90	TBA540Q	1.20	TDA2640	1.80	AC142K	.30	BC214L	.10
ML231B	1.95	TBA550Q	1.45	TDA3560	5.10	AC176	.28	BC237B	.11
ML232B	1.70	TBA560Q	1.45	UPC1156H	2.95	AC176K	.30	BC300	.25
MR475	2.00	TBA750Q	2.30			AC187K	.30	BC303	.26
SAS560S	1.85	TBA800	.80			AC188K	.33	BC337	.11
SAS570S	1.75	TBA810AS	1.15			AD149	.70	BC338	.10
SAS580	2.40	TBA820	1.15			AD161	.42	BC547	.10
SAS590	2.40	TBA890	2.95			AD162	.42	BC548	.10
SL901B	4.80	TBA920Q	1.50			AF126	.38	BC557	.10
SL917B	6.40	TBA950/2X	2.15			AF127	.36	BC558	.10
SL1327Q	1.30	TBA990	1.55			AU110	2.10	BD124P	.55
SN76003N	1.80	TCA270SQ	1.30			AU113	1.85	BD131	.33
SN76013N	1.80	TCA800	1.95			BC107B	.14	BD132	.33
SN76023N	1.80	TCA940	1.55			BC108B	.14	BD201	.70
SN76110N	0.90	TDA1002A	1.50			BC109B	.14	BD202	.70
SN76226DN	1.45	TDA1003A	2.80			BC139	.24	BD203	.70
SN76227N	1.00	TDA1004A	2.70			BC140	.26	BD204	.75
SN76660N	.65	TDA1035	3.20			BC141	.26	BD222	.50
SN76666N	.65	TDA1044	3.10			BC142	.23	BD232	.50
TN7120P	2.05	TDA1170	1.80			BC143	.25	BD233	.37
TA7130P	2.00	TDA1412	.90			BC147	.09	BD234	.40
TA7193P	4.20	TDA2190	3.20			BC148	.09	BD235	.32
TA7205AP	2.80	TDA2020	2.95			BC157	.10	BD236	.43
TAA550	.28	TDA2522	1.80			BC158	.11	BD237	.40
TBA120A	.62	TDA2523	2.25			BC159	.11	BD238	.34
TBA120AS	.70	TDA2530	2.10			BC160	.22	BD410	.50
TBA120B	.90	TDA2532	2.20			BC172	.10	BD434	.50
TBA120SB	.90	TDA2540	1.95			BC177	.22	BD437	.70
TBA120U	1.00	TDA2560	1.80			BC182	.10	BD438	.78
TBA395	1.25	TDA2581	1.70			BC182LB	.11	BD707	1.05
TBA396	.85	TDA2590	2.20			BC183LB	.11	BDX32	1.36

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US		TV ELECTROLYTICS		PUSH BUTTONS/TUNERS		THIS IS ONLY A VERY SMALL PART OF OUR RANGE, WE WILL BE DELIGHTED TO SEND DETAILS OF OUR WHOLE RANGE	
REBUILT TUBES WE STOCK "TELETRONIC" TUBES (25 years in business) *Carriage included. We can rebuild over 700 types of PIL tubes - List on Request. Mullard Tubes available. Please ask for quotes.		DECCA 30(400/400)350V	2.55	DECCA/ITT 4W	6.45	ORDERING Please Add 50p For P/P U.K. Export Orders - Cost, Add 15% To This Total. DELIVERY BY RETURN ON ALL STOCK ITEMS.	
EXAMPLE PRICES:		DECCA 80(100(400)350V	2.90	DECCA/ITT 6W	7.40		
A56 120X	£38.00*	PHILIPS G8(600)300V	2.00	PYE201 6W	15.80		
A66/67 120X	£45.00*	PHILIPS G9(2200)63V	1.15	PHILIPS G8S/L	13.50		
A61 120WR	£23.00*	PHILIPS G11(470)250V	2.20	PHILIPS G8S/Q	12.00		
A66 510X	£63.00*	PYE 6917(2000-300)350V	2.10	HITACHI 4W	8.50		
		RBMA823(2500/2500)30V	1.10	ITT CVC5 7W	9.40		
		THORN1400(150/100/100/100/150)320V	2.40	ITT CVC8/9	12.80		
		THORN3500(175/100/100/400)350V	2.25	PHILIPS G11 (TIP SW.)	23.80		
		THORN3500(1000)70V	85	1043/05TFK	7.95		
		THORN9000(400)400V	2.75	U321 TFK	7.75		
				U322 TFK	7.40		

SPECIAL OFFER SURPLUS STOCK TO CLEAR			
AC127	0.150	BFX68	0.300
AC128	0.150	BY560	0.140
AC187	0.150	BFY51	0.140
AD149	0.480	BT106	0.900
AD161	0.220	BT116	0.900
AD162	0.220	BT119	1.100
AF139	0.220	BT120	1.100
AF239	0.220	BU126	0.700
AU106	1.000	BU205	0.750
AU110	1.000	BU208	0.800
BC107	0.070	BU208A	0.850
BC108	0.070	BU326	0.850
BC109	0.070	BU407	0.750
BC147	0.055	BU526	0.800
BC148	0.055	BY127	0.800
BC149	0.055	BY133	0.080
BC157	0.055	BY164	0.220
BC159	0.055	QA47	0.060
BD131	0.250	OC28	1.000
BD132	0.250	OC29	0.800
BO135	0.200	OC35	1.000
BO136	0.200	R2008B	0.800
BD137	0.200	R2010B	0.800
BD138	0.200	TBA520	0.750
BD139	0.200	TBA530	0.750
BD140	0.200	TBA540	0.750
BD144	1.100	TBA550	0.750
BD150	0.800	TBA560	0.700
BD157	0.380	TBA800	0.350
BD158	0.380	TBA810S	0.600
BD159	0.400	TBA820	0.750
BD166	0.300	TBA920	0.800
BD175	0.300	TBA950	0.800
BD177	0.300	TBA990	0.800
BD179	0.320	TCA800	0.800
BD181	0.450	TCA940	0.850
BD433	0.320	TDA1170	0.900
BD535	0.400	TDA2522	0.800
BD536	0.400	TDA2530	0.800
BD537	0.420	TDA2532	0.750
BD538	0.420	TDA2540	0.700
BDX65	0.800	TDA2560	0.700
BF180	0.150	TDA2593	0.800
BF181	0.180	TDA2640	0.800
BF194	0.050	TIP29	0.150
BF195	0.050	TIP41A	0.220
BF196	0.060	TIP42A	0.220
BF199	0.060	TIP2955	0.340
BF200	0.160	TIP3055	0.340
BF258	0.180	2N3053	0.180
BF337	0.200	2N3054	0.400
BF338	0.200	2N3055	0.320
BF362	0.300	2N3440	0.580
BFX67	0.150	2N3442	0.850
		2N3771	0.950
		2N3772	1.000
		LM309K	1.000
		7805	0.350
		7812	0.380
		7818	0.380
		7824	0.380
		7905	0.350
		78L05	0.300
		78L12	0.300
		78L18	0.300
		78L24	0.300
		2SC495	0.700
		2SC1306	1.000
		2SC1969	1.300
		2SC2029	1.200
		2SC2078	1.200
		MB3712	1.500
		TA7205	1.500
		UPC575	1.000
		LM380	0.500
		LM381A	0.600
		74123	0.160
		74141	0.250
		74393	0.500
		74LS09	0.120
		74LS164	0.300
		74LS197	0.350
		74LS221	0.420
		74LS240	0.580
		74LS244	0.580
		SOCKETS	
		8 PIN	0.070
		14 PIN	0.080
		16 PIN	0.090
		18 PIN	0.120
		20 PIN	0.140
		22 PIN	0.160
		24 PIN	0.180
		28 PIN	0.200
		40 PIN	0.250
		LED	
		3mm Red	0.050
		3mm Yellow	0.100
		3mm Green	0.100
		5mm Red	0.050
		5mm Yellow	0.100
		5mm Green	0.100
		ELECTROLYTIC	
		4700UF	0.850
		16V CAN	0.200

PRECISION VISION LTD.

For modern used colour TVs.

Working or untested. Most makes and tube sizes available. All working TVs are refurbished to an extraordinary high standard.

0865-750212 01-200 7337

HEAD OFFICE MANOR BUILDINGS LONDON BRANCH

67 LONDON RD 21 GOLINDALE AVE

HEADINGTON, LONDON NW9

OXFORD

A.B.C. TRADE SALES

COLOUR T.V.'s

Philips G8, Pye, Decca 30's, Thorn's 3000's, 3500's, 8000's

Prices start from £12 - Working sets from £20

Hundreds of Mono T.V.'s from £2.00

Jap. sets from £30.00

Special prices for quantity

9,000 sq. feet Warehouse

83 SHOWELL ROAD, BUSHBURY, WOLVERHAMPTON, STAFFS.

Tel. Wolverhampton 722637

COLOUR TELEVISION & MUSIC CENTRE

Old Mixon Crescent, Old Mixon Trading Estate,
Weston Super Mare – (15 mins. past Bristol on M5)

NOT EX-RENTAL COLOUR TELEVISIONS SOLID STATE

★ *FANTASTIC OFFER* ★

All in perfect running order

PYE CHELSEA

18", 6 Button, Sliding Controls,
Brilliant Condition

£45.00
Inc. VAT

THE ABOVE ARE WORKS MODIFIED FOR ANY PART OF THE WORLD
VHF - UHF

PYE 721

20"-26", could be mistaken for new

£65.00 each
Inc. VAT

PYE 725

20" as new

£75 each
Inc. VAT

Minimum 5 sets

★ ★ ★

BIG REDUCTIONS FOR EXPORT ORDERS OVER 100 SETS

ALL OTHER MAKES IN STOCK OFF THE PILE

★ ★ ★

(G.E.C., SOLID STATE, FERG 9000 & 8500, G8's, DECCAS etc.)

Ring Now W.S.M. 413537

MANTEL

Manchester's No. 1 in Ex-Rental TVs
Over 2,000 TVs in stock
Special Offer on Working Colour TV's

All sets are Serviced with repolished cabinets ready for sale

Some Examples of UNTESTED TVs available

Philips G8 550s	22/26	£45
Philips 18"		£40
Philips G8 520s	22/26	£35
GEC S/State	from	£35
Thorn 17" 8000		£30
Decca 30	18/20/22/26	£30
Japanese	from	£30

Thorn	10 for	£125
Philips	6 for	£90
Bush	6 for	£80
GEC	6 for	£60
Decca	6 for	£60
Mono TVs avail. s/s		£4 each
New TV trolley stands.		
All sizes		£4.95
All Prices subject to V.A.T.		

Many other makes available from £25

Discount on quantity

Ex Equipment Panels & Tubes Available

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

419 Barlowmoor Road, Chorlton, Manchester 21 2ER.
Tel: 061 861 8501

TOP TWENTY T.V. SPARES

- | | |
|--|-------|
| 1. Philips G8 LOPTX (genuine Philips) | £7.50 |
| 2. Decca 30 Series LOPTX (genuine Decca) | £7.00 |
| 3. Decca 100 Series LOPTX (genuine Decca) | £6.50 |
| 4. ITT CVC 25/30/32 LOPTX (genuine ITT) | £7.00 |
| 5. Pye 713/725/731 Vis Gain Module (replaces expensive 212-27327) | £6.50 |
| 6. 5 x Universal Aerial Socket Kit (replaces most UK and Continental skts) | £5.50 |
| 7. 10 x BU208 | £7.50 |
| 8. 10 x BU208A | £8.50 |
| 9. ITT CVC 5/8/9 EHT Tray | £3.00 |
| 10. Grundig 5010/5011 EHT Tray | £3.00 |
| 11. Decca 1730/1830 Doubler | £2.00 |
| 12. Decca 80 Series EHT Tray | £3.00 |
| 13. GEC 2040 (Hybrid) EHT Tray | £3.00 |
| 14. 50X BY127 Diodes | £3.00 |
| 15. Thorn 1500 (5 Stick) EHT Tray | £3.50 |
| 16. Thorn 8000 Doubler | £2.00 |
| 17. Thorn 1400 EHT Tray | £2.00 |
| 18. Thorn 1690/91 LOPTX | £7.00 |
| 19. Philips G9 EHT Tray | £3.50 |
| 20. ITT Universal EHT Tray | £5.25 |

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.

Please add 15% VAT and 90p P & P

QUICK SAVE T.V. SPARES,

Muxton House, Muxton, Telford, Salop.

REG. OFFICE ONLY
 CALLERS STRICTLY BY APPOINTMENT
 UK ONLY

COLOUR SETS GALORE

Hundreds in Stock.

From £20. Guaranteed Complete.

Mono's and non-complete sets from £3.

Most makes available.

QUALITY COLOUR TUBES

Reconditioned and used tubes.

From £10 Guaranteed.

Don't delay, ring today.

ALPHA TUBES (DUNSTABLE)

53 Lowther Road, Dunstable.

Tel. (0582) 68934

TRADE

APOLLO

HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Delivery 2-3 days.

Just phone for a quotation. Delivery Manchester area free same day. Two year guarantee. Fitting while you wait or in your home £20 extra. Also PIL types & Toshiba.


18"	A47 - 342x343x	£37.00
19"	A49 - 120x/192x	£37.00
20"	A51 - 220x/110x	£38.00
22"	A56 - 120x/123x/140x	£38.00
25"	A63 - 120x	£39.00
26x	A66 - 120x/A67 - 120x/140x/150	£39.00

17" Ferguson Colour T.V.'s fully serviced, ideal as second set for kitchen, bedroom or caravan. £75 inc. delivery anywhere.

Philips Video Spares Available.

061 799 0854 24 hour answering service.
43 Clarke Cres, Little Hulton,
Nr. Manchester M28 6XM.

NEW

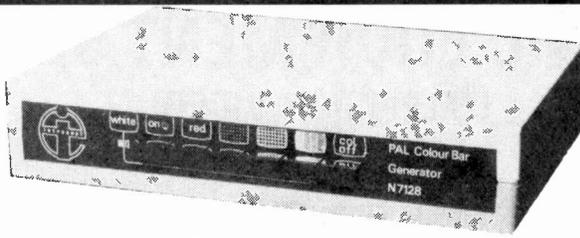

N7128 COLOUR BAR GENERATOR

New improved design with additional features.

- ★ Six Standard Test Patterns viz. Colour Bars, Red Raster, Linear Grey Scale, Cross Hatch, Dots, White Raster.
 - ★ All monochrome patterns available with or without burst signal (for checking colour killer action etc).
 - ★ Crystal controlled sub-carrier, Line and Field frequencies.
 - ★ Three outputs to rear panel: Video at 1V P to P into 75ohm, 800Hz (approx), sine wave audio and modulated UHF (VHF available) 4mV at 75ohm.
 - ★ 6MHz (adjustable to 5.5MHz) intercarrier sound.
 - ★ Front panel LED to indicate "Power On".
 - ★ Integral re-chargeable ni-cad battery plus mains unit/charger.
 - ★ Fully built, tested and guaranteed for 12 months.
- PRICE £85.00.**

N7118 COLOUR BAR GENERATOR KIT

- ★ Five Standard Test Patterns viz. Colour Bars, Red Raster, Linear Grey Scale, Cross Hatch and White Raster.
 - ★ Crystal controlled sub-carrier, Line and Field Frequencies.
 - ★ UHF Output (VHF available).
 - ★ Integral Ni-cad Battery and mains unit/charger.
 - ★ Optional integral sound and video board add-on kits available @ £8.95.
- Still available at special price **£39.95.**

Please add 15% VAT + £2.05 postage and packing per Generator.

Please allow 14 days for delivery.



**INTRACEPT ELECTRONICS LTD., 203 PICTON ROAD, LIVERPOOL L15 4LG.
TEL: 051-733 3042**

TV TUBES TUBE POLISHING WORKING TV's WORKING PANELS FREE DELIVERY*

Quality, High Temperature Reprocessing

Colour Tubes	One year guarantee (optional extension up to three years)	Two year guarantee (optional extension up to four years)
Delta		
90° up to 20"	£26	£29
90° up to 22"	£30	£33
90° up to 26"	£32	£35
110° 26"	£33	£36
(fast heat, narrow neck)		
In Line & PIL		
Up to 20"	£36	£42
Up to 22"	£38	£44
Up to 26"	£40	£46

Please add £12 plus VAT for optional guarantee on any type of colour tube.

MONO TUBES (One Year Guarantee)
A50-120W/R £12, A61-120W/R £13, Mono Portables £16
All tubes exchange glass required.

FOLOWING ITEMS CALLERS ONLY

Solid state working colour TV's, with well view tubes fitted (1 year guarantee on tubes) from **Only £45**

Working TV Panels at Reasonable Prices

Your good, working tubes with scratches or small chips, can be **POLISHED** with our purpose built polishing equipment. **Only £7 per tube.**

Delivery Service up to 40 miles from Luton. Fixed Charge **£3.** *Free Delivery for tube orders over £50 + VAT.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

Send for a fully comprehensive price list and a wall chart of approx 1700 Colour Tube Types that can be processed by us.

WELL VIEW

114-134 Midland Rd.
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:

Retach Ltd., Northwood, Middx. Tel. 9684-27019
West One Distributors Ltd., Gt. Missenden, Bucks. Tel. 024-06-3609
Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901
Daverntry Rentals, Daventry, Northants. Tel. 03272 77436
S.S. TV Services, Bradford, Yorks. Tel. 0274-498180

Please note that we have no connections whatsoever with any other business having similar name to ours.

NOVA COLOUR T.V.'s

ALL MAKES OF EX
RENTAL COLOUR T.V.'s
FROM £10.00 UPWARDS
T.V. STANDS, PANELS
AND T.V. TUBES
ALSO JAPANESE TUBES
CALL ON US AND LOOK AROUND

NOVA COLOUR
HENRY STREET
PARK GATE
RAWMARSH
ROTHERHAM

ELECTRONIC EQUIPMENT SERVICING

(TELEVISION/VIDEO)

full-time College course

TRAINING INVOLVES A HIGH PERCENTAGE OF WORKSHOP FAULT DIAGNOSIS ON MONOCHROME & COLOUR TELEVISION EQUIPMENT. CLOSED CIRCUIT TV & VIDEO CASSETTE RECORDER PRINCIPLES ARE INCLUDED IN THE COURSE

15 MONTHS COURSE

for beginners to include Electronic Fundamentals

6 MONTHS COURSE

for BSc, HND, CGLI, TEC and similar applicants

**COLLEGE
DIPLOMA
AND
TEC**

Next two courses commence on September 19th and January 9th.

Also courses in Computers/Microprocessors, and Robotics leading to Technician Education Council Cert. and Higher Cert. awards.


Prospectus from:

LONDON ELECTRONICS COLLEGE (Dept T3/4)
20 Penywern Road,
Earls Court, London SW5 9SU
Tel: 01-373 8721

UNIVERSAL PROGRAMME SELECTOR FOR VARICAP TUNING

UK Regd. Design No. 1006611

6 way interlocked d.p. switch 100 K tuning potentiometers
Top quality through hole plated pcb
Dimensions: 5" by 2½" by 1"
Ideal for replacement when original parts are obsolete or unobtainable
Template guide supplied for drilling of your own fascia design
Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification
All orders despatched same day

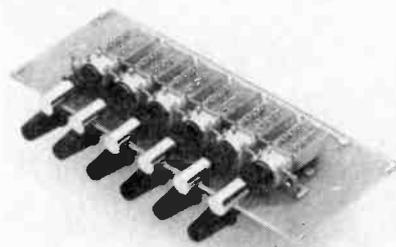

DIRECT REPLACEMENT FASCIA/MOUNTING KITS

- Type 30-80 Replaces 7 piano-key unit as fitted to Decca/Telefunken 30 and 80 chassis
Type 30-C Replaces 7 piano-key unit as fitted to Decca console using long perspex illuminated control panel
Type 100 Replaces 8 position touch tune selector (AEG SAS 660 SAS 670) as used in Decca/Telefunken 100 chassis
Type CVC8-9 Replaces 5 rectangular push button plus thumbwheel as used in ITT

SELECTOR **£11** + VAT

FASCIA/MOUNTING KITS (each) **£2** + VAT

ALDERSON-JAMES LTD

160 KINGS ROAD ● HARROGATE ● N. YORKS
TEL: HARROGATE (0423) 60058 HG1 5JG

HIGH GAIN AERIAL BOOSTERS

B45 H/G UHF Television – Tunable over the complete UHF band. Gain above 20dB, noise 2.8dBs.

B14 – Band 3 VHF Television – Tunable over the complete Band 3 (Channels (E) 5 to 13). Also covers Aircraft & 2 meter Amateur Bands. Gain above 28dBs. Noise 2.8dB.
PRICE each £8.70.

AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

B45 – For Mono or Colour this is tunable over complete UHF television band.

B11 – For stereo or standard VHF/FM radio.

B12 – for VHF television band 1 & 3.

All amplifiers are complete and ready to use Battery type PP3 or 8V to 18V DC next to the set type fitting.
PRICES £6.70 each.

AERIAL SPLITTERS

2 way T-TYPE **£2.70** each

Goods despatched on receipt of order.

All Prices Fully Inclusive. P & P per Order 30p. S.A.E. for Leaflets. Access Cards.

ELECTRONIC MAILORDER LTD,
62 Bridge St, Ramsbottom, via Bury, Lancs. BL0 9AGW.
Tel Rams (070 682) 3036.

THE NO. 1 SOURCE IN THE SOUTH

**GOOD STOCKS OF
MODERN COLOUR
UNBEATABLE PRICE AND QUALITY
DON'T DELAY RING TODAY**

TELETRADERS

ST. LEONARDS WAREHOUSE
ST. LEONARDS ROAD, NEWTON ABBOT, DEVON
Telephone: (0626) 60154

VISIONTEL

**BEST QUALITY EX RENTAL SETS FROM
£10 HERE IN CENTRAL LONDON!**

**Hundreds of sets always in stock
AT VERY COMPETITIVE PRICES**

For Example:

Philips G8
Philips 550
Thorn 3500

Untested
£15
£20
£10

Good Workers
£25
£35
£25

ALL PRICES SUBJECT TO VAT

**We also have PYE, DECCA, GEC, ITT, GRUNDIG, JVC,
PHILIPS G9 + G11, THORN 9000 and PORTABLE TVs**

**FOR FURTHER DETAILS TELEPHONE 328 3787
OR COME ALONG TO
55 KILBURN HIGH ROAD, NW6**

Freeway Components

We can now offer our **post free** service to customers nationwide.

E.H.T. Trays		LOPTS	
Decca 100	7.00	B+O 3000 +3200 EHT	17.00
Decca 1730/1830	6.00	B+O 3100 + 3300	
Thorn 3000/3500	9.00	3400 EHT	19.50
Thorn 8000	4.90	B+O 3500 + 3600	
Thorn 8500	7.95	4000 + 5000	
Thorn 9000	8.50	6400	11.25
Universal Tray	6.20	Decca 30	9.50
		Decca 100	8.00
		Decca 1700	9.50
		Decca 1730 + 1830	9.00
		Dynatron TV202 + 203	10.25
		GEC 2623 20AX	
		Solid State	8.40
Press Buttons		ITT CVC 5	10.00
Hitachi 4 way 190	8.00	ITT CVC 25+30+32	8.40
Nat. Pan. 4 way	8.00	ITT CVC 45	8.50
Decca 4 way 20 Mono	6.60	Philips G8	8.50
Philips G8:		Philips G9	9.00
520 Square	10.50	Philips 210 Mono	10.75
550 Sloping	18.00	Philips 570	9.50
Decca 6 way		Pye 169+569+769	10.25
1730, 30, 80, 100	7.50	Pye 691+697 PCB	14.25
ITT 6 way		Pye 713+715+717	9.50
CVC20, 30, 32	7.50	Pye 725	10.20
GEC 6 way 2110	8.40	Pye 731+735+737+741	10.50
GEC 6 way 2136/7	8.00	Rank T20A	11.50
Pye 6 way 725	13.50	Rank A774	11.00
Pye 6 way		Rank Z718 20"-26"	23.00
715, 207 Chelsea	11.50	Rank Mono Portable 14"	9.50
Rank 6 way T20A	9.50	Tandberg 110°	11.25
GEC 7 way 2112	12.50	Thorn 1615	9.00
Thorn 9000 complete	15.50	Thorn 1690+1691	8.50
(switchbank only)	8.00		
		SPECIAL OFFER	
Co-Ax. Plugs		06 TUNER AEG Made	7.00
Box of 100	12.50		

Add 15% V.A.T. and send cheque or postal order to:

Freeway Components,

The Airport, Weston Super Mare, Avon. BS24 8RA.

Remember that our prices are Post Free. Any queries, quotes or price breaks
- Telephone 0934-419147.

TELEVISION TUBE SHOP LTD

BRAND NEW TUBES AT CUT PRICES

A31-19W/20W	19.95	230DB4CT468.....	31.00
A31-120W/300W.....	17.95	240DB4/240AB4A....	22.00
A31-410/510W	17.95	CT507 equiv	21.95
A34-100W/510W	18.50	310DGB4/DMB4.....	23.00
A34-514W	24.25	310EUB4	19.95
A38-160W/170W	17.50	310EU B4A	18.50
A44-120W/R	25.00	310EYB4	18.75
A50-120W/R	19.00	310FXB4	17.50
A61-120W/R	21.00	310GNB4A.....	31.00
9AGP4	£21.82	310HCB4.....	31.00
190AB4/C4	23.00	340AB4	22.50
		340AYB4.....	30.00
		340AXB4.....	30.00
		340RB4/CB4.....	26.00
		340AHB4	26.00
		RIGONDA 6".....	14.00

**Some Rebuilt Japanese
& European Types
Available from
£14.00 +VAT £2.10**

COLOUR TUBES

(NEW & MULLARD/THORN COLOREX)*

12VARP22	£62.50	A56-120X	£54.00
330AB22	73.50	A56-410X	64.00
A44-271X	60.00	A56-500X/510X	63.00
A47-342X	61.00	A63-120X	63.00
A47-343X	61.00	A66-120X	65.00
A49-191X	53.00	A66-140X/410X	70.50
A51-161X	70.00	A66-500X/510X	65.00
A51-220X	55.00	A67-120X	65.00
A51-500X/510X	64.50	A67-140X/200X	69.50
A51-570X	73.00	A67-150X	75.00

Old Bulb Required for 110° Colorex

ADD 15% VAT TO ALL THE ABOVE PRICES.

ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED
TELEVISION TUBE SHOP LTD

52 BATTERSEA BRIDGE RD., LONDON, SW11.

Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10.

SETS & COMPONENTS

**SOUTH LONDON'S
Ex Rental TV Dealers**

COMPLETE NON-WORKERS

PHILIPS G8 £12
 DECCA BRADFORDS £10
 PYE 725 SERIES £14
 GEC 2110 SERIES £14

Clearing Pye 205's £5 each
 Mono £2 each or 12 for £20
 Working Sets (Colour) from £25
 G8's £30
 Philips 1700 videos complete non
 workers £20

Also spare panels, secondhand tested
 tubes etc.
 (Prices exclusive of VAT)

SOUTH LONDON TELEVISION
 45 Griffiths Road,
 Wimbledon, London SW19
 (01-543 5437)

CASED ISOLATION TRANSFORMERS 500w max,
 suitable TV work £8.00 + £2.85. Working test equip-
 ment. Meters. P.S.U.'s etc. S.A.E. Lists: S.H.E., 5 St.
 Joseph's Park, Ballycruttle, Downpatrick, BT30
 7EN.

**RE-GUNNED
TUBES
DONCASTER**

A56-120 £30
 A51-110 £30
 A49-191 £30
 A47-342 £30
 A47-343 £30
 A44-271 £30
 A66-120 £35
 A67-120 £35

Includes VAT

No need to spend £5 returning old glass
 if you buy from us (except in-line).
 Tubes delivered and insured within a few
 days of receipt of cheque.

£5 delivery per tube, 2 for £9 including
 Scotland and N. Ireland.
 Discounts for more than 2.

**CASH & CARRY
SPECIAL**

Up to 22" Reguns £25 incl. VAT. 26" £30.
 They are good quality seconds.
 Phosper dots etc. which can be viewed
 before purchase.
 With one year guarantee.
 (Limited amount)

U-View (Tubes)

29 Warmsworth Road, Doncaster,
 Yorks DN4 0RP. 0302 855017.

Open 7 days Callers ring first.

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £5.64 per single column centimetre (minimum 2.5 cms). Classified advertisements 33p per word

CLEARANCE SALE

LARGE QUANTITY OF GOOD CLASS COLOUR TELEVISIONS

BUSH, PYE, GEC, THORN, PHILIPS ETC.
 Excellent Cabinet Condition.

Genuine Change Over TV's and Repossessions.

LARGE QUANTITY SOLID STATE BUSH £10 Each

(Minimum quantity 5)

GEC HYBRID £5 **PYE HYBRID £5** **MONO £3**

100's to choose from!!

We export large quantities of TV's weekly. Can we help you?
 Discount on Quantity Orders.

OVER 1,000 MONO TV's IN STOCK FROM £3.

100's colour tubes suitable for reconditioning. Working colour TV's to order ie.
 Bush 20"/22" 21.C. excellent picture, ready to sell. Only £39.

CALL AND SEE OUR SELECTION

WHITE GOODS

All types of Washing machines, Vacs, Fridges, Cookers, etc. Hoover Auto's, Servis,
 Hotpoint, Hoover Uprights, Vacs. 500 always in stock. Fully reconditioned Hoover
 Twin Tubs and Upright Vacs, all models. Phone for details.
 PAY US A VISIT AND YOU WILL NOT BE DISAPPOINTED.

N.W. ELECTRONICS

BOLINGBROOKE STREET (PICKFORD BUILDINGS), BRADFORD 5.
 3 minutes from Motorways. Telephone 0484 714413.

EAST ANGLIA BARRY TV SERVICES

Good quality working colour televi-
 sions (from £35 plus VAT) straight from
 our retail shelves, (with good tubes &
 cabinets). Available at all times -
 delivery available anywhere.

Contact **John, Dave or Steve on**
Cambridge 69215
or Ely 61462

Your Satisfaction Is Our Concern.

WE HAVE MOVED TO NEW PREMISES TEST EQUIPMENT

UHF T.V. Pattern Generators
 Crosshatch & 4 patterns £17.25
 As above but with Greyscale £18.50
 Prices include P&P and VAT.

Also available:

PAL COLOUR BAR GENERATOR
 CAPACITANCE METER
 TRANSISTOR TESTER
 S.A.E. for prices and full details.
 The above items are not kits.
 C.M.J. ELECTRONICS
 Unit 8, 16 Union Mill St., Horseley Fields,
 Wolverhampton, WV1 3DW.
 Tel. (0902) 871563

COLOUR TV PANELS Fully Tested & Working

	IF	CDA	Decoder	LTB	Line Board	Frame Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-	-
DECCA 13/30	3.00	-	5.00	5.00	-	-	4.00
BUSH 'A'	2.00	-	5.00	5.00	2.50	-	2.00
THORN 8-8½"	-	-	7.00	5.00	-	-	3.00
PYE 205	3.00	3.50	5.00	8.00	-	2.00	-
THORN 3+3½K	3.00	-	5.00	8.00	-	-	10.00
G8	6.00	-	8.00	5.00	15.00	-	5.00
BUSH twin chip decoder	10.00	-	-	-	-	-	-

Post & packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

26" CRT's fully tested £10

fitted with
 brand new
 transformer

LAVITE LTD.,

Viaduct Mills, Milnsbridge, Huddersfield. Tel: 0484-643273

Callers by appointment only.

CAMPBELL ELECTRONICS LTD.

Distributors of specialist spares to
 radio and television service depts.

We stock semiconductors, I/Cs, special
 T.V. and audio spares, service aids, rebuilt
 CRTs etc.

Fast off the shelf delivery of stock items.
 Send S.A.E. or telephone for full catalogue
 and price list.

CAMPBELL ELECTRONICS LTD.,

Unit 5, Heath Hill Estate,
 Dawley, Telford, Shropshire.
 Telephone Telford (0952) 502422.

SERVICE PAGES

(minimum 12 words), box number 60p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).

RANK BUSH MURPHY TV PANELS

Repair, exchange, sale service, same day return where possible. 718 chassis lopt panel charges reduced. Also new boards available for T20/22 chassis. Genuine RBM technology.

T. K. Panels Service,
31 Bronte Paths,
Stevenage, Herts.
Tel. (0438) 61567.

TRENT TUBES

31 Radcliffe Road,
West Bridgford,
Nottingham.
0908 613329

IN LINES **NOW** P.I.L.s
AT
CASH AND CARRY
PRICES

TWO YEAR GUARANTEE FOUR YEAR OPTION EXTRA

A61-161x
480 DYB 22 510 CJB 22 510 JCB 22
610 UP4 22 12 VARP 22 510 HWB 22

ONLY **£35.00** exchange + VAT

470 ELB 22 680 HB 22 560 TB 22
560 AKB 22 470 ESB 22

ONLY **£38.00** exchange + VAT

A56-510x A66-510x
510 JKB 22 510 JEB 22

ONLY **£40.00** exchange + VAT
MANY MORE TYPES AVAILABLE.
PLEASE ENQUIRE FOR PRICES

ALL standard DELTA
Colour Tubes

ONLY **£25.00** exchange + VAT
on our Cash & Carry trade counter

TWO year standard GUARANTEE
Four year optional extra

ALL TUBES

- ★ Fitted with High Definition guns
- ★ High Temperature pumped 385°C
- ★ Electronically and Picture tested
- ★ Delivery service available
- ★ Quantity Discount
- ★ Suppliers to Major national companies
- ★ Automated Computer controlled production ensures Quality & Reasonable Prices
- ★ VDU and Mono's certainly
- ★ Technical Advice service available.

NOW YOU HAVE SEEN THE REST
GET THE BEST FROM TRENT TUBES

MONITOR TUBES

"GREEN"

12" 110°

AW31 - 550GH

MEN-TU ELECTRONICS LTD.
SALTERNS LANE,
FAREHAM, HANTS.
Tel: 0329 235116.

LOOK TOP QUALITY SETS LOOK


MAKES	NON-WORKERS	WORKERS
Philips G8's 2 Chip Bush/Murphy	SINGLES £18 FIVES £14 TENS £13	SINGLES £30 FIVES £26 TENS £25
Thorn 3000, 3500 Thorn 8000, 8500	SINGLES £18 FIVES £16 TENS £14	SINGLES £35 FIVES £30 TENS £25
Thorn 8800, 9000, 9800 Touch tune sets etc.	SINGLES £35 FIVES £30 TENS £28	SINGLES £40 FIVES £38 TENS £35
GEC Solid State All types	SINGLES £25 FIVES £20 TENS £18	SINGLES £40 FIVES £35 TENS £28
ITT CVC5 ITT CVC8/9	SINGLES £18 FIVES £16 TENS £14	SINGLES £40 FIVES £35 TENS £28

MONO SINGLE STANDARD
Mono TV's in batches of 20 @ £2.50

SOME SETS ONLY £10 IN QUANTITY
ALL OTHER MAKES AVAILABLE ON REQUEST.

SPARE PARTS & PANELS AVAILABLE AT
VERY COMPETITIVE PRICES.
ALSO SECONDHAND TUBES, AERIALS,
STANDS ETC.

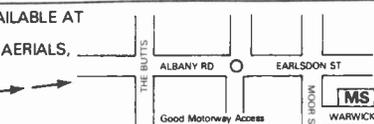COVENTRY BRANCH MAP:
M S ELECTRONICS
UNIT 1
WARWICK STREET
EARLSDON COVENTRY
TEL: (0203) 714213



OPENING HOURS:
9.30-1.00/2.00-5.45
CLOSED ALL DAY THURS
AND SUN.

GLASGOW BRANCH:
72 ROBERTSON ST.
GLASGOW
SCOTLAND
TEL: (041) 221-2146

N.B. Note to give prompt service, please telephone to order
in advance to avoid disappointment.

The VINTAGE WIRELESS COMPANY

NOSTALGIA - COLLECTING
1900-1950s

Publishers of 'The Antique Wireless Newsheet'
(Sample on Request)

Suppliers of: ● Valve Radio sets
& Amplifiers



- Valves, Components
- Repairs & Restorations
- Service Data & Manuals
- Historical Data
- New and Used Books/Magazines

The complete service for the collector and enthusiast
of Vintage Radio.

THE VINTAGE WIRELESS COMPANY

64 Broad Street, Staple Hill, Bristol BS16 5NL
Tel: Bristol (0272) 965472 - 24 hour Ansaphone, Closed Mondays.

WIZARD DISTRIBUTORS MANCHESTER

SPECIALIST DISTRIBUTORS TO THE TRADE OF
T.V. & VIDEO SPARES.

WE STOCK A FULL RANGE OF PARTS &
COMPONENTS INCLUDING C.R.T.'s
RANK - THORN - PHILIPS - ITT - DECCA -
GEC ETC.

THANDER & LEADER STOCKIST
TRADE COUNTER OPEN: 9-4.30
CATALOGUE ON REQUEST.

Mail Order Enquiries Welcomed
EMPRESS STREET WORKS,
EMPRESS STREET,
MANCHESTER M16 9EN.
TEL: 061-848 0060

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

TRADE TV's

For the best quality at the cheapest
prices in Nottingham.

CASTLE TV

100s of ex-rental sets in stock.
S/S colour from £12.50
S/S mono from £3.00

TV Sales & Spares to the Trade.
346 Radford Road,
Nottingham.
Tel. Mr. Atkins
Nottingham 785321.

TRADE COLOUR TV's

Working sets from £20 + VAT
In line working sets from £60 + VAT
Complete sets from £12 + VAT
Various panels available
e.g. Bush Decoder working £9.50 + VAT

Discount for Quantity
Phone for details:
NOTTINGHAM 585484

SETS & COMPONENTS

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

TELEVISION

IRISH T.V. DEALERS

(No. 1 for s/hand T.V.s)

1. 400 sets to choose from.
2. Most leading makes sold.
3. Fresh stocks weekly.
4. Delivery to any part of Ireland.
5. All sets with VHF/UHF tuners.
6. Colour from only £70 mono from £15.

Visit our new spacious warehouse:

TELE SPARES LTD.
Unit 113 Elm Road, Western Ind. Estate,
Dublin 12.
Tel: 01 521756/521211.

TELEVISION TUNER

REPAIRS ALL TYPES
BRITISH, EUROPEAN,
JAPANESE ETC.

MEN-TU ELECTRONICS,
SALTERNS LANE,
FAREHAM, HANTS.
Tel: 0329-235116.

JAPANESE COLOUR TV's, Hitachi, Sony, Panasonic, Mitsubishi, Toshiba, Sharp. Colourland TV. Trade Only. 0484 863489.

RANK BUSH MURPHY TRANSFORMERS

LINE OUTPUT TRANSFORMERS

Z718 (T703A, T706A)

(1) New (Complete) £20.50

(3) Less Focus Module and Rectifier £10.50

Z718 SPARES (T703A, T706A)

Pri. - £5.50, Sec. - £6.00,
Rectifier - £3.00, Lead - £2.50

T20, T22 (T705A) £9.00

T26 (T705B) £9.50

Switch-mode Transformers

T114 A/B £8.00

Genuine RBM Units

Prompt Postal Service.

Add 15% V.A.T. to all Prices.

DISCOUNT For QUANTITIES

WOODSDALE COMPONENTS

MR SKEHAN

34 Field End Road, Eastcote,
Pinner, Middlesex HA5 2QT.
01-868 5580

Agents Office, callers by appointment only.

Thorn 3000/3500

Thorn 9000

UNIVERSAL

1 year guarantee

TRIPLERS

£4.50 inc. p.p.

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pyc, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

CAMPBELL ELECTRONICS LTD. COLOUR T.V. PANEL EXCHANGE/ REPAIR SERVICE

THORN, RANK, PHILIPS, GEC,
DECCA, TELPRO, GRUNDIG etc.

90 Day Guarantee on all repairs - same day postal service.

Telephone Telford (0952) 502422
for catalogue and price list.

CAMPBELL ELECTRONICS LTD.,
Unit 5, Heath Hill Estate,
Dawley, Telford, Shropshire.

TELEVISION

Trade Supplies of Good
Quality Colour & Mono
TV's. Most Makes
available, suitable for
Sale or Re-Rent.

GENERAL FACTORS

UNION STREET,
DONCASTER
(0302) 49583-68416

GOOD MOTORWAY ACCESS

TVDX/SATELLITE EQUIPMENT

VHF to UHF Converter. 12v supply required. Ideal way to start DXing £13.95. Band I/II Mosfet mains preamplifier. High gain, low noise £27.50 (Bill available). SOON TO COME complete 4GHz LNA/downconverter for satellite reception £200 (approx.).

SAE data lists:

H. COCKS

Cripps Corner, Robertsbridge, Sussex TN32 5RY.
Telephone 058083-317

TRADERCO SUSSEX

Main CLEARANCE CONTRACTOR TO RENTAL COMPANIES. Colour Televisions seen working from £19 - Untested from £9.00. Sets for spares from £4. Exchange panels from £3. Untested Mono's from £2.

TELEPHONE RAY ODELL,
'TRADERCO' BRIGHTON 38552.

Northwood Middx (9684) 27019 01-845 2036

RETACH LTD.

Rear 78 High Street, Northwood, Middx.

LOOK G11 PHILIPS (inline tube)	£75
Also:	
PHILIPS G8 550 (22 Slant Button)	£35
PHILIPS G8 520 (22 Flat Button)	£25
PHILIPS G8 522 (26 Flat Button)	£18
PHILIPS G8 526 (26 Slant Button)	£25
PHILIPS G9 585 (26 Remote)	£35
RANK T20/22 Series (Incline Tube)	£75
RANK 823 (White Stocks Last)	£10
RANK 718 (Incline Tube)	£45
THORN 9800 (Incline Tube)	£55
MONO:- PYE T184-24" Mono (Solid State)	£18
VIDEO:- PHILIPS N1700, N1702, videos	£39

TUBES:-	
20" Rebuilt Colour Tube, 2yr Guar.	£29
22" Rebuilt Colour Tube, 2yr Guar.	£33
26" Rebuilt Colour Tube, 2yr Guar.	£35

All Prices +VAT - Callers by Appointment

GRUNDIG NORDMENDE Spares panel exchange service. Complete sets. Circuits, 0785 814643 anytime.

JABCO LOPT TESTER

This instrument is now used in hundreds of Service Workshops and Manufacturers with household names all round the world. Saving countless hours in checking Line O.P stages and the unnecessary fitting of new LOPTS.

Mains operated. Straight forward indication of good or bad by Red & Green Leds. No controls to set up.

Instruction booklet on testing many common Lopts in situ including jellypots.

£16.50 inclusive. C.W.O. delivery 3 days. £18 overseas post by sea. £21 airmail.

J. BAKER & CO.

1, Old Shoreham Rd., Southwick,
Sussex BN4 4RD.
Tel. Brighton 593315.

ARE YOU OVERSTOCKED?

Turn your surplus stocks into cash

£500,000 AVAILABLE

for any surplus electrical stocks ie. TV's,
Video's, Washers etc.

Phone in strictest confidence:

Mr R. Walker,

Brighthouse (0484) 714413

SERVICE PAGES

SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.
Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBANDED TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAINS LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

EX RENTAL C.T.V.'s & REGUN TUBES

RBM, THORN, DECCA, PYE GEC, GRUNDIG, ITT, PHILIPS G8, G9, G11, JAPANESE
From £10

Also all modules from £4 untested.

STARLITE ELECTRONICS,
80 Como St., Romford, Essex.
Telephone Romford 752537
London Code 3.

NEW SUSSEX WAREHOUSE, Trade Televisions.
Colour from £10, mono £3. Tel. Brighton 673482

SECOND HAND COLOUR TV and Tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

CENTREVISION

No. 1 in Wales

Good selection of used Colour Televisions

0222-44754

PROFESSIONAL STICK

De-Gaussing-Coils

£19.50 each inclusive & delivered
1 year guarantee

U-VIEW (TUBES)
29, Warmsworth Rd, Doncaster,
Yorks DN4 0RP.
0302 855017.

BOOKS & PUBLICATIONS

ANY PUBLISHED, full-sized service sheet by return £2 + L.s.a.e. CTV/Music centres £3. Repair data with all circuits, layouts, etc. Your named TV or Video £8.50. Free 50p mag. all orders, queries: TIS (TV), 76 Churches, Larkhall, Lanarkshire.

ARE YOU INTERESTED IN

- Colour TV Renovation
- Video Recording ■ Hi-Fi
- Digital Electronics
- Short Wave Radio ■ DX-TV
- Electronic Projects
- Computers or Programming?

If so, we have a book just for you.

Send 16p in stamps for further details to:

HS PUBLICATIONS
Dept. T(Z), 7 Epping Close, Derby DE3 4HR.

COURSES

CONQUER THE CHIP... Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C4, Reading, Berks RG1 1BR.

AERIALS

AERIALS & ACCESSORIES

QUALITY components at competitive prices. UHF 10 element from £1.10. 18 element from £2.20. FM2 from £2.40. FM4 from £4.95. Lashing Kits from £1.20. Wall Bkts. from 85p. Masts available 2' to 20'. Aluminium coax plugs from 10p. Coax cable from £9.30. Full range of Accessories and Amplification Equipment available.
Comprehensive price list on request.

S.C.S. AERIALS (Aerial Distributors)
14 Tanners Crescent,
Hertford, Herts. SG13 8DS
Tel: 0992 50478

WANTED

WANTED PHILIPS/PYE G11 Colour TVs, any quantities. Hornchurch 58513, Mr. Morris.

WANTED Decca 100/Philips G11. Any quantities, collection arranged. 0803553203 - Mr. Haywood.

WANTED

Modern unused TV components Lopts, Trays, Transistors, Fuses etc. Also VHS spares motors, Clutches, Pinch Wheels, Head Drums etc. Job lots purchased.
Cash waiting.

Confidential Service Box No: TV 177

WANTED - Copies of Radio & Television Servicing from 1978 onwards. Box No. 179.

WANTED FOR CASH. Video, TV's, spares, electronic components. Tel: 965 1230. Box No. TV 175.

MISCELLANEOUS

BULK BARGAIN T.V. SERVICE PACK

Contains at least £50 worth of T.V. service components and accessories. Loads of hard to obtain T.V. spares and components. Ideal for the service engineer. Only £12.50, carr. £2.50. Ref. Guar. HAVE YOU SEEN THE GREEN CAT? 1000s of new components, T.V., radio, and electronic items at unbelievably low prices. Probably the cheapest in the country. Send 40p for GREEN CAT and reserve FREE RECORD SPEED INDICATOR.

MYERS ELECTRONICS, Dept. TV2,
12/14 Harper Street, Leeds LS2 7EA.
Next to Union Jack Clothing Store, Leeds LS2 7EA.
Callers welcome at our NEW retail premises.
Open 9 to 5 Mon to Sat. Tel. 452045.

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 682674.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME.....

ADDRESS

.....

Send to: Classified Advertisement Dept.

TELEVISION

Classified Advertisement Dept., Room 2612,
King's Reach Tower, Stamford Street,
London SE1 9LS. Telephone 01-261 5846.

Rate
33p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

JUNE/83

TECHNICAL INFORMATION SERVICE

SERVICE SHEETS: full size by return – radio, mono, etc. £2 + large sae. CTVs & Music Centres from £3.
SERVICE MANUALS: Sole suppliers most obsolete equipment. Everything stocked to latest releases. Fantastic stocks CTVs/Videos. E.g. A823 £6.50; Autovox (early) £6.50. Tyne 5000/6000 Series £7.50.
COMPREHENSIVE TV REPAIR COURSE – Complete data almost every fault. – Huge beginners section. – Only £8.50.
TV REPAIR MANUALS – All 12 for £75. – Mono portables (new) £6.50. – Early VCR, £10.50.
CIRCUIT DIAGRAM COLLECTIONS IN HUGE BINDERS: British CTV (3) £42.50; Foreign CTV (2) £27; Early VHS/Phillips video £15; Mono TV standard + portables £29.
REPAIR SYSTEMS (REPAIR DATA, CIRCUITS, ETC): Video 1, £24.50; Foreign CTV, £40; Mono TV, £31.50.
SAVE £12 – BRITISH CTV ONLY £60 – LIMITED TIME; Complete integrated TV Repair System £160.
Quotations/free 50p magazine/price lists/etc for large sae.
£2 plus 8" x 10" S.A.E. for service sheet and manual catalogues with £4 vouchers.
PHONE 0698 883334 FOR FAST QUOTES – Open 4-6 daily, 11-1 weekends.
T.I.S., 76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

SANDHURST PUBLICATIONS
 Television Service Sheet Specialists
 Workshop Manuals, large selection of Japanese and European TV Sheets. Callers 5.30-7.00 pm. Upper Floor. Send S.A.E. for Catalogue and Enquiries:
 49C Yorktown Road,
 Sandhurst, Camberley, Surrey GU17 7AG.

30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE
 TV Monos, Radios, £2.00. Tuners £2.00. Tape Recorders, Record Players £3.00. Transistors, Stereograms & Music Centres £3.00 + SAE. Also Colour Available. Car Radios £3.00 + SAE. All Radiograms £3.00. State if Circuit will do if sheets are not in stock. All TV Sheets are full-length 24x12, not in Bits & Pieces. All other Data full-lengths.
 All sheets from £2.00 except Colour. OLD VALVE Radios £3.00 + SAE 9" x 3".
C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. 01-458 4882 **MAIL ORDER S.A.E.**

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.25 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

FOR SALE

TEKTRONIX 555 OSCILLOSCOPE, most valves glowing but no trace, tube intact. Phone Pipegate (063081) 312 after 6 p.m.

B.R.C. 2000 complete, spare-panels, Mullard – Tube £10 only. Amesbury 0980 52864.

TUBE REBUILDING PLANT for sale. Fire salvage in good restorable condition. Offers. Phone 0706 523415.

13 LABGEAR CM6022 Tele-vertas, good condition. £150 or £15 each. Boscastle 448 evenings.

LEADER CRT REJUVENATOR. Still under guarantee, cost £210.00 with extras, will sell £165.00 o.n.o. Telephone 0438 62517.

COMPLETE REGUNNING PLANT for sale. Five electric ovens. Apply: Box No. TV 178.

TELETEXT (Oracle/Ceefax) add-on adaptors for any television. Only £147.50 plus £2.45 postage. Also Viewdata (Prestel). Trade enquiries welcome. Access/Visa. Cytel (T) FREEPOST, Charlton Mead Drive, Bristol BS10 6BR. (0272) 502008 anytime.

SERVICES

TEST EQUIPMENT SERVICED. Scopes, generators, meters, etc. Telford Communications, 3 Park Road, Much Wenlock, Shropshire. Tel: 0952 727719.

N. J. ELECTRONICS
 UNITS 82/83/84 STORFORTH LANE TDG. EST. HASLAND
 CHESTERFIELD, DERBYSHIRE S41 0SN.
 TEL CHESTERFIELD 209079

PUSH BUTTON UNITS		EHT TRAYS	
DECCA 30 6 button	£7.96	DECCA 80	£5.95
GEC 2110	£9.00	DECCA 100	£6.00
GEC 2112 7 button	£13.10	SEIMENS UNIVERSAL	£6.30
GEC 2136/2137	£8.35	GEC 20AX	£6.70
ITT CVC 5	£10.50	GRUNDIG 5011	£6.10
ITT CVC 8	£14.00	KORTING	£7.22
G8 SQUARE (early)	£12.50	PHILIPS KT3	£6.00
G8 SLOPING (later)	£13.55	PHILIPS 550	£6.50
PYE 713 4 button	£9.15	PHILIPS 520	£6.50
PYE CHELSEA	£12.98	ITT CVC5	£6.00
RRI 823 4 button	£8.74	ITT CVC45	£7.00
RRI 823 6 button	£9.45		
RRI Z718 6 button	£9.90		
TELPRO 4 button	£8.75		

LOTXs		ICs	
THORN 1590/91	£9.70	TDA2522	£2.30
THORN 1615	£9.20	TDA2523	£2.40
THORN 1690/91	£8.45	TDA2540	£2.00
RRI T20/22	£11.95	TDA2571	£2.20
RRI 774	£11.50	TDA2581	£1.70
PHILIPS G8	£8.50	TDA2600	£4.25
PHILIPS G9	£9.00	TDA2611	£1.75
PHILIPS 210	£9.50	TDA2680	£1.85
PHILIPS G11	£12.75	TDA2690	£1.80
PHILIPS K30	£14.00	TDA2593	£2.75
ITT CVC30/32	£8.50	TDA1170	£1.80
ITT CVC45	£8.50	TDA1190	£2.00
		MC11358P	£1.40
		MC1327	£1.50
		TBA920	£1.90

ADD 65 PENCE POSTAGE + 15% VAT TO ALL ORDERS.
 (See CONTRAST U.K. advertisement in this copy, all your component, panel and TV needs under one roof).
 Please allow approx. 7 days for delivery.

N.G.T. COLOUR TUBES
 First Independent Rebuilder with
B.S.I. CERTIFICATION
 (Certificate No. 004)

All Colour Tubes are debanded, high temperature pumped and rebanded using new adhesives and new tension band.
 19" £30, 20" £32, 22" £33, and 26" £38.
 No exchange tube required on delta types.
 Delivery U.K. mainland: £7.50.

N.G.T. ELECTRONICS LTD.,
 120, SELHURST ROAD, LONDON S.E.25
 Phone: 01-771 3535.
 20 years experience in television tube rebuilding. add VAT at 15%

NO!

If you see an advertisement in the press, in print, on posters or a cinema commercial which you find unacceptable, write to us at the address below. (TV and radio commercials are dealt with by the I.B.A.)

The Advertising Standards Authority. ✓
If an advertisement is wrong, we're here to put it right.
 ASA Ltd, Brook House, Torrington Place, London WC1E 7HN.

LONDON'S LARGEST TELEVISION WHOLESALER...
with over 4½ thousand sq. feet

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnal Green Road)

LONDON E.2. FREE CAR PARK
TEL: 01-739 2707

ALL MAKES IN STOCK AND GUARANTEED
COMPLETE

PYE 22" COLOUR FROM £7.50

PHILIPS 22" G8 (Teak cabinet) PARCEL OF TEN £12
MONO DUAL STANDARD £2
- SINGLE STANDARD £5

FREE DELIVERY TO THE LONDON AREA!
TELEPHONE 01-739 2707 - NOW!

A.B.C. ELECTRONICS

Rear of 20, HANKINSON ROAD,
WINTON, BOURNEMOUTH.
TEL: 519542

TRADE TV's BEST PRICES
Colour From £12.00 + VAT
B&W From £2.00 + VAT

DISCOUNT ON QUANTITIES

ALL MAKES - ALL SIZES - ALL COMPLETE
CALL IN OR RING FOR COMPETITIVE QUOTE
FULLY REFURBISHED SETS AVAILABLE
+ DELIVERY SERVICE

M W ELECTRICAL

BROOK PARK AVE. (OFF MARINE RD.)
PRESTATYN

"WE DO NOT BOOST TUBES"
COLOUR TV'S

COMPLETE FROM £10.00
TRADE WORKERS FROM £25.00
MINIMUM OF TEN

G8, DECCA, BUSH, THORN. ALSO MONOS ETC.

NEW & GRADED TVs ALSO AVAILABLE

OPEN SAT MORN, LATE NIGHT THURS 8pm

TEL: PRESTATYN (07456) 89849/89970

EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE - TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

THE TELECENTRE, WORCESTER ST.,
WOLVERHAMPTON (0902) 773122

1983 PRICE LIST

DISPLAY ELECTRONICS

GOLD LABEL COLOUR TUBES

2 YEAR GUARANTEE

90° up to 19".....£33
90° up to 22".....£36
90° up to 26".....£39

The above prices are for standard
38mm Delta Gun Types.

Add £5 Gun surcharge for 20AX Types.
Other in-line & P.I.L. Types, prices on
application.

GOLD LABEL MONO TUBES

2 YEAR GUARANTEE

19"/20".....£12
23"/24".....£14

GREEN LABEL COLOUR TUBES

12 MONTHS GUARANTEE

90° up to 19".....£28
90° up to 22".....£31
90° up to 26".....£34

Green Label Prices apply only to stan-
dard 38mm Delta Gun Types. They will
be of particular interest to customers
refurbishing ex-rental sets.

BUDGET CORNER

Buy any 5 mixed types take 20%
discount.

Buy any 3 mixed types take 10%
discount.

Budget prices apply only to colour
tubes. The mix can include Gold &
Green Label Types if required.

CALLERS WELCOME

Late night Thursdays until 8 p.m.
Saturdays until MIDDAY

N.B. Customers intending to collect
orders are requested to telephone in
advance:- even popular types may be
out of stock for short periods.

UNIT 1
SWAN WHARF
WATERLOO ROAD
UXBRIDGE
MIDDLESEX

Telephone: UXBRIDGE 55800

DIODES	
OA 47	10p
OA 90	8p
OA 91	10p
IN 60	5p
IN 541	5p
IN 914	5p
IN 2069a	10p
IN 2070	10p
IN 4001	3p
IN 4002	3p
IN 4004	10p
IN 4005	5p
IN 4006	5p
IN 4007	7p
IN 4148	10p
IN 4448	10p
IN 4742	10p
IN 4722	10p
IN 4751	10p
IN 5235	10p
IN 5254	10p
IN 5392	10p
IN 5928B	10p
IA 5401	10p
IAY 30	10p
IM 72Z55	10p
IR 106a	20p
IR 3051	10p
IS 164	10p
IS 921	10p
IS 3011a	10p
IS 3072a	10p
IS 5024a	50p
IS 5030	50p
ITT 921	10p
ITT 923	10p
ITT 1075	10p
ITT 2001	10p
ITT 2002	10p
ITT 4150	10p
ZE 1.5	10p
ZF 3.0	10p
ZF 3.3	10p
ZF 4.3	10p
ZF 10	10p
ZF 11	10p
ZF 12	10p
ZF 15	10p
ZF 33	10p
ZF 43	10p
ZF 47	10p
ZF 82	10p
ZPD 3.9	10p
ZPD 4.7	10p
ZPD 5.6	10p
ZPD 10	10p
ZPD 47	10p
ZPY 82	10p
ZPY 12	10p
ZPY 16	10p
ZPY 24	10p
ZPY 43	10p
ZPY 47	10p
ZPY 56	10p
ZTE 2	10p
ZTK 22	10p
ZTK 33	10p
ZTK 33a	10p
ZTX 102c	10p
ZTX 107	10p
ZTX 108c	10p
ZTX 109k	10p
ZTX 213	5p
ZTX 341	10p
ZTX 342	10p
ZTX 384	10p
ZTX 450	10p
ZTX 451	10p
ZTX 550	10p
ZW 13	12p
ZW 27	10p
ZW 43	10p
ZW 310	10p
ZY 68	10p
ZY 47	10p
ZY 72	10p
AA 112	10p
AA 113	10p
AA 119	10p
AA 143	10p
AA 144	10p
BA 102c	10p
BA 157	8p
BA 159	8p
BA 173	8p
BA 182	8p
BA 201	8p
BA 202	8p
BQ 243	8p
BA 248	8p
BA 316	8p
BAV 10	10p
BAV 21	10p
BAW 21	10p
BB 103	10p
BB 105A	10p
BB 105B	10p
BB 105G	10p
BB 121a	10p
BZX 46c22	15p
BZX 61c110	6p
BZX 61c15	6p
BZX 61c20	10p
BZX 61c30	10p
BZX 61c220	10p
BZX 70c33	8p
BZX 79c4v7	8p
BZX 79c5v6	8p
BZX 79c6v2	8p
BZX 79c6v8	8p
BZX 79c8v2	8p
BZX 79c12	8p
BZX 79c22	8p
BZX 79c30	8p
BZX 79c43	8p
BZX 79c47	8p
BZX 83c4v3	10p
BZX 83c5v6	10p
BZX 83c8v2	10p
BZX 83b12	10p
BRC 83c13	10p
BZX 83c20	10p
BZX 83c27	10p

Voltage Regulators	
5V/UA78PO5SC	60p
5V/LM79MO5CP	25p
6V/78M06v	20p
8V/79M08c	30p
12V/MC 7812	20p
12V/LM 340T12	25p
15V/78M15	15p
18V/MC78M18	20p
24V/78M24	30p
TIS 90	20p
TIS 91	30p
TIS 92	30p
U 14727	15p
U 19885	40p
U 3832	15p
U 3845	15p
MR 856	10p
MR 508	10p
MR 501	10p
MR 502	20p
MR 852	20p
MR 854	10p
BYF 1202	10p
BYF 1204	10p
BYF 3123	40p
BYF 3126	40p
BYF 3214	40p
BYX 10	6p
BYX 36/600	50p
BYX 38/300	25p
BYX 38/600	50p
BYX 55/350	10p
BYX 71/350	20p
BYX 71/600	50p
BYX 72/300	20p
BYV 95	8p
BYV 96D	10p
BYZ 106	10p
BPW 41	15p
BYW 56 2A/1000v	8p
BZY 93	50p
BZV 15/12	30p
BZV 15/18	30p
BZV 15/30	30p
BZW 70c6v2	10p
Mitsumi tape motor	75p
Sankyo tape motor	75p
Swiss made 250rpm/240V motor very small	75p
Infra red led	
LD57CA	15p
Mono scan coil	£3
G 8 transductor	£1
Thorn 4000 tube base	£4
A1 pots Thorn 3500	50p
2K5 Lin pot with 40mm spindle	20p

BRIDGES	
KBL 005	30p
KBL 02	30p
KBP 04	30p
W02	15p
W004	15p
W005	20p
GEC remote panel. Main transformer 3/1c SAA 1025/SN 74141/TBA 231	£6
AT 2076/55 GEC split diode transformer	£10
AT 2048/11 LOPTI Mullard	£2.50
75R/25 Watt	25p
18R/11 Watt	25p
TV Sound Tuner Kit, ideal for TV sound on your Hi-Fi	£9.50
Front End Music Center. VHF/ MW/LW 13"×3½"	£5
Output Stage for music center	£5
Both items	£9
circuit supplied (as previous ad)	
SONY 1400KV Chroma Panel	£6
SONY 1400KV Tuner unit	£3.50
SONY 1400KV Touch button unit	£3.50
4 books/Electronic Systems/First steps into TV/Guide to Printed Circuits + 1 other	
Special Offer	£1.75

Panel VDP 12/80 D2N 720 Issue 3. Complete with All I.C.'s. Usually £100.	
ONLY £10.	
VIEWDATE	
DECODER	
PANEL TEXAS	

PHILIPS DIY HOME SECURITY ALARMS KITS
Send for details. Prices £54 to £112.

MARDAVE MODEL RACING CARS
Nickel Cadmium Battery driven
Please send for details

Various Tools and Accessories

Sellotape PVC Black	
25mm × 20M	50p
50mm × 20M	70p
Telescopic aerials (radio)	£1
Xcelite pliers	£3.90
Xcelite snips	£5
Xcelite cutters	£3.90
GKN Supascrew kits; 180 items in box with British made screwdriver.	Was £4.99. ONLY £2.50
VU meter	45p
Pull up large aerial	75p
Portable TV aerial	75p
Neon screwdriver	50p
Phillips snips	£2
2 way baby alarm/intercom with long leads	£5
Phillips universal battery tester/charger, fuse/bulb tester	£5
Volt/ohm test meters 1000 ohm/volt	£5
Eisenmann NICAD CHARGER 5.5V/150 ma	£2
¾" × ½" microphone/speaker	50p
Continental 2 pin plug with 5ft mains lead (black & blue) 5 for £1	
7" Ferrite rod with LW/MW coils	50p
Xcekute 5" bent nose plier	£3.50
De-solder pump + 2 nozzles	£5.20
Plastic box for i.c.s with anti-static pad 6"×3"×½"	50p

Quantity Reductions		Mixed Packs	
BY204/4	25 for £1.00	100 Fuses	£2.00
BY206	25 for £1.00	100 W/W Res.	£1.50
BY210/600	25 for £1.00	20 Slider Knobs	70p
BY298 3 amp/fast/R	20 for £1.50	6 Mixed UHF Aerial Isolating Sockets, some with long leads	£1.00
BD239	20 for £2.00		
MR856	20 for £1.50		
BU126	10 for £6.00		
BU208	10 for £5.00		
BU204	20 for £8.00		
BU205	10 for £8.00		
BU105	10 for £8.00		
2SC2122A	10 for £8.00		
BF458	10 for £1.00		
BD136	10 for £1.25		
BF224	20 for £1.40		
OA90	40 for £1.00		
IN4148	40 for £1.00		
IN4448	40 for £1.00		
BYX10	100 for £4.00		
50 High voltage ceramic condensers	£1.50		
Mixed Mounting Kit for Power Transistors	50p		
300 Condensers	£1.50		
300 Resistors	£1.50		
150 Electrolytics	£2.00		
15 Bulbs	40p		
100 Diodes	£1.50		

Mech high speed i.c.s databook (Motorola)	£1.40
Full line condensed catalogue (Fairchild)	£1.40
Opto-electronic data book (Fairchild)	£1.40
10 various data & practical book	£2.00

SENDZ COMPONENTS
63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE
All items subject to availability.
No Accounts : No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then 50p P+P
Add Postage for overseas
Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992

SENDZ COMPONENTS

63 Bishopsteignton,
Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE

All items subject to availability.
No Accounts : No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then 50p P+P
Add Postage for overseas

Callers: To shop at 212 London Rd.,
Southend. Tel. 0702-332992



£5.50

Mains in 110-120-220-240V A.C. 50Hz Adaptor. For black and white camera. Power consumption: 12V A. Output voltage: 14V D.C. Dimensions 150mm (w) x 80mm (h) x 120mm (d).

Accessories: Mains lead and video/audio remote cable (2 metres)

12/300	10p
4.7M/350v	10p
16/350	25p
50/350	10p
220/350	30p
700/350	50p
22/375	15p
330/385 CVC 820HT	60p
0.1/400	15p
56K/400v	20p
8/400	15p
33/400	20p
220/400	50p
400/400	40p
2x10,000PF/400 in box	40p
33/450	15p
220/450	40p
0.1/600	15p
.047/600	15p
0.1/800	15p
0.047/1000	10p
0.01/1000	10p
0.1/1000	10p
0.0047/1500	10p
.0105/1500	10p
1n8/1500	15p
2n2/1500	15p
9n1/1500	15p
G11.11000/1500	15p
G11.8200/2KV	15p
0.1/2KV	20p
10n/2KV	15p
3n9/2KV	15p
210/8KV	10p
0.0015/2KV	10p
5n2/2KV	10p
7500pf/2KV	10p
4n7/2KV	15p
8n2/2KV	15p
0.0082/2500	15p
150/3500	10p
1000/4KV	5p
4.7nf/5KV	10p
170/8KV	10p
180/8KV	10p
210/8KV	10p
270/8KV	10p
1000/10KV	10p
1000/12KV	10p
210/12KV	10p
1200/12KV	10p

Transducer Hand Set insert, crystal, transducer, 11C SAA 1124 & lead	£3.50
THORN 4000 ultra sonic hand set insert with 7 buttons (no case)	£5
4.000 Thorn thick film.	
00S1 012 E004	£1.00
00S1 012 E002	£1.00
00S1 012 010B	£1.00
00S1 018D	£1.00
Rank/Toshiba preh unit 0354	£9.50
4 Push button unit preh	£1.00
6 Push button VHF/UHF for v/cap. GEC-Decca type	£7.00
7 Push button for CVC5 ITT	£8.00
6 Push button Unit Thorn	£1.00
6 Push button unit for GEC 2040 and ELC 1043/05	£6.00
7 Lamps for P.B./Unit	10p

Mains Droppers	
Pye 731 3+56+27R	50p
3500 Thorn 6/1/100	60p
Thorn 50/17/1K5	£1.00
120/20/20/48/117	£1.00
270/10/6 for Thorn 4000	50p
18/320/70/39	£1.10
Thorn 50-40R-1K5	50p
Aerial Socket and Lead	35p
Pyc, Thorn, ITT, Thyristor, Philips G11 122	60p
Rank Toshiba Tube Bases	30p

Speakers	
6x4G11	25 ohm £1.00
54x21	3 ohm £1.20
5x3	80 ohm 70p
5x3	50 ohm 50p
5x3	35 ohm 70p
5x3	15 ohm 80p
6x4	15 ohm £1.00
7x3	70 ohm £1.00
5x3	8 ohm 70p
7x3	16 ohm £1.00
8x5	8 ohm £1.00
2 1/2" dia	8 ohm 75p
3" dia	8 ohm 75p

Diodes	
BY 127	10p
BY 133	10p
BY 134	10p
BY 164	30p
BY 176 type	25p
BY 179	40p
BY 184	40p
BY 187	10p
BY 190	40p
BY 196	30p
BY 198	10p
BY 204/4	8p
BY 206	8p
BY 210/400	5p
BY 210/600	8p
BY 210/800	10p
BY 223	50p
BY 226	15p
BY 227	15p
BY 228	20p
BY 229/400	30p
BY 237	10p
BY 254	10p
BY 255	10p
BY 298	10p
BY 299	10p
BY 527	20p
F 247	10p
XX 3123	50p
Thorn A1	10p

Line Transformers	
G8 Trans. Philips	£7.50
G11 Split Diode	£12.00
CVC820 Split Diode ITT	£10.00
CVC40 Split Diode ITT	£10.00
GEC 2040	£5.00
Pye mono	£3.00
Rank mono T704A	£3.50

International Rectifier EHT Diodes G770/HV34 6KV	3 for 8p
6A/600V Stud Diodes	20p
6A/1000V Stud Diodes	20p
SKE 1/02	20p
20 x W005 Bridge	£2.00

Rec & Trans	
G11 Ultrasonic t/text transmitter G26C 674/02 G22 C66/02	£19
Infra Red (full remote transmitter) Dynatron TV CTV 62, 63, 64	£19
40K Transducer	50p
PHILIPS NE511N	£1.20
LM337M Reg.	30p
Thorn T605 1V NPN TO66 80V 6A	10p
20 GEC Black Spark Caps	£1.00
G11 Line Driver Transformer	35p
2 SD350A BU208A	£1.00
G11 IF Detector	£3.00
G11 Teletext Transmitter	£19.00
BG200/43 Tripler	£3.00
DECCA IF 80-100	£3.50
G11 Time Base Panel	£12.00
AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670	£3.00
Thorn 900 Sound OP Panel NEW	£1.00
U321 T/Unit on Panel Cum 40 ITT	£6.00
Z714 RANK IF Panels 6MHz 1 I.C. SL437F	£3.00
Z909B RANK IF Panels Export 5.5MHz 2 I.C.'s TBA1205B TCA2705Q	£2.50
Z743 RANK IF Panel Export 5.5MHz 3 I.C.'s TBA750+SC9504P+SC9503P	£1.50
Tuner Unit VHF Sylvania GTR Videon MTS900 BIP VHF	£2.50
G11 dynamic correction panel	£6
CVC 20 Front panel with sliders + mains input panel	£4
THORN 3500 Tuner panel (ELC 1043/05 + pots)	£7
CVC 40 PUSH BUTTON ASSY with sliders: complete with lamp assy + pots	£14
CVC 5 Mains on/off + 5 pots	£2
GEC Convergence panel (We have 900) TO CLEAR	£1

Condensers	
1500/16	20p
3300/16	20p
10000/16	25p
15000/16	50p
3300/18	20p
470/25	5p
680/25	5p
1000/25 Radial	10p
1250/25	10p
1500/25	10p
2200/25	10p
3300/25	20p
4700/25	25p
5000/25	25p
1500/30	30p
3300/30	30p
1500/35	10p
2200/35	25p
50/40	5p
220/40	5p
400/40	25p
680/40	5p
1250/40	20p
1500/40	20p
200/40	25p
2000/40	25p
2200/40	25p
2500/40	25p
3300/40	25p
6800/40	35p
750/50	10p
1000/50	10p
1250/50	25p
2000/50	25p
3000/50	25p
15/63	5p
47/63 Bipolar	15p
2200/63	50p
250/64	10p
4.7M/100	5p
140/100	25p
470/100	20p
800/160	50p

Multi-Caps	
Thorn 3500	
175/100/100/350v	£2.00
KT3/200/25/25/385v	£1.00
47/220/350v	60p
150/150/100/100/100/320v	£2.00
2500/2500/63v	50p
470/470/250v	50p
150/200/200/300v	70p
100/200/325v	40p
400/200/200/350v	£1.50
200/200/100/300v	60p
200/350v + 300/100/32/300v	£2.00
200/200/100/32/350v	£1.50
200/47/350v	60p
100/300/200/100/16/350v	£2.00
200/100/100/375v	£2.00
100/100/35v	60p
1000/1000/35v	60p
150/150/100/100/325v	£2.00
100/350 + 300/200/100/16/275v	£2.00

ITT Panels	
CMA 10	£2.00
CMA 11	£2.00
CMA 30	£2.00
CMA 40	£1.50
CMA 10/2	£5.00
CMC 15	£10.00
CMC 16	£4.00
CMC 19	£12.00
CMC 45	£1.50
CMC 47	£1.00
CMC 54	£10.00
CMC 56	£5.00
CMC 58	£8.00
CMC 59	£8.00
CMC 67	£3.75
CMC 67/2	£4.00
CMC 68	£4.00
CMD 12	£10
CMD 40	£5.00
CMF 25	£2.00
CMF 40	£2.00
CMH 10	£1.50
CMH 31	£1.50
CMK 12 (untested)	£4.00
CMN 20	£1.50
CMN 40	£1.00
CMP 10	£2.00
CMP 11	£2.00
CMP 40	£2.00
CMS 11	£2.00
CMS 40	£2.00
CMU 14	£8.00
CMU 30	£7.00
CMU 40	£7.00
CMU 45	£5.00
VMC 34	£5.00
VMC 44 + 45	£4.00

Infra Red and Ultrasonic G11 Teletext Decoder Panel	£30
RANK & ITT Mains Remote On-Off Switch (720R)	£1.50
RANK & ITT Mains Remote Switch 2865 ohm	£1.50
G11 Mains Switch	40p
ITT Mains Switch 4 amp	30p
GEC Mains Switch 4 amp	30p
Petrick Mains Switch 4 amp	30p
G8 Mains Switch	75p
Mains Dropper PYE 3R5+15R+45R	50p
Thyristor 600/4 amp C106/2	24p
G11 Preh Red LED P/Button for C.H. Change	20p
2SC2073 on Heat Sink 150 NPN 1.5 Amps	7p
RANK TOSHIBA Transducers IPC-2011 Remote Unit THORN 11 I.C. Mains Transformers Relay & 5 volt Reg & Component Unit	£2.25
Thorn I.C. board with 11 various sn 74 I.C.'s	£1
CVC 5 Mains on/off +250K+100K+500K+500K Pot on Panel	£2.00

Tuner Units	
ELC1043/05 Mullard	£6.00
ELC1043 (Ex Panel)	£3.75
ELC1042	£5.00
ELC2000	£7.00
EL2060	£7.00
ELC2060 on panel	
NEW	£5.00
U321 (UHF) Mullard	£6.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
ELC1043/05 Thorn	£5.00
Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00
VHF Rotary Mitsumi	£1.00
Portable & rotary Tuners	
Sanyo & Mitsumi UHF	£5.00
Mossfit UHF VHF NSF.	
ET021 DX	£8.00
Sylvania UHF VHF F6013 (Fits Rank)	£4.50
Sylvania UHF	£3.00
Sylvania VHF	£3.00
Decca Bradford Tuner 5	
Button	£4.00
NSF AEG UHF/VHF	£6.00
Small Tuner DX 175-220MHz Auto	
Changeover	£5.00
9000 Thorn Tuner on Panel	£7.00
D.P.D.T. switch Black knob:	
Chassis or PCB mount	4p
each or 40 for	£1.00
THORN 1400 4P.B. Mechanical Tuner	
THORN 1500 4P.B. Mechanical Tuner	
THORN 3500 4P.B. Mechanical Tuner	
THORN 8000 4P.B. Mechanical Tuner	
THORN 8500 4P.B. Mechanical Tuner	
All new & boxed	£4 each + £1 postage each
I.C. Holders	
DIL - DIL	
42 Pin x 5	£1.00
28 Pin x 5	£1.00
16 Pin x 10	£1.00
24 Pin x 5	£1.00
14 Pin x 10	70p
DIL - QIL	
16 Pin x 5	£1.00
Tyne T/V I.C. SN76545N	£3.50
VHF 3 Transistor Rotary Tuner Units D.X. TV. NEW	£1.00
CVC 9 power supply board	£1.50
CVC 20/2 mains panel	£2.00
NEW	
CVC 20/3 chassis	£30.00
FED4/1220/4 3 pin ITT 1. MFD 4 Amp Mains	
Filters	50p
ITT Mains Filter .1/250v/	
CVC 20 to 45 chassis	50p
Pots 10 k with Switch	25p
Pots 47 k with Switch	25p
Mullard Surface Wave Filter RW 153P Colour TV Filter	40p
Mullard Surface Wave Filter RW 154 Colour TV Filter	40p
Thyristors	
BT119	£1.00
BT120	£1.00
BRC4443	75p
G11 Thyristor	60p
Decca 80-100	60p
G11 Teletext Decoder Panel Philips	£30.00

SENDZ COMPONENTS

63 Bishopsteignton, Shoeburyness, ESSEX SS3 8AF
SAME DAY SERVICE
All items subject to availability.
No Accounts : No Credit Cards
Postal Order/Cheque with order
Add 15% VAT, then 50p P+P
Add Postage for overseas
Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992

Diodes	
1 Amp 1600v	7p
3 Amp 100v	7p
3 Amp 1200v	10p
9000 Thorn O/P Transistors with Heatsink T903 8v	£1.00
7 Seg Display, Led Red	50p
TA7607	£1.00
TA7609	£1.00
TA7315	£1.00
Delay Lines	
TAU80	£1.00
DL11	50p
DL20A	80p
DL50	£1.00
DL70	£1.00
DL600	£1.00
DL700	£1.00
Luminance Delay Line MDL-CBL Min.	50p
3.15 Fuses	4p
Co-Ax Joint	12p
Co-Ax Belling Lee Plug	12p
UHF Modulator CCIR	£3.00
Infra Red Emitting Diode NE286H Small Neon Lamps	20p
GEC	5p
Mullard 5 Watt Amps. LPI162 New	75p
T.V. Tubes	
A31/510	£5
12" A31/300 Hitachi	£12
15" A38/170W Hitachi	£8
Add £2 P&P each	
Integrated Circuits	
AM25LS23PC	£1.00
BAV40	40p
BRC-M-200	50p
BRC-M-300	60p
BRC 1330	75p
CA270CE	50p
CA270CW	50p
CA927	40p
CA3065	50p
CA3089Q	50p
CA3094AE	50p
CA3146	£1.00
CA920AE	£1.00
TAA621	40p
TAA641	40p
TBA120A	40p
TBA120AS	40p
TBA120SA	40p
TBA120B	40p

CA1310	£50
DM7492	50p
HEF4011AF	80p
HEF4016	50p
HEF4053BP	50p
M1025	£2.50
M102485	£1.00
MC476p	£1.00
MC1307	75p
MC1327	75p
MC1330	75p
MC1349	50p
MC1352	£1.00
MC1358	£1.00
MC14001	£1.00
MC14013	£1.00
MC14016	£1.00
MC14066BCP	£1.00
MC14069	£1.00
MC1748	80p
MCM2114	£1.00
NE511NE	£1.00
MEM4956PT	£1.00
MS5611	£1.00
N64100	£1.00
NE555	60p
IL-1	30p
OPT600	30p
OPT601	30p
PD2114	£1.00
SAA611	£1.00
SAA1020	£4.00
SAA1021	£4.00
SAA1024	£2.50
SAA1025	£2.50
SAA1130	£2.50
SAA1272	£3.00
SAA5000	£1.50
SAA5000A	£1.50
SAA5010	£3.50
SAA5012	£2.50
SAA5020	£3.50
SAA5030	£3.50
SAA5040	£2.50
SAA5050	£3.50
SAS560	£1.00
SAS570	£1.00
SA5660	£1.00
SAS670	£1.00
SL918-	£2.50
SL917 MOD	£2.50
TAA320A	50p
TAA470	£1.50
TAA550	30p
TAA570	75p
TAA611	£2.00

TBA120SB	40p
TBA120U	40p
TBA120C	40p
TBA1441-	£1.00
TBA440	£1.00
TBA231	75p
TBA395	50p
TBA396	75p
TBA440	£1.00
TBA440C	£1.00
TBA480Q	£1.00
TBA510	£1.00
TBA520	£1.00
TBA530	£1.00
TBA540	£1.00
TBA540Q	£1.00
TBA550Q	£1.00
TBA560CQ	£1.00
TBA560C	£1.00
TBA570	£1.00
TBA641BX1	£2.00
TBA673	£1.00
TBA720A	£1.00
TBA750Q	£1.00
TBA800	40p
TBA810S	70p
TBA820	70p
TBA890	£1.00
TBA920	£1.00
TBA920Q	£1.00
TBA950	£1.00
TBA990Q	£1.00
TMS1943NL	£2.00
SN29848	50p
SN7472N	20p
SN75108AN	£1.00
SN76001	£1.00
SN76003	£1.00
SN76018	£1.00
SN76008	£1.00
SN76023N	£1.50
SN76033	£1.50
SN76115	50p
SN76131	50p
SN76226	£1.00
SN76227	60p
SN76228N	£1.00
SN76530P	60p
SN76532N	50p
SN76533	£1.00
SN76544N	£2.00
SN76546	£1.00
SN76552	£1.00
SN76650	50p
SN76660	40p
SN76620AN	50p
SN76666	50p
SN76707N	75p
SN76708N	75p
ML231	£2.50
ML232R	£1.20
BJT6016	£1.20
ML236E	£1.50
ML237B	£1.50
ML238B	£3.50
BTT822	£1.00
BTT6018-	£1.50
ML237B	£1.50
BTT8124	£1.00
BTT8224	£1.00
TDA2522	£1.00
UA783P3C	40p
UPC1365C	£1.50
KT3 2SD 200 Line Transistor	£2.00
Semiconductors	
BT100A	30p
BT106	£1.00
BT106 Plastic	50p
BC115	10p
BC116	10p
BC125	10p
BC139	10p
BC141	25p
BC142	25p
BC143	25p
BC147	10p
BC148	10p
BC149	10p
BC153	10p
BC154	10p
BC157a	10p
BC158	10p
BC159	10p
BC308	7p
BC309	7p
BC327	10p
BC328	10p
BC337	10p
BC338	10p
BQ347	10p
BC349B	10p
BC187	10p
BC204	10p
BC207	10p
BC212	10p
BC213	10p
BC214	10p
BC237	10p
BC238	8p
BC239	8p
BC250	8p
BC251	10p
BC252	10p
BC256	10p
BC298	10p
BC300	10p
BC301	10p
BC303	10p
BC307	7p
BC308	7p
BC309	7p
BC327	10p
BC328	10p
BC337	10p
BC338	10p
BC355	10p
BC358	10p
BC359	10p
BC365	10p
BC384	10p
BC394	10p
BC413	10p
BC414	10p
BC416	10p
BC440	30p
BC447	10p
BC454	10p
BC455	10p
BC456	10p
BC460	25p
BC462	10p
BC463	10p
BC478	10p
BC527	10p
BC546	10p
BC547	10p
BC548	10p
BC556	10p
BC557	10p
BC558	10p
BC559	10p
BC635	10p
BD116	25p
BD124	50p
BT119	£1.00
BT120	£1.00
BT109	£1.00
BT138/10A	70p
TCA270	£1.00
TCA270Q	£1.00
TCA940	£1.00
TCA4500A	£1.00
TCA640	£1.00
TCA650	£1.00
TCA660	£1.00
TCA270S	£1.00
TCA270SQ	£1.00
TCA740	£1.00
TCA800	£1.00
TCA830	£1.00
TCEP100	£2.25
TDA440Q	£1.00
TDA1003A	£1.00
TDA1010	£1.00
TDA1170	£1.00
TDA1190	£1.00
TDA1327A	£1.00
TDA1412	30p
TDA2010	£1.00
TDA2140	£3.50
TDA2530	£1.00
TDA2532	£1.00
TDA2540	80p
TDA2541	£1.00
TDA2575A	£1.00
TDA2590	£1.00
TDA2593	£1.00
TDA2560	50p
TDA2600	£4.25
TDA2653	£1.00
TDA2002	£1.00
TDA2640	80p
TDA2680	£1.00
TDA2690	£1.00
TDA2593	£1.00
TDA3190	£1.00
TDA3500	£2.00
TDA3560	£3.50
TDA3571Q	£1.50
TDA3950	£1.50
SN74LS125AN	30p
SN16862AN	£1.00
SN16964AN	50p
SN29764	£1.00
SN297728N	50p
RGP308	10p
MPSA43	10p
E1222	20p
MJE51T	25p
MJE340	28p
MJE2801	30p
MJE2955	50p
Sanikron Diode	30p
SKE262/04	30p
SN6550/3R	£1.00
AF367	25p
AL102	£1.75
AU113	£1.20
BD437/438 on heat sink	60p
BD507	50p
BD509	30p
BD510	30p
BD517	30p
BD519	30p
BD532	30p
BD534	30p
BD535	30p
BD544D	30p
BD562	30p
BD595	35p
BD596	35p
BD646	50p
BD681	25p
BD807	20p
BD948	30p
BF115	20p
BF127	20p
BF137	20p
BF157	20p
BF160	20p
BF161	20p
BF167	20p
BF173	10p
BF178	20p
BF179	30p
BF180	20p
BF181	20p
BF182	20p
BF184	20p
BF194	20p
BF195	10p
BF196	10p
BF198	10p
BF199	10p
BF200	20p
BF222	10p
BF224	15p
BF238	20p
BF240	20p
BF245b	20p
BF256	10p
BF257	10p
BF258	25p
BF259	25p
BF262	15p
BF263p	25p
BF264	15p
BF271	10p
BF273	10p
BF274	10p
BF301	10p
BF324	25p
BF336	30p
BF338	25p
BF355	30p
BF362	30p
BF363	15p
BF367	15p
BF391	15p
BF394	10p
BF419	30p
BF423	15p
BF448	30p
BF450	20p
BF457	10p
BF458	10p
BF459	30p
BF468	30p
BF469	30p
BF470	30p
BF480	50p
BF594	10p
BF597	10p
BF694	10p
BF757	30p
BF758	30p
BF761	30p
BF758	30p
BF771	30p
BF779	15p
BF789	15p
BF792	7p
BF793	15p
BF795	15p
BF797	15p
BF798	15p
BF799	15p
BF807	10p
BF808	10p
BF809	10p
BF810	10p
BF811	10p
BF812	10p
BF813	10p
BF814	10p
BF815	10p
BF816	10p
BF817	10p
BF818	10p
BF819	10p
BF820	10p
BF821	10p
BF822	10p
BF823	10p
BF824	10p
BF825	10p
BF826	10p
BF827	10p
BF828	10p
BF829	10p
BF830	10p
BF831	10p
BF8	