

CHARLESTON X


**JULY 1983**

Australia \$1.80; New Zealand \$2.10; Malaysia \$5.50; I.R. £1.15 (inc. VAT)

**90p**

# TELEVISION

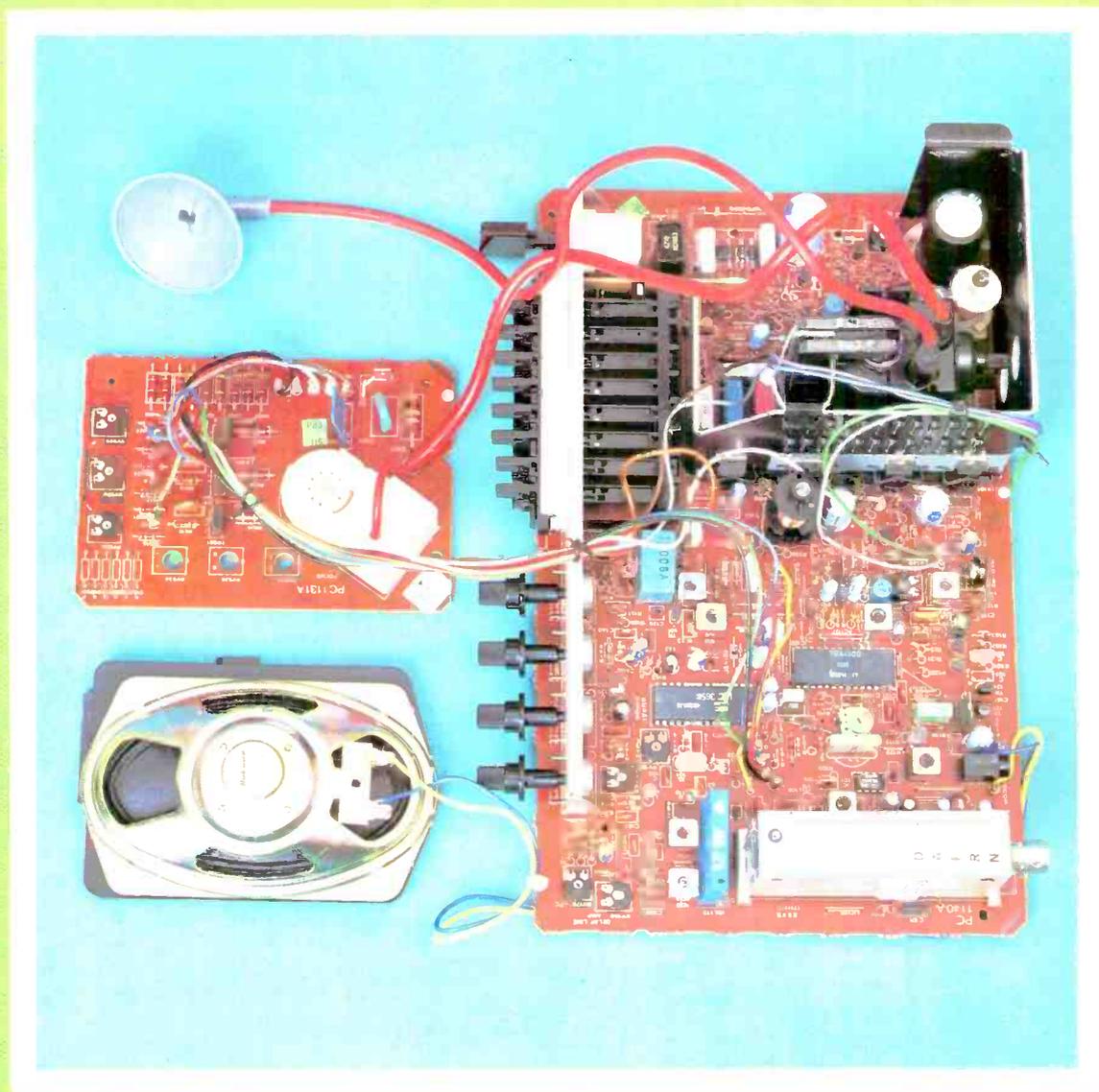**SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS**



**THORN'S NEW TX90 CHASSIS**  
**AERIAL SYSTEMS & FAULTS**  
**VCR CLINIC • TV FAULT REPORT**  
**TELETEXT DECODER**  
**PROJECT UPDATE**  
**AD CONVERSION FOR VCRs**

# Interested in Television Servicing?

## Try a ZED Pack. Effect Repairs at Minimum Cost.

<b>Z1</b>	300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt and miniature resistors	<b>£1.95</b>	<b>Z20</b>	10 Assorted switches including: Pushbutton, Slide, Multipole, Miniature etc. Fantastic Value	<b>£1.20</b>	<b>Z44</b>	TO3 Mounting kits (BU208)	<b>8 for 60p</b>
<b>Z2</b>	150 mixed 1 and 2 watt resistors	<b>£1.95</b>	<b>Z21</b>	100 Assorted Silver Mica caps	<b>£2.20</b>	<b>Z45</b>	TO220 Mounting kits (TIP33)	<b>10 for 60p</b>
<b>Z3</b>	300 mixed capacitors, most types amazing value	<b>£3.95</b>	<b>Z22</b>	10 Mixed TV convergence Pots	<b>£1.00</b>	<b>Z46</b>	TO126 Mounting kits (BD131)	<b>12 for 60p</b>
<b>Z4</b>	100 mixed electrolytics	<b>£2.20</b>	<b>Z23</b>	20 Assorted TV Knobs including: Push Button, Aluminium and Control types	<b>£1.20</b>	<b>Z47</b>	Pack of each Mounting kit. All include insulators and washers	<b>£1.50</b>
<b>Z5</b>	100 mixed Polystyrene Capacitors	<b>£2.20</b>	<b>Z24</b>	10 Assorted Valve bases B9A, EHT, etc.	<b>£1.00</b>	<b>Z48</b>	3a 1000v Diodes (IN5408 type)	<b>8 for £1.00</b>
<b>Z6</b>	300 mixed Printed Circuit Components	<b>£1.95</b>	<b>Z25</b>	10 Spark Gaps	<b>£1.00</b>	<b>Z49</b>	Brushed Aluminium Push Button Knobs, 15mm long x 11mm Diam. Fit standard 3 $\frac{1}{2}$ mm square shafts	<b>10 for £1.00</b>
<b>Z7</b>	300 mixed Printed Circuit resistors	<b>£1.45</b>	<b>Z26</b>	20 Assorted Sync Diode Blocks	<b>£1.00</b>	<b>Z50</b>	Chrome finish 10mm x 10mm Diam as above	<b>10 for £1.00</b>
<b>Z8</b>	100 mixed High Wattage Resistors, wirewounds etc.	<b>£2.95</b>	<b>Z27</b>	12 Assorted IC Sockets	<b>£1.00</b>	<b>Z51</b>	Aluminium Finish, Standard Fitting Slider Knobs. (Decca)	<b>10 for £1.00</b>
<b>Z9</b>	100 mixed Miniature Ceramic and Plate caps	<b>£1.50</b>	<b>Z28</b>	20 General Purpose Germanium Diodes	<b>£1.00</b>	<b>Z52</b>	Decca "Bradford" Control Knobs Black and Chrome. $\frac{1}{4}$ " Shaft	<b>8 for £1.00</b>
<b>Z10</b>	25 Assorted Potentiometers	<b>£1.50</b>	<b>Z29</b>	20 Assorted Miniature Tantalum Capacitors. Superb Buy at	<b>£1.20</b>	<b>Z53</b>	Tuner P/B Knobs, Black and Chrome. Fit most small Diam Shafts. ITT, THORN, GEC etc.	<b>8 for £1.00</b>
<b>Z11</b>	25 Assorted Presets, Skeleton etc.	<b>£1.00</b>	<b>Z30</b>	40 Miniature Terry clips, ideal for small Tools etc.	<b>£1.00</b>	<b>Z54</b>	Spun Aluminium Control Knobs (ITT) $\frac{1}{4}$ " Shaft, suitable for most sets with recessed spindles	<b>8 for £1.00</b>
<b>Z12</b>	20 Assorted VDR's and Thermistors	<b>£1.20</b>	<b>Z31</b>	5 CTV Tube Bases	<b>£1.00</b>	<b>Z55</b>	14 Pin DIL L.C. Sockets	<b>12 for £1.00</b>
<b>Z13</b>	1 lb Mixed Hardware, Nuts, Bolts, Selftappers, "P" clips etc.	<b>£1.20</b>	<b>Z32</b>	10 EY87/DY87 EHT bases	<b>£1.00</b>	<b>Z56</b>	16 Pin Quil L.C. Sockets	<b>12 for £1.00</b>
<b>Z14</b>	100 mixed New and marked transistors, all full spec. includes: PBC108, BC148, BF154, BF274, BC121L, BC238, BC184L and/or Lots of similar types	<b>ONLY £4.95</b>	<b>Z33</b>	20x PP3 Battery Connectors	<b>£1.00</b>	<b>Z57</b>	16 Pin DIL TOQUIL L.C. Sockets	<b>10 for £1.00</b>
<b>(Z14A)</b>	200 Transistors as above but including power types like BD131, 2N3055, AC128, BFY50 etc.	<b>£9.95</b>	<b>Z34</b>	6x Miniature "Press to Make" Switches, Red Knob	<b>£1.00</b>	<b>Z58</b>	22 Pin DIL L.C. Sockets	<b>10 for £1.00</b>
<b>Z15</b>	100 Mixed Diodes including: Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec.	<b>£4.95</b>	<b>Z35</b>	12 Sub Min S.P.C.O. Slide Switches	<b>£1.00</b>	<b>Z59</b>	B9A Valve Bases P.C. Type	<b>20 for £1.00</b>
<b>Z16</b>	20 IN4148 Gen Purpose Diodes	<b>£1.00</b>	<b>Z36</b>	12 Min D.P.C.O. Slide Switches	<b>£1.00</b>	<b>Z60</b>	0.47W $\frac{1}{2}$ Watt Emitter Resistors	<b>40 for £1.00</b>
<b>Z17</b>	20 IN4003/10D2	<b>£1.00</b>	<b>Z37</b>	8 Standard 2 Pole 3 Pos Switches	<b>£1.00</b>			
<b>Z18</b>	20 Assorted Zeners. 1 watt and 400mw	<b>£1.50</b>	<b>Z38</b>	4x HP11 Batt Holders (2x2 Flat type)	<b>4 for £1.00</b>			
			<b>Z39</b>	3.5mm Jack Sockets, switched, enclosed Type	<b>8 for £1.00</b>			
			<b>Z40</b>	100 Miniature Reed Switches	<b>£2.30</b>			
			<b>Z41</b>	100 Subminiature Reed Switches	<b>£4.20</b>			
			<b>Z42</b>	20 Miniature Reed Switches	<b>£1.00</b>			
			<b>Z43</b>	12 Subminiature Reed Switches	<b>£1.00</b>			

High quality COAX PLUGS, silver plated pin, grub screw fixing. **5 for £1**  
**COAX COUPLERS 5 for £1**  
**COAX FLYING SOCKET 3 for £1**

### ELECTROLYTIC

1 $\mu$ f 63v	20 for £1.00
1 $\mu$ f 350v	10 for £1.00
2.2 $\mu$ f 63v	20 for £1.00
4 $\mu$ f 350v*	10 for £1.00
22 $\mu$ f 16v	20 for £1.00
100 $\mu$ f 25v	20 for £1.20
160 $\mu$ f 25v*	20 for £1.50
330 $\mu$ f 25v	10 for £1.00
400 $\mu$ f 40v*	8 for £1.00
470 $\mu$ f 25v	10 for £1.00
470 $\mu$ f 35v	8 for £1.00
1000 $\mu$ f 35v	6 for £1.00
1000 $\mu$ f 40v*	5 for £1

\*Axial. All others are Radial.

### CAN TYPES

22 $\mu$ f 375v (3 pin)	50p
50 $\mu$ f 250v (3 pin)	50p
100+200 350v	£1.00
2000 $\mu$ f 100v	£1.00
1000 $\mu$ f 100v	60p
2,200 $\mu$ f 40v	60p
2,200 $\mu$ f 63v	70p
3,500 $\mu$ f 35v	50p
220 $\mu$ f 400v ITT/RBM	£1.00
6,700 $\mu$ f 70v	£1.00
10,000 $\mu$ f 40v	£1.00

### THEY'RE BACK

We can now again offer our special TV BARGAIN PARCELS. These contain all manner of useful bits and pieces. Components, semiconductors, videogame boards etc. which we have accumulated over the past year and must clear as we need the space.

5kg £9.95 10kg £14.95

### "RIFA"

0-1 $\mu$  1000v Flameproof 5 for £1.00

### EHTDIODES

Very small. 20kV 2.5ma. 30ma peak  
 50p ea. 3 for £1.00

### R.B.M. USERS LOOK!

No more messy soldering. 24 pin I.C. sockets for SL901 etc.  
**SPECIAL OFFER: 5 for £1.00**  
**100 for £12.50.**

### SPECIAL OFFERS

100 Assorted Polyester Capacitors. Mullard C296's and others  
 160v-400v only **£2.00**  
 100 Assorted Mullard C280's Cosmetic imperfections etc. **£2.00**  
 200 Mullard Miniature Electrolytics Cosmetic imperfections etc. **£2.00**  
**PACK OF EACH £5.00**

12V BULBS on leads. Suitable for most VIDEO RECORDERS.  
**70p each 4 for £2**

BY127 Type diodes. Unmarked, untested, Approximately 90% o.k. **100 for £2.95**  
 AC128 untested **100 for £3.95**

### ZENERDIODES

0v7, 2v7, 4v3, 4v7, 5v6, 6v2, 6v8, 7v5, 27v, 30v. ALL 400mw.  
 10 of one value **80p**  
 10 of each **£6.60**  
 1.3 watt, 12v, 13v, 18v  
 10 of one value **£1.00**  
 10 of each **£2.50**

### DIODES

25 x IN4002 **£1.00**  
**100 for £2.50**  
 20 x IN4003 **£1.00**  
**100 for £3.00**  
 20 x IN4005 **£1.50**  
**100 for £5.00**  
 20 x IN4148 **£1.00**  
**100 for £2.50**  
 10 x SKE4F2/06 (600v 2a fast switching) **£1.00**  
 12 x BY127 **£1.00**  
 8 x BY255 (3A 1000V) **£1.00**  
 10 x BA158 (600v 400ma) **£1.00**  
 IN5402 3a 200v **8 for £1.00**  
 6A, 100V. Bridge Rectifier. Very small. **80p ea. 3 for £2.00**

### I.C.'s

CA270AF **£1.00** **6 for £5.00**  
 MC1327P **£1.00** **6 for £5.00**  
 TBA120SB **50p each, 5 for £2.00**  
 TBA820 **£1 each, 6 for £5.00**  
 TBA810P **£1.00** **6 for £5.00**  
 555 Timer **30p** **4 for £1.00**  
 TAA 661B **£1.00** **6 for £5.00**  
 SN76660N **50p** **5 for £2.00**

### THORN SPARES

"3500" Transductor **£1.20, 3 for £3.00**  
 "3500" Focus Assembly with VDR **£1.50**  
 "8500" Focus Assembly, Rotary type **£1.50, 3 for £4.00**  
 "8500" .0022 2000v Line Capacitor **10 for £1.00**  
 "1590/91" Portable metal boost Diode (W11) **5 for £1.00**  
 "1500" Bias Caps 160 $\mu$ f25v **20 for £1.50**  
 "1500" Jellypot. L.O.P.T. Pinkspot **£3.50**  
 "900/950" 3 stick triplers **£1.00, 3 for £2.50**  
 "950" Can. 100 + 300 + 100 + 16 $\mu$ f **£1.00**

### THYRISTOR CONVERGENCE POTS

512, 1012, 2012, 3012, 5012, 10012, 20012, 1K. 8 of one type **£1.00**. 8 of each type **£6.00**.

### REGULATORS

7812 12v 1a **3 for £1.00**  
 7805 5v 1a **3 for £1.00**

### V.C.R. BATTERY PACKS.

HITACHI PORTABLE V.C.R. Nicad pack. Type VTBP60E **£20 each**. Brand New and Boxed **3 for £50**

THORN "VIDEOSTAR" 3V25/26 Nicad pack. Type VA214. Also suitable for J.V.C. etc. Brand new and boxed. **£20 each, 3 for £50**.

THORN "VIDEOSTAR" Nicad packs. Same as above but secondhand, untested. Contain 10 "C" size Nicads (HP11) which can be replaced if necessary. **£10 each, 3 for £25**.

### MISCELLANEOUS


BG100 tripler for CVC45 etc. **only £3.50**  
 Line output transformer for RBM823A **£4.25 each, 3 for £10.00**  
 ITT VC200 4P/B Transistor Tuner. Suitable for some Pye and Philips sets. 3 hole fixing **£2.75 each**  
 Decca Bradford Tuner. 5 button type **£4.00 each, 4 for £12.00**  
 UHF Modulator UHF out Video in. Ch. 36. 2 $\frac{1}{2}$ "x2 $\frac{1}{2}$ " complete with 9 foot coaxial lead and plug. With connection data **£3.00 each, 2 for £5.00**  
 GEC Hybrid 2040 series Focus Assembly with lead and VDR rod **£2.00 each, 3 for £5.00**  
 Convergence Panel for above. Brand new leads and plug. **£3.00 each**  
 GEC 2010 Transistor Rotary Tuner with AE, SKT, and leads **£1.95 each, 3 for £5.00**  
 Buch CTV 25 Quadrupler type Q25B equivalent to ITT TU25 30K **£3.00 each, 2 for £5.00**  
 Focus VDR Rods 2 $\frac{1}{2}$ "x $\frac{1}{2}$ ". Suitable for GEC, Decca etc. **75p each, 3 for £2.00**  
 Grundig UHF/VHF Varicap Tuner for 1500GB, 3010GB. **£12.50 each, 3 for £30.00**  
 EHT Lead with Anode cap (CTV) suitable for split Diodes sets 1m long **60p each, 3 for £1.50**  
 EHT Cable **30p per metre, 10 metres £2.50**  
 Anti Corona Caps **3 for £1.00**  
 4,433 Mhz CTV Crystals **£1.00 each, 3 for £2.50**  
 Cassette Mains Leads. 7ft with fig 8 plug **60p each, 3 for £1.50**  
 6 Mhz sound filters, ceramic 3 pin "TAIYO" type **50p each, 3 for £1.00**  
 10.7 Mhz Ceramic Filters "Vernitron" FM4 **50p each, 3 for £1.00**  
 PYE CT200 Control Knobs **8 for £1.00**  
 Cassette/Calc Leads. 2m long, figure 8 skt. to flat pin. American plug **60p each, 3 for £1.50**  
 3.5mm Jack Plug on 2m of screened lead **5 for £1.00**  
 Degaus VDRs. 1 $\frac{1}{2}$ " diam, for RBM etc. **5 for £1.00**  
 Mains Neons **10 for £1.00**  
 2k2 Screenfeed Resistors. White ceramic. 9 watt, with fusible link. **8 for £1.00**  
 Philips G8 Transductor. **£1.20 each, 3 for £3.00**  
 E.H.T. Discharge probe, with heavily insulated handle. with lead and chassis connector. **60p each, 3 for £1.50**

## GEMINI ELECTRONIC COMPONENTS

Dept. TV, The Warehouse, Speedwell Street, London S.E.8.

Please quote ZED code where shown. Send cheque\* or Postal Order. Add 60p P&P and 15% VAT. \*Schools etc. SEND OFFICIAL ORDER. Allow up to 28 days for delivery. Most orders despatched same day. ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8.

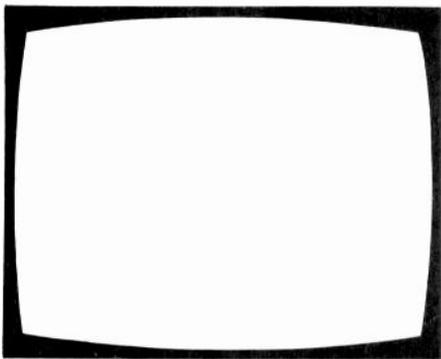Send large S.A.E. for list of Quantity, Prices and Clearance Lines etc.



# TELEVISION

July  
1983

Vol. 33, No. 9  
Issue 393

## COPYRIGHT

©IPC Magazines Limited, 1983, Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

## CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

## SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex.

## BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street; London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

## BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at 85p inclusive of postage and packing.

## QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice in dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

## this month


- 457 Leader**
- 459 Teletopics**  
News, comment and developments.
- 460 Service Briefs – ITT**  
Servicing notes on recent ITT chassis.
- 463 Letters**
- 464 Aerial Systems and Faults** *by Peter Richards*  
A review of basic types of aerial installation and fault conditions.
- 466 Laura's Dead Decca** *by Les Lawry-Johns*  
The darling of the telephone department has Les running around. Amongst other matters, faults experienced with the Fidelity CTV14.
- 467 Next Month in Television**
- 468 Light on Servicing** *by Eugene Trundle*  
The Ledu magnifier turns out to be the ideal solution for bench lighting. A couple of other optical aids have also been found useful.
- 469 The New Thorn TX90 Chassis**  
This new chassis for 14in. colour portables has been designed to compete in price, performance and reliability with anything produced in the Far East. How Thorn managed to achieve this price breakthrough and a description of the circuitry used, including the novel switch-mode boost supply.
- 472 VCR Clinic**  
Reports from Steve Beeching, T.Eng. (C.E.I.), Mike Sarre, Michael J. Cousins, T.Eng. (C.E.I.) and Mick Dutton.
- 474 Long-distance Television** *by Roger Bunney*  
Reports on DX reception and conditions and news from abroad. Also a note on how the performance of coaxial cable can deteriorate.
- 477 Less Common TV Faults** *by S. Simon*  
Following on from the Routine TV Receiver Tests series, some less common faults worth knowing about. Plus a note on interpreting voltages.
- 478 AD Conversion for VCR Control** *by Richard Roscoe*  
Some of the latest VCRs use AD conversion in the user control circuitry. How a typical system works.
- 480 TV Fault Finding**  
Fault finding notes from Richard Roscoe, John Coombes and George R. Wilding.
- 482 Exhibition Report: Cable 83** *by Dave Lauder, B.Sc.*
- 482 VCR Servicing, Part 19** *by Mike Phelan*  
This time the 3V23's capstan servo, which incorporates edit control, and the reel servo used in the fast search mode.
- 487 Teletext Decoder Update** *by Steve A. Money*  
Modifications to the *Television* teletext decoder to deal with the increased number of teletext data lines and Oracle interleaving.
- 488 Test Case 247**
- 489 Service Bureau**

OUR NEXT ISSUE DATED AUGUST WILL  
BE PUBLISHED ON JULY 20

# MANOR SUPPLIES

NEW MKV CHEQUERBOARD & PAL COLOUR TEST GENERATOR FOR TV & VCR.

TEST DEMONSTRATIONS AT 172 WEST END LANE

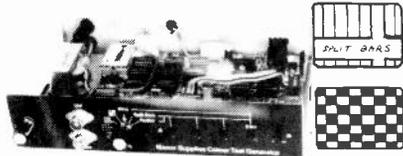

- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots. UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£80.50**

Standard Case (10½"×6½"×2½") **£5.50**

De Luxe Case (10"×6"×2½") **£8.50**

Optional Sound Module (6MHz or 5.5MHz) **£4.50**

Built & Tested in De Luxe Case including Sound Module **£120.75**


SPECIAL TEST REPORT TELEVISION DEC. 1982

Post/Packing £2.50

All above prices include VAT 15%

## PAL COLOUR BAR GENERATOR (Mk4)

4TH SUCCESSFUL YEAR

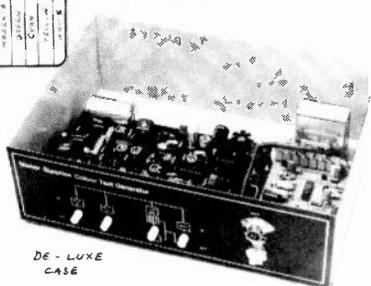

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£34.50**. DELUXE CASE **£8.50**. BATT HOLDERS **£3.20** OR MAINS SUPPLY KIT **£4.80** (Combined P&P **£1.80**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£66.70** + **£1.80** P & P.  
MK 4 DE LUXE (MAINS) BUILT & TESTED **£80.50** + **£1.80** P & P.  
VHF MODULATOR (CHI to 4) FOR OVERSEAS **£6.60**.

EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.

(ALL PRICES INCLUDE 15% VAT)

### MANOR SUPPLIES TELETEXT ADAPTOR KITS

MK 1 (Texas XMII) Cable remote control **£170.20** p.p. **£2.80**.  
MK 2 (Philips/Mullard) Infra-red remote control **£227.70** p.p. **£2.80**.

Further details on request.

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

## TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

### TELEVISION MAGAZINE PROJECT PARTS

NEW COLOUR PORTABLE TV  
MONO PORTABLE TV & SMALL SCREEN MONITOR  
LISTS AVAILABLE & PANEL TEST SERVICE

THORN TX9, TX10 SAW FILTER IF PANELS **£5.75** p.p. 85p.  
SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND tested for T.V. SOUND & VISION **£32.80** p.p. **£1.20** (SUITABLE FOR USE WITH TELEVISION SIGNAL BOARDS).

TV SOUND IF PANELS, FULLY TESTED **£7.82** p.p. **£1.00**.  
SPECIAL OFFER TEXAS XMII TELETEXT DECODER NEW & TESTED, AT REDUCED PRICE **£57.50** p.p. **£1.60**.

PHILIPS-PYE G11 TYPE TELETEXT DECODERS **£34.50** p.p. **£1.60**.  
TELETEXT 23 BUTTON DE-LUXE HANDSET WITH 5 YDS. CABLE **£7.80** p.p. **£1.20**. XMII STAB. POWER SUPPLY **£4.40** p.p. **£1.20**.

CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET **£12.65** p.p. 60p. (ALUM CASE **£2.60** DE LUXE CASE **£5.50** p.p. **£1.20**.)

ADDITIONAL GREY SCALE KIT **£3.35** p.p. 45p.  
UHF SIGNAL STRENGTH METER KIT **£21.60** (VHF version also available). ALUM CASE **£2.60** DE LUXE CASE **£8.50** p.p. **£1.80**.

CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO **£29.40** p.p. **£2.00**.

BUSH A823 POWER **£1.00** BASIC PCB. IN FIBREGLASS **£6.40** p.p.  
BUSH Z718 BC6100 SERIES IF PANEL **£5.75** p.p. 90p.

GEC A816 IF PANEL (SURPLUS) **£1.90** p.p. 90p.  
DECCA "Bradford" T.B. POWER ex rental **£5.75** each p.p. **£1.40**.  
DECCA 80, SERIES, IF FRAME T.B. **£5.75** each p.p. **£1.40**.

DECCA 80, 100 LINE T.B. salvaged **£11.50** each p.p. **£2.00**.  
GEC 2100 Decoder, RGB panels (ex rental) **£5.75** each p.p. **£1.00**.

GEC 2040 Convergence panels **£2.88** p.p. **£1.80**.  
GEC 2040 DECODER PANEL **£2.88** p.p. **£1.60**.

THORN TX9 PANELS ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.75** p.p. **£2.00**.  
THORN TX9 PANELS salvaged ex factory for spares incl. LOPT & mains transformers **£11.50** p.p. **£2.80**.

THORN TX9 PANELS ex factory salvaged complete cond **£23.00** p.p. **£2.80**.  
THORN TX10 T.B. PANELS salvaged ex factory **£17.25** p.p. **£3.00**.

THORN 3000 LINE T.B., POWER PCB **£5.75** each p.p. **£1.30**.  
THORN 8000/8500 IF/DECODER PANELS salvaged **£3.70** p.p. **£1.80**.

THORN 8000/8500 FRAME T.B. PANELS salvaged/spares **£2.88** p.p. **£1.40**.  
THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET **£19.32** p.p. **£1.84**.

THORN 9000 IF/DECODER PANELS Salvaged **£5.75** p.p. **£1.60**.  
PHILIPS 210, 300 Series Frame T.B. Panels **£1.15** p.p. 80p.

PHILIPS G8/G9 IF/DECODER Panels for small spares **£1.75** p.p. **£1.40**.  
G8 IF PANELS for small spares **£1.15** p.p. 95p.

G8 Decoder panels salvaged **£4.25**. Panels for spares **£2.00** p.p. **£1.40**.  
G9 Scan Panel. Basic PCB in fibreglass **£16.68** p.p. **£1.80**.

VARICAP, U321, U322, ELC 1043/06 ELC 1043/05 **£7.82** p.p. 80p; G.I. type (equiv. 1043/05) **£4.00** p.p. 60p. MAKERS VARICAP CONTROLS Pye CT200 4PSN **£8.60**, A823 4PSN **£5.50**, Decca 6PSN **£6.70** p.p. 80p.

ITT CVC5 7 position **£7.82** p.p. **£1.00**.  
SPECIAL OFFER ELEVEN POSITION VARICAP CONTROL UNIT UHF/VHF **£2.10** p.p. **£1.00**.

BUSH "Touch Tune" Varicap Control Z179, Z718 types **£4.40** p.p. 95p.  
VARICAP UHF-VHF ELC 2000S **£9.80**. BUSH TYPE **£7.82** p.p. 85p.  
VARICAP VHF MULLARD ELC 1042 **£7.95** p.p. 80p.

UHF/625 Tuners, many different types in stock. DECCA Bradford 5 position **£2.88** p.p. **£1.80** etc.  
LOPT TESTER Service Dept approved **£17.82** p.p. **£1.20**.

LOPTS NEW & GUAR. P/P Mono **£1.35p**, Colour **£1.45p**, Bobbins 80p.  
BUSH 161 to 186 (twin panel) ..... **£6.80**  
BUSH, MURPHY 774 series ..... **£9.80**  
BUSH, MURPHY A816 series ..... **£9.80**

FERG., HMY, MARCONI, ULTRA  
950, 1400, 1500, 1580, 1590, 1591 ..... **£6.80**  
THORN 1600, 1615, 1690, 1691 ..... **£10.50**  
GEC 2000 to 2038 series ..... **£7.80**  
GEC series 1 & 2 ..... **£9.20**

INDESIT 20/24EGB ..... **£8.80**  
ITT/KB VC 200, 300 ..... **£8.80**  
MURPHY 1910 to 2414 series ..... **£6.80**  
PHILIPS 19TG 170, 210, 300 ..... **£8.80**

PYE, INVICTA, EKCO, FERR.  
368, 169, 569, 769 series ..... **£8.80**  
SPECIAL OFFER  
DECCA 20/24, 1700, 2000, 2401 ..... **£4.40**  
GEC 2114/Junior Fineline ..... **£3.25**  
PYE 40, 67 ..... **£2.00**  
KB VC ELEVEN (003) ..... **£2.00**  
KB VC1 ..... **£3.25**

PHILIPS 88, G9 ..... **£10.15**  
PHILIPS 570 ..... **£7.85**  
THORN 3000/3500 SCAN, EHT ..... **£7.85**  
THORN 8000/8500/8800 ..... **£14.80**  
THORN 9000 to 9600 ..... **£10.15**  
THORN 9800 ..... **£21.90**

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.T.S.  
TRIPLERS Full range available. Mono & Colour.  
Special Offer: Thorn 1400 5 stick EHT Tray **£1.72** p.p. 65p.

TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.72** p.p. 60p.  
6.3V CRT Boost Transformers **£5.80**, Auto Type **£3.20**, p.p. **£1.20**.  
THORN 3000 Mains TX **£5.75** p.p. **£2.00**. 6.3V CRT Boost TX **£5.80** p.p. **£1.40**.

CALLERS WELCOME AT SHOP PREMISES Telephone 01-794 8751/7346  
THOUSANDS OF ADDITIONAL ITEMS. ENQUIRIES INVITED  
LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS

## MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.


NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door  
W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)  
W. Hampstead (Brit. Rail) access from all over Greater London.

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.

ALL PRICES INCLUDE VAT AT 15%  
CLOSED FOR HOLIDAYS JUNE 6th to 18th
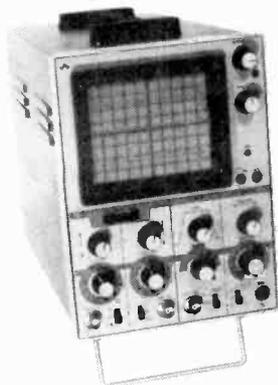
# B.K. ELECTRONICS

INCREASE YOUR PROFITS - IMPROVE YOUR SERVICE  
WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT



## SAFGAN DT-520 DUAL TRACE SCOPE 20MHz-5" C.R.T.


- SPECIFICATION**
- ★ CH1, CH2: 5mV/div-20V/div
  - ★ Time Base: 1 sec/div-100ns/div
  - ★ XY Facility: Matched XY inputs
  - ★ Trigger: Level control, ± slope selection
  - ★ Auto. normal, TV Triggering
  - ★ Z-Modulation
  - ★ CAL output 1V 1KHz
  - ★ Sweep output
  - ★ Graticule blue ruled 10x8 cm (5" C.R.T.) Very sharp trace.
  - ★ Size: H235mm, W177mm, D360mm.
  - ★ Weight: 6.5Kgs.
  - ★ Supply: 200-240V, 40-60Hz.
- Price: **£210.00 + £31.50 V.A.T.**  
Optional Probes as Thandar below.

**BRITISH - NEW MODEL - 12 MONTH GUARANTEE**
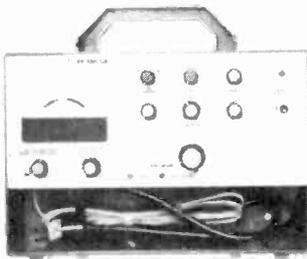
## LEADER LCT-910A C.R.T. TESTER-REJUVENATOR

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.


- ★ Tests for shorts and leakage between electrodes.
  - ★ Tests cathode emission characteristics.
  - ★ Separately checks condition of guns.
  - ★ Removal of shorts and leakage between electrodes.
  - ★ Checks heater warm-up characteristics.
  - ★ Rejuvenation of low emission cathodes with automatic timing.
  - ★ Super rejuvenation with manual control.
  - ★ Complete with tube base adaptors.
- Size: H 230mm W 330mm D 120mm.



PRICE **£151 + £22.65 VAT**
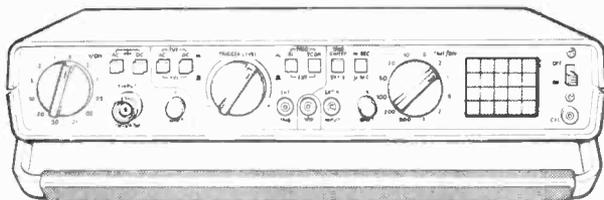
## THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.

The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and controls of a bench oscilloscope. **FITS IN A BRIEFCASE**



One of the most useful and versatile instruments available.

### Full Sized Performance

- ★ 10 MHz bandwidth.
- ★ 10 mV per division sensitivity.
- ★ Full trigger facilities are provided including TV frame, or TV filtering.
- ★ Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- ★ Size 255mm x 148mm x 50mm.

\* Scope **£149.00 + £22.35 V.A.T.**

Carry Case **£5.95 + £0.89 V.A.T.**

× 1 Probe **£7.00 + £1.05 V.A.T.**

× 10 Probe **£8.00 + £1.20 V.A.T.**

× 1/10 Switched Probe **£9.50 + £1.42 V.A.T.**

Rechargeable Batteries **£11.00 + £1.65 V.A.T.**

AC Adaptor **£6.95 + £1.04 V.A.T.**

(Overseas purchasers please state voltage.)

**BRITISH  
MADE**

**FULLY  
GUARANTEED**

## LEADER HIGH VOLTAGE METER EHT PROBE

Measures up to  
40 K.V. D.C. with  
**SAFETY  
BUILT  
IN  
METER**

PRICE  
**£21.75**  
+ **£3.26**  
VAT



**ALSO AVAILABLE**  
Analogue Multimeters  
Digital Multimeters  
Oscilloscopes  
Signal Generators  
Digital Frequency Meters  
Pattern Generators  
CRT Tester/Rejuvenator  
T.V. Field Strength Meter  
Digital Capacitance Meter  
**LARGE S.A.E.  
FOR COMPLETE LIST.**

U.K. Post Paid. Export orders welcome, please deduct V.A.T. and include an additional £5.00 for Overseas carriage. Mail Order only. Callers by appointment. Barclaycard/Access orders welcome, or Cheque, Bank Draft etc., with order please. Large S.A.E. for technical leaflets of complete range.

Delivery normally within 7 days.

**B. K. ELECTRONICS, Dept. 'T',**  
Unit 5, Comet Way,  
Southend-on-Sea, Essex, SS2 6TR.  
Tel: (0702) 527572.



# Technical Training in Television, Radio and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed".

## CITY AND GUILDS CERTIFICATES

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

**Basic Electronic Engineering (C&G/ICS)  
Radio Amateurs**

## CERTIFICATE COURSES

**TV & Audio Servicing  
TV, Radio and Audio Engineering  
Radio & Amplifier Construction  
Electronic Engineering\*  
Computer Electronics\*  
Industrial Electronics\*  
Radio Frequency Electronics\*  
Electrical Engineering\*  
Electrical Contracting & Installation**

\*Quality for IET Associate Membership



Approved by CACC



Div. National Education  
Corporation



Member of ABCC

## POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_



Dept J295  
ICS School of Electronics  
160 Stewarts Road  
London SW8 4UJ



01 622 9911  
(All Hours)

# P. V. TUBES

Just phone your order through, we do the rest.



Telephone: Accrington (0254) 36521  
Accrington (0254) 32611

SUPPLIERS OF TELEVISION COMPONENTS

38A WATER STREET, ACCRINGTON, LANCS BB5 6PX.

TRADE COUNTER OPEN MON-FRI 9 a.m.-5 p.m. SAT 9.30 a.m.-5 p.m.

INTEGRATED CIRCUITS				T.T.L. 74LS SERIES															
AN240	3.84	MSN5807	7.87	TA7202P	4.27	TBA7200	2.12	7906	98	74LS00	19	74LS37	19	74LS92	35	74LS160	60	74LS251	54
AN240	3.91	MS1513L	2.80	TA7204P	3.77	TBA727Q	2.64	7908	98	74LS02	19	74LS38	20	74LS93	35	74LS161	60	74LS253	1.00
AN7150	3.97	MS1515L	3.28	TA7205AP	3.72	TBA750	2.98	7912	98	74LS03	19	74LS40	20	74LS107	46	74LS162	60	74LS257	53
CA555	4.6	SAS580S	1.89	TA7206P	3.40	TBA800	1.62	7915	98	74LS04	20	74LS42	36	74LS108	27	74LS163	60	74LS258	67
CA741	2.5	SAS570S	1.89	TA7210P	6.60	TBA810AS	1.10	7918	98	74LS05	19	74LS44	80	74LS112	27	74LS164	65	74LS259	74
CA748	4.5	SAS580	2.90	TA7222	2.42	TBA820	1.70	7924	98	74LS06	72	74LS48	80	74LS113	27	74LS165	65	74LS273	80
CA3065	1.80	SAS590	2.90	TA7223P	3.74	TBA890	3.94	7925	72	74LS07	72	74LS49	80	74LS114	27	74LS174	57	74LS283	50
LA4031P	3.21	SL901B	5.50	TA7227P	5.98	TBA920(Q)	3.00	7912	72	74LS08	72	74LS51	19	74LS123	52	74LS175	47	74LS293	70
LA4102	3.37	SL917B	6.50	TA7228P	5.98	TBA950(X)	3.05	7915	72	74LS09	19	74LS54	19	74LS124	46	74LS191	66	74LS352	1.54
LA4250	3.05	SL1310	1.80	TA7310P	2.78	TBA970	4.09	7918	72	74LS10	19	74LS55	19	74LS128	46	74LS192	65	74LS353	1.10
LA4400	3.57	SL1327Q	1.20	TA7611AP	4.39	TBA990	1.90	7924	72	74LS11	72	74LS56	2.50	74LS132	46	74LS193	66	74LS355	3.6
LA4422	3.28	SL7654A	2.05	TAA300	58	TCA760	2.30	7925	72	74LS12	72	74LS57	2.95	74LS138	48	74LS194A	69	74LS366	3.6
LC7130	5.93	SN78003N	2.49	TAA310	2.83	TCA2750C	2.50	7925	72	74LS13	72	74LS58	3.40	74LS139	48	74LS197	80	74LS367	3.6
LC7120	5.87	SN78013N	2.49	TAA320	2.00	TCA800	3.10	7925	72	74LS14	72	74LS59	2.95	74LS141	48	74LS240	80	74LS368	3.6
LC7137	5.50	SN78023N	2.00	TAA350A	6.00	TCA940	1.95	7925	72	74LS15	72	74LS60	1.62	74LS142	48	74LS241	80	74LS373	99
LM1303N	2.63	SN76110N	1.15	TAA550	55	TDA400	1.25	7925	72	74LS16	72	74LS61	1.34	74LS143	48	74LS242	76	74LS374	99
HA1151	3.89	SN76115N	2.27	TAA570	1.99	TDA102	1.95	7925	72	74LS17	72	74LS62	2.95	74LS144	48	74LS243	76	74LS383	80
MC1307	1.99	SN76131N	2.00	TAA630	3.99	TDA103A	5.50	7925	72	74LS18	72	74LS63	4.26	74LS145	48	74LS244	80	74LS393	80
MC1310P	1.60	SN76226(ON)	2.00	TAA8400S1	1.96	TDA1004A	2.95	7925	72	74LS19	72	74LS64	7.8	74LS146	48	74LS245	1.18		
MC1327	1.73	SN76227N	1.18	TAA700B	1.70	TDA1006A	2.50	7925	72	74LS20	72	74LS65	1.34	74LS147	48				
MC1351P	2.90	SN76532N	1.50	TAA661B	1.20	TDA1005	4.70	7925	72	74LS21	72	74LS66	1.98	74LS148	48				
MC1330P	9.0	SN76533N	1.70	TBA120A	80	TDA1044	4.37	7925	72	74LS22	72	74LS67	3.95	74LS149	48				
MC1349	1.99	SN76033N	2.49	(A)(S)(AS)(SA)	TDA1170	TDA1044	3.00	7925	72	74LS23	72	74LS68	4.15	74LS150	48				
MC1350	1.30	SN76544N	2.35	TBA120B	1.30	TDA1190	3.50	7925	72	74LS24	72	74LS69	3.45	74LS151	48				
MC1352	1.75	SN76650N	1.05	TBA120S	1.37	TDA1200	2.95	7925	72	74LS25	72	74LS70	4.49	74LS152	48				
MC1358P	1.50	SN76660N	80	TBA120U	1.10	TDA1270	3.95	7925	72	74LS26	72	74LS71	4.49	74LS153	48				
MC1495L	3.00	SN76668N	80	TBA335	1.20	TDA1327	1.70	7925	72	74LS27	72	74LS72	9.06	74LS154	48				
MC1401BCP	66	SN76530A	1.47	TBA336	80	TDA1328	1.60	7925	72	74LS28	72	74LS73	9.06	74LS155	48				
MC14049UB	43	S/W153	2.74	TBA440N (TBA1441)	TDA1412	TDA1412	1.20	7925	72	74LS29	72	74LS74	9.06	74LS156	48				
ML231/ETTR0616	2.20	TA7050P	95	TAA400P	2.75	TDA2002	2.80	7925	72	74LS30	72	74LS75	9.06	74LS157	48				
		TA7051P	95	TBA440P	2.50	TDA2140	5.95	7925	72	74LS31	72	74LS76	9.06	74LS158	48				
		TA7074P	1.00	TBA480(Q)	1.50	TDA2190	4.70	7925	72	74LS32	72	74LS77	9.06	74LS159	48				
		TA7108P	3.43	TBA510	3.00	TDA2020	4.66	7925	72	74LS33	72	74LS78	9.06	74LS160	48				
		TA7120P	2.43	TBA520Q	1.68	TDA2030	2.80	7925	72	74LS34	72	74LS79	9.06	74LS161	48				
		TA7129AP	3.76	TBA530(Q)	1.38	TDA2521	4.17	7925	72	74LS35	72	74LS80	9.06	74LS162	48				
		TA7130P	1.93	TBA540	1.68	TDA2522	2.40	7925	72	74LS36	72	74LS81	9.06	74LS163	48				
		TA7141P	95	TBA550(Q)	1.58	TDA2523	3.40	7925	72	74LS37	72	74LS82	9.06	74LS164	48				
		TA7183P	5.67	TBA570	1.59	TDA2524	2.25	7925	72	74LS38	72	74LS83	9.06	74LS165	48				
		TA7171P	1.85	TBA570	1.79	TDA2540	3.84	7925	72	74LS39	72	74LS84	9.06	74LS166	48				
		TA7172P	1.85	TBA690	1.50	TDA2541	3.84	7925	72	74LS40	72	74LS85	9.06	74LS167	48				
		TA7173P	1.85	TBA691BX1	3.50	TDA2560	3.50	7925	72	74LS41	72	74LS86	9.06	74LS168	48				
		TA7176P	2.50	TBA673	2.45	TDA2571	2.56	7925	72	74LS42	72	74LS87	9.06	74LS169	48				

SEMICONDUCTORS				VOLTAGE REG.				I.C. SOCKETS				'4000 B' SERIES CMOS				NEW VALVES						
AC107	35	(A)(B)(C)	20	BD697	1.24	BF274	24	BT102/500	R2540	2.80	2SC643A	1.50	5mm	30FL2	1.70	EF183	99	PCF200	1.35	PL95	1.00	
AC126	30	BC114	12	BD695	1.39	BF310	30	BT106	1.20	RCA1633A	90	2SC1096	1.72	Red	EF802	98	EF184	1.09	PCF800	1.38	PL504	1.65
AC127	32	BC115	17	BD698	1.50	BF311	30	BT107	1.60	RC1633S	90	2SC1172/2.20	Green	EH86/7	66	EH90	1.02	PCF801	1.13	PL508	2.90	
AC128	32	BC116A	16	BD707	95	BF336	36	BT108	1.89	TP230A	43	2SC1173/1.69	Red	EL31	1.08	EL34	3.50	PCF802	1.12	PL509/19	5.30	
AC128K	40	BC117	30	BDX32	1.20	BF337	41	BT116	1.21	TP230C	43	2SC1306 2.73	Yellow	EL82	98	EL84	1.05	PCF805	1.80	PY88	81	
AC141K	39	BC118	24	BF115	38	BF338	41	BT119	3.66	TP31C	55	2SC1307 3.00	Amber	EC82	98	EL84	1.02	PCF806	1.30	PY500A	2.30	
AC142K	38	BC119	36	BF125	26	BF362	68	BT120	3.66	TP31C	55	2SC1449 1.87		EC83	1.07	EL90	8.05	PCF806	1.30	PY500A	2.30	
AC176	35	BC139	28	BF127	47	BF363	72	BT151/800	1.20	TP32B	72	2SC1520 2.67		EC84	80	EV86/7	68	PCF806	1.63	PY800/1	69	
AC176K	32	BC140	32	BF154	23	BF371	30	BU104	1.20	TP34B	1.06	2SC1678 2.88		EC85	98	EV86/7	68	PCF806	1.63	PY800/1	69	
AC186	41	BC141	26	BF158	70	BF457	35	BU104	2.20	TP41C	47	2SC1909 2.90		EC86	80	EV86/7	68	PCF806	1.63	PY800/1	69	
AC187	35	BC142	30	BF160	27	BF458	43	BU105	1.25	TP42C	50	2SC1913 1.44		EC87	80	EV86/7	68	PCF806	1.63	PY800/1	69	
AC187K	38	BC143	31	BF162	120	BF459	43	BU105	1.58	TP47	70	2SC2028 1.82		EC88	80	EV86/7	68	PCF806	1.63	PY800/1	69	
AC188	35	BC147	13	BF173	22	BF459	43	BU106	1.08	TP47	70	2SC2028 1.82		EC89	80	EV86/7	68	PCF806	1.63	PY800/1	69	
AC188K	39	BC148	9	BF177	52	BF459	43	BU106	1.08	TP47	70	2SC2028 1.82		EC90	80	EV86/7	68	PCF806	1.63	PY800/1	69	
AD143	82	BC149	12	BF178	46	BF474	28	BU124	1.94	TP52	95	2SC2078 1.34		EC91	80	EV86/7	68	PCF806	1.63	PY800/1	69	
AD149	98	BC157	16	BF179	28	BF474	28	BU126	1.75	TP52	95	2SC2166 2.73		EC92	1.84	PC92	9.00	PCF200	2.83	40KDE	5.30	
AD161	54	BC158	16	BF180	39	BF474	28	BU126	1.75	TP52	95	2SC2166 2.73		EC93	1.84	PC92	9.00	PCF200	2.83	40KDE	5.30	
AD161/2	1.15	BC160	25	BF182	36	BF474	28	BU126	1.75	TP52	95	2SC2166 2.73		EC94	1.84	PC92	9.00	PCF200	2.83	40KDE	5.30	
AD162	54	BC161	25	BF182	36	BF474	28	BU126	1.75	TP52	95	2SC2166 2.73		EC95	1.84	PC92	9.00	PCF200	2.83	40KDE	5.30	
AF106	49	BC170B	15	BF182	36	BF474	28	BU126	1.75	TP52	95	2SC2166 2.73		EC96	1.84	PC92	9.00	PCF200	2.83	40KDE	5.30	
AF114	89	BC171	15	BF182	36	BF474	28	BU126	1.75	TP52	95	2SC2166 2.73		EC97	1.84	PC92	9.00	PCF200	2.83	40KDE	5.3	

# P. V. TUBES

REPLACEMENT ELECTROLYTICS		
PYE 169 (200/200/100/32)	2.12	
PHILIPS 320 (400/400/200V)	2.07	
DECCA 30 (400/400/350V)	3.40	
DECCA 80 (400/350V)	3.66	
DECCA 100 (800/250V)	3.97	
DECCA 1700 (200/200/400/350V)	4.83	
PHILIPS G8 (800/300V)	2.30	
PHILIPS G9 (800/300V)	2.21	
PHILIPS G11 (470/250V)	2.90	
PYE 691/7 (200/300/350V)	2.70	
PYE 731 (600/300V)	2.31	
RBM A823 (2500/2500/30V)	1.66	
RBM A823 (800/300V)	2.83	
RBM Z146 (300/300/350V)	3.55	
RR1 T20A (220/400V)	2.00	
ITT CVC5/9 (200/200/75/25)	2.98	
ITT CVC 20 (220/400V)	2.00	
GEC 2110 (800/250V)	1.94	
GEC 2040 (1000/2000/35V)	1.10	
GEC 2040 (300/300/150/100/50)	4.19	
THORN 3500 (400/400V)	1.83	
THORN 950 (100/300/100/16/275V)	1.30	
THORN 1400 (150/100/100/150/320V)	2.79	
THORN 1500 (150/150/100/300V)	2.20	
THORN 1500 (12/300V)	3.11	
THORN 3500 (175/100/100/400/350V)	2.78	
THORN 3500 (1000/63V)	86	
THORN 3500 (1000/70V)	86	
THORN 8000/8500 (2500/2500/63V)	3.38	
THORN 8000/8500 (700/250V)	2.31	
THORN 8000/8500 (400/350V)	2.56	
THORN 9000 (400/400V)	3.28	
GEC (200/200/150/50)	2.64	
PHILIPS 69 2200/63V	1.25	
THORN 4700 P/C 25V	1.20	
PHILIPS 320 400/200V	2.74	
THORN 1591/1691 4700/25V	1.20	

CAPACITORS AXIAL		
Volts	Mfd	Price
6V3	33	9
10V	22	10
	47	10
	100	10
	220	15
	470	20
16V	33	11
	68	11
	220	16
	1000	27
330V	53	
25V	10	11
	22	13
	47	15
	100	15
	220	20
	470	30
	1000	55
	2200	51
4700	98	
40V	10	10
	22	10
	400	48
63V	1	12
	2.2	12
	4.7	12
	10	11
	15	12
	22	13
	47	19
	100	23
	220	37
	470	49
	1000	58
	2200	94
100V	10	13
	22	15
	47	20
	100	36
	220	70
450	1	33
	4.7	30
	10	30
	22	65
	33	75
500	1	32
	10	32
600	1	41

MIXED DIELECTRIC CAPS		
Volts	0.1C	
250V	0.91mF	84
400V	0.22mF	20
600V	0.1mF	38
1000V	0.01mF	24
	0.047mF	46
	0.033mF	33
	0.1mF	35
	0.22mF	66
	0.47mF	98
1250V	0.1mF	59
	0.91mF	1.15
1500V	0.0022mF	28
	0.0047mF	32
	0.022mF	30
	0.033mF	62
	0.005mF	65
2000V	0.0052mF	1.20

ELECTRONIC TUNERS AND ASSEMBLIES		
Mullard ELC1043/05	8.40	
Mullard ELC1043/06	8.40	
4 P/B DECCA/GEC/ITT	6.88	
6 P/B DECCA/GEC/ITT	7.50	
4 P/B PYE	9.00	
6 P/B PYE	16.00	
PHILIPS G8 Tuner	10.50	
PHILIPS G8 Ass. (Square/Early)	13.50	
PHILIPS G8 Ass. (Sloping/Late)	13.90	
PHILIPS G9 Tuner	10.50	
PHILIPS G11 Tuner	9.00	
ITT/PYE/GEC 7 Button P/B	13.95	
GEC 2110 6 way P/B	7.90	
U321 UHF Tuner	7.50	
THORN 8800 SELECTDR	9.00	
(HMV Model 2725/6 way round button)	7.50	
THORN 9000 SELECTOR	11.40	
U322	7.20	
HITACHI 4 way Chan. Selector (Also Rank A823)	10.75	
RR1 T20A 6 way Chan. Selector	9.75	
RR1 T20/22/26	11.00	
PHILIPS 8 way TIP Switch Unit (suitable for all G11)	23.00	
ITT CVC5 (5 wheel modified)	£12	
ITT 6 way with VCR	8.90	
PHILIPS KT3	14.50	
PHILIPS KT30	10.30	
PYE 697 Repair Kits	6.97	

SWITCHES		
4A Double Pole On/Off Switch	1.75	
General Purpose Push/Push	1.35	
Philips G8 Push On/Off Switch	7.50	
4A Double Pole Rotary On/Off	66	
A1 Beam Switch (THORN 3500)	70	
A1 Controls 5m (THORN 3500)	89	
GEC 2110 A1 Control IM5 (Red, Blue, Green)	58	
GEC 2040 On/Off Switch	1.58	
On/Off Switch G11/G12	1.88	
On/Off Switch GEC/TCE TX9/10	1.06	

SLIDER POTENT		
Lin or Log		
470R-1K-2K2-44-		
10K-47K-470K	65	

SKELETON PRE-SET POTS		
Standard or miniature		
Horizontal or Vertical		
100R-2M2	16p	

PANELS + UNITS		
AFC UNIT PHILIPS G8	8.82	
IF GAIN MODULE (Pye/Philips)	9.00	
CDA PANEL (Pye/Invicta/Ecko/Dynatron)	20.00	
REAR CONVERGENCE PANEL (Philips G8)	23.00	

MIDGET CONTROLS		
Insulated Spindle Length 44mm		
Log or Lin Without Switch		
5K-10K-25K-50K-100K-250K-500K-1M	39p	
With D.P.S.T. Switch		
Log: 5K-10K-25K-50K-100K	81p	
250K, 500K, 1M, 2M		
Dual gang Controls	1.25	
16mm Rotary Controls 10K, 22K, 100K, 1M, 10K 39p		

THERMAL CUT OUT		
THORN 3000 2A Metal	1.60	
THORN 8500 2.5 Plastic	1.60	
GEC 2040 Metal	2.50	

MULTITURN POTS		
100K	55	
GEC TCE	55	
PHILIPS G8		
DECCA, RANK	55	

THICK FILM RESISTOR NETWORK		
THORN 3500 (5 pin connection)	1.98	
PYE 731 (6 pin connection)	2.20	
THORN 9000 (Circuit Ref. R704/7)	1.98	

EAGLE PRODUCTS		
Please send large S.A.E. for full EAGLE Catalogue		
DF615 Full Range Speaker 6 1/2"	8.95	
Multimetres		
KEW 7N	2,000	5.25
KE-V 20		14.50
EM5	5,000 opv	9.95
EM10	10,000 opv	11.50
EM50	50,000 opv	19.95
EMC321 Carrying Case for above		2.25
Digital Meter TS1000		44.50
MM20	20,000 O.P.V.	21.95
MM50	50,000 O.P.V.	25.95
MM100	100,000 O.P.V.	36.50
MMT20		16.95
Case for MM100		15.95
T1206 2 Station Intercom		6.95

DATA BOOKS (No VAT)		
Transistor Equivalent		
TVT 80 A-Z only		3.75
TVT 80 2N/2S series only		4.00
TVT 80/80 A-Z and 2N/2S together		7.50
LIN IC Books LIN 1		5.95
LIN 2		5.95

CONVERGENCE POTS		
3 A/5R-6RB-TOR-15R-20R		
50R-100R-200R-500R	60	

METRIC CONVERGENCE POTS		
PHILIPS G8		
5R-10R-20R-50R	60	

EVER READY RECHARGEABLE BATTERIES		
CH1/22 For PP3/NN1604	6.40	
1 battery (RX22)		
CH4/50 For HP7/NN1500	5.55	
14 batteries (RX6)		
CH3/RX6 For SP2/HP2/NN1300/		
SP11/HP11/NN1400/HP7/		
NN1500	14.00	
2-4 batteries in pairs. (RX6-RX14-RX20)		
CH3/RX4 For SP2/HP2/NN1300/		
SP11/HP11/NN1400/HP7/		
NN1500	9.55	
2-4 batteries in pairs. (RX6-RX14-RX20)		

BATTERIES		
RX6 - HP7/NN1500	1.39	
RX14 - SP11/HP11/NN1400	2.17	
RX20 - SP2/HP2/NN1300	2.34	
RX22 - PP3/NN1604	4.69	

VIDEO/AUDIO		
VHS E30	3.06	
VHS E60	3.66	
Scotch E120 Video Tape	5.00	
Scotch E180 Video Tape	5.13	
BETA L500	4.90	
BETA L750	5.80	
PHILIPS VCC 240	5.93	
PHILIPS VCC 360	8.30	
PHILIPS VCC 480	10.21	

VIDEO CASSETTE CASES		
Red/Blue/Green/Brown		
Book Type - Any Format		
Scotch Audio Tape		
C90 Ferric	65	
C90 Super Ferric	96	

ELECTROLUBE PRODUCTS		
Electrolube Adhesive	62	
Electro-Mech lubricant	1.49	
Elect. cleaning solvent	1.62	
Freezer	1.49	
Foam cleanser	1.12	
Heat transfer compound	1.14	
Silicone compound	1.94	
Special contact fluid (Snorkel)	3.20	
Permagard	1.52	
Elec. mech. lubricant pen	74	

P.V. MICROCOMPUTER CENTRE		
Why not pay us a visit and see our range of Micros, Software Books and Peripherals. Please ring for prices.		

Spectrum 16K	Vic 20	Sharp
48K	Commodore 64	Oric
Jupiter Ace	Atari 800	Dragon
Texas	Lynx	

Also authorised dealers for the BBC Micro and accessories		
---	--	--

FUSES		
1 1/2" QUICK BLOW		
100ma	73	
250ma-500ma-750ma-1A	60	
1.5A-2A-2.5A-3A-5A	60	
1 1/2" ANTISURGE		
250ma, 500ma, 800ma, 630ma, 750ma, 850ma, 1A, 1.25A		
1.5A, 2A	1.70	
2.5A, 3A, 5A	2.70	
20mm ANTISURGE		
80ma	4.80	
100ma	2.50	
160ma, 200ma	2.20	
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.6A, 2A	1.30	
2.5A, 3.15A	1.90	
20mm QUICK BLOW		
100ma, 250ma, 500ma, 630ma, 800ma	90	
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	60	
1" MAINS		
2A, 3A, 5A, 10A, 13A	1.00	

AERIAL ACCESS		
Surface Mount	1.70	
Splitter	80	
Surface Mount. Outlets	80	
Cable Clips per 100	1.18	
Cox Clips per 100	1.80	
P.V.C. Tape	35	
F.M. Plugs	25	
P1259 Plugs	40	
Line Connectors	35	
Reducers for P.259	16	
T.V. Filter 50db Rejection	8.25	
27mhz	2.10	
Attenuators 6db, 12db, 18db	1.80	
Olympic II Set Top	7.90	
Aerial	2.30	
M.H.A./P.U. the pair	18.00	
Aerial Isolator Kit	2.08	
4m Fly Lead	1.20	
2m Fly Lead	90	


SUNDRY TUNER ACCESS.		
RANK Tuner P.B.		
1 1/2" x 1/2" x 1/2" x 1/2"	35	
RANK Drive Cams	10	
GEC 2110 Tuner Neons	14	

SUNDRIES		
Delay Lines DL60, DL700, DL50	2.20	
CRT Tube Base	70	
EHT Final Anode Cap	53	
EHT Cable	25p mtr.	
6.3V CRT Boost Trans.	4.35	
13A Plug Set	box 10	4.80
Quick Set Adhesive	78	
Moulded Plastic Hex. 6mm Trim	10	
Tools	10	
Double End 4mm/8mm Trim Tools	20	
Focus Rod	1.25	
Focus Holder	2.00	
Keystone Safe Block (mains)	5.50	
Cassette Drive Belts price each		
35mm	35	
46mm	37	
57mm	37	
66mm	39	
71mm	41	
76mm	43	
90mm	59	
110mm	1.18	
Torch (handy for tool box)	42	
I.C. Insertor	1.18	
SM Neon Screwdriver	40	
DIN Plugs 3 pin	22	
4 pin	22	
5 pin	20	
Stnd. 5 pin	20	
Phono Plugs		
Car Aerial Plug	14	
2.5mm Jack Plug	14	
3.5mm Jack Plug	20	
Stnd. Jack Plug	36	
Stereo Jack Plug (12)	36	
5A Connector Block (12)	5	
Fuse Jira 5A-15A-3CA	28	
Battery Plug Thom TV's	3.25	
Gen. Purpose Power Supply		
9V 200mA		
Mains Connector 4 way 13A	5.00	

RECTIFIER STICKS		
TV11	74	90
TV13	79	1.20

MAINS DROPPERS		
DECCA 20	2.48	
DECCA 2R5	85	

# NOW!

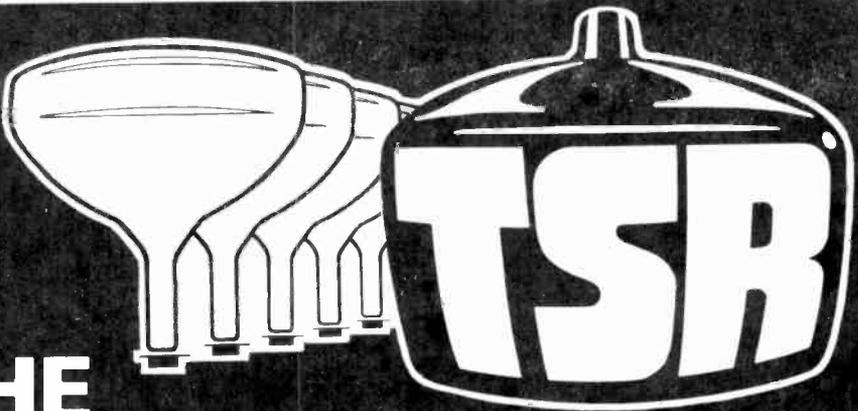

# FOR THE FIRST TIME!

## QUALITY REBUILT CRTs

# ALL SONY CRTs

All In-Line CRTs whatever make.  
All monitor CRTs.  
All gaming machine CRTs.

and PROJECTION SYSTEMS

SONY, HITACHI,  
DZB/VLB glass bought.

# ALL HITACHI CRTs

including the 560DZB22 and  
510VLB22 series

ONE YEAR GUARANTEE  
WITH A FOUR YEAR OPTION  
★  
REBANDED FOR MAXIMUM SAFETY  
★  
SPECIALIST CRTs REBUILT AT OUR  
SCOTTISH FACTORY



SCOTLAND & N. ENGLAND  
T.S.R. Vacuonics Ltd.,  
Tom Stewart Lane,  
St. Andrews, Fife,  
Scotland.  
Tel: (0334) 74035

Available **NOW!**  
only from sole distributors

MIDLANDS

**Express T.V. Supplies**  
33 Fortescue Lane,  
Rugeley, Staffs.  
Tel: (08894) 77600

THE  
**OTV**  
**TUBE SHOP**

LONDON & HOME COUNTIES

OTV House,  
144 Lea Bridge Rd.,  
London E5 9RB.  
Tel: 01-985 6111

NORTHERN ENGLAND

**George Lawson Electronics**  
108 Scotland Rd.,  
Carlisle, Cumbria,  
Tel: (0228) 20358/39693

S.W. ENGLAND

**Torbay Tubes**  
2a Barton Hill Road, Barton Industries,  
Torquay, Devon.  
Tel: (0803) 33035

Information on all other CRTs available on request

## 1000's OF COMPLETE TV'S TUBES & PANELS ALWAYS IN STOCK

Give us the opportunity to quote for all your requirements. Mixed loads delivered to your door directly from source - at unbeatable prices plus special discounts for bulk purchases.

### JUST ARRIVED!

Fresh stocks from our suppliers.



call  
**BRAINTREE**  
**(0376) 43685**  
24 hour service

AMPLE  
FREE  
PARKING

**NEW  
STOCKS  
ARRIVING**

# CELTEL

#### OPENING HOURS

BRAINTREE		LONDON	
Mon-Fri	9-6 pm	Mon-Fri	10-5 pm
Saturday	9-3 pm	Saturday	10-1 pm

Warners Mill, South St. Braintree, Essex. Tel: (0376) 43685  
10 Shackdewell Rd. London N16. Telephone: 01-249 9265

## Switch to the biggest wholesaler of quality late model used TV's

- Thousands of Quality Sets always in stock
- Colour/Mono/VCR's and Audios available
- Murphy/Pye/Philips/Sony/National Panasonic and other big names
- We are big - we buy in bulk - we offer you the keenest prices
- Cash and Carry or we will deliver
- New and used stands always in stock

VISIT OUR NEW SHOWROOM  
TODAY OR RING US ON  
**0562 743735**

**CAMPION  
THOMPSON**  
ELECTRICAL WHOLESALERS

Campion House, Franchise Street, Kidderminster, Worcestershire DY11 6RE



Incorporating



## JUST OUT!

### OUR GREAT NEW CATALOGUE

Presented with a Professional Approach and Appeal to ALL who require Quality Electronic Components, Semiconductors and other Accessories ALL at realistic prices.

There are no wasted pages of useless information so often included in catalogues published nowadays. Just solid facts i.e. price, description and individual features of what we have available. But remember, BI-PAK's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.



We hold vast Stocks "in stock" for fast immediate delivery, all items in our Catalogue are available ex stock.

The Catalogue is designed for use with our 24 hours "ansaphone" service and the Visa/Access credit cards, which we accept over the telephone.

To receive your NEW 1983 BI-PAK Catalogue, send 75p PLUS 25p p&p to:-

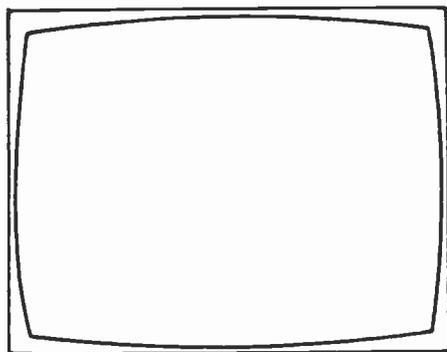
**BI-PAK**

Dept T7  
(Catalogues) PO Box 6  
WARE, Herts. SG12 9AD



Access & VISA accepted  
Ring 0920 3182 for  
immediate despatch





# TELEVISION

## EDITOR

John A. Reddihough

## ASSISTANT EDITOR

Luke Theodossiou

## ART EDITOR

Roy Palmer

## ADVERTISEMENT MANAGER

Roy Smith  
01-261 6671

## CLASSIFIED ADVERTISEMENTS

Barbara Blake  
01-261 5897

## FRONT COVER

Our thanks to Thorn EMI Ferguson who lent us the TX90 chassis and set featured in our cover and inside photographs.

## PCB SERVICE

The Readers' PCB Service continues in operation. Send orders to Readers' PCB Services Ltd. (TV), Fleet House, Welbeck St., Whitwell, Worksop, Notts. The latest boards to become available are as follows: In-circuit Transistor Tester (see page 410, June 1983) £1. Frequency Counter-Timer main board £15, others £1 each. Prices include VAT, postage and packing. Send remittance with orders. For further details see page 211, February 1983.

## The Real Lessons

The success of Japanese industry, in particular its achievements with consumer electronics products, make the methods and techniques used by the Japanese a subject of great interest. Just what makes them tick – those firms that seem to progress inexorably, and the Japanese people? Many suggestions are made, but very often one begins to have doubts when considering them more carefully.

It's said for example that there are no social barriers in Japan (I quote from an official Japanese source), managers and workers mixing freely and using the same canteen. Great emphasis is placed by Japanese management on the workshop as the hub of the firm, the place where wealth is created and the future of the firm is assured or not as the case may be.

This social barrier business calls for some interpretation however. The Japanese are by tradition both race and class conscious, perhaps more so than we are. Remember that Japan was a closed society for many centuries – until 1868. Japanese families go to great lengths to check whether possible in-laws are perhaps say Korean, or maybe part Korean. That doesn't do at all. There is also race consciousness within Japan. The Ainus of the northern island are considered to be a people apart. As for class consciousness, the Japanese know their exact position in the social structure – you simply wouldn't go to work in a car that was even in some superficial way possibly slightly superior to that of your boss. Perhaps the fact that the Japanese readily accept this state of affairs explains why social stresses don't seem to be a problem. There is also however the fact that social mobility is much greater than in many other class structured societies (also the pressure to achieve success). Possibly the very fact that the Japanese worker knows and accepts his current position is part of the success of the communal workplace and canteen. There is also undoubted mutual respect built into the system – provided you play your part, which of course you always do.

Another aspect of this business of the bosses mixing freely with the workforce is the emphasis placed by both on belonging to the firm, which is regarded as an extended family. But even here there's a class system of sorts at work. Those firms we hear so much about are the elite, who can pick and choose. It's an honour therefore to be taken on, and there's extraordinarily little changing from one firm to another – the exact opposite of silicon valley, where a sort of job musical chairs sometimes seems to be in operation. But beneath the well known names there's another layer, the smaller subcontractors who do the labour intensive bits. They can't guarantee jobs for life, neither can they provide the wages and conditions the major concerns can. Life for those at this level is less rosy. At a lower, underlying level there are the firms and organisations that provide basic services rather than branded goods. Life is tough here: the Japanese railways for example are as starved of capital as good old British Rail, and make much larger losses.

In some ways Japanese society is more akin to the Victorian ideals we've been exhorted to study of late. Paternalistic, with success breeding success, and a lot going on that's not exactly in the public eye.

All this leads one to suspect that emulating Japanese success is not going to be a simple matter. We obviously can't become Japanese any more than we can jump out of our skins. We can of course try to appreciate that wealth is created by successful manufacturing activities (amongst other things), to which all sides contribute. What else?

Frankly, the best UK firms appear to be as well run as their Japanese counterparts. Where appropriate investment is made and good labour relations exist, there is little to choose between them. After all, just as TV sets tend to look much the same nowadays whether they're made in Japan, Europe, S.E. Asia or the USA, so do many of the plants in which they are made. Much the same equipment is used, though sadly it comes from Japan or the USA rather than the UK. The fact that the best plants tend to be much of a muchness probably accounts for the fact that the Japanese can produce TVs in S. Wales or Scotland as effectively as in Japan. Maybe the managing director does use the canteen, but this seems unlikely to make much of a difference.

Is there no moral to be found in the Japanese success story then? It occurs to this observer that there are at least two points worth making. First an acknowledgement of the value of manufacturing activity and engineering generally. This never seems to have been quite accepted in the UK, where the captains of industry are apt to make out that they're really gentlemen farmers! We could do with a dose of industrial morale building (some profits would also help), though the politicians of all parties seem quite inept at this. It's strange how producing a specialist sports car or motorcycle at a rate of two a week in a country estate outhouse tends to be more highly regarded than mass producing goods that offer good value for money.

Time and again one finds the captains of Japanese industry emphasizing the prime importance of the end product. We'll only get this right when we learn the second lesson Japan can offer – investment in appropriate education. The Japanese produce large numbers of well qualified engineers whose training is orientated to the needs of industry (tut, tut!). In addition you find engineers at the head of major Japanese firms, which must be part of their success in making the right investment decisions that lead to the production of the right goods at the right time. The example is there for us to see, and there can be no excuse for ignoring it.

# Teletopics

## VIDEO DISC SYSTEMS

Quite a lot to report on the subject this month. First, the RCA CED/Selectavision system is due to be launched in the UK this autumn. The move is to be spearheaded by Hitachi, who at present are the sole manufacturers of CED disc players. The discs themselves are produced by RCA in the US. Players are also expected to be marketed by GEC-McMichael and ITT, both RCA licensees, though ITT have expressed reservations unless an adequate range of discs, say 200 titles, is available. The problem here is that all discs are at present NTSC encoded and will have to be remastered for 625-line PAL. The CED system was launched in the USA in 1981 and last year some 130,000 players were sold. Sales of discs were relatively more successful at 30 per player.

CED players are expected to retail in the UK at about £230-£250. This would be for a basic machine with wired remote control. Infra-red remote control might add something like £35 to the price. Provisionally suggested disc prices are £13 for a one-hour disc and £22 for a two-hour version. Technical details of the CED system have appeared in previous issues – CED stands for capacitance electronic disc, i.e. the signal is encoded in the disc in the form of capacitance variations, with the pickup linked to a resonant circuit.

Substantial reductions in the prices of Philips LaserVision disc players have meanwhile been announced, the aim being to take advantage of the rise in VCR prices recently as a result of the EEC-Japanese agreement on quotas. The basic VLP600 player now has a suggested price of £299 with the remote control VLP700 carrying a price tag of £349. The LaserVision disc catalogue is being expanded with the addition of a further 100 titles, and extensive promotion and advertising are planned. A more versatile player, the VLP830, is to be launched in the autumn at about £575. This machine will provide interactive features, i.e. preprogrammed stills and moving sequences from various sections of the disc, and pause operation with the long-playing (two hour) CLV discs. It will also incorporate the CX noise reduction system originally introduced on the Pioneer version of the player. A further player, Model VLP835, is to be introduced for commercial and educational use.

The JVC VHD disc system was launched in Japan last April. The latest VHD player comes from Mitsubishi – the VDP200 at 148,000 yen (approximately £400). The machine offers random access to any part of the programme on a disc plus a full range of reproduction modes including slow motion, picture search, reverse, still pictures, frame-by-frame advance and repeat. There's also Dolby noise reduction, full function infra-red remote control, and a microphone input to enable external sound to be mixed.

Matsushita's development of a record/playback optical disc has been mentioned in this column before. The system is now being introduced for computer use, offering a far higher storage density than conventional computer discs. Recordings are erasable – discs can be erased and re-recorded up to a million times, an 8mW laser being used for record/playback and a 10mW laser for erasure. During recording, the structure of the disc's recording layer is altered between crystalline and non-crystalline

states to vary the reflectivity, the process being reversible. Matsushita suggest that it will take five to eight years to develop the system as a consumer product.

## VCR LATEST

The start of VCR production at Sanyo's Lowestoft plant has been brought forward by two months to August. Equipment for the assembly of the first machine, the mid-range Betamax Model VTC5150, is at present being set up. Production during the remaining half of Sanyo's current financial year is expected to reach 60,000, rising to an annual figure of 200,000 by 1985. TV receiver production at the plant is now running at 96,000 sets a year. The start of production at Hitachi's Landsberg, Bavaria VCR plant is scheduled for this September. Plans are to start production at the rate of 180,000 machines a year with the prospect of doubling output. Meanwhile increasing criticism of the EEC-Japanese quota agreement is being made because of the inclusion of kits. This is at present hampering plans for increased assembly of VHS and Betamax machines in Europe. J2T are pressing for the removal of kit quotas next year, when the European content of their machines is expected to reach 35 per cent. J2T's production this year should be around 400,000 VCRs, and the group hopes to increase this to 700,000 in 1984.

In an analysis of the total number of VCRs in use world-wide, the May issue of *Screen Digest* estimates that 4.4 million machines are now in use in the UK, a penetration of 22.2 per cent of households with a TV receiver. This compares with 22.8 per cent in Japan, 15.6 per cent in W. Germany, 8.1 per cent in the USA and 5.6 per cent in France. *Screen Digest's* estimate of the total number of VCRs in use world-wide is thirty million.

Any suggestion of reservations about the V2000 system's future has been discounted by the introduction of new models by Philips and Grundig. Philips' "next generation" V2000 VCRs, which will be available this August, are Models VR2334 and VR2340. The former has mono sound and is designed to sell at around £540, the latter being a stereo sound version. The new machines have been substantially reduced in size and represent a complete redesign both mechanically and electrically. The cassette housing is electronically controlled and extra microcomputer i.c.s have been introduced in the control system. Grundig's Video 2x4, which supersedes the 2x4 Super, is also a more compact redesign. More versatile, easier to use timer arrangements are incorporated in all these machines.

Another system that's sprung back to life is Funai's CVC portable system. Grundig are marketing it as Model VP100, which at around £300 makes it extremely competitive – cheaper than VHS-C machines, though the cassettes cannot be used with standard VCRs. Visual Mar-Cam Systems Ltd. are the UK distributors of the "Microvideo Showcase", the Funai/Technicolour version. CVC cassettes are now available with 30, 45, 60 and 120 minute playing times.

An important development of the VHS system has been announced by Matsushita, "stereo high-definition sound". This employs a principle used in a few non-PAL Betamax machines – recording the sound along with the helical video tracks. For this purpose two extra audio heads are mounted in the video head drum. The effect is to increase the relative tape running speed for the audio signal to the same speed as for the video signal, making high-density audio recording possible with sound quality equal to that of state-of-the-art audio equipment. A model using this

technique will be launched in the UK towards the end of the year, in the Panasonic range. An NTSC version of the machine is already on sale in Japan, at the equivalent of around £800.

The latest addition to the Mitsubishi range is the HS304, a compact, easy-to-use front loader designed to sell at around £499. Mitsubishi comment that they hope to start production "soon" at their Haddington plant in Scotland.

A new VHS cassette has been designed by Eko in Ireland. Production is expected to start at the rate of 3-4 million cassettes a year. Amongst the advantages claimed are a new, overhead tape braking system and anti-pirating features.

### **TX10 CHANGES**

In the latest version of the Thorn TX10 chassis the metalwork around the panels has been replaced by a plastic frame with moulded cableform retainers. In addition to offering better value, the plastic frame helps to reduce radiation from within the set. At the same time the main panel layout has been redesigned and two new i.c.s have been introduced in the sync/line oscillator and field timebase sections.

### **MINI TVs**

The Sony Watchman Model FD210, a hand-held TV set measuring  $8 \times 3\frac{1}{2} \times 1\frac{1}{2}$ in. and weighing 1 $\frac{1}{4}$  lb, has now gone on sale in the UK, with a suggested price of around £250. The heart of the set is a flat tube (the gun is mounted at the side of instead of behind the screen) giving a 2in. picture.

Sony have thus entered the market ahead of the Sinclair flat-screen mini TV set, whose production has been delayed by some six weeks by a dispute at the Timex Milton plant in Dundee (the dispute was over the production of watches and had nothing to do with TV). Sinclair's set is designed to sell at around £60 and is appreciably smaller in size. Sinclair claim to use more advanced tube technology, giving longer battery life. There are similarities between the tubes, for example the phosphor screen is at the rear of the tube which is viewed via a transparent biasing electrode at the front. The main difference appears to lie in the deflection arrangements used.

### **SAMSUNG IN UK**

Samsung colour sets are to be marketed in the UK by Heron Electronics. The initial models will have 14 and 20in. tubes and are being produced at Samsung's Portuguese plant.

### **INTERNATIONAL INDUSTRIAL NEWS**

Zanussi and Philips have signed a letter of intent relating to co-operation in the design and production of TV and video equipment. It's understood that talks between the two companies were initiated at the request of the Italian government, and that talks have also been held with the French concern Thomson-Brandt. Though the agreement between Philips and Zanussi is at this stage tentative, working groups are to be set up within the companies to discuss the possibilities of collaboration.

COMPACT, the Committee to Preserve American Colour Television, which has both company and union members, has filed a suit with the US Commerce Department claiming that S. Korea and Taiwan are dumping colour receivers on the US market. S. Korean manufactur-

ers are alleged to be selling CTVs in the USA at a discount of 46 per cent on the price of the same sets sold in S. Korea, while the discount with Taiwanese sets is said to be as high as 60 per cent.

Grundig have decided to close down their TV receiver plant in Taiwan. The plant was originally set up in 1977 and makes tuners and clock radios in addition to both monochrome and colour TV sets. Though production costs are low, the plant has made losses in the last two years and Grundig consider that best results can be achieved by concentrating production at the main plants in Austria and W. Germany.

### **mitsubishi's new colour tube**

Mitsubishi have developed a new 21in. shadowmask colour tube with a squarer, flatter faceplate. The former feature reduces loss of corner information whilst the latter reduces reflections. Improved magnetic and thermal characteristics have made it possible to obtain the increased display area whilst a gun with a multi-stage focus assembly gives improved resolution.

### **CCTV QUALIFICATION**

Until recently there's been no formal national qualification in closed-circuit television. The Educational Television Unit of the West Bromwich College of Commerce and Technology has, in conjunction with the City and Guilds of London Institute, devised a course leading to the award of a C & G certificate entitled "The Special Certificate in Closed Circuit Television" C & G 278. The course starts in September 1983 as a two-year part-time provision for those who already have C & G 222, 224, 272 or sufficient electronics background. Details from the West Bromwich College of Commerce and Technology, Woden Road South, Wednesbury, Sandwell, W. Midlands WS10 0PE.

### **A51-570X REPLACEMENT**

A cautionary tale in the latest issue of *Ferguson Feedback* draws attention to the fact that there are several versions of the Mullard A51-570X tube. The differences relate to the deflection yoke, which is bonded to the tube. Unless the correct type is obtained for a particular TV set, problems such as reduced width and excessive height can arise.

### **TELETEXT SET WITH BUILT-IN PRINTER**

Due for release late this summer is the Philips Model 3890, a top-of-the-range 26in. set with teletext and a built-in printer. A  $4 \times 3$ in. paper copy of any teletext page takes less than thirty seconds to print. The printer uses thermo-sensitive paper to eliminate the need for chemicals, and each set comes with three rolls of paper - enough for 175 teletext pages. The printer is also useful for copying telesoftware transmissions for home computer use.

### **WAR ON PIRATES**

The Copyright Amendment Act, which increases the penalties for video piracy very considerably, received the Royal Assent on May 13th. The new Act divides offences into two categories which can be summarised as follows: (1) Trading in pirate cassettes. Those who rent or sell pirate cassettes face a maximum fine of £1,000 per offence, and a further fine and up to two months' imprisonment for subsequent offences. (2) Making pirate

cassettes. This more serious offence is now triable before a Crown Court and carries an unlimited fine and up to two years' imprisonment per offence. It applies to the making of pirate cassettes for commercial gain. The previous penalty for both offences was a maximum fine of £50. The new Act takes effect from July 1st.

In addition to the increased penalties, the Act gives the police powers to search and seize.

Two men who admitted being involved in an organisation that mass produced and sold pirated and counterfeit tapes were recently ordered by the High Court to pay more than £4 million in damages. The court action was taken under previous legislation by seeking an injunction.

### DBS

The IBA has informed the Home Office that whilst awaiting the legislative changes required it has earmarked funds for a satellite launch slot to be made available at the earliest possible opportunity for ITV use. The IBA feels that it should be made responsible for two of the five satellite TV channels allocated to the UK (the BBC has been given responsibility for providing services on the first two channels).

In the USA, the FCC has given approval to Satellite Television Corporation to start work on a DBS service in the 12-14GHz band. STC are expected to launch a satellite to serve the eastern time zone in 1986. Eight other companies have received preliminary FCC approval for DBS services. Channel allocations and satellite positions for the band are at present being discussed by the western hemisphere Regional Administrative Radio Conference.

RTE in Ireland have expressed the intention of running a satellite TV operation. The Irish Ministry of Posts and

Telegraphs is at present considering the situation. The five channels allocated to Ireland interleave with those allocated to the UK, and the polarisation and satellite positions are the same. It seems that Ireland could have services, which would of course overlap with the UK, in operation by 1987-8. Similar overlapping with satellite positions and interleaved channels applies to France and Luxembourg. The two governments have held talks on possible joint operations.

Wolsey Electronics have introduced a range of DBS dishes in sizes 0.7, 0.9 and 1.5m, with Cassegrain feed. An advantage of this type of feed is that the down-converter can be easily mounted and can be replaced without disturbing the aerial's alignment. Wolsey's down-converter uses four gallium arsenide f.e.t.s, two in the low-noise preamplifier and the other two as mixer and local oscillator, followed by a two-stage i.f. amplifier using bipolar transistors. A.C. power is fed to the converter via the coaxial cable. The converter has an overall gain of 35dB.

### IPRE

The Incorporated Practitioners in Radio and Electronics (IPRE), which was founded in 1935 and came to a temporary end in 1982, has been officially relaunched as a division of the Society of Electronic and Radio Technicians. It will provide a complete range of professional services to staff holding non-ERB qualifications - entry is based on City and Guilds 224 or the previous 222 course, though similar qualifications may be accepted later. IPRE members will receive SERT's monthly journal *Electronic Engineering* and the fortnightly newspaper *Electronics Engineer*. Further details can be obtained from SERT at 57-61 Newington Causeway, London SE1 6BL.

### SERVICE BRIEFS: ITT

The latest issue of ITT's bulletin "Service Information" contains the following advice on particular problems with various ITT chassis.

**CVC30 series chassis:** In the event of tripping at switch on, check that the voltage across the mains bridge rectifier's reservoir capacitor C35 is 320V. If low, suspect C35 or the bridge rectifier diodes D11-14.

**CVC40 chassis:** In the event of low output from the switch-mode power supply at switch on, progressively increasing to the correct 127V, suspect the chopper output smoothing capacitor C11 (22 $\mu$ F).

In the event of failure of the chopper transistor T807 (TE1233), check R833 which provides base bias for the driver transistor T806. The value should be 1.5M $\Omega$ , 5%. The recommendation is to change this resistor whenever a set is serviced.

Intermittent failure of the 1.6A (delay) mains fuse F1001 is often due to the 5.1 $\Omega$  surge limiter resistor R1, which should be replaced even if it appears to be satisfactory.

If the set trips with the scan coils plug disconnected to isolate the line output stage and a 150W lamp connected as a dummy load, check the value of R809 (220k $\Omega$ , 5%) in the trip circuit (on module CMP40). If this item is o.k., suspect the two 1N4148 diodes D8 and D10 associated with the chopper driver transformer.

**ITT 80-110° chassis:** In the event of varying width and height after about a quarter of an hour, suspect R631

(82k $\Omega$ ) - check by substitution. This resistor is in the potential divider chain that provides the sample h.t. feedback to the chopper control circuit.

**CVC801 chassis:** Low h.t. (110V rail) can occur due to zener diode D732 (type ZPD20) being defective - it stabilizes the 20V supply used in the chopper control circuit. In later production two zener diodes (D732/3) are connected in parallel - in this case replace both.

No h.t. (switch-mode power supply shut down) is sometimes caused by a fault in the horizontal shift transformer L506.

In the event of weak sound, replace the 100 $\mu$ F electrolytics C228 and C232 associated with the audio i.c. in the CMR800 r.f./i.f. module.

**CVC802/1 chassis:** This version of the CVC801 chassis features frequency-synthesis tuning (CMR803 r.f./i.f. module). Hunting and a noisy picture may be due to failure of the prescaler i.c. This is IC51, type U465B. The improved type U865B, fitted in current production, can be used as a replacement provided pin 7 is isolated either by cutting the copper on the panel as near as possible to the device, removing the copper pad, or alternatively cutting off the i.c. pin (take care to avoid damaging the i.c.).

**CVC1200 series chassis:** Modifications have been made to the base circuit of T703 in the start-up circuit. These should be carried out in the event of failure of the BU508A chopper transistor T713. Details will be given in an article on this power supply to appear in a forthcoming issue.

### TRANSISTORS

AD161	32p	BCX34	11p	NKT453	1.65
AD162	32p	B0131	30p	PN107	7p
AC131	40p	BF137	20p	R1038	80p
AC138	40p	BF197	15p	R1039	80p
AC153	32p	BF199	15p	R2008B	1.80
AC141K	39p	BF238	20p	R2010B	1.10
AF139	38p	BF240	9p	R2030	70p
AF239	41p	BF255	10p	R2265	1.30
BC107B	15p	BF256S	20p	R2443	25p
BC108A	15p	BF257	28p	RC1A16446	30p
BC109B	15p	BF259	28p	RC1A16599	1.25
BC109C	15p	BF274	11p	RC1A16600	1.40
BC117	21p	BF435	41p	ZN3703	20p
BC142	30p	BF450	43p	2SA473	10p
BC153	16p	BF459	40p	2SC346	8p
BC154	16p	BF480	58p	2SC1162	48p
BC159	15p	BF487	25p	2SC785R	12p
BC171	9p	BF742	30p	2SC3020	15p
BC172	9p	BF743	30p	2SC388A	20p
BC174B	23p	BFY51	34p	R2322	50p
BC182LB	12p	BFY52	34p	R2323	50p
BC184LC	12p	BU105	1.00	TIP31	35p
BC208	9p	BU126	1.10	TIP32	35p
BC237	12p	BU207	1.05	TIP110	80p
BC238	8p	BU208A	1.15	T90110	1.45
BC251	8p	BU326A	1.30	T9016V	1.20
BC307	10p	C1172B	9p	T90117V	1.20
BC308	8p	C1129	9p	T9051V	1.00
BC347	8p	E3005	14p	S2050V	1.50
BC394	8p	E5386	14p	S2052V	1.30
BC454	8p	ME0404	8p	S2053V	1.30
BC455	8p	ME0412	8p	S2054V	98p
BC460-6	40p	MEJ002	8p	S2059V	1.00
BC549	8p	MJE182	47p	S2800B	90p
BC556	8p	MJE340	50p	S2800C	1.00
BC559	8p	MJE520	65p	S2800D	1.25
BC595	8p	NKT241	8p	S2800E	1.40
		NKT276	20p	S2800M	2.00

### MIXED PACKS

300 Mixed Resistors	1.50	10 Spark Gaps	1.00
300 Mixed Capacitors	1.50	10-16 pin Quil IC Socket	90p
150 Mixed Electrolytics	2.00	20 Assorted TV Knobs	1.00
100 W/V Resistors	1.00	10-16 pin Quil to Dil IC Socket	90p
20 Mixed Conv Pots	1.00	100 Mixed Diodes	1.00
40 Mixed Pots	1.50	50 Mixed Mica Washers	65p
20 Mixed Sliders	1.00	300 Mixed Resistors & Capacitors	1.50
40 Mixed Presets	60p	10-16 pin Dil to Dil IC Socket	1.00
20 Mixed VDR & Thermistors	1.00	50 Electrolytics & 50 Capacitors	1.00
20 Mixed Ferrite Cores	50p	50 Mixed Poly Capacitors	1.00
100 Mixed Ceramic Discs	1.00	30 Mixed Neons & Bulbs	1.00
20 Mixed Valve Bases	1.00		

### AERIAL SOCKETS

AE Socket & Lead, Pye, ITT, Thom	25p
AE Socket & Lead, GEC	25p
AE Socket & Lead, (long) GEC	25p
AE Socket & Lead, Pye 691/693	25p
AE Socket & Lead, Philips KT3	25p
AE Socket & Lead, Thom col. portable	25p
AE Socket & Lead, (long) Pye 725/731	25p
AE Socket & Lead, ITT CVC32, etc	25p

UHF TV Aerial for portable 50p  
Indoor Aerial Parabolic Type Reflector to Help Combat Ghosting Problems 2.50  
Line Connectors 38p  
Coax Plugs 10 for 1.65  
Band Change Switch Assy, Pye 725 40p  
Flush Mounting TV/FM Diplexer 1.00  
Switched Flush Fitting Aerial Outlet 1.00

### INTEGRATED CIRCUITS

BRC/M/200	1.00	SN7666N	75p
BRC/M/300	1.00	TAA611	1.40
ML237B	2.00	TBA120CQ	70p
MC1327AP	1.25	TBA395	1.00
MC1358P	1.30	TBA480Q	1.40
SAA5010	6.00	TBA481	2.05
SL432A	1.80	TCA270A	1.05
SL1430	2.50	TCA270C	1.05
SAS590	2.60	TCA270CQ	1.05
SN15846N	60p	TDA1035T	3.50
SN74123N	65p	TDA1170S	1.50
SN74154N	1.40	TDA2540	3.50
SN78013ND/HS	1.80	TDA2690A	1.50
SN76023N	1.80	TDA3560	6.00
SN76033N	2.00	TDA9503	2.90
SN76115	2.00	MC14426P	4.80
SN76226N	1.25	MC14429P	4.50
SN76227N	1.00	MC14514	5.00
SN76544N	1.20	UA758PC	2.50
SN76660N	80p	UPC1365C	5.75
		SW153	2.50

Thorn 10Ω 20W (3500) R751 Safety Resistor 75p  
Pye 713 Speaker 5" x 3" 70Ω 1.00  
Pye 713 Complete Tube Base Panel with Focus Slider & Leads 2.75  
Pye 713 Control Knobs 4 for 50p  
Tube Base Socket ITT CVC32 45p  
Tube Base Socket Thom 3000/8000 etc 50p  
IC Insertor 16 Pin 50p  
Large IC Extractor 50p  
Crystal 4.43MHz 65p  
EHT Lead & Cap for Split Diode Lopt Anode Cap 90p  
Sanyo Anode Cap Assy + Lead, 12TCD-CT-1G 65p  
Degause Thermistors, PT37P, ITT/GEC 35p  
Degause VDR E299D/HP230 3000/8000 Casters Set of 4 1.90  
Double Fuse Holder on Small Pax Board 20mm type 10p  
Single Fuse Holder on Small Pax Board 20mm type 5p  
Direct Panel Mounting 20mm Fuse Clips (pair) 15p  
Single Fuse Holder on Small Pax Board, As per early 3000 mains input 6p  
EHT Cable 12 for 4.80  
13A Plugs 12 for 4.80  
TX9 Tube Base and Panel 65p  
3K PSU PL22 edge connector, + Lum to PSU 40p  
3K5 Complete Lum with all Plugs 2.00  
LM340 T12 on Heatsink 25p  
T9051V on Heatsink 60p  
BF259 with Heatsink 14p  
TIP110 with Heatsink 40p  
L129/130/131 Coil 10p  
6MHz Ceramic Filter 25p  
DL700 (Philips) Chrome Delay Line 1.00  
DL50 Chrome Delay Line 1.00  
T9006A Lum Delay Line 1.00  
8K5/9K Lum. Delay Line 65p  
Plastic Cover for 3K5 SP8385 5p  
TX9 Back Ground Control 10K 15p  
TX9 Gain Control 100R 15p  
1500 Metal Chassis Supports Pair 40p  
Thorn 8K5 Focus Pot 2.40  
Thorn 4000 Focus Pot 2.75  
Mullard EL34 2.80

### CAN TYPES

0.2MF 250V	50p	1250MF 40V	50p
2MF 250V	50p	1250MF 50V	50p
22MF 275V	50p	1500MF 70V Thom 3K	1.00
50MF 275V	50p		1.00
100MF 150V	65p	1500MF 100V	1.05
100MF 250V	70p	2000MF 30V	50p
100MF 450V	75p	2200MF 40V Thom 4K	95p
220MF 400V Thom 9K	1.30	2500MF 35V	95p
		3000MF 40V	65p
		3000MF 30V	65p
220MF 450V Thom 8K	1.30	3300MF 16V	50p
		3300MF 25V	60p
800MF 250V Print type	80p	4700MF 16V	72p
800MF 250V	70p	4700MF 40V	75p

### MULTISECTION CAPACITORS

100+150+150	16+16	450V 45p
220+47	350V 50p	200+100+100+50
200+150+50	350V 65p	350V 60p
200+200+100		350V 55p
32+32+16	275V 52p	200+20C+75+25
200+200+100+32	350V 70p	50+50+8
100+50+150	350V 58p	100+50+100
400+400	200V 72p	16+16
32+32+16	350V 52p	100+50+100
200+32+300+100	350V 70p	2500+2500 (Thorn 8K)
225+25	350V 50p	150+150+100
200+200+100	325V 65p	500+500 175V
200+100	350V 70p	200+47
		250V 65p
		Thorn TX9 1.00

### THICK FILM RESISTOR UNITS

3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90

### TANTALUM CAPACITORS

0.1MF to 470MF	£6 per 100
6.3V/10V/16V/35V	

### MINIATURE CERAMIC DISC

1PF to 10NF	50V/250V/500V
£2 per 100	or £15 per 1000

### HIGH VOLTAGE DISC

Most Values Available	2KV to 12KV
£5 per 100	or from £40 per 1000

With these items No Mixed Values in Lots of 100

### CAPACITORS

3.3PF	350V	3000PF	2KV
6.8PF	63V	3300PF	250V
8.2PF	350V	4700PF	400V
10PF	350V	30047MF	500V
12PF	1000V	0.075MF	2KV
22PF	63V	0.1MF	250V
47PF	350V	0.15MF	600V
182PF	63V	0.2MF	200V
250PF	2000V	0.2MF	250V
330PF	63V	0.22MF	250V
330PF	160V	0.47MF	400V
330PF	8KV	1MF	250V
470PF	250V	1MF	600V
560PF	63V	22MF	400V
1500PF	250V	33MF	250V
1500PF	250V	39MF	250V
1800PF	160V	47MF	250V
2700PF	63V		

Any 10 @ £1.00

### ELECTROLYTICS

1MF 63V	20/£1	100MF 25V	10/£1
1.5MF 63V	20/£1	100MF 160V	30/£1
2MF 350V	10/£1	150MF 25V	20/£1
2.2MF 25V	20/£1	180MF 25V	20/£1
4MF 64V	20/£1	180MF 40V	10/£1
4MF 350V	10/£1	250MF 16V	10/£1
6.8MF 40V	20/£1	250MF 25V	10/£1
10MF 40V	20/£1	330MF 10V	20/£1
10MF 160V	10/£1	330MF 35V	10/£1
15MF 15V	20/£1	330MF 63V	10/£1
15MF 63V	20/£1	470MF 6.3V	20/£1
22MF 10V	20/£1	470MF 10V	10/£1
22MF 63V	20/£1	470MF 25V	10/£1
22MF 160V	10/£1	470MF 40V	10/£1
32MF 275V	10/£1	680MF 40V	10/£1
33MF 40V	20/£1	1000MF 10V	10/£1
33MF 50V	20/£1	1000MF 16V	10/£1
33MF 250V	10/£1	1500MF 16V	10/£1
33MF 350V	10/£1	1500MF 35V	10/£1
50MF 25V	20/£1	2200MF 25V	6/£1
100MF 18V	10/£1	2200MF 40V	6/£1

### WIRE WOUNDS

2R 5W Thorn 3K	30p	36R 17W	23p	330R 7W	16p	4K7 7W Fus.	25p
22R 4W	16p	235R 9W Fus.	25p	370R 17W	23p	5K1 7W	16p
33R 9W	30p	220Ω 7W Fus. (Korting)	15p	1K2 10W Fus.	25p	8K2 7W	15p
10R 9W	18p			2K2 5W Fus.	25p	10K 7W	15p
10R 9W TX9	20p	270R 5W	15p	2K2 7W Fus.	25p	10K 9W	15p
15R 17W	23p	270R 7W	15p	2K7 9W Fus.	25p	12K 9W TX9	20p
22R 9W Fus.	25p	280R 17W	23p	3K9 4.5W Fus.	25p	39K 4W	15p
27R 7W Fus.	25p	330R 5W	15p				

### THORN 8/8K5 ex equip panels

untested PSU	2.88
FTB	3.75
Decoder	4.00

### THORN 9K ex equip panels

untested PSU	12.00
Decoder	5.00

### THORN 9K6 ex equip panel

untested Decoder	5.75
------------------	------

### THORN TX9 main panel

Complete (no tuner) ex-factory	11.00
--------------------------------	-------

### THORN 3/3K5 ex equip panels

untested PSU	3.75
LTB	3.75
Video	2.50
Chrome	2.00
FTB	2.75
IF	1.75
Conv. 3K	3.00
Conv. 3K5	3.75

### THORN 4000 PSU panel ex-factory

new	2.50
boxed	4.75
Thorn 3K5 beam limiter board new	1.75
Thorn 3K5 PSU bottom board PC206 new	2.75
Thorn 3K5 IF panel new	3.00
Thorn 3/3K5, EHT & scan TX + R2008B on alum chassis ex-equip	1.80
Thorn 8/8K5 damaged FTB for spares	1.25
Thorn 8/8K5 damaged decoder for spares	2.25

### DIODES

AA112	8p	IN4007	6p
AA119	8p	IN4742A	8p
AA143	8p	IN5254B	8p
BA115	8p	IN5349	14p
BA154	8p	IS025	8p
BB103	8p	IS131	8p
BR303	46p	IS1658	8p
BT106	1.50	MR854	35p
BT116	1.00	SKE1/02	25p
BY127	12p	MC1406	35p
BY204	26p	TIC106C	40p
BY296	22p	TIC45X	50p
BYX22/400	30p	2N4444	1.50
IN60	8p	Y827	80p
IN2070	8p	ZX150	12p
IN4001	4p	OAS1	1p
IN4002	4p	MC106/7	50p
IN4003	4p	MC106/8	1.50
IN4004	5p	TD3FR00H	2.80
IN4005	5p	TD3FR00R	3.00
IN4006	5p	BY255	30p

### ZENER DIODES

**TOSHIBA 200MV 10p each**  
6.2V, 12V.

**BZY88 10p each**  
3.9V, 5.6V, 12V, 16V, 20V, 30V, 33V.

**TOSHIBA 500MV 10p each**  
5.6V, 6.8V, 7.5V, 8.2V, 11V, 15V.

**BZX61 16p each**  
9.5V, 10V, 11V, 15V, 27V, 72V.

### MAINS DROPPERS

Pye 78+161	50p
Pye 147+260	50p
Thorn 56+1K+47+12	1.00
Thorn 50+40+1K5	60p
Thorn 128+16+1K7+116+462+126	50p
Thorn 120+72+300	50p
RBM 250+14+58 (TV161)	63p
Pye 3R5+15+45 (713)	90p

### EHT TRAYS

Thorn 3000	5.50
Thorn 8000	3.50
Thorn 8500	5.00
Thorn 9000	5.00
Thorn 9600	6.00
Thorn 900/950	3.00
Thorn 1500 3 stick 3.40	
GEC 2100	5.39
Pye 713 4 lead	5.83
Pye 713 5 lead	5.97
Pye 725	6.35

### THERMAL CUT OUT

Thorn 3000 Metal	1.45
Thorn 8/8500 Plastic	1.45

### FUSES

50MA	10 for 70p	250MA	10 for 65p
315MA A/S	10 for 50p	750MA	10 for 65p
500MA	10 for 50p	7A	10 for 50p
1A	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

### SWITCHES ETC

AM-LS-200
-----------

# TOP TWENTY T.V. SPARES

## STOCK NO.

001 Philips G8 Loptx (Genuine Philips)	7.50
002 Decca 30 series Loptx (Genuine Decca)	7.00
003 Decca 100 series Loptx (Genuine Decca)	6.50
004 ITT CVC 25/30/32 Loptx (Genuine ITT)	7.00
371 Pye 713/731 Vision Gain Module (replaces expensive 212-27327)	6.50
270 10 x BU208A	8.50
050 ITT CVC 5/9 EHT Tray	3.00
051 Decca 1730/1830 Doubler	2.00
053 GEC 2040 Hybrid EHT Tray	3.00
054 Thorn 1500 (5 Stick) EHT Tray	3.50
055 Thorn 8000 Doubler	2.00
056 Thorn 1400 EHT Tray	2.00
057 Philips G9 EHT Tray	3.50
058 ITT Universal EHT Tray	5.00
011 Thorn 1690/91 Loptx	7.00
012 Thorn 1615 Loptx	6.50
085 470 MFD 250V Philips G11	1.50
335 50 x BY127 Diodes	3.00
270 10 x BU326	10.00
280 25 x 2N3055	7.50

All components are A1 quality from prime manufacturers, and are dispatched by post same day as order received together with any refund due. All goods should be delivered within 4 working days.

Please add 15% VAT and 90p P & P

## LINE OUTPUT TX

001 Philips G8	7.50
002 Decca 30 Series	7.00
003 Decca 100 Series	6.50
004 ITT CVC 25/30/32	7.00
005 Philips G9	7.50
006 RRI T20	11.82
007 RRI A823	7.90
008 RRI Z718 18"	18.95
009 RRI Z718 20/20/26"	18.95
010 RRI A774 Mono	10.87
011 Thorn 1690/91	7.00
012 Thorn 1615	6.50
013 ITT CVC 45	6.50
014 Phil TX Chass.	5.00
015 RRI Ranger 1/2	5.00
016 ITT CVC 5/9	8.50
017 Philips E2 Chass.	5.00
018 Thorn 9000/9002	8.50
019 Thorn 9500/9600	8.50
020 Polish 161 Mono Loptx	6.00
021 Thorn 3500 Scan	4.50
022 Thorn 8500	11.00
037 Split Diode EHT Lead	1.35

## RECTIFIER TRAYS

050 ITT CVC 5/9	3.00
051 Decca 1730/1830	2.00
052 Decca 80 Series	4.50
053 GEC 2040 Hybrid	3.00
054 Thorn 1500 (5 Stick)	3.00
055 Thorn 8000 Doubler	2.00
056 Thorn 1400	2.00
057 Philips G9	3.50
058 ITT Universal	5.00
059 5 x TV11 For PTV's	1.00
060 3 x TV45 REC	2.718
061 ITT CVC 45	1.00
062 TVK52 Continental	2.50
063 RRI Z179	3.00
064 Pye 691/697	3.50

## CAPACITORS

080 220/400 CVC 32-T20	1.20
081 200 + 300 Pye 691/697	2.00
082 600/300 Philips G8 1.90	
083 175 + 100 + 100 Thorn 3500	1.50
084 2000/100 Can	0.50
085 470/250 Philips G11	1.50
086 400 + 400 Decca 30 2.50	
087 200 + 200 + 75 + 25 ITT5/9	1.50
088 400/400V Thorn 9000	1.50
092 10 x 220MF 16V Elect.	0.50
093 10 x 047MF 400V Poly	0.50
094 5 x 4.7MF/100V C514 T3500	1.25
095 5 x 0047/1500V RRI A823	1.25
096 5 x 91NF Philips G11	1.25
097 10 x 1/2000V 2.00	
098 5 x 1/250 Suppression ITT	2.75

## PUSH BUTTON UNITS

110 Pye 713 4 Wway	7.87
111 Pye 715 6 Wway	11.95
112 Philips G8 (Square)	10.75
113 Philips G8 (Sloping)	12.98
114 Thorn 9000 6 Wway	2.50
115 Thorn 1615 4 Wway	5.75
116 Decca 6 Wway	6.95
117 Decca 4 Wway	6.50
118 GEC 2110 6 Wway	7.95
119 GEC 2136/7 Tapered (6 Wway)	7.95

## TRANSISTORS - DIODES

120 ITT CVC5	9.25
121 ITT CVC8	11.45
122 ITT 6 Wway with V.C.R.	7.95
123 R.R.I. A823 etc. 4 Wway	7.95
124 Hitachi 4 Wway	7.95
125 R.R.I. T20 6 Wway	8.95

## INTEGRATED CIRCUITS

140 5 x TBA440	3.00
141 5 x TBA120AS	1.80
142 5 x TBA540	4.00
143 5 x TBA540Q	4.00
144 5 x TBA550Q	3.25
145 5 x TBA550	3.50
146 5 x TBA810S	3.00
147 5 x TBA920Q	3.50
148 5 x TBA990Q	3.25
149 5 x TBA520Q	4.00
150 5 x TBA530Q	4.25
151 5 x TBA950	4.50
155 5 x MC1327Q	2.50
160 TDA1170	1.35
161 TDA1190	1.90
162 TDA1006A	1.45
164 TDA1035	1.83
165 TDA1044	2.23
166 TDA1190	1.90
167 TDA1412	0.90
172 TDA2002	1.80
173 TDA2020	2.50
174 TDA2030	2.15
178 TDA2523	2.35
179 TDA2532	2.40
180 TDA2540	1.65
181 TDA2541	2.67
182 TDA2580	3.28
183 TDA2571	2.15
184 TDA2591	0.98
185 TDA2593	2.23
190 TDA2600	4.00
191 TDA2611	1.24
192 TDA2640	2.35
210 ETR6016	2.28
211 ETR6016	2.28
212 BT76018	2.38

## SPECIFIC SPARES

350 Thorn 1590/1	2.00
43 x 23 Thorn 1590/1	2.00
357 Thorn 1590/1	2.00
5 x 23 Thorn 1590/1	2.00
352 Thorn 1800 Dropper	0.50
358 5 x Thorn 3500 200R Conv. Pot.	1.00
359 5 x Thorn 3500 50R Conv. Pot.	1.00
370 Pye 731 Thick Film 1.50	
371 Pye 713/731 Vis. Gain Module	6.50
372 Pye 731 3R3 50V Metal clad	1.29
378 Grundig 5010/6010 Video Module	4.00
384 5 x Philips G8/10R Conv. Pot.	2.50
385 5 x Philips G8 Bright	2.50
386 5 x Philips G8 2k2 Lin. Bright	2.50
387 5 x Philips G8 10k Log. Color	2.50
388 5 x Philips G8 47k Log. Vol.	2.50
389 Philips G8 Plastic Mains Sw.	0.75
390 Philips G8 Metal Mains Sw.	1.23
391 Philips G8 Line Eql/ Stor. Coil	2.25

## 403 5 RRI T20 C.R.T.

Base	4.35
434 5 x Decca 30 2M Width Slider	1.00
435 10 x Decca 30 10R Fusible	0.50
436 5 x Decca 30 3R9 Modulohm	1.75
437 Decca 30 47k Vol.+Switch	1.25
453 5 x 5R Universal Conv. Pot.	1.00
454 5 x 20R Universal Conv. Pot.	1.00
455 5 x 100R Universal Conv. Pot.	1.00
456 5 x 470R Universal Conv. Pot.	1.00
457 10 x 100k Tuner Preset TCE etc.	3.00
458 10 x 100k Tuner Preset Philips G8	3.00
459 ELC1043/05 Repaired Tuner	6.00
460 ELC1043/06 Repaired Tuner	6.00
461 U321 New Tuner	7.95
462 U322 New Tuner	7.95
469 Cut Out Metal GEC 2100	1.00
470 5 x GEC2100 3 Leg Thermistor	1.00
479 5 x Gen. Purpose Rotary Switch	3.60
480 5 x Gen. Purpose Push Button SW.	3.75
481 20 x Neons GEC etc.	2.25
482 5 x Universal Aerial Skt.	5.50
483 10 x Metal Coax Plug	1.70
484 Focus Unit T20 Type	1.25
485 Focus Unit Thorn 8500 Type	1.25

# QUICK SAVE T.V. SPARES

MUXTON HOUSE, MUXTON, TELFORD, SALOP.

REG. OFFICE ONLY. CALLERS STRICTLY BY APPOINTMENT. UK ONLY. PLEASE QUOTE STOCK NO.

## N. J. ELECTRONICS

UNITS 82/83/84 STORFORTH LANE TDG. EST. HASLAND CHESTERFIELD, DERBYSHIRE S41 0SN. TEL CHESTERFIELD 209079

### PUSH BUTTON UNITS

DECCA 30 6 button	£7.96
GEC 2110	£9.00
GEC 2112 7 button	£13.10
GEC 2136/2137	£8.35
ITT CVC 5	£10.50
ITT CVC 8	£14.00
G8 SQUARE (early)	£12.50
G8 SLOPING (later)	£13.55
PYE 713 4 button	£9.15
PYE CHELSEA	£12.98
RRI 823 4 button	£8.74
RRI 823 6 button	£9.45
RRI Z718 6 button	£9.90
TELPRO 4 button	£8.75

### EHT TRAYS

DECCA 80	£5.95
DECCA 100	£6.00
SEIMENS UNIVERSAL	£6.30
GEC 20AX	£6.70
GRUNDIG 5011	£6.10
KORTING	£7.22
PHILIPS KT3	£6.00
PHILIPS 550	£6.50
PHILIPS 520	£6.50
ITT CVC5	£6.00
ITT CVC45	£7.00

### LOTXs

THORN 1590/91	£9.70
THORN 1615	£9.20
THORN 1690/91	£8.45
RRI T20/22	£11.95
RRI 774	£11.50
PHILIPS G8	£8.50
PHILIPS G9	£9.00
PHILIPS 210	£9.50
PHILIPS G11	£12.75
PHILIPS K30	£14.00
ITT CVC30/32	£8.50
ITT CVC45	£8.50

### ICs

TDA2522	£2.30
TDA2523	£2.40
TDA2540	£2.00
TDA2571	£2.20
TDA2581	£1.70
TDA2600	£4.25
TDA2611	£1.75
TDA2680	£1.85
TDA2690	£1.80
TDA2593	£2.75
TDA1170	£1.80
TDA1190	£2.00
MC11358P	£1.40
MC1327	£1.50
TBA920	£1.90

ADD 65 PENCE POSTAGE + 15% VAT TO ALL ORDERS.  
(See CONTRAST U.K. advertisement in this copy, all your component, panel and TV needs under one roof.)

Please allow approx. 7 days for delivery.

## COLOUR TV SETS

Philips G8, Pye 222, Decca 30 series, ITT, Pye Chelsea, Thorn 3500/8000, GEC, many others including JAP.

Working hybrids from £15.  
Working solid state from £25.  
Non-working sets, working panels and tubes available.

### Quantity Discounts

Delivery by arrangement.

**SOUTHBRIDGE TV CENTRE**  
120, Selhurst Rd., London, S.E.25.  
Tel: 01-771 3535.

## A.B.C. ELECTRONICS

Rear of 20, HANKINSON ROAD, WINTON, BOURNEMOUTH. TEL: 519542

**TRADE TV's BEST PRICES**  
Colour From £12.00 + VAT  
B&W From £2.00 + VAT

### DISCOUNT ON QUANTITIES

ALL MAKES - ALL SIZES - ALL COMPLETE  
CALL IN OR RING FOR COMPETITIVE QUOTE  
FULLY REFURBISHED SETS AVAILABLE  
+ DELIVERY SERVICE

# Letters

## THORN 9000 CHASSIS

Having serviced sets fitted with the Thorn 9000 chassis for several years, I found your article on it in the May issue full of interest. I'd like to make the following additional points.

(1) As you say, the mains filter capacitor can go short-circuit. You didn't however mention the fact that it can often burn quite intensely – in one particular set I dealt with it seriously burnt the wiring loom, which had not been dressed back properly. In later versions of the chassis the filtering arrangements were altered.

(2) Diode W702 (in series with the Syclops transistor) can go short-circuit as well as open-circuit. When it goes short-circuit R7 (390Ω) on the tuner board usually burns up quite fiercely. This can cause confusion if you're not familiar with the chassis.

(3) As these sets get older I find more and more often that there's little or no first anode supply adjustment available from R721. This can usually be cured by replacing R722 (2.2MΩ) which is in series with R721 on the earthy side.

*M. L. Pattenden,  
Headley Down, Nr. Bordon, Hants.*

## RANK Z718 LOPT

We would like to draw attention to a problem associated with line output transformer harmonic tuning in the Rank Z718 chassis. Looking back through the articles you've published on this chassis, it appears that the side effects of fifth harmonic mistuning have never been touched upon.

On taking over the Rank transformer operation in Dublin some months ago, we carried out an investigation into the high failure rate of these units. This revealed that the vast majority failed as a direct result of 5L3 being mistuned. Judging by the core position on previously returned units, it appears that service engineers had been tuning the coil to eliminate striations on the raster. This simple method is convenient but extremely subjective and should never be relied upon for accurate tuning of this transformer.

To overcome the problem, we now pretune these units on test. We can supply an information sheet entitled "Reliability and Harmonic Tuning" on receipt of a stamped, addressed envelope.

*E. F. Phelan, Technical Manager,  
Woodsdale Components, 34 Field End Road,  
Eastcote, Pinner, Middx. HA5 2QT.*

## ION TRAPS

We recently had in for repair a small monochrome portable of the type that's very familiar these days – it had the almost obligatory shiny white case, and worked quite well after the repair had been carried out (a faulty voltage regulator).

The c.r.t. had a white label, with the familiar red lettering. In place of the usual name Toshiba however it had the name Samsung, made in Korea. The c.r.t. type number was not unusual, though the ten-digit serial number looked somewhat out of place on such a small

tube. Also present in red lettering were the usual warnings about high voltages and so on, and in small print there was the rather startling caution "do not use an ion trap".

Now as an old timer I can remember that ion traps were at one time a very necessary item in order to avoid screen damage from negative ions – since the ions are much heavier than the electrons given off by the tube's cathode, they are less affected by the magnetic deflection fields and thus tend to cause ion burn at the centre of the screen. Special gun arrangements were introduced to operate with an ion trap magnet, the idea being to separate the ions from the electron beam and direct them to an intervening anode. After a period of time it was necessary to readjust the magnet – a deft twist would usually restore a bright picture, and produce the odd fast buck! The ion trap went out with the use of aluminised screens however.

Some later tubes featured a steering magnet, adjustment of which not only restored the picture but would centre it horizontally and vertically. Such memories brought back thoughts of triode tubes, 2V heaters, heater-cathode shorts, round screens, and isolation transformers. On one occasion in a moment of desperation an innocent, unsuspecting audio output transformer was pressed into service as a heater isolation transformer.

It seems odd that a very modern TV set, manufactured by inscrutable gentlemen in a far away country, should trigger off such a trip down memory lane – all due to a strange warning in small print on the c.r.t. label! Or am I missing something?

*A. S. Foster,  
Brixham, Devon.*

*Editorial comment:* Samsung is one of the two major Korean TV manufacturers. The company started to manufacture TV sets in 1969, in collaboration with Sanyo (the partnership was subsequently terminated). You certainly can't use an ion trap magnet on a tube not designed for it – and ion trap tubes were obsolete long before 1969. We can only assume that the warning is one of those things that goes on being repeated long after it's necessary. How many Koreans would know what an ion trap magnet was!?

## TOSHIBA C81B

Reference was made in the June Service Bureau to the problem of h.t. fuse blowing and the line output transistor Q404 going short-circuit in the Toshiba Model C81B. I've also had this fault, which was eventually traced to the 105V h.t. series regulator transistor Q801 going leaky. It's mounted on a large, rather inaccessible heatsink and is type 2SC1195 – a BU126 can be used for improved reliability.

When Q801 goes leaky the h.t. rises and the line output transistor, which is operated with little margin, fails. Fuse F803 then blows.

The 2SC1172 transistor can be replaced with a BU208, which should also be a lot more reliable.

*B. Knapp,  
Cheltenham, Glos.*

## A NEW G8 FAULT?

A customer phoned to say that the picture was taking a long time to appear on his set, an old Philips G8 – anything from five minutes to half an hour. The sound was o.k. Two months previously I'd fitted a new transducer as the old one had burnt out, and at the time I'd checked the

tube emission. This was low, so I'd given the customer a quote for a new tube. It seemed to be just a matter of a quick pick up, fit the new tube, and check for the fault.

I didn't bother to try the set before fitting the new tube, expecting the tube to solve all problems. All was indeed well when the set was switched on, so the convergence was set up and the receiver left on soak test. I later switched off whilst attending to another set, but when I switched on again for a final check before putting the back on there was no picture, no e.h.t., no blown fuses – in fact the set appeared to be just sitting there!

Out with the meter to check for drive and voltage at the line driver transistor, during which time the sound came on and within seconds there was e.h.t. and a picture – but the picture wasn't as bright as during the previous test. I stood back in amazement! Switch off, then on – no picture at all. So I was back to square one, though this time I'd a chance to look around. The line driver transistor's collector voltage was low but there was no fuse blowing, so as these sets are prone to faulty line output transformers a replacement was tried. Problem the same, and time to give up for the day.

The next day offered nothing more interesting than another G8, this time completely dead with a blown h.t. fuse due to shorted turns in the line output transformer – always keep one in stock! I went back to the first set and

decided to try swapping over the line output units complete. The set now worked very well, so I looked around the first panel for the problem. One of the line output transistors had a collector-emitter leak – this has got to be it! Fitted two new BU208s, refitted the panel, but still no go, no e.h.t. or sound.

Out with the scope. The h.t. was disconnected from the line output stage (link PC1) and checks made on the driver stage. Plenty of drive on the primary of the transformer, and the voltages now correct. Replace PC1 and the collector voltage dropped. Attention was turned to the small subpanel which houses the line output transistors' base circuit components. Check all resistors and find that the two 10Ω damping resistors R527/9 are slightly high but within ten per cent tolerance. Tried fitting old scrap subpanel and everything came on smashing. For interest I interchanged the components one at a time and, would you believe it, it was the two damping resistors even though they were within tolerance.

Three days later the line output transformer died, but that's another story. I hope this tale may serve as a warning to others – what with all the running around I think I must have lost money on this one! Book it to experience.

*K. D. Bunting,  
Hartford, Cambs.*

---

## Aerial Systems and Faults

*Peter Richards*

There are many occasions when a service engineer finds that a fault he has been called to attend to is due to the aerial rather than the set. In this event it's a good idea to establish what's wrong with the aerial system so that the customer and/or aerial rigger can be told what needs to be done. A good aerial system will provide at least 1mV of ghost-free signal at the set's aerial socket – this is particularly important for teletext reception.

The TV transmitters in the BBC/IBA network range from very powerful to very weak – some relays are so weak that a line of sight location is no guarantee of good reception. For all transmitters however there's a "service area", which is defined as the area in which a reasonable aerial system will provide a 1mV signal at the set. This is open to interpretation. We will consider the various types of aerial systems in turn and see what can go wrong with them.

### Indoor Aerials

Simplest of all is an indoor aerial, though no self-respecting salesman or engineer will suggest using one. Except for the odd special location, an indoor aerial will not give 1mV, while the strength and number of ghosts always varies as you walk around the room. This means that justice cannot be done to a colour set's performance capability and the customer is never completely happy.

### Simple Aerial Systems

The aerial's job is to gather sufficient signal to overcome the losses in the downlead and leave at least 1mV at the end. For this purpose it must be large enough (depending on the field strength at the location), high enough (to overcome losses from obstruction in front),

and correctly aligned (to avoid ghosts due to signals reflected from trees, buildings, etc.).

A ten-element aerial will suffice in strong signal areas, larger aerials being required towards the edges of a transmitter's service area. It's important that the cable connection to the aerial is secure and watertight, and that the cable itself, which should be of the low-loss u.h.f. type, is fixed securely down the mast, down the roof (every three or four tiles) and into the house, where it should terminate in a good, clean coaxial plug, with the inner conductor soldered.

The faults that can occur with such an installation are not too complicated. The aerial may blow down, or round (giving ghosts). The aerial and/or its connections may become corroded over the years, reducing the system's efficiency. The cable may go open-circuit (with most aerials the cable should normally read short-circuit across the coaxial plug) or short-circuit, or sustain other damage from not being properly fixed. It may also deteriorate from old age.

Renewal is the best policy. It's important however to remember that the installation may not have been adequate in the first place. An aerial in the loft for example will not be high enough in the vast majority of cases, nor free from obstruction, and will thus not provide the required signal.

### Aerial Plus Amplifier

An amplifier must be used where the largest practical aerial does not give 1mV at the set. Amplifiers are available with different gains, according to requirements. To improve a slightly sub-standard signal in an otherwise good area, use a low-gain amplifier (gain 12dB or four times). Medium-gain amplifiers (20dB or ten times) are

used mainly as repeater amplifiers to make up for losses in cables or losses due to the use of splitters in the aerial system. High-gain amplifiers (30dB or thirty times) are needed where the signal is poor, usually outside the service area.

An amplifier system usually consists of two parts, the amplifier itself and a power supply (see Fig. 1). The amplifier should be fixed to the mast near the aerial – but not too near as this can cause feedback. This position for the amplifier is important in order to minimise noise. The stronger the input signal, the more it will swamp the amplifier's noise. Hence mast mounting is preferable to the use of a set-back amplifier. The power supply will be in the house, usually behind the TV set. For safety reasons it must not be wired into the same plug as the television set.

## Amplifier Faults

Faults with this sort of installation consist of those due to the amplifier in addition to those due to the aerial itself (see above). Power unit faults are easy to find simply by disconnecting the unit from the amplifier and making voltage checks. Alternatively the amplifier itself could be faulty: it may read open-circuit (usually an open-circuit powering choke or a connection), short-circuit (usually the zener diode or a connection), it may not be amplifying properly (possibly due to transistor failure), or it may simply be covered in water and corroded to bits because someone hasn't mounted it properly.

A more confusing fault is cross-modulation in the amplifier. This looks like either poor field interlace or one station in the background of another. The basic cause is excessive input signal, or a faulty amplifier. The signal levels in a particular area may be liable to fluctuation with weather conditions, and may have risen somewhat since the system was installed. Once more we must be on our guard against an inadequate installation. The installer may have skimmed on the design of the system in a misguided attempt to save the customer money – the inevitable result of this is that when the system deteriorates a little, as all systems do, snow starts to appear on the screen and a service call is eventually made.

## Multiple Amplifier Systems

Multiple amplifier systems are used when the aerial has to be sited some distance from the house – the distance may be some tens of metres to hundreds of metres up the side of a mountain. The system is similar to that previously

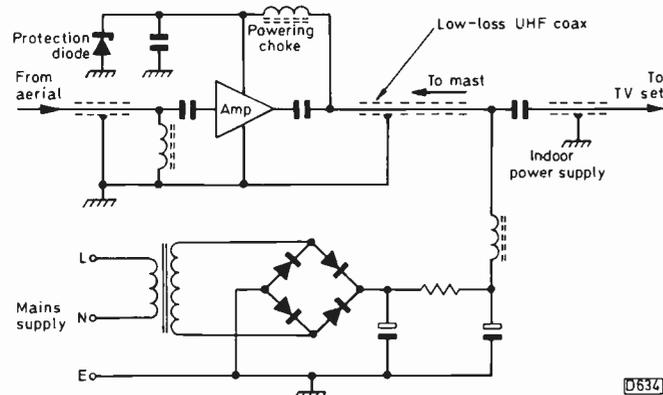


Fig. 1: Aerial amplifier and power supply. The power supply provides 12V or 24V according to type.

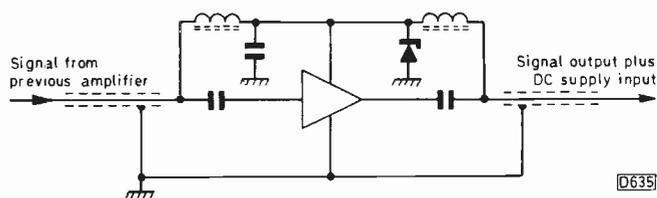


Fig. 2: Amplifier with through powering for use as a repeater in a multiple amplifier system.

described except that there will be repeater amplifiers every 80 metres or so – it may also contain attenuators and equalisers. This type of system is very difficult to design properly. Many are installed using rules of thumb. The results are generally not very good.

Faults are usually simple to identify. The amplifiers will be line powered as shown in Fig. 2. Power supply faults can be sorted out initially by measuring the current taken from the power supply. This will give a clue to the total number of amplifiers taking current. Voltage checks at each amplifier will then probably lead to the fault. If the fault has not been found when you arrive at the aerial, a check on the signal at each amplifier on the way back will locate it.

Because of the accurate design and setting up required, this type of installation is prone to either cross-modulation or low output. The most difficult faults to find are those due to gradual deterioration and loss of performance in almost every item in the system.

## Communal Aerial Arrangements

Communal systems are used to feed blocks of flats or even whole villages in mountainous areas. They are basically an expansion of the multiple amplifier system just described. The signal levels are usually much higher however, 30mV to 100mV being typical. Outlets to individual houses are through "tap-off boxes" which feed a small percentage of the total signal to each customer's house. Isolation is also provided to protect individuals and the system from the mains supply.

It's not unknown for outlets to individual houses to go faulty, generally due to corrosion, but most faults are of a communal nature. These faults are the same as those that affect a multiple amplifier system.

## Conclusions

Finally some general comments. If the picture is snowy, check with a signal strength meter. Grain starts to show at about  $400\mu\text{V}$ . The picture will be watchable at  $200\mu\text{V}$ . If you haven't got a signal strength meter, you can make one very simply from a TV set reserved for test purposes. All that's needed is to connect a voltmeter to the set's a.g.c. line, calibrating this against a known source.

Don't be fooled or misled by trying other sets – they may have slightly different gains or frequency responses. Use another set to prove the point, but not to make the initial diagnosis. Many a tuner has been changed in error!

Skimping on aerial work doesn't pay: remember that a wasted service call to look at a snowy picture can cost the dealer as much as the amplifier or a bigger aerial that should have been fitted in the first place.

The information above should enable an engineer to provide an accurate diagnosis of an aerial fault on any sort of system and advise the customer accordingly.

# Laura's Dead Decca

Les Lawry-Johns

I'm sure you all remember Laura Lovitt, last reported as tampering with Titch the telephone man and giving me the old heave ho when she thought she was going to be busy one afternoon, and me going back to the shop to find another telephone chappie bugging about in the bedroom. Well, every dog has his day, he who laughs last, and all that.

The phone rang and it was Laura to say that her legs had at last given way and the Decca was now a damaged Decca. Could I call this afternoon?

"Are you sure your telephone's not tapped?" I asked.

Laura gave a gurgle. "He was only showing me how to fill in a football coupon. Very patient he was too."

"All right then. I'll be down this afternoon."

## How to Oblige

And down I went to give the legs a close inspection before examining the Decca. The frame's woodwork had given way as though the legs had been asked to support an extra offset weight (perhaps the set had been shoved from the side?). I could see from the front of the Decca that the tube had lost its vacuum, and this was confirmed by the sight of the bowler hat on the rear cover. It was cracked and bowed in, the tube base was in pieces, and the tube's neck was beyond recall. I shook my head sadly. "Sorry Laura. It's right bugged."

"I know it's bugged" said Laura with no trace of sadness, "but it's also insured and I've been wanting a new set for a long time. Now I'm going to get it."

We discussed just what she wanted for some time, and as the bedroom was only a sliding door away I suggested that perhaps a smaller set with remote control would fill the bill, so that she could watch the late night programmes in bed, change channels and switch the thing off without getting up, then wheel it back into the lounge in the morning. This idea seemed to appeal to her, so I nipped back to the shop for a 20in. remote control model and had it installed and working in no time.

She said the picture was good and she liked the remote control but the front presented a sort of blank, black appearance. Would she like to come back to the shop to see some others then? No. They don't look the same in the shop. So she wouldn't really be able to tell.

To cut a long story short, I had to do quite a bit of running around before she finally liked the Pye 3262 with full remote control, and of course she had to be sure that everything worked as she lay on the bed (it's not easy trying to satisfy some people...). She said she'd let me have the cheque when the insurance had been settled. I'm still waiting.

## Les the Bodger

I was asked to do a very quick job the other day. We'd had to write off Mr. Toolong's old 26in. Thorn 3500 as a dead loss. Until he bought a new set he was having to rely on his Philips 16in. portable (KT3 chassis, with remote control). This was in urgent demand by the family there-

fore, but had "gone funny".

The "funny" bit was that the colour was at maximum and couldn't be turned down. The controls consist of plus and minus buttons, but the colour couldn't be turned down no matter how many times the minus button was pressed. I rather suspected i.c. failure, and the first suspect (to me) was the SAF1032P remote control decoder i.c. (IC807), but there wasn't one in stock. The relevant bit of circuitry is shown in Fig. 1. Voltage checks confirmed that the control voltage at the emitter of transistor TS840 was over 4V and remained at this level instead of varying between 2V and 4V. This meant that TS840 was being turned on excessively because its base voltage was high. The voltage at the collector of TS836 was in turn high because there was lack of turn-on bias at its base. This suggested that either IC807 or R832 was faulty. R832 was in order - as were both transistors - so our suspicion of IC807 deepened. Frantic phone calls were made. "Sorry Les." "Sorry Uncle Les." "I'll have to send for one Mr. Toolong."

"But we want it today. Now!"

I looked at the preset R838. It didn't vary the voltage at all, but could be made to do so by wiring a little resistor across C839. Try 22k $\Omega$ . Not really. Try 15k $\Omega$ . Nice variation as the preset was turned.

"Well now Mr. Toolong, this control here is the ideal colour preset, and once I set it to your liking that's it."

He was quite pleased with this bodge up, and carried the set away smiling.

I was relieved too. It didn't have to be that particular i.c., because it gets its input from IC761, and there are various other complications.

## Minimatic, Big Wallop!

Here's a warning - be careful of those small Yugoslavian Minimatics. I was trying to sort out the print side position of a transistor and reached over to locate just where it was with my right hand. I must have jumped a couple of feet in the air (well, say two metres) or more. Whilst the e.h.t. stick is fully shrouded, the e.h.t. connection isn't - it's just a solder blob exposed to all and sundry, including me. You may say that it serves me right for not looking where I put my hands. Quite so. But I wouldn't like you to get the same.

## Fun with Fidelity

We've sold quite a few of these Fidelity CTV14R (and S) sets during the past year or so. Some have required attention recently.

The weak link appears to be the line output transformer, though this is not immediately obvious. The symptoms are that the h.t. builds up after switching on and then collapses with a tick, the process repeating. This

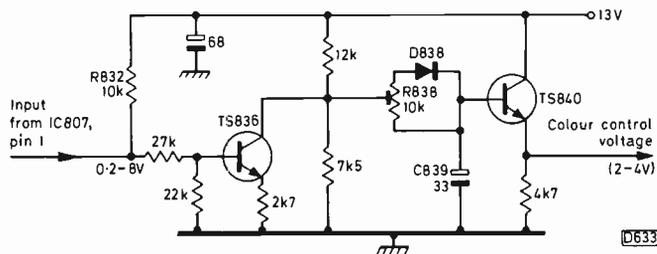


Fig. 1: Preset colour control circuit, Philips KT3 chassis (remote control version).

could of course be due to various overload possibilities or to the TDA2581 chopper control i.c. playing about. When the set is switched off, you may find that e.h.t. is present under the e.h.t. connector cap. This tends to suggest that the line output transformer is working correctly. When a replacement is fitted however the set works normally (for us, so far).

Removal of the transformer in the earlier model is quite easy – unsolder the tags, turn the tag round for exit, and remove the two screws at the top frame. In later models there's an extra strut on the frame. This covers the tag and means that the panel screws have to be removed to allow the panel to be raised from the frame.

Another frequent fault is failure of the chopper transistor TR13 (type BUX84 or BUV46). The transistor tends to go short-circuit, as a result of which the h.t. rises and the set shuts down.

The front control panel is also a bit flimsy and can develop cracked print, dry-joints and the like.

Intermittent operation, with all the channel LEDs coming on for a brief second, is often due to a dry-joint on one of the two long wirewounds at the rear left side. A moment spent resoldering these connections can be very rewarding.

### **Bette's G8**

Bette Hind is a lady with a lot of gusto. It's like a hurricane hitting the place when she comes in. "Hallo Les Luv. Will you get my set out of the car for me only I'm on double yellow lines and can't get away with it now they're all women."

"I can" I smirked. "You've only to rub them all over with soft soap."

Anyway, I got Bette's 20in. Philips G8 out of the car and on to the bench, and caught sight of the worried look on her normally alive with laughter face.

"I think it's had it this time Les. The picture went and there was a hell of a stink, then the lot went off, puff, just like that."

"Don't worry Bette. In five minutes it'll be as good as new."

So I took off the rear cover (a screw in each corner instead of the usual G8 struggle fit). Over on the right side I could see the transducer looking sick, so I removed plug H (the red one) to stop that nonsense and plugged the set in. Nothing. There was voltage at the bottom end of the top section of the "dropper", but nothing at the top. I switched off and decided to short the dropper tag to earth to get rid of the charge on the reservoir capacitor. Bang it went, because I'd not bothered to use a resistor, risking the screwdriver blade instead.

Bette jumped two metres in the air, just as I'd done earlier. "I told you the bloody thing was finished" she bawled. "It'll kill us all. Mrs. Seer said she saw it in the cards the night before last."

"Shut up for Gawd's sake" I snapped. "The thing's nearly done now."

"Done in more like it" she moaned.

I put in the new dropper and checked the fuses. The lower one on the left side (800mA) had blown. With this replaced the set was switched on and a good picture appeared. Being a 20in. model, the absence of raster correction (plug H out) was not noticeable.

"That's bloody marvellous" exclaimed Bette. "What about the smell?"

"It's Ben" I explained. "He's been a bit loose lately."

# next month in

# TELEVISION

## ● THE BETAMAX SYSTEM

Most published material and courses on VCRs are based on the Philips N1500/N1700 or the JVC VHS system, simply because the former was the first to appear on the market while the latter has been the market leader throughout. This means that the Sony Betamax system is probably less well understood than the other systems, though some Beta machines have sold in large quantities. Next month Eugene Trundle sets out to redress the balance with a new series on Beta video. The emphasis will be on areas where there are fundamental differences between the Beta VCR system and its better understood rivals.

## ● SERVICING THE PHILIPS TX CHASSIS

Pye and Philips monochrome portables fitted with the TX chassis have been good sellers for several years. John Coombes provides a quick fault-finding guide.

## ● VINTAGE TV – THE PILOT VS9

Pilot Radio was a well known name just before and after World War 2, mainly because of the firm's innovative radio sets. When the first Pilot TV set, the VS9, came along it too had unusual aspects. Chas E. Miller delves into another interesting bit of TV history.

## ● A MATTER OF SAFETY

Those who deal with dozens of TV sets often tend to become blasé about safety matters. Nevertheless a TV set, especially a defective one, can be a very dangerous object. Tony Thomson deals with the various aspects of the subject, both in the workshop and in the field.

## ● CTV BATTERY OPERATION

George Wilding takes a look at various approaches to supplying colour portables from a 12V or 24V battery. The TA126 converter used with later versions of the Thorn TX9 chassis is considered in detail.

**PLUS ALL THE REGULAR FEATURES**

**ORDER YOUR COPY ON THE FORM BELOW:**

TO .....  
(Name of Newsagent)

*Please reserve/deliver the August issue of TELEVISION (90p), on sale July 20th, and continue every month until further notice.*

NAME .....

ADDRESS .....

.....  
.....

# Light on Servicing

*Eugene Trundle*

IT'S strange how the habits of a lifetime die hard. For years I've been using a conventional spring-arm bench lamp for close illumination while servicing TV equipment – the familiar type with a heavy base, cantilever arm system with compensating springs and a conical shade/reflector. It never occurred to me that anything better might be available. The disadvantages of this type of lamp are several, and perhaps not appreciated until one thinks about it.

The light coming from the small glow area of a filament bulb tends to cast shadows, making it necessary to move the lamp about to get satisfactory illumination. Then the bulb and its shade get uncomfortably hot, which is fine for setting epoxy-resin joints, but inconvenient for the operator and disastrous if the lamp, forgotten for a few minutes perhaps, is allowed to dwell near the plastic cabinets and covers that are common on consumer equipment these days. My lamp seems to suffer more than most from "brewer's droop", and on three occasions lately the 75W bulb has descended on to plastic TV backs and VCR deck covers with strange and fantastic, also expensive and smelly, results. The bulb always seems to fail at the crucial moment, and if a higher rated bulb than specified is fitted the result will be premature failure, often accompanied by an evil smell from the overheated bulbholder. Power consumption is yet another factor. This matters little in mains operated workshops, but I met a man who services radio-telephone equipment recently: he has to count the watts like Les counts the calories!

There are several types of illuminated magnifier on the market for close work on intricate equipment – they've long been used by watchmakers, factory operatives, dental technicians and so on. I found three listed in the catalogues of well known suppliers to our trade, and selected for review the Ledu type 271 which is available from Philips Service.

## **The Ledu Magnifier**

It's the least expensive of the full size types, and seems to offer as much as the competition. The counterpoised cantilever arm stems from a "pod" at the base, in which the fluorescent tube's control gear is housed. The arms are longer than the conventional bench/desk lamp, giving a wide arc of movement. At the business end a 24cm. diameter circular plastic housing contains a ring type 22W fluorescent lamp. An on-off switch is incorporated in the housing, and inset in the middle is a 12cm. diameter precision ground glass lens with a magnification factor of 1.75.

The fluorescent tube is protected from damage by a plastic diffuser with a faceted surface to spread the light wide. The ensemble is fairly heavy, and is supported by means of a clamp-on bench socket. The sockets are available separately, so that one lamp can be used in several positions around the workshop, plugged in and supported wherever needed. The lamp itself has a vaguely medical or dental look about it, which may be daunting to some – especially when laid beside the syringe and scalpel that forms part of our tool kit!

The first thing that struck me in use was the brightness of the illumination provided by the 22W tube. Because of the large source diameter and the action of the diffuser, no shadows are created. The light has a bluish quality – rather like the Gro-Lux tube in my fish tank at home. With the lamp poised over a TV chassis or VCR deck, I found that I could see all that was going on with the lamp a couple of feet away from the works. Used in this way, as a bench lamp, the device can be swung well away when not in use.

The focal length of the central lens is about 30cm., beyond which the defocusing effect is accompanied by a sort of blue/yellow misconvergence! The 30cm. focus depth enabled me to work on panels, mechanics etc. while viewing through the lens – an ideal situation for soldering small assemblies, checking joints, and particularly servicing and adjusting audio and video decks. Some service manuals these days contain circuits in which the equivalent of about three TVs is crammed into a single page – these myopic diagrams are much more easy to read with the aid of this instrument. I found that the cantilever arm assembly is well balanced and well behaved – a couple of knobs are provided to adjust the friction.

A few words on safety. The lamp has a three-core lead, with the earth conductor connected directly to the metal arms and springs. I would have been happier with a twin-core lead, with double insulation if possible, because a large and accessible earthed mass in such close proximity to live electrical equipment is not, so far as I am concerned, a good idea. A shock hazard can arise even when an isolating transformer is used, so I disconnected and insulated the earth wire at the plug end, after checking for good insulation resistance between the mains leads and exposed metalwork.

The other hazard, perhaps not immediately obvious, is the possible fire risk when the magnifier is left unattended with the sun shining on it. Experimenting in the garden one sunny day I had no problem in igniting a newspaper in five seconds flat! A lens cap is provided to prevent such happenings.

A good and worthwhile service aid then for the modern workshop. Good service aids are not cheap, but £52-00 plus VAT (net to the trade) is not excessive for this instrument. Its large physical size is a disadvantage only when one suddenly bobs up from a tape deck or whatever to find oneself crowned and haloed! The Philips Service stock number is 395-37125.

## **Other Optical Aids**

In conclusion it might be worth mentioning a couple of other optical aids I've found helpful for TV and VCR servicing. Both are from the expanding optical aids section of the RS Components catalogue, are relatively inexpensive and very useful.

The first is a watchmaker's eyeglass (stock no. 544-055) with a magnification factor of eight and a focal length of 31mm. It's useful for inspecting video heads, tape guides and small electronic components, and works well for checking beam landing (purity) in shadowmask tubes.

The tape path in a domestic VCR is such that many critical mechanical and electrical deck components are difficult to see, clean and check. Cotton buds are very useful for cleaning, and a dental-style angled inspection mirror is almost indispensable when working on such equipment. The one marketed by RS Components (stock no. 549-319) has the useful feature of being fully insulated. I can heartily recommend it.

# The New Thorn TX90 Chassis

The story behind the Thorn TX90 chassis is no less fascinating than the set itself, with its novel mechanical and electrical arrangements. The challenge was to produce a quality small-screen colour portable that could compete in price with anything likely to come from the Far East. A small-screen portable was seen by Thorn to be important for two reasons. First, this section of the market is expanding faster than any other – sales of colour portables in the UK exceeded 900,000 in 1982 and are expected to reach 1,100,000 this year. Secondly, getting a competitive set into production would have important consequences for Thorn's TV plants in terms of the economies of large-scale production.

Thorn have invested £2.5 million in production facilities for the TX90 at their Gosport plant, where CTV production is being built up from some 500,000 a year to 700,000 a year. Production of TX90 sets is already running at a rate of 150,000 a year and is being built up to 215,000. The plant also produces the 1790 series monochrome portables, with production at present running at a rate of 300,000 a year. An additional 250,000 colour sets, using the TX10 chassis, are produced at the Enfield plant.

These figures give an idea of the importance in terms of scale of having a range of chassis to meet all requirements, from large-screen 110° models with full remote control and teletext to the TX90 14in. portable. There is certainly a market for the TX90, and with its suggested price of around £169 for the initial Model 37140 it's evident that Thorn have got their costs right. Just how is production of sets to sell at this price possible? The answers relate to simple mechanical layout, reduced component count and, in particular, efficient manufacturing technology.

## Production Aspects

The key to the latter is to make maximum use of the capabilities of the latest automatic component insertion equipment. To put it simply, the TX90 has been designed and laid out so that two complete chassis, including the c.r.t. base panels, occupy the space of a single standard panel (made from a 345 × 375mm Euroblank). Since the automatic component insertion equipment is designed to handle this size of panel, two TX90s can be produced simultaneously on the same panel and be separated at a later stage for testing and assembly into complete receivers. In comparison, you get just one TX9 or TX10 chassis from a Euroblank.

The electrical design of the TX90 was to a large extent determined by this need to get two sets out of one standard panel and thus make optimum use of the production facilities. Three factors enabled this requirement to be met. First the choice of suitable circuitry, to which we'll return. Secondly the use of a new i.c., type TDA4500, which incorporates all the signal processing circuitry, including the timebase generators, apart from the decoder. Thirdly much greater use is made of upright (radial) component mounting – there are 184 radially mounted components and 54 axially mounted components. A further constraint on the electronic design was imposed by

the fact that there's a limit to the number of different types of component that the automatic component insertion equipment can handle. This, together with cost considerations, explains the fact that the component count is not as low as theoretically possible, i.e. groups of small resistors are used in several places instead of one larger resistor. The limit to the number of component values that can be used imposes a further discipline on the electronic design.


## Mechanical Arrangements

The other major factor contributing to the low cost of the TX90 is the mechanical arrangement. The moulded cabinet has just two sections, the cabinet itself and the back panel. The main printed panel is held by moulded runners on the left-hand side of the cabinet and is secured by the back panel and a single screw. The user controls are all mounted on the main panel, protruding through cutouts in the front of the cabinet. These arrangements were first used in the 1790 monochrome portable chassis (see *Television*, February 1983). Mounting the controls in this way eliminates the need for separate and costly control panel wiring and assembly work.

The 14in. tube is also a key element in the design. The tube/yoke assembly is of the pincushion distortion free type, eliminating the need of EW correction. The tube neck is of the "mini" type, i.e. the diameter is 22.5mm. This enables a smaller yoke to be used, in turn reducing the scanning energy requirement by 20 per cent – in comparison with the TX9's 90° narrow-neck (29mm) tube. There's a further advantage since the reduced glass weight simplifies the cabinet design.
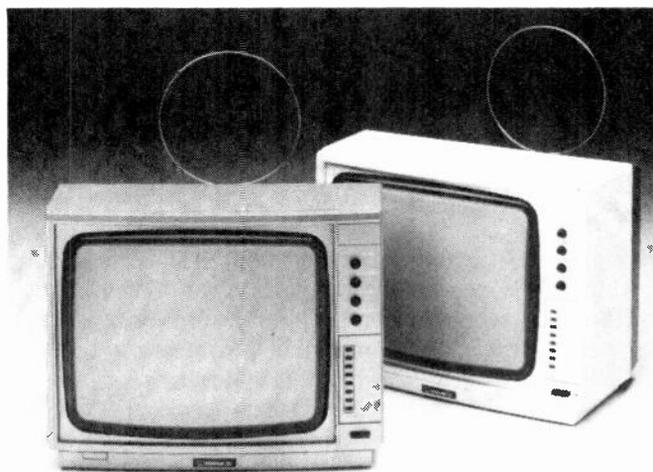
## The Electronics

So much for the production and mechanical aspects. We'll turn now to the electrical design. Fig. 1 shows a block diagram of the electronics. Perhaps the most surprising feature at first sight is the use of a simple mains trans-



The first sets fitted with the new TX90 chassis – the Ferguson Model 37140, in silver or white.

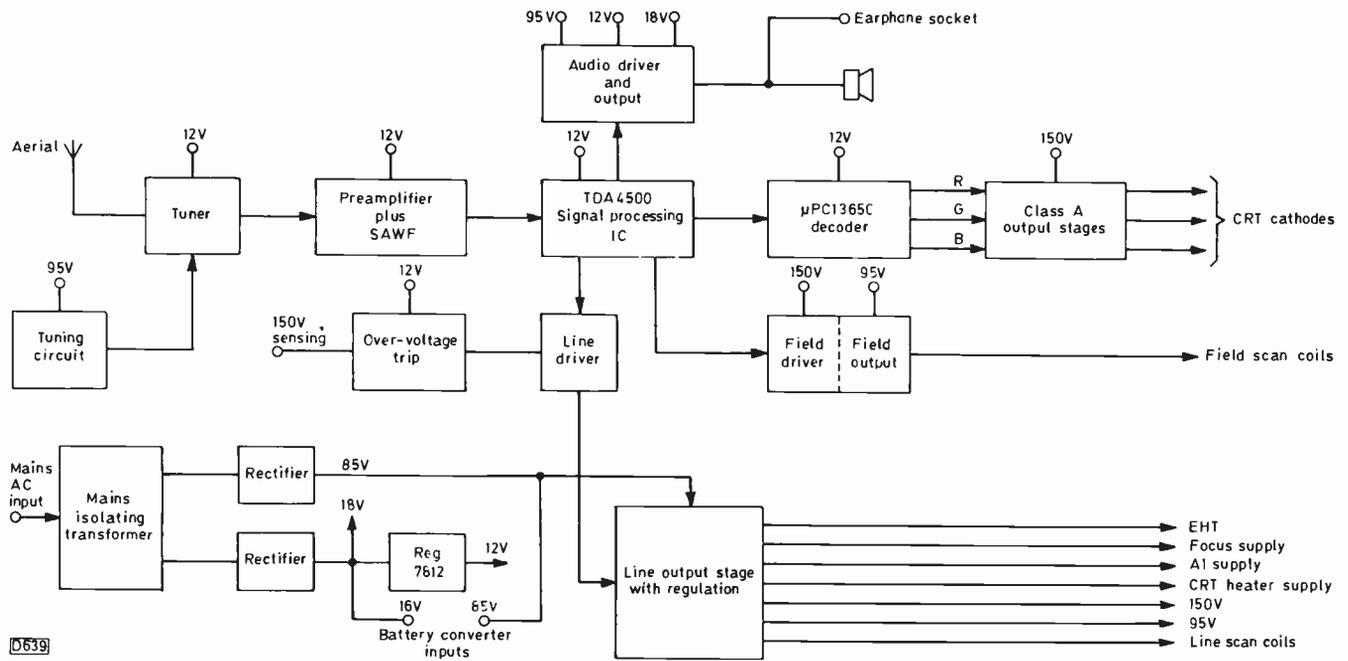


Fig. 1: Block diagram of the TX90 chassis. The power consumption is less than 40W at black level – this compares with 45W for the TX9 chassis.

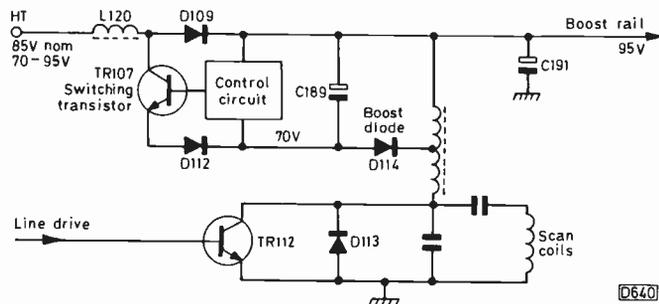


Fig. 2: Principle of the switch-mode boost supply circuit.

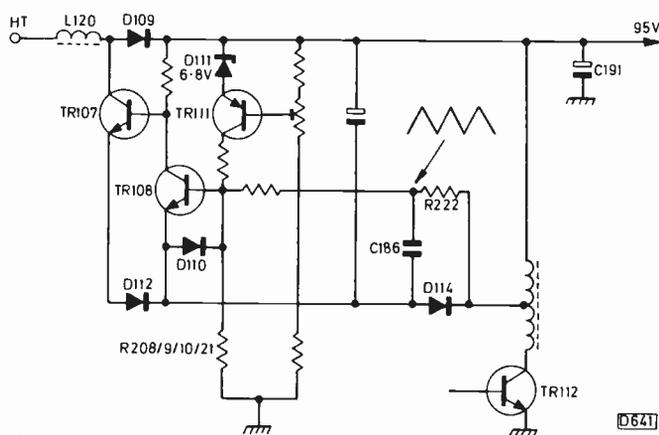


Fig. 3: The switching transistor's control circuit.

former which provides isolation and feeds two rectifier circuits. These provide outputs at 85V and 18V. The latter feeds a 12V regulator that supplies the low-voltage stages in the receiver. This arrangement provokes the question "what no chopper?" The h.t. regulation required is in fact built into the line output stage, which employs what could be described as a switch-mode boost supply (95V) circuit. The use of this novel arrangement instead of a conventional chopper system is part of the process of getting everything on to a small (280 × 172.5mm) main panel. One disadvantage of a chopper circuit is radiation prob-

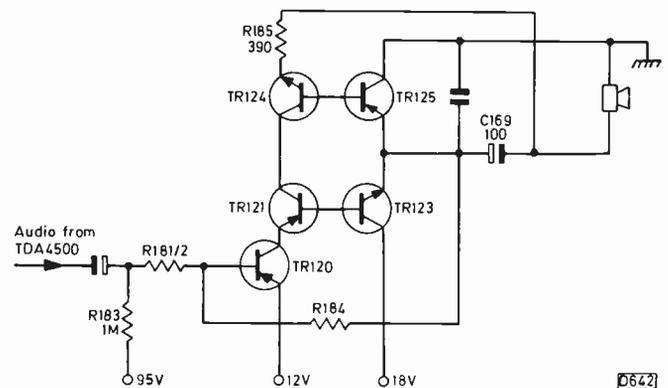


Fig. 4: The audio circuit.

lems, which necessitate elaborate mains filtering plus anti-radiation measures within the chopper power supply. Such problems are neatly avoided by the arrangement adopted. The mains transformer is mounted separately at the right-hand side of the set.

With the exception of the TDA4500 i.c., most of the rest of the circuitry is reasonably conventional. Simple class A RGB output stages are used, with presets to control the black level only. There's provision on the c.r.t. base panel to include high-light controls if required, but the tolerances of the tubes at present being used make this unnecessary. A standard class B field output stage is used, fed from the 95V rail. This is less efficient than the use of a flyback boost system but has the advantage of reduced circuit complexity. For similar reasons the field driver is fed from the 150V rail, obviating the need for a bootstrap network. The lower output transistor and the driver transistor comprise a Darlington pair with a shared encapsulation. The sound output stage incorporates a novel feature to remove crossover distortion and regulate the quiescent current, enabling the output transistors to operate without heatsinks under a wide range of environmental conditions.

The 28-pin TDA4500 was jointly developed by Thorn and Philips for the TX90 chassis, though it will be used in

other chassis at a later date. Basically it accepts the i.f. input from the SAWF and provides a composite video output at pin 16, a post volume control audio signal at pin 12, a field drive output at pin 2 and a line drive output at pin 27. Field feedback is applied to pin 3 and line feedback, for the flywheel sync circuit, to pin 5. Only two adjustable coils are required in the i.f./intercarrier sound department: one is for the sound detector circuit while the other acts jointly for both the video detector and a.f.c. detector (in conjunction with an internal 90° phase shifter). This chip represents a major step in TV circuit integration. There's even sound muting between channels, a feature that was added to meet recent W. German statutory requirements.


### Circuit Features

Fig. 2 shows the basic principle of the switch-mode boost circuit, which is designed to hold the 95V boost rail constant against h.t. variations over the range 70-95V. Let's initially ignore the switching transistor TR107 and its control circuit. D114 is the boost diode which conducts (along with the efficiency diode D113) during the first part of the line scan, when the line output transistor TR112 is off. As a result, the reservoir capacitor C191 is charged to obtain the boost voltage. For the boost rail to be stabilised at 95V, the voltage at the anode of D114 must be held steady at 70V. This is the function of the switch-mode circuit - TR107 and its associated components. To take the extreme conditions, if the voltage at the collector of TR107 rises to 95V, D109 conducts, TR107 is cut off and the boost circuit is shorted out; if the voltage at the collector of TR107 falls to 70V, TR107 remains on, supplying 70V to the anode of D114. At any voltage between 70-95V, TR107 is switched on and off at line rate to hold the voltage at the anode of D114 at 70V, i.e. the control circuit supplies a variable mark-space ratio drive to the base of TR107 so that its on/off times produce 70V at the anode of D114.

The circuit is efficient in operation since when TR107 conducts the excess voltage (h.t. - 70V) appears across the 5μH choke L120. The energy stored in L120 is proportional to this excess voltage and the conduction time of TR107. When TR107 switches off, the voltage at the anode of D109 swings positively: D109 then conducts, charging C191.

The switching transistor's drive circuit is shown in Fig. 3. The error transistor TR111 sets the d.c. conditions at the base of the driver transistor TR108. TR111's emitter voltage is held constant by the 6.8V zener diode D111 while its base senses the boost voltage. The driver transistor TR108 acts as a pulse-width modulator. The line flyback pulses appearing at the cathode of D114 are integrated by R222 and C186 to produce a sawtooth at the base of TR108. The point during the sawtooth when TR108 switches on (and TR107 switches off) is determined by the conduction of TR111 which is in turn determined by the boost voltage. In this way a variable mark-space ratio line-frequency drive waveform is produced to switch TR107 on and off and thus stabilise the voltages in the circuit.

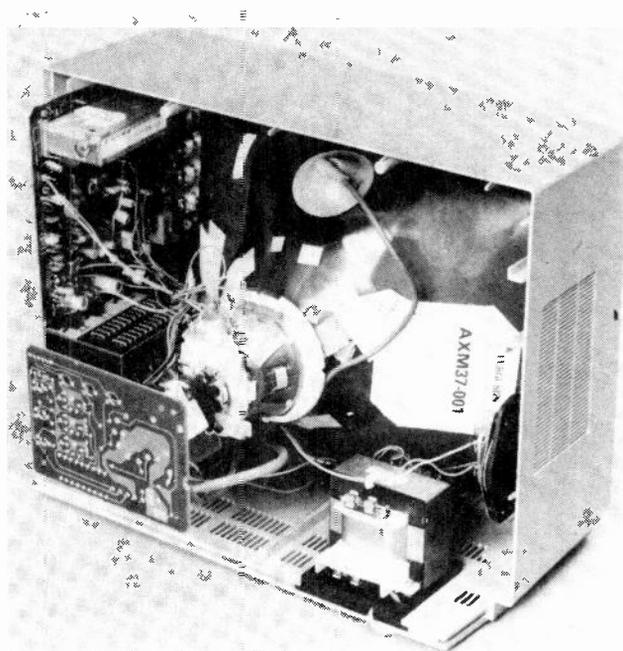The over-voltage trip consists of a pair of transistors in a regenerative switch configuration. In the event of excessive voltage on the 150V line the transistors switch on to remove the line drive. The result is loss of sound and raster - the trip resets automatically when the over-voltage condition clears. In addition, the 12V regulator incor-



Inside the Ferguson Model 37140.

porates overload, thermal and short-circuit protection - the result will again be loss of sound and raster as the TDA4500 will close down.

The audio circuit is shown in Fig. 4. The driver is TR120, whose load resistor R185 is connected in the conventional bootstrap fashion, with C169 acting as the output coupling and bootstrap capacitor. The gain of this stage is set at 12 by the ratio of the feedback resistor R184 to the input resistors R181/2. Bias is supplied from the 95V line via R183 and this, in conjunction with the feedback resistor R184, sets the midpoint voltage of the output stage.

The novel bit consists of transistors TR121 and TR124 which replace the conventional bias stabilising diode. When a transistor is operated with a low collector-emitter voltage, its gain is proportional to that voltage. The voltage across TR121 and TR124 cannot exceed 2.4V (the 0.6V base-emitter voltages of the stabilising and output transistors combined). Stabilisation is achieved since a rise in the voltage across one transistor will result in a compensating decrease in the voltage across the other one. When an audio drive signal is applied, the gains of the two stabilising transistors will change continuously over each cycle, thus maintaining the correct bias conditions in the output stage.

So much for the technical highlights of the chassis. The production time per set brings out the efficiency of the manufacturing process. The total time taken to produce, test and pack a TX90 set is only 1.4 hours. This compares with 3.5 hours in the case of a TX9 receiver and the six hours it took to produce a 9000 series set. During initial production of the TX90, 75 per cent of the components are being auto-inserted. This will rise to 90 per cent when further equipment has been installed.

On a more sombre note, in 1976/7 the Gosport plant required a labour force of 3,204 to produce a total of 600,000 colour and monochrome sets (mainly monochrome). In 1982/3 a reduced workforce of 1,945 will produce 900,000 sets, mainly colour. But as an interesting aside, it appears that there's a shortage of TV development engineers. It seems that newly qualified engineers are mainly interested in digital circuitry.

# VCR Clinic

Steve Beeching, T.Eng. (C.E.I.), Mike Sarre,  
Mick Dutton and Michael J. Cousins, T.Eng. (C.E.I.)

## JVC/Ferguson HR3330/3V00

There are several causes, listed below, for the following fault on these machines – when play is selected the tape threads and starts to run, then the keys release and the tape unthreads.

- (1) The AN318 drum servo i.c. not producing the flip-flop signal and/or connector problems, i.e. the flip-flop signal doesn't arrive at the mechacon panel.
- (2) The take-up spool not rotating and/or the tape counter not rotating, thus no take-up spool signal.
- (3) Defective cassette compartment lamp and/or tape end sensors.
- (4) After loading switch not making contact.
- (5) This one is more difficult – C12 (33 $\mu$ F) in the pause delay circuit on the mechacon panel low in value.

Our method of tackling the problem is to short-circuit to chassis the base of X5 on the mechacon panel to inhibit the key release relay and then check the above items. **S.B.**

## Some Quickies

**Hitachi VT9300:** In the event of no E-E or playback, change units CP205 and CP206 (3MHz filter and phase delay equalizer). The fault is usually in the delay block.

**Sharp VC9300:** Poor replay on a machine only four months old was traced to one video head having an open-circuit winding.

**Toshiba V8600:** Inability to set the hours of the clock display – change the timer microcomputer i.c.

**Sony C7 and C5:** A couple of problems. First no E-E audio: change the TBA120U i.c. in the sound i.f. department. This fault is not uncommon. Secondly no rewind: fit new rewind kit. Lots of these machines will need modifying as it's a very common problem.

**National Panasonic NV7200:** No pushbutton functions can be due to the cassette compartment light. There are two infra-red LEDs wired in series. Check the switching pulses across them: if more than 3-4V, i.e. 12V, change one of the LEDs.

For erratic system control on this range of machines check the voltage dropper diode that provides 5V from the 6V line. **S.B.**

## Ferguson 3V23

We've had a few cases where the remote control system operates the mechanical functions but not the tuner/timer, with no channel selection or tape counter. The remote control unit may be faulty, but the fault is more likely to be on the tuner/timer control panel. If there's no display, change the 400kHz ceramic resonators CF1 and CF2. If there is a display, suspect the TA57 (TA1) remote control gating i.c. associated with the tuner control microcomputer ICI. **S.B.**

## Sanyo VTC5000/5300

We've had complaints of the playback being covered in white spots on several of these machines. The actual symptom is intermittent noisy pictures. This is not due to head clogging or tape damage – the solution is to solder a

short piece of wire to the casing of the video head preamplifier, connecting the other end to a solder tag on the adjacent earthed metal clamp, in order to link the preamplifier screen earthing to the main earth run. **S.B.**

## Advance Warning!

(1) An eccentricity gauge will be required to fit video heads on the new long-play JVC/Ferguson machines – Models HR7655 and 3V32 respectively.

(2) Don't take the covers off the VHS-C portable as an oxide wiring loom for the lower drum assembly can be damaged – a new lower drum assembly will then be required. **S.B.**

## Ferguson 3V23

A 3V23 sent in from another branch had a note attached saying "no sound". On inspection it was clear that various boards had been changed, so we proceeded with care. Pre-recorded tapes could be played back with perfect sound, but there was no E-E sound. Selecting channel set and ramping in a station gave the first clue: as the station was approached, it ramped straight through and continued up the band. In the sweep mode the sound is muted until sync pulses are detected and compared with a line-frequency oscillator (IC15) on the tuner/timer control panel. Investigation showed that the sync comparator IC14 was in the no sync mode, due to X15 (between IC15 and the relevant part of IC14) being short-circuit collector-to-emitter.

Unfortunately the no E-E sound fault was still present, though stations could now be ramped in and stored. Swapping boards revealed that the repaired board produced E-E sound in another machine, while the original fault was still present in the first machine.

An accident gave us the next clue – touching the audio head while in the E-E mode produced a hum through the monitor set, indicating that although the video was supposed to be in the E-E mode it was actually in playback all the time. Checks revealed that the playback line from the mechacon panel was high due to X36 having an emitter-collector leak. When replacing this transistor produced only very low E-E sound we had to move over to the i.f. panel where the core of the 6MHz transformer T5 was found to be missing.

I can only assume that these faults originally came from different machines and were all lumped into one by panel swapping, since there cannot be a logical reason for three different faults all giving the same symptom! **M.J.C.**

## JVC/Ferguson HR7200/3V29

There was no clock display (no illumination) on this machine. As a first step the voltage across the display device's filament pins 1/2 and 25 was checked. It was correct at 2-4V r.m.s. We next checked the supply to the microcomputer control i.c. on this panel, IC401. This was again correct at 10V. Time to use the scope to check this i.c.'s clock oscillator at pins 1 and 42 – this is one of the first things to check, as the clock runs everything else here.

The microcomputer's heart you might say. Well, this one had had a heart attack! Replacing the 400kHz ceramic resonator and the microcomputer failed to get things working, but changing the associated capacitor C407 (220pF) brought everything back to normal. **M.S.**

### **Sony C7**

The fault on this machine was intermittent loss of colour on record – the playback and E-E colour were o.k. To speed things up I started by consulting the video block diagram. The point at which the record and playback chroma diverge is pin 4 of IC2, i.e. at the output from the frequency converter (or rather the following buffer stage). There was plenty of output here but no output from the following amplifier Q55/6, i.e. at test point 26. Tracing back from the base of Q55 brought us to the low-pass filter L30, L29 etc. The fault was that L29 was open-circuit. **M.S.**

### **Sanyo VTC9300**

The counter on this machine went forward in the reverse mode . . . The circuitry concerned is on timer panel W20, the count up/down input being at pin 4 of plug/socket S1602 – it goes high in the rewind modes. This input was o.k. The command is passed to the TMS1070 microcomputer i.c. via a 10k $\Omega$  resistor (R1605) and the switching transistor Q1602. A check at the base of this transistor showed that the voltage was increasing, but not sufficiently to switch it off. There's a smoothing capacitor here, C1618 (0.47 $\mu$ F electrolytic), and this turned out to be leaky. **M.S.**

### **Ferguson 3V30**

We've had several 3V30s in with the fault that the machine threads up but won't play. Everything appears normal except that the pinch roller doesn't engage at the end of the threading cycle. The pin linking the mechanism and the play solenoid was in each case found to be hanging out, refitting and sealing providing a cure. **M.S.**

### **Panasonic NV8600**

The complaint with a National Panasonic NV8600 was that the eject key was jammed. There was no tape in the machine, but we noticed that it was not fully retracted from the play mode – the two guide rollers were part way round the head drum assembly. When the key was pressed nothing happened and the cassette lamp didn't light. A check on the 4A fuse showed that it had blown, due to one half of rectifier D105 being short-circuit. Replacing these items provided a cure. **M.D.**

### **Cassette Fault**

This one was a cassette rather than a VCR fault. The customer's complaint was that his machine sometimes wouldn't record in the timer mode. As the VCR was only a couple of weeks old we decided to take another machine along and swap them over in the interests of good customer relations. This we did but despite a long soak test we could find nothing wrong with the first machine. Then, after a couple of days, the customer phoned to say that he had the same problem with the second machine.

This time we tried doing a timed recording in the

customer's house. Sure enough the machine wouldn't go into record. Removing the tape and replacing it in the machine allowed record to be selected however. A close examination of the cassette then showed that the anti-record tab was weak. What had been happening was that the tab was giving under the push of the sensor arm after the cassette had been in the machine for a while. So the machine thought the anti-record tab was missing. If the tape was pushed into the machine and record was selected straight away the tab was strong enough to hold the sensor out. **M.D.**

### **Toshiba V5250B**

The problem with a Toshiba 5250B was that the motor wouldn't rotate: a quick check revealed that its supply was missing. Tracing back, we found that the stop solenoid switch 59503 was not making proper contact. Replacing this item restored normal operation. **M.D.**

### **Sharp VC9300**

A Sharp 9300 wouldn't wind the tape back into the cassette before ejecting it. We removed the lid and cassette holder and, after finding the appropriate microswitches, put the machine into play. This was o.k. so we pressed stop. The cassette arms retracted correctly, but no drive was supplied to the supply wheel to rewind the tape. This drive is obtained from the motor via a wheel which flips between the take-up and supply spools depending on the mode selected. The problem was that the wheel was slightly tight on its shaft, as a result of which it stuck and would not move over to provide the rewind during tape unthreading. **M.D.**

### **Toshiba V5470B**

The customer's complaint with a Toshiba 5470B was that the machine would intermittently stop playing and go into the stop mode. The problem when the machine reached us was that it was impossible to select play (or any other function) because the stop solenoid operated immediately. We removed the top cover and loaded the machine, without a tape, by pressing the two lever-operated switches in the cassette compartment. The loading system worked, but the head didn't rotate. Pressing play made the stop solenoid operate instantly, and there was still no head rotation.

The bottom cover was removed and the video board hinged out to gain access to the drum drive circuit. The head motor on these machines is of the brushless d.c. type, which requires a supply of 12V and a control voltage of approximately 7.5V to operate the electronic switches used instead of brushes. This latter is the servo-controlled voltage. The 12V supply was present but the control voltage was absent.

We followed the circuit back through the amplifier stage and found that there was no output from the servo panel. In fact there was a short from the output of the servo i.c. to chassis. Removing plug P507 removed this short, and we then noticed that the servo i.c.'s output is also taken to one side of the stop solenoid microswitch. A check here revealed that the switch was permanently shorted to chassis. On dismantling the switch we found that a tiny thread of the brass contact was bridging the switch out. Cleaning it with a relay cleaning strip solved the problem, restoring normal operation. **M.D.**

# Long-Distance Television

Roger Bunney

April was rather a quiet month – too quiet for my liking. The good mid-April Sporadic E opening that indicates a good season in prospect was unfortunately missing, though early May produced an excellent SpE opening, so hopefully an active season will follow.

There was little tropospheric reception during April. A lift was noted over the 13-15th, with W. German u.h.f. signals being just received in the midlands, and a further enhancement occurred on the 30th. MS (meteor scatter) provided signals daily, though less so than in earlier months. F2 layer propagation improved around the 24-25th, reaching to 40MHz (just) at mid-day on a southerly path, but by the 27th had fallen to a struggling 35MHz.

The depleted SpE log is as follows:

- 8/4/83 SR (Sweden) ch. E2.
- 13/4/83 NOS (Holland) and NRK (Norway) ch. E4. Note the short skip distance – NOS was received in Anglesey.
- 21/4/83 TVP (Poland) ch. R1.
- 1/5/83 RTVE (Spain) chs. E2, 3, 4, mid-morning.
- 2/5/83 A good late morning/early afternoon SpE opening. TVP R1, 2, 3; TSS (USSR) R1, 2, 3; ORF (Austria) E2a; CST (Czechoslovakia) R1; DFF (E. Germany) E4 – a really strong signal here at 1345; BR (W. German Bayerischer Rundfunk network) E2; RTVE E2.
- 3/5/83 RTVE E2.
- 6/5/83 SR E2, 4, early morning.

Thanks to Iain Menzies (Aberdeen), Cyril Willis (Ely), Arthur Milliken (Wigan), Hugh Cocks (Sussex), Mel James (Anglesey) and Ryn Muntjewerff (Holland) for sending in reception reports.

Jim Maden (S. Africa) wrote to report an excellent TE (trans-equatorial evening skip) opening that occurred on March 20th, giving him RAI (Italy) ch. 1A and RTVE ch. E2. Unfortunately a lightning strike ended his reception, and two replacement ET021 tuners are now on their way to S. Africa. Jim also reports that the Stat-T 714MHz satellite at 99°E is now using the later USSR electronic pattern with identification "UT = TSA TAY". The satellite is received at 0° elevation in S. Africa, with reasonable quality.

For QSL hunters YLE (Finland) have issued a picture postcard to confirm TV-DX reception. Write to Oy. Yleisradio Ab., Kesakatu 2, 00260 Helsinki 26, Finland with details (and preferably a photo) of your reception. Just for the record, the Tampere ch. E2 outlet has closed and we are left with Tervola ch. E3 20kW e.r.p., Ruka ch. E4 2kW e.r.p. and Vuokatti ch. E4 4kW e.r.p. These stations are all in the TV1 network.

## News Items

**UK:** In case you missed the note in Teletopics last month, the 405-line network (system A) is to close on December 31st, 1984. The 97.6-102.1MHz Band II spectrum at present used by various emergency services is to be

cleared gradually at about 1MHz a year, starting in 1985 and continuing to December 31st, 1989, to accommodate two additional national radio networks. The allocation 102.1-104.6MHz will eventually be given to local radio, extending to 105MHz, while the remaining spectrum to 108MHz will be used for BBC radio network extension.

**Holland:** A new law instructs all cable firms to switch off equipment dedicated to specific channels at close down. The purpose is to prevent pirate TV stations "squatting" on particular channels, reaching the cable subscribers through a network's head-end electronics.

**Italy:** A new video signal transmission technique is being tested by RAI on the Milan-Rome link. To avoid system congestion at times, time-compression is used to enable two video signals to be carried in a common channel. The signals are first separated into their luminance and colour-difference components and then arranged in a time-division multiplex as shown in Fig. 1. Note that the sync pulses are stripped out, a narrow (0.8µsec) line-frequency pulse being added. Signal compression and expansion are carried out digitally.

Coincidentally Bell Labs in the USA have been experimenting with a complex arrangement to enable two TV signals to be carried simultaneously in a single channel. Engineers think that a third signal could be carried in this way, though with some degradation of overall video quality. The intention is to use the system for satellite relay use. In the Bell system, only the differential information for every other field is transmitted; in an upper band by means of double-sideband suppressed-carrier modulation. Elaborate video signal processing is required, with field stores.

**South Africa:** The TV2 and TV3 networks commenced in January. The PM5544 test pattern is used for all three networks. In the case of the English/Afrikaans service from Johannesburg the identification "TV1" is carried at the top, with a centre right digital clock and "SABC/SAUK JHB" at the bottom. The Zulu/Xhosa service has "TV2" at the top and the other identifications as TV1. The Iswana/Sotha service is the same but with "TV3" at the top. A South West African service started last year: the PM5544 pattern carries "Windhoek" at the top and a digital clock at centre right – the lower panel is blank.

## Receiving Equipment

A new tunable head amplifier from Schrader, type RB45, has a gain of 26dB and a noise figure of 1.6dB. A Dutch enthusiast comments that the results are very good. It covers down to the 430MHz amateur band.

Some enthusiasts who built the varicap tuning system featured in the March 1982 issue (page 236), with ET021 tuner unit, have experienced instability at approximately 50MHz. This can be removed by adding a 10 or 22µF 63V electrolytic at the output pin of the 7824 voltage stabiliser IC1.

Issue no. 122 of the BATC magazine *CQ-TV* contains an

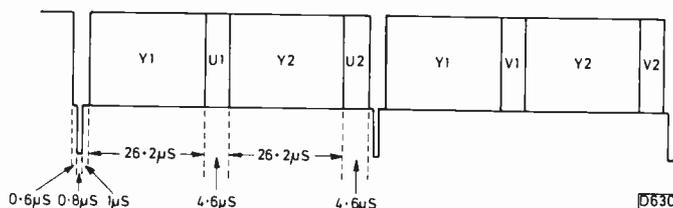


Fig. 1: Two channels in one: time-compressed signal system in experimental use by RAI (Italy).

article, with PCB, on an f.m. TV receiver. It's an ideal system for use as a satellite receiver, and includes sound tap-off facilities. Membership now costs £4 annually – an application form (include SAE) can be obtained from E. Summers, 13 Church Street, Gainsborough, Lincs. BATC interest in 1.3GHz transmission and f.m. video is increasing, and further information is expected in future issues of the magazine – so now may be the time to join! The f.m. TV receiver circuit mentioned above has been used successfully for reception of the Gorizont 3.675GHz signals.

### Amplifiers and Feeders

A problem has become evident with the widely used Labgear CM7060/65/66 etc. series of amplifiers in round, plastic boxes for masthead mounting. If thick low-loss cable is used (as it should be), air flow within the box becomes restricted or the box may be air tight. Cable entry is via two holes in the bottom, through tightly fitting grommets. As a result, condensation can occur with a build up of water droplets inside the case. The solution is to drill a quarter inch hole in the recess between the two cable entry grommets.

The quality of the coaxial cable supplied for TV use has declined in recent years. The braid density has been reduced, and the PVC covering can be affected by exposure to sunlight. During manufacture, the PVC outer cover of domestic type coaxial cable has a plasticizer added to make it more flexible. After installation however a phenomenon called "plasticizer migration" occurs – the added chemical starts to leak through the braid to the polythene dielectric. After a few years the characteristics of the dielectric are altered and the result is increasing signal attenuation. The problem can be minimised by avoiding the use of cellular foam dielectric coaxial cable (air-spaced polythene cables, with four or five air cores, are less affected by this problem) and by routing the cable down the north side of the mast to reduce exposure to direct sunlight.

### From our Correspondents . . .


Interference is becoming an increasing problem and Cyril Willis reports both success and gloom. A 49MHz cordless phone was established recently at Ely, causing severe ch. R1 interference. The operator was recognised but denied using 49MHz. A call from Cyril was monitored "on-air", using a Patrolman 50 Tandy/Taiwan receiver. Cyril then asked the operator to cease using 49MHz and advised British Telecom – eventually contact was made with the "Illicit Attachment Dept."! Communication followed between BT and the operator, who has apparently decided to "go legal" at 47MHz. BT can cut off the phone and press for a fine for the use of non-approved equipment – the new Telecommunications Bill will make the use of 49MHz equipment an offence.

Both Cyril and Iain Menzies report problems as a result of 50MHz amateur radio operation. I've not personally experienced this, though such transmissions will increase dramatically from the end of 1984.

Gosta van der Linden has sent details of the channels available to him in Rotterdam on cable TV – some fifteen in all, including Dutch, UK, French, Belgian and W. German services. The French system L and UK system I signals are converted to system G. The cable service also supplies 23 radio channels from W. European sources – even the American Forces network.
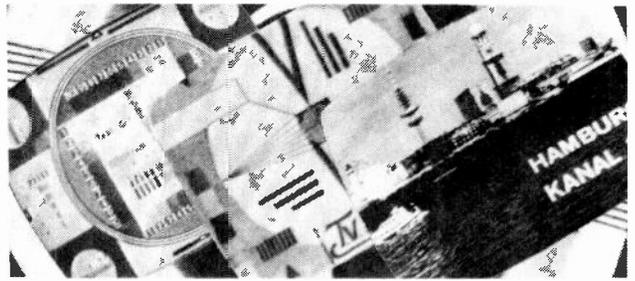
# SOUTH WEST AERIAL SYSTEMS

10 Old Boundary Road, Shaftesbury,  
Dorset. SP7 8ND tel. 0747 4370



As the leading UK aerial mail order company, we carry a comprehensive range of equipment for domestic, fringe, DXing and distribution systems. Satellite equipment (TVRO) is also available.

We supply aerials/equipment for all bands, from large aerials to small filters – and all the bits in between. Aerials for the new 50MHz amateur band are just available.

We are active DXers – your guarantee of honest and accurate advice – efficient equipment at competitive prices.

We've listed just some of our weak signal/DXing UHF aerials below – prices include VAT, packing and Securicor carriage.

<b>Fuba.</b> Gold anodised multi-element high gain (17 dBd), the legendary XC391 (available Groups A,E,W) £59.50	<b>Triax.</b> Unix 44 Gold anodised multi-element (14dBd gain), (Grps. A,K,E,W) £31.65
<b>Jaybeam.</b> JBX8 multi-element (14.5dBd) £24.35	<b>Unix 92.</b> Golden anodised perfection, high gain (17dBd) (Grps. A,K,E,W) £49.20
<b>JBX21</b> High gain multi-element (18.5dBd) (available Grp. A,B,C/D) £47.65	<b>BB Grid.</b> Wideband 4 bay bowtie £21.80
<b>Waisey.</b> Budget high gain (18dBd) multi-element HG36 (Grps. A,B,C/D) £32.75	<b>Twin Grid kit.</b> 15.3dBd gain £54.25
<b>Colour King.</b> Wideband 4 bay bowtie (12.5dBd) £24.35	<b>Quad Grid kit.</b> THE ULTIMATE weak signal system 18.1dBd gain £79.15
	<b>NB.</b> Grid kits include low loss combining filter, clamps, cross support masts.

(allow 10–14 working days for delivery of stock items)

Antiference XGs also available – send 54p for our extensive 1983 catalogue detailing aerials, amplifiers, filters etc. etc. Include SAE for satellite leaflet or for our new 'Wideband UHF Aerials' leaflet – essential reading for fringe UHF enthusiasts. **Access/Barclaycard welcome.**

## TV LINE OUTPUT TRANSFORMERS

If the Transformer you require is not listed please phone.

<b>RANK BUSH MURPHY</b> T20a T22 Pry & Sec 5.51 Z718 Series primary 5.00 Z718 Series EHT overwind 5.00 A774 single std mono 8.50 A816 solid state mono 9.00 Z712 T16a T16b mono portable 9.00 A823 A823b A823av colour 10.00 Z719 Z722 series colour 10.00 Z718 18" series 11.00 Z718 20" 22" 26" series 11.00 T20a T22 series colour 10.00	<b>DECCA</b> MS1700 2001 2020 2401 mono 8.00 MS2404 2420 2424 mono 8.00 1210 1211 1511 portable 11.50 GYPSY portable 11.50 CS1730 1733 colour 8.00 CS1830 1835 colour 8.00 '30' series BRADFORD colour 8.00 80 series colour 8.00 100 series colour 8.00
<b>G.E.C.</b> 2047 to 2105 3112 to 3135 8.00 "GAIETY" FINELINE 8.00 2114 portable mono 8.00 3133 3135 M1501H portable mono 8.00 DUAL STD hybrid colour 11.00 SINGLE STD hybrid colour 10.00 SINGLE STD solid state 90° or 110° 8.50	<b>PHILIPS</b> 210 300 series mono 8.00 320 series solid state mono 8.50 G8 series colour 8.00 G9 series colour 8.50 G11 series colour 14.98
<b>FERGUSON HMV MARCONI</b> 1590 1591 1592 1593 mono 8.00 1612 1613 1712 mono 8.00 1690 1691 mono 8.50 1600 1615 series mono 9.74 3000 3500 EHT or SCAN 8.58	<b>KB-ITT</b> VC200 VC205 VC207 mono 8.00 VC300 VC301 VC302 portable 8.00 CVC1 CVC2 colour 9.00 CVC5 CVC7 CVC8 CVC9 colour 9.00 CVC20 series colour 9.00 CVC30 CVC32 series colour 8.00 CVC40 series 14.56
ADD 15% VAT to ALL prices.	
<b>Tidman Mail Order Ltd.,</b> 236 Sandycombe Road, Richmond, Surrey. Approx. 1 mile from Kew Bridge. Phone: 01-948 3702 Mon-Fri 9 am to 12.30 pm. 1.30 to 4.30 pm. Sat 10 am to 12 pm.	<b>L.O.P.T. TESTER</b> Total Price 16.79
<b>Hamond Components</b> (Midland) Ltd., 416 Moseley Road, Birmingham B12 9AX. Phone: 021-440 6144. Mon-Fri 9 am to 1 pm. 2 pm to 5.30 pm.	

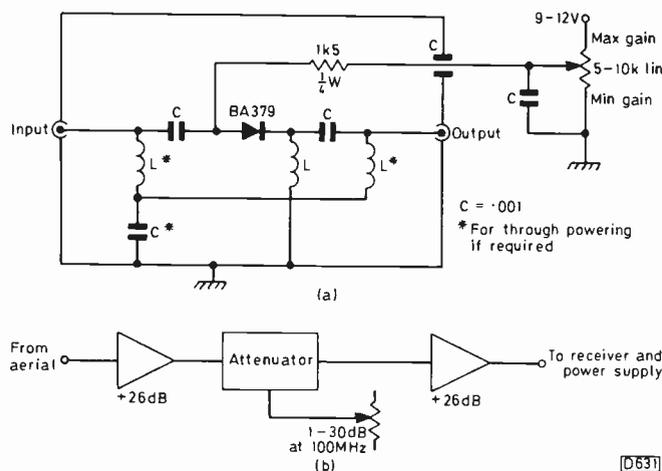


Fig. 2: (a) Simple in-line pin diode variable attenuator, with through powering if required. The chokes have 8 turns close spaced 26g at u.h.f., 14 turns at v.h.f. (b) The arrangement used by Seppo Pirhonen.

Neil Carnegie (Glasgow) has been on holiday in Ireland recently and reports on the "free" TV situation there. The only pirate station is at Trapmore, rebroadcasting UK services. "Nova TV" has equipment but is not yet in operation. Boynesside TV is now off-air due to transmitter failure. Dublin TV has ceased operation.

Seppo Pirhonen (Helsinki) has sent in some remarkable photos of his reception - using stacked Hirschmann aerials. One shot is of ZDF reception on ch. E21. Seppo has also received NDR (W. German) signals at u.h.f. The Russian Tallinn u.h.f. station presents a problem locally and Seppo is trying out a variable-gain system, with the gain at maximum when TSS is off-air. The simple circuit being tried is shown in Fig. 2 - it's fitted between the CM7066 head amplifier and the CM7080 cascade amplifier. Maximum attenuation should be around 30dB, falling to an insertion loss of 1dB.

Petri Pöppönen (Lahti, Finland) has sent in some shots of the UK Satellite TV Ltd. programmes which are now present for some two-three hours a night via the OTS-2 satellite at 11.6GHz. The programmes are available on cable networks at Helsinki, Turku and Rovaniemi, and are shortly to become available at Vaasa and Lahti. Signals from the Gorizont craft at 4GHz are being received successfully on dishes of diameter down to 1.2m.

Finally a note on the installation here at Romsey. All the aerials on the main lattice mast, together with the now hardened cable, have been removed in readiness for a complete change of aerials. It's typical that as soon as derigging was completed on May 2nd, with only temporary aerials available, wide open SpE conditions occurred.

### Band III European Channel Allocations

Last month we discussed reception of European signals in Bands I/II. Table 1 this month lists the Band III European channel allocations.

Long-distance reception in Band III relies mainly on the weather-related phenomenon known as tropospheric propagation - stable, slow-moving high-pressure systems give improved reception of distant v.h.f. and u.h.f. signals. The best times for reception are from dawn through to perhaps 1000-1100 - at sunrise and soon after, the heating effect of the sun often produces a characteristic temperature inversion, with the upper air warmer than the Earth's surface - the reverse happens at dusk. During such

inversion conditions tropospheric ducting can often carry Band III/u.h.f. signals over many hundreds of miles (this phenomenon is common in the Gulf area, where co-channel interference is a problem). Another weather condition helpful to tropospheric propagation is fog with high-pressure, particularly in the autumn. Also watch out for an approaching cold or warm front, which if approaching rapidly can give short-lived signal enhancement along the line of the front.

At times SpE reflection can occur in Band III, particularly when Band II is very active. MS reception also occurs in Band III, though a high-gain receiver with stable timebases and accurate channel frequency setting is essential. Patience is required for Band III MS reception, though it will appear given the right conditions and equipment - at distances akin to SpE.

Tropospheric signals are generally slow-fading and stable, unlike SpE with its characteristics of rapidly fluctuating signal levels and unstable polarisation.

Table 1: Band III Channel Allocations

Channel	Vision (MHz)	Sound (MHz)	System
B6	179.75	176.25	A
B7	184.75	181.25	A
B8	189.75	186.25	A
B9	194.75	191.25	A
B10	199.75	196.25	A
B11	204.75	201.25	A
B12	209.75	206.25	A
B13	214.75	211.25	A
E5	175.25	180.75	B
E6	182.25	187.75	B
E7	189.25	194.75	B
E8	196.25	201.75	B
E9	203.25	208.75	B
E10	210.25	215.75	B
E11	217.25	222.75	B
E12	224.25	229.75	B
ID	175.25	180.75	B
IE	183.75	189.25	B
IF	192.25	197.75	B
IG	201.25	206.75	B
IH	210.25	215.75	B
IH1	217.25	222.75	B
R6	175.25	181.75	D
R7	183.25	189.75	D
R8	191.25	197.75	D
R9	199.25	205.75	D
R10	207.25	213.75	D
R11	215.25	221.75	D
R12	223.25	229.75	D
F5	164	175.15	E
F6	173.40	162.25	E
F7	177.15	188.30	E
F8	186.65	175.40	E
F8A	185.25	174.1	E
F9	190.3	201.45	E
F10	199.7	188.55	E
F11	203.45	214.6	E
F12	212.85	201.7	E
ID	175.25	181.25	I
IE	183.25	189.25	I
IF	191.25	197.25	I
IG	199.25	205.25	I
IH	207.25	213.25	I
IJ	215.25	221.25	I
1*	176	182.5	L
2*	184	190.5	L
3*	192	198.5	L
4*	200	206.5	L
5*	208	214.5	L
6*	216	222.5	L

\*New French channels

System A UK, System B W. Europe, System D E. Europe, System E old French, System I Ireland, System L new French.

# Less Common TV Faults

S. Simon

Common faults in a wide range of popular CTV chassis were discussed in the Routine TV Receiver Tests series of articles. The aim was to assist those perhaps not too familiar with particular chassis. Nearly all these chassis have tricks which can cause most of us headaches from time to time however.

## Thorn 9600 Chassis

For example, we mentioned last month that W810 in the EW diode modulator circuit in the Thorn 9600 chassis has a habit of decomposing and that it should be replaced with a more robust component. The effect when W810 decomposes is to cause the sides of the raster to bow inwards. The other diode in the circuit, W818, is also a BY298. Although it doesn't decompose, it does have the habit of occasionally going short-circuit. The effect of this is more drastic: it causes complete shut down of the chopper circuit, i.e. there's plenty of voltage at the collector of the chopper transistor VT512 but the driver transistor VT511 is rendered inoperative, with a low collector voltage.

If the h.t. supply plug to the centre, horizontal timebase panel is removed (right side as viewed from the rear, i.e. PL801 in Fig. 3 last month), the chopper circuit may burst into life when the set is switched on again. This proves that the fault is on the centre panel, and although it could be due to several things the fact that the three fuses on the supply panel are intact suggests that the trouble is in the line output stage. It is prudent therefore to check this diode for being short-circuit at an early stage in the proceedings in order to save time. A BY298 can be used in this position as it doesn't lead such a strenuous life as W810. It's located more towards the centre of the board.

## Rank T20 and T22 Chassis

The EW modulator diodes 5D6/7 in the Rank T20 and T22 chassis often give trouble. Though it's common to check the diodes in situ, this can be misleading. If 5D6 is leaky, the effect will be irregular edges with the width and pincushion correction controls not having the required effect. The rule should be to remove the diodes for a more accurate check on the reverse reading. The SKE4G type is more suspect than the BYX71.

## GEC C2110 Series

One point we didn't mention when discussing the GEC C2110 series was the habit of the right side field timebase panel developing a poor contact at the earthing pin of the plug and socket. This gives rise to intermittent field roll which is easily mistaken for lack of sync. Locate the earth socket connection and solder a lead direct from this to the main frame (joining up with the other earthing lead).

## Thorn 3000/3500 Chassis

When the chopper in the Thorn 3000/3500 series chassis fails to start and you've checked all the usual things, spare a thought for R620 in the monostable circuit.

If the colours are bright it's probably o.k. If they are not bright, take it out and measure it – you'll probably find that it's fallen in value to something like 500Ω. The correct value is 2.7kΩ. This is not terribly critical, but something like a few hundred ohms certainly won't do. It's under the rear of the power supply panel, towards the mains transformer.

## GEC 20AX CTVs

Still on the subject of switch-mode power supplies, it would appear that many service engineers are still not aware of what causes the BU126 in the GEC 20AX series receivers to go short-circuit. It's been mentioned on various occasions, but in case you didn't notice them the point is to check the value of R515 before replacing the BU126 chopper transistor if you find that this is short-circuit. R515 should be 150kΩ (1W). It tends to go high in value, thus keeping the BU126 turned on for too long. The value of 150kΩ is not too critical (up to 220kΩ will do), but the wattage rating is important. Preferably fit a 2W component for lasting reliability.

## Pye 697 Chassis

There are still plenty of Pye hybrid colour sets around. In the event of intermittent loss of picture signals, remember that the front controls are connected directly to the printed panel. A dry-joint on any one control (mainly the contrast control it seems) can cause a lot of head scratching – particularly if the fault appears for only a brief period every few hours.

Also remember that the audio output i.c. (those sets using an i.c. instead of a module) has its own power supply rectifier at the bottom right side. This can go open-circuit, thus shutting off the sound completely without affecting the other l.t. circuits.

## Thorn TX10 Chassis

Now to a more recent chassis, the Thorn TX10. Repeated failure of the BU208A line output transistor TR831 can well be due to intermittent leakage through the scan coupling/correction capacitor C831 (0.33μF). The misleading thing about this is that C831 may appear to be 100 per cent when tested. An increase in the voltage rating to 1kV would appear to be prudent. The main cause of chopper transistor failure was mentioned in the May letters column – a defective focus unit.

## Interpreting Voltage Readings

These few snippets may have given the impression that normal servicing routines no longer hold good. This is far from true. In ninety cases out of a hundred, careful and painstaking voltage checks, carried out with the circuit in mind, will quickly reveal the source of the trouble. The circuit is the important point in that last sentence.

For example, if the cathode voltages are absent or very low when a tube base check is made on say a Thorn 3500 chassis, you don't immediately chase the voltage supply. You carry on to check the other tube base

voltages, and shouldn't be surprised to find that the first anode supply voltages are also absent. This may well indicate that the basic cause of the trouble lies in the line output stage – because failure of the line output stage will remove the clamp pulses to the video stages, leaving these turned on hard all the time – hence the low cathode voltages.

If you encounter this fault and the h.t. fuse on the power supply panel is intact, remove the beam limiter panel (top right) and check the 60V supply from the left side entry to the line timebase through coil L502. If you're lucky, you could well find that the cause of the trouble is a soldered connection to this coil, i.e. a lovely dry-joint which has probably been sparking for some time, with the

parallel 18Ω resistor R528 burnt out of course. If you're unlucky, the fault could lie deeper in the line output stage.

Whilst a few volts more or less are of little consequence when dealing with an h.t. line of say 200V, such latitude cannot be allowed in low-voltage circuits. If the service manual says that the voltage on the a.g.c. line should be say 8V, a reading of 6V is a serious error and will make the difference between a clear picture and a very grainy one. If one failed to heed the voltage discrepancy, a fault in the aerial input or the tuner unit could be suspected, rather than trouble in say the first i.f. stage.

Small voltage changes can make a big difference when it comes to transistors and i.c.s – 0.1V is indeed a difference of potential!

## AD Conversion for VCR Control

Richard Roscoe

The biggest problem facing the designer of a VCR's control circuitry is interfacing – that is, how to get all the necessary signals to and from the rest of the machine into and out of the microcomputer control chip. Modern large-scale integration technology makes it possible to put the whole control system for even the most sophisticated machines into a single chip. The trouble is that this chip would require 80 to 100 pins. So various arrangements are used to make each available pin (about 40) do as many jobs as possible.

As an example, consider one major source of input signals, the customer controls – that ever increasing array of yummy buttons just waiting to be pressed. Many earlier VCRs used a scanning system in which all the buttons are connected to an arrangement of rows and columns. This technique was described in an article on microcomputer control in the October 1982 issue. The idea is that pulses are used to scan the row/column matrix to discover which switch has been closed by the user. The drawbacks to this are that quite a few pins are still required (sixteen switches require eight pins), and since the microcomputer has to be connected directly to the switches a simple remote control implementation is difficult to achieve. To overcome these problems, later designs have gone over to a system of AD

(analogue-to-digital) conversion.

With this system each button produces a unique analogue voltage when pressed. This voltage is then equated with a corresponding digital code. How this is done can be demonstrated by considering the circuit used in the Ferguson 3V29/30 machines (see Fig. 1). The arrangement is typical of many. It uses a type of analogue-to-digital conversion known as a ramp or count-up converter. There are other types of AD converter, i.e. successive approximation and parallel types, which are faster and more expensive. The slowness of the ramp type is of little consequence for VCR use however, whilst its simplicity in terms of hardware is an advantage.

The operation of the circuit is as follows. Pins C0, 1, 2 and 3 of the microcomputer IC2 supply parallel four-bit pulse trains via the buffer stages in IC11 to the resistor ladder network in resistor pack RA6. The resistors in this network have values in the ratio 2:1. Fig. 2 shows the parallel pulse trains and the effect produced as these are added – a ramp or staircase with sixteen steps between about 0.1V and 9.5V is produced, with the voltage level of each step very precisely defined. Some machines, such as the Hitachi VT series, use a different ladder network called a weighted resistor network, in which each "rung"

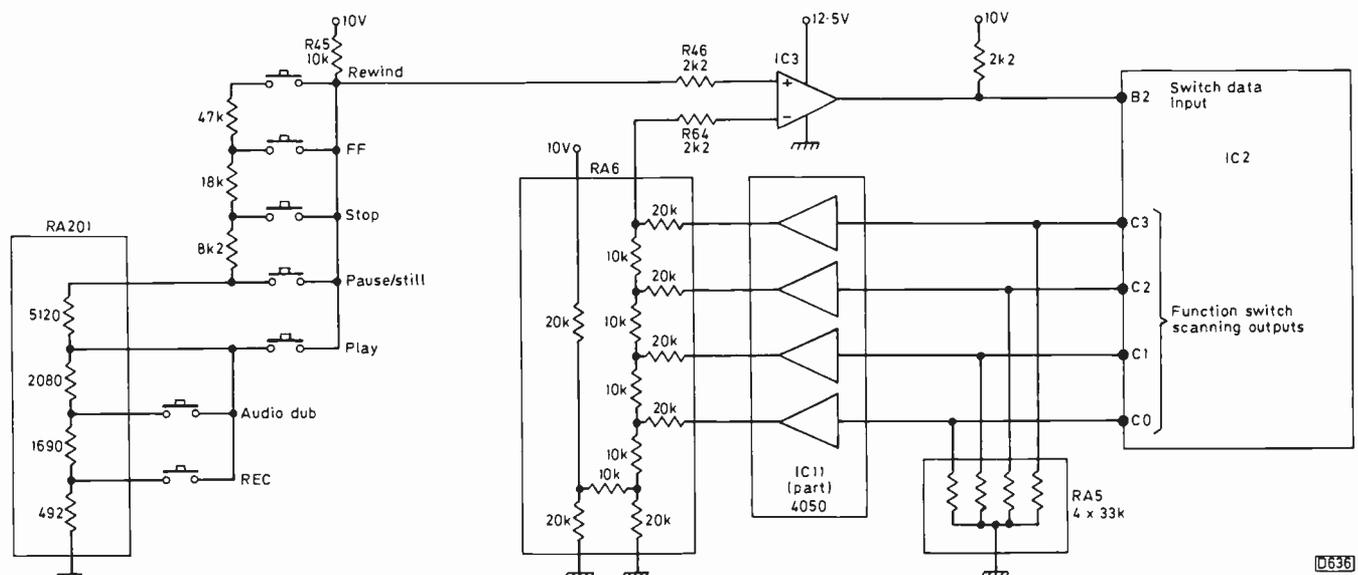


Fig. 1: Ramp type AD conversion circuit used in the Ferguson Models 3V29 and 3V30.

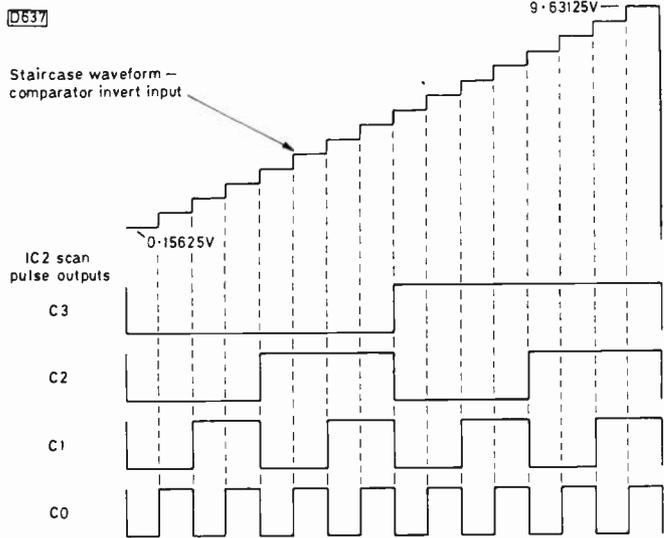


Fig. 2: Scan pulse and staircase waveforms used for AD conversion in the circuit shown in Fig. 1.

of the ladder has twice the value of its neighbour. The result is the same however.

Returning to Fig. 1, the staircase waveform is applied to the inverting input (-) of IC3, which acts as a comparator, i.e. it compares the voltages at its two inputs and sets its output high or low depending on which input is higher than the other. The non-inverting input (+) is initially at 10V, which is applied via R45/6. Note that this voltage is above the level of any of the steps in the staircase applied to the inverting input. Consequently the comparator's output is high, which is read by the microcomputer's B2 input pin as an indication that no operation has been selected.

The function switches are connected between the junction of R45/6 and various points along another resistor chain whose bottom end is connected to chassis. When any switch is closed, R45 and the appropriate portion of the resistor chain in circuit form a potential divider so that the comparator's non-invert input is reduced accordingly. The value of the resistors in this chain are arranged so that each switch or combination of switches when closed produces a voltage that lies between the steps of the staircase waveform.

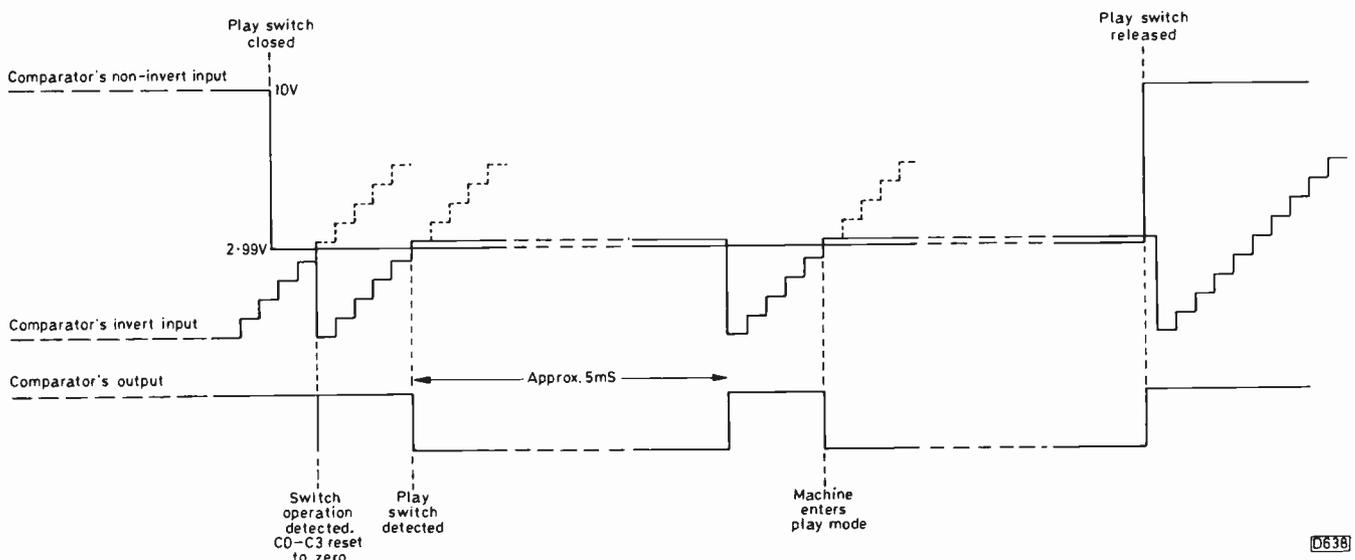


Fig. 3: Operation of the circuit when the play switch is closed.

Fig. 3 shows what happens to the comparator's input and output waveforms when the play button is operated. The principle is the same for each user function. The play switch applies 2.99V to the comparator's non-invert input. When the staircase waveform applied to the other input rises through this value, the output goes from high to low. The microcomputer detects the fact that a function switch has been closed, though at this stage it does not know which one had been operated, and resets the four-bit parallel data to 0000. As a result the comparator's output goes high again and the up-count is restarted. When the comparator's output again goes low, the count is stopped - in this example at 0101, which the microcomputer recognises as the play instruction. The microcomputer then repeats the count sequence as a double check and, if the instruction is verified, it acts accordingly to put the VCR into the play mode. The whole sequence takes between 10 and 20msec.

This AD technique enables up to sixteen commands to be accommodated using just five microcomputer pins, C0, 1, 2, 3 and B2. It's thus economical in the use of microcomputer pins while, because of the way in which the switches are connected, a remote control system using a two-wire cable is easy to arrange - a changeover jack socket is all that's needed.

Whilst the basic principles remain the same, the circuitry and voltage levels used in other VCRs may differ.

As to faults, we had one case (with an Hitachi VT8000) of an open-circuit resistor in the comparator circuit. This led the microcomputer i.c. to misinterpret the mode instructions and, apparently in total confusion, it switched the machine off! Since there's no one-to-one relationship between the switching and the action taken, various wierd and wonderful symptoms could be possible. The explanation given here however, with some scope checks around the comparator and ladder networks, should make it possible to ascertain whether the AD conversion is working properly or not.

All service engineers will by now be aware of the increasing use of digital techniques in TV/video equipment. Inevitably the need to come to terms with things like AD and DA conversion will become more pressing. Hopefully this short article, though dealing with only one aspect of the matter, will have thrown some light on this area of circuit operation.

# TV Fault Finding

Reports from Richard Roscoe,  
John Coombes and George R. Wilding

More often than not the process of repairing a TV set consists of simply changing the component or components that experience tells us are the usual cause of the fault. This means that servicing can be done speedily and cheaply, without the luxury of having to resort to true diagnosis. This is fine of course, but what happens when the usual culprit is not responsible? After fighting back the initial panic we then have to bring our considerable powers of deductive reasoning to bear upon the problem, i.e. where's the service manual? Having found that we can begin to think about the fault itself — but only if the manual has a clear circuit diagram and a sensible circuit description. All too often the manual seems to consist of a photo of the set, followed by fourteen pages of neatly tabulated part numbers and finally a fold-out sheet labelled circuit diagram, apparently produced by dipping mice in ink and letting them run about. Surely the priorities here are wrong? Who amongst us wouldn't swap the knowledge that a 100k $\Omega$   $\frac{1}{4}$ W resistor can be obtained by quoting the appropriate ten-digit code for a bit of a clue as to how the diode modulator or beam limiter is supposed to work?

Given the disincentives, it's hardly surprising that so many engineers can't or won't practice the art of logical fault analysis. Instead, they opt to extend the swap it and see principle until the faulty component is discovered by trial and error. Unfortunately a lot of perfectly good components get damaged or thrown away in the process, the printed tracks can suffer damage, and the quality of the soldered joints may be affected. Thus the whole area under investigation becomes a future trouble spot.

This is all leading up to a certain Pye 731 (later version) chassis that came our way recently. The fault was intermittent field jitter, and the customer told us she'd had it put right some six months ago before she'd moved to our area. When we switched the set on we found that the picture wasn't too bad, if a little flat. But if the scene changed the picture would become unsteady, jump slightly, then settle down again. It was not too bad, but enough to be annoying. Now the cause of this sort of trouble in sets that use a thyristor regulated power supply is usually in the power supply rather than the field timebase. The thyristor itself can be responsible, or its triggering may be defective. Alternatively if the regulation is faulty the h.t. can rise, as a result of which the over-voltage trip operates, producing a picture that flutters (in this chassis, at any rate).

When we removed the back we were appalled at what we discovered. Extensive and not very careful soldering had been carried out all over the power supply panel. Various diodes and capacitors were hanging off the print side, and jumper leads replaced damaged portions of track. The swap it and see policy had obviously been applied with a vengeance.

Without disturbing anything, we connected the meter to the h.t. line. It was continuously varying between about 190V and 200V, depending (or so it seemed) on the picture content. Thus little or no regulating action was taking place, though the h.t. was not far off — a bit on the high side. We next took a look at the presets. The h.t. controls (coarse and fine) were set at minimum. Carefully

advancing the setting of the coarse control increased the picture jitter, with the h.t. jittering in sympathy — clearly the over-voltage circuit was working. Tweaking the over-voltage preset allowed the h.t. to shoot up and we hurriedly backed it off again. It looked as if the previous repair had been no such thing but instead a bodge culminating in a desperate resetting of the presets to disguise the fault. Couple this with a judicious lowering of the contrast control setting (hence the flat picture) to smooth out the current demand and bob's your uncle (for a while).

After the board had been removed and tidied up as best we could we were ready to tackle the fault. We assumed that the obvious things — the thyristor and diac — had been replaced, and concentrated on the clue that there was little or no regulation. This led to a check on the feedback resistor R897, which should have a value of 470k $\Omega$ . It read over 10M $\Omega$ ! Replace it and set up the adjustments and we'd an excellent picture. What a lot of trouble a little thought would have saved! **R.R.**

## Toshiba Model C2295B

We've sold many of these sets and have a number out on rental. Our fault experiences have been as follows.

**Low gain:** Check for 12V at pin 2 of the tuner interface panel on which the a.g.c. amplifier and i.f. preamplifier stages are mounted. If the 12V supply is present here but not at the collectors of the preamplifier transistors 1TR32/3, 1R56 (4.7 $\Omega$ ) is probably open-circuit. If the voltages are present, check the preamplifier transistors 1TR32 (BF198) and 1TR33 (BF199).

**Colour faults:** The decoder module T146A consists mainly of the large decoder chip IC501, type TA7193P, which can be responsible for no colour, intermittent loss of colour, Venetian blind effect and no red, green or blue. Other things to check in the event of no colour are the 4.43MHz crystal XL501 and the delay line driver transistor TR502 (BC557A).

**Loud whistle:** Several things can cause this, but the most likely culprit is the line driver transformer T401. Check by replacement.

**Channel selector locked to one channel – signal tunable but memory inoperative:** This is usually due to the digital control i.c. (ICA01, type TC9002AP) which must be handled with care to avoid damage. Other items to check if necessary are diode DE12 (1N4148) and zener diode DE11 (ZPD24) – by replacement.

**Memory fails to operate:** Check the memory i.c. (ICA02, type TMM841P) by replacement. If necessary check the clock oscillator tuning capacitors CA11 and CA12 (120pF) and the coil (LA01) which can go open-circuit.

**Audible noise when changing channels:** Connect a 4.7 $\mu$ F capacitor between pins 53 and 54 on the main panel, positive side to pin 54. **J.C.**

## Toshiba Model C2095B1

The Toshiba C2095B1 shares many panels in common with the C2295B, the information given above applying to

this set as well. One difference is the use of an over-voltage circuit which shuts down the line oscillator in IC301 (TA7609P). If the circuit comes into operation when the set is otherwise working normally, check the over-voltage transistor TR471 (BC557A) by replacement and its base bias components R476 (1M $\Omega$ ) and D472 (BZX79-B6V2). The zener diode can leak and the resistor can change value.

J.C.

## GEC Series 2

No sound or raster but a slight hum from the speaker confirmed that the valves had warmed up and that h.t. was present. There was ample voltage at the anode of the PL504 line output valve, but not the slightest suggestion of a spark. On touching the PL504's envelope we found that it was running cool. Likely causes were an internal valve defect or the screen grid feed resistor open-circuit. There was full h.t. at the screen grid pins, while the absence of a negative voltage at the control grid pins suggested that the valve was indeed defective. Surprisingly, a replacement failed to restore normal operation. The only possible remaining cause of the fault was an open-circuit connection to the valve's cathode: the print looked all right, but fitting a short jumper lead from pin 8 to an adjacent earthed point finally solved the problem.

G.R.W.

## Saba H Chassis

A Saba Model TS6735 (H chassis) came our way recently with the complaint that while it would usually work for a few minutes after switching on it would then change channels spasmodically and erratically before going off to leave an unmodulated raster with only hiss from the speaker. After this, operation of the remote or on-set channel change controls had no effect.


As with all electronic tuning systems, the chips involved are the prime suspects. There's an SN74141 BCD decoder, an SN74190 BCD counter, and an SN7413 dual-NAND Schmitt trigger. The latter could be ruled out since it's operational on remote control only. Before replacing the other two i.c.s we decided to check the l.t. supplies. The TBA625 5V regulator i.c. was found to be providing only some 3V, though its 10V input was correct. Replacing this i.c. restored normal channel selection, but a few days later the set was back with the complaint "no results" due to a short-circuit diode in the 20V bridge rectifier blowing the associated fuse.

Replacing the diode and fuse restored the l.t. supplies, except that from the 5V regulator. This time we didn't have a TBA625, but found that a 7805 was a satisfactory substitute.

G.R.W.
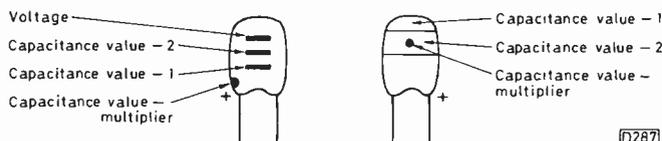
## Capacitor Colour Codes

Miniature tantalum capacitors of various makes are found in continental TV sets. Whilst those manufactured by Bosch and NSF have the values and voltage ratings



0287

Fig. 1: Colour coding systems used on Ero/Frako (left) and SEL (right) miniature tantalum capacitors.

Table 1: Tantalum capacitor colour coding.

Colour	Capacitance ( $\mu$ F)		Multiplier	DC voltage
	First figure	Second figure		
Black	—	0	$\times 1$	10V
Brown	1	1	$\times 10$	1.5V
Red	2	2	—	—
Orange	3	3	—	—
Yellow	4	4	—	6.3V
Green	5	5	—	16V
Blue	6	6	—	20V
Mauve	7	7	$\times 0.001$	50V
Grey	8	8	$\times 0.01$	25V
White	9	9	$\times 0.1$	3V
Pink	—	—	—	35V

printed on them, some Ero/Frako and SEL capacitors use a colour coding arrangement. Details are given in Fig. 1 and Table 1.

G.R.W.

## Rediffusion Mk I Chassis

This hybrid colour set gave perfect results apart from the fact that the width would often vary erratically by about half an inch on either side. The 5M $\Omega$  width control is connected to the usual VDR arrangement and looked decidedly the worse for wear, but replacing it made no difference. Attention was therefore turned to the associated high-value resistors. These sets are now several years old, and the small panel on which the width control and various other components are housed is mounted close to the line output stage valves. R501 (1.5M $\Omega$ ) in series with the width control's slider and R500 (3.3M $\Omega$ ) which is in series with its track were replaced, completely curing the width variations — the heat from the valves was almost certainly responsible for the deterioration of these resistors over the years.

G.R.W.

## B & O 3400 Chassis

The problem with this hybrid colour set was bad NS raster distortion — being an early 110° set, the raster correction circuitry is quite elaborate. Anyway, replacing 12C2 (0.1 $\mu$ F) in the NS output transformer tuning network and readjusting the four presets on the NS correction panel cured the trouble.

An almost equally annoying fault, though apparently not noticed by the set's owner, was the raster's tendency to balloon when the brightness was well advanced. Worse still, the focusing then deteriorated as the e.h.t. fell. The basic cause was poor e.h.t. regulation of course: changing the GY501 e.h.t. rectifier improved matters but didn't completely remove the effect. A new boost diode produced a further marginal improvement, and the trouble was finally resolved by bringing the boost voltage up to the correct figure of 840V from 750V (boost adjustment preset 8R5) then readjusting the preset width control 6R24. In most hybrid sets there's a single preset width control which also sets the boost voltage, but in this chassis there are two independent controls. Measure the boost voltage at test point TP4.

G.R.W.

## Correction

Finally, our apologies for a printing error last month. R913 in the Decca 110 chassis' first anode control network is 220k $\Omega$ , not 22k $\Omega$ .

# Exhibition Report: Cable 83

*Dave Lauder, B.Sc.*

The organisers of the "Cable 83" exhibition and conference, which was held at the Wembley Conference Centre on May 10-12th, described it as "Europe's first major exhibition of cable TV products and services". It was actually two shows combined, the other one being the "London Satellite Television and Cable TV Show" which was due to have been held in July.

Although many exhibits were for cable operators and broadcasters, there was much to interest those of us at the receiving end. Satellite TV receiving systems were conspicuous on a number of stands, as were live displays of Soviet TV via the Gorizont satellite. The prices of such 4GHz equipment have fallen steadily, and Megasat were offering a system comprising a 1.5 metre dish aerial with mount and electronics for £1,250, plus installation and VAT. For maximum enjoyment however a SECAM colour TV receiver and a knowledge of the Russian language would be an advantage!

As it was essentially a trade show, there was little aimed at the amateur constructor: some exhibitors could not even quote prices for individual parts of their systems. March Microwave however were exhibiting 4GHz low-noise amplifiers (LNAs) and combined LNA/down-converters made by Dexcel Inc. in the USA. Although the prices are in the region of £300, some constructors are interested in them due to the difficulties of building a front end to work at these frequencies.

A potential problem for Gorizont viewers is that the satellite's orbit is becoming inclined, and the time may come when auto tracking or twice daily dish adjustment becomes necessary. It's not clear whether the orbit can or will be corrected, as the satellite is intended only as a link between studios and transmitters.

With direct broadcasting at 12GHz due to start in Europe in 1985 there was surprisingly little DBS equipment to be seen. This could in part be due to the lack of any decisions so far about the type of transmission to use. While some dishes on display were suitable for frequencies up to 12GHz, the surface accuracy of many was insufficient for use above 4GHz. No European made equipment was evident in the field of 12GHz electronics. The Japanese appear to have gained a lead in this area – they have after all had a 12GHz direct broadcasting satellite in use, though it's no longer in operation.

BBC Engineering were present and had information sheets mentioning the use of the MAC system for satellite broadcasting. The IBA, which developed MAC, was not represented however. This was somewhat surprising in view of the EBU's favourable view of MAC (despite that however governments and broadcasting organisations are still arguing about what system to adopt).

The cable TV aspects of the exhibition covered all the distribution hardware, much of which consisted of well established US products. There were machines to dig ditches, and even to install cables in sewers... Displays of advanced cable technology included switched stars and optical fibres, and there were simulations of the type of services that interactive cables could provide.

At the end of the day one cannot help but wonder how many viewers will be prepared to bear the cost of satellite receivers/decoders, or of connections to cable, bearing in mind the recurring cost of licences or subscription channels. Large audiences will be attracted only when high quality programmes are available at reasonable cost – but this in turn requires a large audience to start with, a typical chicken and egg situation.

---

## VCR Servicing

*Part 19*

*Mike Phelan*

Having had a month to recover from the 3V23's drum servo, we'll now take a look at the capstan servo (see Fig. 85). This is fairly conventional, with both a speed control loop and a phase control loop, as in the drum servo. The bulk of the circuitry is contained within IC12 (AN6341), but a BA841 is used for still/slow/frame advance/double speed – this operates in the same way as in the 3V16 (see Part 14). There are also facilities for assembly edit, i.e. successive recordings can be made without noise between them, which is essential for camera work.

### **Capstan Motor Drive**

For a change we'll start at the motor end of the circuit, see Fig. 86. The motor is a conventional brush type d.c. motor, but unlike those used in previous models has ballraces instead of sintered bronze bearings. This gave rise to a little problem, more of which later.

The speed error voltage is applied to pin 6 of IC13, the operational amplifier's inverting input. The phase error

voltage is applied to the non-inverting input at pin 5 – the diodes etc. connected to this pin are for the usual limiting and filtering. There is also frequency-sensitive negative feedback. The output at pin 7 combines both error voltages and feeds the motor drive amplifier X21, X2 through D21, which is forward biased of course. The motor's other terminal is normally earthed due to X4 conducting. X22, X3 and X1 are normally off.

When the capstan is rotating, the motor control output from pin 38 of IC14 is high. It goes low to stop the motor. This results in two things. First the two inverters (part of IC10) earth the anode of D21 so that it's cut off. This removes the input to the motor drive amplifier so that the motor comes to rest. Secondly X8 turns on, taking pin 6 of IC13 high and therefore pin 7 low. This prevents pin 7 rising to 12V as the servo tries to correct for the fact that the motor has stopped.

This all happens when we press stop, rewind, fast forward, still or slow. In the latter two modes however the slow-drive circuit takes over. This operates almost exactly

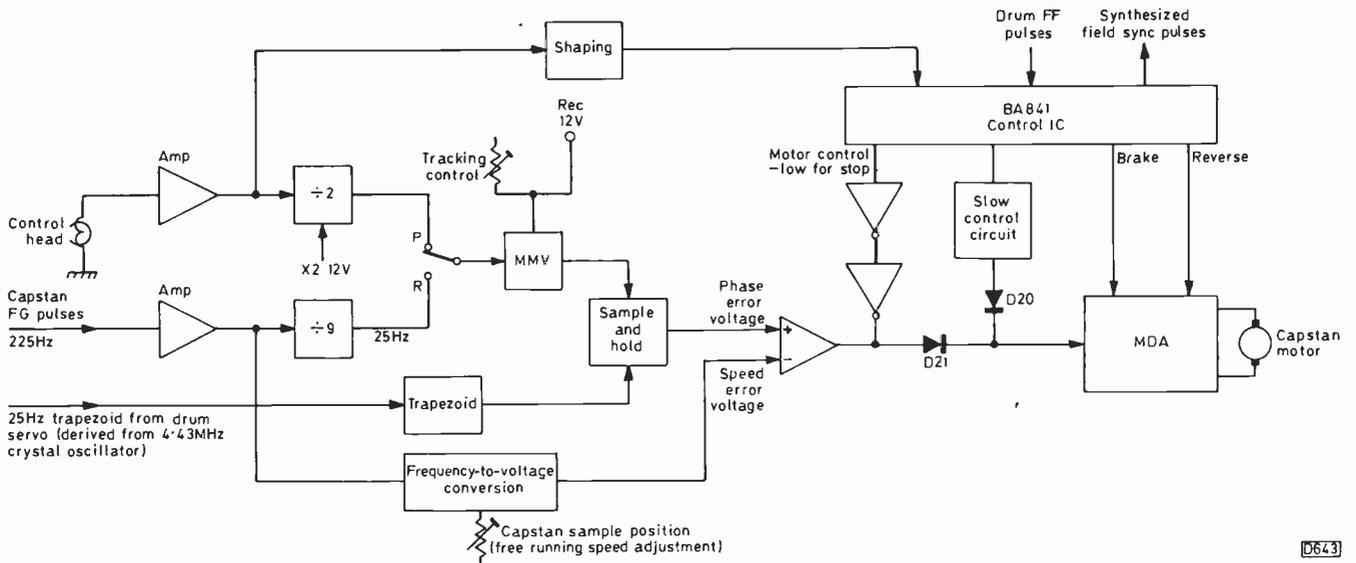


Fig. 85: Simplified block diagram of the capstan servo.

as in the 3V16, but with one slight difference. To recap. If we are in playback, FF2 (IC14 pin 30) is high so that X23 is on and X1 is off. FF1 (pin 29) is low and pin 38 (motor control) is high. When we press pause, pin 38 goes low, turning on X8 and also earthing the anode of D21 via IC10. FF2 also goes low, turning on X1 to brake the motor – as X4 is already on, this effectively places a short-circuit across the motor. With the motor used in the 3V16 this was fine, but the ball-bearing motor used in the 3V23 will not stop instantly even when shorted. This is where the circuit to the right of the motor, connected to pin 28 of IC14, comes in.

Every time FF2 goes low to brake the motor, pin 28 produces a 10msec pulse. This turns on X22, X3 and X24 and turns off X4. So the normally negative end of the motor is connected to 22V for 10msec. As X1 is now on,

this pulls up the motor instantly. To digress briefly, it's important not to fit this type of motor to the 3V16, which doesn't have the reverse brake circuit, as the stopping point will be badly defined, with noise bars on slow and still.

Back to the 3V23. The tape has now stopped and the machine waits for the third drum flip-flop pulse. This changes the states of FF1 and FF2, removing the brake by turning X1 off, and triggering the slow-pulse generator. This, as you may recall, produces a 20msec pulse which is added to a lower amplitude pulse of variable length – the initial part overcomes the motor's inertia. The tape moves, typically for 60msec, until 17msec after an off-tape control pulse is read. FF1 and FF2 then both change state, ending the drive pulse and braking the motor with the 10msec reverse braking pulse. This process is repeated

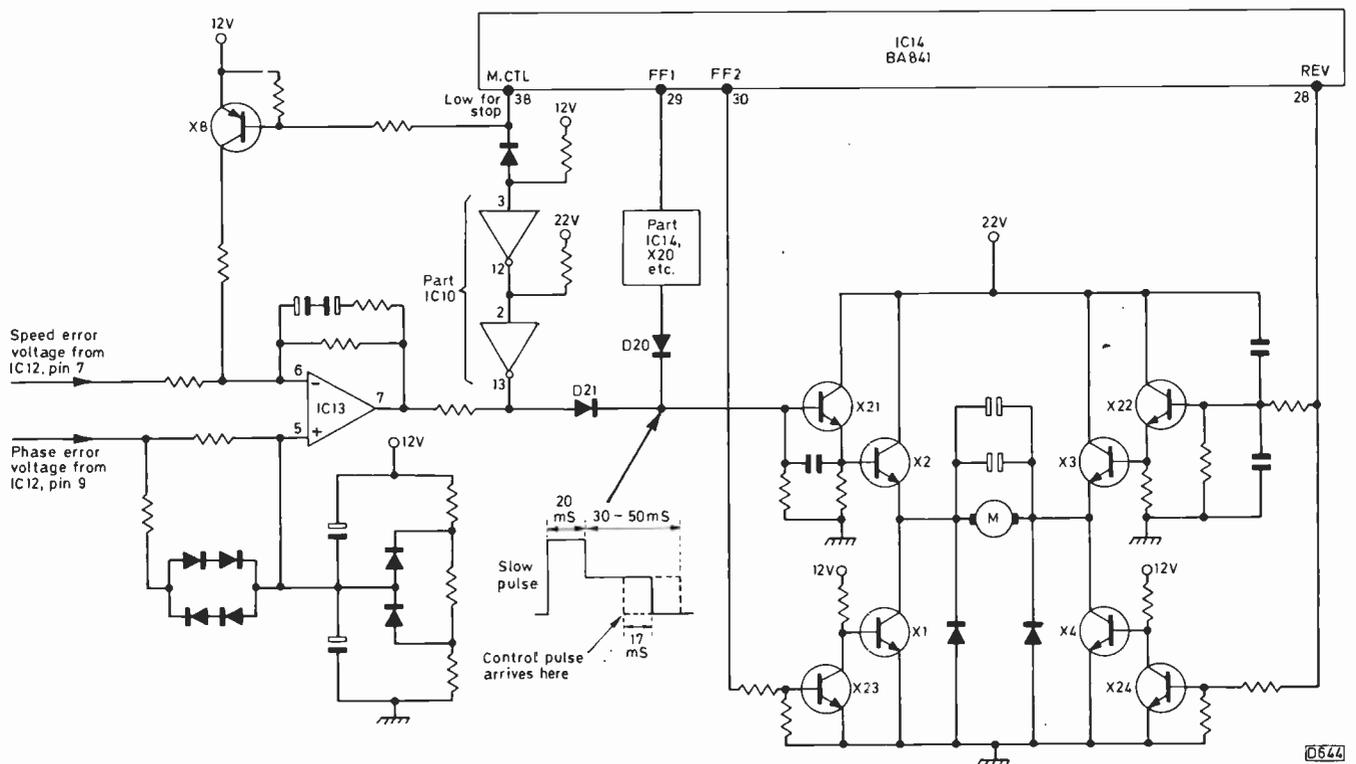


Fig. 86: Capstan motor drive arrangements.

four times, the tape transport then stopping completely, unless in the slow mode when further drive pulses are produced at intervals. The pulse length is adjustable by varying the amplitude of the second part of the pulse. This has the effect of altering the motor current and therefore its speed: the faster it goes, the sooner the next off-tape control pulse arrives, and as this makes the drive pulse end 17msec later the pulse length is varied.

### **Capstan Servo – Playback**

The “front end” of the capstan servo is shown in Fig. 87. During normal playback it operates as follows. First the speed control loop. The 225Hz capstan frequency gear (FG) signal is amplified by IC7 and X5 and presented to pin 16 of IC12 which contains two divide by two flip-flops followed by a frequency-to-voltage converter that works on the same principle as the arrangement used in the drum servo. The speed error voltage is produced at pin 7 of IC12 and then goes to pin 6 of IC13 as previously mentioned. During normal playback D27 is biased off so that the second flip-flop is inoperative. In the double speed mode D27 is forward biased since pin 10 of IC11 goes low: the FG signal, now at 450Hz, is divided by two a second time to restore the correct conditions in the servo.

The phase control loop compares the trapezoid from the drum servo at pin 13 of IC12 with the timing of the off-tape control pulses. The block marked “trapezoid” in IC12 alters the slope and timing of the drum trapezoid.

All the servo functions are controlled by the inputs applied to connections 51, 55 and 58. The latter is the double speed 12V line. 51 and 55 are both low during playback. This sets IC9 so that its Q output (pin 15) is low while its inverted Q output (pin 14) is high. X6 is on, disabling IC8 (we’ll see what this does later). The off-tape control pulses are amplified by IC1 and X1 and then fed to the monostable IC2 whose cycle time is 30msec. As the control pulses are spaced by 40msec, this simply alters their width. X2 inverts the pulses and IC3 shortens them to 13msec, this time being fixed by the two resistors and capacitor connected to pins 1 and 2. X3 is off because pin 10 of IC11 is high, and thus has no effect. X4 inverts the pulses, which next pass through two NAND gates to pin 15 of IC12. The FG pulses from pin 10 of IC6 cannot get through as the first NAND gate (IC4c) is disabled by a low on its second input (from IC9’s Q output). X10 and X11 are off while X13 is on, so the time-constant of the tracking MMV in IC12 is set by the manual and preset tracking controls and R120.

Two things occur in the double speed play mode. First, as we’ve seen, the now 450Hz FG pulses are divided by two again in the speed control loop, since D27 is forward biased. Secondly X3 is turned on by pin 10 of IC11 going low. This shorts out part of the time-constant controlling IC3 so that its cycle period is now 7msec. But, you say, the off-tape control pulses are now arriving at 50Hz! Not so, at least not after IC2: the 30msec period of this MMV now effectively divides them by two, since the pulses are spaced by 25msec at the input and IC2 is now triggered on every other pulse.

### **Capstan Servo – Record**

On record, the 51 and 55 connections are both high, so that IC9’s Q and inverted Q outputs are both changed – Q is high, inverted Q low. The speed control loop remains

the same, but the sample for the phase control loop is now the FG signal divided by nine to give 25Hz. X6 is off, so IC8 is enabled, squaring up the control pulses and sending them to the control head via the noise trap D7/8. These pulses get as far as X4, but no farther, as NAND gate IC4a is blocked by a low input from the inverted Q output of IC9.

The FG signal, after being squared by the Schmitt trigger IC17, is fed to pin 14 of the 4017 IC6. The 4017 can be made to divide by any number up to ten. It has ten output pins, designated Q0-Q9. Each goes low in turn when we feed a pulse to pin 14, the clock input. When pin 15 (reset) is taken low, the count starts at Q0 again. In this application we want to divide by nine, so Q9 is connected to the reset pin via X7 and the NAND gate IC4d which is enabled. Thus every time Q9 goes low so does the reset pin and we get division by nine. The other two NAND gates IC4c/b are enabled, so the output pulse goes to pin 15 of IC12. The Q4 output is used, but any would do. NAND gate IC4d is used as an inverter for the reset pulse – pin 2 is high since NAND gate IC4a is disabled. If one input of a NAND gate is low, the output is high: if one input is high, the gate acts as an inverter. The three gates in this part of the circuit are thus used to route the sample signals.

Finally X11 is on, cutting out the tracking controls. X10 and X13 are both off.

### **Edit Start Control**

We now come to the interesting bit, the edit start control. If you’re unsure what’s meant by editing, consider the case where several recordings are made on one tape – maybe by pressing the pause control during the commercials, or when using a camera (the VCR goes into pause every time the camera’s trigger is released). When the tape is played back there will be lots of noise between each “take” as the servos lock up again. On this machine the drum servo would run free when the signal was interrupted, and would need time to lock up again. Even when pause is pressed during the advertisements and the signal is not interrupted, stopping the tape will alter the spacing between the control pulses on the tape, upsetting the capstan servo on playback. In the worst case there’ll be a 20msec space between the last pulse of the previous section of recording and the first pulse of the next section. Even without this, both servos will take a second or two to relock.

On the 3V23 however we can press pause during record, then restart by pressing the play button, or use a camera trigger to do this, the result on playback being perfect edits – just as if channels have been changed.

How is this magic performed? When record pause is selected, the pinch wheel comes out, the tape winds back through some 25 frames (assuming that there’s already a recording on the tape), then stops. This is controlled by the microcomputer i.c. on the mechacon panel. When recording is restarted, the ESC (edit start control) routine starts. In this state connection 55 is high but 51 is low, unlike normal record. IC9’s Q output is low and its inverted Q output is high, as in playback. Let’s stop at this point to consider exactly what the problem we’re trying to overcome is.

Having wound the tape back, we have 25-30 frames of the previous recording which can be used for comparison purposes and to stall for time while the drum servo locks up. We mustn’t actually record during this time, because we don’t want to erase anything, but the drum servo

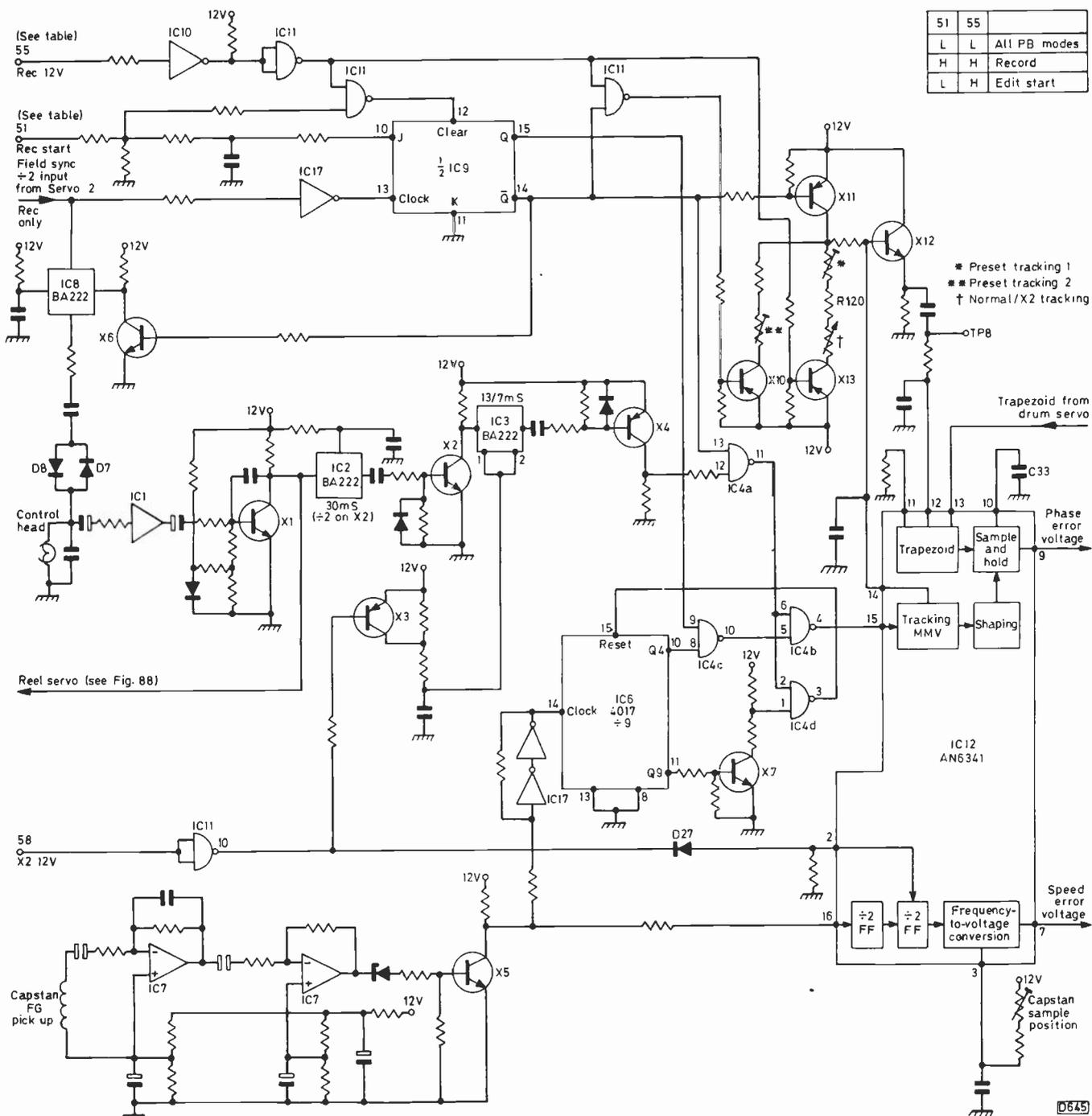


Fig. 87: Capstan servo – the “front end”.

must be in the record mode. This is not quite the whole story, because it's necessary to ensure even spacing of the last control pulse of the previous take and the first control pulse of the next take. This is done by putting the capstan servo into playback, so that it's locked by the control pulses, then somehow switching everything back to record before the 25 or so frames have been passed.

This is how it's done, using the items we've already considered in Fig. 87. Remember that the drum servo is unaltered, remaining in its normal record mode. We're recording and press pause. The tape winds back 25-30 frames then stops. When we restart the recording, the ESC sequence starts – connection 55 stays high, but connection 51 stays low for 12 frames then goes high to put the machine back into normal record. Nothing is recorded on the tape during the ESC period. The drum servo locks up to the new input signal, so that it's well and

truly locked by the end of the ESC time. Remember that it's running at the correct speed all the time, even in the absence of an incoming signal.

It's in the capstan servo however that the interesting things occur. During the ESC period the FG divided by nine output from pin 10 of IC6 is blocked because pin 9 of IC4 (IC9's Q output) is low. IC9's inverted Q output is high, so gates IC4a and IC4b pass the off-tape control pulses to IC12. In other words the capstan servo is in the playback mode, locked to the final off-tape control pulses from the previous recording. IC6 is still fed with amplified FG signals, but can't at first divide by nine because pin 2 of IC4 is not held high as it is in playback, so there are no reset pulses from IC6's Q9 output to its reset pin. The result is division by ten instead, giving an output at 22.5Hz. Pin 2 of IC4 (the reset gate) is fed with the off-tape control pulses in the ESC mode, so this pin goes high

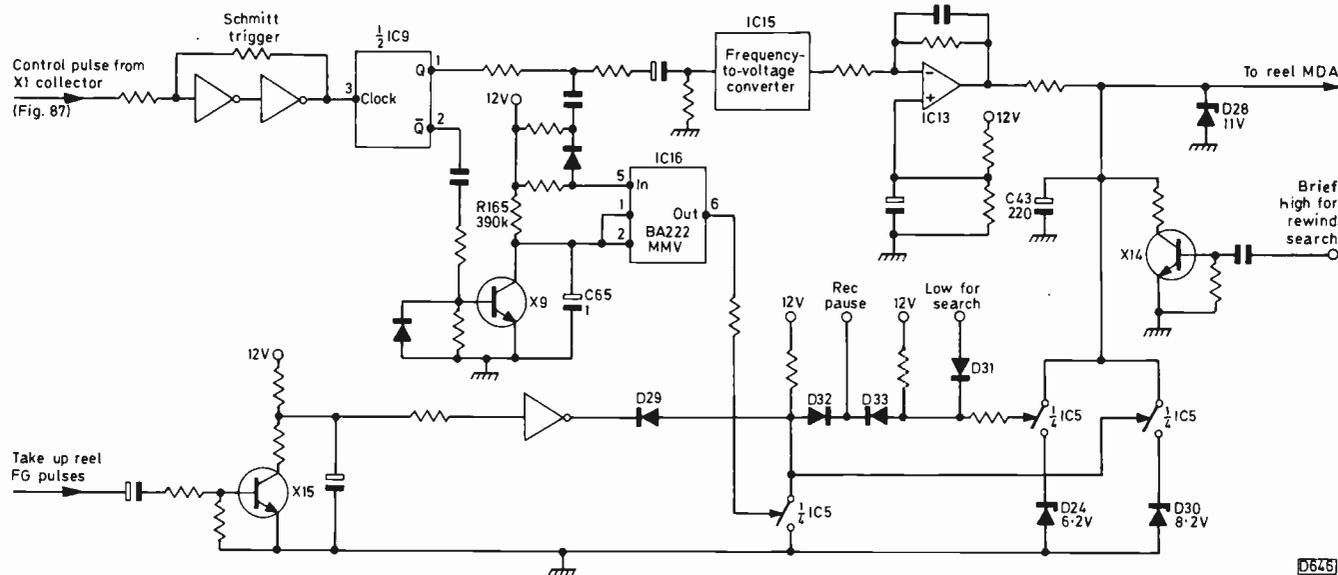


Fig. 88: The reel servo.

25 times a second. As the Q9 output is at 22.5Hz, a control pulse will arrive at pin 2 of IC4 at the same time as the Q9 pulse within the 12 frame period (approximately half a second). IC4d will then pass a low output to the reset pin. If this occurs early in the ESC sequence the counter will divide by nine every time, since the Q9 bit and control pulse are coincident.

At the end of the ESC sequence the machine switches back to record, IC9's Q and inverted Q outputs change state, the gates of IC4 block the control pulses and the reset gate is permanently on. So the new recording starts with a slight overlap, but the clever bits with the reset gate and the counter ensure that there's no "glitch" between the control pulses on playback, while the drum servo has had plenty of time to lock up anyway. The edits are perfect and take place within a single frame.

To summarise, 12 frames of the previous recording are played back, with the drum servo in record and the capstan servo in playback, while the counter is synchronised with the off-tape control pulses being played back. After twelve frames both servos are stable and the machine starts to record.

### The Reel Servo

We'll finally look at the third and simplest servo system, the reel servo – see Fig. 88. We've already seen that the microcomputer's D port (see Fig. 68) controls the reel motor. It does this in conjunction with a series of gates that switch various voltages to the reel motor via transistors. In fast search however the reel motor is servo controlled: the servo controls the speed, the microcomputer the direction.

As the tape is running at ten times the normal speed, the control pulses arrive at 250Hz. After being squared by the Schmitt trigger, the other half of IC9 divides them by two. The 125Hz pulses are then fed to the frequency-to-voltage converter IC15, whose error voltage output is applied to the motor drive amplifier via IC13.

IC16 forms a monostable whose time-constant is approximately 400msec. Any pulse fed to pin 5 of this i.c. is thus stretched to 400msec, unless X9 conducts and shorts out C65, resetting the MMV. As the Q and

inverted Q outputs from IC9 alternately fire and reset the MMV, pin 6 produces a series of pulses whose width varies with frequency. Each pulse closes two switches in IC5, connecting C43 to the 8.2V zener diode D30. This arrangement prevents hunting. When not in search, D31 is forward biased so that D24 maintains the charge on C43 at 6.2V. If C43 was fully charged or discharged when going from play to search, the reel motor would either stall or speed up, with unfortunate results for the tape.

### Reverse Search

When reverse search is selected X14 momentarily conducts, discharging C43, with the result that the motor stops and restarts gradually in reverse as C43 charges – this avoids snatch.

### Edit Start Backspacing

The "record pause" input opens the first two switches of IC5 and closes the last one, setting the speed of the backspacing for the edit start with D30.

### Correction

Next month we'll continue with the 3V23's signal sections, starting with the audio department which has some interesting features. Before going any farther however a correction is required. Due to an editorial misunderstanding, there were several references to forward and reverse slow motion in Part 17 (see page 373). This is incorrect: the two controls are for faster or slower than the preset slow motion speed selected on going from normal play to slow motion.

### Colour Supplement

Another point worth making relates to the photographic colour fault guide in the May issue. In some cases, particularly photos 10 and 13, the fault condition is not easy to see. The reason for this is that it's necessary to use a camera exposure covering two complete fields or more. This unfortunately means that noise and other minor disturbances, being random, tend to be integrated out.

# Teletext Decoder Update

Steve A. Money

The *Television* teletext decoder was updated in 1979 (see June-August 1979 issues) to provide colour. Since then some changes have taken place in the transmission of both Ceefax and Oracle and some modifications to the decoder are required to obtain correct operation. The main change has been the increase in the number of teletext data lines transmitted per field – four lines are now used instead of two, giving faster access to pages and the possibility of larger magazines.

A relatively simple modification will deal with the extra lines. All that's required is to alter the timing and width of the data gating signal. Fig. 1 shows the modification, which involves changing the values of the timing components for the two monostables in IC4 (74221). C5 is reduced to 0.033 $\mu$ F to give a delay of about 650 $\mu$ sec so that data is accepted from about ten lines after the field sync pulse, while the value of C4 is increased to 0.033 $\mu$ F to allow eight-ten lines through to the decoding logic. Because of the relatively wide value tolerance of the capacitors, it's advisable to add a 10k $\Omega$  trimmer potentiometer (RV1) in series with R4, which is reduced in value from 33k $\Omega$  to 27k $\Omega$ .

To set up the decoder for four-line data operation, tune to a BBC channel, select page roll, and adjust RV1 until the text rows are all being displayed. If the delay is too short or too long, one or two lines in every four on the page will be lost.

## Oracle Interleaving

Changes in the Oracle service present a further problem which involves a more complex modification. At the time of adding the extra data lines the transmission sequence of the Oracle data was also changed. Whereas with Ceefax all the lines for a page are sent as a single block, the Oracle data signals for several pages in different magazines are interleaved so that one set of four lines might be for say page 110 while the next four data lines could be for page 250 and so on. This scheme relies on the fact that the magazine code (hundreds in the page number) is sent at

the start of every data row though the complete page number is sent only on header rows. Since the *Television* teletext decoder carries out a page number check only during the header rows, it assumes that all the following data until the next header is for the same page. The result, when trying to receive Oracle, is a scrambled mixture of lines from several different pages.

It was initially thought that the input logic board might have to be virtually rebuilt to resolve the Oracle signals. Several different modification schemes were tried with varying degrees of success. Eventually a relatively straightforward modification involving the addition of just two i.c.s on the board was devised and seems to be successful. The additional logic is shown in Fig. 2.

The flip-flop IC25 (7474) detects a match in the magazine code as each data line is received. This is done by clocking the flip-flop when the magazine code is present on the data lines DB1 to DB8, and setting it to the output state of the code comparator IC24 (pin 6). This output goes to 1 when a match exists, so the Q output of IC25 will be set at 1 when the received data line is from the requested magazine. IC25's Q output is gated with the page accept signal from IC17b, and controls the writing of data into the page memory. Thus only lines with the correct magazine code are written into the memory.

Header rows for pages from other magazines may be interleaved with data for the selected page. To prevent these header rows from resetting the page accept flip-flop IC17b, its clear input from the row 0 detector gate IC20 is disconnected and its clock pulse is gated with the output of IC25. As a result IC17b responds only to page headers from the selected magazine.

Finally, to give correct rolling header operation the signal from IC25 is also fed to gate IC18a so that only header rows from the selected magazine are displayed when the decoder is searching for a newly selected page.

The additional logic shown in Fig. 2 can be mounted on a small piece of 0.1in. pitch Vero stripboard which can be wired directly to the input logic board so that it's supported directly above the i.c.s on the main board.

On the input logic board the tracks to pin 13 of IC17 (7474) must be cut so that pin 13 is isolated. One track is on the component side and the other on the reverse side of the board. A link must be used to bridge the separated parts of the track so that pin 2 of IC17 is still connected to pin 2 of IC15. If IC17 is in a socket, a simpler solution is to bend up pin 13 of IC17 so that it doesn't enter the socket. For reliable operation it's advisable to connect pin 13 of IC17 to the 5V rail. When the tracks are cut this can be done by bridging pins 13 and 14 of IC17.

The track from pin 8 of IC17 to pin 1 of IC18 and the link between pins 3 and 4 of IC18 (7410) must also be cut.

The additional logic circuits are wired into the board by making connections to IC5, IC17, IC18, IC19, IC21 and IC24 as indicated in Fig. 2. Note that 5V and chassis connections are required for the extra i.c.s.

No setting up is required. If the system is working, then with page roll selected only those pages with the selected magazine number will be displayed – i.e. if page 100 is selected, only pages 100 to 199 will appear. Because the decoder has no error detection and correction circuits for address decoding, any errors in the received data for page and magazine codes may cause parts of pages other than the selected one to be displayed. Provided reception is reasonably error free however this problem will be infrequent.


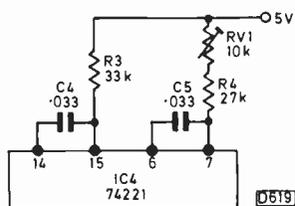


Fig. 1 (left): Modification for receiving extra lines.

Fig. 2 (below): Modification for dealing with Oracle interleaved page lines.

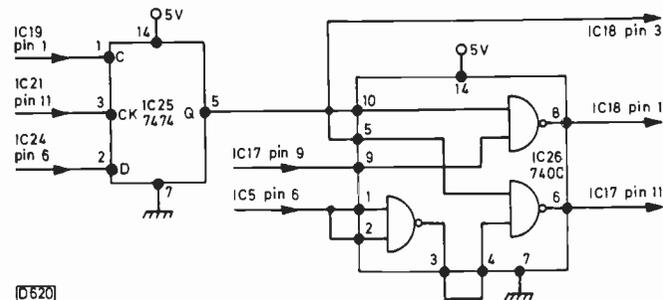



dropped) the flywheel had jolted down the head drum shaft, taking the magnet out of range of the tachometer coil. So no triggering pulses and no squarewave. A couple of minutes with an Allen key put the machine to rights. It now sits on the shop shelf, fearfully awaiting its next customer.

# Service Bureau

*Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon from page 488 and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.*

## ITT FT110

The picture broke into lines whilst the set was being viewed. Switching off and on restored the picture, but after a while the raster collapsed towards the centre. The set is now dead.

First check whether the surge limiter resistor R765 ( $5.1\Omega$ ) is open-circuit or the mains rectifier D708 short-circuit. If these items are in order it's likely that the switch-mode power supply has stopped due to an overload. There's no single common fault unfortunately. First check whether any of the rectifier diodes D713/4/5/11 is short-circuit. If R789 is open-circuit, check the BU208 converter transistor T712. Further possibilities include the BU208 line output transistor T501, the tripler, and C517 ( $0.001\mu\text{F}$ ) at the earthy end of the e.h.t. overwinding. If the power supply comes to life when the tripler is disconnected from the line output transformer, replace the tripler.

## KUBA FLORENCE

There's a bright white line down the centre of the screen, with centre foldover, and R514 across the line coils is cooking. The field scan appears to be normal and there's full width. The original fault was no e.h.t. due to lack of line drive as a result of the l.t. bridge rectifier D606 going short-circuit and blowing the fuse.

The fact that R514 is overheating indicates that there's a break in the scan circuit on the raster correction panel (removing the panel will have the same effect). Check for continuity from pins 5/6 through one winding of the linearity coil L551, then the corner convergence transducer L552, the EW correction transducer L555 (the blue one) and its parallel resistor R561 ( $15\Omega$ ), the second corner correction transducer L553, the other

linearity coil winding and finally pins 7/8. L555 is not fitted on some panels.

## BUSH TV300

The main problem is poor field linearity, which no adjustment will cure – the field linearity control has no effect. The sound output transistor also seems to be excessively hot.

We suggest you check the field drive coupling capacitor C411 ( $47\mu\text{F}$ ) and the output coupler C413 ( $470\mu\text{F}$ ), preferably by substitution, before suspecting the driver and output transistors. These are TR19 (2SC945) and TR20 (2SD152). If the audio output transistor TR15 (2SD152) is excessively hot it's probably leaky.

## SONY KV1800UB

The trouble is the convergence. The blue horizontal lines are wider than the red and green ones and can't be superimposed on them.

Assuming that the static convergence (screen centre) is correct (if not, adjust the vertical static convergence plate, whose tab points upwards), you'll have to move the deflection yoke (flared end) carefully to the right, as viewed from the rear of the set. When the convergence is correct, wedge and seal the yoke.

## GEC 3133

The fault with this set is no results. There's 300V at the collector of the pump transistor TR451, but the start up bias at the junction of R403/4 is only 1.5V instead of 5.8V. The pump and line output transistors are both o.k. and no component defects can be found on the power panel.

We suggest you feed an external 6V supply to the junction of R403/4, i.e. the anode of the start-up diode D403, then check with an oscilloscope whether line drive is present. If so, C404/5 (across R403/4) and D403 are suspect. If not, check the line driver transistor TR202 then suspect the 12V zener diode D201 and the timebase generator IC251.

## THORN 8500 CHASSIS

The picture is very good with the brightness turned down, but there's severe smearing when the brightness is advanced – especially on peak white. The tube has been tested, all voltages seem to be correct and the grey-scale tracking has been set up as per the instructions in the manual.

Flaring at high brightness levels is the result of the RGB output stages bottoming. Make sure that the beam limiter circuit diodes W601/2 on the c.r.t. base panel are o.k., then turn down the preset brightness control R205 – it's in the middle of the signals panel – compensating for this by increasing the settings of the c.r.t. first anode presets. After doing this ensure that all three drive controls R214/6/8 are set to maximum and that the contrast control is not over advanced.

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. "Television" is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# ELECTRONIC EQUIPMENT SERVICING

(TELEVISION/VIDEO)

full-time College course


TRAINING INVOLVES A HIGH PERCENTAGE OF WORKSHOP FAULT DIAGNOSIS ON MONOCHROME & COLOUR TELEVISION EQUIPMENT. CLOSED CIRCUIT TV & VIDEO CASSETTE RECORDER PRINCIPLES ARE INCLUDED IN THE COURSE

## 15 MONTHS COURSE

for beginners to include Electronic Fundamentals
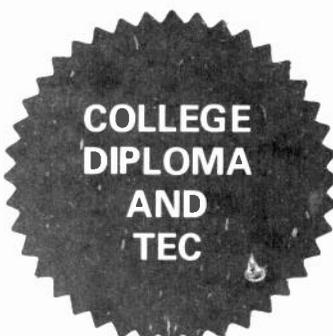
## 6 MONTHS COURSE

for BSc, HND, CGLI, TEC and similar applicants



Next two courses commence on September 19th and January 9th.

Also courses in Computers/Microprocessors, and Robotics leading to Technician Education Council Cert. and Higher Cert. awards.

Prospectus from:

**LONDON ELECTRONICS COLLEGE (Dept T3/4)**  
20 Penywern Road,  
Earls Court, London SW5 9SU  
Tel: 01-373 8721

## TV TUBES TUBE POLISHING WORKING TV'S WORKING PANELS FREE DELIVERY\*

Quality, High Temperature Reprocessing

Colour Tubes	One year guarantee (optional extension up to three years)	Two year guarantee (optional extension up to four years)
Delta		
90° up to 20"	£26	£29
90° up to 22"	£30	£33
90° up to 26"	£32	£35
110° 26" (fast heat, narrow neck)	£33	£36
In Line & PIL		
Up to 20"	£36	£42
Up to 22"	£38	£44
Up to 26"	£40	£46

Please add £12 plus VAT for optional guarantee on any type of colour tube.

MONO TUBES (One Year Guarantee)  
A50-120W/R £12, A61-120W/R £13, Mono Portables £16  
All tubes exchange glass required.

### FOLLOWING ITEMS CALLERS ONLY

Solid state working colour TV's, with well view tubes fitted (1 year guarantee on tubes) from **Only £45**

Working TV Panels at Reasonable Prices

Your good, working tubes with scratches or small chips, can be **POLISHED** with our purpose built polishing equipment. **Only £7 per tube.**

Delivery Service up to 40 miles from Luton. Fixed Charge £3. \*Free Delivery for tube orders over £50 + VAT.

Please add 15% VAT to all prices. Callers welcome. Please phone first.

Send for a fully comprehensive price list and a wall chart of approx 1700 Colour Tube Types that can be processed by us.

## WELL VIEW

114-134 Midland Rd.  
Luton, Beds.

Open Mon-Fri 8am-6pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:

Retach Ltd., Northwood, Middx. Tel. 9684-27019  
West One Distributors Ltd., Chesham, Buckinghamshire. Tel. 0494-778197  
Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901  
Davenport Rentals, Daventry, Northants. Tel. 03272 77436  
S. and B. Electronics Services, Huddersfield, Yorks. Tel. 0484-36706

Please note that we have no connections whatsoever with any other business having similar name to ours.

## APOLLO

### HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Delivery 2-3 days.

Just phone for a quotation. Delivery Manchester area free same day. Two year guarantee. Fitting while you wait or in your home £20 extra. Also PIL types & Toshiba.

18"	A47 - 342x343x	£37.00
19"	A49 - 120x/192x	£37.00
20"	A51 - 220x/110x	£38.00
22"	A56 - 120x/123x/140x	£38.00
25"	A63 - 120x	£39.00
26x	A66 - 120xA67 - 120x/140x/150	£39.00

17" Ferguson Colour T.V.'s fully serviced, ideal as second set for kitchen, bedroom or caravan. **£75 inc. delivery** anywhere.

Philips Video Spares Available.

**061 799 0854 24 hour answering service.**  
43 Clarke Cres, Little Hulton,  
Nr. Manchester M28 6XM.

## M W ELECTRICAL

BROOK PARK AVE. (OFF MARINE RD.)  
PRESTATYN

"WE DO NOT BOOST TUBES"  
COLOUR TV'S


COMPLETE FROM **£10.00**  
TRADE WORKERS FROM **£25.00**  
MINIMUM OF TEN

G8, DECCA, BUSH, THORN. ALSO MONOS ETC.

NEW & GRADED TVs ALSO AVAILABLE

OPEN SAT MORN, LATE NIGHT THURS 8pm  
TEL: PRESTATYN (07456) 89849/89970

# NEW

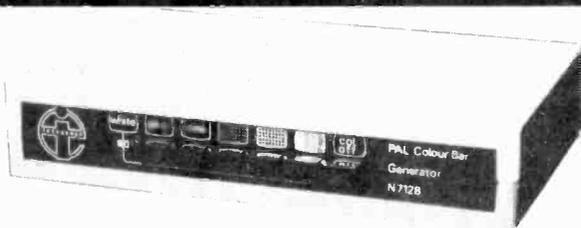

## N7128 COLOUR BAR GENERATOR

**New improved design with additional features.**

- ★ Six Standard Test Patterns viz. Colour Bars, Red Raster, Linear Grey Scale, Cross Hatch, Dots, White Raster.
  - ★ All monochrome patterns available with or without burst signal (for checking colour killer action etc).
  - ★ Crystal controlled sub-carrier, Line and Field frequencies.
  - ★ Three outputs to rear panel: Video at 1V P to P into 75ohm, 800Hz (approx), sine wave audio and modulated UHF (VHF available) 4mV at 75ohm.
  - ★ 6MHz (adjustable to 5.5MHz) intercarrier sound.
  - ★ Front panel LED to indicate "Power On".
  - ★ Integral re-chargeable ni-cad battery plus mains unit/charger.
  - ★ Fully built, tested and guaranteed for 12 months.
- PRICE £85.00.

## N7118 COLOUR BAR GENERATOR KIT

- ★ Five Standard Test Patterns viz. Colour Bars, Red Raster, Linear Grey Scale, Cross Hatch and White Raster.
  - ★ Crystal controlled sub-carrier, Line and Field Frequencies.
  - ★ UHF Output (VHF available).
  - ★ Integral Ni-cad Battery and mains unit/charger.
  - ★ Optional integral sound and video board add-on kits available @ £8.95.
- Still available at special price £39.95.

Please add 15% VAT + £2.05 postage and packing per Generator.

Please allow 14 days for delivery.



**INTRACEPT ELECTRONICS LTD., 203 PICTON ROAD, LIVERPOOL L15 4LG.  
TEL: 051-733 3042**

## TV LINE OUTPUT TRANSFORMERS

*FAST RETURN OF POST SERVICE*

### RANK BUSH MURPHY

Z146 A640 dual std mono	7.00
Bush A792, A793	
single std mono	7.00
A774 single std mono	7.00
A816 solid state mono	9.00

### DECCA

MS1700 2001 2020 2401 mono	7.00
MS2404 2420 2424 mono	7.00
CS1730 1733 colour	8.00
CS1830 1835 colour	8.00
'30' series Bradford colour	8.00
80 series colour	8.00
100 series colour	8.00

### FERGUSON HMV MARCONI

1600	9.50
------	------

### G.E.C.

2047 to 2105	7.00
2000 to 2064 dual std mono	7.00
DUAL STD hybrid colour	11.00
SINGLE STD hybrid colour	10.00

Indesit 20EGB 24EGB mono 9.00

### KB - ITT

VC200 VC205 VC207 mono	7.00
CVC5CVC7CVC8CVC9 col.	8.00
CVC20 series colour	8.00
CVC30 CVC32 series colour	8.00

**PRICES INCLUDE P. & P. & 15% VAT**

### PHILIPS

170 series dual std mono	7.00
210 300 series mono	7.00
G8 & G9 series colour	8.00

PYE I69-173-569-368 7.00

EKCO RV305-769-725-741 8.00

WALTHAM I25 9.00

**REWIND SERVICE** - available for most continental types i.e. Kuba, Luxor, Korting, Tyne, Berry Skantic, K80 £12. Old lopt required

## WINDINGS

### RANK BUSH MURPHY

T20a T22 Pry & Sec	6.00
Z718 series primary	6.00
Z718 series EHT overwind	7.00

### ULTRA THORN

I690 I691 EHT overwind	7.00
I590 overwind	5.00
I615 winding	7.50

### PHILIPS

G6EHT	8.00
G6 primary	6.00

### PYE

691 to 697 EHT overwind	4.00
691 to 697 primary	5.00

All lopts and windings are new and guaranteed

Open Mon-Fri. 9 to 5.30 pm  
Allow 1-2 days for delivery

**PAPWORTH TRANSFORMERS**

80 Merton High Street  
London SW19 1BE

SAE all enquiries  
Barclaycard and  
Access welcome



01-540 3955

For orders placed at the post office  
Trans  
cash  
506 4856

# ARE YOU

## USING YOUR SPARE TIME PROFITABLY?

If not, you're losing money. Money that you could be making by selling **used colour televisions from home** in the evenings. In fact, provided you start correctly and know exactly how to operate, you can easily earn a substantial CASH INCOME with a starting capital of less than £20. Our new unique publication "**How to Deal Successfully in Used Colour Televisions**" enables you to follow in the footsteps of many experts who have a great deal of combined experience in this lucrative home business, and who have 'pooled' their knowledge to help you. After all, to follow the advice of someone who has travelled the ground before you, is to be given the best possible start. And the hundreds of valuable trade secrets, hints, tips and suggestions in the guide show exactly how anyone of average intelligence can **succeed immediately**.

Every aspect, from securing the first television right through to rapid expansion of sales, is covered with the detailed knowledge of experts to ensure **certain success**. Indexed information on almost all makes of television is presented in clear tabular form, describing performance, reliability, price and service. In particular, the tips on expanding the business are very practical, and are almost automatic when put into practice. Pages of unique advice on advertising ensure that maximum sales are secured, and sources of supply are described in detail - for both televisions **and** new/used spares. Monochrome sets are also covered, as are "invisible" cabinet repairs. **Plus FREE on-going advice and FREE regular up-dating service.**

**You can start tomorrow - but you'll need our guide.** The latest big illustrated edition is out now, and costs just **£4.95** - a small price to pay for financial independence!

### ORDER TODAY FROM:

GLOBUS INDUSTRIES LTD., UNIT 18, DARLEY ABBEY MILLS, DERBY.

Please allow up to 28 days for delivery.

To: Globus Industries Ltd., Unit 18, Darley Abbey Mills, Derby.

Please send by return post "How to Deal Successfully in Used Colour Televisions". I enclose cheque/p.o. for **£4.95**.

NAME .....

ADDRESS .....

# MANTEL

**Manchester's No. 1 in Ex-Rental TVs**  
**Over 2,000 TVs in stock**  
**Special Offer on Working Colour TV's**

All sets are Serviced with repolished cabinets ready for sale

Some Examples of UNTESTED TVs available

Philips G8 550s 22/26 £45  
 Philips 18" £40  
 Philips G8 520s 22/26 £35  
 GEC S/State from £35  
 Thorn 17" 8000 £30  
 Decca 30 18/20/22/26 £30  
 Japanese from £30  
 Many other makes available from £25

Thorn 10 for £125  
 Philips 6 for £90  
 Bush 6 for £80  
 GEC 6 for £60  
 Decca 6 for £60  
 Mono TVs avail. s/s £4 each  
 New TV trolley stands.  
 All sizes £4.95  
 All Prices subject to V.A.T.

Discount on quantity

**Ex Equipment Panels & Tubes Available**

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

**419 Barlowmoor Road, Chorlton, Manchester 21 2ER.**

**Tel: 061 861 8501**

## SPECIAL OFFER SURPLUS STOCK TO CLEAR

AC127	0.150	BFX88	0.150	2N3771	0.900	741C8	0.150
AC128	0.150	BFY50	0.140	2N3772	0.950	NE555	0.180
AC187	0.150	BFY51	0.140	2N3773	1.000	LM3900	0.250
AD149	0.480	BT106	0.900	LM309K	1.000	7400	0.110
AD161	0.220	BT116	0.900	7805	0.350	7401	0.110
AD162	0.220	BT119	1.100	7812	0.380	7402	0.120
AF139	0.220	BT120	1.100	7818	0.380	7405	0.100
AF239	0.220	BU126	0.700	7824	0.380	7407	0.200
AU106	1.000	BU205	0.750	7905	0.350	7413	0.190
AU110	1.100	BU208	0.800	78L05	0.300	7414	0.260
BC107	0.070	BU208A	0.850	78L12	0.300	7425	0.110
BC108	0.070	BU326	0.850	78L18	0.300	7441	0.300
BC109	0.070	BU407	0.750	78L24	0.300	7442	0.300
BC147	0.055	BU526	0.800	25C495	0.700	7447	0.400
BC148	0.055	BY127	0.080	25C1306	1.000	7473	0.190
BC149	0.055	BY133	0.080	25C1969	1.300	7474	0.180
BC157	0.055	BY164	0.220	25C2029	1.200	7475	0.150
BC159	0.055	0A47	0.060	25C2078	1.200	7485	0.300
BD131	0.250	0C28	1.000	MB3712	1.500	7486	0.160
BD132	0.250	0C29	0.900	TA7205	1.500	7489	1.100
BD135	0.200	0C35	1.000	UPPC575	1.000	7490	0.220
BD136	0.200	R2008B	0.800	LM380	0.500	7493	0.250
BD137	0.200	R2010B	0.800	LM381A	0.600	74123	0.160
BD138	0.200	TBA520	0.750			74141	0.250
BD139	0.200	TBA530	0.750			74393	0.500
BD140	0.200	TBA540	0.750			74LS09	0.120
BD144	1.100	TBA550	0.750			74LS164	0.300
BD150	0.300	TBA560	0.700	VALVES		74LS197	0.350
BD157	0.380	TBA800	0.950	DY802	0.450	74LS221	0.420
BD158	0.380	TBA810S	0.900	ECC82	0.400	74LS240	0.580
BD159	0.400	TBA820	0.750	ECC83	0.430	74LS244	0.580
BD166	0.300	TBA920	0.800	ECC84	0.400		
BD175	0.300	TBA950	0.800	ECC85	0.400		
BD177	0.300	TBA990	0.800	ECH81	0.490		
BD179	0.320	TCA800	0.800	ECH84	0.520	8 PIN	0.070
BD181	0.450	TCA940	0.850	ECL80	0.570	14 PIN	0.080
BD433	0.320	TDA1170	0.900	ECL82	0.590	16 PIN	0.090
BD535	0.400	TDA2522	0.800	ECL84	0.570	18 PIN	0.120
BD536	0.400	TDA2530	0.800	ECL85	0.570	20 PIN	0.140
BD537	0.420	TDA2532	0.750	ECL86	0.490	22 PIN	0.160
BD538	0.420	TDA2540	0.700	EP80	0.310	24 PIN	0.180
BDX65	0.800	TD A2560	0.700	EP85	0.340	28 PIN	0.200
BF180	0.160	TD A2593	0.800	EP89	0.430	40 PIN	0.250
BF181	0.180	TD A2640	0.800	EY86	0.310		
BF194	0.050	TIP29	0.150	EY87	0.310	LED	
BF195	0.050	TIP41A	0.220	PC97	1.000	3mm Red	0.050
BF196	0.060	TIP42A	0.220	PCF802	0.570	3mm Yellow	0.100
BF199	0.060	TIP2955	0.340	PCL81	0.540	3mm Green	0.100
BF200	0.160	TIP3055	0.340	PCL82	0.700	5mm Red	0.050
BF258	0.180	2N3053	0.180	PCL84	0.500	5mm Yellow	0.100
BF337	0.200	2N3054	0.400	PCL85	0.550	5mm Green	0.100
BF338	0.200	2N3055	0.320	PCL86	0.550		
BF362	0.300	2N3440	0.580	PFL200	0.850	ELECTROLYTIC	
BFX87	0.150	2N3442	0.850	PL504	0.950	4700UF	
				PY500A	1.600	16V CAN	0.200

Please add 40p. P&P and VAT at 15%. Govt. Colleges, etc. orders accepted. Quotations given for Large Quantities. Please allow 7 days for delivery.

All brand-new Components. All valves are new and boxed.

**SUNMIT ELECTRONICS**

9 THE BROADWAY, PRESTON ROAD, WEMBLEY, MIDDLESEX, ENGLAND.

Telephone: 01-904 2093

## COLOUR SETS GALORE

Hundreds in Stock.

From £20. Guaranteed Complete.

Mono's and non-complete sets from £3.

Most makes available.

QUALITY COLOUR TUBES

Reconditioned and used tubes.

From £10 Guaranteed.

Don't delay, ring today.

**ALPHA TUBES (DUNSTABLE)**

53 Lowther Road, Dunstable.

Tel. (0582) 68934

TRADE

## THE NO. 1 SOURCE IN THE SOUTH

**GOOD STOCKS OF  
MODERN COLOUR  
UNBEATABLE PRICE AND QUALITY  
DON'T DELAY RING TODAY**

## TELETRADERS

ST. LEONARDS WAREHOUSE

ST. LEONARDS ROAD, NEWTON ABBOT, DEVON

Telephone: (0626) 60154

# COLOUR TELEVISION & MUSIC CENTRE

## WE HAVE MOVED TO A NEW WAREHOUSE

(NOTE NEW ADDRESS)

### 35 Stafford Road, Weston Super Mare, Avon.

(15 mins. past Bristol on M5)

**NOT EX-RENTAL**

## COLOUR TELEVISIONS

**SOLID STATE**

### ★ *FANTASTIC OFFER* ★

*All in perfect running order*

PYE CHELSEA

18", 6 Button, Sliding Controls,  
Brilliant Condition

**£39.50**

THE ABOVE ARE WORKS MODIFIED FOR MOST PARTS OF THE WORLD  
VHF - UHF

PYE 721

20"-26", could be mistaken for new

**£57.00 each**

PYE 725

20" as new

**£69 each**

*Minimum 5 sets*

★ ★ ★

BIG REDUCTIONS FOR EXPORT ORDERS OVER 100 SETS  
ALL OTHER MAKES IN STOCK OFF THE PILE

★ ★ ★

(G.E.C., SOLID STATE, FERG 9000 & 8500, G's, DECCAS etc.)

## Ring Now: W.S.M. 413537

# G.G.L COMPONENTS

108 SCOTLAND ROAD, CARLISLE, CUMBRIA CA3 9EY  
PHONE (0228) 20358/39693

ACCESS NOW AVAILABLE



(STOP PRESS)  
Hitachi and Sony tubes  
now rebuilt.

INTEGRATED CIRCUITS			TRANSISTORS			LINE O/P TR.		NEW VALVES										
TYPE	PRICE (£)	TYPE PRICE (£)	TYPE PRICE (£)	TYPE PRICE	TYPE PRICE	TYPE PRICE	TYPE PRICE	TYPE PRICE	TYPE PRICE									
LC7120	4.30	TBA480Q	1.40	TDA2591	2.50	AC127	22	BC184L	11	BF115	30	BU205	1.30	RBM T20/22A	11.85	DY802	72	
LC7130	4.50	TBA510	2.30	TDA2593	2.30	AC128	22	BC208	12	BF167	26	BU206	1.35	RBM Z718 18/20/22	22.95	PCF802	86	
MC1327A	1.00	TBA520Q	1.00	TDA2600	4.70	AC128K	30	BC212L	10	BF184	28	BU208A	1.40	PHILIPS G8	7.90	PHILIPS G8	78	
MC1358P	1.60	TBA530Q	1.00	TDA2611A	1.50	AC141K	30	BC213L	10	BF185	29	BU208/021.70	13.50	PHILIPS G9	8.75	PCL84	81	
MC1330P	0.90	TBA540Q	1.20	TDA2640	1.80	AC142K	30	BC214L	10	BF194/394.12	12	BU326A	1.30	PHILIPS G11	13.50	PCL805	90	
ML231B	1.95	TBA550Q	1.40	TDA3560	5.10	AC176	28	BC2378	11	BF195	13	BU407	1.12	THORN 1590/1	8.68	PCL86	81	
ML232B	1.70	TBA560Q	1.45	UPC1156H	2.95	AC176K	30	BC300	25	BF196	11	BU500	1.80	THORN 1690/1	9.68	PFL200	1.35	
MR475	2.00	TBA750Q	2.30			AC187K	30	BC303	26	BF197	11	BU526	2.00	THORN 1615	9.75	PL504	1.50	
SAS560S	1.65	TBA800	80			AC188K	33	BC337	11	BF198	14	BUW81A	2.80	THORN TX10	12.50	PL508	2.90	
SAS570S	1.75	TBA810AS	1.15			AD149	70	BC338	10	BF241	15	MJE340	40	PYE 731/713(110)	10.20	PL509/519	5.85	
SAS580	2.40	TBA820	1.40			AD162	42	BC547	10	BF258	25	R2008B	1.40	ITT CVC 1-9	9.60	PY88	69	
SAS590	2.40	TBA890	2.95	DIODES		AF126	38	BC557	10	BF259	26	R2010B	1.40	DECCA 2230	8.30	PY500A	1.90	
SL901B	4.80	TBA920Q	1.50	BA102	15	AF127	36	BC558	10	BF259	26	R2540	2.35	DECCA 80	8.58	PY81/800	69	
SL917B	6.40	TBA950/2X	2.15	BA115	14	AF127	36	BC558	10	BF259	26	R2540	2.35	DECCA 100	8.58			
SL1327Q	1.30	TBA990	1.55	BA154	07	AF127	36	BC558	10	BF259	26	R2540	2.35	DECCA 100	8.58			
SN7603N	1.80	TCA270SQ	1.30	BB105B	25	AU110	2.10	BD124P	55	BF338	30	TIP29C	45	GEC 2110	9.45	ANTI-SURGE FUSES		
SN76013N	1.80	TCA800	1.95	BB105G	25	AU113	1.85	BD131	33	BF355	32	TIP30C	45	ITT CVC 20	7.75	A/S20MM 80MA	2.75	
SN76023N	1.80	TCA940	1.55	BY127	10	BC107B	14	BD132	33	BF362	38	TIP31C	46	ITT CVC 25/30/32	8.00	100, 160, 200MA	1.70	
SN76110N	0.90	TDA1002A	1.50	BY133	15	BC108B	14	BD201	70	BF458	30	TIP32C	47			315, 400, 500, 630, 800MA,	1.20	
SN76226DN	1.45	TDA1003A	2.80	BY144	40	BC109B	14	BD202	70	BF459	36	TIP33B	46			1A, 1.25, 1.6, 2A	1.20	
SN76227N	1.00	TDA1004A	2.70	BY179	60	BC139	24	BD203	70	BF490	1.50	TIP41C	46			2, 3, 15, 4, 5A	1.35	
SN76666N	0.65	TDA1035	3.20	BY210/800	30	BC140	26	BD204	75	BF442	30	TIP42C	46					
SN76666N	0.65	TDA1044	3.10	BY223	82	BC142	23	BD232	50	BFX85	30	TIP295	70			A/S 1.25"		
TN7120P	2.00	TDA1170	1.80	BY227M	23	BC143	25	BD233	37	BFY51	22	TV106/02 1.60	4.25			250, 500, 630, 750, 1A, 1.25,	1.55	
TA7130P	2.00	TDA1212	90	BYX10	20	BC147	09	BD234	40	BR100	18	2N3054	55			1.5, 2A	1.55	
TA7193P	4.20	TDA2190	3.20	BYX10	20	BC148	09	BD235	42	BR101	32	2N3055	55			2.5, 3, 5A	2.40	
TA7205AP	2.80	TDA2020	2.95	BYX55/600	26	BC157	10	BD236	43	BR103	55	2N3703	12			(PRICES PER PACK)		
TAA550	28	TDA2522	1.80	BYX71/600	78	BC158	11	BD237	40	BT106	1.15	2N5496	50					
TBA120A	60	TDA2523	2.25	OA90	07	BC159	11	BD238	34	BT116	1.15	2SC1172Y	5.00			SUNDRIES		
TBA120AS	72	TDA2530	2.10	1N4001-7	07	BC160	22	BD410	50	BT106/2	1.58		1.85			PYE IF GAIN MOD	7.85	
TBA120B	90	TDA2532	2.20	1N5401-8	12	BC172	10	BD434	50	BT119	2.30	2SC2029	2.00			E/W COIL G11	1.65	
TBA120SB	90	TDA2540	1.95	1N5401-8	12	BC177	22	BD437	70	BT120	2.30	2SC2078	2.00			DECCA 2230	6.30	
TBA120U	1.00	TDA2560	1.80	Y969	85	BC182	10	BD438	78	BU105/02 1.44	1.25	2SC2091	1.10			DECCA 80	6.30	
TBA395	1.25	TDA2581	1.70	BZX61-range	18	BC182LB	11	BD707	1.05	BU126	1.25					DECCA 100	6.20	
TBA396	85	TDA2590	2.20	BZY88-range	11	BC183LB	11	BDX32	1.36	BU204	1.30					GEC 2001H	6.95	
																	ITT CVC 20/30	6.30
																	Universal	5.60

WE WILL ONLY SUPPLY TOP QUALITY, BRANDED COMPONENTS. REPUTATION COUNTS WITH US

**REBUILT TUBES**  
WE STOCK "TELETRONIC" TUBES (25 years in business)  
\*Carriage included. We can rebuild over 700 types of PIL tubes - List on Request.  
EXAMPLE PRICES:  
A56 120X ... £38.00\*  
A66/67 120X ... £45.00\*  
A61 120WR ... £23.00\*  
A66 510X ... 63.00\* available. Please ask for quotes.

TV ELECTROLYTICS	
DECCA 30(400/400)350V	2.55
DECCA 80/100(400)350V (800)250V	2.90
PHILIPS G8(600)300V	2.00
PHILIPS G9(2200)63V	1.15
PHILIPS G11(470)250V	2.20
PYE 691/7(200-300)350V	2.10
RBMA823(2500/2500)30V	1.10
THORN1400(150/100/100/100/150)320V	2.40
THORN3500(175/100/100/400)350V	2.25
THORN3500(1000)70V	85
THORN9000(400)400V	2.75

PUSH BUTTONS/TUNERS	
DECCA/ITT 4W	6.45
DECCA/ITT 6W	7.40
PYE201 6W	15.80
PHILIPS G8S/L	13.50
PHILIPS G8S/Q	12.00
HITACHI 4W	8.50
ITT CVC5 7W	9.40
ITT CVC8/9	12.80
PHILIPS G11 (TIP SW.)	23.80
1043/05TFK	7.95
U321 TFK	7.75
U322 TFK	7.40

THIS IS ONLY A VERY SMALL PART OF OUR RANGE, WE WILL BE DELIGHTED TO SEND DETAILS OF OUR WHOLE RANGE

**ORDERING**  
Please Add 50p For P/P U.K.  
Export Orders - Cost, Add 15% To This Total.  
**DELIVERY BY RETURN ON ALL STOCK ITEMS.**

**LEDU** multi-purpose illuminated magnifier

ONLY **£52.00** plus VAT

Please send LEDU illuminated magnifier/s at £59.80 each, inclusive of VAT. Total value £

\* Please debit my Philips Service account No. \_\_\_\_\_  
My Order number is \_\_\_\_\_

\* I enclose cheque made payable to PHILIPS SERVICE

Deliver to \_\_\_\_\_  
Address \_\_\_\_\_

Tel. No. \_\_\_\_\_

Signature \_\_\_\_\_ \* Delete as applicable

PHILIPS SERVICE,  
Commercial Sales Office, 604, Purley Way,  
Waddon, Croydon CR9 4DR  
Please allow 21 days for delivery.

Or order by ringing  
01 686 0505 ext. 240

Service PHILIPS

## MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

**Mail Order Protection Scheme**

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded.

# HUSSAIN CENTRAL TV

## Clearance deal to the trade

10,000, yes, 10,000 sets to be cleared at ridiculous prices in ones or hundreds, i.e. Pye 205 £3, GEC Hybrid £3, Philips G8 £5, and mono's £1.50.

Hundreds of modern sets at giveaway prices, i.e. Philips G11, G9, Grundig, Bush T20, Thorn 9800, Solid State ITT, Decca 100 and 80, etc.

Ring us today at our Birmingham depot:  
Phone 021 622 1023.  
Chepstow depot: 0291 26652.

## COLOUR T.V. PANELS AND SPARES

Fully refurbished and working with 90 day guarantee for most leading makes. Very competitive prices. Same day postal service.

S.A.E. for price list or telephone:

**JORDAN ELECTRONICS**  
113B Preston New Rd., Blackburn, Lancs.  
Tel: Blackburn 677824.

S.E. LABS OSCILLOSCOPE SM111. Dual Trace 20 MHz Portable .....	£225
COSSOR OSCILLOSCOPE CD110. Dual Trace 15 MHz .....	£150
METRIX WOBBLATOR type 210. 5-220MHz. With manual .....	£25
TELEPART SWEEP GENERATOR type SD3M. 440-920MHz with Fixed Markers .....	£50
Standard I.F. GENERATOR with 12 fixed IFs as used by TV Rental Companies .....	£35
RANK E.H.T. METER 0-30KV DC .....	£30
LABGEAR COLOURMATCH 625 PATTERN GENERATOR type CM6004-PG .....	£25
AVO TRANSISTOR TESTER type TT169 with leads. As New .....	£20
TAYLOR INSULATION TESTER type 130B. 500 Volts Max .....	£20
PYE SCALAMP ELECTROSTATIC VOLTMETER 5-18KV DC; 5-12KV AC .....	£20
METRIX WOBULOSCOPE 232 (Wobblator with built in tube) .....	£50
TRANSFORMER. Isolating. Tapped 115/240 Volts. 5.5 Amps .....	£15
TRANSFORMER. Isolating. Tapped 115/240 Volts. 2.8 Amps .....	£10
ADVANCE FM/AM SIGNAL GENERATOR SGB3A. 7.5-230MHz .....	£75
ADVANCE SIGNAL GENERATOR type 62. 150KHz-220MHz. CW/Mod .....	£30
MARCONI FM/AM SIGNAL GENERATOR TF995A/2M. 1.5-220MHz AM/FM .....	£225
Modulation .....	£25
MARCONI FM/AM SIGNAL GENERATOR TF1066B/1. 10-47MHz. Int & Ext AM/FM .....	£250
Modulation .....	£250

CARRIAGE ALL UNITS £7. VAT on TOTAL of GOODS & CARRIAGE. Many other items of Test Equipment, Computer Equipment & Components available. S.A.E. or Telephone for lists.

**STEWART OF READING**  
110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
Telephone: 0734 68041




Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive


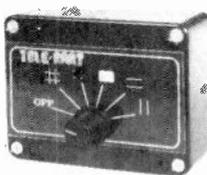
## TELEPART

13 WORCESTER ST.,  
WOLVERHAMPTON,  
WV2 4LJ  
Tel: (0902) 773122  
Telex: 336810




### Telepart Pattern Generator

- \* Exceptionally light and durable
- \* Pocket size for outside service
- \* PP3 battery power source
- \* Five different test patterns for colour and mono TV
- \* Cross hatch grid
- \* Dot matrix
- \* White raster
- \* Horizontals
- \* Vertices

A lightweight, extremely portable and versatile pattern generator for black/white and colour T.V. alignment and service at the customers home. At the turn of a switch, the generator can provide five essential test patterns for correct installation, fast checks and repairs. Pattern stability is first class and compares favourably with other more costly bulky generators only suitable for bench work. The generator is pocket size measuring 10x7.5x4 cm and weighs only 190 grams.

PRICE £14.95 (Subject to V.A.T.)

POST & PACKING £1.15

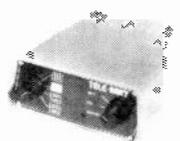

### Telepart Colour Bar Generator

- \* Exceptionally light & durable
- \* Compact 13x17.5x5.5 cms
- \* Battery powered for mobility
- \* Cross hatch grid
- \* White raster
- \* Grey scale
- \* Colour bars
- \* Sound

A Versatile Generator for Servicing or aligning mono or colour TV receivers. Lightweight and very compact for outside service. Features sound facility often not found on more costly generators.

PRICE £49.95 (Subject to V.A.T.)

POST & PACKING £1.15

### Power Supply

A Power Supply can be supplied for the Telepart COLOUR BAR GENERATOR. This compact unit mounts by 2 screws into the Battery compartment and converts the unit to a bench instrument.

PRICE £5.50 (Subject to V.A.T.)

Supplied by return, off the shelf

## 'DO IT THE FREEWAY'

All orders sent **POST FREE** by return

<b>LOPTS</b>		<b>PRESS BUTTONS</b>	
B +0 3000+3200 EHT	17.00	Decca 1730+20 Mono 4 way	6.60
B +0 3100+3300		Decca 1730+30+80+100 6 way	7.40
3400 EHT	19.50	GEC 2110 6 way	8.40
B +0 3100+3300		GEC 2136/7 6 way	8.00
3400	12.00	GEC 2112 +neons 7 way	12.50
B +0 3500+3600		GEC Conversion Unit	
4000+5000		2113+2119+2121+2144	
6000	11.50	2147+2148+2149	14.20
Decca 30	9.50	Hitachi 190 4 way	8.50
Decca 100	8.00	ITT CVC 5 7 way	10.50
Decca 1700	9.00	ITT CVC 8/9 6 way	12.50
Decca 1730+1830	9.00	ITT CVC 20+30+32 6 way	7.40
Dynatron TV202+203	11.00	ITT CVC 25 VCR 6 way	8.50
GEC 2623 Solid State	9.50	National TG85 4 way	8.50
Grundig 5010UE	12.00	Philips G8 520 Square	10.50
6010UE +2222	12.00	Philips G8 550 Stopping	16.50
Grundig 5010	12.00	Pye 713+715 4 way	8.00
Grundig 1500	15.00	Pye 715+207 Chelsea 6 way	12.50
Grundig 5010 EHT	19.50	Pye 725 6 way	13.50
ITT CVC 5	9.60	Rank A823 4 way	9.00
ITT CVC 25+30+32	8.00	Rank A823 6 way	12.50
ITT CVC 45	8.50	Rank T20A 6 way	9.50
Philips G8	8.50	Rank Z718 6 way	12.50
Philips G9	9.00	Salora 5 way	10.00
Philips 210 Mono	10.75	Salora 7 way	12.00
Philips 570	9.50	Skantic/Luxor 6 way	13.75
Pye 189+589+769	10.00	Telpro 4 way	10.00
Pye 691+697 PCB	14.25	Thorn 9000 Switchbank	7.50
Pye 713+715+717	9.50		
Pye 725	10.20	<b>TUNER</b>	
Pye 731+735+737+741	10.50	ELC 1043/06	6.00
Rank T20A	11.50		
Rank A774	11.00	<b>CAPACITOR</b>	
Rank Z718 18"	23.00	G11 470mf/250v Elco	1.60
Rank Z718 20+22+26"	23.00		
Rank Mono Portable 14"	9.50	<b>INTEGRATED CIRCUITS</b>	
Tandberg 110°	11.25	TA7607AP	Pack of 10 5.00
Thorn 1590+1591	10.90	TAA550	Pack of 10 1.50
Thorn 1615	9.00	TDA2540	Pack of 5 5.00
Thorn 1690+1691	8.50	TDA9513	Pack of 10 5.00

Add 15% V.A.T. and send cheque or P.O. to:

### FREEWAY COMPONENTS

The Airport, Weston Super Mare, Avon BS24 8RA  
Tel: 0934 419147

## UNIVERSAL PROGRAMME SELECTOR FOR VARICAP TUNING

UK Regd. Design No. 1006611


6 way interlocked d.p. switch 100 K tuning potentiometers  
Top quality through hole plated pcb

Dimensions: 5" by 2½" by 1"  
Ideal for replacement when original parts are obsolete or unobtainable

Template guide supplied for drilling of your own fascia design

Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification

All orders despatched same day

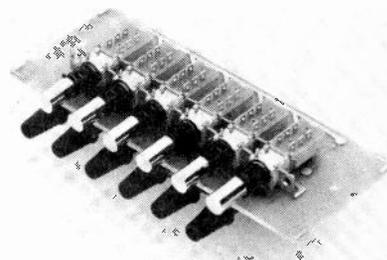

### DIRECT REPLACEMENT FASCIA/MOUNTING KITS

Type 30-80 Replaces 7 piano-key unit as fitted to Decca/Telefunken 30 and 80 chassis

Type 30-C Replaces 7 piano-key unit as fitted to Decca console using long perspex illuminated control panel

Type 100 Replaces 8 position touch tune selector (AEG SAS 660 SAS 670) as used in Decca/Telefunken 100 chassis

Type CVC8-9 Replaces 5 rectangular push button plus thumbwheel as used in ITT

SELECTOR **£11** + VAT

FASCIA/MOUNTING KITS (each) **£2** + VAT

**ALDERSON-JAMES LTD**

160 KINGS ROAD ● HARROGATE ● N. YORKS

TEL: HARROGATE (0423) 60058 HG1 5JG

## CENTREVISION

NO. 1 IN WALES

9000 Sq Ft

2000+ CTV

- ★ DECCA 18" £20 + VAT
- ★ KORTING 22-26 CTV £15 + VAT
- ★ HITACHI CTV FROM £32 + VAT
- ★ THORN 9000 20" £48 + VAT
- ★ RANK Z719-Z718-T20 VARIOUS PRICES
- ★ PHILIPS 550 22" REMOTE £35 + VAT
- ★ GEC SOLID STATE FROM £32 + VAT
- ★ THE TRADE SAY THE BEST QUALITY SETS ON THE MARKET TODAY
- ★ BULK TERMS TO OTHER WHOLESALERS
- ★ ALSO PANEL'S-STANDS AND TUBES IN STOCK

DECCA 30 SERIES 22" IN 10'S £18

SELECTION OF WORKING SETS  
DONT DELAY PHONE TODAY

0222-44754

**CENTREVISION HOUSE,**  
SLOPER ROAD,  
CARDIFF CF1 8AB.

### HIGH GAIN AERIAL BOOSTERS

**B45 H/G UHF Television** – Tunable over the complete UHF band. Gain above 20dB, noise 2.8dB.

**B14 – Band 3 VHF Television** – Tunable over the complete Band 3 (Channels (E) 5 to 13). Also covers Aircraft & 2 meter Amateur Bands. Gain above 28dBs. Noise 2.8dB.  
**PRICE each £8.70.**

### AERIAL AMPLIFIERS

Aerial amplifiers can produce remarkable improvement on the picture and sound in fringe or difficult areas.

**B45** – For Mono or Colour this is tunable over complete UHF television band.

**B11** – For stereo or standard VHF/FM radio.

**B12** – for VHF television band 1 & 3. All amplifiers are complete and ready to use Battery type PP3 or 8V to 18V DC next to the set type fitting.

**PRICES £6.70 each.**

### AERIAL SPLITTERS

2 way T-TYPE **£2.70 each**

Goods despatched on receipt of order.

All Prices Fully Inclusive. P & P per Order 30p. S.A.E. for Leaflets. Access Cards.

**ELECTRONIC MAILORDER LTD,**  
62 Bridge St, Ramsbottom, via Bury, Lancs. BL0 9AGW.  
Tel Rams (070 682) 3036.

# NO!

If you see an advertisement in the press, in print, on posters or a cinema commercial which you find unacceptable, write to us at the address below. (TV and radio commercials are dealt with by the I.B.A.)

**The Advertising Standards Authority.** ✓  
If an advertisement is wrong, we're here to put it right.

ASA Ltd, Brook House, Torrington Place, London WC1E 7HN.

# VISIONTEL

**BEST QUALITY EX RENTAL SETS FROM  
£10 HERE IN CENTRAL LONDON!**

**Hundreds of sets always in stock  
AT VERY COMPETITIVE PRICES**

**For Example:**

Philips G8  
Philips 550  
Thorn 3500

**Untested**  
£15  
£20  
£10

**Good Workers**  
£25  
£35  
£25

ALL PRICES SUBJECT TO VAT

**We also have PYE, DECCA, GEC, ITT, GRUNDIG, JVC,  
PHILIPS G9 + G11, THORN 9000 and PORTABLE TVs**

**FOR FURTHER DETAILS TELEPHONE 328 3787  
OR COME ALONG TO  
55 KILBURN HIGH ROAD, NW6**

## TVs TVs TVs

### PANELS PANELS PANELS

DECCA 18" 20" 22" 26" from £25	BUSH A823 22" 26" from £25	
PHILIPS G8 22" 26" from £25	HITACHI 18" POA	
PHILIPS 570 18" from £35	THORN 3500 20" 22" 26" from £25	
PYE CT200 18" from £35	THORN 8800 22" from £30	
PYE CHELSEA 18" from £40	ITT CVC8 22" from £40	
NAT. PANASONIC 18" POA		

*The above prices are for working TVs. Non workers usually available. Please ring for prices.*

**QUANTITY DISCOUNT FOR 10+**

Panels for most makes available with 3 month guarantee.  
Add £1.70 per panel for postage + 15% VAT.

(Also see N.J. Electronics advertisements, all your TV spares panels etc. under one roof.)

### CONTRAST U.K.

82/83/84 STORFORTH LANE TDG. EST. CHESTERFIELD, DERBYSHIRE S41 0SW  
Tel. Chesterfield (0246) 209061

## TELEVISION TUBE SHOP LTD

BRAND NEW TUBES AT CUT PRICES

A31-19W/20W.....19.95	230DB4CT468.....31.00
A31-120W/300W.....17.95	240DB4/240AB4A....22.00
A31-410/510W.....17.95	CT507 equiv.....21.95
A34-100W/510W.....18.50	310DGB4/DMB4.....23.00
A34-514W.....24.25	310EUB4.....19.95
A38-160W/170W.....17.50	310EUB4A.....18.50
A44-120W/R.....25.00	310EYB4.....18.75
A50-120W/R.....19.00	310FXB4.....17.50
A61-120W/R.....21.00	310GNB4A.....31.00
9AGP4.....£21.82	310HCB4.....31.00
190AB4/C4.....23.00	340AB4.....22.50
	340AYB4.....30.00
	340AXB4.....30.00
	340RB4/CB4.....26.00
	340AHB4.....26.00
	RIGONDA 6".....14.00

**Some Rebuilt Japanese  
& European Types  
Available from  
£14.00 +VAT £2.10**

### COLOUR TUBES

(NEW & MULLARD/THORN COLOREX)\*

12VARP22.....£62.50	A56-120X.....£54.00
330AB22.....73.50	A56-410X.....64.00
A44-271X.....60.00	A56-500X/510X.....63.00
A47-342X.....61.00	A63-120X.....63.00
A47-343X.....61.00	A66-120X.....65.00
A49-191X.....53.00	A66-140X/410X.....70.50
A51-161X.....70.00	A66-500X/510X.....65.00
A51-220X.....55.00	A67-120X.....65.00
A51-500X/510X.....64.50	A67-140X/200X.....69.50
A51-570X.....73.00	A67-150X.....75.00

*\*Old Bulb Required for 110° Colorex\*  
ADD 15% VAT TO ALL THE ABOVE PRICES.*

**ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED  
TELEVISION TUBE SHOP LTD  
52 BATTERSEA BRIDGE RD., LONDON, SW11.  
Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10.**

## PRECISION VISION LTD.

*For modern used colour TVs.*

Working or untested. Most makes and tube sizes available. All working TVs are refurbished to an extraordinary high standard.

0865-750212

HEAD OFFICE

MANOR BUILDINGS

67 LONDON RD

HEADINGTON,

OXFORD

01-200 7337

LONDON BRANCH

21 COLINDALE AVE

LONDON NW9

## SETS & COMPONENTS

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO. 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

Northwood Middx (9684) 27019 01-845 2036

### RETACH LTD.

Rear 78 High Street, Northwood, Middx.

LOOK G11 PHILIPS (inline tube) ..... £75

Also:

PHILIPS G8 550 (22 Slant Button) ..... £35

PHILIPS G8 520 (22 Flat Button) ..... £25

PHILIPS G8 522 (26 Flat Button) ..... £18

PHILIPS G8 526 (26 Slant Button) ..... £25

PHILIPS G9 585 (26 Remote) ..... £35

RANK T20/22 Series (Incline Tube) ..... £75

RANK 823 (White Stocks Last) ..... £10

RANK 718 (Incline Tube) ..... £45

THORN 9800 (Incline Tube) ..... £55

MONO:- PYE T184-24" Mono (Solid State) ..... £18

VIDEO's:- PHILIPS N1700, N1702, videos ..... £39

TUBES:-

20" Rebuilt Colour Tube, 2yr Guar. .... £29

22" Rebuilt Colour Tube, 2yr Guar. .... £33

26" Rebuilt Colour Tube, 2yr Guar. .... £35

All Prices+VAT - Callers by Appointment

GRUNDIG NORDMENDE Spares panel exchange service. Complete sets. Circuits, 0785 814643 anytime.

NEW SUSSEX WAREHOUSE, Trade Televisions. Colour from £10, mono £3. Tel. Brighton 673482

# TELEVISION

JAPANESE COLOUR TVs, Hitachi, Sony, Panasonic, Mitsubishi, Toshiba, Sharp. Colourland TV. Trade Only. 0484 863489.

PHILIPS 550s (Mark 5/Twin Panel/VCR Button) excellent cabinets. Regular supply of working sets. Box T.V. 181.

### TOSHIBA 110° PIL TUBES 20" 22" 26"

20" 510 KCB 22 ..... from £20

22" 560 HB22 ..... from £20

560 TB22 ..... from £20

560 AKB22 ..... from £20

26" 670 XB22 ..... from £20

RING JEFFRIES 01-845 2036

### TRADERCO SUSSEX

Main CLEARANCE CONTRACTOR TO RENTAL COMPANIES. Colour Televisions seen working from £19 - Untested from £9.00. Sets for spares from £4. Exchange panels from £3. Untested Mono's from £2.

TELEPHONE RAY ODELL,  
'TRADERCO' BRIGHTON 38552.

## SUMMER SALE

G8's ..... £8  
Decca Bradfords ..... £6  
Pye Hybrids ..... £5  
Mono, 12 sets for ..... £20  
Philips 1700 Videos ..... £20

PLUS MORE

### SOUTH LONDON TELEVISION

45 Griffiths Road, SW 19.  
Telephone: 01-543 5437.

ISOLATION TRANSFORMERS three 70W 240V outputs (210W parallel) ideal for isolating test equipment £5 + £2.85. Working test equipment, meters, PSU's etc. S.A.E. lists. S.H.E. 5 St. Joseph's Park, Ballycruttle, Downpatrick BT30 7EN.

# SUFFOLK TUBES LIMITED

214 Purley Way, Croydon, Surrey.  
Tel: 01-686 7951/2/3/4

SUPPLIERS OF MONO AND COLOUR TUBES TO MAJOR RENTAL COMPANIES.

ALL COLOUR TUBES HOT PUMPED AT 385c AND REBANDED TO BRITISH STANDARD. 415 1972 CLAUSE 18-2.

19" and 22" TUBES APPROVED. OTHER TYPES PENDING.

BRITAINS LARGEST INDEPENDENT REBUILDER FOR 21 YEARS.

### CAMPBELL ELECTRONICS LTD.

Distributors of specialist spares to radio and television service depts.

We stock semiconductors, I/Cs, special T.V. and audio spares, service aids, rebuilt CRTs etc.

Fast off the shelf delivery of stock items.

Send S.A.E. or telephone for full catalogue and price list.

### CAMPBELL ELECTRONICS LTD.,

Unit 5, Heath Hill Estate,  
Dawley, Telford, Shropshire.  
Telephone Telford (0952) 502422.

### RANK BUSH MURPHY TV PANELS

Repair, exchange, sale service, same day return where possible. 718 chassis lopt panel charges reduced. Also new boards available for T20/22 chassis. Genuine RBM technology.

#### T. K. Panels Service,

31 Bronte Paths, 41, Willesden Lane,  
Stevenage, Herts. Kilburn, N.W.8.  
Tel. (0438) 61567.



\* Britains most reliable source of quality TVs.

\* Hundreds of working polished TVs.

\* New adjustable TV stands.

Krystal Marketing  
Breadon Cross Storage  
Dale Road, Selly Oak,  
Birmingham B29 6AQ. Phone 021-471 3023  
Telex 335540-G  
Ask for Les

### WIZARD DISTRIBUTORS MANCHESTER

SPECIALIST DISTRIBUTORS TO THE TRADE OF T.V. & VIDEO SPARES.

WE STOCK A FULL RANGE OF PARTS & COMPONENTS INCLUDING C.R.T.'s

RANK - THORN - PHILIPS - ITT - DECCA - GEC ETC.

THANDER & LEADER STOCKIST  
TRADE COUNTER OPEN: 9-4.30

CATALOGUE ON REQUEST.

Mail Order Enquiries Welcomed

EMPRESS STREET WORKS,  
EMPRESS STREET,  
MANCHESTER M16 9EN.  
TEL: 061-848 0060

## TRADE TV's

For the best quality at the cheapest prices in Nottingham.

### CASTLE TV

100s of ex-rental sets in stock.

S/S colour from ..... £12.50

S/S mono from ..... £3.00

TV Sales & Spares to the Trade.

346 Radford Road,  
Nottingham.

Tel. Mr. Atkins  
Nottingham 785321.

### COLOUR TV PANELS Fully Tested & Working

	IF	CDA	Decoder	LTB	Line Board	Frame Board	Power
GEC 2040	3.50	3.50	4.00	5.00	-	-	-
DECCA 13/30	3.00	-	5.00	5.00	-	-	4.00
BUSH 'A'	2.00	-	5.00	5.00	2.50	-	2.00
THORN 8-8½"	-	-	7.00	5.00	-	-	3.00
PYE 205	3.00	3.50	5.00	8.00	-	2.00	-
THORN 3+3½K	3.00	-	5.00	8.00	-	-	10.00
G8	6.00	-	8.00	5.00	15.00	-	5.00
BUSH twin chip decoder	10.00	-	-	-	-	-	-

Post & packing: 1 panel £1.50; 2 panels £2.25; 3 panels £3.00 etc.

Hybrid panels do not include valves.

Terms cash with order.

26" CRT's fully tested £10

fitted with brand new transformer

### LAVITE LTD.,

Viaduct Mills, Milnsbridge, Huddersfield. Tel: 0484-643273

Callers by appointment only.

# SERVICE PAGES

## IRISH T.V. DEALERS

(No. 1 for s/hand T.V.s)

1. 400 sets to choose from.
2. Most leading makes sold.
3. Fresh stocks weekly.
4. Delivery to any part of Ireland.
5. All sets with VHF/UHF tuners.
6. Colour from only £70 mono from £15.

Visit our new spacious warehouse:

**TELE SPARES LTD.**  
Unit 113 Elm Road, Western Ind. Estate,  
Dublin 12.  
Tel: 01 521756/521211.

Thorn 3000/3500  
Thorn 9000  
**UNIVERSAL**  
1 year guarantee

**TRIPLERS**  
**£4.50** inc. p.p.

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

**WING ELECTRONICS**  
15 Waylands, off Tudor Rd, Hayes End, Middlesex

**CAMPBELL ELECTRONICS LTD.**  
COLOUR T.V. PANEL EXCHANGE/  
REPAIR SERVICE

THORN, RANK, PHILIPS, GEC,  
DECCA, TELPRO, GRUNDIG etc.  
90 Day Guarantee on all repairs – same  
day postal service.

Telephone Telford (0952) 502422  
for catalogue and price list.

**CAMPBELL ELECTRONICS LTD.,**  
Unit 5, Heath Hill Estate,  
Dawley, Telford, Shropshire.

### BULK BARGAIN T.V. SERVICE PACK

Contains at least £50 worth of T.V. service components and accessories. Loads of hard to obtain T.V. spares and components. Ideal for the service engineer. Only £12.50, carr. £2.50. Ref. Guar. HAVE YOU SEEN THE GREEN CAT? 1000s of new components, T.V., radio, and electronic items at unbelievably low prices. Probably the cheapest in the country. Send 40p for GREEN CAT and reserve FREE RECORD SPEED INDICATOR.

**MYERS ELECTRONICS, Dept. TV2,**  
12/14 Harper Street, Leeds LS2 7EA.  
Next to Union Jack Clothing Store, Leeds LS2 7EA.  
Callers welcome at our NEW retail premises.  
Open 9 to 5 Mon to Sat. Tel. 452045.

### TVDX/SATELLITE EQUIPMENT

VHF to UHF Converter. 12v supply required. Ideal way to start DXing £13.95. Band I/II Mosfet mains preamplifier. High gain, low noise £27.50 (Bill available). **SOON TO COME** complete 4GHz LNA/downconverter for satellite reception £200 (approx.).

SAE data lists:

**H. COCKS**

Cripps Corner, Robertsbridge, Sussex TN32 5RY.  
Telephone 058083-317

### OUTSTANDING VALUE ON PROJECTION T.V.

## SHARP XV720

DUE TO A BULK PURCHASE ON THE CONTINENT WE ARE ABLE TO OFFER THE SHARP XV720 3 TUBE PROJECTION T.V. WITH 72" HIGH GAIN SCREEN & STAND AT AN INCREDIBLE SAVING OF £1,300 ON THE NORMAL LIST PRICE.

- ★ High quality unit beautifully finished.
- ★ Superb 72" Screen and Stand.
- ★ 3-Tube System with Mitsubishi Schimdt optics for superb definition and brightness.
- ★ VHF/UHF Tuners fitted: Remote Control.
- ★ High quality 10w Sound Channel converted to 6mz. for U.K. use.
- ★ Direct Video/Audio In/Out facility.
- ★ Built in Cross Hatch. Easy stable convergence
- ★ Full Warranty and Spares Back up.
- ★ Ideal for Schools & Colleges, Pub's, Club's, Residential homes, Training & Education in Industry and Commerce. Also Computer and Text and many other applications.

LIST PRICE £2,895 + V.A.T.

**SPECIAL OFFER PRICE £1,595**

+ V.A.T. + £50 carriage to any address in U.K.

TRADE ENQUIRIES ALSO INVITED

Contact Mr. J. A. ORR

**TELEVISION & ELECTRONIC SERVICES**

(The Big Screen Specialists)

98 BOTANIC AVENUE, BELFAST BT7 1JR  
NORTHERN IRELAND. TEL: (0232) 230958

## BARRY TV SERVICES

(EAST ANGLIA)

Your friendly wholesalers. We cater for the smaller dealer who requires regular small supplies of quality used colour TV's. From £25 + VAT. Fully working with good tubes and cabinets, straight from our retail shelves, ready to sell or rent.

Delivery available

Contact John, Dave or Steve on  
Ely 61462  
or Cambridge 69215

### WE HAVE MOVED TO NEW PREMISES TEST EQUIPMENT

UHF T.V. Pattern Generators  
Crosshatch & 4 patterns **£17.25**  
As above but with Greyscale **£18.50**  
Prices include P&P and VAT.

Also available:

PAL COLOUR BAR GENERATOR  
CAPACITANCE METER  
TRANSISTOR TESTER

S.A.E. for prices and full details.

The above items are not kits.

**C.M.J. ELECTRONICS**

Unit 8, 16 Union Mill St., Horseley Fields,  
Wolverhampton, WV1 3DW.  
Tel. (0902) 871563

## ARE YOU OVERSTOCKED?

Turn your surplus stocks into cash

**£500,000 AVAILABLE**

for any surplus electrical stocks ie. TV's,  
Video's, Washers etc.

Phone in strictest confidence:

Mr R. Walker,  
**Bradford (0274) 688458**

## TELEVISION TUNER REPAIRS ALL TYPES

BRITISH, EUROPEAN  
JAPANESE ETC.

**MEN-TU ELECTRONICS LTD.**  
SALTERNS LANE,  
FAREHAM, HANTS.  
Tel: 0329-235116

# N.W. ELECTRONICS

## New Modern Warehouse Now Open!!

WHARFEDALE ROAD, EUROWAY ESTATE, BRADFORD  
[M606 DIRECT LINK M62] TELEPHONE [0274]688458

## 100's of Colour T.V.'s at Special Opening Prices

BUSH 22" COLOUR T.V.'s ONLY £8.00 (min quantity 5)  
PHILIPS G8 ..... ONLY £15.00  
THORN 3500 ..... ONLY £10.00  
BUSH P.I.L. TUBES ..... ONLY £35.00 (Repos.)

## Full Spares Back-up on all Models & Makes

★★★★ Delivery arranged anywhere ★★★★★



Makes in stock include Hitachi, Sanyo 9000, G.E.C., Pye 223, Grundig, Bush etc., etc.

All T.V.'s sold complete, untested (Test bench Available)

We also supply new goods from Pye, ITT, Thorn, Amstrad.

Washers and Fridges by Bendix, Zanussi, Tricity, Candy etc.

LARGE SELECTION OF WASHERS FOR RECONDITIONING ...  
TWINs, AUTOS ETC.,


LARGE QUANTITY OF CYLINDER CLEANERS FROM £2.00

"Pay us a visit - you will not be disappointed"

★★★★★ Discount on Quantity Loads ★★★★★

(Sorry - Cheques not accepted)

You Can Reach Us Easily From Anywhere.

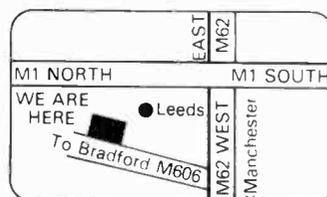

UNIT 1, WHARFEDALE ROAD,  
M606, EUROWAY ESTATE,  
BRADFORD.

[0274] 688458

## COLOUR TVs WORKING

MINIMUM OF 5

THORN

3000 19 inch  
3500 22 inch  
8500 19 inch  
8000 17 inch

FROM £30

8800  
9000

FROM £39

123 PALMERSTON ROAD, BOSCOMBE,  
NR. BOURNEMOUTH, DORSET  
TEL: 0202 721145

## RANK BUSH MURPHY TRANSFORMERS

LINE OUTPUT TRANSFORMERS

Z718 (T703A, T706A)

(1) New (Complete) £20.50

(3) Less Focus Module and  
Rectifier £10.50

Z718 SPARES (T703A, T706A)

Pri. - £5.50, Sec. - £6.00,

Rectifier - £3.00, Lead - £2.50

T20, T22 (T705A) £9.00

T26 (T705B) £9.50

Switch-mode Transformers

T114 A/B £8.00

Genuine RBM Units

Prompt Postal Service.

Add 15% V.A.T. to all Prices.

DISCOUNT For QUANTITIES

WOODSDALE COMPONENTS

MR SKEHAN

34 Field End Road, Eastcote,  
Pinner, Middlesex HA5 2QT.  
01-868 5580

Agents Office, callers by appointment only.

## TELEVISION

Trade Supplies of Good  
Quality Colour & Mono  
TV's. Most Makes  
available, suitable for  
Sale or Re-Rent.

GENERAL  
FACTORS

UNION STREET,  
DONCASTER  
(0302) 49583-68416

GOOD MOTORWAY ACCESS

## ★ TELEBEST ★

We specialise in quality  
working sets.

Trade enquiries only  
Philips + Thorn 22"  
From £30 incl. VAT.

Discount on quantity.

841 Romford Road,  
Manor Park,  
London E.12.  
Tel: 01-514 1333.

Cut Out and Keep



# TUBES £30

INCLUDING VAT

## REGUNS ONE YEAR GUARANTEE

A56-120 A51-110  
A49-191 A47-342 or 3  
A44-270 A67-120  
A66-120 or 140 (26" add £5)

In line Tubes 51-161 £48

Sony up to 19" £65 Others £85

Add £5 per tube for quick insured delivery. No need to spend £5 returning old glass if you buy from us (except in-line).

**U-VIEW (TUBES), 29, WARMSWORTH ROAD,  
DONCASTER, YORKS. DN4 0RP. TEL 0302 855017.**

Callers ring first. Open every day, including Sunday.

## LINE OUTPUT TRANSFORMERS G8 DECCA BRADFORD - STATE MODEL

**£8.95** INCLUDING VAT  
& FAST DELIVERY

G9 or ITT CVC5 £9.95  
Pye 731 £10.50  
Rank T20 £11.95  
Mono Thorn 1615 £9.95  
1690 £8.95

One Year Guarantee

## T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537  
194, Acton Lane, London W.4.

## The VINTAGE

### WIRELESS COMPANY

NOSTALGIA-COLLECTING  
1900-1950s

Publishers of 'The Antique Wireless Newsheet'  
(Sample on Request)

Suppliers of: • Valve Radio sets  
& Amplifiers



- Valves, Components
- Repairs & Restorations
- Service Data & Manuals
- Historical Data
- New and Used Books/Magazines

The complete service for the collector and enthusiast  
of Vintage Radio.

THE VINTAGE WIRELESS COMPANY

64 Broad Street, Staple Hill, Bristol BS16 5NL  
Tel: Bristol (0272) 565472 - 24hour Ansaphone, Closed Mondays.

# CLEARANCE SALE

LARGE QUANTITY OF GOOD CLASS

## COLOUR TELEVISIONS

BUSH, PYE, GEC, THORN, PHILIPS ETC.

Excellent Cabinet Condition.

Genuine Change Over TV's and Repossessions.

## LARGE QUANTITY SOLID STATE BUSH £10 Each

(Minimum quantity 5)

GEC HYBRID  
£5

PYE HYBRID  
£5

MONO  
£3

100's to choose from!!

We export large quantities of TV's weekly. Can we help you?

Discount on Quantity Orders.

OVER 1,000 MONO TV's IN STOCK FROM £3.

100's colour tubes suitable for reconditioning. Working colour TV's to order ie.

Bush 20"/22" 21.C. excellent picture, ready to sell. Only £39.

CALL AND SEE OUR SELECTION

## WHITE GOODS

All types of Washing machines, Vacs, Fridges, Cookers, etc. Hoover Auto's, Servis,

Hotpoint, Hoover Uprights, Vacs. 500 always in stock. Fully reconditioned Hoover

Twin Tubs and Upright Vacs, all models. Phone for details.

PAY US A VISIT AND YOU WILL NOT BE DISAPPOINTED.

# N.W. ELECTRONICS

UNIT 1 WHARFE DALE ROAD EUROWAY ESTATE (M606) BRADFORD  
(M606 Direct Link M62) Telephone Bradford 0274-688458

## SERVICE SHEETS

### 30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £3.00. Tuners £3.00. Tape Recorders, Record Players £3.00. Transistors £3.00. Car Radios £3.00 + SAE. Stereograms & Music Centres £3.00. Radiograms £3.00. Also Colour available. State if circuit will do if sheets are not in stock. All TV Sheets are full length 24 x 12 not in Bits & Pieces. All other Data full lengths. All Sheets £3 except colour. SAE please. Old Valve Radios £3 + SAE 9 x 3.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX.

(MAIL ORDER)

## SANDHURST PUBLICATIONS

Television Service Sheet Specialists  
Workshop Manuals, large selection of  
Japanese and European TV Sheets. Callers  
5.30-7.00 pm. Upper Floor. Send S.A.E. for  
Catalogue and Enquiries:

49C Yorktown Road,  
Sandhurst, Camberley, Surrey GU17 7AG.

## TECHNICAL INFORMATION SERVICE

SERVICE SHEETS: full size by return - radio, mono, etc. £2 + large sae. CTVs & Music Centres from £3.

SERVICE MANUALS: Sole suppliers most obsolete equipment. Everything stocked to latest releases. Fantastic stocks  
CTVs/Videos. E.g. A823 £6.50; Autovox (early) £6.50. Tyne 5000/6000 Series £7.50.

COMPREHENSIVE TV REPAIR COURSE - Complete data almost every fault. - Huge beginners section. - Only £8.50.

TV REPAIR MANUALS - All 12 for £75. - Mono portables (new) £6.50. - Early VCR, £10.50.

CIRCUIT DIAGRAM COLLECTIONS IN HUGE BINDERS: British CTV (3) £42.50; Foreign CTV (2) £27; Early VHS/Phillips video  
£15; Mono TV standard + portables £29.

REPAIR SYSTEMS (REPAIR DATA, CIRCUITS, ETC): Video 1, £24.50; Foreign CTV, £40; Mono TV, £31.50.

SAVE £12 - BRITISH CTV ONLY £60 - LIMITED TIME; Complete integrated TV Repair System £160.

Quotations/free 50p magazine/price lists/etc for large see.

£2 plus 8" x 10" S.A.E. for service sheet and manual catalogues with £4 vouchers.

PHONE 0698 883334 FOR FAST QUOTES - Open 4-6 daily, 11-1 weekends.

T.I.S., 76 CHURCH ST., LARKHALL, LANARKSHIRE ML9 1HE.

## SERVICE SHEETS CONTD.

**BELL'S TELEVISION SERVICES** for service sheets on Radio, TV, etc. £1.25 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

## WANTED

**WANTED.** 9 volumes of the magazine "Television" 1974 to 1982/3. Also colour bar generator. Welcome calls from anywhere in UK. Tel. Sylvester 061747 4192.

**WANTED "TELEVISION" FROM 1975 TO 1982,** state months available and price per copy. T.J. Maccrossan, Newtown Cunningham, Donegal, Eire.

**PHILLIPS, G8, G11 REQUIRED,** working or not, must be good cabinets. Regular supply required. Notts/Derby. Ripley 811124.

**WANTED PHILIPS/PYE G11** Colour TVs, any quantities. Hornchurch 58513, Mr. Morris.

**WANTED OSCILLOSCOPE WORKING** (Midlands preferably) Dual/Single Beam. Cheap price negotiable. Leicester 865457.

**INVALID HOBBYIST REQUIRES** Finlux Peacock Lopt and/or set suitable spares. Box 180.

**WANTED FOR CASH.** Video, TV's, spares, electronic components. Tel: 965 1230. Box No. TV 175.

## BOOKS & PUBLICATIONS

**COMPLETE FULL-SIZE SETS** any published service sheets £2 + LSAE except CTVs/Music Centres from £3 + LSAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications for sale. Repair data/circs almost any named TV/VCR £8.50 by return. TIST, 76 Church Street, Larkhall, Lanarks ML9 1HE. Phone (0698 883334).

**"RADIO AND TELEVISION SERVICING"** books, new editions for the last 6 years always in stock. Prices on request. Bells Television Services, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

## FOR SALE

### TRADE TELEVISIONS

- Wide range of used sets in good cabinet condition.
- Plenty of working sets - try ours!
- Delivery arranged anywhere.

**ALPINE ELECTRONICS**  
39 St Stephen's Road,  
Birmingham B29 7RR.  
Telephone: 021-471 3836.

**TRIO 1562A** 10MHz Double Beam Oscilloscope including probes £210.00 o.n.o. Tel. 061688 4279 (M/CR).

## MISCELLANEOUS

**BURGLAR ALARM EQUIPMENT.** Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 682674.

**LABGEAR TELE-VERTAS CM 6022.** £12.00 each. 1-Megger 500V Battery type £50.00. Tel. 05672-371 evenings.

## COURSES

**CONQUER THE CHIP...** Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C4, Reading, Berks RG1 1BR.

## FULL-TIME COURSES IN

- Microprocessor Computers
- Video Cassette Recorders
- Colour TV.

Diploma - High Diploma or City and Guilds Qualifications.

Apply:

**Registrar,**  
**Reeswood College,**  
**299A Edgware Road,**  
**London W2 1BB.**  
**01-402 9985.**

Courses commence 21st September 1983 and 18th January 1984.

## 1983 PRICE LIST

# DISPLAY ELECTRONICS

## GOLD LABEL COLOUR TUBES

### 2 YEAR GUARANTEE

90° up to 19".....	£33
90° up to 22".....	£36
90° up to 26".....	£39

The above prices are for standard 38mm Delta Gun Types.

Add £5 Gun surcharge for 20AX Types. Other in-line & P.I.L. Types, prices on application.

## GOLD LABEL MONO TUBES

### 2 YEAR GUARANTEE

19"/20".....	£12
23"/24".....	£14

## GREEN LABEL COLOUR TUBES

### 12 MONTHS GUARANTEE

90° up to 19".....	£28
90° up to 22".....	£31
90° up to 26".....	£34

Green Label Prices apply only to standard 38mm Delta Gun Types. They will be of particular interest to customers refurbishing ex-rental sets.

## BUDGET CORNER

Buy any 5 mixed types take 20% discount.

Buy any 3 mixed types take 10% discount.

Budget prices apply only to colour tubes. The mix can include Gold & Green Label Types if required.

## CALLERS WELCOME

Late night Thursdays until 8 p.m.  
Saturdays until Midday

N.B. Customers intending to collect orders are requested to telephone in advance:- even popular types may be out of stock for short periods.

**UNIT 1**  
**SWAN WHARF**  
**WATERLOO ROAD**  
**UXBRIDGE**  
**MIDDLESEX**

Telephone: UXBRIDGE 55800

# LOOK TOP QUALITY SETS LOOK

MAKES	NON WORKERS	WORKERS
Philips G8's 2 Chip Bush/Murphy	SINGLES £18	SINGLES £30
	FIVES £14	FIVES £26
	TENS £13	TENS £25
Thorn 3000, 3500 Thorn 8000, 8500	SINGLES £18	SINGLES £35
	FIVES £16	FIVES £30
	TENS £14	TENS £25
Thorn 8800, 9000, 9800 Touch tune sets etc.	SINGLES £35	SINGLES £40
	FIVES £30	FIVES £38
	TENS £28	TENS £35
GEC Solid State All types	SINGLES £25	SINGLES £40
	FIVES £20	FIVES £35
	TENS £18	TENS £28
ITT CVC5 ITT CVC8/9	SINGLES £18	SINGLES £40
	FIVES £16	FIVES £35
	TENS £14	TENS £28

**MONO SINGLE STANDARD**  
Mono TV's in batches of 20 @ £2.50

**SOME SETS ONLY £10 IN QUANTITY**  
ALL OTHER MAKES AVAILABLE ON REQUEST.

SPARE PARTS & PANELS AVAILABLE AT VERY COMPETITIVE PRICES. ALSO SECONDHAND TUBES, AERIALS, STANDS ETC.

COVENTRY BRANCH MAP:  
M.S. ELECTRONICS  
UNIT 1  
WARWICK STREET  
EARLSDON COVENTRY  
TEL: (0203) 714213



N.B. Note to give prompt service, please telephone to order in advance to avoid disappointment.

OPENING HOURS:  
9.30-1.00/2.00-5.45  
CLOSED ALL DAY THURS  
AND SUN.

GLASGOW BRANCH:  
72 ROBERTSON ST.  
GLASGOW  
SCOTLAND  
TEL: (041) 221-2146

LONDON'S LARGEST TELEVISION WHOLESALER . . .  
with over 4½ thousand sq. feet.

## "TELEMANN"

8-10 RHODA STREET,  
(Off Bethnal Green Road)

LONDON E.2. FREE CAR PARK

TEL: 01-739 2707

ALL MAKES IN STOCK AND GUARANTEED  
COMPLETE

PYE 22" COLOUR FROM £7.50

PHILIPS 22" G8 (Teak cabinet) PARCEL OF TEN £12  
MONO DUAL STANDARD £2

- SINGLE STANDARD £5

FREE DELIVERY TO THE LONDON AREA!

TELEPHONE 01-739 2707 - NOW!

## A.B.C. TRADE SALES

COLOUR T.V.'s

Philips G8, Pye, Decca 30's,

Thorn's 3000's, 3500's, 8000's

Prices start from £12 - Working sets from £20

Hundreds of Mono T.V.'s from £2.00

Jap. sets from £30.00

*Special prices for quantity*

*9,000 sq. feet Warehouse*

83 SHOWELL ROAD, BUSHBURY,

WOLVERHAMPTON, STAFFS.

Tel. Wolverhampton 722637

## N.G.T. COLOUR TUBES

First Independent Rebuilder with

**B.S.I. CERTIFICATION**

(Certificate No. 004)

All Colour Tubes are debanded, high temperature pumped  
and rebanded using new adhesives and new tension band.

19" £30, 20" £32, 22" £33, and 26" £38.

*No exchange tube required on delta types.*

Delivery U.K. mainland: £7.50.

**N.G.T. ELECTRONICS LTD.,**

120, SELHURST ROAD, LONDON S.E.25

Phone: 01-771 3535.

20 years experience in television tube rebuilding. add VAT at 15%

EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES  
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●

### IMMEDIATE CREDIT AVAILABLE — TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY  
TV COMPONENT BY RETURN  
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

*Applies to U.K. only.*

**TELEPART (W'TON)**

THE TELECENTRE, WORCESTER ST.,  
WOLVERHAMPTON (0902) 773122

## Tomorrows Television Today

A HANDBOOK ON  
SATELLITE  
TELEVISION  
RECEPTION

Receive Satellite  
Television at home  
now.

Low Noise Amplifiers,  
Down Convertors,  
Receivers, Dishes &  
Feeds explained in  
detail.

Full information on  
Television  
Broadcasting Satellites  
over Europe.

Complete listing of  
more than 20 T.V.  
Channels on these  
Satellites.

**A5. 140p.**  
**Fully Illustrated**

**£9.85p**

+ 65p p & p

Please allow up to 28 days for delivery.

**YOU COULD BE  
WATCHING  
SATELLITE  
TELEVISION TODAY**

Please send me . . . . .  
copies of  
**Tomorrows Television Today.**

I enclose cheque for £ . . . . .

NAME . . . . .

ADDRESS . . . . .

. . . . .

. . . . .

. . . . .

. . . . .

Post to:  
**M. Stone,**  
47 Filton Avenue, Horfield, Bristol

DIODES	
OA 47	10p
OA 90	8p
OA 91	10p
IN 60	5p
IN 914	5p
IN 2069a	10p
IN 2070	10p
IN 4001	3p
IN 4002	3p
IN 4004	10p
IN 4005	5p
IN 4006	6p
IN 4007	7p
IN 4148	5p
IN 4448	10p
IN 4742	10p
IN 4722	10p
IN 4751	10p
IN 5235	10p
IN 5254	10p
IN 5392	10p
IN 5928B	10p
IA 5401	10p
LAV 30	10p
IM 72Z55	10p
IR 106a	20p
IR 3051	10p
IS 164	10p
IS 921	10p
IS 3011a	10p
IS 3072a	10p
IS 5024a	10p
IS 5030	50p
ITT 921	10p
ITT 923	10p
ITT 1075	10p
ITT 2001	10p
ITT 2002	10p
ITT 4150	10p
ZE 1.5	10p
ZF 3.0	10p
ZF 3.3	10p
ZF 4.3	10p
ZF 10	10p
ZF 11	10p
ZF 12	10p
ZF 15	10p
ZF 33	10p
ZF 43	10p
ZF 47	10p
ZF 82	10p
ZPD 3.9	10p
ZPD 4.7	10p
ZPD 5.6	10p
ZPD 10	10p
ZPD 47	10p
ZPY 8v2	10p
ZPY 12	10p
ZPY 16	10p
ZPY 24	10p
ZPY 43	10p
ZPY 47	10p
ZPY 56	10p
ZTE 2	10p
ZTK 22	10p
ZTK 33	10p
ZTK 33a	10p
ZTK 102c	10p
ZTK 107	10p
ZTK 108c	10p
ZTK 109k	5p
ZTK 213	5p
ZTK 341	10p
ZTK 342	10p
ZTK 384	10p
ZTK 450	10p
ZTK 451	10p
ZTK 550	12p
ZW 11	10p
ZW 27	10p
ZW 43	10p
ZW 310	10p
ZX 68	50p
ZY 47	10p
ZY 72	10p
AA 112	10p
AA 113	10p
AA 119	10p
AA 143	10p
AA 144	10p
BA 102c	10p
BA 157	8p
BA 159	8p
BA 173	8p
BA 182	8p
BA 201	8p
BA 202	8p
BA 243	8p
BA 248	8p
BA 316	8p
BAV 10	10p
BAV 21	10p
BAW 21	10p
BB 103	10p
BB 105A	10p
BB 105B	10p
BB 105G	10p
BB 121a	10p
BZX 46c22	15p
BZX 61c110	6p
BZX 61c15	6p
BZX 61c20	10p
BZX 61c30	10p
BZX 61c220	10p
BZX 70c33	8p
BZX 79c2v4	10p
BZX 79c4v7	8p
BZX 79c5v6	8p
BZX 79c6v2	8p
BZX 79c6v8	8p
BZX 79c8v2	8p
BZX 79c11	10p
BZX 79c12	8p
BZX 79c22	8p
BZX 79c30	8p
BZX 79c43	8p
BZX 79c47	8p
BZX 83c4v3	10p
BZX 83c5v6	10p
BZX 83c8v2	10p
BZX 83b12	10p
BRC 83c13	10p

Voltage Regulators	
5V/UA78P05C	60p
5V/LM79M05CP	25p
8V/79M08c	30p
12V/MC 7912	20p
12V/LM 340T12	25p
15V/78M15	15p
18V/MC78M18	20p
24V/78M24	30p
TIS 90	20p
TIS 91	30p
TIS 92	30p

**CB Radio transistor**  
16119 2A/40v.50Meg  
5 for £1.

U 14727	15p
U 19885	40p
U 3832	15p
U 3845	15p
MR 856	10p
MR 508	10p
MR 501	10p
MR 502	20p
MR 852	20p
MR 854	10p
BYF 1202	10p
BYF 1204	10p
BYF 3123	40p
BYF 3126	40p
BYF 3214	40p
BYX 10	6p
BYX 36/600	50p
BYX 38/300	25p
BYX 38/600	50p
BYX 55/350	10p
BYX 71/350	20p
BYX 71/600	50p
BYX 72/300	20p
BYV 95	8p
BYV 96D	10p
BYZ 106	10p
BPW 41	15p
BYW 56 2A/1000v	8p
BZY 93	50p
BZV 15/12	30p
BZV 15/18	30p
BZV 15/30	30p
BZW 70c6v2	10p

Bush thyristor RCA 76122	£1
ITT computer bookset 2020	£4
G8 20 turn 100K pot	35p
Transformer 240v/20v-500Ma	75p
Viewdata torroidals	£5
+ £2 postage	
Mitsumi tape motor	75p
Sankyo tape motor	75p

Swiss made 250rpm/240V motor very small	75p
Sharp tape motor 400-040	£1.50
Mono scan coil 110" small neck	£1.50
Infra red led LD57CA	15p
Mono scan coil	£3
G 8 transistor	£1
Thorn 4000 tube base	£4
A1 pots Thorn 3500	50p
2K5 Lin pot with 40mm spindle	20p

BRIDGES	
KBL 005	30p
KBL 02	30p
KBP 04	30p
W02	15p
W004	15p
W005	20p
GEC remote panel. Main transformer 3/kc SAA 1025/SN 74141/TBA 231	£6
AT 2076/55 GEC split diode transformer	£10
AT 2048/11 LOPTI Mullard	£2.50
75R/25 Watt	25p
18R/11 Watt	25p
TV Sound Tuner Kit, ideal for your Hi-Fi	£9.50
Front End Music Center. VHF/MW/LW 13" x 3 1/2"	£5
Output Stage for music center	£5
Both items circuit supplied (as previous ad)	£9

SONY 1400KV Chroma Panel  
SONY 1400KV Tuner unit £3.50  
SONY 1400KV Touch button unit £3.50

4 books/Electronic Systems/First steps into TV/Guide to Printed Circuits + 1 other  
**Special Offer £1.75**

Panel VDP 12/80 D2N 720 Issue 3. Complete with All I.C.'s. Usually £100.  
**ONLY £10.**

**VIEWDATE DECODER PANEL TEXAS**

**PHILIPS DIY HOME SECURITY ALARMS KITS**  
Send for details. Prices £54 to £112.

**MARDAVE MODEL RACING CARS**  
Nickel Cadmium Battery driven  
Please send for details

**Various Tools and Accessories**

Sellotape PVC Black 25mm x 20M	50p	50mm x 20M	70p
Telescop aerials (radio)			£1
Xcelite pliers			£3.90
Xcelite snips			£5
Xcelite cutters			£3.90
GKN Supascrew kits; 180 items in box with British made screwdriver.		Was £4.99. <b>ONLY £2.50</b>	
VU meter			45p
Pull up large aerial			75p
Soldering iron 6v/23w			£2.50
Portable TV aerial			75p
Neon screwdriver			50p
Phillips snips			£2
2 way baby alarm/intercom with long leads			£5
Phillips universal battery tester/charger, fuse/bulb tester			£5
Volt/ohm test meters 1000 ohm/volt			£5
Eisenmann NICAD CHARGER 5.5V/150 ma			£2
3/4" x 1/2" microphone/speaker			50p
Continental 2 pin plug with 5ft mains lead (black & blue) 5 for £1			50p
7" Ferrite rod with LW/MW coils			£3.50
Xcckute 5" bent nose plier			£5.20
De-solder pump + 2 nozzels			50p
Plastic box for i.c.s with anti-static pad 6" x 3" x 1/2"			£1.40

Quantity Reductions		100 Fuses	
BY204/4	25 for £1.00	100 W/W Res.	£1.50
BY206	25 for £1.00	20 Slider Knobs	70p
BD132/676a	20 for £2	6 Mixed UHF Aerial Isolating Sockets, some with long leads	£1.00
W005 bridge	20 for £2		
G11 touch button red	5 for £1		
6Meg filter	10 for £2.60		
BY210/600	25 for £1.00		
BD239	20 for £1.50		
BY298 3 amp/fast/R	20 for £2.00		
MR856	25 for £1.50		
BU126	10 for £6.00		
BU208	10 for £5.00		
BU204	20 for £8.00		
BU205	10 for £8.00		
BU105	10 for £6.00		
25C2122A	10 for £8.00		
BF458	10 for £1.00		
BD136	10 for £1.25		
BF224	20 for £1.40		
OA90	40 for £1.00		
IN4148	40 for £1.00		
IN4448	40 for £1.00		
BYX10	100 for £4.00		
KT3 multicaps	10 for £7.50		
50 High voltage ceramic condensers	£1.50		
Mixed Mounting Kit for Power Transistors	50p		
300 Condensers	£1.50		
300 Resistors	£1.50		
150 Electrolytics	£2.00		
150 Bulbs	40p		
100 Diodes	£1.50		
VMOS Data (Ferranti)	£1.40		
Full line condensed catalogue (Fairchild)	£1.40		

**SENDZ COMPONENTS**  
63 Bishopsteignton, Shoeburyness, ESSEX SS3 8AF  
**SAME DAY SERVICE**  
All items subject to availability.  
No Accounts : No Credit Cards  
Postal Order/Cheque with order  
Add 15% VAT, then 50p P+P  
Add Postage for overseas  
Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992


# SENDZ COMPONENTS

**63 Bishopsteignton,  
Shoeburyness, ESSEX SS3 8AF  
SAME DAY SERVICE**

**All items subject to availability.  
No Accounts : No Credit Cards  
Postal Order/Cheque with order  
Add 15% VAT, then 50p P+P  
Add Postage for overseas**

**Callers: To shop at 212 London Rd.,  
Southend. Tel. 0702-332992**

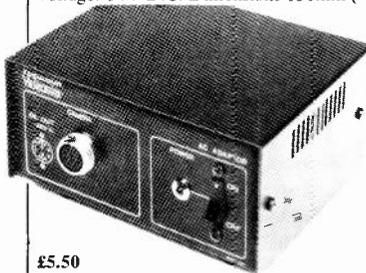Mains in 110-120-220-240V A.C. 50Hz Adaptor. For black and white camera. Power consumption: 12V A. Output voltage: 14V D.C. Dimensions 150mm (w) x 80mm (h) x 120mm (d).



Accessories: Mains lead and video/audio remote cable (2 metres)

£5.50

<p>Transducer Hand Set insert, crystal, transducer, 11C SAA 1124 &amp; lead £3.50</p> <p>THORN 4000 ultra sonic hand set insert with 7 buttons (no case) £5</p> <p>4000 Thorn thick film.</p> <p>00S1 012 E004 £1.00</p> <p>00S1 012 E002 £1.00</p> <p>00S1 012 010B £1.00</p> <p>00S1 018D £1.00</p> <p>Rank/Toshiba preh unit 0354 £9.50</p> <p>4 Push button unit preh £1.00</p> <p>6 Push button VHF/UHF for v/cap. GEC-Decca type £7.00</p> <p>7 Push button for CVC5 ITT £8.00</p> <p>6 Push button Unit Thorn £1.00</p> <p>6 Push button unit for GEC 2040 and ELC 1043/05 £6.00</p> <p>7 Lamps for P.B./Unit 10p</p> <p><b>Mains Droppers</b></p> <p>Pye 731 3+56+27R 50p</p> <p>3500 Thorn 6/1/100 60p</p> <p>Thorn 50/17/1K5 £1.00</p> <p>120/20/20/48/117 £1.00</p> <p>270/106 for Thorn 4000 50p</p> <p>18/320/70/39 £1.10</p> <p>Thorn 50-40R-1K5 50p</p> <p>Aerial Socket and Lead 35p</p> <p>Pye, Thorn, ITT, Thyristor, Philips G11 122 60p</p> <p>Rank Toshiba Tube Bases 30p</p> <p><b>Speakers</b></p> <p>6x4G11 25 ohm £1.00</p> <p>5x3 3 ohm £1.00</p> <p>5x3 80 ohm 70p</p> <p>5x3 50 ohm 50p</p> <p>5x3 35 ohm 70p</p> <p>5x3 15 ohm 80p</p> <p>6x4 15 ohm £1.00</p> <p>7x3 70 ohm £1.00</p> <p>5x3 8 ohm 70p</p> <p>7x3 16 ohm £1.00</p> <p>8x5 8 ohm £1.50</p> <p>5" dia 16 ohm £1.00</p> <p>5" dia 8 ohm £1.50</p> <p>2" dia 8 ohm 75p</p> <p>3" dia 8 ohm 75p</p> <p><b>Diodes</b></p> <p>BY 127 10p</p> <p>BY 133 10p</p> <p>BY 134 10p</p> <p>BY 164 30p</p> <p>BY 176 type 25p</p> <p>BY 179 40p</p> <p>BY 184 25p</p> <p>BY 187 10p</p> <p>BY 190 40p</p> <p>BY 196 30p</p> <p>BY 198 10p</p> <p>BY 204/4 8p</p> <p>BY 206 8p</p> <p>BY 210/400 5p</p> <p>BY 210/600 8p</p> <p>BY 210/800 10p</p> <p>BY 223 80p</p> <p>BY 224/600 50p</p> <p>BY 226 15p</p> <p>BY 227 15p</p> <p>BY 228 20p</p> <p>BY 229/400 30p</p> <p>BY 237 5p</p> <p>BY 254 10p</p> <p>BY 255 10p</p> <p>BY 298 10p</p> <p>BY 299 10p</p> <p>BY 527 20p</p> <p>BY 407a 10p</p> <p>BY 602 F 247 50p</p> <p>XK 3102 50p</p> <p>XK 3123 50p</p> <p>Thorn A1 10p</p> <p><b>Line Transformers</b></p> <p>G8 Trans. Philips £7.50</p> <p>G11 Split Diode £12.00</p> <p>CVC820 Split Diode ITT £10.00</p> <p>CVC40 Split Diode ITT £10.00</p> <p>GEC 2040 £5.00</p> <p>Pye mono £3.00</p> <p>Rank mono T704A £3.50</p> <p><b>International Rectifier EHT Diodes</b> G770/HV34 6KV 3 for 8p</p> <p>6A/600V Stud Diodes 20p</p> <p>6A/1000V Stud Diodes 20p</p> <p>SKE 1/02 20p</p> <p>20 x W005 Bridge £2.00</p>	<p>CVC32 ITT £7.50</p> <p>EHT Split Diode Leads £1.00</p> <p><b>Triplers</b></p> <p>11 TEZ Rank £3.00</p> <p>9000 Thorn £5.00</p> <p>KT3 £4.00</p> <p>CVC-20-25-30 £4.00</p> <p>G9 Philips £4.00</p> <p>GEC 2110 £4.00</p> <p>9500 Thorn £4.50</p> <p>2040 GEC £3.50</p> <p>G8 Philips £4.50</p> <p>Decca 80 100 £4.50</p> <p>LP1194 Pye 731 £3.50</p> <p>Grundig TVK 52 £2.50</p> <p>11TBQ £3.00</p> <p>11THY £4.00</p> <p>D22 for Pye 18" colour portable £4.00</p> <p>LP 1193/63 £4.00</p> <p>BG 100/41 £3.25</p> <p>BG 100/61 £3.25</p> <p>New Philips Infra Red Transmitter 9ch &amp; Vol. &amp; brightness change £7.00</p> <p>THORN Tuner Panel. 6 Slider pots, Knobs, touch button. Ultrasonic transducer, ICs, components &amp; mains switch £3.75</p> <p>GEC Portable Line Trans. £3.00</p> <p>THORN portable mono chassis U788F £10.00</p> <p>9000 front panel £5.00</p> <p>9000 front panel (remote) £8.00</p> <p>G8 Convergence Panel £12.00</p> <p>T/text ultrasonic rec'r panel £14.00</p> <p>Handset G11 (2 button unit) £12.00</p> <p>THORN 9000 Syclops panel £1.50</p> <p>THORN 8000/8500 timebase panel £8.00</p> <p>THORN 8000/8500/8800 chroma panel £15.00</p> <p>THORN 8500 convergence panel £6.00</p> <p>THORN 8800 remote control unit U705 £6.00</p> <p><b>Philips Infra-Red (full remote transmitter)</b></p> <p>Philips KT3 16C928/20C934 £12</p> <p>Pye KT3 7228/7324 K12 26C 797/IST 66K 1826 £12</p> <p>G11 handset. Full remote top £12.00</p> <p>Video cassette lamps on lead. 12-14V. 50p or 3 for £1.00</p> <p>GEC 8 touch unit assy complete with all I.C.'s + pots £6.00</p> <p>9000 Frame Panel £7.00</p> <p>G11: 8 touch button unit £20.00</p> <p>Transmitter Decca RC11 £14</p> <p>Transmitter Decca RC12 £14</p> <p>G11 Tuner Units £6.00</p> <p>G11 6 Button Key Switch £2.00</p> <p>G11 E/W Transformer 50p</p> <p>G11 Line OSE Tran. 50p</p> <p>G11 Transient Suppressors 245V 10 for £1.00</p> <p>G11 Scan Coils £5.00</p> <p>KT3 AE Sockets 25p</p> <p>4000 Thorn Frame Panel £5.00</p> <p>4000 Thorn Power Supply £3.00</p> <p>4000 Thorn Line OP Panel £20.00</p> <p>NPN PNP 80V 6 Amp TO66 O.P. Trans. pair 25p</p> <p>GEC IC CBF16848. SN16861. SN1682 each 50p</p> <p>Thorn 3500 IF Panel NEW £3.00</p> <p>Thorn Tuner Panel 6-100K Pots &amp; Components NEW No Tuner £2.00</p> <p>6 button 100K pots + cursors on panel for varicap tuning £1.50</p> <p>THORN 1600 mains lead: switch: 3 slider assy. £2.00</p> <p>5 button touch tuner BBC1/2 ITV1/2 video with ic SAS 560T/570T £7.00</p> <p>Control panel 5 sliders + mains lead £1.50</p> <p>Tube base + base unit for 820 Euro chassis £4.00</p> <p>CVC 9 IF panel and decoder £7.00</p>	<p>GEC Line O/P Trans. &amp; Rec Stick for Portable £3.00</p> <p>CVC 20/25/30/35/40 decoder panel £10</p> <p>CVC 20/25/30/35/40 decoder panel (untested) £5</p> <p>CVC 40/45 IF panel £5</p> <p>Mains Panel with switch and lead £1.50</p> <p>Thorn 3500 6 push button unit &amp; cable form £1.50</p> <p><b>Rec &amp; Trans</b></p> <p>G11 Ultrasonic t/text transmitter G26C 674/02 £19</p> <p>G22 C66/02 £19</p> <p>Infra Red (full remote transmitter) Dynatron TV CTV 62, 63, 64 £19</p> <p>40K Transducer 50p</p> <p>PHILIPS NE511N £1.20</p> <p>LM337M Reg. 30p</p> <p>Thorn T605 1V NPN TO66 80V 6A 10p</p> <p>20 GEC Black Spark Gaps £1.00</p> <p>G11 Line Driver Transformer 35p</p> <p>2 SD350A BU208A £1.00</p> <p>G11 IF Detector £3.00</p> <p>Complete CVC 825 Chassis (both panels) £40.00</p> <p>G11 Teletext Transmitter £19.00</p> <p>BG200/43 Tripler £3.00</p> <p>DECCA IF 80-100 £3.50</p> <p>G11 Time Base Panel £12.00</p> <p>AEC V/Cap Resistor Unit UHF with IC SAS660 SAS670 £3.00</p> <p>Thorn 900 Sound OP Panel NEW £1.00</p> <p>U321 T/Unit on Panel Cum 40 ITT £6.00</p> <p>1250/50 2000/50 3000/50 15/63 47/63 Bipolar 15p</p> <p>2200/63 250/64 250/64 3300/70 1/100 4.7M/100 140/100 470/100 800/160 800/160 G11 0.91/210 scan coil correction 25p</p> <p>G11 1/250 Pulse 5p</p> <p>G11 0.47/250 10p</p> <p>2.2 250v 10p</p> <p>3n3/250 10p</p> <p>4n7/250 tested 5KV 25p</p> <p>22/250 15p</p> <p>47/250 10p</p> <p>100/250 20p</p> <p>500/250 50p</p> <p>GEC600/250 60p</p> <p>800/250 40p</p> <p>8/300 8p</p> <p>4/350 5p</p> <p>1500/16 20p</p> <p>3300/16 20p</p> <p>10000/16 25p</p> <p>15000/16 50p</p> <p>3300/18 20p</p> <p>470/25 5p</p> <p>680/25 5p</p> <p>1000/25 Radial 10p</p> <p>1250/25 10p</p> <p>1500/25 10p</p> <p>2200/25 10p</p> <p>3300/25 20p</p> <p>4700/25 20p</p> <p>5000/25 25p</p> <p>10000/25 25p</p> <p>1500/30 20p</p> <p>3300/30 20p</p> <p>1500/35 20p</p> <p>2200/35 10p</p> <p>50/40 5p</p> <p>220/40 5p</p> <p>400/40 25p</p> <p>680/40 25p</p> <p>1250/40 20p</p> <p>1500/40 20p</p> <p>200/40 25p</p> <p>2000/40 25p</p> <p>2200/40 25p</p> <p>2500/40 25p</p> <p>3300/40 25p</p> <p>6800/40 35p</p> <p>750/50 10p</p> <p>1000/50 20p</p> <p>1250/50 25p</p> <p>2000/50 25p</p> <p>3000/50 25p</p> <p>15/63 5p</p> <p>47/63 Bipolar 15p</p> <p>2200/63 15p</p> <p>250/64 15p</p> <p>3300/70 50p</p> <p>1/100 5p</p> <p>4.7M/100 5p</p> <p>140/100 25p</p> <p>470/100 20p</p> <p>800/160 50p</p> <p>G11 0.91/210 scan coil correction 25p</p> <p>1/250 Pulse 5p</p> <p>G11 0.47/250 10p</p> <p>2.2 250v 10p</p> <p>3n3/250 10p</p> <p>4n7/250 tested 5KV 25p</p> <p>22/250 15p</p> <p>47/250 10p</p> <p>100/250 20p</p> <p>500/250 50p</p> <p>GEC600/250 60p</p> <p>800/250 40p</p> <p>8/300 8p</p> <p>4/350 5p</p> <p>1500/16 20p</p> <p>3300/16 20p</p> <p>10000/16 25p</p> <p>15000/16 50p</p> <p>3300/18 20p</p> <p>470/25 5p</p> <p>680/25 5p</p> <p>1000/25 Radial 10p</p> <p>1250/25 10p</p> <p>1500/25 10p</p> <p>2200/25 10p</p> <p>3300/25 20p</p> <p>4700/25 20p</p> <p>5000/25 25p</p> <p>10000/25 25p</p> <p>1500/30 20p</p> <p>3300/30 20p</p> <p>1500/35 20p</p> <p>2200/35 10p</p> <p>50/40 5p</p> <p>220/40 5p</p> <p>400/40 25p</p> <p>680/40 25p</p> <p>1250/40 20p</p> <p>1500/40 20p</p> <p>200/40 25p</p> <p>2000/40 25p</p> <p>2200/40 25p</p> <p>2500/40 25p</p> <p>3300/40 25p</p> <p>6800/40 35p</p> <p>750/50 10p</p> <p>1000/50 20p</p> <p>1250/50 25p</p> <p>2000/50 25p</p> <p>3000/50 25p</p> <p>15/63 5p</p> <p>47/63 Bipolar 15p</p> <p>2200/63 15p</p> <p>250/64 15p</p> <p>3300/70 50p</p> <p>1/100 5p</p> <p>4.7M/100 5p</p> <p>140/100 25p</p> <p>470/100 20p</p> <p>800/160 50p</p> <p>G11 0.91/210 scan coil correction 25p</p> <p>1/250 Pulse 5p</p> <p>G11 0.47/250 10p</p> <p>2.2 250v 10p</p> <p>3n3/250 10p</p> <p>4n7/250 tested 5KV 25p</p> <p>22/250 15p</p> <p>47/250 10p</p> <p>100/250 20p</p> <p>500/250 50p</p> <p>GEC600/250 60p</p> <p>800/250 40p</p> <p>8/300 8p</p> <p>4/350 5p</p> <p>1500/16 20p</p> <p>3300/16 20p</p> <p>10000/16 25p</p> <p>15000/16 50p</p> <p>3300/18 20p</p> <p>470/25 5p</p> <p>680/25 5p</p> <p>1000/25 Radial 10p</p> <p>1250/25 10p</p> <p>1500/25 10p</p> <p>2200/25 10p</p> <p>3300/25 20p</p> <p>4700/25 20p</p> <p>5000/25 25p</p> <p>10000/25 25p</p> <p>1500/30 20p</p> <p>3300/30 20p</p> <p>1500/35 20p</p> <p>2200/35 10p</p> <p>50/40 5p</p> <p>220/40 5p</p> <p>400/40 25p</p> <p>680/40 25p</p> <p>1250/40 20p</p> <p>1500/40 20p</p> <p>200/40 25p</p> <p>2000/40 25p</p> <p>2200/40 25p</p> <p>2500/40 25p</p> <p>3300/40 25p</p> <p>6800/40 35p</p> <p>750/50 10p</p> <p>1000/50 20p</p> <p>1250/50 25p</p> <p>2000/50 25p</p> <p>3000/50 25p</p> <p>15/63 5p</p> <p>47/63 Bipolar 15p</p> <p>2200/63 15p</p> <p>250/64 15p</p> <p>3300/70 50p</p> <p>1/100 5p</p> <p>4.7M/100 5p</p> <p>140/100 25p</p> <p>470/100 20p</p> <p>800/160 50p</p> <p>G11 0.91/210 scan coil correction 25p</p> <p>1/250 Pulse 5p</p> <p>G11 0.47/250 10p</p> <p>2.2 250v 10p</p> <p>3n3/250 10p</p> <p>4n7/250 tested 5KV 25p</p> <p>22/250 15p</p> <p>47/250 10p</p> <p>100/250 20p</p> <p>500/250 50p</p> <p>GEC600/250 60p</p> <p>800/250 40p</p> <p>8/300 8p</p> <p>4/350 5p</p>	<p>8/350 8p</p> <p>12/300 10p</p> <p>4.7M/350v 10p</p> <p>16/350 25p</p> <p>50/350 10p</p> <p>220/350 30p</p> <p>300/350 40p</p> <p>700/350 50p</p> <p>22/375 15p</p> <p>330/385 CVC 820HT 60p</p> <p>0.1/400 15p</p> <p>56K/400v 15p</p> <p>8/400 15p</p> <p>33/400 20p</p> <p>220/400 50p</p> <p>400/400 40p</p> <p>2 x 10,000Pf/400 in box 40p</p> <p>33/450 15p</p> <p>220/450 40p</p> <p>0.1/600 15p</p> <p>0.047/600 15p</p> <p>0.047/1000 10p</p> <p>0.01/1000 10p</p> <p>0.1/1000 10p</p> <p>15/1000 20p</p> <p>001K/1250 10p</p> <p>0.0047/1500 10p</p> <p>005/1500 10p</p> <p>0105/1500 10p</p> <p>1n8/1500 15p</p> <p>2n2/1500 15p</p> <p>G11.11000/1500 15p</p> <p>G11.8200/2KV 15p</p> <p>0.1/2KV 20p</p> <p>10n/2KV 15p</p> <p>3n3/2KV 10p</p> <p>210/8KV 10p</p> <p>0.0015/2KV 10p</p> <p>5n2/2KV 10p</p> <p>6n2/2KV 15p</p> <p>7500p/2KV 10p</p> <p>4n7/2KV 15p</p> <p>8n2/2KV 15p</p> <p>0.0082/2500 15p</p> <p>1503/500 10p</p> <p>1800/4KV 5p</p> <p>4.7n/5KV 10p</p> <p>170/8KV 10p</p> <p>180/8KV 10p</p> <p>210/8KV 10p</p> <p>270/8KV 10p</p> <p>1000/10KV 10p</p> <p>210/12KV 10p</p> <p>1000/12KV 10p</p> <p>1200/12KV 10p</p> <p><b>Multi-Caps</b></p> <p>Thorn 3500 175/100/100/350v £2.00</p> <p>KT3/200/25/25/385v £1.00</p> <p>47/220/350v 60p</p> <p>150/150/100/100/100/320v £2.00</p> <p>2500/2500/63v 50p</p> <p>470/470/250v 50p</p> <p>150/200/200/300v 70p</p> <p>400/400/200v £1.70</p> <p>300/100/100/16/275v £1.50</p> <p>100/200/325v 40p</p> <p>400/200/200/350v £1.50</p> <p>200/200/100/300v 60p</p> <p>200/350v + 300/100/32/300v £2.00</p> <p>200/200/100/32/350v £1.50</p> <p>200/47/350v 60p</p> <p>100/300/100/16/350v £2.00</p> <p>200/100/100/375v £2.00</p> <p>100/100/35v 60p</p> <p>100/1000/35v 60p</p> <p>150/150/100/100/320v £2.00</p> <p>100/350 + 300/200/100/16/275v £2.00</p> <p><b>ITT Panels</b></p> <p>CMA 10 £2.00</p> <p>CMA 11 £2.00</p> <p>CMA 30 £1.50</p> <p>CMA 40 £2.00</p> <p>CMC 10/2 £5.00</p> <p>CMC 15 £10.00</p> <p>CMC 16 £4.00</p> <p>CMC 19 £12.00</p> <p>CMC 45 £1.50</p> <p>CMC 47 £1.00</p> <p>CMC 54 £10.00</p> <p>CMC 56 £8.00</p> <p>CMC 58 £8.00</p> <p>CMC 59 £8.00</p> <p>CMC 67 £3.75</p> <p>CMC 67/2 £4.00</p> <p>CMC 68 £4.00</p> <p>CMC 12 £10</p> <p>CMC 25 £5.00</p> <p>CMF 20 £2.00</p> <p>CMF 40 £2.00</p> <p>CMH 10 £1.50</p> <p>CMH 31 £1.50</p> <p>CMK 12 (untested) £4.00</p> <p>CMN 20 £1.50</p> <p>CMN 40 £1.00</p> <p>CMP 10 £2.00</p> <p>CMP 11 £2.00</p> <p>CMP 40 £2.00</p> <p>CMS 11 £2.00</p> <p>CMS 40 £2.00</p> <p>CMU 14 £8.00</p> <p>CMU 30 £7.00</p> <p>CMU 40 £7.00</p> <p>CMU 45 £5.00</p> <p>VMC 34 £5.00</p> <p>VMC 44 + 45 £4.00</p>
--	---	--	---

<b>Tuner Units</b>	
ELC1043/05 Mullard	£6.00
ELC1043 (Ex Panel)	£3.75
ELC1042	£5.00
ELC2000	£7.00
ELC2004	£10.00
EL2060	£7.00
ELC2060 on panel	
NEW	£5.00
U321 (UHF) Mullard	£6.00
U322 (UHF)	£4.00
V314 (VHF)	£5.00
ELC1043/05 Thorn	£5.00
Small V/Cap Mitsumi	
UHF	£4.00
VHF	£3.00
VHF Rotary Mitsumi £1.00	
Portable & rotary Tuners	
Sanyo & Mitsumi UHF	£5.00
Mossfit UHF VHF NSF.	
ET021 DX	£8.00
Sylvania UHF VHF F6013 (Fits Rank) £4.50	
Sylvania UHF £6.00	
Sylvania VHF £6.00	
Decca Bradford Tuner 5 Button £4.00	
NSF AEG UHF/VHF £6.00	
Small Tuner DX 175-220MHz Auto Changeover £5.00	
9000 Thorn Tuner on Panel £7.00	
D.P.D.T. switch Black knob: Chassis or PCB mount 4p each or 40 for £1.00	
THORN 1400 4P.B. Mechanical Tuner THORN 1500 4P.B. Mechanical Tuner THORN 1590 4P.B. Mechanical Tuner THORN 3500 4P.B. Mechanical Tuner THORN 8000 4P.B. Mechanical Tuner THORN 8500 4P.B. Mechanical Tuner All new & boxed £4 each + £1 postage each	
VHF 3 Transistor Rotary Tuner Units D.X. TV. NEW £1.00	
CVC 9 power supply board £1.50	
CVC 20/2 mains panel NEW £2.00	
CVC 20/3 chassis £30.00	
FED4/1220/4 3 pin ITT 1.	
MFD 4 Amp Mains Filters 50p	
ITT Mains Filter .1/250v/	
CVC 20 to 45 chassis 50p	
Pots 10 k with Switch 25p	
Pots 47 k with Switch 25p	
Mullard Surface Wave Filter RW 153P Colour TV Filter 40p	
Mullard Surface Wave Filter RW 154 Colour TV Filter 40p	
<b>Crystal T/V</b>	
T/V 4.433-619KHz 50p	
6 MHz Crystal 50p	
8.8867-238KHz Min Miniature ITT omeg 75p	
<b>Filters</b>	
5-5MHz 15p	
6MHz 35p	
BFU455K 5p	
<b>Thyristors</b>	
BT119 £1.00	
BT120 £1.00	
BRC4443 75p	
G11 Thyristor 60p	
Decca 80-100 60p	
G11 Teletext Decoder Panel Philips £30.00	
<b>Thermistors</b>	
VA1104 35p	
ITP7266312 15p	
PTH451 AOR 15p	
PT37P Fits Pye & Bush PT34 25p	
	20p

# SENDZ COMPONENTS

**63 Bishopsteignton, Shoeburyness, ESSEX SS3 8AF**

**SAME DAY SERVICE**

**All items subject to availability. No Accounts : No Credit Cards**

**Postal Order/Cheque with order Add 15% VAT, then 50p P+P**

**Add Postage for overseas**

**Callers: To shop at 212 London Rd., Southend. Tel. 0702-332992**

<b>Diodes</b>		CA1310 50p
1 Amp 1600v 7p		CBF16848 50p
3 Amp 100v 7p		DM7492 50p
3 Amp 1200v 10p		HEF4001 10p
7 Seg Display, Led Red 50p		HBFA4011AF 10p
		HEF4016 15p
		HEF4053B 30p
<b>Delay Lines</b>		MI024 £2.00
TAU80 £1.00		MI025 £2.00
DL11 50p		MC476p £1.00
DL20A 80p		MC1307 75p
DL50 £1.00		MC1327 75p
DL70 £1.00		MC1330 75p
DL600 £1.00		MC1349 50p
DL700 £1.00		MC1352 £1.00
KT 3 Luminescence 75p		MC1358 £1.00
Luminance Delay Line		MC14001 £1.00
MDL-CBL Min. 50p		MC14013 £1.00
3.15 Fuses 4p		MC14016 £1.00
		MC14066BCP £1.00
		MC14069 £1.00
		MC14514 50p
		MC1748 80p
		MCM2114 £1.00
		NE511NE £1.00
		MEM4956PT £1.00
		MM5387 £1.00
		MM5611 £1.00
		MM5840 £1.00
		NE4100 £1.00
		NE545B (Dolby) 75p
		NE545N (Dolby) 75p
		NE555 60p
		IL-1 30p
		OPT600 30p
		OPT601 30p
		PD2114 £1.00
		SAA611 £1.00
		SAA1020 £4.00
		SAA1021 £4.00
		SAA1024 £2.50
		SAA1025 £2.50
		SAA1124 £2.00
		SAA1130 £2.50
		SAA1272 £3.00
		SAAS000 £1.50
		SAAS000A £1.50
		SAAS010 £3.50
		SAAS012 £2.50
		SAAS020 £3.50
		SAAS040 £2.50
		SAAS050 £3.50
		SAS560 £1.00
		SAS570 £1.00
		SAS660 £1.00
		SAS670 £1.00
		SL918 £2.50
		SL917 MOD
		TAA320A 50p
		TAA470 £1.50
		TAA550 30p
		TAA570 75p
		TAA611 £1.50
		TAA621 £2.00
		TAA641 £1.50
		TA7117 £1.00
		TA7315 £1.00
		TA7607 £1.00
		TA7609 £1.00
		TBA120A 40p
		TBA120AS 40p
		TBA120SA 40p
		TBA120B 40p
		2SB474 30p
		2SB566 10p
		2SC381 10p
		2SC458 50p
		2SC515 10p
		2SC732 10p
		2SC733 10p
		2SC828 10p
		2SC1030 £1.00
		2SC1172 £1.00
		2SC1173 10p
		2SC1311 20p
		2SC1419 20p
		2SC1546 20p
		2SC1617 £1.00
		2SC1684 20p
		2SC1725 20p
		2SC2068 20p
		2SC2073 8p
		2SC2122A £1.00
		2SC2229 15p
		2SC7350 10p
		2SD180 TO3 80v/ 6A 15p
		2SD200 £2.00
		2SK30A 10p
		2SN30A 8p
		FT3055 30p
		BC107 10p
		BC108 10p
		BC109/2N930 5p
		BC113 10p
		BC114 10p
		BC115 10p
		BC116 10p
		BC117 20p
		BC125 10p
		BC139 10p
		BC141 25p
		BC142 25p
		BC143 25p
		BC147 10p
		BC148 10p
		BC149 10p
		BC153 10p
		BC154 10p
		BC157a 10p
		BC158 10p
		BC159 10p
		BC160 25p
		BC171 10p
		BC172 10p
		BC173 10p
		BC174 10p
		BC182L 10p
		BC183 10p
		BC184 10p
		BC187 10p
		BC204 10p
		BC207 10p
		BC212 10p
		BC213 10p
		BC214 10p
		BC237 10p
		BC238 8p
		BC238/338 pair 10p
		BC239 10p
		BC250 8p
		BC251 10p
		BC252 10p
		BC262 10p
		BC263b 20p
		BC294 30p
		BC298 10p
		BC300 30p
		BC301 30p
		BC303 30p
		BC307 7p
		BC308 7p
		BC309 10p
		BC327 10p
		BC328 10p
		BC337 10p
		BC338 10p
		BC347 10p
		BC349b 10p
		BC350 20p
		BC365 10p
		BC384 10p
		BC394 10p
		BC413 8p
		BC414 10p
		BC416 10p
		BC440 30p
		BC447 10p
		BC454 10p
		BC455 10p
		BC456 10p
		BC460 25p
		BC462 10p
		BC463 10p
		BC478 10p
		BC527 10p
		BC532 10p
		BC546 10p
		BC547 10p
		BC556 10p
		BC557 10p
		BC558 10p
		BC559 10p
		BC565 10p
		BCX31 25p
		BCX34/36 pair 50p
		BD116 25p
		BD124 50p
		BD124 (metal) £1.20
		BD130Y 25p
		BD131 30p
		BD132 30p
		BD135 25p
		BD136 30p
		BD140 30p
		BD146 25p
		BD182 £1.00
		BD202 60p
		BD203/204 pair £1.25
		BD204 60p
		BD207 30p
		BD221 20p

TBA120SB 40p	BT119 £1.00	BD437/438 on heat sink 60p
TBA120SO £1.00	BT120 £1.00	BD507 50p
TBA120U 40p	BT138/10A 70p	BD509 30p
TBA1441 £1.00	BT146 30p	BD510 30p
TBA440	TC270 £1.00	BD517 30p
TBA231 75p	TCA270Q £1.00	BD519 30p
TBA395 50p	TCA940 £1.00	BD532 30p
TBA396 75p	TCA4500A £1.00	BD534 30p
TBA440 £1.00	TCA640 £1.00	BD535 30p
TBA440C £1.00	TCA650 £1.00	BD544D 30p
TBA4800 £1.00	TCA660 £1.00	BD562 30p
TBA510 £1.00	TCA270S £1.00	BD595 35p
TBA510Q £1.00	TCA270SQ £1.00	BD596 35p
TBA520 £1.00	TCA740 £1.00	BD646 50p
TBA530 £1.00	TCA800 £1.00	BD678 50p
TBA540 £1.00	TCA830 £1.00	BD681 25p
TBA540Q £1.00	TCA940 £1.00	BD807 20p
TBA550Q £1.00	TCEP100 £2.25	BD948 30p
TBA560CQ £1.00	TDA440Q £1.00	BF15 20p
TBA560C £1.00	TDA1003A £1.00	BF127 20p
TBA570 £1.00	TDA1010 £1.00	BF137 20p
TBA641BX1 £2.00	TDA1170 £1.00	BF157 20p
TBA651 £1.00	TDA1190 £1.00	BF160 20p
TBA673 £1.00	TDA1327A £1.00	BF161 20p
TBA720A £1.00	TDA1412 30p	BF164 60p
TBA750Q £1.00	TDA2010 £1.00	BF167 20p
TBA800 40p	TDA2140 £3.50	BF173 10p
TBA810S 70p	TDA2522 £1.00	BF178 25p
TBA820 70p	TDA2530 £1.00	BF179 30p
TBA890 £1.00	TDA2532 £1.00	BF180 20p
TBA920 £1.00	TDA2540 80p	BF181 20p
TBA920Q £1.00	TDA2541 £1.00	BF182 20p
TBA950 £1.00	TDA2575A £1.00	BF184 20p
TBA990Q £1.00	TDA2590 £1.00	BF194 20p
TMS1943NL £2.00	TDA2593 £1.00	BF195 10p
TMS9980 £12.00	TDA2560 50p	BF196 10p
TMS9901 £6.00	TDA2600 £4.25	BF197 12p
TMS2716 £6.00	TDA2653 £1.00	BF198 10p
TMS3529 £6.00	TDA2002 £1.00	BF199 10p
TMS4014 £2.50	TDA2640 80p	BF200 20p
TX012 £5.00	TDA2680 £1.00	BF222 10p
TMS9902 £6.00	TDA2690 £1.00	BF224 15p
UPD2114C 4K RAM 75p	TDA2593 £1.00	BF238 20p
SN29848 50p	TDA3190 £1.00	BF240 20p
SN74107 £1.00	TDA3500 £2.00	BF245b 20p
SN7472N 20p	TDA3560 £3.50	BF256 20p
SN75108AN £1.00	TD3571Q £1.50	BF257 20p
SN76001 £1.00	TDA3950 £1.50	BF258 25p
SN76003 £1.00	SN74LS 125AN 30p	BF259 25p
SN76018 £1.00	SN16862AN £1.00	BF262 15p
SN76008 £1.00	SN16964AN 50p	BF263p 25p
SN76023N £1.50	SN29764 £1.00	BF264 10p
SN76033 £1.50	SN297728N 50p	BF271 10p
SN76115 50p	RGP30G 10p	BF273 10p
SN76131 50p	MPSA43 10p	BF274 10p
SN76226 £1.00	E1222 20p	BF201 10p
SN76227 60p	MJE51T 25p	BF324 25p
SN76228N £1.00	MJE340 28p	BF325 30p
SN76530P 60p	MJE660 25p	BF338 25p
SN76532N 50p	MJE661 25p	BF355 30p
SN76544N £2.00	MJE3055 £1.00	BF362 20p
SN76545 £3.50	MJE2801 30p	BF363 15p
SN76550 30p	MJE2955 50p	BF367 15p
SN76552 30p	Sanikon Diode SKE262/04 30p	BF391 10p
SN76650 50p		BF394 10p
SN76660 40p		BF419 30p
SN76620AN 50p		BF423 15p
SN7666		