

R. Charleston. X.

APRIL 1984

Australia \$1.60; New Zealand \$2.10; Malaysia \$5.50;

£1.00

TELEVISION

SERVICING-VIDEO-CONSTRUCTION-DEVELOPMENTS

**ALL ABOUT
FIELD
STRENGTH**

**THE RIGONDA
VLI00 PORTABLE**

VCR CLINIC


**WIDEBAND UHF
PREAMP**

DX-TV

**TEST REPORT:
B & K 467
CRT TESTER**

TV FAULT FINDING

**SENSING OUT
FAULTS**

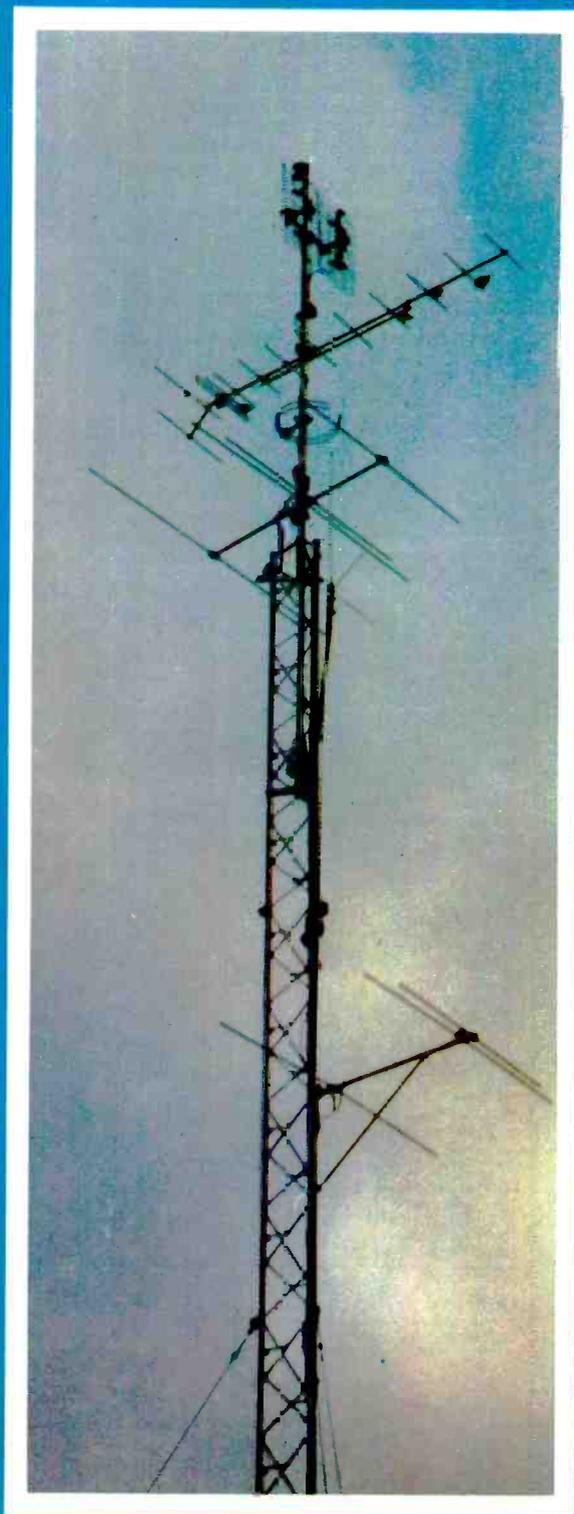

Interested in Television Servicing?

Try a ZED Pack. Effect Repairs at Minimum Cost.

Z1 300 mixed $\frac{1}{2}$ and $\frac{1}{4}$ watt and miniature resistors £1.95	Z20 10 Assorted switches including: Pushbutton, Slide, Multipole, Miniature etc. Fantastic Value £1.20	Z44 TO3 Mounting kits (BU208) 8 for 60p
Z2 150 mixed 1 and 2 watt resistors £1.95	Z21 100 Assorted Silver Mica caps £2.20	Z45 TO220 Mounting kits (TIP33) 10 for 60p
Z3 300 mixed capacitors, most types amazing value £3.95	Z22 10 Mixed TV convergence Pots £1.00	Z46 TO126 Mounting kits (BD131) 12 for 60p
Z4 100 mixed electrolytics £2.20	Z23 20 Assorted TV Knobs including: Push Button, Aluminium and Control types £1.20	Z47 Pack of each Mounting kit. All include insulators and washers £1.50
Z5 100 mixed Polystyrene Capacitors £2.20	Z24 10 Assorted Valve bases B9A, EHT, etc. £1.00	Z48 3a 1000v Diodes (1N5408 type) 8 for £1.00
Z6 300 mixed Printed Circuit Components £1.95	Z25 10 Spark Gaps £1.00	Z49 Brushed Aluminium Push Button Knobs, 15mm long x 11mm Diam. Fit standard $3\frac{1}{2}$ mm square shafts 10 for £1.00
Z7 300 mixed Printed Circuit resistors £1.45	Z26 20 Assorted Sync Diode Blocks £1.00	Z50 Chrome finish 10mm x 10mm Diam as above 10 for £1.00
Z8 100 mixed High Wattage Resistors, wirewounds etc. £2.95	Z27 12 Assorted IC Sockets £1.00	Z51 Aluminium Finish. Standard Fitting Slider Knobs. (Decca) 10 for £1.00
Z9 100 mixed Miniature Ceramic and Plate caps £1.50	Z28 20 General Purpose Germanium Diodes £1.00	Z52 Decca "Bradford" Control Knobs Black and Chrome. $\frac{1}{4}$ " Shaft 8 for £1.00
Z10 25 Assorted Potentiometers £1.50	Z29 20 Assorted Miniature Tantalum Capacitors. Superb Buy at £1.20	Z53 Tuner P/B Knobs, Black and Chrome. Fit most small Diam Shafts, ITT, THORN, GEC etc. 8 for £1.00
Z11 25 Assorted Presets, Skeleton etc. £1.00	Z30 40 Miniature Terry clips, ideal for small Tools etc. £1.00	Z54 Spun Aluminium Control Knobs (ITT) $\frac{1}{4}$ " Shaft, suitable for most sets with recessed spindles 8 for £1.00
Z12 20 Assorted VDR's and Thermistors £1.20	Z31 5 CTV Tube Bases £1.00	Z55 14 Pin DIL I.C. Sockets 12 for £1.00
Z13 1 lb Mixed Hardware, Nuts, Bolts, Selftappers, "P" clips etc. £1.20	Z32 10 EY87/DY87 EHT bases £1.00	Z56 16 Pin Quil I.C. Sockets 12 for £1.00
Z14 100 mixed New and marked transistors, all full spec. includes: PBC108, BC148, BC154, BF274, BC212L, BC238, BC184L and/or Lots of similar types ONLY £4.95	Z33 20xPP3 Battery Connectors £1.00	Z57 16 Pin DIL TO QUIL I.C. Sockets 10 for £1.00
(Z14A) 200 Transistors as above but including power types like BD131, 2N3055, AC128, BFY50 etc. £9.95	Z34 6x Miniature "Press to Make" Switches, Red Knob £1.00	Z58 22 Pin DIL I.C. Sockets 10 for £1.00
Z15 100 Mixed Diodes including: Zener, Power, Bridge, Signal, Germanium, Silicon etc. All full spec. £4.95	Z35 12 Sub Min S.P.C.O. Slide Switches £1.00	Z59 B9A Valve Bases P.C. Type 20 for £1.00
Z16 20 1N4148 Gen Purpose Diodes £1.00	Z36 12 Min D.P.C.O. Slide Switches £1.00	
Z17 20 1N4003/10D2 £1.00	Z37 8 Standard 2 Pole 3 Pos Switches £1.00	
Z18 20 Assorted Zeners. 1 watt and 400mw £1.50	Z38 4x HP11 Batt Holders (2x2 Flat type) 4 for £1.00	
	Z39 3.5mm Jack Sockets, switched, enclosed Type 8 for £1.00	
	Z40 100 Miniature Reed Switches £2.30	
	Z41 100 Subminiature Reed Switches £4.20	
	Z42 20 Miniature Reed Switches £1.00	
	Z43 12 Subminiature Reed Switches £1.00	

High quality **COAX PLUGS**, silver plated pin, grub screw fixing. **5 for £1**
COAX COUPLERS **5 for £1**
COAX FLYING SOCKET **3 for £1**

R.B.M. USERS LOOK!
 No more messy soldering. 24 pin I.C. sockets for SL901 etc. **SPECIAL OFFER: 5 for £1.00**
100 for £12.50.

ELECTROLYTIC

1µf 350v	10 for £1.00
2.2µf 63v	20 for £1.00
4µf 350v*	10 for £1.00
10µf 25v	20 for £1.00
22µf 16v	20 for £1.00
100µf 25v	20 for £1.20
160µf 25v*	20 for £1.50
330µf 25v	10 for £1.00
400µf 40v*	8 for £1.00
470µf 25v	10 for £1.00
470µf 35v	8 for £1.00
1000µf 35v	6 for £1.00
1000µf 40v*	5 for £1

*Axial. All others are Radial.

SPECIAL OFFERS

100 Assorted Polyester Capacitors. Mullard C296's and others 160v-400v only **£2.00**

100 Assorted Mullard C280's Cosmetic imperfections etc. **£2.00**

200 Mullard Miniature Electrolytics Cosmetic imperfections etc. **£2.00**

PACK OF EACH £5.00

12V BULBS on leads. Suitable for most **VIDEO RECORDERS**. **70p each 4 for £2**

CAR RADIO SUPPRESSOR KIT
 Comprises: in line aerial suppressor, power lead suppressor and clock/accessory suppressor. With leaflet. **£1.95 each, 10 for £12**
Further Discount on large quantities

CAN TYPES

22µf 375v (3 pin)	50p
50µf 250v (3 pin)	50p
100µf 350v	80p
2000µf 100v	£1.00
1000µf 100v	60p
2,200µf 40v	60p
2,200µf 63v	70p
3,500µf 35v	50p
220µf 400v ITT/RBM	£1.00
6,800µf 70v	£1.00
10,000µf 25v	£1.00

"MITSUMI" MINIATURE ROTARY UHF TUNERS
 Single nut fixing as used in various JAP portables **£3.95**
 "Mitsumi" varicap tuner "AM-UF-125" **£4.95**

SPECIAL OFFER
PHONO PLUGS, metal with plastic tops. Red, grey or black. **20 of ONE colour £1**
20 of EACH colour £2.50
100 of ONE colour £4
100 of EACH colour £10

SPECIAL OFFER
LIGHTWEIGHT STEREO HEADPHONES. Good quality with 3.5mm stereo jack plug. **£2.95 each, £25 for 10**. Further discount available on large quantities.

ZENER DIODES
 0v7, 2v7, 4v3, 4v7, 5v6, 6v2, 6v8, 7v5, 27v, 30v. ALL 400mw.
 10 of one value **80p**
 10 of each **£6.60**
 1.3 watt, 12v, 13v, 18v, 47v
 10 of one value **£1.00**
 10 of each **£3.00**

DIODES

25 x 1N4002	£1.50
100 for £2.50	
20 x 1N4003	£1.00
100 for £3.00	
20 x 1N4005	£1.50
100 for £5.00	
20 x 1N4148	£1.00
100 for £2.50	
10 x BYX10	£1.00
12 x BY127	£1.00
8 x BY255 (3A 1,300V)	£1.00
10 x BA158 (600v 400ma)	£1.00
1N5402 3a 200v	8 for £1.00
6A. 100V. Bridge Rectifier.	
Very small.	80p ea. 3 for £2.00

I.C.'s

CA270AE	£1.00	6 for £5.00
MC1327P	£1.00	6 for £5.00
TBA120SB	50p each	5 for £2.00
TBA820	£1 each	6 for £5.00
TBA810P	£1.00	6 for £5.00
555 Timer 30p		4 for £1.00
TAA661B	£1.00	6 for £5.00
SN76660N	50p	5 for £2.00

THORN SPARES

"3500" Transductor	£1.20, 3 for £3.00
"8500" Focus Assembly, Rotary type	£1.50, 3 for £4.00
"8500". 0022 2000v Line Capacitor	10 for £1.00
"1590/91" Portable metal boost Diode (W11)	5 for £1.00
"1500" Bias Caps 160µf 25v	20 for £1.50
"1500" Jellypot. L.O.P.T. Pinkspot	£3.50
"900/950" 3 stick triplers	£1.00, 3 for £2.50
"950" Can. 100 x 300 x 100 + 16µf	£1.00

THYRISTOR CONVERGENCE POTS

SS106 (BT106)	75p each	5Ω, 10Ω, 20Ω, 30Ω, 50Ω, 100Ω.
3 for £2.00, 10 for £5.50		200Ω, 1K. 8 of one type £1.00, 8 of each type £6.00.

V.C.R. BATTERY PACKS.
HITACHI PORTABLE V.C.R. Nicad pack. Type VTBP60E **£20 each**. Brand New and Boxed **3 for £50**

THORN "VIDEOSTAR" 3V25/26 Nicad pack. Type VA214. Also suitable for J.V.C. etc. Brand new and boxed. **£20 each, 3 for £50**.

THORN "VIDEOSTAR" Nicad packs. Same as above but secondhand, untested. Contain 10 "C" size Nicads (HP11) which can be replaced if necessary. **£10 each, 3 for £25**.

MISCELLANEOUS

BG100 tripler for CV45 etc. **only £3.50**

Line output transformer for **RBM823A** **£4.25 each, 3 for £10.00**

ITT VC200 4P/B Transistor Tuner. Suitable for some Pye and Philips sets. 3 hole fixing **£2.75 each**

Decca Bradford Tuner. 5 button type **£4.00 each, 4 for £12.00**

UHF Modulator UHF out Video in. Ch. 36. 2" x 2" x 1/4" complete with 9 foot coaxial lead and plug. With connection data **£3.00 each, 3 for £5.00**

GEC Hybrid 2040 series Focus Assembly with lead and VDR rod **£2.00 each, 3 for £5.00**

Convergence Panel for above. Brand new leads and plug. **£3.00 each**

GEC 2010 Transistor Rotary Tuner with AE, SKT, and leads **£1.95 each, 3 for £5.00**

Bush CTV 25 Quadrupler type Q25B equivalent to ITT TU25 3QK **£3.00 each, 2 for £5.00**

Focus VDR Rods 2" x 1/4". Suitable for GEC, Decca etc. **75p each, 3 for £2.00**

Grundig UHF/VHF Varicap Tuner for 1500GB, 3010GB. **£12.50 each, 3 for £30.00**

EHT Cable **30p per metre, 10 metres £2.50**

4.433 Mhz CTV Crystals **70p each, 3 for £2**

75Ω 2 1/2 Loudspeaker **60p each, 4 for £2**

6 MHz sound filters, ceramic 3 pin "TAIYO" type **50p each, 3 for £1.00**

PYE CT200 Control Knobs **8 for £1.00**

Degaus VDRs. 1 1/2" diam, for RBM etc. **5 for £1.00**

Mains Neons **10 for £1.00**

2k2 Screened Resistors. White ceramic, 9 watt, with fusible link. **8 for £1.00**

E.H.T. Discharge probe, with heavily insulated handle, with lead and chassis connector. **£1 each, 3 for £2.50**

UNIVERSAL TEST LEAD KIT
 Comprises: Red and black meter leads with 12 interchangeable probes, clips, points, plugs etc with screw threads. **ONLY £2.50**

I.C. EXTRACTING TOOLS


Small	90p	Large	£1.20
-------	-----	-------	-------

SMART ALUMINIUM FINISHED 1/2" SHAFT KNOBS
 3/8" diam. Ideal for TV or Hi-Fi. **10 for £1 100 for £8**

GEMINI ELECTRONIC COMPONENTS

Dept. TV, 48, Deptford Broadway, London S.E.8.

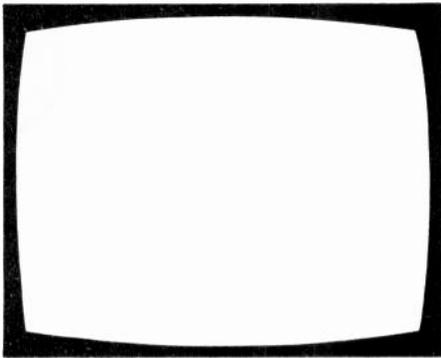Please quote ZED code where shown. Send cheque* or Postal Order. Add 60p P&P and 15% VAT.
 *Schools etc. SEND OFFICIAL ORDER. Allow up to 28 days for delivery. Most orders despatched same day.
ZED PACKS now available for CALLERS at 50 Deptford Broadway, London, S.E.8.
 Send large S.A.E. for list of Quantity, Prices and Clearance Lines etc.



TELEVISION

April
1984

Vol. 34, No. 6
Issue 402

COPYRIGHT

©IPC Magazines Limited, 1984. Copyright in all drawings, photographs and articles published in *Television* is fully protected and reproduction or imitation in whole or in part is expressly forbidden. All reasonable precautions are taken by *Television* to ensure that the advice and data given to readers are reliable. We cannot however guarantee it and we cannot accept legal responsibility for it. Prices are those current as we go to press.

CORRESPONDENCE

All correspondence regarding advertisements should be addressed to the Advertisement Manager, "Television", King's Reach Tower, Stamford Street, London SE1 9LS. Editorial correspondence should be addressed to "Television", IPC Magazines Ltd., King's Reach Tower, Stamford Street, London SE1 9LS.

SUBSCRIPTIONS

An annual subscription costs £11 in the UK, £12 overseas (by surface mail). Send orders with payment to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex, RH16 3DH.

BINDERS AND INDEXES

Binders (£4.50) and Indexes (45p) can be supplied by the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Prices include postage and VAT. In the case of overseas orders, add 60p.

BACK NUMBERS

Some back issues are available from the Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF at £1.20p inclusive of postage and packing.

QUERIES

We regret that we cannot answer technical queries over the telephone nor supply service sheets. We will endeavour to assist readers who have queries relating to articles published in *Television*, but we cannot offer advice on modifications to our published designs nor comment on alternative ways of using them. All correspondents expecting a reply should enclose a stamped addressed envelope. Requests for advice on dealing with servicing problems should be directed to our Queries Service. For details see our regular feature "Service Bureau". Send to the address given above (see "correspondence").

this month


- 297 **Leader**
- 298 **Notes on the Rigonda VL100** *Malcolm Burrell*
Large numbers of these 6in. Russian monochrome portables were imported into the UK. They are robustly constructed but tend to be put on one side when anything goes wrong because of the Russian transistors etc. used. Notes on the circuitry employed, transistor substitutes and possible fault conditions.
- 300 **Next Month in Television**
- 303 **Wideband UHF Preamplifier** *Roger Bunney*
The emphasis in this design is on low noise, which for best results is more important than a high gain figure.
- 304 **Teletopics**
News, comment and developments.
- 306 **VCR Clinic**
Reports on VCR servicing and fault conditions from Steve Beeching, T.Eng. (C.E.I.), Derek Snelling and Mike Phelan.
- 308 **All About Field Strength** *Harold Peters*
How field strength is measured, how to make use of the measurements and how to convert them to voltage at the aerial socket. Covering both terrestrial and satellite transmissions and the relationship between field/signal strength and receiver performance.
- 312 **Sensing out Faults** *Tony Thompson*
How to make maximum use of your senses in seeking the causes of fault conditions.
- 313 **Book Notice**
Recent books on the techniques used in VCRs.
- 314 **Letters**
- 316 **This Little Ting Here** *Les Lawry-Johns*
The customers decided to wait and have a fag whilst Les sorted out the Z718 whose tuning was up the creek.
- 318 **VCR Servicing, Part 27** *Mike Phelan*
The 3V24's capstan servo, still/slow and edit start systems.
- 320 **The B & K 467 CRT Tester/Reactivator** *Eugene Trundle*
Test report on this impressive instrument that even boosts Trinitron tubes.
- 322 **TV Fault Finding**
Notes on TV faults and servicing procedures from Richard Roscoe, John Coombes, Tony Thompson and M.S. Barakat.
- 324 **Long-distance Television** *Roger Bunney*
Reports on DX reception and conditions and news from abroad. Plus how to receive ATV transmissions.
- 327 **Service Bureau**
- 328 **Test Case 256**

OUR NEXT ISSUE DATED MAY WILL
BE PUBLISHED ON APRIL 18

MANOR SUPPLIES

NEW MKV PAL COLOUR TEST GENERATOR FOR TV & VCR

TEST DEMONSTRATIONS AT 172 WEST END LANE

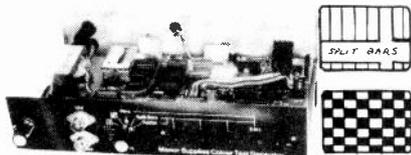

- ★ 40 different patterns and variations.
- ★ Broadcast transmission accuracy (fully interlaced sync pulses with correct picture blanking).
- ★ EBU colour bars, BBC colour bars, whole rasters & split bars (specially useful for VCR service), white, yellow, cyan, green, magenta, red, blue and black.
- ★ Chequerboard.
- ★ Mono outputs with border castellations, cross hatch, grey scale, vertical lines, horizontal lines and dots.
- ★ UHF modulator output plugs straight into receiver aerial socket.
- ★ Additional video output for CCTV & VCR.
- ★ Facilities for sound output.
- ★ Easy to build kit. Only 2 adjustments. No special test equipment required.
- ★ Mains operated with stabilised power supply.
- ★ All kits fully guaranteed with back-up service.
- ★ Also available with VHF Modulator.

Price of Kit **£80.50**
 De Luxe Case (10" x 6" x 2 1/2") **£8.50**
 Optional Sound Module (6MHz or 5.5MHz) **£4.50**
 Built & Tested in De Luxe Case including Sound Module **£120.75**


SPECIAL TEST REPORT TELEVISION DEC. 1982

Post/Packing £2.50

All above prices include VAT 15%

PAL COLOUR BAR GENERATOR (Mk4)

4TH SUCCESSFUL YEAR

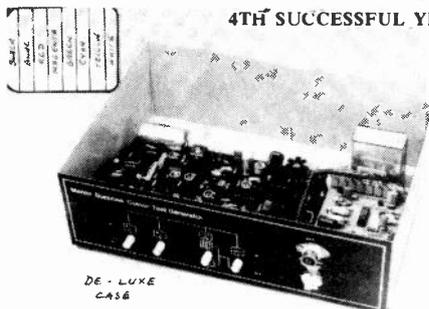

- ★ Output at UHF, applied to receiver aerial socket.
- ★ In addition to colour bars R-Y, B-Y etc.
- ★ Cross-hatch, grey scale, peak white and black level.
- ★ Push button controls, battery or mains operated.
- ★ Simple design, only five i.c.s on colour bar P.C.B.

PRICE OF MK 4 COLOUR BAR GENERATOR KIT **£34.50**. DELUXE CASE **£8.50**. BATT HOLDERS **£3.20**. MAINS SUPPLY KIT **£4.80** (Combined P&P **£1.80**).

MK 4 DE LUXE (BATTERY) BUILT & TESTED **£66.70** + **£1.80** P & P.
 MK 4 DE LUXE (MAINS) BUILT & TESTED **£78.20** + **£1.80** P & P.
 VHF MODULATOR (CHI to 4) FOR OVERSEAS **£6.60**.
 EASILY ADAPTED FOR VIDEO OUTPUT & C.C.T.V.
 (ALL PRICES INCLUDE 15% VAT)

MANOR SUPPLIES TELETEXT ADAPTOR KITS

MK 1 (Texas XMII) Cable remote control **£158.70** p.p. **£2.80**.
 MK 2 (Philips/Mullard) Infra-red remote control **£198.40** p.p. **£2.80**.

Further details on request. Tel 01-794 8751/7346

Goods available if in stock immediately over shop counter (Mail order between 3 days and 1 week from receipt of order).

TV SERVICE SPARES

BACKED BY TWENTY YEARS EXPERIENCE & STAFF OF TECHNICAL EXPERTS

TELEVISION MAGAZINE PROJECT PARTS

COLOUR PORTABLE TV
 MONO PORTABLE TV, SMALL SCREEN MONITOR
 LISTS AVAILABLE, PANEL TEST SERVICE

PHILIPS UHF MODULATOR (AUDIO & VIDEO INPUT) **£17.25** p.p. **£1.00**.
 MULLARD TELETEXT DECODER + INTERFACE suitable for Thorn, TX10 **£69.00** p.p. **£1.80**. (Decoder only **£57.50** p.p. **£1.80**).
 SAW FILTER IF AMPLIFIER PLUS TUNER COMPLETE AND tested for T.V. SOUND & VISION **£32.80** p.p. **£1.20**.
 THORN TX9, TX10 SAW FILTER IF PANEL **£9.80** p.p. **80p**.
 PAL DECODER KIT FOR RGB MONITORS **£31.00** p.p. **£1.00**.
 SPECIAL OFFER TEXAS XMII TELETEXT DECODER NEW & TESTED, AT REDUCED PRICE **£46.00** p.p. **£1.60**.
 PHILIPS-PYE G11 TYPE TELETEXT DECODERS **£28.75** p.p. **£1.60**.
 TELETEXT 23 BUTTON DE-LUXE HEADSET WITH 5 YDS. CABLE **£7.80** p.p. **£1.20**. XMII STAB. POWER SUPPLY **£4.40** p.p. **£1.20**.
 CROSS HATCH UNIT KIT, AERIAL INPUT TYPE, INCL. T.V. SYNC AND UHF MODULATOR. BATTERY OPERATED. ALSO GIVES PEAK WHITE & BLACK LEVELS. CAN BE USED FOR ANY SET **£12.65** p.p. **60p**. (ALUM CASE **£2.90** DE LUXE CASE **£5.50** p.p. **£1.20**).
 ADDITIONAL GREY SCALE KIT **£3.35** p.p. **45p**.
 UHF SIGNAL STRENGTH METER KIT **£23.00** (VHF version also available). ALUM CASE **£2.90** DE LUXE CASE **£8.50** p.p. **£1.80**.
 CRT TESTER & REACTIVATOR PROJECT KIT FOR COLOUR & MONO **£32.20** p.p. **£2.80**.
 BUSH Z718 BC6100 SERIES IF PANEL **£5.75** p.p. **90p**.
 BUSH A816 IF PANEL (SURPLUS) **£1.90** p.p. **90p**.
 DECCA 80, SERIES, IF, FRAME T.B. **£5.75** each p.p. **£1.40**.
 DECCA 80, LINE SCAN UNIT salvaged **£11.50** each p.p. **£2.00**.
 GEC 2040 Convergence panels, Decoder panels **£2.88** each p.p. **£1.80**.
 GEC 2040 IF PANELS **£3.22** p.p. **£1.60**.
 THORN TX9 PANELS ex factory for small spares. Includes I.C.s & Semiconductors etc. **£5.75** p.p. **£2.00**.
 THORN TX9 PANELS salvaged ex factory for spares incl. LOPT & mains transformers **£11.50** p.p. **£2.80**.
 THORN TX9 PANELS ex factory salvaged complete cond **£23.00** p.p. **£2.80**.
 THORN TX10 T.B. PANELS salvaged ex factory **£17.25** p.p. **£3.00**.
 THORN TX10 SIGNAL BOARDS salvaged ex factory **£17.25** p.p. **£2.00**.
 THORN 3000 LINE T.B., PCB **£5.75** each p.p. **£1.30**.
 THORN 8000/8500 IF/DECODER PANELS salvaged **£3.70** p.p. **£1.80**.
 THORN 8000/8500 FRAME T.B. PANELS salvaged/spares **£2.88** p.p. **£1.40**.
 THORN 9000 SERIES TOUCH TUNE REMOTE CONTROL UNIT PLUS ULTRASONIC TRANSMITTER HANDSET **£19.32** p.p. **£1.84**.
 THORN 9000 IF/DECODER PANELS Salvaged **£5.75** p.p. **£1.60**.
 PHILIPS G8/G9 IF/DECODER Panels for small spares **£1.75** p.p. **£1.40**.
 G8 Decoder panels salvaged **£4.25**. Panels for spares **£2.00** p.p. **£1.40**.
 G9 Scan Panel. Basic PCB in fibreglass **£16.68** p.p. **£1.80**.
 GRUNDIG 8630 Series Varicap Tuners **£7.82** p.p. **£1.00**.
 VARICAP, U321, U322, ELC 1043/06 ELC 1043/05 **£7.82** p.p. **80p**; G.I. type (equiv. 1043/05) **£4.00** p.p. **60p**. MAKERS VARICAP CONTROLS Pye CT200 4PSN **£8.60**, A823 4PSN **£5.50**, Decca 6PSN **£6.70** p.p. **80p** etc.
 SPECIAL OFFER ELEVEN POSITION VARICAP CONTROL UNIT UHF/VHF **£2.10** p.p. **£1.00**.
 BUSH "Touch Tune" Varicap Control Z179, Z718 types **£4.40** p.p. **95p**.
 VARICAP UHF-VHF ELC 2000S, ELC2060 **£11.30** p.p. **90p**.
 VARICAP VHF MULLARD ELC 1042, PHILIPS, BUSH **£7.95** p.p. **80p**.
 UHF/625 Tuners, many different types in stock. DECCA Bradford 5 position **£2.88** p.p. **£1.80** etc.
 T.V. SOUND IF Panels **£7.82** p.p. **£1.00**.
 LOPT TESTER Service Dept approved **£17.82** p.p. **£1.20**.
 LOPTS NEW & GUAR. P/P Mono **£1.35p**, Colour **£1.45p**, Bobbins **80p**.
 BUSH 161 to 186 (twin panel) **£6.80**
 BUSH, MURPHY 774 series **£9.80**
 BUSH, MURPHY A816 series **£9.80**
 FERG., HMV, MARCONI, ULTRA 950, 1400, 1500, 1580, 1590, 1591 **£6.80**
 THORN 1600, 1615, 1690, 1691 **£10.50**
 GEC 2000 to 2038 series **£7.80**
 GEC series 1 & 2 **£9.20**
 INDESIT 20/24EGB **£8.80**
 ITT/KB VC 200, 300 **£8.80**
 MURPHY 1910 to 2414 (twin panel) **£6.80**
 PHILIPS 170, 210, 300 SERIES **£8.80**
 PYE, INVICTA, EKCO, FERR. 368, 169, 569, 769 series **£8.80**
 SPECIAL OFFER
 DECCA 2024, 1700, 2000, 2401 **£4.40**
 GEC 2114J/Junior Fineline **£3.25**
 PYE 40, 67 **£2.00**
 KB VC ELEVEN (003) **£2.00**
 KB VCI **£3.25**

R.B.M. A823 **£5.60**
 R.B.M. Z179 **£11.30**
 R.B.M. T20, T22 **£11.30**
 R.B.M. T20, T22 Bobbin **£6.44**
 DECCA Bradford (state Mod No.) **£10.15**
 DECCA 80, 100 **£10.15**
 GEC 2028, 2040, 2100 **£6.70**
 GEC 2110 Series **£12.20**
 ITT CVC 5 to 9, CVC20 **£11.30**
 ITT CVC25, CVC30 series **£10.15**
 PYE 691-697 **£11.50**
 PYE 713, 715 **£7.85**
 PYE 725 (90°) 731 to 741 **£10.60**
 PHILIPS G8 **£10.15**
 PHILIPS G9 **£11.30**
 PHILIPS 570, 571 **£7.85**
 THORN 3000/3500 SCAN, EHT **£7.85**
 THORN 8000/8500/8800 **£14.80**
 THORN 9000 to 9600 **£14.80**
 THORN 9800 **£21.90**

OTHERS AVAILABLE, PRICES ON REQUEST. ALSO F.O.P.TS.
 TRIPLERS Full range available. Mono & Colour.
 Special Offer: Thorn 1400 5 stick EHT Tray **£1.72** p.p. **65p**.
 TRANSDUCTORS suitable for G8, A823, Bradford etc. **£1.72** p.p. **60p**.
 6-3V CRT Boost Transformers **£5.80**, Auto Type **£3.20**, p.p. **£1.20**.
 CALLERS WELCOME AT SHOP PREMISES
 THOUSANDS OF ADDITIONAL ITEMS, ENQUIRIES INVITED
 LARGE SELECTION TESTED COLOUR PANELS POPULAR MODELS
 Telephone 01-794 8751, 794 7346

MANOR SUPPLIES

172 WEST END LANE, LONDON, N.W.6.

NEAR: W. Hampstead Tube Stn. (Jubilee) Buses 28, 159, C11 pass door
 W. Hampstead British Rail Stns. (Richmond, Broad St.) (St. Pancras, Bedford)
 W. Hampstead (Brit. Rail) access from all over Greater London.
 Mail Order: 64 GOLDERS MANOR DRIVE, LONDON N.W.11.
 ALL PRICES INCLUDE VAT AT 15%

BI-PAK

VALUE PACKS

Pak No.	Qty	Description	Price
VP1	300	Assorted Resistors Mixed Types	£1.00
VP2	300	Carbon Resistors 1/2 Watt Pre-Formed	£1.00
VP3	200	1/2 Watt Min Carbon Resistors Mixed	£1.00
VP4	150	1/2 Watt Resistors 100 ohm - 1M Mixed	£1.00
VP5	200	Assorted Capacitors All Types	£1.00
VP6	200	Ceramic Caps Miniature - Mixed	£1.00
VP7	100	Mixed Ceramic Disc. 1pf - 56pf	£1.00
VP8	100	Mixed Ceramic Disc. 68pf - .015pf	£1.00
VP9	100	Assorted Polyester/Polystyrene Caps	£1.00
VP10	60	C280 Type Caps Metal Foil Mixed	£1.00
VP11	100	Electrolytics - All Sorts	£1.00
VP12	60	Bead Type Polystyrene Min Caps	£1.00
VP13	50	Silver Mica Caps Ass. 5.6pf - 150pf	£1.00
VP14	50	Silver Mica Caps Ass. 180pf - 4700pf	£1.00
VP15	50	High Voltage Disc. Ceramic 750v - 8Kv Mixed	£1.00

BI-PAK'S OPTO SPECIAL

A selection of large and small sized LED's in various shapes, sizes & colours, together with 7 Segment Displays both anode & cathode plus photo transistors, emitters and detectors. Cadmium Cell ORP12 and Germ. photo transistor OCP71 included. In all a total of 25 Opto pieces valued over £12 Normal Price.

Order No. VP57
Our Super Value Price Just **£5.00**



VALUE PACKS

Pak No.	Qty	description	Price
VP28	10	Rectangular 2" Green LED'S	£1.00
VP29	30	Ass. Zener Diodes 250mW - 2W Mixed Vts. Coded	£1.00
VP30	10	Ass. 10W Zener Diodes Mixed Vts. Coded	£1.00
VP31	10	5 Amp SCR's T0-66 50-400v Coded	£1.00
VP32	20	3 Amp SCR's T0-66 Up To 400v Uncoded	£1.00
VP33	200	Sil. Diodes Switching Like IN4148 DD-35	£1.00
VP34	200	Sil. Diodes Gen. Purpose Like OA200/BAX13/16	£1.00
VP35	50	1 Amp IN4000 Series Sil. Diodes Uncoded All Good	£1.00
VP36	8	Bridge Rects. 4 x 1 Amp 4 x 2 Amp Mixed Vts. Coded	£1.00
VP37	8	Black Instrument Type Knobs With Pointer 1" Std	£1.00
VP42	10	Black Heatsinks To Fit T0-3, T0-220 Ready Drilled	£1.00
VP43	4	Power-Fin Heatsinks 2 x T0-3 2 x T0-66 Size	£1.00
VP44	1	Large Power Heatsink 90 x 80 x 35 mm Drilled For Up To 4 T0-3 Devices	£1.00
VP45	50	BC107/8 Type NPN Transistors Good Gen. Purpose Uncoded	£1.00
VP46	50	BC177/8 Type PNP Transistors Good Gen. Purpose Uncoded	£1.00
VP47	10	Silicon Power Trans. Similar 2N3055 Uncoded	£1.50

SILICON BRIDGE RECTIFIERS

Comprising 4 x 1/2 Amp rectifiers mounted on PCB. VRM - 150 vts IFM - 1.5 Amps

Size: 1 inch square
10 off **£1.00**
50 off **£4.50**
100 off **£7.50**

ORDER NO: 4R1 B Rect.

VP38 100 Silicon NPN Transistors - All Perfect. Coded Mixed Types With Data And Eqvt. Sheet No Rejects. Fantastic Value **£3.00**
VP39 100 Silicon PNP Transistors - All Perfect. Coded Mixed Types With Data And Eqvt. Sheet No Rejects. Real Value**£3.00**


IC BARGAINS

VP40	30	Assorted 74 Series TTL I.C.'s Gates, Flip-Flops & M.S.I.'s + Data Book. All New. Normal Retail Value Over £8.00. Our Price	£2.50
VP41	30	Assorted CMOS I.C.'s CD4000 Series Pack Includes 00/09/12/14/18/21/23/25/28/30/35/44/58 AY/AE Types Plus Data Sheet Value Over £8.00. Normal retail	£2.50

RATCHET SCREWDRIVER KIT

Comprises 2 standard screwdriver blades 5 & 7mm size. 2 cross point size 4 & 6. 1 Ratchet handle. 5-in-1 Kit **£1.45 each.** O/No 329B

HYBRID LED COLOUR DISPLAYS

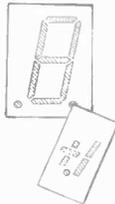

Red, Green, Yellow - 3/5/6 inch Mixed types and colours
NUMERIC & OVERFLOW
Common Anode/Cathode. GaAsP/GaP.

Brand New, Full Data incl.
10 pieces (our mix)**£4.00**
Normal Retail Value Over £10.00
Order No. VP58

VALUE PACKS

Pak No.	Qty	Description	Price
VP16	50	Wirewound Res. 9W (avg) Ass. 1 ohm - 12K	£1.00
VP17	50	Metres PVC Covered Single Strand Wire Mixed Colours	£1.00
VP18	30	Metres PVC Covered Multi Strand Wire Mixed Colours	£1.00
VP19	40	Metres PVC Single/Multi Strand Hook-Up Wire Mixed	£1.00
VP20	6	Rocker Switches 5 Amp 240v	£1.00
VP21	20	Pcs. 1 - 2 & 4 mm Plugs & Sockets Matching Sizes	£1.00
VP22	200	Sq. Inches Total, Copper Clad Board Mixed Sizes	£1.00

VALUE PACKS

Pak No.	Qty	Description	Price
VP23	20	Assorted Slider Pots. Mixed Values	£1.00
VP24	10	Slider Pots. 40 mm 22K 5 x Log 5 x Lin	£1.00
VP25	10	Slider Pots. 40 mm 47K 5 x Log 5 x Lin	£1.00
VP26	20	Small .125" Red LED'S	£1.00
VP27	20	Large 2" Red LED'S	£1.00

TRANSISTOR CLEARANCE

100 All Sorts Transistors. A mixed Bag NPN-PNP Silicon & Germ. Mainly Uncoded You To Sort Pack Includes Instructions For Making Simple Transistor Tester. Super Value. Order No VP60 **£1.00**

Send your orders to Dept. 74
BI-PAK PD BOX 6
3, BALDOCK ST
WARE HERTS



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail. Remember you must add VAT at 15% to your Total order. Postage add 75p per Total order.



FREE CAREER BOOKLET

Train for success in Electronics Engineering, T.V. Servicing, Electrical Engineering—or running your own business!

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the fields of electronics, T.V., electrical engineering—now it can be your turn. Whether you are a newcomer to the field or already working in these industries, ICS can provide you with the specialised training so essential to success.

Personal Tuition and 80 Years of Success


The expert and personal guidance by fully qualified tutors, backed by the long ICS record of success, is the key to our outstanding performance in the technical field. You study at the time and pace that suits you best and in your own home.

You study the subjects you enjoy, receive a formal Diploma, and you're ready for that better job, better pay.

TICK THE FREE BOOKLET YOU WANT AND POST TODAY

ELECTRONICS ENGINEERING

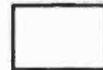A Diploma Course, recognised by the Institute of Engineers & Technicians as meeting all academic standards for application as an Associate.



T.V. & AUDIO SERVICING

A Diploma Course, training you in all aspects of installing, maintaining and repairing T.V. and Audio equipment, domestic and industrial.



ELECTRICAL ENGINEERING

A further Diploma Course recognised by the Institute of Engineers & Technicians, also covering business aspects of electrical contracting.



RUNNING YOUR OWN BUSINESS

If running your own electronics, T.V. servicing or electrical business appeals, then this Diploma Course trains you in the vital business knowledge and techniques you'll need.



Name

Address

ICS ICS
Dept EG144,
160 Stewarts Road,
London SW8 4UJ.



01-622 9911
(all hours)

P. V. TUBES

Just phone your order through, we do the rest.



Telephone: Accrington (0254) 36521
Accrington (0254) 32611

SUPPLIERS OF TELEVISION COMPONENTS

38A WATER STREET, ACCRINGTON, LANCS BB5 6PX.

TRADE COUNTER OPEN MON-FRI 9 a.m.—5 p.m. SAT 9.30 a.m.—5 p.m.

INTEGRATED CIRCUITS				T.T.L. 74LS SERIES									
AN240	3.84	MSN5807	7.87	74LS00	50	74LS37	19	74LS92	35	74LS160	60	74LS251	54
AN214Q	3.91	MS1513L	2.80	74LS02	50	74LS38	20	74LS93	35	74LS161	60	74LS252	1.00
AN715Q	3.97	MS1515L	3.28	74LS03	50	74LS40	20	74LS94	20	74LS162	85	74LS257	53
CA555	46	SAS560S	1.89	74LS04	50	74LS42	36	74LS95	20	74LS163	60	74LS258	67
CA741	25	SAS570S	1.89	74LS05	50	74LS47	80	74LS96	20	74LS164	65	74LS259	74
CA748	45	SAS580	2.80	74LS08	50	74LS48	80	74LS97	20	74LS165	65	74LS273	80
CA3065	1.80	SAS590	2.90	74LS09	50	74LS49	80	74LS98	20	74LS166	65	74LS274	74
LA4031P	3.21	SL901B	5.50	74LS10	50	74LS51	19	74LS99	20	74LS167	65	74LS283	50
LA4102	3.37	SL917B	6.50	74LS11	50	74LS54	19	74LS00	20	74LS168	65	74LS284	50
LA4250	3.57	SL1310	1.80	74LS13	50	74LS55	19	74LS01	20	74LS169	65	74LS285	1.14
LA4400	3.05	SL1327Q	1.20	74LS14	50	74LS56	19	74LS02	20	74LS170	65	74LS286	1.50
LA4422	3.28	SL7654A	2.05	74LS15	19	74LS57	28	74LS03	20	74LS171	65	74LS287	36
LC7130	5.93	SN76033N	2.49	74LS16	19	74LS58	28	74LS04	20	74LS172	65	74LS288	36
LC7120	5.87	=SN76013N	2.83	74LS17	19	74LS59	28	74LS05	20	74LS173	65	74LS289	36
LC7137	5.50	SN76023N	2.00	74LS18	19	74LS60	28	74LS06	20	74LS174	65	74LS290	36
LM1303N	2.63	SN76110N	1.15	74LS19	19	74LS61	28	74LS07	20	74LS175	65	74LS291	36
HA1151	3.89	SN76115N	2.27	74LS20	19	74LS62	28	74LS08	20	74LS176	65	74LS292	36
MC1307	1.99	SN76131N	2.00	74LS21	19	74LS63	28	74LS09	20	74LS177	65	74LS293	36
MC1310P	1.60	SN76226(DN)	2.00	74LS22	19	74LS64	28	74LS10	20	74LS178	65	74LS294	36
MC1327	1.70	SN76227N	1.18	74LS23	19	74LS65	28	74LS11	20	74LS179	65	74LS295	36
MC1351P	2.93	SN76532N	1.50	74LS24	19	74LS66	28	74LS12	20	74LS180	65	74LS296	36
MC1330P	90	SN76533N	1.70	74LS25	19	74LS67	28	74LS13	20	74LS181	65	74LS297	36
MC1349	1.99	SN76033N	2.49	74LS26	19	74LS68	28	74LS14	20	74LS182	65	74LS298	36
MC1350	1.50	SN76544N	2.35	74LS27	19	74LS69	28	74LS15	20	74LS183	65	74LS299	36
MC1352	1.75	SN76650N	80	74LS28	19	74LS70	28	74LS16	20	74LS184	65	74LS300	36
MC1358P	1.50	SN76660N	1.05	74LS29	19	74LS71	28	74LS17	20	74LS185	65	74LS301	36
MC1495L	3.00	SN76666N	80	74LS30	19	74LS72	28	74LS18	20	74LS186	65	74LS302	36
MC14011BCP	66	SN76530A	1.47	74LS31	19	74LS73	28	74LS19	20	74LS187	65	74LS303	36
MC14094UB	43	S/153	2.74	74LS32	19	74LS74	28	74LS20	20	74LS188	65	74LS304	36
ML231/ETTR6016		TA7050P	95	74LS33	19	74LS75	28	74LS21	20	74LS189	65	74LS305	36
		TA7051P	95	74LS34	19	74LS76	28	74LS22	20	74LS190	65	74LS306	36
MC232	2.20	TA7074P	1.00	74LS35	19	74LS77	28	74LS23	20	74LS191	65	74LS307	36
ML236	5.35	TA7108P	3.43	74LS36	19	74LS78	28	74LS24	20	74LS192	65	74LS308	36
ML237	2.50	TA7120P	2.43	74LS37	19	74LS79	28	74LS25	20	74LS193	65	74LS309	36
ML238	6.00	TA7129AP	3.76	74LS38	19	74LS80	28	74LS26	20	74LS194	65	74LS310	36
ML239	2.50	TA7130P	1.93	74LS39	19	74LS81	28	74LS27	20	74LS195	65	74LS311	36
ML920	4.12	TA7141P	95	74LS40	19	74LS82	28	74LS28	20	74LS196	65	74LS312	36
ML922	3.29	TA7193P	5.67	74LS41	19	74LS83	28	74LS29	20	74LS197	65	74LS313	36
ML926	2.18	TA7171P	1.85	74LS42	19	74LS84	28	74LS30	20	74LS198	65	74LS314	36
ML928	2.18	TA7172P	1.85	74LS43	19	74LS85	28	74LS31	20	74LS199	65	74LS315	36
MRF475	2.50	TA7173P	1.85	74LS44	19	74LS86	28	74LS32	20	74LS200	65	74LS316	36
MRF477	10.00	TA7176P	2.50	74LS45	19	74LS87	28	74LS33	20	74LS201	65	74LS317	36
		TA7202P	4.27	74LS46	19	74LS88	28	74LS34	20	74LS202	65	74LS318	36
		TA7204P	3.77	74LS47	19	74LS89	28	74LS35	20	74LS203	65	74LS319	36
		TA7205AP	3.72	74LS48	19	74LS90	28	74LS36	20	74LS204	65	74LS320	36
		TA7208P	3.40	74LS49	19	74LS91	28	74LS37	20	74LS205	65	74LS321	36
		TA7210P	6.60	74LS50	19	74LS92	28	74LS38	20	74LS206	65	74LS322	36
		TA7222	2.42	74LS51	19	74LS93	28	74LS39	20	74LS207	65	74LS323	36
		TA7223P	3.74	74LS52	19	74LS94	28	74LS40	20	74LS208	65	74LS324	36
		TA7227P	5.98	74LS53	19	74LS95	28	74LS41	20	74LS209	65	74LS325	36
		TA7228P	5.98	74LS54	19	74LS96	28	74LS42	20	74LS210	65	74LS326	36
		TA7310P	2.78	74LS55	19	74LS97	28	74LS43	20	74LS211	65	74LS327	36
		TA7609P	4.39	74LS56	19	74LS98	28	74LS44	20	74LS212	65	74LS328	36
		TA7611AP	2.92	74LS57	19	74LS99	28	74LS45	20	74LS213	65	74LS329	36
		TA7613P	5.8	74LS58	19	74LS00	20	74LS46	20	74LS214	65	74LS330	36
		TA7614P	2.8	74LS59	19	74LS01	20	74LS47	20	74LS215	65	74LS331	36
		TA7615P	2.83	74LS60	19	74LS02	20	74LS48	20	74LS216	65	74LS332	36
		TA7616P	2.83	74LS61	19	74LS03	20	74LS49	20	74LS217	65	74LS333	36
		TA7617P	2.83	74LS62	19	74LS04	20	74LS50	20	74LS218	65	74LS334	36
		TA7618P	2.83	74LS63	19	74LS05	20	74LS51	20	74LS219	65	74LS335	36
		TA7619P	2.83	74LS64	19	74LS06	20	74LS52	20	74LS220	65	74LS336	36
		TA7620P	2.83	74LS65	19	74LS07	20	74LS53	20	74LS221	65	74LS337	36
		TA7621P	2.83	74LS66	19	74LS08	20	74LS54	20	74LS222	65	74LS338	36
		TA7622P	2.83	74LS67	19	74LS09	20	74LS55	20	74LS223	65	74LS339	36
		TA7623P	2.83	74LS68	19	74LS10	20	74LS56	20	74LS224	65	74LS340	36
		TA7624P	2.83	74LS69	19	74LS11	20	74LS57	20	74LS225	65	74LS341	36
		TA7625P	2.83	74LS70	19	74LS12	20	74LS58	20	74LS226	65	74LS342	36
		TA7626P	2.83	74LS71	19	74LS13	20	74LS59	20	74LS227	65	74LS343	36
		TA7627P	2.83	74LS72	19	74LS14	20	74LS60	20	74LS228	65	74LS344	36
		TA7628P	2.83	74LS73	19	74LS15	20	74LS61	20	74LS229	65	74LS345	36
		TA7629P	2.83	74LS74	19	74LS16	20	74LS62	20	74LS230	65	74LS346	36
		TA7630P	2.83	74LS75	19	74LS17	20	74LS63	20	74LS231	65	74LS347	36
		TA7631P	2.83	74LS76	19	74LS18	20	74LS64	20	74LS232	65	74LS348	36
		TA7632P	2.83	74LS77	19	74LS19	20	74LS65	20	74LS233	65	74LS349	36
		TA7633P	2.83	74LS78	19	74LS20	20	74LS66	20	74LS234	65	74LS350	36
		TA7634P	2.83	74LS79	19	74LS21	20	74LS67	20	74LS235	65	74LS351	36
		TA7635P	2.83	74LS80	19	74LS22	20	74LS68	20	74LS236	65	74LS352	36
		TA7636P	2.83	74LS81	19	74LS23	20	74LS69	20	74LS237	65	74LS353	36
		TA7637P	2.83	74LS82	19	74LS24	20	74LS70	20	74LS238	65	74LS354	36
		TA7638P	2.83	74LS83	19	74LS25	20	74LS71	20	74LS239	65	74LS355	36
		TA7639P	2.83	74LS84	19	74LS26	20	74LS72	20	74LS240	65	74LS356	36
		TA7640P	2.83	74LS85	19	74LS27	20	74LS73	20	74LS241	65	74LS357	36
		TA7641P	2.83	74LS86	19	74LS28	20	74LS74	20	74LS242	65	74LS358	36
		TA7642P	2.83	74LS87	19	74LS29	20	74LS75	20	74LS243	65	74LS359	36
		TA7643P	2.83	74LS88	19	74LS30	20	74LS76	20	74LS244	65	74LS360	36
		TA7644P	2.83	74LS89	19	74LS31	20	74LS77	20	74LS245	65	74LS361	36
		TA7645P	2.83	74LS90	19	74LS32	20	74LS78	20	74LS246	65	74LS362	36
		TA7646P	2.83	74LS91	19	74LS33	20	74LS79	20	74LS247	65	74LS363	36
		TA7647P	2.83	74LS92	19	74LS34	20	74LS80	20	74LS248	65	74LS364	36
		TA7648P	2.83	74LS93	19	74LS35	20	74LS81	20	74LS249	65	74LS365	36
		TA7649P	2.83	74LS94	19	74LS36	20	74LS82	20	74LS250	65	74LS366	36
		TA7650P	2.83	74LS95	19	74LS37	20	74LS83	20	74LS251	65	74LS367</	

P. V. TUBES

REPLACEMENT ELECTROLYTICS		
PYE 169 (200/200/100/32)	3.40	
PHILIPS 320 (400/400/200V)	2.07	
DECCA 30 (400/400/350V)	3.40	
DECCA 80 (400/350V)	3.00	
DECCA 100 (800/250V)	3.97	
DECCA 1700 (200/200/400/350V)	4.83	
PHILIPS G8 (600/300V)	2.30	
PHILIPS G9 (600/300V)	2.21	
PHILIPS G11 (470/250V)	2.90	
PYE 691/7 (200/300/350V)	2.70	
PYE 731 (600/300V)	2.31	
RBM A823 (2500/2500/30V)	1.66	
RBM A823 (600/300V)	2.83	
RBM Z146 (300/300/350V)	3.55	
RR1 T20A (220/400V)	2.00	
ITT CVC5/9 (200/200/75/25)	2.98	
ITT CVC 20 (220/400V)	2.00	
GEC 2110 (800/250V)	1.94	
GEC 2040 (1000/2000/35V)	1.19	
GEC 2040 (300/300/150/100/50)	4.10	
THORN 3500 (400/400)	3.78	
THORN 950 (1100/300/100/16/275V)	1.83	
THORN 1400 (150/100/100/150/320V)	2.79	
THORN 1500 (150/150/100/300V)	2.20	
THORN 1500 (12/300V)	3.1	
THORN 3500 (175/100/100/400/350V)	2.31	
THORN 3500 (1000/63V)	86	
THORN 3500 (1000/70V)	86	
THORN 8000/8500 (2500/2500/63V)	3.38	
THORN 8000/8500 (700/250V)	2.31	
THORN 8000/8500 (400/350V)	2.56	
THORN 9000 (400/400V)	3.28	
GEC (200/200/150/50)	2.64	
PHILIPS 69 2200/63V	1.25	
THORN 4700 P/C 25V	1.20	
PHILIPS 320 400/400/200V	2.74	
THORN 1591/1691 4700/25V	1.20	

CAPACITORS		
Volts	Mfd	Price
6V3	33	9
10V	22	10
	47	10
	100	10
	220	15
	470	20
16V	33	11
	68	11
	220	16
	1000	27
330V	53	10
25V	10	11
	22	13
	47	15
	100	15
	220	29
	470	30
	1000	55
	2200	51
470V	98	10
40V	10	10
	22	10
	400	48
63V	1	12
	2.2	12
	4.7	12
	10	11
	15	12
	22	13
	47	19
	100	23
	220	37
	470	49
	1000	98
	2200	94
100V	10	13
	22	15
	47	20
	100	36
	220	70
450	1	33
	4.7	30
	10	30
	22	65
	33	75
	47	32
	600	41

DISC CERAMIC CAPACITORS		
8kV (12kV /Mlg)		
39pF 200pF each		
150pF 220pF 40p		
180pF 250pF		

CERAMIC CAPACITORS		
63V A range of pref. values	each	
22pF-4700pF	6p	

SPECIAL DIDDIES		
SKE 49	£1.09	
SKE 5F	£1.19	
Y723	£1.30	
Y827	£1.42	

MIXED DIELECTRIC CAPS		
Volts D.C.		
250V 0.91mF	84	
400V 0.22mF	29	
600V 0.1mF	38	
1000V 0.01mF	24	
0.047mF	46	
0.033mF	33	
0.1mF	35	
0.22mF	66	
0.47mF	98	
1250V 0.1mF	59	
0.91mF	1.15	
1500V 0.0022mF	28	
0.0047mF	32	
0.022mF	30	
0.033mF	62	
0.005mF	65	
2000V 0.0052mF	1.20	

ELECTRONIC TUNERS AND ASSEMBLIES		
Mullard ELC1043/05	8.40	
Mullard ELC1043/06	8.40	
4 P/B DECCA/GEC/ITT	6.88	
6 P/B DECCA/GEC/ITT	7.50	
4 P/B PYE	9.00	
6 P/B PYE	16.00	
PHILIPS G8 Tuner	10.50	
PHILIPS G8 Ass. (Square/Early)	13.50	
PHILIPS G8 Ass. (Sloping/Late)	13.90	
PHILIPS G9 Tuner	10.50	
PHILIPS G11 Tuner	9.00	
ITT/PYE/GEC 7 Button P/B	13.95	
GEC 2110 6 way P/B	7.98	
U321 UHF Tuner	7.50	
THORN 8800 SELECTOR (HMV Model 2725/6 way round button)	7.50	
THORN 9000 SELECTOR	13.40	
U322	7.20	
HITACHI 4 way Chan. Selector (Also Rank A823)	10.75	
Splitter	1.70	
Surface Mount. Outlets 80	11.00	
Cable Clips per 100 1.18		
Coax Plugs per 10 1.80		
P.V.C. Tape	35	
F.M. Plugs	25	
PL259 Plugs	40	
Line Connectors	35	
Reducers for PL259	16	
T.V. Filter 50db Rejection	8.25	
27mhz	2.10	
Attenuators 6db, 12db, 18db	1.80	
Top Tenna Set	2.30	
Aerial	1.80	
M.H.A./P.U. the pair	2.00	
Aerial Isolator Kit	2.00	
4m Fly Lead	1.20	
2m Fly Lead	90	

SWITCHES		
4A Double Pole On/Off Switch		
General Purpose Push/Push	75	
Philips G8 Push On/Off Switch	1.38	
4A Double Pole Rotary On/Off	66	
A1 Beam Switch (THORN 3500)	70	
GEC 2110 A1 Control IMS (Red, Blue, Green)	58	
GEC 2040 On/Off Switch	88	
On/Off Switch G11/G12	1.58	
On/Off Switch GEC/TCE TX9/10	1.06	

SLIDER POTENT		
Lin or Log		
470R-1K-2K2-44-		
10K-47K-470K	65	

SKELETON PRE-SET POTS		
Standard or miniature		
Horizontal or Vertical		
100R-2M2	16p	

PANELS + UNITS		
AFC UNIT PHILIPS G8	8.82	
IF GAIN MODULE (Pye/Philips)	9.00	
CDA PANEL (Pye/Invicta/Ecko/Dynatron)	20.00	
REAR CONVERGENCE PANEL (Philips G8)	23.00	

MIDGET CONTROLS		
Insulated Spindle Length 44mm		
Log or Lin Without Switch		
5K-10K-25K-50K-100K-250K-500K-1M	39p	
With D.P.S.T. Switch		
Log: 5K-10K-25K-50K-100K	81p	
250K, 500K, 1M, 2M		
Dual ganged Controls	1.25	
16mm Rotary Controls 10K, 22K, 100K, 1M, 10K 39p		

THERMAL CUT OUT		
THORN 3000 2A Metal	1.60	
GEC 2040 Metal	2.50	
THORN 8000 Plastic	2.35	

MULTITURN POTS		
100K	55	
GEC TCE	55	
PHILIPS G8		
DECCA, RANK	55	

THICK FILM RESISTOR NETWORK		
THORN 3500 (5 pin connection)	1.98	
PYE 731 (6 pin connection)	2.20	
THORN 9000 (Circuit Ref. R704/7)	1.98	

EAGLE PRODUCTS		
Please send large S.A.E. for full EAGLE Catalogue		
DF615 Full Range Speaker 6"	8.95	
Multimetres		
KE-W 7N	2,000	5.25
KE-W 20		14.50
EM5	5,000 opv	9.95
EM10	10,000 opv	11.50
EM50	50,000 opv	19.95
EMC321 Carrying Case for above		2.25
Digital Meter TS1000		44.50
MM20	20,000 O.P.V.	21.95
MM50	50,000 O.P.V.	25.95
MM100	100,000 O.P.V.	36.50
MMT20		16.95
Case for MM100		15.95
T1206 2 Station Intercom		6.95

DATA BOOKS (No VAT)		
Transistor Equivalent		
TVT 80 A-Z only	3.75	
TVT 80 2N/2S series only	4.00	
TVT 80/80 A-Z and 2N/2S together	7.50	
LIN IC Books LIN 1	5.95	
LIN 2	5.95	

P.V. MICROCOMPUTER CENTRE		
Why not pay us a visit and see our range of Micros, Software Books and Peripherals. Please ring for prices.		
Spectrum 16K	Vic 20	Sharp
48K	Commodore 64	Oric
	Atari 800	Dragon
Texas	Lynx	
Quantity discounts on application (Trade Only). Minimum of 5.		

FUSES		
Per type	Pack of 10	
1 1/2" QUICK BLOW		
100ma	73	
250ma-500ma-750ma-1A	66	
1.5A-2A-2.5A-3A-5A	60	
1 1/2" ANTISURGE		
250ma, 500ma, 600ma, 630ma, 750ma, 850ma, 1A, 1.25A	1.70	
1.5A, 2A	2.70	
2.5A, 3A, 5A		
20mm ANTISURGE		
80ma	4.80	
100ma	2.50	
160ma, 200ma	2.20	
315ma, 500ma, 630ma, 800ma, 1A, 1.25A, 1.5A, 2A	1.30	
2.5A, 3.15A	1.90	
20mm QUICK BLOW		
100ma, 250ma, 500ma, 630ma, 800ma	90	
1A, 1.25A, 1.6A, 2A, 2.5A, 3.15A, 5A	60	
1" MAINS		
2A, 3A, 5A, 10A, 13A	1.00	

AERIAL ACCESS		
Surface Mount.	1.70	
Splitter	1.70	
Surface Mount. Outlets 80	11.00	
Cable Clips per 100 1.18		
Coax Plugs per 10 1.80		
P.V.C. Tape	35	
F.M. Plugs	25	
PL259 Plugs	40	
Line Connectors	35	
Reducers for PL259	16	
T.V. Filter 50db Rejection	8.25	
27mhz	2.10	
Attenuators 6db, 12db, 18db	1.80	
Top Tenna Set	2.30	
Aerial	1.80	
M.H.A./P.U. the pair	2.00	
Aerial Isolator Kit	2.00	
4m Fly Lead	1.20	
2m Fly Lead	90	

SUNDY TUNER ACCESS.		
RANK Tuner P.B.		
1 1/2" x 1/2" x 1/2" x 1/2"	35	
RANK Drive Cams	10	
GEC 2110 Tuner Neons	14	

SUNDRIES		
Delay Lines DL60, DL700, DL50	2.20	
CRT Tube Base	70	
EHT Final Anode Cap	53	
EHT Cable	25p mtr	
6.3V CRT Boost Trans.	4.35	
13A Plug Top	box 10 4.80	
Quick Set Adhesive	78	
Moulded Plastic Hex. 6mm Trim Tools	10	
Double End 4mm/8mm Trim Tools 20		
Focus Rod	1.25	
Focus Holder	2.00	
Keynector Safe Block (mains)	7.00	
Cassette Drive Belts price each		
35mm	35	
46mm	37	
57mm	37	
66mm	35	
71mm	41	
76mm	42	
90mm	50	
110mm	50	
Torch (handy for tool box)	1.18	
I.C. Inserter	40	
SM Neon Screwdriver	22	
DIN Plugs 3 pin	22	
4 pin	22	
5 pin	20	
Stnd. 5 pin	28	
Phono Plug	12	
Car Aerial Plug	18	
2.5mm Jack Plug	14	
3.5mm Jack Plug	11	
Stnd Jack Plug	20	
Stereo Jack Plug	36	
5A Connector Block (12)	4	
Fuse Wire 5A-15A-30A	5	
Battery Plug Thorn TVs	28	
Mains Connector 4 way 13A	5.00	

BATTERIES RECHARGEABLE		
RX6 - HP7/NN1500	1.39	
RX14 - SP11/HP1/NN1400	2.17	
RX20 - SP2/HP2/NN1300	2.34	
RX22 - PP3/NN1604	4.69	

VIDEO/AUDIO		
VHS E30	3.06	
VHS E60	4.00	
Scotch E120 Video Tape	5.00	
Scotch E180 Video Tape	5.13	
BETA L500	4.90	
BETA L750	5.80	
PHILIPS VCC 240	6.20	
PHILIPS VCC 360	8.30	
PHILIPS VCC 480	10.21	
PHILIPS LVC 1700	15.70	

VIDEO CASSETTE CASES		
Red/Blue/Green/Brown		80
Book Type - Any Format		
video Heads		
3HSS	38.00	
4HSS	38.00	
PS3B	42.00	
Video Recorder Heads		
Philips V2000	52.00	

ELECTROLUBE PRODUCTS		
Electrolube Adhesive	62	
Electro-Mech lubricant	1.49	
Elect. cleaning solvent	1.62	
Freezer	1.49	
Foam cleanser	1.12	
Heat transfer compound	1.14	
Silicone compound	1.94	
Special contact fluid (Snorkel) 3.20		
Permagard	1.52	
Elec. mech lubricant pen	74	

TEST EQUIPMENT		
Portable Oscilloscope	155.00	
Probes x10	10.90	
CRT Tester/Rejuvenator	172.00	
KHP30 Measuring Probe (3 okw)	29.95	
EHT	29.95	
T120 RF Signal Injector	4.00	
Test Lead Set	4.20	
Degaussing Coil (stick type)	17.00	
Degaussing Coil (disc type)	24.00	


INCREASE YOUR PROFITS IMPROVE YOUR SERVICE WITH RELIABLE COST EFFECTIVE TEST EQUIPMENT

**LEADER LCT-910A
C.R.T. TESTER-REJUVENATOR**

Our top selling instrument is designed to readily test the various characteristics and rejuvenation of both colour and B/W C.R.T's.

- ★ Tests for shorts and leakage between electrodes.
- ★ Tests cathode emission characteristics.
- ★ Separately checks condition of guns.
- ★ Removal of shorts and leakage between electrodes.
- ★ Checks heater warm-up characteristics.
- ★ Rejuvenation of low emission cathodes with automatic timing.
- ★ Super rejuvenation with manual control.
- ★ Complete with tube base adaptors.

Size: H 230mm W 330mm D 120mm.

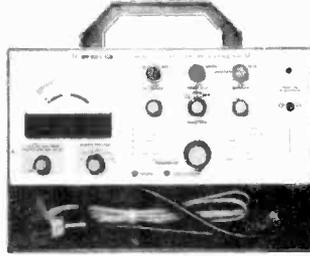


PRICE £175 + £26.25 VAT

LOPT TESTER

BK's REVOLUTIONARY DYNAMIC 'LOPT' TESTER
Revolutionary L.O.P.T. tester. Operates in dynamic mode which actually tests the L.O.P.T. under high voltage conditions without de-soldering or removal.
Size 75x100x40 mm. Supply 240V AC


PRICE £25.99 + £3.VAT

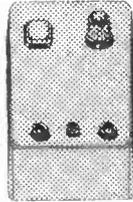


CRT TESTER-REJUVENATOR

BK's C.R.T. TESTER-REJUVENATOR
Tests and rejuvenates blue, green & red guns separately. Fitted with delta and P.I.L. sockets. Compact size 120 x 65 x 60 mm. Supply 240V AC

PRICE £32.00 + £4.80VAT

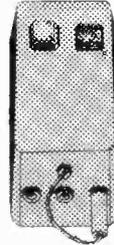

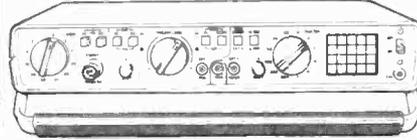THE VERY LATEST SC110A LOW POWER, FULLY PORTABLE OSCILLOSCOPE.



The new Thandar SC110A represents a break-through in oscilloscope development. The SC110A is ONLY TWO INCHES thick and weighs under two pounds, yet retains the standard features and FITS IN A BRIEFCASE

Full Sized Performance

- 10 MHz bandwidth
- Full trigger facilities are provided including TV frame, or TV filtering
- Runs on 4 to 10V DC via disposable batteries, re-chargeable cells, or AC adaptor.
- Size 255mm x 148mm x 50mm.

PRICE £165.00 + £24.75 VAT


Accessories Carry Case £8.98 + £0.89 V.A.T.
x 1 Probe £7.00 + £1.05 V.A.T.
x 10 Probe £8.00 + £1.20 V.A.T.
x 1 x 10 Switched Probe. £8.50 + £1.42 V.A.T.
Rechargeable Batteries £11.00 + £1.65 V.A.T.
AC Adaptor £8.98 + £1.04 V.A.T.

HAMEG HM 203-4 20MHz DUAL TRACE OSCILLOSCOPE

SPECIFICATION:

- *BANDWIDTH DC-20MHz
- *SENSITIVITY CH1,CH2 2mV-50V/DIV
- *TIMERASE 40ns to 0.2S CM
- *TRIGGER DC-40MHz. Auto-Normal-TV
- *CALIBRATION OUTPUT
- *CH1 ADD AND INVERT FACILITY
- *ALT/CHOP SWITCH
- *LARGE RECTANGULAR SCREEN 8 x 10 cms.
- *BUILT IN SEMICONDUCTOR COMP. TESTER
- *SIZE 285mm x 145mm x 380mm.
- *SUPPLY 110-125-220-240V AC 50-60Hz

2 YEAR WARRANTY

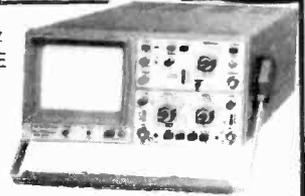


WITH COMPONENT TESTER

PRICE £264.00 + £39.60 VAT
Optional probes as above

LEADER HIGH VOLTAGE METER EHT PROBE

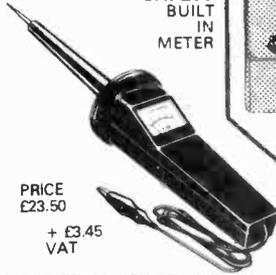Measures up to 40 K.V. D.C. with SAFETY BUILT IN METER



PRICE £23.50 + £3.45 VAT

* FULLY GUARANTEED

U.K. Post Paid, Export orders welcome, please deduct V.A.T. and enquire for Overseas carriage cost. Barclaycard/Access orders welcome, or Cheque, Bank Draft, etc., with order please. Large S.A.E. for technical leaflets of complete range. Delivery normally within 7 days.



B. K. ELECTRONICS Dept. 'T'

UNIT 5, COMET WAY, SOUTHEND-ON-SEA, ESSEX. SS2 6TR TEL: 0702-527572



**CUSTOMER CAN'T PAY?
DONT LOSE HIM FIT A TV METER**



COINAGE AVAILABLE
10p
50p
£1

COMPLETELY VARIABLE TIMINGS

Alberice METERS LIMITED

MANUFACTURERS OF TV COIN OPERATED METERS CONTACT (0202) 674272
87-89 Sterte Avenue,
Poole, Dorset. BH15 2AW.
Telex: 418253 LUMIC G

Switch to the biggest wholesaler of quality late model used TV's

- Thousands of Quality Sets always in stock
- Colour/Mono/VCR's and Audios available
- Murphy/Pye/Philips/Sony/National Panasonic and other big names
- We are big - we buy in bulk - we offer you the keenest prices
- Cash and Carry or we will deliver
- New and used stands always in stock

VISIT OUR NEW SHOWROOM TODAY OR RING US ON
0562 743735


CAMPION THOMPSON
ELECTRICAL WHOLESALERS

TRADE ONLY

Incorporating



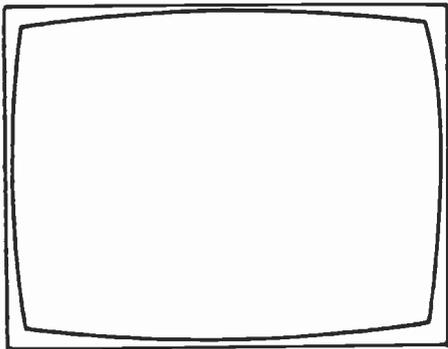Campion House, Franchise Street, Kidderminster, Worcestershire DY11 6RE



TELEVISION

The Skills Required

At the end of last month's leader I commented that there's probably no harm in manufacturing under licence rather than undertaking the original research. The subject deserves to be kicked around a bit more, since it has great relevance to the UK's present industrial condition and where we go from here.

The point I wished to make was that there's no advantage to be gained from a bone-headed insistence on being scientifically or technologically self-sufficient. At the other extreme, to abandon research and come to rely entirely on imported technology, becoming in the process a nation of odd-jobbers for multinational companies based elsewhere, won't do either. To cut ourselves off from original technological development would in the long run be asking to cease to be a country with a substantial industrial base. The problem is what sort of balance to strike, how to allocate funds, resources and know-how, and in deciding what's worth doing and what's best left to others. There is also the interesting business of joint venture efforts, which can be quite different from simply manufacturing under licence.

The history of the UK's television industry has been a rather mixed one. There's been plenty of research and development, but not quite the same degree of success with applied technology for mass production. The UK did not develop a colour TV system, neither has it developed a VCR system. It did however pioneer TV development initially, played a major role in the application of solid-state technology to TV receiver use, developed teletext and viewdata and, more recently, the MAC system for satellite transmission. Plenty of R and D then, but not all along the line. This is as it should be. The world would have been no better a place with a UK colour or VCR system to add to the confusion in these fields. The basic technology here can be had under licence agreement. It's beneficial however if one has something to offer in return.

Joint venture agreements in the fullest sense involve two-way collaboration, with both sides contributing to the technology involved. Merely assembling bought in kits on the other hand means opting out of the technology concerned. An interesting example of a joint venture with technological commitment on both sides was highlighted last month – RCA and Hitachi's collaboration over the CED disc system. Joint venture arrangements that involve technical collaboration end up with both sides having a foot in the research department door.

It's not always easy to get at the full details of such joint ventures – they must, after all, be subject to a degree of commercial secrecy. But this sort of arrangement is an important way in which a country with limited means and technological resources can keep in touch with technical development. Provided of course one is in a position to offer technological collaboration. What one needs here above all else is qualified manpower. And this seems to be something of a problem.

UK universities are at present producing some 2,000 electronics and electrical graduates a year. This is nothing like enough, and is appalling in view of the hopes placed on the electronics industry in particular for future industrial regeneration. Plessey alone is on record as stating that it would like to employ another 700 graduates "in the electronics and other numerate disciplines". The company has reached the point where it has had to send recruiting officers to Australia and New Zealand and advertise on the continent. Plessey's personnel director Parry Rogers thinks that "the situation of skill shortages will get worse, and threatens to become the major limiting factor in our growth".

There is something deeply disturbing about this. Shortage of trained manpower affects not only companies like Plessey, which tend to do much of their own R and D work: it also affects the prospects for joint venture operations, whose importance for a country such as the UK we've just noted. A recent paper on foreign investment in the UK, produced by the Royal Institute of International Affairs, pointed out that one of the main attractions of the UK has been the availability of "scientific skills". It seems that this means much more to a foreign multinational company contemplating investment in the UK than the offer of hand-outs to locate plants in depressed areas. It may be that we have a just adequate pool of skilled people to meet current needs, but it's quite clear that the government and the educational authorities have been doing nothing like enough to ensure an adequate supply of trained personnel to meet future needs.

Unfortunately the problem doesn't stop with the need for a few more new graduates and technicians. The skills required are increasingly of a wider variety than numeracy and a specialist degree or certificate. Creative engineering ability tends to come with experience and means the ability to see opportunities in business and production terms as well as basic technological ones. How many engineers are there who've taken a course in business studies? The need is possibly for some restructuring of higher education. We need only look to certain other countries to see how it can be done. There are also some perhaps less obvious aspects of the need for a wide range of skills. There's been a fascinating correspondence recently in the *Financial Times* on the need for engineers to be able to speak Japanese. We tend to think of English as the international language of electronics, as indeed it is, but if you have to talk business to a senior Japanese engineer you will soon appreciate the importance of being able to do so in his own tongue. The significance of this in making joint venture agreements work is clear enough. But how many engineering degree courses include Japanese as an option? It's not entirely unknown, but hardly commonplace!

EDITOR

John A. Reddihough

ASSISTANT EDITOR

Luke Theodossiou

ART EDITOR

Roy Palmer

ADVERTISEMENT MANAGER

Roy Smith
01-261 6671

CLASSIFIED ADVERTISEMENTS

Barbara Blake
01-261 5897

COVER PHOTO

Our cover photo this month shows the aerials in use on Roger Bunney's lattice mast at Romsey, Hants. At the top a double stacked Triax BB u.h.f. grid system which is also at present being used for ATV reception. Lower down there's a 13-element wideband Triax Band III array, an omnidirectional Triax 88-108MHz f.m. array and a three-element wideband Band I array.

NEXT MONTH

Watch out for next month's bumper issue – see page 300 for details.

Notes on the Rigonda VL100

Malcolm Burrell

These small (6in. tube) monochrome portables have been around for many years and were imported in considerable quantities. I've not had a lot to do with them but recently I wanted a small set for use as a simple video monitor. I bought a couple of VL100s in pieces and set about getting one of them going. Whilst most shops are reluctant to handle these sets, you quite often come across one in the corner of a workshop. The problem is lack of information and the Russian components with markings that tend to cause confusion. This is a bit of a pity. Although the design is very basic, they are interesting sets that can in most cases be repaired quite economically provided the tube is known to be good. The Television Tube Shop advertises the tubes at £14 plus VAT, and even this major replacement could still be a viable proposition.

The first point to note when servicing these sets is the Russian symbols for the transistor connections. As near as we can get, K is the collector, b the base and 3 the emitter (sometimes the shield as well).

Power Supply Circuits

The mains unit screws to the rear and supplies about 14V d.c. to the input socket at the back. If you haven't got one, it should be a fairly straightforward item to build. Alternatively a 12V car battery can be used.

The input from the mains unit or battery is fed to a series regulator which provides a 10.5V supply to operate the set. The bulk of this circuit lives on the top panel, with adjustment provided by R132. This is set for 10.5V at the collector of T27 (later version, see Fig. 2), which is mounted on a heatsink at the rear.

The main difference between the two versions of this chassis (Models VL100 and VL100M) lies in the power supply, see Fig. 1. In the earlier version a simple emitter-follower T26, with feedback to its base, drives the series regulator transistor T27. Three transistors are used in the later version. T30 provides sensing, driving the emitter of T26 by emitter-follower action. T27 is the series regulator as before.

Excessive voltage with a hum bar may well indicate a fault in the regulator. Check the transistors – the types don't seem to be very critical and things like the BC142 or

BFY50 (npn) and the BC143 or 2N2905 (pnp) work well for the smaller types while a TIP32 can be used for T27 with modifications to the mounting.

The Signals Side

On the r.f. side, the rotary u.h.f. tuner can be one of two or three types and tends to occupy quite a large area within the set. In some versions there's a separate preamplifier stage. The main i.f. strip employs three transistors followed by a diode detector. The sound signal is extracted at the collector of the video driver transistor. There are two intercarrier sound amplifier transistors followed by a ratio detector. The five-transistor audio circuit uses a two-transistor class A output stage. While the video driver/output transistors, the audio driver and the a.g.c. transistors are npn types, the rest of the signal transistors are pnp types with their collector circuits returned to chassis.

One of the vision i.f. transistors in my rebuilt set was open-circuit. An AF117 put that right. The audio output transistors T28/29 were missing and, after replacing the bias diode D21 which was short-circuit, acceptable audio was obtained by inserting a pair of AC128s. One of the a.g.c. transistors was missing while the other was short-circuit. That good old standby the BC107 worked a treat in both positions.

A BF337 can be used in the video output transistor position (T5).

Timebase Circuits

The line output transistor T25 is mounted inconspicuously alongside the top regulator panel, which also houses the line output transformer. I was interested to see what might happen if you need to replace the line output transistor, so I wired in a TIP32 – it worked! An AU110 is reputed to work here, with possibly some alteration required to the values of the flyback tuning capacitors C81/2. The deflection power requirements are very low, due to the 70° tube with its extremely narrow neck. One bonus from this is the lack of heat developed, and I would think that most line output transistor failures are likely to be the result of the inherent problems with germanium

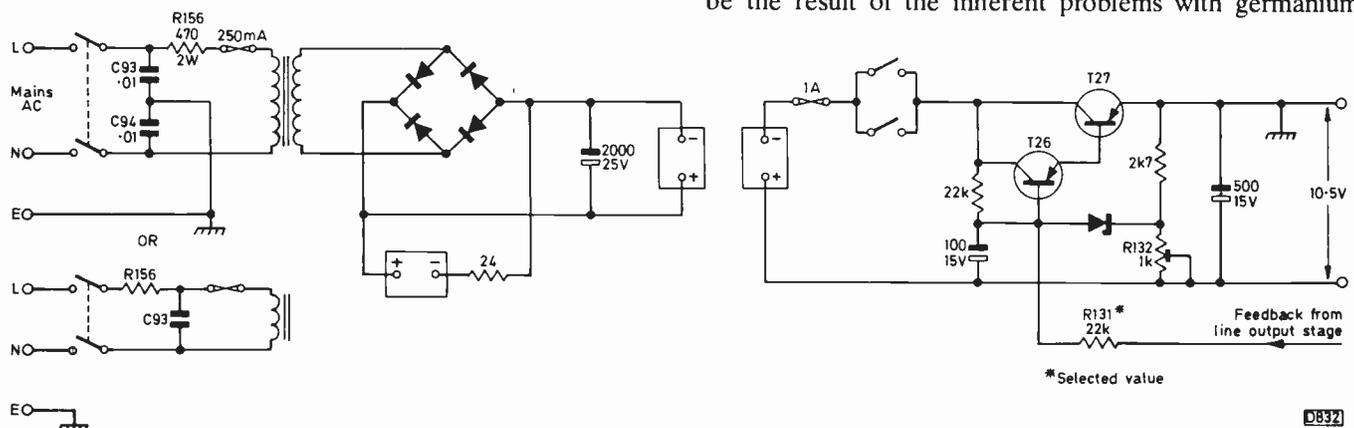


Fig. 1: Mains unit, with battery charging socket, and the earlier two-transistor series regulator circuit.

next month in

TELEVISION

● **BUMPER ISSUE**

The May *Television* will be another of our larger, 68-page issues.

● **TV PATTERN GENERATOR**

Now that off-air BBC and IBA test card transmissions are so infrequent, service engineers are having to rely increasingly on test pattern generators. Our latest design features a circle, crosshatch, grey scale, frequency gratings, colour bars, border and patterns for I.f. response and chroma delay checks etc. Most of the patterns are held in an EPROM. TTL, composite video and u.h.f. outputs are provided and construction is on PCBs.

● **PROBLEMS WITH OLDER VCRs**

Various things happen to a VCR as it gets older – basically wear of one sort or another begins to cause problems. Many dealers and rental concerns simply suggest a new machine, but with a bit of insight much can be done to get a worthwhile second lease of life from a VCR. Nick Lyons describes test and repair procedures.

● **CLASSIFICATION OF OSCILLATORS**

Oscillators are fundamental to electronics but come in a bewildering variety of forms. Despite the profusion of circuit techniques, examination of the principles of operation shows that there are only three basic types of oscillator, employing positive feedback, negative resistance, or the selective amplification of noise.

● **SERVICING FEATURES**

More fault reports in VCR Clinic and TV Fault Finding, plus Service Briefs – notes on recent Thorn and ITT chassis.

● **THE MYSTERIOUS MULLARD**

Vintage TV this time takes a look at one of the earliest Mullard sets – the single-channel, 9in. Model MTS389. One odd feature was the strange selection of valves used in the set.

PLUS ALL THE REGULAR FEATURES

ORDER YOUR COPY ON THE FORM BELOW:

TO
(Name of Newsagent)

Please reserve/deliver the May issue of TELEVISION (£1), on sale April 18th, and continue every month until further notice.

NAME

ADDRESS

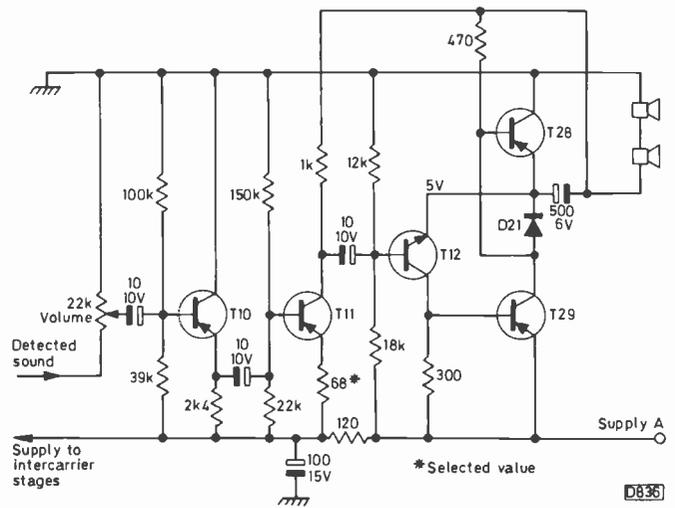


Fig. 5: The audio circuit.

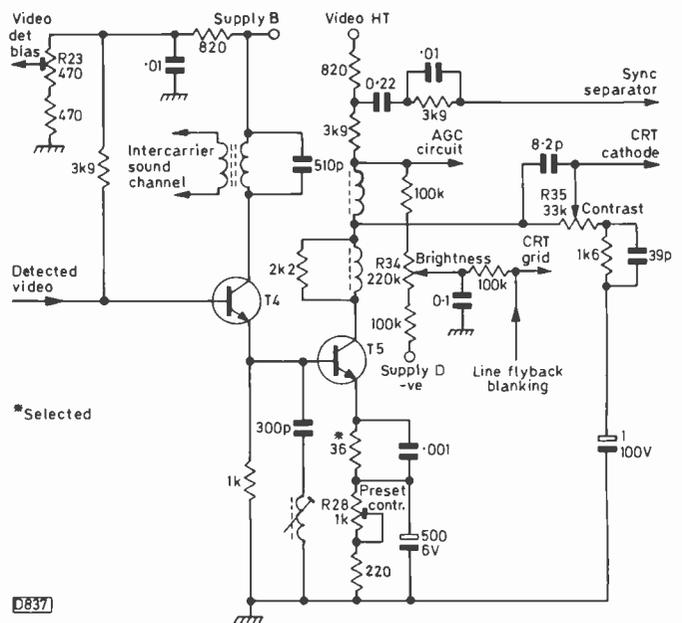


Fig. 6: Video driver and output stages.

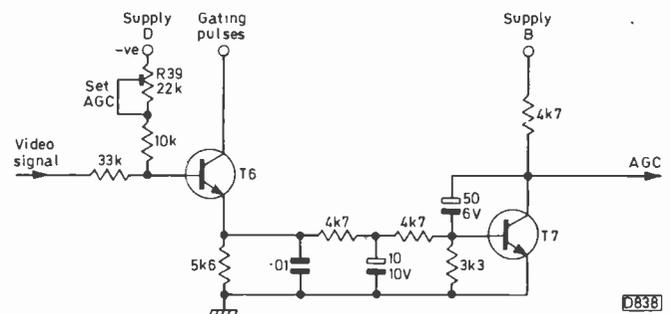


Fig. 7: A.G.C. circuit.

chassis-mounting coaxial socket – some difficulty was experienced as the tuner connections tended to foul this when the panel was hinged down. No isolation components are required.

Spare parts are available from Rigonda Supplies, 332 Cann Hall Road, London E11. Send a s.a.e. with enquiries.

These are quite nice little sets, soundly built and probably better than some small screen portables from other parts of the globe.

POST A PART ELECTRONICS

236 FURTHERWICK ROAD,
CANVEY ISLAND, ESSEX

Telephone 0268 690868

Telex 99305 ROSSER G.



TRADE COUNTER NOW OPEN

ORDERS DESPATCHED SAME DAY

ADD 60p P&P, THEN 15% VAT.

ADD POSTAGE FOR OVERSEAS ORDERS.

ORDERS WITH AEROSOLS, PLEASE ADD 25p PER CAN.

Thorn 10K 20W (3500) R751 Safety Resistor	75p
Pye 713 Speaker 5" x 3" 70Ω	1.00
Pye 713 Complete Tube Base Panel with Focus Slider & Leads	2.75
Pye 713 Control Knobs	4 for 50p
Tube Base Socket IIT CVC32	45p
Tube Base Socket Thorn 3000/8000 etc	50p
IC Inserter 16 Pin	50p
Large IC Extractor	50p
Crystal 4.43MHz	65p
EHT Lead & Cap for Split Diode Opt	90p
Anode Cap	47p
Sanyo Anode Cap Assy + Lead 12TCD-CT-16	65p
Degauss Thermistors PT37P IIT/GE/C	35p
Degauss TH9 E299D/HP230 3000/8000	25p
Casters Set of 4	1.90
Double Fuse Holder on Small Pax Board 20mm type	10p
Single Fuse Holder on Small Pax Board 20mm type	5p
Direct Panel Mounting 28mm Fuse Clips (pair)	15p
Single Fuse Holder on Small Pax Board. As per early 3000 mains input	6p
EHT Cable	Metre 25p
13A Plugs	12 for 4.80
BF259 with Heatsink	14p
TIPT10 with Heatsink	10p
LI28/130/131 Coil	10p
6MHz Ceramic Filter	25p
DL700 (Philips) Chroma Delay Line	1.00
DL50 Chroma Delay Line	1.00
T9006A Lum Delay Line	1.00
8K5/9K Lum Delay Line	65p
Plastic Cover for 3K5 SP8385	5p
TX9 Back Ground Control 10K	15p
TX9 Gain Control 100R	15p
1500 Metal Chassis Supports Pair	40p
Thorn 8K5 Focus Pot	2.40
Thorn 4000 Focus Pot	2.75
Thorn 18Ω 9W (3K5) R752	30p

SERVICE AIDS

Ambersil M54 Silicone Grease	12oz 2.15
Ambersil Freezer	12oz 1.99
Ambersil Amberlube	6oz 1.89
Ambersil Ambertron	16oz 1.95
Ambersil Anti-Static Screen Cleaner	7oz 1.95
Ambersil 40+ Protective Lubricant	14.1oz 2.15
Ambersil Amberlons Foaming Cleaner	13oz 1.25
Ambersil Circuit Lacquer	14oz 2.15

THICK FILM RESISTOR UNITS

3500 Thorn (5 Pin Connection) video	1.70
4000 Thorn (4 Pin Connection)	1.90
725/731 Pye (6 Pin Connection)	2.20
713 Pye (6 Pin Connection)	2.20

FUSES

20mm		11"	
50MA	10 for 70p	250MA	10 for 65p
315MA A/S	10 for 50p	750MA	10 for 65p
500MA	10 for 50p	7A	10 for 50p
1A	10 for 50p	10A	10 for 50p
2.5A	10 for 1.00	20A	10 for 50p
3.15A	10 for 1.00	50A	10 for 50p

Thorn Mains TX 3000/3500	7.50
Thorn Mains TX 8000/8500	10.00
Thorn S.O.P.T 8000/8500	3.50
Thorn Scan TX 3000/3500	6.00
Thorn EHT TX 3000/3500	6.00
Thorn LOPT 9600	12.00
Thorn LOPT 1615	7.25
Thorn LOPT 1580/91	7.25
Thorn LOPT 1630/91	7.25
Thorn LOPT 8000	9.80
Thorn LOPT 8500	9.80
Thorn LOPT TX9	9.85
Pye LOPT 713	10.00
Pye LOPT 725	9.85
Pye LOPT 731	10.18
Philips LOPT G9	8.80
Philips LOPT G11	13.75
GEC LOPT 3113	7.40
Diode Split LOPT AT2076/35	14.75
Sanyo LOPT AM-WM-21	6.75
Sanyo LOPT AM-WM-4	7.30
Philips LOPT G8	7.80
Sanyo LOPT (CW21) 4-2751-44700	5.00
IIT LOPT CVC5-9	9.50
IIT LOPT CVC30	8.75
IIT LOPT CVC45	9.75
Baird 8750	9.25
Baird 8752	10.25
Korting AZ9100	10.25
Korting B92-170	10.25
Korting AZ2101	10.25
Korting AZ2103	10.25
Korting ZTR1001	10.25
Siemens V1155	11.75
Siemens V1823	11.75
Zanussi BS2222	10.25
Zanussi BS2223	10.25
Salora FR0057	10.25
Salora FR0029	10.25

300 Mixed Resistors	1.50
300 Mixed Capacitors	1.50
150 Mixed Electrolytics	2.00
100 W/W Resistors	1.00
20 Mixed Conv Pots	1.00
40 Mixed Pots	1.50
20 Mixed Sliders	1.00
40 Mixed Presets	60p
20 Mixed VDR & Thermistors	1.00
20 Mixed Ferrite Cores	50p
100 Mixed Ceramic Discs	1.00
20 Mixed Valve Bases	1.00

AC128	39	BC171	9	BC558	10	BF179	29
AC131	40	BC172	9	BC559	8	BF180	33
AC138	40	BC174B	23	BC595	8	BF181	30
AC141K	39	BC177	24	BCX33	22	BF184	30
AC142K	38	BC182LB	12	BCX34	11	BF185	30
AC153	39	BC183L	12	BD115	49	BF194	16
AC176	33	BC184L	13	BD131	30	BF195	16
AC176K/	33	BC187	24	BD132	46	BF196	16
AC128K	93	BC204	15	BD133	59	BF197	15
AC188	38	BC208	9	BD139	36	BF198	15
AD142	1.18	BC212L	9	BD140	38	BF199	15
AD143	1.06	BC213L	12	BD144	1.70	BF223	18
AD149	96	BC237	12	BD163	96	BF224	19
AD161	32	BC238B	8	BD201	74	BF238	20
AD162	32	BC238L	8	BD203	78	BF240	9
AD263	1.05	BC250A	15	BD204	99	BF241	21
AF127	45	BC251	8	BD222	48	BF255	10
AF139	38	BC252A	20	BD225	52	BF256	10
AF239	41	BC294	37	BD232	50	BF257	28
AU113	2.10	BC321	60	BD233	60	BF259	28
BC107	15	BC303	31	BD234	60	BF271	25
BC108	15	BC307	10	BD237	55	BF274	11
BC109	15	BC308	8	BD238	65	BF337	29
BC115	16	BC309	14	BD241	59	BF338	34
BC117	21	BC327	18	BD244	85	BF355	40
BC125	26	BC328	18	BD278A	81	BF362	50
BC126	23	BC337	17	BD386	68	BF391	21
BC139	27	BC338	17	BD433	71	BF394	16
BC141	34	BC347	8	BD437	83	BF422	47
BC142	30	BC394	8	BD592	1.20	BF423	53
BC143	31	BC454	8	BD599	1.20	BF450	43
BC147	12	BC455	10	BD677G	1.35	BF453	53
BC148	12	BC456	10	BD707	95	BF458	37
BC149	12	BC460	10	BD708	95	BF459	40
BC153	16	BC463	22	BDX10	93	BF461	59
BC1540R	16	BC546	8	BDY20	1.09	BF566B	35
BC154YL	16	BC547	12	BDY8	1.09	BF596	15
BC157	12	BC548	12	BF137	20	BF694	16
BC158	12	BC549	8	BF153	20	BF757	62
BC159	15	BC557	10	BF154	25	BF852	31

INTEGRATED CIRCUITS

BRC1330	1.40	SN76013ND	1.80
BRC3064	1.00	SN76023N	1.80
BRC/M/200	1.00	SN76033N	2.00
BRC/M/300	1.00	SN76115	2.00
CA3060	1.58	SN76131N	1.58
LM1303P	1.48	SN76226N	1.25
ML231B	2.20	SN76227N	1.00
ML237B	2.00	SN76530P	1.00
ML239B	2.86	SN76622N	1.00
MC1327AP	1.25	SN76680N	80p
MC1358P	1.30	SN76686N	75p
MC1455P	18p	SN76744	1.92
MC14516BCP	60p	TA7117P	2.00
SAA1025	7.20	TA7109AP	2.80
SAA1124	4.50	TAA611	1.40
SAA5010	6.00	TBA120B	1.20
SL432A	1.80	TBA120C	1.20
SL1430	2.50	TBA120CQ	70p
SN15846N	60p	TBA120S	70p
SN74123N	65p	TBA120U	1.00
SN74154N	1.40	TBA395	1.00
SN76001N	1.40	TBA480Q	1.40
SN76110N	1.14	TBA510	1.90

Thorn 8/8K5 ex equip panels untested	2.88	Thorn 3/3K5 ex equip panels untested	3.75	Thorn 4000 PSU panel ex-factory	2.50
PSU	3.75	LTB	3.75	Thorn 3K5 beam limiter board	1.75
FTB	4.00	Video	2.50	Thorn 3K5 PSU bottom board	2.75
Decoder	4.00	Chroma	2.00	PC206 new	2.75
Thorn 9K ex equip panels untested	12.00	IF	1.75	Thorn 3K5 IF panel new	3.00
PSU	5.00	Conv. 3K	3.00	Thorn 3/3K5 EHT & scan TX +	1.80
Decoder	5.00	Conv. 3K5	1.75	R2008B on alum chassis ex-factory	1.80
Thorn 9K6 ex equip panel untested	5.75	Autovox Decoder FG/01 new	1.25	Thorn 8/8K5 damaged FTB for spares	1.25
Decoder	5.75	Thorn 4000 Convergence panel	3.75	Thorn 8/8K5 damaged decoder for spares	2.25

UHF TV Aerial for portable	50p	Coax Plugs	10 for 1.65
Indoor Aerial Parabolic Type Reflector	2.50	Band Change Switch Assy, Pye 725	40p
to Help Combat Ghosting Problems	30p	Flush Mounting TV/FM Diplexer	1.00
Line Connectors	30p	Switched Flush Fitting Aerial Outlet	1.00

10 Spark Gaps	1.00
10-16 pin Quil IC Socket	90p
20 Assorted TV Knobs	1.00
10-16 pin Quil to Dil IC Socket	90p
100 Mixed Diodes	1.00
50 Mixed Mica Washers	65p
300 Mixed Resistors & Capacitors	1.50
10-16 pin Dil to Dil IC Socket	1.00
50 Electrolytics & 50 Capacitors	1.00
50 Mixed Poly Capacitors	1.00
30 Mixed Neons & Bulbs	1.00

BF167	24	BF862	28	NKT276	20
BF173	29	BF871	29	NKT453	1.65
BF179	32	BF878	25	OT112	1.92
BF180	33	BF890	1.74	OT121	2.08
BF181	30	BF891	2.08	R1038	80
BF184	30	BF742	30	R1039	80
BF185	30	R2008B	1.40		
BF194	16	BFY38	40	R2010B	7.0
BF195	16	BFY50	30	R2030	1.10
BF196	16	BFY51	34	R2265	1.80
BF197	15	BFY52	34	R2305	80
BF198	15	BFY59	1.50	R2322	50
BF199	15	BRC1693	1.43	R2443	25
BF223	18	BU105	1.00	RCA1644E	1.25
BF224	19	BU126	1.10	RCA16599	1.30
BF238	20	BU207	1.05	RCA1660C	1.40
BF240	9	BU208	1.15	RCA16799	1.13
BF241	21	BU208A	1.15	RCA16800	1.42
BF255	10	BU326A	1.30	CA16802	1.28
BF256	10	BU407	1.70	SI299	2.25
BF257	28	BU408	2.76	S28000	1.25
BF259	28	BU500	2.30	S6800A/B	3.50
BF271	25	BU526	2.46	T6050V	1.30
BF274	11	BU807	2.94	T6052V	1.30
BF337	29	CI1129	9	T9003V	1.25
BF338	34	CI1728	9	T9010V	1.45
BF355	40	ES386	54	T9053V	1.30
BF362	50	E9003	28	T9054V	1.00
BF391	21	E9005	25	T9039V	1.10
BF394	16	ME0404	10	TIC45X	50
BF422	47	ME0412	10	TIC46	48
BF423	53	ME8002	10	TIC106C	40
BF450	43	MJ2501	2.36	TI229	42
BF453	53	MJ3001	2.21	TI320	42
BF458	37	MJE182	47	TI321	35
BF461	40	MJE340	50	TI332	43
BF566B	35	MJE350	50	TI333	61
BF596	15	MJE3055	15	TI342	45
BF694	16	NKT241W	8	TI3110	61
BF757	62	NKT241G	8	TI391	25
BF852	31	NKT241Y	8	ZTX550	30

1.26	DAA2030	2.10
1.00	DAA2522	2.10
1.82	DAA2530	2.61
1.50	DAA2540	3.50
2.05	DAA2560	3.50
2.50	DAA2581	3.00
2.00	DAA2591	1.95
2.49	DAA2811A	1.95
2.20	DAA2840	2.90
1.62	DAA2890A	1.50
2.08	DAA3560	6.00
1.95	DAA9603	2.90
1.92	TCEP100	3.48
1.05	TEA1009	1.95
1.05	MCI4426P	4.80
4.50	MCI4429P	4.50
1.05	MCI4514	5.00
4.00	UA758PC	2.50
3.50	UA1008A	2.66
2.72	ULN2165	1.30
1.50	ULN2216A	1.25
2.42	UPC1365C	5.75
2.76	SC9488P	1.40
2.53	SC9511P	1.40
2.80	SW153	2.50

VIDEO HEADS

MONOLITH
electronic products

RECORDER Model No.	Head Price £ + VAT	RECORDER Model No.	Head Price £ + VAT	RECORDER Model No.	Head Price £ + VAT
AKAI		HITACHI		PHILIPS	
VS9300	29.95	VT3000E	38.69	1500	54.07
VS9500	29.95	VT5000ER	38.69	1502	54.07
VS9700	29.95	VT8500E	38.69	N1700	59.50
VS9800	29.95			N1702	59.50
BUSH		JVC		N2000	59.50
BU6900A	38.95	HR3300	29.95	SANYO	
FERGUSON		HR3660EK	29.95	5000	47.24
3V00	29.95	HR7200EK	29.95	5300	47.24
3V16	29.95	PANASONIC		5600	47.24
3V22	29.95	NV2000	29.95		
3V24	29.95	NV2010	29.95		
3V30	29.95	NV366B	38.13		
		NV777B	63.64		
GRUNDIG					
SUR4004	72.45				
2000GB	63.00				


Telephone us now for details if your requirements are not on this list



Ask for our **FREE** AUDIO HEAD REPLACEMENT GUIDE and full catalogue

● Audio + Video Heads ● Motors ● Parts

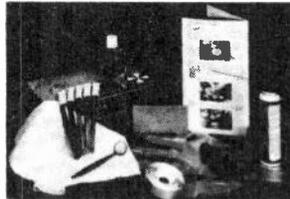UNIVERSAL VIDEO HEAD REPLACEMENT KIT £8.25



KIT CONTAINS: Eccentricity gauge, handling gloves, cleaning fluid, 5 cleaning tools, air blast, inspection mirror, antistatic cloth, screwdriver, replacement instructions, motor speed disc, service label.

£5 OFF

ON ORDERS OVER £100

PLEASE ADD VAT + £1.50 P&P PER ORDER

MOST DELIVERIES EX-STOCK BUT PLEASE ALLOW UP TO 28 DAYS.

SUPPLIER TO MOST OF THE U.K.'s LEADING DISTRIBUTORS AND SERVICE ORGANISATIONS

THE MONOLITH ELECTRONICS CO. LTD

5-7 Church Street, Crewkerne, Somerset, TA18 7HR, England
Telephone: Crewkerne (0460) 74321
Telex 46306 MONLTH G

TELETRADERS

Forde Road, Brunel Industrial Estate,
Newton Abbot, Devon
Telephone: (0626) 60154

The Best Quality Sets Available Anywhere

All First Class working order and excellent cabinets.

Bush	£25
Philips G8 550	£40
Philips G11	£85
Decca Bradford	£25
ITT CVC 58	£30
GEC Solid State	£35
Thorn 3500 Electronic 22"	£35

Full spares back-up of tubes and panels – send for list e.g. PL509 £1, PY500 £1
Bulk terms to other wholesalers



THE NO. 1 WHOLESALER IN THE SOUTH

"NORTH LONDON WHOLESALER'S" TV SALES

Example of working set prices:

GEC Hybrid £19, Decca 30 £27, 22" Philips 520 £26,
22" Philips 550 £38, Thorn 3000 £27,
19" Thorn 8500 £36, Twin Chip Bush £24.

Mono from £4 etc.

Prices for other models or non-workers on request.

Re-gunned tubes available. 5 mins. M.1.

Please telephone us for details on:—

WATFORD 45590

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfill orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, Television will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

(1) You have not received the goods or had your money returned; and
(2) You write to the Publisher of Television summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc., received as a result of answering such advertisements. Classified advertisements are excluded."

Wideband UHF Preamplifier

Roger Bunney

For minimal displayed noise (snow) on the screen, a preamplifier for use with weak signals should have the lowest possible noise figure, lower than that of the tuner's first r.f. amplifier stage. The ubiquitous OM335 hybrid preamplifier is not good enough in this respect: despite its high gain, typically 27dB, the noise figure of 6dB is somewhat above that of a u.h.f. tuner's first stage. It's a sad fact that many enthusiasts go for an amplifier with a high gain figure without considering the noise level: a 20dB gain with 5dB noise will produce degraded performance compared to a gain of 10dB with a 2dB noise figure.

The unit described in the present article was constructed for indoor use as a first-stage amplifier. It has linear operation across the u.h.f. bands, freedom from overload or instability, a lowish gain (typically 11.5dB) and a low noise figure (typically 2dB). If the amplifier is used following a mast-head amplifier there will be little improvement in weak signal performance since the system noise figure will have been set up the mast. It's vital that the first stage of electronic amplification contributes as little noise as possible.

Fig. 1 shows the circuit, which uses a BFR91 low-noise wideband amplifier transistor capable of operating at over 1GHz. With a collector current of 3mA, the noise figure at 500MHz is 1.8dB. Between 2-5mA the noise figure is under 2dB. The circuit is arranged so that Tr1 passes 4.5mA at 9V. Tr1's collector load consists of the u.h.f. choke L2 and the series damping resistor R3, the ratio of the turns to the value of R3 giving a slight lift towards the top of Band V. The value of R3 could be reduced to say 68Ω or 82Ω to flatten the response. Using an extra turn for

L2 will move the peak in the response to group A or B. The winding is made from one of R3's leadout wires. D1 provides reverse polarity protection.

Construction

The smallest RS diecast box (35mm wide) was used, with the amplifier built across it on a small piece of copper-clad laminate held by the coaxial socket mounting bolts via 6BA tags soldered to the copper side. Use short lead lengths following normal u.h.f. practice. Since a 9V battery cannot be accommodated within the box, 2mm sockets are fitted for the supply.

Performance

I've found the design to be repeatable – the amplifier was originally conceived as part of a forthcoming DX-TV project. No alignment is required and the amplifier should work on completion.

For DX reception I use the ET021 series tuner, whose MOSFET amplifier has a very low noise performance. Because of this, many preamplifiers provide no improvement. With the present design however recognisable pictures are obtained with inputs as low as simply line syncs (P₁ to P₁½-2 on the ATV scale). There's complete stability across the spectrum with or without input termination. At 9V the noise figure is typically 2dB and the gain is as follows: 11.5dB at 470MHz; 11.5dB at 500MHz; 11.2dB at 600MHz; 11.6dB at 700MHz; 13.8dB at 800MHz; 13dB at 860MHz. The unit will work happily at up to 12V, but don't exceed this voltage.

Use of a tuned collector circuit, i.e. two turns tuned with a 2-10pF trimmer and with R3 deleted (and the value of R4 increased to compensate) would increase the gain and reduce the bandwidth. For increased wideband gain, C3 could be taken to the base of a second BFR91 transistor.

The amplifier is particularly useful where a nearby high-powered transmitter makes the use of a mast-head amplifier impractical.

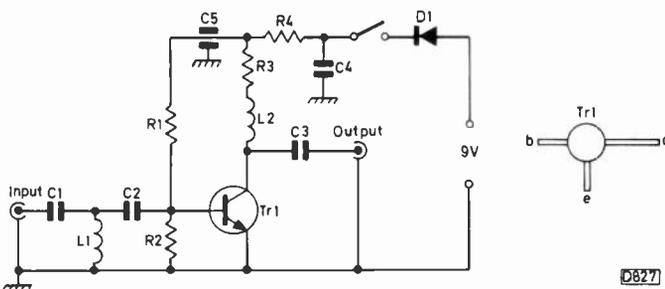


Fig. 1: Circuit diagram.

Component details			
C1, C2	4.7pF	L1, L2	2½ turns,
C3	5.6pF		½in. diameter
C4	0.001μF	Tr1	BFR91
All 63V ceramic plate		Available from Ambit	
C5	0.001μF	D1	BA148 etc.
feedthrough		Box RS509-923.	
R1	10k	Coaxial sockets	
R2	1.5k	RS455-539, surface	
R3	120	mounting	
All ½W, 10% low-noise		Subminiature SPST	
carbon film		switch	
R4	220, ½W		

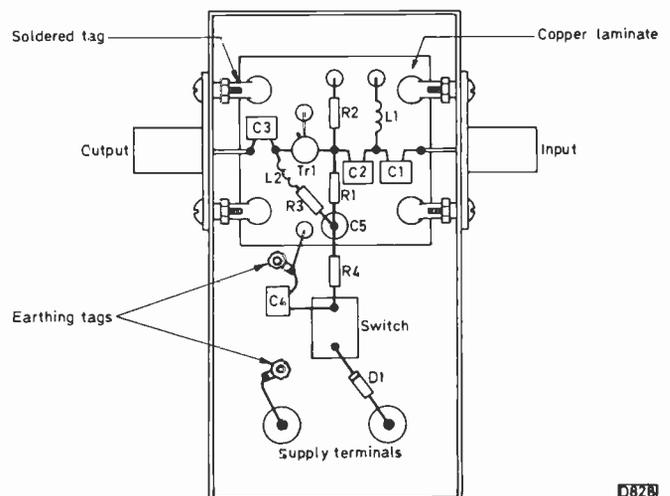


Fig. 2: Constructional details.

Teletopics

SATELLITE PROSPECTS

Douglas Hurd, the Home Office minister responsible for broadcasting, is on record as saying that the government would like to see a UK satellite TV service using a UK satellite. Wouldn't we all? But progress towards this aim seems to be painfully slow following the collapse of the BBC's plans to start a service in 1986. The tripartite working party set up to investigate the possibility of a co-operative DBS project, with representatives from the BBC, the IBA and the Independent Television Companies Association, has completed its initial investigation and has reported back to Jeffrey Sterling, the chairman of P & O and special adviser to industry secretary Norman Tebbit. Having identified the main problems, the working party has now set to work on a suggested plan of action.

Unfortunately, many of the problems are not of the sort that can be resolved quickly. There is in particular the problem of who should be authorised to spend money from which sources on setting up a DBS service? This is compounded by the fact that the present ITV companies' franchises will come up for review within the time scale of the establishment of a DBS system. Do we, this time round, ignore the elaborate legal requirements that were laid down to ensure the accountability of ITV companies to the public? Or do we alter the franchise system, as is being suggested? Whatever the answer, legislative action will be required and will introduce delays. This is something that can't be got round, as the government's recent problems over cable prove (see below).

Another problem is the likely cost of satellite receiving equipment. An official estimate that an installation could cost some £500, implying a monthly rental of around £16, is considered to be beyond what the public would find acceptable. The BBC's chairman Stuart Young has suggested a £50 subsidy for each adaptor and tax incentives to TV rental companies to enable them to keep their charges down. Sir Clive Sinclair has made a characteristic contribution to this aspect of the subject in announcing that Sinclair expect to be able to provide DBS installations, including the dish, down-converter and descrambling electronics, at around £100. The broadcasting authorities have welcomed this prospect, though other manufacturers expressed doubts. One wonders whether the idea would be to offer such units as loss leaders initially until production built up? Apparently however Sir Clive's main interest is in producing high-definition sets for DBS reception at around £500 each.

Douglas Muggerridge, managing director of BBC External Broadcasting, has suggested that an international satellite TV service should be established, i.e. a TV version of the BBC's world radio service. The BBC has been conducting an enquiry into the prospects for an international TV news service. Anything of this sort would require government funding of course.

In Japan, Mitsubishi have announced a DBS receiver system for use with the BS2a satellite, which is due to start transmissions this May. The satellite's main purpose is to eliminate areas of poor reception, but it's also expected to signal the start of the DBS age in Japan. Of particular interest is the use of digital pulse code modulation for the

sound channels, giving high-quality sound similar to that obtained from the new compact audio discs. Mitsubishi's receiver system consists of a 75cm offset-type dish with low-noise converter and tuner. The use of Mitsubishi's dual-mode horn gives the aerial an aperture efficiency of over 70 per cent, which compares with 55-56 per cent for a conventional parabolic dish.

CABLE TV

The eleven cable operators who were awarded interim franchises last December have been told that due to legal problems firm licences will not be granted until late this summer, nine months later than originally planned. The government has discovered that it doesn't have the legal authority to issue licences until the Cable Television Bill and the Telecommunications Bill receive royal assent. Instead, the government has offered to issue letters of intent or provisional licences under the 1981 Telecommunications Act. The problem the operators have is in raising finance to start developing their systems, which is in turn delaying prospective start-up dates for the services. Michael Storey, managing director of Westminster Cable, commented that "it's not clear what has been achieved by the whole frenetic business of the interim franchises".

British Telecom has been awarded a contract to supply its Gamestar cable TV games service to Rediffusion's one million subscribers in the UK. A connection fee plus £9.95 a month rent for a Sinclair Spectrum microcomputer will be charged: twenty games a month will be provided, five being changed each month. A British Telecom spokesman commented "we expect to supply a growing number of interactive services as the cable industry expands."

BLUE TUBES

A reader recently sent us a cutting on the subject of tubes with light blue screens. Not that you would expect to find them in use in the UK. The idea is to use a phosphor system that filters out light in the yellow/green spectrum to give sharper contrast and improved brightness under brilliant lighting or sun-drenched viewing conditions. The rare earth element that gives the screen the blue appearance when the set is switched off is neodymium oxide. Sets fitted with these tubes are on sale in Japan and the USA.

AYR AGAIN

GEC-McMichael have acquired Ayr Viewdata, the manufacturer of teletext and Prestel adaptors that went into voluntary liquidation just over a year ago, and have resumed production of the former range at Ayr's West Byfleet, Surrey factory. Dealers interested in stocking these adaptors should contact GEC-McMichael Ltd. at Sefton Park, Bells Hill, Stoke Poges, Slough SL2 4HD.

VIDEO

Mitsubishi and Sanyo are both to double assembly of VCRs in the UK, from the present rate of 5,000 machines a month to 10,000. Sanyo has also announced plans to start production of VHS machines in Bavaria. Tatung and Binatone are expected to set up VCR assembly lines in the UK - Binatone is at present negotiating a licencing agreement with JVC. ITT's plans are to start production of VHS machines at their Bochum TV factory in W. Germany. The tape transport system will be imported but the electronics and control systems will be ITT designed, using some of ITT's digital TV electronics (Digivision).

Sharp is the latest firm to join the ranks of those who've announced their intention to introduce an 8mm camcorder later this year.

A new edition of the Ferguson "100 Questions and Answers on Video" has been published: 85,000 copies of the first edition were distributed. Copies can be obtained from the Ferguson Video Advisory Service, PO Box 121, Lea Valley Trading Estate, London N18 3BP. The new edition has been updated and revised to include the latest generation of video products.

New VCRs have been introduced by Mitsubishi, Hitachi and JVC. The Mitsubishi HS330 is a full-specification, two-speed machine with a suggested retail price of just under £700. Hitachi's VT33 front loader will replace the popular VT11 at a suggested price of around £450. JVC's new budget model HR110 is a non-remote control version of the HR120.

David Rozalla, managing director of Warner Home Video in the UK, has commented on the successes achieved against video piracy in the UK. He attributes this to the establishment of the Federation Against Copyright Theft in January 1983. Estimates suggest that piracy at present accounts for some 35 per cent of the UK market, down from a level of 65 per cent two years ago. Pirate cassettes with a street value of over £1m were seized in the UK last year. It seems that the pirates have moved to the continent, where they are said to be supplying some 70 per cent of the W. German, French and Benelux markets.

A somewhat contentious report on head wear with different brands of video tape has been released by 3M. The tests were not carried out under normal operating conditions, and the scale of the investigation was so small as to be statistically worthless. Measurements were made by comparing photomicrographs obtained using a scanning electron microscope before, during and after exposure of the sample head assemblies to the tape, the accuracy of the measurements being limited by the resolution of the photographs and the repeatability of the measuring operator. For what it's worth, Scotch, Maxell, Fuji and Memorex tapes all came out well.

The latest suggestion for entertaining bored pub-goers is the coin-operated video jukebox. The idea is that you get a three-minute film along with the music you select.

SONY'S MOVE

Sony (UK) have moved to a new head office in Staines, after fourteen years at Pyrene House Sunbury with offshoots at Slough and Andover. The new address is Sony (UK) Ltd., Sony House, South Street, Staines, Middx TW18 4PF (Staines 61688).

AVO'S LCR METER

An LCR meter, Model B183, has been added to the AVO range - it's very similar in appearance to the 2001 digital multimeter reviewed in these pages last February, being a hand-held, 9V battery-operated unit with LCD display. There are six inductance ranges from 2mH to 2H, seven capacitance ranges from 200pF to 200µF and seven resistances ranges from 20Ω to 20MΩ. Measurements are made using a sinewave test signal at a frequency of 1kHz or 100Hz depending on the range selected by the eight-position slide switch. Price to the trade is £185 plus VAT.

TV EQUIPMENT

At an expected inclusive retail price of around £400, Fidelity's latest introduction, the AVS1600 audio/TV rack

system, should be a considerable success. The AVS1600 incorporates a 16in. colour set with remote control, eight preset channels, stereo sound capability and a spatial sound option to create a stereo effect through the separate, floor-standing speakers. It also incorporates a full monitor function for video and computer games sources via a 21-pin SCART socket, an anti-glare glass front and a headphone socket with volume control. The three-waveband tuner covers stereo f.m. plus MW and LW with synthetic stereo. The belt-driven record turntable glides in and out from behind an automatic flip-up inspection window at the touch of a button. Above this is the cassette recorder which can record from any of the other items including the TV set. The amplifier provides 8W r.m.s. output per channel (24W total music power) and can be used with all the other items including the TV set. Its features include dynamic noise reduction on all inputs, headphone and microphone sockets, and a comprehensive set of controls. The speakers are of the bass reflex type, with separate tweeters.

Ferguson and ITT have both introduced infra-red remote control versions of their 14in. colour sets. The Ferguson 37141 is fitted with the TX90 chassis and has voltage synthesis tuning with station memory.

The first Luxor models fitted with the new SX9 chassis (see article in our January issue) have now been released. These are the 22in. 5636 and the 26in. 6736.

FOCUS ADJUSTMENT

A new method of focus adjustment is being introduced at ITT's Basildon plant. It's based on the use of a meter to measure the light output from the tube phosphor in a way quite different from that employed by an ordinary photometer. A property of this measured light output has been found to coincide with optimum focus.

CRT REBUILDING EQUIPMENT

The Faircrest Engineering Ltd. range of c.r.t. rebuilding equipment is now being distributed by V.N. Barrett and Co., Ltd. of 1 Mayo Road, Croydon, Surrey CR0 2QP (01-684 9917). The company can supply all the equipment required for reprocessing both monochrome and colour tubes and in addition offers a full training scheme.

CCTV SYSTEM

Frowds Ltd. (4 Northharbour Road, Cosham, Portsmouth, Hants PO6 3TJ) have introduced a sophisticated CCTV surveillance system using a fully weatherproofed camera that can be fitted with various types of tube. The circuitry incorporates refinements to maintain performance over a wide range of lighting conditions, and an optional built-in telemetry system enables the camera to be remotely controlled via the coaxial cable at up to 1.7km.

PHILIPS-GRUNDIG

Further details of Philips' plan to take control of Grundig (see page 177, February) have been announced. The scheme is a complex one in which Philips, while achieving effective day-to-day control of Grundig, will actually end up with a smaller stake in the company - a reduction from 24.5 per cent to 22.9 per cent. Philips will first take over a further 7.1 per cent of Grundig's nominal capital, but at the same time a group of banks led by Dresdner Bank will take over a block of Grundig AG profit participation rights certificates which will later be converted into ordinary voting shares, leaving the banks with a 27.5 per

cent interest in Grundig. The aims of these moves seem to be to satisfy the W. German Federal Cartels Office, provide Grundig with fresh investment funds, and ensure that joint Philips-Grundig administration is achieved whilst maintaining Grundig's operational independence. A Philips' nominee is to become chairman of the Grundig board of management on the retirement of Dr. Max Grundig, who will be 75 on April 1st.

HDTV

A new volume, "Compatible Higher-Definition Television", has been published by the IBA as the twenty first in the series of occasional engineering texts that have been provided as a service to broadcast engineers and students since 1972. The profusely illustrated 48-page book reflects interest in the development of TV systems capable of

providing significantly higher quality colour pictures than are possible using any of the present broadcasting standards. In particular the argument is put forward that the MAC system proposed by the IBA and accepted by the government for satellite TV broadcasting is also capable of providing higher definition displays with a wider aspect ratio. The suggested E-MAC (extended-definition MAC) system would make optimum use of the information handling capacity of European satellite channels to give results at least comparable in quality with the HDTV system proposed and developed by NHK (Japan), without incurring the severe bandwidth and non-compatibility problems inherent with the NHK system.

Enquiries about the book should be sent to the IBA Engineering Information Service, Crawley Court, Winchester SO21 2QA.

VCR Clinic

Ferguson 3V36

A Ferguson 3V36 was sent in by a dealer from another dealer, with a vague account that there was a servo fault and that the dealer of the first part had apparently contacted Ferguson who had suggested replacing the servo board. The dealer of the second part didn't know whether this had been done. So it was up to us to play "spot the fault", a game most readers in service departments will have played when customers or sales staff can't be bothered to give any more comprehensive details than "faulty".

The first symptom encountered was a spotty picture not unlike that caused by a dirty video head, but with my luck it would turn out to be more complicated. Andy was optimistic however and got on with cleaning the heads (regular readers will note Andy's promotion to Head Cleaner). This, amidst cries of "told you so", did little good, so the replay f.m. signal was checked. Only one output was evident, and the drum flip-flop signal was only a single pulse instead of the usual symmetrical squarewave. Misadjustment of the drum PG pulse level control R459 was the cause of the incorrect waveform, and after setting up the drum and capstan servos normal record/playback functions were restored. Great, on with the covers.

That was when Andy decided to check the still frame performance. The tape stopped dead in its tracks with a very spotty picture, showing that the frame advance circuits were not operating to give a clear picture. If that wasn't bad enough, we couldn't get back into play. In fact we couldn't select anything or even switch the machine off to standby. The little red lights for stop, fast forward etc. followed the buttons, but the operate light stayed on. The only way to restore operation was to unplug the machine at the mains supply. It then worked normally until we selected pause, when it again locked out.

Measurement showed that the microcomputer IC201 was holding the capstan motor forward/reverse selector IC206 fully off. In a vain attempt to restore operation, I applied a full reset to the microcomputer chip by earthing pin 22. Surprise, surprise, everything then worked correctly, including the still picture circuit. So the noise bar and anti-bounce potentiometers could be set up, giving a very good still frame. Andy remarked that one of our own customers had had the same problem, and that unplugging

*Reports from Steve Beeching, T.Eng. (C.E.I.),
Derek Snelling and Mike Phelan*

the machine for a while at the mains had cured it. I wonder if this is a problem? Great, on with the covers.

Andy then suggested trying picture search and the timer before the machine went out. It was unlikely that picture search would be faulty, as it would have shown up whilst we were doing other things, but we tried it. Clang. Off with the covers. Selecting picture search is simple. The picture then broke up into horizontal lines which got bigger until there were no lines at all, indicating that the heads were not whizzing round. The safety circuit then operated and the tape unthreaded.

Various checks were made, including connecting one of the inputs (pin 12) to the servo operational amplifier IC406 to earth when picture search was selected. This stopped the drum servo. We're getting somewhere! The circuit back to pin 6 of the main servo chip (IC403) was then followed through (see Fig. 1). During playback there's a squarewave here. It was still present in picture search, but the output from the integrator (R456 etc.) was absent. R456 had a voltage at the IC403 end, but not at the IC406 end. Something was earthing the servo output between IC403 and IC406, and that something was IC405. By isolating pins 10 and 11 of IC405 we found that when pin 12 went high pin 10 would be earthed by an internal fault within the i.c. So the chip was changed to a CD4016.

Great. Now I can put the covers on. At least the timer worked! **S.B.**

Mitsubishi HS700

Some Mitsubishi repairs this month. First a common fault with the HS700 portable. The symptoms are intermittent play with excessive rewind speed and possibly tape dam-

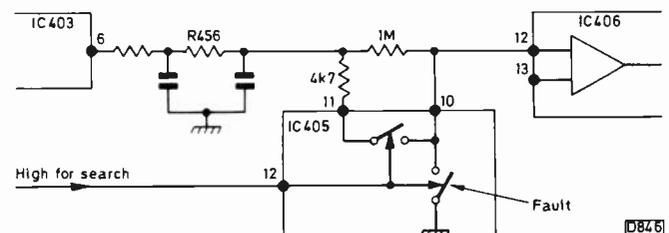


Fig. 1: Picture search fault, Ferguson 3V36.

age. This is caused by the small pinion wheel that drives the take-up spool. It's a push fit on the motor spindle, and has a tendency to come off slowly (see Fig. 2). Eventually the point is reached where it fails to mesh with the take-up spool. The result is intermittent play as the take-up spool stops rotating when the teeth slip. The drive from this motor is also used to provide back tension and some control of the other motor's rewind speed, so when there's failure to engage rewind becomes a bit frantic. The cure is to push the cog fully home and seal it in place with red paint.

Another common fault with Mitsubishi machines is intermittent failure to erase the previous sound recording. The cause is the plugs and sockets that connect the erase head to the bias oscillator: the official cure is to remove these and solder the wires directly to the full erase head and the board. We've had the fault about eight times in the last few weeks. **D.S.**

Mitsubishi HS303

The problem with an HS303 was an intermittent clock. Every so often the clock display would blank out – if it reappeared it would be flashing, as though the power had been disconnected. Checks showed that all the power supply lines to the clock board were correct, but when we came to the clock chip the "init" pin was at 10.5V instead of 4.7V. This pin is fed from the 12V rail via the tantalum capacitor C8F2 – the idea is that the capacitor charges at switch on, supplying the chip with a reset pulse. The capacitor was found to have a varying leak – when the voltage at this pin was high enough the i.c. would be held in the reset condition, blanking out the display. A new capacitor put matters to right. **D.S.**

Ferguson 3V23

The tuner/timer board seems to be responsible for various obscure faults in this model. In a recent case the machine did everything except rewind and fast forward – it wouldn't even acknowledge these commands. We connected an oscilloscope to pin 16 of the serial-to-parallel converter IC38 to check whether the serial code was arriving from the keyboard. It was. The 8-bit parallel outputs were also correct, i.e. in accordance with the truth table. These go via inverters in IC33 to the data selector i.c.s, so checks were carried out in this area. We found that bit D3 was permanently low after IC33 – it should be high in the rewind and fast forward modes. Five of the bits, which carry remote tuner/timer commands, go to the tuner/timer board as well as to the data selector i.c.s. The next logical step therefore was to disconnect this board by pulling out the interconnecting plug. Magic – we now had rewind and fast forward. The fault on the tuner/timer board was a short-circuit in one of the TA57 transistor array i.c.s. **M.P.**

Ferguson 3V35/3V36

We've had a few faulty Ferguson 3V35/36s recently. In the first one the cassette couldn't be ejected. After studying the operation it became apparent that the flap on the front of the machine wasn't opening to let the cassette out, though the eject mechanism was doing its best to push the cassette through, flap or no flap. We eventually discovered that the cog which operates the flap had tripped out of mesh. This apparently happens on these

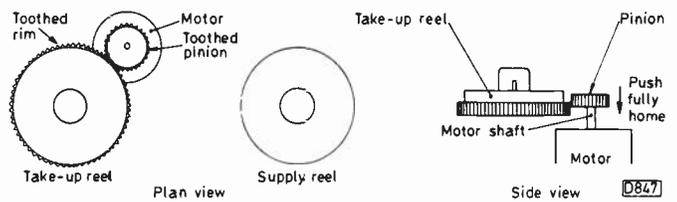


Fig. 2: Pinion wheel trouble with the Mitsubishi HS700.

machines for no apparent reason, and the cog has been modified in production to prevent the fault.

Unfortunately in its efforts to eject the tape the machine had, unknown to us, bent the loading switches. This had no immediate effect, but a couple of weeks later a call came that the machine "switched off on prerecorded tapes". Sure enough it worked perfectly on my cassette and all the customer's cassettes, but switched off after a few seconds when a prerecorded tape from the local library was inserted. This cassette couldn't be blamed since it apparently worked on a neighbour's machine – and they'd had the same trouble with another cassette from the library.

On removing the top of the machine I found that the take-up spool wouldn't rotate with the prerecorded cassette in position, hence the switch off. This in turn was because the cassette wasn't going down the last quarter of an inch – it fouled the loading switches that had been bent by the previous fault. Why this cassette and not the others? The cassette was found to be about a millimetre longer, front to back, than the others – it was of the type where the flap is a different colour from the rest of the cassette.

The next machine was a 3V35 with a noisy take-up clutch. Replacement cured this – it appears to be of the same type as that used in the 3V29/30.

Finally, if someone attempts to insert a cassette in one of these machines when it's switched off (at the operate button) and uses sufficient force a small plastic pip can be broken off. We've had only one instance of this so far, but the problem is sufficiently common for Ferguson to have modified these machines in production – more than twice the force is now required to cause damage. One hopes that users will check that the machine is switched on before this point is reached. **D.S.**

Ferguson 3V29

The colour was good with playback of a prerecorded tape, but on its own recordings the chroma was very noisy and broke up into horizontal lines. A check on the signal at the input to the colour converter (pin 16 of IC401) showed that it was of excessive amplitude. Clearly the preceding a.c.c. stage (between pins 1 and 17) was operating at maximum gain. A check at pin 3 then revealed that there were no burst gate pulses, and on moving back we found that L407 in the ringing circuit was open-circuit. **M.P.**

Ferguson 3V29

This machine had really fast search – in fact it was faster than the rewind speed. The supply to the reel motor goes via Q2, which is in turn controlled by Q16. This transistor receives commands at its base via diodes D15/16/17. Both transistors were being turned on hard – in fact the voltage at the base and emitter of Q16 was about 15V. The diodes were tested first but proved to be o.k. That left Q16 which was found to have a 1kΩ leak from collector to emitter. **M.P.**

of four programmes with vision and sound: 30mV is the sum of four 5mV vision signals and four 2mV sound signals, so overloading will take place at some 5mV of wanted signal. The more signals there are, the earlier the a.g.c. crossover has to be set. With the advent of VCRs and TV games units, the ideal setting is coming to be around 2mV. But 2mV of what?

Measuring the Signal

Today's average colour set has as many as seven automatic control circuits whose action depends on some part of the composite vision signal, so there's little point in applying a known amount of plain r.f. signal from the generator. The answer you'll get will not be the same as that shown by the picture. During the line sync period however the transmitter is radiating at full power regardless of the scene (see Fig. 2). This is the reference point to which all signal levels are referred: thus the 1mV (etc.) we've been quoting is "the r.m.s. value of the sync tips of a composite vision signal appearing across a terminated load". In our case the terminating load, i.e. the TV set, presents an impedance of 75Ω.

Signal generators, even if you can modulate them with a video signal, are misleading because their output is calibrated in e.m.f. – the voltage that appears across the unterminated (open-circuit) output terminals. To get this output into the set you have to connect a coaxial lead and then connect the set as the termination, so the true output drops to half (-6dB) of what is shown by the output indicator, i.e. for the set to receive 1mV of signal the generator needs to be set at 2mV (see Fig. 3). The Philips series of pattern generators adopts a more realistic approach: their attenuators, though a little vague, do indicate the signal level appearing at the set.

Field Strength


Having dealt with workshop signals, we'll consider the situation outside.

Broadcasters have a totally different approach to signal levels. Their interest is in ensuring that there is an adequate level of signal available at your location. This open-circuit field strength is measured in microvolts per metre ($\mu\text{V}/\text{m}$) of free space – in other words the amount of signal picked up by a one metre long rod suspended in the signal path. It takes no account of the tuning effect of the rod, so some conversion is needed.

The BBC practice is to make measurements using a log-periodic aerial, whose response is substantially flat, mounted on top of a 10m pole, i.e. at the chimney level of an average house. The measurement is made using an accurate millivoltmeter, and all known errors are corrected. The boundary of a primary service area is the 60dB $\mu\text{V}/\text{m}$ contour on the map, i.e. 60dB above 1 $\mu\text{V}/\text{m}$, or 1mV/m to us (see Table 1). As propagation varies

Table 1: Basic dB $\mu\text{V}/\text{m}$ to voltage conversion.

dB $\mu\text{V}/\text{m}$	Voltage	dB $\mu\text{V}/\text{m}$	Voltage
20	10 μV	70	3.2mV
30	32 μV	74	5mV
40	100 μV	80	10mV
48	250 μV	88	25mV
54	500 μV	90	32mV
60	1mV	94	50mV
68	2.5mV	100	100mV

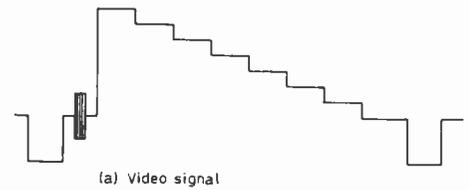

(a) Video signal

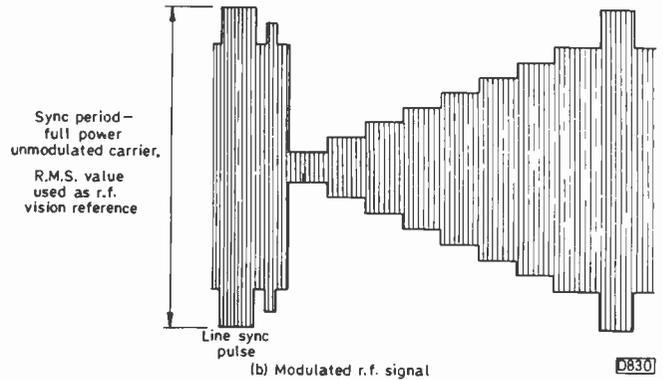


Fig. 2: The sync pulse is the reference point to which all signal levels are referred. Note that 1mV r.m.s. = 2.83mV peak-to-peak seen on an oscilloscope.

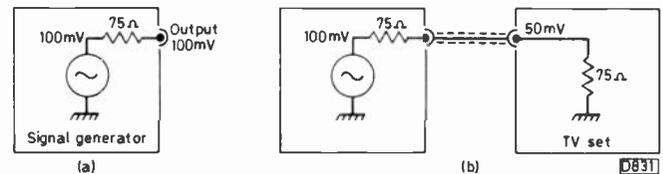


Fig. 3: Signal generators usually indicate their output as an e.m.f. at a certain impedance, as shown at (a). In use, the generator will be terminated by the TV set. The e.m.f. then becomes a voltage of half the value (-6dB) stated on the generator.

throughout Bands IV and V, there is a variation from 58dB $\mu\text{V}/\text{m}$ on ch. 21 to 64dB $\mu\text{V}/\text{m}$ on ch. 68.

Relating Field and Signal Strengths

Field strength is related to signal strength by the factor λ/π , where λ is the wavelength. On average this works out as follows:

- 0.2 (-14dB) in Band IV (aerial group A);
- 0.15 (-16dB) at the lower end of Band V (aerial group B);
- 0.12 (-18dB) at the upper end of Band V (aerial group C/D).



The Manor Supplies signal strength meter.

To this has to be added the aerial's gain, which is typically 11dB for a standard Yagi array. We then have to subtract the downlead loss (10m of low-loss cable introduces a loss of -3dB) and another 6dB since the field strength is an open-circuit e.m.f. while signal strength is the voltage at the set.

The following two examples will make this conversion business clear. You'll then be able to use the BBC table (see Table 2) with ease.

(1) A London BBC-2 signal at a standard installation. Field strength 3mV/m.	
3mV/m \approx 70dB μ V/m, i.e. 70dB above	
1 μ V/m.	+70dB
Receiving aerial gain (standard Yagi)	+11dB
Downlead loss (10m cable)	-3dB
Conversion factor 0.2 (ch. 33)	-14dB
Less 6dB for set termination	-6dB
	58dB

i.e. 58dB above 1 μ V/m, or 790 μ V input at the set.

(2) A weak Channel 4 signal in Norfolk. Field strength 500 μ V/m.	
500 μ V/m = 54dB μ V/m	+54dB
Fringe Yagi array	+17dB
Downlead loss	-3dB
Conversion factor 0.12 (ch. 65)	-18dB
Less 6dB for set termination	-6dB
	44dB

i.e. 44dB above 1 μ V or some 200 μ V at the set.

Satellite TV

The same principles apply to satellite signals, but the quantities are different. Since the incoming signal is collected by a dish, which has area rather than length, square metres replace metres. And because the transfer of the signal from the dish to the set doesn't suppose the use of 75 Ω coaxial cable, watts are used instead of volts. The term field strength is replaced by P.F.D., or power flux density, and the dB ratios are $10 \times \log P1/P2$ instead of $20 \times \log V1/V2$ as before. P.F.D. is thus expressed in dB W/m².

Think of the signal collected by a perfect dish of area 1m² (1.12m diameter) and you'll see how convenient it is to stick to the chosen units. You'll want to be able to relate these s.h.f. signals to the u.h.f. ones with which you're familiar, and once more a worked example will make this clear.

The Russian Gorizont 7 satellite, which took over recently from Gorizont 4, has a P.F.D. in this country of about -120dB W/m², in other words one picowatt per square metre. Not a lot! Now watts = V²/R (or Z), and Z, the transfer impedance of a dish, is given as 377 Ω (120 π) per m² of free space. So we have 1pW = V²/377. Crossmultiply, V = $\sqrt{(377 \times 10^{-12})}$ or 19.4 μ V/m² which looks a lot better!

Similarly the OTS signal P.F.D. of -118dB W/m² works out at 24.4 μ V/m² and the projected BBC/ITV DBS signal P.F.D. of -103dB W/m² works out at 137.5 μ V/m².

EIRP

Satellite signal strengths are often given in terms of E.I.R.P. (effective isotropic radiated power), in other words how many watts beamed our way leave the satellite.

To relate E.I.R.P. to P.F.D. you have to subtract the path loss, which is proportional to the square of the distance between yourself and the satellite, plus 0.5dB for losses on route (more if it's raining hard). So the lower the satellite is to the horizon, the greater the path loss.

Noise

Noise performance is even more important with satellite TV than it is at u.h.f. Everything in the chain contributes to it - even the dish, which picks up noise from the ground and from outer space to pass on to the set. For satellite purposes, noise figures are given in degrees Kelvin. Zero $^{\circ}$ K is absolute zero, and the reference temperature of 290 $^{\circ}$ K corresponds to a room temperature of 17 $^{\circ}$ C.

To convert noise in $^{\circ}$ K to dB, the following formula is used:

$$\text{dB} = 10 \log (^{\circ}\text{K}/290 + 1).$$

From this, 1dB corresponds to 75 $^{\circ}$ K and 3dB to 290 $^{\circ}$ K. Noise figures, if given in dB, would give a very optimistic indication of performance. Hence the use of $^{\circ}$ K.

Because of the use of f.m. for satellite video transmission, the signal-to-noise ratio required is much lower than for our a.m. u.h.f. signals. For results comparable to the 36dB previously quoted, a satellite signal need have only a 10dB carrier-to-noise ratio. Pictures are in fact quite watchable down to a ratio of 6dB, when colour is lost. What counts, as with f.m. stereo radio, is the noise threshold. This is the level above which no further improvement can be seen or heard. Also the fact that f.m. noise is triangular, i.e. worse at the higher frequencies (which accounts for the hiss going when you switch the radio from stereo to mono).

With f.m. TV, up to 3dB improvement can be obtained by reducing the receiver's bandwidth from 30MHz to 15MHz at the expense of some loss of definition and the appearance of "sparklies" on transients, an effect with which video engineers will be familiar.

So with an expected DBS receiver gain of around 110dB and a predicted BBC/ITV satellite signal strength of -103dB W/m², it looks as if there will be some 7dB to play with. Allowing for an aerial efficiency of about 55 per cent., most of us should get by with an 0.6m diameter dish. The moral seems to be to save your old dustbin lids - they might come in useful.

Measuring Signal Strength

When it comes to readily available equipment for measuring signal strength we come into a grey area, a need crying out to be filled. Most aerial riggers known to the writer treasure their ten year old Labgear meters like gold. The broadcasters' gear is well beyond our reach and is totally uneconomic unless used full time.

On the face of it all you have to do is to calibrate the a.g.c. voltage of a standard i.f. strip and you'll get an indication proportional to the incoming signal strength. Not so. The average i.f. strip takes about half an hour to settle down, during which time any meter linked to the a.g.c. line will show a gain reduction of as much as 6dB. This can be tolerated in the workshop if the warm-up time occurs before work starts, but a better tool is the writer's panoramic monitor (see *Television*, November 1971) which shows the instant state of all four vision and sound carriers in the local group simultaneously.

The Siemens S43202MC signal strength meter has the right idea, at around £1,500. It has a small oscilloscope

Table 2: Terminated signal voltages in known signal fields.

Field strength in dB referred to $1\mu\text{V}/\text{m}$. Signal strengths are terminated voltages assuming a downlead length of approximately 10m, taking account of the λ/π field strength/signal strength conversion factor.

Aerial	Gain dB	Field strength/signal strength conversion						
		65dB	70dB	75dB	80dB	85dB	90dB	95dB
Group A								
Log-periodic	8.5	330 μV	590 μV	1mV	1.9mV	3.3mV	5.9mV	10mV
Standard Yagi	11	440 μV	790 μV	1.4mV	2.5mV	4.4mV	7.9mV	14mV
High-gain Yagi	15	700 μV	1.2mV	2.2mV	3.9mV	7mV	12mV	22mV
Fringe Yagi	17	880 μV	1.5mV	2.8mV	4.9mV	8.8mV	15mV	28mV
Group B								
Log-periodic	8.5	250 μV	440 μV	780 μV	1.4mV	2.5mV	4.4mV	7.8mV
Standard Yagi	11	350 μV	630 μV	1.2mV	2mV	3.5mV	6.3mV	11mV
High-grain Yagi	15	550 μV	980 μV	1.75mV	3.1mV	5.5mV	9.8mV	17.5mV
Fringe Yagi	17	690 μV	1.2mV	2.1mV	3.9mV	6.9mV	12mV	22mV
Group C/D								
Log-periodic	8.5	200 μV	350 μV	630 μV	1.1mV	2mV	3.5mV	6.3mV
Standard Yagi	11	280 μV	500 μV	890 μV	1.6mV	2.8mV	5mV	8.9mV
High-gain Yagi	15	440 μV	790 μV	1.4mV	2.5mV	4.5mV	7.9mV	14mV
Fringe Yagi	17	560 μV	1mV	1.8mV	3.1mV	5.6mV	10-mV	17mV

tube to display the detected vision or sound signal, with a gap in the display in which a vertical bar can be moved up and down by adjusting an attenuator calibrated directly in dB above $1\mu\text{V}$. When the test set is on tune, the bar is at its maximum, and is then set to lay alongside the sync tips with the attenuator. The cursor then gives the terminated signal strength into the set in accordance with the definition we gave earlier. The electronics consist of a high quality tuner/i.f. strip, to which a.g.c. is applied, and a stable oscillator whose output is fed via a variable attenuator and displayed in the gap. Thus drift in the i.f. strip doesn't affect the calibration.

At the other end of the scale, an inexpensive kit is marketed by Manor Supplies. This consists of an a.g.c. indicator with a conventional i.f. strip. The meter reads from 100 μV minimum to 10mV maximum on a logarithmic scale. An LED provides indication that a vision carrier is present – it lights up in the presence of field sync pulses, which are detected by a TBA550 i.c. Tuner a.g.c. is applied at over 10mV for overload protection. There's also the Unaohm EP730FM field strength meter which provides a c.r.t. panoramic display. Its cost is around £640 plus VAT. A test report by Eugene Trundle will appear in these pages shortly.

If you don't need a field strength meter, what other methods are available to enable you to calibrate a receiver or test set? As mentioned before, there is the Philips series of pattern generators – never spot on, but never far out. If you can get to meet any of the broadcasters' field strength measuring teams, they will usually be able to pinpoint a place close by where they've measured the field strength with precision. Alternatively you can check a batch of new receivers whose a.g.c. crossover point is given in the manual. Connect a meter to the tuner's a.g.c. line, check that the manual specifies a crossover at say 2mV of input signal, then feed the output from a signal generator to the aerial socket, increasing the input until the meter connected to the a.g.c. line just begins to record a measurement. That's the crossover point, and implies that you are feeding 2mV to the set. Take the average of as many sets as you can – factory people are always in a hurry, and this is a touchy adjustment to make.

It should seldom be necessary to those other than aerial

riggers to know the signal level. Your main interest lies in checking that with 800 μV applied at the aerial input a 34dB signal-to-noise ratio (or a just snow free picture) is obtained on the c.r.t. The cheapest way of doing this is with a pattern generator of known output and a suitable Belling-Lee attenuator in series. There remains the need for something rugged for aerial riggers – and in due course a simple way of checking the 12GHz output just behind an 0.6 or 0.9m dish.



Bind it

It's so easy and tidy to file your copies away using the Easibind binder. Each binder is designed to hold twelve issues and is attractively bound and blocked with the TELEVISION logo.

UK price £4.50 including postage, packing and VAT. For overseas orders add 60p. Please allow three-four weeks for delivery. Why not place your order now? Send the completed form below with the remittance payable to: IPC Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

it's easy with **EASIBIND**

Order Form

I enclose p.o./cheque value
 for binders
 Years required
(BLOCK LETTERS PLEASE)
 Name
 Address

 Date

Sensing out Faults

Tony Thompson

Just in case anyone's forgotten, our five senses are sight, hearing, taste, smell and touch. We use the first two constantly without giving them a second thought. As for taste, I can think of no occasion when I've licked a set into submission! It's a different matter with touch and smell however. The heated casing of a tripler, for example the Thorn 9000 type, will tell the tale to the fingertips of an engineer: as for the smell, that's an experience in itself – a really bad one will make your eyes water. This is not a very subtle piece of smell diagnosis, but with practice you'll find that you can sniff out too warm carbon and wirewound resistors, and sometimes leaky capacitors. Other wirewound components make their distress known as the varnished wire heats.

This sort of thing can save time in comparison with the testmeter before all else approach to servicing, enabling us at least to locate the area of the fault before delving in too deeply. In other cases our senses can provide confirmation, where our instruments and intellect already suggest to us the location of the fault.

Most experienced engineers do this sort of thing automatically. But to think about it can sharpen our minds and make the approach more useful. For the less experienced, attention to the signals our senses provide gives an insight into fault conditions rarely obtainable from technical college instruction.

Sense of Touch

The sense of touch is a great asset in TV servicing, but before I go any further a word of warning to the less experienced. Don't stick your fingers into a dead set without disconnecting it from the mains supply by removing the plug, and remember that an open-circuit dropper or h.t. wirewound resistor can leave smoothing and reservoir electrolytics fully charged, lying in wait for your finger. If in doubt, discharge the points you're likely to touch, using a resistor of say $1k\Omega$ to chassis. It's not a good idea to bridge across with a screwdriver – amongst other things, the electrolytic won't like the spark you'll make.

With these words of warning in mind, let's suppose you are confronted with a dead set. The fuses seem o.k., so you disconnect, discharge as necessary, and feel along the dropper sections or wirewounds with your fingers. If current has been flowing, you'll sense the warmth. If there's been excessive current, you'll burn yourself – so tap lightly. Where a dropper is known to be a continuous winding but one section is cold while the next along is warm, you've got your culprit. In cases where the dropper has split windings and one set seems normal whilst another is cold, at least you've a clue where to start. It won't pinpoint the fault to a defective dropper section, but will tell you that for reasons yet to be determined there's lack of h.t. or l.t. here. The fact that droppers are often responsible for the dead set condition is something to bear in mind.

Still on the subject of power supplies, a bridge rectifier with common encapsulation should not feel more than warm. One that's hot after the set has been on for only a short time is likely to have a short-circuit diode. Single h.t.

rectifier or heater chain dropper diodes should also take time to warm up and should never attain a temperature that's uncomfortable to touch.

Imagine a potential divider network where the junction between the two resistors reads either very low or zero voltage. If a resistance check is inconclusive you may go on to unsolder components, including transistors, to remove parallel paths. There is no way round this unsoldering, though it should be limited to as few items as possible in order to save time and to avoid damaging delicate print and components. Before you attack with the soldering iron however, lick your fingertip and touch the upper resistor. In power circuits even a carbon resistor should be slightly warm if it's conductive, though the test is inconclusive in itself.

A wirewound resistor that's passing current will be just warm. A too-warm resistor of either type tells you that there's a leak at the junction, especially if the bottom one is cold. In this event it's profitable to disconnect bypass electrolytics for resistance checks or to suspect the valve or transistor being fed. A cold upper resistor on the other hand could well be open-circuit, or maybe of greatly increased value.

This example of the potential divider is just one of a number of checks that can be quickly carried out by hand, and I readily admit that diagnosis of this sort is likely to contain a goodly sprinkling of very likelies, probablies and possiblies. This doesn't detract from the usefulness of the exercise however. The chief benefit lies in saving time, enabling you to get to the source of the trouble before seeking additional information. There are also some instances where sensing methods reign supreme.

Line Output Stage Checks

Triplers have already been mentioned, but there's more to add on this subject. A tripler should run cool: a hot spot, especially localised on the casing, is a sign of trouble. A warm spot on the other hand cannot definitely be regarded as showing up a fault. This is a grey area where experience must be your guide. There are several variables such as the design of the tripler, its location within the set and the time it takes to warm up. It's fair to say that a tripler which heats up in a few minutes at most is likely to be faulty. Remember that, though rare, an internally shorting c.r.t. can result in a heavy current flowing via the tripler, giving the quick-heat symptom.

The best check is to disconnect the c.r.t.'s final anode connector, drape it carefully away from sensitive areas and the chassis, then run the set. This avoids placing a strain on the line output transformer etc. A neon tester held near the connector (don't touch!) will light up if there's an a.c. field present, confirming the tripler's demise. Keep the tester away from the line output transformer's field or you'll get a false reading.

The line output transformer is another touch-sensitive component. Take the no e.h.t. condition. If the line output stage uses valves, you'll have already ascertained whether they are being driven by making top cap spark checks and perhaps by switching off and touching the valve envelopes.

Where the line output valve and the boost diode are both cool, a finger check on the line output valve's screen grid feed resistor is a good test – it's likely that the stage is not being supplied with h.t. if all these items are cool.

If the valves etc. feel more or less o.k., try touching the transformer. I repeat – disconnect the set before doing any of this. If the transformer is cool, it's likely to be all right. Note the word cool, not cold: transformers vary, as do their operating conditions, but a warm transformer, especially one that warms up rapidly, is a bad sign.

This test works the same with transistor line output stages – touch the output transistor, which should be warm but definitely not hot. A very hot one suggests an internal short-circuit. In cases where all three major items in the line output stage – transistor, transformer and tripler – are overheating, the most likely cause of the trouble is the tripler, since a short-circuit transistor or shorting transformer will place no strain on the tripler (there are occasions when a faulty transistor will upset the transformer). When in doubt, it's always worth disconnecting the tripler at its input from the transformer: an internal fault can cause excess current in the stage even when the tripler's e.h.t. output is to all intents and purposes disconnected – triplers usually feed networks that remain in circuit when the c.r.t.'s final anode is disconnected.

What Valves Can Tell Us

There are some other useful points to remember about valves. We can always "test" a valve of the output type for evidence of stress: the sight of a dull, spreading redness on the anode structure is the telltale sign here. In such cases it's prudent to look before you touch, to prevent sore fingertips. Such problems are often apparent even before the set's back has been removed, as the overheating valve will singe the dust on its envelope.

Video output valves run hot or very hot. If cool they are either at fault or not receiving an anode or screen grid supply, or just possibly the cathode circuit is open. This also applies to colour-difference output valves, though these should run warm. A cool one gives the clue.

Valves used for other functions, i.e. in the i.f. stages and as oscillators, don't lend themselves so easily to this kind of testing, the results at best being inconclusive.

Remember that valves are active devices of an inherently fragile nature, and are thus the most likely cause where a fault occurs, particularly in a hard working output stage. Modern valves don't seem to be as reliable as those in days gone by.

Transistor Video Output Stages

With transistor RGB output stages, fingertip checks on the heatsinks or, where possible and perhaps more accurately, on wirewound load resistors, aids diagnosis. These items should all be warm.

Listening for Faults

There are many ways in which our hearing helps with fault finding, the obvious one being no sound. Take field collapse. If you can hear the field output transformer buzzing and can increase this buzz by adjusting the height control, you've immediately narrowed down the cause of the collapse to a few items at the output end of the field timebase – the scan coils, secondary components around the transformer, or an open-circuit connection between

the two. All this without lifting a test prod!

Sound distortion at low volume levels, clearing as the volume is increased, points towards a faulty loudspeaker – one with an off-centre speech coil. Gently pressing the cone whilst the set is working will prove the point.

Audible whistles from wound, cored components such as line output transformers can be very annoying, though nowadays it's mostly the case that components other than the line output transformer whistle – at an annoying submultiple of the line frequency. Gentle pressure on suspects with an insulated prod will help to identify the offending part: tighter core clamping or a dab of sealant may then help. Otherwise the cure must be replacement. The effect is due to magnetostriction: the core buzzes in sympathy with the coil's field. It follows that air-cored components cannot suffer from this malady. Some mains transformers are notorious for buzzing, which the customer often mistakenly attributes to the loudspeaker.

A dead set with a heavily buzzing mains transformer is a warning of possible excessive load on the h.t. supplies or, less likely, a leak such as a faulty electrolytic in the power supply.

In Conclusion

We use our senses in many diverse ways when fault finding: the back of the hand brushed across the c.r.t. face to sense the presence of e.h.t.; sniffing for ozone when we suspect corona discharge; touching i.c.s to see if they are warm when they shouldn't be (other than specific output types, they should remain fairly cool – a hot one is definitely a sign of trouble); taking the temperature of a decoupling capacitor which we know should be cold; or looking for the split in the casing of a mains filter capacitor that's saying "change me, don't waste your fuses". Ours is a sensitive trade. Use yours to the full, read the signs, and maybe you'll be the next one to apparently possess an ability that others speak of reverently as a gift.

Book Notice

BEGINNER'S GUIDE TO VIDEOCASSETTE RECORDERS by Eugene Trundle, published by The Butterworth Group, Borough Green, Sevenoaks, Kent TN15 8PH at £4.50.

Q & A: VIDEOCASSETTE RECORDERS by Eugene Trundle, published by The Butterworth Group (address above) at £2.65.

Our friend Eugene Trundle, who writes regularly for this magazine, has been busy! I read the beginner's guide through from start to finish and found it an excellent technical introduction to the subject. It cleared up a number of points about which I'd been uncertain, which is always to me proof of a book's usefulness. Don't be put off by the "beginner's guide" bit – it goes into the subject in enough depth to meet the needs of technicians.

The Q and A doesn't go into the subject in quite the same depth, being intended for "salespeople, bosses, prospective VTR owners, equipment reviewers and technical people whose present knowledge is in other fields". It's main concern is nevertheless the techniques used in VCRs.

Both books cover the three formats at present in use. I have no hesitation in recommending them to readers who want to get their teeth into the subject.

J.A.R.

Letters

GRUNDIG GREMLINS

Mick Dutton provided a comprehensive list of faults experienced with the Grundig CUC series chassis in the February issue (page 202). One component not mentioned however was R646 (270k Ω) in the power supply – it's the equivalent of R165 in the later Thorn TX9 chassis, mentioned in my letter last month. In the Grundig chassis it goes open-circuit, with the result that the chopper transistor goes short-circuit at switch on.

On the theme of Grundigs, the h.t. smoothing resistor R607 (91 Ω , 17W) in the 1510 has a habit of disintegrating. It also forms part of the excess current limiting arrangement (see Fig. 1). This works as follows. The mains rectifier thyristor Ty604 is triggered at its gate via the RC network R615/C611. In the event of excess current the voltage at the junction of R607/R608 will fall and transistor Tr612 will conduct, short-circuiting the gate and cathode of the thyristor which is thus cut-off. The circuit is designed to trip at approximately 8Hz, R608 going open-circuit in the event of a sustained overload.

Our experience has been that in the event of failure of R607 it's necessary to replace the following items for a no-comeback repair: Ty604, Di604, Tr612, R614, Di614, the main smoothing block C607/608/616/617 and of course R607.

Some time back we had this fault and replaced the components listed above. The set was given a soak test but after two hours R607 again disintegrated. The fault was eventually traced to the screened wire that couples the line drive to the gate of the flyback thyristor Ty501. This wire is routed below the power resistors, and had carbonised at this point, thus upsetting the operation of the thyristor line output stage. Since then it's been our policy always to check this length of wire visually and if in any doubt to replace it.

Brian Francis, Tech. (C.E.I.),
Plympton, Plymouth.

SHARP C2072

A Sharp Model C2072 came in for repair recently, the symptoms being as follows: during bright scenes the colour would disappear, accompanied by a loud whistling at a frequency which seemed to be below the usual 15.625kHz. There would also be severe line pairing and picture break-up, particularly at the edges. The symptoms would still appear, but much less frequently, if the contrast and brightness controls were turned down to give a dark, washed-out picture.

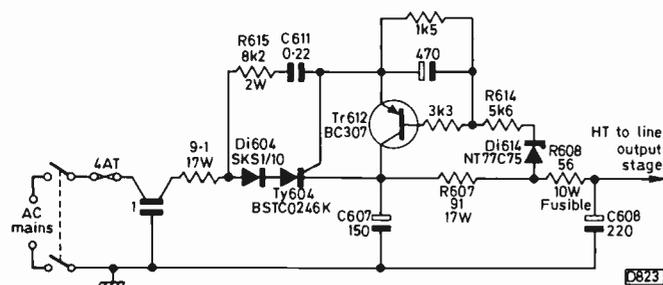


Fig. 1: H.T. rectifier circuit, Grundig 1510 series.

The customer told us that the set had started to go wrong about a year ago, but he could restore the picture to normal by either changing channels or turning the brightness down. As the problem had become progressively more frequent, he decided to have the set repaired. Another engineer had quoted £95 to replace the chopper and line output transformers, the tripler, and the chopper and line output transistors, but the customer decided to seek a second opinion.

We recalled that similar symptoms occur with the Thorn 9000 chassis when the 90V supply smoothing capacitor C715 deteriorates. The Sharp C2072 is not quite the same – it uses a series chopper circuit to produce a 120V h.t. line – but it seemed worthwhile trying the h.t. smoothing capacitor C717, which is a 47 μ F radial electrolytic rated at 200V. We extracted it and sure enough the telltale sign of a faint white powdery deposit was present near one of the leads. A replacement 47 μ F, 250V electrolytic immediately restored normal operation. Incidentally the faulty capacitor read all right on the meter – the best course is to check by substitution. We wondered what the other engineer would have done after replacing all those innocent components!

T. Barrett,
London E17.

VIDEO AMPLIFIER TRANSISTORS

I've received several letters asking about the transistors used in the video amplifier circuit shown in my article in the February issue (Fig. 1, page 189). Any small-signal npn/pnp/npn transistors will do, but those actually used were two BC548s and a BC558.

Harold Peters,
Oulton Broad, Suffolk.

METER REPAIR?

Many years ago, when Lisle Street was occupied by tarts and electronics shops rather than Chinese restaurants and blue movie shows, I bought a "faulty" meter for £1 from the collection of odds and ends on display outside one of the shops. It seemed to be in working order apart from reading 25 per cent low on all ranges. I was using it recently to check a faulty rear lamp on a vehicle parked on a slope: unfortunately the vehicle ran a foot or so down the slope and over the meter. The back of the case was shattered and the internal battery was squashed. Apart from that there appears to be little damage – and what's more the meter now reads accurately!

D.B., Tunbridge Wells.

BEOVISION BLANKING MODIFICATION

Those readers who keep their old 2600 and 3200 series Beovision colour sets going may be interested in the following method of improving the field flyback blanking. The problem arose when I noticed teletext signals flashing at the top of the picture. It seems that the use of more lines for teletext results in their showing up on receivers that have either slow flyback or inadequate blanking. Rather than trying to speed up the flyback, I thought it would be better to attempt to improve the blanking.

The original circuit is shown in Fig. 2. After inversion by the strapped triode sections of two ECL84 valves the flyback blanking pulses are fed via a screened cable to the "earthy" ends of the tube's first anode decoupling capaci-

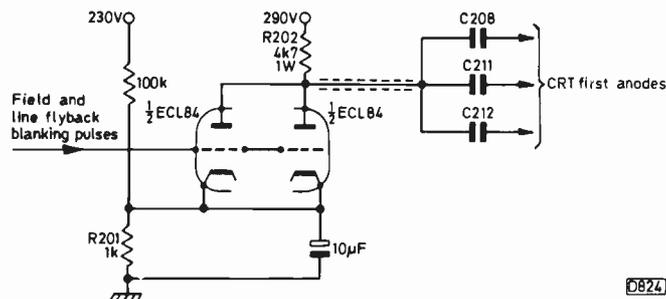


Fig. 2: Flyback blanking in the B and O 2600/3200 chassis.

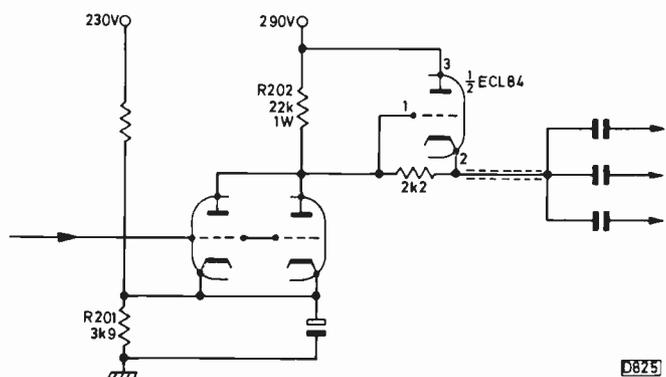


Fig. 3: Modification to remove teletext signals.

tors. One way of increasing the amplitude of the pulses would be to increase the value of the anode load resistor R202. Unfortunately this slows down the circuit's recovery time on the positive-going edges of the pulses, since the capacitance of the cable etc. has to charge via the anode load resistor. The result is a brightness gradient on the left-hand side of the screen.

Fortunately there's a third, unused ECL84 triode section – it's in the middle ECL84 of the colour-difference output trio. The circuit can easily be modified, on the back of the panel, to that shown in Fig. 3. Using a cathode-follower in this way ensures a quick pull up, the initial pull down being via the 2.2kΩ resistor. Sufficient blanking pulse amplitude is obtained to blank out the offending teletext lines. There are no tracks going to pins 1, 2 and 3 of the cathode-follower, so the necessary connections can be made without having to "hack and bodge".

Note the change in the value of the bias resistor R201 from 1kΩ to 3.9kΩ.

Keith Cummins,
Shirley, Southampton.

LOPT TESTER

I've made up the line output transformer tester featured in your February issue (page 180), having etched a board and using components from the junk box. It works well, but the emitter-follower transistor Tr3 got warm – the whole board took 38mA on load (connected to a trans-

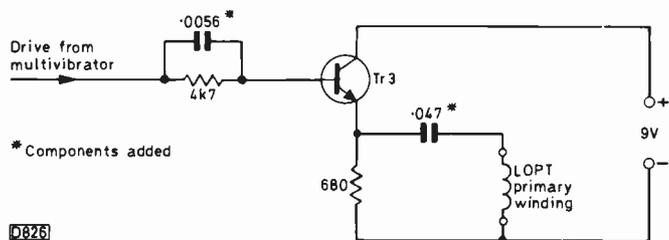


Fig. 4: LOPT tester modifications.

former), 8mA off load (with Tr3 cold). Adding an 0.047µF output coupling capacitor as shown in Fig. 4 provided the cure, the board taking 9mA on load with the transistors cold and the output reading unaffected. The addition of this coupling capacitor also saves Tr3's emitter resistor from being shorted out by either a faulty transformer or accidental contact between the line output valve anode/transistor collector lead and the negative lead of the 9V battery – this does Tr3 no good, and sometimes stops the circuit oscillating until switched on a second time.

Adding a small capacitor across Tr3's base resistor increases the output reading a little – the value I used was 0.0056µF.

H. Owens,
N. Ferriby, Yorks.

HOMES WANTED

Due to shortage of space, I must jettison from my collection of vintage and semi-vintage TV sets and radio receivers three Murphy V310s and a V320. The V320 and one of the V310s are workers, the other two requiring new line output transformers. Any takers?

W. J. Knight,
532, Rochester Way, London SE9 1SQ.

SATELLITE/CABLE TV

I've been following recent editorials concerning satellite and cable television with very great interest. These two transmission systems make strange bedfellows, the first being the ultimate in providing wide geographical coverage, the second a strictly limited method of distribution. Much publicity has been given to their marriage recently, a TV service in one UK town receiving the satellite signals and passing them on to viewers via cables. Despite all the ballyhoo about the high technology involved, a dispassionate consideration of the scheme must lead one to the conclusion that it's the definitive example of the use of a sledgehammer to crack a walnut. Since the programme matter apparently consists of taped or filmed offerings, the object of the exercise could have been achieved at a tiny fraction of the cost by simply installing a VCR and maybe telecine equipment at the cable company's distribution centre. Indeed even more money could have been saved by ignoring cables altogether and employing a low-power local TV transmitter. Other reports have mentioned a pirate TV station, whose backers seem to wish to dispel the contrived belief that only the combination of a government agency and huge finance can make such services possible.

The objections to the use of cheap, purely local TV transmitters are two-fold. On the one hand the establishment wishes to preserve the present BBC/IBA control of public broadcasting. Satellites provide a means of getting round this, distributing technically foreign programmes. On the other hand all programmes sent out via the existing terrestrial transmitter network are in effect free to the viewer once he's bought his set and his licence, whereas cable distribution makes it possible to charge him for every minute of screen time he watches. There's nothing much wrong with this, provided it's optional and doesn't affect the quality of the present services. The danger is that if cable TV ever achieved the coverage desired by its promoters, it might well corner the market in popular TV material, leaving off-air viewers very much poorer relations. It must not be forgotten that very large

areas of the country will never be served by cable, due to the sparse or scattered population.

The BBC would in this event hope to raise its licence revenue so that it could fight back, but what of ITV? Already saddled with the burden of financing Channel 4, faced with the growth of VCR use, and anxious to maintain viewing figures so as to sustain advertising revenue, the independent companies could find themselves very hard pressed. For the BBC and the IBA, either

separately or jointly, to finance a superfluous DBS service is in these circumstances as appropriate as a bankrupt third-world nation operating its own prestige air line. High technology is all very well, but not for its own sake. The BBC and the IBA have virtually complete coverage with their present transmitter network: they should swallow their pride and forget about DBS services.

*Chas E. Miller,
Woodseaves, Staffs.*

This Little Ting Here

Les Lawry-Johns

I suppose we all get a trifle confused over the various Bush models and chassis, and it's not till we take a closer look that our spirits rise or fall. So when these two rather elderly men puffed into the shop carrying a 22in. Bush colour set I immediately thought it was a late 823 chassis.

"There's a white line across the screen" said the tall one.

"No it isn't, it's a red line" said the short one.

"Fret not" I assured them, "'twill be put right in a trice."

The Bush Z718

I whipped the back off and my spirits fell. Seeing the swing down panel across the rear section I thought it was a T20. Then I saw the two line output transistors on the right-hand side and realised it was a Z718. My spirits fell further.

"Umm, it won't be put right in a trice."

"Don't worry. We've all the time in the world" said the tall one.

"Sure it's only a little ting" said the short one.

"That's because you don't have to find the little ting" I growled.

"Oh you'll find it in no time at all" he continued. "We'll just have a cigarette while you're doing it. Just carry on John."

Honey Bunch smiled and chatted to them about the weather while I delved into the field timebase. The transistors appeared to read right on a cold check, except for one of the output transistors, VT7. It gave a low reading from collector to emitter, the same on reversing the prods. Out came VT7, off its heatsink. In went a new 16905. Switch on and we had a nice, full-sized raster.

"There" said the short one, "didn't I tell you it was just a little ting you'd find in no time at all?"

I growled to myself something about what would happen to his little ting if he wasn't careful, then plugged in the aerial. No signals, just noise. None of the touch sensors were alright, so I touched the first one and dropped down the flap to tune it in. Wind the red pointer up and down but there was nothing except for a few flutters to reward my efforts. I then touched sensor two and with slight adjustment BBC-2 showed a news sheet. I felt better. Touch sensor three and the news sheet remained, even when I ran the number three red pointer up and down. It was still there in positions four and five, even though the pointers were in different positions. Position six could be tuned and I ran it up to BBC-1. Select sensor

two and BBC-1 is still present.

"You didn't tell me this lot was up the creek" I moaned.

"It's not up the creek" said the short one, "it's just a little ting here."

Whilst I was trying to read the tuner voltages on the connecting plug, looking for the tuning voltage in particular, he was spinning the little wheels and thus making me angry.

"See John, you have to get all these little pointers on the same line. Then they work."

I was fast losing my cool.

"All right then, if that's all there is to it you can take the set away now."

"No need to get upset over such a little ting."

The tall one saw how the wind was blowing and intervened.

"Leave it to Mr. Johns, Paddy. It's not working right and he'll sort it out if we leave him alone."

"Yes, leave it to him to tink out."

I chose my words carefully. "That's what I'm here for, tinkering tings out all day long".

Honey Bunch fled to the kitchen. I heard her talking to Ben. "He's out there tinkering. He'll need a bath tonight or he'll be tinkering tomorrow too." It didn't help. My logic, fragile at the best of times, had gone.

I removed the three nuts and took out the touch tuner panel, then accused the ETT6016 of bugging about. I took it out, having earthed myself to the live mains, and sustained a bleeding hand. "Calm down now. Try to think logically like ET does."

That little brass image still looks down at me, his finger pointing. Always pointing. Saying "you're not doing it right Les. Get the voltages right." But I didn't listen. I fitted another ETT6016 and what do you know - the neons started to work. They lit up when touched, and I was sure I was there. I wasn't.

Although they lit when touched, only six was tunable - and tuned the other five for God's sake.

Shorty moved in again. "It's this little ting here", pointing to the a.f.c. button. Out he moved, and ET's finger continued to point at me.

I checked the voltages against those given in the circuit. There should have been 188V at 9R39 on the touch tuning panel (Fig. 1). The reading was more like 30V - I'd previously taken this to be the tuning line, but it wasn't, it

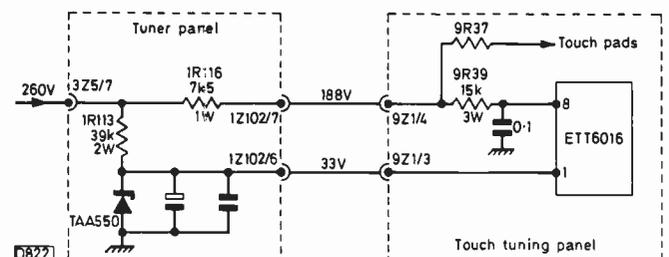


Fig. 1: Supplies to the touch tuning panel.

was the supply to the ETT6016. I traced the line back to the tuner panel, where I promptly got confused between 1R113 and 1R116. Like a fool I first accused 1R113, but it was 1R116 that was open-circuit of course. Replacing it restored normal channel selection and tuning.

Shorty looked at the faulty resistor. "Just a little ting..."

Having disposed of the comedy duo, we can consider the circuit briefly. 1R116 takes 260V at one end and drops 72V, providing a 188V supply at the other end for 9R37 and 9R39, the latter feeding the ETT6016. Hence the crazy behaviour when this supply is absent. I should have gone straight to it. Like you would, but I don't think like you.

Sparko's Return

I was just settling down for five minutes' read of the magazine when the door crashed open and in fell Mr. Sparks. Till that moment he'd been carrying his Thorn 8500. "Nice of you to drop in" we greeted him.

"Get this bloody set off my foot, Len" he bawled.

First it's John from Paddy, now it's Len from Sparko. What it is to be well known.

So I lifted the set off his foot and he hopped around like a wounded kangaroo.

"Why do I have to bring this bloody thing to you each time? Why can't you call out like civilised people do?"

"Because I'm too lazy and don't want to work too hard, that's why. Now what do you want me to do for you?"

"Just fix it for me Len. I don't care how much it costs as long as it's not more than a fiver."

I ignored that because Sparko never argues about the

bill. Mind you he does like to stop and watch and murmur every now and again "thank gawd it's not me with my hand in there."

So we took the back off, plugged the set in, and switched on. A blurred picture with no sound appeared. We switched off and checked the speaker, which was o.k. We then removed the power panel which, as you know, is where the MJE340 audio output transistor VT701 lives. It had base-emitter leakage, so out it came. I looked in my little drawer marked MJE340 and took one out. It was of entirely different construction, and I stared at it in disbelief. The one from the set was of the TO126 type, like the BD131. The one in my hand was of the TO220 type. The base and emitter leads were reversed, so it had to go in on the reverse side of the heatsink to get the connections right. When fitted, the sound was loud and clear, so the voltage rating was right. Later investigation proved that the transistors in the drawer should have been marked MJE340K (30W rating). Ho hum.

The blurred picture didn't respond to adjustment of the focus control, so the e.h.t. rectifier unit came under suspicion (the built in resistor goes high in value). Smiling at Mr. Sparks, we removed the suspect unit and fitted a new one. The focus was now good and the sound loud and clear. "Did you say a fiver Sparko?"

"Just joking Len."

Hallo Stan!

Hardly had Sparko left than Mr. Murray walked in. He's been coming in for seventeen years.

"Hallo Stan, how's your luck?"

"My name's Hilda Mr. Murray..."

TOP TWENTY T.V. SPARES		LINE OUTPUT TX		CAPACITORS		INTEGRATED CIRCUITS		SPECIFIC SPARES		NEW PRODUCTS	
STOCK NO.		001 Philips G8	7.50	066 Pye CT200 5 Lead	4.50	140 5 x TBA440	3.00	350 Thom	1590/1	423 Thom	1590/91
001 Philips G8 Loptx (Genuine Philips)	7.50	002 Decca 30 Series	7.00	067 Korting Hybrid	5.00	141 5 x TBA120AS	1.80	43 x23	2.00	461 U321 New Tuner	7.95
002 Decca 30 series Loptx (Genuine Decca)	7.00	003 Decca 100 Series	6.50	068 Grundig 3010/1500	3.00	142 5 x TBA540	4.00	357 Thom	1590/1	462 U322 New Tuner	7.95
003 Decca 100 series Loptx (Genuine Decca)	6.50	004 ITT CVC 25/30/32	7.00	080 220/400 CVC 32-	1.20	143 5 x TBA540Q	4.00	371 Pye 713/731 Vis. Gain	6.50	463 Cut Out Metal GEC	2100
004 ITT CVC 25/30/32 Loptx (Genuine ITT)	7.00	005 Philips G9	7.50	081 200 + 300 Pye 691/	2.00	145 5 x TBA590	3.50	370 Pye 731 Thick Film	1.50	464 5 x GEC2100 3 Leg	Thermistor
005 Philips G9	7.50	006 RRI T20	9.92	082 600/300 Philips G8	1.90	146 5 x TBA810S	3.00	371 Pye 713/731 Vis. Gain	6.50	465 ELC1043/05 Repaired	Tuner
006 RRI T20	9.92	007 RRI A823	7.00	083 175+100+100 Thorn	3500	147 5 x TBA920L	4.50	352 Thom	1800	466 ELC1043/06 Repaired	Tuner
007 RRI A823	7.00	008 RRI Z718 18"	18.95	084 2000/100 Can	0.50	148 5 x TBA990Q	3.25	352 Thom	1800	467 ELC1043/06 Repaired	Tuner
008 RRI Z718 18"	18.95	009 RRI Z718 20/20/26"	18.95	085 470/250 Philips	G11	149 5 x TBA520Q	4.00	352 Thom	1800	468 ELC1043/06 Repaired	Tuner
009 RRI Z718 20/20/26"	18.95	010 RRI A774 Mono	10.87	086 400+400 Decca 30	2.50	150 5 x TBA530Q	4.25	352 Thom	1800	469 ELC1043/06 Repaired	Tuner
010 RRI A774 Mono	10.87	011 Thorn 1890/91	7.90	087 200+200+75+25	1.50	151 5 x TBA950	4.50	352 Thom	1800	470 5 x GEC2100 3 Leg	Thermistor
011 Thorn 1890/91	7.90	012 Thorn 1615	6.30	088 400/400V Thorn	9000	155 5 x MC1327Q	1.50	358 5 x Thorn 3500 200R	Conv. Pot.	471 U321 New Tuner	7.95
012 Thorn 1615	6.30	013 ITT CVC 45	5.90	092 10 x 220MF 16V	Elect.	161 TDA1170	1.90	359 5 x Thorn 3500 50R	Conv. Pot.	472 U322 New Tuner	7.95
013 ITT CVC 45	5.90	014 Phil TX Chess.	5.90	093 10 x 047MF 400V	Poly	162 TDA1008A	1.45	370 Pye 731 Thick Film	1.50	473 5 x Gen. Purpose Rotary	Switch
014 Phil TX Chess.	5.90	015 RRI Ranger 1/2	5.90	094 5 x 4.7MF/100V C514	T3500	163 TDA1035	1.83	371 Pye 713/731 Vis. Gain	6.50	474 5 x Gen. Purpose Push	Button
015 RRI Ranger 1/2	5.90	016 ITT CVC 5/9	8.50	095 5 x 91NF Philips	G11	164 TDA1094	2.23	372 Pye 731 3R3 50W	Metal clad	475 5 x Gen. Purpose Push	Button
016 ITT CVC 5/9	8.50	017 Philips E2 Chess.	5.90	096 5 x 1200V 2.0C	097 10 x 1/250 Suppression	172 TDA2002	1.80	372 Pye 731 3R3 50W	Metal clad	476 5 x Gen. Purpose Push	Button
017 Philips E2 Chess.	5.90	018 Thorn 9500/9800	8.50	098 5 x 1/250 Suppression	ITT	173 TDA2020	2.50	372 Pye 731 3R3 50W	Metal clad	477 5 x Gen. Purpose Push	Button
018 Thorn 9500/9800	8.50	020 Polish 161 Mono	Loptx	099 10 x 1/250 Suppression	ITT	174 TDA2030	2.15	372 Pye 731 3R3 50W	Metal clad	478 5 x Gen. Purpose Push	Button
020 Polish 161 Mono	Loptx	021 Thorn 3500 Scan	4.50	100 10 x 220MF 16V	Elect.	175 TDA2523	2.35	372 Pye 731 3R3 50W	Metal clad	479 5 x Gen. Purpose Push	Button
021 Thorn 3500 Scan	4.50	022 Thorn 8500	11.00	101 10 x 047MF 400V	Poly	176 TDA2532	2.40	372 Pye 731 3R3 50W	Metal clad	480 5 x Gen. Purpose Push	Button
022 Thorn 8500	11.00	023 Thorn 8500	11.00	102 10 x 047MF 400V	Poly	177 TDA2540	1.85	372 Pye 731 3R3 50W	Metal clad	481 20 x neons	GEC etc.
023 Thorn 8500	11.00	024 Thorn 8500	11.00	103 10 x 047MF 400V	Poly	178 TDA2540	1.85	372 Pye 731 3R3 50W	Metal clad	482 5 x Universal Aerial	Skt.
024 Thorn 8500	11.00	025 Thorn 8500	11.00	104 10 x 047MF 400V	Poly	179 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	483 10 x Metal Coax	Plug
025 Thorn 8500	11.00	026 Thorn 8500	11.00	105 10 x 047MF 400V	Poly	180 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	484 Focus Unit	T20 Type
026 Thorn 8500	11.00	027 Thorn 8500	11.00	106 10 x 047MF 400V	Poly	181 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	485 Focus Unit	Thorn 8500 Type
027 Thorn 8500	11.00	028 Thorn 8500	11.00	107 10 x 047MF 400V	Poly	182 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	486 Focus Unit	Thorn 8500 Type
028 Thorn 8500	11.00	029 Thorn 8500	11.00	108 10 x 047MF 400V	Poly	183 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	487 Focus Unit	Thorn 8500 Type
029 Thorn 8500	11.00	030 Thorn 8500	11.00	109 10 x 047MF 400V	Poly	184 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	488 Focus Unit	Thorn 8500 Type
030 Thorn 8500	11.00	031 Thorn 8500	11.00	110 10 x 047MF 400V	Poly	185 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	489 Focus Unit	Thorn 8500 Type
031 Thorn 8500	11.00	032 Thorn 8500	11.00	111 10 x 047MF 400V	Poly	186 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	490 Focus Unit	Thorn 8500 Type
032 Thorn 8500	11.00	033 Thorn 8500	11.00	112 10 x 047MF 400V	Poly	187 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	491 Focus Unit	Thorn 8500 Type
033 Thorn 8500	11.00	034 Thorn 8500	11.00	113 10 x 047MF 400V	Poly	188 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	492 Focus Unit	Thorn 8500 Type
034 Thorn 8500	11.00	035 Thorn 8500	11.00	114 10 x 047MF 400V	Poly	189 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	493 Focus Unit	Thorn 8500 Type
035 Thorn 8500	11.00	036 Thorn 8500	11.00	115 10 x 047MF 400V	Poly	190 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	494 Focus Unit	Thorn 8500 Type
036 Thorn 8500	11.00	037 Thorn 8500	11.00	116 10 x 047MF 400V	Poly	191 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	495 Focus Unit	Thorn 8500 Type
037 Thorn 8500	11.00	038 Thorn 8500	11.00	117 10 x 047MF 400V	Poly	192 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	496 Focus Unit	Thorn 8500 Type
038 Thorn 8500	11.00	039 Thorn 8500	11.00	118 10 x 047MF 400V	Poly	193 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	497 Focus Unit	Thorn 8500 Type
039 Thorn 8500	11.00	040 Thorn 8500	11.00	119 10 x 047MF 400V	Poly	194 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	498 Focus Unit	Thorn 8500 Type
040 Thorn 8500	11.00	041 Thorn 8500	11.00	120 10 x 047MF 400V	Poly	195 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	499 Focus Unit	Thorn 8500 Type
041 Thorn 8500	11.00	042 Thorn 8500	11.00	121 10 x 047MF 400V	Poly	196 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	500 Focus Unit	Thorn 8500 Type
042 Thorn 8500	11.00	043 Thorn 8500	11.00	122 10 x 047MF 400V	Poly	197 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	501 Focus Unit	Thorn 8500 Type
043 Thorn 8500	11.00	044 Thorn 8500	11.00	123 10 x 047MF 400V	Poly	198 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	502 Focus Unit	Thorn 8500 Type
044 Thorn 8500	11.00	045 Thorn 8500	11.00	124 10 x 047MF 400V	Poly	199 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	503 Focus Unit	Thorn 8500 Type
045 Thorn 8500	11.00	046 Thorn 8500	11.00	125 10 x 047MF 400V	Poly	200 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	504 Focus Unit	Thorn 8500 Type
046 Thorn 8500	11.00	047 Thorn 8500	11.00	126 10 x 047MF 400V	Poly	201 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	505 Focus Unit	Thorn 8500 Type
047 Thorn 8500	11.00	048 Thorn 8500	11.00	127 10 x 047MF 400V	Poly	202 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	506 Focus Unit	Thorn 8500 Type
048 Thorn 8500	11.00	049 Thorn 8500	11.00	128 10 x 047MF 400V	Poly	203 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	507 Focus Unit	Thorn 8500 Type
049 Thorn 8500	11.00	050 Thorn 8500	11.00	129 10 x 047MF 400V	Poly	204 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	508 Focus Unit	Thorn 8500 Type
050 Thorn 8500	11.00	051 Thorn 8500	11.00	130 10 x 047MF 400V	Poly	205 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	509 Focus Unit	Thorn 8500 Type
051 Thorn 8500	11.00	052 Thorn 8500	11.00	131 10 x 047MF 400V	Poly	206 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	510 Focus Unit	Thorn 8500 Type
052 Thorn 8500	11.00	053 Thorn 8500	11.00	132 10 x 047MF 400V	Poly	207 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	511 Focus Unit	Thorn 8500 Type
053 Thorn 8500	11.00	054 Thorn 8500	11.00	133 10 x 047MF 400V	Poly	208 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	512 Focus Unit	Thorn 8500 Type
054 Thorn 8500	11.00	055 Thorn 8500	11.00	134 10 x 047MF 400V	Poly	209 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	513 Focus Unit	Thorn 8500 Type
055 Thorn 8500	11.00	056 Thorn 8500	11.00	135 10 x 047MF 400V	Poly	210 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	514 Focus Unit	Thorn 8500 Type
056 Thorn 8500	11.00	057 Thorn 8500	11.00	136 10 x 047MF 400V	Poly	211 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	515 Focus Unit	Thorn 8500 Type
057 Thorn 8500	11.00	058 Thorn 8500	11.00	137 10 x 047MF 400V	Poly	212 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	516 Focus Unit	Thorn 8500 Type
058 Thorn 8500	11.00	059 Thorn 8500	11.00	138 10 x 047MF 400V	Poly	213 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	517 Focus Unit	Thorn 8500 Type
059 Thorn 8500	11.00	060 Thorn 8500	11.00	139 10 x 047MF 400V	Poly	214 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	518 Focus Unit	Thorn 8500 Type
060 Thorn 8500	11.00	061 Thorn 8500	11.00	140 10 x 047MF 400V	Poly	215 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	519 Focus Unit	Thorn 8500 Type
061 Thorn 8500	11.00	062 Thorn 8500	11.00	141 10 x 047MF 400V	Poly	216 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	520 Focus Unit	Thorn 8500 Type
062 Thorn 8500	11.00	063 Thorn 8500	11.00	142 10 x 047MF 400V	Poly	217 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	521 Focus Unit	Thorn 8500 Type
063 Thorn 8500	11.00	064 Thorn 8500	11.00	143 10 x 047MF 400V	Poly	218 TDA2541	2.67	372 Pye 731 3R3 50W	Metal clad	522 Focus Unit	Thorn 8500 Type
064 Thorn 8500	11.00	065 Thorn 8500	11.00	144 10 x 0							

VCR Servicing

Part 27

Mike Phelan

The 3V24's capstan servo has provision for still frame and slow motion, the latter by remote control. We'll look at normal record and playback operation first.

Capstan Servo

A block diagram of the capstan servo is shown in Fig. 122. It's a dual-loop arrangement, i.e. with both speed and phase control. The speed control loop uses a VC1029, as in the drum servo, but this time operating at 126Hz. If the capstan speed increases, the voltage at pin 10 of the VC1029 falls. There's no inversion in the motor drive amplifier, so the capstan motor speed falls to compensate for the initial rise. Stable conditions are obtained at about 3-8V. The phase control loop is mainly contained in IC1, where the 32.768kHz oscillator is shared with the drum servo.

On record, the only need is for close control of the speed. So the phase control loop compares the 21Hz trapezoid derived from the crystal oscillator with the 21Hz pulse train obtained by dividing the FG signal by six. Test point TP5 is included to enable the trapezoid and pulse to be viewed simultaneously. The error voltage of about 4-5V at pin 25 goes positive to decrease the motor's speed, because the inverting input of IC15 is used. C101, C102, R223 and R224 form the loop filter.

On playback the oscillator and divider produce a 25Hz trapezoid which is gated by the amplified pulses from the control head. The pulses are passed through monostable IC6 which provides a delay of about 20msec.

In record and playback (also audio dub) two sections (S1 and S2) of IC14 are closed because pins 5 and 6 are high (inverter X40's output is high). S3 and S4 are both open. The loop filter is thus in operation. In stop, fast forward and rewind, X42 turns the motor off. In search fast forward, search rewind, slow and still D40 or D41 conducts, S3 and S4 close, and X40 opens S1 and S2. This removes the phase error voltage from the motor drive input, connecting the latter to the junction of R225 and R226 instead to give the correct free-running speed. This point is also connected to the junction of C101 and C102 in the loop filter to maintain the charge on these capacitors - otherwise the lock-up time on returning to normal play would be excessive. If the off-tape control pulses are lost during playback (or audio dub) D39 conducts, producing the same effect, i.e. S3/4 closed and S1/2 open. Severe hunting would occur if it were not for this.

Fig. 123 shows the control pulse detector circuit. During playback and audio dub, C99 and D38 d.c. restore the pulses, biasing X38 on. The after-load switch is closed, biasing X9 on. C100 charges to 9V, holding X39 and D39 off. The servo then works normally. If the control pulses are interrupted, due to mechanical shock for example, C100 discharges, X39 turns on, D39 receives forward bias and the servo switches to the free-running condition. We don't want this part of the circuit to operate in record, when servo control is essential. This condition is met by supplying the emitter of X39 from the PB 9V line.

Though the motor is stopped via X42 in the stop, fast forward and rewind modes we want the free-run condition to maintain the charge on the loop filter. The after-load switch is open in these modes, so X9 is off. X39 is still powered from the PB 9V line however, so D39 conducts to give the free-running condition.

Still and Slow Drive

The still and slow capstan drive system is shown in Fig.

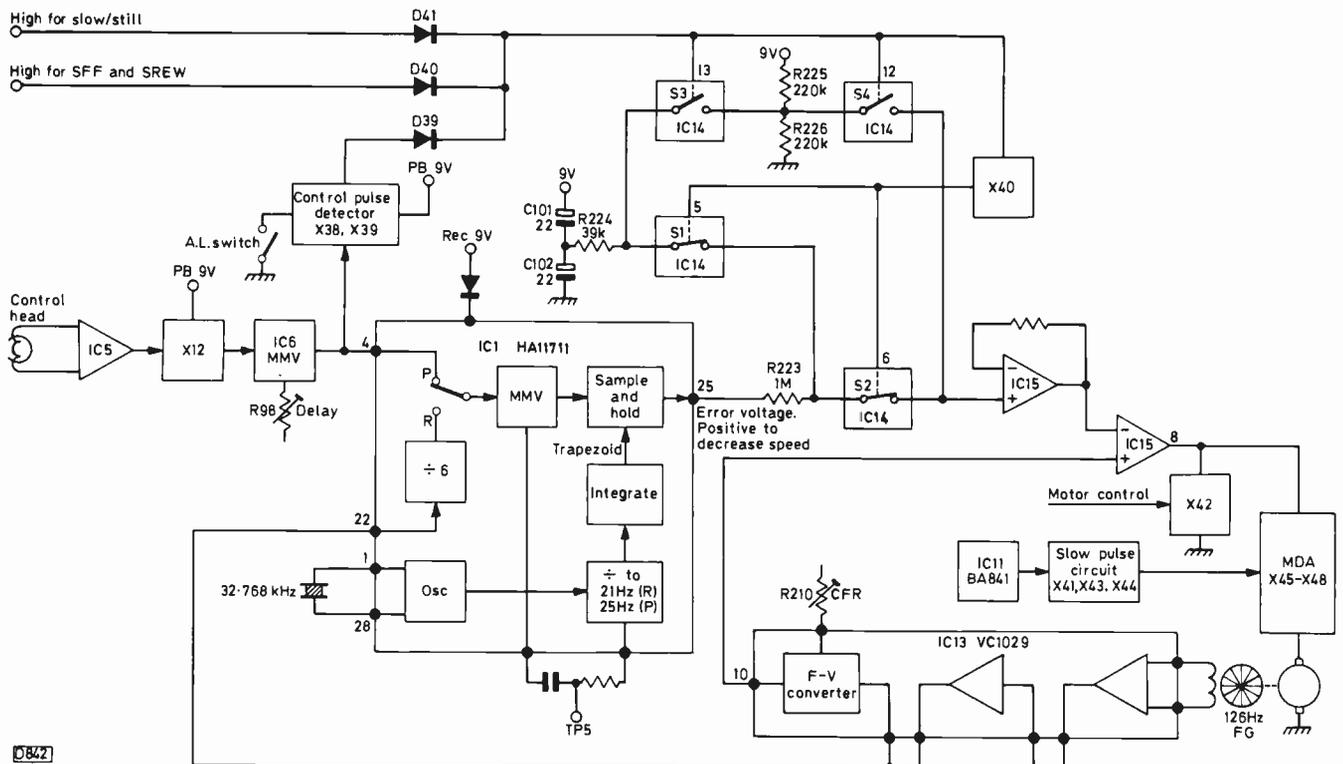


Fig. 122: Block diagram of the capstan servo.

124. It may look a bit complicated, but is not too bad if split into two sections. As in the previous machines we've dealt with, a BA841 i.c. is used for slow motion/still frame capstan control, though the circuit is less complex than that used in the 3V23.

In modes other than playback, record, audio dub and shuttle search, X42 is on, removing the control voltage from the motor drive amplifier by turning off D45. This turns X45 on and the Darlington X47 off, stopping the motor. X46 and X48 are used in slow/still as a brake, normally being off. D46 ensures that X47 is off when X46 is on, otherwise the 12V rail would be shorted out.

When D45 is off, we can drive the motor with a slow pulse as in the 3V23 – a large amplitude pulse to overcome the inertia, followed by a smaller pulse. D33, D34, X33 and X34 form an OR gate to supply 9V to the slow-pulse network in the slow or still modes. Pin 30 of the BA841 is the FF2 output – we don't use FF1 here. Pin 30 goes high to move the motor, low to stop it. During normal running it's high, so that X41 is on and X43 is off: the path to chassis via X41 forward biases D45 and X45, closing the servo loop.

The internal workings of the BA841 have been dealt with in previous articles on the 3V23 and 3V16. Suffice it to say that flip-flop FF2 is set by the drum FF signal and reset by the control head pulses, so that the tape stops at an exact position with reference to the latter. The process is repeated four times, as the tape position at the start of the process is indeterminate. For slow motion further single pulses are generated to drive the capstan, the interval between the pulses being set by the slider control on the remote hand unit.

When still is selected (or the camera trigger is released), X42 turns on, stopping the motor, and FF2 resets. FF2 next sets, turning X41 on and X43 off so that R229 supplies X45 with some 9V. The motor starts. X44 is off at this point, because when FF2 sets X36 is turned on, triggering the monostable connected to pin 26 of IC11. This gives a high at pin 27 after 18msec, turning on X44 and reducing the drive pulse to 2.3V due to the network

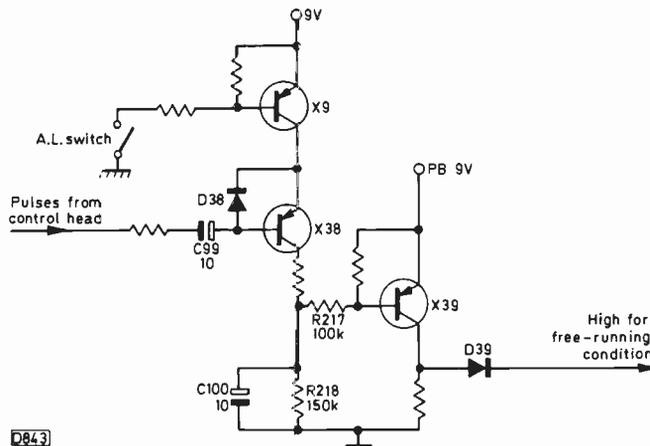


Fig. 123: The control pulse detector circuit.

R229/R243. The pulses at the collector of X36 are also applied to the vibrate circuit in the drum servo to minimise sideways movement of the picture in slow motion. The tape moves until a control pulse arrives from the tape. This resets FF2, turning X41 off and X43 on, X46 and X48 conducting to brake the motor. R189 and R191 adjust the width of the slow pulse.

Pin 37 of the BA841 provides dummy field sync pulses, as in the 3V16, one of the pulses being user adjustable to minimise jitter.

Edit Start System

Before leaving the capstan servo to look at the reel servo we must explain the edit start system. If you read the articles on the 3V23, you will recall that when record pause is selected the tape winds back by approximately 30 fields and then stops. When restarted, the capstan goes into the playback mode to lock to the previous recording's control pulses, the record capstan reference (FG) being synchronised to the control track pulses by resetting the counter before the record mode is entered. In addition, if

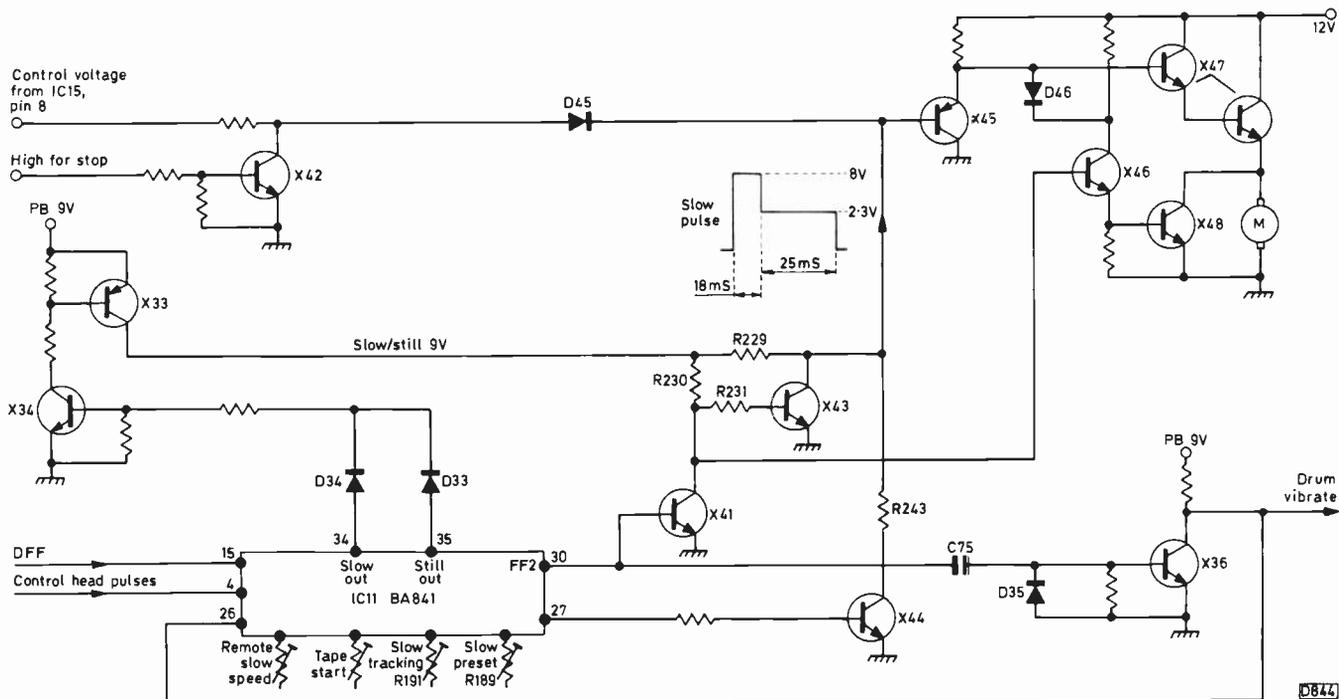


Fig. 124: Still and slow drive system.

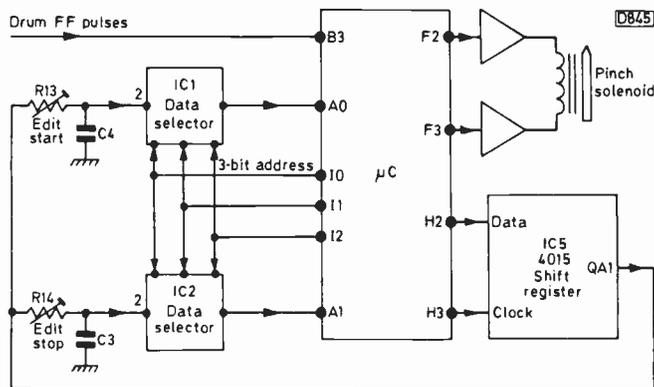


Fig. 125: The edit start system.

the signal is interrupted, as will happen with channel change or possibly when editing out adverts, the drum servo relocks to the sync before the machine recommences recording. The system is complicated but gives perfect edits.

A very much simpler system is used in the 3V24 (see Fig. 125). The circuit may not make much sense at first glance – there appear to be only two extra presets and capacitors. It works like this. If the tape is stopped at a precise point in time with reference to the incoming signal

(say when the drum FF changes state, as this is locked to the field sync) and is restarted at the same point, the control track pulses should be evenly spaced – they are derived from the field sync pulses. Adjustments are required because pinch wheel movement takes a finite time. This movement must be kept to a minimum, typically 0.1mm clearance from the capstan to the pinch wheel in pause.

On the next positive-going excursion of the drum FF signal after record pause has been selected, IC5 produces a high at QA1. The microcomputer i.c. sorts this out. It coincides with the end of the ch. B head trace. Because of the presence of R14 and C3, input 2 of IC2 does not go high immediately. When it does, the data fed to A1 tells the pinch solenoid to release.

On pressing the play button or operating the camera trigger to restart the tape, the opposite sequence occurs – the microcomputer waits for the drum FF to go positive, QA1 then goes low, C4 discharges through R13, the input to IC1 goes low, the output to A0 changes and the pinch solenoid is re-engaged.

R13 and R14 are adjusted for the same delay at stop and start, subject to variables such as solenoid inertia and variation in the high and low logic threshold levels for IC1 and IC2.

We'll deal with the reel servo next month.

The B & K 467 CRT Tester/Reactivator

Eugene Trundle

Fear of tube failure has been a dominant worry ever since the start of domestic TV services, and was if anything stronger in the monochrome-only era. It's probably been the main reason for the British habit of TV rental – only recently has there been a trend away from this. It's true to say that in 1984 few TV sets, either monochrome or colour, justify tube replacement on economic grounds. The reasons for this are the increasing cost of transport and labour, the diminishing (in real terms) price of new sets, and the fact that good second-hand sets are plentiful. I for one am reducing my expensive stockholding of spare tubes!

Over the years there have been any number of boosters, jackers, reactivators and rejuvenators, call them what you will, all serving the purpose of staving off the day of the picture tube's demise. Constructional projects and reviews of such devices have often appeared in these pages. All work on the same basic reactivation principle – passing a heavy forward current through the diode formed by the tube's cathode and control grid in order to disturb and break up the cathode's emissive surface. The operation can be likened to removing the skin of a rice pudding by bringing it to the boil! The process is rather crude, and needs to be carefully controlled to avoid stripping the emissive coating from the cathode's nickel surface.

Many early reactivators were rather heavy-handed in this respect. Some were probably responsible for killing almost as many tubes as they rejuvenated, especially when used by clumsy or inexperienced hands. Boosters vary in their degree of sophistication: I've come across most types, both gentle and brutal, in my servicing career.

The advent of colour saw the introduction of new types, basically similar but with gun-switching facilities and often clumsy base connector boxes to cater for the different pinning arrangements used in different tubes. Many of

these early boosters could not easily cater for the new tube types introduced in recent years – I never did find one that could do much for a Sony Trinitron tube, even with a suitable base socket in use.

Our faithful workshop reactivator gave up the ghost some months ago, and we took the decision to pension it off rather than patch it up again. Eleven years' service is not a bad record, and we've certainly had our money's worth during this time. Whilst looking at what's now available I found that the choice is somewhat limited. The main contenders come from Leader and B and K – Japanese and American respectively. The latter is far more expensive, but after enquiring among several satisfied users I decided to try it out.

Features

The 467 is much more sophisticated than other tube testers/reactivators. The array of dials, lights, buttons and knobs is reminiscent of a helicopter's flight deck, and impresses the customer no end! The instrument is built into a tough polyethylene attache case, with carrying handle and lead storage. The operating panel is revealed when the lid is opened. There are three moving-coil meters at the top, one for each gun of the tube under test. The operating controls and indication lamps are grouped beneath these meters in a logical layout – setting controls on the left, checking and restoring controls on the right. A pocketed flap in the lid holds the operating instructions and set-up charts. Behind this there's a foam-moulded storage tray for the various base adaptors for monochrome and colour tubes.

The three meters enable the emission and warm-up times of the three guns to be assessed simultaneously. Each meter serves two purposes, so that the heater,

control grid and mains voltages can also be read accurately. The heater voltage (0-14V) is set by a switch and a potentiometer: 2A is available at up to 7V, 600mA beyond. Neon bulbs provide interelectrode leakage indication and, unusually, a continuity check to the focus electrode. Another uncommon feature is the "life test" which gives a prognosis at the press of a button. There's a remove-short facility for shifting grid-cathode leaks, and the rejuvenation process is available in two forms – a gentle clean-and-balance operation, or the more thorough type of routine. Each of these is a special timed process, as we shall see.

Testing Methods

There's not space here to provide a detailed account of the instrument's unique operating principles, so I'll confine myself to a brief description of the main functions.

In the emission test mode the tube's three guns are individually and sequentially addressed by a clocked digital logic system. Each gun is pulsed about twenty times a second, the peak current for each gun being indicated on its own meter. This pulsing technique allows a digitally-programmed first anode voltage regulator to set the cut-off point for each gun, even with a common anode assembly or the first anodes strapped together. During the tracking test, in which the gun characteristics are compared, the duty cycle of each gun is reduced and the resulting beam current indicated on the corresponding meter. Provided the best and worst guns have an acceptable emission ratio (less than 1.5:1), the meter indications will stay within the yellow tracking segments.

The life test is a useful feature. It works by reducing the heater current by fifteen per cent – achieved by switching primary taps on the mains heater transformer. If the emission of all guns remains satisfactory under these conditions, it can be assumed that the tube has at least a year or two's life left.

Interelectrode leakage is indicated by five neons, one each for the cathodes, heater and commoned grids. Because of the sequential gun-addressing system, the position of any leak, including intercathode ones, can be ascertained. Shorts between grid and cathode are blown clear by a capacitor discharge initiated by the remove-shorts button. A further neon is used in the focus electrode continuity test. This detects an open-circuit by reducing the first anode voltages and looking for an increase in the current flowing via the focus electrode. The increase is sufficient for the neon to strike, and by observing the emission meters during this test an open-circuit focus electrode in a strapped triple-gun assembly can be detected.

Reactivation

So we come to the B and K 467's main feature, its rejuvenation process. To prevent rupturing the cathode and thus ruining the tube, the current flowing during and also the duration of the "blasting" process must be precisely controlled. Two levels of reactivation current can be used, a low one for the clean/balance process, which can be safely used with any tube regardless of its condition and value, and a high one for rejuvenation.

So far so good, but cathodes can vary enormously, not only regarding contamination and wear but also in physical shape and size. Modern tubes use tiny quick-heat cathodes with a small emissive surface, whereas most

monochrome and delta-gun tubes have large cathodes with a considerable coated surface area. Plainly each case calls for a different degree of blasting, and the problem is to ensure that justice is done in all cases without over cooking things.

The 467 achieves this by making the cathode itself the arbiter of its treatment. The heater current is first automatically increased to bring the cathode to an abnormally high temperature. The heater is then turned off and the rejuvenation current is simultaneously applied. A heavy current flows initially, but as the cathode temperature drops so the current falls, soon decaying to zero. This means that a large, robust and thermally inert cathode will get (and withstand) a sustained rejuvenation cycle, whereas the more fragile Trinitron and quick-heat cathodes will be restored without being wrecked.

Use and Performance

To test any monochrome or colour tube, reference is first made to the set-up chart. This lists virtually all known tube types and gives the approximate heater voltage and adaptor socket number. Once the correct adaptor has been fitted the test procedure is fairly simple, involving initial setting of the heater, grid and first anode voltages, followed by the emission test and then push-button checks on the tube's various conditions. This becomes routine after using the instrument a few times, and I soon learnt the adaptor types and procedures for the limited number of tube types I have cause to test. It was necessary to order one optional extra adaptor, for the small Trinitron tubes, but all the other tubes I encounter are catered for by the six adaptors that come with the instrument.

The auto-timing feature made me feel more at ease when rejuvenating tubes, and as far as I can see the only way to wreck a tube would be to continually repeat the rejuvenation process until the cathode finally died – this would call for a conscious and determined effort! The instrument will not do anything for heater-cathode leaks (neither will any other I know of), but on the one occasion that I encountered a cathode-grid leak the remove-shorts procedure revealed all – in the red picture, since the short was in the red gun.

I was very pleased with the results of the reactivation process. Given that the tube has all three heaters alight and no mask or screen defects, a useful and long-lived boost can almost always be obtained – unless the tube is completely worn out or has been previously over cooked by another reactivator. Certainly this is the first instrument I've come across that can give a new lease of life to a Trinitron tube: I've dealt with several of these successfully, and only one (about twelve years old) subsequently died. I believed (and still do!) that Trinitron tubes are manufactured with some sort of anti-jack characteristic in their cathode coatings . . .

The life test and tracking check facilities enabled me to get a pretty good idea of the condition and performance of the tube under test, and a reasonable indication of how long it could be expected to last. This is particularly useful for those testing ex-rental or second-hand sets before buying them. I chose not to use the little guarantee cards packed with the tester for dispensing to the happy owners of tested and rejuvenated tubes!

As with any tube tester, it's important to unplug the set under test from the mains supply, and in particular to discharge any e.h.t. from the anode cavity of a tube being treated. The test procedure necessarily turns on the guns,

whereupon a conductive path is established to the tube's final anode. This conductive path will raise the instrument (and the operator!) to whatever e.h.t. level was stored in the Aquadag coating. Nasty . . .

I dismantled the instrument to assess its quality and the workmanship. The bottom deck consists of a fibreglass board containing a pair of 7400 series logic chips, ten transistors, lots of resistors and an army of diodes and rectifiers. Surprisingly, a lone valve sits on this board, a 12BH7A double triode. Elsewhere are a couple of heavy mains transformers and the potentiometers, pushbuttons and meters associated with the operating panel.

From long experience of commercial tube testers I find that the weak spots are the set-heater potentiometer, the function switch and particularly the multicore test cable and its terminations. I carefully examined all these items in the 467. The heater potentiometer is very beefy, rated at 12W, so I wouldn't expect any problems here. The function switch has scores of connections and would be difficult to change, but it looks reliable – a similar switch in my old tester has given no trouble during its many years' use. The test lead is terminated in a way that prevents stress or fatigue at either end, while the multipin flying plug (into which the base adaptors fit) looks rugged – it needs to be! I suspect that the most commonly used base sockets will eventually wear out, but these are available as spares at about £8 plus VAT each.

I'm told that all spares are available, in or out of guarantee, from the importers (address at end). They also

carry out guarantee service during the first year and operate a free updating service (on request) for new tube types as they appear. As new base adaptors become necessary, these will be made available from the same source.

Conclusion

In conclusion, the instrument is now a feature of our workshop. Three hundred and sixty pounds plus VAT is a lot of money, and there's less here than in £360's worth of new colour TV set. There are many reasons for this however – and you can't rejuvenate tubes with a CTV! It may be difficult to justify the expense in a situation where the instrument won't get a lot of use, say in a one-man-band concern. In a busy workshop where a lot of servicing is carried out however my opinion is that the instrument is worth every penny! In an organisation such as mine it will probably pay for itself in a very few months. One of the crosses I have to bear is taking decisions on whether to continue maintenance contracts on old sets. The possession of this instrument has lately tipped the balance in favour of renewing many border-line contracts I might not have agreed to continue before. Let that speak for itself!

The B and K Model 467 is available to the trade at around £360 plus VAT from Radio Supplies Components Ltd., PO Box 27, Hartlepool, Cleveland TS24 7BR (telephone 0429 75750) and from various wholesale distributors.

TV Fault Finding

Reports from Richard Roscoe, John Coombes, Tony Thompson and M.S. Barakat

A Plague of Portables

Down here beyond the Tamar, the tempo of service life alters subtly as the days lengthen and temperatures rise. Triplers and line output transformers are packed up and put away ready for next winter's onslaught of dampness and mains surges. In their place are set out the weapons for the summer campaign: fuses, diodes, thyristors, mains droppers and smoothing capacitors to deal with our warm weather foe – the annual Plague of Portables.

Each year swarms of summer visitors, or "Emmets" if you're stuck behind one in a country lane, descend on our county carrying with them all they think they'll need for a fortnight of fun. Along with the caravan, kids, dinghy, dog, broly, bucket and spade, a large number of them bring the portable from the bedroom or kitchen. Unfortunately they rarely bring the instruction book, which they've never read anyway, so connecting the set to the car battery the right way round is a matter of luck for them – and work for us. Hence the fuses, diodes, etc.

Some get through this first hurdle only to falter at the next. They find that the set hasn't taken kindly to being torn from its warm, comfy shelf, pitched into a bucking caravan with a motley assortment of household items, driven 400 miles and then plugged into an alien power supply. Years of reliable service are wiped out at a stroke in an orgy of dry-joints, drifting tuner potentiometers, dirty presets or other, more expensive, acts of vengeance. The latter also come our way, usually on the last day of the family holiday. Like the Ferguson Colourstar portable we had to deal with recently.

It was a Model 3756, with 14in. screen, and had gone

dead the night before. This proved to be because the 1.6A mains fuse had blown, which is not an uncommon occurrence with these TX9 sets. Often there seems to be no cause, and Thorn have introduced several modifications to combat the problem, including an improved reservoir choke (L65), type 90D3-028-002, and over-voltage sensing zener diode (W85), type 02V4-718. So we decided to try a new fuse and if all seemed well advise the customer to consult his local dealer. We needn't have worried. The fuse popped off immediately, and a meter check at the mains bridge rectifier showed that two of the diodes were short-circuit. In went four new 1N4007s just to be safe. This caution was wasted because the next fuse went the same way. This time the regulator thyristor SCR1 (Y1044) was short-circuit, so in went a replacement for that. Bang went the next fuse.

By this time we were getting a bit worried. Apart from anything else, we'd only one 1.6A fuse left! So we did what we should have done in the first place and checked the resistance between the h.t. line and chassis. Not surprisingly there was a short, so we began to disconnect likely culprits. It wasn't the line output transistor, and it wasn't the crowbar thyristor. It turned out to be W77 (BY210-400), the "efficiency diode" in the power supply. Having made doubly sure that there were no further measurable shorts we tried our last fuse. Success! The set burst into life after the customary TX9 heart-stopping pause.

Another colour portable we've seen quite a bit of is the Hitachi CPT1471/CPT1473. They've all had the same fault. Indeed it's one of the few things akin to an old-

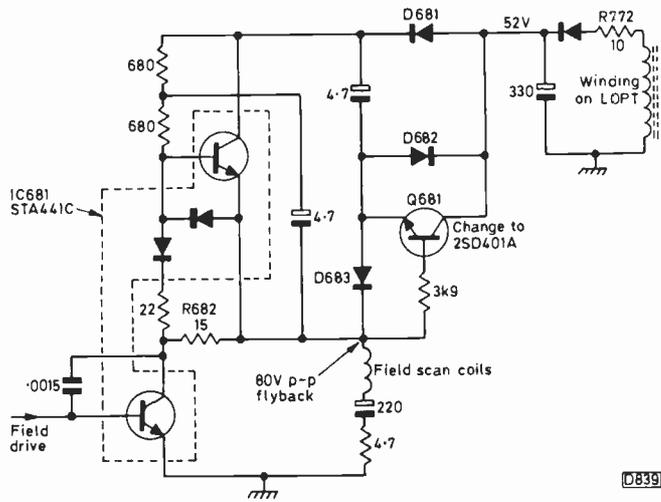


Fig. 1: Field output circuit, Hitachi CPT1471/CPT1473.

fashioned stock fault we've come across lately. The symptom is no results, sometimes intermittent but usually permanent. The first thing to do is to check Q681 (2SC1213A) in the field output stage (see Fig. 1). If this is faulty the following steps will have to be taken. Replace Q681 with the more robust 2SD401A. Also replace the switch-mode power supply chip IC901, type STR6020, part number 2366451 (it's a safety component). Hitachi say that when faulty this chip can produce excessive output, which leads to the demise of Q681. In addition, we would strongly recommend replacing R772 (10Ω), even if it seems all right. This is the surge limiter in the rectifier circuit that produces the supply for the field output stage and is also a safety component, part number 0119514. Hitachi comment that if R682 (15Ω) fails the STA441C field output chip will also have failed, but we haven't had one go yet.

The bulk of the summer portables we have to deal with are little monochrome ones of course. They come with all kinds of weird and wonderful names on the front, though their backsides tend to be much the same – not unlike their owners we sometimes think. One of the more interesting faults we've had recently concerned a GEC 2114 Junior Fineline which had normal sound but a blank, noise-free raster. Now the fact that the sound signal, which is tapped from the collector of the final i.f. transistor, was all right would tend to throw suspicion on the video circuitry. Everything here was o.k. however. As the more experienced of you will know, the intercarrier sound signal often gets through despite the i.f. strip proper being faulty. In this instance voltage checks proved that the final i.f. transistor was not conductive, due to its 120Ω emitter resistor R122 being open-circuit.

R.R.

Amstrad CTV2000

We've had another case of no sound or raster with one of these sets. The STR451 switch mode power supply chip IC502 should produce 103V at pin 2. The fault was due to C509 (0.0033μF, 1.6kV) which is connected to one end of the chopper transformer's secondary winding (T501). J.C.

ITT CD652

This set (CVC25 chassis with CMC60 remote control system) was stuck on channel one. We checked through the i.c.s in the control circuit and found that the command

went missing between IC3 and IC4. Replacing these two i.c.s failed to provide a remedy so I decided to check round IC3 with a meter. Unfortunately no pin voltages are given on the circuit, so guesswork is required. Pin 9 was found to read 16V, which was clearly wrong (see Fig. 2). The 1MΩ resistor R21 is fed from a zener diode stabilised 8.2V rail while C5 is connected to an 18V line. So either C5 was leaky or IC3 was at fault. We'd already eliminated IC3, so a check was made on C5 which was found to read 80kΩ. Replacing this restored all functions to normal.

M.S.B.

GEC C2110 Series

This 20in. solid-state set had come in for repair through the trade, the symptom being low gain. The picture had a washed out look, like me first thing in the morning... There was no observable graininess however, so I didn't suspect the tuner. Also the sound was o.k. One clue came when I removed the aerial, because instead of the expected visible and audible noise there was a blank raster and silence. Something was clearly amiss in the i.f. strip, so the next step was to check transistor voltages. This brought us to the emitter of the final i.f. transistor TR102 (BF197) where the reading was way out at more than 9V instead of 2.8V. The cause was found to be a severe leak in C113 (see Fig. 3). Replacing this restored full contrast and an excellent picture.

T.T.

Thorn 9000 Chassis

This set had flyback lines all over the picture and a distinctly tubey look about it. Increasing the contrast tended to produce slight smearing. The next thing I noticed was that the brightness control had been set well down to keep the level correct. This led to a check on the c.r.t. voltages, where the first anodes were found to be at around 1kV instead of 700V. The cause was R722 (2.2MΩ) in the first anode supply potential divider network having gone high in value. Incidentally, if you get one of these sets with the complaint of flashovers (a hell of a crack at that) and the e.h.t. is correct it's probably the tripler – the casing tends to break down. I've had similar trouble with the 8500 recently.

T.T.

GEC C1401H

For a grainy picture with noisy sound, first check whether the programme indicator light is a little dark. If so check for 33V at connector F5. If there's no voltage at this point R334 (10kΩ) is probably open-circuit.

J.C.

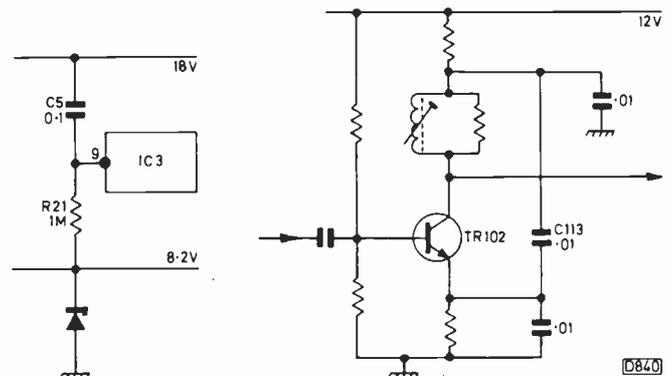


Fig. 2 (left): Channel sticking, ITT Model CD652.

Fig. 3 (right): Final i.f. stage, GEC C2110 series.

Long-distance Television

Roger Bunney

January was disappointing with regard to reception though dramatic in respect of winter fury. We have news of at least four aerial structures being damaged. During hurricane force winds Arthur Milliken (Wigan) lost his complete system (though his XG21s may be repairable). Both Cyril Willis (Ely) and Robin Crossley (Dunstable) report bent poles, but perhaps with most dramatic report comes from David Martin at Shaftesbury, Dorset. A guy on his 30ft mast snapped: this was followed by collapse of the mast when an anchoring bolt sheered, and destruction of the aerials. Fortunately the structure missed nearby buildings.

Tropospheric reception has been poor, which is hardly surprising in view of the weather. The Quadrantids meteor shower produced increased signal pings throughout Band I, with isolated bursts in Band III, January 4th being particularly active. Much of the MS activity occurred during the day, allowing positive identification of many of the signals. There's been some Sporadic E activity, the log being as follows:

8/1/84 TSS (USSR) chs. R1, 2; ORF (Austria) E2a.
9/1/84 TSS R1.
11/1/84 NRK (Norway) E2.
12/1/84 RAI (Italy) 1A, B; JRT (Yugoslavia) E3; RTVE (Spain) E2, 3, 4; RTP (Portugal) E3.
16/1/84 RTVE E2, 3, 4.
18/1/84 JRT E3, 4, RTSH (Albania) C; ORF E2a; RTVE E2; TVP (Poland) R1, 2; TSS R1.
2/2/84 RTP E3.

A glimmer of light during the winter gloom has come from Jim Maden (S. Africa) who confirms that ZTV (Zimbabwe) ch. E2 Gwelo is still in operation – he's received the station recently via SpE.

Following recent 405-line transmitter closures, Band I is relatively clear for many enthusiasts. This is especially so in E. Anglia now that Tacolneston Ch. B3 is off air.

A further sixty experimental amateur 50MHz transmitting licences have now been offered. Reports on any interference from this source on chs. E2/R1 during the coming season would be appreciated. Simple filtering should remove most problems, but those experiencing difficulties (or solving them!) are asked to write in!

News Items

France: The fourth channel Canal Plus has started to transmit an identification slide and a half hour film giving details of the service. Paris, Rhône-Alpes, Provence and the Côte d'Azur will be the first areas to receive signals. A twelve-hour daily service is expected to start on November 1st, with mainly films.

S. Africa: A TV service (BOP-TV) has been started in Bophuthatswana. Details: ch.E37 vertical, 200W e.r.p. directional, modified PM5544 test pattern.

Spain: The authorities have closed down the pirate Band III transmitter at Fuenjirola, South Spain. It had been relaying the GBC (Gibraltar) service.

Australia: The Aussat DBS is due to be launched next year. The two main spot beams will be used for the national ABS service. Lower-level broad beams will be used as a means of distributing commercial services to local stations.

Radio Amateurs: Mention has been made in previous columns of the possibility that the spectrum 50–52MHz will be allocated to ham use. No specific date for such an allocation has been officially announced and in a letter the RSGB general manager/secretary David Evans writes that "any view expressed as to a future allocation to UK amateurs at 50MHz is purely speculation".

New EBU Listings

The height of the Maasser el Chouf, Lebanon mast has been increased from 45m to 70m. Transmissions are on ch. E4 at 60kW e.r.p.

Considerable reductions in e.r.p. are given for various Syrian Band I transmitters – Abou-Kamal and Nabi-Saleh (both ch. E3) 400W instead of 400kW and Hassake (ch. E4) 95W instead of 35kW. I suspect that previously supplied information was incorrect – similar changes are given for a number of Band III transmitters.

1984 Meteor Showers

The main 1984 meteor shower dates are as follows:

Quadrantids	January 1st–6th.
Lyrids	April 19th–25th, peaking on the 21st/22nd.
May Aquarids	May 1st–10th, peaking on the 5th/6th.
Delta Aquarids	July 15th–August 15th, peaking on July 28th/29th.
Perseids	July 25th–August 20th, peaking on August 11th/12th.
Orionids	October 16th–26th, peaking on the 20th–23rd.
Taurids	October 20th–November 30th, peaking on November 1st–10th.
Leonids	November 15th–20th, peaking on the 17th–18th.
Geminids	December 7th–15th, peaking on the 13th.
Ursids	December 19th–24th, peaking on the 22nd.

Our thanks to George Spalding, Director of the BAA Meteor Section, for supplying these dates.

Ryn Muntjewerff

DX-TV reception by Ryn Muntjewerff at Beemster, Holland, has often been reported in this column. Ryn started – as so many do – after accidentally noting distant signals on his domestic TV set – in his case bull fights from Spain in the summer of 1961. After further reception he installed a roof-mounted mast and achieved some of the first DX reception at u.h.f. In the spring of 1970 he erected a 22.5m mast for tropospheric reception, leaving a wideband array (chs. E2-R4) mounted on the roof for SpE reception.

Due to the exposed location, Ryn has lost several aerial systems, mainly as a result of the U-bolt/clamp section of the diecast housing of bell-type rotors snapping. To prevent this trouble Ryn now uses an alignment bearing on top and an internal sleeved pipe inside the mast atop the rotor.

His achievements in Band I have been remarkable, with reception from Australia (ch. 0), Korea (AFKN Seoul ch.

A2), Malaysia (ch. E3) and southern Brazil (Port Allegre ch. A2) – in total some 47 countries. His farthest u.h.f. reception has been from Pajala, Sweden (SR-2 on ch. E34).

At present he has double stacked group A, C and E Fuba XC391 arrays on the mast plus horizontally and vertically mounted Wise 24-element wideband Band III arrays and a nine-element Fuba v.h.f./f.m. array. Three-element ch. E3 and ch. E4 arrays are mounted vertically and horizontally on the house along with a nine-element ch. E2-R4 BDXC system.

Satellite Location/Bearing Service

Neville Cresdee (14 Arminers Close, Clayhill, Gosport, Hants PO12 2HB) is now providing, on a commercial basis, print-outs for given locations showing all available TV carrying satellites. Here at Romsey for example some 48 craft are visible: at 4GHz, signals from some 20 craft should be resolvable using a small dish. These craft are underlined in the print-out, the more powerful satellites, such as the Gorizont series, being underlined in red. Explanatory notes, including satellite leasing information, come with the print-out. The service costs £10 and if there's sufficient interest additional information such as E.I.R.P. levels will be included.


From our Correspondents . . .

A letter from Brussels reports that both BBC TV services are now carried by the Coditel, Brutele and Radio-Public cable networks. The Coditel network provides 18 channels at 67 Belgian Francs annually. UK TV quality is "most satisfactory", though there have been occasional problems with the sound due to the need to change it from 6MHz to 5.5MHz. Reception of UK teletext has still to be tried. Our contact also reports that the TV5 ECS downlink service is in Secam, with an f.m. sound carrier at 6.5MHz. The terrestrial ECS downlink transmissions on ch. E56 in Brussels carry colour bars and the identification "CNCT Bruxelles".

Isik Yildirim (Turkey) is receiving signals from the 99°E Ekran satellite, though rather weakly, using a Fuba XC391D aerial and AKV145 junction box amplifier, a Teldis masthead amplifier and a standard v.h.f./u.h.f. Crown portable TV receiver. The latter has been fitted with an f.m. demodulator, and the results to date have been encouraging. It's now apparent that the side radiation from the Ekran satellite is very low in comparison with the high signal levels received in S. Africa from the rear.

Ronald Exeter (Bishopston), whose DX signal detector/ alarm was featured last month, uses mostly home-built equipment for DX reception. His receiving system consists of a home-built tuner and parallel vision-sound i.f. strip, a tunable intercarrier sound channel, a vision detector and a quartz-locked resync and blanking unit based on a ZNA134 chip. The output is fed to a VCR for remodulation back to u.h.f. and finally goes to a Barco PAL/Secam colour set. The detector also drives a CMOS logic board for recording on the VCR – the resync unit maintains VCR servo locking, which would otherwise be upset by "messy" DX signals, while the blanking is inserted to prevent the VCR's clamp pumping in the presence of interfering beat signals. An experimental SAWF i.f. strip is under development: results obtained so far show that a weak ch. R1 vision signal (49.75MHz) can be viewed even when a very strong ch. E2 vision signal (48.25MHz) is present.

SOUTH WEST AERIALS

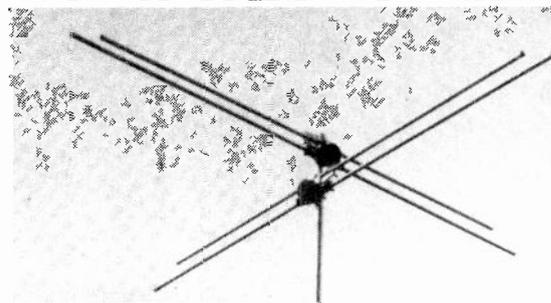

With the 1984 Sporadic E season nearly here, now is the time to consider new aerials for the Summer months. Our Band 1 wideband range covers 47–68MHz from a wideband dipole to a 4 element yagi, and omni directional/bi-directional switched options. South West quality ensures seamless hard drawn alloy tubing, all open ends plugged, bright Zinc plating and an overall high standard designed and made by DXers with the DXer in mind! Send an SAE for a leaflet describing this exclusive range. We even have TVDXing receivers both colour and mono!

South West Aerials provide an exclusive service for the DXer (TV and FM), the multiple channel installation, weak/fringe area and screened/deflector country. Our range of filters is unique, with the increasing numbers of 50–52MHz amateurs careful filter design should ensure continuance of ch.E2/R1 reception – we have suitable Band 1 notch filters ex stock!

Send now for our extensive catalogue (54p) detailing aerials, amplifiers – mast-head and indoor, filters, rotors, installation/mounting hardware, cables and accessories. Our customer consultancy service will ensure correct units for your specific application.

WB1 – SWAS wideband dipole, Band 1, 24" stub mast (incl. clamp)	£25.60
WB2 – SWAS wideband 2 element, Band 1, 47" long	£28.40
WB3 – SWAS wideband 3 element, Band 1, 72" long	£32.40
WB4 – SWAS wideband 4 element, Band 1, High gain, 113" long	£36.40
WB5 – SWAS wideband crossed dipoles, Band 1, 24" stub mast	£35.10
WB6 – SWAS wideband crossed dipoles + spaced reflector screen	£38.85

(suitable combining filter Triax 7200 for WB5, giving omni-directional coverage £9.85, or switch each dipole for bi-directional coverage) Hirschmann R0250 aerial rotor, control unit, 3 core control feeder £47.85, (alignment bearing for above £16.90).

Plustron TVR5D dual standard 5" mono VHF/UHF TVDXing receiver £91.40

The above prices include VAT, postage/packing – large items Securicor. Access Barclaycard accepted. Include SAE with ALL enquires. Delivery 10–14 working days. Comprehensive catalogue 54p.

South West Aerials, 11 Kent Road, Parkstone, Poole, Dorset BH12 2EH. Tel. 0202 738232.

TV LINE OUTPUT TRANSFORMERS

FAST RETURN OF POST SERVICE

RANK BUSH MURPHY	PHILIPS
Z146 A640 dual std mono 7.00	170 series dual std mono 7.00
Bush A792, A793	210 300 series mono 7.00
single std mono 7.00	G8 & G9 series colour 8.00
A774 single std mono 7.00	PYE 169-173-569-368 7.00
A816 solid state mono 9.00	EKCO RV305-769-725-741 8.00
DECCA	WALTHAM 125 9.00
MS1700 2001 2020 2401 mono 7.00	REWIND SERVICE - available for most continental types, i.e. Kuba, Luxor, Korting, Tyne, Berry Skantic, K80 £15.00 inc pp, VAT. Old lopt required.
MS2404 2420 2424 mono 7.00	WINDINGS
CS1730 1733 colour 8.00	RANK BUSH MURPHY
CS1830 1835 colour 8.00	T20a T22 Pry & Sec 6.00
'30' series Bradford colour 8.00	2718 series primary 6.00
80 series colour 8.00	2718 series EHT overwind 7.00
100 series colour 8.00	ULTRA THORN
FERGUSON HMV MARCONI	1690 1691 EHT overwind 7.00
1600 8.00	PYE
G.E.C.	691 to 697 EHT overwind 4.00
2047 to 2105 7.00	691 to 697 primary 5.00
2000 to 2064 dual std mono 7.00	PRICES INCLUDE
DUAL STD hybrid colour 8.00	15% VAT
SINGLE STD hybrid colour 10.00	
Indesit 20EGB 24EGB mono 9.00	
KB - ITT	
VC200 VC205 VC207 mono 7.00	
CVC5 CVC7 CVC8 CVC9 col. 8.00	
CVC20 series colour 8.00	
CVC30 CVC32 series colour 8.00	
CVC45 8.00	

Add 65 pence postage to all lopts and windings
All lopts and windings are new and guaranteed

Open Mon.-Fri. 9 to 5.30 pm
Delivery normally by return.

PAPWORTH TRANSFORMERS

80 Merton High Street,
London SW19 1BE

S.A.E. all enquiries
Barclaycard and
Access welcome



For orders placed at the post office
Trans cash 506 4856

01-540 3955



Left: The identification slide now in use by the French fourth channel Canal Plus. Centre: ATV reception by Ryn Muntjewerff (Holland) from Saintes, a distance of 871km. Power just 2W. Right: ATV reception by Robin Crossley (Dunstable) from G6HMS at Lincoln.

Mel Thurlbourne is back at Leighton Buzzard after several months' duty and DXing in the Falklands. Whilst there he received signals on chs. A2 and A3, but nothing in Band III or at u.h.f. SpE signals from Argentina have been identified: other signals await identification from photographs. Argentina had delivered ch. A7 PAL N transmission equipment for the intended Port Stanley TV service.

Robin Crossley recently moved to Dunstable, which by all accounts is a much improved location. He's using a wideband, 92-element Triax array at u.h.f., an eight-element Jaybeam ABM8 array for Band III, a four-element Band II array and crossed dipoles for Band I. Belgian f.m. radio is always present, in stereo, and an f.m. radio pirate (Skyline Radio) is heard daily on 103.6MHz at a distance of some 45 miles.

Amateur Television

Since I first started to mention ATV in this column several letters have arrived asking about reception. Transmissions are usually between 434-438 MHz, which in general terms is below the efficient operation of a group A or wideband array. For a start however it would seem best to press the normal DX-TV system into service. Experience shows that a stacked bowtie aerial system such as the Wolsey Colour King or Triax BB grid provides reasonable performance (in terms of gain and directivity) down to 435MHz. A group A Yagi could be adapted by using 13in. reflector elements – something of a compromise as regards efficiency, though this should provide reception of local ATV signals. If interest develops, a 435MHz array can be obtained – units are available in the Jaybeam and Tonna ranges. Since many ATV signals will be, at a low level, a masthead amplifier is advisable – most wideband u.h.f. amplifiers will provide amplification at 435MHz.

One problem is that the use of a standard u.h.f. array and a wideband amplifier can result in overloading, particularly with local group A broadcast signals. Suitable bandpass (or bandstop) filtering should minimise this problem – the overloading usually occurs in the tuner's r.f. amplifier rather than at the masthead. I've used both Labgear and Wolsey wideband u.h.f. amplifiers satisfactorily at 435MHz.

Tuning over 434-438MHz is usually done with a standard u.h.f. tuner, possibly modified, or a frequency converter. Many u.h.f. tuners will cover the ATV band with no modification. The ET021, ELC1043 series, ELC2060 and the ELC2000 series will generally reach down to 435MHz at minimum voltage on the tuning line. If a particular tuner won't reach 435MHz, a slight increase in

the length of the mixer and oscillator tuned lines should be all that's required by way of modification. Many Japanese and Far Eastern portable sets tune down to 435MHz, as do certain VCRs. In view of the cheapness of surplus tuners, it's reasonable to obtain one and tweak it for maximum output at 435MHz.

The use of frequency conversion is simpler but more expensive. Upconverters that accept the 435MHz band and provide an output in the ch. 37/38 spectrum are available at about £30. They generally use bipolar transistors and if confronted with high-level group A signals can cause cross-modulation. I experienced this problem – the four local group A signals were at 40mV each. Use of a simple two-pole bandpass filter for 435MHz resolved the problem. Commercial converters are housed in diecast boxes and are untuned. ATV products are available from the following firms: Wood and Douglas, Aldermaston, Nr. Reading; Microwave Modules, Aintree, Liverpool; Fortop, Warrington, Stoke on Trent.

A standard system I receiver can be used. For those living near the south coast there's the bonus of French ATV signals, though a system L receiver (or converter) will be required. Many French amateurs switch to negative-going video when in contact with UK stations however.

The emphasis is on test card/pattern transmission, though increasing enthusiasm for computer graphics is evident. Call signs, often with details of the transmission site, are given: otherwise the "locator" is shown – this is a code number that refers to a European reference grid and is sufficient to identify the approximate source of a transmission. Camera operation is also extensive.

Communication with ATV operators is usually done at 144.75MHz, the main calling frequency in the UK. If you're not licensed and don't have a 144MHz transceiver, the cheapest way of monitoring this frequency is to use a Daiwa SR9 receiver. This has continuous coverage at two metres with provision for crystal control – crystals can be obtained for 144.75MHz and for each side of the calling frequency at a spacing of 25kHz. It's not essential to hear the ATV talkback, but this is helpful in deciding whether there's any activity and if so where it's from.

I'd be pleased to assist with any queries on ATV reception (include a s.a.e. for a speedier reply). Anyone with a strong interest in the subject should join the British Amateur TV Club (BATC) which publishes a regular journal and also three guide books. For membership details send a 9 x 4in s.a.e. to Mr. B. Summers, 13 Church Street, Gainsborough, Lincs. In good openings, signals should be received at up to 500 miles. Let us know how you get on, with details of equipment, aerials etc.

Service Bureau

Requests for advice in dealing with servicing problems must be accompanied by a £1.00 postal order (made out to IPC Magazines Ltd.), the query coupon printed below and a stamped addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets nor answer queries over the telephone.

FERGUSON 3V22

A buzzing noise in the background on the sound has developed, increasing to a higher level when recorded programmes are played back. This sound is not so prominent with a commercial prerecorded tape. Tuning doesn't improve matters, except at the expense of the picture.

Remove the top and left-hand side of the machine, unsolder the two white leads from the servo (left-hand) panel, swing this out and clean both slide switches. Make sure that the switch bars *don't* go into the holes in the switches when replacing the board. If E-to-E buzz persists, try reducing the E-E level (bottom board).

TYNE 5224

The problem is line output transformer arcing – it's been rewound three times during the last six months. The last time the fault occurred R502 (820k Ω , 2W) associated with the tripler was found to be open-circuit.

It seems that either the h.t. is excessive or the line output transformer tuning is incorrect. Adjust P301 for 135V at C348 and if necessary replace C353 (5,100pF, high-ripple pulse type).

THORN 1525 CHASSIS

There's a weak picture that goes negative when the brightness control is advanced. I've tried boosting the tube's heater voltage but this hasn't helped. Can't find any references to this chassis.

The 1525 chassis is a variant on the well-known 1500. The symptom is not uncommon and is usually due to a fault in the video output stage. Suspects, in order of likelihood, are as follows: the video output transistor VT9 (a BF337 can be used); its collector load resistors R40 (2.2k Ω) and R41 (5.1k Ω); and the supply decoupler C38 (12 μ F).

PHILIPS N1700

There is continuous flutter on prerecorded and recently recorded tapes, though the machine has recently been serviced, with a new pressure roller and belt amongst other things.

If the flutter is on sound, check the adjustment of R3 (capstan servo ripple) in the U320 module, using a scope or AVO and diode probe. If the flutter is on the picture, check that the tape is not wrinkling due to dirt on the guide near the audio/sync head and for severe wear in the latter – also check the head bearing for wear or lack of oil.

Finally adjust R2 (head servo ripple) in module U219. If neither ripple can be reduced to zero, the capstan or head motor could be faulty.

THORN 8000 CHASSIS

The problem with this set is vision buzz on sound. Is there a stock fault to check?

This chassis is not the best performer as regards vision buzz. First check C140 (47pF) in the quadrature tuned circuit, then carefully tune the coil (L110) for minimum buzz. If the buzz persists, check the intercarrier sound chip's supply decoupler C133 (80 μ F) and the ceramic input filter CF101. Finally try a very small (less than half a turn) adjustment of L102 in the i.f. passband filter circuit.

SONY KV1810UB

The trouble is pincushion distortion. The two controls VR585 (amplitude) and VR586 (bias) have been adjusted for optimum results, but there's still a half-inch bow-in at each side of the raster. VR585 is at one end of its travel.

The usual cause of this fault is that the coupling capacitor C585 (4.7 μ F, 100V) between the field output stage and the pincushion correction circuit has dried up.

THORN 3000 CHASSIS

There's a good, clean monochrome picture but this becomes increasingly noisy as the colour is turned up. At the correct colour control setting the noise gives the impression of a poor level signal from the aerial, but the signal strength here is first class.

If the colour is locked, check transistor VT110 and the a.c.c. smoothing capacitor C173 (2.5 μ F) on the i.f. panel. If necessary, check the chroma amplifier transistor VT309 and the blanking diodes W316/7 on the decoder panel.

BUSH BM6514

The set is all right when first switched on, but the picture and sound deteriorate after ten-fifteen minutes, leaving a grainy picture and poor sound. Touching the aerial socket with a screwdriver restores the signals, but only for five-ten minutes.

The tuner is almost certainly faulty. Before replacing it, remove the sides and check carefully for dry-joints and solder blobs. A magnifying glass would help.

FERGUSON 3V31

Is it possible to convert the clock in this VCR to operate on a twelve-hour cycle?

You will have to gain access to the 08 display panel. Locate the display control chip IC401 (μ PD552C-079) and then link pins 40 and 41.

QUERY COUPON

Available until 18th April 1984. One coupon, plus a £1.00 (inc. VAT) postal order, must accompany EACH PROBLEM sent in accordance with the notice above.

TELEVISION APRIL 1984

COMPUTER USE

I intended to use a Sinclair ZX Spectrum with my Grundig 1645GB colour portable (GSC200 chassis). This set gives an excellent off-air picture but won't resolve the Spectrum computer's colour, giving a perfect monochrome display instead. A large-screen Philips set with manual tuning gives a very good colour display however.

Sweep tuning is sometimes a mixed blessing. If this is the trouble and the fine tuning buttons won't get a grip on the chrominance signal, some other means of getting the signal into the set will have to be found. First try an attenuator (say 6dB) in the aerial lead. Alternatively adjustment of preset RV on the vision i.f. module may achieve the desired result.

TEST CASE

256

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

A great deal of on the job training takes place in our workshop on an informal basis, depending on the workload and the suitability of the items in for repair. These days the emphasis is mainly on VCR servicing – we find that a “hands on” session is much more valuable (though more time consuming!) than a verbal or written description of symptoms, diagnosis, practical repairs and adjustments.

A suitable recent case consisted of a fairly new Sony SLC6UB VCR. Although it's a Betamax machine, the story to be told would apply equally to other types and models. The symptom reported was that the picture was rolling and juddering vertically. This was bad on library tapes, and intolerable with self-recorded tapes. E-to-E and direct r.f. picture reproduction were faultless. After a test to confirm that the symptoms were as described, the machine was given to a trainee to ponder over – with the proviso that he checks with his colleague before doing anything drastic, either mechanically or electrically.

Off he went with his scope, finding a start at the video output socket. By examining the field rate waveform here he found that the E-to-E signal was perfect whereas the off-tape signals had bad deficiencies in the field sync pulse train and during the first few lines of the picture. These lines were of low amplitude and noisy compared with the video signal during the rest of the field period. None of the playback waveform was as clean and sharp as the off-air signals, and further checking showed that during playback of the machine's own recordings the field sync signals were virtually obliterated by noise.

After some thought our trainee decided to check the r.f. envelope pattern (from the head preamplifiers) during playback, and demanded an alignment tape for the purpose. This was refused as the remains of a chewed up alignment tape (a sad story we won't recall here) had only recently been enshrined. He was told that he was on the right lines and given a known good prerecorded tape with colour bars.

Access to the relevant test points on the RF4 board is not easy on this model as the AD6 and RF4 panels have to be half-cocked over the whizzing head drum. When the waveform was displayed however a significant dent in the envelope pattern at the left of each head's trace was seen. Knowing that the field sync pulse comes at the start of each head sweep, our trainee correctly surmised that this was the cause of the symptoms. Adjusting the tracking control made little difference to the envelope shape – it reduced in amplitude without changing shape much when the control was adjusted.

Careful head, drum and tape guide cleaning made little improvement, and after consulting the adjustment manual and with the approval of his colleague our man cautiously adjusted the tape entry guides, after carefully marking their initial positions by scribing, then counting turns. The result of all this was disappointing. Screwing the guides up and down gave a “Christmas cracker” effect at the left-hand side of the signal envelope, with corresponding mistracking bars on the monitored picture, but the envelope's round shoulder shape remained. The senior technician had a good idea all along what the trouble was – have you? We'll come back to it again next month.

ANSWER TO TEST CASE 255

– Page 271 last month –

The incredible situation described last month concerned a 22in. Tandberg colour set: the parts of the display that should have been red were blue, those that should have been green were red and the blue bits (!) came out green. Merely setting it out like this, and knowing that the tube's cathodes were being driven by the correct signals, gives the clue to the whole thing – especially in view of the fact that a purity error was present.

What our quack doctor had done of course was to grossly twiddle the purity rings, to a point where the beam landing was taking place on the wrong phosphor dots. Thus the red beam was bombarding the blue dots and so on. Thorough degaussing, alternating with purity adjustment, eventually produced correct purity. Adjustment of the drives and cut-off points then put the grey scale to rights. The root of the trouble seems to have been the proximity of the TV set to some large metal mass – our customer deals in scrap metal.

Our hope is that his friend with the screwdriver doesn't graduate to VCRs. The thought of taking our turn after him with say a Sony C9 is a daunting one. I hear that he mends lorries, oil tanks and chairs as well, which certainly indicates versatility . . .

Published on approximately the 22nd of each month by IPC Magazines Limited, King's Reach Tower, Stamford Street, London SE1 9LS. Filmsetting by Trutape Setting Systems, 220-228 Northdown Road, Margate, Kent. Printed in England by The Riverside Press Ltd., Thanet Way, Whitstable, Kent. Distributed by IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. Sole Agents for Australia and New Zealand – Gordon and Gotch (A/sia) Ltd.; South Africa – Central News Agency Ltd. Subscriptions: Inland £11, overseas (surface mail) £12 per annum, payable to Quadrant Subscription Services Ltd., Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. “Television” is sold subject to the following conditions, namely that it shall not, without the written consent of the Publishers first having been given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to currency exchange fluctuations and VAT, and that it shall not be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

FREEWAY COMPONENTS

TEL:
0934 - 419147

TRANSISTORS	BC327 16	BU807 2.08	TBA120S 75	LINE OUTPUT TRANSFORMERS	Pye 691, 697 15.68	Rank Z718 12.75	MULTI-SECTION ELECTROLYTICS
AC117 30	BC337 10	MJE340 50	TBA120T 1.10	Autovox 90° 11.70	Pye 731 12.23	Decca 1730, 30, 80, 100, 6 way 9.08	Rank 823 600/300v 2.05
AC127 30	BC338 10	R2008B 1.80	TBA120U 1.10	Autovox 110° 14.48	Pye 713, 715, 717 10.50	Decca 1730, 20, Mono 4 way 7.43	Rank 823 2500+2500/30v 1.30
AC128 30	BC477 25	R2010B 1.80	TBA395 1.75	Baird 26° 90° 13.13	Pye 725 11.78	Decca 1730, 20, Mono 4 way 7.43	Rank 823 300+300/300v 2.20
AC141 26	BC479 30	R2540 2.40	TBA396 1.00	Baird 26° 110° 13.13	Pye 169, 569, 769 11.95	Decca 1730, 20, Mono 4 way 7.43	Rank 120 220/400v 1.50
AC142 27	BD124 60	TIP29C 46	TBA480 95	B&O 3100, 3300, 3400 EHT 22.88	Rank A823 13.58	Decca 1730, 20, Mono 4 way 7.43	PHG8/GEC 600/250v 1.80
AC176 28	BD131 32	TIP30C 45	TBA510 3.20	B&O 3100, 3300, 3400 13.60	Rank A640, 793 13.05	Decca 1730, 20, Mono 4 way 7.43	PHG9/GEC 600/300v 2.20
AC181 28	BD132 32	TIP31C 50	TBA520 1.30	EHT 22.50	Rank A774 12.55	Decca 1730, 20, Mono 4 way 7.43	PHG9 2200/63v 1.25
AC187 30	BD139 30	TIP32C 50	TBA530 1.45	B&O 3500, 3600, 4000, 5000, 6000 13.95	Rank 14° Port 9.50	Decca 1730, 20, Mono 4 way 7.43	PHG9 2200/63v 1.25
AC188 28	BD140 30	TIP41C 50	TBA540 1.35	Decca 30, 2230, 10.05	Rank Z20A 12.55	Decca 1730, 20, Mono 4 way 7.43	PHG11 470/250v 1.60
AD140 96	BD144 1.40	TIP42C 50	TBA550 1.50	Decca 80 10.05	Rank Z718 18° 27.00	Decca 1730, 20, Mono 4 way 7.43	Pye 691 200+300/350v 2.40
AD142 96	BD160 1.45		TBA560 1.50	Decca 100 9.38	Rank Z718 22° 27.00	Decca 1730, 20, Mono 4 way 7.43	Pye 691 1000+1000/40v80
AD143 90	BD20185	INTEGRATED CIRCUITS	TBA570 1.40	Decca 1730, 1830 12.30	Rank Z718 110° 13.95	Decca 1730, 20, Mono 4 way 7.43	Pye 731 800/250v 2.10
AD149 88	BD20260	ETT6016 1.80	TBA720A 2.60	Decca 1700 10.80	AEG 05 (1043/05) 9.95	Decca 1730, 20, Mono 4 way 7.43	GEC 2000 200+200+150+50/350v 2.50
AD161 45	BD23542	ETTR6016 1.80	TBA750 1.50	Dynatron 731, 735, 737, 741 10.50	AEG 06 (1043/06) 9.95	Decca 1730, 20, Mono 4 way 7.43	GEC 2010 1000+2000/35v95
AD162 45	BD24370	HA1155W 1.25	TBA800 1.05	Decca 80 10.05	AEG 202 (U321) 8.00	Decca 1730, 20, Mono 4 way 7.43	Thorn 3500 1000/70v 1.00
AF117 40	BD24470	HA1166 3.50	TBA800S 1.35	Decca 80 10.05	AEG 204 (U322) 9.00	Decca 1730, 20, Mono 4 way 7.43	PHG9/Pye 731 600/300v P.C.B. 3.00
AF124 50	BD37960	HA1366W 1.70	TBA810AS 1.35	Decca 80 10.05	Mitsumi Rotary (Portables) 8.00	Decca 1730, 20, Mono 4 way 7.43	
AF126 40	BD38060	LM1303P 4.95	TBA810S 1.35	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
AF127 40	BD44160	LM1327P 1.20	TBA820 1.20	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
AF139 48	BD44260	MC1303P 1.00	TBA820M 1.95	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
AL102 1.80	BD53550	MC1351P 1.35	TBA920 1.70	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
AL113 1.80	BD53650	MC1358P 1.35	TBA950 1.80	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
AU106 2.00	BD53750	NE545B 2.90	TBA990 1.60	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
AU110 2.00	BD53850	NE55545	TCA270Q 1.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
AU113 2.00	BDX32 1.60	SAA5000 3.50	TCA270S 1.30	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC107 12	BF17832	SAA5010 4.80	TCA800 2.10	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC108 12	BF17932	SAS560S 1.96	TCA940 1.80	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC109 12	BF17932	SAS570S 1.96	TDA1002 1.15	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC140 35	BF19611	SL901B 6.20	TDA1003A 1.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC141 35	BF19712	SL917/918B 4.95	TDA1004A 2.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC142 25	BF19817	SN76023D 1.99	TDA1035T 3.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC143 25	BF19915	SN76103N 2.45	TDA1107S 2.70	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC147 10	BF25828	SN76131N 1.40	TDA1112S80	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC148 10	BF25928	SN76226N 1.65	TDA2020 2.55	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC149 10	BF33732	SN76227N 1.10	TDA2030H 2.95	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC157 10	BF33832	SN76510N 1.90	TDA2190 3.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC158 10	BF45836	SN76533N 1.80	TDA2522 2.00	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC159 10	BF45936	SN76660N 1.60	TDA2523 4.30	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC161 30	BF50027	SN76666N 1.75	TDA2530 2.20	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC171 10	BU108 1.78	TA7176P 1.00	TDA2532 2.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC172 10	BU126 1.75	TA7205P 1.30	TDA254095	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC177 18	BU204 1.55	TA7217AP 1.80	TDA2541 2.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC178 18	BU204 1.55	TA7611AP 3.45	TDA2560 2.00	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC179 18	BU205 1.40	TAA350A 1.90	TDA2571A 2.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC182 10	BU206 1.65	TAA55025	TDA2581 1.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC187 20	BU208A 1.80	TAA621AX1 3.50	TDA2590/91 2.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC212 10	(Pack of 10) 12.00	TBA120A95	TDA2593 2.50	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC237 10	BU326A 1.40	TBA120AS75	TDA2600 5.80	Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC238 10	BU407D 2.49			Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	
BC303 30	BU806D 2.00			Decca 80 10.05		Decca 1730, 20, Mono 4 way 7.43	

SPECIAL PROMOTIONAL OFFER

BUY 3 OR MORE

A56-120X ONE YEAR GUARANTEE (OPTIONAL EXTENSION UP TO THREE YEARS)

ONLY £23.80 + VAT

OFFER ENDS 31st MARCH

Callers only. To Luton or any of the stockists - Please phone first. - Send for a fully comprehensive price list and a wall chart of approx. 1800 colour tube types (including Base Connection Diagrams) that can be reproduced by us.

TV TUBE POLISHING AT Your Own Premises
with our DIY Polishing Kit

The Kit includes:
Everything you need to polish approx. 25° tubes to a high standard. Detailed instructions on how to do the polishing. All you require is an Electric Drill.
Practical instructions available to buyers of kit, please enquire for details.

Kit Price £45 inc P&P and VAT.
Available from Luton only.

*Depends on depth and area to be polished.

WELL VIEW 114-134 Midland Rd, Luton, Beds.
Open Mon-Fri 9am-6pm, Sat 9am-5pm. Tel. 0582-410787

Your Local Tube Stockist:
Well View, Southampton. Tel. 0703 331837.
Retach Ltd., Northwood, Middx. Tel. 09274-27019
West One Distributors Ltd., Chesham, Buckinghamshire. Tel. 0494-778197
Rushden Rentals Ltd., Rushden, Northants. Tel. 0933-314901
Daventry Rentals, Daventry, Northants. Tel. 03272 77436

Please note that we have no connections whatsoever with any other business having similar name to ours.

INTRODUCING!

Midlands Newest Wholesalers

★ ★ ★

ALL MAKES IN STOCK AT COMPETITIVE PRICES

Philips, Pye, G.E.C., Decca, ITT, National, Hitachi, Mitsubishi, etc.

★ ★ ★

TRY US NOW AND BE SURPRISED!

Ring us NOW on:
021 557 2233

or visit us at:
94 Soho Hill, Hockley, Birmingham B19 1AD.

N J ELECTRONICS

82 - 84 STORFORTH LANE TRADING ESTATE

HASLAND
CHESTERFIELD

S41 OSN

TEL. (0246) 209079

INTEGRATED CIRCUITS

BTT 822	1.90	TA 7609P	4.00
CA 3089	1.20	TA 7611AP	2.90
ETTR 6016	1.95	TA 75902P	2.03
ETTR 6016	1.95	TAA 320A	1.30
MC 1307P	1.70	TAA 470	2.30
MC 1310P	1.20	TAA 550	0.39
MC 1327P	1.10	TAA 691	1.95
MC 1330P	1.50	TAA 700	1.65
MC 1349P	1.10	TBA 120A	0.75
MC 1351P	1.20	TBA 120AS	0.75
MC 1352P	1.50	TBA 120B	0.78
MC 1358P	1.20	TBA 120C	0.75
ML 236E	3.00	TBA 120SA	0.75
ML 237B	1.80	TBA 120U	0.75
SAA 1021	3.80	TBA 231	1.65
SAA 1024	2.40	TBA 396	1.70
SAA 1025	4.40	TBA 395	1.70
SAA 1124	2.40	TBA 480	0.99
SAA 1130	4.30	TBA 510	1.20
SAA 5040	7.50	TBA 520	1.50
SAS 560	1.80	TBA 530	1.45
SAS 570	1.80	TBA 540	1.70
SAS 660	2.30	TBA 550	1.80
SAS 670	2.30	TBA 560C	1.90
SL 901B	4.50	TBA 570	1.10
SL 917B	6.20	TBA 750	1.50
SN 16862AN	2.50	TBA 800	1.10
SN 16964AN	2.50	TBA 810S	0.90
SN 29848	2.25	TBA 820	1.20
SN 57108AN	1.95	TBA 890	3.50
SN 76001AN	1.60	TBA 920	2.00
SN 76003	2.20	TBA 950	2.65
SN 76013N	2.50	TBA 990	1.60
SN 76013ND	2.50	TBA 1440	2.70
SN 76023N	2.20	TBA 1441	2.70
SN 76131N	1.35	TCA 270S	1.90
SN 76226DN	1.60	TCA 270SQ	1.90
SN 76227N	1.20	TCA 640	2.60
SN 76532	2.00	TCA 650	2.40
SN 76550	0.29	TCA 660	2.80
SN 76546	1.80	TCA 740	2.90
SN 76660	0.90	TCA 800	2.00
SN 76666N	1.10	TCA 830S	1.60
SN 76707	1.70	TCA 940	1.80
TA 7061AP	3.60	TCA 4500A	2.00
TA 7063AP	3.50	TDA 1003	2.00
TA 7066P	3.90	TDA 1004A	2.20
TA 7072P	2.90	TDA 1044	2.50
TA 7073AP	3.20	TDA 1170	2.80
TA 7074P	3.30	TDA 1180	2.10
TA 7076P	3.30	TDA 1190	2.00
TA 7089P	2.40	TDA 1327	1.70
TA 7093P	2.90	TDA 1412	1.00
TA 7108P	2.44	TDA 2002	1.90
TA 7117P	3.20	TDA 2010	1.80
TA 7120P	1.61	TDA 2522	2.40
TA 7129AP	3.20	TDA 2523	2.20
TA 7130P	1.38	TDA 2530	2.20
TA 7137P	2.00	TDA 2532	2.70
TA 7139P	2.75	TDA 2540	2.20
TA 7146P	2.00	TDA 1365	5.75
TA 7157P	3.20	TDA 2541	2.30
TA 7171P	3.20	TDA 2560	2.05
TA 7172P	3.30	TDA 2571	2.10
TA 7176AP	3.00	TDA 2581	1.30
TA 7193P	5.20	TDA 2582	1.80
TA 7202P	3.30	TDA 2593	2.70
TA 7203P	3.30	TDA 2600	5.00
TA 7204P	2.16	TDA 2611A	1.15
TA 7205P	1.40	TDA 2640	1.80
TA 7208P	2.70	TDA 2653	2.10
TA 7210P	5.60	TDA 2680	2.10
TA 7222P	1.70	TDA 2690	2.20
TA 7223P	3.50	TDA 3560	5.10
TA 7227P	5.10	TDA 3561	6.50
TA 7310P	1.70	TDA 3950	2.40
TA 7313P	2.80	TDA 4600	2.10

DIODES

UPC 41C	3.50
UPC 393C	2.90
UPC 554C	1.34
UPC 555H	0.80
UPC 556H3	1.70
UPC 557H	0.92
UPC 566H3	3.50
UPC 574J	0.55
UPC 575C2	1.49
UPC 577H	3.50
UPC 585C	1.49
UPC 741G	0.95
UPC 1009H	2.41
UPC 1017G	2.50
UPC 1018C	1.19
UPC 1023H	0.63
UPC 1024H	0.63
UPC 1025H	1.70
UPC 1026C	1.60
UPC 1028H	2.40
UPC 1031H2	2.40
UPC 1032H	0.98
UPC 1035C	2.50
UPC 1037H	1.62
UPC 1041H	1.28
UPC 1042C	2.60
UPC 1043C	2.60
UPC 1156H	2.40
UPC 1158H	0.78
UPC 1161C3	1.58
UPC 1163H	0.98
UPC 1167C2	1.58
UPC 1168C	2.75
UPC 1170C	1.75
UPC 1171C	1.62
UPC 1173C	2.14
UPC 1176C	2.43
UPC 1177H	2.60
UPC 1178C	2.14
UPC 1180C	3.00
UPC 1181H3	1.62
UPC 1182H	2.70
UPC 1183H	2.30
UPC 1185H2	3.50
UPC 1186H	0.98
UPC 1187V	1.70
UPC 1188H	3.60
UPC 1190C	2.00
UPC 1191V	1.70
UPC 1197C	1.70
UPC 1198H	1.41
UPC 1200V	1.97
UPC 1204C	1.63
UPC 1208C	2.00
UPC 1211C	4.00
UPC 1212C	1.34
UPC 1213C	1.53
UPC 1215V	2.70
UPC 1216V	1.99
UPC 1217G	3.59
UPC 1218H	3.00
UPC 1222	2.00
UPC 1223	3.70
UPC 1225	3.00
UPC 1226	2.49
UPC 1227	2.00
UPC 1228H	0.90
UPC 1230H	3.60
UPC 1238V	1.90
UPC 1245	2.20
UPC 1250	2.40
UPC 1350C	4.50
UPC 1353C	2.80
UPC 1356C2	3.00
UPC 1358H	3.00
UPC 1360C	3.50
UPC 1361C	3.70
UPC 1363C	3.50
UPC 1365C	5.00

ZENERS

400MW	
2V4 to 75V	0.10
1.3W	
2V7 to 91V	0.18
100V to 200V	0.19
15 WATT	
BZV15C12R	1.18
BZV15C24R	1.18
BZV15C30R	1.18

BRIDGE RECT.

B40	0.80
BY164	0.50
BY179	0.70
W005	0.25

TRANSISTORS

AC127	0.30
AC128	0.30
AC153K	0.36
AC176	0.30
AC186	0.30
AC187	0.30
AC188	0.30
AD149	0.88
AD161	0.45
AD162	0.45
AF139	0.48
AF239	0.60
AU113	2.60
BC107	0.10

UPC 1366C	3.00
UPC 1367C	3.00
UPC 1368H	4.00
UPC 1370C2	4.00
UPC 1373H	1.11
UPC 1377C	4.50
UPC 1378H	4.00
UPC 1382C	1.97
UPC 1384C	5.70
UPC 1447W	0.98
UPC 1470H	0.90
UPC 2002V	2.80

DIODES

BA148	0.18
BA159	0.10
BB103	0.20
BB105B	0.20
BY127	0.11
BY133	0.11
BY176	1.35
BY184	0.40
BY187	0.69
BY190	0.60
BY210-800	0.29
BY223	0.95
BY226	0.27
BY227	0.31
BY295	0.25
BY296	0.25
BY298	0.25
BY299	0.25
BYX10	0.21
BYX36-600	0.50
BYX71-350	0.50
BYX71-600	0.99
BYX55-600	0.33
BR100	0.35
DA47	0.10
DA90	0.08
DA91	0.08
SKESF	1.40
IN60	0.08
IN4001	0.05
IN4002	0.05
IN4003	0.05
IN4004	0.06
IN4005	0.07
IN4006	0.07
IN4007	0.07
IN4148	0.03
IN5402	0.13
IN5404	0.15
IN5406	0.17
IN5408	0.18
Y969	0.87

ZENERS

400MW	
2V4 to 75V	0.10
1.3W	
2V7 to 91V	0.18
100V to 200V	0.19
15 WATT	
BZV15C12R	1.18
BZV15C24R	1.18
BZV15C30R	1.18

BRIDGE RECT.

B40	0.80
BY164	0.50
BY179	0.70
W005	0.25

TRANSISTORS

AC127	0.30
AC128	0.30
AC153K	0.36
AC176	0.30
AC186	0.30
AC187	0.30
AC188	0.30
AD149	0.88
AD161	0.45
AD162	0.45
AF139	0.48
AF239	0.60
AU113	2.60
BC107	0.10

BC108	0.11
BC109	0.10
BC116	0.13
BC140	0.30
BC141	0.30
BC142	0.22
BC143	0.27
BC147	0.09
BC148	0.10
BC149	0.09
BC154	0.11
BC157	0.10
BC158	0.11
BC159	0.11
BC170	0.13
BC171	0.10
BC172	0.13
BC173	0.12
BC174	0.12
BC182L	0.09
BC183L	0.09
BC184L	0.09
BC207	0.09
BC212L	0.09
BC213L	0.11
BC237	0.10
BC238	0.10
BC250	0.11
BC251	0.11
BC252	0.10
BC253	0.11
BC301	0.31
BC302	0.31
BC303	0.33
BC307	0.13
BC308	0.13
BC327	0.11
BC328	0.11
BC337	0.11
BC338	0.13
BC350	0.12
BC365	0.30
BC413	0.11
BC460	0.48
BC461	0.52
BC462	0.53
BC463	0.53
BC527	0.13
BC528	0.13
BC546	0.10
BC547	0.09
BC548	0.09
BC557	0.10
BC558	0.10
BD131	0.30
BD132	0.36
BD135	0.30
BD136	0.30
BD139	0.33
BD140	0.60
BD150A	0.70
BD207	0.90
BD221	0.40
BD228	0.35
BD233	0.53
BD234	0.38
BD238	0.38
BD239	0.42
BD253B	0.65
BD416	0.42
BD534	0.33
BD595	0.55
BD596	0.55
BD681	0.58
BD807	0.50
BDX32	1.70
BF127	0.30
BF137	0.30
BF180	0.29
BF181	0.27
BF182	0.28
BF185	0.32
BF194	0.10
BF195	0.11
BF196	0.13
BF197	0.13
BF198	0.16
BF199	0.18
BF200	0.34
BF240	0.16
BF245	0.30
BF256L	0.40
BF258	0.27
BF259	0.32
BF264	0.40
BF273	0.13

BF274	0.11
BF337	0.32
BF338	0.32
BF355	0.56
BF458	0.48
BF459	0.51
BFR79	0.26
BFY50	0.24
BFY51	0.23
BFY52	0.23
BU105	1.40
BU108	1.60
BU124	0.98
BU126	1.60
BU137	1.40
BU204	1.40
BU205	1.40
BU208	1.55
BU208A	1.90
BU208D	2.30
BU326	1.80
BU407	1.40
BU426V	1.70
BU526	1.62
BUW81A	2.55
E1222	0.35
FT3065	0.65
MJE340	0.50
MJE520	0.45
R2008B	1.70
R2009	1.90
R2010B	1.90
R2028	1.90
R2029	1.90
R2030	1.90
R2265	1.90
R2305	

N. J. ELECTRONICS		FOCUS UNITS		SMOOTHING CAPACITORS		RESISTORS (CARBON)		EHT TRAYS					
SERVISOL		PLUGS-SOCKETS		RRI T20 1.80 Thorn 8500 1.90 Focus Rods 1.10					Decca 1830 5.90 Decca 2230 6.25 Decca 80 6.25 Decca 100 6.25 GEC 1028 6.25 GEC 2040 6.25 GEC 2110 6.25 GEC 2200 6.25 Grundig 5011 6.25 ITT CVC 5/8 6.25 ITT CVC 20 6.25 ITT CVC 45 6.25 Korting 90° 6.95 Philips 520 6.50 Philips 550 6.50 Philips G9 6.25 Philips 570 6.50 Philips KT3 8.95 PYE 691/697 6.30 PYE 713 5 lead 6.50 PYE 713 4 lead 7.60 PYE 725/731 6.25 RRI 823 7.75 RRI T20 6.50 Tandberg TV2-2 6.50 Thorn 1500 3 stick 4.95 Thorn 1500 5 stick 5.50 Thorn 3000/3500 7.70 Thorn 8000 4.95 Thorn 8500 6.80 Thorn 9000 7.80 Telpro 561 7.00 Seimens Universal 5.50 TV11 0.65 TV13 0.65 TV18 0.70				
Super Servisol 0.88 Freezer 1.04 Aero Kleen 0.86 Silicone Grease (aerosol) 1.10 Silicone Grease (tubes) 1.70 Foam Cleaner 0.92 Plastic Seal 0.96 Heatsink Compound 1.20 Solder Mop 0.75 Video 40 0.93 Super 40 1.60 Add 30p per can additional post	Phono Plug Plastic (red or black) 0.12 Phono Plug Metal 0.22 Phono Line Skt 0.18 Phono Chassis Skt 0.19 DC Plug 2.1mm 0.19 DC Plug 2.5mm 0.19 DC Chassis Skt 2.1mm & 2.5mm 0.19 Coax Plug 0.15 Coax Coupler 0.15 1/2" Mono Jack Plug 0.15 1/2" Stereo Jack Plug 0.27 3.5 Mono Jack Plug 0.12 3.5 St Jack Plug 0.25 1/2" Jack Line Coupler Mono 0.22 1/2" Jack Line Coupler Stereo 0.25 1/2" Mono Jack Chassis Socket 0.24 1/2" Stereo Jack Chassis Socket 0.24 3.5mm Socket 0.10 2.5mm Socket 0.10	CAPACITORS MIN PLATE CERAMIC 63V 1.8PF to 12,000PF 0.05 10,000PF to 12,000PF 0.06 POLYSTYRENE 160V 10PF to 820PF 0.07 10,000PF to 15,000PF 0.09 TANTALUM BEAD .1MF 35V 0.16 .15MF 35V 0.16 .22MF 35V 0.16 .33MF 35V 0.16 .47MF 35V 0.16 .68MF 35V 0.16 1MF 35V 0.16 1.5MF 35V 0.16 2.2MF 35V 0.17 3.3MF 35V 0.18 4.7MF 35V 0.18 6.8MF 35V 0.20 10MF 35V 0.20 22MF 16V 0.24 MIXED DIELECTRIC .01 1000V 0.24 .01 1500V 0.25 .02 1000V 0.28 .03 1000V 0.28 .1 1000V 0.30 .1 1250V 0.46 .1 2000V 0.75 .22 1000V 0.48 .22 1250V 0.60 .47 1000V 0.79 8KV OISCS 180PF, 210PF, 270PF, 330PF, 500PF 0.30 POLYESTER 250V .01MF 0.06 .02MF 0.06 .03MF 0.06 .04MF 0.06 .068MF 0.06 .1MF 0.07 .22MF 0.08 .33MF 0.08 .47MF 0.13 .68MF 0.13 1MF 0.16 MYLAR FILM 100V .001MF 0.06 .002MF 0.06 .0047MF 0.07 .01MF 0.07 .022MF 0.07 .033MF 0.08 .047MF 0.08 .068MF 0.09 .1MF 0.09 .22MF 0.13 .47MF 0.22 DISC CERAMIC 50V .01MF, .022MF, .047MF, .1MF 0.04 S CORRECTION .91MF G11 0.55 ELECTROLYTIC 25V 10MF 0.08 22MF 0.08 47MF 0.09 100MF 0.09 220MF 0.15 470MF 0.22 1000MF 0.33 2200MF 0.50 ELECTROLYTIC 40V 470MF 0.30 2200MF 0.70 ELECTROLYTIC 63V 1MF 0.08 2.2MF 0.08 4.7MF 0.08 10MF 0.08 22MF 0.11 47MF 0.12 100MF 0.19 220MF 0.30 470MF 0.42 1000MF 0.65 ELECTROLYTIC 100V 0.47MF 0.10 1MF 0.10 2.2MF 0.10 4.7MF 0.10 10MF 0.12 22MF 0.16 47MF 0.17 100MF 0.26 220MF 0.45 330MF 0.55 ELECTROLYTIC 250V 0.47MF 0.11 1MF 0.14 10MF 0.28 22MF 0.31 ELECTROLYTIC 450V 10MF 0.50	Decca 200/200/400 350V 2.70 Decca 400/400 350V 2.90 Decca 400/800 350V/250V 2.90 Philips 600 300V 2.50 Philips 2200 63V 1.55 Philips 470 250V 2.00 Philips (G9) 600 300V 2.80 PYE 200/200/100/32 2.85 PYE 600 300V 2.80 RRI 2500/2500 30V 1.20 RRI 220 400V 2.90 Thorn 150/160/100 300V 1.90 Thorn 4700 25V 0.85 Thorn 1000 70V 0.70 Thorn 200/100/100 350V 2.85 Thorn 175/100/100 400V 2.40 Thorn 400 400V 2.50	1/2 Watt IRO to 10M (10 Pack) 0.18 1 Watt 2R2 to 10M (10 Pack) 0.39 2 Watt 4R7 to 10M (10 Pack) 0.60 RESISTORS (WIREWOUND) 2 1/2W DR22 to 10R 0.15 5W OR47 to 6K8 0.15 7W OR47 to 12K 0.15 11W DR1 to 18K 0.18 17W IRO to 6K8 0.24 PRESETS Horizontal and Vertical Standard and sub mid sizes 100R to 4M7 0.12 MAINS DROPPERS Decca 20 mono 1.35 Decca 30 3R9 0.60 Philips G8 2R2 + 68R 0.84 Philips G8 47R 0.50 Philips 210 (no link) 1.10 Philips 210 (with link) 0.95 PYE 725 3R3 1.79 UMc B69 8B L + 56R 1.40 PYE 725 + 56R + 3R 1.55 RRI 823 56R - 68R 0.85 Thorn 1500 1.55 Thorn 1600 1.45 Thorn 3500 0.97 Thorn 8000 1.20 Thorn 8500 0.97 Thorn 8800 0.97 Thorn 9800 0.90 GEC 2110 0.85 CONVERGENCE CONTROLS 5R 7R 10R 12R 15R 20R 50R 100R 200R 500R 0.38 G8 Metric 10R 15R 20R 0.50 Thorn 50R 200R 0.50 FUSES 20mm A/S (10 Pack) 100mA, 160mA, 250mA 1.50 315mA 1.20 500mA, 630mA, 800mA 0.95 1A, 1.25A, 1.6A, 2A 0.95 2.5A, 3.15A, 4A, 6.3A 0.95 20mm Q/B (10 Pack) 160mA, 250mA, 315mA, 500mA, 630mA, 800mA, 1A, 1.6A, 2A, 3.15A 0.45 1 1/2" A/S (10 Pack) 250mA, 500mA, 630mA 1.50 800mA, 1A, 1.25A, 2A 1.50 2.5A, 3A, 5A 2.30 1 1/2" Q/B (10 Pack) 250mA, 1A, 1.5A 0.60 2A, 3A, 5A 0.60 Mains Fuse (10 Pack) 2A, 3A, 5A, 13A 0.90 LOUDSPEAKERS 8 x 5 16 ohm 2.98 6 x 4 16 ohm 2.60 6 x 4 25 ohm 4.30 8 x 3 70 ohm 3.40 5 x 3 50 ohm 3.00 7 x 3 1/2 16 ohm 3.00 5 1/2 x 3 80 ohm 2.90 Thorn 1590 large 4.00 TUNERS 1043/05 7.95 1043/06 7.95 U321 7.25 U322 7.25 G8 11.75	Decca 1830 5.90 Decca 2230 6.25 Decca 80 6.25 Decca 100 6.25 GEC 1028 6.25 GEC 2040 6.25 GEC 2110 6.25 GEC 2200 6.25 Grundig 5011 6.25 ITT CVC 5/8 6.25 ITT CVC 20 6.25 ITT CVC 45 6.25 Korting 90° 6.95 Philips 520 6.50 Philips 550 6.50 Philips G9 6.25 Philips 570 6.50 Philips KT3 8.95 PYE 691/697 6.30 PYE 713 5 lead 6.50 PYE 713 4 lead 7.60 PYE 725/731 6.25 RRI 823 7.75 RRI T20 6.50 Tandberg TV2-2 6.50 Thorn 1500 3 stick 4.95 Thorn 1500 5 stick 5.50 Thorn 3000/3500 7.70 Thorn 8000 4.95 Thorn 8500 6.80 Thorn 9000 7.80 Telpro 561 7.00 Seimens Universal 5.50 TV11 0.65 TV13 0.65 TV18 0.70								
SOLDER	D.I.N PLUGS 2 Pin 0.10 3 Pin 0.10 4 Pin 0.14 5 Pin 180° 0.19 5 Pin 240° 0.19 5 Pin 360° 0.19 6 Pin 0.23 7 Pin 0.23	D.I.N. LINE SOCKETS 2 Pin 0.11 3 Pin 0.22 5 Pin 180° 0.22 5 Pin 240° 0.22 6 Pin 0.23 7 Pin 0.23	D.I.N. CHASSIS SOCKETS 2 Pin Switched 0.10 2 Pin Unswitched 0.12 3 Pin 180° 0.22 5 Pin 180° 0.22 5 Pin 240° 0.23 6 Pin 0.23 7 Pin 0.25	O.I.N. PCB SOCKETS 2 Pin Unswitched 0.25 5 Pin 180° 0.24 FM Plug 0.20 FM Socket 0.19 AM Plug 0.20 AM Socket 0.19	BATTERY HOLDERS HP7 2 per side, end to end 0.28 HP7 2 per side, side by side 0.28 HP11 4 end to end 0.37 HP11 2 rows single sided 0.37 PP9 Press Stud 0.10 PP3 Press Stud 0.10	CRT-VALVE BASES T20 CRT Base 1.35 Toshiba CRT Base 1.40 B9A EHT Base 0.55 B7G Ceramic 0.55 B9A Ceramic 0.55 B10B Ceramic 0.55	TRIM TOOLS Twin Bladed Bronze-Phosphor 0.25 Long Plastic, Hex at one end 0.11	MIXED PACKS Mixed Dust Cores 0.70 Transistor Mount Kit 0.70 10 yds Assorted Wire 0.50 100 Capacitors 1.00 300 Carbon Res 1.00 100 2 1/2 Watt Wirebonds 2.00	REGUN C.R.T.s (2 year warranty) A44-271X 32.00 A47-342X 32.00 A47-343X 32.00 A49-192X 32.00 A51-110X 32.00 A56-120X 32.00 A56-140X 33.00 A56-500X 45.00 A66-120X 37.00 A66-140X 38.00 A67-120X 38.00 A50-120WR 14.00 A61-120WR 15.00 Carriage £8.00 per tube + VAT	AERIAL ISOLATORS 40mm x 40mm with 500mm Lead 0.60 67mm x 65mm with 430mm Lead 0.60 Philips Plastic Moulded Type for KT3 Chassis 0.80	VIDEO HEADS 3HSS Ferg-JVC-Akai 34.00 4HSS Nat Pan 34.00 PS3B Sony-NEC-Toshiba 39.00	BOOKS A-Z Equivalent Book (Two Parts) 7.50 NB: Zero VAT on Books	LINE OUTPUT TRANSFORMERS Autovox 90° 9.75 Autovox 110° 9.75 Decca 1700 Mono 9.80 Decca 1830 9.80 Decca 2230 8.30 GEC 2110 9.50 GEC 20AX (diode split) 12.00 Grundig 1500 mono 13.70 Grundig 5010 11.50 ITT CVC5/8 10.25 ITT CVC20 10.75 ITT CVC30 8.75 ITT CVC45 9.75 Indesit mono 10.75 Korting 90° 10.75 Korting 110° 12.50 Philips 210 9.90 Philips G8 8.90 Philips G9 8.50 Philips G11 12.95 Philips K30 14.95 Philips KT3 7.95 Philips 570 9.50 PYE 691 P.C. 13.00 PYE 725 8.95 PYE 731 8.95 PYE 169 10.75 RRI 640/793 11.75 RRI 774 12.90 RRI 823 11.90 PCL82 12.90 PCL84 12.50 PCL85 12.50 PCL86 12.50 PFL200 7.00 PL36 7.00 PL504 10.50 PL508 10.00 PL509 8.75 PY800 10.90 PY500A 10.90

PLEASE ADD 65 PENCE POST/
PACKING TO YOUR ORDER TOTAL
AND THEN 15% VAT. GOODS ARE
DESPATCHED BY RETURN AND
SHOULD BE RECEIVED WITHIN 4
WORKING DAYS.

VIDEO CASSETTE RECORDER SERVICING COURSE

3 WEEKS

APRIL 24th to MAY 12th
(2 p.m.–6.30 p.m. Monday–Friday)

Intensive course intended for qualified TV Service Engineers who have a sound knowledge of Colour TV principles — some previous background of VCR principles would be advantageous.

Training includes theoretical concepts together with practical project and fault diagnosis work on state of the art VCR's using electronic test and mechanical alignment equipment.

On successful completion of the course a College Diploma will be awarded.

(Also courses of between 6 months and 15 months in Electronic Equipment Servicing — TV/Video, Computers, Microprocessors and Robotics leading to Business and Technician Education Council (BTEC) Certificate and/or Higher Certificate awards.

Further details from:

LONDON ELECTRONICS COLLEGE (Dept T3/4)
20 Penywern Road,
Earls Court, London SW5 9SU
Tel: 01-373 8721

TV LINE OUTPUT TRANSFORMERS

ADD 15% VAT to ALL prices.

Delivery by return of post

If the Transformer you require is not listed please phone.

RANK BUSH MURPHY

Z146 A640 dual std mono	8.51
Bush A792, A793 single std mono	8.51
A774 single std mono	8.50
A816 solid state mono	9.00
Z712 T16a T16b mono portable	9.00
A823 A823b A823av colour	10.00
Z179 Z722 series colour	10.00
T20a T22 series colour	10.00
Z718	P.O.A.

DECCA

MS1700 2001 2020 2401 mono	8.00
MS2404 2420 2424 mono	8.00
1210 1211 1511 portable	11.50
GYPY portable	11.50
CS1730 1733 colour	8.00
CS1830 1835 colour	8.00
'30' series BRADFORD colour	8.00
70, 80, 100 series	8.00
110, 130 series	8.00

WINDING

T20A T22 Z179 T26	5.51
-------------------	------

FERGUSON HMV MARCONI

1590 1591 1592 1593 mono	8.00
1612 1613 1712 mono	8.00
1690 1691 mono	8.50
1600 1615 series mono	9.74
3000 3500 EHT or SCAN	P.O.A.
8000 8500 8800	11.70
9000 9200 9300	11.52
9500 9600 9650	9.56
9800 TX9 TX10	P.O.A.

PHILIPS

210 300 series mono	8.00
320 series solid state mono	8.50
G8 series colour	8.00
G9 series colour	8.50
G11 series colour	14.98
KT2 Lopt	9.00
KT3 Lopt	10.60

KB-ITT

VC200 VC205 VC207 mono	8.00
VC300 VC301 VC302 portable	8.00
CVC1 CVC2 colour	9.00
CVC5 CVC7 CVC8 CVC9 colour	9.00
CVC20 series colour	9.00
CVC30 CVC32 series colour	8.00
CVC40 series	14.56

L.O.P.T TESTER

Total Price Including VAT.	£16.79
----------------------------	--------

G.E.C.

2047 to 2105 3112 to 3135	8.00
"GAIETY" FINELINE	8.00
2114 portable mono 1201H	8.00
3133 3135 M1501H portable mono	8.00
DUAL STD hybrid colour	11.00
SINGLE STD hybrid colour	10.00
SINGLE STD solid state 90°	8.50

**INDESIT, GRUNDIG, TANDBURG,
TELEFUNKEN, FIDELITY,
KORTING, TYNE, B+O.**
Price on application.

**HAMOND COMPONENTS
(Midland) Ltd.**
416, Moseley Road,
Birmingham B12 9AX.
Phone 021-440-6144

**Tidman Mail Order Ltd.,
236 Sandycombe Road,
Richmond, Surrey.**

Approx. 1 mile from Kew Bridge.

Phone: 01-948 3702

Mon-Fri 9 am to 12.30 pm.

1.30 to 4.30 pm.

Sat 10 am to 12 pm.

TVs FOR EXPORT

BUSH, PHILIPS, DECCA AND PYE
All with 6 button VHF/UHF Tuners
suitable for countries using PAL system

TELE SPARES LTD.

Unit 113, Elm Road,

Western Industrial Estate,

Dublin 12, Ireland.

Telephone: Dublin 521211/521756

TUNERS + TUNERS

- ★ If you repair sets regularly — phone us today and we will dispatch immediately — no need to send cash 'up front'.
- ★ All tuners dispatched by first class post for receipt by you the next day.
- ★ All popular tuners/tuner repairs supplied 'off the shelf'.
- ★ Unusual types repaired same day as received (subject to spares availability).

TELEPART

13 Worcester Street,
Wolverhampton, WV2 4CJ.
Phone: (0902) 773122.

**ALL SETS HAVE BEEN
ENGINEERED
AND ARE IN PERFECT
WORKING ORDER**

*PRICES AVAILABLE ON
THESE SETS NOW!!!*

**PYE CHELSEA's
PYE 721s, 731s, 725s
PHILIPS 520s, 550s and G11s
BUSH T20, T22, T24s**

(Remote Control)

**THORN 8000 & 8800s
THORN 9000, 9200, 9600**

(Remote Control)

**ITT CVC 32/33/45
HITACHI & NAT/PANASONIC
Minimum 5 Sets**

Big reductions for export orders over 100 sets

**COLOUR TELEVISION
& MUSIC CENTRE**

35 Stafford Road, Weston Super Mare

Opening hours: 9-6 Mon-Sat, 9-1 Sundays

(W-S-M 413537)

Avon

(W-S-M 413537)

(Note new address)

(15 minutes past Bristol Southward on M5)

HUSSAIN CENTRAL TV

No. 1 distributor in U.K.

Special sale for this month only

G8 520 26" £6. 520 22" £9. G8 550 26" £10. 550 22" £20. G9 £18. Thorn 26" £5. Thorn 22" £12. Thorn 8500 £20. GEC Hybrid £4. GEC Solid State £20. Pye Hybrid £4. Pye Solid State £20. Chelsea £20. ITT Hybrid £15. Decca Hybrid £15. Also latest stock G11, ITT, Decca 80 and 100 series.


*Guaranteed all T.V.'s are untouched off the floor.
Buy now while stocks last.*

**Ring us today 021-622 1023 or 021-622 1517
48/52 Pershore St., Birmingham City Centre.**

UNIVERSAL PROGRAMME SELECTOR FOR VARICAP TUNING

UK Regd. Design No. 1006611

6 way interlocked d.p. switch 100 K tuning potentiometers
Top quality through hole plated pcb
Dimensions: 5" by 2½" by 1"
Ideal for replacement when original parts are obsolete or unobtainable
Template guide supplied for drilling of your own fascia design
Range of pre-cut and drilled fascia/mounting kits for selected TV chassis enabling our unit to be fitted without further cutting drilling or modification
All orders despatched same day

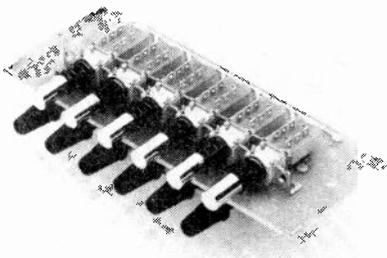

DIRECT REPLACEMENT FASCIA/MOUNTING KITS

- Type 30-80 Replaces 7 piano-key unit as fitted to Decca/Telefunken 30 and 80 chassis
Type 30-C Replaces 7 piano-key unit as fitted to Decca console using long perspex illuminated control panel
Type 100 Replaces 8 position touch tune selector (AEG SAS 660 SAS 670) as used in Decca/Telefunken 100 chassis
Type CVC8-9 Replaces 5 rectangular push button plus thumbwheel as used in ITT

SELECTOR £11 + VAT

FASCIA/MOUNTING KITS (each) £2 + VAT

All orders despatched on day of receipt.

ALDERSON-JAMES LTD

**160 KINGS ROAD ● HARROGATE ● N. YORKS
TEL: HARROGATE (0423) 60058 HG1 5JG**

SATELLITE RECEIVING EQUIPMENT

1.9M, 2.5M and 5M Harrison Dishes
Sat-Tec R5000 4GHz Receivers
Avcom COM-2B 4GHz Receivers
California Amplifier 4GHz LNAs
Chaparral Feed Horns

*Demonstrations by appointment only
Dealers wanted*

HARRISON ELECTRONICS

**22 Milton Road,
Westcliff-on-Sea, Essex SS0 7JX.
Telephone: Southend (0702) 332338**

PRECISION VISION LTD.
67 LONDON ROAD, HEADINGTON, OXFORD

SPECIAL OFFER THIS MONTH:-

- ☆ Large quantity of 10" Decca 700 Tube 80 Series, all in good working order.
- ☆ Limited quantity of Toshiba Colour Portables.
- ☆ Used VHS, Beta, 2000 System Videos in excellent working order.
- ☆ Good selection of modern colour TV's.

**PLEASE PHONE FOR CURRENT STOCK POSITION
(0865) Oxford 750212**

AA117	0.090	BC157	0.055	BD222	0.310	BU108	1.000	DC72	0.500	TIP29C	0.250	3N.128	0.550	2SA473	0.370	28 pin	0.200	PCL82	0.630	LM723	0.320	LED 5mm	
AA119	0.090	BC159	0.055	BD225	0.310	BU110	1.100	DC200	1.800	TIP30	0.160	3N.143	0.650	2SB54	0.250	40 pin	0.250	PCL84	0.500	LM741	Dil.0150	YELLOW	0.100
AA132	0.090	BC182	0.060	BD232	0.310	BU111	1.400	DCP71	1.000	TIP31A	0.240			2SB77	1.200			PCL85	0.550	LM741		LED 5mm	
AC107	0.170	BC182L	0.060	BD237	0.210	BU126	0.700	DRP12	1.000	TIP32	0.240	IN.914	0.020	2SB337	0.200			PCL86	0.550	Met	0.450	GREEN	0.100
AC126	0.170	BC183	0.060	BD238	0.240	BU204	0.750	DRP60	1.000	TIP32A	0.240	IN.4001	0.040	2SB405	0.220			PCL805	0.550	LM3900	0.250		
AC127	0.150	BC183L	0.060	BD437	0.280	BU205	0.750	DRP61	1.000	TIP33	0.500	IN.4002	0.040	2SC460	0.210			PCL86	0.550	NE555	0.150	BRIDGE	
AC128	0.480	BC184	0.060	BD437	0.280	BU208	0.750			TIP34	0.500	IN.4003	0.040	2SC495	0.800			PCL86	0.550	NE556	0.400	RECTIFIERS	
AC129K	0.230	BC184L	0.060	BD535	0.380	BU208A	0.800	R2008B	0.800	TIP41A	0.220	IN.4004	0.040	2SC733	0.400			PFL200	0.850	NE555	0.150	1A 50V	0.160
AC141K	0.230	BC212	0.060	BD536	0.380	BU208D	1.200	R2010B	0.800	TIP41C	0.250	IN.4005	0.040	2SC733	0.400			PFL200	0.850	NE556	0.400	1A 100V	0.180
AC142K	0.220	BC212L	0.060	BD537	0.400	BU326	0.850	SAS560	1.100	TIP42A	0.220	IN.4006	0.040	2SC1161	1.100			PFL200	0.850	NE555	0.150	1A 200V	0.190
AC153K	0.220	BC213	0.060	BD538	0.400	BU406	0.850	SAS570	1.100	TIP42C	0.250	IN.4148	0.020	2SC1172Y	1.500			PFL200	0.850	NE555	0.150	1A 400V	0.210
AC176	0.180	BC213L	0.060	BDX32	1.000	BU407	0.750	SN76003N	1.400	TIP47	0.400	IN.5400	0.080	2SC1279	0.240			PFL200	0.850	NE555	0.150	1A 600V	0.230
AC176K	0.200	BC214	0.060	BDX65	0.800	BU408	1.000	SN76013N	1.400	TIP48	0.400	IN.5401	0.100	2SC1306	1.000			PFL200	0.850	NE555	0.150	1A 800V	0.280
AC187	0.150	BC214L	0.060	BF180	0.160	BU500	1.100	SN76033N	1.400	TIP49	0.400	IN.5402	0.100	2SC1307	1.000			PFL200	0.850	NE555	0.150	2A 100V	0.350
AC187K	0.200	BC237	0.070	BF181	0.180	BU526	0.800	SN76033N	1.500	TIP110	0.470	IN.5403	0.110	2SC1307	1.000			PFL200	0.850	NE555	0.150	2A 200V	0.360
AC188	0.170	BC238	0.070	BF183	0.200	BY126	0.060	SN76110N	0.700	TIP112	0.540	IN.5404	0.110	2SC1307	1.000			PFL200	0.850	NE555	0.150	2A 400V	0.420
AC188K	0.230	BC300	0.180	BF184	0.200	BY127	0.080	SN76115	0.700	TIP115	0.450	IN.5405	0.120	2SC1307	1.000			PFL200	0.850	NE555	0.150	2A 600V	0.540
AC198	0.480	BC301	0.180	BF185	0.200	BY133	0.080	SN76115	0.700	TIP117	0.450	IN.5406	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	2A 800V	0.580
AD149	0.480	BC302	0.180	BF194	0.050	BY164	0.220	SN76226	0.900	TIP120	0.430	IN.5407	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	3A 200V	0.660
AD159	0.450	BC303	0.180	BF195	0.050	BY176	0.050	SN76227	0.800	TIP121	0.460	IN.5408	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	3A 400V	0.880
AD161	0.220	BC382	0.060	BF199	0.060	BY179	0.350	T2800	0.520	TIP122	0.470	IN.5409	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	3A 600V	1.000
AD162	0.220	BC337	0.060	BF200	0.180	BY184	0.320	TAG06-60	0.420	TIP125	0.470	IN.5410	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	3A 800V	1.000
AF124	0.250	BC328	0.060	BF257	0.180	BY187	0.320	TAG521-200	0.720	TIP127	0.560	IN.5411	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	4A 200V	0.660
AF125	0.250	BC357	0.060	BF258	0.180	BY196	0.220	TAG4443	0.760	TIP295	0.340	IN.5412	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	4A 400V	0.880
AF126	0.250	BCY32	1.500	BF259	0.180	BY206	0.110	TAG4444	0.760	TIP305A	0.380	IN.5413	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	4A 600V	1.000
AF127	0.250	BCY33	1.500	BF336	0.200	BY207	0.120	TAA550	0.160	TIP305B	0.380	IN.5414	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	4A 800V	1.000
AF139	0.220	BCY34	1.500	BF337	0.200	BY223	0.070	TBA120S	0.450	TIS61	0.150	IN.5415	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	5A 200V	0.660
AF239	0.220	BCY42	0.200	BF338	0.280	BYX10	0.150	TBA395	0.600	TIS90	0.150	IN.5416	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	5A 400V	0.880
AL112	0.700	BCY56	0.160	BF362	0.300	CA270	0.400	TBA396	0.600	TIS91	0.180	IN.5417	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	5A 600V	1.000
AL113	0.800	BCY70	0.160	BF422	0.210	CA3086	0.250	TBA520	0.750			IN.5418	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	5A 800V	1.000
ASZ15	1.000	BCY71	0.160	BF458	0.190	CA3089	1.500	TBA530	0.750			IN.5419	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	6A 200V	0.660
ASZ17	1.000	BCY72	0.160	BF459	0.190	CA3240	0.900	TBA540	0.750			IN.5420	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	6A 400V	0.880
AU106	1.000	BD115	0.260	BFX29	0.200	C106D	0.230	TBA560	0.700			IN.5421	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	6A 600V	1.000
AU110	1.100	BD124P	1.500	BFX84	0.200	MC1327	0.700	TBA800	0.350			IN.5422	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	6A 800V	1.000
AY102	1.800	BD124	1.100	BFX85	0.200	MJ2500	1.000	TBA810S	0.500			IN.5423	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	7A 200V	0.660
AY106	1.800	BD128	0.350	BFX87	0.150	MJ2501	1.000	TBA820	0.750			IN.5424	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	7A 400V	0.880
BA145	0.100	BD131	0.250	BFX88	0.150	MJ2501	1.000	TBA820	0.750			IN.5425	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	7A 600V	1.000
BA148	0.100	BD135	0.250	BFY50	0.140	MJ2501	1.000	TBA820	0.750			IN.5426	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	7A 800V	1.000
BA154	0.060	BD136	0.200	BFY51	0.140	MJ3000	1.550	TBA820	0.750			IN.5427	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	8A 200V	0.660
BA157	0.120	BD137	0.200	BFY52	0.140	MJ3001	1.150	TBA820	0.750			IN.5428	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	8A 400V	0.880
BB101	0.130	BD138	0.200	BFY53	0.140	MJ3001	1.150	TBA820	0.750			IN.5429	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	8A 600V	1.000
BB103	0.160	BD139	0.200	BFY54	0.140	MJ3001	1.150	TBA820	0.750			IN.5430	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	8A 800V	1.000
BB105B	0.180	BD140	0.200	BFY55	0.140	MJ3001	1.150	TBA820	0.750			IN.5431	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	9A 200V	0.660
BB205B	0.240	BD144	0.900	BFY56	0.250	MJ3001	1.150	TBA820	0.750			IN.5432	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	9A 400V	0.880
BC107	0.070	BD150	0.300	BFY57	0.250	MJ3001	1.150	TBA820	0.750			IN.5433	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	9A 600V	1.000
BC108	0.070	BD157	0.380	BFY58	0.250	MJ3001	1.150	TBA820	0.750			IN.5434	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	9A 800V	1.000
BC109	0.070	BD158	0.380	BFY59	0.250	MJ3001	1.150	TBA820	0.750			IN.5435	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	10A 200V	0.660
BC115	0.100	BD166	0.300	BFY60	0.250	MJ3001	1.150	TBA820	0.750			IN.5436	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	10A 400V	0.880
BC118	0.110	BD175	0.300	BFY61	0.250	MJ3001	1.150	TBA820	0.750			IN.5437	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	10A 600V	1.000
BC140	0.190	BD177	0.300	BFY62	0.250	MJ3001	1.150	TBA820	0.750			IN.5438	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	10A 800V	1.000
BC141	0.190	BD179	0.320	BFY63	0.250	MJ3001	1.150	TBA820	0.750			IN.5439	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	11A 200V	0.660
BC142	0.190	BD181	0.350	BFY64	0.250	MJ3001	1.150	TBA820	0.750			IN.5440	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	11A 400V	0.880
BC143	0.190	BD201	0.330	BFY65	0.250	MJ3001	1.150	TBA820	0.750			IN.5441	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	11A 600V	1.000
BC147	0.055	BD202	0.380	BFY66	0.250	MJ3001	1.150	TBA820	0.750			IN.5442	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	11A 800V	1.000
BC148	0.055	BD203	0.420	BFY67	0.250	MJ3001	1.150	TBA820	0.750			IN.5443	0.130	2SC1307	1.000			PFL200	0.850	NE555	0.150	12A 200V	0.660

MANTEL

Manchester's No. 1 in Ex-Rental TVs
Over 2,000 TVs in stock
Special Offer on Working Colour TV's

All sets are Serviced with repolished cabinets ready for sale

Philips G8 550s	22/26	£45
Philips 18"		£40
Philips G8 520s	22/26	£35
GEC S/State	from	£35
Thorn 17" 8000		£30
Decca 30	18/20/22/26	£30
Japanese	from	£30
Many other makes available from £25		

Discount on quantity

Some Examples of UNTESTED TVs available

Thorn	10 for	£125
Philips	6 for	£90
Bush	6 for	£80
GEC	6 for	£60
Decca	6 for	£60
Mono TVs avail. s/s		£4 each
New TV trolley stands.		
All sizes		£4.95
All Prices subject to V.A.T.		

Ex Equipment Panels & Tubes Available

Deliveries may be arranged to the North and Scotland.

Ring for quote. Callers welcome.

419 Barlowmoor Road, Chorlton, Manchester 21 2ER.
Tel: 061 861 8501

TELEVISION TUBE SHOP LTD

BRAND NEW TUBES AT CUT PRICES

A31-19W/20W.....	19.95	230DB4CT468.....	31.00
A31-120W/300W.....	17.95	240DB4/240AB4A.....	22.00
A31-410/510W.....	17.95	CT507 equiv.....	21.95
A34-100W/510W.....	18.50	310DGB4/DMB4.....	23.00
A34-514W.....	24.25	310EUB4.....	19.95
A38-160W/170W.....	17.50	310EUB4A.....	18.50
A44-120W/R.....	25.00	310EYB4.....	18.75
A50-120W/R.....	19.00	310FXB4.....	17.50
A61-120W/R.....	21.00	310GNB4A.....	31.00
9AGP4.....	£21.82	310HCB4.....	31.00
190AB4/C4.....	23.00	340AB4.....	22.50
		340AYB4.....	30.00
		340AXB4.....	30.00
		340RB4/CB4.....	26.00
		340AHB4.....	26.00
		RIGONDA 6".....	14.00

Some Rebuilt Japanese & European Types Available from £14.00 +VAT £2.10

COLOUR TUBES

(NEW & MULLARD/THORN COLOREX)*

12VARP22.....	£62.50	A56-120X.....	£54.00
330AB22.....	73.50	A56-410X.....	64.00
A44-271X.....	60.00	A56-500X/510X.....	63.00
A47-342X.....	61.00	A63-120X.....	63.00
A47-343X.....	61.00	A66-120X.....	65.00
A49-191X.....	53.00	A66-140X/410X.....	70.50
A51-161X.....	70.00	A66-500X/510X.....	65.00
A51-220X.....	55.00	A67-120X.....	65.00
A51-500X/510X.....	64.50	A67-140X/200X.....	69.50
A51-570X.....	73.00	A67-150X.....	75.00

Old Bulb Required for 110° Colorex

ADD 15% VAT TO ALL THE ABOVE PRICES.

Please allow 7 days for delivery

ALL TUBES TESTED BEFORE SALE & FULLY GUARANTEED

TELEVISION TUBE SHOP LTD

52 BATTERSEA BRIDGE RD., LONDON, SW11.

Tel. 228 6859/223 5088 CARRIAGE: Mono £3, Colour £10.

20AX APOLLO 30AX

HIGH TEMPERATURE PUMPED COLOUR TUBES

Fast Mail Order service to any part G.B. Delivery 2-3 days.

Just phone for a quotation. Delivery Manchester area free same day. Two year guarantee. Fitting while you wait or in your home £20.

18"	A47 - 342 x343	470 BEB22 (£45.00)	£37.00
19"	A49 - 120 x/192 x		£37.00
20"	A51 - 220 x/110 x/161 - 510JKB22	(£45.00)	£38.00
22"	A56 - 120 x/123 x/140 x/410		£38.00
25"	A63 - 120 x		£39.00
26 x	A66 - 120 xA67 - 120 x/140 x/150/200		£39.00
20AX	56-510		£48.00
30AX	56/66-540		£48.50
20" - 22" SOLID STATE COLOUR TVs FULLY SERVICED & SOAK TESTED. VERY RELIABLE WITH GOOD TUBE £61.00, WITH NEW TUBE £83.00 inc DELIVERY			

061 799 0854 24 hour answering service.

43 Clarke Cres, Little Hulton, Nr. Manchester M28 6XM.

A.B.C. TRADE SALES

COLOUR T.V.'s

Philips G8, Pye, Decca 30's,

Thorn's 3000's, 3500's, 8000's

Prices start from £12 - Working sets from £20

Hundreds of Mono T.V.'s from £2.00

Jap. sets from £30.00

Special prices for quantity

9,000 sq. feet Warehouse

83 SHOWELL ROAD, BUSHBURY,

WOLVERHAMPTON, STAFFS.

Tel. Wolverhampton 722637

LONDON'S LARGEST TELEVISION WHOLESALER ...

with over 4½ thousand sq. feet.

"TELEMANN"

8-10 RHODA STREET,
(Off Bethnal Green Road)

LONDON E.2. FREE CAR PARK

TEL: 01-739 2707

ALL MAKES IN STOCK AND GUARANTEED COMPLETE

PYE 22" COLOUR FROM £7.50

PHILIPS 22" (Teak cabinet) PARCEL OF TEN £15

MONO DUAL STANDARD PARCEL OF 20 £1

- SINGLE STANDARD £3

FREE DELIVERY TO THE LONDON AREA!

TELEPHONE 01-739 2707 - NOW!

CENTREVISION

For Video, Television, Audio
MANUFACTURERS SECONDS

Plus selection of modern TV's: T20 9000 etc.

Hybrids at give-away prices.

Also:

Tubes, Parts, Stands etc, plus working sets.

Sloper Road, Cardiff.

Telephone: 0222 44754

IRISH T.V. DEALERS

Large quantity of working Colour & B/W T.V. sets UHF-VHF. Nordmende, Bush, Philips, Ferguson, Pye, etc. at very competitive prices.

Working colour sets at £70

Fresh stocks weekly, quantity discount, delivery arranged.

(SPECIALISTS IN OVERSEAS ORDERS)

For further details ring:

J. HYDE at 01-264139 Extn. 11.

T.V. TRADE SALES, E.D.I. House, Kylemore Pk. West, Dublin 10.

(Open 10 to 5.30 pm)

Prices exclude VAT.

EMCO - EUROSONIC - GRUNDIG - TELETON + ALL BRITISH MAKES
ETC., ETC. ● ALL SPARES READILY AVAILABLE ●

IMMEDIATE CREDIT AVAILABLE - TRADE ONLY

If you are a trader simply phone for the part you require and we will send it - no quibble - no hold up for status check. Satisfy us over the phone that you are a trader and we will supply almost any TV component by return "off the shelf". e.g. LOPTX - EHT trays - droppers - OSC coils - switches - cans - smoothers - I.C.'s, etc. etc.

**YOU CAN BE 95% SURE WE CAN SUPPLY ANY
TV COMPONENT BY RETURN
IF YOU NEED SPARES FAST - RING NOW!**

ACCESS AND BARCLAYCARD ACCEPTED.

Applies to U.K. only.

TELEPART (W'TON)

THE TELECENTRE, WORCESTER ST.,
WOLVERHAMPTON (0902) 773122

**SCOTTISH TV
DEALERS**

Working TV's from £18.00
BUSH 'A' & THORN 3,500

TV PANELS

WORKING & SOAK TESTED

	Bush 'A'	Thorn
Speaker	5p	5p
I.F. Panel	1.75	2.50
Field/Line drive	2.75	
Field/Sound output		2.75
Convergence	1.50	3.75
Power Supply	2.00	10.00
Tuner Mechanical	3.75	3.50
Tuner on panel complete	4.75	5.75
L.O.P. plug-in chassis, complete	5.75	
Line Output Panel		7.50
Video Panel		4.00
2 Chip Decoder - Chroma	10.50	3.50

Other working parts available

NO VAT just add £1.50 p&p per 1 item
and 75p per each additional item

Cheques etc. payable to: "TV PANELS"

DISCOUNT T.V. SERVICES

"TV PANELS"

Unit 11,

Mayfield Industrial Estate,

Mayfield, Dalkeith,

Midlothian, EH22 4AD.

Tel: 031-633 0380 9am-4pm

other times 031-663 8940

TOP 20 VIDEO SPARES

Cassette lamps (Ferg/JVC)	£1.80
Cassette lamps (Panasonic)	£1.80
Take-up clutch (Ferg)	£5.95
Belt kit (Sony 8000)	£6.50
Belt kit (Ferg early)	£6.50
Belt kit (Pan NV7000)	£6.50
Belt kit (Sanyo 9300)	£6.50
Rewind kit (Sony C7)	£6.50
Reel idler (Sharp VC)	£3.45
Video Head (Sony C7)	£39.50
Video Head (Ferg)	£37.50
Video Head (Pan)	£37.50
Head cleaning fluid	£1.50
Head cleaning Tape (VHS)	£5.95
Head cleaning Tape (Beta)	£5.95
Loading belt (SL8000)	£1.50
Loading belt (Sanyo 9300)	£1.50
Overhaul kit (Ferg)	£19.95
Overhaul kit (Sony)	£19.95
Overhaul kit (Sharp)	£19.95

TOP 20 T.V. SPARES

G8 LOPT	£8.45
Decca 100 LOPT	£8.45
Decca 80 LOPT	£8.45
Bush T20 LOPT	£13.50
Thorn 9000 Tripler	£9.95
Decca Bradford Tripler	£7.95
Universal Tripler	£6.95
BU 208A	£1.20
Philips G11 Smoother	£1.95
G11 Tip switch tuner head	£25.50
VA1104 thermistor	£0.75
Mullard 1043 tuner	£7.95
Decca Bradford LOPT	£8.45
0.47uF 1000V capacitor	£0.99
0.1uF 1000V .mains filter	£0.60
Tuner pots 100k (Pk 6)	£3.00
BU 326	£1.20
Bush T20 Tripler	£7.50
Philips G8 mains dropper	£1.20
Thorn 9000 push button unit	£3.25

TELEVIDEO SERVICES

NOTTINGHAM (0602) 226070

76 Wollaton Road, Beeston, Nottingham

Please add 50p post & packing and then add 15% VAT to total.

ALL ORDERS DESPATCHED BY RETURN OF POST

SETS & COMPONENTS

SCRATCHED TELEVISION TUBES. Don't despair, send for repair, 20 years experience. Retube Limited, North Somercotes, Louth, Lincolnshire. Phone 0507 85300.

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO, 103 South Brink, Wisbech, Cambs. 0945 584188. Immediate settlement.

GRUNDIG MILLIVOLTMETERS 100u/300V. Working order £15 + £3.00 p&p. Also P.S.U.'s isolating transformers, etc. S.A.E. Lists. S.H.E. 5 St. Josephs Park, Ballycruttie, Downpatrick BT30 7EN.

TELEVISION

No other consumer magazine in the country can reach so effectively those readers who are wholly engaged in the television and affiliated electronic industries. They have a need to know of your products and services.

The prepaid rate for semi display setting £6.00 per single column centimetre (minimum 2.5 cms). Classified advertisements 35p per word

THORN COLOUR TVs

Most models. Excellent condition. Working or untested.

- ★ Philips 550/660
- ★ Decca 1051/1052
- ★ Pilot (JVC) etc.

Phone or call for competitive prices.
Regular supply.

REPOSSESSED TV CENTRES LTD.,
335-341 Stockport Rd., Longsight, Manchester.
Tel. 061-273 2854.

GRUNDIG. We sell complete working sets from £40. Reconditioning panels from £4. We buy remote control handsets. OCHREMILL 0785-814643.

SECOND HAND Colour TV spares and tubes. Most makes. Telephone Southport (0704) 74411. Anytime.

THORN SPARES AND PANELS. Nothing over £5. S.A.E. S. Knight, 2 Claremont, Hastings, E. Sussex.

SCHRADER TUNABLE UHF Masthead Amplifier RB45 A.S. MV.30DB gain, 1.6DB noise. CH. 17-65. P.S. inclusive £39.50 P&P £1.50. R. VAN REYSEN, 28 Pemberton Road, East Molesey, Surrey.

Trent Tubes

31 RADCLIFFE ROAD,
WEST BRIDGFORD, NOTTINGHAM
TELEPHONE (0602) 813329

"THE" QUALITY REBUILDER

Cash & carry price list

TWO YEAR GUARANTEE
FOUR YEAR OPTION EXTRA

ALL STANDARD DELTA TYPES
ONLY £25.00

A51-161. A51-162. A51-163
£35.00

A51-510. A56-510. A66-510 etc.
560 AKB. 560 CXB22. A51-570
£40.00

A56-540. A66-540 (30AX)
£49.00 (COMPLETE WITH
MULTI POLE)

SPECIAL OFFER 560 DZB22
£39.00

MONOS 20" & 24" only £14.00

LARGE discounts for quantity.
DELIVERY service available.

ALL TUBES picture & electronically
tested.

ALL tubes supplied on exchange basis
& all prices are plus VAT.

1000's of other types available.

AGENTS REQUIRED

TV's solid state from £65.00 + VAT
All working & fitted with a Trent
Tube.

A.B.D. TELEVISION LTD.

100's Colour TV's in stock in excellent
condition - working sets for the trade.

Fresh stocks weekly
Untested - complete
(Majority working)

Mono TV's	£2
Bush 22"-26" CTV Solid State	£5
Hybrid Decca - ITT	£12
Philips G8 - 550	£18
G.E.C.	£20

Philips G11, Bush T20, ITT CS 600
Prices on quotation

Many other makes to choose from
Refurbished Sets - Showroom Condition
Ready to Retail

BRC 9000	£50
Bush T20	£75
ITT CS 600	£85

WE ARE OPEN SEVEN DAYS A WEEK
Unit 3 & 3A, Meadow Trading Estate,
Meadow Lane,
Nottingham, NG2 3HQ.
Nottingham (0602) 864627

EX RENTAL C.T.V.'s & REGUN TUBES

RBM, THORN, DECCA, PYE GEC,
GRUNDIG, ITT, PHILIPS G8, G9, G11,
JAPANESE
From £10

Also all modules from £4 untested.

STARLITE ELECTRONICS,
80 Como St., Romford, Essex.
Telephone Romford 752537
London Code 3.

WANTED

T.V.s, VIDEOS,
HI FI, AUDIO

£100,000 TO SPEND

If you have a surplus, we
would be delighted to make
an offer.

Contact:

Mr Fred Tuck
(0934) 413537



- * Britains most reliable source
of quality TVs.
- * Hundreds of working pol-
ished TVs.
- * New adjustable TV stands.
- * Pye 18" Chelsea's working &
polished £35.00 in quantity.

Krystal Marketing Ltd.,
Breedon Cross Storage,
Dale Road, Selly Oak,
Birmingham B29 6AQ.

Phone 021-471 3023
Telex 335540-G
Ask for Les

RANK BUSH MURPHY TV PANELS

Repair, exchange, sales service, prompt effi-
cient service. All chassis covered. New PCB
available to replace burnt T20 line Panel. We
charge only £16 to repair switch mode power
supply. Ring Monday to Saturday and ask for
Mr. Kheli.

T. K. Panels Service,
31 Bronte Paths, Stevenage, SG2 0PG.
Tel. (0438) 61567.

SATELLITE TV RECEIVER

Receives 4GHz band. Ideal for demon-
stration terminal in U.K. 100 degree
Kelvin LNA. £392 + VAT (+ Carr).
LNA/down converter PCB's stocked for
the constructor. SAE data.

HUGH COCKS TV SERVICES,
Cripps Corner, Robertsbridge,
Sussex TN32 5RY. Tel. 058083 317.

SERVICE PAGES

(minimum 12 words), box number 70p extra. All cheques, postal orders etc., to be made payable to Television, and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Television Room 2612, IPC Magazines Limited, Kings Reach Tower, Stamford Street, London SE1 9LS. (Telephone 01-261 5846).



HAVE MOVED!

We have moved into additional warehousing
and are now offering
MORE CHOICE AND BETTER VALUE


Guaranteed - Complete Sets from £10.00
Trade Workers from £25.00
Panels By Post from £3.00
Mono's from £1.00
Stands — Aerials — Accessories Etc.

Make '84 your most
Profitable year with
SCREENPLAY'S unbeatable
Stocks and Prices
OPEN 5 DAYS —

Phone: Hitchin 31644

Baldock 894905

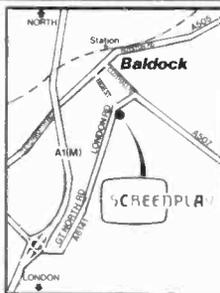SECTION THREE, UNIT FOUR, SERL COMPLEX,
LONDON ROAD, BALDOCK, HERTS.



★ TELEBEST ★

We specialise in working sets.

BUSH · DECCA · G.E.C.
GRUNDIG · PYE · PHILIPS
THORN Etc.

From £25 plus VAT.

Non workers available
Panels, Tubes etc. available.

Call Ronnie on:
01-514 1333

for stock availability
**841 Romford Road,
Manor Park, London E12.**

REBUILT COLOUR TUBES DELTA TYPES

Example Prices

All sizes up to 22" — **£28.00**
All sizes up to 26" — **£32.00**

*All In Line P.I.L. Mono
Gaming Machine C.R.T.s*

Fast U.K. Delivery

Call or Phone:

RE-LIFE T.V. TUBES
PLANE STREET,
OLDHAM, LANCs.
061-665 2668

*Big reductions on Contract Orders
Home or Overseas.
Wholesalers Required
in certain parts of the U.K.*

WOODSDALE COMPONENTS RANK BUSH MURPHY TRANSFORMERS

Line Output
Z718 (T703A, T706A) **£20.50**
New (Complete)
Less Focus Module and
Rectifier **£10.50**
T20, T22 (T705A) **£9.00**
T26 (T705B) **£9.50**
Switch Mode
T114A/B **£8.00**

Genuine RBM Units.

AERIALS

UHF Aerials P & C Wideband 4 Bay
Bowtie (12.5 dB) **£20.00**
Above with built-in Broadband amp.
(27dB) plus stabilised power
supply **£45.00**

Prompt Postal Service.

Add 15% VAT to all prices.

DISCOUNT for QUANTITIES.

34 Field End Road, Eastcote,
Pinner, Middlesex. HA5-2QT.
Tel: 01-868 5580.

N. Skehan

Agents Office. Callers by appointment only.

WETSTED TUBES PRESENTS AN UNBEATABLE OFFER

£26 ALL DELTAS ONE PRICE

£40 ALL P.I.L. ONE PRICE

- * SPECIAL CRT POLISHING SERVICE
WHILE U WAIT **Only £5**
- * ALL DELTA SIZES FROM STOCK
- * DISCOUNT FOR ORDERS OF 5 CRTs OR
OVER
- * FREE DELIVERY WITHIN 20 MILE
RADIUS OF MAIDSTONE

Ring Now
Maidstone 872400
or visit our factory.

Unit 32, Branbridges Ind Est.
East Peckham, Kent.

- * Agents required in South
Prices do not include VAT

GLOBETEL

Tel: 807 6992

Les & Phil — Ex. S.T.S. Colindale
Rear of Globestone Ltd.,
1-7 CHURCH ST., EDMONTON.

We have now opened our own
warehouse for used T.V.'s at
very fair prices.

All popular makes in stock, eg:
Philips, Pye, Grundig,
Jap. sets, etc.

Look forward to seeing both old
and new cust.

We also stock & buy used videos
— VHS only.

TV VALVES

COLOUR VALVES PY500/A-65p, PL509/519-£1.50.
MONO VALVES ECC82, EF85, EF183, EF184, DY87,
DY802, PCF80, PCF802, PCL82, PCL83, PCL84, PCL85/
805, PCL86, PCC84, PCC89, PC92, PC97, PC86, PC88,
PFL200, PL36, PL504, PY800, PY88 ETC.
MONOCHROME VALVES ALL 35p EACH.
ALL VALVES EX-EQUIPMENT & TESTED.
P&P 50p Per order, Access/Visa Cards welcome.
ELECTRONIC MAILORDER, 62 Bridge St.,
Ramsbottom, Lancs, BL0 9AG. Tel. (070682) 3036.

TELEVISION

Trade & Retail supplies of s/h colour & mono TVs. Most makes available, workers or non-workers

SOUTHPARK DISTRIBUTORS

Unit 4 Rubastic Road,
Brentpark Industrial Estate,
Southall, Middx. UB2 5LL.
01-574 4631, Ext 28

TVs WANTED FOR CASH IN EIRE

UHF/VHF colour and black and white, any quantity. Working or non working. Will collect any part of Eire.

BOX NO TV 185.

TRADE TELEVISION SUPPLIES now available in Boumemouth. From £15. (Min 5 sets). Telephone Boumemouth 38081. Some working sets available £20.

JABCO LOPT TESTER

Used by Mullard, Plessey, Ministry of Defence, BBC, IBA, and worldwide etc. etc.
£16.50 inclusive. C.W.O. delivery 3 days. £18 overseas post by sea. £21 airmail.

J. BAKER & CO.

1 Old Shoreham Road, Southwick,
Sussex BN4 4RD.
Tel: Brighton 593315

Thorn 3000/3500
Thorn 9000

UNIVERSAL 1 year guarantee

TRIPLERS
£4.50 inc. p&p

The UNIVERSAL TRIPLER can be used in most G.E.C., I.T.T., Pye, Rank, Decca & Continental sets.

WING ELECTRONICS

15 Waylands, off Tudor Rd, Hayes End, Middlesex

COLOUR BAR GENERATOR

Pal Colour Generator with 11 patterns plus sound. Grey scale, Colour Bars, Red, Green & Blue Raster, Crosshatch, Dots, Chequer Board, Black Raster, White Raster, Half Black & White £75.90.



BLACK AND WHITE GENERATOR

Crosshatch, Peak White, Dots, Half Black & White and Grey Scale £18.50
In Circuit Transistor Tester £14.25
Capacitance Meter measures 10pF to 1µF complete with moving coil meter £14.75

Prices include P&P & VAT.

C.M.J. ELECTRONICS

Unit 8, 16 Union Mill Street, Horseley Fields,
Wolverhampton WV1 3DW.
Tel: (0902) 871563

TELEVISION

TOP QUALITY

SPECIAL CLEARANCE

TOP QUALITY

Makes	Example Prices	Non-Workers	Working
Philips G8S, 2 chip Bush/Murphy		£16	£30
Thorn 3000, 3500, 8000, 8500		£18	£30
Thorn 8800, 9000, 9800, Touch Tune Sets etc.		£30	£45
Bush T20's, Philips G11's		£50	£70
GEC Solid State, all types		£25	£45
ITT CVC 5/8/9		£14	£30

MONO IN BATCHES OF 20 at £2.00 EACH. Discount for quantity. Other makes available on request.

Spare TV parts and panels available for the above sets mentioned at competitive prices. Please refer to last month's issue of Television for price list.

MS ELECTRONICS

Unit 1, Warwick Street,
Earlsdon Coventry.

N.B. Note to give prompt service, telephone to order in advance to avoid disappointment.

COLOUR TV'S
FROM £15.50 + VAT
GUARANTEED COMPLETE GOOD CABINETS

VHS VIDEOS PLUS VIDEO SPARES

PYE CT205/CT200, BUSH A823, TH3500/8500 Phil G8.
DECCA. BRAD. ITT. CVC5. GRUNDIG

SMITHS ELECTONICS

43 PARK PARADE

LONDON NW10

01-965 1230

01-961 3997

When replying to Television Classified Advertisements please ensure:

- That you have clearly stated your requirements.
- That you have enclosed the right remittance.
- That your name and address is written in block capitals, and
- That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

CANVEY COLOUR TUBES

Unit 3, Charfleets House, Charfleets Industrial Estate, Canvey Island, Essex.

Tel: Canvey Island (0268) 690577

CURRENT PRICE LIST

DELTA TUBE TYPE FROM £27.50 to £31.50

INLINE TUBE TYPE FROM £35.00

MONO TYPES P.O.A.

ALL PRICES EXCLUSIVE OF VAT.

All Tubes Guaranteed for 2 YEARS and Reprocessed to Original Manufacturers Specifications.

NORTHERN IRELAND DEALERS

We have the best value in second televisions. And our low, low prices are second to none. Phillips 550, Decca 100/80/302, Pye 741 series and many other makes available.

Prices: Non workers (complete) from £20.

Guaranteed worker from £38.

We deliver bulk orders anywhere in Northern Ireland. New loads arriving regularly so phone now for latest stocks.

SM ELECTRONICS

11 Sandholes Road, Cookstown N. Ireland.

Tel: Cookstown (NI) 06487/64277.

TO ADVERTISE
IN THIS SPACE

RING
MANDI

01-261 5846

SERVICE PAGES

TUBES £29.00 INCLUSIVE, REGUNS ONE YEAR GUARANTEE, QUANTITY DISCOUNTS
TUBES £14.50 SIX MONTH GUARANTEE SLIGHTLY USED

A56-120 A51-110 A49-191 A47-342 or 343 A44-270-1 A66-120 A67-120 (All 26" add £5)

IN-LINE 51-161 From £35 plus 100's more

Professional Stick **DE-GAUSING COILS £19.50** inclusive of delivery. One year guarantee.

Delivery £5 per tube. British Isles. No need to spend £5 returning old tube if you buy from us.

U-VIEW TUBES, 29 WARMSWORTH ROAD, DONCASTER, YORKSHIRE DN4 0RP.

Tel: 0302-855017

Local stockists. Cash & Carry only at the above prices. Ring first. Please bring old tube if possible. Callers ring first. Open every day including Sunday

DELTA TVs, Unit 5A, Union Mill, Union Mill Street, WOLVERHAMPTON 0902 870757

K. M. ELECTRONICS, 8 Hillfield Place, Aberporth, DYFED 0239 810963

OTHER STOCKIST REQUIRED

COLOUR T.V.s

THE BEST IN LONDON
200 + TVs WEEKLY

LOADS SMALL SCREEN
WORKING SETS TO
ORDER — ALL MAKES

WINDSOR WHOLESALE
TEL: 01-968 8771.

BARRY TV SERVICES (EAST ANGLIA)

Your friendly wholesalers. We cater for the smaller dealer who requires regular small supplies of quality used colour TV's. From £25 + VAT. Fully working with good tubes and cabinets, straight from our retail shelves, ready to sell or rent.

Delivery available

Contact John, Dave or Steve on Ely 61462 or Cambridge 69215

TELEVISION

Trade Supplies of Good Quality Colour & Mono TV's. Most Makes available, suitable for Sale or Re-Rent.

GENERAL FACTORS

UNION STREET,
DONCASTER
(0302) 49583-68416

GOOD MOTORWAY ACCESS

TORBAY (TRADE) T.V.

For Good Quality Used Colour & Mono T.V.'s, Popular Makes, Quantity Discounts, Trade Workers from £22.50 + VAT. (un-tested available)

6, CASTLE CHAMBERS,
HIGHER UNION STREET,
TORQUAY, DEVON
Tel: (0803) 22767.

WIZARD DISTRIBUTORS MANCHESTER

SPECIALIST DISTRIBUTORS TO THE TRADE OF T.V. & VIDEO SPARES.

WE STOCK A FULL RANGE OF PARTS & COMPONENTS INCLUDING C.R.T.'s, VIDEO HEADS ETC.
RANK - THORN - PHILIPS - ITT - DECCA - GEC ETC.

TRADE COUNTER OPEN: 9-4.30
CATALOGUE ON REQUEST. TRADE ONLY.

Mail Order Enquiries Welcomed

EMPRESS STREET WORKS,
EMPRESS STREET,
MANCHESTER M16 9EN.
TEL: 061-848 0060.

T.V. SPARES, PANELS AND MANUALS PHILIPS · GRUNDIG

TELEVIEW 01-994 5537
194, Acton Lane, London W.4.

TELEVISION TUNER REPAIRS ALL TYPES

BRITISH, EUROPEAN
JAPANESE ETC.

MEN-TU ELECTRONICS LTD.
SALTERNS LANE,
FAREHAM, HANTS.

Tel: 0329-235116

TRADE COLOUR TV's ALWAYS 200 IN STOCK

Phillips G8 from £10
Bush Twin Chip from £8
Pye Chelsea from £15

Avo repairs prompt service scopes etc.
Colour TV's in good working order from £35.
E.G. Phillips G8's 22" £35.
Ring us for spares and type availability anytime.

Also Videos. V2020 and V2023's etc.

ALL STOCK CHANGES WEEKLY
(0934) 514047/512792/27560
P&R SUPPLIES, Unit 5,
Worle Industrial Estate,
Weston-Super-Mare. Exit 21 M5.

VIDEO

VIDEO WEST

COMMUNICATION LTD

258 HIGHER UNION STREET - TORRE - TORQUAY TQ2 50U
Telephone (0803) 20898 and 211880

V.H.S. VIDEO RECORDERS "EX RENTAL"

QUANTITY SUPPLIED

J.V.C. FERGUSON
TRADE ONLY ★ ALL GOOD ★
THE SPECIALISTS

EUROLEC VIDEO SERVICES

Tel: 01-669 2611

Telex: 893819 Eurlac

Address for correspondence only:

35 Sandy Lane South, Wallington, Surrey SM6 9RF

Thank you for the interest shown in last month's advertisement. We still have LVC 60 at prices shown, also a quantity of VC30, used but tested at £2.50 each + 25p postage per item.

For those licensed amateurs sending live TV and who wish to upgrade the quality of recording, we are due to receive a number of JVC 6000/6060 and Sony 1810 Umatic recorders at a price between £150-£250. SAE for notification when full details available. (Mark envelope Umatic).

Note we are in process of buying in large quantity of Philips cassettes. No details yet, but an SAE will bring full details and 10% discount offer over advertised prices as soon as details available.

Half inch tape, high and low density on 7" Spools £2.50 including P&P. (Not suitable for Philips format cassettes).

Bulk branded VHS cassettes still available, any length. Phone for details.

Professional equipment including cameras and edit suites still available.

We have one Philips series 80 TV studio, complete at a most realistic price. Please phone for details.

We have one further Philips projection TV, 60CP 2605 integral tuner, including new 72" screen £750.

NTSC - PAL Transfers, ring for quote.

VAT Reg. No. 335 7096 45.

AERIALS

AERIALS AND ACCESSORIES. Terrific range of quality equipment including some off-beat items and some real clearance bargains. Keen prices. New catalogue 50p (refundable). WRIGHTS AERIALS, 43 Greaves Sike Lane, Micklebring, Rotherham.

2 METRE PARABOLIC DISHES

Glassfibre Construction
Suitable for 4 and 12 GHz £290
Polar Mounts and Feed Supports Available.

Send S.A.E. for Details

SP ANTENNA SYSTEMS,
3 Woolpack Corner, Biddenden,
Ashford, Kent TN27 8BU
Tel: 0580 291090

AERIALS AND ACCESSORIES

North London's Specialist Aerial Supplier
Wholesale and Mail Order.

VHF/UHF antennas, masts, brackets, cable, amplification and distribution equipment etc. All types of aerial hardware and software supplied. Single and multipoint systems planned and installed.

Send 50p for our new 1983 catalogue and price list.

S.C.S. AERIALS

(Aerial Distributors)

26-28 Port Vale, Hertford, Herts. SG14 3AB.
Tel: 0992 50478.

AERIAL BOOSTERS

Next to the set fitting

B45H/G-JHF TV, gain about 20db, Tunable over the complete UHF TV band. Price £8.70.

B11-VHF/FM RADIO, gain about 14db, when on the off position connects the aerial direct to the radio. Price £7.70.

All boosters we make work off a PP3/006p/BF22 type battery or 9V-18V DC. P&P 30p per order.

ELECTRONIC MAIL ORDER, 62 Bridge St, Ramsbottom,

Lancs BL0 9AG. Tel. (07062) 3036

Access/Visa Cards Welcome SAE Leaflets

SERVICE SHEETS

TELEVISION SERVICE SHEET SPECIALISTS

Thousands of British, European, and Japanese models in stock.
Colour £2.00 Mono £1.50 (post free)
 Manual prices on request.

Send stamped envelope for free catalogue and enquiries

SANDHURST PUBLICATIONS (MAIL ORDER)
 49C Yorktown Road, Sandhurst, Camberley, Surrey GU17 7AG

30,000 SERVICE SHEETS IN STOCK. COLOUR MANUALS ALSO AVAILABLE

TV Monos, Radios, £3.00. Tuners £3.00. Tape Recorders, Record Players £3.00. Transistors £3.00. Car Radios £3.00 + SAE. Stereograms & Music Centres £3.00. Radiograms £3.00. Also Colour available. State if circuit will do if sheets are not in stock. Circuits £3 - colour. All TV Sheets are full length 24 x 12 not in Bits and Pieces. All other Data full lengths. All Sheets £3 except colour. SAE please. Old Valve Radios £3 + SAE 9 x 3. Ensure payment with order.

C. CARANNA, 71 BEAUFORT PARK, LONDON NW11 6BX. (MAIL ORDER)

WANTED

G11's WANTED in 1's or 100's. Let us know what you have. Please telephone: TV SALES on Watford 45590.

COMPLETE TUBE RE-GUNNING plant. Electric ovens also Lopt winding machine. **KELLEHER BROS.** TV House, Kanturk, Cork, Ireland. Tel. 029 50046.

WANTED. QUANTITY G11's or other late colour T.V.s. No rubbish. Can collect Sussex/Kent. (0424) 439260.

WANTED PHILIPS PM5334 Television Sweep Generator. Telephone 01-328 7641.

WANTED. We will clear any amount of colour sets from small Rental Companies, Hotels, etc. Please phone P & R Domestic Electrical Clearance Supplies, Weston Super Mare (0934) 514047.

WANTED TELEVISION MAGAZINES, Jan. 73 to May 81. State price. Telephone 0382 817013. McGhee, 86 Haldane Terrace, Dundee.

WANTED - WANTED - WANTED TV's - TV's - TV's Colour & Mono. Also Videos (regular supplies if possible). Any quantity, any make. Telephone Bradford 0274 480281. Manchester 061-798 0037.

WANTED

By established company, large or small quantities of Colour/Mono/Video Recorders from Rental Companies, Holiday Camps, Hotels etc. On local or national scale, contracts undertaken. Special prices.

Contact:
TV TRADE DISPOSALS
 184 Cross Street, Sale, Cheshire.
 Tel. 061 962 8471

BUSINESS/PROPERTY FOR SALE

FOR SALE. Cardiff Established Video, Domestic TV shop. Main road, vacant flat above, freehold audit ACC's. Profitable. Ideal Owner/Engineer. £35,950 o.n.o. Please ring 0222 372185/627878.

FOR SALE

A small television repair business in East Devon seaside town. Considerable number of T/V, Radio Service Sheets 1934 to date. Elderly Test, P.A. and similar gear.

TELEPHONE
(0297) 20201

MISCELLANEOUS

BURGLAR ALARM EQUIPMENT. Latest discount catalogue out now. Phone C.W.A.S. ALARM 0274 682674.

BELL'S TELEVISION SERVICES for service sheets on Radio, TV, etc. £1.50 plus S.A.E. Service manuals on colour TV and Video Recorders, prices on request. S.A.E. with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

BOOKS AND PUBLICATIONS

"**RADIO AND TELEVISION SERVICING**" books, new editions for the last 6 years always in stock. Prices on request. **BELLS TELEVISION SERVICES**, 190 Kings Road, Harrogate, N. Yorkshire. Tel. 0423 55885.

COMPLETE FULL-SIZE SETS any published service sheets £2 + LSAE except CTVs/Music Centres from £3 + LSAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists, unique technical publications for sale. Repair data/circs almost any named TV/VCR £8.50 by return. TIST, 76 Church Street, Larkhall, Lanarks ML9 1HE. Phone (0698 883334).

EARN CASH NOW With New Published Manuals

Domestic appliance reconditioning and repair, Two volumes only £12.50 post free. Also, a professional guide to sewing machine repair for profit. Two volumes only £8.50 post free. Both with full repair and fault guides. Leaflets available.

MARCHANT (Dept TVT),
 30 Chester Road East,
 Shotton, Clwyd, N. Wales.

FOR SALE

JAPANESE COLOUR TV's, Panasonic, Hitachi, Mitsubishi, Toshiba, Sharp. Fully refurbished - to trade only. J. M. PEARSON TELEVISION 0484 863489.

WORKING COLOUR £35. Top trade value. Delivery available. Telephone 061 797 3604.

TECHNICAL INFO SERVICES

76 Church St - Larkhall - Lanarks

Giant TV & VCR DIAGRAM MANUALS

Brit CTVs 3 vols £45
 Vol. 1 Decca G.E.C. ITT £17
 Vol. 2 Philips Pye Redif. £17
 Vol. 3 Rank Bush Thorn £17
 Foreign CTVs (now updated) 2 vols £32
 Mono (Stand + Port) 2 vols £32
 Early VCR (VHS/Philips) £17
 VCR later models inc. Betamax £17
 Domestic Equipment Exploded Diagrams in 2 huge binders for £32

New T.V. Rep. Manuals £7.50 each
 1983 Brit. CTV or Foreign CTV 4
 Complete set of 15 TV Rep Mans for £105

Unique T.V. Repair course £9.50
 The only practical radio servicing and repair course £9.50

Large SAE brings FREE 50p magazine inc. service sheet/details of unique T.V. publications. Any quotation plus price lists, etc.

Full size service sheets £2 + I.s.a.e.
 CTVs/Music Centres £3 + I.s.a.e.

Worlds largest collection of service manuals 1930 to date. From £4.50 to £35 each.

e.g. Autovox/G8/A823 £7.50 each
 Integrated TV repair system £195.
 Contains over £250 normal prices.

**FOR FAST QUOTES
 RING 0698 883334**

COURSES

CONQUER THE CHIP... Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C4, Reading, Berks RG1 1BR.

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Television for

insertions. I enclose Cheque/P.O. for £

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd and made payable to Television)

NAME

ADDRESS

Send to: Classified Advertisement Dept

TELEVISION

Classified Advertisement Dept., Room 2612,
 King's Reach Tower, Stamford Street,
 London SE1 9LS. Telephone 01-261 5846.

Rate
 35p per word, minimum 12 words. Box No. 70p extra.

Company registered in England Registered No. 53626 Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

4/84

N.W. ELECTRONICS

25 YEARS SUPPLYING THE TRADE

'Our Prices take some beating'

HIGH QUALITY COLOUR TV's

PHILIPS 520	£15
PHILIPS 550	£28
GEC 2010 Plastic or Wood	£25
HITACHI 19" Push Button	£35
SANYO	£35
BUSH 2 CHIP	£15
BUSH 1 CHIP	£10
THORN 900	£45
BUSH 718	£35
BUSH T22 Exc. Cond.	£65

**OTHER MODELS IN STOCK
INCLUDE: SONY, ITT, PYE,
MITSUBISHI, etc.**

MONO TV's

MIXED BUSH, GEC, PYE, PHILIPS, etc.
600 CAN BE SOLD IN ONE LOT **£350**
OR LOTS OF 10 ... **£2 EACH**
(mainly 20")

WORKING TV's TO ORDER

EXCELLENT CABINETS -
READY TO SELL OR RENT

BUSH 2 CHIP	£29
PHILIPS G8 550	£43
PHILIPS G11	£85
BUSH T20, T22	£85
GEC 210 Plastic or Wood	£38
BUSH 718	£45
ADJUSTABLE STANDS	EACH £3
LATER MODELS: PHONE FOR QUOTATION	

WHITE GOODS

HOOVER TWINS	FROM £7
HOTPOINT 1460	FROM £10
AUTO's	FROM £15

SPARES! SPARES! TV PANELS

	I.F.	DECODER	LINE O/P	POWER	CONVERG	VIDEO	FRAME TS
BUSH 2 CHIP	3.00	8.00	6.00	3.00	3.00	-	5.00
3000/3500	2.00	4.00	8.00	8.00	5.00	5.00	6.00
G8	5.00	7.00	14.00	8.00	5.00	-	5.00
with sound panel							
GEC 2110	10.00	5.00	12.00	6.00	5.00	5.00	5.00
BUSH 718	8.00	15.00	25.00	3.00	5.00	-	15.00
BUSH T20	8.00	15.00	20.00	20.00	5.00	-	15.00

P&P 1 panel £1.50, 2 panels £2.00, 3 panels £2.50 etc.
QUICK DESPATCH - C.W.O. PLEASE

CASH ONLY - DELIVERY CAN BE ARRANGED
YOU CAN REACH US EASILY FROM ANYWHERE

(0274) 688458

Unit 12, Wharfedale Road OPEN MON-SAT 9-5.30
M606 Euroway Estate Bradford Don't forget! We are open
all day Saturday!

VISIONTEL

BEST QUALITY EX-RENTAL
SETS FROM £10 HERE IN
CENTRAL LONDON!

**100's OF SETS
ALWAYS IN STOCK -
COMPETITIVE PRICES**

VIDEO RECORDERS

(SUBJECT TO AVAILABILITY)

We also have PYE - DECCA -
GEC - ITT - GRUNDIG - JVC -
PHILIPS G9 - THORN 9000 and
MANY - MANY - MORE!

FOR CURRENT STOCK DETAILS
TELEPHONE 01 328 3787
OR VISIT US AT
55 KILBURN HIGH ROAD NW6

COLOUR TV SETS

Philips G8, Pye 222, Decca 30 series, ITT,
Pye Chelsea, Thorn 3500/8000, GEC,
many others including JAP.

Working hybrids from £15.
Working solid state from £25.
Non-working sets from £5.
Working panels and tubes available.

REBUILT TUBES

Delta - In Line - PIL.
SOUTHBRIDGE TV CENTRE
120, Selhurst Rd., London, S.E.25.
Tel: 01-771 3535.


WORKING COLOUR TV's TO THE TRADE.

FRESH STOCK DAILY
GOOD CABINETS

ALL MODELS INC. NAT PAN. & JVC. Prices From **£25.00**
Lots of Spares for All TV's, incl. Line Panels for 3000/3500
THORN's - **£5.00 each**

**WEST SIDE TV.
CENTRE**

17 West Side Centre, LUTON. Tel: 24177

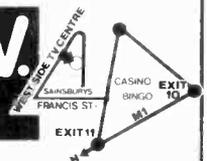

All diodes at 10p or less in this list 20 of one type £1.00 OA 47 8p (NA) 90 8p IN 60 5p IN 541 5p IN 914 3p IN 2069a 10p IN 2070 10p IN 4001 3p IN 4002 3p IN 4003 4p IN 4004 4p IN 4006 4p IN 4007 4p IN 4148x40 10p IN 4448x40 10p IN 4742 10p IN 4722 10p IN 4751 10p IN 5235 10p IN 5254 10p IN 5349 10p IN 5392 10p IN 5393 10p IN 5928B 10p IAV 30 10p IM 72Z55 10p IR 106a 20p IR 3051 10p IS 164 10p IS 921 10p IS 3011a 10p IS 3072a 10p IS 5024a 50p IS 5030 50p ITT 210 10p ITT 921 10p ITT 923 10p ITT 1075 10p ITT 2001 10p ITT 2002 10p ITT 4150 10p ZE 1.5 10p ZF 3 10p ZF 3.3 10p ZF 4.3 10p ZF 10 10p ZF 11 10p ZF 12 10p ZF 15 10p ZF 33 10p ZF 43 10p ZF 47 10p ZF 82 10p ZPD 3.9 10p ZPD 4.7 10p ZPD 5.6 10p ZPD 10 10p ZPD 47 10p ZPY 8v2 10p ZPY 12 10p ZPY 16 10p ZPY 24 10p ZPY 43 10p ZPY 47 10p ZPY 56 10p ZTE 2 10p ZTK 22 10p ZTK 33 10p ZTK 33a 10p ZW 13 12p ZW 27 10p ZW 4.3 10p ZW 310 10p ZX 68 30p ZY 47 10p ZY 72 10p AA 112 10p AA 113 10p AA 119 8p AA 143 10p AA 144 10p BA 102c 10p BA 157 8p BA 159 8p BA 173 8p BA 182 8p BA 201 8p BA 202 8p BA 243 8p BA 248 8p BA 316 5p BAV 10 10p BAV 21 10p BAW 21 10p BB 103 10p BB 105Ax12 10p BB 105Bx12 10p BB 105Gx12 10p BB 121a 10p BRC 83c13 10p BZX 46c22 15p BZX 61 9-1 6p BZX 61c10 6p BZX 61c15 6p BZX 61c20 10p BZX 61c220 10p BZX 70c6v2 8p BZX 70c12 20p BZX 70c33 8p BZX 79c3v9, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 11, 12, 30, 47 10p each BZX 83c4v3, 5v6, 8v2, 12, 13, 24, 27, 33 10p each BZX 84c6v8x10 30p BZX 85c8v2 10p BZX 88c0v7, 3v9, 4v3, 6v2, 8v2, 12 10p each CV 8617 10p Wire 3300/50 Ends 25p	Min 12 volt Relays £75 Y 716 10p Y 729 30p Y 730 10p Y 827: 6A/1KV 20p Y 860 30p Y 933 5p Y 969 5p Y 997 30p R 1038 40p R 1039 40p R 2009 80p R 2010b 10p R 2029 50p R 2210 60p R 2257 60p R 2265 50p R 2305 50p R 2306 50p R 2322/2323 pair 80p R 2323 15p R 2396 50p R 2461 80p R 2030 50p R 2443=BD124 40p R2737 40p R2738=TTP41 30p R2775=TTP41c 40p R3129=TTP47 40p S 2008b 80p BU 105/04 80p BU 108 10p BU 124 50p BU 126 80p BU 180a 65p BU 204 70p BU 206 10p BU 207 10p BU 208 80p BU 208 on heat sink 70p BU 208A 10p BU 208D 90p BU 222 10p BU 326 10p BU 407 60p BU 426V 60p BU 500 10p BU 526 75p BUX 84 50p BUW 84 30p BUW 79 10p E 1579 25p E 1580 25p E 1611 25p E 5359 10p E 5444 10p E 5577 10p E 8018 25p E 9004 10p E 9005 10p TIC 106a 30p TIC 116m 40p TIC 116m/Y 1003 35p TIC 126n 40p TIC 206m 30p TIC 225S 40p TIC 226E 40p TIC 226m 30p TIC 236m 30p TICV 106D (T092 case 2A/400V) 10p TIP 29 20p TIP 29C 25p TIP 30 35p TIP 30A 35p TIP 30B 40p TIP 30C 45p TIP 31 30p TIP 31A/RCA 16334 75p TIP 32 25p TIP 33B 50p TIP 33C 70p TIP 34A 50p TIP 34B 60p TIP 34C 70p TIP 35B 50p TIP 35C 70p TIP 35D 80p TIP 36 50p TIP 36C 70p TIP 41B 40p TIP 41D 70p TIP 42/BRC 6109 30p TIP 48 30p TIP 49 30p TIP 57 30p TIP 100 30p TIP 112 30p TIP 115 50p TIP 117 50p TIP 120 35p TIP 125 35p TIP 130 30p TIP 131 25p TIP 136 30p TIP 140 50p TIP 147 50p TIP 640 50p TIP 2955 35p T 6032 30p T 6036 40p T 6040 40p T 6047 40p T 6049 40p T 6051 40p T 9004 40p T 9005 40p ZTX 102c 10p ZTX 107 10p ZTX 108c 10p ZTX 109k 5p ZTX 213 5p ZTX 341 10p ZTX 342 10p CVC 25/3 chassis (no modules) 15p SPECIAL OFFER CVC 21 15p Chassis complete 35p Computer Transformer 20v/2.25A; 20v/1.5A; 17v/5A; 19v/5A; 28v/0.5A 15p	ZTX 384 10p ZTX 451 10p ZTX 550 10p MJ 2253 60p MJ 3040 60p MV 2209 10p SP 8385 50p Voltage Regulators +5V/LA78P0SSC 30p -5V/LM79M0SCP 25p -8V/79M08c 30p +6V/78M06c 30p +10v/78LA10 20p LM 337 30p LM 342/12 30p -12V/MC 7912 20p +12V/LM 340T12 50p +15V/78M15 15p +18V/MC78M18 20p +24V/78M24 30p MC 7724cp 40p MC 7824 40p TIS 90 10p TIS 91 20p TIS 92 20p TIS 93 20p CB Radio transistor 16119 2A/40v.50Meg 5 for £1. U 14727 15p U 19885 40p U 3832 15p U 3845 15p MR 508 10p MR 501 10p MR 502 10p BYF 1202 10p BYF 1204 10p BYF 3123 40p BYF 3126 40p BYF 3214 40p BYX 10 6p BYX 36/600 35p BYX 38/300 25p BYX 55/350 10p BYX 55/600 (Bead) 10p BYX 71/350 20p BYX 71/600 50p BYX 72/300 20p BYV 95B 10p BVY 95C 12p BYV 96D 10p BYZ 106 10p BPW 41 15p BYW 56 2A/1000v 8p BZY 93c75 50p BZV 15/18 30p BZV 15/30 30p BZW 70c6v2 10p Bush thyristor RCA 76122 10p ITT computer bookset 2020 10p G8 20 turn 100K pot 35p Transformer 240v/20v-500Ma 75p Viewdata torroids 66p CVC 20 tube base 10p Mitsumi tape motor 75p Sankyo tape motor 75p Swiss made 250rpm/240V motor very small 75p Sharp tape motor 400-040 10p Mono scan coil 110" small neck 15p Infra red led 15p LD57CA 15p Mono scan coil 10p G 8 transductor 10p AT 4041/41 transductor 10p 2K5 Lin pot with 40mm spindle 20p 1982 Hitachi Ae isolator 50p Mullard FM decoder 1401 10p Philips service pack, flat films, 57 condensers 56nf-2.2uf 10p VHF 3 Transistor rotary tuner 10p DX-TV 10p 15K-20 turn pots 20p Thorn panel 6x100 pot + changeover switch (Irish) 50p Battery converter TA 75 for colour TV. 12/24v Thorn 3787 10p Thorn 3500 2A cut out 25p Stereo GEC amp 20 watt + pre-amp with 4 pots + mains power unit with circuit 66p	PHILIPS DIY HOME SECURITY ALARMS KITS Send for details. Prices £54 to £112. <table border="1"> <tr> <td> 10 Mixed TV & radio speakers £5 + £2 post 8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 10p 22/100v x 10 10p 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kv 10p </td> <td> Philips GP422.4CH (£40 cost) £6 Stereo Dynamic Cartridge 12 Volt Aerial Changer over Relays £1 GEC Hitachi V/Cap tuner, after 1979 Series £13 6 Push Button Unit for GEC 2100 Series £12 Replacement for Touch Button Unit </td> <td> 10 Mixed TV & radio speakers £5 + £2 post Mullard Broadband R.F. power modules VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783 </td> </tr> </table>	10 Mixed TV & radio speakers £5 + £2 post 8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 10p 22/100v x 10 10p 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kv 10p	Philips GP422.4CH (£40 cost) £6 Stereo Dynamic Cartridge 12 Volt Aerial Changer over Relays £1 GEC Hitachi V/Cap tuner, after 1979 Series £13 6 Push Button Unit for GEC 2100 Series £12 Replacement for Touch Button Unit	10 Mixed TV & radio speakers £5 + £2 post Mullard Broadband R.F. power modules VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783
	10 Mixed TV & radio speakers £5 + £2 post 8Ω 4" speakers £1 4700/10v x 10 50p 68/16 x 10 50p 150/16 x 10 50p 47/25 x 10 50p 220/25 x 10 50p 1/250 x 10 50p 8000/30v 50p 470/40v x 10 10p 22/100v x 10 10p 100/350v 70p 400/350v 70p 47/500v 25p 1/600v 25p .022/1kv 10p	Philips GP422.4CH (£40 cost) £6 Stereo Dynamic Cartridge 12 Volt Aerial Changer over Relays £1 GEC Hitachi V/Cap tuner, after 1979 Series £13 6 Push Button Unit for GEC 2100 Series £12 Replacement for Touch Button Unit	10 Mixed TV & radio speakers £5 + £2 post Mullard Broadband R.F. power modules VHF. BGY33 £15 UHF. BGY22E £5 PT4236C £5 PT9783			
Various Tools and Accessories G11 Neon Switch 10p GPO 5 way plug 25p 12v screwdriver tester with lead + croclip 25p Mains timer. 13 amp — up to 2 hours: easy to use, plugs into socket 10p Sellotape PVC Electric Insulation 50p 25mm x 20M 70p Telescopic aerials (radio) 50p 50mm x 20M 70p UHF Radio Aerial 10p Xcelite pliers 10p Xcelite snips 10p Xcelite cutters 10p GKN Supascrew kits 10p VU meter 10p Pull up large aerial 75p "V" TV aerial 10p Soldering iron 6v/23w 10p Portable TV aerial 75p Philips snips 10p 2 way baby alarm/intercom with long leads 10p Philips universal battery tester/charger, fuse/bulb tester 10p Volt/ohm test meters 1000 ohm/volt 10p Eisenmann NICAD CHARGER 5.5V/150 ma 10p 12V Nicad pack. "AA" 10p Hitachi TP 007 Battery pack 7.2v/1.6A 10p "AA"/1.25V Nicad 10p "C" Nicad 10p "D" Nicad 10p Duracell PP3 60p 1/2" x 1/2" microphone/speaker 50p Continental 2 pin plug with 5ft mains lead (black & blue) 5 for 10p 7" Ferrite rod with LW/MW coils 50p Xceute 5" bent nose plier 10p De-solder pump + 2 nozzles 10p Plastic box for i.c.s with anti-static pad 6"x3"x1/2" 75p Can of handy oil "mobil" 40p Flat Red LED 10p 500gm 60/40 solder reel 10p Clearweld glue pack 30p Dual v/u meter -20 - +10db 10p 15 service manuals, Thorn 3504 & 3448, etc 10p 3 x C90 Cassettes 10p Can Freezer 10p K30 thermistor 232266298009 75p 75R/25 Watt 25p 18R/11 Watt 25p 120R/17 Watt 20p Front End Music Center. VHF/MW/LW 13"x31" 10p Output Stage for music center 10p Both items 10p circuit supplied (as previous ad) SONY 1400KV Chroma Panel 10p SONY 1400KV Tuner unit 10p SONY 1400KV Touch button unit 10p 3 books, Electronic Systems/Guide to Print Circuits/1st Steps in TV 10p Texas Viewdata Decoder VDP 12/8C Issue 3 with all IC's 10p						

SENDZ COMPONENTS

TO ORDER SEE BACK PAGE

Thorn Spares		BY 223	£1
9000 tube base and panel	£1.50	BY 224/600: 4.8A/600v bridge	50p
9000 Front Panel	£5	BY 226	15p
9000 Front Panel (remote)	£8	BY 227	15p
8800/9000 remote unit U705 receiver	£6	BY 228	20p
9000 Frame panel	£8	BY 229/400	30p
9000 Cyclops panel	£1.50	BY 234	10p
8000/8500/9000 chroma panel	£15	BY 237	15p
8500 convergence panel	£6	BY 238	15p
4000 Frame panel	£5	BY 254	10p
4000 Power supply	£3	BY 255	30p
1600 Mains lead, switch		BY 298	10p
3500 6 push button + cable form	£1.50	BY 299	10p
T605 1vNPN 1066 80v/6A	10p	BY 406	8p
9000 Sound output panel	£1	BY 407	10p
3500 Focus unit	£1.50	BY 602	10p
4000 thick film, 00S1-012-1.002	£1	F 247	10p
00S1-012-0108	£1	XK 3102	50p
00S1-018D	£1	XK 3123	50p
3500 2amp thermal cutout	75p	Hitachi 2A/1500V metal case wire end	20p
3500 IF panel	£2	Line Transformers	
3500 Frame panel	£4	G8 Trans. Philips	£7.50
3500 Video panel	£5	G11 Split Diode	£12.00
3500 Line panel	£5	CVC820 Split Diode IIT	£10.00
3500 A1 Diode	20p	CVC40 Split Diode IIT	£10.00
Export 3500 IF panel	£2	Thorn B/W AD5308F + Stik + Lead	£1.50
Remote unit, 1lic, transformer, relay + 5 volt unit	£2	GEC 2040	£5.00
IC board with set of SN74LS	£1	GEC 2110	£7.00
4000 Tube base	£4	Mullard AT 2036	£1.50
3500 A1 pots	50p	Pye mono	£3.00
9000 Frame panel	£7	Rank mono T704A	£3.50
3 Way regulated adaptor 240V 6V/7.5V/300mA		GEC C32 IIT	£7.50
Rank/Toshiba preh unit 0354	£9.50	GEC Portable Line Trans.	£3.00
2 banks of 3 PB unit, Pye 731	£2	EHT Split Diode Leads	£1.00
4 Push button unit preh	£1.00	EHT Cable/Metre	20p
6 Push button VHF/UHF for v/cap, GEC-Decca type	£1.00	Triplers	
7 Push button for CVC5 IIT	£8.00	11 TEZ Rank	£3.00
KT3 12 Push button unit	£2.00	G9 Philips	£4.00
KT3 (Export) 12 P.B.u	£2	GEC 2110	£4.00
6 Push button Unit Thorn	£1.00	9000 Thorn	£6
6 Push button unit for GEC 2040 and ELC 1043/05	£6.00	9500 Thorn	£4.50
6 Push button unit PYE 713	£7.00	2040 GEC	£3.50
7 Lamps for P.B./Unit	£10p	GEC TVM25 Tripler	£2.00
Mains Droppers		Universal Tripler	£6.00
Pye 731 3+56+27R	50p	TKV 76/9	£3.00
3500 Thorn 6/1/100	60p	G8 Philips	£4.50
Pye 3R5/15R/45R	60p	Decca 80 100	£4.50
Thorn 50/17/1K5	£1.00	Grundig TVK 52	£2.50
120/20/20/48/117	£1.00	11TBO	£3.00
270/10/6 for Thorn 4000	50p	11T1Y	£4.00
18/320/70/39	£1.10	D22 for Pye 18" colour portable	£4.00
Thorn 50-40R-1K5	50p	I.P. 1193/63	£4.00
Ac Socket & Lead	25p	BG 100/41	£3.25
GEC, IIT, Philips, Pye	each	BG 100/61	£3.25
Rank Toshiba Tube Bases	30p	BG 200/43	£3.00
Speakers		T/text ultrasonic rec'r panel	£14.00
6x4 G11 25 ohm	70p	Video cassette lamps on lead, 12-14V.	50p or 3 for £1.00
54x24 3 ohm	£1.00	GEC 8 touch unit assy complete with all I.C.'s + pots	£4.00
5x3 80 ohm	70p	G11 E.W. coils	£1.00
5x3 50 ohm	50p	G11 6 Button Key Switch	£2.00
5x3 35 ohm	70p	G11 Transient Suppressors 245V	10 for £1.00
5x3 15 ohm	80p	G11 Scan Coils	£5.00
6x4 15 ohm	£1.00	G11 100K tuner pots	12 for £1
7x3 70 ohm	£1.00	KT3 IF panel	£6.00
5x3 8 ohm	70p	KT3 AE Sockets	25p
7x3 16 ohm	£1.00	NPN PNP 80V 6 Amp TO66 O.P. Trans.	pair 25p
5" dia 16 ohm	£1.00	5 button touch tuner BBC1/2	
5" dia 8 ohm	£1.50	PIV1/2 video with ic SAS 5601/7	£7.00
6 1/2" dia 4 ohm	£1.50	570T	£7.00
6 1/2" dia 3 ohm	£1.50	Control panel 5 sliders + mains lead	£1.50
2 1/2" dia 8 ohm	75p	G11 8 touch button unit replaces old 6 P.B.U.	£24
3" dia 8 ohm	75p	Tube base + base unit for 820 Euro chassis	£4.00
KT3 speaker 3" dia	75p	GEC Line O/P Trans. & Rec Stick for Portable	£3.00
Diodes		CVC 20/25/30/35/40 decoder panel	£10
BY 127	10p	CVC 20/25/30/35/40 decoder panel (untested)	£5
BY 133	10p	CVC 40/45 IF panel	£5
BY 134	10p	40K Transducer	50p
BY 164	50p	PHILIPS NE511N	£1.20
BY 176	25p	LM337M Reg.	30p
BY 179	40p	20 GEC Black Spark Gaps	£1.00
BY 184	25p	G11 Line Driver Transformer	35p
BY 187	10p	Condensers	
BY 196	40p	470/16	6p
BY 198	30p	1500/16	20p
BY 204/4	10p	3300/16	20p
BY 206	8p	10000/16	25p
BY 210/400	5p	15000/16	50p
BY 210/600	8p	3300/18	20p
BY 210/800	10p	4725	5p
International Rectifier EHT Diodes	20p	470/25	5p
6A/600V Stud Diodes	20p	680/25	5p
6A/1000V Stud Diodes	20p	1000/25 Radial	10p
BTW 30/50	50p	1500/25	10p
		3300/25	20p
		4700/25	25p
		5000/25	25p
		3500/30	20p
		470/35	8p
		2200/35	25p
		100/40	5p
		220/40	5p
		400/40	20p
		1250/40	20p
		1500/40	20p
		2500/40	25p
		1000/50	20p
		1250/50	25p
		2000/50	20p
		3000/50	25p
		470/16	6p
		1500/16	20p
		3300/16	20p
		10000/16	25p
		15000/16	50p
		3300/18	20p
		4725	5p
		470/25	5p
		680/25	5p
		1000/25 Radial	10p
		1500/25	10p
		3300/25	20p
		4700/25	25p
		5000/25	25p
		3500/30	20p
		470/35	8p
		2200/35	25p
		100/40	5p
		220/40	5p
		400/40	20p
		1250/40	20p
		1500/40	20p
		2500/40	25p
		1000/50	20p
		1250/50	25p
		2000/50	20p
		3000/50	25p
		470/16	6p
		1500/16	20p
		3300/16	20p
		10000/16	25p
		15000/16	50p
		3300/18	20p
		4725	5p
		470/25	5p
		680/25	5p
		1000/25 Radial	10p
		1500/25	10p
		3300/25	20p
		4700/25	25p
		5000/25	25p
		3500/30	20p
		470/35	8p
		2200/35	25p
		100/40	5p
		220/40	5p
		400/40	20p
		1250/40	20p
		1500/40	20p
		2500/40	25p
		1000/50	20p
		1250/50	25p
		2000/50	20p
		3000/50	25p
		470/16	6p
		1500/16	20p
		3300/16	20p
		10000/16	25p
		15000/16	50p
		3300/18	20p
		4725	5p
		470/25	5p
		680/25	5p
		1000/25 Radial	10p
		1500/25	10p
		3300/25	20p
		4700/25	25p
		5000/25	25p
		3500/30	20p
		470/35	8p
		2200/35	25p
		100/40	5p
		220/40	5p
		400/40	20p
		1250/40	20p
		1500/40	20p
		2500/40	25p
		1000/50	20p
		1250/50	25p
		2000/50	20p
		3000/50	25p
		470/16	6p
		1500/16	20p
		3300/16	20p
		10000/16	25p
		15000/16	50p
		3300/18	20p
		4725	5p
		470/25	5p
		680/25	5p
		1000/25 Radial	10p
		1500/25	10p
		3300/25	20p
		4700/25	25p
		5000/25	25p
		3500/30	20p
		470/35	8p
		2200/35	25p
		100/40	5p
		220/40	5p
		400/40	20p
		1250/40	20p
		1500/40	20p
		2500/40	25p
		1000/50	20p
		1250/50	25p
		2000/50	20p
		3000/50	25p
		470/16	6p
		1500/16	20p
		3300/16	20p
		10000/16	25p
		15000/16	50p
		3300/18	20p
		4725	5p
		470/25	5p
		680/25	5p
		1000/25 Radial	10p
		1500/25	10p
		3300/25	20p
		4700/25	25p
		5000/25	25p
		3500/30	20p
		470/35	8p
		2200/35	25p
		100/40	5p
		220/40	5p
		400/40	20p
		1250/40	20p
		1500/40	20p
		2500/40	25p
		1000/50	20p
		1250/50	25p
		2000/50	20p
		3000/50	25p
		470/16	6p
		1500/16	20p
		3300/16	20p
		10000/16	25p
		15000/16	50p
		3300/18	20p
		4725	5p
		470/25	5p
		680/25	5p
		1000/25 Radial	10p
		1500/25	10p
		3300/25	20p
		4700/25	25p
		5000/25	25p
		3500/30	20p
		470/35	8p
		2200/35	25p
		100/40	5p
		220/40	5p
		400/40	20p
		1250/40	20p
		1500/40	20p
		2500/40	25p
		1000/50	20p
		1250/50	25p
		2000/50	20p
		3000/50	25p
		470/16	6p
		1500/16	20p
		3300/16	20p
		10000/16	25p
		15000/16	50p
		3300/18	20p
		4725	5p
		470/25	5p
		680/25	5p
		1000/25 Radial	10p

